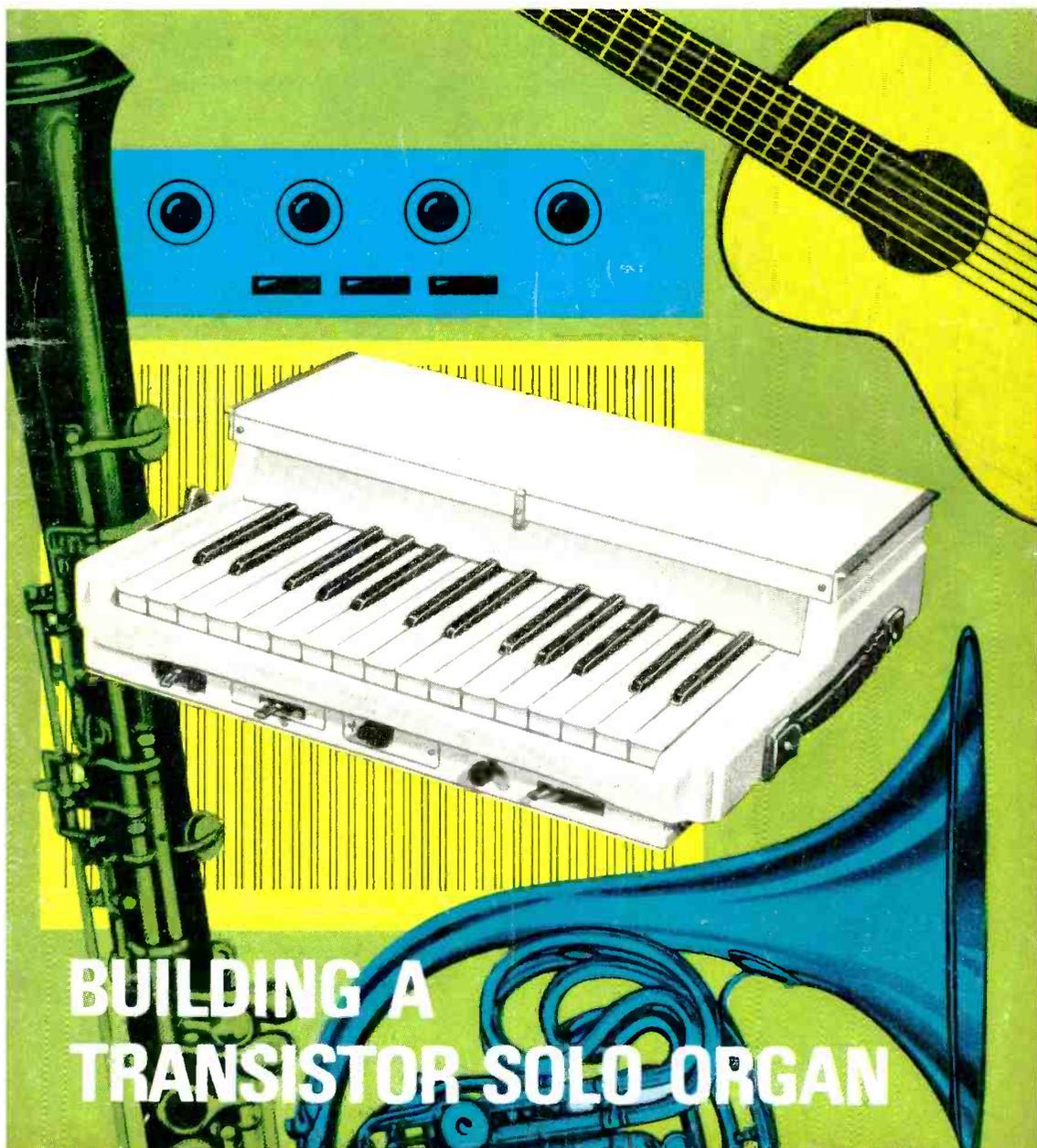


PRACTICAL WIRELESS

FEBRUARY 1965

2¹/₂



**BUILDING A
TRANSISTOR SOLO ORGAN**



SOLDERING INSTRUMENTS AND EQUIPMENT



DESIGNED FOR THE AMATEUR'S RADIO STATION

ILLUSTRATED
List No. 70 $\frac{1}{8}$ " BIT
IN
PROTECTIVE
SHIELD
List No. 68

for catalogue apply direct to:—
Sales and Service Dept.

**ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD, LONDON, S.W.4**

Telephones
MACaulay 4272 & 3101

Telegrams
SOLJOINT LONDON SW4

The
SUPER 6
LONG & MEDIUM WAVE
TRANSISTOR RADIO



A quality radio available as a kit or ready built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12.12.0 commercial model.

★ All new parts, can be built in 2 hours. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit, Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet, 11 x 7½ x 3½ in. ★ Vinyl covered in various colours. ★ 6 x 4 in. speaker giving good bass and treble response. ★ Full instruction booklet 2½. Free with kit. ★ I.F. frequency 470 kc s. ★ Lining up service if required. ★ All parts supplied separately. Write for list. S.A.E. please. ★ 9v. battery required. VT9 or P.P.9 (3/9 with kit).

COMPLETE KIT ONLY £4.17.6
PLUS 5/- POST

OR FULLY BUILT £6.17.6 Tax & Carr. paid

TRANSISTORS

Packet of 3 coded RF transistors (equivalent of OC44.5) 7/6 post paid. Set of 6 transistors and diode with circuit diagram. Neatly packed in foam-lined box; useful for presentation. 15/-, post paid.


TRADE SUPPLIED

ELECTRONICS (Camberley) LTD.
15 VICTORIA AVENUE, CAMBERLEY, SURREY
(Closed Saturdays)

JACKSON 
the big name in **PRECISION** components

Precision built radio components are an important contribution to the radio and communications industry. Be sure of the best and buy Jackson Precision Built Components.

"00" Twin Condenser

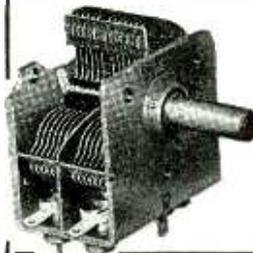

Designed for use in miniature transistor receivers. The front (aerial) section is 208pF to provide coverage for medium waves, and the rear section is 176 pF, which may be padded to match the oscillator—very robust yet light-weight. Front area 1½ in. x 1½ in. x 1½ in. deep.

In the "ten five" receiver used 3 gang type F price 18/6. 2 air tune pF 6/9 each caliband drive at 28/-.

JACKSON BROS. (LONDON) LTD.

(Dept. P.W.) KINGSWAY-WADDON,
CROYDON, SURREY

Phone: Croydon 2754-5. Grams: Walfico, Souphone, London

SURBITON PARK RADIO LTD.

ALL ORDERS DESPATCHED SAME DAY • WE PAY POSTAGE AND INSURANCE
MONEY REFUND GUARANTEE

LEADING STOCKISTS OF MARTIN RECORDAKITS AND AUDIOKITS

MARTIN RECORDAKITS

	Dep.	▲	Mthly pmt. of
HALF TRACK			
TAPE AMPLIFIER FOR STUDIO DECK with ready wired printed circuit, control and input panels, mains and output transformers, knobs, plans, screws, etc. EF96, ECC83, EZ80, EM85 and 2 EL84. 3 watts output. Magic eye, Radio and Mic. inputs. Ex. speaker socket. Tone and Monitor controls. Can be used as an amplifier. £11.11.0	47/-	8	25/6
COLLARO STUDIO DECK. Very latest model. 3 speeds. 3 motors and 7-in. spools. £10.19.6	44/-	8	24/6
CASE for above with 8 1/2 in. speaker, two-tone grey £5. 5.0			
COMPLETE KIT with tape and microphone. £29.19.6	120/-	12	44/-
QUARTER TRACK			
TAPE AMPLIFIER FOR STUDIO DECK as above £12.12.0	52/-	8	27/6
CASE as above with speaker, two-tone grey £5. 5.0			
COLLARO STUDIO DECK fitted Marconi "N" series heads £13.19.6	56/-	12	20/6
COMPLETE KIT with tape and microphone. £33.19.6	136/-	12	49/10
TAPE PRE-AMPLIFIERS			
HALF TRACK for STUDIO deck. 400mV out £8. 9.0	34/-	6	25/8
QUARTER TRACK as above £9. 9.0	39/-	6	28/4
TAPE HEADS			
BRADMATIC Half track Record/Playback and Erase on plate £1.19.6			

MARTIN AUDIOKITS

The new MARTIN all-transistor **TEN WATT AMPLIFIER** kits represent excellent value for money. Each unit is complete, requiring only to be connected to the next. We show only the popular units here. Others are available. Leadlet upon request.

UNIT 1. FIVE INPUT SELECTOR. Size 3 1/2 x 3in. Mag. P.U., Crystal P.U., Radio, Mic, Tape head. 9-15 Volts. Must be used with Unit 4. £2. 7.6

UNIT 4. PRE AMPLIFIER AND CONTROL. Size 6 1/2 x 2 1/2in. Volume out/off, Bass and Treble control. 9-15 Volts. Must be used with Unit 1. £3. 2.6

UNIT 7. MAIN AMPLIFIER. 10 watts. 6-transistor Transformerless Push-pull output. Mounted on Heat sink. 15 ohms output. 40 Volts supply. £8.12.6

UNIT 8. POWER SUPPLY. Gives 9 and 40 Volts. Heavy duty transformer, rectifier and smoothing £2.15.0

CONTROL PANEL for Units 1 and 4. 10.6

ALL FOUR ABOVE UNITS WITH PANEL. 15 ohms output. 24 Volts £15. 8.0

UNIT 5. MAIN AMPLIFIER. As Unit 7 but 3 ohms output. 24 Volts £5.12.6

UNIT 6. POWER SUPPLY. As Unit 8, use with Unit 5 £2.12.6

ALL FOUR UNITS 1, 4, 5 & 6 WITH PANEL. 3 ohms output. 24 Volts £15. 8.0

STEREO VERSIONS NOW AVAILABLE. LEAFLET UPON REQUEST.

	Dep.	▲	Mthly pmt. of
UNIT 5. MAIN AMPLIFIER. As Unit 7 but 3 ohms output. 24 Volts	62/-	12	22/6
UNIT 6. POWER SUPPLY. As Unit 8, use with Unit 5			
ALL FOUR UNITS 1, 4, 5 & 6 WITH PANEL. 3 ohms output. 24 Volts	57/-	12	20/10

NEW ARMSTRONG TUNERS AND AMPLIFIERS



Model	Price	Dep.	▲	Mthly pmt. of
Model 222 SELF-POWERED				
224 F.M.	£29.10.0	96/-	12	33/-
228 A.M./F.M.	£28.15.0	115/-	12	42/2
Model 223				
● TUNER/AMPLIFIERS, MONO				
127 A.M. F.M. with 5 watt amp	£28.10.0	106/-	12	38/10
227 A.M. F.M. with 10 watt amp	£36.15.0	147/-	12	53/-
● TUNER/AMPLIFIERS, STEREO				
127 A.M. F.M. with 5+5 watt amp	£37.10.0	150/-	12	55/-
227 A.M. F.M. with 10+10 watt amp	£52.15.0	211/-	12	77/4
228 As 227 plus Mag. P.U.	£56. 0.0	214/-	12	82/1
● STEREO AMP 222 10+10 watt	£27.10.0	110/-	12	40/4
● SHIP MOUNTING TRAY CASE £3.10.0 EXTRA ALL MODELS				

SEND FOR NEW LEAFLET GIVING FULL TECHNICAL DETAILS.

MONO AMPLIFIERS

LINEAR L 45/A 3 valve, 3 watt	£6. 6.0			
DULCI GA5 Integrated, 5 watts, ECL86 valve	£13. 2.6	52/8	12	19/8
TRIPLETONE HI-FI MAJOR 10 watts output, 2 EL84	£15.18.9	64/9	12	23/3
LEAK TL12 10 watt MAIN AMPLIFIER	£20. 0.0	80/-	12	29/4
LEAK VARISLOPE Mono Pre-amplifier	£15.15.0	63/-	12	23/1
DULCI DPA15 15 watt with 2 valve Pre-amp.	£26.5.0	105/-	12	38/6

STEREO AMPLIFIERS

ROGERS CADET Mk. 2 with P.A.	£26.15.0	107/-	12	39/2
LEAK TRANSISTOR STEREO 30 P.A.	£40.10.0	195/-	12	72/7
LEAK STEREO 20 P.A. and main amplifier	£55. 9.0	229/-	12	80/8

HI FI LOUDSPEAKERS

GOODMANS AXIETTE 8-inch	£5. 5.7			
GOODMANS AXIOM 10 inch	£6. 5.11			
GOODMANS SK 20 XL Tweeter and crossover	£7. 7.0			
GOODMANS X0500, £2.01.11. X0950, £6.10.0				
GOODMANS 210 12in. unit, Full range, 15 watt	£10.17.6	43/6	8	24/3
GOODMANS 301 12in. unit, Full range, 20 watt	£5. 4.6	61/-	12	22/4
GOODMANS "MAXIM" 12in. unit, Full range, 15 watt	£17.10.0	70/-	12	25/8
W.B.HF1012 10in. unit, 3.75, 7.5 & 15 ohms	£4.12.0			
WHARFEDALE SUPER 5 Tweeter	£5.16.8			
WHARFEDALE SUPER 5 Tweeter	£5.19.7			
WHARFEDALE SUPER 8 RS/DD	£6.14.2			
WHARFEDALE SUPER 10 RS/DD. Full range	£10.18.0	44/-	8	24/3
WHARFEDALE RS/12/DD 12in. unit, Full range	£11.10.0	46/-	8	25/8
WHARFEDALE SUPER 12 RS/DD	£17.10.0	70/-	12	25/8

LEAFLETS BY WHARFEDALE AND GOODMANS ON REQUEST.

SURBITON PARK RADIO LTD.

48, SURBITON ROAD, KINGSTON-UPON-THAMES, SURREY

F.M. TUNERS

TRIPLETONE F.M. TUNER, Less power	£13.19.6	46/-	12	20/8
TRIPLETONE F.M. TUNER, With power	£15.14.6	62/-	12	24/1
JASON JTV2 F.M. and T.V. sound, Switched, self-powered	£2. 5.0	69/-	12	23/7

GRAMOPHONE UNITS

NEW ESR UA25 with Mono Cart.	£8. 6.0			
GARRARD SRP10, Single player, Mono cart.	£5.10.0			
GARRARD AUTOSLIM, 4 speed changer, Mono £8.12.6	42/-	8	23/6	
GARRARD AT6 AUTOSLIM DE LUXE, Mono £10.10.0	34/-	6	17/4	
GARRARD AT7.5 P. Imprvd Autolim (Stereo) £9. 0.0				
GARRARD AT8.3000 LM as AT7.5 with 5in. arm (stereo)	£11.12.0	46/8	8	25/8
GARRARD "DECCADEX" Single Player with Decca Detran Cartridge	£15.15.0	63/-	12	23/1
GARRARD HF Transcription Unit, Mono	£17. 0.0	68/-	12	24/11
GARRARD LAB "A" Transcription changer	£19.14.8	79/-	12	28/11
GARRARD 301 STROBE Transcription unit	£22. 0.0	89/-	12	32/8
PHILIPS AG1018, Stereo cartridge, will change 7in. records with adaptor, 10" extra	£12.12.0	50/8	12	18/6
GOLDRING GL58 with arm but less cartridge	£17. 1.0	69/-	12	24/11
GOLDRING GL70 with arm but less cartridge	£27. 9.14	111/4	12	40/1
GOLDRING "68" Transcription, less arm	£18.18.5	76/8	12	27/8

GUITAR SPEAKERS

PANEL 12in. Heavy duty unit, 20 watt	£5. 5.0			
WHARFEDALE W12/EG 12in. 15 watt LFAD	£10.10.0	42/-	8	23/6
WHARFEDALE W15/EG 15in. 15 watt LFAD	£17.10.0	70/-	12	25/8
GOODMANS AUDIOM 81 12in. 15 watt BASS	£9. 2.6	36/8	6	27/8
GOODMANS AUDIOM 61 12in. 20 watt LEAD or BASS	£14. 7.8	57/8	12	21/4
GOODMANS GUITAR Speaker Audiom 81-15in.	£25. 0.0	100/-	12	38/8
GOODMANS AUDIOM 91 18in. 50 watt BASS	£27.10.0	110/-	12	40/4

WRITE FOR GOODMANS LEAFLET "LOUDSPEAKERS FOR ELECTRIC GUITARS"

GUITAR AMPLIFIERS

LINEAR DIATONIC 12 watt, 2 inputs	£13. 2.6	62/8	12	19/8
LINEAR CONCORD 30 watt with COVER	£19. 4.6	77/-	12	28/8
LEAK TL25 with Pre-amp, 25 watt	£42. 5.0	169/-	12	61/11
LEAK TL50 with Pre-amp, 50 watt	£51. 5.0	205/-	12	75/8

MICROPHONES AND FLOOR STANDS

RESLO RBH/T Ribbon	£11. 2.6	44/6	8	24/9
RESLO RBH/T Ribbon with on/off switch	£13.10.0	54/-	12	19/9
RESLO Heavy Duty Floor Stand	£7. 0.0			
TEISCO DM304 Dual Impedance with switch	£2.10.0			
PIEZO BM3 Crystal with switch	£2.10.0			
JAP. FLOOR STAND	£3. 3.0			

EASILY REACHED BY FREQUENT TRAINS FROM WATERLOO TO SURBITON

- Order for Cash, C.O.D. or Terms
- Hours 9 a.m.-6 p.m. (1 p.m. Wed.)
- Open Lunch Time and all day Sat.

SHORTWAVE RECEIVERS
'AMATEUR' EQUIPMENT




INSTRUMENTS FOR TEST,
SERVICE AND WORKSHOP

World-Famous kit-sets anyone can build.
**Quality you can see, quality you can compare...
by appearance, by performance.. by any standard**
DEFERRED TERMS ON ORDERS UK OVER £10. ALL MODELS ALSO AVAILABLE ASSEMBLED

TEST INSTRUMENTS


TELEVISION ALIGNMENT GENERATOR, Model HFW-I.

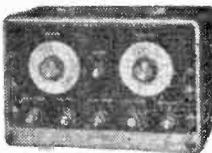Accurate alignment of TV receivers achieved in minimum time at low cost. Covers 3.5 to 220 Mc/s on fundamentals. A must for the service man. **£34.18.0 Kit**



£44.10.0 Assembled

HFW-I

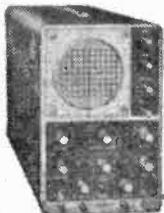

10-12U

5in. OSCILLOSCOPE Model 10-12U. Laboratory quality at utility oscilloscope price. Wide band amplifiers essential for T.V. servicing. F.M. alignment, etc. T/B covers 10 c/s-500 kc/s in 5 ranges. **£41.10.0 Assembled £32.12.6 Kit**

PORTABLE 'SCOPE Model OS-I A compact portable oscilloscope, ideal for servicing and general work. Printed circuit board. Case 7½ x 4½ x 12½in. long. Vt. only 10½ lbs. **£22.18.0 Kit £30.8.0 Assembled**

ELECTRONIC SWITCH, Model S-3U. Converts a single beam oscilloscope into double beam operation at low cost. **£18.10.0 Assembled £12.18.0 Kit**



V-7A

VALVE VOLTMETER, Model V-7A. The world's best selling VTVM. Measures up to 1,500 volts (d.c. and r.m.s.) and 4,000 pk. to pk. Res. 0.1Ω 1,000 MΩ. Centre zero dB scale, d.c. input resistance 11MΩ. 4½in. meter. Complete with test prods, leads and standardising battery. **£19.18.6 Assembled £13.18.6 Kit**

DE-LUXE 6" VALVE VOLTMETER, Model 1M-13U. Similar spec. to model V-7A but with improved accuracy. Larger meter. Unique gimbal mount. **£26.18.0 Assembled £18.18.0 Kit**

RF PROBE, 309-CU extends range to 100 Mc/s. Indication to 300 Mc/s. **£1.13.6 Kit**

HV PROBE, HV-336 measures up to 30,000V d.c. **£2.19.6 Kit**

RF SIGNAL GENERATOR, Model RF-1U. Up to 100 Mc/s fundamental, 200 Mc/s harmonics. Up to 100 mV output on all bands. **£19.18.0 Assembled £13.8.0 Kit**

MULTIMETER, Model MM-1U. Ranges: 0.1.5 v. to 1,500 v. a.c. and d.c.; 150µA to 15A d.c.; 0.2Ω to 20MΩ. 4½in. 50µA meter. **£18.11.6 Assembled £12.18.0 Kit**

A wide range of other test instruments available including: R/C Bridge C-3U £10.10.0. AF V/Voltmeter AV-3U £16.10.0. Wattmeter AW-1U, £17.5.0. (Capacitance meter) CM-1U £15.15.0. Power supplies. Decade boxes etc. Many other instruments available under American Mail Order scheme. Why not send for full details?

DAYSTROM LTD.
Dept. P.W.-2, GLOUCESTER, ENGLAND

TRANSISTOR RECEIVERS

"OXFORD" LUXURY TRANSISTOR DUAL WAVEBAND RECEIVER.

The ideal domestic or personal portable receiver. 10 Semi-conductors. Solid leather case. Send for full details.

Incl. P.T. **£14.18.0 Kit**



6 TRANSISTOR PORTABLE, Model UXR-1. Prealigned I.F. transformers. Printed circuit, 7in. x 4in. high flux speaker. Real hide case. Very easy to build.

Incl. P.T. **£12.11.0 Kit**

7 TRANSISTOR PORTABLE, Model RSW-1. Two short trawler and medium wave bands. Incl. P.T. **£19.17.6 Kit**

"MOHICAN" GENERAL COVERAGE RECEIVER, Model GC-1U. Excellent portable or general purpose receiver for "amateur" or short wave listening. See full spec. leaflets. **Assembled £45.17.6 £37.17.6 Kit**



GC-1U

MONEY BACK GUARANTEE

Daystrom Ltd. unconditionally guarantee that each Heathkit product assembled in accordance with our easy-to-understand instruction manual must meet our published specifications for performance or the purchase price will be cheerfully refunded.

SPEAKER SYSTEMS

SSU-1 MODEL



A practical solution to the problem of a moderately priced speaker suitable for Stereo Mono amplifiers, where the equipment has to be compact. Two speakers, balance control ducted port reflex cabinet. Horizontal or vertical (with matching legs)

Incl. P.T. **£11.12.0 Kit**

COTSWOLD STANDARD MODEL

Acoustically designed enclosure "in the white" 26 x 23 x 15½in. 12in. bass speaker, elliptical middle speaker, 2in. pressure unit. Covers 30-20,000 c/s. Complete kit with all controls.



MFS SYSTEM

A minimum floor space model for the smaller room. 26in. high x 16½in. x 14in. deep. Similar performance to standard model

Price either model **£23.4.0 Kit**

SPEAKERS FOR YOUR OWN ENCLOSURE

12" Heavy-duty Bass (Fane 122/12) **£7.7.0.**
2" Tweeter (Fane 301) **£3.1.6.**
(both as used in the Cotswold systems)
12" Goodman's General Purpose G81A **£5.10.6.**
8" Goodman's General Purpose G8 **£1.8.6.** incl. P.T.
Two Speakers + Cross-over, System SCM-1.
(As used in model SSU-1) with details for enclosure **£4.12.0.**

RPM INDICATOR (Electronic rev counter). A must for the motoring enthusiast. For 4 cylinders, 12V. pos. or neg. earth. **£8.19.0 (complete).** Send for details.

A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO. PLEASE SEND FOR LISTS OR PRICES.

THE WORLD'S BEST
SELLING KIT-SETS



HIGHEST QUALITY
AT LOWER COST




S-33

6W STEREO AMPLIFIER Model S-33. 3 w.ch. Inputs for radio, tape and gram. Stereo/Mono ganged controls. Sensitivity 200mV. £18.18.0 Assembled **£13.7.6** Kit

6W DE-LUXE STEREO AMPLIFIER. Model S-33H. An inexpensive stereo/mono amplifier with high sensitivity. Suitable for use with Decca Deram cartridge. £15.17.6 Kit **£21.7.6** Assembled

TAPE RECORD/REPLAY AMPLIFIER KITS. Will operate with most tape decks. Send for details.

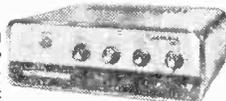TA-1M (Mono). £19.18.0. Kit **TA-1S (Stereo),** £25.10.0 Kit



18W STEREO AMPLIFIER Model S-99. Ganged controls. Stereo Mono gram, radio and tape recorder inputs. P/B selection. £37.19.6 Assembled **£27.19.6** Kit

5W HI-FI MONO AMPLIFIER. Model MA-5. A low priced amplifier based on the S-33. Printed circuit construction makes it easy to build. £15.10.0 Assembled **£10.19.6** Kit

HI-FI MONO POWER AMPLIFIER. Model MA-12. Ideal for use with Models USC-1 and UMC-1, 0.1 THD at 10 W. Wide freq. range. £15.18.0 Assembled **£11.18.6** Kit

More and more people are buying and specifying Heathkit models because:

- ★ **Easy-to-Follow instructions** . . . The step-by-step instruction manuals tell you what to do and how to do it. Large size pictorial diagrams show you how.
- ★ **A satisfying Hobby** . . . assemble any Heathkit model, switch on and find that it performs exactly like an expensive, factory-built set. You will be proud of your model, your friends will admire it, and you built it successfully yourself.
- ★ **You save money** . . . and get better performance at lowest possible cost.

HI-FI-TUNERS

Model FM-4U. Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s I.F. (£2.15.0 inc. P.T.) I.F. Amp. (FMA-4U) complete with cabinet and valves (£13.3.0).

Total **£15.18.0** Kit



FM-4U

AM/FM TUNER. Covers FM 88-108 Mc/s. A.M. 16-50, 200-550 900-2,000 m. Tuning heart (£4.13.6 inc. P.T.), and I.F. Amp. (£21.16.6)

Send for leaflets.

Total **£26.10.0** Kit

EQUIPMENT CABINETS



A large range, in kit form or assembled and finished, available to meet most needs. Illustrated details on request.

Prices from **£7.7.0** to **£37.16.0**

Many other models covering a wide range of equipment for HOME, OFFICE or Workshop

SEND FOR FREE BRITISH CATALOGUE

American Catalogue sent for 1/- post paid

PUBLIC ADDRESS AMPLIFIER, PA-1. 50 w. output, two heavy duty speakers, variable Tremolo. Ideal for use with guitars, etc. £74.0.0 Assembled **£54.15.0** Kit

Legs optional extra 17/6. Set of 4.



50 W POWER AMPLIFIER, MA-50 Ideal for PA work, electronic organs etc. £27.18.0 Assembled **£19.18.0** Kit

DAYSTROM LTD.

Dept. P.W.-2, GLOUCESTER, ENGLAND

A subsidiary of Weston Instruments Group manufacturers of the

WORLD'S LARGEST-SELLING ELECTRONIC KITS

"AMATEUR" EQUIPMENT

AMATEUR BANDS RECEIVER Model RA-1. Covers all amateur bands from 160-10 m. Half lattice crystal filter. 8 valve, "S" meter, tuned R.F. amplifier stage.


£39.6.6 Kit
Assembled **£52.10.0**



RA-1

AMATEUR TRANSMITTER, Model DX-100U. Covers all amateur bands 160-10M. 150 w. d.c. input, self contained with power supply. Modulator, VFO

Assembled **£104.15.0** **£79.10.0** Kit

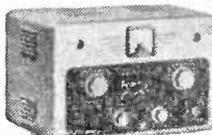


DX-40U

AMATEUR TRANSMITTER Model DX-40U. Covers 80-10 m. Power inputs 75 w. C.W., 60 w. peak C.C. phone. Output 40 w. to aerial. Prov. for V.F.O.

£33.19.0 Kit
Assembled **£45.8.0**

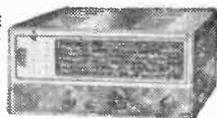COMMUNICATIONS TYPE RECEIVER RG-1. A high performance low cost receiver for the discriminating listener. Freq.: cov. 600 kc/s-1.5 Mc/s and 1.7 M/s to 32 M/s. Send for details. £39.16.0 Kit **£53.0.0** Assembled



Other kits in the amateur range include: SSB Adaptor SB-10U, £39.5.0 Variable freq. Oscillator VF-1U, £10.17.6. Balun Coil Unit, B-1U, £4.15.6. Grid-Dip Meter GD-1U, £10.19.6. Q Multiplier QPM-1, £8.10.0. Wide range of models under American Mail Order Scheme.

Please send me **FREE BRITISH CATALOGUE** (Yes/No)

Full details of model(s)

NAME

ADDRESS

..... P.W.2



MAIL ORDERS TO:

54 WELLINGTON STREET, LEEDS 1
Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please. Personal shoppers welcomed at any of the branches below. Open all day Saturday.

BRADFORD 54 Morley Street, Nr. Alhambra Theatre
Opening early February 1965, spacious new premises at 10 North Parade. (Half-day Wednesday).

BRISTOL 14 Lower Castle Street (Half-day Wednesday)

BIRMINGHAM 30/31 Gt. Western Arcade, opp. Snow Hill Station
(No half-day) Personal shoppers now open

DERBY 26 Osaston Rd., The Spot (Half-day Wednesday)

DARLINGTON 13 Post House Wynd (Half-day Wednesday)

EDINBURGH 133 Leith Street, (Half-day Wed.)

GLASGOW 326 Argyle Street, (Half-day Tuesday).

HULL 51 Savile Street (Half-day Thursday)

LEICESTER 32 High Street (Half-day Thursday)

LEEDS 5-7 County (Mecca) Arcade (No half-day closing)

LIVERPOOL 73 Dale Street (No half-day closing)

LONDON 238 Edgware Road W2 (Half-day Thursday)

MANCHESTER

60A-60B Oldham Street
New large store. No half-day.

MIDDLESBROUGH 106 Newport Rd. (Half-day Wednesday)

SHEFFIELD 13 Exchange Street, Castle Market Bldgs. (Half-day Thursday)

EX. GOV. 2V. ACCUMULATORS, 16 A.H. Size 7 x 4 x 2 1/2. Brand new, 4/8 each. Three for 12/6, carr. 3/-.

MULTI-METERS CABY MI. Sensitivity 2,000 ohms per volt. A.C. and D.C., 54/-, A.10. Basic Meter sensitivity 155 microamps A.C. and D.C. ranges 64-11.6, 14.4m. Sensitivity up to 10,000 ohms per volt. A.C. and D.C., 28-2.6. 30,000 ohms per volt, with overload buzzer. 28.18.6. Other types in stock from 39/9.


EX GOVT. SELENIUM RECTIFIERS 12v 15 AMP (BRIDGE) F.W. ONLY 19/9

EX. GOVT. SMOOTHING CHOKES, 200 mA, 3-5 H, 50 ohms. Parmeko 8/9 150 mA, 10 H, 50 ohms 9/9; 120 mA, 12 H, 100 ohms, 8/9; 100 mA, 10 H, 100 ohms, 6/9; 60 mA, 5-10 H, 250 ohms, 2/11.

HI-FI 10 WATT AMPLIFIER Brand New Complete Units **£7.19.6** Carr. 6/6

Manufacturer's discontinued Model. Push-pull output. Latest high efficiency valves. Dual separately controlled inputs for "Mike" and gram. Separate Bass and Treble Controls. High Sensitivity. Output for 3 or 15 ohm speaker. Guaranteed tested and in perfect working order.

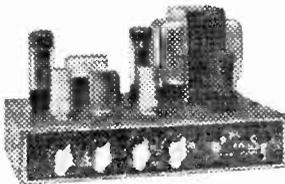R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10



A highly sensitive Push-Pull high output unit with self-contained Pre-amp, Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response ± 3 dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, EOC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS or OUT-DOOR FUNCTIONS, etc. For use with Electronic ORGAN, BASS, LEAD, OR RHYTHM GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required perforated cover with carrying handles can be supplied for 10/9. The amplifier built with factory built with EL34 output valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

11 Gns. Carr. 10/-

TERMS: DEPOSIT 33/8 and 9 monthly payments of 33/8. Suitable microphones and speakers available at competitive prices.

FANE HEAVY DUTY HI-FI SPEAKERS

12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 122/10 20watt, 5 gns. 121/1 A 20watt, 6 gns. 122/12 20watt, 7 gns. 122/12A 20watt, 8 gns. 122/14 22watt, 9 gns. 122/14A 22watt, 10 gns. 122/17 25watt, 211.17.8 122/17A 25watt, 218.17.6
16in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 152/12 20watt, 12 gns. 152/12A 20watt, 13 gns. 152/14 27watt, 14 gns. 152/14A 27watt, 15 gns. 152/17 35watt, 16 gns. 152/17A 35watt, 17 gns. "A" indicates dual cone type. 30-17,000 c.p.s. Send S.A.E. for leaflets. Terms available.

GOODMANS QUALITY LOUSPEAKERS

8in. Axletree 5 gns. 10in. Axloom 28.5-11. 12in. Axloom 51 (15 watts) 25.2.8
12in. Axloom 61 (20 watts) 24.7.8
12in. Axloom 201 (15 watts) 210.17.4
12in. Axloom 301 (20 watts) 215.4.6
15in. Axloom 81 (25 watts) 235.0.0.
16in. Axloom 91 (20 watts) 227.10.0.
Available cash or terms.

12 in. 10 WATT HIGH QUALITY LOUSPEAKER



In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only 24.19.6. Carr. 5/-. Terms: Deposit 11/3 and 9 monthly payments of 11/3. Size 18 x 18 x 10in. Finish as above.

Terms: Deposit 17/9 and 9 monthly payments of 17/9. Only 27.19.6. Carr. 8/6. For larger types see opposite page.
R.S.C. POWER PACK, 39/9. Louvred metal case only 8 x 5 1/2 x 2 1/2. Stove enamelled. For 200-250 v. A.C. mains. Output at 4-pin plug and socket 250 v. 60 mA. Fully smoothed at 8.3 v. 2 a. Suitable for power requirements of almost any Pre-amp, or Radio Tuner.

TRANSISTOR SALE

Mullard OC71 3/8, OC45 4/11, OCC44 4/11, OC72 4/9, OC81 8/11, OC171 8/9, Ediswan XA101 3/8, XB102 3/8, XA112 3/8, XB113 3/8, XB104 3/8, XC101A 3/8. Postage 6d. for up to 3 transistors.

R.S.C. 4/5 WATT A5 HIGH-GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home, school club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest High-fidelity Pick-up heads in addition to all other types of pick-ups and practically all "mikes". Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 dB down, 15 dB of Negative feedback is used. H.T. of 300 v. 25 mA and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-250 v. 50 c/s. and includes fully punched chassis (with baseplate) with Gold Hammer finish and point-to-point wiring diagrams and instructions. Exceptional value at only 24.15.0, or assembled ready for use 25/- extra. Plus 3/6 carr., or deposit 22/8 and 5 monthly payments of 22/8 for assembled unit.

TANNOY RE-ENTRANT LOUSPEAKERS. For outdoor or Factory use. 8 Ohms. 8 watts. Only 25/9

ARMSTRONG RADIOGRAM CHASSIS Stereo and Mono Full Range in stock at all Branches. Cash or Terms

FANE EXTRA HEAVY DUTY LOUSPEAKERS. Total Flux 375,000 lines. Extremely high sensitivity. Exceptionally robust 3in. Diameter voice coil assemblies. Impedance 15 ohms. Model 153 15 in 40 watts. Deposit 37/8 and twelve monthly payments of 31/6. Model 183 18 in 30 watts. Deposit 51/- and twelve monthly payments of 42/8. Send S.A.E. for leaflet.

TRANSISTORISED SOUND MIXER

Enables mixing of up to 4 inputs, i.e., mic., tape, gram., tuner, etc., into single output. Compact and completely self-contained, uses standard 9 Volt battery. Four standard Jack Inputs. PRICE 49/6

R.S.C. BABY ALARM or INTER-COMM KIT. Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity for 200-250 v. A.C. mains. Fully isolated. Controllable at both units. An inter-comm. of this class would normally cost £20-£30. Only 89/6, carr. 6/- or assembled ready for use 8 gns.



R.S.C. BASS-MAJOR 30 Watt AMPLIFIER


A MULTI-PURPOSE HIGH FIDELITY HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS

Eminently suitable for BASS, LEAD or RHYTHM GUITAR and all other musical instruments

- ★ Incorporating two 12in. heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2in. diameter speech coils. Designed for efficient handling full output of amplifier at frequencies down to 25 c.p.s.
- ★ Dual Cone in second speaker reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 28 x 15 x 13in. has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250 v. to 50 c.p.s. A.C. mains operation.
- ★ Four Jack socket inputs and two independent vol. controls for simultaneous connection of up to four instrument pick-ups or microphones.
- ★ Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

39¹/₂ Gns.

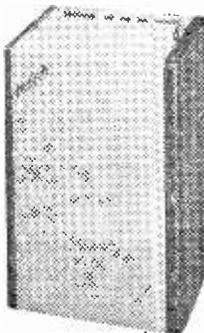Send S.A.E. for leaflet
OR DEPOSIT of £4.3.0 and 12 monthly
payments of £3.9.11. Carr. 17/6.



R.S.C. BASS-REGENT 50 WATT AMPLIFIER


AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT
For bass, lead or rhythm guitar and all other musical instruments -
For vocalist, gram, radio, tape and general public address

- ★ UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15 in. 30 watt unit and a FANE 12 in. 20 watt unit with extended frequency response.
- ★ 4 Jack Socket inputs and two independent volume controls for simultaneous use of up to four instruments, pick-ups, or mikes.
- ★ Separate Cabinets fully covered with Rexine and Vynair in contrasting tones for Amplifier and Speakers.
- ★ Separate Bass and Treble controls for "Boost" and "Cut".

Send S.A.E. for leaflet. Or callat one of our many branches and compare the Bass-Regent with units at more than 3 times the cost.

44

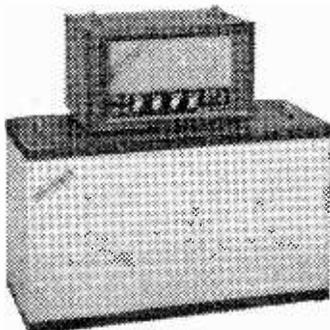Cash Price GNS. Carr. 19/6 Or Deposit £4.10.0 and 12 monthly payments of £3.16.8



THE BASS-REGENT AMPLIFIER UNIT ONLY CAN BE SUPPLIED SEPARATELY AT 21 Gns. Depest 48/6 and 9 monthly instalments of 48/6. Carr. 10/-.

The speaker unit is not separately available.

30W. HIGH QUALITY AMPLIFIER

A Four Input, two volume control, Hi-Fi unit with separate Bass and Treble "Cut" and "Boost" controls. Designed for vocal or instrumental groups. For Bass, Lead or Rhythm Guitar. Six Mullard or Brimar latest type valves. Housed in strong Rexine covered cabinet with twin chrome carrying handles. Attractive black and gold perspex fascia plate. For 200-250 v. A.C. mains. Output for 3 or 15 ohm speakers. Send S.A.E. for leaflet.

16¹/₂

Carr. 10/- or Deposit £2.1.6 and 12 monthly payments of £1.8.4

HEAVY DUTY LOUDSPEAKERS IN SUBSTANTIAL REXINE COVERED CABINETS

TYPE B41 Suitable for Bass Guitar. Speaker Unit 15in. High Flux, 15 ohms, 30 watts. Cabinet size approx. 21 x 21 x 13in. Only Or Deposit 19¹/₂ Gns. 4/- and 12 monthly payments of 34/-.

TYPE B43/2 Suitable Bass and Lead Guitar. Two 12in. high flux 15 ohm 25 watt speakers, one with aluminium speech coil and dual cone to provide smooth frequency response from 25 to 17,000 c.p.s. Cabinet size approx. 30 x 21 x 14in. Covered in two contrasting tones of grey Vynair and Rexine. Rating 50 watts. Only 29 Gns. Or Deposit £3.7.6. and 12 monthly payments of 50/-.



R.S.C. G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, "Mike", Gram, Tape or Radio

High-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Sturdy cabinet is covered in pleasing shades of Rexine/Vynair. Model Size approx. 18 x 18 x 8in. Only 19 Gns. Carr. 10/-

Send S.A.E. for leaflet. Or DEPOSIT 39/11 and twelve monthly payments of 33/4



R.S.C. BASS/20 AMPLIFIER

A multi-purpose unit especially suitable for BASS GUITAR

A highly efficient unit incorporating massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Operation from 200-250 v. 50 c.p.s. A.C. mains. Three sockets are for two inputs and Foot Switch. ONLY 4 Gns.

Send S.A.E. for leaflet 29¹/₂ Gns. £3.2.0 and 12 monthly payments of 51/8. Carr. 17/6.

R.S.C. G5 AMPLIFIER

for Guitar, "Mike", Gram or Radio 5-watt high quality output. Incorporating high flux 12in. 10 watt 12,000 line loudspeaker. Sensitivity 50 m.v. High impedance Jack input. Handsome strongly made cabinet (Size 14 x 14 x 7in. approx.) finished in complementary shades of Rexine/Tygan. 200-250 A.C. mains. Suitable for Lead or Rhythm Guitar in the home or small club, etc.

£9.19.6 Or DEPOSIT £22/3 and 9 monthly payments of 22/3. Carr. 7/6.

LINEAR TREMOLO/PREAMP. UNIT Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.F. and 6.3 v. A.C. L.T. The unit plugs into power supply point and any input socket or amplifier. Controls are Speed (frequency of interruptions). Depth (for heavy or light effect). Volume and Switch. Three sockets are for two inputs and Foot Switch. ONLY 4 Gns.

R.S.C. COLUMN SPEAKERS

Finished in polished veneered walnut. Ideal for vocalists and Public Address. Normally supplied for 15 ohm matching but can be supplied for 100 v. line for 85% extra.

Type C57, 10-15 watts. Fitted five 6 x 4 elliptical speakers. Overall size approx. 26 x 9 x 4in. 9 Gns. Carr. 7/6


Type C58, 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 42 x 10 x 5in. 12 Gns. Carr. 20/-

Or deposit 97/6 and 12 monthly payments 97/6



Introducing the R.S.C. STEREO/20 HIGH FIDELITY AMPLIFIER

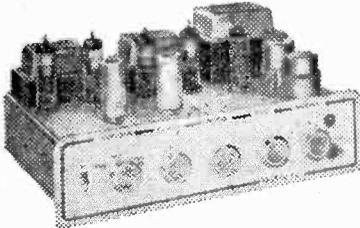PROVIDING 10/14 WATTS ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL



R.S.C. STANDARD BASS REFLEX CABINET. For 12in. loudspeakers, acoustically lined and ported. Size 20 x 14 x 13in. Beautiful walnut veneer finish. Especially recommended for use with Audiotrine Speaker System £519.8.



Set of four legs can be supplied with brass ferrules for 19/8.

AUDIOTRINE CORNER CONSOLE CABINETS. Strongly made. Beautiful polished walnut veneered finish. Pleasing design.

JUNIOR MODEL. To take up to 8in. speaker. Size approx. 20 x 11 x 8in. Only £29.9.

STANDARD MODEL. To take up to 10in. speaker. Size 27 x 18 x 16in. £411.9.

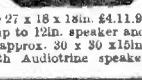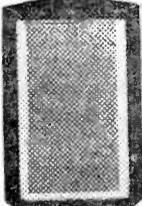SENIOR MODELS. To take up to 12in. speaker and with Tweeter cut-out. Size approx. 30 x 30 x 16in. (Recommended for use with Audiotrine speaker system) 7 gns. or 17/9s.



W.B. "STENTORIAN" HIGH FIDELITY P.M. SPEAKERS HF1012. 10 watts rating. Where a really good quality speaker at a low price is required we highly recommend this unit with an amazing performance. £412.0. Please state whether 3 ohm or 15 ohm required.


R.S.C. JUNIOR BASS REFLEX CABINET. Designed for above speaker, but suitable for any good quality 8in. or 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18 x 12 x 10in. Strongly made. Handsome appearance. Ensures superb reproduction for only £38.8s.

Features include:

- ★ Three-position tone compensation switch
 - ★ Stereo/Mono switch so that peak monaural output of 28 watts can be obtained.
 - ★ Separate Bass "lift" and "cut" and treble "lift" and "cut" controls.
 - ★ Neon panel indicator
 - ★ Handsome Perspex Frontplate. 12 Gns.
- Send S.A.E. for illustrated leaflet. Carr. 10/-
- Complete set of parts with point to point wiring diagrams and instructions, or Factory assembled, tested and supplied with our usual 12 months' guarantee for 15 gns. or DEPOSIT 37/9 and nine monthly payments of 37/9. Protective wooden cabinet covered in pleasing shade of leathercloth and fitted carrying handles and plastic feet 58/9 extra or DEPOSIT 6/9 and nine monthly payments of 6/9.

AUDIOTRINE 3D/1

A complete three diaphragm high fidelity loudspeaker unit designed to occupy a minimum of space. Depth is only approx. 8in. Height 24in. Width 16in. This has been made possible by the latest developments in loudspeaker design. The 12in. cast chassis. Bass unit has a resonant frequency which is extraordinarily low. It has a second diaphragm which extends the frequency range to 17,900 c/s. A further speaker operates only on the middle frequencies and ensures a smooth response from 40-17,000 cps. Rating 20 watts. Imp. 15 ohms. Cabinet finish is either polished walnut veneer, or leathercloth to match stereo/20 cabinet. Highly recommended for any Stereo or Mono Amplifier. Surely the best value ever at 11 gns. Or Deposit 26/9 and nine monthly payments of 26/9.

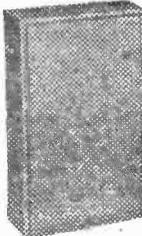


R.A. 12in. DUAL CONE 3 ohm or 15 ohm speakers. Ideal for Stereo. Only 38/9 ea.

LOUDSPEAKERS 29in. to 18in. at these prices. 12in. 28 x 4 ohms 29/11. 12in. 10 watt 12,900 lines 3 ohms or 15 ohms 59/9. TWEETERS, 4in. R.A. 3 ohms 25/9. R.A. 15 ohms 25/9. W.B. 16 ohms 32/3. 16 x 10 ohms. Pressure type £3.15.0. Eagle CT 10-15 ohms 27/8.

AUDIOTRINE EQUIPMENT CABINETS

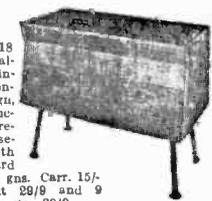Size 36 x 15 x 18 in. Beautiful walnut veneered finish. Elegant contemporary design. Robust construction. Usenet removable baseboard. Depth above baseboard 5 1/2 in. Only 124 gns. Carr. 15/-



Term: Deposit 28/9 and 9 monthly payments 26/9. Full range of equipment cabinets available.

R.S.C. JUNIOR HI-FI REPRODUCER.

The very latest Goodman's Axiette 8 High Fidelity loudspeaker (retailing at £5.67), fitted in a specially designed Bass Reflex cabinet, size 12 x 18 x 10in. Acoustically lined and ported and finished in polished walnut veneer. Matching impedance 15 ohms. Frequency range 40-15,000 c/s. Power handling 6 watts nominal. Ideal for Stereo Carr. 4/6. Deposit £1 and nine monthly payments of £1. **£8.19.6**

LINEAR L45 MINIATURE 4-5 WATT QUALITY AMPLIFIER.

Suitable for any record playing unit and most microphones. Negative feed-back 12dB. Separate Bass and Treble Controls. For min. 200-250 v. 30 c/s. Output for 2-3 ohm speaker. Mullard valves E280, ECC83, EL84. Size only 7 x 5 x 5 1/2 in. high. Guaranteed 12 months. On 6 gns. Send S.A.E. for leaflet. Terms: Deposit 24/9 and 5 monthly payments of 24/9.

JASON FM/IT V.H.F./F.M. Radio Tuner design.

Total cost of parts including valves, Tuning dial, Escutcheon, etc. £6.19.6.

WE STOCK AT ALL BRANCHES

ARMSTRONG, TRUVOX, LINEAR ROGERS, LEAK and JASON EQUIPMENT, GOODMAN'S, W.B. and FANE SPEAKERS, GARRARD AND GOLDRING T/ABLES, LUSTRA-PHONE, GRAMPHON, RESLCO AND SHURE MICROPHONE, CASH OR TERMS.


SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delivered A.V.C. Controls are Tuning, W/C, and Vol. Only 250 v. 15 mA H.T. and L.T. of 6.3v. lamp required from amplifier. Size approx. 9 x 6 x 7 in. high. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and priced parts list with illustrations, 2/6. Total building cost £5.5.0. S.A.E. for leaflet.

AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £419.8. Carr. 20/- or Senior £419.8. Carr. 7/8.

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram., as in A10 High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, EL84, E281. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response ± 3 dB 30-20,000 c/s. Six negative feedback loops. Hum level 60 dB down. ONLY 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for STANDARD or LONG PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING BASS, LEAD OR RHYTHM GUITARS, etc.

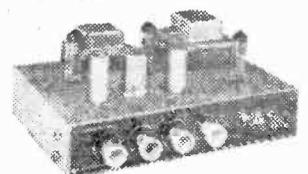

OUTPUT SOCKET with plug provides 300 v. 30 mA. and 6.3 v. 1.5 a. For supply of a RADIO FEEDER UNIT. Size approx. 12 x 9 x 7 in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 15 ohm speaker. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only 8 Gns. Carr. (Or factory built 51/- extra.) If required loured metal cover can be supplied for 18/9. TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9 and 9 monthly payments of 24/9. Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

LINEAR TAPE PRE-AMPLIFIER. Type LP/1. Switched Negative feedback Equalisation. Positions for Record 1in., 3 1/2in., 7in. and Playback. FM84 Recording Level Indicator. Designed primarily as the link between a Collaro Tape Transcriber and a high fidelity amplifier, but suitable for almost any Tape Deck. Only 8/1 gns. S.A.E. for leaflet.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal stereo heads. Ganged Bass and Treble Control give equal variation for "Lift" and "Cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point-to-Point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. Carr. 10/-



Kit can be supplied assembled and ready to use for 58/6 extra.

AUDIOTRINE HI-FI TAPE RECORDER KIT 25 1/2 GNS. Carr. 17/6

REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR
 Incorporating the latest Collaro Studio Tape Transcriber, The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet, tastefully covered in two contrasting shades of Roxine and Vynair, size 14 1/2 x 15 x 9 1/2-in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £200 class. S.A.E. for leaflets.
TERMS. Deposit £2.13.9 and 12 monthly payments of 4/- Cash price if settled in 3 months.



R.S.C. GRAM AMPLIFIER KIT. 3 wats output. Negative feedback. Controls Vol., Tone and Switch. Mains operation 200-250 v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.

BRADOMATIC RECORDING HEADS. High Impedance Record/Playback 22/- Low Impedance Erase. 12/6.
MARRIOTT RECORDING HEADS. High Impedance, Record/Playback, Low Impedance, Erase. 25/- pair.

ONLY 3 PAIRS OF SOLDERED JOINTS PLAIN MAINS


SELENIUM RECTIFIERS
F.W. BRIDGE
 6/12 v. 1a. .. 3/11 H.T. TYPES H.W.
 6/12 v. 2a. .. 6/11 150 v. 40 mA .. 3/9
 6/12 v. 3a. .. 9/9 250 v. 50 mA .. 3/11
 6/12 v. 4a. .. 12/3 250 v. 60 mA .. 4/11
 6/12 v. 6a. .. 15/3 250 v. 80 mA .. 4/11
 6/12 v. 10a. .. 22/9 250 v. 250 mA .. 11/9
 6/12 v. 15a. .. 35/9
CONTACT COOLED. 250 v. 75 mA. F.W. (Bridge), 10/11. 250 v. 50 mA. F.W. (Bridge), 8/11. H.W. 250 v. 60 mA. 5/11.

THE SLYFOUR T.R.F. RECEIVER.
 A design for a 3 valve long and medium wave 200-250 v. A.C. Mains receiver with selenium rectifier. High gain H.F. stage and low distortion detector. Valve line-up: 6K7, SP61, 6V6G. Selectivity and quality excellent. Simple to construct. Point-to-point wiring diagrams, instructions and parts list 1/9, maximum building costs 24.19.6. inc. attractively walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

HI-FI CRYSTAL PICK-UP HEADS. (Cartridges.) Acos Standard replacement for Garrard, B.S.R. arm Collaro, 16/9. Acos Stereo-Monaural 29/9. Ronette Stereo-Monaural 39/9. B.S.R. Stereo 39/9.
PICK-UP ARMS. Complete and with latest Acos/hi-fi Turnover Cartridge 29/11
CRYSTAL MICROPHONES. Hand type NP110 12/6. T.G. 19/9. Acos Mic 40 25/9. Acos Mic 45 29/9. Stick type Acos 33-1 39/9. BM3 with neck band and heavy table stand 59/9. Lapel type 29/9.
COLLARO JUNIOR. 4-speed Single Player Unit and Crystal Pick-up with hi-fi Turnover head. Only 59/6.
B.S.R. UA14 4-sp/4. **AUTO-CHANGERS** with hi-fi turnover head. £5.19.6. Carr. 4/6.
GARRARD AUTO-SLIM 4-SPEED AUTO-CHANGER with high fidelity pick-up. Latest model. For 200-250 v. A.C. mains. £27.17.6. Carr. 4/6.
GARRARD AT6 AUTO-SLIM DE-LUXE 4-SPEED AUTO-CHANGERS. Turnover GC8 head, for 200-250 v. A.C. mains. £11.9.0.

HE-40 De-Luxe 4 COMMUNICATION RECEIVERS HE-30 4 Band

Band. 220/240 v.
 50/60 c.p.s. A.C. mains operation. Frequencies covered 550 Kc/s to 30 Mc/s continuous. Incorporates 5in. speaker. Slide rule tuning dial. 'S' meter. Internal ferrite aerial for medium wave. Telescopic whip aerial 59in. 10 section for short waves. Fitted sockets for optional outdoor aerial. Headphone, external speaker socket. Other features are electrical bandspread tuning, 0-100 logging scale. Noise limiter. A.V.C., B.F.O., stand by switch. Size approx. 14 x 8 1/2 x 5 1/2 in. Handsome grey crackle finished metal cabinet with chromium fittings. Brand new with full instructions manual. Usual guarantee.

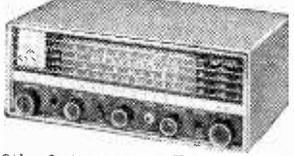


Continuous coverage 550 Kc/s to 30 Mc/s. Illuminated slide rule dial. Edgewise 'S' meter. 0-100 logging scale. Built-in 'Q' multiplier aerial trimmer. Electrical bandspread noise limiter. controls are: Function switch, audio gain, selectivity, frequency (B.F.O.), Band selector, B.F.O. trimmer, A.V.C. M.V.C. Switch, ANL switch, main tuning, bandspread tuning. Output for H/Phones or standard speaker. Provides 1.5 watts output. Size 15 x 10 x 7 1/2 in. For 220/240v, 50/60 c.p.s. A.C. mains. A highly efficient receiver representing exceptional value at only

Only 19 Gns. Carriage 7/6 £35.0.0 Carriage 10/-

SENSATIONAL STEREO OFFER

A complete set of parts to construct a good **4 Gns.** quality Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Sensitivity 180 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. Stereo Pick-up Head 19/9 extra with above only.

R.S.C. BATTERY CHARGING EQUIPMENT

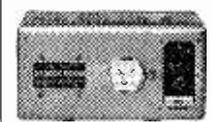

charging. Louvered steel case with grey hammer finish. Fused and ready for use with mains and output **59/9** leads and battery clips. Carr. 4/6
 Terms: Deposit 12/- and 5 monthly payments of 12/-.

All for A.C. Mains 200-250v. 50c/s.
ASSEMBLED 4 amps 6/12 v. Fitted Ammeter and selector plug for 6 v. or 12 v. Louvered metal case finished attractive hammer blue. Fused, ready for use with mains and output leads **39/9** Carr. 3/9.
 6/12v. 1 amp 27/9 Less meter.

BATTERY CHARGER KITS Consisting of Mains Transformer F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse-holders, Grommets, panels, Heavy Duty Clips, circuit. Carr. 3/6 extra.
 6v. or 12v. 1 amp 22/9
 As above with Ammeter .. 25/9
 6v. or 12v. 2 amps 25/9
 6v. or 12v. 2 amps, including Ammeter 35/9
 6v. or 12v. 4 amps, with Ammeter and variable charge rate selector 52/9

COMPLETE POWER PACK KIT

Consisting of Mains Trans., Metal Rectifier, Double electrolytic, smoothing chasis and circuit. For 200-250 v. A.C. mains. Output 250 v., 60 mA. **6.3 19/11**

HEAVY DUTY CHARGER KIT 6/12 v. 6 amps, variable output.

Consisting of Mains Transformer 0.200-250 v.; F.W. (Bridge) Selenium Rectifier, Ammeter, Variable Charge Rate Selector panels, Plugs, Fuses, Fuse-holder and circuit. 59/9. Carriage. 4/6.

CHARGER AMMETERS 0-1.5 a., 0-4 a., 0-7 a., 8/9 each.
CHARGER KIT, 12v. 10 Amp. with variable charge rate selector and ammeter. **24.19.6.** Carriage 10/-.

R.S.C. MAINS TRANSFORMERS FULLY GUARANTEED

Interlaced and Impregnated. Primary 200-230-250 v. 50 c/s. Screened.
TOP SHROUDED DROP THROUGH
 250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a 17/9
 350-0-350v. 80mA. 6.3v. 2a. 0-5-6.3v. 2a 19/9
 250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a. .. 21/9
 250-0-250v. 100mA. 6.3v. 3.5A. C.T. .. 19/9
 250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 25/9
 300-0-300v. 130mA. 6.3v. 4a. 6.3v. 1a. for Mullard 510 Amplifier 37/9
 300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 27/9
 350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 27/9
 350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a 35/9

FULLY SHROUDED UPRIGHT
 250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3v. 2a 17/11
 Midret. type 2k x 3 in. 18/9
 250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 28/9
 300-0-300v. 100mA. 6.3v. 4a. C.T. 3a .. 28/9
 300-0-300v. 130mA. 6.3v. 4a. C.T. 6.3v. 1a. for Mullard Amplifier 35/9
 350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 28/9
 350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a 37/9

FULLY SHROUDED (continued)
 425-0-425v. 200mA. 6.3v. 4a. C.T. 5v. 3a 57/9
 425-0-425v. 200mA. 6.3v. 4a. C.T. 6.3v. 4a. C.T. 5v. 3a .. 59/9
 450-0-450v. 250mA. 6.3v. 4a. C.T. 5v. 3a 69/9

OUTPUT TRANSFORMERS
 Standard Pentode 70000 to 30 .. 4/6
 etc. Small Pentode 5,000 to 30 .. 4/6
 Small Pentode 7,8000 to 30 .. 4/6
 Standard Pentode 5,000 to 30 .. 5/9
 Standard Pentode 7,000 to 30 .. 5/9
 10,000 to 30 .. 5/9
 Push-Pull 8 watts, EL84, or 6V6 to 30 or matched to 150 .. 5/9
 Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-8 to 150 .. 19/9
 Following types for 3v. and 150 speaker
 Push-Pull 10-12 watts 6V6 or EL84 .. 18/9
 Push-Pull 15-18 watts 6L8, KT66 .. 22/9
 Push-Pull Mullard 510 Ultra Linear .. 29/9
 Push-Pull 20 watts, sectionally wound 6L, KT66, EL34, etc. .. 49/9

MIDGET MAINS Primaries 200-250 v. 50 c/s. 250v. 60mA. 6.3v. 2a. .. 11/9
 250-0-250v. 60mA. 6.3v. 2a. .. 12/11
 Both above size 2 1/2 x 2 1/2 in.

FILAMENT TRANSFORMERS
 All with 200-250v. 50 c/s primaries 6.3v. 1.5a. 5/9; 6.3v. 2a. 7/6; 12v. 1a. 7/11; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6; 12v. 1.5a. twice, 17/6.

SMOOTHING CHOKES
 60mA. 7-10 H. 250 ohms .. 11/9
 100mA. 10 H. 200 ohms .. 8/9
 80mA. 10 H. 350 ohms .. 5/9
 60mA. 10 H. 400 ohms .. 4/11

CHARGER TRANSFORMERS
 All with 200-230-250v. 50 c/s Primaries: 0-9-15v. 1a. 21/9; 0-9-15v. 2a. 14/9; 0-9-15v. 3a. 18/9; 0-9-15v. 5a. 19/9; 0-9-15v. 6a. 23/9; 0-9-15v. 8a. 28/9.

AUTO (Step up/Step down) TRANS.
 0-110-120-230/250v. 50-80 watts, 13/9; 250 watts, 49/9; 150 watts, 27/9.

MICROPHONE TRANSFORMERS
 120:1 high grade, clamped, 8/9.



BRADFORD, BRISTOL, BIRMINGHAM, DERBY, DARLINGTON, EDINBURGH, GLASGOW, HULL, LEICESTER, LEEDS, LIVERPOOL, LONDON, MANCHESTER, MIDDLESBROUGH, SHEFFIELD

PAGE 916 FOR ADDRESSES

Brand new individually checked and guaranteed VALVES

Table of vacuum tube types and their specifications, including AC/HL, AC/FP, ALN0, etc.

Table of vacuum tube types and their specifications, including KT63, KT66, KT67, etc.


Table of vacuum tube types and their specifications, including 6A174G, 6AR4CY, 6AT7, etc.

Table of vacuum tube types and their specifications, including 9D6, 9D6B, 9D6C, etc.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. All U.K. orders below £1 P. & P. 1/-; over £12, P. & P. free. Overseas Postage extra at cost.

MARCONI COMMUNICATION RECEIVER CR 150/2 Frequency coverage 1.5-22 Mc/s in 4 bands. Two IF's 1st 1,600 kc/s, 2nd 463 kc/s. Image signal protecting over 40 dB up to 30 Mc/s and 20-40 dB from 30-60 Mc/s. Self-checking calibration (built-in calibrator). Stabilisation of supply and temperature compensation. Electrical and mechanical bandspread. Metering and visual tuning indicator. Bandpass from 100 c/s to 10 kc/s in 5 stages. Acoustic filter associated with 100 c/s. Bandpass position for CVT reception. Facilities for diversity reception. Excellent checked condition £35. Mains P.S.U. by P.C. Radio £4.10.0. Carr. 30/-.

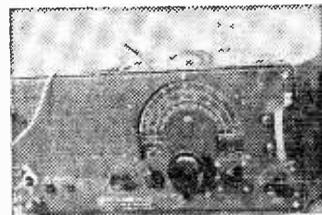WELL PROVEN RELIABLE COMMUNICATION RECEIVER P.C.R.2



(Made by Pye). 120 kc/s-350 kc/s. 525 kc/s-1600 kc/s. 6 Mc/s-22 Mc/s. Overall sensitivity 1-2µV. S/Noise ratio 10 dB at 6µV. Circuit incorporates an RF stage, two i.f. stages, tone control, A.V.C. antenna trimmer. 6V6 output. Set in fully working condition together with headphones and speaker plug. £7.12.6. Carriage 15/- Ditto but with built-in power supply for 210-250V A.C. £9.19.6. Carriage 15/-.

EVERSHED MEGGER CIRCUIT TESTER. 2 ranges 0 to 1,000Ω, 100Ω to 200,000Ω. With test leads, leather carrying case. Tested £4.19.6. P. & P. 3/6 32/44ft. AERIALS each consisting of ten 3ft. 2in. dia. tubular screw-in sections. 14ft. (7 section) whip aerial with adaptor to fit the 2in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer etc. Absolutely brand new and complete, ready to erect, in canvas bag £2.19.6. P. & P. 10/6.

ARR8D RECEIVERS. Fully reconditioned, £55; rebuilt models, £85; brand new, £95. Carriage paid U.K. CHR HIGH RESISTANCE HEADPHONES. New, 14ft. P. & P. 1/6.

Table of electrical components and their prices, including Panel Meters, resistors, capacitors, etc.

P.C. RADIO LTD 170 GOLDHAWK ROAD, W.12 Shepherd's Bush 9946 Open 9.5-5.30 p.m. Thursday 9-1 p.m.

WIRECOMP ELECTRONICS BARGAINS FOR THE RADIO ENTHUSIAST

NEW COMMUNICATION RECEIVERS



MODEL HE30

Covers range from 540 Kc/s. to 30 Mc/s. Ham Band is provided with a scale for direct reading, and can also be band spread. Facilities: A.N.L., A.V.C. and M.V.C. Q Multiplier also serves as B.F.O. H.F. stage and two up: 3x6BA6, 2x6BE6, 2x6AV6, 1x6Q5 and 5Y3. 2 Aerial Sockets. Standby position for use with a transmitter. S meter fitted. 200-250v. A.C. mains. Brand new and unused. Boxed with full instruction manual, in attractive steel cabinet, grey crackle finish. Cabinet size 15x8x10in. Dial 12x4in.

I.F. stages ensure high sensitivity and selectivity. Valve line up: 3x6BA6, 2x6BE6, 2x6AV6, 1x6Q5 and 5Y3. 2 Aerial Sockets. Standby position for use with a transmitter. S meter fitted. 200-250v. A.C. mains. Brand new and unused. Boxed with full instruction manual, in attractive steel cabinet, grey crackle finish. Cabinet size 15x8x10in. Dial 12x4in.

WIRECOMP'S PRICE 33 GNS. Carr. and Pack. free

Available in KIT Form, 25 GNS. Carr. and Pack. free.

H.P. Terms (Ready Built): £6.13.0 deposit and 11 monthly payments of £2.16.0.

MODEL HE40

Covers medium wave band and 1.6-4.4 Mc/s., 4.5-11.0 Mc/s. 11.0-30.0 Mc/s. in separate switched band spread ranges. Controls include B.F.O. Sensitivity, A.N.L. Receiver—Stand-by-Switch, Tone Switch, S-Meter, For 200/250v. A.C./D.C. Internal loop and telescopic aerials fitted. Valve line-up: 12BE6, 12BA6, 12AV6, 50C5, and metal rectifier. Size 13x8x10x1in. Instruction manual included. No Kits available.

WIRECOMP'S PRICE 19 GNS. Carr. and Pack. free.

H.P. Terms £4. dep. and 11 months at £1.12.0.

MODEL HE 80

14-valve super sensitive communication receiver. Freq. range 540 Kc/s.-30 Mc/s. and 14-146 Mc/s. Dual conversion on 2 metres with extra R.F. stage. Single R.F. stage, two I.F. stages on all other bands. B.F.O. and Q-multiplier circuits. Improved A.N.L. and voltage regulated power-pack. "S" meter, band spread on amateur bands, large illuminated dial with logging scale. All controls fitted. Outputs for speaker and phones. Valve line-up: 4x6AQ8, 3x6BA6, 2x6BE6, 1x6BL8, 6AL5, 6AQ5, 6CA4 and OA2. Steel case 17x7x10in. For 200/250v. A.C. mains. Brand new with full instruction manual. No Kits available.

WIRECOMP'S PRICE 59 GNS. Carr. and Pack. free.

H.P. Terms £12.19.0 dep. and 11 mths. at £4.18.0.

Ready Built BOY'S TRANSISTOR RADIOS

2 transistor pocket radio. In plastic case. Size only 4in. x 2 1/2in. x 1in. Fitted with 2in. speaker. Socket for personal earpiece. Works from PP3 type batt. tunable over full medium wave-band. Supplied comb. with earpiece, carrying purse and 9-volt batt. Ideal present.

WIRECOMP'S 42/- Post Free

6 transistor model available only 89/6. Post Free.

NEW SUPER MINIATURE POCKET RADIOS



THE SINCLAIR MICRO-6. Self-contained pocket radio. Size only 1 1/2 x 1 1/2 x 1/2 in. A marvel of modern miniaturisation—truly amazing performance. May be built in an evening. Complete with earphone and detailed construction data. **59/6**

Can be built for only **49/6** Mercury cell 1/11 extra (2 required).

THE SINCLAIR SLOTLINE. The new 2-transistor pocket radio size only 2 1/2in x 1 1/2in x 1in. Micro alloy transistorised and printed circuit. All components available separately. Easy to assemble. Can be built for **49/6**

SUPER AMERICAN TAPE

INTERNATIONAL BRAND, FULLY GUARANTEED

MYLAR BASE	7in. Triple play, 3,600ft.	75/-
5in. Double play, 1,200ft.	15/-	
5in. Long play, 1,200ft.	15/-	
5in. Double play, 1,800ft.	22/6	
7in. Stand. play, 1,200ft.	12/6	
7in. Long play, 1,800ft.	19/6	
7in. Double play, 2,400ft.	25/-	
3in. Triple play, 4,500ft.	12/6	
4in. Triple play, 900ft.	22/6	
5in. Triple play, 1,800ft.	42/6	
5in. Triple play, 2,400ft.	55/-	

P. & P. 1/- extra per reel. 4 reels and over Post Free.

NEW BRANCH NOW OPEN

Personal callers invited to our new, London branch—
323 Edgware Road, W.2 Tel. AMB 7115
Full range of the latest Hi-Fi equipment, components, etc.

WIRECOMP'S BARGAIN STORE

48 Tottenham Court Road, London, W.1
Thousands of bargains: Transistor Radios—Record Players
—Tape Recorders—Radiograms—etc.
Stocks constantly changing—Rock Bottom Prices

SUPER TAPE RECORDER OFFER

SIEMENS STEREO TAPE RECORDERS

High precision machines offering a maximum of facilities for the enthusiast and connoisseur. General specification ★ Completely self-contained Record-replay and Audio amplifiers built in. ★ All transistorised. ★ Three heads—separate record-replay, erase (also provide sound-on-sound recording). ★ Three speeds—7 1/2, 3 1/2, 1 1/2 i.p.s. ★ 4 tracks. ★ Takes 7" reels. ★ Record level indicators on both channels. ★ Remote control facilities for these exceptional machines include: push button controls; tape end stop; separate switched bass boost and treble cut; sep. inputs for 2 microphones—2 radios and 2 pick-ups with provision for mixing 3 inputs. Outputs provided are 2 at 4 ohms; 2 sets headphones; 2 external amplifiers. Power output 21 watts per channel. All brand new, boxed and fully guaranteed.



MODEL 12 (illustrated) self contained portable with 2 built in speakers. List price 94 gns.

WIRECOMP'S PRICE 59 GNS. Carr. and Ins. 15/-

MODEL 10 self contained portable recorder with one built in speaker. List price 89 gns.

WIRECOMP'S PRICE 52 GNS. Carr. and Ins. 15/-

MODEL 14 built on a contemporary styled wood plinth with one built in speaker. List price 87 gns.

WIRECOMP'S PRICE 49 GNS. Carr. and Ins. 15/-

THE "REALISTIC" 7

Transistorised Portable Receiver made to the highest professional standard. Components: Mullard Trans. plus Crystal Diode. 350 milliwatt output to 4in. speaker.—I.F. frequency 470 Kc/s.—fully tunable over medium and long wavebands. Two-tone plastic cabinet with handle—size 7 x 10 x 3 1/2in. fitted socket for car aerial. Complete with full instructions.



MAY BE BUILT £5.19.6 All parts sold separately

Battery 3/9 extra. P. & P. 4/6 extra. (Circuit diagram 2/6, free if all parts bought.) Also De Luxe Model with superior PVC covered wood cabinet and full view tuning dial. **ONLY £1 EXTRA.** All parts sold separately. Battery 3/9 extra. P. & P. 4/6.

GUITAR AND P.A. AMPLIFIER


THE VIKING "TRANSISTOR 50"

50 watts output. Superb amplifier for all music and P.A. work—ideal for guitarists, groups, etc. Fully transistorised for maximum efficiency. 4 inputs with mixing facilities plus reverbation/echo chamber. Bass and treble controls. Fully built and guaranteed. In strong wood cabinet covered in washable material. Size approx. 22 x 10 x 6in. Output imp. 15 ohms. For operation on 200/250v. A.C. mains.



WIRECOMP'S PRICE 45 GNS. Carr. and Pack. 10/6
ALSO VIKING SOUND 30—30 watt valve model. 8 inputs, 4 sep. vol. controls plus bass and treble. 15Ω out. **PRICE 35 GNS.** Carr. and Pack. 7/6.

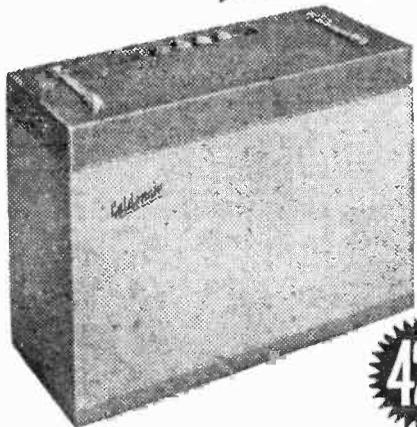The **Goldenaire** GROUP-MASTER 30 WATT AMPLIFIER



A VERSATILE UNIT FOR INSTRUMENTALISTS AND VOCAL GROUPS
being suitable for clubs and public address

Ideal for bass, lead or rhythm guitar, and all other musical instruments.

- ★ The two 12 inch 25 watt heavy duty loudspeakers are specially designed for this type of amplifier, and give outstanding reproduction.
- ★ Robust attractive two-tone finished cabinet of compact size, 28" x 20" x 10 1/2" fitted with carrying handles.
- ★ For standard AC mains 50 c/s operation.
- ★ Four inputs provided can be used simultaneously with instrument pickups or mikes.
- ★ Separate Bass and Treble controls are incorporated.

Full 12 months guarantee

GO GOLDENAIRE Twice the Quality at Half the Price

Customers are invited to see and hear this amplifier at our shop premises in Lambert's Arcade. Send S.A.E. for leaflet.

or deposit of £4.12.0 and twelve monthly payments of £8.12.5.

Carriage and insurance 25/- to be sent with deposit.

42 GNS

The **Goldenaire** "THIRTY" HI-FI AMPLIFIER

A high quality 30 watt amplifier developed for use in large halls and clubs etc. Ideal for bass lead or rhythm guitars, schools, dance halls, theatres and public address. Suitable for any type of mike or pickup.

Valve line-up: two EF86; one ECC83; one GZ34; two EL34.

Four separate inputs are provided with two volume controls. Bass and Treble controls are incorporated. Amplifier operates on standard 50 c/s mains. 3 ohm and 15 ohm speakers may be used.

Perforated cover with carrying handles can be provided if required price

21/-


Full 12 months guarantee

Customers are invited to see and hear this amplifier at our shop premises in Lambert's Arcade.

Send S.A.E. for leaflet.

16 GNS

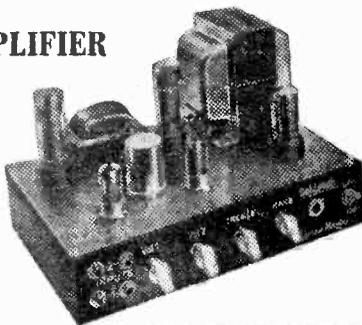or deposit of £1.10.0 and twelve monthly payments of £1.9.0. Carriage 15/- to be sent with deposit.



TANK AERIALS

Fully interlocking copper rods, one foot sections. Ideal for car or scooter aerials. Will make excellent dipoles. Six sections complete with canvas carrying case. Price 3/6. P. & P. 1/6.

19 SET TX/RX MAINS POWER PACK

Operate your 19 Set receiver straight off the mains. Ready built power unit complete with modification and fitting instructions. Price 59/6. P. & P. 3/6.

SONA SOUNDMASTER TRANSISTORISED MIXER

A compact, ultra modern, low channel, fully transistorised microphone mixer, which permits the mixing of up to 4 instruments, i.e. Mic, Tape, Gram, Tuner, etc. Self-contained and operating from a standard 9v. battery. Handsomely finished case. Inputs and outputs take standard plugs. Price 47/6. P. & P. 2/6.

CRYSTAL SET

A wonderful educational kit for all children. Provides hours of amusement while following the easy step by step instructions. It is powered entirely by wireless waves, eliminating the expense of batteries. No soldering required. Receives all main stations. Price 25/- P. & P. 2/6.
An Ideal Christmas present for the children



LOUDSPEAKERS

TYPE 1. Model G.G.25. A heavy duty loudspeaker by famous manufacturer. Diameter 12in. Frequency response 60-5,000 c.p.s. Power handling 25 watts. Impedance 15 ohms. Ideally suitable for Bass Instruments used with high power amplifiers. Price £9.19.6. P. & P. 5/- Send S.A.E. for leaflet.
TYPE 2. A 12in. Heavy Duty Loudspeaker unit. 25 watts power handling. Frequency response 30-14,000 o.p.s. Pure aluminium cast frame. British made by famous manufacturer. Price 5 gns. P. & P. 5/- Send S.A.E. for leaflet.

METER TEST KITS

Comprising insulated leads and test probes, insulated croc. clips and meter terminal connectors. All contained in plastic holdall. Price 9/11. P. & P. 1/3.

CONSTRUCTORS PARCEL NO. 2

All brand new items, not Government surplus. Six Phono Plugs, 2 continual plugs 3 and 5 pin, 12 small croc. clips, 12 large croc. clips, 24 assorted new resistors, 3 pointer knobs, 3 coax plugs, 6 sheets of paroxin approx. 6 x 4in., two sturdy panel mounting fuse holders, six multi-colored solder packs, one copier laminate board, one 30 watt lightweight soldering iron. Price 29/11. P. & P. 3/6.

PLUG-IN DISCRIMINATOR UNITS

Used as pulse count demodulators for FM. Compact and lightweight. Size approx. 4 x 2 1/4 x 1 1/2 in. containing 185 valve F.M. Demod. Coil, tag board with 6 miniature capacitors and 6 miniature resistors. Price 7/6 each. P. & P. 1/6

CONSTRUCTORS PARCEL NO. 1

Ten assorted working valves, 50 assorted resistors, 6 assorted pots, 1 smoothing choke, 5 assorted mains metal rectifiers, 10 assorted valve holders, 6 wafers for making wave change switches, 1. 6-foot copper rod aerial, 2 gov. surplus jack plugs, 2 panel mounting fuse holders. All for 19/11. P. & P. 5/-.

RESISTOR COLOUR CODE INDICATOR

Enables you to determine value of resistor at a glance. A must for the constructor. Price 1/6. P. & P. 3d.

SONA MORE BARGAINS OPPOSITE

TRANS/RECEIVER NO. 46

Compactly built to be carried by one man. This has a range of approx. 10 miles and being crystal controlled, tuning is avoided, and operation is as accurate as a telephone. Frequency 3.6-9.1 Mc/s. Complete stations comprising receiver transmitter, rod aerial. One set of headphones and mike. In canvas carrying bag. Crystal coil unit available for only 35/- per set. Post Free. Brand new in maker's sealed cartons. Price per station **£4.10** P. & P. 10/- each Two stations for **£9.10** Post free



No 19 SET TRANSMITTER RECEIVER

New stocks just arrived. Equipment comprises 3 separate units built into one chassis and separate power pack. Specification: "A" Set Transmitter/Receiver Frequency coverage 2-4.5 Mc/s and 4.5-8 Mc/s (150-37 metres). For R.T., C.W., or M.C.W. Range on R.T. 16 miles. C.W. 50 miles. Superbet R.X. I.F. 465 Kc/s. B.F.O. etc. R.X. valve line-up: 6K7, R.F.: 6K8 mixer. 2 6K7 I.F.: 6B8 det. A.F. phone output. T.X.: 6K8 mixer R.P.O. EF30 buffer. EB34 ADC. and output stage which has to be de-commissioned to conform with GPO requirements. Transmitter/Receiver 229/241 Mc/s. Local use up to 1 mile. Valve line-up CV5, 6K7 and 6V6. Intercom set 2 valve A.F. amplifier for vehicle crew inter-communication. Valve line-up 6K7 and 6V6. A 24in. meter is built in reading I.P. and H.T. voltages, drive etc. **POWER UNIT** 12 volt DC input. Output 275 volts 110 m/a and 500 volts 50 m/a. Equipment is of American or Canadian manufacture and is supplied in good condition. **£4.10.0**

PRICE complete with Power Pack **£4.10.0**
 Carriage 17/6
 19 set only **£3.10.0**
 Carriage 10/-
Power Unit only £1
 Carriage 19/-
 Two 19 sets complete with **£8.10.0**
 Power Packs
 Carriage 30/-

Accessories
 Handbook .. 8/6 P. & P. 6d.
 Connectors 12 pin .. 12/6 P. & P. 2/6
 8 pin .. 7/6 P. & P. 2/6
 Whip Aerials 8ft. 6in. .. 7/6 P. & P. 2/6
 5ft. .. 4/6 P. & P. 2/6

TRANSFORMERS

TYPE 1 Filament Transformer. 200/250 primary 50 c/s. Secondary 6.3 volts at 2 amps. Price 5/11. P. & P. 2/3.
TYPE 3 Primary 200/250 50 c/s. Secondary tapped as follows: 5 v., 11 v. and 17 v. all at 4 amps. Price 29/6. P. & P. 3/6.
TYPE 4 Primary 200/250 50 c/s. Secondary tapped as follows: 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 12 v., 15 v., 18 v., 20 v., 24 v. and 30 v. all at 4 amps. Price 39/6. P. & P. 3/6.
TYPE 6 A really excellent well-made robust transformer. Fully shrouded and upright. Primary 200/250 50 c/s. Secondary 450. 0.450 v. 250 m.a. 6.3 v. at 4 amps. 5 v. at 3 amps. Price 65/-. P. & P. 5/-.

2-WAY SOUND POWERED TELEPHONE


As used by the armed forces. These sound powered earpieces will work up to a distance of one mile without the use of batteries. Beautifully made. ideal for use in the house, office or garden. Complete with connecting cable. 17/6. P. & P. 2/6.

VERSATILE MICROPHONE

List Price one 35/-. Beautifully made in strong plastic case complete with cable and jack plug. Response 50-13,000 c.p.s. **11/6** P. & P. 2/-. While stocks last

TEST OSCILLATOR TYPE 4

A useful piece of equipment for the radio ham, this precision equipment will produce an oscillatory current of freq. range 20 to 100 Mc/s simply by plugging in one of the appropriate coils that are provided with the set. Contained in a robust metal case. The unit has a built-in 6 to 250 volt Power Pack plus many items, including valves, tuning condensers, transformers and vibrators. Price 25/- each. P. & P. 10/- or 2 for 55/-, post free.

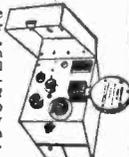

OPERATORS UNIT

Huge Purchase enables us to offer at give-away price operator's Unit containing standard jack socket, 250 mfd. electrolytic condenser, 4-way telephone socket, midjet selenium rectifier, etc. Price 2/6. P. & P. 1/-.

MORSE KEYS

Morse key assembly. Key with base, cover and terminals. Complete with lead 6/11. P. & P. 2/-. 2 Morse Keys for 12/6 post free.



HIGH IMPEDANCE HEADPHONES

lightweight. Suitable for all applications. 11/- per pair. P. & P. 1/6. 2 pairs for 22/6. Post free.

R.A.F. SHORT WAVE RECEIVER

35 to 40 Mc/s. Power supplies 12 volts and 250 volts D.C., in excellent condition with exceptionally fine tuning and clean component layout. Price 42/18. P. & P. 6/-

SONA STREAMLINE BM3

MICROPHONE CRYSTAL INSERTS

Price 7/6. P. & P. 8d.

TRANSISTOR BATTERIES

Save pounds this winter. PP3 type replacement 6 for 10/-. P. & P. 1/9. 12 for 15/6. P. & P. 2/6. Limited stocks.


SUPERHET RADIO CHASSIS

These well-made radio receivers were made for the Government for Forces entertainment. Valve line-up: 6K8, 6K7, 6J7 and 6V6. Choke smoothing, slow motion tuning and clean tuning, printed scale 200-650 metres, complete with all valves and 6 v. power pack. Provided with a robust cabinet and an 8in. speaker to fit. Only 33.19.6. P. & P. 10/-. Few only left.



TEST SET TYPE 46

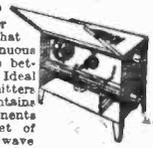A sturdily built oscillator in metal cabinet, that will generate a continuous note on all frequencies between 12 and 24 metres. Ideal for calibrating transmitters and receivers. Contains many useful components including a superb set of short wave coils and wave change switches, an oscillator valve and an excellent slow motion tuning Vernier Dial. Price 25/-. P. & P. 10/-.



TRANSMITTER RECEIVER NO. 46

and No. 38 SET H.T. POWER PACKS
 Power your 46 trans./rec. or 38 trans./rec. set straight from the mains. This valuable unit provides a stabilised D.C. H.T. for these sets. Robustly and compactly made. Only 39/6. P. & P. 5/-.

No. 19 SET INSTRUCTION

HANDBOOK 3/6 each P. & P. 6d.

I155 INSTRUCTION HANDBOOK

3/6 each P. & P. 6d.

H.R.O. INSTRUCTION HANDBOOK

3/6 each P. & P. 6d.

TRANS RECEIVER NO. 46

INSTRUCTION HANDBOOK

3/6 each P. & P. 6d.

FREQUENCY METER BCC221

HANDBOOK 3/6 each P. & P. 6d.

PAXOLIN PANELS

High quality paxolin sheets, size 10 1/2 x 8 1/2 x 1 1/2 in. 3 for 5/-. P. & P. 1/6 for 10/-, post free.

TRANS. RADIO TUBULAR SPEAKER

Booster Speaker. Plugs into earpiece socket of most radios and tape recorders. Gives double the volume and a hi-fi stereo effect that will amaze you. Size 2 1/2" x 2 1/2". Price 25/-. P. & P. 2/6.

LEAD ACID ACCUMULATORS (Unspillable)

2 volts at 16 A.H. Brand New. Size 4 x 7 x 2 1/2 in. 4/11 each. 3 for 12/6. P. & P. 3/- per cell.



HIGH IMPEDANCE PERSONAL LISTENING EARPIECES

Suitable for all types of crystal sets and transistor sets. Complete with plug. Price **4/11** P. & P. 6d.



NEW WALK ROUND STORE OPEN IN LAMBERT'S ARCADE, LOWER BRIGGATE, LEEDS 1. NEXT TO HALFORDS CYCLE SHOP. OPEN ALL DAY SATURDAY. ALL MAIL ORDERS TO OUR BRIGGATE HOUSE ADDRESS. Postage rates apply to U.K. only, send 1/- for full lists.

TERMS:


CASH WITH ORDER
 5/- EXTRA ON C.O.D. ORDERS
 No C.O.D. under 30/-



**TRADE SUPPLIES
 ORDERS FROM
 ABROAD WELCOMED**

SONA ELECTRONIC CO. (Dept. PW14) BRIGGATE HOUSE, 13 ALBION PLACE, LEEDS

LOUDSPEAKERS

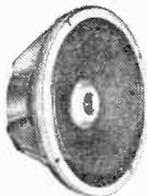

We supply a complete range of Goodmans, Wharfedale, Stentorian, TSL Speaker Units and complete systems. A comprehensive leaflet is available on request this covers technical specifications and prices of

nearly 50 types including:—

- Celestian Model CX1512 (as illustrated) £11.10.0.
- Celestian Model CX2012 £16.10.0.
- Stentorian HF312 3 watts £3.16.0.
- Stentorian HF012 10 watts £4.12.0.
- Goodmans Axiote 8 6 watts £5.5.7.
- Goodmans Axiom 10 10 watts £6.5.11.
- Goodmans Axiom 201 15 watts £10.17.4.
- Wharfedale Super 8/RS/12/DD 6 watts £8.14.2.
- Wharfedale Golden RS/DD 8 watts £7.17.5.
- Wharfedale RS/12/DD, 15 watts £11.10.0.

Guitar Speakers include:—

- Wharfedale W12EG 15 watts £10.10.0.
- Wharfedale W15EG 20 watts £17.10.0.
- Goodmans Audiom 51B, 15 watts £9.2.8.
- Goodmans Axiom 61B, 20 watts £14.7.8.

Carr. and Ins. extra

THE TRAVLER Mk. II CAR RADIO

Our ready built transistorised car radio for only

9 1/2 Gns.

P. & P. 5/-



Including 7 x 4in. speaker fitted to baffle, fixing brackets, filter unit, all nuts and bolts with fitting instructions.

STAR FEATURES

- ★ Handsomely Styled ★ Mullard Valves and Transistors. ★ Push Buttons. ★ 1 1/2 watts Output. ★ Long and Medium Wavebands.
- ★ Quality Speaker (5 M.I.) ★ Easily fitted. ★ Radio Luxembourg (and many other foreign stations). ★ 12-volt Positive Earth only (applies to 99.8% of cars on the road). ★ Dimensions: 7 x 2 x 7in. depth. Optional extras: 3-section chromium plated weatherproof telescopic aerials type 1, 17in./44in. 19/6. Type 2, 21in./43in. 29/6, both plus p. & p. 2/6 if purchased separately.

THE "HIGHWAYMAN" CAR RADIO TO BUILD YOURSELF

Similar in appearance to above but with on/off push-button switch. Complete set of parts only **£7.19.6** P. & P. 5/-

MICROPHONES

Acos Crystal Model MIC 45/19/6.
Acos "Stick" Microphone. Crystal, MIC 39/1 32/6. DM.303 Dynamic High Impedance Desk Microphone complete with Stand. Metallic Green Finish 5 gns. **EM.3** Quality Crystal Microphone with Muting Switch. Complete with Lead, Neck Harness and Removable Stand Adaptor 39/6. Matching Table Stand 12/6 extra. **DX.29** Dynamic High Impedance Black Chrome Finish with Desk Stand 59/6. **DM.301** Dynamic High Impedance with On/Off Switch. Omnidirectional. Chrome plated diecast frame 99/6. **DM.304** Dynamic Dual High or Low with On/Off Switch. Satin chrome finish 89/6. **DM.107** Dynamic High Imp. with Switch. Chrome and black enamel finish 69/6.

MICROPHONE STANDS

MS.4 3 section floor stand 59/6.
MS.8 2 section floor stand 105/-.
MS.2 2 section desk stand 22/6.
P. & P. 2/6 extra on all above.

TRANSISTORISED SOUND MIXER

Mixing 4 channels from high impedance source giving professional results. Inputs for high impedance Microphone, Tuner, Gram and/or Tape Recorder, 9 v. battery operation. Compact and beautifully styled, size 6 x 2 1/2 x 2 1/2 in. Standard Jack socket inputs. Price 55/- P. & P. 2/6. Complete with PT3 0 v. battery. Circuit diagram and instructions. **STEREO VERSION** available, Price 72/6. P. & P. 2/6.

STEREON

GREAT BRITAIN'S GREATEST

STERN-CLYNE HI-FI EQUIPMENT
Ready built or Kits of Parts.

	Complete kit of parts	Ready built and tested	Carr. and Ins.	Instruction book available separately
Stern Mono-Gram Amplifier 3 watts	£4 10 0	£6 0 0	3/6	2/6
Mullard 2 valve Audio Pre-amplifier	£6 6 0	£9 10 0	5/-	2/-
Mullard 3 valve Audio Pre-amplifier	£10 0 0	£13 13 0	5/-	3/6
Mullard "3-3" Amplifier with Tone Control Unit 3S/RC 3 watts	£8 8 0	£11 10 0	6/6	2/-
Mullard "5-10" Main Amplifier Model 510/M. 10 watts	£10 0 0	£13 10 0	6/6	2/-
Mullard "5-10" Amplifier with Tone Control Unit. 10 watts	£12 0 0	£16 0 0	7/6	2/-
Stern JL10 Double Feature Pre-amplifier for Audio and Tape	£13 13 0	£19 19 0	5/-	5/-
Stern JL10 Main Amplifier Mono. 10 watts	£10 0 0	£13 13 0	8/6	3/-
(The above two items purchased together)	£23 13 0	£32 10 0	10/-	—
Stern Twin Three Stereo Amplifier, 3 watts per Channel	—	£9 0 0	5/-	—
Stern Twin Three Stereo Amplifier in Portable Case with Two Speakers and Leads	—	£16 10 0	10/-	—
Mullard "10+10" Stereo Amplifier. 10 watts per Channel	£16 0 0	£20 0 0	8/6	3/-
Mullard "10+10" Stereo Amplifier with Passive Control Unit	£20 0 0	£24 0 0	10/-	3/-
Mullard 4-channel Electronic Mixer Unit Model 211 for 2 Mics. Radio and Gram.	£8 8 0	—	5/-	2/6
Mullard 4-channel Electronic Mixer Unit Model 1L	£10 5 0	—	5/-	2/6
HF/TR3 Tape Amplifier with Power Unit	£13 13 0	£19 0 0	7/6	3/6
Type "C" Tape Pre-amplifier with Power Unit	£14 0 0	£19 10 0	7/6	3/6
STP-1 Tape Pre-amplifier with Power Unit. Mono and Stereo	£22 0 0	£28 0 0	8/6	5/-
CR3/8 Tape Recorder with Studio Deck	£33 8 0	—	15/-	3/-

INDIVIDUAL DESCRIPTIVE LEAFLETS GIVING TECHNICAL SPECIFICATIONS, DIMENSIONS, PRICES, TERMS, ETC. FREE ON REQUEST

TAPE EQUIPMENT AND ACCESSORIES

- AMERICAN ACETATE TAPE**
- 5in. 600ft. Standard 8/6
 - 5in. 900ft. Long Play 10/-
 - 5 1/2in. 1,200ft. Long Play 12/6
- AMERICAN MYLAR TAPE**
- 3 1/2in. 600ft. Double Play 11/6
 - 7in. 1,300ft. Standard Play 12/6
 - 5in. 1,200ft. Double Play 15/-
 - 7in. 1,800ft. Long Play 20/-
 - 5 1/2in. 1,800ft. Double Play 25/6
 - 7in. 2,400ft. Double Play 25/-
- BEL CLEAR ACETATE TAPE**
- 5in. 600ft. Standard 12/6
 - 5in. 900ft. Long Play 15/-
 - 5 1/2in. 1,200ft. Long Play 18/6
 - 7in. 1,200ft. Standard 18/6
 - 7in. 1,500ft. Long Play 25/-
- Postage and Packing 1/- per Reel extra. 4 or more Reels POST FREE.
- FULLY AUTOMATIC TAPE SPLICER**
14/6. P. & P. 1/6.
- PLASTIC TAPE SPOOLS** 2 1/2in. 1/-;
3in. 1/3; 4in. 2/-; 5in. 2/-; 5 1/2in. 2/3;
7in. 2/6.
- PLASTIC SPOOL CONTAINERS.** For spool sizes 5in. 1/6; 5 1/2in. 2/-; 7in. 2/3. Any single item plus 6d. P. & P. Orders over £1 post free.
- We carry fully comprehensive stocks of Tape Recorders, Decks and Accessories at all Branches or order with confidence by mail.

Here's vital time-saving data

to earn money for you!

NOW READY—12th EDITION—NEWNES RADIO & TV SERVICING

This is the set you **MUST** have to beat the frustration and time loss which fritter away your opportunities to earn more. To-day with the vast number of models needing repair and maintenance, more and more difficult repair jobs will crop up. Yet these complicated jobs become so simple when you have the right information at hand. Here, always ready, is your complete library of data—Newnes famous **RADIO & TV SERVICING**. Nearly 55,000 sets of previous editions have been sold . . . solid proof of its importance to you—the engineer in Radio and TV. You can use this new edition for a week free. Post leaflet to-day!

3,500 PAGES OF REPAIR INFORMATION FOR NEARLY

2,300 Popular Models!

DATA FOR OVER 90 MAKES

1964 BACK TO 1958

Ace, Aerodyne, Ajax, Alba, Argosy, Baird, Beethover, Berec, B.R.C., B.S.R., Bush, Capitol, Champion, Channel, Collaro, Corsor, Cydon, Dansette, Decca, Deliant, Doric, Dynatron, E.A.E., Eddystone, Eko, Elizabethan, Elpico, E.M.L., Emerson, Emisonic, Lumig, Ever Ready, Ferguson, Ferranti, Fidelity, Ford Motor Co., Garrard, G.B.C., G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B., Magnavox, Marconiophone, Masteradio,

McMichael, Motorola, Murphy, National, Newmatic, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Playmate, Portadyne, Portogram, Pye, Pye Telecommunications, Radiomobile, Raymond, Recording Devices, Rediffusion, Regentone, Retra, Revelation, R.G.D., Roberts' Radio, Sobell, Sonolor, Sony, Sound, Spencer-West, Standard, Stella, Stereo-sound, Stuzzi, Thorn, Trans Arena, U.K.W., Ultra, Vidor, Volmar, Walter, Waltham-Standard, Zenith

- TELEVISION
- RADIO
- RADIOGRAMS
- TAPE RECORDERS
- RECORD REPRODUCERS
- CAR RADIOS

NEARLY 1,200
CIRCUITS

HUNDREDS OF
DIAGRAMS

PACKED WITH
REPAIR HINTS

*A Complete
Reference Library
in Six Volumes*

Post leaflet Now for FREE TRIAL

SEE IT—USE IT—PROVE IT—IN YOUR OWN WORKSHOP
WITHOUT OBLIGATION!

www.americanradiohistory.com

Newnes Radio & TV Servicing

THE ONLY WORK OF ITS KIND

Apart from complete data for nearly 2,300 models you'll keep right up-to-date with the SECTION OF LATEST DEVELOPMENTS AND SERVICING HINTS. It includes Low-voltage transistor radios. Transistor radio A.G.C. systems. Stabilising transistor output stages. Direct-coupled car radio audio stages. Short-wave reception. Transistor receiver servicing by signal injection. Mercury batteries and alkaline-manganese cells. Tape recorder speed regulation. Dual-standard techniques. Stabilised timebases. White-spot suppression. New flywheel sync. circuit. U.H.F. test card and aerials. Up-to-date B.B.C. TV & I.T.A. Station lists.

READ THE REVIEW OF COLOUR TV SYSTEMS & PAY TELEVISION

Servicing Data on terminal units for Wired TV Systems

Latest Valve and Picture Tube data • Quick-Ref. Data Sections

A Special Offer

You can also examine **NEWNES RADIO & TELEVISION Engineers' Reference Book**

Broadcasting, Communications, Servicing, Navigation Components, Transistors and Transistorised Equipment, U.H.F. Television, Satellite Communications Systems, Video-tape Recorders, Industrial TV, Projection TV, Equipment for Overseas Progress and Developments, etc.

To examine it simply tick form on right.

Over 1,800 pages
2,000 Diagrams
A "must" for your technical library

GOODWILL IS IMPORTANT!

Many a radio shop selling electrical appliances has gained profitable sales on this side through goodwill built up by efficient servicing of Radio & TV sets. If you have never before examined this famous Newnes reference set now is your opportunity—send for it on Free Trial without obligation to purchase. Complete section on right, fold leaflet and post to-day—no stamp required.

Presented free with every set—**NEWNES TV ENGINEERS' POCKET BOOK Value (12/6)**

An invaluable companion to your set for on-the-spot repairs. 272 pages of reference data on installing, fault-tracing and repairing, servicing equipment, etc. Over 200 illustrations.

Postage will be paid by George Newnes Ltd.

No Postage Stamp necessary if posted in Gt. Britain or Northern Ireland

BUSINESS REPLY SERVICE

Licence No. W.C. 1129

GEORGE NEWNES LIMITED,

15-17, LONG ACRE,

LONDON, W.C.2

www.americanradiohistory.com

Tick ✓ where applicable
The address on left is—
My Property
Rented unfinished
Parents' Home
Furnished Accom.
Temporary Address
(RV/RB)41:38/934

Mrs. / Miss / Miss

If under 21 your father must fill up coupon.

RADIO & TV REF. BK.

10/- then 10/-
6/- dep., then 10/-
monthly for 12 months, Full Name, paying £6/6/- in all. Cash (BLOCK LETTERS) in 8 days £6/6/-.

RADIO & TV SET

16/- dep., then 16/-
monthly for 20 months, Cash in 8 days £16/16/-.
21/- dep., and only 21/-
monthly for 21 months, Cash in 8 days £23/2/-.

HOW TO FOLD THIS LEAFLET



Finally post to-day—no stamp required

Signature

RECORD PLAYERS



Garrard SRP10 Single Player \$5.9.1. Carr. and Ins. 4/6. BSR UA14 Auto-changer \$5.19.6. BSR UA15 Auto-changer \$5.19.6. Garrard Autoslim Autochanger \$6.10.0. Garrard AT6 Autochanger \$10.19.6. BSR Super Slim Autochanger \$9.19.6. Garrard AT5 LM Autochanger (3000LM) \$11.11.11. Philips AG1016 Stereo/Mono Record Player \$12.12.0.

Carriage and Ins. 5/- on above.

Garrard 4HF Single Player \$16.17.6. Goldring Lenoq Model 88 Transcription Turntable \$18.18.5. Garrard Laboratory Type "A" Autochanger \$19.15.0. Garrard Model 301 Transcription Turntable \$20.19.0. Goldring Lenoq GL58 with 580 Cartridge \$21.19.0. Goldring Lenoq GL70 less Pick-up Head \$27.9.4.

Carr. and Ins. 7/6 on above.

Descriptive leaflet including prices with alternative cartridges, dimensions, terms etc., free on request.

NEW LOW PRICE COMMUNICATION RECEIVERS



Model HE 40. Frequency range 550 Kc/s-30 Mc/s in 4 bands. PRICE \$18.19.0. Carr. 10/-.

Model HE 30. Frequency range 550 Kc/s-30 Mc/s in 4 bands. PRICE \$34.19.0. Carr. Paid.

Model KT 320. Specification as HE-30 but offered as complete kit of parts. PRICE \$26.5.0. Carr. Paid.

Model HE 80. Frequency range 540 Kc/s-30 Mc/s and 142-148 Mc/s in 5 bands. PRICE \$61.19.0. Carr. Paid.

Model HA 63. Frequency range 530 Kc/s-31 Mc/s in 4 bands. PRICE \$25.4.0. Carr. Paid.

Starfire 90 Watt Transmitter

Hand coverage 80 - 40 - 20 - 15 and 10 Metres.

PRICE \$30.9.0. Carr. 15/- (H.P. Terms available).

Send S.A.E. for fully descriptive brochure.

TUNER UNITS



STERN FIDELITY Mk. II VHF/FM Kit of Parts \$10.10.0. Built and Tested \$14.5.0. Carr. and Ins. 5/-

ARMSTRONG

Mono/Tuner Amp. Model 127M \$28.10.0.

Stereo/Tuner Amp. Model 127 \$37.10.0

AM/FM Tuner Model 223. \$23.15.0.

FM Tuner Model 224 \$22.10.0. Carr. and Ins. 7/6.

JASON

FM1 FM Tuner. Kit of Parts \$8.15.0.

FM2 FM Tuner. Kit of Parts \$10.12.6.

FM23 FM Tuner for Fringe Areas. Kit of Parts \$12.5.0.

FM74 FM Tuner \$20.0.4.

JV2/FM/TV Sound. Kit of Parts \$15.15.0.

Carr. and Ins. on above 5/- each.

TRIPLETONE

FM Tuner unpowered. \$18.19.6.

FM Tuner Self-powered. \$18.14.0.


Carr. & Ins. 5/- each.

Descriptive leaflets free on request. Please state model required.

CLYNE

ELECTRONIC HOBBIES ORGANISATION

**THE PEAK 60
60 WATT AMPLIFIER**

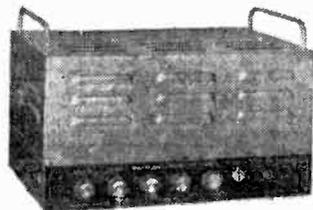

A multi-purpose high output power amplifier for MICROPHONE and INSTRUMENTAL applications or for providing high quality sound for Auditoriums—Halls—Dance Bands and Outside Public Address functions.

★ Bass and Treble controls. ★ Master Volume Control. ★ Full mixing facilities. ★ Built-in pre-amplifier and control unit. ★ 60 watt undistorted output. ★ Switched output for 2 or 15 ohm loudspeakers. ★ Two inputs. High gain and low gain with individual volume controls. Silver hammer finish. Black perspex front panel. Overall size 14in. x 9in. x 7 1/2in. high including cover (plus 1 1/2in. high handles).

COMPLETE KIT OF PARTS \$18/10/-. C. & I. 5/- ASSEMBLED AND TESTED \$28/14/-.

C. & I. 5/- (Ventilated Cover with chrome plated handles as illustrated 35/- extra) Full details on request

VISIT YOUR NEAREST STERN-CLYNE ELECTRONICS CENTRE

LONDON

18 Tottenham Court Road, W.1. MUSEum 5929/0085. Half Day Saturday.
23 Tottenham Court Road, W.1. MUSEum 3451/2. Half Day Thursday.
300 Edgware Road, W.2. PADdington 6983. Half Day Thursday.
109 Fleet Street, E.C.4. FLEet Street 5812/3. Half Day Saturday.
182 Holloway Road, N.7. NORth 7941. Half Day Thursday.
9 Camberwell Church Street, S.E.5. RODney 2875. Half Day Thursday.

CROYDON

12 Suffolk House, George Street, MUNicipal 3250. Half Day Wednesday.

BRISTOL

28 Merchant Street, BRistol 1 BRistol 20261. Open 6 days a week.

LIVERPOOL

62 Lord Street, ROyal 7450. Open 6 days a week.

MANCHESTER

20/22 Withy Grove, MANchester 4. BLAckfriars 5379/5246. Open 6 days a week.

SHEFFIELD

125 The Moor, SHEffield. SHEffield 29993. Half Day Thursday.

MAIL ORDERS AND ENQUIRIES TO:

Dept. P.W. 3/5 Eden Grove, Holloway, London N.7. NORth 8161/5.

Lewis have the Cabinet for you

We can supply any cabinet to your own specification. These are only two examples of —THE LARGEST RANGE OF CABINETS IN THE COUNTRY

Equipment is also our speciality.



The Grosvenor
Price 18 gns.



The Lowboy
Price 27 gns.



100(P265) Chase Side Southgate
London, N.14. Tel 3733/9666

FREE CATALOGUE

Send today for the new Lewis Catalogue

Designed to assist your choice of cabinet. Sent absolutely free. The new Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Choose from 49 different Models.

Please send your new free 24 page colour cabinet catalogue.

Name _____
Address _____

BLOCK CAPITALS PLEASE

AMERICAN TRANSISTORS

200 Types - New - Guaranteed

2N63	7/-	2N637	14/-
2N64	5/-	2N696	20/-
2N147	9/6	2N706	25/-
2N173	17/6	2N1022	17/-
2N176	12/6	2N1046	50/-
2N214	6/-	2N1109	7/6
2N217	5/-	2N1265	3/11
2N235A	14/6	2N1283	17/-
2N274	11/-	2N1294	17/6
2N307A	17/6	2N1307	7/-
2N359	9/6	2N1375	8/9
2N382	7/-	2N1377	8/-
2N385A	5/-	2N1433	12/-
2N414	5/-	2N1907	55/-
2N441	24/6	2N2048	19/6
2N443	17/6	2N396	8/9
2N458	15/3	2N1706	6/3
2N520A	5/6	AUY10	45/-

I.B.M. Computer Boards loaded with transistors, diodes, resistors, etc.

4 transistors, 10/-
6 transistors, 15/-

Modules (solid state); Silicon Rectifiers; Zener Diodes etc., etc. Data circuits for all items.

Send 1/- for complete reference catalogue.

J. & J. ELECTRONICS
15 Kensington High Street
London W.8

AMATEUR RADIO CIRCUITS BOOK

An RSGB Publication

7/6 Postage 9d.

SIMPLIFIED MODERN FILTER DESIGN by P. R. Geffe, 50/-, Postage 1/-.

AN ELECTRONIC ORGAN FOR THE HOME CONSTRUCTOR by A. Douglas, 20/-, Postage 1/-.

SIMPLE RADIO CIRCUITS by A. T. Collins, 7/6, Postage 6d.

FREQUENCY DIVIDER ORGANS FOR THE CONSTRUCTOR by A. Douglas, 25/-, Postage 1/-.

HI-FI YEAR BOOK 1964, 10/6, Postage 1/-.

AMATEUR RADIO CALL BOOK RSGB Pub. 1965, 5/-, Postage 6d.

BASIC THEORY & APPLICATION OF TRANSISTORS. U.S. Dept. of Army, 10/-, Postage 1/-.

RADIO VALVE DATA. 7th Edition Compiled by "VW" 7/6, Postage 10d.

COMPLETE CATALOGUE, 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET
LONDON, W.2

Phone: PADdington 4185
Open 6 days 9-6 p.m.

HARVERSON AMPLIFIER BARGAINS!

Special offer of Manufacturers Surplus
2 VALVE GRAM AMPLIFIERS
UY85 Rectifier and UCL82 Triode/Pentode giving 3 1/2 watts output. Overall chassis size (inc. valves) 5 in. high x 5 1/2 in. wide x 2 in. deep. Each amplifier new and tested and supplied complete with valves, 3 ohm output transformer and knobs for tone and volume/on off controls.

ONLY 37/6 P. & P. 3/6.

Can be used with 80v. motor tap or 1.5k. mains dropper U78 extra if required. *Owing to the limited number available and the extremely high value we regret we cannot enter into any correspondence.*

TWO VALVE GRAM AMPLIFIER ON PRINTED CIRCUIT BOARD

(UY85, ULS4). Can be used with 80 v. tap off motor. O.P. Trans. volume and tone control. Size 6 1/2 in. wide x 2 in. deep x 3 1/2 in. high overall. ONLY 39/6 P. & P. 2/6. Mains dropper req. for filaments if required. 2/6 extra.

SPECIAL OFFER

HIGH GRADE 2-STAGE GRAM AMPLIFIERS

Made by very well-known manufacturer Using a double-wound mains transformer (fully isolated chassis) with tapped primary, full wave contact cooled rectifier, and Mullard 6XLS2 triode-pentode valve output. Separate tone and volume controls. Overall size 6 1/2 in. wide x 3 in. deep x 4 1/2 in. high. Each amplifier Brand New and tested and supplied complete with valve, 3 ohm output transformer and knobs.

PRICE 49/6 P. & P. 4/-.

BRAND NEW 3 OHM LOUDSPEAKERS

2 1/2 in., 12/8; 5 in., 12/8; 6 1/2 in., 15/-; 8 in., 21/-; 10 in., 25/-; 12 in., 27/8; (12 in. 15 ohm, 30/-). 10 in. x 6 in. 28/- latest type E.M.I. 13 1/2 x 8 in. with high flux ceramic magnet, 11,000 gauss. Aluminium centre cone. 10 watts, 50 c/s to 10 Kc/s., 42/- P. & P. up to 6 in. 1/6; over 6 in. 2/6 per speaker.

SPECIAL OFFER !!

BRAND NEW HEAVY DUTY 12 in. SPEAKERS Response 45 c/s-13 Kc/s. 1 1/2 in. voice coil. Available in 3 or 15 ohm. Guaranteed full 16 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE AT 89/6, P. & P. 5/6. Also 25 watt (guitar) coils available at 25.5.0.

BARGAIN OFFER CORNER

ROLA CELESTION. Approx. 9 in. x 6 in. 3 ohm Middle register speaker, 10/6. P. & P. 2/6.

MAINS TRANSFORMER

Drop thru type. Tapped primary 110v., 200v., 220v., 240v., 250-0-250v. at 50ma and 6.5v. at 3 amps. Generous core, stack size 3 1/2 x 2 1/2 in. Weight 4 lbs. ONLY 15/- P. & P. 3/6.

ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity, 18/8. P. & P. 1/6.

TSL CRYSTAL STICK MIKE. Listed at 45/- Our price 18/8. P. & P. 1/6.

T.C.C. SUPPRESSOR CONDENSERS. 250v. A.C. .005 + .005 x .1. In tubular can 1 1/2 in. long x 1/2 in. dia. 2 for 3/- Post free.

TRANSISTOR DRIVER and O/P TRANSFORMERS. (Tapped 3 ohms and 15 ohms output), plus 4 suitable Transistors giving approx. 1 watt output, 25/- P. & P. 2/6.

CONDENSERS. 5,000 mF. 12v. wkg. Size 3 x 1 1/2 in. dia. 2/- each. P. & P. 6d each.

T.V. or AMP/FREQ. EDGE CONTROL PANELS. Two 500k Lin. pots; one 500k Log; one D/P mains switch. Brand new 3/6 panel. P. & P. 1/-.

CONTACT COOLED BRIDGE RECTIFIERS. 250v. at 125 mA. Size 1 1/2 x 1 1/2 in. 7/6. P. & P. 1/-.

MATCHED PAIR OF 24 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair, plus 2/- P. & P. Won double.

TWIN TELESCOPIC AERIAL. Comprising two 3-section heavily chromed rods. Closed 12 in. each extending to 32 in. each. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, approx. 36 in. of coax. and standard coax. plug. Suitable for F.M. or T.V. 12/8 plus 2/- P. & P.

MARCONI QUARTZ CRYSTALS Types ZHB. Still available as previously advertised.

Harverson Surplus Co. Ltd. ▶

3-VALVE AUDIO AMPLIFIER MODEL HA34



Designed for Hi-Fi reproduction of records A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 in. d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves, heavy duty double-wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls.


The HA34 has been specially designed for us and our quality order enables us to offer them complete with knobs, valves, £4.50 P. & P. etc., wired and tested for only 5/-

TAPE DECKS

COLLARO STUDIO DECK. 3 motors, 3 speeds, push button control. Up to 7 in. spools. \$10.10. P. & P. 5/6.
B.S.R. MONARDECK. Single speed, 3 1/2 in. per sec. simple control unit 5 1/2 in. spools. £6.15.0 plus 5/6 Carr. and ins. (Tapes extra on both).

STEREO AMPLIFIERS

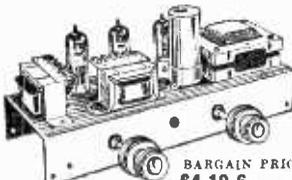Incorporating 2 ECC82's and 1 E280 heavy duty double-wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



BARGAIN PRICE £4.19.6 P. & P. 5/-

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet
 ● Printed circuit board (size 8 1/2 x 2 1/2 in.) ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite rod aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. ● All parts sold separately. Set of parts if purchased at one time.

ONLY £4.50 P. & P. 2/6.
 Circuit diagram 1/6 (free with set of parts).

35 OHM SPEAKERS

Suitable for use with above 250 Goodman. Ideal replacement for most pocket portables, 8/6, 3 1/2 in. 12/6; 5 in. 17/6; 7 x 4 in., 21/- P. & P. 1/6 per speaker.

Portable CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker, 25/- P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers, one milliar coil, one driver transformer and wound Ferrite aerial (mech., long and car aerial coupling). 32/6 complete, post 1/- 6 transistor printed circuit board to match, 8/6 Post 9d. Circuit diagram 1/6 extra.

SPECIAL TRANSISTOR BARGAINS

ALL BRAND NEW
 GET 15 (Matched Pair) 15/-; V15/10, 10/-; OC78 8/-; AF117 7/6; ORP12 10/6
 Set of Mullard 6 transistors, OC44, 2—OC45, OC81D matched pair, OC81, 25/-
EDISWAN MAZDA
 RFA101 8/6; XA108 8/6.
 R.F.11. Pack: 1—PX102 Mixer: 2—PX101 I.F. Amp.; (Equip. OC44 and OF43)..... 10/6
 R.F. 2 Pack: 2—PX101 I.F.—PX102 (Occ: 1—PX102 Mixer 12/6
 L.F. & P. Pack: Consisting of PXB113 Driver, Matched pair PX1171, mounted complete with heat sinks (Equip. OC81D and OC81)..... 12/6
ALL TRANSISTORS POST FREE

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. Size 7 in. w. x 2 1/2 in. d. x 5 1/2 in. h. This amplifier (which is used in a 250 gm. record player) employs heavy duty double wound mains transformer, ECC83, EL84, E280 valves. Separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Ready built and tested
PRICE 69/6 P. & P. 3/6
ALSO AVAILABLE. Mounted on board with output transformer and 5 in. speaker, ready to fit into cabinet below. **PRICE 88/6. P. & P. 4/6.**

QUALITY PORTABLE R/PLAYER CABINET

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autochanger or single Record Player Unit. size 18 x 14 x 8 1/2 in.
PRICE £39.6. Carr. 5/-

EMBASSY PORTABLE RECORD PLAYER CABINET.

Will accommodate amplifier, up to 7 x 4 in. speaker and B.S.R. or GARRARD auto-changer or single player unit. Attractive resin covered finish. Overall size 17 x 16 x 8 1/2 in. with uncut motor board. **PRICE 68/6. Carr. 5/-.**

4-SPEED PLAYER UNIT BARGAINS

All Brand New in Makers' Original Packaging
SINGLE PLAYERS
 B.S.R. TU12 £3.10.0 Carr. 2/6
 B.S.R. GU7 7 1/2 in. unit mounted pick-up arm £4.18.8. Carr. 4/-
AUTO CHANGERS
 B.S.R. UA14, £5.19.8; B.S.R. UA15/16, £6.19.6
 Latest B.S.R. L24 Super 8 1/2 in. £8.8.0
 Latest Garrard AT5 Mono £8.8.0 Stereo £9.0.0
 Standard Garrard Autoslim £6.10.0
 Garrard AT6 Mono... £10.10.0 Carr. 5/- on each

NEW CARTRIDGE BARGAINS

B.S.R. T083. High output compatible Stereo Cartridge. Brand new. Complete with Stereo LP/78 sapphire stylus and universal mounting bracket. Original price 44/11. OUR PRICE 28/6. P. & P. 1/6.
RONETTE STEREO 106 CARTRIDGE. Stereo/LP/78. Complete with two sapphires. Original list price 67/9. OUR PRICE 24/- P. & P. 1/6.
COLLARO HI-FI STEREO 7/0 CARTRIDGE Complete with complete universal bracket and stylus for stereo L.P. and 78. Original list price 68/8. OUR PRICE 25/- P. & P. 1/6.


E.M.I. 4-Speed Player and P.U.

FURTHER HUGE SAVINGS enables us to offer these at
67/6 P. & P. 4/6.
 Heavy 8 1/2 in. metal turntable. Low flutter performance 200/200 v. shaded motor with tap at 45 v. for amplifier valve filament if required. Turnover LP/78 head




THE NEW HARVERSON KIT FOR THE HOME CONSTRUCTOR

A really excellent all purpose A.C. mains 200/240v. **AMPLIFIER KIT TYPE EHL FOUR** 8 VALVE, 4 WATT using ECC83, EL84, E280 VALVES
 Special features include:
 ● Heavy duty double-wound mains transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar, microphone or record player. ● Provision for remote control of volume direct on chassis. ● All this builds onto a chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves, output transformer (3 ohm only), screened lead, wire, nuts, bolts, solder etc. (No extras to buy).
79/6 P. & P. 3/6
 Comprehensive circuit diagram, practical layout and parts list 2/6. (Free with Kits).

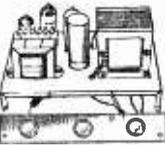


10 1/4 WATT HI-FI AMPLIFIER KIT

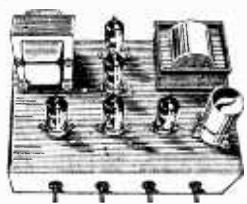

A stylish finished monaural amplifier with an output of 14 watts 1 ohm 2 EL84's in push-pull reproduction of both music and speech with negligible hum. Separate inputs for mike and gram. allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and independent volume control and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84's, ECC83, EF86, and E280 rectifier. Simple instruction booklet 1/6. (Free with parts).
All parts sold separately. ONLY £6.19.6 P. & P. 6/6
 Also available ready built and tested complete with standard input jack sockets. £8.15.0. P. & P. 6/6
 Carrying Case for above 28/6 P. & P. 4/-

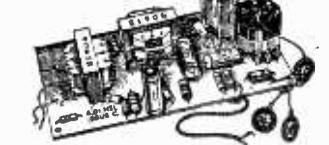
HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI



● Peak output in excess of 14 watts. ● All standard British components. ● Built on printed circuit board size 6 x 8 in. ● Gezonora size Driver and Output Transformers. ● Output transformer tapped for 3 ohm and 16 ohm speakers. ● Transistors (GET114) or 51 Mullard OC81D and matched pair of OC81 n/p. ● 9 volt operation. ● Everything supplied, wire, battery clips, solder, etc. ● Comprehensive, easy to follow instructions and circuit diagram 1/6. (Free with kit). All parts sold separately.
SPECIAL PRICE 45/- P. & P. 2/6.
 Also ready built and tested, 52/6. P. & P. 2/6.
A pair of TAI's are ideal for stereo.

HARVERSON'S F.M. TUNER Mk. I

● F.M. tuning head by famous tone maker. ● Guaranteed non-drift tuning. ● Frequency coverage 88—100 Mc/s.
 ● Balanced diode output. ● Two I.F. stages and discriminator. ● Attractive maroon and gold dial (7 x 5 in. glass). ● Self-powered, using good quality mains transformer and valve rectifier. ● Valves used EX785, two EP80's and E280 (rectifier). ● Fully drilled chassis. ● Size of completed tuner 8 x 6 x 4 1/2 in. ● All parts sold separately. Set of parts if purchased at one time £5.18.5. plus 8/6 P. & P. and ins. (Circuit diagram and instructions 1/6 post free. Mark II Tuner as above but complete with magic 578 front panel and brackets, £6.12.6. P. & P. 8/6.
 Mark III Tuner as Mark I but with output stage (EP82) and tone control. £7.7.0. P. & P. 8/6.
Handsome Metal Cabinets. Choice of Grey, Black or Green. To fit Mark I, 25/- P. & P. 2/6. To fit Mark II, 17/6. P. & P. 2/6.

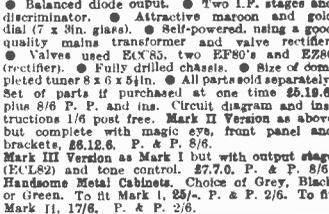

SPECIAL PURCHASE TURRET TUNERS

By famous maker. Brand new and unused. Complete with PX134 and PUF80 valves, 34-38 Mc/s I.F. circuits for Channels 1 to 5 and 8 and 9. Circuit diagram supplied. **ONLY 25/- each.** P. & P. 2/6.

BRAND NEW CYLON F.M. TUNER HEAD

Permeability Tuned. 88-100 Mc/s. Printed circuit. A completely screened unit ready for direct mounting in chassis. 10.7 Mc/s. I.F. O/P. Supplied complete with EC808 valve and full circuit diagram. Aerial input circuit suitable for either 75 ohm unbalanced or 300 ohm balanced. Size only 3 in. w. x 2 1/2 in. x 1 1/2 in. (2 1/2 in. high with valve). Limited number only at 27/6. P. & P. 1/6.
 Also available 10.7 Mc/s. I.F. trans. and disc. trans. 11/6 valv. P. & P. 1/6.
GORLER F.M. TUNER HEAD
 88-100 Mc/s. 10.7 I.F. 15/- plus 1/9 P. & P. (EC808 valve, 8/6 extra).

HARVERSON SURPLUS CO. LTD.
 170 HIGH ST., MERTON, S.W.19 CHerrywood 3985
 Open all day Saturday Early closing Wed. 1 p.m.
 A few minutes from South Wimbledon Tube Station (Please write clearly)
 PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS
 ORDERS CHARGED EXTRA
 SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEE LEFT HAND PAGE FOR MORE ITEMS


BENTLEY ACUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ARE CURRENTLY IN STOCK. ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE.

0A2	4/8	61887	25/-	7A7	12/6	25V5	7/9	AC2PEN/	E450	1/6	EL35	10/-	KTW62	5/6	QP25	5/6	U47	8/6	AF124	11/-
0B2	4/8	638W6	8/9	786	12/6	25V5G	7/9	DD 12/6	E476	5/6	EL36	8/9	KTW63	5/6	Q8720	10/6	U50	8/6	AF155	10/6
0ZAG	4/8	638W7	5/-	787	7/-	25V4G	5/-	EA280	5/6	EL37	5/6	KTW64	5/6	Q8150/16/6		U57	4/6	AF158	10/6	
1A3	2/4	618X4	4/-	793	6/-	25Z5	7/8	YD 23/3	EAC91	3/3	EL41	7/3	L83	3/-	R10	15/-	U76	4/6	AF127	9/6
1A4	12/6	6184	2/3	798	6/9	25Z6GT	8/-	AC6FEN 4/9	EAC42	7/6	EL42	7/6	LN152	6/-	R12	5/6	U78	3/6	BY213	11/6
1A5	5/-	618C5	4/-	707	5/-	27R8	23/3	AC/PEN	EB34	1/-	EL81	8/9	LN309	7/9	R16	29/-	U84	10/6	G03	5/6
1A7GT	7/9	61806	3/4	713	15/-	28107	6/9	(6)	17/6		EB41	4/9	EL83	6/9	LN319	8/6	R17	17/6	U101	10/6
1C1	4/-	618C4	3/-	715	14/6	30C1	6/6	AC/PEN	EC61	2/3	EL84	6/9	LP2	5/6	R18	9/6	U107	17/6	G14	11/6
1C2	8/6	61809	10/9	708	14/6	30C15	9/-	(7)	17/-		EB53	20/6	EL85	7/9	LZ319	6/6	R19	6/6	U191	9/6
1C3	8/6	61810	8/-	717	5/9	30R18	10/6	AC/SG	22/6		EB53	6/-	EL86	7/3	LZ329	6/6	R52	7/6	U251	9/6
1C5	5/-	61812	6/-	717	12/6	30P5	5/9	AC/SG/VW			EB54	6/6	EL1	2/6	ME41	13/6	U280	8/6	GET103	7/-
1C6	10/6	61810G	18/-	757	5/6	30P11	9/3	12/-			EB58	5/9	EL15	5/6	ME91	12/6	U47	2/6	GET106	17/6
1D5	6/6	618H6	5/-	734	5/-	30L15	5/6	ACTH 15/6	EC39	5/6	EL20	5/6	MHD4	7/6	RK34	7/6	U301	11/3	GET113	6/9
1D7	7/9	618W4	2/4	812	2/6	30L15	3/3	AC/UTP 15/-	EB91	5/6	EL220	16/6	MHD4	7/6	R130	22/6	U329	9/6	GET114	6/6
1FD1	6/6	61811	1/6	984	9/6	30P14	12/3	AC/VW12/-	EBF80	5/9	EL282	18/6	MHD1212/6		SP4B	19/6	U339	9/6	GEN35	3/6
1FD9	3/6	61813	9/6	912	3/-	30P12	7/6	AC/VW22/6	EBF83	7/3	EL280	13/6	ML6	5/9	SP1C	12/6	U403	9/6	GEN36	10/6
1G6	6/-	61816	3/-	917	7/6	30P16	5/3	ATP4 2/3	EPF89	6/3	EM4	17/6	MS4B	20/6	SP41	7/6	U454	5/6	GEN37	11/6
1H5GT	7/9	61825	9/6	1003	8/9	30P19	12/3	AZ1 5/9	EM121	10/6	EM34	4/6	MS4	12/-	SP42	12/6	U501	18/3	GEN38	10/6
1I4	2/3	61817	9/6	1062	12/3	30P13	8/6	AZ31 6/6	FC52	4/3	EM35	12/6	ML1214/4		SP61	2/-	U4020	6/6	GEN36	15/-
1L54	17/6	618P6	3/9	1001	7/-	30P14	9/6	AZ41 6/6	FC53	12/6	EM71	13/6	MX40	8/9	SP25	27/2	VMP4G	11/9	MAT100	7/9
1L4E	16/10	618P6T	7/6	1002	11/8	30P14	12/6	B36	4/9	FC54	6/-	EM80	6/3	N37	23/3	T41	9/6	VMP4B	12/3	
1L15	4/-	61870	5/-	1094	10/9	33	12/6	BL65	10/6	FC70	4/9	EM81	7/-	N78	36/6	TDD2	12/6	VP2B	9/6	
1L35	4/6	61871	5/6	1095	11/8	35A27	12/6	CL 17/6	FC90	6/6	EM84	6/9	N104	29/2	T104	7/6	VP2B	9/6	MAT121	8/6
1N5GT	8/6	61811	17/9	1018	9/9	35A3	20/6	FCR35	12/6	FC91	3/-	EM85	8/9	N39	15/-	TH4B	15/6	VP4	14/6	
1P1	6/-	61812	3/-	1013	6/3	35L6GT	6/6	FCR36	6/6	FC92	6/6	EM87	7/6	P41	3/6	TH21C	10/6	VP4A	14/6	
1P10	4/6	61813	3/9	1011	9/6	35W3	4/9	CJ4 19/6	FCR31	7/3	FN31	2/6	P81	2/6	TH360	14/6	VP4B	29/6		
1P11	5/3	61814	23/3	1013	8/3	35Z3	16/2	CL35 11/6	FCR32	5/-	FN91	5/6	PC86	10/3	TH233	6/6	VP4C	29/6		
1R5	4/6	61815	8/9	1014	11/8	35Z4GT	16/2	CL36 11/6	FCR33	29/1	FN92	5/6	PC87	10/3	TH233	6/6	VP4D	29/6		
1R4	5/-	61817	12/6	1103	17/6	35Z5GT	15/9	CV63 10/6	ECR34	21/7	FN81	7/3	PC88	9/6	TP25	5/6	VP41	5/6		
1R53	3/6	61818	13/5	1105	17/6	36	12/6	CV65 14/6	ECR35	5/-	FN83	9/3	PC89	5/6	TP26	17/6	VP43	9/6		
1T2	29/-	61823	8/3	1161	15/-	39	2/6	CV27 12/6	ECR40	7/-	FN84	8/6	PC97	7/3	TP46Z	11/8	VR75	21/6		
1T4	2/3	61824	9/6	1163	17/7	408U4	8/6	CV428 19/6	ECR31	3/6	FN85	8/6	PC98	6/6	TP46Z	11/8	VR75	21/6		
1U4	5/6	61825	2/6	1164	11/8	41MTL	8/6	CV428 19/6	ECR32	3/6	FN86	8/6	PC98	6/6	TP46Z	11/8	VR75	21/6		
1U3	5/3	61823	3/6	1248	18/6	41STH 15/-	5/6	CY1C 6/6	ECR33	4/6	FN91	3/-	PC98	8/6	UB41	10/6	VT61A	7/-		
2A7	12/6	61826	2/6	12A06	8/6	42	10/6	CY13 5/6	ECR34	5/6	FN92	3/6	PC98	8/6	UB41	10/6	VT61A	7/-		
2C26	2/9	61846	1/6	12A16	9/6	43	10/6	D1 1/3	ECR35	5/9	FN93	5/3	PC98	8/6	UB41	10/6	VT61A	7/-		
2D130	7/9	61856	3/6	12A26	8/6	45	10/6	D15 13/6	ECR36	8/6	FN94	5/3	PC98	8/6	UB41	10/6	VT61A	7/-		
2D21	5/6	61847	2/6	12A27	8/6	45Z6	12/6	D15 13/6	ECR37	11/6	FN95	5/3	PC98	8/6	UB41	10/6	VT61A	7/-		
2P	23/3	6186	3/6	12A48	10/9	50A5	21/10	D63 5/6	ECR80	15/-	FN91	4/-	PC98	8/6	UB41	10/6	VT61A	7/-		
2X2	3/-	61876	4/6	12A76	4/6	50B5	6/6	D77 2/3	ECR90	6/6	FN99	8/9	PC98	8/6	UB41	10/6	VT61A	7/-		
3A4	3/9	61874T	7/9	12A 47	2/6	50C5	3/6	DAC32 7/9	ECR92	6/3	FN2	14/6	PC98	8/6	UB41	10/6	VT61A	7/-		
3A5	6/9	61881	12/6	12A36	5/6	50C6GT	4/6	DAC91 3/6	ECR93	6/6	FN3	14/6	PC98	8/6	UB41	10/6	VT61A	7/-		
3A6	5/-	61882T	12/6	12A17	5/6	50C6GT	6/3	ECR94 2/6	ECR94	2/6	FN4	14/6	PC98	8/6	UB41	10/6	VT61A	7/-		
3D6	3/9	61871	1/3	12A26	6/6	52KU	14/6	DC030 6/9	ECR33	23/3	FN30	17/6	PC98	8/6	UB41	10/6	VT61A	7/-		
3Q4	5/3	61874T	4/-	12A 7	4/6	53KU	14/6	D14 12/6	ECR21	9/6	FN47	5/6	PC98	8/6	UB41	10/6	VT61A	7/-		
3Q5GT	7/-	61883G	3/3	12A 7	9/9	72	6/6	DD14 10/6	ECR33	22/8	FN48	5/6	PC98	8/6	UB41	10/6	VT61A	7/-		
384	4/6	61883GT	7/9	12A 6	5/9	77	5/6	EDT 74 7/6	ECR35	6/3	FN49	5/6	PC98	8/6	UB41	10/6	VT61A	7/-		
3Y4	5/3	61825	2/6	12B 8	7/6	78	4/6	EDT 74 7/6	ECR32	4/6	FN50	5/6	PC98	8/6	UB41	10/6	VT61A	7/-		
4D1	3/9	6111	10/6	12B87	6/-	80	5/3	DF33 8/6	ECR81	5/9	GN20	7/6	PC98	8/6	UB41	10/6	VT61A	7/-		
5R4G	6/6	6155G	12/6	12E1	16/9	83	22/6	DF66 15/6	ECR83	6/6	GN22	8/6	PENADD	12/6	UF42	4/9	X14	7/9		
5T4	7/-	6186G	6/6	12H6GT	11/6	83V	8/-	DF72 30/6	ECR84	9/6	GN23	17/6	25/-	UF80	6/3	X15	8/6			
514G	4/6	6157G	6/6	12J5GT	2/6	84E	12/6	DF81 2/3	ECR86	11/6	GN24	8/6	PEN401	12/6	UF80	6/3	X15	8/6		
61V4G	8/6	61810	10/6	12J2	7/3	90AG	6/7	DF96 8/6	ECR82	6/6	GN25	14/6	25/-	UF86	9/6	X41	15/6			
5Y8GT	4/9	6119	19/6	12K5 10/6	90AV	6/7	DF97 10/6	DF97 10/6	ECR83	9/6	H30	5/-	PEN45 7/-	UF89	8/6	X61	6/3			
5Y4	9/6	61D3	6/6	12K7GT	3/6	90CC	4/2	DH130 15/6	ECR86	8/9	HAB080	9/3	PEN45D	12/6	UF41	7/3	X63	6/9		
5Z3	7/-	61D13	7/9	12K8GT	9/1	90CV	4/2	DH176 11/6	ECR80	11/6	HL2	2/6	12/-	UF44	23/3	X64	7/3			
5Z4	7/6	61829	6/6	12K71T	3/6	90D1	4/6	DH75 4/6	ECR85	6/9	HL3	4/6	12/-	UF46	23/3	X64	7/3			
63012	9/-	61871	9/6	12K87	6/6	150B2	16/6	DF78 3/6	EP6	20/6	HL23	12/6	12/-	PEN3810/3	UL84	6/6	X66	7/3		
6A0G	3/9	61P1	9/3	12M2	4/-	150C2	4/6	DL181 25/3	EP9	20/6	HL23D5	5/6	12/-	PEN45D	UM4	15/2	X76M	9/6		
6A80	5/9	61P25	6/9	12M07	3/-	161	13/6	DL101 25/3	FP22	6/6	HL41	3/9	10/6	UM4	15/2	X78	20/6			
6A87	4/-	61P26	9/6	12M17	3/-	185BT	34/11	DL10711/11	FP36	3/3	HL41DDB8	8/6	10/6	PEN44	7/3	X79	27/6			
6A87	5/6	61P27	11/6	12M17	5/-	235GT	7/6	DL107 11/6	FP37	3/3	HL41DDB8	8/6	10/6	UL84	6/6	X81M	29/6			
6A85	2/6	607G	8/6	12M87	4/-	220B	10/6	DR40 15/6	FP39	3/9	HL133D	4/6	10/6	4020	17/6	U5	7/6			
6AG7	5/9	607GT	7/9	12M07	8/-	301	20/6	DK91 4/-	EP40	8/9	HL33D	4/6	10/6	PL33	9/6	U06	9/6			
6A15	6/6	61R74	5/3	12K21	5/-	302	10/6	DK92 8/6	EP41	8/9	HN309	25/6	PL36	9/6	U07	7/6				
6AK5	4/9	61R7GT	11/6	12L50	7/6	303	15/-	DK96 6/6	EP42	3/9	HN312	8/6	PL38	18/6	U08	11/6				
6AK9	6/-	61R87	5/6	13D1	5/6	304	15/-	DL23 7/6	EP50	2/6	HN32A	9/6	PL41	6/9	U09	5/3				
6AK8	5/9	61R87	4/6	13D3	5/6	305	13/6	DL35 5/6	EP54	3/6	HN33	8/6	PL42	5/3	U102	4/6				
6A15	2/3	61R87	4/6	14B6	20/9	306	13/6	DL63 5/3	EP73	5/6	HW4350	5/6	PL43	5/3	UY1N	10/3				
6AM5	2/6	61H7																		

INCREASE YOUR KNOWLEDGE

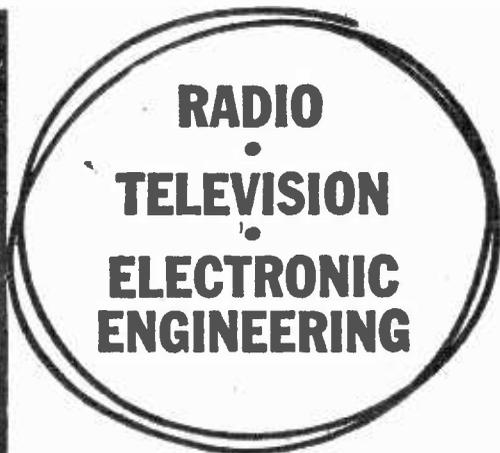

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING,
INDUSTRIAL TELEVISION, RADIO AND
TELEVISION SERVICING, ELECTRONICS,
COMPUTERS AND PROGRAMMING,
ELECTRONIC TECHNICIANS, SERVOMECH-
ANISMS, TELEMETRY, COLOUR TV,
INSTRUMENTATION, AND PRINCIPLES OF
AUTOMATION.

ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers
C. & G. Telecommunication Techns' Cert.
C. & G. Supplementary Studies
R.T.E.B. Radio/TV Servicing Cert.
P.M.G. Certificates. Radio Amateurs' Exam.

LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of
Radio as you build YOUR OWN 5-valve superhet
Receiver and Transistor, Portable Signal Generator
and High Quality Multitester. At the end of the course
you have invaluable practical equipment and a fund of
personal knowledge and skill. ICS Practical Radio
Courses open a new world to the keen amateur.

THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to com-
plete your technical qualifications, or further special-
ised knowledge, ICS can help you with a course
individually adapted to your requirements.

There is a place for you among the fully-trained men.
They are the highly paid men—the men of the
future. If you want to get to the top, or to succeed
in your own business, put your technical training in
our experienced hands.

ICS Courses are written in clear, simple and direct
language, fully illustrated and specially edited to
facilitate individual home study. You will learn in
the comfort of your own home—at your own speed.
The unique ICS teaching method embodies the
teacher in the text; it combines expert practical
experience with clearly explained theoretical training.
Let ICS help you to develop your ambitions
and ensure a successful future. Invest in your own
capabilities.

**FILL IN AND POST THIS COUPON
TODAY**

You will receive the FREE ICS Prospectus listing the
examinations and ICS technical courses in radio, television
and electronics. PLUS details of over 150 specialised
subjects.



PLEASE SEND FREE BOOK ON _____

NAME _____

ADDRESS _____

OCCUPATION _____ AGE _____

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEX HOUSE, PARKGATE RD, London SW11 2.65

LASKY'S RADIO

Offer the Finest Value and HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days when the sum paid will be refunded less postage.



The "SKYROVER" RANGE

GENERAL SPECIFICATION:

7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-94 M. and also 4 separate switched band-spread ranges, 13M, 16M, 19M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow stage by stage instructions.

SPECIFICATION:

Superhet 470 Kc/s. All Mullard Transistors and Diode Uses 4-U2 batteries, 5in. Ceramic Magnet PM Speaker. Easy to read Dial Scale. Band Spread Tuning, 500 MW Output. Telescopic Aerial & Ferrite Rod Aerial. **WAVEBAND COVERAGE:** 180-576M; 31-94M and Band Spread on 13, 16, 19 and 25 metre Bands.

A simple additional circuit provides coverage of the 1100/1150 M. band (including 1500 M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with detailed construction data. **Only 10/- extra Post Free.** This conversion is suitable for both models that have already been constructed.

NEW! The SKYROVER MkII

Now supplied with redesigned cabinet, edgewise controls, new colour tuning scale and cabinet in Sierra Tan. Controls: Waveband Selector, Volume Control with on/off Switch, Tuning Controls in plastic cabinet, size 10 x 6 1/2 x 3 1/2 in. with metal trim and carrying handle. **Can now be £8.19.6 P. & P. built for 5/- H.P. Terms: 20/- deposit and 11 months at 16/6.**

The SKYROVER DE LUXE

Tone Control Circuit is incorporated with separate Tone Control in addition to Volume Control, Tuning Control and Waveband Selector. In a wood cabinet size 11 1/2 x 6 1/2 x 3 1/2 in. covered with a wa-hable material with plastic trim and carrying handle. Also car aerial socket fitted. **Can now be built for £10.19.6 P. & P. 5/- H.P. Terms: 25/- deposit and 11 months at 20/-.**

Data for each Receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries 3/4 extra. All components Available Separately.


The "Sixteen" Multirange METER KIT

This outstanding meter was featured by *Practical Wireless* in the Jan. '64 issue. Lasky's are now able to offer the complete kit of parts as specified by the designer. **RANGE SPECIFICATION:** D.C. volts: 0-2.5-25-50-250-500 at 20,000 Ω /V A.C. volts: 0-2.5-50-250-500 at 1,000 Ω /V. D.C. current: 0-50 μ A. 0-2.5-50-250 mA. Resistance: 0-2,000 Ω . 0-200 Ω . C. 0-20M Ω Basic movement: 40 μ A I.s.d. moving coil. With universal shunt full scale deflection current is 50 μ A. Size/finish: Black plastic case, 3 1/2 x 5 1/2 x 1 1/2 in. Controls: 12 position range switch; separate slide switch for A.C. volts—D.C. ohms; ohms zero adjustment pot. meter; meter zero. External connections: Two 4mm. sockets for test lead plugs. Power requirements: One 1.5V. and one 1.5V. batteries. Complete with all parts and full construction details. Data and circuit available separately 2/6 refunded if all parts bought. Pair of Batteries. 2/5 extra.

LASKY'S PRICE £5.19.6

P. & P. 5/- H.P. Terms: 21/- deposit and 5 months at 21/-.

SINCLAIR MICRO-6

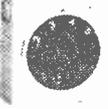

NEW SINCLAIR SUPER MINIATURES

THE MICRO-6 Self-contained pocket radio. Size only 1 1/2 x 1 1/2 x 1/2 in. A marvel of modern miniaturisation—truly amazing performance without a doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data. **59/6** Mercury cell 1/11 extra (2 required). Can be built for only **59/6** All parts sold separately.

THE SLIMLINE The new 2-transistor pocket radio. Size only 2 1/2 x 1 1/2 x 1 1/2 in. Micro alloy transistorised and printed circuit. All components available separately. **49/6** Easy to assemble. **CAN BE BUILT FOR 49/6**

THE X10 10 watt power amplifier fitted with integrated pre-amplifier. Requires only 1 mV. for an output of 10 watts undistorted. Frequency response is flat \pm 3 dB from 5 c/s. to 20 kc/s. Size only 6 x 3 x 1 1/2 in. Quiescent current 50z. Built on printed circuit. Operates from 12 v. D.C. at 75 mA. **3 quiescent. Circuit uses 2 transistors. KIT PRICE £5.19.6** Free 7 M.A.T.s and 4 RF power transistors.

AVAILABLE READY BUILT, TESTED AND GUARANTEED, £6.19.6, Post Free. 3 pots, 10 volume, Bass and Treble, 7/6 the 3 extra. Mains power pack, if required, 54/-

E.M.I. 4-SPEED RECORD PLAYER New, unused and individually boxed fitted with lightweight 9in. metal turntable is fitted. For use on 200/250 volt A.C. Mains, with Auto-stop. The stereo cartridge will play all types of Mono Records, 78's L.P.'s etc.

LASKY'S PRICE 79/6 P. & P. 3/6 EXTRA

The "REALISTIC" Seven

★ 7-transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker. ★ All components mounted on a single printed circuit board. ★ Full medium and long wave cover. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. Blue/Grey or all Grey. ★ Easy to read dial. ★ External socket for car aerial. ★ I.F. frequency 470 Kc/s. ★ Ferrite rod internal aerial. Operates from PP9 or similar battery. ★ Full comprehensive data supplied with each receiver. All coils and I.F.'s etc. fully wound ready for immediate assembly. An Outstanding Receiver. **LASKY'S PRICE** for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data. Can be built for **£5.19.6 P. & P. 4/6** PP9 Batt. 3/6 Data and Instructions separately 2/6. Refunded if you purchase the parcel.



REALISTIC Seven DE LUXE

With the same specification as standard model—PLUS a superior wood cabinet in contemporary styling. ALSO a full vision circular dial. **FOR ONLY £1 EXTRA P. & P. as std. model.**

RECORD PLAYERS

45 r.p.m. 6 volt Batt. operated complete with pick-up fitted crystal cartridge. Size only 7 1/2 in. x 6 1/2 in. Fitted auto. stop and start. New and perfect. **45 r.p.m. Model 49/6 P. & P. 2/5** 2 speed model for 33 and 45 r.p.m. (as illustrated) **59/6 P. & P. 2/6**



TRANSISTORS

ALL BRAND NEW & GUARANTEED

GET S1, GET S5, GET S6, 2/6; 873A, 874P 3/6; OC45, OC71, OC81D 4/6; OC44, OC70, OC76, OC81 (match pair 10/6) 5/6; AF117, OC75, OC170, OC200 6/6; OC43, OC73, OC82D 7/6; OC201, OC204 15/-; OC205, OC206 19/6; OC28 24/6.

TRANSISTORISED TELEPHONE AMPLIFIER

Powerfully amplifies the incoming call. The pick-up is suction fixed to phone. Battery-operated at negligible cost. Fitted with on/off switch and vol. control. Size: 4 1/2 x 3 x 1 1/2 in. Complete with PP3 battery. **LASKY'S PRICE 69/6, P. & P. 2/6.**

GUITAR PICK-UPS

CGM5 Crystal-high imp. Size only 1 1/2 x 1 1/2 x 1 in. Clips to finger board—no screws. Complete with cable.

LASKY'S PRICE 15/11, P. & P. 1/- CG M35, Fully adjustable pick-up position carrier. Simply fixed. Separate tone and volume control. Heavy chrome finish. Pick-up size 3 1/2 x 1 1/2 in., control size 2 1/2 x 1 1/2 in. Complete with long lead and back plug. **LASKY'S PRICE 59/6 P. & P. 1/6**

LASKY'S FOR D.I.Y. CONSTRUCTION BARGAINS

Service in Great Britain to both & HI-FI ENTHUSIASTS

NOTE! THERE WILL BE NO INCREASE IN OUR PRICES ON IMPORTED GOODS WHILE STOCKS LAST

SPEAKER OFFERS !!!

PANE 12in. Type 122/17
Shown right. Listed at £11.17.8
Power handling 25 watts—15
ohms imp. Flux density 17,000
gauss. Special Aniso-tropic
magnet. Limited stock.



LASKY'S PRICE
£5.19.6 P. & P.
5/-

WHARFEDALE WNA. 12

12"—15Ω Impedance. Flux density 14,000 oer/lin.
Max. input 30 watts peak. Frequency range 25—
4,000 c.p.s. (Cone fitted with roll surround).

WHARFEDALE SUPER 5

5"—mid-range and high frequency speaker. 15Ω
impedance. Frequency range 300-17,000 c.p.s.
Aluminium voice coil.

These two speakers provide an ideal matched pair
for a full range Hi-Fi speaker system. Both brand
new and individually boxed.

LASKY'S PRICE £12.19.6 THE PAIR
(P. & P. 10/- extra.)

THE HARROW CVI VARIABLE CROSSOVER

Gives variable volume control of Woofer and
Tweeter. Strong metal construction. Size 4 x 2 1/2
x 1 1/2in. Screw tag connections.

LASKY'S PRICE 22/6 P. & P. 1/6.

NOW IN STOCK THE NEW STUDIO RANGE OF CELESTION HI-FI SPEAKERS

TRANSISTORISED MICROPHONE MIXER

The Harrow will mix 4 high impedance channels;
Wax, tape rec's, turners, gram, etc. 9 v. battery
operated. Neatly styled, size only 6 x 2 1/2 x 2 1/2in.
Standard Jack sockets. Complete with PP3 batt.,
full circuit diagram and operating instructions.

Model TM4 Mono 59/6 P. & P. 9/6

Model SM5 Stereo 72/6 P. & P. 2/6

"HARROW" POWER PACK

Battery eliminator—converts your battery
portable to A.C. mains. Replaces 6 v. 4 1/2 v. or
9 v. batteries. State voltage required when
ordering. Size only 3 x 2 x 2 1/2in.

LASKY'S PRICE 29/6 P. & P. 1/6

INTERNATIONAL TAPE

Famous American Brand—Fully Guaranteed

5in. Double play, 1,200ft., Mylar base	15	0
5in. Long play, 900ft., Acetate base	10	0
5in. Standard play, 600ft., P.V.C. base	8	0
6 1/2in. Long play, 1,200ft., Mylar base	15	0
6 1/2in. Double play, 1,800ft., Mylar base	23	6
6 1/2in. Long play, 1,200ft., Acetate base	12	6
6 1/2in. Standard play, 800ft., P.V.C. base	11	6
7in. Standard play, 1,200ft., Mylar base	12	6
7in. Long play, 1,800ft., Mylar base	19	6
7in. Double play, 2,400ft., Mylar base	25	0
7in. Long play, 1,800ft., Acetate base	15	0
3in. Message tape, 150ft.	3	6
3in. Message tape, 225ft.	4	11
3in. Message tape, 300ft.	7	6
3in. Triple play, 450ft., Mylar base	12	6
4in. Triple play, 900ft., Mylar base	22	6
6in. Triple play, 1,800ft., Mylar base	42	6
6 1/2in. Triple play, 2,400ft., Mylar base	55	0
7in. Triple play, 3,600ft., Mylar base	75	0

P. & P. 1/- extra per reel; 4 reels and over Post/Free

207 EDGWARE ROAD, LONDON, W.2.

Near Praed St. PADDINGTON 3271/2

BOTH OPEN ALL DAY SAT. Early Closing Thurs. Mail Orders to Dept. X.W., Edgware Rd.



LASKY'S RADIO
THE NEW "KUBA"
IMPORTED AM/FM
STEREO RADIOGRAM
CHASSIS

Long, medium and short wavelength coverage plus VHF/FM. Piano key wave-change. Separate flywheel
tuning on AM and FM Bass, treble and balance controls. Magic-eye tuning indicator. Ferrite rod aerial.
The very latest printed circuitry. Provision for multiplex adaptor. 5 valves—line-up: 6X85, 6CH801,
6XN83, 6LL80, 6AF801. Full vision tuning scale, size 21 x 6in. Overall dimensions: 21 x 6 1/2 x 8in.
Lasky to the very highest standards.

LASKY'S PRICE 29 1/2 GNS.

Carriage & Insurance 12/6 extra.

SUPER TAPE RECORDER OFFER SIEMENS STEREO TAPE RECORDERS

High precision machines offering a maximum of
facilities for the enthusiast and connoisseur. Exceptional
fine performance standards ensuring superb
reproduction. All models have the following general
specification: ★ Completely self contained. Record,
replay and Audio amplifiers built in. ★ All trans-
istorised—no warming up period. ★ Three heads—
separate record, replay, erase (also provides sound-
on-sound recording). ★ Three speeds—7 1/2, 3 1/2,
1 1/2 i.p.s. ★ 4 tracks. ★ Taken 7" reels. ★ Record level
indicators on both channels. ★ Remote control
facilities. Other facilities on these, exceptional
machines include: push button controls; tape end
stop; separate switched base boost and treble cut;
sep. inputs for 2 microphones, 2 radios and 2 pick-ups with provision for mixing 3 inputs. Outputs
provided are 2 at 4 ohms; 2 sets headphone; 2 external amplifiers. Power output 2 1/2 watts per channel
All brand new, boxed and fully guaranteed.

MODEL 12 (illustrated). Self contained portable
with 2 built in speakers. List price 94 gns.

MODEL 10 self contained portable recorder with
one built in speaker. List price 69 gns.

MODEL 14 built in a contemporary styled wood
plinth with one built in speaker. List price 94 gns.

Carriage and insurance 15/- extra on each.



LASKY'S PRICE 59 GNS.

LASKY'S PRICE 52 GNS.

LASKY'S PRICE 49 GNS.

VIKING "TRANSISTOR 50"

50 watt amplifier. Superb amplifier for all music and
P.A. work—ideal for guitars, groups etc. Fully trans-
istorised for maximum efficiency. 4 inputs with
mixing facilities plus reverb/echo chamber.
Bass and treble controls. Fully built and guaranteed.
In strong wood cabinet covered in washable material.
Size approx. 22 x 10 x 9in. Output imp. 15 ohms.
For operation on 200/250v. A.C. mains.

LASKY'S PRICE 45 GNS. Carr. & Pack. 10/6



VIKING "SOUND 30" High quality guitar and P.A. amplifier. A.C. Mains
operated—30 watt output. 8 inputs. Fitted with 4
separate volume controls for mixing, also Bass and Treble controls. 16 ohms out. British made—highest
quality components used throughout—fully guaranteed. In strong portable case, size approx. 20 x 9 x 6in.

LASKY'S PRICE 35 GNS.

Carr. & Pack. 7/6 extra.

THE BH-14 AMPLIFIER High quality 14 watt power amplifier with bass and
treble controls and separate volume controls on each
input. Output 3 or 15 ohms. Valve line-up: 2 x EL84, 1 x EF86, 6X85 and EZ81. Frequency res.
front panel. Complete kit of parts with detailed construction data. Instruction book avail. sep. 1/6.

LASKY'S KIT PRICE 9 GNS.

AVAILABLE READY BUILT AND TESTED LASKY'S PRICE 11 GNS. Post and Packing 7/6

LAST FEW B.S.R. AUTOCHANGERS AT LOWEST EVER PRICES


All brand new and fully guaranteed—complete with cartridge and
stylus.

U116 4 speed, mains \$4.19.6

UA14 4 speed, 9v. battery operated \$5.19.6

UA20 4 speed, mains \$6.19.6

Aid 5/- carriage and packing on each.

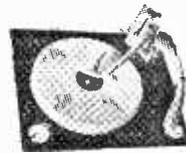

33 TOTTENHAM COURT ROAD, W.1.


Nearest Stn., Goudge St. MUSEUM 2605

152/3 FLEET STREET, LONDON, E.C.4

Telephone: Fleet Street 2833


Open all day Thursday. Early closing Sat.

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

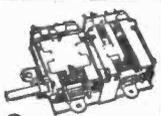

2

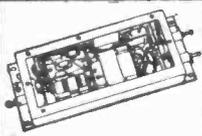3 to 4 watt Amplifier Kit comprising chassis $8\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$ in. Double wound mains transformer, output transformer, volume and tone controls, resistors, condensers etc. Valves 6V6, ECC81 and metal rectifier. Circuit 1/6 free with kit. 29/6 plus 4/- P. & P.



4

3

1. 6 VALVE 15 WATT PUSH-PULL AMPLIFIER, $15 \times 17 \times 1\frac{1}{2}$ in. A.C. Mains 200-250 volts. 4 inputs with controls for same and bass and treble lift controls. Tapped for 3 and 15 ohm speakers. Extra H.T. and L.T. for F.M. Tuner supplies etc. Built and tested. 7 gns. P. & P. 12/6.
2. CYLON A.M. F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION. Size $2\frac{1}{2} \times 2\frac{1}{2}$ in. approx. By famous manufacturer. A.M. I.F. 470 Kc/s. F.M. I.F. 10.7 Mc/s. A.M. coverage from 1620 Kc/s-525 Kc/s. F.M. coverage 108 Mc/s-88 Mc/s. Circuit diagrams 2/6. FREE with Tuner, 1st, 2nd and 3rd A.M. I.F.'s, 1st, 2nd, 3rd and 4th F.M. I.F.'s V.H.F. Osc. choke, A.M. I.F. trap, A.F. 114 and A.P. 115. All the above are the R.F. end of an A.M./F.M. receiver car radio etc. The above six items, £2.10.0.

3. AMPLIFIER KIT.

4. TRANSISTOR INVERTOR, 50 v. D.C. Input. Output 240 v. A.C. 40 watts incorporating transformers, choke, condensers and 2 GFT1573. In solid 16 gauge aluminum case, size $15 \times 6 \times 2\frac{1}{2}$ in. by famous manufacturer. 19/6, plus 6/- P. & P.



6



5

5. FLUORESCENT LIGHT FITTING. Twin 40 watt 200/250 v. less tubes 58/6. P. & P. 6/-.

6. SIGNAL GENERATORS: Cash £7.5.0. P. & P. 6/6. Coverage 100 Kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case $10 \times 6\frac{1}{2} \times 5\frac{1}{2}$ in. Three miniature valves and Metal Rectifier. A.C. mains 200/250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 multivolts, 0-5v. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy 2 per cent.



7



8

7. A.C. MAINS MOTOR. Can be used for a variety of purposes, silent running, satisfactory in every way. 230/250v. A.C. 9/6. P. & P. 2/-.


8. POCKET MULTI-METER. Size $3\frac{1}{2} \times 2\frac{1}{2} \times 1\frac{1}{2}$ in. Meter size $2\frac{1}{2} \times 1\frac{1}{2}$ in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts. 0-15, 0-150, 0-1,000. D.C. current 0-150 m.A. Resistance 0-100K Ω . Complete with test leads, battery and full instructions, 58/6. P. & P. 2/6. FREE GIFT for limited period only. 30 watt Electric soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.



10

9. CHANNEL TUNER I.F. 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCC80 and PCC84 (in series). Covers BBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/- . P. & P. 3/-.

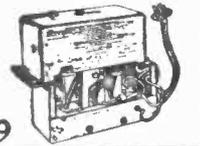10. THE MOTORISTS' REV. COUNTER. Kit of parts comprising 270 degree 3in. moving coil movement. Manufacturer's present price of this movement would be at least £7. Complete with full instructions and circuit diagram. Scale calibrated up to 8,000 r.p.m. Can be used with any 4 or 6 cylinder car. 49/6, plus 3/6 P. & P.



9

11. B.S.R. MONARCH UA14 WITH FULL FI HEAD, 4-speed, plays 10 records, 12in., 10in., or 7 in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position: colour brown. Dimensions: $12\frac{1}{2} \times 10\frac{1}{2}$ in. Space required above baseboard 4 $\frac{1}{2}$ in., below baseboard 2 $\frac{1}{2}$ in. Fitted with Full FI turnover crystal head. £5.19.6. P. & P. 6/6.

12. 50 MICRO-AMP METER movement by world famous manufacturer. Size $3 \times 2\frac{1}{2}$ in., 25/-, plus 1/6 P. & P.




11




12

13. 8-watt PUSH-PULL 5 VALVE AMPLIFIER. A.C. mains 200-250v. Size $10\frac{1}{2} \times 6\frac{1}{2} \times 2\frac{1}{2}$ in. 5 valves. For use with all makes and types of controls for same. Negative test hook. Two input, mike and gram. and pick-up and mike. Separate controls for Bass and Treble lift. Responses flat from 40 cycles to 15 Kc/s. 2 dB down to 20 Kc/s. Output 8 watts at 5 per cent total distortion. Note level 40 dB down all hum. Output transformer tapped for 3 and 15 ohms speech coils. For use with Rd. or L.P. records, musical instruments such as guitars, etc. Suitable for small halls, £3.19.6. P. & P. 7/- . Crystal mike to suit, 15/-, P. & P. 2/- . 5in. P.M. Speaker to suit, 12/6, P. & P. 2/-.

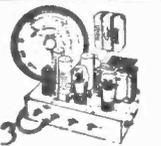14. FLUORESCENT LIGHT KIT. Twin 30 choke instant start, complete with 4 bi-pin 200/250v. holders, 11/6, P. & P. 4/- . Twin 40 choke instant start with 4 bi-pin 200/250v. holders, 17/6, P. & P. 4/-.



13

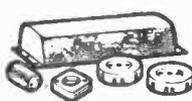

14


15. RINGO BURGLAR ALARM SYSTEM, A.C. mains. 200/240 volts. Fire salvage slightly tarnished. List price 7 gns. Our price, complete with double gong bell, five micro switches and full instructions, 49/6. P. & P. 4/-.

16. FIXED FREQUENCY SIGNAL GENERATOR. Crystal controls in metal case, size $10 \times 6 \times 6$ in. Incorporating two 6CL3 valves, mains transformer, metal rectifier, choke, indicator, lamp, crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new, 38/6, plus 6/- P. & P. A.C. mains 200-250 volts.

SILICON RECTIFIERS, 250v. P.I.V. 750 mA. Six for 7/6 post paid.



15

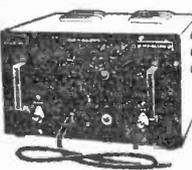

16

RADIO & T.V. COMPONENTS (ACTON) LTD.

21b High Street, Acton, London, W.3.

All enquiries S.A.E. Goods not despatched outside U.K.

Shop hours 9 a.m.—6 p.m. Early closing Wednesday

SPECIAL OFFER! FROM R. & T.V. LTD.

Elegant Seven

COMBINED PORTABLE & CAR RADIO

The Radio with the STAR features
4in. SPEAKER


- ★ 7-transistor superhet. Output 350mVv.
- ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12½x8½x3½in.
- ★ Horizontal tuning scale size 1½x2½in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. 470 K/cs.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket.
- ★ Full after-sale service.

ONLY
£4.19.6


Plus 5/6 P. & P. Parts list & circuit diagram 2/6. FREE with parts.

SPECIAL OFFER—POWER SUPPLY KIT to purchasers of "Elegant Seven" parts, incorporating mains transformer etc. A.C. mains 200-250v. Output 9v, 100mA, 7/6.

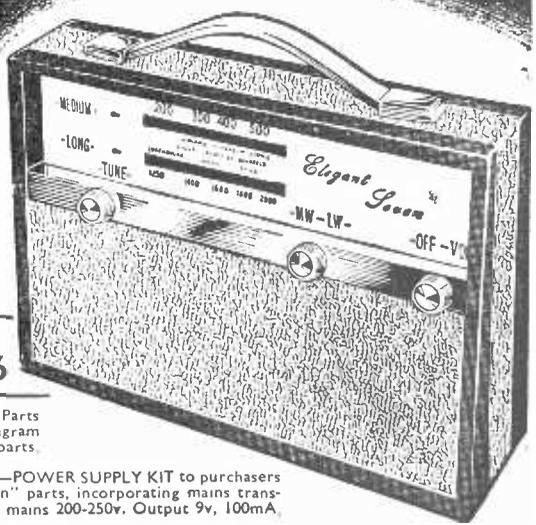Goods not despatched outside U.K. All enquiries S.A.E. Terms C.W.O.



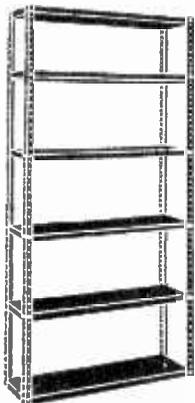RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3
Open 9 a.m.—6 p.m. including Sats. Early closing Wed.



STEEL SHELVING

BRAND NEW

C.W.O. or C.O.D. FREE DELIVERY within 14 days. N. Scotland, Ireland, L.O.M. 10% extra.

60/-

71in. high x 34in. wide 12in. deep with 6 shelves as illustrated.

Each shelf will hold over 3 cwt. Shelves adjustable every 2 in. Stove enamelled dark green. White enamel units 50% extra.

Height	Width	Depth	No. of shelves	Price	Price each 3 or more	Extra shelves
71 in.	34 in.	9 in.	6	58/-	56/-	7/-
71 in.	34 in.	12 in.	6	60/-	58/-	8/-
71 in.	34 in.	15 in.	6	69/-	67/-	9/6
71 in.	33½ in.	18 in.	6	81/-	79/-	11/6
85 in.	34 in.	12 in.	6	68/-	66/-	8/-
85 in.	42 in.	12 in.	6	86/-	84/-	11/-

Contractors to H.M. Govt. and United Kingdom Atomic Energy Authority. Exporters of Steel Shelving.

Buy direct from the manufacturers

R **ROCHDALE METAL PRODUCTS**
Dept. P.W. **WATERFOOT — LANCS.**
Phone: Rossendale 2450

BARGAINS FROM BROADWAY ELECTRONICS

- GARRARD A.T.6 Hi-Fi Autochanger G.C.8 mono cartridge—£9.19.6, post free.
- GARRARD AUTOSLIM 4 speed changer—£6.10.0, post free.
- 12in. ALTHAM SPEAKER with built in tweeter 3 ohm or 15 ohm 7,000 Gauss Magnet. Only 29/6, postage 3/6.
- HAYDON CABINET (17 x 15 x 8in.) designed to take a 12in. Heavy Duty Speaker. 50/-, postage 7/6.
- The Famous B.M.3 XTAL MICROPHONE with neck lanyard 30/- table stand for above 2/6 extra. Xtal insert 7/3.
- 4-UTAR PICK-UP complete with clip and screened lead—12/6.
- 3-WAY PUSH BUTTON UNITS Each button operates a 4-pole 2-way switch—4/6.
- BARGAINS IN TRANSISTORS Mullard RF Packs OC44 two OC45, 12/6; AF Packs OC81D two OC81, 8/6; OC44, 3/6; OC45, 3/-; OC71, 2/6; OC72, 3/-; OA81 diode 2/3; OC170, 6/6; AF 117, 6/6; ORP12, light cell, 7/6; OC29, 12/6; OC35, 12/6.
- TRANSISTOR ELECTROLYTICS 1, 2, 4, 5, 8, 10, 16, 32, 50, 100 Mfd. all at 15 volts—1/3 each.
- McMICHAEL TELESCOPIC TV AERIAL 23in. extends to 45ins. Fitted with coax plug, will suit any set. Only 7/6.
- CARTRIDGES Acos 67-1G Low Output, 67-2G Medium Output, GP59-5 High Output, Garrard GC2 or GC8 all with mounting bracket 15/-.
- Ronette Stereo with mounting bracket, 25/-.
- EARPIECES with cord and 3.5mm plug, 8 ohm magnetic 3/-; 250 ohm, 4/-; 180 ohm magnetic with clip 6/6; Xtal, 4/-; 3.5mm plugs with nice long shank complete with jack, 3/-; 3.5mm plugs with nice long shank complete with jack SCREENED, 4/-.
- TOGGLE SWITCHES Single pole with on/off plate, 2/6.
- NEON PANEL LIGHTS 240v. A.C. Arcoletric, 2/6.

TERMS: C.W.O. OR C.O.D.

BROADWAY ELECTRONICS
92 MITCHAM ROAD, TOOTING, S.W.17

Phone: BALham 3984
(four minutes from Tooting Broadway Underground Station)

QMAX CHASSIS CUTTER

Four parts; a die, a punch, an Allen screw and key

tin.	14/8	14in.	18/-	2in.	34/8
tin.	14/6	14in.	18/6	2 1/2in.	37/9
tin.	18/6	1 1/2in.	20/-	2 1/2in.	44/9
tin.	18/9	1 1/2in.	20/-	2in. sq.	31/6
tin.	18/-	1 1/2in.	20/8	1 1/2in. sq.	28/6
1 1/2in.	18/-	1 1/2in.	22/6		

THE TRIPLETONE HI-FI MAJOR

PRICE ONLY **£15.18.9** COMPLETE
Guaranteed 12 Months

A 12 watt amplifier with a pre-amp for mic. and mic./gram mixing. Frequency response ± 1 dB 10-20,000 c/s. Distortion only 0.15% with noise and hum -80 dB. Separate Bass, Middle and Treble lift controls. Valve line-up, 12AX7, 12AX7, EL84, EL84 and E231. Push-pull output 200/250v. A.C. input. Size 12 x 5 x 8in. high.
De Luxe Case: 14in. x 9in. x 7 1/2in. 30/- extra.

New R.C.S. Valves 90 day guarantee

1R3	6/-	6QT6	6/-	6BC4	8/-	6CL84	5/-
1R5	6/-	6BX7	5/-	6EB3	8/-	6FL81	10/-
1T4	3/-	6V6GT	6/-	6BF60	8/-	6FL83	8/-
3R4	7/-	6X4	5/-	6ECH42	9/-	6PY80	7/-
3V4	7/-	6X5	5/-	6ECH81	9/-	6PY81	8/-
5Y4	8/-	12AT7	6/-	6CL80	9/-	6PY82	7/-
603	6/-	12AU7	6/-	6EL82	10/-	6P91	6/-
604	6/-	12AX7	7/-	6EL83	7/-	6U2	7/-
6Z4	9/-	12K7	5/-	6E184	7/-	6UB4	8/-
6AM6	6/-	12K8	14/-	6E186	10/-	6UB81	8/-
6AT5	9/-	12Q7	7/-	6E189	8/-	6UB82	9/-
6BA7	9/-	20Y6G	9/-	6EL84	7/-	6UB83	9/-
6BE6	6/-	6E8	6/-	6E185	8/-	6UB84	9/-
6BU	3/-	3R2Z4	5/-	6E186	9/-	6UL82	10/-
6J5	5/-	904	2/-	6E240	5/-	6E189	9/-
6J6	5/-	6A2P96	8/-	6E280	7/-	6EA1	9/-
6J7G	6/-	6DF96	8/-	6E281	7/-	6Y41	5/-
6K6	5/-	6K96	5/-	6M14	10/-	6U35	5/-
6K7G	5/-	6L96	5/-	6P08	7/-	6U9	7/-
6R9G	5/-	6ABC80	5/-	6PC84	8/-	6VR100	7/-
6N7M	6/-	6EB91	4/-	6PC80	8/-	6W81	8/-

I.F. TRANSFORMERS 7/6 pair
465 k/s Sing Tuning Miniature Can. 31in. dia.
High Q and good bandwidth with Data Sheets.

NEW ELECTROLYTICS

TUBULAR	TUBULAR	CAN TYPES	
1/350V	2/-	50/350V	9/-
9/350V	8/-	100/250V	8/-
4/450V	8/-	150/450V	12/-
1/450V	3/-	500/150V	7/6
1/450V	3/-	1000/12V	5/-
32/450V	9/-	5,000/8V	6/-
50/25V	1/8	8/1450V	3/8
25/50V	3/-	8/1450V	3/8
50/25V	3/-	16/1450V	4/8
50/50V	2/-	32/3250V	1/8
50/50V	2/-	50/250V	1/8

TELESCOPIQUE CHROME AERIALS, 12 to 33in., 6/6.
TRIPLETS REX III, LII, 12/6. COAX PLUGS, 1/-.
LEAD SOCKETS, 2/-. PANEL SOCKETS, 1/-.
OUTLET BOXES (Surface or flush), 4/- each.
BALANCED TWIN FEEDER Yd. 6d., 90 or 300 ohms.
TWIN SCREENED per yd. 1/-, 80 ohms only.
Wire-wound Ext. Speaker Control, 10 Ω 3/6, 25 Ω 3/6
WIRE-WOUND POT. 3 WATT, 25 Watt Min.
TV Types. All values up to 10 ohms to 25K, 3/- ea.
30K, 4/-. (carbon 30K to 2 mcr. 3/6).
WIRE-WOUND 4 WATTS POT. Long spindle.
Values from 50 ohms to 50K, 9/8; 100K, 7/6.
PHILIPS TRIMMERS, 0.10 pF, 3.30 pF, 1/6.
TRIMMERS, Ceramic, 30, 50, 70 pF, 2/-, 100pF
150pF, 1/3; 250pF, 1/6; 500pF, 750pF, 1/8.
TV etc. TRIMMERS, 1000pF., with knob, 2/-.
RESISTORS, Preferred Values, 10 ohms to 10 meg.
20% \pm w. 1 w., 4d.; 1 w., 8d.; 2 w., 1/-.
High Stability, 1 w., 1/3; 2 w., Preferred values
10 Ω to 10 meg., upto 32, 10 Ω to 22 meg., 8d.
SEMICONDUCTORS: 2N1, 3/8; 2N2, 2/6; 2N3, 1/8.

5 watt	WIRE-WOUND RESISTORS	1/3
10 watt	10 ohms-10,000 ohms	2/-
15 watt		3/-
12.5K to 25K 10 w.		8/-
Toggle Switches, s.p., 2/6; d.p., 3/6; d.p.d.t., 4/-		
Min. Slide d.p.d.t., 2/6		

Volume Controls 80 ohm COAX
Linear or Log Tracks Semi-air spaced tin.
Long spindles. Midged 40 yds. 17/6
5 K ohms to 2 Meg. 60 yds. 25/-
L.S., 3/-. D.P., 4/6.
Stereo L/R 10/8; D.P. 14/6
1mm. long 4-1mm. A/og, 7/6.

MAINS TRANSFORMER 200/250 v. A.C.

Postage 2/- each transformer
STANDARD 250-0-250, 80mA 4.3 v. 3.5 a.
tapped 4 v. 4.4, 100V 6.3 v. 1 a., 3 v.
2 a. or 4 v. 2 a., 22/6, ditto, 350-0-350 29/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 a. 10/6
MIDGET, 320 v. 45 mA, 6.3 v., 2 a. 18/6
SMALL 250-0-250, 45 mA, 6.3 v. 2 a. 17/6
SFD, 250-0-250, 65 mA, 6.3 v. 3.5 a. 17/6
HEATER TRAPS, 6.3 v., 18 a. 7/6
Ditto tapped 1.4, 2.3, 4, 5, 6.3 v. 8/6
Ditto, sec. 6.3 v. 4 amp. 10/6
GENERAL PURPOSE LOW VOLTAGE, 2 amp.
3, 4, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. 22/6
AUTO TRANSFORMER, 150 w. 22/6
0, 115, 200, 250, 250 v. 500 w. 82/6
MULLARD "510" Mains Transformer 33/6
MAINS POWER PACKS. Ready built with
Transformers, Rectifiers, Condensers, providing
H.T. and cut-outs.
20V v. 20 mA. D.C. 6.3 v. 1 a. A.C. 25/6
220 v. 50 mA. D.C. 6.3 v. 2 a. A.C. 35/6
250 v. 80 mA. D.C. 6.3 v. 3.5 a. tapped 4v
and 6.3 v. 1 a. tapped 5 v. 4 v. 2 a. 45/6

INTERVAL TRANSFORMERS, 3:1 or 5:1, 9/-
O.P. TRANSFORMERS, Heavy Duty, 5/6, Multi-ratio,
7/6. Multi-ratio heavy duty push-pull, 10 w.
18/6. Battery, 4/8. Sub min. D1.96, 3/4, etc. 6/9.
10 w. output matching trans. 3, 7, 15, 12/6, 12/6.
L. OILCOILS, 10/10H, 50/85 mA, 5/-; 10H, 35 mA,
10/6; 10H, 150 mA, 14/-.

C.R.T. BOOSTER TRANSFORMERS
for heater cathode short or tubes with
failing emission. Full instructions.
Mains input, PRICE 10/6, Post 2/-
Type A optional 25% and 50% boost
2v. or 4v. or 6.3v. or 10.5v. or 12.6v.
State voltage required.

TINNED COPPER WIRE 14 to 24 swg., 4 lb. 3/8-
ENAMEL COPPER WIRE 16-22, 2/9; 24-30, 3/8;
32-40, 4/8; D.C.C. 28, 34, 36, swg., 2oz., 3/6.
FULL WAVE BRIDGE SELENIUM RECTIFIERS:
2, 6 or 12 v., 1 1/2 amp., 8/9; 2 a., 12/6; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/
350 v. for charging at 2, 6 or 12 v., 1 1/2 amp., 15/6;
2 amp., 17/8; 4 amp., 22/6. Circuit included.
AMMETER 0 to 5a, 10/6.

BOOKS list S.A.E.

Stroboscopic Disc 33, 45, 75 r.p.m. 1/-
How to receive Foreign T.V. 1/-
Boy's Book of Crystal Sets 2/6
"W.W." Radio Valve Data 7/6
High Fidelity Speaker Enclosure 5/-
Valve and TV Tube Equivalents 9/6
TV Fault Finding 5/-
Mullard Amplifier Manual 3/6
Radio Valve Guide, Books 1, 2, 3,
4 or 5 5/- each
Practical Radio Inside Out 3/6
Master Colour Code Chart 1/6
Transistor Controlled Models, 7/6
International Radio Stations 2/6

4 TRANSISTOR AMPLIFIER

A ready built miniature push-pull amplifier with
Driver and output transformers, 4 transistors,
for record players, intercoms. BARY ALARMS
Price 47/6 Complete instructions and circuit.
9v. Batt. 2/8. 2 1/2in. Speaker 15/-

1965 RADIOGRAM CHASSIS



THREE WAVEBANDS FIVE VALVES
S.W. 16m -50m. LATEST MULLARD, etc.
M.W. 200m -550 m. RCHM, EFR80, EFC81,
L.W. 800m -2,000m. EL84, 12286
12-month Guarantee
A.C. 200/240 v. Short-Medium Long/Grand.
Ferrite Aerial A.C.V. 3 ohm output 5 watts.
Tape Sockets. Glass dial. horizontal winding
size 18 x 7mm. Aligned and calibrated isolated.
Chassis size 13 1/2in. x 7in. high x 9in. deep.
£9.15.6 Carr. & Ins. 4/6.

Post 1/- (unless otherwise stated)
C.O.D. 2/- extra. Full list 1/-.

BAKERS 'Selhurst'

25 WATT 5 Gns. 12" GUITAR HEAVY DUTY



18 OHM VOICE COILS
Response 80-10,000 cps
Bass Resonance 30 cps
Genuine Musical Instrument Loudspeaker

BAKERS 12in. STALWART 15w. 5 gns.
or 15 ohms voice coils. Unlimited applications.
Response 45-13,000 cps. Magnet 12,000 lines.

BAKERS 12in. STANDARD 30w. 7 gns.
More powerful magnet 14,000 lines special sus-
pension. 40-14,500 cps. Recommended wherever
a high standard of reproduction is desired.

BAKERS 18in. BASE 25w. 18 gns.
New 1955 high power model. Aluminium coil
former with magnetic damping 25-15,000 cps.
Ideal for all electric circuits.

BAKERS 18in. AUDITORIUM 25w. 18 gns.
Improved slocom magnet with heavy plated
assembly weight 16lbs., 17,000 lines, 30-15,000
cps. Heat proofed coil former.

Full repair service. Specials made to order.
Other types up-dated. Re-coned. Re-energized.

LOUDSPEAKERS P.M. 3 OHM. 2 1/2, 3, 4, 6in.

7 x 4in., 15/8; 9in., 18/8; 6in., 17/8; 9 x 6in.,
8 x 3in., 21/-; 10 x 6in., 22/6; 10in., 30/-; 12in., 30/-;
EMI Double Cone Ceramic magnet 10w. 13 x 8in.
45/-, Horn Tweeter 104 dB 2 Kc/s to 16 Kc/s, 89/6
STENTORIAN HP102, 10in. 3 to 15 ohms 10 w.
92/-; 8in. HP121, 78/-; Croscever CX3000, 139/-
EXTENSION SPEAKER CABINET, 5in., 30/6;
6in., 18/8; 8in. 19/8; 10in., 20/8; 12in., 20/-.
TWIN GANG TUNING CONDENSERS, 365 pF.
1in. x 1 1/2in. x 1 1/2in., 300 pF Standard with
trimmers, 9/-; midgigt, 7/8; with trimmers, 9/-
500 pF slow inaction tuning standard, 9/-. Transistor
gang 208 + 170 pF with trimmers, 10/6. SMALL
3 gang 500 pF, 17/-, SINGLE 365 pF, 7/6. SINGLE
10 pF, 25 pF, 50 pF, 75 pF, 100 pF, 150 pF, 1/6.
Solid dielectric 100, 500, 500 pF, 8/6.
E.H.T. CONDENSERS, 0.001, 7kV, 8V; 20kV, 10V;
7kV, 10V, 8/6.
CERAMIC CONDS, 500v. 1 pF to 0.01 mfd., 9d.
DISCS, 470 pF to 0.01 mfd., 1/- each.
SILVER MICA CONDENSERS, 10% 50pF to 5000pF
9d.; 600 pF to 3,000 pF, 1/-, Close tolerance (+1pF)
2.2pF to 47pF, 1/-. Ditto 1/2 to 50pF to 810pF,
1/-. 1,000pF to 5,000pF, 1/8.

PAPER TUBULARS

550v. 0.1 9d.; 0.5 1/8.
500v. 0.001 to 0.05 2d.; 0.1 1/-; 0.25 1/8; 0.5 3/8.
1,000v. 0.001, 0.002, 0.005, 0.01, 0.02, 1/4; 0.05,
0.1 2/-; 0.25, 0.5 2/6.
2,000v. 0.005, 0.01, 0.02 2/6; 0.05 3/6.

WAVELENGTH SWITCHES

4 p. 4-way 2 wafer long spindle 4/6
2 p. 2-way or 2 p. 6-way long spindle 3/6
4 p. 2-way or 4 p. 3-way long spindle 3/6
3 p. 4-way or 1 p. 12-way long spindle 3/6

Wavechange "MAKITS". Wafers avail-
able: 1 p. 12 way, 2 p. 6 way, 3 p. 4 way,
4 p. 3 way, 6 p. 2 way, 1 wafer switch, 9/8;
2 wafer switch, 12/6; 3 wafer switch, 16/-;
additional wafers up to 12, 3/6 each extra.
Valveholders, EA50, 6d.; B2A, CRT 1/8.
Mazda and int. oct., 6d.; B7G, B8A, B8C,
B9A, 9d.; Ceramic EF50, B7G, B9A, int. oct.,
1/-; B7G, B8A cans 1/- each. Valve pins B7G,
B9A, int. octal, 2/3.

HIGH GAIN TV PRE-AMPLIFIERS


B.C.C. Channel 1 to 5. Gain 18dB.
ECC84 valve. Kit price 99/8 or 49/6
with power pack. Details 6d. (PC84
valve if preferred). Coils only 9/6.
H.A.N.I. III L.T.A. - Same prices
Tunable channels 7 to 13. Gain 17dB.
Circuit and coils only, 9/6. Chassis 4/9.

THE ORIGINAL

RADIO COMPONENT

OPEN ALL DAY (Wed. 1 p.m.)

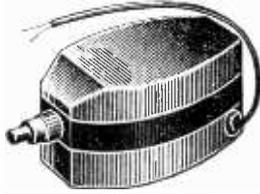THE "INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER 300/250 v. A.C.



35/-

Post 1/6

Leaflet S.A.E.

PLASTIC RECORDING TAPE

Double Play 7in. reel, 2,400ft. 25/6	Spare Plastic Reels
5in. reel, 1,200ft. 15/6	3in. 1/6
Long Play 7in. reel, 1,800ft. 15/6	5in. 2/-
5in. reel, 1,200ft. 12/6	7in. 2/6
5in. reel, 900ft. 10/6	5in. 2/-
Standard 7in. reel, 1,200ft. 12/6	5in. 2/6
5in. reel, 900ft. 8/6	7in. 2/6

"EASISPLICE" Tape Splicer 5/-
Leader tape 4/6; Splicing tape 3/-

CRYSTAL SET BOOKLET 1/-
CRYSTAL DIODE G.E.C. 2/-, OASI 3/-
HIGH RES. PHONES, 4,000 ohms, 15/-, 2,000 ohms 12/6. MOVING COIL PHONES, 100 ohms, 10/-
SWITCH CLEANER. Fluid squirt spout, 4/6 tin.

"6+1"

RADIO
First class components to make a 6 transistor 2 waveband superhet chassis. Ideal for portable or table radio. All parts including BVA transistors, ferrite aerial, 100% cut aerial coil, printed circuit, 8in. x 2in., but EXCLUDING Speaker and cabinet.
Speakers, 35 ohms, 6x4in., 21/-
5in., 17/6; 3in., 15/6. **£4.5.0**

BULGIN PLUGS AND SOCKETS. Non-reversible P7, 2-pin, 4/3; P73 3-pin, 4/6; P194, 6-pin, 6/6. JACKS, standard open circuit, 2/6. Closed circuit, 4/2. Grounding type, 3-pin, 1/3, 5-pin 1/6. Grounding lead jack, 3/6.

JACK PLUGS. Standard Type screened, 3/-; Grounding 3-pin, 3/6, 5-pin, 4/6. Phono Plugs, 1/-; Sockets, 1/-.
ALADIN FORMERS and cores, 4in., 8d.; 7in., 10d. 6in., Formers and cores T1 or 2, 2in. sq., x 2 1/2in. cr. sq., x 1 1/2in., 2/-, with cores.

SLOW MOTION DRIVES, 6-1, 4/3; 36-1, 10/6.
SOLON IRON, 25w, 24/-; 65w, 29/-, 200 or 250 v.
ANTEX SUB MIN IRON, 15w, 200 or 250 v., 32/6.
EMCH STANDS for above, 12/4. Spares in stock.
Paxolin Panels, 10 x 8 x 1/4in., 2/-.
Miniature Contact Coiled Rectifiers, 250V, 60mA, 7/6; 250V, 85mA, 9/6. Selenium Rect., 300V, 85mA, 5/-, K3/25, 600V, 5mA, 5/-, RM4, RM5, 14A116, 10/- each. FC31, 20/-.
TV etc. silicon sub. Min. Rectifiers, 250V, 45mA, 10/-; 250V, 150mA, 5/6.

465 kcs. SIGNAL GENERATORS
Price 10/6, ready made with valve 155.
POCKET SIZE 2 1/2 x 4 1/2 in. One resistor to change, full instructions supplied.
Battery 8/6 extra. Details Free

Coils Weirite "P" Type, 4/- each.
Osmer Midget "Q" type, ad. dust core, from 4/- each. All ranges. List S.A.E.
Repiano D.R.2, L and Med. T.R.F. with reaction, 4/6. Med. wave D.R., 3/6. Ferrite Aerials, M, 8/9; M. and L., 12/6. Osmer Ferrite Rod Aerials, L. and M. for transistor circuits, 10/- each.
Ferrite Rod, 8 x 3in., x 3in., 5 x 3in., 3/- ea.
H.F. Chokes, 2/6. Osmer Q.C.T. 6/9.
T.R.F. Coils, A/HF, 7/- pair; HAX, 3/6. Screwdriver, 5in., 6d. Test Prods, 2/9. Neoside Trimming Tool, 1/9.
Neon Mains Tester Screwdriver, 5/-.
Multicore Solder, 4d. yd. Dispenser, 2/6.
Mains Input Filter 4 amp, 7/-.
Car Radio Suppressors, 2/-.

Blank Aluminium Chassis, 18 s.w.g. 4 sides, riveted corners, lattice fixing holes, 2 1/2in. sides, 7 x 4in., 4/9; 9 x 7in., 5/9; 11 x 7in., 6/9; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6.
Aluminium Panels, 18 s.w.g., 12 x 12in., 4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/3; 8 x 6in., 2/-; 6 x 4in., 1/6.

MARTIN TAPE PRE-AMPLIFIERS (PLAY BACK THROUGH YOUR OWN AMPLIFIER)
For Collaro 2 Track Decks 8 gns. COMPLETE RECORDING & PLAY BACK AMPLIFIERS
For 2 Track Collaro £11.11.0

TAPE DECKS
Collaro Studio 2 Track £10.15.0
BSR TD2 2 Track Tape Deck £7.5.0
Collaro Record/Erase Heads, 2 track Upper or lower 35/- dr. 4 track £5.10.0

MAINS DROPPERS. Midget adjustable slide 0.3/2, 1,000 ohms, 6/-; 0.2A, 1,200 ohms, 6/-; 0.15A, 1,500 ohms, 6/-; 0.1A, 2,000 ohms, 6/-.
LINE CORD. 3-way 100 ohms ft., 1/- ft.
MIKE TRANSFORMERS. 50-1, 3/9.
P.V.C. Covered Wire, single or stranded, 2d. yd. Sleeving, 1, 2 or 4 mm., 3d.; 6 mm., 5d. yd.

R.T.H. TAPE MOTORS. 115 v. A.C., 25w, pair for £20 v. (in series), 12/6. Post Free.

SPEAKER-FRET. Tysan, various colours 52in. wide from 10/- ft.; 26in. wide from 5/- ft. Samples 1/-. Expanded Metal, Gold, 12 x 12in., 6/-. Panel, mounting fuse holder, 2/-. Fuses 1 1/2in. 60mA 3A. 6d. Insulated slide cutters, 8/6. Bib Strippers, 3/6.

RADIO AND TELEVISION SPARES
All leading makes, volume controls, etc., fine output transformers, etc., B. V. A. valves (current and obsolete types). Send S.A.E. for quotation.

WEYRAD P50

COILS AND TRANSFORMERS FOR 2-WAVE TRANSISTOR SUPERHET
Long and Medium aerial—RA2W 6in. rod 208 pF tuning, with car aerial coil 12/6
Osc. Coil P50LAG 17pF tuning, 5/4
1st and 2nd I.F. P502CC 470 kc/s 5/7 each
3rd I.F. P503CC 6/-, Spare Cores, 6d.
Driver Transformer—LPDT4 9/6
Wavechange Slide Switch d.p.d.t. 3/6
Printed Circuit—PCAL Size 2 1/2 x 8 1/2in.
Ready drilled and printed 9/6
Volume Control, 5K-DP 4/6
35 ohm Speakers, 3in., 15/6; 5in., 17/6; 6 x 4in., 21/-.
6 Mullard Transistors and Diode 25/-
J.B. Tuning Gang with trimmers 10/6
Constructor's Booklet 2/-
3 ohm O.P. Trans. O.P.T.1 10/6

NEW MULLARD TRANSISTORS
OC71 6/-, OC72 7/6, OC8D 7/6, OC8I 7/6, OC44 8/-, OC45 8/-, OC71 10/6, AF17 9/6.
Sub Miniature Condensers, 0.1 mfd., 30V, 1/3, 2, 4, 5, 6, 18, 25, 30, 50, 100mFd. 15 volt, 2/6 ea. Transistor Holders, 1/3.
SINCLAIR "SLIMLINE" RADIO
Earphone, ferrite aerial, 9 x 1 1/2 in. Kit 49/6. No aerial required.
SINCLAIR MICRO-4 Kit, 59/6.

Transistor 4 Channel Mixer with 4 separate input-output controls 59/6.
PM9 Mains Unit 9 volt for Transistor Radios, Same size as P.P.9.
Also Miniature P.P.3 model, 19/6.

ADAstra 3-J AMPLIFIER 3 WATTS



Price £5.9.6 Details S.A.E.

A.C. 200-250v. Valves ECL86 and E280. 3 ohms output. Controls: bass, treble and volume. Separate front panel with 6 lux Finish. Chassis 6in. x 5in. x 3in. "Performs agreeably well" (The Gramophone)

BUILD YOUR PLAYER FROM £8.19.6 AND SAVE POUNDS!!



4-Speed Autochanger or Single Player Brand New 2-tone de luxe Cabinets 17x15x8 1/2in. Strong handle. Used by Famous Maker for 20 gns. models. Cut out motor board 14 x 13in. baffle with high flux loudspeaker, 3 watt valve amplifier built on metal chassis. Quality 3 ohm output, low hum level circuit. Volume and Tone controls. All items fit together perfectly. Special instructions enable assembly in 30 minutes, only 5 wires to join 12-month written guarantee. Available separately or package deals as below.

AUTOCHARGE KITS COMPLETE (as above)

B.S.R. Monarch	£10.19.6 P.P. 5/6
Garrard Autolinn	£11.19.6 P.P. 5/6
SINGLE PLAYER KITS, Complete (as above)	
B.S.R. Junior	£8.19.6 P.P. 5/6
Garrard SRP10	£10.19.6 P.P. 5/6

OR SEPARATELY
Cabinet with board 14 x 13in. cut out to your choice... £2.9.6 P.P. 3/6
Amplifier with speaker... £3.17.6 P.P. 2/6

AUTOCHARGERS
B.S.R. UA25 Superlinn... £8.19.6 P.P. 4/6
Garrard Autolinn... £8.17.6 P.P. 4/6

SINGLE PLAYERS
Garrard SRP10... £5.5.0 P.P. 4/6
B.S.R. auto stop/start... £4.15.0 P.P. 4/6
B.S.R. Junior... £3.7.6 P.P. 3/6

TRANSCRIPTION UNITS

Garrard 4HF	£15.15.0 P.P. 5/-
Philips AG1018	£12.5.0 P.P. 3/-
Garrard AT6	£13.10.0 P.P. 3/-
Garrard AT5	£13.10.0 P.P. 3/-

BARGAIN XTAL PICK-UP ARM
Complete with ACOS LP-78 Turnover Head, 20/-

Replacement Sapphire 5 1/2 in. diamond 15/- Mono ACOS Xtal 15/-; Stereo from 25/-

BARGAIN SINGLE PLAYER KIT 200/250v. A.C. £5.15.0 (less cabinet) Post 3/-

With 2-star Amplifier; 3 watt; 2 valves, UCL82, UY85. High-tux 6in. speaker; 4-speed B.S.R. Turntable 16, 33, 45, 78 r.p.m.; Crystal Pick-up for LP/STD. Records, 7in., 10in., 12in. Cabinet Mounting Boards 12 1/2 x 9in.

ARDENTE TRANSISTOR TRANSFORMERS
D8035, 7.3 C.T. Push-pull to 3 ohms output 11/-
D8034, 1.75:1, C.T. Push-pull Driver 11/-
D8038, 11.5:1 Output to 3 ohms, etc. 11/-
D239, 4.5:1 Driver, 1in. x 1in. x 1in. 11/6
D240, 8.5:1 Driver, 1in. x 1in. x 1in. 11/6
ARDENTE TRANSISTOR VOLUME CONTROLS
VC1545, 5K with switch dia. 9in. 5/3
SUB-MIN. EARPIECE XTAL or magnetic 7/6
SUB-MIN. JACK AND FLUG 2.5 or 3.5 mm. 3/6 p/b

MINIATURE PANEL METERS
Size 1in. sq. Precision jewelled bearings, 2% accuracy, silvered dials, black numerals and line pointers, zero adjustment screw on front of meter.
1mA .. 27/6 50µA .. 39/6
5mA .. 27/6 500µA .. 32/6
300V .. 27/6 "S" Meter .. 35/-

MOVING COIL MULTIMETER TK 30a
C-100v. A.C./D.C., ohms 0-100k, etc. 0-150 mA pocket size with 2in. scale, 49/6.

CRYSTAL MIKE INSERTS, 6/6
High output, Size 1 1/2in. dia. 1in. 8/6
ACOS MIC insert 1 1/2in. dia. x 1in. 8/6
ACOS 351 DELUXE STICK MIKE 35/-
TSL QUALITY STICK MIKE .. 25/-
TELEPHONE TAP MIKE .. 10/6
GUITAR XTAL MIKE .. 15/6
PROFESSIONAL MAGNETIC GUITAR MIKE with Volume and Tone Controls .. 59/6
MOVING COIL MIKE, high or low impedance, 90/- FLOOR STAND, 57/-

COMPONENT SHOP SPECIALISTS

337 WHITEHORSE ROAD WEST CROYDON

Telephone: THO 1665

Exports welcome. Send remittance, and extra postage, no C.O.D.


Buses 133 or 68 pass door. S.R. Station, Selhurst



Stentorian

MODEL H.F. 1016 'MAJOR'

This unit makes use of the high flux density available in the magnet system of the previous H.F.1016 unit. A curved diaphragm is used with a rigid centre section coupled to the voice coil. The rigid coupling and the design of the cone termination give a balanced response over the whole audio range. The unit is specially suitable for use in the smaller type of enclosure having a volume of approximately 1½ cubic feet.

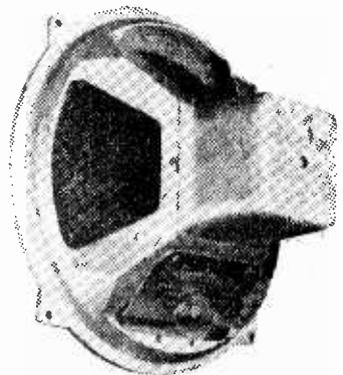

Type	Flux Density	Price	Type	Flux Density	Price
8" H.F.816*	16,000 gauss	£6.6.0	T.816	16,000 gauss	£5.19.3
8" H.F.812*	12,000 gauss	£3.16.6	T.12 tweeter	16,000 gauss	£13.17.9
8" H.F.810	10,000 gauss	£2.17.0	T.10 tweeter	14,000 gauss	£4.12.9
6" H.F.610	10,000 gauss	£2.7.3 Steel £2.9.3 diecast	T.359 tweeter	9,000 gauss	£1.12.3

*These two speakers incorporate a universal impedance speech coil.

Specification:

Chassis—die cast aluminium
Cone—graded pulp cambric surround; Cone dia.—10 ins.,
Pole dia.—1 in.; Flux density—16,000 gauss; Total flux—64,000 maxwells; Impedance—15 ohms.


Price: £9.8.6 (inc. tax)

WHITELEY ELECTRICAL RADIO CO. LTD. MANSFIELD, NOTTS.

Telephone: MANSFIELD 1762-5

London Office: 109 Kingsway, W.C.2
WA3

BUY AND BUILD STAGE BY STAGE

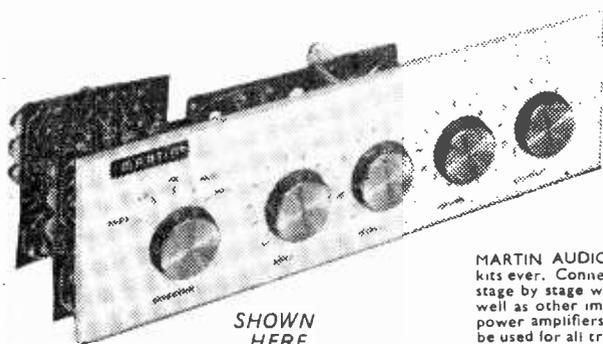

SHOWN
HERE

5-stage selector. Tone Control and Pre-amp Stages. In Stereo complete with attractive escutcheon. This with two amplifiers and power supply comes to well under £30.

FROM A PRE-AMPLIFIER TO A 20 WATT INTEGRATED HI-FI STEREO ASSEMBLY

- ★ FULLY TRANSISTORISED PRE-FABRICATED ADD-ON UNITS.
- ★ PROFESSIONAL STANDARDS OF PERFORMANCE AND APPEARANCE.

MARTIN AUDIOKITS are the most efficient and imaginatively designed kits ever. Connections are arranged to enable you to expand your assembly stage by stage with ease. The range includes a unique 3-channel mixer as well as other important pre-amplifier stages, and you can choose 10 watt power amplifiers with either 3 or 15 ohms output. Martin equipment can be used for all true hi-fi requirements. Power pack Units are also available. We shall be pleased to send you the latest leaflet.

A NEW
F.M. TUNER

An F.M. Tuner will shortly be ready to add to your Audiokit assembly or existing audio equipment. Send coupon for details now.



MARTIN ELECTRONICS LTD.
154/5 High St., Brentford, Middlesex. Phone 15Leworth 1161/2

MARTIN ELECTRONICS, 154 HIGH ST., BRENTFORD, MIDDLESEX.
Details of all MARTIN AUDIOKITS please, including FM Tuner.

NAME

ADDRESS

BLOCK LETTERS

F.W.2

Practical Wireless

Vol. XL No. 696 FEBRUARY, 1965

Editorial and Advertisement
Offices:

PRACTICAL WIRELESS

George Newnes Ltd., Tower House
Southampton Street, W.C.2

© George Newnes Ltd., 1965

Phone: Temple Bar 4363

Telegrams: Newnes, Rand, London

SUBSCRIPTION RATES

including postage for one year

To any part of the world £1.9.0

Contents

Editorial	937
Round the World of Wireless	938
Building a Transistor Solo Organ	940
Cabinet and Chassis Tech- niques	946
On the Short Waves	952
Books Reviewed	954
Understanding Semiconduc- tors	955
Transistor Receiver Servicing Step-by-Step	960
Preselector and B.F.O. Unit Walkie/Talkies	964
Preparing for the R.A.E.	970
Hints for Improved F.M.	984
Improved Communications through the Ground	985
Practically Wireless	986
Trade News	989
S.W.R. Indicator	993
Club News	998
Letters to the Editor	1001

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Owing to the rapid progress in the designs of wireless apparatus and to our efforts to keep readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

FELLOWSHIP OF AMATEUR RADIO

ONCE again, as we enter another brave New Year, the Annual P.W. Film Show is upon us. Now very firmly established as part of the P.W. calendar, it continues to attract "full houses" year after year. There are, of course, a number of obvious reasons why this event is so popular and you can be sure that the social aspect has some bearing on its success.

Which leads us to ponder on the part that social contacts have in this hobby of ours. Amateur radio enthusiasts are naturally friendly and sociable and there is no doubt that by its very nature the hobby stimulates this frame of mind, while at the same time depending on it for success.

Other hobbies, we agree, draw their adherents together by the bond of a common interest, yet surely in amateur radio there is more to it than that? The familiar clichés about the Ham Spirit and World Friendship Through Radio may sound trite or naive to the sceptical but there undoubtedly exists an atmosphere of mutual co-operation and camaraderie in the amateur radio movement which is perhaps unrivalled.

One of the firm foundations on which this is built is the great network of local radio clubs—local RSGB groups, clubs affiliated to the RSGB and other societies, those with no particular ties, works radio clubs, school societies, etc. They all present the opportunity to mix with fellow enthusiasts in practically all walks of life, to participate in club activities such as contests, constructional programmes, discussions.

Those who stay with amateur radio (and most do) cannot fail to absorb the spirit which prevails. Those who were glad to receive a helping hand when they were learning the ropes, in turn encourage and advise yet newer recruits.

Visiting a strange town, or having moved home, one can be sure of a welcome at the local club or at the homes of local enthusiasts. A good deal of visiting takes place between amateurs of different countries, including exchange holidays. There are organisations, run by amateurs, to help the less fortunate who are bedridden or disabled. There are schemes, sometimes by groups or even by individuals, to repair radio sets for old age pensioners.

Even the "lone wolf" is never so isolated as might be expected. In the first place he has the choice of a number of lively periodicals to keep him in touch and keep the spark of interest kindled. Many have pen friends or swap tapes. Many more are members of specialised short wave societies, who issue news sheets and organise services—mostly on a non-profit basis.

Those with short wave sets can keep in touch with the whole world. And those who acquire a transmitting licence can not only hear the world but talk to it as well (when the bands are open!).

Yes, the "ham spirit" is a real thing. Whether it really contributes to world peace and fellowship in a materially effective way is perhaps open to dispute. But it certainly does more to bring mutual tolerance and understanding than many activities on a higher level!

And we can be sure that the average amateur radio enthusiast will continue instinctively to promote goodwill in his own quiet way, not as a duty or an obligation but simply because that's the way he is.

Our next issue dated March will be published on February 4th



of WIRELESS

**NEWS AT HOME
AND ABROAD**

New Semiconductor Light Source

SOMETHING new in light sources has recently been placed on the market by Ferranti Ltd. The new device is based on radiative recombination at a p-n junction, and subsequently has been termed

a crystal lamp. In fact it is a "semiconductor light" which in operation acts as a forward biased gallium phosphide diode being suitably doped to produce electroluminescent radiation of 7,000 anstroms (red).

Its physical appearance is of a cylindrical encapsulation of transparent plastic with two wire leads emerging from one end (see accompanying illustration).

Ferranti claim many potential applications for the lamp, in industry generally but particularly in instrument and indicator applications where its small size—typically 0.03in. x 0.04in.—and low operating currents, are particularly advantageous. An obvious environment is transistorised equipment in which the voltage and current levels are suited to its use as, for example, a simple on/off indicating device.

P.W. Gift Puts School on the Air


IN response to an appeal for help in choosing a short wave radio set from the headmaster of Pilgrims School for asthmatic boys at Seaford, the Managing Editor of PRACTICAL WIRELESS, Mr. A. T. Collins, and the Assistant Editor, Mr. L. E. Howes, recently made the trip to Seaford to visit the school on behalf of the magazine. With them however, went a new Lafayette communications receiver which, it was decided, would prove of more use to the boys in setting up a short wave receiving station than mere advice.

The headmaster Mr. R. Brooks, had written to PRACTICAL WIRELESS as he felt a set which would receive amateur transmissions would be helpful to his 58 pupils. So early in October, Mr. Collins made the presentation of the receiver to the school and accompanied it by a set of books on basic radio.

Now local radio enthusiasts have volunteered to help in setting up the station so that the boys of Pilgrim School can begin their short-wave listening hobby.



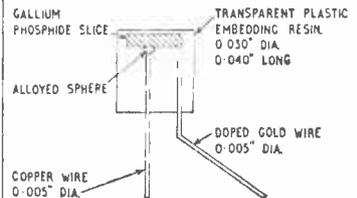Boys of Seaford's Pilgrims School surrounding the Lafayette receiver donated by "Practical Wireless".




This illustration makes clear the construction of Ferranti's new crystal lamp—a semiconductor light source. The average brightness of this unique lamp is 10-40ft. lamberts and it remains visible under an illumination of 20ft. candles.

NEW NATO AERIAL IS EUROPE'S LARGEST


THE largest aerial system in Europe has recently been completed at Anthorn, near Carlisle. The aerial has been erected for the North Atlantic Treaty Organisation's Anthorn v.l.f. radio station and consists of 13 masts, arranged as a "six-pointed star" with a centre point, supporting a network of diamond-shaped panels forming the aerial (see illustration below).

The main contractor for the station was Continental Electronics Systems Inc. of Dallas, Texas, working to the requirements of the British Post Office, with British Insulated Callender's Construction Company Limited undertaking the design, supply and erection of the masts.

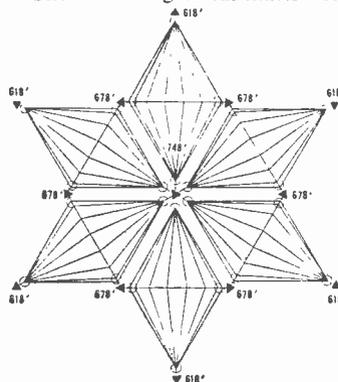The outer ring of six masts—each 618ft. tall—is 2,148ft. in radius, with the inner ring of 678ft. tall masts having a radius of 1,277ft. The central mast from which the aerial panels radiate, has a height of 748ft.



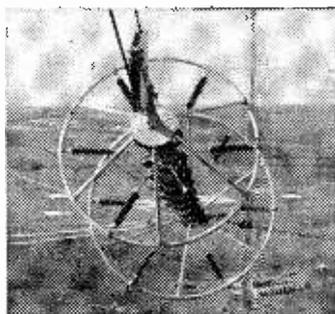A further impression of the immense size of the system may be gained by considering the specifications for the station earthing system. This is virtually a copper mat covering the whole of the site, 9 to 12in. below ground. Lines of 8s.w.g. soft copper wire radiate from the centre mast with 2° of arc between each, requiring in all, a total of 75 miles of copper wire. The construction of the aerial



Looking down on the Anthorn v.l.f. station from one of the outer masts, showing one of the massive insulators in the foreground.

panels called for some 20 miles of steel-cored aluminium conductor, which were cut and pre-stressed on the site before their assembly. At each corner of each panel, 40ft. long insulators support the aerial. These insulators are fitted with two corona rings, one 15ft. in diameter, the other 12ft. in diameter.

The Radio Show Goes International

FOR the first time ever, this year's Radio Show at Earls Court, London, will be international in scope. Ever since the days of Radiolympia, it has always been a national show with a British-made-only policy. Now it is hoped that exhibitors from abroad will help boost attendances.

The promotion and organisation of the annual exhibition has been taken over this year by Industrial and Trade Fairs Limited from the previous organisers, the British Radio Equipment Manufacturers' Association.

The dates of the 1965 Radio Shows have already been announced as 25th August to 4th September.

100kW Transmitters for Malaysia

THE Gates Radio Company, a subsidiary of the Harris-Intertype Corporation of the U.S.A., has recently completed a Government of Malaysia contract for three high powered 100kW short wave broadcast transmitters. The transmitters will be the most powerful in Malaysia, and will be used by Radio Malaysia for long-range international broadcasting to inaugurate its new "Foreign Broadcast Service" to neighbouring South-East Asian countries.

These transmitters are of a new air-cooled design, employing high level plate modulation and utilising conservatively rated components especially chosen for reliable service in areas of extreme temperature and humidity; conditions such as may be expected in Malaysia.

RENOVATIONS AT RUGBY


THE 16kc/s world-wide transmitter at Rugby (callsign G.B.R.) is to be renovated.

This was announced recently by the G.P.O. and now another announcement from the English Electric Valve Company Limited has confirmed that its output stage will be re-equipped with EEV BY1144 triodes. This modification means the replacement of the 54 water-cooled triodes, type CV1600 previously installed in three banks of 18, where two banks provided the 210kW output and the third remained on standby. All these will be replaced by only three of the English Electric valves, these being vapour-cooled power triode types, two of which will provide double the original output and leave the third on standby.

HEREFORD'S NEW RELAY STATION

THE sound transmitters at the BBC's v.h.f. sound and television relay station at Hereford were brought into service during November last year. Transmissions of the Midland Home Service is on 94.1Mc/s, the Light Programme on 89.7Mc/s, and the Third Programme/Network Three on 91.9Mc/s. Horizontal polarisation is used.

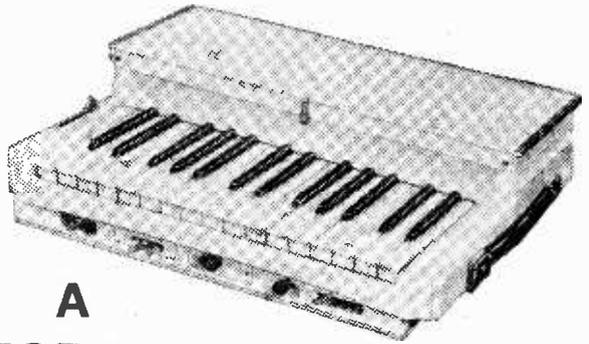The new station will improve v.h.f./f.m. reception for the 40,000 people in the City of Hereford and its environs.



BUILDING A TRANSISTOR SOLO ORGAN

by
G. W. Hardy

AFTER many experiments with various types of audio oscillator, the author decided to build a musical instrument, using the well-known multivibrator circuit. This will be familiar to many readers, as it is frequently used for a signal probe in radio fault finding.

In the instrument about to be described, instead of the usual thin reedy tone, we have a really musical output which can be fed into any amplifier and will provide tones resembling the oboe, horn and cello.

Furthermore the tones can be varied with slow, medium and French or continental vibrato: (the latter resembling a French accordion).

Percussion is also provided with (1) fast decay; (2) slow decay; thus simulating plucked strings of banjo, guitar, etc.

Note Generator Circuit

The circuit (Fig. 1b) will now be explained. This is divided into two sections, as recommended in actual construction. Section 2 is the musical note generator—a straightforward multivibrator except that instead of one, we have a series of resistances in the base of Tr4.

R11 is a limiting resistor to protect this transistor. VR2 is a variable resistor used for setting up the tuning to correct pitch. For convenience it is brought out handy to the keyboard.

Playing the highest note on the keyboard connects VR2 to the negative line and sounds the highest note. The remainder of the resistors in the series are tapped off to the key contacts; and when the bottom note on the keyboard is played, the whole series will be in circuit and sound the lowest note.

The range of the author's instrument, as described here, is 29 notes from C in the bass to E in the treble (see Fig. 2).

It will be appreciated from the foregoing why chords cannot be played, and if more than one key is played together, only the uppermost note will sound. This is a very practical advantage in a monophonic organ such as this.

The series tuning has some disadvantage and it

is not desirable to extend the range for any single oscillator much beyond the two octaves.

Vibrato Circuit

The base of Tr3 receives the low frequency impulses, generated by the oscillator (Section 1, Fig. 1), which provides vibrato. The $1M\Omega$ variable resistor VR1 is a preset by which adjustment can be made to obtain a slow vibrato.

One turn of the vibrato switch places R3 in parallel with VR1 and we obtain a medium speed; one more turn of the switch and we have a fast speed. It is possible that these two resistors may need some slight alteration of values owing to difference in tolerances; however, it would be easy to experiment here as they are soldered directly on to the switch. Obviously slow speed must be correct before alterations are made.

The vibrato switch S1 (Fig. 1c) is mounted under the keyboard for easy adjustment whilst playing. Another switch S2, cuts out vibrato when not in use.

Buffer Stage Circuit

The output of the note generator is taken from base of Tr3 via the $0.01\mu F$ mica coupling capacitor C6. This gives a more useful waveform for our purpose than if taken from the collector of Tr4. A mica capacitor is preferred here for stability.

This output is fed into a buffer stage (Fig. 3a), otherwise changing over of tone circuits would affect the pitch.

Tone Circuit

This is shown in Fig. 3a and follows usual practice except that instead of using three separate stops it was decided to use another 3-way switch (S3).

This way the tones cannot be added as in usual organ practice, but experiments proved that there was nothing to be gained by so doing.

Pre-amplifier and Percussion

The final stage is a pre-amplifier which, with the aid of one extra contact per key, has the

additional function of providing percussion. This is a trick circuit and with the key action devised by the author works very effectively.

In normal playing L-M (Fig. 3a) is shorted (mid-position S4A—see Fig. 3a). The percussion key contacts, although still working, are now inoperative. Only the key primary contacts (Fig. 1b) are now effective, being normally open and contacting the -3V (No. 1) negative strip when keys are pressed down in playing.

For percussion, short circuit on I-M is removed and replaced by a 1-2 μ F capacitor. Current is now diverted via the secondary key contacts (Fig. 3a) which are normally closed, at the same time

It would seem a good idea to switch in a further stage of amplification when using percussion. However, as this would lead to further complications, it was decided to do the reverse and cut down volume on normal playing—after all we shall have plenty of amplification to spare in the main amplifier which follows.

When changing over from percussion to normal, switch S4B will close and bring R30 in parallel with the lower part of the expression control. This will reduce the volume according to the value of R30 which, in the writer's case, is 20k Ω . This works quite well, once adjusted to a level volume.

VR3 (Fig. 3a) is the expression (volume) control,

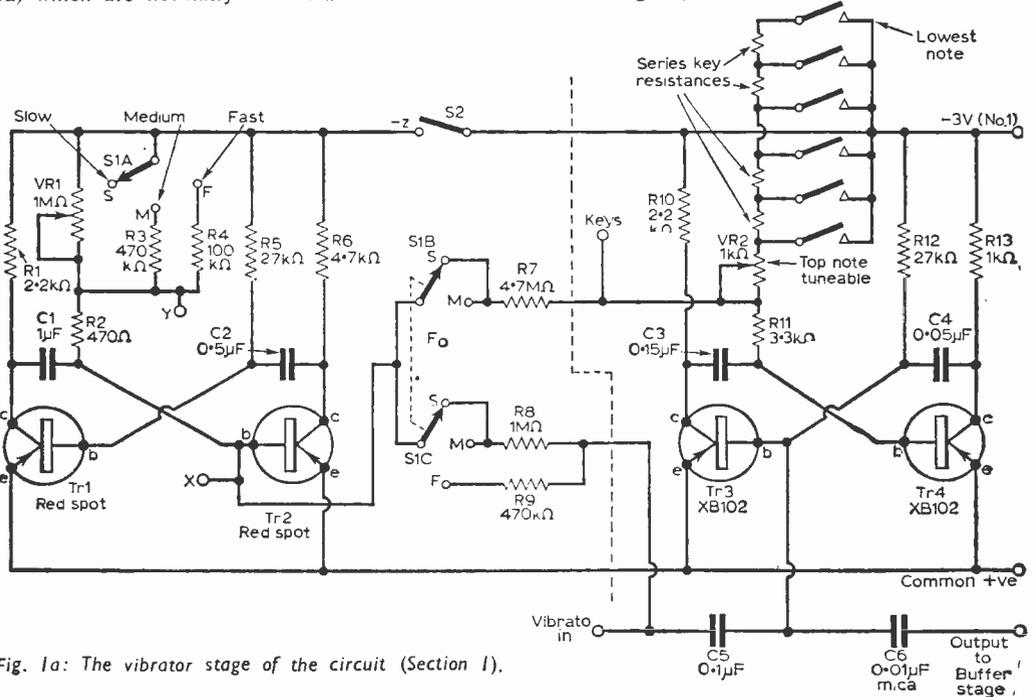


Fig. 1a: The vibrator stage of the circuit (Section 1).

Fig. 1b: The note generator stage (Section 2).

charging up the selected capacitor.

When a key is now depressed, the primary contact is made and sounds the note selected, immediately afterwards the secondary contact is broken and cuts off the sound, which however fades away or decays slowly or fast according to the value of the capacitor now spanning L-M.

When using this device in playing, it will be necessary to use "clean" fingering (staccato) as in fact it will seem natural to do, with the percussive sound produced.

Conversely, with percussion switched off and playing normally, a lingering (legato) touch is desirable but playing technique will be gone into more fully later in this article.

It will be noticed that a 47k Ω resistor R28 is in series with the percussion contacts. This eliminates unpleasant contact noises when playing. Unfortunately it also reduces the volume, so that there is too much contrast when percussion is switched off.

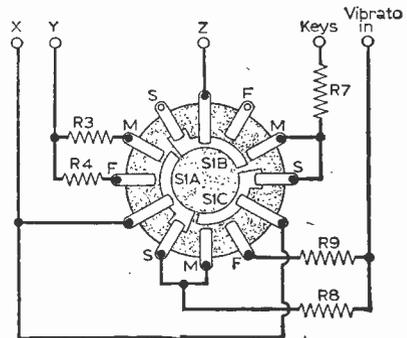


Fig. 1c: Details of the S1 switch connections.

Fig. 2: The tonic sol-fa range of the organ.



in the writer's case controlled by a foot pedal to be described later from which a two yard length of screened cable can be plugged into a socket fitted to the organ case.

Connecting to Main Amplifier

Another screened socket of a different type—to avoid accidental interchange—will receive the screened lead from the constructor's amplifier.

This can be a transistor amplifier, in which case the coupling capacitor C17 can be increased in value to 10μF.

It is not advisable to use an amplifier with live chassis, but if one is used a high voltage 0.005—0.01μF capacitor should be inserted between the organ and chassis. This will probably give rise to some hum, which however slight, will mar the tone of the organ.

Should there be a volume control on the amplifier, this should be set at full volume when

the pedal is fully depressed and then left at that setting. A tone control, if fitted, can be adjusted to one's liking.

Design of the Case

The writer's instrument is built around a discarded accordion keyboard of 29 notes. The note generator is designed to sound the notes from C in the bass to F in the treble (Fig. 2).

The case measures 1ft. by 1ft. 2in. and 4½in. deep. A leather strap handle is fitted at one end. The amplifier which contains an 8in. speaker is of similar size also with a handle, so that the outfit is quite portable.

All organ controls are brought out to the front, just below the keys; and each end of the case has a length of ¼in. x ¼in. aluminium angle, so fitted that two flanges can slide upon two runners fitted under the treble of a piano.

The expression control being pedal operated leaves the left hand free for accompanying on the piano. With the cable connected to the amplifier, the outfit is ready for use.

Alternatively the instrument could be designed to play as an accordion. In this case, the controls (including expression) could be arranged for the left hand and then only needing one screened cable to the amplifier.

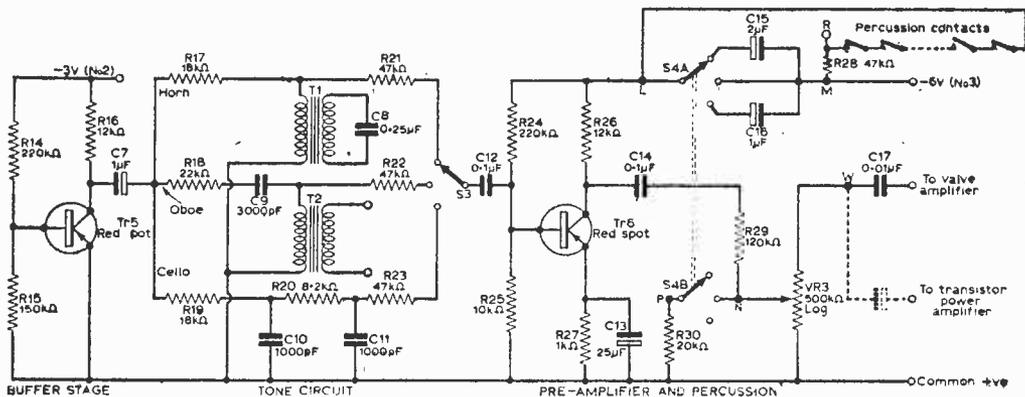


Fig. 3a: The buffer stage, tone and preamplifier and percussion sections of the circuit.

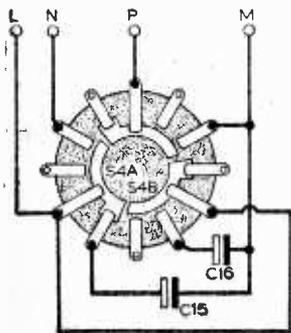


Fig. 3b: Wiring details of the percussion on/off switch, S4.

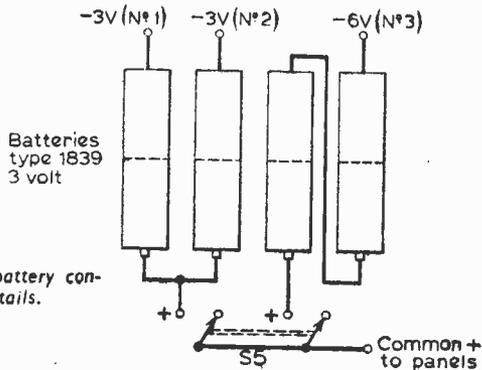


Fig. 4: S5 and battery connection details.

Also it could be designed as a solo (upper) manual, to use with a single manual electronic or reed organ.

Power Supplies

Battery No. 1 (3V) supplies power for vibrato and note generator. Battery No. 2 (3V) supplies the buffer stage. Percussion and pre-amplifier stage is powered by two similar 3V batteries connected in series to give 6V.

All positives are common and taken to a two-pole on/off switch S5 and wired as shown in Fig. 4. Although they are shown as being together, it is preferred to secure each battery with a clip near each panel.

A two-pole switch is necessary owing to the 3V difference in potential between the batteries. Type No. 1839 3V batteries have been used throughout, and as they last at least a year, all connections are soldered.

It is recommended that the two cells in each battery are pushed out of the case and the negative of one cell connected to the positive of the other with a short length of thin stranded flex and then reinserted into the case.

Remember that the cell case is negative, especially before finally connecting to their respective panel tags, otherwise damage will result to the transistors.

Wiring Note Generator (Fig. 5)

It is advisable to start by wiring up the note generator, for which a $\frac{1}{8}$ in. paxolin panel about 3in. x 4in. is required.

The components are mounted on this panel, the wire ends being cleaned and bent over at right angles and pushed through holes in the panel for wiring up on the underside.

Thin insulated connecting wire should be used and where a junction has to be made, if a piece of systoflex of a sliding fit has been previously slipped over the connecting wire covering, this can be pushed down over the junction after it has been soldered. Leave transistor leads full length, even if they have to be long routed.

All wires should be cleaned and tinned before soldering. A heat shunt should be applied to the wire between the iron and transistor, as well as wires to small electrolytics.

A common dodge is to use a pair of tapered flat-nose pliers and stretch a rubber elastic-band across the handle, thus leaving both hands free for soldering.

"Red spot" transistors have been used throughout with the exception of this note generator, for which we desire good stability in order that musical pitch will remain reasonably constant with varying temperature. After experiments it was decided to use the Mazda XB102 transistors which were found to be very stable.

Before drilling the panels it is a good idea to lay out the components on a piece of cardboard of same size as the panel, piercing holes where required and trying the layout, which should include space for five soldering tags.

When satisfactory, the card can be used to mark out the holes on the paxolin for subsequent drilling. Five soldering tags should be fitted at one side, convenient for external connecting and with a sharp pointed awl, the following legend

COMPONENTS LIST

Resistors:

R1	2.2kΩ	R16	12kΩ
R2	470Ω	R17	18kΩ
R3	470kΩ*	R18	22kΩ
R4	100kΩ*	R19	18kΩ
R5	27kΩ	R20	8.2kΩ
R6	4.7kΩ	R21	47kΩ*
R7	4.7MΩ	R22	47kΩ*
R8	1MΩ	R23	47kΩ*
R9	470kΩ	R24	220kΩ
R10	2.2kΩ	R25	10kΩ
R11	3.3kΩ*	R26	12kΩ
R12	27kΩ	R27	1kΩ
R13	1kΩ	R28	47kΩ
R14	220kΩ	R29	120kΩ
R15	150kΩ	R30	20kΩ*

All 10% $\frac{1}{2}$ W carbon.

* May need slightly different value.

Tuning Resistors:

Recommended list of preferred values, all $\frac{1}{2}$ W.

1 x 680Ω	2 x 4.3kΩ	} For parallel connecting to obtain half values
2 x 820Ω	2 x 4.7kΩ	
5 x 1kΩ	2 x 5.6kΩ	
4 x 1.2kΩ	2 x 6.8kΩ	
4 x 1.5kΩ		
4 x 1.8kΩ		
4 x 2.2kΩ		} For single and parallel connecting
4 x 2.7kΩ		
4 x 3.3kΩ		

Capacitors:

C1	1μF paper
C2	0.5μF
C3	0.05μF
	0.10μF
	0.05μF
C4	0.05μF
C5	0.1μF 150V
C6	0.01μF mica
C7	1μF electrolytic 12V
C8	0.25μF paper
C9	3,000pF
C10	1,000pF
C11	1,000pF
C12	0.1μF 150V
C13	25μF electrolytic 12V
C14	0.1μF 150V
C15	2μF electrolytic 12V*
C16	1μF electrolytic 12V*
C17	0.01μF 350V

* Subject to experiment—see text.

Transformers:

T1, T2 See text

Potentiometers:

VR1	1MΩ skeleton type pre-set	VR2	1kΩ w.w.
		VR3	500kΩ log.

Switches:

S1	3-pole, 3-way wafer	S4	3-pole, 3-way
S2	S.P. on/off toggle	S5	2-pole, 2-way on/off push-pull type
S3	S.P. 3-way		

Transistors:

Tr1	Red spot	Tr4	XB102
Tr2	Red spot	Tr5	Red spot
Tr3	XB102	Tr6	Red spot

Sockets:

SK1	Coaxial
SK2	Phono (panel mounting)
SK3	3-pin Continental (panel mounting)

should be scratched on the paxolin adjacent to the appropriate tag: + VIB.IN. O.P. KEYS—No. 1 3V O.P.; being of course for output from that panel.

Care should be taken that the transistors are wired correctly, as layout is reversed upon turning the panel over for wiring; and it is therefore suggested that the letters C B and E are scratched on the underside of the panel against each hole through which these wires will pass from each transistor.

Assuming that all wiring has been checked and found correct, it will now be possible to try out the oscillator by connecting tags + and O.P. to high resistance headphones.

A variable resistor of about $5k\Omega$ should be connected across tags marked keys and — No. 1 3V. Then connect the positive of a 3V battery to the + tag and if a lead is taken from the battery negative, this when touching the — tag should produce a sound which can be varied in pitch by rotating the variable resistor.

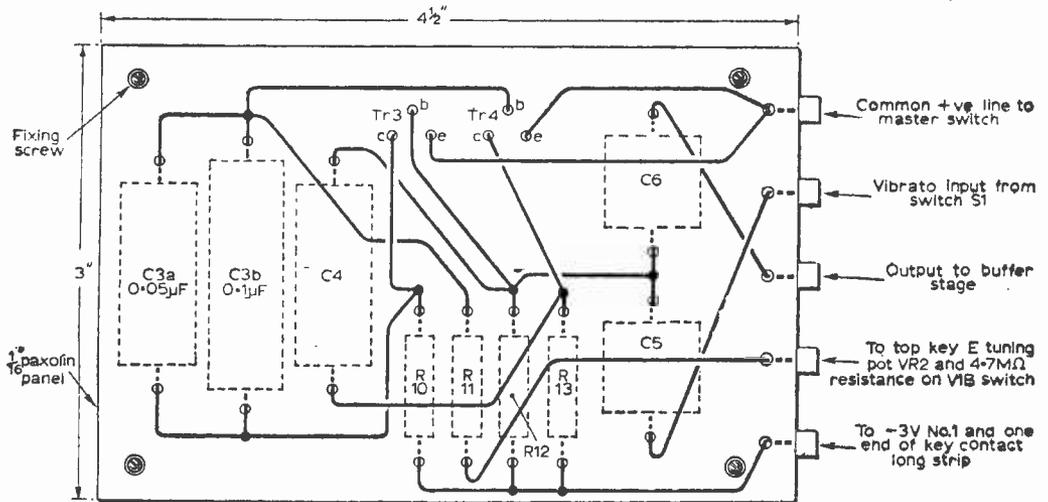


Fig. 5: Wiring and layout of the note generator.

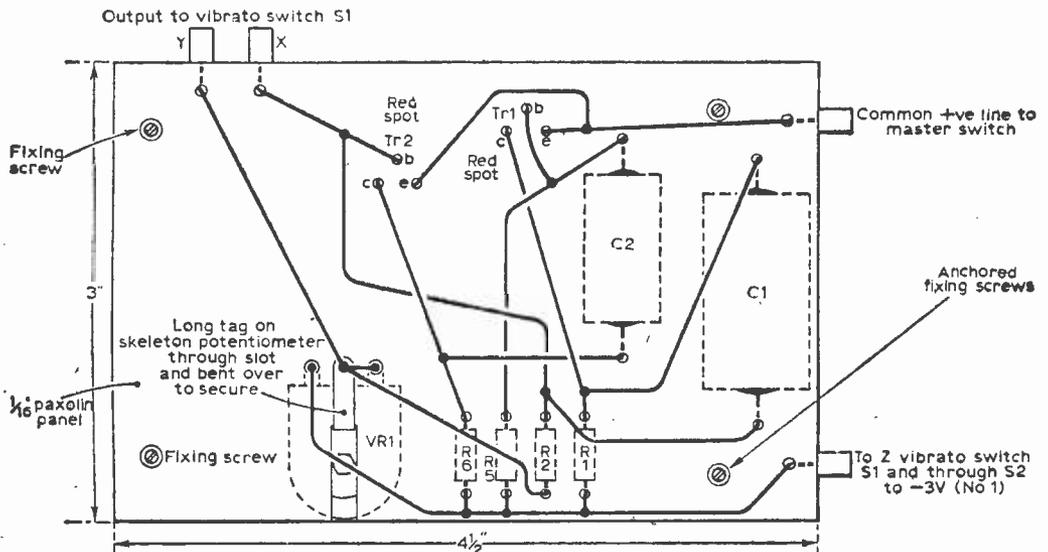


Fig. 6: Vibrator wiring details.

Wiring the Vibrato Oscillator (Fig. 6)

This panel can be of same size and wired up in a similar manner. The $1M\Omega$ potentiometer VR1 is a skeleton type preset and is mounted on the upper side of the panel.

Four soldering tags should be conveniently positioned and bear the legend: + O.P.(Y) O.P.(X) - (Z).

The wiring of the three-way switch is clearly shown in Fig. 1c. As drawn it is in the slow

clicks should now be heard, if not the $1M\Omega$ potentiometer may need adjustment.

If there are still no clicks, set the potentiometer about halfway and place a fixed resistance of about $470k\Omega$ in parallel with same by spanning -Z and Y, again slowly rotating the track arm.

If no clicks are heard, it is possible that one or both transistors are unsuitable and substitution should be tried. When working properly it should be possible to obtain four to five beats per second, without the fixed resistor in parallel.

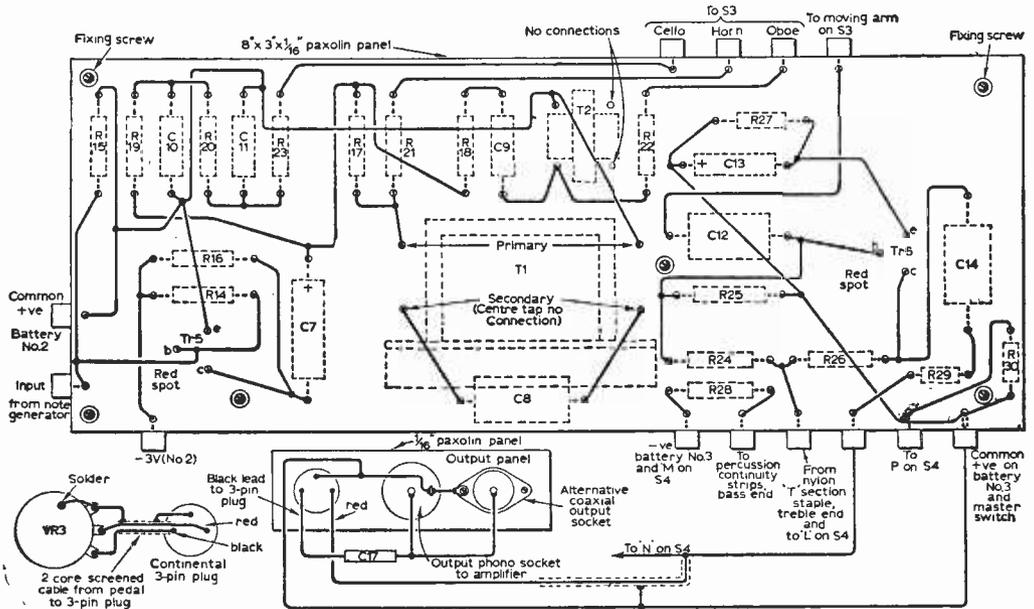


Fig. 7: Layout of components and wiring connections of the buffer stage, tone and preamplifier panel.

position, next is medium and finally fast (French vibrato). The purpose of R7 ($4.7M\Omega$) is to increase the amplitude or depth of slow and medium vibrato.

The layout of the wiring in these panels is not critical, but panel inter-connections should be as short as possible and miniature microphone screened cable has been used as much as anything for its tidiness.

This also applies to connecting up switches to panels, including vibrato negative and on and off switch. This latter is in the negative lead from battery No. 1, a lead from the switch going to - (Z) on vibrato panel.

This panel can now be tested (without the three-way switch) in a similar manner to the note generator, but in this case we connect a $0.1\mu F$ capacitor to tag O.P.(X) the other side of the capacitor to one side of headphones, and the other side of headphones to + tag.

A 3V positive battery is now connected and a lead from the negative of the battery, preferably with a crocodile clip connected to - (Z). Slow

Buffer Stage, Tone Circuit and Pre-amp (Fig. 7)

This is our last panel (Fig. 7) and for a suggested layout see Fig. 7. The soldering tags are arranged to suit the writer's particular layout and may be found suitable by other constructors.

The buffer stage must have a separate battery as shown. T1 is a driver transformer as used in small transistor radios with push-pull output. A capacitor is wired across one winding and the centre tap ignored. T2 is a small transistor type interstage transformer and one winding is left open.

There is scope for experimenting here, with whatever types one has to hand. Switches S3 and S4 are brought out to the front of the instrument under the keyboard.

R21, R22 and R23 could of course have been wired as a single resistor of $47k\Omega$ between switch arm and C12, but this layout was adopted as these three resistors also serve to level off the volume of each separate tone output as may become necessary with other transformers.

NEXT MONTH — THE KEYBOARD AND CABINET

PART ONE

CABINET AND CHASSIS TECHNIQUES

BY F. L. THURSTON

IT is the object of this short series to deal with the "non-electronic" side of the hobby; what can be loosely termed the "Ironmongery" side of it—chassis construction, cabinet making and finishing.

The series is aimed primarily at the novice, but more experienced readers may find much of interest, particularly in such matters as glass fibre cabinet construction, chemical finishing of metals, etc.

Chassis Construction

The most elementary type of chassis is the "breadboard", consisting simply of a slab of wood on which components and controls can be easily mounted when making temporary hook-ups or testing experimental layouts.

Components such as transformers, chokes, tag strips, terminal blocks, etc., are fixed with ordinary wood screws. Valve bases and controls may be mounted on additional strips of wood or metal at right angles to the breadboard. "Bus-bars" may be used for h.t. and negative return lines.

An improvement on the conventional breadboard is to cover the entire upper surface with a single sheet of aluminium or copper foil, glued to the wooden surface with a suitable compound. Such a board provides electrical continuity, for earthing, etc.

These systems should be used *only on temporary lash-ups*, as the boards will be subject to heating and age and will bend or crack after prolonged use, resulting in unstable operation.

For permanent set-ups, excepting for transistor equipment, an aluminium chassis is preferable. A

number of manufacturers produce ready-made chassis of excellent quality and reasonable price. Nevertheless, many readers will prefer to make their own, and the following notes may be of some use.

A very simple method of construction, which involves no bending of metal at all, is shown in Fig. 1. Sheets of aluminium are cut to form the top and sides of the chassis and are bolted together with pieces of angle aluminium along the edges of the sheets. Additional lengths of angle may be used where extra rigidity is needed.

The angle should be between $\frac{1}{4}$ — $\frac{3}{4}$ in. in width for all but the exceptionally large or small chassis, and the aluminium used for the chassis should be 20s.w.g. up to about $2\frac{1}{2}$ x 3 in., 18s.w.g. up to about 9 x 7 in. and 16s.w.g. for sizes larger than this.

The most generally used chassis is the "single sheet" type, and Figs. 2a 2b show two alternative ways to produce the same size chassis. Fig. 2a is probably the more difficult but more effective of the two methods. As well as bending to form the sides it is also necessary to add the four "lips", marked A, B, C and D.

When the chassis is finally formed, these lips must be on the inside of the two shorter side pieces and should be drilled through and bolted or riveted to make the chassis a rigid structure. In Fig. 2b these lips are not used, but separate pieces of angle or other strengthening fixtures take their place to give almost equal rigidity.

Bending

The actual method of bending the metal will depend on the facilities available to the construc-

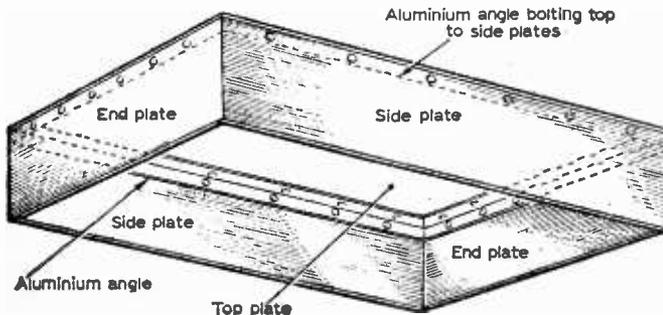


Fig. 1: An underside view of a chassis assembled from flat aluminium plates bolted to aluminium angle. This form of chassis construction involves no bending of metal at all.

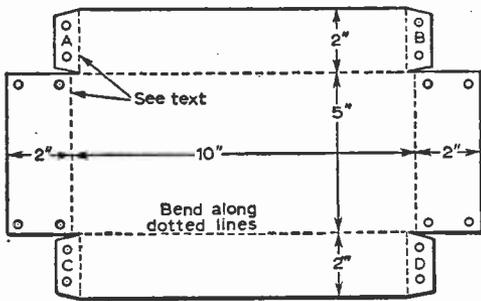


Fig. 2a: With this single-piece chassis all holes are drilled AFTER bending is completed, and the line of bend of lips is set back from main bend—see text.

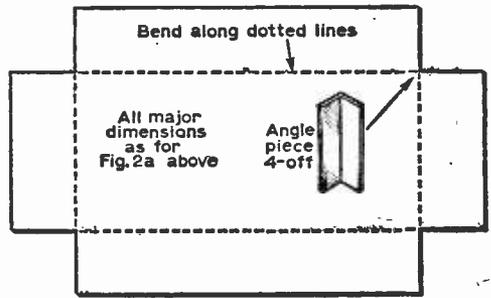


Fig. 2b: With this form of construction, "lips" are replaced by aluminium angle. After bending, the sides of the chassis are secured with the angle pieces.

tor. For those that can afford it, special sheet metal folding machines are available and are a good investment. Those for amateur use range in price from about £6 10s. to £12.

For the average constructor, a good vice may be used as a bending tool. Smooth faced jaws should be used to avoid marking the aluminium unduly when bending it.

First cut the aluminium sheet to size and score with a scribing tool along the proposed lines of bend, on the underside of the sheet. The lines should not be scribed too deeply, or it may be found that when the bending is nearly completed fatigue fractures will occur along them.

If, say, the vice is of the 4in. type the bending procedure for Fig. 2a will be as follows: insert lip A into the vice and ensure that the bending line is flush with the top of the vice jaws along the whole of its length, and tighten the jaws.

Note that this bending line falls behind the bending line for the short side piece by the thickness of the basic material.

Apply pressure and bend the metal over, making sure that the scribed line is on the underside, otherwise the lip will tear away or fracture along the line. A soft mallet can be used to help the bending operation along.

A final sharp corner is obtained by placing a piece of scrap aluminium over the bend area and hammering down on it until the desired result is obtained. Repeat the operation with the remaining three lips.

Next, bend the 5in. sides, and finally the 10in.

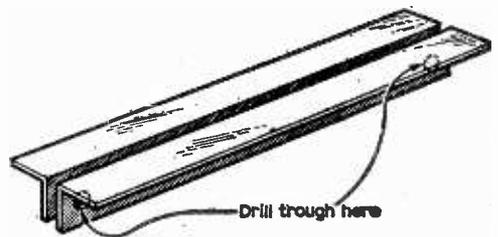



Fig. 3: A simple device for extending the effective length of vice jaws.

sides. When the side to be bent is longer than the vice jaws it should be bent in a number of stages, starting with a small angle of bend at the left and then working along the length of the side until the same angle of bend is obtained throughout, returning to the left again with a greater angle of bend, repeating the procedure until the final sharp angle is obtained.

The effective length of the vice jaws can be extended with the simple gadget shown in Fig. 3. Made from two lengths of angle iron or steel and held parallel by bolts passing through the two guide holes, the gadget can be made even more useful by filing the top faces flush with each other and case hardening the whole assembly.

The device can then be used when sawing or filing a straight edge along aluminium, etc., as well as for marking out and bending.

Fig. 4: Two types of hole-cutting tools for chassis work. Holes of several inches in diameter down to holes less than one inch in diameter can be cut easily in aluminium sheet with both tools.

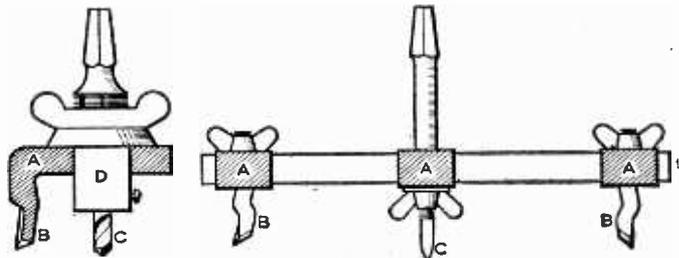

A.....Cutting tool
B.....Cutting edge
C.....Pilot drill
D.....Body slotted to allow movement of 'A'

A.....Carrier
B.....Cutting tool
C.....Pilot drill or point

Holes in Sheet Aluminium

A number of manufacturers produce punches that cut holes of fixed size, ranging from about $\frac{3}{8}$ in. to $2\frac{1}{2}$ in. diameter and ranging in price from a few shillings to a couple of pounds each. Usually of the "screw down" type, with a punch in two parts drawn together by a bolt, a pilot hole must be drilled through the aluminium before the punches can be used.

At least one manufacturer produces a double-ended punch so that one gets, in effect, two punches for the price of one. Punches are available for cutting square as well as round holes.

The advantages of these punches are the ease with which holes can be cut with them and the fact that almost no "cleaning up" is needed with a file afterwards. The major disadvantage is their cost.

Another tool that is available for cutting round holes is shown in Fig. 4. Consisting of a central drill and a bar set at right angles to it, with an adjustable cutting bit on the bar, the device enables

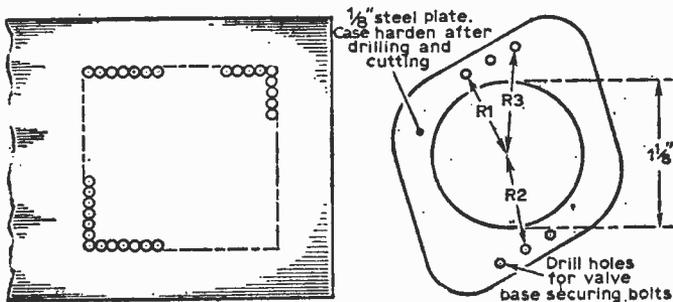


Fig. 5 (left): A simple method of cutting rectangular holes.

Fig. 6 (right): A case-hardened template for cutting $1\frac{1}{4}$ in. valve base holes.

holes ranging in diameter from less than an inch to several inches to be cut with a single tool.

Some of these adjustable cutters are provided with a bar extending on both sides of the drill and have a bit on each extension, resulting in a smoother cutting operation (Fig. 4). Both types are available from most radio and tool stores.

With these tools the holes need to be cleaned up with a file after cutting, but they are an excellent investment and are the only tools that will cut large diameter holes reasonably well.

When drilling holes in aluminium the drill will tend to wander and unless care is taken the final hole will be off-centre. It is therefore advisable to start off with a small pilot drilling to reduce this wander as much as possible, and to cut the hole in a series of progressively larger drillings rather than in one single operation. For a similar reason, power drills must not be used unless they are mounted in a stand.

When cutting holes for valve bases, etc., and punches are not to hand, a carpenter's bit makes an excellent alternative. This tool, like the adjustable hole cutter, is best used mounted in a carpenter's brace.

When cutting rectangular holes in sheet metal the method that most text books recommend is shown in Fig. 5. The size of the required hole is carefully marked out with a scribing tool and a second set of scribe lines are drawn about $\frac{1}{16}$ in. inside of the first set.

A $\frac{1}{16}$ in. drill is then used to drill a complete series of holes along the entire length of the inner lines until the entire strip is cut away and the centre section can be pushed out. The jagged edges of the hole are then carefully filed down to the outer set of scribe lines and the hole is finished off. Note that if a 4 x 4 in. hole is cut by this method a total of 128 small holes must be drilled!

A better method is to first drill a $\frac{1}{16}$ in. hole in each corner after marking out the outer scribe lines, and then simply cut out the hole using a fret saw with a metal cutting blade, or a "Keyhole" or pad saw. The whole centre section can then be removed within a couple of minutes!

The metal cutting blades can be purchased very cheaply from most tool shops and are surprisingly strong in spite of the fact that they are less than $\frac{1}{16}$ in. deep. They could, in fact, be used to cut a hole only $\frac{1}{16}$ in. square if required!

The least expensive method of all for cutting large round holes is to make up a template in about $\frac{1}{16}$ in. sheet steel which is then case hardened. In use the template is bolted down to the chassis and the hole cut out with the fret saw. Fig. 6 shows such a template; made for cutting $1\frac{1}{4}$ in. valve base holes.

Manufacturers of valve bases do not seem to have standardised the radius from the centre hole of the base securing bolts, so provision has been made for three sets of bolts at different radii. A slot could also be used here.

Printed Circuit Techniques


Printed circuit boards consist of a sheet of copper foil bonded to a sheet of Paxolin or similar insulating base, surplus foil being removed by etching. Un-etched boards are available from the larger radio stores, but are fairly expensive.

The experimentally minded constructor can make his own boards by bonding a sheet of copper foil to a suitable base, using a waterproof adhesive such as Durofix, Araldite, etc.

The base should preferably be Paxolin or a similar type of insulation, but less expensive materials, such as 3-ply wood, can be used, providing steps are taken to ensure that they are made non-porous. This can be done with plywood by first thoroughly drying it in an oven at a fairly low temperature over a long period of time and then soaking the assembly in a good quality varnish. The base must have very good insulating properties.

An alternative to copper foil is aluminium foil with an electro-plated copper deposit on it. The plating can be carried out with a minimum of facilities. Bond a sheet of aluminium cooking foil to the base; and, after it has thoroughly dried, clean

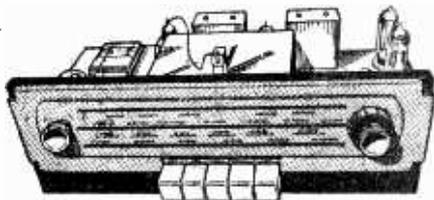BRAND NEW AM/FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)



Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/4 x 4 in. in 2 colours, predominantly gold. 200-260v. A.C. only. Pick-up. Ext. Speaker. Ac. E. and Dipole sockets. Five push buttons—OFF L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone control. 1000-1800 M.; 200-550 M.; 89-88 Mc/s. Valves EZ80 rect.; EC81; EF89, EAC80, EL84, ECC85. 10 x 6 in. ELLIPTICAL SPEAKER 25/- to purchasers of this chassis. **TERMS:** (Chassis) £8.19.0 down and 5 monthly payments of £2.4.0. Cheap Boom Dipole for V.H.F., 12/8. Feeder 6d. per yard. **ALTERNATIVE DESIGN.** L.W. 1000-1800 M.; S.W. (9-15 Mc/s); M.W. 190-475 M.; V.H.F. 87-100 Mc/s.; Gram position. Otherwise similar to above chassis. Price £15.15.0 (car. paid). **TERMS:** £3.10.0 down and 6 monthly payments of £2.4.0. Circuit diagram 2/6.

PUSH-PULL O.P. AMPLIFIER £5.50



(6/- Carr.) Brand new 200-240 A.C. mains Base, treble and vol. controls with valves EZ80, ECC83 and 2-EL84's giving full 8 w. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "drying panel."

LAFAYETTE BRAND TAP

FULLY GUARANTEED AT RECORD LOW PRICES


MYLAR BASE	
7in. Stand. play, 1,200ft.	13/6
7in. Long play, 1,800ft.	21/6
5in. Double play, 1,200ft.	16/6
5 1/2 in. Double play, 1,800ft.	24/6
7in. Double play, 2,400ft.	27/6
3in. Triple play, 450ft. (Plain white boxes).....	13/6
4in. Triple play, 900ft. (Plain white boxes).....	24/6
5in. Triple play, 1,800ft. (Plain white boxes).....	46/6
5 1/2 in. Triple play, 2,400ft. (Plain white boxes).....	60/6
7in. Triple play, 3,600ft. (Unboxed).....	82/6

ACETATE BASE	
5in. Stand. play, 600ft.	8/10
7in. Stand. play, 1,200ft.	12/3
5in. Long play, 900ft.	11/3
5in. Long play, 1,200ft.	12/3
7in. Long play, 1,800ft.	16/8

MESSAGE TAPES	
3in. Stand. play, 150ft.	3/6
3in. Long play, 225ft.	5/6
3in. Double play, 300ft.	3/3
3in. Triple play, 450ft.	15/6


Postage 1/- per reel (4 or more post free)

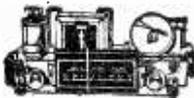SELF-POWERED VHF TUNER CHASSIS. Covering 88-95 Mc/s. Mullard permeability tuner. Dims. 8 x 6 x 6 in. high. Valves ECC85 and 2-EF89's plus 2 diodes with EZ80 rectifier. Mains transformer. Fully wired and tested **ONLY £8.17.8** (car. paid). Boom dipole 12/8. Feeder 6d. per yard.



6-TRANSISTOR PORTABLE — Fully Built

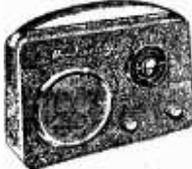The "SCALA" for only £7.10.6 car. paid. 8 1/2 x 2 x 5 1/2 in. high. Choice of colours. Resine. M.W. and L.W. Ferrite aerial Battery 3/9 extra. Printed circuit. Nicely styled. A professional job 3 1/2 in. speaker. Fully tunable M.W. and L.W. Superhet circuit.



BATTERY ELIMINATOR

For 4 Low Consumption Valves (65 range) 90v. 15mA and 1.4v. 125mA 42/8 (4/-). 200-250v. A.C. Also for 200mA. 1.4v. and 90v. 15mA at same price. Two separate units to replace existing batteries. 4 x 2 1/2 x 2 1/2 in. and 3 x 2 1/2 x 1 1/2 in.


ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH. Delivery by return. **TERMS** available on items over £5. Send 6d. (stamps will do) for 20 page illustrated catalogue. C.O.D. 2/6 extra. **ALL ITEMS GUARANTEED 12 MONTHS. VALVES 8 MONTHS.** Regret overseas orders cannot be executed.

GLADSTONE RADIO

NOTE NEW ADDRESS:— **66 ELSM ROAD, ALDERSHOT, Hants.** (CLOSED WED.) (2 mins. from Station and Buses). Aldershot 22240

"REALISTIC" 'SEVEN'

7 Transistor Superhet. 350 Milliwatt output, 4-inch speaker. All components mounted on a single printed circuit board size 5 1/2 x 5 1/2 in. In one complete assembly. Plastic cabinet, with carrying handle, size 7 x 10 x 3 1/2 in. External Socket for car aerial. Ferrite rod aerial. Price for the complete parcel including Transistors, Cabinet, Speaker, etc. and full Construction Data: **£5.19.6** P. & P. 4/6.

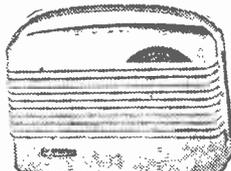

PP9 Battery 3/9. Data and instructions separately 2/6. Refunded if you purchase the parcel. Any parts supplied separately.



4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE

PRINTED CIRCUIT. 4in. x 2 1/2 in. 1 1/2 in. over transformers. Output for 3-ohm speaker. Suitable for microphone, record player, guitar and Intercom. 9 volt battery required. Frequency range 100 cps. to 25 Kcps. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Two types: 260 mw. 29/6; 1 watt. 41/6. P. & P. 2/6.

4 to 5 WATT HIGH GAIN AMPLIFIER

Only £5.15.0. (P. & P. 5/-). Suitable for record player, radio tape after equalisation. Double wound mains transformer. Fully built. For A.C. mains of 200/250 v. 14 d.b. neg. feedback. Controls are volume on/off, treble and bass. Contact cooled metal rectifier (bridge); ECC 83 and EL 84 valves. Output for 3 ohm speaker. Chassis size 6 1/2 x 6 in. (including spindle) overall height, including valves, 5 1/2 in. High and low input by Phono sockets.

E.M.I. 4-SPEED PLAYER & P.U. (separate)

8 1/2 in. metal turntable. 200-260v. motor. Turnover head. Our price 59/6 (P. & P. 4/6).

2 1/2 WATT AMPLIFIER—SPECIAL OFFER TO CLEAR STOCKS

Our price **ONLY 29/8** (post free); a few only: valves EF91 and ECL82 with metal rectifier; 6 x 4 x 1 in. high (5in. over ECL82). Mains trans. and o.p. with vol. and tone controls; on-off; co-ax. input.

GRAMOPHONE AMPLIFIERS AND PLAYERS

1) 1 watt type. With 6 x 4 in. speaker. Baffle 13 1/2 x 7 1/2 in. 200-240v. A.C. ECL82 and Rectifier. Tone and Volume On/Off switch. Two knobs. Ready to play. 49/8, post 5/-.
4 watt type. Valves UY85, UF80 and UL84. 200-240v. A.C. Covered baffle 13 1/2 x 7 1/2 in. (6in. speaker), 3 front controls; bass, treble, on-off/vol. 60/-, post 5/-. Double wound mains transformer. Cabinet to fit either type with plain motor board £3 car. pd. Complete record player in beautifully styled cabinet, fully built (NOT A KIT), £10.17.6, with UA14 4-speed autochanger or with Garrard Autolium 4-speed autochanger, £11.15.0.
Single player in Cab. 13 1/2 x 5 1/2 in. B.R.R. Monarch 4-speed deck, £8.17.6.

ADVANCE INFORMATION ON 30 WATT TRANSISTORISED AMPLIFIER

Chassis size 7 x 7 x 4 in. Input for 300-ohm (50mV for full output) and 500K (5mV for full output). 14 d.b. neg. feedback. Controls are volume (on/off), bass, treble. Transistors 2 x NKT 401, 1 x 452, 2 x 222, 1 x 264. Fitted with carrying handle. Input standard Jack sockets. Output and supply on terminal block. Black mat finish. Price £15.15.0 (P. & P. 6/-).

Write for details

TAPE RECORDER AMPLIFIER

Fully built. Front panel 12 1/2 x 3 in. Chassis size 10 1/2 x 5 1/2 in. Valves EF86, EC83 and 2-EL84's. Controls (1) MIC. Vol. (2) Tuner/P.U. Vol. (3) Play back or monitor. (4) Tone. 2 Jack sockets for Tuner/P.U. and MIC-switch for superimpose. Separate power pack containing transformer and rectifier. For Collaro studio deck only. Price £8.14.0 (6/- P. & P.).

4-SPEED AUTOCHANGERS

BSR-UA14	£5.19.6
GARRARD AUTOSLIM	£5.10.0
STEREO	£7.5.0
AUTOSLIM DE LUXE AT6	£10.19.6
STEREO	£11.10.0

(Carr. 5/- each)

13 x 8 in. LOUDSPEAKERS 49/6 (post 3/6).

Three ohm. Ceramic magnet of latest type. BRAND NEW.

GM21. CRYSTAL MICROPHONE

With 3.5 mm. Jack plug, 12/6 (Post 1/6).

HEATER TRANSFORMER

Mains input giving 8.2v. 2 amp. Size 2 1/2 x 1 1/2 in. (2 1/2 in. over winding). 5/8 ea. Less 10% for 12, or 20% for 50. P. & P. 2/- for 1 to 6, post free more than six.

Make Your Ability PAY

UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let ICS's tuition develop your talents and help you to succeed.

STUDY IS EASY with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. MODERATE FEES INCLUDE ALL BOOKS.

Take the right course now . . .

ADVERTISING & ART

- Copy-writing
- Layout & Typography
- Commercial Illustrating
- Oil & Water Colour
- BUILDING & CIVIL ENGR'G**
- Architecture, Bricklaying
- Building Construction
- Builders' Draughtsmen
- Builders' Quantities
- Interior Decoration
- Quantity Surveying
- Heating & Ventilation
- Carpentry & Joinery

COMMERCE

- Book-keeping
- Accountancy & Costing
- Business Training
- Office Training
- Purchasing, Storekeeping
- Secretaryship
- Shorthand & Typing
- Computer Programming
- Small Business Owners

DRAUGHTSMANSHIP

- Architectural Mechanical
- Drawing Office Practice

ELECTRONICS

- Computer (Educ. Subj.)
- Electronic Technicians
- Industrial Electronics

FARMING

- Arable & Livestock
- Pig & Poultry Keeping
- Farm Management & Accounts

GENERAL EDUCATION

- G.C.E. subjects at Ordinary & Advanced Level
- Good English
- Foreign Languages

INTENSIVE COACHING for all principal examinations —G.C.E., Secretaryship, Accountancy, Engineering, Work Study, Management, Radio, Architecture and Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges

Start today the I.C.S. way!

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 172)
Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on.....

Name.....

Address.....

Occupation.....

2.65

INTERNATIONAL CORRESPONDENCE SCHOOLS

RETURN-OF-POST

ON CASH OR C.O.D. ORDERS

● **SPECIAL OFFER!! STEREO CARTRIDGES**
RONETTE 105 Stereo/Mono Cartridge. Complete with fixing bracket and styl. List 59/4. OUR PRICE 23/6. Post Free.

● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-3, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer. Fully detailed list on any of these sent upon request.

Instruction Manual: All Mullard Audio Circuits in "Circuits of Audio Amplifiers", 9/5. Post Free.

● LATEST TEST METERS

	Cash Price	Deposit	Hire Mthly/Pmts.	Purchase
AVO Model 8 Mark III	£24. 0/0	£4.16. 0/0	12 of £15. 2/6	
AVO Model 7 Mark II	£22. 5/0	£4. 9/0	12 of £12. 3/6	
AVO Multimeter Mark 4	£9.10. 0/0	£1.18. 0/0	12 of 14/4	
T.M.K. TP10	£4. 7/6	£1. 7/6	3 of £1. 3/4	
T.M.K. TP58	£6.11. 6/0	£1.11. 6/0	6 of 19/2	
T.M.K. Model 500	£9.17. 6/0	£1.17. 6/0	12 of 15/-	
T.M.K. Model 127A	£10.10. 0/0	£2. 2/0	12 of 15/8	

Full details of any of the above supplied free on request.

● TAPE RECORDING EQUIPMENT

	Cash Price	Deposit	Hire Mthly/Pmts.
ALL CARTRIDGE FREE			
COLLARO STUDIO, latest model, two track, Bradmatic Heads	£10.19. 6/0	£2.3. 6/0	12 of 16/4

● MARTIN TAPE AMPLIFIER KITS

Tape Amplifiers
For Collaro 8311-V 2-Track £11.11.0. 8311-4-V 4-Track £12.12.0.
Tape Pre-Amplifiers
For Collaro 8319-CP 2-Track £8.8.0. 8319-CP 4-Track £9.9.0.
Assembly for mounting 8319 Pre-Amp under Collaro Deck 31/6.
H.P. with speaker. For Collaro Deck and 8311 Amp. £5.5.0.
J.P. TERMS available on decks, amp. and cases. Ask for quote.

● **MULLARD TAPE AND PRE-AMPLIFIER KIT**
We stock complete kits and all separate components for the Mullard Tape Pre-Amplifier. Fully detailed list available.

● GRAMOPHONE EQUIPMENT

ALL LATEST MODELS	Cash Price	Deposit	Hire Mthly/Pmts.
ALL POST FREE			

RECORD CHANGERS

GARRARD AUTOSLIM (Mono PU fixed head)	£6.10. 0/0	£1. 5/0	6 of £1
GARRARD AUTOSLIM De-Luxe AT5 (Mono PU)	£11. 9/0	£2. 6/0	12 of 16/11
GARRARD AUTOSLIM AT6 (Stereo/Mono PU)	£12. 5/4	£2. 9/4	12 of 18/-
GARRARD AUTOSLIM (Mono PU plug in head)	£7.19. 6/0	£1.10. 6/0	6 of £14.0
GARRARD AT5 L.M. (300 L.M) Low mass pick-up arm (9TA Stereo/Mono PU)	£12.15.0	£2.15.0	12 of 18/4
GARRARD A.T.5 (Mono PU plug in head)	£10. 8/2	£2. 4/2	12 of 15/4
B.S.R. U.A.15 (TC8 Mono PU)	£8.19. 6/0	£1.14. 6/0	6 of £1. 0/0
B.S.R. U.A.15 (TC8 Stereo/LP78)	£7.19. 6/0	£1.19. 6/0	6 of £1. 2/6

See our Gramophone List for details of Single Record Players and Transcription Units.

● HI-FI LOUDSPEAKERS

GOODMANS: Axlette 8in., £5.5.7; Axiom 10in., £8.5.11; 12in. Axiom 201, £10.17.4; 12in. Axiom 301, £15.4.6; 12in. Audiom 31 Bass, £9.2.8; 12in. Audiom 61 Bass, £14.7.8; Trebax Tweeter, £6.10.2; CX3000 Cross-over unit, £2.0.11.
WITELDY: HF1016 10in., £7.7.0; HF1012 10in., £4.12.0; HF816 8in., £6.6.0; T816 8in., £5.19.6; T10 Tweeter, £4.12.0; T359 Tweeter, £1.12.3; CX3000 Cross-over Unit, £1.13.3; CX1500 Cross-over unit, £2.2.0. H.P. Terms available on all speakers.

● STEREO COMPONENTS

Morganite ganged potentiometers as specified for the Mullard circuits. ★ Log/Anti-Log, 500k, 1 meg., 2 meg. ★ Log/Log, 50k, 250k, 1 meg., 2 meg. ★ Lin/Lin 250k, 1 meg., 2 meg. All 10/6 each. Postage extra.

● JASON F.M. TUNERS

We stock all parts needed for the construction of these excellent tuners. All parts can be supplied separately but we can offer attractive reductions in price if all items are purchased at same time as follows:

FMT2 (less power), £8.5.0; FMT2 (with power), £10.2.6.
FMT3 (less power), £9.19.6; FMT3 (with power), £11.17.6.
FMT1, £6.12.6.

Hire Purchase Terms available. Ask for list.

● MAINS & OUTPUT TRANSFORMERS

GILSON AND PARMEKO TYPES for many popular circuits stocked. Send for list.

WATTS RADIO (Mail Order) LTD

54 CHURCH STREET, WEYBRIDGE, SURREY

Telephone Weybridge 47556

Please note: Postal business only from this address. Callers welcome by appointment.

the surface lightly with a piece of fine emery paper, removing all traces of oil and oxidization.

Mix a solution of 2oz. copper sulphate to a pint of water in a shallow dish of glass, plastic or china. Place the board in the solution, face upwards, and connect a lead by crocodile clip between the foil and the negative terminal of a low voltage battery (less than 6V). Connect the positive terminal to a loop of heavy copper wire suspended over the surface of the foil but not in contact with it, the loop to be submerged in the solution.

As soon as the final connection is made, bubbles will rise from the copper, indicating that electrolysis is taking place. After 5 or 10 minutes the foil should be covered with a fine coating of copper and can be removed from the solution and washed under a tap.

The plating should not rub off under normal finger pressure. If it does it will be because either the surface was not cleaned fully at the beginning of the operation or too high a voltage has been used, resulting in excessive current flow and soft plating. After plating, the board is left to dry at room temperature and it is then ready for use.

The printed circuit board, home-made or purchased, is now ready to be prepared for the etching process. When the layout of the board has been decided, it should be carefully marked out with the pattern and the position of the holes for the components determined. A drill, about $\frac{1}{16}$ in. diameter, is then used to drill gently through the board from the copper side.

The area of the board *not* to be eaten away in the etching process is now painted over with an acid resistant paint, such as Valspar, or with nail varnish, which is very quick drying. Make sure that the paint covers the copper exposed by the hole-drilling process.

A solution of about 3oz. ferric chloride to one pint of water, is now made up or purchased from the chemist, and placed in a shallow dish and the painted board gently immersed in the liquid, face upwards. The untreated metal will slowly dissolve, helped along by rocking of the dish.

When the entire untreated surface is seen to be eaten away the board is removed and washed under the tap to remove all traces of the solution. Finally, the paint is removed with a suitable spirit or paint remover and the board is ready for use.

The above etching process may take as long as an hour or so, depending on the strength of the solution, **which must not be allowed to come into contact with the eyes or clothes.**

When soldering the boards, the iron must not be held against the copper foil for too long, or the foil might become detached from the base.

When the circuit has been finally built up and tested it is often a good plan to dip the entire assembly in a good quality insulating paint or shellac, to protect the circuit from dampness and dust damage.

Encapsulation

A method of construction often used on military equipment is to loosely assemble a circuit in three dimensions using the connecting wires to support it, and then encapsulate the entire assembly in an

epoxy resin, so that the finished product is a solid block of resin enclosing the circuit.

Such a circuit is incredibly strong, very compact, can be submerged in water with no ill effect, and is impervious to most acids. The only snag is that servicing is difficult!

If a piece of gear of this type does break down, it is necessary to chip away the resin until the faulty component is exposed, cut it away and replace it with a good part and then re-encapsulate the unit.

The procedure for making home-built units of this kind is as follows. Decide on the dimensional layout, wire the unit up and test it. If valves are used, they must be mounted external to the block, with the top of their valve holders flush with the top of the resin. Transistors may be fully submerged. Coat the whole assembly with varnish: this will facilitate salvaging of components during repairs.

Prepare a mould of tin, cardboard, or similar material to accommodate the wired-up unit, with a little space to spare all round, and line the inner surface with Vaseline, to stop the resin sticking to the mould.

Prepare the resin as per manufacturer's instructions. (Bondaglass "Clear Casting Resin", costing 10s. 6d. for 10 oz., is recommended, available from Bondaglass Ltd., of 53-55 South End, Croydon, Surrey), and pour into the mould to a depth of between $\frac{1}{4}$ and $\frac{1}{2}$ in., and allow to set.

When this layer has dried, lower the painted circuit on to it, keeping it central in the mould. The paint should still be wet. Pour in more resin, until the circuit is covered, and warm slightly to remove any air bubbles. The resin is translucent and these will be visible. Place the unit aside to dry. This should take no more than 12 hours. Finally, remove the block from the mould and check that the circuit is still functioning correctly.

The main snag with this type of encapsulation is the expense. An alternative is to use Plasticine in place of resin as the encapsulating medium. The loss in strength can be made up by leaving the block in its mould. Such a technique retains the advantages of compactness, acid resistance, water proofing and ability to withstand hard knocks, without the disadvantage of being very difficult to service.

An alternative method of construction to the printed circuit that has many of its advantages may be used in conjunction with the Plasticine encapsulation technique, the resulting assembly being very cheap to make. Instead of using a piece of printed circuit to hold the components in place, a piece of Paxolin or similar material is used.

Holes are drilled to take the components in the normal way, and the components are pushed through the holes from one side of the board and ordinary connecting wires used to wire them up on the other side.

The components are thus held firmly in one plane, but are still subject to movement in the vertical. By now encapsulating in Plasticine, all movement of the components under natural forces is finally arrested and the unit is complete.

Part Two Next Month

on the Short Waves

MONTHLY NEWS FOR DX LISTENERS

All times are in G.M.T.

All frequencies are in kc/s.

The Broadcast Bands—by John Guttridge

CONDITIONS in the short wavebands are now at their lowest ebb, with even the 11Mc/s band offering very limited openings after about 2100. Things should start improving, though, as winter recedes.

Station observations come from three listeners this month. Firstly up in the Shetlands reports good reception of *Radio Peking's* transmission to Australia from 0800—1030 on 9.457.

In Elgin, Paul Harris has been having some success with the 2100—2150 transmission of *Radio Nederland* on 6.085/9.590. He has also observed *Radio South Africa* in the evenings on 9,525/7,270. The former frequency, he says, is good with close down at 2115.

E. H. Conduit of Wolverhampton sends the schedule of English transmissions from *Radio Berlin International* (the East German state radio) to Europe. These are on the air from 1700—1800 on 6,080/6,115/7,132/7,300/9,730. At 2015—2045 these same frequencies are used with the addition of 1,510 medium wave. The last transmission of the evening is at 2200—2230 on 6,080/6,115/7,300 and 1,430 medium wave.

He also sends the schedule of United Nations transmissions to Europe. These are aired over *Voice of America* transmitters from 1800—1900 on Fridays and consist of ten minute programmes in Arabic, English, French, German, Greek and Turkish. Between 1800—1830 the programme is carried on 21,485 (Bethany), 15,250/17,800 (Greenville) and 9,710 (Tangier). From 1830—1900 frequencies used are 15,315 (Bethany), 15,150/11,780 (Bound Brook), 9,610 (Tangier).

African stations have been giving the best evening reception on 19 metres. *Voice of America*, Monrovia, being audible until after 2200 with English programmes. A surprise station in this band was *Trans World Radio*, Bonaire, (Netherlands Antilles) which was heard testing, with a weak signal and asking for reports at 1915 on 15,300.

One of the few signals to reach readability 3 in the 25 metre band in the late evening was *Radio Abidjan*, Ivory Coast. This was heard in London in French with Music on 11,820 at 2245.

If you haven't logged a Venezuelan yet try 4.970. If c.w. interference is not too bad you should be able to hear *Radio Rumbos*. Identification is given at 2230. The address for reports, which are verified, is Apt. 2618, Caracas, Venezuela.

The Kuwait Broadcasting Service, P.O. Box 397, Kuwait, currently uses two short wave outlets. These are a 50kW transmitter on 9,520 and a 10kW

transmitter on 4,967.5. An English programme is carried on the latter frequency from 1700—1900. An attractive QSL-folder is sent for correct reports by this station.

Extensive changes have been made by *Radio Moscow* in its European English winter schedule valid until June 4th, the only unchanged transmission being that from 1200—1230. Details of the other transmissions are 0700—0730 on 9,590/7,280/7,240/5,980; 1900—1930 on 7,330/7,280/6,100/5,980/1,320; 2000—2030 on 7,330/7,280/6,100/6,200/1,380; 2100—2200 on 7,330/7,280/7,260/6,050/1,490; 2200—2230 as 2100 plus 5,960/1,380/1,320.

Radio Japan, Tokyo, Japan, now uses 7,195 in its 1500—1630, 1645—1845 and 1900—2000 transmissions to South Asia, the Middle East, and Africa respectively. The other frequency used is 9,525 with the addition of 9,705 for the 1500 transmission. General service transmissions between 1200 and 1930 (the first half of each hour) are now on three 31 metre band outlets 9,505/9,605/9,740.

Full verification details are given on the QSL issued by *Radio Voice of the Gospel*, ETLF, P.O. Box 654, Addis Ababa, Ethiopia. Unfortunately it neglected to send a programme schedule. This station transmits 12—13 hours of shortwave broadcasts in 13 languages every day over two 100kW transmitters.

The date is the only verification detail included by all India Radio, Post Box 500, New Delhi, India, on its otherwise colourful QSL Card. Several changes have been made in this station's winter schedule valid until March 6. The English transmission to Australia from 1000—1100 is now on 11,710/15,165 with 9,655/11,700/15,105/17,855 being used at the same time to Asia. The East African English transmission from 1840—1930 is now on 7,180/9,680/11,815/11,940. Although the frequencies—6,130/7,235/9,915—of the European English transmission at 1945—2045 remain unchanged, the relay to West Africa at the same time is now on 7,125/9,690/11,740.

Transmissions to the Caribbean and South America in Portuguese from 2331—2400 and Spanish from 0000—0045 from the Canadian Broadcasting Corporation, P.O. Box 6000, Montreal, Canada, are now going out on 11,760/9,625/5,990. This winter this station not scheduled to use a frequency lower than 9,630 to Europe, although it used the 49 metre band last year. Full verification is given by this station to correct reports.

Monthly programme schedules are not to be distributed by *Radio Nederland*, P.O. Box 222, Hilversum, Holland, in future. Instead schedules will be issued four times a year to coincide with the changes of season and frequencies. During January and February programmes remain basically unchanged with D_x Juke Box on Thursdays. Frequencies are as December.

The winter schedule of the *Voice of America* gives the following frequency usage for English to Europe: 3.980 0300—0730, 1400—2345; 5.995 0300

—0730, 1630—2245; 6.040 0500—0730; 6.080 0300—0730; 7.200 0300—0730; 7.205 1500—1800, 1830—2245; 9.545 0500—0730; 9.670 1915—2215; 9.740 0500—0730, 1830—2245; 11.790 0500—0730; 11.825 1900—2215; 15.205 1400—2215; 15.290 1400—1630; 17.780 1400—1800. The medium wave outlet on 1.196 is used from 0400—0430, 0500—0730, 1700—1830, 2200—2345.

Finally, a collective "thank you" to many readers who have sent along news and reports. Sorry we cannot mention you all!

The Amateur Bands—by David Gibson G3JDG

FIRST this month a big "Thank you" to all those SWLs who sent in reports on the various bands.

1.8Mc/s

Top band seems to be rather abandoned by most reporters and no one appeared to listen out very much. I had a couple of very hectic one-hour sessions on November 14-15th in the M.C.C. 1.8 Mc/s contest. Many G stations were worked and the best "DX" was GW6GW at Blackwood in Monmouthshire. A ten-minute listening period, Sunday, November 29th, between 1800 and 1810, logged G2PT, G3SYX, G3TLE, G3OCA, PA0PN, GC3ECC, DJ3JZ.

Master Darrell Earnshaw (Preston) seems to have things pretty well organised in that his sister does a turn at the receiver. They offer the following log for 1.8: G3EXU, G3FIF, G3DMO, G3SSU, G3RFN, G3KE, G3NVN, G3GGS, G3TNN, G3KKU, G3WLQ, G3GEU, G3SWM, G3HFD, G3TFN, G3ERY, G3BES, G3JMA, G3NSW/M, G6ES/M, the stroke M signifying that the station is mobile and operating from a vehicle. All these stations on phone.

3.5Mc/s

This band also seems passed over by most listeners and only one letter offers any log at all. T. Cridland, of Canvey Island, uses a Codar CR45 (TRF) with an 18ft length of wire mounted vertically up the side of the house, heard these on November 14th between 0932—1016: G3PLR, G3HRD, G3SJ, G2WJ, G3MY, G2BSA, G3PZX, November 15th (1220—1342): G3PIX, G3RAO, G3POC, G3GFJ, G3PMC, G3PFT, G2AFR, G3RBF, G3MUW, G3SNI, G3TIZ.

7Mc/s

Forty metres also is sadly bypassed by all and sundry and no one mentioned it this month. It must be confessed that a quick listen most evenings would deter all but the very brave. This is a shame because after a while odd call signs start to appear and a little perseverance can produce quite an interesting log, especially early morning. Ten minutes on November 29th (1800—1810) logged LZ2ANB, G3GJX, YO8KAF, IZ1KBD, YO5KAI, PA0LV, UR2AO, UB5KCE and CR6AI.

14Mc/s

And so to the h.f. bands where 20 and 15m are firm favourites—not surprising considering the volume of traffic, particularly on 20. From 1738—

1746 (yes, just eight minutes) W4BV, W1BFA, W2KXV, W2LSW, W2AZS, W3BYX, W4KFC, W2PCJ, HZCN, K3JCT, GB2SM, K8KKB, K1BBV were heard and these were only the loud ones.

Immediately after (at 1748) the bandswitch was set to 21Mc/s, same antenna, 60ft long wire, same receiver (r.f., f.c., i.f., det., o-p.), and guess what I heard—nothing, absolutely nothing!

J. R. Hunt (London) has an R1155 into a 67ft long wire, 15ft high, and reports between 0700—0905: 9G1DY, W3KFO, W2LOY, WA2KIC, ZL3OP, VK6MM, all on 14Mc/s. P. D. Coull (Littlestone, Kent) reports (14Mc/s) VK3VJ, VS9MG; at 1600 VE8MJ, VE8RG; at 1800 OX3MN at 1530 and TG9RJ, W2OKM at 1915. On 21Mc/s: 9G1FC, ZB1RM at 1030 and W1ONK at 1410. The gear—a Codar CR66 and a 60ft long wire.

M. Woollin (Leeds) uses a modified 19 set, an RF24 unit and a 100ft long wire. This little set-up raked in KA2RG, VK8KK, VK2JZ on s.s.b. at 1540 on 14Mc/s, while on 21Mc/s he really twists the knife into your poor scribe with ZC4MO, 9Q5YL, 9Q5PN, ZS1AB, SU1DL, VS9APT, 9G1DM, and all on a.m., phone too.

D. Howarth in Bolton, Lancs., uses a PCR3 receiver and a 20ft vertical. However, he also confesses to using a long wire with a 600Ω resistor at the far end. (The wattage is not stated, so don't write in and ask!) Fourteen Mc/s produced SP5ACD, OE6UX, OY7S, OE1HKW, CT1LX, W8RRT, OH1WI, F5KE, OE1GE, OH5NQ, EA3NA.

Down in wild and woolly Wales stations are coming in very well according to M. Carter, who listens at Colwyn Bay. On 14Mc/s VK2KM (s.s.b.) and 21Mc/s KV4CX (a.m.), W6BMG (s.s.b.) received on a 19 set Mk. 3 with a Labgear front end converter. A recently purchased H.R.O. Junior, also with a pre-selector, brought in VK3UN, WA6ZZ (s.s.b.), Z11AY (a.m.) and KA7CLH (s.s.b.). The twist in the end of this story is that the antenna is an indoor dipole and the house is not more than 50ft a.s.l. Flat-dwellers proceed to the loft immediately with 33ft of wire! Incidentally, Michael says that most Pacific DX was received between 0730 and 0830 hours before going to school or 0730 to 1000 hours at weekends.

Bernard Hughes, BR525901 (Worcester), runs an Eddystone 840C and a Codar pre-selector with a choice of either a 20m dipole or a 70ft long wire. With this set-up his 20m log is: 5ZHAO,

—continued on page 969

BOOKS REVIEWED

RADIO SERVICING ("Teach Yourself" Books), by L. Butterworth.
Published by The English Universities Press Ltd.
257 pp. with index. 7½in. x 4½in. Hard cover. Price 10s. 6d.

THE "Teach-yourself" books have come in for a lot of banter. "How to be a physicist in six easy lessons", chaffs the comedian. But, in fact, a remarkable amount of useful information is contained in these 19 chapters, and the student with some access to practical workshop (or kitchen table) facilities would find this book a very inexpensive course on the subject.

The emphasis on the practical approach is evident from the outset. There is no opening gambit of long-drawn theory but an immediate attack on diagrams, soldering and simple measurement, leading to a second chapter which manages to slip a good deal of theory into a practical discussion of resistance and resistors. This is the technique throughout the book: the author demonstrates his theory by practical exercises, much as the lecturer would at technical college. Each chapter has a terminating list of exercises.

After resistance, series and parallel circuits, a.c. is dealt with, in a masterly chapter only a dozen pages in length, yet managing to bring in sine and square waveforms, frequency, measurement and even a description of the oscilloscope. Capacitors, inductances and transformers follow, with the usual protracted electromagnetic theory chopped down to the necessary minimum.

Chapter 7 deals with rectifiers, and this leads naturally to power supplies and thence to amplifiers, bringing in various valves and their characteristics and treating transistors as a natural parallel. Not, as so often, an adjunct to the business of radio servicing. Chapter Ten takes the reader straight from the triode amplifier to the junction transistor a.f. amplifier.

The next chapter, The Output Stage, reverts again to valve operation before leading to the rather special field of output transistorised stages. Here, there is a tendency to gloss over the subject with a remark: "*A number of other arrangements of output transistors may be encountered, . . .*" However, the student who has progressed thus far with the aid of this book should have little difficulty in developing his reading along sound lines.

After a chapter on low frequency amplifiers there is a surprising reversion to tuned circuits and oscillators, and thus to transmission and reception, r.f. circuits, selectivity, bandpass circuits and an

introduction to alignment entering at this point, before a discussion of the superhet receiver itself. The book is rounded off with a chapter on workshop equipment and methods, which is, for a work of this nature, quite inadequate. The essence of radio servicing is the alliance of practical testing with theoretical knowledge, which the remainder of the book most admirably presents. This final chapter could have been much more comprehensive.—H.W.H.

GUIDE TO BROADCASTING STATIONS—14th EDITION
Compiled by the staff of "Wireless World" magazine.
Published by Iliffe Books Ltd.
128 pp. 7½in. x 4½in. Price 5s.

THE greater part of the contents of this extremely useful reference book appear under two main sections: Long and Medium-wave European Stations, and Short-wave Stations of the World, and these two headings almost describe the book's coverage of the subject sufficiently to make further comment superfluous. To elaborate, however, each section gives a comprehensive list of stations in order of frequency, also listing country of origin, power in kilowatts and the wavelength equivalent in metres. In the list of world s.w. stations, call signs are also given, while in the European list, channel numbers are quoted. Each section also provides a separate geographical list of the stations.

The book contains one other list which gives the international allocation of call signs by countries. A short list of the s.w. broadcasting bands precedes the short-wave section and in this section also, stations operated by "extra-territorial" organisations (e.g. British Forces Network, Voice of America) are indicated by abbreviations.

There remains one other contents item to be mentioned, at which can be levelled the only unfavourable comment the book as a whole warrants. A map showing the broadcasting regions of the world in the centre of the book, which would normally have been of much value and interest, is rendered indistinct through the use of poor quality paper. However, as already said this was the only adverse criticism of the book and this, when considered against the reasonable price can amount to no very great objection. Otherwise this book must be considered excellent value to the short-wave listener and the DX-er: cheap enough to discard for a new one as each revised edition appears.—P.R.R.


"PRACTICAL WIRELESS" INDEX

Indices for "Practical Wireless" Volume 39 (May 1963 to April 1964) are now available from Post Sales, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2., price 1s. 3d. including postage.

PART 5—FEEDBACK IN TRANSISTOR CIRCUITS

Understanding SEMICONDUCTORS

BY LESLIE MOORE

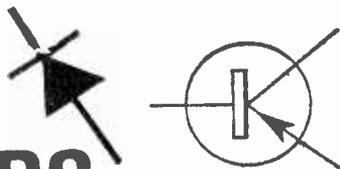

CONTINUED FROM PAGE 890 OF THE JANUARY ISSUE

ANY natural oscillation tends to obey a sine law unless some interference or other, is used to distort that oscillation. Non sinusoidal oscillators exist which produce waveforms that may be square, saw tooth, staircase etc.; these are known as relaxation oscillators. One relaxation oscillator called the "astable multivibrator" or the "free running multivibrator", a fairly common cir-

- (ii) As time passes the capacitor charges hence causing a voltage drop across itself.
- (iii) We could assume that finally no current would flow and hence no voltage drop across the resistor.

If the growth of potential drop across the capacitor were drawn on a graph with respect to time the result would be as in Fig. 34. This growth of potential obeys an "exponential" law. The bottom of the curve appears to be linear.

Suppose the rate of change of voltage across the capacitor at the beginning of the operation were sustained until a voltage equal to that of the supply voltage were reached. The time in which this operation would take place is known as the time constant. As the actual rate of change obeys an exponential law, in the first time constant the voltage rises by approximately 63.2% of the supply voltage. If the supply voltage were 100V then after one time constant 36.8V would appear across R. After a second time constant 63.2% of the 36.8V would further be dropped across C. The process is unending; theoretically current never stops flowing in the circuit, but in practice after a few time constants have passed any current flowing can be neglected—depending, of course, on the requirements of the circuit.

The time constant of a circuit is the product of capacitance and resistance.

E.g. If an 0.1μF capacitor were in series with a 1kΩ resistor the time constant would be:

$$\begin{aligned}
 &0.1 \times 10^{-6} \times 1 \times 10^3 \text{ seconds} \\
 &= 0.1 \times 10^{-3} \text{ seconds} \\
 &= 0.1 \text{ milliseconds (mS)}.
 \end{aligned}$$

A capacitor discharging across a resistive load also loses its voltage exponentially.

The circuit in Fig. 35 is known as a "differentiating circuit". If a square wave were to be applied

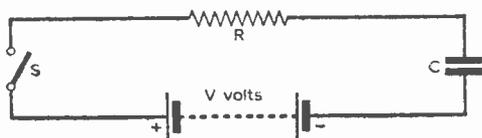


Fig. 33: A C/R series circuit.

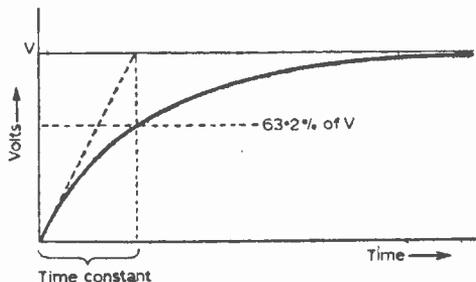


Fig. 34: A graph of the voltage "growth" across a capacitor in a C/R circuit.

cuit throughout the electronics field, produces an almost perfect square wave.

An important factor in the design of the free running and other multivibrators, is that of the charge and discharge characteristics of a capacitor in a d.c. circuit.

Fig. 33 shows a series circuit including a capacitor C, resistor R, a battery of potential V volts and a switch S. When the switch is closed an instantaneous value of current would flow equal to R/V Amps. Current flowing in the circuit "charges" the capacitor, the charge acting in opposition to the flowing current; the value of charging current then decreases, the voltage across R will decrease so a potential will appear across C.

Taking this series circuit at face value we could assume three things:

- (i) At the first instant there is voltage drop across the capacitor.

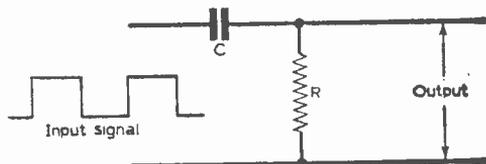


Fig. 35: The differentiating circuit.

across the input the output would be a function of the combination of capacitive and resistive values. Suppose the time constant is very short compared with the time of existence of any one pulse, the capacitor would be able to charge almost fully to the applied voltage. Fig. 36a shows the output of such a circuit.

A square wave applied to the differentiating circuit with a long time constant compared with the wave time length would produce an output shown in Fig. 36b; this is because the capacitor is not allowed sufficient time to charge fully.

The circuit of a free running multivibrator is shown in Fig. 37. R1 and Tr1 are in series as also are R4 and Tr2. Because these two series circuits are not quite exactly the same in resistive values due to tolerances etc., one transistor may conduct slightly more current than the other. Assume that Tr1 conducts a higher value of current than Tr2, more voltage will be dropped across R1 than R4,

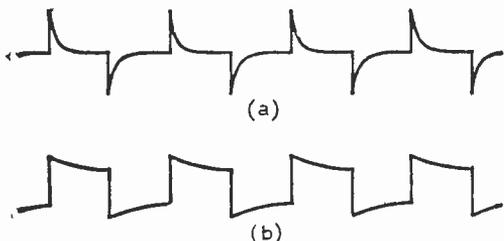


Fig. 36: (a) The output waveform of a differentiating circuit with a short time constant. (b) The output waveform of a differentiating circuit with a long time constant.

then Tr1 collector will be more positive than Tr2 collector. In the first instant of applying the supply voltage, the voltage across R1 will also be seen across R3. The base of Tr2 will be almost the same potential as the emitter, therefore current conduction through Tr2 will reduce, hence the collector of Tr2 will rise towards the negative supply voltage. The base of Tr1 also rises towards this value and Tr2 will continue to conduct even more current. This action continues until Tr1 is conducting its maximum value of current (determined by the value of R1) and Tr2 is cut off. The capacitors C1 and C2 begin to charge as soon as current flows to their plates, therefore the base of Tr1 begins to hold a positive going potential and Tr2 a negative going one. A point is reached where conduction through Tr1 and Tr2 is switched due to the changing base potentials. The switching between Tr1 and Tr2 will continue because of the action of capacitors C1, R3 and C2, R2. The values of C1, C2, R2 and R3 are important as their time constants determine the circuit's switching frequency.

The output of the circuit is taken from any one of the transistor collectors. If a fairly good square wave is required the value of the output capacitor, C, and the resistive value of the load should form as long a time constant as possible.

The free running multivibrator is often used as a signal generator as there are very few components required and can be built very inexpensively.

Conclusion

Semiconductors have been seen to have a variety of uses; as a rectifier enabling the conversion of alternating currents into direct current, as an amplifier in the form of a transistor, as sinusoidal and square wave generators, they can be used as switches to half-pulse frequencies—these are only a few of their applications.

Numerous forms of semiconductor devices exist, the majority of which have not been mentioned in this series, they include the tunnel diode making possible the solving of problems at ultra high speeds, the variable capacity diode which is now used in frequency modulating circuitry replacing cumbersome and inefficient components, the four layer diode and unijunction transistor, each of which can produce saw tooth generations with as

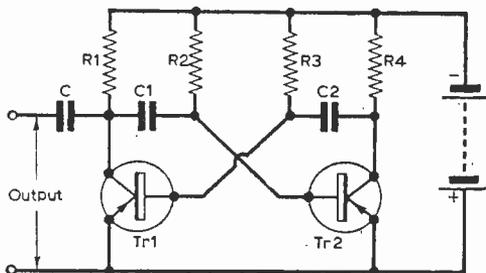


Fig. 37: Free-running multivibrator circuit.

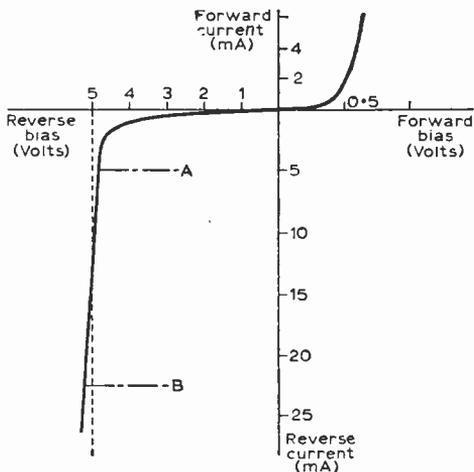


Fig. 38: A typical characteristic curve of a zener diode.

Why

NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

BACKED BY OUR SUPER AFTER SALES SERVICE

ROAMER SEVEN Mk III


5 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification ★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned heavy duty "Celestion" speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Real leather look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP7 battery available anywhere).

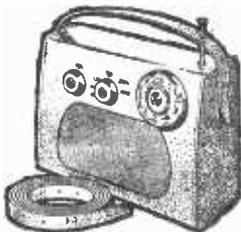Total cost of parts now only **£5.19.6** P. & P. 5/6
Parts Price List and easy build plans 3/-



"... amazed at volume and performance... has really come up to my expectations."
S. G. Stockton-on-Tees.

● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tuned circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial. Push-pull output.

MELODY SIX



Wonderful reception of B.B.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2in. approx. with gilt speaker grille and supplied with hand and shoulder straps.
Total cost of all parts now only **£3.9.6** P. & P. 3/-
easy build plans 2/-

New TRANSONA FIVE

"Home, Light, A.F.N., Lux. all at good volume"
G.P. Durham

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2in. speaker etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2in. (Uses 1289 battery available anywhere.)

with red speaker grille. (Uses 1289 battery available anywhere.)
Total cost of all parts now only **42/6** P. & P. 3/6
Parts Price List and easy build plans 2/-

TRANSONA SIX

● 8 stages—6 transistors and 2 diodes



This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2in. (Uses PP4 battery available anywhere.)


Total cost of all parts now only **59/6** P. & P. 3/6
Parts Price List and easy build plans 2/-

POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. Ontest Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2in. moving coil speaker, built into attractive black case with red speaker grille. Size 5 1/2 x 1 1/2 x 3 1/2in. (Uses 1289 battery available anywhere.)
Parts Price List and easy build plans 1/6

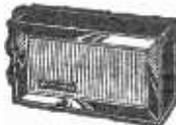Total cost of all parts now only **42/6** P. & P. 3/-



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful

reception. Special circuit incorporating 2 RF Stages, push-pull output, 3in speaker (will drive large speaker). Size 7 1/2 x 5 1/2 x 1 1/2in. (Uses 9v battery, available anywhere.)
Total cost of all parts now only **£3.19.6** P. & P. 3/6
Parts Price List and easy build plans 2/-

ROAMER SIX NEW!!

NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS
● 6 WAVEBAND !!



● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 8 waveband portable. Tunable on Medium and Long waves, Trawler band and three Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2in. Carrying strap 2/6 extra.

★ EXTRA BAND FOR EASIER TUNING OF LUX, ETC.
Parts Price List and easy build plans 2/- Total cost of all parts now only **£3.19.6** P. & P. 3/6

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at prices stated. Overseas post 10/-.

RADIO EXCHANGE CO.

61, HIGH STREET, BEDFORD. Phone: 2367

Callers side entrance
Barratts Shoe Shop
Open 9—5 p.m.
Sats. 10—12.30 p.m.

NEW CONSTRUCTORS PARADISE — FAST POSTAL SERVICE

ADAstra 3 WATT AMPLIFIER



Recently introduced highest quality ready built British Made Amplifier. Separate Bass, Treble and Volume Controls. Separate high quality finished front panel. Output, 3 watts into 3 ohms. Excellent mains transformer 200/250 volts AC input. Enamelled chassis. Size 9 x 7 x 4 in. Price 89/6. Post and packing 3/6.

LOUDSPEAKERS

Famous make 10 x 6 in., 3 ohms brand new. Our price whilst stock last, only 29/6. Post and packing 2/6 Heavy duty 15 watts, 12 in. Loud speakers. Heavy die-cast chassis. 3 or 15 ohms. Speech coil. Frequency response 30 to 14,000 Cycles. Price 45.10.0.

FAMOUS LINEAR AMPLIFIERS

Stereophonic Amplifier, two channel high impedance input. Sensitivity is high enough to load fully the output when connected to practically any make of stereo head. Can also be used for normal bands. Output as stereo in excess of 2 watts, and as monaural over 8 watts. Separate volume, tone and balance controls, for 3 ohms speaker. Size 9 x 7 x 3 in. Price 27.19.6. Post and packing 3/6. Attractive matching protective cover 25/-.

LINEAR DIATONIC 10 WATT HI-FI including pre-amplifier

Ultra linear push-pull. Two separate controlled input sockets for gram/mike etc. (two different inputs can be simultaneously applied). Maximum output exceeds over 14 watts. Separate control for Bass, Treble and Volume. Output 3 or 15 ohms. Reserve power supply for tuner etc. Price 113.2.6. Post and packing 4/6. Chrome handled protective cover available at 25/-.

SENSITIVE CRYSTAL SET




Ready built and complete with personal earphone etc. Size 3 1/2 x 2 1/2 in. in beautiful plastic case. Price 15/-. Post and packing 1/6. (Ideal Christmas Present).

MAINS RADIOS 5 Valve Superhet Circuits

Attractive quality plastic cases. 200/250 volts. Medium waves coverage. Price 97/6. Post and packing 2/6. Makes ideal Christmas present (All waves models 7 gns).

QUALITY MULTI-METER

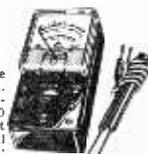

Pocket size 4 x 2 1/2 x 1 1/2 in. High sensitivity of 1,000 ohms per volt on AC as well as DC ranges: 0 to 15 volts, 0 to 150 volts, 0 to 1,000 volts. Same range when switched to AC. Current range 0 to 150 mA. Resistance 0 to 100 Kohms. Weight only 8 oz. Sturdy instrument complete with test leads, battery, instructions etc. Price 38/-. Post and packing 2/6.

TRANSISTORIZED SIGNAL INJECTOR



Complete with batteries, extra long life and full instructions for fault tracing on radios or television sets (shows alternate black and white bars when injected into a television). Will pay for itself over and over again in fault finding. Price 37/6. Post and packing 2/6.

PP3 BATTERY CHARGER

Same size as PP3 battery it either replaces it by plugging into the mains or charges your PP3 Battery. Boxed with full details etc. Price 17/6. Post and packing 1/6.

SLIMLINE CRYSTAL MICROPHONE

With aluminium die cast casing with satin chrome finish. Incorporates On/Off locking switch. Complete with cable, chrome stand holder etc. etc. Sensitivity — 52 dB. Frequency Response 60 to 10,000 Cycles. Termination of over 500,000 ohms. Price 47/6. Post and packing 3/-.

FOUR TRANSISTOR AMPLIFIER



(Ready built) only 4 x 1 1/2 x 3 1/2 in. Includes own output transformer with standard 3 ohms output, and four transistors giving nearly 4 watt output from standard 9 volt PP3 type battery. Complete with full instructions. Price 37/6. Post and packing 2/-.

TRANSISTOR RADIOS

6 Transistor covering Medium waves, beautifully boxed and complete with all extras. Price 69/6. Post and packing 2/6. (Two wave models 89/6).

JETRONIC ENGINEERING CO. LTD.

(Dept. P.W.J. 2) 19 GARDNER STREET, BRIGHTON P. C.O.D. 3/- ex. Catalogue of every item in stock 1/- post free MAIL ORDER ONLY.

— all these and hundreds more

Mon. Sat. 9 a.m.—5.45 p.m. Wednesday 1 p.m. Lunch 1.30 to 2.30

Special 24 Hour Express Mail Order Service

AZ31 12/6	EBF89 7/6	EF89 8/-	EZ41 7/-	PCL83 9/-	U25 10/-	UL84 6/-	5Y3GGT 8/-	6C5GT 8/-	6U9G 7/6	12AX7 5/6
DAF91 4/6	EC81 4/-	EP91 4/-	EZ80 5/6	PCL84 7/-	U26 10/6	UY41 7/6	6A7 8/6	6C6 6/6	6V6G 4/-	12BA6 7/6
DAF96 6/6	EC82 5/-	EP92 4/-	EZ81 5/6	PCL85 7/6	U191 13/6	VY85 5/6	6A7 12/6	6C6D6G 25/-	6V6GT 7/6	12BE6 7/6
DF91 3/-	EC83 5/6	EP93 10/-	GZ32 12/6	PCL86 10/-	U301 18/6	VP43 17/6	6A5 8/6	6C6H6 10/-	6X4 4/6	12K7GT 5/-
DF96 6/6	EC84 6/6	EP93 8/-	HL4DD 1/6	PL8 1/6	U801 19/6	VR150/30 6A15 3/6	6A5 3/6	6C8 5/6	6X5G 5/6	12K8GT 10/-
DK91 5/6	EC85 6/-	KF184 8/-		PL81 7/6	UABC80 5/6	6A7 6/6	6A6 4/6	6F6 5/6	FX3GT 8/6	12Q7GT 9/-
DK92 7/-	EC85 12/6	EL23 17/6	KT66 12/6	PL82 7/6	UAF42 8/6	6A6 6/6	6A4 6/6	6H6 2/-	630L2 12/6	12Q8GT 12/-
DK96 7/6	EC842 8/6	EL41 9/6	KT61 10/6	PL83 7/6	UBC41 8/-	X61M 13/6	6A76 4/6	6J56G/GT 7/6	21/-	19A95 8/-
DL92 5/-	EC841 7/-	EL42 9/6	KT66 7/-	PL84 7/-	UBF80 7/6	X79 20/-	6B8G 2/6	6J74 5/6	7B7 9/6	25Z4 7/6
DL94 7/-	EC843 5/6	EL84 5/6	MU14 17/6	PY82/3 10/-	UBF89 7/6	X79 40/-	6BA6 5/6	6K7G 2/6	7C8 10/6	35L6GT 8/6
IL96 6/6	EC80 6/6	EL95 9/6	N78 22/6	PY81 6/-	UCH42 8/6	IR5 5/6	6BD6 5/6	6K7G 2/6	7H7 6/-	35W4 6/6
EAC80 5/6	EC82 8/6	EM80 8/-	OZ 5/-	PY82 5/6	UCH81 7/-	IR5 5/6	6B16 6/6	6K8G 2/6	7H7 6/-	35Z4 6/6
EAF42 8/6	EC86 8/6	EM81 8/-	PC84 8/-	PY83 7/6	UCL82 8/6	IT1 3/-	6BH7 10/6	6K8G 4/-	787 18/-	30C5 8/6
EB01 3/6	EF41 7/6	EM84 8/-	PC89 8/6	PY80 8/6	UCL83 8/6	ST 5/6	6B8S 12/6	6K8GT 9/6	7Y4 2/-	80 7/6
EB41 8/-	EF80 5/-	EY51 7/6	PCF80 7/6	PZ30 12/6	UF41 7/6	3V4 2/-	6BW6 9/-	6C6 7/6	8D3 4/-	90C6 25/-
EBF80 7/6	EF85 5/-	EY86 7/6	PCF86 8/6	SP61 3/-	UF89 7/-	5U4G 4/6	6BW7 9/-	6Q7G 6/-	10F1 10/-	99CV 25/-
EBF83 8/-	EF86 7/-	EZ40 7/-	PCL82 7/6	U14 9/-	UL41 7/6	5V4G 9/-	6C4 3/6	6Q7GT 10/-	12AU7 5/-	807 9/6

COMPLETE VALVE LIST FREE WITH ORDER

OBsolete VALVES A SPECIALITY SEND FOR QUOTATION

TERMS OF BUSINESS C.W.O. or C.O.D. 4/2 PACKING CHARGE ON ALL C.O.D. ORDERS. POSTAGE 6d. per VALVE

Mon.—Sat. 9 a.m.—5.45 p.m. Weds. 1 p.m. Lunch 1-30 to 2-30

BRAND NEW TRANSISTORS			
OC35 10/-	OC72 8/-	OC81D 5/-	
OC42 6/-	OC74 8/-	OC81M/pr 12/6	
OC44 5/-	OC75 8/-	OC82 8/-	
OC45 5/-	OC77 8/-	OC82D 6/-	
OC71 5/-	OC81 5/-	OC170 6/-	

SILICON RECTIFIERS
400 volts 350 mA 7/6 each

SETS OF VALVES			
IR5, IS5, IT4, 354, 3V4	Set of 4, 17/-		
DAF91, DF91, DK91, DL92, DL94	Set of 4, 17/-		
DAF96, DF96, DK96, DL96	Set of 4, 25/-		

R.S.T. VALVE MAIL ORDER CO.

211a STREATHAM ROAD MITCHAM SURREY

Tel: MITcham 6202
Open Daily to Callers

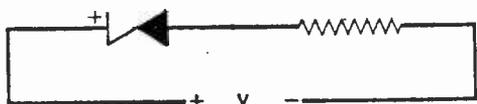


Fig. 39: In this circuit arrangement the zener diode is operating under reverse bias conditions.

few as two other components and a voltage supply, the list is unending.

One particular special purpose semiconductor device of interest to nearly all electronic enthusiasts, is the "Zener diode".

A normal pn junction diode under reverse bias conditions will begin to conduct current when the voltage applied to the diode is in the region of one to two hundred volts. This voltage is known as the breakdown voltage. A scientist named Zener examined this effect and because of his work the Zener diode, which has a breakdown voltage of only a few volts, is now in general use.

Zener diodes are used as voltage stabilisers, several types are in existence, each with a different breakdown voltage. Typical characteristics of a Zener diode are shown in Fig. 38. From the slope of the characteristic curve between points A and B, it is seen that for a large change in current through the diode, voltage across the diode changes only minutely. The Zener diode is worked on this part of its characteristic as a voltage stabiliser.

A Zener diode is shown in Fig. 39 in series with a resistor, a voltage supply is across the series circuit. Any small change in the supply voltage would cause a current variation in the series circuit. Providing the diode is in that part of its working region equivalent to being between points A and B in Fig. 38, for all practical purposes the voltage across the diode would not change; therefore the difference in supply voltage causes an equal voltage difference across the resistor.

If only a small stabilised voltage was required,

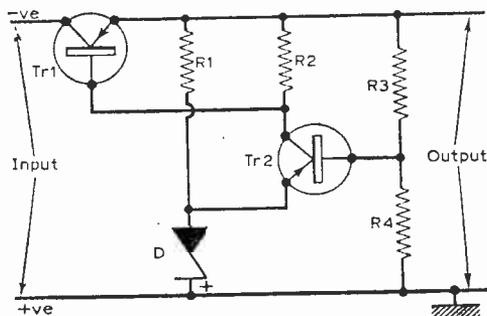


Fig. 40: A voltage stabiliser circuit, employing a zener diode, used as the last stage of a power amplifier. The circuit symbol of the zener diode used in these diagrams is only one of several in general use.

say 5V; a suitable Zener diode would be chosen for a circuit such as that shown in Fig. 39, the output would be taken from across the diode. This is an obvious application of the device, there are many, one of which incorporates the use of further semiconductors, again, as a voltage stabiliser.

The action of a power supply was explained earlier in this series; many circuits require a larger voltage supply than the breakdown voltage of a Zener diode to be stabilised. Fig. 40 shows the type of stabiliser that may be used as the last stage of a power supply.

The stabiliser has two purposes.

- (i) to remove any ripple resulting from insufficient smoothing.
- (ii) to give a stable d.c. output for any variation of mains voltage to the power supply.

Tr1 is acting as a variable resistor in the form of an "emitter-follower" circuit. D produces a constant emitter bias for Tr2. If the collector voltage of Tr1 were to change, the emitter would try to follow that change, but in doing so the base bias of Tr2 alters. The conductance of Tr2 changes as a result. The change in emitter-collector voltage of Tr2 is directly fed back to the base of Tr1. The conductance change of Tr1 due to this compensates for the change in Tr1 collector voltage and the emitter of Tr1 stays at a steady potential.

The stability of this circuit is due to D as it holds the emitter of Tr2 at a steady bias voltage.

There are many advantages of semiconductors over thermionic devices. They include, the small working voltages required for their operation, their comparatively small physical sizes, no power supply is required for their operation. One disadvantage of domestic type semiconductors (e.g. those found in portable radios) is that they must not be overheated.

Many of the problems encountered in electronics are associated with power supplies, and because of this power supplies have been dealt with fairly fully compared with the other subjects covered in this series, but the subject is not quite complete.

It is quite often required to have more space on a chassis to make minor alterations—a method of providing that space, if not already done, is to convert the thermionic rectifier into one using pn junction diodes. A small mounting on the mains transformer would be sufficient to hold the rectifying circuit, as diodes now exist with ratings of "peak inverse voltage" of 800V and "peak forward current" of 0.5A and are only as large as a 1/4W resistor.

Semiconductors, although they appear to be extremely complicated, have much to offer—there are numerous types doing many operations, there are also many publications explaining in vivid detail the uses of semiconductors. I hope this series has helped you understand them. ■

TRANSISTOR RECEIVER SERVICING

STEP-BY-STEP

EXPERIMENTERS and enthusiasts brought up on valve equipment sometimes have difficulty in switching their thoughts to transistor circuits and the relatively low voltages that these work with. When dealing with transistor equipment, the author finds it best to forget valve techniques altogether and look upon the transistor circuit as something new.

Although there are several parallels between valves and transistors, as brought out in the classic descriptions of transistor operation, there are often times during a fault tracing exercise when a transistor fault condition has no resemblance whatever to a valve fault condition.



This can complicate matters if one has stuck too rigidly to valve/transistor parallels.

With this in mind, this article is concerned not with how transistors and their circuits work particularly, but what to do when a transistor circuit ceases to function. Fortunately, a transistor is a simple device to work with since it has only three electrodes, these being called the base, the emitter and the collector, as shown on the transistor symbol in Fig. 1.

by Gordon J. King

There are two basic types of transistor, the p-n-p type which is used extensively in all transistor radios and small amplifiers and the n-p-n type which, until comparatively recently, was rarely seen in domestic equipment. However, mixtures of both types are now finding their way into the new radios and amplifiers, particularly in the output stage where their use together forms the so-called "complementary amplifier".

This type of output stage has the great advantage of requiring neither a driver transformer nor an output transformer, the speaker being connected direct to the transistors.

P-N-P and N-P-N Polarities

Symbols p-n-p and n-p-n are shown at (a) and (b) respectively in Fig. 1, and one important point to note at this juncture is that the collector of the p-n-p type is connected to supply negative while the electrode of the n-p-n type is connected to supply positive. If something is done during a servicing operation to cause a reversal of this potential, then it is likely that the transistor will burn out or be impaired considerably in efficiency.

When working as an amplifier, a transistor passes current through its collector/emitter circuit, but the current in the emitter circuit is very slightly higher than the current in the collector circuit since the emitter circuit carries also a little base current.

Collector current will not flow unless a little base current is flowing, and in order to satisfy this latter requirement the base of a p-n-p transistor must be connected to a negative potential while that of an n-p-n transistor must be connected to a positive potential.

Both the collector and base potentials are relative to the emitter, as shown in Fig. 2 at (a) for p-n-p transistors and (b) for n-p-n transistors.

The input signal may be applied either at the emitter or the base and extracted from either from the collector or emitter. The three resulting methods are shown in Fig. 3. That at (a) is the "common-emitter", at (b) the "common-base" and at (c) the "common-collector". Note that the common electrode in each instance is that which carries both the input and output signals.

Circuit Configurations

The common-emitter circuit has the highest power gain and is the most frequently used. The input impedance is medium and the output impedance medium to high.

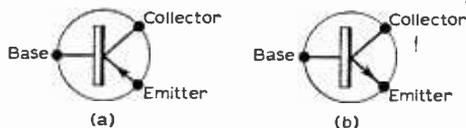


Fig. 1: Transistor circuit symbols; (a) p-n-p and (b) n-p-n. Note change in direction of emitter arrow head.

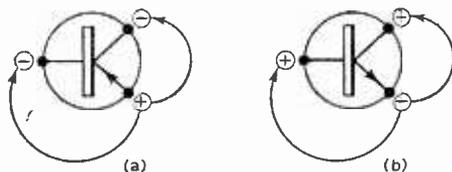


Fig. 2: Transistor polarity; (a) p-n-p and (b) n-p-n. Voltages are relative to emitter.

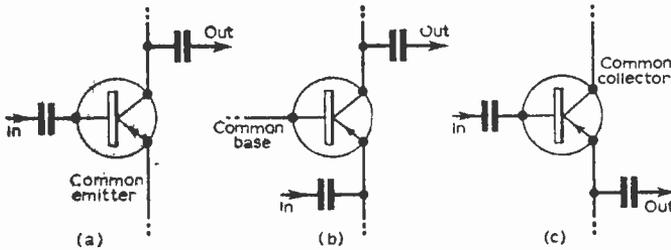


Fig. 3: Transistor configurations; (a) common-emitter, (b) common-base and (c) common-collector.

Transistor amplifiers can be subjected to both negative and positive feedback by applying from the output out-of-phase or in-phase signals to the input. In the latter respect, therefore, coupling for positive feedback turns the amplifier into an oscillator, the frequency of which is controllable either by CR or LC circuits in the usual manner.

The most usual method of applying the base and collector potentials to an amplifier is shown at (a) in Fig. 4. The potential-divider R1/R2 allows the base to be biased from the same supply source as feeding the collector. It also stabilises the base bias.

The emitter resistor R3 also serves to stabilise the transistor against an increase in collector current which can otherwise arise due to temperature increase, this being a characteristic of the transistor.

With R3, if the collector current rises, the emitter current also rises and the increase in volts drop across the resistor pulls back the base voltage and thus reduces the collector current.

D.C. Feedback

This gives d.c. feedback, but a.c. feedback is avoided in the common-emitter configuration by bypassing the emitter resistor with a capacitor having a low reactance at the signal frequency. In the common-collector configuration the basic stage is subjected to full negative feedback, since the emitter resistor cannot be bypassed as it represents the signal load.

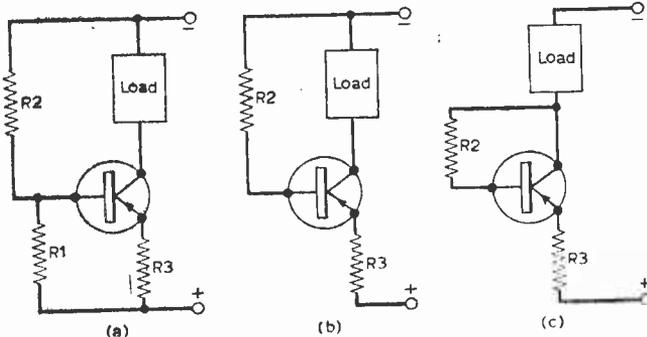


Fig. 4: Base biasing and stabilising arrangements; (a) base potential-divider R1/R2 (this is the most popular and effective), (b) with a single resistor to the supply line (stability poor) and (c) single base resistor returned to collector (improved stability).

Fig. 4(b) shows an alternative method of biasing the base by the use of a single, higher value resistor between base and the supply line. This, unfortunately, suffers from the misfortune of rather poor d.c. stability. A better arrangement is shown in Fig. 4(c), where the base resistor is returned to the collector end of the load instead of to the supply line.

Now armed with the basic facts of transistor circuits, we can investigate a few fault conditions.

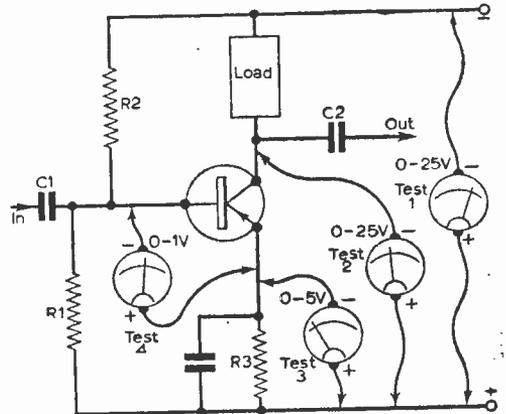


Fig. 5: Four major voltage tests which avoid breaking the circuits to insert a current meter. These are fully described in the text.

Let us suppose that we have a single stage amplifier, as shown in Fig. 5, that fails to work. What should be done first? The obvious thing, of course, is to ensure that the supply voltage is present. A voltmeter with a full-scale deflection of about 25V connected as for Test 1 in Fig. 5 will soon prove this possibility.

Open-circuit Collector Load

If the supply is correct, the negative lead of the voltmeter should be transferred to the collector as shown by Test 2 in the diagram. The load whether it be inductive or resistive, should have continuity, so this time we should read something a little

less than the supply voltage, depending upon the resistance of the load and on the current in it. If there is no collector voltage, then the fault is due simply to an open-circuit load.

If the collector voltage is about the same as the supply voltage and the load is resistive, this would indicate very little or no collector current. On the other hand, if the volts drop across the load is excessive one may conclude that the collector current is abnormally high. The best way of checking the collector current is to measure the voltage across the emitter resistor, as shown by Test 3 in the diagram.

If, for instance, the emitter resistor is $1,000\Omega$ and 2V is measured across it, then we know from Ohm's law (current equals the voltage divided by the resistance) that the emitter current is 2mA.

The collector current is a little less than this calculated value, of course, since base current also flows in the emitter resistor. However, as the base current is only a matter of $100\mu\text{A}$ or so, the current difference between emitter and collector can usually be ignored when making simple tests.

If there is zero volts drop across the emitter resistor, then either the transistor is faulty or there is no base current (always remember that there must be base current to produce collector/emitter current of measurable magnitude). It could happen, of course, that the emitter resistor bypass capacitor has a short-circuit, but this is unlikely.

How, then, would one ascertain whether the trouble lies in the transistor or in the base bias circuit? One way would be to test the transistor either on a tester or by substitution. This is a time-consuming exercise and is not always easy on a densely-mounted printed circuit board.

There is also the danger of ruining the transistor or nearby components by excessive and prolonged heat from the soldering iron. By far the best idea is to ensure that the transistor is faulty *before* contemplating its removal from the circuit.

Final Test

If we have followed all the tests up to date, a final test, shown as Test 4 in Fig. 5, should verify the matter one way or the other. Here we are measuring base voltage pure and simple relative to the emitter. The voltage will be very small, for it needs only a fraction of a volt to give a base current of $100\mu\text{A}$ or thereabouts.

However, if there is a deflection on the test meter, one can be reasonably sure that the lack of collector current is due to transistor fault, as distinct from a fault in one of the associated components.

There are two important points. One is that the polarities given in Fig. 5 are for a p-n-p transistor. With a n-p-n transistor, the tests would be the same but the meter polarity would need to be reversed. The second, concerns test meter application and sensitivity.

Voltage and current transients can spoil a good transistor, so to avoid such happenings the meter should be connected and removed for the various tests with the circuit disconnected from the power supply. Also, the very small voltages, especially emitter and base voltages, call for a test meter with a full-scale deflection not exceeding about 2.5V. A f.s.d. of 1V is to be preferred.

It is important that the meter has a sensitivity of at least, $10,000\Omega/\text{V}$, otherwise the loading effect of the connected meter will disturb the circuit voltages and probably lead to incorrect interpretations.

So far we have considered very low or zero voltage across the emitter resistor. What do we do if the voltage here is abnormally high? It is true that this condition does arise, and an abnormal voltage on a small transistor would be considered in excess of that produced by a maximum current of 2mA.

For example, if 4V is measured across a $1,000\Omega$ emitter resistor, the current would be 4mA, which is abnormally high for a small signal transistor.

High Base Current

This condition can be brought about by two major factors. One is excessive leakage in the transistor itself and the other a too high value of base current. Thus, it would be best to check first on the base voltage, as in Test 4, Fig. 5.

Make sure that the meter clip is actually contacting the base wire, for should the base end of R1 develop a dry joint on the printed wiring, the meter connected to that point would register zero volts, when in actual fact the base of the transistor proper would be highly negative. This is because the potential-divider effect would be destroyed (with R1 disconnected from the base wire) and base current would be limited only by the value of R2. It would thus rise to a far higher value than is normal when held down by the connected R1.

This, incidentally, is a frequent cause of high emitter current, not so much by R1 actually going open-circuit but by a dry-point developing at one end.

Capacitor Leak

It sometimes happens that the base and collector potentials are affected by a leak in the input or output coupling capacitors—C1 and C2 respectively in Fig. 5. This can be proved easily enough simply by disconnecting one end of the component and measuring the electrode voltages again.

A significant difference between the original reading and that made with the coupling capacitor disconnected, should lead to replacement of that capacitor. In audio circuits electrolytics are used extensively in these positions, and these tend to leak with age or when connected round the wrong way.

With p-n-p transistors, the negative side of an interstage coupling capacitor should be connected to the collector of the preceding transistor and the positive side to the base of the following transistor. The polarity is reversed, of course, with n-p-n transistors.

Self-oscillating Mixer

Basically, the majority of transistor stages can be resolved to that in which the tests are shown in Fig. 5. Fig. 6 gives the basic circuit of a self-oscillating mixer, as is found in most transistor portables. This has all the basic features. We have the base potential-divider comprising R1 R2, the emitter

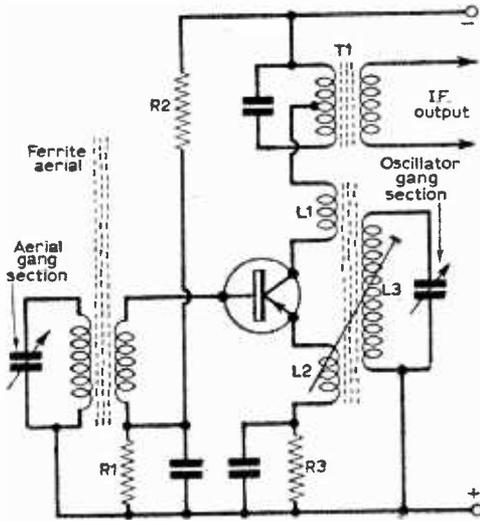


Fig. 6 (left): Basic self-oscillating mixer, as used in the majority of transistor portables.

resistor R3 with its bypass and the collector load which, in this case, consists of L1 and the primary of the i.f. transformer T1.

This, then, amplifier-wise, is a common-emitter circuit with the aerial signal applied to the base. Both the collector and emitter are loaded by L1 and L2 of the oscillator coil respectively. Positive feedback is thus applied from the collector to the emitter, causing the stage to oscillate. The difference-frequency (that is, the i.f.) is developed across the i.f. transformer which also acts as a second load in the collector circuit.

The transistor is biased by R1/R2 to approximate class A conditions, but when oscillation commences the transistor is driven towards class B conditions. This is because the base/emitter junction of the transistor rectifies the oscillatory signal.

Oscillator Test

Test 3 of Fig. 5 would give a slightly higher reading when the stage is oscillating than when it is quiescent. Here, then, is a test for oscillation. If there is a small decrease in voltage across the emitter resistor when the oscillator gang section of the tuning capacitor is shorted, then one can be sure that the stage is oscillating, at least.

By following the reasoning given in this article

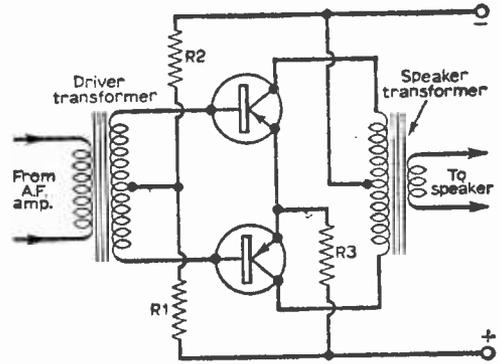


Fig. 7: The basic class B output stage.

almost any transistor circuit fault can be diagnosed without having a great deal of experience in the servicing of transistor equipment.

Output stages have the same basic set-up, but here it is usual to find them biased towards class B conditions. Fig. 7 reveals a typical class B output stage, in which R1 and R2 form the potential-divider which biases both transistors and R3 is the common-emitter resistor. The bases are biased not exactly to cut-off, since this produces an unpleasant noise, called "crossover distortion", but to a small quiescent current.

Note that the emitter resistor is not bypassed in this circuit, and a thermistor may be employed instead of an ordinary resistor to enhance the thermal stability. The voltage across this component would normally be very low at zero signal due both to the low resistive value and the small quiescent current. However, the current rises to high values, as does the voltage across the emitter element, with increase in sound output.

Distortion

Excessive distortion can be caused by (i) unbalance in the transistors, (ii) incorrect biasing (due, for instance, to alteration in value of R1 or R2) and (iii) low battery voltage. ■



P.W. Film Show

as a reader of "Practical Wireless" ...

YOU ARE INVITED to attend this annual event held in collaboration with Mullard Limited at Caxton Hall, Westminster, on February 5th. The programme this year includes "Electromagnetic Waves" and "The New Panorama Tubes".

Send NOW for your free ticket to the "Practical Wireless" offices, enclosing a stamped addressed envelope.

PRESELECTOR & B.F.O. UNIT

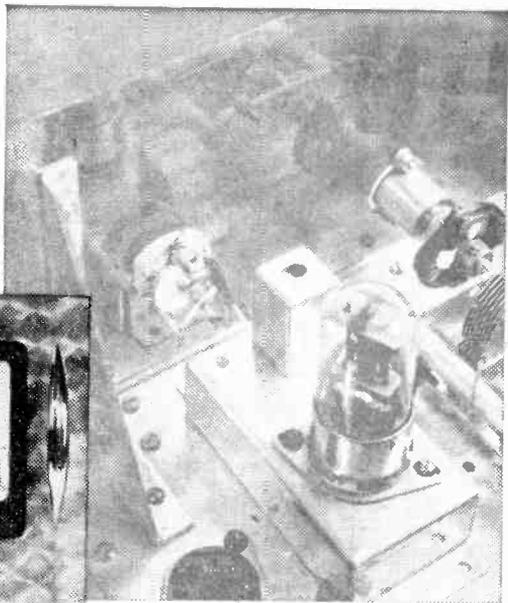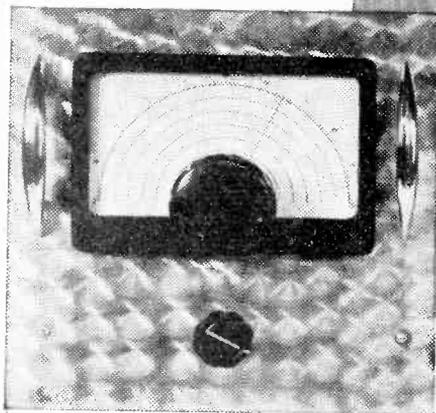

FOR THE BEGINNER

IN the December, 1964, issue of PRACTICAL WIRELESS the author described the construction of a short wave superhet receiver particularly suited to the beginner. The receiver has now been in use for several months and has given an extremely good account of itself. In the interests of simplicity several desirable features were omitted from the original receiver. The chief

among these were a stage of radio frequency amplification prior to the frequency changer and a beat frequency oscillator (b.f.o.) to enable continuous wave (c.w.) transmissions to be received.

The author has now incorporated these features in the original design and achieved a worth-while increase in performance. For the benefit of the

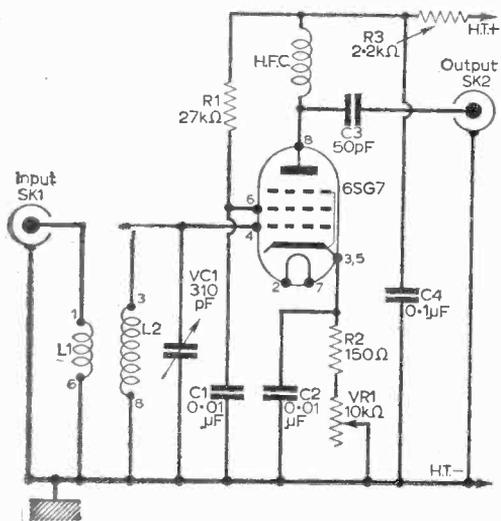


Fig. 1: The preselector unit circuit diagram.

COMPONENTS LIST

Resistors:

- R1 27k Ω R3 2.2k Ω
 R2 150 Ω
 All 1W carbon
 VR1 10k Ω w.w. potentiometer

Capacitors:

- C1 0.01 μ F tubular
 C2 0.01 μ F tubular
 C3 50pF silver mica
 C4 0.1 μ F tubular
 VC1 310pF (Jackson E1)

Miscellaneous:

- VI 6SG7
 L1, L2 Aerial coil, Denco Maxi-Q, Blue,
 Ranges 3, 4, 5
 SK1, SK2 Coaxial sockets

Two international octal ceramic valveholders. H.F. choke (Eddystone 1066). Universal chassis 8in. x 5in. x 3in. (Home Radio) and chassis top plate 9in. x 9in. 7-way tag strip. Flexible shaft coupler (Eddystone 50), dial (Eddystone 598), handles, knob, etc.

beginner and particularly for those who built the receiver a full description of these adjuncts is given.

The Radio Frequency Amplifier

For peak performance over 10Mc/s or so, a stage of amplification at the signal frequency is a desirable feature in any receiver. Not only does it improve the signal-to-noise ratio but also a distinct reduction in second channel interference is obtained. For a brief discussion of this effect the reader is referred to the original article in the December issue. Noise in a receiver arises not only from man-made and natural interference but also from the receiver itself. Generally most of the noise is contributed by the first stage of the receiver and then principally by multi-electrode valves such as the frequency changer. Since this noise in the preliminary stage is amplified by the later stages then in effect only this early noise is of importance. A weak signal presented to the mixer would obviously be largely masked by the noise arising in this stage. An improvement in the signal-to-noise ratio would therefore be

objective an increase in selectivity. Although the author has freely used both terms in the text the distinction should be borne in mind.

The r.f. amplifier described in this article enhanced the performance of the original receiver, particularly on the 14 and 30Mc/s bands. With the amplifier in circuit hitherto weak signals were easily resolved.

Circuit Description

The circuit diagram of the instrument is given in Fig. 1. As will be seen, the circuit is quite simple and consists of a single-ended semi-variable mu pentode which is a 6SG7, used in conjunction with the Denco series of octal-based plug in coils. Tuning of the unit is by means of a 300pF variable capacitor C1. Since this is the value of the variable capacitor in the main receiver, excellent agreement between the unit and receiver dial readings is obtained. The gain of the amplifier is regulated by VR1, which is a wire-wound component. The r.f. output is fed via C4 to the output socket SK2.

ER'S S. W. SUPERHET

H. WEBSTER

obtained by a stage of r.f. amplification prior to the mixer. Although such a stage is correctly called a preamplifier, frequently it is referred to as a preselector, the two terms being regarded as synonymous. A preamplifier increases the sensitivity of a receiver, while a preselector has for its

A variable mu 6SK7 may be used in place of the 6SG7 with a slight loss in gain. The author also found that with VRI set at maximum both the 6AC7 and 6SH7 types gave an extremely good performance. Both these types are, of course, non-variable mu.

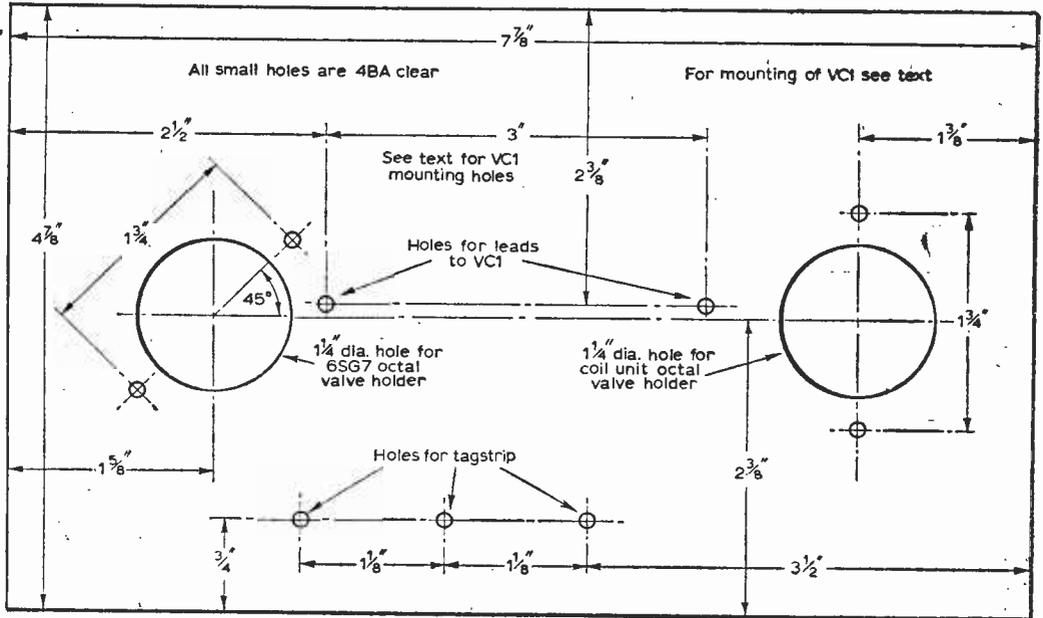


Fig. 2: Above-chassis drilling details for the preselector.

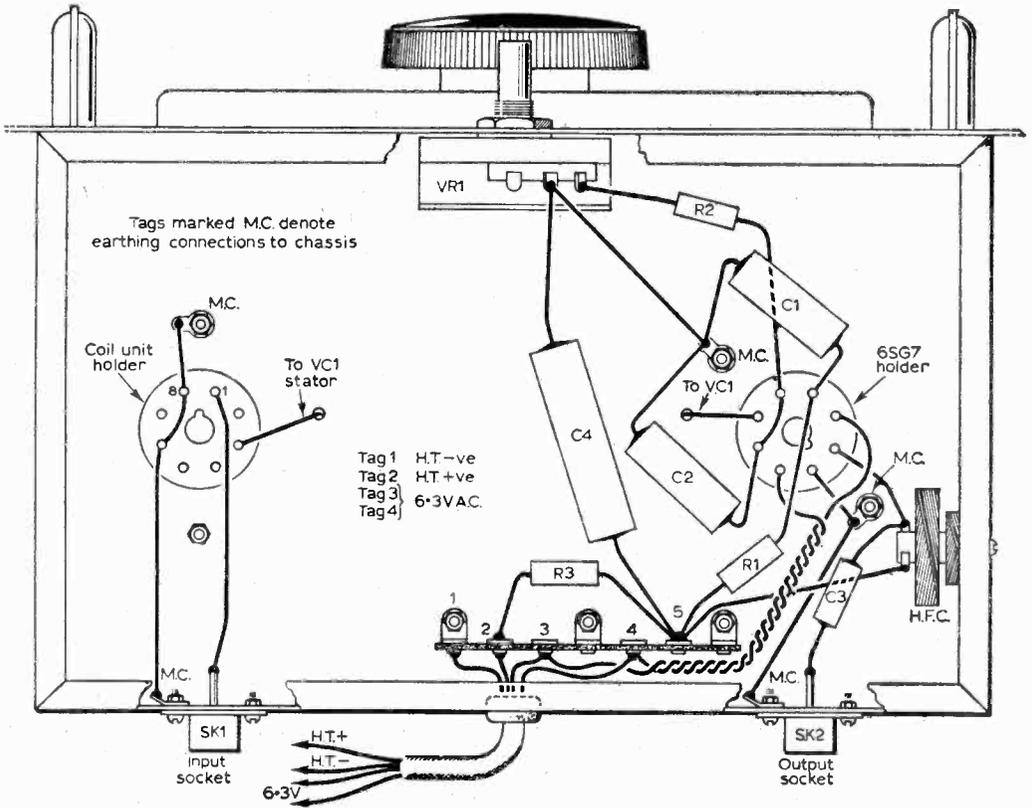


Fig. 5: Underchassis wiring diagram of the preselector.

the front panel are applicable to this dial.

When drilling of the front panel and chassis is complete the unit is temporarily assembled. The flexible coupler is placed on the dial shaft and the variable capacitor offered up to the coupler. Ensure that the capacitor shaft is in exact alignment with the dial spindle. Spacing washers under the mounting feet may be found to be necessary to achieve an accurate fit. When alignment is satisfactory the chassis holes are marked by pricking through the capacitor mounting feet. The panel and chassis may now be dismantled and the holes for the variable capacitor bored at the appropriate points. The fitting and wiring of components is facilitated by working on the dismembered chassis. The ceramic coil and valve holders are mounted, making sure the holders are correctly orientated. The mounting of the screening can for L1, L2 is described in the leaflet which accompanies the coils.


Great care is necessary when cutting the screening can base, since slight distortion of the thin gauge metal will cause an unsatisfactory fit. It is recommended that cutting of the base is done with a sharp razor blade of the singled-edged type.

As an aid to easy coil changing the author found that a preliminary polish of the threaded portions of the can and base with metal polish greatly facilitated the removal of the can. The remaining components are assembled as shown in Figs. 5 and 6. Since the frequency stability of the unit is important, all wiring should be carried out in heavy gauge copper wire. Wiring of the gain control, coaxial sockets and high frequency choke is completed when the chassis is assembled. A short piece of copper braid stripped from a piece of coaxial cable is used to earth the frame of the variable capacitor to the fixing screw on the holder of L1, L2. Do not rely on the fixing feet of the capacitor as being a sufficient earth.

When wiring is complete a range 3 coil is plugged into the holder and a check made of the resistance between h.t. positive and chassis. This, of course, is a wise precaution before connecting any new equipment to a power supply. A slight reading will be obtained initially due to C2 and C5. After a little time the meter should register practically infinite resistance. The unit is connected to the receiver power pack. In the author's unit an additional octal valve holder was

Fig. 6 (right): Layout and wiring above-chassis.

fitted to the power unit and the amplifier power leads terminated in an octal plug. The same wiring convention used in the main receiver was adopted for the wiring to the plug and socket. A short length of coaxial cable which terminates in a coaxial plug at each end is connected between SK2 and the main receiver aerial socket. A set of range 3 coils is plugged into the main receiver and the power unit switched on. When steady conditions are obtained the following voltage readings should be obtained. The author used a 10,000Ω/V meter set to the 1,000V range for h.t. measurement and the 10V range for bias voltage measurement.

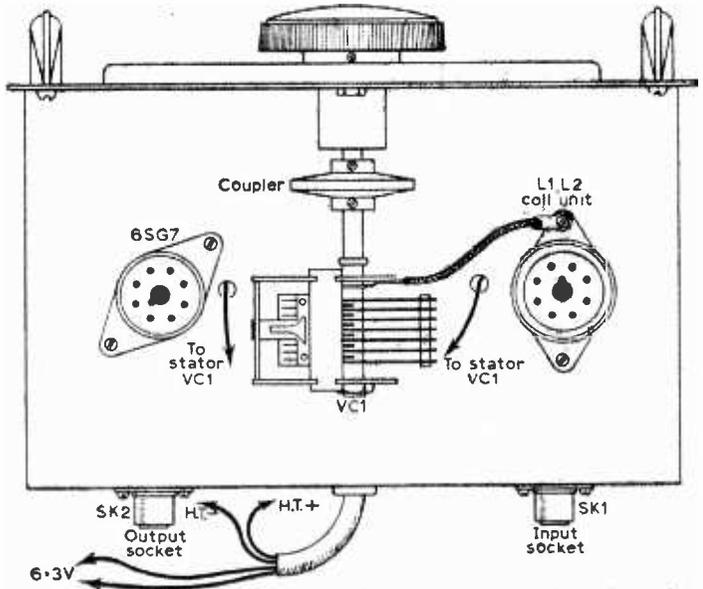

Voltage Readings at 6SG7. Gain Control Maximum:

Anode Pin 8	Screen Pin 6	Cathode Pins 3, 5
205V	110V	2.1V

The aerial is connected to SK1 on the amplifier and the amplifier and receiver dials set to 85°. After setting the gain control to maximum the iron core of L1, L2 is adjusted until a marked increase in noise level occurs. The core of L1, L2 may now be secured either with a blob of sealing compound or by running a 6BA nut down the free end of the thread. If this latter device is adopted the core must be held securely by a screwdriver while the lock nut is tightened.

The remaining coils (ranges 4 and 5) are dealt with in a similar fashion. It will be found that

simultaneous adjustment of the unit and receiver is very simple. Over a small range of frequencies such as an amateur band the amplifier may be peaked in the centre of the band and fine tuning done on the main receiver. Slight adjustment of the amplifier will only be necessary at the band edges.

With VR1 set for maximum gain it may be found that oscillation occurs on the highest frequencies. A slight reduction in the setting of VR1 will therefore be necessary. The author found that the unit was quite stable and no trouble should be experienced on this score. If the constructor encounters this effect a 10Ω resistor wired in series with the grid leak of the 6SG7 should provide a cure. This resistor should be mounted as near as possible to the grid pin.

NEXT MONTH - THE B.F.O. UNIT

Now read these two great February issues

Practical Television ★

- CLOSED CIRCUIT TV—a new series for the experimenter.
- VIDEO A.G.C. SYSTEMS—the whys and wherefores.
- RESONANT LINES INSTEAD OF INDUCTORS.
- PLUS—Regular DX TV features, Your Servicing Problems Solved and other articles.

ON SALE JANUARY 21st

ON SALE JANUARY 14th

- LOW POWER GUITAR AMPLIFIER—3½W, two channels.
- REMOTE BABY SITTER—transistorised microphone amplifier and relay unit. Automatic break-through on radio or TV receiver.
- PLUS—The Colour TV Controversy, The Hall Effect and other features.

★ **Practical Electronics**

“WALKIE-TALKIES”

A CLARIFICATION OF THE POSITION

FOLLOWING our recent editorial comments on the subject of amateur radio pirates, which touched upon the question of the various walkie-talkie transceivers being sold in this country, we feel it would be helpful both to readers of this magazine and to advertisers to print below a communique issued by the GPO. This makes clear any doubts which may exist concerning the use of such equipment.

“WALKIE-TALKIES”

Any use of radio communication in the United Kingdom must be licensed by the Postmaster-General, and the Post Office has recently conducted successful prosecutions for the unlicensed use of “walkie-talkie” radio equipment operating on frequencies around 27.12Mc/s. It may not be generally known that the Postmaster-General will not license the transmission of *speech* on these frequencies as the band has been designated for industrial, scientific and medical use.

Transistorised transmitter/receivers are also available working on slightly higher frequencies, e.g. 28.5Mc/s, but this frequency falls in one of the bands assigned for use by licensed radio amateurs. Before an amateur licence is granted the applicant has to pass the Radio Amateur (Technical) Examination and the Post Office 12-words-per-minute Morse sending and receiving test.

Dealers would therefore be well advised to bear in mind, when offered “walkie-talkie” equipment using a frequency of 27.12Mc/s or thereabouts, that the Post Office will not issue licences to purchasers of this equipment and any use, including that for demonstration purposes, without a licence would be contrary to the law. Furthermore, equipment operated by licensed amateurs in the 28.0—29.7Mc/s band must be capable of operating within the terms of the Amateur (Sound) Licence—for example, a satisfactory method of frequency stabilisation must be employed in the sending apparatus and frequency measuring equipment must be provided capable of verifying that the sending apparatus operates within the frequency band of 28.0—29.7Mc/s.

Facilities are available for private mobile radio services using speech in the 80, 160, 170 and 460Mc/s bands and suitable equipment which conforms to the relevant Post Office specification can be obtained through the trade.

It is also worth mentioning that most of the ex-Service mobile radio equipment on the market operates on frequencies not available for private mobile radio services in the United Kingdom and could not be adapted to operate satisfactorily within the narrow v.h.f. channel available. The use of such equipment is therefore not permitted by the Post Office on private mobile radio services.

On the Short Waves

—continued from page 953

9X5GG/P, K4ASR/MM, WA2EJZ/M, W1EQP/4, VK2AHT, OX3JD, ZB1RS, EL1H, OX3LP, K1JTN/P4, 5H3JR, ZB1RM, ZS6U, CR7CO, all s.s.b. or a.m.

A. H. Trickey (Bristol) has an R208 and on erecting a 20m dipole found he only had a 15m garden, so a “bit” was lopped off each end. Although it now resonates at about 17Mc/s and is bridged across for other bands, 21Mc/s proved lively with F5BV, G3OYF, W5PFY/MM, W3UGW, WA4FWN, W3KFK, PY1SZ, W4SUF, G5FS, KV4CX, W1BNH/MM, OH55M, YO2DZ, UA3KND, W2AWD, K3CMH, W1NRK, K4BIY, W2WLI, W2JY, W1ZER, W2KLN and W4ZLB.

E. Conway (Exeter), using the antenna I described in the November issue, heard PJ2NA and VP7NT in Nassau. M. Opie (Dorset) uses a domestic receiver, HMV model 511446, with an end-fed long wire. A one and a-half hour session one Sunday raised WA4TLI, WA4SAN, W4TUQ, W2BLQ, K1IJF, K3MBF, WA0HHX, all on

21Mc/s. While on 14Mc/s: OH5NQ, IIPAD, VE3ATU, TF3WJC, W8GZL, W4BBW, WASKBO, WB2LRN. A week later another period of one and three-quarter hours on 21Mc/s: KV4CX (Virgin Islands), EL5LA, ON4PH, W8RLT, K2JDW, K3HQM, and on 14Mc/s: IIVK, IIRT, OH5RZ, VO1VR, VE2AKZ.

In General

W1BB is definitely “at it” on 160m and if you are set on hearing something special on top band then the early mornings are well worth a try.

Gough Island is reported active under a ZD9 call sign and there is a lonely soul in Antarctica signing OR4VN. If you should hear UA1KED don't pass him over as just another Russian station—he's located in Franz-Joseph Land.

Contest enthusiasts have the affiliated societies contest on January 23rd-24th and on January 30th-31st, the ether will really be humming for this period with three contests. There's a C.W. contest on 2m, while at the other end of the scale is the CQWW 1.8Mc/s contest. The French REF contest C.W. section is also on for Morse fans, so all in all this period should give SWLs quite a busy period.

PREPARING R.A.E. FOR THE

BRIAN ROBINSON.

4: IMPEDANCE, RESONANCE—COUPLED CIRCUITS

4.1 Impedance

If a circuit contains not only resistance but also reactance (either capacitive or inductive) the combined effect of the two is called *impedance*. Although impedance strictly refers to a combination of resistance and reactance, the terms "resistive impedance", "capacitive impedance" and "inductive impedance" are often met. Impedance is represented by the letter Z.

4.2 Reactance and Resistance in Series

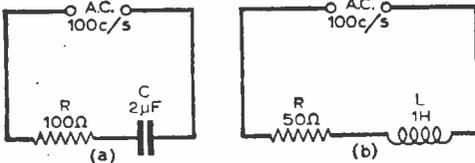


Fig. 30—Resistance in series with (a) capacitance and (b) inductance.

When reactance and resistance are connected in series, as shown in Fig. 30, the impedance will be given by—

$$Z = \sqrt{R^2 + X^2}$$

—where X is either the reactance of the capacitance in Fig. 30a, or the reactance of the inductance in Fig. 30b.

To find the impedance of the series circuit in Fig. 30a, firstly find the reactance of the capacitance—(f in cycles per sec. and C in farads)

$$X_c = \frac{1}{2\pi f C}$$

$$= \frac{1}{6.28 \times 100 \times 0.000002}$$

$$= 796 \Omega \text{ (approx.)}$$

Therefore the impedance Z equals—

$$Z = \sqrt{R^2 + X_c^2}$$

$$= \sqrt{100^2 + 796^2}$$

$$= \sqrt{643,500}$$

$$= 802 \Omega$$

or in Fig. 30b firstly find the value of the inductive reactance—(f in cycles per sec. and L in henrys)

$$X_L = 2\pi f L$$

$$= 6.28 \times 100 \times 1$$

$$= 628 \Omega$$

Therefore $Z = \sqrt{R^2 + X_L^2}$

$$= \sqrt{50^2 + 628^2}$$

$$= \sqrt{396,870}$$

$$= 630 \Omega$$

(Remember that in a series reactance/resistance circuit where two or more reactances are connected in series the total reactance is)—

$$X = X_1 + X_2 + X_3$$

4.3 Resistance, Capacitance and Inductance in Series

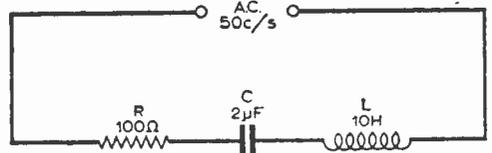


Fig. 31—Inductance, capacitance and resistance in series.

When resistance, inductance and capacitance are connected in series as shown in Fig. 31, the impedance of the combination will be given by—

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

For example, in Fig. 31, the value of X_C is 1,592 Ω and that of X_L is 3,140 Ω ,

Therefore $Z = \sqrt{100^2 + (3,140 - 1,592)^2}$
 $= \sqrt{10,000 + 2,396,600}$
 $= 1,551 \Omega$

4.4 Resistance and Inductance or Capacitance in Parallel

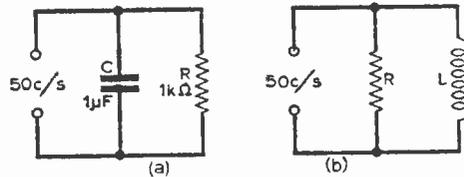


Fig. 32—Resistance in parallel with (a) capacitance and (b) inductance.

In the circuits shown in Fig. 32, the impedance is given by the expression—

$$Z = \frac{RX}{\sqrt{R^2 + X^2}}$$

—where X is equal to X_C in Fig. 32a and X_L in Fig. 32b.

In Fig. 32a, $R = 100 \Omega$ and $X_C = 3185 \Omega$.

Therefore $Z = \frac{100 \times 3185}{\sqrt{100^2 + 3185^2}}$
 $= \frac{318500}{3186}$
 $= 99.9 \Omega \text{ (approx.)}$

4.5 Impedance applied in Ohm's Law

Impedance, current and voltage can be connected by the form of Ohm's Law

$$I = \frac{E}{Z} \text{ or } E = IZ \text{ or } Z = \frac{E}{I}$$

For example, if in Fig. 32a the applied voltage was 250, the current flowing in the circuit would be given

SOUTH SUPPLIES

(ELECTRICAL LTD.)

Post orders to 95 Old Kent Road, London, S.E.1

95, OLD KENT RD., S.E.1
72, BOROUGH HIGH ST., S.E.1
90, HIGH ST., EDGWARE
17, WOODFORD AVE., ILFORD
291, HIGH ROAD, CHISWICK, W.4

BER 5810
HOP 2125
EDG 6751
GRE 4815

EECO Model S.E.37B

Push Button 20,000 O.P.V. Test Meter
D.C. Volts. 0-1
10-50-250-500-
1000
A.C. V.
-10-50-
250-500
-10000
D.C. C.
Current 0-
50A, 10mA,
50mA.
Resistance 0-5K Ω -500K Ω -5M Ω .
Inductance 50H-5000H. Capacitance
150pF-0.02 μ F. D.B. -20 Ω +22DB
20 Ω 351B. The simplest and most
efficient meter on the market at 42%
below its true value. **£5.15.0** P. & P.
value. 2/6



TECH. MODEL PV-58 VACUUM TUBE VOLTMETER

Finest design for stable and accurate measurement. 1% tolerance on all resistors. Large design 4in. x 200mA meter for accurate readings 11 meg. ohm input.
Ranges:
- D.C.V. 0-1 5-5-15-50-150-500-1500V.
+ D.C.V. 0-1.5-5-15-50-150-500-1500V.
A.C.V. 0-1.5-5-15-50-150-500-1500V. RMS
- 0-1 4-4-14-40-140-1400-1400 P.P.
Resistance: 2 ohms to 1000 megohm.
Decibels: -10dB to +60dB.
Operation: 220/240V A.C. Size 7 x 4 1/2 x 4in.

Each tester is supplied brand new and fully guaranteed complete with probe and operating instructions. The finest value in testers available at only **£12.19.6** P. & P. Complete 3/6 ex.

EECO Model S.E.550

100,000 O.P.V. PROFESSIONAL TEST METER
Highest accuracy
3% on D.C.V. -amps -ohms.
% on A.C.V.
D.C. Volts: 0-0.5-2.5-10-50-250 at 100,000 O.P.V.
0-500-1000 at 25,000 O.P.V.
D.C. Volts: 0-0.5-2.5-10-50-250-1000 at 12,500 O.P.V.
D.C. Amps: 0-0.01A at 500mV.
0-250mA-2.5mA-250mA-10 at 100mA.
Resistance: 0-20-2M-200K-20K.
100K-16K-160 Ω Centre Scale.
Decibels: -20 to 62 (0dB) -0.775V.
£7.19.0 P. & P. 3/-




EECO MODEL S.E.100 TRANSTORISED VARIABLE D.C. POWER SUPPLY

Meter Ranges: Voltage Range: Volt 0-20 V D.C. 0-20 Volts Current 0-200mA Variable 0-200mA Intermittent. 0-20V, 100mA continuously.
Impedance Source: Current position, 3.3 ohms. Voltage position 0.2 ohms.
Power Input: 220-240 V. Size 6 x 3 1/2 x 2in.
Fuse: 0.5 amp slow blow in 1A. circuit.
The extremely wide variable voltage range, low A.C. ripple and source impedance of the S.E.100 makes it a most satisfactory power supply to operate transistor radios, hearing aids, pre-amplifiers, instruments and other electronic devices under repair. The S.E.100 can be used in television and radio servicing, as an A.V.C. or voltage source as a D.C. filament supply, operate relay, recharge small batteries and light electro plating as in dentistry. **£6.10.0** P. & P. 4/6. Fully guaranteed and complete with test lead, croc. clips and operating instructions.

EECO MODEL S.E.200 MINI-LAB TESTER



This remarkable meter has seven test instruments packed into one pocket size case which can be taken and used anywhere.
Resistance Substitution 100 Ω - 1K Ω - 10K Ω - 100K Ω - 1M Ω . Capacitance Substitution .002mid-.005mid. - .02mid. - .1mid. and 1mid.
R.F. Signal Generator. Frequency fixed at 445 Kc. (adjustable to 700 Kc) output 35mV approx.
Audio Generator Frequency 400 c/s. Output 35mV approx. D.C. and A.C. Volts. 4 ranges 0-15-50-150-500 volts at 4000 O.P.V.
R.F. Field Strength Indicator Frequency range 1 to 140 Mc. Antenna 5 sections, length 10 1/2in. Size 6 x 2 1/2 x 3 1/2in.
The Mini-Lab is completely battery operated and suitable for quick checks in the service shop and Home Service calls **£8.19.6** each. Complete

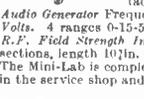


With Test Prods. and Battery Fully Guaranteed.

EECO Model MS4 FLOOR STAND

Height fully opened 55 1/2in Fully closed 38in. Three sections fully telescopic. 2 or 3in. mic. adaptor Price **£16.00** ea. P. & P. 3/-
Heavy cast iron base. Wonderful value.


MC 110 CRYSTAL MIC.

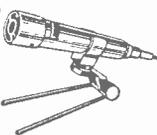26/6 P. & P. 2/6 with on/off switch and holder. Satin chrome finish.



NEW!!! NEW!!!

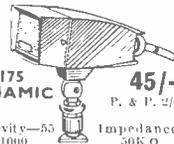CM61—High Impedance Crystal Mic. with built-in on/off switch. Complete with Table Stand, Plug-in Mic. lead and neck holder, all in a wonderful satin chrome finish. ★ VALUE AT **33/6** Plus 1/9 P. & P.



MD 175 DYNAMIC MIC 45/- P. & P. 2/- Sensitivity—55 Impedance 4dB at 1000 50K Ω non-directional, latest American design.

ACOS 45

Die cast, hand shaped body. Special offer 15/6 plus P. & P. 2/6.

MULTI METER BARGAIN. EECO Model 2205

4,000 O.P.V. on both A.C. and D.C. D.C. volts 0-5-20-125-500-2500, A.C. volts 0-10-50-250-1000. D.C. current 0-250A-0-250mA. Resistance 0-10 K Ω -0-1meg- Ω Decibels -20 to +22 dB. Meter size 4 1/2 x 3 1/2 x 1 1/2in. Complete with test prods and battery. Wonderful Value at **63/-** plus 3/- P. & P.

RONETTE BINOFLUID B.F.40 STEREO CARTRIDGE

Freq. Res. 30-12,000 c/s. Sensitivity 140m A/cm/sec. Load 1m Ω 100 pF Complete with Sapphire Stylus. OUR PRICE 12/6 each, P. & P. 1/-.

RONETTE STEREO O.V.S. TURNOVER CARTRIDGE

with 2 Sapphire Stylus. OUR PRICE 19/6 each. P. & P. 1/-.

SUN ACE




4 transistor new push button Super deluxe tape recorder circuit 4 transistor. Recording D.C. bias 1/2 track built in 2 1/2in. P.M. speaker. Recording time 17 mins. approx. on 200ft. tape. Batteries 1 U-2-1 1/2P3. Complete with crystal microphone, personal car phone, 200ft. tape and reel, spare spool carrying strap and batteries. Wonderful value. At only **£4.15.0**, plus 4/9 P. & P. Fully guaranteed.

MINIATURE PUSH-PULL AUDIO AMPLIFIER

4 Transistor Output 200 mW. Low and high gain inputs. To operate 5 Ω speaker. Wonderful value **31/6** P. & P. Complete with operating instructions.

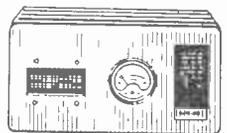A GENUINE 4 AMP BATTERY CHARGER for Only 49/6 P & P. 4/6



Made in England to our own specification and fully guaranteed. High-Low-Med. charge rate, 6V, or 12V. Selector Plug. 200/250V. Fuses Selector Plug. 1 amp Cartridge Fuse protection. Complete with mains lead charging lead and crocodile clips.

PERSONAL CALLERS ONLY

The very latest Super Slim Line Auto-changer Record Player. Built and ready to go. Incorporating the new B.S.R. 1 A25 Super Slim Deck in the latest design cabinet. 2" watt output with tone and Volume Controls. Fully Guaranteed **11 Gns.**

VANTONE MAINS RADIOS

5 valve superhet with built in Ferrite tuning bar. **£3.15.0** plus 3/9 P. & P. Fully Guaranteed.



This wonderful little radio will receive all stations on Med/wave band and clear line. Luxembourg. Ideal for bedrooms kitchens or as a second mains radio.

EHRECORDER



4 Transistor Tape Recorder. Easy to operate single lever function control. 200mW output complete with microphone—5in. Type—square. Personal expander and batteries. Wonderful value **£4.19.6** plus 5/- P. & P.

EECO 4-Ch. Transistorised MICROPHONE MIXER

49/6 P. & P. 2/6
Give all your recordings that professional touch. The Eeco mixer allows you to mix 4 signals such as—Mic-tape, records and tuner into a single output. Wonderful for groups, amateurs recorders, etc. Guaranteed to give hours of pleasure

FAMOUS MAKES AMPS & PRE-AMPS

at Vastly Reduced Prices
3/4 watts, **£4.15.0**. 4/5 watts, **£5.7.6**. 5/5 Stereo, **£11.5.0**. 10 watt with separate Pre-amp, **£14.3.6**. 30 watt, **£15.2.6**. 50 watt, **£20.14.3**. Tremolo Unit, **£3.15.6**. Tape Pre-amp, **£8.10.0**.

NEW not just 1 but 2 NEW NEW TUNER-AMPLIFIERS

model 127 Stereo £37.10.0

model 127 Mono £26.10.0




Armstrong

Optional case (both models)
TEAK & VINYL HIDE £3. 10. 0
For full details, technical specifications and
list of over 300 stockists, post coupon or
write mentioning PVW.2.65

Name

Address

PW.2.65

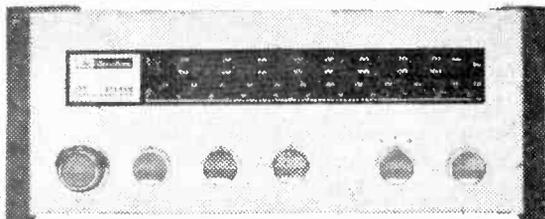

Wright + Conner

ARMSTRONG AUDIO LTD. WALTERS ROAD, LONDON N7

HOUSING HI-FI?

The Longfellow hi-fi cabinet measures 77 in. long. It takes records, turntable, tape-recorder, amplifier, tuner—all of your hi-fi set up in one superb cabinet!



Walnut or Mahogany 39 gns.
Teak 42 gns.

RECORD HOUSING

Write now for Catalogue of full range and nearest stockist.

(Dept. P.W.2), Brook Road, London, N.22
Telephone: Bowes Park 7487

LEARN ELECTRONICS AS YOU BUILD 25 CIRCUITS EXPERIMENTS TEST GEAR

including:

- MINIATURE CATHODE RAY OSCILLOSCOPE
- VALVE EXPERIMENTS
- BASIC AMPLIFIER
- BASIC RECTIFIER
- PHOTO ELECTRIC CIRCUIT
- TIME DELAY CIRCUIT
- SQUARE WAVE GENERATOR
- SIMPLE TRANSMITTER
- TRANSISTOR EXPERIMENTS
- BASIC OSCILLATOR
- ELECTRONIC SWITCH
- SIGNAL TRACER
- BASIC COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- MORSE CODE OSCILLATOR ETC., ETC.

This complete practical course will teach you all the basic facts of electronics by making experiments and building apparatus. You learn how to recognise and handle all types of components—their symbols and how to read a circuit diagram. You see how circuits are built and how they work BY USING THE OSCILLOSCOPE PROVIDED. Applications of all the main electronic circuits are demonstrated—radio reception and transmission; photo-electrics; computer basics; timers; control circuits; etc. including servicing techniques. **NO MATHS USED OR NEEDED. NO THEORY NEEDED. NO PREVIOUS KNOWLEDGE OR EXPERIENCE NEEDED.** Tutor service available. No extras needed—tools provided. Send now, for **FREE DETAILS** without obligation, to address below.

TO: LERNAKIT, Dept. K 10, RADIO HOUSE, 40 RUSSELL STREET, READING

Please send free details—

POST NOW

NAME

ADDRESS

by—

$$I = \frac{E}{Z} = \frac{250}{99.9} = 0.25 \text{ amps (approx.)}$$

4.6 Power Factor

In a circuit containing resistance and reactance, only the resistance actually consumes power. The *power factor* of a circuit in which an alternating current is flowing is the ratio of the *actual power* consumed to the *apparent power* consumed.

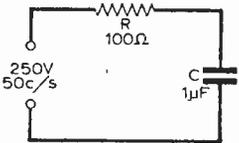


Fig. 33—Resistance and capacitance in series with a 250V a.c. supply.

In Fig. 33 the applied voltage is 250 and the impedance of the circuit is 3186 ohms. The current flowing in the circuit is given by

$$I = \frac{E}{R} = \frac{250}{3186} = 0.0638 \text{ amps.}$$

Therefore the *apparent power* consumed is

$$W = EI = 250 \times 0.0638 = 15.9 \text{ watts.}$$

Only the resistance actually consumes power however and this is given by

$$W = I^2R = 0.0638^2 \times 100 = 0.41 \text{ watts.}$$

Therefore the *power factor* will be—

$$\frac{\text{Actual Power}}{\text{Apparent Power}} = \frac{0.41}{15.9} = 0.026$$

The Power Factor may also be expressed as a percentage—and remembering that for a *purely resistive* circuit the power factor is 1 (or 100%)—the power factor in the above example would be 2.6%.

4.7 Resonance

The frequency at which the inductive reactance and capacitive reactance are equal, in a radio frequency circuit, is called the *resonant frequency*.

$XL = X_c$ substitute in the expres-

sion, $2\pi fL$ for XL and $\frac{1}{2\pi fc}$ for X_c and we obtain—

$$f = \frac{1}{2\pi\sqrt{LC}} \text{ where } f \text{ is in cycles per}$$

second, L is in Henrys and C is in Farads.

For radio frequency work it is often much easier to use the expression

$$f = \frac{10^6}{2\pi\sqrt{LC}} \text{ where } f \text{ is in kilocycles}$$

L is in microhenrys ($L \times 10^{-6}$) and C is in microfarads ($C \times 10^{-12}$). Resistance does not affect the resonant frequency of a circuit.

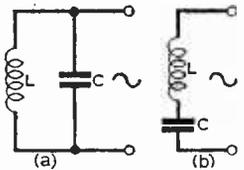


Fig. 34—Resonant circuits; (a) parallel and (b) series.

The above formulae for finding the resonant frequency of a circuit are true for both series and parallel circuits at the resonant frequencies—however the two circuits shown in Fig. 34 behave differently at frequencies other than the resonant frequency. The reader is urged to study further the differences between series and parallel resonant circuits and also to look into the *quality factor (Q)* of a coil or capacitance which is basically the ratio of the reactance of the component to its resistance.

4.8 Coupled Circuits

If energy from one circuit is transferred to a second circuit the two circuits are said to be *coupled*. Coupled circuits may be used also to match the impedance of one circuit to that of another so that maximum power can be transferred. The circuit receiving power is called the *secondary circuit* and that supplying power is called the *primary circuit*.

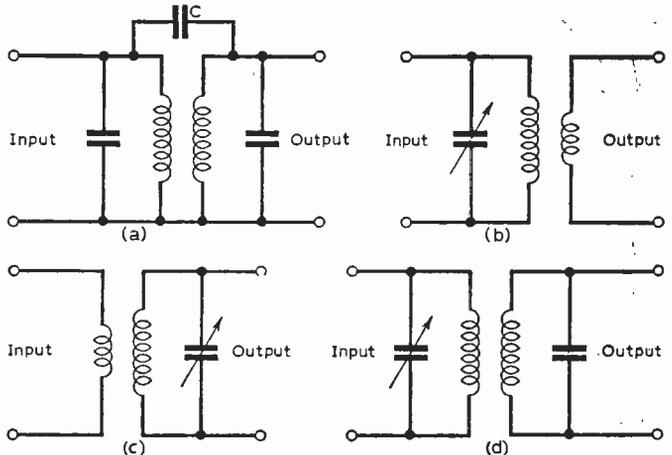


Fig. 35—Four examples of coupled circuits.

Four methods of coupling circuits are shown in Fig. 35. In (a) the capacitance C is used as a common feature to both circuits and therefore permits a transfer of power. In (b) the primary circuit only is

—continued on page 990

Hints for improved f.m.

BY K. ROYAL

NOW that it is becoming increasingly more difficult to use the medium-wave band after dusk, due to the rising whistles and "monkey chatter" from closely adjacent and "on-frequency" interfering stations, especially at the top end of the band, more and more serious listeners are turning their attention to the possibilities of achieving improved results on the f.m. (frequency modulation) band.

In the v.h.f. Band II spectrum—from 87.5 to 100 Mc/s—the BBC transmit at relatively high quality the Home, Light and Third programmes and also regional programmes in some areas. Under normal reception conditions these signals are totally immune from the interference troubles of the medium waves.

the f.m. service have been obtained by a little attention to detail and by one or two simple adjustments, which this article sets out to describe. Firstly, however, it should be remembered that the vast majority of the British Isles is now adequately embraced by the f.m. service, either from main transmitters or from booster or relay stations. Table I gives a complete list of such stations, existing and projected.

Signal Propagation

Secondly, to understand the v.h.f. system, an elementary idea of how the signals are propagated is desirable. Under normal conditions the v.h.f. signals from the transmitting aerial follow a very

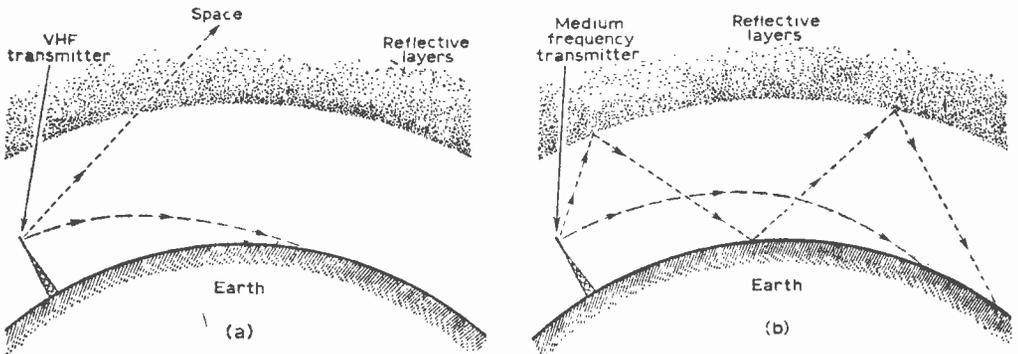


Fig. 1: Signal propagation. (a) Here the v.h.f./f.m. signal follows a slightly curved path from transmitter to set, while sky signals pass through the reflective layers. At (b) is shown that at medium frequencies the ground wave hugs the earth over a greater distance while the sky signals are reflected back to earth from the upper atmospheres. Thus, while the range of a v.h.f. signal is limited, medium frequency signals are propagated over far greater distances.

However, a listener going over to f.m. for the first time may be sadly disappointed in the results, for instead of the clear reception expected he may find the programmes badly disturbed by things like crackles from passing cars, by a peculiar warbling note effect marring the tuned programme, and in some cases by a distortion of a kind that leaves the impression of an incorrectly centred loudspeaker speech coil.

These apparent shortcomings, coupled with the possible difficulty of tuning in the required station, may cause the listener to abandon the f.m. service and resort back to the medium frequencies with the "monkey chatter" and whistles.

In the majority of cases of this nature investigated by the author, greatly improved results on

slight curve over the local surface of the earth, as shown in Fig. 1(a). This means that at distances exceeding the curved path length the receiver is virtually outside the range of the transmitter.

This gives the service area of a v.h.f. station which, rarely, for consistent reception, exceeds 50 to 60 miles from transmitter to receiver, though height of the receiving aerial above sea-level will, of course, have some bearing on this, as would be expected.

The v.h.f. service is thus a "local" service, for consistent use of listeners only within the range of the service area. This is the reason for the large number of transmitters required to cover the country as revealed in Table I.

Now, the signal propagation at medium

FOR PEAK PERFORMANCE AT LOW COST —

PICK CODAR AMATEUR RADIO EQUIPMENT



Advanced design and craftsmanship plus an unequalled reputation proved by the many hundreds of testimonials received from CODAR users is your guarantee of complete satisfaction. Only the best is good enough for CODAR—Mullard, Brimar, Jackson, Deneo, Electroniques, Thorn, A.E.I. are just some of the famous names built into CODAR equipment. CODAR-KITS are supplied with clear pictorial diagrams and easy to follow instructions—no technical knowledge or special tools are required for complete success. Build your Short Wave Station with CODAR-KIT's and enjoy peak performance and world wide reception previously possible only from much more expensive equipment.
For illustrated leaflets giving fullest details send 6d. in stamps.

CODAR R.F. PRE-SELECTOR. Will considerably improve the performance of any superhet receiver. Results are amazing. "Well worth the money."
MODEL P.R. 30. Uses EF83 Frame Grid tuned R.F. Amplifier and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12 M/A H.T. 6.3 volts. 3 amp L.T. Size 8 1/2 in. x 5 1/2 in. x 4 1/2 in. Ready built, complete with cables, plugs and instructions. £4.17.6. Carr. 3/-
MODEL P.R. 30X. Self powered version for 200-250 V. A.C. and also provides 25 M/A at 200V. H.T. and 6.3V. 1 amp L.T. for other accessories. £7.2.0. Carr. 3/-

CODAR "Q" MULTIPLIER. MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either speaking or rejecting a signal on AM, CW or SSB. Both PEAK and NULL functions tunable over receiver. I.F. passband. B.F.O. facility included. Size 8 1/2 in. x 5 1/2 in. x 4 1/2 in. Power requirements 180-250V. H.T. at 5 M/A 6.3V. 3 amp L.T. Ready built complete with cables, plugs and instructions. £8.15.0. Carr. 3/-
MODEL R.Q. 10X. Self powered version for 200-250V A.C. and also provides 25 M/A at 200V. H.T. and 6.3V. 1 amp L.T. for other accessories. £8.8.0. Carr. 3/-


CODAR A.T.5. 12 WATT 3 BAND TRANSMITTER. The newest, most compact transmitter for fixed or mobile use on 160/80 metres. "The tiny TX with the BIG voice." Size only 8 1/2 in. x 5 1/2 in. x 4 1/2 in. (Base area is less than two-thirds of this page.) High stability new-type calibrated V.F.O. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR-QOIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate/screen modulator. AM/CW switch and "Panic" key jack. Plug changeover for 8 or 12 volt heater supply. Ready built £13.10.0 Carr. 4/-
A.T.5 POWER SUPPLY UNITS. Type 250/S. For 200/250V. A.C. with Standby/Net/Transmit and aerial changeover switching, stabilised V.F.O. supply, neon standby/transmit indicator. £8.0.0. Carr. 5/- Type 12/MS 12V. Transistor power supply unit available shortly. (H.P. Terms Available)

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER
★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4 page instruction manual. PRICE 39/6. Carr. 2/6. Extra Coils 4/9 each. Instruction Manual only 2/- (credited on order). Electrical Bandsread available. Provision to add 2 transistor amplifier.

CODAR-KIT CR45 MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandsread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output, 3 watts for 2/3 ohm speaker. ★ Valve line up: ECC81, EL84, E220. **CODAR-KIT CR45** complete with valves, 3 coils (10-28, 25-75, 60-176 metres) and 11 page instruction manual (LESS Cabinet). £7.5.0. Carr. 4/6. **CR.45 CABINET.** 12 in. x 5 1/2 in. x 7 in. with sliding door for easy coil changing. 28/6. Extra coils 4/9 each. Instruction manual only 4/- (credited on order). (Can now be supplied ready built—price on request.) (H.P. terms available.)

CODAR-KIT CR 66 COMMUNICATION RECEIVER. The finest superhet kit ever offered. ★ Covers 540 Kc/s—30 Mc/s in 4 bands. ★ Separate electrical bandsread. ★ Factory aligned Coll unit and I.F. Transformers. ★ Regenerative I.F. stage for maximum gain and B.F.O. for C.W. reception. ★ Power output 3 watts for 2/3 ohm speaker.
★ Panel controls: Aerial Trimmer, A.V.C., Standby, Bandswitch, A.F. Gain, I.F. Gain, B.F.O., etc. ★ Valve line up: ECH81, EBF89, ECC81, EL84, E220, EM84. ★ Size 16 in. x 6 1/2 in. x 8 1/2 in. **CODAR-KIT CR 66** complete with 17 page instruction manual. £19.10.0 (Ready-built £22.10.0) Carr. 6/6 "S" Meter Model Kit £21.10.0 (Ready-built £24.10.0) Carr. 7/6 extra on all models. (H.P. terms available.) Instruction Manual only 7/6 (credited on order).

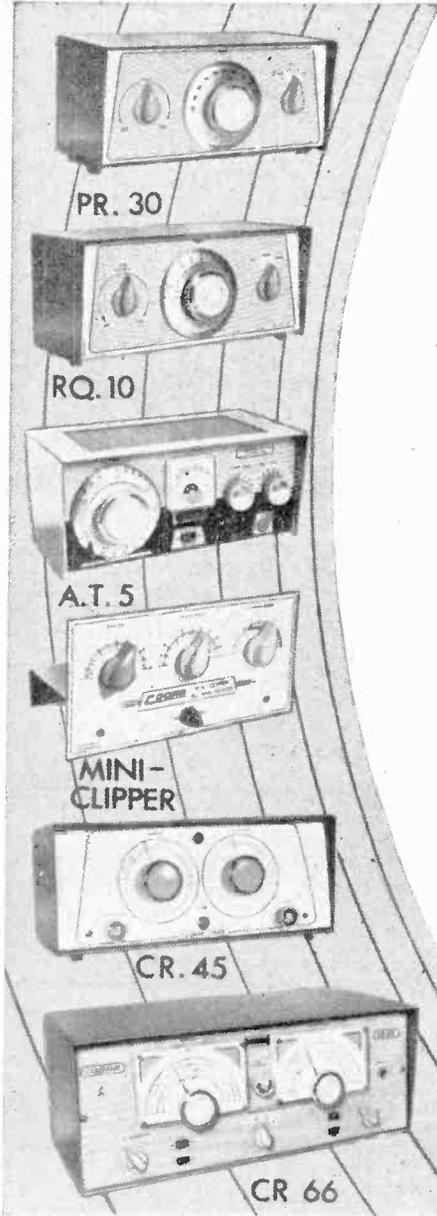AS EXHIBITED AT THE 1964 R.S.G.B. RADIO COMMUNICATIONS EXHIBITION




CODAR RADIO COMPANY BANK HOUSE, SOUTHWICK SQUARE, Southwick, Sussex. Tel. 3149

G3IRE G4HGQ

Canada: Codar Radio of Canada, Tweed, Ontario.

UNUSUAL SINGLE SPEAKER SYSTEM

A CONCRETE COLUMN

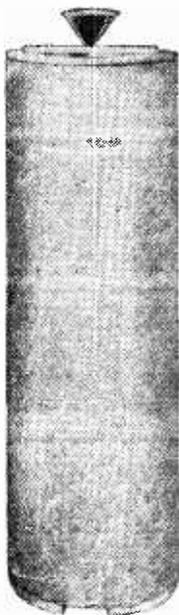

An inexpensive column speaker constructed from a concrete pipe and fitted with a good 8in or 10in. unit has attracted much interest and admiration because of its clean open sound. Complete kits of wooden fixtures are available including absorbent wadding and diffusing cone.

Price £3.15.0 for 8" model. Recommended 8" unit—Super 8/RS/DD £6.14.2 including purchase tax.

Price £4.18.0 for 10" model. Recommended 10" units—Super 10/RS/DD £10.18.8; Golden 10/RS/DD £7.17.5; 10" Bronze/RS/DD £4.12.9. Prices include purchase tax.

Suitable concrete pipes can be purchased from builders' merchants at about 12/6 and 17/6.

Descriptive leaflet free on request from:



WHARFEDALE WIRELESS WORKS LTD.
 IDLE BRADFORD YORKSHIRE
 Grams: Wharfedel Bradford
 Phone: Idle 1235/6

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1B5, 1T4, 3B4, 3V4, DAF91, DF91 DK91 DL92, DL94: Set of 4 for 18/-. DAF90, DF90, DK90, DL90: 4 for 28/6.

1A7GT	7/6	7H7	8/-	DF33	8/-	ECL82	7/-	PC95	6/9	U47	8/6
1D5	6/6	7C5	7/9	DF91	2/6	ECL86	8/-	PC97	7/-	U48	8/6
1H3GT	8/6	7C6	7/6	DF96	6/-	EP39	6/6	PC94	8/6	U49	8/-
1N3GT	8/-	7H7	6/9	DH76	3/6	EP41	6/6	PCCS9	6/6	U52	4/6
1R5	4/6	7V4	6/-	DH77	3/6	EP42	4/6	PCF80	6/6	U54	8/9
1S5	3/6	1A4T7	3/9	DH81	12/6	EP80	4/3	PCF82	6/6	U78	8/9
1T4	2/6	12AU7	4/9	DK32	8/-	EP85	6/-	PCF84	7/9	U191	9/-
2P	18/6	12AX7	4/9	DK91	4/8	EP86	6/6	PCF86	9/6	U261	8/6
3A5	6/9	12K7GT	4/9	DK92	6/8	EP89	4/8	PCF85	9/6	U291	9/-
3Q4	4/10	12K9GT	3/9	DK94	6/8	EP91	2/6	PCF82	6/6	U301	12/-
3B4	4/9	12Q7GT	4/9	DL33	7/8	EP92	3/9	PCF84	9/-	U301	16/9
3V4	5/6	19B86G	6/9	DL35	6/8	EP188	7/6	PCF84	7/6	U4020	8/9
5U4G	4/6	20L1	12/6	DL92	4/8	EL38	11/6	PCF86	8/6	U4C80	8/9
5Y3GT	5/-	20P4	13/6	DL84	8/8	EL41	7/6	PEN44	6/6	U4F42	8/-
8Z49/GT	8/-	20P5	11/9	DL66	6/-	EL44	4/9	PEN383	8/8	UBC41	7/8
8AL5	2/-	25L6GT	4/9	EABC80	6/-	EL65	6/6	PEN3920	8/8	UBC81	8/8
8AQ5	6/-	30C18	9/8	EAF42	8/-	EM34	7/11	10/-	UC92	8/6	
8AT6	3/6	30P11	9/8	EB41	4/-	EM80	6/8	PEN4VA	UBF80	8/6	
8BA8	6/-	30L15	9/8	EB91	2/-	EM84	7/8	18/6	UBF89	6/8	
8B56	5/6	30P4	13/6	EB38	3/-	EM84	6/8	PEN38C	UC084	8/-	
8BG5G	12/6	30P10	13/6	EB41	7/8	EM87	7/8	10/-	UC085	8/6	
8BH6	5/-	30P11	8/-	EBF80	6/-	EY31	6/-	PL36	UCF80	8/6	
8B16	5/6	30P11	10/6	EBF83	7/6	EY46	8/6	PL81	UCR42	7/8	
8F13	3/6	30P11	12/3	EBF89	6/-	EZ40	8/8	PL82	UCR81	7/8	
8F14	9/-	35A5	14/6	EPL21	10/6	EZ41	7/8	PL88	UCU42	7/8	
8J7G	4/6	35L0GT	6/8	ECC35	4/9	EZ80	4/-	PL84	UCU88	8/9	
8K7G	1/6	35Z4GT	4/11	ECC40	6/9	EZ81	4/6	PL23	UF41	7/8	
8KGT	4/-	38KU	8/8	ECC81	3/9	FW4/800	6/3	PY82	UF42	4/9	
8E8G	4/3	AGV/P2	ECC82	4/9	G753	14/6	EY46	8/8	UF49	6/8	
8K8GT	7/8	12/6	ECC83	7/-	48/7	8/8	PY80	8/8	UL1	7/-	
8P4	9/8	AZ31	6/6	ECC84	6/8	KT82	4/6	PY81	8/9	UL4	15/-
8Q7G	4/9	B36	4/6	ECC35	6/8	KT76	8/-	PY82	8/8	UL44	7/8
8Q7GT	7/9	CCH35	12/9	ECP50	6/8	ME1400	18/-	PY83	8/9	UY91	7/8
8L7GT	4/9	ECL33	6/8	ECP82	6/8	MU14	5/-	PL38	UY91	8/9	
8N7GT	3/9	CV1	18/6	ECP81	10/8	VS/PEN	8	PY80	UY91	4/9	
8V8GT	3/9	DAC32	8/3	ECH35	6/-	12/6	TH310	6/8	UY95	5/-	
8V6GT	6/6	DAF91	3/9	ECH42	8/8	N18	4/10	TR288	W78	8/8	
8X4	3/8	DAF96	6/8	ECH81	6/-	N108	10/8	U35	W77	8/8	
8X3GT	6/8	DCC90	6/9	ECL80	6/8	OD3	4/8	U26	W79	18/8	

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL, LONDON N.16
 STA. 4587

Post 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d extra.
 Ans C.O.D. Parcel 4/8 extra.

LISTEN TO THE WORLD ON TELSTAR OUR I-VALVE



SHORT WAVE RADIO

Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 meters. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. Total Building Costs 35/- P. & P. 2/-.

All parts available separately

READY TO USE POCKET RADIO



P. & P. 2/- 9/11
 Covers Medium waveband. No batteries needed. Complete with earpiece.

R.C.S. PERSONAL SET

Designed for personal listening without disturbing others. Supplied complete with battery and earpiece—no extras to buy! Sensitive one transistor diode circuit gives quality reproduction over medium wave band. Attractive case with large tuning dial. Ideal for use as tape tuner. Size only 3 1/2 x 2 1/2 x 1 1/2 in. ONLY 27/6 P. & P. 2/-.



BATTERY ELIMINATORS

The ideal economical and safe way of running any TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. requiring voltages shown. Types Available: 9 v., 6 v., 4 1/2 v. (single output). Size 3 1/2 x 3 x 1 in. PRICE 39/6 each. P. & P. 2/8. 9 v. + 9 v., 6 v. + 6 v., 4 1/2 v. + 4 1/2 v. (Two separate outputs.) Size 3 1/2 x 3 x 2 in. PRICE 42/6 each. P. & P. 2/8. (Please state output required.)

All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

FOR THE CONSTRUCTOR

Easy to build CRYSTAL RECEIVER, 8/8 P. & P. 2/-
 Easy to build PERSONAL SET with earpiece 27/6 P. & P. 2/-
 Easy to build 3-TRANSISTOR SET with speaker. 37/6 P. & P. 2/-.

All parts available separately

R.C.S. PRODUCTS (RADIO) LTD.

11 Oliver Rd., London, E.17. (Mail Order only)
 Export Trade Enquiries Invited

TABLE I

Station	Main	Relay Booster	Frequency Mc/s		
			Light	Third	Home
Ashkirk (S.E. Scotland)		*	89-1	91-3	93-5
Blaen-plwyf (W. Wales)	*		88-7	90-9	93-1
Divis (Belfast)	*		90-1	92-3	94-5
Douglas (Isle of Man)	*		88-4	90-6	92-8
Dover	*		90-0	92-4	94-4
Enniskillen		*	88-9	91-1	93-3
Fort William		*	89-3	91-5	93-7
Haverfordwest (Pembrokeshire)		*	89-3	91-5	93-7
Holme Moss (Huddersfield)	*		89-3	91-5	93-7
Kinlochleven		*	89-7	91-9	94-1
Kirk o' Shotts	*		89-9	92-1	94-3
Les Platons (Channel Islands)	*		91-1	94-75	97-1
Llanddona (Anglesey)	*		89-6	91-8	94-0
Llandrindod Wells		*	89-1	91-3	93-5
Llangollen (N.E. Wales)	*		88-85	91-05	93-25
Londonderry		*	88-3	90-55	92-7
Meldrum (Aberdeen)	*		88-7	90-9	93-1
North Hessary Tor (S. Devon)	*		88-1	90-3	92-5
Oban		*	88-9	91-1	93-3
Orkney	*		89-3	91-5	93-6
Oxford		*	89-5	91-7	Mid 93-9 West 95-85
Peterborough	*		90-1	92-3	94-5
Pontop Pike (Newcastle)	*		88-5	90-7	92-9
Redruth (Cornwall)		*	89-7	91-9	94-1
Rosemarkie (N. Scotland)	*		89-6	91-8	94-0
Rowridge (Isle of Wight)	*		88-5	90-7	92-9
Sandale (Carlisle)	*		88-1	90-3	Nth 94-7 Scot 92-5
Sheffield		*	89-9	92-1	94-3
Skye		*	—	—	93-9
Sutton Coldfield	*		88-3	90-5	92-7
Tacolneston (Norwich)	*		89-7	91-9	94-1
Thrumster (Wick)	*		90-1	92-3	94-5
Wenvoe	*		89-95	96-8	Welsh 94-3 West 92-125
Wrotham	*		89-1	91-3	93-5

NOTE—"Relay Booster" indicates a transmitter which derives its signals "off-air" from a main transmitter and re-radiates them on different frequencies into the "screened" area locally. Stations indicated "Main" may be high or low power transmitters.

frequencies differs substantially from that at v.h.f. as shown in Fig. 1(b). Here one transmitter covers large slices of country because the signal not only follows a curvature closely analogous to that of the earth itself for a relatively greater distance than the v.h.f. signal, but also because the signal rises skywards and is reflected earthwards by "reflective" layers in the ionosphere and troposphere so that great laps of the earth are embraced.

The reflective effect is influenced by time of the day (and night), and after dusk distant stations which do not cause interference during the hours of daylight start putting strong signals into receivers which are tuned to local stations having frequencies close to or the same as those of the interfering stations.

There is nothing that can be done about this by the listener: it is just the result of the crazy congestion which has been developing steadily over the years and must, unfortunately, be accepted by those whose desire it is to tune to the top end,

in particular, of the medium-wave band after dusk.

There is no need for listeners of the local programmes to suffer the disturbances, however, for the v.h.f. service, launched at very great expense by the BBC for the purpose of improving local reception, can solve the problem.

As is shown in Fig. 1(a) skyward signals from a v.h.f. transmitter normally fail to be reflected by the layers in the upper atmosphere, which means that distant stations cannot normally affect local reception, even though frequency sharing may be adopted.

Capture Effect

There are times, however, when the v.h.f. signals are reflected due to abnormal weather conditions and during settled periods during the spring and summer months. The f.m. system can handle this problem, nevertheless, and this it does because of an f.m. characteristic—called the "capture effect"

—which causes the f.m. set to lock on to the strongest signal and almost completely reject the weaker interfering signal, even though this may be on the same frequency as the wanted signal.

Thus, listeners to the f.m. service are pretty well assured of good interference-free reception under all conditions. That is, provided their receiving installations are correctly tuned and adjusted.

One of the reasons why good v.h.f. reception is not achieved in practice in some cases is that the signal applied to the set from the aerial is far too weak. Nearly all commercial f.m. and a.m./f.m. receivers contain an internal compressed dipole for Band II operation, and while this may deliver sufficient signal when the set is operated reasonably close to a transmitter and in a building and local area which is not unduly screened, it is far from adequate at distances in excess of about 10 miles from the station.

Modern sets are remarkably sensitive, and even on a very weak signal they will give some sort of results, and quite loud signals at full volume, but operated under this condition any local interference will almost certainly be stronger than the signal itself.

Unless the set (or tuner) is a very elaborate type, the interference will break through as crackles on sound, and this applies especially to car ignition and electrical interference from domestic appliances.

Amplitude Limiting

Given a reasonably high level of wanted signal, all but the very poorly designed and inexpensive receivers will automatically suppress normal electrical interference due to the amplitude limiting action which is inherent to f.m. sets.

All interference of this kind is amplitude modulated. Thus, it follows that a set which is sensitive only to f.m. signals and considerably insensitive to a.m. signals will give interference-free results even when operated in an interference-infested area that would render ordinary a.m. reception almost impossible.

Assuming, then, that the f.m. set is in good order and correctly tuned (for incorrect tuning will affect the pick-up of interference, as we shall see later), a high level of interference should lead immediately to a check of the aerial system.

If nothing more than the internal aerial is used, one could be fairly safe to expect a "dramatic" improvement in reception by the use of an external aerial. Unless one happens to reside in an area outside the range of an f.m. station (see Table 1), the external aerial need not be too elaborate.

Often a simple room or loft type aerial is sufficient, provided it is cut to the optimum length, turned for maximum signal pick-up and connected to the receiver through the type of cable (twin feeder or coaxial) as recommended by the manufacturer.

Basic F.M. Aerial

Fig. 2(a) shows the basic f.m. aerial. This consists of a dipole, comprising two lengths of conductor each of dimension l , giving an overall length of 2 times l plus the length of the insulator. In practice, the distance between the holes in the insulator, carrying the two halves of the dipole, is about $1\frac{1}{2}$ in., but this is not critical.

For all areas in Great Britain, the overall length of an f.m. dipole is 5ft. 2½ in. Thus, the length of each half will depend upon the length of the insulator employed.

To the centre of the two conductors is connected the feeder cable to the set. The diagram shows the connection to coaxial cable, but the connection to twin feeder would be similar; that is, one conductor to each half of the dipole.

If screened twin feeder is used, the outside screening braid should be dressed back and left disconnected.

Now, an aerial of this nature, when mounted horizontally, as is required by the horizontally polarised signal from the f.m. stations, is bi-directional. It has two directions of maximum response, and two directions of minimum response, as shown in Fig. 2(b).

For the best results, then, the aerial should be positioned so that it looks broadside on towards the station. If necessary, a map should be used to establish the direction of the station relative to the receiving site.

Two practical aerials which can easily be constructed by the enthusiast are shown in Fig. 3. At (a) the dipole is formed by two lengths of insulated wire supported between a pair of insulated hooks in the roof-space, while at (b) the dipole is made of ¼ in. diameter tube supported on a wooden frame and mounted on insulators. Both types will give good reception up to distances of about 25 miles from a station.

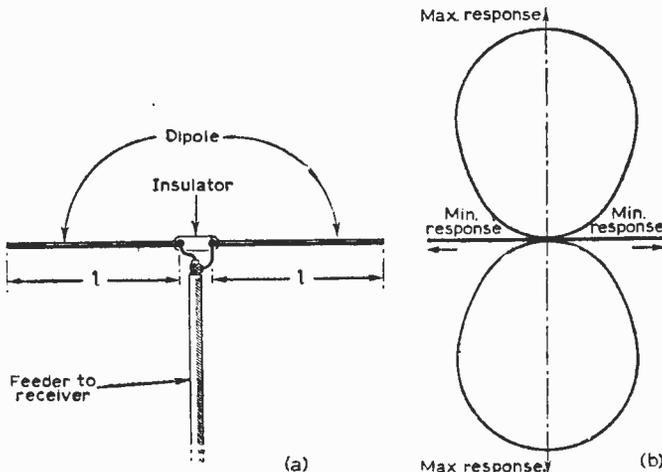


Fig. 2: The basic f.m. aerial at (a) and its polar diagram at (b).

ELECTRONICS

LEARN - THE PRACTICAL WAY . . .

your career . . .
hobby . . .
own business . . . ?

The demand for good Electronic Engineers is increasing almost daily throughout the world. Electronics is now the most rapidly expanding of all industries with its applications reaching into almost every sphere of human activity. If you are looking for a new career with new opportunities, then now is the time to choose—Electronics. If you are already employed in this field—then now is the moment to seek high qualifications to secure the top jobs which are waiting to be filled. Most of all, the great potential of electronic development means unlimited scope for the future and will ensure a secure occupation for you—unlikely to be affected by possible future recessions in other industries.

The British National Radio School has had 25 years' experience of HOME STUDY coaching for students wishing to master the fascinating subjects of Electronics—whether the object be career or as a hobby or new interest. The School is entirely independent and specialises ONLY in the teaching of electronic subjects. It employs only fully qualified staff to conduct and supervise each individual course taken by a student and it is this close and personal contact between Tutor and Student which we believe makes possible the successful completion of a course of study.


A special feature of our system is that all courses start right from the beginning and no previous knowledge or experience is necessary or expected. Training is carried out in easy step-by-step stages using the most modern methods of tuition. The great advantage of the home study method is that it provides a complete self-contained course giving everything needed for the subject concerned and enabling work to be done in the comfort of one's own home and over any period of time desired.

EXAMINATION COURSES

- CITY & GUILDS TELECOM. TECHNICIANS CERT.
- CITY & GUILDS FULL TECHNOLOGICAL CERT.
- A.M.Brit.I.R.E. EXAMINATION
- RADIO AMATEURS LICENCE EXAMINATION
- P.M.G. CERTIFICATES FOR RADIO OPERATORS.
- R.T.E.B. SERVICING CERTIFICATES.

OTHER COURSES

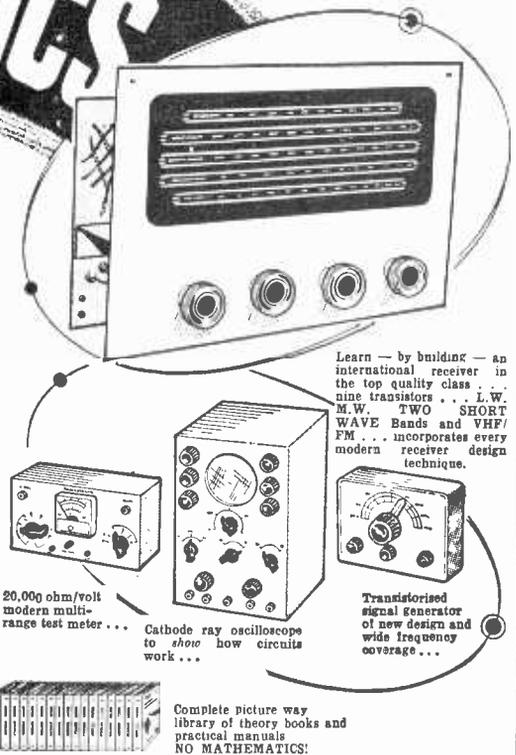- MATHEMATICS
- TELEVISION
- TRANSISTORS
- SERVO-MECHANISMS
- COMPUTERS
- RADAR & NAVIGATIONAL AIDS



BUILD AND EXPERIMENT WITH ALL THE ABOVE—AS—YOU—LEARN . . .

This is a new complete experimental course comprising a mixture of theory and practical work using a very full range of electronic components and apparatus. Starting right from the beginning—or at a later stage if needed—the course enables the student to build up all the basic electronic circuits—amplifier; oscillator; rectifier; detector; etc.—and finally to the design, construction, testing and servicing of a latest design fully transistorised receiver using nine transistors and covering long and medium wave and TWO SHORT WAVEBANDS plus VHF/FM reception. It is of real luxury quality throughout—operates from a 9V. battery and can be used anywhere in the world. Every present day technique in circuitry is covered and the course also includes multi-range test meter; signal generator and oscilloscope. By the end of the course the student will be able to deal with any type of servicing work with confidence and will also have a very useful workshop of equipment. Nearly 100 interesting and absorbing EXPERIMENTS are carried out during this comprehensive course enabling anyone to gain full mastery of electronics.

FREE



POST NOW

TO: BRITISH NATIONAL RADIO SCHOOL, RADIO HOUSE, READING, BERKS.
Please send me your free Brochure, giving details of your Courses, without any obligation, to —


NAME

ADDRESS } Block Caps Please

I am interested in courses above

(We do not employ representatives) PWV 2/65

British National Radio School

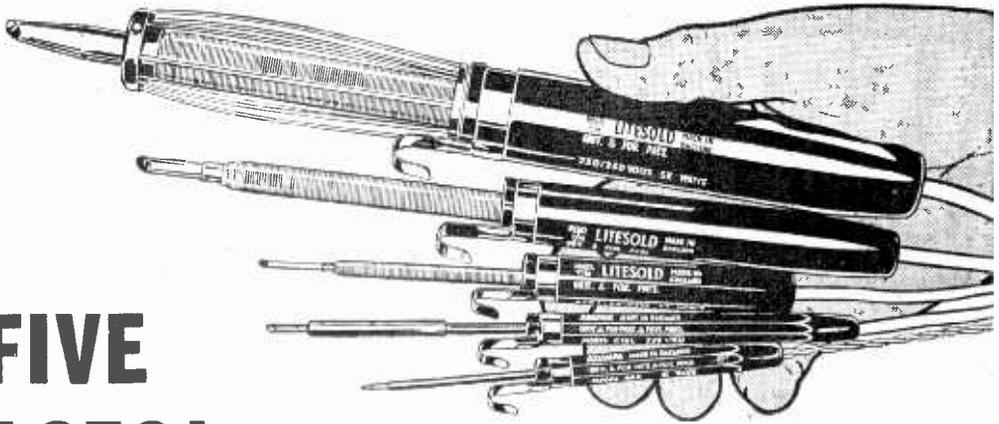

FIVE ACES!

This is a hand that can't be beaten. Five models from our tremendous range of soldering instruments. Superb performance. Amazingly compact. Developed to simplify YOUR soldering. Copper bits for greatest speed. Permatip bits for long life. May we deal you in?

Brochure P.W.10 post free on request

LIGHT SOLDERING DEVELOPMENTS LTD., 28, Sydenham Road, Croydon, Surrey
Telephone: CROYdon 8589

Shall we toss it to the *Totters?*

Every year at this time we find ourselves with some perfectly good equipment which must be disposed of to make room for new items. Finally it becomes a choice between loading it on the junk man or offering it at prices that will just cover the cost of the advertisements. So here are the items we have decided to offer at far below list prices. Buy now and profit by our loss!

- | | | | |
|---|----------|--|--------|
| (One only) Leak Stereo 50 Amplifier No pre-amp. (List £42)..... | £19.10.0 | (7 only) Steel Cases for Globe King 300A. Grey Hammer finish, 12" x 8½" x 8½", hinged lid, speaker grill, complete with metal chassis 10½" x 7½" x 1½" | £1.9.6 |
| (One only) H.M.V. 10 watt + 10 watt Stereo. No pre-amp. (List £31.10.0)..... | £10.10.0 | (2 only) Steel Cases for the Centurion (Grey Hammer finish) 12" x 6½" x 7", complete with chassis 11" x 6" x 1½"..... | £1.9.6 |
| (One only) H.M.V. 4 watt + 4 watt Stereo (List £27.6.0)..... | £9.10.0 | (One only) Hiwayman Case in plain white wood with handle. Ideal for any small portable | £1.2.6 |
| (One only) Heath Kit S88 Stereo Amplifier, ready built (List £27.10.0) | £12.10.0 | Chassis for the Shirley Stereo Amplifier, with engraved front panel | £1.0.0 |
| (One only) Goodmans Axiette enclosure Kit (List £14.1.6) | £5.10.0 | Meters 500 Micro-amp, scaled 0-15 and 0-600 | 15.0 |
| (One only) Johnsons 500A S.W. Mains Set, ready built | £5.10.0 | | |
| (One only) Rotary Converter, ruggedly built to Government Specification in strong wooden carrying case. Input 12 Volts D.C. Output 230 Volts A.C. 50 cycles | £8.10.0 | | |
| B.S.R. Tape Decks | £7.15.0 | | |

Please add 1/6 for post and packing on all items.

However . . . if the above items don't interest you, and you require new standard components, write for our famous Catalogue. It costs 5/-, plus 1/- postage, and it contains five Coupons, each worth a shilling!

HOME RADIO LTD. 187 LONDON RD., MITCHAM, SURREY 'Phone MIT 3282


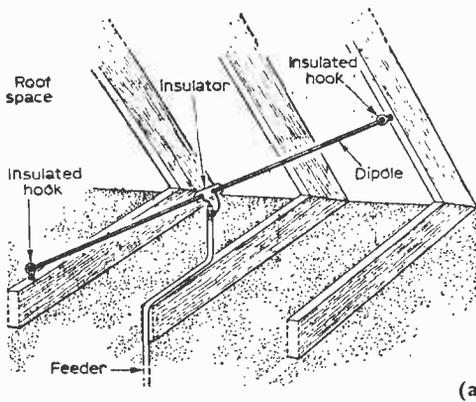


Fig. 3: Practical aeriels. (a) Roof-space type. (b) Self-supporting on wooden frame.

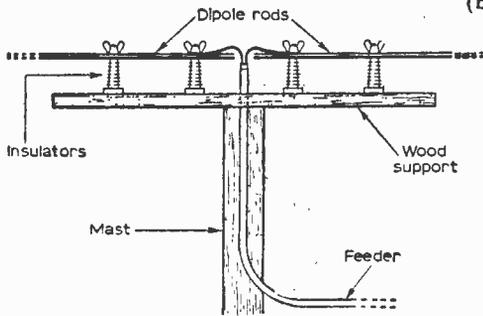

When installing the aerial in the roof-space it is desirable to keep it as clear as possible from metal pipes and water tanks, as these can affect the pick-up efficiency and tend to encourage instability at the set.

Multipath Interference

A cause of poor f.m. reception not generally known is multipath interference due to the v.h.f. signal being reflected from a nearby hill or large building and arriving at the receiving aerial a very small fraction of a second after the arrival of the direct signal. Readers versed in the arts of television reception will know that such reflections of the television signals produce ghost pictures on the screen.

The direct and reflected signals at the f.m. aerial produce a characteristic distortion which, as already intimated, sounds not unlike a badly adjusted loudspeaker. Should this trouble be experienced, a check should first be made to ensure that the set itself is free from blame, and the best way of doing that is either to run it on records, if a radiogram, or to switch to a.m. reception if of the a.m./f.m. variety. If the effect is present on an f.m.-only set or f.m. tuner, it may pay to try it out at a different location, on a friend's aerial, for example.

However, the cure for the multipath interference

is cutting out the reflected signal or, at least, making the strength of the direct signal about 100 times that of the reflected signal. This discrimination can only be handled at the aerial—there being no way of tackling the problem at the set itself.

With a directional aerial, the orientation can be arranged so that the reflected signal arrives along the axis of minimum response, assuming, in the case of a simple dipole, that the direct signal is arriving approximately at right-angles to this.

Multi-element Aeriels

In severe cases of multipath interference, an aerial of greater directivity than given by the simple horizontal dipole may be required. This would comprise the dipole and a director—or a dipole, director and reflector (or a dipole and reflector). The director and reflector are called "parasitic elements" because they are not connected electrically to the dipole.

Their purpose is to strengthen the pick-up of the signal along the axis of maximum response and further to reduce the pick-up along the axis of minimum response. What happens is that the aerial becomes responsive to signals arriving essentially along one major axis, as shown in Fig. 4.

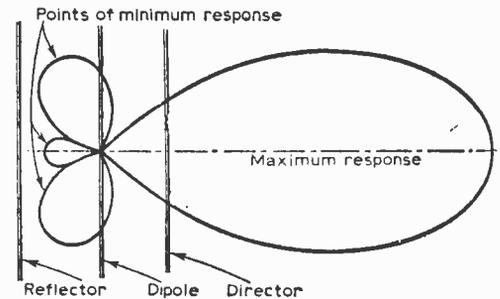


Fig. 4: The addition of a director and reflector increases the forward pick-up and reduces the pick-up at the rear. This type of aerial may be required where multipath interference is troublesome. (Dimensions in text.)

This improved directivity makes it more feasible for the aerial to discriminate between the direct and reflected signals, especially if the reflected signals are arriving at an angle close to that of the direct signal.

Note from Fig. 4 that the director is placed in front of the dipole and the reflector at the rear. The reflector is always a little longer than the dipole and the director a little shorter, optimum lengths being 5ft. 6in. and 4ft. 10½in. respectively. The spacings are also critical, being 32½in. from reflector to dipole and 19½in. from dipole to director.

Distortion due to multipath interference can often be reduced simply by altering the direction of the aerial. Sometimes this will result in a decrease in pick-up of the direct signal, but provided the signal is still sufficiently strong to overcome car and electrical interference this does not matter much.

However, if the direct signal is greatly reduced at the point of minimum distortion, a small transistorised booster could be used to restore the level of the signal.

Signal Strength Indication

Most tuners and receivers have some sort of tuning indicator for f.m., and this is useful for giving a rough idea as to how the signal pick-up has been increased or decreased by orientation of the aerial, by the use of a booster and by the use of different aerials.

Not only multipath interference, but interferences of other types are aggravated by the use of an incorrect aerial. For example, one may be tempted to use the television aerial on f.m. This invariably works, but optimum results are obtained only if the aerial system has Band II facilities. Television sets equipped with f.m. are often expected to work from the television aerial without an f.m. attachment.

This compromise is bad because the television aerial is not cut to the lengths required for Band II reception and also because the f.m. signal is horizontally polarised (needing a horizontally mounted aerial) while the TV signal in many areas is vertically polarised (with the aerial mounted as a vertical "H" for instance).

It then often happens that at times when interference from distant stations is troublesome, as explained earlier, the interfering signal picked up on the incorrect aerial is stronger than the wanted local signal! This causes the "warbling" interference effect on top of one (or more) of the local f.m. programmes.

Combined Aerials

Fig. 5(a) shows how an f.m. aerial can be connected along with the TV aerials, so that all the signals pass through the common coaxial downlead. If it is required to separate the signals at the set end of the downlead, the arrangement shown in Fig. 5(b) should be employed. At (a) the signals are combined by a triplexer while at (b) they are separated by an f.m. diplexer (passing the TV signals at one outlet and the f.m. signals at the other).

Where installation is on a main road and passing traffic interference is troublesome in spite of a good aerial system, use of one of the small transistorised f.m. boosters can be of great assistance. This is because the greater the signal applied to many sets, the better the amplitude limiting.

Thus, if the signal without the boost is just about strong enough to commence the limiting action, heavy car interference will cause trouble. The extra boost, however, often pushes the set well into limiting and considerably reduces the interference effect.

A little extra attention should also be given to the tuning-in of an f.m. set, for unless the tuning is accurate the full attributes of the f.m. system will not be realised, and both distortion and interference could cause trouble. There are usually three tuning points close to where the station is tuned, two small responses either side of the main, maximum response.

It is imperative that the set is tuned to the

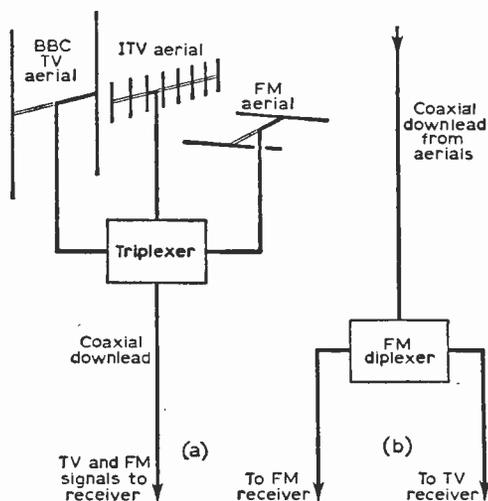


Fig. 5: A triplexer is used at the top of the downlead to connect an f.m. aerial (a). An f.m. diplexer, or similar device, must be used at the bottom of the lead if it is required to separate the signals, as shown at (b).

maximum response. Always tune for maximum deflection as shown on the tuning indicator, where fitted.

If there seems to be two major tuning points close together, the set or tuner itself may be out of alignment, and this, again, is a fundamental cause of poor f.m. reception. A f.m. set is not easily aligned properly without instruments and since so much relies upon correct alignment, it often pays to have a good radio dealer perform the necessary trimmer adjustments.

Since the many f.m. stations are placed with both geographic and frequency consideration, interference from adjacent channel signals does not occur under normal conditions. This means that full expansion can be given to the sidebands of the higher audio frequencies, and treble cut and passband cutting, which are essential on medium frequencies, are not required on f.m.


Thus, the quality of reception on a correctly working installation is far above that of the a.m. system. However, incorrect alignment can suppress the treble and make tuning difficult. Moreover, if the i.f. passband is restricted, excessive tuning drift will be noticed as the set warms up and as its temperature rises during use.

Tune to the Local Station

One final point, and that is since pretty well every local area has its own f.m. transmitter now, it is possible to pick up the signals from transmitters in adjacent areas. These signals, being weaker than the local signals (although carrying the same programmes), will be more prone to interference.

One should always ensure, therefore, that the receiver is, in fact, tuned to the local transmitter and not to an adjacent area one. ■

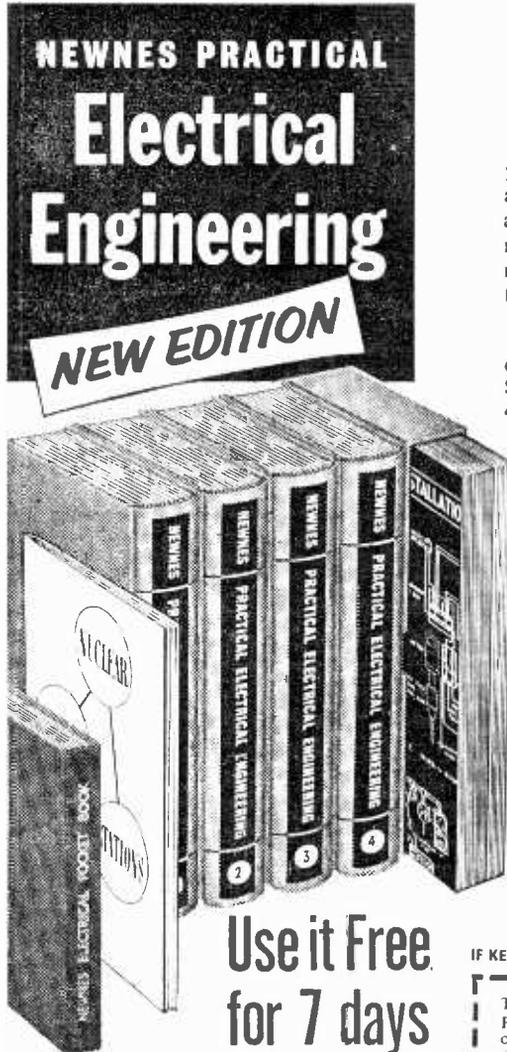87 Experts guide you to advancement and higher rewards



**Use it Free
for 7 days**

ABSOLUTELY COMPREHENSIVE!

This is what you receive without cost or obligation—

4 Volumes strongly bound in Grey Moroquette, 9 1/4 in. x 6 1/4 in. 2,352 Pages of instructive information on latest practice. Over 2,000 Photos, Diagrams, Perspective and Working Drawings, Electrical Circuits, and Data on test procedures, etc.

o o o

24 Data Sheets in colour and 12 Quick-reference Blueprint Charts complete in strong Chart Case.

o o o

Nuclear Power Stations Booklet Contains fascinating cut-away sections in full colour with explanatory text.

o o o

Free! Newnes Electrical Pocket Book (Value 10/6) Nearly 400 pages with 258 illustrations, diagrams, tables.

YOUR FUTURE, if it is in electrical engineering, depends on your ability and the services you can render. The more experienced you are the better your prospects, the better your income . . . it's as simple as that! This New Edition of Newnes comprehensive and authoritative publication is invaluable to you if you mean to progress. Produced with the full technical resources of NEWNES it covers every facet of the vast field of modern electrical engineering.

INSTALLATION WORK OF ALL KINDS

Commercial Buildings, Small Houses and Flats, Hospitals, Schools, Theatres, Cinemas, Electric Appliances, Alarm Systems.

INSTRUMENTS, MACHINES, EQUIPMENT

Electric Motors, Control Gear, Transformers, Rectifiers, Electronic Control in Industry, Measuring and Recording Instruments and Electricity Supply Meters.

OPERATION, MAINTENANCE, REPAIR

Welding Plant, Electric Traction, Cranes, Lifts, X-Ray Equipment, Testing Domestic Equipment, Batteries.

GENERATION, TRANSMISSION, DISTRIBUTION

Power Stations, Power Cables, Public Supply, Underground Distribution Systems, Town and Rural Supplies, Cable-laying and Faults.

Over 2,000 Instructive Action Photographs, Diagrams, Working Drawings, Circuits. Many Concise Data Tables.

SEND TO-DAY—FREE EXAMINATION will enable you to check it for your day-to-day problems—it will surprise you!

IF KEPT SAME PRICE CASH OR TERMS—NOTHING EXTRA IF YOU PAY MONTHLY

To: GEORGE NEWNES LTD., 15-17 Long Acre, London W.C.2
Please send Newnes PRACTICAL ELECTRICAL ENGINEERING without obligation to buy. In 8 days I will return it or post only 16/- deposit, then 20/- monthly for 16 months, paying £16. 16s. in all. Cash in 8 days £16. 16s.

*If under 21 your father must fill up coupon.
If married woman your husband must fill it up.*

Full Name _____ (BLOCK LETTERS) (Mr., Mrs., Miss)

Address _____

Occupation _____

Signature _____ (Mr., Mrs., Miss)

Tick ✓ where applicable
The address on left is—

My Property	<input type="checkbox"/>
Rented unfurnished	<input type="checkbox"/>
Parents' Home	<input type="checkbox"/>
Furnished Accom.	<input type="checkbox"/>
Temporary Address	<input type="checkbox"/>

(PEE)72/1092

WEYRAD

TRANSISTOR COILS

The P50 series remain the most popular and widely used components for Medium and Long-wave Transistor Superhets:—

P50/1AC Oscillator Coil for 176 pF tuning	5/4 ea.
P50/2CC 1st & 2nd I.F. Transformers	5/7 ea.
P50/3CC 3rd I.F. Transformers	6/- ea.
All mounted in individual cans $\frac{1}{16}$ in. diam. x $\frac{3}{4}$ in. high.				
RA2W Ferrite Rod Aerial 208 pF Tuning	12/6 ea.
LFDT4 Driver Transformers	9/6 ea.
OPTIA Output Transformers	10/6 ea.
PCAI Printed Circuit Panel	9/6 ea.
Constructor's Booklet	2/- ea.

VALVE RECEIVER COILS

Our individual "H" type iron-cored coils are without equal for the construction of a wide range of receivers. For the simplest T.R.F. sets covering one or more wave-bands the Aerial and H.F. Transformer coils are ideal. The standard superhet circuit using the ever-popular triode-hexode frequency change layout would employ the Aerial and Oscillator coils and the coverage can be selected from 7 different bands ranging from 12.5 to 2,000 metres. For a really high-performance receiver an R.F. stage can be added by using the Aerial, H.F. Transformer and Oscillator Coils and a circuit is provided illustrating such a layout.

H Coils 3/9 each.

WEYMOUTH RADIO MANUFACTURING CO. LTD.

REGENT FACTORY, SCHOOL STREET,

WEYMOUTH, DORSET

EXPRESS ELECTRONICS

FOR THE FOLLOWING BRAND NEW UNITS

AMPLIFIERS

TRIPLETONE HI-FI MAJOR	12 watt	£15.18.4
TRIPLETONE CONVERTIBLE	5 watt	£6.19.6
LINEAR	3 watt	£6.6.0
LINEAR DIATONIC	12 watt	£12.12.0
LINEAR CONCHORD	30 watt	£16.16.0
ADAstra 3-3	4 watt	£4.19.6
LEAK TL12	14 watt	£18.18.0
LEAK VARISLOPE PRE-AMP	£15.15.0
LEAK TL50	50 watt	£33.12.0
QUAD	15 watt	£22. 1.0
QUAD STEREO/MONO PRE-AMP	£25. 0.0

LOUDSPEAKERS

GOODMANS AXIETTE 8in.	6 watt	£5. 5.0
GOODMANS AXIOM 10in.	10 watt	£6. 6.0
GOODMANS AXIOM 20i	15 watt	£10.15.0

BAKERS 'SELHURST' 3 or 15 ohm

JUNIOR 8in	8 watt foam	£5. 5.0
STALWART 12in.	15 watt	£5. 5.0
BASS GUITAR 12in.	20 watt	£5. 5.0
STANDARD Heavy Duty 12in.	20 watt	£7. 7.0
BASS Heavy Duty 12in.	25 watt	£12.12.0
AUDITORIUM 15in.	35 watt	£18.18.0

RECORD PLAYERS

GARRARD SRP10 4-speed	£4.17.5
GARRARD AUTOSLIP 4-speed	£6. 7.6
GARRARD AT6 TRANSCRIPTION	£9.17.6
GARRARD 4HF TRANSCRIPTION	£14.17.6
GARRARD A LAB SERIES	£17.10.0
GARRARD 301 LAB SERIES	£19. 5.0

DELIVERED FREE U.K.

S.A.E. WITH ALL ENQUIRIES

EXPRESS ELECTRONICS

32 SOUTH END, CROYDON, SURREY

Telephone: Croydon 9186

Another famous
"Beginner's" book—a must
for all interested in
electronics ...

BEGINNER'S GUIDE TO ELECTRONICS

By Terence L. Squires, A.M.Brit.I.R.E.

An up-to-date introduction to electronics which assumes no prior technical knowledge of the subject. Early chapters

explain the nature of electric currents, pulses and waveforms. The components and circuits that are the basis of electronics are then described and illustrated, and their operation clearly explained. Chapters are devoted to test instruments; the principles of and the basic techniques used in the main branches of electronics—radar, radio, television, medical electronics, electronics in space, industrial electronics and computers, and on training to be an electronics engineer.

192 pages, 128 line diagrams.

15s. FROM ALL BOOKSELLERS

... or, in case of difficulty, 16s. 6d. by post from George Newnes Ltd., Tower House, Southampton St., London WC2.

NEWNES

IMPROVED COMMUNICATIONS THROUGH THE GROUND

Some further notes on this novel method of transmission and reception previously described in P.W.

BY C. R. BRADLEY

IN the May 1964 issue of PRACTICAL WIRELESS, an article of mine was published on a system of communication through the ground. I was quite unprepared for the tremendous response I received to this article and wish to thank all readers who wrote to me—if replies have been delayed it does not mean your letters have not been appreciated.

Well over a hundred letters arrived in the first week and they are still coming in from abroad! Most of the letters have been from readers who have had success with the method—a few thought

the whole thing was a hoax!

I have received many practical results and much historical information from readers on the subject, some of which I take the liberty of reproducing here.

The kind of ground communication described in my article was used extensively during the 1914-1918 war for morse communication through heavily shelled areas. The equipment was bulky and often in poor repair, yet ranges of up to 8,000 yards were achieved!

It seems however, from readers' letters, that the greatest distance practical with hi-fi or guitar amplifiers is about two miles. Results with amplifiers with power ratings below 8W have been disappointing; this is not surprising considering the tiny fraction of the transmitted signal which reaches the receiver.

The resistance from point to point of the ground varies so much with locality that no convenient formula giving the maximum achievable distance for a particular transmitter power can be found. The strength of the received signal will depend on a multitude of factors, including soil moisture, temperature and type.

Generally however, best performance is obtained by having both transmitter and receiver earths as far apart as possible and set in roughly the positions shown in Fig. 1b.

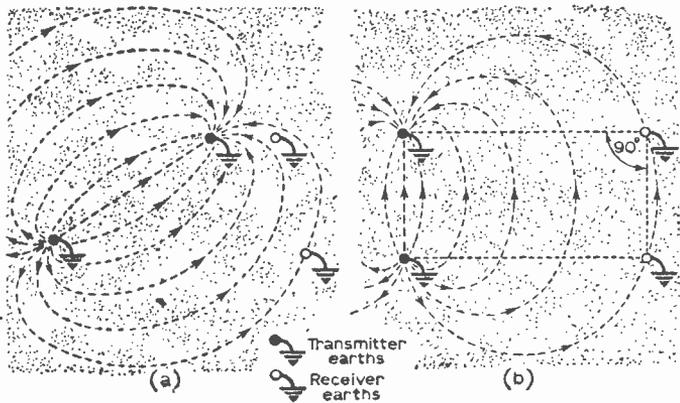


Fig. 1: Reception is better with the arrangement of transmitter and receiver earths in (b) than in (a) as the transmitting earths have a distinct "radiation pattern".

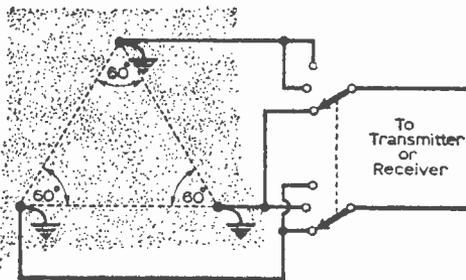


Fig. 2: A multi-directional earth system. The two-pole three-way switch selects different pairs of earths and hence different directions.

A certain amount of mains hum is always received; this is caused by a.c. currents flowing through the ground, due mainly to the earthing of mains equipment. This hum limits the weakest signal that can be received but is only prominent in built-up areas. There is no way of reducing it.

Some readers have encountered interference from nearby radio stations and even wired relay systems. In one case, ground communication experiments were found to interfere with a neighbour's telephone—unfortunately no cure could be found and they were terminated.

Because of the limited (but useful) range of ground communication there seems no need for a national "Ground Ham" club although it may prove an interesting sideline for existing local radio clubs. I am pleased my article has stirred up so much enthusiasm for a long forgotten idea which shows how far from "dead" the ground can be! ■

A COMMENTARY BY HENRY

PRACTICALLY WIRELESS

No. 6 Trouble Aloft

THE Fill-Dyke month: when gutters are full of sleet, gales howl about our ears, and Henry feels as old as his children imagine him. The time, in short, when the aerial blows down.

Aerials—yes, those remote and spindly refugees from a modern art show that so many radio users still believe they are simply an adjunct to television. Aerials—the first, most important, and most often neglected link in the chain of radio reception. Many of us continue to believe that a few microvolts in the hand are worth any amount of watts in the bush. Consequently, our eaves groan in the gales, and the ice on the insulators makes a climb up the most a daunting prospect.

Which reminds me of a story, which really I should not tell you, for it concerns a television aerial—and my spies tell me there is another magazine across the way which specialises in that upstart offshoot.

The adventure happened in the very early days, when there was only one Dimpleby and folks used to tune to the morning test signal for the fun of watching the Palio horse-race. I was called to investigate a set with no modulation, and immediately jumped to



An enthusiastic teenager and a hint of the Big Beat.

the obvious. Sure thing, a dead short across the aerial.

Defying the gales and risking everything on the sleety tiles, I shinned up to the chimney and began to unship what seemed like half the GPO tower. It was not until the ladder was shaking beneath my descending clodhoppers that I realised what I was carrying. One of the original Duplex aerials, no less. A Band I folded dipole, which even Henry should have known would give a dead short' reading on the ohmmeter—if he had only taken the trouble to look.

How many riggers, I wonder, fit a small resistor across the remote terminals of an open dipole for future bad-weather checks on possible open circuits?

It's a bit difficult, however, when one is using the length of the garden for an old-fashioned receptor, and the weight of the snow, aided by the gathering of our feathered population, and augmented by ravages of rust at the staybolts has torn the whole contraption from the garage wall and left a drooping trail of destruction through the cabbages.

Even the dinky, but effective ferrite rod has its drawbacks: mainly the extreme brittleness of the material. Aided by so many manufacturers' designs, where a long, thin rod is supported by a couple of barely padded clamps about a third of the way along.

Given an enthusiastic teenager and a hint of the Big Beat and the end of the rod droops dismally, like the end of a comedian's cigar. Even where the rod is supported more adequately, its dimensions and its brittleness make it vulnerable to shock.

Where so many folk get caught, we regret, is in writing the broken rod off as a dead loss. This device is a magnetic, not an electrical, circuit. Thus, we need only reassemble the parts, particularly if the break was clean, to regain the flux concentration.

Provided the rod can be put



Some wicked manufacturer, with a warehouse full of replacement rods.

together really well, with split ends butting, splinted like a C.D. experiment and tightly bound, there should be very little loss in aerial gain. Such loss as is apparent can often be overcome by slightly repositioning the coils. As any reader with a loose coil will have found, the positioning is quite critical.

One day, we presume, the boffins will come up with a material less prone to stress failure. They may have done so already, for all I know. Maybe some wicked manufacturer, with a warehouse full of replacement rods, is sitting on the patent rights.

In my pocket I have a useful aid to tape recordings, a piece of magnetic rubber. This is what it says it is — rubber with magnetic properties, made by impregnating the rubber in the forming stage with tiny magnetic particles. As a similar process is used in the manufacture of ferrite rods, but with ceramic instead of rubber as the base, perhaps some genius will think of a way of making them more flexible.

In the meantime, I must return to my frozen-fingered efforts to splice steel wire through the egg insulator before the 20 metre band re-opens.

End of Febrifuge—over and out.

Pioneers in build it yourself tuners and test equipment

JASON KITS

Jason were first to produce a stable switched f.m. tuner for reception of BBC transmissions and an outstanding success has been achieved with the introduction of simple-to-operate switched tuners to receive both f.m. and TV sound transmissions. Jason tuners and test equipment offer a wide choice of models designed to meet present-day requirements and are a delight to build.

OTHER JASON KITS


- FMT1 F.M. TUNER, less valves £5.19.0.
- MERCURY II Switched Tuner, less valves, £9.15.4.
- ARGUS Transistor m.w. Tuner, complete, £7.10.0.
- OG10 Oscilloscope, less c.r.t., £18.10.0.
- W11 Wobulator, complete, £14.19.0.
- EM10 Valve voltmeter, complete £23.0.0.
- SB26 Tape Deck (built only) 1-track mono 31 gns.
- 4-track stereo 39 gns.




JTV2 SWITCHED TUNER for the reception of all BBC f.m. transmissions and BBC-I and ITV television sound channels at the turn of a switch. Foster-Seely discriminator. Built-in power supply. Sensitivity 10 μ V for 40 dB quieting. Audio output 0.4V approx. All components including turret and coil plate but less four valves £14.0.4.



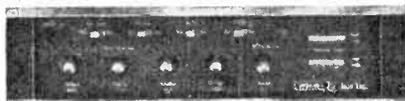FMT2 F.M. TUNER covering 88—108 Mc/s. Built-in power supply. All components, less four valves £9.9.0, less power supply components £7.15.0.
FMT3 TUNER similar appearance to above, but for fringe area reception. All components, less valves £10.9.0, less power supply components £8.15.0.



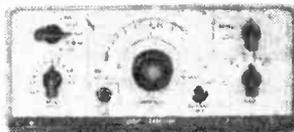JTL TAPE PREAMPLIFIER designed to suit any tape deck or head. Will simultaneously record and playback stereo or mono using two or four track heads. Especially recommended for use with the Lorin SB26 tape deck. (Send for details). All components including valves £22.1.0. Ready built and tested £30.9.0.




AG10 AUDIO GENERATOR. Excellent stability with constant output over entire range. Tunes from 10 c/s to 100 Kc/s in four switched ranges. Square wave or sine wave outputs. Square wave rise time less than 2 μ sec. at all frequencies. Minimum calibrated output 100rV. Self powered. All components, including valves £15.19.0.

Write for descriptive leaflets and name of nearest stockist.

JASON KITS

VISIT OUR
NEW WEST END
SHOWROOM

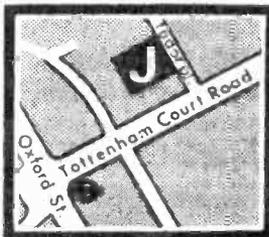18 TUDOR PLACE, TOTTENHAM CT. RD., LONDON W.1.
Tel: MUSeam 4666/8



THE LINEAR SUPER 30 HIGH FIDELITY P.A. AMPLIFIER

TECHNICAL DETAILS

SENSITIVITY FOR 30 WATTS

Gram. — 50 millivolts
 Mic. 1 — 5 millivolts
 Mic. 2 —150 microvolts

FREQUENCY RESPONSE

±2 dB, 30 c.p.s.-20,000 c.p.s.

BASS CONTROL

+15 dB to -10 dB at 50 c.p.s.

TREBLE CONTROL

+15dB to -10 dB at 10 Kc/s.

HUM AND NOISE

-60 dB.

HARMONIC DISTORTION

0.5% for 30 watts.

VALVES


Mullard ECC83, ECC83, ECC83, EL34, EL34, GZ34.

NEGATIVE FEEDBACK

20 dB.

DAMPING FACTOR

12.

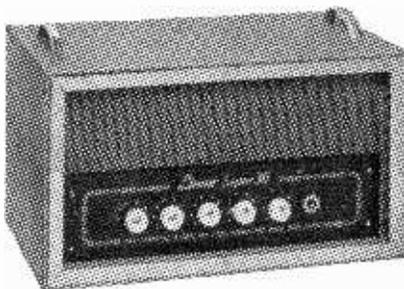

RETAIL PRICE **33 Gns.**

Send S.A.E. for leaflet.

For operation on standard 200-250v., 50 c.p.s., A.C. mains. 110/120v. models available for export.

Trade and export enquiries invited

LINEAR PRODUCTS LTD.
 ELECTRON WORKS, ARMLEY, LEEDS

A HIGHLY EFFICIENT 30 WATT GENERAL PURPOSE PUBLIC ADDRESS UNIT

With input mixing facilities and outputs for 3-7.5-15 and 330 ohms (100y line)

A special feature of the SUPER 30 is its high degree of stability, ensuring that the longest output leads can be used without fear of the usual troubles associated with instability.

Three high sensitivity standard Jack inputs with provision for high and low impedance microphones.

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee
“NO PASS — NO FEE”

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £80 a week, send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

WHICH IS YOUR PET SUBJECT ?

Mechanical Eng.,
 Electrical Eng.,
 Civil Engineering,
 Radio Engineering,
 Automobile Eng.,
 Aeronautical Eng.,
 Production Eng.,
 Building, Plastics,
 Draughtsmanship,
 Television, etc.

GET SOME LETTERS AFTER YOUR NAME !

A.M.I.Mech.E.
 A.M.I.C.E.
 A.M.I.Prod.E.
 A.M.I.M.I.
 A.I.O.B.

B.Sc.
 A.M.I.E.R.E.
 City & Guilds
 Gen. Cert. of Education
 Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.I.E.R.E., City & Guilds
 Radio Amateurs' Exam. R.T.E.B. Certificate
 F.M.G. Certificate
 Practical Radio
 Radio & Television Servicing
 Practical Electronics
 Electronics Engineering
 Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training as home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page
 “ENGINEERING OPPORTUNITIES”
 (Write if you prefer not to cut page)
 NAME.....
 ADDRESS.....

SUBJECT OR EXAM THAT INTERESTS ME..... SE/21

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
 (Dept. SE/21), 29 Wright's Lane, London, W.8

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

TRADE NEWS • TRADE NEWS TRADE NEWS • TRADE NEWS TRADE NEWS • TRADE NEWS TRADE NEWS • TRADE NEWS


New 5in. Oscilloscope Tube

MULLARD announce the D13-27GH, a further addition to their range of oscilloscope c.r.t.s.

The new D13-27GH is an inexpensive 5in. tube with an overall length under 14in., and this compactness enables it to be substituted with advantage for the small screen types often employed in monitor applications.

This tube has a flat faced, medium persistence green phosphor screen with a helical post deflection accelerator. In common with other recently introduced Mullard tubes, a separate electrode arrangement permits direct beam blanking to be accomplished. The deflection blanking voltage required to blank the tube is 60V maximum under 3kV operating conditions.

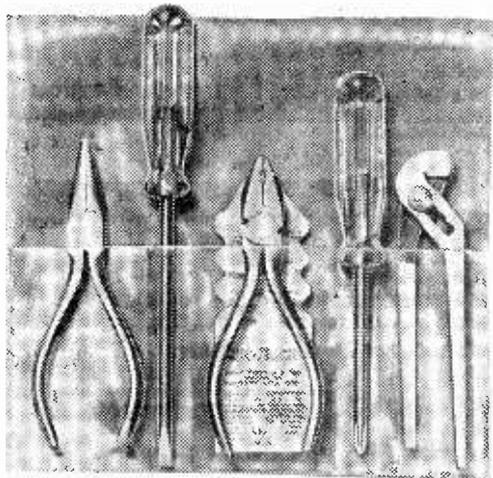
The deflection sensitivity, also under 3kV operating conditions, is better than 27V/cm for the X direction and 13V/cm for the Y direction. *Mullard Ltd., Mullard House, Torrington Place, London, W.C.1.*



W. K. & C. Peace's handy tool kit in plastic roll-pack wallet.

Compact Tool Kit

FROM W. K. & C. Peace Ltd., comes a new kit of small hand tools. Made from drop forged carbon steel, the kit consists of three of the most universally used pliers (the handles of which are un-insulated) and two screwdrivers—one for conventional slotted screws and a Phillips-type recessed head driver. These tools come complete with a card of 5, 10 and 15A fusewire in a roll-pack wallet, and retail at 28s. *W. K. & C. Peace Ltd., Templeborough Works, Sheffield, F.*

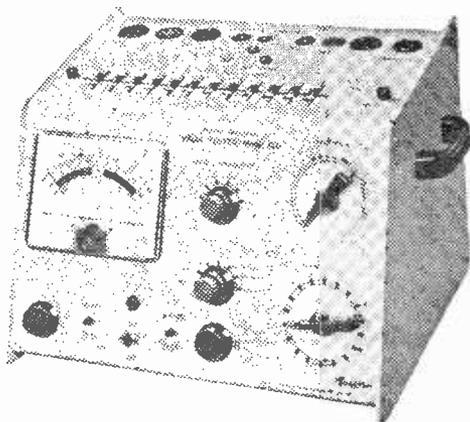

Model 45D valve tester from Taylor Electrical Instruments Ltd.

New Valve Tester

TAYLOR Electrical Instruments (M. I. Group) has introduced a new modern styled valve tester, Model 45D. This supersedes the Model 45C.

Main features of the 45D are the ten valve bases which enable tests to be carried out on the latest types of valves.

A valve chart which is included gives testing data for over 7,000 British, American, Continental and Russian valves. The manufacturers of this instrument are *Taylor Electrical Instruments, Montrose Avenue, Slough, Buckinghamshire.*


Amateur Radio Equipment

NEW additions to the American Heathkit range of amateur radio equipment are: single sideband receiver, model SB-300E at £133 14s., single sideband transmitter SB-400E at £165 4s., and 80m s.s.b. transceiver HW-12 at £60 1s., and a single monitor oscilloscope HO-10E priced at £34 10s.

Instruments in the Heathkit range that have been re-styled are the 5in. oscilloscope 10-12U for £32 12s. 6d., television alignment generator HFW-1 at £34 18s., and the 6in. valve voltmeter 1M-13U priced at 18 guineas. *Daystrom Limited, Gloucester, England.*

Tape Splicer Kit

MASTERTAPE announce the introduction of a new and improved Mastertape splicer kit retailing at 21s., and containing a tape splicer and cutter, five different coloured leader tapes, metallic strip and jointing tape. Full operating instructions for the splicer are printed inside the lid of the distinctive carton. *MSS Recording Company Limited, Poyle Trading Estate, Colinbrook, Slough Buckinghamshire.*

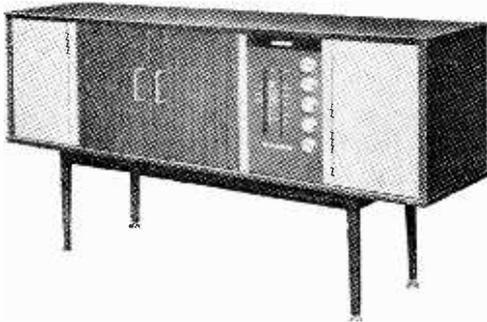

Baird's model 100 transistorised stereo radiogram.

Stereo Radiogram

MODEL 100 is Baird's first stereophonic radiogram. It is completely transistorised and power is obtained via a mains transformer so isolating the chassis.

Separate bass and treble controls are incorporated and there is a balance control for equalising the volume of the two audio outputs. Waveband selection is by push-button control.

There is provision for connecting extension speakers separately to each audio channel so that, where required, full stereo reproduction is available at an extension position. A tape recorder socket is incorporated to provide facilities for recording from radio or records, and tape recordings can be

replayed through the stereogram amplifier/speaker system.

Built-in aerials are fitted for both a.m. and f.m. and there is provision for rotating the ferrite a.m. aerial. There is also provision for the connection of an external f.m. aerial.

The cabinet is finished in high gloss polyester and adjustable glides are fitted to the legs.

The circuit embodies 19 transistors and 4 crystal diodes. The record changer is a B.S.R. UA15 fitted with a B.S.R. stereo dual stylus.

The overall size of the Model 100 is 50½in. wide, 28in. high and 14½in. deep, and the price is 70 guineas including purchase tax. *Baird TV Distributors, Ltd., Empire House, 414 High Road, Chiswick, London, W.4.*

Morse Records

RECENTLY released by The Morse Centre is "The Beginners' Course", a new addition to their range of morse records. The Beginners' Course consists of two records, one 12in. instruction record plus one 7in. EP containing two simulated GPO amateur morse tests. Each is available at 9, 12 and 21 words per minute, plus an instruction book. The cost of this course is £3. 0s. 6d.

Also available is the Complete Course which consists of three records as well as instruction books, a Beginners' 12in. LP, an Advance Students' 12in. LP and a 7in. EP, all of which are played at three speeds. The overall cost, including postage in the UK is £4 4s. *The Morse Centre, 45 Green Lane, Purley, Surrey.*

PREPARING FOR THE R.A.E.

—continued from page 973

resonant—the secondary circuit being a link winding. In C the secondary circuit only is resonant—the primary being a link winding and in (d) both circuits are resonant. (a), (b), (c) and (d) couple the circuits in different ways but (b), (c) and (d) are all coupled because of the mutual inductance between the coils.

4.9 Acceptor and Rejector Circuits

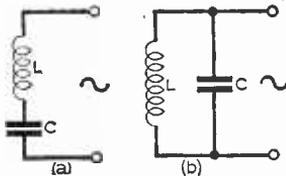


Fig. 36—Acceptor and rejector circuits.

A series connected circuit, as shown in Fig. 36a is called an *acceptor circuit*, because if two equal voltages, at different frequencies, one of which was the same as the resonant frequency of the circuit, were applied to the circuit the *maximum* current would flow for that voltage at the resonant frequency, i.e. the resonant frequency is more readily accepted.

Conversely in Fig. 36b the circuit is a *rejector circuit*, because at the resonant frequency of the circuit the current in the circuit is *minimum*.

Question

In Fig. 37 find at what frequency the circuit would be resonant and calculate the value of the capacitance

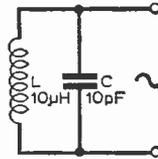


Fig. 37—Inductance and capacitance in parallel across an a.c. supply.

which would have to be placed in parallel with C to make the circuit resonate at half this frequency.

Answers to last Month's Problem

(a)

$$X_c = \frac{1}{2\pi fc} = \frac{1}{6.28 \times 50 \times 0.000002}$$

$$= \frac{1}{0.000628} = 1592 \Omega$$

$$I = \frac{E}{R + X_c} = \frac{250}{1592}$$

$$= 0.157 \text{ amps.}$$

(b)

$$X_L = 2\pi fL$$

$$1592 = 6.28 \times 50 \times L$$

$$1592 = 344.00 L$$

$$\therefore L = \frac{1592}{344}$$

$$= 4.63$$

Value of Inductance is 4.63 Henrys.

Part 5 Next Month



LAFAYETTE HA 63 COMMUNICATION RECEIVER

7 valves + Rectifier, 4 Bands 550 Kc/s—31 Mc/s. 'S' Meter-BFO-ANL-Bandspread Tuning 200/250v A.C. Brand New. 25 Gns. carr. paid.



LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYZER
2 pF, 2,000 mF.d. 2 ohms, 200 megohms. Also, checks impedance. Turns ratio. Insulation 200/250v. A.C. Brand New £15, carr. 5/-.

LONDON AGENTS FOR CODAR EQUIPMENT

LAFAYETTE HE-40 COMMUNICATION RECEIVER
4 Bands 550 Kc/s—30 Mc/s. 'S' Meter-BFO-ANL-Bandspread Tuning - Built in speaker. 200 250v A.C. Brand New. 19 Gns. Carriage 10/-.



LAFAYETTE HE-30 RECEIVERS, 9 valves, 550 Kc/s—30 Mc/s. Semi Kit form. 24 Gns. Carr. paid.

TE-22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20 c.p.s. to 200 Kc/s. Square: 20 c.p.s. to 25 Kc/s. 200/240 v. A.C. Brand new Guaranteed. £5. Carr. 5/-.



RK140 STEREO TAPE DECKS WITH BUILT-IN PREAMPLIFIER
4 Transistors, 4 Valves. Will record or playback 1/2 Track Stereo or Mono at 7 1/2 or 3 1/2 I.P.S. 7in. spool size. Twin meter level indicators, 4 inputs. Output 500 MW. 40-18,000 CPS., response. Size 15 x 10 x 6in.. 200/250 volt A.C. operation. Brand New 42 Gns. P. P. 15/-.

S.A.E. FOR DETAILS OF ALL EQUIPMENT




RCA AR.88 RECEIVERS

L.F. Model 75-550 Kc/s and 1.5-30.5 Mc/s Guaranteed Perfect Order £35, carr. 30/-. D. Model 550 Kc/s—32 Mc/s. Guaranteed "As New Condition" £25, carr. 30/-.

LAFAYETTE TE-20A R.F. SIGNAL GENERATOR

120 Kc/s—390 Mc/s on 6 ranges Variable R.F. and A.F. outputs Large clear scale. Size 7 1/2 x 10 x 4 1/2in. 200/250v. A.C. Operation. Brand New £12.10.6. carr. 5/-.

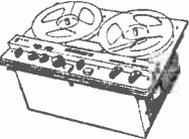

Transistor 4-channel Microphone Mixer 49/6

Mullard OC81 Two for 5/-

VARIABLE VOLTAGE TRANSFORMERS
Brand New Guaranteed. Fully Shrouded. Input 230v. 50/60 c/s output 0-230v.
1 Amp £4.10.0. 5 Amp £9.10.0. 2.5 Amp £5.17.6. 10 Amp £18.10.0. 12 Amp £18.15.0. 2.5 Amp Portable. 20 Amp £32.10.0. Metal Case with Meter Fuses etc. £9.17.6.



ARMY FIELD TELEPHONE TYPE F
Generator Bell Ringing, 2 Line Connection. With Wood Carrying Case. Fitted Batteries. Supplied Fully Tested. £4.18.6. Pair Carr. 5/-.

CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantities. Available as follows: Type MR. 38P. 1 2 1/2in. square fronts.



2mA	..	22/6	10V. DC	..	22/6
5mA	..	22/6	20V. DC	..	22/6
10mA	..	22/6	50V. DC	..	22/6
50mA	..	22/6	100V. DC	..	22/6
100mA	..	22/6	150V. DC	..	22/6
150mA	..	22/6	300V. DC	..	22/6
200mA	..	22/6	600V. DC	..	22/6
300mA	..	22/6	750V. DC	..	22/6
500mA	..	22/6	15V. AC	..	22/6
750mA	..	22/6	50V. AC	..	22/6
1-0-1mA	..	22/6	150V. AC	..	22/6
1A. DC	..	22/6	300V. AC	..	22/6
5A. DC	..	22/6	600V. AC	..	22/6
3V. DC	..	22/6	"S" Meter 1mA	..	29/6

500µA	..	22/6
100µA	..	22/6
200µA	..	27/6
500µA	..	25/-
30-0-30µA	..	29/6
100-0-100µA	..	27/6
300-0-300µA	..	22/6
1µA	..	22/6

POST EXTRA. Larger sizes available—send for lists. ILLUMINATED "S" METER. 1 1/2in. square front. Cal. in 8 units. 6V. lamp. 29/6. P.P. 1/-. Ditto 2 1/2in. square 39/6. P.P. 1/-.



16Ω — 25-15,000 Cycles. Air Cushioned Headband with cables and overload Junction Box. Brand New Guaranteed. 82/6. P. & P. 2/6.

LAFAYETTE HI-FI STEREO HEADPHONES



TS-76 20,000 O.P.V. PUSH BUTTON MULTI-TESTER

Large clear plastic scale, simple operation. D.C. volts up to 1,000V. A.C. volts up to 1,000V. Resistance up to 10 megohm. Current up to 25mA. Decibels. 20 to +36dB. Size 6in. x 4 1/2in. x 2 1/2in. Complete with leads, batteries and instructions. ONLY £5.5.0. P. & P. 2/-.

TYPE 13 DOUBLE BEAM OSCILLOSCOPES

Perfect order. £27.10.0. Carr. 20/-.

AMERICAN TAPE

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.
3in. 200ft. L.P. mylar 4/-
3in. 600ft. T.P. mylar 10/-
3in. 900ft. std. plastic 9/6
3in. 900ft. L.P. acetate 10/-
3in. 1200ft. D.P. mylar 15/-
3in. 1200ft. L.P. acetate 18/6
5 1/2in. 1800ft. D.P. mylar 22/6
7 1/2in. 1200ft. std. mylar 12/6
7 1/2in. 1800ft. L.P. acetate 15/-
7 1/2in. 1800ft. L.P. mylar 20/-
7 1/2in. 2400ft. D.P. mylar 25/-
Postage 2/- Over £3 post paid.

RECORDING HEADS

Reuter: 1/2 track, set of 2 19/6
Minifix: 1/2 track, set of 3 29/6
Bradmatic: 1/2 track, set of 2 99/6
Post Extra

HEADSETS

D.L.R.'S. LOW IMP 10/8
R.C.A. LOW IMP 15/6
Chamois padded moving coil with jack plug 22/6
Ditto with Mic. 25/-
All New—Post Extra

MULTI-METERS

Brand New—Fully Guaranteed. Lowest ever prices. Supplied with leads, batteries and instructions.



MODEL NH-201
30,000 o.p.v.
0/25/10/50/250/500/
1,000V. D.C.
0/10/50/250/500V. A.C.
0/50/1A/10/250mA
0/5K/500K/5 Meg Ω
99/6. P.P. 2/6.

MODEL AR-420
20,000 o.p.v.
0/10/50/250/500/1,000V.
A.C. and D.C.
0/500µA/6/60/600mA
0/10K/100K/1 Meg Ω
250pF—.02mFd
0-500 Henry's
92/6. P.P. 2/6.

MODEL TE-12

20,000 o.p.v.
0/6/6/30/120/600/1,200/
3,000F.000V. D.C.
0/6/3K/120/600/1,200V.
A.C.
0/60µA/6/60/600mA
6/6K/600K/6 Meg/60
Meg Ω
5pF—.2mFd
£5.19.6. P.P. 2/6.

MODEL NH-400
10,000 o.p.v.
0/3/3/30/120/300/600/
1,200V. DC.
0/12/60/120/300/1,200V.
AC.
0/120 Ω A/30/300mA DC
0/2K/200K/2 Meg Ω
100pF—.2mFd
79/6. P.P. 2/6.

MODEL 250J
2,000 o.p.v.
0/10/50/500/2,500V. DC
0/10/50/500/2,500V. AC
0/2 Meg Ω
0/250mA
—20 to +36dB
49/6. P.P. 2/6.

MODEL ITI-2

2,000 o.p.v.
0/5/25/250/500/2,500V.
DC.
0/10/50/500/1,000V. AC
0/50 Ω A/25/250mA DC
0/50K/6 Meg Ω
.01—.3mFd
82/6. P.P. 2/6.

MARCONI TFI44G/4 STD SIGNAL GENERATORS

35 Kc/s-25 Mc/s. Perfect order. £25. Carr. 39/6.

SILICON RECTIFIERS	750mA	3/-
250 P.I.V.	6 amp	5/6
200 P.I.V.	1,000 P.I.V.	650mA
800 P.I.V.	500mA	2/6
400 P.I.V.	3 amp	7/6
400 P.I.V.	500mA	3/6
150 P.I.V.	165mA	1/-
70 P.I.V.	1 amp	3/6
95 P.I.V.	1 amp	5/6

Post extra

MINE DETECTOR No. 4A
Will detect all types of metals. Fully portable. Complete with instructions. 39/6 each. Carr. 10/-. Battery 8/6 extra.

BEST BUY!
Send 1/- P.O. for full catalogue and lists.
Open 9 a.m. to 6 p.m. Every day. Monday to Saturday. Trade supplied.

GW SMITH & CO (RADIO) LIMITED
Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

NOW ANYONE CAN AFFORD TO TRAIN TO BE AN EXPERT IN RADIO, TV, AND ELECTRONICS

Anyone can afford these amazing courses—anyone can understand this practical training—No complicated mathematics to hold you back—No old fashioned, obscure explanations to frustrate you! The lessons are **CRYSTAL CLEAR, PRACTICAL, EASY TO MASTER AND USE**—Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical "know-how" of an expert! Compares favourably with some courses costing very much more! By creating a new market through large volume sales and eliminating individual letter writing we are able to pass on these savings directly to you! Each course is printed on extra large quarto size sheets and bound into one manual to simplify handling and distribution. Please select the course most suitable for your requirements from the following:

No. 1. RADIO COURSE. Fundamental facts—Electrons—Conductors and Insulators—Radio Batteries—Circuits—Magnetism—Ohm's Law—Resistor Colour Code—Chart—What resistor to use—Electro-Magnetism—Electromagnetic Induction—Self Induction—Radio Frequency Inductances—Capacity Coupling—I.F. Transformers—Radio Coils—Radio Capacitors—The Farad—Dielectric—Capacitor Colour Code—Alternating Current Theory & Filters—Reactance and Resistance—Charts to calculate Capacity Frequency and Inductance—Handy Radio Formulae—Practical Aspects of Radio Servicing—Radio Valves—Transistor Theory—N Type Germanium—P Type Germanium—Diode Action—Transistor Action—D.C. Stabilization—Transistor Bias Adjustment—R.F. Amplification—Superheterodyne Principles—A.C.V. Power Supplies—Meters—Multimeters and Valve Testers—Point to Point Servicing, Signal Generators and Signal Tracers—Using an Oscilloscope for Servicing—Alignment—Amplifiers and Test Equipment—High Fidelity—Advantages of Inverse Feedback—Speakers—Frequency Modulation—How to Obtain Radio Jobs. Price for the complete course. **ONLY 36/-**. Plus postage 1/6.

No. 2. ELECTRONICS COURSE. Includes most of the above lessons plus L.C. and R. Combined Circuits—Resonance Phenomenon—Behaviour at Resonance—How Meters Work—Making a Voltmeter—Ohm meter Connections—Valves—Electron Beam Tubes—Characteristic Curves—Power Supplies—Audio Amplifiers—Microphones—Resistance Coupling—Obtaining Grid Bias—Push, Pull and Parallel—Phase Inverter Circuit—Radio Frequency Voltage Amplifiers—I.F. and Multiband Coils—Detection—Receiver Circuits—Results of Frequency Mixing—A.V.C.—Electronic Oscillators—Quartz Crystals—Radio Transmitter Circuits—Modulation and Tuning—Lines, Antennas and Radiation—Test Equipment Using Meters—Electronic Test Equipment—Thyratrons—Photo-Cell Equipment—Radio Compass—H.F. Heating—Electronic Shaping Circuits—Electron Microscope—Electric Strain Gauges—Inter-Communicators—Radio Servicing Techniques—Servicing Printed Circuits. Price for the complete course **ONLY 36/6**. Plus postage 1/6. Graduates of the Electronics Course can qualify for a certificate—details sent with each order.

No. 3. TELEVISION COURSE. Effect of Mis-adjusted controls—Pictures of various faults—Service adjustments—Circuit Faults Indicated by a Poor Picture—Finding Bad Valves by observing Picture Faults—Separate Channel I.P. System—Intercarrier I.F. System—Negative Picture—Interference—Antenna Principles and Practices—U.H.F. Transmission Lines—Facts About the T.V. Signal to Help you in Service Work—Synchronizing Separators—T.V. Interference Aids—All about Cathode Ray Tubes—Explanation of T.V. Circuits—Video Detector—Video Amplifier—D.C. Restorer Circuit—Automatic Gain Control Circuits—Oscillators—Detection Coils—Automatic Frequency Control Circuits—Analysis of Stagger Tuned I.F. Receiver—Analysis of Three Inter-Carrier Type Receivers—The Vertical Deflection Circuit—The Horizontal Deflection Circuit—Waveforms—Schematics of various sections of a T.V.—U.H.F. Converters and Tuners—T.V. Test Equipment and Alignment—Analysis of Various Problems. Price for the complete course. **ONLY 36/-**. Plus postage 1/6.

UNCONDITIONALLY GUARANTEED TO GIVE COMPLETE SATISFACTION You must be convinced that this is the best value you have ever seen in Electronic, Radio or T.V. training, otherwise you can return the course (or have your money refunded if sent **W.S.** order) after you have examined it in your own home for a full seven days.

IF YOU SEND CASH WITH ORDER WE WILL INCLUDE A FREE 70-PAGE BOOK. Tick on the coupon one book for each course ordered with full cash, **RADIO SERVICING FAULT FINDING BOOK, TELEVISION FAULT BOOK, OSCILLOSCOPE BOOK.** These free books are authoritative, and loaded with information. Would cost at least 5/- each if bought separately—by sending cash you reduce book-keeping and other costs, which savings we pass back to you.

FREE TRIAL OFFER Pay only 5/- per week if you wish. Clip coupon right now for this special offer. To: Slim-Tech Book Company, Dept. CWB, Gater's Mill, West End, Southampton, Hants.

Please send the following courses for a full seven days' trial.

No. 1. RADIO COURSE. 37/6, incl. postage. No. 2. ELECTRONICS COURSE. 41/-, incl. postage.

No. 3. TELEVISION COURSE. 37/6, incl. postage.

(Free trial customers tick only one please).

If not delighted, I may return the course post-paid without further obligation on my part. Otherwise I will pay cash price **OR** 5/- weekly until purchase price plus 2/6 service charge has been paid.

Tick here if enclosing full purchase price.

Please send me **FREE, RADIO FAULT FINDING BOOK.**

FREE, T.V. FAULT FINDING BOOK, FREE, OSCILLOSCOPE BOOK. Amount enclosed £.....

I understand that you will refund this money in full if I am not 100% satisfied. Overseas customers please send full amount (including Ireland).

NAME

ADDRESS

CITY

County



The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. Ersin Multicore Solder is also available in high tin quality alloys. 60/40 in 22 s.w.g. for printed circuits, transistors, etc.

THE HANDY DISPENSER

Easy to find in the tool box—simple to use. Virtually a third hand for tricky soldering jobs. 12 feet 5-core 18 s.w.g. **ERSIN MULTICORE SAVBIT** alloy in a continuous coiled used direct from free-standing dispenser. **2/6 each**

SAVBIT ALLOY saves wear on soldering iron bits

SAVBIT SIZE 1 CARTON

Contains approximately 30 feet of 18 s.w.g. **SAVBIT**. It is also supplied in 14 s.w.g. and 16 s.w.g. Obtainable from radio and electrical stores.

5/- each

BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, adjustable to most thicknesses. Splits extruded plastic twin flex. **3/6 each**

MULTICORE SOLDERS LTD.
 MULTICORE WORKS · HEMEL HEMPSTEAD · HERTS. (BOXMOOR 3636)
 CHMS 24

DUKE & CO. (LONDON) LTD. TELEPHONE HANDSET

621/3 Romford Road, Manor Park, E.12
 Liverpool St.—Manor Pk.—10 mins.
 Phone: ILFord 6001/2/3. Stamp for Free List

15/6 pair

VALVES 9d. each. 1,000's available. Send for List.
 CONDENSERS. 100—10/-. New. Assorted electrolytics and pfs. P. & P. 2/6.
 V/CONTROLS. 20—10/-. A selection of types and sizes. P. & P. 2/6.
 SPEAKERS, 7/9. 6in., 8in., 7 x 4in. and 8 x 3in. 1x. mfd. valves. P. & P. 2/3.
 NEONS, 25 box 2/-. (S.B.C.D.P. fittings), Maine tester and visual reminders. P. & P. 1/-

G.P.O. pattern. House to Workshop, Garage, Inter-Office, etc.
 Works of any small battery. P. & P. 4/6

EX-RENTAL T.V. SETS

Coloured **FREE** LIST. Demonstrations daily from our large selection

12 months written guarantee

Channels for all areas.

17in. **£11.10.0**

14in. **£7.10.0**

14in. 20/-
 17in. 30/-
 Carr. Personal Collection Advised

AERIALS. BBC/ITA combined Loft and room aerials—from 25/-, BBC2/UHF and colour aerials—from 37/6. SEND FOR FREE LIST.

EX-MAINTENANCE TESTED TUBES

17in. — 35/- 14in. — 15/-
 Carriage 5/- Satisfaction Guaranteed.

RE-GUNNED TUBES

Guaranteed one year

121 in. **99/6**

Carr. 10/6. Add 10/- refundable on OLD TUBE (110° Tubes in stock).

17 in. **79/6**

15,14 **59/6**

12 in.


S. W. R.

STANDING WAVE RATIO

INDICATOR

for 1.8Mc/s-30Mc/s

by D. Gibson, G3JDG

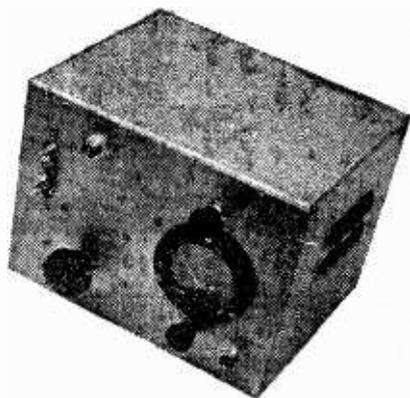

It is sometimes said that an amateur station can be judged by its auxiliary equipment. The station operator who has transmitter, receiver, and frequency meter as the sum total of his possessions can barely claim to be a "ham".

The subsidiary equipment mostly consists of small easily built units and any excuses such as lack of time or ready cash are, to say the least, a little thin. A grid dip meter is no more than a single valve oscillator with its grid current metered. An absorption wave meter consists of even less.

When it comes to loading the aerial and radiating r.f. the need for a means of tuning and loading accurately is definitely desirable. At this point, our tyro with minimum equipment will triumphantly exclaim that his pi-tank matches most things he feeds it into. That the meter situated in the h.t. to the p.a. gives all the indication that is needed as regards loading, and that by using the "tuning for a slight dip" technique, contacts have been made.

Since the proof of any pudding is in the eating, it should, therefore, surely follow that the p.a. is working efficiently, loading is correct and that the radiated r.f. furnishes all the necessary proof of this. Unfortunately, tuning for the proverbial slight dip does *not* mean that everything is working efficiently.

It is possible to tune a rig by this method and have a standing wave ratio much higher than is either desirable or necessary, and the higher the s.w.r. on the line, the less efficient the whole thing becomes. It is not proposed to split technical hairs over this business of s.w.r., nor is it proposed to launch into a discussion on transmission lines, as books exist which already do this.

However, whenever experts meet, the first thing they usually do is to define terms to make sure that they all mean the same thing, and that they are all "talking the same language". What is good enough for the experts is good enough for us.

When we say that a standing wave ratio exists we shall take it to mean that some of the power which should have radiated into space from the aerial is, in fact, being reflected back down the feeder, and thus the efficiency of the aerial system

is not 100%. In other words, we are wasting power, heating the coaxial, or warming the worms.

Obviously, a device which can give a direct indication of this s.w.r. is very desirable because it would allow things to be adjusted until a minimum was obtained. Fig. 1 shows a simple arrangement used by many amateurs and SWL's. It is a half-wave dipole, and is fed at the centre with 75Ω coax, thus offering a good match.

The centre of the dipole, has an impedance of around 75Ω; the coaxial has an impedance of 75Ω so any r.f. proceeding up the coaxial "sees" no difference of impedance, and we have a perfect match. (For the purpose of simplifying matters we are ignoring the fact that the dipole is a balanced system and that coaxial is not.) The s.w.r. is said to be 1:1.

Our dipole is only a perfect match, however, at one frequency, the frequency for which it is cut, and directly the rig is tuned up the band a few kc/s we have a mis-match. The dipole no longer exhibits a pure resistance of 75Ω. It now shows reactance as well, and this reactance will either be capacitive or inductive depending on whether we are above or below the original frequency. All this boils down to the fact that now, we have a s.w.r. on the line.

NOTE:—Tuning our pi-tank for the above mentioned dip will not tell us much. As far as the meter is concerned it merely indicates a dip in p.a. current. An r.f. ammeter in the feeder is of little

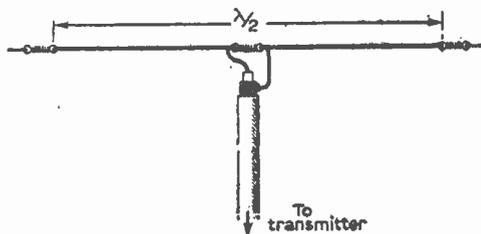


Fig. 1: A simple half-wave dipole.

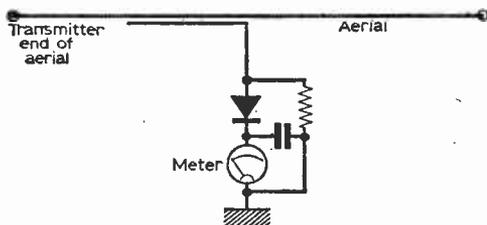


Fig. 2: This arrangement although favoured by some does not, however, provide much information about the s.w.r.

use in informing us of any s.w.r. and its reading would vary depending on where it was situated in the feed line.

This, of course, applies to odd lengths of wire tuned up by our faithful pi-tank on different bands. On one band it may be at a point in the system of high current and indicate a reading of say "7" and on another band it may be at a point of high voltage where very little current exists, and the maximum reading on this band may well be only 1 or 2.

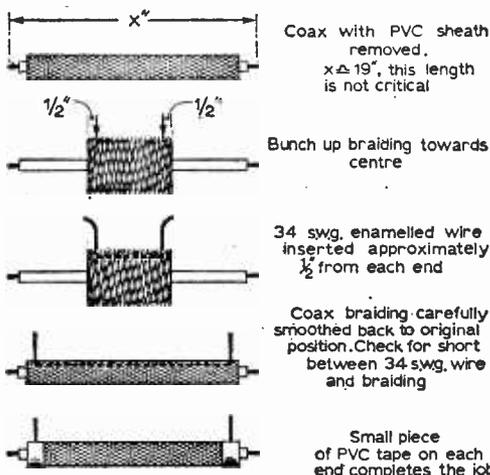


Fig. 4: Stages in the construction of the coaxial conductor element of the circuit.

One possibility is to construct an r.f. voltmeter to pick up a "sniff" of r.f. off the line, rectify it, and apply the resultant voltage to a suitable meter. This circuit can be very simple, and also very small in size (Fig. 2). This method is favoured by some, but once again although it now indicates output, and not just p.a. current it still tells us very little about the s.w.r.

If we are still determined to have some means of visual indication of s.w.r. we may well delve into the appropriate text books and find that a circuit exists which will perform this elusive function. It is referred to by the very grand name of an "H.F. Reflectometer".

The arrangement seen by the writer, required that "the concentric line be converted to a parallel plate line". It then went on to describe how the various strips of the conductors were mounted with pieces of perspex spacers and lengths of 16s.w.g. wire. The setting up of the monster so frightened the writer that it was thought that perhaps our tyro has a point. So long as sufficient r.f. was radiated to bring contacts why worry?

It was not until a circuit appeared which was a brilliant piece of simplicity called the Moni Match that things really appeared interesting. This circuit suggested that instead of two diodes and attendant "Meccano" of the concentric/parallel plate line business, why not use an ordinary piece of coaxial and add to it a length of ordinary thin enamelled copper wire and switch the r.f.? Result—super simplicity, compactness, and a reduction in the number of components required.

The circuit of the entire instrument is shown in Fig. 3. Note that it is not unlike Fig. 2 but with a very great advantage that it can read the output or reflected wave (s.w.r.) merely by flicking a switch. It uses components, which are easily obtainable and inexpensive, and the entire instrument might perhaps be constructed in one of the sloping fronted meter cases available.

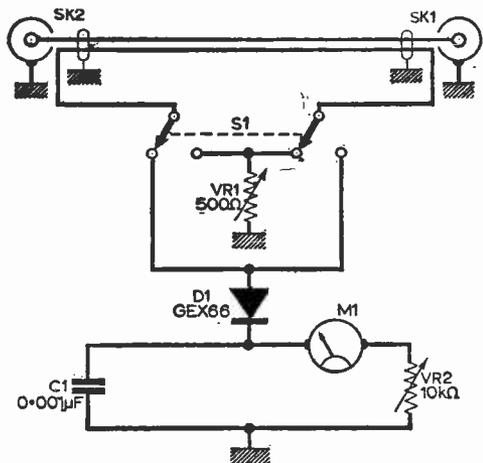


Fig. 3: The complete circuit of the instrument, representing a considerable improvement on Fig. 2.

COMPONENTS LIST	
VR1	500Ω carbon pot.
VR2	100kΩ carbon pot.
C1	0.001μF
M1	0-500μA f.s.d.
D1	GEX66
S1	2-Pole, 2-way switch
SK1, SK2	Coaxial socket chassis mounting
	19 inches coaxial cable
	24 inches 34 s.w.g. enamelled wire
	Case, Messrs. H. L. Smith, Edgware Road

THE KEENEST TAPE RECORDER BARGAIN OF THE YEAR!



A 24 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- carr. Supplied in 3 Units already wired and tested. A modern Circuit for quality recording from Mike, Gram or Radio using latest B.B.R. Twin Track Monarch Type TD2 valve line up—EP86, EOL22, EM84, EZ80 and Selenium Diode. Send for detailed list—8d. stamp.

Complete Kit comprising items below. **BARGAIN PRICE 15 Gns.** +10/- Carr.

- 2-tone Cabinet and 8in. x 6in. Speaker. Size 14in. x 10 1/2in. x 7 1/2in. \$8.10.0 + 5/- Carr.
- Wired Amplifier complete with 4 Valves, front Panel, Knobs, etc. \$16.0 + 3/6 Carr.
- B.B.R. Monarch Type TD2 \$7.7.0 + 4/8 Carr.
- Accessories: Mike, Tape, empty Reel, screened Lead and Plugs, Instructions, etc. \$1.0.0 + 2/- Carr.

RECORDING TAPE

Famous American Columbia (CBS) Premier quality tape at NEW REDUCED PRICES. A genuine recommended quality Tape—TRY IT Brand new boxed and fully guaranteed. Fitted with leader and top flaps.

Standard	Double Play	Long Play	SPECIAL OFFER, 3" Meas-
5' 600' 13/-	1,200' 21/6	900' 9/0	17/8 sagc tape 100', 3/8; 3' L.P.
6 1/2' 900' 16/-	1,800' 27/6	1,200' 12/0	19/6 225', 4/8; 3' D.P. 300'. 6/6.
7' 1,200' 21/-	2,400' 47/8	1,800' 15/0	28/6 P. & P. per reel 6d.

Post & Package per reel, 1/- plus 6d. each for additional reels.

Condensers—Silver Mica. All values 5pF to 1,000pF, 8d. each. Ditto, Ceramic 8d. Tub. 450V T.A.C. etc. 0.001 mFd to 0.01 and 0.1/350V, 9d. 0.02-0.1/350V, 1/-, 0.20 Hants 1/6, 0.5 T.C.C. 1/8, etc., etc. Close Tol. M/Mica—1.0% 3pF-500pF 3d. 600-0.000pF 1/-, 1% 2pF-100pF, 9d. 100pF-500pF, 11d. 575pF, 4,000pF, 1/6. Resistors—Full Range 10 ohms-10 meg. ohms 20% 1/4 and 1/2 W. 5d. Midget type (modern rating) 1W, 6d. 2W 9d. 1/2 W. 5d. 1/4 W. 6d. (100 ohms-1 meg). Other values 9d. 1/4 W, 1/8, etc., etc.

ALUMIN. CHASSIS. 1st. plain Undrilled, folded 4 sides. 2in. deep. 6in. x 4in. 4/6. 7in. x 4in. 5/8. 10in. x 7in. 6/8. 12in. x 6in. 7/8. 12in. x 6in. 9/-. etc., etc.

Volume Controls—5K-2 Meg. ohms, 4in. Spindles Morganite Midget Type 14in. diam. 1 year. LOG or LIN. ratios less 5/-, DP. Sw. 4/6. Twin Stereo less 5/-, 8/6. DP. Sw. 8/-. Specials to order.

WAVECHANGE SWITCHES. 1 p. 12-way, 2 p. 3-way, 4 p. 6-way, 3 p. 4-way, 4 p. 2-way, 4 p. 3-way, long spindle, 9/6 ea.

RECORD PLAYER CABINETS 58/6

Carr. & Ins. 5/- Contemporary style, refined covered cabinet in two-tone maroon and cream. Size 14 1/2" x 24", fitted with all accessories including back board and Vynair fret space available for all modern amplifiers and auto-changers etc. Output record player mounting board 14 1/2" x 12 1/2" supplied.

2-VALVE 2 WATT AMPLIFIER EZ80 and Twin stack 2CL with vol. and neg. feedback tone control A.C. 200/250v. with knob, etc., ready wired to fit above cabinet. \$2.17.6. P. & P. 1/6. 7" x 4" Speaker and trans., 22/-. P. & P. 2/-.

COMPLETE R/PLAYER KIT. As ill. inc. BBR U414 Unit. New Bargain Price. Now only \$11.10.0. 7/8 carr. Double wound tape Tr. no free chaste.

BONDACOVET Speaker Cabinet Acoustic Wadding (1in. thick approx.) 12in. wide, any length cut, 1/6 ft. 4/- yard. **TINNED COPPER WIRE** 16-22x. 2/6 1/2 lb. **EMIN MULTICORE SOLDER.** 60/40 4d. per yard. (Cartons 2/6 each)

TYGAN FRET (contem. pat.) 12 x 12in. 3/-; 12 x 18in. 3/-; 12 x 24in. 4/-, etc. **VYNAIR** (ditto) 21 sq. ft. **EXPANDED ANODISED METAL.** Attractive gilt finish 4in. x 4in. diamond mesh 4/6 sq. ft. Multiples of 6in. cut. Max. size 4ft. x 3ft. 4/76 plus carr. Do. finer patterned mesh, 4/6 sq. ft. multiples of 12in., max. size 3 ft. x 3 ft. 8/76 sheet.

ENAMELLED COPPER WIRE—4in. reels 14g-20g, 2/8; 22g-28g, 3/-; 30g-34g, 3/8; 36g-38g, 4/8; 39g-40g, 4/8, etc.

JASON FM TUNER UNITS Designer-approved kits of parts. **FMT1, 6 gns.** 4 valves. 80/-, **FMT2, 7 gns.** 5 valves. 35/-, **JTV MERCURY 10 gns.** I.T.V.E \$18.10.6, 4 valves, 28/6. **NEW JASON FM HANDBOOK, 9/6.** 48 hr. Alignment Services, 7/6. P. & P. 2/6.

TRIMMERS. Ceramic (Compression Type)—30pF-500pF, 70pF, 9d., 100pF/100pF, 1/8; 250pF, 1/8; 600pF, 1/8.

PHILIPS. Bee Hive Type (conc. spaced)—2-8/6. 1/-; 3-30pF, 1/-.

KNOBES—Modern Continental Types Brown or Ivory with Gold Ring; 1" dia., 9d. each; 1 1/2" dia., 1/6 each; Brown or Ivory with Gold Centre, 1" dia., 10d. each; 1 1/2" dia. each. **LARGE SELECTION AVAILABLE.**

METAL RECTIFIERS, 570 Types—R.M.L. 4/8; R.M.S. 2/6; R.M.S. 7/8; R.M. 18/-; R.M.S. 21/-; R.M.48, 17/8.

TUB-ELECTROLYTIC-CAN 25/25v, 60/12v, 1/8; 8+8/450v, 4/8; 50/50v, 100/100v, 9/-; 88+88/275v, 4/6; 8/450v, 4/350v, 2/8; 60/50/350v, 6/8; 16+16/450v, 5/8; 60/250/275v, 12/6; 32+32/450v, 6/8; 100+200/275v, 12/6



Est 1949



MULLARD "3.3" & "5.10" HI-FI AMPLIFIERS "3.3" Amp., 3 valves, 3 w.

Hi-Fi Amplifier at reasonable cost Bass Boost and treble controls quality sectional output transformer, 40 0/5-25 kc/s + 1 dB, 100mV for 3V, less than 1% distortion. Bronze escutcheon panel. Power take-off available. Complete Kit only \$8.19.6. Carr. 5/-

Wired and tested 8 gns.

MULLARD "5.10" AMPLIFIER. 5 valves 10W 3 and 15 ohms output. Mullard's famous circuit with heavy duty ultra-linear quality output transformer. Carr. and Ins. 7/6.

Basic amplifier kit price \$8.19.6

Ready built 11 1/2 gns.

CONTROL PANEL KIT. Bass, Treble and Volume controls with 4-position selector switch for radio tape and 11in. x 4in. escutcheon panel.

AMPLIFIER KIT AND CONTROL PANEL KIT. \$11.19.8. Ditto, ready wired \$14.19.8.

2-VALVE PRE-AMP. UNIT. Based on Mullard's famous 2-valve (2xEF86) circuit with full equalisation, with volume, bass, treble and 5-position selector switch. Size 9x6x2 1/2in. Complete Kit \$8.19.6. Carr. 3/6. Ready Built \$7.19.8.

6 VALVE AM-FM TUNER UNIT Med. and VHF 190 M-550 M. 85Mc/s-102Mc/s. 6 valves and metal rectifier. Self contained power unit. AC 200-250v. operation. Magic eye indicator. 3 push-button controls, on/off, Med., VHF diode and high output sockets with gain control. Illuminated 2-cool. perspex dial 11 x 4in. Chassis 18 x 4 x 6 1/2in. recommended Fidelity Unit for use with Mullard 3/5 5-10 amplifiers. Available only at present as built-up units, aligned and tested ready for use. Bargain price \$12.10.0. Carr. 5/-. We hope to produce this popular unit in kit form very shortly.



DE-LUXE RECORD PLAYER KIT

Incorporating 4 Sp. Garrard Auto-81mm unit and Mullard latest 3 watt printed circuit amplifier (ECL 86 and EZ 80), vol. bass and treble controls, with 3" x 5" 10,000 line speaker. Contemporary styled 2-tone cabinet, charcoal-sprey and off-white with matching blue relet. Size 17 1/2" x 18" x 8". A stylish unit capable of quality reproduction. Circuit and const. details 2/6 (free with kit)

COMPLETE KIT Carr. and Ins. 10s. **£13.19.6**

Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250v. operation. Magic-eye tuning. Circuit diagram now available. Aligned and tested ready for use \$12.10.0. Carr. & Ins. 7/6

Complete with 4 Knobs—walnut or ivory to choice. Indoor FM speaker 8/6 extra 3 ohm F.M. Speaker only required. Recommended Quality Speakers 10in. R.A. 27/6; 12 1/2 x 4in. E.M.A. 'Fidelity' 8/76; 12in. R.A. with conc. Tweeter, 42/6. Carr. 2/6.

TRANSISTOR COMPONENTS

Midget 1 P.F.—465 Kcs 9/18in. diam. 0/2-0.5/8

Osc. Coil M. & L.W. 5/19

Midget Driver Trans. 3.5.11. 6/9

Midget Output Trans. Push-Pull—3 ohms 6/9

Elect. Condensers—Midget Type 1 mFd.-50 mFd. ea. 1/8, 100 mFd. 2/-, 12V

Condensers 150 v. working: .01 mFd., .02 mFd., .03 mFd., .04 mFd. 9d.; .05 mFd., .1 mFd., 1/-; .25 mFd., 1/3; .5 mFd., 1/6, etc.

Midget Tuning Condensers, J.B. "O" 200 pF and 125 pF, 8/6, ditto with trimmers, 9/6, J.B. 220 pF and 105 pF conc. slow motion 10/8. 385pF single 7/6. Sub. min. 4in. Dialexin 100 pF, 300pF, 500pF, 7/- each.

FERRITE AERIALS, M. & L.W. car aerial coil 9/6.

Midget Vol. Control with edge control knob. 5 K/ohms. with switch 4/9. Ditto less switch 3/9.

Speakers: F.M.; 2in. Pleasay 7/6 ohms 1/6. 2 1/2in. Continental 5 ohms, 13/6. 7 x 4in. Pleasay 35 ohms, 22/6.


Ear Plug Phones—Min. Continental type 3ft. lead, lock plug and socket. High Imp. 8/-, Low Imp. 7/6.

Brand New. Mfrs. 1st grade. 1 OC44 & 2 OC45, 16/6, 1 OC81D & 2 OC81, 16/6. All above and OAS1, 22/6. Post Free.

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up EGCS5, ECH81, EF89, EAB30, EL84, EM81, EZ80. Three Waveband and Switched Gram. Positions. Med. 200-550 m. Long 1,000-2,000 m. V.H.F./M. 88-100 Mc/s. Philips Continental Tuning Inset with permeability tuning on FM and combined AM/FM IF transformers. 400 Kc/s. and 10.7 Mc/s. Dual cone tuning all calls. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 12 1/2 x 6 1/2in. Height 7 1/2in. Edge illuminated glass dial 11 x 4 1/2in. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250v. operation. Magic-eye tuning. Circuit diagram now available. Aligned and tested ready for use \$12.10.0. Carr. & Ins. 7/6

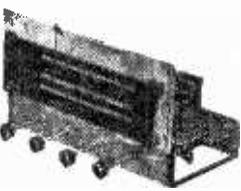Complete with 4 Knobs—walnut or ivory to choice. Indoor FM speaker 8/6 extra 3 ohm F.M. Speaker only required. Recommended Quality Speakers 10in. R.A. 27/6; 12 1/2 x 4in. E.M.A. 'Fidelity' 8/76; 12in. R.A. with conc. Tweeter, 42/6. Carr. 2/6.



We manufacture all types Radio Mains Transf., Chokes, Quality O/P Trans., etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain lists, 3d stamp.

RADIO COMPONENT SPECIALISTS
70 Bristock Rd., Thornton Heath, Surrey. Hours: 9 a.m.-6 p.m., 1 p.m.-Wed. THO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 1 lb. 9d.; 1 lb. 13s. 3.6d. 2/8; 5 lb. 2/8; 8 lb. 3/6.



EAGLE STOCKISTS

The following are available:

TF703	Transistor tape recorder	£18.76
T1206	Transistor intercom	£4.60
TA790	Telephone amplifier	£3.46
730	Zephyr 7 transistor radio	£4.16
SA80	8 watt stereo amplifier	£10.56
100C	Microphone	£1.15
DM175	Microphone	£2.10
MC70	Microphone	£2.17
DM17HL	Microphone	£4.95
DM18HL	Microphone	£4.17
DS2	Microphone Desk Stand	£1.20
FS3	Microphone Floor Stand	£3.24
GT60	Radio Jack	£1.70
TD78	Tape head demagnetizer	£1.20

TRANSISTORS

AC115	4/-	OA79	3/-	OC75	5/6
AC155	4/-	OA81	2/-	OC76	8/6
AC156	5/6	OA85	3/-	OC78	8/-
AC154	5/6	OA86	4/-	OC79	8/-
AC113	5/6	OA90	3/-	OC81	5/6
AC307	7/-	OA91	3/-	OC82	10/-
AD340	25/-	OA95	3/6	OC83	4/-
AF102	27/6	OC16W	35/-	OC84	8/-
AF111	11/-	OC19	25/-	OC139	8/-
AF116	10/6	OC26	25/-	OC140	19/-
AF119	5/-	OC35	12/-	OC141	31/-
AF117	8/6	OC36	21/6	OC189	10/-
AF118	20/-	OC41	8/6	OC170	8/6
AF119	11/-	OC42	6/-	OC171	6/-
AF120	10/6	OC43	12/6	OC200	10/6
AF126	10/-	OC44	5/-	OC201	29/-
AF127	9/6	OC45	5/-	OC202	24/6
BY100	7/6	OC70	6/6	OC203	13/-
BY114	6/-	OC71	4/3	OC204	19/-
GEF113	8/6	OC72	5/6	OC812	8/-
GEF114	6/6	2XOC72	5/6	MAT100	7/6
GEF115	9/6	matched		MAT101	8/6
GEF116	17/-	pair	16/-	MAT120	7/6
OA70	3/-	OC73	18/-	MAT121	8/6
OA73	3/-	OC74	8/-	ADT140	15/-

MM4	Microphone mixer	£2.13.6
PS35	3.5mm plug and socket	2.8
PS25	2.5mm plug and socket	2.8
F01	Standard jack plug	2.8
SP31	Standard shielded jack plug	3.0
OC34	Standard socket	2.3
SS3271	Sub-min slide switch DPDT	2.3
SS219	Min. slide switch DPDT	2.3
MR4	Earphone low res	3.3
MR30	Earphone with ear hanger	4.4
CR5	Earphone crystal	4.4
T501	Vernier dial	13.8
T502	Vernier dial	15.0
T503	Vernier dial	17.3
TC301	Turnover cartridge	11.0
K418	Volume control	3.3
PVC105	Variable condenser	3.3
LT44/700	Transistor transformers (pair)	8.9
TP100	Telephone pick-up coil	10.3
SP20	High resistance headphone	13.0
BM36R	Lapel microphone magnetic	3.3
MCI	Microphone crystal cartridge	4.9
TP26G	21in. speaker	9.3
CM16	Guitar pick-up	13.6
CM35	Guitar microphone	£3.4.6
EP50K	50,000 O.P.V. multimeter	£10.16.0
EP30K	30,000 O.P.V. multimeter	£7.11.0
EP20K	20,000 O.P.V. multimeter	£5.7.6
EP10K	10,000 O.P.V. multimeter	£4.6.0
TK20A	1,000 O.P.V. multimeter	£2.13.0
L20	Leather Case for EP30K	£1.1.0
MR2P	500 microamp panel meter	£2.3.0

MR2P	500 microamp panel meter	£1.12.0
MR2P	1 mA panel meter	£1.12.0
MR2P	5 mA panel meter	£1.12.0
MR2P	300 volt panel meter	£1.12.0
SR2P	"S" panel meter	£1.13.0
MR3P	1 mA panel meter	£2.13.6
L71/1	Signal injector	£1.18.0
RF40	Field Indicator	£3.15.6
AR13	Test lead kit	£1.0.3

Record Player and Tape Deck Units

BSR Monarch UA25	£6.80	
BSR Monarch UA15	£6.19.6	
The new BSR Monarch UA15SS fitted with C1 ceramic stereo cartridge	£10.18.11	
TD2	Tape deck, half track	£8.18.0
TD10	Tape deck, half track	£10.5.0
BSR Monarch TU12	£3.10.0	
BSR Monarch GU7	£3.17.6	
Garrard Autoslim	£7.15.0	
Garrard AT6	£11.5.0	
Garrard SR710	£6.0.11	

All the above are also available with stereo cartridges at slight extra cost.
Sinclair Kits
 Sinclair Micro 6 £2.19.6
 T3750 Power amplifier £1.19.6
 Sinclair Micro Injector £1.7.8
 Sinclair Micro Amplifier £1.8.6
 Sinclair X10 Kit £5.19.6
 Sinclair X10 ready built £8.19.6
 Mains Unit for above £2.14.6
 Trade Enquiries Invited

SETS OF TRANSISTORS


Set No. 1: comprising OC81, 2 x OC45, OC81, matched pair OC81, 204.
 Set No. 2: comprising OC81, matched pair OC81, 12/6.

CATALOGUE

Our latest 1964/65 Catalogue is now available. Copies have been sent to many of our regular customers. If you have not received your copy please drop us a card. Please send it in stamps. Wholesale terms to Schools, Universities and Business Houses. Trade Catalogue now available. Please apply on business letter heading.

TERMS: Cash with Order or C.O.D. Postage and Packing Charges extra. Single valves 9d. Minimum Parcel Post charges 2/-. Please include sufficient postage with your order. Minimum C.O.D. fees and postage 3/6. These Postal Rates apply to U.K. only. For full terms of business see inside cover of catalogue. Personal shoppers 9 a.m. to 5 p.m. Mon. to Friday, Saturday 10 a.m. to 1 p.m.

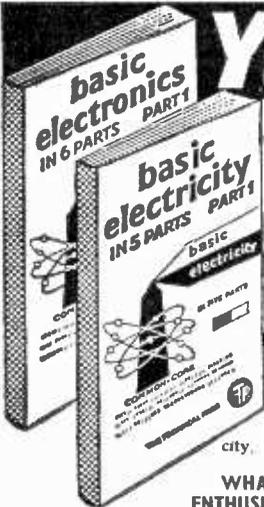ALPHA RADIO SUPPLY CO., 103 LEEDS TERRACE, WINTOUN ST., LEEDS 7



YOURS FREE FOR 7 DAYS

The New 'Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate, cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

EVERY DAY WE RECEIVE LETTERS PRAISING THESE BOOKS, HERE ARE A FEW FROM THIS MONTH'S POSTBAG. "The Manuals have my wholehearted support." I never fail to recommend them," signed Student Teacher. "Your Manuals have taught me more in one week than I have learned during the past eight years," A.C.D., Blackpool. "Thank you for a really first class set of Manuals; I am delighted." D.E.F., Manchester. A TECH-PRESS PUBLICATION

To Selray Book Co.
 60 Hayes Hill, Hayes, Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts). 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).
 BASIC ELECTRICITY BASIC ELECTRONICS

Signature
 (If under 21, signature of parent or guardian)

Name
 BLOCK LETTERS BELOW
 FULL POSTAL
 Address

POST NOW FOR THIS OFFER!!


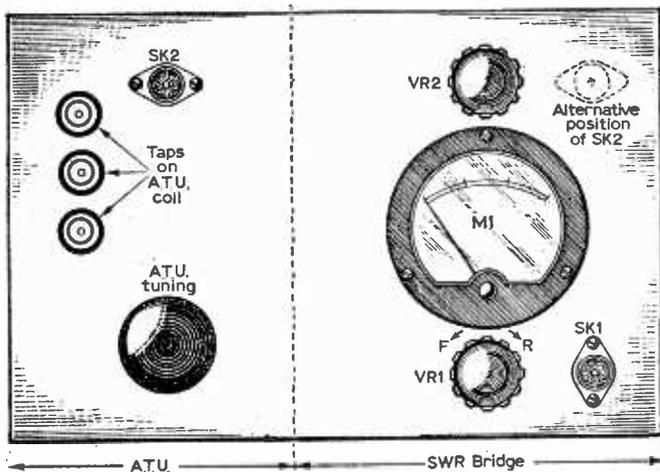


Fig. 5: The front panel of the controls, sockets, etc. SK2 could take the alternative position indicated.

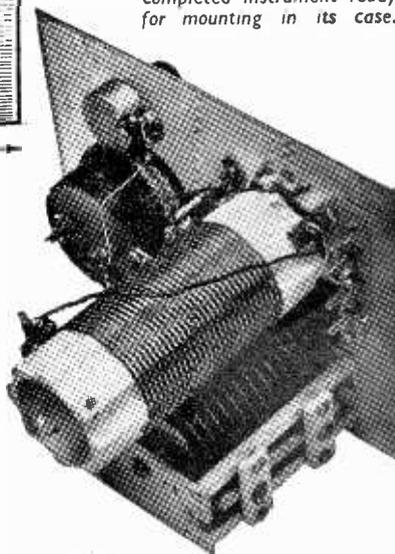Below: A rear view of the completed instrument ready for mounting in its case.



The unit shown was constructed in an aluminium case because an a.t.u. was also built into the same case. The a.t.u. is nothing more than a coil and capacitor both purloined from one of the T.U. series. The meter used is a 0-500 μ A and is from the ex-Govt. 19 set. These are freely available at 15s. or less on the market, although any similar meter would be suitable.

The only part of the unit requiring any special treatment is the length of the coaxial with its added conductor, and this is really quite a simple matter when it comes down to actual construction.

Take a piece of 75 Ω coaxial as shown in Fig. 4 and bunch up the braiding a little. Next take one of the XYL's sewing needles and thread a length of 34s.w.g. enamelled wire. Push the needle under the co-ax braiding about $\frac{1}{4}$ in. from the end and work the needle along and out of the coaxial $\frac{1}{4}$ in. from the other end (By means of a magnet perhaps?).

Warning:—Work the needle along, don't work the wire, you might accidentally scratch off some of the insulating enamel.

Next, check with the meter that there is no short between the piece of enamelled wire and the coaxial braiding. A small scrap of p.v.c. tape around each end completes the job. Apart from keeping all leads (especially around the switch) as short as possible the wiring-up requires no further comment.

When the unit is completed, it has to be calibrated, and to do this a dummy load is required. A carbon resistor of the same value as the line is required i.e. for 75 Ω coaxial a 75 Ω resistor is required. It should be capable of withstanding the power output of the transmitter, and a number of resistors may be wired in series/parallel if desired or the transmitter power may be reduced.

For those who are unable to obtain a 500 Ω carbon pot. (R1), a number of carbon resistors may be substituted one at a time until a good null has been obtained (See notes on setting up). Although this method may take a little longer it is an improvement on using a pot., since any slight reactance offered by the pot. is then eliminated.

Setting-up

The actual setting up follows a logical pattern, and if taken a step at a time the whole process is fairly straightforward.

1. Plug transmitter output into SK1 and connect dummy load to SK2.
2. Switch S1 to forward and tune transmitter. This is best done on the highest band to be used.
3. Adjust R2 so that M1 reads f.s.d. or highest reading on its scale, which ever is the greater.
4. Turn S1 to reflected and again adjust R2 for maximum reading or f.s.d. whichever is the greater.
5. Adjust R1 for minimum reading.
6. Switch back to forward and readjust R2 slightly for maximum reading on M1.
7. Switch S1 to reflected and check that the null is still there.
8. Swap the transmitter and dummy load i.e. plug transmitter into SK2 and dummy load into SK1.
9. The readings should still tally near enough with the previous ones obtained in 6 and 7.
10. The unit is now ready for use, the transmitter is plugged back into SK1 and the dipole or a.t.u. etc., into SK2. ■

CLUB

NEWS

BRADFORD RADIO SOCIETY

Hon. Sec.: Eric G. Barker, G3OTO, 63 Woodcot Avenue, Baildon, Nr. Shipley, Yorkshire.

On 15th December there was a Ladies' Night, and members brought along their colour slides for a film show.

At an informal meeting held on 5th January, the guests were members of the Spen Valley Amateur Radio Society and the Leeds Radio Society.

BROMSGROVE AMATEUR RADIO CLUB

J. Harvey, 22 Elm Grove, Bromsgrove, Worcestershire.

A meeting will be held in the Co-operative Rooms (corner of High Street and Stratford Road, Bromsgrove) on Friday, 8th January, at 8 p.m.

As this was an inaugural meeting, radio amateurs and short wave listeners were invited to attend with suggestions and comments.

CHESTER AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: P. J. Holland, Field House, 19 Kingsley Road, Great Boughton, Chester.

A technical film show was seen by members on 8th December, and on the 15th there was a Christmas Surprise Night. On 22nd December there was a general discussion and the month's activities concluded with a Net Night on 29th December.

CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec.: J. Ross, G3OGE, 63 Broomfield Road, Beckenham, Kent.

The annual Constructional Contest was held on 4th December, and an informal social was held later on in the month.

Workshop improvements have now been completed, thanks to a handful of members, and meetings are held on Wednesday and Friday evenings.

COVENTRY AMATEUR RADIO SOCIETY

Hon. Sec.: E. E. Snow, G3TKO, 11 Lupton Avenue, Coventry.

On 7th December there was a film show, and on the 14th there was a demonstration and lecture on construction of the Club top band transmitter. On 21st December there was a social evening, and on the 28th, A Night on the Air. A film show was seen by members and friends on 4th January.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

There was a surplus sale on 2nd December, and on the 9th there was a constructors' contest for the Founder Members' Trophy, with a contest for the G5YY Trophy on the 13th.

The 16th December was an Open Evening with a Juniors' meeting and a members' committee meeting. The Annual Christmas Party was held on 23rd December and on the 30th there was a film show entitled "The Year in Retrospect" when members brought along transparencies which they had taken during the year.

GOSPORT AND DISTRICT RADIO CLUB

Hon. Sec.: J. T. Nightingale, 9 Beatty Drive, Alverstoke, Gosport.

This Club's meetings are held every Monday evening at 7 p.m. at the Gosport Community Centre, Bury House, Bury Road, Gosport. Local radio enthusiasts and would-be enthusiasts are welcome to go along and join in the numerous activities.

GUILDFORD AND DISTRICT RADIO SOCIETY

Hon. Sec.: D. H. Mead, G3OXI, 41 Egley Road, Woking, Surrey.

The speaker on 11th December was Mr. M. Childs, F.S.A., President, who spoke on "The Operation of Practical Equipment from 1900-1922".

On 19th December there was a Christmas Social Evening at "The Otter". This was a light-hearted evening in the seasonal spirit to which all members, their ladies and friends were invited.

HALIFAX AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: J. Ingram, G3RMQ, Lambert House, Greetland, Halifax, Yorkshire.

On 29th December, members brought along their receivers and had a general discussion on their equipment.

On 26th January, there will be a talk entitled "Radio a long time ago", given by Mr. J. J. Platt, G2VO.

Huddersfield Amateur Radio Club

R. Highton, 5 Brian Avenue, Dalton, Huddersfield, Yorkshire.

Meetings are held fortnightly on Thursday evenings, beginning at 7 p.m. The evening usually begins with c.w. practice for the short wave listeners, followed by lectures. Field days and outings are held regularly. Members were very pleased with GB3CMS which was the "Jamboree on the Air" station.

MELTON MOWBRAY AMATEUR RADIO SOCIETY

Hon. Sec.: D. W. Lilley, G3FDF, 23 Melton Road, Ashfordby Hill, Melton Mowbray, Leicestershire.

On 31st December, Mr. L. Fisher, G4MK, and Mr. D. Fisher, gave a talk on the use of test gear. There will be a lecture on 28th January, by Mr. J. L. Warrington, G2FNW, entitled "Flat Line Equipment for 23 cms."

MID-WARWICKSHIRE AMATEUR RADIO SOCIETY

Hon. Sec.: T. Inkester, 13 Dormer Place, Leamington Spa, Warwickshire.

The 2nd November meeting saw the inauguration of a series of informal lectures on the fundamentals of radio. These lectures will alternate with evenings at which the newly acquired A/T gear will be operated by G3HBX/A.

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY

Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogdon, Halifax, Yorkshire.

The Club's Annual Dinner was held on 9th December, and a ragchew was held on the 23rd.

On 6th January A. W. Waldsley, G3ADQ, gave a talk entitled "SSB Trends".

PLYMOUTH RADIO CLUB

Hon. Sec.: R. Hooper, G3SCW, 2 Chestnut Road, Peverell, Plymouth, Devon.

On Saturday, 19th December, the Club supported the Torbay Amateur Radio Society Christmas Party and Quiz.

Saturday, 6th February, is the Club's Annual Dinner and Social Evening.

READING AMATEUR RADIO SOCIETY

Hon. Sec.: R. G. Nash, G3EJA, "Peacehaven," 9 Holybrook Road, Reading.

The meeting held on 19th December was devoted to the judging of the Constructional Contests.

The Annual Dinner will be held at the White Hart, St. Mary's Butts, Reading, on 9th January.

SLADE RADIO SOCIETY

Hon. Sec.: D. T. Wilson, 177 Dower Road, Four Oaks, Sutton Coldfield, Warwickshire.

An annual Fun and Games Evening was held on 11th December. The evening included the annual Cricket Match between the President's and Secretary's teams.

WELLINGBOROUGH RADIO CLUB

Hon. Sec.: J. Baker, 34 Essex Road, Rushden, Northamptonshire.

On 3rd December, members heard a talk on Radio Control. There was a General Meeting on the 10th and the annual Christmas Dinner on the 17th. On 7th January members saw a film show entitled "The Race for Space".

MR. M. A. TRICKETT, G3SAT, and licensee of club radio G3SOH is attempting to obtain a concession in the licence conditions of Club Radio Stations so that anyone may speak into the microphone under the supervision of the licensee or authorised additional operator, provided that the aforesaid actually operates the apparatus.

Mr. Trickett seeks the support of other club members who may be interested in this cause and will forward further information if they will write to him at: 15 Egerton Road, Bembridge, Isle of Wight.

New list of Bargains


Transistor ferrite rod aerial with medium and long wave coils with circuit. 7/6.
 Oscillator Coil and set of 3 I.F. transformers for transistor set with circuit. 12/6.
 Tuning Condenser to suit. air-spaced with trimmer. 9/-.
 Dittio but sub. min. 7mm. 10/- the set; two gang. Condensers to suit. 8/6 (request sub. min. circuit).
 Midget Sin. P.M. Loudspeaker 3 ohm 12/6, 80 ohm 13/6.
 Midget 208 pF + 176 pF two-gang Tuning Condenser with trimmers for transistor set Price 9/-.
 Push-Pull Transformer. Sub-miniature 8/6. 0005 mfd. Single Tuning Condenser. Solid dielectric 1in. aptitude for transistor or crystal set, with spindle tapped 6 BA. 2/6.
 48 Sets (Receiver/Transmitter pack set). Unused sets complete except for crystals. Packed with parts and easily rebuildable into other gear. 19/6 each. Post 3/-.
 Battery Charger Kit. Comprises 5 amp. transformer, 5 amp. rectifier, metal case and meter to charge 6 or 12 volt batteries up to 5 amps. With variable charge rate, 39/6 each. Post and insurance, 3/6.
 Mains Transformer. 250-0-250 at 80 mA. 6.3 volts, 5a (normal mains input). 12/6 each. Carriage 2/6.
 Output Transformer. Standard pentode matching type. 3/6 each. 36/- per doz.
 Slide Switch. Sub-miniature but d.p.d. 2/- each, 18/- per doz.
 T.C.C. or Dubilier Tubular Condensers.
 .5mf 500 v. 10/- doz.
 .25 mf 500 v. 7/6 doz.
 .25 mf 350 v. 6/- doz.
 .05 mf 500 v. 5/- doz.
 .0001 mf 1,000 v. 9/- doz.
 .001 mf 1,000 v. 8/- doz.
 .002 mf 1,000 v. 7/6 doz.
 .005 mf 1,000 v. 9/- doz.
 .02 mf 750 v. 8/8 doz.
 .01 mf 1,000 v. 10/- doz.
 Battery Charger Rectifier—selenium 12.15 v. 5 amp. 9/6.
 Metal Chassis—punched for Mullard 510 Amplifier, complete with inner screening sections and stove enamelled. 12/6 set.
 Filament Transformer, 6.3 v. 14 amps. 6/6.
 Neon Lamp—midget wire ended. Ideal mains tester, etc. 2/-. Ex. Govt. 1/8.
 Phillips Trimmers—0.20pF 1/- ea., 9/- doz.
 Tag Panels. Ideal for constructors, experimental circuits, etc. 3 of each of 12 different types. 5/-.
 Snydlok Panel Mounting Fuses with carrier. 5 amp. 2/- each. 15 amp. 2/6 each.
 Metal Rectifier. 250 v. 60-80 milliamperes ideal for mains set or instrument or to replace that expensive valve. 4/6.
 Piano Key Type Switches. 3 key type 2/-. 11 key type 3/6. 5 key type 4/6, post and packing 1/- regardless of number ordered.
 Ozone Outfit, for removing smells and generally improving any oppressive atmosphere. Kit consists of Philips ozone lamps and mains unit, only needs box. 19/6 + 3/6 postage and insurance.
 Black Light Unit, 125 watt intensity, comprises quartz lamp, adjustable lamp holder and 125 watt choke. Only 29/6 + 6/6 carriage and insurance.
 Packard Bell Pre-Amp. Contains a relay, push-pull input and output transformers and many useful spares. Less valves 6/6 each + 2/6 post and insurance.
 Fridge Handles, with Yale type locking mechanism, two keys and striking plate. 3/6 + 2/- post, 8 or 30/-, post free.
 0-1mA Meter made by the American Westinghouse Co. 3in. diameter, flush mounting scale calibrated in volts. 25/- + 2/- post and insurance.
 Ferranti Fire Bar. 500 watt 10in., 3/6 each + 1/6 post. Three or more post free.
 67G Valve Holder. Best make (Amphenol). 3/- dozen, post 1/6. 3 dozen, post free.
 Precision Wheatstone Bridge. opportunity to build—1,00k wire wound 15 watt potentiometer, price 5/- + 1/- postage.
 Cydon Turret Tuner. 25 Mr.s. with hand 1 and band 3 coils. Brand new. 9/6 each post 2/6.

GOOD COMPANION MARK IIIB

The 6 transistor set with the 5 transistor performance. Incorporating all the latest requirements. Anyone who can solder can make it. Many thousands already in use all over the country. Full coverage of Long and Medium wavebands. Fine looking cabinet, size 11 x 8 x 3in. Q.F.P. Output approx. 750 mW. Excellent reception of difficult stations like 208. Variable feedback gives excellent tone. **£5.19.6**
 Plus 4/- post and insurance.



OUR BARGAIN OF THE YEAR

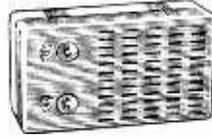

A complete kit of parts to build 6 transistor 2 wave superhet receiver at only 45/-. Post and Ins. 3/6.
"CORONET" Mk. IV
 It fully covers the medium waveband and that part of the long wave band to bring in B.B.C. Light. The circuit includes a highly efficient slab aerial and 2 1/2in. P. M. speaker. Overall size approximately 4 1/2 x 2 1/2 x 1 1/2in. Supplied complete with carrying case.

Infra Red Heater


Make up one of these latest type heaters, ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—nice silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt element and metal casing as illustrated 19/6 plus 2/6 post and insurance. Pull Switch. 3/- extra.



-THIS MONTH'S SNIP-
 Superhet Heart comprising a three waveband coil pack, 3 460kc I.F. transformers, valves type 6X5 frequency changer, 6K7 1P7 and 6X7 D.D.T. and 3 octal valve-holders with circuit diagram showing how to make superhet receiver or tuner unit, to drive amplifier, tape recorder, etc. etc. Retail value over £4 this month's snip offer, all for 19/6 plus 3/6 post and insurance.

INTERCOM BARGAIN

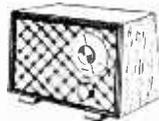Cabinet as illustrated, less knobs, ideal if you are making small radio, office intercom, amplifier, etc. Has the modern look; originally sold at 29/6, limited quantity available at 15/-. Plus 2/6 postage. All components to make two of the intercoms described in "Practical Electronics," 75/-.



LAST OF THESE CABINETS & PICK-UPS

Made for a famous company intending to make a Battery Record Player but changing their minds. This is an extremely fine looking cabinet must have cost at least £2 to make. It is complete with handle and fasteners as illustrated. Also included in the parcel is a CosmoCORD pick-up with crystal cartridge and sapphire stylus. Both items new and perfect. Only 19/6, plus 4/6 post and insurance.



POWER PACK FOR TRANSISTORS

Designed to operate transistor sets and amplifiers. Adjustable output 6v-9 to 12 volts for up to 500mA (class B working). Take the place of any of the following batteries: P1, P2, P3, P4, P5, P6, P7, P8 and others. Kit comprises mains transformer-rectifier, smoothing and load resistor 3000 and 500 mfd condensers, zener diode and instructions. Real snip at only 14/6, plus 2/6 post.

FLUORESCENT LIGHTING BARGAINS


Complete 40 watt slimline white enamelled fitting, ready for use with choke control gear, radio suppressed starter and tube. Originally intended to sell at £3.15.0. offered at only 39/6, plus 5/- carriage and insurance; two or more carriage free.
 Dittio 30, 50 watt 49/6, plus 7/6 carriage and insurance, two or more, carriage free.

400 WATT FLUORESCENT LIGHTING OUTFIT

Built type 400 watt lamp to hang from 1 1/2 lampholder. Intended for street-lighting, ideal large open space, yard etc. Complete with choke. 40/-, plus 7/6 carriage and insurance.

MAKING AN FM TUNER

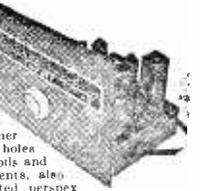Available at present, is a very nice cadmium-plated P.M. Tuner chassis with holes punched for coils and other components, also a nicely printed perspex front, calibrated usual F.M. frequencies. Real bargain 6/6 + 2/- or with two-gang tuning condenser 10/- + 2/- postage.



Speaker Bargain

12in. high-ndict loudspeaker. High flux permanent magnet type with either 3 ohm or 15 ohm speech coil. Will handle up to 100 watts. Brand new, by famous maker. Price 27/6 + 3/6 post and insurance.



Waterproof Heater Wire
 16 yds length. 70 watts, self regulating temperature control. 10/-, post free.

TRANSISTOR SET CASE

Very modern cream cabinet, size 5 1/2 x 3 x 2 1/2in. with chrome handle, tuning knob and scale. Price 4/6 plus 1/6 postage.



Building a 'Scope



3in. oscilloscope tube. American made type No. 3P17, 6.3 v. 0.6 amp. heater electrostatic deflection, brand new and guaranteed with circuit diagram of 'scope, 15/- each. Plus 2/6 post and insurance.

Simmerstat Heater Regulator
 Suitable to control elements, heaters, soldering irons and boiling rings up to 2,500 watts. Complete adjustable, normal price 55/- each, special snip price 12/6, plus 1/6 postage and insurance.

THERMOSTATS
 Type 'A' 15 amp, for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob, quickly adjustable from 30-80°F, 9/6 plus 1/- post. Suitable box for wall mounting, 5/-, P. & P. 1/-.
 Type 'B' 15 amp. This is a 17in. long rod type made by the famous Sunbig Co. Spindle adjusts this from 50-350 F. Internal screw alters the setting so this could be adjustable

over 90° to 1,000°P. Suitable for controlling furnace, oven, kiln, immersion heater or to make flame, stat or fire alarm. 8/6 plus 2/6 post and insurance.
 Type 'C' is a small porcelain thermostat as fitted to electric blankets etc. 14 amp setting adjustable by screw through side. 3/6, P. & P. 6d.
 Type 'D'. We call this the Ice-stat as it cuts in and out at around freezing point. 2 1/2 amp. Has many uses, one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (16 yds. 10/-) is wound around the pipes. 7/6, P. & P. 1/-.
 Type 'E'. This is a standard refrigerator thermostat. Spindle adjustments over normal refrigerator temperatures. 7/6 plus 1/- post.

Timer Kit
 Special offer of all components except metal box to make mains operated interval timer for photography etc. 12/6 plus 2/6 post.

Where postage is not definitely stated add 2/- all orders under £3.

ELECTRONICS (CROYDON) LTD

266 LONDON ROAD WEST CROYDON SURREY
 Post orders to: 43 Silverdale Road, Eastbourne, Sussex

TEST METERS



50,000 O.P.V. MODEL TP 58. Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in., £5.19.6.

2,500 O.P.V. MODEL TP 10. Reads A.C. and D.C. Volts up to 1,000; D.C. Current to 500mA; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +36; Output jack for Audio Measurements. Size 2 1/2 x 5 x 1 1/2 in., £5.19.6.

50,000 OHMS PER VOLT MODEL 500. Reads voltages up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 15,000 O.P.V.; D.C. current to 12 amp. Resistance to 60 Megs.; Decibels from -20 to +36; Incorporates internal buzzer for audible warning of direct shorts and blocking condenser for A.F. output measurements. Size 3 1/16 x 6 1/16 x 2 1/4 in., £5.19.6.

LINEAR AMPLIFIERS. LG34, 4 watts, size 8 1/2 x 4 1/2 x 2 1/2 in. high, £5.5.0. L45A 5 watts, size 7 x 7 x 5 1/2 in. high, £5.19.6. Protective cover, 12/6. L5/55 5 watts stereophonic, size 10 1/2 x 8 x 6 in., £12.12.0, cover with carrying handles 25/-. "Diatonic" 10 watts Hi-Fi Ultra Linear Push-Pull, size 9 x 7 x 6 1/2 in. high, £12.12.0. Cover with carrying handles, 12/6. L1/13 10 watts Hi-Fi Ultra Linear size 9 x 7 x 5 1/2 in. high, £12.12.0. Cover with carrying handles, 12/6. "Conchord" 30 watts Hi-Fi Ultra Linear size 12 1/2 x 9 x 7 1/2 in. high, £18.18.0. Cover with carrying handles, 25/-. L50 50 watts Hi-Fi Ultra Linear, size 14 x 10 x 8 in. high, £22.2.0. Cover with carrying handles, 22/6. All amplifiers for normal A.C. mains, and ex stock. Details on request.

'Tripletons' Convertible Amplifier. Size 10 x 3 x 4 1/2 in. high. 4 watts output matched for 2-3 ohms. OR 2 amplifiers can be coupled together for STEREO £6.19.6 each.


'Tripletons' F.M. Tuner, size 11 x 4 x 3 in. high. Coverage 86-104 Mc/s. £18.19.6 (unpowered), or £15.14.6 (self powered). Details on request.

SPEAKERS. Special heavy duty 15 ohms 12in. £5.5.0. Wharfedale 15 ohms 12in. for Lead Guitars £10.12.0, 16in. for Bass Guitars £17.10.0. 3 ohms 10in. 20/6. 3 ohms 8in. 22/6.

MICROPHONES. Crystal Types. Guitar 12/6. Desk, with built-in stand 15/-. Acee 39/1 Stick, and Table Stand 32/6. Super Stick, with heavy Desk Stand 42/6. Moving Coil Types. Stick, with heavy Desk Stand 59/6. "Slimline" Stick, 50K impedance, with switch 75/-. Omni-directional, chrome plated die-cast frame. 50K. with switch 99/6.

VALVE VOLT METER

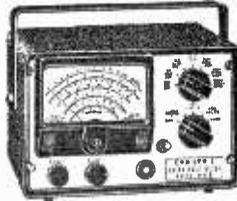D.C. Input Impedance 11 Megohms. 7 Voltage ranges, D.C. to 1,500, A.C. to 1,500 R.M.S., 4,200 Peak to Peak. Resistance 2 ohm to 1,000 Megohms. Centre zero setting for receiver alignment. Complete with A.C./D.C. probe and leads. Full illustrated details on request. **ONLY £3.19.6** (Post 3/6).



TRANSISTORISED TEST EQUIPMENT. Fully guaranteed, brand new. By NOMBREX: 150 Kc/s.—350 Mc/s. Signal Generator, £2.10.0. Resistance-Capacitance Bridge, £3.5.0. 1-16 volts D.C. Power Supply, £6.10.0. Audio Generator 10/100,000 c/s., £12.15.0. Inductance Bridge, £18.0.0.

V.T.M.K. INSULATION TESTER. Measures up to 500 megohms at 3 testing voltages, 100, 250 and 500. Supplied with leather case and leads. £17.10.0. Illustrated details on any of the above sent on request.

HETERODYNE FREQUENCY METERS, TYPE LM14. Frequency range 125-20,000 kc/s. in 2 band. This is the United States Navy Model of the well-known B2021 Frequency Meter, but has many additional features which increase its usefulness. Voltage stabilisation circuits and crystal control ensure extreme accuracy and in addition it is fitted with an Internal Modulation switch to allow use as a Signal Generator. Size only 8 1/2 x 8 x 8 1/2 in. Perfect working order, £25.0.0.

ADJUSTABLE MIKE STANDS, with heavy bases and plastic stems. Table type 22/6, door type 25/-. £19.6.

20/- CONSTRUCTOR'S PAROUL. Assorted colours wiring wire, solder, resistors, condensers, volume control, tag panel. ALL NEW post 2/6.

SPRAGUE CONDENSERS. Metal case, wire end. New .01 mfd. 1,000 volt and 0.1 mfd. 500 volt, 7/6 per dozen. Special quotes for quantities.

CONDENSERS. 100 assorted mica and silver mica. NEW 10/-.

HARRIS ELECTRONICS (London) LTD.
138 GRAY'S INN ROAD, LONDON, W.C.1

Telephone *T*ERMINUS 7937 Please include carriage cost on A.I.I. items
Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross

BARGAINS FROM BRITAINS

SILICON RECTIFIERS. Type BY100 (1/2 in. x 1/2 in.) will handle 250 volts at up to 500 mA. Replaces any TV metal rectifier. **BRAND NEW**—not seconds, 7/-. £17.10.0. Carr. 10/-.

VHF COMMUNICATIONS RECEIVER R-1843. This is the Air Force version of the well-known Hallicrafters S-27 or S-36. Covers 27 to 145 Mc/s. in three wavebands. It is complete with all valves, stabiliser, "S" meter etc., but requires an external power supply to give 250 volts HT and LT. Picks up police, amateurs etc. and could easily be used for mobile operation. Tested and in good condition. £17.10.0. Carr. 10/-.

AR 88 VIBRATOR PACKS. For 6V. operation. Complete with vibrator and OZ4 rectifier. **NEW** in original cartons, 15/- P. & P. 5/-. £17.10.0. Carr. 10/-.

AR 88 SPARE VALVES. Complete Set of **BRAND NEW** individually boxed original valves (1-4), 50/-. Plus 2/6 P. & P.

MOVING COIL PHONES. Finest quality Canadian with Chamols ear muffs and leather covered headband. With lead and jack plug. Noise excluding, supremely comfortable **BRAND NEW** 22/6. Post 1/6

MAGNETIC COUNTERS (ex G.P.O.). 4 figures to 9,999. Coils 500V for 24V operation. Tested. (No reset), 5/- each. P. & P. 1/6. **SPECIAL OFFER!** 10 for 30/-. P. & P. 6/-. £17.10.0. Carr. 10/-.


MICRO AMMETER. 0-500µA. Made by R.C.A., Weston Westinghouse and other famous American manufacturers. Circular 2 1/2 in. dust panel mounting. Dials are engraved 0-15 0-600 volts. As used in the American version of the "19 SET". **TESTED AND GUARANTEED 15/-.**

HEAVY DUTY TRANSFORMER. Input 220 to 250 volts A.C. mains (tapped every 5 volts). Output 50V. at 15 amps. A really rugged job, very conservatively rated. Size 7 1/2 x 5 1/2 x 7 1/2 in. Weight 28 lbs. **ONLY 25.19.6.** Carr. 7/6.

CHARLES BRITAIN RADIO LTD.
11 UPPER SAINT MARTINS LANE, LONDON W.C.2

TEMPLE BAR 0545
Shop hours 9-6 p.m. (8-1 p.m. Thursday). Open all day Saturday

GUITAR AMPLIFIERS WITH TREMOLO

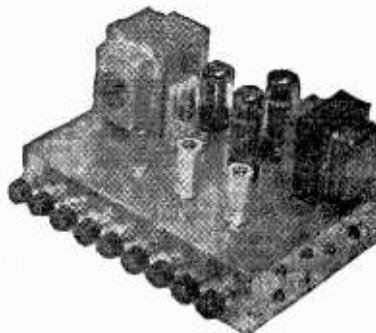

Five jack socket inputs, four with separate mixing volume controls, and one input 'straight through.' All inputs are of very high sensitivity, only 10 millivolts input is required for full output, making them suitable for all types of guitars and microphones. Separate Bass and Treble gain control. Tremolo speed and depth controls. Jack socket for remote tremolo switching. Outputs for 3 and 15 ohms speakers. Valves used in the 30 watt and 50 watt amplifier ECC83, ECC85, EL34, EL34, E231. An extra valve ECC83 is used in the tremolo circuit. The chassis is complete with baseplate and is solidly made of 18 gauge steel, finished silver grey hammer. Size 12 x 8 x 6 1/2 inches high.

PRICES—
50 watt with tremolo £20.10.0
50 watt less tremolo £19.10.0
30 watt with tremolo £15.10.0
30 watt less tremolo £14.10.0
15 watt with tremolo £12.10.0
15 watt less tremolo £11.10.0
Add carriage 10/- any amplifier. Send for free descriptive leaflet.

STROUD AUDIO
PAGANHILL LANE, STROUD, GLOS. Stroud 788



LETTERS TO THE EDITOR

THE RSGB AND PIRATES

SIR.—I have followed with interest your recent editorials on pirate operation.

I agree there is no excuse for operating a transmitter without a licence—the qualifications should not be beyond the capabilities of anyone who is really keen. In this connection I am particularly pleased to see that you are currently publishing a series of articles designed to help the newcomer pass the Radio Amateurs' Examination.

This society has itself been very active in this sphere for many years and publishes in August and September each year extensive lists of centres at which courses in preparation for the R.A.E. are being held. In addition, the society publishes a "Radio Amateurs' Examination Manual". More recently, an education and training committee has been set up, one of the objects of which is to foster the dissemination of information intended to help people to take part in amateur radio to the full.

Your practical efforts in this field are therefore particularly welcome. — J. A. ROUSE (General Manager, Radio Society of Great Britain).

NATIONAL FRATERNITY

SIR.—We were interested in the letter concerning Boys' Clubs, written by Mr. Overbury in the January issue. Our society and club has been forwarding just such a movement for about four years now. We have had great success in the field of exhibitions and social work. As a society, we have links with boys in Brighton, Welwyn, H.M.S. Ganges (Ipswich) and Australia, and correspondents in India and Nigeria. Work in co-operation with other bodies such as the British Association and, of course, the R.S.G.B. proceeds internationally together with the "Science Service" of the USA.

However, a club is vital to this work, and forms a focal point for all concerned. Boys in our locality have a club room and equipment, regular meetings, lectures and other club activities. It is vital to set up local activity, and let a larger organisation grow.

Because of the nature of work with young people, their particular outlook, lack of resources and responsibility, recognition under the Law, the difficulties are, and always have been, peculiar to this type of work.

It is important to have skilled, dedicated leadership. Also, assistance from all those who can give it is absolutely vital.

We are preparing one or two articles for publication with information on Boys' Radio Club for-

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of the cover.

The Editor does not necessarily agree with the opinions expressed by his correspondents.

mation. See also "QUA Associates", *R.S.G.B. Bulletin*.

We shall be delighted to hear from anybody keen on this social work, and any offers of help, advice, views will be welcome from lads wherever they are.—KEN SMITH B.Sc., G3JIX (82 Granville Road, Walthamstow, London, E.17).

QSL CARDS BETTER THAN WALLPAPER

SIR.—Correspondent C. P. Finn, of Yorkshire (P.W. January 1965 issue), asks about Electronic patterned wallpaper for his shack/bedroom.

When I had my shack/bedroom in 1932, we didn't worry about wallpaper. The main trouble was insufficient number of walls for QSL cards, blueprints, pencilled QSO's etc.

There are plenty of abstract patterns which could soon be converted to the "Electronic" theme, but for my choice, the old-type shack is unbeatable.—P. O. HUBBART (West Croydon, Surrey).

COMPETENT CONSTRUCTORS

SIR.—I wonder how many readers of this magazine pride themselves on being competent constructors of electronic equipment? Probably the majority, but there is, nevertheless, an increasing number of people who, having assembled some transistor set, half of which has already been made in the factory and which has been prefabricated: pre-cut, pre-aligned etc., insist on calling themselves competent radio constructors.

Furthermore, many of these people are not even interested in how their apparatus works, but merely in the noise that it produces, and an increasing number of manufacturers are catering for the person with this type of outlook.

Naturally, this seems rather a snobbish attitude to take, but it would be nice to know, for the benefit of our status as radio constructors, that we are not confused with the "step-by-step" man who only buys an f.m. tuner kit because it is cheaper than commercially available ones of the same quality.


I leave readers of this letter with a quote from George Orwell. "The boards I buy are ready planed, and the legs are ready turned by the lathe. I can even go to the woodshop and buy all the parts of the table ready-made and only needing to be fitted together; my work being reduced to driving in four pegs and using a piece of sandpaper . . . Making a table will be easier and duller than peeling a potato".—C. J. COLLISTER (Cheltenham, Gloucestershire).

LATE PASS

SIR—As a reader of your journal since the days of *Amateur Wireless* (I am now 66) I fully endorse every word you say about "pirates". As you say, the RAE never stopped the real enthusiast. I know an amateur who has passed the RAE, passed the morse test, and has been on the air for a year. He is in his 70's! If this doesn't shame some of those who want the "freedom of the air", it ought to. Thank goodness these are only a minority.

I am all for encouraging the youngsters. And what a goldmine of knowledge these young people of today have in their local library—enough for them to take the MIRE examination, let alone the RAE!

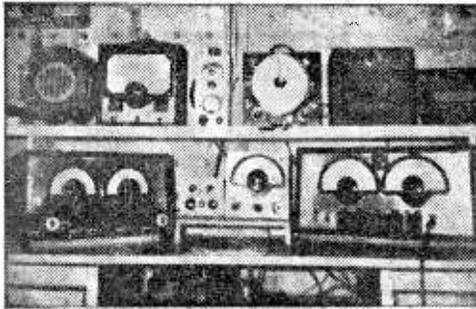Enclosed is a photograph of my den, which might be of interest. — T. W. MIDDLETON ex-G2FTM (Gravesend, Kent).



Mr. Middleton's den, where equipment based on P.W. designs is still providing him with a hobby in his enforced retirement.

P.W. SIGNAL INJECTOR

SIR—With reference to the signal injector described in the August issue of *PRACTICAL WIRELESS*, after having difficulty in obtaining a 35mm film cassette tin, I found that an "Anadin" aspirin tin was ideal for the job.—J. H. BORROWDALE (Hounslow, Middlesex).

CORRESPONDENTS WANTED

SIR—I would like to correspond with other radio enthusiasts of my own age (13).—EDWARD TWEEDLY (27 Orchard View Drive, Kirkfieldbank, Lanark, Scotland).

SIR—I would like to correspond with someone of my own age (14) who is interested in radio.—G. JACKSON (50 Bury Street, off Sandy Lane, Stockport, Cheshire).

SIR—I would like to hear from readers in any country who have an interest in radio and television.—S. A. ARJYASENA ("Sirisewana" Nawagamuwa, W.P., Ranala, Ceylon).

SIR—I am a regular reader of *P.W.* and interested in radio technology. I would like to correspond with any radio technician from Great Britain. I will answer all letters received promptly.—T. HENRY C. PEIRIS (Watinapaha, Dewlapola, Ceylon).

REQUESTS FOR INFORMATION ARE INSERTED IN THIS COLUMN ON THE UNDERSTANDING THAT READERS USING THE SERVICE UNDERTAKE TO REPLY TO ALL OFFERS RECEIVED AND TO RETURN ALL DATA NOT REQUIRED. BECAUSE OF THE LARGE NUMBER OF REQUESTS RECEIVED, ILLEGIBLE WRITING WILL AUTOMATICALLY DISQUALIFY LETTERS FROM PUBLICATION. FOR THE SAME REASON, WE CANNOT GIVE SPACE FOR REQUESTS FOR PAST ISSUES OF "PRACTICAL WIRELESS."

Sir—I would be grateful if any reader could sell or loan me . . .

. . . circuit diagram or any information on ex-army receiver R1466, Ref. No. 10D/1409.—BRIAN WOOD, 99 Kinnaird Road, Sheffield 5.

. . . information and circuit values of ex-government photocell 0/33281 CV243 and how to make it work a relay when the light beam is cut off.—M. GARDINER, 15 Windmill Fields, Four Marks, Nr. Alton, Hampshire.

. . . the circuit or service sheet or any details of the Ultra Ultrascope oscilloscope Mk. 1.—D. CHADWICK, 40 Abbots Road, Abbots Langley, Watford, Hertfordshire.

. . . any information, circuit diagram, etc., concerning the R 1392 v.h.f. receiver.—H. A. FORRESTER, 58 Bede Avenue, Sherburn Road Estate, Durham.

. . . any details whatsoever on the American receiver type BC624.—C. E. R. LISLE, Red Hill School, East Sutton, Nr. Maidstone, Kent.

. . . service sheet for the Veritone "Venus" tape recorder.—D. POTTERILL, 30 Dryden Crescent, Stevenage, Hertfordshire.

. . . the schematic diagram or any information on the wireless set 38 A.F.V.—W. B. NEEL, Landguard Lodge, Manor Terrace, Felixstowe, Suffolk.

. . . circuit and service details of the Delco Remy Hyat car radio, model 342.—J. STONEMAN, 46 South Hall Drive, Rainham, Essex.

. . . the circuit diagram or manual of transmitter type 1154M.—A. MAWHINNEY, 11 Donaghadee Road, Millisle, Co. Down, N. Ireland.

. . . a circuit diagram and operating manual for a No. 38 Mk. 2 set, and a manual for a 1132A Receiver.—S. G. BARNES, 13 Surrey Grove, Sutton, Surrey.

. . . information concerning the modifications of the R109 Receiver (year 1943).—S. ALDERTON, 2a Goldings Road, Loughton, Essex.

. . . information on fixing a tunable oscillator in a Bendix Receiver, BC 624A type R5019.—R. C. HART, "Brookmead", Rudwick Close, Felpham, Nr. Bognor, Sussex.

. . . the operating manual for the Gelson 209 Receiver.—R. BUNTOCK, 38 Bittell Road, Barnet Green, Nr. Birmingham.

. . . any information on the Marconi No. 9 Transmitter-receiver, and any information on the No. 46 Transmitter-receiver.—R. J. SHAWE, South Supplies, 71 High Street, Poole, Dorset.

. . . the circuit and/or manual of the R116A communications receiver.—A. D. COUCHMAN, 3 Manor Grove, Sittingbourne, Kent.

. . . the circuit diagram and/or any other details regarding the No. 19 Set.—T. BRIGGS, Lindfield School, Slindon House, Slindon, Sussex.

. . . circuit details of the HalliCroft S77.—C. CLARK, 94 Pensby Road, Heswall, Wirral, Cheshire.

. . . the circuit for the PCR2 receiver.—W. BURKE, GMJTOH, 6 Belgrave Terrace, Glasgow W2.

. . . the circuit diagram or details of the PCR2 receiver.—G. DARLING, 80 Seaton Gardens, Ruislip Manor, Middlesex.

. . . the handbook on the communication receiver DST100.—R. A. ELLIS, 32e Abbey Road, St. John's Wood, London N.W.8.

. . . information regarding the conversion of communication receiver 1392/62H from v.h.f./a.m. to v.h.f./f.m.—J. A. STIMSON, 236 Fullwell Avenue, Clayhall Ilford, Essex.

. . . any information, service manual and circuits for the ex U.S. army transmitter/receiver BC620F and p.s.u.—D. W. VITOU, 169 Worthing Road, Laindon, Basildon, Essex.

. . . the valve line-up for the Perth radio.—C. L. DIBBLE, c/o The Exchange Telegraph Co. Ltd., 17-21 Curtain Road, London E.C.2.

. . . any information regarding the "Hersteller" b.o. type R2, battery/mains portable radio, also the circuit, etc., for the Pye 47X a.c./d.c. receiver.—R. H. JACKSON, Braithwaite, Summerbridge, Harrogate, Yorkshire.

. . . the circuit diagram and any other information regarding the BC-624A v.h.f. receiver.—J. S. MORTLOCK, 36 Valleyfield Road, Streatham, London S.W.16.


. . . the circuit for a P104 v.h.f. receiver. I cannot get this set to oscillate, and any advice on this would be most welcome.—G. SPICER, 186 St. William's Way, Rochester, Kent.

TRANSISTOR DESIGNS BY SINCLAIR 1

SINCLAIR X-10

COMBINED 10 WATT
AMPLIFIER AND
PRE-AMP

A 100%
British
Design!

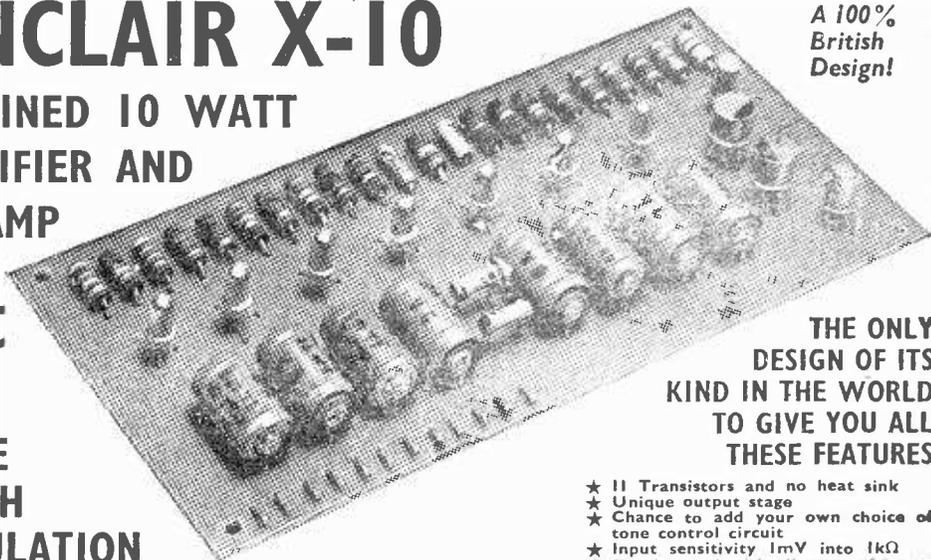

1st
WITH
PULSE
WIDTH
MODULATION

THE ONLY
DESIGN OF ITS
KIND IN THE WORLD
TO GIVE YOU ALL
THESE FEATURES

AND SUPERB STANDARDS OF PERFORMANCE


- ★ 11 Transistors and no heat sink
- ★ Unique output stage
- ★ Chance to add your own choice of tone control circuit
- ★ Input sensitivity 1mV into 1kΩ
- ★ Can be used with all types of inputs including low-output pick-ups and microphones
- ★ Total harmonic distortion less than 0.1%
- ★ Output power up to 10 watts
- ★ Frequency response 5-20,000 c/s ± 1dB
- ★ Speaker impedance 15Ω
- ★ Damping factor—greater than 100
- ★ Supply voltage 12 volts from batteries or mains supply unit
- ★ Size 6" x 3"

The principle of P.W.M. used in this remarkable amplifier which is complete with its own pre-amp stage and unique output stage results in an entirely new conception of amplifier design and performance. When the input signal is at any frequency up to 20 kc/s (which although well above the range of audibility is of vital importance in hi-fi reproduction) the net current is an exact replica of the input signal and is independent of the transfer characteristics of the output transistors. This makes the distortion figures incredibly low. Due to the way in which P.W.M. operates and the special output stage of the X-10, the output transistors actually act as switches and so dissipate negligible power. This enables 5 Mc/s transistors to be used with great savings in space, current consumption and costs. It makes having a heat sink unnecessary, and the X-10 may be satisfactorily operated from two 4/- batteries if so required.

THE MOST EXCITING ADVANCE IN AUDIO-ELECTRONICS FOR YEARS, AND IT'S BRITISH!

SINCLAIR X-10 MANUAL

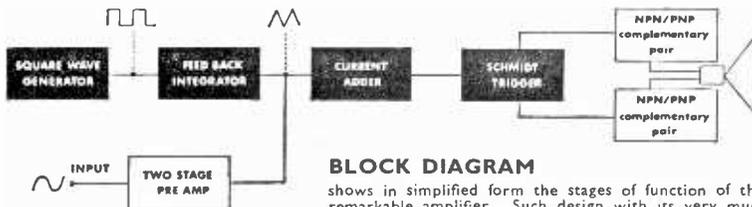Included with every X-10. It explains how the amplifier functions and how you can add the correct tone and volume control system to suit your precise requirements. A variety of systems is shown, none of which will add more than a few shillings to the original cost of your Sinclair X-10, be it for MONO or STEREO. Obtainable separately, price 1/-.



BLOCK DIAGRAM

shows in simplified form the stages of function of this remarkable amplifier. Such design with its very much better standards of performance is made possible by use of the very latest transistors and high quality components.

Guarantee,
Order form
and more

Sinclair

Designs on
pages following

All parts including 11 transistors, building instructions and X-10 Manual come to

£5.19.6

Ready built and tested, with X-10 Manual

£6.19.6

X-10 Power Supply Unit (ready built) for A.C. Mains 200-240V. Will power two X-10's if required.

£2.14.0



SINCLAIR RADIONICS LTD.
COMBERTON Cambridge

Telephone COMBERTON 682

TRANSISTOR DESIGNS BY SINCLAIR 2

SINCLAIR MICRO-6

The smallest radio set in the world

SIZE-1⁴/₅" X 1³/₁₀" X ¹/₂"
WEIGHT- LESS
THAN 1-oz.



ACTUAL SIZE

EVERY CONSTRUCTOR SHOULD BUILD IT!

It's the ultimate in personal radio, as thousands of constructors can tell you. For power, range and robustness, the Micro-6 is out of all proportion to its minute size, and it is found to function excellently where other sets cannot be used at all. That is why it is the one radio set you will be glad to have with you always, indoors or out. It will never intrude upon the privacy of other people no matter where you are using your Micro-6 and you can even wear it like a wrist watch. This world famous British receiver cannot be too highly recommended both as an intriguing design to build and a most practical set to use—IT PLAYS ANYWHERE.

- ★ AMAZING POWER AND RANGE
- ★ TUNES OVER MEDIUM WAVEBAND
- ★ BANDSPREAD FOR EASY LUXEMBOURG RECEPTION


EASILY BUILT IN AN EVENING!

All parts including MAT transistors, diodes, printed circuit board, lightweight earpiece, case and dial, and well-printed instructions come to


59/6

Sinclair "Transista" well-styled, strong black nylon wrist strap ... 7/6

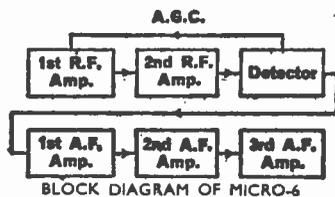Mallory Mercury Cell Type ZM312 (2 required) each 1/11
 Pack of 6 ... 10/6



The Micro-6 uses three special Sinclair Micro-Alloy transistors (MATs) in an original and very efficient circuit. Two stages of R.F. amplification are followed by an efficient double diode detector which drives a high-gain 3-stage A.F. amplifier. Powerful A.G.C. applied to the first R.F. stage ensures fade-free reception from the most distant stations tuned in. Tuning is by means of a unique vernier control which extends over the medium wave band.

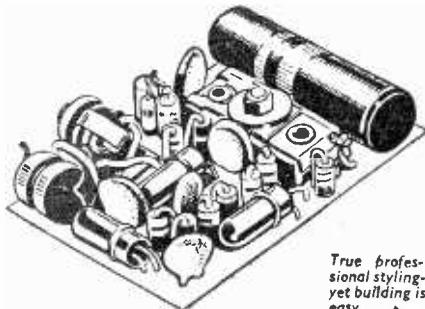

True professional styling—yet building is easy.



SINCLAIR RADIONICS LTD
 COMBERTON, CAMBRIDGE

Telephone: COMBERTON 682


TRANSISTOR DESIGNS BY SINCLAIR 3

They have success built in to them from the start!

SINCLAIR TR750 AMPLIFIER

Designed specially for Micro-6 and Slimline Users

SIZE
2" x 2"

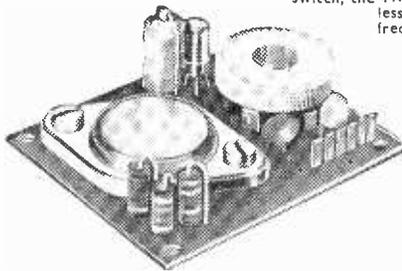

Another highly original Sinclair design which enjoys enormous popularity. The TR750 amplifier makes a powerful car, portable or domestic radio used with the Micro-6 or Slimline receivers and a plug is included for connecting to these sets. With its own built in volume control and on-off switch, the TR 750 has a full 750 milliwatt transformer-less output for 10mV into 10K ohms and a frequency response from 30 to 20,000 c/s \pm 1dB. It will also make an efficient hi-fi record reproducer used singly or paired for stereo and there are many other uses for the TR 750 which is available for building or ready built.

All parts with instructions come to **39/6**

Ready built and tested **45/-**

SINCLAIR SLIMLINE

The ideal Sinclair design for beginners

4-STAGE POCKET RECEIVER




Here's a fine performing set which is ideal for newcomers to transistor building. It has a self-contained aerial and takes a standard PP5 battery. Measures only 2 1/2 x 1 1/4 x 3/8 in. Tunes over medium waveband by means of vernier type control.

The Slimline has great power and quality and will bring in B.B.C. and European programmes with great ease. Countless thousands have been built by enthusiasts ranging from schoolboys to their grandfathers!

All parts including royal blue and gold case, ear-piece and easy to follow instructions come to **49/6**

Trace that fault with a Sinclair MICRO-INJECTOR

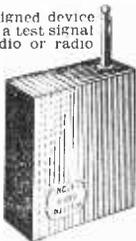This ingeniously designed device generates and injects a test signal into any part of audio or radio equipment at any frequency from 1 kc/s to 30 Mc/s by means of which it becomes easy to locate faults rapidly and accurately. Measures 1 1/2 x 1 3/16 x 1 in. excluding probe. With full instructions. No constructor should be without a Micro-injector.



Parts and instructions come to **27/6**

Ready built and tested **32/6**

SINCLAIR MICRO-AMPLIFIER

- Makes an F.M. Transmitter
- Makes an Audio or Broad Band R.F. Amplifier
- Smaller than a 3d. piece



This fantastically small amplifier gives phenomenal performance. Its exceptionally wide frequency coverage enables it to be used in many interesting and original ways. Frequency response 30 to 50,000 c/s \pm 1dB. Power gain 60dB (1,000,000 times). Instructions show you how to make a broadband R.F. amplifier, F.M. transmitter or a sub-miniature hi-fi amplifier with an output suitable for any earpiece or even loudspeaker. A fascinating design for experimenters, modellers etc. Parts and instructions come to

28/6

WHAT THE FAMOUS SINCLAIR GUARANTEE MEANS TO YOU

Every purchase you make from Sinclair Radionics Ltd., is covered by the following guarantee:

If you are not completely satisfied with your purchase (we are confident you will be delighted) the amount you have paid for it will be refunded in full instantly and without question.

FULL SERVICE FACILITIES ALWAYS AVAILABLE TO ALL SINCLAIR CUSTOMERS

SINCLAIR X-10

THE WORLD'S MOST ORIGINAL QUALITY AMPLIFIER

PLEASE SEE PAGE 1003

If you do not wish to cut coupon from page when ordering, please mention "Practical Wireless", February, when writing.

TO SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE Phone: COMBERTON 682

Please send items detailed below £ s. d.

NAME

ADDRESS

TOTAL £

For which I enclose cash cheque money order

BLOCK LETTERS P.W.265

RECEIVERS & COMPONENTS

SILICON TRANSISTORS p-n-p. max. ratings 20V., 50mA., 300mW., 2uA leakage. Minimum beta of 10 at 5mA., 1/6 each. Detector Diodes 6d. "By return" service. **LONGLANDS**, 341 Hounslow Road, Hanworth, Middx.

DIRECT TV REPLACEMENTS LTD., largest stockists of TV Components in the UK. Line Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. For quotes, Day and Night Telephone GIPsy Hill 6166, 126 Hamilton Road, West Norwood, S.E. 27.

R & R RADIO & T V SERVICE

Dept. P.W.

MARKET STREET, BACUP, LANCS.
Telephone 466

SALVAGE VALVES		Tested before dispatch	
6F13	4/6 10P14	6/-	PL82 3/6 20P4 6/6
6L18	4/6 20P5	6/6	U801 7/6 30P16 5/-
6F85	1/6 30P4	7/-	10F1 1/6 PC24 4/-
6C83	3/- 6F15	5/-	20P2 1/6 PCL83 3/6
6C18	3/6 6R91	1/-	20F11 5/- P481 3/6
30P5	5/- 6F85	5/-	PT32 6/- U301 6/-
PL35	6/- 6R10L2	4/-	6T4GT 5/- 10P13 5/6
PCP90	4/- 30P3	6/-	6F1 2/6 20D1 2/6
PL21	5/- 30P1	4/-	ECX11 3/- 30P12 5/-
6F20	5/- PL36	6/-	6Y86 4/- FY82 5/-
U320	5/- PCL83	5/-	

Speakers, Hi-TV, Fla. round, 6 x 4in. 2/6; 8in. round, 6/-; post 2/-.
Line Output Transformers available. Quote set model No.

Turret Tuners, 3/-, post 2/-.
Scan Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

TRANSISTORISED SIGNAL INJECTOR. Complete kit of components and circuit of injector for testing an amplifier or radio. 7/6d. only. Post free. **C. F. MILWARD**, 17 Peel Close, Drayton Bassett, Staffs.

COMPONENTS at give-away prices! Transistors: Valves: Coaxial Cable: Electrolytics: Vol Controls: Pre-sets: Speakers: Test Meters: Recording Tapes: Wiring Cable: Microphones: Pick-up Cartridges: Soldering Irons: Plugs, Sockets, Panels etc. Send a 5d. stamp for full price list. **DIAMOND** (Mail Order) Products. (P.W.) BMO/DIA, London, W.C.1.

DOUBLE BEAM OSCILLOSCOPES

Mullard L101, £25; Nagard 103, £30.

SINGLE BEAM

Furzehill 166-40 and 0100, £15; Philips 5640, £25; Nagard 103, £25.

X-Band Spectrum Analyser Type XL—made by Winston Electronics, £15.
UHF Signal Generators

Type No.: TF 5H7D 150-300 Mc/s; TF 390G 10-150 Mc/s; 517E 150-300 Mc/s } £5 each

Stabilized Voltage Supplies Type 12, £10. 0-450V DC @ 120mA. 500V DC not stabilized. 6.3V C.T. @ 10A. 6.3V C.T. @ 5A. 4V C.T. @ 5A.

All the above at clearance prices buyer collects.

WESTWOODS

46 George Street, Oxford. Tel. 47783

RATES: 7/3 per line or part thereof average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., London W.C.2.

RECEIVERS & COMPONENTS
(continued)

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.**, Dept. P.W./79, 126 Hamilton Road, West Norwood, S.E.27. GIPsy Hill 6166.


19 SETS for spares from 12/6 each. Sets complete 35/-. Sets complete with Power Pack control unit and aerial tuner £3. Mk II and Mk III, 38 sets, 15/- each. 38 sets for spares 5/- each. Spare valves for all above sets 2/6 each. Vibrator units new & unpacked 25/- each. **MAIN ROAD GARAGE**, South Green, Billericay, Essex.

TRANSISTORS now half price. unmarked but tested packets of 16; unmarked, untested packets of 40; 40cds suitable as diodes, packets of 80. All packets, 10/- each, postage 1/-. Four packets post free. **C.W.O. K. R. WHISTON** (Dept. PWT), New Mills, Stockport.

NEW VALVE TESTERS £12.
Mollineux, Lowfield Heath, Sussex.

RCA AR88D RECEIVER

(BRAND NEW)
Prog. 540 Kc/s.
32 Mc/s. 6 wave-band. Mechanical Bandspread with Logging scale Auto and Man. volume control, ditto Noise Limiter, SFO, Pitch and Var. F Tone controls. RF and AF Gain, Var. selectivity with Crystal Filter. Complete with Instruction/Service Manual, Spare Valves, H/Bat. Aerial etc. 27/- Carr. 2/-
CON ELTOR. Run your mains shaver, radio, record player, etc. from car battery. New type vibrator converts 12v. D.C. to 240v. D.C. at 100% low Drain. Brand new complete with spare fuses, battery clips, etc. 25/- Carr. 1/6.

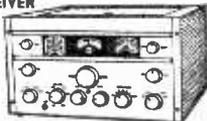

TELESCO 'IC AERIAL MASTS. Tubular steel copperplated, spray finish, ring cam locking on each section provides for full or any height required. Suitable all fixings and base locations. Bottom section 18in. diameter.
20ft. (4 section) Closed 5ft 9in. Weight 16lbs. 35/-. Carr. 5/-
34ft. (6 section) Closed 6ft. 8in. Weight 20lbs. 75/-. Carr. 5/-
Further height by adding 3-4ft. Whip sections 13/6. Carr. 1/6
Special price for quantities.
CRED TELE-RITERS. 73 Used condition £12.10.0. Carr. 30/-
TRANSMITTER. 1.75-16 Mc/s 3 waveband tuneable, grid modulation using 813. Used complete with all valves. circuit 27.10.0. Carr. 6/- 10/-

MOVING COIL HEADPHONES. BRAND NEW. Chamols padded, complete with lacc plus 15/6. Post 2/-
ROTARY TRANSFORMERS. 12V. D.C. input. 300V. D.C. 120mA output. note size only 4 x 2in. 15/-. Post 2/6.
POWER UNIT. Type ZEL1. Designed for Canadian No. 32 receiver. 52/6. Carr. 5/-
All No. 15 set parts available.
B44 Mk II & III. Diode and rod aerials 300/- set. P. & P. 5/-. Microphone with connecting plug 15/6. P. & P. 2/-. Battery input and phone plugs, 5/- each. P. & P. 1/6.
Many other bargains. S.A.E. all enquiries.

A. J. THOMPSON

"ELING LODGE"

CODICOTE, RITCHIN, HERTS

Phone: CODICOTE 242

RECEIVERS & COMPONENTS
(continued)

TRANSISTORS! Give away price. NKT124/5 Power Type. 6 for 10/-. 2SC17 4W, up to 60Mc/s 5/- each. Post free. **C. F. MILWARD**, 17 Peel Close, Drayton Bassett, Staffs.

SPEAKER REPAIRS, cones fitted. Satisfaction guaranteed. **L. S. REPAIRS**, Pluckley, Ashford, Kent.

AERIAL MATCHING TUNING UNITS

LATEST AMERICAN RELEASE BULK PURCHASE

These well-made tuning units made for the American 10 T.X.-R.X. are housed in a metal case (Green or Brown) using a large precision calibrated scale. are an essential piece of equipment for the serious T.X. or R.X. operator. This unit will match an untuned wire or whip aerial to almost any short wave receiver or transmitter, exceptionally good for mobile top band use. This American version being well noted as far superior to any other. **GUARANTEED BRAND NEW** only 30/-, post 7/6. Instructions supplied.

U.H.F. RADIO RECEIVER R10. F14840 Mc/s.-4475 Mc/s. (4.2-9.7 Cm/s.). These recently made sets are supplied in two units.

(1) Receiver. This is manual or auto-tuned by an internal motor using a total of 14 valves, see mixer CV90, i.f. 45 mc/s. aerial input via ordinary Pye coaxial plug (supplied).

(2) Power unit and output stage, contains 200 v.h.t. and -30 v. Bias Supplies, also receiver auto-tune supply. Both units housed in matching metal cases, size 17 1/2 x 8 x 10in. Supplied in first-class order complete with circuit and connecting cable from power unit to set. Mains 230 volt input. Offered at a fraction of cost, \$4.10.0 per unit, carr. 10/-.

19 in. Raads. 5 ft. and 6 ft. high. 50/- each carr. 10/-.

J. T. SUPPLY (Dept. D)
38 MEADOW LANE, LEEDS 11

TV CHASSIS, 110" with V.H.F., store soiled, £5 incl carr. **NEW 19in. TUBES** with smallspot burns, £4 incl carr. **C.W.O. T.V.S. LTD.**, Carclew Street, Truro, Cornwall.



V.H.F. Receivers P104 (R1892), 100 to 150 Mc/s. 13 valves. B.F.O., A.C.G., R.F. and L.F. gains. Tuning Meter. In good condition complete with instructions to convert to tuneable; can be used crystal controlled as is. £3.10.0 carriage 15/-.

Also **V.H.F. Receivers (R1182)**. Tunable 100 to 125 Mc/s. Easily altered for other frequencies. 11 valves, Tuning Meter. B.F.O. etc. Good condition. £5 carriage 15/-.
Power Unit Type 3 for 230 volts a.c. input suits above R1182 and P104. £2.5-0 carriage 10/-

Aerial Tuning Units. Made for Collins TCS12. 1 to 12 Mc/s. Good condition, 12/6 post paid.
(Carriage charges apply to England and Wales only).



FOR SALE

5-TON FACTORY CLEARANCE. Radio, TV Electrical Components, in mixed parcels. Example; 28lb. mixed parcel £1 pp 7/6d. Speakers, grilles, valves, bases, i.f.s. covers, condensers etc. Hundred other items. S.A.E. List and Postal Orders to **P. NEWTON**, 16 Shalcross Crescent, Hatfield, Herts.

NOW READY!

A modern way of case assembly using our "Die Strip" and Stelvetite panels. The strip has been specially made for us at Birmingham on qty. production, for low price to the public. It is made of high strength alloy and will enable anyone to assemble an instrument case or cabinet in minutes. The Stelvetite sheet is cut to size ready for use. Full details of these products will be sent free. Please send large envelope self addressed.

Also available Key Switches. 4 pole 2 throw 3/6 each or 3 position D.P. plus D.P. centre off 5/- or rotary switch 6 pole 3 way 3/-.

Bank of 4 Pye Sockets with plugs and leads 5/- set. Ever Ready Batteries, 90 volts plus 7 1/2 volts 4/6 each.

Plessey 2-4-12-25 way plugs and sockets all 5/- pair.

Jones Plugs and Sockets 4-12-18-24-32 way all 5/- pair.

Special Lightweight 7in. x 4in., 3 ohm P.M. Speaker 6/-.

88 set transmitter receiver. Chassis less valves, 20/- each. Post paid.

10in. RACK FITTING CABINET. 34" high by 21" deep with telescopic drawer slides. Loxvred sld s. back and top. Brand new Swedish make. £4 only, plus V.R.S. delivery

ECR Tube with Screen and Base with ECR 36 data, 25/-.

SUP7 Tube with Screen and Base, with data, 30/-.

COLLARO AUTO CHANGE

3 speed Gramophone Decks
Tested and Guaranteed
Post free 50/- each
Brown or Cream

Copper Laminate Board, single or double sided, 5/- per square foot panels, either type 3ft. by 4 ft., 33/-.

High Stab Resistors, 5%, 6%, 2%, 9d., 1% 1/-. Every six packed in 7-compartment linen finish component box. Unmarked.

Speakers, 3 ohm P.M. 5in., 5/-, 6in., 6/-, 7 x 4in., 7/-, 8in., 8/-, 10in., 12/6.

U.K. ONLY

E. R. NICHOLLS

Mail Order and Retail Shop
40 LOWFIELD ROAD
off SHAW HEATH, STOCKPORT,
CHESHIRE

FOR SALE

(continued)

HAMMER FINISH PAINT. The modern finish for electronics. Can be brushed or sprayed. Blue or silver. 24oz. tins 3/6, 1 pint 7/6, 1 pint 15/-. Post 6d. on any order. Trade supplied. **FINNIGAN SPECIALITY PAINTS** (1pw), Mickley Square, Stocksfield, Northumberland.

ELECTRIC SOLDERING-IRON



NEW IMPROVED PATTERN WITH BUILT-IN SWITCH
Lightweight Pistol Grip handle 40 watt. 240/250v. A.C. Solid copper bit. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handy-man. A boon to mode, makers and a necessity for every wireless enthusiast. P. & P. 1/-

ONLY 12/6

G. H. SERVICE (Dept. P. W. 3), Lusted Hall Lane, Tatfield, Kent

CONDENSER BARGAIN! Miniature paper condensers, 1in. x 1/2in. Ideal for transistor sets. .0001, .001, .002, .005, .02, .04mf. Your choice 7/8 per 100 or £3 per 1,000. **G. F. MILWARD,** 17 Peel Close, Drayton Bassett, Staffs.

TESTED TRANSISTORS

All new few equivalent.

OA202

1/- each, Red or White Spots.

2/- each, XA101, XA102, XB103, OA90, OC430, XA112, XA111.

3/- each, OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET 16.

4/- each, AF114, AF115, AF117, OC170, OC171, SX658, XU611.

5/- each, OC72, OC139, OC140, OC204, ORP60, BY100, GET8.

10/- each, OC35, OC26, OC28, GET57, 2SO13. All new, few equivalent.

ZENER DIODES 4.7 v. to 33 volt 1/2 watt, 3/6 each. 1.5 watt, 5/- each, 7 watt, 6/- each.

Send 3d stamp for Full Price List, and Free Equivalent Chart.

B. W. CURSONS
78 BROAD STREET
CANTERBURY, KENT

FOR SALE

(continued)

MORSE MADE EASY!

The famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum!

One student, aged 20, took only 13 DAYS and another, aged 71, took only 6 WEEKS to obtain a G.P.C. pass certificate. If you wish to read Morse easily and naturally, please enclose two 3d. stamps for full explanatory booklet. **T. GCHS, THE MORSE CENTRE, 45 GREEN LANE, PURLEY, SURREY.**

ARMATURE REWINDS — Hoover Junior Exchange Service Models, 375/119/1224. 32/6 inc. post. Fields 15/-. Rolls washing machine spares Trade discounts. Send for list. **JERVIS & TONGE LTD. (Dept P.W.),** Ringwood Road, Brimington, Chesterfield, Derbyshire. Telephone: Chest 76287.

240watt ELECTRIC POWER ANYWHERE
ANYTIME from 12 CAR BATTERY
with the **AMERICAN DYNAMOTOR UNIT**
Input 12v. 40 amp 240/250v at 150 to 220 watts
Perfect for television, power tools and all universal A.C./D.C. ELECTRICAL EQUIPMENT, plus essential results. Price only £26.00 - no postage.
Send stamped envelope for full literature details.
"SCIENTIFIC PRODUCTS, CHELSEA, LONDON"

WANTED

WE BUY new valves for cash, large or small quantities, old types or the latest. Send details quotations by return. **WALTON'S WIRELESS STORES,** 15 Church Street, Wolverhampton.

WANTED: Handbook or information re Xtals and Power Supplies. A.M. Trans/Recvr., No. 5043 (USA Sig. Corp SCR522), Hebden, 13 Ootham Street, London S.E.17.

WANTED VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. **R.H.S.,** Beverley House, Mannville Terrace, Bradford 7.

WE BUY new Valves and transistors. Amplifiers, Short-wave Receivers and Components etc. **A.D.A. MANUFACTURING CO.,** 116 Alfreton Road, Nottingham.

MISCELLANEOUS

LOUDSPEAKER REPAIRS, all makes. prompt delivery, 25 years' service to radio trade. Dept. P.W. **SOUND SERVICE RADIO,** 28 Gibbon Road, Kingston-on-Thames.

MISCELLANEOUS
(continued)

CONVERT ANY TV SET into an oscilloscope. Instructions and diagrams 12/6. REDMOND, 42 Dean Close, Portslade, Sussex.

SCHOBER ELECTRONIC ORGAN KITS

Send 6d. stamp for catalogue of these world-famous fully transistorised Organ kits, which you can build at home with no previous knowledge of electronics.

C. D. BRANDON

The White House, Higher Denham Bucks.

Sole U.K. Agents

A WELL-KNOWN British Manufacturer of sound equipment seeks new ideas or inventions, and will be glad to consider any novel developments. Please write in full confidence to Box No. 56.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swings.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2d. stamp.

METAL WORK

METAL WORK. All types cabinets, chassis, racks, etc., to your specifications. PHILPOTTS METAL WORKS LTD., Chapman St., Loughborough.

CABINETS • CASES CHASSIS

Anything in metal. "One-offs" a pleasure. Send your drawing for quote. Stove enamelled in any professional finish.

MOSS, WATSON

40 Mount Pleasant Street, Oldham Lancs. MAIN 9400

EDUCATIONAL

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career ICS DEPT. 541 PARKGATE ROAD, LONDON S. W. 11.

EDUCATIONAL
(continued)

BECAME "TECHNICALLY QUALIFIED" in your spare time. Guaranteed Diploma and Exam Home-study Courses in Radio, TV Servicing and Maintenance. R.T.E.B., City and Guilds etc. Highly informative 120 page Guide — FREE. CHAMBERS COLLEGE (Dept. 363), 148 Holborn, London, EC1.

TRAINING

Full-time courses in RADAR and RADIO-TELEGRAPHY for prospective marine Radio Officers. Govt. approved exam. centre.

Also courses in basic ELECTRONICS, RADIO, TELEVISION and PRACTICAL SERVICING.

Apply:—Director, British School of Telegraphy, 20 Penywern Road, Earls Court, London, S.W.5.

RADIO OFFICERS see the world. Seagoing and shore appointments. Our many recent successes provide additional trainee vacancies during 1964/65. Day and Boarding Students. Grants and scholarships available. Stamp for Prospectus. WIRELESS COLLEGE, Colwyn Bay.

THE INCORPORATED PRACTITIONERS IN RADIO AND ELECTRONICS (I.P.R.E.) LTD., Membership Conditions booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/-. post free. Secretary, Dept B, 32 Kidmore Road, Caversham, Reading, Berks.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

DON'T FUMBLE with Formulae. Master Mathematics quickly and easily the Understandable Way.

1st lesson and details FREE

The Dryden School of UNDERSTANDABLE MATHEMATICS

11 J. Dryden Chambers, Oxford Street, London W.1

Name.....
Address.....
.....
.....

SITUATIONS VACANT

YOUNG MAN required, over 18 years to work in busy Radio Shop and Mail Order Dept. Some previous experience necessary. For appointment telephone Paddington 1008/9. HENRY'S RADIO LTD., 303 Edgware Road, London, W2.

RADIO AND TV Exam, and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E. City and Guilds' Amateurs' Licence. R.T.E.B., P.M.G. Cert., etc. FREE brochure from BRITISH NATIONAL RADIO SCHOOL, Russell Street, Reading.

SITUATIONS VACANT
(continued)

TELEVISION DEVELOPMENT ENGINEER, E. K. Cole Limited. Southend-on-Sea, have a vacancy in their television development laboratories for a young man who has had practical training and has reached H.N.C. or Final City and Guilds in radio and television servicing. Write stating age and experience to Personnel Manager.

TV and Radio—A.M.I.E.R.E., City & Guilds. R.T.E.B. Cert., etc., on "No pass—no fee" terms over 95% successes. For details of exams and home training courses (including practical apparatus in all branches of radio, TV and electronics) write for 148-page Handbook—free. B.I.E.T. (Dept. 242G), 29 Wright's Lane, London W.8.

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home-study organisation. I.E.R.E., City and Guilds, R.T.E.B., etc. Also Practical Courses with equipment. All books supplied. Write for FREE Prospectus stating subject to I.C.S. (Dept. 542), Intertext House, Parkgate Road, London, S.W.11.

A.M.I.Mech.E., A.M.I.E.R.E., City & Guilds. G.C.E., etc., brings high pay and security. "No pass—no fee" terms. Over 95% successes. For details of Exams, and courses. In all branches of Engineering, Building, Electronics, etc. write for 148-page Handbook—FREE. B.I.E.T. (Dept. 242B), London. W.8.

RADIO TECHNICIAN

A number of suitably qualified candidates will be required for training, leading to permanent and pensionable employment. (Normally at Cheltenham but with opportunities for service abroad or appointment to other U.K. stations.)

Applicants must be 19 or over and be familiar with the use of Test Gear and have had Radio/Electronic workshop experience. They must offer at least "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19, £722, at 25, £929 (highest pay on entry) rising by four increments to £1,067.

Prospects of promotion to grades in salary range £997—£1,634.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days.

Normal Civil Service sick leave regulations apply.

Apply:

RECRUITMENT OFFICER (RT 37)
Government Communication
Headquarters, Oakley Priors Road
Cheltenham

SOUND RECORDINGS

A UNIQUE BUY! Recording tape top brand. 7in. 2,400ft. D.P. 25/-; 5in. 1,200ft. 19/6d. P. & P. 1/6d. per spool. Bargains in all sizes. S.A.E. for list. We repair, buy and sell recorders. E. C. Kingsley & Co. Ltd., 132 Tottenham Court Road, London.

INCREASE YOUR INCOME
 WIDEN YOUR KNOWLEDGE
 MAKE NEW FRIENDS
 JOIN THE

ARMY EMERGENCY RESERVE

R.E.M.E.

WIRELESS AND TELECOMMUNICATION MECHANICS with or without previous military service are required as volunteers to train for 15 days in the summer on modern equipment. Generous pay and bounties. For details write:

HQ AER, R.E.M.E., BROXHEAD HOUSE, Bordon, Hants.

**MECHANICAL
 ELECTRICAL
 ELECTRONIC
 INSPECTORS/EXAMINERS**

MINISTRY of AVIATION

Skilled men required as Inspectors and Examiners of a wide range of equipment for the Armed Forces. There are vacancies (1) at Contractors' works in: LONDON, THE HOME COUNTIES and many other provincial locations in ENGLAND and WALES.

(2) In laboratories at: BROMLÉY (KENT), HAREFIELD (MIDDX.) and WOOLWICH.

**ELECTRICAL
 INSPECTION
 DIRECTORATE**

Is responsible for the inspection of RADIO, RADAR, NAVIGATIONAL and similar ELECTRONIC/ELECTRICAL equipment and components.

QUALIFICATIONS To have served a recognised apprenticeship or have equivalent experience or training.

PAY (London Area) £16.0.0 rising by annual increments of 10/- to £17.10.0.
 (Provincial) £15.10.0 to £17.0.0 for a 42-hour (5 day) week.

HOLIDAYS Two weeks (84 hrs.) rising to three weeks (126 hrs.) after five years' service in the grade—8½ days public holidays in addition.

PROSPECTS Excellent prospects for promotion to the Technical Class within a salary scale £913—£1,244 for

**AERONAUTICAL
 INSPECTION
 DIRECTORATE**

Is responsible for the inspection of AIRCRAFT, ENGINES, GUIDED WEAPONS and associated equipment.

suitable candidates who possess or obtain the necessary qualifications.

OTHER INFORMATION After serving a qualifying period there is a paid sick leave scheme in operation.

APPLICATION To be made in writing giving:—
 (a) Brief details of apprenticeship and/or experience.
 (b) Whether E.I.D. or A.I.D. is preferred and for what type of work.
 (c) Location(s) preferred, stating alternatives, if possible.

**MINISTRY OF AVIATION, E.I.D. (A.O./P.2)
 "AQUILA", GOLF ROAD, BROMLEY, KENT.**

SERVICE SHEETS

SERVICE SHEETS, Radio and Television, 3/6 post paid. VEST AND EMERY, 17 Holgarth St., Durham.

SERVICE SHEETS: Radio, TV, 5,000 models List 1/- S.A.E. Inquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for all makes of Radio and TV 1925-1964. Prices from 1/- with free faultfinding guide. S.A.E. inquiries. Catalogues of 6,000 models, 1/6. Valves, modern and obsolete Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St Leonards, Sussex.

SERVICE SHEETS, also current and obsolete Valves for sale. JOHN GILBERT'S TELEVISION, 1b Shepherd's Bush Road, London, W12. Phone: SHE 8441.

SERVICE SHEETS (75,000) 4/- each. Callers Welcome: Always Open. 5 South Street, Oakenshaw, Bradford.

S.A.S. SERVICE SHEETS for all TV Radio and Tape Recorders, etc. List 1/8 plus S.A.E. SUN ELECTRICAL SERVICES, 38 St. George's Road, Hastings, Sussex.

SERVICE SHEETS

4/- ea., plus postage

We have the largest display of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc., in the country, and can supply by return of post.

To obtain the Service Sheet you require, please complete the attached coupon:

From:

Name: _____

Address: _____

To: **S.P. DISTRIBUTORS**
44 Old Bond St., London, W.1
Please supply Service Sheets for the following:

Make: _____

Model No.: _____ Radio/TV

Make: _____

Model No.: _____ Radio/TV

Make: _____

Model No.: _____ Radio/TV

I also require list of Service Sheets at 1/6.

I also require list of Manuals at 1/- (please delete items not applicable)

Enclose remittance of _____

MAIL ORDERS ONLY



Only £29-19-6

- Easily fitted
- No soldering or Technical knowledge necessary
- Fits almost any cabinet with minimum trouble
- Modernises your old radiogram
- 3 wave bands, Medium, Long and Short
- Complete with two 10in. elliptical Hi Flux loudspeakers
- And Hi Fi 4-speed stereo/mono automatic record changer
- Built-in ferrite rod aerial
- Piano key switching
- Luxembourg and Caroline received in full strength
- Listen to U.S.A., Russia, Africa, Canada and even Australia in your armchair
- Unique Lewis Radio 365 day guarantee, even on all the valves
- All British make
- Everything brand new and fully guaranteed

SPECIAL terms available of £3 deposit followed by 18 monthly payments of **£1.14.6**, postage and packing 12/6 extra.

INDIVIDUAL CABINETS SUPPLIED ON REQUEST



Avoid disappointment send cheque or P.O. immediately LEWIS RADIO (P.W.), 100 CHASE SIDE, SOUTH-GATE, LONDON, N.14 Telephone: PAL 3733/9666

RADIO CLEARANCE LTD.

27 TOTTENHAM COURT ROAD, LONDON W.1. Telephone: MUSEum 9188
Trade enquiries invited. The oldest component specialists in the trade Est. 35 yrs.

LOUDSPEAKER BARGAINS STILL AVAILABLE

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job. **COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.**

SCHEDULE OF LOUDSPEAKERS AVAILABLE

Diameter				Gauss				Imped.			
in	in	in	in	in	in	in	in	in	in	in	in
inches	lines	ohms	Price	inches	lines	ohms	Price	inches	lines	ohms	Price
2 1/2	7000	33	8/6	3 1/2	9500	50	10/8	5	7000	3	8/6
2 1/2	7000	50	8/6	4	7000	25	11/6	5	7500	3	9/6
2 1/2	7000	80	8/6	4	6000	35	10/8	5	8500	3	9/6
3	8500	3	10/6	4	7000	35	11/6	5	9500	3	10/6
3	8000	5	8/6	4	9500	35	11/6	5	9500	5	10/6
3	7000	5	9/6	4 Twtr.	10000	3	11/6	5	9500	15	12/6
3	7000	35	9/6	4	9500	15	12/6	5	8500	25	10/6
3 1/2	9500	3	10/6	5	6000	3	8/6	5	9500	35	11/6
3 1/2	9500	8	10/6	5	6000	5	8/6	6 1/2	6000	3	11/6

Elliptical				Gauss				Imped.			
Size	in lines	in ohms	Price	Size	in lines	in ohms	Price	Size	in lines	in ohms	Price
5 x 3	6000	3	7/6	6 x 4	9500	35	12/6	8 x 2 1/2	7000	5	9/6
5 x 3	7000	3	8/6	7 x 3 1/2	7000	3	9/6	8 x 2 1/2	8500	5	9/6
5 x 3	9000	3	8/6	7 x 4	9500	3	10/6	8 x 2 1/2	9500	3	10/6
5 x 3	9500	35	11/6	7 x 4 1/2	9500	30	12/6	8 x 2 1/2	9500	4	10/6
5 x 3	9500	3	9/6	7 x 4	9500	3	11/6	8 x 2 1/2	9500	5	10/6
6 x 4	6000	3	8/6	7 x 4	9500	30	12/6	8 x 5	8500	3	11/6
6 x 4	7000	3	9/6	7 x 4	9500	35	12/6	8 x 5	10000	3	13/6
6 x 4	8500	3	9/6	8 x 2 1/2	6000	3	8/6				
6 x 4	9500	3	10/6								

SELECTED BARGAINS

Beautifully geared AM/FM 2gang Condensers, 4/6; AM/FM IFT's 465 kc/s and 10.7 Mc/s 4/6 pair; Magnavox Crystal Tape Recorder Mikes, 12/6; 3 watt Stereo Amplifiers, complete, ready to switch on, 79/6; Sentercell rectifiers R3/2D-D3-2-1-Y, 2/6 each. DIODES—OA79, OA90, CG46H, GD10, 2/- each.
TRANSISTORS: OC45 4/6, PXA101, 3/9, AF115, 4/6, Sub min. Germanium diode 1/3, M1 diode 6d. each, Silicon diodes, 200 p.i.v. 200 mA, 1/- each, 400 p.i.v. 330mA, 2/6 each. Please send STAMPED and ADDRESSED envelope with any enquiry. We refer no catalogue—our stocks move too quickly! Kindly make provision for additional postage and packing charge to avoid delay. Terms: Cash With Order or C.O.D. on Orders over 10/-.

TIME TESTED BY THE PIONEERS OF LOW PRICED KITS!

MAKE 5 DIFFERENT TRANSISTOR RADIOS FOR 35/-



NO EXPERIENCE NECESSARY. No Soldering. Only 8 connections for first radio to work.

A.B.C. Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. YES — EVERYTHING! Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Mr. H. O'D. of Londonderry writes:— "... I received your components and I must say that I am very satisfied with them. I have it already set up! ..."

COMPLETE HOME RADIO COURSE, Originally 88 SEND ONLY 35/- plus 2/6 post etc. (C.O.D. 3/- extra).

NEW RADIO ANYONE CAN BUILD IN 2-3 HOURS 19/6



EVEN THE OLDER CHILDREN BUILD THEM! ... no soldering—only 16 connections! then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 x 1 1/4 in. Many Testimonials: M.H. of Bradford writes: "... I have just completed one of your sets successfully, it is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them ..."

Direct from Manufacturers to You. SEND 19/6 plus 1/6 post etc. (C.O.D. 2/6 ex.).

PARTS AVAILABLE SEPARATELY

AMAZING CIGARETTE RADIO! ONLY 18/6



Yes, a perfectly ordinary packet of cigarettes!—but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 Cigarettes—yet cleverly concealed highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file, Mr. D.B. of Huddersfield writes:— "... I have fitted the parts in and it is working wonderfully ..."

ALL PARTS including Semiconductors, A.B.C. Plans, etc. ONLY 18/6 plus 1/6 post, etc. (C.O.D. 2/6 ex.). (Parts available separately).

READ WHAT SATISFIED CUSTOMERS SAY

R.C. of HARRINGAY writes
Received with thanks Skyrama ... Very pleased. Working well.

B.M. of HARROGATE writes
... I would like to thank you ... It is a real bargain.

L.S. of LONDON W.8 writes
... given it a good try out and I am very pleased with the results.

S.B. of SOMERSET writes
... delighted with this radio ... glad if you could send one more.

D.R. of GLASGOW writes
... it is a lovely little thing and as clear as a bell.

J.W. of BRIGHTON writes
... I have recommended your radio to many of my friends.

T.F. of STEVENAGE writes
... would just like to say how pleased my son is with this radio.


W.H. of MIDDLESEX writes
Thank you for my dear little radio. It is a real treasure to me.

SEND 1/- FOR FULL LIST OF OTHER KITS AND STOCK RANGE LTD. (Dept. P.W.16) 9 Western Road, Hove, Sussex

CONCORD ELECTRONICS

FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS

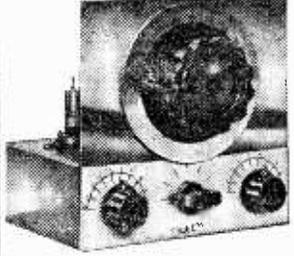

H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Bams, etc.

IMPROVED 1965 RANGE

1-Valve model "OX", complete kit, Price 34/6

Customers say: 'Definitely the best one-valve S.W. kit available at any price. This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and, of course, as all our products, fully guaranteed. **PULL RANGE** of other kits still available including the famous model "K", price 77/-

Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to:—

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. T.H.), 44 Old Bond St., London W.1

WORLD RADIO & TV HANDBOOK 1965 26/-

by JOHANSEN, postage 1/-

Amateur Radio Circuits Book, new ed. by R.S.G.B. 7/6, postage 1/-

Amateur Radio Call Book 1965 by R.S.G.B. 5/-, postage 6d.

Practical Tape Recording Handbook, new ed. by Guy, 7/6, postage 1/-

101 Ways to Use your Signal Generator by Middleton, 18/-, postage 1/-

Computer Circuit Projects you can Build by Boschen, 21/-, postage 1/-

Guide to Broadening Stations 1965 by W.W., 5/-, postage 6d

A.B.C. of Computers by Lytel, 16/-, postage 1/-

Transistor Inverters and Converters by Roddam, 42/-, postage 1/6.

UNIVERSAL BOOK CO.
12 Little Newport Street, London, W.C.2 (adjoining Lisle Street)

FOOTBALL POOL COMPUTER

Novel low-cost circuit for forecasting

Analogue Computer. Multiplication and division by electrical analogue. Simple demonstration of computer principles. Both above circuits for 3/6 post free.

Knights and Crosses Machine. Full circuit and instructions for our fabulous design 3/6. Cannot be beaten! ew simplified circuit.

Multimeter Kit. 15,000 o.p.v. 25 range kit with Weston 50 uA meter, only 65/- (25.5A range 4/- extra). Stamp for details.

Multimeters. Illus. leaflet on request. TK20A, 1,000 o.p.v. 28/-, post 1/6; KP10K, 10,000 o.p.v. 66/-, post 1/6; EP20K, 30,000 o.p.v. 103/-, post 2/-; EP60K, 90,000 o.p.v. 143/-, post 2/6.

Hirk Stab. Resistors. 1W, 1%, 2/-.

PLANET INSTRUMENT CO.
25 DOMINION AVENUE, LEEDS 7

NEW VALVES!

Guaranteed Set Tested 24-HOUR SERVICE

1R5, 1R5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET OF 4, 14/-

DAF96, DF96, DK96, DL96, SET OF 4, 22/6!

0A2	3/9	DL35	6/6	PCL83	7/9
1D5	4/9	DL92	4/3	PCL84	7/-
1R5	4/9	DL94	5/7	PL39	7/9
1S5	3/3	DL4	5/9	PL80	6/6
1T4	4/9	EABC80	5/9	PL82	5/-
3S4	4/3	EBC41	6/3	PL83	5/-
3V4	5/-	EBF80	5/6	PL84	5/-
5Y3GT	5/-	ECC81	3/7	PY32	8/6
6K7G	1/3	ECC82	4/-	PY33	8/6
6K8G	3/-	ECC83	4/6	PY80	4/9
607G	4/-	ECC84	6/3	PY81	5/-
6SL7GT	4/6	ECC85	6/-	PY82	4/11
6V8G	3/6	ECF80	5/9	PY83	5/6
6X5GT	6/3	ECF82	5/9	PY800	5/11
12K8GT	3/3	ECH42	7/3	U25	5/6
12K8GT	8/6	ECH81	5/3	U26	7/9
12Q7GT	3/3	ECL80	5/9	U191	6/9
20P4	13/3	ECL82	6/3	U192	15/-
25L6G	4/9	EF9	5/9	U193	15/-
30P11	7/9	EF90	4/3	UAF42	6/9
35LACT	6/-	EF85	4/6	UBC41	6/-
35Z4GT	4/6	EF86	5/9	UBF80	5/6
85A2	5/6	EF93	4/3	UC34	7/11
85A2	6/6	EL141	7/-	UC85	5/6
DAC32	7/9	EL94	4/6	UCF80	8/3
DAF91	3/3	EY51	5/6	UCH42	6/9
DAF96	5/6	EY86	5/6	UCH81	5/9
DF33	7/6	EZ40	5/-	UC84	5/3
DF91	2/3	EZ90	3/9	UCL83	7/9
DF96	5/6	EZ81	4/3	UF41	6/3
DH77	3/6	PCC84	5/3	UF89	5/9
DK32	7/6	PCC89	6/6	UL41	6/6
DK91	4/3	PCF80	8/9	UL84	5/9
DK92	6/9	PCF82	6/-	UR1C	5/9
DK96	6/-	PCF83	6/9	UY41	3/11
DL33	6/9	PCL82	6/3	UY85	4/9

Postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD, STOKE NEWINGTON, LONDON, N.16.

SEMI-AUTOMATIC "BUG" SUPER SPEED MORSE KEY



TRANSISTORISED MORSE OSCILLATOR

Fitted 21in. Moving Coil Speaker. Uses type P23 or equiv. 9 v. battery. Complete with latest design Morse Key, 22/6, plus 1/6 P. & P.

TRANSISTORS—1st Grade only, no seconds, no rejects, no surplus.

OC29	17/-	OC77	9/-	GE1105	10/-
OC29*	18/-	OC81*	8/-	GE7573	12/6
OC41	7/-	OC83*	6/-	ZN7064	17/6
OC44	6/6	OC139	12/-	2N458	20/-
OC45*	5/-	OC140	18/-	SB345	7/6
OC71	5/-	OC111	10/6	AC107	14/6
OC72*	7/-	OC200	10/6	AF114	11/-
OC73	6/-	OC201	21/6	AF115	10/6
OC75	7/-	OC203	14/-	AF116	10/-
OC76	6/-	GET104	6/-	AF117	9/6

Available in matched pairs.

SIEMENS SEALED IN'S RELAYS

H96A	2.2 ohm + 2.2 ohm. new	12/6
H96B	50 ohm + 50 ohm. new	12/6
H96C	145 ohm + 145 ohm. new	12/6
H96D	500 ohm + 500 ohm. new	12/6
H96E	1700 ohm + 1700 ohm. ex-equip.	16/6

BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6

The ideal instrument for workshop, lab. or factory. This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/6 P. & P.

NSP2 CV2296 STROBOTRON FLASH-TUBE made by Ferranti, brand new, I.O. base. Price 15/-, P. & P. 1/-.



VARIABLE VOLTAGE TRANSFORMER

Post Paid Input 230 v. A.C. Output 0-260 v. at 1 amp., fully shrouded, new. Also available 2.5, 5, 8, 10, 12 and 20 amp. Write for details.

LIGHT SENSITIVE SWITCH
Kit of parts including ORP, 21 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. ORP 12 including circuit, 10/6 each, plus 1/- P. & P.

D.C. AMMETERS

0-15 amp. D.C. M-Coil 2 1/2 in. round	12/6
0-5 amp. D.C. M.I. 2 1/2 in. round	11/6
0-500 Microamp. sub-min. 1 1/2 in. dia.	21/-

Scaled 0-1 milliamperes. Postage extra.

ULTRA VIOLET BULBS

Easy to use source of UV for dozens of practical and experimental uses.

12 volt 36 watt AC/DC SBC 6/6, P. & P. 1/-
12 volt 60 watt AC/DC SBC 8/6, P. & P. 1/-
Transformer to suit the above; Input 200-240 A.C. Output 12 Volt A.C. 36 watt, 16/6, P. & P. 2/6; Input 200-240 A.C. Output 12 volt A.C. 60 watt, 22/6, P. & P. 3/6.

Set of four colours **FLUORESCENT PAINT**, Orange, Yellow, Green and Red, in 1/2 oz. tins. Ideal for use with the above Ultra Violet Bulbs, 9/6, P. & P. 1/6.

VAN DE GRAAFF ELECTRO-STATIC GENERATOR

fitted with Motor drive for 230 v. A.C. giving a potential of approx. 50,000 volts. Supplied absolutely complete, including accessories for carrying out a number of interesting experiments, and full instructions. This instrument is completely safe, and ideally suited for School demonstrations. Price 26.8.0, plus 4/- P. & P.

A.C. VOLTMETERS

0-15 v. A.C. M.I. 2 1/2 in. F.L.	12/6
0-200 v. A.C. Rect. M-Coil 3 1/2 in. Type W23	45/-
0-300 v. A.C. M.I. 2 1/2 in. F.L.	22/6
0-300 v. A.C. Rect. M-Coil 2 1/2 in.	29/-
0-300 v. A.C. Rect. M-Coil 3 1/2 in. Type W23	36/-

A.C. AMMETERS

0-1, 0-5, 0-10, 0-15, 0-20 amp F.R. 2 1/2 in. dia.	11/6
--	------

All at 2/6 each.

SERVICE TRADING CO All Mail Orders. Also Callers at: 47-49 High St., Kingston-on-Thames Telephone: Kingston 9450. Closed Saturdays

Personal Callers only: 9 Little Newport St., Leicester, Leic. Ger 0576 (off Leicester Square)

PADGETTS RADIO STORES
OLD TOWN HALL, LIVERSEDGE, YORKS
Telephone: Cleckheaton 2968

USA Bomb Computers in original transit case, full of gears, motors, vibrator counter, gyro, etc., 37/-, carriage 10/-.

PCR, 12 volt Vibrator pack, in original packing case, 25/-, carriage 8/-.

RAF Sighting Heads. Complete with lamp lens etc. No details. Packed in original metal case, 15/-, carriage 10/-.

Single Phase 250 volt, 1,400 r.p.m., 1/2 h.p. motor with pulley, 26/-, less pulley 24/-, fully guaranteed, ex washing machine. Carriage 8/6.

One sixth h.p. motor, 250 V A.C. 15/-, post 6/9.

New Indicator Unit CRT. 100, complete with two tubes, type VCRX393 and VCRX282, plus 21 small valves, relays removed, 57/- or less valves 32/-, carriage 10/-, Sorry no details on the unit.

New 12in. Speakers with built-in Tweeter, 15 or 30 ohms, 28/6, post paid.

P.M. Speakers, all 3 ohms ex TV sets, 6in. model 6 x 4in. and 5in. 3/-, post 2/-, 6 or 20/-, Post paid. 3in. round 6/-, post 2/-, 7 x 4in. 5/-, post 2/-.

RES/CAP. BRIDGE 39/6 p. & p. 2/6.
Checks all types of resistors, condensers 6 RANGES
Built in 1 hour Direct reading
READY CALIBRATED
Stamp for details of this and other kits.
RADIO MAIL (Dept. J)
Raleigh Mews, Raleigh Street, Nottingham

Lyons Radio Ltd.
3 Goldhawk Rd. LONDON W.12

POWER UNIT TYPE 234. Input 200/250v. A.C. mains. Output approx. 220v. smoothed D.C. at 110mA and 6.3v. A.C. at 4iA. Originally designed to operate Receivers type 1R12 and R.332 but of course suitable for most communications receivers. Double section filter unit gives high degree of H.T. smoothing. For bench or rack mounting 19 x 7 x 1 1/2 in. Fitted with 2 1/2 in. dia. 9300v. resistor for indicating input and output volts Ex Govt., in good condition at working order. Price only 65/-, carriage 14/6. Plugs to fit input and output terminations 4/-.

2 METRES 4

The thrills of VHF Amateur Radio can now be yours for as low as 42/6 complete kit (by post, carriage and packing 2/6 extra). Tuning range 70-150 Mc/s. Stamped addressed envelope for free copy of literature and full details. Newcomers to Short-Wave Radio ask for details of the famous "Globe-King" kits and receivers. Home and Overseas Sales.

JOHNSONS (Radio)
St. Martins Gate, Worcester

VALVE LIST
Ex equipment. 3 months guarantee Post free

EL91	1/6	U801	8/6	PCL82	5/-
ECL80	2/-	U281	5/-	PCL84	5/-
EY282	3/-	U282	5/-	PL36	5/-
EF80	2/6	U283	5/-	VR150/30	3/-
EYB6	5/-	KT36	5/-	174	1/9
EBF50	4/6	KT66	8/-	12A7	3/-
EB91	6d.	6V6GT	4/-	8CH6	1/6
EL38	5/-	6B6	1/6	6X4	3/-
EF91	6d.	6C32	5/-	R18	3/6
6F1	4/-	6P25	3/6	ARP12	1/6
6F14	5/-	6U4	5/-	807	5/-
6F15	5/-	6Y33	6/-	EF50	5/-
10C2	1/6	6Y33	5/-	Doz. 5/-	
10F1	4/-	6Y81	3/-	6K7	1/3
10P13	5/-	PL81	4/-	Doz. 10/-	
10P14	5/-	PL82	3/-	6V6	1/9
20D1	2/-	PL83	3/-	Doz. 18/-	
20L1	5/-	PL84	3/-	6K3	1/9
20F3	3/-	PF82	4/-	Doz. 18/-	
20P1	4/-	PCF90	4/-		
20P4	8/6	PC84	4/-		

BATTERY CHARGER AND MODEL RAILWAY POWER UNIT COMPONENTS:

RECTIFIERS, full wave bridge type for outputs up to 12v. D.C. 1 amp 5/3, 2 amp 8/8, 4 amp 12/6, 6 amp 14/6. P.P. see below.

TRANSFORMERS. Pri. 200/250v. A.C. mains. Sec. tapped at 31, 9, 17v. for producing 2, 6 or 12v. D.C. respectively when used with above rectifiers. 1 amp 10/-, 2 amp 14/6, 4 amp 16/6, 6 amp (Tapped 9 and 17v.) 25/9. Postage 2/6 up to 10/-, over 3/6. Wiring diagram supplied.

"PROGRESSIVE" SHORT WAVE RECEIVER. Specially designed kits employing vacuum coils with exceptionally clear wiring diagrams and instructions to enable even the very beginner to construct a short wave receiver with every confidence of success. A second and then a third valve stage can be added if desired, the chassis supplied already being punched to take all three stages. Can be operated from dry batteries or from a simply constructed mains power unit, Price 32/6. Cost of all parts to build a One Valve S/W Radio including one coil 40/100 metres, Only 35/-, 1/2 Valve Conversion Stage ONLY 7/6, 2/3 Valve Conversion Stage ONLY 10/-. Extra plug in coils to cover 10/20, 20/40, 100/200, 200/450 metres 4/- each. Kits supplied separately 1/9, credited if kit ordered.

COMMON CORE BOOKS

THIS SERIES OF BASIC MANUALS EXPLAINS IN SIMPLE, STRAIGHT FORWARD WORDS AND CLEAR EXPLANATORY PICTURES: AS ADOPTED BY H.M. FORCES

BASIC SYNCHRO & SERVO MECHANISMS: Learn what automation is possible. Two parts, 18/6 each. Contents Part I Synchro Torque Transmitters—Synchro Differential—Synchro Capacitor. An elementary servo—Re-designed with Balanced Potentiometers, etc. 100 illus.

Part II The Function of an Error-Detector—The Control Transformer Error-Detector—The DC Servo Amplifier—Gas-filled Valves in DC Servo Amplifiers—Phase-shift control in Servo Amplifiers—An AC Servo Amplifier with Thyatron Valves, etc. 100 illus.

BASIC ELECTRONIC CIRCUITS Part I and II This two part series explains a selection of the principal circuits used in electronic engineering, both valve and transistor circuits are illustrated and explained in the picture caption technique.

BASIC RADAR compiled by REME, DECCA RADAR LTD. and the RAF. Part I, 17/-, post free. Contents include—Measurement of Angle, Range and Height—Frequency Bands Used—Basic Pulsed System—Wave-guides—The Transmit-Receive (TR) Switch, etc. 100 illus.

All books include postage. List S.A.E.

SELRAY BOOK CO.
60 HAYES HILL, HAYES, BROMLEY

Breaking Up Mark III Type 19 Sets, Meter 500 micro-amp., 5/-, post 1/9. Jack Socket, 1/-, post 6d., Doz. 10/-, post paid. Jack, 1/6, post 6d. Toggle Switch, metal, 6d., post 6d. Doz. 10/-, post paid. Relay, type 3000, 1/9, post 1/3, doz. 20/-, post paid. Any other spare send 2/- plus post to cover.

Reclaimed Tubes, 6 months guarantee, 14in. Mullard and Mazda 17/-, carriage 10/-, 17in. 30/-, carriage 10/-.

Z & I AERO SERVICES LTD.

Head Office and Warehouse:
44A WESTBOURNE GROVE
LONDON W4
Tel.: WAK 5641/2/3

Please send all correspondence and Mail Orders to the Head Office
When sending cash with order, please include 2/6 in 2 for postage and handling
MINIMUM CHARGE 1/6. No C.O.D. orders accepted

Retail Shop:
55 TOTTENHAM COURT ROAD
LONDON W7
Tel.: LAN 9ham 8403

0A2	4/-	6AK6	7/-	6N7	8/-	6P1	14/-	958	4/-	DM70	5/-	EF36	4/6	GU22	10/-	QV08-10	TRANSISTORS						
0B2	6/-	6AM6	4/-	6R7G	6/-	6P3	12/-	959	6/-	DX80	7/-	EF37A	8/-	GU24	10/-	35/-	OC28	3/-	OC71	5/-	OC171	9/-	
0B3	6/-	6AN5	10/-	6SL7GT	5/-	6P4	14/-	6696	6/-	DX86	8/-	EF39	5/-	KT66	16/-	TT15	35/-	OC28	17/8	OC72	8/-	OC204	10/6
0C3	6/-	6AQ3	6/-	6SN7GT	4/6	6P5	12/-	5763	10/-	EM8CC	14/-	EF40	0/-	KT88	20/-	TT21	32/-	OC35	16/8	OC75	6/-	AF114	9/-
0D3	5/-	6A6	8/6	6V3GT	10/8	6ZAG	5/-	6680	25/-	EAB080	7/-	EF41	7/6	TT8	15/-	TT22	32/-	OC42	9/-	OC76	6/-	AF116	8/-
1A0GT	8/-	6AR5	6/-	6L8	7/6	6ZLGT	8/-	6146	27/6	EAF32	8/6	EF42	6/-	NP81	25/-	U25	11/-	OC44	6/-	OC77	9/-	AF117	7/8
1A0T	8/-	6A87G	25/6	6V8	6/-	6ZAG	7/-	9002	5/6	E41	5/-	EF34	6/-	NAP2	22/-	U20	11/-	OC45	6/-	OC139	12/-	AF118	90/-
1A0T	7/-	6AT0	4/-	6V6GT	7/6	6Z5	7/6	9003	9/-	EBC33	7/-	EF55	8/-	OCF7	24/-	U191	11/-	OC70	6/-	OC170	8/-		
1H0GT	7/-	6AU6	6/-	6X4	4/-	6Z6GT	8/6	AZ1	9/-	EBC41	7/-	EF80	5/-	ORP12	12/-	U251	12/6	OC84	two matched	OC81	and one		
1L6	17/-	6AV6	6/-	6X6GT	6/6	6Z6C15	10/-	AZ1	9/-	EBC81	6/6	EF83	10/-	ORP60	10/-	U261	13/-	OC84	12/6				
1N6GT	8/-	6B7	6/-	6Y6G	6/-	6Z6T	12/-	AZ41	6/6	EF80	6/6	EF85	6/-	PC86	12/-	U262	14/-	R.C.A. 2N410 (OC4)	3/6				
1N6GT	8/-	6B8	5/-	6Y7	8/-	6Z6F5	9/-	CIC	5/-	EF83	7/6	EF86	7/-	PC88	12/-	U301	12/-	G.E.C. 2N412 (OC4)	3/6				
1R4	6/-	6BA6	4/6	6C6	7/-	6Z6L1	11/-	CBLL	15/-	EF89	6/6	EF89	4/6	PC97	9/-	U403	7/-	R.C.A. GET115, 7/-	8/-	GET73,	20/-		
1R5	5/-	6BE6	5/-	6D8	7/-	6Z6L17	13/-	CL33	9/-	EC53	12/6	EF91	4/-	PC84	6/6	U801	18/-	Matched pair of GET373, 35/-					
1R4	5/-	6BH6	7/-	6K7	12/-	6Z6P12	10/-	CY31	6/6	EC80	8/-	EP93	4/6	PC86	7/6	U4020	7/6	POST OFFICE COUNTERS					
1R5	4/6	6B6	9/-	6K7	16/-	6Z6P19	14/-	DA32	7/-	EC88	12/6	EP94	4/6	PC88	12/-	U4080	6/-	4-digit non-cancelling type					
1T0GT	6/-	6BK4	20/-	6B5W6	7/-	6Z6P11	11/6	DA70	7/-	EC90	2/6	EP95	5/6	PC99	11/-	UAF42	8/-	Standard, 2300 P Coil, sec. hand	5/6				
1U4	5/-	6BK7A	8/-	6D7	7/-							EP98	10/-	PC189	10/-	UBC41	7/-	Miniature, 2300 P Coil, sec. hand	6/6				
1U5	6/-	6BN6	7/-	6C1	10/-							8/-	PCF80	7/-	UBC81	8/-	500 D Coil, sec. hand	6/6					
1X2A	7/-	6BQ7A	8/-	6C2	12/-						8/-	PCF82	7/6	UBF80	6/6			4.1 U Coil, sec. hand	8/6				
1X2B	7/-	6B87	11/6	6D1	7/-						10/-	PCF84	8/-	UBF89	7/6								
2C4	12/-	6BR8	5/-	6D1P1	14/-						12/6	PCF86	9/-	UBL21	11/-			SEMICONDUCTOR RECTIFIERS					
2D21	9/-	6B87	10/-	6D3	8/-						10/-	PCF801	10/-	UCS4	9/-			(Half wave diodes)					
3A1	4/-	6B86	9/-	6D9	10/-						17/6	PCF802	10/-	UCS5	5/6			BY100, 800p.l.v., 450 mA, Silicon	7/6				
3A5	7/-	6BW7	9/-	6D1F8	9/-						8/-	PCF806	13/-	UCF80	9/6			BY2, 10 800 p.l.v., 5 amps, Silicon	7/6				
3D6	4/-	6C4	2/6	6D1L1	7/6						9/-	PCF81	9/-	UCH21	8/6			G3M, 900 p.l.v., 400/800mA, Germ.	3/6				
3Q4	6/6	6C31	12/-	6D1L11	10/-						8/6	PCF82	7/6	UCH42	8/6			G3M, 900 p.l.v., 400/800mA, Germ.	3/6				
3Q4GT	6/6	6C3B	6/-	6D1H3	12/6						5/6	PCF83	8/6	UCH81	7/6			GJ7M, 80 p.l.v., 500/1000mA, 3/6					
3S4	5/-	6C8G	17/6	6D1A	12/6						8/-	PCF83	9/6	UCH82	8/6			POWER UNITS TYPE 234					
4THA	10/-	6C16	9/-	6D2A8	11/-	35A5	11/-	DAF91	4/6	EC031	5/-	EL86	7/6	PCF85	9/-	UCL33	10/-	(Mains powered (230v. A.C.) 10m. Rack					
5R4G	9/-	6C4W	12/-	6D2A5	7/-	35W4	5/-	DAF96	6/-	EC04	4/-	EL821	6/-	PL36	10/-	UF42	7/6	Instantly power supply unit providing					
5T4	8/-	6D84	15/-	6D2A76	5/-	35Z4G	4/-	DF66	6/-	EC034	6/6	EM31	5/-	PL39	18/-	UF80	6/6	10/0 by means of primary taps from 150					
5U4G	5/-	6F6	8/-	6D2T7	4/-	35Z5GT	6/-	DF72	7/-	EC05	6/6	EM34	6/6	PL81	7/6	UF85	8/6	270v. Heater supplies 0.3v. at 4 amps.					
5U4GB	6/6	6E7	8/-	6D2U6	6/-	6D5	7/-	DF91	3/-	EC08	10/-	EM60	6/6	PL82	6/6	UF88	10/6	On-Off switch, panel lamp and I.T.					
5V4G	8/6	6F8G	5/-	6D2U7	5/-	50C5	6/6	DF96	6/6	ECF80	7/6	EM81	7/6	PL83	6/6	UF89	8/6	fuses second hand, in perfect condition.					
5Y3GT	5/-	6F11	6/-	6D2A7	6/-	50C6DG	25/-	DK91	5/-	ECF82	7/6	EM84	8/-	PL84	6/6	UL41	8/-	23.10.0. P. & P. 15/-					
5Z3	6/-	6F13	6/6	6D2A8	6/-	50LGT	8/6	DK92	7/6	ECF86	10/-	EM85	8/-	PL60	15/-	UL44	6/6	SEMICONDUCTOR DIODES					
5Z4GT	8/-	6F17	9/6	6D2B6	5/-	55A2	8/6	DK98	7/6	ECF81	10/-	EM87	7/6	UM60	7/6	UL60	7/6	(CG10E 1/8 OA86	8/-	8X641	8/-		
6B0L2	10/-	6F23	9/6	6D2B7	6/-	55Z4G	9/-	DL66	12/-	ECB35	13/-	EN31	10/-	PC33	9/-	UL10	9/6	(GX23 1/8 OA86	3/6	8X642	3/6		
6B5	9/-	6F24	11/-	6D2GT	7/6	82	20/-	DL68	10/-	ECB42	8/-	EN32	10/-	PC31	6/6	UY21	8/6	OA81	2/6	8A45	15/6		
6A3A	6/6	6F28	10/-	6D2K7	7/6	868A	14/-	DL69	12/6	ECB81	6/-	EY51	7/-	PC82	6/6	UY41	6/6	OA81	2/6	8A509	5/-	8X781	4/6
6A65	2/6	6F33	6/-	6D2K8	10/-	931A	60/-	DL70	7/-	ECB83	7/6	EY81	8/-	PC83	6/6	UY85	5/6						
6A47	6/-	6J4	9/-	6D2Q7	5/-	964	5/-	DL73	12/-	ECL30	6/6	EY83	9/6	PC88	8/6	W31M	6/6						
6A56	10/-	6J7GT	7/6	6D2A5	6/-	965	9/-	DL92	5/-	ECL32	7/6	EY86	6/6	PC90	8/6	X66	5/6	IN21	4/-	IN25	9/-	IN73	4/6
6A45	9/-	6K7	7/-	6D2P2	14/-	966	2/-	DL95	5/6	ECL33	8/6	EZ80	5/6	QV02-6	X66			IN23	4/-	IN28	20/-	LN81	4/6
6A45	5/6	6L18	5/-	6D2L1	14/-	967	5/-	DL96	6/6	ECL36	9/6	EZ81	4/6		45/-	X79	20/-	IN235	4/6	IN34A	40/-		

FIRST QUALITY



BRAND VALVES

BBC2 (625 LINE) TV AERIALS



Most Mounting Arrays, 9 element 45/-; wide spaced high gain, 11 element 55/-; 14 element 62/6. Wall Mounting with Cranked Arm, 9 element 60/-; wide spaced high gain, 11 element 67/6; 14 element 76/6. Chimney Arrays Complete, 9 element 72/-; wide spaced high gain, 11 element 80/-; 14 element 87/6. Loft Arrays, 7 element 32/6; wide spaced high gain, 11 element, with Tilting Arm, 62/6; 14 element 70/-. All high gain units have special Multi-rod Reflector. Low loss co-axial cable 1/8 per yard.

BBC · ITV · F.M. AERIALS



B.B.C. (Band 1). Telescopic loft 21/6. External S/D 30/-.
I.T.V. (Band 3). 3 Element loft array 25/-, 5 element 35/-, Wall mounting, 3 element 35/-, 5 element 45/-.
Combined B.B.C./I.T.V. Loft 1+3, 4M3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/8; 1+5, 71/3.
F.M. (Band 2). Loft S/D 12/6. "H" 30/- element, 52/6. External units available. Co-ax cable 8d. yd., Co-ax plugs, 1/3. Outlet boxes 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & F. 9/- Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept P.W.)
3b Godstone Road, Kenley, Surrey
CO 2527

FIRST-CLASS RADIO AND T.V. COURSES

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how:

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.I.E.R.E. Guide also gives details of range of diploma courses in Radio/T.V. Servicing Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication, it may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES

CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)
(Dept. 41), 148 HOLBORN
LONDON, E.C.1



The PUNCH you need!

HOLE PUNCHES


Instant Type	6/10 ea.
Screw-up Type
1 1/2" diameter Toggle switch	8/6 ..
1 1/2" diameter	8/6 ..
1 1/2" diameter B7G	9/6 ..
1 1/2" diameter B8A, B9A	9/6 ..
1 1/2" diameter	10/2 ..
1 1/2" diameter	10/8 ..
1 1/2" diameter	11/8 ..
1 1/2" diameter Int. Octal	13/4 ..
1 1/2" diameter	16/2 ..
1 1/2" diameter	18/10 ..
1 1/2" diameter B9G	21/8 ..
1 1/2" diameter	24/4 ..
1 1/2" diameter Meter	33/2 ..
2 1/2" diameter

Complete Set £9.3.6.
No extra charge for postage and packing in the U.K.

Oliver & Randall Ltd

Dept. 7
9 KELSEY PARK ROAD
BECKENHAM, KENT
Tel.: Beckenham 8262

Inexpensive books for all enthusiasts...

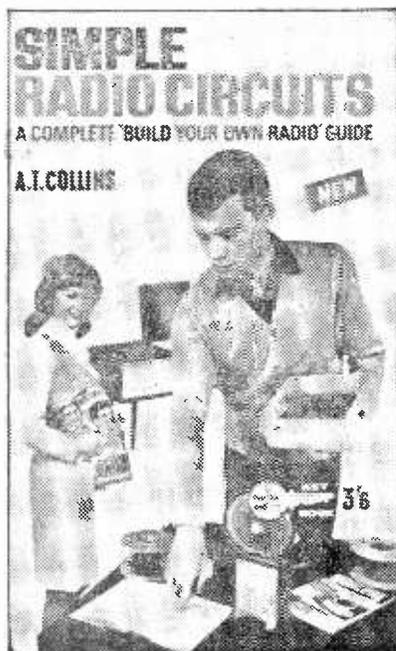

Each 96 pages. Extensively illustrated with easy-to-follow diagrams.



—KEY BOOK— —paperbacks—

SIMPLE RADIO CIRCUITS

by A. T. Collins

A Complete 'Build Your Own Radio' Guide. Simple Mains Short Wave Receiver, Medium Wave Transistor Receiver, Dual Wave One-valver, Broadcast Bands Receiver, Two-valve Short Wave, Amateur Bands Hybrid, Transistor Superhet Tuner, Battery-operated Short Wave Converter, Five-transistor T.R.F. Receiver. Four-valve Superhet Portable.
With 55 diagrams 3s 6d

HI-FI AND AUDIO

by A. T. Collins

Modern Designs for the Amateur Constructor. High Sensitivity Amplifier, Two-valve Pre-amp and Equaliser, Mains Gramophone Amplifier, Output Transformers and Loudspeakers, Crossover Networks for Loudspeakers, Seven-watt Quality Amplifier, Five-valve Stereo Amplifier, Design for a Bass Reflex Cabinet, Radiogram Cabinet Design, etc.
With 51 diagrams 3s 6d

Only 3s 6d each

FROM ALL BOOKSELLERS, including all branches of W. H. Smith, Wymans, Menzies, and Boots or in case of difficulty use this handy order form below...

order here

Please send me the following KEY BOOKS:—

.....SIMPLE RADIO CIRCUITS

.....HI FI AND AUDIO

ORDER

NOW

3s 6d each (4s by post)

Name

Address

Simply send this form with your remittance of 4s each title to George Newnes Ltd., Tower House, Southampton Street, London, WC2.

P.W. 2.65.

NEWNES

GUARANTEED

★ VALVES ★

by return of post
THE MOST ATTRACTIVE COMPETITIVE VALVE LIST IN THE COUNTRY

All valves are new and unused unless otherwise advised

POST 3 MONTHS FREE TRANSIT INSURANCE. Satisfaction or Money back Guarantee on Goods if returned within 14 days.

1 Valve 6d., 2-11 1/-, FREE for 12 or more in writing with every valve.

024	4/6 6K9GT	6/- 20L1	16/- DL82	9/- EZ20	5/9 U22	6/9
1A70T	3/8 6K7	5/9 20P1	9/6 DL82	5/- EZ21	6/- U24	12/6
1050T	7/- 6K7G	9/- 20P2	12/6 DL84	9/6 F04	4/- U22	10/6
1D5	7/- 6K7GT	4/9 20P4	17/- DL96	7/3 FW/500 7/-	U28	8/6
1D6	9/6 6K8G	5/- 20P5	15/- EA50	1/3 G13C 12/6	U81	7/-
1165GT	3/- 6K9GT	11/- 25A8G	6/- EABC0	6/9 G232	7/6 U33	14/6
114	3/- 6K25	3/8 26L6GT	7/9 EAC91	4/- G234	11/6 U35	12/6
1D55	4/6 6L1	9/6 23V6G	8/- EF42	3/8 H190	9/6 U37	22/6
1N5	4/6 6L6G	7/6 23V4G	7/- EB34	1/3 HL41DD 8/6	U50	4/9
1N50T	3/9 6L18	7/6 23Z5	8/- EB41	5/- H309 19/-	U52	4/9
1R5	5/6 6L19	11/6 25Z8G	8/- EB91	3/- HV22	8/- U76	5/6
1R5	6/9 6LD20	7/6 27U7	17/6 EB333	4/9 K732	6/9 U78	4/6
184	7/6 6P1	7/6 30C1	6/9 EB33	11/6 P023	4/- U107	7/9
184	9/6 6P1	7/6 30C1	6/9 EB33	7/9 K734	14/- U101	11/6
174	3/- 6P25	8/6 30P5	7/6 EB30	6/9 K744	6/- U281	9/6
2D21	5/6 6P28	9/9 30P11	9/6 EB38	6/9 K756	17/6 U282	12/6
3A4	4/- 6Q9G	6/6 30L1	6/6 EB39	10/9 K761	11/- U301	13/-
3A5	8/9 6Q7GT	3/9 30L15	9/6 EB39	10/9 K761	11/- U301	13/-
3E4	4/6 6Q7G	9/6 30P4	9/6 EC91	4/9 K766	13/6 U329	9/6
3Q4	7/- 6A4T	9/6 30P12	5/6 EC91	4/9 K778	3/9 U339	11/6
3B4	5/- 6C7	4/9 30P19	13/6 EC92	8/6 K788	19/- U403	10/6
3K4	6/6 6G7	4/9 30P11	9/6 EC95	7/6 K79	5/6 U404	8/6
3E4GY	9/9 6G7	3/- 30P11.3	9/6 EC95	4/9 K768	5/9 U404	17/6
3E4	9/9 6G7	3/- 30P11.3	9/6 EC95	4/9 K768	5/9 U404	17/6
504G	6/6 6K7	5/6 25C5	9/6 EC93	4/9 K726 11/-	U4P42	7/9
5V4G	7/6 6L7GT	8/6 35W4	8/6 EC95	5/6 L67	3/- U41	7/6
5V3G	4/6 6L7GT	4/9 35Z4GT	5/6 EC95	5/6 L67	3/- U41	7/6
5Y8GT	6/6 6G7	5/9 35Z4GT	7/- EC92	6/6 U14	6/6 U41	7/6
5E4	9/6 6S7	3/6 41	6/9 EC92	6/6 N57	10/6 U4P30	7/6
5Z4G	7/6 6U4GT	9/6 52	6/9 EC98	6/6 N58	17/6 U4P30	7/6
5Z4GT	9/6 6V6G	4/6 50B5	5/6 EC98	7/6 N108	17/6 U4E1	12/6
6S0L3	6/6 6V6G	6/6 50B5	6/6 EC98	7/6 N152	5/6 U4E2	7/6
6A6	5/6 6X4	4/9 60L6GT	7/6 EC90	9/6 P41	7/6 U4C84	9/6
6A7	9/6 6X6G	5/6 68K9	9/6 EC92	9/6 P81	2/9 U4C85	10/6
6A8G	7/6 6X6GT	6/6 61BT	17/6 EC98	8/6 PAB80 8/9	U4C80	7/6
6A8G	12/6 7B6	10/6 68RT	13/6 EC98	10/9 PC83	11/6 U4C81	9/6
6AC7	3/- 7B7	7/6 75	5/6 EC91	8/6 PC84	6/6 U4C82	7/9
6A95	6/6 7C5	7/6 75	5/6 EC93	7/6 PC85	7/6 U4C83	9/6
6A97	4/6 7C6	7/6 75	5/6 EC93	8/6 PC88	11/6 U4C83	12/6
6AK5	5/- 7H7	7/6 80	9/6 EC98	6/6 PC89	9/6 U4F1	8/6
6AL6	5/- 7H4	6/6 83	9/6 EC92	6/6 PC89	13/6 U4F2	14/6
6AM6	8/6 7Z4	6/6 185BT	19/6 EC98	10/6 PF80	6/9 U4F3	9/6
6AQ5	6/6 8D3	3/6 185BTA	19/6 EC98	12/6 PCF22	7/6 U4F6	9/6
6AT8	6/6 10C1	11/6 807	7/6 ECG85	10/6 PCF94	12/6 U4F9	3/6
6AV6	7/6 10C6	14/6 818	4/9 EF22	7/6 PCF80	11/6 U4L1	8/6
6AV6	5/9 10P9	10/6 866A	12/6 EF37A	8/6 PCF82	9/6 U4L4	14/6
6BBG	5/6 10F18	10/6 854	3/9 EF39	7/6 PCF84	7/6 U4L8	9/6
6BA6	5/6 10LD11	14/6 865	2/8 EF40	11/- PCF85	10/6 U4M0	3/6
6BB6	6/6 10P13	9/6 866	3/6 EF41	6/6 PCF86	10/6 U4C1	7/6
6BE6	15/- 10P14	9/6 868	5/6 EF42	6/9 PCF85	3/8 U4B	11/6
6BH6	6/6 12A6	2/8 9057	9/6 EF50A (2)	6/6 PCF86	4/6 U4B	13/6
6BR7A	6/6 12A8H	11/6 9067	9/6 EF54	3/- PL32	9/6 U4Y1	11/6
6BR7	8/6 12A7E	6/6 9001	3/6 EF58	7/6 PL32	9/6 U4Y1	11/6
6BR9	9/6 12A7T	5/6 9002	4/9 EF96	7/6 PL31	8/3 U4Y5	6/6
6BR9S	7/6 12A7T	9/6 9008	5/9 EF91	6/9 PL32	6/6 U4Y5	9/6
6C4	3/6 12A7E	6/6 ATP4	2/8 EF91	3/- PL32	6/6 U4Y5	9/6
6C5	5/6 12A7T	6/6 AZ41	7/6 EF18S	9/6 PL820	5/3 U4Y1	9/6
6C6	3/6 12B2A	6/6 B36	6/9 EF184	8/6 PM84	8/- U4Y5	6/6
6C8	11/- 12B2E	6/6 C10	8/- EK32	7/6 PX4	12/6 U4Y5	6/6
6C9G	16/6 12B2T	9/6 CB181	13/6 EL32	3/9 EX25	9/- W81	7/9
6D2	3/6 12C8	5/6 CB183	5/6 EL32	11/- F121	8/6 X61M	11/6
6D3	3/6 12E1	17/6 CY31	7/6 EL34	11/6 FY32	10/6 X65	9/6
6D3	9/6 12H8	1/6 D77	3/6 EL35	6/- FY33	10/6 X65	11/6
6D6	3/- 12J5GT	6/6 DA30	11/6 EL38	12/6 FY80	6/6 X66	7/6
6E1	4/6 12K7	4/6 DAC32	8/- EL41	8/- FY83	6/3 X78M	11/6
6E2	7/6 12K7GT	4/6 DAP9	4/6 EL42	9/6 F022	7/6 X78	21/6
6E6G	4/6 12K8	9/9 DAP96	7/6 EL51	8/9 FY83	6/9 X78	21/6
6F13	4/6 12K9GT11	6/6 DF38	8/9 EL94	6/6 FY88	6/9 X81M	9/6
6F14	9/6 12K7GT	4/9 DFN1	3/- EL85	6/9 FY900	7/9 Y83	6/6
6F19	6/6 12M7	7/6 DFN6	7/6 EL91	8/9 FY901	7/9 Z83	4/9
6F32	4/6 12M7	3/6 DH68	5/6 EM34	8/9 R19	9/6 Z66	8/6
1F33	4/- 12M7	6/6 DH78	4/6 EM30	7/6 RL18	11/6	
6G6	1/6 12K7	4/6 DK39	9/6 EM81	8/9 SP41	2/8	
6G6	1/6 12K7GT	6/6 DK39	5/6 EM85	9/6 SP61	2/8	
6G9G	3/6 12M7	8/6 DK92	7/- EN61	16/- S122	15/-	
6J6GT	4/6 12D3	6/6 DK96	7/9 EY1	7/6 ST9150	4/6	
6J6	3/6 12A9G	7/9 DL33	7/6 EY6	7/6 T41	6/9	
6J7	4/6 12B9G	4/- DL35	7/6 EY8	9/6 TDD4	3/6	
6J7G	4/6 20D1	8/6 DL63	9/- EZ40	7/- U14	7/6	
6J7GT	7/6 20F2	9/6 DL73	6/- EZ41	7/- U18	7/6	

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 10 lbs. 4/-, etc. (C.O.D. extra). ALL VALVES LEAS 5% and POST FREE IN DOZENS.

★ Tubes ★

HIGHEST QUALITY—COMPARE OUR PRICES

GUARANTEED

Carr. & Ins. 12/6

MOST MULLARD,	12in.	\$2. 0.0	\$3. 0.0	MW 31/74
MAZDA, OOSBOR,	14in.	\$2.10.0	\$3.10.0	\$3.15.0
EMITROM, EMI,	15—17in.	\$3. 5.0	\$4. 5.0	MW 32/94
SCOPE, BRIMAR,	19in.	\$3. 5.0	\$4. 5.0	\$4.15.0
FERRANTI TYPES,	21in.	\$3.15.0	\$5.15.0	CRM 172
OUR OWN	23in.	\$3.15.0	\$5.15.0	MW 43/64
FACTORY				\$6.0.0

SATISFACTION GUARANTEED

TRANS RECEIVERS
 Type 5TR908, latest 9 Transistor
 Loudspeaker type. 4-4 miles range.
 Few at pre-increase price of **\$25**

PROFESSIONAL TAPE RECORDER
 MAYPAIR FT157. Six Transistor.
 Capstan Drive, Two Speeds, Dual Track,
 Push-button Controls, Tape, Ideal
 Speech and Music, Many Reimendments,
 Only 3%. Wow Flutter. Beautiful
 Finish, with Mike, 5in. Tape, Telephone
 adaptor **£17.17.0**

TRANSISTORS
 GUARANTEED TOP QUALITY
 Huge reduction. Red Spot
 standard I.F. type only
 White Spot B.F. **1/6**
 Mullard Matched Output Kits **12/6**
 OC91D and 2-OC81
 R.F. Kits OC44, OC45 (2), **12/6**
 3 transistors.
 3 AF14 8/- OC44 5/6
 AF115 7/6 OC45 5/6
 AF116 7/6 OC72 5/6
 AF117 7/- OC81 5/6
 AF127 9/6 OC1D 5/6
 OC82 12/6 OC82 6/6
 OC86 14/- OC170 8/6
 OC171 8/8

GERMANIUM DIODES
 General Purpose miniature detector.
 A.V.C. etc.
 or 6/6 doz.
 Gold Banded highest quality. Individually
 tested. **1/-**
 9/6 doz.

SILICON RECTIFIERS
 Guaranteed performance. Top makes
 Tested 250V working.
 100mA **3/9** 250mA (3 for 10/6) **7/6**

CONNECTING WIRE
 P.V.C. Bright Colours. Five
 20ft. coils only. **4/-**

MAINS TRANSFORMERS
 Excellent Quality Guaranteed.
 Upright mounting 250-0-250 V
 60 mA, 6.5 V 3 A (SMA 12/6)
 Ditto semi-shrouded 9/6 **9/6**

13 CHANNEL T.V.s
 Table Models. Famous Makes. Absolutely
 Complete. These sets are un-
 equalled in value due to huge purchase
 direct from source. They are untested
 and not guaranteed to be in working
 order. Carr. etc. 15/-
 14in. **£2.19.0** 17in. **£4.19.0**

TURRET TUNERS
 Most makes, your choice if avail-
 able, with valve 15/-, less valves
 10/- S.A.E. enquiries.

★ BULK BARGAINS ★
 12 POTS. Popular values. 5K to
 2 Meg. Unaug. mixed. prev-
 set. Using sp. switch. etc. **4/6**
 CONDENSERS. 25 Mixed Electrolytic.
 Many popular sizes. List **10/-**
 Value £5. Our price

100 RESISTORS 6/6
 Excellent. Sizes 1-3 watt.

100 CONDENSERS 9/6
 Miniature Ceramic and Silver Mica
 Capacitors. 2 pf to 2,000 pf. LIST
 VALUE OVER £5.

25 TAG STRIPS 4/-
 2, 4, 6, 8 way etc. Unwired.

100 HI STABS 9/6
 1% to 5% 100T to 5 M Ω.

100's TYPES NOT LISTED S.A.E. ENQ.

355 352 Fratton Road, Portsmouth Tel: 22034
 ALL MAIL ORDER. RETAIL SHOP AND HI-FI ROOM
 DEVONIAN COURT PARK CRESCENT PLACE,
 BRIGHTON. Tel. 608722

TECHNICAL TRADING CO.

We supply from stock most of the components and items specified or circuits published in this and other magazines and radio books. Let us quote for your circuit, first grade components at realistic prices.

PW 6 Superhet
PWS.W. Converter
PW Beginners SW2.
PW Transistor Inverter.
PW Mains Power Pack
PW Build and Learn Series.
PW Transistor SW Converter.

All parts in stock for practically all "PW" circuits and designs. Send stamp with list of parts required for Quotations.

CATALOGUE
90 pages fully detailed and illustrated with hundreds of new items and price reductions. PRICE 2/6 Post Paid.

● OUR STOCKS ARE TOO VAST TO ADVERTISE—A CATALOGUE IS THEREFORE, A MUST ●



MAINS AND BATTERY RECORD AND TAPE DECKS
(p.p. 3/6 any type)

- All Decks Complete with Cartridges**
- ★ BSR UA14 4-speed Auto ... £5 16 6
 - ★ BSR UA15 4-speed Auto ... £6 19 6
 - ★ Garrard Autoslim Auto ... £6 10 0
 - ★ Unpluggable Hd. Versn. Auto ... £6 19 6
 - ★ Battery Autoslim ... £8 19 6
 - ★ Stereo Version Auto ... £7 19 6
 - ★ SRP10 4-speed Single Player ... £5 0 0
 - ★ SRP10 Battery Version ... £5 19 6
 - ★ BSR GU7 4-speed Single Player ... £5 0 0
 - ★ Garrard AT6 with Stereo Cartridge Autochanger... £10 19 6
 - ★ AT6 Mono ... £10 10 0
 - ★ Collaro 2-track Studio Deck £10 10 0
 - ★ Collaro Studio 4-track Deck £13 19 6
 - ★ BSR TD2 2-track Deck ... £7 19 6
- P. & P. 3/6 any type above.
- ★ 9 volt Starr 45 r.p.m. ... 39/6
 - ★ 45 or 33 r.p.m. Starr 9V ... 89/6
 - ★ 45 r.p.m. Garrard 6V ... 35/-
 - ★ 4-speed B.S.R. 9V ... 5 gns
 - ★ Garrard 9V, 2-speed, 2-track Tape Deck with cassette ... £10 10 0
- Fully guaranteed. P. & P. 3/-

TRANSISTOR PORTABLE TRANSCIVERS

9-transistor Portable Transceivers. Supplied complete with leather cases, batteries, aerials, etc. in presentation case. Range up to 5 miles in favourable conditions. Size 6 1/2 x 3 x 1 1/2 inches. Superhet crystal controlled on transmit and receive. Price £21 Per Pair. P.P. 3/6

TRANSISTOR TRANSCIVER
3-transistor crystal controlled version of above. Range up to 1/2 mile. Price £8.19.6 Per Pair. P.P. 2/6.

A SELECTION FROM OUR STOCKS—NEW PRICES
See Catalogue for full details.

- Sinclair Micro-6 (to build)..... 59/6
- Sinclair TR 750 amps. (to build) ... 39/6
- Sinclair Micro Injector (to build)... 27/6
- PP3 9 volt Battery Eliminator 18/6
- Tape Jack Tuner 29/6
- 10-Watt Horn Tweeter..... 27/6
- 2-Watt Super Tweeter 69/6
- 20-channel Mixer 15/-
- 1 to 200 Mc/s F/str. Meter 59/6
- 1/2-Watt 4-transistor 9 v. 3 ohm ... 49/6
- 5-hole Chassis Punch Kit 49/6
- Headphones 2 K ohm 12/6; 4K ohm 14/6
- Stereo Headphones 8 x 8 ohm 3 gns.
- Stereo Stethoscope Headsec 8 x 8 ohm 25/-
- Resistor Substitution Box..... 32/6
- Crystal Mono Stethoscope Headset 10/6
- Magnetic Mono Stethoscope Headset 12/6
- Transistor Signal Injector 35/-
- Fully Disappearing Car Aerial 39/6
- Test Lead Kit with Pouch 8/6
- Capacitor Substitution Box 22/6
- De Luxe Stereo Headsets with junction box £6
- 4-channel transistor mixer 49/6
- ★ 3-Transistor MW Superhet tuner 67/6
- ★ 4-Transistor Superhet MW/SW Tuner..... £79.6
- Transistor Telephone Amplifier 59/6

FM VHF TUNING HEART

Printed circuit construction. RF stage and osc./mixer stage, fully tunable 85 to 105 Mc/s. Completely screened. Requires UC85 (8/6). Brand new in maker's cartons 15/-. P.P. 1/-. Supplied with circuit.

MULLARD POT CORES

LA1 12/6	LA5 17/6	LA45 15/-
LA2 15/-	LA6 22/6	LA2503 15/-
LA3 19/6	LA9 17/6	LA2504 15/-
LA3 19/6	LA10 17/6	LA2505 17/6
LA4 12/6		

- 30 watt Soldering Iron 14/6 P.P. 1/-. Tape Demagnetiser 29/6
- 2 K ohm 1 in. diam. mag. mic..... 15/-
- Antex 15 watt min. soldering iron 29/6
- Earphones Mag. or Crystal 5/-
- Telephone Recording attachment... 9/6
- Crystal Guitar contact mic. 12/6
- ★ 7-transistor Record Player or tuner amplifier with treble/bass and vol. controls, £5.19.6.
- ★ 4-transistor 1/2 watt amplifiers. Kit, 39/6. P.P. 1/6. Built 49/6. P.P. 1/6.

RECORDING TAPE

5in. 600ft., 12/6; 5in. 900ft., 15/-; 7in. 1,200ft., 18/6; 7in. 1,800ft., 25/-; 7in. 2,400ft., 27/6. Excellent quality.

● SCOTCH BOY TAPE. 3 1/2in., 300ft. L.P. Complete with spare spool. 5/6 P.P. 9d.

● SINCLAIR X10 AMPLIFIERS in stock. Kit £5.19.6. Built £6.19.6.

BUILD A QUALITY TAPE RECORDER
Leaflet on request



- ★ 6 Valve Printed Circuit designs. 2-track or 4-track units. 11 gns. 2-track, 12 gns. 4 track.
 - ★ Collaro Studio Decks. 2-track 10 gns. P.P. 3/6. 4-track £14. P.P. 3/6.
 - ★ Portable cabinets with Speakers, 5 gns. P.P. 3/6.
- Complete Systems
2-track £26, P.P. 8/6. 4-track £30, P.P. 8/6.
● Complete in Every Detail ●

NOMBREX TEST EQUIPMENT



All transistor portable units supplied with full instructions. Leaflets on Request.

- ★ 150 Kc/s to 350 Mc/s generator. RF Mod. AF, 8 ranges. Leads, batteries, instructions, £9.10.0.
 - ★ Resistance/Capacitance Bridge, £8.5.0.
 - ★ Transistorised Power Supply, £6.10.0.
 - ★ Audio Generator, £16.15.0.
 - ★ Inductance Bridge. £18.
- Fully Guaranteed.



CRYSTAL MICROPHONES

(See Catalogue for Full Range)

- Acos 39-1 Stick Microphone 32/6
- Acos 60-1 Stick Microphone 19/6
- Acos 40 Deck Microphone 15/-
- Acos 45 Hand Microphone 19/6
- Lapel/Hand Microphone 12/6
- 100C Stick with Stand 32/6
- BM3 Stick with Stand 49/6
- Lapel/Hand Magnetic 8/6

● MINIGRAM PORTABLE TRANSISTOR RECORD PLAYER KIT, as previously advertised. 79/6 P.P. 3/6 (Battery) 3/9.

QUARTZ CRYSTALS

100 kc/s 15/-; 500 kc/s 15/-; 455 kc/s 12/6; 456 kc/s 15/-; 27.255 Mc/s 15/-.
Twin Crystal, 1 Mc/s, and 100 kc/s 22/6.
Over 800 frequencies in stock.

Henry's Radio Ltd.
PADDINGTON 1008/9

303 EDGWARE RD., LONDON W.2
Open Monday to Sat. 9-6. Thurs. 1 o'clock.

PLEASE TURN TO BACK PAGE

NEW LOW PRICES

MULTI-METERS



Multi-range test meters featuring easy to read scales and provided with full operating instructions, lead and batteries. Suitable for amateurs, designers repair shops, all domestic uses. Full details and specifications in our catalogue.

PT34	1 K ohm/volt.....	£1 19 6
M1	2 " " ".....	£2 9 6
THL33	2 " " ".....	£3 15 0
★ EPI0K	10 " " ".....	79/6
★ ITL2	20 " " ".....	89/6
★ TP55	20 " " ".....	£5 19 6
★ EP30K	30 " " ".....	£5 10 0
★ 500	30 " " ".....	£8 19 6
★ EP50K	50 " " ".....	£8 10 0
★ EPI00K	100 " " ".....	£9 19 6

★ Leather Cases available.

RECORD/REPLAY/ERASE TAPE HEADS



Marriot Type R/RP3 1/2 track record/replay head and Mullard type TS erase head with mounting post. Bargain offer 15/- pair P.P. 9d.

TRANSISTOR POCKET RADIOS

Ready to use complete with Battery. Leather Case. Earphone. P.P. 2/- any type. Fully Guaranteed.

- 6-Transistor De Luxe ... 69/6
- 7-Transistor Zephyr ... 79/6
- 6-Transistor MW/LW ... £5.19.6

PRACTICAL WIRELESS

blueprints

MOST of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for these marked thus (*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-SIDED BLUEPRINTS

The Strand Amplifier	}	*
The PW Signal Generator		
The Savoy VHF Tuner	}	*
The Mayfair Pre-amplifier		
The Berkeley Loudspeaker Enclosure	}	*
The Luxembourg Tuner		
The PW Troubadour	}	
The PW Everest Tuner		
The PW Britannic Two	}	*
The PW Mercury Six		
The PW Regency	}	*
The PW International Short Wave Two		
Beginner's Short Wave Two	}	*
S.W. Listener's Guide		
Beginner's 10-watt Transmitter Transmitting and Aerial Data	}	*
P.W. "Sixteen" Multirange Meter Test Meter Applications Chart		
The Celeste 7-transistor Portable Radio	}	*
The Spinette Record Player		
The P.W. 35-watt Guitar Amplifier ...		*
Transistor Radio Mains Unit	}	*
7 Mc/s Transceiver		

RECEIVERS

5/-	The Tutor *	3/-
5/-	The Citizen *	5/-
5/-	Dual-Wave Crystal Diode PW95	2/6
5/-	Modern one-valver PW96	2/6
	All-dry Three PW97	3/6
7/6	Modern Two-valver PW98	3/6
	A.C. Band-pass Three PW99	4/-
6/-	A.C. Coronet-4 PW100	4/-
5/-	A.C./D.C. Coronet PW101	4/-
	The PW Pocket Superhet	5/-

MISCELLANEOUS

5/-	The PW 3-speed Autogram	8/-
	The PW Monophonic Electric Organ ...	8/-
5/-	The PT Band III TV converter	1/6
5/-	The Mini-amp *	5/-
	The PT Olympic *	7/6
5/-	The PT Multimeter *	5/-

PLEASE NOTE that we can supply no blueprints other than those shown in the above list. Nor are we able to supply service sheets for commercial radio, TV or audio equipment.

QUERY SERVICE

The P.W. Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot supply detailed information for converting war surplus equipment, or supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 4th February, 1965 and must accompany all queries in accordance with the rules of our Query Service.


PRACTICAL WIRELESS, FEBRUARY, 1965

First Class Designs — Proven Unbeatable Performance

★ CIRCUITS AND DETAILS ON REQUEST — FULL AFTER SALES SERVICE AND GUARANTEE ★

CALL IN FOR DEMONSTRATION

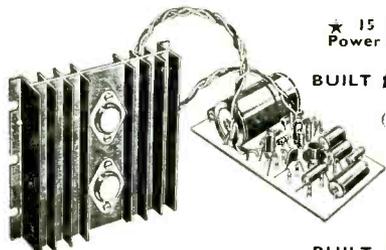● TRANSISTOR HIGH FIDELITY EQUIPMENT MONO or STEREO 10 WATTS and 20 WATTS



★ 15 ohm 10 watt Power Amplifier

BUILT £5.19.6 P.P. 2/6

(OR KIT £5.10.0 P.P. 2/6)

★ 3 ohm 10 watt power amplifier

BUILT £5.10.0 P.P. 2/6

(OR KIT 99/6 P.P. 2/6)

★ MAINS UNITS 59/6 for one amplifier, or 69/6 to power two amplifiers

PREAMPLIFIERS

● Mono full function pre-amplifier with 8 input positions. Low noise, high quality and sensitivity. Gives 10 watts with one power amplifier or 20 watts with two amplifiers. Size: 9 × 2½ × 2in.



BUILT £5.10.0 P.P. 2/-

(KIT 99/6 P.P. 2/-)

★ Brown and Gold detailed front panel plate 8/6.



● STEREO PREAMPLIFIER
For use with two power amplifiers.
Size: 9 × 3½ × 1½in.

PRICE BUILT £10.19.6

P.P. 3/6
★ Dark Brown with Gold front panel 12/6

● MULTI-INPUT PREAMPLIFIER

Simplified preamplifier for use with one or two power amplifiers, 8 inputs.

PRICE BUILT 65/- P.P. 1/6


★ Front Panel Plate 6/6.



All the above preamplifiers can be used with any valve or transistor power amplifier requiring 250mV plate for full output. They can be operated with two 9 volt batteries in series or from the power amplifiers.

● 10 Watts plus music power or 20 watts peak per amplifier.

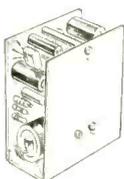TWO NEW PACKAGED TRANSISTOR QUALITY AMPLIFIERS



4 WATT and 1½ WATT

● 6-Transistor printed circuit designs. Push-pull output for 3 to 5 ohm speakers. Can be battery operated. 6mV into 1 Kohm sensitivity Response 30 c/s to 15 kc/s. Input suitable for mics., pick-ups, tuners, etc. Can be used with above preamplifiers for mono or stereo in any application requiring a low distortion low cost amplifier.

OVERALL SIZES: 2½ × 2 × 1½ inches.

● 4-watt version operates from 12 to 18 volts.

PRICE BUILT 79/6 P.P. 1/6

● 1½ watt version operates from 9 to 12v.

PRICE BUILT 65/- P.P. 1/6

“REGENT-6”

New!

● MEDIUM and LONG WAVE POCKET SUPERHET RADIO

A New 6-transistor printed circuit designed with full coverage on both wavebands. Features “Cleartone” push-pull speaker output, geared tuning and complete set of 1st grade components. Moulded two tone cabinet size 5 × 3 × 1½”. Easy to follow building details. All parts sold separately.



● Total cost of all parts **85/-** P. & P. 2/- (Battery 2/6 extra)

Available mid-January

“CONVAIR” PUSH-BUTTON PORTABLE/ CAR RADIO

● UNBEATABLE FOR PERFORMANCE AND DESIGN —

Printed circuit 6-Transistor 2-Diode superhet radio with full tuning on medium and long wave bands. Quality push-pull output up to 1 watt. Attractive portable cabinet, size 10 × 7 × 3½”, with horizontal slow motion tuning dial and push button wave change. Easy to build with superb performance. All parts sold separately. After sales service and guarantee.



● Total cost of all parts **£7.19.6** P.P. 3/6. (Batteries 6/- extra) ★ The finest portable available.

ALL TRANSISTOR CAR RADIO

● 1 HOUR TO BUILD WITH PRE-ASSEMBLED CHASSIS AND PANELS

6-Transistor 3 diode med. and long wave superhet design. Features double tuned IFTS, AVC, permeability tuning with geared drive. Push-pull car filling volume. Full tuning on both wavebands. A high sensitivity printed circuit professional design to fit any type of vehicle. Case size 7 × 4 × 2”. For 12 volt positive earth or dry battery. All parts available separately.




THE “ROADSTER” **£8.19.6** P.P. 3/6.
● Total cost to build 7 × 4” Hi-Flux speaker with baffle and car fixing kit 20/- extra.

VHF TRANSISTOR FM TUNER

● HIGH STABILITY — HIGH SENSITIVITY ●

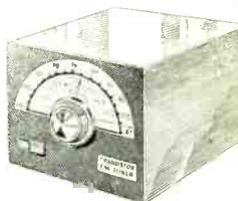Features 5-Mullard transistors with 4 diodes, compact printed circuit, high gain, low distortion, superhet design. Full tuning from 87.105 Mc/s with geared tuning. AVC and AFC. 9 volt 9 mA operation. 50 dB S.N. Output up to 1 volt audio. Easy to build and align. Overall size in cabinet 3½ × 2½ × 4in. All parts sold separately.



● Total cost with front panel: **£6.19.6** P.P. 2/6 (Cabinet Assembly 20/- extra).

HENRY'S RADIO LTD.

PADDington 1008/9.

303 EDGWARE ROAD, LONDON, W.2.

(Open Monday to Saturday all day 9 a.m. to 6 p.m. Half-day Thursday 1 p.m.)

● Trade and Export enquiries invited ●

PLEASE TURN TO INSIDE PAGE