





PRACTICAL WIRELESS

MAY 1965

2¹/₂

**FREE
INSIDE!**

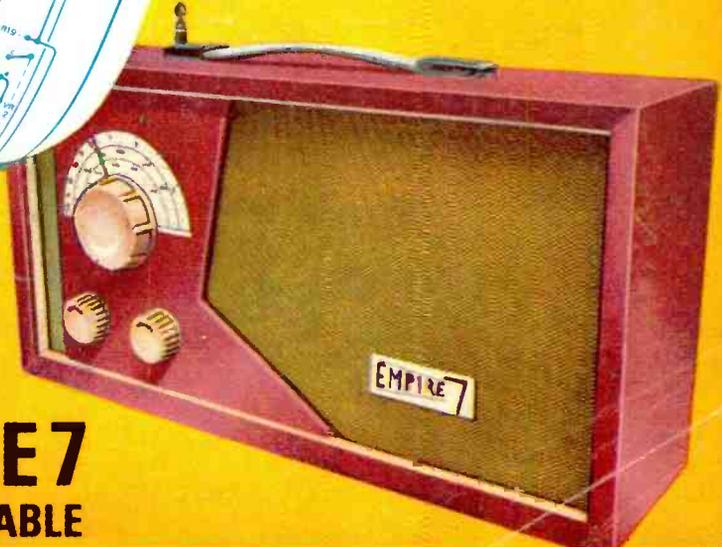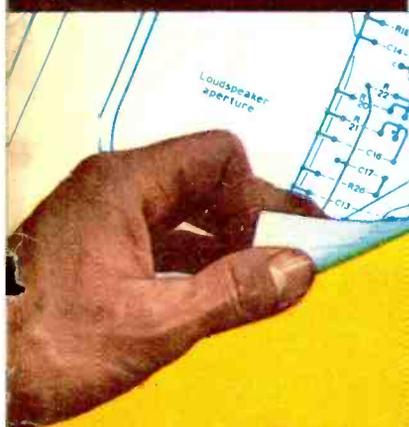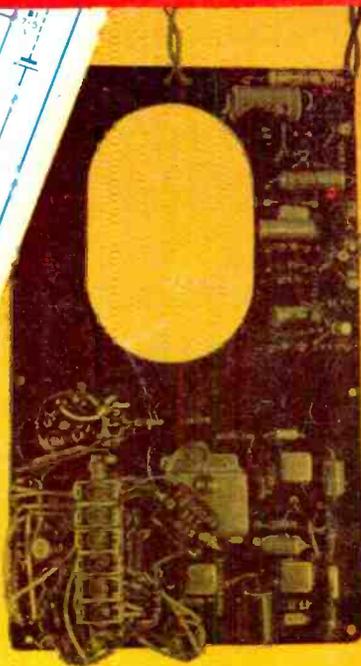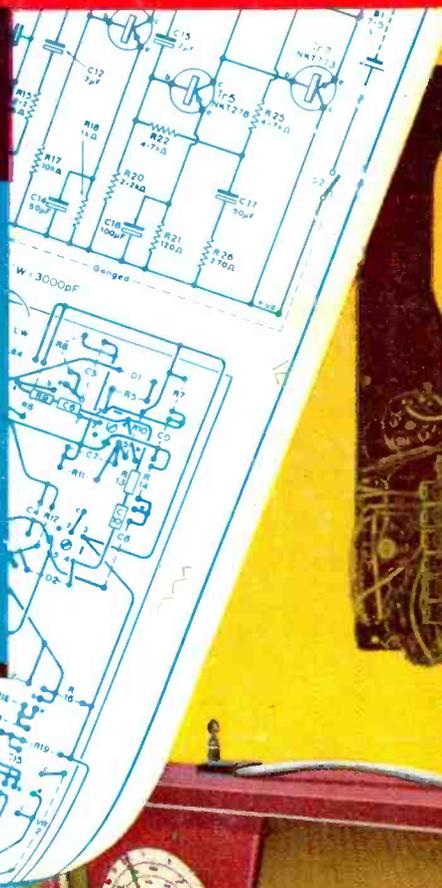**DOUBLE-SIDED
BLUEPRINT**
to build this
**3-WAVE BAND
7-TRANSISTOR
RECEIVER**




THE EMPIRE 7
TRANSISTOR PORTABLE



SOLDERING EQUIPMENT

FOR THE RADIO CONSTRUCTOR

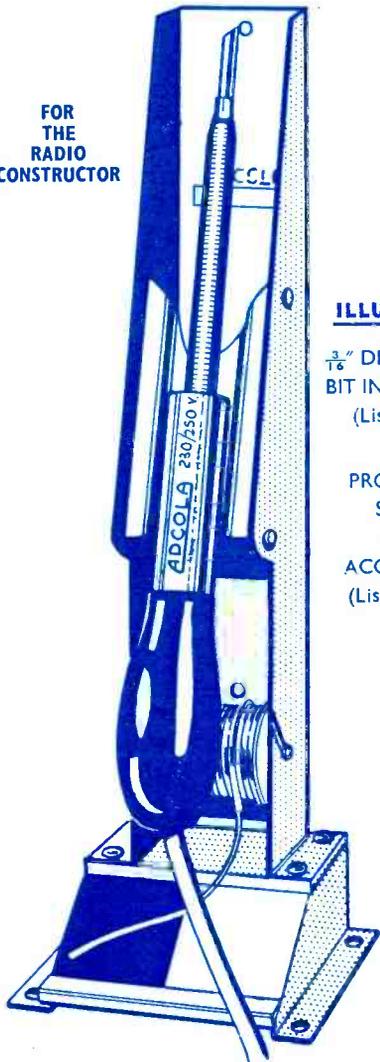

ILLUSTRATED

3/8" DETACHABLE BIT INSTRUMENT
(List No. 64)


IN PROTECTIVE SHIELD WITH ACCESSORIES
(List No. 700)

FOR CATALOGUES APPLY DIRECT
ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4

Telephones:
MACaulay 3101
4272
LONDON SW4

Telegrams: "SOLJOINT"

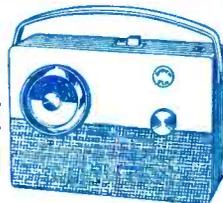The
SUPER 6
LONG & MEDIUM WAVE
TRANSISTOR RADIO



A quality radio available as a kit or ready built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12.12.0 commercial model.
★ All new parts. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit, Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet, 11 x 7 1/2 x 3 1/2 in. ★ Vinyl covered in various colours. ★ 6 x 4 in. speaker giving good bass and treble response. ★ Full instruction booklet 2/- Free with kit. ★ I.F. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately. Write for list. S.A.E. please. ★ 9v. battery required. VT9 or P.P.9 (3/9 with kit).

COMPLETE KIT ONLY **£4.17.6**
PLUS 5/- POST
OR FULLY BUILT £6.17.6 Tax & Carr. paid

Volume and Tone Controls. In order, value; with or without mains switch; spindle length from fixing face; body dia.; price. A—2Mlog, SP, 2 1/2, 1 1/2, 3/-; B—2Mlog, NO, 2 1/2, 1 1/2, 2/-; C—1Mlog, DP, 1, 1, 3/-; D—1Mlog, NO, 1 1/2, 1, 2/-; E—500Klog, DP, 1 1/2, 1 1/2, 3/-; F—500Klin, NO, 1, 1, 2/-; G—100Klin, DP, 2 1/2, 1 1/2, 3/-; H—100Klog, DP, 2 1/2, 1 1/2, 3/-; I—100Klin, NO, 1 1/2, 1 1/2, 2/-; K—50Klin, DP, 2 1/2, 1 1/2, 3/-; L—5Klog, DP, 2 1/2, 1 1/2, 3/-; M—1Klin, NO, 2 1/2, 1 1/2, wirewound, 2/-; N—150lin, NO, 1 1/2, 1, wirewound, 2/-; post 9d. (1); 1/- (2 or more). Parcel 1 of each, 13 controls, 25/-, post paid.

ELECTRONICS (Camberley) LTD.
15 VICTORIA AVENUE, CAMBERLEY, SURREY
Post orders only please



SAVBIT ALLOY
saves wear on soldering iron bits

The world-famous copper loaded alloy containing 5 cores of non-corrosive flux, that saves the soldering iron bit. Ersin Multicore Solder is also available in high tin quality alloys. 60/40 in 22 s.w.g. for printed circuits, transistors, etc.

SAVBIT SIZE 1 CARTON

Contains approximately 30 feet of 18 s.w.g. SAVBIT. It is also supplied in 14 s.w.g. and 16 s.w.g. Obtainable from radio and electrical stores.



5/- each

THE HANDY DISPENSER



Easy to find in the tool box—simple to use. Virtually a third hand for tricky soldering jobs. 12 feet 5-core 18 s.w.g. ERSIN MULTICORE SAVBIT alloy in a continuous coil used direct from free-standing dispenser.
2/6 each

BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, adjustable to most thicknesses. Splits extruded plastic twin flex.
3/6 each



MULTIGORE SOLDERS LTD.

MULTIGORE WORKS • HEMEL HEMPSTEAD • HERTS. (BOXMOOR 3636)

★ VALVES ★

by return of post
THE MOST ATTRACTIVE COMPETITIVE VALVE LIST IN THE COUNTRY

All valves are new and unused unless otherwise advised

POST 3 MONTHS FREE TRANSIT INSURANCE. Satisfaction or Money back (transfer on Goods if returned within 14 days)

074	4/6	6K8G1	6/-	20L1	16/-	DL92	5/-	EZ90	5/9	U22	6/9
1A70T	8/3	6K7	5/9	20P1	9/9	DL94	6/6	EZ81	6/-	U24	12/6
1050T	7/-	6K7G	2/-	20P3	12/6	DL96	7/8	FC4	8/-	U25	10/6
1D5	7/-	6K7GT	4/9	20P4	17/-	EA32	1/3	FW/4500	7/-	U26	8/6
1D6	9/9	6K8G	5/-	20P5	15/-	EA8C80	6/9	GTIC	12/6	U31	7/-
1H50T	8/9	6K8GT	11/-	25AAG	8/-	EAC91	4/-	GZ32	7/6	U33	14/-
1L4	3/-	6K25	8/9	25L6GT	7/9	EAF42	8/3	GZ34	11/6	U35	12/6
1LD5	4/3	6L1	9/9	25S5G	8/-	EBB34	1/3	HK90	9/6	U37	20/-
1LW5	4/6	6L6G	7/6	25ZAG	7/-	EC41	5/-	HL4DD	8/6	U39	4/9
1N5GT	8/9	6L18	7/9	25Z6G	8/-	EB91	3/-	HN309	10/-	U52	4/9
1R5	5/6	8L19	11/6	25Z6G	8/-	EBC33	4/9	HVR2	9/-	U56	5/6
1U5	5/6	8LD20	7/9	27SU	17/6	EBC41	7/9	KT32	6/9	U78	4/6
1S4	7/6	8N7	7/9	30C15	11/6	EBC81	7/8	KT33C	4/9	U107	12/6
1S5	4/6	8P1	9/6	30C15	11/6	EBC81	7/8	KT34	14/-	U191	11/6
174	3/4	8P1	9/6	30F5	6/6	EBC83	9/6	KT44	6/-	U26	9/6
2D21	5/6	8P25	8/6	33FL1	9/6	EBCF89	7/9	KT55	17/6	U282	12/-
3A4	4/-	8Q2G	9/9	30L1	6/6	EBL21	10/9	KT61	11/-	U301	12/-
3A5	8/9	8Q2GT	8/9	30L15	9/9	EC52	4/9	KT63	4/6	U309	6/6
3D6	4/9	8Q2GT	8/9	30E1	6/6	EC31	4/6	KT78	17/-	U329	9/6
3E4	7/-	8R7G	9/-	30P12	7/6	EC32	5/6	KT78	8/6	U329	9/6
3Q4	5/-	8SA7	5/9	20P19	13/6	EC34	4/6	KT88	19/-	U403	10/6
3V4	6/6	8SC7	4/9	30PL1	9/3	EC32	4/-	KTW61	5/9	U404	6/-
5R4GY	9/6	8S67	4/6	30PL13	9/6	EC33	4/9	KTW62	6/6	U801	17/6
5T4	8/9	8S7	3/4	35C5	8/6	EC34	9/-	KTW63	5/9	UAB630	7/-
5V4G	7/6	8SK7	5/6	35C5	8/6	EC34	9/-	L7	17/-	UAF42	7/9
5V4G	7/6	8SK7	5/6	35W4	6/-	EC40	9/6	L87	3/-	UB41	7/9
5Y3G	4/9	8SL7GT	5/9	35Z4GT	5/6	EC81	5/6	LN152	6/6	UB41	7/9
5Y3GT	5/6	8SN7GT	4/9	35Z6GT	7/-	EC82	5/6	LN152	6/6	UBC31	7/9
5Y4G	9/6	8S47	5/9	41	6/6	EC83	6/6	N37	10/6	UBF80	7/9
5Z4	9/-	8S57	4/6	42	6/6	EC34	6/6	N78	17/-	UBF89	7/9
5Z4G	7/6	8U4GT	9/6	50B85	7/9	EC85	6/6	N108	17/-	UBL1	12/6
5Z4GT	9/6	8V8G	4/6	50C5	8/6	EC88	8/6	N152	8/7	UC92	7/9
6/30L2	9/-	8V8GT	6/9	50L6GT	7/6	ECF80	8/9	P41	7/6	UCCR4	9/9
6A6	3/6	8K4	4/9	50E3K	9/6	ECF82	8/3	P61	2/9	UCC55	7/6
6A7	9/-	8K5G	5/-	61ET	17/6	ECH21	10/9	PAB30	8/-	UCF30	10/6
6A8G	7/6	8K5GT	6/6	61SPT	11/-	ECH35	11/6	P36	11/6	UCH21	9/6
6A8GT	12/6	7B8	10/9	62BT	13/6	ECH42	8/6	PC97	9/6	UCH42	7/9
6AC7	3/-	7B7	7/9	75	5/6	ECH81	7/-	PC84	6/6	UCH81	7/9
6AG5	2/9	7C5	7/9	78	5/-	ECH83	8/6	PC85	7/9	UCH82	9/6
6AG7	6/9	7D2	7/6	80	5/6	EC180	6/6	PC88	11/6	UCH33	12/-
6AK5	5/-	7H7	7/6	83	9/6	EC82	8/6	PC89	9/6	UF41	8/-
6AL5	3/3	7Y4	6/-	185BT	19/6	EC183	10/6	PC189	12/-	UF42	5/6
6AM6	3/-	7Z4	6/-	185BTA	19/6	EC184	12/-	PCF80	6/9	UF80	3/-
6AQ5	6/-	8D3	3/-	807	7/9	EC186	10/3	PCF82	7/-	UF85	7/6
6AT6	5/-	10C1	11/6	813	4/6	EF22	7/-	CF34	13/-	UF39	3/-
6AV6	7/-	19C2	14/6	822	14/-	EF36	3/8	PCF86	11/-	UL41	2/-
6AV6	9/9	10F1	4/9	866A	12/6	EP37A	8/-	PC182	7/3	UL44	14/-
6B7	8/6	10F9	10/6	954	3/9	EP39	7/6	PLC33	9/6	UL46	9/9
6B8G	3/-	10P18	10/-	955	2/3	EP40	11/-	PLC14	7/3	UL34	6/6
6BA9	5/6	10LD11	14/6	963	2/-	EP41	8/-	PLC33	8/6	UM80	3/9
6BE6	5/6	10P17	8/6	1025	5/6	EP42	6/9	PLB85	10/6	U10	7/6
6BGG	15/-	10P14	9/6	1060	7/6	EP50-3R16	12/6	PEN25	3/9	UUG	11/6
6BH6	6/6	10P18	7/-	6057	9/6	EP50(A)-2	11/6	PEN45	8/6	U07	9/6
6B36	5/9	12A8	2/3	3067	9/6	EP54	3/-	PEN46	4/6	U09	13/6
6BQ7A	6/6	12AH8	11/6	3703	3/6	EP80	4/6	PL38	9/6	UY1N	11/-
6BR7	8/6	12AT6	6/6	89001	3/6	EP85	6/6	PL38	9/6	UY21	9/6
6BR9	7/9	12AD6	5/6	9002	4/9	EP89	6/6	PL38	15/-	UY41	6/-
6BW8	7/9	12AD6	9/-	9003	5/9	EP89	6/6	PL51	8/3	UY35	6/-
6BW7	5/-	12A07	6/-	ATP4	2/6	EP91	3/-	PL82	6/6	VP4B	9/-
6C4	2/3	12AV6	6/9	A231	7/9	EP92	3/-	PL83	6/6	VP23	2/9
6C5	5/6	12AX7	6/-	R38	6/9	EP183	9/6	PL84	9/6	VF41	6/6
6C8	3/6	12B26	6/6	C18	8/-	EP194	9/6	PL820	8/3	VR105	5/6
6C9	11/6	12B26	6/6	C18	8/-	EP194	9/6	PMS4	8/6	VR150	5/6
6CD6G	10/6	12BH7	8/9	CHL31	13/6	EL32	3/6	PK4	12/6	W76	4/9
6CH6	6/3	12C3	5/6	CHL31	13/6	EL33	11/-	PK25	9/-	W81	7/3
6D2	3/6	12E1	17/6	D77	3/3	EL34	11/6	PK3	10/-	X63	11/6
6D3	9/6	12F9	17/6	DA30	11/6	EL35	6/-	PY32	10/6	X63	11/6
6D8	3/6	12G7	9/-	DA32	8/3	EL38	12/6	PY30	9/6	X680	7/9
6F1	4/9	12J7GT	4/9	DA31	4/6	EL41	8/-	PY31	6/3	X76M	11/-
6F6	7/9	12K7GT	4/9	DA36	7/3	EL42	9/6	PY32	9/6	X78	2/3
6F6G	4/6	12K8	9/9	DF33	8/9	EL41	8/9	PY33	6/9	X79	2/3
6F13	4/6	12K83GT	11/6	DF91	3/-	EL34	3/6	PY88	8/9	X81M	9/-
6F14	9/6	12S7GT	4/9	DF96	7/3	EL35	9/9	PY80	7/9	Y63	6/-
6F15	9/6	12S7	8/9	DF96	7/3	EL35	9/9	PY80	7/9	Y63	6/-
6F19	6/-	12S7G	4/6	DH63	5/6	EL35	6/-	PZ2	8/6	Z63	4/9
6F32	4/9	12S7H	3/6	DH76	4/6	EM34	8/9	R19	9/6	Z63	4/9
6F83	4/-	12S7J	5/6	DK32	9/6	EM30	7/6	LL18	11/6		
6H6	1/6	12S7K	4/6	DK51	5/6	EM31	0/9	SP41	2/3		
6H5	4/3	12S7N	6/6	DK92	7/-	EM35	9/6	SP61	2/3		
6H5G	3/-	12S7P	8/9	DE96	7/6	EM39	18/6	SUS5	5/6		
6J5GT	4/3	13D3	6/6	DL33	7/6	EY1	7/6	EY2150	4/6		
6J6	3/6	19A25	7/9	DL35	7/6	EY88	7/3	T41	6/9		
6J7	8/9	19B98	14/-	DL63	8/-	EY88	9/6	TDD4	8/6		
6J7G	4/9	20D1	8/6	DL76	8/-	EZ40	7/-	U14	7/6		
6J7GT	7/6	20E2	9/6	DL82	9/-	EZ41	7/-	U18	7/6		

Tubes

Carr. & Ins. 12/6

MOST MULLARD	12in.	£2. 0. 0	£3. 0. 0	NEW TYPES
MAZDA, COSOR	14in.	£2.10. 0	£3.10. 0	MW 31/74
EMITRON. EMISCOPE. BRIMAR.	15-17in.	£3. 5. 0	£4. 5. 0	MW 38/24
FERRANTI TYPES, PROCESSED IN OUR OWN FACTORY	19in.	£3. 5. 0	£4. 5. 0	MW 38/24
	21in.	£3.15. 0	£5.15. 0	ORM 172
	23in.	£3.15. 0	£5.15. 0	MW 43/64
				£6.0.0

SATISFACTION GUARANTEED

TRANS/RECEIVERS

Type STR808. Latest 9 Transistor Loudspeaker type. 4-4 miles range. Few at pre-increase price of **£25**

PROFESSIONAL TAPE RECORDER

MAYFAIR FT157. Four Transistor, Capstan Drive, Two Speeds, Dual Track, Push-button Controls, Tape, Ideal Speech and Music, Many Refinements, Only 3 1/2" Wav Flatter, Beautiful Finish with Mike, Sm. Tape, Telephone adaptor. **£17.17.0**

TRANSISTORS

GUARANTEED TOP QUALITY Huge reduction. Red Spot standard L.P. type now only White Spot R.F. **1/6**
2/-

Mullard Matched Output Kits OC311 and 2-OC81 **12/6**
R.F. Kits OC44, OC45 (2) **12/6**

AP14	8/-	OC44	5/6
AF15	7/6	OC45	5/6
AF16	7/6	OC72	5/6
AF17	7/-	OC81	5/6
AF127	9/6	OC81D	5/6
OC26	13/6	OC82	6/-
OC36	14/-	OC170	8/6
	OC171	8/6	

CO-AX.

low loss, 6d. yd., 25 yards, 11/6; 50 yds., 22/-; 100 yds., 42/6; Co-ax Plugs, 1/3. Wall outlet boxes 3/6.

SPECIAL C.R.T. OFFER

Due to huge Bulk Special Purchase we are offering MW 31/74 Tubes at the unrepeatable price of 29/-, MW 36/24 at 39/-, P.P. 12/6. The above are guaranteed for 6 months.

LOUDSPEAKERS

3Ω Top Makes
6 1/2in. **7/6** 6in. **8/6**
8in. **7 x 4in. 8/6**

GERMANIUM DIODES

General Purpose miniature detector, A.V.C. etc. **8d.**
or 6/6 doz.
Gold Bonded highest quality. Individually tested. **1/-**
9/6 doz.

SILICON RECTIFIERS

Guaranteed self performance. Top Makes Tested 250V working.

100mA	250mA
(3 for 9/6)	3/9 (3 for 19/6)
	7/6

CONNECTING WIRE

P.V.C. Bright Colours. Five 25ft. coils only. **4/-**

VALVE HOLDERS.

B76, 6d. ea., with Screen 8d. ea., 19A 8d. ea., with Screen 8d. ea. 14L Octal 6d., Mazda Octal 4d. 8A 6d. (less 15% in dozens).

MAINS TRANSFORMERS

Excellent Quality Guaranteed. Upright mounting 250-0-250 V. 6.3 V. 3 A (80mA 12/6) **9/6**
110 to semi-shrouded 9/6.

LINE TRANS

Huge quantity, most makes at S.A.E. enquiries. **29/-**

13 CHANNEL T.V.s

Table Models, Famous Makes. Absolutely Complete. These sets are unequalled in value due to huge purchase direct from source. They are untested and not guaranteed to be in working order. Carr. etc., 15/-.

14in. **£2.19.0** 17in. **£4.19.6**

ELECTRIC MOTORS.

AC/DC 3-8 volts. Totally enclosed standard mounting, powerful V pulleys, square flanges, 2 1/2 x 2 1/2. **7/6**

ELECTROSTATIC SPEAKERS

Type LSHT5. Originally 25/-. As fitted to Gorman Hi-Fi Radios, Bargain 5/- ea. 9/6 pair

TURRET TUNERS

Most makes, your choice if available, with valve 16/-, less valves 10/6. S.A.E. enquiries.

ACCUMULATORS

Small 2 volt 3 amp/hour, 3/6 each.

H.T. TRANSFORMERS

200/250V ea. 350-0-350V 15 mA 6.3V 5 amp, 5V 3 amp. Gift 27/6.

★ BULK BARGAINS ★

12 POTS. Popular values. 5K to 2 Meg. Unused, mixed, pre-set, long sw., etc. **4/6**

CONDENSERS, 25 Mixed Electrolytic.

Many popular sizes. List Value £5. Our price **10/-**

TUNING CONDENSERS

F.M. 2 gang 15-415pF standard with slow motion, 3/9. AM/EM 50 pF and 15 pF 2 gang with slow motions, 4/9. Standard 1.0005 2 gang, 4/6. Binaid .0005 2 gang, 4/6.

100 RESISTORS

Excellent. Sizes 3 watt. **6/6**

A.C. MOTORS

For 230V ea. Powerful, self-starting, weight 1 1/2 lb. 12/6.

100 CONDENSERS

Miniature Ceramic and Silver Mica Condensers, 3 pF to 5.0

R.S.C.
(MANCHESTER) LTD.

MAIL ORDERS TO:
54 WELLINGTON
STREET, LEEDS 1

Terms: C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please. Personal shoppers welcomed at all of the branches below. Open all day Saturday.

BRADFORD 10 North
Parade & 54-56
Morley Street
(Half-day, Wednesday).

BRISTOL 14 Lower Castle Street
(Half-day Wednesday)
Tel. 22904

BIRMINGHAM

30/31 Gt. Western Arcade, opp. Snow Hill Station. CENRAL 1279. No half-day

DERBY 26 Osmaston Rd., The Spot
(Half-day Wednesday)
Tel: 41361

DARLINGTON 13 Post House
Wynd (Half-day
Wednesday) Tel: 68043

EDINBURGH 133 Leith Street,
(Half-day Wed.)
Tel: WAverley 5766

GLASGOW 326 Argyle Street.
(No Half-day).
Tel: CITY 4158

HULL 51 Savile Street (Half-day
Thursday) Tel: 20505

LEICESTER 32 High Street (Half-day
Thurs.) Tel: 56420

LEEDS 5-7 County (Mecca) Arcade
(No half-day) Tel: 28252

LIVERPOOL 73 Dale St. (No half-day)
Tel: CENtral 3573

LONDON 23B Edgware Road W2
(Half-day Thursday)
Tel: PADdington 1629

MANCHESTER

60A-60B Oldham St. Tel: Central 2778
(No half-day) New large store.

MIDDLESBROUGH 106 New-
port Rd.
(Half-day Wednesday) Tel: 47096

SHEFFIELD 13 Exchange Street
Castle Market Bldgs.
Tel: 20716

EX. GOV., 2V ACCUMULATORS,
16 A.H. Size 7 x 4 x 2 1/2. Brand new,
4/9 each. Three for 12/6, carr. 5/-.

MULTI-METERS CABY MI. Sensitivity
2,000 ohms per volt. A.C. and D.C. 54/-.
A.10. Basic Meter sensitivity 155 micro-
amps A.C. and D.C. ranges £411.6, 14-40.
Sensitivity up to 10,000 ohms per volt A.C.
and D.C. £6.2.6. 30,000 ohms per volt. with
overload buzzer. £8.18.6. Other types in
stock from 3/8/.

TRANSISTOR SALE Mullard OC71 3/9,
OC45 4/11, OC44 4/11, OC73 2/9, OC81 4/11,
Ediswan XA101 3/9, XA112 3/9, XB113 3/9,
XB104 3/8, XC101A 3/8. Postage 6d. for up
to 3 transistors.

EX GOVT. SELENIUM
RECTIFIERS 12v 15 AMP **19/9**
(BRIDGE) F.W. ONLY


EX. GOVT. SMOOTHING CHOKES,
200 mA, 3-5 H, 50 ohms. Parmeko 8/9;
150mA, 10 H, 50 ohms 9/9; 120mA, 12 H, 100
ohms, 8/9; 100mA, 10 H, 100 ohms, 6/9; 100
mA, 5-10 H, 250 ohms, 2/11.

TANNOY RE-ENTRANT LOUD-
SPEAKERS. For outdoor use **25/9**
Factory use, 8 ohms, 8 watts. Only

HI-FI 10 WATT AMPLIFIER
Brand New Complete **£7.19.6** Carr.
5/6

Manufacturer's discontinued Model. Push-
pull output. Latest high efficiency valves.
Dual separately controlled inputs for
'Mike' and gram. Separate Bass and
Treble Controls. High Sensitivity. Output
for 8 or 15 ohm speaker. Guaranteed tested
and in perfect working order.

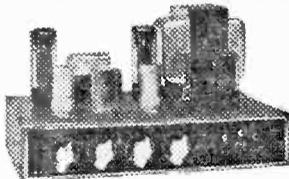**R.S.C. 30-WATT ULTRA LINEAR
A10 HIGH FIDELITY AMPLIFIER**



A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 dB down. Frequency response ± 3 dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that ANY KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS, or OUTDOOR FUNCTIONS, etc. For use with ELECTRIC ORGAN; BASS, LEAD OR RHYTHM GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDES L.T. and H.T. for RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250v, 50 c/s. A.C. Mains and has output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required handles can be supplied.

11 Gns.
Carr. 10/-
for 19/9. The amplifier can be supplied factory built with EL34 output valves and 12 months' guarantee, for 14 gns. Send S.A.E. for leaflet.

TERMS: DEPOSIT 3/6 and 9 monthly payments of 33/6 (Total 18 gns.) Suitable microphones and speakers available at competitive prices.

R.S.C. 4/5 WATT A5 HIGH-GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest High-fidelity Pick-up heads in addition to all other types of pick-ups and practically all "mikes", separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 71 dB down. 15 dB of Negative feedback is used. I.T.T. of 300 v, 25 mA and L.T. of 6.3 v, 1.5A, is available for the supply of a Radio Feeder Unit, or Tape-Deck, pre-amplifier For A.C. mains input of 200-250 v 50 c/s. Output for 2-3 ohms speaker. Chassis is not live. Kit is complete in every detail and includes fully punched chassis (with baseplate) with Gold Hammer flush and point-to-point wiring diagrams and instructions. Exceptional value **£4.15.0** or assembled ready for use 22/6 carr. deposit 22/6 and 5 monthly payments of 22/6 (Total £8.10) for assembled unit.

TERMS: DEPOSIT 22/6 and 5 monthly payments of 22/6 (Total £8.10) for assembled unit.

JASON FMTI

V.H.F./P.M. RADIO TUNER DESIGN of parts including valves, tuning dial, escutcheon, etc. Total cost **£6.19.6**

SUPERHET FEEDER UNIT. Design of a high quality Radio Tuner (specially suitable for use with our Amplifiers). Delayed A.V.C. Controls are Tuning, W/Ch. and Vol. Only 250v, 15mA H.T. and L.T. of 6.3v. 1 amp. required from amplifier. Size approx. 9 x 6 x 7 1/2 in. High. Simple alignment procedure. Point-to-point wiring diagrams, instructions and priced parts list with illustrations. 2/6. Total builds costs 25.5.0. S.A.P. for leaflet.

TRANSISTORISED SOUND MIXER

Enables mixing of up to 4 inputs, i.e. m.c., tape, gram., tuner, etc., into single output. Compact and completely self-contained, uses standard 9 volt battery. Four standard Jack inputs.



PRICE **49/6**

FANE HEAVY DUTY HI-FI SPEAKERS


12in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 122/10 20watt, 8gns. 122/12 20watt, 7gns. 122/13 20watt, 8gns. 122/14 22watt, 8gns. 122/14A 22watt, 10gns. 122/17 25watt, £11.17.6 122/17A 25watt, £12.17.6

15in. 15 ohms. Cast chassis. Exceptionally robust 2in. diam. Voice Coil Assemblies. 152/12 20watt, 12gns. 152/12A 20watt, 13gns. 152/14 27watt, 14gns. 152/14A 27watt, 15gns. 152/17 35watt, 16gns. 152/17A 35watt, 17gns. "A" indicate dual cone type. 30-17,000 c.p.s. Send S.A.E. for leaflets and terms

R.S.C. GRAM AMPLIFIER KIT. 3 watts output. Negative feedback. Controls Vol., Tone and Switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.

GL3A MINIATURE 2-3 WATT GRAM AMPLIFIER. For use with any single or auto-change unit. Output for 2/8 ohm speaker. For 200-250v. A.C. mains. Size 1 1/2 x 2 1/2 x 2 1/2 in. Controls: Vol. and Tone with Switch. Only 59/6.

12 in. 10 WATT HIGH QUALITY LOUDSPEAKER

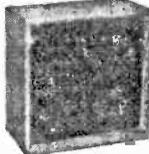

In walnut veneered cabinet. Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only Carr. 5/- **£4.19.6**

Terms: Deposit 11/3 and 9 monthly payments of 11/3. (Total £5.12.6)

12" 20 WATT HI-FI LOUDSPEAKERS IN CABINETS. Size 18 x 18 x 10 in. Finish as above. Only £7.19.6. Terms: Deposit 7/9 and 9 monthly payments of 17/9 (Total £8.17.6). Carr. 8/6.

LINEAR TREMOLO/PRE-AMP. UNIT Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3v. A.C. L.T. The unit plugs into power supply point and any input socket or amplifier. Controls are Speed (frequency of interruptions). Depth (for heavy or light effect). Volume and Switch. Three sockets are for two inputs and Foot Switch. ONLY **4 Gns.**

R.S.C. G5 AMPLIFIER

for Guitar, 'Mike', Gram or Radio

5 watt high quality output. Incorporating high flux 12in. 10 watt 12,000 line loudspeaker. Sensitivity 30 m.v. High impedance pick input. Handsome strongly made cabinet (size 14 x 14 x 7in. approx.) finished in complementary shades of Rexline/Tyran. 200-250v A.C. mains. Suitable for Lead or Rhythm Guitar in home or small club, etc. £9.19.6. OR DEPOSIT 22/3 and 9 monthly payments of 22/3 (Total £11.2.6). Carr. 7/6.

R.S.C. BABY ALARM or INTER-COMM KIT. Complete set of parts with diagrams, etc. Housed in two polished walnut finished cabinets of pleasing design. High sensitivity. For 200-250v. A.C. mains. Fully isolated. Controllable at both units. An intercomm. of this class would normally cost £20-30. Only 8/6, carr. 5/- or assembled ready for use. 6 Gns.





R.S.C. G100 100 WATT AMPLIFIER

TERRIFIC POWER OUTPUT FOR ALL PURPOSES!


For **ELECTRIC ORGAN, LEAD, RHYTHM and BASS GUITAR** and any other musical instrument. FOR **VOCALIST, Gram, RADIO and Tape etc.**

- ★ Incorporating **SIX 12in. PLUS TWO 15in. HEAVY DUTY LOUD-SPEAKERS.** Total Rating, 140 watts.
- ★ Housed in 4 substantial Wood Cabinets of pleasing design and covered in contrasting shades of Rexine and Vynair with 'gold' trimmings.
- ★ 4 Jack Inputs in **TWO CHANNELS** with 4 Independent Volume Controls.
- ★ Separate Bass and Treble Controls on each channel.
- ★ For standard 200-250v. A.C. mains operation.

Fantastic Value **89¹/₂** Carr. 30/-
Gns.

Or Deposit **£10.14.2** and 52 weekly payments of 35/- (Total 97¹/₂ Gns.)

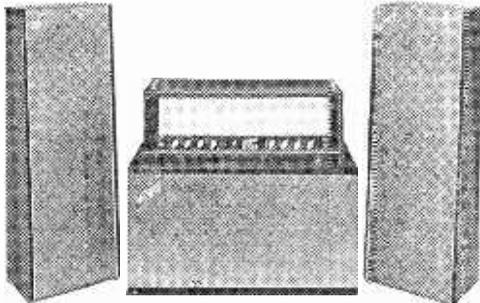
Send S.A.E. for full descriptive leaflet, or visit one of our many branches and hear this fabulous amplifier



ALL INTEREST CHARGES REFUNDED IF SETTLEMENT MADE WITHIN 6 MONTHS

R.S.C. BASS-REGENT 50 WATT AMPLIFIER

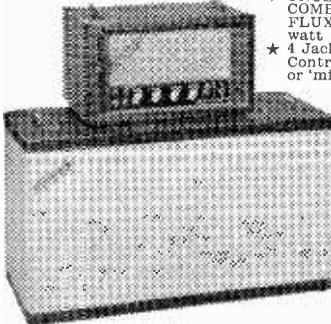AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT For lead, rhythm, bass guitar and all other musical instruments For vocalist, gram, radio, tape and general public address



- ★ UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a **PANE HIGH FLUX 15in. 30 watt unit PLUS A FANE 12in. 20 watt unit** with extended frequency response.
- ★ 4 Jack Socket Inputs and two Independent Vol. Controls for simultaneous use of up to 4 pick-ups or 'mikes'.

★ Separate cabinets fully covered in contrasting tones of Rexine/Vynair with 'gold' trimmings, for speakers and amplifiers.

★ Separate Bass and Treble Controls giving 'boost' and 'cut'.

Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at more than three times the cost. Carr. 17/6.


47 Cash Price **£5.11.0**
Gns. Or Deposit and 12 monthly payments of **£4.** (Total 51 Gns.)

INTEREST CHARGES REFUNDED IF SETTLED IN 6 MONTHS

HEAVY DUTY LOUDSPEAKERS IN SUBSTANTIAL CABINETS

TYPE BGI
Two Tone Rexine/Vynair covered. Suitable for Bass Guitar. Speaker Unit 15in. High Flux, 15 ohms, 30 watts. Cabinet size approx. 24 x 21 x 13in. Only **19¹/₂ Gns.**

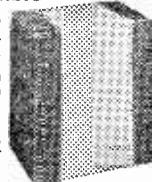Or Deposit 5/9 and 9 monthly payments of 4/5. (Total 21¹/₂ Gns.)



R.S.C. BASS/20 AMPLIFIER

SUITABLE FOR BASS GUITAR

A highly efficient unit incorporating massive 15in. high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample 'Boost' and 'Cut'. Two jack socket inputs separately controlled. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24 x 21 x 13in. Carr. 17/6
Send S.A.E. **29¹/₂ Gns.** Or deposit for leaflet **£3.4.6** & 12 monthly payments of 5/6. (Total 32¹/₂ Gns.)

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. Normally supplied for 15 ohm matching but can be supplied for 100v. line for 35/- extra.
Type C38. 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 42 **12¹/₂ Gns.** Carr. x 10 x 5in. **10/-**
Or deposit of 29/- and 9 monthly payments 29/- (Total £14.10.0).
Type C42. 40 watts. Fitted four 12in. 12,000 line 10 watt speakers. Overall size 52 x 13 x 7in. approx. **19¹/₂ Gns.** Carr. 15/-
Or Deposit of 31/9 and 9 monthly payments of 44/5 (Total 21¹/₂ Gns.)



R.S.C. BASS-MAJOR 30 WATT AMPLIFIER


A MULTI-PURPOSE HIGH FIDELITY HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTAL GROUPS

Eminently suitable for lead, rhythm, bass guitar and all other musical instruments

- ★ Incorporating two 12in. 25 watt Heavy Duty. High Flux Fane Loudspeakers, one with dual cone for high frequencies.
- ★ Robust wood cabinet with exceptionally attractive covering of Rexine/Vynair with gold trimmings.
- ★ Four Jack Socket Inputs and two Independent Volume Controls for simultaneous connection of up to four Pick-ups or 'Mikes'
- ★ Separate Bass and Treble Controls.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.


39¹/₂ Gns. Carr. or call for demonstration at any branch. Send S.A.E. for leaflet 17/6

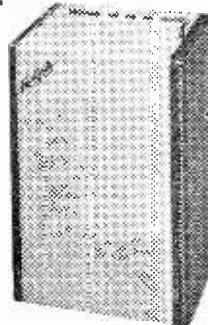Terms: Deposit **£4.3.0** and 12 monthly payments of **£3.8.4** (Total 43 Gns.)



R.S.C. G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, 'Mike', Gram, or Radio


High-fidelity push-pull output. Separate bass and treble "Cut" and "Boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Loudspeaker is a heavy duty high flux 12in. 20 watt model with cast chassis. Cabinet is covered in contrasting shades of Rexine/Vynair. Size App. 18 x 18 x 8in. Carr. **19 Gns.** 10/-
Send S.A.E. for leaflet Or DEPOSIT 2 Gns. and 12 monthly payments of 33/3 (Total 21 Gns.)

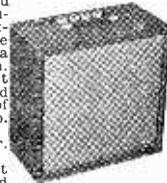

30W. HIGH QUALITY AMPLIFIER


A Four Input, two volume control Hi-Fi unit with separate Bass and Treble "Cut" and "Boost" controls. Designed for vocal or instrumental groups. For Bass, Lead or Rhythm Guitar. Six Mullard or Brimar latest type valves. Housed in strong Rexine covered cabinet with twin chrome carrying handles. Attractive black and gold perspex fascia plate. For 200-250v. A.C. mains. Output for 3 or 15 ohm speakers. Send S.A.E. for leaflet.

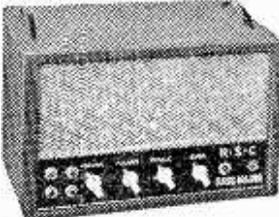16¹/₂ Carr. or Deposit 2 Gns. and 9 monthly payments of 38/6 **Gns.** (Total 18¹/₂ Gns.)



R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER

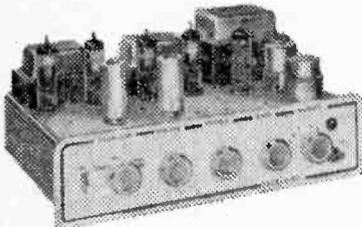PROVIDING 10/14 WATTS ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL



SUITABLE FOR "MIKE" GRAM., RADIO OR TAPE. INTENDED FOR THE HOME OR STUDIO BUT SUITABLE FOR LARGE HALLS OR CLUBS

Features include:

- ★ Four-position tone and compensation Input Selector switch.
 - ★ Stereo/Mono switch so that peak monaural output of 22 watts can be obtained.
 - ★ Separate Bass "Lift" and "Cut" and treble "Lift" and "Cut" controls.
 - ★ Neon panel indicator.
 - ★ Handsome Plexiplex Frontplate. **13 Gns.**
- Send S.A.E. for illustrated leaflet. Carr. 10/- Complete set of parts with point to point wiring diagrams and instructions, or Factory assembled, tested and supplied with our usual 12 months' guarantee for 18 gns, or DEPOSIT 2 gns. and nine monthly payments of 4/6 (Total £11.5)

Based on a current Mullard design and employing valves ECC83, ECC85, ECL86, ECL86, ECL86, ECL86, E281. Output transformers are high quality sectionally wound to required specification. Output matchings for 3 and 16 ohm speakers on each channel.

FREQUENCY RESPONSE ± 2dB. 20-20,000 c.p.s.
HUM LEVEL 65dB down.
SENSITIVITY: 15 millivolts maximum.
HARMONIC DISTORTION (each channel) 0.2%.

For operation on 200/250v. A.C. Mains.

AUDIOTRINE HI-FI TAPE RECORDER KIT 25 1/2

REALISM AT INCREDIBLY LOW COST. CAN BE ASSEMBLED IN AN HOUR
Incorporating the latest Colliaro Studio Tape Transcriber. The Audiotrine High Quality Tape Amplifier with negative feedback equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a Handsome Portable Carrying Cabinet, tastefully covered in two contrasting shades of Rexine and Vynair, size 14 1/2 x 15 x 9 1/2 in. high and circuit. Total cost if purchased individually approximately £40. Performance equal to units in the £60-£80 class. S.A.E. for leaflets. TERMS: Deposit £3 and 12 monthly payments of 4/-. (Total £26.00)

1 GNS.
Carr. 17/6



ONLY 3 PAIRS OF SOLDERED JOINTS PLUS MAINS

INTEREST CHARGES REFUNDED

on H.P. and CREDIT SALE Accounts settled in 6 months

HI-FI CRYSTAL PICK-UP HEADS (Cartridges). Acoos Standard replacement for Gerrard, S.S.E. and Colliaro. 10/9. Acoos Stereo-Monaural 29/9. Ronette's Stereo-Monaural 39/9. B.S. Stereo 30/9. **PICK-UP ARMS.** Complete and with latest Acoos/hi-n Turnover Cartridge 29/11. **CRYSTAL MICROPHONES.** Hand type NF110 19/9. R.C.C. 18/9. Acoos Mic. 40 25/9. Acoos Mic. 45 29/9. Stick type Acoos 33-1 39/9. BM3 with neckband and heavy table stand 49/6. Lapel type 29/9.

COLLIARO JUNIOR. 4-speed Single Player Unit and Crystal Pick-up with hi-fi Turnover head. Only 59/6. **B.S.R. UA14 4-speed AUTO-CHANGERS** with hi-fi turnover head. 25-19.6. Carr. 4/6. **GARRARD AUTO-SLIM 4-SPEED AUTO-CHANGER** with high fidelity pick-up. Latest model. For 200-250 v. A.C. mains. 26-19.6. Carr. 4/6. **GARRARD AT5 AUTO-SLIM DELUXE 4-SPEED AUTO-CHANGERS.** Turnover GC8 head, for 200-250 v. A.C. mains. £11-0-0.

R.S.C. POWER PACK. 39/6. Louvered metal case only 8 x 9 1/2 x 2 1/2 in. Stove enamel. For 200-250v. A.C. mains. Output at 4-pin plug and socket 250v. 50 m.A. Fully smoothed and 6.3v 2a. Suitable for Pre-amp. or Radio Tuner.

SCOOP PURCHASE OF HIGH QUALITY BRAND NEW RECORD CHANGERS GARRARD 3000 LM


Very latest model. Normal **10 Gns.** Retail price approx. £12.15.0. Heavy Turntable and light Carr. 5/6. weight pick-up arm. High fidelity Stereo/Mono cartridge. Fully guaranteed.

5/4 STEREO AMPLIFIER
A complete set of parts to construct a good quality Stereo amplifier with an undistorted output total watts. For A.C. mains input of 200-250v. Sensitivity 180 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and wiring diagrams supplied. **5 Gns.**

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES

Two input sockets with associated controls allow mixing of "mike" and gram., as in A10 High sensitivity. Includes 5 valves, ECC83, ECC83, EL84, E281. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut".** Frequency response ±3 dB 30-20,000 c/s. Six negative feedback loops. Hum level 30 dB down. ONLY 23 mV VOLTS INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for STANDARD or LONG PLAYING RECORDS. FOR MUSICAL INSTRUMENTS such as STRING BASS, LEAD or RHYTHM GUITARS, etc.

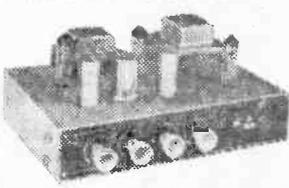

OUTPUT SOCKET with plug provides 300v, 20m.A. and 6.3v. 1.5a. For supply of a RADIO FEEDER UNIT. Size approx. 12 x 8 x 7in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 16 ohm speaker. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Only **8 Gns.** Carr. 10/-

If required louvered metal cover with 2 carrying handles can be supplied for 18/6. TERMS ON ASSEMBLED UNITS. DEPOSIT 9/- and 9 monthly payments of 9/- (Total £12-10-0). Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

LINEAR TAPE PRE-AMPLIFIER. Type LP/1. Switched Negative feedback Equalisation. Positions for Record In., 3In., 7In. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Colliaro Tape Transcriber and a High fidelity amplifier, but suitable for almost any Tape Deck. S.A.E. for leaflet. **Only 9 1/2 Gns.**

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereophonic amplifier giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable for all crystal and ceramic heads. Ganged Bass and Treble Control give equal variation for "Lift" and "cut". Provision is made for use as straight (monaural) 10-watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point-to-Point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. **8 Gns.** Carr. 10/-

Or supplied factory assembled with 12 months guarantee for £11.7.6. Terms: Deposit 2 gns. and 9 monthly payments of 2/6 (Total £12-19-6).

AVAILABLE AT ALL BRANCHES

ARMSTRONG, TRUVOX, LINEAR ROGERS, LEAK and JASON EQUIPMENT, GOODMAN'S, W.B. and FANE SPEAKERS, GARRARD AND GUILDING TURNTABLES, LUSTRAPHONE GRAMPHAN, RESLO AND SHURE MICROPHONES

CASH OR TERMS

W.D. "STENOGRAN" HIGH FIDELITY P.M. SPEAKERS H1012. 10 watts rating. Where a really good quality speaker at a low price is required, we highly recommend this unit with an amazing performance. £4-18-0. Please state whether 3 ohm or 16 ohm required.

R.S.C. JUNIOR BASS REFLEX CABINET. Designed for above speaker, but suitable for any good quality 8in. or 10in. speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18x12x10in. Strongly made. Handsome appearance. Enhance superb reproduction for only £3-19-6.

R.S.C. STANDARD BASS REFLEX CABINET. For 12in. loudspeakers, acoustically lined and ported. Size 20 x 14 x 13in. Beautiful walnut veneer finish. Especially recommended for use with Audiotrine Speaker System.

AUDIOTRINE CORNER CONSOLE CABINETS. Strongly made. Beautifully polished walnut veneered finish. Pleasing design. **JUNIOR MODEL.** To take up to 8in. speaker. Size approx. 20x11x18in. 49/9.

STANDARD MODEL. To take up to 10in. speaker. Size 27 x 18 x 13in. £4-11-9.

SENIOR MODEL. To take up to 12in. speaker and with Tweeter cut-out. Size approx. 30 x 30 x 18in. (Recommended for use with Audiotrine speaker system.) 7 gns. or terms.

AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12in. 12,000 line. 15 ohm high quality speaker; crossover unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating. £4-19-6. Carr. 5/-. Or Senior 20 watt. £6-19-6. Carr. 7/6.





BRADFORD, BRISTOL, BIRMINGHAM, DERBY, DARLINGTON, EDINBURGH, GLASGOW, HULL, LEICESTER, LEEDS, LIVERPOOL, LONDON, MANCHESTER, MIDDLESBROUGH, SHEFFIELD

SEE PRECEDING PAGES FOR ADDRESSES

SELENIUM RECTIFIERS

F.W. BRIDGE	H.T. TYPES H.W.
6/12 v. 1a. 3/11	150 v. 40 mA 3/9
6/12 v. 2a. 6/11	250 v. 50 mA 3/11
6/12 v. 3a. 9/9	250 v. 60 mA 4/11
6/12 v. 4a. 12/3	250 v. 80 mA 5/11
6/12 v. 6a. 15/3	250 v. 250 mA 11/9
6/12 v. 10a. 28/9	
6/12 v. 15a. 35/9	
250 v. 75 mA. F.W. (Bridge), 10/11.	
250 v. 50 mA. F.W. (Bridge), 8/11.	
H.W. 250 v. 60 mA. 5/11.	

Contact Cooled

250 v. 75 mA. F.W. (Bridge), 10/11.
250 v. 50 mA. F.W. (Bridge), 8/11.
H.W. 250 v. 60 mA. 5/11.

COMPLETE POWER PACK KIT

Consisting of Mains Trans., Metal Rectifier, Double electrolytic smoothing choke chassis and circuit. For 200-250v. A.C. mains. Output 250v., 60mA, 6.3v., 2a. **19/11**

CHARGER AMMETERS **8/9**

0-1.5 a., 0-4 a., 0-7 a., each.

R.S.C. BATTERY CHARGING EQUIPMENT

Guaranteed 12 months



charging. Louvered steel case with grey hammer finish. Fused and ready for use with mains and output leads and battery clips. Carr. 4/6. Terms: Deposit 12/- and 5 monthly payments of 12/- (Total £5.12.0).

All for A.C. Mains 200-250v., 50c/s ASSEMBLED HEAVY DUTY CHARGER KIT 6/12 v. 6 amps, variable output Mains Transformer 200-230-250v. F.W. (Bridge) Selenium Rectifier. Ammeter. Variable Charge Rate Selector panels. Plugs. Fuses. Fuse-holder and circuit. 59/9. Carriage 4/6

BATTERY CHARGER KITS Consisting of Mains Transformer F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuse-holders, Grommets, panels, Heavy Duty Clips, circuit. Carr. 3/6 extra. 6v. or 12v. 1 amp. 22/9 As above with Ammeter .. 25/9 6v. or 12v. 2 amps. 25/9 6v. or 12v. 2 amps. including Ammeter 35/9 6v. or 12v. 4 amps. with Ammeter and variable charge rate selector 52/9

SELENIUM RECTIFIER

Brand New 3 for 7/9
6/12v. 2a. F.W. Bridged

ASSEMBLED CHARGER

6/12 v. 1 amp. in enamelled case. Fused and with mains and output leads. **27/9**

CHARGER KIT, 12v. 10 Amp.

with variable charge rate adjustment and ammeter. Fuses, F.W. Metal Rectifier, Mains Trans., 200-250v. 50 c.p.s. and circuit. Carr. 10/-

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened

TOP SHROUDED DROP THROUGH

250-0-250v. 70mA, 6.3v. 2a, 0-5-6.3v. 2a	17/9
350-0-350v. 30mA, 6.3v. 2a, 0-5-6.3v. 2a	19/9
250-0-250v. 100mA, 6.3v. 2a, 6.3v. 1a	21/9
250-0-250v. 100mA, 6.3v. 3.5a, C.T.	19/9
250-0-250v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a	27/9
300-0-300v. 130mA, 6.3v. 4a, 6.3v. 1a, 10r	37/9
10r Mullard 510 Amplifier	37/9
300-0-300v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a	27/9
350-0-350v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a	27/9
350-0-350v. 150mA, 6.3v. 4a, 0-5-6.3v. 3a	37/9

FULLY SHROUDED

250-0-250v. 60mA, 6.3v. 2a, 0-5-6.3v. 2a	17/11
Midjet type 2x 3 x 3in.	28/9
250-0-250v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a	28/9
300-0-300v. 100mA, 6.3v. 4a, 5v. 3a	28/9
300-0-300v. 130mA, 6.3v. 4a, C.T. 6.3v. 1a, for Mullard Amplifier	35/9
350-0-350v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a	28/9
350-0-350v. 150mA, 6.3v. 4a, 0-5-6.3v. 3a	37/9

FULLY SHROUDED (continued)

425-0-425v. 200mA, 6.3v. 4a, C.T. 5v. 3a	57/9
425-0-425v. 200mA, 6.3v. 4a, C.T., 6.3v. 4a, C.T. 5v. 3a	59/9
450-0-450v. 250mA, 6.3v. 4a, C.T. 5v. 3a	60/9
OUTPUT TRANSFORMERS	
Midjet Battery Pentode 66:1 for 3S4, etc.	4/6
Small Pentode, 5,000 Ω to 3 Ω	4/6
Small Pentode, 7,000 Ω to 3 Ω	4/6
Standard Pentode 5,000 Ω to 3 Ω	5/9
Standard Pentode 7,000 Ω to 3 Ω	5/9
10,000 Ω to 3 Ω	5/9
Push-Pull 8 watts, EL84, or 6V6 to 3 Ω or matched to 15 Ω	9/9
Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-8 to 15 Ω	19/9
Following types for 3 and 15 Ω speakers	18/9
Push-Pull 10-12 watts 6V6 or EL84	22/9
Push-Pull 15-18 watts, 6L6, KT66	22/9
Push-Pull Mullard 510 Ultra Linear	29/9
Push-Pull 20 watts, sectionally wound 6L, KT66, EL34, etc.	49/9

MIDGET MAINS Primaries 200-250 v.

50 c/s. 250v. 60mA, 6.3v. 2a.	11/9
250-0-250v. 60mA, 6.3v. 2a.	12/11

Both above size 2 1/2 x 2 1/2 in.

FILAMENT TRANSFORMERS

All with 200-250v. 50 c/s primaries 6.3v. 1.5a. 5/9; 6.3v. 2a. 7/6; 12v. 1a. 7/11; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6; 12v. 1.5a. twice 17/6.

SMOOTHING CHOKES

150mA 7-10 H, 250 ohms	11/9
100mA, 10 H, 200 ohms	8/9
80mA, 10 H, 350 ohms	5/9
60mA, 10 H, 400 ohms	4/11

CHARGER TRANSFORMERS

All with 200-230-250v. 50 c/s Primaries: 0-9-15v. 11a. 12/9; 0-9-15v. 2a. 14/9; 0-9-15v. 3a. 16/9; 0-9-15v. 5a. 19/9; 0-9-15v. 6a. 23/9; 0-9-15v. 8a. 28/9.

AUTO (Step up/Step down) TRANS.

0-110/120-230/250v. 50-80 watts. 13/9; 250 watts. 49/9; 150 watts. 27/9.

MICROPHONE TRANSFORMERS

120-1 high grade, clamped. 8/9.

FREE TO AMBITIOUS ENGINEERS - THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee
“NO PASS — NO FEE”

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.,
- Electrical Eng.,
- Civil Engineering,
- Radio Engineering,
- Automobile Eng.,
- Aeronautical Eng.,
- Production Eng.,
- Building, Plastics, Draughtsmanship, Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I. Mech. E.
- A.M.I.C.E.
- A.M.I. Prod. E.
- A.M.I.M.I.
- A.I.O.B.

R.S.O. A.M.I.E.R.E. City & Guilds Gen. Cert. of Education Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.S. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

POST COUPON NOW!

Please send me your FREE 156-page “ENGINEERING OPPORTUNITIES” (Write if you prefer not to cut page)

NAME _____

ADDRESS _____

SUBJECT OR EXAM THAT INTERESTS ME _____

SE/21

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

(Dept. SE/21), 29 Wright's Lane, London, W.8

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

BARGAINS GALORE

Transistor ferrite rod aerial with medium and long wave coils with circuit, 7/6.
 Oscillator Coil and set of 3 L.F. transformers for transistor set with circuit, 12/6.
 Tuning Condenser to suit air-spaced with trimmers, 9/-.
 Dttto but min. 10mm. 12/8 the set; two gang Condensers to suit. 8/6 (request sub. min. circuit).
 Midret 3in. F.M. Loudspeaker 3 ohm, 12/6. 80 ohm, 13/6.
 Midret 200 pF + 176 pF two-gang Tuning Condenser with trimmers for transistor set Price 9/-.
 Push-Pull Transformer. Sub-miniature, 8/8. 0005 mfd. Single Tuning Condenser. Solid dielectric tin. spindle for transistor or Crystal set, with spindle tapped 8. BA. 2/6. 46 Sets (Receiver/Transmitter pack set). Unused sets complete except for crystals. Packed with parts and easily rebuildable into other gear. 19/6 each. Post 3/-.
 Mains Transformer. 250-0-250 at 80 mA. 6.3 volts, 5a (normal mains input), 12/6 each. Carriage 2/6.
 Output Transformer. Standard pentode matching type, 8/6 each. 86/- per doz.
 Slide Switch. Sub-miniature but dptd. 2/2 each, 18/- per doz.
 Other gear, 19/6 each. Post 3/-.
 Battery Charger Kit. Comprises 5 amp. transformer, 5 amp. rectifier, metal case and meter to charge 6 or 12 volt. starts up to 5 amps. With variable charge rate, 29/6 each. Post and insurance, 3/6.
T.O.C. or Dubilier Tubular Condensers.
 .5 mf 500 v. 10/- doz.
 .25 mf 500 v. 7/6 doz.
 .15 mf 500 v. 6/- doz.
 .05 mf 500 v. 5/- doz.
 .001 mf 1,000 v. 5/- doz.
 .001 mf 1,000 v. 6/- doz.
 .002 mf 1,000 v. 7/6 doz.
 .005 mf 1,000 v. 8/- doz.
 .02 mf 750 v. 8/6 doz.
 .01 mf 1,000 v. 10/- doz.
 Battery Charger Rectifier—selenium 12.15 v. 5 amp., 9/6.
 Metal Chassis—punched for Mullard 510 Amplifier, complete with inner screening sections and stove enamelled, 12/6 set.
 Filament Transformer, 6.3 v. 14 amps., 6/6.
 Neon Lamp—midjet wire ended. Ideal mains tester, etc., 2/-. Ex Govt., 1/6.
 Philips Trimmers—0.30pF, 1/- ea. 8/- doz.
 Tag Panels. Ideal for constructors, experimental circuits, etc. 3 of each of 12 different types, 5/-.
 Silydlok Panel Mounting Fuses with carrier, 5 amp., 2/- each. 15 amp., 2/6 each.
 Metal Rectifier. 90 v. 60-80 milliamps. Ideal for mains set or instrument or to replace that expensive valve, 4/6.
 Piano Key Type Switches, 3 key type, 3/- 1 key type 2/9, 5 key type 4/6, post and packing 1/-, regardless of number ordered.
 Ozone Ouflet, for removing smells and generally improving any oppressive atmosphere. Kit consists of Phillips ozone lamps and mains unit, only needs box. 19/6 + 3/6 postage and insurance.

Black Light Unit. 125 watt intensity comprises quartz lamp, adjustable lamp holder and 125 watt choke. Only 29/6 + 6/6 carriage and insurance.
 Packard Bell Pre-Amp. Contains a relay push-pull input and output transformers and many useful spares. Less valves 6/6 each + 2/6 post and insurance.
 Fridge Handles, with Yale-type locking mechanism, two keys and striking plate, 3/9 + 2/- post, 2 for 80/-, post free.
 0-1mA Meter made by the American Westinghouse Co., 3 in. diameter, flush mounting scale calibrated in volts. 25/- + 2/- post and insurance.
 Ferrant Fire Bar. 500 watt, 10in., 3/6 each 1/6 post. Three or more post free.
 375 Volt Holder. Best make (Amphenol). 3/- dozen, post 1/6. 3 dozen, post free.
 Precision Wheatstone Bridge, opportunity occurs to build—100k wire wound 15 watt potentiometer price 5/- 1/- postage.
 Cydon Tuner; Tuner. 35 Mhz. with band 1 and band 8 coils. Brand new, 9/6 each post 2/6.


Waterproof Heater Wire
 16 yds. length, 70 watts, self regulating temperature control. 10/- post free.

VERO BOARD

We stock this very useful material in the following sizes: 2 1/2 x 5in., 4/6; 2 1/2 x 3 1/2in., 3/9; 3 1/2 x 6in., 6/6.

Where postage is not definitely stated add 2/- all orders under £3.

7 VALVE 5 WAVE SUPERHET

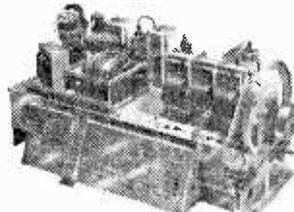

Standard octal types 6K7, 6K8, 6K7, 6Q7, 6V6, 6V4 available, price 20/- the set. **DON'T MISS THIS!** Carriage and insurance, 7/6.

INFRA-RED BINOCULARS

These if fed from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lens for TV camera—light cell etc. (details supplied). The binoculars form part of the army night driving (Tabby) equipment. They are unused and believed to be in good working order, but sold without a guarantee. Price 22.17.6 plus 10/- carriage and insurance. Handbook 2/6.



MAINS POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 5v—9 to 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1-PP3-PP4-P6-PP7-PP9 and others. Kit comprises: mains transformer-rectifier, smoothing and load resistors 5000 and 500 mfd condensers, zener diode and instructions. Real snip at only 14/6 plus 2/6 post.

THIS MONTH'S SNIP

Garrard Auto-Slim Record Changer
 One of the nicest record changers that this famous company make—Automatic selection of records which may be mixed—may also be played manually. Finger tip adjustment of Stylus pressure. Fitted with mono head—but pickup wired for stereo—suitable 900/250 A.C. mains—cabinet space required 14 1/2 x 12 1/2 in. with 4 1/2 in. above and 2 1/2 in. below.
DON'T MISS THIS SPECIAL SNIP only 25.15.0 (post and insurance, 6/6).

EX-ROYAL NAVY SOUND-POWERED TELEPHONE

These require no batteries and will go for long periods without attention. Complete with generator and sounder which gives a high-pitched note easily heard above any other noise. Also fitted with an indicator lamp which in quiet situations can be used instead of the sounder or, where several telephones are used together, will indicate which one is being called. Size 7 1/2 x 9 x 7 1/2 in., wall mounting, designed for ship's use but equally suitable for home, office, warehouse, factory, garage, etc. In good order but sold. Price 29/6 each, plus 6/6 carriage.

750 mW TRANSISTOR AMPLIFIER

4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feed back loop—sensitivity 3 mV/-.
Price 19/6
 Post and insurance 2/6.
 35 ohm Speaker, 12/8 extra.

MAKING AN FM TUNER

Available at Present is a very nice calcium-plated F.M. Tuner chassis with holes punched for coils and other components, also a nicely printed perspex front, calibrated usual F.M. frequencies. Real bargain 6/8 + 2/- or with two-gang tuning condenser 10/- + 2/- postage

Speaker Bargains

12in. High fidelity loudspeaker. High flux permanent magnet type, with either 3 ohm or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 27/8 + 3/6 post and insurance.

Hi-Fi Speakers

Hi-Fi Speakers—E.M.I. Ceramic magnet 12,000 lines, size: 18 x 8in. (roughly equivalent to 1.1in. round speaker). Bass frequency 40-30 c/s. Handles up to 10 watts. Price 35/6 plus 5/- carriage and ins. State whether 15 ohm or 3 ohm.

TRANSISTOR SET CASE

Very modern cream cabinet, size 6 1/2 x 3 x 1 1/2 in. with chrome handle, tuning knob and scale. Price 4/8 plus 1/6 postage.

Building a 'Scope

3in. o-scope tube. American made type No. 3P17, 6.3 v. 0.4 amp. heater electrostatic deflection, brand new and guaranteed with circuit diagram of 'scope, 15/- each. Plus 2/6 post and insurance.

Simmerstat Heater Regulator
 Suitable to control elements, heaters, soldering irons and boiling rings up to 2,500 watts. Complete adjustable, normal price 35/- each, special snip price 12/6, plus 1/6 postage and insurance.

THERMOSTATS

Type 'A' 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knob, quickly adjustable from 30-80°F. 9/6 plus 1/- post. Suitable box for wall mounting, 6/6. P. & P. 1/4.
 Type 'B' 15 amp. This is a 17in. long rod type made by the famous Sylvania Co. Spindle adjusts this from 60-550°F. Internal screw alters the setting so this could be adjustable over 30° to 1,000°F. Suitable for controlling furnaces, over kiln, immersion heater or to make flame-stat or fire alarm. 8/6 plus 2/6 post and insurance.
 Type 'C' is a small porcelain thermostat as fitted to electric blankets etc. 1 1/2 amp. setting adjustable by screw through side, 2/6. P. and P. 6d.
 Type 'D'. We call this the Ice-stat as it cuts in and out at around freezing point, 2-3 amps. Has many uses, one of which would be to heat the loft pipes from freezing, if a length of our heater wire (16 yds. 10/-) is wound around the pipes, 7/6. P. & P. 1/4.
 Type 'E'. This is a standard refrigerator thermostat. Spindle adjustments over normal refrigerator temperatures, 7/6 plus 1/- post.

ELECTRONICS (CROYDON) LTD
 266 LONDON ROAD WEST CROYDON, SURREY
 Post orders to: 43 Silverdale Road, Eastbourne, Sussex

UNIQUE BARGAINS — DEPOT MUST BE CLEARED

SPOT OR FOG LAMP

Made by Lucas. Flat or Pencil beam, 36 watt. Suitable for car, boat, caravan etc. Complete with 6 or 12v. bulb, flex, cables and fixing bolt. Remarkable bargain, 12/6 plus 2/6 post & insurance.



LUCAS 12v IGNITION COIL

Ex-W.D. Unused, guaranteed perfect order. Best most cars, 12/6 plus 1/6 post.



JUMBO VALVE BASES

Ceramic 4 pin for transmitting valves. Price 3/6 each.



SELF ENERGISED TELEPHONES

These require no batteries: in fact they have only to be connected by a pair of wires. They can thus be fitted into existing bell circuits. Results are extremely good and maintenance costs are nothing.

Handsets only 15/- each, post etc. 2/6. Two post free

CATHODE RAY TUBES



	Carr. and Ins.		
VCR 517, 6in.	9/6	8/6	
(replaces VCR 97 new and unissued)			
VCR 139A, 2 1/2in.	27/6	4/6	
VCR 138, 3 1/2in.	27/6	5/6	
VCR 4/1, 3in.	32/6	4/6	
VCR 112, 5in.	27/6	5/6	
CV 99b, 6in.	22/6	5/6	
VCR 97, 6in.	22/6	4/6	
CV 1140, 1 1/2in.	27/6	12/6	
CV 1590, 1 1/2in.	27/6	12/6	

10 WAY CABLE ideal for interconnecting units and for remote switching circuits—each way has a flex copper core capable of carrying 6 amps and insulated to 50v.—the cable is P.V.C. covered overall. Price 1/6 per yd. 10 yds. post free otherwise add 3/6 post.
5 WAY CABLE similar to 10 way 8d. yd., 20 yds. or more post free otherwise add 2/6.
TWIN RUBBER HIGH CURRENT FLEX 110 strands in each core—250v. grade—carry a length of this in your car—if you are ever stuck with a flat battery—you can join up to another car—regular price of this cable is 3/- per yd. our price 17/6 for 10 yds. post paid.

BAKELITE WALL SWITCHES Normal household type for lighting etc. 9/- doz. one way or 10/- 2 way—36 or over post free otherwise add 2/6.
A.C. METER, WALL or PANEL MOUNTING Volt meter 6in. dia. in metal box for flush mounting—install one in your workshop and you will always know how the mains are. 35/- each, 3/6 post and ins.

BLOWER MOTOR If you are thinking of making a heater or cooler for your car or equipment, this could be the basis—intended for cooling aircraft equipment, runs OK off 12 volt. Price 12/6 plus 2/6 post and ins.
ELECTRICAL REV COUNTER This is a dynamo with flex drive shaft, simply take output to a volt meter which you can calibrate in R.P.M.—beautiful instrument must have cost a fortune, 10/6 each, post 2/6.


SPOT OR FOG LAMP Flat or Pencil beam, 36 watt. Suitable for car, boat, caravan etc. Complete with 6 or 12v. bulb, flex cables and fixing bolts, remarkable bargain 12/6 plus 2/6 post and insurance.

Where postage is not definitely stated add 2/- all orders under £3.

TELEPHONE REPEATER No. 1 MARK 1


This equipment is for amplifying telephone signals in both directions of traffic and also to remedy line distortion of speech. It is intended for use with two wire or four wire circuits, has four amplifiers and is in fact two quite independent repeaters mounted on the same panel and having a common power supply. The power supply may be operated from a 12-volt car battery or from standard A.C. mains. The units are absolutely new in original packing complete with spares and instructional manual. Price £7.10.0 each. Post and packing 12/6.

KLYSTRON RECEIVER

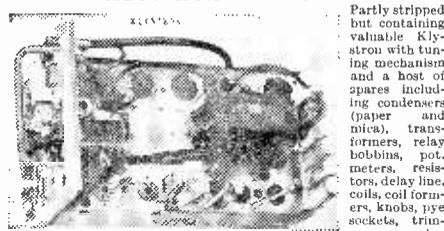


Partly stripped but containing valuable Klystron with tuning mechanism and a host of spares including condensers (paper and mica), transformers, relay bobbins, pot. resistors, delay line, coils, coil formers, knobs, type sockets, trimmers, valve holders, a very useful chassis and case size approx. 15 x 9 x 7 1/2 in. and hundreds of other useful sundries. Price only 9/6 plus 7/6 carriage and packing.

BUILDING AN AMPLIFIER

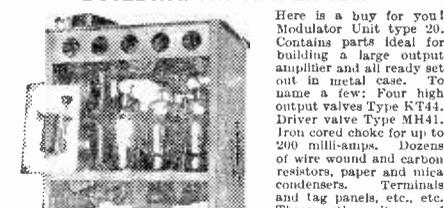

Here is a buy for you! Modulator Unit type 20. Contains parts ideal for building a large output amplifier and all ready set out in metal case. To name a few: Four high output valves Type KT44. Driver valve Type 6H4. Iron cored choke for up to 200 milli-amps. Dozens of wire wound and carbon resistors, paper and mica condensers. Terminals and tag panels, etc., etc. Three other items of interest to everybody and well worth the price asked for the unit are: 1. Transformer Reference 10K/143. This can act as auto-transformer to convert 230 to 110 or 230 to 460, and also as a filament transformer 230 to 6.3 or 230 to 12.0 volts. 2. Miniature Circuit Breaker. For breaking 10 amps A.C. reset by pushing knob. 3. Steel Case. With heavy gauge chassis, all ready cut out and fitted valve holders, etc. Price for complete unit is 12/6. Carriage 7/6.

UNITS FOR CONTROLLED AUTOMATIC ROTATION

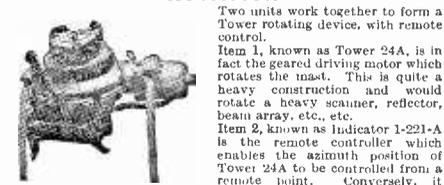

Two units work together to form a Tower rotating device, with remote control.
 Item 1, known as Tower 24A, is in fact the geared driving motor which rotates the mast. This is quite a heavy construction and would rotate a heavy scanner, reflector, beam array, etc., etc.
 Item 2, known as Indicator 1-221-A is the remote controller which enables the azimuth position of Tower 24A to be controlled from a remote point. Conversely, it enables the azimuth position of the Indicator to be controlled from the tower. Both the Tower and the Indicator contain selytn transmitter/receivers and it is these that provide the impulses which cause the aerial to rotate backwards or forwards. The equipment intended for 117 volt A.C. mains but will operate from our mains if connected through step down transformer of 1 kW rating. Prices: 1-221-A, £25. TR24A, £25. special discount of £5 for cash with order or C.O.D. if both units purchased together.


TETRODE TYPE VT 31 TRANSMITTING VALVE

This is a high-powered air-cooled tetrode, specification of which is as follows: Heater volts 11.25, heater current 8 amp, maximum anode voltage 5 kV, anode dissipation 250 watts, size approximately 1 1/2 in. long and 6 1/2 in. across the bulb. Limited quantity only at £1 and 4/6 P/T each, still in original packing.

INSTRUMENT COMPANY

43 SILVERDALE ROAD, EASTBOURNE
 CASH WITH ORDER
 Mail Order only from this address—goods may be seen by appointment in Oxfordshire.

CHARGING SWITCHBOARDS

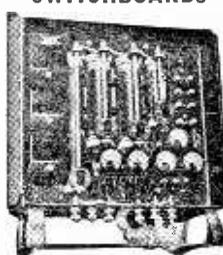


Type A, 550 w. 18 v.—contains three reverse current relays, one voltmeter rated 25 v. f.s.d. one main ammeter rate 40 amps f.s.d., one secondary ammeter rated 16 amps f.s.d., and two secondary meters rated 20 amps f.s.d., one 2 ohm variable resistor, one 11 ohm variable resistor, one main ammeter rated at 40 amps f.s.d., four secondary meters rated at 20 amps f.s.d., and one voltmeter rated at 50 volts, and two reverse current relays. Complete in metal case—size approximately 2 1/2 in. x 2 1/2 in. Price £2.15.0. Carr. & Ins. 15/-.

Type B, 1260 w. 60 v. 12 amps—contains one 14 ohm variable resistor and four 1 ohm variable resistors, one main ammeter rated at 40 amps f.s.d., two secondary meters rated at 20 amps f.s.d., and one voltmeter rated at 50 volts, and two reverse current relays. Complete in metal case—size approximately 2 1/2 in. x 2 1/2 in. Price £4.15.0. Carr. 15/-.



CONTACTOR

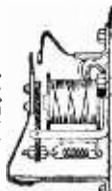For breaking 25 amps, coil voltage is 24 v. D.C., but with a re-wind or a small rectifier these will close off A.C. mains. Very heavy duty contacts. Enclosed in bakelite case. Price 2/6 each, 24/- doz.



INDICATOR LAMP

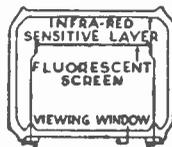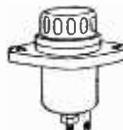Fitted Perspex top. Takes standard screw-in flash light bulb. Price 18/- doz. Singular thing but dush, 12/- doz.




SNIPERSCOPE

Famous wartime "cats eye" used for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. It follows that as light from an ordinary lamp is rich in infra-red these cells will work burglar alarms, counting circuits, smoke detectors and the hundred and one other devices as will the simpler type of photo cell. Here then is a golden opportunity for some interesting experiments, price 5/- each. Post 2/-. Data will be supplied with cells if requested.

SLIDER RESISTORS

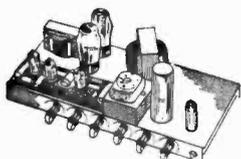Heavy Duty Type. Size 7 x 1 1/2 in. 11 ohms 4.5 amp, 22/-, Size 9 x 1 1/2 in. 1.2 ohms 16 amp, 15/-, Size 1 1/2 x 1 1/2 in. 3 ohms 10 amp, 15/-, 1 ohm 25 amp, 15/-, A ohm 100 amp, 10/- plus post.






6 VALVE 15 WATT PUSH-PULL AMPLIFIER. 15 v. 7 x 1 1/4 in. A.C. Mains 200-250 volts. 4 inputs with controls for same and bass and treble lift controls. Tapped for 3 and 15 ohm speakers. Extra H.T. and L.T. for F.M. Tuner supplies etc. Built and tested. 7 gns. P. & P. 12/6.




FIRST QUALITY PVC TAPE

P. & P. on each 1/8. 4 or more post free.

5 1/2 in.	Std.	850ft.	9/-
7 in.	Std.	1200ft.	11/6
3 in.	L.P.	240ft.	4/-
5 1/2 in.	L.P.	1200ft.	11/6
7 in.	L.P.	1300ft.	13/6
6 in.	D.P.	850ft.	10/6
3 in.	T.P.	600ft.	8/-
6 in.	T.P.	1800ft.	20/6
7 in.	T.P.	8600ft.	37/6

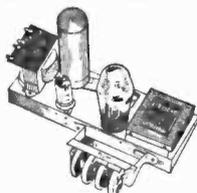


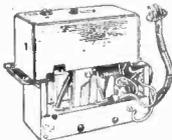3 TO 4 WATT AMPLIFIER KIT comprising chassis 8 1/2 x 2 1/4 x 1 in. Double wound mains transformer, output transformer, volume and tone controls, resistors, condensers, etc. Valves 6V6, ECC81 and metal rectifier. Circuit 1/10 free with kit. 29/6 plus 4/- P. & P.



CHANNEL TUNER I.P. 16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCF80 and PCC84 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxi, etc. Brand new by famous maker. 10/- P. & P. 3/6.

RADIO & T.V. famous for Components

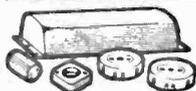

40W FLUORESCENT LIGHT KIT incorporating G.E.C. Choke size 8 1/2 x 1 1/2 x 1 1/2, 2 bi-pin holders, starter and starter holder. 11/6. P. & P. 3/6. Similar to above: 80W Fluorescent Light Kit incorporating G.E.C. Choke size 11 1/2 x 1 1/2 x 1 1/2, 2 bi-pin holders, starter and starter holder. 17/6. P. & P. 4/6.

SILICON RECTIFIERS, 250 v. P.I.V. 750 mA. Six for 7/6 post paid




SIGNAL GENERATORS: Cash £7.5.0. P. & P. 6/6. Coverage 100 Kc/s to 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Case 10 x 6 1/2 x 5 1/2 in. Three miniature valves and Metal Rectifier. A.C. mains 200/250v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output. Magic eye as output indicator. Accuracy plus or minus 2 per cent.



8-WATT PUSH-PULL 5 VALVE AMPLIFIER. A.C. mains 200-250v. Size 10 1/2 x 6 1/2 x 2 1/4 in. 5 valves. For use with all makes and types of pick-ups and mikes. Negative feed back. Two input, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 Kc/s. 2dB down to 20 Kc/s. Output 8 watts at 5 per cent total distortion. Note level 4dB down all thru. Output transformer tapped for 3 and 15 ohms speech coils. For use with 801 or L.P. records, musical instruments such as guitars, etc. Suitable for small halls. 23.19.6. P. & P. 7/- Crystal mike to suit. 15/- P. & P. 2/- 8in. P.M. Speaker to suit. 12/6. P. & P. 2/-

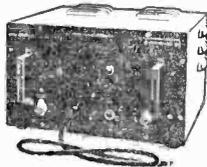
FIXED FREQUENCY SIGNAL GENERATOR. Crystal control in metal case, size 10 x 6 x 6 in. Incorporating two FC13 valves, mains transformer, metal rectifier choke, indicator, lamp, crystal and numerous components. Modulated and unmodulated output socket. Originally used for I.T.V. frequencies. Brand new, 39/6, plus 6/- P. & P. A.C. mains 200-250 volts.




RINGO BURGLAR ALARM SYSTEM. A.C. mains, 200/240 volt. Fire salvage slightly tarnished. List price 7 gns. Our price, complete with double gong bell five micro switches and full instructions. 49/6. P. & P. 4/-




POCKET MULTI-METER. Size 3 1/2 x 2 1/4 x 1 1/4 in. Meter size 2 1/4 x 1 1/4 in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. A.C. and D.C. volts. 0-15, 0-150, 0-1,000. D.C. current 0-150 mA. Resistance 0-100KΩ. Complete with test leads, battery and full instructions. 39/6, P. & P. 2/6. FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

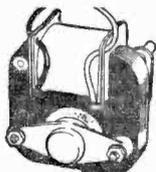

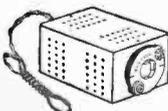A.C. MAINS MOTOR. Can be used for a variety of purposes, silent running satisfactory in every way. 230/250 v. A.C. 9/6, P. & P. 2/-.



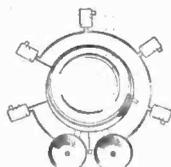POWER SUPPLY KIT in metal case, size 3 1/2 x 2 1/4 x 2 in. incorporating mains transformer, rectifier and condensers. 230/250v. A.C. mains. Output: 9v 100mA. Price 10/6 plus 2/6 P. & P.



RINGO BURGLAR ALARM SYSTEM. A.C. mains, 200/240 volt. Fire salvage slightly tarnished. List price 7 gns. Our price, complete with double gong bell five micro switches and full instructions. 49/6. P. & P. 4/-

RADIO & T.V. COMPONENTS (ACTON) LTD.

21B High St., Acton, London, W.3.

All enquiries S.A.E. Goods not despatched outside U.K. Shop hours 9 a.m.—6 p.m. Early closing Wednesday. Terms: Cash with order

SPECIAL OFFER! FROM R. & T.V. LTD.

Elegant Seven

COMBINED PORTABLE & CAR RADIO

The Radio with the STAR features
4in. SPEAKER


- ★ 7-transistor superhet. Output 350mW.
- ★ Two-tone grey wooden cabinet, fitted handle with silver coloured fittings. Size 12¼ x 8½ x 3½ in.
- ★ Horizontal tuning scale, size 11¼ x 2⅝ in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. 470 Kc/s.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket.
- ★ Full after-sale service.

ONLY
£4.4.0

Plus 5/6 P. & P Parts list & circuit diagram 2/6. FREE with parts.

SPECIAL OFFER—POWER SUPPLY KIT to purchasers of "Elegant Seven" parts, incorporating mains transformer etc. A.C. mains 200-250v. Output 9v, 100mA, 7/6.

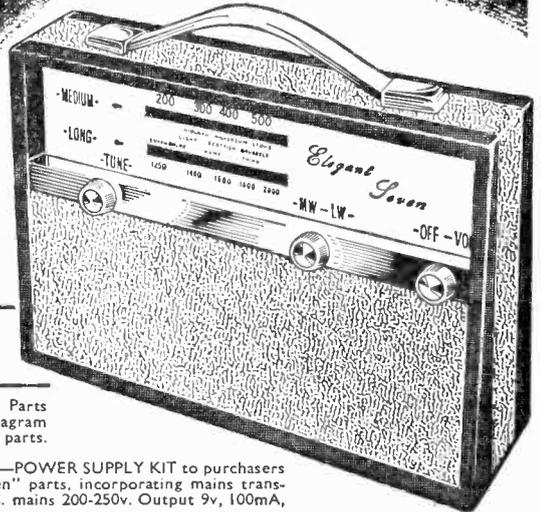Goods not despatched outside U.K. All enquiries S.A.E. Terms C.W.O.



RADIO & TV COMPONENTS (ACTON) LTD 21C High St., Acton, London W3

Open 9 a.m.—6 p.m. including Sats. Early closing Wed.

**SOLON
GETS THINGS
TOGETHER
FOR
GOOD**



SOLON ELECTRIC SOLDERING IRONS are made by AEI. Seven models suitable for all soldering jobs. The 15 and 25 watt for radio work, the 65 watt for heavier duties. All parts are replaceable. Prices from 24/8.

SOLON
TRADE MARK

From your radio or electrical supplier.

BARGAINS FROM BROADWAY ELECTRONICS

- GARRARD A.T.6 Hi-Fi Autochanger G.C.8 mono cartridge—£9.19.6. post free.
- GARRARD AUTOSLIM 4 speed changer—£6.10.0. post free.
- 12in. ALTHAM SPEAKER with built in tweeter 3 ohm or 15 ohm 7,000 Gauss Magnet. Only 28/6. postage 3/6.
- HAYDON CABINET (17 x 15 x 9in.) designed to take a 12in. Heavy Duty Speaker. 50/-, postage 7/6.
- The Famous B.M.3 XTAL MICROPHONE with neck lanyard 30/-, table stand for above 9/6 extra. Xtal insert 7/3.
- GUITAR PICK-UP complete with clip and screened lead—12/6.
- 3-WAY PUSH BUTTON UNITS. Each button operates a 4-pole 2-way switch—4/6.
- BARGAINS IN TRANSISTORS. Mullard RF Packs OC44 two OC45. 12/6; AF Packs OC81D two OC81. 8/6; OC44. 3/6; OC45. 3/6; OC71. 2/6; OC72. 3/-; OA81 diode 2/3; OC170. 6/6; AF 117. 6/6; ORP12. light cell. 7/6; OC29. 12/6; OC35. 12/6.
- TRANSISTOR ELECTROLYTICS 1, 2, 4, 5, 8, 10, 16, 32, 50 100. Mid. all at 15 volts—1/3 each.
- MICHAEL TELESCOPIC TV AERIAL 23in. extends to 45in.. Fitted with coax plug. will suit any set. Only 7/6.
- CARTRIDGES. Acos 67-IG Low Output, 67-2G Medium Output GP59-5 High Output. Garrard GC2 or GC8 all with mounting bracket 15/-.
- Ronette Stereo with mounting bracket, 25/-.
- EARPIECES with cord and 3.5mm plug. 8 ohm magnetic 3/-; 250 ohm. 4/-; 180 ohm magnetic with clip 6/6; Xtal. 4/-; 3.5mm plugs with nice long shank complete with jack. 3/-.
- 3.5mm plugs with nice long shank complete with jack SCREENED. 4/-.
- TOGGLE SWITCHES. Single pole with on/off plate. 2/6.
- NEON PANEL LIGHTS. 240v. A.C. Arcoelectric, 2/6.

TERMS: C.W.O. OR C.O.D.

BROADWAY ELECTRONICS 92 MITCHAM ROAD, TOOTING, S.W.17

Phone: BALham 3984
(four minutes from Tooting Broadway Underground Station)



TWO-WAY RADIOS

A compact V.H.F. Transceiver that can be held in the hand. Size approx. 12 x 9 1/2 x 2 1/2 in. Range up to 3 miles under favourable conditions. Utilises 3 miniature valves and self-contained standard batteries. Easy to operate, economical to run. Ideal for authorised fleet or mobile operation. British manufacture. Limited number in stock. Price 12 gns. per pair. post free.

CRYSTAL SET

A wonderful educational set for all children. Provides hours of amusement while following the easy step by step instructions. It is powered entirely by wireless waves eliminating the expense of batteries. No soldering required. Receives all main stations. Price 19/11. P. & P. 2/6.



19 SET TRANS/REC MAINS POWER PACK

Operate your 19 set receiver straight off the mains. Ready built power unit complete with modification and fitting instructions. Price 49/6. P. & P. 3/6. Please state Mk. II or III.

TRANCEIVER No. 38 A.F.V.

This lightweight Trans/Rec. has a transmitting range of 3 to 5 miles. Frequency coverage 7.3 to 16 mcs. Operates from 12 and 120 volt supplies. Large clearly numbered tuning control with tuning lock. Price 24 per pair post free.

Handy Power Pack. Housed in compact metal case. 200/250V mains input. Output 250V D.C. 60mA fully smoothed. 6.3V at 2 amps. Can be used for powering almost any preamp or radio tuner. Price 39/6. P. & P. 2/6.


Morse Keys. Morse Key Assembly. Key with case, cover and terminals. Complete with lead. 6/11. P. & P. 2/-, 2 Morse Keys for 12/6 post free. M.A.T. Transistors. M.A.T. 100. 7/8; M.A.T. 120 7/9; M.A.T. 121. 8/6. Ferrite slab aerials suitable for Transistor sets. 3/-, P. & P. 6d. Operator's Unit. Huge purchase enables us to offer at give-away price this unit containing standard jack socket, 250mF/d electrolytic condenser, 4-way telephone socket, midge selenium rectifier, etc. Price 3/6. P. & P. 9d. Loud Alarm Transistors. One OC81 driver. Two OC81 output stage matched pair. Price 6/11 the set. P. & P. 1/-.

American Signal Generator V.H.F. Model - a well made instrument with a built-in crystal oscillator. Exceptionally fine slow motion tuning with easily read scale. Stepped output and adjustable amplitude. Ideal for 2 metres and V.H.F. calibration. Price 49/6. P. & P. 5/-.

THE Goldemair "THIRTY" HI-FI AMPLIFIER

A high quality 30-watt amplifier developed for use in large halls and clubs, etc. Ideal for bass lead or rhythm guitars, schools, dance halls, theatres and public address. Suitable for any type of mike or pick-up.

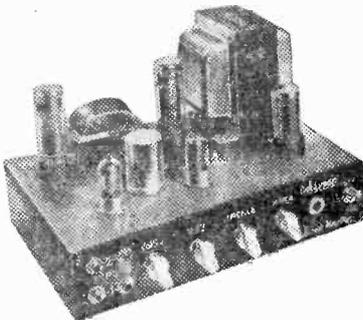Valve line-up: two EF86; one ECC83; one GZ34 two EL34. Four separate inputs are provided with two volume controls. Bass and Treble controls are incorporated. Amplifier operates on standard 50 c/s mains. 3 ohm and 16 ohm speakers may be used. Perforated cover with carrying handles can be provided if required.



go Goldemair

Customers are invited to see and hear this amplifier at our shop premises in Lambert's Arcade. Send S.A.E. for illustrated leaflet. Or deposit of £1.16.0. and twelve monthly payments of £1.9.2. Total H.P. price £19.6.0. Carr. 15s. to be sent with order.



TWICE THE QUALITY HALF THE PRICE

TANK AERIALS

Fully interlocking copper sections one foot in length. Will make ideal dipoles, car or scooter aerials. Price, six sections, complete with canvas carrying case, 3/6. P. & P. 1/6. Additional sections 6d. each. Please include sufficient postage.

19 set Instruction Handbook 3/8 each, P. & P. 6d. 1155 Instruction Handbook 3/8 each, P. & P. 6d. H.R.O. Instruction Handbook 3/8 each, P. & P. 6d. Frequency Meter, BC 221 Instruction Handbook 3/8 each, P. & P. 6d. 46 Walkie Talkie Set Circuit and Notes 3/8 each, P. & P. 6d.

B.F. Unit 24 Circuit Diagram and Details. Price 1/6, P. & P. 3d.

B.F. Unit 25 Circuit Diagram and Details. Price 1/6, P. & P. 3d.

B.F. Unit 26 Circuit Diagram and Details. Price 1/6, P. & P. 3d.

Receiver R1855 Circuit Diagram and Details. Price 1/6, P. & P. 3d.

Receiver R1224A Circuit Diagram and Details. Price 1/6, P. & P. 3d.

R1116/A Circuit Diagram and Details. Price 1/9, P. & P. 3d.


Wave Meter Class D Handbook, Mk. I, II and III. Price 3/6. P. & P. 6d.

TWO-WAY SOUND POWERED TELEPHONE

As used by the Armed Forces. These sound powered earpieces will work up to a distance of 1 mile without the use of batteries. Beautifully made. Ideal for use in the house, office or garden. Complete with connecting cable 17/6. P. & P. 2/6.

HEAVY DUTY LOUDSPEAKERS


in Robust Resine Covered Cabinets.

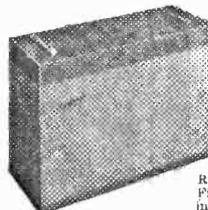

Price 27 gns. or H.P. terms available. Deposit £21.7.0 and 12 monthly payments of £2.6.9. Total H.P. price £20.18.0. Carriage 15/- to be sent with order.

(a) Suitable for base and lead guitars. Incorporating two 12in. high flux 25 watt 15ohm loudspeakers, providing excellent frequency response. Cabinet size approx. 28 x 20 x 10 in. Rating 50 watts. Fitted with carrying handles.

VEHICLE RADIO-TELEPHONE

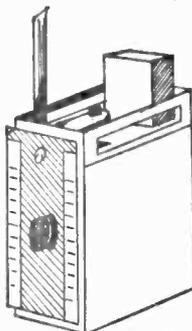

Originally used by the Armed forces for field communication. This compact little unit can be powered by a car battery, and two 90V or 90V H.T. batteries. Communication is possible up to a distance of 3 miles in favourable terrain, and on testing the receiver we were able to receive many Continental and Maritime stations. Battery drain is less than 1 of an amp. Output stage de-commissioned to conform with regulations. Full wiring instructions provided. Price each, carriage free, 2 for £10, carr. free 5 Gns.

POSTAGE RATES APPLY U.K. ONLY. S.A.E. WITH ALL ENQUIRIES. NEW WALK ROUND STORE OPEN IN LAMBERT'S ARCADE, LOWER BRIGGATE, LEEDS 1. NEXT TO HALFORD'S CYCLE SHOP. OPEN ALL DAY SATURDAY. ALL MAIL ORDERS TO OUR BRIGGATE HOUSE ADDRESS.

TERMS:
CASH WITH ORDER
5/- EXTRA ON C.O.D.
ORDERS
No C.O.D. under 30/-.



SEND 1/- FOR LISTS
TRADE SUPPLIED
ORDERS FROM
ABROAD WELCOMED

SONA ELECTRONIC CO. (Dept. PW17) BRIGGATE HSE, 13 ALBION PL, LEEDS

ADVERTISEMENT

AN IMPORTANT ANNOUNCEMENT**DENCO (CLACTON) LIMITED, OLD ROAD,
CLACTON-ON-SEA, ESSEX**

15 YEARS AGO (1950) our Octal Plug In Coils Blue-Yellow-Red-White retailed at 4s. 1d. each and the Green at 5s. 1d. Today they are the same price 4s. 1d. each and the Green even lower at 4s. 9d. Anyone of the thousands of home constructors and industrial users will confirm the great technical and mechanical improvements that have also been made on these coils.

15 YEARS AGO (1950) our IFT.8 Transformers 465 kc/s and 1.6 Mc/s sold at 9s. 9d. each. Today these are known as IFT.11 465 kc/s and 1.6 Mc/s selling at one third less 6s. 6d. each, they are more robust, more accurate and spot-on aligned. And so we can go on and on with very many static priced improved products.

15 YEARS AGO WE sold a simple Spot Frequency 465 kc/s and 1.6 Mc/s Alignment Oscillator known as the DAO.1 at £2.7.6. Today we sell an almost fantastic improvement known as the MTO.1. Modulated Test Oscillator with two ranges continuously variable through the 170-475 kc/s and 550-1,600 kc/s frequencies, at least three times the value but at the low price of £3.17.6.

DURING THIS 15 YEARS wages have more than trebled, Local Council Rates have multiplied five times, Nationalised "Services" Gas Electricity Transport, Road, Rail and Post, and General Taxation have gone up "Sky High".

This is the sort of thing our Chancellor of the Exchequer, is asking for and an achievement on which we are justifiably proud, brought about on your behalf by our constant watch on improved materials available, improved designs and modern tooling methods.

Our General Catalogue which fully illustrates our range of productions is priced at 1s. 6d. inclusive of postage, and in the interest of continued economy and price stability we shall appreciate a stamped addressed envelope with all requests for assistance or information on particular components.

Arthur W. Allwright.
Managing Director

LOUDSPEAKERS



We supply a complete range of Goodmans, Wharfedale, Stentorian, TUL Speaker Units and complete systems. A comprehensive leaflet is available on request this covers technical specifications and prices of

- nearly 50 types including—
- Celestion CX1512 (illus.) £11.10.0
- Celestion Model CX2012, £16.10.0
- Stentorian HF312 5 watts £3.16.0
- Stentorian HF1012 10 watts £4.16.0
- Goodmans Axiote 8, 6 watts £3.10.11
- Goodmans Axiom 10, 10 watts £6.5.11
- Goodmans Axiom 201, 15 watts £10.17.4
- Wharfedale Super 8/RS/12/DD 5 watts £6.14.2
- Wharfedale Golden RS/DD 8 watts £7.17.5
- Wharfedale RS/12/DD 15 watts £11.10.0
- Guitar Speakers include:—
- Wharfedale W12EG 15 watts £10.10.0
- Wharfedale W15EG 20 watts £17.10.0
- Goodmans Audiom 51B 15 watts £9.2.3
- Goodmans Axiom 61B, 20 watts £14.7.8
- Carr. and Ins. extra

THE TRAVLER Mk. II CAR RADIO

★MEDIUM AND LONG WAVES

★12 VOLT POSITIVE EARTH

★Push Button Wave Change

★SIZE 7 x 2 x 7 inches

★TRANSISTORISED




ONLY **9 1/2 gns.**
P & P 5/-

Ready built complete with 7 x 4in. speaker fitted to baffle, fixing brackets, filter unit, all nuts and bolts and fitting instructions.

Optional Extras: 3-section chromium plated weatherproof telescopic aerials. Type 1, 17in./44in. 19/6. Type 2, 2in./43in. 29/6. both plus P. & P. 2/6 if purchased separately.

The "HIGHWAYMAN" Car radio to build yourself. Similar in appearance to above but with on/off push button switch. Complete set of parts only £7.19.6. P. & P. 5/-.

TUNER UNITS

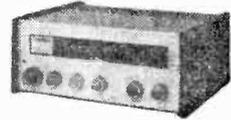

ARMSTRONG

- Mono/Tuner Amp. Model 127M £26.10.0
- Stereo/Tuner Amp. 127.. £27.10.0
- AM/FM Tuner 223 .. £29.15.0
- FM Tuner 224 £22.10.0
- Carr. and Ins. 7/6

STERN FIDELITY Mk. II VHF/FM Built and tested. £14.5.0
Carr. and Ins. 5/-.

JASON

- FMT1 FM Tuner, Kit of Parts £6.15.0.
- FMT2 FM Tuner, Kit of Parts £10.12.6
- FMT3 FM Tuner for Fringe areas. Kit of Parts .. £12.5.0
- FMT4 FM Tuner .. £20.0.4
- JTV2/FM/TV Sound. Kit of Parts .. £15.15.0
- Carr. and Ins. on above 5/- each.

TRIPLETONE

- FM Tuner unpowered .. £13.19.6
- FM Tuner Self-powered .. £15.14.6
- Carr. and Ins. 5/- each
- Descriptive leaflets free on request. Please state model required.

STERN

GREAT BRITAIN'S GREATEST

STERN-CLYNE HI-FI EQUIPMENT
Ready built or Kit of Parts

	Complete Kit of parts	Ready built and tested	Carr. and Ins.	Instruction book available separately
Stern Mono-Gram Amplifier 3 watts	£4 10 0	£6 0 0	3/8	2/6
Mullard 2 valve Audio Pre-Amplifier	£6 0 0	£9 10 0	5/-	2/-
Mullard 3 valve Audio Pre-Amplifier	£10 0 0	£13 13 0	5/-	3/6
Mullard "3-8" Amplifier with Tone Control Unit 33/RC 3 watts	£8 8 0	£11 10 0	6/6	2/-
Mullard "5-10" Main Amplifier Model 610/M. 10 watts	£10 0 0	£13 10 0	6/6	2/-
Mullard "5-10" Amplifier with Tone Control Unit, 10 watts ..	£12 0 0	£16 0 0	7/6	2/-
Stern Twin Three Stereo Amplifier, 3 watts per Channel ..	—	£9 0 0	5/-	—
Stern Twin Three Stereo Amplifier in Portable Case with Two Speakers and Leads	—	£16 10 0	10/-	—
Mullard "10+10" Stereo Amplifier, 10 watts per Channel ..	£16 0 0	£20 0 0	8/6	3/-
Mullard "10+10" Stereo Amplifier with Passive Control Unit	£20 0 0	£24 0 0	10/-	3/-
Mullard Dual Channel Pre-Amplifier	£12 10 0	£15 0 0	7/6	3/-
The above two items purchased together	£27 0 0	£34 0 0	15/-	—
Mullard 4-channel Electronic Mixer Unit Model 2H for 2 Mics. Radio and Gram.	£8 8 0	—	5/-	2/6
Mullard 4-channel Electronic Mixer Unit Model LL	£10 5 0	—	5/-	2/6
HF/TR3 Tape Amplifier with Power Unit	£13 13 0	£19 0 0	7/6	3/-
Type "C" Tape Pre-Amplifier with Power Unit	£14 0 0	£19 10 0	7/6	3/6
STP-1 Tape Pre-amplifier with Power Unit, Mono and Stereo	£22 0 0	£28 0 0	3/6	5/-
CR3/S Tape Recorder with Studio Desk	£33 8 0	—	15/-	3/-

INDIVIDUAL DESCRIPTIVE LEAFLETS GIVING TECHNICAL SPECIFICATIONS, DIMENSIONS, PRICES, TERMS ETC., FREE ON REQUEST

RECORD PLAYERS



- Garrard BRP10 Single Player £5.9.1.
- BSR UA25 4-speed changer £5.19.6
- Garrard Autolinn changer .. £10.10.0
- Garrard AT6 changer .. £10.19.6
- BSR Super Slim changer .. £9.19.6
- Garrard AT5 LM Auto-changer (3000LM) .. £11.11.11
- Philips AG1018 Stereo/Mono Record Player .. £13.13.0
- Carriage and Ins. 5/- on above.
- Garrard 4HF Single Player £16.17.6.
- Goldring Lenco Model 88 Transcription Turntable .. £18.18.5
- Garrard Laboratory Type "A" Autochanger .. £19.15.0
- Garrard 301 Strobe Transcription Turntable .. £22.0.6
- Goldring Lenco GL55 with 580 Cartridge .. £21.19.0
- Goldring Lenco GL70 less Pick-up Head .. £27.9.4
- Carr. and Ins. 7/6 on above.
- Descriptive leaflet including prices with alternative cartridges, dimensions, terms etc. free on request.

MICROPHONES

Extensive range available. Send S.A.E. for illustrated brochure.

ANOTHER STERN-CLYNE BARGAIN OFFER!!

SAVE £10!

STEREO AM/FM RADIOGRAM CHASSIS *by famous maker*

List Price **OUR** Carr. **PRICE** **19** Gns. **7/6**

BRAND NEW WITH FULL GUARANTEE

Full Med um, Long and VHF Coverage.

3 watts per channel output, 3 ohm output impedance, internal aerial for A.M. Provision for Multiplex adaptor. Pick up and Tape input sockets. A.C. Mains 200/250 volts.



FREE!!

Two 10 x 6in. matching speakers supplied free if the following items are purchased together. CHASSIS 19 GNS. and GARRARD Autolim with stereo plug in head £8.7.0. (or any unit above £8.7.0.) Carr. 15/- extra.



NEW LOW PRICE COMMUNICATION RECEIVERS

HE 40, 550 Kc/s-30 Mc/s in 4 bands. £19.19.9.
Carriage 10/-.

HE 30, 550 Kc/s-30 Mc/s in 4 bands. £24.13.0.
Carriage Paid.

KT 320, Specification as HE 30 but offered as complete kit of parts. £26.5.0. Carriage Paid.

HA 63, 550 Kc/s-31 Mc/s in 4 bands. £25.4.0.
Carriage Paid.


Starlight 90 Watt Transmitter
Band coverage 80 - 40 - 20 - 15 and 10 Meters.
£30.9.0. Carr. 15/- (H.P. Terms available.)

Send S.A.E. for fully descriptive brochure.

CLYNE

ELECTRONIC HOBBIES ORGANISATION


DOUBLE FEATURE PRE-AMPLIFIER

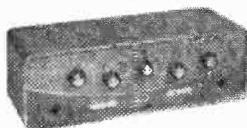

Inputs for microphones, crystal or magnetic pick-ups, tuner unit and in addition offers full facilities for tape recording and high fidelity replay. This unique feature means that should you wish to include tape in your hi-fi system at a later date all that is required is a suitable tape deck. Push-button switching for 3 tape speeds equalised.

KIT OF PARTS 11 GNS.
BUILT AND TESTED 18 GNS. (Carr. and Ins. 5/-)

11L10 POWER AMPLIFIER

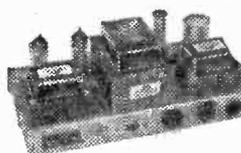

Incorporates the latest diode/pentode ECL86 valves in push-pull PARTRIDGE ultra linear output transformer, PARTRIDGE mains transformer and smoothing choke. 10 watts power output, surplus power output, surplus power available for tuner.

KIT OF PARTS 91 GNS.
BUILT AND TESTED 12 GNS.
(Carr. and Ins. 7/6)

Prices if both units purchased together:
KIT OF PARTS 181 GNS.
BUILT AND TESTED 29 GNS. (Carr. & Ins. 10/-)

AMERICAN RECORDING TAPE

5in.	600ft.	Standard Acetate	8/6
5in.	900ft.	Long Play Acetate	10/-
5in.	1,200ft.	Long Play Acetate	12/6
3in.	600ft.	Double Play Mylar	11/6
7in.	1,200ft.	Standard Play Mylar	12/6
5in.	1,200ft.	Double Play Mylar	15/-
7in.	1,800ft.	Long Play Mylar	20/-
5in.	1,800ft.	Double Play Mylar	22/6
7in.	2,400ft.	Double Play Mylar	25/-

Postage and Packing 1/- per Reel. Extra 4 or more Reels POST FREE.

FULLY AUTOMATIC TAPE SPLICER

14/6. P. & P. 1/6.

PLASTIC TAPE SPOOLS 2 1/2in., 1/-; 3in., 1/6; 4in., 2/-; 5in., 2/-; 5 1/2in., 2/3; 6in., 2/6.

PLASTIC SPOOL CONTAINERS. For spool sizes 5in., 1/6; 5 1/2in., 2/-; 7in., 2/3. Any single item plus 6d. P. & P. Orders over £1 post free.

We carry fully comprehensive stocks of Tape Recorders, Decks and Accessories at all Branches or order with confidence by mail.

VISIT YOUR NEAREST STERN-CLYNE ELECTRONICS CENTRE

LONDON

18 Tottenham Court Road, W.1. MUSEum 5929/0095. Half Day Saturday.
23 Tottenham Court Road, W.1. MUSEum 3451/2. Half Day Thursday.
309 Edgware Road W.2. PADddington 6963. Half Day Thursday.
109 Fleet Street, E.C.4. FLEEt Street 8812/3. Half Day Saturday.
162 Holloway Road, N.7. NORTH 7941. Half Day Thursday.
9 Camberwell Church Street, S.E.5. RODNEY 9876. Half Day Thursday.

CROYDON

12 Sunnol House, George Street, MUNICIPAL 3250. Half Day Wednesday.

BRISTOL

26 Merchant Street, Bristol 1, Bristol 20261. Open 6 days a week.

LIVERPOOL

52 Lord Street, Royal 7450. Open 6 days a week.

MANCHESTER

20/22 Withy Grove, Manchester 4, BLAckfriars 5376/5246.

SHEFFIELD

125 The Moor, Sheffield, Sheffield 29993. Half Day Thursday.

MAIL ORDERS AND ENQUIRIES TO:

Dept. P.W. 3/5 Eden Grove, Holloway, London N.7. NORTH 8161/3.

LASKY'S RADIO

Offer the Finest Value and HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, your may return it as received within 7 days when the sum paid will be refunded less postage.



A simple additional circuit provides coverage of the 1100/1950 M. band (including 1500 M. Light programme). All components and detailed construction data. **Only 10/- extra** Post Free. This conversion is suitable for both models that have already been constructed.

Data for Receiver 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries 3/4 extra. All Components Available Separately.

THE "SKYROVER" RANGE

GENERAL SPECIFICATION

7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5 v. torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full Medium Waveband and Short Waveband 31-94 M. and also 4 separate switched band-spread ranges, 13M, 16M, 19M and 25M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow stage by stage instructions.

NEW—The SKYROVER Mk III

Now supplied with redesigned cabinet, edgewise controls, black and chrome plastic cabinet. Size 10 x 6 1/2 x 3 1/2 in. with carrying handle

Can now be built for **£8.19.6** Post 5/- H.P. Terms: 20/- dep. and 11 months at 16/6. Total H.P. Price £10.1.6.

The SKYROVER DE LUXE

Tone Control Circuit is incorporated with separate Control. In a wood cabinet, size 11 x 6 1/2 x 3 1/2 in. covered with a washable material with plastic trim and carrying handle. Car aerial socket fitted.

Can now be built for **£10.19.6** H.P. Terms: 25/- dep. and 11 mths at 20/- Post 5/-. Total H.P.P. £12.5.0.

The "REALISTIC" Seven

★ 7-transistor Superhet. ★ 350 milliwatt output into 4in. high flux speaker.

★ All components mounted on a single printed circuit board ★ Full medium and longwave cover. ★ Plastic cabinet with carrying handle, size 7 x 10 x 3 1/2 in. Blue/Grey or all Grey. ★ Socket for car aerial. ★ i.F. frequency 470 Kc/s. ★ Ferrite rod internal aerial. Operates from PP9 or similar battery. ★ Full data supplied. All coils and I.F.'s etc. fully wound ready for immediate assembly. An Outstanding Receiver. **Can be built for £5.19.6** Post 4/6



REALISTIC Seven DE LUXE

With the same specification as standard model—PLUS a superior wood cabinet in contemporary styling with full vision circular dial.

ONLY £1 EXTRA

NEW SINCLAIR SUPER MINIATURES


THE MICRO-6
Self-contained pocket radio. Size only 1 1/2 x 1 1/2 x 1/2 in. Amazing performance. Complete with earphone and detailed construction data. (Can be built for only **59/6** Mercury cell 1/11 extra. All parts sold separately.

THE SLIMLINE
The new 2-transistor pocket radio. Size only 2 1/2 x 1 1/2 x 1 1/2 in. Micro alloy transistor-ised and printed circuit. All components available separately. Easy to assemble. **CAN BE BUILT FOR 49/6**

THE X10
10 watt power amplifier fitted with integrated pre-amplifier. Requires only 1 mV. for an output of 10 watts. Only 6 x 3 x 1 1/2 in. **KIT PRICE £5.19.6** Post Free

AVAILABLE READY BUILT TESTED AND GUARANTEED, £6.19.6. Post Free 3 pots for volume, Bass and Treble, 7/6 the 3 extra. Mains power pack, if required 54/-.

RECORD PLAYERS

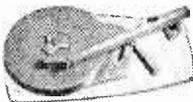

45 r.p.m. 6 volt Bat. operated Complete with pick-up fitted crystal cartridge. Size only 7 1/2 in. x 6 in. Fitted auto stop and start. New and perfect. **45 r.p.m. Model 49/6** Post 2/6
2-speed model for 33 and 45 r.p.m. (as illustrated) **59/6** Post 2/6

GUITAR PICK-UPS

CGM5 Crystal-high imp. Size 1 1/2 x 1 1/2 x 1 1/2 in. Clips to finger board. Complete with cable **LASKY'S PRICE 15/11** Post 1/-

CGM15. Fully adjustable pick-up position carrier. Separate tone and volume control. Pick-up size 3 1/2 x 1 1/2 in. Comp. with lead and plug. **LASKY'S PRICE 59/6** Post 1/6

We are pleased to announce the opening of our premises at **42 TOTTENHAM COURT ROAD, LONDON, W.1.** This branch, will be devoted exclusively to the quality High Fidelity equipment—Tape Recorders, Record Reproducers, Radios, Tuners, etc. Custom built installations will provide balanced comparisons of the best in Hi-Fi in ideal surroundings. Open all day Thursday, early closing Saturday.

REFLECTOGRAPH MODEL A

SEMI-PROFESSIONAL TAPE RECORDER
These recorders are new and guaranteed in the maker's original cartons. They represent an excellent opportunity for the professional and the quality conscious amateur to acquire the best at almost half price. Brief specification: Frequency response 35 to 15,000 c/s at 7 1/2 i.p.s.; two speeds—7 1/2 and 3 1/2 i.p.s.; 3 motors; 8 1/2 in. reel capacity; record level meter; separate record and play back volume controls; bass and treble controls; fast forward and rewind; built in 8 x 6 in. speaker with extension L.S. socket; monitoring facilities provided through the internal speaker; outlet from pre-amplifier for extra amplification; for 200/250V 30 c.p.s. mains use; tape position indicator fitted. Inputs for microphone and radio pick-up. The recorder is finished in grey and is mounted in free standing mahogany plinth—size 20 x 16 x 9 in.



List price of this recorder is £110.50. Few only—carrying cases for the Reflectograph. **LASKY'S PRICE 6 1/2 Gns.** Post 5/-.

LASKY'S PRICE 69 GNS.

PAMPHONIC VR 53 STUDIO RIBBON MICROPHONE
For use with the Reflectograph Model A recorder as shown above with the recorder. High quality. New and unused in maker's original packing. High impedance. Listed at £9.19.6. **LASKY'S PRICE £4.19.6.** Post 7/6. **POST FREE** if ordered with the Reflectograph recorder.

THE NEW "KUBA" IMPORTED AM/FM STEREO RADIOGRAM CHASSIS
Long medium and short waveband coverage plus VHF/FM. Piano key wave-change. Separate flywheel tuning on AM and FM Base, treble and balance control. Magic-eye tuning indicator. Ferrite rod aerial. The very latest printed circuitry. Provision for multiplex-adaptor. 5 valve—line up: EC'85, ECH801, ECC83, ELL80, EAF801. Full vision tuning scale, size 21 x 6 in. Overall dimensions: 21 x 6 1/2 x 8 in. Made to the very highest standards. **LASKY'S PRICE 29 1/2 GNS.** Carriage & Insurance 12/6 extra.

E.M.I. 4-SPEED RECORD PLAYER
New, unused and individually boxed fitted with lightweight pick-up with ACOS G.P. 73/2 stereo cartridge. Cabinet space required 13 1/2 x 12 1/2 x 4 1/2 in. A 9in. metal turntable is fitted. For use on 200/250 volt A.C. Mains with Auto-stop. The selected **LASKY'S PRICE 79/6** Post 3/6 extra cartridge will play all types of Mono Records, 7 1/2, L.P.'s, etc.

INTERNATIONAL TAPE		Famous American Brand—Fully Guaranteed	
3in. Message tape, 150ft.	3 6	3 1/2in. Double play, 1,800ft., Mylar base ...	22 6
3in. Message tape, 225ft.	4 11	5 1/2in. Long play, 1,200ft., Acetate base ...	12 6
3in. Message tape, 300ft.	7 6	5 1/2in. Standard play, 850ft., PVC base ...	11 6
3 1/2in. Triple play, 600ft., Mylar base ...	15 0	5 1/2in. Triple play, 2,400ft., Mylar base ...	45 0
4in. Triple play, 900ft., Mylar base ...	17 6	7in. Standard play, 1,200ft., Mylar base ...	12 6
5in. Double play, 1,200ft., Mylar base ...	15 0	7in. Long play, 1,800ft., Mylar base ...	19 6
5in. Long play, 900ft., Acetate base ...	10 0	7in. Double play, 2,400ft., Mylar base ...	25 0
5in. Standard play, 600ft., PVC base ...	8 6	7in. Long play, 1,800ft., Acetate base ...	15 0
5in. Triple play, 1,800ft., Mylar base ...	35 0	7in. Triple play, 3,600ft., Mylar base ...	58 6

LASKY'S FOR D.I.Y. CONSTRUCTION BARGAINS

Service in Great Britain to both & HI-FI ENTHUSIASTS

COMPLETE MONO/STEREO SYSTEMS TO YOUR SPECIFICATION AT LASKY'S SUPER PRICES



COMMUNICATION RECEIVERS

MODEL HE30 Covers range from 540 Kc/s to 30 Mc/s. 9 valves. 200-250v. A.C. mains. Brand new with full instruction manual, in steel cabinet. Size 15 x 8 x 10in.

LASKY'S PRICE 33 GNS. KIT PRICE 25 GNS. POST FREE
H.P. Terms (Ready Built): £6.13.0. dep. and 11 monthly payments of £2.16.0. Total H.P.P. £37.9.0

MODEL HE40 Covers Medium wave band and 1.6-4.4 Mc/s. 4.5-11.0 Mc/s. 11.0-30.0 Mc/s. 4 valves plus metal rectifier for 200/250v. A.C. mains. size 13 1/2 x 9 1/2 x 5 1/2in. Brand new with instruction manual. No Kits available.


LASKY'S PRICE 19 GNS.
H.P. Terms: £4.0.0. dep. and 11 months at £1.12.0. Post 10/- Total H.P.P. £21.12.0.

MODEL HE80 14-valve super-sensitive communication receiver. Freq. range 540 Kc/s-30 Mc/s. and 144-146 Mc/s. Dual conversion 2 metres with extra R.F. stage. Steel case 17 x 7 1/2 x 10in. For 200/250v. A.C. mains. Brand new with full instruction manual. No Kits available.

LASKY'S PRICE 59 GNS.
H.P. Terms: £12.10.0 dep. and 11 monthly payments of £4.18.0. Total H.P.P. £68.17.0. POST FREE.

CAR RADIO SCOOP! BY FAMOUS BRITISH MANUFACTURER READY TO FIT

Standard Model. A high quality all transistor car radio covering the full Medium waveband. For use on all 12v. D.C. systems—positive or negative earth. Very attractively styled in silver and black to harmonise with all interior styles. Standard dimension steel case 7 x 7 x 2 1/2 in. complete with metal fixing brackets. Illuminated dial, "easyhold" control knobs. Tunable over full medium waveband—200/550 Metres. Leads are fitted for battery, aerial and loudspeaker connections. A fuse is incorporated in the battery lead. Technical details: 12 v. D.C., positive or negative earth; tuned R.F. stage superhet; fully transistorised using 7 semi conductors; power transistor with 3 ohm output sufficient for the largest car; permeability tuning for positive selection and stability. Instruction book and service manual including circuit diagram supplied. New and unused in maker's original cartons. Fully guaranteed. Today's value almost double.

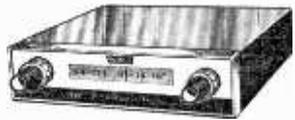

LASKY'S PRICE £6.19.6 (Excluding speaker and aerial) Post & Pack 5/6 extra



De Luxe Model. Incorporating push-pull output providing 6 watts output together with fully variable tone control and five push-button station selectors. Ready to fit. Size, finish, etc. as standard model. Brand new and unused in maker's original cartons. Fully guaranteed.

LASKY'S PRICE £8.19.6 (Excluding speaker and aerial) Post and Pack 5/6

Suitable loudspeakers available: 3in. round, 10/8; 7 x 4in. elliptical, 11/6; 8 x 3in. elliptical, 12/6. Post 1/6 extra.
Fully retractable: Type A28 open 4 1/2in., closed 9 1/2in., 50/-; Type A24 open 6 1/2in., closed 16 1/2in., 55/-; Type A20 open 4 1/2in., closed 9 1/2in. (with lock-in device) 62/8; Wing Mounting: Type A13 opens to 4 1/2in., 26/-; Type A40 opens to 6 1/2in., 43/-, Post 2/-.

B.S.R. AUTOCHANGERS AT LOWEST EVER PRICES

Brand new and fully guaranteed—complete with cartridge and stylus.
UA16 4 speed mains £4.19.6 UA20 4 speed, mains 25.10.8
Add 5/- carriage and packing on each.

207 EDGWARE ROAD, LONDON, W.2 | 33 TOTTENHAM COURT ROAD, W.1. | 152/3 FLEET STREET, LONDON, EC.4.
Near Praed St. PADDINGTON 3271/2 | Nearest Stn., Goudge St. MUSEUM 2605 | Telephone: Fleet Street 2833
BOTH OPEN ALL DAY SAT. Early closing Thurs., Mail Orders to Dept. X.W., 207 Edgware Rd., W.2 | Open all day Thursday. Early closing Sat.

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

Designed for the electronics age...
PRIMAX and PRIMAXA solder guns

S
P
O
T
L
I
G
H
T

S
O
L
D
E
R
G
U
N
S



PRIMAX
60 W SPOTLIGHT
86/8d ea.

PRIMAXA
100 W SPOTLIGHT
112/8d ea.

Distributed by **S. KEMPNER LTD.**
384 FINCHLEY ROAD, LONDON, N.W.2 Tel: HAM 6365

LEARN ELECTRONICS AS YOU BUILD 25 CIRCUITS EXPERIMENTS TEST GEAR

- including:
- MINIATURE CATHODE RAY OSCILLOSCOPE
 - VALVE EXPERIMENTS
 - BASIC AMPLIFIER
 - BASIC RECTIFIER
 - PHOTO ELECTRIC CIRCUIT
 - TIME DELAY CIRCUIT
 - SQUARE WAVE GENERATOR
 - SIMPLE TRANSMITTER
 - TRANSISTOR EXPERIMENTS
 - BASIC OSCILLATOR
 - ELECTRONIC SWITCH
 - SIGNAL TRACER
 - BASIC COMPUTER CIRCUIT
 - BASIC RADIO RECEIVER
 - MORSE CODE OSCILLATOR ETC. ETC.

This complete practical course will teach you all the basic facts of electronics by making experiments and building apparatus. You learn how to recognise and handle all types of components — their symbols and how to read a circuit diagram. You see how circuits are built and how they work BY USING THE OSCILLOSCOPE PROVIDED. Applications of all the main electronic circuits are demonstrated—radio reception and transmission; photo-electrics; computer bases; timers; control circuits, etc; including servicing techniques. NO MATHS USED OR NEEDED. NO THEORY NEEDED. NO PREVIOUS KNOWLEDGE OR EXPERIENCE NEEDED. Tutor service available. No extras needed—tools provided. Send now, for FREE DETAILS without obligation, to address below.

TO: LERNAKIT, Dept. K 10, RADIO HOUSE, 40 RUSSELL STREET, READING

POST NOW Please send free details—
NAME
ADDRESS
..... to address below

THE PRACTICAL WAY
TO ENJOY ELECTRONICS



HIGHEST QUALITY
AT LOWER COST

World-famous kit-sets anyone can build

The clearly written instruction manuals, issued with each kit, show you how
A KIT FOR EVERY INTEREST . . . FOR HOME, WORKSHOP, LABORATORIES



HI-FI F.M. TUNER. Tuning range 88-108 Mc/s. Tuning unit (FMT-4U) with 10.7 Mc/s. I.F. output (£2.15.0 inc. P.T.). I.F. Amp. (FMA-4U) complete with cabinet and valves. (£13.3.0). Total kit £15.18.0. Assembly can be arranged.

"OXFORD" DE-LUXE TWO WAVEBAND TRANSISTOR PORTABLE. Model: UXR-2. The ideal domestic, car, or personal portable receiver. 10 Semi-conductors. Send for full details. £14.18.0 Kit (inc. P.T.). Assembly can be arranged.




HI-FI A.M./F.M. TUNER. Covers F.M. 88-108 Mc/s. A.M. 16-50, 200-550, 900-2,000m. Tuning heart (£4.13.6 inc. P.T.) and I.F. Amp. £21.16.6. Printed circuit board. Total Kit £26.10.0
6W DE LUXE AMPLIFIER. Model S-33H. An inexpensive Stereo-Mono amplifier, with high sensitivity. Suitable for Decca Deram Cartridge. Kit £15.17.6. Assembled £21.7.6
6 TRANSISTOR PORTABLE. Model UJXR-1. Prealigned I.F. transformers. Printed circuit, 7 x 4in. high flux speaker. Real hide case. Very easy to build. Kit £12.11.0 incl. P.T.
SHORTWAVE TRANSISTOR PORTABLE. Model RSW-1. Two short bands, trawler and medium wave Kit £19.17.6 incl. P.T.

5W HI-FI MONO AMPLIFIER. Model MA-5. A low-priced well designed amplifier. Printed circuit construction makes it easy to build. Kit £10.19.6. Assembled £15.10.0
"COTSWOLD" HI-FI SPEAKER SYSTEMS. MF5 or Standard. Range 30-20,000 c/s. Kit £23.4.0. Assembled £30.15.0
MONO CONTROL UNIT. Model UMC-1. Ideal for use with MA-12 or similar amplifier. Kit £8.12.6. Assembled £13.12.6
HI-FI EQUIPMENT CABINETS. Large range, in kit form or assembled and finished, incl. record housing range, available to meet various needs. Details on request. From £7.15.0 to £44.2.0



5in. OSCILLOSCOPE. Model 10-12U. Wide band amplifiers essential for T.V. servicing, F.M. alignment etc. T/B covers 10 c/s-500 kc/s in 5 ranges. Kit £32.12.6. Assembled £41.10.0. The ideal low-priced 'scope.

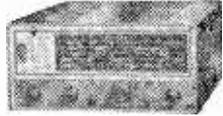
COMMUNICATIONS TYPE RECEIVER. Model RG-1. Freq. cov: 600 kc/s.-1.5 Mc/s; 1.7 Mc/s.-32 Mc/s. A two-speed tuning drive. R.F. "Front end" supplied assembled and aligned. Kit £39.16.0. Assembled £53.0.0.



SEND FOR FREE BRITISH HEATHKIT CATALOGUE—MANY MODELS TO CHOOSE FROM

All models available assembled. Deferred terms available over £10. Free delivery U.K.

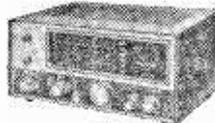PA AMPLIFIER. Model PA-1. 50W output. For vocal and instrumental groups, guitars, etc. 4 inputs 2 speakers, Tremolo. Send for full details. Kit £54.15.0. Legs optional extra 17/6 set. Assembled £74.0.0.



PA-1

50W POWER AMPLIFIER. Model MA-50. Ideal for PA work etc. Kit £19.18.0. Assembled £27.18.0. Suitable Control Unit, model UMC-1.


AMATEUR BANDS RECEIVER. Model RA-1. Covers the amateur bands from 160 to 10m. Special features incl.: half lattice filter; 8 valves; Tuning meter; tuned RF amplifier stage. Kit £39.6.6. Assembled £52.10.0.

Q MULTIPLIER. Model QPM-1. For 450/470 kc/s. I.F. Kit £8.10.0. Assembled £12.14.0. QPM-16 for 1.6 Mc/s I.F. same prices.

2½in. PORTABLE SERVICE OSCILLOSCOPE. Model OS-1. An ideal light, compact 'scope for servicing and general work. Printed circuit construction. Kit £22.18.0. Assembled £30.8.0
"MOHICAN" TRANSISTOR GEN-COVERAGE RECEIVER. Model GC-1U. An excellent portable for the short wave listener. Kit £37.17.6. Assembled £45.17.6
VALVE VOLTMEETER. Model V-7A. Measures up to 1,500 v. (D.C. and r.m.s.) and 4,000 pk-to-pk. Res. 0.1Ω to 1,000 MΩ. Kit £13.18.6. Assembled £19.18.6.

LATEST AMERICAN SINGLE-SIDE-BAND AMATEUR EQUIPMENT. Now available from Gloucester. Please send for details.

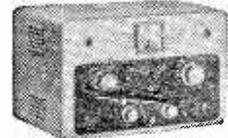MULTIMETER. Model MM-1U. Ranges: 0-1.5 v. to 1,500 v. A.C. and D.C. 0-150μA—15A D.C. 0.2Ω to 20MΩ 4½ in. 50μA meter. Kit £12.18.0. Assembled £18.11.6
R.F. SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s. fundamental, 200 Mc/s. on harmonics. Up to 100 mV output all bands. Kit £13.8.0. Assembled £19.18.0



TELEVISION ALIGNMENT GENERATOR. Model HFV-1. Accurate alignment of TV receivers achieved in minimum time at low cost. Covers 3.6 to 220 Mc/s. fundamentals. Kit £34.18.0. Assembled £44.10.0

AMATEUR TRANSMITTER. Model DX-40U. Self-contained. 80-10 m. Power input 75 w. CW, 60 w. peak C.C. phone. Output Kit £33.19.0. Assembled £45.8.0

AMATEUR TRANSMITTER. Model DX-100U. Covers all amateur bands. 160-10 m. 150 w. D.C. input, self contained with power supply Modulator. VFO Kit £79.10.0. Assembled £104.15.0



DX-100U

DAYSTROM LTD.

Dept. P.W. 5, GLOUCESTER, ENGLAND

A subsidiary of Weston Instruments Group, manufacturers of the
WORLD'S LARGEST-SELLING ELECTRONIC KITS

Please Send me **FREE BRITISH CATALOGUE (Yes/No)**

Full details of model(s).....

NAME

ADDRESS


PW5

Here's vital time-saving data


to earn money for you!




NEARLY 1,200 CIRCUITS

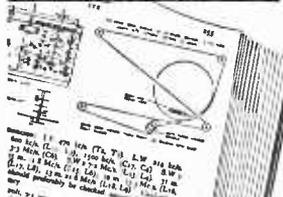

HUNDREDS OF DIAGRAMS

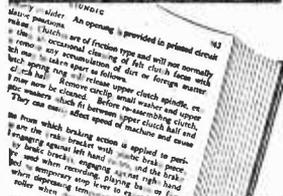

PACKED WITH REPAIR HINTS

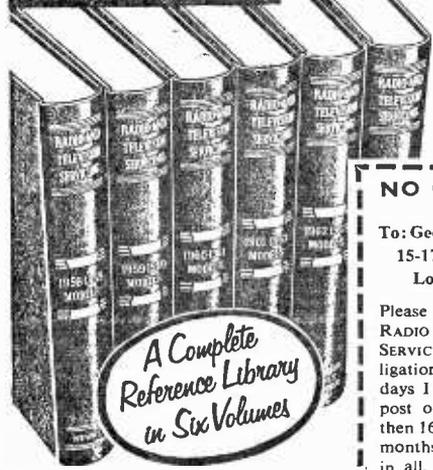

A Complete Reference Library in Six Volumes

NEW—12th EDITION OF NEWNES RADIO & TV SERVICING
 This is the set you **MUST** have to beat the frustration and time loss which fritter away your opportunities to earn more. To-day with a very great number of models needing repair and maintenance, more and more difficult repair jobs will crop up. Yet these complicated jobs become so simple when you have the right information at hand. Here, always ready, is your complete library of data—Newnes famous **RADIO & TV SERVICING**. Nearly 60,000 sets of previous editions have been sold... solid proof of its importance to you—the engineer in Radio and TV. You can use this new edition for a week free.

3,500 PAGES OF REPAIR INFORMATION FOR NEARLY 2,300 Popular Models!

DATA FOR OVER 90 MAKES 1964 BACK TO 1958

Acc, Aerodyne, Ajax, Alba, Argosy, Baird, Beethoven, Berec, B.R.C., B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Doric, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, Elpico, E.M.I., Emerson, Emisonic, Eumig, Ever Ready, Ferguson, Ferranti, Fidelity, Ford Motor Co., Garrard, G.B.C., G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, Magnavox, Marconiphone, Masteradio, McMichael, Motorola, Murphy, National, Newmatic, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Playmate, Portadyne, Portogram, Pye, Pye Telecommunications, Radiomobile, Raymond, Recording Devices, Rediffusion, Regentone, Retra, Revelation, R.G.D., Roberts' Radio, Sobell, Sonolor, Sony, Sound, Spencer-West, Standard, Stella, Stereosound, Stuzzi, Thorn, Trans Arena, U.K.W., Ultra, Vidor, Volmar, Walter, Waltham-Standard, Zenith.

- TELEVISION
- RADIO
- RADIOGRAMS
- TAPE RECORDERS
- RECORD REPRODUCERS
- CAR RADIOS

POST COUPON NOW FOR 7 days FREE TRIAL

NO CHARGE FOR CREDIT IF KEPT AFTER FREE TRIAL

*If under 21 your father must fill up coupon.
 If married woman your husband must fill it up.*

To: George Newnes Ltd.,
 15-17 Long Acre,
 London, W.C.2

Full Name _____
 (BLOCK LETTERS) (Mr., Mrs., Miss)

Address _____

Please send Newnes RADIO & TELEVISION SERVICING without obligation to buy. In 8 days I will return it or post only 16/- deposit, then 16/- monthly for 20 months, paying £16 16s. in all. Cash in 8 days £16 16s.

Occupation _____

Signature _____
 (Mr., Mrs., Miss)

Tick ✓ where applicable

The address on left is—

My Property	<input type="checkbox"/>
Rented unfurnished	<input type="checkbox"/>
Parents' Home	<input type="checkbox"/>
Furnished Accom.	<input type="checkbox"/>
Temporary Address	<input type="checkbox"/>

(RV)41/1189

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone: PRIMROSE 9090

NEAREST UNDERGROUND: CHALK FARM. ALL GOODS LISTED BELOW ACTUALLY IN STOCK ALL GOODS ARE NEW, BEST QUALITY BRANDS ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE, PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS 'NEW AND TESTED' BUT HAVE A SHORT AND UNRELIABLE LIFE

0A2	4/6	6B87	25/-	736	12/6	25Y3/9	7/9	AC6PEN 4/9	EABC80 5/9	EL81	8/3	LN309 11/-	R17	17/6	U101	18/6	GD3	5/6	
0B2	4/6	6B86	3/9	737	9/6	25Z4/9	7/9	AC1/CPEN	EAC91 3/3	EL83	6/9	LN319 10/6	R18	9/6	U107	17/6	GDB	5/6	
0ZAGT	4/3	6B87	5/-	703	3/-	25Z5	7/3	(5) 17/6	EAL2 7/6	EL84	4/6	LP2	9/6	R14	6/6	U11	9/6	GD14	10/-
1A3	2/6	6B86	4/-	706	6/0	25Z6/27	8/-	AC1/CPEN	EB34 1/-	EL85	7/6	LZ319 6/6	RS2	7/6	U251	9/9	GET103	7/-	
1A4	12/6	6C4	2/3	707	5/-	278U 28/3	(7)	17/-	EB41 4/9	EL86	7/3	LZ329 6/6	RG1/240A	U2M1	8/9	GET104/10			
1A5	5/-	6C5	4/-	703	15/-	2817	6/9	AC/SG 22/6	EB91 2/3	EL91	2/6	MHD4 7/6	54/-	U282	12/3	GET104/78			
1A7GT	7/9	6C6	3/-	705	14/6	30C1	6/6	AC/SG/VM	EB93 20/6	EL95	5/6	MHD1612/6	RE34	7/6	U301	11/6	GET111/2		
1C1	4/-	6C8	3/-	706	14/6	30C17	17/6	AC/SG/VM	EB93 20/6	EL95	5/6	MHD1612/6	RE34	7/6	U301	11/6	GET113 6/9		
1C2	8/-	6C9	10/9	747	3/9	30C18	10/6	AC/TH10/-	EB44 6/6	EL92	16/4	MS4B 20/5	SP4B	1/6	U399	9/6	GET114 6/6		
1C3	6/6	6C10	8/-	747	12/6	30F5	5/9	AC/T/18/-	EB81 5/9	EL92	18/6	MS4 12/-	SP13C	12/6	U403	9/9	GET116/17		
1C5	5/-	6C12	5/9	774	5/-	30L1	5/6	AC/V/12/-	EB90 3/9	EL96	13/6	MHD12/14 6/6	SP41	2/-	U404	6/6	GET1873 9/3		
1C6	10/6	6C9D6	18/-	774	5/-	30L15 9/3	5/6	AC/V/12/-	EB90 3/9	EM4 17/9	MX40	8/9	SP42	12/6	U801	16/3	GET1874 9/6		
1D3	6/6	6C18	8/12	812	12/6	30P4	19/3	AT/1 2/3	EM3 5/9	EM3 11/6	N07	10/6	SP61	3/4	U420	9/6	GET13 6/9		
1D6	9/6	6C14	24/-	919W/6	9/6	30P12	5/3	AT/1 2/3	EM3 5/9	EM3 11/6	N07	10/6	SP61	3/4	U420	9/6	GET13 6/9		
1FD1	6/-	6D1	1/6	912	3/-	30P16 9/3	5/3	AZ31 6/6	EBF89 6/6	EM71	15/6	N108 26/2	T41	9/-	VM84B 12/-	GEX36 10/6			
1FD9	3/6	6D3	9/6	907	7/6	30P19 12/3	5/3	AZ41 6/6	EBL21 10/6	FM50	6/3	N339 15/6	T1D2	12/6	VP2	3/6	GEX45 6/6		
1G6	8/-	6D8	3/9	10C1	8/9	30P11 10/3	5/3	B36 4/9	EC52 4/3	EM51 7/3	P41	3/6	TDD4	7/6	VP2B	9/6	GEX44 11/6		
1HGT	7/6	6E2	9/6	10C2	12/3	30P14 14/3	5/3	B39 5/6	EC53 12/6	EM54 6/9	PE1	2/6	TH4B	12/6	VP2C	2/6	GEX43 9/6		
1L4	2/3	6F1	9/6	10D1	1/6	35/1	12/6	B719 5/9	EC54 6/9	EM85 8/9	PABC80 6/9	TH12C 10/6	VP44	14/6	VP4B	12/6	MAT100 8/6		
1L4A	17/6	6F6G	3/9	10D2	11/8	35/5	12/6	BL63 10/6	EC70 4/9	EM87 7/6	PC86 10/3	TH130C 14/6	VP4B	12/6	VP4B	12/6	MAT101 8/6		
1L4A	16/10	6F6GT	7/6	10F1	10/1	35A5	20/9	CL 12/6	EC90 2/3	EN31 10/6	PC88 9/6	TH41 10/6	VP13C	7/6	VP13C	7/6	MAT120 8/6		
1LD5	4/-	6F7G	5/-	10F9	9/9	35L6GT 6/3	6/3	CCH35 12/6	EC91 4/9	EN91 5/6	PC95 6/9	TH233 6/9	VP23	2/6	MAT121 8/6				
1LN5	4/-	6E7G	5/-	10G1	9/9	35L4 6/3	6/3	CK506 6/6	EC92 6/6	EN91 5/6	PC95 6/9	TH233 6/9	VP23	2/6	MAT121 8/6				
1NPT	8/6	6F11	17/9	10LD3	8/6	35Z3	16/6	CL 19/6	ECC31 7/3	EY81 7/3	PC84 5/6	TP25 5/6	VP13	3/6	VP133	9/9	OA10 6/6		
1P1	6/-	6F12	3/9	10LD11	9/6	35Z4GT 4/6	4/6	CL3 11/6	ECC32 4/9	EY83 9/3	PC85 6/9	TP2620 7/6	VP7	21/6	VP7	21/6	OA70 3/6		
1P10	4/6	6F13	3/9	10P13	8/3	35Z5GT 5/9	5/9	CV6 2/6	ECC33 20/1	EY84 9/6	PC88 10/6	TP86F 11/8	VP105	3/6	VP105	3/6	OA73 3/6		
1P11	5/3	6F14	23/3	10P14	11/6	36	12/6	CV63 10/6	ECC34 29/7	EY86 5/9	PC89 8/6	TP86F 11/8	VP105	3/6	VP105	3/6	OA73 3/6		
1P12	4/6	6F15	14/6	10P15	12/6	36	12/6	CV63 10/6	ECC34 29/7	EY86 5/9	PC89 8/6	TP86F 11/8	VP105	3/6	VP105	3/6	OA73 3/6		
184	5/-	6F17	12/6	11D5	17/6	408U4	4/6	CV271 12/6	EC040 7/6	EY91 3/6	PCF90 6/6	UB41 10/6	VT601	3/6	VT601	3/6	OA85 3/6		
185	3/6	6F18	13/5	11E1	15/-	41MTL 8/6	8/6	CV428 19/6	ECC41 3/6	EY85 4/6	PCF82 6/3	UCB41 6/3	VU11	5/6	VM84B 12/-	GEX36 10/6			
1T2	29/-	6F23	6/3	11E3 17/7	41STH 10/6	CYL 16/4	EC82 4/6	EZ40 5/3	EC82 4/6	EZ40 5/3	PCF84 8/6	UBC81 6/3	VU120 10/6	OA90 3/6					
1T4	2/3	6F24 9/6	12A6	2/3	42 5/-	CY1C 6/6	EC83 4/6	EZ41 6/3	EC83 4/6	EZ41 6/3	PCF86 7/9	UBC81 6/3	VU120A10/6	OA91 3/6					
1U5	5/3	6F25 9/6	12A6	2/3	42 5/-	CY1C 6/6	EC83 4/6	EZ41 6/3	EC83 4/6	EZ41 6/3	PCF86 7/9	UBC81 6/3	VU120A10/6	OA91 3/6					
1U7	5/3	6F23 3/6	12A6C	8/6	45 17/6	D1 1/3	EC85 9/9	EZ81 4/6	EC85 9/9	EZ81 4/6	PCF80 10/6	UBC81 6/3	VU121 10/9	W21 5/6	VM84B 12/-	GEX36 10/6			
2A7	12/6	6G6 2/6	12A6D6	9/6	45Z6GT/6/3	D15 13/3	EC88 9/9	EZ90 3/9	EC88 9/9	EZ90 3/9	PCF86 10/6	UC92 6/3	W42 12/-	OA210 9/6					
2C26	2/9	6H6 1/6	12A6E 8/-	50A5 21/10	D42 10/6	ECC189 11/6	FC2 14/6	PCL82 6/6	ECC189 11/6	FC2 14/6	PCL82 6/6	UC88 8/6	W61M 24/6	OA2210 7/6					
2D13G	7/6	6J5G 3/9	12A7H 5/-	50B5 6/6	D63 5/3	ECC80 9/6	FC4 8/9	PCL83 11/6	ECC80 9/6	FC4 8/9	PCL83 11/6	UC88 8/6	W61M 24/6	OA2210 7/6					
2D31	5/3	6J5G 3/9	12A7H 5/-	50B5 6/6	D63 5/3	ECC80 9/6	FC4 8/9	PCL83 11/6	ECC80 9/6	FC4 8/9	PCL83 11/6	UC88 8/6	W61M 24/6	OA2210 7/6					
2P 23/3	6J6 3/6	12A7G 4/6	50C6D6/40/6	DAC22 7/9	ECF80 6/6	FC13 17/6	PCL85 8/6	UC82 8/6	ECF80 6/6	FC13 17/6	PCL85 8/6	UC82 8/6	W77 2/6	OC19 25/6					
2X2	3/-	6J7G 4/6	12A7J 3/6	50E6GT 6/3	DFA91 3/6	ECF82 6/6	FC13 17/6	PCL86 8/6	ECF82 6/6	FC13 17/6	PCL86 8/6	UC82 8/6	W77 2/6	OC19 25/6					
3A4	3/9	6J7GT 7/6	12A7U 5/9	52KU 14/8	DFA96 6/6	ECF86 11/6	FC13 17/6	PCL88 12/6	ECF86 11/6	FC13 17/6	PCL88 12/6	UC81 8/6	W101 26/2	OC23 57/6					
3A5	9/9	6K6GT 5/8	12A7U 4/6	53KU 14/8	DDC90 8/9	ECF80/4 24/6	FTW 9/9	PCL88 12/6	DDC90 8/9	ECF80/4 24/6	FTW 9/9	UC82 8/6	W107 10/6	OC25 12/6					
3D6	3/6	6K7GT 4/6	12A7X 6/6	53 6/6	DD41 10/6	ECH21 9/6	GZ30 7/6	PEN45 7/6	DD41 10/6	ECH21 9/6	GZ30 7/6	UC82 8/6	W107 10/6	OC25 12/6					
3D4	5/3	6K8G 3/6	12A7Y 7/9	77 8/8	DD4 7/6	ECH33 22/8	GZ32 8/6	PEN45 7/6	DD4 7/6	ECH33 22/8	GZ32 8/6	UC82 8/6	W107 10/6	OC25 12/6					
3Q5GT	7/-	6K8GT/6/6	12BA6 5/9	80 5/3	DD25 7/6	ECH35 6/3	GZ33 17/6	PEN46 4/6	DD25 7/6	ECH35 6/3	GZ33 17/6	UC82 8/6	W107 10/6	OC25 12/6					
384	4/6	6K25 24/6	12BE6 4/9	83V 3/6	DF33 8/6	ECH42 8/6	GZ34 10/6	PEN46 4/6	DF33 8/6	ECH42 8/6	GZ34 10/6	UC82 8/6	W107 10/6	OC25 12/6					
3Y4	5/3	6L12 10/6	12BE7 8/6	85A2 4/6	DF41 2/3	ECH43 23/3	GZ50 55/6	PEN47 14/6	DF41 2/3	ECH43 23/3	GZ50 55/6	UC82 8/6	W107 10/6	OC25 12/6					
4D1	3/6	6L5G 12/6	12BE1 1/6	90AG 67/6	DF72 3/9	ECH83 9/6	H30 5/6	PEN43D 12/6	DF72 3/9	ECH83 9/6	H30 5/6	UC82 8/6	W107 10/6	OC25 12/6					
5A4G	8/6	6L6GT 7/6	12H6GT 1/6	90AV 67/6	DF91 2/3	ECH84 2/6	HABC80 6/6	PEN43D 12/6	DF91 2/3	ECH84 2/6	HABC80 6/6	UC82 8/6	W107 10/6	OC25 12/6					
5T4	7/-	6L6GT 7/6	12J5GT 2/6	90GC 42/-	DF96 6/6	ECL80 8/6	HL2 7/6	PEN44 7/6	DF96 6/6	ECL80 8/6	HL2 7/6	UC82 8/6	W107 10/6	OC25 12/6					
5U4G	6/6	6L18 10/6	12J7GT 7/3	90CV 42/-	DF97 10/6	ECL82 6/6	HL3C 4/6	PEN44 7/6	DF97 10/6	ECL82 6/6	HL3C 4/6	UC82 8/6	W107 10/6	OC25 12/6					
5Y4G	3/6	6L19 12/6	12K5 10/6	90C1 16/6	DF130 15/6	ECL86 8/6	HL3D 12/6	PEN44 7/6	DF130 15/6	ECL86 8/6	HL3D 12/6	UC82 8/6	W107 10/6	OC25 12/6					
5Y3GT	4/6	6L19 12/6	12K7GT 6/6	150B2 4/6	DH63 6/6	ECL86 8/6	HL3D 12/6	PEN44 7/6	DH63 6/6	ECL86 8/6	HL3D 12/6	UC82 8/6	W107 10/6	OC25 12/6					
5Y4	9/6	6L13 7/6	12K8GT 9/9	150C2 4/6	DH76 3/6	ECF6 20/6	HL41 3/9	PL1 200/20/5	DH76 3/6	ECF6 20/6	HL41 3/9	PL1 200/20/5	UM4 15/2	X78 20/6	OC45M 8/6				
5Z3	6/6	6L20 5/6	12Q7GT 3/6	161 13/1	DH77 3/9	EF9 20/6	HL41DD12/-	PL36 9/6	UM4 15/2	X78 20/6	OC45M 8/6	UM4 15/2	X78 20/6	OC45M 8/6					
5Z4	7/6	6N7GT 7/6	12SA7GT/6/6	185B2 34/11	DH81 23/3	EP22 6/6	HL42D11/2/-	PL38 16/6	UM4 15/2	X78 20/6	OC45M 8/6	UM4 15/2	X78 20/6	OC45M 8/6					
6/30L2	2/6	6N7GT 7/6	12SA7GT/6/6	185B2 34/11	DH81 23/3	EP22 6/6	HL42D11/2/-	PL38 16/6	UM4 15/2	X78 20/6	OC45M 8/6	UM4 15/2	X78 20/6	OC45M 8/6					
6A6G	3/9	6P25 6/9	12S6GT 7/6	2159G 6/6	DH101 125/-	EP26 3/3	HL133D11/6	PL82 8/6	UM4 15/2	X78 20/6	OC45M 8/6	UM4 15/2	X78 20/6	OC45M 8/6					
6A8G	5/9	6P26 9/9	12S6GT 7/6	2159G 6/6	DH101 125/-	EP26 3/3	HL133D11/6	PL82 8/6	UM4 15/2	X78 20/6	OC45M 8/6	UM4 15/2	X78 20/6	OC45M 8/6					
6A7	4/-	6P28 11/6	12S7 5/9	392 15/-	DK32 7/9	RF40 8/9	HN309 26/6	PL83 6/6	UM4 15/2	X78 20/6	OC45M 8/6	UM4 15/2	X78 20/6	OC45M 8/6					
6AC7	3/6	6Q7G 4/6	12S7 5/9	393 15/-	DK40 15/6	RF41 6/9	HVR2 8/3	PL84 6/6	UM4 15/2	X78 20/6	OC45M 8/6	UM4 15/2	X78 20/6	OC45M 8/6					
6AC5	3/6	6Q7GT 7/6	12S7 5/9	394 15/-	DK92 5/6	RF42 6/9	HVR2A 8/3	PL85 15/6	UM4 15/2	X78 20/6	OC45M 8/6	UM4 15/2	X78 20/6						

ELECTRONICS


LEARN - THE PRACTICAL WAY . . .

your career . . .
hobby . . .
own business . . . ?

The demands for good Electronic Engineers is increasing almost daily throughout the world. Electronics is now the most rapidly expanding of all industries with its applications reaching into almost every sphere of human activity. If you are looking for a new career with new opportunities, then now is the time to choose—Electronics. If you are already employed in this field—then now is the moment to seek high qualifications to secure the top jobs which are waiting to be filled. Most of all, the great potential of electronic development means unlimited scope for the future and will ensure a secure occupation for you—unlikely to be affected by possible future recessions in other industries.

The British National Radio School has had 25 years' experience of HOME STUDY coaching for students wishing to master the fascinating subjects of Electronics—whether the object be career or as a hobby or new interest. The School is entirely independent and specialises ONLY in the teaching of electronic subjects. It employs only fully qualified staff to conduct and supervise each individual course taken by a student and it is this close and personal contact between Tutor and Student which we believe makes possible the successful completion of a course of study.

A special feature of our system is that all courses start right from the beginning and no previous knowledge or experience is necessary or expected. Training is carried out in easy step-by-step stages using the most modern methods of tuition. The great advantage of the home study method is that it provides a complete self-contained course giving everything needed for the subject concerned and enabling work to be done in the comfort of one's own home and over any period of time desired.

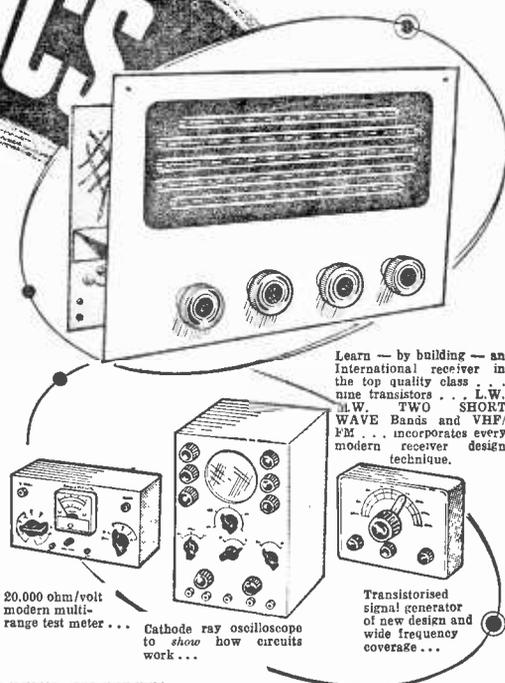

Learn — by building — an International receiver in the top quality class . . . nine transistors . . . L.W. TWO SHORT WAVE BANDS and VHF/PB . . . incorporates every modern receiver design technique.

20,000 ohm/volt modern multi-range test meter . . .

Cathode ray oscilloscope to show how circuits work . . .

Transistorised signal generator of new design and wide frequency coverage . . .



Complete picture way library of theory books and practical manuals
NO MATHEMATICS!

BUILD AND EXPERIMENT WITH ALL THE ABOVE—AS—YOU—LEARN . . .

This is a new complete experimental course comprising a mixture of theory and practical work using a very full range of electronic components and apparatus. Starting right from the beginning—or at a later stage if needed—the course enables the student to build up all the basic electronic circuits—amplifier; oscillator; rectifier; detector; servicing of a latest design fully transistorised receiver using nine transistors and covering long and medium wave and TWO SHORT WAVEBANDS plus VHF/PM reception. It is of real luxury quality throughout—operates from a 9V. battery and can be used anywhere in the world. Every present-day technique in circuitry is covered and the course also includes multi-range test meter; signal generator and oscilloscope. By the end of the course the student will be able to deal with any type of servicing work with confidence and will also have a very useful workshop of equipment. Nearly 100 interesting and absorbing EXPERIMENTS are carried out during this comprehensive course enabling anyone to gain full mastery of electronics.

EXAMINATION COURSES

- CITY & GUILDS TELECOM. TECHNICIANS CERT.
- CITY & GUILDS FULL TECHNOLOGICAL CERT.
- A.M.Brit.I.R.E. EXAMINATION
- RADIO AMATEURS LICENCE EXAMINATION
- P.M.G. CERTIFICATES FOR RADIO OPERATORS
- R.T.E.B. SERVICING CERTIFICATES

OTHER COURSES

- MATHEMATICS
- TELEVISION
- TRANSISTORS
- SERVO-MECHANISMS
- COMPUTERS
- RADAR & NAVIGATIONAL AIDS

FREE



POST NOW

TO: BRITISH NATIONAL RADIO SCHOOL, RADIO HOUSE, READING, BERKS.
Please send me your free Brochure, giving details of your Courses, without any obligation, to:—

NAME _____

ADDRESS _____

I am interested in _____ (We do not employ representatives)

} Block Caps Please

courses above PW 5/65

British National Radio School

PRACTICAL WIRELESS

MAY 1965
VOL 41 NO 699

SPRING, SPRING, SPRING

IT is said that in the Spring, a young man's fancy turns lightly to all sorts of frivolous things. But what of the amateur radio enthusiast? Where do his electronic fancies lie in these early months of the year?

It was once fondly imagined that the epitome of radio work was to spend a dark Winter's evening huddled up round an oil stove wearing a set of headphones. This was never really true, for the real enthusiast cares little about seasons, except perhaps for such aspects as their effect on F-layer propagation.

We agree that there may be less bench work during the Summer months, and maybe some slight slackening off in ham radio activities. (Then there is always the lady of the house who has the temerity to uproot occupants of radio dens for the frivolity of Spring cleaning. Sacrilege!) But radio fans like to follow the sun (or the rain) and there has always been a large Summer activity.

We would say, then, that this Spring, many P.W. readers will be fancying mobile operation or Field Days with the club. Others may be thinking of radio control of models. (Some will digress from radio, of course, and for those who find themselves more afloat than on dry land our July issue contains an article on building a marine radiobeacon direction finder.)

Thus, in divers ways, many shack-bound enthusiasts will again stumble out into the great open spaces, shading their eyes from the unaccustomed sunlight. So too, alas, will the Daleks of the Decibels—the gruesome plague bearers of transistor portables, vainly attempting to get ten watts output from a pair of OC81's and a three-inch speaker. Not to condemn all users of transistor portables, of course—only the moronic tone-deaf. However, this is to digress ourselves.

CONTENTS

	<i>page</i>
News and Comment	22
The Empire 7	24
Designing a Multimeter	28
On the Short Waves	35
Artificial Aerial Transmitter Loads	37
Grounded Inverted L Antenna	39
High-fidelity Amplification	43
A.F./R.F. Signal Generator	48
News and Comment	52
Transformerless Transistor Amplifier	54
Practically Wireless	58
Books Reviewed	61
Cabinet and Chassis Techniques—Part 4	66
Club News	73
Preparing for the R.A.E.—Part 7	74

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes Rand London. Subscription rates, including postage: 29s. per year to any part of the world. © George Newnes Ltd., 1965. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. **THE JUNE ISSUE WILL BE PUBLISHED ON MAY 6TH.**

PCR2 Transformers

I AM building an s.s.b. receiver which is to employ three of the i.f. transformers taken from an old PCR2 receiver.

After drilling the chassis, I found one of the iron dust slugs to be faulty, and the other two missing! These slugs appear different to any I have seen before and the more modern ones which are available cannot readily be adapted. Likewise, I shudder at the thought of changing the chassis to accept a different type of unit. I have made up the rest of the chain with trimmer-tuned transformers and, in any case, have no more slug-tuned transformers in my junk box.

Is it possible that some reader will have these transformers lying idle and be kind enough to spare three of the slugs, or, better still, three complete transformers? I shall, of course, cover all expenses.

G. H. Scholey,
G3CDR.

157 Dartford Road,
Dartford,
Kent.

Mr. Scholey and other readers may be interested to know that in next month's issue of P.W. we will be publishing an article describing several useful modifications to this interesting ex-government receiver.—Editor.

Science Museum Party

THE Roding Boys' Society is arranging a conducted tour round the Radio and Electronic Gallery of the Science Museum, with an afternoon lecture which will be chosen to cover an electronic subject. I would be delighted if any of your young readers who live in, or who are visiting London would like to join in.

We are fixing a provisional date as Saturday, April 24th, and meeting at 10 o'clock in the morning at South Kensington Underground Station.

If lads who intend to come along drop me a card, we will have a rough idea as to how big the party will be, as well as knowing in advance something about our companions for the day.

Ken Smith,
G3JIX.

82 Granville Road,
Walthamstow, E.17.

NEWS AND.

R.S.G.B. CONVENTION

The Eleventh International V.H.F./U.H.F. Convention organised by the Radio Society of Great Britain, will be held at the Kingsley Hotel in London, on Saturday, April 10th.


The Convention will open with a trade show in the morning, followed by a programme of lectures in the afternoon. A dinner in the evening will end the Convention, when Mr. C. G. Phillips, Chief Telecommunications Engineer of the Ministry of Aviation, will be among special guests.

QUADRUPLE-PLAY TAPE AT AUDIO FAIR

At this year's Audio Fair, soon to be held at the Russell Hotel in London, Kodak will be demonstrating their P.400 quadruple-play tape. This demonstration, to be illustrated by colour slides, will emphasise the superior low-speed performance obtainable from what Kodak's claim to be the world's first quadruple-play tape.

Other Kodak tapes will be seen and heard at their stand, including the P.300 triple-play tape.

A DELICATE TOUCH

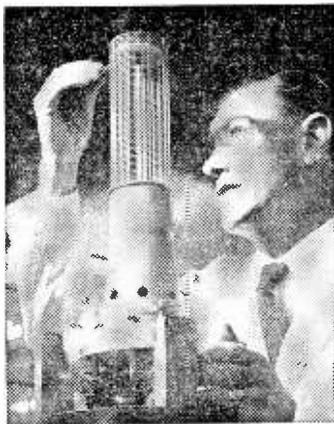

This STC technician's task (left) is a delicate one. He is lining up the cage grid of a powerful radio broadcast valve which has been manufactured at the Paignton works of Standard Telephones and Cables Limited.

From this same plant—Devon's biggest industrial unit—STC ship tubes, capacitors and thin-film circuits to the markets of Australia, South Africa, Brazil, India, the USA and many European countries.

TINY, TINY CAPACITORS

Solid electrolyte tantalum capacitors from a new range recently introduced by Plessey-UK Limited are small, very small; smaller than a lighter flint in some cases.


Designated type 'M', the capacitors are available in values ranging from 0.047 μ F to 10 μ F, with working voltages of from 50V to 1.5V. Produced at the Dielectric and Magnetic Division at Towcester, Northants, the capacitors are expected to find application in many domestic circuits—hearing aids, paging systems, electric wrist-watches—where miniaturization is essential.

.. COMMENT

TRANSISTOR TRANSCEIVER FROM US

A new transistorized transceiver (shown below) made by Sideband Engineers, a unit of the Raytheon Company of the USA, offers the amateur single sideband communications on 80, 40, 20 and 15m. The receiver's circuit of 23 transistors, 18 diodes, a zener diode, a varactor diode and only three valves, ensures cool operation with less battery drain when run mobile. The basic receiver (model SB-34) uses a built-in power supply for either 117V a.c. or 12V d.c. and has a sensitivity of $1\mu\text{V}$ for 10dB signal-to-noise ratio.

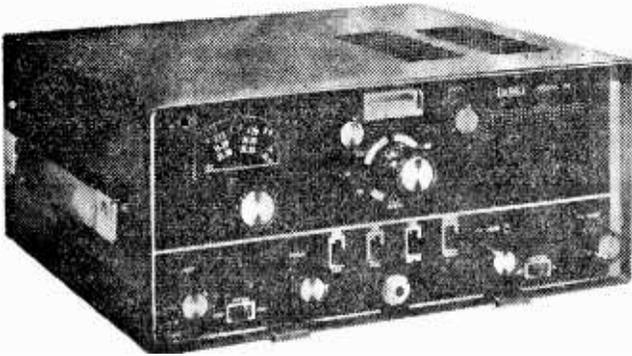Several advanced tuning devices are included for convenient dial calibration, quick frequency shift, smooth vernier adjustments, etc. Full specifications of the SB-34 are available from Cossor Communications Co. Ltd., The Pinnacles, Elizabeth Way, Harlow, Essex.



14-YEAR-OLD GIRL GETS LICENCE

Fourteen-year-old Elizabeth Allen of Westport, New Zealand, is likely to put every 'pirate' operator in the world to shame, for only two days after her 14th birthday, she received her amateur radio transmitting licence and callsign. This makes Elizabeth the youngest licensed amateur of either sex in her own country, which must be an embarrassing fact for young male aspirants in many countries, but especially so for those in New Zealand.

In fact it was the volume of letters published in P.W. for and against the R.A.E. that prompted reader Robert Turnbull of New Zealand to send the Editor the newspaper account of Elizabeth's achievement.

Apparently amateur radio runs in the Allen family as both Elizabeth's parents are licensed hams. Now she is continuing the line by building her own transceiver, soon to be on the air under the callsign ZL3AA1.

NEW STYLE PORTABLE

The latest medium and long wave portable from Roberts Radio Co. Ltd. (Molesey Avenue, West Molesey, Surrey) employs new cabinet styling in teak and black 'Rexine'. The 7-transistor circuit incorporates a 1W transformerless output stage, driving a 7in. x 4in. loudspeaker. The new receiver, model R404, joins the R300 and R500 in the Roberts range of portables at a retail price of 17 guineas.

more News and Comment

Amazing Change

I RECENTLY acquired most of the copies of P.W. dating from about 1950-59. I expected them to be somewhat different from ones which I have been getting for the last few years, but I was totally unprepared for the amazing change in the articles and general style. The old issues were completely uninteresting, dealing mainly with clumsy valve medium wave receivers and other dull projects. Modern P.W. articles offer a vast variety of general electronics as opposed to radio.

Also, in earlier issues, advertisements appeared offering transistors at 25s. or more, which I can now obtain for less than 1s.

All these things combined with the huge purchase tax on radio equipment of about 1950, brings me to the conclusion that although I spend a considerable amount of my time on radio and electronics, and intend to take it up as a profession, had I been born 10 years earlier, I doubt if I would ever have considered spending my time on radio.

L. Ruddock.

Co. Fermanagh,
N. Ireland.

We would disagree with Mr. Ruddock's point of view that bygone issues of P.W. were uninteresting, as for the radio enthusiasts of the time P.W. brought them data and designs which, unlike transistor circuits of today, were hard to come by. However, thanks for the compliment. — Editor.

P.W. and P.T. Issues

I SHALL be going abroad at the end of May or June, and I am willing to offer my issues of P.W. and P.T. of the last four years and certain issues of Radio Constructor, to other readers of your magazine.

I must stress, however, that ample postage and a stamped addressed envelope must be sent with requests for copies. First come will be first served and postage will be returned if the copy is not available.

4200894 Sac. White, R. W.

Fire Section,
R.A.F. Ballykelly,
Limavady,
Co. Derry, N. Ireland.

on page 52

Pin R.....L.W.=6,M.W.=2,S.W.=4

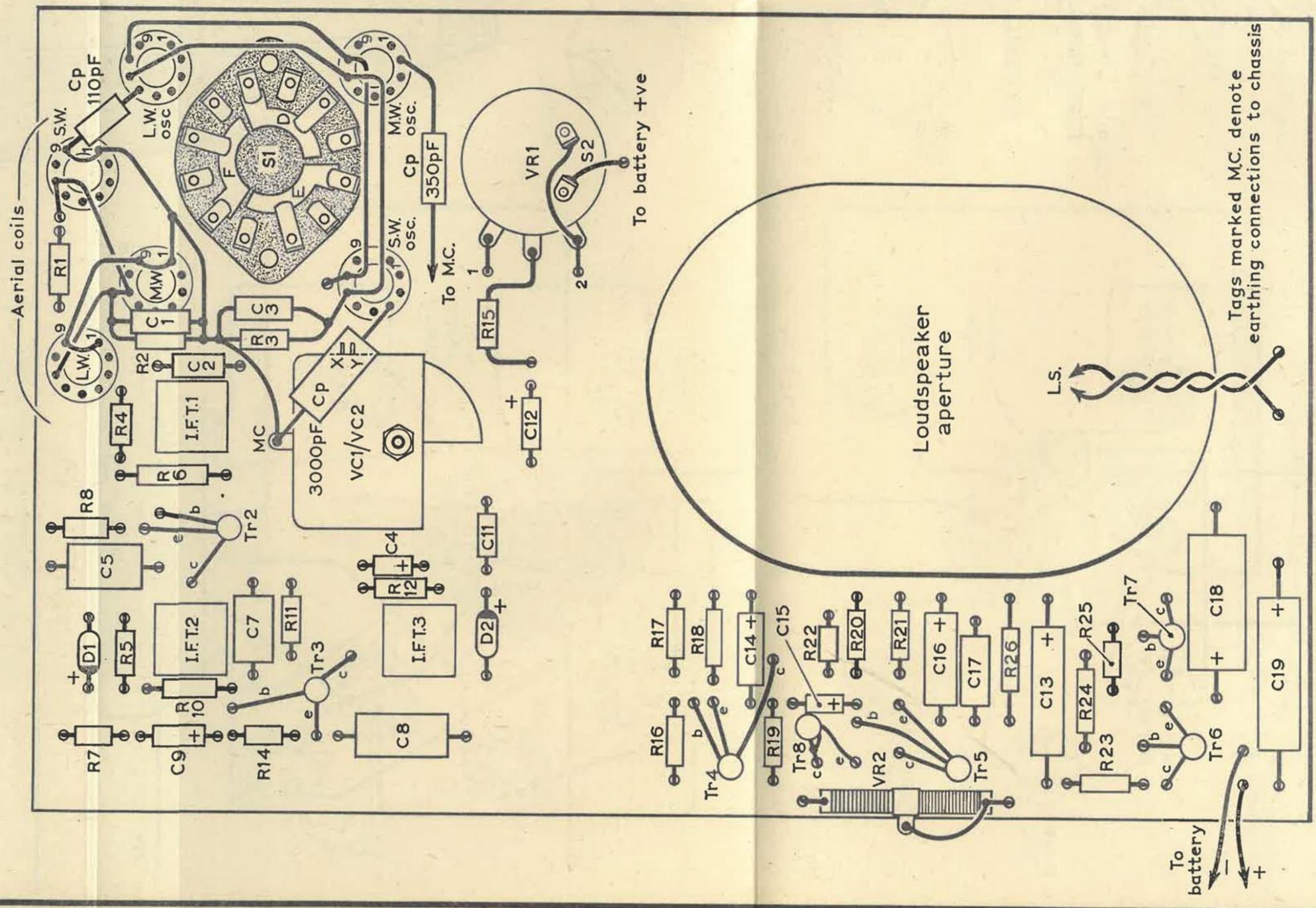


FIG. 2

CP.....L.W.=110pF, M.W.=350pF, S.W.=3000pF

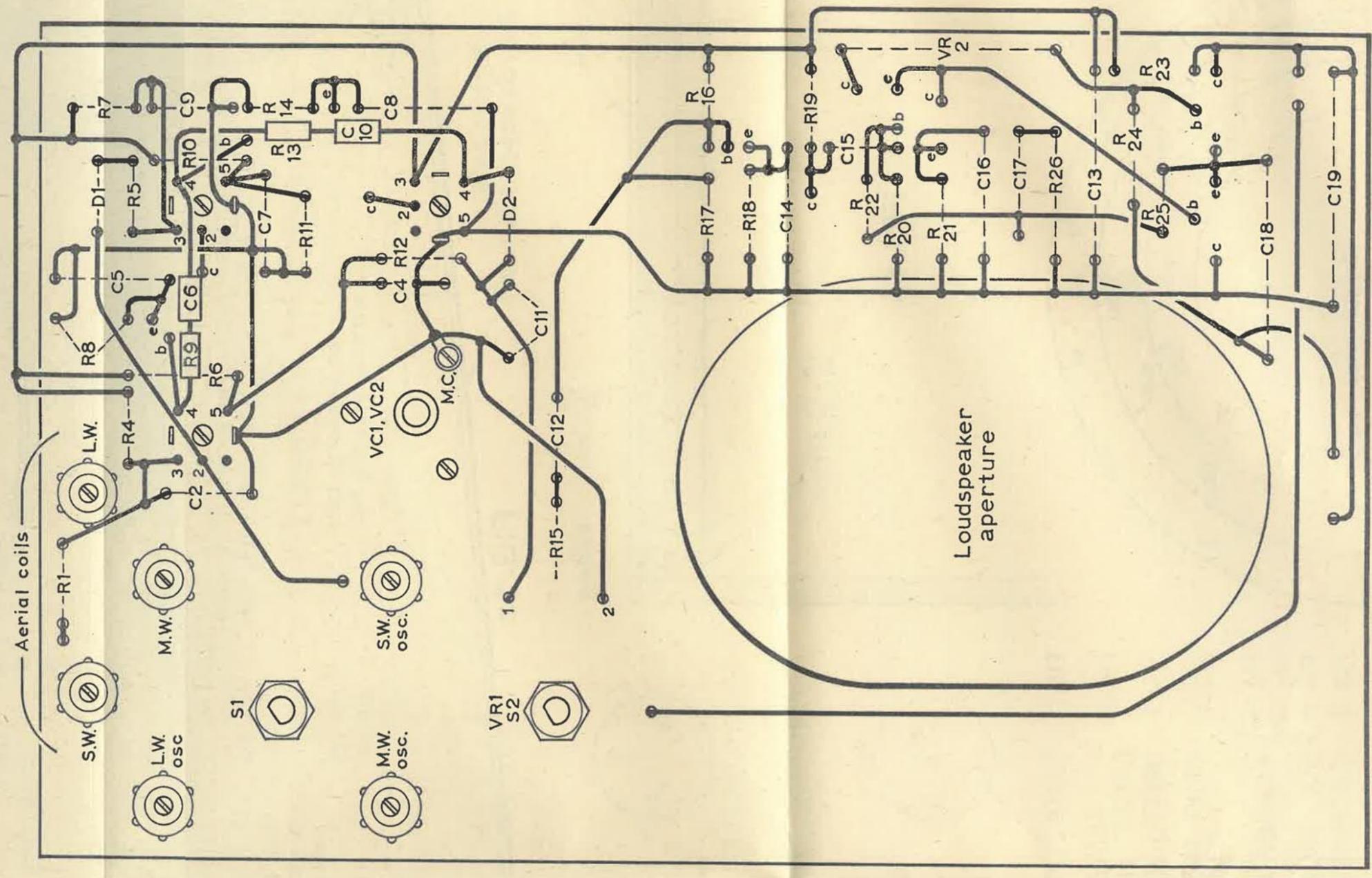


FIG. 3

COMPONENTS LIST

- Resistors:**
 R1 10kΩ R14 1kΩ
 R2 2.7kΩ R15 2.2kΩ
 R3 1kΩ R16 56kΩ
 R4 1.2kΩ R17 10kΩ
 R5 680Ω R18 1kΩ
 R6 68kΩ R19 3.9kΩ
 R7 2.2kΩ R20 2.2kΩ
 R8 680Ω R21 120Ω
 R9 1.2kΩ R22 4.7kΩ
 R10 22kΩ R23 680Ω
 R11 4.7kΩ R24 680Ω
 R12 8.2kΩ R25 4.7kΩ
 R13 3.9kΩ R26 270Ω
 All 10% 1/4W miniature carbon
 VR1 5kΩ log. potentiometer, with switch, S2
 VR2 50Ω variable 'slider' resistor, w.w.
 (Home Radio)

- Capacitors:**
 C1 0.01μF miniature paper 150V
 C2 0.01μF miniature paper 150V
 C3 0.01μF miniature paper 150V
 C4 8μF electrolytic 6V
 C5 0.25μF miniature paper 150V
 C6 56pF silver mica 2%
 C7 0.1μF miniature paper 150V
 C8 0.25μF miniature paper 150V
 C9 2μF electrolytic 6V
 C10 18pF silver mica 2%
 C11 0.01μF miniature paper 150V
 C12 2μF electrolytic 6V
 C13 100μF electrolytic 12V
 C14 50μF electrolytic 6V
 C15 2μF electrolytic 6V
 C16 100μF electrolytic 6V
 C17 50μF electrolytic 6V
 C18 250μF electrolytic 15V
 C19 100μF electrolytic 12V
 CP Coil-set padder: 110pF for l.w.; 350pF for m.w.; 3,000 pF for s.w.
 VC1, VC2 365-365pF slow-motion twin-gang variable (Jackson 02)
 TC1 60 pF trimmer
 TC2, 3, Bank of six 60pF compression trimmers (Denco)

- Inductors:**
 IFT1, 2 470kc/s i.f. transformers (Denco IFT13)
 IFT3 470kc/s i.f. transformer (Denco IFT14)
 L1 Transistor aerial coils (Denco Blue coils ranges 1, 2 and 4)
 L2 Transistor oscillator coils (Denco Red coils, ranges 1, 2 and 4)

- Semiconductors:**
 Tr1 OC170 Tr2 OC45 Tr3 OC45
 Tr4 NKT275 Tr6 NKT271 } Newmarket
 Tr5 NKT278 Tr7 NKT773 } matched
 Tr8 NKT279. S1 thermal diode } set
 D1 OA79 or GD9
 D2 OA70, OA81 or GD9

- Cabinet Materials:**
 3/8 in. 3-ply wood 12 3/8 in. x 4 in. ... 2 off
 3/16 in. 3-ply wood 6 3/4 in. x 4 in. ... 2 off
 1 1/2 in. x 6 3/4 in. hardboard panels ... 2 off
 1 1/2 in. length 1/4-round beading ... 2 off
 7 in. length 1/4-round beading ... 2 off
 4 ft. length 1/4 in. x 1/4 in. stripwood

- Miscellaneous:**
 S1 3-way, 6-pole, 2-wafer rotary switch
 S2 On/off switch on VR1
 15Ω 4 in. x 7 in. loudspeaker. Telescopic aerial.
 6 1/2 in. x 10 1/2 in. piece of paxolin. Battery plug.
 Aerial socket. Flex, knobs, etc.



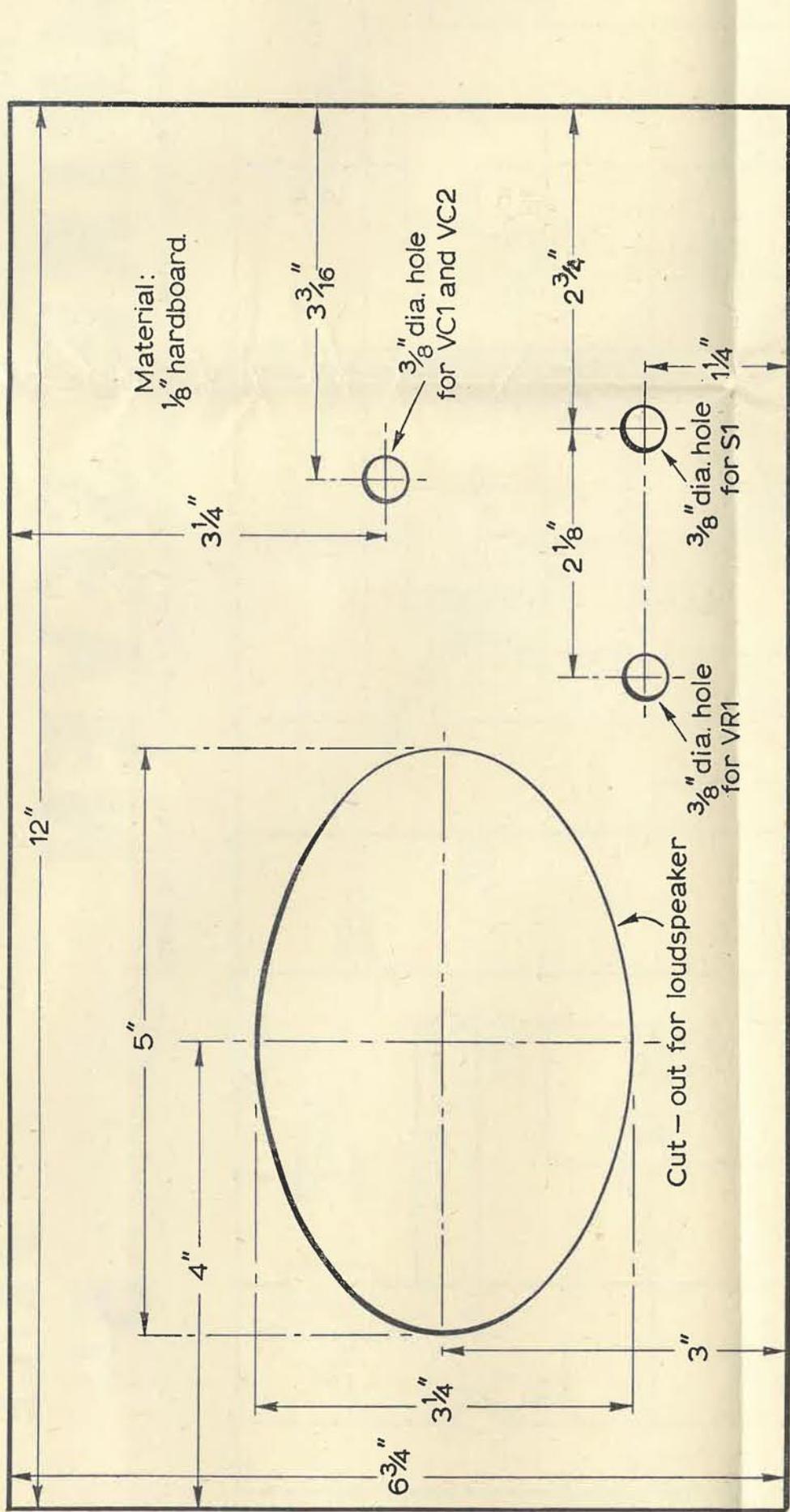


FIG. 4

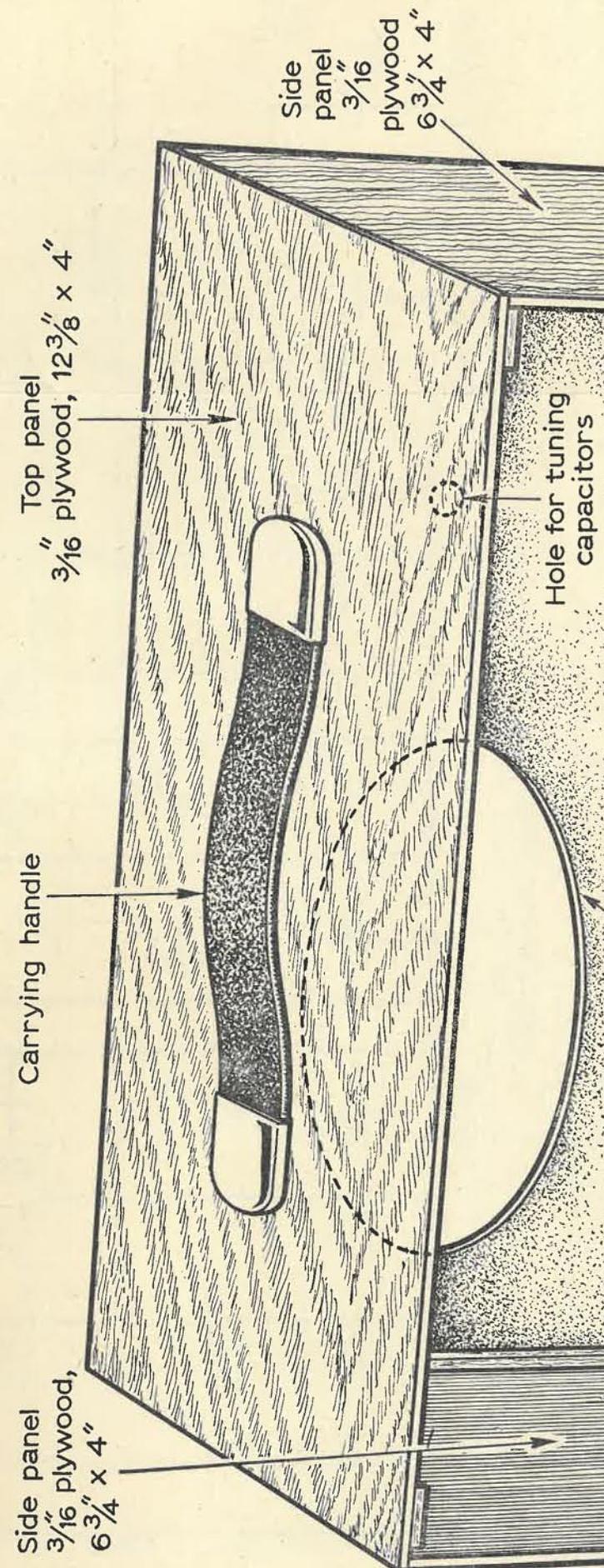

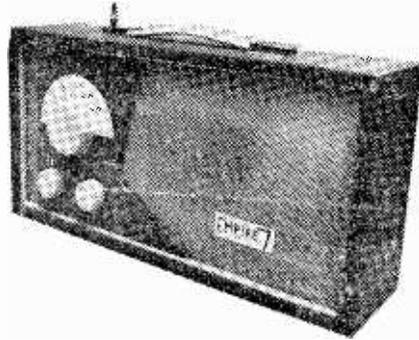

efficiency with powerful signals. Bias for this diode is obtained from the voltage drop in R7. When signal levels exceed the bias voltage the diode conducts, reducing gain and preventing overloading on strong signals.

Tr2 and Tr3 are intermediate frequency amplifiers fed by the 465kc/s transformers i.f.t.1, i.f.t.2. C6 and R9 neutralise feedback over Tr2, while C10 and R13 provide neutralising for Tr3. This is to avoid instability (oscillation) in the i.f. amplifier.

Diode D2 provides demodulation and automatic volume control at lower signal levels. When a strong signal is received a positive voltage is developed

across VR1 and applied to Tr2 base through R12 and i.f.t.1 secondary. When this bias increases, the gain of Tr2 is reduced. This helps to maintain a more stable output from the loud-speaker with changes in signal strength due to fading.

The audio output is taken from the slider of VR1 to the first audio amplifier Tr4. The amplified output is taken through C15 to the driver transistor Tr5.

Push-pull output is provided but no transformer is necessary because Tr6 and Tr7 are a matched

THIS receiver uses ten semiconductors in all, and covers long, medium and short wavebands. It should be of particular interest to constructors who want short-wave coverage of the most popular frequencies in addition to reception on the normal long and medium bands. Good reception is obtained with the telescopic aerial which is fitted. An external aerial may be connected instead when wanted. This is useful if the receiver is taken in a car as screening by the vehicle then usually makes the external aerial essential.

The EMPIRE 7

by F. G. Rayer

This month's Blueprint design—a 7-transistor portable receiver covering long, medium and short wave-bands.

The whole receiver is self-contained and of similar size to that of popular non-miniature transistor portables.

The receiver circuit is shown in Fig. 1 and a few details on this should be helpful. Each wave-band uses its own aerial and oscillator coils (coils for one band only appear in Fig. 1). This has the advantage that each band can be dealt with separately when trimming. A three-way switch selects the required pair of coils and there are six coils in all. The three "blue" coded coils are for aerial tuning, while the three "red" coils are for oscillation. Each coil has its own trimmer, a small six-bank trimmer strip being used for this purpose.

When wiring up it will be noted that all the aerial coils have the same pin connections, so connections are duplicated for each band. With the oscillator coils pins 1, 5, 7, 8 and 9 are also the same for each coil. However, the padding capacitor pin P is different on each coil. This is pin 6 for long waves, pin 2 for medium waves and pin 4 for short waves. The padding capacitor CP also has to be different for each coil—110pF for l.w., 350pF for m.w. and 3,000pF for s.w.

Transistor Tr1 is an OC170 and functions as a self-oscillating mixer. Diode D1 is a clamp diode greatly increasing the automatic volume control

pnp and npn output pair, driving the 15Ω speaker direct. This type of circuit has a low current consumption and gives very good reproduction. The thermal diode Tr8 is a diode-connected thermal transistor to stabilise working conditions and it is used in conjunction with the miniature pre-set slider potentiometer VR2 so that operating conditions can be set to optimum when first using the receiver. Transistors Tr4, Tr5, Tr6, Tr7 and the thermal diode Tr8 may be obtained in a matched set. This assures that operating conditions in this part of the receiver will be correct.

The capacitor C18 feeds the speaker, which is a 7 x 4in. or similar oval unit (a circular speaker can be used equally well if to hand). Feedback to Tr5 base is through R22 and R25.

COMPONENT TOLERANCES

Most transistors have the base voltage set by two resistors as a potential divider. For example, R1 and R2 for Tr1 or R10 and R11 for Tr3, etc. Proper working conditions will be obtained for transistors of the type given if, 10% tolerance resistors are fitted. All such resistors have a silver band in addition to the colour coding showing the value. Emitter bias is also used (R3 for Tr1, R8

for Tr2, etc.) and this further helps stabilise working conditions.

With bypass capacitors the values are not very important but should not generally be smaller than shown. There will be no change in results if near values or larger capacitors, already to hand, are fitted. Other capacitors, notably C3, C6, C10 and all padders, should be of the value indicated.

SECTIONAL TEST

The receiver may be built completely before testing. Alternatively, part may be tested when wired.

Initially, coils for one waveband only may be connected. Coils for the other ranges can then be added after satisfactory results are obtained on the first range. This greatly reduces chances of errors in connecting the wavechange switch.

When Tr1, Tr2 and Tr3 stages are wired up to R15, this section of the receiver may be tested by wiring medium impedance phones from R15 to positive line and connecting a 6V battery across C13 (observe polarity). The first three stages should draw 2-3mA. The i.f.t.s and coils may be roughly aligned for good phone reception.

If the a.v.c. circuit from D2 is in order, battery current will drop slightly when a strong signal is tuned in.

The clamp diode circuit can be checked by temporarily leaving D1 and R5 disconnected. If a strong signal is tuned in, volume should fall considerably when D1 and R5 are joined. But joining D1 and R5 should make no difference to the volume of a weak signal.

When the first stages are found to work correctly the audio amplifier from C12 may be wired.

CONSTRUCTION: PANEL

The receiver is built on a 10½ x 6½ in. paxolin panel which has a cut-out to clear the loudspeaker magnet. It is best to drill all large holes first, checking that components fit as this proceeds. Many small holes, for resistors and other small items, can also be made, using a ⅛ in. drill.

If any small holes are missed these can be drilled after wiring has begun. But at this stage care is needed so that fragments of paxolin do not get into the wavechange switch or elsewhere.

The gang capacitor has an integral reduction drive and it is secured with three 4BA bolts. These bolts must be very short or have extra washers or nuts under their heads so that they only project the thickness of the capacitor frame. A soldering tag under one bolt is an earth return (MC) connecting point.

The coils fit in holes and are held with a finger nut which should not be tightened with too much force. All coils have nine pins as shown in Fig. 2.

REAR OF PANEL

Fig. 2 shows components on the panel. The wire ends of resistors and capacitors are bent to pass through the holes and are then spread to keep these items in position. All the electrolytic capacitors (2µF to 250µF) have positive and negative ends which are placed as shown. It is best to leave the transistors and coils until last.

VR2 has a short piece of thin flex soldered from

its slider to one outer tag. The i.f. transformers are held by spreading the tags which are attached to the screening cans.

The easiest method of construction is to insert a number of components then turn the panel over and connect them. It is suggested that the outline of each part is marked with coloured pencil as it is inserted. Each connection is marked in the same way when it is soldered. This takes only very little time and shows at once what remains uncompleted. If it is done systematically there is no likelihood that a connection will be overlooked or some other error made.

PANEL WIRING

All connections on the front of the panel are shown in Fig. 3. Some 26s.w.g. tinned copper wire with 1mm sleeving can be used throughout. Joints should be soldered quickly and the iron removed as lengthy heating is unnecessary and may damage parts.

One tag of each i.f. transformer screening can is joined to the earth line which returns to the tag MC. This tag is held by a bolt fixing the ganged capacitor. The i.f. transformers have five tags with wide spacing between tags 4 and 5, so connections will be correct if the pins are located as in Fig. 3. A ¼ in. hole is needed under each transformer so that the core can be adjusted.

The neutralising components R9 and C6 are soldered together and taken directly from pin 4 of the first i.f.t. to pin 4 of the second i.f.t. C10 and R13 are similarly joined between pin 4 of the second i.f.t. and pin 4 of the final i.f.t.

The diodes D1 and D2 have positive and negative ends which are placed as in Fig. 2. Leave the wires at least ¼ in. long and solder quickly to avoid damage from excessive heat.


Battery leads are anchored in holes near the top of the panel. Thin black flex is used for negative and red flex for positive as it is most important that polarity is correct. With the 7-5V type of battery a two-pin plug is required and the large pin is positive. The receiver may be run from a 9V battery if preferred.

Tr1 is best left until coils are wired. Tr2 and Tr3 both have a red spot to identify the collector. A piece of sleeving about ¼ in. long can be placed on each centre lead (base) and the wires are then threaded through in the positions shown in Fig. 2. The panel is turned over and the leads cut and soldered. Tr2 emitter goes to C5 and R8. Tr3 emitter is taken to C8 and R14. Each base wire goes to pin 4 of the adjacent i.f.t. Each collector is soldered to pin 2 of the next i.f.t. There is no need to cut any of the transistor leads very short.

All transistor wires may, however, be left almost full length, sleeving being placed on connections as required. There is little danger of damaging the transistors from excessive heat if the wires are long and the connections are soldered quickly.

Tr4 base goes to R16 and R17. Emitter goes to C14 negative and R18, with collector to R19 and C15 negative.

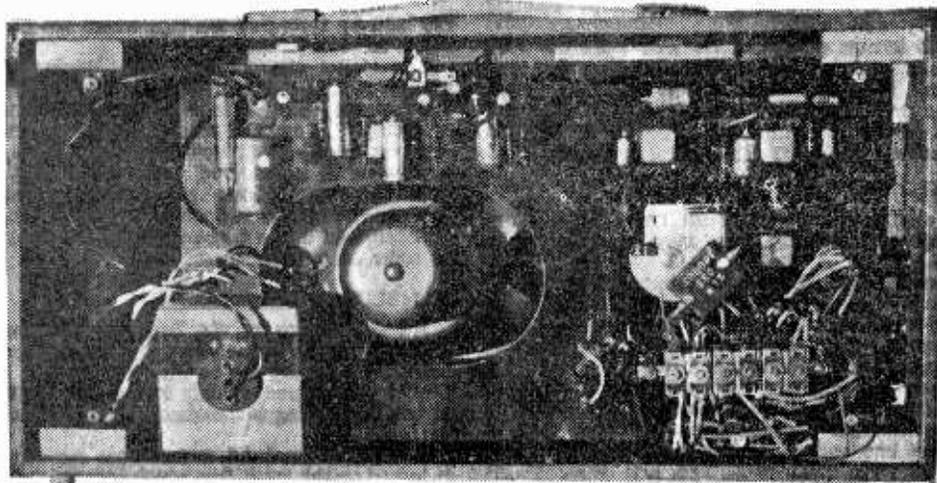Tr5 base is taken to R20 and R22, with emitter to R21 and C16 negative. Tr5 collector goes to the base of Tr7 and emitter of the thermal diode Tr8. Base and collector wires of the thermal diode are joined by the maker, so this item has



A look into the back of the completed receiver. This view shows clearly how the cut-out on the panel fits round the loudspeaker cone. At the bottom-right of the panel can be seen the bank of six trimmers which is mounted on bolts, above the wave-change switch.

only two long leads. The lead marked C goes to VR2.

When soldering in Tr7 note that this is of npn type. The arrow still indicates emitter though pointing away from the base. Collector goes to positive line. Tr6 collector goes to negative, with base to R24 and VR2. Tr6 and Tr7 emitters are joined and go to positive on C18 and R25.

SETTING VR2

This is pre-set to allow best possible working. Initially move the slider so that no resistance is in circuit (fully towards R19 in Fig. 2). The slider is then moved along until the output transistors take 1.5mA to 2mA with no signal tuned in.

This adjustment will not normally be made until the receiver is ready to test and the speaker must be connected. The setting of VR2 is not critical.

COIL CONNECTIONS

Fig. 2 shows coil connections, excluding those to the switch. The oscillator coils are red and the aerial coils blue. Insert each coil with pins 1 to 9 as shown. Pins 7 on the three oscillator coils are then joined. R3 and C3 are soldered to pin 7 of the short wave coil and to a lead which passes to the gang capacitor frame tag. These leads and connections to switch and coils should be short and direct.

Pins 7 on the aerial coils are also joined and go to C1 and R2. Pins 1 and 9 on each aerial coil are joined and returned to the earth line MC at the capacitor.

Each oscillator coil has a different padder capacitor and the connection is to a different pin. This is shown in Fig. 2. The 3,000pF s.w. coil padder goes from pin 4 to MC. Leads should be quite short. The m.w. padder is 350pF and from pin 2 to an earth return point. The l.w. coil

requires a 110pF padder from pin 6 to a convenient earth return.

Note that a lead goes from pin 7 of the s.w. aerial coil to R1, which is fixed to the panel.

SWITCH CONNECTIONS

These are shown in Fig. 7 and the front wafer (that nearest the paxolin panel) is best wired first. In Fig. 7 the front wafer is shown in the upper sketch and in the m.w. position.

Leave a few inches of connecting wire projecting from pin 6 of each aerial coil and from pin 1 of each oscillator coil circuit. These leads are later taken to the trimmers.

The rear wafer is wired last. Tr1 is first soldered to the contacts. This transistor is placed over the centre of the switch so that leads are quite short. Emitter, base, screen and collector leads are marked E, B, S and C in Fig. 7, the space coming between S and C wires.

The screen wire (S) is soldered to the earth return to MC on the gang capacitor.

TRIMMERS

The six-band trimmers (TC2/TC3) are mounted about 1½ in. from the panel, using two 6BA or 4BA bolts 2 in. long. Extra nuts are required on the bolts or spacing sleeves. A soldering tag is held under each nut and connected to MC at the gang capacitor. The earthed tags should be those which come from the top plates of the trimmers.

The projecting leads are then cut to length, covered with sleeving and soldered to the trimmers as in Fig. 7.

METER TEST

A meter may be included in one battery lead when first testing the receiver. This should show about 10mA with no signal or with low volume if a 7.5V supply is used. Current will be slightly

higher with a 9V battery. With good volume, current will rise to about 20-30mA, this depending solely on the volume chosen.

If a high current is found the set should be switched off and a check made for short-circuits or wrong connections.

BAND COVERAGE

The coils are intended to give bands approximately as follows:

Long waves.—150-400kc/s or 2,000-750m.

Medium waves.—515-1,545kc/s or 580-194m.

Short waves.—5-15Mc/s or 60-20m.

These coverages are with a twin-gang 315pF capacitor. The gang capacitor listed has a maximum value of 365nF and is chosen because of its small size and reduction drive. This means that band coverage at the low frequency end of each band is slightly increased.

I.F. ALIGNMENT

If no signal generator is available tune in any station and rotate the i.f. transformer cores for best volume. A completely insulated tool, such as can be made from a plastic knitting needle, should be used for all adjustments.

If a signal generator is available set it to give a 465kc/s modulated output. Inject this at the base of Tr3 and adjust i.f.t.3 core. Then inject at the base of Tr2 and set i.f.t.2 core for best response. Finally apply the signal at the base of Tr1 and adjust i.f.t.1 core.

An accurate indication of output can be obtained by having a meter in one battery lead and adjusting VR1 so that current rises to some 20mA or so as adjustments are peaked for best results. This is more accurate than adjustments by ear.

When the i.f.t.s have been aligned they do not need any further attention and should be left alone.

COIL ALIGNMENT

Each range is treated separately and it is probably best to do the m.w. range first. Adjustments are most easily carried out in two steps: (1) Band coverage, (2) tracking.

(1) If a signal generator can be used couple it to the aerial socket of the receiver through a 400Ω resistor or place a lead from the generator near the receiver aerial. Open the gang capacitor, set the generator to 1,545kc/s and adjust the m.w. trimmer TC3 until the signal is tuned in. Then set the gang capacitor 10° from closed, tune the generator to 515kc/s and adjust the m.w. oscillator coil core until the signal is tuned in. Check at the h.f. end of the band, readjusting the trimmer slightly if necessary.

(2) Tune the generator to 1,390kc/s, tune in the signal with the receiver tuning knob and adjust the m.w. aerial circuit trimmer TC2 for best reception. Then adjust the generator to 566kc/s, again tune in the signal with the receiver and adjust the m.w. aerial coil core for best results. Repeat as before, since one adjustment is modified to some extent by the other.

For l.w. alignment adjust coverage for 150-400kc/s and track at 165kc/s and 370kc/s. The trimmers are l.w. TC3 and l.w. TC2.

For the s.w. band adjust coverage for 5-15Mc/s and track at 5.5Mc/s and 13.5Mc/s. The trimmers are s.w. TC3 and s.w. TC2.

When making adjustments to the s.w. band it will be found that aerial trimming slightly modifies the oscillator tuning, so the receiver control knob should be adjusted to keep the signal in tune.

If alignment is carried out by ear first choose strong stations near the ends of the band to allow approximate adjustments. Adjust the trimmers at the h.f. end of the band (capacitor nearly open) and the coil cores at the l.f. end (tuning capacitor nearly closed). Afterwards find weak stations and repeat the adjustments until no further improvement is obtained.

When aligning do not use a long aerial as this makes adjustments difficult. Accurate tuning points will more easily be found with the aerial only slightly extended. Final alignment is with the aerial fully erected.

On the s.w. band, reception is possible with the aerial circuit tuned above the oscillator frequency. This is the second channel or image frequency and is not required. It will not be encountered if the oscillator circuit trimmer (s.w. TC3) is opened and the aerial circuit trimmer (s.w. TC2) is screwed down in advance. Also begin with the s.w. oscillator coil core somewhat unscrewed so that adjustment is approached from the high-frequency position. When adjustment is correct (oscillator on the h.f. side of the aerial frequency) image frequency reception of the signal generator or a strong station will arise at 930kc/s (2 x 465kc/s) points higher in frequency than the correct tuning point and at reduced volume.

CABINET FIXING

The receiver requires a cabinet a little larger than 10½ x 6in. inside to give clearance and 3in. deep internally. Ready-made cabinets may be adapted. If necessary new holes can be cut for the control spindles and old holes may be obscured with a fingerplate of coloured plastic or paxolin or other material.

The loudspeaker should be screwed to a baffle board which has an aperture to match the speaker cone. This board is then screwed inside the cabinet. Proper reproduction is not to be expected until the speaker is in its cabinet.

Strips or blocks of wood are glued and screwed inside the cabinet so that the paxolin panel can rest against them.

The tuning capacitor spindle is in two sections and the pointer is attached to the rear part. A standard ½in. diameter hole knob fits the front part of the spindle.

The telescopic aerial may be screwed to the outside of the case or it may be fixed inside and drawn up through a hole. The aerial lead goes to one fixing screw.

A socket for an external aerial can be added at the back or anywhere convenient. To maintain reasonable selectivity in the aerial tuned circuit the trimmer TC1 is added in series with the socket lead. A fixed capacitor of about 15pF to 25pF may be used here instead. ■



designing a MULTIMETER

by K. Berry

Theory, Design and
Construction of
Simple Instruments

THIS article is intended to cover the theory and practice of multi-range meter design in its simpler forms.

The basis of this treatment is the moving coil meter. It is not proposed to go into details here regarding the principles of operation and construction of such meters since this may be found in any text-book covering electricity and magnetism.

The usual proprietary moving coil meter movement is a low resistance device and is capable of measuring a certain maximum current, this current is known as the full-scale deflection (f.s.d.). A meter movement may be used as it stands to measure the current in a circuit, but more often than not, it will be used with a resistor (known as a "shunt") connected in parallel with it, for measuring currents which are greater than the full-scale deflection, or, alternatively, with a resistor connected in series with it (known as a "multiplier") for measuring voltages. It is the latter use which will be considered first.

Voltage Measurement—D.C.

If a typical moving coil meter, having a full scale deflection of 1mA and a resistance of 100Ω is used as a voltmeter, then the potential across the meter when a current of 1mA is flowing through it will be (by Ohm's Law) $100 \times 0.001V = 0.1V$. That is to say, the meter will read 0–100mV. If now a resistor of 900Ω is connected in series with the meter, and the whole is used as a voltmeter, then when a current of 1mA is flowing, the potential across the meter and resistor will be $(100 + 900) \times 0.001 = 1,000 \times 0.001 = 1V$, i.e. the meter will read 0–1V. The combined resistance of the meter and its series resistor (multiplier) is 1,000Ω, and this results in the meter reading 1V full scale.

This can be expressed by saying that the meter has a sensitivity of "1,000Ω per volt", and this is normally written "1,000Ω/V". Thus if it is desired to make such a meter read 0–1,000V, the meter must be connected in series with a multiplier whose resistance is such that the combined resistance of the meter and multiplier is $1,000 \times 1,000 = 1M\Omega$. Since the meter resistance is 100Ω, the multiplier resistance required is 999,900Ω. This is

obviously so near to 1MΩ, that this is the value of multiplier which would be used in practice.

It will be seen therefore, that if a meter is required to read "X" volts at full scale, the value of the multiplier required is simply "X" times "the Ω/V" of the meter concerned. The resistance of the meter itself may be ignored if it is less than 2% of the calculated multiplier resistance. The "Ω/V" of a meter is simply the reciprocal of its full scale deflection in amperes, i.e. $f.s.d. = 1mA$

$= 0.001A$, hence $\Omega/V = \frac{1}{0.001} = 1,000\Omega/V$. The

number of ohms/volt required for multipliers for some common meters is listed below.

Meter F.S.D.	Ω/V
10mA	100
5mA	200
1mA	1,000
500μA	2,000
100μA	10,000
50μA	20,000

For measurement on radio and electronic equipment, the lowest resistance normally acceptable is 1,000Ω/V, and higher values than this are, in fact, to be preferred.

Current Measurement—D.C.

If a typical moving coil meter having a full-scale deflection of 1mA and a resistance of 100Ω is used as an ammeter it will measure a current of up to 1mA only. If it is desired to measure a current in excess of this, then a resistor must be connected in parallel with the meter to shunt or divert some of the current in the circuit. For example, if this meter is required to measure 10mA full scale, then a resistor must be connected in parallel with it of such a value that 9mA will flow through the

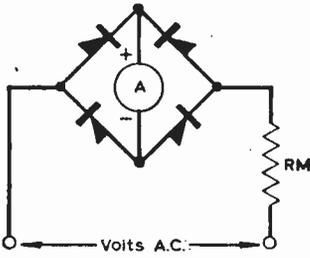


Fig. 1: The basic rectifier voltmeter bridge.

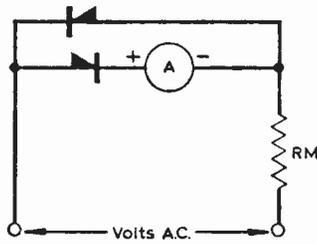


Fig. 2: An alternative half-wave rectifier voltmeter.

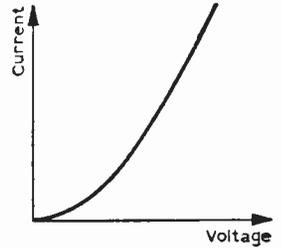


Fig. 3: The characteristic curve for a typical rectifier.

resistor when 1mA flows through the meter, hence the shunt (resistor) must be 1/9th of the meter resistance = $\frac{100}{9} = 11.1\Omega$. To read 100mA full scale,

the shunt resistor would have to be 1/99th of the meter resistance, i.e. $\frac{100}{99} = 1\Omega$ (approximately).

The value of shunt required is thus given by the following expression:

$$R_s = \frac{\text{meter resistance} \times \text{meter f.s.d.}}{\text{required f.s.d.} - \text{meter f.s.d.}}$$

It will be seen from the two examples quoted above that if the meter f.s.d. is small compared with the required (or shunted) f.s.d., i.e. 1% or less, then the resistance of the shunt is given with sufficient accuracy by the expression:

$$R_s = \frac{\text{meter resistance}}{\text{required f.s.d.}} \times \text{meter f.s.d.}$$

Voltage Measurement—A.C.

A moving coil meter gives a reading which is proportional to the average current flowing through it. Since with alternating current, the average value (over one cycle) is zero, the meter will give no reading when connected to an a.c. supply. To use a moving coil meter to measure a.c. it is necessary to use a rectifier to convert the a.c. into a direct or unidirectional current which can be measured by the meter.

The usual circuit is the bridge rectifier circuit. The meter is directly connected to the d.c. terminals of the bridge, while the a.c. terminals of the bridge are connected to the voltage to be measured via the usual multiplier (Fig. 1).

An alternative circuit uses only two rectifiers instead of the four required for a rectifier bridge. The meter is connected in series with one diode, whilst the other diode is reverse-connected across the meter and diode combination. The whole is connected in series with a multiplier (Fig. 2).

The resistance of the multiplier required for a.c. measurements is different to that required for d.c. measurements. There are two reasons why this should be so.

The first, is that because the meter gives a reading which is proportional to the average current flowing, but a.c. voltmeters are normally calibrated in r.m.s. volts. The r.m.s. value of a.c. is 1.11 x the average value, or rearranging this:

$$V \text{ average} = \frac{V \text{ r.m.s.}}{1.11}$$

Thus to obtain a meter reading in volts r.m.s. it is necessary to reduce the resistance of the multiplier by 1.11. For example, a meter with an f.s.d. of 1mA requires a multiplier of 100kΩ in order that it may read 100V d.c. full scale. The same meter with a rectifier would require a multiplier of $\frac{100}{1.11} = 90k\Omega$ in order that it may read 100V a.c. full scale (r.m.s.) using a bridge rectifier circuit.

The second reason for the difference compared with a d.c. multiplier is the resistance of the rectifier circuit. A further complication is that the impedance of the rectifier elements varies according to the current flowing in them.

A typical rectifier characteristic is shown in Fig. 3. The horizontal (x) axis is the voltage across the rectifier, and the vertical (y) axis is the current flowing through the diode. The shape of the curve at any point is a measure of the rectifier forward resistance at that point. It will be seen that as the current falls to zero, the shape of the curve becomes greater thus indicating a higher resistance.

This changing resistance of the rectifier results in non-linearity of the meter scale. Fortunately this defect can be overcome by certain methods, if this is essential. If the value of the multiplier is high compared with the resistance of the rectifier, then the latter is "swamped" and a linear scale results. This, obviously, only applies on the high voltage ranges. When it is desired to read, say, 10V full scale, a linear scale can be obtained by using a potential transformer, i.e. a voltage step-up transformer. This gives a high voltage output thus enabling a high resistance multiplier to be used. In view of the difficulty of designing and constructing such transformers no details will be given here.

A greater degree of linearity on low voltage ranges can be obtained by using the half-wave rectifier circuit shown earlier in Fig. 2. In practice, if the meter is calibrated at, say, 6.3V on the 10V

range, the error over the range 2—8V will be no worse than about 0.5V, i.e. the meter will read 10V when the actual voltage is 9.5. For most purposes this is not a serious complaint, as when measurements of a.c. voltages are made great accuracy is not generally required.

Germanium Diodes

Meter rectifiers are obtainable—these are made specially for this purpose and are usually of the copper oxide type. However, there is no reason why point contact germanium diodes should not be used, in fact the author always uses them himself. Suitable diodes are the Mullard OA70, OA71 or OA81.

It should be noted that the value of multiplier required to measure a particular voltage depends upon whether the bridge or the half-wave rectifier circuit is used. If the latter is used, the multiplier resistance will be about half of that required for use with the former.

The approximate value of multiplier for use with the bridge rectifier circuit is given by the

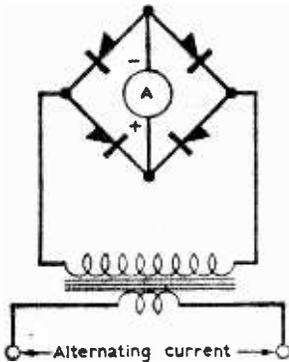


Fig. 4: A rectifier meter connected to a current transformer.

expression:

$$R_M = \frac{\text{required f.s.d. (volts)}}{\text{meter f.s.d. (amps)}} \div 1.11.$$

Current Measurement—A.C.

Whilst measurement of direct current with a moving coil meter is simply a matter of providing the required shunt, measurement of alternating current is not so simple. As was mentioned earlier, the impedance of a rectifier changes with the applied voltage hence the application of a shunt will just result in a variable shunting effect and consequently a non-linear scale. In any case, such a meter would have a voltage drop which would be unduly high for an ammeter.

The solution to this problem is the current transformer. This is in effect a step-up transformer, the large current to be measured is passed through the primary, and results in a small current at a higher voltage in the secondary. This is connected to the rectifier and meter (see Fig. 4).

The design of current transformers is not a simple matter. Considerable care is necessary to ensure that the transformer has a very low iron loss. This is achieved by running the core at a low flux density. In view of the difficulty of designing and constructing current transformers, no further details will be given here.

Resistance Measurement

Precise measurement of resistance is usually made by means of the Wheatstone bridge or its variants. However, in multirange meters, measurement of resistance is affected by more simple (though less accurate) means. The basic movement is connected in series with a dry battery, a fixed resistor, and a variable resistor (Fig. 5). The values of the resistors being chosen so that with the meter terminals short circuited, the meter reads full scale. This therefore is the reading corresponding to zero resistance in the external circuit.

If, for example, a meter with an f.s.d. of $100\mu\text{A}$ was connected in series with a 1.5V dry cell and suitable resistors the resistance required to give a full-scale reading would be $15\text{k}\Omega$, i.e. when $15\text{k}\Omega$ is connected in series with the meter and cell a current of $100\mu\text{A}$ will flow. If a further (external) resistance of $15\text{k}\Omega$ is connected into the circuit the meter will read $50\mu\text{A}$. The addition of yet a further $15\text{k}\Omega$ external resistance will cause the meter reading to fall to $33\frac{1}{3}\mu\text{A}$. In other words, the scale will be non-linear. In proprietary instruments the calculated resistance values will be printed on the scale but when one is making a multi-range meter with a standard meter scaled, say, from 0 to 100 units, it is best *not* to attempt to add a resistance scale by hand as this is a very difficult operation to effect in a neat manner and if done clumsily will completely spoil the appearance of the meter.

In any case the majority of the time, the resistance range of a meter is used just to check that a circuit or component is continuous and no knowledge of the magnitude of the resistance involved is required. In these cases where it is desired to measure the resistance of a component, if the meter reading is noted, a small calculation will give the required answer. For example, if the $100\mu\text{A}$ meter previously quoted was used (with a 1.5V cell) to measure the resistance of a component and a reading of $36\mu\text{A}$ was obtained, then the resistance of that component would be

$$\frac{1.5}{0.00036} - 15,000 = 44,500 - 15,000 = 29.5\text{k}\Omega.$$

However, if the prospect of an occasional calculation does not appeal or, alternatively, if one has a steady hand and plenty of confidence, then one can always calibrate the meter with a resistance scale.

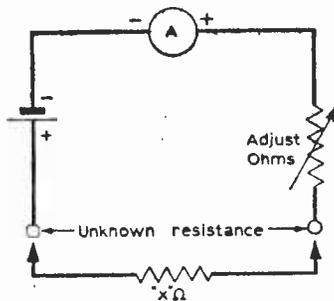


Fig. 5: The basic ohmmeter for resistance measurement.

Practical Multirange Meters

Having set out the methods by which the various quantities can be measured it is now proposed to consider some practical designs for multirange meters.

When embarking on the construction of a multirange meter for the first time there is a tendency to attempt to cover all the requirements that can possibly be thought of. Whilst this is a good idea in theory, in practice one finishes up with such a formidable design that either one baulks at the prospect of such a labour or else the job is begun but the task proves too much and the project is never completed. Accordingly, three multirange meter designs will be given. The first two are simple designs suitable for a beginner, whilst the last design is more complex and is more suited to the more experienced constructor.

Design No. 1


This is a simple multirange meter measuring both a.c. and d.c. voltages up to 500V, also resistance.

No current range is included and in consequence there is no switching. The accuracy on the lowest a.c. range is not high owing to the non-linearity of the rectifier elements as explained earlier. It is, however, a very useful general purpose testmeter and what it lacks in facilities it makes up for in its simplicity.

Specification

Voltage—D.C.	Voltage—A.C.	Resistance
0—5	0—10	3,000Ω mid scale
0—10	0—50	
0—50	0—100	
0—100	0—500	
0—500		

The meter used was an ex-Government 2in. round, 500μA meter scaled 0—500. The voltage ranges have been chosen so that the meter reading gives the actual voltage measured or else it is necessary merely to double the scale reading. This is a point worth noting when deciding on meter ranges. An ill-advised choice of full-scale voltage makes a meter more difficult to read. For instance, if a range of 0—20V was included it would be necessary to mentally multiply the meter reading by four and the average person will not find this to be very convenient.

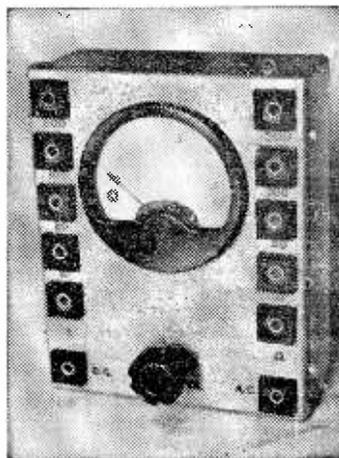

How the prototype of Design No. 1 looks when constructed and housed in a readily obtainable die-cast box.

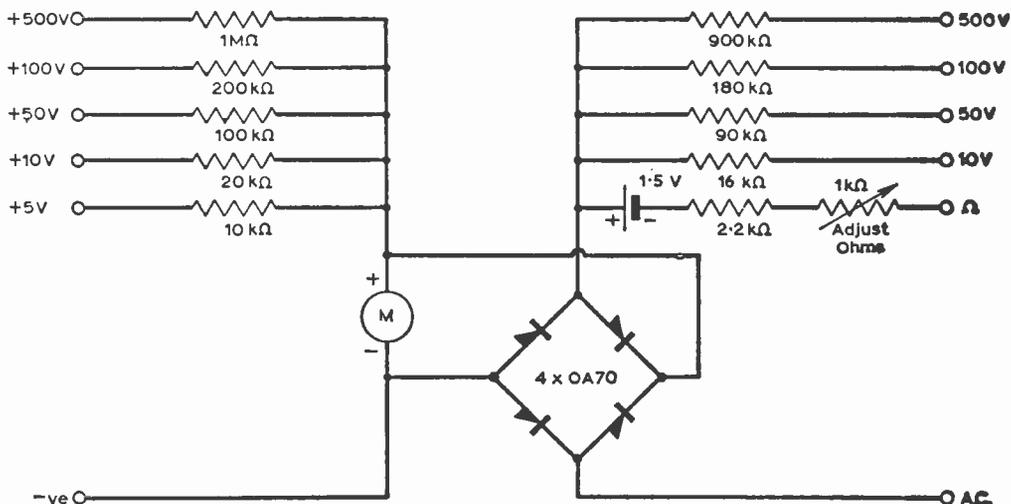


Fig. 6: The circuit of the simple multimeter of Design No. 1. This measures a.c. and d.c. voltages and resistance.

No details of construction have been given. The choice is left to the constructor. A meter made to this design is shown in the photograph. Access to the meter circuits is by means of sockets, an arrangement which gives a neat appearance, but terminals could be used if so desired. The circuit is given in Fig. 6.

The accuracy of the meter will depend upon the accuracy of the multipliers. For the d.c. ranges 1% or 5% high-stability resistors would be the most suitable. For the a.c. ranges it will probably be more convenient to use 10% composition resistors as the values required are non-standard and a series or parallel connection of two resistors will probably be needed. The values quoted for the a.c. ranges are only approximate, since the precise value will depend on the particular meter and rectifier used. The exact resistance required can be found easily by the following method:

Connect the meter to a suitable d.c. supply and adjust the supply voltage to 60% of the f.s.d. of the a.c. range to be calibrated. This may be done by using a potentiometer across the supply and measuring the voltage with the already completed d.c. ranges of the meter. If now the meter is connected to read a.c. the multiplier may be chosen so that the meter reads 66.6% of full scale. For example, to calibrate the 10V a.c. range connect the meter to a 6V d.c. supply, measure the exact voltage on the 10V d.c. range, then connect the meter to read 0—10V a.c. The multiplier should then be chosen so that the meter reads 6.66V. This may sound somewhat complicated but it is in fact very easy to do. The choice

of a d.c. voltage of 60% of full scale is necessary only on the 10 and 50V ranges. For the 100 and 500V ranges a voltage of between 40% and 90% will do.

COMPONENT LIST FOR DESIGN NO. 1

Multipliers	D.C.	A.C.
5V	10k Ω	—
10V	20k Ω	16k Ω
50V	100k Ω	90k Ω
100V	200 Ω	180k Ω
500V	1M Ω	900k Ω

Resistance range

1.5V dry cell,
2,200 Ω $\frac{1}{4}$ W resistor,
1k Ω potentiometer.

Miscellaneous

M moving coil meter 0—500 μ A f.s.d.
4 germanium diodes, type OA70,
12 sockets.

The meter shown in the photograph is housed in a specially made case. A suitable case may be found in the range of "Eddystone" die-cast boxes or, alternatively, a small plastic container sold for use as a sandwich box might be used.

NEXT MONTH, TWO MORE SIMPLE MULTIMETER DESIGNS WILL BE DESCRIBED.

DON'T BUY

THESE
TWO
DOUBLE
SIDED

BLUEPRINTS

GET THEM FREE!


- Audio Oscillator & Output Meter
- Microphone Mixer
- Simple Short Wave Receiver

IN
PRACTICAL ELECTRONICS
MAY ISSUE—OUT APRIL 15


In the May issue of
Practical
TELEVISION —
building the i.f. stages
of the
"OLYMPIC II"
Transistor TV

DON'T MISS THIS
IMPORTANT INSTALMENT
ON SALE APRIL 22nd—2/-

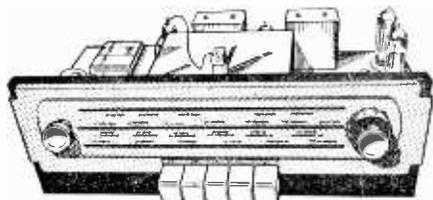BRAND NEW AM FM (V.H.F.) RADIO GRAM CHASSIS AT £13.13.0 (Carriage Paid)



Chassis size 15 x 6 1/2 x 5 1/2 in. High. New manufacture. Dial 14 1/2 x 4 in. in 2 colours, predominantly cream. 200-250V. A.C. only. Pick-up, Ext. Speakers, A.C., E., and Dipole Sockets. Five pushbuttons—OFF L.W., M.W., P.M., and Gram. Aligned and tested O.V.P. Transformer. Tone control, 1000-1900 Mc.; 200-350 Mc.; 88-98 Mc/s. Valves E280 rect.; EC81, EF89, EABCS0, EL84, EOCN5, 3-ohm speaker required. 10 x 6 in. ELLIPTICAL SPEAKER 25/- to purchasers of this chassis. TERMS: (Chassis) £3.10.0 down and 5 monthly payments of £2.4.0. Cheap Room Dipole for V.H.F. 12/6. Feeder 6d. per yard. ALTERNATIVE DESIGN, L.W. 1000-1900 M.C., S.W. (9-15 Mc/s); M.W. 190-475 M.; V.H.F. 87-100 Mc/s. Gram position. Otherwise similar to above chassis. Price £15.15.0 (carr. paid). TERMS: £3.10.0 down and 5 monthly payments of £2.4.0. Total H.P. price £16.14.0. Circuit diagram 2/6.

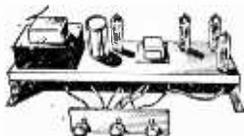

PUSH-PULL O.P. AMPLIFIER £5.5.0
(6/- Carr.)

Brand new 200-240 A.C. mains Bass, treble and vol. controls, with valves E280, EOCN3 and 2-EL84's giving full 8 w. Chassis 12 x 3 1/2 x 3 1/2 in. With o.p. trans for 2-ohm speaker. Front panel (normally screwed to chassis) may be removed and used as "dialing panel".


GUITAR AMPLIFIER—8 WATTS. £5.4.0
(6/- P. & P.)

Chassis as above. Valves E280 2 x EL84, 6 BR8. Output for 3 and 15 ohms Bass, treble and volume controls. On/off. Input 200/240V A.C. Also suitable for pick-up, radio, etc. £5.4.0. (6/- P. & P.)

AMERICAN BRAND TAPE FULLY GUARANTEED AT RECORD LOW PRICES

MYLAR BASE		
7in. Stand play, 1,200ft.	12/6	
7in. Long play, 1,800ft.	13/6	
5in. Double play, 1,200ft.	15/-	
5 1/2 in. Double play, 1,800ft.	22/6	
7in. Double play, 2,400ft.	25/-	
3in. Triple play, 450ft. (Plain white boxes)	12/6	
3 1/2 in. Triple play, 600ft. (Plain white boxes)	14/-	
4in. Triple play, 900ft. (Plain white boxes)	22/6	
5in. Triple play, 1,200ft. (Plain white boxes)	42/6	
7in. Triple play, 3,600ft. (Untoxed)	75/-	
ACETATE BASE		
5in. stand play, 600ft.	8/-	
7in. stand play, 1,200ft.	11/-	
5in. Long play, 900ft.	10/-	
5 1/2 in. Long play, 1,200ft.	12/6	
7in. Long play, 1,800ft.	15/-	
Postage 1/- per reel (4 or more post free)		
MESSAGE TAPES		
3in. Stand play, 150ft.	3/6	
3in. Long play, 225ft.	4/11	
3in. Double play, 300ft.	7/6	

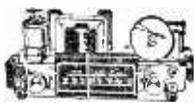SELF-POWERED V.H.F. TUNER CHASSIS. Covering 88-95 Mc/s. Mullard permeability tuner. Dims. 8 x 6 x 6 in. high. Valves EOCN5 and 2-EF89's plus 2 diodes with E280 rectifier. Mains transformer. Fully wired and tested ONLY £8.17.6 (carr. paid). Room dipole 12/6. Feeder 6d. per yard.



BATTERY ELIMINATOR

For 4 Low Consumption Valves (96 range) 90v. 15 mA and 1.4v. 125mA. 42/6 (4/-). 200-250V. A.C. Also for 250MA. 1.4v. and 90v. 15mA at same price. Two separate units to replace existing batteries. 4 x 2 1/2 x 2 1/2 in. and 3 x 2 1/2 x 1 1/2 in.

ALL ITEMS ARE NEW AND FULLY BUILT UNLESS OTHERWISE STATED. TESTED BEFORE DESPATCH. Delivery by return. Terms available on items over 55. Send 6d. (stamps will do) for 20 page illustrated catalogue. C.O.D. 2/6 extra.


ALL ITEMS GUARANTEED 12 MONTHS VALVES 3 MONTHS
Regret overseas orders cannot be executed.

GLADSTONE RADIO

NOTE NEW ADDRESS:—
66 ELMS ROAD, ALDERSHOT, Hants.
(2 miles from Station and Buses.) Aldershot Z2240
CLOSED WEDNESDAY AFTERNOON

"REALISTIC" 'SEVEN'

7 Transistor Superhet. 350 Milliwatt output. 4-inch speaker. All components mounted on a single printed circuit board size 5 1/2 x 5 1/2 in. in one complete assembly. Plastic cabinet, with carrying handles, size 7 x 10 x 3 1/2 in. External Socket for cat aerial. Ferrite rod aerial. Price for the complete parcel, including Transistors, Cabinet, Speaker, etc., and full Construction Data: £5.19.6 P. & P. 4/6.

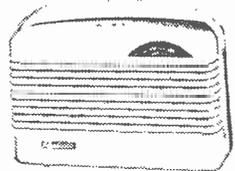

PP9 Battery 3/8. Data and instructions separately 2/6. Refunded if you purchase the parcel. Any parts supplied separately.



4 TRANSISTOR MINIATURE PUSH-PULL AUDIO AMPLIFIER HIGH IMPEDANCE

PRINTED CIRCUIT. 4in. x 2 1/2 in. x 1 1/2 in. over transformers. Output for 3-ohm speaker. Suitable for microphone, record player, guitar and intercom. 9 volt battery required. Frequency range 100 cps. to 25 Kcps. Push-pull output class B. Instruction sheet provided. Fully wired ready for use. Two types. 200mW. 35/-; 500mW. 41/- (P. & P. 2/6 each.)

4 to 5 WATT HIGH GAIN AMPLIFIER

Only £4.19.6. (P. & P. 6/-). Suitable for record player, radio, tape after equalisation. Double wound mains transformer. Fully built. For A.C. mains of 200-250V. 14 db. neg. feedback. Controls are volume (on/off), treble and bass. Contact cooled metal rectifier (bridge); EC83's and EL84 valves. Output for 3 ohm speaker. (Chassis size 6 1/2 x 6 in. (over spindle) overall height, including valves, 5 1/2 in. High and low input by Phono sockets. Stereo amplifier on above chassis. Valves 2 x UCL82. Metal rectifier. 2 x 2 W. Input and output by Phono sockets, 3 ohm speakers required. Suitable for record player, etc. Price £5.2.6. (P. & P. 6/-).

E.M.I. 4-speed PLAYER & P.U. (separate)

8 1/2 in. metal turntable, 200-250V. motor. Turnover head. Our price 59/6 (P. & P. 4/6).

GRAMOPHONE AMPLIFIERS AND PLAYERS

1 1/2 watt type. With 6 x 4 in. speaker. Baffle 13 1/2 x 7 1/2 in. 200-240V. A.C. ECL82 and Rectifier. Tone and Volume On/Off switch. Two knobs. Ready to play. 49/6, post 5/-.

4 watt type. Valves UY85, UF90 and UL84. 200-240V. A.C. Covered baffle 13 1/2 x 7 1/2 in. (6in. speaker), 3 front controls: bass, treble, on/off/vol. 60/-, Post 5/- Double wound mains transformer. Cabinet to fit either type with plain motor board £3 carr. paid. Complete record player in beautifully styled cabinet, fully built (NOT A KIT), £10.17.6. with UA14 4-speed autochanger, or with Garrard Autoslim 4-speed autochanger, £11.5.0.

Single Player in Cab. 13 1/2 x 13 x 5 1/2 in. B.S.R. Monarch 4-speed deck, £8.9.6.

30 WATT TRANSISTORISED AMPLIFIER

Chassis size 7 x 7 x 4 in. Input for 500-ohm (50mV for full output) and 500K (5mV for full output), 14 db. neg. feedback. Controls are volume (on/off), bass, treble. Transistors 2 x NKT 401, 1 x 452, 2 x 262, 1 x 264 Fitted with carrying handle. Input standard Jack sockets. Output and supply on terminal block. Black matt finish. Price £11.19.6 (P. & P. 6/-).

TAPE RECORDER AMPLIFIER

Fully built. Front panel 12 1/2 x 3 in. Chassis size 10 1/2 x 5 x 4 in. Valves EF86, EOC83 and 2-EL84's. Controls (1) MIC. Vol. (2) Timer/P.U. Vol. (3) Play back or monitor. (4) Tune. 2 Jack sockets for Tuner/P.U., and MIC-switch for superimpose. Separate power pack containing transformer and rectifier. For Collaro studio deck only. Price £8.14.0 (6/- P. & P.)

4-SPEED AUTOCHANGERS

BSR-UA14	£5.19.6
GARRARD AUTOSLIM	£6.10.0
STEREO	£7.5.0
AUTOSLIM DE LUXE AT76	£10.19.6
STEREO	£11.10.0
(Carr. 5/- each)	

13 x 8in. LOUSPEAKERS 49/6

Three ohm. Ceramic magnet of latest type. BRAND NEW. (post 3/6)

CM21 CRYSTAL MICROPHONE

With 3.5 mm. Jack plug, 12/6 (Post 1/6.)

HEATER TRANSFORMER

Mains input giving 6.2v. 2 amp. Size 2 1/2 x 2 x 1 in. (2 1/2 in. over winding). 5/6 ea. Less 10% for 12, or 20% for 50. P. & P. 2/- for 1 to 6, post free more than six.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- Institution of Electronics & Radio Engineers (Brit.I.R.E.)
- C. & G. Telecommunication Techns' Certs.
- C. & G. Supplementary Studies
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students Coached until Successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, signal generator and multi-test meter—all under expert tuition. Three courses to choose from.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.) _____

NAME _____

ADDRESS _____

5.65

INTERNATIONAL CORRESPONDENCE SCHOOLS

1,000 EX-RENTAL 17 INCH TV SETS

● All believed to be working but are untested

● Slimline and standard
OUR PRICE 30/- each

NOTE:

PERSONAL COLLECTION ADVISED

We are prepared to send for 15/- extra, but this only undertaken at Buyers' risk.


L.K. ELECTRONICS (VICTORIA) LTD.

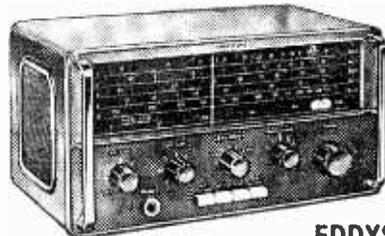7-17 GILLINGHAM ROW
VICTORIA, LONDON, S.W.1

Tel: VIC 5091



*The Sensational
ALL-TRANSISTOR!
Communications Receiver*



**EDDYSTONE
EC10**

for use in the home, caravan, car or boat.

H.P. facilities. **Only £48** Part exchanges.

Write for brochure

**170-172 CORPORATION ST.
BIRMINGHAM 4**
Telephone CEN 1635

on the Short Waves

MONTHLY NEWS FOR DX LISTENERS

All times are in G.M.T.

All frequencies are in kc/s.

The Broadcast Bands—by John Guttridge

INFORMATION first this month about QSL cards. All verification details (time, date and frequency) continue to be given by *Radio Australia*, A.R.F.S. New York, *Radio Luxembourg*, *Radio Sofia* and *Radio Warsaw*, Sofia and Warsaw having colourful cards according to Wilfred Smith of West Bromwich, who has also obtained a full verification from the Swiss Broadcasting Corporation.

Radio Bucharest, Bucharest, Rumania, has issued six new cards, each carrying a different photograph. Listeners who send in six reports, numbered from 1 to 6 during 1965 will receive the cards in sequence plus a surprise gift at the end of the year. Unfortunately the cards only carry details of date and frequency. The station has English for Europe at 1930—2000 on 7,195/7,225/9,510; 2100—2130 5,990/6,190/7,195 and 2230—2300 on 155/5,990/6,190/7,195.

The Canadian Broadcasting Corporation (P.O. Box 6,000, Montreal) has changed the design on its card. Full verification details are given on its reverse.

Another station giving full details is *Radio Lomé*, Togo. This card is interesting in that apart from the station name it is the same as that issued by *Radio Abidjan*. It gives Radio Lomé's schedule as weekdays 0530—0800, 1200—1400, 1200—2300; Saturdays 0530—0800, 1200—2300, and Sundays 0600—2300. Morning and evening transmissions are on 5,047 and afternoon transmissions are on 7,265.

Radio Sweden, Box 955, Stockholm, Sweden, gives date and frequency only on its card, which includes various facts about Sweden. Information on schedule changes has come both direct from Radio Sweden and from A. Waddelow of Norwich. The main change is the introduction of morning transmissions to Europe (not Sundays) on 9,620. Languages are French 0930, German 1000, Swedish 1030, and English 1100—1130. New frequencies are being used for several other transmissions. Details are English 1230—1300 11,810/15,440, 1445—1515 15,440/9,765, 1615—1645 15,240/11,705, 1400—1430 15,300, 0145—0215 5,990 and 0315—0345 9,705; Swedish 1300—1345 11,810/15,440, 1515—1600 15,240/9,765, 0100—0145 5,990, 0230—0315 9,705; French 2145—2215 6,095. Air Mail report forms are now available from Radio Sweden incidentally.

Good reception of the European English transmissions from *Radio Sofia* is reported by Wilfred Smith. They are aired from 1930—2000 and 2130—2200 on 6,070. This frequency is also used for the

English transmissions to North America from 0000—0030 and 0400—0430.

Two Middle-Eastern stations he has heard are the Arabic Home Service of *Radio Baghdad* which was SINPO 33222 between 1930 and 2020 on 7,180 and *Radio Tehran*, Iran. He heard the home service of the latter station at 0800 on 15,125. There is some confusion about this station so readers' observations would be especially welcome.

A recent Swiss Broadcasting Corporation Dx bulletin gave the home service schedule as 1245—1730 on 3,785/7,065/7,165/11,750 and 1730—2030 on 3,785/7,065. The Foreign Service was said to be transmitted from 1730—2130 on 7,165/11,750. A. Waddelow, however, gives the foreign service frequencies as 7,135/11,730, whilst in London I have heard some segments on approximately 7,405. Languages are believed to be Russian 1730, Turkish 1800, Arabic 1830, French 1930, German 2000 and Persian 2030—2130.

Radio Tirana, Albania, is the last station mentioned by Wilfred Smith. He has heard English from 2000—2030 and French from 2030—2100 on 9,390. A parallel frequency is believed to be 7,090.

According to Roy Patrick, of Derby, two of the most persistent North American medium wave stations at his location have been CBA Sackville on 1,070 and WEZE Boston on 1,260.

Several changes have been made by Radio Nederland (P.O. Box 222, Hilversum). Here are some of the affected transmissions, metre bands (e.g. 16m) are given where the exact frequency is not known. If you can discover the correct frequency please let us know. Afrikaans 1530—1630 16m/15,425; Arabic 1430—1550 15,445/11,730; Dutch 0230—0350 31m (Bonaire), 0900—1020 Sunday 21,570/21,480/15,445/16m/6,020, 1800—1920 15,220/25m/6,020, 2100—2220/19m (Bonaire); English (not Sundays) 0400—0450 31m (Bonaire), 1400—1450 16m/15,425/6,020, 2000—2050 25m/9,590/6,020; Spanish 0130—0220 49m (Bonaire), 2230—2320 19m (Bonaire); Happy Station (Sundays) 0600—0720 9,715/49m, 1400—1520 16m/15,425/6,020, 1530—1650 16m/9,590.

Frequency usage has been revised by the *Voice of America* for its European English transmissions which can now be heard on 1,196 Munich from 0400—0430, 0500—0730, 1700—1830, 2200—2230; 3,980 Munich 0300—0730, 1400—2330; 5,995 Greenville 0300—0730; 5,995 Tangier 1630—2230; 6,040 Munich 0500—0730; 6,080 Tangier 0300—0730; 7,200 BBC 0300—0730; 7,205 Thessaloniki 1500—2230; 9,540 0300—0730; 9,670 Greenville 2015—2200; 9,740 BBC 0300—0730; 9,740 Tangier

1900—2200; 11,760 1900—2200; 15,205 Greenville 1400—2200; 15,290 Tangier 1400—1630; 15,295 0500—0730; 17,780 Greenville 1400—1830. Many of the V.O.A. Russian service programmes consist of light music and give good U.K. reception. Frequencies are 1,196 0300—0400; 6,020 0300—0500; 6,040 0300—0500, 1500—2100; 6,150 0300—0500; 7,170 0300—0500, 1730—2100; 9,540 1715—2100; 11,710 1500—2100; 15,315 1500—1715.

Extension of its European service to 2400 is the big feature of the latest schedule from *Radio New York Worldwide*, New York 19, U.S.A. Frequency

usage to the UK and Europe is now 15,440 1200—2045, 15,220 1245—1600, 17,840 1615—2000, 11,875 2015—2145, 9,525 2100—2400. Transmissions are directed to Africa from 1500—2145 on 17,730 and to the Caribbean from 1200—2400 on 15,440, 1500—2200 on 17,730 and 2200—2400 on 11,855. Radio New York will supply listeners with addresses of stations if wanted and will also try and identify unknown stations if sent a tape recording of the signal. Requests for this help should be sent to the station's "Dxing Worldwide" programme.

The Amateur Bands—by David Gibson G3JDG

THE 1f. bands, particularly Top Band, have been very interesting. Also, ten metres is just beginning to awaken, and as the sunspot cycle starts to build up will again become a good DX band. On February 28th, ZE's and ZS's were coming through.

20 metres keeps open later as the evenings get longer and many reporters noted that it also opens up again late at night when some quite good DX sneaks through. This band still produces some rare ones, at the expense of beauty sleep. A rough guide to the openings is: 0530 to 2000.

On 40, the usual din persists but one can usually hear a VK around 0700 to 0800.

Fifteen is, as usual, spasmodic. One period will produce call signs from all over the globe while the next session will be rewarded with the monotonous noise of frying eggs. Most fruitful times are from around 0800 to 1800 with afternoon peaks.

80 Metres

This is getting more like 40, what with G side-band gatherings, teleprinters, intruders, phantom v.f.o. swishers—and weak DX. Many listeners comment on the noise level; this will get worse as summer comes along. Best time for DX is either around 0600 or from 2300. Early evenings usually produce Europeans only.

Top Band

The last of the Transatlantic tests took place on February 21st. Conditions were much poorer than on previous tests. However, an all-night session using an Eddystone 888A, a 132ft. longwire, and two dozen cups of cocoa, produced the following on C.W.:—OH2HK (559), OK1KG, OK2BHX, K2KGD (449), HB9CM, OK2HHX, GI3PDN, OK1AI, PAØPN, W1BB/1 (459), OK1ADM, GW3TJE, W2GGL (349), GM3TMK, OK1AKU, OK1AER, HB9TT (589), OE1KU, VO1FB (459) and numerous G's. The best DX was HP1IE (449) Panama, heard working W1BB/1. As regards 160m in general, a little careful searching can usually produce W1, W2, VO1, 9L1, OH and OK. Top Band is used at certain times by amateur stations sending slow morse and for those who want to learn c.w. Check with your nearest radio club and see if there is a schedule in your area.

Listener's Reports

Thanks to all who have sent along reports again. We can't use them all but the information is

still of value. Don't forget to mention time, date, call sign, frequency, RST, or RS report. First this month, a colossal log from A3699 in Elderslie, Scotland. The number after call signs is the time in G.M.T.

1-8Mc/s. W1BB/1 0600 (C.W.) DL9KRA1 2359 (SSB).

3-5Mc/s. CW: W8ATA 0129, AL4IE 0752, W2KH 0755, SSB: W1HKK 2244, W1JAE 2250, W3PHL 2255, UR2CC, OD5AX 0049, KP4BL 0320, W1BU 0628, W5CAI 0705, W5KNV 0709, TF1AC 2355.

7-0Mc/s. SSB: YV3KX 0907, VK2AVA 0745.

14Mc/s. SSB: 7X3VW 0740, HS1HS 1255, DU1EH 1256, HS1X 1300, YA4A 1315, 7Q7PBD 1732, VP9FR 1855, ZS4F 1859, EL6E 2251, SL3UY 0950, HC5NW 1230, VK7CK 1305, YS1AGM 1307, VK5HY 1317, XE1CE 1322, VK6EZ 1415, W5HWR/VP9 1959. Plus several W6. VE4, 5, 6, 7 between 1600—1900.

21Mc/s. SSB: 9K2AU 1134, YA3TNC 1230, KP4AOO/MM 1240, EL6E 1650. AM: TN8AA 1119, ZE2JA 1150, 9L1WN 1641, CR4AD 1108. CW: CN8CF 1500, W21YH 1708, K1EPØ 1805, K1YER 1815.

If you still think the bands are quiet then look at the log from W. L. Clarke of Yelverton Devon.

3-5Mc/s. SSB: VE7DU, VE3DJE, VO1B7, W6ITZ/P/4, K1PNE, W8YBZ, (all between 0540—0740).

7-0Mc/s. SSB: VK2AKW, VK2AVA 0845. AM: SVØWM, W8MAZ/P/VO2, VP4LR, AP2HB (between 1000—1130).

14Mc/s. SSB: PY6LP, ZL4BO, LU2DAW, KG1BO 1620, ZS6FT 1915, ZS6ADS 1755, 9Q5RB 1830, 4U1TU 1240, KV4CX 1245, VU1EN 1330, ET3USA 1335, 5A1PZ 1615, KR6UL, VK2NN, VK3AF, JA1CZE, KP4APS 1130, VK4YG, ZL1SJ, KG6AG, SU5ETO 1545, MP4TBO 1550, ZL3AS, HL9TM, KR6DA, BV1UST 1000, HM2BD 1010, VKØTL, 9K2AN 1330, CR9AR 1425 (Pacific area DX 0830—1130). AM: W8MAZ/P/VO2 1100, VP4LR 1120, AP2HB 1135.

21Mc/s. AM: ZE8WY, KV4CX, ZE2JA, WØFLM, (St Lucia A.R.C.) 9Q5RB, 9L1WN, ZS1DBV, CR7FC, 5A1TG, CP1LJ, KC4US, VP9FE, CR7AX, CR7IT (all between 1330—1630).

ISWL/GH362, Worcester, reports 14Mc/s on an 84OC, Codar pre-selector, 20 metre dipole and

—continued on page 70



ARTIFICIAL AERIAL TRANSMITTER LOADS

by
G
3
O
G
R

MANY transmitter tests are best made with an artificial aerial. This avoids unnecessary radiation (and interference with other transmissions on crowded bands) and may allow output power, p.a. efficiency, or other factors to be checked.

If the same type of socket is used throughout, an aerial tuner, dipole, or artificial aerial load may be connected in a few seconds. The feed impedance of a half-wave dipole is usually about 65 to 75 Ω , so it is convenient to use a length of 65-75 Ω co-axial cable as the output lead of the transmitter. This ends with the popular type of co-axial plug, and sockets to match can be fitted to a tuner, artificial load, or feeder to a dipole. If the transmitter has a co-axial output socket, a piece of feeder with two plugs will allow easy connecting up with other circuits.

Lamp Loads

A domestic lamp is quite useful for 1.8 to 28Mc/s. It is suitable as a load for a phone transmitter, or for loading adjustments etc., with a c.w. transmitter. It cannot be used for keying tests with much success because its resistance changes considerably when hot.

A simple base, like that in Fig. 1, and fitted with a socket and lampholder, will prove handy. The lamp wattage may be similar to the d.c. input of the p.a. stage. For top band (10W) a 15W lamp is satisfactory. A 100W lamp will take the output of a 120W transmitter, if a 150W lamp is not to hand.

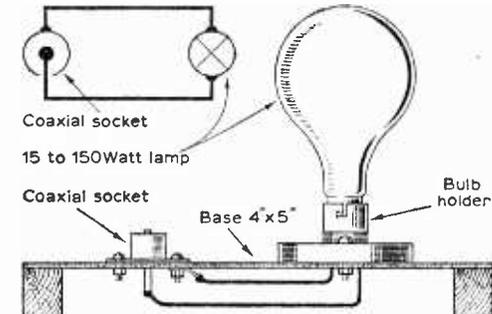


Fig. 1 (above): An arrangement for using a domestic lamp as an r.f. load.

Fig. 2 (right): A carbon resistor load used in conjunction with an r.f. ammeter.

A 100W lamp will actually do for 50W upwards, though a 25W, 40W or 60W lamp is useful for smaller power.


The average pi-output circuit can be loaded directly into the lamp, as described later. If necessary, some indication of output power may be obtained by comparing brilliance with another lamp of the same type, run from the mains. The lamps should be exchanged, to check their brilliance. A photographic exposure meter is also useful for this. P.A. efficiency can be checked at loading points which give 15W, 25W, 40W, 60W and similar outputs. That is, full brilliance with the artificial load lamp, to agree with a similar lamp run from mains supplies.

Resistor Load

A carbon resistor load can be used for 'phone, and a c.w. transmitter when loading or keying. Large resistors which will take the output of a 150W p.a. are obtainable, some being very inexpensive as surplus. For very large outputs, two or more resistors can be used in series or parallel.

Fig. 2 indicates how the load resistor and a r.f. ammeter may be fitted to a base or box. Output power can be found from $I^2 \times R$, so a 350mA meter with 70 Ω or similar load will do for a top band or similar low power transmitter. For high power, a 1.5 or 2A meter is satisfactory.

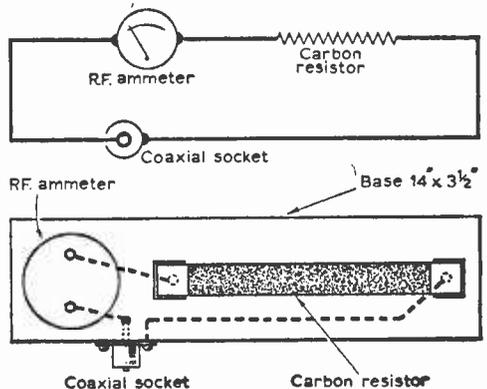A table of approximate power levels can be glued on the base for easy reference, or the meter may be calibrated in powers. With a 70 Ω load, the approximate power for various current readings



will be as follows:

Current (Amps)	Watts	Current	Watts
0.1 A	0.7	0.8	44.8
0.2	2.8	0.9	56.7
0.3	6.3	1	70
0.4	11.2	1.1	92.4
0.5	17.5	1.2	101
0.6	25.2	1.3	118
0.7	34.3	1.4	137

The resistor value and meter can be checked, if high accuracy is wanted. Some error will not influence comparative tests of efficiency. The average r.f. meter is most accurate at about 1/4 to 1/2 full-scale reading.

Low Power Load

A load for a small transmitter is easily made from several ordinary carbon resistors, wired as in Fig. 3. Six 1W resistors will take the output of the average 10W transmitter. Larger resistors, such as 2W, may be used for more power or the number of resistors can be increased.

When all resistors are of the same value and in parallel, the value of each resistor equals the load multiplied by the number of resistors, e.g. four 2W resistors are to be used, and a 75Ω load is wanted. $75 \times 4 = 300$. So each of the resistors is 300Ω.

Loading with Pi-Output

For those who are just getting started with a transmitter, Fig. 4 shows the usual pi-output circuit. To load the power amplifier into the lamp or resistor, first close VC2 to maximum capacity. If necessary, check p.a. grid current, to see that the stage is being driven correctly. H.T. is then applied to the p.a. and VC1 is rapidly turned until a dip is seen in the anode current meter in the h.t. circuit.

With some valves, the anode dissipation will easily be exceeded if the circuit is not tuned to resonance, and this is why VC1 is quickly tuned. When VC1 is adjusted for minimum h.t. current, this will probably be far too low. So VC2 is opened, VC1 being re-adjusted for minimum h.t. current.

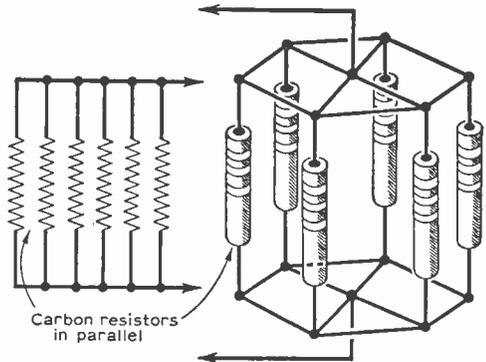


Fig. 3: Several carbon resistors connected as shown form a suitable load for top band or low power transmitters.


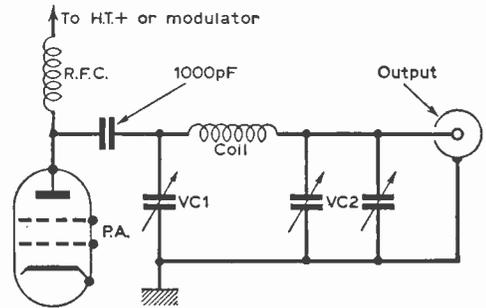


Fig. 4: The usual sort of pi-output circuit used with transmitters.

The h.t. current will now normally be higher. This procedure is repeated until the p.a. draws its full rated h.t. current, with VC1 tuned for *minimum* current. It is convenient to use both hands, VC2 is generally a 2-gang or 3-gang 500pF capacitor.

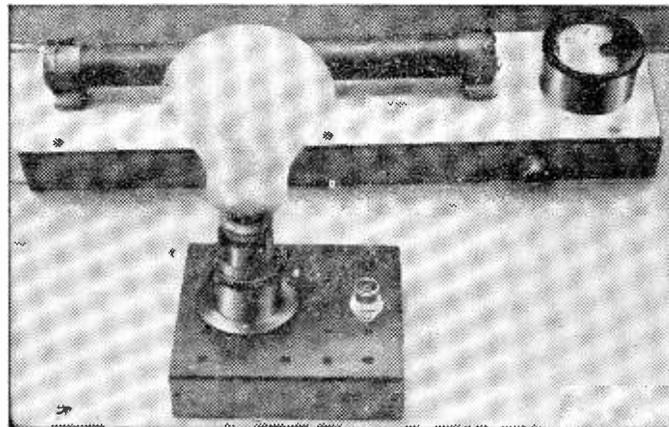As loading has progressed, the lamp will have grown much brighter, or the r.f. meter will have increased its reading.



The two loads described in the text and illustrated in Figs. 1 and 2 are shown together in this photograph.

Input and Output

The p.a. input is $I \times V$. For example, if the p.a. draws 100mA at 500V, this is $0.1 \times 500 = 50W$ input.

Efficiency, as a percentage, is:

$$\frac{\text{Input}}{\text{Output}} \times \frac{100}{1}$$

E.g., output is 30W. In the example, $50/30 \times 100 = 60\%$. Efficiencies of 60% and higher should be anticipated.

When a r.f. meter is present to show output, changes can be made to grid drive, bias, screen grid voltage, etc., in an attempt to secure best efficiency. That

—continued on page 40

GROUNDING INVERTED L ANTENNA

by P. W. Waters, 630JV

A CHANGE of QTH recently set the writer thinking about the re-erection of the antenna system. Having been used to a half-wave on 160 metres at about 40ft. high, it came as somewhat of a shock to find that at the new QTH the maximum straight run possible would be about 30ft. Even bending the antenna to fit the garden would not allow anything approaching the quarter wave mark on Top Band.

The writer wanted to operate principally on the 160 and 80 metre bands and so a considerable amount of thought was given as to how to accommodate a radiating system for these two bands. If a bent horizontal wire were to be used it would not only have to have several supports in addition to the usual ones at either end, but it would also have to run through several trees. This idea was obviously not practicable.

Thoughts were then turned to a vertical system. This seemed a much sounder idea from the practical aspect. The problem with this method was that the transmitter was located in the top of the house and a considerable length of coaxial cable would have to be run down the side of the house and across the lawn in order to feed the antenna at the base. This would also involve insulating the base and constructing a weather-proof matching network.

It then occurred to the writer that it should be possible to feed the antenna from the top and ground the far end. This seemed quite a good idea as well as solving constructional problems. The final antenna is shown in Fig. 1 and has been in use for several months now.

The transmitter is very close to the window only requiring a 2ft. lead in. However, an extra few feet should not effect performance much and a length of 10ft. inside the room was found to leave the performance unaffected.

Due to the higher impedance present at the top of the antenna, coaxial cable cannot be used to feed the system. A 30ft. length of wire has, therefore, been used between the transmitter and the vertical section. The vertical part of the antenna consists of a 34ft. alloy mast which is electrically connected to the far end of the 30ft. wire. The whole, thus forming a 64ft. radiating system. The wire is connected to the top of the mast by means of an alloy nut, bolt, and washer to avoid rusting, and the whole bound with insulating tape.

The mast is supported at the base by means of a sleeve fitted over a piece of gas barrel of slightly smaller diameter driven into the ground. In view of this point being the position of maximum current irrespective of band or frequency it is essential to provide a very good earth connection owing to the heavy losses that can occur at such low impedances. The existing connection is thus not sufficient. While on this point I would like to mention that if several earth spikes are driven into the ground at the base of the mast, a noticeable increase in aerial current will be obtained. Further, the radials were similarly buried to provide an even better earth and in my case they are 30ft long, although the length can be increased if space permits, and may be bent if desired in order to fit the space available. It must be stressed, however, that the better the earth connection the better the results.

The earth spikes are copper rod or tube, and heavy gauge wire is soldered to the top of each spike. These wires, together with the radials, are all con-

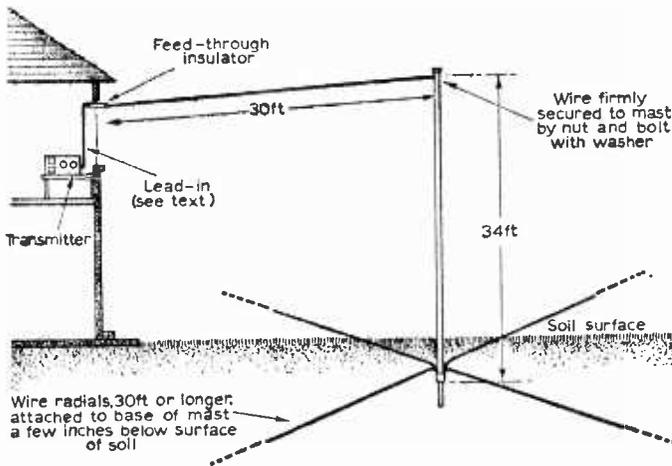


Fig. 1: The antenna arrangement and dimensions, showing the underground system of radial wires.

nected to the base of the mast by means of a wrap-round, home-made alloy clamp, and bound with insulating tape to protect the connection from the weather. The only point of the system where insulation needs attention is at the feed end where on some bands the aerial is voltage fed and should, therefore, be kept away as much as possible from gutters and walls, etc.

Any reader who requires to know the impedance at the input end for any band can easily calculate it by reference to the base which is always of low impedance. Thus for an odd number of quarter wavelengths the impedance will be high and for even numbers the impedance will be low.

The impedance at the feed point of the antenna will be medium on 160 metres and high on 80 metres.

The current at this point will thus be found to be much higher on 160 metres than on 80 metres and the station aerial tuning unit should be used to match the antenna to the transmitter.

Results have been very encouraging. It has been found possible to work over most of England and Wales on 160 metres c.w. and s.s.b. from the writer's QTH in Essex. On 80 metres coverage of the whole of Europe has been found possible with an input of c.w. of 50W and reports averaging strength 7.

Whilst fantastic results are not claimed for this antenna, it does appear to operate much more efficiently than a horizontal wire of similar length. It is hoped, therefore, that this article will be of interest to people who like the writer suffer from lack of space. ■

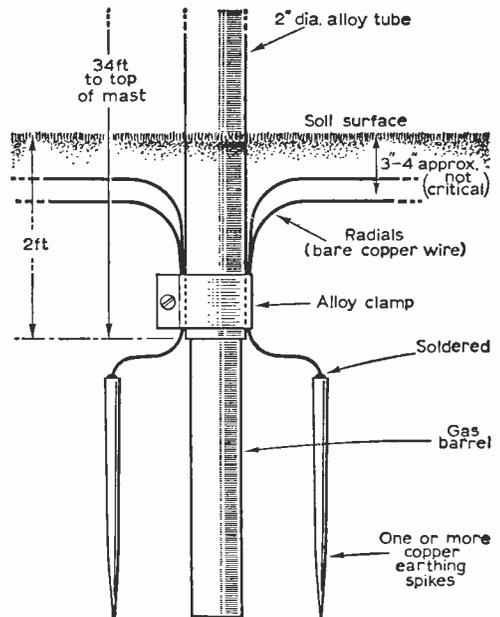


Fig. 2: Details of the base of the mast, buried below ground with all its earthing attachments.

ARTIFICIAL AERIAL TRANSMITTER LOADS

—continued from page 38

is, maximum r.f. output, for a given p.a. d.c. input.

Harmonic Tests Etc.

If the presence of harmonics is to be checked, it is convenient to take the transmitter output to an aerial tuner, or coil. The lamp or other artificial load can be tapped across part of the coil, to secure suitable loading. Harmonics or other unwanted frequencies can then be checked for by placing a wavemeter near the coil. When an end fed aerial is operated through a tuner, the transmitter can be loaded into the 70Ω resistive load. Transmitter tuning can then be left unchanged, aerial tuning or tappings being adjusted to secure the same loading of the transmitter.

When making speech quality tests, or checking modulation with a scope, enough r.f. can be picked up by placing a lead near the lamp or resistor, or by looping an insulated wire round the connection running from the centre of the co-axial socket.

If the transmitter is home built and cannot be loaded into a 70Ω or similar artificial aerial, note the positions of VC1 and VC2 (Fig. 4). If VC1 is fully closed without resonance, the coil needs more turns for that band, or VC1 is too small. But if VC1 has to be fully open, the coil is too large. Many combinations of VC1, coil inductance, and VC2 will permit loading to full anode current. Small values for VC1 are best for the h.f. bands (14, 21 and 28Mc/s). That is, r.f. output is largest with VC1 nearly fully opened, the coil being of

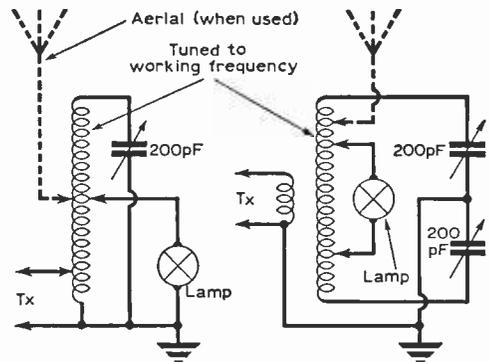


Fig. 5: Two methods of obtaining low impedance loads with high impedance lamps.


sufficient inductance to allow this. The output of a multi-band transmitter can be expected to fall off somewhat on the h.f. bands, compared with 3.5Mc/s,

A domestic lamp used as a load may have too high impedance for some transmitters. If so, this can be overcome by using an aerial tuner similar to that in Fig 5. That is, as required for an end-fed half-wave aerial.

The resistor load can be used to set up a standing-wave indicator for the i.f. bands. With pi-output, standing-wave indicator, and load all of the same value, there should be a steady flow of r.f. into the resistor, and no reflected power. ■

FOR PEAK PERFORMANCE AT LOW COST —

PICK **CODAR** AMATEUR RADIO EQUIPMENT

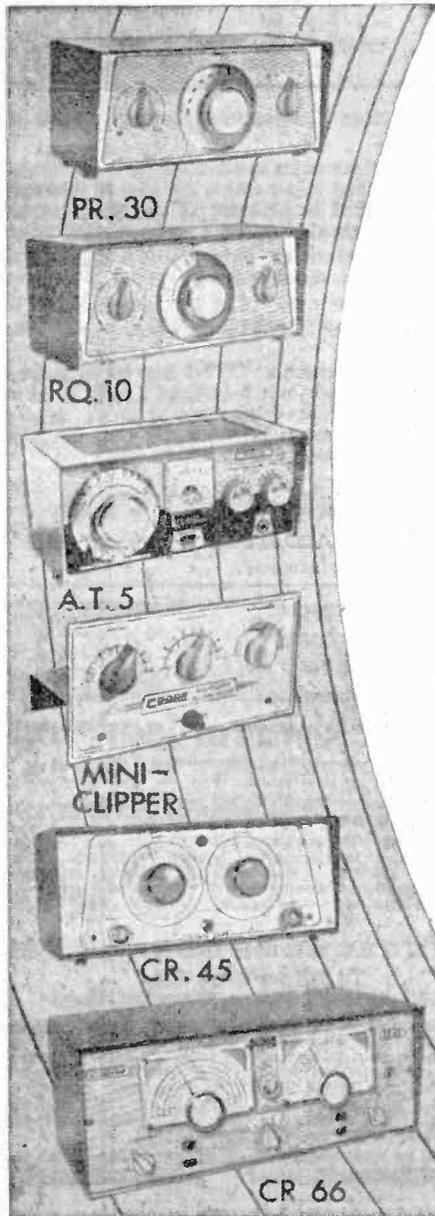

Advanced design and craftsmanship plus an unequalled reputation proved by the many hundreds of testimonials received from CODAR users is your guarantee of complete satisfaction. Only the best is good enough for CODAR—Mullard, Brimar, Jackson, Denco, Electroniques, Thorn, A.E.I., are just some of the famous names built into CODAR equipment. CODAR-KITS are supplied with clear pictorial diagrams and easy to follow instructions—no technical knowledge or special tools are required for complete success. Build your Short Wave Station with CODAR-KITS and enjoy peak performance and world wide reception previously possible only from much more expensive equipment.

For illustrated leaflets giving fullest details send 6d. in stamps.

CODAR R.F. PRE-SELECTOR. Will considerably improve the performance of any superhet receiver. "Results are amazing." Well worth the money. **MODEL P.R. 30.** Uses EF83 Frame Grid tuned R.F. Amplifier and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12 M/A H.T. 6.3 volts, 9 amp L.T. Size 8 1/2" x 5 1/2" x 4 1/2". Ready built, complete with cables, plugs and instructions, £4.18.6. Carr. 3/-.

MODEL P.R. 30X. Self powered version for 200-250V. A.C. and also provides 25 M/A at 200V. H.T. and 6.3V. 1 amp L.T. for other accessories. £7.4.0. Carr. 3/-.

CODAR "Q" MULTIPLIER MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity (or either peaking or rejecting a signal on AM, CW or SSB. Both PEAK and NULL functions tunable over receiver. I.F. passband. B.F.O. facility included. Size 8 1/2" x 5 1/2" x 4 1/2". Power requirements 180-250V. H.T. at 5 M/A 6.3V. 3 amp L.T. Ready built complete with cables, plugs and instructions. £8.15.0. Carr. 3/-.

MODEL R.Q. 10X. Self powered version for 200-250V. A.C. and also provides 25 M/A at 200V. H.T. and 6.3V. 1 amp L.T. for other accessories. £8.8.0. Carr. 3/-.

CODAR A.T. 5, 12 WATT 2 BAND TRANSMITTER. The newest, most compact transmitter for fixed or mobile use on 180/80 metres. "The tiny TX with the BIG voice." Size only 8 1/2" x 5 1/2" x 4 1/2". (Base area is less than two-thirds of this page!) High stability new type calibrated VFO 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR-GOIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate/screen modulator. AM/CW switch and Panel key jack. Plug changeover for 9 or 12 volts heater supply. Ready built £16.10.0. Carr. 4/-.

A.T. 5 POWER SUPPLY UNITS. Type 250/S. For 200/250 V. A.C. with Stand by/Net/Transmit and aerial changeover switching, stabilised V.F.O. supply, neon standby/transmit indicator £8.0.0. Carr. 5/-.

Type 12/M/S 12 volt solid state power supply unit £11.5.0. Carr. 5/-.

Type 12/R/C Remote Control and Aerial Switching unit, £2.7.8. Carr. 2/6. (H.P. terms available.)

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER.

- ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost.
- ★ Supplied complete with valve, one coil 25-75 metres and 1 page instruction manual. PRICE 39/6. Carr. 2/6. Extra Coils 4/9 each. Instruction Manual only 2/- (credited on order). Electrical Bandsread available. Provision to add 2 transistor amplifier.

CODAR-KIT CR45 MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs; Shipping, etc. ★ Separate electrical bandsread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line-up: ECC81, EL84, EZ80. **CODAR-KIT CR45** complete with valves, 3 coils (10-28, 25-75, 60-178 metres) and 11 page instruction manual (LESS Cabinet), £7.5.0. Carr. 4/6.

CR45 CABINET, 12in. x 5 1/2in. x 7 1/2in. with sliding door for easy coil changing. 35/-. Extra coils 4/9 each. Instruction manual only 4/- (credited on order). (Can now be supplied ready built—price on request.) (H.P. terms available.)

CODAR-KIT CR 66 COMMUNICATION RECEIVER. The finest superhet kit ever offered. ★ Covers 540 Kc/s—30 Mc/s in 4 bands. ★ Separate electrical bandsread. ★ Factory aligned Coil unit and L.F. Transformers. ★ Regenerative I.F. stage for maximum gain and B.F.O. for C.W. reception. ★ Power output 3 watts for 2/3 ohm speaker.

★ Panel controls: Aerial Trimmer, A.V.C., Standby Bandswitch, A.F. Gain, I.F. Gain, B.F.O., etc. ★ Valve line up: ECH81, EB98, ECC81, EL84, EZ80, 6BM4. ★ Size 18in. x 6 1/2in. x 3 1/2in. **CODAR-KIT CR 66.** Complete with 17 page instruction manual, £19.15.0 (Ready-built £29.0.0) CR 66 "S" Meter Model Kit £22.0.0 (Ready-built £25.0.0). Carr. 7/6 extra on all models (H.P. terms available). Instruction Manual only, 7/6 (credited on order).

CODAR COILS AIR-SPACED INDUCTORA. A complete range of low loss air-spaced inductors developed by CODAR. Over 40 different sizes from 1/2in. to 3in. diameter suitable for all types of circuit application including V.F.O. P.A. Tank, Pi-network, A.T.U., aerial loading, etc. Full data and prices on request.

CODAR RADIO COMPANY


G31RE G3HQ

BANK HOUSE, SOUTHWICK SQUARE, Southwick, Sussex Tel. 3149

Canada: Codar Radio of Canada, Tweed, Ontario.



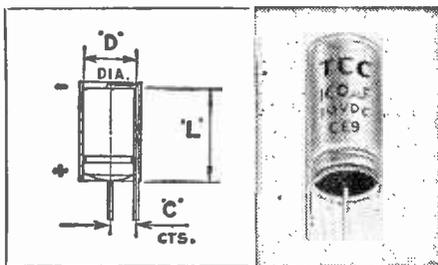Sub-miniature Electrolytics for Transistor Circuits



T.C.C. TYPE No.	Case Size in inches			Maximum D.C. Wkg. Voltages and Cap. (µF)					
	D	L	C	3V.	6V.	9V.	12V.	15V.	25V.
CE.2 'V' or 'H'	1/8	1/4	0.07	8	6	4	3	2	—
CE.3 "	1/8	1/4	0.1	25	20	15	10	6	4
CE.4 "	1/8	1/4	0.1	40	30	20	15	8	6
CE.5 "	1/8	1/4	0.14	50	40	25	20	10	8
CE.6 "	1/8	1/4	0.14	80	60	40	30	15	12
CE.7 "	1/8	1/4	0.18	100	75	50	40	20	15
	D	L	C	3V.	6V.	10V.	15V.	25V.	50V.
CE.8 "	1/8	1/4	0.14	100	80	60	40	25	8
CE.9 "	3/16	1/2	0.2	250	200	160	100	60	20

V=Vertical Mounting H=Horizontal Mounting

Operating Temperature Range. —20°C. to +60°C.

Connection wires are welded for low resistance contact, and solder-coated for ease of assembly, the standard length being 1 1/2" for the horizontal range, cropped to 3/8" long for the vertical range.


The capacitors are in insulated seamless aluminium cases, sealed with a synthetic rubber bung.

Cap. Tolerance. The standard tolerance of all capacitors is —20% + 100% of the rated capacitance.

Leakage Current. CE.2-7 may be determined from the following: 1 (µA)=·01 C.V. + 10 at applied working voltage and at 20°C. CE.8-9 may be determined from : ·02 C.V. + 20 at applied working voltage and at 20°C.

THE TELEGRAPH CONDENSER CO. LTD.

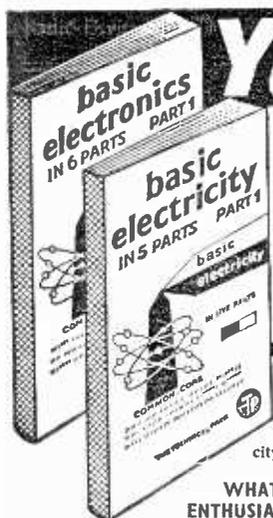Radio Division · NORTH ACTON · LONDON · W.3 · Tel. ACORn 0061 · Telex: 261383
also at CHESSINGTON, SURREY and BATHGATE, SCOTLAND



YOURS FREE FOR 7 DAYS

The New 'Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

EVERY DAY WE RECEIVE LETTERS PRAISING THESE BOOKS, HERE ARE A FEW FROM THIS MONTH'S POSTBAG. "I am delighted with them and consider them a most excellent set of books. They are all your other readers claim for them." G.P., Harrogate. "You must get endless praise about these works. What a change from the heavy going snob books which abound today. It is more like reading a gripping novel and indeed I find it almost impossible to put the work down. I shall not hesitate to spread the good work among my friends." B.M., Liversedge, Yorks.

To Selray Book Co.
60 Hayes Hill, Hayes, Bromley, Kent

Please send me Without Obligation to Purchase, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts). 91/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).
BASIC ELECTRICITY BASIC ELECTRONICS

Signature
(If under 21, signature of parent or guardian)

NAME
BLOCK LETTERS BELOW
FULL POSTAL ADDRESS

POST NOW FOR THIS OFFER !!

HIGH-FIDELITY AMPLIFICATION

BY J. D.
HASKELL

THE true appreciation of any topic is best tackled with a firm grounding in the basic relevant concepts. To start with, a short list of terms associated with amplifier systems and their performance is given.

Frequency Response

This is usually quoted as a band of frequencies covered within a certain number of decibels (dB for short). A frequency response curve is usually plotted on semi-log. paper. Frequency along the log. scale and decibels along the linear scale Fig. 1. (The definition of a decibel (dB) may be found in a text book on sound.) In general the dB nought point is taken to coincide with the "zero" frequency of 1,000c/s. All scales are referred to this frequency. This is because the quietest sound that the ear can hear is 1,000c/s at a pressure of 0.002 dynes per square cm and

this is the standard reference. A good amplifier should have a frequency response of at least 20c/s to 20kc/s \pm 1 dB, preferably even wider. It may be argued that the average adult cannot hear beyond about 15kc/s, nevertheless if the total bandwidth is less than that mentioned transient response will suffer and the reproduction will lack attack. The freq. response is usually quoted for an output of 1 watt. This is not necessarily the same at full output. The response at full output is termed *power response* and this is far more important. A good figure for the latter is 30c/s to 15kc/s \pm 1dB. A figure of 20c/s to 20kc/s \pm 1dB is excellent.

Power Output

With a loudspeaker of average efficiency a low distortion output of 10 to 12W is ample for home listening. Average efficiency is about 7%.

Signal to Noise Ratio

This is simply wanted signal/unwanted signal. Obviously a figure as large as possible is desired here. This figure is quoted in decibels, and a minimum figure of 60dB is required for quality reproduction. Remember that hum and noise are counted as distortion as they are not present in the original signal!

Harmonic and Intermodulation Distortion

Any signal that appears in the output of an amplifier is distortion if not present in the original input signal. The two main types of distortion will be discussed here.

Harmonic

As the title implies harmonic distortion is due to harmonics of the original frequencies being present in the output. This is due to the inherent curvature of valve characteristics, transformer limitations etc. A block diagram in Fig 2 shows how this is measured. A filter removes any harmonics that may be present in the audio

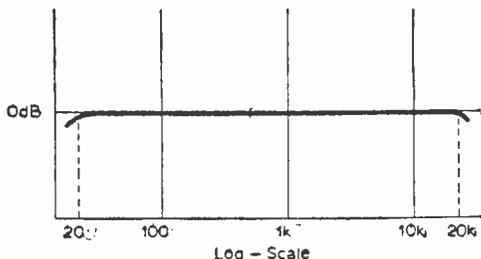


Fig. 1: A frequency response graph. The horizontal scale is measured in cycles per second (c/s).

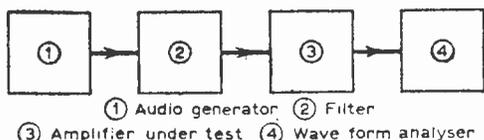


Fig. 2: Illustrating how a wave-form generator is used to test an amplifier for harmonic distortion.


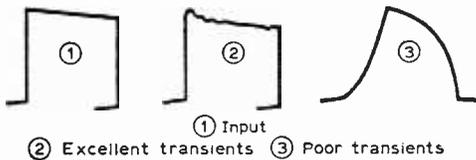


Fig. 3: Investigating transient distortion with square waves.

Fig. 4: The "distributed load" output circuit; a variation of the familiar push-pull output stage.

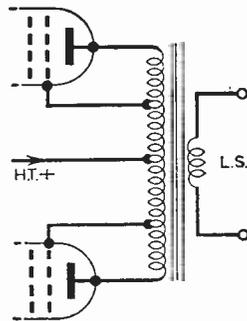

generator. The wave analyser is tuned to harmonics of the applied frequency (usually 400c/s) and the readings are expressed as follows:

D Total

$$= \frac{\sqrt{[(E_2)^2 + (E_3)^2 + (E_4)^2 + \dots]}}{\sqrt{[(E_1)^2 + (E_2)^2 + (E_3)^2 + (E_4)^2 + \dots]}} \times 100\%$$

where E_1 is the amplitude of the fundamental, and E_2 the amplitude of the second harmonic, etc.

Intermodulation Distortion

Measured by applying a combined high and low frequency to the amplifier (40c/s and 10kc/s). This distortion is due to the two frequencies adding or subtracting, in this case giving 10,040c/s or 9,960c/s. This may occur with any frequencies. The distortion figures for a good quality amplifier are normally of the following order:—Total Harmonic Distortion $\leq 0.2\%$. Total Intermodulation Distortion $\leq 0.5\%$ for the full output.

Another type of distortion is transient distortion, and although it is rarely mentioned it is none the less important. This appears as the inability of the amplifying system to respond to sudden changes of amplitude and frequency. It is usually evaluated by measuring the rate of decay of a suddenly interrupted steady frequency. If this distortion is severe it is very probable that the frequency emitted at decay would be different from the steady frequency that was interrupted. It is difficult for a listener to differentiate between this type of distortion and that due to resonance. A much more convincing test is carried out by using square waves. See Fig. 3.

It is time now to discuss some typical circuits, their merits and functions.

MAIN AMPLIFIERS

The basic requirements of a main amplifier are low harmonic distortion, linear frequency response, adequate power output, good transient response, low hum and noise level, and low output impedance. The last item on the list has not yet been discussed but will be tackled under Negative Feedback.

Output Stage

The most common type of output stage on a main amplifier is the Ultra-Linear type. This is also referred to as "distributed load" and is a modified form of the conventional push-pull output stage, the tetrode screens being connected toappings on the output transformer to give a mode of operation between tetrodes and triodes. See Fig. 4.

This distributed load has a number of advantages; less overall feedback is required for a given result giving a greater margin of stability, reduction of harmonic distortion, greater efficiency (36% against 27% for triodes or triode connected tetrodes) and much lower peak variations in current than are inherent with triode output stages.

Damping and Negative Feedback

The damping factor is the ratio of load impedance/output impedance. By applying overall feedback to the amplifier (including the output transformer) the output impedance as seen by a speaker at the output terminals is considerably reduced. As an example a damping factor of 30 would reduce a normal 15Ω output impedance to one of 0.5Ω. A high damping factor or low output impedance improves the transient response of the speaker by bringing it quickly to rest. The principle is much the same as shunting a galvanometer to bring the needle quickly to rest. A little thought here will tell you that from the laws of electro-magnetic induction there will be a current induced in the coil that will oppose its motion.

Some amplifiers have a variable damping control and the range covered is from about 30 to infinity. This helps to attain the critical damping required for less expensive speaker systems —this seems rather fruitless in a hi-fi system. A good quality speaker will gain little with a damping factor greater than about 30, especially if the speaker is properly housed.

Negative Voltage Feedback

This entails that a portion of the output voltage appears in the grid circuit of the input valve. See Fig. 5. From the circuit, and typical figures of 20 volts across the o/p transformer at full output we have

$$\begin{aligned} \text{Voltage across Rf} &= \frac{200 \times 470}{470 + 3,600} \\ &= 2.3V \end{aligned}$$

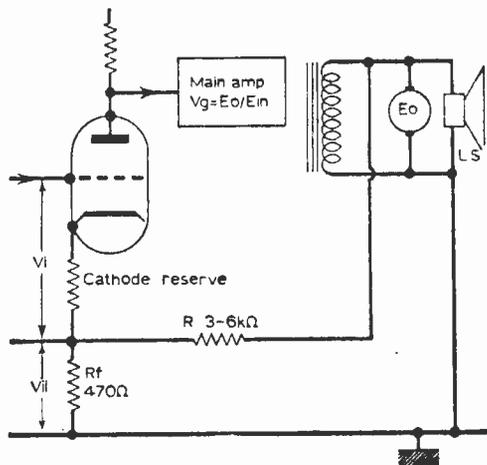


Fig. 5: Negative voltage feedback circuit.


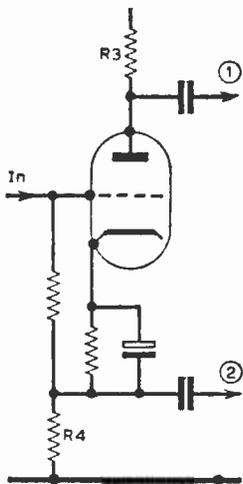


Fig. 6: A cathode-follower phase splitter circuit.

Fig. 7: A cathode-coupled phase inverter stage.

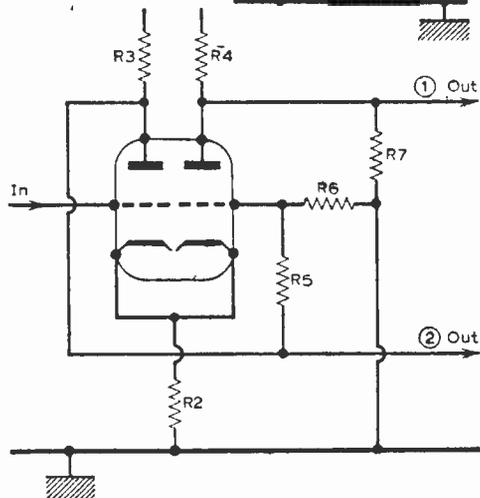

hence the total input now required for full output would be that required for full output without feedback plus 2.3V. The feedback ratio is V_i/V_{ii} .

Instability

One form is transient, and is usually triggered off by a transient signal, the sound tending to be slurry. A good amplifier should be stable even when a capacitive load of up to 2μF or an inductive load of up to 150mH is connected across the output terminals.

Phase Shift

To reduce phase shift at low frequencies the first stage is coupled directly to the phase inverter. To reduce phase shifts in the output transformer at high frequencies a capacitor is connected in parallel with the feedback resistor.

Phase Splitters

There are three basic types. (1) The Cathode Follower. (2) The Paraphase. (3) The Cathode-Coupled.

The Cathode Follower

The criteria for selecting a particular type of phase splitter are linearity, voltage gain, and maximum voltage available. The circuit is shown in Fig. 6. Briefly, the gain is less than unity and the output is fed to the output valve grids. The anode load is split up equally (R3 and R4). The linearity is best for small voltage inputs and matched values of R3 and R4 are essential. The main disadvantage is that the two outputs are at different impedances, the cathode follower being the lower. This phase splitter is also sometimes referred to as the "split load" version.

Paraphase

This consists of one output being fed directly to the grid of one of the output valves; whilst the other goes via a single stage whose sole purpose is to reverse the phase. The gain of this additional stage must obviously be unity.

Cathode Coupled

The circuit in Fig. 7 is virtually self-explanatory; but a brief description will not be out of place. The basic circuit requires that $(R5+R6)=R7$; and that $R5/R6=V_g$ where V_g is the voltage gain of the first section—this depends on valve used and values of resistors linked with the stage. The omission of the by-pass capacitor across R2 gives a better balance of the two outputs. A modification rarely seen is to split the anode load R3 into two resistors R3a and R3b say, where $R3a/R3b=V_g$. This also requires an additional capacitor to feed into the grid of the second stage from the junction of these two resistors. The modification extends the high frequency response.

Another variation of this type of phase inverter used for direct coupling to the previous stage is shown in Fig. 8. C3 is to provide correct bias conditions for the second section and together with R2 it controls the low frequency response of this stage.

Input Stages

These are straight amplifier stages with few additions. The two most common are the inclusion of a CR network in the anode of the valve: this produces an advance in phase which increases the stability of the amplifier at high

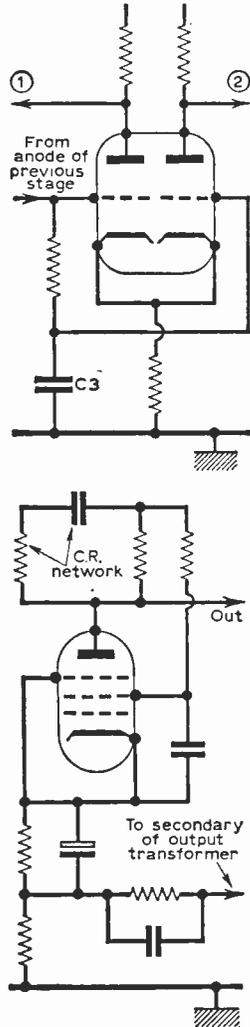


Fig. 9: An input stage of an amplifier in which a CR network in the anode circuit helps stability at high frequencies.

frequencies. The feedback loop from the output stage terminates at the cathode of this stage and occasionally at the grid. A typical stage is shown in Fig. 9. As with all stages preceding the main amplifier the noise level and distortion must be kept at a low level. This is why the resistors in the anode and grid are low noise high stability components.

Preamplifiers

Pre-amplification may be required with the main amplifiers to provide an adequate output with different inputs. The preamplifier also includes treble and bass controls, and can be designed to give compensation for the bass attenuation and treble boost which have been applied by the manufacturers during recording to obtain a better signal to noise ratio. The more comprehensive types also provide equalisation facilities for tape recording and playback.

Hum and noise introduced in the pre-amplifier count as a signal and are further amplified—they are not reduced by feedback. Fully comprehensive pre-amplifiers are very difficult to design as frequency selective networks are likely to produce large phase shifts and hence instability, if they are included in the feedback loop.

Fig. 8: A variation on the circuit of Fig. 7.

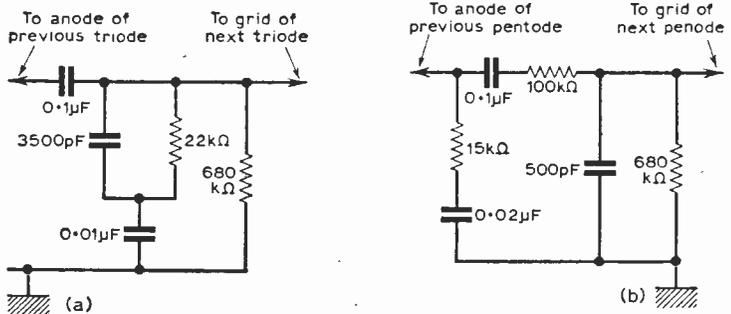


Fig. 10: Record equalisation arrangements for preamplifiers with (a) triode circuits and (b) pentode circuits.


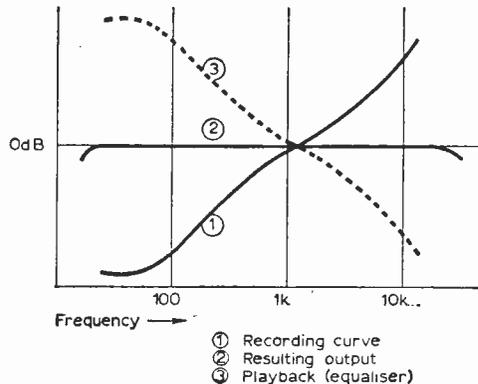


Fig. 10 (c): Illustrating graphically the action and effect of record equalisation.

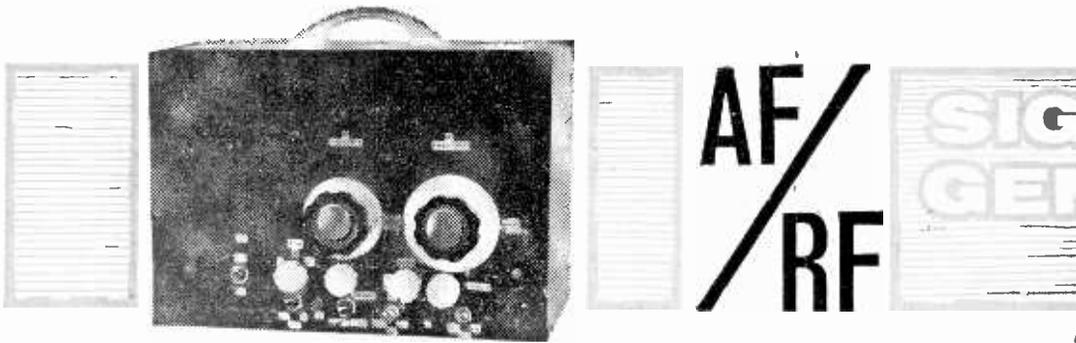

THE author's main interest lies in audio amplifiers, and in order to be able to make any worthwhile assessment of their performance, a fairly good quality audio oscillator is needed. The oscillator to be described here was designed to meet the two basic demands of moderate quality and extreme economy.

The complete signal generator is built on three 7in. x 4in. x 2½in. aluminium boxes. The first contains the power pack, which also provides excess power for use with external equipment, the second houses the audio oscillator, and the third holds a simple r.f. oscillator. If the r.f. oscillator is not required it may be omitted and the case made smaller.

THE CIRCUIT OF THE AUDIO OSCILLATOR

The audio oscillator had to be simple, stable, able to be accurately calibrated, and have a wide range. The multivibrator provides a stable, steady signal and can have a wide range when used in conjunction with a frequency dependent Wein bridge, and it is this type of oscillator that is used in many cheaper signal generators. Its main disadvantage is its poor wave-form, usually being

somewhere between a sine and a square wave.

The waveform of the multivibrator can be considerably improved by reducing the gain of one or both of the valves in the loop until a point is reached when the valve is only just oscillating. It is then producing quite a fair sine wave. In this unit, this is done by lowering the value of one of the anode resistors, R3. The value given is just sufficient to maintain oscillation over the whole range, but with some valves it may be necessary to increase it slightly to maintain oscillation.

To obtain the square waveform, an EF91 which was running with about 25V on its anode, was overdriven. This has the effect of clipping the top 80% of the sine wave, leaving quite a good square wave.

The audio oscillator does not provide a constant output over the whole range, and two compensating networks have been introduced to give a lift to frequencies above about 10kc/s, and to those below about 75c/s. R8, R9, C9 all form the treble boost circuit and R16, R17, C14 form the bass boost circuit. These components also form an attenuator to keep the output at the required level to prevent overloading.

The second half of the ECC82 (V2B) is used as a cathode follower output stage. This provides a low output impedance, the output being taken


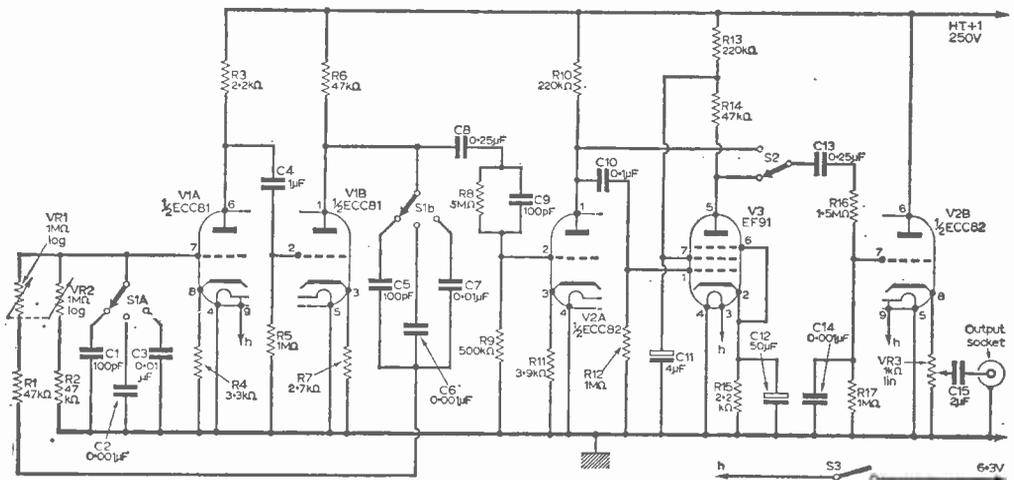


Fig. 1: The circuit of the audio oscillator section of the signal generator. This stage can be built and used as a separate unit.

AUDIO GENERATOR

C. MARSHALL

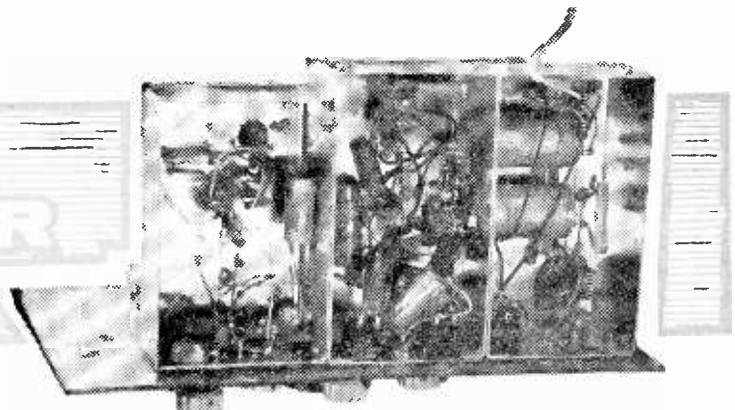

from the potentiometer in the cathode circuit via C15, a 2 μ F capacitor. The unit is therefore suitable for transistor circuits, as well as valves. The power supply circuit is quite conventional. Two h.t. feeds are provided, one for the audio, the other for the r.f.; this is to prevent interaction. A simple filter is included in the mains lead. Better smoothing can be obtained by replacing R28 by a 10H 30mA smoothing choke and reducing the two 4-7k Ω resistors (R26, R27) to 1k Ω . This also makes much better regulation. If the power pack is to be used to supply external apparatus as well, choke smoothing is essential. A larger transformer can be used if extra power is required.

ASSEMBLING THE A.F. OSCILLATOR

The chassis should be carefully marked out as in Fig. 2. The holes on the front panel should be marked with particular accuracy, as with standard sized switches and potentiometers there is only a small margin to spare. Their positioning should be checked with the components to be used before the holes are drilled. The holes on the side are counter-sunk. A small aluminium bracket is drilled to take the fine frequency control and this is firmly bolted to the chassis. The spindle should be about 2in. above the top of the chassis.

Wire-up the frequency band switch (S1a, b) then the fine frequency control VR1. 2. The oscillator valve (V1) is then wired, all leads being kept short and direct as possible to reduce stray capacities to a minimum. This valve should be tested, by connecting it to the power supply and switching on. When a pair of headphones are connected from the anode of V1a to chassis, via a 2 μ F paper capacitor, a note of variable frequency should be audible. If oscillation ceases on any part of the band, this is probably due to slightly low gain in V1, and can be remedied by slightly increasing R3. The relative positions of the component are shown in Fig. 3; the connections of the components are omitted to avoid congestion, but they may easily be found by referring to Fig. 1, the circuit diagram.

The whole of the base of V2 should then be wired, leaving C10 "flying" for the time being. The wiring of the waveform switch S2 is included in this part. When the waveform switch is put to "sine", the unit functions fully, providing a compensated output over the range 15c/s—15kc/s at a voltage of about 6V, the amplitude remaining constant on each band within \pm 3dB. This should be tested now, and if compensation is not sufficient, it should be altered. Component values for these networks given in Fig. 1 are meant only as a rough guide.

AUDIO GENERATOR COMPONENTS LIST

Resistors:

R1*	47k Ω	R10	220k Ω
R2	47k Ω	R11	3.9k Ω
R3	2.2k Ω 5% H.S.	R12	1M Ω
R4	3.3k Ω H.S.	R13	220k Ω
R5	1M Ω	R14	47k Ω
R6	47k Ω 5% H.S.	R15	2.2k Ω
R7	2.7k Ω H.S.	R16*	1.5M Ω
R8*	1M Ω	R17*	1M Ω
R9*	500k Ω		* See text

All 10% $\frac{1}{2}$ W carbon unless otherwise stated.
 VR1, 2 1M Ω log. twin-gang potentiometer.
 VR3 1k Ω lin. carbon or w.w. potentiometer.

Valves:

V1	ECC81	V2	ECC82	V3	EF91
----	-------	----	-------	----	------

Switches:

S1	2-pole, 3-way	S3	On/off toggle
S2	1-pole, 2-way		

Capacitors:

C1	100pF mica 2%
C2	0.001 μ F mica 2%
C3	0.01 μ F mica 2%
C4	1 μ F paper
C5	100pF mica 2%
C6	0.001 μ F mica 2%
C7	0.01 μ F mica 2%
C8	0.25 μ F paper
C9*	100pF mica
C10	0.1 μ F paper
C11	4 μ F electrolytic
C12	50 μ F electrolytic 12V
C13	0.25 μ F paper
C14*	0.001 μ F paper
C15	2 μ F paper 150V

All 350V unless otherwise stated
 * See text

Miscellaneous:

Two B9A and one B7G valveholders. 7in. x 4in. x 2 $\frac{1}{2}$ in. aluminium chassis. Output socket, etc.

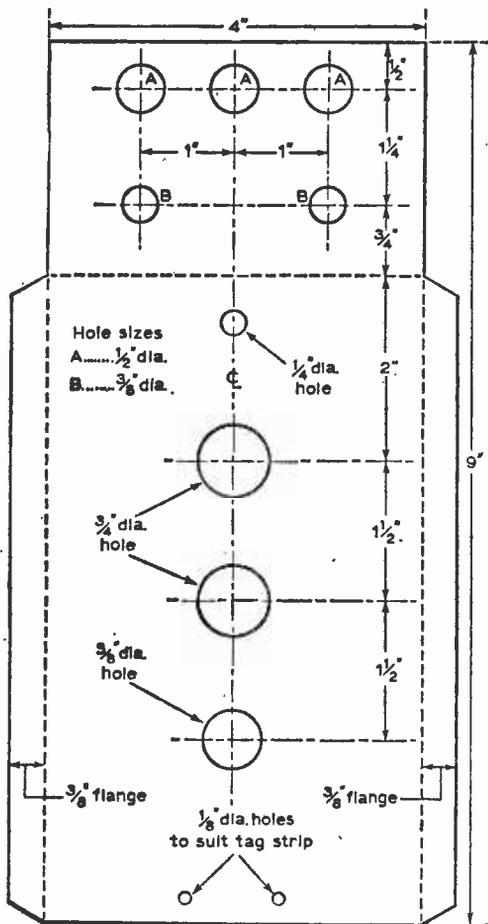


Fig. 2: Drilling layout for the audio oscillator chassis. Dimensions may have to be altered for different components.

THE COMPENSATING NETWORKS

R8, R9, C9 form a high-pass filter increasing the gain as the output falls at the higher frequencies. R9 should be 500k Ω . R8 is adjusted to give about 13V r.m.s. at the anode of V2a at a frequency of about 5kc/s. Various values of C9 may be tried, to find a value that will raise the output at the highest frequency, yet not affect the lower frequencies too much. If the output at V2a anode rises to about 15V r.m.s. at any point, R8 should be increased a little, and the value of C9 altered.

When satisfaction is gained here, attention can be turned to the low-pass filter C14, R17, R16. This boosts the output at the low frequency end of the scale. R16 is adjusted to give about 5.5V r.m.s. output at the cathode of V2b at 20c/s. C16 is then experimented with, to keep the level of signals above 50c/s, below 6V r.m.s.. If the output rises above 6V, distortion will begin in the output stage. When this stage is working correctly, final

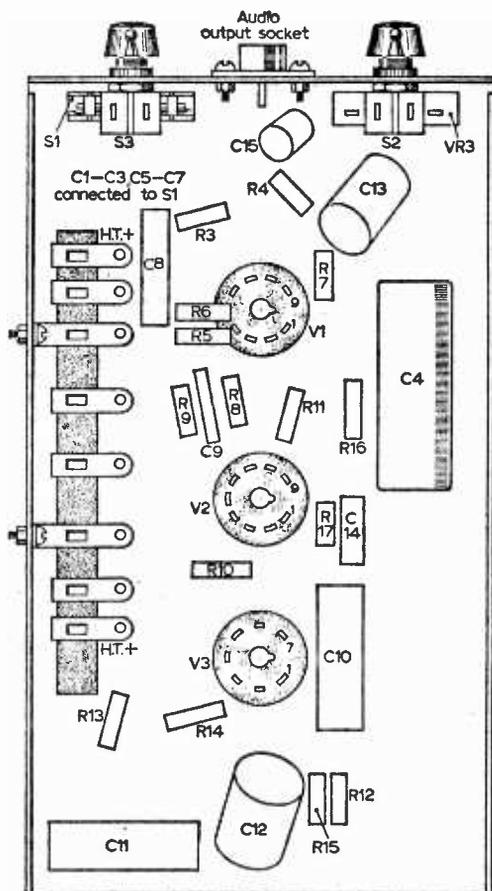


Fig. 3: Component layout from the underside. Valve-holder spigots should be taken to chassis. VR1, 2, R1, R2 are above the chassis.

adjustments should be made to the first network to give the correct output. A final check on the constancy of the output should be made.

COMPLETING THE UNIT

The EF91 (V3) should now be wired. All wiring should be as used in v.h.f. circuits—extremely short and direct. An impaired high frequency response here means a worsening of the rise time of the square wave. The EF91 is a valve designed for high frequency use, and this is one reason for its choice for this function. The other is its low cost.

When all the wiring is complete, it should be checked for constructional errors and short circuits. A pair of high impedance headphones may now be connected to the coaxial output socket and the unit fully tested if a power supply is available. If not, a suitable unit will be described next month.

Check that the frequency controls are fully

variable, that the sine/square switch works (smooth and rough note) and that the output control is functional. Check the compensation (with a sine wave, into a resistive load).

CALIBRATING THE AUDIO OSCILLATOR

When the author had built the audio oscillator he was faced with the problem of calibrating it. As he had no access to an oscilloscope he decided on using a frequency dependent Wein Bridge network. The circuit and method of using this network is given in Fig. 4a.

R1 should be as near as possible twice R2, measured on an ohmeter. Values of about 20kΩ and 10kΩ are about optimum. The frequency of the network giving null on the indicator is then given by

$$F = \frac{10^6}{2\pi RC}$$

where R is the resistance of one half of the double variable resistor VR (both halves always equal) in ohms, and

$$C = \sqrt{C1^2 + C2^2} \text{ in } \mu\text{F.}$$

If C1 = C2 then C also = C2 or C1.

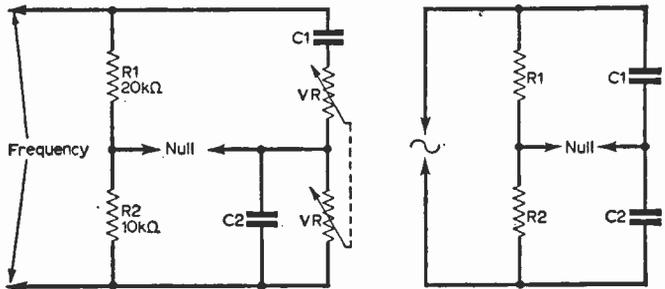


Fig. 4a (left): The frequency measuring circuit VR is a 1m Ω twin-gang log-potentiometer. Fig. 4b (right): The bridge circuit.

R1 and R2 are opposite halves of a potentiometer, measured on the ohmeter. When the value of C2 has been found, calculate the value of C, then connect up the frequency measuring bridge.

Fix a temporary scale, marked in degrees, onto the frequency control, and turn to the highest frequency and switch to the highest range. Rotate the variable resistance until a null, or lowest reading is obtained. Measure the resistance of VR and note it. Turn the control down about 30° and repeat. When the whole range has been thus noted, repeat the procedure twice more for each dial setting, then take the average. An example of the table is given in Table 1.

When range 3 has been calibrated, turn to the highest frequency of range 2. Take three resistance readings at this dial setting. Take the average

TABLE I

1st R Value	2nd R Value	3rd R Value	Average R	C	RC	2πRC	F	Range	Dial
90kΩ	92kΩ	88kΩ	90kΩ	0.013μF	1,147	7,350	136c/s	II	20°
75kΩ	85kΩ	80kΩ	80kΩ	0.013μF	1,040	6,300	159c/s	II	60°
27kΩ	29kΩ	30kΩ	29kΩ	0.013μF	380	2,400	420c/s	II	100°
15kΩ	17kΩ	16kΩ	16kΩ	0.013μF	204	1,300	760c/s	II	150°
12kΩ	12kΩ	12kΩ	12kΩ	0.013μF	156	980	1.02kc/s	II	200°
7kΩ	7kΩ	7kΩ	7kΩ	0.013μF	91	565	1.77kc/s	II	250°

The null indicator may be a low-reading a.c. voltmeter or a magic eye.

Using an ordinary bridge circuit, compare the value of C1 (a 1,000pF 1% mica capacitor). A circuit is given in Fig. 4b. Here,

$$\frac{C2}{C1} = \frac{R1}{R2} \text{ at null}$$

$$C2 = \frac{C1.R1}{R2}$$

resistance and calculate the frequency. Replace C1 and C2 by two nominally 0.01μF capacitors, and take three more resistance readings.

As the dial has not been moved, the frequency must still be the same, therefore R.C. must still be the same. From this a new value of C can be found, which is used for calibrating range 2. This value of C corresponds also to √(C1² + C2²).

Repeat the above instructions to calibrate range 2, and also the highest frequency of range 1. Replace the two capacitors by two more, of say 0.1μF., and find the corresponding value of C. Calibrate range 1.

—continued on page 73

Correspondents

I AM 14 years old and my hobbies are short wave listening and electronics. I would like to correspond with readers who share these interests.

Rashad Mohamed.

9/13 Eldhams Road,
Madras—18,
South India.

Competence

I HEARTILY agree with Mr. Collister's letter in the February issue. However, I would go further and suggest that no one can call himself a competent constructor until he has designed some of his own circuits.

No really competent constructor would ever contemplate the use of International Octal valves, except in the rare case where he needed high powered valves (i.e. 807's). Manufacturers will not even look at an I.O. valve now we are in the transistor age, so why should the constructor? I am sure that P.W. could take the lead in this, and not publish circuits using out-of-date valves. In the last 12 months, circuits using over 30 standard valves have been published in it, and considering they could easily be replaced by more efficient miniature valves, it would seem highly desirable to do so. So let's see a little less of the 6K8's, and 6V6's and more ECH81's and ECL86's.

R. A. Packer.

Sevenoaks,
Kent.

Some circuits feature Octal-type valves because so many constructors have stocks of these in their "junk boxes". We get many letters requesting designs based on these valves from beginners and "old timers" alike.—Editor.

Correspondents

I WOULD like to correspond with a boy of my own age (13½) who has a tape recorder (with a view to tape messages) and an interest in short wave radio.

M. Mouldsdale.

Forest House,
Sandiway,
Nr. Northwich,
Cheshire.


NEWS AND.

A CALLSIGN THE HARD WAY

Ronald Vincent of Cricklewood, London, took less than a year to pass the G.P.O. Morse Test and the City and Guilds R.A.E. which allows him to transmit under the callsign G3TXB. Not a remarkable feat under normal circumstances, perhaps, but a tremendous achievement if you are both blind and handless like Ron Vincent.

Mr. Vincent, who is a member of St. Dunstan's, lost his sight and his hands in World War II while serving with the Royal Artillery, but with the help and guidance of a friend, he has overcome these disadvantages and obtained his "ticket". Now with his own s.s.b. transceiver, fitted with a tuning device which audibly tells him when the transmitter is accurately tuned, he is regularly making amateur contacts throughout the world.

DO-IT-YOURSELF EQUIPMENT HOUSING

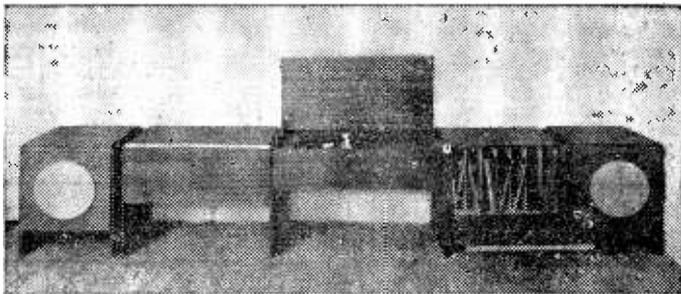

The hi-fi installation above is a combination of individual units all made from "Vipboard". "Vipboard" is veneered chipboard which is available in a large number of standard sizes. The edges as well as both faces of the board are veneered and the surfaces are sanded ready for finishing. All this greatly simplifies cabinet construction especially if "Vipboard" designs, such as these new audio equipment housings, are adopted. The installation illustrated is only one of a large number of combinations of units which can be achieved to house tuners, tape decks, record decks, amplifiers, records and loudspeakers.

Free instructions for these designs are available from G.W.E. Boards Ltd., 6 John Street, London, W.C.1, or from do-it-yourself shops.

OUT—ONE I.F. STAGE

A new development by Mullard which will probably cut down the number of i.f. stages in domestic transistor radios, was announced recently. This development is a new r.f. transistor designed for use at frequencies up to 100Mc/s, with a high-gain, low-noise, good power-efficiency performance.


The Mullard type number for the transistor is BF115. It is, in fact, a silicon epitaxial planar device having high forward gain, coupled with a low value of feedback capacitance. These features enable a high overall gain to be achieved which means that in some applications, at least one stage of i.f. amplification can be dispensed with.

.. COMMENT

POCKET BLOW-TORCH

There are times, even with radio work, when an ordinary soldering iron has not sufficient heat capacity to make a satisfactory joint in a short time, and when a healthy gas flame would do a much better job. Previously this would have involved special equipment but now Henri Picard & Frere Ltd. (34 Furnival Street, London, E.C.4) are marketing a hand-held blow-torch which screws directly on to an ordinary gas lighter refill.

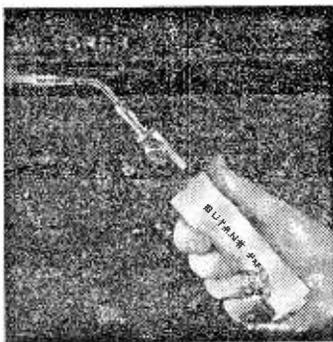The device—called the "Supa Nova"—will provide a flame up to 3in. in length, with one refill lasting from 1½ to 2½ hours.



DIAL " WHITEHALL 1212 "

When Scotland Yard moves to its new building at No. 10 Broadway, Westminster, next year, its world-famous telephone number, "Whitehall 1212" will go with it. But it will be a completely new telephone exchange which handles all calls to that number.

Standard Telephones and Cables Limited will instal the new 1,800-extension exchange as well as a 150-line automatic teleprinter exchange.

PIPELINE COMMUNICATIONS

In the face of strong international competition, an order worth well over £½ million has been placed with The Marconi Company by Sui Northern Gas Pipelines Ltd. of Karachi. This order is for telecommunications and other equipment for the first 300 miles of a new natural gas pipeline to be laid in the northern part of West Pakistan. This pipeline will run from Multan—a pipeline terminal fed from one of the world's largest natural gas fields at Sui—to the major industrial centres of North Pakistan.

The Marconi equipment, which will comprise a v.h.f. multi-channel communications system, will follow the route of the pipeline to provide full telemetry, telephone and teleprinter facilities. A standby h.f. radio system will also be installed under the contract.

NEW PORTABLE PROFESSIONAL TAPE RECORDER

A new portable professional tape receiver, which weighs only 10½ lb., is announced by EMI Electronics Ltd., Hayes, Middlesex. Facilities incorporated in the new model (type L4) include provision for a fourth magnetic head for sound sync for film recording, remote control, press-button operation and mixing for two mic. inputs.

Power is supplied by a 14V rechargeable battery and the recorder is available in half and full track versions.

Leader Changes

I WOULD like to congratulate you on the new presentation of the "leader page". I think that the way the contents are set so that the article subject, the author and the page number, can be seen at a glance, will prove very handy when looking through old issues for that "elusive article".

Keep up the good work, this new style of presentation gives new life to the magazine.

S. Milton.

Woodford Bridge,
Essex.

Ex-government Equipment

I WAS pleased to see the article on s.s.b. reception for the R1155 by Mr. McKinney (P.W., April issue).

With so much ex-government equipment still on the market, it is always good to see these modifications as they give the constructor a chance to obtain first-class equipment at a very moderate price, and apart from P.W. articles, information is almost non-existent.

G. Fry.

Harlow,
Essex.

Tapespondents

I WOULD like to tapespond with any ham/s.w.l. enthusiasts. My tape recorder is a Robuk (3-speed, 7in. spool). All tapes will be answered. My age is 37, but I will be glad to hear from any age group.

R. Moseley.

80 Gordon Street,
Northampton.

Correspondents

I AM interested in radio and electrical servicing as well as ham radio. I would be delighted to correspond with radio amateurs and Servicemen from any country.


N. J. Weerasuriya.

9/1 St. Peter's Lane,
Moratuwa,
Ceylon.

TRANSFORMERLESS

Transistor Amplifier

By A. J. McEvoy, B.Sc.

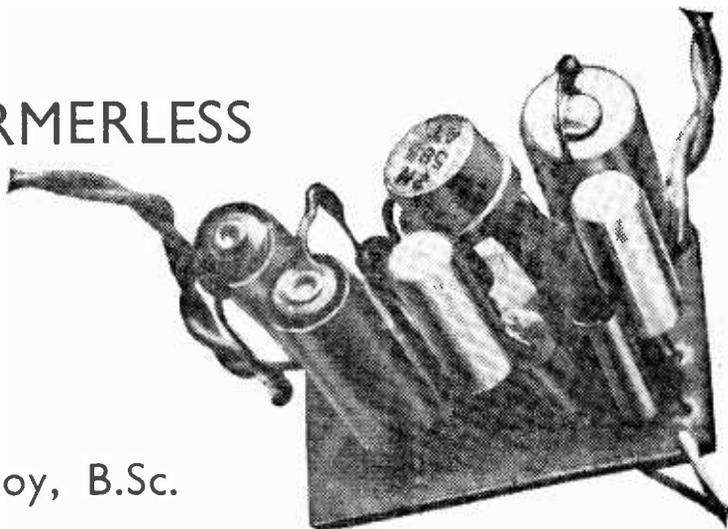

A THREE-TRANSISTOR PRINTED-CIRCUIT DESIGN

SINCE the introduction of the transistor it has become standard practise to employ a pair of transistors in class B push-pull in the audio output stages of portable apparatus. This is done in order to obtain a reasonable power output with due regard to battery economy.

Amplifier Outputs

However, at the start, expensive transformers were required, one as phase-splitter to ensure that opposite halves of the cycle were applied to each

transistor, and the other to match the output of the transistors to the loudspeaker. Some years ago, use of this second transformer was rendered unnecessary by the introduction of the single-ended push-pull arrangement using a loudspeaker of higher impedance to match the output directly. The driver transformer is also eliminated so that an even smaller and cheaper output stage is made possible with no loss of performance. In this circuit use is made of the now familiar n-p-n junction transistor. This device is a "mirror image" of the more familiar p-n-p type, that is, all the polarity-dependent properties are reversed. Therefore, if a

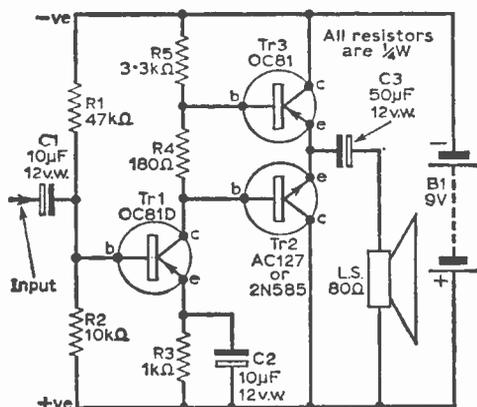


Fig. 1: The three-transistor, transformerless circuit of the amplifier.

COMPONENTS LIST

Resistors:

R1 47k Ω	R4 180 Ω
R2 10k Ω	R5 3.3k Ω
R3 1k Ω	All 1/4W carbon

Capacitors:

C1 10 μ F electrolytic 12V
C2 10 μ F electrolytic 12V
C3 50 μ F electrolytic 12V

Transistors:

Tr1 OC81D	Tr3 OC81
Tr2 AC127 or 2N585	

Miscellaneous:

B1 9V battery
80 Ω loudspeaker. Piece of copper-clad paxolin laminate. Some concentrated ferric chloride, (see text).

HERE COMES THE BIG BREAKTHROUGH IN EDUCATIONAL ELECTRONICS — BASIKITS



AND THIS IS **BASIKIT** No. 1

A brilliantly devised radio kit that can be put together with ease.

YOUR KEY TO THE FASCINATING WORLD OF ELECTRONICS

All circuits are designed around top quality components, not near equivalents. Full size printed circuits with every component position marked. Makes construction extraordinarily simple. No fiddling with microscopic connections—no inspired guesswork called for. A lavish instruction manual not only tells you how to construct your BasiKit but also advises you on its use and explains exactly how your BasiKit works.

- * VOLUME CONTROL
- * PRECISE TUNING
- * PULLS IN A HOST OF STATIONS
- * MORE THAN TWENTY FULL SIZE HIGH QUALITY COMPONENTS

59/- complete for your biggest and best ever opportunity to learn as you build!

ALSO AVAILABLE: The *BasiKit mains battery Power Unit* which powers all BasiKits. Yours for **42/6**. The *BasiKit Amplifier* that brings real full-voiced power to your BasiKit No. 1 Radio. **57/6** complete.

Watch out for more BasiKits.

ORDER YOUR **BASIKIT** ON THIS COUPON:


TO: BASIKITS DIVISION, K.L.B. ELECTRIC LTD. 335 WHITEHORSE RD, CROYDON

Please supply BK1 Radio @ **59/-**
 BK2 Audio amplifier @ **57/6**
 BK3 Power unit @ **42/6**
 Illustrated leaflet on BasiKits (enclose stamped addressed envelope)

From: **NAME** _____
ADDRESS _____
P.O. CHEQUE P.W. _____

STB2 - STB2 - STB2

ANOTHER BRILLIANT DESIGN from BRENELL

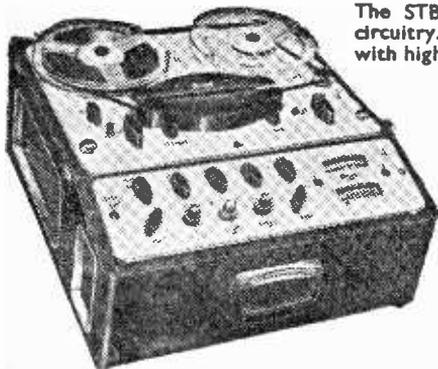

The STB2 is a masterpiece in mechanical engineering and electronic circuitry. It is a versatile mono/stereo tape recorder and has been designed with high fidelity stereo installations particularly in mind.

SPECIFICATION (STB 2/5/2)

It has all the standard Brenell features of 4 tape speeds, frequency correction at all speeds, three Papst outer rotor motors, pause control, monitoring and superimposing, 8 1/2 in. dia. reels, fast rewind, etc., plus—adjustable attenuators on all input channels to ensure perfect matching with all auxiliary equipment—dual concentric recording level and playback level controls—cathode follower output—four channel mixing on mono programme sources—twin recording and twin playback pre-amplifiers—comparison of original and recorded signal—adjustable bias level—recording facilities for 1/2 and 2/2 track—playback facilities for 1/2, 2/2, 1/4 and 2/4 track—sound on sound facilities—two edgewise meters for recording level, tape output level and bias level—optional extra: stereo power amplifiers and monitoring speakers.

ALTERNATIVE MODEL STB 2/510/2 has special deck to accommodate 10 1/2 in. N.A.B. reels.

Please write for full details to the sole manufacturer:—



BRENELL ENGINEERING CO. LTD

231/5 Liverpool Road, London, N.1

Telephone: NORth 8271 (5 lines)

INTERNATIONAL
AUDIO FAIR · STAND No. 12
DEMONSTRATION ROOM 337

© 1965

— all these and hundreds more

Mon. Sat. 9 a.m.—5.45 p.m. Wednesday 1 p.m.
Lunch 1.30 to 2.30

Special 24 Hour Express Mail Order Service

AKS1	12/8	EBF89	7/8	EF99	6/-	EZ41	7/-	PCL83	9/-	U25	10/-	UL44	6/-	5Y3G/GT	6C5GT	8/-	6U5G	7/6	12AX7	5/6		
DAP01	4/6	EOC81	4/-	EP91	4/-	EZ80	5/6	PCL84	7/-	U26	10/6	UY41	7/8	6A7	12/8	6CD80	25/-	6V6GT	7/8	12BA6	7/8	
DAP96	6/6	EOC82	5/-	EP92	4/-	EZ81	5/6	PCL85	7/8	U191	13/6	UY85	5/8	6A8	8/6	6CH16	10/-	6X4	4/6	12K7GT	6/-	
DP01	3/-	EOC83	6/6	EP98	10/-	GZ32	12/6	PCL86	10/-	U301	13/6	VF48	17/6	6A15	3/6	6C8	5/8	6X5G	9/-	12K8GT10/-	6/-	
DP96	6/6	EOC84	6/6	EP183	9/-	HL41D	12/6	PL87	11/6	U901	13/6	VB150/30	6/-	6A15	3/6	6C8	5/8	6X5G	9/-	12K8GT10/-	6/-	
DK91	5/8	ECC85	6/-	RF184	8/-		12/6	PL81	7/8	UABC80	5/8		7/-	6AM5	4/-	6P6	5/8	6X5GT	8/6	12Q7GT	6/-	
DK92	7/-	ECH32	12/8	EL33	17/6	KT66	17/6	PL82	7/8	UAF42	8/8	WR1M	6/-	6AQ5	6/6	6H6	2/-	6J30L2	12/6	12R7	12/-	
DK96	7/6	ECH32	8/6	EL41	9/-	KT81	10/6	PL83	7/8	UBC41	13/6	X01M	13/6	6AT8	4/6	6J50G/GT	7B9	21/-	19AQ5	8/8		
DL92	5/-	ECH81	7/-	EL42	9/-	KTW61	7/6	PL84	7/-	UBR0	7/6	X78	22/-	6BR0	2/6	6B7	5/8	7B7	6/8	25Z4	7/8	
DL94	7/-	ECH83	5/8	EL44	5/8	MU14	17/6	PY22/3	10/-	UBP89	7/8	K79	40/-	6BA5	5/8	6J7G	5/-	7C5	10/8	36LGT	8/8	
DL96	6/6	ECH85	6/6	EL95	9/6	N78	22/6	PY81	6/-	UCH42	8/8	IR5	5/6	6BR5	5/8	6K7G	2/-	7CA	9/8	35W4	6/8	
ELBC80	5/6	ECL82	8/8	EM80	8/-	OZ4	5/-	PY82	5/6	UCH81	7/-	IR5	4/6	6BJ6	8/8	6K7GT	2/6	7H7	8/-	35Z4	6/8	
EAP49	8/6	ECL86	8/8	EM81	8/-	POC84	8/-	PY83	7/8	UCL82	8/6	IT1	1/-	6BR7	10/8	6K8G	4/-	7B7	18/-	60C8	8/8	
EH01	3/8	EP41	7/8	EM84	8/-	POC89	8/8	PY80	8/6	UCL83	8/-	ST4	5/-	6BR8	12/6	6L8GT	9/8	7Y4	6/8	40	7/6	
ELC4L	8/-	EP80	6/-	EY51	7/6	PCF80	7/-	PZ30	12/8	UP41	7/8	SV4	7/-	6BR9	9/-	6L8G	7/8	8D3	4/-	90CG	25/-	
ED90	7/8	EP85	5/-	EY86	7/6	PCF88	8/6	RB61	3/-	UP89	7/-	SU40	4/-	6HW7	9/-	6Q7G	6/-	10F1	10/-	99CV	25/-	
EH91	8/-	EP86	7/-	EZ40	7/-	PCL82	7/8	U14	9/-	UL41	7/6	SV4G	8/-	6CA	8/6	6Q7GT	10/-	12AU7	5/-	807	9/6	

COMPLETE VALVE LIST FREE WITH ORDER

OBsolete VALVES A SPECIALITY SEND FOR QUOTATION

TERMS OF BUSINESS C.W.O. or C.O.D. 4/2 PACKING CHARGE ON ALL C.O.D. ORDERS. POSTAGE 6d. per VALVE

Mon.—Sat. 9 a.m.—5.45 p.m. Weds. 1 p.m. Lunch 1-30 to 2-30

BRAND NEW TRANSISTORS					
OC35	10/-	OC72	8/-	OC81D	5/-
OC42	6/-	OC74	8/-	OC81M/pr	12/6
OC44	5/-	OC75	8/-	OC82	8/-
OC45	5/-	OC77	8/-	OC82D	6/-
OC71	5/-	OC81	5/-	OC170	6/-
SILICON RECTIFIERS					
400 volts 350 mA					
— — — — — 7/6 each					

SETS OF VALVES				
IR5, IS5, IT4, 354, 3V4	—	—	—	Set of 4, 17/-
DAF91, DF91, DK91, DK91, DL92, DL94	—	—	—	Set of 4, 17/-
DAF96, DF96, DK96, DL96	—	—	—	Set of 4, 25/-

R.S.T. VALVE MAIL ORDER CO. Tel: MITcham 6202
211a STREATHAM ROAD, SURREY Open Daily to Callers

signal is fed equally to a p-n-p and a n-p-n transistor, both biased in class B, opposite half-cycles are amplified; a separate phase-splitter is not required.

The Circuit

The circuit employs a conventional p-n-p common-emitter driver, directly coupled to the p-n-p/n-p-n pair. R4 is inserted to eliminate crossover distortion by ensuring that both transistors draw some current throughout the cycle. The circuit of Tr1 is arranged so that, with 9V h.t., the emitters of Tr2 and Tr3 are at approximately 4.5V, and each has thus a slight forward bias, built up across R4. The characteristics of Tr2 and Tr3 should be closely matched, and such pairs are now available, although instructions are given below for a method of compensating for any mismatch.

The Printed Circuit Board

The prototype, after "breadboard" development, was assembled on a printed circuit, and this version will now be described. Fig. 2 shows the layout of the copper-clad paxolin panel used. Holes were first drilled for the components, and then those portions of the copper foil which were to form the conductors varnished. The unwanted copper was then unprotected, and was removed by etching in concentrated ferric chloride. This process was described a number of times in more detail by previous writers in this magazine.* On completion of the etching process, the circuit panel was cleaned and the components mounted and soldered to the conductors. The transistors were added last of all.

Testing

A test may now be made with a suitable signal input, e.g. a crystal mike or gram. pick-up. The unit should draw about 3mA with no input and up to 13mA at full output. This output should be comparable in volume and quality with that of conventional units. If distortion is noticed, it may be that the input signal is too high and is overdriving the unit. However, if it persists at a lower input, it is probably due to mismatch of the output transistors, and this can be compensated for to some extent by a suitable change of the working points of the output transistors. Now R3 sets the bias of, and hence the current in, Tr1; and thus it fixes the operating conditions of the output pair, since the base and emitter voltages depend on this current. Temporary substitution of a variable (say a 5kΩ, which could later be used as a volume control) would enable a suitable value to be chosen easily.

The writer considers that many constructors will have applications at hand for this type of unit, and therefore a discussion of its employment is omitted. As well as its immediate practical uses, it is an interesting introduction to the possibilities opened up by the introduction of the n-p-n transistor.

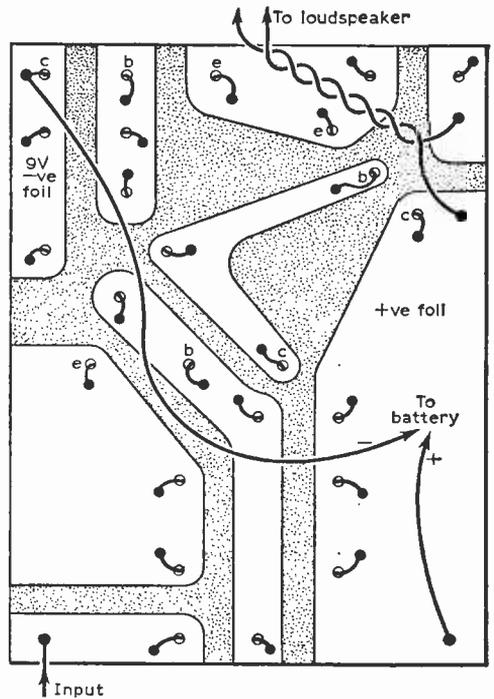


Fig. 2: The layout for the printed circuit. The shaded portions are etched clean of the copper.

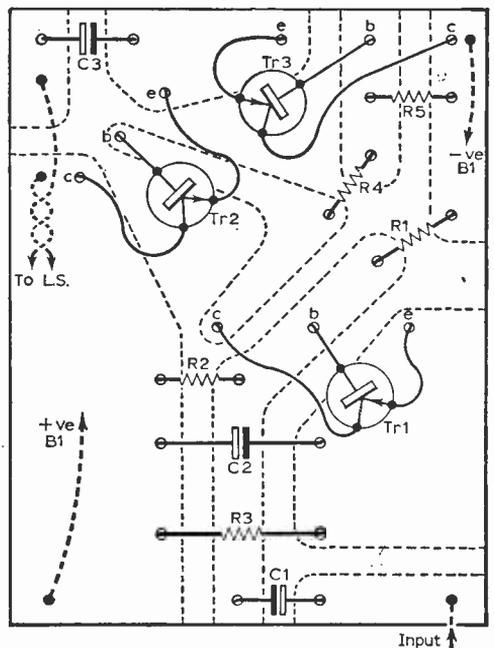


Fig. 3: The layout of components on the plain side of the board. The actual size of the board is 1 in. x 1 3/4 in.

* 'The Home Production of Printed Circuit Boards' by H. W. Rutt, October 1963, "Practical Wireless."

A COMMENTARY BY HENRY PRACTICALLY WIRELESS

No. 9 Space Age Spawn

FACT has a nasty habit of catching up with fiction. Yesterday's wonders are old hat tomorrow, so we spend today churning out prophecies, sure that some of our random shots will score bulls-eyes. Or, Cassandra-like, bemoan the march of progress that we see carried to frighteningly logical conclusions.

Our sympathy goes out to the Luddites, even modern ones who object to tape recording transcripts in the hallowed halls of justice. As one who developed part of his thick skin by indulging in a short spell of time-and-motion study Henry feels a twinge of *rapport* with enthusiasts like C. J. Collister (*Letters to the Editor*, January, 1965), who worry about the prefabrication of our hobby.

This worry goes deeper, as any student of the radio trade will know. The educationalists, for example, look with trepidation to the TV-teaching techniques that are now almost a necessity with the explosion of learning population and the dearth of competent instructors.

Until the designers bring out a monitor screen that will yell *Wake up at the back there* at the first signs of inattention we feel the day of the tutor is not over.



A monitor screen that will yell.

But let's carry it a bit farther. Why bother to learn electronics at all? After all, as IBM have already stated, the formal circuit designer cannot hope to compete with a properly programmed computer. "Reliable circuit design" (their quote) can be better performed by a machine than a man.

All right, let's all concentrate on the mystique of programming. After all, the heroes of the women's magazines, who were once airline pilots or heart surgeons just out of medical school, are now computer programmers—hadn't you noticed?


You can forget about that idea—it's already out of date! Again quoting, this time from "New Thinking" in *Electronics Weekly* of January 13: *One of the stumbling-blocks which have to be overcome in extending the use of computers is the human dislike of admitting that many routine but nevertheless skilled designs tasks can be performed better by one of these "idiot" and "stupid" machines than by arduously learned human skills.*

Given the original inspiration of a human brain the computer can be made to design a circuit, supervise the machinery that will assemble it, cross-check for errors and even modify to improve its own design.

You see where this is leading? One of these beasts can now *design and build* another.

This concept at first leaves me rather breathless . . . until I think again of that "H" factor. No matter how carefully the programmer checks his dots, how rigorously the error test is applied, it only needs one tiny fly in the ointment to throw the whole project out of gear. With automation on this scale 99.9% reliability is not enough.

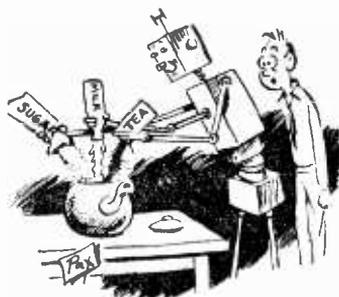Do you need more reassurance? Then turn to the fairly



Performed better by machines.

recent criticisms of both the Society of Electronic and Radio Technicians and the Television Society. At a meeting of SERT it was claimed that many well-qualified service engineers were leaving the radio trade to go into industry. Their reason was not lack of pay or slave-driving conditions but a *dislike of the design and the quality of construction of some of the current TV models.*

In the ensuing correspondence in the trade Press—which has to be seen for its acrimony to be believed—one quotable phrase was: *" . . . jungle circuits may be needed in these designs but there is no excuse for jungle layouts".*

He has a case. Any radio enthusiast who worries about his "kitchen-table construction" need only take a glance at some of the latest TV receivers to gain fresh confidence. Bits and pieces hang everywhere like decorations on a Christmas tree. All done in honour of the great god "Production Economy".

So Henry has no fears for our electronic future. Let the Tin Men proliferate as they will—but so long as a radio bod can *make* a set, instead of merely assembling a standardised receiver, his contribution is still acceptable.

This month's specials

TAPE RECORDER CENTRE

TAPE RECORDERS

The largest, most comprehensive selection: 2-track, 4-track, Mono and Stereo, Mains and Battery Models

BRENNEL

BUTOBA

B. & O.

COSSOR

ELIZABETHAN

FERGUSON

FERROGRAPH

GRUNDIG

LOEWE OPTA

PHILIPS

SABA

SANYO

STANDARD

STELLA

TANDBERG

TELEFUNKEN

TRUVOX

UHER

VORTEXION

VIKING TRANSISTOR 50-WATT AMPLIFIER

50 watts output. Superb amplifier for all music and P.A. work—ideal for guitars, groups, etc. Fully transistorised for maximum efficiency, 4 inputs with mixing facilities plus reverberation/echo chamber. Fully built and guaranteed. In strong wood cabinet covered in washable material, size approx. 22 x 10 x 6in. Output imp. 15 ohms. For operation on 200/250 v. A.C. Mains. Tape Recorder Centre Price 45 Gns. P. & P. 10/-. (\$135 + P. & P.)

VIKING 30-WATT AMPLIFIER

High quality valve model. Guitar and P.A. amplifier. A.C. Mains operated—30 watt output. 8 inputs, fitted with 4 separate volume controls for mixing, also Bass and Treble controls. 15 ohms out. British made, highest quality components used throughout, fully guaranteed. In strong portable case, size approx. 20 x 9 x 6in. T.R.C. Price 35 Gns. P. & P. 7/6 extra. (\$105 + P. & P.)

T.R.C. 20-WATT AMPLIFIER

2 inputs, mixing, Bass & Treble tone controls. British made. Fully guaranteed. A.C. Mains operated. T.R.C. Price 15 Gns. (\$45)

PLI FULLY AUTOMATIC RECORD PLAYER

B.S.R. Changer, 2 watts output. Attractive Rexine covered cabinet. A.C. Mains. Separate volume/tone controls. T.R.C. Price £11.19.6. Tax Paid. P. & P. 10/-. (\$33.50 + P. & P.)

TRANSISTOR RADIOS

Pocket size: "Bestone", Medium Waveband, 6 Transistors. complete T.R.C. Price 59/6 (\$8.35) plus P. & P.
"Gold Spot" 2 Wave Band, M.L., Telescopic Aerial. Leather Carrying Case.

T.R.C. Price £5.9.6. (\$15.40) plus P. & P.

"Binatone" 3 Wave Band, M.L.S., Telescopic Aerial. Attractive 2 Tone Plastic Cabinet.

T.R.C. Price £11.19.6 (\$33.50) plus P. & P.

"Empress" 3 Wave Band, M.L.S., Telescopic Aerial. Leather Case. T.R.C. Price 12½ Gns. (\$38.50) plus P. & P.

TAPE DECKS

Collaro Studio 2 Track 3 Speeds	£10.10.0 (\$30)
B.S.R. TD2 2 Track 33in. per sec.	£7.7.0 (\$21)
4 Track 33in. per sec.	£8.19.6 (\$25.10)

AUTOMATIC RECORD CHANGERS

B.S.R. UA1 4 4 Speed	£4.10.6 (\$13.30)
B.S.R. Slim Line 4 Speed	£4.19.6 (\$13.90)

NEWMATIC CAR RADIO

All Transistor, complete with Speaker, Baffle and Brackets. £13.2.6 Tax Paid (\$36.75)

HI-FI EQUIPMENT

Speakers

Amplifiers

Pre-amps

Pick-ups

Tuners

ARMSTRONG

GARRARD

GOLDRING-LENCO

GOODMANS

LEAK

LOWTHER

LUSTRAPHONE

QUAD

ROGERS

S.M.E.

THORENS

WHARFEDALE

W.B. STENTORIAN

Tape

AGFA

B.A.S.F.

E.M.I.

FERROGRAPH

GRUNDIG

MASTERTAPE

PHILIPS

SCOTCH BOY

TELEFUNKEN

Pre-recorded Tape

Microphones

Styli

Accessories



THE TAPE RECORDER CENTRE LTD · 82 HIGH HOLBORN LONDON WC1 · TELEPHONE CHAncery 7401

Attractive H.P. terms

WEYRAD

TRANSISTOR COILS

The P50 series remain the most popular and widely used components for Medium and Long-wave Transistors Superhets—

P50/1AC Oscillator Coil for 176 pF tuning	5/4 ea.
P50/2CC 1st & 2nd I.F. Transformers	5/7 ea.
P50/3CC 3rd I.F. Transformers	6/- ea.
All mounted in individual cans $\frac{1}{16}$ in. diam. x $\frac{3}{8}$ in. high.				
RA2W Ferrite Rod Aerial 208 pF Tuning	12/6 ea.
LFDT4 Driver Transformers	9/6 ea.
OPTIA Output Transformers	10/6 ea.
PCAI Printed Circuit Panel	9/6 ea.
Constructor's Booklet	2/- ea.

VALVE RECEIVER COILS

Our individual "H" type iron-cored coils are without equal for the construction of a wide range of receivers. For the simplest T.R.F. sets covering one or more wave-bands the Aerial and H.F. Transformer coils are ideal. The standard superhet circuit using the ever-popular triode-hexode frequency change layout would employ the Aerial and Oscillator coils and the coverage can be selected from 7 different bands ranging from 12.5 to 2,000 metres. For a really high-performance receiver an R.F. stage can be added by using the Aerial, H.F. Transformer and Oscillator Coils and a circuit is provided illustrating such a layout.

H Coils 3/9 each.

PLEASE NOTE OUR CHANGE OF NAME

WEYRAD (ELECTRONICS) LIMITED

REGENT FACTORY, SCHOOL STREET,
WEYMOUTH, DORSET

THIS WAY TO THAT BETTER PAID JOB IN RADIO

Learn Transistor radio servicing by building a set.

The National Extension College offers unique home-study courses using the very latest teaching techniques with optional residential study at weekends.

PRACTICAL RADIO

An introduction to radio practice and theory based upon the construction by the student of a radio from parts supplied by the college. An ideal starting place for higher technical skills—and a better paid job in radio!

Courses in Electronic Engineering also available.

The National Extension College is a non-profitmaking organisation created by the Advisory Centre for Education.

Write for free brochure to 1

 NATIONAL EXTENSION COLLEGE (Dept. 10)
Burlington House • Cambridge

Roitone



10 WATT MONO AMPLIFIER. Complete with built in pre-amplifier in metal case, plastic veneer covered 6 inputs, 3 each level. With equalisation each input. 1 input switch selected each level with separate vol. control for mixing. Wide range tone controls. Separate Bass and Treble. For use on 220-250v. A.C. mains. Case isolated from mains. ECL86 valves in output for low distortion. Suitable all high impedance Microphones and pick-ups. Size overall including plastic feet: Height 4 1/2 in., Width 1 1/2 in., Depth 9 1/2 in.

READY BUILT AND TESTED \$14.10.0
POST AND PACKING 5/-

3W + 3W STEREO AMPLIFIER. As above amplifier but 2 separate amplifiers giving full 3 watts each channel controls. 1 Mono-Stereo, 2 Balance, 3 Left Vol, 4 Right Vol., 5 Bass, 6 Treble. Input and output sockets at rear. A.C. mains. 220-250v. Case isolated.

READY BUILT AND TESTED \$14.15.0
POST AND PACKING 5/-

RADIOGRAM CHASSIS. Latest style 3 waveband chassis. Tandem controls through vertical glass dial 6 x 1 3/4 in. Printed Gold on Black. Controls: 1 Waveband, LW., MW., SW., GRAM., 2 Tuning, 3 Vol., 4 Tone on/off. Ferrite Rod Aerial. A.V.C. negative feedback. Full 3 watts output for 3 Q speaker. Pilot Lamp, 220-250v. A.C. mains chassis isolated. Overall size: Height 1 3/4 in., Depth 9 in., Width 8 in.

Complete with knobs. Dial Aligned and Tested. **\$9.15.0**
POST AND PACKING 5/-

TERMS: C.W.O. or C.O.D. 3/6 extra. 7-Day Money Back Guarantee. Mail Order address only.

ROITONE (Dept. P.W.)

61, HIGH STREET, OUNDERFORD, GLOUCESTER



*By using this combined Charger & AC Eliminator you can use your Transistor Radio or Intercom on domestic AC mains. **and charge Dry Batteries (000P) 9v. Ever-Ready PPS used in Transistor Radios and Intercom. Unbeatable value. Save your £££'s on batteries. P.P. 2/6. Complete with Plug, Lead, and Snap Cord.



This 4-Channel Mixer permits to mix 4 inputs, Gram., Mic., Tuner and Tape into a single output. Delightful to amateur and professional recorders alike. Post free.



This two-way Intercom is fully transistorised. Master & Sub., two units in Ivory plastic cabinets with stands. Both units operate on a single battery which lasts months. Also useful as Baby Alarm. Indispensable necessity in Home, Office, Shop, Warehouse. Size: 4 x 2 1/4 x 1 1/2 in. Complete with 60ft. long connecting wire and battery. Ready to operate. P.P. 2/6. Also 4-Way Intercom. 1 Master, 3 Sub Stations, same as above, 29.15/6, P.P. 4/6.

WEST LONDON DIRECT SUPPLIES
(Dep. FW111)
8 CHIGNELL PLACE
WEST EALING, LONDON, W.13

BOOKS REVIEWED

PHILIPS PAPERBACKS

Prepared by Centrex Ltd., Eindhoven, a subsidiary of N. V. Philips. The English editions are distributed in this country by Iliffe Books Ltd.

All have the same page size (8½in. x 5½in.) and are square back bound with glossy stiff card covers.

The first three in the series were reviewed in the January 1965 issue—the four following reviews complete the story on the first batch of titles.

||| P4: DIRECT CURRENT AND MAGNETISM

120 pp., 92 illus. Price 10s. 6d.

||| P5: ALTERNATING CURRENT AND ACOUSTICS

116 pp., 86 illus. Price 10s. 6d.

||| P6: RADIO VALVES

126 pp., 90 illus. Price 10s. 6d.

||| P7: A. F. AMPLIFICATION

109 pp., 82 illus. Price 10s. 6d.

THESE four books form the first part of a radio servicing series and are based on the original *From the Electron to the Superhet* by J. Otte, F. Salverda and C. J. Van Willigen. The present editions are edited by Edgar J. Black.

The books follow much the same pattern as the other Philips paperbacks to which, of course, they form companion volumes. All are written in simple language and each chapter is followed by a short summary of the ground covered, together with a few test questions.

Direct Current and Magnetism starts off at the ground floor, giving an easy-to-read account of basic electrical theory, the actual coverage of the volume taking in the nature of electricity and its behaviour, resistors, batteries and accumulators, magnetism and meters. This is all good basic material, highly suitable for the raw beginner. The text is enlivened with some good illustrations which go a long way to put over the points being discussed.

Alternating Current and Acoustics is really in two parts. The first deals with the origin and generation of alternating current, the construction of coils and capacitors and the effect of R, L and C on alternating current. The second part covers the nature of acoustics and the construction and operation of the various devices used for sound recording and reproduction.

Radio Valves deals in the established pattern with the equipment needed for the reception of radio waves, the amplification and demodulation of signals, power supplies and, of course, the radio valve itself.

A.F. Amplification elaborates on the audio side of things but also covers oscillators of various types, r.f. amplification, a.g.c. and some notes on measuring instruments.

It will be clear from the above that the titles of each individual volume are to some extent titles of convenience, since there is a certain amount of overlapping between the adjacent volumes. This is to be expected, perhaps, when a larger work is

being chopped up into more manageable portions. If one is buying the complete series of books no problems arise, but it might prove disconcerting for a purchaser to obtain, for instance, **A.F. Amplification**, only to find that half the book does not deal with a.f. at all!

This reservation apart, however, a reviewer can only highly commend these volumes as extremely good value for the beginner to radio work. Read in sequence they will provide a good insight into the understanding of what makes radio work.—*W.N.S.*

||| TRANSISTOR CIRCUIT MANUAL

By Allan Lytel

Published and distributed in U.K. by W. Foulsham & Co. Ltd.

255 pp., 8½in. x 5½in. Price 35s.

DO you know anything about transistors? Could you draw out from memory or know where you could lay your hands on a particular circuit? Let's see—how about a diode f.m. transmitter or a 300V regulated power supply? What about a self-excited 70Mc/s oscillator, a tunnel diode square wave oscillator or a 125W class B push-pull amplifier? Been caught out yet? Because if not it is easily possible to list over 200 different circuits using transistors with no more to hand than the "Transistor Circuit Manual".

This contains in one volume just about every conceivable application from a non-saturated flip-flop to a UJT timer. Nearly all circuits are accompanied by text which explains their function, use and the action of the circuit. There can be little doubt that this work would be a decided asset to anyone interested in semiconductor devices.

However, although the book is one of the most interesting it is also one of the most frustrating. In many of the circuit diagrams an odd component is not marked and no value is given in the text. This is particularly so in the case of coils and/or transformers. PP 174 depicts a self-oscillating mixer 6—26Mc/s and components are marked C1, C2, etc., but no values at all are given. The only information furnished is the transistor type and the battery voltage. Again, in the circuit depicted on page 103 one SCR is unmarked and a variable resistance is shown bridging two 3.9kΩ fixed resistors, but this has no value assigned to it and no mention is made of it in the text.

There are numerous omissions of this nature throughout the book and although this volume made interesting reading this lack of odd component values did rather tend to spoil what would otherwise be a very excellent book.—*D.J.G.*

TAPE RECORDERS—HOW THEY WORK

By Charles G. Westcott and Richard F. Dubbe
Published and distributed in U.K. by W. Foulsham & Co. Ltd.
177 pp., 8½in. x 5½in. Price 24s.

ATOME of knowledge suitable for all who possess, or are interested in tape recorders. Contained in its 177 pages is a full and interesting discussion of practically every aspect of the subject.

The enthusiast will gain knowledge, knowledgeable ones will gain enthusiasm and even the group of hi-fi types whose sole delight is splitting hairs over trifling details will benefit. They will, of course, continue to split hairs but after reading this volume will be able to do it with greater technical accuracy.

The book is sensibly divided into chapters in such a way that each section of the tape recorder can receive adequate discussion. Bias oscillators have a complete chapter all to themselves as have equalisation circuits, record/playback and erase heads, drive motors, and there are, in fact, 11 such divisions each treating a different facet of recording.

The text is simply written and although such a subject is of necessity technical by nature, the reader is not dragged into boring discussions with pages of higher mathematics. As this is an American publication there is a two-page introduction which carefully points out any differences in the text which might confuse.

Many interesting and useful circuits are given complete with values and there are numerous illustrations and photographs especially in the section dealing with the mechanical side.

This book can confidently be claimed as a useful addition to any bookshelf not only from an interest point of view but also as a source of reference.—*D.J.G.*

PRACTICAL STEREOPHONY, by H. Burrell Hadden

Published by Iliffe Books Ltd.
159 pp. 8½in. x 5½in., stiff cover.
Price 37s. 6d.

THE author of this book, as an instructor of the Central Programme Operations Department of the BBC, has been delving into the problems of listening for many years. *Practical Stereophony* is really a review of the subject, with much more weight given to the recording side of the technique than to the domestic situation.

Nevertheless, the amateur hi-fi fan has much to learn from his professional brothers, and this book will shatter a few illusions and perhaps instil a few ideas.

Mr Hadden is not concerned (unlike too many writers in recent years) to beat a big drum for one or other of the rival systems of stereo recording and reproduction. He begins with chapters on the theory of hearing, the stereo effect, some of the significant history, and the technical production of stereo signals.

Most weight is given to the co-incident microphone technique, with only a few paragraphs on the widely spaced omni-directional microphone method.

In a later chapter, however, various types of microphone arrangement are impartially discussed. Tape club people should be particularly interested in some of the methods, and the effects that can be achieved with quite modest equipment, intelligently sited.

Sandwiched between these chapters the author discusses some "pseudo-stereophony" devices. Surprisingly, he does not wholly deprecate the artificial production of "the true, the whole" sound. Indeed, he reveals that several methods of reflection and diffusion were used in standard broadcasting techniques for years before true stereo became practicable.

Chapter 8 (Domestic Recording) enlarges upon some of the earlier discussion of microphone techniques and goes on to describe, with circuits, pre-amplifiers and mixers. Chapter 9 (Domestic Reproduction) deals with loudspeaker placing, matching, stereophonic radio and the necessary decoders, and gives as a bonus, the circuit of the Quad 22 stereo control unit.

It is indeed regrettable, as the author implies, that stereo broadcasting is so long coming to this country, and no doubt true also that stereo tape recording will not come into its own until stereo radio is an accepted part of life. (Although just what gods Mr. Hadden propitiated when he made that anti-copyright statement we are not in a position to disclose!)

The final chapter is a short review of some systems of spreading the sound source in large auditoria, fascinating for the detail given of the problems that earlier experimenters met.

If the flavour of this book is a little donnish, that is only to be expected: it is certainly a guarantee of accuracy. Recommended reading for anyone with more than one ear!—*H.W.H.*

REQUESTS FOR INFORMATION ARE INSERTED IN THIS COLUMN ON THE UNDERSTANDING THAT READERS USING THE SERVICE UNDERTAKE TO REPLY TO ALL OFFERS RECEIVED AND TO RETURN ALL DATA NOT REQUIRED. BECAUSE OF THE LARGE NUMBER OF REQUESTS RECEIVED, ILLEGIBLE WRITING WILL AUTOMATICALLY DISQUALIFY LETTERS FROM PUBLICATION. FOR THE SAME REASON, WE CAN NO LONGER GIVE SPACE FOR REQUESTS FOR PAST ISSUES OF "PRACTICAL WIRELESS".

Str—I would be grateful if any reader could sell or loan me . . .

. . . any information on a 12V d.c. amplifier Ad. Patt. W4935, type 615A with an output of 15W and valve line-up NR77 (2) and NR73 (2).—*W. CAMPBELL, 286 Rigby Street, Camtyne, Glasgow, E.2.*

. . . the circuit diagram of the PCR3 communications receiver.—*M. GREENSHULDY, Sea Point, Cape Town, South Africa.*

. . . modification details (2m and 4m) for the R220.—*T. RICHARDS, 28 Deane Road, Liverpool, 7.*

. . . the circuit and booklet of Marconi communications receiver CR100.—*H. LEWIS, 1 Western Road, Portadawe, Swansea.*

. . . circuit, handbook or conversion data of BC 624 C.—*S. J. BULLENSE, 119a Bridge Road, East Molesey, Surrey.*

. . . the circuit diagram and any other information on the monitor type 61 oscilloscope.—*A. ANGLICAS, 49 Latrigg Crescent, Langley, Middleton.*

. . . any circuit information on the Mullard crystal calibrator No. 7 Mk. 2.—*W. BOURKE, 33 Victoria Street, Rutherglen, Lanarkshire, Scotland.*

. . . the circuit and practical diagram, with any servicing data for the No. 36 set sender and power unit.—*E. CARR, G3SDE, 21 Eastfield Crescent, Holmsley Lane, Woodlesford, Nr. Leeds, Yorkshire.*

Why

NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...


BACKED BY OUR SUPER AFTER SALES SERVICE

ROAMER SEVEN Mk III

5 WAVEBAND PORTABLE OR CAR RADIO
 ★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS
 ● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and two Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich tone, heavy duty "Celestion" speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S Waves. Real leather look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4 in. approx. The perfect portable and the ideal car radio. (Uses PP7 battery available anywhere.)

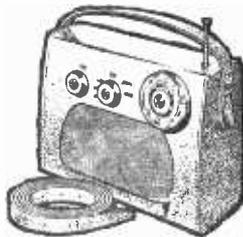Total cost of parts now only **£5.19.6** P. & P. 5/6
 Parts Price List and easy build plans 3/-




"... amazed at volume and performance... has really come up to my expectations."
 S. G. Stockton-on-Tees.

New TRANSONA FIVE

"Home, Light, A.F.A., Lux. all at good volume".
 G. P. Durham.

● 7 stages—5 transistors and 2 diodes

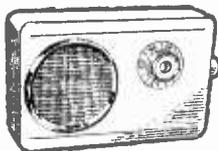Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2 1/2 in. speaker etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2 in. (battery available anywhere.)



with red speaker grille. (Uses 1280 battery available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/6
 Parts Price List and easy build plans 2/-

TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3 in. speaker makes listening a pleasure. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere.)



Total cost of all parts now only **59/6** P. & P. 3/6
 Parts Price List and easy build plans 2/-



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful

reception. Special circuit incorporating 2 R.F. Stages, push-pull output, 3 in. speaker (will drive large speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses 9V battery available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6
 Parts Price List and easy build plans 2/-

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans supplied free with sets of parts or available separately at fixed prices stated. Overseas post 10/-.

MELODY SIX



● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3 in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 3 in. ferrite rod aerial. Push-pull output.


Wonderful reception of B.F.C. Home and Light, 28 and many Continental stations, Luxembourg and many Continental stations were received loud and clear. Designed round super-sensitive Ferrite Rod Aerial and fine tone 2 1/2 in. moving coil speaker, built into attractive black case with red speaker grille. Size 6 1/2 x 4 1/2 x 3/4 in. (Uses 1280 battery available anywhere.)

Parts Price List and Total cost of all parts now only **£3.9.6** P. & P. 3/-

POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round super-sensitive Ferrite Rod Aerial and fine tone 2 1/2 in. moving coil speaker, built into attractive black case with red speaker grille. Size 6 1/2 x 1 1/2 x 3/4 in. (Uses 1280 battery available anywhere.)

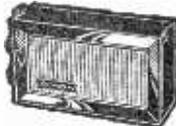

Parts Price List and easy build plans 1/6.

Total cost of all parts now only **42/6** P. & P. 3/-

ROAMER SIX NEW!!

NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND !!



● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tuneable on Medium and Long waves, Trawler band and two Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2 in. Carrying strap 2/6 extra.

★ EXTRA BAND FOR EASIER TUNING OF LUX, ETC.

Parts Price List and Total cost of all parts now only **£3.19.6** P. & P. 2/-

RADIO EXCHANGE CO.
 61, HIGH STREET, BEDFORD, Phone: 2367

Callers side entrance
 Barratts Shoe Shop
 Open 9—5 p.m.
 Sats. 10—12.30 p.m.


WIRECOMP ELECTRONICS

WIRECOMP'S BARGAIN STORE
48 Tottenham Court Road, London, W.1

Thousands of barquins: Transistor Radios—Record Players
—Tape Recorders—Radiograms—Rock Bottom Prices

FAMOUS MAKE TRANSISTOR RADIO THE "STELLA"

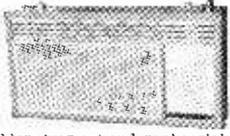7 transistor portable radio. Long, Med. and Short wavebands. Fitted tone switch and sockets for personal earphone and external aerial; chrome telescopic aerial. Uses four 1.5 V torch batts. Plastic cabinet in beige and red, size 4 x 7 x 1 1/4 in. Excellent tone, 3 in. p.m. speaker, Comp. with shoulder strap ext and aerial. Full guarantee. List price 17 gns. **WIRECOMP'S PRICE £9.19.6 P. & P. 5/-**



NEW SUPER MINIATURE POCKET RADIOS

THE SINCLAIR MICRO-6. Self-contained pocket radio. Size only 1 1/2 x 1 1/10 x 1/4 in. Complete with earphone and detailed construction data. Can be built for only Mercury cell 1/11 extra (2 required). **59/6**

THE SINCLAIR SLIMLINE. The new 2-transistor pocket radio size only 2 1/4 x 1 1/4 x 1/4 in. Micro alloy transistorised and printed circuit. All components available separately. Easy to assemble. Can be built for **49/6**

INTERNATIONAL BRAND TAPE

MYLAR BASE		Fully Guaranteed	
3 1/2 in. Triple play, 600ft.	15/-	ACETATE BASE	
4 in. Triple play, 900ft.	17/6	3 in.—150ft.	3/6
5 in. Double play, 1,200ft.	19/-	3 in.—225ft.	4/11
5 in. Triple play, 1,800ft.	35/-	3 in.—300ft.	7/6
5 1/2 in. Double play, 1,800ft.	22/6	5 in. Long play, 900ft.	10/-
5 1/2 in. Triple play, 2,400ft.	45/-	5 1/2 in. Long play, 1,200ft.	12/6
7 in. Stand play, 1,200ft.	12/6	7 in. Long play, 1,800ft.	15/-
7 in. Long play, 1,800ft.	19/6	P.V.C. BASE	
7 in. Double play, 2,400ft.	25/-	5 in. Standard play, 600ft.	8/6
7 in. Triple play, 3,600ft.	58/6	5 1/2 in. Stand. play, 840ft.	11/6

P. & P. 1/- extra per reel, 4 reels and over Post Free

PAMPHONIC 3001 INTEGRATED STEREO AMP

New, unused and fully guaranteed. Brief spec.: 7 watts per channel; freq. response 40 c/s to 20 Kc/s; sep. inputs for crystal and magnetic pick-ups, radio and tape; 15 Ohms out.; sockets for tape recording; volume, bass, treble and balance controls. For A.C. mains 100/250 V. In free standing housing, size 13 x 10 x 4 1/4 in. Makers list price £38.10.0. **WIRECOMP'S PRICE 23 GNS. Carr. and Pack 10/6**

PAMPHONIC 1002A CONTROL UNIT

Inputs for pick-up, radio, tape and microphone. Controls for volume, bass, treble, filter and selector. Fitted with 2-ECC40 valves. **WIRECOMP'S PRICE £4.19.6 Carr. and Pack 2/6**

PAMPHONIC 1002B CONTROL UNIT/PREAMP

An individual push-button correction network is provided for every important recording characteristic with separate inputs for radio, tape and mic. Max. output is 1 volt. Unpowered. Volume, bass, treble and filter controls provided. 1-EF86 and 2-ECC81 valves fitted. Size 10 x 4 x 5 in. Brand new and boxed. Makers list price £35.4.0. **WIRECOMP'S PRICE £6.19.6 Carr. and Pack 2/6**

PAMPHONIC 2001A PRE-AMPLIFIER

Sensitivity from 3 to 120 mV. for 1 V. out. Fitted with 2-ECC40 valves. Inputs for radio, tape, pick-up and mic. with pre-set level controls. Bass, treble, filter and selector controls fitted. Unpowered. Size 10 x 4 x 4 in. **WIRECOMP'S PRICE £5.19.6 Carr. and Pack 3/6**

PAMPHONIC 732A SWITCHED RADIO TUNER

Gives instant pre-selection of 3 medium wave stations and 1 long wave station (easily adjustable to your local frequencies). Self powered. For use on 200/250 V. A.C. 3 valves. Fitted with tone and volume controls for use in conjunction with a power amplifier. In metal case, size 16 x 7 x 3 in. **WIRECOMP'S PRICE £5.19.6 Carr. and Pack 7/6**

323 EDGWARE RD., LONDON, W.2. AMBassador 7115
All branches open all day Saturday Early closing Thursday

378 HARROW RD., LONDON, W.9. CUNningham 9530
Mail Orders to the above address for prompt service

THE PEMBRIDGE COLLEGE OF ELECTRONICS PROVIDES TRAINING IN RADIO AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 27th April, 1965.

This Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:
The Pembridge College of Electronics (Dept. P11)
34a Hereford Road, London, W.2.


Please send, without obligation, details of the Full-time Course in Radio and Television.

Name _____

Address _____

FREE
IN NEXT MONTH'S

**PRACTICAL
WIRELESS**

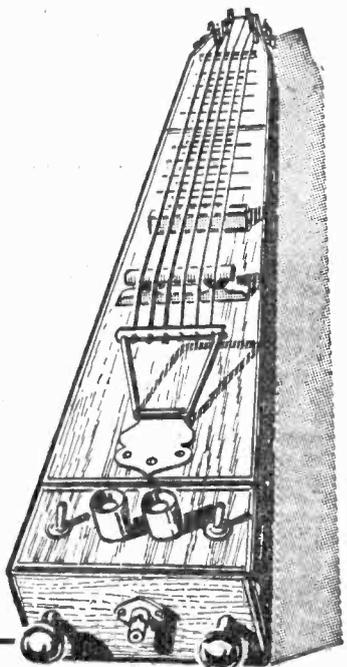

Also in next month's issue.

MODIFYING THE PCR2

How to improve the performance of these readily-obtained war surplus receivers by adding Noise Limiter, B.F.O., Product Detector, Tuning Indicator and voltage regulated built-in Power Supply.

2-TRANSISTOR RECEIVER FOR BEGINNERS

For M.W. and L.W. reception. Uses ferrite rod aerial, with provision for external aerial. May be used with loud-speaker in good signal areas.

AUTOMATIC CONTROL SYSTEM FOR HAMS

Fully automatic changeover system from send to receive with only 2 relays. "Press-to-talk" switch for listening through between words and on telephony. Adjustable time delay from a few milliseconds to 1 second.

**DOUBLE-SIDED
BLUEPRINT
TO BUILD
ELECTRONIC
HAWAIIAN
GUITAR**

Includes complete constructional details for:—

- (a) Wooden guitar body, with home-made pick-up head.
- (b) Preamplifier/control unit, built on 2in. square of Veroboard, using 3 transistors and incorporating gain, tone and rhythm controls.

**ORDER FROM YOUR NEWSAGENT
TODAY!**

To
.....(Name of Newsagent)

Please send/reserve the June issue of **Practical Wireless**, on sale May 6th, and continue until further notice.

NAME

ADDRESS

JUNE ISSUE on sale May 6th

PART FOUR

CABINET AND CHASSIS TECHNIQUES

BY F. L. THURSTON

THERE is nothing more demoralising to the enthusiast who, after hours of loving labour, produces a piece of equipment and proudly announces "I built it myself", than to receive the reply, "yes, it looks like it!".

It is probably true to say that the most neglected part of the whole constructional operation is the final finishing off of the cabinet and front panel, and it is with these stages that this part of the series is concerned.

The Cabinet

The three most generally used methods of cabinet finishing are painting, covering with Rexine or a similar material, and varnishing. The varnishing of wood has already been dealt with in P.W.*, so we shall deal only with painting and covering.

For a really professional looking job, there is nothing to beat the use of Rexine or imitation leather for radios, tape recorders, etc. Additionally, these materials are a perfect way of camouflaging inadequate carpentry such as gaping holes and badly overlapping sides!

When sticking Rexine to wood, use a glue such as Copydex, which is semi translucent when dry and will not show up if splashed on the outside of the covering by accident. On metal, use an impact adhesive.

Painting should generally be used only on test equipment and front panels. Two paints which give special finishes are worth a mention. The first is the range of Hammer Finish paints, produced by Finnigan Speciality Paints, of Mickley Square, Stocksfield, Northumberland.

These paints have a resin base, which is mixed with a suspended spray of polarised aluminium particles and blended to include silicon. As a result of the polarised particles, the paint dries completely opaque, even when only the thinnest of coats is applied to a base which is a totally different colour to the actual paint.

The "depth" of hammer, due to the unusual blend of paint, is quite astonishing. In the case of the thin coat mentioned above, a visual illusion of depth to $\frac{1}{8}$ in. is general. The silicon additive

* Cabinet Care, by M. A. Quales, August, 1964.

results in a good hard wearing glossy finish, particularly if baking is used.

The manufacturers claim that perfect finishes can be obtained using brush application. This may be so in the case of an expert, but my own experience suggests that a spray gun should be used, in which case *really* good results are obtained.

The second special type of paint worth mentioning is the well known PANL black crackle paint, produced by The Bruce Miller Co. Ltd., 249 Coastal Chambers, Buckingham Palace Road, London, S.W.1. When dry, this paint gives a deep black glossy crackle, just like you see on a good camera or piece of optical equipment, or on a piece of first-class ex. govt. electronic gear.

Formerly, this paint had to be dried in a gas oven in order to obtain the required crackle, but within the last year the blend has been modified and the paint is now air drying. Good results can be obtained even when the paint is applied with a brush. If the painted panel or cabinet is dried in a gas oven, a particularly good and hard wearing finish results. This, of course, should only be done in the case of metal equipment.


Both of the above types of paint can be laid on without an undercoat, but as with all paints, better results are obtained with an undercoat. Also, if painting on to a metal base, the wearing qualities can be considerably enhanced by stoving.

This applies with nearly all paints, but it is advisable to experiment on a piece of scrap before going on to the prototype job, to check the suitability of the particular paint for the process and to find the best temperature.

Particularly attractive results are obtained if equipment is given either a two tone or two colour finish. Greys and greens are particularly suitable.

Front Panels

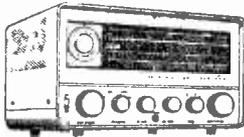The advice for painting or covering cabinets also applies for front panels. A most important point, paint will take very well if applied directly to aluminium. This is because aluminium oxidises almost as soon as it comes into contact with the



LAFAYETTE HA 63 COMMUNICATION RECEIVER

7 valves + Rectifier, 4 Bands 550 Kc/s—31 Mc/s. 'S' Meter-BFO-ANL-Bandspread Tuning 200/250V. A.C. Brand New. 24 Gns. carr. paid.



LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYZER

2 pF, 2,000 mF Ω , 2 ohms, 200 megohms. Also, checks impedance, Turns ratio, Insulation 200/250V. A.C. Brand New £15, carr. 7/6.

MAIN LONDON AGENTS FOR CODAR EQUIPMENT

STAR SR 40 COMMUNICATION RECEIVER
4 Bands 550 Kc/s—30 Mc/s. 'B' Meter-BFO-ANL-Bandspread Tuning - Built in speaker. 200/250V. A.C. Brand New. 18 $\frac{1}{2}$ Gns. Carriage 10/-.



LAFAYETTE HE-30 RECEIVERS, 9 valves, 550 Kc/s—30 Mc/s. Semi Kit form. 25 Gns. Ready built 33 Gns. Both carr. paid.


TE-22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 2 c.p.s. to 20 Kc/s on 4 bands. Square: 20 c.p.s. to 25 Kc/s. Output Imp. 5000 ohms. 200/250 v. A.C. Brand new Guaranteed. £15. Carr. 7/6.




RK140 STEREO TAPE DECKS WITH BUILT-IN PREAMPLIFIER
4 Transistors, 4 Valves. Will record or playback 1/4 Track Stereo or Mono at 7 $\frac{1}{2}$ or 3 $\frac{1}{2}$ IPS. 7in. spool size. Twin meter indicators, 4 inputs. Output 500 MW. 40-18,000 CFS., response. Size 15 x 10 x 4in. 230/250 volt A.C. operation. Brand New 42 Gns. P. P. 15/-.

S.A.E. FOR DETAILS OF ALL EQUIPMENT

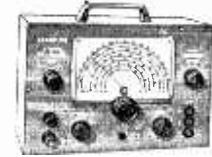

LAFAYETTE TE-20A R.F. SIGNAL GENERATOR

120 Kc/s—390 Mc/s on 6 ranges Variable R.F. and A.F. Outputs Large clear scale. Size 7 $\frac{1}{2}$ x 10 $\frac{1}{2}$ x 4in. 200/250v. A.C. Operation. Brand New £12.10.6. Carr. 5/-.

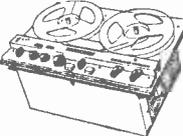

Transistor 4-channel Microphone Mixer 49/6

Mullard OC81 Two for 5/-

VARIABLE VOLTAGE TRANSFORMERS

Brand New Guaranteed. Fully shrouded. Input 230v. 50/60 c/s output 0-23v.
1 Amp £4.10.0. 2 Amp £4.10.0.
2.5 Amp £5.17.6. 10 Amp £16.10.0.
5 Amp £9.10.0. 12 Amp £18.15.0.
2.5 Amp Portable 20 Amp £32.10.0.
Metal Case with Meter Fuses etc. £9.17.6.



MODEL ZQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A, B and Ic. Equally adaptable for checking diodes, etc. Spec. A: 0.7-0.9867. B: 5-200. Ic: 0-50 microamps 0-5 mA. Resists: range for diode 200 Ω —1 MEG. Supplied complete with instructions, battery and leads. £6.19.6. P. & P. 2/6.



ARMY FIELD TELEPHONES TYPE F

Generator Bell Ringing, 2 Line Connection. With Wood Carrying Case. Fitted Batteries. Supplied Fully Tested £4.19.6. Pair Carr. 5/-.



LAFAYETTE HI-FI STEREO HEADPHONES

Cushioned Headband with cables and overload Junction Box. Brand New Guaranteed. £2/6. P. & P. 2/6.



CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters, available ex-stock, S.A.E. for illustrated list. Discounts for quantity. Available as follows.
Type M.R. 2 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " square fronts.
5mA ... 22/6 10V. DC ... 22/6
10mA ... 22/6 20V. DC ... 22/6
50mA ... 22/6 50V. DC ... 22/6
100mA ... 22/6 100V. DC ... 22/6
150mA ... 22/6 150V. DC ... 22/6
300mA ... 22/6 300V. DC ... 22/6
500mA ... 22/6 500V. DC ... 22/6
750mA ... 22/6 750V. DC ... 22/6
15V. DC ... 22/6
50V. AC ... 22/6
150V. AC ... 22/6
300V. AC ... 22/6
500V. AC ... 22/6
"S" Meter 1mA 22/6
Larger sizes available—send for lists.

500 μ A	32/6
100 μ A	22/6
200 μ A	27/6
500 μ A	26/-
60-0-500 μ A	29/6
100-0-100 μ A	27/6
500-0-500 μ A	22/6
1 μ A	22/6
2 μ A	22/6

ILLUMINATED "9" METER, 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " square front. Cal. in 8 units. 6V. lamp. 29/6. P.P. 1s. Ditto 2 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " square 39/6. P.P. 1s.



TS-76 20,000 O.P.V. PUSH BUTTON MULTI-TESTER

Large clear plastic scale, simple operation, D.C. volts up to 1,000V. A.C. volts up to 1,000V. Resistance up to 10 megohm. Current up to 250mA. Decibels, 20 to +36dB. Size 6in. x 4 $\frac{1}{2}$ in. x 2in. Complete with leads, batteries and instructions. ONLY £5.5.0. P. & P. 2/-.

TYPE 13 DOUBLE BEAM OSCILLOSCOPES

Perfect order. £27.10.0. Carr. 20/-.

AMERICAN TAPE

First grade quality American tapes. Brand new and guaranteed. Discounts for quantities.
4in. 200ft. L.P. mylar 4/-
4in. 600ft. T.P. mylar 10/-
5in. 600ft. std. plastic 8/6
5in. 900ft. L.P. acetate 10/-
5in. 1200ft. D.P. mylar 15/-
5in. 1200ft. L.P. acetate 19/6
5in. 1800ft. D.P. mylar 23/6
7in. 1200ft. std. mylar 12/6
7in. 1800ft. L.P. acetate 15/-
7in. 1800ft. L.P. mylar 20/-
7in. 2400ft. D.P. mylar 25/-
Postage 2/- Over £3 post paid.

MULTIMETERS

Brand New—Fully Guaranteed. Lowest ever prices. Supplied with leads, batteries and instructions.



MODEL TE-12
20,000 o.p.v.
0.1/0.6/30/120/600/1,200/3,000/6,000V. D.C.
0.6/30/120/600/1,200V. A.C.
0.6/6/1A/6/80/900mA
6/6K/900K/6 Meg/60 Meg Ω
5P.F.—2nF P.P. 2/6.
£5.19.6. P.P. 2/6.

MODEL NH-201
30,000 o.p.v.
0.25/1/10/50/250/500/1,000V. D.C.
0.1/30/120/500/500V. A.C.
0.3/30A/10/250mA
4.4K/500K/6 Meg Ω
99/6. P.P. 2/6.

MODEL AR-620
20,000 o.p.v.
0.1/10/50/250/500/1,000V. A.C. and D.C.
0.3/30A/10/250mA
0.1/10K/100K/1 Meg Ω
250pF—0.2mF
0-500 Henrys
92/6. P.P. 2/6.

MODEL PT-34
1,000 o.p.v.
0.1/10/50/250/1,000V. AC and DC.
0.1/100/500mA DC.
0/100K Ω
39/6. P.P. 1/6.

MODEL NH-400
10,000 o.p.v.
0.1/3/30/120/300/1,200V. D.C.
0.12/60/120/300/1,200V. AC.
0.12/0A/30/300mA DC
0.2K/200K/2 Meg Ω
100pF—2mF
79/6. P.P. 2/6.

MODEL 250J
2,000 o.p.v.
0.1/10/50/500/2,500V. DC
0.1/10/50/500/2,500V. AC
0/2 Meg Ω
0.250mF
—20 to +36dB
49/6. P.P. 2/6.

MODEL ITI-2
20,000 o.p.v.
0.5/25/250/500/2,500V. D.C.
0.1/10/50/500/1,000V. AC
0.5/0A/25/250mA DC
0.6/6K/6 Meg Ω
0.1—3mF
82/6. P.P. 2/6.

MARCONI TF144G/4 STD SIGNAL GENERATORS
65 Kc/s—25 Mc/s. Perfect order. £25. Carr. 30/-.

SILICON RECTIFIERS
250 P.I.V. 750mA 3/-
1,000 P.I.V. 6 amp 5/6
1,000 P.I.V. 850mA 7/6
600 P.I.V. 500mA 5/6
400 P.I.V. 3 amp 7/6
400 P.I.V. 500mA 3/6
150 P.I.V. 1 amp 1/6
70 P.I.V. 1 amp 3/6
95 P.I.V. 3 amp 5/6
Post extra

MINE DETECTOR No. 4A
Will detect all types of metals. Fully portable. Complete with instructions. 39/6 each. Carr. 10/- battery 8/6 extra.

BEST BUY!
Send 1/- P.O. for full catalogue and lists.
Open 9 a.m. to 6 p.m. Every day. Monday to Saturday. Trade supplied.

RECORDING HEADS
Reuter: 4 track, set of 2 19/6
Miniflux: 1 track, set of 3 29/6
Bradmatic: 1 track, set of 2 99/6
Post Extra

CLASS D WAVEMETER
No. 1 Mk. II Crystal controlled covering 1.5-5 Mc/s on 2 bands. 6V. D.C. operation. Supplied brand new with handbook, headset and case. 59/6, carr. 5/-.

G.W. SMITH & CO (RADIO) LIMITED
Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISE LEST, LONDON, W.C.2

UNUSUAL SINGLE SPEAKER SYSTEM

A CONCRETE COLUMN

An inexpensive column speaker constructed from a concrete pipe and fitted with a good 8in. or 10in. unit has attracted much interest and admiration because of its clean open sound. Complete kits of wooden fixtures are available including absorbent wadding and diffusing cone.



Price £3.15.0 for 8" model. Recommended 8" unit—Super 8/RS/DD £6.14.2 including purchase tax.

Price £4.18.0 for 10" model. Recommended 10" units—Super 10/RS/DD £10.18.8; Golden 10/RS/DD £7.17.5; 10" Bronze/RS/DD £4.12.9. Prices include purchase tax.

Suitable concrete pipes can be purchased from builders' merchants at about 12/6 and 17/6.

Descriptive leaflet free on request from



WHARFEDALE WIRELESS WORKS LTD.
IDLE BRADFORD YORKSHIRE

Grams: Wharfedel Bradford
Phone: Idle 1235/6

RETURN-OF-POST

ON CASH OR C.O.D. ORDERS

● MARTIN FM TUNER KIT

Fully transistorised, unit construction, front end and I.F. Amplifier supplied all ready built and tested. Illustrated leaflet available. £12.17.6. Deposit £2.11.6 and 12 monthly payments of 18/11. Total, credit price £13.18.6.

● MARTIN AUDIO KITS

High quality, easy to assemble Hi-Fi Units. Fully Transistorised for mono and stereo/working. All units are assembled and tested and the constructor has only to link together units chosen for any particular installation. The following mono units available.

- Unit 1 Input selector 47/6.
- Unit 2 Pre-amplifier with volume control 37/6.
- Unit 3 Mixer Unit 79/6.
- Unit 4 Pre-amplifier with tone and volume controls 62/6.
- Unit 5 Main Amplifier 10 watt, 3 ohm output £5.12.6.
- Unit 7 Main Amplifier 10 watt, 15 ohm output £6.12.6.
- Unit 8 Power unit for unit 5 52/6
- Unit 9 Power Unit for unit 7 55/-
- Unit 9A Special pre-amplifier for low output Pick-ups 55/-

Units 1, 2, 3 and 4 are available for stereo working at twice the prices shown. Smart plastic escutcheons are available for all combinations of units. Full details in the Martin Illustrated Leaflet, available free. H.P. Terms available on any combination of units.

● SPECIAL OFFER !! STEREO CARTRIDGES

RONETTE 105 Stereo/Mono Cartridge. Complete with fixing bracket and stylus. List 59/4. OUR PRICE 23/6. Post free.

● ILLUSTRATED LISTS

Illustrated lists are available on LOUDSPEAKERS, TAPE DECKS, TEST GEAR, GRAMOPHONE EQUIPMENT, AMPLIFIERS. Any will be sent free upon request.

● AMPLIFIER KITS

We have full stocks of all components for the Mullard 510, Mullard 3-J, Mullard 2 and 3 Valve Pre-amp, Mullard Stereo, Mullard Mixer. Fully detailed list on any of these sent upon request.

Instruction Manual: All Mullard Audio Circuits in "Circuits for Audio Amplifiers", 9/5 Post Free.

● LATEST TEST METERS

	Cash Price	Deposit	Monthly Payments	Credit terms	Total Credit Price
AVO Model 8 Mark III	£24. 0. 0	£4.16. 0	12 of 35/2		£25.18. 0
AVO Model 7 Mark II	£22. 5. 0	£4. 8. 0	12 of 32/9		£24. 1. 0
AVO Multimeter Mark 4	£9.10. 0	£1.18. 0	12 of 14/4		£10.10. 0
T & K TP10	£4. 7. 6	£1. 7. 6	3 of 23/4		£4.17. 6
T M K TP55	£6.11. 6	£1.11. 6	6 of 19/2		£7. 6. 6
T M K 500	£9.17. 6	£1.17. 6	12 of 15/-		£10.17. 6
TAYLOR Model 127A	£10.10. 0	£2. 2. 0	12 of 15/8		£11.10. 0

● GRAMOPHONE EQUIPMENT

ALL LATEST MODELS. ALL POST FREE

RECORD CHANGERS	Cash Price	Deposit	Monthly Payments	Credit terms	Total Credit Price
GARRARD AUTOSLIM (Mono PU fixed head)	£6.10. 0	£1. 5. 0	6 of 20/-		£7. 5. 0
GARRARD AUTOSLIM De-AT6 (Mono PU)	£11. 9. 0	£2. 6. 0	12 of 16/11		£12. 9. 0
GARRARD AUTOSLIM AT6 (Stereo/Mono PU)	£12. 5. 4	£2. 9. 4	12 of 18/-		£13. 5. 0
GARRARD AT5 LM (3000 LM) Low mass pick-up arm (9TA Stereo/Mono PU)	£12.15. 0	£2.15. 0	12 of 18/4		£13.15. 0
GARRARD AT5 (Mono PU plug-in head)	£10. 8. 2	£2. 4. 2	12 of 15/4		£11. 8. 2
B.S.R. UA15 (TCS Stereo/LP/78)	£6.19. 6	£1.14. 6	6 of 20/-		£7.14. 6
B.S.R. UA15 (TCS Stereo/LP/78)	£7. 19. 6	£1.19. 6	6 of 22/6		£8.14. 6

See our Gramophone List for details of Single Record Players and Transcription Units.

● STEREO COMPONENTS

Morganite ganged potentiometers as specified for the Mullard circuits. ★ Log/Anti-Log 500k, 1 meg., 2 meg. ★ Log/Log, 50k, 250k, 1 meg., 2 meg. ★ Lin/Lin 250k, 1 meg., 2 meg. All 10/6 each. Postage extra.

● OUTPUT TRANSFORMERS

GILSON: W0696A, W0696B, 60/6, post 2/6. W0692, 75/-, post 2/9. W0767, 92/6, post 1/6. W01736, 66/-, post 2/5. W1796A, 66/-, post 2/6. W01932, 92/6, post 3/-.
PARTRIDGE: P2667, 75/-, post 2/9. P4131, 75/-, post 2/9.
PARMEK: P2629, 52/3; P2642, 49/9; P2643, 52/3. All plus post 2/9. P2641, 32/3, post 2/-; P2928, 17/6, post 2/-; P2832, 45/3, post 2/6.

● MAINS TRANSFORMERS

GILSON: W0741A, 75/-, post 4/-; W0689, 58/6, post 2/9; W01328, 69/6, post 3/6; W01288, 69/6, post 3/6; W01566, 96/-, post 4/6; W01341, Choce, 43/-, post 2/-.
PARMEK: P2631, 39/9, post 2/9; P2630, 60/-, post 3/3; P2644, 84/-, post 4/-; P2630, 45/3, post 3/-; P2631, 62/6, post 3/3.

WATTS RADIO (Mail Order) LTD

54 CHURCH STREET, WEYBRIDGE, SURREY

Telephone Weybridge 47556

Please note: Postal business only from this address
Callers welcome by appointment

air, and the thin layer of surface oxidation acts as a barrier which prevents the paint from reaching the aluminium. It is this same barrier which makes normal soldering or welding of aluminium impossible. Paint applied directly to aluminium will peel off very easily.

To overcome this difficulty, the aluminium should be roughened slightly (mechanically, electrochemically or chemically) prior to painting, and a special primer paint should be used.

Roughening the Surface

The most satisfactory way of roughening, or etching, the metal, is by chemical means. Four possible methods are worthy of mention. (1) A caustic soda solution is made up to a strength of between 5 and 15% concentration and heated to between about 120 and 160°F. Great care should be taken when mixing the solution that no splashing takes place. The mix should be kept well away from the eyes, clothes and children. When ready, pour into a Pyrex dish or photographic developing dish, and immerse the aluminium in it.

The degree of etch will be clearly visible to the operator while the panel is immersed. The etched finish that results from the treatment is itself very attractive and is often used as a decorative finish on commercial components and articles, the pattern obtained depending on a number of factors, including time of immersion, and the temperature and strength of the mix.

When ready, remove the panel from the tank, using a pair of tongs, and wash under the running water. After drying, do not touch the treated surface with bare hands.

It may be found that, after removing the panel from the mix, areas of black smut are evident on the surface of the panel. This shows that the panel is an aluminium alloy containing copper, and should also be immersed in a solution containing 5% of nitric acid and 5% hydrofluoric acid, removed from the bath and washed again.

(2) This involves etching in a solution of 10% sodium carbonate instead of caustic soda. Both of the above methods give a finish that is decorative and useful in their own rights.

(3) This method is most recommended. Mix a solution containing 5% of anhydrous Sodium Carbonate and 1% of Sodium Chromate. Bring the solution to a temperature of between 90 and 100°C, i.e., near boiling point. Immerse the aluminium in the hot mix for between 3 and 10 minutes. On removing the aluminium from the mix, it should be seen to be covered with a uniform velvety film, which may vary in colour, depending on the composition of the alloy, from light grey to near black. Finally, the treated plate should be washed off in boiling water. Note that the aluminium should be free from grease before starting the treatment.

All of the chemicals involved should be well stoppered up in glass containers when not in use, and must on no account be allowed to come into contact with the eyes, clothing or children. When working with chemicals, always do so in a room that is well ventilated or in the open.

- An alternative (though inferior) to the above

methods, is scouring with steel wool or emery paper.

The best priming paints for use on aluminium and its alloys are the zinc chromate types, but either red oxide or red or white lead primers will prove satisfactory.

Labelling

Wording on the front panel will generally be done with transfers, and the only point that needs mentioning here is that the wording should be painted over with a coat of clear mat varnish to improve the damage resistance qualities of the finished job.

A far more permanent method of labelling a panel is with tool stamps: they consist of a short steel bar with a raised number or letter formed in one end. They are struck with a hammer to form an indentation of the character. The metal removed from the indentation should be removed with a fine file.

Marking should be carried out before painting. If the panel is subsequently baked or is not painted at all, a good way to emphasise the markings is to apply a smear of paint, in a contrasting colour to the rest of the panel, over the general area that has been marked, and then immediately wipe it off again with a rag made damp in thinners. All of the newly laid on paint will be removed except that which is out of reach of the rag in the indentations.

Alternatively, or on panels that have not been baked, a similar process can be used employing soft coloured wax pencils, rubbing well into the indentations, and removing the surplus with a clean, soft rag.

Readers who have access to photographic equipment may find the following method of marking panels with monograms, etc., of particular interest: The panel may first be anodised. The process is not difficult, but it is hardly worthwhile for a single job in which case the local electro-plating works can do it. Alternatively a priming coat of white cellulose should be laid on the panel, preferably by spray gun.

The prepared surface can now be made into a photographic plate, which is equivalent to grade 3 Bromide paper and will be developed and fixed as such, as follows. Obtain a small quantity of Johnsons Granulated Emulsion, obtainable directly from the manufacturers, Johnsons of Hendon Ltd., A 1oz. sample tin costs 15/- and will cover about 25 square feet when made up.

Pour a quantity of the emulsion in a lightproof glass container and mix with cold water in a ratio of about 90:1 by weight and stir well. Leave for about an hour, occasionally stirring with a glass rod. Place the complete container and its contents in a bath of hot water and bring the temperature of the liquid emulsion to 100°F. Strain the warm liquid through a double thickness of undressed lint into a second container which has been pre-warmed, and the mixture is ready for use.

It may be applied to the treated aluminium panel either by spray gun or by brush, but care should be taken to ensure that a very even coat is obtained. After application the panel should be left flat and allowed to dry at a temperature of less than 100°F in a dry room.

All of the above work should, of course, be carried out in a darkened room. An image can now be projected into the prepared surface, and meter dials. For radios, etc. the process can be developed and fixed in the normal way.

A similar process can be used for making up used for making really professional-looking dials on glass, but here the glass is pre-treated as follows. Dissolve 1.37 grams of Crome Alum in 100 cc of water, and then add the mix to 50 grams of Gelatin, with both solutions raised to a temperature of between 130 and 160°F. Finally, add water to make the solution up to 1,000 cc. The solution can be fixed to the glass by immersion.

General Points on Design and Accessories

One of the sure signs that a piece of gear is home-built is to see the control spindles and securing nuts and bolts sticking through the front panel. The way around this fault is to mount all the controls, etc., on a panel bolted directly to the chassis, and mount a separate front panel, nicely finished off, in front of this on stand-off mountings.

If handles must be fitted to the equipment, their style and position deserves a certain amount of thought. On test equipment, which may be used "stacked", with one piece of gear on top of another, the handles should preferably be submerged below the top of the case when not in use, and should, in any case, be flexible.

A point also worth remembering is that if fixed handles are mounted on the front panel, and

arranged so that they project out beyond the rest of the controls, they will give a measure of protection to the whole panel, and glass fronted meters in particular.

Small rubber feet, fitted to the base of pieces of test gear are very desirable, but remember that, like a stiletto heel, they result in quite a high contact pressure, and are not necessarily suitable for domestic gear that will be placed on top of furniture. Stuck on strips of rubber are to be preferred.

As mentioned in part 2 control knobs, handles, etc., can be copied and moulded in glass fibre materials. It was also mentioned that a range of pigment colourings are available to give the resins a nice finish.

With these points in mind, it is of particular interest that a range of metal fillers or pigments is available from Tiranti's, of 72 Charlotte Street, London W.1. The following range of colours are available:—Aluminium, Iron, Bronze, Copper, Gold/Brass, Nickel Silver and Lead. Available in minimum quantities of 1 lb., at which size prices vary between 4s. 3d. and 11s., these fillers are highly recommended.

The resulting glass fibre is so metallic-looking that it is often very difficult to tell that it is not metal at all. This is made even more so by the fact that the finished articles react to metal polish and that some of the "metals" will even tarnish, just like the real thing. A wide range of normal, non-metallic pigments is also available from the same firm. ■

ON THE SHORT WAVES

—continued from page 36

70ft. longwire. **SSB:** FY7YL 1105, HV1CM, KP4CL, OA7G, OA7J 1350, OD5BZ 1100, SV0WB 1100, TG9PM 1318, VE6NX 1600, VE6BR, VE6AO, VE5LM 1540, VK9ZJK 1255, VQ8AMR 1700, VK9JK 1230, W6GVM, W6LDD 1655, XW8AL 1300, ZE1BL 1830, ZLIAKM/MM 1444, YN9JUL 1310, YA4A 1315, SZ4AA 1355.

P. Coull, New Romney, went fishing with his Codar CR66 and 60ft. longwire. He collected:

14Mc/s. **SSB:** HV1CN 1045, KV4CF 1130, PY2PA 1000, TF3WHI 1055, XE1AB 1330, KV4GR 1135. **AM:** OX3HM 1445.

21Mc/s. **AM:** ET3USA 1105, VK6QL 1055, ZE1BK 1420, ZE7JR 1055, ZS6OF 1100, 5N2EBL 1155. **SSB:** KV4CX.

All the above averaged R5 S8 and SWL Coull says that at the time of writing CE0AG is still at it on SSB (1245—1430).

From Clackmannanshire **J. W. Inglis** got these with an R1155 and 66ft. longwire. 3.5Mc/s. **SSB:** OZ8KR 2340, VE1IE 2345, GD3GMH 1425, CN8AQ 2100, W2ZPO 0730. 14Mc/s. **HB0AFM** 1515, **UN1BK** 1520, **VE3CPA** 1525, **4U11TU** 1610, **W6HX** 1610, **3A2DD** 0855.

L. G. Williams (Hayes) bought a Philco 7 transistor receiver, and attached 8ft. of lighting flex to the aerial. Rewards on 14Mc/s a.m. between 1400 and 1630 included: **W1CDR**, **OK1AD**, **OE1CEW**, **OK1AGH**, **UQ2KDD**, **W6RTR**, **CT1GE**, **OH1NX**, **SM5OV**, **SP5ACE**, **W4TK**, **W3BW**, **UA1TT**, **WINB**, **SV1BT**, **W1JFJ**, **W20MM**, **W1BNS**, **K1TTY**, **W8ZO**, **W1DMN**, **W1ZRN**, **VE1IP**,

W4HDY, **EP3RT**. Wonder what it would do on the end of a three-element beam?

C. E. Lloyd informs that **Z6AP/KC4** is a genuine station and is located in Queen Maud Land, Antarctica. For those who want to know just where, it's 70°S., 2°W.

General News

An interesting contest this month is the Goose Bay QSO party. Licensed amateurs have only to work three members of the Goose Bay A.R.C. to receive a W.A.G. certificate. The contest lasts fifteen days, all bands, all modes. VO2 or VO2 are the call signs to look for if you are an SWL.

Islands and varieties active at the time of writing are Jan Meyen Island (prefix LA) where 6 or 7 are active. Willis Island: **VK4TE** is on C.W. There are three or four **VK9S** on Christmas Island and one **CR4** on Cape Verde Island. **MP4MAH** uses mainly SSB from Muscat and Oman. **KG6IG** Bonin and **KG6IF** Marcus Island are quite active. Ascension Island is on with the call **ZD8**. Also look for Jarvis and Palmyra Island (**KP6AZ**), **FB8WW** on Crozet Island, Virgin Islands (**KV4**), Macquarie Island (**VK0**), and **VU2NRA** Andaman Island. Then there's still Kerguelen Island **FB8**, New Amsterdam and St. Paul Island **FB8**, and Tokelau Island **ZM7AE**.

Contests for April include: April 3—4th International **SRKB** V.H.F. Contest, April 4th **QRP** Contest (low power), 10—11th **CQ**, **WW** **SSB** Contest, April 24—25th **PACC** Contest (phone and C.W.), 1—15th Goose Bay **ARC** **QSO** Party, May 2nd, 144Mc/s Portable Contest.

Deadline for this month is 27th.

L.K. ELECTRONICS

Under the personal direction of D. Miller, late C.B.S.

The Cheapest - The Best - The Quickest Service

SPRING SALE — Fantastic reductions for one month only

● **SCOOP! B.S.R. U.A. 25 Autochangers.** T.C. 8 Mono P.U. Brand new and boxed. Wired for stereo. Note OUR price £5.10.0. P.P. 5/-. The very very, latest model.

● **SCOOP! B.S.R. U.A. 14 Autochangers.** T.C. 8 Mono P.U. Brand new and boxed. Wired for stereo. Note OUR price £5.10.0. P.P. 5/-. Latest model.

● **SCOOP! Garrard Autoslim.** Mono P.U. Brand new and boxed. Wired for stereo. Latest model. Note OUR price £6.0.0. P.P. 5/-.

● **SCOOP! Garrard A.T.5.** Wired for stereo, inclusive of head and mono cartridge (A.T.5 is an auto transcriber). The finest changer of them all. OUR price, brand new and boxed £7.5.0 only. P.P. 5/-.

AUTOCHANGERS Single Players

E.M.I. Autostop, Mono	£5.10.0 P.P. 4/6
Garrard S.R.P. 10, Mono	£5.10.0 P.P. 4/6
E.M.I. Separate Pick-up	£3.5.0. P.P. 3/6
Transcription Units Stereo Head Mono	
Garrard 4 H.F. Stereo	£15.10.0 P.P. 5/-
Phillips A.G. 10/16 Stereo	£12.10.0 P.P. 5/-
Garrard A.T.6. Stereo	£9.19.6 P.P. 5/-
Garrard 301	£16.10.0 P.P. 5/-

● **SCOOP! Record Player Cabinets.** Two-tone, de-luxe finish with cut-out board. These are brand new and product of very famous national manufacturer. OUR price £3.5.0 only P.P. 4/6.

● **SCOOP! 3-watt Gramophone Amplifier.** Complete with Sin. Speaker, 4/6. P.P. 5/-.

The amplifier is complete, on a fabric-covered baffle board. Output transformer included. Tone and volume controls and on/off switch. Ready to switch on and play. Terrific volume. Size 12 1/2 x 6 x 3 1/2 in. back to front. For 200-250v. A.C. Output 3 watts. **WHY NOT BUILD A QUALITY RECORD PLAYER THE ABOVE PRICES SAVE YOU POUNDS.** We give you free a 12in. or 10in. L.P. Record of our choice (new) with every Auto-changer purchased.

● **SCOOP! Diodes**—over 1,000,000 in stock—ideal substitute O.A.81 vision detector.

Note OUR price £1.0.0 per 500. P.P. 2/- (in 500 lots only).

● **SCOOP! Transistor Tape Recorder.** The best obtainable by very famous manufacturer. Brand new, boxed, guaranteed Reduced from 12 gns. OUR price £7.10.0. P.P. 3/6. Complete with microphone, tape, batteries and operational booklet Features push-pull amplifier, two motors, single switch operation, pause speed, wind, rewind, record, play back. Can be used in any position, indoor or outdoor.

● **SCOOP! 5 valve Superhet Radio Chassis**—Brand new—fully aligned and tested. Valve line-up 35W4, 50C5, 12BA6, 12BE6, 12AV6. Ferrite Rod Aerial, dial, etc. OUR price 6 guineas only. P. & P. 4/6.

FREE while stocks last, attractive Plastic Cabinet in choice of pastel colours and matching Speaker to every purchaser.


● **SCOOP! Tune your T.V. receiver from your armchair.** Beautiful Remote Control Units by Ekco, Ferguson, etc. In manufacturers sealed carton, original cost 3-4 guineas. OUR price £1.1.0 only, P.P. 2/6. A thousand and one uses for this splendid equipment. Limited stocks only.

● **SCOOP! Radio Cabinets**—attractive pastel colours (plastic). Approx. size 6 x 4 x 1 in. OUR price 7/6 only. Limited stocks only.

● **SCOOP! For 1 guinea only, P.P. 2/6. Wavox Capacity Aerial.** The only aerial with additional short wave feed for hypersensitive reception on short and ultra-short waves with the Wavox A.1 performance on medium and long waves.

THE SIOUX 60 WATT MULTIPURPOSE AMPLIFIER

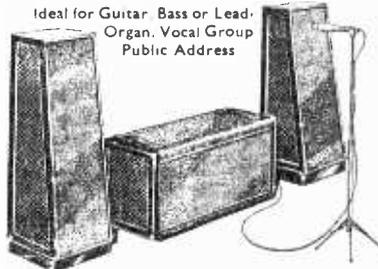Ideal for Guitar, Bass or Lead-Organ, Vocal Group, Public Address



ONLY 39 GNS.

PACKING & CARR. EXTRA

Incorporating Ten High Duty Speakers in two columns of five designed to handle efficiently the full output of Amplifier at frequencies down to 25 c.p.s. Heavily made Cabinet in two-tone Vynair. For 200-250 v. to 50 c.p.s. A.C. Mains operation. Four jack socket inputs and two independent volume controls for simultaneous connection of up to four instrument pick-ups or microphones. Level frequency response throughout the Audible Range. **OUR INCLUSIVE PRICE FOR AMPLIFIER MIKE, STAND, SPEAKERS, LEADS, ETC. ONLY 39 Gns. (REGRET NO H.P.)**

Now used by Leading Groups and Guitarists throughout the country. By request we will supply all units separately. Cabinet 10 guineas, P.P. 10/6. Amplifier 20 guineas, P.P. 5/6. Speakers (pair) 7 guineas, P.P. 5/6. All leads supplied where applicable—complete assembly time under 30 minutes. Sioux Junior Mk. II, 15 watts, as above but incorporating one 12 in. speaker. £15.15.0, P.P. 10/6.

● **SCOOP! Cartridges**—Ceramic Diamond Stylus—Stereos by Acos. Limited number only at one quarter of original price—15/- only. P.P. 1/-. While stocks last.

TRANSISTOR SECTION

● **SCOOP! A first-class 2 wave-band 8 transistor superhet chassis** by world famous manufacturer. Fully built, aligned, tested, guaranteed. Full coverage long and medium waves. Note OUR price only £6.0.0, P. & P. 2/6. Suitable speaker 10/6, P. & P. 1/6. A few cabinets can be supplied at 22/6 each. P. & P. 2/-. OUR price for the package deal £7.4.0 only, plus 3/6 P. & P. Ideal for Carolines.

S.A.E. enquiries please. Our Complete Lists 1/- only—credited against your order.

● **IF NOT ADVERTISED IT IS STILL IN STOCK**

L.K. ELECTRONICS (Victoria) LTD.

7-17 GILLINGHAM ROW, WILTON ROAD, LONDON, S.W.1

All correspondence to Number 7

SURBITON PARK RADIO

● IMMEDIATE ATTENTION TO ORDERS BY POST

MARTIN AUDIOKITS & RECORDAKITS

F.M. TUNER Units Nos. 15, 16 and 17..... Cash £12.17.6d.
 Or Dep. 5/16 and 12 m. pmts. of 18/10. (H.P. Price £13.17.6d.)
TRANSISTORISED AMPLIFIER with 5 stage input selector, pre-amp and controls, 10 watt 15 ohm amplifier and power pack. Cash £15.8.0d.
 Or Dep. 6/2/- and 12 m. pmts. of 22/6. (H.P. Price £16.12.0d.)
TRANSISTORISED AMP. ASSEMBLY as above but for 10 watts output at 3 ohms. Cash £14.5.0d.
 Or Dep. 5/7/- and 12 m. pmts. of 20/10. (H.P. Price £15.7.0d.)
 Above include front panels, knobs and instructions.
HALF TRACK RECORDAKIT AMP. (Valve) FOR STUDIO DECK incl valves, controls. Cash £11.11.0d.
 Or Dep. 4/7/- and 8 m. pmts. of 25/6. (H.P. Price £12.10.0d.)
COLLARO STUDIO DECK, 3-sp., latest. Cash £10.19.6d.
 Or Dep. 4/4/- and 8 m. pmts. of 24/6. (H.P. Price £12.0.0d.)
COMPLETE KIT with tape, mic, case & spkr. Cash £29.19.6d.
 Or Dep. 12/3/- and 6 m. pmts. of 44/- (H.P. Price £32.8.0d.)
 x TRACK ASSEMBLY inc. Collaro Studio Deck with Marriott "X" Heads, case, Type, Mic and Amp. Cash £33.19.6d.
 Or Dep. 13/6/- and 12 m. pmts. of 49/10. (H.P. Price £36.14.0d.)
 x TRACK PRE-AMP for Studio Deck. Cash £3.9.0d.
 Or Dep. 3/4/- and 6 m. pmts. of 25/8. (H.P. Price £9.8.0d.)
 x TRACK as above, self powered. Cash £3.9.0d.
 Or Dep. 3/9/- and 6 m. pmts. of 28/4. (H.P. Price £10.9.0d.)
 We are leading stockists for all Martin constructional kits. Leaflets of full ranges on request.

AMPLIFIERS · TUNERS Selection

ARMSTRONG 222 10+10w STEREO AMP..... Cash £27.10.0d.
 Or Dep. 11/0/- and 12 m. pmts. of 40/4. (H.P. Price £29.14.0d.)
ARMSTRONG 224 F.M. TUNER, powered. Cash £24.10.0d.
 Or Dep. 9/0/- and 12 m. pmts. of 32/2. (H.P. Price £24.6.0d.)
ARMSTRONG 127M, 5w Amp. with AM/FM..... Cash £26.10.0d.
 Or Dep. 10/6/- and 12 m. pmts. of 38/10. (H.P. Price £28.12.0d.)
ARMSTRONG 127S Ditto, stereo. Cash £37.10.0d.
 Or Dep. 15/0/- and 12 m. pmts. of 55/- (H.P. Price £40.10.0d.)
ARMSTRONG 227M, 10w Amp. with Am/FM..... Cash £36.15.0d.
 Or Dep. 14/7/- and 12 m. pmts. of 53/10. (H.P. Price £39.13.0d.)
ARMSTRONG 226S, 10+10w Amp. with Am/FM. Cash £61.0.0d.
 Or Dep. 26/0/- and 12 m. pmts. of 88/- (H.P. Price £65.16.0d.)
 We stock the Complete Armstrong Range.
LINEAR L.45A, 3w. Cash £6.6.0d.
LEAK 20 stereo Amp. and pre-amp. Cash £55.9.0d.
 Or Dep. 29/- and 12 m. pmts. of 80/8. (H.P. Price £59.17.0d.)
QUAD MAIN AMP. Cash £22.10.0d.
 Or Dep. 9/0/- and 12 m. pmts. of 39/- (H.P. Price £24.6.0d.)
QUAD CONTROL UNIT (Stereo). Cash £25.0.0d.
 Or Dep. 10/0/- and 12 m. pmts. of 36/8. (H.P. Price £26.0.0d.)
TRIPLETON F.M. TUNER, powered. Cash £15.14.6d.
 Or Dep. 6/3/- and 12 m. pmts. of 23/1. (H.P. Price £17.0.0d.)

LOUDSPEAKERS Selection

GOODMANS' Maxion Cash £17.10.0d.
 Or Dep. 7/0/- and 12 m. pmts. of 25/8. (H.P. Price £18.18.0d.)
GOODMANS' Axion, 10in. Cash £6.12.3d.
GOODMANS' 300, 12in., 15 watt. Cash £11.8.9d.
 Or Dep. 4/6/9 and 8 m. pmts. of 25/3. (H.P. Price £12.8.9d.)
GOODMANS' 301, 20 watt, 12in. Cash £15.19.9d.
 Or Dep. 6/4/9 and 12 m. pmts. of 27/3. (H.P. Price £17.9.9d.)
WHARFEDALE Super 12, RS/DD. Cash £17.10.0d.
 Or Dep. 7/0/- and 12 m. pmts. of 25/8. (H.P. Price £18.18.0d.)
WHARFEDALE Super 8, RS/DD. Cash £6.14.9d.
 Full ranges of Goodmans', Wharfedale, W.B. etc., always available. Leaflets on request.

MOTORS · PICK-UPS Selection

GARRARD—all models, including following:
 Autoslim 4-sp. changer, mono. Cash £6.12.6d.
 AT 6 Autoslim 4-sp. changer, mono. Cash £10.10.0d.
 Or Dep. 4/2/- and 8 m. pmts. of 23/6. (H.P. Price £11.10.0d.)
'DECCADECK' Single player, with 'Deram'. Cash £15.15.0d.
 Or Dep. 6/3/- and 12 m. pmts. of 23/1. (H.P. Price £17.0.0d.)
LAB 'A' Transcription changer. Cash £9.4.9d.
 Or Dep. 7/9/- and 12 m. pmts. of 28/11. (H.P. Price £21.6.0d.)
301 Trans. with strobe. Cash £22.10.0d.
 Or Dep. 8/1/- and 12 m. pmts. of 32/3. (H.P. Price £23.15.0d.)
PHILIPS AG 1016, with Stereo cart. Cash £13.13.0d.
 Or Dep. 5/5/- and 12 m. pmts. of 19/11. (H.P. Price £14.14.0d.)
GOLDRING GL 70, with arm but less cartridge. Cash £27.9.4d.
 Or Dep. 11/14 and 12 m. pmts. of 40/11. (H.P. Price £29.12.4d.)
BSR UA25 with cartridge. Cash £26.6.0d.
 We stock full ranges by all makers shown above

● SATISFACTION OR MONEY REFUND GUARANTEE

SURBITON PARK RADIO LTD.

48-50 SURBITON PARK ROAD, KINGSTON-ON-THAMES SURREY
KIN. 5549 · HOURS 9-6 daily (Weds. 1pm)

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1B5, 1T4, 384, 3V4, DA991, DF91, DE91, DL92, DL94, set of 4 for 15/-, DA996, DF96, DK96, DL96; 4 for 23/6.

1A7GT	7/6	6V6GT	6/6	1AC32	8/3	ECF82	7/3	MU14	5/-	TH233	7/9
1D5	6/6	6X4	3/9	DA991	3/9	ECF86	10/9	N18	4/10	U26	8/6
1H5GT	8/3	6X5GT	8/3	DA996	6/-	PCF85	6/-	N108	10/8	U26	8/9
1N5GT	8/-	7B7	8/-	DF90	6/9	ECF42	8/3	OD3	4/6	U7	8/8
1R5	4/8	7C8	7/8	DF91	8/-	ECF81	8/3	OZ4	4/8	U9	8/6
1S6	3/9	7C9	7/8	DF91	2/6	ECF83	6/6	PC85	6/9	U50	5/3
1T4	2/6	7H7	5/9	DF96	6/-	ECL80	6/2	PC97	7/-	U52	4/6
2P	19/6	7V4	5/-	DH76	3/3	ECL82	7/3	PC94	5/6	U54	8/9
3A5	6/9	10L D13	7/8	DH77	4/-	ENL86	8/-	PC98	9/6	U78	3/9
3Q4	4/10	12AT7	3/9	DH81	12/6	EP29	3/9	PCF80	6/9	U191	10/-
384	4/9	12A7	4/9	DK32	8/-	EP41	6/6	PCF82	6/9	U281	8/6
3V4	5/9	12AX7	4/9	DK91	4/9	EP40	4/3	PCF84	7/9	U291	9/-
6U40	4/9	12K7GT	4/3	DK92	8/-	EP55	5/-	PCF86	9/6	U301	11/9
6Y3GT	5/3	12K8GT	8/9	DK96	8/6	EP86	6/11	PCF805	9/6	U301	15/9
6Z40/GT84	12/6	GT	4/3	DL33	7/3	EP89	4/3	PCF82	6/6	A8080	5/9
6BM12	8/9	19R6GG	6/9	DL55	6/9	EP91	2/9	PCF83	9/-	UA472	7/9
6AL5	2/-	20L1	12/6	DL92	4/9	EP92	2/9	PCF84	8/5	UB441	6/8
6AM6	2/9	20P4	13/6	DL94	5/8	EP93	7/8	PCF85	8/6	UB481	7/3
6AQ5	6/-	20P5	11/8	DL96	6/-	EL38	11/8	PEN44	6/6	UB980	6/1
6AT6	4/-	25LGT	4/9	DM70	4/11	EL41	7/3	PEN383	9/6	UBF89	6/9
6BA6	4/9	25U4GT	1/6	DY86	6/9	EL84	5/-	PEN4VA	1/6	UC084	8/-
6BE6	4/9		10/6	DY87	8/-	EL95	5/8		12/6	UC085	6/9
6R6G	12/6	30C18	9/6	EABCO8	6/-	EM34	7/11	PEN36C		UCF80	8/6
6RH6	5/-	30FL1	9/6	EB42	8/-	EM80	6/3		15/-	UCF42	7/6
6R16	5/6	30L15	10/3	EB41	4/-	EM81	7/3	PL36	8/9	UCF81	6/8
6BW6	7/9	30P4	13/6	EB91	2/-	EM84	6/3	PL41	7/-	UCF82	7/6
6FL3	3/6	30P19	13/6	EBCC3	5/-	EM87	7/-	PL82	5/6	UCL83	9/9
6FL4	9/-	30PL1	9/6	EBM41	7/3	EV51	6/-	PL83	6/-	UF41	7/3
6J7G	4/8	30PL13	10/8	EBF80	6/-	EV86	5/6	PL84	6/3	UF99	6/3
6G7G	1/6	30PL14	11/6	EBF83	7/6	EZ40	6/6	PX35	7/6	UL41	7/6
6R7GT	5/3	35A5	14/-	EBH89	6/9	EZ41	6/6	PY32	9/-	UL44	15/-
6K8G	4/3	35L0GT	6/3	EBL21	10/6	ER80	4/-	PY33	9/-	UL84	6/3
6K8GT	7/8	35V4	4/9	ECC40	6/9	EZ81	4/6	PY80	5/3	UY21	7/-
6P2	9/6	36ZAGT	5/6	ECC81	3/9	FW4500G	6/3	PY81	6/9	UY41	4/9
6U7G	4/9	38U4	9/6	ECC82	4/9	GZ33	14/6	PY82	5/1	UY85	5/8
6G7GT	4/9	AC/VP212/8	10/6	CC83	7/-	GZ37	3/9	PY88	5/9	VP14	12/6
6BL7GT	4/9	BC36	4/6	ECC84	6/3	KT32	4/9	PY88	7/3	W76	3/8
6SN7GT	4/9	CL33	9/6	ECC85	6/3	KT76	8/-	PY800	8/6	W77	2/6
6Y6G	3/9	CL91	12/6	ECF80	7/6	ME140015/-	TH21C			9/6	7/7

READERS RADIO

24 COLBERG PLACE, and at 85 TORQUAY GARDENS, STAMFORD HILL, REDBRIDGE, ILFORD, LONDON, N.16. STA 4587 | ESSEX. CRE 7441
 Post 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d extra. Any C.O.D. Parcel 4/3 extra.

THE Radio Constructor

TWO SHILLINGS & THREEPENCE

APRIL issue, now on sale, features The 'ATHENIAN', a 15-2,000 metres Beginner's Receiver

FROM YOUR NEWSAGENT

CLUB RALLY

ACTON, BRENTFORD AND CHISWICK RADIO CLUB
Hon. Sec.: W. G. Dyer, G3GEH, 188 Gunnersbury Avenue, Acton, London, W.13.

At the meeting on Tuesday, 13th April, at 66 High Road, Chiswick, there will be a tape recorded lecture with colour slides, on 160m DX working, by W15B. This should have been given on 16th March but had to be postponed.

BURSLEM AMATEUR RADIO CLUB
Hon. Sec.: J. R. Sherratt, G3SAJ, 23 Ash Way, Ash Bank, Bucknall, S.O.T.

The Club will be on the air looking for contacts and renewing old ones with Mobiles coming into the district en route to the Midlands Mobile Rally. Call signs: Top Band: G3HVI (south), G3SAJ (east), G3COY (west) and G4QD (north).

CHESTER AND DISTRICT RADIO SOCIETY
Hon. Sec.: P. J. Holland, Field House, 19 Kingsley Road, Gt. Boughton, Chester.

On 13th April, Mr. H. Morris, G3ATZ, will give a second talk for the beginners, and on the 20th, Mr. B. Fallows, G3OWY, will give a demonstration of v.h.f. converters.

CLIFTON AMATEUR RADIO SOCIETY G3GHN
Hon. Sec.: J. Rose, G3OGE, 63 Broomfield Road, Beckenham, Kent.

The "junk sale" began on 15th January and had to be continued on the 22nd. The following week, SWL D. Reed presented a quiz. Plans are now in hand to extend the activities of the Club station to the h.f. bands.

Meetings are held every Friday at 8 p.m. at 225 New Cross Road, London, S.E.14.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY
Hon. Sec.: F. C. Ward, G2CVV, 5 Uplands Avenue, Littleover, Derby.

At the A.G.M. on 3rd February, B. J. Speakman was elected Chairman and J. C. Brown, G3JFD, Vice-Chairman. It was reported that membership was 175, out of which 72 are licensed.

The Annual Dinner and Dance was held on 13th February and over 180 attended. Mr. J. Clarricoats, O.B.E., G6CL, Secretary of the International Amateur Radio Union, Region 1, was among the Guests of Honour.

FAREHAM AMATEUR RADIO CLUB
Hon. Sec.: N. Carless, G3EER, 16 Waterloo Road, Alverstoke, Gosport.

Club H.Q. is now situated at the Clubroom, Bugle Hotel, West Street, Fareham, and a regular monthly session of Morse and Technical Classes is now in full swing. Meetings are held first Sunday in each month at 7.30 p.m.

HARLOW AND DISTRICT RADIO SOCIETY
Hon. Sec.: G. O'Donald, G3TLJ, 'Great East', Roydon Road, Roydon, Harlow, Essex.

Our Mobile Rally will be held on 26th September. The venue, as last year—Magdalen Village Hall, near Harlow.

HUDDERSFIELD RADIO CLUB
R. Highton, 5 Brian Avenue Dalton, Huddersfield, Yorkshire. The Club held an exhibition of home-built equipment, and is preparing for other exhibitions, competitions etc. A Club station

will be formed at a favourable QTH in the near future.

MELTON MOWBRAY AMATEUR RADIO SOCIETY
Hon. Sec.: D. W. Lilley, G3DFD 23 Melton Road, Ashfordby Hill, Melton Mowbray Leicestershire.

On 25th March there was an illustrated lecture, based on Mullard film strips, entitled Basic Valve Circuits. There will be an 8mm cine film evening and a Ragchew.

MID-WARWICKSHIRE AMATEUR RADIO SOCIETY
Hon. Sec.: H. C. Loxley, 5 Guy Street, Warwick.

On 5th April, Part 4 of the Radio Theory lecture was held. This was entitled Valve Performances.

There will be no meeting on 19th April (Easter Monday).

NORTHERN HEIGHTS AMATEUR RADIO SOCIETY
Hon. Sec.: A. Robinson, G3MDW, Candy Cabin, Ogden, Halifax.

On 14th April, the A.G.M. will be held and on the 28th there will be a discussion on the N.F.D.

There will be a visit to Manchester Civil Airport on 12th May.

OXFORD AND DISTRICT AMATEUR RADIO SOCIETY
Hon. Sec.: B. Green, G3PMI, H.Q., Cherwell Hotel, Water Eaton Road, N. Oxford.

The Annual Dinner was held in March, and the event of the year, the 10th Anniversary Mobile Rally will be held on 11th July.

PETERBOROUGH AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: D. Byrne, G3KPO, Jersey House, Eye, Peterborough.

A talk on Radio Astronomy will be held on 7th May. Members are organising a Mobile Rally on 4th July at Peterborough.

PRESTON AMATEUR RADIO SOCIETY
Hon. Sec.: C. Noblet, 178 West Park Avenue, Ashton, Preston Lancashire.

At the meeting on 9th March, there was a discussion on National Field Day, and on the 23rd, a talk by the Club Secretary entitled Exchanging QSLs. There will be a discussion on Receivers on 13th April.

RADIO SOCIETY OF HARROW
Hon. Sec.: C. J. Rees, G3TUX, 17 Colburn Avenue, Hatch End, Pinner, Middlesex.

Meetings are held every Friday in the Science Lab. of Roxeth Manor School, South Harrow. On 12th March there was a lecture on Ham Band Convertors, and on the 26th a Junk Sale.

READING AMATEUR RADIO CLUB
Hon. Sec.: N. Taylor, G3TOQ, 83 Stoneham Close, Reading, Berkshire.

At the A.G.M., the following officers were elected: Chairman, C. Nairn, G3GHE; Treasurer, B. Carter, G3AAG; Vice-Chairman, Lt. Col. N. Bower, O.B.E., G5HZ; and Hon. Sec., N. Taylor, G3TOQ.

SALOP AMATEUR RADIO SOCIETY
Hon. Sec.: Dr. K. E. Jones, G3RRN, Greystones, Shrewsbury Road, Church Stretton, Salop.

L. F. Ivin, G5IC, gave a talk on 11th February, entitled Neutralisation. J. N. Walker, G5JU, gave a talk on Receivers, and demonstrated the Eddystone EA12 and EC10 receivers. There will be a Construction Competition on 8th April.

A.F./R.F. SIGNAL GENERATOR

—continued from page 51

Frequencies can now be calibrated, and a graph drawn for each band, plotting frequency against dial reading. A new dial can then be drawn, giving frequency directly. The accuracy of fixing the position of the dial can be checked by taking one more frequency check with the bridge.

The accuracy of the calibration depends on two things. Firstly upon the accuracy with which the resistances are measured. A multimeter, battery and series limiting resistor will do the job well, if 1% resistors, a new battery and a slide rule are

used. The second factor is the accuracy of the capacitors. This depends on the accuracy of the original C1 and the finding of the values for C. Accuracy of about 2% can be obtained with some trouble and patience.

The output control is best given a linear scale of 0—10, as output varies from one band to another.

At this stage the audio oscillator is complete and ready for use. However next month, the construction of the mains unit and calibration of a suitable r.f. oscillator will be described, to make the complete generator fully versatile.

PREPARING R.A.E. FOR THE

BRIAN ROBINSON.

7. MULTIELECTRODE VALVES; VALVES AS OSCILLATORS

7.1 Interelectrode Capacitances in the Triode

IN the triode there are three interelectrode capacitances which affect the performance of the valve. These interelectrode capacitances are present because the various electrodes act like the plates of a normal capacitance.

In the triode there will be interelectrode capacitances between the anode and the grid; the anode and the cathode; the grid and the cathode. The value of these capacitances is generally only of the order of a few picofarads — pF (micromicrofarads — $\mu\mu\text{F}$) but at radio frequencies their reactance is very low, and this means that a virtual short circuit can exist between the electrodes at r.f. Fig. 59 shows in diagram form the various interelectrode capacitances in a triode.

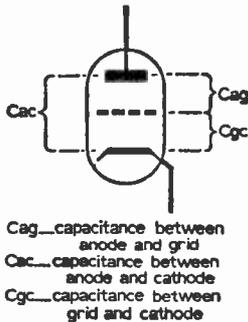


Fig. 59: Interelectrode capacitances in the triode valve.

It is easy to see therefore that if a triode is to be used as an amplifier or oscillator at r.f. (radio frequencies), the capacitance between grid and cathode could short circuit the input circuit, and the capacitance between the anode and cathode could short circuit the output circuit.

Obviously some way has to be found of reducing interelectrode capacitances and one simple way is to introduce a second grid called the *screen grid*.

7.2 The Screen Grid Valve or Tetrode

The *tetrode* is a four electrode valve which has a *screen grid*. This screen grid is positioned between the control grid and the anode and acts

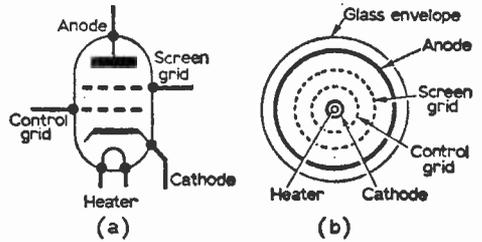


Fig. 60 (a): Circuit representation of a tetrode; (b) a horizontal cross-section of the actual valve.

as an electrostatic shield which prevents coupling between the anode and control grid.

A positive voltage must be applied to the screen and this attracts electrons from the cathode. Most of these electrons are travelling so fast that they pass through the mesh of the screen and are attracted towards the anode. Some of the electrons however strike the screen and therefore *screen current* flows. Some form of connection of the screen to the cathode must, however, be made if the screen is to be an efficient shield. This connection will generally take the form of a capacitance called a *by-pass* capacitance which has a reactance of only a few hundred ohms at the frequency being used.

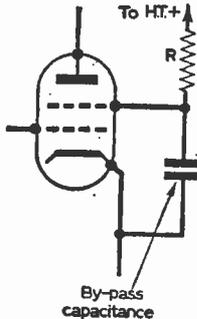


Fig. 61: Connection of the screen grid by-pass capacitance.

One of the effects of adding a screen grid is that the anode resistance of the valve becomes very high, e.g. in the region of $20,000\Omega$ to $2\text{M}\Omega$. It should be remembered that the screen grid is positioned nearer the cathode than the anode.

7.3 Anode Characteristics for the Tetrode

The circuit used to obtain the anode characteristics for the tetrode is the same as that used to obtain the anode characteristics for the triode, (see article 6); except that the screen grid is connected to the h.t. through a resistance of a few thousand ohms. A typical graph of the result of plotting V_a against I_a is shown in Fig. 62.

The screen current of the tetrode is shown by a dotted line also in Fig. 62, it will be noticed on the graph that until an anode voltage of about 65 is reached the screen current is greater than the anode current.


Brand new individually checked and guaranteed VALVES

AC/HL 4/8	D1840 8/-	EF91 2/9	KT63 4/-
AC/PL 6/-	D1849 15/-	EP92 2/-	KT66 12/6
AC/SPEN 5/-	EF9F 25/-	EF95 5/-	KT67 8/6
AL60 5/-	EL148 2/6	EF78 3/-	KT68 20/-
ARS 5/-	E1266 50/-	EF184 8/-	KT69 15/-
AR3 3/-	EL145 30/-	EF185 300/-	KTW61 4/6
AR/12 2/6	E1534 12/6	EL32 3/9	KTW63 2/6
AR/21 7/-	EA50 1/-	FL34 10/-	KTZ 6/-
AR/24 3/6	EA73 7/-	FL36 5/-	KTZ63 5/-
AR/34 4/-	EAB080 5/-	EL38 17/6	LP2 10/-
ART/1 6/-	EA91 3/6	EL41 7/-	ML10 6/-
AT/7 2/3	EA92 3/-	EL42 3/-	ML16 6/-
AT/7 5/6	EH34 1/6	EL50 8/-	N106 8/-
AU 7 55/-	EB91 3/-	EL81 8/-	NE17 7/-
BL63 10/-	EBC23 6/-	EL83 6/3	NGT2 10/-
B84 9/-	EH41 7/-	EL84 5/-	OP3 5/-
B85 80/-	EH42 5/-	EL85 8/6	OD3 5/-
B894 37/6	EHF80 5/-	EL91 4/6	OD44 5/-
B214 16/-	EF83 7/6	EL95 5/-	PCC84 5/-
BT35 25/-	EF89 6/3	EL96 20/-	PC85 7/-
BT45 15/6	EG32 12/6	EM84 6/3	PC89 10/-
BTS3 35/-	EL70 3/-	EM84 6/3	PC90 8/6
CC3L 2/-	EC90 2/-	EM85 3/-	PC91 9/-
CL33 9/-	EC91 3/-	LN31 10/-	PC92 9/-
CV71 3/-	EC91 4/-	ESU208 6/-	PC93 9/-
CV77 5/-	EC92 5/-	EX31 3/-	PC94 9/-
CV102 1/-	EC92 8/-	EL96 7/6	PC95 10/-
CV103 4/-	EC94 5/6	EY91 3/-	PL36 7/6
CV414 7/-	EC96 6/6	KZ40 5/-	PL38 12/-
CV415 5/-	EC99 4/-	EZ41 6/6	PL81 7/-
CV4025 10/-	ECF42 7/-	EZ80 5/6	PL82 7/-
CV4046 40/-	EL10 10/-	EL98 8/6	PL83 8/6
D1 1/6	ECU18 5/-	F/6057 5/-	PL84 6/6
D41 3/3	ECU83 7/6	F/6061 5/-	PL24A 5/-
D61 6/6	ELC80 6/-	F/6063 4/-	PT15 10/-
167 3/6	ELC82 7/6	FW4300 6/6	PT25H 7/6
DA30 12/6	ELC86 10/-	G/1266 9/-	PT28 7/6
DA60 75/-	EP36 3/6	G/1371K119/-	PN4 14/-
DAF96 6/-	EP37 7/-	G50/2G 5/-	PY33 8/6
D141 4/-	EP39 5/-	GZ22 10/-	PY80 8/6
DE75 8/-	EP42 8/-	EL281 10/-	PY81 8/6
DE79 2/-	EP50 2/6	H/3 7/-	PY82 5/-
DE725 15/-	EP52 6/-	HK54 22/6	PY83 6/-
DF73 5/-	EP53 4/6	HL2K 2/6	PY80 6/6
DP91 3/-	EP55 8/-	HL23 6/-	PZ1-35 8/-
DP92 3/-	EP71 7/6	HL23DD 5/-	PZ1-75 12/-
DP96 6/-	EP72 5/-	HL41 4/-	Q121 6/-
DK92 6/6	EP74 4/-	HR2 9/-	Q25 5/-
DK96 5/6	EP80 5/-	K3A 30/-	Q230 5/-
DL92 5/-	EP81 6/-	K78C 22/-	QS180/15 10/-
DL93 6/-	EP85 4/6	K792 8/6	
DL94 5/6	EP86 6/6	KT33C 8/-	Q895/10 5/6
DL96 5/6	EP89 3/6	KT44 5/6	QS1202 8/-

QV04/7 8/2	W21 5/-	5T4 7/-	636 3/6	12AX7 6/-	78 5/-	9001 3/-
RV 8/-	W118 8/-	5U4 4/6	636B 6/6	12AX7 10/-	80 5/6	9002 4/6
RG4/1250 6/-	W110 8/-	5V4G 8/-	637G 6/6	12B6 8/-	81 9/-	9003 6/-
RR72 6/-	X118 8/-	5X4G 8/6	637M 8/-	12B6H 7/-	82 8/6	9004 2/6
SL30P 15/-	X145 8/-	5Y3G 4/6	638 5/6	12BH7 7/-	84 8/6	9006 2/6
SL30 12/6	YF 1/6	5Y3GT 5/-	638T 4/6	12C8 3/-	85 2/6	
SL30P 15/-	X68 7/6	5Y3GT 5/-	638T 4/6	12C8 3/-	85 2/6	
SL30 12/6	YF 1/6	5Y3WGT 5/-	638T 4/6	12C8 3/-	85 2/6	
SP2 8/6	Y63 5/-	9/-	638T 4/6	12C8 3/-	85 2/6	
SP41 1/6	Y65 4/-	5Z4G 6/6	638T 4/6	12C8 3/-	85 2/6	
SP61 1/6	Y68 8/-	6AB7 4/6	638T 4/6	12C8 3/-	85 2/6	
SP210 3/6	Z21 6/-	6A7 2/6	638T 4/6	12C8 3/-	85 2/6	
STV380/40 20/-	Z800U 20/-	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
STV70/808/1 1A3 3/-	Z801U 10/-	6A7 2/6	638T 4/6	12C8 3/-	85 2/6	
STU150A 1ASGT 5/-	1A3 3/-	6A10 10/-	638T 4/6	12C8 3/-	85 2/6	
T41 6/6	1C5GT 6/6	6A17 4/6	638T 4/6	12C8 3/-	85 2/6	
TT22 5/-	1D6GT 6/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
TP25 15/-	1E7G 7/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
TT11 5/-	1P2 6/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
TT13 35/-	1G6GT 6/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
TT31 45/-	1I4 2/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
TZ020 4/-	11LA6 6/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
TZ20 18/-	1A86 7/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
TZ40 30/-	11L14 4/-	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN1 30/-	LN21 4/-	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN12/4 8/6	LN13 4/-	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN17 5/-	LN24 4/-	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN70 4/-	LN74 4/-	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN4 5/-	LN4 5/-	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN5 3/6	LN5 3/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN6 2/6	LN6 2/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN7 2/6	LN7 2/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN8 2/6	LN8 2/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN75 2/6	LN75 2/6	6A5 2/6	638T 4/6	12C8 3/-	85 2/6	
LN76 2/6	LN7					

THE WORD **MAXI-Q** IS THE REGISTERED
 REGD. TRADE MARK
 OF DENCO (CLACTON) LIMITED
 IT IS ALSO A GUARANTEE OF
 WORKMANSHIP AND
 TECHNICAL PERFORMANCE

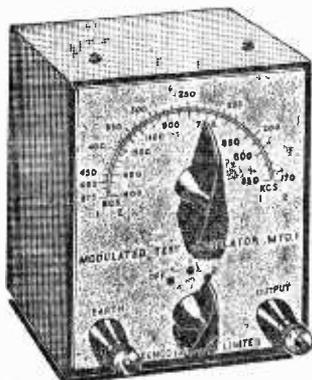OUR RANGE OF PRODUCTS IS SO GREAT THAT WE NOW HAVE TO REQUEST THE AMOUNT OF 1s. 6d. FOR OUR GENERAL CATALOGUE AND TO SAVE YOU POSTAL ORDER POUNDAGE CHARGE WE REQUEST SEND 1s. 6d. IN STAMPS.



MODULATED TEST OSCILLATOR MTO.1

- ★ Provides modulated signal suitable I.F. alignment, also trimming and tracking R.F. circuits.
- ★ Frequency is continuously variable from 170-475 kc/s and 550-1,600 kc/s.
- ★ Suitable for the alignment of transistor receivers.
- ★ Operates from a single 9-volt grid-bias battery (not supplied) which is housed within the unit.
- ★ The case is manufactured from steel and is finished in silver hammer. The front panel is gloss black bearing white lettering. Dimensions are 5- $\frac{1}{8}$ in. x 4- $\frac{1}{16}$ in. x 3 in.
- ★ Supplied with full operating instructions.

PRICE £3/17/6


Stop Press 3 Pole 3 Way 3 Bank Switch 7s. 6d. each 1 Pole 8 Way 4s. 3d.

DENCO (CLACTON) LTD.
 (DEPT. P.W.)

357/9 OLD ROAD, CLACTON-ON-SEA, ESSEX

NOW ADD F.M. RADIO to your MARTIN AUDIOKIT SET-UP

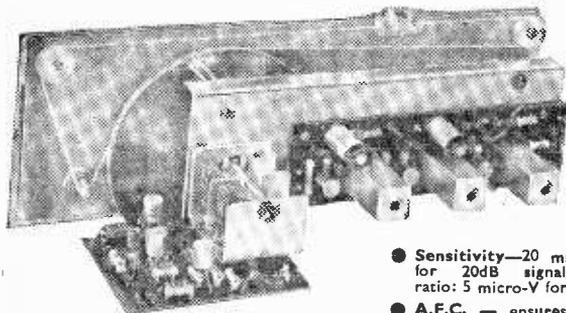
with only 3 easy-to-assemble
 prefabricated units



- Sensitivity—20 micro-V for 20dB signal/noise ratio; 5 micro-V for 40dB
- A.F.C. — ensures easy accurate tuning.
- Tuning—88 to 108 Mc/s
- Audio Response—Flat from 30 to 15,000 c/s
- Controls—Tuning, and on/off with switch through stage for recording, etc.

The unique and outstandingly successful system developed by Martin Electronics whereby prefabricated transistorised units can be assembled to make your own choice of hi-fi now brings 3 further Units, No. 15, 16 and 17 to enable you to build a modern F.M. Tuner of exceptionally good design and performance. Intended primarily for those who have chosen an Audiokit hi-fi set-up, the Tuner may also be used with other good amplifiers if desired. With a few simple connections, you will have a tuner of excellent appearance to please the most critical ear, yet it is surprisingly inexpensive.

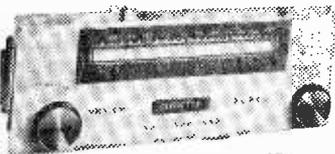A whole range of Audiokit Units is available which you can assemble to your own choice with ease and complete success. Ask for the Audiokit leaflet.



View above shows Units 15, 16 and 17 assembled.
 Below, the attractive escutcheon.

UNIT 15
 F.M. Head
 & tuning
 condenser
£5.12.6

UNIT 16
 I.F. Amp.
£5.7.6

UNIT 17
 Mounting drive
 escutcheon &
 controls
£1.17.6

SUPERB QUALITY FOR VERY MODEST OUTLAY

From Radio and Hi-Fi Stockists

MARTIN ELECTRONICS LTD. 154/5 High Street, Brentford, Middlesex

Trade enquiries invited

15Leworth 116172

MARTIN ELECTRONICS

154 High Street, Brentford, Middlesex
 F.M. Tuner Leaflet ● Audiokit Leaflet ●
 Tick as required

Name _____

Address _____

P.W.5

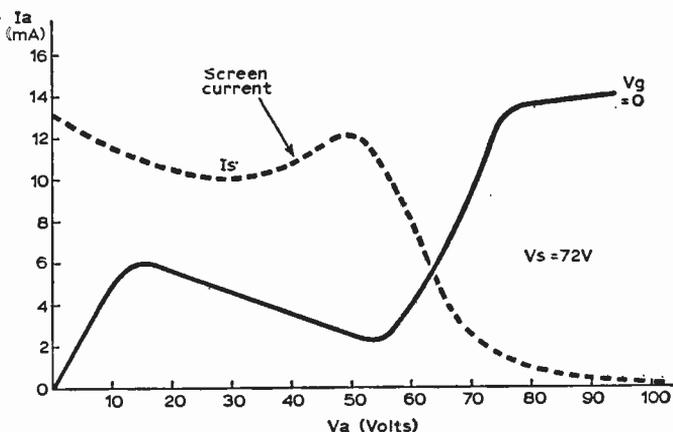


Fig. 62: I_a/V_a curve for a tetrode. (Screen current against screen voltage shown dotted.)

sion does occur after this point but as the anode voltage is now greater than that of the screen the electrons will return to the cathode and their effect will be very small.

7.5 Adding a Third Grid—The Pentode

In the tetrode the irregularity of the I_a/V_a curve is likely to cause distortion in a circuit in which the valve is used. If this distortion is to be reduced some way must be found of overcoming the effects of secondary emission. The simplest way to do this is to introduce a *third grid* between the anode and the screen grid. This third grid is called a *suppressor grid*. The suppressor grid is always connected to the cathode with the result that it is always at zero or negative potential with respect to the anode. Therefore any electrons which are liberated from the anode will now pass into the space between the anode and the suppressor grid: but as the anode is always at a higher potential than the suppressor grid the liberated electrons will return to the anode. In the *pentode* (valve with five electrodes) the effects of secondary emission is therefore overcome. A typical I_a/V_a curve for a tetrode has been shown as a dotted line for comparison purposes.

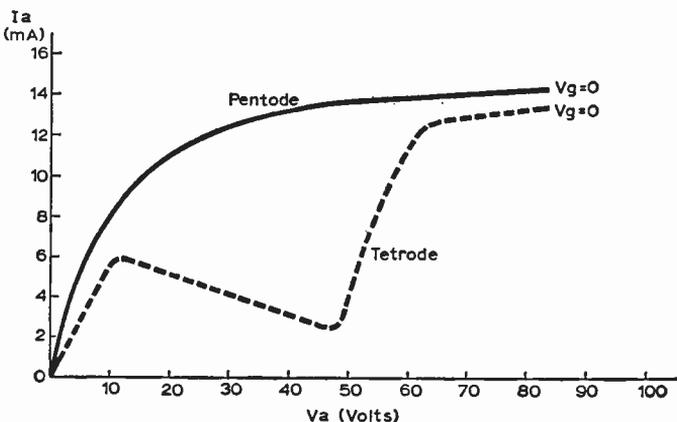


Fig. 63: I_a/V_a curve for a pentode. (Same curve for tetrode shown dotted for comparison.)

7.4 Secondary Emission in the Tetrode

As can be seen from Fig. 62, the V_a/I_a curve for the tetrode is unusually irregular. This is due to a phenomena called *secondary emission*. Briefly, some electrons strike the anode with sufficient speed to liberate an electron from the anode surface. This electron which has been liberated moves into the space between the anode and the screen grid. Because the screen is at a higher potential than the anode the electron will move towards the screen. This causes an increase in the screen current and a decrease in the anode current; in Fig. 62 it can be seen that the anode continues to lose secondary electrons until an anode voltage of about 65 is reached. Secondary emis-

7.6 Other Multielectrode Valves

Valves for special applications, such as for frequency changing in a superheterodyne receiver, may have more than three grids. The *heptode*, which has seven electrodes, and the *octode*, which has eight electrodes, are typical examples. Space is, however, too limited to allow any detailed description of these types of valve.

electrodes, and the *octode*, which has eight electrodes, are typical examples. Space is, however, too limited to allow any detailed description of these types of valve.

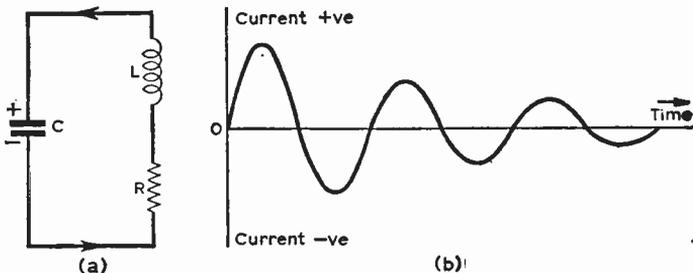


Fig. 64: (a) Discharging a capacitance through a coil; (b) damped oscillations.

7.7 The Triode as an Oscillator

If a charged capacitance is discharged across a coil of inductance L and resistance R , free oscillations will be set up. If a graph of current against time is drawn it will take the form shown in Fig. 64.

As can be seen from the graph the *period* of the oscillations is constant, but as the capacitor discharges the *amplitude* of the oscillations decreases. This type of oscillation is called a *damped* oscillation. If the oscillations are to be maintained they must be *undamped* oscillations, and in this case the amplitude would be constant as well as the period of oscillation. A valve can be used to supply the energy required in order to maintain undamped oscillations, but this energy must be supplied under certain specified conditions.

7.8 The Conditions for Oscillation

When a valve, such as a triode, is to be used as an oscillator the valve must supply its energy under the following conditions.

- 1 The energy delivered by each impulse must be large enough to make up for the energy lost between impulses.
- 2 The impulses must be in the *correct phase* so as to deliver the energy to the oscillating system.
- 3 The energy, or impulse, must be supplied at the *same frequency* as that of the oscillatory circuit.

7.9 A Simple Valve-driven Oscillator

A simple valve driven oscillator is shown in Fig. 65. If oscillations are to be maintained, feedback from the output circuit to the input circuit must be ensured. In this oscillator the feedback is obtained because of the *mutual inductance* between the grid coil, $L1$, and the anode circuit $L2$ $C1$. The correct phase relationship between the anode and grid voltages can only be maintained if—

- a the anode and grid coils are wound in the same direction;
- b the ends of the windings are connected as shown so as to ensure the correct phase difference.

It is obvious therefore that the power supplied to the valve in the form of d.c. supplied by the battery is converted into power in the form of an alternating current in the anode circuit.

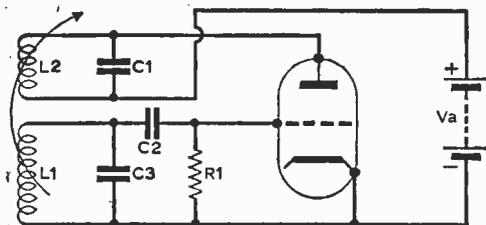


Fig. 65: A simple oscillator circuit.

7.10 Grid Bias in an Oscillator

In Fig. 65 the components $C2$ and $R1$ have not yet been mentioned. These components produce a *grid bias voltage* which helps to make the oscillator more efficient. In an oscillator with no grid bias (negative) grid current will flow during the positive half cycle of the grid voltage and the power produced is dissipated in the grid in the form of heat and reduces the efficiency of the oscillator. If the oscillator is to operate with high efficiency the grid must be biased beyond *cut-off* value. If a battery were used to supply the grid bias the initial small oscillations in the circuit would not cause any anode current to flow and oscillation would cease. The bias voltage produced by $C2$ and $R1$ however starts at zero and increases with the amplitude of the alternating component of the grid circuit, and therefore permits oscillations to continue. The method of providing grid bias which has been described also helps to maintain the amplitude of the oscillations in the circuit constant.

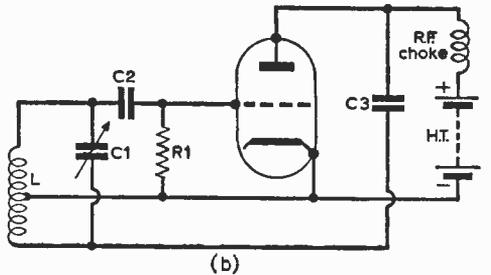
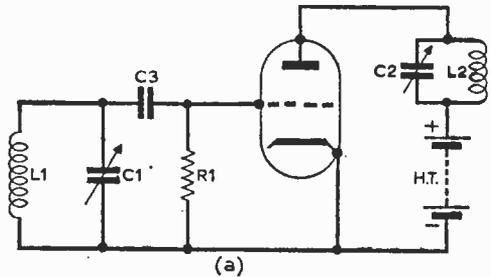


Fig. 66: (a) A tuned-anode, tuned-grid oscillator; (b) The Hartley oscillator.

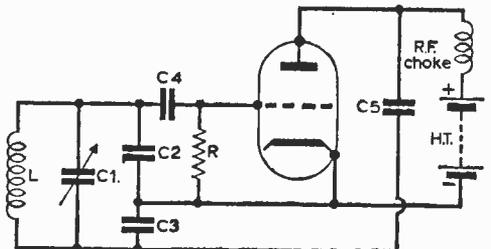


Fig. 66: (c) The Colpitts oscillator.


SOUTH SUPPLIES

(ELECTRICAL LTD.)

Post orders to 95 Old Kent Road, London, S.E.1

95 OLD KENT RD., S.E.1.
72 BOROUG HIGH ST., S.E.1
90 HIGH ST., EDGWARE
17 WOODFORD AVE., ILFORD
291 HIGH RD., CHISWICK, W.4
BER 5810
HOP 2125
EDG 6751
GRE 4815
CHI 0154

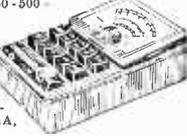ECCO Model S.E.37B
Push Button 20,000 O.F.V. Test Meter
D.C. Volts: 0-1
10-50-250-500-1000
A.C. Volts 0-10-50-250-500-10,000
D.C. Current 0-50mA, 10mA, 50mA.
Resistance 0-5K Ω -5000K Ω -5M Ω .
Inductance 50H-5000H. Capacitance 150pF-0.02 μ F. D.B. -20 Ω +22DB 20 Ω 36DB. The simplest and most efficient meter on the market at 42% below its true P. & P. value. **£5.15.0** 2/6




ECCO Model S.E.550
100,000 O.P.V. PROFESSIONAL TEST METER
Highest accuracy
3% -amps -ohms.
4% on A.C.V.
D.C. Volts:
5-2.5-10-50-0-6 at 100,000
250 O.P.V.
0-500-1000 at 35,000 O.P.V.
A.C. Volts:
0-2.5-10-50-250-1000 at 12,500 O.P.V.
D.C. Amps: 0-10 μ A at 500mV.
0-250 μ A-2.5mA-250mA-10 at 150mA.
Resistance: 0.20-2m-200k-20k.
160K-16k-160 Ω Centre Scale.
Decibels: -20 to +62 (0dB-0.775V).
£7.19.0 P. & P. 3/-



ECCO Model U.D.801
UNI-DIRECTIONAL DYNAMIC MICROPHONE
Dual impedance (600 Ω 50k Ω)
Frequency Characteristics: 100 Ω . 14,000 c/s. 15dB.
Sensitivity: -75dB -3dB at 600 Ω
-55dB \pm 3dB at 50K Ω 0dB = 1V μ bar.
Directionally uni-directional (60 Ω 27,000 c/s over 15 dB at 180 $^\circ$). This is a new and high class dynamic uni-directional microphone, very high in sensitivity and excellent in frequency characteristics, maintains high stability even against poor ambient conditions. Complete with 12ft. twin screened mic. cable. **£9.10.0** P. & P. Fully Guaranteed. 3/6



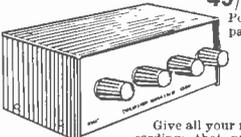ECCO 4-Ch. Transistorised MICROPHONE MIXER
49/6 Post paid
Give all your recordings that professional touch. The Ecco mixer allows you to mix 4 signals such as—Mic-tape, Records and tuner into a single output. Wonderful for groups, amateurs recorders, etc. Guaranteed to give hours of pleasure.



FAMOUS MAKES AMPS & PRE-AMPS
at Vastly Reduced Prices
3/4 watts, £4.19.0. 4/5 watts, £5.13.6.
5/5 Stereo, £11.16.3. 10 watt with separate Pre-amp, £15.2.6. 30 watt, £16.2.6. 50 watt, £16.2.6. Tremolo Unit £9.15.9. Tape Pre-amp, £9.0.0.

TECH. MODEL PV-58 VACUUM TUBE VOLTMETER
Finest design for stable and accurate measurement. 1% tolerance on all resistors. Large design 4in. 200 μ A meter for accurate readings 11 meg. ohm input.
Ranges:
—D.C.V. 0-1 5-5-15-50-150-500-1500V.
+ D.C.V. 0-1.5-5-15-50-150-500-1500V.
A.C.V. 0-1.5-5-15-50-150-500-1500V. RMS
0-1.4-4-14-40-140-1400-4000 P.P.
Resistance: 2 ohms to 100 megohms.
Decibels: -10dB to +65dB.
Operation: 220/240V A.C. Size 7 x 4 $\frac{1}{2}$ x 4in.
Each tester is supplied brand new and fully guaranteed complete with probe and operating instructions.
The finest value in testers available at only **£12.19.6** P. & P. Complete 3/6 ex.



ECCO MODEL S.E.100
TRANSISTORISED VARIABLE D.C. POWER SUPPLY
Meter Range: Volt 0-20 V.D.C. Current 0-20mA
Voltage Range: 0-20 Volts continuously variable 0-200mA
Maximum Current Gap. 0-10V 200mA Intermittent 0-20V. 150mA continuously.
Impedance Source: Current position 3.3 ohms. Voltage position 0.2 ohms.
Power Input: 220/240 V. Size 6 x 3 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in.
Fuse: 0.5 amp slow blow in D.C. circuit.
The extremely wide variable voltage range, low A.C. ripple and source impedance of the S.E.100 makes it a most satisfactory power supply to operate transistor radios, hearing aids, pre-amplifiers, instruments and other electronic devices under repair. The S.E.100 can be used in television and radio servicing, as an A.V.C. or voltage source as a D.C. filament supply operate relays, recharge small batteries and light electro plating as in dentistry. **£6.10.0** P. & P. 4/6. Fully guaranteed and complete with test lead, croc. clips and operating instructions.



ECCO MODEL S.E.200 MINI-LAB TESTER
This remarkable meter has seven test instruments packed into one pocket size case which can be taken and used anywhere.
Resistance Substitution 100 Ω - 1K Ω - 10K Ω - 110K Ω - 1M Ω . Capacitance Substitution .002mfid-.20mfid. - .02mfid. - .1mfid and 10mfid.
R.F. Signal Generator. Frequency fixed at 445 Kc. (adjustable to 700 Kc) output 35 mV approx.
Audio Generator Frequency 400 c/s. Output 35mV approx. D.C. and A.C. Volts. 4 ranges 0-15-50-150-500 volts, at 4,000 O.P.V.
R.F. Field Strength Indicator. Frequency range 1 to 140 Mc. Antenna 5 sections, length 10 $\frac{1}{2}$ in. Size 6 x 2 $\frac{1}{2}$ x 3 $\frac{1}{2}$ in.
The Mini-Lab is completely battery operated and suitable for quick checks in the service shop and Home Service clubs. **£8.19.6** each Complete
With Test Prods and Battery Fully Guaranteed.




FANTASTIC OFFER!
(Ready built and working). 4-speed Record Player. Incorporating a 2 $\frac{1}{2}$ watt output amplifier, 6in. 1000 line speaker and the latest B.S.R. single player unit. Beautifully designed wood cabinet covered with two-tone fabric in blue and grey. Mains voltage 220/260 volts A.C. only. Wonderful value at **£7.19.6** P. & P. 7/6



ECCO Model MS4 FLOOR STAND
Height fully opened 35 1/2 in. Fully closed 33 in. Three sections fully telescopic, $\frac{1}{2}$ or $\frac{3}{4}$ in. mic. adaptor £3/9/6 ea. P. & P. 5/-
Heavy cast iron base. Wonderful value.

MD 175 DYNAMIC MIC
Sensitivity—55 dB at 1000 non-directional, latest American design. **45/-** P. & P. 2/-
Impedance 50K Ω

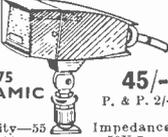ACOS
Die cast. hand shaped body. Special offer 15/6 plus P. & P. 2/6.
MULTI TUBE BARGAIN. ECCO Model 220S
4,000 O.P.V. on both A.C. and D.C. D.C. volts 0-5-25-125-500-2500. A.C. volts 0-10-50-250-1000. D.C. current 0-250 μ A-0-250mA. Resistance 0-10K Ω -0-1Meg. Ω Decibels -20 to +22dB. Meter size 4 $\frac{1}{2}$ x 3 $\frac{1}{2}$ x 1 $\frac{1}{2}$ in. Complete with test prods and battery Wonderful Value at 68/- plus 3/- P. & P.
RONETTE BINOFIELD B.F.40 STEREO CARTRIDGE
Freq. Res. 30-12,000 c/s. Sensitivity 150mV/cmsec. Lead 1m Ω 100 pf Complete with Sapphire Stylus. OUR PRICE 12/8 each. P. & P. 1/-.
RONETTE STEREO O.V.S. TURN-OVER CARTRIDGE
with Sapphire stylus. OUR PRICE 19/6 each. P. & P. 1/-.


SUN ACE
Ready built 4 transistor new push button Super-deluxe tape recorder circuit 4 transistors. Recording D.C. bias $\frac{1}{2}$ track built in 2 $\frac{1}{2}$ in. P.M. speaker. Recording time 17 mins. approx. on 200ft. tape. Batteries 1 U2-1 PP3. Complete with crystal microphone personal car phone, 200ft. tape and reel, spare spool carrying strap and batteries. Wonderful value. At only £4.15.0 plus 4/9 P. & P. Fully guaranteed.



MINIATURE PUSH-PULL AUDIO AMPLIFIER
4 Transistor
Output 200 mW. Low and high gain inputs to operate 3 Ω speaker. Wonderful value **3/6** P. & P. 2/-
Complete with operating instructions.
A GENUINE 4 AMP BATTERY CHARGER for Only 4/9 P. & P. 4/6




Made in England to our own specification and fully guaranteed. High-Low-Med. charge rate. 6V. or 12V. Selector Plug. 200-250V. Mains Selector Plug. 4 amp Cartridge Fuse protection, complete with mains lead charging lead and crocodile clips.
NEW!!! NEW!!!
CM01—High Impedance Crystal Mic. with built-in on/off switch. Complete with Table Stand. Plug-in Mic. lead and neck holder, all in a wonderful satin chrome finish.
★ VALUE AT 33/6 Plus 1/9 P. & P.
VANTONE MAINS RADIOS
Ready built 5 valve superhet with built-in Ferrite tuning bar. **£3.15.0** plus 3/9 P. & P. Fully Guaranteed.
This wonderful little radio will receive all stations on Med/wave loud and clear inc. Luxembourg. Ideal for bedrooms kitchens or as a second mains radio.

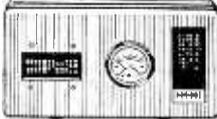

EHRECORDER
4 Transistor Tape Recorder. Ready built. Easy to operate single lever function control 200mV output complete with microphone—3in. Tape—Spare spool—Personal earpiece and batteries. Wonderful value **£4.19.6** plus 5/- P. & P.



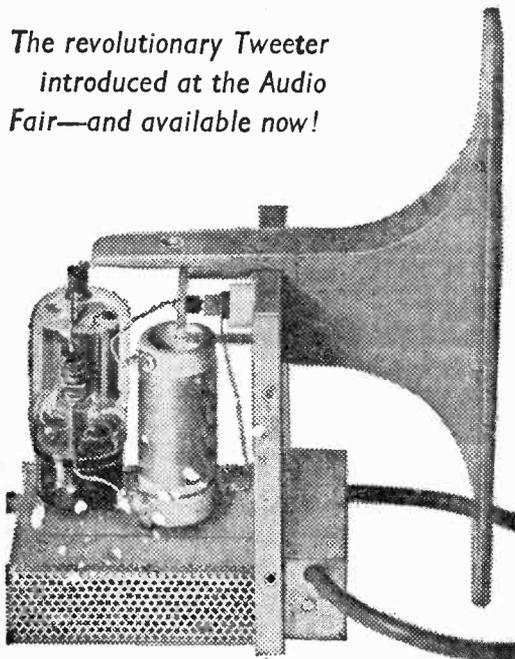The revolutionary Tweeter
introduced at the Audio
Fair—and available now!



THE NEW SUPERB IONOFANE LOUDSPEAKER

MODEL 601

The basic H.F. unit ready for building into a speaker assembly. It will handle the treble of 20 watts of music.

28 Gns.

MODEL 602

The basic Ionofane H.F. unit, together with a special 5in. mid range unit, cross-over and provision for connection to an existing bass unit of up to 20 watts capacity.

45 Gns.

MODEL 603

A full range speaker assembly of the highest quality, consisting of the Ionofane H.F. unit, new 5in. mid range and new 15in. bass unit. Will handle up to 20 watts.

75 Gns.

The IONOFANE operates on the Ionophone principle invented by Klein of Paris and is covered by British Letters Patent No. 756546.

It is a high frequency loudspeaker having a perfectly uniform response from 3 to 30 kilocycles, quite free from resonances and colourations and with perfect reproduction of transients.

It is fully guaranteed.

WRITE NOW FOR
ILLUSTRATED LEAFLET

FANE

acoustics
LIMITED

HICK LANE
BATLEY
YORKSHIRE

Enquiries for these Speakers including the Wholesale and Retail Trade may be sent direct to FANE ACOUSTICS LTD., BATLEY, YORKSHIRE, or to LINEAR PRODUCTS LIMITED, ARMLEY, LEEDS

JASON

KITS

Jason were first to produce a stable switched f.m. tuner for reception of BBC transmissions and an outstanding success has been achieved with the introduction of simple-to-operate switched tuners to receive both f.m. and TV sound transmissions. Jason tuners and test equipment offer a wide choice of models designed to meet present-day requirements and are a delight to build.



JTV2 SWITCHED TUNER for the reception of all BBC f.m. transmissions and BBC-I and ITV television sound channels at the turn of a switch. Foster-Sealey discriminator. Built-in power supply. Sensitivity 10μV for 40 dB quieting. Audio output 0.4V approx. All components including turret and coil plate but less four valves £14.0.4.



JTL TAPE PREAMPLIFIER designed to suit any tape deck or head. Will simultaneously record and playback stereo or mono using two or four track heads. Especially recommended for use with the Lorlin SB26 tape deck. (Send for details). All components including valves £22.1.0. Ready built and tested £30.9.0.

OTHER JASON KITS

FMT1 F.M. TUNER, less valves	_____	£5.19.0
FMT2, F.M. TUNER, less valves	_____	£9. 9.0
(less power supply components)	_____	£7.15.0
FMT3 F.M. TUNER, less valves	_____	£10. 9.0
(less power supply components)	_____	£8.15.0
MERCURY 2 Switched Tuner, less valves	_____	£9.15.4
ARGUS Transistor m.w. Tuner, complete	_____	£7.10.0
AG10 Audio Generator, complete	_____	£15.19.0
OG10 Oscilloscope, less c.r.t.	_____	£18.10.0
W11 Wobbulator, complete	_____	£14.19.0
EM10 Valve voltmeter, complete	_____	£23.0.0
SB26 Tape Deck (built only) 1-track mono	_____	31 gns.
4-track stereo	_____	39 gns.

Write for descriptive leaflets and name and address of nearest stockists

JASON ELECTRONIC DESIGNS LTD.

18 Tudor Place, Tottenham Court Road
LONDON W.1

Telephone: MUSEum 4666/8

7.11 The Frequency of Oscillation in an Oscillator

The frequency of oscillation in a valve driven oscillator can be found by referring to Section 4-7 in the February, 1965 issue of this magazine.

7.12 The Efficiency of an Oscillator

The efficiency of an oscillator is simply given by the relationship—

$$\text{Efficiency} = \frac{\text{Output power}}{\text{Input power}} \times 100\%$$

7.13 Specific Oscillator Circuits

Shown in Fig. 66 a, b, c are three oscillator circuits which are commonly used in amateur radio work. Space does not permit a description of the mode of oscillation of each type and the reader is advised to find out the mode of operation from a suitable text book. (See Article 1.) The reader is also advised to read up more fully the basic principles which must be observed when dealing with valve oscillator circuits.

Question

Using Figs. 62 and 63 as a basis, draw graphs to show—

- a The I_a/V_a curves, for a tetrode similar to that dealt with in Fig. 62, for values of control grid voltage of 0, -1 and -2V.
- b The I_a/V_a curves, for a pentode similar to

that dealt with in Fig. 63, for values of control grid current of 0, -1 and -2V. (Curves of the correct shape and approximate position will be acceptable.)

Answer to Last Month's Question

- 1 Mutual conductance is given by the change in anode current divided by the change in grid voltage which produces this. In the question, the change of anode current was 2.8mA, or 0.0028A, and the change in grid voltage which produced this was 1.6V.

$$\begin{aligned} \text{Therefore gm} &= 0.0028/1.6 \\ &= 0.00175 \text{ mhos} \\ &\text{or } 1.750 \text{ micromhos } (\mu\text{mhos}). \end{aligned}$$

Mutual conductance in mA/V will be given by $2.8/1.6 = 1.75 \text{ mA/V}$.


- 2 In Fig. 58 a change in anode voltage of 40V, (100-60), caused a change in anode current of 2.8mA. The same change in anode current was brought about by a change in grid voltage of 1.6V. Therefore the amplification factor of the valve is given by $60/1.6$

$$\mu = 37.5.$$

- 3 Cut off for $V_a = 100V$ is $V_g = -3V$.
- 4 Cut off for $V_a = 60V$ is $V_g = -1.5V$.

Part 8 Next Month

Selling Out Fast!
HURRY FOR YOURS

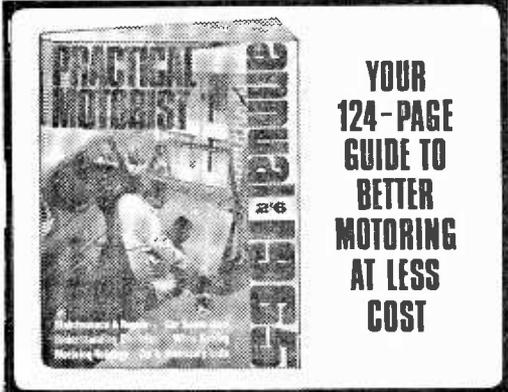


**YOUR
124-PAGE
GUIDE TO
BETTER
MOTORING
AT LESS
COST**

**PRACTICAL MOTORIST
annual 1965**

2/6

**PRACTICAL HOUSEHOLDER
ANNUAL 1965**

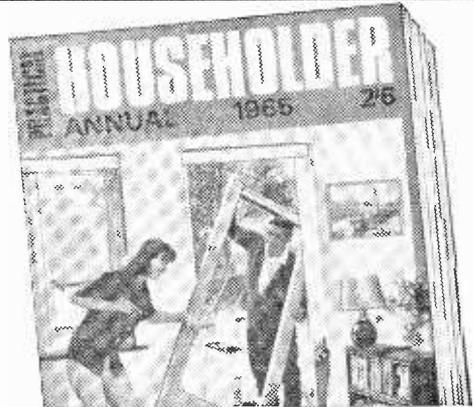

**PACKED WITH NEW IDEAS AND EXPERT
KNOW-HOW ON IMPROVING YOUR HOME**

2/6 from all Newsagents and Bookstalls

BIG DEMAND! GET YOURS NOW!


© 1965 American Radio History

World-challenging

SINCLAIR X-10

INTEGRATED 10 WATT
AMPLIFIER AND
PRE-AMP

SIZE
6" x 3"

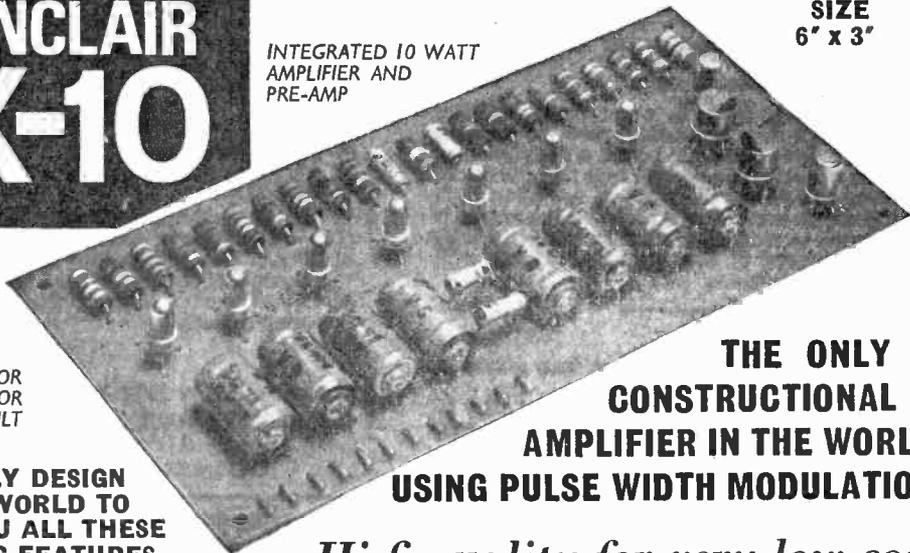

AVAILABLE FOR
BUILDING OR
READY BUILT


**THE ONLY DESIGN
IN THE WORLD TO
GIVE YOU ALL THESE
EXCITING FEATURES**

- ★ Pulse width modulated amplification.
- ★ Eleven transistor circuitry.
- ★ Unique four transistor output stage.
- ★ Input sensitivity of 1mV into 1K ohms.
- ★ 10 watts peak output into 15 ohms.
- ★ Total harmonic distortion less than 0.1%.
- ★ Choice of tone control system for mono or stereo to match pick-up, micro and radio inputs.
- ★ Power requirements—12 to 15 volts, D.C.
- ★ Very easy assembly.

**THE ONLY
CONSTRUCTIONAL
AMPLIFIER IN THE WORLD
USING PULSE WIDTH MODULATION**

Hi-fi quality for very low cost

By using pulse width modulation, the Sinclair X-10 integrated amplifier and pre-amp offers the constructor entirely new concepts of amplifier design and performance. Everything, except the tone and volume controls, is contained on the printed circuit board which measures only 6 x 3 in., and since no heat sink is necessary, the saving in space is enormous. This gives the constructor the opportunity to build a modern sleek hi-fi installation. In performance, the X-10 is a revelation in quality and power. There is no falling off at higher frequencies up to 20Kc/s, transient response is superb and current consumption for the power output obtained is appreciably less than in comparably rated conventional amplifiers. In fact the X-10 will operate perfectly well from two 6-volt lantern batteries. The Sinclair X-10 Manual included with every X-10 Amplifier explains how it functions and gives tone control and stereo matching circuits none of which costs more than a few shillings.

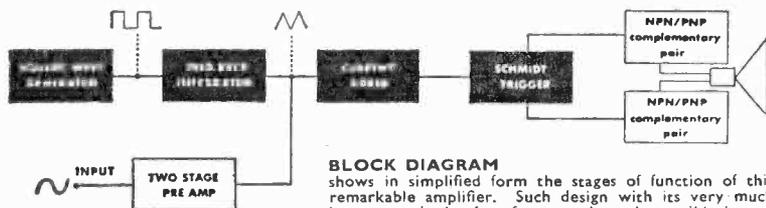

BLOCK DIAGRAM

shows in simplified form the stages of function of this remarkable amplifier. Such design with its very much better standards of performance is made possible by use of the very latest transistors and high quality components.

All parts for building, including 11 transistors, with X-10 Manual and instructions come to

£5.19.6

Ready built and tested with X-10 Manual

£6.19.6

X-10 Power Supply Unit (ready built) for A.C. Mains.

£2.14.0

★ FULL SERVICE FACILITIES ALWAYS AVAILABLE TO SINCLAIR CUSTOMERS

sinclair

SINCLAIR RADIONICS LTD.
COMBERTON Cambridge


Telephone
COMBERTON
682

Sinclair Designs

**A LONG RANGE, POWERFUL
RADIO SMALLER
THAN A MATCHBOX**


**SINCLAIR
MICRO-6**

IT'S THE WORLD'S SMALLEST

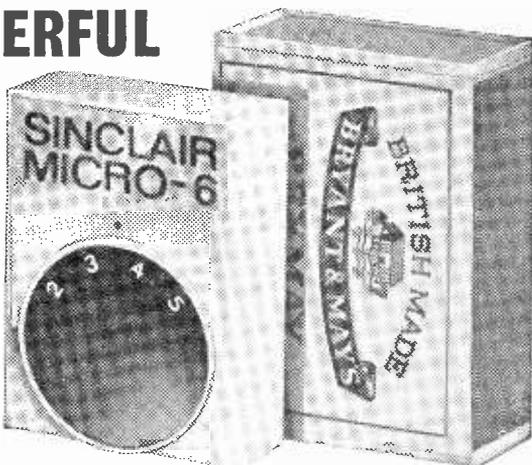

No transistor set has ever yet compared with the Micro-6 for size, power, performance and design and thousands upon thousands are now in use throughout the world. Everything except the lightweight earpiece is contained within the smart minute white, gold and black case. Unique features include bandspread over the higher frequency end of the medium waveband for easy reception of Luxembourg, powerful A.G.C. to counteract fading of distant stations, and vernier type tuning. Quality of reproduction is outstandingly good. Order your Micro-6 now and prove for yourself why it cannot be too highly recommended as an intriguing design to build and a most practical radio to use, and you can build it in an evening.

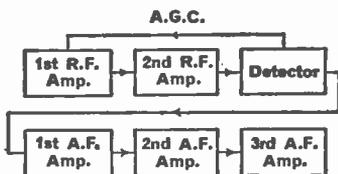★ Measures 1 1/5" x 1 3/10" x 1/2" and Weighs Less than One Ounce



BLOCK DIAGRAM OF MICRO-6
Six stage circuit using 3 special Micro-alloy transistors (M.A.T.s) provides 2 stages of R.F. amplification, double diode detector and high gain 3-stage A.F. amplifier plus A.G.C. Tunes over the Medium Waveband. Two self-contained batteries give about 70 hours working life.

All parts including M.A.T.s, lightweight earpiece and instructions come to

59'6


MALLORY MERCURY CELL Type ZM.312 (2 required) each 1/11

Pack of 6, 10/6

'Transista' black nylon wrist strap 7/6

SINCLAIR TR750 POWER AMPLIFIER

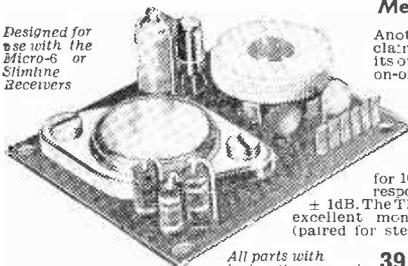Designed for use with the Micro-6 or Slimline Receivers



Measures only 2" x 2"


Another outstanding Sinclair design. Incorporates its own volume control and on-off switch. Used with the Micro-6 or Slimline, makes a powerful high quality car portable or domestic radio. 750 milliwatt output into a standard 25-30 ohm speaker for 10mV input. Frequency response from 30-20,000 c/s ± 1dB. The TR750 will also make an excellent mono record reproducer (paired for stereo) baby alarm, etc.

All parts with instructions come to **39/6** Ready built, and tested **45/6**

Trace that fault with a SINCLAIR MICRO INJECTOR

This ingeniously designed device generates a test signal at any frequency from 1K c/s to 30 Mc/s which is injected via the probe into any part of audio or radio equipment enabling the user to trace faults rapidly and accurately. The case measures only 1.8 x 1.3 x 1 in. with self contained battery. With full instructions.

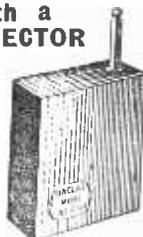Parts for building **27/6** come to Ready built **32/6** and tested



SINCLAIR SLIMLINE

An extra-easy to build high performance pocket radio. Ideal for beginners. Case, **49/6** parts, earpiece and instructions come to

TO SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE

Phone: COMBERTON 682

Please send items detailed below

£ s. d.

NAME

ADDRESS

TOTAL £

For which I enclose cash/cheque/money order

BLOCK LETTERS

P.W.5

RECEIVERS & COMPONENTS

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD. Dept. PW7/9, 126 Hamilton Road, West Norwood, S.E.27. GIPsy Hill 6166.

TRANSISTORISED SIGNAL INJECTOR. Complete kit of components and circuit of injector for testing amplifier or radio. 10/- only. Post free. G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

WE HAVE large stock of surplus components to dispose of, so we have decided to offer you a mixed parcel of 200 items for 45/- post paid. You won't be disappointed. — **GEORGE HANNINGTON**, 88 Latimer Road, London, W.11.

R & R RADIO & T V SERVICE

Dept. P.W.

MARKET STREET, BACUP, LANCS.
Telephone 465

SALVAGE VALVES		Tested before despatch	
6F13 4/6	10P14 5/-	PL82 3/6	20P4 4/8
6L18 4/6	20P5 6/6	U801 7/6	30P16 5/-
EF80 1/6	30P4 7/-	10F1 1/8	PC084 4/-
EC082 3/6	6F15 5/-	20P2 5/8	PC183 4/-
ECL8 3/6	EB91 1/-	30FL1 6/-	PF81 3/6
6F8 5/-	6F83 6/-	U301 6/-	
PL38 6/-	6/30L2 4/-	6U40C 5/-	10P13 5/8
PCF80 4/-	20P3 6/-	6F1 2/6	20D1 2/-
PL81 5/-	30PL1 4/-	ECC81 3/-	30P12 5/-
PZ30 5/-	PL36 6/-	EY88 4/-	PY83 5/-
U329 5/-	POL82 5/-		

Speakers, Ek-TV. 6in. round, 6 x 4in., 3/6; 8in. round, 6/-; post 2/.

Line Output Transformers available. State set model No.

Turret Tuners, 8/-, post 2/-.

Sean Colla, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

DIRECT TV REPLACEMENTS LTD. largest stockists of TV Components in the UK. Line Output Transformers, Frame Output Transformers, Deflector Coll for most makes. Official sole suppliers for many set makers. Same Day Dispatch Service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes. Day and Night Telephone GIPsy Hill 6166, 126 Hamilton Road, West Norwood, S.E.27.

TRANSISTORS, UNMARKED, UNTESTED. 40 for 10/-, p. and p. 10/-, 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc., 5,000 items free. **K. R. WHISTON** (Dept. PRW), New Mills, Stockport.

GUARANTEED NEW AND TESTED TRANSISTORS

Money returned if not satisfied

XA 102; XA 103; XA 104; XA 111; XA 112, 1/9 each
XB 113; OC 169, 2/4d. each
OC 42; OC 43; OC 44; OC 45; OC 73, 3/- each
XC 101; XC 121, 4/6 each
GET 8, 5/6d each
XA 701; XC 141, 6/3 each.
OC 26, 8/- each
XA 702, 11/- each
XA 703, 13/6 each
Red, White or Green Spots, 8d. each
General purpose diode, 6d. each
Rectifier GJ 3M, 8/- each; BYZ 13, 6/- each.
Send S.A.E. for full Price Lists of transistor components values, etc.

CLEVELEYS ELECTRICAL ENGINEERING COMPANY
Dept. P.W., Bank Chambers, Poulton le Fyde, Lancs.

82P 375V Unused Tag-ended Electrolytics, 11/- per doz, post paid. 2 Colebrook Avenue, Southampton.

RATES: 7/3 per line or part thereof average five words to line, minimum 2 lines, Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., London W.C.2.

RECEIVERS & COMPONENTS

(continued)

BARGAIN PACKS

Assorted Resistors 1-2W.

300 — £1 60 — 5/-

130 — 10/- 25 — 2/6

Money with order

KINRAY COMPONENTS

575 Rayleigh Road
Eastwood, Leigh-on-Sea

A1 POST FREE BARGAINS: Guaranteed set tested Valves, EF80, EB91, 9d. each; ECL80, 2/6; ECC82, PY31, PZ30, 3/6 each; F30, PY82, 3/3 each; PL53, 3/6; PL82, PCF80, 4/3 each; 20P1, 4/6; EBF80, N37, 4/3 each; PL33, 4/6; PL81, 4/6; 10P13, 5/3, S.A.E. for list or enquiries. All RADIO COMPONENTS, 14 The Borough, Canterbury, Kent.

PRINTED CIRCUIT PANELS make construction of 10W Push Pull Stereo or mono amplifiers dead easy! The Symphony Panel provides all circuitry from input (50mV) to output transformer secondary. Measure only 4 1/2 x 3 1/2. Price 40/- each or with valves (2x ECC85's, 2x EL84's 80/-). N.R.S. (Dept. PW) 16 Kings College Road, London, N.W.3. PRI 3314.

POWER TRANSISTOR BARGAINS: ISOL12A 60W 5Mc/s, 25/-; OC44/45/82 Equiv., 2/-; OA70/79, 8d.; BY100, 4/6. SAE for list. **D. & W. LTD.**, 220 West Road, Westcliff-on-Sea, Essex.

SPEAKER REPAIRS, cones fitted. Satisfaction guaranteed. **L. S. REPAIRS**, Pluckley, Ashford, Kent.

TRANSISTORS AT GIVE-AWAY PRICE! NKT 124/5 Switching transistors. Also capable of being used in all stages of a superhet. 6 for 10/-. OC71 equivalent 1/- each. 25 for £1 or £3 per 100. Miniature earphones with plug and lead 5/-. Transistor electrolytics 1/6 each. Brand new 4in. speakers 10/-. Goods under 10/- add 6d. postage please. **G. F. MILWARD**, 17 Peel Close, Drayton Bassett, Staffs.



V.H.F. Receivers P404 (R1392), 100 to 150 Mc/s, 13 valves, tuning meter. Good condition and complete with conversion instructions. £3-10-0, carriage 15/-.
230 Volts A.C. Rack Mounting Amplifiers. 4 watts 600 ohms output. Valves, 5Z4, 6V6, 6J7, 6X5, only 35/-, carriage paid.
Canadian Chamois Padded Head and Mike Sets for 19 and 22 set, etc., 10/-, post 2/6. Canadian Carbon Mikes with lead and jack, 4/6, post 1/6. Low Impedance Headphones, with lead and jack, 6/6, post 1/6.
(Carriage charges apply to England and Wales only)

Telephone: Worthing 9087



TRANSUNITS LIMITED

All items listed are new, of current manufacture and available by return of post.

Makers' Name & Ref. No. Price

CAPACITORS			s. d.
50 MFD 50V	DuBilier BR 4070	..	9
500 MFD 50V	DuBilier C.T. Sleeced	..	2 8
1 000 MFD 50V	DuBilier C.T. Sleeced	..	3 6
100/200 MFD 275V	DuBilier C.T. Sleeced	..	7 4
1 MFD 25V	Hunte SM20	..	6
400,000 PF 125V	1% S.T.C. 465LWR	..	7 6
	102EF	..	
35,200 PF 125V	1% S.T.C. 465LWR	..	2 9
	103GF	..	
210,000 PF 125V	1% S.T.C. 465LWR	..	5 6
	102CV	..	
423,000 PF 125V	1% S.T.C. 465LWR	..	7 6
	102EM	..	

CONDENSER GLIPS
1in. and 1 1/4in. TOC Type H2 3

CHASSIS PLUGS
3 Pin B. & L. Type LIS49/OP 4 6

FREE SOCKETS
3 Pin B. & L. Type LIS49/FS 3 0

CHASSIS PLUGS
12 Pin Painton 500686] .. 4 6

FREE SOCKETS
12 Pin Painton 500686] .. 6 9

INSULATED STAND-OFFS
Types 4A, 4C, and 10C 5

MIDGET P.C. PRESET POTS
Types LPH 5K and 10K 11

Types LPH 5K and 10K 10

NEON INDICATORS
110V Red and Amber Type 8L78 5 9

POTENTIOMETERS
1in. Slotted Spindle 2 watt W.W. 1K, 5K 3 0

1in. Slotted Spindle 2 watt W.W. 10K 3 8

POTENTIOMETER KNOBS
Bulgin K107 6

FLEESBY SWITCHES
4 Pole 6 way Type GA2 Size 3 5 0

RESISTORS			s. d.
180 ohm 6 watt	1 7
460 ohm 6 watt	1 7
1K 6 watt	1 7
1.5K 6 watt	1 7
2.2K 6 watt	1 9
2.7K 6 watt	1 9
3.3K 6 watt	1 9
4.7K 6 watt	1 9
12K 6 watt	2 6
120 ohm 3 watt	1 6
460 ohm 10 watt	1 8
3.3K 14 watt	1 8
4.7K 14 watt	1 8
12K 14 watt	1 8

TRANSISTORS		DIODES	
OC35	..	11 0	O.A.5 .. 2 10
OC72	..	8 0 1 7
OC84	..	3 9	ED300 .. 3 0
OC140	..	11 6	ED400 .. 3 8
OC200	..	5 2	SD91 .. 2 10
OC201	..	14 6 2 10
OC202	..	13 0 2 10
OC203	..	7 0	SD93 .. 3 4
OC205	..	14 6	SD94 .. 3 4
OC206	..	14 6 3 4
2N1418	..	10 6 3 4

ZENNER DIODES			s. d.
KR60	..	21 0	Z6 .. 5 6
IN2048-1	..	14 6	Z10 .. 5 6
OA2200	..	6 0	Z15 .. 5 6
OA2206	..	4 2	Z110 .. 12 3
VZ10F	..	7 0	ZL12 .. 12 6
VZ475F	..	6 6	ZL18 .. 12 8
Z5	..	5 6	ZB20 .. 4 0

VOLTAGE ADJUSTMENT BOARDS
McMurdo 2790/A 9 4

Orders less than £1 P. & P. 1/-, up to £5, P. & P. 2/- above £5. P. & P. free.

TRANSUNITS LIMITED

79, HIGH STREET,
WALTON-ON-THAMES,
SURREY

Tel: Walton-on-Thames 21361

RECEIVERS & COMPONENTS

(continued)

TRANSISTORS: Silicon pnp, minimum beta 10 at Ic=5mA, 1/6; Germanium npn, minimum beta 50 at Ic=5mA, 5/-; pnp power studs, minimum beta 50 at Ic=2A, 12/6. **LONGLANDS,** 6 Mansfield Place, Ascot, Berks.

2 YEARS' WRITTEN GUARANTEE.

Brand New, Unused and Boxed. Complete range of Radio and Television Valves.

S.A.E. lists.

AMATEUR ELECTRONICS.

240 Lichfield Road, Aston, Birmingham 6 (Dept. P.W.).

SYMPHONY STEROPHONER, patent device invented by Swiss Orchestral Conductor Hermann Scherchen. Converts any mono radio, gram or tape recorder to stereo for only 42/- (plus cost of 2nd speaker). Illustrated brochure from N.R.S. (Dept. PW), 16 Kings College Road, London, N.W.3. PRI 3314.

SCINTILLATION COUNTER 1098 (B). Using CV2316 Photo tube plus 10 other valves, magnetic counter with lens, each unit in case but made for 19in. rack mounting x 8 1/2in.

POWER UNIT 1098 (B) 0-9, 0-5, K Volt; (2) 0-300 V at 120 mA both adjustable, meter for checking voltages same size as above, made by Ferranti. These two units are the complete set and are checked complete, but as we know very little about this kind of equipment no enquiries can be answered. **ONLY £12/10/0.** BRN 10/-, or either unit 27/0/0. BRN 7/6. Soaling Units 109 (A) & (B) S.A.E.

BULK PURCHASE OF STABILISED POWER



UNITS made by MARCONI or EDISWAN all inputs 200-50 AC

- (1) General Purpose P.U. two adjustable independent output (1) — 0/250 V at 50 mA; (2) + 0/250 or 0/500 V at 250 mA. Also 6.3 at 9 amps using 6-0232, 3-12B1 and 7 other valves, meter for checking output voltage or current, both voltages adjustable, 19in. rack mounting x 10 1/2in. **ONLY £14/10/0.** Matching Case 20/-, BRN 10/-.
- (2) Transistor P.U. Mk II Two adjustable independent outputs (1) — 0/10, — 0/100 V; (3) + 0/10, + 0/100 V metered output and same in looks and size as above power unit, using 20 valves £14/10/0. Matching Case 20/-, BRN 10/-.
- (3) As above but 0/16 V, 0/150 V.
- (4) Three outputs 200-255, 255-350, at 200 mA, 350-400 at 150 mA all adjustable 6.3 C.T. 4 amps twice 19in. rack mounting x 8 1/2in. £8/10/0. Matching Case 20/-, BRN 10/- (Two meters Voltage and Current).
- (5) Output 120-250 Variable at 50 mA, 6.3 C.T. 4 amps, using two meters Voltage, Current, 19in. rack mounting x 7in. £5/10/0. Matching Case 20/-, BRN 10/-.



Relector Units 1.8-10 m.e.z. in 4 switched ranges. Ideal for harmonic suppression of TX, or as a station relector for RXs. Just plug aerial into one socket and connect to other socket, large tuning knob and dial in small grey case. **BRAND NEW ONLY 35/-**, post 5/-.

We have been informed by many well satisfied customers that these units have been used for Grid-Dip Osc., Signal Generators, Receivers, R.F. Preselector, etc., with very little modification. **FEW ONLY LEFT.**

J. T. SUPPLY

38 MEADOW LANE, LEEDS II

RECEIVERS & COMPONENTS

(continued)

MUST CLEAR! Silly Prices! Turret Tuners, mostly Plessey, 2/6 plus 2/- post or £1 dozen post free. Worth more for the components alone. Speakers, removed from TVs, all tested, 7in. x 4in., 5in., 5/- plus 2/- post or £2 dozen post free. **STROUD AUDIO,** Paganhill Lane, Stroud, Glos.

RESISTORS! You can't resist these! 1,000 assorted wattage and value. Cannot be repeated at £2/10/- per 1,000. G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

MISCELLANEOUS

CONVERT ANY TV SET into an Oscilloscope. Instructions and diagrams 12/6. **REDMOND,** 42 Dean Close, Portslade, Sussex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 30 Maude Street, Darlington, Durham. Send 2id. stamp.

METAL WORK

METAL WORK. All types cabinets, chassis racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.,** Chapman St., Loughborough.

CABINETS • CASES CHASSIS

Anything in metal. "One-offs" a pleasure. Send your drawing for quote. Stove enamelled in any professional finish

MOSS, WATSON

40 Mount Pleasant Street, Oldham Lancs. MAIN 9400 P.W.

FOR SALE

CONDENSER BARGAIN! Miniature Paper Condensers, 1/2in. x 1/2in. Ideal for transistor sets. .0001, .001, .002, .005, .02, .04µF. also small 500µF and 2.2µF Condensers. All 7/6 per 100, £3 per 1,000. G. F. MILWARD, 17 Peel Close, Drayton Bassett, Staffs.

ELECTRIC SOLDERING-IRON



FANTASTIC BARGAIN OFFER

Lightweight Pistol Grip handle 40 watt, 240/250V. A.C. Solid copper bit. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handyman. A boon to model makers and a necessity for every wireless enthusiast. Offered to P. & P., 1/- you at this new amazing price.

9/6

C. H. SERVICE, (Dept. P.W.3) Lusted Hall Lane, Tatsfield, Kent.

FOR SALE

(continued)

MORSE MADE!

The famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum!

One student aged 20. took only 13 DAYS, and another, aged 71, took only 6 WEEKS to obtain a G.P.O. Pass Certificate. If you wish to read Morse easily and naturally, please enclose two 3d. stamps for full explanatory booklet to **G3CHS, THE MORSE CENTRE, 45 GREEN LANE, PURLEY, SURREY.**

CONSTRUCTORS, Hi-fi enthusiasts, Service Engineers cannot afford to be without our bargain lists. Guaranteed to save you pounds. **F. D. Co. Ltd.,** 1 Richmond Place, Portsmouth.

240watt ELECTRIC POWER ANYWHERE

ANYTIME from 12th CAR BATTERY



WITH THE AMERICAN DYNAMOTOR UNIT
Type 12x, output 240/250v. at 150 or 220watts. Perfect for TELEVISION, POWER TOOLS of all universal AC/DC ELECTRICAL EQUIPMENT, gives wonderful results. Price ONLY £8 + 10/- carriage. Send stamped envelope for full illustrated details to "SCIENTIFIC PRODUCTS, CLEVELYTES, LINES"

HAMMER FINISH PAINT. The modern finish for electronics. Can be brushed or sprayed. Blue or silver. 2oz. tins 3/6, 4-pint 7/6, 1 pint 4/6. Post 6d. on any order. Trade supplied. **FINNIGAN SPECIALITY PAINTS (pw),** Mickley Square, Stocksfield, Northumberland.

NOW READY!

A modern way of instrument case assembly using our "Die Strip". The strip has been specially made for us at Birmingham on qty. production, for low price to the public. It is made of high strength alloy and will enable any one to assemble an instrument case or cabinet in minutes. Full details of these products will be sent free. Please send large envelope self addressed.

88 set transmitter receiver. Chassis less valves, 20/- each. Post paid.

Copper Laminate Board, single or double sided, 5/- per square foot panels either type 3ft. by 4ft., 33/-.

High Stab Resistors, 5%, 6d.; 2%, 9d.; 1%, 1/-, Every six packed in 7-compartment linen finish component box.

Speakers, 3 ohm P.M. 5in., 5/-, 6in., 6/-, 7 x 4in., 7/-, 8in., 8/-, 10in., 12/6.

Please send S.A.E. for full Lists of other goods on offer.

U.K. ONLY

E. R. NICHOLLS

Mail Order and Retail Shop
46 LOWFIELD ROAD
off SHAW HEATH, STOCKPORT
CHESHIRE

FOR SALE

SINE COSINE POTENIOMETER ASSEMBLIES

Contents:— 21 W.W. Pots: 1/2 in. shafts, 10 x 1 K.ohms 5 x 2.5 K.ohms, 4 x 500 ohms, 2 x 5 K.ohms. 90 W.W. resistors, 3 pairs of gears, 12 alids res. Brand new. PRICE 22/6 plus 6/- post.

MONITOR UNIT Type 61

I/P 200/250v. 50 c/s, contains:—C.R.T type VCRI38A and valves CV1065 x 3, CV1121, CV140, H.T. supply is 450v. at 70Ma and E.H.T. is 2Kv. Metal rectifiers are used in H.T. and E.H.T. supplies. Brightness, Focus controls etc., fitted. Unit is complete with outer cover size 11 x 10 x 9in. Supplied in new condition. PRICE 24.15.0 plus 12/6d carriage.

POWER UNIT Type 311

I/P 200/250v. 50 c/s O/P's +300 at 250Ma. —130 at 40Ma and +12v. D.C. connected at 4 amps, valves 5U4 or 5V4 x 2, 6X5. The O/P's are all fused and can be switched remotely by relays in the P.U. All H.T. circuits employ choke I/P filter, some increase in H.T. can be obtained by using cond. filter. The unit is complete with outer cover and circuit, in very good condition. PRICE 25.10.0 plus 1 carriage.

VHF RECEIVER Type 3683/4

I/P 200/250v 50 c/s. Two types available. Tuning 190 to 210 Mc/s and 155 to 165 Mc/s, these are readily adaptable to other frequencies. Valve line up EF54 R.F. EB91 Mix, EC52 L.O., CV118 x 5 I.F.S., EB91 DET, CV118 Amp, CV588 C.F.O./F., 6U4 Rect. I.F. is 18 Mc/s and H.T. supply is 275v at 100Ma. Complete with outer cover in new condition. Please state frequency range required. PRICE 23.15.0 plus 10/- carriage.

HEADPHONES American type HS33

600 ohms Impedance. Light-weight type with soft rubber ear pads in good condition but less lead and plug. PRICE 22/6d plus 1/6d post. 4ft. G.P.O. cords with plug 5/- post paid.

P.C.R. COMMUNICATIONS R.X.

Covers long and medium wave and S.W. 6 to 18 Mc/s. Made by PYE and PHILIPS, 6 valves R.F. and 2 I.F. stages, built in 6in. speaker. There is ample room to build an Internal Power Pack. Supplies required 250v 50Ma and 12v. 1.5a or 6v 2a. R.E.M.E. reconditioned and tested. PRICE 26.10.0 plus 10/- carriage.

A R C-3 Junction Boxes

Contains 6 24v relays, Cond.; Hash Chokes etc. American manufacture. PRICE 10/6 plus 3/6 post.

SELENIUM RECTIFIERS

Half wave type I/P 300v R.M.S. O/P 100Ma with mounting brackets. American manufacture, new and boxed. 2/6 each plus 6d post or 4 for 10/- post paid.

MAINS TRANSFORMERS

Type 10K13178
230v Prim.; Sec.; 350-0-350 at 95Ma, 5v 3a and 6.3v 3.7a. PRICE 25/- plus 5/- post.

Type 10K16929

230v Prim.; Sec.; 350-250-0-250-350 at 180Ma, 5v 3a. PRICE 17/6d plus 4/6d post.

Type 10K16702

110/230v Prim.; Sec.; 12v 1.5a or 6v 3a or it can be used as a 40W Auto transformer. Totally enclosed construction with terminal block connections on I/P and O/P. PRICE 11/6d plus 2/6d post. All above transformers are new and boxed.

B CI033 V.H.F. R X

Small 3 valve remote control R.X., tuning 70 to 80 Mc/s, uses valves 6SH7 R.F. Amp, 6BL7 DET/L.F., 12SN7 relay control valve, also very sensitive 10K/ohm relay I/P C/O. Ideal for conversion to 27 Mc/s. American manufacture with circuit. PRICE 22/6d plus 2/6d post.

SEND FOR FREE LISTS

B. SLATER

34 Lifford Street, Sheffield 9.

FOR SALE

(continued)

TELEVISION SETS, not working, for callers only. 17in. 21/10/-; 21in. 23/10/-; 14in. mains portables 22/10/- Phone: Bournemouth 26849.

TRANSISTORS

1/- each. Red or White Spots.

2/- each. XA101, XA102, XB103, OA90, XA111, XA112, OC430, V10/15.

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, XA151, XB104, XC101, XC101A, OC169, OC200.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171, XA103, XA116, XB102, XB105, XC121, XU611.

5/- each. OC139, OC140, OC204, ORP60, XA701, XA703, GET7, GET8, GET9, XC141, BY100, OA211.

10/- each. OC19, OC22, OC25, OC26, OC28, OC35, 2S013.

ZENNER DIODES

4.7v. to 30v., 1/4w. 3/6, 1.5w. 5/-, 7w. 6/- each.

Plus many more. Send 6d. in stamps for full list and eq. chart.

B. W. CURSONS
78 BROAD STREET
CANTERBURY, KENT

WANTED

WE BUY New Valves for cash, large or small quantities, old types or the latest. Send details. Quotations by return. WALTONS WIRELESS STORES, 15 Church Street, Wolverhampton.

WE BUY New Valves and Transistors, Amplifiers, Short-wave Receivers and Components, etc. A.D.A. MANUFACTURING CO., 116, Alfreton Road, Nottingham.

VALVES wanted, reclaimed, tested, TV, especially 30I15. State quantity and price.—Box No. 58.

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors, R.H.S., Beverley House, Mannville Terrace, Bradford 7.

WANTED

VALVES ONLY

Must be new and boxed

Payment by return

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

SERVICE SHEETS

SERVICE SHEETS, Radio and Television, 3/6 post paid. VEST AND EMERY, 17 Holgarth St., Durham.

SERVICE SHEETS, Radio, TV, 5,000 models. List 1/- S.A.E. inquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for all makes of Radio and TV, 1925-1964. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models 1/6. Valves, modern and obsolete, Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, also current and obsolete Valves for sale. JOHN GILBERT'S TELEVISION, 1b Shepherd's Bush Road, London, W.12. Phone: SHE 8441.

S.E.S. SERVICE SHEETS for all TV, Radio and Tape Recorders, etc. List 1/6 plus S.A.E. SUN ELECTRICAL SERVICES, 38 St. George's Road, Hastings, Sussex.

SERVICE SHEETS (75,000) 4/- each. Callers welcome. Always open. 5 South Street, Oakenshaw, Bradford.

SERVICE SHEETS

4/- ea., plus postage

We have the largest supply of Service Sheets for all makes and types of Radios, Televisions, Tape Recorders, etc., in the country. Speedy service.

To obtain the Service Sheet you require, please complete the attached coupon.

From:

Name:

Address:

To: S.P. DISTRIBUTORS
44 Old Bond St., London W.1
Please supply Service Sheets for the following:

Make:

Model No.:..... Radio/TV

Make:

Model No.:..... Radio/TV

Make:

Model No.:..... Radio/TV

I also require list of Service Sheets at 1/6

(please delete items not applicable)

I enclose remittance of.....

MAIL ORDERS ONLY Ma PW.

BOOKS & PUBLICATIONS

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—list free. **WILLEN** (Dept. 46), 61a Roadway, London, E.15.

SOUND RECORDINGS

A UNIQUE BUY. Recording tape top brand. 7in. 2,400ft., D.P. 25/-; 5 1/2in. 1,200ft., 19/6. P. & p. 1/6 per spool. Bargains in all sizes. S.A.E. for list. We repair buy and sell Records. **E. C. KINGSLEY & CO. LTD.**, 132 Tottenham Court Road, London.

EDUCATIONAL

RADIO OFFICERS see the world. Seagoing and shore appointments. Our many recent successes provide additional trainee vacancies during 1965. Grants available. Day and boarding students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

TRAINING

Full-time courses in **RADAR** and **RADIO-TELEGRAPHY** for prospective marine Radio Officers. Govt. approved exam. centre. Also courses in basic **ELECTRONICS**, **RADIO**, **TELEVISION** and **PRACTICAL SERVICING**. Apply—Director, British School of Telegraphy, 20 Penywern Road, Earls Court, London, S.W.2.

THE INCORPORATED PRACTITIONERS IN RADIO AND ELECTRONICS (I.P.R.E.) LTD. Membership Conditions booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/-, post free. Secretary, Dept B, 32 Kidmore Road, Caversham, Reading, Berks.

BECOME "TECHNICALLY QUALIFIED" in your spare time. Guaranteed Diploma and Exam. Home-study Courses in Radio, TV Servicing and Maintenance. **R.T.E.B.**, City and Guilds, etc. Highly informative 120-page Guide—FREE. **CHAMBERS COLLEGE** (Dept. 363), 148 Holborn, London, E.C.1.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs') **R.T.E.B.**, etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor. Write for **FREE prospectus** and find out how **ICS** can help you in your career. **ICS DEPT. 541, PARKGATE ROAD, LONDON, S.W. 11.**

SITUATIONS VACANT

RADIO AND TV Exam. and Courses by Britain's finest Home-study School. Coaching for **Brit.I.R.E.**, City and Guilds, Amateur's Licence, **R.T.E.B.**, **P.M.G. Cert.**, etc. **FREE** brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russell Street, Reading.

TV AND RADIO—A.M.I.E.R.E., City & Guilds, **R.T.E.B. Cert.**, etc., on "No pass—no fee" terms, over 95% successes. For details of exams and home training courses (including practical apparatus in all branches of radio, TV and electronics) write for 148-page Handbook—free. **B.I.E.T.** (Dept. 242G), 29 Wright's Lane, London W.8.

A.M.I.Mech.E., **A.M.I.E.R.E.**, City and Guilds, **G.C.E.**, etc., brings high pay and security. "No pass—no fee" terms. Over 95% successes. For details of Exams and Courses in all branches of engineering, Building, Electronics, etc., write for 148-page Handbook—FREE. **B.I.E.T.** (Dept. 242B), London, W.8.

RADIO TECHNICIAN

A number of suitably qualified candidates will be required for training, leading to permanent and pensionable employment. (Normally at Cheltenham but with opportunities for service abroad or appointment to other U.K. stations.)

Applicants must be 19 or over and be familiar with the use of Test Gear and have had Radio/Electronic workshop experience. They must offer at least "O" level GCE passes in English Language, Maths, and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19, £722; at 25, £929 (highest pay on entry) rising by four increments to £1,067.

Prospects of promotion to grades in salary range £997—£1,634.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days.

Normal Civil Service sick leave regulations apply.

Apply:

RECRUITMENT OFFICER (RT 37)
Government Communication Headquarters, Oakley Priors Road
Cheltenham

MULTIMETERS

illus. booklet on request. **EP10K**, 10,000 o.p.v. 77/-, post 1/6; **EP30K**, 30,000 o.p.v. 103/-, post 2/3; **EP50K**, 50,000 o.p.v. 143/-, post 2/4.

MULTIMETER KIT

18,000 o.p.v., 25 ranges, AC/DC Volts up to 1000V, Direct Current to 2.5A, Ohms to 10 Meg., 69/-.

High Stab. Resistors, 4W, 1%, 2/-, Full range.

Signal Injector Kit, 10/-, post 1/-.

Simple Analogue and Football Pool Computers, Two very popular circuits, 3/6. **Noughts and Crosses Machine**, New Mark 2 version, still unbeaten, circuit 3/6.

Binary Digital Adder/Subtractor, The very simplest digital machine, circuit 3/6.

PLANET INSTRUMENT CO.
25(W) DOMINION AVENUE, LEEDS 7

Lewis have the Cabinet for you

We can supply any cabinet to your own specification—These are only two examples—**THE LARGEST RANGE OF CABINETS IN THE COUNTRY**
Equipment is also our speciality.



The Grosvenor
Price 18 gns.



The Lowboy
Price 27 s

LEWIS radio

10c (P565) Chase Side Southgate
London N.14. Tel 3733/9666

FREE CATALOGUE

Send today for the new Lewis Catalogue


Designed to assist your choice of cabinet. Sent absolutely free. The new Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Choose from 49 different Models. Please send your new free 24 page colour cabinet catalogue.

Name _____
Address _____

BLOCK CAPITALS PLEASE

10/14 WATT HI-FI AMPLIFIER KIT

A stylish finished monaural amplifier with an output of 14 watts from 2 EL84's in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mikes and gram. allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-16Ω speaker and independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84's, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 1/6. (Free with parts).

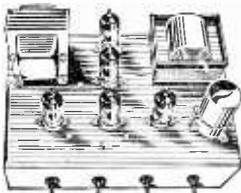

All parts sold separately. ONLY £6.19.6 P. & P. 6/6. Also available ready built and tested complete with standard input sockets. £8.15.0. P. & P. 6/6. Carrying Case for above 25/- P. & P. 4/-.

SPECIAL HARVERSON OFFER!!! BRAND NEW HEAVY DUTY 12in. SPEAKERS. Response 45 c/s-13 Kc/s. 14in. voice coil. Available in 3 or 15 ohms. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE AT 89/6. P. & P. 5/- Also 25 watt Guitar Model available at 85.5.0.

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI



Peak output in excess of 1 1/2 watts. All standard British components. Built on printed circuit panel size 6 x 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (BT114) or 91 Mullard OC81D and matched pair of OC81 o/p. 9 volt operation. Everything supplied, wire battery clips, solder, etc. Comprehensive, easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately. SPECIAL PRICE 45/- P. & P. 2/5. Also ready built and tested, 52/6. P. & P. 2/6. A pair of TAI's are ideal for stereo.

HARVERSON'S F.M. TUNER MK.



F.M. tuning head by famous maker. Guaranteed non-drift. Permeability tuning. Frequency coverage 88-100 Mc/s. Balanced diode output. Two I.F. stages and discriminator. Attractive maroon and gold dial (7 x 3in. glass). Self-powered, using a good quality mains transformer and valve rectifier. Valves used ECC85, two EF80's and EZ80 (rectifier). Fully drilled chassis. Size of completed tuner 8 x 6 x 5 1/2in. All parts sold separately. Set of parts if purchased at one time £5.19.5 plus 8/6 P. & P. ins. Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye, front panel and brackets, £6.12.6. P. & P. 8/6. Mark III Version as Mark I but with output stage. (ECL82) and tone control. £7.7.0. P. & P. 8/6. Handsome Metal Cabinets. Choice of Black or Green. To fit Mark I, 25/- P. & P. 2/6. To fit Mark II, 17/6. P. & P. 2/6.

SPECIAL PURCHASE TURRET TUNERS By famous maker. Brand new and unused. Complete with PCC84 and PCF80 valves, 34-38 Mc/s I.P.F. Biscuits for Channels 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 25/- each. P. & P. 2/6. GORLER F.M. TUNER HEAD 88-100 Mc/s 10.7 Mc/s. I.F. 15/- plus 1/9 P. & P. (ECC85 valve 8/6 extra).

4-SPEED PLAYER UNIT BARGAINS

All Brand New in Maker's Original Packing SINGLE PLAYERS GARRARD SRP10.....£5.9.11. Carr. 4/- B.S.R. GUY with unit mounted pick-up arm. £4.15.8. Carr. 4/- AUTO CHANGERS LATEST B.S.R. UA25 Super Slim mono. £6.2.6 B.S.R. UA15 £6.19.6; B.S.R. UA16. £6.29.6 LATEST GARRARD AT5£6.8.0 Standard GARRARD Autolinn.....£6.19.0 GARRARD AT6£10.0.0. Carr. 5/0 on each. All the above units are complete with t/fo mono head and sapphire styli or can be supplied with compatible stereo head for 12/6 extra.

SPECIAL OFFER! Limited number of E.M.I. 4 SPEED SINGLE RECORD PLAYER DECKS

with unit mounted pick-up. Incorporating the following special features: Heavy 8 1/2in. shaded pole motor for 200/250V. A.C. with 90V tap. Latest ultra lightweight pick-up (5 grammes tracking weight). High output mono ceramic cartridge. Autostop. Overall motorplate size. 12 x 10 x 2 1/2in. below and 2in above. UNREPEATABLE OFFER AT 89/6 Carr. 4/-

THE NEW HARVERSON KIT FOR THE HOME CONSTRUCTOR

A really excellent all purpose A.C. mains 200/240V. AMPLIFIER KIT TYPE HSL 'FOUR' 3 VALVE 4 WATT USING ECC83 EL84, EZ80 VALVES Special features include: Heavy duty double-wound mains transformer with electrostatic screen. Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. Heavy negative feedback loop over 2 stages ensures high tone output at excellent quality with very low distortion factor. Suitable for use with guitar, microphone or record player. Provision for remote mounting of controls or direct on chassis. All this builds onto a chassis size only 7 1/2in. wide x 4in. deep. Overall height 4 1/2in. All components and valves are brand new. Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder etc. (No extra to buy). PRICE 79/6 P. & P. 5/- Comprehensive circuit diagram, practical layout and parts list 2/6. (Free with Kits.)



QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. Size 7in. w. x 2 1/2in. d. x 5 1/2in. h. This amplifier (which is used in a 29 in. record player) employs heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate bass, treble and volume controls. Complete with output transformer matched for 3 ohm speaker. Ready built and tested PRICE 69/6 P. & P. 3/6. ALSO AVAILABLE. Mounted on board with output transformer and 6in. speaker, ready to fit into cabinet below. PRICE 89/6. P. & P. 4/6.

QUALITY PORTABLE R/PLAYER CABINET

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autochanger or single Record Player Unit. Size 18 x 14 x 6 1/2in. PRICE £39.6. Carr. 5/-

LATEST MODEL B.S.R. TU/12 4-SPEED PLAYER AND PICK-UP

ONLY 69/6 Carr. 4/- 7in. metal turntable Low flutter performance. 200/250 v. shaded pole motor. 90 v. tap for valve heaters. High gain crystal pick-up with turnover L/178 head complete with sapphire styli.



3-VALVE AUDIO AMPLIFIER MODEL HA34




Designed for Hi-Fi reproduction of records A.C. Mains operation. Ready built on plated heavy gauge metal chassis size 7 1/2in. w. x 4in. d. x 4 1/2in. h. Incorporates ECC83 EL84 EZ80 valves heavy duty double-wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, etc. £4.5.0 P. & P. wired and tested for only..... 5/-

NEW CARTRIDGE BARGAINS

ACOS 715 single sided crystal cartridge for Stereo and L.P. records. Complete with diamond stylus and universal mounting bracket. List price £26.4. Our price 18/6. P. & P. 1/- RONETTE STEREO 105 CARTRIDGE. Stereo/LP/78. Complete with two sapphires. Original list price 67/9. Our PRICE 24/- P. & P. 1/- GARRARD GC2 Mono complete. List price 24/11. OUR PRICE 12/6. P. & P. 1/-

STEREO AMPLIFIERS

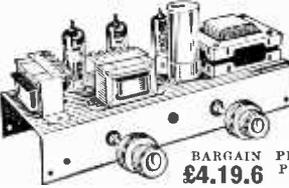Incorporating 2 EL82's and 1 EZ80 heavy duty double-wound mains transformer. Output 4 watts per channel Full tone and volume controls. Absolutely complete.



BARGAIN PRICE £4.19.6 P & P. 5/-

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. Printed circuit panel (size 9 1/2 in.). 8 pre-aligned I.F. transformers. High-gain Ferrite Rod Aerial. All First-grade transistors. Car aerial winding. Push-pull output. All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time. ONLY £45.0. P. & P. 2/6. Circuit diagram 1/6 (free with set of parts).

35 OHM SPEAKERS

Suitable for use with above. 2in. Goodmans. Ideal replacement for most pocket portables, 8/6, 3 1/2in., 12/6; 5in., 17/6; 7 x 4in., 21/-, P. & P. 1/6 per speaker.

Portable CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2in. Suitable for above using 3 1/2in. speaker, 25/- P. & P. 2/-

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers, one oscillator coil, one driver transformer and wind Ferrite aerial (med., long and car aerial coupling). 32/6 complete, post 1/- 6 transistor printed circuit board to match, 8/6. Post 9d. Circuit diagram 1/6 extra.

SPECIAL BRAND NEW TRANSISTOR BARGAINS

GET 15 (Matched Pair) 15/-; V15/10p, 10/-; OC71 5/-; OC76 6/-; AP17 7/6; ORP12 10/6. Set of Mullard 6 transistors, OC44, 2—OC45. OC81D matched pair, OC81, 25/- EDISWAN MAZDA PXA101 6/6; XA103 6/6. P.F. Pack: 1—PXA102 Mixer; 2—PXA101 I.F. Amp. (Equip. OC44 and OC45).....10/6 R.F. 2 Pack: 2—PXA101 I.F. 1—PXA102 Osc.; 1—PXA102 Mixer12/6 L.P.6 Pack: Consisting of PNB13 Driver, Matched pair PX171 mounted complete with heat sinks (Equip. OC81 and OC81).....12/6 ALL TRANSISTORS POST FREE.

HARVERSON SURPLUS CO. LTD. 170 HIGH ST., MERTON, S.W.19 CHERRYWOOD 3985 Open all day Saturday Early closing Wed. 1 p.m. (Please write clearly) A few minutes from South Wimbledon Tube Station PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA. SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEE RIGHT HAND PAGE FOR MORE ITEMS

HARVORSON AMPLIFIER BARGAIN

Special offer of Manufacturers' Surplus
2 VALVE GRAM AMPLIFIERS

Valves UY85 Rectifier and UCL82 Triode/ Pentode giving 31 watts output. Overall chassis size (inc. valves) 5in. high x 5 1/2 in. wide x 2 in. deep. Each amplifier new and tested and supplied complete with valves, 3 ohm output transformer and knobs for tone and volume/on off controls.
ONLY 37/6 P. & P. 3/6

Can be used with 80v. motor tap or 1.5k. mains dropper 2/6 extra if required. Owing to the limited number available and the extremely high value we regret we cannot enter into any correspondence.

BRAND NEW 3 OHM LOUDSPEAKERS

6in., 12/6; 6 1/2in., 15/-; 8in., 21/-; 10in., 25/-; 12in., 27/6; (12in. 15 ohm, 30/-); 10in. x 6in., 26/-
Latest type E.M.I. 13 1/2 x 8in. with high flux ceramic magnet, 11,000 gauss. Aluminium centre cone. 10 watts, 50 c/s to 10 Kc/s, 42/-, P. & P. up to 6in. 1/6; over 6in. 2/6 per speaker.

TAPE DECKS

COLLARO STUDIO DECK. 3 motors, 3 speeds, push button control. Up to 7in. spools. £10.10.0. P. & P. 5/6.

B.S.E. MONARDECK. Single speed, 3 1/2in. per sec., simple control uses 6 1/2in. spools, £8.15.0 plus 5/6 carr. and ins. Tapes extra on both.

BARGAIN OFFER CORNER

PRECISION 6 MINUTE DELAY ACTION SWITCH. Clockwork actuated. Made by Smiths. Separate switching actions at intervals up to 6 mins. Each switch action designed for current loading up to 15 amps at 250 volts. Suitable for photographic timer, automatic washing operations, etc., etc. Brand new and unused units offered at a fraction of their true value. **OUR PRICE ONLY 10/- each.** Post Free. 2 for 17/6. Special quotations for quantity.

MAINS OPERATED WATER COOK. A solenoid actuated flow control valve. 200/230v. 60 c/s. A.C. operation. Operating solenoid is isolated by rubber diaphragm from valve mechanism which is contained in heavy cast brass base. 4in. O.D. plain tub outlet. 3/4in. inlet hose fitted with filter. As used in automatic washing machines and ideal for any application where remote flow control of fluids is required. Brand New. Approx. size 3 1/2 x 1 1/2 x 3 1/2in. high. 12/6 each. **POST FREE.**
HEAVY DUTY NON INDUCTIVE D/P MICRO SWITCH. Conservatively rated 10 amps at 250v. Standard one-hole fixing. Body size 1 1/2 x 1 1/2in. deep, inc. terminals. 3/- each. Post Free.
A.C. MAINS NEON INDICATOR. For panel mounting, cut out size 1 1/2 x 3/4in. deep inc. terminals. With case with red lens giving bright light. A.C. 200/250v. 2/6 each. Post Free.

ROLA CELESTION. Approx. 9 x 6in. 3 ohm Middle register speaker, 10/6. P. & P. 2/6.

EMAIR AND REXINE SPEAKER AND CABINET FABRICS. Approx. 5 1/2in. wide. Usually 35/- yard. **OUR PRICE 13/6 per yard length.** P. & P. 1/9 (min. one yd.). S.A.E. for samples.

ACOS CRYSTAL MIKES. High imp. For desk, or hand use. High sensitivity, 18/6. P. & P. 1/6.

SSL CRYSTAL STACK MIKE. Listed at 45/-. **OUR PRICE 13/6.** P. & P. 1/6.

T.C.C. SUPPRESSOR CONDENSERS. 250v. A.C. .005 + .005 x .1. In tubular can 1 1/2in. long x 1 1/2in. dia. 2 for 3/-. Post Free.

TRANSFORMER DRIVER and O/P TRANSFORMERS. (Tapped 3 ohms and 15 ohms output). Plus 4 suitable Transistors giving approx. 1 watt output. 25/-, P. & P. 2/6.

CONDENSERS. 5,000 mFd, 12v. wkg. Size 2 x 1 1/2in. dia. 2/- each. P. & P. 1/6.
0-GANG .0005 TUNING CONDENSERS. 2 1/2in. h. x 2 1/2in. d. x 5in. w. with built-in trimmer. 4/6. P. & P. 1/-.

CONTACT COOLED BRIDGE RECTIFIERS. 250v. at 125 mA. Size 1 1/2 x 1 1/2 x 1 1/2in., 7/6. P. & P. 1/6.

MATCHED PAIR OF WATT RESISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 x 2in. Output trans. tapped for 3 and 15 ohm output. 10/- pair. P. & P. 2/6.

BRAND NEW PLESSEY 12v. 4 pin non-synch. vibrators. Type 12.1.48D. ONLY 3/6. P. & P. 1/6 each.

TWIN TELESCOPIC AERIAL. Comprising two 3-section heavily chromed rods. Closed 12in. each extending to 32in. each. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting brackets, coax lead and plug. Suitable for F.M. or T.V. 12/6 plus 2/- P. & P.

4-WAY NON-TANGLE TELEPHONE CABLE. Latest design back coil type, extends 12in. to 6ft. Complete with rubber bushes, 4/6 each. P. & P. 1/6.

Harverson Surplus Co. Ltd.



SENSATIONAL HALF-PRICE OFFER!

THE FAMOUS
'Continental'
RADIOGRAM
AT
HALF PRICE!

Magnificent Stereophonic Radiogram Chassis complete with two 10in. elliptical loudspeakers. Plus a Mono Stereophonic 4-speed automatic record changer

Only £29-19-6

- Easily fitted
- No soldering or technical knowledge necessary
- Fits almost any cabinet with minimum trouble
- Built-in ferrite rod aerial
- Piano key switching
- Luxembourg and Caroline received at full strength
- Listen to U.S.A., Russia, Africa Canada and even Australia
- Unique Lewis Radio 365 day guarantee, even on all the valves
- All British make

SPECIAL terms available of £3 deposit followed by 18 monthly payments of £1.14.6 (Total H.P. payments £34.1.0) post and packing 15/- extra.

INDIVIDUAL CABINETS SUPPLIED ON REQUEST

To avoid disappointment send cheque or P.O. for £3.15.0 immediately



LEWIS RADIO (P.W.55) 100 Chase Side, Southgate, London, N.14. Telephone: PAL 3733/9646

RADIO CLEARANCE LTD.

27 TOTENHAM COURT ROAD, LONDON W.1. Telephone: MUSEUM 9188
Trade enquiries invited. The oldest component specialists in the trade. Est. 35 yrs.

LOUDSPEAKER BARGAINS STILL AVAILABLE

Enormous purchases of Brand New and Guaranteed Plessey loudspeakers enable us to offer these units at THE LOWEST PRICES EVER! Don't miss this golden opportunity to obtain a first-grade permanent-magnet LOUDSPEAKER off the production line at LESS THAN THE MANUFACTURER'S COST! Read carefully the prepared list below and choose just the right speaker for the job—COMPARE THE PRICES ANYWHERE! SELLING FAST—STOCKS CHANGING RAPIDLY.

SCHEDULE OF LOUDSPEAKERS AVAILABLE															
Diameter				Gauss				Imped.							
in.	lines	in.	ohms	Price	in.	lines	in.	ohms	Price	in.	lines	in.	ohms	Price	
2 1/2	7000	80	8 1/2	3 1/2	9500	3	10/8	4	9500	25	11/8	4	9500	3	8/-
2 1/2	7000	35	8/6	3 1/2	9500	3	10/8	5	9500	3	8/-	5	7000	3	8/6
2 1/2	7000	80	8/6	3 1/2	7000	35	8/6	5	7000	3	9/6	5	7000	3	9/6
2 1/2	7000	80	8/6	3 1/2	9500	50	10/6	5	7500	3	9/6	5	7500	3	9/6
3	8500	3	10/-	4	6000	25	11/8	5	8500	3	10/8	5	8500	3	10/8
3	6000	5	8/6	4	6000	35	10/8	5	9500	3	12/6	5	9500	15	12/6
3	7000	5	9/-	4	7000	35	9/6	5	8500	25	10/8	5	8500	25	10/8
3	7000	35	9/-	4	7500	5	9/6	5	9500	35	11/6	6 1/2	6000	3	11/-
3	6500	80	9/6	4	9000	50	11/8	5	9500	35	11/6	6 1/2	6000	3	11/-
3 1/2	6000	15	10/-	4	9500	35	11/8	5	8500	15	12/6	6 1/2	6000	15	13/6
3 1/2	7000	3	9/6	4	9500	15	12/-	8	6000	15	13/6	8	6000	15	13/6

ALLOW 2/- each Speaker for postage and packing and handling charge and please specify the exact requirements—the nearest available will be sent.

BEAUTIFULY REARED AM/FM 2 GANG CONDENSERS. 4/6: AM/FM IFT'S 485 kc/s and 10.7 Mc/s 4/6 pair; Magnavox Crystal Tape Recorder Mikes, 12/6; 3 watt Stereo Amplifiers, complete, ready to switch on, 79/6; Sentercell rectifiers R3/2D-D3-2-1-Y. 2/6 each. DIODES—OAT9, OA90, CG46H, GD10, 2/- each. TRANSISTORS: OC45 4/6, FXA101, 3/6, AF115, 4/6. Sub. min. Germanium diode 1/3, M1 diode 6d. each. Silicon diodes, 200 p.p.t. 200 mA. 1/- each. 400 p.p.t., 300mA, 2/6 each please send STAMPED and ADDRESSED envelope with any enquiry. We reserve no catalogue—our stocks move too quickly! Kindly make provision for additional postage and package charge to avoid delay. Terms: Cash With Order or C.O.D. on Orders over 10/-.

TEST METERS



90,000 O.P.V. MODEL TP 55. Reads voltage up to 1,000 D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500ma; Resistance to 10 Megs.; Capacitance to 0.1µF; Decibels from -20 to +36. Size 3 1/2in. x 5 1/2in. x 1 1/2in. £5.19.6.

90,000 O.P.V. MODEL TP 10. Reads A.C. and D.C. Volts up to 1,000; D.C. Current to 500ma; Resistance to 1 Meg; Capacitance to 1µF; Decibels from -20 to +36; Output jack for Audio Measurements. Size 3 1/2 x 5 x 1 1/2in. £8.19.6.

80,000 OHMS PER VOLT MODEL 500. Reads voltages up to 1,000 D.C. at 30,000 ohms per volt and A.C. at 15,000 O.P.V.; D.C. current to 12 amps. Resistance to 50 Megs.; Decibels from -20 to +56; Incorporates internal buzzer for audible warning of a.c. shorts and blocking condenser for A.F. output measurements. Size 3 1/2 x 5 1/2 x 2 1/2in. £8.19.6.

TRANSISTORISED TEST EQUIPMENT. Fully guaranteed, brand new. By NOMBREX: 150 Kcs.—350 Mc/s. Signal Generator, £9.10.0. Resistance-Capacitance Bridge, £5.5.0. 1.5 volts D.C. Power Supply, £8.10.0. Audio Generator 10/100,000 c/s., £16.15.0. Inductance Bridge, £18.0.0.

By T.M.K. INSULATION TESTER. Measures up to 500 megohms at 3 testing voltages, 100, 250 and 500. Supplied with leather case and leads, £17.10.0. Illustrated details on any of the above sent on request.

LINEAR AMPLIFIERS. LG34, 4 watts, size 8 1/2 x 4 x 2 1/2in. high, £5.5.0. L45A 5 watts, size 7 x 7 x 5in. high, £5.19.6. Protective cover, 12/9. L55/55 5 watts stereophonic, size 10 1/2 x 8 x 6in., £12.0. Cover with carrying handles 25/-. "Dialonic" 10 watts Hi-Fi Ultra Linear Push-Pull size 9 x 7 x 4 1/2in. high, £12.12.0. Cover with carrying handles, 19/6. L1/10 10 watts Hi-Fi Ultra Linear size 9 x 7 x 6in. high, £13.13.0. Cover with carrying handles, 19/6. "Onchord" 30 watts Hi-Fi Ultra Linear size 12 1/2 x 9 x 7 1/2in. high, £18.16.0. Cover with carrying handles, 25/-. L50 50 watts Hi-Fi Ultra Linear, size 14 x 10 x 8in. high, £23.2.0. Cover with carrying handles, 32/6. All amplifiers for normal A.C. mains, and ex stock. Details on request.

"Tripletone" Convertible Amplifier. Size 10 x 3 x 4 1/2in. high. 4 watts output matched for 2-3 ohms. OR 2 amplifiers can be coupled together for STEREO, £8.19.6 each.

"Tripletone" F.M. Tuner, size 11 x 6 x 3in. high. Coverage 86-104 Mc/s. £13.19.6 (unpowered), or £15.12.6 (self powered). Details on request.

MICROPHONES. Crystal Types. Guitar 19/6. Desk, with built-in stand 15/-. Acos 39/1 stick, and Table Stand 32/6. Super Stick, with heavy Desk Stand 49/6. Moving Coil Types. Stick, with heavy Desk Stand 59/6. "Slimline" Stick, 50K impedance, with switch 75/-. Omni-directional chrome plated die-cast frame, 50K, with switch 99/6.

ADJUSTABLE MIKE STANDS, with heavy bases and plated stems. Table type 29/6, floor type 55/-. Details on request.

HARRIS ELECTRONICS (London) LTD.

138 GRAY'S INN ROAD, LONDON, W.C.1
Telephone: TERminus 7937
Please include carriage cost on ALL items
Trading hours 9 a.m. - 6 p.m. Monday - Friday. Closed Saturday. We are 2 mins. from High Holborn (Chancery Lane Station) and 6 mins. by bus from King's Cross.

NEW VALVES!

Guaranteed Set Tested 24-HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET OF 4, 14/-, DAF96, DF96, DK96, DL96, SET OF 4, 22/6.

0A2	3/9	DY86	6/6	PCL83	7/9
1D5	4/9	DY87	7/6	PCL84	7/9
1R5	4/3	EABC80	5/9	PL36	7/9
1S5	3/3	EBC41	6/3	PL41	6/9
1T4	2/3	EBF80	5/9	PL82	5/-
3S4	4/3	ECC81	3/6	PL83	5/11
3V4	5/-	ECC82	4/6	PL84	6/3
5Y3GT	5/3	ECC83	4/9	PY32	8/6
6KT6	1/3	ECC84	6/3	PY33	8/6
6K9C	3/3	ECC85	6/-	PY80	4/9
6QT6	4/3	ECF80	7/6	PY81	5/3
6SL7GT	4/6	ECF82	7/-	PY82	4/11
6V6G	3/6	ECH42	7/3	PY83	5/6
12K7GT	3/3	ECH81	6/-	PY800	5/11
12K9GT	9/6	ECL80	5/11	U25	8/-
12Q7GT	3/3	ECL82	6/6	U26	8/6
20P4	13/3	ECL86	8/-	U191	9/6
25L6G	4/9	EF39	3/6	U301	11/-
35L6GT	6/-	EF41	5/9	U301	15/-
8A2	5/9	EF49	4/9	U301	5/-
DL33	8/6	EF85	4/6	UAF42	6/11
DAC92	7/6	EF86	6/3	UBC41	6/-
DAF91	3/3	EF89	4/3	UBF80	5/6
DAF96	5/6	EL41	7/-	UCC84	7/11
DF33	7/6	EL84	4/9	UCC85	6/-
DF91	2/3	EY51	5/6	UCR80	8/3
DF96	5/6	EY86	5/6	UCH42	6/9
DH77	3/6	EZ40	5/-	UCH81	5/9
DK32	7/6	EZ80	3/9	UCL82	7/3
DK91	4/3	EZ80	4/3	UCL83	9/6
DK92	8/-	KT41	6/6	UF41	6/3
DK96	6/3	PCC84	5/6	UF89	5/9
DL33	6/9	PCC89	8/6	UL41	7/-
DL35	5/-	PCF80	6/9	UL84	5/9
DL82	4/3	PCF82	6/-	ULC	5/9
DL84	5/-	PCF805	9/-	UY41	3/11
DL96	5/6	PCL82	5/3	UY85	4/11

Postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD, STOKES NEWINGTON, LONDON, N.16.

1965 EDITION RADIO AMATEUR HANDBOOK

40/- by ARRL Postage 2/- WORLD RADIO TV HANDBOOK 1965, 26/-, Postage 1/-.

RADIO SERVICE TRAINING MANUAL by E. F. Rice. 30/-, Postage 1/-.

UNDERSTANDING TRANSFORMERS & COILS by E. J. Bukstein. 16/-, Postage 1/-.

TAPE RECORDERS—How they work by C. G. Westcott and R. F. Dubbe. 26/-, Postage 1/-.

RADIO WAVE PROPAGATION VHF & ABOVE by P. A. Matthews. 28/-, Postage 1/-.

INTER: G.E.C. TRANSISTOR MANUAL. 7th Ed. 18/-, Postage 1/6.

HI FI YEAR BOOK 1964. 10/6, Postage 1/-.

AN ELECTRONIC ORGAN FOR THE HOME CONSTRUCTOR by A. Douglas. 20/-, Postage 1/-.


COMPLETE CATALOGUE 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books
19-21 PRÆD STREET LONDON, W.2
Phone: PADDington 4185
Open 6 days 9-6 p.m.

FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS

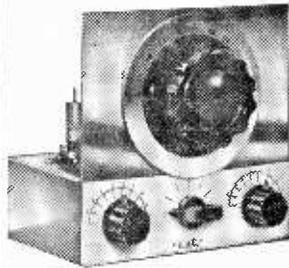

H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hms, etc.

IMPROVED 1965 RANGE

1-Valve model "CX", complete kit, Price 34/6
Customers say: 'Definitely the best one-valve S.W. kit available at any price'. This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and, of course, as all our products, fully guaranteed. FULL RANGE of other kits still available including the famous model 'K', price 77/-.

Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to:—

"H.A.C." SHORT-WAVE PRODUCTS (Dept. T.H.), 44 Old Bond St., London W.1

ONLY 7" 6" LONG! LISTEN AND ENJOY THE WORLD'S RADIO AMATEUR AND BROADCAST STATIONS WITH THE GREATEST OF EASE !!!

WE HAVE SOLVED your aerial problem for WORLD-WIDE RECEPTION—NO MATTER WHERE YOU LIVE !!!

World Expert Radio Amateur WIBB (U.S.A.) claims the "JOYSTICK" aerial—easier to read stations than with his massive 520' VEE aerial 70' high!!! ZL4GA, who is probably NEW ZEALAND's best known Radio Amateur, has scrapped his outstanding 300' 45' high aerial and has WORKED ALL CONTINENTS on the "JOYSTICK" in under 12 hours !!!

"CQ" the Radio Amateur's Journal claims "JOYSTICK" better for reception than the world popular DIPOLE (four different receivers used to confirm this decision!)

YOU CAN BE THE PROUD OWNER OF THE WORLD'S MOST VERSATILE & COMPACT "JOYSTICK" COMPLETE RECEIVING SYSTEM FOR AS LITTLE AS

£5.11.0 (Standard system) p. & p. included or the De Luxe system for £6.11.0 p. & p. included.

Money Back if not Delighted. Not convinced? Then send for brochure and showers of testimonials to:—

PARTRIDGE ELECTRONICS LTD

(Dept. PW)
7 SOWELL ST., BROADSTAIRS, KENT

CONCORD — Pioneers of the Low Priced Kits

MAKE 5 DIFFERENT TRANSISTOR RADIOS FOR
35/-

NO EXPERIENCE NECESSARY.
 No soldering. Only 8 connections for first radio to work. Just look, you get

A.B.C. Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. YES — EVERYTHING! Loud clear English and Foreign reception. As supplied to Educational Authorities. H.M. Forces, etc. **TESTIMONIALS GALORE.** Mr. R. O'D. of Londonderry, writes: "... I received your components and I must say that I am very satisfied with them. I have it already set up!..." **COMPLETE HOME RADIO COURSE** Originally 50/- **SEND ONLY 35/- plus 2/6 post etc. (C.O.D. 3/- extra).**



NEW RADIO ANYONE CAN BUILD
IN 2-3 HOURS
19/6

EVEN THE OLDER CHILDREN BUILD THEM!... no soldering—only 16 connections! then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 x 1 1/2 in. Many Testimonials: M.H. of Bradford, writes: "... I have just completed one of your sets successfully. It is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them..." Direct from Manufacturers to You. Send 19/6 plus 1/6 post etc. (C.O.D. 2/6 extra). **PARTS AVAILABLE SEPARATELY**



AMAZING CIGARETTE RADIO!
ONLY 18/6

You get a perfectly ordinary packet of cigarettes! — but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 Cigarettes—yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our glowing testimonial file, Mr. D. B. of Huddersfield writes: "... I have fitted the parts in and it is working wonderfully..." **ALL PARTS** including Semi-Conductors, A.B.C. Plans, etc. **ONLY 18/6 plus 1/6 post, etc. (C.O.D. 2/6 ex.)** (Parts available separately).



READ WHAT SATISFIED CUSTOMERS SAY

- | | | | |
|--|---|--|---|
| R.C. of HARRINGAY writes
Received with thanks Skyrama
... Very pleased. Working well. | L.S. of LONDON W.8 writes
... given it a good try out
and I am very pleased with
the results. | D.R. of GLASGOW writes
... it is a lovely little thing
and as clear as a bell. | J.W. of BRIGHTON writes
... I have recommended your
radio to many of my friends. |
| B.M. of HARROGATE writes
... I would like to thank
you ... It is a real bargain. | S.B. of SOMERSET writes
... delighted with this radio
... glad if you could send one
more. | T.F. of STEVENAGE writes
I would just like to say how
pleased my son is with this
radio. | W.H. of MIDDLESEX writes
Thank you for my dear little
radio. It is a real treasure
to me. |

CONCORD ELECTRONICS SEND 1/- FOR FULL LIST OF OTHER KITS AND STOCK RANGE LTD. (Dept. P.W.19) 9 Western Road, Hove, Sussex

*"I had six faithful serving men,
 Who taught me all I knew,
 Their names were 'How' and 'Why' and 'What',
 And 'When' and 'Where' and 'Who'"*

We wonder what the six faithful serving men would say, if you asked them:—

1. **Where** can I buy a special-purpose screw-driver that holds the screws firm on the end of the blade?
2. **Who** makes the "Transmatch" Transistor pre-amplifier?
3. **What** is the resistance of an Electrovoice 101G L.F. Choke?
4. **How** is a PA1 coil wired up?
5. **Why** cannot a Ribbon Microphone be used out of doors?
6. **When** must a parcel be sent by road or rail?

Poor faithful serving men... even a pile of encyclopaedias would not help them here! If only they had known that these and thousands of other such questions can be answered with a Home Radio Catalogue!

You may not be seeking a situation as a faithful serving man, but we are sure you will be interested in having a complete reference of some 5,000 modern electronic components, showing sizes, data and prices, and illustrating over 800 of them. This Catalogue will save you not only money, but time, trouble and temper. Incidentally, in each Catalogue are 5 coupons each worth a 1/- when used as directed. Send us 6/- to-day with the coupon. This unique Catalogue will be sent by return post.

Please write your name and address in block capitals

NAME

ADDRESS

.....

.....

HOME RADIO LTD., Dept. P.W., 187 LONDON ROAD, MITCHAM

VEROBOARD

The perforated Copper Board for Modern Circuitry

- .15 x .15 pitch
- 2.5 x 3.75 .. 3/- 3.75 x 3.75 .. 3/8
- 2.5 x 5 .. 2/8 Spot face cutter 9/-
- 3.75 x 5 .. 3/-
- Special Veropins, Pkts. 200 .. 14/-
- P. & P. on all items 1/-

TRANSISTORISED MORSE OSCILLATOR

Fitted 2 1/2in. Moving Coil Speaker. Uses type PP3 or equiv. 9v. battery. Complete with latest design Morse Key, 22/6, plus 1/6 P. & P.

- TRANSISTORS—1st Grade only, no seconds, no rejects, no surplus.
- OC28 17/- OC77 9/- GET105 10/-
 - OC29* 15/- OC81* 8/- GET573 12/6
 - OC41 7/- OC83* 6/- ZN706A 17/6
 - OC44 6/6 OC19 12/- 2N458 20/-
 - OC45* 5/- OC149 19/- SEB35 7/6
 - OC71 8/- OC171 10/8 AC107 14/6
 - OC72* 7/- OC200 10/8 AF114 11/-
 - OC73 6/- OC201 21/- AF115 10/6
 - OC75 7/- OC203 14/- AF116 10/-
 - OC76 6/- GET104 6/- AF117 9/6

*Available in matched pairs

SIEMENS SEALED H/S RELAYS

- H96A, 2.2 ohm + 2.0 ohm, new .. 12/6
- H96B, 5.0 ohm + 5.0 ohm, new .. 12/6
- H96C, 145 ohm + 145 ohm, new .. 12/6
- H96D, 500 ohm + 500 ohm, new .. 12/6
- H96E, 1700 ohm + 1700 ohm, ex-equip. ... 16/6

BUILD AN EFFICIENT STROBE UNIT FOR ONLY 37/6.

This wonderful device enables you to "freeze" motion and examine moving parts as stationary. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. New modified circuits bring price down to 37/6 plus 3/- P. & P.

NSP2 CV236 STROBOTRON FLASH-TUBE made by Ferranti, brand new, I.O. base. Price 15/- P. & P. 1/-.

NEW 1/2 AMP FULL RANGE

Variable Voltage Transformer
 Input 230v. A.C., Output continuously variable from 0-230v. at 1 amp. Open type as illustrated, £3.3.0., inc. post. 1 amp type fully shrouded £4.10.0. Also available, 2.5, 4, 5, 8, 10, 12, 20, 37, 5 and 50 amp. Write for details.



£3.3s.0d.1/-

LIGHT SENSITIVE SWITCH
 Kit of parts, including ORP .12 Cadmium Sulphide Photo-cell, Relay Transistor and Circuit, etc., price 25/- plus 2/6 P. & P. ORP .12 including circuit, 10/6 each, plus 1/- P. & P.

D.C. AMMETERS

- 0-20 amp. D.C. M-Coil 2 1/2in. round .. 12/6
- 0-5 amp. D.C. M.I. 2 1/2in. round .. 11/6
- 0-500 Microamp, sub-min. 1 1/2in. dia. .. 21/-
- Scaled 0-1 milliamperes .. 21/-

ULTRA VIOLET BULBS

Easy to use source of UV for dozens of practical and experimental uses.

12 volt 36 watt AC/DC SBC 8/6, P. & P. 1/-

12 volt 60 watt AC/DC SBC 8/6, P. & P. 1/-

Transformer to suit the above: Input 200-240 A.C. Output 12 Volt A.C. 36 watt, 16/6, P. & P. 2/6. Input 200-240 A.C. Output 12 volt A.C. 60 watt, 22/6, P. & P. 3/6.

Set of four colours FLUORESCENT Paint. Orange, Yellow, Green and Red, in 1oz. tins. Ideal for use with the above Ultra Violet Bulbs, 9/6, P. & P. 1/6.

VAN DE GRAAF ELECTRO-STATIC GENERATOR

fitted with Motor drive for 230v. A.C. giving a potential of approx. 50,000 volts. Supplied absolutely complete, including accessories for carrying out a number of interesting experiments, and full instructions. This instrument is completely safe, and ideally suited for School demonstrations. Price £6.8.0., plus 4/- P. & P.



A.C. VOLTMETERS

- 0-200v. A.C. Rect. M-Coil 3 1/2in. type W23 45/-
- 0-300v. A.C. M.I. 2 1/2in. F.L. ... 22/6
- 0-300v. A.C. Rect. M-Coil 2 1/2in. ... 29/-
- 0-300v. A.C. Rect. M-Coil 3 1/2in. type W23 55/-

A.C. AMMETERS

- 0-1, 0-5, 0-10, 0-15, 0-20 amp. F.R. 2 1/2in. dia. All at 21/- each.

SERVICE TRADING CO

PADGETTS RADIO STORES

OLD TOWN HALL, LIVERSEDGE, YORKS.
 Telephone: Cleckheaton 2866

17in. 13 Channel Untested complete TV Sets, 50/-, carriage 10/-

14in. 13 Channel Untested TV sets, 30/-, carriage 10/-, Well packed but sent out at owner's risk.

Special Offer. Brand new rebuilt TV Tubes, 12 months guarantee (not seconds), A.W43/80, MW36/24/44, 37/6, carriage 10/-

Single Phase 240 volt 1400 r.p.m. 1-h.p. motor with pulley, 28/-, less pulley, 24/-, fully guaranteed, ex. washing machine. Carriage 8/6.

One Sixth H.P. Motor. 240 volts, 15/-, post 6/9.

VALVE LIST

Ex equipment, 3 months' guarantee			
EL91	1/6	20P4	8/6
EL80	2/-	U801	8/6
ECC82	3/-	U281	5/-
EY51	2/6	U282	5/-
EY80	5/-	U229	5/-
EF80	4/8	KT36	5/-
EB91	9d.	6V6GT	4/-
EL38	5/-	6B3	1/6
EF91	9d.	6K25	5/6
6F14	1/6	6F25	3/6
6F15	5/-	6U4	5/-
10C2	5/-	PY30	3/-
10P1	1/-	Y81	3/-
10P13	5/-	PL81	4/-
10P14	5/-	PL82	3/-
20D1	2/-	PL83	3/-
20L1	5/-	PL38	3/-
20P3	4/-	Y82	3/-
20P1	4/-	PCP80	4/-
		PCC84	4/-
		PCL82	5/-
		PCL85	5/-
		PL36	5/-
		12A-T7	3/-
		6CH6	1/6
		R18	3/6
		AR12	1/6
		807	5/-
		EF50	1/-
		Doz.	6/-
		EF90	1/6
		Doz.	10/-
		6KT	10/-
		Doz.	10/-
		6V6	1/9
		Doz.	18/-
		6K8	1/9
		Doz.	18/-
		U25	4/-

Bush 9in. TV Set, BBC Only. Untested but complete, 21/-, carriage 10/-.

Just the Job for a Scope. Tested with good tube, 55/-; BBC-ITV. All channels 75/-, carriage 10/-. Well packed but sent at owner's risk.

Spare Tubes, 100%. 17/-, carriage 7/6.

FM Speakers, ex TV sets. All perfect. Rola, 6 x 4, 3/-, post 2/-; six for 20/-, post free.

Goodmans, 7 x 4, 5/-, post 2/-; six for 32/-, post paid. 8in. round 6/-, post 2/-.

Philips, G.E.C., Plessey, 6in. and 5in. round, 3/-, post 2/-.

Reclaimed TV Tubes, Six Months' Guarantee. Mullard MW 43/80, 30/-; Mullard MW 43/68, 30/-; Mazda CRM 172, 30/-; Mazda CRM 142, 17/-, carriage 10/-.

Pumps removed from Washing Machines 7/6, post 2/6.

"GLOBE-KING"

Amateur Short-Wave Radio

For over twenty years the famous incomparable "Globe-King" single-valve kits have been used by enthusiasts in almost every country in the world where low cost but high precision standard equipment was essential and demanded. We now take pleasure in announcing the new transistor version, model TR2—just two transistors gives a tremendous performance. Send s.a.e. today for interesting free literature on this and other equipment. Overseas enthusiasts, note we despatch to all parts of the world via International Postal Services.

JOHNSON (RADIO)

St. Martins Gate, WORCESTER

A.R.R.L. RADIO AMATEURS HANDBOOK 1965

New Edition 40/-. Postage 2/6.

World Radio and T.V. Handbook 1965 by Johansen, 26/-, P. & P. 1/-

How to Listen to the World, new ed. by Johansen, 17/-, P. & P. 1/-

Transistor Substitution Handbook, American, Jap., etc. 12/6, P. & P. 1/-

Amateur Radio Circuits, new ed. by R.S.G.B. 7/6, P. & P. 9d.

101 Ways to use your Oscilloscope by Middleton, 21/-, P. & P. 1/-

British Transistor Directory by Bradley, 8/6, P. & P. 6d.

Guide to Broadcasting Stations, new ed. by W.W. 5/-, P. & P. 6d.

T.V. Fault Finding, new ed. by D.A.T.A. 6/-, P. & P. 6d.

UNIVERSAL BOOK CO.

12 Little Newport Street, London, W.C.2 (adjoining Lisie Street)

Please mention "Practical Wireless" when replying to Advertisements

BBC2 (625 LINE) TV AERIALS



Mast Mounting Arrays, 9 element 45/-; wide spaced high gain, 11 element 55/-; 14 element 62/6. Wall Mounting with Cranked Arm, 9 element 60/-; wide spaced high gain, 11 element 67/6; 14 element 75/-, Chimney Arrays Complete, 9 element 72/-; wide spaced high gain, 11 element 80/-; 14 element 87/6. Loft Arrays, 7 element 32/6; wide spaced high gain, 11 element, with tilting Arm, 62/6; 14 element 70/-. All high gain units have special Multi-rod Reflector. Low loss co-axial cable 1/6 per yard.

BBC • ITV • F.M. AERIALS



B.B.C. (Band 1). Telescopic loft 21/-. External S/D 30/-.

I.T.V. (Band 3). 3 Element loft array 25/-, 5 element 35/-, Wall mounting, 3 element 35/-, 5 element 45/-.

Combining B.B.C./I.T.V. 4/0L1 + 3, 41/3, 1 + 5, 48/9; Wall mounting 1 + 3, 56/3; 1 + 5, 63/9; Chimney 1 + 3; 63/9; 1 + 5, 71/3.

F.M. (Band 2). Loft S/D 12/6, "H", 30/-, 3 element, 52/6. External units available Co-ax cable 8d. vd., Co-ax plugs, 1/3. Outlet boxes, 4/0L1, Duplexer Cross-over Boxes, 12/6, C.W.O. or C.O.D. P. & P. 3/-.

Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept P.W.)

3b Godstone Road, Kenley, Surrey CRO 2527

RES/CAP. BRIDGE 39/6

Checks all types of resistors, condensers 6 RANGES


Built in 1 hour. Direct reading

READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept. K)

Raleigh Mews, Raleigh Street, Nottingham

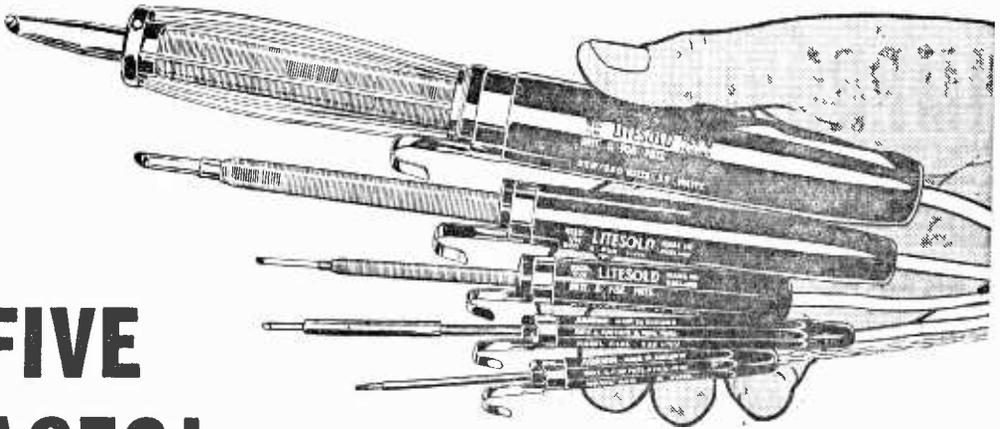


FIVE ACES!

This is a hand that can't be beaten. Five models from our tremendous range of soldering instruments. Superb performance. Amazingly compact. Developed to simplify YOUR soldering. Copper bits for greatest speed. Permatip bits for long life. May we deal you in?

Brochure P.W. 10 post free on request

LIGHT SOLDERING DEVELOPMENTS LTD., 28, Sydenham Road, Croydon, Surrey
Telephone: CROydon 8589

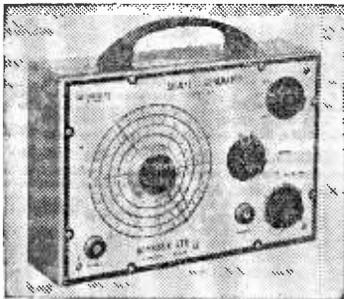NOMBREX INSTRUMENTATION TRANSISTORISED SIGNAL GENERATOR Model 27 £9.15.9



Also available:


- ★ INDUCTANCE BRIDGE 66 ... £18. 5.9
- ★ POWER SUPPLY UNIT 61 ... £6.13.6
- ★ C.R. BRIDGE 62 ... £8.10.9
- ★ AUDIO GENERATOR 63 ... £17.0.9

All Prices include Battery, Post and Packing.
Prompt delivery

S.A.E. for Technical Leaflets

Trade and Export enquiries invited

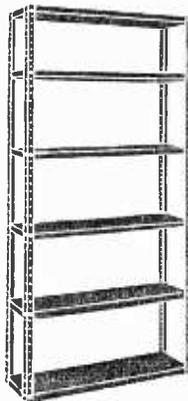NOMBREX LTD. Phone: 3515
Estuary House, Camperdown Ter., Exmouth, Devon



STEEL SHELVING

BRAND NEW

C.W.O. or C.O.D. FREE DELIVERY within 14 days. N. Scotland, Ireland, I.O.M., 10% extra.

65/-

71in. high x 34in. wide 12in. deep with 6 shelves as illustrated.

Each shelf will hold over 3 cwt. Shelves adjustable every 2in. Stove enamelled dark green. White enamel units 60% extra.

Height	Width	Depth	No. of shelves	Price	Extra 3 or more shelves
71 in.	34 in.	9 in.	6	68/-	61/-
71 in.	34 in.	12 in.	6	65/-	63/-
71 in.	34 in.	15 in.	6	74/-	72/-
71 in.	34 in.	18 in.	6	86/-	84/-
35 in.	34 in.	12 in.	6	73/-	71/-
85 in.	42 in.	12 in.	6	81/-	89/-

Contractors to H.M. Govt. and United Kingdom Atomic Energy Authority. Exporters of Steel Shelving.

Buy direct from the manufacturers

R **ROCHDALE METAL PRODUCTS**
WATERFOOT — LANC'S
Lept. F.W. Phone: Rossendale 3221/3

IMPROVED

Modern styling in light grey with legible black engraving.

Constructed to withstand adverse climatic conditions.

Ever ready case, including leads, prods and clips.

Improved internal assemblies.

Re-styled scale plate for easy rapid reading. 2 basic scales, each 2.5 inches in length.

New standards of accuracy, using an individual calibrated scale plate d.c. ranges 2.25% f.s.d. a.c. ranges 2.75% f.s.d.

Available accessories include a 2500V d.c. multiplier and 5, 10 and 25A shunts for d.c. current measurement.



Mk 4

MULTIMINOR

- D.C. Current: 100µA f.s.d. — A f.s.d. in 5 ranges
- A.C. Voltage: 10V f.s.d. — 1,000 f.s.d. in 5 ranges
- D.C. Voltage: 2.5V f.s.d. — 1,000 f.s.d. in 6 ranges
- D.C. Millivolt range: 0 — 100mV f.s.d.
- Resistance: 0.2 MΩ in 2 ranges using 1.5V cell.
- Sensitivity: 10,000Ω/V on d.c. Voltage ranges. 1,000Ω/V on a.c. Voltage ranges.


● For full details of this great new pocket-size instrument, write for descriptive leaflet.

AVO LTD AVOCET HOUSE • 92-96 VAUXHALL BRIDGE ROAD • LONDON, S.W.1 • VICTORIA 3404 (12 lines) **M** Verob

MM17

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up ECC85, ECH81, EFX9, EA8C80, EL84, EM81, EZ80. Three Waveband and Switched Gram. positions. Med. 200-550 m. Long 1,000-2,000 m. VHF/FM 88-95 Mc/s. Philips Continental Tuning Insert with permeability tuning on FM and combined AM/FM IF transformers. 470 Kc/s. and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13½ x 6½ in. Height 7½ in. Edge illuminated glass dia 11½ x 3½ in. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250v. operation. Magic-eye tuning. Circuit diagram now available. Aligned and tested ready for use £18.10.0. Carr. and Ins. 7/8. Complete with 4 Knobs—walnut or ivory to choice. Indoor FM aerial 3/8 extra. 3 ohm P.M. Speaker only required. Recommended Quality Speakers 10in. R.A. 27/8; 13½ x 8in. E.M.L. 'Fidelity' 7/8; 12in. R.A. with conc. Tweeter 42/8. Carr. 2/6

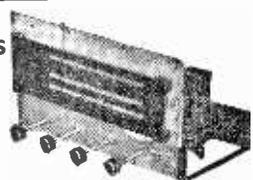

6 VALVE AM/FM TUNER UNIT

Med. and VHF 190 M-550 M, 85Mc/s-103Mc/s, 6 valves and metal rectifier. Self contained power unit. AC 200-250 v. operation. Magic eye indicator, 3 push-button controls, on/off. Med., VHF diode and high output sockets with gain control. Illuminated 2-col. perspex dial 11½ x 4in. Chassis 11½ x 4 x 5½ in. A recommended Fidelity Unit for use with Mullard 3/5-510 amplifiers. Available only at present as built up units, aligned and tested ready for use. Bargain price £18.10.0 Carr. 5/- We hope to produce this popular unit in kit form very shortly.

TRANSISTOR COMPONENTS

- Midget I.F.'s—465 Kc/s⁷/₁₆ in. diam. 5/3
- Osc. Coil M. & L.W. 5/9
- Midget Driver Trans. 3.5-1 6/9
- Output Trans. Push-Pull 3 ohms ... 6/9
- Elect. Condensers—Midget Type 1 mfd. 50 mfd. ea. 1/8, 100 mfd. 2/-, 12V.
- Condensers 150 v. working; .01 mfd., .02 mfd., .03 mfd., .04 mfd. 9d.; .05 mfd. 1 mfd., 1/-, .25 mfd., 1/3; 5 mfd., 1/6 etc.
- Midget Tuning Condensers. J.B. "OO" 208 pF and 176pF, 8/6; ditto with trimmers, 9/6. J.B. 220pF and 105pF conc. slow motion 10/6. 366pF single 7/6.

CONDENSERS—Silver Mica. All values, 2 pf. to 1,000 pf. 6d. each. Ditto ceramic 9d. Tub. 450 v. T.C.C. etc. .001 mfd., .01 and 1/350 v. 9d. .02-1/500 v., 1/-, .25 Hunts 1/6. .5 T.C.C. 1/9 etc. CLOSE TOL. S/MICAS. 10% 5 pf-500 pf. 8d. 600-5,000 pf. 1/-. 1% 2 pf.-100 pf. 9d. 100 pf.-500 pf. 11d. 575 pf.-5,000 pf. 1/6.

JASON F.M. TUNER UNITS Designer-approved kits available. FMT1. 5 gns. 4 valves 20/-. FMT2. 7 gns. 5 valves 35/-. JTV Mercury. 10 gns. 3 valves 22/6. JTV2. £18.19.6. 4 valves 28/6. NEW JASON F.M. HANDBOOK 2/6. 48 hr. Alignment Services, 7/6 plus 2/6.

BARGAIN BUY !

A 34 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- carr. Supplied in 3 Units already wired and tested. A Modern Circuit for quality recording from Mike, Gram or Radio, using latest B.S.R. Twin Track Monardeck Type TD2. Valve line up—EF86, ECL82, EM84, EZ80, and Selenium Diode. Send for detailed list—3d. stamp.



- Complete Kit Comprising items below:
- 2-tone Cabinet and 3in. x 5in. Speaker. Size 14 x 10½ x 7½ in. £8.10.0 Carr. 5/-
 - Wired Amplifier complete with 4 Valves, front Panel, Knobs, etc. £5.15.0 Carr. 3/6
 - B.S.R. Monardeck Type TD2. 27. 7.0 Carr. 4/6
 - Accessories: Mike, Tape, empty Reel, screened Lead and Plugs, Instructions, etc. £1.0.0 Carr. 2/-

BARGAIN PRICE 15 GNS. Carr. 10/-

RESISTORS—Modern ratings full range 10 ohms to 10 megohms. 20% ½-½ w. 3d. ea., ditto 1 w. 6d. ea., 2 w. 9d. ea., 10% ½-½ w. 4d. ea., 5% Hi-stab, ½-½ w. 6d. ea. (below 100 ohms and over 1 meg. 9d. ea.). 1% Hi-stab., ½ w. 1/8 ea. (below 100 ohms 2/- ea.)

WIREWOUND. 25 ohms to 10K. 5 w. 1/8. 10 w. 1/6. 15 w. 2/-.

VOLUME CONTROLS—5K—2 Meg. ohms, 3in. SPINDLES MORGANITE MIDGET TYPE. 1½ in. dia. Guar. 1 year. LOG or LIN, ratios, less Bw. 3/-. D.P. Sw. 4/6. EFL83 10/6. PLS3 10/6. EFX90 7/6. PLS1 9/8. EFS6 8/6. PLS3 8/-.

ENAMELLED COPPER WIRE—½ lb. reels 14g-20g, 2/8; 22g-28g, 3/-; 30g-34g, 3/9; 36g-38g, 4/8; 39g-40g, 4/6. etc.

TINNED COPPER WIRE. 16-22g. 2/8 ½ lb.

Boxed	Reduced
New VALVES	Bargain Prices
1T4 3/8	EY86 9/8
1K5, 135 6/-	EZ81 7/8
884, 374 7/-	EZ82 8/6
ECC81 7/-	PCC84 8/6
ECC82 7/-	PCF80 8/6
ECC83 7/-	PLC83 10/-
ECC85 7/-	PLC84 10/-
ECL82 9/-	PCL84 11/6
ECL83 10/6	PLS3 10/6
EF80 7/6	PLS1 9/8
EFS6 8/6	PLS3 8/-
EL33 12/6	FY33 10/6
EL34 12/6	FY33 7/8
EL34 7/-	U35 10/6
EY51 9/-	UL84 9/8



Send for detailed bargain lists, 3d. stamp. We manufacture all types Radio Mains Transf. Chokes. Quality O/P Trans., etc. Enquiries invited for Specials, Prototypes for small production runs. Quotation by return.

RADIO COMPONENT SPECIALISTS
70 Briggscock Road, Thornton Heath, Surrey.
THO 2138. Hours: 9 a.m.-5 p.m., 1 p.m. Wed.
Terms C.W.O. or C.O.D. Post and Packing up to ½ lb. 9d., 1 lb. 1/3, 3 lb. 2/3, 5 lb. 2/9, 8 lb. 3/6.

Est. 1946

EXPRESS ELECTRONICS

FOR THE FOLLOWING BRAND NEW UNITS

AMPLIFIERS

TRIPLETONE HI-FI MAJOR	12 watt	£15.18.6
TRIPLETONE CONVERTIBLE	5 watt	£6.19.6
TRIPLETONE GEMINI STEREO	5 watt	£15.15.0
LINEAR	3 watt	£6. 6.0
LINEAR DIATONIC	12 watt	£12.12.0
LINEAR CONCHORD	30 watt	£16.16.0
ADAstra 3-3	4 watt	£4.19.6
LEAK TL12	14 watt	£18.18.0
LEAK VARISLOPE PRE-AMP	---	£15.15.0
LEAK TL50	50 watt	£33.12.0
QUAD	15 watt	£22. 1.0
QUAD STEREO/MONO PRE-AMP	---	£25. 0.0

LOUDSPEAKERS

GOODMANS AXIETTE 8in.	6 watt	£5. 5.0
GOODMANS AXIOM 10in.	10 watt	£6. 6.0
GOODMANS AXIOM 20i	15 watt	£10.15.0

BAKERS 'SELHURST' 3 or 15 ohm

JUNIOR 8in.	8 watt foam	£5. 5.0
STALWART 12in.	15 watt	£5. 5.0
BASS GUITAR 12in.	25 watt	£5. 5.0
STANDARD Heavy Duty 12in.	20 watt	£7. 7.0
BASS Heavy Duty 12in.	25 watt	£12.12.0
AUDITORIUM 15in.	35 watt	£18.18.0

RECORD PLAYERS

GARRARD SRP10 4-speed	---	£4.17.5
GARRARD AUTOSLIM 4-speed	---	£6. 7.6
GARRARD AT6 TRANSCRIPTION	---	£9.17.6
GARRARD 4HF TRANSCRIPTION	---	£14.17.6
GARRARD 4 LAB SERIES	---	£17.10.0
GARRARD 301 LAB SERIES	---	£19. 5.0
DECCADEC WITH DERAM HEAD	---	£14.15.0

DELIVERED FREE U.K.

S.A.E. WITH ALL ENQUIRIES

EXPRESS ELECTRONICS

32 SOUTH END, CROYDON, SURREY

Telephone: Croydon 9186

ONE YEAR GUARANTEED TUBES



100% REGUNNED

21 in.	99/6
17 in.	79/6
15,14	59/6
12 in.	

Add 10/- or Old Tube. All 110°, 99/6 plus 30/- refundable on Old Tube. Carr. 10/6.

EX-MAINTENANCE TESTED TUBES

17in.—35/- Most makes and types available. 14in.—15/- Guaranteed good picture. Carriage 5/- extra.

EX-RENTAL TELEVISIONS

14 in.
£7.10.0

17 in.
£11.10.0



Coloured FREE LIST
Demonstration daily from our large selection

12 months written guarantee
Channels for all areas.

Personal collection advised, or insured Carr., 14in. 20/-; 17in. 30/-

AERIALS, BBC/ITA combined Loft and room aerials—from 95/-
BBC/UHF and colour aerials—from 29/6. SEND FOR FREE LIST.

TELEPHONE HANDSETS

15/6 pair

G.P.O. pattern House to Workshop, garage, inter-office, etc. Works off any small battery. P. & P. 4/6.

CONDENSERS, 100—10/-. New Amortised electrolytics and pfs. P. & P. 2/6.

SPEAKERS 12/8. Braund new, 7 x 4in. and 8 x 3in. P. & P. 2/8.

SPEAKERS 7/6. 6in., 8in., 7 x 4in. and 8 x 3in. Ex. Mid. Salvage. P. & P. 2/8.

VALVES 9d. each. 1,000's available. Bend for List.

V/CONTROLS, 20—10/-. A selection of types and sizes. P. & P. 2/6.

DUKE & Co. (LONDON) Ltd.
621/3 Romford Road, Manor Park, E.12
Liverpool St.—Manor Pk.—10 mins.

Phone: ILFord 6001/2/3 Stamp for Fee List

THE THINKING MACHINE

We are told that the electronic thinking machine may very well become a reality in twenty or thirty years time... Ultimately, we will be able to leave most of the important business and government decisions to the impartial machine!

This could result in some very interesting possibilities!

But, how about the immediate future? Are you prepared for the electronic age that is now with us? Or more vitally still—are you ready to face the age of automation!

Most readers of this message have already thought about this important topic and realise that the major impact of the electronic age is yet to be felt!

As each day passes, more and more semi-skilled jobs are disappearing. As each day passes, more machines are controlling electronically... Yet the electronic technician and engineer are becoming more in demand.

Are you considering electronics seriously? Would you like to try a short course that will prove to you whether you should make electronics your future work? We offer a short course that will get you started the right way... Completion of the course will give you assurance that you should take more advanced study with one of the very fine schools we have in this country... But it is essential to start somewhere, so why not start with Sim-Tech and prove to yourself that you have what it takes to learn electronics easily—the cost is very modest—the course excellent—the lessons crystal clear, practical, easy to master and use. Early lessons make fundamentals clear even to the beginner, while other lessons will give you the practical knowledge of an expert!

This is a real home study course of 38 lessons that has been bound into one giant eight by eleven inch, 216 page manual. Each page is divided into two columns. A wide column features the text, while a narrow column at the side has the instructor's comments, helpful suggestions and additional pictures to simplify the more difficult parts.

Everyone can benefit from this practical course, including those who's main interest may be nothing more than a desire to have a clearer appreciation of electronics as it relates to their present work or hobby.

In addition to the course, Sim-Tech offer the opportunity to take an examination in radio and electronics to those who have studied the electronics course and feel that they have attained a sufficiently high standard of proficiency. There is an additional fee of one guinea for the examination. (Which is entirely optional.) Further details are given with each course ordered.

Sounds good doesn't it, but how can you be sure that you are not wasting your money? Well, we will send you this course, on the understanding that you must be convinced this is the best value you have ever seen in electronic training, otherwise you may return the course (or have your money refunded if sent with order) after you have examined it in your own home for a full seven days.

The price? Only 39/6d plus postage 1/6d. Terms? Why, of course! See coupon. Open to all permanent residents of the U.K. excluding Ireland.

SPECIAL! SEND CASH WITH ORDER AND WE WILL INCLUDE A FREE 70 PAGE BOOK ON THE OSCILLOSCOPE OR RADIO FAULT FINDING.

These books are regularly sold at 5/- each and are loaded with useful information. By sending cash you reduce bookkeeping and other costs, which savings we are able to pass back to you.

FREE TRIAL OFFER!

To: Sim-Tech Book Company, Dept. XT1., Gater's Mill, West End, Southampton, Hants.

Please send your **ELECTRONICS AND RADIO COURSE** for a full seven days' trial. If not delighted, I may return the course post paid without further obligation on my part. Otherwise I will pay cash price. OR 10/9 fortnightly until purchase price of 41/- plus 2/- service charge has been paid.

- Tick here if enclosing full purchase price.
- Please send me **FREE. RADIO FAULT FINDING BOOK.**
- FREE. OSCILLOSCOPE BOOK.**

Amount enclosed £.....
I understand that you will refund this money in full if I am not 100% satisfied. Overseas customers please send full amount (including Ireland).

NAME

ADDRESS

.....

City..... County.....

PRACTICAL WIRELESS

blueprints

MOST of these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, constructional details are available free with each blueprint except for those marked thus (*).

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, London W.C.2.

DOUBLE-SIDED BLUEPRINTS

The Strand Amplifier	*	5/-
The PW Signal Generator		
The Savoy VHF Tuner	*	5/-
The Mayfair Pre-amplifier		
The Berkeley Loudspeaker Enclosure	*	5/-
The Luxembourg Tuner		
The PW Troubadour		7/6
The PW Everest Tuner		
The PW Britannic Two	*	6/-
The PW Mercury Six		
The PW Regency	*	5/-
The PW International Short Wave Two		
Beginner's Short Wave Two	*	5/-
S.W. Listener's Guide		
Beginner's 10-watt Transmitter	*	5/-
Transmitting and Aerial Data...		
P.W. "Sixteen" Multirange Meter	*	5/-
Test Meter Applications Chart		
The Celeste 7-transistor Portable Radio	*	5/-
The Spinette Record Player		
The P.W. 35-watt Guitar Amplifier	*	5/-
Transistor Radio Mains Unit	*	5/-
7 Mc/s Transceiver		

RECEIVERS

The Tutor *	3/-
The Citizen *	5/-
Dual-Wave Crystal Diode	PW95	2/6
Modern One-valver	PW96	2/6
All-dry Three	PW97	3/6
Modern Two-valver	PW98	3/6
A.C. Band-pass Three	PW99	4/-
A.C. Coronet-4	PW100	4/-
A.C./D.C. Coronet	PW101	4/-
The PW Pocket Superhet	5/-

MISCELLANEOUS

The PW 3-speed Autogram	8/-
The PW Monophonic Electric Organ	8/-
The PT Band III TV converter	1/6
The Mini-amp *	5/-
The PT Olympic *	7/6
The PT Multimeter *	5/-

PLEASE NOTE that we can supply no blueprints other than those shown in the above list. Nor are we able to supply service sheets for commercial radio, TV or audio equipment.

QUERY SERVICE

The P.W. Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 6th MAY, 1965 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, MAY, 1965


ALL TRANSISTOR DESIGNS

FULL AFTERSALES SERVICE AND GUARANTEE

DETAILED
LEAFLET
OF ANY
MODEL ON
REQUEST

MONO or STEREO

10 WATTS and 20 WATTS

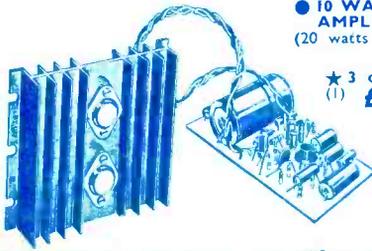

● 10 WATT POWER AMPLIFIER
(20 watts peak output)

★ 3 ohm Version (1) **£5.10.0** P.P. 2/6

★ 12.15 ohm Version (2) **£5.19.6**
P.P. 2/6

● MAINS UNITS 59/6 to power one amplifier, or 69/6 to power two (state 3 or 15 ohm Versions).

● MONO FULL FUNCTION PREAMPLIFIER (3)



1½mV Sensitivity with 8 input positions. Low noise, high quality and sensitivity. Gives 10 watts with one power amplifier or 20 watts with two amplifiers. Size 9 x 2½ x 2in.

PRICE **£5.10.0** P.P. 2/- (Dark brown with Gold front panel, 8/6).

(Also Multi-Input Preamp as previously advertised, 65/-, P.P. 1/6)

● STEREO PREAMPLIFIERS (5)



Two channel version of above for Mono/Stereo, to power two 10 watt amplifiers. Size 9 x 3½ x 1½in.

PRICE **£10.19.6**
P.P. 3/6.
(Front Panel 12/6).

● Above units are PRE-BUILT and TESTED. Items (3) or (4) can be used with one or two amplifiers—Items (1) or (2), with a mains unit. For Stereo Item (5) with two of (1) or (2) plus mains unit.

● VHF TRANSISTOR TUNER



★ PRE-ASSEMBLED UNITS
★ 6 TRANSISTORS
★ 88 to 108 Mc/s.
★ 100mV, 100k ohm output

TOTAL COST **£12.17.6**

Units available separately.

CALL FOR DEMONSTRATION

FOR ALL OUR TRANSISTORISED UNITS.

HENRY'S RADIO LTD.
303 EDWARERD., LONDON W2

PADdington 1008 9

Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday

90 Pages

Latest fully detailed and illustrated components and equipment catalogue.
Price **2/6** post paid.

LET US QUOTE FOR COMPONENTS FOR YOUR CIRCUIT

● PUSH-BUTTON PORTABLE SUPERHET RADIO to BUILD

- ★ 6 TRANSISTOR
- ★ PUSH-PULL OUTPUT UP TO 1 WATT
- ★ PRINTED CIRCUIT
- ★ MW/LW TUNING
- ★ SIZE 10 x 7 x 3½in.
- ★ ALL PARTS AVAILABLE SEPARATELY
- ★ EASY TO BUILD



Total Cost **£7.19.6** P.P. 3/6
to Build (Batteries 6/- extra)

● TWO WAVEBAND SUPERHET CAR RADIO

- ★ PRE-ASSEMBLED UNITS
- ★ 6 TRANSISTORS
- ★ PUSH-PULL OUTPUT
- ★ SIZE 7 x 4 x 2in.
- ★ FITS ANY CAR
- ★ UNITS SOLD SEPARATELY



Total Cost **£8.19.6** P.P. 3/6
to Build

7 x 4 inch SPEAKER and BAFFLE with Car Fixing Kit, 20/-, 3-section Chromed Car Aerial, 19/6.

● Also NEWMATIC 'ROUTEMASTER' MW/LW CAR RADIO with 3 watts output. Built, tested, ready to use, with Speaker, etc, £12.19.6.

● TWO WAVEBAND POCKET SUPERHET RADIO to Build

- ★ 6 TRANSISTORS
- ★ MW/LW TUNING
- ★ PRINTED CIRCUIT
- ★ SPEAKER PUSH-PULL OUTPUT
- ★ CABINET SIZE 5 x 3 x 1½in.
- ★ ALL PARTS SOLD SEPARATELY



Total Cost **85/-** P.P. 2/-
to Build (Battery 2/6, Phone 5/-)

● VHF FM TUNER to BUILD

- ★ FULL TUNING 87/105 Mc/s
- ★ 5 TRANSISTOR, 4 DIODES
- ★ AVC, AFC
- ★ OUTPUT UP TO 1 VOLT
- ★ 9 VOLT, 9mA.
- ★ CABINET SIZE, 3½ x 2½ x 4in.
- ★ ALL PARTS SOLD SEPARATELY



Total Cost **£6.19.6** P.P. 2/6
to Build (Complete with front panel)
CABINET ASSEMBLY 20/- EXTRA

● 4 watt and 1½ watt Package AMPLIFIERS

- ★ 6-TRANSISTOR DESIGNS, output to 3 ohm SPEAKER, 6mV into 1k ohm. 1½ watt 9 to 12 volts. 4 watt 12.18 volts. SIZES: 2½ x 2 x 1½in.

4-watt **79/6** P.P. 1/6
Built

1½ watt **65/-** P.P. 1/6
Built

