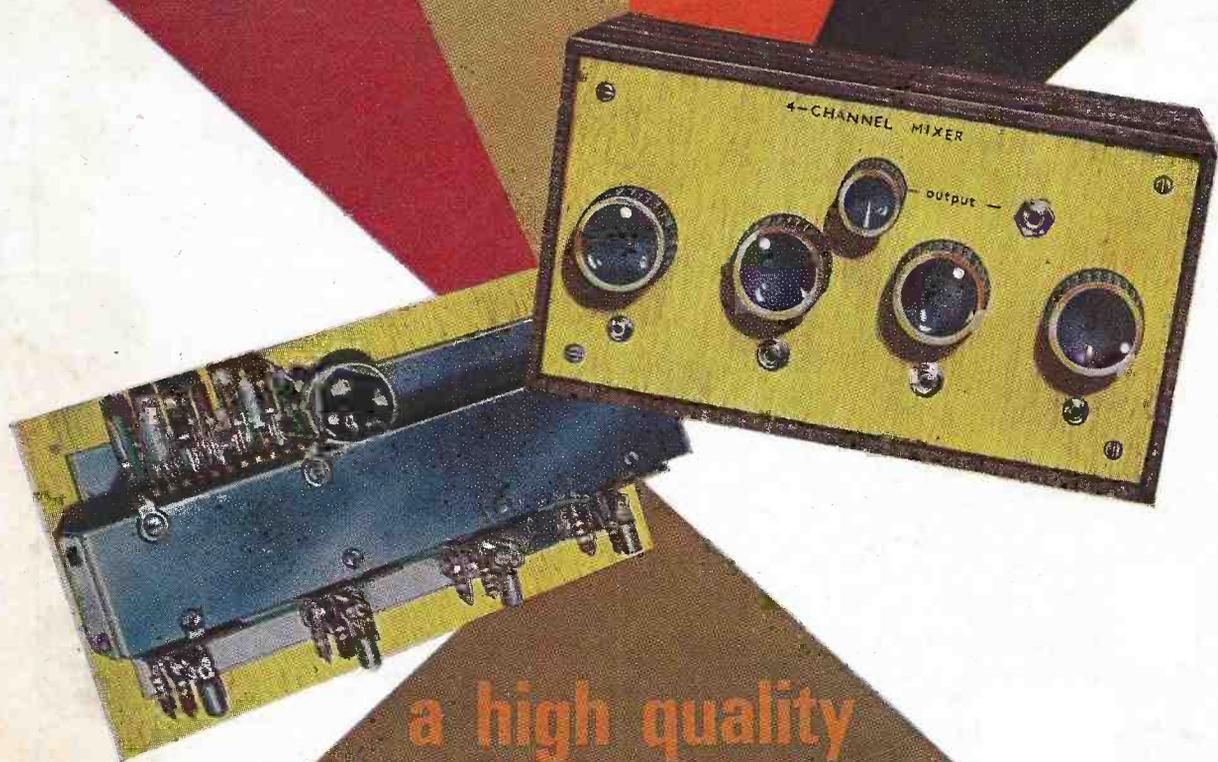


PRACTICAL WIRELESS

SEPTEMBER
1966


216



a high quality
FOUR-CHANNEL
AUDIO MIXER

SOLDERING EQUIPMENT

FOR
THE
RADIO
CONSTRUCTOR

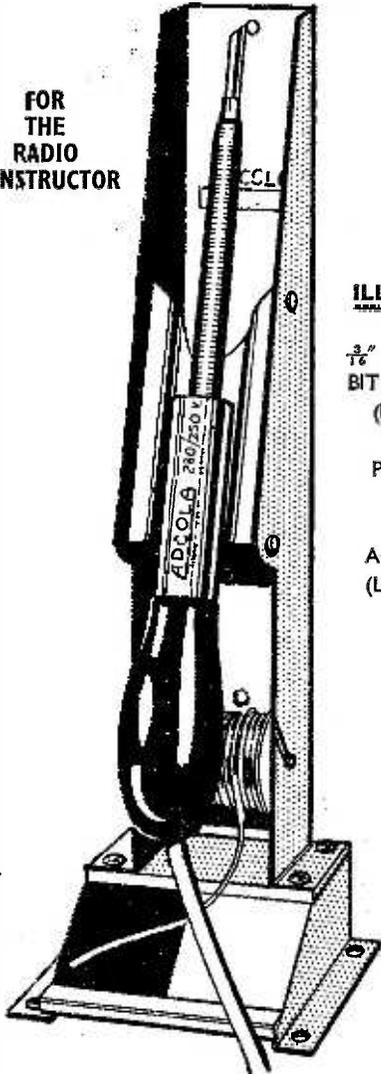

ILLUSTRATED

$\frac{3}{16}$ " DETACHABLE
BIT INSTRUMENT
(List No. 64)
IN
PROTECTIVE
SHIELD
WITH
ACCESSORIES
(List No. 700)


FOR CATALOGUES APPLY DIRECT

**ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4**

Telephones:
MACaulay 0291/3

Telegrams: "SOLJOINT" LONDON SW4

NOMBREX INSTRUMENTATION

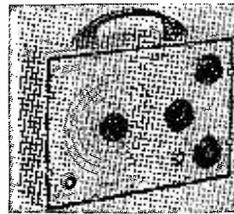

**WIDE RANGE
TRANSISTORISED
SIGNAL GENERATOR
MODEL 27**

- ★ Range 150Kc/s-350Mc/s
- ★ Direct Calibration
- ★ Mod. or Unmod. output
- ★ Accuracy better than 2%
£10.16.9.

ALSO AVAILABLE

Audio Generator 63	..	£17.1.9
Inductance Bridge 66	..	£18.6.9
Power Supply Unit 61	..	£6.14.6

WIDE RANGE TRANSISTORISED C.R. BRIDGE—Model 62

6 Ranges: 1Ω to 100M
1pF to 100μF

- ★ Visual null indicator
- ★ Power factor check
- ★ Electrolytic leakage test
- ★ Battery operated
£9. 6. 9.



All prices include battery, post and packing

S.A.E. for
Leaflet

Trade & Export
Enquires Invited

Prompt
Delivery

NOMBREX LTD INSTRUMENTS DIVISION

Estuary House, Camperdown Ter., Exmouth, Devon



**For quick, easy
faultless
soldering**

Ersin Multicore 5-core solder is easy to use and economical. It contains 5 cores of non-corrosive flux, cleaning instantly heavily oxidised surfaces. No extra flux is required. Ersin Multicore Savbit Alloy considerably reduces the wear of copper soldering iron bits.



HANDY SOLDER DISPENSER

12 ft. of 18 s.w.g.
SAVBIT alloy in a
continuous coil, used
direct from free-
standing dispenser.
2/6 each



LOW TEMPERATURE SOLDER

Size 9 pack contains
24 ft. of 60/40 high
tin quality 22 s.w.g.
2/6 each
Size 10 pack 212 ft.
15/- each.



SAVBIT

SIZE 1 CARTON
Contains approx. 30ft.
of 18 s.w.g. SAVBIT
alloy. Also available
in 14 and 16 s.w.g.
5/- each



BIB WIRE STRIPPER AND CUTTER

Strips insulation,
cuts wire cleanly.
Adjusts to any size.
4/- each

Available from all Electrical and Hardware shops.
If unobtainable write to:

MULTICORE SOLDERS LTD.

Multicore Works, Hemel Hempstead, Herts. Hemel Hempstead 3636
M-4/B


VALUE IN VALVES GUARANTEED 3 MONTHS BY RETURN OF POST

Satisfaction or Money Back Guarantee on goods if returned unused within 14 days. ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED. FREE TRANSIT INSURANCE. POSTAGE £1 valve 9d., 2-11 6d. per valve. Free over 12.

1L4	2/3	6L8G	7/-	80F5	8/3	E0F80	7/6	KT61	11/-	TDD4	7/-
1R5	4/9	6L18	7/9	80FL1	9/9	E0F82	7/6	KT63	5/9	U18	7/6
1S4	4/9	6LD20	8/6	80FL5	9/6	E0H21	10/-	KT66	14/-	U22	6/6
1S5	4/9	6P25	11/-	80P4	9/6	E0H35	11/-	KT88	21/-	U25	6/6
1T4	3/-	6P26	8/6	80P12	9/6	E0H39	8/6	KTW81	5/9	U26	8/9
2D21	9/8	6Q7G	5/8	80PL1	9/3	E0H31	9/8	KTW63	5/-	U35	12/6
3A5	6/-	6Q7GT	8/9	85E5	3/8	E0H83	7/8	KTZ63	7/-	U37	11/-
3Q4	5/8	6SL7GT	5/8	85L6GT	8/-	E0L80	5/9	MU14	7/-	U107	12/6
3U4	4/8	6SN7GT	4/8	85W4	6/-	E0L82	7/6	N37	9/8	U191	9/6
5Y3GT	4/9	6U4GT	9/8	85Z4GT	8/6	E0L83	9/8	N73	13/-	U281	8/6
5Z4G	6/9	6V6G	4/8	86L6GT	5/6	E0L86	9/8	N108	13/-	U282	15/-
6Z4GT	9/8	6V6GT	5/9	80	6/-	E0E36	3/3	PC06	10/-	U329	8/6
6/30L2	9/8	6X4	4/8	185BTA19	6/-	E0E39	5/-	PC07	7/6	U301	13/-
6A8G	7/9	6X5G	5/-	807	8/-	E0F40	10/-	PC094	6/6	UA B080	6/6
6AK5	4/9	6X5GT	6/-	955	2/6	E0F41	8/-	PC085	7/6	UAF42	7/9
6AQ5	9/-	7B6	9/6	956	2/6	E0F50	3/2	PC088	11/9	UB41	6/6
6AT6	5/-	7B7	6/8	AZ31	7/9	E0F80	4/3	PC089	9/9	UBC41	7/6
6B48	5/8	7C7	7/9	CE31	13/-	E0F85	6/-	PC189	11/-	UBC81	6/6
6BE6	5/8	7C6	6/9	CL33	8/-	E0F89	7/6	PCF80	6/3	UBF80	7/6
6EH6	5/-	7H7	5/-	CY31	7/6	E0F89	6/6	PCF82	6/-	UBF89	7/6
6E16	5/-	7H7	14/6	DAF96	7/3	E0F91	3/-	PCF86	8/3	UBL31	9/9
6BR7	7/8	7Y4	5/-	DF92	3/-	E0F92	3/-	PC182	7/9	UC02	6/3
6B16	5/-	10C1	11/-	DF96	7/3	E0F83	8/-	PC183	8/9	UC05	7/3
6C4	2/3	10C2	12/8	DL92	7/-	E0F134	8/-	PC184	8/3	UCF50	8/6
6C5	5/6	10L1D11	14/8	DL82	5/-	E0L32	8/9	PC185	8/6	UCB21	9/3
6C6	4/-	10P13	8/6	DL94	6/6	E0L34	11/-	PL33	8/6	UC42	8/6
6C9	11/-	10P14	9/8	DL86	7/3	E0L35	6/-	PL36	8/9	UCB31	7/-
6GD6G	17/-	12A7	4/9	EABCS0	6/6	E0L38	15/-	PL33	12/6	UCL82	8/-
6D6	3/-	12A7G	4/9	EAF42	7/6	E0L41	8/6	PL81	7/9	UCL83	10/-
6F1	6/6	12AX7	6/-	E041	4/-	E0L42	8/6	PL82	5/9	UF42	6/9
6F6G	4/-	12B7GT	4/8	E0C33	6/-	E0L43	6/6	PL83	6/-	UF85	7/6
6F18	4/8	12K7GT	4/8	E0C33	6/-	E080	7/6	PL84	7/-	UF89	5/9
6F14	5/-	12K8GT	9/6	E0C41	6/6	E0M31	7/3	PY31	7/6	UL41	8/9
6F15	8/8	12Q7GT	5/-	E0C51	6/6	EM84	7/9	PY32	9/-	UL44	14/-
6F23	8/6	1487	14/6	E0F80	7/6	EY51	7/3	PY33	9/-	UL46	8/3
6J5G	3/-	19A45	5/-	E0F89	7/6	EY86	7/3	PY80	5/9	UL46	8/3
6J5GT	4/8	20P1	8/9	E0C41	6/6	EY81	5/6	PY31	5/9	UL84	6/9
6J6	3/3	20P2	9/8	E0C40	6/9	EZ40	6/6	PY82	5/8	UM80	9/6
6J7G	4/9	20L1	16/-	E0C81	4/9	EZ41	6/6	PY83	5/9	UY21	8/9
6J7GT	7/9	20P1	9/6	E0C82	4/9	EZ80	5/6	PY88	8/6	UY41	6/-
6K7G	1/6	20P8	9/6	E0C83	5/9	EZ81	6/6	PY80	6/6	UY85	5/6
6K7GT	4/9	20P8	9/6	E0C84	7/-	F04	8/-	PZ30	9/-	VK105	5/-
6K9G	3/-	25L6GT	7/9	E0C85	6/6	GZ32	8/6	SP61	2/6	VL150	5/-
6K9GT	8/-	85Z4G	6/6	E0C88	8/-	GZ34	10/6	T41	6/9	X66	7/9

Transistorised FM Tuner

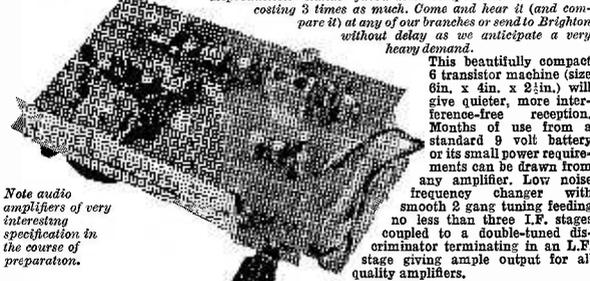HIGH QUALITY: LOW NOISE: BATTERY OR MAINS OPERATION



Note audio amplifiers of very interesting specification in the course of preparation.

15 WATT TUNER AMPLIFIER KIT consisting of FM41 tuner and the excellent Sinclair Z18 (built) together with complete integrated control kit consisting complete vol. on/off, treble and bass, component sets with complete connecting instructions and circuits.

£13.19.0 or complete with AC mains power pack £17.18.6. Complete control kit only with circuits 25/-.

avoid disappointment
ORDER NOW £8-10

100 HI-STABS 1% to 5% 9/6
100 Ω to 5m Ω
CO-AX, low loss, 6d. yd., 25 yds. 11/6;
50 yds. 22/-; 100 yds. 42/6. Plugs, 1/3.

100 RESISTORS SIZES 1/2-3 watt 6/6
MICROPHONE CABLE. Highest quality black, grey, white, 9d. per yard.

100 CONDENSERS 9/6
Miniature Ceramic, Silver Mica, etc.
3pF to 1μF. LIST VALUE OVER £5.

BARGAIN 71b. PARCELS
Including variable condensers, I.F. coils, loudspeaker plugs/sockets, knobs, pots, condensers, resistors, nuts, bolts, cabinet fittings, switches, transformer choke, rectifier, transistors. List value over £6. Carr. 5/-. Try me! 17/6

DUNCI (VHF) FM TUNERS
Model FMT/5. Self powered 200/250 v. A.C. A.F.C. High sensitivity for fringe and long distance reception. Size 1 1/2" x 3 1/2" x 3 1/2" high. Weight 7 1/2 lb. in case finished in satin chrome and black. We can offer these high fidelity instruments. Normally £21.13.5. 15 Gns. Limited number only at

LOUDSPEAKERS. 3 Ω Top Makes. 5in. 7 x 4in. 8/6

HITACHI PORTABLE TAPE RECORDER

STOCKS GOING FAST! Latest Hitachi. Fabulous quality reproduction of music, 6-transistor, 1 1/2in. and 3 1/2in. speeds. Output 500 mW high quality speaker. Fast forward and rewind. Battery level and record level meter. Precision cassette drive. Size 8 1/2" x 3 1/2" x 6 1/2". Genuine normal price of 35 gns. Unrepeatable. All spares available. With tape, 19 Gns. tape reel, mike, etc.

GAR RADIOS
Latest Autolux fully transistorised complete with speaker and fittings. Large purchase enables us to sell these superb sets (normally approx. 14 gns.) at the amazing price of 8 Gns.

RADIOGRAM CHASSIS QUALITY BARGAINS
Heavy duty A.C. mains, complete with large dials.
Stereo AM, 6 valve, all wave (normally 17 gns.) 11 Gns.
Mono AM/FM, 6 valve (normally 15 gns.) 12 Gns.
Stereo AM/FM, 7 valve (normally 23 gns.) 17 Gns.

HALF PRICE STEREOGRAMS

Large purchase well known portable Record Players with ingenious Split Cabinet giving two separate high quality loudspeakers, plus main unit with Garrard Deck and crystal clear amplifiers. Compact, powerful, amazing value. Autochanger Model complete Diamond Cartridge normally 38 gns., 19 gns. Non-Autochange model with SRP2 Deck, normally 29 gns., 14 gns. S.A.E. Full description.

ENORMOUS PURCHASE GUARANTEED APPROX. HALF PRICE. WORLD FAMOUS MAKE

★ TAPE ★
We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-hi wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF.

Standard Play		Double Play	
3in. 150ft. 2/3	3in. 300ft. 4/-	4in. 300ft. 4/6	4in. 600ft. 8/6
5in. 600ft. 7/6	5in. 1,200ft. 15/-	5in. 900ft. 10/6	5in. 1,800ft. 19/6
7in. 1,200ft. 12/6	7in. 2,400ft. 27/-	Long Play	
3in. 225ft. 2/9	4in. 900ft. 13/-	Triple Play	
4in. 450ft. 5/6	5in. 1,800ft. 25/-	Quadruple Play	
5in. 900ft. 10/6	5 1/2in. 2,400ft. 34/-	3ft. 600ft. 3/-	
5 1/2in. 1,200ft. 13/-	7in. 3,000ft. 44/-	Post Free less 5% on three reels.	
7in. 1,800ft. 18/6		Quantity and Trade enquiries invited.	

ELPIGO MONO PREAMPS
DPA15. Latest black/satin chrome finish multiple input channels selector, bass and treble controls. Matches all pick-ups and mikes. Provision tape recording. Normally 10 gns. our price 5 Gns.

TRANSISTORS
GUARANTEED TOP QUALITY
Millard Matched Output
Kits OC81D and 2-OC81 9/6
R.F. Kits OC44, OC45 (2) 9/6
3 transistors

GERMANIUM DIODES
General Purpose miniature detector A.V.C. etc. 6/6 doz. 8d.
Gold Bonded highest quality Individually tested 9/6 doz. 1/-

SILICON RECTIFIERS
Guaranteed performance. Top makes. Tested 250v. working.
120 ma. 500 ma.
(3 for 6/6) 2/9 (3 for 1C/6) 7/6

LATEST GARRARD

Stereo cartridge fitted for 17/6 extra.
SRP12 Mono (Single) Player £4.19.0
SP25 Semi-Transcription £11.19.0
AUTOSLIM Standard Auto. £5.19.0
AT5 Slimline—similar to AT6 £7.15.0
Model 1,000—10 records £6.19.0
Model 2,000—larger turntable £7.19.0
Model 3,000—wear £10.10.0
AT60—Heavy Automatic £11.19.0
AT70—Automatic £15.19.0
LAB80—Transcription Auto. £27.10.0
401—Transcription £29.19.0
Model 50—Automatic £8.10.0

All Factory Fresh. All with cartridge.
B.S.R.
TU14—Single player Complete 59/-
GU17—Single Deck Complete £4.5.0
UA14—Auto Changer £4.17.6
UA16—Blue-silver £5.10.0
UA25SS—Super Slim £5.15.0

TUBES SATISFACTION GUARANTEED

Garr. & Ins. 12/6	6 Months	12 Months	NEW TYPES
MOST MULLARD.	12in. £2. 0.0	£3. 0.0	AW47-91
MAZDA. COSSOR.	14in. £2.10.0	£4. 10.0	£5. 15.0
EMITRON. EMI-SOFT.	15-17in. £3. 5.0	£4. 5.0	AW55-91
SCOTT. BRIMAR.	19in. £3. 5.0	£4. 5.0	£7. 10.0
FERRANTI TYPES PROCESSED IN OUR OWN FACTORY	21in. £3.15.0	£4. 15.0	AW48-80
	23in. £3.15.0	£5. 15.0	£5. 5.0

Satisfaction Guaranteed or money refunded if returned unsoiled within 14 days

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone, Linear, Rogers Truwoz, Ferragraph, Warrisdale, etc., etc.

TECHNICAL TRADING

Post: 11b. 1/6, 1 1/2b. 2/6, 21b. 2/9, 41b. 3/3, 61b. 4/-, 141b. 5/6

All Mail Orders:—DEPT. E7, Devonian Court

★ BRIGHTON Park Crescent Place, Tel. 680722

★ LONDON 10 Tottenham Court Road. Tel. MU5EUM 2639.

★ PORTSMOUTH 350-352 Fratton Road, Tel. 22034.

★ SOUTHAMPTON 72 East Street, Tel. 25851.

All Branches—E.C. Weds.

Fully guaranteed Individually packed VALVES

AC/HL 4/8	DK92 8/-	EP40 8/-
AC/PA 6/-	DK96 6/8	EP50 2/8
AC/PPEN 5/-	DL92 4/8	EP52 4/8
AL60 5/-	DL92 4/8	EP81 6/8
ARP3 3/-	DL94 5/8	EP85 5/8
ARP12 2/6	DL96 7/-	EP71 7/8
ARP24 3/6	DL810 8/-	EP72 5/8
AR8 5/-	DY86 7/8	EP73 5/8
ARTP1 6/-	EP50F 23/-	EP74 4/8
ATP4 2/3	ES80C 12/-	EP80 5/8
ATP7 5/8	EL148 2/8	EP85 4/8
AU7 55/-	EL148 2/8	EP85 4/8
AZ31 9/-	EL266 50/-	EP86 6/8
B6H 15/-	EL145 30/-	EP89 5/8
BD78 40/-	EL124 12/8	EP91 3/8
BL68 10/-	EL30 1/-	EP92 2/8
BS4 8/-	EL73 7/-	EP93 2/8
BS5 20/-	EABCS0 5/8	EP183 3/8
BSS4 37/6	EA91 3/8	EP184 3/8
BZ134 16/-	EAF42 3/8	EIM90 7/8
BT19 35/-	EB34 1/8	EM17 800/-
BT35 25/-	EB31 3/8	EL32 3/8
BT45 150/-	EB23 6/-	EL34 10/-
BT85 35/-	EB34 1/8	EL36 5/8
CC8L 2/-	EB31 3/8	EL38 17/8
CF23 10/6	EBF80 6/8	EL41 8/-
CL38 9/-	EBF88 7/8	EL42 8/-
CV71 3/8	EC91 3/8	EL50 8/8
CV77 5/-	EBL81 20/-	EL81 8/-
CV102 1/-	EC52 4/-	EL84 5/8
CV103 4/1	EC53 12/8	EL86 5/8
CV4004 7/-	EC70 4/8	EL91 4/8
CV4014 7/-	EC90 2/-	EL95 5/8
CV4015 5/-	EC91 3/8	EL96 5/8
CV4025 10/-	EC081 4/8	EL360 20/-
CV4049 6/-	EC082 5/-	EM80 9/-
CY31 6/8	EC083 6/-	EM81 7/8
D1 1/8	EC084 5/8	EM84 6/8
D41 6/-	EC085 6/8	EM81 10/-
D61 6/-	EC088 5/-	ESU74 80/-
D77 3/3	EC091 4/1	ESU208 6/-
DAB3 12/6	EC0180 9/6	EY51 5/8
DAF96 6/1	ECF82 7/-	EY86 6/8
DD41 4/-	ECF82 7/-	EY91 3/8
DEFS 3/8	ECF83 7/-	EZ40 6/8
DET20 2/8	ECF88 7/8	EZ41 6/8
DET25 15/-	ECL80 6/-	EZ80 5/8
DEFT3 5/-	ECL82 7/6	EZ81 4/8
DF91 3/8	ECL83 10/-	F/0087 5/-
DF92 3/8	ECL85 6/-	F/0061 5/-
DF96 6/8	EP362 3/8	PC186 3/8
DE63 6/-	EP37A 7/-	FW4/500 6/8

PEN46 3/-	TTR31 45/-	Y63 5/-	5R4GY 9/-
PEN200A3/-	TZ020 4/-	Y65 4/-	5T4 7/-
PFL200 17/6	TZ20 16/-	Y66 8/-	5U4G 4/6
PL36 9/-	U1 18/-	Z80T 20/-	5Y4G 8/8
G50/2G 5/-	PL38 18/-	Z80IU 10/-	5X4G 8/8
PL180/2M15/-	PLS1 7/-	U17 5/-	5Y3G 4/6
GM4 45/-	PLS2 6/8	U18 6/-	5Y3GT 5/-
GZ22 10/-	PLS3 6/8	U19 11/-	5Y3WGTB 6/-
GZ24 10/-	PLS4 6/8	U26 11/-	1C5GT 6/-
HL34 25/8	PL50 15/-	U27 6/-	5Z4G 9/-
HL2K 9/8	PM24A 5/-	U60 4/8	1B7G 7/6
HL23 6/-	PT15 10/-	U92 4/6	1P2 3/-
HL23DD 5/-	PT25H 7/6	U191 11/8	1G6GT 6/-
HL41 4/-	PT25M 7/6	U801 17/-	1L4 2/6
HYR2 9/8	PX4 14/-	UABCS0 6/8	1L6A 6/8
K3A 60/-	PX25 9/8	UAF42 9/-	1L6C 7/8
PY33 6/8	PY33 6/8	UCB41 6/8	1L6E 4/8
PX80 5/8	PY80 5/8	UBF89 5/8	1N21B 4/8
PY81 5/8	PY81 5/8	UBF89 6/8	1N43 4/8
PT35H 7/6	U191 11/8	1G6GT 6/-	1N70 4/8
PT25M 7/6	U801 17/-	1L4 2/6	1R4 5/8
PX4 14/-	UABCS0 6/8	1L6A 6/8	1R4 5/8
PX25 9/8	UAF42 9/-	1L6C 7/8	1R4 5/8
PY33 6/8	UCB41 6/8	1L6E 4/8	1R4 5/8
PY80 5/8	UBF89 5/8	1N21B 4/8	1R4 5/8
PY81 5/8	UBF89 6/8	1N43 4/8	1R4 5/8
PT35H 7/6	U191 11/8	1G6GT 6/-	1R4 5/8
PT25M 7/6	U801 17/-	1L4 2/6	1R4 5/8
PX4 14/-	UABCS0 6/8	1L6A 6/8	1R4 5/8
PX25 9/8	UAF42 9/-	1L6C 7/8	1R4 5/8
PY33 6/8	UCB41 6/8	1L6E 4/8	1R4 5/8
PY80 5/8	UBF89 5/8	1N21B 4/8	1R4 5/8
PY81 5/8	UBF89 6/8	1N43 4/8	1R4 5/8
PT35H 7/6	U191 11/8	1G6GT 6/-	1R4 5/8
PT25M 7/6	U801 17/-	1L4 2/6	1R4 5/8
PX4 14/-	UABCS0 6/8	1L6A 6/8	1R4 5/8
PX25 9/8	UAF42 9/-	1L6C 7/8	1R4 5/8
PY33 6/8	UCB41 6/8	1L6E 4/8	1R4 5/8
PY80 5/8	UBF89 5/8	1N21B 4/8	1R4 5/8
PY81 5/8	UBF89 6/8	1N43 4/8	1R4 5/8
PT35H 7/6	U191 11/8	1G6GT 6/-	1R4 5/8
PT25M 7/6	U801 17/-	1L4 2/6	1R4 5/8
PX4 14/-	UABCS0 6/8	1L6A 6/8	1R4 5/8
PX25 9/8	UAF42 9/-	1L6C 7/8	1R4 5/8
PY33 6/8	UCB41 6/8	1L6E 4/8	1R4 5/8
PY80 5/8	UBF89 5/8	1N21B 4/8	1R4 5/8
PY81 5/8	UBF89 6/8	1N43 4/8	1R4 5/8
PT35H 7/6	U191 11/8	1G6GT 6/-	1R4 5/8
PT25M 7/6	U801 17/-	1L4 2/6	1R4 5/8
PX4 14/-	UABCS0 6/8	1L6A 6/8	1R4 5/8
PX25 9/8	UAF42 9/-	1L6C 7/8	1R4 5/8
PY33 6/8	UCB41 6/8		

Why

NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS... FIRST FOR PERFORMANCE, QUALITY & PRICE!

BACKED BY OUR SUPER AFTER SALES SERVICE

"A wonderful range of transistor radios using first grade components for guaranteed results."



Parts Price List and easy build plans 3/- (Free with kit)

NEW ROAMER SEVEN Mk IV

Amazing performance and specification

★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS

FULLY TUNABLE ON ALL WAVEBANDS


● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned 7 x 4in. speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M. & L. Waves and telescopic aerial for S. Waves. Real leather-look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx.

The perfect portable and the ideal car radio. (Uses PP7 batteries, available anywhere.)

★ EXTRA BAND FOR EASIER TUNING OF PIRATE STATIONS, etc.

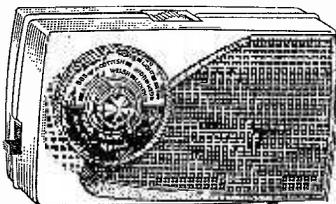Total cost of parts now only **£5.19.6** P. & P. 5/6



NEW MELODY MAKER SIX

3 WAVEBAND PORTABLE


● 8 stages—6 transistors and 2 diodes

Covers Medium and Long Waves and EXTRA BAND FOR EASIER TUNING OF PIRATE STATIONS, etc. Top quality 3in. Loudspeaker for quality output. Two RF stages for extra boost. High "Q" 6in. Ferrite Rod Aerial. Approx. 350 milliwatts push-pull output. Handsome pocket size case with gilt fittings. Size 6½ x 3½ x 1½in. (uses long-life PP6 battery). Carrying strap 1/6 extra.

This amazing receiver may be built for only

£3.9.6 P. & P. 3/6

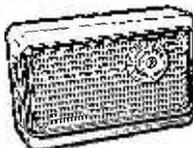Parts Price List and easy build plans 2/- (Free with kit).



NEW TRANSONA FIVE

"Home, Light, A.F.N., Lux. all at good volume."

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser volume control, new type fine tone super dynamic 2½in. speaker, etc. Attractive case. Size 6½ x 4½ x 1½in. with red speaker grille. (Uses 1289 battery, available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)

POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 2½in. moving coil speaker, built into attractive black and gold case. Size 6½ x 1½ x 3½in. (Uses 1289 battery available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/6

Parts Price List and easy build plans 1/6 (Free with kit)



STOP PRESS!
Pocket 5 med and Long wave version with miniature speaker.

29/6 P. & P. 3/-



NEW ROAMER SIX

NOW, WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND !!

● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long Waves, Trawler Band and two Short Waves. Sensitive Ferrite rod aerial and telescopic aerial for short waves. Top grade transistors. 3-inch speaker, handsome case with gilt fittings. Size 7½ x 5½ x 1½in. (Carrying strap 1/6 extra.)

★ EXTRA BAND FOR EASIER TUNING OF LUX., etc.

Total cost of all parts now only **£3.19.6** P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)


TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Push-pull output. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6½ x 4½ x 1½in. (Uses PP4 battery available anywhere.) Carrying Strap 1/- extra.

Total cost of all parts now only **59/6** P. & P. 3/6

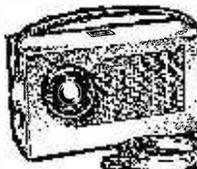Parts Price List and easy build plans 1/6. (Free with kit)



MELODY SIX

● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering Medium and Long Waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. Ferrite rod aerial. Push-pull output. Wonderful reception of BBC, Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6½ x 3½ x 1½in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

Total cost of all parts now only **£3.9.6** P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 RF Stages, push-pull output, 3in. speaker (will drive large speaker). Size 7½ x 5½ x 1½in. (Uses 9V battery, available anywhere.)

Total cost of all parts now only **£3.9.6** P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)

Callers side entrance
Barratts Shoe Shop.

RADIO EXCHANGE CO.

Open 9—5 p.m.
Saturdays 9—12.30 p.m.

61 HIGH STREET, BEDFORD Telephone: Bedford 52367

R.S.C.
(MANCHESTER) LTD.

MAIL ORDERS TO:
102 Henconner Lane
Bramley, Leeds 13

Terms: C.V.O. or C.O.D. No C.O.D. under £1. Postage 3/6 extra under £2. 5/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please. Personal shoppers welcome at our HI-FI CENTRES as below. Open all day Sats.

BRADFORD 10 North Parade. Tel. (Half-day Wed.) 25349

BRISTOL 14 Lower Castle St. Tel. (Half-day Wed) 22904

BIRMINGHAM 30/31 Gt. Western Arcade, opp. Snow Hill Station. CENTral 1279. No half-day

DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel.: 41361

DARLINGTON 13 Post House Wynd (Half-day Wednesday) Tel.: 68043

EDINBURGH 133 Leith Street (Half-day Wed.)

GLASGOW 326 Argyle St. Tel.: (No half-day) CITY 4158

HULL 51 Savile Street (Half-day Thursday) Tel.: 20505

LEICESTER 32 High Street (Half-day Thurs.) Tel.: 56420

LEEDS 5-7 County (Mecca) Arcade (No Half-day) Tel: 28252

LIVERPOOL 73 Dale St. (No half-day) Tel: CENTral 3573

238 Edgware Road, W2 (Half-day Thursday)

LONDON Tel.: PADdington 1629

96, High Holborn WC1 Opening Late August

MANCHESTER New large store. (No half-day)

60A-60B Oldham St. Tel.: CENTral 2778

MIDDLESBROUGH (Half-day Wednesday)

106 Newport Road. Tel.: 47096

NEWCASTLE Blackett Street New branch opens Mid-August

SHEFFIELD 13 Exchange Street Castle Market Bldgs. Tel.: 20716 (Half-day Thursday)

R.S.C. A15 15 WATT (R.M.S.) HI-FI TRANSISTOR AMPLIFIER with integral pre-amp tone control stages. Output for 3, 7.5 and 15 ohm speakers. Kit of parts consisting of Printed Circuit and all components for same including 9 Mullard or Newmarket Post latest semi-conductors. 5/ Heat sink and wiring instructions or with printed circuit fully wired and tested 30/- extra. Frequency Response: $\pm 1\text{dB}$ 20-20,000 c.p.s. Harmonic Distortion: 0.1% measured at 1000 c.p.s. Hum and Noise: -80dB . Sensitivity: 2mV. Bass Control: $+8\text{dB}$ to -14dB at 40 c.p.s. Treble Control: $+8\text{dB}$ to -13dB at 10 Kc/s. Suitable Power Pack Kit 39/6 or ready built 59/6.

ALL LEADING MAKES OF HI-FI EQUIPMENT STOCKED Cash or Terms

LONDON 96 HIGH HOLBORN OPEN LATE AUGUST

HI-FI LOUDSPEAKER ENCLOSURES

All types of pleasing modern "slimline" design acoustically lined and ported and in alternative finishes of Light Teak or medium Walnut.

SE8. For optimum performance with any Hi-Fi 8in. speaker. Size 22 x 15 x 7in. Carr. 7/6 **£5.15.0**

SE10. For 10in. Hi-Fi speaker with provision for tweeter. Size 24 x 15 x 7in. Or Deposit 21/- and 9 mthly pmts of 15/4 (Total £7.19.0) **£6.19.9**

SE12. For outstanding performance with any 12in. Hi-Fi speaker. Cut for tweeter. Size 24 x 20 x 7in. Or Deposit 27/- and 9 monthly payments of 18/2 (Total £9.10.6) Carr. 10/- **8 Gns.**

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser etc.) and Tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating. Or **£4.19.9**

Senior 20 watt inc. Pane 122/10 speaker £6.19.9. Carr. 5/6 7/6. Or Dep. 21/- and 9 mthly pmts of 15/4 (Tot. £7.19.0).

AUDIOTRINE HF100D 10in. 15W HI-FI Loudspeakers. Heavy cast construction. Dual cone. Smooth frequency response 20-20,000 c.p.s. Speech coil 3 or 15 ohms. Exceptional value. Carr. 5/9 **£5.15.0**

AUDIOTRINE HF12D 12 in. 20 w HI-FI SPEAKER Heavy cast chassis. Latest high efficiency ceramic magnet. Aluminium speech coil and Tweeter Cone for extended frequency range. Response 30-20,000 c.p.s. Impedance 15 ohms. Only **£6.15.0**

TWEETERS R.A. 3 ohm 25/9. 15 ohm 25/9

SPECIAL PURCHASE OF 15 in. 25 WATT 15 ohm BASS SPEAKERS Very limited number. Famous make. Fully Guaranteed. ONLY **£9.19.9**

R.S.C. GRAM AMPLIFIER KIT. 3 watts output. Negative feedback. Controls: Vol., Tone and Switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 44/9. Carr. 3/9.

R.S.C. STEREO 10/4 WATT (R.M.S.) HI-FI TRANSISTOR AMPLIFIER with integral pre-amp tone control stages. Output for 3, 7.5 and 15 ohm speakers. Kit of parts consisting of Printed Circuit and all components for same including 9 Mullard or Newmarket Post latest semi-conductors. 5/ Heat sink and wiring instructions or with printed circuit fully wired and tested 30/- extra. Frequency Response: $\pm 1\text{dB}$ 20-20,000 c.p.s. Harmonic Distortion: 0.1% measured at 1000 c.p.s. Hum and Noise: -80dB . Sensitivity: 2mV. Bass Control: $+8\text{dB}$ to -14dB at 40 c.p.s. Treble Control: $+8\text{dB}$ to -13dB at 10 Kc/s. Suitable Power Pack Kit 39/6 or ready built 59/6.

ALL LEADING MAKES OF HI-FI EQUIPMENT STOCKED Cash or Terms

HIGH FIDELITY LOUDSPEAKER UNITS

MINI-8, 8 watt, 9 ohms or 15 ohms incorporating specially designed highly efficient 5 in. speaker with low fundamental resonance and high flux density ceramic magnet. Frequency response 50-13,000 c.p.s. Handsome Teak veneered cabinet, size 10 $\frac{1}{2}$ x 6 $\frac{1}{2}$ x 7 $\frac{1}{2}$ ins. 6 Gns. Carr. 5/9.

AUDIOTRINE PETITE

Really astounding performance. Size only 10 $\frac{1}{2}$ x 6 $\frac{1}{2}$ x 7 $\frac{1}{2}$ in. Rating 10 watts. Frequency range 45-20,000 c.p.s. Cabinet beautifully finished in Teak (light) or Walnut (medium). Fitted with specially designed Heavy cast 5in. speaker with large pole pieces, extra large voice coil and rubber cone surround. Impedance 9 ohms or 15 ohms. 11 Gns. Or Deposit 36/- and 9 monthly payments of 25/- (Total £13.1.0). Carr. 7/6

THE GLOUCESTER

Handsome "slimline" cabinet, acoustically lined. Size 24 x 20 x 6 $\frac{1}{2}$ in. Finished light Teak or medium Walnut. 12in. high flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Smooth response 40-20,000 c.p.s. Impedance 15 ohms. Or Deposit 36/- and 11 Gns. 9 monthly payments 25/- (Total £13.1.0). Carr. 15/-

THE BRONTE

Handsome cabinet of modern styling. Acoustically lined and finished Teak or Walnut. Size 22 x 15 x 7 $\frac{1}{2}$ in. Fitted Wharfedale Super 8 RSD Speaker with Roll surround and dual cone. Rating 6 watts. Impedance 15 ohms. Or Deposit 39/- and 9 monthly payments 27/8 (Total £14.4.3). Carr. 15/- 12 Gns.

CORNER CONSOLE CABINETS

Strongly made. Beautiful polished walnut veneered finish. Pleasing design. Junior Model. For up to 8in. speaker. Approx. 2 $\frac{1}{2}$ x 49/9 11 x 8in. Carr. 7/6 5 Gns. Standard Model. To take up to 10in. speaker. Size 27 x 18 x 8in. Carr. 7/6 5 Gns. Senior Model. To take up to 12in. speaker and with Tweeter cut-out. Size approx. 30 x 30 x 15in. (Recommended for use with Audiotrine speaker system.) Terms available. Carr. 8/6 8 Gns.

LINEAR TAPE PRE-AMPLIFIER. Type LP1. Switched Equalisation. Positions for Recording at 1in., 3in., 7in. per sec. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and a Hi-Fi amplifier, suitable most Tape 10 $\frac{1}{2}$ Gns. Decks. Terms available.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a stereo amplifier giving 5 watts high quality output on each channel (Total 10 watts). Sensitivity is 50 millivolts. Suitable all crystal or ceramic stereo heads. Ganged Bass and Treble Control for equal variation of "lift" and "cut". Provision is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point to point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. Or supplied factory assembled with 12 months' guarantee for 11 gns. Terms: Dep. 36/- and 9 monthly payments 25/5 (Total £13.4.3). Carr. 11/6 **£8.15.0**

R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER

PROVIDING 10/4 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, R.D.M., ETC. Employing valves ECC83, ECC83, ECL86, ECL86, ECL86, ECL86, E281. Frequency Response: $\pm 2\text{dB}$ 30-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 5 millivolts maximum. Harmonic Distortion: (each channel): 0.2%. ★ Four-position tone compensation and Input Selector Switch. Output transformers are high-quality sectionally wound to required specification. Output matching for 15, 16, 18, 20 ohm speakers on each channel. Complete set of parts with point-to-point wiring diagrams and instructions. Carr. 12/6 14 Gns. Send s.a.e. for leaflet. Or factory assembled, tested and supplied with our usual 12 months guarantee. Or Deposit 23 and 9 monthly payments 43/2 (Total £22.4.6). Carr. 12/6 19 Gns.

R.S.C. SUPER 15 HI-FI AMPLIFIER APPEARANCE AND TECHNICAL SPECIFICATIONS COMPARE MORE THAN FAVOURABLY WITH SIMILAR AMPLIFIERS AT TWICE THE COST

FULLY TRANSISTORISED 200/250v. A.C. Mains. OUTPUT 10 WATTS R.M.S. cont. into 16 ohms. Maximum instantaneous Peak power output 28 watts. PRINTED CIRCUIT CONSTRUCTION. LATEST MULLARD TRANSISTORS. AD149, AD149, OC127Z, OC81Z, OC44, OC44, OC81Z, OC44, AC107. 5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: $\pm 2\text{dB}$ 20-20,000 c.p.s. TREBLE CONTROL: $+15\text{dB}$ to -14dB at 10 Kc/s. BASS CONTROL: $+12\text{dB}$ to -15dB at 20 c.p.s. HUM LEVEL: -75dB . HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.3%. NEGATIVE FEEDBACK: 52dB. Complete Kit of parts with full constructional details and 2 point to point wiring diagrams. Or ready for use 14 $\frac{1}{2}$ Gns. Attractive Walnut or Teak finished cabinet 5 gns. or Deposit 17/- and 9 monthly payments 11/3 (Total £5.18.3). Or unit factory built and tested, complete with cabinet and with our usual 12 months' guarantee. 15 $\frac{1}{2}$ Gns. Or Deposit £3.9.0 and 9 mthly pmts 40/6 (Total £21.13.6). Carr. 12/6.

R.S.C. SUPER 30 STEREO AMPLIFIER

A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits. Close tolerance Ganged Pots. Matched Components. CROSS-TALK: -52dB at 1,000 c.p.s. CONTROLS: 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch. INPUT SOCKETS (Matched Pairs). (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of the Input Selector Switch assures appropriate equalisation. Rigid 18 s.w.g. Chassis. Size approx. 12in. Wide. 3in. High and 8in. Deep. Neon Panel Indicator. Attractive Facia Plate and Spun Silver Matching Knobs. Above facilities, etc., except for Ganging and Balance Control, apply also to Super 15. THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE. Crystal, Ceramic, Magnetic, Moving Coil, Ribbon CURRENTLY AVAILABLE. SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions. Carr. 12/6 18 Gns. Attractive Walnut or Teak finished cabinet 5 gns. or Deposit 17/- and 9 monthly pmts 11/3 (Total £5.18.3). Or unit completely assembled ready for use housed in cabinet 29 GNS. Carr. 15/- Or Deposit £4.12.0 and 9 mthly pmts 64/10 (Total £33.15.6). Send S.A.E. for leaflet.

AUDIOTRINE HI-FI TAPE RECORDER KIT


REALISM AT INCREDIBLY LOW COST.
CAN BE ASSEMBLED IN AN HOUR.
ONLY 4 PAIRS OF SOLDERED JOINTS PLUS MAINS.
Incorporating the latest Magnavox Tape Deck. The Audiotrine High Quality Tape Amplifier with switched equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a handsome Portable Cabinet of latest styling finished in dark grey leathercloth with silver chrome trimmings etc. Size 14 1/2 x 17 x 8 1/2 in. and circuit. Purchased separately would total approx. £34. Performance equal to units in the £50-£60 class. S.A.E. for leaflets. TERMS: Deposit 4 gns. and 9 monthly payments of 5/6 (Total 23 1/2 gns.). 4 Track Model 3 gns. extra.

26 1/2 Gns.
Carr. 1/6



R.S.C. 4/5 watt A5 HIGH GAIN AMPLIFIER

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P.U. heads and practically all "mikes". Separate Bass and Treble controls giving "lift" and "cut". Hum level 71dB down. Negative Feedback 15dB. H.T. of 300v. 25mA and L.T. of 6.3v. 1.5a. available for supply of Radio Tuner or Tape Deck pre-amp. For A.C. mains 200-250v. Speaker output 3 ohms. Kit is complete in every detail with fully punched Hammer finished chassis, point-to-point wiring diagrams and instructions. Exceptional value **£4.17.9**

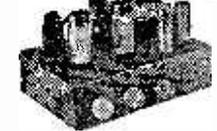

or assembled ready for use 6 gns. plus 5/6 carr.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER


A highly sensitive Push-Pull high output unit with Pre-amp/Tone Control Stages. Performance figures compare equally with most expensive amplifiers available. Hum level -70dB. Frequency response $\pm 3dB$ 30-20,000 c/s. Specially designed sectionally wound ultra linear output transformer with 807 output valves. All first grade components. Output 3 ohms. Valves EF86, EF88, ECC83, 807, 807, CZ24. Separate Bass and Treble Controls. Sensitivity 12 millivolts so that any kind of Microphone or Pick-up is suitable. The unit is designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram and/or Tape. Output socket provides L.T. and H.T. Output 3 ohms. Kit complete with fully punched chassis and point-to-point wiring diagrams and instructions. 12 Gns. Carr. 10/-



Such as String Bass, Electronic Guitars, etc. Output Socket provides 300v. 30mA. and 6.3v. 1.5a. for supply of a Radio Tuner. Size approx. 12 x 9 x 7 in. For A.C. mains 200-250v. 50 c.p.s. punched. Full instructions and point-to-point wiring diagrams supplied. (or factory built £11.15.0). Metal covers with 2 carrying handles can be supplied for £1. TERMS ON ASSEMBLED UNITS: Deposit 36/6 and 9 monthly payments of 25/9 (Total £13.8.3). Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Mikes, etc.

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP Two input sockets with associated controls allow mixing of "mike" and gram, etc., etc. High sensitivity. Valves ECC83, ECC83, EL84, EL84, EZ34. High quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE. Frequency response $\pm 3dB$ 30-20,000 c/s. Six negative feedback loops. Hum level -60dB. SENSITIVITY 23 millivolts. Suitable for Crystal or Ceramic P.U.s, all types "mikes". Comparable with the very best designs. For Musical Instruments such as String Bass, Electronic Guitars, etc. Output Socket provides 300v. 30mA. and 6.3v. 1.5a. for supply of a Radio Tuner. Size approx. 12 x 9 x 7 in. For A.C. mains 200-250v. 50 c.p.s. punched. Full instructions and point-to-point wiring diagrams supplied. (or factory built £11.15.0). Metal covers with 2 carrying handles can be supplied for £1. TERMS ON ASSEMBLED UNITS: Deposit 36/6 and 9 monthly payments of 25/9 (Total £13.8.3). Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Mikes, etc.

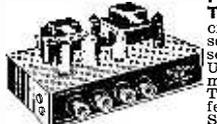

ONLY **£8.15.0**
Carr. 11/6

R.S.C. BASS-REGENT 50 WATT AMPLIFIER

AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT For lead, rhythm, bass guitar and all other musical instruments. For vocalists, gram, radio, tape and general public address

★ UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS a FANE 12in. 20 watt unit with 4 jack inputs and two Volume Controls for simultaneous use of up to 4 pick-ups or "mike" type

★ Cabinets covered in two-tone Rexine/Vynair with gold trimming. Fitted carrying handles. ★ Separate Bass and Treble Controls giving "lift" and "cut".

49 1/2 Gns. Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at three times the cost. Or deposit 27.17.6 and 9 monthly payments of 25.10.10. (Total 55 gns.)



R.S.C. B20 MULTI-PURPOSE AMPLIFIER

especially suitable for Bass Guitar
Incorporating massive 15in. high flux loudspeaker. Rating 25 watts. Individual bass and treble controls. Two jack inputs separately controlled. Substantial cabinet attractively finished in Rexine and Vynair. Size approx. 24 x 21 x 11 in. Send S.A.E. for leaflet. Or **29 1/2 Gns.** Deposit £4.14.6 and 9 monthly payments of 66/- (Total £34.8.6) Carr. 17/6



G15 5 WATT AMPLIFIER for Lead or Rhythm Guitar, Mike, Gram or Radio

High-fidelity output. Separate bass and treble controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Heavy Duty 12in. 20 watt Speaker. Cabinet covered in attractive Rexine/Vynair. Size 18 x 18 x 8in. **19 1/2 Gns.** Deposit 5 gns. and 9 monthly payments of 43/7 (Total £22.15.3). Send S.A.E. for leaflet.

G20 SUPER TWIN AMPLIFIER

Rating 20 watts (max.) for Lead or Rhythm Guitar etc. Twin separately controlled inputs. Two 12in. High Flux Speakers (Total rating 30 watts). Attractive Rexine/Vynair covered cabinet. Carr. 17/6
TERMS: Deposit £4.8.8 and 9 monthly payments 50/- (Total £26.16.8) **23 Gns.**

TRANSISTORISED SOUND MIXER Enables mixing of up to 4 standard jack inputs, i.e., microphone, tape, gram, tuner, etc., into single output. Compact and completely self-contained. Uses standard 9v. battery. **49/9**

SPECIAL PURCHASE! 12in. 30 WATT HEAVY DUTY 15 ohm LOUDSPEAKERS

Flux Density 17,000 lines. Fully Guaranteed. Outstanding value at normal price of approx. £12 but a real snip at **7 Gns.** Carr. 12/6


FANE HEAVY DUTY HI-FI SPEAKERS

12in. 20 watt. Type 122/10. **5 Post 5/6. GNS.**



R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. 15 ohm matching. Type 58, 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 42 x 10 x 5in. Or Deposit 23 and 9 monthly pmts 28/- (Total £14.12.0) Carr. 10/- Type C412, 40 watts. Fitted four 12in. 12,000 line 10 watt speakers. Overall size 58 1/2 x 9in. approx. Carr. 15/- Or Deposit 3 gns. and 9 monthly payments of 43/7 (Total £22.15.3). **12 1/2 Gns.** **19 1/2 Gns.**

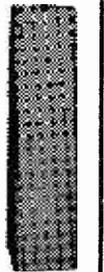


18in. 60 WATT EXTRA HEAVY DUTY LOUDSPEAKERS

Famous make. Normal price over £25. Very limited number to clear with full guarantee. Terms available. Carr. 15/- **17 Gns.**

12in. HIGH QUALITY LOUDSPEAKERS

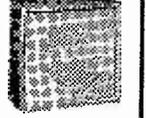In walnut veneered cabinet. 10 Watt Model. Gauss 12,000 lines. **£4.19.6** Speech coil 3 or 15 ohms. Terms: Deposit 15/- and 9 Carr. 5/6 monthly payments of 11/2 (Total £5.15.6) **20 Watt Model.** Size 18x18x10in. Terms: Deposit 24/6 and 9 Carr. 8/6 monthly payments of 17/3 (Total £8.19.9) Carr. 8/6



30 Watt Model. 15 ohms. Or **10 Gns.** Carr. 10/- payments of 22/4 (Total £13.8.0). Any of above in extra heavy Rexine covered Cabinets, £1 extra.

30 WATT HI-FI AMPLIFIER

for Guitar, Vocal or Instrumental Groups

A Four Input, two volume control Hi-Fi unit with separate Bass and Treble "cut" and "boost" controls. Latest type valves. Housed in strong Rexine covered cabinet with twin carrying handles. Attractive black and gold perspex fascia plate. For 200-250v. A.C. mains. Output for 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 23 and 9 monthly payments of 37/5 (Total £19.16.9). Carr. 12/6. **17 Gns.**



HEAVY DUTY SELENIUM RECTIFIERS

12v. 15 amps. F.W. (Bridge). **Only 19/9**

TRANSISTOR SALE Mullard OC71 2/11, OC45 3/11, OC44 3/11, OC72 2/11, OC75 6/9, OC81 2/11, OC71 3/9, AF117 6/9. Ediswan XA101 3/9, XA112 3/9, XC101A 3/9. Postage 6d. for up to 3 transistors.

INTEREST CHARGES REFUNDED

on H.P. and Credit Sale Accounts settled in 3 months.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250v. 50 c/s. Screened. MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in. 250v., 60mA, 6.3v. 2a 14/11 250-0-250v., 60mA, 6.3v. 2a 15/11

FULLY SHROUDED UPRIGHT MOUNTING 250-0-250v., 60mA, 6.3v. 2a, 0-5-6.3v. 2a, 2.5 x 3in. 19/9 250-0-250v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a, 3in. 33/9 300-0-300v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a, 3in. 33/9 300-0-300v. 130mA, 6.3v. 4a ct., 6.3v. 1a. For Mullard 510 Amplifier 41/9 350-0-350v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a, 3in. 33/9 350-0-350v. 150mA, 6.3v. 4a, 0-5-6.3v. 3a, 3in. 42/9 425-0-425v. 200mA, 6.3v. 4a, ct., 5v. 2a 63/9 425-0-425v. 200mA, 6.3v. 4a, 6.3v. 4a, 5v. 2a 63/9 450-0-450v. 250mA, 6.3v. 4a, ct., 5v. 2a 79/9

TOP SHROUDED DROP-THROUGH TYPE 250-0-250v. 70mA, 6.3v. 2a, 0-5-6.3v. 2a, 2in. 19/9 250-0-250v. 100mA, 6.3v. 3.5a 21/9 250-0-250v. 100mA, 6.3v. 2a, 6.3v. 1a 22/9 350-0-350v. 80mA, 6.3v. 2a, 0-5-6.3v. 2a 22/9 250-0-250v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a 32/9 300-0-300v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a 32/9 300-0-300v. 130mA, 6.3v. 4a, 0-5-6.3v. 1a suitable for Mullard 510 Amplifier 39/9 350-0-350v. 100mA, 6.3v. 4a, 0-5-6.3v. 3a 32/9 350-0-350v. 150mA, 6.3v. 4a, 0-5-6.3v. 3a 39/11

FILAMENT/TRANSISTOR P/P TRANSFORMERS 6.3v. 1.5a 6/9, 6.3v. 2a 7/9, 6.3v. 3a 9/9, 6.3v. 6a 19/9, 12v. 1a 8/9, 12v. 3a or 24v. 1.5a 19/9, 42v. 2a 27/9.

AUTO (STEP UP/STEP DOWN) TRANSFORMERS 0-110/120v. 200-230-250v. 50-80 watts 14/9 250 watts 49/9 150 watts 29/11 500 watts 99/9

CHARGER TRANSFORMERS 0-9-15v. 1 1/2a 13/9 0-9-15v. 5a 21/9 0-9-15v. 2 1/2a 16/9 0-9-15v. 6a 25/11 0-9-15v. 3a 18/9 0-9-15v. 8a 31/9

OUTPUT TRANSFORMERS Standard Pentode 5,000 Ω to 3 Ω or 7,000 Ω to 3 Ω 7/9 Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 11/9 Push-pull 10-12 watts 6V6 to 3 Ω or 15 Ω 19/9 Push-pull 10-12 watts to match 6V6 to 3, 5, 8 or 15 Ω 21/9 Push-pull EL84 to 3 or 15 Ω 10-12 watts 18/9 Push-pull Ultra Linear for Mullard 310, etc. 35/9 Push-pull 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15 Ω 29/9 Push-pull 20 watt high-quality sectionally wound, EL84, 6L6, KT66, etc., to 3 or 15 Ω fully shrouded 55/9

SMOOTHING CHOKES 150mA, 7-10H, 250 Ω 12/9. 80mA, 10H, 350 Ω 7/9. 100mA, 10H, 200 Ω 9/11. 60mA, 10H, 400 Ω 4/11.

LINEAR TREMOLO PRE-AMP UNIT

Suitable for use with any of our Amplifiers. Controls are Speed (frequency of interrupting) Depth (for heavy or light effect). Volume and Switch. **4 1/2 Gns.**

POWER PACK KIT

Consisting of Mains Transformer, Metal Rectifier, Smoothing choke, chokes and circuit. 200/250v. A.C. mains. Output 250v. 60mA, 6.3v. 2a or with metal cover **22/9**

R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BMI. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries applying 1.4v. and 90v. where A.C. mains. 200/250v. 50 c/s is available. Complete kit with diagram **44/9** or ready for use 59/6.



R.S.T. VALVE MAIL ORDER CO.

144-146 WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.—5.45 p.m.
No Early Closing
Open Daily to Callers
Tel. STR 0199, 1649

OA2	5/3	6BH6	7/-	6K7G	1/6	7Y4	5/-	20F2	11/-	78	4/6	DK32	7/9	ECH21	19/-	EM84	6/-	PCC189	10/-	S130	12/6	UL84	5/6
OC8	5/3	6B7G	7/6	6K7GT	4/6	9BW6	8/-	20L1	15/-	80	5/6	DK91	5/-	ECH35	13/-	ESU150	27/6	PCR80	6/6	SP4	9/-	UM80	7/-
LD5	6/-	6B7A	7/6	6K8M	3/6	10C1	12/6	20P4	14/-	85A2	8/6	DK92	7/9	ECH42	8/-	EY31	6/-	PCR82	6/-	SP41	1/6	UU7	13/6
LD5	7/6	6BR8	7/6	6K8GT	3/3	10C2	12/-	20P5	12/-	180B3	14/6	DK96	6/6	RCH81	5/6	EY36	6/3	PCR84	8/-	SP61	1/6	UU7	13/6
LD5	7/6	6BR8	7/6	6K8GT	3/3	10C2	12/-	20P5	12/-	150C4	12/6	DL70	7/-	RCH83	6/6	EZ35	4/9	PCR86	8/6	SU25	19/6	UU9	8/-
LD5	5/-	6BS7	15/-	6K25	20/-	10F3	12/-	25L6GT	4/6	801	5/-	DL92	4/9	RCL80	5/6	EZ40	5/6	PCR801	9/9	SU2150	12/6	UY21	7/6
1N5GT	8/-	6BW6	8/6	6LL	9/6	10F9	9/9	25Y5	6/-	807	7/9	DL93	3/6	ECL82	6/6	EZ41	6/6	PCR802	9/9	T41	9/-	UY41	4/6
1R5	5/-	6BWT	8/9	6L6G	7/-	10F13	9/-	25Z4	6/3	813	80/-	DL94	6/-	ECL83	9/-	EZ50	5/6	PCR805	10/6	TDD4	7/-	UY35	4/9
1S4	5/-	6C4	1/9	6L8	7/6	10L1	10/-	25Z6	8/6	954	4/-	DL96	6/-	ECL86	8/6	EZ51	3/6	PCR806	12/6	TH41	25/-	VMP4G	17/-
1R5	3/3	6C5G	4/-	6Q7G	5/6	10L11	10/-	25Z7	7/-	896	13/-	DL95	8/6	ECL88	8/6	EZ52	3/6	PCR808	12/6	U10	7/-	VP4B	27/6
1T4	2/6	6C6	3/9	6Q7GT	9/-	10L12	10/-	25D7	5/-	1625	5/-	DM70	5/-	EF36	3/-	GZ22	9/-	PCL82	6/6	U14	7/-	VR105/30	5/-
3A4	3/6	6C8G	6/-	6SA7	7/-	12AT6	4/6	30C1	6/6	4022AR	15/-	DY86	7/9	EF37A	9/6	GZ34	9/9	PCL83	8/6	U19	30/-	VR150/30	5/-
3Q4	6/6	6CD6G	22/6	6SC7	6/6	12AT7	3/3	30C15	9/6	5763	10/6	DY87	7/9	EF39	5/-	KT36	22/6	PCL84	7/6	U26	10/-	VT25	29/-
3Q5	6/6	6CH6	8/-	6SG7	4/-	12AU6	5/9	30C17	12/-	7193	1/6	ES9CC	14/-	EF41	6/6	KT61	17/6	PCL85	7/3	U26	10/-	VT31	59/-
3S4	4/9	6CW4	14/-	6SH7	2/6	12AU7	5/9	30F5	9/-	7475	2/6	RA50	2/-	EF50	2/-	KT66	20/-	PCL86	8/9	U78	8/6	VU111	6/-
3V4	6/-	6D6	2/9	6S7	5/-	12AU7	5/9	30F11	10/6	ATP4	1/9	RABCS0	5/6	EF50	4/6	KT81	10/-	PEN44	20/-	U191	11/-	VU120	9/-
5R4G	8/-	6E5	5/9	6SK7GT	4/9	12AX7	4/6	30L15	12/-	ATP5	7/-	BAF42	7/6	EF85	4/6	KT88	28/-	PEN84	20/-	U251	11/6	VU505	25/-
5U4G	4/-	6F1	9/-	6SL7GT	4/9	12BA6	6/-	30L17	12/6	ATP7	4/6	BB41	4/6	EF86	6/6	KTW61	4/3	PEN45	6/-	U301	12/-	WS1M	5/-
5V4G	8/-	6F6G	5/-	6SN7GT	4/-	12BB7	5/9	30F12	10/-	AU2	80/-	EB91	3/-	EF89	4/-	KTZ41	8/-	PEN46	2/9	U403	6/6	X78	26/6
5Y3GT	4/6	6F6G	4/-	6SQ7	6/-	12BH7	5/9	30F19	14/-	AU5	6/-	EB333	6/-	EF91	2/9	ML4	17/6	PL81	9/6	U801	18/6	X79	41/-
5Z4	10/6	6F8G	4/6	6U4GT	10/-	12C8GT	7/6	30PL1	11/-	AZ1	8/9	EB041	6/6	EF92	2/6	ML6	12/6	PL81	7/-	UABC80	5/6	XH1-5	5/-
6/30L2	10/-	6F11	12/6	6U6G	7/6	12E1	19/6	30PL13	12/6	AZ81	7/9	EB090	3/6	EF98	10/-	MSP4	12/6	PL82	5/6	UABC41	7/-	XP1-5	10/-
6A7	15/-	6F13	5/-	6V6M	8/-	12F6GT	2/3	30PL14	12/6	CB131	28/6	EBF80	5/-	EF183	6/6	MU14	4/-	PL83	6/-	UBC41	6/6	XSG1-3	10/-
6A8G	12/6	6F14	12/6	6V6G	6/6	12G7GT	7/3	35A5	17/-	CK502	5/-	BBF83	7/3	EF184	6/6	MX40	12/6	PL84	6/3	UBC81	7/-	Y63	7/6
6A7C	3/-	6F23	9/6	6V6GT	7/-	12K7GT	3/-	35A6	5/9	CL33	19/6	EBF89	5/9	EL32	3/-	N37	10/-	PL500	14/6	UBF80	5/9	Tubes	
6AK5	4/6	6G6	2/6	6X4	3/6	12K8GT	8/3	35W4	4/9	CU1	10/-	EB117	17/6	EL33	17/6	N35	15/-	PX4	18/6	UBF89	6/3	3EG1	40/-
6AL5	3/-	6H6	1/3	6X5G	4/9	12Q7GT	3/-	35Z3	10/-	DAC32	7/6	EB121	10/6	EL34	9/6	N108	15/-	PY33	8/6	UCC84	8/6	3FF7	12/6
6AM5	2/6	6J7M	6/6	6X5GT	7/6	12SA7	6/6	35Z4GT	3/9	DAF91	3/3	EB131	27/6	EL41	7/3	NGT1	3/-	PY81	5/6	UCC85	6/6	5CP1	30/-
6AM6	2/9	6J5G	2/6	7B6	11/-	12S67	3/9	35Z5	5/6	DAF96	6/-	ECC81	3/3	EL42	7/6	NGT7	25/-	PY82	5/6	UCF80	8/6	CV1826	40/-
6AQ5	6/-	6J5GT	4/6	7B7	7/-	12S77	3/9	37	5/-	DCC90	8/-	ECC82	5/6	EL84	4/8	OZ4	4/-	PY83	6/-	UCH42	7/-	ACR13	
6AS7	22/6	6J6	3/-	7C6	10/-	12S87	2/9	42	4/6	DF33	8/-	ECC83	4/6	EL90	6/-	PC86	10/-	PY800	5/9	UCH81	6/3	VC907	28.00
6AT6	3/6	6J7M	8/6	7C8	8/-	12S8K7	2/9	40B5	6/6	DF70	5/-	ECC84	5/6	EL95	6/-	PC88	9/3	PY801	6/3	UCL82	7/9	VC997	27/6
6AU6	6/-	6J7G	4/3	7D5	8/-	12S8R7	5/-	40C5	6/3	DF91	2/6	ECC85	5/9	EL96	6/-	PC89	7/7	R2	4/-	UCL83	8/9	VC9517B	
6BSG	2/9	6J7GT	8/6	7H7	5/-	12S9	20/-	50CD6G	35/-	DF92	2/6	ECC88	8/9	EM34	12/6	PC97	7/-	R19	7/-	UF41	7/-	VC9517C	
6BA6	4/9	6K6GT	5/-	7R7	19/6	19AQ5	7/6	50L6GT	6/-	DF96	28/-	ECC89	6/6	EM30	6/-	PCC84	5/9	RG5/500	6/6	UF89	6/6	VC9517D	
6BE6	4/9	6K7M	5/-	7S7	18/6	20D1	10/-	75	5/-	DH77	3/6	ECC92	6/-	EM81	7/-	PCC89	8/6			UL41	6/6		30/-

SPECIAL 24 HOUR SERVICE
OBSOLETE TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
Postage 6d. per Valve C.W.O. No C.O.D.
Send S.A.E. for list
Manufacturers and Export Inquiries Welcome

Special 24 Hour
Express Mail
Order Service

DAF91	DF91	DK91	DL92	DL94	...	Set of 4	19/-
DAF96	DF96	DK96	DL96	Set of 4	25/-
BRAND NEW TRANSISTORS							
AF114	9/-	OC35	9/6	OC77	8/-	OC82D	6/-
AF115	7/-	OC44	4/6	OC81	4/-	OC93	6/-
AF116	8/-	OC45	3/6	OC81m/pr	4/-	OC170	7/6
AF117	5/6	OC71	4/6			OC200	8/-
OC25	11/-	OC72	6/-	OC81D	12/6		
OC28	16/-	OC75	6/-	OC82	4/-		

PLEASE NOTE OUR NEW ADDRESS

THE PEMBRIDGE COLLEGE OF ELECTRONICS PROVIDES TRAINING IN RADIO AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 6th September, 1966.

This Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:
The Pembridge College of Electronics (Dept. P11)
34a Hereford Road, London, W.2.

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name _____

Address _____



Heathkit models offer outstanding performance plus highest quality – at lowest cost

Anyone can build a Heathkit model. Easy-to-follow instruction manuals issued with each kit-set show you how. You will be proud of the professional appearance and performance of your finished model.

A KIT FOR EVERY INTEREST . . . FOR HOME, WORKSHOP, SERVICE AND TEST DEPTS.

TEST & SERVICE INSTRUMENTS



- | | | |
|--|----------|-----------|
| ● 5in. OSCILLOSCOPE, 10-12U
TB 10 c/s—500 kc/s. ... | Kit | Assembled |
| ● 3in. OSCILLOSCOPE, OS-2
TB 20 c/s—200 kc/s. ... | £35 17 6 | £45 15 0 |
| ● 4in. VALVE VOLTMETER,
V-7A ... | £22 18 0 | £31 18 0 |
| ● 6in. VALVE VOLTMETER,
IM-13U ... | £13 18 6 | £19 18 6 |
| RF and HV probes available as extras | £18 18 0 | £26 18 0 |

- | | | |
|---|----------|-----------|
| ● REGULATED POWER SUPPLY, 1P-20U (Transistor), 0-5-50v D.C. to 1-5A ... | Kit | Assembled |
| ● TV ALIGN'N'T GENERATOR, HFW-1, 3-6-220 Mc/s ... | £35 8 0 | £47 8 0 |
| ● RF SIGNAL GENERATOR, RF-1U. (Up to 100 Mc/s fund.) ... | £38 18 0 | £49 15 0 |
| ● MULTIMETER, MM-1U (V, A, Res, dB) ... | £13 18 0 | £20 8 0 |
| | £12 18 0 | £18 11 6 |



V-7A


- | | | |
|--|----------|-----------|
| ● ELECTRONIC SWITCH, S-3U
Scope Trace doubler ... | Kit | Assembled |
| ● AUDIO SIGNAL GENERATOR, AG-9U
10 c/s—100 kc/s ... | £13 10 0 | £19 10 0 |
| ● AUDIO SINE/SQ GENERATOR, A0-1U
Sine wave 20 c/s-150 kc/s ... | £23 15 0 | £31 15 0 |
| ● SINE/SQ GENERATOR, 1G-82U
Freq. range, 20 c/s-1 Mc/s ... | £14 15 0 | £21 5 0 |
| ● AUDIO VALVE MILLIVOLTMETER, AV-3U. 10 c/s-400 kc/s ... | £25 15 0 | £37 15 0 |
| ● HAR. DISTORTION METER, IM-12U
Many other instruments available.
Send for free Instrument Brochure. | £17 15 0 | £24 5 0 |
| | £26 15 0 | £36 0 0 |

AMERICAN HEATHKIT MODELS

- A wide range available including:
- DE-LUXE AM/FM PORTABLE TRANSISTOR RADIO, GR-43. An outstanding Luxury model ... Kit £102 10 0 incl. PT
 - SHORT-WAVE RECEIVER, GR-64E. For short-wave listening at low cost ... Kit £22 10 0
- Send for American Catalogue, 1/- incl. Post.

TRANSISTOR RADIOS

- "OXFORD" LW/MW RECEIVER, UXR-2. Kit £14.18.0, incl. P.T.
 - 6 TRANSISTOR PORTABLE, UXR-1, LW/MW. Kit £12.11.0, incl. P.T.
 - "MOHICAN" GENERAL COVERAGE RECEIVER, GC-1U ... Kit £37 17 6 Assembled £45 17 6
 - ELECTRONIC WORKSHOP, EW-1 (experimental Kit) ... £7 13 6 incl. P.T.
 - JUNIOR RADIO, UJR-1 ... £2 7 6 incl. P.T.
- Headphones 30/- extra. Additional amplifier stage (will work speaker), 16/6 extra.

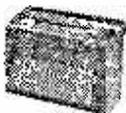

A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO. PLEASE SEND FOR LISTS AND PRICES.

- All prices quoted above are Mail Order prices ●

WELCOME TO OUR LONDON HEATHKIT CENTRE

233 Tottenham Court Road

We open MONDAY-SATURDAY 9 a.m.-5.30 p.m.
(THURSDAY ... 11 a.m.-2.30 p.m.)

Telephone No: MUSEUM 7349

WHEN YOU ARE IN TOWN, WE HOPE YOU WILL VISIT US THERE

AUDIO Hi-Fi

- F.M. TUNER (in two parts), 88-108 Mc/s. Total price Kit £16.8.0, incl. P.T.
 - A.M./F.M. TUNER (in two parts), 88-108 Mc/s, L-M-S waves. Total price Kit £27.5.0, incl. PT.
- 
- F.M. TUNER
Kit Assembled
- 3+3W STEREO AMPLIFIER, S-33H. Inputs for P.U. (Deram) radio, Aux. ... £15 17 6 £21 7 6
 - 3+3W STEREO AMPLIFIER, S-33. Inputs for P.U. (crystal) or radio ... £13 7 6 £18 10 0
 - 9+9W STEREO AMPLIFIER, S-99. Inputs for radio, tape, Aux., all P.U.s ... £28 9 6 £38 9 6
 - 20+20W STEREO AMPLIFIER, AA-22U. Transistor, inputs for P.U. (Mag.) and 4 other ... £39 10 0 (less cabinet)
 - 5W MONO AMPLIFIER, MA-5. Inputs for P.U. and radio ... £11 9 6 £15 15 0
 - 10W POWER AMPLIFIER, MA-12. For use with Control units, UMC/USC ... £12 18 0 £16 18 0
 - 50W POWER AMPLIFIER, MA-50 ... £19 18 0 £27 18 0
 - 4 CHANNEL MIXER TM-1. Transistor, battery operated ... £11 16 6 £16 17 6
 - TAPE PRE-AMP (MONO) TA-1M. Needs P.S. and Audio Amplifier ... £19 18 0 £28 18 0
 - MAGNAVOX 363 DECK, ½ Track ... £13 10 0

SPEAKER SYSTEMS

- 
- Berkeley
- | | | |
|---|---------------------|-----------|
| ● BERKELEY slim-line, 2-LS. Cabinet fully finished ... | Kit | Assembled |
| ● COTSWOLD standard, 3-LS Cabinet (in the white) ... | £19 10 0 | £24 0 0 |
| ● COTSWOLD MFS, 3-LS, Cabinet (in the white) ... | £25 12 0 | £33 17 0 |
| ● SSU-1 Low-priced System, 2-LS Cabinet (in the white, less legs) ... | £25 12 0 | £33 17 0 |
| Ancillary speakers also available. | £11 17 6 incl. P.T. | |

'AMATEUR' EQUIPMENT

- A wide range of models including:
- AMATEUR BANDS RECEIVER, RA-1 (160-10m). The ideal fixed station, portable or mobile receiver. Many features incl.: 'S' meter. Kit £39.6.6, Assembled £52.10.0
 - COMMUNICATIONS TYPE RECEIVER, RG-1, MW and 32 Mc/s-1.7 Mc/s ... £39 16 0 £53 0 0
 - 160-10M TRANSMITTER, DX-100U ... £81 10 0 £106 15 0
 - 80-10M TRANSMITTER, DX-40U ... £29 19 0 £41 8 0
- Other kits in range include: SSB Adaptor, SB-10U £39 5 0
Variable Freq. Oscillator, VF-1U £10.17.6
Balun Coil Unit, B-1U, £4.15.6
Grid-Dip Meter, GD-1U £11.9.6
Multiplier, QPM-1, £8.10.0
Reflected Power Meter, HM-11U, £8.10.0
- Also wide range of American models. Please send for details. Send for Amateur Brochure, free.



To: DAYSTROM LTD., Dept. P.W.-9 GLOUCESTER, ENGLAND

Please send me FREE BRITISH CATALOGUE (Yes/No)
INSTRUMENT BROCHURE (Yes/No)
AMATEUR BROCHURE (Yes/No)

Full details of model(s).....

American Catalogue, 1/- Post Paid (Yes/No).....

NAME


ADDRESS

LASKY'S RADIO

FOR THE FINEST VALUE AND TO HOME CONSTRUCTORS

TRANSISTOR PORTABLES

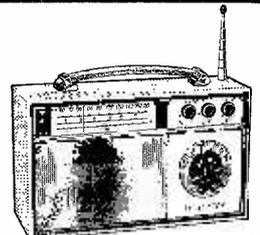We consider our Construction Parcels to be the finest value available on the home construction market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded less postage.



THE SKYROVER De Luxe

7 transistor plus 2 diode superhet, 6 waveband portable receiver covering the full Medium Waveband and Short Waveband 31-84M and also 4 separate switched band-spread ranges, 12M, 16M, 19M, and 22M, with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions. Superhet, 470 Kc/s. All Mullard Transistors and Diode. Uses 4 U2 batteries. 5in. Ceramic Magnet P.M. Speaker. Easy to read Dial Scale, 500 MW Output. Telescopic Aerial and Ferrite Rod Aerial. Tone Circuit is incorporated, with separate Tone Control in addition to Volume Control. Tuning Control and Waveband Selector. In a wood cabinet, size 11½ x 6½ x 3in. covered with a washable material, with plastic trim and carrying handle. Car aerial socket fitted.

★ LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THE SKYROVER

A simple additional circuit provides coverage of the 1100/1950M. band (including 1500M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data.

Only 10/- extra Post Free. This conversion is suitable for receivers that have already been constructed.


Data 2/6 extra: Refunded if you purchase the parcel. Four U2 batteries 3/4 extra. All components available separately.

Can now be built for **£8. 19. 6** Post 5/- extra
 H.P. Terms: 45/- deposit and 11 monthly payments of 14/2. Total H.P.P. £10.0.10

REALISTIC SEVEN

Fully tunable long and medium bands. Uses 7 Mullard Transistors; plus Diode OA70.

STAR features:
 ● 7 Transistor Superhet. ● 350 Milliwatt output 4in. high flux speaker. ● All components mounted on a single printed circuit board. Size 5½ x 5½in. in one complete assembly. ● Plastic cabinet, with carrying handle, size 7 x 10 x 3½in. in blue/grey. ● Easy to read dial. ● External socket for car aerial. ● I.F. frequency 470 Kc/s. ● Ferrite rod internal aerial. ● Operates from PP9 or similar battery. ● Full comprehensive data supplied with each Receiver. ● All coils and I.F.s, etc., fully wound ready for immediate assembly. An outstanding Receiver.
 Battery 3/9 extra. (All components avail. sep.) Data and ins. 2/6, refunded if you purchase parcel.

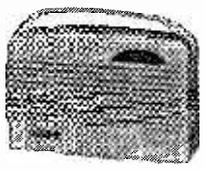

Can be built for P. & P. 4/6
£5. 19. 6

CONSTRUCTORS BARGAINS

SPECIAL PURCHASE—UHF/VHF TUNERS

Well known British makers surplus stocks. Now available for the first time to the Home Constructor.

TRANSISTORISED UHF MINIATURE MODEL

Shielded metal case only 3½ x 1½ x 3in. Fully tunable—complete with two AF139 transistors. **LASKY'S PRICE 32/6**

VALVE UHF MODEL (illustrated)

In metal case size 4 x 6 x 1½in. Fully tunable—complete with PC86 and PC88 valves. **LASKY'S PRICE 32/6** Without valves **19/6**

TRANSISTORISED VHF MODEL 1

Miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case size 4 x 2 x 3½in. **LASKY'S PRICE 29/6**

TRANSISTORISED VHF MODEL 2

Sub-Miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case size 3 x 1½ x 2½in. **LASKY'S PRICE 37/6**
 Add 2/6 Post and Packing on each.

GORLER UT 340 FM/VHF TUNING HEART

Permeability tuned—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case, size 3 x 2½ x 1½in. Circuit supplied.
LASKY'S PRICE 15/11 Post 2/-, ECC85 valve 9/- extra.

TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET 81, GET 85, GET 86 8/8; 873A, 874P 3/8; OC45, OC71, OC81D 4/8; OC44, OC70, OC76, OC81 5/8; (match pair 10/8); AF117, OC200 8/8; OC42, OC43, OC73, OC82D 7/8; OC201, OC204 15/-; OC205, OC206 19/8; OC28 24/8; OC76 8/-.


TRANSFILTERS

by BRUSH CRYSTAL CO., Available from stock.

TO—01B 465 kc/s. ± 2 kc/s. TO—02D 470 kc/s. ± 1 c/s.
 TO—01D 470 kc/s. ± 2 kc/s. TP—01B 465 kc/s. ± 2 kc/s.
 TO—02B 465 kc/s. ± 1 kc/s. TP—01D 470 kc/s. ± 2 kc/s.

7/6 each
 Post 6d.

TAPE RECORDERS

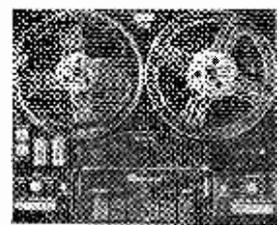

THE NEW GARRARD STEREO DECK


Now available from stock—superb specification: three ½ track stereo/mono heads; 3 speeds—1 3/4, 7 1/2 i.p.s.; takes 7in. spools; fast forward and rewind; tape position indicator; pause control; separate record, replay and erase heads—4 tracks; piano key controls interlocked for all functions; stop/start can be remotely controlled; auto, tap-and-stop. Heavy duty motor, capacitor start and run, large dynamically balanced fly-wheel. Deck finished in grey plastic, size: 14½ x 12 x 6in., depth below plinth 4in. For 110v. 50 c.p.s. Mains operation. Auto-transformer for 200/250v. included free.

LASKY'S PRICE 29½ GNS. Carriage & Packing Free

MAGNAVOX-COLLARO 363 TAPE DECKS

The very latest 3 speed model—1 3/4, 3 1/2, 7 1/2 i.p.s. available with either ½ track or 1 track head. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor, interlocking keys. Size of top plate 13½ x 11in. x 5½in. deep below unit plate. For 200/250v. A.C. mains, 50 cps operation. New, unused and fully guaranteed.

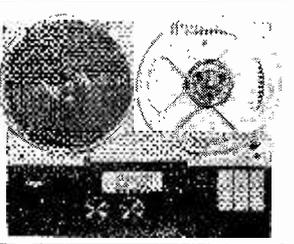Lasky's Price ½ track model £10.10.0
Lasky's Price 1 track model £13.9.6
 Carriage and Packing 7/6 extra.



SPECIAL BARGAIN—"THE ARROW" PORTABLE DICTATION/TAPE RECORDER



High Quality British Manufacture: Fully transistorised
 ● Battery operated ● Simple Cassette loading and single control lever (cassette takes 3in. spools giving 2 x 22 mins. twin track recording and 3½in. spools giving up to 2 x 30 mins.) ● Volume control ● Accidental erasure safety device ● Fast rewind ● Operates on 4 1/2 type cells. ● Strong tone-tone plastic case size 9in. x 6in. x 3½in., with transparent cover. ● Fully guaranteed ● Complete with all these accessories: * Cassette with 3in. spools and tape. * Microphone with lapel clip and remote pause control (doubles as speaker on replay). * Stethoscope type headset. * Telephone adaptor. * Foot Switch. * Desk speaker. * Reference pad. List price £21.

LASKY'S PRICE £7. 19. 6
 Carriage 5/-, 4 long life Rayovac Batt. 6/- extra.

INTERNATIONAL TAPE Famous American Brand—Fully Guaranteed

3in. Message tape, 150ft.	2 6	5½in. Long play, 1200ft. Acetate	12 6
3in. Message tape, 225ft.	3 9	5½in. Standard play, 850ft. PVC	11 6
3in. Message tape, 300ft.	7 6	5½in. Long play, 1200ft. Mylar	15 0
3½in. Triple play, 600ft. Mylar	10 0	5½in. Triple play, 2400ft. Mylar	20 0
4in. Triple play, 900ft. Mylar	17 6	7in. Standard play, 1200ft. Acet. 12 6	
5in. Double play, 1200ft. Mylar	15 0	7in. Standard play, 1200ft. Mylar	12 6
5in. Long play, 900ft. Acetate	10 0	7in. Long play, 1800ft. Mylar	19 6
5in. Standard play, 600ft. PVC	8 6	7in. Double play, 2400ft. Mylar	25 0
5in. Triple play, 1800ft. Mylar	35 0	7in. Long play, 1800ft. Acetate	15 0
5½in. Double play, 1800ft. Mylar	22 6	7in. Triple play, 3600ft. Mylar	58 6

P. & P. 1/- extra per reel, 4 reels and over Post Free

SPECIAL INTEREST ITEMS!

HIGH QUALITY EQUIPMENT CABINETS

Designed to take the Magnavox 363 Tape Deck and the Princess Auto Record Changer with space for amplifier and speaker (the motor board is ready cut out for the deck and changer). Soundly constructed from solid Afromosia wood with natural oiled finish. Removable hinged lid. Removable metal legs. Internal dimensions 26½in. x 14½in. x 5in. depth below motor board plus 4in. deep lid—16in. legs. Post 7/6.

LASKY'S PRICE £4. 19. 6

SINCLAIR SUPER MINIATURE KITS


THE MICRO-6 miniature radio only 1½ x 1½ x 1½in.	£2 19 6
THE SLIMLINE 2-transistor pocket radio	£2 19 6
THE MICRO-FM (tuner/receiver)	£5 19 6
THE X-20 20 watt P.W.M. amplifier	£7 19 6
Available ready built, tested and guaranteed	£9 19 6
THE X-10 10 watt amplifier and pre-amp	£5 19 6
Available ready built, tested and guaranteed	£6 19 6
THE Z-12 12 watt amp. and pre-amp, fully built	£4 9 6

LASKY'S RADIO FOR FINEST VALUE and COURTEOUS SERVICE

SERVICE IN GREAT BRITAIN AND HI-FI ENTHUSIASTS

LASKY'S RADIO

RECORD PLAYERS

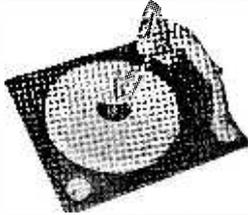

B.S.R. 4-Speed Autochangers

BRAND NEW AT LOWEST EVER PRICES

Brand new and fully guaranteed—complete with cartridge and stylus.

UA14 4 speed mains model	£4. 9.6
UA16 4 speed mains model	£4.19.6
UA16 9v. battery model	£5.19.6
UA20 4 speed mains model	£5.19.6

Add 5/- carriage and packing on each.

GARRARD AUTOCHANGERS NEW LOW PRICES!

Auto-Slim Mono	£4 19 6	A1000 with GCS cartridge	£6 6 0
AT6 Mono	£8 19 6	A2000 with GCS cartridge	£8 6 0
AT6 Stereo	£9 9 0	SRP12 with cartridge	£4 7 6
3000LM with stereo cartridge	£7 19 6	SRP10 Mains, with cartridge	£4 19 9
SP25 Mono	£9 19 6	SRP10 Battery, with cartridge	£4 19 6
SP25 Stereo	£10 19 6		
AT60 with stereo cartridge	£10 19 6	GARRARD BASES	
A70 less cartridge	£19 19 0	WB1	£8 12 8
A50 less cartridge	£9 14 6	WB2	£5 0 8

Postage and Packing on all above 5/-.

GREENCOAT RECORD PLAYER

2 speed model for 33 1/3 and 45 r.p.m. 6v. Battery operated. Complete with pick-up and fitted with crystal cartridge. Size only 7 1/2 x 6 in. Fitted with auto. stop and start.


LASKY'S PRICE 59/6 Post 2/6

207 EDGWARE ROAD, LONDON, W.2 Tel. PAD 3271
 33 TOTTENHAM CT. RD., LONDON, W.1 Tel. MUS 2605
 Both open all day Saturday. Early closing Thursday.

CONSTRUCTORS BARGAINS

NEW—LASKY'S MINIATURE TRANSISTOR AMPLIFIER MODULES

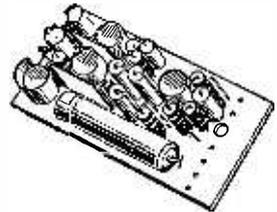Incorporating the very latest circuitry to provide high sensitivity and good quality in conjunction with extreme small size and compactness. High quality Newmarket transistors used throughout. All designed to operate on 9v. miniature battery.



TYPE PC1. 3 transistor. Input sens. 50mV, output 150mW, output imp. 40Ω, size 2 1/2 x 1 1/2 in. PRICE 27/6

TYPE PC2. 5 transistor. Input sens. 1mV, output 330mW, output imp. 15Ω, size 2 1/2 x 1 1/2 in. PRICE 22/6

TYPE PC3. 5 transistor. Input sens. 5mV, output 400mV, output imp. 15Ω, size 2 1/2 x 1 1/2 in. PRICE 25/-

TYPE PC4. 5 transistor. Input sens. 150mV, output 330mW, output imp. 15Ω, size 2 1/2 x 1 1/2 in. PRICE 22/6

TYPE PC5. 6 transistor. Input sens. 8mV, output 3W, output imp. 8Ω, size 5 1/2 x 1 1/2 in. PRICE 59/6

TYPE PC7. 6 transistor. Input sens. 8mV, output 1W, output imp. 8Ω, size 3 x 1 1/2 in. PRICE 39/6

Add 1/- on each for Post and Packing.

Mail Orders and correspondence to 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel.: STEpney Green 4821/2

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAME Block
 ADDRESS Caps.
 Please
 9.66

BRITISH NATIONAL RADIO SCHOOL

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!


SETS		1R5, 1R5, 1T4, 8S4, 8V4, DAF91, DF91, DK91, DL92, DL84. Set of 4 for 16/-, DAF96, DF96, DK96, DL96, 4 for 24/6	
1A7GT 7/8	10P13 8/6	DH77 4/-	EF91 3/6
1H5GT 7/8	12AT7 3/8	DH81 12/6	EF92 2/3
1N3GT 7/8	12AU6 4/8	DK33 7/8	EF97 7/6
1R5 4/8	12AU7 4/8	DK91 8/6	EP133 6/8
1S4 4/8	12AX7 4/8	DK92 8/6	EP184 6/8
1R5 3/8	12K7GT 3/6	DK96 6/6	EL33 6/8
3A5 6/8	12K8GT 8/6	DL33 6/8	EL38 11/8
3Q4 5/8	12Q7GT 8/6	DL35 5/-	EL41 7/8
8S4 4/8	20P2 9/-	DL92 4/8	EL42 7/8
5V4 5/8	20L1 11/8	DL94 5/8	EL84 14/-
5Y4G 4/8	20P1 9/-	DL96 6/-	EL90 4/8
6Y3GT 4/11	20P3 10/8	DY86 6/8	EL95 5/-
8Z4G/GT6/8	20P4 13/6	DY87 6/8	EM80 5/8
6X012 8/8	214GT/6	EAC80 9/-	EM81 7/8
6AL5 2/3	30C15 9/3	EAP22 7/8	EM84 5/8
6AM6 3/8	30C15 8/-	EB41 4/-	EM87 6/8
6AQ5 4/8	30F5 7/8	EB91 2/3	EY51 6/3
6AT6 4/-	30PL1 9/6	EB83 6/8	EY86 6/-
6BA6 4/8	30L15 10/8	EB041 6/8	EZ40 6/3
6BE6 4/3	30L17 12/-	EBF80 9/-	EZ41 6/8
6B76 5/8	30P4 13/6	EBF89 5/8	EZ50 3/8
6BW6 7/8	30P12 7/8	ECC04 6/8	EZ81 1/8
6FL3 3/8	30P19 13/6	ECC81 3/8	GZ23 12/6
6FL4 9/-	30PL1 11/8	ECC82 4/8	KT61 6/8
6F23 9/-	30PL13 10/8	ECC83 7/-	KT63 4/-
6K7G 1/8	35L6GT 4/8	ECC84 6/3	N18 5/8
6K8G 4/8	35W4 4/8	ECC85 5/8	N78 14/8
6K8GT 7/8	35Z4GT 4/8	ECC86 7/8	PC97 6/8
6L18 7/8	85A2 5/8	ECC82 6/8	PC84 5/8
6Q7G/GT	6063 12/8	ECC86 10/8	PCC89 9/-
	AZ31 8/8	ECC85 8/-	PC0189 9/-
6S17GT 4/8	B36 4/8	ECL42 8/8	PCF80 6/8
6V6G 3/8	B729 10/-	ECH81 5/8	PCF82 6/8
6V6GT 5/8	CL33 9/6	ECH84 9/-	PCF86 8/3
6X4 3/8	CY1 12/6	ECL80 6/-	PCF800 10/6
6X5GT 6/3	DAC32 7/3	ECL82 8/8	PCF801 9/8
7B6 3/8	DAF91 8/8	ECL86 7/8	PCF80 8/8
7B7 7/8	DAF96 6/-	EP39 3/8	PCL82 6/8
7C5 8/8	DCC90 6/8	EP41 6/8	PCL83 9/-
7H7 5/8	DF33 7/8	EF80 4/8	PCL84 7/6
7Y4 5/8	DF91 2/8	EF85 5/8	PCL85 7/8
9BW6 8/8	DF96 8/-	EF86 6/8	PCL86 8/8
10C2 11/8	DH76 3/6	EF89 4/6	PEN44 6/6
			UCH42 8/-
			UCH81 7/6
			UCL82 6/3
			UCL83 8/8
			UF41 6/8
			UF80 5/8
			UF89 5/8
			UL41 6/8
			UL44 15/-
			UL84 5/8
			UY21 8/8
			UY41 4/8
			UY85 4/8
			VP48 11/-
			W76 3/8
			W77 2/8
			Z77 3/8

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. CRE 7441

Postage on 1 valve 9d. extra. On 2-valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

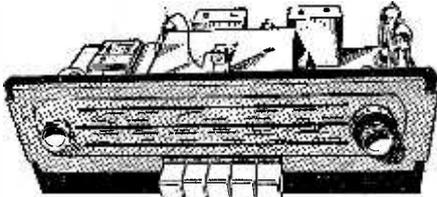BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £15.15.0 (Carriage Paid)



Chassis size 15 x 6½ x 5½in. high. New manufacture. Dial 14½ x 4in. in 2 colours, predominantly cream. 200-250v. A.C. only. Pick-up Ext. Speaker. Ac., E., and Dipole Sockets. Five push-buttons—LW, MW, SW, FM and Gram. Aligned and tested. O.P. Transformer Tone control 1000-1900M; 200-550M; 88-98 Mc/s. 6-17 Mc/s. EZ80 rect.; EC8S1, EF89, EABC80, EL84, ECC85. 3-ohm speaker required. **TERMS:** (Chassis) £4.0.0 down and 5 monthly payments of £2.10.0. Total H.P. price, £16.10.0. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. per yard. Circuit diagram, 2/6. Carriage to N. Ireland, 20/- extra.


NEW 6 PUSH-BUTTON STEREOGRAM CHASSIS. M.W.; S.W.1; S.V.2; V.H.F.; Gram; Stereo Gram. Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6½in. high. Dial cream and red. 15 x 3in. 190-550M; 18-51M; 60-187M; VHF 86-100 m/cs. Valves: ECC85, EC8S1, EF89, 2 x ECL86, EM84 and Rect. Price £19.19.0, carr. paid or £5.0.0 deposit and 5 monthly payments of 68/- . Total H.P. price. £20.15.0 Cream moulded escutcheon included.

TAPE AMPLIFIER FOR COLLARO OR MAGNA-VOX TAPE DECKS — 2 TRACK

Chassis 12½ x 5½ x 4½in. high. Plastic front panel "gold" finish—12½ x 4½in. 200-250 A.C. Record/Playback amp. switch; Off/On-Tone; Vol/Mic; Vol/Gram; Mic. Input; Gram. Input; Monitor; Speaker Sockets. Valves 6BR7; 12AX7; EM84; EL84; 6X4 Separate power pack. Complete amp. and power pack, £5.19.6 (6/- P. & P.). Resins covered cabinet fitted to take amplifier and Collaro Deck. 16½ x 17 x 9½in. high Sliding front for amp.; complete with two tweeter speakers; Tan, 75/- (plus 5/- rail charge). Cabinet and special brackets for adapting cabinet for Magnavox Deck 85/- (plus 8/- carr.), including tweeters.


SELF-POWERED VHF TUNER CHASSIS

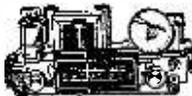Covering 88-95 Mc/s, Dims. 8 x 6 x 6in. high. Valves ECC85, EABC80 and 2-EF89 with metal rectifier. Mains transformer. Fully wired and tested **ONLY** £8.17.6 (carr. paid). Room dipole. 12/6. Feeder 6d. per yard.



The
SUPER 6

LONG & MEDIUM WAVE TRANSISTOR RADIO

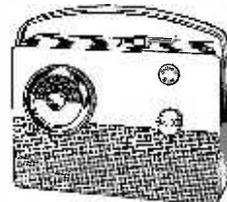

A quality radio available as a kit or ready-built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12.12.0 commercial model.

★ All new parts. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit ★ Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet 11 x 7½ x 3½in. ★ Vinyl covered in various colours. ★ 6 x 4in. speaker giving good bass and treble response. ★ Full instruction booklet, 2/-. Free with kit. ★ 1.1. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately.

Write for list, S.A.E. **COMPLETE KIT ONLY** £4.0.0 P. & P. 5/- **OR FULLY BUILT** £6.7.6. Tax and Carr. Paid.

TRANSISTORS AND DIODES

OC26, 7/8; OC44, 3/6; OC45, 3/6; OC71, 3/-; OCT2, 4/-; OC81, 3/6; OC81D, 3/6; OC83, 8/-; OC83, 3/6; OC169, 8/-; OC170, 7/-; OC171, 8/-; OC172, 8/6; AC127, 7/6; AF115, 8/6; AF116, 8/-; AF117, 5/-; AF118, 7/6; AF119, 7/6; WG4B, 9d.; OAS1, 2/6; OA79, 2/6; OA85, 2/6; BY100, 4/-. Post 4d. any quantity.

BATTERY ELIMINATOR for Transistor Radios requiring 9v. Fully smoothed (5000+1000mfd). 5 x 3½ x 1½in. overall. Tapped input for 200/10, 220/30, 240/50v. Output 9v. at 100ma. Good Regulation. Price 25/- (3/- P. & P.).

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.


(2 mins. from Station and Buses). Aldershot 22240

CLOSED WEDNESDAY AFTERNOON CATALOGUE 6d.

Bulk enquiries invited for Export.

ADAMIN
Micro Soldering Instruments

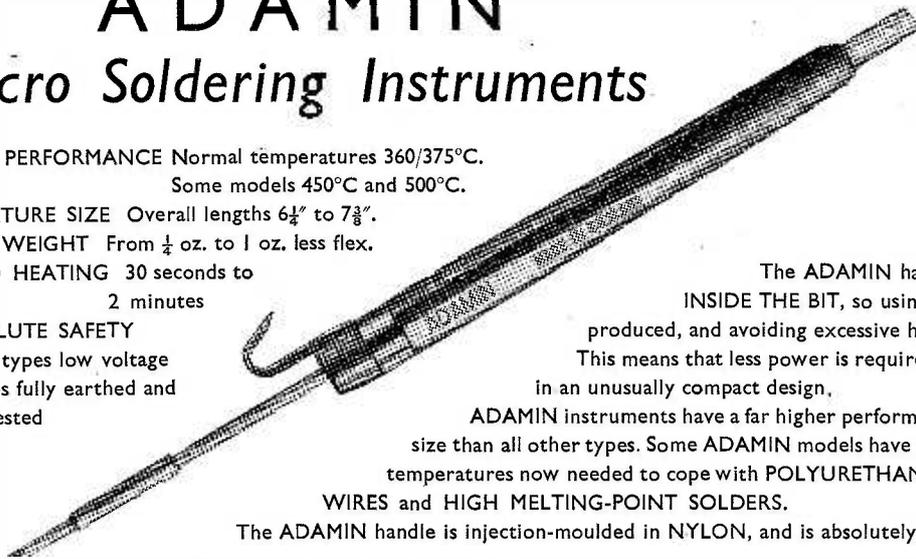- **HIGH PERFORMANCE** Normal temperatures 360/375°C. Some models 450°C and 500°C.
- **MINIATURE SIZE** Overall lengths 6¼" to 7⅝".
- **LOW WEIGHT** From ¼ oz. to 1 oz., less flex.
- **RAPID HEATING** 30 seconds to 2 minutes
- **ABSOLUTE SAFETY**
A & B types low voltage
C types fully earthed and flash tested



The ADAMIN has its element **INSIDE THE BIT**, so using all the heat produced, and avoiding excessive heat radiation. This means that less power is required and results in an unusually compact design,

ADAMIN instruments have a far higher performance for their size than all other types. Some ADAMIN models have the higher bit temperatures now needed to cope with **POLYURETHANE COVERED WIRES** and **HIGH MELTING-POINT SOLDERS**.

The ADAMIN handle is injection-moulded in **NYLON**, and is absolutely unbreakable.

Free details in brochure **SP10**.

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, Surrey

Telephone: **CROYdon 8589**

INCREASE YOUR KNOWLEDGE



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

CHOOSE THE RIGHT COURSE FROM:

RADIO AND TELEVISION ENGINEERING,
INDUSTRIAL TELEVISION, RADIO AND
TELEVISION SERVICING, ELECTRONICS,
COMPUTERS AND PROGRAMMING,
ELECTRONIC TECHNICIANS, SERVOMECH-
ANISMS, TELEMETRY, CLOSED CIRCUIT TV,
INSTRUMENTATION, AND PRINCIPLES OF
AUTOMATION.

ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers
C. & G. 'Telecommunication Techns'. Cert.
C. & G. Supplementary Studies
R.T.E.B. Radio/TV Servicing Cert.
P.M.G. Certificates. Radio Amateurs' Exam.

LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet Receiver and Transistor, Portable Signal Generator and High Quality Multitester. At the end of the course you have invaluable practical equipment and a fund of personal knowledge and skill. ICS Practical Radio Courses open a new world to the keen amateur.

THERE IS AN ICS COURSE FOR YOU


Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialised knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

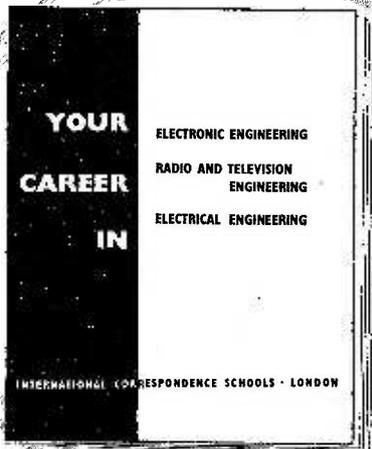You will receive the FREE ICS Prospectus listing the examinations and ICS technical courses in radio, television and electronics. PLUS details of over 150 specialised subjects.



PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS.....

.....

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEXT HOUSE, PARKGATE ROAD, London, SW11
9.66

BSR MONARCH UAI6 with FULL-FI HEAD

4-speed, plays 10 records, 12in., 10in. or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in., and 12in. records of the same speed. Has manual play position: colour, brown. Dimensions: 12½ x 10½in. Space required above baseboard 4½in., below baseboard 2½in. Fitted with Ful-Fi-turn-over crystal head.



£4.19.6
P. & P. 7/6.


Complete Amplifier Kit comprising E.C.L. 82 Mains transformer, metal rectifier, volume control, smoothing condenser, metal chassis, speaker, etc.
To the purchasers of the above changer only 19/6 plus 3/- P. & P.



POCKET MULTI-METER

Size 3½ x 2½ x 1½in. Meter size 2½ x 1½in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150 0-1,000. D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test prods, battery and full instructions. 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

Type E MOTOR

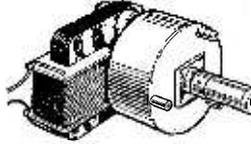

Small A.C. mains motor 230/250 volts complete with gearbox. 6 r.p.m. Price 15/- plus 3/- P. & P.
Similar to above motor but without gearbox. Price 9/6 plus 2/- P. & P.

8-WATT 5-VALVE PUSH-PULL AMPLIFIER & Metal RECTIFIER



Size: 9 x 6 x 1½in. A.C. Mains, 200-250v. 5 valves. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Output 8 watts at 5 per cent of total distortion. Separate bass and treble lift control. Two inputs, with controls for gram and mike. Output transformer tapped for 8 and 15 ohm speech coils. Built and tested, **£3.19.6**. P. & P. 10/-.

"MAYFAIR" 5-Transistor TAPE RECORDER



£11.11.0

Capstan-driven, battery operated. 7½ and 3½ ip.s. Precision made. Push-button controls. High quality 2½in. speaker. Push-pull circuit. Output 400mW. Frequency response: 200-7,000 k/s. Fast rewind. Up to 1 hour twin track playing time. Automatic crasing for re-recording. Dimensions: 8in. x 11in. x 3½in. Weighs only 7lb. Takes 5in. spools. plus 7/6. P. & P.




FIRST QUALITY P.V.C. TAPE

5½in. Std. 850ft. .. 9/-	5in. L.P. 850ft. .. 10/6
7in. Std. 1200ft. .. 11/6	3in. T.P. 600ft. .. 11/6
3in. L.P. 240ft. .. 4/-	5in. T.P. 1800ft. .. 25/6
5½in. L.P. 1200ft. .. 11/6	5in. T.P. 2400ft. .. 32/6
7in. L.P. 1800ft. .. 13/6	7in. T.P. 3600ft. .. 42/6
5½in. D.P. 1800ft. .. 13/6	4in. T.P. 900ft. .. 15/-

P. & P. on each 1/6, 4 or more post free.

40W FLUORESCENT LIGHT KIT

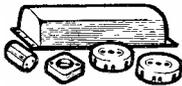

Incorporating GEC Choke size 8½in. x 1½in. x 1½in., 2 bi-pin holders, starter and starter-holder. P. & P. 4/6. **11/6**

Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 11½in. x 1½in. x 1½in., 2 bi-pin holders, P. & P. **17/6** starter and starter holder. 5/6

Twin 40W Choke instant start for 2 x 2ft. tubes 17/6. P. & P. 5/6.


MAGNAVOX COLLARO



Set of three Tape Deck Motors. These are made for 110 v. but suitable auto. transformer is supplied. Three motors 39/6. P. & P. 6/-.

CYLDON U.H.F. TUNER

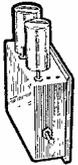
Complete with PC.88 and PC.86 Valves. Full variable tuning. New and unused. Size 4½ x 5½ x 1½in. Complete with circuit diagram. **35/-** plus 2/6 P. & P.



SILICON RECTIFIERS

250 v. P.I.V. 750 milliamps. Six for 7/6, post paid.

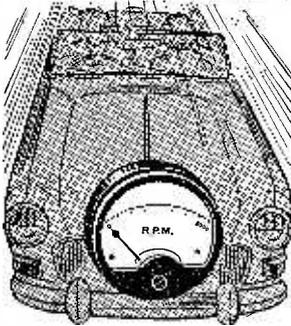MOTORISTS! — it's so easy to build your own



REV COUNTER

Fully Transistorised

for only **19/6**

Can be used for 4 or 6 cyl. engines. It would cost you at least £8 to buy one new, at today's prices, but with a few simple tools you can make one at a fraction of the price! This kit makes a modern efficient rev-counter that is essential to your engine's welfare: it contains moving coil movement and all parts including transistors and a circuit diagram. Maximum reading 8000 r.p.m. for 12 volt operation negative or positive earth. Send for your kit today, enclosing a P.O. 21/6 which includes 2/- postage—it will save you £'s and your engine.

OSCILLOSCOPE


for D.C. & A.C. Applications

Push-pull X amplifier. Flyback suppression; Internal Time-base Scan Wave form available for external use; pulse output available for checking TV line O/P Transformers, etc. Provision for external—I/P and C.R.T. Brightness Modulation. A.C. mains 200/250 v., **£18/18/-**. P. & P. 10/-.



3 to 4 WATT AMPLIFIER KIT

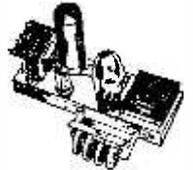Comprising chassis 8½in. x 2½in. x 1in. Double wound mains transformer, output transformer. Volume and tone controls, resistors, condensers, etc. 6V6 ECC81 and metal rectifier. Circuit 1/6, free with kit. **29/6** plus 4/6 P. & P. The above Amplifier built and tested. 10/6 extra.



POWER SUPPLY KIT

A.C. MAINS 200/250V
Incorporating "C" core type mains transformer, full wave metal rectification and smoothing condenser. Smooth output 250 v. 250 ma and 6.3 v. 4 amp. for Heaters.

25/- P. & P. 7/6




RADIO & T.V. COMPONENTS (ACTON) LTD.

21B HIGH STREET, ACTON, LONDON W.3

SHOP HOURS 9 a.m. to 6 p.m. EARLY CLOSING WEDNESDAY

Goods not despatched outside U.K. All enquiries stamped addressed envelope. Terms C.W.O.

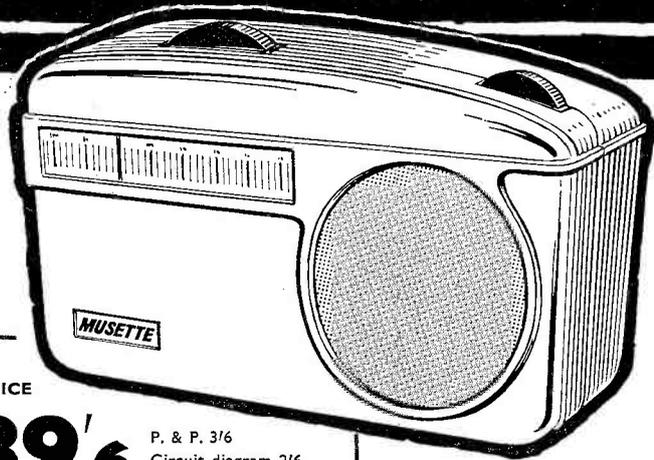MUSETTE 6 TRANSISTOR SUPERHET PORTABLE RADIO



PRICE


39'6

P. & P. 3/6
Circuit diagram 2/6.
Free with parts.

INCLUDING CARRYING STRAP.

- 2½" Speaker.
- 6 Transistors Superhet Output 200mw.
- Plastic Cabinet in red, size 4¾" x 3" x 1⅜"
- and gold speaker louver.
- Horizontal Tuning Scale.
- Ferrite Rod Internal Aerial.
- IF 470 Kc.
- All components, Ferrite Rod and Tuning Assembly mount on printed board.
- Operated from PP3 Battery.
- Full comprehensive instructions and point-to-point wiring diagram.
- Printed Circuit Board.
- Tunable over medium and long wave band. Car aerial and ear piece socket.

NEW TRANSISTORISED SIGNAL GENERATOR

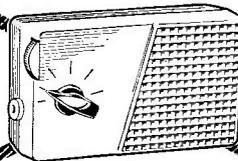

Size 5½" x 3½" x 1½". For IF and RF alignment and AF output 700 c/s frequency coverage 460 Kc/s to 2 Mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and **39/6** P. & P. Musette. Built and tested.

Elegant Seven Mk II

COMBINED PORTABLE *and* CAR RADIO

The Radio with the STAR features

- ★ 4in. Speaker.
- ★ 7-transistor superhet. Output 350mW.
- ★ Wooden cabinet, fitted handle with silver coloured fittings. Size 12½ x 8½ x 3½in.
- ★ Horizontal tuning scale, size 11½ x 2⅝in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. neutralisation on each stage 460 kc/s.
- ★ D.C. coupled output stage with separate A.C. negative feed back.
- ★ All components: ferrite rod and tuning assembly mount on printed board.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket. Full after-sale service.

ONLY **£4.4.0**

Plus 6/6 P. & P. Parts list and circuit diagram 2/6. FREE with parts.



POWER SUPPLY KIT

To purchasers of "Elegant Seven" parts, incorporating mains transformer, etc. A.C. mains 200-250v. Output 9v. 50mA. 7/6 extra.

ALL ENQUIRIES STAMPED ADDRESSED ENVELOPE

RADIO & TV COMPONENTS (ACTON) LTD
21C HIGH STREET · ACTON · LONDON · W.3


OPEN 9 a.m.—6 p.m. INCLUDING SATS. EARLY CLOSING WED. GOODS NOT DESPATCHED OUTSIDE U.K. TERMS C.W.O.

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

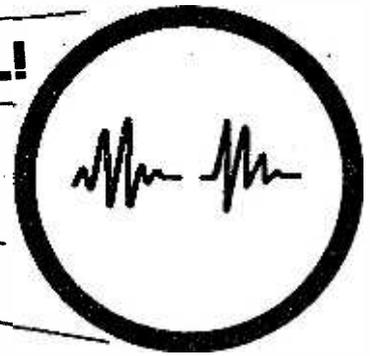


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

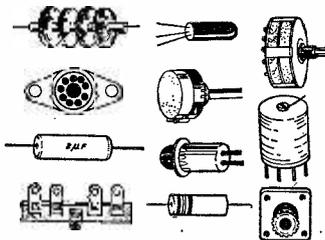complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

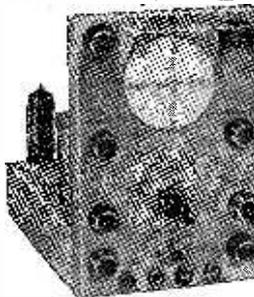a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND **CIRCUIT DIAGRAMS**

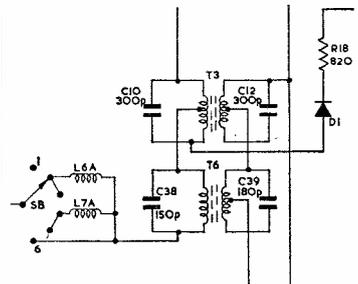

4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME BLOCK CAPS

ADDRESS PLEASE **PW9**

PRACTICAL WIRELESS

VOL 42 No 5

issue 715

SEPTEMBER 1966

TOPIC OF THE MONTH

The Right Formula?

IN a few weeks from now, the doors of the Earls Court Exhibition building will swing open and the turnstiles will begin clicking as the first visitors to the 1966 Radio Show pass into the halls.

After several years of travail and controversy, it may well be that at last some stability has been introduced into this important event in the calendar of the radio trade.

"Trade" is the key word. No longer have the organisers attempted to effect a compromise between a public exhibition and a trade show, a marriage in which incompatibility became increasingly manifest and has led to the inevitable divorce.

Changing patterns and balances dealt a death blow to the type of show which had prospered for so many years without much radical alteration, although many attempts were made to check the slide and to inject new zest into the enterprise. Either the signs were misread or the changes inadequate, for the Radio Show degenerated into the shambles of recent years with many companies mounting their own splinter exhibitions throughout London's hotel-land.

It emerged, however, that (1) Exhibitors found it more economical and profitable to restrict their shows exclusively to the trade, and (2) Foreign manufacturers could no longer be excluded. Arising from this, springs the 1966 Exhibition—a trade-only exhibition, with British and overseas manufacturers, under the same roof.

But although the conclusion is inevitably reached that a combined trade/public show is economically unviable is it, in fact, desirable or wise to abandon the traditional show?

Figures for attendances steadily declined. The public could see little more at the shows than they could in the radio shops and stores. Elaborate displays and entertainments were a financial luxury for the broadcasting organisations. And genuine radio enthusiasts found dwindling technical and hobbyist interest.

It seems, therefore, that the right solution has been found in dealing with the problem child of the industry. A few weeks hence, we will probably know.

W. N. STEVENS, Editor

NEWS AND COMMENT

Leader	319
News and Comment	320, 344
Practically Wireless <i>by Henry</i>	330
On the Short Waves <i>by John Guttridge and David Gibson, G3JDG</i>	352
Club Spot—The Civil Service Radio Society, GB2SM	364

CONSTRUCTIONAL

Four Channel Audio Mixer <i>by F. L. Thurston</i>	322
Modifications to the Ten-Five <i>by A. S. Carpenter, G3TYJ</i>	326
Modifications—Autostop for BSR Tape Decks . . . <i>by C. R. Marflow</i>	
. . . Alternative Frequency-Changer for the Progressive Short Wave Receiver	333
Short Wave Mains Two <i>by H. T. Kitchen</i>	334
Transistorised Indicators <i>by D. Bollen</i>	340
The Multitest—Part II <i>by R. D. Owen</i>	346
Crystal Controlled Oscillators and Transmitters <i>by F. G. Rayer, G3OGR</i>	356

OCTOBER ISSUE WILL BE PUBLISHED ON
SEPTEMBER 8th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes Rand London. Subscription rates, including postage: 36s. per year to any part of the world. © George Newnes Ltd., 1966. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

An Explanation

IN response to my letter entitled "Any Offers?" in the February issue of PRACTICAL WIRELESS, I have received innumerable offers from readers all over Great Britain.

However, I have received an anonymous letter admonishing me of alleged misdemeanour and advising me not to live on others' gift subscriptions! If readers would carefully peruse my letter, they will note that I never expected anything free, and my proposition was strictly reciprocal. In fact, I have so far spent a little over the cost of a year's subscription in answering my correspondents and if anyone still thinks that this is a hell of a way of living on others' free gifts, he must surely be an imbecile.

Incidentally, I have since been authoritatively informed that contrary to my belief, technical publications are exempted from exchange restrictions.

B. G. Kamath.

Bombay-52,
India.

Rabble?

IN reply to S. Peat on UHF and VHF Designs (P.W. March 1966).

A G8 licence may be an easier way to get a callsign, but to design, construct and operate equipment on u.h.f. is much more of a challenge.

At these frequencies, a hairpin can be a coil, two metal discs with an air gap a capacitor and the amateur has to be a highly proficient metalworker besides being able to solder.

This is the frontier of amateur radio communications and those of us who operate here are not following the well-worn pattern of proven design but are experimenting in the true spirit of amateur radio.

T. C. Challis, G8ALC.

Hull,
East Yorkshire.

Transistor Solo Organ

I SHOULD like to thank you for publishing the above-mentioned article. Having built this organ, I then rearranged the circuitry by the addition of another oscillator taking the range to $4\frac{1}{2}$ octaves and added several other tonal effects, feeding each oscillator to a channel of a stereo amplifier, producing the bass section from one speaker and the treble from another. The result is startling with two hand playing—even if with only one finger of each hand.

J. C. Mitchell.

Wallasey,
Cheshire.


NEWS AND..



THE DUKE OF EDINBURGH VISITS MARCONI TEST SITE

The Duke of Edinburgh flew by helicopter the other week to Marconi's test site at Rivenhall, Essex, where he saw Britain's "break-through" in space communications overseas. He inspected the Cable and Wireless Ltd.'s satellite earth station undergoing tests at Marconi's and which has since been dismantled and shipped to Ascension Island, where it is to be used for Apollo "man-on-the-moon" communications. The photograph shows the Duke of Edinburgh chatting to engineers at the site. In the background can be seen the satellite earth station.

LOUDSPEAKER FROM RANK WHARFEDALE

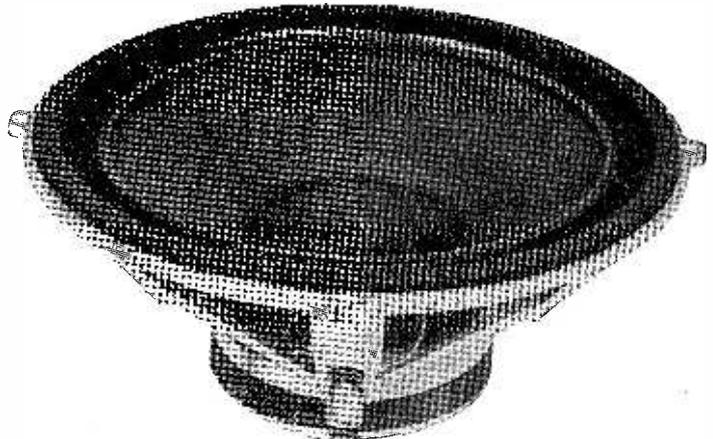

First shown at this year's Audio Fair, Rank Wharfedale Ltd. have introduced a new 12in. bass unit to their range.

Retailing at £11 15s. the W12/FRS replaces the W12/PST and is the first chassis using Flexiprene cone surround to be offered to the public.

Bass units with Flexiprene are used in the Linton and Dovedale systems. When mounted in a suitable enclosure the W12/FRS will produce clean firm bass down to 25 c.p.s.


Bass resonance is 23/28 c/s. Flux density, 14,000 oersteds; total flux, 156,000 maxwells; baffle opening, $10\frac{3}{4}$ in.; chassis diam., $12\frac{3}{4}$ in.; pole size, $1\frac{3}{4}$ in.; frequency range, 30-4,000 c/s and weight, 12 lbs.

RADIO TRADERS MOVE PREMISES

Radio Traders Ltd. (radio, electronic and electrical wholesalers) formerly of Tudor Place, W.1. have now moved to 8 Stephen St., Tottenham Court Rd., W.1 (Mus 4666). Radio Traders Ltd. have for many years served the trade with a wide variety of components. Enquiries for bulk and manufacturing quantities are invited.

...COMMENT

TWO NEW CROWN TAPE RECORDERS

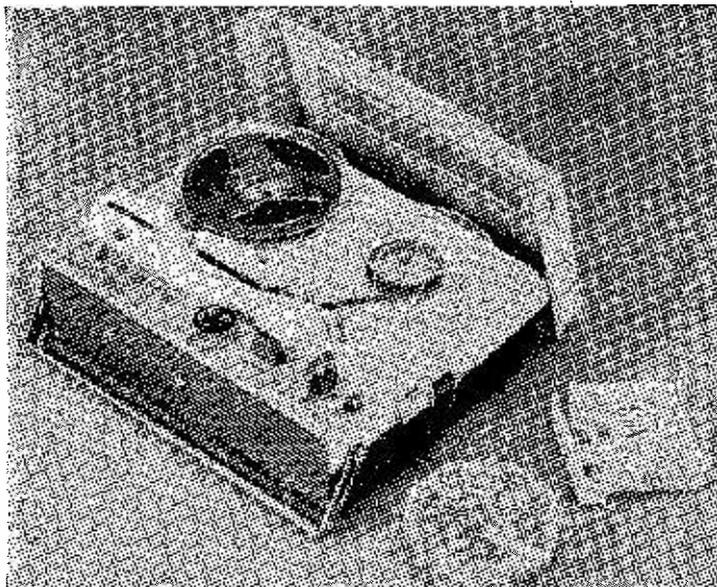

Two new Crown portable tape recorders, model CTR 5450 and model CTR 3000 are introduced by the Heddon-Smith Group Ltd.

Model 5450—shown in the photograph—operates from four U2 cells or a.c. mains, is twin track, and has two speeds $1\frac{7}{8}$ and $3\frac{3}{4}$ i.p.s. Incorporating 5 transistors it takes up to 5in. spools and has 700mW output. It weighs 7.9 lbs. and measures $11\frac{1}{2} \times 8\frac{3}{4} \times 4\frac{3}{8}$ in. Price, complete with remote control dynamic microphone and magnetic earphone, is 29½ guineas.

Model CTR 3000 incorporates 5 transistors, takes up to $3\frac{1}{2}$ in. spools and has an output of 800mW. It is twin track, has two speeds ($1\frac{7}{8}$ and $3\frac{3}{4}$ i.p.s.), weighs 5.1 lbs. and measures $8\frac{1}{8} \times 8\frac{9}{16} \times 3\frac{7}{16}$ in. Price complete with remote control microphone, magnetic earphone, 3in. reel and 3in. tape is 19 guineas.

UNISIL-CORED TRANSFORMERS AND CHOKES

Belclere Company Limited, 385/387 Cowley Road, Oxford, have for the past few years produced a range of Transformer Design Kits. Up to the present, this range has consisted of three types of core: Mumetal, Radiometal and Silicor. Belclere have now added a fourth material—Unisil—to this range.

For power transformers the use of Unisil allows for an increase in output of approximately 25% compared with the Silicor equivalent.

Two leaflets have been printed describing the full range of sixty-two Transformer Design Kits available. These include full dimensional details and necessary design data. Should any reader require copies of these leaflets or details of "one off" transformers, write to Belclere direct.

WEATHER SATELLITE STATIONS

An order for five satellite receiving stations has been placed with Hawker Siddeley Dynamics Ltd.

The stations will be used at meteorological offices around the world to collect information transmitted from American weather satellites. The receivers will pick up television-type pictures of the earth and cloud formations as seen by the satellites' cameras 875 miles up.

International Short Wave Club

We shall be pleased to send any readers a copy of "International Short Wave Radio" if they make application to the Secretary of the International Short Wave Club at the address below.
Arthur E. Bear.

100 Adams Gardens Estate,
London, S.E.16.

The Meaning of Amateur

YOUR correspondent Mr. R. Hasler has missed one point, and that is that amateur radio is still to a very large extent a "creative" hobby.

It is agreed that followers of other hobbies must of necessity purchase, say for example, a camera to enjoy the results to the full but nevertheless they get the creative end-product that they have set out to achieve.

I have never built a bike, nor knitted my own football socks (spare the thought!) but there are those amongst us who are unfortunately not in a position to enjoy the process of building their own equipment through some physical handicap but this does not detract from their "status" if you like, of amateur.

So, let us enjoy our QSO's during the coming years irrespective of whether our contact owns a "super XYZ at £2,000" or a "one-lung perker", meanwhile scanning the advertisement columns for hand-made bicycles and second-hand socks!

E. W. Bonson, G3JHY.

London,
E.12.

Mobile Registration

MAY I be permitted to wonder if any of your readers are the owners of distinguished motor vehicle registrations, for example, EF 86, ECC 83 or even perhaps, now that 1966 is with us, OC 81D?

C. P. Finn.

Tamworth,
Staffordshire.

Well, has anybody a distinguished registration number? We would be interested to hear of any.—Editor.

Correspondent Wanted

I WOULD like to correspond with somebody of my own age (14) who is interested in transistors and Hi-Fi.


Roger Murphy.

203 Bills Lane,
Shirley, Solihull,
Warwickshire.

More News and Comment on Page 344

4 CHANNEL AUDIO MIXER

F. L. THURSTON

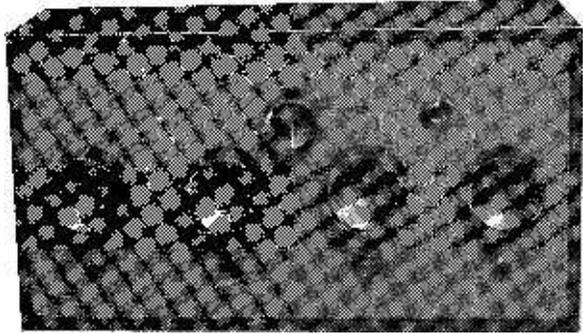

ONE item that is essential in any audio workshop is a good quality audio mixer, this item enabling a number of individual sound sources to be "mixed" or added together to give a single, composite output; the volume level of each of the input channels can be individually controlled, to emphasise or minimise the presence of each channel on the final output, as required.

In practice, audio mixers vary considerably in quality and price, ranging from the simple "passive" types at a couple of pounds each, to the higher quality "active" types, having seven or more transistors, at prices in the order of £17 or more. The unit to be described fits into this latter category as far as quality is concerned, although, being home built, it can be constructed for a fraction of the "normal" retail price.

TYPES AVAILABLE

In view of the diversity of mixture types that are available, it is worth while digressing a little and explaining the basic principles of mixer circuitry, before dealing with the constructional aspects of the actual mixer that forms the basis of this article.

An example of the so called "passive" mixer circuit is shown in Fig. 1 and, as might be expected, the unit consists of a purely resistive network. For the sake of simplicity, only a 2-channel circuit is shown, one input being applied across R1 and the other across R5, while the output is taken from across R3.

The input that is applied across R1 is also connected across the series combination R2-R3, and causes a current to flow in both resistors. If the input equals 1 volt, the resultant current in each of these two resistors will be $10\mu\text{A}$ since they total $100\text{ k}\Omega$. Similarly, the input that is applied across R5 is also connected across the series combination R3-R4 and, if a 1 volt

input is applied, a current of $10\mu\text{A}$ will result through these two resistors. Thus, each input causes a current to flow in the common resistor, R3, and the total current through this resistor is proportional to the sum of the input signals. In the above example, the total current through R3 will be approx. $20\mu\text{A}$. It may be noted that, although this circuit is referred to as a "mixer", it is in fact an adding circuit.

INTERACTION

A certain amount of interaction takes place in these simple circuits, but can be minimised in a number of ways. The attenuation factor between input and output could for example, be increased by reducing the value of R3, and thus reducing the interaction between inputs at the expense of loss of signal strength at the output. Alternatively, the attenuation factor can be increased by increasing the values of R2 and R4, but in this case the reduction in interaction is obtained at the expense of an increase in the unwanted "noise" generated by the circuit. Again, the interaction can be reduced by reducing the values of R1 and R5, so that the attenuation factor between (say) input 1 and the output is unchanged, but the attenuation between the output and input 2 is increased, the reduction in interaction being obtained, in this case, at the expense of a reduction in input impedance to the mixer circuit.

Either of these methods may be used to reduce the interaction between inputs but each has its own particular disadvantages, and all practical designs are a compromise between the different "evils". Never-the-less, this "passive" mixer circuit is widely used in electronics, and forms the basis of all audio mixers, including "active" types, in general use.

ACTIVE MIXERS

The next step up from the purely "passive" mixer involves adding an amplifier, using either valves or

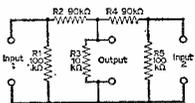


Fig. 1: Simple passive two-channel mixer.



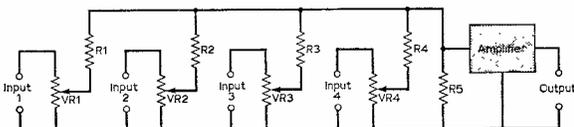


Fig. 2: This four-channel mixer has been made active by adding an amplifier.

Fig. 3: Block schematic diagram of the mixer described in this article shown on the right.

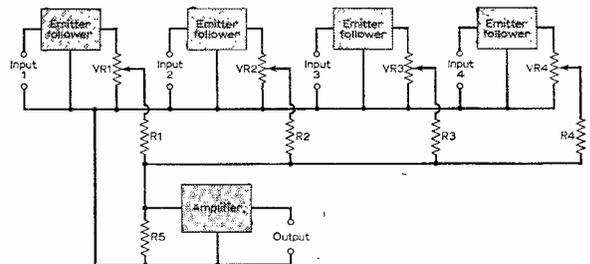

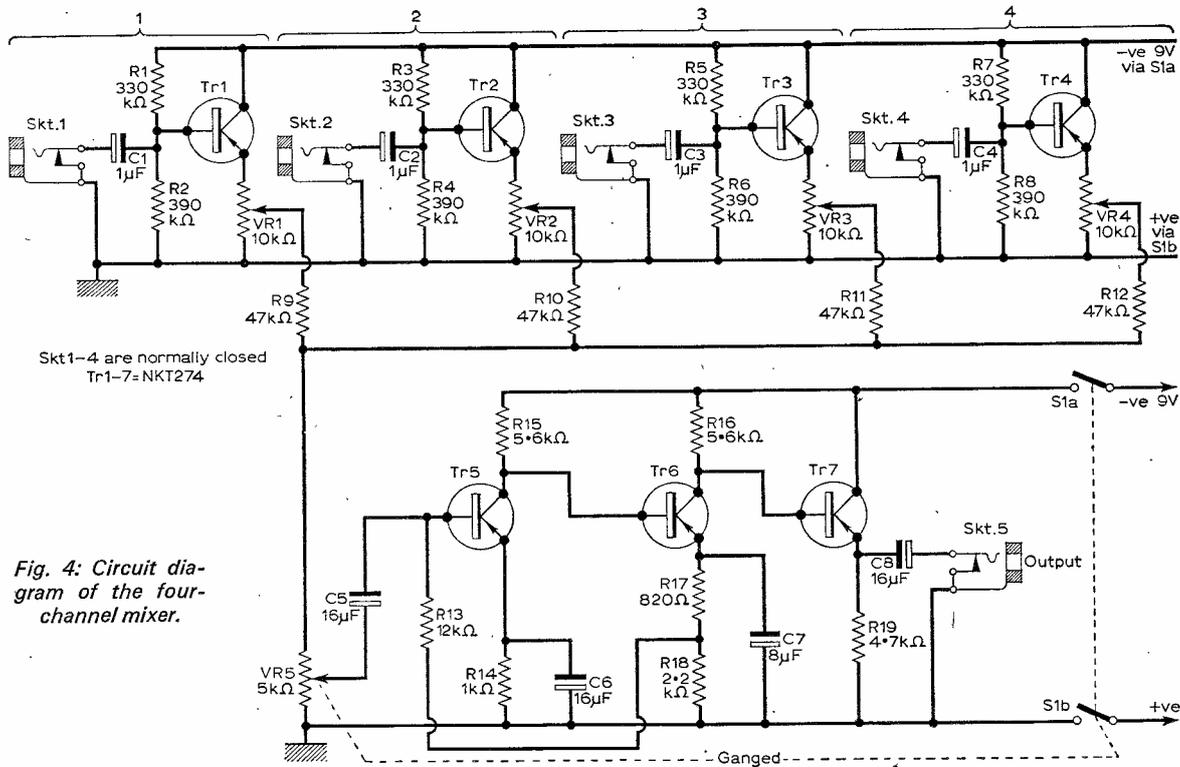

transistors, connected between the output of the passive network and the output terminal of the complete unit, the amplifier being used merely to make up for the attenuation that normally occurs between the mixer input and output. A simplified diagram of a 4-channel active type of mixer is shown in Fig. 2. As can be seen, each input is applied to a variable resistor, giving individual volume control, and the required proportion of input signal is fed, via a series resistor (R1-R4) to the common resistor, R5, where the signals are added or "mixed". The resulting complex signal is then fed to the amplifier, which compensates for the loss of signal strength that occurred in the mixing stage, and the final compensated signal is fed on to the output terminal.

Finally, we come to what may be called the "high quality" types of mixer. Here, the "passive" section of the circuit is designed to give minimum noise, attenuation, and interaction, at the expense of reduced input impedance, and the actual input impedance to the unit



is then increased artificially by interposing an emitter follower between the input socket and the input to the passive stage. A "block" diagram of a typical unit is shown in Fig. 3.

CIRCUIT DESCRIPTION

Each of the four emitter followers are identical. Taking input 1 as an example the signal is fed via blocking capacitor C1 to the base of Tr1, which is held at 4.5V by resistors R1 and R2 enabling input signals of up to approx. 8 volts peak-to-peak to be accommodated. The input impedance to each emitter follower is approx. 150k Ω , irrespective of the settings of the volume controls.

Each of the signals from the emitter follower stages is fed to the passive mixer, the "mixed" signal appearing across VR5. Transistors Tr5 and Tr6 are wired as common emitter amplifiers, using direct coupling to minimise the number of components. To give good d.c.

Fig. 5: Two views of the mixer. These should help the constructor locate the position of the major items.

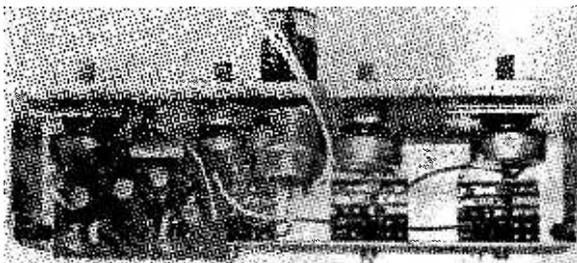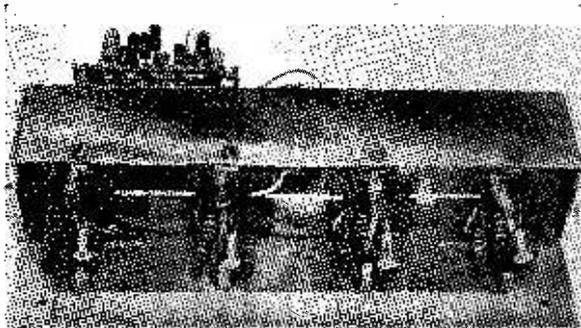

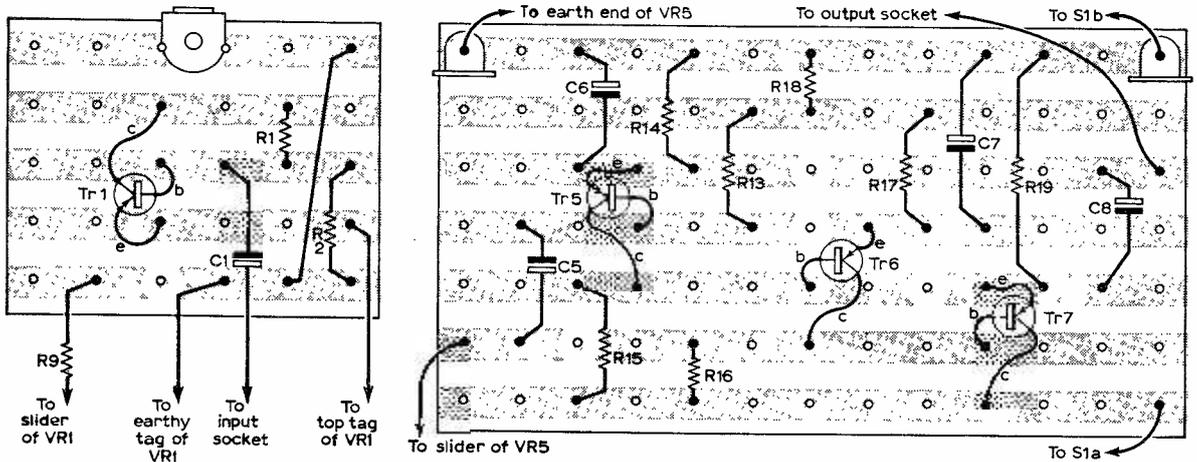


Fig. 6: One of the four identical emitter follower panels shown left along with the main amplifier panel.

and temperature stability, the base-bias to Tr5 is derived from the emitter circuit of Tr6, resulting in a d.c. negative feedback loop. Should the mean emitter current of Tr6 increase for any reason (such as an increase in ambient temperature), the negative voltage at the R17-R18 junction will increase, causing the mean emitter current of Tr5 to increase and the base voltage of Tr6 to fall.

The mixed and amplified signal that appears at Tr6 collector is directly coupled to the base of Tr7, another emitter follower stage, which gives a low impedance output.

CONSTRUCTION

Start construction by cutting the front panel to size. Then drill the holes for mounting the volume controls,

sockets, etc., as shown in Fig. 7. When this has been done, the panel can be finished off by covering it with Fablon or a similar self-adhesive plastic decorative material. At this stage, the five small jack sockets can be secured in place, the size and type being chosen to suit individual tastes.

Next, cut the three small brackets to size, and bend and drill them as shown. Screw the three brackets together, and secure the resulting assembly to the front panel by means of VR1 and VR4, after first cutting the spindles of all five variable resistors to the lengths required by the front panel control knobs that are to be used. The remaining three volume controls can also be secured in place at this stage.

Make the four small emitter follower panels, as shown in Fig. 6a, first cutting the panels to size, then breaking the copper strips as shown with the aid of a small drill or the special cutting tool, and finally soldering the electronic components in place. When complete, bolt these panels in place on the main bracket.

Similarly, make up the main amplifier sub-panel, as shown in Fig. 6b, and, when complete, bolt it in place on the main bracket by means of the two modified solder tags.

Now complete the circuit by wiring up the inter-connecting links, etc., as shown in Fig. 8, first soldering each of the input capacitors on the emitter follower panels to its respective input socket, and each of the


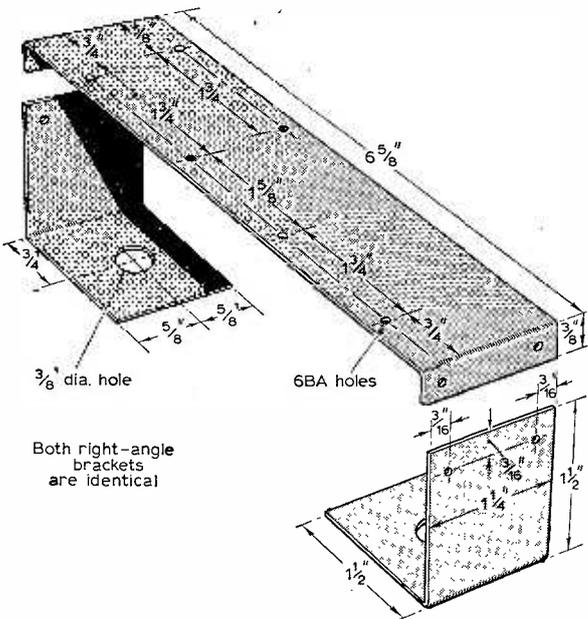


Fig. 7: Constructional details for the front panel and the brackets.

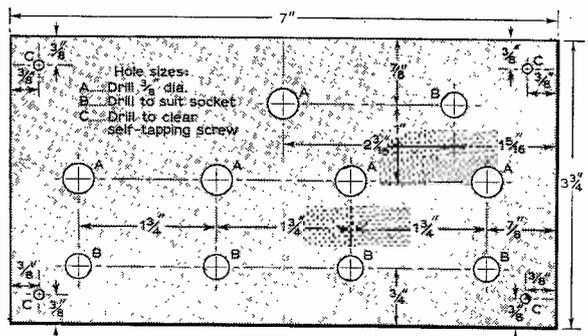

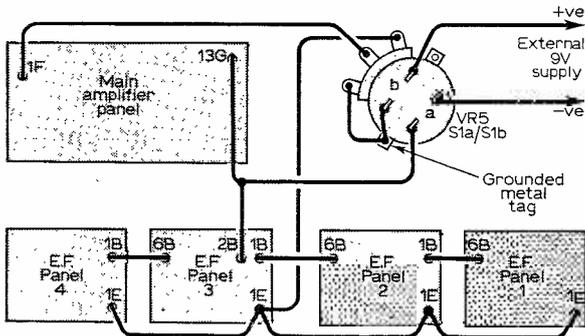


Fig. 8: Exploded view showing the internal connections.

47k Ω series resistors to the centre tag of its respective volume control. When the interconnecting leads have all been soldered in place, finish off by soldering a positive supply lead to the grounded metal tag on VR5, and solder one side of the negative line from the ON/OFF switch on VR5 to the relevant connections on the main amplifier panel and the emitter follower panel, and solder the external negative supply lead to the remaining tag on the ON/OFF switch.

The case can be made from either wood or metal, but must be provided with corner brackets to which the front panel can be screwed. When complete, the case may be covered with Fablon or a similar material.

★ components list

Resistors (all $\frac{1}{4}$ watt 10% carbon):

R1	330k Ω	R11	47k Ω
R2	390k Ω	R12	47k Ω
R3	330k Ω	R13	12k Ω
R4	390k Ω	R14	1k Ω
R5	330k Ω	R15	5.6k Ω
R6	390k Ω	R16	5.6k Ω
R7	330k Ω	R17	820 Ω
R8	390k Ω	R18	2.2k Ω
R9	47k Ω	R19	4.7k Ω
R10	47k Ω		

Capacitors (all sub-min):

C1	1 μ F 12V electrolytic
C2	1 μ F 12V electrolytic
C3	1 μ F 12V electrolytic
C4	1 μ F 12V electrolytic
C5	16 μ F 12V electrolytic
C6	16 μ F 12V electrolytic
C7	8 μ F 12V electrolytic
C8	16 μ F 12V electrolytic

Potentiometers:

VR1	10k Ω log	VR4	10k Ω log
VR2	10k Ω log	VR5	5k Ω log with switch
VR3	10k Ω log		

Transistors (Newmarket):

Tr1	NKT274	Tr5	NKT274
Tr2	NKT274	Tr6	NKT274
Tr3	NKT274	Tr7	NKT274
Tr4	NKT274		

Miscellaneous:

SKT1	Normally closed miniature types to suit individual requirements
SKT2	
SKT3	
SKT4	
SKT5	9 volt battery, Veroboard, wire, solder, tags, etc.

NEXT MONTH'S



COMMUNICATIONS T.R.F.

A highly selective and super-sensitive 6-stage unit covering 1.6-30 Mc/s. continuous in 3 switched bands. Receives 6 amateur bands, plus all short waves down to 10 metres and up to M.W. Light Programme. Completely self-contained, 12 x 8 x 7in.

GETTING GOING ON V.H.F.

This introduction to v.h.f. bands and techniques begins a new v.h.f. series.

IMPROVING TRANSISTOR RADIOS


How to improve the cheaper transistor set. Covers better a.g.c.; adding diode output socket; extra r.f. amplifier and audio amplifier stage; battery economy.

FIVE-WATT AMPLIFIER

A compact 5-transistor 5-watt transformerless amplifier, built on a single board, measuring only 3 $\frac{1}{2}$ x 2 $\frac{1}{4}$ x 2 $\frac{1}{2}$ in., with constructional details for preamplifier and mains power supply unit.

OCTOBER ISSUE ON SALE SEPT. 8th

ORDER YOUR COPY NOW!

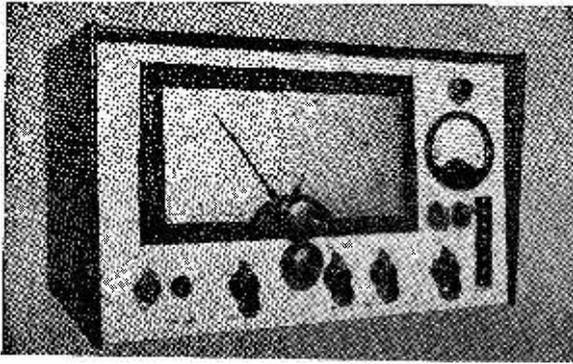

MODIFICATIONS TO THE '10-5' RECEIVER

A. S. CARPENTER G3TYJ

THE "Ten-Five" was described initially in the October and November, 1964, issues of PRACTICAL WIRELESS. A further article suggesting minor changes appeared in the April, 1965 issue and in the November, 1965, constructional details were given for converting the "front end" to a much more efficient band-switched system.

Tr1 and Tr2 form, with their associated components, a tunable front end converter, producing a 1.6Mc/s output. One coil transformer only for each stage is shown, but fuller details relating to the section may be found in the November, 1965, issue.

After amplification by Tr3, the signal passes to the second mixer/oscillator, the 470kc/s output being fed to a two-stage i.f. amplifier Tr5, Tr6. The i.f. signal is demodulated by D2. The diode D3 acts as a series noise limiter, while D1 is an a.g.c. damping diode. Tr7 is a feedback oscillator, functioning as b.f.o. The audio amplifier consists of driver Tr8 and push-pull output Tr9, Tr10.

I.F. MODIFICATIONS

The new double-tuned i.f. transformers are fitted at i.f.t.1, i.f.t.2, i.f.t.3 and i.f.t.4. Transformers

i.f.t.5 and T5 remain unchanged. Other circuit changes are made to the S-meter arrangement, the a.g.c. switching and the noise limiter circuitry. As far as possible, components bear their original references and most are identical. Some minor changes have been made, however, and a complete check is advisable. i.f.t. base connections are shown in the circuit diagram inset.

I.F. transformers 1 and 2 are tuned to 1.6Mc/s to feed transistor Tr4 and it may be noted that the fine tuner (TC4) which was previously connected to the front-end oscillator has now been moved and now may be used to vary the tuning of T4 slightly. T4 is normally fixed-tuned by means of C16, but TC4 proves additionally useful in cases where interference is experienced; it is also an aid to making c.w. and s.s.b. transmissions readable.

Damper diode, D1, is arranged to be non-conductive under weak or no signal conditions, its anode being held slightly negative with respect to its cathode by about 0.4V. If, with the a.g.c. switch set to "In" a strong transmission is tuned in, the base of Tr5 is driven in the positive direction and its collector current falls.

The resultant voltage change across R18 permits

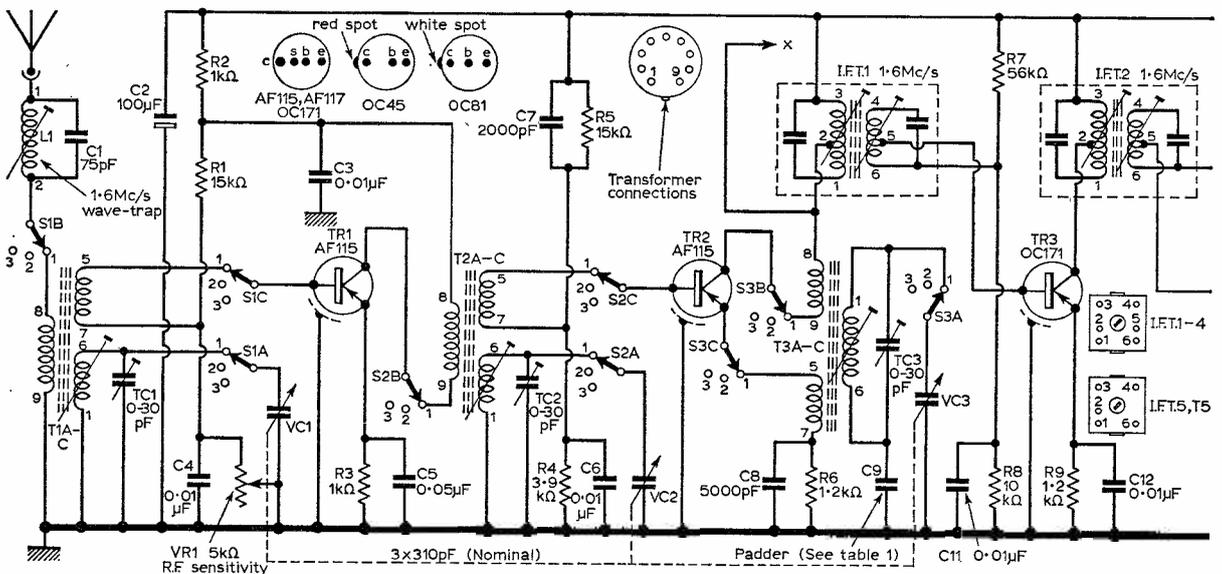


Fig. 1: Circuit of the bandswitched front end model. Only one transformer coil is shown in each stage in the interests of clarity.

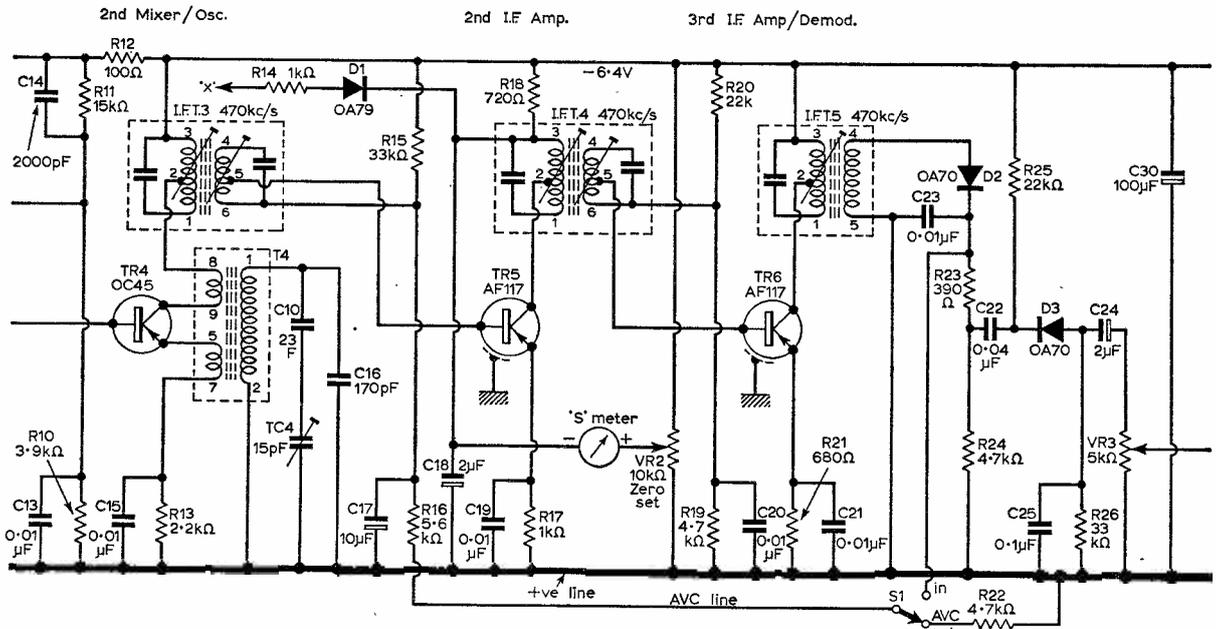


Fig. 2: The complete i.f. amplifier including second frequency changer/mixer.

the diode to conduct to damp the primary of the first i.f. transformer; the "S" meter balance as set by VR2, is also upset and the meter pointer moves across the scale in a forward reading direction by an amount depending on the strength of the received signal. The a.g.c. may be switched in and out irrespective of whether the b.f.o. is in circuit or not, switch S1 being in fact the item originally used in connection with the limiter. Here the revised limiter is left in circuit at all times diode D3 normally being conductive.

In the b.f.o. stage the pitch control is connected between the collector of Tr7 and the positive line yet is effectively across the main winding of T5 when S2 is closed due to C30.

Demodulated output is available at the slider of gain control VR3.

AUDIO STAGES

These are almost unchanged. R38 value is increased. C30 and C31 are transposed. Sockets for use with a monitor volt-meter are provided across C34 and are essential when the receiver is to be run from a healthy 12V car battery—which might easily provide up to 14V under certain conditions.

The voltage reading will also be governed to a certain extent by the position of S3 since when on phone considerably less current is demanded; 10V maximum should be allowed. No meter need be used if the receiver is to be powered by a dry battery—a PP9 for example—which may be connected to the pole of S5 and earth, in which case the remainder of the circuitry can be omitted.

MAINS/BATTERY

By adding the circuitry shown in Fig. 3, optional a.c. mains or car battery powering becomes possible. In the latter case the voltage must be monitored as described above and kept under control by means of VR4. Great care to obtain correct polarity is

required and connections should be in the sense shown.

When S5 is moved to position 2 the receiver may be powered from the domestic mains supply when S4 is closed to bring the panel-fitted neon to life. A d.c. potential of 9V is fed to positive and negative lines respectively and is obtained via mains transformer T8 and diodes D4 and D5 connected in a full-wave rectification circuit.

The receiver is prevented from functioning, however, if the rectifier diode cathodes are lifted from the positive line and this suggests a suitable muting circuit. No muting is necessary when the receiver is to be used purely for listening but when it is to work in conjunction with a transmitter some form of disabling circuit must be fitted to the front end or the r.f. transistors will be damaged.

In the prototype a flying lead is taken from pin 2 of the muting link socket to switch SF which is one section of a ganged Function switch contained within the transmitter. Pin 2 of the link plug is automatically grounded when SF is in the "Receive" and "Net" positions and as a result the receiver is made operative.

Immediately "Transmit" is selected, however, the receiver supply is "killed" by breaking the +ve connection. To enable the receiver to remain operative when no transmitter is in use the muting link plug may be moved to connect points 1 and 3.

It should be noted that this muting system will not function when S5 is at "Battery" although it might be possible to achieve it by lifting the +ve terminal of SK1 and connecting it to pin 2 of the link socket. To date, however, the "Ten-Five" has not been used with a transmitter under /M or /P conditions, mainly due to laziness!

ALIGNMENT

Alignment has been dealt with previously and consists mainly of getting the i.f. stages "on the nose". Use of a signal generator with its output

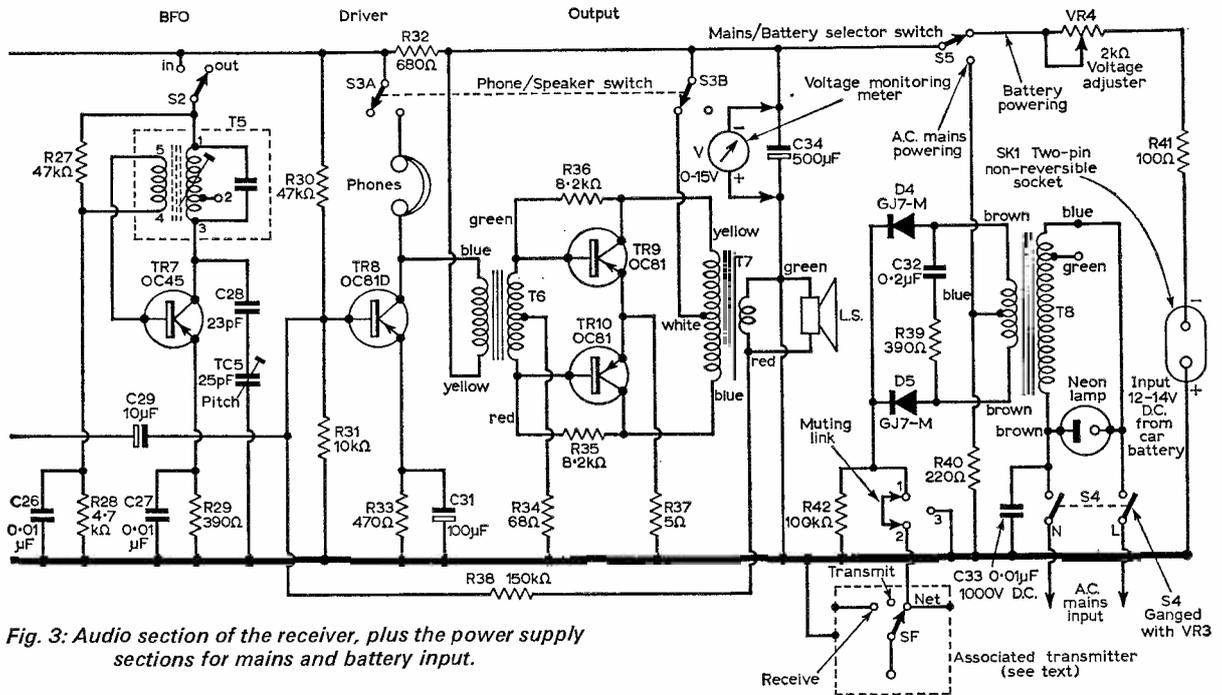


Fig. 3: Audio section of the receiver, plus the power supply sections for mains and battery input.

TABLE I

Front end coverages

Maker's Range No.	Blue/Yellow transformers		White transformers	
	Coverage		C9	Padder Pin No.
	Mc/s	Metres		
3	1.67-5.3	57-180	340pF	3
4	5.0-15.0	20-60	960pF	4
5	10.5-31.5	9.5-28	2000pF	6 ¹

¹Automatic 2nd harmonic mixing occurs on this range

TABLE II

Front end Tracking Points in Mc/s

Range	LF Band end	LF Tracking Point	HF Band end	HF Tracking Point
3	1.67	1.83	5.3	4.5
4	5.0	5.50	15.0	13.5
5	10.5	11.50	31.5	28.5

well attenuated is recommended, whereupon i.f.t.5, i.f.t.4 and i.f.t.3 in that order are peaked for maximum output at 470kc/s.

In the case of i.f.t.5 only one winding is tuned, whereas for all others two cores require adjustment. The core tuning the secondary—or base winding—should be the first one attended to in each case and as small differences will occur the operation should be repeated several times to make certain no improvements can be made.

Reset the signal generator to 1.6Mc/s and inject this to the base circuit of Tr4, with TC4 set to half capacity. The core of T4 is then adjusted to resolve the signal, after which i.f.t.2 and i.f.t.1 may be attended to; the generator output being fed to the collector circuit of Tr2. At all times the signal generator output must be kept as low as is possible.

The b.f.o. is then switched in and the modulation switched out at the generator. TC5 is set to half mesh and the core of T5 adjusted until oscillation is heard. Careful manipulation of the core will now produce the desired zero beat, when the trimming tool may be removed. Subsequent rotation of TC5 slightly either side of centre should result in a beat

note of adjustable pitch being heard.

Normally the a.g.c. should be switched out when the b.f.o. is in use as it will be when receiving c.w. and single sideband transmissions.

FRONT-END ADJUSTMENT

Referring to Fig. 1, three transformer coils are required for each stage and these are coded blue in the case of T1A-C, yellow in the case of T2A-C and white for T3A-C. These are supplied by Denco and conform to the maker's range numbers 3, 4, 5. Trimmers (TC) are adjusted at the h.f. tracking points and the coil cores are adjusted at the l.f. tracking points on each range. Details are given in Tables I and II, with the full frequency ranges made available on each band. The core of coil L1 should be adjusted to produce minimum output at 1.6Mc/s.

Should overloading or blocking result on receipt of strong signals, exchange the 5kΩ sensitivity control (VR1) for a 3.9kΩ fixed value resistor and fit instead an r.f. gain control in the form of a 100kΩ potentiometer wired as a variable resistor between one end of R1 (15kΩ) and pin 7, T1A-C. ■

★ components list for the 10-5 receiver

Note: Asterisks denote items not found in the original design

Resistors:

R1 15kΩ	R22 4.7kΩ
R2 1kΩ	*R23 390Ω
R3 1kΩ	*R24 4.7kΩ
R4 3.9kΩ	*R25 22kΩ
R5 15kΩ	*R26 33kΩ
R6 1.2kΩ	R27 22kΩ
R7 56kΩ	R28 4.7kΩ
R8 10kΩ	*R29 390Ω
*R9 1.2kΩ	R30 47kΩ
R10 3.9kΩ	R31 10kΩ
R11 15kΩ	R32 680Ω
R12 100Ω	*R33 470Ω
R13 2.2kΩ	R34 68Ω
R14 1kΩ	R35 8.2kΩ 5%
R15 33kΩ	R36 8.2kΩ 5%
*R16 5.6kΩ	R37 5Ω
R17 1kΩ	*R38 150kΩ
R18 720Ω	R39 390Ω
R19 4.7kΩ	R40 220Ω
R20 22kΩ	*R41 100Ω
R21 680Ω	*R42 100kΩ

Capacitors:

C1 75pF mica
C2 100μF electrolytic 12V.
C3 0.01μF ceramic or paper
C4 0.01μF ceramic or paper
C5 0.05μF paper
C6 0.01μF ceramic or paper
C7 2000pF ceramic
*C8 5000pF ceramic
C9 See Table I
*C10 23pF mica
C11 0.01μF ceramic or paper
C12 0.01μF ceramic or paper
C13 0.01μF ceramic or paper
C14 2000pF ceramic
C15 0.01μF ceramic or paper
*C16 170pF mica
C17 10μF electrolytic 6V.
*C18 2μF electrolytic 6V.
C19 0.01μF ceramic or paper
C20 0.01μF ceramic or paper
C21 0.01μF ceramic or paper
*C22 0.04μF paper
C23 0.01μF ceramic or paper
*C24 2μF electrolytic 6V.
*C25 0.1μF paper
C26 0.01μF ceramic or paper
C27 0.01μF ceramic or paper
C28 23pF mica
C29 10μF electrolytic 6V.
*C30 100μF electrolytic 12V.
*C31 100μF electrolytic 6V.
C32 0.2μF paper
C33 0.01μF paper 1000V.
C34 500μF electrolytic 15V.

Variable capacitors:

VC1/2/3 310pF (nominal) 3-gang tuning capacitor Jackson type "F".
*TC 0-30pF Beehive trimmers (9)

*TC4 15pF variable "Air Tune"
TC5 25pF variable "Air Tune"

Coils and Transformers:

*IFT1 I.F. transformer. Denco IFT18/1.6Mc/s
*IFT2 I.F. transformer. Denco IFT18/1.6Mc/s
*IFT3 I.F. transformer. Denco IFT18/470kc/s
*IFT4 I.F. transformer. Denco IFT18/470kc/s
*IFT5 I.F. transformer. Denco IFT14

The following are Miniature dual-purpose transistor coils by Denco.

T1A Range No. 3. Code Blue
T1B Range No. 4. Code Blue
T1C Range No. 5. Code Blue
T2A Range No. 3. Code Yellow
T2B Range No. 4. Code Yellow
T2C Range No. 5. Code Yellow
T3A Range No. 3. Code White
T3B Range No. 4. Code White
T3C Range No. 5. Code White

Other Transformers:

T5 BFO I.F. transformer. Denco IFT14
T6 Driver transformer, Ardente D3053
T7 Output transformer, Ardente D3027
T8 Mains isolating transformer. MT9. (Norcol or Osmor)
L1 Miniature dual-purpose valve type coil. Denco. Range 2. Code Red.

Semiconductors:

Tr1 AF115	Tr9 OC81	} matched
Tr2 AF115	Tr10 OC81	
Tr3 OC171	D1 OA79	
Tr4 OC45	D2 OA70	
Tr5 AF117	D3 OA70	
Tr6 AF117	D4 GJ7-M	
Tr7 OC45	D5 GJ7-M	
Tr8 OC81D		

Switches:*

*S1 Single-pole changeover
*S2 Single-pole changeover
*S3 2-pole, 2-way
*S4 D.P. On/Off with VR3
*S5 Single-pole changeover

Potentiometers:

VR1 5kΩ	VR3 5kΩ with switch S4
VR2 10kΩ	VR4 2kΩ

*Switch

*S1A/B/C	} (Front-end). 3-wafer, 3-pole, 3-way rotary (Radiospares, etc.)
*S2A/B/C	
*S3A/B/C	

Miscellaneous:

*Meter (Miniature panel type, 200μA f.s.d) G. W. Smith & Co. Tag strips (10) Lektrokit LK-2231. Aerial socket. Non-reversible 2-pin socket. Phone and L.S. sockets. Transistor mounting clips for OC81's (2). Jackson "Caliband" dial and drive. Epicyclic reduction drive. Control knobs, *3-way muting link socket, sockets for monitoring voltmeter, *Neon warning lamp, 250V, Paxolin sheet 9½ x 6 x 1/8 in., panel and cabinet material. *Oddment aluminium 4 x 3½ in. for coil pack, solder tags, etc.

practically wireless

commentary by **HENRY**

NOW and again, some journalist "does a Gower", usually citing the involved clauseology of politico-legal regulations, and thundering "How is the man in the street expected to understand this?"

The short answer, of course, is that the man in the street can jolly well stay there—leaving legal arguments to those trained in the unravelling of complexities. But sometimes the charge comes nearer home, as when technical writers are accused of making their contributions too specialised and their language too introvertive.

The fun really begins when these specialists deliberately set out to confuse. An hilarious example occurred recently in "Systems and Communications", where readers were invited to provide their descriptions of a "Yack-Yack". They were assured it was a genuine device and given



Yak-Yak or baby alama

a single-sentence hint of its construction and use—deliberately vague.

The response was amazing! Some believed it to be a walkie-talkie set, used in Tibet. Others said it was a "widget designed to

produce at the user's ears a sound field which exactly cancels unwanted external noise—such as nagging wives". Many plumped for a two-way telephone system for housewives, or even more way-out, mini-mothers-in-law. One brilliant inventor announced it to be a balanced Yaw-Assisted Cranium Kicker, which tended to keep the inebriated wanderer upright working on rectified brain waves.

The real Yack-Yack is almost as way-out as some of the inventive descriptions. It is an "undercom" for underwater communications between skin divers. It has a face mask with microphone and sound diffuser "to eliminate bubble noise", and a non-corrosive plastic case containing amplifier, battery and speaker. Range, 50 feet. Produced by Raytheon Ltd.

All very fine, but the absolute gem of a letter from S. E. Dinwiddy must be quoted in its entirety to prove my point:

"The information transponder receives dynamic aerial disturbance which it transduces into an electrical analogue which may be propagated along a conducting path to a corresponding installation. The device also contains the complementary transducer which re-transmits, providing conditions are acceptable, a recognisable imitation of the excitation presented to the remote installation.

The transducers are housed in a single module which rests on the second module of the installation when dormant. This second module contains an electro-acoustic transducer employed to attract attention in the event of a request for communication from a distant installation. It also contains a rotating perforated disc by the manipulation of which electrical impulses are transmitted to the complex intermediate apparatus by means of which communication may be effected to any one of a large

number of similar apparatus in other locations.'

The example shows clearly what can be done to render a commonplace object practically unidentifiable by a straightforward factual description, using "plain" technical language. No gobbledegook; no copywriters' garblese. Yet the technical man, at whom other technical writers



Down from their high horses

are aiming their contributions, finds it quite clear. Hence the stupidity of those who complain of the unintelligibility of technical articles, when they have not taken the trouble to learn the vocabulary.

We may mention that articles in *Practical* group magazines are deliberately written to be clear to both the technical man and the beginner, without boring the one by babytalk or confusing the other by unexplained terms. It often astounds me that some writers, whom I know personally, can get down so nimbly from their high horses of erudition and meet us common mortals elbow to elbow at the bar.

As a final note—the latest issue of *S & C* asks for descriptions of "A Whirley"—which is agile, weighs 833 tons and can be swept into position effortlessly. Henry can hardly wait for the answers.



PEAK SOUND


Cir-kit

**WHAT EVERY
CONSTRUCTOR,
EXPERIMENTER
AND DESIGNER
SHOULD HAVE**

THE NEW WONDER CIRCUIT SYSTEM

for making your own **INSTANT** circuits

Think what it means to be able to have just **ONE** printed circuit to the design you want and you will see immediately just how wonderfully **CIR-KIT** more than fills that long felt need. **CIR-KIT** is quick—you simply lay the self-adhesive strip on the board, drill holes for the components and you are ready to solder them in at once. **CIR-KIT** is clean—there are no chemicals, acids or etching processes involved. **CIR-KIT** is adaptable—you can amend a circuit again and again quickly and easily. Ideal for experimenters, this **CIR-KIT** is economical—the No. 3 Constructor's Kit advertised here contains enough material to make up about 10 circuits, and components may be closely mounted if desired. You can also repair damaged conventional printed circuits; you can experiment quickly and cheaply. In fact, **CIR-KIT** is the most revolutionary advance in circuit techniques since the printed circuit itself was invented and is already being used by many of the most famous houses in electronics.

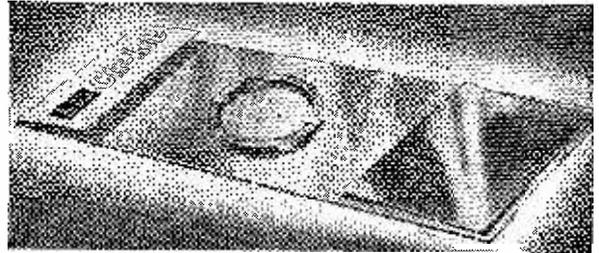


This is Kit No. 3 complete with instructions, board and material in sealed polythene pack ready for immediate use. Price 15/-

NO CHEMICALS, ETCHING
HEAT, SPECIAL TOOLS OR
RESTRICTIONS to LAYOUT

**Enough for about
ten circuits**


CIR-KIT KIT No. 3 contains high quality mounting board (Bakelite laminate E.10) size 6" x 12", 4" x 6" **CIR-KIT** special adhesive copper sheet and 15ft. of $\frac{1}{8}$ " **CIR-KIT** special adhesive copper strip. Land areas and special shapes are cut from the **CIR-KIT** sheet. The heat-resistant adhesive used will last indefinitely with normal use even if you strip and remount your **CIR-KIT**. With full instructions.

15/-

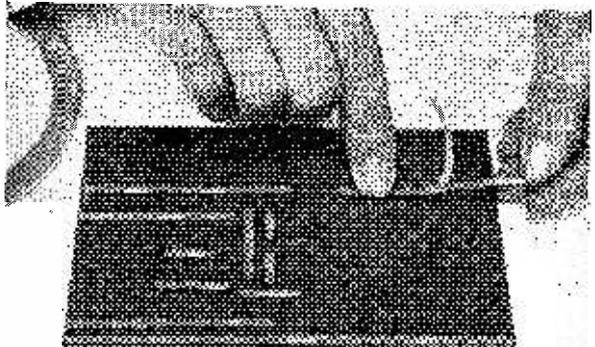

PROFESSIONAL IN EVERY WAY

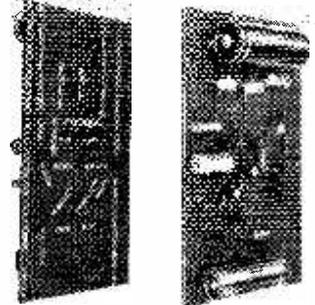Lay the strip and land areas, drill holes for the components and your circuit is ready for the components. Nothing could be simpler, yet the result is 100% professional.



Please quote Dept. PW.9 if you prefer not to cut coupon out.

PEAK SOUND Cir-kit

**PEAK SOUND (HARROW) LTD.,
10, ASHER DRIVE, ASCOT, BERKSHIRE**
Phone OEH47-3217

Distributors to the Wholesale and Retail Radio Trade in the U.K.

**TECHNICAL SUPPLIERS LTD.,
63, GOLDHAWK ROAD, LONDON, W12**

Phone 01-603-2581: 01-603-4794

To PEAK SOUND (HARROW) LTD., 10 Asher Drive, Ascot, Berks.
Please send CIR-KIT(s) for which I enclose
NAME
ADDRESS.....
BLOCK LETTERS PLEASE
PW.9

3-VALVE AUDIO AMPLIFIER MODEL HA34




Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, etc., wired and tested for only **£4.5.0** P. & P. 6/-.
£4.5.0

QUALITY RECORD PLAYER AMPLIFIER
This top quality amplifier (was used in a 29 gm. player) employs heavy duty double wound mains transformer. ECC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 in. w. x 2 1/2 in. d. x 5 1/2 in. h. Ready built and tested. PRICE 6/9/6. P. & P. 4/9.
ALSO AVAILABLE mounted on board with output transformer and 6in. speaker ready to fit into cabinet below. PRICE 8/9/6. P. & P. 5/9.

QUALITY PORTABLE R/P CABINET
Uncut motor board. Will take above amplifier and B.S.E. or GARRARD Autochanger or Single Record Player Unit. Size 18 x 14 x 8 1/2 in. PRICE £8.8.6. Carr. 7/6.

SPECIAL OFFER! FM/AM TUNER HEAD

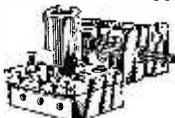


Beautifully designed and precision engineered by Dorrner and Wardsworth Ltd. Supplied ready fitted with twin '0005 tuning condenser for AM connection. Presligned FM section covers 86-102 Mc/s. I.F. output 10.7 Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly! Limited number also available with precision geared 3:1 reduction drive, 80/-, P. & P. 3/-.

Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly! Limited number also available with precision geared 3:1 reduction drive, 80/-, P. & P. 3/-.

STEREO AMPLIFIER

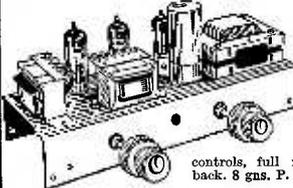Incorporating 2 ECL82s and 1 EZ80, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



ONLY £4.19.6
P. & P. 6/6

Super Deluxe version with ECL86 valves sep. bass & treble

controls, full negative feedback. 8 gns. P. & P. 6/6.


HSL 'FOUR' AMPLIFIER KIT

A.C. Mains 200V/250v., 4 watt, using ECC83, EL84, EZ80 valves. Heavy duty double-wound mains transformer with electrostatic screen. Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. Heavy negative feedback loop over 2 stages ensures high output, at excellent quality with very low distortion factor. Suitable for use with guitar, microphone or record player. Provision for remote mounting of controls or direct on chassis. Chassis size 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in. All components and valves brand new. Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. Supplied complete with 3 ohm output transformer. (No extras to buy.) PRICE 7/9/6. P. & P. 6/-. Comprehensive circuit diagram practical layout and parts list 2/6 (free with kit).
This kit is similar in appearance to HA34 but employs entirely different and advanced circuitry.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI

Peak output in excess of 1 1/2 watts. All standard British components. Built on printed circuit panel, size 6 x 3 in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET 114 or 81 Mullard OC81D and matched pair of OC81 o/p). 9 volt operation. Everything supplied wire, battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 45/-, P. & P. 3/-. Also ready built and tested, 52/6. P. & P. 3/-. A pair of TAIs are ideal for stereo.

10/14 WATT HI-FI AMPLIFIER KIT

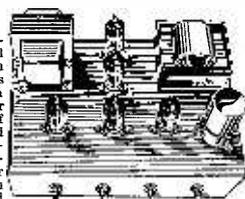

A Stylishly finished monaural amplifier with an output of 14 watts from 2 EL34s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for microphone and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86, and EZ80 rectifier. Simple instruction booklet 1/6. (Free with parts.) All parts sold separately. ONLY £79.8.6. P. & P. 5/6. Also available ready built and tested complete with std. input sockets, £85.0.0. P. & P. 8/6. Carrying case for above 28/6. P. & P. 7/6.

4-SPEED PLAYER UNIT BARGAINS

All brand new in maker's original packing.
SINGLE PLAYERS
B.S.E. TU/12 £3.9.6 Carr. 5/6.
GARRARD SP25 De Luxe £12.10.6 Carr. 5/6.
B.S.E. GU7 with unit mounted pickup arm. £4.18.3 Carr. 5/6.
AUTO CHANGERS
Latest B.S.E. UA26 Super slim £6.2.6
GARRARD Antoslim £5.10.0
GARRARD AT6 £9.10.0 Carr. 6/6 on each.
All the above units are complete with t/o mono head and sapphire stylus or can be supplied with compatible stereo head for 12/6 extra.

WELL-KNOWN MAKERS SURPLUS! ONE TRANSISTOR PRE-AMP.

Suitable for use with Medium or High Impedance mikes, guitars, gram pickups, tape decks etc. For operation from 200/300 volt H.T. rail or 9 volt battery. Gain approx 14:1. Fully isolated input by Mu-Metal screened transformer. Size 4 1/2" x 1" x 1". Ready built complete with full circuit diagram and instructions. ONLY 15/-. Post free.
MINIATURE PRECISION AIR-SPACED TWO GANG TUNING CONDENSER. 176 + 176 p.F. size 1 1/2" w. x 1" d. x 1 1/2" h. with vanes open. Built in trimmers 5/-, P. & P. 1/-.

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon
Tube Station

HARVERSON SURPLUS CO. LTD.
170 HIGH STREET, MERTON, S.W.19 CHERYWOOD 3985
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES
QUOTED APPLY TO U.K. ONLY.
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.

LATEST RADIOGRAM CABINETS £9.10.0.




Brand new long low design in veneered English walnut, dia. 40 x 16 x 15 1/2 in. Carr. 30/-. Also Mini Gram Cabinets £3.0.0. Radiogram/Cocktail Cabinets (Personal Shoppers.) Free List.

RESISTORS, 5/- per 100. New. Mostly High Stabs. Assorted. P. & P. 2/-. Overseas 3/6.
VALVES 4/- per 100. Assorted TV and Radio. Surplus ex-rental dismantled receivers. Post 4/6. Send for list.
RECORD PLAYER CABINETS, 49/6. Latest designed covered cabinets. Takes any modern Autochanger.
SINGLE PLAYER CABINETS, 10/6. P. & P. 5/6

EX-RENTAL TELEVISIONS

17 in. — £11.10.0

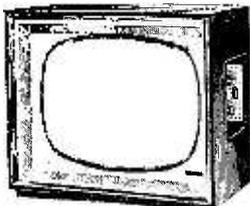12 months' 3 star Guarantee
★Tube ★Valves ★Components
FREE ILLUSTRATED LIST
Channels for all areas
Demonstrations daily from Large Selection.
Personal collection or Insured
17 in. 30/-.



TWO-YEAR GUARANTEE On all our slimline TVs, send for free list.

TWO-YEAR GUARANTEED TUBES

14 in. 59/6

17 in. 79/6

21 in. and all Slimline Tubes 99/6




100% REGUNNED
Add 10/- or old tube.
Carr. 10/6.

Ex-Maintenance Tested Tubes
17" 35/- 14" 15/-
Most Makes and Types
Carr. 5/-

DUKE & CO. (LONDON) LTD.
621/3 Romford Road, E.12 ILF 6001-2-3

R S G B AMATEUR RADIO HANDBOOK

Third Edition

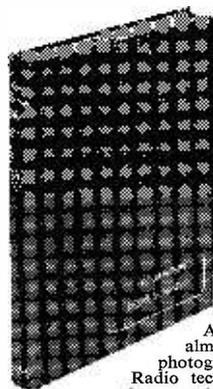

An invaluable volume of 544 pages, containing almost 700 circuits and charts, with over 100 photographs, and covering the whole field of Amateur Radio techniques from fundamentals to u.h.f. transmitters, aerials, test equipment, single sideband, propagation, etc. Each of the 22 chapters contains much information in suitable form for beginners to experienced amateurs and radio enthusiasts.

MORE THAN 30,000 COPIES ALREADY SOLD

Bound in maroon, buckram linson. Price 34s. (by post 36s.6d.) and \$5.50 post paid in USA and Canada.

Further details of other R S G B publications, information about membership of the society, including a free copy of the monthly R S G B BULLETIN, and the Amateur Radio Handbook may be obtained from the publishers:

RADIO SOCIETY of GREAT BRITAIN

Dept. PW, 28 Little Russell Street,
London, W.C.1. HOLborn 7373, 2444


MODIFICATIONS

To add autostop facilities to a BSR tape deck . . .

A PHOTOCELL plus a couple of inexpensive transistors, a lamp and a relay are all the components needed to add autostop facilities to a BSR tape deck. None of the components are critical and most readers should already have the items at hand. The relay will probably cause the most difficulty as it has to disconnect the power (mains voltage) to the tape motor.


Almost any photocell will do (the ORP12 is an example) and can be anchored by one of its lead wires to the pinch wheel assembly—see the accompanying illustrations. The lamp (a tiny “pea” bulb) is also anchored to the pinch wheel assembly, but in a position which puts the tape between it and the photocell.

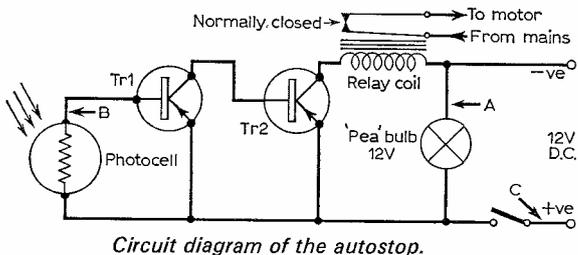With the tape running from one spool to the other, the light to the photocell from the “pea” bulb is blocked by the tape and the circuit is



inoperative. When the leader portion of the tape (the translucent part at either end of the tape) passes between the photocell and lamp there is sufficient light to fire the photocell. This will switch on the control transistor Tr1, which in turn switches the other transistor on, allowing maximum current to flow through the relay coil which causes it to operate and break the power supply connections to the tape motor.

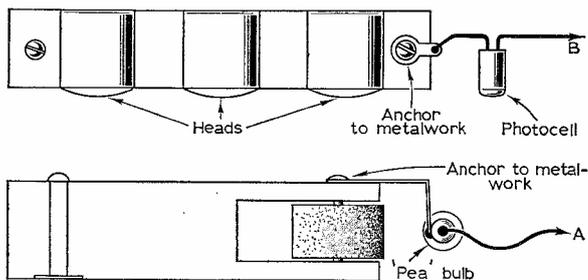
Since the pinch wheel is not brought up to the tape on fast wind, the sensitivity of the circuit is not so high as the lamp is further away from the photocell and the circuit will not operate until all the tape has passed the photocell.



Location information for the photocell and the “pea” bulb.

The transistors are not at all critical and almost any p-n-p device can be used in the Tr1 position. In the other position, a power transistor is needed since it has to be able to draw enough current to operate the 12-volt relay. You may find it necessary to include another transistor to increase the sensitivity to the desired level. If this is the case, it should be inserted between Tr1 and Tr2: connecting the base to the collector of Tr1 and the emitter to the base of Tr2. The author used an OC72 in the Tr2 position.

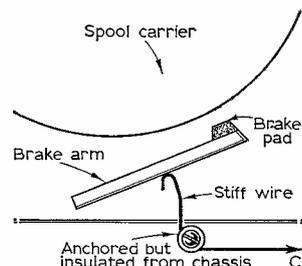
Power for the circuit is taken from a 12-volt battery, via a simple switch on the brake arm on the right-hand spindle which isolates the circuit when the control lever is in the central position.



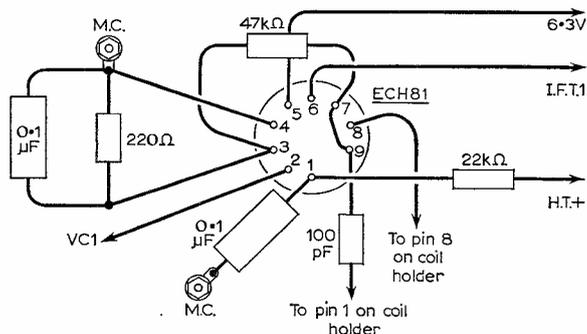C. R. Marflow

Alternative Frequency-Changer for the Progressive Short Wave Receiver

Since publishing the Progressive Short Wave Receiver in the February issue, the 12AH8 triode/pentode valve specified for the front end has become difficult to obtain. An ECH81 may, however, be used in the V1 position, but the valve base wiring has to be modified and R1 has to be altered to 22k Ω .



The wiring alterations to the valve base are as follows: remove the chassis connection to pin 5 and connect to the 6.3V heater line; disconnection pin 9 from the heater line and connect it with a short lead to pin 7 on the same base. The diagram shows valve-holder V1 modified for an ECH81.

THE receiver to be described was designed to provide efficient but inexpensive reception of the short wave bands without the use of cumbersome batteries which sooner or later (and usually at a most inconvenient time) require replacement.

The disadvantage of any basic t.r.f. is that it is relatively insensitive and not very selective, and ways and means have had to be sought to improve both state of affairs. The universal method is by feeding a portion of the amplified signal back to the grid and reamplifying it ad nauseum! In Fig. 1 this function is performed by L3 which is the reaction coil, and which must be connected so that the feedback is positive; i.e., in phase with the signal at the grid of V1.

The feedback must be made variable so that it can at all times be kept just, and only just, below the point of oscillation at which point both sensitivity and selectivity are at optimum. There are two ways of performing this function, one is by making the trimmer TC1 a variable and using it to adjust the reaction, and the other (which is used in this design) in which TC1 is adjusted initially and then subsequent reaction is controlled by the potentiometer in the screen grid of V1. By varying



the potential applied to the screen of V1 we can vary the gain much more smoothly.

Referring to VC1, the greater the band-width covered and the smaller the separation between adjacent stations for every degree of rotation, making it extremely difficult to separate stations who may be separated by only a few kc/s or so. Fortunately, the addition of another tuning capacitor connected in parallel with the main tuning capacitor (VC1), and having a total capacity much less than the former, can considerably assist tuning. The frequency shift is therefore related to the difference in capacity between the main or bandset capacitor and the ancillary or bandspread capacitor.

The anode load of V1 is composed of an r.f. choke and a resistor R1 in series. R.F.C. forms the r.f. anode load across which the feedback voltage is developed. Its inductive reactance is very high to

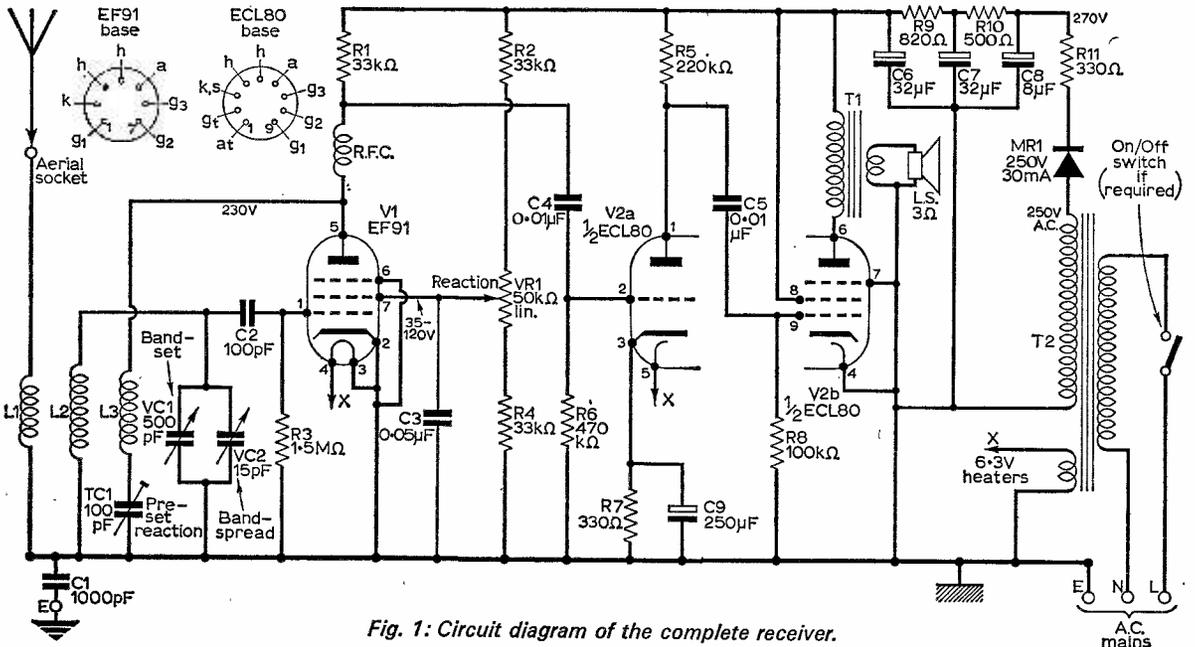


Fig. 1: Circuit diagram of the complete receiver.



LAFAYETTE HA-43 COMMUNICATION RECEIVER

7 valves plus Rectifier. 4 Bands, 550 kc/s-31 Mc/s. "S" Meter—BFO—ANT—Band-spread Tuning. 200/250v. A.C. Brand New 24 Gns. Carr. paid.

LAFAYETTE HA-230 AMATEUR COMMUNICATIONS RECEIVER

Supersedes model HE-30. 8 valves + rectifier. Continuous coverage on 4 bands. 550 Kc/s. 30 Mc/s. Incorporates 1 RF & 2 IF stages. Q Multiplier, B.F.O., ANL, "S" meter, Electrical bandspread, Aerial trimmer, etc. Supplied brand new and guaranteed. £33. S.A.E. for full details. Also available in semi Kit Form, 25 Gns.




LAFAYETTE HA-55A AIRCRAFT RECEIVER

108-136 Mc/s. High selectivity and sensitivity. Incorporates 2 RF stages including 6CW4 Nuvistor 8 tubes for 11 tube performance, solid state power supply, adjustable squelch control, slide rule dial, built-in 4in. speaker and front panel phone jack. 220/240V. A.C. Supplied brand new and guaranteed £19.7.6. Carr. 10/-.

HAM-I COMMUNICATION RECEIVER

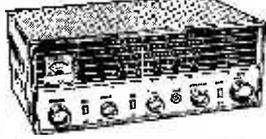5 valve superhet receiver covering 550 kc/s—30 Mc/s on 4 bands. Special features include slide rule dial. Bandspread tuning. "S" Meter. B.F.O. Built-in 4in. speaker. Operation 220/240 v. A.C. Brand New with handbook 16 GNS. Carr. 10/-. S.A.E. for details.



MAIN LONDON AGENTS FOR CODAR EQUIPMENT

All items available as advertised.

SINCLAIR TRANSISTOR AMPLIFIERS

Z12 Amplifier 89/8; P23 Power Pack 79/8; X10 Amplifier Built £6.19.6. Kit £5.19.6; X10 Power Pack 54/-; X20 Amplifier Built £9.19.6. Kit £7.19.6; X20 Power Pack £4.19.6. Micro FM Radio Kit £5.19.6. Micro 6, 59/8; Micro amp 23/6; Micro Injection 27/6. Post paid.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM.

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.10.0 pair. P. & P. 3/6.



LAFAYETTE 2-WAY RADIOS

Super quality. Brand new and guaranteed. 3 transistor £7.10.0 pr. 6 transistor £17.10.0 pr. 10 transistor with range boost £22.10.0 pr. Post extra.



These cannot be operated in U.K.

VOLTAGE STABILIZER TRANSFORMERS

Input 80-120v. and 160-240v. Constant output 110v. or 240v. 250 watts. Brand New. £10.10.0. Carr. 7/6.



VARIABLE VOLTAGE TRANSFORMERS

Brand New — fully Shrouded. Input 230v. 50/60 c/s. Output 0-260 Volts.
 1 Amp £41.00
 2.5 Amp £5.17.6
 5 Amp £9.00
 8 Amp £13.10.0
 10 Amp £17.00
 12 Amp £19.10.0
 20 Amp £22.10.0
 2.5 Amp Portable Metal Case with Meter, Fuses, etc. £9.17.6.




SILICON RECTIFIERS

209v. PIV, 200mA 2/6
 400v. PIV, 3 amp 7/6
 1,000v. PIV, 650mA 6/6
 800v. PIV, 300mA 5/6
 800v. PIV, 5 amp 7/6
 400v. PIV, 500mA 3/6
 70v. PIV, 1 amp 3/6
 150v. PIV, 165mA 1/-
 Discounts for quantities. Post extra.

TEST EQUIPMENT

PORTABLE OSCILLOSCOPE CT-52

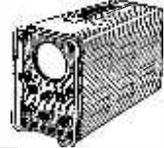A compact (9in. x 5in. x 16in.) general purpose scope T/B 10c/s-40 kc/s. Band width 1 Mc/s. Mullard DG 7/6 2 1/2in. CRT. For operation on 200/250v. A.C. Supplied complete with metal transit case, strap, test leads, and visor hood. Brand new, £22.10.0 Carr. 10/-. Supplied complete with instructions.



OS/8B/U OSCILLOSCOPES

High quality Portable American Oscilloscope, 3in. c.r.t. T/B 3c/s-50 kc/s X Amp: 0-500 kc/s Y Amp: 0.2 Mc/s. Power requirements 105-125v. A.C. Supplied in brand new condition, Fully tested. £25. Carr. 10/-. Suitable 230-115 v. Transformer, 15/6.



ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPE

Time base 2 c/s-750 kc/s. Calibrators at 100 kc/s and 1 Mc/s. Separate Y1 and Y2 amplifiers up to 5.5 Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. £22.10.0 Carrage 20/-.

TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated. Variable 3 dB attenuator. Operation 200/240v. A.C. Brand new with instructions. £12.10.0. P. & P. 7/6. S.A.E. for details.



LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 PF—2,000 MFD, 2 ohms—200 Megohms. Also checks impedance, turns ratio insulation 200-250 v. A.C. Brand New £15. Carr. 7/6.


LAFAYETTE NUVISTOR GRID DIP METER

Compact, true one hand operation. Frequency range 1.7 - 180 Mc/s. 230v. A.C. operation. Supplied complete with all coils and instructions. £12.10.0. Carr. 5/-.



TE22 SINE SQUARE WAVE AUDIO GENERATORS

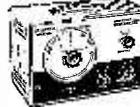Sine: 20 cps to 200 kc/s. on 4 bands. Square: 20 cps to 30 kc/s. Output impedance 6,000 ohms. 200/250v. A.C. operation. Supplied Brand New and guaranteed with instruction manual and leads. £15. Carr. 7/6.




NOMBREX EQUIPMENT

Transistorised Audio Generator 10-100,000 c/s. Sine or square wave. £16.15.0. Transistorised Signal Generator 150 kc/s. 350 Mc/s. £10.10.0. Transistorised resistance capacity bridge 1Ω. 100 MegΩ. 1pF-100pF. £9.0.0. Transistorised Induction bridge, 1μN-100H. £18. Mains operated Transistor power supply unit, output 1-15v. up to 100mA. £6.10.0. All above post paid with battery.

CLEAR PLASTIC PANEL METERS

First grade quality, Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type MR, 88P, 1 21/82in. square fronts.
 100-0-100μA 27/6 200mA 22/6 100V D.C. 22/6
 500-0-500μA 22/6 300mA 22/6 150V D.C. 22/6
 1-0-1mA 22/6 500mA 22/6 300V D.C. 22/6
 1mA 22/6 750mA 22/6 500V D.C. 22/6
 2mA 22/6 1A D.C. 22/6 750 D.C. 22/6
 5mA 22/6 2A D.C. 22/6 15V A.C. 22/6
 10mA 22/6 5A D.C. 22/6 50V A.C. 22/6
 20mA 22/6 3V D.C. 22/6 150V A.C. 22/6
 50mA 22/6 10V D.C. 22/6 300V A.C. 22/6
 100μA 22/6 20V D.C. 22/6 500V A.C. 22/6
 500μA 22/6 50V D.C. 22/6 8" Meter 1mA 22/6
 50-0-50μA 22/6
 POST EXTRA. Larger sizes available—send for lists.

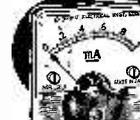

TE-51 NEW 20,000 VOLT MULTIMETER

0 / 6 / 60 / 120 / 1,200V. A.C.
 0 / 3 / 30 / 60 / 300 / 600/3,000V. D.C.
 0 / 60μA / 12 / 300 MA. D.C.
 0 / 60K / 6 Meg.Ω
 85/-, P. & P. 2/6.



MODEL PV-58 VALVE VOLTMETER

11 meg. input. 7 D.C. volt ranges. 1.5-1,500 v. 1,500 v. 7 A.C. volt ranges. 1.5-1,500 v. 4,000 Peak to Peak. Resistance 2 ohm to 1,000 megohm. Decibels -10db to +65db. Supplied brand new with instructions, leads and probe. £12.10.0. P. & P. 3/6.



TS-76 20,000 O.P.V. PUSH BUTTON MULTI-TESTER

Simple operation, D.C. volts up to 1,000 v. A.C. volts up to 1,000 v. Resistance up to 10 megohm. Current up to 250 mA. Decibels -20 to +36 db. £5.50. P. & P. 2/-.



MODEL 500, 30,000 opv. 0/5/12.5/10/25 / 100 / 250 / 500 / 1,000 v. A.C. 0 / 25 / 10 / 25 / 100 / 250 / 500 / 1,000v. A.C.
 0 / 50μA / 5 / 80 / 500mA. 12 amp D.C.
 0 / 60K / 6 Meg. / 60 MegΩ. £8.17.6. Post paid.

MAGNAVOX 363 TAPE DECKS

New 3-speed tape deck, supersedes old Collaro studio deck. 2-track £10.10.0, 4-track £13.10.0, Carr. Paid.

P.C.R.3 RECEIVERS

Absolutely brand new. 3 wavebands. 190-550 metres and 2.2-23 Mc/s. With circuit, £5.19.6. Carr. 10/6. Also PCB1 with built in speaker. Covering LW, MW and SW 6-15 Mc/s £8.19.6. Carr. 10/6. Plug-in power supply 12v. D.C. 19/6; 230v. A.C. 35/-.

AMERICAN TAPE

First grade quality American tapes. Brand new. Discounts for quantities.
 3in., 225ft. L.P. acetate 4/-
 3 1/2in., 600ft. T.P. mylar 10/-
 5in., 600ft. std. plastic 3/6
 5in., 900ft. L.P. acetate 10/-
 5in., 1,200ft. D.P. mylar 15/-
 5in., 1,800ft. T.P. mylar 35/-
 5 1/2in., 1,200ft. L.P. acetate 12/6
 5 1/2in., 1,800ft. D.P. mylar 22/6
 6 1/2in., 2,400ft. T.P. mylar 45/-
 7in., 1,200ft. std. mylar 12/6
 7in., 1,800ft. L.P. acetate 15/-
 7in., 1,800ft. L.P. mylar 20/-
 7in., 2,400ft. D.P. mylar 25/-
 7in., 3,600ft. T.P. mylar 58/6
 Postage 2/- Over £3 post paid.

CALLERS WELCOME!


Open 9 a.m. to 6 p.m. every day Monday to Saturday. Trade supplied.

GW SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155
 Cables: SMITHEX LESQUARE
 3-34 LISLE STREET, LONDON, W.C.2



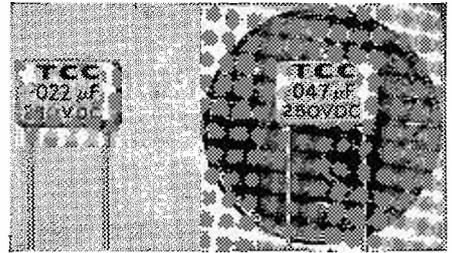MINIATURE METALLIZED POLYESTER CAPACITORS




Ideally suitable for printed wiring panels and transistorised circuits.

Incorporating a new dielectric material and of unique construction, they are of small physical size and meet the requirements of H.5 D.E.F. 5011 Specification. The windings are virtually non-inductive and the wire terminations are soldered direct to the metal electrodes eliminating contact resistance and ensuring the minimum possible inductance.

Typical 250 volt range

Cap. μ F	Dimensions		T.C.C. Type No.
	H.	T.	
0.01	$\frac{1}{16}$ " 9mm	$\frac{7}{32}$ " 5.5mm	PM X1
0.022	$\frac{1}{16}$ " 9mm	$\frac{7}{32}$ " 5.5mm	PM X2
0.047	$\frac{1}{16}$ " 9mm	$\frac{7}{32}$ " 5.5mm	PM X3
0.1	$\frac{7}{32}$ " 11mm	$\frac{3}{16}$ " 7.2mm	PM X4

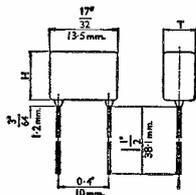

Cap Tolerance: $\pm 20\%$.

Voltage Ratings:

Ranges available 63, 250, and 400 volts D.C.

Power Factor:

<0.01 at 1 Kc/s at $+20^\circ\text{C}$.

Temperature Rating:

Suitable for working at $+85^\circ\text{C}$. without derating.

Details of the full range are given in T.C.C. Bulletin 93, available on request.

Insulation Resistance:

10,000 megohms or 2,000 ohm farad whichever is less.

Terminations:

22 s.w.g. solder-coated parallel wires for vertical mounting.

Finish:

Insulated — special non-cracking heat resisting thermosetting compound providing good insulation and good protection against the ingress of moisture.

THE TELEGRAPH CONDENSER CO. LTD.

Electronics Division • NORTH ACTON • LONDON • W.3 • Tel: ACOrn 0061 • Telex: 261383
also at CHESSINGTON, SURREY and BATHGATE, SCOTLAND

DE LUXE PLAYERS

4-Speed Players 2-tone Cabinets 17" x 15" x 8 1/2". High Flux Loudspeakers and High Quality Amplifier, ready built. Quality output. Volume and Bass controls. All items fit together perfectly. Special instructions enable assembly in 90 minutes, only 5 wires to join. 12 months' guarantee.

TO BUILD YOURSELF

Portable Cabinet 59/6. As illustrated. To fit any standard player or auto-changer.
RUS 3 watt amplifier 59/6 Ready made and tested. Complete with UCL82 triode pentode valve and loudspeaker.
SINGLE PLAY UNITS
BSR Junior £3. 9/6
BSR GUY £4.19.6
Garrard SRP12 £4.19.6
Garrard SP25 £10.19.6
Garrard A70 £19.19.6
Garrard LAB80 £24.19.6
Garrard 401 £29.19.6

Superior Amplifier 89/6. Ready made and tested. Guaranteed better sound! Fully isolated AC Mains Transformer 4 watt output. ECL86 triode pentode valve. Volume and tone controls with knobs. High Flux Quality Loudspeaker.
AUTOCHANGE UNITS
BSR Monarch £4.19.6
Garrard 1000 £5. 9/6
Garrard 2000 £6.19.6
Garrard 3000 £8. 9/6
Garrard AT70 with discast turntable £10.19.6

POST FREE

NEW ELECTROLYTICS FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES
2/350 v. 2/3	100/25 v. 2/1	9/600 v. 9/-
4/350 v. 2/3	250/25 v. 2/8	16/800 v. 18/-
8/450 v. 2/3	500/15 v. 3/-	18+16/500 v. 7/8
16/450 v. 3/-	8-8/450 v. 3/8	32+32/450 v. 6/-
32/450 v. 3/8	8-16/450 v. 3/8	50+50/350 v. 7/-
25/25 v. 1/9	16+16/450 v. 4/8	64+120/350v. 11/8
50/50 v. 2/-	32+32/350 v. 4/8	100+200/275v.12/6

PAPER TUBULARS
350v.-0.1 9d., 0.5 1/8; 1 mfd. 3/-; 2 mfd. 150v. 3/-.
500v.-0.001 to 0.05 9d.; 0.1 1/-; 0.25 1/6; 0.5 2/6.
1,000v.-0.001, 0.002, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1 2/-;
0.22, 0.47, 3/-; 2,000v.-0.005, 0.01, 0.02 2/6; 0.05 3/8.
E.H.T. CONDENSERS. 0.001mfd, 7kV., 6/8; 20kV., 10/6.

SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 500, 1,000 mfd. 15v. 2/8; 1,000 mfd. 50v. 7/6; 2,000/50 11/6.
CERAMIC. 500 v. 1 pF. to 0.01 mfd. 9d. DISC CERAMICS
1/-, PULSE CERAMICS 10 pF. to 180 pF., 12 kV., 2/6.
SILVER MICA. Close tolerance (plus or minus \pm pF.), 5 to 47 pF., 1/-; ditto 1% 50 to 800 pF., 1/-; 1,000 to 5,000 pF., 2/-.
TWIN GANG. *0-0* 208 pF., +176 pF., 10/6; 365 pF., miniature 10/-; 500 pF. standard with trimmers, 9/-; midget, 7/8; midget with trimmers, 9/-; 500 pF. slow motion, standard 9/-; small 3-gang 500 pF., 18/6; Single *0* 365 pF. 7/8.
SHORT WAVE. Single 10 pF., 25 pF., 50 pF., 75 pF., 100 pF., 150 pF., 5/8 each. Can be gauged. Couplers 9d. each.
TUNING. Solid dielectric. 100 pF., 300 pF., 500 pF., 3/8 each.
TRIMMERS. Compression ceramic 30, 50, 70 pF., 9d.; 100 pF., 150 pF., 1/8; 250 pF., 1/6; 600 pF., 750 pF., 1/9.

BAKER LOUDSPEAKERS

HANDMADE BY CRAFTSMEN

HIGH FIDELITY MODELS

12in. STALWART	15w. ALL POST FREE
3 or 15 ohms	£5. 5.0
12in. STANDARD	£8. 0.0
12in. DE-LUXE	£9. 0.0
12in. BASS	£12.10.0
12in. SUPERB	£15. 0.0
15in. BASS	£18. 0.0

LABORATORY STANDARD MODELS
12in. D.W.1 cone £22.10.0
15in. D.W.1 cone £28.10.0
PLANS AND CATALOGUE FREE!
GROUP MODELS FOR VOCALS
BASS LEAD AND RHYTHM GUITARS
30-10,000 cps. Voice Coils 15 ohms. Heavy duty.
'Group 25' 'Group 35' 'Group 50'
12in. 5gns. 12in. 8gns. 15in. 18gns.
25w. 35w. 50w.

LOUDSPEAKERS P.M. 3 OHMS. 2 1/2in., 3in., 4in., 5in., 7in. x 4in., 15/6 each; 8in. 17/6; 6in. 16/6; 12in. 30/6; (15 ohms 25/-); 10in. x 6in. 22/6; 8in. x 5in. 21/-; 6in. x 6in. 21/-; E.M.I. Double Cone 1 1/2 x 8in., 3 or 15 ohm models, 45/-; Stentorian 10in. HF1012, 25.10; 8in. HF612, £4.10; Crossover 35/-; Horn Tweeters 3-16 Kc/s. 10 w 29/6; 20 w 20 Kc/s. 99/6.

Q MAX CHASSIS TURNER

Complete: a die, a punch, an Allen screw and key

1in.	1 1/2in.	18/-	1 1/2in.	22/6
2in.	1 1/2in.	18/-	2in.	34/3
3in.	1 1/2in.	18/6	2 1/2in.	37/9
4in.	1 1/2in.	20/-	2 1/2in.	44/3
1in.	18/7	20/6	1in. sq.	31/6

CRYSTAL MIKE INSERTS

1 1/2 x 3/8, 6/8; BM3 1 x 3/8, 7/8; ACOS 1 1/2 x 3/8, 3/8
TANNAY CARBON MIKE with Switch 5/6
MOVING COIL HEADPHONES 100 ohms 12/6
(Slightly sotted but guaranteed).
BARGAIN KIT PICK-UP ARM Complete with ACOS LP-78 Turnover Head and Stylus 20/-; Stereo 30/-.

BEST BRITISH PVC RECORDING TAPES

L.P. 7in. 1800ft. 19/6	D.P. 7in. 2400ft. 29/6
L.P. 5in. 1800ft. 14/6	D.P. 5in. 1800ft. 24/6
L.P. 5in. 900ft. 11/6	D.P. 5in. 1200ft. 18/6

Spare Spools 2/6. Tape Splicer 5/-. Leader Tape 4/6.
Tape Heads: Collaro 2 track 29/6 pair. 4 track 70/- pair.

MAINS TRANSFORMERS

250-0-250, 80 mA, 6.3 v. 3.5 a. Rectifier 6.3 v. 1 a. or 5 v. 2 a. 25/-; Ditto 350-0-350	29/6
MF510 0-0-000 v. 120 mA, 6.3 v. 4 a.	29/6
MINIATURE 200 v. 20 mA., 6.3 v. 1 a.	10/6
MIDGET 220 v. 45 mA., 6.3 v. 2 a.	15/6
SMALL 300-0-300 v. 70 mA., 6.3 v. 4 a.	19/6
HEATER TRANS. 6.3 v. 1 1/2 a., 7/8; 6.3 v. 4 a.	10/6
DITTO tapped sec. 1.4 v., 2.3 v., 4.5 v., 6.3 v. 1 1/2 amp.	10/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a.	25/-
Ditto. 1 amp. 5, 10, 15, 20, 25, 30, 40, 45, 50, 55, 60 29/6	
AUTO TRANS. 150 w., 0, 115 v., 230 v., 25/-; 500 w. 82/6	

JACK SOCKETS Std. open-circuit 2/8, close-circuit 4/6. Lead Socket 8/-. Grundig 3-pin 1/3; Lead 3/6.
Phono Plugs 1/-. Socket 1/-. Banana Plugs 1/-. Sockets 1/-.
JACK PLUGS STANDARD. Screened 5/-. Grundig 2-pin 3/6.
WAVE-CHANGE SWITCHES WITH LONG SPINDLES.
2 p. 2-way, or 2 p. 8-way, or 3 p. 4-way or 1 p. 12-way; ea. 3/6
4 p. 2-way, or 4 p. 3-way, 3/6; 8 p. 4-way, 2 wafers. 6/8
Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way. Prices include dielectric spindles, adjustable stops, spacers, etc., 1 wafers, 3/6; 2 wafers, 12/6; 3 wafers, 18/-; 4 wafers, 19/6; 5 wafers, 23/-; extra wafers, 2/6
TOGGLE SWITCHES, 3 p. 2/-; d.p. 3/6; d.p.d. 4/-.
SPEAKER-FRET. Tysan various colours, 52in. wide from 10/-; 12in. wide from 5/- ft. Samples, large, 8.8.E.
EXPANDED METAL. Gold or Silver 18 x 12in. 8/-.

RETURN OF POST DESPATCH Minimum P.P. Charge 1/6 per order unless otherwise stated. Full List 1/-. C.O.D. 2/6 extra. CALLERS WELCOME
RADIO COMPONENTS SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON
Written guarantee with every purchase. (Export—Send remittance and extra postage, no C.O.D.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel: THO 1665

r.f. signal but negligible at a.f. and so R1 is included across which the a.f. voltage is developed. This a.f. voltage is derived from the rectification of the modulated r.f. voltage by the grid and cathode of V1 acting as a diode in parallel with the tuned winding L2. This type of detector is commonly called the grid leak detector.

From the junction of R1 and r.f.c. the a.f. voltage is passed, via C4, to the grid of V2a which is the triode portion of the ECL80 triode pentode audio amplifier. V2b is the power output stage, having as its anode load the primary of the output

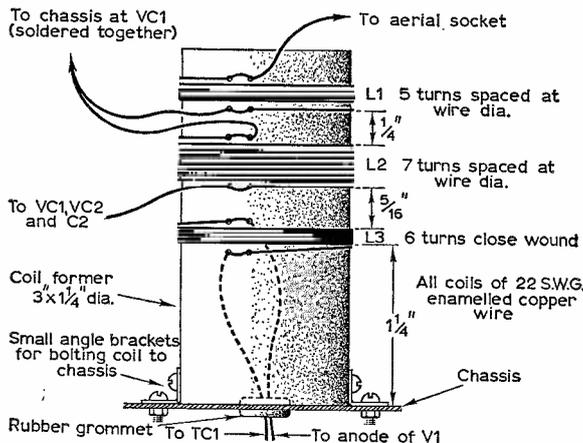


Fig. 2: Details of the tuning coil L1, L2, L3.

transformer, the secondary of which feeds a small loudspeaker.

As far as valves are concerned, we need only consider V1 because on its characteristics will depend the ultimate performance of the receiver. An EF91 was chosen for this position because it has an excellent r.f. performance and can be purchased very cheaply indeed. Identical replacements are Z77, 6AM6, 6F12, CV138 and 8D3.

All the components to be used should be to hand before any attempt is made at constructing the chassis and front panel so that any changes necessary due to a difference in component size can be allowed for. Both the chassis and front panel were made from 18 s.w.g. aluminium, although brass or tinplate could be used with the advantage that all earth connections could be soldered directly to the metalwork. After all the holes have been made the chassis and panel may either be paint sprayed or given a crackle finish. Suitable transfers may be fitted to the front panel giving the unit a really smart finish.

COIL WINDING

The aerial coupling, tuning and reaction windings are all wound on the same former which should be 3in. long with an outside diameter of 1 1/4in. The wire used was 28 s.w.g. enamelled wire, but this is not critical and other gauges not too far removed from 28 would prove acceptable.

L3 should be wound first and in order to do so two small holes should be pierced in the coil former about 1/8in. apart as in Fig. 2. The end of the wire is threaded through the two holes two or three times to hold it firm and then six complete turns are

wound tightly on side by side or "close wound". Two further holes are pierced and the wire threaded through as before. About 6in. should be left at both ends to connect to anode of V1 and to TC1.

L2 is next to be wound and to do this a further pair of holes should be pierced 5/16in. away from L3. The winding is wound in the same direction as L3, but the turns are spaced from each other by the diameter of the wire. Seven complete turns are wound tightly on and a further pair of holes pierced through which the end is threaded. The ends of this winding can be about 4in. long.

L1 is wound in the same manner as L2 but is spaced from it by 1/4in. The start of L1 can be left about 4in. long but the finish should be left some 8in. long so that it can be soldered directly to the aerial input socket. Results comparable to those obtained with the prototype will only be obtained when the coil is wound exactly as the original, but, and this is an important but, results will still be obtained if individual coils vary in diameter, coil spacing, wire diameter and wire spacing.

Actual construction can commence with the fitting of all major components except the coil which should be left until last. The coil is bolted coaxially about a grommet through which

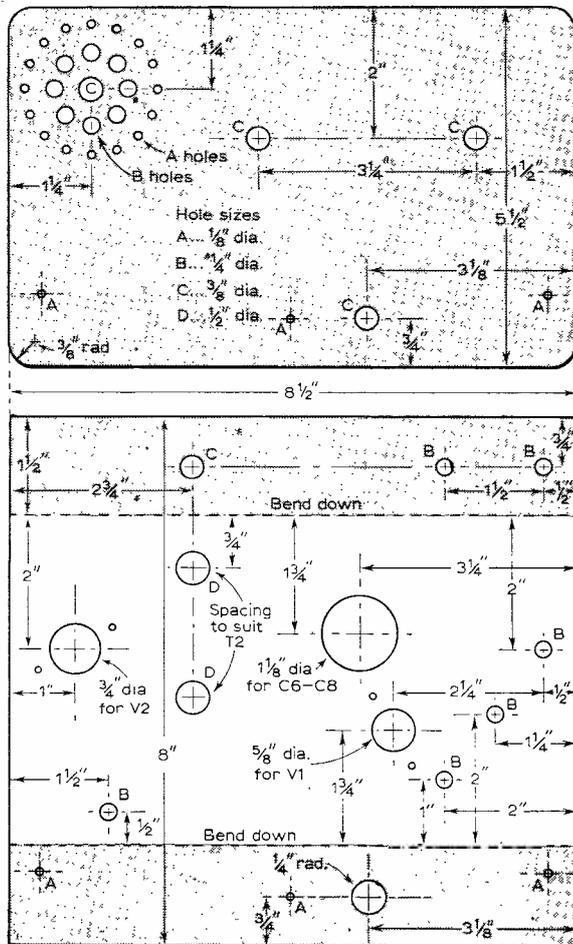


Fig. 3: Layout and drilling details of the front panel and chassis.

be set at maximum capacity and VR1 rotated anticlockwise so that its wiper is at the tag connected to R4. The mains can now be connected and a short while after a rustling noise and possibly a faint amount of hum should be heard from the loudspeaker. VR1 should now be advanced slowly towards its fully clockwise position at which point some signals may be heard, assuming, of course, that an aerial has also been plugged into the aerial socket. If signals cannot be heard by rotating VC2, the bandspread capacitor, TC1, should be slowly screwed in to increase its capacity until signals can be heard on rotating VC2. VR1 should now be backed off slightly and TC1 again slowly screwed in until signals can be heard. The screen grid voltage of V1 should now be in the region of 120V and TC1 can be assumed to be finally adjusted and all subsequent reaction controlled by VR1. As the frequency is increased by unmeshing VC1, the reaction control VR1 will require adjusting in an anticlockwise direction. The ideal range of VR1 is from excessive reaction at the low frequency end of the band to the high frequency end, at its most clockwise or maximum position, to insufficient reaction at its anticlockwise or minimum position. If reaction cannot be obtained with VR1 fully clockwise and TC1 fully tightened up, the coil connections are wrong and the leads from L3 to V1 anode and TC1 will have to be transposed. The mains should be disconnected for this operation and VR1 and TC1 returned to minimum. Upon reconnecting the mains, the reaction circuit should function normally.

FREQUENCY CHECKING

Unless it is desired to cover a particular bandwidth, the receiver can be considered as being fully operational. If a signal generator is available, dial calibration can be checked easily and quickly. If not, reliance will have to be placed on transmissions for calibration. One of the greatest disadvantages common to all simple t.r.f. receivers employing reaction is that the feedback voltage varies with frequency, necessitating an adjustment to the reaction control every time the frequency is changed. This is a fundamental difficulty and one the individual will have to accept if he is to make the most of his own set. The point of optimum sensitivity is when the set is just, and only just, below the point of oscillation. If the reaction is advanced to the point where the set actually oscillates all that will be heard is a high pitched hiss and whistles wherever there is a transmission. If the reaction is not sufficiently advanced only very strong transmissions, or perhaps no transmissions at all, will be heard. The point of correct reaction can be easily determined by slowly advancing the control until a "plop" is heard followed by a hiss and whistles. This is excessive reaction and the control should be "backed off" to a point where the set does not go "plop", and transmissions of voice, music and morse should be heard naturally. The reception of morse is often improved by employing fractionally excessive reaction.

A headphone jack can be easily incorporated between V2a and V2b as shown in Fig. 5 so that with the jack withdrawn the signal from V2a is fed normally, via C4, to V2b when the jack is inserted the connection is broken and the signal is fed to

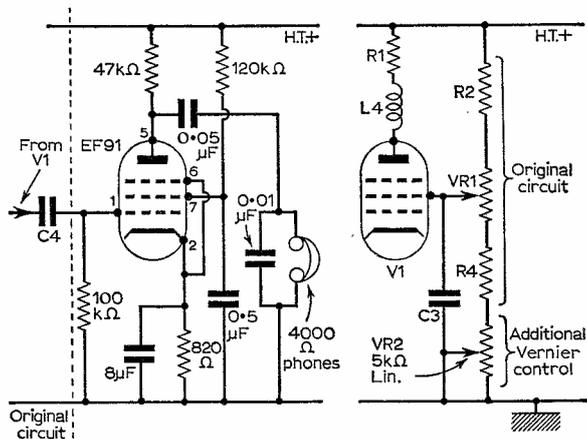


Fig. 6 (left) One way to run headphones only. The EF91 replaces V2.

Fig. 7 (right) Modification for Vernier reaction control.

the headphones instead of V2b thereby muting the speaker (and output stage).

An essential requirement is that the grid leak of V2b, which is R8, must be wired as originally, that is on to the grid pin.

The last modification is a somewhat unusual one and concerns the incorporation of a vernier reaction control; Fig. 7 shows how this can be done.

It makes the adjustment of optimum reaction quite easy, a feature that will be much appreciated when very weak stations are being sought.

Every receiver from the very simple to the very complex benefits from the use of a really first-class aerial and earth system, though both do not, unfortunately, receive the attention they deserve. ■

★ components list

Resistors:

All 10% ½W except where stated.

R1	33 kΩ	R7	330 Ω
R2	33 kΩ	R8	100 kΩ
R3	1.5 MΩ	R9	820 Ω 3W wire wound
R4	33 kΩ	R10	500 Ω 3W wire wound
R5	220 kΩ	R11	330 Ω wire wound
R6	470 kΩ	VR1	50 kΩ wire wound

Capacitors:

C1	1000 pF	C9	250 μF electrolytic
C2	100 pF	VC1	500 pF
C3	0.05 μF	VC2	15 pF
C4	0.01 μF	TC1	100 pF Pre-Set
C5	0.01 μF		
C6	32 μF		
C7	32 μF		
C8	8 μF		

} Common
} Can electrolytic

Miscellaneous:

T1	40:1 o/p transformer, 3 ohms Sec'
T2	PRI. 240V Sec. 250V at 30mA 6.3V at 1A.
L1 L2 L3	See Text.
MR1	Contact Cooled rectifier 250V at 30mA.
L.S.	3 ohms 2½ in. square.
	R.F.C. Short Wave R.F. Choke.

Valves:

V1	EF91.	6AM6	V2	ECL80
----	-------	------	----	-------

TRANSISTORISED IND

*A.C. PROBE

*AUDIO MONITOR

THREE items of test gear are described in this article—an a.c. probe with a 100mV sensitivity in the frequency range 3kc/s to 30Mc/s, a simple audio frequency monitor that will respond to 1mV signal level changes and a 16 to 64Mc/s receiver-oscillator. None of these instruments require expensive components such as moving coil meter movements and all use cheap transistors. A little ingenuity is, however, required in the construction, particularly when putting the r.f. probe together, since part of an old gas lighter refill holds most of the components.

A.C. PROBE

This general purpose instrument is designed to indicate visually the presence of audio or radio frequency voltages in a circuit under test. The sensitivity is such that a clear response can be obtained from signals of less than 100 millivolts in the frequency range 3kc/s-30Mc/s.

Unlike the familiar signal tracer, which relies on audible detection of the signal, unmodulated r.f. may be checked by this probe. The input is deliberately attenuated at low audio frequencies to

enable much higher voltages to be inspected without overloading the instrument; even mains supplies can be tested.

A typical application of the instrument is to check if the oscillator of a superhet receiver is functioning. If the probe needle is touched on the oscillator section terminal of the tuning capacitor the torch bulb should glow brightly if all is well. Similarly, the glow of the bulb can give a useful indication of the comparative output of a radio control transmitter, and will check the quench action of a super-regenerative receiver. To achieve minimum circuit loading and self-capacitance, the torch may be held in the fingertips by its plastic reflector holder, instead of by the metal barrel.

Circuit Description

From the circuit diagram, illustrated in Fig. 1, it can be seen that two transistors are d.c. coupled in a Darlington Pair configuration, with the bulb load in the common supply line, providing a degree of negative feedback. Additional thermal stability results from the diodes D1 and D2 across the base-emitter junctions of the transistors. These diodes



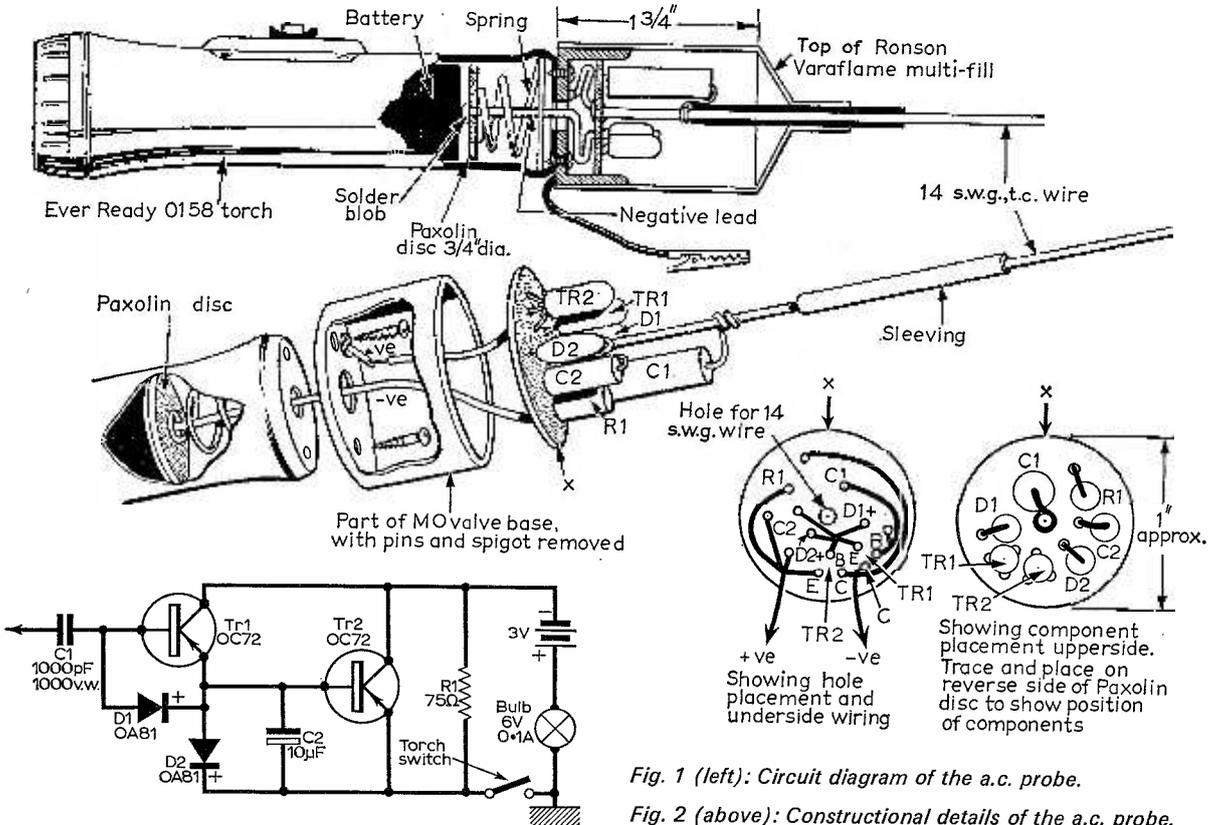


Fig. 1 (left): Circuit diagram of the a.c. probe.

Fig. 2 (above): Constructional details of the a.c. probe.

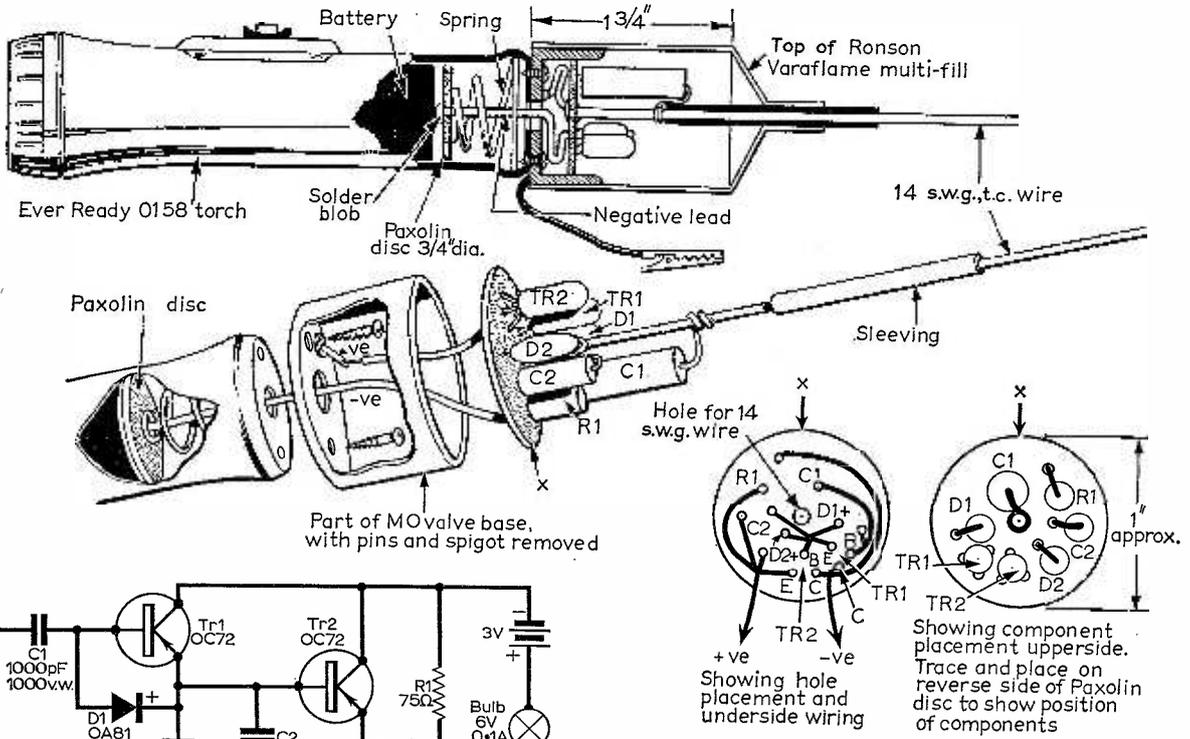

INDICATORS

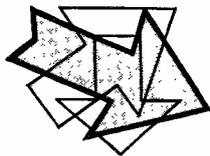

BY D. BOLLEN

*16-64 MC/S RECEIVER-OSCILLATOR

also rectify the signal. Resistor R1 is selected to bias the bulb so that it will just glow faintly with no input applied. In the original circuit a resistor of 75 ohms was used, but variations between individual bulbs may necessitate a slightly different value.

The earth return lead can be dispensed with when measuring r.f., and also when testing mains supplies, but it should be brought into use for low level audio checks. The bulb specified was found to give the best all round results and is of the type normally used in bicycle dynamo front lamps.

Probe Construction

Constructional details of the probe are given in Fig. 2. The torch is drilled at the battery end to take self-tapping screws and the negative battery lead. A paxolin disc is placed between the battery spring and battery case. This is fitted with a flexible lead and retained by a generous blob of solder which makes contact with the negative end of the battery. The centre spigot and pins are removed from a Mazda octal valve base—taken from an old valve of the ARP 12 variety—and this is retained on the end of the torch by self-tapping screws.

A used Ronson lighter refill is first shaken to ensure that no liquid fuel remains inside. If not, the contents may be emptied into a lighter. Residual pressure in the refill is released by inserting a 1/16in. drill into the rubber valve and twisting until the hissing stops. **BE VERY CAREFUL AS THIS OPERATION CAN BE DANGEROUS.** The drill's grooves provide a gap for the gas to escape freely and the operation should be performed well away from naked flames. When the refill is completely de-pressurized, the alloy body may be cut with a fine saw to form a cap. After the burr has been removed with sandpaper or a file, the cap should be found to be a good force fit on the valve base. If it is too tight the base may be lightly sanded. The valve portion of the refill is finally drilled out to take the probe needle insulating sleeve.

A disc of paxolin, approximately 1in. in diameter, is cut and filed to suit the inside of the valve base and is then drilled as shown in the placement diagrams in Fig. 2. If desired, the disc could be copper clad on one side and etched to make a circuit, but with the prototype the component's leads were inserted in the holes, bent over and soldered together. To ensure correct positioning of components, a tracing may be made from the placement diagram and pasted on the upperside of the drilled disc. This can be torn away after construction is completed.


One must ensure that C1 has an adequate voltage rating, and that the insulation of the probe needle is impeccable if the instrument is to be used at mains voltages. The value for C1, 0.001 μ F, represents a reactance greater than 3M Ω at 50c/s, reducing to about 30k Ω at 5kc/s. If a flat response is required down to the low audio frequencies C1 may

be increased in value to, say, 0.1 μ F, but the instrument must not then be used for mains checking as the high voltage input would severely overload the circuit.

AUDIO MONITOR

The circuit shown in Fig. 3 is a straightforward development of that given in Fig. 1. Here the bulb is employed as the collector load of Tr3 and a stage of a.f. amplification has been added. The monitor may be used as a modulation peak level indicator in tape recorders and portable transmitters; the complete unit occupying much less space than a meter. Other possible applications are as a null detector in a c.r. bridge, and as a pulse rate monitor in a simple Geiger counter. Response to a signal is unambiguous and changes of less than 1mV in signal level are discernible. As a rough indication of sensitivity, when a crystal microphone insert is connected directly to the input of the monitor the bulb will flash brightly in response to a human whistle five yards away. Standing current is around 10mA, rising to approximately 100mA on signal peaks.


When comparing close audio frequencies, both may be simultaneously fed into the monitor and the slow resulting beats counted and timed with a stopwatch, giving an exact determination of frequency when one of the inputs is a closely controlled standard, such as the 1000c/s tone radiated by the BBC at commencement of transmissions. This is more positive than aural methods since beats of only a few cycles per second are not easily resolved by either ordinary amplifying equipment or the human

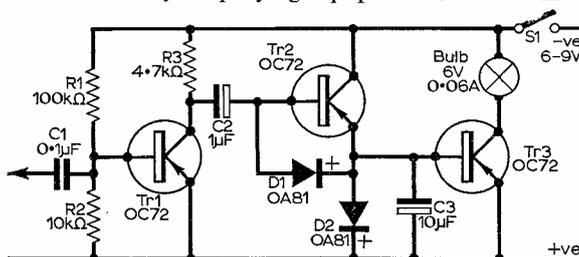

ear, but the bulb's rate of flashing is obviously plain when the difference between compared frequencies is a fraction of a cycle per second, and up to as fast as the operator can count.

Fig. 3 (above): Circuit diagram of the audio monitor.

Fig. 4 (right): Layout and wiring diagrams for the audio monitor.

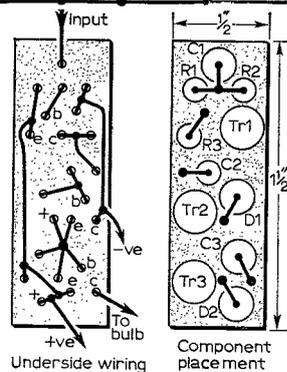

On 9 volts the bulb will be overrun at high input levels. This was not thought to be critical as such levels would seldom be sustained for lengthy periods and bulb replacement could hardly be termed expensive. However, when running with large inputs Tr2 and Tr3 tend to warm up and, with d.c. coupling, their leakage current increases. Under such conditions the bulb will not extinguish completely when the signal is removed, until the transistors have had a chance to cool. To minimise this effect, Tr2 and Tr3 may be fitted with heat sinks, when the application demands continuous illumination of the bulb.

In this case, construction is almost certain to be a matter of individual preference as the unit would normally be incorporated with some larger item of equipment. As a guide the layout of the prototype, on a paxolin panel measuring 1½" x ½", is given in Fig. 4.

If a light dependant resistor is coupled to the bulb this can be used as a noiseless, remote volume control in an amplifier or radio receiver. A small a.c. voltage injected into the monitor will control the effective resistance of the LDR, and a feedback loop can be arranged to provide volume compression.

RECEIVER-OSCILLATOR

Anyone who has tried winding their own coils will appreciate the usefulness of an instrument which confirms that n turns on a d diameter former do, in fact, produce the required value of inductance. When a radio control receiver is first constructed its tuned circuit, or circuits, may peak many megacycles above or below the allotted band. Without a signal generator or grid-dip meter, much time can be spent screwing cores in and out, in the hope that at a certain stage in the proceedings the receiver will respond to a nearby transmitter, assuming that the transmitter is on frequency also. The major problem with most types of home-built frequency standards is that of initial calibration, and the same applies to conventional short-wave receivers. Although a dial marked 0-100 may look good, it is better to know what the divisions represent in terms of megacycles or metres.

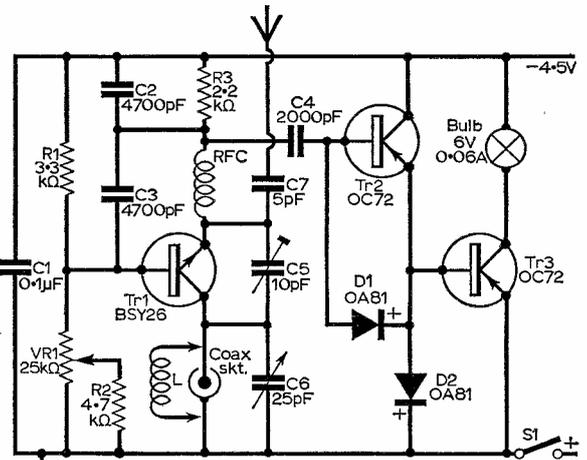


Fig. 6: Circuit diagram of the Receiver-Oscillator.

With little more than a simple 1Mc/s crystal marker and a length of wire, the Receiver-Oscillator may be accurately calibrated for use as a frequency sub-standard, to check the resonance of both passive and active tuned circuits. In other words, the instrument has more uses than can be listed here. Sufficient to say that it may be utilized to test field strength meters; receivers, oscillators, TV, many instruments, and will stand-in as a signal generator. Even if a signal generator is already available, together with a wide range communications receiver, it is often quite useful to have a means of duplicating their functions, or to transfer a signal from one piece of equipment to another.

Circuit Description

The super-regenerative detector offers a convenient and simple way of arranging for two-terminal plug-in coils, with one end of the winding earthed. It is also highly sensitive, and with careful design will cover a wide frequency range without complicated switching and adjustments.

The circuit, Fig. 6, gives the salient details. An n-p-n epitaxial transistor is used for Tr1, allowing the coil L to be connected directly to the earth rail, thus ensuring stability and ease of operation. These

transistors are now readily available at moderate prices and give excellent results.

The unusual point about the circuit is that the quench frequency, arising from the mode of operation, is used to bias the bulb amplifier; via C4 from the emitter network of Tr1, and is controlled by VR1, which also determines the operating point of the detector, and hence its sensitivity. If VR1 is fully advanced to its minimum resistance position

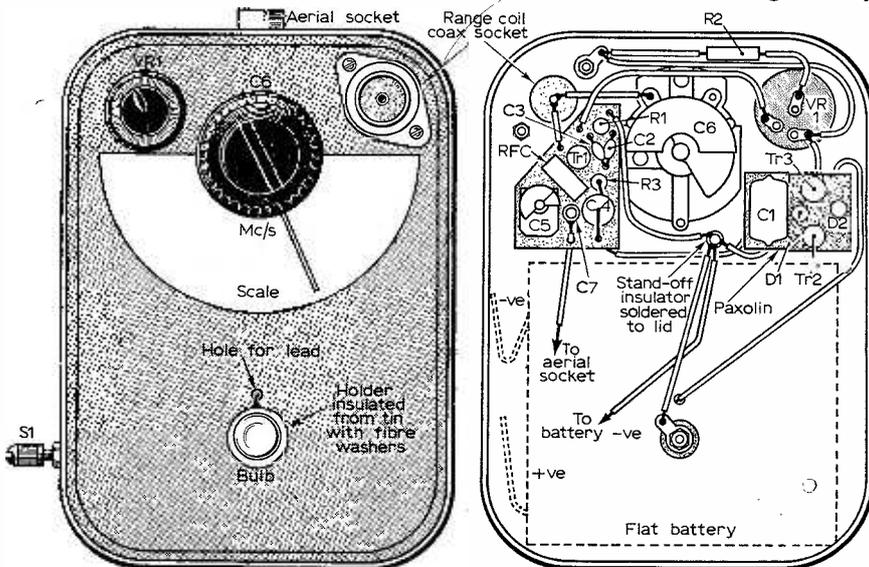


Fig. 5: Constructional diagrams of the Receiver-Oscillator. Range scale and coil-winding details are included in Fig. 7.

the quench disappears and the circuit oscillates only at r.f. The feedback trimmer C5, once set, can be left alone and the instrument will operate quite successfully over the entire frequency range—with or without quench—covered by adjustment of the main tuning control C6 and non-critical rotation of VR1. The choice of range, 16-64 Mc/s, may appear arbitrary, but this covers those frequencies not normally to be found on ordinary short-wave receivers, to link up with the lower television bands, and also embraces model control, two amateur bands and the Industrial, Scientific, and Medical allocation at 40.68 Mc/s. If switched values for C5 can be tolerated then the instrument could be made to cover 10-150Mc/s, but tests indicate that operation at those limits would tend to be critical. Many circuits claim to cover a wide range but this desirable end is seldom achieved without complexity or unreliable operation.

It will be noted that the electrolytic capacitor, shown in the previous circuits, across the base-emitter junction of the output transistor, has been omitted. This is to allow a pair of low-impedance headphones to be connected in place of the bulb for the purpose of identifying certain signals when calibrating the instrument. Without the electrolytic capacitor, the bulb current consists of rectified a.c., resulting in slightly less brilliance, but this has no important effect on performance.

The circuit is not at all critical where component spreads are concerned. The r.f.c. may be pile wound, with one or two hundred turns of 40 s.w.g. wire on the body of a miniature resistor, or can be a pi winding taken from a small medium wave coil or an i.f. transformer, as in the original. Provision for an aerial is made, feeding via 5pF capacitor C7 into the low impedance side of Tr1. Even if the aerial socket is shorted to earth no resetting of the dial is necessary to compensate for frequency variation with load, hence this socket may be confidently used both as an input and output without impairing the instrument's accuracy.

Construction

A 2oz. tobacco tin is not the most ample of all-metal containers, even if it is easy to come by, consequently a slightly unconventional mode of assembly was resorted to when building the instrument, allowing for the fact that most of the internal space was taken up by a large long-life battery. The 25pF capacitor, C6, could just be accommodated without packing under its bush so a thick paxolin panel was out of the question; C6, VR1, coaxial coil socket, and bulb holder were mounted as shown in Fig 5. After a certain amount of brooding and twiddling of spindles it was realised that the only space left for wired components were two discretely small areas of bare metal on either side of C6, squeezed between the battery, VR1 and socket. In response to this challenge, two pieces of paxolin were cut and drilled and after the components were mounted, soldered, and tested, these panels were glued to thin pieces of foam plastic which were then, in turn, glued to the tin-lid in the positions shown in Fig. 5. With the battery in place there was not even enough room for the most miniature of switches so S1 was made up with a 6BA screw and nuts, soldered to the side of the tin, so that when screwed in it shorts the positive terminal of the battery to the instrument's case.

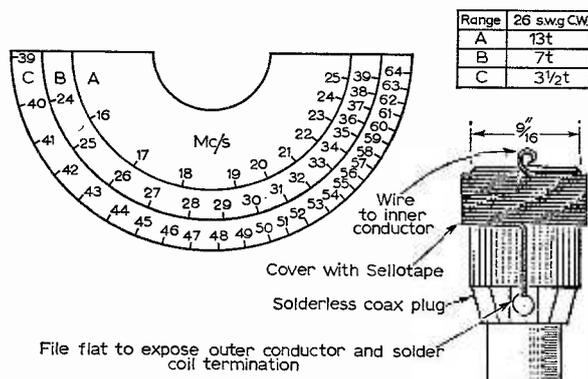


Fig. 7: Calibration data and coil-winding information for the Receiver-Oscillator.

Three coils were wound, according to Fig. 7, on a modified Radiospares 'Normal' coaxial plug, with 26 s.w.g. enamelled wire. Part of the plug outer-casing is filed away to expose the outer conductor and the end of the enamelled wire—after being scraped clean—is soldered to this before winding the coil. Also, a length of insulated 20 s.w.g. wire is fitted to the centre conductor by means of the solderless connector supplied with the plug, as a winding anchorage. The prototype's scale is given as a guide and may be referred to when calibrating the instrument. The rest of the construction and link-up wiring should be plain from the diagrams. C5 is a miniature solid-vane printed-circuit trimmer, but if its replica cannot be found, two insulated wires, twisted together, may be used in place of C5 as the value of capacitance required is only a few pF. C2 and C3 are very small high K ceramic sub-miniature capacitors. All resistors used were also sub-miniature types.

Calibration and Use

The battery may be temporarily connected to negative lead and tin-lid, and coil 'A' inserted in its socket. Rotation of VR1 should cause the bulb to glow. If not, the wiring must be re-checked, and a signal can be applied from an audio oscillator to the base of Tr2 to ensure that bulb and associated amplifier are working. C5 is set to the mid-capacitance position and can be used later to shift the dial calibration points so that the ranges meet or overlap slightly. Even with the vanes fully out of mesh, however, the original circuit oscillated reliably.

When the bulb lights, back off VR1 to approximately half brilliance and then couple the aerial socket to a 1Mc/s crystal marker. The bulb's glow should peak up sharply at each 1Mc/s division as C6 is slowly rotated. If a piece of paper is lightly glued to the lid, the points of maximum brilliance may be marked with a pencil.

Repeat the procedure for coils B and C, slightly re-adjusting VR1 to maintain maximum sensitivity at different dial settings. The resulting scale should consist of a number of regular pencil marks, with a taper towards closer spacing at the high frequency end of the dial, representing 1 Mc/s intervals. To identify the marks numerically, plug in coil C and about two yards of aerial. Replace the bulb with a

—continued on page 351

In answer to Henry

ON opening my copy of PRACTICAL WIRELESS this month, I was shattered to find that Henry had done me the honour of bringing his big guns to bear on me and my "polite reprimand". Did I really stick my neck out that far? Rallying from the shock however, I take my courage in both hands and a pen in one and set out to defend myself.

Given Henry's fuller explanation of the more sophisticated uses to which synthesizers may be put, I see where the misunderstanding has arisen. In his first article, Henry said: "By transmitting a great number of channels *simultaneously*" whereas, in his second, he modifies the description to "both transmitter and receiver can be continually *changing* frequency"—a very different thing since "simultaneously" implies that the channels are all being used at the same instant in time, as in the simultaneous broadcasting system of the BBC where the same programme is radiated on various frequencies by several transmitters throughout the country. Incidentally, *channels* are not transmitted, surely it is information which is transmitted *on* channels.

All this, of course, only serves to underline the difficulties which a columnist faces when he attempts a general description of apparatus or technique; inevitably, absolute accuracy must be sacrificed to the limitations of space.

Pax Henry!—our differences are semantic, not technical.

John Niven Douglas.

Glasgow, N.W.

Roding Boys Society folds

WE would like to inform your readers that, following the resignation of the leader of the Roding Boys' Society, this Society has been disbanded. However, some of the ex-members have now formed the Redbridge Scientific Society, meeting at the same premises: Wanstead Community Centre, The Green, E.11.

We would be obliged if you would print this letter as an announcement to those earlier members of the Roding Boys' Society, who remained loyal to the Society although distant from its core.

R. J. Lipscombe.

187 Markhouse Road,
Walthamstow E.17.

Wrong address

THANK you for printing my request in the Sell or Loan section of August PRACTICAL WIRELESS. Unfortunately the address is wrong; it should be:—Mr. D. Mines, 41 Sandringham Road, Bitterne Park, Southampton.

NEWS AND..

"CIR-KIT" FROM PEAK SOUND

From Peak Sound (Harrow) Limited, 10 Asher Drive, Off Mill Ride, Ascot, Berkshire, comes "CIR-KIT", 0.002in. copper-coated on one side with a special heat-resistant adhesive which in turn has a protective paper backing. It can be used for modifying existing printed circuits, building up prototype or experimental circuits, small quantity production runs on simple circuits or as flexible connectors, etc.

"CIR-KIT" is available in kit form. Kit No. 1 consists of 1ft. of 6in. wide CIR-KIT; three 6 x 12in. Bakelite E.10 laminate boards; 25ft. of $\frac{1}{8}$ in. wide CIR-KIT and 25ft. of $\frac{1}{16}$ in. wide CIR-KIT. Kit No. 2 contains 4ft. of 6in. wide CIR-KIT; five 6 x 12in. Bakelite E.10 laminate boards; 100ft. of $\frac{1}{8}$ in. wide CIR-KIT; 200ft. of $\frac{1}{16}$ in. wide CIR-KIT; one Craft knife and a spare blade. There is also a trial kit, which contains 4 x 6in. sheet of CIR-KIT; one piece of 12 x 6in. Bakelite E.10 laminate board, and 15ft. of $\frac{1}{8}$ in. wide CIR-KIT.



FI-CORD INTERNATIONAL RELEASE THE "300"

A new pocket-sized battery-operated dictating machine, the Fi-Cord 300 has recently been introduced. It is a compact lightweight Swiss precision-built fully transistorised unit, complete with all transcribing facilities for the office. Fitting into the palm of the hand, the 300 measures $6\frac{3}{8} \times 3\frac{1}{2} \times 1\frac{3}{8}$ in. and weighs 25 ounces. It provides simple and rapid 1-2-3 operation for record-rewind-listen in addition to fast forward and stop.

Tape speed is $1\frac{7}{8}$ i.p.s. and tapes recorded on this machine can be played back on any tape recorder having the same speed and using $\frac{1}{2}$ in. tape. A digital counter is employed and a warning buzzer indicates the end of the tape.

The exclusive Fi-Cord accessory socket for both input and output accepts a choice of accessory microphones, stop-start (remote control) and lapel types, either for reducing background noise or for general purpose.

Price of the Fi-Cord 300 is £63 retail. For further details contact Fi-Cord International, Charlwoods Road, East Grinstead, Sussex.

FIRST INTERNATIONAL TV & RADIO SHOW

For the first time London will be the centre for a major international trade exhibition of audio and video electronic equipment—including colour television receivers—when The Television and Radio Show is at Earls Court, London from August 22 to 26, 1966. As well as many thousands of retailers and wholesalers and their salesmen and service technicians, attendance will include hundreds of traders from abroad.

Unlike previous national public radio shows at Earls Court, this year's is international and trade-only. Organised with the backing of the distributing side of the trade and British and foreign manufacturers and import agencies, it is timed to enable the home trade prepare for an exceptionally vigorous sales drive this winter.

The show will highlight the way in which compact transistor equipments and small but good loudspeakers are making good quality reproduction available to everyone, not just the comparatively small group of hi-fi music/electronic enthusiasts.

...COMMENT

STEREO—AT LAST !

Regular stereo transmissions started from the BBC on July 30. At present, the ration is two to three stereo programmes each day, using the fully compatible pilot-tone system (as used in the U.S.A., Germany, France, Italy and Holland) which was previously tested in the Music Programme.

The stereo service is broadcast from the Third Network v.h.f. stations at Wrotham and Dover, but it is planned to increase coverage to Sutton Coldfield within a year and then to Holme Moss some months later.

Emphasis will, naturally, be on music—both recorded and live—and it is hoped to cover the Promenade Concerts during the forthcoming season. All stereo programmes will be identified in the *Radio Times*.

Further extensions of the service, both in relation to coverage and character of programmes, will be considered in the light of public reaction and the economic resources available.

MINI SOLDERING IRON

Rawlplug Co. Ltd., Rawlplug House, 147 London Road, Kingston, Surrey, are marketing a miniature soldering iron for light use. Its copper alloy tip is ready for use in 2 minutes, and it reaches 750°F in less than 4 minutes. The cork handle is a good insulator which is also very comfortable to hold over long periods, and which enables the soldering iron to be laid on the bench without the danger of the tip touching the surface. Obtainable from Ironmongers and Hardware shops, the Mini iron costs 19s. 6d.

R.S.G.B. NATIONAL MOBILE RALLY

The R.S.G.B. National Mobile Rally is to be held by kind permission of His Grace the Duke of Bedford, at Woburn Abbey, Bedfordshire, on Sunday, September 11, 1966. The park opens at 11 a.m. There are ample car parking facilities and there is a children's playground, pets' corner and a boating lake for the youngsters.

The talk-in stations will be GB2VHF and GB3RS on 2m (144.86 Mc/s), 4m (70.260 Mc/s), 80m s.s.b. (3.75 Mc/s) and 160m (1940 kc/s).

SECAR SECONDARY RADAR SYSTEM

This photograph shows the prototype Marconi/Thompson SECAR control and indicator unit, mounted above a standard radar (PPI) display. The display screen shows secondary radar responses with a video-map of the airways and coastline of southern England and parts of France, Belgium and Holland.

Secondary radar is a ground-to-air data link designed to provide the radar controller with the identity and height of any aircraft, to supplement the "plan position" information given by the normal, or "primary" radar.



Station interference

WITH reference to N. D. Mugford's letter in July 1966 *PRACTICAL WIRELESS*.

It's not only the Communist Bloc that is responsible for the chaos on the short waves.

The Voice of America with its excessive bandwidth caused through deliberate mis-operation as a counter to jamming is responsible for a lot of interference. There is not a single Missionary radio station that beams to the U.K. that does not suffer either the whole time, or part time from V.O.A. or A.F.R.S. interference. Even the 260 kW Bonaire station suffers.

Radio Free Europe and Radio Liberty also offend as they attract jamming. HCJB was coming through the best for some time on 15.115 Mc/s. until one of the latter opened up nearby, causing HCJB to shift to 15.325 Mc/s, where reception is not so good.

The BBC also is not wholly blameless. Despite protests the interference at critical times to the transmissions of Transworld Radio Monte Carlo on 7.26 Mc/s is notorious.

Lastly, some commercial operators of communication transmitters are also to blame. I'm certain that while the bulk of such interference is image reception, some is not.

Present day high power transmitters have taken the interest out of the hobby, and the shortwaves are being misused for a verbal slanging match between East and West. Missionary radio stations together with the stations belonging to some of the smaller nations are an oasis in an otherwise dry and uninteresting territory.

D. O. French.

Stroud Green,
London, N.4.

Can anyone help?

I WOULD like to purchase a copy of *PRACTICAL WIRELESS* for October 1964 and wonder if any of your readers could oblige, I will gladly refund the postage with the price of the book.

G. E. Newman.

4 Laburnum Grove,
Hayling Island,
Hants.

★ ★ ★


I SHALL be grateful if any reader will sell me a copy of "Amplifiers, Design and Construction" by F. J. Camm since all efforts to purchase through normal trade channels have failed.

Cyril H. Rowe.

16 Ty Fry Road,
Rumney,
Cardiff.

THE MULTITEST

MULTIMETER • MULTIVOMETER
 D.C. BRIDGE • A.C. BRIDGE
 SIGNAL TRACER • SIGNAL
 INJECTION TESTER • INSL

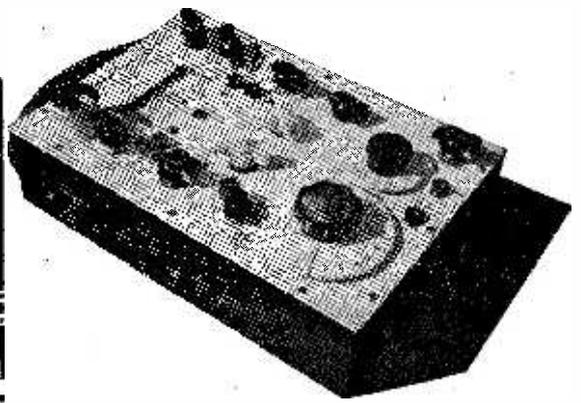

PART II

R.D. OWEN

CIRCUIT details of the multimeter section of this instrument were given last month along with details on how to work out the various shunt and load resistor values. In this part, the bridge section is discussed and constructional information is given on the complete instrument.

An important point to remember when constructing measuring equipment is that the accuracy of the instrument can only be as good as the components that are used in it. The author specifies high-stability 1% resistors for the bridge section and has achieved an overall accuracy of $\pm 3\%$ on most of the resistance ranges. He has achieved the same accuracy on the two lowest capacitance ranges, but has sacrificed accuracy on the higher capacitance ranges owing to the cost of the necessary components. This is not too serious as accuracy is not all that important on the higher ranges as often one only requires to know if a component is serviceable and not its precise value.

BRIDGE

A circuit diagram of the bridge section of this instrument appears in Fig. 6. Also included in this diagram are the three valve stages which are also


associated with the signal injection and tracing circuits. The bridge itself is fairly straightforward, making use of a single direct reading scale which carries all nineteen ranges. Null indication is by means of a magic eye (V2).

A full list of the bridge ranges was given in Part I (Fig. 2), but recapping there are eight resistance ranges from 4Ω to $40M\Omega$, five capacitance ranges from $400pF$ to $4\mu F$ and six inductance ranges from $40mH$ to $4000H$. All ranges are in multiples of 10.

CIRCUIT DESCRIPTION

The basic bridge circuits for resistance, capacitance and inductance are shown in Figs. 7a, 7b and 7c. Depending upon the range selected, one of the resistors R34 to R40, or R42, is used as a standard for one arm of the bridge on the inductance and resistance ranges. The standard in the other arm is then R43 for resistance, or C6 for inductance.

The $2.5k\Omega$ potentiometer VR3 is the power factor control. This gives an idea of the efficiency of the inductance being tested. D.C. resistance or leakage in the inductance causes a phase change relative to the phase of the a.c. if a pure inductance were present. The power factor control VR3 in effect

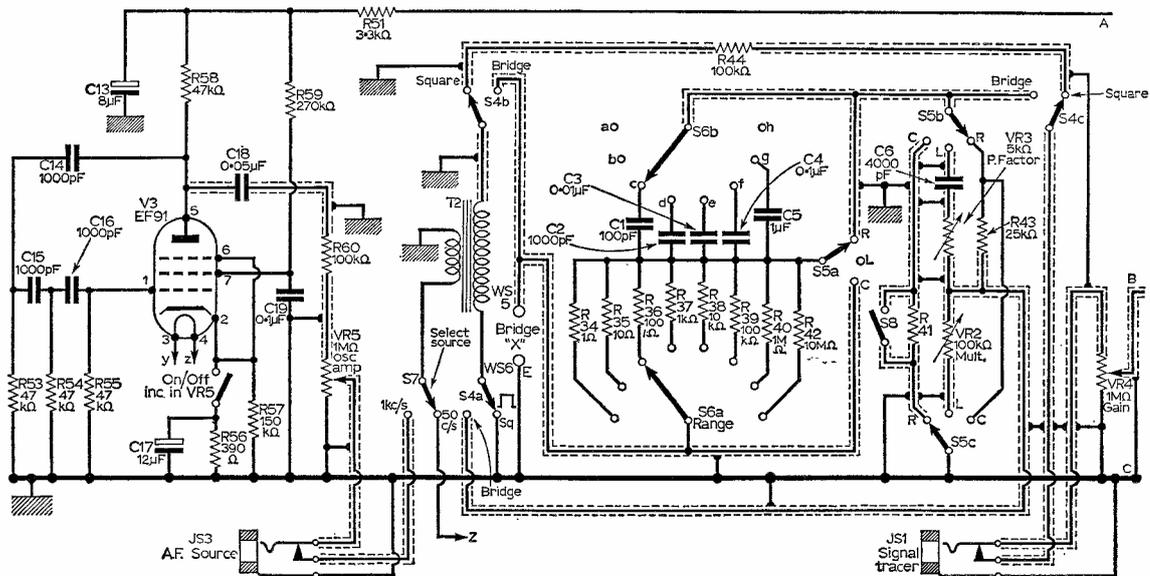

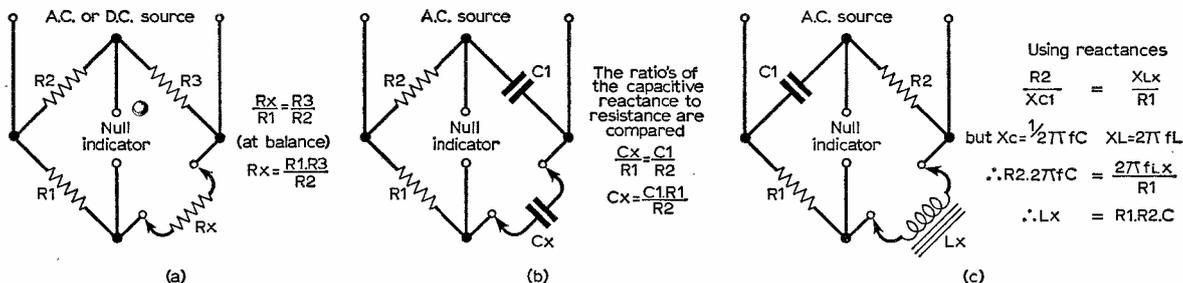


Fig. 7: Basic resistance (a), capacitance (b) and inductance (c) circuits as used in the bridge section. Circuit component references in these diagrams do not tie-in with those given on the main circuits.

varies the efficiency of the standard C6 and hence can be adjusted to produce the same phase shift as the inefficiency in the inductance being measured. In the author's unit the power factor control was only calibrated in resistance, since the actual power factor corresponding to a particular resistance depends upon the range to which the bridge is switched. If, for best null point, the power factor control is set at low resistance, then the power factor is obviously good, and vice-versa.

On capacitance ranges, C1 to C5 are standards in one arm of the bridge and R43 in the other. The positions of VR2 and the one standard are interchanged on the capacitance ranges so that the direction of the calibrations on VR2 scale remain constant.

The bridge circuit is arranged so that one "X" connection is in fact earth, to minimise external pick-up.

The 50c/s bridge source is derived from the heater winding of the mains transformer and is isolated and stepped up by T2; a three-to-one transformer. The 1kc/s source is derived from a phase shift oscillator employing an EF91 (V3) and is fed to the bridge via a switched jack JS3. This permits the 1kc/s supply to the bridge to be cut-off and used as a signal injector.

The null indicator part of the bridge circuit

consists of a pentode amplifying stage V1, coupled to a magic eye indicator V2. The connection with the actual bridge is via a switched jack, JS1, which serves to disconnect the bridge and allow the null indicator to be used as a signal tracer when a jack plug is inserted.

SIGNAL INJECTOR

The phase-shift oscillator V3 is switched on and off by the switch included in the amplitude control, VR5. When the switch closes it connects R56 and C17 in parallel with R57, which is left in circuit when the oscillator is switched off to avoid cathode poisoning of the valve.

If a square wave output is desired S4 is switched to "square" and the output taken from the monitor socket. In this position V3 is then connected to V1 via step-up transformer T2 (bridge is disconnected) which gives a very large voltage swing at the grid of V1. The valve "bottoms" when the grid voltage exceeds 2V positive, and the valve cuts off when it goes more than 2V below the zero line. The output of the oscillator is thus squared by the limiting action. Further squaring is achieved by zener diode D1, which is in the output side of V1. This shorts out all negative and positive excursions in excess of 6V.


The 50c/s square wave output can also be used for synchronising purposes, testing amplifiers in conjunction with an oscilloscope and for signal injection into r.f. circuits since it has a high harmonic content.

SIGNAL TRACER

The pentode amplifying stage, V1, has a gain of about 350. For visual indication in signal tracing the output of V1 is rectified by D2, and the resulting negative voltage is smoothed by R48 and C10 before being applied to the grid of the magic eye. Null point (maximum "opening" of the magic eye) corresponds to minimum negative grid voltage.

An external amplifier or a crystal earpiece are advised for signal tracing, whereas the magic eye gives the better null indication.

Fig. 6: Circuit diagram of the bridge section of the multimeter. Only one connection has to be made to the multimeter section of this instrument and that is to R33 from the h.t. rail—the junction of C11 and R52. The circuit for the multimeter section was given in Part I, Fig. 1 (last month).

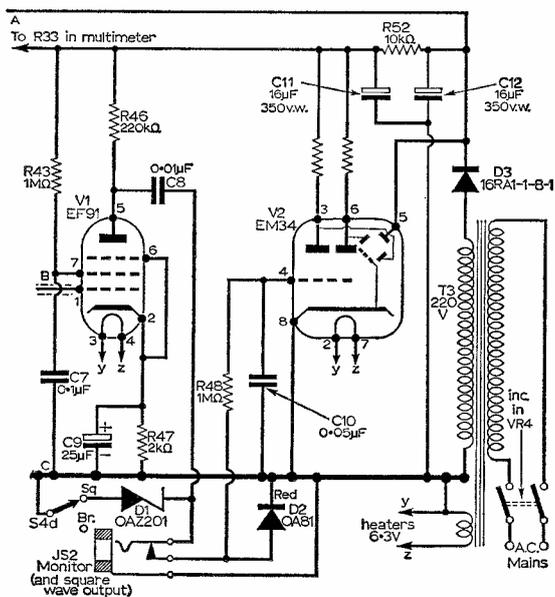

R.F./A.F. PROBE

S9 is the r.f./a.f. selector switch. On a.f. it simply connects the probe tip, via isolating capacitor C22 (500VW) to the output jack JS4. This is connected by a screened lead (terminating in jack

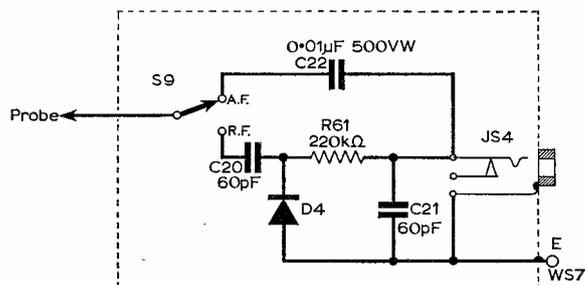


Fig. 8: Circuit of the probe attachment.

plugs at both ends) to the "signal tracer" input, JS1. When switched to r.f. the signal is fed via a 60pF capacitor to diode D4 which functions as a detector. The output is "smoothed" (to remove the r.f. component) by R61 and another 60pF capacitor and then fed to jack JS4. WS7 is the earth connection to the probe and should be connected to the chassis of the set being tested. (Beware of live chassis sets!)

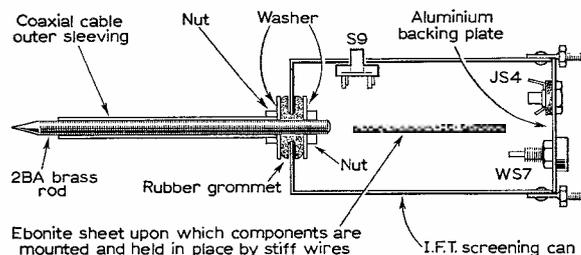


Fig. 9: Cross-sectional drawing of the author's metal work for the probe.

CONSTRUCTION

No difficulties should arise in constructing this instrument, particularly if readers use one of the universal chassis with the separate sides and top. One can, of course, do the "tin bashing", but the author found the manufactured chassis to be more robust than the home-built units. Also, one can purchase one with a hammer finish which gives the finished job the professional touch. These chassis are available through most dealers: the author's unit, which measures 10 x 7 x 3in., came from Home Radio Ltd., 187 London Road, Mitcham, Surrey.

The completed unit is rather compact and the author recommends the instrument should be constructed in the following sequence: multimeter section, bridge section, power supply, power feed lines, etc., and finally mounting the separately constructed sub-chassis for V1 and V3. Following this sequence will minimise disturbance to wiring already done.

The switch layout used by the author is illustrated in Fig. 3 and the position of the main under-chassis components is shown in Fig. 5: both of these illustrations appeared in Part I of this article. Layout is not critical and can be varied to suit individual

readers' needs. One should, however, be careful to ensure that the major components (including the switches) all go in without touching one another before drilling any holes.

MARKING THE CONTROLS

Several methods are available to the constructor for marking the front panel controls nowadays, including the instant, self-adhesive lettering. The range switch S6 will probably cause the most difficulty as nineteen ranges have to be included. A close-up of this switch is illustrated in Fig. 10. This gives the information that has to be written on the card which can be covered with a varnish or some perspex before it is glued to the control knob.

The companion control VR2 may also cause a little trouble, as again one has to prepare a card.

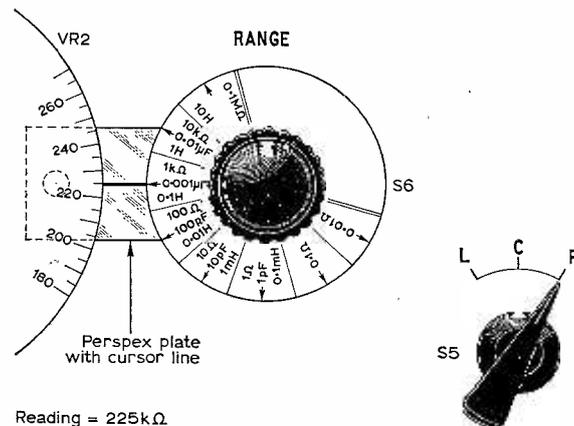


Fig. 10: Close-up of the range switch and the multiplier.

One should first find the electrical maxima and minima, using an ohmmeter. This will give you the total angle of rotation, which has to be divided into 80 equal divisions; every second division being drawn longer than the rest since it corresponds to tens. The scale is thus calibrated in fives and tens from zero to four hundred.


It is extremely important that the calibration markings are accurately drawn since the accuracy of the bridge depends upon it. Reference to the front panel illustration shows how the two scales are arranged. The perspex cursor is simply glued to the front panel.

To read the value of a component under test, one simply adjusts for null indication and then multiplies the reading on the range scale (S6) by the reading on the multiplier scale (VR2).

COMPENSATION RESISTOR VALUE

To obtain the correct value for R41, the bridge section should be switched to the 0-400 pF range, switch S8 closed and the 1kc/s bridge source selected (with maximum gain). The null indicator gain is then reduced until the course section of the magic eye is about three-quarters closed. The multiplier is then rotated until the null point is found; the null indicator gain being increased as necessary to provide a more sensitive indication. The correct value for R41 in kΩ is one quarter of the indicated capacitance.

continued on page 351

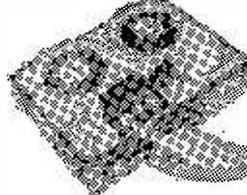

TAPE RECORDER BARGAIN

Capstan Driven, 5 Transistors

SPECIFICATION: 200/7,000 c.p.s.—400 mW. output—double track—twin speed (3 $\frac{1}{2}$ and 7 $\frac{1}{2}$)—fast wind time 5 min.

spool gives one hour playing with standard tape, weight 7 lb. Size 8in. x 11in. x 3in. Complete with batteries, microphone—tape spool and instruction manual. Nothing to go wrong if you use a good tape and keep heads clean. Demonstration gladly given at our Croydon shop. Special Snip Price This Month £11.11.0, post and insurance 6/6.

HI-FI SPEAKER BARGAIN

12in. High fidelity loudspeaker. High flux permanent magnet type with either 8 or 15 ohm speech coil. Will handle up to 10 watts. Brand new, by famous maker. Price 29/6, or with built-in tweeter 35/- plus 3/6 post and insurance.



MAINS POWER PACK

MAINS POWER PACK designed to operate transistor sets and amplifiers. Adjustable output 6V-9 to 13 volts for up to 500mA (class B working). Takes any of the following batteries, PRL, PP3, PPA, PP6, PP7, PP9, and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor, 5,000 and 500 mfd. condensers. zener diode and instructions. Real snip at only 14/6, plus 3/6 post.

ACOS GP83 TURNOVER PICK-UP CARTRIDGE



For Stereo—LP—and 78 records fitted with two Styl. Diamond for LPs, Sapphire for 78s. This is mounted in standard replacement for most record players using Garrard—B. S. R.—Collaro etc., etc. The regular price of this cartridge is 55/-. We offer these new and perfect for 15/- (less than the price of styl.) plus 2/- post and insurance.

DEAC RECHARGEABLE BATTERIES

These nickel cadmium cells have negligible internal resistance. Will deliver current you require, reduce distortion and are completely reliable. They may be recharged indefinitely. Replacements for PP3, 37/-, U7, 12/6, U2 32/6, PP9, 125/- or send for list.



AUTOCHARGER Battery Operated



An excellent unit for playing 33's and 45's. Just right for a portable player. Complete with Cosmoord crystal cartridge and sapphire stylus. This also has pick-up lock and auto stop button. Size 10 in. x 8 in. Clearance 3 in. above, 2 $\frac{1}{2}$ in. below. Price only 89/6 plus 6/- carr. ins.

TWO WAY RADIOS

Gives communication over 1 mile. FULLY transistorised—crystal controlled, built-in telescopic aerial—press button operation—PP3 batteries—pair instruments—complete and ready to use £8.19.6 plus 5/- post and insurance. Big 5-mile range model £12.19.6 plus 5/- post and insurance. These cannot be operated in U.K.



MOVING COIL METER BARGAIN

Panel meters are always being needed and they are jolly costly when you have to buy them in a hurry—so you should take advantage of this offer: 2in. moving coil flush mounting meters only 5/6 each or 48/- a dozen. These are actually R.F. meters and cost about £3 each but if you don't want them for R.F. then all you have to do is to remove the thermo-couple and you will have a 2-3 m.a. meter which you can make into almost anything by adding shunts or series resistor. These are ex-government, of course.

TOURMASTER CAR RADIO




Medium and long wave (push button change) perm. tuning—six transistors including power output—undoubtedly one of the nicest car radios available today—currently being sold at 14 gns., our price £9.19.6. Not a Kit but built and ready to use.

GOOD COMPANION Mk V


Saves you work—It's partly built.

Like its predecessors this latest Companion has full performance such as only a good wooden cabinet and hi-fi speaker can give, and due to its being partly built you will have it going in an evening. Note these features:
● All Mullard Transistors including 3 x AF17.
● Two tone Cabinet, size 11in. x 8in. x 3in.
● All circuit requirements Push Full output—A.V.C. and feed back etc.
● Printed circuit board all wired only connections, e.g., to Volume control—WIC. Switch and Tuning Condenser
● Pre-aligned IF stages complete with full instructions. Price only £4.12.8 plus 6/6 post and ins.

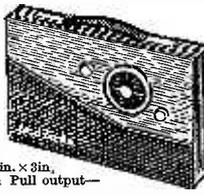


NIM COMPUTER

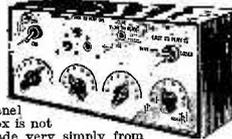This computer will play games and do simple tricks and will provide endless amusement as well as education into computerisation. Kit comprises all the components the printed front panel and full instructions. The box is not included but this can be made very simply from plywood. Price £4.17.6 plus 3/6 post and insurance.



ADJUSTABLE TIMER AND DELAY MECHANISM

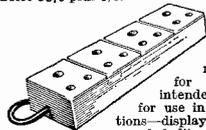This is a fine American made unit designed for precision. The time period is adjusted by a knurled screw. The delay period can be set anywhere from hours or seconds. The end of the delay operates a micro switch and resetting can be remote controlled or manually reset. The unit is for wall mounting and is approx. 4in. x 7in. x 4in. Price 39/6 plus 3/6.



DIS-BOARDS FOR QUICK MAINS

These are 4 x 15 amp. sockets mounted on a metal box already intended for mounting on bench or wall—intended for use in workshops—laboratories—exhibitions—displays, etc. They avoid the use of dangerous bakelite multipugs and adaptors and other hook-ups. Price only 19/6 plus 3/- post and insurance.



CORONET PARCEL

Here's a bargain for you—parcel comprises: plastic case, printed circuit board, two dial knobs, volume control, carbon socket and plastic carrying case, all for 5/6 plus 1/6 post.




AUTOCHARGER BARGAIN—GARRARD AUTO RECORD PLAYER Model 2000

This is one of the latest products of the World's most experienced maker of fine record reproducers—its superior features include—automatic playing of up to 8 mixed size records—stopping and starting without rejecting—manual playing—pick-up pivots to give low stylus pressure—large diameter turntable for dropping position and stylus pressure. Size is 13 $\frac{1}{2}$ in. x 11 $\frac{1}{2}$ in. clearances 4 $\frac{1}{2}$ in. above 2 $\frac{1}{2}$ in. below—fitted with latest hi-compliance cartridge for stereo—and mono., L.P. and 78. Supplied complete with mounting template and service sheet. Offered this month at the Special Snip price of £8.9.6 plus 7/6 carriage and insurance.



STUPENDOUS OFFER—£11 for £2

The Princess superhet described below is a very fine little set that has been carefully designed for high performance. Only recently (under another name of course) this was on offer in many radio shops, for £10.19.6, but we have been fortunate in obtaining the parts at a very low price and now pass this saving on to you. If you act quickly you can purchase this for only 39/6 plus 3/6 post and insurance. Note these features:
● Long and Medium Wave ● Long clear dial with travelling pointer and slow motion drive ● Push pull output approximately 350 mw ● A.V.C. and feed back ● Dust cored H.Q. I.F. transformers ● High selectivity ferrite aerial ● Six tested transistors ● Printed circuit board for fool-proof assembly ● Economy output circuit gives long life from PP3 battery ● Permanent magnet moving coil speaker ● Cabinet size 4 $\frac{1}{2}$ in. x 3in. x 1 $\frac{1}{2}$ in. You get over 100 parts (list value over £10). In fact everything you need and easy to follow wiring and alignment instructions. Don't miss this wonderful offer. Make up several while you have the chance. Use them as presents and you'll be loved for ever. Made up chassis 10/- extra. Battery 1/9 extra. Data purchased separately 2/6.

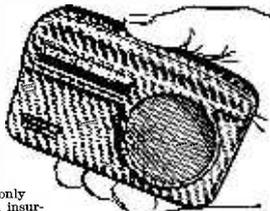

ELECTRICAL BARGAINS

SWAN KETTLE ELEMENTS



Made by famous "Best" company also suitable for most kettles—1800 watts 230/250v—normally 30/- each—our price 18/6 each.

G.E.C. I3A SWITCHED SOCKETS

Suitable for ring mains etc. takes the modern fused plug—surface or sunk (flush) mounting type 4/9 each, 54/- doz.

750W INFRA-RED WALL HEATER



750 watt silica enclosed element elliptical polished reflector—bracket mounting—pull-cord switch. Money back guarantee.


Made to sell at 24. You can buy at only 32/6. P. & Ins. 3/6.

CIRCULAR FLUORESCENT

Brings sunshine into your home 150 watts of light but uses only 40w. Beautiful fitting with glass, non-plastic centre, fluorescent tube and choke control. Made by Philips. Regular price £4.13.0. Special Bargain Price, 65/- plus 8/6 carr. and ins. Please state colour of glass centre, white, pink, blue, red, black, yellow or cream. Also whether plug into lamp holder or ceiling mounting model. 80 watt model, 99/6 for callers only.



FLUORESCENT LIGHT KITS

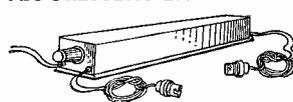

Our 80 watt kit for 5ft. fluorescent tube is the best money can buy it contains latest slim line (easy to hide away) choke made by one of England's largest companies—starter—tube ends—two chrome clips. All wired up ready—fit it in a jiffy with just a few screws—price only 22/6 complete plus 4/6 post and ins., or complete as listed but not wired up. 17/6 plus 4/6.

SEMI-CONDUCTOR BARGAINS

Type No.	Price	Type No.	Price	Type No.	Price
2N1737	15/-	MAT101	8/6	OC71	4/-
2N1728	100/-	MAT120	7/9	OC72	5/-
2N1742	25/-	MAT121	8/9	OC73	6/-
2N1747	25/-	OA5	5/-	OC75	5/-
2N1748	10/-	OA10	6/-	OC77	7/-
AC307	9/-	OA47	3/-	OC78	5/-
AC127	9/-	OA70	2/-	OC78D	5/-
AC197	8/6	OA79	2/6	OC81	5/-
ACY18	5/6	OA81	2/6	OC81D	5/-
ACY19	6/6	OA85	3/-	OC82	5/-
ACY20	5/6	OA90	2/6	OC83	5/-
ACY21	6/-	OA91	2/6	OC84	6/-
ACY22	4/6	OA200	3/3	OC139	8/6
AF114	7/-	OA202	4/3	OC140	12/6
AF115	6/6	OC22	10/-	OC170	5/-
AF116	7/-	OC23	17/6	OC171	6/-
AF117	5/-	OC24	22/6	OC200	9/-
AF118	12/6	OC25	7/6	OC201	19/6
AF139	17/6	OC29	15/-	OC202	13/6
AF186	19/6	OC32	16/-	OC203	12/6
AF212	15/-	OC33	12/6	OC271	19/6
AS221	15/-	OC38	15/-	ORP12	8/6
BC107	14/6	OC42	6/6	ORP60	5/-
BY100	5/6	OC44	5/-	SB075	6/6
BY123	7/6	OC45	4/-	SB305	8/6
MAT100	7/9	OC70	4/-	SB251	10/-

THERMOSTATS

Type 'A' 15 amp for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob, quickly adjustable from 30°—50°F. 9/6 plus 1/- post. Suitable box for wall mounting, 5/- P. & P. 1/-.
Type 'B' 15 amp. This is a 17in. long rod type made by the famous Svanic Co. Spindle adjusts this from 50-550°F. Internalscrew allows the setting so this could be adjustable over 30° to 1,000°F. Suitable for controlling furnace, oven, kiln, immersion heater or to make flammestat or fire alarm, 3/6 plus 2/9 post and insurance.
Type 'D'. We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amps. Has many uses, one of which would be to keep the loft pipes from freezing if a length of our blanket wire (16 yds. 10/-) is wound round the pipes. 7/6, P. & P. 1/-.
Type 'E'. This is a standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature, 7/6 plus 1/- P. & P.

ELECTRONICS (CROYDON) LIMITED

102/3 TAMWORTH ROAD, CROYDON, SURREY (Opp. West Croydon Station)
post orders to: Dept. PW, SPRINGFIELD ROAD, EASTBOURNE, SUSSEX

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/9.

Make Your Ability PAY

UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let ICS's tuition develop your talents and help you to success.

STUDY IS EASY with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. MODERATE FEES INCLUDE ALL BOOKS.

Take the right course now . .

ADVERTISING & ART

Copywriting, Cartooning
Layout and Typography
Commercial Illustrating
Oil & Water Colour

BUILDING & CIVIL ENGINE

Architecture, Bricklaying
Building Construction
Builders' Draughtsman
Builders' Quantities
Interior Decoration
Quantity Surveying
Heating & Ventilation
Carpentry & Joinery

COMMERCE

Book-keeping
Accountancy & Costing
Business Training
Office Training
Purchasing, Storekeeping
Secretarialship
Shorthand & Typing
Computer Programming
Small Business Owners

DRAUGHTSMANSHIP

Architectural, Mechanical
Drawing Office Practice

ELECTRONICS

Computers
Electronic Technicians
Industrial Electronics

FARMING

Arable & Livestock
Pig & Poultry Keeping
Farm Management & Accounts

GENERAL EDUCATION

G.C.E. subjects at Ordinary &
Advanced Level
Good English
Foreign Languages

HORTICULTURE

Home Gardening
Park Gardening
Market Gardening

MANAGEMENT

Business Management
Hotel Management
Industrial Management
Office Management
Personnel Management
Public Relations (I.P.R.)
Transport Management
Works Management
Work Study
Foremanship

MECHANICAL & MOTOR ENGINE

Engineering Maths.
Diesel Engines, Welding
Industrial Instrumentation
Workshop Practice
Refrigeration
Motor Mechanics, etc.

POLICE

Entrance Examination
Police Promotion (Educ. Subj.)

PHOTOGRAPHY

Practical Photography

RADIO, TV & ELECTRICAL

Servicing & Engineering
Radio Construction (with Kites)
P.M.G. Certificates
Telecommunications
Electricians'
Electrical Contractors'

SELLING

Company Reps.
Sales Management
Marketing

WRITING FOR PROFIT

Television Scriptwriting
Short-story Writing
Free-lance Journalism

INTENSIVE COACHING for all principal examinations
—G.C.E., Secretaryship, Accountancy, Engineering,
Work Study, Management, Radio, Architecture and
Surveying. Special course for G.C.E. French Oral Test.

Member of the Association of British Correspondence Colleges

Start today the I.C.S. way!

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on.....

Name.....

Address.....

Occupation..... 9.66

INTERNATIONAL CORRESPONDENCE SCHOOLS

CONDENSER BARGAINS! ELECTROLYTIC

32µF .. 1.5 volt	25µF .. 6 volt	100µF .. 10 volt
25µF .. 3 volt	30µF .. 6 volt	1µF .. 50 volt
2µF .. 3 volt	2µF .. 9 volt	5µF .. 50 volt
8µF .. 3 volt	6µF .. 9 volt	8µF .. 50 volt
20µF .. 3 volt	20µF .. 9 volt	2µF .. 84 volt
100µF .. 3 volt	64µF .. 9 volt	5µF .. 70 volt
200µF .. 3 volt	250µF .. 9 volt	4µF .. 100 volt
2µF .. 6 volt	10µF .. 10 volt	2µF .. 150 volt
10µF .. 6 volt		8µF .. 275 volt

All at 1/- each or 9/- per dozen.

3µF .. 12 volt	8µF .. 15 volt	4µF .. 25 volt
4µF .. 12 volt	10µF .. 15 volt	25µF .. 25 volt
6µF .. 12 volt	30µF .. 15 volt	32µF .. 25 volt
10µF .. 12 volt	50µF .. 15 volt	64µF .. 25 volt
25µF .. 12 volt	100µF .. 15 volt	150µF .. 25 volt
100µF .. 12 volt	750µF .. 15 volt	16µF .. 30 volt
200µF .. 12 volt	2.5µF .. 25 volt	6.4µF .. 40 volt
6µF .. 15 volt	3µF .. 25 volt	12.5µF .. 40 volt

All at 1/3 each or 11/3 per dozen.

5,000µF .. 12 volt 4/- each 500µF .. 25 volt 3/- each

PAPER CONDENSERS

	each	doz.	100	1000	
-001µF	500 volt	7d.	5/3	29/5	27/5/0
-001µF	1000 volt	8d.	6/9	37/6	29/7/6
-002µF	500 volt	7d.	5/3	29/5	27/5/0
-015µF	300 A.C.	9d.	6/9	37/6	29/7/6
-005µF	750 volt	7d.	5/3	29/5	27/5/0
-02µF	350 volt	6d.	4/6	25/-	26/5/0
-02µF	500 A.C.	1/3	11/8	62/8	215/12/8
-1µF	350 volt	7d.	5/3	31/3	27/10/3
-1µF	750 volt	8d.	6/9	37/6	29/7/6
-25µF	350 volt	10d.	7/6	41/8	210/8/0
-5µF	150 volt	1/-	9/-	50/-	212/10/0
-5µF	350 volt	1/3	11/8	62/6	215/12/8
-5µF	500 volt	1/6	18/6	75/-	218/15/0

SILVER MICA, CERAMIC, POLYSTYRENE, Mixed types, values 10/- per 100.

RESISTORS, 1/2 watt to 3 watt. Close Tolerance. Mixed values. Polythene wrapped on cards of 10. Fantastic value! Only 50/- per 1,000 plus 5/- post and packing. Resistors for Transistor Work. Low values, 1/2 watt, 5% tolerance. Long leads. Excellent quality. 50 for 10/-. Our selection only.

TRANSISTORS. Untested, unmarked. Excellent value at 12/6 for 50, 21/0/0 for 100. I.B.M. Computer Switching Transistors. Very small. NPN or PNP. 6 for 10/-.

NKT 124/5 Switching Transistors. 6 for 10/-.

Diodes 1/- each, 9/- per dozen, 50/- per 100, 212/10/0 per 1,000.

SIGNAL INJECTOR. Transistors, components, circuit, to make, 10/- only.

REV. COUNTER. Transistors, components (excluding meter), 10/- only.

LOUDSPEAKERS. 3in., 4in. or 5in., 10/- each.

MICROPHONES. Magnetic, Lapel. 10/- each with plug and lead.

EARPIECES. Magnetic. 5/- each with plug and lead.

PICK-UP HEADS. MONO 14/-, STEREO 21/-. DIAMOND STEREO 28/9 ACOS MAKE. G. F. MILWARD, 17 PEEL CLOSE, DRAYTON BASSETT, Nr. TAMWORTH, Staffs. Phone: Tamworth 2321. Orders Under 10/- please include 1/- post and packing.

Richard Allan
HIGH FIDELITY

Module



SPECIFICATION—Bass Unit: Natural resonance 40 c.p.s. Flux density 14,000 Gauss. Total flux 56,000 Maxwells. **Tweeter Unit:** Flux density 5,000 Gauss. Total flux 9,000 Maxwells. Overall: Height 11in. (28 cm), width 6in. (16.5 cm), depth 2in. (5.4 cm), weight 5 lb. (2.3 kg). Power handling 10 watts in recommended enclosure, Impedance 5, 8 or 15 ohms.

TECHNICAL DETAILS:
The unit is a compact and self contained loudspeaker system which only needs to be fitted into a simple cabinet of the recommended design to produce a high fidelity loudspeaker of the highest quality.
The unit consists of a 5in. bass unit, 4in. tweeter and crossover network mounted on a duralumin plate which forms the front panel of the complete enclosure.
The method of assembly of the module is unique in that the cone and synthetic rubber surround of the 5in. bass unit are mounted directly on to the duralumin front panel and the ceramic magnet is supported on substantial pillars attached to the panel. The conventional chassis with all its disadvantages is thus eliminated.
The tweeter is a special version of the 460T unit with a doped cambric surround and extremely light suspension system.
The crossover network is a five element circuit using ferrite cored inductors and reversible electrolytic capacitors mounted on a printed circuit board.
Where larger power handling is required several units may be mounted in a larger cabinet, multiple units may also be mounted in a column enclosure to form a high power handling, high quality line source. The unit may also be mounted directly into existing equipment or in cavities in walls etc.
The unit forms the drive system of the 'Minette' enclosure, for details see separate leaflet. Patents applied for.

Price £8 plus £1.59 tax

For further details contact:
RICHARD ALLAN
RADIO LIMITED
Bradford Rd., Gomersal,
nr Leeds, Yorks.
Tel: Cleckheaton 2442/3



—continued from page 348

Insertion of R41 should transfer the null point to 0pF when switch S8 is opened. If it does not, slight adjustment should be made to its value until it does. With R41 set correctly, capacitances as low as 2pF can be measured.


OPERATION

While it is not worth laying down strict operating details, it is probably worth pointing out that the 1kc/s source is best for low capacitance and inductance measurements and the 50c/s source for measuring low value resistors. Generally speaking, for all other values either a.c. source may be used, although one or the other usually gives a better null point.

When making insulation tests it is necessary to bridge the negative terminal to earth with a “jumper” and connect the test leads to WS3 and WS4.

Although the switch incorporated in the “ohms

Fig. 11: This crocodile clip come wander plug is ideal for capacitance measurements since it keeps the stray capacitance to a minimum.

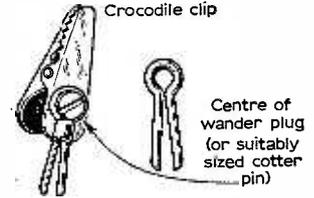

set zero” control has no effect on most ranges, one must be careful to ensure that it is left open while measuring a.c. voltages as if closed it would shunt the meter through R16, T1 and R17. The control must, however, be closed for alternating current measurements.

The circuit diagram of the multimeter section given last month is incorrect. The lead at present shown connected to the 2.5V position of S1a should, in fact, go to 0.1mA position on the same switch wafer; the 2.5V position is blank (no 2.5V range on a.c.).

Transistorised Indicators

—continued from page 343

pair of low impedance headphones soldered to an old bulb screw. It should be possible to hear, at good strength, a local Band I television transmission, sound and vision. The frequencies for these are given in the table. Obviously, given the 1Mc/s points, a single known identification of any point on

★ components list

A.C. Probe:	Receiver-Oscillator:
R1 75Ω	R1 3.3kΩ
C1 0.001μF 1,000VW	R2 4.7kΩ
C2 10μF 9VW	R3 2.2kΩ
D1, D2 OA81	VR1 25kΩ miniature
Tr1, Tr2 OC72 or near equivalent	C1 0.1μF
Torch Ever-Ready 0158, with battery	C2, C3 4,700pF sub-min ceramic
Bulb 6 volt, 0.1A	C4 2,000pF tubular
Misc. Empty Ronson Multi-fill refill, paxolin, Mazda octal valve base. 14 s.w.g. wire	C5 10pF Oxley SMT9/10.9 printed circuit
	C6 25pF Jackson C804
	C7 5pF tubular ceramic
	Tr1 BSY26
	Tr2, Tr3 OC72 or near equivalent
Audio Monitor:	D1, D2 OA81
R1 100kΩ	Bulb 6 volt 0.06A
R2 10kΩ	RFC See text
R3 4.7kΩ	S1 See text
C1 0.1μF 100VW	L See text and Fig. 7
C2 1μF 9VW	Misc. Three Radio-spares ‘Normal’ type coax plugs, one coax socket, bulb holder, aerial socket, knobs, 4.5 volt 1289 battery, paxolin.
C3 10μF 9 VV	
D1, D2 OA81	
Tr1, Tr2, Tr3 OC72 or near equivalent	
S1 On-off, single pole	
Bulb 6 volt, 0.06A	
Misc. Bulb holder, paxolin, 6 or 9 volt battery	

the scale will enable the whole range to be calibrated.

The C range can be used as a reference for the other two ranges. The 2nd harmonic of a 27Mc/s signal will be heard, or will cause the bulb to glow brighter, at precisely 54Mc/s on scale C, and will correspond to a pencil mark on range B representing 27Mc/s. If the signal is 27.5Mc/s, the harmonic will then coincide with 55 on range C, and will be

BAND I TELEVISION FREQUENCIES

Mc/s		
Vision	Sound	
45	41.5	Crystal Palace, Divis.
51.75	48.25	Holme Moss, North Hessary Tor, Truleigh Hill and Dover, Londonderry, Rosemarkie.
56.75	53.25	Kirk O'Shotts, Norwich, Rowridge, Blaen Plwyf.
61.75	58.25	Sutton Coldfield, Sandal, Meldrum, Folkstone and Les Platons.
66.75	63.25	Wenvoe, Pontop Pike, Douglas, Orkneys.

half way between divisions on Range B. A 16Mc/s signal will appear at 16, 32, 48 and 64Mc/s. It is possible also, with a good length of aerial, to pick up several short-wave transmissions on ranges A and B, as further frequency checks. If a calibrated short-wave receiver is to hand, it may be tuned to the self-radiated characteristic hiss of the instrument's super-regen, as added confirmation of calibration points.

Finally, when satisfied that all dial markings are correct, the piece of paper may be removed, traced, and an inked scale made. When in use, a passive tuned circuit brought near the instrument's coil will cause bulb brilliance to dip, and a nearby oscillator will increase the brilliance of the bulb. The aerial socket can be utilized for very weak input signals, and for injecting a signal into other apparatus when the instrument is employed as a signal generator. ■

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times in GMT
Frequencies in kc/s

THE BROADCAST BANDS

by JOHN GUTTRIDGE

Austria: *Osterreichischen Rundfunk* (Wien IV, Argentinieistrasse 30a) now has a regular overseas service which follows the schedule pattern established during a long period of test transmissions. The station has been noted in Europe at 0900—1100 on 6,155/7,245/17,755 and 1500—1700 on 9,770/11,785/17,750.

Brazil: *Radio Bandeirantes* (Casilla Postale 372, Sao Paulo) has been sending out silk World Cup shields. *Radio Jornal do Comercio* (Rua Marquez do Reife, Pernambuco) may be heard after 2100 on 9,565. *Agencia National* (Setor Radio and TV, Casilla Postale 95, Brasilia) is believed to be using 14,730 instead of 14,690 for the 2230—2330 transmission over PSF.

Bulgaria: *Radio Sofia* (4 Bd. Dragan Zankov Street, Sofia) now uses 9,560 in addition to 6,070 for its European English transmissions at 1930—2000 and 2130—2200.

Colombia: *Radio Sutatenza* (Accion Cultural Popular, Aereo 1770, Bogota) heard at 2300 over HAGC, 5,075.

Cuba: *Radio Habana Cuba* (Apartment Postal 7026, Habana) now transmits in English at 0100—0330 9,525; 0330—0600 6,135; 1800—1900 17,735; 2010—2140 15,155 (Europe) and 2050—2150 15,300/15,340.

Czechoslovakia: *Radio Prague* (2 Vinohradská 12) has English at 0330—0430 on 5,930/7,120/7,345/9,795 and at 0100—0200 on same frequencies plus 11,910. There is a further English transmission at 1730—1830 on 5,930.

Denmark: *Radio Denmark* (Shortwave Department, Radio House, Copenhagen V) is now using 15,165 for its 1945—2015 and 2145—2215 transmissions.

Ecuador: *La Voz de los Andes* (HCJB) (Casilla 691, Quito) is now using 15,325/17,880 for the 1800—2400 transmission to Europe. English is at 1845—2000, 2100—2130 and 2330—2400. The morning European transmission is 9,645/11,910 and the new frequency of 6,025 between 0430—0630.

Finland: Finnish Broadcasting Company (Unioninkatu 16, Helsinki) has a DX programme on 9,555/11,805/15,185 at 1600—1700 on Fridays, 1215—1315 on Saturdays and on 6,120 at 2100—2200 on Fridays.

German Federal Republic: *Deutsche Welle* (Bruederstrasse 1, Postfach 344, Skoln) is now using 11,945/9,530 for the 0300—0340 English transmission. Other English transmissions affected by changes include 0845—0940 11,925/15,275/17,845; 1550—1630 17,875/15,295; 0130—0250 11,945/9,640; 0500—0540 11,890/9,735; 1510—1555 9,675/15,405/11,925.

Holland: *Radio Nederland Wereldomroep* (P.O. Box 222, Hilversum) now has one of the most attractive QSL cards. A special Spanish vocabulary for use when reporting on Spanish stations is available on application. Frequencies for English transmissions are 0020—0110 800 (Bonaire); 0130—0220 9,590 (Bonaire); 0730—0820 11,730/9,715/9,525; 1430—1530 17,810/15,425/6,020; 1900—2000 11,730/9,590/6,020; 2000—2050 11,730/9,590/6,020; 2100—2150 15,425/11,730; 2130—2220 15,220 (Bonaire).

Monaco: *Trans World Radio* (Rue de la Poste 5, P.O. Box 141, Monte Carlo) is now using the Radio Monte Carlo transmitter on 1,466 in the early morning and evening. English is at 2130—2230. The new frequency of 11,760 is being used for the Russian programme from 1805—1840 when it swamps the Voice of America transmitter on the same frequency.

Netherlands Antilles: *Trans World Radio* (5c Zootpannenweg, Bonaire) now has English 2115—2130 instead of 2115—2145 on 15,245. On Sundays there is a DX programme at 0330 on 11,820.


Radio New York Worldwide has moved its offices and studios to 485 Madison Avenue, New York, N.Y., 10022, U.S.A., and has changed its call sign from WRUL to WNYW. New transmitters are expected to be on the air next year.

U.S.A.: WWVH (Box 578, Puunene, Maui, Hawaii) has been heard at between 1150—1210 on 15,000 under the more powerful WWV. Both these stations are standard frequency time signal stations. Positive identification was possible due to the split second difference between signals at the receiver because of the different transmission paths.

Voice of America (U.S. Information Agency, 330 Independence Avenue, S.W., Washington 25, D.C.): Frequency usage for English to Europe is now 3,980 0300—0730, 1400—2345; 5,965 0300—0730, 1630—2200; 5,995/7,200/7,250/9,540/9,635/9,740, 0300—0730; 7,210 1500—2245; 9,565 1700—2245; 9,760 1700—2215; 11,760 0500—0730; 11,790 0300—0730, 1700—2200; 15,205/17,780 1400—2215; 15,290 1400—2245; 15,295 0600—0730; 1,196 0400—0415, 0500—0730, 1600—1830, 2200—2345.

—————

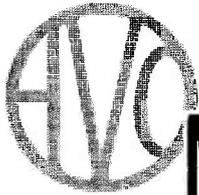A special word of thanks this month to the Swiss Broadcasting Corporation which is now supplying "On the Short Waves" with the script of its broadcast band Dx News programme. Help has also come this month from S. Shaw, J. W. Smith, S. Ormerod, M. Goodwin, A. B. Thompson, J. Clark, G. Roberts, P. de Lacey and Sweden calling Dx-ers.





MULTIMINOR Mk4

The Avo Multiminor Mk4 is the latest version of this well-proven multi-range measuring instrument. Designed and assembled to high standards of reliability, the Avo Multiminor offers simple yet instant range selection with a single rotary switch. There is only one pair of sockets for all measurements, and the scale plate is clearly marked for easy reading.

Accuracy is within the limits laid down in B.S.S. 89/1954 for up to 3 1/4" scale length industrial portable instruments.

Panclimatic construction enables the Multiminor to be used in all types of climatic conditions. The instrument is supplied in an attractive black carrying case, complete with interchangeable test prods and clips, and a multi-language instruction booklet.

Inexpensive Easy-to-use Pocket Size

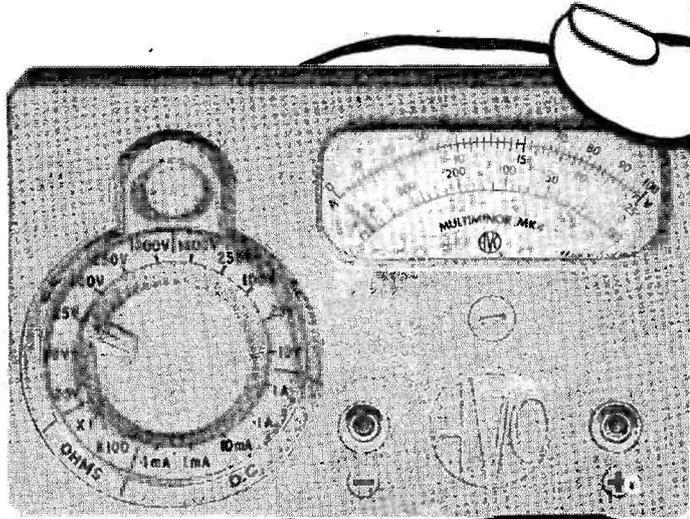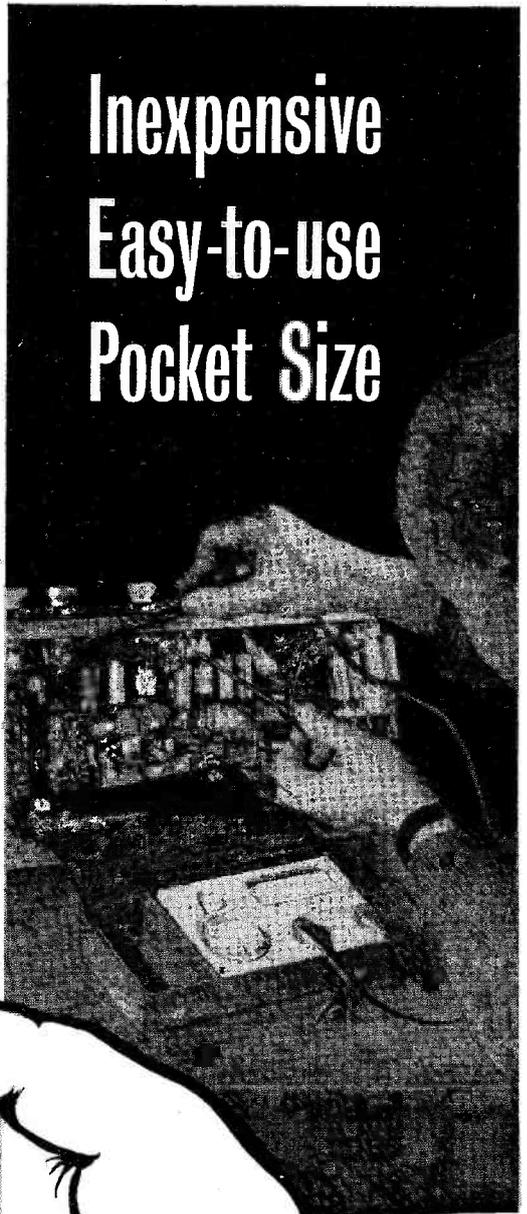

AVO INSTRUMENTS
DIVISION
**is now at
DOVER**

Write for full details.

AVO LTD AVOCETHOUSE · ARCHCLIFFE ROAD · DOVER · KENT Telephone: Dover 2626 **M** GROUP

KEDOCO TRANSISTORISED MODULES BRING TOP QUALITY TO HOME CONSTRUCTION HI-FI TAPE EQUIPMENT - AT INCREDIBLY LOW COST!

KEDOCO STAR FEATURES ■ Kedoco quality control ensures high product performance—always. ■ Transistorised modules ready-assembled for simple, speedy wiring into circuit. ■ Units operate from 12 volts—ideal for out-and-about recording. ■ Miniaturization of modules permits compact packaging. ■ Complete flexibility in design from seven basic units. ■ Money-back guarantee on all products.

(1) PRE-AMPLIFIERS

TAPE PRE-AMP SSTR/7. Compensates for the higher frequency attenuation present on all tape recordings to give a flat response output up to 15 kc/s. Makes a complete hi-fi tape amplifier if used in conjunction with a Miniclassic. All silicon transistor; zero hum; high gain and equalised at 7½ per sec. to give flat response output. Simple mod., described in accompanying instructions allows equalisation at all speeds. Suitable for all medium impedance heads, Collaro, B.S.R., etc. **Assembled 29/6.**

(2) MINICLASSIC PRE-AMP SSPA/50. Tone controlled high gain pre-amplifier designed specially for application with the SS3/9. All silicon transistor; zero hum; requires 12 volt + H.T. High fidelity complete with tone and volume controls. Separate inputs for crystal ceramic cartridge and radio enable Miniclassic to be used with ceramic cartridge or magnetic pickup. **Assembled 45/-.**

(3) MINICLASSIC SS3/10. High fidelity 4 watt main amplifier; ideal for use with SSTR/7 and makes complete tape amplifier, 16 c/s to 30 kc/s. Requires 12 volt + HT and will operate directly from crystal pickup. 6 transistors and two diodes all mounted on precision printed circuit board. Max. music power 4 watts into 3 ohm speaker. **Assembled 69/-.**

MINICLASSIC 12/12. Similar to SS3/10 but gives greater power. 12 watts R.N.S. **Assembled 89/-.**

MICROPHONES

CRYSTAL MICROPHONE. Complete with detachable desk stand; smooth slim round design with satin chrome finish, supplied with locking on/off switch, 7 ft. cable. Response 60 to 10,000 cps. **£1.18.0.**

OMNI-DIRECTIONAL DYNAMIC MICROPHONE. A beautifully finished professional microphone. Response 30 to 13,000 cps. Supplied with desk stand and cable **£4.3.0.**

LAPEL DYNAMIC MICROPHONE. 1" diameter. Very sensitive and supplied with long lead and plug. **12/6.**

LEVEL METER. Miniature moving coil meter specially produced for level indication in tape recording. **£1.4.9.**

(4) RECORD AMPLIFIER SSH9/3. Fully transistorised. High voltage HT rail derived from oscillator. Provides substantially constant current record signal. 1 volt input sensitivity. Power consumption 1mA at 12 volts and 1mA at 75 volts. Latter derived from erase oscillator SS013. **Assembled 45/-.**

(7) RECORD LEVEL PRE-AMPLIFIER & MICROPHONE AMPLIFIER SR8. **29/6.**

(5) TAPE OSCILLATOR SS013 Complete unit incorporating push pull transistor oscillator giving adequate erase power and recording bias. Ferrite pot core push-pull oscillator, frequency 50-60 kc. All silicon transistor. Provides high voltage (75v.) D.C. Rail for operating record amplifier. High efficiency unit requiring 12v. D.C. at 250mA. The only unit on the market at such an economical price. **Complete 69/-.**

POWER SUPPLIES. 12 volt, 1 amp and Zener stabilised 69/-. 30 volt, 3 amp designed to power Kedoco hi-fi 20 watt power amplifiers. **69/-.**

KEDOCO ELECTRONICS also manufacture a range of 20 watt hi-fi amplifiers. SS20/7, **£9.19.6.** SS20/8 de luxe, 11 gns. SS20/9 table model, 19 gns.

(6) LEVEL METER AMPLIFIER 42/3.

TV/FM Booster battery operated, bands I and 2, 32/3. De luxe mains model, band III, **45/-.**

Transistors, zeners, resistors and capacitors. See *Practical Electronics* for details of some of these other top-quality Kedoco transistorised products or send large 9d. stamped envelope for brochure.

All KEDOCO products are fully guaranteed. Should you not be completely satisfied we will immediately refund your money if purchases are returned within seven days of receipt.

KEDOCO ELECTRONICS

Subsidiary of Adams-Norcken Limited

Dept. PW, 76 Victoria Road, Swindon. Tel. Swindon(OSW3) 27660 Open 9 a.m.—6.30 p.m. weekdays. Wednesday early closing

NEW SHOWROOMS AND MAIL ORDER DEPARTMENT

Personal callers welcome.

HOME RADIO LTD. Dept. PW, 187 London Road, Mitcham, Surrey. Phone: MIT 3282

"Read about it!"

Translated into the Queen's English... "Read all about it!" The gentleman is referring to the fact that Reprint No. 12 of the Home Radio Catalogue is hot off the press. As always, its pages (all 210 of them) are packed with good things, things of absorbing interest to every radio and electronics enthusiast. No increase in price... better than ever value at 7/6, plus 1/6 post and packing. And remember, every copy contains five coupons, each value 1/- when used as directed. If you have never had the good fortune to own one of these famous components catalogues, or if your own copy is now a bit long in the tooth, send the attached coupon with your cheque or P.O. for 9/-. Our pleasure in sending you the catalogue will be exceeded only by your pleasure in receiving it.



Please write Name and Address in block capitals

Name

Address

Home Radio Ltd., Dept. PW, London Rd., Mitcham, Surrey

HHEY ho! It's been one of those months between 1.8 and 30Mc/s. Reports coming in from all over the country bear the same story as that told by the G3JDG rx, incidentally now an HA-230. To sum-up the month and conditions at the time of writing would sound rather like the usual weather forecast—variable with occasional showers of DX. One "Colin", 840A and a bent nail, informs that 20 was a hive of activity around 1 a.m. BST, yet on one recent late session at '3JDG the only signals which stirred any excitement in the 130 ft. l.w. were numerous Boris's and Vlads happily chirping to each other with T3 notes. (Needless to add T9's were being exchanged.)

Fifteen metres has been wide open to the Far East at times and JA's running 20 watts have romped in at 5 and 7.

Ten metres is becoming more and more interesting with a bit of DX showing up now. The 28Mc/s logs this month are from people with modestly priced receivers and straightforward wire antennas. If you want to be with it "like I dig 10 man" then take 16 ft. 8 ins. of wire, cut it in the middle and feed it with co-ax (any length). Try Sundays for a first listen.

7 Mc/s and Down

A horrible state of affairs this month, almost too terrible to relate but alas I must. Out of all the piles of logs that arrived only two were for the l.f. bands. (Pauses, dries eyes on dirty hanky, and continues). The first log from **E Goonan** (Manchester), 19 set plus a.t.u., 30 ft. end fed, logged some forty odd stations on 7Mc/s. Mostly Europeans (EU's) but from further out came UI8KNA, HM4CS and HM2AXU. Another log from **M Pemberton** (Bucks) CR150, 66 ft. end fed heard G, GC, GW, and DJ, DL, F2, ON5, on eighty, while on forty DJ, DL8, EI, G, GM, LA3 ON5, OZ6, and PY8QM (Brazil).

No reports for top band although several EU's are about down the l.f. end. How about an l.f. month? 1.8/3.5/7Mc/s only. I know this is quite a task and much more difficult than 20 and 15 where the DX just falls like ripe plums. To request someone to listen on 40 metres is like asking them to walk through a pack of mad dogs with a pork chop on each ear—nevertheless, I'm asking! One hour on 40 for each hour on the h.f. bands. Go on live dangerously—I dare you. (No—I will not provide the pork chops!)

The Aitch Eff Bands

Never any shortage of logs for these bands particularly 20 and 15. So many at times that I sort them into those who took the trouble to put the log in alphabetical order and those who did not. Here are reports from those who did. **Chris Claydon** (Fife) 840C, 60 ft. l.w. had a brief listen on 20 and heard BV1USA (Taipei), CR3KD (Bissau, Port Guinea) CR4BC, HI8LC (Santa Domingo), KH6FRI (Hawaii), LU1ZC (Deception Is. Antarctica) UAØ KAE, UWØIF, VP2AZ, VP8IN (Base F, Grahamland Antarctica). **D. Skidmore** (Belper), HE40, 100 ft. end fed, 20 metres all s.s.b.—CN8BB, CR6GC, CX9AAK, EA8AH, EL3C, ET3WH, HV3SJ, IS1VAZ, JA4BJO, JA6AD, KL7EBK,

KM6SEN (Midway Is), KR6DI, PY2BEH, SVØWV, TF3EA, UA9TE, UL7BF, VE2ABJ/SU, VE8MP, VK5MS, VP6KL, WA6EKD, W6EDB, XE1FFW, XW8BJ, YV1EC, YV3CN, ZB2AK, ZD7RH, ZD9BE, ZE3MV, 4X4AM, 5N2AAW. **Ian Haworth** (Preston) CR100, 33 ft. end fed, 20—BV1USA, CR6BX, CX2CO, HI7ATM, HK3RQ, HP1FR, JA1,2,6, MP4BBA, KZ5PW, OA3PZ, OX3BF, PY1,2,3,4,5,7, ST2SA, TI8LN, VK1,2,3,4,6,7, 9VW, VP2GR, YV5BIG, ZL5AA (Antarctica), 4X4VH, 5A1CV, 9Q5HF, all phone.

On 15 a log from **F. Le Blancq** (Jersey, C.I.), Pye domestic rx 50 ft. end fed, CR5CA, CR6GL, CX8PS, HB9GR/P, KP4AXC, LU5DJV, LX1DC (Luxembourg), OD5ET, PY2CDY, PZ1BO, SV1BL, TR8IAD (Gabon), TU2BA, XE1RC, ZC4MO, ZS1DV, 5A1TK, 6W8DD (Senegal), 9H1R, 9Q5CB. **Michael Leck** (Lancs) 870A, 66 ft. end fed, CR6KR, CR7FM, CT1CJ (Portugal), EAØJM, EP3RO, JA2GDT, JA7DTF, K1FZS, K2YXY, K4DI, LX1YL, MP4BBA, PI1HTG, SV1CX, SV1DL, VE3FRV, ZC4HR, ZE2JA, ZE6JL, ZSBD, 4X4KX, 5A1TK, 5A5TE, 5N2AAR, 5X5JK, 9J2K, 9N1JP, 9Q5IA.

Colin Morris (see Ten Metres), found twenty busy with FM8CD, FL8AC, HC8JG, HM9DL, HR1SO, HS1AK/P2, KH6FMS, KW6EJ, KX6BU, OA5W, PJ2MI, PJ3CR, ST2BSS, TI3AA, VP2KD, XE1FFW, YK1AA, 3A2CP, 9M6WQ. **M. Levy** (Kirkella), runs a "not so very good receiver", an S38E. With 66 ft. of wire twenty yielded EP2GF, HC1SM, HS1AK/2, HV3SJ, JA3HF, KL7EBK, KR6MM, LU1CM, MP4BCC, OX3KI, VK2PP, VP6KL, ZD9BE, 5Y3GT, 5Z4IR.

Ten Metres

Yes a separate heading again. Brazil coming in 59, Cyprus 57, Venezuela 59, half Africa at 58 average, this is the story now. **Colin Morris** (Tenbury Wells), double s/het homebrew, dipole—DJ7RD 1852, EL2AK 1724, OD5BU 1853, PY1BYK/P7 1814, PY2BYI 1816, YV5BPJ 1812, YV5AGM 1755, ZC4MO 1747, 5H3JJ 1746, 5Z4AA 1726, 7X2AH 1340, 9H1A 1748, 9J2VX 0825, 9J2MM 1806. Times g.m.t. **Paul Baker** (Pontygasseg) (Fancy sending that on c.w.!) HE30 60 ft. end fed, CT1, DJ, DL, DM, EA4, F, HB9, I1, IT1, OE, ON, OZ, SM, SP, UA2, UB5, UC2, UR2, YO, CR6GP, CR7IZ, K4DI, PY1CRC, ZC4MO, ZS1BV, 4X4IH, 5N2AAR, 9J2VX, 9Q5GW.

News and Notes

Little items of gossip passed my way and now offered for your discerning palates includes VP8IK (Antarctica) bottom end of 7Mc/s (still no pork chops—not even if you hear him!) VS9OC back in business again on the h.f. bands on s.s.b. Kure Island at it on 20 metres look for a /KH6. Also Japanese amateurs, at present JA's are also to include JH call signs shortly. A reminder that now is the time to check the local schools and technical colleges for R.A.E. classes, enrolment usually being early September. Contests for sunny August—alas just one, the WAE c.w. section contest. September 3-4th VHF-NFD. Deadline for next month is the 25th, how about a log from you?



CRYSTAL CONTROLLED OSCILLATORS and TRANSMITTERS



by F.G. RAYER G3OGR

CRYSTAL control of a transmitter has several advantages. Such circuits are simple, easily made and adjusted, and a single h.t. supply can be used for oscillator, p.a. and modulator. There is no need for voltage stabilisation, buffer stages, or other means of avoiding frequency drift with changes in loading, etc. The output frequency is also known from the crystal. For these reasons, crystal control is popular with simple transmitters, or those for portable use. Two or three crystals can provide quite a range of operating frequencies in a number of bands. In addition, the crystal controlled circuit can generally be adapted for a v.f.o. later, the crystal oscillator stage then acting as a buffer.

Triode Oscillators

These are not much used, but are worth considering for a very small or simple transmitter. Two circuits are shown in Fig. 1. The "a" circuit requires no coil, output being at the crystal frequency. A 6C5, 6J5, 6C4 or other triode can be used, or the triode section of a triode-pentode. With the latter, the pentode serves as p.a., allowing very small size in the 5W-10W input range. Most valves and crystals require some capacity from grid to cathode. The 30pF trimmer is adjusted from zero capacity until all crystals oscillate well. About 100-150V will be sufficient for the anode, so the anode resistor can be adjusted or replaced by an r.f. choke, if only a low voltage is available.

Fig. 1b uses a coil L1, tuned to near crystal frequency. If a meter is included in the h.t. circuit, a dip in current is found when oscillation commences. Tune for nearly minimum current, which gives nearly maximum r.f. output. Normally, L1 is not tuned *exactly* to resonance, because the circuit will then not start oscillating when switched on.

With these circuits, output is generally at crystal frequency. This does not matter with single-band operation, but is rather a limitation for multi-band working.

Crystal Harmonics

Various tetrode and pentode oscillators allow output to be obtained on the crystal frequency, and multiples of this frequency. It is necessary that the harmonic falls within the higher frequency band in view. This will be so with some crystals, but not with others. As example, a 3520kc/s crystal would allow working on 3.52, 7.04, 14.08 and 21.12Mc/s. But a 3650kc/s crystal has harmonics (multiples) falling outside the 7, 14 and 21Mc/s bands.

The circuit in Fig. 2 is particularly easy to adjust. L1 is tuned to the crystal frequency, or the wanted harmonic. A fixed or plug-in coil can be used, or coils can be selected by switching. A single fixed coil can sometimes be used for two adjacent bands.

At high multiples, output falls off, until sufficient grid drive for the following stage is no longer obtained. With values shown, a 3.5Mc/s crystal should provide enough grid drive for a 6146, 807, or similar p.a., on 3.5, 7, 14, and 21Mc/s. The 6CH6 requires about 25mA. Grid current in the following stage can be adjusted by slightly detuning L1.

When first setting up an oscillator or transmitter of this kind, check that the correct harmonic is being used. This is most readily done with a wavemeter. Wrong harmonics can then be avoided.

It is helpful to prune L1, or have an adjustable core, so that only one correct harmonic is tunable

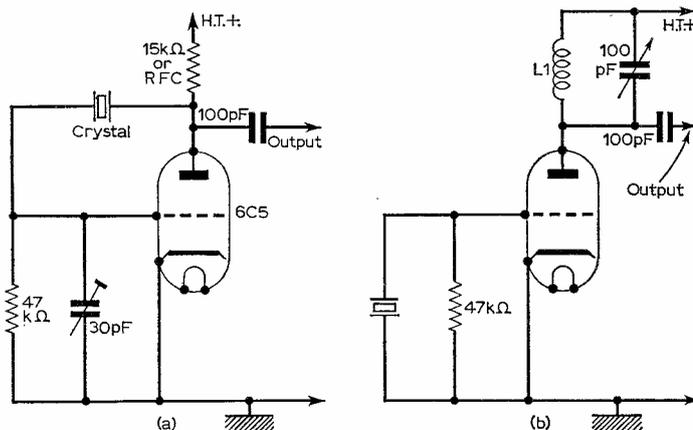


Fig. 1 (a and b): Two simple triode oscillators.

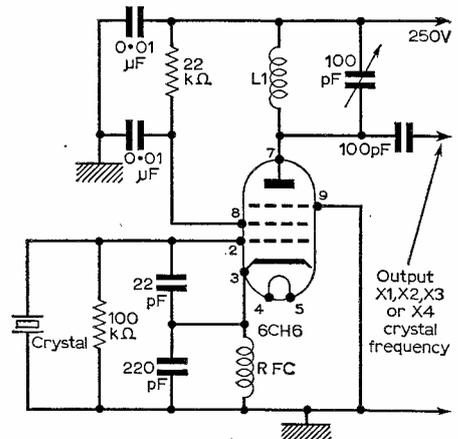


Fig. 2: Oscillator with output on fundamental and harmonics.


SELECTED BARGAINS FOR PRACTICAL WIRELESS READERS!

Very Limited Import Quota—Direct to You
Saving you Wholesaler's Profit and
Retailer's Profit!



7 TRANSISTORS +
VARIABLE WAVE BAND
 Our Price **44/11**

Never before has a 7 Transistor Radio been offered at such a low price—compare prices locally! Staggering reception from revolutionary ferrite internal aerial—works in car, boat or plane—ropes in stations galore—B.B.C., Pirates, Luxembourg—the lot! Room filling volume and more. Rich HIFI tone from famous "Foster" speaker. Brand new in carton. *Save pounds!*—Send 44/11 plus 4/7 P. & P. **Money back guarantee.** (Quality case, battery, personalphone, etc. 7/6 ex.). Demonstrations Daily.

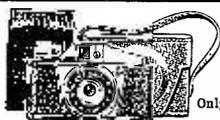

MINIATURE
PRECISION
SPY CAMERA

Only **14/6** Plus p. & p.

Offered at a fraction of its Real Worth. Brand new precision made photographic instrument in chromed steel and leather. Two speed shutter, 2 1/2 in. x 1 1/2 in. Easily concealed in palm-of-hand! and takes crystal clear photographs. The rage of America and offered at the absurd price of 14/6, incl. solid leather case—add 6/- for pack of 6 films which give 60 photos, superb craftsmanship in miniature. Send immediately.

NO SOLDERING
AMAZING
CIGARETTE
RADIO

ONLY **18/6**




Yes a perfectly ordinary packet of cigarettes! But watch your friends astonishment on hearing it! It fetch in station after station, loud and clear! Still holds 10 cigarettes—yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file. Mr. D. B. of Huddersfield, writes: "... I have fitted the parts in it and it is working wonderfully..." ALL PARTS including Semi-Conductors, ABC Plans, etc. ONLY 18/6, plus 2/6 post, etc. *Parts available Separately.*

Make 5 different
TRANSISTOR
RADIOS for


35/- No Experience Necessary

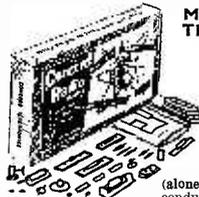No soldering. Only 5 connections for first radio to work. Just look. You get Easy ABC Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, Coils, Condensers,



Resistors, Tuner, Switch, Screws, etc. **YES—EVERYTHING!** Loud clear English and foreign reception. As supplied to Educational Authorities, H.M. Forces, **TESTIMONIALS GALORE.** Mr. R. O'D of Londonderry writes: "... I received your components and I must say that I am very satisfied with them, I have it already set up!..." **COMPLETE HOME/RADIO COURSE.** Originally **£6** **SEND ONLY 35/-**, plus 3/6 post etc. *Parts available separately.*

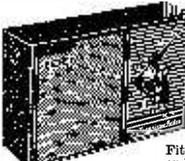TRANSISTOR POCKET RADIOS
with Loudspeaker. Bulk Purchase
Enables us to Make
this Fantastic Offer



Only **28/6** No more to pay

The "SAN REMO" so tuned that it brings the voices of star vocalists dramatically to life—in your home, office, etc. Only 4 1/2 x 2 1/2 x 1 1/2 in. Fits easily into your pocket or handbag. Works for months off 1/2d. battery. Should last a lifetime, anyone can assemble it in an hour or two with our easy plan. Miniature speaker—everything, only 28/6, 2/6 p. & p. (Parts can be bought separately). Limited supply—so rush your order before it's too late.

NEW FULLY
TRANSISTORISED
PORTABLE RADIOS

with Full Variable waveband. NOW A FRACTION OF THE NORMAL PRICE

ONLY **35/-**



WHY PAY MORE? All the latest advancements are packed into this new **MULTI-STATION A.I.L.** Transistor radio—the internal aerial picks up even the remote stations and the powerful built-in speaker gives room filling volume. Individual tuning, fine adjustment. Purchase with confidence—packed in original manufacturer's cartons. *Personal carpiece and battery 4/6.* Send 35/- plus 4/6 p. & p.

Miraculous Scoop from Swiss Manufacturers Limited Shipment
NEW 23 JEWELLED AUTO-
MATIC DATE DIVER'S
WATCH



with Rotating Timing Bezel. Should Retail at 12 gns. 950 only at **97/6**

Now, your chance to make a genuine **LARGE CASH SAVING** on this high-quality watch. 200 vacuum tested for depth. Super waterproof. 23 jewelled movement, shockproof, electronically timed, luminous dial, hands and rotating bezel. Ideal for skin-divers, sailing, motoring, research work for accuracy. **FULLY GUARANTEED.** Send only 97/6 plus safe p. & p. 4/6. Money back guarantee. Rotproof diver's strap 5/- extra or matching expanding bracelet 12/6 extra.

SOLID STATE "7"
Direct Import Scoop. 2 complete crates
only with 1750 of these
amazing 7 TRANSISTOR full
variable waveband radios.



You could pay 6 gns. for this performance. **OUR CRAZY 58/6 PRICE**

Your chance to own this remarkable **FULL SIZE 7 TRANSISTOR PORTABLE** at the lowest ever price. The improved internal ferrite aerial—works in car, boat or plane—pulls in loud and clear all the programmes—B.B.C., Luxembourg, Pirates, etc. The full sized speaker gives high sensitivity and room filling volume. Brand New and Boxed in Maker's carton—1750 only at 58/6 plus 3/6 p. & p. Money back guarantee. (Carrying case, Battery and Earpiece 7/6 extra). Demonstrations Daily.

NEW RADIO No soldering
VOLKSRADIO
ANYONE CAN BUILD
IN 2-3 HOURS

ONLY **19/6**



EVEN THE OLDER CHILDREN BUILT THEM!... no soldering—only 16 connections! Then hear it reach out bringing in station after station, loud and clear. Palm-of-hand size 4 1/2 x 2 1/2 x 1 1/2 in. Many Testimonials: M. H. of Bradford writes: "... I have just completed one of your sets successfully, it is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me. Your instructions and plans have obviously been very carefully thought out so that even the most dim can follow them..." **Direct from Manufacturers to You.** Send 19/6 plus 3/6 post, etc. **PARTS AVAILABLE SEPARATELY.**

Limited Import Quota from Behind the Iron Curtain, 1,200 only
Famous New Full Size
3-SPEED FOOD MIXER




Same features and extras as 29 gns. model. **Now Yours £7.19.6** for only **NO MORE TO PAY**. New in Makers' Carton. Amazing deal direct with the Famous Manufacturers, whose name we have agreed not to mention due to the give-away price! Why pay 29 gns. when you can have all this for only £7.19.6, plus 6/6 p. & p.? Gleaming white metal unit complete with full size heat resistant Oven Glass Mixing Bowl—Whisks—Coffee Grinder, etc. (Liquidising attachment £1 extra). Ample lead plugs into standard A.C. 220 to 240v. supply. Money instantly returned if not delighted.

Limited Import Shipment
INTERNATIONAL
SATELLITE 8


PORTABLE
Transistor RADIO
2 Full Wave Bands
Why Pay 12 gns.?

NOW 74/6

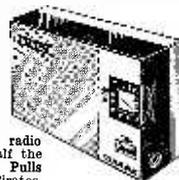ONLY Famous Satellite portable radio now offered well below half the price of comparable models. Pulls in your favourite stations, (Pirates, B.B.C., Luxembourg, etc.)—even International. Internal aerial, larger speaker, combine to give crystal clear reception **INDOORS and OUT.** Why pay 12 gns. ? Send 74/6 plus 4/6 p. & p. (Cowhide carry case, earpiece, battery etc. 8/6 extra.)



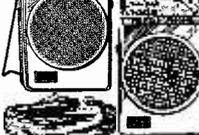SAVE YOUR LEGS!
INTERCOM OUTFIT
& BABY ALARM
Ready Built



Only **52/6**
 Save £3.16.6.

Robustly made, brand new current models. You get 2 separate fully transistorised intercommunicating sets—each can speak or listen to the other—complete with 60ft. connecting wire. Fixed in a flash. Ends baby-crying worries. Ideal for Workshop to House, Sickroom, hundreds of useful Hangs on wall or stands up. Our absurd price 52/6, battery 2/6 extra. Post, etc. 3/6. Money back guarantee.

New Sensational Price
Breakthrough DIRECT
IMPORT 1000 only

High powered
PORTABLE
TAPE RECORDERS
 You've seen recorders at more than twice our price **ONLY £5.19.6**




At last a highly sensitive full-sized tape recorder at a price you can afford. "NOT A TOY"—but a beautifully designed instrument which is solidly assembled on a rigid steel chassis. You'll be amazed at the fine reproduction of sound! for all purposes including dictating, notes, party fun, etc. Fingertip control for volume and selector switch. Hand Microphone has unique **REMOTE CONTROL** on/off switch for accurate recording and playback. 1000 only at **£5.19.6**, plus 5/6 p. & p. **TRY AT HOME**, your money back if not delighted. (Tape, Spare Spool, Microphone, Batteries and Earphone 15/- extra.)

Miraculous Import Purchase

200 Only NOW
HAVE MUSIC IN
EVERY ROOM
Extension speaker

More than doubles the value of your radio. For **29/6** Complete

Just place this ultra modern extension speaker in any room and tune in to your favourite programmes—Now you can relay even from HIFI radiograms down to transistor portables. Simply place in position or fix on wall and plug in the long lead supplied. What could be easier? **DON'T MISS THIS AMAZING BARGAIN.** remember 200 only at this price 29/6, plus 3/6 p. & p. Money instantly refunded if not worth more than double.

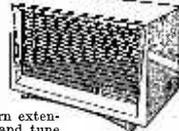

Scoop at the Docks—a
Complete Unopened Crate
FULLY AUTOMATIC
SELF-WINDING 21 JEW-
ELLED DATE WATCHES
 Originally 12 Gns.



Now ONLY **98/6** You save £7.13.6


1,500 only to be cleared at below Bal price. Gent's calendar watch by reputable Swiss maker. Luxurious gold finish, stainless steel screw back—shock resistant, anti-magnetic, waterproof. Unbreakable—21 Fully Working Jewels. Electronically timed. Send 98/6, plus 3/6 p. & p. Matching expanding bracelet 10/6 extra. Brand New and guaranteed.

CONCORD ELECTRONICS LIMITED

(DEPT. P.W.31) 87-89 TABERNACLE ST., LONDON, E.C.2
 Callers Welcome, Open all day Saturdays

AMATEUR RADIO
CHAS. H. YOUNG LTD.

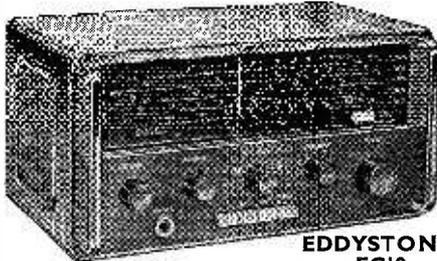The Sensational
ALL-TRANSISTOR!
Communications Receiver



**EDDYSTONE
EC10**

for use in the home, caravan, car or boat,
H.P. facilities. Only £48 Part exchanges.

Write for brochure

**170-172 CORPORATION STREET
BIRMINGHAM 4**

Telephone CEN 1635

BROADWAY ELECTRONICS
92 MITCHAM ROAD, TOOTING, S.W.17

Phone BALham 3984

(four minutes from Tooting Underground Station)

GARRARD 4 SPEED DECKS WITH CARTRIDGE: Auto-changers: AT60, £10.10.0; 3000, £8.8.8; 200, £7.7.0; 1000, £6.6.0; Autoslim £5.5.0; De Luxe Autoslim with plug-in head, £5.15.0. P. & P. 6/- Single Players: SP25, £10.10.0; SRP12, £5.0.0; Garrard Plinth. W.B.1, £3.12.6. P. & P. 4/8 for plinth. Motor boards 6/6 each.

CARTRIDGES: Ronette Stereo 25/-; Acos GP67, 15/-; G.C.2 Garrard 15/-; AT6 shells 5/-; P. & P. 6d. HG83/2 Stereo 20/-.


SPEAKER ENCLOSURES: "TONY" Corner Cabinet 20 x 10 x 7in., takes 10 x 6in. speaker, covered in grey Rexine and Vynair, 45/-; P. & P. 5/-; "BLAKE" Heavy Duty Cabinet with port, 24 1/2 x 18 x 9in. Baffle 1in. thick. Covered Rexine and Vynair, £5. P. & P. 10/-; Extra baffle for 8 or 10in., 3/6; "BLAKE DE LUXE" veneered with wood-grain Formica and standing on smart 6in. legs, £6.5.0. P. & P. 10/-; "HAYDON" 16 1/2 x 15 x 7 1/2in., fabric covered, suitable 12in. speaker, 45/-; P. & P. 7/6; Crystal Mike 200C replaces BM3, 30/-; P. & P. 2/-; Stand for same, 9/6; P. & P. 1/6; Guitar Pick-up with Screened Lead, 12/6; P. & P. 6d. Crystal Lapel Mike, 7/6; Neon Panel Light Arcoelectric 240v. A.C., 2/6; P. & P. 6d. Tape Spools: 3in., 9d.; 4in., 1/-; 5in., 1/3; 5 1/2in., 1/9; 7in., 2/- each.

BARGAINS IN TRANSISTORS. AC127, AF 114, 115, 116, 117, 118, 119, OC189, 170, 171, 172, 5/6 each. OC72, 75, 82, 3/6. OC71, 83M, 3/-; RF Packs—1 OC44, 2 OC48, 8/6. AF Packs—1 OC81D, 2 OC81, 6/-; AF Pack—1 GET118, 2 GET119, 5/6. OC28, 28, 29, 7/6. ORP12 Light Cell, 7/6. Diodes OA81, 2/3, OA91, 1/9; P. & P. on all these 6d.

EARPIECES with cord and 3.5 mm plug, 8 ohm magnetic 3/-; 250 ohm, 4/-; 180 ohm Magnetic with clip, 6/6; Crystal, 4/-; P. & P. 6d.

SPEAKERS: ELAC Heavy duty Ceramic Magnet, 11,000 lines, 10in. round, 10 x 6, 15 or 3 ohm, 42/6; P. & P. 3/8. 8in. round 15 or 3 ohm, 38/6; P. & P. 3/6. EMI 134 x 8in. 15 or 3 ohm, 42/6; P. & P. 3/6.

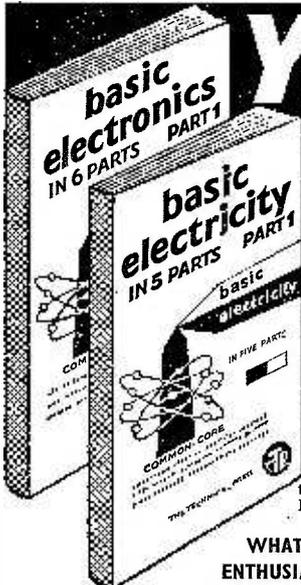Stockists for Eagle Products, Goodmans, W.B. Wharfedale, Bakers, Tripletone, Linear, all makes of amplifiers and speakers supplied. Let us quote for your requirements. S.A.E. please. **NO C.O.D.** Trade terms to bona fide dealers.



YOURS FREE FOR 7 DAYS

The New 'Picture-Book' way of learning
BASIC ELECTRICITY (5 VOLS.)
BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the **Pictorial Approach** to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

**WHAT THIS MONTH'S
ENTHUSIASTIC READERS SAY**

"... I did not believe it would be possible to learn so much from a book as I have from studying Basic Electronics..." T. W., Shepperton.

"... This series has been of the greatest help to me as I have just started work in the electronics industry..." S. J. T., Bristol.

"... The speed of your service is excellent and, as for the volume definitely the finest thing that ever happened to electronics..." T. H., Chelmsford.

POST NOW FOR THIS OFFER!!

TO SELRAY BOOK CO.
60 HAYES HILL, HAYES, BROMLEY, KENT

Please send me **Without Obligation to Purchase**, Basic Electricity/Basic Electronics on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-; Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts), 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).

BASIC ELECTRICITY **BASIC ELECTRONICS**

Signature

(If under 21, signature of parent or guardian)

NAME

BLOCK LETTERS BELOW

FULL POSTAL ADDRESS

with each coil. If this is done, the capacitor can be reduced to 25pF. Wrong harmonics cannot then be reached.

When obtaining maximum grid drive to the next stage, with a high frequency multiplication, L1 should be chosen so that the parallel capacity is small. This is not important on 3.5, or 7Mc/s, and may not matter on 14Mc/s, but may make all the difference on 21 and 28Mc/s. With switching, absorption by unused coils can also cause losses which reduce grid drive.

Crystal Switching

It is often convenient to have the crystal holder on the front panel or fit a switch for easy changes in frequency. Fig. 3 shows a suitable circuit for three crystals, X1, X2 and X3.

Fig. 3 also allows the input from a v.f.o. to drive the crystal stage. Even with a v.f.o. available, it is sometimes convenient to have a crystal or two for frequency checks.

A co-axial lead takes the v.f.o. output to the socket shown. To avoid instability or frequency pulling it is generally better to use the crystal stage as a doubler. So the v.f.o. can be on 1.8Mc/s for 3.5Mc/s, or 7Mc/s for 14Mc/s (doubling). The crystal stage can also triple (21Mc/s operation with 7Mc/s v.f.o.) with good results. A v.f.o. giving outputs on 1.75Mc/s and 7Mc/s bands will permit working all frequencies from 3.5-28Mc/s.

Crystal Holders

Crystals have a wide range of bases, with holders to suit. It is best to have all with similar pins. If some different crystals are to hand, an adapter can be made as in Fig. 4. This has two pins to fit the normal crystal holder, mounted on a paxolin strip. Two "sockets" bent from brass receive the pins of the crystal. The adaptor allows a small crystal to be used in a large holder, or the reverse, according to construction. Holders can also be purchased which take either ½in. pin spacing or ¾in. pin spacing crystals, but some of these will no longer be satisfactory with small pin crystals once a large pin crystal has been inserted.

An ordinary octal holder will take FT243 type crystals. Other sockets can be used for heater and h.t. circuits, as in Fig. 4. This allows a crystal or v.f.o. to be plugged into the same panel mounted octal holder.

The ¾in. spacing type of crystal will fit a UX5 (807 type) holder. Again, spare sockets can be used

to supply power to an optional v.f.o. It is also possible to have crystal/v.f.o. switching, with power for the v.f.o. from a separate power pack, or taken from the transmitter by means of a separate multi-way plug.

Multi-Band Transmitter

Fig. 5 is a transmitter circuit allowing multi-band working with a minimum of difficulty. L1 is tuned to the crystal frequency, or required multiple. About 3mA to 4mA grid current is usual for the 807, and a 3.5Mc/s crystal should give 5mA drive on 14Mc/s and lower frequency bands.

For a single band, L1 and L2 can be fixed. This simplifies building when interest is mainly in one band. For multi-band work, plug-in coils or switching is required. Normally, the p.a. (807) is always driven on the same frequency as the output, because doubling here reduces efficiency.

H.T. for the crystal oscillator can be drawn from the same pack as supplies the p.a. If so, add a series resistor so that about 250-300V is obtained. A single meter, with switching, can be used for p.a.

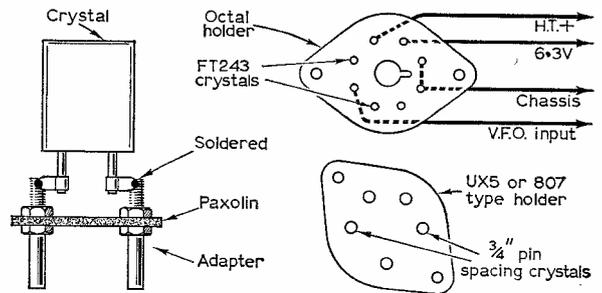


Fig. 4: Crystal adapter and plug-in holder for v.f.o.

grid and anode, but separate meters are an added convenience. A switch to apply h.t. to the oscillator only is also very useful indeed, so that grid current can be checked and operating frequency noted with the receiver.

The p.a. anode anti-parasitic choke can be 5 turns of 20 s.w.g. wire in a coil ½in. long and ¾in. diameter, around a 1-watt 47 ohm resistor. The 807 works well with 100mA anode current. This is 30W input with 300V, 40W with 400V, and so on up to 60W with 600V. The screen resistor Rs is adjusted to obtain about 250-275V on the screen grid, measured with the transmitter working.

For c.w., any of the usual keying methods can be employed. Cathode keying is most simple. For phone, a push-pull modulator furnishing an audio output equal to about one-half the p.a. input gives excellent results. Fixed capacitors should have a voltage rating at least twice that of the h.t., or preferable 1.5kV or higher for 600V.

VC1 should be wide spaced. A 200pF capacitor is suitable for all bands, but for h.f. bands only 100pF is easily sufficient. VC2 is a 2-gang or 3-gang broadcast receiver type component, with a maximum total capacity of about 800pF to 1500pF in all. The p.a. should not be operated without a load—aerial, r.f. output meter, 60-watt domestic lamp, or other equivalent device. With VC2 closed, VC1 is dipped for minimum anode current. VC2 is then opened until the dip on VC1 corresponds to 100mA (or other chosen input).


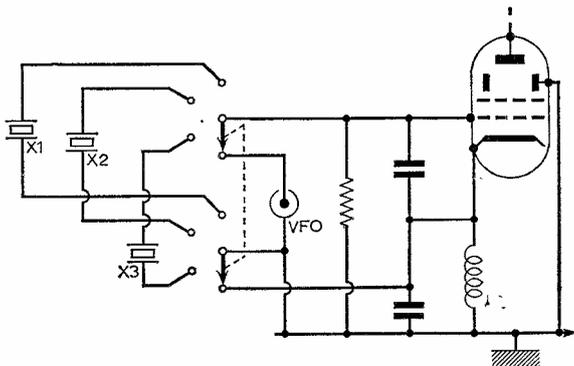


Fig. 3: Crystal switching and v.f.o. input circuitry.

HERE'S VERSATILITY FOR YOU...


The **Brenell**

MONO/STEREO HI-FI TAPE LINK

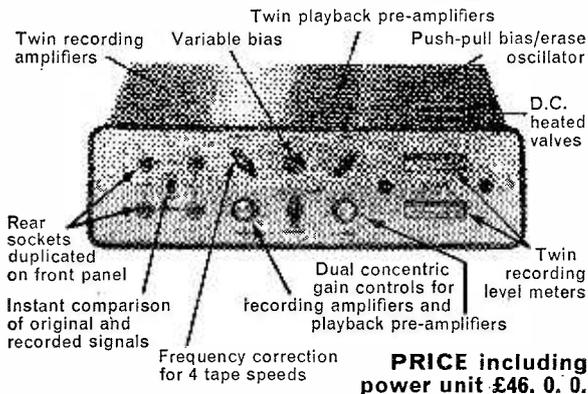

Designed for use with 2/2 or 2/4 track heads

Built to the same high standards as our tape recorders and decks this HI-FI TAPE LINK has been developed for use with your high fidelity equipment. It is capable of giving superb results when matched to one of our Mark 5 Series 3 decks fitted with the appropriate heads. Write for full details of this amplifier and deck and complete range of tape recorders.

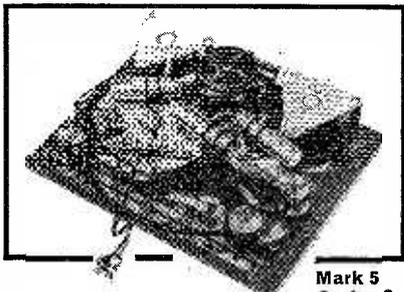


Mark 5
Series 3
Deck

Brenell

BRENNELL ENGINEERING CO. LTD.,
231/5 Liverpool Road, London, N.1.
Telephone: NORTH 8271 (5 lines)

GD378

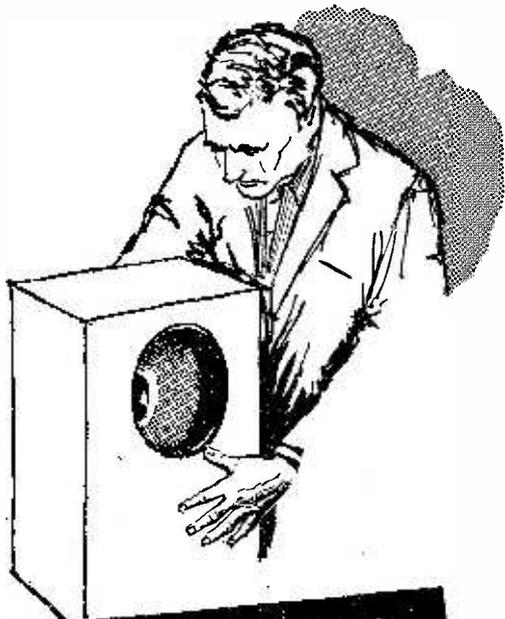

**USE
A WHARFEDALE SPEAKER**

... IT SOUNDS BETTER

Undoubtedly the best and most popular 8" unit ever made in this Country

SUPER 8/RS/DD

(inc. 20/- p.t.)

Frequency range 40 c/s — 20,000 c/s
Impedance 10/15 ohms.

£7

Power handling capacity 6 watts (12 watts peak)

In your next system use world famous Wharfedale Super Range Loudspeakers — there's no better value for money — anywhere. Each is fitted with roll surround for low resonance and double diaphragm assembly for extended H.F. response.

Send today for further details of these units plus free cabinet construction leaflets to enable you to build a top quality Hi-Fi loudspeaker system.



RANK WHARFEDALE LTD

IDLE, BRADFORD,
YORKSHIRE

Tel Bradford 612552/3
Grams 'Wharfedale' Bradford

FREE
CONSTRUCTION LEAFLETS

Complete this coupon for 8 page booklet on Wharfedale Speaker units plus FREE CABINET CONSTRUCTION LEAFLETS for your own Hi-Fi system. (Dept, PW.9.)

NAME _____

ADDRESS _____

TOWN _____

COUNTY _____

W
WHARFEDALE

A New Martin Recordakit

designed specially for the MAGNAVOX 363


3 WATTS OUTPUT

●
OUTLET FOR HI-FI AMP

●
SOLDERING NOT NECESSARY

●
SEPARATE RECORDING LEVEL AND VOLUME CONTROLS

Get the best out of your MAGNAVOX STUDIOMATIC TAPE DECK with a Martin Recordakit assembly. This comprises everything you want to make a superb two or four track 3-speed recorder (taking 7 in. reels) at a price that will save you pounds. The basic Martin units are assembled and tested, making it necessary for you simply to fit and connect them together in accordance with the detailed instructions book supplied. When built, your Martin Recorder appears as shown here. The lid is detachable. Case with speaker, and deck also available. Details on request. MARTIN RECORDAKITS have long been famous for their high performance standards, quality of materials, simplicity and dependability. The latest is the best yet.

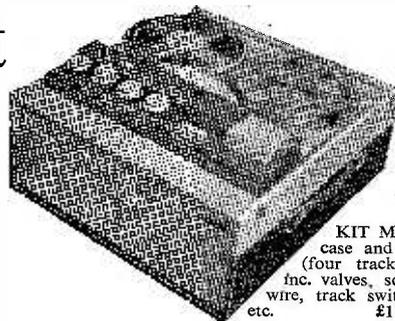

KIT M4 less case and deck (four track) but incl. valves, screws, wire, track switching etc. £15.19.6
KIT M2 less case and deck (two track) but incl. valves, wire, screws, etc. £14.19.6

Martin Audiokits for Hi-Fi

The uniquely reliable kits with "Add-on-ability"

No other system allows you to enlarge your installation stage by stage as Audiokits do. They comprise a wide range of very well made prefabricated transistorised units in which connections are standardised throughout and from which anything from a simple straight amplifier to an elaborate hi-fi stereo amplifier with FM tuner can be built. The Recordakit described above can be combined with your Audiokit assembly if you wish.

- 5-stage input Selector £2.7.6
- Pre-amp/vol. control £1.17.6
- Pre-amp/tone controls £3.2.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0

FROM PRE-AMP TO A HI-FI STEREO/FM ASSEMBLY

Martin Recordakits and Audiokits are obtainable from good stockists everywhere. In cases of difficulty please write direct. Trade enquiries invited.

MARTIN ELECTRONICS LTD

154/155 HIGH ST., BRENTFORD, M'SEX Phone: ISLeworth 1161/2

MARTIN ELECTRONICS LTD.
154 High St., Brentford, Middlesex

Full details of Recordakits Audiokits please


NAME

ADDRESS

(Block letters) P.W.9

FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS

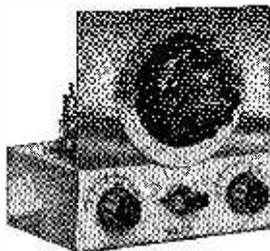

H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1966 RANGE
1-Valve model "CX", complete kit, Price 34/6 Customers say: 'Definitely the best one-valve S.W. kit available at any price'. This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and of course, as all our products, fully guaranteed. FULL RANGE of other kits still available including the famous model 'K', price 77/-. Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to:—

"H.A.C." SHORT-WAVE PRODUCTS (Dept. P.W.), 44 Old Bond St., London W.1

W. E. PEARCE

author of

An Introduction to Wireless

Electronics for Young Experimenters

an exciting new book

71 exciting, lastingly helpful experiments in electronics, for the young home enthusiast without limitless funds. By a well-known deviser of such experiments. *Fully illustrated.* 18/6

ORDER FROM ANY BOOKSHOP

Bell

TRANSISTORS, COMPONENTS ETC.

Types:—
AC 127 2/-; AF 115 4/6; AF 117 4/-;
BY 100 2/9; OC 19 4/6; OC 26 4/6;
OC 44 2/-; OC 71 2/-; OC 72 2/-; OC 81 2/-;
OC 81D 2/-; OC 170 4/6; OC 171 4/-;
2G 339A 2/-; 2G 371 2/-; GET 883 4/-;
GET 884 4/-; S1ST (Match paired output) 6/-; Signal Diode 1/-.

All types of semi-conductor rectifiers from 50V-400V.

Price on request.

MULLARD MINIATURE ELECTROLYTIC CAPACITORS

RANGE:—C426/AE A64; C426/AE/A250; C426 AM; A400; C426/AE/B50; C426/AM/B500; C426 CF F25; C426/AM/C40; C426 AE; C250; C426/CE/F125; C425/AF/D25; C426 CE/D320; C425/CI/F10; C425/AL E2.5; C425/AL/E16; C425/CF/F10; C426 CE E200; C426/CM/E200; C426/CM/E100; C426 AM E200; **CASH WITH ORDER. SAME DAY DESPATCH.**

EURAMASIA LIMITED

3 POPLAR COURT PARADE, RICHMOND RD., TWICKENHAM, MIDDXX. POP 6689.

Construction

The construction of a transmitter with a circuit such as that in Fig. 5 is very straightforward and snags are unlikely. A normal layout permits L1 to be under the chassis, with L2 and all anode components in the p.a. above the chassis. Wiring is short and direct, with by-pass capacitors directly to the chassis.

When first using the transmitter, a test should be made that grid drive is in fact on the correct frequency, as mentioned. The tuning of the p.a. anode coil should be done on low power; by reducing h.t. or temporarily fitting a 47k Ω screen grid resistor. Some change to grid current, with anode tuning, is normal, especially on the h.f. bands.

Adjusting VC1, Fig. 5, should cause a smooth dip in anode current. Changes in anode current at other settings are unlikely, but indicate parasitic or other unwanted oscillation. Stray back coupling from anode to grid, due to a poor layout, is a likely cause.

With the crystal removed, grid current should be zero, and no r.f. output obtained. For these tests, p.a. input (with an 807) should not exceed 20-25 watts.

Overtone Oscillator

For h.f. and v.h.f. bands, an overtone crystal oscillator has several advantages. A typical circuit is shown in Fig. 7. One or more stages of multiplication will be avoided, and the lowest frequency obtained is the overtone frequency (not the crystal frequency).

One application of this circuit is in a 144Mc/s transmitter. A 8Mc/s overtone crystal will provide a direct output on 24Mc/s, L1 being tuned to this frequency. A tripler stage then gives 72Mc/s, with a doubler providing the final conversion to 144Mc/s.

C1 may often be omitted, or is very small (say 2.5pF). If a number of crystals are used, a miniature variable capacitor, panel controlled by an insulated extension, is handy to obtain reliable starting and best output. The crystal should be an overtone type. Some are marked with the overtone frequency they produce (e.g., 24 Mc/s) while others have the fundamental (not used) specified.

When first testing the circuit, the tapping T on L1 may have to be moved. If this is too near the crystal end C, output may be poor, or no oscillation obtained. But if T is too near the anode end A, oscillation may arise on any frequency to which L1 is tuned, and is no longer crystal controlled. With T correctly placed, oscillation only arises as L1 is tuned through the overtone frequency, as with a conventional oscillator (shown in Fig 1b).

For 24Mc/s output with an 8Mc/s 3rd overtone crystal, 20 turns of 26s.w.g. wire on a $\frac{1}{4}$ in. diameter cored former should be found suitable, using a 1.5pF fixed, or preferable 2.5pF pre-set or variable capacitor in the C1 position. The tapping T can initially be 7 turns from C.

Similar circuits can be used for 28Mc/s band working, to avoid multipliers. The overtone obtained by L1 should be checked with a grid dip oscillator or wavemeter. The coils needed may appear unusually large for the band, because of the extremely small capacity.

Wavemeter

A simple wavemeter for checking in the 3.5-28Mc/s range can be made from a coil and parallel variable capacitor. It can be calibrated from a grid dip oscillator, signal generator, or receiver. To calibrate from a receiver, loosely couple the wavemeter to a loop in the aerial connection, and tune it to produce a dip on the signal strength meter of the receiver, with transmissions for the wanted bands.

An easily made wavemeter is shown in Fig. 8. If made *exactly* as described, calibration should be of sufficient accuracy to allow the Amateur bands

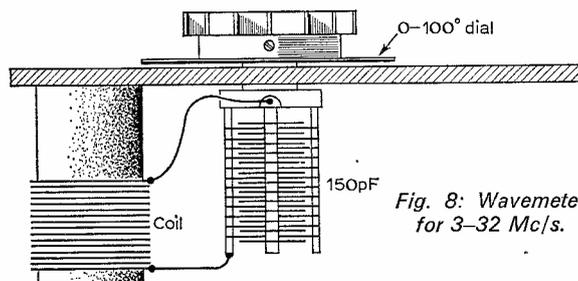


Fig. 8: Wavemeter for 3-32 Mc/s.

to be identified, and a check on readings can be made, so that they can be corrected, if necessary. Two coils are required. In view of the few items needed, it is easy to make two complete wavemeters, one for each band.

Each coil is wound on 1in. diameter smooth paxolin, using 24 s.w.g. enamelled wire, with turns side by side. The small coil has seven turns, and the large coil 35 turns. The free ends of windings are 2in. long. The capacitor is 150pF, with semi-circular vanes. The dial is 0-100, zero being with the plates unmeshed. The following calibration was obtained:

Small coil		Large coil	
Frequency (Mc/s)	Dial Reading	Frequency (Mc/s)	Dial Reading
10.0	8	32	8
9.0	9	30	9
8.0	12	28	10
7.0	15	26	12
6.0	20	24	14
5.0	30	22	16
4.5	38	20	20
4.0	57	18	25
3.5	62	16	31
3.0	82	15	36

To check the p.a. drive frequency, place the wavemeter coil near the oscillator anode coil L1, and tune the wavemeter until a dip is observed in p.a. grid current. The band (crystal harmonic) can then be seen on the wavemeter dial.

An initial check of p.a. anode tuning can be made with no h.t. applied to the p.a. If VC2 (Fig. 5) is closed a fairly steep rise in signal strength, as shown by a receiver signal strength meter, will be seen when VC1 is tuned to resonance. That is, L1, L2 and the receiver all tuned to the same frequency. Normally, a small dip in grid current can also be seen on the grid meter when L2 is tuned through resonance. This is extremely small on 3.5Mc/s, but may be 0.1mA or so on the h.f. bands. ■



The Science Museum Radio Society, founded in 1955 by a small group of Civil Servants on the Museum staff, widened its membership to take in all Civil Servants and those in allied occupations in 1957. At the same time the Society's name was changed to the Civil Service Radio Society. Today the Society is over one hundred strong and has a balanced membership—about half holding transmitting licences.

REGULAR MEETINGS

Monthly meetings take place on the third Tuesday of the month throughout the year in the Demonstration Room, First Floor, Science Museum. Members may operate the well-known GB2SM transmitter and meet in the less formal atmosphere of a general gathering. These "informal" meetings are very popular and the evening PRACTICAL WIRELESS attended, two other visitors came along—Rev. Fr. Ray Sturzenhecker DJ5SJ from Frankfurt, Germany, and David Jeanes VK2BSJ from Rockdale, NSW, Australia. Although neither visitor operated GB2SM, Dave spent all Sunday on-the-air at the chairman's home (John Stuart G3TUM) before returning to Australia. Ray will be in Britain for some time lecturing at Wimbledon College, where he plans to start a boys' radio club.

UNLICENSED STATION

Station GB2SM listens out for members from 6 to 6.45 p.m. on club nights. This station is unique in as much as it is unlicensed (being on Crown property) and is extremely well equipped—most of the gear being on "permanent loan" from manufacturers.

The Society provides operators for station GB2SM for many of the amateur contests and their



NO. 10 CIVIL SERVICE RADIO SOCIETY GB2SM
 Left to right: David Jeanes VK2BSJ (visitor), Peter Hearson G3SIU (treasurer), A. E. Roberts G3RUR, R. J. Pigou G3CRP, John Stuart G3TUM (chairman), E. K. Williams G8VY, George Herbert (assistant secretary), J. A. Payter G3GXA, Rev. Fr. Ray Sturzenhecker DJ5SJ (visitor) and Gordon Lloyd-Dalton (secretary).

skills (coupled with the first-class gear) can be seen from the premier awards displayed in the clubroom. The Society also runs a "ham" competition, open to all members, annually awarding a trophy known as the "Museum Key". John Springate G3CAZ, is the current recipient.

WORKSHOP FACILITIES

Later this year the Society will be able to offer workshop facilities to members, through the co-operation of the Civil Service Sports Council—at a Westminster address.

Beginners to radio and audio are already made welcome at the Society and most members are only too willing to loan technical publications and textbooks.


FORTHCOMING LECTURES

Although the 1966/67 winter season meetings have not yet been finalised, the society hope to include talks on the following subjects: relays, their uses, and practical circuits; short-wave listening; the Post Office Tower; general approach to aerials (by a consultant); building-up kits; a hi-fi demonstration by a noted manufacturer; and propagation, etc. These meetings will be additional to the "informal" meetings.


MEMBERSHIP

Full membership is only granted to members of H.M. Civil Service and their wives, whereas anyone in comparable employments (in the railway service, banking, industry, etc.) can become associate members.

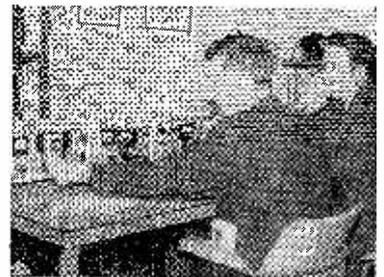Readers interested in joining the Society should either go along to one of the "informal" meetings held at the Science Museum or drop a line to the secretary: G. Lloyd-Dalton, 2, Honister Heights, Purley, Surrey.



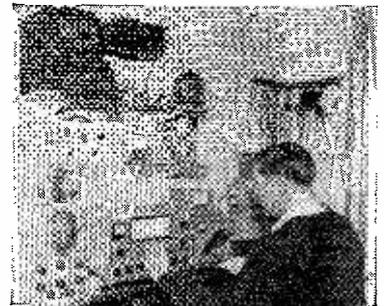
G3CRP and G3RUR operating the GB2SM s.s.b. transceiver.




Peter Hearson G3SIU has just completed the s.s.b. transceiver (G2DAF, Mk.II) shown in centre of the photograph. It took him the best part of two years to build.



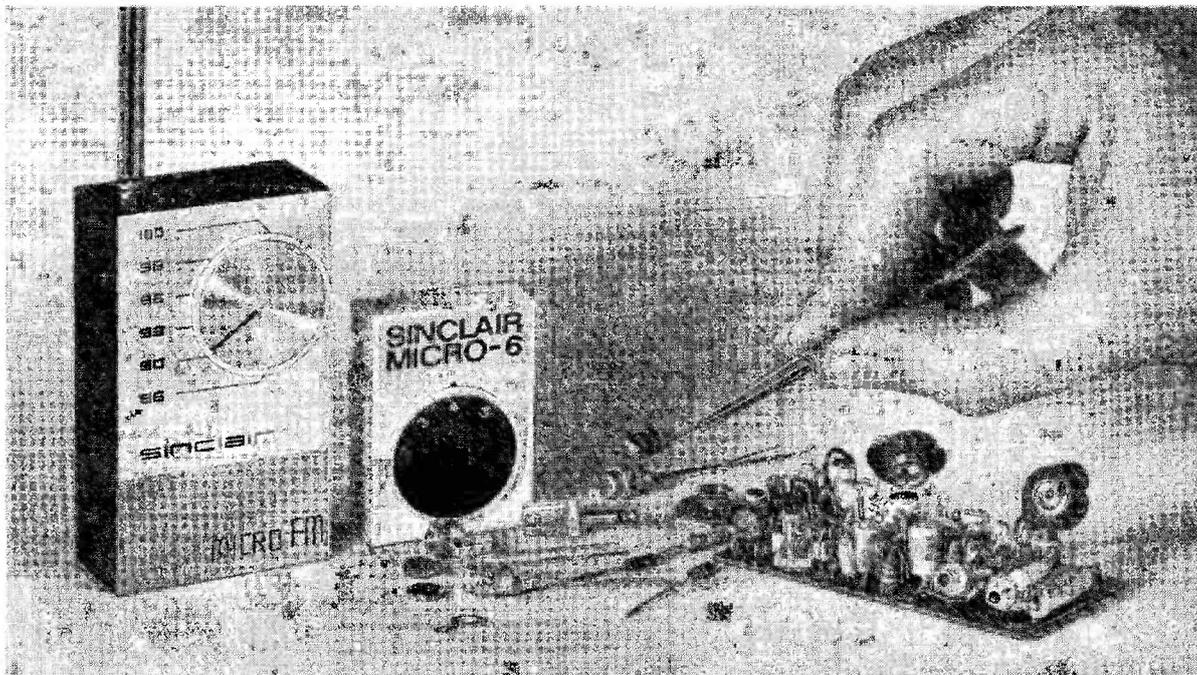John Stuart uses two transmitters, a home-made top-band job with 10 watts output and a Heathkit DX 40U with v.f.o.



*the world's
most unique
design*

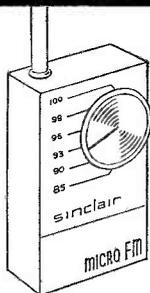

**IMPORTANT NEW
HI-FI DEVELOPMENT
FROM SINCLAIR**
See next pages



**THE SMALLEST SET
IN THE WORLD**

SINCLAIR MICRO FM

7 TRANSISTOR SUPERHET FM TUNER/RECEIVER

This unique, superbly engineered superhet FM set is going to give enormous satisfaction, first in building and then in using it. It is completely professional in styling inside and out. When built, the performance of the Sinclair Micro FM is fantastic. It is the only set in the world which can be used both as an FM tuner and as an independent FM pocket receiver just whenever you wish. Problems of alignment which have previously made it almost impossible for a constructor to com-

plete an FM set for himself have been completely eliminated in the Micro FM. It is ready to use the moment you have built it. The pulse counting discriminator ensures best possible audio quality; sensitivity is such that the telescopic aerial included with the kit assures good reception in all but the very poorest reception areas. The Sinclair Micro FM will give you all you want in FM reception and the satisfaction of building a unique design that will save you pounds.

★ TECHNICAL DESCRIPTION

THE SINCLAIR MICRO FM is a completely self-contained double-purpose FM, superhet. It uses 7 transistors and 2 diodes. The R.F. amplifier is followed by a self-oscillating mixer and three stages of I.F. amplification which dispenses with I.F. transformers and all problems of alignment. The final I.F. amplifier produces a square wave which is converted so that the original modulation is reproduced exactly. A pulse-counting discriminator ensures better audio quality. One output is for feeding to amplifier or recorder and the other enables the Micro FM to be used as an independent self-contained pocket portable, A.F.C. "locks" the programme tuned in. The telescopic aerial included is sufficient in all but the worst signal areas.

- ★ Size: 2¹³/₁₆" x 1¹¹/₁₆" x 1"
- ★ Powerful A.F.C.
- ★ Pulse counting discriminator
- ★ Low I.F. completely eliminates alignment problems
- ★ Tunes from 88 to 108 Mc/s
- ★ Audio response: 10 to 20,000 c/s ±1dB
- ★ Signal to Noise Ratio: 30dB at 30 microvolts
- ★ Operates from standard 9V battery, self-contained
- ★ Plastic case with brushed and polished aluminium front and spun aluminium tuning dial

*Complete kit
inc. telescopic
aerial, case,
earpiece and
instructions*

£5.19.6

SINCLAIR MICRO-6 — Build it in an evening

This is the set to build if you want a minutely sized receiver which will slip into a waistcoat pocket without even showing. It is the smallest set in the world, against which a matchbox looks enormous. Yet the Micro-6 is completely self-contained, including aerial and batteries and it virtually plays anywhere. Its clever six-stage circuit (2 R.F., double diode detector, 3 A.F.) ensures all you want in a radio today—power, range, quality and selectivity. It is very simple to build and useful to have with you always. A.G.C. counteracts fading from distant stations, bandsread brings in Luxembourg like a local station. There is great pleasure to be had in building the Micro-6, and it makes a highly acceptable gift: once others have seen its white, gold and black case and heard its amazing performance.


*Complete kit including case, aerial,
lightweight earpiece & instructions*

59/6

FULL SERVICE FACILITIES AVAILABLE FOR THESE SINCLAIR DESIGNS

sinclair **sinclair radionics Ltd.**
22 newmarket road, cambridge

Telephone OCA3—52731

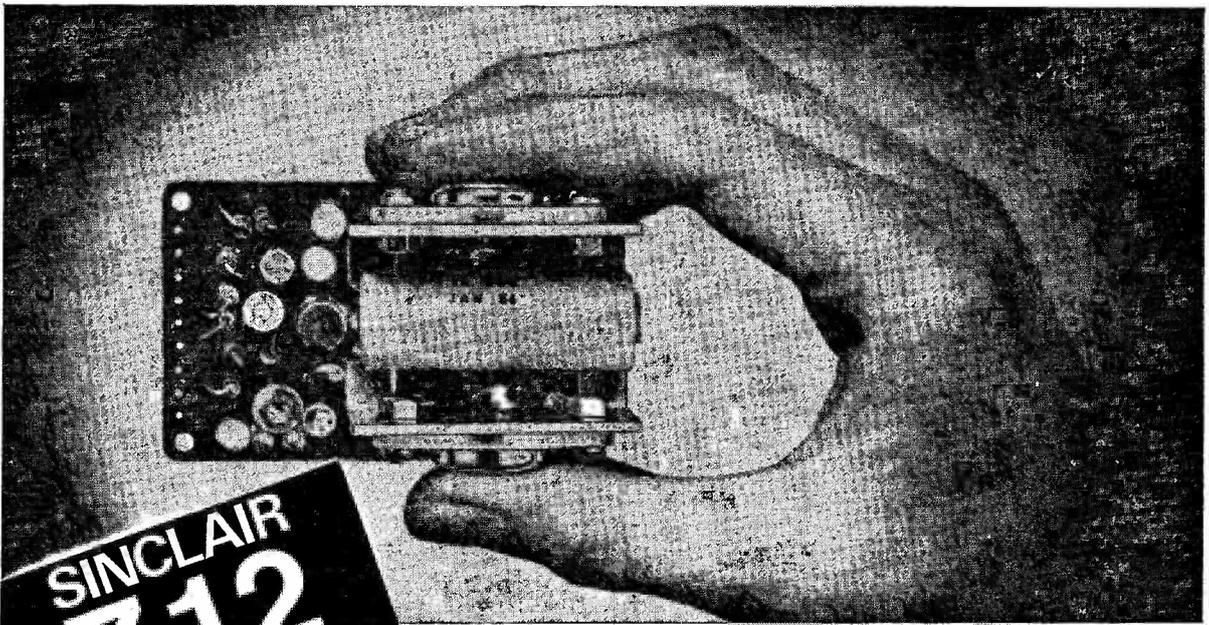

**SINCLAIR
Z.12**
INTEGRATED 12 WATT
AMPLIFIER AND PRE-AMP

UNEQUALLED FOR QUALITY AND POWER

12 WATTS R.M.S. OUTPUT
CONTINUOUS SINE WAVE (24 W. PEAK)
15 WATTS R.M.S. MUSIC POWER
(30 W. PEAK)

SIZE: 3" x 1 3/4" x 1 1/4"

**IDEAL ALSO FOR CAR
RADIO, GUITAR, P.A.,
INTERCOMS, ETC.**

The Sinclair Z.12 has been developed to the highest possible standards for an amplifier of its size and power. At the same time its rugged construction and its amazing adaptability make it possible to use just ONE type of amplifier in an exceptionally wide variety of applications. Eight special H.F. transistors are used in a highly original circuit to achieve the characteristics demanded of any quality amplifier, irrespective of price, yet this Sinclair unit costs well under £5.0.0, including its own integrated pre-amplifier stage. It will function efficiently from anything between 6 and 20 volts, making it very

convenient to run the Z.12 from a car battery, for example. Where it is required to run the Z.12 from mains supply, the PZ.3 is recommended. The Z.12 accepts radio, microphone and pick-up inputs, and detailed instructions for connecting these in mono and stereo are given in the manual supplied with every unit, together with a variety of matching control networks. Those wishing to have the very finest pre-amplifier and control system can connect inputs via the Stereo 25, a new unit designed specially for use with the Z.12 to produce the very finest stereophonic hi-fi you have ever heard—and the saving to you in cost is fantastic.

TECHNICAL SPECIFICATION

The Sinclair Z.12 combined twelve watt amplifier and pre-amplifier uses eight H.F. transistors in an original design developed by Sinclair Radionics to ensure exceptional standards of reproduction. The pre-amp incorporated accepts all types of inputs. For the very best possible hi-fi stereo, two Z.12's should be used with the Sinclair Stereo 25 described opposite.

- **OUTPUT**—Class B, ultra-linear, with generous negative feedback
- **FREQUENCY RESPONSE**—15 to 50,000 c/s ± 1dB
- **INPUT SENSITIVITY**—2 mV into 2 K ohms
- **SIGNAL TO NOISE RATIO**—better than 60dB
- **OUTPUT IMPEDANCE**—suitable for 3, 7.5 and 15 ohm loudspeakers. Two 3 ohm speakers may be used in parallel.
- **POWER REQUIREMENTS**—6 to 20 volts D.C. or Sinclair PZ.3.
- **QUIESCENT CURRENT CONSUMPTION**—15 mA

Z.12 USERS WRITE

"I fitted it up for a guitar. It (Z.12) is a marvellous instrument and money well spent." *R.M.K., Lanark.*

"Members of our staff are ordering Z.12's for personal use they were so impressed by the one we have in use now. I now need a second Z.12 (by air mail please)."


A.J.V., O'sea Telecommunications Commission, New Guinea.

"I am most pleased with its terrific performance." *H.R.L., Weston-super-Mare.*

"Fidelity is well up to the standards I require for a tuner and record player system." *A.C.R., Nottingham*

"It gave us all the power we required to compete with all comers as well as traffic. We can thoroughly endorse your claims for this truly remarkable piece of equipment."

H.T.N., Orpington, Kent.

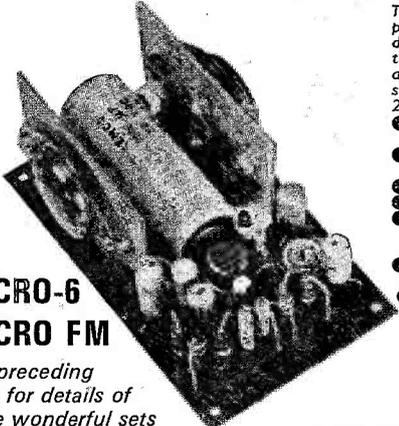

**MICRO-6
MICRO FM**

See preceding page for details of these wonderful sets


BUILT, TESTED AND GUARANTEED

89/6

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS

sinclair radionics Ltd.
22 newmarket road, cambridge

Telephone OCA3—52731

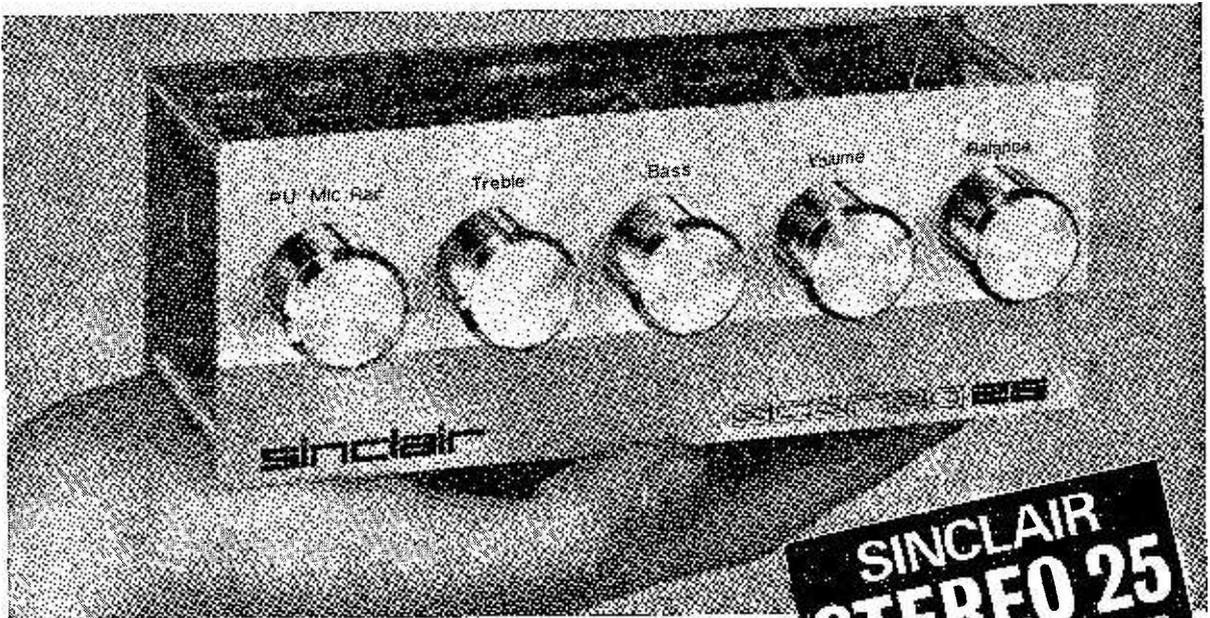

A new design built to the finest standards of high fidelity

Sinclair's newest unit, the Stereo 25 has been designed specially to obtain the very finest results used in conjunction with the Sinclair Z.12 for stereo reproduction. The best quality components, individually tested before acceptance, are used in its construction, ganged controls are carefully checked for matching, whilst the overall appearance of this very compact de-luxe pre-amp control unit reflects the professional elegance which characterises all Sinclair designs. The front escutcheon panel is in solid brushed and polished aluminium with beautifully styled solid aluminium knobs. Mounting the unit is simple, and the generous output of the P.Z.3 is more than enough to power the Stereo 25 together with two Z.12's for stereo. Hi-fi enthusiasts seeking the ultimate in equipment for domestic listening will find all they want from this combination of Sinclair units, and with a Micro FM to provide the radio, their installation will compare favourably with anything costing up to five times as much. When fitted, the Sinclair 25 will grace any type of hi-fi furniture.

TECHNICAL SPECIFICATION

Performance figures quoted here were obtained using the Sinclair Stereo 25 fed to two Z.12's and the entire assembly powered by a P.Z.3 Mains Power Supply Unit.

- **SENSITIVITY** for 10 watts into 1.5 ohms load per channel
Mic.—2 mV into 50 K ohms
Pick-up—3 mV into 50 K ohms
Radio—20 mV into 4.7 K ohms
- **FREQUENCY RESPONSE** (Mic. and Radio) 25 c/s to 30 kc/s \pm 1dB extending to 100 kc/s \pm 3dB
- **EQUALISATION FOR P.U.**
Correct to within \pm 1dB on RIAA curve from 50 c/s to 20 kc/s.
- **TONE CONTROLS**
Treble +12dB to -10dB at 10 kc/s
Bass +15dB to -12dB at 100 c/s
- **SIZE**—6½ × 2½ × 2½ ins. overall, plus knobs
- **FINISH**—Front panel in brushed and polished solid aluminium with solid aluminium knobs. Black figuring on front panel.

BUILT TESTED AND GUARANTEED


£9.19.6

SINCLAIR STEREO 25
DE-LUXE PRE-AMPLIFIER AND CONTROL UNIT

A COMPLETE HIGH FIDELITY STEREO ASSEMBLY FOR £22.18.0

All you need is one Stereo 25 Pre-amp Control Unit (£9.19.6), two Z.12's (£8.19.0) and one P.Z.3 Mains Power Supply Unit (£3.19.6) to possess the finest possible hi-fi stereo installation. As a very desirable optional extra, you could include the Micro FM (£5.19.6) described on page one of our advertising. The overall saving to you in cash will be staggering, and you will have an installation second to none irrespective of price.

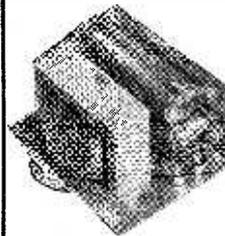SINCLAIR P.Z.3 TRANSISTORISED POWER SUPPLY UNIT



Designed specially for the very high standards of the Z.12, this entirely NEW power supply unit uses advanced transistorised circuitry to achieve exceptionally good smoothing. Ripple is a barely measurable 0.05 V. The P.Z.3 will power two Z.12's and the Stereo 25 with ease.

79/6

If you prefer not to cut this page, please mention PW.9 when writing your order.

Your Sinclair Guarantee

If you are not completely satisfied when you receive your purchase from us, your money will be refunded at once in full and without question.



To SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send

 for which I enclose
 CASH/CHEQUE/MONEY ORDER for
 £ s. d. PW.9

NAME
 ADDRESS

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/6d. per word (minimum order 18/-), box number 1/6d. extra. Semi-displayed setting £4. 12s. 6d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL WIRELESS, George Newnes Ltd., Tower House, Southampton Street, London, WC2, for insertion in the next available issue.

SOUND RECORDINGS

A UNIQUE TAPE BUY! Top brand 7in., 2,400ft., 25/-; 5 $\frac{1}{2}$ in., 1,200ft., 15/-. P. and P. 1 at 2/-, 2 at 2/9, 3-6 at 3/6. Bargains in all sizes. S.A.E. for list. E.C. KINGSLEY AND CO. LTD., 93 Tottenham Court Road, London, W.1. EUSton 6500.

SERVICE SHEETS

SERVICE SHEETS for all makes, Radio, T/V, Tape Recorders, 1925-1966. Prices from 1/-. Catalogue 6,000 models 2/6d. Free fault-finding guide with all Sheets. All types of valves, components, books, S.A.E. lists. Please send stamped addressed envelope with all orders/enquiries. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio and Television, 4/- post paid. VEST AND EMERY, 17 Hallgarth Street, Durham.

SERVICE SHEETS, Radio TV, 5,000 models. List 1/-. S.A.E. inquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS (75,000), 4/- each. Callers welcome. Always open. 5 South Street, Oakenshaw, Bradford.

SERVICE SHEETS

4/- each, plus postage

We have the largest display of Service Sheets for all makes and types of Radios and Televisions, etc., in the country. Speedy service. To obtain the Service Sheet you require please complete the attached coupon.

Name:

Address:

.....

To: **S.P. DISTRIBUTORS**
 44 Old Bond St., London, W.1
 Please supply Service Sheets for the following:

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

I require the new 1966 List of Service Sheets at 1/6 each plus postage.

(please delete items not applicable)
 I enclose remittance of.....
 (which includes postage)

MAIL ORDERS ONLY Sept. PW

RECEIVERS & COMPONENTS

TRANSISTORS, UNMARKED, UNTESTED, 40 for 10/-, p. and p. 1/-, 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc. (5,000 items), free. K. R. WHISTON (Dept. PRW), New Mills, Stockport.

ORIGINAL Dry Batteries for 38 and 18 Walkie Talkie, recent manufacture, 7/6 each, post 3/6 any number. G.W.M. Radio Ltd., 40/42 Portland Road, Worthing.

6 OC170s & 24 SUB-MIN DIODES (OA90s) on printed circuit board. Send SAE for details. **BOX No. 62.**

31 Set WTs, complete with 15 valves and 2 crystals. Operate up to 48 MEG tunable with circuit and details. 25/- each. Part post 5/-. Spare Set Valves and Crystals, 12/6. Chassis less valves, 12/6. P. & P. 5/-. No other spares available.

Assorted High Stub Resistors, 7/6, 100. Assorted Syflex P.F. Condensers, 7/6, 100. Paxolin Sheet, 1/16" x 12" x 12", 3/-. Thin Paxolin Sheet, approx. 1/16" x 12" x 12", 6 sheets for 5/-.

White Plastic Sheet, approx. 1/32" x 6 $\frac{1}{2}$ " x 24". Suitable diais, insulation, case fronts, etc. 4 sheets for 5/-.

Small E.M. Counters, 5 digit, 500 ohm, 6/6. Bulgin Extra Sensitive Micro Switch, 5/-. P.O. Relay 2000 ohm, 1B, 5/-, 1M, 1B 6/-. Key Switches, 4 pole, 2 throw, 3/6. 3 position DP+DP centre off, 5/-. 3 c/o+4 c/o centre off, 6/-. DP+DP 2 for 5/-.

Plessey Plugs and Sockets, 12 way, 3/- pr. 6 way, 5/- pr. 6 or 12 way screened cable to match, 3/- yd. Breast Mike, 6/-. Carbon Inserts, 1/6.

Power Pack and L.F. Amplifier for 38 Set, 15/-. Battery Ever-Ready, 90v+7 $\frac{1}{2}$ v, 4/6, 12 for 30/-. Small Component Boxes, 12/6, for 60 samples 6d. Mu. Metal Screen for 5uP7 with fittings 6/6.

250mA Fuses 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ", 5/-. 100. 100 volt Hand Generator, 7/6.

Valves New Boxed 6V6, 4/6. EF91, 3/-. 6AL5, 3/-. Rheostat WW Rotary, 15 ohms, 3.6 amp, 12/6. Details of Instrument Case Assembly. Free, send large addressed envelope.

Elac Speakers, 5", 5/-. 7" x 4", 7/-. 8", 8/-. Terms Cash with Order. Post 2/- on orders under 20/-.

Rotary Transformer. Input 12 volts, output 250v at 125mA, 9/-. Rotary Transformer. Input 12 volts, output 490v at 65mA, 9/-.

Siemens H.S. Sealed Relay. One c/o, 1700+1700 Ohms, 6/-. Rotary Transformer. 12v. input, 300v output, at 0.2 amp., 35/-. Elephantide Insulation Board, 4 pieces, 12" x 12" 5/-. Thin Ebonite Insulation Board, 12" x 12", 4 sheets for 5/-.

Modern lightweight Breast Mikes, Polythene fittings. New, 7/6, spare insert 2/6. Ebonite Tube, 7/16" OD x 12", 5 for 4/-.

.....

E. R. NICHOLLS
 Mail Order and Retail Shop
 46 LOWFIELD ROAD
 OF SHAW HEATH, STOCKPORT
 CHESHIRE

RECEIVERS & COMPONENTS

(continued)

R & R RADIO & TV SERVICE

Dept. P.W.
 MARKET STREET, BACUP, LANCOS.
 Telephone 465

SALVAGE VALVES		Tested before despatch	
6P13	4/6	U329	5/-
6L18	4/6	PL36	6/-
EP80	1/6	PL82	3/6
ECC82	3/-	U801	7/6
ECL80	3/6	10F1	1/6
30F5	5/-	U801	6/-
PL88	6/-	U801	5/6
PCF80	4/-	10P13	5/6
PL81	5/-	20D1	2/-
PZ30	5/-	30P12	5/-
		PY83	5/-

Speakers. Ex-TV. 5in. round 6 x 4in., 3/6; 8in. round 6/-; post 2/-.

Line Output Transformers available. State set model No. Turret Tuners, 8/-, post 2/-.

Sean Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD., Dept. PW79, 126 Hamilton Road, West Norwood, S.E.27. GIPsy Hill 6166.

BI-PAK SEMICONDUCTORS

8 RADNOR HOUSE
 93/97 REGENT STREET
 LONDON, W.1

LOW COST SILICON CONTROLLED RECTIFIERS
 50 PIV 1 amp, 8/6 400 PIV 7 Amp, 30/-
 100 PIV 7 Amp, 10/6 100 PIV 16 Amp, 16/6
 Free Circuit Diagrams with SCR orders.

FREE One 10/- Pack of your own choice with orders valued £4 or over. FREE

50 Trans. mixed untested	10/-
3 OC139 Trans. NPN Mullard	10/-
2 Drift Trans. 2N1225 100 M/cs	10/-
6 Matched Trans. OC44/45/81/81D	10/-
4 OA10 Diodes Mullard	10/-
15 Red Spot AF Trans. PNP	10/-
15 White Spot HF Trans. PNP	10/-
4 Sil. Rects. 3A, 100/400 PIV	10/-
4 NPN Trans. OC139, 2N1308	10/-
2 10 Amp Sil. Rect. 50/100 PIV	10/-
8 Diodes 4 OA70, 4 OA79	10/-
1 12 Amp SCR 100 PIV	10/-
3 Sil. Trans. 2N333 PNP	10/-
10 Assorted Computer Diodes	10/-
4 Zeners 5, 6.8, 10, 12 Vits	10/-
4 2G417 Trans. Eqvt. AP1116/7	10/-
2 200 M/cs Sil. Trans. BSY26/7	10/-
2 Bi-directional Trans. ASY66	10/-
4 High Current Trans. OC42	10/-
2 Power Trans. OC26/35	10/-
5 Sil. Rects. 400 PIV 250mA	10/-
3 OC71 Trans. Mullard	10/-
3 OC75 Trans. Mullard	10/-
3 NPN Sil. Trans. 70 M/cs	10/-
1 Power Trans. OC20 100 Vits	10/-
5 OA47 Gold Bonded Diodes	10/-
4 OA202 Sil. Diodes Sub-Min.	10/-
8 OA81 Diodes Sub-Min.	10/-
3 Sil. Rects. 400 PIV 500mA	10/-

Tunnel Diodes IN3720 15/-
 Unijunction Trans. 2N2646 15/-
 6 BY100 Sil. Rects. 20/-

100s of semiconductor bargains incl. Logic Modules send 2/6 for 3 months mailing. Add 1/- p. & packing per order. CASH WITH ORDER PLEASE. MAIL ONLY.

NEW—BIGGER—BETTER "EXPERIMENTAL" PRINTED CIRCUIT KIT

- (1) 2 Copper Laminate Boards 4½ x 2½in.
- (2) 1 Board for Matchbox Radio.
- (3) 1 Board for Wrist-Watch Radio, etc.
- (4) Resist. (5) Etchant. (6) Resist Solvent.
- (7) Cleanser/Degreaser. (8) 16-page booklet.

"PRINTED CIRCUITS FOR AMATEURS" containing full etching instructions

- (9) 2 Miniature Radio Dials SW/MW/LW. also free with each kit. (10) Circuits and Plans of easy-to-build transistorised

30 SUGGESTED PROJECTS

which you can build with your own components on a chassis made from this kit. Drawings. Photographs. Many recently developed very efficient designs you probably haven't heard of yet. (1) Crystal set with biased detector. (2) Crystal set with voltage-quadrupler detector. (3) Crystal set with dynamic loudspeaker. (4) Crystal tuner with audio amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRIFLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio.

3 SUBMINIATURE RADIO RECEIVERS

The smallest 3 designs yet offered to the Home Constructor anywhere in the World. Based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage-Stamp Radio. Size only 1.62 x .95 x .25in. (11) Wrist-watch Radio, 1.15 x .30 x .55in. (12) Ring-Ranger, .70 x .70 x .55 in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Receiver. (15) Transistor P/P amplifier. (16) Intercom. (17) 1-valve amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal. Guided Missile. (20) "Perpetual Motion" Machine. Atmospheric Engine. (21) Metal Detector. (22) Simple Transistor Tester. (23) Human Body Radiation Detector. (24) Electronic Man/Woman Discriminator. Thermal Proximity Fuse. (25) Pocket Signal Injector. (26) Pocket Transceiver (Licence Required). (27) Constant volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive Loop Transmitter. (30) Pocket Triple Reflex 6-transistor sensitive receiver with transformer-less push-pull output.

P.C. Kit Price 3/6. Post and Packing 1/6. Extra Laminate Board available.

STOP PRESS! PHOTOELECTRIC PRINTED CIRCUIT KIT Build 10 EXCITING PHOTOELECTRIC DEVICES

on a Printed Circuit Chassis. Basic Kit: 39/6. Post and Packing 2/6. Contents: 2 Copper Laminate Boards and all chemicals required. Etching Manual. Latching Relay and Bracket. Infra-red sensitive Photocell and Hood. 2 high-gain Transistors. Resistors, cond. Terminal Block. Elegant Plastic Case. Essential Data, Circuits and P.C. chassis plans of

10 PHOTOELECTRIC PROJECTS

- (1) Simple Photo-switch. (2) Modulated Light Alarm. (3) Long-Range Stray-Light Alarm. (4) Relay-less Alarm. (5) Warbling Tone Electronic Alarm. (6) Closed-Loop Alarm. (7) Projector Lamp Stabiliser. (8) Electronic Projector Modulator. (9) Mains Power Supply Unit. (10) Car Parking Light Controller. BASIC KIT enables you to build an efficient unmodulated light Photo-Switch/Burglar Alarm, Counter etc. (Project No. 1) which can be modified for modulated light operation by the addition of a few extra components obtainable separately. (No. 2, 3.)

OPTICAL KIT

2 lenses, 2 mirrors, Infra-Red Filter Low-consumption bulb and holder (for Projects No. 8 and 9). Plans for making straight and folded-beam Projectors and Photocell Receivers. Details of home-made long-life batteries for B/A Projectors etc., etc. Price 19/6. Post and Packing 1/6.

"YORK ELECTRICS"
181a YORK ROAD, LONDON, S.W.11
Send S.A.E. for details and photographs

RECEIVERS & COMPONENTS (continued)

COMPARE OUR PRICES

Sub-min. Electrolytics. Per doz. 2-6-8-10µf 15v, 9/-. 50-100µf 15v., 11/-
Garrard Lab. 80 with stereo PU.....£24
401 Transcription Unit (no PU).....£27
All carriage paid. Lists on request.

J. C. WOODWARD
94 Great Brickkiln Street
Wolverhampton.

SILICON PLANAR TRANSISTORS, high gain NPN from 2/9, brand new. 5% resistors 2/3 doz., your selection. BY238, mains ½A rectifiers, 4/6. Catalogue 6d. ELECTRO-VALUE, 6 Mansfield Place, Ascot, Berkshire.

6 TRANSISTOR PRINTED CIRCUIT RADIO



Components for the above as follows:—
6 transistor printed circuit 1/8. 2½in. speaker 6/6.
Ferrite block 1/-. Edge volume control D.P.5K. 1/8
IF. and Osc. coils (set of 4) 8/8 set. Slide switch
D.P.D.T. 1/-. Ganged condenser 5/-. P.P. output
transformer 7/8. Driver transformer 7/8. Circuit 1/6.
37/6 All the above made specially and
ready for assembly. Any item supplied
separately. Add 1/6 P. & P. when
order less than 10/-.
CLEVELEYS ELECTRICAL ENGINEERING Co.
Holmfield Av., Cleveleys, Nr. Blackpool

TAPE RECORDERS, TAPES, Etc.

TAPES TO DISC — using finest professional equipment 45 rpm—18/-. S.A.E. leaflet. DEROY, 52 Hest Bank Lane, Lancaster.

AMPEX SERIES 600 Professional Recording Tape. Type 641. 1,800ft. Mylar on 7in. spool. Complete with leader. Brand new in maker's boxes. Usual price £3. Limited quantity available at 67/- for two spools, P. and P. 2/- (or 37/- singly, P. and P. 1/6). E. C. KINGSLEY & Co., 93 Tottenham Court Road, London W.1. EUSTON 6500.

FOR SALE

TERRIFIC BARGAINS in high-class Hi-Fi Radio, Gramophone and Tape equipment always available. Save £££s. Send now for latest BARGAIN LIST or call Mon-Fri. 9-6, Sat. 9-4, or phone PRIMROSE 3314. NRS, Dept. FW, 16 King's College Road, off Adelaide Road, London, NW3.

SPECIAL OFFER

GEVAERT TAPE. New, Boxed, 5½, 600ft. with Stop and Leader Tapes, 9/- or 6 for 50/-, post paid.
GRUNDIG MAI. 2 Transistor Pre-amps for Tape Monitoring or Microphone Boosters, 57/6, post paid.
LIST PRICE 4 GNS.
LEE ELECTRONICS
400 Edgware Road, Paddington 5521
Send for Free Lists and details of above

FOR SALE (continued)

MORSE MADE EASY!

The Famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum.

One student, aged 20, took only 13 DAYS, and another, aged 69, took under a week to read 18 wpm. If you wish to read Morse easily and naturally please enclose 8d. in stamps or two international reply coupons for full explanatory leaflet to:

G3CHS, 45 Green Lane, Purley, Surrey.

ADHESIVE STRIP LABELS. ½" embossed Glossy. P.V.C. various colours. 1½d. letter. C.W.O. & S.A.E. to:—MR. BROWN, 1 Effie Place, London, S.W.6.

HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS AND BOXES

• THE PATTERN IS IN THE TIN •
ALL YOU DO IS BRUSH IT ON!

2½ oz. tins 3/6 ½ gallon 35/-*
½ pint 7/8 1 gallon 53/-*
1 pint 15/- (*sent by road)
Carriage. Orders up to 5/-, 9d.; up to 10/-, 1/9; over 10/-, 2/9. Colours: blue, silver, black or bronze. Return of post service, Monday to Friday.

From your component shop or direct from the manufacturer:

FINNIGAN SPECIALTY PAINTS (FW)
Mickley Square, Stockfield, Northumberland.
Tel. Stockfield 2280.

SPECIAL OFFER

1 watt S.T.C. 300 mc/s N.P.N. Silicon Planar, 100% Transistors limited stocks. £1 for 6.

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16, GET20.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171.

5/- each. OC139, OC140, GET7, GET8, GET9, XC141, BY100, OA211.

SUN SOLAR CELL KITS

24 page Booklet on Experiments inc. 4 Sun Solar Cells, 11/- set.

G.P.O. DIAL TELEPHONES

20/- each. 35/- pair.

Send 6d. for full lists:—
inc., S.C.R., Zeners.

CURSONS

78 BROAD STREET
CANTERBURY, KENT

YUKAN SELF-SPRAY

GET THIS AIR DRYING
HAMMER FINISH NOW!

So professional—the YUKAN aerosol way!

YUKAN Aerosol spraykit contains 16 ozs. fine quality, durable, easy instant spray. No stove being required. Available in Grey, Blue, Gold, Bronze at 14/11 at our counter, or 15/11 carriage paid, per push button self-spray can. SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11, carr. paid. Choice of 13 self-spray plain colours and primer (motor car quality) also available. Please enclose cheque or P.O. for total amount to:

YUKAN Dept. P.W.9 307a Edgware Road, London W.2 (Open all day Saturday, Closed Thurs. afternoon.)



FOR SALE*(continued)***ELECTRIC SOLDERING-IRON****FANTASTIC BARGAIN OFFER**

Lightweight Pistol Grip handle 40 watt, 240/250v. A.C. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handyman. A boon to model makers and a necessity for every wireless enthusiast. Offered to you at this new amazing price.

ONLY
10/-
Post Free

G. H. SERVICE (Dept P.W.)

Lusted Hall Lane, Tatsfield, Kent.

WANTED

VALVES WANTED, brand new popular types boxed. **DURHAM SUPPLIES (C)**, 175, Durham Road, Bradford 8, Yorkshire.

WE BUY New Valves and Transistors. State price. **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

DAMAGED AVO METERS wanted. Models 7 and 8. Any condition. Any quantity. **HUGGETTS LTD.**, 2-4 Pawson's Road, West Croydon.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.

103 North Street, Leeds 7

WANTED: Popular Brand New Valves. R.H.S. Stamford House, 538 Great Horton Road, Bradford 7.

WE BUY New Valves for cash, large or small quantities, old types or the latest by return. Send details. Quotations by return. **WALTON'S WIRELESS STORES**, 15 Church Street, Wolverhampton.

EDUCATIONAL

OCEAN LINERS and other ships require Radio Officers. State if Attendance or Postal Course desired. Approved Training Centre: Radio School, 91 Lancaster Road, Preston, Lancs.

EDUCATIONAL*(continued)*

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies during 1967. Grants available. Day and Boarding students. Stamp for prospectus. Wireless College, Colwyn Bay.

CITY AND GUILDS (Electrical, etc.) on "Satisfaction or refund of fee" terms. Thousands of passes. For details of modern courses in all branches of Electrical Engineering, Electronics, Radio, TV Automation, etc., send for 156-page handbook—FREE. B.I.E.T. (Dept. 168K), 29 Wright's Lane, London, W.8.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs) R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how **ICS** can help you in your career.

ICS, DEPT. 541 PARKGATE ROAD, LONDON, S.W. 11.

MISCELLANEOUS**BERNIESOUND (AUDIO ENGINEERS)**

DESIGN—BUILD—REPAIR—MODIFY
ELECTRONIC EQUIPMENT, write for estimate.

Mr. BROWN

1 Effie Place, London, S.W.6.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write **NOW** for free leaflet and further details to **C & S, 20 Maude Street, Darlington, Durham.** Send 3d. stamp.

CONVERT ANY TV SET into an Oscilloscope. Diagrams and instructions 12/6. **REDMOND**, 42 Dean Close, Portslade, Sussex.

SITUATIONS VACANT

A.M.I.Mech.E., A.M.I.E.R.E., City and Guilds G.C.E., etc. Become a Technician or Technologist for high pay and security. Thousands of passes. For details of Exams and Courses in all branches of Engineering, Building, Electronics, etc., write for 156-page handbook—FREE. B.I.E.T. (Dept. 169K), London, W.8.

RADIO TECHNICIANS

A number of suitably qualified candidates will be required for training, leading to permanent and pensionable employment. (Normally at Cheltenham but with opportunities for service abroad or appointment to other U.K. establishments including London.)

Applicants must be 19 or over and be familiar with the use of Test Gear and have had Radio/Electronic workshop experience. They must offer at least "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19 £747, at 25 £962 (highest age pay on entry) rising by four annual increments to £1,104.

Prospects of promotion to grades in salary range £1,032-£1,691. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days.

Normal Civil Service sick leave regulations apply.

Apply

Recruitment Officer (RT 54)
Government Communications Headquarters
Oakley, Priors Road
CHELTENHAM, Glos.

TV AND RADIO: A.M.I.E.R.E., City and Guilds R.T.E.B. Cert., etc., on "Satisfaction or refund of fee" terms. Thousands of passes. For details of Exams and Home-training Courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 156-page handbook—FREE. B.I.E.T. (Dept. 137K), 29 Wright's Lane, London, W.8

hnd**HIGHER NATIONAL DIPLOMA**

in Applied Chemistry, Electrical Engineering and Production Engineering. Entry Qualifications: One "A" level or good O.N.C. or O.N.D.

Full particulars from: *The Academic Registrar ref. M9/1*

ENFIELD COLLEGE OF TECHNOLOGY

Queensway, Enfield, Middlesex. Tel.: HOWard 1126

**Telecommunications**

Vacancies exist for Young Men keen to make Electronics their career who have not necessarily acquired great practical or theoretical knowledge, but who have suitable interest and who have possibly already constructed some equipment themselves. Training will be provided and applicants will be encouraged to take technical studies to further their careers. Applications to Personnel Manager, Cambridge Works Ltd., Haig Road, Cambridge. Telephone Cambridge 51351.

SITUATIONS VACANT
(continued)

**Transistor
Radio
Service
Engineers**

**can earn £20 plus
per week**

Applicants must have practical
experience in all types of
Transistor Receivers

write or phone for appointment to

Mr. H. Gee
Perdio Products Limited
Lowther Road
Stanmore Middlesex

Telephone Wordsworth 0020

RADIO AND TV Exam. and Courses by
Britain's finest Home-study School. Coaching
for Brit.I.R.E., City and Guilds Amateur's
Licence, R.T.E.B., P.M.G. Cert., etc. FREE
brochure from BRITISH NATIONAL RADIO
SCHOOL, Russell Street, Reading.

**RADIO
TECHNICIAN**

with a sound knowledge of at least three
of the following types of equipment is
required immediately for Meteorological
Office Ocean Weather Ships:

Single Side-Band Transmitter,
Radar (Navigational),
Radar Height Finding,
Echo Sounders and Radio Receivers,
Automatic D.F., V.H.F. and M.F. Low
Voltage Servo Recorders,
Digital Telemetering Equipment.

Salary Scale: £678-1104 per annum, accord-
ing to age, plus £120 per annum overtime
allowance. Free food and accommodation
provided on board ship.

Applicants must be natural born British
subjects.

Full details from

SHORE CAPTAIN
Ocean Weather Ship Base,
Great Harbour, Greenock
Telephone: Greenock 24291

METAL WORK

METAL WORK: All types cabinets, chassis
racks, etc., to your specifications. **PHILPOTTS
METAL WORKS LTD.**, Chapman Street,
Loughborough.

BOOKS & PUBLICATIONS

AUDIO, America's foremost journal. Year's
subscription 43/-, specimen copy 4/-. All
American radio journals supplied—list free.
WILLEN (Dept. 40), 61a Broadway, London,
E.15.

BOOKS & PUBLICATIONS
(continued)

SURPLUS HANDBOOKS

19 set Circuit and Notes ... 4/6 p/p 6d.
1155 set Circuit and Notes ... 4/6 p/p 6d.
H.R.O. Technical Instructions 3/6 p/p 6d.
38 set Technical Instructions... 3/6 p/p 6d.
46 set Working Instructions ... 3/6 p/p 6d.
88 set Technical Instructions... 5/- p/p 6d.
BC.221 Circuit and Notes ... 3/6 p/p 6d.
Wavemeter Class D Tech. In-
structions 3/6 p/p 6d.
18 set Circuit and Notes ... 3/6 p/p 6d.
BC.1000(31set)Circuit & Notes 3/6 p/p 6d.
CR.100/B.28 Circuit and Notes 8/6 p/p 9d.
R.107 Circuit and Notes ... 5/- p/p 6d.
AR.88D Instruction Manual ... 15/- p/p 1/6
62 set Circuit and Notes ... 4/6 p/p 6d.

Circuit Diagrams 3/- each post free.
R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and
26, A.1134, T.1154 (all models), BC.312,
BC.342, BC.348J, BC.348, (E.M.P.). BC.624
Resistor colour code indicator, 1/6 p/p 6d.
S.A.E. with all enquiries please.
Postage rates apply to U.K. only.

Mail order only to:

**INSTRUCTIONAL HANDBOOK
SUPPLIES**

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8


**A.R.R.L. RADIO AMATEURS
HANDBOOK 1966**

New Edition 40/-, Postage 3/-.
ABC's of Silicon Controlled Rectifiers
by Lytel. 16/-, P. & P. 1/-.
**Transistor Specifications and Substitution
Handbook** by Techpress. 15/-, P. & P.
1/-.
Transistor Ignition Systems Handbook
by Ward. 22/6, P. & P. 1/-.
Digital Computers in Automation by
Lytel. 35/-, P. & P. 1/-.
**How to build Proximity Detectors and
Metal Locators for Shields.** 20/-, P. & P. 1/-.
**Transistor Circuits for Radio Controlled
Models** by Boys. 7/6, P. & P. 9d.
Where possible 24-hour service guaranteed.

UNIVERSAL BOOK CO.
12 LITTLE NEWPORT STREET,
LONDON, W.C.2
(Leicester Square Tube Station)



**EQUIPMENT CABINETS
OF DISTINCTION**

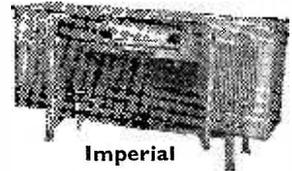

Imperial

- Illustrated in this advertisement are two fine cabinets from the Lewis Radio Range.
- These cabinets are just two of a really extensive range.
- Each one carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex

**FREE THE NEW LEWIS
RADIO CATALOGUE**

Designed to assist your choice of
Cabinet.
The New Lewis Radio Cabinet Cata-
logue—the most comprehensive ever
prepared. Sent absolutely FREE!
Please send your FREE cabinet catalogue.

NAME

ADDRESS

..... (Dept. P96)
Capitals please

LEWIS radio

100 Chase Side, Southgate, London
Tel.: Palmer's Green 3733 9666

6 VALVE AM-FM TUNER UNIT



Med. and VHF 190m-350m, 86 Mc/s.-103 Mc/s., 6 valves and metal rectifier. Self-contained power unit A.C. button controls, on/off, Med., VHF. Diodes and high output sockets with gain control. Illuminated 2-colour perspex dial 1 1/2 in. x 4 in., chassis size 1 1/2 in. x 4 in. x 5 1/2 in. A recommended Fidelity Unit for use with Mullard "3-3" or "3-10" Amplifier. Bargain Price. Complete kit of parts, inc. Power Pack as illustrated, £10.18.6. Carr. 7/6. Ditto less Power Pack, £9.18.6. Carr. 7/6. Circuit and Const. details, 4/6. Free with kit.

MULLARD "3-3" & "5-10" HI-FI AMPLIFIERS

3 OHM AND 15 OHM OUTPUT. "3-3" Amp. 3-valve, 3 watt Hi-Fi quality at reasonable cost. Bass Boost and Treble controls, quality sectional output transformer, 40 ohms-25 kOhms 1 + dB, 100mV for SW, less than 1% distortion. Bronze esoteric panel. Complete Kit only 7 gns. Carr. 5/-. Wired and tested £8.10.0.

MULLARD "5-10" AMPLIFIER. 5 valves 10W, 3 and 15 ohms output, Mullard's famous circuit with heavy duty ultra-linear quality output tr. Basic amplifier kit price £9.18.6. Carr. 7/6. Ready built 11 1/2 gns.

2-VALVE PRE-AMP UNIT. Based on Mullard's famous 2-valve (2 x EF86) circuit with full equalisation with volume, bass, treble, and 5-position selector switch. Size 8in x 8in x 2 1/2 in. Complete kit 6 gns. Ready built, £7.18.6. Carr. 3/6.

CO-AX 80 OHM CABLE. High grade low loss Cellular air spaced Polythene—1/4 in. diameter. Stranded core. Famous manufacturers. Still only 6d. per yard.

Bargain Prices—Special lengths:
20 yds. 9/-. P. & P. 1/5. 40 yds. 17/6. P. & P. 2/-.
60 yds. 25/-. P. & P. 3/-.
Co-ax Plugs 1/-. Sockets 1/-.
Couplers 1/8. Outlet boxes 4/6.

**VOLUME CONTROLS—5K—2 Meg ohms. 3in. SPINDLES, MORGANITE MIDGET TYPE 1 1/2 in. dia. GUAR. 1 year LOG or LIN, ratios, less Sw. 3/8. D.P. Sw. 5/-. Twin Stereo less Sw., 7/6, 100K to 2mΩ ohm with D.P. Sw., 9/6. Some log/anti log valves less Sw., 9/-.
TYGAN FRET (Contem. pat.) 12in. x 12in., 2/-; 12in. x 18in., 3/-. 12in. x 24in., 4/-. etc.
YENAIR various patterns, 2/- sq. ft.
**RESISTORS—Modern ratings full range 10 ohms to 10 megohms. 20% 1/2 w. 3d. ea., ditto 1 w. 6d. ea., 2 w. 8d. ea., 10% 1/2 w. 4d. ea., 5% Hi-stab., 1/2 w. 6d. ea. (below 100 ohms and over 1 meg. 9d. ea.). 1% Hi-stab., 1/2 w. 1/6 ea. (below 100 ohms 2/- ea.).
WIREWOUND. 25 ohm to 10K. 5 w. 1/3. 10 w. 1/6. 15 w. 2/-.
BONDACOUST Speaker Cabinet Acoustic Wadding. Approx. 1in. thick, 18in. wide, any length cut, 2/3 ft. 6/- yd.
CONDENSERS Silver Mica. All values, 2 pF to 1,000 pF. 6d. each. Ditto ceramics 9d. Tub. 450v. T.C.C., etc. 0.01 mFd.—0.1 mFd. 6d., 0.1 mFd. 850v. 10d., .02-500 v. 1/-. .25 Hunts 1/8. 5 T.C.C. 1/8, etc.
CLOSE TOL. S/MICAS. 10%, 5 pF—500 pF 9d. 600-5,000 pF 1/-. 1% 2 pF-100 pF 9d. 100-500 pF 1d. 575 pF-5,000 pF 1/6.
ENAMELLED COPPER WIRE—NEW PRICES. 2 oz. reels 14s-20s, 3/-; 22s-28s, 3/6; 36s-38s, 4/8; 39s-40s, 5/- etc.
ALUMIN. CHASSIS. 18g. plain, undrilled, folded 4 sides, 2in. deep, 6in. x 4in., 4/6; 8in. x 6in., 5/8; 10in. x 7in., 6/8; 12in. x 6in., 7/6; 12in. x 8in., 8/- etc.
ALUMIN. SHEET. 18g. 8in. x 6in., 1/-. 6in. x 9in., 1/6; 6in. x 12in., 18/-; 12in. x 12in., 4/6, etc.****

EMPTY TAPE REELS (Plastic)
3" 1/3 4" 2/- 5" 2/- 7" 2/3

PLASTIC REEL CONTAINERS
(cassettes) 3" 1/3 5" 1/9 5 1/2 2/- 7" 2/3

ELECTROLYTICS ALL TYPES NEW STOCK
TUBULAR CAPACITORS
25/25v. 50/12v., 1/6 50/50v. 100/25v. 2/-; 8/450v. 4/850v., 2/8; 16/60/450v., 5/8; 32/32/450v., 6/8; 8-8/450v., 4/8; 32+32/275v., 4/8; 50+50/350v., 6/8; 60+250/275v., 17/8; 100+300/275v., 12/8.
Transistor Midget types—all values 1 mFd. to 50 mFd., 1/8 ea. 100 mFd., 2/-, all 5v. working.

Only a small selection from our vast stocks. Send for full bargain lists, 3d.

TRS RADIO COMPONENT SPECIALISTS
Est. 1946

70 Brigstock Rd., Thornton Heath, Surrey.
TEO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 3lb., 1/-; 1 lb., 1/8; 3 lb., 3/-; 5 lb., 3/8; 8 lb., 4/6
Hours: 9 a.m.—6 p.m., 1 p.m., Wed.

LOOK! AT OUR PRICES

OC71 TRANSISTORS
or 27/16 doz. P. & P. 6d. **2/6** EACH P. & P. 4d.

MAT TRANSISTORS
Mat 100 or 120 **7/9** post 4d.
Mat 101 or 121 **8/6** post 4d.

GERMANIUM RECTIFIERS **2/6** EACH P. & P. 6d.
GJ7M 24v 1/2 amp.
or 24/- doz., post 1/-.

MINIATURE GERMANIUM DIODES Postage 6d. **6/-** Doz.

SILICON RECTIFIERS **5/-** EACH P. & P. 6d.
800v. P.I.V. 500 mA.

TRANSISTOR HOLDERS **11/6** dozen. P. & P. 6d.
3 or 5 Pin.
1/- each, post 4d.

VEROBOARD
2 1/2" x 5" 3/8 **2 1/2** x 3" 3/-
3 3/4" x 3 3/4" 3/8 **3 3/4** x 5" 5/2
Postage 6d. each extra.

RECORDING TAPE
International first grade quality American tape.
5 1/2" 1800ft. D.P. Mylar 22/6, post 1/6
7" 2400ft. D.P. Mylar 25/-, post 2/-

PETHERICK'S RADIO SUPPLIES
Dept. P.
22 HIGH STREET, BIDEFORD, N. DEVON
Tel.: Bideford 3217

NEW RANGE U.H.F. AERIALS FOR BBC 2 (625) line transmissions

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 35/-; 11 element, 42/6; 18 element, 50/-; 18 element, 57/6. Wall Mounting with Cranked Arm, 7 element, 80/-; 11 element, 67/-; 14 element, 75/-; 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6; 11 element, 55/-; 14 element, 62/-; 18 element, 70/-.

Chimney Mounting Arrays, 7 element, 72/6; 11 element, 80/-; 14 element, 87/6; 18 element, 95/-. Complete assembly instructions and hints on installation with every unit. **Low Loss Cable, 1/6 yd. U.H.F. Preamps, from 75/-.** State clearly channel number required on all orders.

BBC · ITV · F.M. AERIALS

BBC (Band 1). Telescopic loft, 21/-; External S/D, 30/-; "H" £2.10.0

ITV (Band 3). 3 Element loft array, 25/-; 5 element 35/-; Wall mounting, 3 element, 35/-; 5 element, 45/-.

Combined BBC/ITV. Loft 1+3, 41/3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3.

VHF transistor pre-amps 75/-.

F.M. (Band 2). Loft S/D, 12/6, "H", 30/-, 3 element, 52/6. External units available. Co-ax cable, 8d. yd. Co-ax plugs, 1/3. Outlet boxes, 4/6. Diplexer Cross-over Boxes, 12/6. C.W.O. or C.O.D. P. & P. 4/6. Send 6d. stamps for illustrated lists.

Quotations for special arrays available on request

K.V.A. ELECTRONICS (Dept. P.W.)
27 Central Parade, New Addington
Surrey
LOD 2266

DANE Electronics

39 Barrack Rd. Northampton

SOUND BARGAINS



LAB.80 Transcription Player
Made for the connoisseur, with advanced features including record changing facilities, low-resonance wood pick-up arm, anti-static turntable mat, heavy alloy turntable, magnetic repulsion auto-trip pick-up arm bias compensator and cueing facilities on manual. Less cartridge. **£26.10.0**

SP.25
High quality single player, features include integral cueing device which raises or lowers pick-up at any point on record. Less cartridge. **£11.10.0.**

AT.60
Accepted as the automatic turntable foremost in its class. Manual and auto. Less cartridge. **£11.19.0.**

3000
Low mass tubular pick-up arm designed for use with high compliance cartridges is a special feature of this most efficient model. Stereo with sonotone 9 T.H. cartridge, and Diamond stylus. **£10.10.0**

SRP.12
Extremely compact and inexpensive single player with good performance. **£5.5.0.**

1000
Automatic model 10in. turntable. Exceptional value at very low cost. **£6.19.0**

All above models wired for STEREO.

High Quality Cartridges
Acos GP.83 Stereo 11/6
Acos GP.73 Stereo 10/-
Acos GP.67 Mono 9/-
SONOTONE 8T less shell 15/-
EV.26 with shell and Diamond stylus 27/6
As above with Sapphire 21/6
All goods fully guaranteed. Post and packing paid.

To DANE ELECTRONICS
39 Barrack Rd. Northampton
I am interested in please send me

Cheque/PO enclosed for
PO No.
NAME
ADDRESS

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values, details of which are given in the latest edition of the Constructors' Booklet Priced at 2/-.

Oscillator Coil.....	P50/1AC (For OC45)	P50/1AC (For AF117).....	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117).....	5/7
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117).....	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117).....	6/-
Rod Aerial	RA2W		12/6
Driver Transformer	LFDT4/1		9/6
Output Transformer	OPT1		10/6
Printed Circuit	PCAI		9/6

I.F. TRANSFORMERS & COILS FOR VALVE CIRCUITS

Production of Tuning Coils (Type "H") and I.F. Transformers is being continued and details of these and our other components are given in an illustrated folder which will be forwarded on request with 4d. postage please.

WEYRAD (ELECTRONICS) LIMITED
SCHOOL STREET, WEYMOUTH, DORSET

FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio and Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

SATISFACTION OR REFUND OF FEE

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £30 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.M.I.
A.I.O.B.
B.Sc.
A.M.I.E.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.


PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc., A.M.I.E.R.E., City & Guilds Radio Amateur's Exam R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

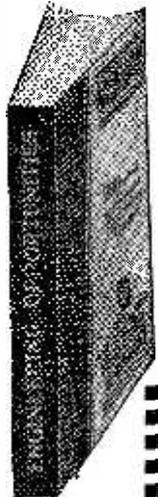

POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME

ADDRESS

SUBJECT OR EXAM THAT INTERESTS ME..... 344B

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

(Dept. 344B), 29 Wrights Lane, London, W.8

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

SURBITON PARK RADIO

AMPLIFIERS · TUNERS Selection

ARMSTRONG 221 10-10 watts Stereo, Mag PU and Filter Cash £23.15.0
Or Dep. 135/- and 8 m. pymts. 49/6 (H.P. Price £36.9.0)
ARMSTRONG 222 10-10 watts Stereo Amplifier Cash £27.10.0
Or Dep. 110/- and 12 m. pymts. 40/4 (H.P. Price £29.14.0)
ARMSTRONG 224 F.M. TUNER Powered. Cash £22.10.0
Or Dep. 90/- and 12 m. pymts. 33/- (H.P. Price £24.5.0)
ARMSTRONG 223 AM/FM TUNER Powered Cash £25.15.0
Or Dep. 115/- and 12 m. pymts. 42/2 (H.P. Price £31.1.0)
ARMSTRONG 127 MONO SW with AM/FM Cash £26.10.0
Or Dep. 106/- and 12 m. pymts. 38/10 (H.P. Price £28.12.0)
ARMSTRONG 127 STEREO as above Stereo amp. Cash £27.10.0
Or Dep. 150/- and 12 m. pymts. 55/- (H.P. Price £40.10.0)
ARMSTRONG 227 MONO 10W amp. with AM/FM Cash £26.15.0
Or Dep. 147/- and 12 m. pymts. 58/10 (H.P. Price £39.15.0)
ARMSTRONG 227 STEREO as above with Stereo Amp. Cash £25.15.0
Or Dep. 211/- and 12 m. pymts. 77/4 (H.P. Price £26.19.0)
ARMSTRONG 226 STEREO as above, but Mag. P.U. Filter Cash £21.0.0
Or Dep. 250/- and 12 m. pymts. 88/- (H.P. Price £25.16.0)
 Teak Cases for all Armstrong Units £3.10.0

MOTORS · PICK-UPS Selection

GARRARD SRP10 Mono Cash £5.10.0
GARRARD Model 1000 Mono Cash £7.10.0
Or Dep. 34/- and 6 m. pymts. 26/- (H.P. Price £9.10.0)
GARRARD Model 9000 Stereo Lightweight arm Cash £11.11.0
Or Dep. 47/- and 8 m. pymts. 25/6 (H.P. Price £12.11.0)
GARRARD S.P.25 Less cart.: Single player Cash £12.10.0
Or Dep. 50/- and 8 m. pymts. 27/6 (H.P. Price £13.10.0)
GARRARD A760 Less cart.: Heavy table Cash £13.0.0
Or Dep. 32/- and 12 m. pymts. 19/- (H.P. Price £14.0.0)
GARRARD LAB80 Push button oper. less cart. Cash £27.10.0
Or Dep. 110/- and 12 m. pymts. 40/4 (H.P. Price £29.14.0)
GARRARD 401 Transcription Table. No arm. Cash £32.10.0
Or Dep. 130/- and 12 m. pymts. 47/8 (H.P. Price £35.2.0)
GOLDRING G66 Mono Single Player Cash £11.11.0
Or Dep. 47/- and 8 m. pymts. 25/6 (H.P. Price £12.11.0)
GOLDRING G168 Less cart. Pickup lift. Cash £19.10.0
Or Dep. 78/6 and 12 m. pymts. 28/7 (H.P. Price £21.1.6)
GOLDRING G170 Less cart. P.U. lit. Heavy table Cash £29.18.6
Or Dep. 120/6 and 12 m. pymts. 43/9 (H.P. Price £32.5.6)
 Terms: C.W.O. or C.O.D. ALL ITEMS CARRIAGE FREE
 Leaflets available upon receipt of 6d. stamp

48-50 Surbiton Road, Kingston-on-Thames, Surrey

Phone KIN. 5549

Hours 9 a.m. to 6 p.m. daily (1 p.m. Weds.)

PADGETTS RADIO STORE

OLD TOWN HALL,
LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

Reclaimed Tubes, Six months' guarantee.
 AW43/80, 30/- MW43/80, 30/- MW43/65, 30/-
 CRMT2, 30/-, CRM142, 17/-, 12" Tubes, 10/-,
 17" tubes perfect but without guarantee, 17/-
 each. Carriage on any tube in G.B., 10/-.

Specialty Selected Nearly New Valves with
 6 months' guarantee. Single valves. Post 7d.

PY33	6/-	807	5/-	EF91	2/-
PC084	5/6	ARP12	1/6	6K7	1/2
PC080	5/6	ECL80	3/6	6K8	2/-
PL36	6/-	ECC83	5/-	6V6	1/9
PL81	5/6	ECC82	4/3		

VALVE LIST

Ex. Equipment, 3 months' guarantee.
 Single Valves Post 7d.

EF90	1/6	KT36	5/-	6F14	5/-
ECL80	1/6	POF80	2/-	10C2	5/-
EF91	9d.	PC84	2/-	10P13	2/6
EB91	9d.	PCL82	4/-	10P14	5/-
EBF80	3/-	PCL83	3/-	20D1	2/-
ECC81	3/-	PCL84	3/-	20L1	5/-
ECC82	3/-	ECL85	3/6	20P1	5/-
ECC83	4/-	PZ30	3/-	20P4	8/6
EL84	5/-	PY81	1/6	U801	8/6
EY51	2/6	PY82	1/6	U329	5/-
RF50	1/-	PL81	4/-	U301	5/-
EY86	5/-	PL96	5/-	U191	5/-
6K25	5/-	PY33	2/-	U281	5/-
6U4	5/-	6B8	1/6	U282	5/-
6P25	5/-	6F1	1/-	U25	5/-

Special Offer. Bush TV56 17" 13-channel TV Sets in good working order fitted with good tube. Cabinet condition fair. 28. Carriage 10/-.
 Untested 17" TV Sets, complete fitted with all BBC and ITV coils 50/-. Carriage 10/-.

New Jap Earpieces complete with lead and plug. 8 ohms 3 or 5mm., 1/11 or 20/- per doz. Post Free.

Perfect Speakers removed from T.V. sets. Round 8", 6", 4", 3", 2", 1 1/2", 1", 3/4", 5/8", 1/2", 1/4", 1/8", 1/16", 1/32", 1/64", 1/128", 1/256", 1/512", 1/1024", 1/2048", 1/4096", 1/8192", 1/16384", 1/32768", 1/65536", 1/131072", 1/262144", 1/524288", 1/1048576", 1/2097152", 1/4194304", 1/8388608", 1/16777216", 1/33554432", 1/67108864", 1/134217728", 1/268435456", 1/536870912", 1/1073741824", 1/2147483648", 1/4294967296", 1/8589934592, 1/17179869184, 1/34359738368, 1/68719476736, 1/137438953472, 1/274877906944, 1/549755813888, 1/1099511627776, 1/2199023255552, 1/4398046511104, 1/8796093022208, 1/17592180444416, 1/35184360888832, 1/70368721777664, 1/140737443555328, 1/281474887110656, 1/562949774221312, 1/1125899548442624, 1/2251799096885248, 1/4503598193770496, 1/9007196387540992, 1/18014392775081984, 1/36028785550163968, 1/72057571100327936, 1/144115142200655712, 1/288230284401311424, 1/576460568802622848, 1/115292113760524576, 1/230584227521049152, 1/461168455042098304, 1/922336910084196608, 1/184467382016839216, 1/368934764033678432, 1/737869528067356864, 1/147573905613471328, 1/295147811226942656, 1/590295622453885312, 1/1180591244907770624, 1/2361182489815541248, 1/4722364979631082496, 1/9444729959262164992, 1/1888945991852432992, 1/3777891983704865984, 1/7555783967409731968, 1/1511156793481947136, 1/3022313586963894272, 1/6044627173927788544, 1/12089254347855577088, 1/24178508695711154176, 1/48357017391422308352, 1/96714034782844616704, 1/19342807556569233408, 1/38685615113138466816, 1/77371230226276933632, 1/15474246045255387264, 1/30948492090510774528, 1/61896984181021549056, 1/123793968362043098112, 1/247587936724086196224, 1/495175873448172392448, 1/990351746896344784896, 1/1980703493792689569792, 1/3961406987585379139536, 1/7922813975170758278784, 1/15845627950341516557568, 1/31691257900683033115136, 1/63382515801366066230272, 1/126765037602732132460544, 1/253530075205464264921088, 1/507060150410928529842176, 1/1014120300821857059684352, 1/2028240601643714119368704, 1/405648120328742823873728, 1/811296240657485647747456, 1/1622592801314971291494912, 1/3245185602629942582989824, 1/6490371205259885165197968, 1/1298074241051977130395936, 1/2596148482103954260791872, 1/5192296964207908521583744, 1/10384593928415817043166784, 1/20769187856831634086333568, 1/41538375713663268172667136, 1/83076751427326536345334272, 1/16615350285465307269066944, 1/33230700570930614538133888, 1/66461401141861229076267776, 1/132922802283722458152535552, 1/265845604567444916305071104, 1/531691209134889832610142208, 1/1063382418697799665220284416, 1/2126764837395599330440568832, 1/4253529674791198660881137664, 1/850705934958399722177227328, 1/170141186991679544435445456, 1/340282373983359088870890912, 1/680564747966718177741777824, 1/136112949593343535543556448, 1/272225891983487071090871136896, 1/5444517839669741421801722273728, 1/1088903579333942843603444547456, 1/2177807158667885687206889094912, 1/4355614317335771374413778189824, 1/8711228634671542748827556379648, 1/17422457269340854977655117593968, 1/34844914538681709955311318793728, 1/69689829077363419910622637587456, 1/139379658154726839821245151751136, 1/278759316309453679642490303502272, 1/557518632618907393284980607004448, 1/1115037265237814785689761214008896, 1/223007453047562957137377522801779328, 1/44601490609512591446755045603554656, 1/892029812190251831493510092071091136, 1/17840596243805036629870201841822272, 1/35681192487610073259740403683644544, 1/71362384975220146119480807367289088, 1/14272476995044029239896164755777776, 1/285449539900880584797923295111555552, 1/5708990798017611695958465902231111104, 1/114179815960352333919173118044222208, 1/2283596319207046678383462360884444416, 1/456719263841409335676692481770888896, 1/9134385276828187113133338435417777728, 1/1826877055365637426266666870835555552, 1/3653754110731274852533333741671111104, 1/7307508221462549705066666483342222208, 1/146150164492508941101333331666444444416, 1/292300328985017822202666633288888896, 1/5846006579700356444053333665777777728, 1/11692013159400712881066667311555555552, 1/23384026318801425722133334623111111104, 1/46768052637602851444426669246222222208, 1/9353610527520570288853338492444444416, 1/1870722105504114577666667388488888896, 1/3741444211008228915333334769777777728, 1/7482888422016577830666675339555555552, 1/14965776440331555413333310679111111104, 1/29931552880663111086666213558222222208, 1/59863105761326222217333332716444444416, 1/1197262115226244443466665471328888896, 1/23945242304528888979333331092711111104, 1/4789048460905777786666621844444444416, 1/957809692181155555413333337368888896, 1/1915619243623111108888884716777777728, 1/3831238487246222221777777943555555552, 1/7662476974492444435555551887111111104, 1/15324953948984888871111113774222222208, 1/3064990789796977782222222748444444416, 1/61299815795939555644444454888888896, 1/12259963591918911110888888109777777728, 1/24519927183837822221777777219555555552, 1/4903985436767564444355555537111111104, 1/9807970873535128888911111174222222208, 1/19615941747070577782222222744444444416, 1/392318834941411555554444444588888896, 1/78463766988282311110888888117677777728, 1/1569275399765442222177777723555555552, 1/3138550799530884444355555571111111104, 1/6277101599061768888911111114222222208, 1/12554203981323577782222222744444444416, 1/251084079626471555554444444588888896, 1/50216815925294311110888888117677777728, 1/10043363851058862222177777723555555552, 1/200867277021771555554444444588888896, 1/40173455404354311110888888117677777728, 1/8034691080870862222177777723555555552, 1/160693816177417155555444444458888896, 1/321387632354834311110888888117677777728, 1/64277526470966862222177777723555555552, 1/128555052939337155555444444458888896, 1/257110105878674311110888888117677777728, 1/51422021175734862222177777723555555552, 1/102844042354689155555444444458888896, 1/205688084709378311110888888117677777728, 1/41137616941875662222177777723555555552, 1/822752338837513155555444444458888896, 1/1645504676775026311110888888117677777728, 1/329100935355005262222177777723555555552, 1/658201870710010525444444458888896, 1/1316403731420020511110888888117677777728, 1/263280746284004102222177777723555555552, 1/526561492568008204444444458888896, 1/10531229713760160888891111111767777728, 1/2106245942752032177777723555555552, 1/421249188550406435555551887111111104, 1/842498377100812888891111111377422222208, 1/16849967420162577782222222744444444416, 1/33699934840325155555444444458888896, 1/67399869680650311110888888117677777728, 1/13479973936130062222177777723555555552, 1/269599478722601254444444458888896, 1/539198957445202511110888888117677777728, 1/107839791490405102222177777723555555552, 1/215679582980810204444444458888896, 1/4313591659616200888891111111767777728, 1/862718331923240177777723555555552, 1/17254366394248035555551887111111104, 1/345087327884960711110888888117677777728, 1/69017465576992142222177777723555555552, 1/138034931139844284444444458888896, 1/2760698622796885688891111111767777728, 1/552139724559377137777723555555552, 1/1104279489117554755555444444458888896, 1/220855897823511110888888117677777728, 1/4417117956470222177777723555555552, 1/883423591294044435555551887111111104, 1/1766847822788088891111111377422222208, 1/3533695645576177782222222744444444416, 1/7067391291154355555444444458888896, 1/1413478582308711110888888117677777728, 1/282695716461742222177777723555555552, 1/56539143292348444435555551887111111104, 1/113078285744696888891111111377422222208, 1/22615657149339377782222222744444444416, 1/45231314298678755555444444458888896, 1/90462628597357511110888888117677777728, 1/18092525194715502222177777723555555552, 1/36185050389431004444444458888896, 1/7237010077886200888891111111767777728, 1/1447402015772400177777723555555552, 1/289480403154480035555551887111111104, 1/5789608063089600711110888888117677777728, 1/1157921612679200142222177777723555555552, 1/2315843225358400284444444458888896, 1/463168645071680056888891111111767777728, 1/9263372901433601137777723555555552, 1/18526748028672002755555444444458888896, 1/37053496057344005511110888888117677777728, 1/7410699211468801102222177777723555555552, 1/1482139842937600204444444458888896, 1/296427968587520040888891111111767777728, 1/59285593717504008177777723555555552, 1/11857118743008001635555551887111111104, 1/237142374860160032711110888888117677777728, 1/474284749720320064444444458888896, 1/948569499440640012888891111111767777728, 1/18971389888012800257777723555555552, 1/379427797760256005155555444444458888896, 1/75885559552051200102222177777723555555552, 1/151771119104102400204444444458888896, 1/30354223820820480040888891111111767777728, 1/6070844764164096008177777723555555552, 1/1214168952832819200163555555188711


PRICE SPECIAL RADIO CHASSIS OFFERS

HI-FI CONTINENTAL STEREOPHONIC RADIOGRAM CHASSIS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed autochanger. Complete £29.19.6. Chassis only 19½ gns. Special terms available of £7.10.0 deposit followed by 18 monthly payments of £1.9.1 (total H.P. of £33.13.6) + 15/- P. & P. Send £8.5.0 now.

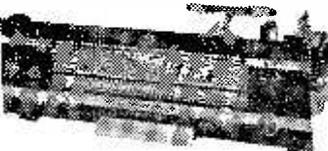IMPERIAL HI-FI STEREOPHONIC RADIOGRAM CHASSIS



The Imperial Stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons. Long-Medium-Short and VHF bands. Complete with two 10" loudspeakers plus a mono-stereo 4 speed automatic record changer. Complete £41.9.6. Chassis only 29½ gns. Special terms available of £10.7.6 deposit followed by 24 monthly payments of £1.11.8 (total H.P. of £48.7.6) + 17/6 P. & P. Send £11.5.0 now.

EMPRESS HI-FI AM/FM STEREOPHONIC CHASSIS




This most advanced radiogram chassis with automatic push button selection covers short, medium and long wavebands plus V.H.F. FM. Offered complete with 2 10 x 6 speakers 4 speed Stereo Mono autochanger only £35.19.6. Chassis only 25½ gns. Special terms available of £9 deposit followed by 24 monthly payments of £1.7.6. (total H.P. £42) + 15/- P. & P. Send £9.15.0 now.

All Lewis Radio equipment including valves are fully guaranteed for one year free of charge. Send your cheque or P.O. today while stocks last to Dept. P.96.

LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE LONDON, N.14. Telephone: PAL 3733/9666

4-STATION INTERCOM

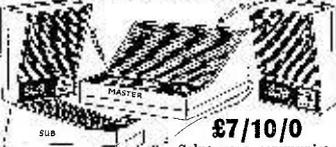

£7/10/0
Solve your communication problems with this new 4-Station Transistor Intercom (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 4/6.

INTERCOM/BABY ALARM

Usually £6.95 - Our Price ONLY

55/-

Modernise business or home with this new two-way Portable Transistor Intercom. Consisting of Master and Sub, in strong plastic cabinets, with chromium stands. Designed as a two-way instant communication system. Call/talk/listen from Master to Sub and Sub to Master. Operates on one 9V battery. Complete with 60ft. wire. Battery 2/6, P & P. 2/6.

Transistor TELEPHONE AMPLIFIER

Usually £6.95 - Our Price ONLY

55/-

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A status symbol? Yes, but very useful one. On/off switch. Volume Control. Operates on one 9V battery. P. & P. 2/6. Battery 2/6 extra. Full money refunded if not satisfied in 7 days.
WEST LONDON DIRECT SUPPLIES (PW/9)
169 KENSINGTON HIGH STREET, LONDON, W8.

2 METRES 4

The thrills of VHF Amateur Radio! Complete Kit, 70-150 Mc/s, costs only 42/6 (by post, UK, 8/3 extra) also now available, new transistor Short-Wave kit model TR2 10-180 metres, ideal for beginners to Ham radio via simplified 'Easy-Build' step-by-step instructions from 79/6. Write today enclosing a stamped addressed envelope for literature and full details. Overseas enthusiasts note we despatch to all parts of the world—local stamp OK for literature. "GLOBE-KING" (Regd.) precision standard products tried and trusted by Amateurs everywhere.

JOHNSONS (Radio)
St. Martins Gate, Worcester

AROUND THE WORLD

GO A.E.N. DIAL TELEGRAPH SEARCH WAGON

396

Pat. App. For

£2 POST FREE

On your own **TRANSISTOR PORTABLE!**

- ★ Boosts Pirate and distant stations.
- ★ No Plugs—No Connections! Just place Dewtron Wave Trap near radio.
- ★ Extends Battery life reduces 'fading'.
- ★ Use in car caravan without aerial. With PP3 battery (life several months).

D.E.W. LTD., Dept. P.W., Ringwood Road, FERNDOWN, Dorset.

Hark! Hark! —the DX is calling!



Special RX tuner
4 3/4" x 3 3/4" x 3 3/4"

JOYSTICK Variable Frequency ANTENNA SYSTEM

This revolutionary and pat. pend. aerial system possesses the unique property of an even response over all frequencies between 1.4-80 Mc/s. Every JOYSTICK Aerial System is supplied complete with feeder and an aerial matching unit. Just connect your RX—it is ready to go and gives an unprecedented 'hit' to signal strengths especially for 'air' and 'wave' dwellers—EVEN FROM UNDERGROUND! Naturally the advantages of using the 'JOYSTICK' 'up-in-the-clear' are even greater! 4,000 Joystick aeriels all over the world have already shown that this is the first major breakthrough for 20 years in the field of aeriels. The performance for such a compact unit (7.6in. assembled) is staggering. Even the sceptics have been convinced once they have understood the basic principles and have followed the simple 'tune-up' procedure given in the detailed instructions.

New Joystick Range
There is now a whole new range of Joystick Aerial Systems—made to match your QTH, your rig and your pocket! The SYSTEMS cover SWL, TX/RX, indoor and outdoor, mobile and even a new JOYMAST! Made only in the finest materials the SYSTEMS are reliable and permanent! Read all about them in our new brochure—

GUARANTEE: Partridge operate a rigid, 100% Money Back Guarantee if you're not completely satisfied!
Read testimonials from all over the world! "Four different receivers showed improved performance over a dipole" reports the U.S.A. C.Q. Magazine.
"Excellent results, Australia, Ceylon, South Africa at good strength although lately reception conditions have been poor." W. Cummings, Lossiemouth, Scotland.
WA5LEM—Henry Wilkins III of Houston Texas, writes: "The Joy-stick really surprised me! It really works like you said it would. . . I took all my dipoles down."
J.G. Rigden, Leighton Buzzard: "I cannot speak too highly of my internal Joystick which continues to give most excellent reception."
GBUGB—A. Wolfenden, Bristol: "I have used the Joystick for some months now and am more than pleased with its performance. . . extremely good reports on 180M and 80M."

READ ALL ABOUT IT!
This ticket will bring you the new brochures by return of post!

PARTRIDGE ELECTRONICS LTD.
Caister House, Prospect Road,
Broadstairs, Kent Tel. THANET 62535

NAME

ADDRESS

P.W.9

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3
Over 2500 Types in stock. Please
send s.a.e. (foolscap) for full Catalogue.

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling
 Minimum CHARGE 1/6. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANGHAM 8403
Open all day Saturday

First Quality Fully Guaranteed



ELECTRONIC VALVES

0A2	6/-	6KA6	7/-	6F4	30/-	7A6	7/-
0A3	11/-	6AL5	3/-	6F5	5/-	7A7	6/-
0B2	6/-	6AM6	2/-	6F6	8/-	7A8	8/-
0B3	6/-	6AM7	6/-	6F6G	13/-	7AF7	13/-
0C3	6/-	6AN4	15/-	6F8G	5/-	7AG7	7/-
0D3	5/-	6AN5	10/-	6F13	6/6	7BA	8/-
1A3	3/-	6AQ4	5/-	6F14	15/-	7B5	10/-
1A5GT	6/-	6AQ5	6/-	6F15	11/-	7B6	11/-
1A7GT	6/-	6AQ5A	7/6	6F17	6/-	7B7	7/-
1B3GT	7/-	6AQ6	8/-	6F19	6/8	7C4	4/8
1C5GT	6/-	6AR5	6/-	6F20	10/-	7C5	10/-
1D5	7/6	6AR6	6/-	6F23	11/6	7C6	7/-
1D6	8/-	6AR8	17/6	6F24	12/-	7C7	5/-
1E4GT	8/-	6AR5	5/-	6F25	12/-	7D3	8/-
1E6GT	7/-	6AS5	5/-	6F28	10/6	7D5	8/-
1F6GT	7/-	6ASG	20/-	6F32	7/-	7D8	7/-
1L4	2/6	6AT6	4/6	6G6G	2/6	7E5	5/-
1L6	17/6	6AUG	6/6	6H6	2/-	7E6	4/-
1N5GT	8/-	6AV6	6/-	6J4	9/-	7B7	10/-
1R4	6/-	6AW8A	14/-	6J5G	4/-	7H7	3/-
1R5	5/-	6BR4	18/-	6K7GT	5/-	7J7	14/-
1S4	5/-	6B5	5/-	6J6	3/8	7K7	10/-
1S5	4/6	6B8	7/-	6J7	9/-	7Q7	9/-
1T4	3/-	6BA5	5/-	6J7G	5/-	7R7	12/-
1T5GT	8/-	6BA7	15/-	6K6GT	8/6	7S7	18/-
1U4	5/-	6BB5	5/6	6K7G	8/-	7Y4	3/-
1U5	6/-	6BF6	6/-	6K7GT	5/-	7Z4	3/-
1V	5/-	6BGG	11/-	6K8	5/-	8W6	7/-
1V2	10/-	6BH6	7/6	6K23	7/6	8D2	3/8
1X2B	7/-	6BJ5	15/-	6K25	24/6	10C2	13/8
2A3	5/-	6B36	8/-	6L1	10/-	10D1	7/-
2C26A	5/-	6BK4	25/-	6L6G	6/-	10F1	14/-
2CWA	12/-	6BL7GT	6/-	6L6CC	6/-	10F3	8/-
2D2L	6/-	6BN6	6/-	6L7	7/-	10F8	8/-
2E2A	40/-	6BQ6	11/-	6L18	8/-	10F13	9/-
2G2L	12/-	6BQ7A	8/-	6LD20	6/-	10P13	12/6
2X2A	8/-	6BR7	12/-	6N7	3/-	10P14	12/6
3A4	4/-	6BR5	5/-	6P1	11/-	10Y	15/-
3A5	8/-	6B3	12/-	6P25	12/6	12A5	10/-
3ASGT	8/-	6BW6	9/6	6P28	6/-	12A6	8/-
3D6	4/-	6BW7	10/-	6Q7G	6/-	12A7	10/-
3E29	60/-	6BZ6	6/-	6R7	6/-	12A8	10/-
3Q4	6/6	6BZ7	11/-	6S7	7/-	12A9	5/-
3Q5GT	6/6	6C1	2/6	6S7	8/-	12AT6	5/-
3V4	6/-	6C4	9/-	6S7G	8/-	12AT7	6/-
4THA	10/-	6C6	4/-	6S7GT	4/6	12A7G	6/-
5R4GY	9/-	6C8G	7/-	6S7	7/-	12A7G	6/-
5T4	8/-	6C9	11/-	6S7	8/-	12A7G	6/-
5T4GB	6/6	6C9L	12/-	6S7GT	6/-	12A7G	6/-
5V4G	6/-	6C9L	12/-	6S7GT	6/-	12A7G	6/-
5X4G	8/-	6C6GA	6/-	6S7GT	4/6	12A7G	6/-
5Y3GT	5/-	6CG7	17/-	6S7	7/-	12A7G	6/-
5Y4G	6/-	6CG7	10/-	6S7	7/-	12A7G	6/-
5Z3	7/6	6CH6	6/-	6S7	7/-	12A7G	6/-
5Z4G	8/-	6CL6	12/-	6S7GT	10/-	12A7G	6/-
6/30L2	11/-	6CWA	12/-	6S7GT	10/-	12A7G	6/-
6A8	8/-	6CV5	10/-	6U4GT	10/6	12A7G	6/-
6AB4	6/6	6C7	11/-	6U8	7/6	12BA4	9/-
6AB7	4/-	6D1	2/-	6V6	9/-	12BA6	6/-
6AC7	4/-	6D3	7/6	6V6G	5/-	12BB6	5/6
6AD4	15/-	6D4	15/-	6V6GT	7/6	12BB7A	7/-
6AD7G	10/-	6D5	3/-	6W5C	7/-	12B7A10	10/-
6AFA	10/-	6D6	12/6	6X4	4/-	12C8	4/-
6AF6G	11/-	6DK6	6/-	6X5	7/-	12E1	20/-
6AFG5	2/6	6DQ	11/-	6XS5GT	6/-	12F5GT	8/-
6AG7	6/-	6EA8	11/-	6Y6G	10/-	12H6	3/-
6AL6	10/-	6E75	12/-	6Z4	5/-	12H6GT	3/-
6AK5	5/6	6F1	14/-	7A4	8/-	12J7GT	7/6

12K7GT	7/-	35B5	12/-	6150	32/-	E91H	8/-
12K8	8/-	35C5	6/6	6197	20/-	E92CC	7/-
12Q7G	4/-	35D5	12/-	6550	30/-	E180CC	8/-
12S47	7/-	35L6GT	7/-	7551	30/-	E180F	20/-
12S67	4/-	39W4	5/-	7586	22/6	E91E	62/6
12S7GT	10/-	3Z22	10/-	7825	22/6	EAT6	8/6
12S87	4/-	35Z4GT	8/6	8186	15/-	EABC80	7/6
12SH7	4/-	35Z5GT	6/-	9001	4/-	EAC91	4/-
12S7	4/-	43U	8/-	9002	5/6	EAF42	9/6
12S87	5/-	50A5	12/-	9003	9/-	EB41	5/-
12S87	10/-	50B5	7/-	9006	2/6	EB91	3/-
12S87	6/-	50C5	6/-	A2293	16/-	EB92	7/6
12S7	6/-	50D6G87	6/-	AC/HLLD	8/-	EB93	7/6
12Y4	2/6	50L6GT	6/-	ADD	10/-	EB94	6/6
13D8	5/-	50Y6GT10	6/-	AC/TH10	8/-	EB95	6/6
1487	18/-	75B1	5/6	ADD	10/-	EB96	6/6
18A03	5/-	75C1	12/-	ADD	10/-	EB97	6/6
20L1	14/-	80	6/-	AZ11	6/-	EB98	7/6
20P1	14/-	82	8/-	AZ12	9/-	EBF83	9/-
20P3	14/-	85A1	2/6	AZ4	7/-	EBF89	7/-
20P4	14/-	85A2	8/6	AZ4	7/-	EBL1	14/-
20P5	12/-	85A3	5/6	B65	4/6	EBL2	11/-
25A6G	5/-	90C1	12/-	C1C	12/-	EBL2	11/-
25C5	10/-	185BTA15	12/-	CBL31	17/-	EC86	12/-
25L6GT	8/-	220TA	7/-	CY31	7/-	EC88	12/-
25Y5	10/-	85	30/-	D41	5/-	EC82	4/-
25Z4G	8/-	807	9/-	DA30	10/-	EC84	10/-
25Z5	10/-	815	40/-	DA41	10/-	EC85	6/6
25Z6GT	11/-	822	20/-	DAC92	7/-	EC86	7/6
28D7	7/-	837	17/6	DAF91	4/6	EC87	6/6
30	4/-	866A	14/-	DAF92	6/-	EC88	6/6
30A5	7/-	872A	35/-	DAF96	7/-	EC89	6/6
30C1	7/6	884	15/-	DC70	12/-	EC90	6/6
30C15	11/-	954	8/-	DA1	10/-	EC91	4/-
30C17	11/-	955	3/-	DF91	3/-	EC92	8/-
30C18	11/-	956	3/-	DF92	2/6	EC93	12/-
30F5	11/-	957	5/-	DF96	7/6	EC94	12/-
30FL1	12/-	958	4/-	DH63	6/-	EC95	6/6
30FL2	12/-	959	8/-	DH76	5/6	ECF82	7/6
30FL3	12/-	961	7/-	DK40	11/-	ECF86	11/-
30FL4	12/-	2050	12/6	DK91	11/-	ECH21	5/-
30L1	6/6	4687	17/6	DK92	9/-	ECH22	15/-
30L15	12/6	5642	13/-	DK96	8/6	ECH35	11/-
30L17	14/-	5654	8/-	DL33	6/6	ECH42	9/6
30P12	10/-	5670	10/-	DL35	5/-	ECH51	6/6
30P16	7/6	5684	35/-	DL88	10/-	ECH83	7/6
30P18	7/-	5687	7/-	DM70	5/6	ECH84	10/-
30P19	14/-	5814A	10/-	DM160	10/-	ECL80	7/6
30P11	12/-	5840	10/-	DY80	7/-	ECL82	7/6
30P13	12/-	6060	5/-	DY86	8/-	ECL83	9/6
30P14	12/6	6080	25/-	DY87	9/-	ECL84	12/-
35A3	12/-	6136	9/-	EB8CC	14/-	ECL86	9/6
35A5	11/-	6146	27/6	E90CC	12/-	EP22	7/-

EF86	5/-	EZ22	6/-	PCL800	12/-	U201	6/6
EF87A	5/6	EZ35	5/6	PCL601	12/-	U281	13/-
EF89	5/6	EZ40	7/6	PEN45	7/-	U282	14/6
EF40	10/-	EZ41	8/-	PEN45D	5/6	U301	12/6
EF41	8/6	EZ40	6/6	PEN46	12/-	U40	7/-
EF42	8/-	EZ51	5/6	PEN46	6/6	U404	6/6
EF50	2/-	EZ90	4/-	PEN220A	8/-	U801	18/-
EF55	3/-	G551K	18/-			UABC80	5/6
EF62	6/-	GDB8W	10/-	PEN388	8/-	UAF42	9/-
EF60	6/6	G510H	40/-	PEN384	10/-	UB41	11/-
EF65	6/-	GZ175M	7/-	PEN384	7/-	UBC41	8/-
EF86	8/-			PEN463	10/-	UBC81	8/-
EF89	5/6	GU20	12/-	DD	10/6	UBC80	7/-
EF91	4/-	GU50	25/-	PF1200		UBF84	7/6
EF93	5/-	GZ30	8/-			UBF89	7/6
EF94	5/-	GZ32	10/-	PL86	10/-	UCB21	11/-
EF95	5/6	GZ34	10/-	PL85	16/6	UCB24	10/-
EP96	2/-	H4BC80	8/-	PL82	7/6	UCB28	10/-
EP98	12/6	HBC90	5/-	PL87	7/6	UCB28	10/-
EP188	3/-	HBC91	6/-	PL87	7/6	UCB28	10/-
EP184	3/-	HP93	6/-	PL87	7/6	UCB28	10/-
EP804	21/-	EAC91	4/-	PL302	14/-	UCF42	9/6
EPF60	10/-	HK90	5/-	PL301	15/-	UCF81	7/6
EH90	7/6	HL2	3/-	PL81	10/-	UCF81	7/6
EK3	10/-	HL2K	3/-	PP5/40010		UCF81	7/6
EK32	6/-	HL23	6/-	PY25	10/-	UF41	9/-
EK90	5/-	HL23DD	6/-	PY31	8/-	UF42	9/-
EL32	3/-	HL41	4/-	PY33	9/6	UF43	8/-
EL33	12/6	HL46	16/-	PY31	6/6	UF80	8/-
EL34	12/6	KT88	22/-	PY81	6/6	UF85	8/-
EL35	5/-	KT2A1	6/-	PY82	6/6	UF85	8/-
EL36	9/-	KT263	9/-	PY83	7/-	UF89	7/6
EL37	17/6	L78	6/-	PY88	8/6	UL41	9/-
EL38	17/6	N8	15/-	PY301	11/6	UL54	6/6
EL41	9/6	OC71	2/6	Y800	8/6	UMA	10/-
EL42	9/-	ORF12	12/-	PY301	8/6	UM4	7/6
EL50	6/-	ORF60	10/-	PZ30	10/-	UT8	8/-
EL51	9/6	PABC80	7/6	PQ25	5/-	UU7	8/-
EL52	8/-	PC86	12/-	QQV03-10		UU8	5/-
EL53	8/-	PC87	12/-			UU9	7/-
EL54	5/-	PC87	12/-	QQZ04-15		UU10	8/-
EL55	8/-	PC90	12/-			UY1N	9/-
EL56	8/-	PC84	6/6	QS105/45		UY21	9/-
EL90	6/-	PC85	8/-			UY41	6/6
EL91	2/6	PC88	12/-	QS150/158		UY82	9/6
EL95	6/-	PC89	12/6	QS1200/10		UY85	6/6
EL96	22/-	PC88	12/6	R1	8/-	VP23	3/6
EL97	10/-	PC89	12/6	R18	7/6	VP41	5/6
EMA	10/-	PC806	14/6	R18	12/6	VP10	1

The following blueprints are available from stock. Descriptive text is not available but the date of issue is shown for each blueprint. Send, preferably, a postal order to cover the cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

The Strand Amplifier } (Oct. 1962)	5/-	The Celeste 7-transistor Portable Radio } (June 1963)	5/-
The PW Signal Generator }		The Spinette Record Player }	
The Berkeley Loudspeaker Enclosure... } (Dec. 1962)	5/-	Transistor Radio Mains Unit } (June 1964)	5/-
The Luxembourg Tuner }		7 Mc/s Transceiver }	
The PW Troubadour } (June 1962)	7/6	The Citizen (December 1961) }	5/-
The PW Everest Tuner }		The PW 35-watt Guitar Amplifier (May 1964) }	5/-
The PW Britannic Two } (May 1962)	6/-	The Mini-amp (November 1961) }	5/-
The PW Mercury Six }		The PT Multimeter (October 1961) P.T. }	5/-
Beginner's Short Wave Two } (Nov. 1963)	5/-	The Beginner's Short Wave Superhet (Dec. 1964) }	5/-
S.W. Listener's Guide }		The Empire 7 Three-band Receiver (May 1965) }	5/-
Beginner's 10-watt Transmitter } (Dec. 1963)	5/-	Electronic Hawaiian Guitar (June 1965) }	5/-
Transmitting and Aerial Data }		Progressive S.W. Superhet (February 1966) }	5/-
P.W. "Sixteen" Multirange Meter } (Jan. 1964)	5/-		
Test Meter Applications Chart }			

★ PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL RADIO, TV OR AUDIO EQUIPMENT. ★

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) **We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

QUERY COUPON

This coupon is available until 7th September, 1966 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, SEPTEMBER 1966


MANY PRICE REDUCTIONS THIS MONTH



VALVE TRANSISTOR LIST
Send 3d. stamp for New Edition.
All types of Transistors, Scr's, Diodes, etc. Valves and Crystals.




(1)

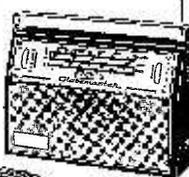

(2)



(3)

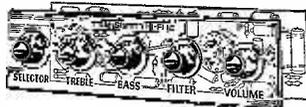


(4)



(5)




(6)

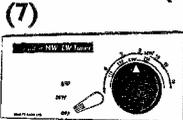

(7)



(8)

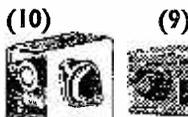


(9)




(10)




(11)

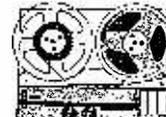

(12)

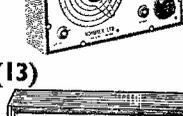


(13)

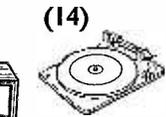

(14)



(15)

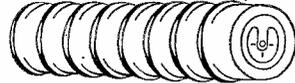

(13) HIGH FIDELITY EQUIPMENT.
Complete range in stock, all makes. Special parcel prices. Quotations by return to your requirements.

VISIT OUR NEW HI-FI ROOM

(9) TOURMASTER CAR RADIO

★ 7-Transistor Superhet with RF Stage.
★ Full tuning on Med. and Long waves.
★ 3 watts output. ★ 12 volts +VE earth.
★ Very sensitive and selective. ★ Push button wavechange. Brand new British made with maker's current guarantee. Complete with speaker, baffle and car fixing kit in cartons. Fully guaranteed.

PRICE **£9.90** P.P. 3/-

CATALOGUE

Latest 150-page edition. 5000 Stock Lines. The finest range of components and equipment available. FREE Discount Vouchers. PRICE 6/- (Post paid).



ASK FOR FREE 4-PAGE NEW STOCK LINES CATALOGUE AND 14-PAGE TRANSISTOR, DIODE, SCR LIST

(1) GLOBEMASTER MW/LW/SW PORTABLE

Full 3-waveband tuning, Pushbutton wavechange. Superhet printed circuit. Black-chromed cabinet 11 x 7½ x 3¼in. (SW 17-50 metres). Ear-Record sockets.
TOTAL COST £7.19.6 P.P. 3/6
TO BUILD
Large new purchase reduces price

(8) V.H.F. FM TUNER

87/105 Mc/s Transistor Superhet. Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3½ x 2½in.
TOTAL COST £6.19.6 P.P. 2/6
TO BUILD
(Cabinet Assembly 20/- extra)

10 AND 20 WATT MONO

(3) POWER AMPLIFIERS. 10 watts RMS output. 100mV input. 30 c/s to 20 kc/s ± 1dB. 6-Transistor Push-Pull. Panel size 4 x 2½ x 1in. H/S 4 x 4in.
TPA10/3 3-5 ohm speaker. £4.10.0, p.p. 2/6
TPA10/15 12-16 ohm speaker. £5.5.0, p.p. 2/6
(Mains unit for 1 or 2 amplifiers. 59/6, p.p. 2/6) (State 3 ohm or 15 ohm)
New Low Amplifier Prices

AND STEREO HI-FI UNITS

(4) PREAMPLIFIERS. 8 input selector Treble, bass, volume, filter controls. 1½mV to 300mV inputs. Battery operated or from Mains Unit. Output up to 150mV RMS.
For 10 or 25 Watt Amplifiers.
MP2 Mono 9½ x 2½ x 2in. £5.10.0, p.p. 2/6. (Brown and gold front panel 8/6.)
SP4 Mono/Stereo, 9 x 3½ x 1½in., £10.19.6, p.p. 3/6 (front panel plate 12/6.)

The Finest High Fidelity at Unbeatable Prices

● ALL UNITS BUILT AND TESTED

(12) BUILD A QUALITY TAPE RECORDER

Three speeds—3 watts.
Complete kits with new "363" decks. Supplied as preassembled sections. Complete with amplifiers, portable cabinets and Speaker—excellent quality. 1,200ft. tape and spool.
★ TWO TRACK **£26** P.P. 8/6
★ FOUR TRACK **£30** P.P. 8/6
Decks separately: 2-Track 10 gns. 4-track £13.10.0.

(10) 5 WATT AMPLIFIER

6-Transistor Push-pull, 3 ohms. 6mV into 1K. 12/18V supply. 2½ x 2 x 1½in. New Low Price.
BUILT AND TESTED 69/6 P.P. 2/-
(optional mains units 54/- p.p. 2/-) (1½ watt version 59/6 p.p. 1/6.)
New matching Preamplifier, 6 inputs, treble/bass/selector/volume controls. 6-10mV o/p. 9-18V supply. 79/6, p.p. 2/- for use with any Transistor Amplifier.

(6) REGENT-6 MW/LW POCKET RADIO

6-Transistor superhet. Geared tuning. Push-pull output. Moulded cabinet 5 x 3 x 1¼in. Phone socket. Printed circuit design.
TOTAL COST 69/6 P.P. 2/-
TO BUILD
Special new large purchase reduces price.

DEAC CHARGER
To charge 3.6 volt and 9.6 volt packs. Fully mains isolated. In moulded case.
Price 45/- P.P. 2/-

(11) NOMBREX SIGNAL GEN
150 kc/s to 350 Mc/s £9.10.0 P.P. 2/6
10 c/s-100 kc/s AUDIO GEN. £18.15.0 P.P. 2/6

(15) DEAC CELLS RECHARGEABLE BATTERIES

● 3.6 volt 500 mA/H. Size: 1½in. x 1½in. dia. 12/6. P.P. 1/6.
● 9.6 volt 225 mA/H. Size: 2-½in. x 1in. dia. 20/- P.P. 1/6.
BRAND NEW — Offered at a fraction of normal retail price.

25 WATT AMPLIFIER

New 8-Transistor design. Push-pull output for 7½ to 16 ohm speaker. 150mV input. 30 c/s to 20 kc/s ± 1dB. For use with valve or transistor preamplifiers as item (3) above. Size 2½ x 2½ x 6½in.
PRICE BUILT AND TESTED £7.19.6 P.P. 3/-
(Mains unit 79/6, p.p. 2/6)

NOW IN STOCK.—SCR'S, LDR'S., Thermistors, Transistors, Rectifiers, Diodes, also Relays, Motors—new range. Latest Supplement Lists on request.

CT52 OSCILLOSCOPE

Mains Portable Scope with 2½in. Mullard Tube. Full facilities for Transistor or Valve Equipment. For use up to 2 Mc/s. Full range of Controls and Inputs. Complete with Handbook and Circuit. Detailed Leaflet on Request. PRICE **£22.10.0** (Carriage 10/-)

(14) GARRARD DECKS

(P.P. 5/- any type)
1000 mono **£5.19.6** stereo **£6.6.0**
2000 mono **£6.6.0** stereo **£6.6.0**
*SP25 mono **£10.10.0** stereo **£10.19.6**
*SRP12 mono **£5.5.0** stereo **£5.15.0**
*AT6 mono **£8.19.6** stereo **£9.10.0**
*AT60 mono **£10.10.0** stereo **£10.19.6**
LAB80 **£25.0.0** 3000LM stereo **£8.8.0**
(*Deram cartridge add 60/- to mono price.)
All autochange (except SP25), complete with cartridge. Brand new. Send for complete list.

(2) MULTI-METERS

PT34 1kV **39/6** TPSS 20kV **£5.19.6**
M1 2kV **49/6** EP30k 30kV **£6.10.0**
TP10 2kV **75/-** EP50k 50kV **£8.15.0**
EP10k 10kV **79/6** 500 30kV **£8.17.6**
IT1-2 20kV **69/6** EP100k 100kV **£10.10.0**
EP20k 10kV **99/6**

See Catalogue for complete range of test equipment in stock.

(7) MW/LW QUALITY SUPERHET RADIO TUNER

Fully tunable superhet with excellent sensitivity and selectivity. Output up to 100mV peak. Complete with front panel, etc. 9 volts operated. For any Amplifier or Recorder.
TOTAL COST £12.17.6 P.P. 2/6
TO BUILD 79/6 P.P. 2/6

HENRY'S RADIO LTD.
303 EDGWARE ROAD, LONDON, W.2
PADdington 1008/9

Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday.

SPECIALISTS FOR TRANSISTORS AND ALL MINATURE COMPONENTS. MOST PARTS IN STOCK FOR ALL PUBLISHED CIRCUITS. LET US QUOTE FOR COMPONENTS AND ACCESSORIES FOR YOUR CIRCUIT. SEND A LIST FOR QUICK REPLY. ALL ADVERTISED AND CATALOGUED ITEMS ARE FULLY GUARANTEED UNLESS STATED.