

PRACTICAL WIRELESS

51. Neo
MARCH
1967


216





SOLDERING EQUIPMENT

FOR
THE
RADIO
CONSTRUCTOR

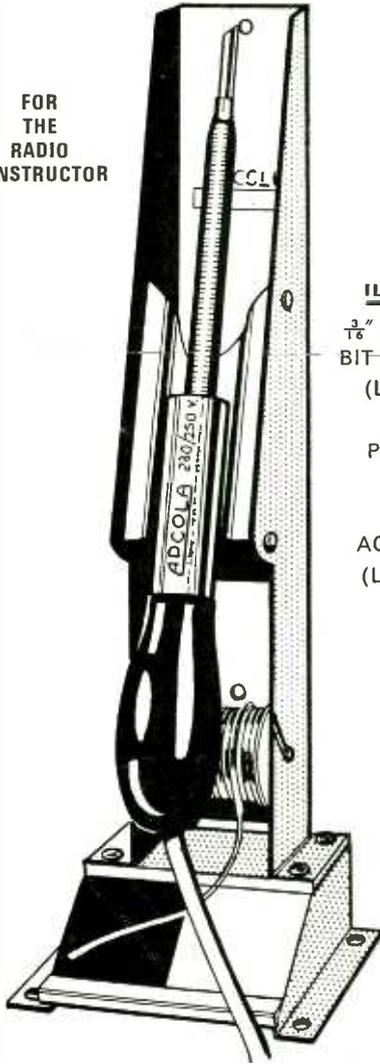

ILLUSTRATED
 $\frac{3}{16}$ " DETACHABLE
BIT-INSTRUMENT
(List No. 64)
IN
PROTECTIVE
SHIELD
WITH
ACCESSORIES
(List No. 700)


FOR CATALOGUES APPLY DIRECT

ADCOLA PRODUCTS LTD.
ADCOLA HOUSE
GAUDEN ROAD,
LONDON, S.W.4

Telephones:
MACaulay 0291/3

Telegrams: "SOLJOINT" LONDON SW4

NOMBREX INSTRUMENTATION

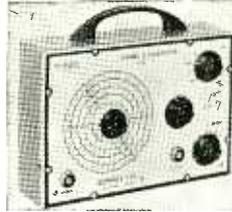

**WIDE RANGE
TRANSISTORISED
SIGNAL GENERATOR
MODEL 27**

- ★ Range 150Kc/s-350Mc/s
- ★ Direct Calibration
- ★ Mod. or Unmod. output
- ★ Accuracy better than 2%
£10.16.9.

ALSO AVAILABLE

Audio Generator 63	..	£17.1.9
Inductance Bridge 66	..	£18.6.9
Power Supply Unit 61	..	£6.14.6

WIDE RANGE TRANSISTORISED C.R. BRIDGE—Model 62

6 Ranges: 1Ω to 100M
1pF to 100μF

- ★ Visual null indicator
- ★ Power factor check
- ★ Electrolytic leakage test
- ★ Battery operated
£9. 6. 9.



All prices include battery, post and packing

S.A.E. for Leaflet	Trade & Export Enquiries Invited	Prompt Delivery
-----------------------	-------------------------------------	--------------------

NOMBREX LTD INSTRUMENTS DIVISION

Estuary House, Camperdown Ter., Exmouth, Devon

For quick, easy faultless soldering



Easy to use and economical. Containing 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy reduces wear of copper soldering iron bits.



SIZE 5 HANDY SOLDER DISPENSER

Contains 12 ft. of coil 18 s.w.g. Ersin Multicore Savbit Alloy. Quick and easy to use.
2/6 each



NEW SIZE 15
21 ft coil of 60/40 Alloy, 22 s.w.g. in a dispenser. Ideal for small components, transistors, diodes, etc.
3/- each



SIZE 12
Ideal for home constructors. Contains 102 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each (Also available in other sizes)




**BIB MODEL 3
WIRE STRIPPER
AND CUTTER**
Strips insulation without nicking the wire, cuts wire and splits plastic twin flex.
4/- each

From Electrical or Hardware shops. If unobtainable write to:
MULTICORE SOLDERS LTD., Hemel Hempstead, Herts. M29 B

Household Heating Supplies LTD brings central heating price down

you save £150 on D.I.Y installations!

**OIL —
GAS —
SOLID FUEL**

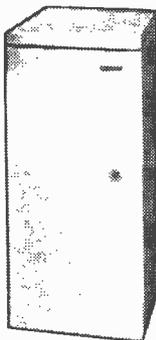

Powell Duffryn
G48 Gas Boiler

You can do better than buy Central Heating at "frozen" prices—you can save at least £150 by doing-it-yourself—and you get FREE advice before and during installation.

Free delivery to your home. NO DEPOSIT—5 YEARS TO PAY. Branches at Croydon, Wood Green, Tottenham, Bedford, Manchester and Leicester.



To: Household Heating Supplies Ltd.
7 Ilford Lane, Ilford, Essex ILF 5098J9

Please send further details.

Name
Address
Telephone

Make Your Ability **PAY**

UNLIMITED OPPORTUNITIES exist today for "getting on" . . . but only for the fully trained man. Let ICS's tuition develop *your* talents and help you to success.

STUDY IS EASY with ICS guidance. The courses are thorough. Printed manuals, fully illustrated, make study simple and progress sure.

YOUR ROAD TO SUCCESS can start from here—today. Complete this coupon and post it to us, for full particulars of the course which interests you. MODERATE FEES INCLUDE ALL BOOKS.

Take the right course now . .

ADVERTISING & ART
Copywriting, Cartooning
Layout and Typography
Commercial Illustrating
Oil & Water Colour

BUILDING & CIVIL ENG'NG
Architecture, Bricklaying
Building Construction
Builders Draughtsman
Builders Quantities
Interior Decoration
Quantity Surveying
Heating & Ventilation
Carpentry & Joinery

COMMERCE
Book-keeping
Accountancy & Costing
Business Training
Office Training
Purchasing, Storekeeping
Secretaryship
Shorthand & Typing
Computer Programming
Small Business Owners

DRAUGHTSMANSHIP
Architectural, Mechanical
Drawing Office Practice

ELECTRONICS
Computers
Electronic Technicians
Industrial Electronics

FARMING
Arable & Livestock
Pig & Poultry Keeping
Farm Management & Accounts

GENERAL EDUCATION
G.C.E. subjects at Ordinary &
Advanced Level
Good English
Foreign Languages

HORTICULTURE

Home Gardening
Park Gardening
Market Gardening

MANAGEMENT
Business Management
Hotel Management
Industrial Management
Office Management
Personnel Management
Public Relations (I.P.R.)
Transport Management
Works Management
Work Study
Foremanship

MECHANICAL & MOTOR ENG'NG
Engineering Maths.
Diesel Engines, Welding
Industrial Instrumentation
Work-shop Practice
Refrigeration
Motor Mechanics, etc.

POLICE
Entrance Examination
Promotion Examinations

PHOTOGRAPHY
Practical Photography

RADIO, TV & ELECTRICAL
Radio Construction (with Kits)
P.M.G. Certificates
Telecommunications
Electricians
Electrical Contractors
SELLING
Company Reps.
Sales Management
Marketing
WRITING FOR PROFIT
Television Scriptwriting
Short-story Writing
Free-lance Journalism
Technical Writing

INTENSIVE COACHING for all principal examinations—G.C.E., Secretaryship, Accountancy, Engineering, Work Study, Management, Radio, Transport and Surveying. Special courses for G.C.E. French, German Oral Tests.

Member of the Association of British Correspondence Colleges

Start today the I.C.S. way!

INTERNATIONAL CORRESPONDENCE SCHOOLS

(Dept. 172)

Intertext House, Parkgate Rd., London, S.W.11

Send FREE book on

Name

Address

Occupation

3.67

INTERNATIONAL CORRESPONDENCE SCHOOLS

LAFAYETTE HA-63 COMMUNICATION RECEIVER



Outstanding value. High-class 4 band receiver covering 550kc/s-31 Mc/s. Seven valves plus rectifier, RF stage, illuminated "S" meter, 1.5µV sensitivity. Electrical bandspread on 80/40/20/15 and 10 metre bands. Slide rule dial, aerial trimmer. B.F.O., ANL, Output for phones or speaker. 115/220/240V. A.C. Brand new, guaranteed, with manual. 24 Gns. Carr. 10/-.

LAFAYETTE KT-340 COMMUNICATION RECEIVER SEMI-KIT

Build this wonderful receiver and save pounds. Supplied semi completed, main components ready mounted. R.F. section already wired and aligned. Full and precise instructions supplied. Specifications—8 valves + rectifier, 4 bands covering 550kc/s-30 Mc/s. Incorporates 1 R.F. and 2 I.F. stages, 'Q' multiplier, B.F.O., A.N.L., 'S' meter, band spread aerial trimmer etc. Operation 115/230V. A.C. Price 25 Gns. Carr. 10/-.



HAM-1, 4 BAND COMMUNICATION RECEIVER

4 wavebands covering 535 kc/s to 30 Mc/s 5 valve superhet circuit. Incorporates 8 meter B.F.O., BANDSPREAD TUNING, BUILT-IN 4in. SPEAKER, FERRITE AERIAL AND EXTERNAL TELESCOPIC AERIAL. Operation 220/240 v. A.C. Supplied brand new with handbook. £16.10.0. Carr. 10/-.



GARRARD RECORD PLAYERS

SRP12 Player mono £44.0; 1000 changer mono or stereo 5 gns.; 2000 changer mono or stereo £66.0; A50 Changer mono or stereo £71.0; 3000 Changer stereo £77.0; A73 Mk II £8.19.6; 8P25 Player mono or stereo £9.19.6; A760 Changer mono or stereo £9.19.6; A70 less cartridge £19.19.0; LAB 80 Stereo £25.0.0; 401 Transcription 28 gns. Brand new and guaranteed. All plus post and packing 5/-.

MAIN LONDON AGENTS FOR CODAR EQUIPMENT

All items available as advertised.

SINCLAIR TRANSISTOR AMPLIFIERS

Z12 Amplifier 89/6; Z12 Power Pack 79/6; Stereo 25 Pre-Amplifier £8.19.6; Micro P.M. Radio Kits £5.19.6; Micro 6 Itadio Kit 59/6; Micro Amp. Kit 28/6 Post Paid.

2-WAY RADIOS

Super quality. Brand new and guaranteed.

- 3 transistor £6.15.0 pr.
- 4 transistor £7.19.6 pr.
- 5 transistor £8.4.0 pr.
- 6 transistor £9.19.6 pr.
- 6 transistor De Luxe £17.10.0 pr.
- 10 transistor £22.10.0 pr.
- 13 transistor 500MW £31.10.0 pr.
- 13 Trans. 1W £35.0.0 pr. Post extra. These cannot be operated in U.K.

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM.

Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection, 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.10.0 pair. P. & P. 3/6.

ZQM TRANSISTOR CHECKER

It has the null-test capacity for checking on A, B and C etc. Equally adaptable for checking diodes, etc. Spec.: A: 0.7-0.9997, B: 0.5-200, len; 0-50 microamps, 0.5 mA. Resistance for diode 200Ω-1 MEG. Supplied complete with instructions, battery and leads. £6.19.6. P. & P. 2/6.



P.C.R.1. RECEIVERS

Brand New Condition—Fully Tested and Checked before despatch. 3 Waveband with RF Stages—Wonderful value. 600-2000 metres 100-570 metres 5.6-18 Mc/s. with internal speaker £8.19.6. Carr. 10/6 with circuit. Plug in external power units. 230V A.C. 35/-, or 12V D.C. 19/6.

MAGNAVOX 363 TAPE DECKS

New 3-speed tape deck, supercedes old Collaro studio deck. 2-track £10.10.0. 4-track £13.10.0. Carr. Paid.

AMERICAN TAPE

First grade quality American tapes. Brand new. Discounts for quantities.

3in., 255ft. L.P. acetate	4/-
3 1/2in. 600ft. T.P. mylar	10/-
5in., 600ft. std. plastic	8/6
5in., 900ft. L.P. acetate	10/-
5in., 1,200ft. D.P. mylar	15/-
5in., 1,800ft. T.P. mylar	35/-
5 1/2in., 1,200ft. L.P. acetate	12/6
5 1/2in., 1,800ft. D.P. mylar	22/6
6in., 2,400ft. T.P. mylar	45/-
7in., 1,200ft. std. mylar	12/6
7in., 1,800ft. L.P. acetate	15/-
7in., 1,800ft. L.P. mylar	20/-
7in., 2,400ft. D.P. mylar	25/-
7in., 3,600ft. T.P. mylar	55/6

Postage 2/-, Over £3 post paid.

VARIABLE VOLTAGE TRANSFORMERS

Brand New—fully Shrouded. Input 230v. 50/60 cps. Output 0-260 Volts.

1 Amp	£4.10.0
2.5 Amp	£5.17.6
5 Amp	£9.0.0
8 Amp	£13.10.0
10 Amp	£17.0.0
12 Amp	£19.10.0
20 Amp	£32.10.0
2.5 Amp Portable—Metal Case with Meter.	
Fuses, etc. £9.17.6.	



SILICON RECTIFIERS

200v. PIV, 200mA	2/6
200v. PIV, 6 amp	5/6
400v. PIV, 3 amp (SCR)	10/-
400v. PIV, 3 amp	7/6
1,000v. PIV, 650mA	6/6
800v. PIV, 500mA	5/6
800v. PIV, 5 amp	7/6
400v. PIV, 500mA	3/6
70v. PIV, 1 amp	3/6
150v. PIV, 165mA	1/-
150v. PIV, 25 amp	19/9
700v. PIV, 100 amp	49/6

Discounts for quantities. Post extra

PORTABLE OSCILLOSCOPE CT-52

A compact (9in. x 8in. x 16 1/2in.) general purpose 'scope T/B 10c/s-40 kc/s. Band width 1 Mc/s. Mullard DG 7/5 3 1/2in. CRT. For operation on 200/250V. A.C. Supplied complete with metal transit case, strap, test leads, and visor hood. Brand new, £22.10.0. Carr. 10/- Supplied complete with instructions.



F.M. WIRELESS MICROPHONE

94-104 Mc/s. Transistorised. Operates from 9v. battery. Complete with additional secret tie clip microphone. List £12.10.0. ONLY £7.10.0. P. & P. 2/6. These cannot be operated in U.K.



ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPE

Time base 2 c/s-750 kc/s. Calibrators at 100 kc/s and 1 Mc/s. Separate Y1 and Y2 amplifiers up to 5.5 Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. £22.10.0. Carriage 20/-.

TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-280Mc/s on 6 bands. Directly calibrated. Variable B.F. attenuator. Operation 200/240v. A.C. Brand new with instructions. £12.10.0. P. & P. 7/6. S.A.E. for details.



LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 PF-2,000 MFD, 2 ohms-200 Megohms. Also checks impedance, turns ratio insulation 200-250 v. A.C. Brand New £15. Carr. 7/6.

TE-900 20,000Ω/VOLT GIANT MULTIMETER

6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000V A.C. 1/25/12.5/10/50/250/1,000/5,000 V. D.C. 0/50µA/110/100/500mA/10 amp D.C. 0.2K/200K 20 Meg. Ohm. £12.19.6 P.P. 5/-.



TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20 cps to 200 kc/s. on 4 bands. Square: 20 cps to 30 kc/s. Output impedance 5,000 ohms. 200/250v. A.C. operation. Supplied Brand New and Guaranteed with instruction manual and leads. £15 Carr. 7/6.



TRANSISTORISED F.M. TUNER

6 transistor, high quality, size only 6 x 4 x 2 1/2in. 3 I.F. stages, double tuned discriminator. Ample output to feed most amplifiers. Operates on 9v. battery. Covers 88-108Mc/s. Ready built, ready to use. Fantastic value for money. £6.19.6. P. & P. 2/6.



CLEAR PLASTIC PANEL METERS

First grade quality, Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type MR, 38P, 1 1/2/32in.

100-0-100µA	27/6	200mA	22/6	100V D.C.	22/6
500-0-500µA	22/6	300mA	22/6	150V D.C.	22/6
1-0-1mA	22/6	500mA	22/6	300V D.C.	22/6
1mA	22/6	750mA	22/6	500V D.C.	22/6
2mA	22/6	1A D.C.	22/6	750V D.C.	22/6
5mA	22/6	2A D.C.	22/6	15V A.C.	22/6
10mA	22/6	5A D.C.	22/6	50V A.C.	22/6
20mA	22/6	3V D.C.	22/6	150V A.C.	22/6
100µA	29/6	50mA	22/6	10V D.C.	22/6
200µA	27/6	100mA	22/6	20V D.C.	22/6
500µA	25/6	150mA	22/6	50V D.C.	22/6
50-60µA	28/6			50 Meter Ima	22/6

POST EXTRA. Larger sizes available—send for lists.

TE-51 NEW 20,000Ω/VOLT MULTIMETER

0 / 6 / 60 / 120 / 1,200V. A.C.
0 / 3 / 30 / 60 / 300 / 600/3,000V. D.C.
0 / 60µA / 12 / 300 MA. D.C.
0 / 60K / 6 Meg.Ω
35/-, P. & P. 2/6.



MODEL TE-12

20,000 O.P.V. 0/06/6/30/120/600/1,200/3,000/6,000V. D.C. 0/6/30/120/600/1,200 v. A.C. 0/60µA/6/60/600 mA. 0/6K/600K/6 Meg./60 Meg.Ω. P.F. -2 MFD. £5.19.6. P. & P. 3/6.



MODEL 500. 30,000

opv. 0/5/12.5/10/25/100/250/500/1,000V. D.C. 0/2.5/10/25/100/250/500/1,000V. A.C. 0/50µA/5/50/500mA. 12 amp. D.C. 0/10K/6 Meg.Ω/60 Meg.Ω. £8.17.6. Post paid.



CALLERS WELCOME!

Open 9 a.m. to 6 p.m. every day Monday to Saturday. Trade supplied.

G.W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

R.S.T. VALVE MAIL ORDER CO.

144-146 WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.—5.45 p.m.
No Early Closing
Open Daily to Callers
Tel. STR 0199, 1649

All valves
brand new
and boxed

0A2 5/3	6BE6 4/6	6K6GT 5/-	7R7 19/6	19AQ5 7/6	50L6GT 6/-	DF96 6/-	ECF80 7/-	EM81 7/-	PC189 10/-	S130 25/-	UM80 7/-
OC3 5/-	6BH6 7/-	6K7M 5/-	787 17/9	20D1 10/-	75 5/-	DH77 3/6	ECF82 7/-	EM84 7/-	PCF80 6/6	SP4 9/6	UU6 13/6
1A7 7/9	6BJ6 7/-	6K7G 1/3	7Y4 7/6	20F2 11/-	78 4/6	DK32 7/6	ECB21 19/-	ESU16027/6	PCF82 6/-	SP41 1/6	UU7 13/6
1D5 6/-	6BQ7A 7/-	6K7GT 4/6	9BW6 8/-	20L1 15/-	80 5/-	DK91 5/-	ECB35 11/-	EY51 7/-	PCF84 8/-	SP61 1/6	UU9 8/-
1E8 7/6	6BR7 10/6	6K8M 8/6	10C1 9/-	20P4 17/-	35A2 8/6	DK92 8/-	ECB42 9/-	EY86 6/6	PCF86 8/-	SU25 19/6	UY21 7/6
1LD5 5/-	6BR8 7/6	6K8G 3/6	10C2 12/-	20P5 16/-	150B2 14/6	DK96 6/6	ECB81 5/3	EZ35 4/9	PCF801 8/9	SU2150 12/6	UY41 6/3
1N6GT 8/-	6BS7 16/9	6K8GT 8/3	10F1 14/-	25A6 6/6	150C4 12/6	DL66 15/-	ECB83 7/-	EZ40 7/-	PCF802 9/9	T41 9/-	UY85 5/6
1R5 5/-	6BW6 7/6	6K26 20/-	10F3 12/-	25L6GT 4/6	801 5/-	DL92 4/9	ECL80 6/6	EZ41 8/-	PCF808 10/9	TDD4 7/-	VMP4 17/-
1B4 5/-	6BW7 8/6	6L1 9/6	10F9 9/9	3D5Y 6/-	807 7/9	DL93 3/6	ECL82 6/6	EZ80 5/-	PCF806 12/-	U10 7/-	VP4B 27/6
1B5 3/3	6C4 3/-	6L6G 4/6	10F18 9/9	25Z4 6/3	813A 80/-	ECL83 8/-	ECL83 8/-	EZ81 5/-	PCF808 11/6	U14 7/-	VR106/30
1T4 3/6	6C5G 4/-	6L18 7/6	10L1 10/-	25Z5 7/-	866 10/-	ECL86 8/-	EZ82 8/-	GZ30 8/6	PCL82 7/-	U19 30/-	5/-
3A4 3/6	6C6 3/9	6Q7G 5/6	10L11 10/-	25Z6 11/-	954 4/-	DL96 6/-	EF9 20/-	GZ32 9/6	PCL83 8/6	U25 10/6	VR150/30
3Q4 6/6	6C8G 6/-	6Q7GT 9/-	10P13 14/-	28D7 5/-	1625 5/-	DM70 5/-	EF36 3/-	GZ34 10/-	PCL84 7/6	U78 10/6	5/-
3Q5 6/6	6C9G 22/6	6A7 7/-	11E3 27/6	30C1 6/6	4022AR 15/-	DY86 6/6	EF37A 7/6	KT36 22/6	PCL85 8/6	U78 3/6	VT25 29/-
3B4 4/9	6CH6 5/9	68C7 6/6	12AT6 4/6	30C15 11/6	3783 10/6	DY87 7/9	EF39 6/-	KT81 17/6	PCL86 8/6	U91 11/6	VT31 58/-
3V4 3/6	6C12 12/-	68G7 4/-	12AT7 3/6	30C17 12/-	7193 1/6	EB80C 12/-	EF41 8/6	KT66 20/-	PEN44 20/-	U251 12/6	VU11 6/-
5R4G 3/9	6C14 12/-	68H7 2/6	12AT7 3/6	30F5 13/-	7475 2/6	EAB5 2/-	EF50 2/-	KT81 10/-	PENB4 20/-	U301 13/-	VU120 12/6
5U4G 4/-	6D6 2/6	68J7 5/-	12A7 4/9	30F11 13/6	ATP4 1/9	EABC90 5/9	EF80 5/-	KT88 27/6	PEN45 6/-	U403 6/6	VU508 30/-
5V4G 3/-	6E5 5/9	68K7GT 4/9	12AX7 5/9	30L15 12/6	ATP5 7/-	EAF42 7/6	EF85 6/6	KTW61 4/3	PEN46 2/9	U401 18/6	W81M 5/6
6Y3GT 5/-	6F5G 5/-	68L7GT 4/9	12BA6 6/-	30L17 12/-	ATP7 4/6	EB41 4/6	EF86 6/3	KTZ41 8/-	PL36 9/-	UABC80 5/6	X79 41/-
6Z4G 8/-	6F6G 4/-	68N7GT 4/-	12BE6 5/3	30P12 10/-	AU2 30/-	EB41 3/6	EF88 5/6	M14 17/6	PL81 6/6	UAF42 8/9	XH1-5 5/-
6/30L2 11/3	6F8G 4/-	68Q7 6/-	12C8GT 7/6	30P19 14/-	AU5 6/6	EB43 3/6	EF91 3/6	M16 12/6	PL82 6/6	UC41 8/-	XPI-5 5/-
6A7 15/-	6F8G 4/6	6U4GT 10/-	12C8GT 7/6	30P1L 14/-	AZ1 8/9	EBC41 8/3	EF92 2/6	MSF4 17/6	PL83 6/-	UCB81 7/6	XSG1-510/-
6A8G 12/6	6F11 12/6	6U5G 7/6	12E1 19/6	30P1L3 14/-	AZ31 7/9	EBC90 3/9	EF98 9/-	MU14 4/-	PL84 6/6	UBF80 5/9	Y83 7/6
6AC7 3/-	6F13 5/-	6V6M 8/-	12J6GT 2/8	30P1L4 14/-	CHL31 15/-	EBF80 6/6	EF183 6/6	MX40 12/6	PL500 14/6	UBF89 6/6	Tubes
6AK5 4/6	6F14 12/6	6V8G 3/6	12J7GT 7/3	35A5 17/-	OCB35 21/-	EBF83 7/-	EF184 6/6	N37 10/-	PX4 18/6	UCB84 8/6	3EG1 40/-
6AL5 5/-	6F23 11/-	6V8GT 7/-	12K6GT 3/-	35L3 5/9	CL33 12/6	EBF89 6/6	EL2 3/-	N78 15/-	P33 3/6	UCB85 6/6	3FP7 12/6
6AM5 2/6	6G6 2/6	6X4 3/6	12K8GT 8/-	35W4 4/6	CV31 10/-	EBL1 17/6	EL33 17/6	N108 15/-	PY81 6/-	UCB80 8/6	SCP1 30/-
6AM6 3/3	6H6 1/3	6X6G 4/9	12Q7GT 3/-	35Z3 10/-	DAC32 7/6	EBL21 10/6	EL34 9/6	NGT1 3/-	PY82 5/6	UCH42 8/6	AC1526 40/-
6AQ5 5/6	6J5M 6/6	6X5GT 7/6	128A7 6/6	35Z4GT 3/9	DAF91 3/3	EBL21 20/6	EL41 8/6	NGT7 25/-	PY83 6/-	UCH81 6/3	AC113
6AS7G 19/6	6J6G 2/6	7B6 11/-	12S07 3/6	35Z5 5/6	DAF96 6/-	ECC31 3/9	EL42 7/6	OZ4 4/-	PY801 7/-	UCB82 7/6	23 18.0
6AT6 3/9	6J6GT 4/8	7B7 7/-	12S7 2/6	35Z6 5/6	DK90 8/-	ECC32 4/9	EL44 4/6	PC86 9/-	PY801 7/-	UCB83 8/9	VCB97 35/-
6AU6 6/-	6J6 3/-	7C5 10/-	12S7 2/6	42 4/6	DF33 8/-	ECC83 5/9	EL90 5/6	PC88 9/-	R2 4/-	UCF1 8/-	VCR517B
6B8G 2/-	6J7M 8/6	7C6 6/-	12K8K7 2/9	50B5 6/6	DF70 5/-	ECC84 5/6	EL95 6/-	PC97 7/6	R19 7/-	UCF89 6/9	30/-
6B4G 10/-	6J7G 4/9	7D5 8/-	12R87 5/6	50C5 5/9	DF91 2/6	ECC85 5/6	ELL80 20/-	PC94 5/6	RG5/500	UL41 8/9	VCR517C
6BA6 4/6	6J7GT 8/6	7H7 5/-	14H7 9/-	50C8G32/6	DF92 2/6	ECC88 7/-	EM80 7/-	PC89 10/-	59/	UL84 6/-	30/-

SPECIAL 24 HOUR SERVICE

OBsolete TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Postage 6d. per Valve C.W.O. No C.O.D.

Send S.A.E. for list

Manufacturers and Export Inquiries Welcome

Special 24 Hour
Express Mail
Order Service

SETS OF VALVES

DAF96, DF96, DK96, DL96 Set of 4, 24/6

BRAND NEW TRANSISTORS

AC197 8/-	OC25 11/-	OC71 4/6	OC81 4/-	OC82D 6/-
AF114 7/-	OC28 18/-	OC71 6/-	OC81m 6/-	OC83 6/-
AF115 7/-	OC35 9/6	OC75 6/-	OC81 12/6	OC170 7/6
AF116 7/-	OC44 3/6	OC76 6/-	OC81D 4/-	OC171 7/-
AF117 5/-	OC45 3/6	OC77 8/-	OC82 6/-	OC200 8/-

PLEASE NOTE OUR NEW ADDRESS

This Martin Recordakit


is designed specially for the MAGNAVOX 363

3 WATTS OUTPUT

3 SPEEDS : 7" REELS
OUTLET FOR HI-FI AMP

SOLDERING NOT
NECESSARY

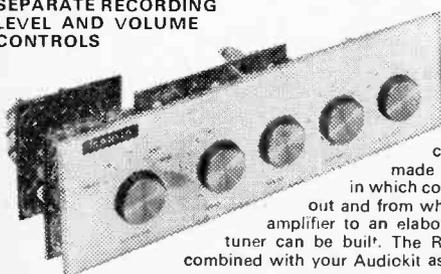SEPARATE RECORDING
LEVEL AND VOLUME
CONTROLS



You need a MARTIN RECORDAKIT to do full justice to this excellent deck. With it, you will have a 2 or 4 track instrument of outstanding quality and dependability. MARTIN RECORDAKITS consist of basic Martin units assembled and tested, making it necessary for you simply to fit and connect in accordance with the detailed instructions book supplied. When built, your 3 speed Martin Recorder appears as shown here. The lid is detachable. Case with speaker, and deck also available. Details on request. MARTIN RECORDAKITS have long been famous for their high performance standards, quality of materials, simplicity and dependability. The latest is the best yet.

Martin Audiokits for Hi-Fi

The uniquely reliable kits with "Add-on-ability"

No other system allows you to enlarge your installation stage by stage as Audiokits do. They comprise a wide range of very well made prefabricated transistorised units in which connections are standardised throughout and from which anything from a simple straight amplifier to an elaborate hi-fi stereo amplifier with FM tuner can be built. The Recordakit described above can be combined with your Audiokit assembly if you wish.

- 5-stage input Selector £2.76
- Pre-amp/vol. control £1.17.6
- Pre-amp/tone controls £3.2.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0
- FM Tuner £12.17.6

THE UNITS THAT ENABLE YOU TO BUILD BY STAGES FROM PRE-AMP TO A HI-FI STEREO/FM ASSEMBLY

Martin Recordakits and Audiokits are obtainable from good stockists everywhere. In cases of difficulty please write direct. Trade enquiries invited.

MARTIN ELECTRONICS LTD

154/155 HIGH ST., BRENTFORD, M'SEX Phone: ISLeworth 1161/2

MARTIN ELECTRONICS LTD.
154 High St., Brentford, Middlesex

Full details of Recordakits or Audiokits please

NAME

ADDRESS


(Block letters) P.W.37



KIT M4 less case and deck (four track) but inc. valves, screws, wire, track switching etc. £15.19.6

KIT M2 less case and deck (two track) but incl. valves, wire, screws, etc. £14.19.6

CODAR — QUALITY

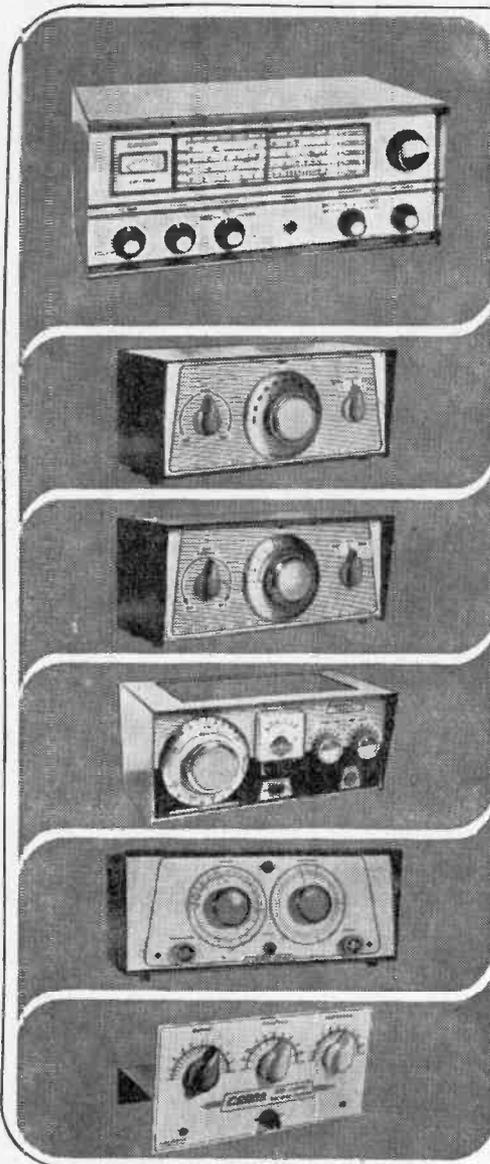

ANOTHER CODAR TRIUMPH!

THE CR.70A COMMUNICATION RECEIVER.

This completely new receiver sets a new high standard for performance and finish unequalled at the price, and is a worthy addition to the outstanding range of CODAR quality communication equipment. Frequency range: 560 Kc/s-30 Mc/s (540-10 metres) in four ranges; 560 Kc/s-1.5 Mc/s; 1.5 Mc/s-4.2 Mc/s; 4.2 Mc/s-11.5 Mc/s; 11.5 Mc/s-30 Mc/s. Slide rule scales for each band calibrated in frequencies plus an additional logging scale in degrees. Two speed vernier tuning control with reverse slow tune action. Unique aerial input stage exclusive to the CR.70A employing High 'Q' Air-spaced CODAR-COIL inductor giving extremely high gain with low noise level. Panel aerial trimmer for peaking weak signals. Double tuned I.F. Iron cored transformers, 470 Kc/s with EF183 frame grid valve for maximum gain and selectivity; 5 valves (including two twin triodes) giving 7 valve line-up. Separate B.F.O. stage for CW and SSB reception. Calibrated signal strength 'S' meter, illuminated. Automatic Volume control. Panel phone jack for 'private' listening. 2-3 ohm output for external speaker. (Matching unit optional extra.) Superb finishing, metal cabinet in the new Organazol Satin lustre finish. Size: 13" x 5 1/2" x 7 1/2". For A.C. 200/250v Ready built. Not a Kit at the fantastic low price of £19.10.0. Carr. 7/6.

CODAR R.F. PRE-SELECTOR MODEL P.R.30. Considerably improves the performance of any superhet receiver over 1.5-30 Mc/s. Uses EF183 Frame Grid Valve, and provides up to 20dB gain plus substantial image rejection, improved signal noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12mA H.T. 6.3 volts. 3 amp L.T. Size 8 1/2 x 5 x 4 in. Ready built, complete with cables, plugs and instructions, £5.10.0. Carr. 4/6. **MODEL P.R.30X.** Self powered model for 200-250v. A.C. Also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £7.4.0. Carr. 4/6.

CODAR "Q" MULTIPLIER MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW, or SSB, BFO. Size 8 1/2 x 5 x 4 in. Power requirements 180-250v. H.T. at 5mA 6.3v. 3 amp L.T. Ready built complete with cables, plugs and instructions, £6.15.0. Carr. 4/6. **MODEL R.Q.10X.** Self powered version for 200-250v. A.C. and also provides 25mA at 200v. H.T. and 6.3v. 1 amp. L.T. for other accessories £8.8.0. Carriage 4/6.

CODAR A.T.5. 12 WATT 2 BAND TRANSMITTER. The newest most compact transmitter for fixed or mobile use on 160-80 metres. "The tiny TX with the BIG voice", size only 8 1/2 x 5 x 4 in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR COIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate-Screen modulator. AM/CW switch and Panel key jack. Plug change over for 6 or 12 volts heater supply. Ready built £18.10.0. Carr. 4/6. **A.T.5 POWER SUPPLY UNITS.** For 200-250v. A.C. and 12v. Solid state for Mobile use, complete with all Transmit/Receive changeover switching available.

CODAR-KIT CR.45K MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandspread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line-up: ECC81, EL84, E280. Size 12 x 5 1/2 x 7 in. **CODAR-KIT CR.45K** complete with valves, 3 coils (10-28, 28-75, 80-175 metres) and 11 page instruction manual, £9.10.0. Carr. 6/- . Extra coils 5/- each. Instruction manual only 4/- (credited on order). (Can also be supplied ready built—price on request).

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 39/6. Carr. 3/- . Extra coils 5/- each. Instruction manual only 2/- (credited on order). Electrical bandspread available. Provision to add 2 transistor amplifier.

Send 6d. in stamps for illustrated leaflets of the Codar range

• H.P. terms available

• World-Wide Mail Order Service

CRC

CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE


SOUTHWICK, SUSSEX. Tel. 3149

G3IRE

G3HGQ

Canada: Codar Radio of Canada, Tweed, Ontario

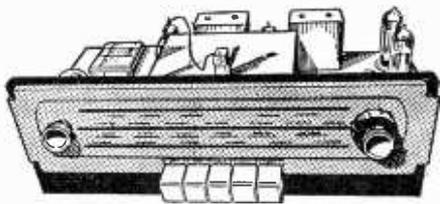BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £15.15.0 (Carriage Paid)



Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/2 x 4 in. in 2 colours; predominantly cream. 200-250v. A.C. only. Pick-up Ext. Speaker. Ae., E. and Dipole Sockets. Five push-buttons—LW, MW, SW, FM and Gram. Aligned and tested. O.P. Transformer Tone control 1000-1900M; 200-550M; 88-98 Mc/a. 6-17 Mc/a. EZ80 rect.; ECH81 EP89 EABCS0 EL84, ECC85, 3-ohm speaker required. 9 x 6 in. ELLIPTICAL SPEAKER, 20/- to purchasers of this chassis. **TERMS:** (Chassis), £5.5.0 down and 5 monthly payments of £2.5.0. Total H.P. price, £16.10.0. Cheap Room Dipole for V.H.F., 1/6. Feeder 6d. per yard. Circuit diagram 2/6. Carriage to N. Ireland, 20/- extra.

NEW 6 PUSH-BUTTON STEREOGRAM CHASSIS. M.W.; S.W.1; S.W.2; V.H.F.; Gram; Stereo Gram. Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6 1/2 in. high. Dial cream and red. 15 x 3 in. 190-550M; 18-51M; 60-187M; VHP 96-100 Mc/a. Valves: ECC85, ECH81, EP89, 2 x ECL86, EM84 and Rect. Price £18.19.0, carr. paid or £8.13.0 deposit and 5 monthly payments of 50/6. Total H.P. price £20.15.6. Cream moulded escutcheon included.

TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS — 2 or 4 TRACK (4 TRACK 25/- EXTRA)

Chassis 12 1/2 x 5 1/2 x 4 1/2 in. high. Plastic front panel "gold" finish — 12 1/2 x 4 1/2 in. 200-250 A.C. Record/Playback amp. switch; Off/On-Tone; Vol/Mic; Vol/Gram; Mic. Input; Gram. Input; Monitor; Speaker Sockets. Valves 6BR7, 12AX7, EM84; EL84; 6X4 Separate power pack. Complete amp. and power pack, £10.17.6. (6/- P. & F.). Rexine covered cabinet (tan) 15 1/2 x 17 x 9 1/2 in. high with sloping front for amp; complete with two tweeter speakers, and special adapting brackets for Magnavox Deck—85/- (8/- carr.) 3 speed Magnavox 2 track tape deck £10.17.6; 4-track £12.16.0. Complete Recorders (with speed compensation) 2-track £29; 4-track £32 (carr. 25/-). Worth £10 more on normal retail prices.

The
SUPER 6
LONG & MEDIUM WAVE TRANSISTOR RADIO



A quality radio available as a kit or ready-built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £21.12.0 commercial model.

★ All new parts. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit ★ Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet 11 x 7 1/2 x 3 1/2 in. ★ Vinyl covered in various colours. ★ 6 x 4 in. speaker giving good bass and treble response. ★ Full instruction booklet, 2/-. Free with kit. ★ I.F. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately. Write for list, S.A.E. **COMPLETE KIT ONLY £4.0.0** P. & P. 5/- **OR FULLY BUILT £8.7.6.** Tax and Carr. Paid.

TRANSISTORS AND DIODES

OC26, 7/6; OC44 3/6; OC45 3/6; OC71, 3/-; OC72, 4/-; OC81, 3/6; OC81D, 3/6; OC82, 6/-; OC83, 3/6; OC169, 8/-; OC170, 7/-; OC171, 8/-; OC172, 8/6; AC127, 7/6; AF115, 8/6; AF116, 8/-; AF117, 5/-; AF118, 7/6; AF119, 7/6; WG4B, 9d.; OA81, 2/6; OA79, 2/6; OA85, 2/6; BY100, 4/-.

STEREO-AMPLIFIER 2 x 4 WATT

Valves ECC83, 2 x EL84, on printed circuit approx. 4 x 4 in. Neg. feed back. Controls (vol. or tone) on separate panel, 6 1/2 x 2 in. Separate power pack with rect. double wound mains trans., connection socket, etc. Supplied fully wired and tested with two O.P. transformers for 3-ohm speakers, only £4.15.0 (7/6 P. & F.). Two speakers, 8 in. 3-ohm for 20/- each, post paid, if ordered with above Amp.

BATTERY ELIMINTOR. 5 1/2 x 4 1/2 x 2 1/2 in. for 90 v. H.T. at 20mA and 1.5 v. at up to 250mA. Fully built, 55/- carriage paid.


GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses) **CLOSED WEDNESDAY AFTERNOON** Aldershot 22240
CATALOGUE 6d.
Bulk enquiries invited for Export.

AMATEUR RADIO
CHAS. H. YOUNG LTD.

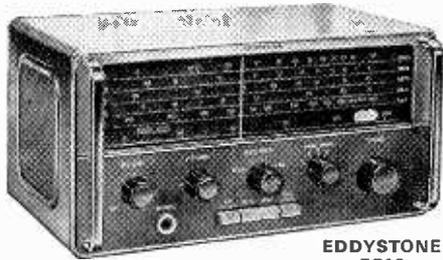The Sensational
ALL-TRANSISTOR
Communications Receiver



EDDYSTONE EC10

for use in the home, caravan, car or boat, H.P. facilities. Only £48 Part exchanges

Write for brochure

170-172 CORPORATION STREET BIRMINGHAM 4
Telephone: 021-236-1635

OLRUS ELECTRONICS LTD. PAD 1515
9 Norfolk Place (off Praed St.) London, W.2

FACTORY NEW FULLY GUARANTEED

Valves—Transistors—Diodes—Zener

DAF91 4/8	GZ34 10/-	68N7GTB	AF139 15/-	OAZ202 8/6	OC59 18/6
DAF96 6/8	PC88 11/-	7/-	AF186 19/6	OAZ203 8/6	OC60 17/6
DF91 3/-	PC87 11/-	6V6GT 6/8	AF119 22/6	OAZ204 8/6	OC65 22/6
DK96 7/-	PC87 7/6	6C32T 7/-	AF211 17/-	OAZ205 8/6	OC66 25/-
DK91 5/6	PC84 6/-	25L6GT 6/6	AF172 12/6	OAZ206 8/6	OC70 4/-
DK92 8/-	PCC89 11/-	30C15 10/-	ASV26 6/6	OAZ207 8/6	OC71 8/-
DK96 7/-	PCC189 11/-	30FL2 10/6	ASV28 6/6	OAZ208 8/6	OC72 5/-
DL92 5/-	PCF80 7/-	30PL14 11/-	ASZ20 7/6	OAZ209 8/6	OC73 7/6
DL94 6/8	PCF86 8/6	30L15 11/-	AE750 10/-	OAZ210 8/6	OC75 6/-
DL96 7/-	PCL82 7/-	30P12 9/-	GET102 6/-	OAZ211 8/6	OC76 5/-
DY86 6/4	PCL83 8/6	30P19 13/-	GET103 4/6	OAZ212 6/6	OC77 7/-
EB41 7/6	PCL84 7/6	30PL2 10/6	GET105 8/6	OAZ213 6/6	OC78 5/-
EB081 6/3	PCL85 9/-	30PL13 12/-	GET113 5/-	OAZ222 8/6	OC78D 5/-
EB096 4/8	PCL86 8/6	35LACT 6/-	GET114 4/-	OAZ242 4/6	OC81 5/-
EHP89 6/8	PL36 9/-	35Z5GT 5/6	GET115 9/-	OAZ245 4/6	OC81D 5/-
ECC81 4/-	PL81 7/-	50L6GT 6/6	GET116 12/6	OAZ246 4/6	OC81M 5/-
ECC82 5/-	PL82 6/6	AC107 10/-	NKT213 6/-	OAZ247 4/6	OC81DM 5/-
ECC83 5/6	PL83 6/6	AC126 6/6	NKT216 7/6	OAZ290 8/6	OC81Z 9/-
ECC85 5/-	PL84 6/6	AC127 7/6	NKT251 5/-	OAZ291 8/6	OC82 6/-
ECP80 7/-	PL85 6/6	AC127Z 9/6	NKT255 6/6	OAZ292 8/6	OC83 5/-
ECH35 10/8	PL600 13/6	AC128 6/6	NKT304 8/-	OC16 20/-	OC83 5/-
ECH42 9/-	PY32 8/6	AC176 7/6	NKT403	OC19 7/6	OC84 6/-
ECH81 5/2	PY81 6/-	ACY17 8/6	OA5 17/6	OC22 10/-	OC122 15/6
ECH84 8/10	PY82 5/6	ACY18 5/6	OA5 4/-	OC23 12/6	OC139 7/6
ECL80 7/-	PY83 6/-	ACY19 6/6	OA7 4/6	OC24 17/6	OC140 9/6
ECL82 6/8	PY88 7/3	ACY20 5/6	OA10 3/-	OC25 12/6	OC140 9/6
ECL86 9/-	UBC41 7/6	ACY21 6/-	OA47 3/-	OC26 7/6	OC170 5/-
EP80 5/-	UBC81 7/6	AD140 16/-	OA70 2/-	OC28 12/6	OC171 6/-
EP86 8/3	UC86 6/6	AD149 16/-	OA73 2/6	OC29 15/-	OC200 7/6
EP183 6/4	UCH42 8/6	AD161 11/-	OA79 2/6	OC35 12/6	OC201 11/6
EL84 6/4	UCH81 6/3	AD162 11/-	OA81 2/6	OC36 12/6	OC202 13/6
EL84 9/6	UCL82 7/3	ADT140 15/-	OA85 3/-	OC41 6/-	OC203 10/6
EL41 8/6	UL41 8/6	AF102 18/-	OA86 4/-	OC42 5/-	OC204 15/-
EL84 4/8	UL84 8/3	AF114 6/6	OA90 2/6	OC43 9/-	OC205 15/-
EM84 7/-	UY85 5/6	AF115 6/6	OA91 2/6	OC44 5/-	OC206 22/6
ET31 7/-	U25 9/6	AF116 6/6	OA95 3/6	OC44M 5/6	ORP12 8/6
EY86 6/8	U26 8/6	AF117 5/-	OA200 3/3	OC45 4/-	ORP60 5/6
EZ40 7/8	5U4GB 6/6	AF118 12/6	OA202 4/3	OC45M 4/-	RS202 4/6
EZ80 5/-	5Y30T 5/-	AF124 9/-	OA210 7/6	OC46 5/6	RS012 20/-
EZ81 5/-	5Z4GT 5/-	AF125 8/6	OA211 9/6	OC47 7/6	RS012A 25/-
EZ90 4/-	6F23 10/-	AF130 8/-	OAZ200 11/-	OC57 15/-	RS013 20/-
OZ29 10/-	6L6G 7/6	AF137 8/-	OAZ201 11/-	OC58 17/6	

C.W.O. only P. & P. 2/- in £ 1/- minimum
METAL WORK—PANELS—CHASSIS
For P.W. P.E. Constructional Projects

JOYSTICK VFA turns PRO!

History repeats itself!


Throughout the development of radio communication the keen private experimenter has contributed largely to the advance of our science. The amateurs of the thirties pioneered reliable shortwave transmission and reception. Basic theories and their practical application are to this day hatched in the fertile minds of ingenious men who are the leading amateurs of our time.

The Joystick Aerial System can now be regarded as the perfect example of a purely amateur development "turning professional". Thousands of Joystick variable frequency aerial systems have been sold. The enormous number of enthusiastic testimonials that have accumulated at the Joystick factory are now in themselves calling for a separate filing room! The continuing success of the VFA has not only spread right round the world but has finally penetrated the barrier of professional and official circles. Professional bodies in the USA, Europe, Africa and the Far East have ordered VFA systems for operational use and for experimental work. Security forbids the whispering of names but clearance has been given to mention the Nigerian Police and an Australian fire control organisation.

In the Scottish fishing boats which have installed the system, communication with other ships and shore stations has become considerably more reliable over difficult paths.


This VFA system is a remarkable invention and its unique quality of high performance at any selected frequency from 1 M/c to 30 M/cs—particularly from difficult locations—has radically changed the attitude of both the licensed amateur and the shortwave listener towards their aerial problems.

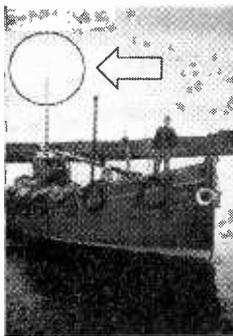Each Joystick VFA system is complete with a Joymatch matching unit suitable for each type of operation.




Scottish Fishing Boats Aerial Problems solved!

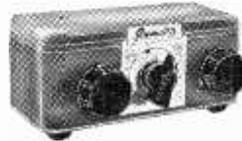The Joystick aerial was successfully subjected to the most rigorous tests under appalling weather conditions aboard the MFV *Crystal Sea* OB104 and the MFV *Margaret Ann* OB79 out of Mallaig. Previously the old-fashioned wires had to be lowered every time the ships' derricks were used. Communication with shore stations and other ships was consistently good.



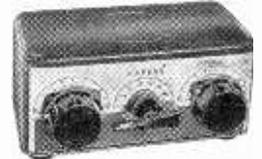Joymatch Type 2A—General medium wave coverage extending over short wave spectrum.



Joymatch Type 3A—General short wave coverage for SWL. Bandswitched for amateur bands. **Joymatch Type 4**—(similar to Type 3A). For transmission and reception. Bandswitched on 160—10 metres.



Joymatch Type 4RF—For transmission and reception on 160—10 metres. Includes RF meter for peak efficiency.



Joymatch Type 3—General short-wave coverage SWL (Junior model).

You cannot afford to ignore the potential of the Joystick VFA. The system is simple to use—the Joystick VFA will clip to a chimney, tree or mast, can be laid upon a pelmet, stood in the corner of a room, will even give a good account of itself in a basement.

Mobile Joystick systems are available and a new marine model has been introduced for the nautical types!

You are strongly recommended to contact the Joystick factory immediately (or one of our agents) for a brochure with full details.

U.K. Agents: G. W. Smith & Co. (Radio) Ltd., 3 Lisle Street, London, W.C.2. Stephens-James Ltd., 70 Priory Road, Liverpool, 4. Chas. H. Young, 170/172 Corporation Street, Birmingham, 4. R.S.C. (Manchester) Ltd., 326 Argyle Street, Glasgow, C.1 (and all branches) or ask your local dealer.

Overseas: France: Vareduc-Cominex, 2 Rue Joseph-Riviere, Paris, Courbevoie, France.

Scandinavia: Permo, Nygaardsgaten 42, Fredrikstad, Norway.

West Germany: Ing. Hannes Bauer, 86, Bamberg, Hornthalstrasse, 8, Stotz & Goessl, 8 Munchen 15, Bayerstrasse 3, and World Wide Agencies.

U.S. Patent No. 3274690. S. Africa Patent No. 63/4989. U.K. and World Patents applied for.

Post this coupon in the morning—without fail!

PARTRIDGE ELECTRONICS LTD.

Caister House, Prospect Road, Broadstairs, Kent

NAME.....Call Sign.....

ADDRESS

.....PWB

BRADFORD 10 North Pde. (Half-day Wed.) Tel. 25349
BRISTOL 14 Lower Castle St. (Half-day Wed.) Tel. 22904
BIRMINGHAM 30/31 Gt. Western Arcade, opp. Snow Hill Station. CENTRAL 1279. No half-day
DERBY 26 Osmonston Rd., The Spot (Half-day Wed.) Tel. 41361

DARLINGTON 13 Post House Wynd (Half-day Wednesday) Tel.: 68043

EDINBURGH 133 Leith Street (Half-day Wed.)

GLASGOW 326 Argyle St. (No half-day) Tel.: CITY 4158

HULL 91 Paragon Street (Half-day Thursday) Tel.: 20505

R.S.C.

HI-FI CENTRES LTD.

MAIL ORDERS TO: 102 Hencoller Lane, Bromley, Leeds 13. No C.O.D. under 121. Postage C.V.O. or C.O.D. Terms 4/6 extra under 22. 5/9 extra under 25. Trade supplied. S.A.E. with enquiries please. HI-FI CATALOGUE NOW AVAILABLE price 3/3 post paid. Personal shoppers welcome. Open all day Sats. except High Holborn branch.

LEICESTER 32 High Street (Half-day Thurs.) Tel.: 56420

LEEDS 5-7 County (Mecca) Arcade (No half-day) Tel.: 28252

LIVERPOOL 73 Dale St. (No half-day) Tel.: CENTRAL 3573

LONDON 238 Edgware Road, W2 (Half-day Thurs.) Tel.: PAD 1629. 96 High Holborn, WC1 Tel.: HOL 9374 (Half-day Sat.)

MANCHESTER (No half-day) 60A Oldham St. Tel.: CENTRAL 2778

MIDDLESBROUGH 106 Newport Road (Half-day Wednesday) Tel.: 47096

NEWCASTLE UPON TYNE 41 Blackett Street Opp Fenwick's Store (Half-day Wed.) Tel.: 21469

SHEFFIELD 13 Exchange Street, Castle Market Bldgs. (Half-day Thursday) Tel.: 20716



66- RECORD PLAYING UNITS
 Ready for plugging in to Amplifier or Tape Recorder.
RP2 Consisting of Garrard SP25 fitted Goldring CS90 high compliance ceramic Stereo/Mono ctrge with dnm'd stylus above. Only **19/2 Gns.**
RP3 As above but with Goldring Lenco G168 Transcription unit and CS90 Cartridge. Normally over £33. Terms available both units. Carr. 15/- **26/2 Gns.**

SPRING CLEARANCE SALE
 Send S.A.E. for list of brand new lines which must be cleared. Includes Record Playing Units, Amplifiers, Tape Decks, Cabinets, etc.

AUDIOTRINE HI-FI 'SPEAKER SYSTEMS
 Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit and Tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating. Or **5 Gns.** Senior 20 watt inc. Fane **5 Gns.** 122/10 speaker 7 Gns. Carr. 8/9. Carr. 6/9

AVAILABLE price 3/3 post paid. Personal shoppers welcome. Open all day Sats. except High Holborn branch.

ALL LEADING MAKES OF HI-FI EQUIP. STOCKED Cash or Terms

HI-FI LOUDSPEAKER ENCLOSURES

All types of pleasing modern design acoustically lined and ported and in finishes of light Teak or medium Walnut. Credit terms available.
SE8. For optimum performance with any Hi-Fi 8in. speaker. Size 22 x 15 x 9in. Carr. 7/6 **£5.17.9**
SE10. For 10in. Hi-Fi speaker with provision for tweeter. Size 24 x 15 x 9in. Carr. 10/- **£6.19.9**

SE12. For outstanding performance with any 12in. Hi-Fi speaker. Cut for tweeter. Size 24 x 20 x 10in. Or Deposit 27/- and 9 monthly payments of 19/2 (Total £9.10.6) Carr. 10/- **8 Gns.**
FHE8. Folded Horn type. Size 27 x 16 x 10in. Designed for high flux 8in. speaker with which exceptional quality can be obtained. Carr. 10/- **9 Gns.**

HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets of latest styling Satin Teak or Walnut, acoustically lined (and ported where appropriate). Credit Terms available on all units.

MINI 8 8 WATT rating, 3 or 15 ohm. Frequency response 50-15,000 c.p.s. Specially designed high flux 5in. speaker with low fundamental resonance. Handsome Teak veneered cabinet. **£6/19/11**
 9 1/2 x 7 1/2 in. Carr. 7/6

THE DORSET Size 16 x 11 x 8in. Response 45-18,000 c.p.s. Rating 10 watts. Fitted Audioline HF811D speaker. Impedance 3 or **£7/15/0**
 15 ohms. Carr. 7/6


THE DORCHESTER Size 24 x 15 x 10in. Fitted Audioline HF10D Speaker. Rating 12 watts. Impedance 3 or 15 ohms. Frequency Response 30-20,000 c.p.s. Carr. 15/- **12 1/2 Gns.**

THE GLOUCESTER Size 24 x 20 x 8in. 12in. High flux Cross-over speaker and Tweeter. Rating 10 watts. Smooth response 40-20,000 c.p.s. Impedance 15 ohms. Carr. 15/- **12 Gns.**
THE BRONTE Size 22 x 15 x 9in. Fitted Wharfedale Super 9 B5DD or Audioline HF 815D Speaker, with Roll surround and dual cone. Rating 6/10 watts. Impedance 3 or 15 ohms. Carr. 15/- **12 1/2 Gns.**

Tweeters R.A. 3 ohm or 15 ohm 25/9

15 watt HI-FI TRANSISTORISED AMPLIFIER TYPE A15

With integral pre-amplifier tone control stages. Output 15 W. 3 A.M. & C. into 15 ohms. 7.5 and 15 ohm spkrs. Kit includes Printed Circuit and all parts including 9 latest type semi-conductors. **£4.12.9** Post Heat sink and full wiring instructions or with printed circuit fully wired and tested 21/- extra. Frequency Response: ±1dB 20-20,000 c.p.s. Harmonic Distortion: 0.1%. Hum and Noise: -80dB. Sensitivity: 2mV. Bass Control: -9dB to +6dB at 40 c.p.s. Treble Control: +8dB to -13dB at 10 Kc/s. Will operate from batteries giving 24v. Suitable Power Pack Kit 47/9 or ready built 69/9

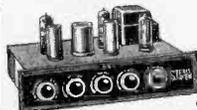

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a unit giving 5 watts high quality output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable all crystal or ceramic stereo heads. Ganged Bass and Treble Controls. Provision is made for use as straight (monaural) 10 watt amplifier. Value line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point to point wiring diagrams and instructions supplied. Send S.A.E. for leaflet.
 Or supplied factory assembled with 12 months' guarantee for 11 gns. **£8.15.0**
 Terms: Dep. 36/- and 9 monthly payments 25/5 (Total £13.4.9). Carr. 11/6

R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER

PROVIDING 10/4 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL. SUITABLE FOR 'MIKE', GRAM, RADIO OR TAPE. Employing valves ECC83, ECC83, ECL86, ECL86, E281. Frequency Response: ±1dB 20-20,000 c.p.s. Hum Level: 85dB down. Sensitivity: 5 millivolts maximum. Harmonic Distortion: (each channel): 0.2%. ★Four-position tone compensation and Input Selector Switch. ★Stereo/Mono switch. ★Will amplify direct from Tape Heads. ★Neon panel indicator. ★Handsome Perspex Frontplate. ★Separate Bass "Lift" and "Cut" and treble "Lift" and "Cut" controls. Output transformers are high quality sectionally wound to required specification. Output matching for 3 and 15 ohm spkrs. on 4 channels each channel. Complete set of parts, point-to-point wiring diagrams and instructions. Carr. 12/6 **14 Gns.**
 Or factory assembled, tested and supplied with our usual 12 months guarantee. Carr. 12/6 **19 Gns.**
 Or Deposit £3 and 9 monthly payments 43/2 (Total £22.4.6). Send S.A.E. for leaflet.



R.S.C. TFM1 TRANSISTORISED VHF/FM RADIO TUNER

Total cost of parts with detailed wiring diagrams and instructions. Carr. 10/- **12 1/2 Gns.**
 Or factory built 151 Gns. Or in Teak finished cabinet as illustrated 191 Gns. Terms: Deposit 25 and 9 monthly payments 39/- Total £22.11.0.



★ High-sensitivity ★ 200-350v. A.C. Mains operation. ★ Sharp A.M. Rejection. ★ Drift-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Simple alignment instructions. ★ Output available for feeding tuning meter. ★ Output for feeding Stereo Multiplexer. ★ Tuner head using Silicon Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Made to visually match our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. The pre-wired tuning head facilitates speed and simplicity of construction. Printed circuitry. Only first grade transistors and components used. Our latest product giving you the best at half the cost of comparable units. Stereo Multiplexer available.

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS


Heavy cast construction. Latest high efficiency ceramic magnets. Dual Cone for extended frequency range. Plastic treated surround giving low fundamental resonance. Response 35-20,000 c.p.s. Impedance 8 or 15 ohms. Carr. 5/6.
HF811D 8in. 10 WATT 4 Gns.
HF101D 10in. 12 WATT 5 Gns.
HF100D 10in. 15 WATT £5.15.0
HF121D 12in. 20 WATT £6.15.0
HF131D 12in. 30 WATT 9 Gns.



R.S.C. SUPER 15 HI-FI AMPLIFIER

FULLY TRANSISTORISED 200/250v. A.C. Mains. OUTPUT 15 W. cont. into 15 ohms. 15 WATTS R.M.S. cont. into 3-4 ohms. Maximum instantaneous Peak power output 28 watts. PRINTED CIRCUIT CONSTRUCTION. LATEST MULLARD TRANSISTORS. AD149, AD149, OC12Z, OC31Z, OC34, OC34, OC34, AC107. 3 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s. TREBLE CONTROL: +15dB to -14dB at 10 Kc/s. BASS CONTROL: +12dB to -15dB at 50 c/s. HUM LEVEL: -75dB. HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.25%. NEGATIVE FEEDBACK: 52dB. Complete Kit of parts with full constructional details and point to point wiring diagrams. Carr. 11/- Supplied factory built 151 Gns. Carr. 12/6. Terms: Deposit 49/- and 9 monthly payments 33/9 (Total £17.12.9). Or fitted in beautiful Walnut or Teak veneered cabinet as illustrated. 4 Gns. extra. ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING BRITISH MANUFACTURERS.

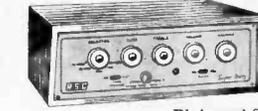TECHNICAL SPECIFICATIONS COMPARE MORE THAN FAVOURABLY WITH SIMILAR AMPLIFIERS AT TWICE THE COST




11 Gns.

R.S.C. SUPER 30 STEREO AMPLIFIER

A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuit. Close tolerance Ganged Pots. Matched Components. CROSS TALK: -52dB at 1,000 c.p.s. CONTROLS: 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch, BALANCE SELECTOR (Matching Pairs). (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of the Input Selector Switch assures appropriate equalisation. Rigid 18 s.w.g. Chassis. Size approx. 12in. Wide, 3in. High and 8in. Deep. Neon Panel Indicator. Attractive Facia Ganging and Balance Control, apply also to Super 15. THESE UNITS ARE ESSENTIALLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon) CURRENTLY AVAILABLE. SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions. Carr. 13/9 **18 Gns.**
 Unit factory built 251 Gns. or deposit 83/9 and 9 monthly payments 56/9 (Total £29.14.6). Fitted cabinet as Super 15 291 Gns. Carr. 15/- or leaflet £4.14.9 and 9 mthly paymts 65/10 (Total £24.7.3). Send S.A.E. for leaflet.

AUDIOTRINE HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST. S.A.E. for leaflet. CAN BE ASSEMBLED IN AN HOUR. ONLY 4 PAIRS OF SOLDERED JOINTS PLUS MAINS. Incorporating the latest Magnavox Tapedeck. The Audiotrine High Quality Tape Amplifier with switched equalisation for each of 3 speeds. High Flux 2 1/2" Sp. Tape Speed. Special Order of Best Quality Tape and a handsome Portable Cabinet of latest styling finished dark grey leathercloth. Size 14 1/2 x 17 x 8 1/2 in. and circuit. Purchased separately would total approx. £34. Performance equal to units in the £50-£60 class. Deposit 4 gns. and 9 monthly payments 5/6 (Total 29 gns.) 4 Track Model 4 gns. extra. Carr. 19/8

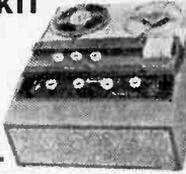

26 1/2 Gns.

LINEAR TAPE PRE-AMPLIFIER. Type LP/1 Switched Equalisation. Positions for Recording at 1/4, 3/16, 7/16 in. Per sec. and Playback. EM34 Recording. Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier suitable most Tape Decks. Terms available. 10 1/2 Gns.

R.S.C. 4/5 watt A5 HIGH GAIN AMPLIFIER
A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P. U. heads and practically all "mikes". Separate Bass and Treble controls giving "lift" and "cut". Hum level 70dB down. Negative Feedback 15dB. Reserve power supply 300v 2 1/2 ma., 6.3v 1.5 a. for Radio Tuner or Tape Pre-amp. For A.C. mains 200-250v. Speaker output 3 ohms. Complete in every detail with fully punched enamelled chassis, point-to-point wiring diagrams and instructions. Or assembled ready for use 6 gns. plus 5/6 carr.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp./Tone Control Stages. Performance figures equal to most expensive amplifiers available. Hum level -70dB. Frequency response +3dB 30-20,000 c/s. Specially designed sectionally wound ultra linear output transformer with 807 output valves. All first grade components. Valves EF98, EF86, EF87, EF807, 807. Separate Bass and Treble Controls. Sensitivity 12 millivolts so that any kind of Microphone or Pick-up is suitable. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve Power for Radio Tuner or Tape Pre-amp. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50 c.p.s. A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts fully punched chassis, point to point wiring diagrams and instructions. 12 Gns. Carr. 12/6. Supplied factory built with EL34 output valves, 12 months guarantee for 15 gns. If required perforated cover with carrying handles can be supplied for 21/- . Send s.a.e. for leaflet. TERMS: Deposit 4/8- and 9 monthly payments of 3/7 (Total £17.10.).

JASON VHF/FM TUNER Complete kit with valves. £6.19.11
Miniature Transistorised VHF/FM Tuner Battery operated. In plastic case complete with Telescopic Aerial. Carr. 5/- £6.19.11

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allow mixing of "mike" and gram, etc. etc. High sensitivity. Valves ECC83, ECC81, EL84, E27B. High quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE. Frequency response +3dB 30-20,000 c/s. Six negative feedback loops. Hum level -70dB. SENSITIVITY 22 millivolts. Suitable for Crystal or Ceramic P. U. all types "mikes". Comparable with the very best designs. For Musical Instruments such as String Bass, Electronic Guitars, etc. Reserve Power provides 300v. 30mA, and 6.3v. 1.5a. for Radio Tuner or Tape Pre-amp. Size approx. 12 x 9 x 7 1/2 in. For A.C. mains 200-250v. 50 c.p.s. Output for 3 and 15 ohm speakers. Kit complete in every detail with fully punched, Full instructions and point-to-point wiring diagrams and instructions. £8.15.0 built £11.5.0. Metal cover with 2 handles available for 21/- . TERMS ON Carr. 11/6 ASSEMBLED UNITS: Deposit 3/6 and 9 monthly payments of 2/5 (Total £13.3.). Send S.A.E. for illustrated leaflet of Cabinets, Speakers, Mikes, etc.

R.S.C. BASS-REGENT 50 WATT AMPLIFIER

AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT For lead, rhythm, bass guitar and all other musical instruments. For vocalists, gram, radio, tape and general public address.
★ UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS a with extending wire mesh speaker. ★ 4 Jack Inputs and two Volume Controls for simultaneous use of up to 4 pick-ups or "mikes". ★ Cabinets covered in two-tone Rexine/Vynair with gold trimming. Fitted carrying handles. ★ Separate Bass and Treble Controls giving "lift" and "cut". ★ Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at three times the cost. Carr. 30/- Or deposit £7.17.6 and 9 monthly payments of £5.10. (Total 55 gns.)

B20 MULTI-PURPOSE AMPLIFIER especially suitable for Bass Guitar

Incorporating massive 15in. high flux loudspeaker. Rating 25 watts. Individual bass and treble controls. Two jack inputs separately controlled. Substantial cabinet attractively finished in Rexine and Vynair. Size approx. 24 x 21 x 11 in. Send S.A.E. for leaflet. 29 1/2 Gns. Or Deposit £4.14.8 and 9 monthly payments of 6/6- (Total £24.8.6). Carr. 17/6.

G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, Mike, Gram or Radio

High-fidelity output. Separate bass and treble controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Heavy Duty 12in. 20 watt Speaker. Cabinet covered in attractive Rexine/Vynair. Size 18 x 8 1/2 in. Deposit 3 gns. 19 1/2 Gns. 15/- . (Total £22.15.3.). S.A.E. for leaflet.

G20 SUPER TWIN AMPLIFIER

Rating 20 watts (max) for vocalists, Lead or Rhythm Guitar etc. Twin separately controlled inputs. Two 12in. High Flux speakers (Total rating 30 watts). Rexine/Vynair covered cabinet. Terms: Deposit £4.6.8 and 9 monthly payments 5/0- (Total £26.16.8). 23 Gns.

POWER PACK KIT Consisting of Mains Transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250v. A.C. 22 1/11 mains. Output 250v. 60mA. 6.3v. 2a. Supplied with case in lieu of chassis 28/11. Or assembled 39/11.

HEAVY DUTY BATTERY CHARGER KITS 6/12 v. Consisting of Mains Trans. 200-250 v., Rectifier, Ammeter, Variable Charge Rate Selector, Panels, Plugs, Fuses and Holders. Fully punched stove enamelled case and circuit. 4a 49/11 6a 69/11

SELENIUM RECTIFIERS F.W. (Bridged) All 6/12 v. D.C. output. Max A.C. input 18 v. 1a. 3/11. 2a. 6/11. 3a. 9/8. 4a. 12/8. 6a. 15/8. **HEAVY DUTY SELENIUM RECTIFIERS 19/9** 12v. 15 amps. F.W. (Bridged). Only

LONDON-NEWCASTLE

New branches now open — see addresses

R.S.C. COLUMN SPEAKERS Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. 15 ohm impedance. Type C58, 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 14 Gns. 4 1/2 x 10 x 5 in. Or Deposit 4/4- and 9 monthly payments 31/5 (Total £16.6.9) Carr. 10/- Type C42, 40 watts, Fitted four 12in. 12,000 line 10 watt speakers. Overall size 21 Gns. 5 1/2 x 14 x 9 in. approx. Carr. 15/- Or Deposit £3.11.0 and 9 monthly payments of 46/7 (Total £24.10.3).

30 WATT HI-FI AMPLIFIER for Guitar, Vocal or Instrumental Group A Four input, two volume control Hi-Fi unit with separate Bass and Treble "cut" and "boost" controls. Lafores type valves. Housed in strong Rexine covered cabinet with twin carrying handles. Attractive black and gold perspex face plate. For 200-250v. A.C. mains. Output for 3 or 15 ohm speakers. 17 Gns. 12/6. £3 and 9 monthly payments of 37/5 (Total £19.16.9).

12in. HIGH QUALITY L'SPEAKERS

In walnut veneered cabinet. 10 Watt Model. Gauss 12,000 lines. 3 1/2 x 10 in. 15 ohms. Carr. 7/6 £4.19.11

20 Watt Model. 15 ohm. Size 18x12x10in. Gauss 12,000 lines. £7.19.11

Terms available on both. Carr. 10/6

FANE HEAVY DUTY HI-FI SPEAKERS 5 Gns.

12in. 20 watt. Type 122/10. Post 8/9. 12in. 30 WATT HEAVY DUTY 15 ohm LOUDSPEAKERS Flux Density 17,000 lines. Fully Guaranteed. Outstanding value at normal price of approx. £12. Or deposit 23/10 and 9 monthly payments of 15/6 (Total £23.4.4). Carr. 12/6

R.S.C. GRAM AMPLIFIER KIT. 3 watts output. Negative feedback. Controls: Vol., Tone and Switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc. supplied. 10/9/11.

HIGH QUALITY 12in. 10 WATT SPEAKERS 59/11

Flux Density 12,000 lines. 3 or 15 ohms. TRANSISTOR SALE Mullard OC71, OC72, OC81, 2/11, OC44, OC45, 3/11, OC75, 7/9, AF117, 6/9, Ediswan XA101 XA112, XC101A, 3/9, Postage 6d. for up to 3 transistors.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primary 200-250 c/s. Screened. MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in. 250v. 60mA. 6.3v. 2a 14/11 250-0-250v. 60mA. 6.3v. 2a 15/11 FULLY SROUDED UPRIGHT MOUNTING 250-0-250v. 60mA. 6.3v. 2a. 0-5-0-5v. 3a. 2 1/2 x 3 1/2 in. 19/9 350-0-350v. 100mA. 6.3v. 4a. 0-5-0-5v. 3a. 33/9 300-0-300v. 100mA. 6.3v. 4a. 0-5-0-5v. 3a. 33/9 300-0-300v. 130mA. 6.3v. 4a. c.t. 6.3v. 1a. 41/9 For Mullard 510 Amplifier 350-0-350v. 100mA. 6.3v. 4a. 0-5-0-5v. 3a. 33/9 350-0-350v. 150mA. 6.3v. 4a. 0-5-0-5v. 3a. 42/9 425-0-425v. 200mA. 6.3v. 4a. c.t. 6v. 3a. 67/9 425-0-425v. 200mA. 6.3v. 4a. 6.3v. 4a. 6v. 3a. 6v. 3a. 69/9 450-0-450v. 250mA. 6.3v. 4a. c.t. 6v. 3a. 79/9

TOP SROUDED DRO-THROUGH TYPE 250-0-250v. 70mA. 6.3v. 2a. 0-5-0-5v. 3a. 19/9 250-0-250v. 100mA. 6.3v. 3.5a. 21/9 250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a. 22/9 350-0-350v. 80mA. 6.3v. 2a. 0-5-0-5v. 2a. 23/9 250-0-250v. 100mA. 6.3v. 4a. 0-5-0-5v. 3a. 32/9 300-0-300v. 100mA. 6.3v. 4a. 0-5-0-5v. 3a. 32/9 300-0-300v. 130mA. 6.3v. 4a. 0-5-0-5v. 1a. 39/9

Suitable for Mullard 510 Amplifier 350-0-350v. 100mA. 6.3v. 4a. 0-5-0-5v. 3a. 32/9 350-0-350v. 150mA. 6.3v. 4a. 0-5-0-5v. 3a. 39/11

FILAMENT or TRANSISTOR POWER PACKS 6.3v. 1.5a 8/9. 6.3v. 2a 7/9. 6.3v. 3a 9/9. 6.3v. 6a 19/9. 15v. 1a 8/9. 12v. 3a or 5v. 1.5a 19/9. 0-9-18v. 1 1/2a. 15/9. 0-25-35-42v. 2a 27/9.

CHARGER TRANSFORMERS 0-15v. 1 1/2a. 18/11 2 1/2a. 16/11. 5a. 18/11. 5a. 21/11. 6a. 25/11. 6a. 31/11 AUTO (Step UP/Step DOWN) TRANSFORMERS 0-110/120v. 200-250v. 50-80 watts. 14/9 150 watts. 29/11. 250 watts. 49/8. 600 watts. 99/9

OUTPUT TRANSFORMERS Standard Pentode 5,000Ω to 3Ω or 7,000Ω to 3Ω 7/9 Push-Pull 8 watts EL34 to 3 or 15Ω 11/9 Push-pull 10-12 watts 6V6 to 3Ω or 15Ω 19/9 Push-pull 10-12 watts to match 6V6 to 3, 5, 8 or 15Ω 21/9 Push-pull EL84 to 3 or 15Ω 10-12 watts. 19/9 Push-pull Ultra Linear for Mullard 510, etc. 35/9 Push-pull 15-18 watts sectionally wound 6L6, KT66, etc. for 3 or 15Ω 22/9 Push-pull 20 watt high quality sectionally wound, EL34, 6L6, KT66, etc. to 3 or 15Ω fully shrouded. 55/9

SMOOTHING COILS 150 mA, 7-10H. 250/0.29/9. 100 mA, 10H. 200 0.9/11. 80 mA, 10H. 350 0.7/9. 60 mA, 10H. 400 0.4/11.



HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT


Type TA1

- Peak output in excess of 14 watts.
- All standard British components.
- Built on printed circuit panel, size 6 x 9in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 3 ohm and 15 ohm speakers.
- Transistors (GET 114 or S1 Mullard OC81D and matched pair of OC81 o/p).
- 9 volt operation.
- Everything supplied, wire, battery clips, solder, etc.
- Comprehensive easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately.

SPECIAL PRICE 45/-, P. & P. 3/-. Also ready built and tested, 52/6. P. & P. 3/-. A pair of T.A.s are ideal for stereo.

STEREO AMPLIFIER

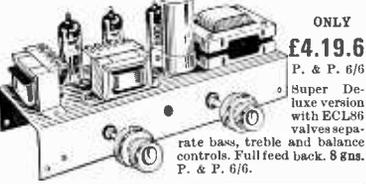Incorporating 2 ECL86s and 1 E230, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



ONLY

£4.19.6

P. & P. 6/6

Super Deluxe version with ECL86 valves separate bass, treble and balance controls. Fully fitted back. 8 Ans. P. & P. 6/6.

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 8 1/2 x 2 1/2 in.). ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite Rod Aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time **ONLY 25.5.0**, P. & P. 2/6. (Circuit diagram 2/-, Free with set of parts.)

35 OHM SPEAKERS

Suitable for use with above. 2in. Goodmans. Ideal replacement for most pocket portables, 8/6; 3 1/2in. 12/6; 7 x 4in. 21/-; P. & P. 2/- per speaker.

Portable CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker, 25/-, P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers one oscillator coil one driver transformer and wound Ferrite aerial (incl. long and cut aerial coupling). 22/6 complete post 2/-. 6 transistor printed circuit board to match 5/6. Post 1/-. Circuit diagram 1/6 extra.

MINIATURE PRECISION AIR-SPACED TWO GANG TUNING CONDENSER. 176+176 p.F. size 1 1/4" x 1 1/4" with vanes open. Built in trimmers 5/-, P. & P. 1/-

BRAND NEW TRANSISTOR BARGAINS

GET 15 (Matched Pair) 15/-; V15/10p, 10/-; OCT1 5/-; OC76 6/-; AF117 7/6. Set of Mullard 6 transistor OC44, 2—OC45 OC81D matched pair OC81 25/-, ORP12 Cadmium Sulphide Cell 10/6.

EDISWAN MAZDA

PXA101 6/6; XA103 8/6. R.F.I. Pack: 1—PXA102 Mixer; 2—PXA101 I.F. Amp. (Equiv. OC44 and OC45) 10/6. PXA102 Mixer 12/6. R.F. 2 Pack: 2—PXA101 I.F. 1—PXA102 Osc. 12/6. L.F. 6 Pack: Consisting of PXB113 Driver Matched pair. PX171 mounted complete with heat sinks (Equiv. OC81D and OC81) 12/6. ALL TRANSISTORS POST FREE.

TAPE DECKS

B.S.R. MONARDEK (Single speed) 3 1/2 in. per sec. simple control, uses 6 1/2 in. spools, £6.15.0 plus 7/6 carr. and ins. (Tapes extra).

LATEST COLLARO MAGNAVOX 363 TAPE DECK DE LUXE. Three speeds, 2 track, takes up to 7in. spools. 10 gs. Plus 7/6 Carr. & ins. on each (Tapes extra).

PORTABLE TAPE RECORDER CASE

Beautifully made and expensively finished in dark grey heavy grade rexine. Satin Chrome metal grille front and chrome fittings. Speaker aperture 9" x 4". Overall size 15 1/2" w. x 15" d. x 7 1/2" h. Will take any standard tape deck or single record player. Limited number only. Worth at least 25. OUR PRICE 49/6. P. & P. 3/-. Brand new and unused.

ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity. 18/6. P. & P. 1/6. **TSL CRYSTAL STICK MIKE.** Listed at 45/-. Our price 18/6. P. & P. 1/6.

QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. This amplifier (was used in a 29 gm. record player) employs heavy duty double wound mains transformer, ECC83, EL84, E230 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 4 1/2 in. d. x 5 1/2 in. h. Ready built and tested. PRICE 89/6. P. & P. 4/9. ALSO AVAILABLE mounted on board with output transformer and 6in. speaker ready to fit into cabinet below. PRICE 89/6. P. & P. 5/9.

QUALITY PORTABLE R/P CABINET

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autochanger or Single Record Player Unit. Size 18 x 14 x 8 1/2 in. Price 23.9.6. Carr. 7/6.

4-SPEED PLAYER UNIT BARGAINS

All brand new in maker's original packing. **SINGLE PLAYERS**
B.S.R. TU/12 23.9.6 Carr. 5/6.
GARRARD SP25 De Luxe £10.10.0 Carr. 5/6.
B.S.R. GU7 with unit mounted pickup arm. £4.18.8 Carr. 6/6.

AUTO CHANGERS

Latest B.S.R. UA25 Super silu 26.2.6
GARRARD 1000 with special Hi-Fi cartridge. 26.19.6
GARRARD AT60 29.19.6 Carr. 6/6 or extra.
All the above units are complete with 1/2 mono head and sapphire styli or can be supplied with compatible stereo head for 12/6 extra.

BRAND NEW CARTRIDGE BARGAINS!

ACOS GP67-1. Mono complete. List price 21/-. Our price 13/6. P. & P. 1/-.

BRAND NEW 3 OHM LOUSPEAKERS

5in., 12/6; 6 1/2 in., 15/-; 8in., 21/-; 10in., 25/-; 7in. x 4in., 15/-; 10in. x 6in., 26/-. E.M.I. 8" x 5" with high flux ceramic magnet, 23/6. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet, 42/- (15 ohm, 45/-). P. & P. 3/- 2/-, 6 1/2" & 8" 2/6, 10" & 12" 3/6 per speaker.

SPECIAL OFFER!

Limited number of 12in. 10 watt "R.A." Speakers: 3 ohm 25/-; 15 ohm, 27/6. P. & P. 3/6.

E.M.I. PLASTIC CONED TWEETERS. 2 1/2" 3 ohm. Limited number 12/6 each. P. & P. 1/6.

BRAND NEW HEAVY DUTY 12in. SPEAKERS

Response 45 c/s-13 Kc/s. 1 1/2 in. voice coil. Available in 3 or 15 ohms. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE at 89/6 P. & P. 5/-. Also 25 watt Guitar Model available at 25.5.0. And 35 watt Guitar Model 23.8.0.

VYNAIR AND REXINE SPEAKER AND CABINET FABRICS.

Approx. 54in. wide. Usually 35/- yard. OUR PRICE 13/6 per yard length. P. & P. 2/6 (incl. one yd.) S.A.E. for samples.

SPECIAL OFFER!

GENUINE HIGH QUALITY TYGAN FABRIC. 48in. wide. Our price 10/- per foot run. P. & P. 1/6. 30/- per yard run. P. & P. 2/6.

SEMI SHROUDED DROP THRO' MAINS TRANSFORMER.

Tapped pri 200/250v. Sec. 40-0-40 at 1 amp (with electrostatic screen) and 6.3v at 5 amp for dial lamps etc. Drop thro mounting. Stack size 1 1/2 x 3 1/2 x 1 1/2 in. 30/-. P. & P. 3/6.

MAINS TRANSFORMER.

For transistor power supplies. Pri. 200/240v. Sec. 9.0-9v. at 500mA. 11/-, P. & P. 2/6.

MAINS TRANSFORMER.

For transistor power supplies. Tapped pri 200/250v. Sec. 40-0-40 at 1 amp (with electrostatic screen) and 6.3v at 5 amp for dial lamps etc. Drop thro mounting. Stack size 1 1/2 x 3 1/2 x 3 1/2 in. P. & P. 4/6.

MATCHED PAIR OF 2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS.

Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/-. P. & P.

7-10 watt OUTPUT TRANSFORMERS to match pair of ECL 86's in push-pull to 3 ohm output. ONLY 11/-.

P. & P. 2/6.

WELL-KNOWN MAKERS SURPLUS! ONE TRANSISTOR PRE-AMP

Suitable for use with Medium or High Impedance mikes, guitars, gram pickups, tape decks etc; For operation from 200/300 volt H.T. rail or 9 volt battery. Gain approx 14:1. Fully isolated input by Mu-Metal screened transformer. Size 4 1/2" x 1 1/2" x 1". Ready built complete with full circuit diagram and instructions. ONLY 15/-. Post free.


Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser.

35/-, P. & P. 3/-.

TWIN TELESCOPIC AERIAL.

Comprising two 3-section heavily chromed rods. Closed 12-in. each extending to 32in. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, coax lead and plug. Suitable for F.M. or TV. 12/6. P. & P. 2/6.

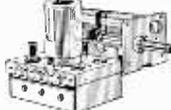SPECIAL HARVERSON OFFER! FM/AM TUNER HEAD



Beautifully designed and precision engineered by Dornier and Wadsworth Ltd. Specially tuned ready fitted with twin .0005 fitting condenser for AM conversion. Prealigned FM section covers 86-102 Mc/s. I.F. output 10.7 Mc/s. Comprising 1st I.F. and 2nd I.F. discriminator (465kc/s /10.7Mc/s). Size 1 x 1 1/2 x 2 1/2 in. High. Will match above tuner head. 11/- pair. P. & P. 2/-. Order quickly! Limited number also available with precision geared 3:1 reduction drive. 30/-, P. & P. 3/-.

MATCHED PAIR AM/FM I.F.'s

Comprising 1st I.F. and 2nd I.F. discriminator (465kc/s /10.7Mc/s). Size 1 x 1 1/2 x 2 1/2 in. High. Will match above tuner head. 11/- pair. P. & P. 2/-.

SPECIAL PURCHASE! TURRET TUNERS

By famous maker. Brand new and unused. Complete with PCC84 and PCF80 valves 34-38 Mc/s I.F. Biscuits for channel 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 25/- each. P. & P. 3/9.

GORLER F.M. TUNER HEAD

89-100 Mc/s 10.7 Mc/s I.F., 15/-, plus 2/- P. & P. (ECC85 valve 8/6 extra).

3-VALVE AUDIO AMPLIFIER MODEL HA34

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 in. h. Incorporates ECC83, EL84, E230 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, etc., wired and tested for only **£45.0**, P. & P. 6/-.

HSL 'FOUR' AMPLIFIER KIT

A.C. Mains 200/250v., 4 watt, using ECC83, EL84, E230 valves.

- Heavy duty double-wound mains transformer with electrostatic screen.
- Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss.
- Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor.
- Suitable for use with guitar, microphone or record player.
- Provision for remote mounting of controls or direct on chassis.
- Chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in.
- All components and valves are brand new.
- Very clear and concise instructions are given to even the unskilled amateur to construct with 100% success.
- Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder, etc. (No extras to buy.) PRICE 79/6. P. & P. 6/-.
- Comprehensive circuit diagram, practical layout and parts list 2/6 (free with kit).

This kit although similar in appearance to HA34 employs entirely different and advanced circuitry.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 1/2 speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86, and E230 rectifier. Simple instruction booklet 1/6. (Free with parts.) All parts sold separately. ONLY 27.9.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, 29.5.0, P. & P. 8/6. Carrying case for above 28/6. P. & P. 7/6.

NEON A.C. MAINS INDICATOR. For panel mounting, cut out size 1 1/2 x 1 1/2 in. deep inc. terminal. White case with lens giving brighter light. For mains 200/250v. 2/6 each. P. & P. 6d. (6 or more post free).

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.
170 HIGH ST., MERTON, S.W.19 CHERYWOOD 3985
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

INCREASE YOUR KNOWLEDGE



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

CHOOSE THE RIGHT COURSE FROM
RADIO AND TELEVISION ENGINEERING,
INDUSTRIAL TELEVISION, RADIO AND
TELEVISION SERVICING, ELECTRONICS,
COMPUTERS AND PROGRAMMING,
ELECTRONIC TECHNICIANS, SERVOMECH-
ANISMS, TELEMETRY, CLOSED CIRCUIT TV,
INSTRUMENTATION, AND PRINCIPLES OF
AUTOMATION.

ALSO EXAMINATION COURSES FOR:

Inst. of Electronic and Radio Engineers
C. & G. Telecommunication Techns'. Cert.
C. & G. Supplementary Studies
R.T.E.B. Radio/TV Servicing Cert.
P.M.G. Certificates. Radio Amateurs' Exam.

LEARN AS YOU BUILD

Practical Radio Courses: Gain a sound knowledge of Radio as you build YOUR OWN 5-valve superhet Receiver and Transistor, Portable Signal Generator and High Quality Multitester. At the end of the course you have valuable practical equipment and a fund of personal knowledge and skill. ICS Practical Radio Courses open a new world to the keen amateur.

THERE IS AN ICS COURSE FOR YOU


Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

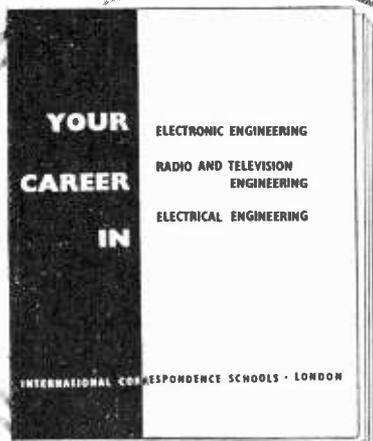You will receive the FREE ICS Prospectus listing the examination, and ICS technical courses in radio television and electronics PLUS details of over 150 specialised subjects.



PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS

.....

OCCUPATION..... AGE.....


INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170, INTERTEXT HOUSE, PARKGATE ROAD, London, SW11
3/67

LASKY'S RADIO

FOR THE FINEST VALUE AND TO HOME CONSTRUCTORS

TRANSISTOR PORTABLES

THE SKYROVER De Luxe

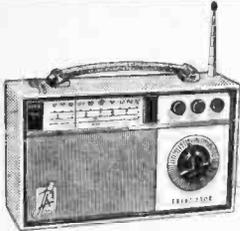

7 transistor plus 2 diode superhet, 6 waveband portable receiver covering the full Medium Waveband and Short Waveband 31-94M and also 4 separate switched bandspread ranges, 13M., 16M., 19M. and 25M., with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions. Superhet, 470 Kc/s. All Mullard Transistors and Diodes. Uses 4 U2 batteries. 51a Ceramic Magnet P.M. Speaker. Easy to read Dial Scale, 500 MW Output. Telescopic Aerial and Ferrite Rod Aerial. Tone Circuit is incorporated, with separate Tone Control in addition to Volume Control. Tuning Control and Waveband Selector. In a wood cabinet, size 11 1/2 x 8 1/2 x 3 1/2, covered with a washable material, with plastic trim and carrying handle. Car aerial socket fitted.

Can now be built for **£8.19.6** Post 5/- extra

H.P. Terms: 60/- deposit and 11 monthly payments of 18/9. Total H.P.P. £10.0.3. Four U2 batteries 3/4 extra.

★ **LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THE SKYROVER**
A simple additional circuit provides coverage of the 1100/1950M. band (including 1500M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data.

Only 10/- extra Post Free.
This conversion is suitable for receivers that have already been constructed.
Data 2/6 extra: refunded if you purchase the parcel.
All components available separately.

SINCLAIR SUPER MINIATURE KITS

Write for details of Package Deals

THE MICRO-6 miniature radio only 1 1/2 x 1 3/4 x 1 1/4 in.	£2 19 6
THE MICRO-FM (tuner/receiver)	£5 19 6
THE X-20 20 watt P.W.M. amplifier	£7 19 6
Available ready built, tested and guaranteed	£9 19 6
The Z-12 12 watt amp. and pre-amp, fully built	£4 9 6
PZ-3 power pack for Z-12	£3 19 6
STEREO 25 Pre-amplifier control unit, fully built	£9 19 6

TAPE RECORDERS


MAGNAVOX 363 TAPE DECKS

The very latest 3 speed model—1 1/2, 3 1/2, 7 1/2 ips, available with either 1 track or 2 track head. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys. Size of stop plate 1 3/4 x 1 1/4 x 5/16 in. deep below unit plate. For 200/250V. A.C. mains, 50 cps operation. New, unused and fully guaranteed.

Lasky's Price 1 track model **£10.10.0**

Lasky's Price 2 track model **£13.9.6**

Carriage and wiring 7/6 extra.

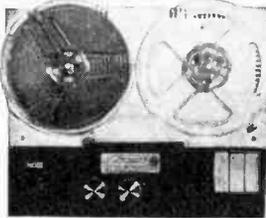

NEW MARTIN TAPE RECORD/REPLAY AMPS.

Now available from stock—for use with the Magnavox 363 Tape Deck.
1 track model..... LASKY'S PRICE **£14.19.6** Carriage and 1 track model..... LASKY'S PRICE **£15.19.6** Packing 4/6 extra.
Optional extra: Control panel escutcheon to take deck and amplifier controls.
LASKY'S PRICE 12/6 Post & Packing 2/6.

INTERNATIONAL TAPE

Famous American Brand—Fully Guaranteed

3in. Message tape, 150ft.	2 6	5 1/2in. Long play, 1200ft. Acetate	12 6
3in. Message tape, 225ft.	3 9	5 1/2in. Standard play, 850ft. PVC	11 6
3in. Message tape, 300ft.	7 6	5 1/2in. Long play, 1200ft. Mylar	15 0
3 1/2in. Triple play, 600ft. Mylar	10 0	5 1/2in. Triple play, 2400ft. Mylar	45 0
4in. Triple play, 900ft. Mylar	17 6	7in. Standard play, 1200ft. Acet.	12 6
5in. Double play, 1200ft. Mylar	15 0	7in. Standard play, 1200ft. Mylar	12 6
5in. Long play, 900ft. Acetate	10 0	7in. Long play, 1800ft. Mylar	19 6
5in. Standard play, 900ft. PVC	8 6	7in. Double play, 2400ft. Mylar	25 0
5in. Triple play, 1800ft. Mylar	35 0	7in. Long play, 1800ft. Acetate	15 0
5 1/2in. Double play, 1800ft. Mylar	22 6	7in. Triple play, 3600ft. Mylar	50 0

P. & P. 1/- extra per reel. 4 reels and over Post Free

MICROPHONES

THE TTC MODEL B4002 FM WIRELESS MICROPHONE

Highly sensitive—suitable for either static or mobile use. Signals can be picked up by any FM radio or tuner which receives frequencies between 96—104 Mc/s over several hundred yards. Size only 3 x 2 1/2 x 1 1/2 in. (in leather case). Operates in one PP3 type battery. Complete with neck cord, clip on dynamic extension mike (1 1/2 x 1 1/2 in.) and battery. LASKY'S PRICE 10 Gns. Post Free anywhere in world.

THE TTC MODEL 13/500. More powerful version of above—size 7 1/2 x 1 1/2 x 1 1/2 in. Operates on one PP3 type battery. LASKY'S PRICE 12 Gns. Post Free anywhere in world. These cannot be operated in the U.K.



CONSTRUCTORS BARGAINS

SPECIAL PURCHASE—UHF/VHF TV TUNERS

Well known British makers surplus stocks. Now available for the first time to the Home Constructor. Add 2/8 Post and Packing on each.

TRANSISTORISED UHF MINIATURE MODEL 1

Shielded metal case only 3 1/2 x 1 1/2 x 3/16 in. Fully tunable—complete with two AF139 transistors. LASKY'S PRICE 39/6

TRANSISTORISED UHF MODEL 2

Metal case size 3 1/2 (plus spindle) x 2 1/2 x 1 1/2 in. Fully tunable with slow motion drive. Complete with two AF186 transistors. LASKY'S PRICE 25/6

VALVE UHF MODEL (illustrated)

In metal case size 4 x 6 x 1 1/2 in. Fully tunable—complete with PC86 and PC88 valves. LASKY'S PRICE 29/6 Without valves 12/6

TRANSISTORISED VHF TUNER


Sub-Miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case size 8 x 1 1/2 x 2 1/2 in. LASKY'S PRICE 37/6



TREMENDOUS BARGAIN!

TV UHF TUNER AND TV AMPLIFIER PANEL

Model No. 89384 made by famous manufacturer as standard conversion unit to 625 line reception (BBC 2) for 19" and 25" 406 line convertible model Cossor, Philips, Scott and Stella television receivers. The units are boxed, brand new and fully guaranteed, complete with detailed conversion and operating instructions. To effect conversion on the sets mentioned above you need only a pair of pliers and a screwdriver! The units are fitted with 7 Mullard valves—PC80 x 2, EP135, EP134, ECC82, PC86, PC88. Size of unit: tuner 7 1/4 x 4 1/2 in., IF panel on 9 x 4 1/2 in. printed circuit board x 2 in. deep. Complete with all leads, screws, washers etc. Original Price £10.10.0.

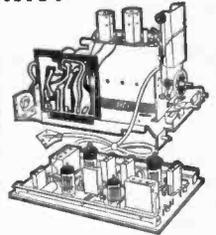

LASKY'S PRICE 49/6 Post 5/-

TREMENDOUS VALUE IF BOUGHT ONLY FOR THE VALVES AND COMPONENTS

NEW—LASKY'S MINIATURE TRANSISTOR

AMPLIFIER MODULES

Incorporating the very latest circuitry to provide high sensitivity and good quality in conjunction with extreme small size and compactness. High quality Newmarket transistors used throughout. All designed to operate on 9v. miniature battery.

Add 1/- on each for Post and Packing.

TYPE LRPC 1. 3 transistor. Input sens. 50mV, output 150mW, output imp. 40Ω, 2 x 1 x 1 in. PRICE 27/6

TYPE LRPC 2. 5 transistor. Input sens. 1mV, output 330mW, output imp. 15Ω, size 2 1/2 x 1 1/2 x 1 in. PRICE 22/6

TYPE LRPC 3. 5 transistor. Input sens. 5mV, output 400mV, output imp. 15Ω, size 2 1/2 x 1 1/2 x 1 in. PRICE 25/-

TYPE LRPC 4. 5 transistor. Input sens. 150mV, output 330mW, output imp. 15Ω, size 2 1/2 x 1 1/2 x 1 in. PRICE 22/6

TYPE LRPC 5. 6 transistor. Input sens. 8mV, output 3W, output imp. 3Ω, size 5 1/2 x 1 1/2 x 1 in. PRICE 59/6

TYPE LRPC 6. Tape record/playback amp. (for use with self oscillating erase head). Output 750mW, output imp. 8Ω. Size 4 1/2 x 2 x 1 in. PRICE 39/6

FULLY ENCAPSULATED MODULES

Special function modules—all one size 1 1/2 x 1 x 1 1/2 in. Complete with detailed function and installation instructions. Send S.A.E. for specification sheets.

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-

TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-

TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-

TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-

TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-

TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-

TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-


TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones, 3Ω output imp. PRICE 30/-

TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3Ω output imp. PRICE 30/-

TYPE CO-1. Morse code practice oscillator—for use with morse key and 3Ω speaker. PRICE 20/-

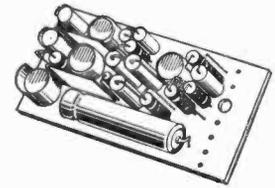TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3Ω speaker or indicator lamp). PRICE 22/6



TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET 81, GET 85, GET 86 2/8; 873A, 874F 3/8; OC45, OC71, OC81D 4/8; OC44, OC70, OC76, OC81 5/8; (match pair 10/8); AF117, OC200 6/8; OC42, OC43, OC73, OC82D 7/8; OC201, OC204 15/-; OC205, OC206 19/8; OC28 24/8; OC75 8/-.

TRANSFILTERS

by BRUSH CRYSTAL CO., Available from stock.


TO-01B 465 kc/s. ± 2 kc/s.	TO-02D 470 kc/s. ± 1 kc/s.	9/6 each Post 6d.
TO-01D 470 kc/s. ± 2 kc/s.	TF-01B 465 kc/s. ± 2 kc/s.	
TO-02B 465 kc/s. ± 1 kc/s.	TF-01D 470 kc/s. ± 2 kc/s.	

NOW AVAILABLE—OUR NEW BARGAIN BULLETIN. 24 foolscap pages packed with hundreds of bargains for the "ham" and service man—exclusive to Lasky's—plus full list of regular stock items. PRICE 6d. POST FREE.

SERVICE IN GREAT BRITAIN AND HI-FI ENTHUSIASTS



RECORD PLAYERS

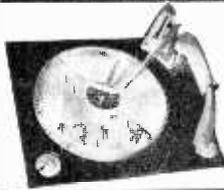

B.S.R. AUTOCHANGERS AT LOWEST EVER PRICES

Brand new and fully guaranteed—complete with cartridge and stylus.
 UA 14 4 speed mains model \$4. 9. 6
 UA16 4 speed mains model \$4.19. 6
 UA16 9v. battery model \$5.19. 6
 UA20 4 speed mains model \$5.19. 6
 Add 5/- carriage and packing on each.

GARRARD AUTOCHANGERS NEW LOW PRICES!

AT6 Mono	\$8 19 6	SRP25 Mono	\$9 19 6
AT6 Stereo	\$9 9 0	SRP25 Stereo	\$10 19 6
30001.M with stereo cartridge ..	\$7 9 6	SRP12 with cartridge ..	\$4 7 6
AT60 with stereo cartridge ..	\$10 9 0	SRP10 Mains, with cartridge ..	\$4 19 9
A70 less cartridge	\$19 9 0	SRP10 Battery with cartridge ..	\$4 19 6
A50 less cartridge	\$7 10 0	GARRARD BASES	
A1000 with GC8 cartridge ..	\$6 6 0	WB1 \$3 16 3 Clearview cover	\$3 10 0
A2000 with GC8 cartridge ..	\$6 6 0	WB2 \$5 5 0 Clearview cover	\$4 17 6

Postage and Packing on all above 5/-.

GREENCOAT RECORD PLAYER
 33 $\frac{1}{3}$ and 45 r.p.m. 6v. Battery operated Comp. with pick-up and crystal cartridge.
LASKY'S PRICE 49/6 Post 2/6 Size 7 $\frac{1}{2}$ x 6in.

207 EDGWARE ROAD, LONDON, W.2 Tel. PAD 3271
 118 EDGWARE ROAD, LONDON, W.2 Tel. PAD 9789
 33 TOTTENHAM CT. RD., LONDON, W.1 Tel. MUS 2605
 All the above branches open all day Saturday. Early closing Thursday.

Mail Orders and correspondence to 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel.: STEpney Green 4821/2

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

SPECIAL INTEREST ITEMS!

NEW! LASKY'S CLEAR PLASTIC PANEL METERS



Precision made in Japan by HIOKI. Each meter boxed and fully guaranteed with all fixing nuts and washers. Sizes are of front panel. Add 1/6 Post on each.

Type KE-52 3 x 2 $\frac{1}{2}$ in. (Illustrated)
 1 mA DC 32/6 300 V DC 32/6
 5 mA DC 32/6 50 μ A 42/6
 1 mA S Meter 39/6

Type MK-38A 2in. square		Type KR-65 3 $\frac{1}{4}$ x 3in.	
1 mA DC	22/6	1 mA DC	36/-
5 mA DC	22/6	5 mA DC	35/-
300 V DC	22/6	300 V DC	35/-
50 μ A	32/6	50 μ A	47/6
1 mA S Meter	29/6	1 mA S Meter	39/6

Type MK-45A 1 $\frac{1}{2}$ in. square		Type MK-65A 3in. square	
1 mA DC	25/-	1 mA DC	36/-
5 mA DC	25/-	5 mA DC	35/-
300 V DC	25/-	300 V DC	35/-
50 μ A	39/6	50 μ A	49/6
1 mA S Meter	35/-	1 mA S Meter	37/6

THE HARROW POWER PACK

Battery eliminator for portable radios, etc. Converts your Battery radio to A.C. mains Replaces 4 $\frac{1}{2}$ v., 6v. and 9v. batts. Size only 3 x 2 x 2 $\frac{1}{2}$ in. State voltage required when ordering.

LASKY'S PRICE 29/6 Post 2/-

42 TOTTENHAM CT. RD., LONDON, W.1 Tel. LAN 2573
 152/3 FLEET STREET, LONDON, E.C.4 Tel. FLE 2833

Both open all day Thursday. Early closing Saturday.

HOME RADIO LTD. Dept. PW, 187 London Rd., Mitcham, Surrey, CR4 2YQ Phone MIT 3282

And what do you mean by Q.C. Mr Brief?

"M'Lud, I had in mind Quality Components. There is a well-known publication which lists out some 6,000 Electronic Components of the highest quality, over 1,000 of them illustrated and arranged so scientifically that a mere child could pick out his requirements."

"One would assume you are referring to the HOME RADIO CATALOGUE."

"Quite so, M'Lud."

"Then I think you might add that each catalogue contains five vouchers each worth one shilling if used as directed."

"I am, as usual, astounded at M'Lud's erudition!"



If you would like to be astounded, send off today for the Home Radio Catalogue. Only 7/6 plus 1/6 postage and packing. Please include *code* in our address.

Please write your Name and Address in block capitals

NAME


ADDRESS

HOME RADIO LTD Dept. PW, 187 London Rd., Mitcham, Surrey, CR4 2YQ

Adamin

Micro Soldering Instruments

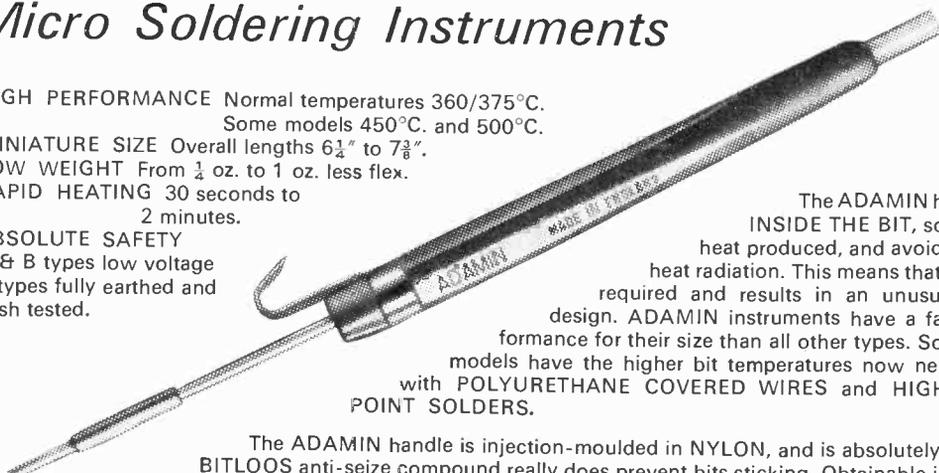- HIGH PERFORMANCE Normal temperatures 360/375°C.
Some models 450°C. and 500°C.
- MINIATURE SIZE Overall lengths $6\frac{1}{4}"$ to $7\frac{3}{8}"$.
- LOW WEIGHT From $\frac{1}{4}$ oz. to 1 oz. less flex.
- RAPID HEATING 30 seconds to 2 minutes.
- ABSOLUTE SAFETY
A & B types low voltage
C types fully earthed and flash tested.



The ADAMIN has its element INSIDE THE BIT, so using all the heat produced, and avoiding excessive heat radiation. This means that less power is required and results in an unusually compact design. ADAMIN instruments have a far higher performance for their size than all other types. Some ADAMIN models have the higher bit temperatures now needed to cope with POLYURETHANE COVERED WIRES and HIGH MELTING-POINT SOLDERS.

The ADAMIN handle is injection-moulded in NYLON, and is absolutely unbreakable. BITLOOS anti-seize compound really does prevent bits sticking. Obtainable in 2-oz. tubes.

Free details in brochure SP10.

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, Surrey

Telephone: CROydon 8589 and 4559

surprise



surprise



FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 132-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio and Electronic Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Appointments Dept. and shows you how to qualify for five years promotion in one year.

SATISFACTION OR REFUND OF FEE

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £30 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE

WHICH IS YOUR PET SUBJECT

Mechanical Eng.
Electrical Eng.
Civil Eng.
Radio Eng.
Automobile Eng.
Aeronautical Eng.
Production Eng.
Building, Plastics
Draughtsmanship
Television etc.

B.Sc.
City & Guilds
Gen. Cert. of
Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc. A.M.I.E.R.E., City & Guilds Radio Amateur's Exam R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.



POST COUPON NOW!

Please send me your FREE 132-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)
 NAME
 ADDRESS

 SUBJECT OR EXAM THAT INTERESTS ME 344B

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

344B, Aldermaston Court, Aldermaston, Berks.

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

Perhaps you will be as surprised as the pundits when you hear the facts* about the BSR C1 ceramic cartridge "... another milestone on the public right-of-way to high fidelity"—said *The Gramophone*.

You could even be surprised to know that the BSR UA70 manual/automatic turntable unit is fitted with such a splendid cartridge and that its all round performance is equal to such high standards. But maybe not ... you could be one of those sensible people who knew all along that BSR don't just make a lot of autochangers but a lot of *very good* autochangers.

*If you'd like to read the independent test reports write to Arthur Nicholls at:

BSR Limited, Monarch Works, Old Hill, Staffordshire.



for better sound reproduction

BSR UA70 SPECIFICATION

Turntable
Wow Less than -2%
Flutter Less than -06%
Long term speed variation
Less than -5%
(mains voltage ± 10%)

Rumble (ref.1kHz) —29 dB

Pick-up arm

Counterbalanced lightweight arm with calibrated tracking pressure control, integral cueing device and automatic lock.

Tracking pressure (depending on cartridge) 2 grams. min.

Cartridge

The now famous C1 ceramic

Compliance 5.2 × 10⁻⁶ cm/dynes

Frequency response 20-15,000 Hz ± 2dB

Standard UA70 player £12.18.3*

C1 Ceramic Cartridge

sapphire stylus £2. 7.0*

diamond stylus £3. 1.9*

*Inc. P.T. surcharge

VIKING TRANSISTOR

40-50 WATT AMPLIFIER

OPERATING INSTRUCTIONS GENERAL. An extremely reliable lightweight amplifier capable of giving 40-50 watts of undistorted sound, made possible by the use of the latest semi-conductors (transistors) and techniques which ensure space-age reliability under the most rugged conditions. It is designed as a general purpose amplifier particularly suitable for use with musical instruments that require exceptionally high treble response (not recommended for Bass Guitar). Tremolo facilities are available on Channel 1 only. **INPUTS—CONTROLS—CHANNEL 1 (Tremolo):** this contains two high gain input jack sockets controlled by **Volume Control 1** which is mounted directly above the two sockets marked tremolo. **BASS 1:** gives a controlled boost to the lower frequencies on Channel 1 only. **TREBLE 1:** gives a controlled boost to the high frequencies on Channel 1 only. **TREMOLO:** this operates on Channel 1 only and the variations of intensity and speed of the Tremolo beat is adjusted by the controls **DEPTH** and **SPEED**. A socket is provided in the rear of the amplifier so that the Tremolo may be switched on and off by the use of a footswitch plugged into the socket. If you wish the Tremolo to be used without the foot-switch, this is possible as the footswitch is only used to short out the effect. **INPUTS AND CONTROLS—CHANNEL 2 (Normal):** this contains two high gain input jack sockets controlled by **Volume Control 2** which is mounted directly above the sockets marked Normal. **TREBLE 2:** gives a controlled boost to the treble frequencies on Channel 2 only. **MAINS VOLTAGE:** fully adjustable, 200-250 volts, A.C. 50 cycles. **POWER OUTPUT:** 40-50 watts sine wave British rating. Very little distortion. **OUTPUT IMPEDANCE:** 3 ohms. Price 21 gns. plus 4/- postage and packing.



WOLSEY U.H.F. AERIAL AMPLIFIER, two stage, gain 23 db, noise factor 8 db, power consumption 6 ma at 14 volts. Two AF186 transistors, complete with built-in power supply in metal case, list price 9 gns., our price 4½ gns. plus 2/6 postage and packing.

MAINS TRANSFORMER, primary 200/250 volt, secondary 425/425 volt, 250 mA, 6.3 volt 4 amp, 5 volt 3 amp; fully shrouded, chassis mounting. Price £25.0 plus 7/6 postage and packing. Auto transformer step-up-step-down, 240/110 volt 400 watt. Price £15.0 plus 7/6 postage and packing.

MAINS TRANSFORMER 200/250 volt, secondary 250/250 volt, 70 mA, 6.3 volt, 3 amp drop through. Price 12/6 plus 4/6 postage and packing. Elac 10 inch, 10,000 lines ceramic magnet, 3 or 15 ohms, 7½ watt, £19.6 plus 4/6 postage and packing.



POCKET MULTI-METER

Size 3¼ x 2¼ x 1¼ in. Meter size 2¼ x 1¼ in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150 0-1000. D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test prods. battery and full instructions, 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

40W FLUORESCENT LIGHT KIT

Incorporating GEC Choke size 8¼ in. x 1¼ in. x 1¼ in., 2 bi-pin holders, starter and starter-holder. P. & P. 5/6. **11/6**
Similar to above. Fluorescent Light Kit incorporating GEC choke size 11¼ in. x 1¼ in. x 1¼ in. 2 bi-pin holders start and starter holder. P. & P. 6/6. **17/6**
Twin 40W Choke instant start for 2 x 2ft tubes 17/6. P. & P. 5/6.



MUSETTE 6 TRANSISTOR SUPERMET PORTABLE RADIO



39/6

P. & P. 3/6.
Circuit diagram 2/6.
Free with parts.

INCLUDING CARRYING STRAP

- 2½" Speaker.
- 6 Transistors Superhet Output 200mW.
- Plastic Cabinet in red, size 4½" x 3" x 1½" and gold speaker louver.
- Horizontal Tuning Scale.
- Ferrite Rod Internal Aerial.
- IF 470 kc.


- All components, Ferrite Rod and Tuning Assembly mount on printed board.
- Operated from PP3 Battery.
- Full comprehensive instructions and point-to-point wiring diagram.
- Printed Circuit Board.
- Tunable over medium and long wave-band. (Car aerial and car piece socket).

RADIO & TV COMPONENTS (ACTON) LTD
21C HIGH STREET · ACTON · LONDON · W.3


MULTIPLEX DECODER

For receiving Stereo FM

Now is your chance to benefit in full from the new B.B.C. stereo transmissions with our Multiplex Decoder. Design features: Highly efficient Mullard vinkor pot cores. Two semi-conductor diodes. Double purpose valve. Printed circuit type construction high input impedance. Specification: Cross talk minus 26 dB at 1 kc/s. Input requirements 0.5-1.5 RMS. Stability plus or minus 0.1%. Voltage requirements H.T. 190-250 volts. D.C. at 5 mA. heaters 6.3 volts. A.C. at 300 mA. Self powered unit shortly available, price to be announced. Size 5½" x 3¼" x 1". Fully built and tested.

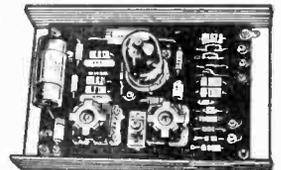

Price £4.4.0 P. & P. 3/-

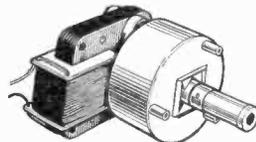

Type E MOTOR

Small A.C. mains motor 230/250 volts complete with gearbox. 6 r.p.m. Price 15/- plus 4/- P. & P.
Similar to above motor but without gearbox. 1/price 9/6 plus 3/- P. & P.



FIRST QUALITY P.V.C. TAPE

5½ in. Std. 850ft. 9/-	5 in. L.P. 850ft. 10/6
7 in. Std. 1200ft. 11/6	3 in. T.P. 600ft. 10/6
3 in. L.P. 240ft. 4/-	3 in. T.P. 1800ft. 25/6
5½ in. L.P. 1200ft. 11/6	5½ in. T.P. 2400ft. 32/6
7 in. L.P. 1800ft. 13/6	7 in. T.P. 3600ft. 42/6
5½ in. D.P. 1800ft. 18/6	4 in. T.P. 900ft. 15/-

P. & P. on each 1/6, 4 or more post free.



£11.11.0

"MAYFAIR" 5-Transistor TAPE RECORDER

Capstan-driven, battery operated 7½ and 3½ ips. Precision made. Push-button controls. High quality 2½ in. speaker. Push-pull circuit. Output 400mW. Frequency response: 200-7,000 kc/s. Fast rewind. Up to 1 hour twin track playing time. Automatic erasing for re-recording. Dimensions: 8 in. x 11 in. x 3¼ in. Weighs only 7½ lb. Takes 5 in. spoke. plus 9/- P. & P.

SILICON RECTIFIERS

250 v. P.I.V. 750 millamps. Six for 7/6 post paid.

3 to 4 WATT AMPLIFIER


3-4 watt Amplifier built and tested. Chassis size 7 x 3½ x 1 in. Separate bass, treble and volume control. Double wound mains transformer. metal rectifier and output transformer for 3 ohms speaker. Valves ECC81 and 6V6. The above in Kit Form. 29/6 plus 5/6 p. & p.



POWER SUPPLY KIT

A.C. MAINS 200-250V
Incorporating "C" core type mains transformer, full wave metal rectification and smoothing condenser. Smooth output 250 v. 250 mA and 6.3 v. 4 amp. for Heaters.

25/- P. & P. 9/6

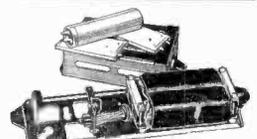

NEW TRANSISTORISED SIGNAL GENERATOR

Size 5½" x 3¼" x 1½". For IF and RF alignment and AF output 700 c/s frequency coverage 460 kc/s to 2 mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and Musette. Built and tested.

39/6 P. & P. 3/6

CYLDON U.H.F. TUNER

Complete with PC88 and PC86 Valves. Full variable tuning. New and unused. Size 4½ x 5½ x 1¼ in. Complete with circuit diagram. plus 3/6 P. & P.



★ ALL ORDERS BY POST MUST BE SENT TO OUR ACTON ADDRESS

★ Our new branch at
323 EDGWARE ROAD, LONDON, W.2.
IS NOW OPEN ● PERSONAL SHOPPERS ONLY
ALL ENQUIRIES STAMPED ADDRESSED ENVELOPE
OPEN 9 a.m.—6 p.m. INCLUDING SATS. EARLY CLOSING WED.
GOODS NOT DESPATCHED OUTSIDE U.K. TERMS C.W.O.

Elegant Seven Mk II A

SPECIAL OFFER

7" x 4" P.M. Speaker at no extra charge

Buy yourself an easy to build 7 transistor radio and save at least £10.0.0. Now you can build this superb 7 transistor superhet radio for under £4.10.0. No one else can offer such a fantastic radio with so many de luxe star features.


- ★ De luxe grey wooden cabinet size 12½" x 8½" x 3½".
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 1½" x 2".
- ★ High 'Q' ferrite rod aerial.
- ★ I.F. neutralization on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback.
- ★ Room filling output 350 mW.
- ★ Ready etched and drilled printed circuit board back printed for fool proof construction.
- ★ Fully comprehensive instructions and point-to-point wiring diagrams.
- ★ Car aerial socket.
- ★ Fully tunable over medium and long wave. 168-535 metres and 1250-2000 metres.
- ★ All components ferrite rod and tuning assembly mount on printed board.
- ★ Full after sales service.
- ★ Parts list and circuit diagram 2s. 6d., free with parts.

ONLY £4.4.0

Plus 7/6 P. & P. Parts List and circuit diagram 2/6 FREE with parts.

To purchasers of 'Elegant Seven' parts, incorporating mains transformer, rectifier and smoothing condenser, A.C. mains 200/250 volts. Output 9v 100mA. 7s. 6d. extra.

COMBINED PORTABLE and CAR RADIO

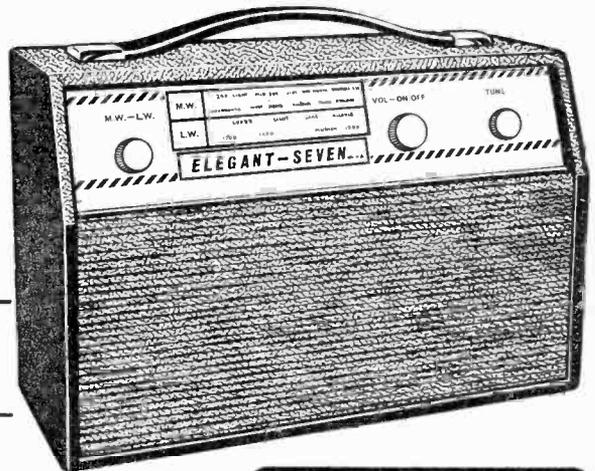

***Our new branch at**
323 EDGWARE ROAD, LONDON, W.2.
IS NOW OPEN
PERSONAL SHOPPERS ONLY

All orders by post must be sent to our Acton address.

ALL ENQUIRIES STAMPED ADDRESSED ENVELOPE
OPEN 9 a.m.—6 p.m. INCLUDING SATS. EARLY CLOSING WED.
GOODS NOT DESPATCHED OUTSIDE U.K. TERMS C.W.O.

RADIO & TV COMPONENTS (ACTON) LTD
21C HIGH STREET · ACTON · LONDON · W.3

BUILD YOUR CIRCUITS ON VEROBOARD

— the Universal Wiring Board —
obtainable from your local Retailer

Retail enquiries to:

NORMAN ROSE (ELECTRICAL) LTD.
8 ST. CHAD'S PLACE, GRAYS INN ROAD, LONDON, W.C.1

Technical enquiries to:

VERO ELECTRONICS LTD., Chandler's Ford, Hampshire

ELECTRONICS GALORE! IN THE NEW dca CATALOGUE

THE CONVENIENT WAY TO SHOP FOR ALL YOUR ELECTRONIC NEEDS. EVERYTHING FROM SINGLE COMPONENTS TO COMPLETE EQUIPMENT ALL AT BEST VALUE PRICES.

SEND 1/6d. NOW FOR YOUR COPY TO:—
Dept. PW/3

dca ELECTRONICS LIMITED
28 UXBRIDGE ROAD, EALING, W.5

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 1B5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94, Set of 4 for 16/-, DAF96, DF96, DK96, DL96, 4 for 24/6

1A7GT 7/6	10C2 11/6	DH76 3/6	EF91 3/6	PEN36C15/ 7/6	UCH81 8/-
1H5GT 7/3	10F1 9/9	DH77 4/-	EF92 2/6	PEN388 9/8	UCL82 7/-
1N6GT 7/9	10P13 8/6	DH81 12/6	EF97 7/6	PFL200 14/-	UCL83 8/9
1R5 4/9	12A17 3/9	DK32 7/9	EF183 6/9	PL36 8/9	UF41 8/-
1B4 4/9	12A16 4/9	DK91 4/9	ET184 6/-	PL81 8/9	UP80 7/-
1B5 3/9	12A17 4/9	DK92 6/-	EL33 6/6	PL82 6/6	UP89 5/9
1T4 2/9	12A17 4/9	DK96 6/6	EL41 8/6	PL83 6/-	UL41 8/9
3A5 7/-	12K7GT 3/6	DL33 6/9	EL42 7/9	PL84 6/3	UL44 15/-
3Q4 5/6	12K8GT 7/9	DL35 5/-	EL84 4/9	PL600 13/6	UL84 5/9
3B4 4/9	12Q7GT 3/6	DL92 4/9	EL90 4/9	PL801 7/6	UY21 8/9
3V4 5/6	20P2 10/6	DL94 5/6	EL95 5/6	PX25 7/9	UY41 4/9
5U4G 4/6	20L1 14/-	DL96 6/-	EM80 5/9	PY31 6/6	UY85 4/9
5V4G 7/9	20P1 9/-	DY86 6/6	EM81 7/3	PY32 8/8	VP4B 11/-
5Y3GT 5/-	20P3 9/-	DY87 6/6	EM84 5/9	PY33 8/8	VP1321 21/-
8Z-0 6/9	20P4 13/6	EAB380 6/-	EM87 6/6	PY80 5/3	W76 3/6
6X0L2 9/8	25L4GT11/6	EAF42 7/6	EY61 6/3	PY81 5/3	W77 2/9
6AL5 2/3	30C15 10/6	EB41 4/-	EY86 6/-	PY82 5/-	Z77 3/6
6AM6 3/6	30C17 11/6	EB91 2/3	EZ40 6/3	PY83 5/9	Transistors
6AQ5 4/9	30F5 9/9	EB33 6/-	EZ41 6/6	PY88 7/3	AC107 10/-
6AT6 4/-	30L1 10/6	EB41 7/9	EZ80 3/9	PY800 6/8	AC127 7/6
6BA1 4/9	30L15 11/-	EBP80 9/-	EZ81 4/-	PY801 8/-	AD140 15/6
6BE6 4/3	30L17 12/-	EBP89 5/9	GZ32 9/-	R19 7/6	AF102 18/-
6BJ6 5/6	30P4 11/6	ECC81 3/9	KT61 6/9	R20 12/9	AF115 6/9
6BW6 7/3	30P12 9/9	ECC82 4/9	N18 5/6	U25 9/-	AF116 6/9
6F1 7/9	30F19 11/6	ECC83 7/-	N78 14/9	U26 8/9	AF117 5/-
6F13 3/6	30L11 12/9	ECC84 6/3	PC37 5/9	U47 5/6	AF118 13/6
6F14 9/-	30L13 11/6	ECC85 5/6	PC800 3/9	U49 9/6	AF124 9/-
6F23 9/9	35L6GT 6/3	ECP80 7/6	PCC84 5/6	U52 4/6	AF125 8/6
6K7G 1/6	35W4 4/6	ECP82 6/9	PCC89 9/9	U78 3/6	AF126 8/-
6K8G 4/3	35Z4GT 4/6	ECP86 9/-	PCC189 3/6	U91 10/6	AF127 8/-
6X9GT 7/6	85A2 5/9	ECL35 6/-	PCF80 6/6	U301 11/9	OC22 17/6
6L18 7/6	185BT 20/-	ECH42 9/-	PCF82 6/-	U801 16/3	OC25 9/6
6Q7G 5/6	60S3 12/6	ECH11 5/-	PCF86 8/3	UABC80 5/9	OC26 9/6
6V9G 3/6	AZ31 8/9	ECH184 8/6	PCF800 10/6	UAP42 7/9	OC43 4/3
6V9GT 6/6	B36 4/6	ECL80 6/6	PCF801 8/9	UBC41 6/9	OC45 3/3
6X4 3/6	B799 10/-	ECL82 6/3	PCF802 6/6	UF80 6/-	OC71 3/6
6X3GT 6/3	DAC32 7/9	ECL86 7/9	PCF805 8/-	UBF89 5/9	OC72 4/9
7B6 10/9	DAF91 3/9	EF39 3/9	PCL82 6/9	UBL21 9/-	OC75 5/9
7B7 7/-	DAF96 6/-	EF41 6/3	PCL83 8/6	UC84 7/9	OC81 3/6
7C5 9/6	DC90 7/-	EF80 4/9	PCL84 7/6	UC85 6/6	OC81D 3/6
7C6 6/9	DF33 7/9	EF85 5/-	PCL85 8/3	UCF80 8/3	OC82 5/9
7H7 5/-	DF91 2/9	EF86 6/3	PCL86 8/6	UCH21 9/3	OC82D 5/6
7Y4 5/-	DF96 6/-	EF89 5/-	PENA4 6/9	UCH42 8/9	OC170 5/6

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. CRE 7441

Postage on 1 valve 6d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

LOOK!

PRACTICAL!

VISUAL!

EXCITING!




a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing . . .


1 OWN and HANDLE a

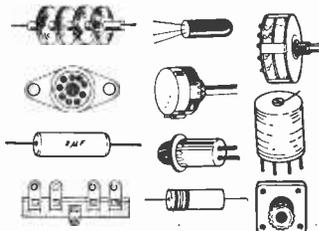complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 BUILD and USE

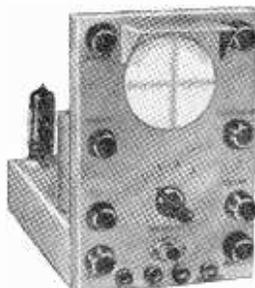a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 READ and DRAW and

UNDERSTAND **CIRCUIT DIAGRAMS**

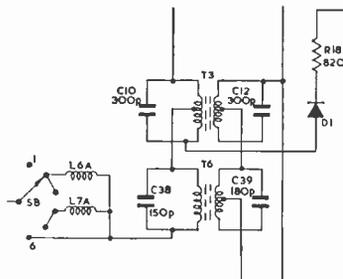

4 CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME BLOCK CAPS

ADDRESS..... PLEASE PW3

PRACTICAL WIRELESS

VOL 42 No 11

issue 721

MARCH 1967

TOPIC OF THE MONTH

More 'Pop' & Local Radio

The White Paper issued recently on Broadcasting has done a jolly good job of whitewashing and it is difficult from this document to comprehend the Government's attitude towards broadcasting in the United Kingdom. It has denied Independent Television the right to broadcast in colour (which would not cost the general public an extra penny), yet has permitted the BBC to start a popular music programme in the medium wave band and to run an experimental chain of local radio stations in the v.h.f. band.

"It has of course been the Government's duty," the White Paper explains, "to consider what the proposals for further extending the broadcasting services should seek to serve, and what organisation could best promote these purposes. The Government have also had to consider to what extent it would be in the national economic interest to allow the extensions. It is not enough that they should be desirable in themselves. The overriding consideration is whether the country can afford them."

What a lot of rubbish! The "pirate" radio stations have clearly shown that there is a need for "pop" music and that in general, listeners are not offended by the accompanying advertising. The Government have totally disregarded public opinion in deciding to set up a "popular" music station of a character which will not replace the "pop pirates".

Nine experimental local radio stations operating in the v.h.f. band are to be set up by the BBC in different parts of the country during the year. Locations have not yet been decided, but the stations are hoped to offer a full-scale local service and to be financially supported from local sources. Commercial advertising will not be accepted, yet the BBC will be prepared to accept financial support from local authorities, Chambers of Trade and Commerce, local Councils of Churches, arts associations and other representative bodies active in the social and cultural life of the community. The BBC will not, however, take a direct grant from the local rate fund, but will accept money from local authority departments, such as education. Thus, it would appear that this scheme is just another burden upon the ratepayer.

W. N. STEVENS—*Editor*

NEWS AND COMMENT

Leader	819
News and Comment	820, 844
On the Short Waves <i>by John Guttridge and David Gibson, G3JDG</i>	831
Practically Wireless <i>by Henry</i>	835
The MW Column <i>by Alistair Woodland</i>	843
Future Broadcasting Plans	848
New Books	865

CONSTRUCTIONAL

Top Band Transceiver <i>by T. Simon</i>	822
Balance Controls for Stereo Amplifiers <i>by J. B. Willmott</i>	826
Improving the R1155 <i>by C. Molloy</i>	837
2-Transistor Personal Portable <i>by R. Leyland</i>	840
Low Cost PSU <i>by F. L. Thurston</i>	857
Tape Position Indicator <i>by J. Lowrie, Grad.I.E.E.</i>	866

GENERAL ARTICLES

Solid State Thermometers and Thermostats <i>by K. T. Wilson</i>	846
Pse QSL <i>by David Gibson, G3JDG and Alan Thompson</i>	850

APRIL ISSUE WILL BE PUBLISHED ON
MARCH 3rd

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes Rand London. Subscription rates, including postage: 36s. per year to any part of the world. © George Newnes Ltd., 1967. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Power supplies

I WAS unable to follow the reasoning in the article by H. T. Kitchen that appeared in the January 1967 issue.

Obviously $\frac{250}{25} \times \frac{60}{230}$ is not equal to 38

ohms as he states. Of course $\frac{250}{25} \times \frac{230}{60}$ is equal to 38 but what happened to the milliamps, that 10^{-3} bit, and how on earth did he come by the equation $\frac{E^1}{I} \times \frac{E^2}{I^2} = R$ (internal) and then confuse the product IR as being internal resistance?

P. Murphy.

Aldermaston,
Berkshire.

The author replies:

I admit guilt in committing the sin of confusing my multiplication and division signs. The error is undoubtedly mine, and as the perpetrator thereof I must, bravely smiling, take the consequences.

It is, I regret, yet another example of the fallibility of human nature; of how a temporary loss of sync between brain and pen can virtually ruin much otherwise painstaking and accurate work.

As I see it, however, the bone of contention is the ultimate equation for calculating IR. Here, of course, I was well and truly up the creek when I used a multiplication sign instead of a minus one. The equation should have read $\frac{E^1 - E^2}{I^2 - I^1}$

Using the new set of rules the IR for my power supply works out at 571 "point something" ohms. And as for forgetting our little milliamp friends, I hang my head in shame.—H. T. Kitchen.

THE P.W. FILM SHOW


The annual film show, organised jointly by Mullard Ltd. and Practical Wireless, is to be held, as before, at Caxton Hall, Caxton Street, Westminster, London, S.W.1. The date is Friday, April 14th, and the show will start at 7.30 p.m. prompt.

The programme will include a film *Electrons in Harness* and a topical talk on *Transistors and Television*. Refreshments will be served in the interval.


Applications for tickets—which are free—should be made now to Film Show, Practical Wireless, Tower House, Southampton Street, London, W.C.2. A stamped addressed envelope must be included with all applications.

NEWS AND..

TWO NEW MODELS FROM K.W. ELECTRONICS

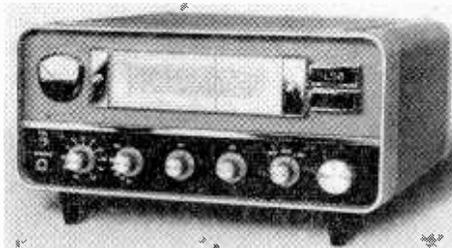

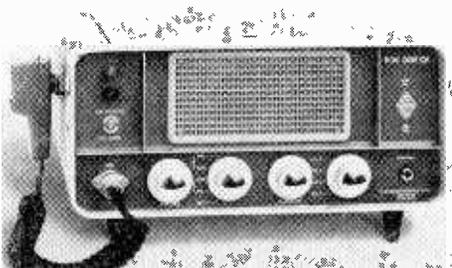KW201
Amateur Band Receiver
 11 ranges, 1.8—30 Mc/s. Crystal mixer. Crystal BFO. Q Multiplier.
 Sens: $1\mu V/500mW$.
 S/N: $1\mu V/20dB$.



KW2000CA
SSB Transceiver
 3—19 Mc/s. 180W p.e.p. (SSB), 75 watts (CW), 25 watts (AM). Mains or Battery.
 Transceiver—18 lb.
 A.C. p.s.u.—23 lb.
 D.C. p.s.u.—6½ lb.

The KW201 incorporates a mechanical filter which gives an i.f. selectivity of 3.1 kc/s at 6dB and 6 kc/s at 60dB. The Q multiplier (optional extra) gives a range of 3.1 kc/s to 200 c/s selectivity. The slide-rule vernier dial is accurate to 1 kc/s. The KW201, designed for optimum performance on single sideband, measures 13½ x 6 x 12½ in. and weighs 19 lb. Power supply is 200—240V, but a 115V version is available. The price is £105, complete with 13 crystals.

The KW2000CA is a commercial long range unit with a frequency stability of 1 part in 10⁶ in ambients between +70°C to -10°C. Enquiries to K.W. Electronics Ltd., 1 Heath Street, Dartford, Kent.

SILICON PLANAR TRANSISTORS—NEW TYPES

Mullard have added seven new p-n-p types to their range of silicon planar transistors. Because of their linear gain/current characteristics they are all suitable for both switching and linear applications.

The BCY70 and BCY72 are both 350mW type, the former having a high V_{ceo} of 40V and low saturation voltage and intended for medium-speed switching applications. The BCY72 is a general purpose type.

Low leakage current, low saturation voltage and high cut-off frequency (in excess of 200 Mc/s) are features of the new 600mW transistors 2N2904, 2N2904A and 2N3133 (high speed switching and driving) and 2N1131, 2N1132 (medium speed switching).

Mullard also announce new additions to their range of miniature and sub-miniature glass-encapsulated quartz crystal units. An AT-cut unit is available for a range of 1.6—87 Mc/s. There is also a special 10 Mc/s unit for secondary frequency standards (QX3100). A data book with full specifications is available on request.

IMPROVED SURFORM TOOLS

Stanley Works announce a completely redesigned range of their well-known Surform tools which have replaceable blades and can be used on materials from balsa wood to mild steel. Most readers will be familiar with these tools and will be interested to hear that an additional heavy duty blade specifically recommended for use on harder materials such as metals is now available for the first time.

...COMMENT

NEW YORK STATE LAW ENFORCEMENT FACSIMILE SYSTEM

Recently Governor Nelson A. Rockefeller, and Mayor John Lindsay and Commissioner Howard Leary, inaugurated a new communication system to aid New York State criminal justice agencies in fighting crime.

The equipment being supplied by Western Union for New York State Identification and Intelligence System is manufactured by the Muirhead Group of Companies.


Prior to the installation of this equipment when a suspect was fingerprinted, identification could take 7 to 10 days, it now takes 2 to 3 hours.

The suspect's fingerprint card is placed on a photographic transmitter and within 14 minutes is sent over a telephone circuit to an automatic photographic facsimile recorder. The received copy is automatically processed within the machine to produce a finished photographic copy of the original fingerprint card. This automatic processing takes approximately 12 seconds.

Once the suspect's identity is verified, a copy of his criminal history is transmitted by a rapid message facsimile system to the originating agency in 4 minutes.

The installation is one of some 105 similar systems to be installed during the next 18 months, linking the various criminal justice agencies throughout the State with the State's Division of Identification in Albany.

WORLD'S LARGEST TELEGRAPH CENTRE

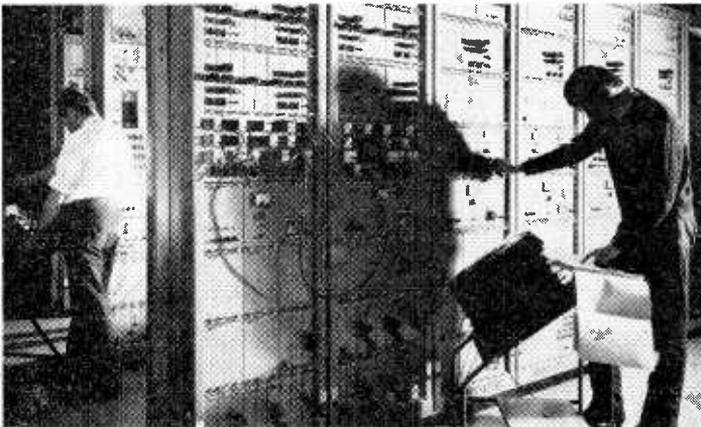

Automatic error-correcting telegraph equipment has been installed by The Marconi Company at the GPO's Fleet Building Telegraph Centre, the largest of its kind in the world. Situated in the heart of London, the equipment will provide for a substantial increase in the traffic handling capacity of radio telegraph services. Already the telex calls through Fleet Building exceed the total overseas telephone traffic from the whole of the United Kingdom, and the telex service is still expanding.

The photograph shows the Marconi equipment, which is known as Autoplex, undergoing final acceptance tests at the GPO's Telegraph Centre.

Autoplex is completely transistorised and housed in tall slim racks. At Fleet Building, 36 of these have been installed, increasing the centres radio-telegraph capacity to 296 circuits, each capable of carrying four separate telegraph links.

No news is good news

YOUR editorial and four-column article on the prosecution of pirate radio stations was a waste of space. Everyone interested had heard the outcome on radio, TV and read it in newspapers long beforehand.

I'm not against editorial comment about such issues, after all that is what maintains a magazine's individuality, but a full account and a promise of another detailed case is too much. The space could have been put to better use as constructional articles.

If this is going to be the future policy of P.W. how about the prosecutions of "ham" pirates, not to mention a sound version of Underneath the Dipole (from P.T.)?

A far better policy would be to refuse advertised non-convertible 27 Mc/s walkie talkie spreads unless boldly indicated as such.

I.N.R.W. Newport.

New Marston,
Oxford.

[Although we cannot obviously compete with newspapers in reporting news items we feel it is reasonable to devote some space to important happenings in the radio world. A newspaper is usually thrown away after reading, whereas most readers retain their copies of hobby magazines. This provides a useful reference source for the future.]

With regard to 27 Mc/s walkie-talkies, readers can be left in no doubt of our feelings on this point. Advertisers are asked to state that such equipment cannot be used in the U.K. (for P.W. has a worldwide circulation, including countries where C.B. facilities are available). For the benefit of those who may still be unaware of the facts may we again point out that the use of 27 Mc/s walkie-talkies for communications purposes (however limited the range) is strictly illegal and renders the user liable to prosecution]—Editor.

Club spot


I would like to say how much I enjoy reading the Club Spot feature in this magazine. It is very useful to members of other clubs as it shows the activities that can be enjoyed from club membership and gives club committees ideas for their own organisations.

Brian Smith.

Ilford,
Essex.

[We are pleased to hear that you enjoy the Club Spot feature. We would like to take this opportunity to appeal to clubs to send in information about themselves together with one or two photographs of QTH's and/or members and equipment. All will be considered for publication.]—Editor.

More News and Comment on Page 844

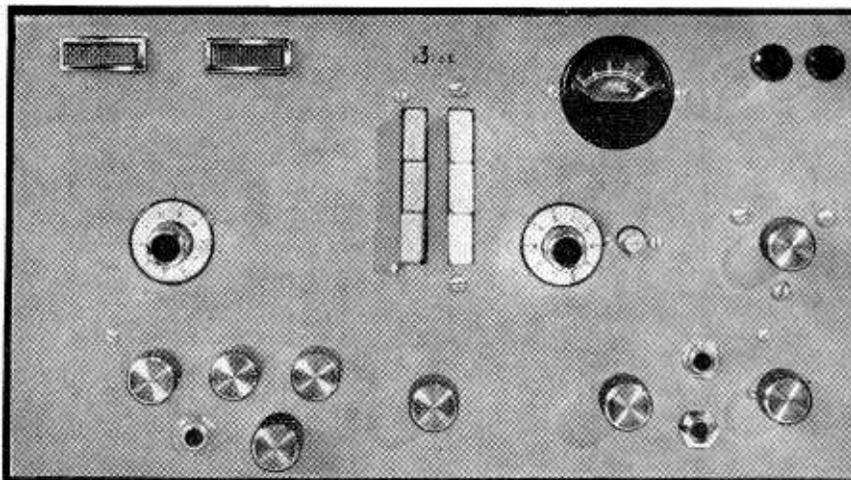

TOP BAND TRANSCEIVER

BY

T. SIMON



THE trend in amateur circles these days is toward compact units as opposed to the huge rack and panel arrangements of earlier years.

In a multi-band transmitter running 150W, it becomes necessary to "loose" 140W if topband is to be included and the 10W power limit observed. The unit to be described is based on observing the first statement above, while avoiding all the complications implied by the second.

The cheapest commercial topband transmitter on the market sells at around £15 and then requires the additional expense of a power supply. The unit described here cost less than £15 to construct and is not merely a transmitter. This price included the power supply unit; built-in frequency marker including crystal; and a receiver to boot. Briefly, the unit comprises a complete self-contained phone/c.w. station for the 1.8—2.0Mc/s amateur band, occupying a space $12 \times 6\frac{1}{2} \times 4\frac{1}{2}$ in. It is based on economy and simplicity and uses only six valves, two in the transmitter, one in the modulator, and three in the receiver.

The circuit diagrams of the complete unit are divided into two sections; transmitter, and receiver plus power unit. Thus just the transmitter could be built, this would form the basis of a useful miniature topband rig, or just the receiver portion might be constructed, this being of particular interest to s.w.l.'s., and again the unit could be very small indeed.

Receiver Circuitry

This section of the unit employs three valves all Mullard type EFC82/6U8. The aerial input circuit ignores the coupling winding on L1 and the coil is top-capacity coupled to the transmitter tank circuit via C49 and S1e on the T/R switch. In this way the extra stage of selectivity afforded by the tank circuit is utilised on receive. In the writer's area there is strong break-through from the BBC at Brookmans Park (908kc/s 2nd harmonic). This is entirely eliminated by the tank circuit which peaks quite sharply.

V1 is a standard frequency changer circuit but with the inclusion of an extra potentiometer in the cathode of the pentode section. The original idea was to provide variable mute on transmit in order

to monitor one's transmissions on the receiver, but due to the very close proximity of the transmitter this does not function quite as well as was hoped, and the substitution of a fixed resistor of some 10k Ω should prove adequate. An alternative would be complete screening of the receiver section—a complication which did not justify the effort required since the simple arrangement shown does work tolerably well. On receive, the T/R switch shorts the muting resistor to earth via S1a and the circuit functions as a normal frequency changer.

The pentode sections of V2 and V3 are used as i.f. amplifiers at 465kc/s whose gain is effectively controlled by VR2. These stages are quite stable providing the anode and screen volts are not too high, hence the larger than usual values of the screen resistors R7, R12. In the prototype the optimum valves for R7/R12 were found to be 82k Ω , however to allow for different layouts, etc., it was considered safer to specify the values shown in Fig. 1. The values quoted are for maximum gain consistent with stability, however, if it is found that on peaking the i.f.t. cores the circuit becomes unstable, then it is better to drop the h.t. to the i.f. stages rather than leave the i.f.t.'s. slightly off tune. If this latter procedure is adopted the receiver will work but the selectivity will suffer.

The triode of V2 is a straightforward audio amplifier fed from the diode detector D1. The triode section of V3 functions as a b.f.o. with VC2 as a pitch control for resolving s.s.b. and c.w. while S2 switches the b.f.o. out for a.m. reception. The high value decoupling and load resistors R10/R11, and the consequent low volts on the anode of V3b were found to be a necessity. Even with two 47k Ω resistors here there was still too much b.f.o. injection. Also note there is no b.f.o. coupling capacitor as such. This proved to be superfluous presumably due to the coupling afforded by the inter-electrode capacity within the valve V3 itself.

Transmitter Circuitry

This section utilises the remaining three valves in which the first stage comprises another ECF82/6U8 as a Clapp v.f.o. and tuned buffer-amplifier/crystal oscillator (V5).

The v.f.o. is cathode coupled to the buffer stage

via the v.f.o. crystal switch S6. With this switch depressed the v.f.o. output is disconnected and the pentode section resonates at 1.9Mc/s thus forming a frequency meter giving a marker right in the centre of the band. It might be possible to use a 100kc/s crystal and get a 1.9Mc/s point plus two very useful band-edge points on 1.8 and 2.0Mc/s but this idea has not been tried.

The p.a. V6 is a 5763, this valve merely because it happened to be in the junk box. Other suitable valves would be the 6BW6 or 6AQ5. Note alternative valves might require adjustment of circuit values, and some are B7G bases not B9A as for the 5763.

Departure from the time honoured pi-tank might shock some, since this has become almost an accepted standard. However the present system does permit odd lengths of wire presenting all sorts of impedances to be matched quite precisely and accurately. Those who still prefer a pi-tank might

p.a. valve to limit the anode current to a safe value during the key-up periods, when there would otherwise be no bias (due to there being no drive) on the 5763 or p.a. valve used. If the v.f.o. were keyed, the buffer amplifier would also require cathode bias, or some means of protection during key-up.

The modulator section V4, provides frequency modulation and uses the two triodes of a 12AX7 in cascade. Doubtless one section might prove sufficient, but with two stages the QSO can be conducted in a confidential whisper with the mike gain half way up. Frequency modulation was chosen mainly because of the modest requirements both in circuitry and components, not to mention its tendency *not* to aggravate t.v.i. as opposed to, say, amplitude modulation. A class A audio amplifier suitable for a.m. would be required to produce around 5 watts of audio with attendant consumption of some 40-50mA of h.t. current plus the heavy and somewhat bulky modulation choke or

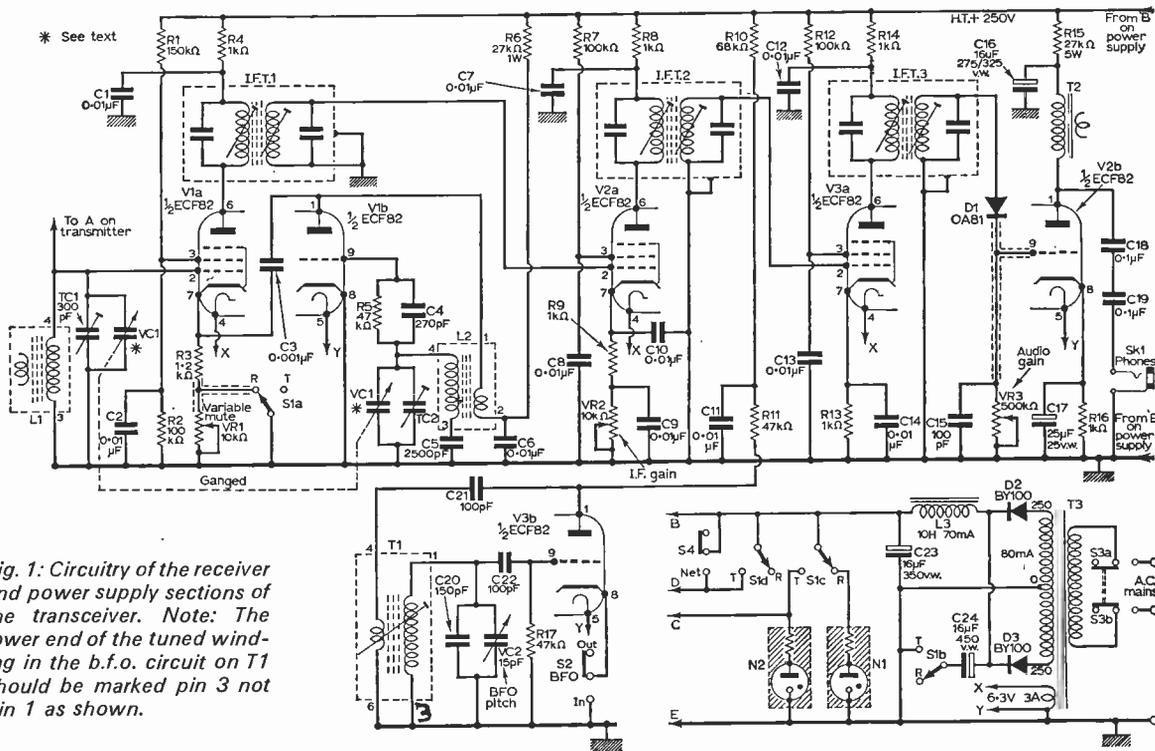


Fig. 1: Circuitry of the receiver and power supply sections of the transceiver. Note: The lower end of the tuned winding in the b.f.o. circuit on T1 should be marked pin 3 not pin 1 as shown.

substitute a 500 + 500 pF variable capacitor, both sections in parallel, for the tank coil tapping switch S7. Due allowance for this should be made in the layout and size of chassis when planning. If this procedure is adopted then VC4 would also benefit from being a higher value, say 200-300pF. In the event of very short antennas such as whips being used, then the 500 + 500pF suggested for the pi-tank modification would benefit from being increased by the inclusion of a 1,000pF capacitor wired in parallel.

The transmitter is keyed in the cathode of the p.a. since this method has proved satisfactory in the past. If keying is inserted in the buffer or v.f.o. then a bias resistor and decoupling capacitor should be included in the cathode return of the

transformer. The 12AX7 on the other hand consumes but a few mA, thus one gets a bonus of being able to use a much smaller mains transformer, less complex circuitry, and fewer components. There has, to date, been no sign of t.v.i. at any time with the prototype.

The input circuit is intended for a crystal mike and although the input impedance is not matched, the 500kΩ pot. VR4 being an abnormally low value for a crystal mike, there is sufficient gain and the speech quality is quite good. The 100pF capacitor across the mike input is included to avoid the BBC being re-radiated due to the mike lead acting as an aerial. The 500kΩ audio gain control is really a luxury, as once set for a particular mike it requires very little adjustment, thus a fixed resistor

could be substituted if desired. The value will depend on the particular mike used, but around 330k Ω would be a good starting point for most crystal mikes.

The modulator receives its h.t. supply whenever

In the prototype design the place now occupied by the crystal held two 85A2 stabiliser valves wired in series to provide 85 volts stabilised to the v.f.o. and buffer screen, and 170 volts stabilised to the buffer anode. The v.f.o. tuned 900kc/s-1Mc/s,

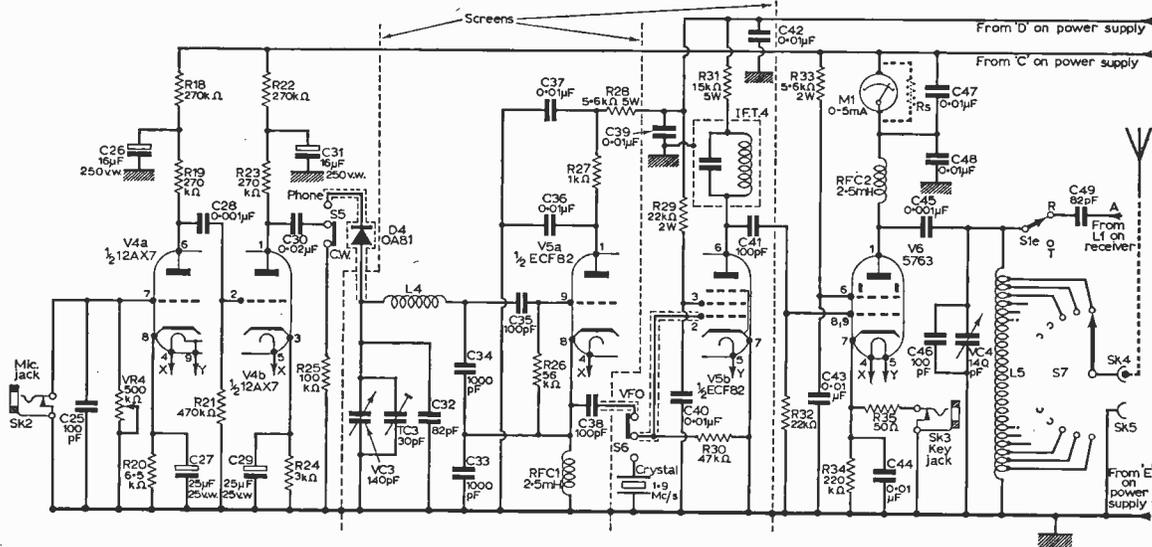


Fig. 2: Circuit of the transmitter and modulator sections. Note complete screening of the modulator diode.

the T/R switch S1c is in the transmit position, but it is not coupled to the transmitter until the phone c.w. switch S5 is depressed.

Although the p.a. tuning capacitor and the modulator section are in the same compartment and are not screened from each other, there is no interaction nor any trace of feedback.

Power Supply Circuitry

This scarcely needs any comment since it boasts well proven circuitry with little originality, consisting of standard full-wave rectification with choke or capacity input.

and its anode load consisted of a 1.6Mc/s i.f.t. modified to form a wide-band coupler. The buffer anode also had one of these and the system worked extremely well. However once the p.a. was brought in, there was so much r.f. in so small a space that the p.a. just could not be tamed. Those who prefer this arrangement might consider using a slightly larger case to allow better screening and improved layout. The stability of the present v.f.o. tuning 1.8-2.0Mc/s was found quite adequate without any stabilisation, thus the 85A2's were omitted.

The two neons in the power unit illuminate to show immediately on the front panel whether the station is on transmit or receive. For those build-

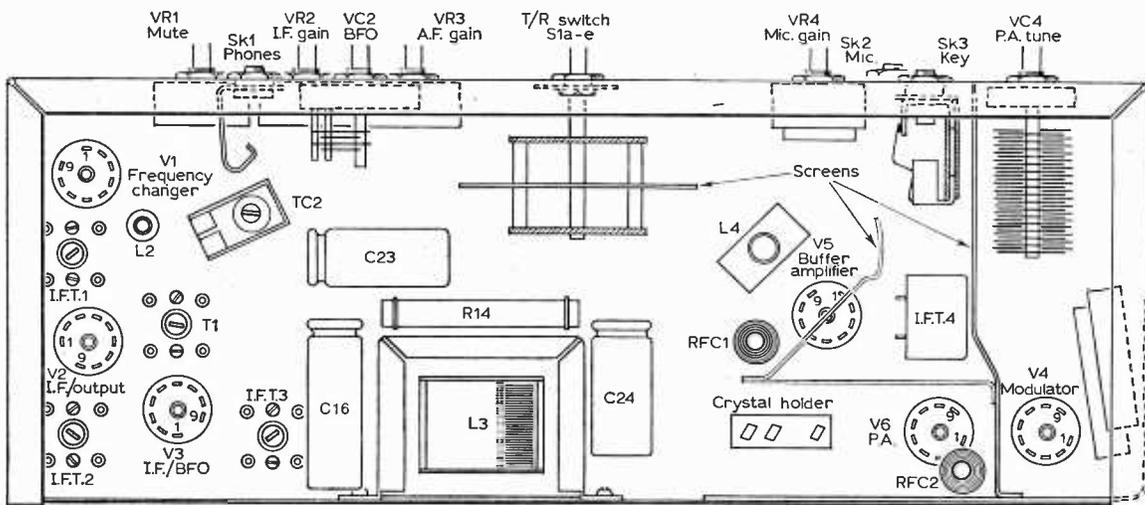


Fig. 3: Under chassis view showing positioning of main components and screens.

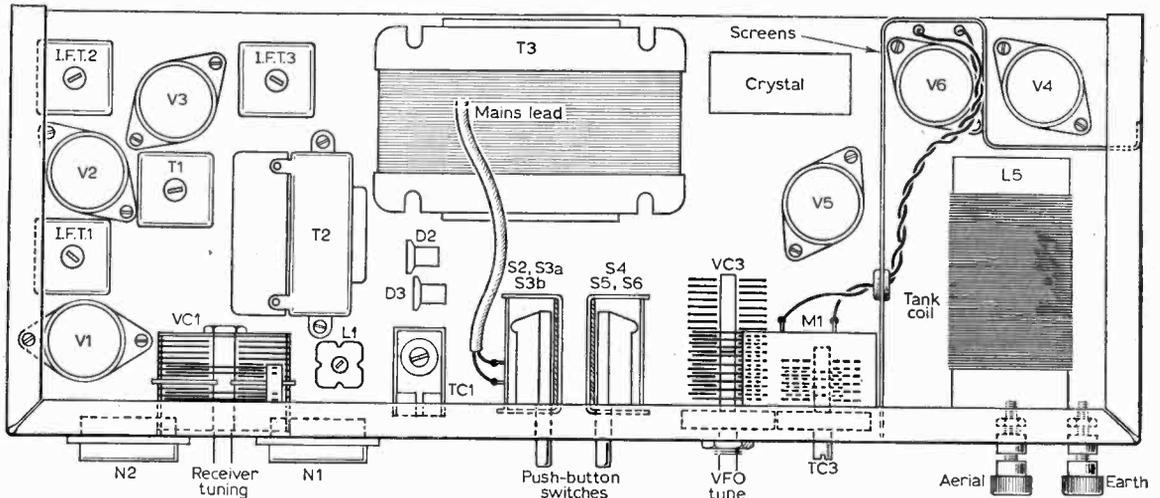


Fig. 4: Layout of the main components above chassis. Smaller items omitted for clarity

ing the rig, a fuse from the mains transformer centre tap to earth is strongly recommended, perhaps on the front panel in place of the variable mute control or the mike gain pot. VR4.


None of the components in the power section are unduly critical, for example any choke that will fit in will suffice from 8-20H providing it is capable of passing some 70mA. A 60mA component might tend to run a little warm.

It is not advisable to use a larger value electrolytic for C24, 16 μ F being considered rather high by some and 8 μ F is perhaps a safer value. It will be noted that on receive the power unit uses choke input, whereas on transmit, capacitor input is used by switching in C24 via S1b on the T/R switch in order to obtain a higher h.t. voltage. This is optional and if preferred choke input can be successfully employed on both functions. In addition to switching the neons the T/R switch also provides h.t. to the p.a. and modulator via S1c, and

h.t. to the v.f.o./b.a. via S1d. When the T/R switch is in the receive position, the Net switch, when depressed, supplies h.t. to the v.f.o. and buffer stages. This allows the operator to zero beat the v.f.o. with an incoming signal on the receiver without radiating a note which could annoy others. (V.F.O. swishers please note.) This facility also allows the crystal oscillator to be used to line up the receiver dial. Also, if the transmitter is now zero beat with the note from the crystal oscillator, it is possible to line up the transmitter dial at the same time.

Next month, the layout and constructional details will be given, and would-be constructors are urged to wait for these before attempting construction as certain snags could arise which can be avoided if they are known in advance.

to be continued

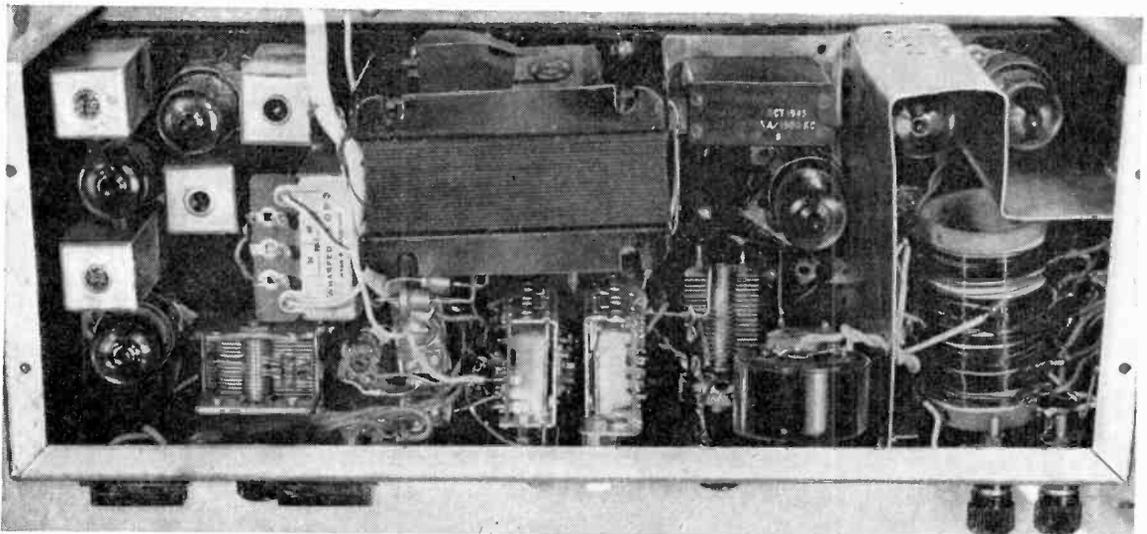

Photograph of the top chassis. Compare this with Fig. 4 above. Receiver section is on the left, transmitter and modulator on the right, power supply in the centre.

BALANCE CONTROLS

for stereo amplifiers

By J. B. Willmott


ADDDING a stereo balance control unit to a hi-fi installation often improves the end product. It is not readily appreciated that a pair of amplifiers of the same make and type do not necessarily have the same gain characteristics. Nor, for that matter, do the other links in the chain (such as loudspeakers, preamplifiers, microphones, etc.) of the same make and type always match up. In order to overcome this difficulty, one can adjust the individual controls of the main amplifiers, but this is rather a clumsy way of doing things when it is relatively simple to add a balance control which will increase the gain of one amplifier and at the same time reduce the gain of the other.

Nine different circuits are touched upon in this article. This is by no means all, but should fire the imagination of the serious constructor and give the novice a good insight.

Before considering the various circuits, one must also appreciate that environment is important. Most hi-fi installations are accommodated in rooms that are not acoustically perfect, and the positioning of the loudspeakers in relation to the furnishings can have a marked effect on the end product. Also it is worth considering your own hearing; possibly that is not perfectly balanced. So to obtain the best results, why not let your ears be the judge?

SUGGESTED CIRCUITS

Possibly the simplest system of all is that shown in Fig. 1, in which the the gain of channel "A" is made variable by the insertion of a 100k Ω potentiometer, in place of the 47k Ω fixed resistor used in the same position in channel "B". However, it may be found that there is insufficient variation of gain of channel "A" to achieve balance under certain conditions. In Fig. 2 use is made of a twin-gang potentiometer wired up so

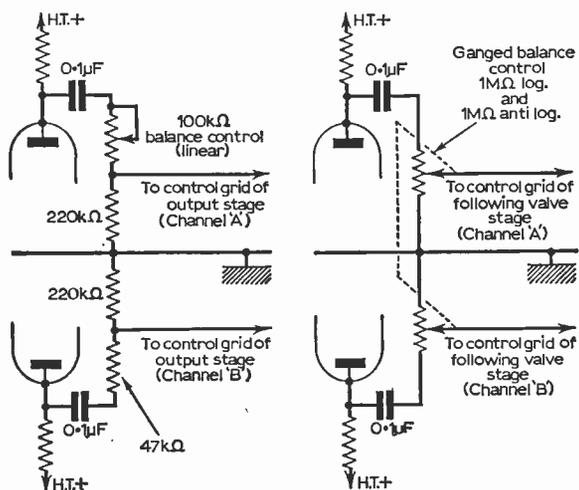

that channels "A" and "B" are controlled in reverse (i.e., as the gain of one channel is increased, that of the other is correspondingly decreased). This, however, requires the use of a specially designed twin potentiometer, known as "log./anti-log.," obtainable from most component suppliers. The advantage of this system is that either channel can be reduced to "zero" (with a corresponding rise to maximum gain in the other channel) so that even the most widely differing output requirements can be met, the only drawback is that at no setting of the control can both channels be working at full gain simultaneously.


Figure 3 depicts a very simple but effective inter-stage control of balance, in which only a single linear law 1M Ω potentiometer is used. The slider of this control is connected to earth (chassis) line, and the control grids of the following valve stages are fed from the "top" and "bottom" of this same potentiometer. Note the inclusion of 47k Ω resistors in the grid leads to each of the subsequent valves. These should be connected as close as possible to the valveholder grid tag; the components serve as grid stoppers (reducing the danger of instability) and prevent the control grid of the succeeding valve from being connected directly to chassis (and thus cutting off grid bias) should the balance control be adjusted to the limit of its setting in either direction. Component values of the cathode bias resistor and capacitor are not shown, as these will depend on the type of valve employed in the output stages. With the popular EL84, suitable values would be 150 Ω and 25 μ F (25 VW). The previous valve stage can be any high or medium impedance triode (or the two halves of a double triode such as an ECC83).

By way of a change, Fig. 3 shows a circuit for incorporation directly across the pick-up, and for sake of completeness, the associated volume and tone (top cut) controls are included in

Fig. 1 (far left): Simple form of balance control.

Fig. 2 (near left): A ganged log./anti-log. potentiometer is needed for this circuit.

Fig. 3 (right): A single linear potentiometer is used in this circuit to vary the bias to the p.a. valves.

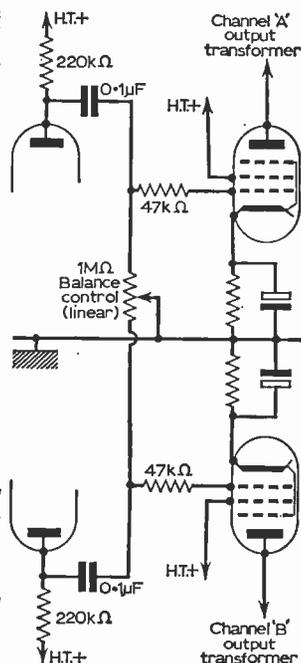


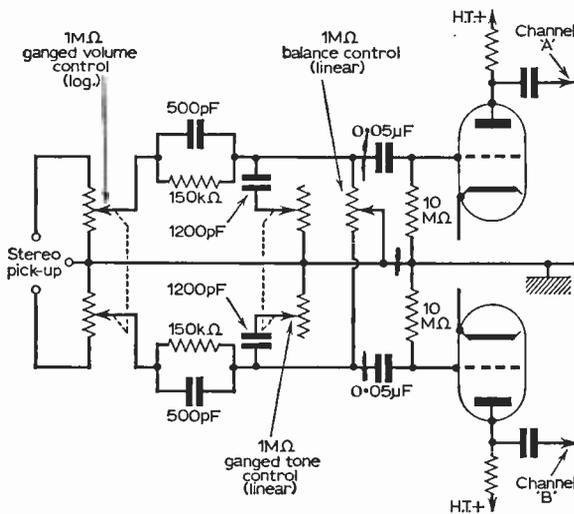
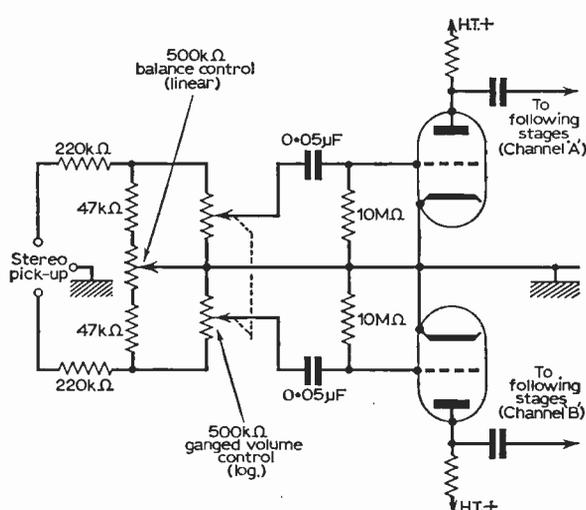
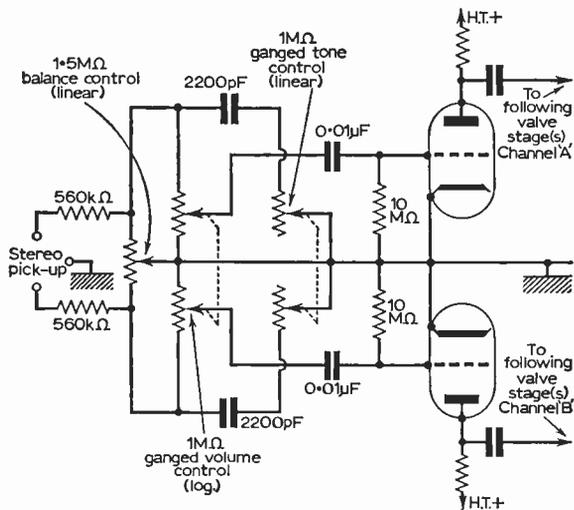


Fig. 4 (top left): Tone and volume controls are included in this circuit which balances the signals at the pick-up.

Fig. 5 (top right): Another circuit in which the signals are balanced before being amplified.

Fig. 6 (lower left): In this circuit the tone and volume controls are also directly connected across the pick-up.

Fig. 7 (lower right): Part of the signal is shunted through the h.t. rail to achieve balance.

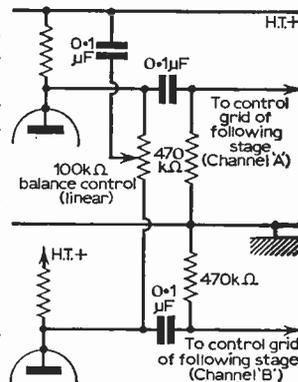

the circuit diagram. The system would be ideally suited to a simple inexpensive two stage amplifier. Note that the grid bias for the first valve stage is provided by the voltage resulting from the minute grid current flow through the high value grid leak resistor (10MΩ). No cathode bias components are then required for this stage, and this system works very well indeed in stages where the signal level is quite low. The component values suggested have been used by the author in an amplifier fed from a crystal pick-up in a B.S.R. "Monarch" auto-changer unit, and should suit any of the popular crystal pick-ups in the modest price range.

A further circuit suitable for insertion directly across the pick-up is shown in Fig. 4. In this circuit, the tone controls, either a simple "top cut" or more elaborate separate Bass and Treble, would be incorporated in the coupling between the valve stage shown and that following.

As in the previous circuit, bias for the first valve is obtained through a high value grid leak resistor. The component values of the anode load resistors and coupling capacitors to the following stage are not given, as these will vary according to the type of valve employed. Practically any

triode or pentode valve can be used, but for convenience, the use of one half of a double triode (such as an ECC83 or 6SL7) in each channel is recommended.

Another design eminently suitable for two stage audio amplifiers is shown in Fig. 6. In this arrangement the volume and "top-cut" tone controls are connected directly across the pick-up (which with the component values suggested, should be of the high output crystal type referred to earlier), followed by the balance control, which is a 1MΩ linear potentiometer. The 500pF capacitor paralleled by a 150kΩ resistor (in between the volume control slider and the coupling to the grid of the first valve in each channel) are inserted to provide a degree of frequency correction from the pick-up.

Figure 7 and the following two circuits, represent a less conventional approach to the control of balance. In the first circuit, the 0.1μF capacitor connected to the slider of the balance control (100kΩ linear), shunts a proportion of the audio signal away from the following stage to the h.t. line, and eventually via the power supply smoothing capacitor, to "earth". The proportion of signal so by-passed depends on the position of the balance control slider; movement of this decreases the signal passed on from channel "A", for example, at the same time as increasing that passed on from channel "B", or vice versa. Whereas all the

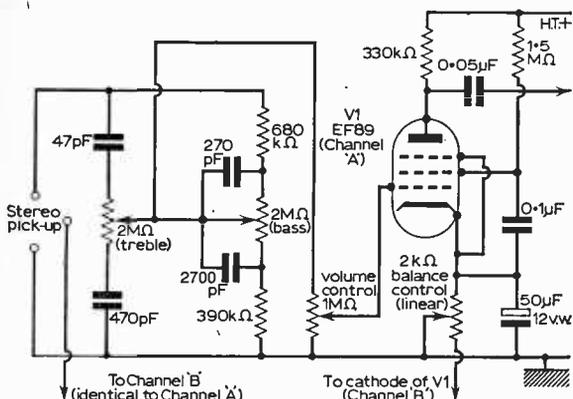



Fig. 8 (above): This circuit shows how it is possible to vary gain using vari-mu valves.

Fig. 9 (right): The level of negative feedback is varied to achieve balance in this circuit.

Note: The Channel 'B' circuits to match those given in Figs. 8 and 9 are identical, with the volume and tone controls ganged with those of Channel 'A'.

previous circuits have made use of potentiometers varying the signal strength fed between one valve and the next, or between pick-up and first amplifier valve stage, Fig. 8 shows how it is possible to vary the gain of an amplifier with vari-mu valves. This is, of course, common practice in r.f. and i.f. circuitry in radio receivers; it is not always realised that vari-mu valves can, in certain circumstances, be used in audio frequency circuits. The main proviso is that the signal level should be fairly low, as any attempt to deal with large swings of signal voltage in a vari-mu valve will introduce an intolerable level of distortion. However, if such a valve is used at low signal level, quite satisfactory control of gain can be secured by varying the grid bias. In the example shown, the author used EF89 valves, with very satisfactory results. Bass, treble and volume controls are shown and the circuit will give all the necessary controls for an inexpensive stereo amplifier. A valve such as the popular EL84 could follow the EF89's in each channel, and would provide some 4 watts output. The actual control of balance is provided by the 2kΩ linear wirewound potentiometer, which should have a rating of about 5 watts. The slider is connected to chassis, and variation of its setting will vary the bias between wide limits. *One word of warning*, operation of the amplifier with the balance control set at the extreme ends of its track will leave one valve with zero bias, and if operated for any length of time in this position, will damage the valve. This can be avoided, if thought necessary, by inserting a fixed value resistor of say 100Ω between each valve cathode and the balance control.

There is another method of varying the gain of an amplifier, Fig. 9, and that is by adjusting the amount of negative feedback. In the example shown, the balance control is a 100Ω wirewound potentiometer inserted between the junction of the negative feedback line (the 2.2kΩ resistor from output transformer secondary to the lower end of the cathode bias resistor of the first valve stage) and chassis. Variation in the setting of this control

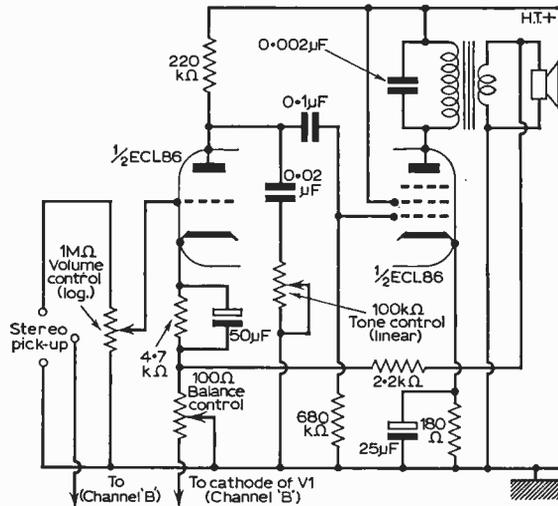

changes the amount of negative feedback applied; it will be seen that both channels are controlled simultaneously, but in an inverse manner, i.e., increased feedback in channel "A" would be accompanied by simultaneous decreased feedback in channel "B", and vice versa. The purist will no doubt exclaim that variation in negative feedback not only varies the gain of an amplifier, but also affects the frequency response; a greater degree of feedback giving a better low frequency response, so that relative volume levels will be controlled. This does not appear to have any serious effect in practice, at any rate in amplifiers in the inexpensive class. Indeed a system similar to this has been used by a number of commercial manufacturers of stereograms. The circuit diagram represents one complete channel of a stereo amplifier, using the two halves of an ECL86 valve; the second channel is identical, and only a power supply is needed to complete the equipment. As in all circuits using negative feedback, it is important to ensure that the feedback is correctly phased, otherwise positive feedback, resulting in uncontrollable oscillation, will result. The amplifier should be first constructed with the connections to the secondary of the output transformer (other than the speaker speech coil of course) omitted, and once tested and found to be working satisfactorily, the earth and feedback connections can be made temporarily to the output transformer secondary. If an uncontrollable howling results, the connections to the output transformer should be reversed.

One word of warning, the control potentiometers used should be of first class manufacture, and in the case of "ganged" components, must be properly matched during manufacture. Cheap surplus, or salvaged, potentiometers just will not do; they will lead to more annoying intermittent faults and noisy operation and can ruin the enjoyment of reproduction from an otherwise impeccable amplifier system.

Finally, don't let your enthusiasm for straining your ears to hear every grain of "movement" hamper your enjoyment of listening to stereo recordings. Get your tone and balance controls adjusted to your liking, and then leave them well alone.



I should like a copy of the *Electroniques Hobbies Manual*.
Enclosed is a cheque/P.O. for 10/6.

NAME


ADDRESS

PW.3

Two items from the *Electroniques Manual*...

Brilliant Valved 'QOILPAX'

● Highly sensitive ($1\mu\text{V}$ for 15dB S/N ratio when followed by a normal IF Strip) ● High-sensitivity RF stage is designed around EF 183, connected in a Miller compensating circuit, followed by an ECH81 triode heptode frequency changer, using oscillator circuits. These give optimum mixing conductance on each waveband without any pulling. Each oscillator not in use is shorted out ● General coverage and hamband models available both designed for an IF output of 1620 Kc/s ● Exceptionally low second channel

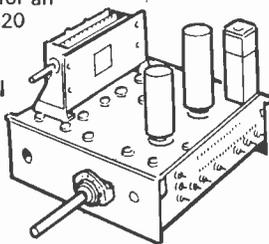

interference ● Units are completely wired, tested and aligned.

Both Models: £12.12.0 each complete p.p. 4/-.


Today's most advanced aerial rotator

● Aims within ONE DEGREE of transmitter location ● Twin synchronised motors ● No guesswork, no irritating gear-clicks. Precise fine adjustment through 365° location ● Continuous Instant Direction Indication—even when motor is not in use ● Accurate repeatability—aerial position can always be pinpointed ● Turns the heaviest arrays easily under ALL weather conditions.

Price Automatic Model: £17.17.0.

Compass Model: £12.12.0 + p.p. 3/6.

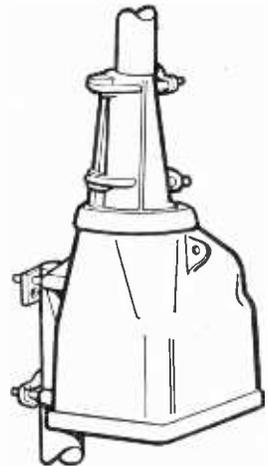
Electroniques (Prop. STC Ltd.)
Edinburgh Way, Harlow, Essex.
Telephone: Harlow 26777.



High-grade components for amateur communications

electroniques

HIGH QUALITY

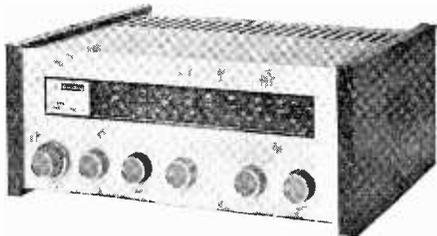

LOWER COST

Combine an Armstrong Tuner and Amplifier and you have all the advantages of separate units, plus compactness, easier installation, and equivalent performance at a lower price.

Stereo model 127, above, derived from the more expensive 227, has an identical AM-FM tuner section, with an amplifier section designed for those whose power requirements are more modest.

It has a more modest price too, as does the mono version model 127M.

Each Armstrong Tuner-Amplifier is ideal as the basis of a high fidelity system for radio and record reproduction tape recording, and playback, and each unit may be built into your own cabinet or used in our optional case, of teak and vinyl hide, as shown.

For full details and technical specifications of all models plus list of over 300 stockists, post coupon or write mentioning 3PW67.

- model 127 STEREO TUNER AMPLIFIER £39.10.0
- model 127M MONO TUNER AMPLIFIER £29.10.0
- optional case £3.10.0



ARMSTRONG AUDIO LTD. WARLTERS ROAD, N.7
Telephone: NORTH 3213

Name

Address

.....

3PW67

TRAIN AS A TECHNICIAN

If you are aged 17-25, here's your chance to train as one of the Army's top technicians in:

ELECTRONICS or AIRCRAFT

Your 18-month technical training course will take you up to City and Guilds standard. Six months after completing the course successfully you are promoted to Corporal. Then it's up to you! Promotion's wide open in the technical field today!

You'll be working on the exciting and advanced equipment today's Army uses when it swings into action: radio transmitters, closed circuit TV, gunfire control equipment, radio transceivers, helicopters.

There are also opportunities for young men aged 15-17 to join as Junior Entrants and train as technicians or tradesmen.

GOOD PAY!

This year every soldier in the Army is better off. Trainee Technicians get £477 a year from age 17—and all your food and lodging are free! At the end of 18 months, your pay will go up automatically to £714; at the end of two years, to £805! From there, you'll be given every chance to work for promotion and *still* better pay.

WANT TO KNOW MORE? SEND OFF THE COUPON TODAY!

TO: ARMY CAREERS MP6(A),
LANSDOWNE HOUSE, LONDON W.1
Please send me full details of how to become a Technician

NAME

ADDRESS

TOWN

COUNTY

DATE OF BIRTH

M221402 *(You must be resident in the UK)*

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times in GMT
Frequencies in kc/s

THE BROADCAST BANDS

by JOHN GUTTRIDGE

EUROPE

Denmark: *Radio Denmark* (Shortwave Department, Radio House, Copenhagen V) now transmits on 15,165 to South America in Danish at 1600-1645 and Spanish at 1645-1715.

German Federal Republic: *Deutsche Welle* (Brueckerstrasse 1, Postfach 344, 5 Köln) has made changes recently:—the following English transmissions: 0300-0345 7,160/9,530; 1550-1630 11,765/9,535; 0130-0250 9,735.

German Democratic Republic: *Radio Berlin International* (116 Berlin Nalepastrasse 18-50) now uses 1,430 / 6,080 / 6,115 / 7,185 / 7,300 for the 2200-2230 English transmission.

Radio Volga (Menzelstrasse 5, Potsdam) is now using shortwave as well as the 263 long wave outlet. Has been heard in Russia in evening on 9,680.

Italy: R.A.I. (Via del Babuino 9, Rome) now uses following outlets for English transmissions: 2115-2135 (Europe) 7,240/6,050; 2205-2225 9,710/6,010; 2020-2040 7,265/5,990; 0100-0120 9,630/6,010. New languages introduced are Maltese 1225-1230 on 9,575/7,235 and Amharic 2020-2040 15,150/11,810/9,570.

Norway: *Radio Norway* (Oslo) now using two 11 m.b. outlets. Schedule is 0300-0430 9,550/9,610/11,850/1,578; 0700-0830 21,670/11,850/9,610/17,825/25,900; 1100-1230 9,610/11,850/21,730/25,730/25,900; 1300-1430 21,670/21,630/17,825/25,730/25,900; 1500-1630 21,670/15,175/17,825/25,730/21,730; 1700-1830 21,670/15,175/17,825/11,850; 1900-2030 11,850/15,175/9,610/21,670/21,730; 2100-2230 11,850/9,610/11,735; 2300-0030 11,850/9,550/9,610.

Poland: *Radio Warsaw* (Al Niepodleglosci 75/77, Warsaw) now transmits in English as follows: To Europe 1830-1857 7,145/6,135; 1930-2000 9,540/7,145/6,135/1,502; 2030-2100 7,125/5,950; 2130-2155 7,145/6,135; 2230-2300 5,950/9,540/1,502; 2303-2330 818; To Africa 1200-1230 and 1300-1330 7,145/11,840/15,275; to Australasia 0730-0800 and 0830-0900 9,675/11,840/15,275.

Rumania: *Radio Bucharest* (P.O.B. III, Bucharest) now has six new QSL cards which may be obtained by sending six reception reports numbered one to six.

Sweden: *Radio Sweden* (Box 955, Stockholm 1) has completely revised English schedule which includes use of 13 m.b. for first time. Times and frequencies are 0900-0930 6,065/21,690; 1100-1130 6,065/9,705; 1230-1300 9,705/21,690; 1400-1420 11,810/17,840; 1600-1630 11,705/17,840; 1900-1930 6,065/11,705; 2245-2315 7,270 11,705; 0030-0100, 0200-0230, 0330-0400 5,990; 0515-0545 11,705; 2015-2045 6,065/11,705; 2330-2400 1,178.

U.S.S.R.: *Radio Moscow*. There is a new service entitled "Radio Station Peace and Progress, the Voice of Soviet Opinion". Programmes are English 0900-1000 and French 1000-1030 on 12,060/15,200/15,360/15,450/17,710/17,795.

Radio Minsk (Minsk) may be heard in Bielorrussian from 2130-2200 on 5,940.

Yugoslavia: *Radio Belgrade* (2 Hilendrska, Belgrade) now using 6,100/7,200 only for the 1830-1900 English transmission.

AFRICA

Cape Verde Islands: *Radio Clube de Cabo Verde* (Casilla Postale 26, Praia) gives good reception on 3,883 in Portuguese 2000-2200.

Ethiopia: *Radio Voice of the Gospel* (P.O. Box 654, Addis Ababa) has changed the following English transmissions recently: 1345-1400 15,315; 1900-1910 9,705; 0430-0455 11,810; 0530-0555 11,785; 1655-1710 6,065; 1900-1945 15,115; 1630-1645 11,925; 1755-1810 9,565.

Morocco: *Radiodiffusion Television Marocaine* (1 Piere Paient, Rabat) now transmits English at 1800-1900 over 15,408.

Voice of America relay, Tangier (Washington 25, D.C., U.S.A.) now using the new outlet of 9,660 to Eastern Europe.

Nigeria: *Nigerian Broadcasting Corporation* (Broadcasting House, Lagos) now carrying foreign service from 1300-2200 over 7,275/9,690/11,900. English is at 1500-1600, 1700-1900, and 2100-2200.

Rwanda: *La Voix de l'lem Fé* (Kigali) broadcasts from 2000-2200 over 9,575/11,715 in French.

South Africa: *Radio South Africa* (P.O. Box 8606, Johannesburg) has replaced 15,205 by 15,215 for the 2200-2255 European English transmission. Other frequencies are 9,720/11,785.

Tanzania: *Radio Tanzania* (Box 9191 Dar es Salaam). Test transmissions over a 240kW transmitter have been reported as follows 0930-1000 21,600; 1000-1300 15,435; 1530-1600. Reports are wanted. It is believed a regular service may now be in operation.

ASIA

Saudi Arabia: Saudi Arabian Broadcasting (Ministry of Information, Airport Road, Jeddah) is now using 9,670 after the scheduled 2100 close down time.

Ceylon: *Radio Ceylon* (Department of Broadcasting, P.O. Box 574, Colombo 7) broadcasts in its External Service as follows: 0700-0815 to Europe, West Africa and Middle East on 15,330; 0915-1030 to South Asia on 17,850. The station is considering changing the times of its broadcasts and would appreciate listeners' views. QSL cards for the station commercial service may be obtained from Radio Advertising Services (Radio Ceylon) Cecil Court, Lansdowne Road, Bombay, India.

News was received this month from J. D. Ashworth, T. Ibbitson, D. Hobro, S. L. Brunt, A. B. Thompson, World Communications Club of G.B., P. Quin, International Short Wave Club, J. N. Newport, Radio New York Worldwide, Swiss Broadcasting Corporation W. E. Bartlett J. W. Smith S. Ormerod.

ONE puzzling question posed to experts and laymen alike is "Where do all the flies go in the wintertime?". Variations on a theme now prompt me to enquire "Where do all the s.w.l.'s go at Christmas?". Either nobody listened, or else you've all gone shy and are not going to confess to Auntie Dave what you got up to in the festive season. Only a handful of letters in the postbag this month (sobs quietly into dirty hanky), so let's hope you are all saving those lovely logs for next month.

Top band has been surprisingly good at times and GDX has been about at quite good signal strength. GM stations and the North and Midlands have been heard near London at 5 and 6 on a.m. phone. Topband addicts might be interested to hear that G3JDG is now mobile/M on 160 and many Northern stations have been received on the loaded whip.

Frank Videan (St Albans) AR88, long wire, listened on 160 in the wee small hours. His log for the period 0103-0630 however is certainly neither wee nor small—DJ4SS, HB9CM, OK2KHF, OL9-KRA, PAØPN, VP6TK, W1HGT, W1BTK, W8A-NO, ZD8J, 9H1AE. Who said 160 has had it? When one considers that these stations were received through fish-phone, Loran, v.f.o. swishers and all the other noise on 160, it's a very fine effort indeed.

Mc/s Mixture

Often an s.w.l. will send in a log for several bands, and in order to get in as many logs as possible I usually take one or perhaps two bands from each report. This month however, I thought I'd put in the complete log, just to show how seriously and diligently some s.w.l.'s listen.

Robert Iball (Notts), AR88D, 80ft. top and 35ft. of 72Ω co-ax feeder running S/N. Bob skimmed just the cream from his logs and offers—1.8 Mc/s—K8CRJ, K8HKB, K8RRH, K9PAW, OE5KE, VE3-BWY, VO1FB, W1BHQ, W1HGT, W1WY, W2FYT, WA8EMJ, W8GDQ, W8HGW. 3.5Mc/s—VE2BZL, W4YWX, W8JMC, W9BGX, YV2GC. 14Mc/s—KL7EB, LA2NK/MM, TN8AA, VE5US, VE8BB, VP9FK, VP9DH, YV5ALK, 5Z4SS. 28Mc/s—CR-7CZ, CX2CO, H18XAL, HKØAL, KP4CQZ, KZ5-TW, LA2MA/MM, UA9EU, UA9WJ, VK5DS, VK7SM, 4X4DH, VS9AJC.

N. Henbrey (Sussex), EA12, 20 metre dipole at 25ft. Offers a five-band log starting with 80—H18X-AL, K2DXV, K2ISP, K2RBT, K8YWG, UAØBP, VE1ABZ, VE2KC, VE3XK, VO1FX, VO2AW, VS-9AJC, W1FZJ/KP4, W3BMS, W4GFV, YV5BTS. 40—CN8AW, EP2BV, IS1DMN, K5HWA, PY6WA, PY7KOG, UA9BE, UW9AF, VK2AVA, VP2AA, VP6KL, W3BMS, W4AZK, ZD8ARP, 5A3TW, 5N2AAS, 9H1AL, 9H1AM, 9X5MH. 20—CE6EZ, CR5SP, HP9FC/MM, KR6CO, KL7EBK, OD5AR, U5ARTEK, UA9YO, ZP3AB, ZS3XG, ZD8L, 3A-2CQ. 15—K2UTC, K3TGS, K4DI, K8RHK, K9HCG, MP4BBA, UF6FE, UL7JA, VE1AIT, VE2BDT, VE3FJZ/SU, VP5RB, WA1FDU, W5P-MZ, YA1FV, ZS4MZ. 10—FH8CD, OD5CN, VE3-WQ, VK6CF, ZC4CI, ZC4CN, ZC4RM, ZE5JS, 4U1SU.

J. Farrer (Herts), HMV domestic receiver, 90ft.

l.w. says W6 and W7 are now breaking through on 28Mc/s, while down the other end John remarks on the increase in s.s.b. stations on topband. His log for 3.5Mc/s reads—CN8AW, CT1EE, DJ1SU, EA-2FF, EI4J, F2MO, H18XAL, K3UZE, K4YGU, K8YWG/P (using 50 watts), LA2PM/MM, MP4T-BO, OZ1SF, SV2MB, UA3TN, UC2LVK, UP2OJ, UR2REK, VE1AIJ, VE2AUU, VE3DMU, VO1FG, VS9AJC, W1DRS, W2ZPO, W3AQH, W4RNG, W4UHA/P, ZL1BDW, ZL3AKJ, ZL3JC, ZL3RK, ZL4KE, ZL4OD, 4X4OV.

Higher up

I did wonder, some little while ago, if 14 and 21 were dying or losing their popularity. Not so, as some logs prove a different story.

Paul Baker (Mon.) HE30, 45ft. l.w. sends in a log for 14 and 21 of stations heard at various hours. 20—FB8YY, HL9TH, HS4AK, UAØEH, VK9AG, VP-8CW, VS9OC, YK1AA, 4S7PB. 15—CO8RA, CR3K-D, CR4BC, FL8RA, KL7CSR, KV4CX, MP4BBA, OH2BBF/MM, PX1PA, ST2SA, TF2WK, VEØMB, K4OMM, VK9XI, W7ETD, YA5RG, ZL1AFN, ZL2AJV, ZL2KP, 5N2AAR, 6Y5RS, 7XØWW, 9M2DQ. Paul reckons to hear Australia, New Zealand and Japan on 15 metres between 0830—0930 and very often from 1200—1500 during a second opening.

J. Dunnett (Singapore), Racal 17, 7Mc/s dipole at 70ft. for all bands writes in with a report on 14 and 21Mc/s from way out East. All that lovely sunshine and he has to pinch my best DX too! On 14 c.w. Jim logged—EA8FG, EA9EO, FK8AH, FM7-WP, MP4MAW, VP6PJ, ZD8J, 5R8AW, 6W8CQ. While on 14 s.s.b.—CN8CB, CT2YA, CT3AU, G5A-AV/K5ZKN, KJ6BZ, KG6IJ, KL7FRY, KW6EG, U5ARTEK, VK9XI (Christmas Is.), 3W8AD, 7Q-7EC, 9Y4AR. On 21Mc/s c.w.—HP1RP, PZ1BX, VS6FS, 5N2AAW, 5Z4JW, 9G1RW. With a b.f.o. in, s.s.b. stations heard were CR7AN, CT3AU, GB3MM, VK9CJ, (Papua), 6O6BW, 9M1AF. Jim says "We also hear lots and lots of G's here".

Mumblings

News and natterings from here and there. First, for those trying to brush up their c.w. The RSGB organise slow c.w. most evenings on topband. The ARRL station has set sessions on most bands most days and does a special run at up to 35 w.p.m. for those who really reckon they can take c.w. Ten metres, still going strong. An interesting letter from **Barry Tew** (G8AVW). Barry says he tuned his CR150 down below 28 and heard American Citizens Band Stations between 27 and 28Mc/s. He thinks these stations are restricted to 5 watts and a 60 inch antenna. Anyone else heard anything? Mind you don't pick up 28Mc/s image if it's a single conversion superhet. Contests for the chilly 4 weeks called February: 4th.—5th., ARRL phone contest; 12th., First 70Mc/s contest; 18th.—19th., First 1.8Mc/s c.w. contest; 18th.—19th., ARRL c.w. contest; March 4th.—5th., Second 2 metre contest. The deadline for reports this month is the 20th. How about an epistle from you?

SULTAN

solid-state integrated Stereo amplifier



The most advanced design in brilliant new kit form—so simplified you can build it to professional standards without specialized knowledge and with simple tools. Designed for kit builders from the beginning with a system of wiring that enables you to complete each solder joint as you proceed; nothing is soldered twice and there are no unfinished joints left waiting to overlook! SULTAN performance is a natural result of superb design incorporating the most advanced fully proved semi-conductors, and modular substage construction that permits searching quality control and precise matching at every stage of assembly. Particular attention has been given to the provision of all the additional input, output, and power take-off facilities ever likely to be required. The compact sized, craftsman finished rack cabinet and restrained styling ensures unobtrusive, harmonious matching with almost any floor.

Sultan kit of parts **£29.80** Assembled and Tested **£39.18.0**
Carr. & Ins. 8/6 Carr. & Ins. 8/6

Terms: Deposit £13.6.0 and 12 monthly payments of £2.8.10. Total credit price £42.12.0. Carriage and Insurance 8/6.

- Descriptive leaflet free on request.
- Assembly Manual available separately 5/6 incl. P. & P.



DUVIDAL DM-391 DYNAMIC 25/- P. & P. 2/6

High grade dynamic insert in black plastic body with grey and silver trim. With pull-out stand for desk use. Direct replacement for many recorders; standard 50 K ohms impedance permits use with most other equipment. Size 2 1/4 x 1 1/4 x 1 in. deep. With 4ft. cable and standard phono plug.



DUVIDAL BM-3 CRYSTAL MICROPHONE

Matching desk stand 12/6 extra. **39/6** P. & P. 2/6

Versatile stick microphone with muting switch, can be used with floor or desk stand, neck cord or in the hand. Finished in chrome and black enamel, supplied complete with lead, neck harness, and removable stand adaptor. High impedance only.

DUVIDAL DM 51 DYNAMIC MICROPHONE

● Omni-Directional ● Ideal for high quality recording and P.A. work


£6.19.6

P. & P. 3/6

A superb non-directional microphone magnetized with constant use effect is cumulative and leads to only in extremely expensive professional units. An excellent frequency response of 50-15,000 cycles permits use in high quality recording high-fidelity reproduction and all general microphone usage. Robust, engine turned body has integral slide switch. Beautifully styled with fluted detachable head; matt black and satin silver finish. Complete with desk stand and clamp, floor stand adaptor, and 5ft. lead and plug. In fitted pack. Impedance 50,000 ohms.



*** TAPE RECORDING EQUIPMENT

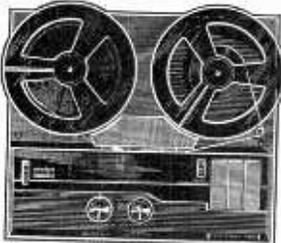

MAGNAVOX 363 TAPE TRANSPORTER

Manufactured to precise limits that permit recording and tape playback to the highest standards set by the Music Industry.

Simple reliable design employs a single high-duty motor with heavy flywheel. Features include fast wind on and rapid rewind, pause control, 3-speed selection with interlock, built-in revolution indicator, piano key controls. Speeds 1 1/2, 3 1/2 and 7 1/2 l.p.s. Wow and flutter 0.15% on 7 1/2 l.p.s. Max. spool size 7in. Playing time up to 120 min. per track from 1,200ft. standard tape. Size 13 1/2 x 11in. plus 5 1/2in below mounting board.

With 1/2 track heads **£10.10.0**

With 1/2 track heads **£13.10.6** Add 10/- carriage and insurance


Specially developed by Mullard Laboratories for use with high quality replay systems and supplied specifically matched for use with the Magnavox 363 tape deck.

Features include: Ferroxcube pot core inductors for treble equalization, push-pull oscillator incorporating ferroxcube transformer, adjustable output for matching to existing high-quality amplifier systems; inputs for Mic. Pick-up, Radio, etc. Valves: 3 x EF86, EC82 and EM81. Totally enclosed in case. Size 11 1/2 x 6 1/2 x 3 1/2in. high (Panel 11 1/2 x 3 1/2in.). Power supply of 300 v. d.c. at 25 mA. and 6.3 v. at 1.5 A. is on separate sub-chassis. Size 6 1/2 x 4 1/2 x 4 1/2in. high to facilitate remote location from tape heads.


Pre-amp. and power **£14.10.0** Assembled and tested **£20.10.0**
Kit of parts Add 7/8 carriage

Terms: Deposit £6.17.0 and 12 monthly payments of £1.6.11. Total credit price: £23.

TYPE 'C' TAPE PREAMPLIFIER

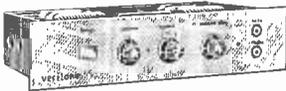

HF/TR3 TAPE AMPLIFIER

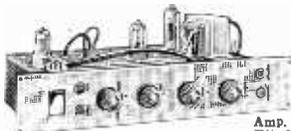

Amp. power pack. **£14.10.0** Assembled and tested **£20.15.0** Add 7/6 carr.

Terms: Deposit £6.19.0 and 12 monthly payments of £1.7.2. Total Credit Price £23.5.0. Carrying Case specially designed to take Magnavox 363 and HF/TR3 unit. Superbly constructed finish, dark grey cloth, £5 extra. 10in. x 6in. elliptical speaker suitable for use with above.

* stern-clyne's TREMENDOUS PRICE BREAKTHROUGH IN NEW UNIVERSAL RECORDING TAPES

- TENSILIZED, prestretched, extra strong
- Fully frequency spectrum response
- Guaranteed playing times

STERN-CLYNE make huge bulk purchases of recording tapes from the world's biggest manufacturers—and hand on the enormous price advantage to their customers. The quality is unequalled: Tensilized to ensure the most permanent type of base. Highly resistant to breakage, moisture, heat, cold or humidity. Highly polished, splice-free finish. Smooth output throughout entire audio range. Ideal for your most treasured recordings, cheap enough to use all the time.

Double-wrapped—distinctively boxed. Available in both P.V.C. and Polyester qualities.

TENSILIZED P.V.C.	
3in. 250ft. Long Play ..	5 6
5in. 600ft. Standard ..	8 6
5in. 900ft. Long Play ..	10 0
5 1/2in. 1,200ft. Long Play ..	12 6
7in. 1,200ft. Standard ..	12 6
7in. 1,800ft. Long Play ..	15 0

TENSILIZED POLYESTER	
3 1/2in. 600ft. Double Play ..	11 6
5in. 1,200ft. Double Play ..	15 0
5 1/2in. 1,800ft. Double Play ..	22 6
5 1/2in. 2,400ft. Triple Play ..	37 6
7in. 2,400ft. Double Play ..	25 0
7in. 3,600ft. Triple Play ..	50 0

TRIPLE BARGAIN OFFER
3-Reel packs of 3in. Professional quality tape in self mailing boxes with all-in address label on reverse. Works on all tape recorders. 250ft. per reel. Famous Audio Magnetic brand. **13/6**
P. & P. 1/6d.

3B1 RECORDER CASE £5



Houses a complete tape recorder. Designed to take the Magnavox 363, Stern-Clyne HF/TR3 Tape Amplifier and Power Pack plus 10 x 6in. speaker. Size overall 19 1/2in. wide x 14 1/2in. deep x 10 1/2in. high.



TAPE HEAD DEMAGNETIZER

29/6
P. & P. 2/-

A must for serious tape users! Tape heads become permanently magnetized with constant use; effect is cumulative and leads to background noise that prevents the achievement of perfect recordings. Highly effective, mains operated device is simply applied to recording head and carries magnetic condition through series of hysteresis loops of diminishing amplitude leaving head substantially free of magnetism. Cleans any tape head in seconds.

DUVIDAL TAPE SPLICER 14/6

Carriage 1/6.



Essential for editing the making immaculate joints in broken tape. Twin clamps hold broken ends in perfect alignment; integral cutting tool makes diagonal splice and trims away surplus splicing tape when join is complete. Size only 3 x 2 x 1 1/4in. high.

SEND FOR CATALOGUE

A 1/- P.O. brings new 100-page Sound and Science Catalogue packed with unique items; profusely illustrated.

Mail Order & all enquiries to Dept. P.W.3,
3-5 EDEN GROVE, LONDON, N.7
Tel. NORTH 8161/5

LONDON:
18 Tottenham Court Road, W.1. MUS 5929
23 Tottenham Court Road, W.1. MUSEUM 3451
309 Edgware Road, W.2. PADDINGTON 6963
109 Fleet Street, E.C.4. FLEET Street 5812
162 Holloway Road, N.7. NORTH 7941.
9 Camberwell Church Street, S.E.5. RODNEY 2875
220 Edgware Road, W.2. PADDINGTON 5607

CROYDON:
12 Suffolk House, George Street. MUNICIPAL 3250

BRISTOL:
26 Merchant Street, Bristol 1. Bristol 20261

LIVERPOOL: 52 Lord Street. Royal 7450

MANCHESTER:
20/22 Withy Grove, M/c 4. Blackfriars 5379/5246

SHEFFIELD: 125 The Moor. Sheffield 29993


NOTTINGHAM:
Easton House, Lincoln Street. Nottingham 45889



**What is new
from
Richard Allan
for the
Audio Fair?**

Well, for the moment we're keeping it dark, but we'll whet your appetite by telling you that it is a superb new Loudspeaker containing three units. This, however is where conventional similarity between it and other loudspeakers end, as it combines a refreshingly new approach to stereophonic reproduction with great flexibility and economy.

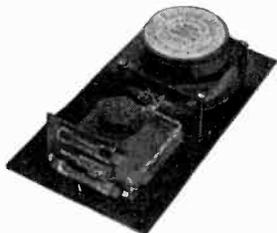Designed and developed by the same team that produced the brilliant high fidelity module (which will also be making an appearance of course), you can be certain that something special will be heard in our demonstration room at the Audio Fair.



For further details please contact:
**RICHARD ALLAN
RADIO LIMITED**
Bradford Rd., Gomersal,
Nr. Leeds, Yorks.
Tel.: Cleckheaton 2442/3

Richard Allan

THE BEST OF ALL CIRCUIT BOARD SYSTEMS


Best because it is the only one in the world by which you can produce a single circuit board to your own requirements without having to use chemicals, etching, heat or special tools, yet the end result equals a printed circuit in all respects and is even better in others. Applying this system, called "Cir-Kit" is very cheap, quick and it can be easily modified. As such, it is used in laboratories and by experimenters as well as all up-to-date constructors. Basically, "Cir-Kit" comprises 95% pure copper strip and sheet backed by a unique adhesive protected by an easily removed backing. "Cir-Kit" Pack No. 3 contains approx. 15ft. of 1/8 in. strip, 6 x 4 in. sheet and a 12 x 6 in. laminate board—enough for about 10 average circuits. In sealed pack with instructions—15/-.

A 16 WATT HI-FI STEREO AMP USING "CIR-KIT" FOR ECONOMY AND EFFICIENCY

The Peak Sound SA.8-8 integrated stereo amplifier and pre-amp with tone controls is a first-class compact design using 14 matched transistors, "Cir-Kit" and ready-drilled metal chassis. Assembly is exceptionally simple. For use with high-quality ceramic or crystal stereo cartridges and 3-5 and 8-15 ohm loudspeakers. This Peak Sound constructor's kit is absolutely complete, even down to wire and solder and includes excellent step-by-step illustrated instructions. With front panel, 14 transistors, chassis, "Cir-Kit" etc.

£12.19.6 Peak Sound Mains Power Pack 75/-.

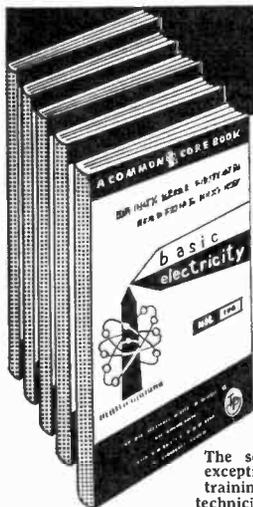From good stockists or direct in case of difficulty
PEAK SOUND (HARROW) LTD. 10 ASHER DRIVE, MILL RIDE, ASCOT, BERKS. Winkfield Row 3217
Distributors to the radio wholesale and retail trade
TECHNICAL SUPPLIERS LTD., 63 GOLDHAWK ROAD, W.12. (01-603-2581)



YOURS FREE FOR 7 DAYS

The New 'Picture - Book' way of learning

BASIC

- ELECTRICITY (5 Vols)**
- ELECTRONICS (6 Vols)**
- ELECTRONIC CIRCUITS (2 Vols)**
- INDUSTRIAL ELECTRICITY (2 Vols)**
- SYNCHROS & SERVOMECHANISMS (2 Vols)**

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

"My praise for a fine set of books . . ." L. O., Welling.
"I am very satisfied with these carefully written and well expressed manuals . . ." A. W., Shanklin.
"They are concise and easily understood and I agree with everything that other readers have said in their favour . . ." W. W., Darlington.

**TO SELRAY BOOK CO.
60 HAYES HILL, HAYES, BROMLEY, KENT**

Please send me Without Obligation to Purchase, one of the above sets on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 7 days or send the following amounts. Basic Electricity 70/- Cash Price or Down Payment of 15/- followed by 4 fortnightly payments of 15/- each. Basic Electronics 82/- Cash Price or Down Payment of 15/- followed by 5 fortnightly payments of 15/- each. This offer applies to UNITED KINGDOM ONLY.

Tick set required (only ONE set allowed on free trial).

- BASIC ELECTRICITY 70/-
 - BASIC ELECTRONIC CIRCUITS 40/-
 - BASIC INDUSTRIAL ELECTRICITY 40/-
 - BASIC SYNCHROS & SERVOMECHANISMS 38/-
 - BASIC ELECTRONICS 82/-
- ALL PRICES INCLUDE POSTAGE**

Signature (If under 21, signature of parent or guardian)

NAME BLOCK LETTERS BELOW

FULL POSTAL ADDRESS

POST NOW FOR THIS OFFER!


practically wireless

commentary by **HENRY**

WE began this series—so long ago, it seems—with a passing glance at the kitmaker. From time to time we have taken a harder look. Now, with the glittering commercial confections of the Radio Show behind us, and our corns beginning to heal, we may return to glare more closely at the subject. Recently, the need arose for an inexpensive portable amplifier. Inexpensive, for Henry's relations all appear to be touchingly impecunious. Portable, because the thing had to be lugged around the country as an aid to illustrated lectures.

Obviously, a transistorised version was called for. Equally obviously, the various commercial products had to be ruled out—first because their prices indicated the parts were at least gold-plated, and second because no manufacturer considered that mono production was worthwhile. The answer—build it yourself.

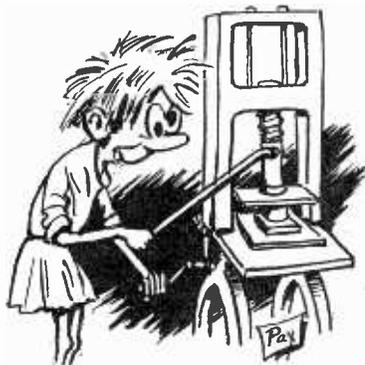But the particular kit that seemed appropriate for the purpose, and remarkably cheap, was from a firm a little less illustrious. A preliminary (unofficial) glance



An old Caxtonian duplicator

at the circuit showed it to come from a fairly trustworthy stable. The advertisement showed an

attractive finished job. So Henry showed his money and plunged . . . up to his top-knot in trouble!

The kit came in a tatty cardboard box, each piece wrapped in a screw of crumpled paper. Careless unpacking could easily have whittled away half the contents. But the greatest disappointment was the literature that pretended to be a guide to construction.

Apparently run off by a shell-shocked operator of an old Caxtonian duplicator, on Government surplus blotting paper, pinned in a Chinese order of page numbering, it should have deterred us from the start.

Between us we managed to make some sense of the hieroglyph and laid out the parts for checking against the list. (My typewriter nearly wrote 'lost'—and it would have been more appropriate.) Several components were missing, and remained so, despite a ferreting amidst the packing. Others had been substituted, which only became confirmed as we ploughed through the barely legible text. We made up the missing quantity—secretly commiserating with some innocent not blessed with a pretty full spares box. Then we amended the given list, if only for the sake of posterity.

The actual building was not too bad, provided one already had a fair knowledge of the techniques. The absolute beginner, despite what the advertisements claimed, would have been bogged down before the third page. The selector switch was physically different from the diagram, and connections had to be worked out. One or two unexplained wires appeared, and the projected colour coding could not be followed because different lengths of different colours had been included. Again, no obstacle to the experienced, but . . .

We shall skate mercifully over some other points—vital paxolin spacers missing; too many nuts of one size, not enough of another; an extra switch on the



The thing refused to work

diagram, not mentioned in the text; no flats on the control spindles; no spigot holes drilled, and chassis holes out of alignment. And, incidentally, no solder!

The important point was that the thing refused, pointblank, to work. At this stage, the novice slings it back to his supplier and pays the fee he could have laid out *before* his hair went grey, to have his pet rebuilt. We reverted to first principles and cast aside the instructions, checked the diagram against the original design in an old technical magazine, made due allowances for the alterations that had obviously been done more with a view to economy than efficiency, and eventually got results.

An unlucky case? Maybe, but we would like to hear of other experiences. We would even like to see a Constructors' Guide to Kits. Henry reckons he knows which firms would top the list as 'Best Buys'.

FREE

INSIDE EVERY COPY OF

PRACTICAL WIRELESS NEXT MONTH!



33 $\frac{1}{3}$ R.P.M.

RADIO FAULT-FINDING RECORD

The sounds made by a variety of radio faults...r.f. and i.f. instability, overloading, component noise—are reproduced on this record, together with identifying commentaries and fault-free passage for comparison.

TEN TYPES OF FAULTS

This unique record has been specially made to launch a new series on REPAIRING RADIO SETS, beginning in next month's PRACTICAL WIRELESS. Written by two top experts in the field, and supplemented by the record, this important series will enable you to diagnose and remedy faults in radio receivers, amplifiers and other equipment.

APRIL ISSUE
ON SALE MARCH 3rd

MAKE SURE OF YOURS!
Hand this Form to your Newsagent

TO

NAME OF
NEWSAGENT

Please reserve/deliver the April issue of PRACTICAL WIRELESS (2/6), on sale March 3rd, and continue until further notice.

Name

Address

IMPROVING THE R1155

C. MOLLOY

ALMOST twenty years have gone by since the first R1155 communications and direction finding receiver became available to the public through the surplus market. Since that time a lot of useful information has been published on this R.A.F. aircraft h.f. receiver in the technical journals, but often in issues that are now out of print. This article does not include a complete circuit diagram, but gives general information plus details of improvements that the author has made to his own receiver.

The standard model covers the range 75kc/s to 18.5Mc/s in 5 bands, with a gap from 500kc/s to 600kc/s and another from 1.5Mc/s to 3.0Mc/s. A second, less common version, designated L or N, omits the lowest range, 75kc/s to 200kc/s, but covers the Trawler Band, 1.5Mc/s to 3.0Mc/s. The two types are otherwise identical, having a single r.f. stage, mixer, two i.f. stages, a b.f.o. and a triode output stage feeding high impedance phones. An external power unit is used.

REMOVAL OF D.F. COMPONENTS

As the R1155 is a dual purpose receiver, many of the d.f. components can be removed without affecting the performance of the communications section leaving space for additional items to be added and, incidentally, reducing the total power consumption. A circuit diagram of the R1155 together with notes, is available from an advertiser in PRACTICAL WIRELESS. From this the readers can locate the d.f. components and decide which of them he would like to remove. The associated valves are V1, V2 and V8 and these are shown in Fig. 1. The meter balance control, meter amplitude control, meter deflection switch, aural sense switch, and associated wiring also can be taken out, to give extra front panel space.

The job of removing the d.f. components should

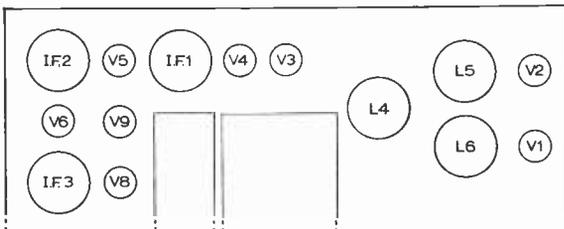


Fig. 1: Top view of the receiver showing position of the major components.

be tackled systematically, removing one item at a time and checking in each case that the receiver's performance is unaffected. If a mistake is made it should then be easy to pin point where it occurred. Care should be taken, especially at valve bases, not to break the continuity of the heater and h.t. lines.

DECOUPLING CAPACITORS

At this stage a check of all paper decoupling capacitors is advisable. There are two types, both of which are metal cased. Those mounted above the chassis are easily found, being cylindrical (3/4 in. diameter, 3 in. high) and secured to the chassis by a large nut. Age may have brought about leakage and an easy method of checking is to use a voltmeter set to a range suitable to measure the h.t. supply. Connect the meter positive lead to the receiver's h.t. positive line and the negative to the capacitor to be tested after electrically removing it from the h.t. line. A good capacitor will make the meter needle kick and then return to zero; this is caused by the charging current flowing into the capacitor. A faulty capacitor will either give a steady reading or the needle will gradually fall to a low value. Any faulty capacitors should, of course, be replaced. The lot had to be changed on the author's receiver (using modern components of the same value).

A number of smaller cylindrical decouplers can be found in several places within the coil compartment. These seem to be less prone to leakage and can probably be left alone. But it is well worth checking all the paper decoupling capacitors, as a defective one can make a considerable difference to the performance of the receiver.

LINING UP

No difficulty should be experienced lining up the i.f. stages. Figure 1 shows the position of the three i.f. transformers and the dust cores are readily accessible through the screening cans. The i.f. frequency is 560kc/s.

Disconnect the top cap of the frequency changer valve V4 and apply 560kc/s to the valve from a signal generator. The magic eye can be used as a peaking indicator, but make sure the a.v.c. is inoperative by turning the master switch to either the OMNI or O position. Set the volume control to maximum (reducing signal generator output as necessary) and adjust the cores of each i.f. transformer in turn, starting at the last stage (number 3) and working towards the front end.

The r.f., mixer and oscillator circuits can be lined up on each band in turn by choosing alignment points near the ends of the bands and inject-

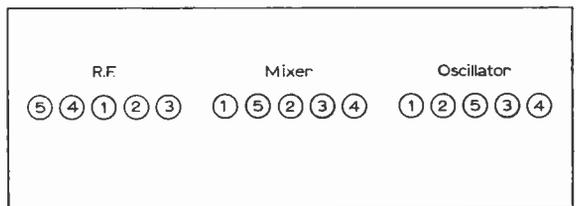


Fig. 2: Layout of the trimmers, viewed from the front of the receiver.

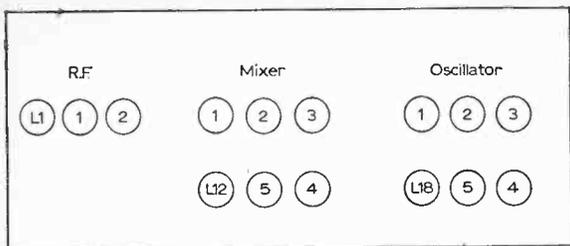


Fig. 3 (above): Side of the coil compartment viewed from front of the receiver.

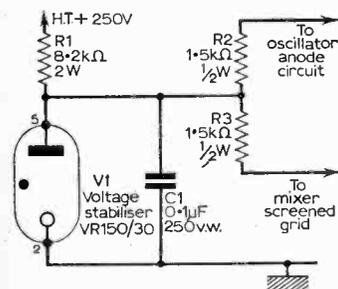


Fig. 4 (left): Simple stabiliser, see text for details.

ing an appropriate signal to the aerial input. If a signal generator is not to hand tune to a broadcasting station of known frequency and use it instead. This is not really a satisfactory method owing to the difficulty of obtaining a steady signal, but at a pinch it will do. Switch off the a.v.c., turn the gain control to maximum and use the tuning indicator. The trimmers are adjusted at the h.f. end of the band and the dust cores at the other. It will not be necessary to touch the oscillator section unless the scale calibration is out of adjustment: often peaking the r.f. and mixer trimmers will suffice. The location of all trimmers is shown in Fig. 2. A 4BA box spanner will be required to adjust the majority of them. The layout of the coils is shown in Fig. 3. The cores can be adjusted without removing the cover of the coil compartment.

L18 comprises 2 tuned chokes which assist in maintaining a constant oscillator voltage throughout ranges 1 and 2. They should not be adjusted.

L12 is an i.f. rejector and is connected to the mixer grid circuit on ranges 3 and 4. To adjust, inject 560kc/s to the r.f. circuits, then tune the receiver to the l.f. end of range 3 or the h.f. end of range 4 and adjust the core for *minimum* output.

L1 is only used on d.f. and can be ignored.

L4, L5 and L6 are the r.f. coils for ranges 3, 4 and 5 respectively. These are located above the chassis inside large cylindrical cans (see Fig. 1) and the cores are accessible from the top.

AERIAL TRIMMER CONTROL

A simple but very useful addition to any receiver is an aerial trimmer. A small variable capacitor of 50pF will do, connected in parallel with the r.f. section of the main tuning capacitor. It is used to counteract any loading effect the aerial may have on the first tuned circuit. The capacitor can be mounted on the front panel in the space vacated by the meter deflection or aural sense switches. The moving vanes are connected to chassis and a short length of coaxial cable is run from the fixed vanes to the rear section of the main tuning capacitor; the cable braiding should be earthed. The r.f.

trimmers will now have to be re-adjusted on all bands and this is done with the aerial trimmer set to minimum capacitance (vanes out). The aerial trimmer is used to peak signals after they have been tuned in and the effect will be most apparent at the h.f. end of each band.

BANDSPREADING

Although the slow motion drive, especially the later type, is excellent, a bandspread control is a definite advantage on the higher frequencies. It can also be used for dial setting to counter the effects of oscillator drift on lower frequencies. Ideally, a twin-gang variable capacitor of about 20pF per section can be used, mounted below the chassis underneath the main tuning capacitor. One section should be connected in parallel with the oscillator (front section) and the other to the mixer (centre section) of the main tuning capacitor. The writer was unable to obtain a twin-gang capacitor of suitable dimensions and as two single variable capacitors were to hand, decided to use these instead. It was found advantageous to have two controls instead of one, though of course they were less convenient to use. After making this modification, the oscillator and mixer trimmers have to be re-peaked and this should be done at the h.f. end of each band with the vanes of the band spread control fully open.

Care should be taken when drilling through the front panel as it is of double thickness at this point. Swarf may fall between the inner and outer sections and later find its way into other parts of the receiver. It is not too difficult to remove the outer panel including the scale cover, if the slow motion drive is taken off first.

VOLTAGE STABILISER

Frequency drift, especially on the higher frequencies, can be a nuisance and a considerable improvement can be obtained by stabilising the voltage at the oscillator anode. A type VR150/30 voltage stabiliser was used (Fig. 4 shows the connections). This stabiliser has an octal base and can be plugged into the valveholder previously used for V8. All the d.f. wiring should, of course, be removed from this valveholder including the heater supply. The 22kΩ resistor (R28) in the oscillator anode circuit has to be replaced with a 1.5kΩ ½ watt resistor. Resistor R28 is located inside the coil pack on a small tag-board which is mounted on the chassis at the left hand side as viewed from the rear of the receiver. One side of this resistor is connected to h.t. positive and the other side goes to a common lead which runs between L15, L16, L17 and L18. Remove the strap to the h.t. positive line and run a wire to pin 5 on the base of the stabiliser.

It was thought worthwhile to stabilise the voltage at the screened grid of the frequency changer too. Voltage changes on the screen grid can cause small changes to the oscillator frequency. Since the screen grid voltage can vary in sympathy with the a.v.c. voltage it is possible for some kinds of fading to produce variations in the oscillator frequency which will give rise to objectionable distortion. The majority of receivers do not apply a.v.c. to the mixer valve, probably for this reason. An obvious solution is to disconnect the mixer from the a.v.c.

line, however, the a.v.c. on the R1155 is very efficient and rather than disturb it, it was thought better to stabilise the screen grid voltage. Only one additional resistor is required to do this and it is shown in Fig. 4 connected between pin 5 of the stabiliser valve and pin 4 of V4. The two resistors connected to pin 4, a 22k Ω and a 27k Ω , should be removed but the connection to the decoupler should be left.

R.F. GAIN CONTROL

The volume control on the R1155 is a little unusual as it consists of a twin-gang potentiometer. One section (0.5M Ω) is an audio volume control while the other (50k Ω) controls the gain of V3, V4, V5 and V6 by applying a steady controllable voltage to the a.v.c. line. When the master switch is in the a.v.c. position only the audio gain control is effective, V3 to V6 being controlled by the normal a.v.c. voltage. When the master switch is in the OMNI position, the 0.5M Ω section is out of circuit allowing maximum audio gain. Also, the a.v.c. line is disconnected from the a.v.c. diode load and joined to the 50k Ω section which then forms part of a biasing network situated between h.t. negative and the chassis.

In short, when the a.v.c. is *on*, the receiver output is controlled manually by the audio gain control. When the a.v.c. is *off*, the audio gain is fixed and the combined r.f./i.f. gain control is effective. This is a sensible arrangement and is more or less how one would use a receiver with separate r.f. and audio gain controls. There are occasions though when one wants to reduce only the r.f. gain to avoid overloading the frequency changer with a strong signal. However, to do this with the R1155, the i.f. gain has to be reduced too.

A separate r.f. gain control will solve this problem and one can be installed quite easily by placing a 5k Ω potentiometer between the chassis and pin 8 of V3. The potentiometer can be fitted underneath the chassis so that the shaft projects through the front panel below and to the right of the main tuning capacitor, maintaining symmetry of control layout (including the two bandspread controls). Alternatively, the potentiometer can be fitted in one of the spaces along the top of the front panel which were previously occupied by d.f. components.

The left hand terminal of the potentiometer as viewed from the rear, is connected to chassis. The strap from V3 pin 8 to chassis is removed and a

wire is run to the central terminal of the r.f. gain control. A 0.1 μ F decoupling capacitor must be connected from pin 8 to chassis and it is essential to connect this component direct to pin 8 and not to the centre terminal of the potentiometer, otherwise instability will occur.

TAPE OUTLET

The phones output from the R1155 is suitable for direct connection to a tape recorder. In a previous article a description was given of how to fit a front panel phones socket. Adjacent to this, a second socket can be fitted for use as a tape outlet. A 0.1 μ F 350VW capacitor was used to isolate the headphones from the input of the tape recorder and it was wired between the line terminals of the phones and tape socket, at the rear of the front panel. The second terminal of each socket was connected to the chassis which should be earthed.

An attenuator may be required for some recorders. Figure 5 shows a simple attenuator which, if it is required for permanent use, can be wired between the tape and phones socket.

NOISE LIMITER

A subject that is almost certain to start a discussion among radio enthusiasts is that of noise limiters. Many circuits have appeared: some are good, others not so good; the method of operation of some is simple, of others it is obscure; some operate on the i.f. stages of the receiver, others are used on the audio; some automatically adjust themselves to the signal level, others have to be set manually; and so on. Unfortunately there are snags of one sort or another connected with many noise limiters. To be effective, some of them have to be set so that they tend to clip the signal causing distortion, which may, of course, be acceptable. It is obviously better to have a partly distorted signal that is audible, than one which is lost in noise.

It was finally decided that a simple audio limiting circuit applied to the phones output of the R1155 would probably be as good as any. Figure 6 shows the circuit of a parallel type of audio limiter. Either valve or semiconductor diodes can be used but in each case the main drawback of this circuit is the same. The diodes have to be reverse-biased so that they will only conduct when the bias voltage is exceeded. If 1.5V dry cells are used, the limiter will not act until 3V peak-to-peak is applied to it, which is ample to drive a pair of headphones.

It is possible to throw away the biasing batteries and use silicon diodes in the noise limiter circuit; since these devices do not conduct in the forward direction until a forward bias is applied (the level of which varies according to type). Figure 7 gives details of such a circuit using 0A202 diodes. Germanium diodes were tried, but discarded as they distorted the output.

The limiter is connected between the output transformer and the phones socket; it is convenient to mount the components at the rear of the socket itself. The effect of the limiter is immediately apparent, removing the usual clicks, bangs and static crashes. As the volume is turned up a point is reached where no further increase in output is obtained. Any further advance of the volume control only brings about distortion. ■

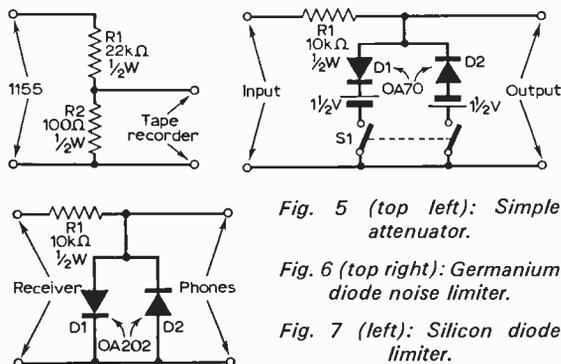



Fig. 5 (top left): Simple attenuator.

Fig. 6 (top right): Germanium diode noise limiter.

Fig. 7 (left): Silicon diode limiter.

a two-transistor PERSONAL PORTA

R. L.

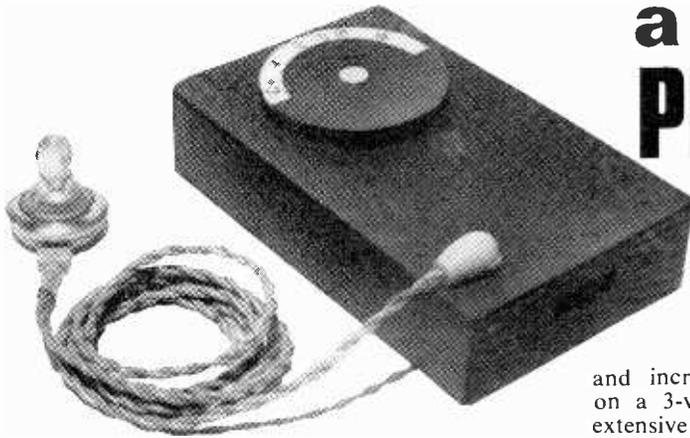

REFLEXING in this personal radio makes two transistors do the work of four. Often it is not easy to carry out successfully, but works reasonably well in this circuit, even over an output stage feeding an earpiece. The quality depends upon using a good earpiece and the type specified is Ardenite ER250.

Alignment problems do not exist in a receiver that has only one tuned circuit. On the other hand, as it takes as many as four tuned circuits to suppress a powerful transmission and enable a weak signal to be heard, it is mainly a local station receiver. Reaction could be added to sharpen selectivity, but risks instability, and there is probably some r.f. feedback already. It is almost unavoidable when a t.r.f. circuit is put into miniature form, since the input and output of the r.f. amplifier are working at the same frequency, and are close together.

With a ferrite aerial, an r.f. amplifier is essential, because a detector can only respond effectively to strong signals. At low signal levels the detector is insensitive and produces increased distortion. A.F. amplification cannot, in general, make up for a lack of r.f. amplification.

and increased volume could have been obtained on a 3-volt supply, but this would have involved extensive modification. Most of the difficulties of a t.r.f. circuit would disappear if it were designed to receive a single frequency like the i.f. amplifier of a superhet. Instead it has to be tunable over a wide frequency band, and conditions vary considerably over the tuning range. Here the circuit is aperiodic except for the input, although L3 with only 20 turns should assist in maintaining the r.f. gain at the high-frequency end.

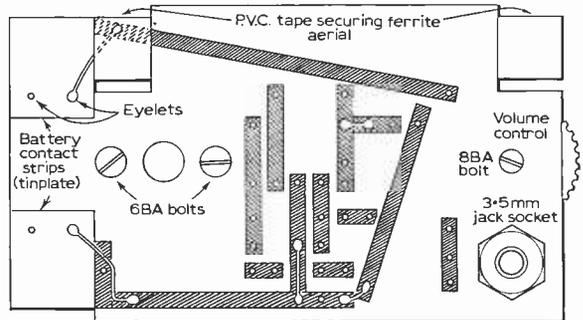


Fig. 2: Mounting board using "Cir-kit".

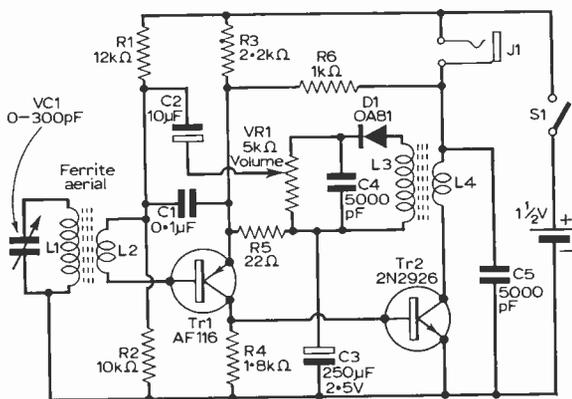



Fig. 1: Circuit diagram of the two-transistor radio.

A 1.5V battery is capable of providing all the volume needed in an earpiece. The low voltage, however, accentuates the non-uniformity of gain over the medium waves, and sensitivity decreases towards the high-frequency end. Improved sensitivity

Tuning is effected by a 300pF miniature plastic dielectric capacitor across a 70 turn winding on the ferrite aerial, and this is coupled by a coil of five turns to the base-emitter input of Tr1. The two transistors serve first as r.f. stages feeding the detector via a small step-up transformer, and then as a.f. stages amplifying the a.f. from the detector. The overall a.f. gain is about 40 times with negative feedback applied by means of R5 to reduce distortion in the output stage. A step-up ratio to the detector is possible because the detector is working at a rather low signal level at which its impedance is fairly high. Ideally there would be a further step-up to a tuned circuit, but this, though desirable, would involve the complication of ganged tuning.

R.F. TRANSFORMER

The r.f. transformer is wound on a ½ in. ferrite ring because this has very little external field and avoids r.f. instability through magnetic feedback to the ferrite aerial. It is more compact than a ferrite pot core, and can be wound fairly easily. Very little of the a.f. at the collector of Tr2 can reach the detector via this transformer, although winding the coils L3 and L4 on separate rings coupled by a

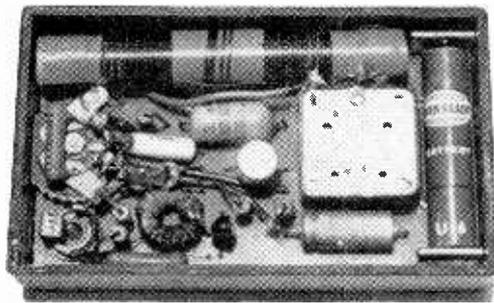

capacitor of about 200pF might be a better arrangement, and would still give a step-up to the detector. The r.f. at the collector of Tr2 is passed via the transformer to the detector, but after the modulation is extracted, it too must be filtered out, and only the resulting a.f. is passed back to the base of Tr1 so that the transistors can now function as a.f. amplifiers.

The success of reflexing depends upon this sequence of filtering, and r.f. current must also be kept out of the earpiece leads in order to prevent re-radiation and hand-capacity effects when tuning. This is the purpose of the bypass capacitor C5.

TRANSISTORS

A direct-coupled circuit requires fewer components, and a complementary arrangement of a p-n-p transistor followed by an n-p-n can take a form which does not require any adjustment. D.C. feedback to overcome drift is applied via R6 to the emitter of Tr1. The potential divider consisting of R1 in series with R2 provides a "reference voltage". The resistance R3 is necessary mainly because of the low supply voltage. D.C. stability would be somewhat better on a higher supply voltage, because the base-emitter potential drops of the transistors would be a smaller part of the total voltage.

A silicon transistor 2N2926 is deliberately chosen for Tr2 because of its large base-emitter drop. This permits a larger current in Tr1 for a given load resistance R4. The total current of the receiver is under 2mA and of this about one-third of a milliamp flows in Tr1. The first transistor could also be

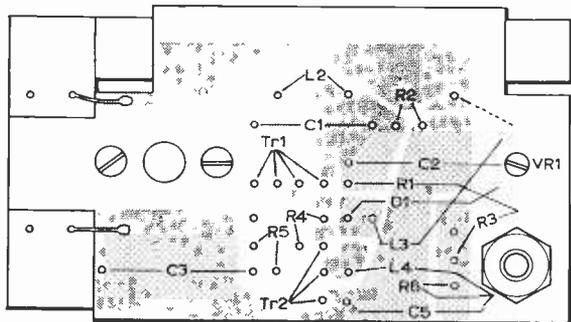


Fig. 3: Printed circuit as alternative to Fig. 2.

a silicon transistor, but of the p-n-p type, such as 2N3702. However it was found that the germanium r.f. transistor AF116 gave a larger output. Complementary circuitry can be confusing, and the lead

arrangements of the two transistors should be studied carefully before insertion into the circuit. The lead arrangements of the silicon and germanium transistors are depicted in Fig. 5 which also shows the positions of the corresponding holes in the mounting board.

The detector diode D1 is connected with the red end towards the volume control. The polarities on the electrolytic capacitors should also be carefully observed, otherwise the circuit will stop working in a short time. The metal case of C2 is connected to the junction of R1 and R2, while that of C3 is connected to the negative side of the battery. The battery itself must be correctly inserted, although no damage appears to occur from an accidental reversal when the rest of the circuit is in order.

CONSTRUCTION

The components are assembled on a small mounting board of $\frac{1}{16}$ in. insulating material. "Cir-Kit" strip on the underside is an alternative to a printed circuit, although rather close spacing is involved. Holes for component leads are drilled with a No. 60 drill. Guide marks are then made

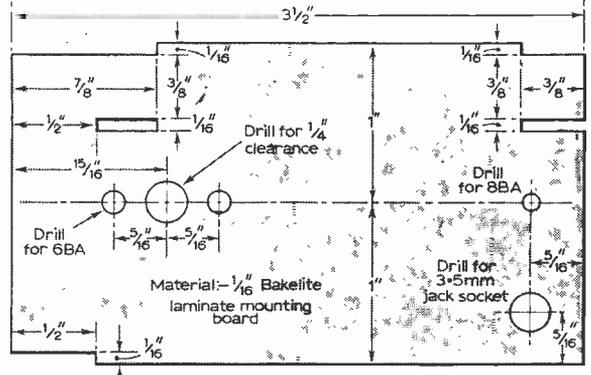


Fig. 4: Details of the mounting board.

with a scribe for the edges and ends of the strips. The "Cir-Kit" strip is cut to length, then the paper backing is prised off with the point of the scribe, holding the end of the strip with small forceps or tweezers. When all the strips have been pressed down in position, the mounting board is placed with the copper side downwards on a flat wooden surface, and the holes can then be drilled through the strips, smoothing them afterwards where necessary. Joins between adjacent strips can be made by soldering short pieces of 24s.w.g. tinned copper wire across them, and in one or two instances, gaps between the strips can be widened by cutting away some of the strip.

FERRITE AERIAL

The 3 x $\frac{3}{8}$ in. ferrite rod is a piece broken off from a longer rod. A method of doing so is to wind two turns of $\frac{1}{8}$ in. Sellotape tightly round at the point where the break is required. Place the rod on a hard surface and position a metal chisel at the edge of the Sellotape. A sharp tap with a hammer will usually produce a clean break at this point. The ferrite rod is then covered with p.v.c. tape and wound with 70 turns of 24s.w.g. enamelled wire. The ends of the wire are fixed with a strip of p.v.c.

tape. A piece of the tape is then applied around the middle of the winding and the five-turn coupling is then wound on top. Owing to the shortness of the aerial the winding has to be in the middle for maximum signal. The ferrite aerial is fastened on to the

applied around the perimeter of the ring and folded inwards. It can be pushed into the centre from each side to cover the ring completely. The 40-turn winding requires 27in. of 36 s.w.g. wire. Double silk-covered may be used, but should be waxed before winding since the wire has to be threaded through the core 40 times and this can impair the insulation. The 20-twin winding may consist of 15in. of 30s.w.g. wire.

Battery contacts may be formed by folding strips of tinfoil to the shape shown in Fig. 6, and are attached underneath the mounting board by small eyelets. The smallest eyelets obtainable are the type made for insertion in Veroboard, and are thus suitable for $\frac{1}{16}$ in. material. In assembly, the component leads are passed through their respective holes, bent over, clipped, and soldered to the copper strips with printed circuit

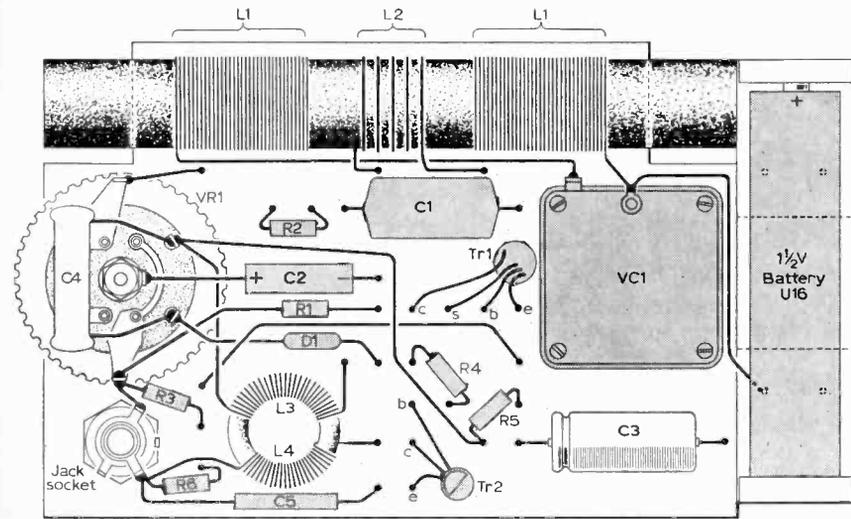


Fig. 5: Component arrangement above circuit board.

mounting board by strips of p.v.c. passed through slots in the board. It is raised above the surface by $\frac{1}{8}$ in. squares of the $\frac{1}{16}$ in. material cemented to the mounting board under the ends of the rod.

TUNING CAPACITOR

The round-head screws supplied with the 300pF Dilemin capacitor are too short for mounting on the $\frac{1}{16}$ in. material and can be replaced by similar 6BA screws $\frac{1}{8}$ in. long. The washers supplied are

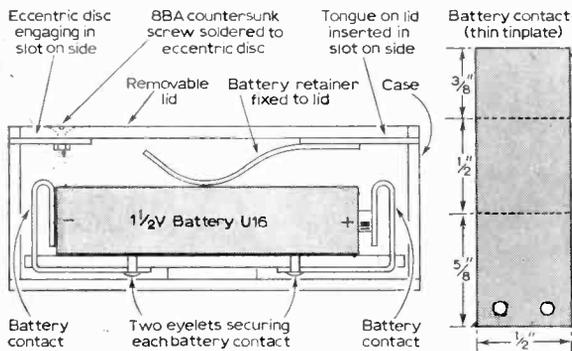


Fig. 6: Sectional elevation showing battery contacts.

placed between the capacitor and the board, as it requires to be raised slightly to clear a ridge around the tuning shaft. A check should be made on the length of the screws projecting through the board, as the capacitor will be damaged if these screw in too far. It should also be kept in mind that the end stops of the capacitor will be damaged if the shaft is turned beyond its normal range, especially as it is a little stiff to turn at first.

Before winding the two single-layer windings on the ferrite ring (type FX1593), $\frac{1}{2}$ in. Sellotape is

solder. Ease of construction is more important than the ultimate in compactness. Resistors stand vertically on the board. A heat shunt, e.g., the Antex type, can be used when soldering the transistors and diode. Special care is needed as the leads are made very short so that the transistors project no higher than the variable capacitor. Although it takes longer, the best method is perhaps to apply the soldering iron for a second at a time, followed by an adequate cooling interval. The high frequency performance of transistors seems often to be impaired by soldering without adequate precautions.

CABINET

The case is made from $\frac{1}{16}$ in. material glued at the edges with Bostik clear adhesive. A strip of leathercloth is glued round the sides of the box and trimmed with scissors. A piece is glued over the top and trimmed neatly round the edge so that the join is almost imperceptible. The back, too, is covered with leathercloth, and is removable by giving a small screw half a turn with a screwdriver. The locking device consists of an eccentric disc which enters a slot in the side. The three slots required in the sides are made before assembly by drilling series of holes with a No. 60 drill. These can then be merged by inserting the tapered end of a nail file.

There is an opening in the end of the case for the edge-type volume control, which also incorporates the on-off switch; and to enable the chassis of the receiver to drop into place, the hole in the case for the tuning shaft is elongated slightly. This can be done by using the $\frac{1}{4}$ in. drill in the manner of a saw.

A combined tuning knob and dial is constructed from three discs as shown in Fig. 8, and is fixed on the shaft by a piece of wire through a hole drilled in

★ components list

Resistors:

- R1 12kΩ
- R2 10kΩ
- R3 2.2kΩ
- R4 1.8kΩ
- R5 22Ω
- R6 1kΩ

Capacitors:

- C1 0.1μF 125V polyester
- C2 10μF 15V electrolytic
- C3 250μF 2.5V electrolytic
- C4 5,000pF tubular ceramic
- C5 5,000pF tubular ceramic
- VC1 300pF Jackson "Dilemin"

Coils:

- L1 70 turns 24swg enam. wire
 - L2 5 turns 24swg enam. wire
 - L3 20 turns 30swg dsc wire
 - L4 40 turns 36swg dsc wire
- } see text

Miscellaneous:

Earpiece, Ardenite type ER250 with cord and 3.5 mm jack plug. Jack socket 3.5 mm. Ferrite rod. Ferrite ring core type FX1593. Battery, 1.5V type U16. Edgewise pot. (Volume and on/off switch) 5kΩ with switch.


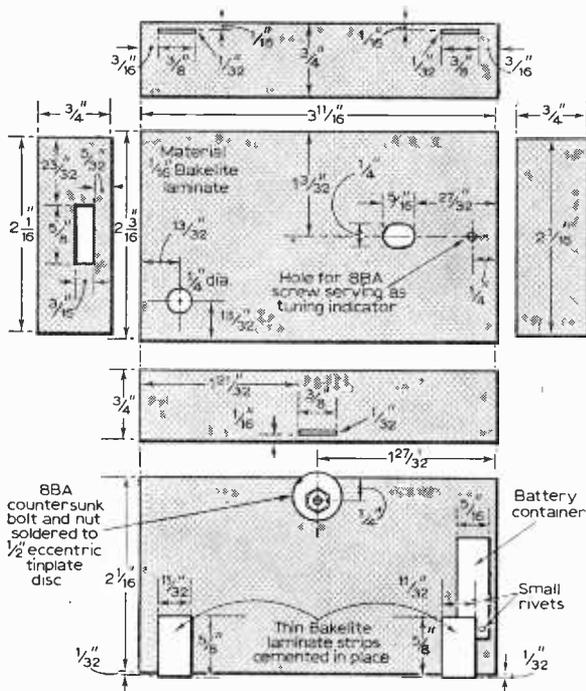


Fig. 7: Constructional details of the case.

Fig. 8: Individual parts for the tuning scale.

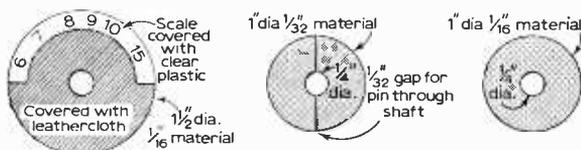

the shaft with the No. 60 drill. The knob is covered with leathercloth to match the case, except for the end of the shaft exposed in the centre for decorative effect. The scale round the edge is marked approximately in hundreds of kilocycles and is covered with clear plastic.

THE MW COLUMN

THIS month we will take a look at the Americas. The prolific stations of South America are usually best heard in the spring, when North America is less favourable. Some of the most consistent are PRG3 (1280kc/s), PRA3 (860); YVQO (650), HJED (820), LR4 (910), LRI (1070), PRF4 (940), PRA2 (1040), ZFY (760).

Central America and the Caribbean are usually more difficult to hear except for a few outstanding ones such as Radio Americas, Swan Island (1157, but frequency varies) and PJB Bonaire (800). Others to look for include CMBC Havana (690), CMCA (830), Jamaica (650), St. Lucia (840), Guadeloupe (640), ZBM1 Bermuda (1235—together with spurious pop pirate signal!), HOL55 (1315), TGRB (1120) TIRICA (625), PJD2 (1295), Belize (834) and the regular St. Pierre et Miquelon on 1375. A consistent one last season was XEW Mexico City, now suffering from splash from Milano; however it is often strong from 0500.

The east coast USA and Canadian stations, of course, can be heard very early in the evening when conditions are good, long before the Europeans sign off and loggings have occurred as early as 1730! With peak conditions they can be heard as late as 0900. Early arrivals to look for include WHDH (850), CJCH (920), CJON (930), WAVY (1350), WINS (1010), CBA (1070), CJCB (1270). Even mid-West stations have been heard comparatively early—WOAI (1200) and KMOX (1120) both before 2300.

Some channels are known as "graveyards" because they are occupied by dozens of low-powered local stations and no dominant station is apparent—just one weak signal on top of another. 1240, 1340 and 1400 are examples. Some stations make use of two frequencies (shared time), e.g. WFAA and WBAP both operate on 570 and 820. Other stations operate during daytime only. Also remember that on many channels both USA and Canadian stations operate. Which makes it important to take care in identification.

Some easy ones are WNBC (660), WCBM (680), WABC (770), WCBS (880), WBZ (1030), WHN (1050), WBAL (1090), WNEW (1130), WCAU (1210), WKBW (1520), WQXR (1560). More difficult high power stations include WFAA/WBAP (820), WCCO (830), WJR (760), WSB (750), WOWO (1190), WLS (890), WHO (1040).

You should add a few Indian stations to the log this month in the early hours between 0030—0200. Most have some English programmes (mainly newscasts). Most likely ones are Rajkot (910), Lucknow (760), Sangli (1250), Ajmer (600), Ahmedabad/Baroda (in parallel on 850), Delhi (1070), Bombay (1040). Several others have been logged. Radio Pakistan is more difficult but look for Lahore (630), Quetta (750), Rawalpindi (1150).

Japan is heard only rarely in Britain (but often in Sweden due to polar paths reflection). But try around 1500 on 1250 for Vladivostok, a good catch.

Alistair Woodland

Cycles for ever

WHAT a strange point of view Mr. Covington has (PRACTICAL WIRELESS, January, 1967). Surely, the only sane outlook is to have descriptive terms wherever possible. Everyone who can remember back must realise the difficulty a beginner has in memorising a multitude of non-descriptive terms. If all Mr. Covington is worried about is verbal speed, what can be quicker than the usual "cycles"?

Regarding written speed, surely the three letter m.p.h. is simpler than the five letter plus oblique mile/h.

I think that the answer to the change for changings' sake group is to simply ignore them—I shall certainly continue to write c/s and say cycles for cycles per second.

W. Lee.

Hull.

R1155 information

RECENTLY there have been letters in this magazine concerning the R1155, from Mr. Tye and myself. I would like to state that although I said I would get copies made of any information I received, I cannot get them done free. Many readers have written asking for the information and only one has sent the money for the copying. The charge for this is 1s. per page.

A. R. Preston.

London, S.E.8.

Phonetics again

I AGREE entirely with the letter of Charles Mitchell (November 1966 issue). Most amateur radio operators operate fairly powerful transmitters. They are fully competent to operate their equipment or else they wouldn't be licensed amateurs. The one quality they lack, is use of codes and abbreviations. Mr. Mitchell says he had heard a ham on 80m using very different phonetics when repeating his callsign in the same transmission. I have listened to hams doing this many a time. Sometimes the callsign is given without the use of phonetics, and we, the S.W.L. fraternity and the amateur who he is in QSO with, are subject to "garbled" call signs. I think that before licences are granted the applicants should be tested on their knowledge of abbreviations, etc., set down in the Geneva Radio Regulations, 1959. It would be interesting to hear what other readers think of my idea.

S. Haagensen.

Grimbsy,
Lincolnshire.

Price correction

The price of the Electronics (Croydon) Ltd., "Supertone G.C.V." radio, as advertised on page 779 of February issue, should be £3 19s. 6d. and not as printed.

NEWS AND..

COBRA AND THE COMMODORE FROM K-B



The latest in the K-B range of portable radios are the Cobra (left) and Commodore (right). Both models feature modular construction which makes servicing a very easy job—the r.f., i.f. and a.f. sections being three plug-in units. The transistor complement is the same in both receivers: 2 × AF117, OC70, 2 × AC127 and 2 × OC81.

The Cobra embodies a 5in. speaker and cabinet dimensions are $5\frac{1}{2} \times 10\frac{1}{8} \times 2\frac{3}{8}$ in. and the Commodore having a $7 \times 3\frac{1}{2}$ in. speaker, measures $7 \times 12\frac{3}{8} \times 2\frac{3}{8}$ in. Both receivers cover long waves and have bandspread on the medium wave band and have provision for an earpiece which is provided as an optional extra and both sets have a car aerial socket. Tape recordings can be made from the Commodore.

The cabinet of the Cobra is Arabian blue plastic with a chrome plated fascia and satin finished aluminium fold-down handle. The Commodore is in a wooden cabinet covered in grey leathercloth with chrome finished knobs and trim. The Cobra costs $12\frac{1}{2}$ gns. plus 3s.8d. surcharge and the Commodore 18 gns. plus 5s.3d. surcharge.

CHRISTMAS MAYDAY CALL FOR RARE DRUG

A ham radio broadcast from Vienna promptly translated into action by a Swedish newspaperman resulted in the emergency despatch from the Wellcome Chemical Works, Dartford, on Christmas Day of 100 tablets of a rare drug which may be the last hope of prolonging the life of a patient in Zagreb, Yugoslavia.

The emergency call, put out on behalf of Dr. Otto Schinkler of Vienna, was for the drug Alkeran needed by his sister, a doctor at the 1st Polyclinic in Zagreb, to treat Eviord Storjok, a 35-year-old patient suffering from cancer. With pharmacies closed and continental telephone lines jammed with Christmas goodwill messages, Dr. Schinkler enlisted the help of Friedrich Stobel, a ham whose Mayday call was picked up by a fellow ham in Stockholm.

Action began when Fred Bramberg, on duty at the Stockholm newspaper "Expressen", received news of the broadcast by telephone. At about 4 p.m. Bramberg was able to reach by telephone Dr. Fred Wrigley, Overseas Director of The Wellcome Foundation Ltd.

With the aid of Mr. W. L. Jeffrey, general manager in the overseas unit and Mr F. G. Rundall, General Works Manager, the tablets were located in the Wellcome Chemical Works. They were handed to Mr. Alan Stubbs, head of the Works despatch section who, despite having one leg in a plaster cast, delivered them to B.E.A. Export Cargo Unit to be put on the first connecting plane for Zagreb.

...COMMENT

THE BRITISH ACOUSTICAL SOCIETY

A significant milestone in the history of British Acoustics has been the formation of the British Acoustical Society. This resulted from meetings arranged by the Royal Society between representatives of architecture, engineering, medicine and pure science.

Appropriately, in view of its importance to large sections of the community, the first meeting was a two-day symposium on aircraft noise. Subsequently, symposia have been held on such diverse subjects as underwater acoustics and acoustical investigations of defects in solids.

For full particulars of membership apply to Dr. R. W. B. Stephens at the Physics Department, Imperial College, London, S.W.7.

RADIO 390 LOSE APPEAL BUT BACK ON THE AIR

An order of *certiorari* to quash the convictions against Radio 390 and two Company directors (see last month's issue for court report), was dismissed by a two-to-one majority in the High Court of Justice on 13th December. Estuary Radio Ltd., who own Radio 390, switched their transmitter on again New Year's Eve in open defiance of the Post Office, and are now broadcasting as before from the former anti-aircraft fort on Red Sands in the Thames Estuary. The other 'pirate' radio station BBMS, which was also prosecuted for illegally broadcasting from another fort in the Thames Estuary, is still, as far as we know, operating in the medium wave band.

GRUNDIG SV80 POWER AMPLIFIER



Grundig announce a range of high quality Hi-Fi units, amongst which is the SV80; a fully transistorised mains powered stereo amplifier with a transformerless output stage. Provision is made for the connection of a radio tuner, tape recorder and record player and there are output sockets for loudspeaker assemblies and headphones. Finished in light walnut or teak the cabinet matches other items in their Hi-Fi range.

Technical specification: Mains voltage, 110—130—220—240V 50/60c/s; Power Consumption, 120W max.; Transistors, 14 × BSY76—4 × BSY51—2 × BSX40—AD152—8 × 2N2148; Diodes, 2 × ZF27—2 × GF580—2 × ECO1106—8 × ECO3390—DZ62; Channel Separation, better than 46dB; Frequency Response, 20—20,000c/s ±1dB; Damping Factor 20 at 5Ω, 60 at 15Ω; Input Sensitivities, Mic 7.5mV/100kΩ, P.U. (Magnetic) 4mV/47kΩ, P.U. (Crystal) 220mV—3V/1MΩ, Radio/Tape Recorder 250mV/470kΩ; Output Sockets, Speaker 2 × 5Ω (4—16Ω), Headphones 2 × 300Ω; Output Power is 2 × 40W (Music Power) and Controls are: Volume, Stereo Balance, Bass and Treble; Distortion Factor is less than 0.5%; Power Bandwidth, 10—50,000c/s—1% distortion; and Balance Regulation, up to 10dB.

Starting a club

I WAS glad to read the letter from G3VLJ last month, and I would like to encourage any young reader in that area to contact him. There may be older readers who know young beginners and who could tell them of the proposed club. Mr. Hansen and I have corresponded earlier on the topic, and I know he is keen.

I have always thought and hoped that the next move in the youth service would be a growth of radio and science clubs, so best wishes to the Croydon area.

By the way, if there are any interested young people in the Holloway/Camden Town area who would like to contact me, I would be very pleased to hear from them.

Ken Smith, G3JIX. 82 Granville Road, Walthamstow, E.17.

Foreign equipment

FROM time to time I have observed letters published in your journal from readers who have purchased foreign-made receivers and equipment which have broken down and been left inactive due to requirement of special parts which the suppliers are unable to supply or have a "I couldn't care less" attitude when letters are written to them requesting data and availability of parts in the country the product is marketed in.


I am surprised to see, why persons in Great Britain who have such an abundant source to draw from in their own country, purchase products made abroad. It could be in my opinion, the price at which they are sold. A similar product made at home (Great Britain) does cost more, I agree, but there is always the dependability of the manufacturer being able to supply the necessary parts if they are of a special nature to the instrument concerned.

I have had similar experiences with American-made products, which I ordered from New York. Certain parts in an oscilloscope purchased in kit form were missing when the parcel arrived, and after a correspondence that lasted over a period of years, I was told that the kit-maker had gone out of business and they were sorry they couldn't supply parts; would I be interested in ordering another kit?!?! The result has been that I have a white elephant in the house.

I have, however, experienced that the British manufacturers are most co-operative in supplying technical information of their products, and any special parts for many of the test equipment that I own, and service has been very prompt.

S. M. Sharifi.

Teheran,
Iran.

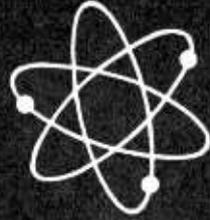

SOLID STATE THERMOMETERS AND THERMOSTATS


K. T. WILSON

MOST textbook descriptions of transistor action pay a fair amount of attention to the effect of varying temperatures on the operation of transistor circuits. As far as the normal operation of circuits is concerned, the temperature dependence of all the transistor parameters is a problem which must be taken care of in the design of equipment. If we wish to use transistors as temperature detectors, however, we must find a way to obtain the maximum temperature sensitivity in order to make the thermometer action as sensitive as possible.

The most temperature dependent parameters of any transistor are the leakage currents, and of the two leakage currents of importance, the more sensitive is the collector leakage current in the common emitter connection with the base open cir-

one milliamp flows in the collector of Tr2 at room temperature. VR2 is then adjusted so that the meter reads zero at room temperature.

The circuit as drawn provides a range of ten degrees centigrade (eighteen degrees Fahrenheit) for full scale deflection. It is therefore very suitable for interior use where temperatures fall within this range (15-25 degrees centigrade). The experimenter can readily devise methods of extending this range; for example the collector loads of Tr2 and Tr3 could be dropped to 680Ω and a 5mA meter used. Alternatively, the circuit of Fig. 3 could be used. Here the temperature sensitive transistor forms one of the long-tailed pair of the meter circuit, and the Zener diode has been replaced by a resistor. It should be noted that these circuits are entirely unsuitable for car radiator measurements,

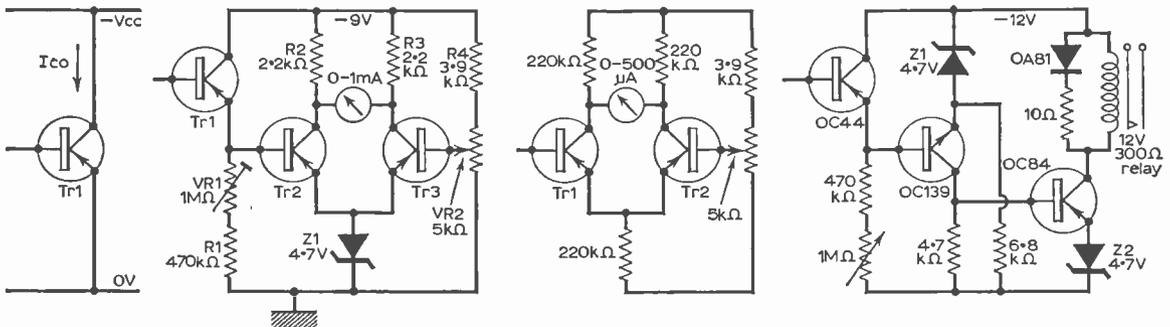

Left to right. Fig. 1: Path of leakage current I'_{co} . Fig. 2: A simple thermometer circuit using I'_{co} to record temperature fluctuations. Fig. 3: Alternative circuitry using a long tailed pair. Fig. 4: Circuit of a simple thermostat. (Tr1, Tr2, Tr3—OC70, 71, 44 etc).

cuted. This mouthful is usually shortened to I'_{co} . For most germanium transistors, the value of I'_{co} approximately doubles for every ten degrees centigrade rise in temperature; or, to put it another way, the I'_{co} increases by about ten per cent per degree centigrade.


A thermometer circuit using this principle is shown in Fig. 2. Tr1 is the temperature sensitive transistor with the base open-circuited. VR1 is adjusted so that the leakage current at room temperature produces a voltage I'_{co} . ($R1 + VR1$) which is slightly greater than the stabilising voltage of the Zener diode Z1 (4.7 volts in this case). This voltage produces a current in the base of Tr2, and hence an amplified current in the collector of Tr2. The value of VR1 should be adjusted so that

as the temperatures encountered may be destructive to the transistors.

Finally, Fig 4 shows a sensitive thermostat using the same principle. In this case the resistance in the emitter of the sensing transistor is high for the maximum sensitivity. To enable the first stage to be coupled directly to the second, Tr2 is an n-p-n type. In some cases where great sensitivity is not required and a low-current relay is available, the n-p-n transistor can operate the relay directly. As shown, the output of Tr2 is directly coupled to a power transistor Tr3 which operates the relay. This arrangement is capable of controlling temperature very closely, the only backlash being due to the relay.

RADIO • HI-FI • COMPONENTS • TEST EQUIPMENT

H.T. 20 Rectangular Horn Tweeter

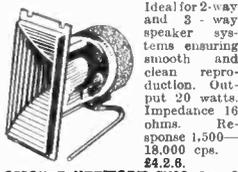


Ideal for 2-way and 3-way speaker systems ensuring smooth and clear reproduction. Output 20 watts. Impedance 16 ohms. Response 1,500-18,000 cps. £4.2.6.



CROSSOVER NETWORK CN23, 3 Ω 2 way 14/8. CN216, 16Ω, 2 way, 14/6.


ALL TRANSISTOR MONO & STEREO PRE AMPLIFIERS
Provide extra stage of amplification for use with magnetic cartridges, tape and microphone inputs. Both models feature wide band pass range, 20-20,000 cps. As reviewed in *The Gramophone*, Dec. 1966.

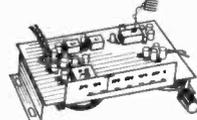PRE 301 MONO £4.12.6
PRE 302 STEREO £5.15.0



EAGLE FMT41. FM TUNER
Sub-miniature 6 transistor 3 diode F.M. Tuner. Covers 88-108 Mc. Operates from 9-volt battery, micro miniature circuit giving brilliant FM reception. Ready to use, simply connect to your Hi Fi amplifier. Instructions supplied.

£8.10.0

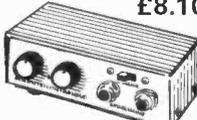

REMOTE CONTROL STEREO HEADPHONE STATION L.S.2.

A junction box for connecting stereo headphones to a stereo or monaural system. Separate controls for each channel. On/off switch. Stereo sockets allow two sets of headphones to be used. With instructions and 20ft. of 5 conductor cable.

£3.5.0



EEK28. 28 PROJECT CONSTRUCTION KIT

This advanced educational kit is excellent for beginners as well as the more advanced experimenter. Not even a soldering iron is needed. Complete with 60 page booklet giving full details of suggested circuits.

£6.10.0




LA5P. AC ELIMINATOR

with a double wound step down transformer to operate 9v. Radios, etc., from AC Mains.

£1.8.6

TAPE HEAD DEMAGNETIZER

MODEL TD. 79

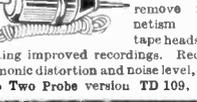

Compact, easy to handle. Will remove magnetism from tape heads permitting improved recordings. Reduces harmonic distortion and noise level, 35/8. Also Two Probe version TD 109, 35/8

ALL ITEMS SENT POST FREE



AIWA TP.712 2-SPEED 5" REEL MAINS AND BATTERY TAPE RECORDER

Loaded with features hitherto only found in more expensive tape recorders: AVC system automatically adjusts recording volume level. TWO-WAY OPERATION: A.C. mains or batteries TWO HOURS OF RECORDING TIME: Using 1.5 mil 600 ft. tape. REMOTE CONTROL: TONE CONTROL: LEVEL METER: Indicates recording and battery levels. Other features include 1½ and 3½ i.p.s. speeds, smooth operating push-button keyboard, input for radio, record player, TV, etc., socket for an external speaker. Complete with Dynamic microphone, earphone, 5in. 600ft. tape, 5in. empty reel batteries and A.C. lead. Size: 12½in. x 10½in. x 3½in.

26½ Gns.


EAGLE PRODUCTS MAGNETIC STEREO CARTRIDGES

M1007G GOLD Response: 20-20,000 cps Output: 5MV at 1Kc/5cm/sec.
M1007F SILVER Response: 20-18,000 cps Output: 10MV at 1Kc/5cm/sec.
Stylus: 0.5 Mil diamond Tracking Pressure 1-2.5 grams.
Stylus: 0.7 Mil diamond Tracking Pressure 2-4 grams.

£6.12.6 £5.14.6

As reviewed in *Hi Fi News* Sept. 1965. Both feature singularly smooth reproduction and incisive separation of stereo channels

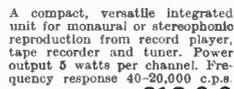EAGLE SA100. 10W INTEGRATED STEREO AMPLIFIER



A compact, versatile integrated unit for monaural or stereophonic reproduction from record player, tape recorder and tuner. Power output 5 watts per channel. Frequency response 40-20,000 c.p.s.

£18.0.0

EAGLE AFM100. AM-FM TUNER
Combines a host of advanced features that easily make it the finest AM-FM tuner in its class. A tuned RF stage on FM, AFC circuit and a heavy flywheel giving smooth but effortless tuning, built in AM Ferrite aerial. FM.88-108Mc. £29.0.0

MS80. 20W ROSEWOOD SPEAKER SYSTEM

The perfect answer for the music lover who wants full range fidelity in a compact system. Features an 8in. full range high compliance speaker with an output capacity of 20 watts RMS. Resonant frequency: 30-40 c.p.s. Sensitivity: 97 db/w. Flux density: Over 12,000. Impedance: 16 ohm. Size 14½in. high x 10½in. wide x 8in. deep.

£14.14.0

As well as this beautifully designed speaker there are two other models MS65, 10 watts RMS at £12.12.0 and MS40 5 watts RMS £8.10.0. All three speakers are finished in magnificent rosewood and the entire cabinet filled with acoustic damping material.

UD40H CARDIOD DYNAMIC MICROPHONE

Features a pop-proof diaphragm and superior anti-feedback properties, reduces feedback and room reverberation. O/p: -42 db. Response: 60-12,900 cps; 50K ohm impedance £6.6.

DM31G CARDIOD DYNAMIC MICROPHONE

Superb quality with ball head for distributed cardioid front-al pick-up. Output: -52db. Response: 40-13,000 cps. Impedance 50 Kohm. £7.7.0.

DM24HL

A goose-neck dual impedance microphone 600 ohm - 50K ohm. Response: 50-11,000 cps £6.6.0.

27 other microphones available.



SR165. ALL BAND COMMUNICATION RECEIVER

This entirely new professional type communication receiver features frequency coverage of 535 Kc/s-30 Mc/s for complete general coverage. In particular ham bands are arranged in the same calibration scale, so that the band switching can be accomplished rapidly.

£48.0.0

FOR FULL DETAILS OF THESE AND MANY OTHER ITEMS SEND FOR FREE COMPREHENSIVE CATALOGUE, EAGLE NEWS AND ORDER FORM. ALL ITEMS AVAILABLE POST FREE AND COVERED BY 12 MONTHS' GUARANTEE.

CALLERS WELCOME AT OUR HI-FI SHOWROOM

RELDA RADIO LTD

(Dept. P.W.15) 87 Tottenham Court Road, London, W.1.

TT.144 DYNAMIC TRANSISTOR TESTER

Tests in-circuit or out of circuit. Identifies PNP and NPN types. Indicates electrode open circuits, short circuits and current drain. Complete with instructions.

£4.10.0




TT.145 DE-LUXE TRANSISTOR DIODE TESTER

MULTI METERS
T.20A 1,000 o.p.v. £2.15.6
TK.25 1,000 o.p.v. £2.15.6
EP.10K 10,000 o.p.v. £4.17.6
EP.10KN 10,000 o.p.v. £5.8.0
EP.20K 20,000 o.p.v. £5.19.6
EP.20K8 20,000 o.p.v. £6.8.0
EP.30K 30,000 o.p.v. £7.18.6
EP.30KN 30,000 o.p.v. £9.0.0
EP.50KN 50,000 o.p.v. £11.9.6
EP.100KN 100,000 o.p.v. £14.19.6

RF. 40 RF FIELD INDICATOR

Broad tuning covers 1-250 Mc/s in five calibrated bands. Can also be used as frequency checker. Detects undesired radiation or spurious frequencies. RF is measured on an accurate 200 µA panel meter.

£4.10.0

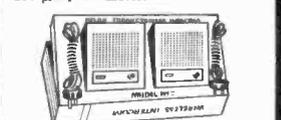


WI-2. TRANSISTORISED WIRELESS INTERCOM

No wires, no installation needed, simply plug them into AC power point and talk. Units have press-to-talk lock switch and on-off volume control. Ideal Intercom or Baby Alarm for home, office, £14.12.0 complete.

DP303. DOOR PHONE INTERCOM

Ultra sensitive transistorized intercom designed so that you may answer the door from within for greater convenience and safety.

£4.12.6 Other intercoms available.

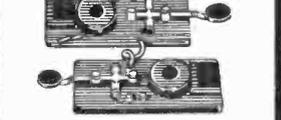

MCK.2. MORSE CODE KIT

Two station morse code kit supplied with instructions, 50ft. of connection wire and morse code charts. £2.2.0

WIRELESS MICROPHONES

WM909 (as illustrated) Pocket FM Wireless transmitter complete with tie-pin microphone. Transmits clearly up to 100 yds. and is fully tunable over the entire FM band. Simply used with an FM radio or tuner. £14.0.0

Also available WM808 £21.0.0

Professional stick type FM Wireless Microphone. These cannot be operated in U.K.



FUTURE BROADCASTING PLANS

THE Postmaster General, Mr. Edward Short, has at last presented Parliament with the long overdue White Paper dealing with broadcasting. Although the contents of this Paper (Cmmd. 3167, obtainable from Her Majesty's Stationery Office, price 1s. 6d.) will not affect many readers directly, it is interesting to note the Government's views on broadcasting.

"The Government have under review various major aspects of broadcasting policy," the White Paper states. "First among them was the question of the BBC's finances. Besides this, there were various proposals for the further extension of the broadcasting services; that there should be a fourth television service; that a service of local sound broadcasting should be introduced; and that there should be an extra service of sound broadcasting entirely given over to music . . ."

"In reaching the conclusions announced in this review, it has of course been the Government's duty to consider both what purposes the proposals for further extending the broadcasting services should seek to serve, and what organisation would best promote those purposes. The Government have also had to consider to what extent it would be in the national economic interest to allow these extensions. It is not enough that they should be desirable in themselves. The overriding consideration is whether the country can afford them."

FINANCES OF THE BBC

The first thing the White Paper looks at in detail is the finances of the BBC. Reference is made to the fact that the BBC have already started another television service (BBC-2); that they are providing self-contained television services for Scotland and Wales; that they have greatly increased the number of hours of broadcasting on the Third Programme and in Network Three; that more time has been allocated to adult education on television; that a colour service is to start on BBC-2; and that the BBC are developing stereophonic broadcasts in the v.h.f. transmission of the Third Programme.

To carry out these improvements, it is recorded in the review that the BBC now receive the full proceeds of the £5 combined sound and television licence and of the sound only licence, which now costs £1 5s. In mentioning that the Government have completed their enquiry into the BBC's finances, the review continues, "Practically speaking, the only possible ways of providing finance for the BBC are: by direct Government subvention, by the sale of advertising time in the Corporation's services, or by the licence fee system.

"A Government subvention would be liable to expose the Corporation to financial control in such detail as would prove incompatible with the BBC's independence. The money would, of course, have to be found from general taxation.

"Under their Licence and Agreement (Cmmd. 2236) the BBC are not allowed to broadcast commercial advertisements without having sought and obtained the Postmaster General's permission. Because of the probable long-term effect on the

character of their services, the BBC have never sought this permission. The BBC have reported that, by making special economies they will—on certain assumptions—be able to do so until 1968 when they would need an increase of £1.

"In order to make these special economies, the BBC will restrict activities which they have hitherto considered well justified but which, against the background of continued financial stringency, can be sacrificed to the overriding national need for economy. The Corporation have conducted a searching examination of all their ancillary services and operations, with a view to making the maximum retrenchment in detail. By itself, however, this will not suffice. Some larger scale projects, desirable in themselves, for enlarging and modernising the Corporation's programme production capacity, will be foregone for the present. But the BBC will be able to maintain their present level of programme output and to proceed with extensions and developments of their services already authorised or about to be authorised.

"One assumption on which the BBC have based their undertaking to manage without an immediate increase in the licence fee is that counter measures against licence evasion will prove effective. It has been reliably estimated that, of the gross revenue amounting to some £80M, payable in a full year, some £10M is lost through evasion. This is far too much to be tolerated. Honest viewers and listeners are, in effect, paying for the dishonesty of the evaders.

"Steps have already been taken by the Postmaster General to tighten up counter evasion measures, but, by themselves, they will not suffice. Further measures are required. The Government are reviewing the penalties which Magistrates may impose on convicted evaders, and are discussing with the associations representing retailers and the rental companies ways in which dealers could help in the enforcement of the licence system. The Government will announce their proposals as soon as these discussions have been completed; and legislation will be brought before Parliament in the current session. The Government recognise the effort which the Corporation are making . . . and are satisfied that no increase in the fee will be required before 1968."

A FOURTH TELEVISION SERVICE

Explaining the Government's decision not to alter the present number of television services, the White Paper suggests that there is room for only one more television service in the next ten years or so, since two of the allocations in the u.h.f. bands will be needed for the changeover of the two present 405-line television services to 625 lines. The review continues, "When the Television Act 1963 was before Parliament, the Government of the day stated their intention to allocate this service [the vacant channel in the u.h.f. bands] to a second programme of independent television during 1965 unless the financial or other obstacles were insurmountable. However it were allocated, a fourth

television service would make large demands on resources. The three main services of television already provide a large volume of programmes of various kinds and the Government do not consider that another television service can be afforded a high place in the order of national priorities.

"Moreover, before deploying the last frequencies certainly available for television for many years to come, the Government would need to be satisfied that the case for committing them to any new service had been fully established. The Government have decided that no allocation of frequencies to a fourth television service will be authorised for the next three years at any rate.

"Besides the claim of independent television to the frequencies required for a fourth television service network, there is also the possibility that the network would be required for a specialised service of educational television, forming part of the structure of the Open University. The decision to reserve the fourth network would enable the requirements of the Open University to be appraised more closely in the light of practical experience."

COLOUR TELEVISION

The White Paper restates the Government's intentions to start a colour service on BBC-2 during 1967. "It is the Government's view that the cost of colour programmes, which are likely at the outset to be available only to a small minority of viewers because of the cost of the receivers, should not fall upon viewers in general. Accordingly a supplementary licence fee of £5 will be required from those equipped to receive colour programmes."

POPULAR MUSIC PROGRAMME

Introducing a new popular music programme, the White Paper claims the fact that there is a ready-made audience for continuous popular entertainment is not new. "What is new is that, by appropriating wavelengths allotted to other countries and by largely disregarding copyright in gramophone records, the pirate stations have been able to exploit the fact. Legislation to end the activities of these stations has been introduced. The Government recognise that there is, however, a need for a new service devoted to the provision of a continuous popular music programme. The question is how the need can legitimately be met: legitimately in that it would be broadcast only on wavelengths available under international agreement to this country, and in that it would respect the rights of performers, composers and others in the material broadcast.

"It is necessary to weigh also any implications for present services to the listening public generally; and, in particular, whether the need to provide frequencies on which to transmit a popular music programme would involve an unacceptable curtailment of the present services of sound broadcasting.

"Because a popular music programme does not need to differ from place to place, the most economical way of broadcasting it will be by relatively few stations, each with a large transmission area. The characteristics of wavelengths in the

medium wave band suit them to this objective. But, as the medium wavelengths available to this country are already intensively used, room for an extra service can only be found by redeploying them. There is not room enough in them for all the present sound radio services and for a popular music programme with anything like sufficient coverage.

"The Government have therefore discussed with the BBC what rearrangement of their services they would need to make in order to find room for the additional service. In the past, the Corporation have considered that they could best serve their various audiences by providing the Light Programme on both long and medium wavelengths, in order to attain the widest possible coverage at an acceptable standard of reception. Now, however, that the long wave transmission of the Light Programme is reinforced by the BBC's v.h.f. transmissions, which have themselves attained virtually complete population coverage, and now that portable v.h.f. transistor sets, at reasonable cost, are available, the Corporation feel free to devote the medium wave channel of 247 metres to a popular music programme.

"The BBC have informed the Government that, on weekdays, the programme would broadcast popular music continuously from 5.30 a.m. to 7.30 p.m. and again from 10 p.m. to 2 a.m., and on Sundays, for most of the day's broadcasting. Over six hours of music each day would be played from gramophone records. The remainder would be either live broadcasts or BBC recordings of popular music especially made for the service. The programme would provide each day a blend of output to meet the needs of the audience for popular music.

"In the Government's view, the provision of a popular music programme on the medium wavelength, 247 metres, would, on an overall appraisal, provide an extension of choice to the listener. They will authorise the BBC to provide the new service at an early date."

LOCAL SOUND RADIO

"No general service of local sound broadcasting, which would be available during the hours of darkness as well as in daylight, can be provided only on medium wavelengths allotted to the United Kingdom," the White Paper states. "The only possibility for such a service lies in v.h.f. In practical terms, some 150 towns and cities could be served. Of the proposals put to the Government for the provision of a service, some advocate that it should be provided by commercial companies, others that it should be provided by the BBC.

"In a worthwhile service of broadcasting a local station should, the Pilkington Committee concluded, transmit for a *sufficient part of the broadcasting day (material) of particular interest to the community served by that station rather than to other localities*. In their White Paper of July 1962 (Cmmd. 1770) the Conservative administration agreed that the *justification for local sound broadcasting would be the provision of a service genuinely 'local' in character*. The Government share this view.

—continued on page 854

PSE QSL

Will You Please QSL . . .

MANY newcomers must have looked at John Guttridge's page and asked themselves, "How do they pick up so-and-so, when I only hear the same stations over and over again?" This article is not intended to teach old-hands new tricks or newcomers old tricks but is simply an account of one man's methods of receiving, and obtaining verification from some of the less common stations heard on the shortwave broadcasting bands.

First of all, it is necessary to have the kind of receiver and aerial which give one a sporting chance of receiving the less common station. The depth of one's pocket and personal choice influence the selection, as does the question whether one should build or buy. What is important is that the receiver should have adequate selectivity and sensitivity to enable the weak signal to be heard through the strident blasts of the major broadcasters on both sides of the Iron Curtain, and also it should have reasonably accurate tuning calibration.

Secondly, the idea should be laid to rest that one person hears all the DX that is going whilst another just does not have the luck. The real answer is that the "lucky" man is usually the one who sets a trap for the DX and then waits for his quarry to appear in it. This is the purpose of this article—to suggest a way in which the trap may be baited, without moving from the fireside, and even without the receiver being switched on. If the "shack" is in an uncomfortable location it makes a pleasant way of pursuing the hobby when the fireside, slippers and background tele are more inviting.

Another myth is that one must speak—or at least understand—a number of languages. This just is not so. What is important is that one should be able to recognise a number of languages, and this ability comes with practice. Very soon one finds that one has a working knowledge of the words which make up station identifications in a number of languages, and as this knowledge is gained it becomes easier to identify stations using languages other than English.

So far as reporting to DX stations is concerned, English is almost universally acceptable, and only a small number of stations ask for reports in other languages. Several short-wave clubs issue QSL report forms in a number of languages, and these help to overcome the language difficulty.

The first 20 or 30 overseas stations can be logged and reported without any difficulty—even if the

A QSL card is a written confirmation of either a contact with, or the reception of, a Radio Station. On the Medium and Short Wave bands, broadcasting stations will often send their QSL cards on receipt of a report. This also applies to "Ham" Stations. However the reports received must be of some use to the station concerned, merely to inform briefly that "I heard you Thursday at 0745 hrs" is virtually useless. The following article is split into two sections. Alan Thompson describes some techniques for the 'commercial' enthusiasts, and David Gibson, G3JDG writes from the amateur's point of view.

receiver and aerial fall far short of the ideal. As the QSL cards for these begin to come in, you will begin to notice some significant—and surprising—gaps in your list. The answer is likely to be that they are countries—not necessarily difficult to receive in themselves—which either do not use English, use low-powered transmitters or only broadcast for a short time each day. It is now that the fireside work begins and perhaps an actual example of the writer's method will best illustrate what is involved.

An essential tool is the "World Radio TV Handbook". This is published in Denmark annually, but is written throughout in English. It can be obtained through all booksellers, but any good reference library should have a copy. The Handbook lists all the radio stations of the world and gives details of their programme schedules and frequencies.

Another invaluable publication is the "Kurzwellensender Frequenzliste" which is issued free by Sender Freies Berlin two or three times a year. This list is in German—with English notes—and gives, in frequency order, brief transmission details of the main radio stations heard in Europe (excluding Radio Moscow, Radio Peking and Radio Free Europe). Armed with one, or preferably both, of these publications one can settle down and set the "trap".

Let us say that one is anxious to hear Saudi Arabia. A glance at the WRTH will show that the foreign service is carried in a group of Middle Eastern and Indian languages and is clearly not destined for the U.K. Since transmitters are normally beamed to the area in which reception is intended such services are not likely—as a general rule—to be heard or heard well in a totally different direction. (This is a dangerous generalisation, but the exceptions are outside the scope of this article).

There is, however, a Saudi Arabian General Service in Arabic which is clearly intended for the Middle East and North Africa—an area much nearer the U.K. Both the WRTH and the "Frequenzliste" publish tables showing the broadcast bands which are most likely to give good reception in a particular area at any time, and these show that the Middle East is likely to be best heard in the U.K. on the 9Mc/s band in the evening.

Reference back to the WRTH shows that Saudi Arabia uses two frequencies in the 9Mc/s

Build Your Own Heathkit Electronics

A kit for every interest—Home Workshop—Hi-Fi—Radio—Test—'Amateur'
 Treat yourself to superb LW, MW entertainment with the
High-Performance Car Radio Kit. CR-1.



Complete your motoring pleasure with this small, compact, high-performance car radio. It can be fitted to any make of car having 12 volt positive or negative earth system. Tastefully styled in neutral grey with matching black knobs and chrome trim to harmonise with any car colour scheme.

Features include:— Six transistor, 2-diode circuit. Completely pre-assembled and aligned tuning unit. High sensitivity, combined with wide range automatic gain control (AGC), minimises fading under weak reception conditions. Easy-tune dial. Push button long, medium, and tone selection.

The car radio is available for your convenience, in two separate units: RF Amplifier Kit CR-1T, £1.13.6 incl. P.T. IF/AF Amplifier Kit CR-1A, £11.3.6.

TOTAL PRICE KIT (excluding loudspeaker) £12.17.0 incl. P.T.
 8 x 5in. Loudspeaker, Pt. No. 401-505, £1.8.6 incl. P.T.

The Transistor Amplifier you have been looking for !

3 + 3W Stereo Amplifier Kit, TS-23



Breaks the price barrier in quality transistor amplifier cost

Incorporates all the essential features for good quality reproduction from gramophone records, radio and other sources. Its many features include: 3 watts rms (15Ω) each channel. Good frequency response for outstanding fidelity. Compact slim-line styling. Ganged BASS, TREBLE and VOLUME controls. Six position SELECTOR switch for programme sources. Attractive perspex front panel, two-tone. 16 transistor, 4 diode circuit. Handsome fully finished walnut veneered cabinet. Outputs for 8 or 15 ohm loudspeakers. Printed circuit boards for free-standing or cabinet mounting. Size 3½ x 13 x 8in. deep.

Prices Amplifier Kit **£17.15.0**
 Amplifier kit & Cabinet **£18.19.0**

Walnut veneered Cabinet separate **£2.0.0**

Hi-Fi performance from a "Mini" speaker kit with the 'AVON' BOOKSHELF SPEAKER SYSTEM



The challenge to our acoustic engineers was to design a speaker occupying the minimum space consistent with first class reproduction. The result of our efforts was the AVON, a compact unit of exceptional quality. Features two special speakers 6½in. BASS, 3½in. HF unit and cross over network. Good frequency response. Beautiful fully finished walnut veneered cabinet. Size only 7½ x 13½ x 8½in. deep. Supplied in two units. Can be built for a total price

KIT £13.16.0 incl. P.T.


A 3" Service Oscilloscope kit with outstanding features. Model OS-2

The attractively styled OS-2 is a compact, lightweight, portable and surprisingly versatile oscilloscope that fulfils many of the general requirements in Laboratories, Service Departments and Educational Training. It is ideal for use in production line testing where otherwise expensive equipment would be tied up on ordinary routine tests. The bandwidth of the OS-2 is from 2 c/s-3 Mc/s ± 3dB, this 'scope can therefore be used in applications ranging through audio, ultrasonic and radio frequencies. The time base operates from 20 c/s to 200 kc/s in four ranges and is self-synchronising.

Size 5 x 7¼ x 12in. deep. Weight 9½ lb.

KIT £23.18.0 Assembled **£31.18.0**

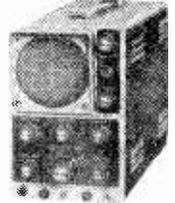Optional extra. L/Cap Probe kit, PK-1. **KIT £3.12.6**



Many other models in wide range.

Prices quoted are Mail Order

Full specification sheets of any model available upon request.

FREE

BRITAIN'S LARGEST ELECTRONIC KIT CATALOGUE
 GET YOUR LATEST COPY NOW →

WHEN IN LONDON visit our
HEATHKIT CENTRE
 233 Tottenham Court Road, W1
 Tel: MUSEum 7349

See a full range of British models and a selection of American Heathkit models.

HEATHKIT

DAYSTROM LTD., Dept. PW-3
 GLOUCESTER, ENGLAND

Please send me model(s)
 for which I enclose £ s d post paid.

Please send me FREE British Heathkit Catalogue.

NAME

ADDRESS

.....

COMPARE THESE PRICES

ELECTROLYTIC CONDENSERS

64μF ..	2.5 volt	30μF ..	10 volt
125μF ..	2.5 volt	3μF ..	12 volt
640μF ..	2.5 volt	4μF ..	12 volt
0.25μF ..	3 volt	25μF ..	12 volt
2μF ..	3 volt	200μF ..	12 volt
40μF ..	3 volt	2.5μF ..	16 volt
4μF ..	4 volt	64μF ..	16 volt
500μF ..	4 volt	200μF ..	16 volt
5μF ..	6 volt	750μF ..	18 volt
20μF ..	6 volt	2.5μF ..	25 volt
25μF ..	6 volt	3μF ..	25 volt
30μF ..	6 volt	4μF ..	25 volt
50μF ..	6 volt	10μF ..	25 volt
100μF ..	6 volt	25μF ..	25 volt
3.2μF ..	6.4 volt	12.5μF ..	40 volt
40μF ..	6.4 volt	3.2μF ..	64 volt

All at 1/- each, 9/- per dozen or mixed packet (our selection), 20 for 10/-.

150μF, 25 volt; 500μF, 25 volt, 2/6 each. 5,000μF, 12 volt, 4/- each. 200/100 275 volt; 200/200 275 volt; 125/300/50 275 volt, 5/- each; 3 for 10/-.

PAPER CONDENSERS SPECIAL CLEARANCE!

0.35μF, 150 volt; 0.02μF, 350 volt; A.C. 0.25μF, 350 volt; 0.5μF, 350 volt; 0.5μF, 500 volt; ALL at 15/- per 100.

Mixed packet containing 0.0001μF, 200 volt, to 0.5μF, 500 volt. Very useful for service work! 50 condensers for 10/-.

RESISTORS. ½ watt, well assorted values, 10/- per 100; 55/- per 1,000. ¾ watt to 3 watt, well assorted values, 10/- per 100; 55/- per 1,000. TO CLEAR: 10 Meg. 1/6th watt resistors—to clear £1 per 1,000.

TRANSISTORS. Untested, mixed, 50 for 10/- . NPN Switching transistors, Min. 200 m/cs., 6 for 10/- . PNP Switching transistors, Min. 200 m/cs., 6 for 10/- .

DIODES. Suitable for keying electronic organs, 20 for 10/- . BY100 type rectifiers, 30/- per dozen. ORP12 light cells, 9/- each.

TRANSISTOR BATTERY ELIMINATOR—same size as PP9. 30/- . PP6, £1.

BATTERY CHARGERS with meter, 4 amp., 6 or 12 volt, 55/- .

LABEL MICROPHONES, crystal or magnetic, 10/- each.

MINIATURE EARPIECES complete with plug and lead, 5/- each.

SIGNAL INJECTOR, parts and circuit to make, 10/- each.

SIGNAL TRACER, parts and circuit to make, 10/- each.

MOTOR CAR REV. COUNTER, parts and circuit to make, 10/- each.

PORTABLE RADIOS—complete with leather case, earpiece etc., fully guaranteed, 79/6 complete.

ACOS PICK-UP HEADS, Mono, 10/-; Stereo, 12/6; Diamond, 17/6.

SAPPHIRE STYLI, TC8LP, GC2LP, GC8LP, BF40LP, GP67LP, TC8 Stereo LP, Studio O LP, GP37, GP59, ALL at 3/6 each.

POTENTIOMETERS—pre-set, 100 ohm to 680 K.ohm., 12 for 10/- (mixed).

MAGNETIC RECORDING TAPE

British made, fully guaranteed

Standard Play. 3", 150 ft., 3/6; 5", 600 ft., 10/6; 5½", 900 ft., 13/6; 7", 1,200 ft., 16/3.

Long Play. 3", 225 ft., 4/-; 5", 900 ft., 12/9; 5½", 1,200 ft., 15/9; 7", 1,800 ft., 21/6.

Double Play. 3", 300 ft., 6/6; 5", 1,200 ft., 20/-; 5½", 1,800 ft., 28/-; 7", 2,400 ft., 34/-; 2½", 300 ft., 6/9.

Triple Play, Polyester. 3", 600 ft., 12/6; 4", 900 ft., 16/6.

WELLER INSTANT HEAT SOLDERING KIT, 72/6 complete.

WELLER DUAL-HEAT SOLDERING GUN, only 57/6 complete.

PISTOL GRIP SOLDERING IRON only 10/-.

PHILIPS/STELLA/COSSOR remote control unit, value 3 gns., our price 10/-.

RUMBLE AND SCRATCH FILTER parts and circuit to make, 30/-.


TRANSISTORS, COMPONENTS, AND CIRCUIT to convert 1ma. meter to 0 to 10 Meg. ohmeter, 10/-.

G. F. MILWARD

17 PEEL CLOSE, DRAYTON BASSETT, Nr. TAMWORTH
Staffs. TAMWORTH 2321 POST ONLY

Due to recent heavy increase in parcel rates, please include part postage cost.

RECORD HOUSING

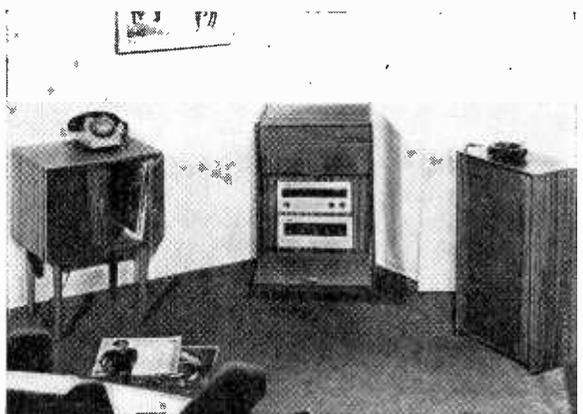

Does your hi-fi cause disharmony in the home? Does it clutter up the room? Does it irritate your wife? Why not bring harmony into the home with Record Housing? Our Compact Record Cabinet (£8.8.0) with matching Nielsen Equipment Cabinet (£18.8.0) and Folded Horn Speaker Enclosure (£10.19.0) will blend harmoniously into any setting.

Whatever your set up there's a Record Housing Cabinet to meet your needs. Amplifiers, tuners, turntables, loudspeakers, records, tapes, tape decks—and even a complete tape recorder—you name it—we'll house it! Send for fully illustrated catalogue describing over 20 different cabinets and U.K. stockists' lists.

FREE HI-FI HOUSING ADVISORY SERVICE

RECORD HOUSING (Dept. P.W.3)

Brook Road, London N.22

Tel.: BOWes Park 7487

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAME

Block

ADDRESS

Caps.

.....

Please

3.67

BRITISH NATIONAL RADIO SCHOOL

band in the evening—9,670 and 9,720kc/s. The WRTH will also show that the Swiss Broadcasting Service utilises 9,665kc/s for its evening service to the U.K. from 1845 to 2015 G.M.T. in English.

This transmission can hardly be missed and it then becomes a question of finding the Swiss programme, waiting for the close down and then listening for a station using Arabic as its main language on a channel only 5kc/s away. With the bandwidth of the average receiver, as S.B.C. leaves the air so Jeddah will (one hopes) be heard, and the tuning knob will only need to be moved a fraction to bring it in at maximum strength.

It should be mentioned that S.B.C. uses the same channel again at 2030 G.M.T. for its Spanish and Portuguese service, so one must look snappy and get the pencil recording details of the Saudi Arabian programme if one is to submit a report and ask for a QSL.

The instance mentioned is an actual case history, and the same method has been used on numerous occasions to locate the less familiar countries. At the time this article was written the frequencies mentioned were in use by the stations concerned but they may, of course, be changed when this article appears.

A "scientific approach often pays off, but luck can also play a part. The author, while on holiday, was determined to find four elusive countries. The approved method produced not a flicker of the "S"-meter, not a sound. A fortnight later, idly tuning the bands, not looking for anything in particular, three of the countries concerned were logged and the fourth followed, on a similar occasion, a week later. The best laid schemes of DX listeners often fail to trap the quarry, but when they do succeed (or even if it is just luck) it is nice to write "Will you please QSL?"

Finally a word regarding reception reports. Most of the world's broadcasting stations require a minimum of 10 minutes programme details before they will verify a report, and some require longer. Essential information in a report is:

- (a) the date and time (in G.M.T.).
- (b) the frequency or wavelength of the broadcast.
- (c) details of the receiver and aerial used and
- (d) a report in the SINPO code, or else a general indication of the strength of the signal, the interference and noise level (identifying the source of interference, if possible) together with an estimate of the overall quality of reception.

In addition brief programme details should be given together with the times of the various items—for example:

- 1955 G.M.T.: Station identification in French and News (give items if possible).
2000 G.M.T.: Time signal (pips) and station identification.
2001 G.M.T.: Announcement—Frank Sinatra song (give titles of musical items if possible).

Before sending off a report—indeed, before even writing it, if only to save the cost of Air letters—it is essential to consider whether you have given all the information one can to enable the station to be certain that you have received their programme. You must provide sufficient definite data to permit a check against the station log.

Making SWL Reports . . .

OVER the past years, the writer has received a large number of s.w.l. reports. It is an unhappy fact that out of every hundred received only about two are of any real use and warrant the sending of a QSL card. This startling figure (2%) is borne out in conversations with other amateurs who also appear to be inundated with useless scraps of paper.

If a station receives a useful report from an s.w.l., it is highly probable that a QSL card will be sent. The following notes are intended as a general guide for those s.w.l.'s. who don't get replies, or for those just starting to listen on the amateur bands and short-waves.

1. First, the report should be legible. About 10% fail on this count. Remember that amateurs in other countries may not speak or read fluent English, so legibility is of paramount importance.

2. The time should be specified in G.M.T. using the 24-hour system and the letters G.M.T. written after to avoid any misunderstanding.

3. Your QTH or locality. If you live in a small village, then a reference to the nearest large town should be included i.e. Harpenden—6 miles N.W. of St. Albans. Also if possible the height a.s.l.

4. Equipment in use. Don't just put "superhet" for the receiver. It might be a simple 3 valve job or a 16 valve triple-conversion unit.

5. Aerials are very important. The type of aerial, and the length in the case of a longwire should be noted. Also, most important, the direction it points, that is looking straight down the wire. The height is also a useful item to put down, too. An example of this, for a longwire might be—68ft. end fed running N.E./S.W., 30ft. high. Again if a dipole is used this fires broadside to the direction of the wire, i.e., 90° to it and this should be remembered when giving a report.

6. The following are the standard items and are usually the only things put down. Those s.w.l.'s. who only include these items and nothing else can be congratulated on producing a near useless report in most cases. By themselves they aren't much use, but with all the other information referred to they are vital.

- (a) RST. Readability, Signal strength, and (in the case of c.w.) Tone.
- (b) QRM. Interference.
- (c) QRN. Atmospherics.
- (d) QSB. Fading.
- (e) QRG Frequency.

Relevant reports on other signals received during the same period are very useful too, especially from the same area if the station happens to be either very strong, very weak, or perhaps fading compared with the other signals on the band.

7. The frequency should be given accurately. If possible a simple crystal frequency standard should be fitted to the station and the receiver dial calibrated against it. At each session of listening, after the receiver has warmed up, the dial should be checked and adjusted to ensure that the receiver dial reads accurately.

8. S-Meter readings should be qualified. Many S-meters are included in the receiver in such a

way that they are affected by different settings of the various controls. Perhaps the best way is to set the controls to a particular setting and feed in a signal of known strength, i.e. so many microvolts and mark this on the meter as say S9 plus 40dB.

Or perhaps a signal with an S9 carrier could be used to make some form of calibration. This reference, however the meter is set up, should be put in the report. The signal level of the other station in the QSO together with callsign should also be included, if it can be heard.

The above notes are not rigid. However a report based on these would stand a very much greater chance of a QSL than the more usual "Heard you 5 and 7 here on a superhet, please QSL".

An example report is given below in order to show the general pattern. Compare this with the classic "Heard you here 5 and 7" etc.

M. Jenkins, 38 Malsen Road, Menton, Bedfordshire, England. Six miles S.W. Bedford. Latitude Longitude Approximately 300 ft. a.s.l.

Equipment.

Seven valve single conversion superhet. One r.f., f.c., two i.f., two a.f., b.f.o. Headphone reception.

Antenna.

Half wave dipole co-ax fed plus balun, 40ft. high running N.E./S.W.

Date/Time/Frequency.

Monday 28th March, 1966. 0022 G.M.T. 14155 kc/s.

Signal Report.

W6ZZZ/P. Your a.m. signals RST 58. In QSO with—AP2XXX. His a.m. signals RST 55.

QRN/QRM/QSB.

QRN: Nil. QRM: Slight/moderate from local G 5 kc/s h.f. QSB: Slight from 57/58.

S-Meter.

S-Meter calibration, 1 μ V in reads S9.

Remarks.

Also heard W6XXX/M at 5 and 5 but no QSB. W1/W2's received 0001-0130 all average 5 and 7, no QSB. Heard you on March 20th, 1966 in QSO with ZL9XXX when you were 559, conditions about the same as above.

Would very much appreciate a QSL card. Stamps/IRC's enclosed.

PRACTICAL TELEVISION

WIDE RANGE WOBBULATOR

All transistor design covering 400 kc/s to 39 Mc/s

U.H.F. AERIALS

Details of aerial design—including constructional details

HUM IN TV RECEIVERS

How to locate and cure this common fault

February issue on sale now 2s.

FUTURE BROADCASTING PLANS

—continued from page 849

"They consider that this objective would prove incompatible with the commercial objectives of companies engaging in local sound broadcasting; and that, in result, the former would be likely to suffer. While the Government do not, in principle, rule out advertising as a means of financing broadcasting stations in public ownership, it is in their view of first importance to maintain public service principles in the further development of the broadcasting services; and accordingly they reject the view that a service of local sound radio should be provided by commercial companies.

"Evidence of the expertise and professional enthusiasm which the BBC could bring to local sound broadcasting is to be found in the 'trial programmes' they have prepared. They lend much support to the view that, properly organised, local radio would provide a valuable service to the local community; and, by giving a new means of expression to its particular interest and aspirations, serve to reinforce its distinctive character and sense of identity.

"The Government believe that local radio organised and produced as a public service, would be most likely to realise those social purposes to the full; and would at its best prove an integrating and educative force in the life of the local community. But it is, they consider, important to establish how far the claim for a local station is likely to rest on genuinely local initiative having these purposes as its objectives; and how far local sources of finances are likely to be available to meet the expenditure required by such an initiative. In sum, not only is it important to establish that a local service of high quality could be maintained, month-in, month-out. There is also the question whether it would command enough support, including financial support, to justify the development of a service on a widespread and permanent footing . . .

"In considering how an experiment should be conducted, the Government have had regard not only to the need to avoid an excessive diversion of resources for the purpose but also the undesirability of entering into a commitment at this stage to any permanent form of constitution and organisation. They conclude that these various requirements will best be met if the experiment is conducted by the BBC as a venture in co-operation with local interests; and they have therefore decided to authorise the BBC to go ahead with a nine-station project in v.h.f. The stations would offer a full-scale local service. They would come into operation after about a year; and after a year or so of operation, should have provided the information on which to found the final solution . . .

"The Government reserve until the conclusion of the experiment any decision on the question whether a general and permanent service should be authorised, and, if so, how it should be constituted, organised and by whom provided, as well as how it should be financed. The decision that the BBC should conduct the experiment implies no commitment that the Corporation should provide a permanent service; if it were decided to authorise one."



EVERYTHING YOU WANT IN COMPONENTS

Accessories, equipment, service

TRS FM STEREO DECODER

Outstanding Value and Performance

Based on Mullard's proven circuitry, this is a six transistor, printed circuit unit size 5 1/2 x 2 1/4. Two stage transistor Stereo Beacon Indicator is incorporated. Operates from 12 v. supply. Neg. earth. Basic Kit supplied suitable for Transistor Tuner input and Transistor Amplifier output. With simple mods (data supplied with Kit) the unit is easily adapted for Valve Tuners and Valve operated equipment. Kit and assembly instructions, complete with Mullard specified Inductors, Type WF2949 and WF2951. Complete kit as described.

£4.19.6 With coils tested and pre-aligned **£5.50**
Carriage either kit 2/6. 6d. stamp for circuit and data.

MULLARD FM DECODER COILS

Designed and made by Mullard, these inductors are as used in T.R.S. Decoder above. TYPE WF2949 and WF2951, each 25/- Per pair 49/6. Post free.

ENAMELLED COPPER WIRE—2 oz. reels. 14 g.-20 g. 3/-; 22 g.-28 g. 3/8; 30 g.-34 g. 4/3; 36 g.-38 g. 4/3; 39 g.-40 g. 5/- etc.
TINNED COPPER WIRE. 16-25 g. 4/- 2 oz.
BONDACOUST Speaker Cabinet Acoustic Wadding (lin. thick approx. 1 1/8 in. wide, any length cut, 6/- yard, 2/3 per foot.
VEROBORD—All sizes including 2 1/2 in. x 3 in. 3/8; 2 1/2 in. x 3 1/2 in. 3/4; 3 in. x 5 1/2; 3 1/2 in. x 3 1/2 in. 3/8; 3 in. x 1 7/8; 1 7/8. All accessories and tools in stock.

VOLUME CONTROLS. LOG and LINEAR. We carry very large stocks in the widest possible range of values, single and ganged. 5K-2 M 1/2 3in. Spindles Morganite Midget Type 1 1/2 in. dia. n. Guar. 1 year. LOG or LIN ratios less Sw. 8/6. D.P. Sw. 5/- Twin Stereo less Sw. 7/6. D.P. Sw. 8/6 (100k to 2 Meg. only).

STEREO BALANCE CONTROLS. Log/Anti-Log 5K Ohm. 1/2, 1, 2 Meg. 9/- each.

ERSIN MULTICORE SOLDER. 60/40 4d. per yard. Cartons 6d. 1/4 2/6 etc.

WIREWOUND RESISTORS. 25 ohm to 10 K 5 w. 1/3. 10 w. 1/8. 15 w. 2/-

CONDENSERS Silver Mica. All values 2 pf to 1,000 pf. 6d. ea. Ditto ceramic 8d. Tub. 450 v. T.C.C. etc. .001 mfd to 01 100. and 1/250 v. 10d. .02 MF to 0.1 MF. 500 v. 1/- .25 T.C.C. 1/8. 5 T.C.C. 2/-

CLOSE TOL. S/MICAS. 10% 5 pf. 500 pf. 9d. 500-5,000 pf. 1/- 1% 2 pf.-100 pf. 11d 100 pf.-250 pf. 1/2. 270 pf.-800 pf. 1/4. 800 pf.-5,000 pf. 2/-

ALUMIN. CLASSIS. 18g. Plain undrilled folded 4 sides. 2in. deep. 6in. x 4in. 4/8; 8in. x 6in. 5/9; 10in. x 7in. 6/9; 12in. x 6in. 7/6; 12in. x 8in. 8/- etc.


ALUMIN. SHEET. 18 g. 6in. x 6in. 1/-; 6in. x 9in. 1/6; 6in. x 12in. 2/-; 12in. x 12in. 4/- each.

TYGAN FRET (Contem. patt.) 12in. x 12in. 2/-; 12in. x 18in. 3/-; 12in. x 24in. 4/- etc.

6 VALVE A.M./F.M. TUNER UNIT

In Kit Form with or without Power Pack

Med. 190 m., 550 m., V.H.F.—86 Mc/s. 103 Mc/s., 6 valves and metal rectifier. Self contained power unit. Magic-eye, 3 push-button controls, on/off, Med., V.H.F. Diodes and high output sockets with gain control. Illuminated 2-colour perspex dial 1 1/2 in. x 4 in. chassis size 1 1/2 in. x 4 in. x 5 1/2 in. Strongly recommended for use with Mullard amplifiers. For A.C. mains 200/250 v. Unstable value. Complete kit, inc. Power Pack as illustrated, 11 gns. Carr. 7/6. Ditto Test Power Pack, 10 gns. Carr. 7/6. Circuit and construction details, 4/6. Free with kit.

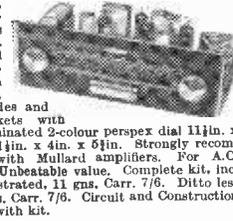

- ★ VERY LARGE RANGES ALWAYS AVAILABLE
- ★ PERSONAL ATTENTION TO ALL ORDERS AND INQUIRIES
- ★ PROMPT RETURN SERVICE
- ★ GENUINE BARGAINS IN ALL DEPARTMENTS
- ★ SATISFACTION GUARANTEED ON ALL TRANSACTIONS

TRS ALWAYS HAVE THEM!

Resistors in widest possible range of values and tolerances. Examples:—
1% Hi-Stab 1 w. 100Ω-100Ω each 2/-
1% Hi-Stab 1 w. values over 100Ω each 1/6
5% Hi-Stab 10Ω to 1 meg. 1 w. 5d. 1/2 w. 6d.
10% Hi-Stab 2 to 10 meg. 1 w. 6d. 1/2 w. 6d.
10% Standard 1 w. 1 w. 4d. 1/2 w. 6d.
Send to TRS first for all you want!

TRANSISTOR COMPONENTS

Midget I.F. Trans. 9/16 in. dia. Weyrad, etc. 1st, 2nd or 3rd IF ea. 5/6. Osc. Coil 9/16 in. dia. Med. and LW 5/-. Ditto REPANCO 1/2 x 1/2 x 1/2 in. standard type 1st, 2nd and 3rd IF. Osc. Med. and LW ea. 6/-. Double Tuned type ea. 6/9. Miniature Push-Pull Driver Transist. (Type TT45) Ratio 9:1 6/-. Miniature Push-Pull O/P Transist. (Type TT46) Ratio 8:1 6/-. Midget RF Chokes (for Med. and LW) 2.5mH, 8mH, 7.5mH, 10mH ea. 2/6.
POLYESTER MINI CONDENSERS—Ideal for P/ct use. 200 v wg. .01 9d.; .022 9d.; .033 11d.; .047 11d.; .068 1/-; .1 1/1.

MIDGET TRANSISTOR ELECTROLYTICS—T.C.C. etc. 8d. range, all values 1 mfd-50 mfd. 15 volt, working each 1/8. 100 mfd 12 v. 2/-, 1000 mfd 6 v. 2/3.
Special Electrolytics for Transistor Mains Units. 1000 mfd 25 v. 4/6; 2000 mfd 50 v. 6/8; mfd 75 v. 7/6; 3000 mfd 15 v. 5/9.

TRANSISTOR CONDENSERS—Hunt's, T.C.C. etc. 150 v. working. 0.1 mfd., .02 mfd., .03 mfd., .04 mfd. 10d. .05 mfd., .1 mfd 1/- .22 mfd 1/3. 47 mfd 1/6.

3 WATT TRANSISTOR AMPLIFIERS—(Newmarket PC3+), 6 Transistor, 3 ohm Output. Size 5 1/4 x 1 1/2 x 1 1/2. 5-8 mV sensitivity. Excellent High Gain Med. Imp. Audio Amp. 75/- Post 1/- 9 v. PP3 battery 2/8 and 3 ohm speaker extra.

SUB-MIN. RESISTORS 1/10th watt, 10% tolerance, each 6d.

BATTERY HOLDER—Takes 4 U7 Batteries, 2/9.

MAINS UNIT for TRANSISTOR SETS—200/250 v. AC for replacing or reactivating PP3 or PP6 Battery Units 24/6. Post 1/-. Ditto for PP9 batteries 29/6. Post 1/-.

TUNING CONDENSERS—J.B. "000", 208 pf x 176 pf 8/6. Ditto with Trimmers 8/6, 220 pf x 105 pf with concentric slow motion drive 10/8. Single 365pf 7/6. Sub-min. 1 in. J.B. DILEMMIN .0003 or .0005 mfd 8/- each.

MIN. Slide Type WAVE CHANGE SW—1 x 1 1/2 x 2 p. 2 way 2/8. 3 Way Push Button W/O Change SW—3 push buttons engraved Long, Med., OR. 1 1/2 x 1 1/2 in. Manufacturers surplus. Bargain 5/6.

VOLUME CONTROLS—Midget Transistor type. 5K with Switch, complete with edge Control Knob, ea. 4/9. Ditto less Switch 3/8.

MINIATURE DEAF-AID EARPHONE. Continental Type—high imp. Xtal Earpiece, supplied with earplug insert, 3ft. lead and miniature Jack plug, ea. 8/-. Ditto low impedance magnetic type, ea. 7/6.

ROCKER SWITCH—Mains voltage type. Chassis mounting size 1/2 x 1 in. S.P., D.P. or change over, 3/6. Transistor Holders. 3 pin 1/-; 6 pin 1/3. Ferrite Aerial Rods. 4 x 3/16 in. 1/6; 5 x 1/8 in. 2/-; 6 x 1/4 in. 2/-; 6 x 1/2 in. 3/6; 8 x 1/2 in. 2/9; 8 x 3/16 in. 2/9; 8 x 1/2 in. 3/6. Ferrite Slab 3 x 1/2 in. 1/6.

TRANSISTOR DRIVEN SPEAKERS
3ohms—2 1/2 in. High-Flux EMI. Ideal for pocket Transistor Kits. 17/6. P. & P. 1/9. 8 ohms—2 1/2 in. Continental Speaker. Exceptional value. 13/6. P. & P. 1/9. 35 ohms—5in. Goodmans. 21/6. P. & P. 1/9. 75 ohms—2in. Pleseey. Ideal Push-Pull. OCS1 etc. BARGAIN 15/6. P. & P. 1/9. 80 ohms—2 1/2 in. Pleseey. 15/6. P. & P. 2/-.

BARGAIN OPPORTUNITY

7 valve AM/FM/RG Replacement Chassis

A superbly powerful, high performance instrument which makes the ideal way to modernise old equipment whilst retaining good cabinet work. Provides tuning on long, medium and F.M. wavebands with permeability tuning on F.M. Large clear dial with stations clearly named. A.V.C., good neg. feedback, Magic eye. Connections for speaker, P.U. and Tape outlet, 3 w. output. A.C. 200/250 v. Circuit diagrams available.
Aligned, tested and ready for use. (Carr. and ins. 8/6.)
£13.19.6 S.A.E. brings full details.

T.R.S. MULLARD 3-3 AMPLIFIER. Kit £7.10.0. Built and tested £9.10.0.
T.R.S. MULLARD 5-10 AMPLIFIER. Kit £9.19.6. Built and tested £12.1.6. Carr. on any of above items 7/6 each.
MULLARD Stereo Pre-amp and 10 + 10 watt Amplifier in process of production. AVAILABLE VERY SHORTLY.

PEAK SOUND STEREO AMP

With integrated pre-amp. Uses Cir-Kit for easy building. Model SA-8-8 has 14 matched transistors; 20-20,000 c/s + 3dB. Specially for use with high quality ceramic P.U.s. For 3-ohm speakers. Output 8.5 watts per channel. A high quality instrument for easy building and reliability. Will fit in safely under motor board to keep your cabinet work looking slim. Complete with instructions £12.19.6. P. & P. 4/- PEAK SOUND POWER PACK 75/- (p/p 5/6)

"CIR-KIT" INSTANT CIRCUITS

Enables you to produce "printed circuits" quickly and cleanly without chemical or elaborate processes. Kit No. 3 includes baseboard, processed copper strip and 15/- sheet as advertised.

TAPE BARGAINS

1500ft. 7in. REEL. American professional tape. Leader and stop folds. In sealed boxes. 17/6 per reel (p. & p. 1/- for one. 6d. each after first when ordered together).
UNIQUE DOUBLE SIDED TAPE. 5 1/2 in. reels. Superb quality used normally. Ideal for experimenters too. 650ft. 9/-, 600ft. 8/6. (P. & P. 1/- per single reel. 6d. for each additional).
PLASTIC REELS. 3in. 1/3; 4in. 2/-; 5in. 2/-; 5 1/2 in. 2/-; 7in. 2/8.

SINCLAIR KITS

We carry full stocks of these world-famous all-British designs including the very latest as advertised by this famous firm and give prompt delivery.

NEW MICROMATIC World's smallest radio. As advertised. Kit 59/8. Ready built 79/6. **MICRO FM** 7 transistor FM Tuner Kit £5.19.6. Z18 Amp and pre-amp. built £4.9.6. **STEREO** 25 Pre-amp built £9.19.6. PZ3 Power Pack £3.19.6.

A UNIQUE TRANSFORMER SERVICE

We manufacture Transformers and Chokes of all types to stock or customer specification. Enquiries invited for prototype and small runs.

GARRARD UNITS & PLINTHS

LM.3000 Record Player with 9T.P. Stereo Cartridge. Limited number available. Brand new as from factory 8 gns.
AT.80 De-luxe Auto-change. 12in. turntable. Superbly engineered. Less carriage 9 1/2 gns.
SP.25 De-luxe single record player, less cartridge 9 1/2 gns.
Packing and carriage on any one of above, 7/6 extra.
Garrard Plinth. The ideal modern mounting for the Garrard Units offered here. Will readily suit any hi-fi set-up. Drop-on plastic cover. Packing and carriage 9/- 72/6
Garrard Mono Cartridges from 15/-; Stereo from 25/-

A SURPRISING 3d. WORTH

When you send a 3d. stamp for the latest TRS Bargain List (Feb. issue), you will find not only bargains galore to make genuine savings but even more advantages that come from buying the TRS way.

PACKING AND CARRIAGE

Terms: Cash with Order or C.O.D. Post and Packing—1lb. 1/-; 1lb. 1/9; 2lb. 3/6; 6lb. 5/-; 10lb. 6/6; 14lb. 8/-; over 10/6. Please mention P.W. when ordering.

TRS RADIO COMPONENT SPECIALISTS

Est. 1946

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

Phone: THO 2188 • Daily 9.0 a.m. to 6.0 p.m. • Wednesdays 1.0 p.m.

A few doors from Thornton Heath Stn. S.R. from Victoria

Why

NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

FIRST FOR PERFORMANCE, QUALITY & PRICE!

BACKED BY OUR SUPER AFTER SALES SERVICE

"A wonderful range of transistor radios using first grade components for guaranteed results."

NEW ROAMER SEVEN Mk IV

7 WAVEBAND PORTABLE OR CAR RADIO
 Amazing performance and specification ● Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS

FULLY TUNABLE ON ALL WAVEBANDS ● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned 7 x 4in. speaker. Air spaced ranged tuning condenser. Ferrite rod aerial for M. & L. Waves and telescopic aerial for S. Waves. Real leather-look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx.


The perfect portable and the ideal car radio. (Uses PP7 batteries, available anywhere.)

★ EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, etc.

Total cost of parts now only **£5.19.6** P. & P. 5/6



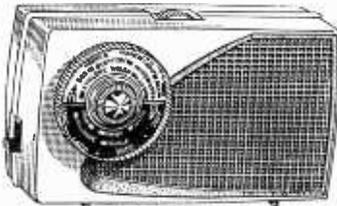Parts Price List and easy build plans 3/- (Free with kit)



NEW MELODY MAKER SIX

3 WAVEBAND PORTABLE 8 stages—6 transistors and 2 diodes

Covers Medium and Long Waves and EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, etc. Top quality 3in. Loudspeaker for quality output. Two RF stages for extra boost. High "Q" 6in. Ferrite Rod Aerial. Approx. 350 milliwatts push-pull output. Handsome pocket size case with gilt fittings. Size 6½ x 3½ x 1½in. (Uses long-life PP6 battery.) Carrying strap 1/6 extra.

This amazing receiver may be built for only

£3.9.6 P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit).



NEW TRANSONA FIVE

Now with 3in. Speaker!
 "Home, Light, A.F.N., Lux. all at good volume." G.P., Durham.

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser volume control, new type fine tone super

dynamic 3in. speaker, etc. Attractive case. Size 6½ x 4½ x 1½in. with red speaker grille. (Uses 1289 battery, available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/6 Parts Price List and easy build plans 2/- (Free with kit)

POCKET FIVE Now with 3in. Speaker!

● 7 stages—5 transistors & 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 3in. moving coil speaker built into attractive black and gold case. Size 5½ x 1½ x 3¼in. (Uses 1289 battery available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/- Parts Price List and easy build plans 1/6 (Free with kit)



STOP PRESS!
 Pocket 5 med. and long wave version with miniature speaker.
29/6 P. & P. 3/-



NEW ROAMER SIX

NOW, WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND !!

● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and

Long Waves, Trawler Band and two Short

Waves. Sensitive Ferrite rod aerial and telescopic aerial for short waves.

Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 7½ x 5½ x 1½in. (Carrying strap 1/6 extra.)

★ EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, ETC.

Total cost of all parts now only **£3.19.6** P. & P. 3/6 Parts Price List and easy build plans 2/- (Free with kit)

TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade 3in. speaker makes listening a pleasure. Push-pull output. Ferrite rod aerial.

Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6½ x 4½ x 1½in. (Uses PP4 battery available anywhere.) Carrying Strap 1/- extra.

Total cost of all parts now only **59/6** P. & P. 3/6 Parts Price List and easy build plans 1/6 (Free with kit)



MELODY SIX

● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering Medium and Long Waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. Ferrite rod aerial. Push-pull output. Wonderful

reception of BBC, Home and Light, 208 and many Continental stations. Hand-

some leather-look pocket size case, only 6½ x 3½ x 1½in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

Total cost of all parts now only **£3.9.6** P. & P. 3/6 Parts Price List and easy build plans 2/- (Free with kit)



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 RF Stages. Special push-pull output, 3in. speaker (will drive large speaker). Size 7½ x 6½ x 1½in. (Uses 8V battery, available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6 Parts Price List and easy build plans 2/- (Free with kit)

Callers slide entrance
 Barratts Shoe Shop.


RADIO EXCHANGE CO.

Open 9—5 p.m.
 Saturday 9—12.30 p.m.

61 HIGH STREET, BEDFORD Telephone: Bedford 52367

LOW COST PSU

F. L. THURSTON

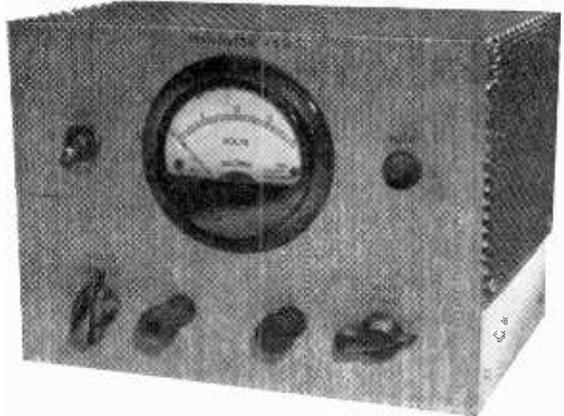

IN professional laboratories, considerable use is made of stabilised power supply units for experimental and development work, since these units have a low output impedance and give a constant output voltage over a very wide range of current demands.

To be really useful, a variable voltage power supply unit should have an output impedance, or effective internal resistance, that is comparable to that of a conventional battery, and should be reasonably well stabilised against changes in mains supply voltage, etc. The unit that forms the basis of this article has been designed with these points in mind.

Simplest form

The simplest way of obtaining a variable voltage power supply is to wire a variable resistor across a normal power supply, and take the output from across the slider, as shown in Fig. 1a. This, however, is rather wasteful of power, gives a high effective internal resistance, and does not guard against changes in the supply voltage. An improvement over this basic system is shown in Fig. 1b. Here Tr1 is wired as an emitter follower, with its base connected to the slider of VR1, and the output voltage is taken from across R1 in the emitter line of Tr1. The emitter voltage of this transistor "follows" very closely the voltage on the base. Taking very little power from VR1, the transistor presents a high input impedance while at the same time giving a low output impedance, and thus presenting a low effective internal resistance.

A further improvement which is shown in Fig. 1c, increases the effective gain of the transistor. Here, Tr1 and Tr2 are connected as a Darlington (or Super-Alpha) pair, the emitter current of one transistor feeding directly into the base of the other, with a current gain equal to the product of the individual gains of Tr1 and Tr2.

For example, if both transistors have current gains of 50, the effective current gain of the combination "transistor" will be 2,500 and the output impedance of the circuit will be correspondingly low.

Both of these transistor circuits give a variable voltage output with little power wastage and have reasonably low effective internal resistance, but neither circuit is stabilised against changes in supply voltage. This problem can be overcome by modifying the circuit as shown in Fig. 1d. Here, the voltage that is used to feed VR1 and the base of Tr1, is stabilised by the Zener diode, D1, the actual supply that is connected across the transistor circuit is not. However, the output voltage is approximately the same value as that at the slider of VR1 and is thus stabilised against changes in the mains voltage. This circuit (shown in Fig. 1d) is very useful, but its power handling requirements are limited by the output transistor, Tr2. If the unit is to give output voltages up to 18 volts, it is necessary to use an un-stabilised input supply of at least 22 volts. If an output of 6 volts is required, 16 volts must be dropped across the output transistor. This means Tr2 will have to dissipate 16 watts with a 1A output current.

Finalised circuit

These problems are overcome in the circuit of the finished power supply unit, as shown in Fig. 2. Here, the output voltage is varied in three ranges, and the un-stabilised input voltage is varied to suit the range in use, thus ensuring that a minimum of power is lost across the output transistor Tr3. A complete description of the circuit follows:

The mains supply is connected to transformer T1 via switch S1. Switch S2a selects either the 5, 11, or

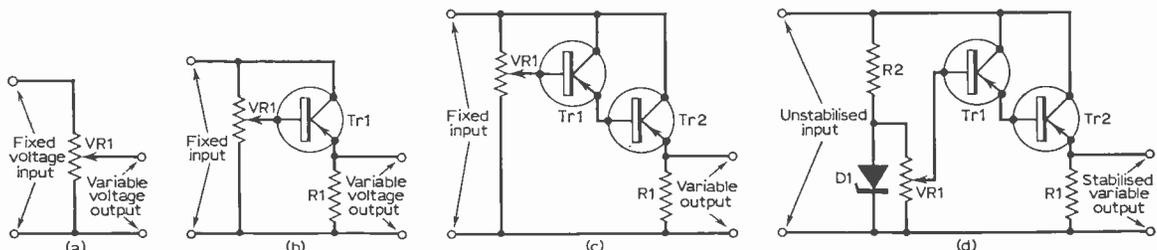


Fig. 1: (a) Basic circuit, (b) improvement by the addition of an emitter follower, (c) replaced by super-alpha pair emitter follower, (d) the Zener diode stabilises the circuit against changes in the supply voltage.

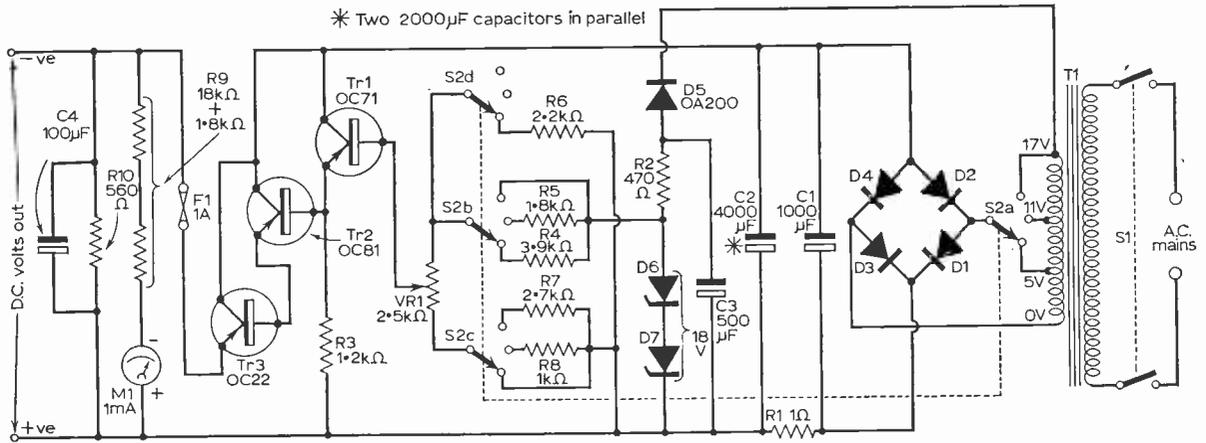


Fig. 2 (above): Complete circuit of the power supply unit. S2 is a four-pole, three-way wafer switch. D6-D7 could be a single 18V $\frac{1}{2}$ W Zener diode.


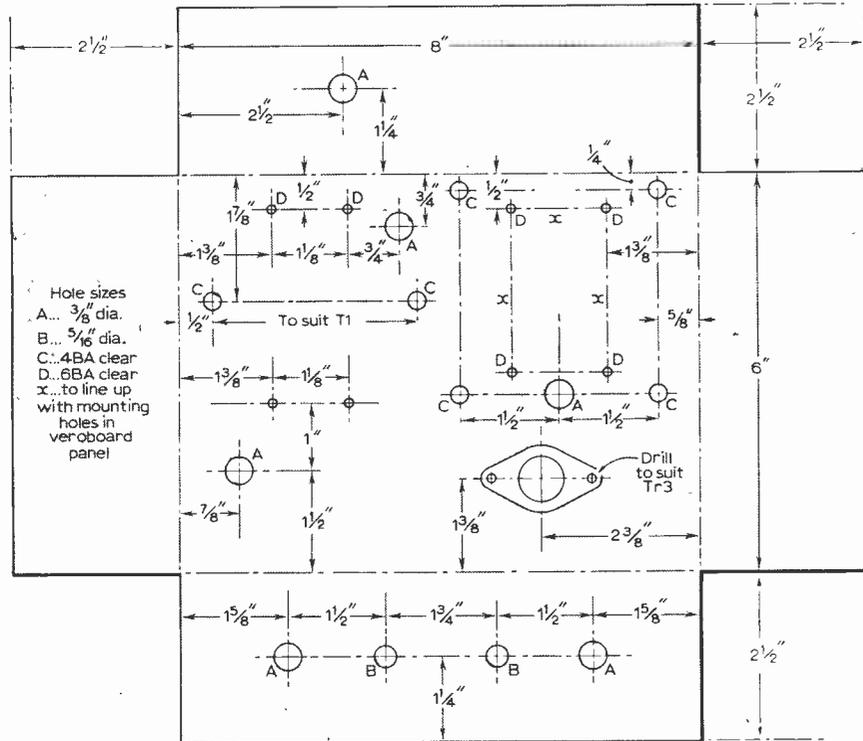


Fig. 3 (left): The main chassis dimensions. Note that Tr3 is insulated from the chassis by the use of insulated washer and spacers.

Fig. 4 (bottom left): The front panel dimensions.

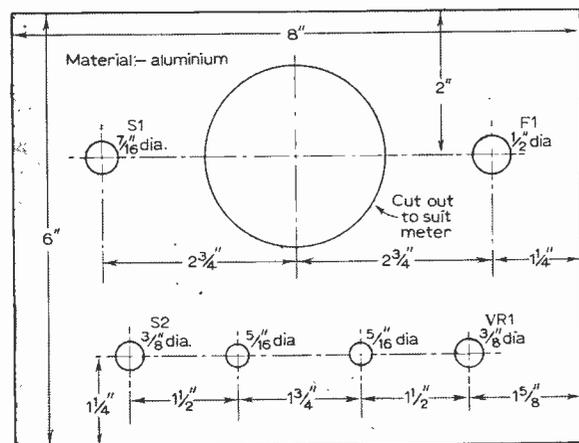

17 volt tapping on the secondary of T1 and connects it to the bridge rectifier, which comprises D1—D4. The rectified output is smoothed by the C1-R1-C2 filter network and passed to the control circuitry.

An additional line is taken from the 17V tap on the secondary of T1 to D5, and the resulting rectified a.c. is smoothed by C3 and fed to the R2-D6-D7 network, to give a final stabilised reference voltage across the Zener diodes. This stabilised voltage is applied across VR1, making a variable stabilised output available at the slider; the available voltage swing of VR1 is limited on each range by the R4—R8 series resistors.

The voltage from the slider of VR1 is fed to the base of Tr1, which is wired as an emitter follower with emitter load R3. The voltage at Tr1 emitter is fed to the Super-Alpha pair, Tr2—Tr3;

**Be first this year
SEED AND
PLANT RAISING**



Soil heating wire and transformer. Suitable for standard size garden frame. 19/6 plus 3/6 post and ins.



PP3 Eliminator—play your pocket radio from the mains! Save £'s. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions. Only 6/6 + 1/- post.

HI-FI SPEAKER BARGAIN

12in. High fidelity loudspeaker. High flux permanent magnet type with either 3 or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 29/6 with built-in tweeter 35/- plus 3/6 post and insurance.



2 1/2 kW FAN HEATER

3 heat positions to suit changes in weather: 1kW, 1 1/2kW, 2 1/2kW; also blows cold for summer, has thermostatic safety cut out "Proper" price £5.17.6. Yours for only £3.15.0. Plus 7/6 post and insurance.



MAINS TRANSFORMER. Upright mounting with primary tapped 200, 220, 240 v. H.T. secondary is 250-0-250 v. at 100 mA. and it has two L.T. secondaries of 6.3 v. 1 1/2 amp.—unused (removed from equipment), 15/- plus 3/6 post and insurance.

"CO" CORE POTTED OUTPUT TRANSFORMER. Made by the famous "Farneko" company these are the best money can buy, we can offer a bargain 15 watt rating, centre tapped primary with secondary for 3 ohm speaker. Potted and in black stove enamelled case for upright mounting these will make your amplifier or rig look perfect at only 12/6 plus 3/6 carriage and insurance—hurry for these.

1 MEG. POTS. By Erie, standard 1in. spindle, 1in. long, 7D. each in doz. lots, otherwise 10d.

1 MEG. POTS WITH D.P. SWITCH. Again by Erie, Standard size spindle 1in. length, 10d. each in doz. lots, otherwise 1/3 each.

MINIATURE PICK-UP. For pop records—this is made by Cosmoco—has a crystal cartridge and long play sapphire stylus—offered for less than the wholesale price of the stylus only—namely 3/6 each or 36/- doz.

MINIATURE RELAYS with removable covers. Very sensitive (will close on only 20 mA). Coil resistance 10,000 ohms—contacts are three sets; triple set for change over pair to open circuit and the third pair to close circuit—perfect order unused (removed from equipment), 7/6 each.

CAR CHARGER OUTFIT 1 amp. transformer and selenium full wave rectifier only 27/6 plus 3/6 post.

FLOUORESCENT LIGHT KITS. Comprising choke, lampholders, starter and two chrome tube clips. 20 watt 19/6, 40 watt 11/6, Super Silent 40 watt 17/6, 80 watt 17/6, 65 watt 19/6. All 4/6 P. & P.

SEMI-CONDUCTOR BARGAINS


Type No.	Price	Type No.	Price	Type No.	Price
2N1727	15/-	MAT101	8/6	OC71	4/-
2N1728	10/-	MAT120	7/6	OC72	5/-
2N1742	26/-	MAT121	8/6	OC76	6/-
2N1747	25/-	OA5	5/-	OC76	5/-
2N1748	10/-	OA10	5/-	OC77	7/-
AC107	9/-	OA47	3/-	OC78	5/-
AC127	9/-	OA70	2/-	OC78D	5/-
ACY17	8/6	OA79	2/6	OC81	5/-
ACY18	5/6	OA81	2/6	OC81D	5/-
ACY19	6/6	OA86	5/-	OC82	5/-
ACY20	5/6	OA90	2/6	OC83	5/-
ACY21	6/-	OA91	2/6	OC84	6/-
ACY22	4/6	OA200	3/3	OC139	8/6
AF114	7/-	OC202	4/3	OC140	12/6
AF115	6/6	OC22	10/-	OC170	5/-
AF116	7/-	OC23	17/6	OC171	6/-
AF117	5/-	OC24	22/6	OC200	9/-
AF118	12/6	OC26	7/6	OC201	12/6
AF139	17/6	OC28	15/-	OC202	13/6
AF186	19/6	OC29	12/6	OC203	3/6
AFZ12	15/-	OC35	12/6	OCPT1	19/6
ASZ21	15/-	OC36	15/-	ORP12	8/6
BC107	14/6	OC42	6/6	ORP60	5/-
BY100	5/6	OC44	5/-	SB078	8/6
BYZ13	7/6	OC45	4/-	SB085	8/6
MAT100	7/6	OC70	4/-	SB251	10/-

100v. S.C.R.'s THYRISTORS. 1 amp. 6/6, 3 amp. 7/6, 12 amp. 15/-, 400v. 1 amp. 15/-, 3 amp. 17/6, 5 amp. 22/6, 25 amp. £3. 50v. 1 amp. 6/6, 3 amp. 7/6, 10 amp. 10/-, 25 amp. 30/-.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/6.

HEAT AND LIGHT UNIT

Bring luxury to your bathroom—have comforting heat where you now only have light—all the parts to build a full size (16in. diameter) model are now available—you will build it in an hour—12in. 750 watt circular silica glass encased element—opal bowl for up to 100 watt lamp—non-rust spun reflector—white enamelled base heat shield—pull switch magnificent unit as sold normally at £4.5.0 only 49/6 plus 7/6 carr. and insurance.

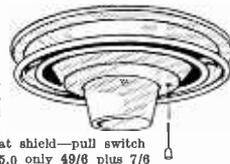

SUPERTONE G.C.V.

Saves you work—It's partly built

Like its predecessors this latest Companion has full fi performance—such as only a good wooden cabinet and biflux speaker can give, and due to its being partly built you will have it going in an evening. Note these features:

- All Mullard Transistors including 3 x AF117.
- Two-tone Cabinet, size 11 x 8 x 3in.
- All circuit requirements—Push-pull output—A.V.C. and feed back etc.
- Printed circuit board all wired only W.C. Switch and Tuning Condenser.
- Pre-aligned IF stages complete with full instructions. Price only £3.19.6 plus 6/6 post and insurance.



connections, e.g. to Volume control—

THIS MONTH'S SNIP

3M SCOTCH TAPE


brand new, unused and guaranteed perfect and not second in any way—a connoisseur's tape on normal spools.

Standard Play 5in.	600ft.	9/-	Long play 5in.	900ft.	11/6
	5in.	900ft.	11/6	5in.	1,200ft.
	7in.	1,200ft.	16/-	7in.	1,800ft.
					23/-

£3 post free otherwise add 2/- post and ins.


INFRA-RED HEATERS

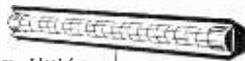Make up one of these latest type heaters. Ideal for bathroom, etc. They are simple to make from our easy-to-follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watts element, all parts, metal casing as illustrated. £1/6, plus 3/6 post and insurance. Pull switch 3/- extra.



F.M. TUNER

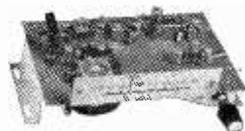
of exceptional quality, giving really fantastic results with virtually no noise. Suitable for mains or battery operation. 6 transistors—three IF stages—double tuned discriminator. Complete, new, and built up all ready to work on chassis. Size 6in. x 4in. x 2in. with tuning scale and slow motion drive. A £12.12.0 tuner for only £3.10.0.



NOW INSTANT START

CIRCULAR FLOUORESCENT

Brings sunshine into your home. 150 watts of light but uses only 40 w. Beautiful fittings with glass, non-plastic centre, fluorescent tube and choke control. Made by Philips. Regular price £4.15.0. Special budget price 65/-, plus 8/6 c. and ins. Please state colour of glass centre, white, pink, blue, red, black, yellow or cream. Also whether plug into lamp holder or ceiling mounting model. 80 watt model 99/6, 10/- carr. & ins.

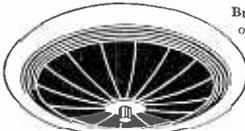

FINE RECORD PLAYERS ARE GARRARDS

and because they have been making record players for so long, GARRARD are your best choice—big range always in stock. 7/6 for post and ins.

2000	£6 9 6	LAB80	£25 0 0
3000	£7 19 6	SRP12	£3 9 0
AT60	£11 11 0	Complete with service sheet and template.	
SP25	£10 9 0		

MAINS TRANSISTOR POWER PACK


Designed to operate transistor sets and amplifiers. Adjustable output 6 v. 9 v. 12 volts for up to 500 mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor, 5,000 and 500 mfd. condensers, Zener diode and instructions. Realign at only 14/6, plus 3/6 post.

BATTERY CHARGER — FREE

9v. Nickel Cadmium Battery type PP3 (fits all popular pocket transistors.) Can be recharged 800 times. Price with battery charger, only 37/6, p. & l. 3/-. Chargeable replacements also in stock for U7 12/6; U11 23/-; U2 22/-.


**See in the Dark
INFRA-RED BINOCULARS**

These infra-red from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lenses for T.V. cameras—light cells, etc. (details supplied). The binoculars form part of the Army night driving (Tabby) equipment. They are unused and believed to be in good working order, but sold without a guarantee. Price £2.17.6, plus 10/- carr. and ins. Handbook 2/6.

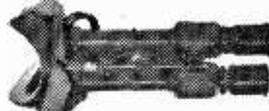

SNIPERSCOPE

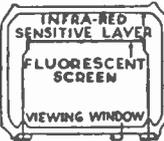Famous war-time "cat's eye" used for seeing in the dark. This is an infra-red image converter cell with a silver osmium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it.



A golden opportunity for some interesting experiments, 5/- each, post 2/-. Data will be supplied with cells, if requested.

TUBULAR HEATERS

New and unused made by G.E.C. rated at 60 watts per ft.—these are ideal in airing cupboards, bedrooms, offices, stores, greenhouses, etc., curtains or papers can touch them without fear of scorching or fire. Supplied complete with fixing brackets and available in the following sizes. Prices which are about 1/2 of list price include carriage by B.R.S. 8ft. 50/-; 10ft. 36/-; 12ft. 42/-. Also in twin assemblies (one pipe above the other) 4ft. 40/-; 5ft. 46/-; 6ft. 52/-.

THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob quickly adjustable from 30-80°F., 9/6, plus 1/- post. Suitable box for wall mounting, 5/- P. & P. 1/-.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-550°F. Internal screw walters (thesetting so this could be adjustable over 30° to 1000°F. Suitable for controlling furnaces, oven kilns, immersion heater or to make flame-stat or fire alarm. 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point. 2 1/2 amps. Has many uses, one of which would be to keep the pipes from freezing, if a length of our blanket wire (18 yds. 10/-) is wound round the pipes, 7/6 P. & P. 1/1.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperatures, 7/6, plus 1/- post.

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 50° to 150°F. Price 13/-, plus 2/- post and insurance.

750mW TRANSISTOR AMPLIFIER

4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feed back loops—sensitivity 5 mV.

Price 19/6 Post and insurance 2/6. Speakers 3in. 12/6; 5in. 13/6; 6 x 4 in. 14/6.

PHOTO ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit, laminated Boards and chemicals, Latching relay, Infra-red sensitive Photocell and Hood. 3 Transistors, cond., Terminal block. Plastic case. Essential data, circuits and P.C. chassis plans of 10 photo electric devices including auto. car parking light, modulated light alarm. Simple invisible ray switch—counter—strobe light alarm—warbling tone electronic alarm—projector lamp stabiliser, etc., etc. Only 39/6 plus 2/- post. and insurance.

ELECTRONICS (CROYDON) LIMITED

(Dept. P. W.) 102/3 TAMWORTH RD., CROYDON, SURREY (Opp. W. Croydon Stn.)

also at 266 LONDON ROAD, CROYDON, SURREY

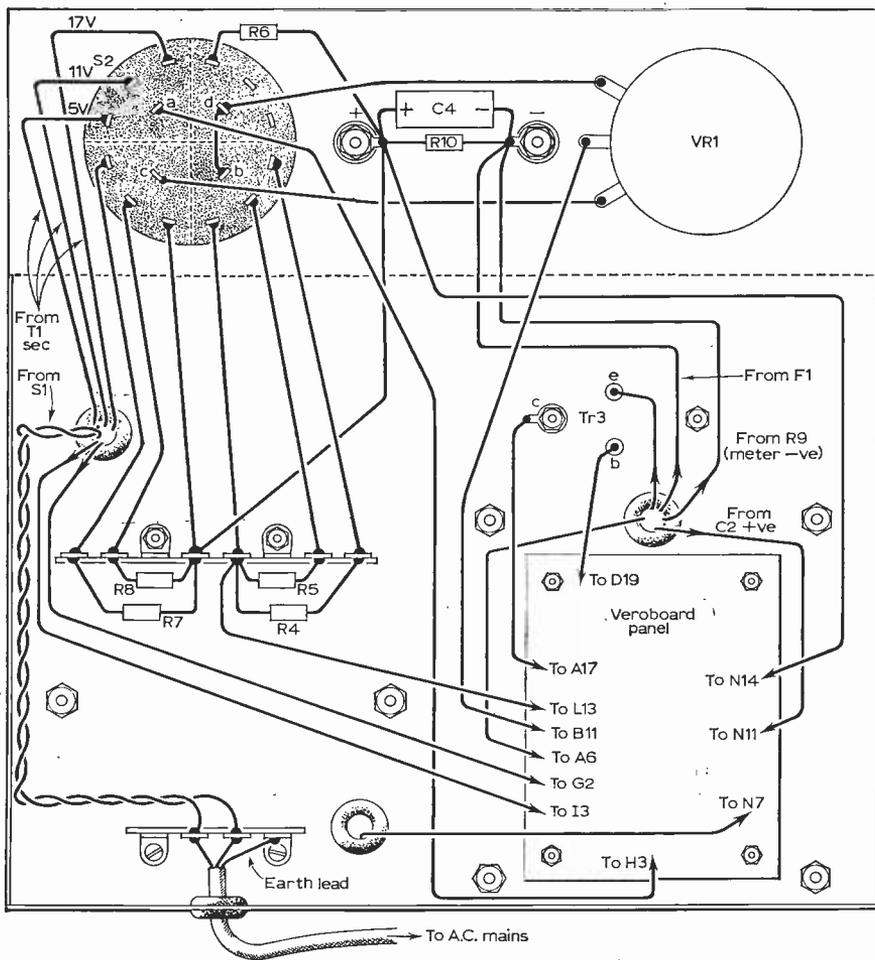


Fig. 7: Wiring of the under chassis.

of the chassis with the aid of small 6BA screws, taking care to use rubber grommets as spacers between the Veroboard and the main chassis to prevent short circuits occurring.

Now, using insulated washers and spacers, bolt transistor Tr3 in place on the top of the chassis, and complete the under-chassis wiring as shown in Fig. 7. Secure the F1 fuse holder, switch S1, and the moving coil meter to the front panel, and complete the wiring of the top of the chassis as shown in Fig. 6. When complete, double check all wiring and then carry out a functional test, checking the output voltages and currents on all ranges. With the component values shown, the voltage swings should be as follows: Range 1, 0.5—3.5V, Range 2, 3—10.5V, Range 3, 9—18V. These voltages are without external load.

The meter circuit

On the prototype, a 1mA moving coil meter was used as the monitor, wired as a 20V (f.s.d.) d.c. voltmeter. It is not essential to use a 1mA meter movement and in fact almost any meter may be used for this job, but one must know the sen-

sitivity of the movement. If it is not marked on the face of the instrument in ohms-per-volt, but the internal resistance is given, it is a simple matter of Ohm's law: $E = I \times R$. For example, a 1mA movement with an internal resistance of 1,000Ω, will drop 1V and, thus, have a sensitivity of 1,000Ω per volt. To increase the voltage range of the movement to 20V f.s.d. the total series resistance has to be increased by the same factor—twenty. Thus an external series resistor of 19,000Ω is required (20,000Ω less the 1,000Ω internal resistance).

Usually, the internal meter resistance will be indicated on the face of the meter, but if it is not it can be determined by connecting the meter in series with a 4.5 to 12V battery and a high value series resistor and variable resistor, and adjusting the values of these two resistors until the meter reads f.s.d. A variable resistor should now be connected in parallel with the actual meter and adjusted until the meter pointer falls to half f.s.d., at which point the values of the internal meter resistance and the

parallel resistance will be equal. Thus, the internal meter resistance can now be determined by removing the parallel variable resistor and measuring its resistance on an ohmmeter. It should be noted that, if any attempt is made to measure the internal meter resistance directly with the aid of the ohmmeter, severe damage may result.

The specified transformer is capable of supplying currents up to 1.5A. If higher currents are required, an alternative transformer should be used, and the four rectifiers, D1—D4, should have suitably increased ratings.

The transistor types used are not critical. Tr1 may be any small a.f. transistor capable of working with a collector voltage of approx. 25V or greater, but should preferably be a fairly high gain type. Tr2 may be any type capable of working with a collector voltage of approx. 25V, and able to handle powers of at least 100mW. Tr3 may be any power type capable of working at collector voltages of approx. 25V or greater, able to handle emitter currents of at least 1A, and dissipating powers of 16W or more on a large heat sink. If larger currents are required, the ratings of Tr3 should be suitably increased, or, alternatively, two or more power transistors wired in parallel. ■

DE LUXE PLAYERS

4-Speed Players 2-tone Cabinets 17 x 15 x 8 1/2 in. High flux loudspeakers and High Quality Amplifiers ready built. Quality output. Volume and Bass controls. Special instructions for cable assembly in 30 minutes only 5 wires to join. 12 months' guarantee.

TO BUILD YOURSELF

PORTABLE CABINET
As illustrated to fit standard player **69/6** or autochanger.

3 WATT AMPLIFIER.
Ready made and tested. With UCL32 triode pentode valve and **59/6** loudspeaker.

SINGLE PLAY UNITS
BSR GV7 £4.19.6
Garrard SRP12 £4.19.6
Garrard SP25 £10.19.6
Philips AG1016 £12. 9.6
Garrard A70 £19.19.6
Garrard LAB90 £24.19.6
Garrard A41 £29.19.6
Garrard Peak Wood Base W31. Ready cut for mounting. 1000, 2000, 3000, SP25, AT60. **72/6**

SUPERIOR AMPLIFIER
Ready made and tested. Guaranteed better sound. Fully isolated AC Mains Transformer 4 watt output. ECL36 triode pentode valve. Volume and tone controls with knobs. Quality Loudspeaker **89/6**

AUTOCCHANGE UNITS
BSR Superlim £5.19.6
Garrard 1000 £5.19.6
Garrard 2000 £8.19.6
Garrard 3000 £8. 9.6
Garrard AT60 with diacast turntable £10.19.6
72/6

INTEGRATED STEREO AMPLIFIER. 4 watts per channel. A splendid example of functional design and value. Gold enamel cabinet size 7 x 3 x 8in. 200/250v. AC. Separate Gram and Tuner inputs. Self-contained pre-amp and all controls. **£9.19.6**

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key
 1in. 14/9 1in. 15/9 1in. 18/- 1in. 20/0 2 1/2in. 37/9
 1in. 14/9 1in. 18/- 1in. 18/6 1in. 22/6 2in. 44/3
 1in. 15/6 1 1/2in. 18/- 1in. 20/- 2in. 34/3 1in. sq. 31/6

BARGAIN XTAL PICK-UP ARM Complete with ACOS LP-7 Turnover Head and S3H 201 - Stereo 30/-
SPEAKER FRET Tysan various colours. 52in. wide from 10/- to 1/26in. wide from 5/- to 1/16. Samples S.A.E.
EXPANDED METAL Gold or Silver 12 x 12in. 6/-
NEW GARRARD GRAM MOTORS 100-130v. A.C. 150/- pair for 200/250v. (in series), or 10/- each (Post Free).

FULL WAVE BRIDGE SELENIUM RECTIFIERS:
 2, 6 or 12v. outputs. 1 1/2 amp. 8/9; 2 a. 11/3; 4 a. 17/6.
CHARGER TRANSFORMERS P. & P. 2/6 Tapped 200/250 v. for charging at 2, 6 or 12 v. 1 1/2 amp. 17/6; 2 amp. 21/-; 4 amp. 25/-; Circuit included. Amp meter 5 amp. 10/6.

MOVING COIL MULTIMETER TK 25. 0-1.000 v. A.C./D.C. ohms 0 to 100k. etc. **47/6**
MOVING COIL MULTIMETER EP10K. 0-1.000 v. A.C./D.C. ohms 0 to 3 meg. etc. **79/6**
MOVING COIL MULTIMETER EP20K. 0-2,500 v. D.C. 20,000 ohms per volt. 0-1,000 v. A.C. Ohms 0 to 6 meg. 50 Microamps full scale. **99/6**

NEW MULLARD TRANSISTORS

OC71 6/-; OC72 7/6; OC81D 6/-; OC81 6/-; AF115 8/-;
 AF114 8/6; OC44 8/-; OC45 8/-; OC171 9/-; OC170 8/6;
 AF1177/-; OC2812/6; AD140 15/-; OC3515/-; Holders 1/3.

ARDENT TRANSISTOR TRANSFORMERS
 D8035. 7.3 CT : 1 Push Pull to 3 ohms for OC72, OC81. 11/-
 D8034. 1.75 : 1 CT. Push Pull Driver for OC72, OC81. 11/-
 D8058. 11.5 : 1 Output to 3 ohms for OC72, OC81. 11/-

TRANSISTOR MAINS ELIMINATORS
 Famous "Power-Mite" 9 volt. Same size as PP9 battery. Fully smoothed. 150mA. full-wave circuit. **45/-**

WEYRAD P50 - Transistor Coils
 RA2W 6 in. Ferrite Aerial with car aerial coil. 12/6
 Osc. P50/AIC. 5/4
 470 k/5 L.F. P50/2CC. 5/7
 3rd L.F. P50/3CC. 6/-
 Spare Cores 6d.
 Driver Trans. LFD4T. 9/6
 Printed Circuit. PCAL. 9/6
 J.B. Tuning Gang. 10/6
 Weyrad Booklet. 2/-

VOLUME CONTROLS
 Long spindles. Midket Size 5 K. Ohms to 2 Meg. LOG or L.N. L/S 3/-; D.P. 5/-
STEREO L/S 10.6 D.P. 14/6.

80 Ohm Coax 6d yd.
 Semi air-spaced Cable 40 yd. 17/6. 60 yd. 25/-
FRINGE LOW LOSS. 1/6
 Ideal 625 lines. yd.

COAXIAL PLUG 1/1. PANEL SOCKETS 1/1. LINE SOCKETS 2/-. OUTLET BOXES. SURFACE OR FLUSH 4/6.
BALANCED TWIN FEEDERS 6d. yd. 80 or 300 ohms.
TELESCOPIC CHROME AERIAL. 6in. extends to 23 in. 6/6.

TV REMOTE CONTROL

For PHILIPS 19TG11A, 121A, 125A, 142A, 23TG11A, 113A, 121A, 131A, STELLA ST1033A, 39A, 43A, 53A, COSSOR CT1910A, 21A, CT2310A, 21A, 31A, PHILIPS. Price 3 gns.

Our Price **12/6** Post Free
 Brand New, includes 11ft. 7-way cable, MULLARD OA81 2 pots, 3 switches, 5 resistors.



STELLA RECORD PLAYER AMPLIFIER

4 watt, 2 stage, 3 to 7 ohm. Neg. feed back. UCL82. UY85. 200-250v. A.C. tapped input. Chassis size 8 x 2 1/2 x 4in. high. Gold/Walnut knobs. Volume and Tone controls on separate Polished Wood Panel 6 x 2in. Brand new with makers' guarantee. Bargain price. P. & P. 1/6. **78/6**

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350	2/3	100/25 v. 2/-	9/600 v. 9/6
4/350 v.	2/3	250/25 v. 2/-	16/600 v. 12/6
9/450 v.	2/3	500/25 v. 3/-	18/- 16/500 v. 7/6
16/450 v.	2/3	8+1/450 v. 3/6	32/- 32/450 v. 6/-
32/450 v.	2/3	8+16/450 v. 3/6	50+50/350 v. 7/-
25/25 v.	1/9	16-16/450 v. 4/9	60+100/350 v. 11/8
50/50 v.	2/-	32-32/350 v. 4/9	100+200/275 v. 12/6

PAPER TUBULARS
 350v.-0.1 9d., 0.5 2/6; 1 mid. 3/-; 2 mid. 150v. 3/-
 500v.-0.001 to 0.05 9d.; 0.1 1/-; 0.25 1/6; 0.5 3/-
 1,000v.-0.001, 0.0022, 0.0047, 0.01, 0.02, 0.1 6/-; 0.047, 0.1 2/6.

E.H.T. CONDENSERS. 0.001mfd. 7kV. 6/6; 20kV. 10/6.
SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mfd. 15v. 2/6; 500, 1000mfd. 15v. 3/6; 2,000mfd. 25v. 7/-
CERAMIC 500v. 1 pF. to 0.01mfd. 9d.

SILVER MICA. Close tolerance (plus or minus μ F.). 5 to 47 pF. 1/-; ditto 1% 50 to 800 pF. 1/-; 1,000 to 5,000 pF. 2/-
TWIN GANG. "0-0" 208 pF. + 176 pF., 10/6; 365 pF. miniature, 10/-; 500 pF. standard with trimmers, 6/-; 500 pF. midket less trimmers, 7/6; 500 pF. slow motion, standard 9/-; small 3-gang 500 pF. 18/8. Single "0" 365 pF. 7/6. twin 10-SHORT WAVE. Single 10 pF., 25 pF., 50 pF., 75 pF., 100 pF., 160 pF., 5/6 each. Can be ganged. Couplers 8d. each.
TUNING. Solid dielectric. 100 pF., 300 pF., 500 pF., 9/6 each.
TRIMMERS. Compression ceramic 30, 50, 70 pF., 9d.; 100 pF., 50 pF., 1/3; 250 pF., 1/6; 600 pF., 750 pF., 1/9.
250v. RECTIFIERS. Selenium 1 wave 100mA 5/-; BY100 10/-
CONTACT COOLED 1 wave 60mA. 7/6; Full wave 75mA 10/-

SPECIAL OFFER! NEW B.A.S.F. TAPE

7 in. L.P. 1,800 ft. (Cat. LGS35) 45/-
 7 in. D.P. 2,400 ft. (Cat. LGS26) 70/-
 Spare Spools 2/6. Tape Splitters 5/-, Leader Tape 4/6.
 Tape Heads: Collaro 2 track 28/6 pair. B.S.R. 4 track 99/6.


MAINS TRANSFORMERS

	Post 2/6 each
E.M.I. 280-0-280. 100mA, 6.3 v. 4 a. 6.3 v. 2 a.	19/6
250-0-250. 80 mA, 6.3 v. 3.5 a. Rectifier 6.3 v.	25/-
1a or 5 v. 2 a. Ditto 350-0-350	29/6
MT 50 300-0-300. 120 mA, 6.3 v. 4 a.	29/6
MINIATURE 200 v. 20 mA. 6.3 v. 1 a.	10/6
MIDGET 220 v. 45 mA. 6.3 v. 2 a.	15/6
SMALL 300-0-300. 70 mA. 6.3 v. 4 a.	18/6
HEATER TRANS. 6.3 v. 1 1/2 a. 7/6; 6.3 v. 4 a.	10/6
Ditto tapped sec. 1.4 v., 2.3 v., 4.5 v., 6.3 v. 1 1/2 amp.	10/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a.	25/-
Ditto. 1 amp., 5, 10, 15, 20, 25, 30, 40, 45, 50, 55, 60 29/6	
AUTO TRANSFORMERS 0-115-230 volt Input/Output. 80 v. 18/6; 150w 25/-; 500 w. 82/6.	

CRYSTAL MIK INSERTS

1 1/2 x 3in. 6/6; ACOS 1 1/2 x 3in. 8/6; BMS 1 x 3in. 7/6
TANNOY CARBON MIKE with switch 15/-
HEADPHONES 2000 ohms 12/6. 4000 ohms 15/-

1967 GRAM CHASSIS £10.10

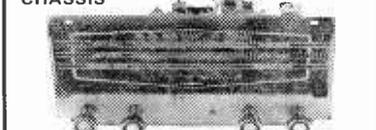

Three Wavebands: Five Valves: ECH81, EF89, Lonc., Med., Short, Gram. EBC91, EL84, EZ80.
 12-month guarantee. A.C. 200-250 v. Ferrite Aerial 5 watt 3 ohms. Chassis 13 1/2in. x 7in. x 5in. dial size 13in. x 4in. Two Pilot Lamps. Four Knobs. **£10.10.**
 Aligned calibrated. Chassis isolated from mains. **£10.10.**
DE-LUXE STEREO GRAM CHASSIS. V.H.F., M.W., S.W.1. 19-50m. S.W.2. 60-180 m. Magic eye. push buttons. 6 valve + rect. AC only 200/250v. **£19.19.0**
 Size 15 x 7 1/2 x 6in. high.

HIGH GAIN TV. PRE-AMPLIFIER BAND 1 B.B.C.
 Tunable channels 1 to 5. Gain 18 dB. EOC84 valve. Kit price 32/6 or 55/- with power pack. Details 6d.
BAND III I.T.A. - same price. Tunable channels 7 to 13. Band I or III. Coils and circuit only. 9/6. Chassis 4/9.
B.B.C.2 Super Booster. UHF Transistor Model ready made 75/-

BLANK ALUMINIUM CHASSIS. 18 s.w.F. 2 1/2in. sides, 4in., 5/6; 9 x 7in., 6/8; 11 x 3in., 6/8; 11 x 7in., 7/6; 3 x 9in., 9/6; 14 x 11in., 12/6; 15 x 14in., 15/-
ALUMINIUM PANELS 18 s.w.F. 12 x 12in. 5/6; 14 x 9in. 4/6; 12 x 8in. 3/6; 10 x 7in. 2/9; 8 x 2in. 2/6; 8 x 4in. 1/6.


ALL PURPOSE TRANSISTOR PRE-AMPLIFIER
 Gain 14-1. 250v. or 9v. input. Ready built with Mu Metal input transformer for Mikes. Pick-Ups, Tuners **15/-**
 Instructions and circuit supplied. Post Free.

THE INSTANT BULK TAP ERASER AND RECORDING HEAD DEMAGNETISER

200/250 v. A.C. Lead 8 S.A.E. **35/-**

BAKER 12 in. STANDARD

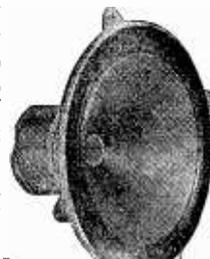The ideal High Fidelity Loudspeaker for high output at home or public address, etc. Built in concentric tweeter cone. Voice coil impedance 15 ohms. Max. Power 20 watts. Bass Res. 40/50 opa. Flux 10,000 gauss. Voice Coil material 1/4in. Response 40-14,500 cps. Chassis Solid Aluminium, overall dia 12 1/2in., overall depth 6in.



Price **£8** Post Free

CATALOGUE S.A.E.
GROUP MODELS FOR VOICALS.
BASS, LEAD AND RHYTHM GUITARS
 30,000-ops. Voice Coils 15 ohms. Heavy Duty.
'Group 25' 'Group 35' 'Group 50'
 12in. 5gns. 12in. 8 1/2gns. 15in. 18gns.
 25w. 35w. 50w.

LOUDSPEAKERS P.M. 3 OHMS. 2 1/2in., 3in., 4in., 5in., 7in. x 4in., 15/6 each; 8in. 22/6; 6in. 18/6; 10in. 30/-; 12in. 30/-; (15 ohms 35/-); 10in x 6in. 30/-; 8in. x 5in. 21/-
E.M.I. Double Cone 13 1/2 x 8in., 3 or 15 ohm outputs, 45/-
Stentorian 10in. HF1012. 45.10; 5in. HF812. 24.10; Crossover 35/-; Horn Tweeters 3-16 Kc/s. 10 w. 20/6; 30 w. 20 Kc/s. 30/6
JACK SOCKETS Std. open-circuit 2/6, close circuit 4/6.
Chrome Lead Socket 7/6. DIN 3-pin 1/3; Lead 3/6.
Phono Plugs 1/-; Socket 1/-; Banana Plugs 1/-; Sockets 1/-
JACK PLUGS STANDARD. Chrome 3/-; DIN 3-pin 3/6.
WAVE-CHANGE SWITCHES with **SIXT EIGHT SPINDLES.**
 1 p. 2-way or 2 p. 2-way, or 2 p. 4-way, 3/6 each.
 1 p. 12-way or 4 p. 2-way, or 4 p. 3-way, 3/6 each.
 Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way. Prices include die spindles, adjustable stops, spacers, etc. 1 water, 10/6; 2 water, 15/-; 3 water, 19/6; 4 water, 24/-; 5 water, 29/6; extra water, 4/6.
TOGGLE SWITCHES. s.p. 2/-; d.p. 3/6; d.p.d.t. 4/-

DE LUXE TAPE SPLICER.

Cuts, trims, joins. **14/6**
 For editing and repairs. With 3 blades.

4-CHANNEL TRANSISTOR MICROPHONE MIXER.

Add musical highlights and sound effects to recordings. Will mix microphone, records, tape and tuner with separate controls into single output. **59/6**

3-WAY INTERCOM AND BABY SITTER.

All transistor. 3-way call buzzer. Desk or wall mounting. Good Volume. For home, office and shop. With long leads, battery, etc. **59/6**

AM TUNER MEDIUM WAVE Three Transistor Superhet.

Ready built. Printed circuit. Ferrite aerial. Size 5 1/2 x 3 1/2 x 1 1/2 in. Ideal for Tape Recorders. **79/6**

3-WATT QUALITY AMPLIFIER 4 Transistor

Push-pull. Ready built with volume control. New Manufacturers' SUPPLIES UHF BBC-2 AERIALS
 BBC-2 Double Gold Ring Set Top Model 32/6
 BBC-2 Five Element Loft Model 32/6
 BBC-2 Five Element Outdoor Wall Mounting 42/6

RADIO BOOKS * (Postage 9d.)
 Radio, TV Valves, Diodes, Transistor equivalents 10/6
 High Fidelity Speaker Enclosures and Plans 5/6
 Transistor Superhet Commercial Receivers 7/6
 Mullard Radio Amplifier Manual 5/6
 Radio Valve Guide, Books 1, 2, 3, 4 or 5 each 5/6
 Practical Radio Inside Out 4/6
 Transistor Audio Amplifier Manual 3/6
 Shortwave Transistor Receivers 9/6
 Transistor Communication Sets 6/6
 Modern Radio Stations List 2/6
 Modern Transistor Circuits, for Beginners 7/6
 Sub-Miniature Transistor Receivers 9/6
 Wireless World Radio Valve Data 9/6
 At a glance Valve equivalents 6/-

RESISTORS. Preferred values, 10 ohms to 10 meg.
 1 w. 1 w. 20% 4d.; 1 1/2 w. 8d.; 2 w. 1/-; 1 w. 10% 6d.
HIGH STABILITY. 1 w. 1% 2/-; Preferred values, 10 ohms to 10 meg. Ditto 5%, 10 ohms to 22 meg. 9d.
 5 watt 1/9
 15 watt 2/6
WIRE-WOUND RESISTORS
 10 ohms to 6,800 ohms 3/-
 10K, 15K, 20K, 25K, 10W.

MAINS DROPPERS. Midket. With sliders. 0.3 a., 1K., 0.2 a., 1.2 K., 0.15 a., 1.5 K. 6/- each.
LINERCORD 100 ohms lit. twin plus resistance 1/- ft.

WIRE-WOUND 3-WATT 1/9
WIRE-WOUND 4-WATT 2/6
POTS. Miniature T.V. 9/6
STANDARD SIZE POTS. Values 10 ohms to 30K, 3/3.
LONG SPINDLE VALUES 50 OHMS to 100 K, 7/8

VALVE HOLDERS. Int. Oct. 6d. Mazda Oct. 6d.; B7G, B8A, B8G, B9A Moulded 9d. Ceramic 1/-; B7G, B9A cans 1/-
 Valve base plugs B7G, B9A, Int. Oct. 2/3.

C.R.T. BOOSTER TRANSFORMERS

for heater cathode short or falling emission. 25% and 50% BOOST. 200/250v. A.C. input. STATE TUBE VOLTAGE VOLTAGE REQUIRED. 2 or 6 or 13v. PRICE **15/6**


BRAND NEW QUALITY EXTENSION LOUSPEAKER

In tough cream plastic cabinet with 20ft. lead and adaptors. For any transistor radio intercom, mains radio, tape recorder, etc. Chassis 30 K. to 2 meg. 31-100 K. to 100 K, 7/8
 Size: 7 1/2 x 5 1/2 in. **30/-** FREE

RETURN OF POST DESPATCH Minimum P.P. Charge 1/6 unless otherwise stated. C.O.D. 5/- extra. Full List 1/-.
RADIO COMPONENTS SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON
 Written guarantee with every purchase. (Export—send remittance and extra postage, no C.O.D.) (Buses 133, 68 pass door). S.R. Stn. Selhurst. Tel. THO 1665

Hi Fi

EQUIPMENT CABINETS OF DISTINCTION

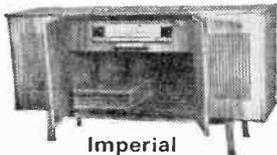

Imperial

- Illustrated in this advertisement are two fine cabinets from the Lewis Radio Range.
- These cabinets are just two of a really extensive range.
- Each one carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex

FREE THE NEW LEWIS RADIO CATALOGUE

Designed to assist your choice of Cabinet. The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE! Please send your FREE cabinet catalogue.

NAME

ADDRESS

(Dept. P37)
Capitals please

LEWIS radio

100 Chase Side, Southgate, London N.14.
Tel.: Palmer's Green 3733/9666

4-STATION INTERCOM



£6/9/6

Solve your communication problems with this new 4-Station Transistor Intercom (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9v battery. On/off switch. Volume control. Complete with 3 connecting wires each 8ft. and other accessories. P. & P. 8/6.

INTERCOM/BABY ALARM



Usualy ~~£6/9/6~~
Our Price ONLY

49/6

Modernise business or home with this new two-way Portable Transistor Intercom. Consisting of Master and Sub. in strong plastic cabinets, with chromium stands. Designed as a two-way instant communication system. Call/talk/listen from Master to Sub and Sub to Master. Operates on one 9v battery. Complete with 8ft. wire and battery. P. & P. 2/6.



Transistor TELEPHONE AMPLIFIER

Usualy ~~£6/9/6~~
Our Price Only

55/-

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. Indispensable in office/home. On/off switch. Volume Control. Operates on one 9V battery. P. & P. 2/6. Battery 2/6 extra. Full price refunded if returned in 7 days.

WEST LONDON DIRECT SUPPLIES (PW/3)
169 KENSINGTON HIGH STREET, LONDON, W.8.

Rapid Servicing of Transistor Equipment

A systematic guide to the servicing of transistor radio television, tape and hi-fi equipment.

by G. J. King

30/- Postage 1/-

GUIDE TO BROADCASTING STATIONS. 15th edition. Compiled by "W.W." 6/-. Postage 6d.

QUESTIONS & ANSWERS TRANSISTORS, by C. Brown. 8/6. Postage 6d.

HI-FI YEAR BOOK, 1966/67. 15/- Postage 1/6.

TRANSISTOR POCKET BOOK, by R. G. Hibberd. 25/- Postage 1/-.

RADIO VALVE DATA. 8th edition. Compiled by "W.W." 9/6. Postage 1/-.

REFERENCE MANUAL OF TRANSISTOR CIRCUITS, by Mullard. 12/6. Postage 1/-.

MEASURING METHODS AND DEVICES IN ELECTRONICS, by A. C. J. Beerens. 35/- Postage 1/6.

100 IDEAS FOR DESIGN, by Electronic Design. No. 66. 15/- Postage 1/-.


THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
British and American Technical Books

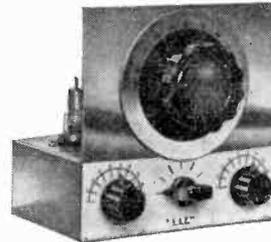19-21 PRAED STREET
LONDON W.2

Phone: PADDington 4185

H.A.C. SHORT-WAVE KITS NEW RELEASE: MODEL "DX"



Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hms, etc.

IMPROVED 1967 RANGE

One-valve model "DX", complete kit—price 58/8 (Post 3/6).

Customers say: "Definitely the best one-valve S.W. Kit available at any price." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other kits still available, including the famous model "K". Before ordering, call and inspect an assembled receiver,—or send for a descriptive catalogue and order form to:—

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

TRANSISTORS CHEAPER by the DOZEN

OC71 TRANSISTORS, 2/6 each, post 4d. or 27/6 dozen, post 6d.

OC44 TRANSISTORS, 3/6 each, post 4d. or 37/6 dozen, post 6d.

OC45 TRANSISTORS, 3/- each, post 4d. or 32/6 dozen, post 6d.

OC81 TRANSISTORS, 3/- each, post 4d. or 32/6 dozen, post 6d.

OC170 TRANSISTORS, 4/- each, P & P 4d. or 42/6 dozen, post 6d.

OC171 TRANSISTORS, 4/6 each, P & P 4d. or 48/- dozen, post 6d.

AF115 TRANSISTORS, 4/3 each, P & P 4d. or 45/- dozen, post 6d.

AF117 TRANSISTORS, 4/- each, P & P 4d. or 42/6 dozen, post 6d.

AC107 TRANSISTORS only 6/- each, P & P 4d. or 65/- dozen, post 6d.

THIS MONTH'S SPECIAL

GT45 P.N.P. TRANSISTORS for med. freq. amplifier or for high speed switching. Only 2/6 each, P & P 4d. or 27/6 dozen, post 6d.

These will replace red or white spot transistors which are no longer available.

GERMANIUM RECTIFIERS, GJ7M, 24v, 1 amp., 2/6, post 8d. or 24/- dozen, post 6d.

MINIATURE GERMANIUM DIODES, down in price to 4/6 dozen, post 6d.

SILICON RECTIFIERS, 800v, P.I.V. at 500mA, 5/- each, post 6d.

Latest Wireless World Valve and Semiconductor Data Book. Data on 7,000 types, 9/6, P & P 1/-.

PETHERICK'S RADIO SUPPLIES
22 HIGH STREET, BIDEFORD, N. DEVON
Telephone: Bideford 3217

new books



NEWNES RADIO AND TELEVISION SERVICING (1965-66 Models) By J. P. Hawker and J. Reddihough. 496 pages, 9 x 6in. Now published by Buckingham Press Ltd. Price 85s.

EVERY year a new edition of Newnes well-known Radio and Television Servicing is published. Always in great demand, these annual volumes contain a wealth of circuits, data and repair hints for popular television and radio receivers, tape recorders and record reproducers. The new 1966 edition has just been published and deals with 1965-66 models, nearly 50 principal makes.

The publishers, Buckingham Press Ltd. who are the successors to S.B. Division of George Newnes Ltd. have asked us to mention that their address has not changed, it remains—15-17 Long Acre, London, W.C.2. Copies of Radio and Television Servicing are available on free trial, direct from Buckingham Press Ltd.—PEM.

THE LAW AND YOUR TAPE RECORDER
By Andrew Phelan. Published by Print and Press Services Ltd. 30 pages. 7 x 5in. Paperback. Price 3s. 6d.

IN these days of rules and regulations it is almost impossible to draw breath without breaking some law or other; and ignorance is no excuse. Practically every time the enthusiast uses his tape recorder he is inviting prosecution—or so it would appear after a perusal of this interesting little booklet.

The author is a barrister-at-law, and the text occasionally betrays this, but otherwise, a lucid account of the pitfalls of the laws of copyright as related to tape recording will be found here.

It is perhaps unfortunate that amid all this frightening legal stricture we find no hint of aid. "This is the law"—says Mr. Phelan, in effect, without adding that application to the Performing Rights Society, or Phonographic Performances Ltd., would solve many of the immediate problems of the local impresario.

For the ordinary user, the problem seldom arises: one can take down broadcast material for one's private enjoyment so long as it is not covered by a separate copyright, but as this permission *does not* extend to gramophone records, whether broadcast or not, Junior is contravening the Acts of 1956, 1958 and 1963 every time he tapes down "Top of the Pops". Replaying his recording to someone else compounds the felony and accepting payment for the privilege is so reprehensible that we shudder to think of the consequences!

Whether one intends to make a business of tape recording or simply indulges in the hobby for pleasure, it is wise to know the legal limitations and this pocket book is a cheap and easy introduction.—MAQ.

SHORT WAVE LISTENING
By J Vastenhoud. Published by Iliffe Books Ltd. 107 pages. Size 8½in. x 5½in. Price 12s. 6d.

IF the PRACTICAL WIRELESS feature "On the Short Waves" has given you an appetite for listening to foreign radio stations this book will provide a meaty dish. All the beginners' questions—What frequency bands should I listen to and when? What is a QSL card? How do I send a reception report? Can I join the DX Club?—are well answered. Established DXers will not be surprised for the author is Jim Vastenhoud, regularly heard on Radio Nederland's DX programme.

As well as the chapters dealing with the practical side of DXing the book contains chapters on the principles of short wave transmission, the aerial and the correct choice of receiver, which seems to be a standard in any book dealing with radio these days. Other useful selections include comprehensive frequency prediction tables, an English-French-Spanish dictionary of commonly used DX terms, and DXing with a tape recorder.

I started by saying that this was the book for the newcomer. Old hands shouldn't be put off by this as they will find new ideas here. I certainly did.—JMG.

SILICON CONTROLLED RECTIFIERS
By Allan Lytel. Published by W. Foulsham & Co. Ltd. 128 pages. Size 8½ x 5in. Price 16s.

THOSE who are not aware of the importance of silicon controlled rectifiers in power switching and control applications should find this book most rewarding. SCR's, or thyristors, operate in much the same way as gas filled thyatrons, but are much simpler to use and have many more applications. In fact, it is possible to control kilowatts of power with these four-layered semiconductor devices from extremely small signals—i.e., the output of a photocell or a thermocouple.

Silicon controlled rectifiers are comparatively new in this country—outside the professional and industrial fields—and it will not be too long before the majority of domestic electrical appliances and electronic equipment make use of them. They are ideal for controlling electric motors.

This book first deals with the theoretical aspects of SCR's, then goes on to explain in detail how they work, with various types of triggering circuits, necessary.

As the book originates from the United States, the publishers have thought it necessary to include a specially written chapter for the English reader. It states, in three pages, that the mains supplies are different and that American components are used throughout. It also gives an incomplete list of British suppliers to the home constructor.—JRC.

MAKING THE MOST OF TAPE POSITION INDICATORS

By J. LOWRIE Grad I.E.E.

MOST tape recording enthusiasts keep a detailed record of each tape with a list of the material recorded on it. In order to spot individual items some method of cataloguing must be used. Coloured indicators can be attached to the tape or note taken of the scale reading on the tape usually marked from 0 to 10. Most modern tape recorders are, however, fitted with a rev. counter



After one revolution the tape unwound at A is much longer than that at B. Length unwound = $2\pi R$ where R is radius from centre of tape spindle to outer layer of tape.

Dial reading	0	45	92	145	208	279	370	420
Time (minutes)	0	5	10	15	20	25	30	32

Fig. 1: Diagram and Table showing why the relationship between dial reading and footage is not linear.

which is geared to the tape spindle and automatically records the number of revolutions. The disadvantage of this method is that dial readings do not correspond directly to the footage of tape which has passed the head. Why this is so can be seen from Fig. 1. As the tape runs off the spool the length of tape which unwinds gets less—length of tape unwinding = $2\pi \times$ radius of outside of tape.

The person using the tape then faces an obvious difficulty: if the rev. counter shows a reading of say 400 at the end of the tape and after a recording has been made the reading is 200, how much recording time is left? At first sight it would appear that only half of the tape has been used whereas more than half has been run off as can be seen when the situation represented in Fig. 1 is considered. It is possible to time the first recording and subtract this from the total playing time but it becomes tedious if this has to be done for each tape; it is much better to compile a graph relating tape footage to dial reading and reference to this will show at a glance the time difference between various dial readings.

The procedure for making a graph is as follows;

Take a full spool of tape and set it into position for playback.

Set dial readings to zero.

Start playing back at fastest speed on machine.

Note time at start and take dial readings every five minutes.

Note the time when all the tape has been used.

The results obtained will form a table similar to the table, Fig. 1, which was obtained using 1,200ft. of L.P. tape on a $5\frac{3}{4}$ in. spool running at $7\frac{1}{2}$ in./sec. The results of Table 1 are plotted on a graph to give Fig. 2. It is easy to see at a glance the recording time represented by various dial readings. Thus for example, if recording started at 180 and ended at 310 the recording time would be $27-18=9$ minutes.

If the relationship between recording time and dial reading had been direct the graph would have been straight as shown by the dotted line. Thus after reading 100 serious errors would arise if the correction supplied by the graph were not applied. The graph can be adapted for other speeds simply by multiplying the time scale by the correct factor (e.g. $3\frac{3}{4}$ in./sec. would require scale to be doubled) leaving the dial reading unchanged. The exact figures on the graph are affected by the spool size and whether L.P. or standard tape is used. Thus graphs should be drawn up for each spool size used, one for standard tape and one for L.P. tape.

Once armed with these graphs the enthusiast can

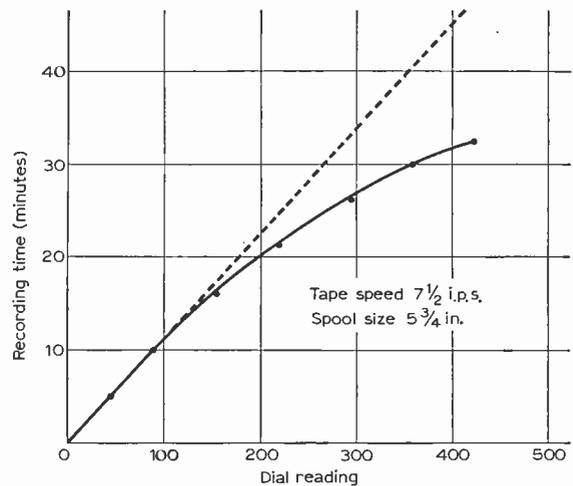


Fig. 2: Graph showing variation of recording time with dial reading.

safely record new material in between two sections which he wishes to preserve knowing exactly how much recording time is available and being certain that there is no danger of inadvertently erasing material which he wants to keep. ■

NEW!



THE WORLD'S SMALLEST RADIO

Photograph shows actual size

SINCLAIR MICROMATIC

PROFESSIONALLY RIGHT IN EVERY DETAIL

- ★ ONLY ONE CONTROL
- ★ CALIBRATED DIAL
- ★ SIZE — 1 1/2" x 1 1/4" x 1"
- ★ POLISHED ALUMINIUM FRONT PANEL WITH SPUN ALUMINIUM DIAL
- ★ AMAZING RANGE POWER & SENSITIVITY
- ★ NEW CIRCUITRY
- ★ BANDSPREAD FOR EASY RECEPTION OF 'POP' STATIONS
- ★ A.B.C.
- ★ IN KIT FORM OR READY BUILT
- ★ 5 YEAR GUARANTEE

THE SINCLAIR MICROMATIC is a brand new design from an organisation world-famous for its production of micro-electronic equipment for constructors. It has behind it the Sinclair tradition of specialisation in micro-radio circuitry which, in the MICROMATIC, reaches fantastically high levels of performance. We have combined new circuitry with new elegance to make the SINCLAIR MICROMATIC professionally right in every detail whether you build it yourself or buy it complete in presentation case. This makes the perfect personal radio, ready to serve wherever and whenever required.

Its minutely proportioned case houses transistors, ferrite rod aerial and batteries and yet is considerably smaller than an ordinary matchbox. The MICROMATIC has an elegantly designed aluminium front panel with matching calibrated slow motion dial. New circuitry assures reception from a wide range of stations over the medium waveband, with excellent selectivity and quality. Here is a new set you will be proud to be seen using. You will also find it an ideal gift to give anyone. **YET THIS BRILLIANT NEW DESIGN IS THE EASIEST OF ALL SINCLAIR RADIO SETS TO BUILD— AND IT IS BRITISH!**

TECHNICAL DESCRIPTION

The Sinclair Micromatic is housed in a neat plastic case with attractive aluminium front panel and aluminium tuning dial to match, calibrated in Kc/s and metres. Three special Sinclair transistors are employed in a six stage circuit of exceptional power and sensitivity. Two stages of powerful R.F. amplification are followed by a double diode detector from which the signal tuned in is passed to a high gain three stage audio amplifier. Automatic Gain Control counteracts fading from distant stations and maintains signal strength. The set is powered by two Mallory Mercury Cells Type ZM.312 which are readily obtainable from radio shops, Boots Chemists, Stores, etc., and cost 1/7 each. The cells will give approximately 70 hrs. continuous working life. Inserting the earpiece plug switches the set on, withdrawing it switches off.

Complete kit of parts to build Sinclair Micromatic including lightweight earpiece, case and instructions

59/6
79/6

Sinclair Micromatic ready built with lightweight earpiece, in presentation case.

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS

sinclair

SINCLAIR RADIONICS LTD., 22 Newmarket Rd., CAMBRIDGE

Telephone 52996 (STD Code OCA3)

Order form and more Sinclair designs on pages following



SINCLAIR STEREO 25 DE-LUXE PRE-AMP CONTROL UNIT

THE SINCLAIR STEREO 25 has been designed specially to ensure the highest possible standards of reproduction when used with two Z.12s or any other first class stereo power amplifier. Best possible components are used in the construction of this superb unit, whilst its appearance reflects the professional elegance characteristics of all Sinclair designs in hi-fi, radio and TV. The front panel of the Stereo 25 is in solid brushed and polished aluminium with beautifully styled solid aluminium control knobs. Mounting the unit is simple, and power is conveniently obtainable from the Sinclair PZ.3 which can also be used to supply two Z.12s to make a complete stereo assembly. Hi-fi enthusiasts seeking the ultimate in domestic listening will find all they want from this combination of Sinclair units. With a Micro-FM for tuner, they will have an installation to compare favourably with anything costing from four to five times as much.

FOR USE WITH ANY GOOD STEREO SYSTEM

TECHNICAL SPECIFICATIONS

Performance figures obtained using Stereo 25, two Z.12s and a PZ.3.

■ **SENSITIVITY** for 10 watts into 1.5 ohms load per channel. Mic.—2 mV into 50K ohms. Pick-up—3 mV into 50K ohms. Radio—20mV into 4.7K ohms.

■ **FREQUENCY RESPONSE** (Mic. and Radio)—25 c/s to 30 kc/s ± 1 dB extending to 100 kc/s ± 3 dB.

■ **EQUALISATION** — Correct to within ± 1 dB on RIAA curve from 50 c/s to 20 kc/s.

■ TONE CONTROLS

Treble +12dB to -10dB at 10 kc/s. Bass +15dB to -12dB at 100 c/s.

■ **SIZE**—6½in. x 2½in. overall, plus knobs.

■ **FINISH** — Front panel sectioned in brushed and polished solid aluminium with solid aluminium knobs. Black figuring on front panel.

BUILT, TESTED AND GUARANTEED

£9.19.6

"Although a complete novice to radio I was able to assemble it (Micro-FM) without undue difficulty thanks to your clear and lucid instructions. I receive all B.B.C. programmes etc. very strongly."

H.T., Warrington, Lancs

"Far more sensitive (Micro-FM) than many commercial models."

M.M. New Romney, Kent

"Z.12 received in perfect order. It is wonderful to hear records properly."


J. de H.S., London, N.2

"I consider your after sales service is excellent. I wish very much that other suppliers treated their customers in the way you do. I have tried out the Micro-FM with the Z.12 and my Quad speaker and am very pleased with the results."

H.A., London, N.6

SINCLAIR MICRO-FM

COMBINED FM TUNER AND POCKET FM RECEIVER

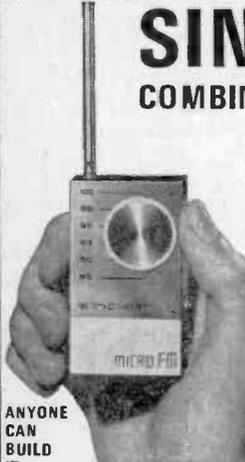

ANYONE CAN BUILD IT

- 7 TRANSISTORS
- NO ALIGNING
- PULSE COUNTING DISCRIMINATOR
- A.F.C.
- TUNES 88-108 Mc/s
- SIZE—less than 3" x 1½" x ¾"

FM superhet using 7 transistors and 2 diodes. The R.F. amplifier is followed by a self-oscillating mixer and three stages of I.F. amplification which dispense with I.F. transformers and all problems of alignment. The final I.F. amplifier produces a square wave which is converted to produce the original modulation exactly. A pulse counting discriminator ensures better audio quality. One output is for feeding to amplifier or recorder and the other enables the Micro-FM to be used as an independent self-contained pocket portable. A.F.C. "locks" programme tuned in. Signal to noise ratio 30dB at 30 microseconds.

Complete kit, including transistors, case, aerial, earpiece, etc.


£5.19.6

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS

sinclair

SINCLAIR RADIONICS LTD, 22 Newmarket Rd., CAMBRIDGE

Telephone 52996 (STD Code OCA3)

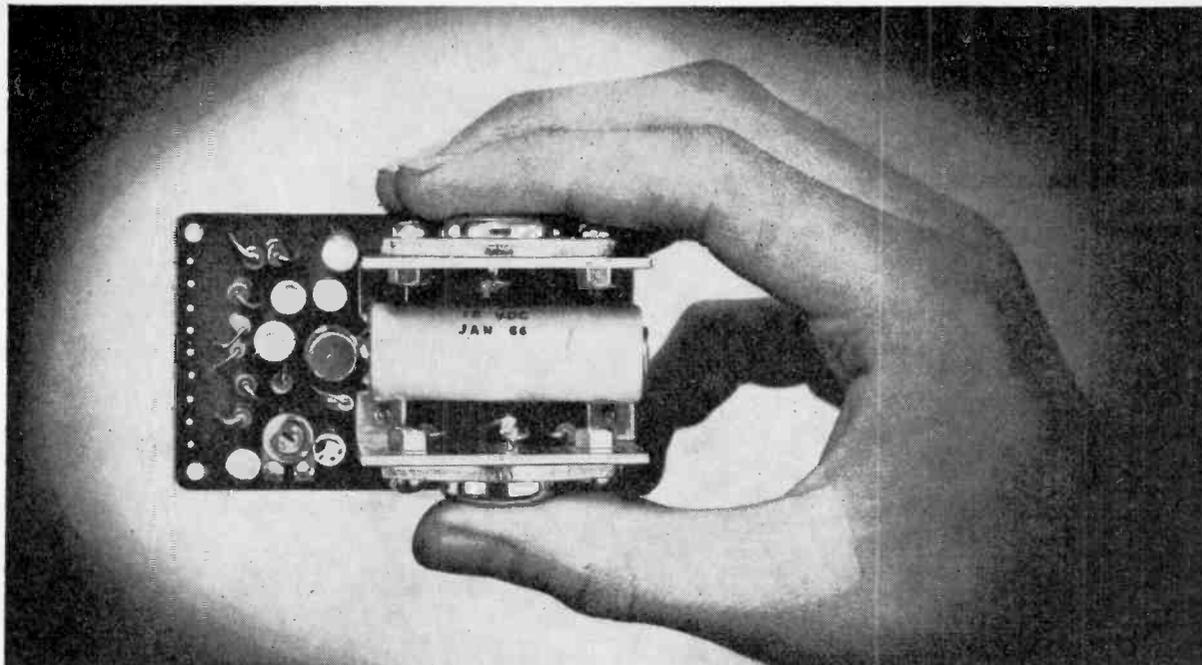


SINCLAIR Z.12 COMBINED 12 WATT HIGH FIDELITY AMPLIFIER AND PRE-AMP

12 WATTS R.M.S. OUTPUT
CONTINUOUS SINE WAVE (24W. PEAK)

**8 TRANSISTOR CIRCUIT WITH
CLASS B ULTRALINEAR OUTPUT**

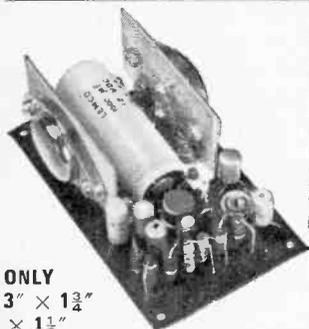IDEAL FOR HI-FI (STEREO OR MONO)
CAR RADIO, ELECTRIC GUITAR, P.A.,
INTERCOM, ETC.



ONLY
3" x 1½"
x 1½"

PZ.3 MAINS POWER SUPPLY UNIT

This special power supply unit uses advanced transistorised circuitry to achieve exceptionally good smoothing. Ripple is a barely measurable 0.05 V. The PZ.3 will power two Z.12s and a Stereo 25 with ease. **79/6**

The amazing adaptability and rugged construction of this very powerful and exceptionally compact amplifier make it possible to use just one type of unit with outstanding success in an unusually wide variety of applications. Eight special H.F. transistors are used in a highly original circuit to achieve the characteristics demanded of any quality amplifier irrespective of price, yet this Sinclair unit costs well under £5, including its own integrated pre-amplifier. The Z.12 accepts radio, microphone and pick-up inputs. Detailed instructions for connecting

these in mono and stereo are given in the manual supplied with every unit. A number of different control networks are also shown. The Z.12 will operate efficiently from any supply between 6 and 20 V. d.c. making it very convenient to run the amplifier from a car battery. Where it is required to run the Z.12 from mains supply, the PZ.3 is recommended. Those wishing to have a ready made pre-amp control unit can feed inputs via the Stereo 25, which, with two Z.12s will provide the finest stereophonic hi-fi possible—and the saving in cost is fantastic.

TECHNICAL SPECIFICATIONS

- Size 3 in. x 1½ in. x 1½ in.
- Class "B" ultralinear output.
- **RESPONSE** 15-50,000c/s ± 1dB.
- Suitable for 3, 7.5 or 15Ω speakers. Two 3Ω speakers may be used in parallel.
- **INPUT**—2mV into 2kΩ.
- **OUTPUT**—12 watts R.M.S. continuous sine wave (24 w. peak); 15 watts music power (30 w. peak).
- Signal to noise ratio better than 60dB.
- Quiescent current consumption—15mA.


Built, tested and guaranteed.
Ready for immediate use.
With Z.12 manual.

89'6

YOUR SINCLAIR GUARANTEE

If you are not completely satisfied when you receive your purchase from us, your money will be refunded at once in full and without question.

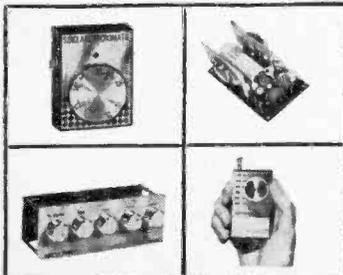If you prefer not to cut this page, please quote PW.367 when writing your order.



To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send items detailed below:

.....
.....
.....
.....

For which I enclose cash/cheque/money order

NAME

ADDRESS

.....
.....
.....

PW.367

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/6d. per word (minimum order 18/-), box number 1/6d. extra. Semi-displayed setting £4. 12s. 6d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL WIRELESS, George Newnes Ltd., Tower House, Southampton Street, London, WC2, for insertion in the next available issue.

TRADE MARK

TRADE MARK No. 791010 consisting of the word **PATHFINDER** and registered in respect of "Radio transmitting and radio receiving apparatus, none being for use in direction finding purposes by not including domestic broadcast radio receivers and parts thereof", was assigned on 7th April, 1966 by Ronald Albert Wilson of 1 Newry Avenue, Felixstowe, Suffolk, to Standard Telephones and Cables Limited, of STC House, 190 Strand, London, W.C.2, WITHOUT THE GOODWILL OF THE BUSINESS IN WHICH IT WAS THEN IN USE.

METAL WORK

METAL WORK: All types cabinets, chassis racks, etc., to your specifications. PHILPOTTS METAL WORKS LTD. Chapman Street, Loughborough.

EDUCATIONAL

"BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, T.V. servicing and maintenance. T.I.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. CHAMBERS COLLEGE (Dept. 857K), 148 Holborn, London. E.C.1."

CITY & GUILDS (electrical, etc.) on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc., send for 132 page Handbook—FREE. B.I.E.T. (Dept. 168K) Aldermaston Court, Aldermaston, Berks.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs) R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for *FREE prospectus* and find out how ICS can help you in your career.

ICS DEPT. 541 PARKGATE ROAD
LONDON, S.W.11.

EDUCATIONAL

(continued)

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies during 1967. Grants available. Day and Boarding students. Stamp for prospectus. Wireless College, Colwyn Bay.

BOOKS & PUBLICATIONS

A GUIDE TO SURPLUS COMMUNICATION RECEIVERS

A detailed guide to thirty-one receivers, including the HR0, AR88, CR100, R107, R1155, PCR, 52 set, etc.
7/6, P. & P. 1/-. *Mail order only to:*
ADKINS, 72 Courtenay Ave, Harrow Middlesex.

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—list free. WILLEN (Dept. 40), 61a Broadway, London, E.15.

SURPLUS HANDBOOKS

19 set Circuit and Notes	4/6 p/p 6d.
1155 set Circuit and Notes	4/6 p/p 6d.
H.R.O. Technical Instructions	3/6 p/p 6d.
38 set Technical Instructions	3/6 p/p 6d.
46 set Working Instructions	3/6 p/p 6d.
88 set Technical Instructions	5/- p/p 6d.
BC.221 Circuit and Notes	3/6 p/p 6d.
Wavemeter Class D Tech. Instr.	3/6 p/p 6d.
18 set Circuit and Notes	3/6 p/p 6d.
BC.1000 (31 set) Circuit and Notes	3/6 p/p 6d.
CR.100/B.28 Circuit and Notes	8/6 p/p 9d.
R.107 Circuit and Notes	5/- p/p 6d.
AR.88D Instruction Manual	15/- p/p 1/6
62 set Circuit and Notes	4/6 p/p 6d.
Circuit Diagrams 3/- each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.824, 22 set, C.R.300/1/2, 52 set Sender and Receiver circuits 6/- post free	
Resistor colour code indicator, 1/6 p/p 6d.	
S.A.E. with all enquiries please.	
Postage rates apply to U.K. only.	

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

SITUATIONS VACANT

RADIO & TV Exam. and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E., City & Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from BRITISH NATIONAL RADIO SCHOOL, Russell Street, Reading.

SITUATIONS VACANT

(continued)

ALDERMASTON COURT POSTAL TRAINING for B.Sc. (Eng) Part 1., A.M.I.E.R.E., A.M.S.E., City & Guilds, G.C.E., etc. prepares you privately for high pay and security as Technician or Technologist. Thousands of passes. For details of Exams & Courses in all branches of Engineering, Building, Electronics, etc. (including latest information on C.Eng.) write for 132-page handbook—FREE. Please state interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

TV and Radio, City & Guilds, R.T.E.B., Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page handbook—FREE. Please state subject. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

RADIO TECHNICIANS

A number of suitably qualified candidates are required for permanent and pensionable employment (mostly in Cheltenham, but from time to time there are some vacancies in other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to candidates who can offer "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19—£747, at 25—£962 (highest age pay on entry) rising by four annual increments to £1,104.

Prospects of promotion to grades in salary range £1,032—£1,691. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

Recruitment Officer (RT),
Government Communications
Headquarters
Oakley, Priors Road
CHELTENHAM, Glos.

SERVICE SHEETS

SERVICE SHEETS. Television. All makes all models. Great new selection. Over 3,000 types. Only 3/- each. Post Paid. D. & B. TELEVISION (WIMBLEDON) LTD., 131 Kingston Road, South Wimbledon, London, S.W.19. Tel.: CHerrywood 3955.

SERVICE SHEETS for all makes. Radio, T/V, Tape Recorders. 1925-1966. Prices from 1/-. Catalogue 6,000 models 2/6d. Free fault-finding guide with all Sheets. Please send stamped addressed envelope with all orders/enquiries, HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio TV, 5,000 models, List 1/-, S.A.E. inquiries. TELRAY 11 Maudland Bank, Preston.

SERVICE SHEETS (75,000) 4/- each. Callers welcome. Always open. 5 South Street, Oakenshaw, Bradford.

RADIO TELEVISION over 8,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS

4/- each, plus postage

We have the largest display of Service Sheets for all makes and types of Radios and Televisions, etc., in the country. Speedy service.

To obtain the Service Sheet you require please complete the attached coupon.

Name:

Address:

To: S.P. DISTRIBUTORS

35/36 Great Marlborough Street, London, W.1

Please supply Service Sheets for the following

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

I require the new 1967 List of Service Sheets at 1/6 each plus postage.

(please delete items not applicable)

I enclose remittance of (which includes postage)

MAIL ORDERS ONLY (Mar.) PW

RECEIVERS & COMPONENTS

MIDLAND ELECTRICAL
61 Priorsfield Road, Kenilworth, Warwicks.

NEW VALVES

CWO	P and P free	Min.	order	three valves	
ECC82	5/-	EL84	5/-	PCL82	6/3
ECC83	5/-	EY51	6/-	PCL83	8/6
ECL80	6/-	EY86	6/-	PCL84	7/-
ECL82	7/6	PCC84	5/-	PCL85	7/6
ECL86	9/-	PCC89	9/-	PL81	6/3
EF80	5/-	PCF80	6/-	PY81	5/3
EF85	5/3	PCF82	6/-	PY80	6/-
EF86	6/6	PCF86	8/-	BY100	4/-

RECEIVERS & COMPONENTS

(continued)

A.I. POST FREE BARGAINS

SPECIAL OFFERS ALL BRAND NEW

V/controls w/wound s.p. switch 25k or 50k 4/9
V/controls carbon less switch all values 3/6
V/controls carbon D.P. switch all values 5/9
Mixed resistors per 100 7/8

12AU7. 8/- PCF80. 5/-.

3w. Record Player Amplifiers, 84/-.

2-way socket panels 9d. each. 4/9 dozen.

Recording TAPE

3in. 300ft. 4/9 3in. 150ft. 3/3

5 1/2in. 1800ft. 20/- 5in. 900ft. 12/-

7in. 1800ft. 19/- 7in. 3600ft. 57/6

3in. 600ft. 12/6 3in. 225ft. 3/9

5in. 600ft. 8/3 5in. 1200ft. 14/6

7in. 1200ft. 14/3 4in. 900ft. 14/6

3 Reels and over 5% discount.

S.A.E. All enquiries. Satisfaction guaranteed.

A.I. RADIO COMPONENTS

14 The Borough Canterbury Kent

COMPONENTS, transistors ex-W.D. and surplus. Call at ROGERS, 31 Nelson Street, Southport. (List 6d stamp.)

SAVE ON SILICON

28302, 40 volt PNP Silicon transistors. Ideal for switching and general applications. Unmarked but fully guaranteed: 2/6 each or 5 for 10/-.
28002, 45 volt NPN Silicon transistors. 4 Mc/s. ft. Ideal complementary to 28302. Unmarked but fully guaranteed: 2/- each or 6 for 10/-.
18130, 50v. 200 mA Silicon diodes, 6/- dozen.
18131, 100 v. 200 mA Silicon diodes, 9/- dozen. Unmarked, fully guaranteed.
BY100, 800 p.i.v., 650 mA. Silicon Rectifiers. Unmarked. Fully guaranteed. 3 for 10/-.

BRAND NEW MULLARD BARGAIN.

OC81 EACH 2/-

Postage and packing 9d. Catalogue 1/-. Callers welcome

L.S.T. COMPONENTS

23 NEW ROAD, BRENTWOOD, ESSEX

RECEIVERS & COMPONENTS

(continued)

STELLA NINE RANGE

A new range of instrument cases including most of the designs used in Practical Wireless and Practical Electronics, from September 1966 issues.

These will be made for stock, ready for return-of-post service.

Send now for free photostats and price lists.

Money back guarantee on all goods if not satisfactory.

E. R. Nicholls

46 Lowfield Road, Stockport, Cheshire.

(continued on next page)

BI-PAK SEMICONDUCTORS

8 RADNOR HOUSE
93/97 REGENT STREET
LONDON, W.1

LOW COST SILICON CONTROLLED RECTIFIERS (THYRISTORS) FACTORY TESTED

1 AMP (TO-5 can)	7 AMP (STUD)	16 AMP (STUD)	Free SCR Literature including Circuit Diagrams for Light Dimmers, speed Controllers, AC Power Switch, etc., with SCR orders or on request.
PIV EACH 9/6	PIV EACH 10/6	PIV EACH 16/6	
50 9/6	100 10/6	400 30/-	
100 22/6	400 45/-	600 55/-	
400 22/6	400 PIV Power SCR 30 Amp, Special Price		80/-

FREE One 10/- Pack of your own choice free with orders valued £4 or over **FREE** and/or, LOGIC MODULES, Timer Units, etc., details free **FREE** UNMARKED, UNTESTED VOLTAGE RANGE 1 Amp 50-400 PIV **20/-**

VALUE PAK 50 TRANSISTORS MIXED UNTESTED **10/-**

3 OC139 Trans. NPN Mullard	10/-
2 DR18 Trans. 2N1225 100 M/Cs PNP	10/-
6 Matched Trans. OC44/45/81/81D	10/-
4 OA10 Diodes Mullard	10/-
15 Red Spot AP Trans. PNP	10/-
15 White Spot RP Trans. PNP	10/-
4 Sil. Rects. 3A 100/400 PIV	10/-
4 NPN Trans. OC139 2N1302	10/-
2 10 Amp. Sil. Rect. 50/100 PIV	10/-
8 Diodes 4 OA70, 4 OA79	10/-
1 5 AMP SCR 100 PIV	10/-
3 Sil. Trans. 28303 PNP	10/-
5 GET884 Trans. Eqty. OC44	10/-
10 Assorted Computer Diodes	10/-
4 Zeners 5, 6.8, 10, 12 Vits	10/-
2 2G417 Trans. Eqty. AF1116/117	10/-
4 200 M/Cs Sil. Trans. B8Y26/27	10/-
2 Bi-directional Trans. ASY66	10/-
4 High Current Trans. OC42	10/-
2 Power Trans. OC26/35	10/-
5 Sil. Rects. 400 PIV 250mA	10/-
3 OC71 Trans. Mullard	10/-
3 OC75 Trans. Mullard	10/-
3 NPN Sil. Trans. 79 M/Cs	10/-
1 Power Trans. OC20 100 Vits	10/-
5 OA47 Gold Bonded Diodes	10/-
4 OA202 Sil. Diodes Sub-Min	10/-
3 OC77 Trans. Mullard	10/-
8 OA81 Diodes CV445	10/-
3 Sil. Rects. 400 PIV 500 mA	10/-

Our vast stocks change daily with hundreds of Semiconductor bargains becoming available. Just send 2/6 to cover 3 months mailing of our latest stock lists, eqvt. charts, circuits, etc.

Minimum Order 10/-. CASH WITH ORDER PLEASE. Add 1/- postage and packing per Order. GUARANTEED by return postal service. Overseas add extra for Airmail.

RECEIVERS & COMPONENTS

(continued)

NEW COMPONENTS

- ★ ASSORTED TRANSISTORS—6 Tested A.F. Devices 9/6
- ★ ASSORTED RESISTORS—Hi-Stab. 300 off (5% or better, worth £3) 15/-
- ★ SELECTED COMPONENTS—Over 100 Hi-Stab., Pots, Capacitors, Rectifiers, Switches etc. 10/-
- ★ TRANSISTORS—Matched Output Kit: OC8D and 2-OC81 9/6
R.F. Kit: OC4J and 2-OC45 9/6
OC44, 45, 70, 71, 72, 81 and 81D Equivalents, each 3/-
- ★ CAPACITORS—Polyester Foil: 160 VDC/100 VAC.
33 pF to 1µF: 5 off, one preferred value.. 3/6
.15µF to .47µF: 5 off, one value 5/-
(P. & P. 1/8 per order, C.W.O.)

ELMBRIDGE INSTRUMENTS LTD.
Island Farm Avenue, West Molesey, Surrey

R.1475 RECEIVERS (TYPE 88)



Highly stable, especially accurate, calibrated Marconi design R.A.F. Communication Receiver covering 2-20 Mc/s. in 4 bands with built-in 609


Kc/s. xtal reference oscillator for checking dial which can be reset by special panel trimmer control. 11 valves: 3-6K7, 6K8, 6J5, 3-607, 686, Y63 tuning indicator and VR150/30 voltage regulator. Two-stage I.F. with 8 tuned circuit. Xtal controlled B.F.O., 4 position selectivity with audio filters for narrow bandwidth. C.W. Fast and slow A.V.C. High and low suppression. A plug-in unit with additional mixer provides a "listening through" guard channel of either 2-4 or 4.75 Mc/s. Receiver 18 1/2 in. x 9 in. x 1 1/2 in. Very good condition. Complete with mains power unit. Fully tested before despatch. £15.10.0. Carriage paid.

NATIONAL H.R.O. SENIOR RECEIVERS 5T MODEL



In excellent tested condition. Complete with 9 coils 50Kc/s. 30Mc/s. and Power Unit. £31.10.0. Carr. 30/-.

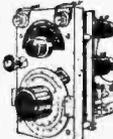REJECTOR UNITS 1.2-10Mc/s
REJECTOR, 4 ranges. Primarily designed as station rejector for R.C. Suitable for harmonic suppression and many other uses with slight alteration. Tuning dial with lock. Aerial in and out sockets. Brand new 25/-, P. & P. 5/-.



4 VALVE 4 WATT AMPLIFIER



"O" Core transformers A.C. Mains 110/230 volts 600 ohms of high impedance input. Output 3 or 600 ohms (state choice). Controls: On/Off switch Gain control. Indicator light. Valve inspection panel 19 x 7 x 7 in. Brand new in maker's carton. 79/6. Carr. 10/-.

32ft. TELESCOPIC AERIAL MASTS

Comprising 20ft. 4 section tubular steel telescopic mast and 12ft. folding whip; can be erected in less than 5 minutes. Close to 5ft. 9in. Weight 21lbs. Must have cost well over £20. Price 67/6. P. & P. 7/6.

ROTARY TRANSFORMER

12v. D.C. input, 250v. D.C. output at 125mA. Size 3 1/4 x 5 1/4 in. Brand new, 17/6. P. & P. 5/-.

AMERICAN DYNAMOTOR UNIT

12v. D.C. input 240v. output, 150 watts approx. Suitable for Universal A.C./D.C. equipment, 45/-, Carr. 7/6. Many other types.

R.F. ANTENNA TUNER (A.T.U.)

Calibrated scale, ideal 160/80/40 metres. Limited number only. Brand new with instructions. 17/6. P. & P. 7/6.

ALL 19 SETS AND PARTS AVAILABLE

Complete list of other bargains, 1/-.
S.A.E. all enquiries. Credit Terms available.

A. J. THOMPSON (Dept. P.W.)

"BILING LODGE", CODICOTE, HITCHIN, HERTS.
Phone: CODICOTE 242


RECEIVERS & COMPONENTS

(continued)

TRANSISTORS, UNMARKED, UNTESTED, 40 for 10/-. p. and p. 1/- .4 packs post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc. (5,000 items), free. K. R. WHISTON (Dept. PRW), New Mills, Stockport.

JOHN'S RADIO (Dept. B) OLD CO-OP, WHITEHALL ROAD DRIGHLINGTON, BRADFORD

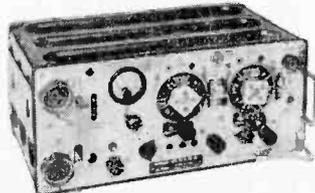FAMOUS ARMY SHORT-WAVE TRANSMITTER MK. III



This set is made up of 3 separate units: (1) a two valve amplifier using a 6V6 output valve; (2) (some only) a V.H.F. transceiver covering 229-241 Mc/s. using 4 valves; (3) the main shortwave transmitter/receiver covering in two switched bands, just below 2 Mc/s. 4 Mc/s. and 4 1/2 Mc/s.-8 Mc/s. (approx. 160-37.5 metres) using 9 valves. For R.T., C.W. or M.C.W. The receiver is superheterodyne having 1 R.F. stage, frequency changer, two IF (465 Kc/s.) signal detector, A.V.C. and output stage. A B.F.O. included for C.W. or single side-band reception. TX output valve 807, other valves octal bases. Many extras, e.g. netting switch, quick flick dial settings, squeak etc. Power requirements LT 12 volts, HT receiver 275 volts D.C., HT transmitter 500 volts D.C. Size approx. 17 1/2 x 7 1/2 x 11 in. Every set supplied NEW in carton with a 12 pin connector and full book including circuits at only £4.10.0. carriage 15/- with V.H.F. TX/RX, 10/- extra. Brand New and boxed No. 10 head and mike set (made for this set), only 15/-, post 2/6. New 12 volt D.C. power unit for these sets 30/-, carriage 5/- New aerial tuning units, 20/-, post 7/6. We make a mains 200/50 volt A.C. power unit in louvered metal case to plug direct into set power socket to run (1) receiver, 20/-, post 5/-; (2) TX and RX, £6.10.0, post 7/6. A charge of 10/- to unpack and test the receiver of these sets is made only if requested, to cover the cost of repacking set. We do however, repeat, all sets and equipment are NEW and boxed, being of fairly recent manufacture. ALL will be sent via B.R.S. within 24 hours of receiving order.

R & R RADIO & TV SERVICE

Dept. P.W.
MARKET STREET, BAGUP, LANGS.
Telephone 465

SALVAGE VALVES

Tested before despatch

6F13	4/6	U329	5/-	30P11	4/-	20P4	6/6
6L18	4/6	10P14	5/-	PL36	6/6	PCC84	4/-
EF80	1/8	20P5	6/6	PL82	3/6	PY81	3/6
EXC82	3/-	30P	7/-	U801	7/6	U301	6/-
ECL80	3/6	6F15	5/-	10F1	1/6	10P13	5/6
30F5	5/-	E191	1/-	30F1.1	5/-	20D1	2/-
PCF80	4/-	EF85	5/-	PY32	6/-	30P12	5/-
PL81	5/-	630L2	4/-	6T4G7	5/-	PY83	5/-
P230	5/-	30P3	6/-	EY85	4/-		

Speakers. Ex.T.V. 5in. round 6 x 4in., 3/6; 8in. round 6/-; post 2/-.

Line Output Transformers available. State set model No. Turret Tuners, 8/-, post 2/-.

Scan Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

Please mention
"Practical Wireless"
when replying to
Advertisements

RECEIVERS & COMPONENTS

(continued)

TRANSISTORS

For the short wave experimenter. All brand new at economy prices. Guaranteed.
Silicon NPN. 2N2926, 100 M/c., 4/-, ME3011, 800 M/c., 5/6. 2N3662, 1200 M/c., 13/-, 2N697, 50 M/c., 2 watt, 13/-, BFY17, 245 M/c., 2.5 watt, 17/6.
Germanium PNP. AF139, 800 M/c., 13/6, GM290, 800 M/c., 16/6. AFY19, 225 M/c., 0.8 watt, 24/-, Send stamp for full list.

G. ELLIOTT

3 Sandgate Avenue, Tilehurst, Reading, Berks.

31 Set WTs, complete with 15 valves and 2 crystals. Operate up to 48 MEG tunable with circuit and details. No rear case, 25/- each. Part post 5/-.

Spare Set Valves and Crystals, 12/6.

Chassis less valves, 12/6. P. & P. 5/-.

No other spares available.

Assorted High Stab Resistors, 7/6, 100.

Assorted Syflex P.F. Condensers, 7/6, 100.

Paxolin Sheet, 1/16" x 12" x 12", 3/-.

Thin Paxolin Sheet, approx. 1/64" x 12" x 12", 6 sheets for 5/-.

White Plastic Sheet, approx. 1/32" x 6 1/2" x 24". Suitable dials, insulation, case fronts, etc. 4 sheets for 5/-.

Small E.M. Counters, 5 digit, 500 ohm, 6/6.

Bulgin Extra Sensitive Micro Switch, 5/-.

P.O. Relay 2000 ohm, 1B, 5/-, 1M, 1B, 6/-.

Key Switches, 4 pole, 2 throw, 3/6. 3 position DP+DP centre off, 5/-, 3 c/o+4 c/o centre off, 6/-, DP+DP 2 for 5/-.

Plessey Plugs and Sockets, 12 way, 3/- pr., 6 way 5/- pr.

6 or 12 way screened cable to match, 3/- yd. Breast Mike, 6/-, Carbon Inserts, 1/6.

Battery Ever-Ready, 90v+7v, 4/6, 12 for 30/-.

Small Component Boxes, 12/6, for 60 samples 6/1.

Mp Metal Screen for 5µP7 with fittings, 6/6. 250mA Fuses 1 1/2" x 1", 5/-, 100.

100 Volt Hand Generator, 7/6.

Rheostat WW Rotary, 15 ohms, 3/6 amp, 12/6. Details of Instrument Case Assembly Free, send large addressed envelope.

Rotary Transformer, Input 12 volts, output 490v at 65mA, 9/-.

Rotary Transformer, 12v. input, 300v output, at 0.2 amp, 35/-.

Modern lightweight Breast Mikes, Polythene fittings, New, 7/6, spare insert 2/6.

Ernest Turner meter 2 1/2" fitting (round) 1-0-1M/A. Centre zero, 12/6.

Carpenter's relay type 3SE1, 250 ohm +200 ohm each side. Fitted with plug in base, 17/6 each.

Type 3000 P.O. relay. New 6000 ohm coil, 2 sets of change-over, 8/6.

Transistors 2G302, 2/-.

Printed circuit board, 11" x 5 1/2" ideal for reuse with 28 diodes CV448 plus some high stab resistors, 10/- post paid.

A new range of instrument cases ready send for free list. S.A.E. please.

Polyethylene capacitors 125 volts wkg., 120,000. Recent manufacture for computer co. Prices 6d. each, 5/- doz., 25/- per 100. Your choice of values stock up now and save pounds, FREE sample with lists of values.

Siemens High Speed Relay. S.P.C.O. 1000.+ 1,000 ohms, 6/-.
Small Sealed Relay 1,700 +1,700 ohms S.P.C.O., 6/-.

P.O. Relay, 200 ohms 2 change over, 6/-.

Mains transformer output 350-0-350v at 100 M/A +2 x 5v at 2A. 1 x 2v at 1A, 1 x 6.3v at 2a, 15/-.

Extra Small Rotary Transformer by Hoover, 12v in output 300v suitable razors etc. with cooling fan new boxed, 10/-.

E. R. NICHOLLS

Mail Order and Retail Shop

46 LOWFIELD ROAD


OF SHAW HEATH, STOCKPORT

CHESHIRE

RECEIVERS & COMPONENTS
(continued)

BRAND NEW TELEVISION TUBES!
2 YEAR GUARANTEE. VAST RANGE
12" £3; 14" £4 (not CRM141)
17" £5.15.6; 19" £6.17.6 etc. etc.
Carriage 12/-
Also British valves, lists free!
PHILIP H. BEARMAN, 6 Potters Road,
New Barnet, Herts. Bar 1934/7873.

EXPERIMENTER'S PRINTED CIRCUIT CHASSIS KIT
BUILD 30 TRANSISTORISED PROJECTS
on a printed circuit chassis with parts and transistors from your spares box. Latest very efficient designs for Radios, Amplifiers, Scientific Devices etc., etc., to suit everyone's needs and interests. The kit comprises 4 assorted PC laminate boards, etchant, resist, solvent, degreaser, 16-page etching manual "Printed Circuits for Amateurs", 2 miniature Radio Diodes. Also Essential Design Data, Circuits and Printed Circuit Chassis Plans for building
30 SUGGESTED PROJECTS

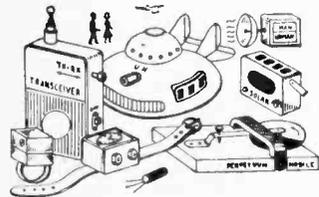

Many recently developed circuits published for the first time including **THE SMALLEST 3 RADIOS IN THE WORLD:** Ring Radio (70 x .70 x .55in.), Watch Radio (1.16 x .80in.), Postage Stamp Radio (1.6 x .95in.). Recently invented Triple Reflex with self-adjusting regeneration. (Pat. Pen.). Neutralised Double Reflex. Pocket Transceiver (licence required). Solar Loudspeaker Radio. Battery Powered Radio. Control of Models by Induction (not radio). Light-seeking Robot. Guided Missile. Electronic Man/Woman Discriminator. Perpetual Motion Machine. 4 Pocket Transistor Radios. 4 Amplifiers. 2 Intercoms. Burglar Alarm. 4 Unusual Crystal Sets, etc., etc.
All designs suit PC boards enclosed.
Price of Kit: 8/8. Post and Pack. 1/6. (U.K.)
Send S.A.E. for full details & Photographs.

YORK ELECTRICS
181a YORK ROAD, LONDON S.W.11

MISCELLANEOUS

CONVERT ANY TV SET into an Oscilloscope Diagrams and instructions 12/6. REDMOND, 42 Dean Close, Portslade, Sussex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data, available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.
Write NOW for free leaflet and further details to **C & S, 20 Maude Street, Darlington, Durham.** Send 3d. stamp.

ALUMINIUM CHASSIS, PANELS, etc. Quick service, "One-off's" welcome. Send sketch for quotation (stamp please). Trade supplied. **FAIRISGRADES LTD.,** Barling, Nr. Southend, Essex.

BERNIESOUND (AUDIO ENGINEERS)

Design-Build-Repair-Modify
All types of Electronic Equipment
For estimates write to:—
Mr. Brown, 1 Effie Place, London, S.W.6.

FOR SALE

LEE ELECTRONICS

The Tape Recorder and Hi-Fi Specialists

MINIFLUX 4-Track Stereophonic/Monophonic Record/Playback Heads. List Price 6 gns. Special Offer, 55/- each.

MINIFLUX 4-Track Stereophonic/Monophonic Ferrite Erase Heads. List Price £3.10.0. Special Offer 32/6 each, or supplied together (one of each) at £3.17.6. (Send S.A.E. for details.) All Heads are supplied complete with fixing plates and Technical Specifications. Also available—Miniflux Heads Type SKN4 SKM4. Half Track Stereo at 55/- each. Full Track Erase 30/- Half Track Erase 22/6

400 EDGWARE ROAD, PADDINGTON, W2
Paddington 5521

MORSE MADE EASY!

The Famous RHYTHM RECORDED COURSE cuts the practice time down to an absolute minimum.

One student, aged 20, took only 13 DAYS, and another, aged 69, took under a week to read 18 wpm. If you wish to read Morse easily and naturally please enclose 8d. in stamps or two in international postal coupons for full explanatory leaflet for: C3CH/S/P
45 Green Lane, Purley, Surrey. UPLands 2896

ELECTRIC SOLDERING IRON



FANTASTIC BARGAIN OFFER
Lightweight Pistol Grip handle
40 watt, 240/250v. A.C. Detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handy man. A boon to model ONLY makers and a necessity for every wireless enthusiast. Offered to YOU at this new amazing price. 10/- Post Free

C. H. SERVICE (Dept. P.W.)
Lusted Hall Lane, Tatsfield, Kent.

"A COMPUTER FOR 59/11d? YOU MUST BE JOKING!"

Digi-Comp is no joke. It is a complete mechanical equivalent of a giant electronic brain, designed so that you can see just what it is that makes a computer function. Digi-Comp calculates, solves problems and plays games, and is accompanied by an instruction and programming manual that explains binary methods and elementary logic in terms comprehensible to anyone who can count—primary school to Ph.D.! Send 59/11 or 4d. stamp for details to:

I-COR SYSTEMS (Mechanical Div.)
18 STAMFORD HILL, LONDON, N.16

YUKAN SO PROFESSIONAL THE YUKAN AEROSOL WAY
Get these AIR DRYING GREY HAMMER or BLACK WRINKLE (CRACKLE) Finishes
Yukan Aerosol sprays contain 16 ozs. fine quality durable easy instant spray. No stove baking required. Finishes available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/11 at our counter or 15/11, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 3/11 carriage paid.
SPECIAL OFFER: 1 can plus optional transferable soap-on trigger handle (value 5/-) for 18/11, carriage paid. Choice of 12 different plum colours, one primer (Motor car quality) also available.
Please enclose cheque or P.O. for total amount to:
YUKAN, Dept.
307a EDGWARE ROAD, LONDON, W.2.
Open all day Saturdays. Closed Thursday afternoons.

Dept. PW/3

FOR SALE
(continued)

HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK

3/6 TIN • JUST BRUSH ON • WITHSTANDS 150°C. OIL, WATER ETC.
2 1/2 oz. tins ... 3/6 1 gallon ... 35/-
1 pint ... 7/6 1 gallon ... 58/-
1 pint ... 15/- (* sent by road)
Carriage: Orders up to 5/-, 8d.; up to 10/-, 1/9; over 10/-, 3/-. Colours: blue, silver, black or bronze. Return of post service, Monday to Friday.
From your component shop or direct from the manufacturer:
FINNIGAN SPECIALTY PAINTS (PW)
Mickley Square, Stockfield, Northumberland.
Tel. Stockfield 2230.

SPECIAL OFFER. GRUNDIG MA1. 2 Transistor Pre-amps for Tape Monitoring or Microphone Boosters, 47/6, post paid. LIST PRICE 4 GNS. LEE ELECTRONICS, 400 Edgware Road, Paddington 5521

TRANSISTORS SPECIAL OFFER

1 watt S.T.C. 300 mc/s N.P.N. Silicon Planar, Transistors limited stocks £1 for 6.

WITH DATA

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16, GET20.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171.

5/- each. OC139, OC140, GET7, GET8, GET9, XC141, BY100, OA211.

BSY27 7/6 each OC20 10/- each

ZENER DIODES

All volts between 3.9v. and 26v.
1/2w 3/6 each, 1.5w 5/- each, 7w 6/- each.

Send 6d. for full lists:— inc., S.C.R., Zeners.

CURSONS

78 BROAD STREET
CANTERBURY, KENT

TAPE RECORDERS, TAPES, Etc.

TAPES TO DISC—using finest professional equipment 45 rpm—18/-. S.A.E. leaflet. **DEROY, High Bank, Hawk Street, Carnforth, Lancs.**

SOUND RECORDINGS

A UNIQUE TAPE BUY! Top brand 7in. 2,400r.p.m., 25/-; 5 1/2in., 1,200r.p.m., 15/- P. and P. 1 at 2/-, 2 at 2/9, 3-6 at 3/6. Bargains in all sizes. S.A.E. for list. **E. C. KINGSLEY AND CO. LTD.,** 93 Tottenham Court Road, London W.1., EUSton 6500.

WANTED

VALVES WANTED, brand new popular types boxed. DURHAM SUPPLIES (C), 175, Durham Road, Bradford 8, Yorkshire.

WE BUY New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

WANTED: Popular Brand New Valves. R.H.S. Stamford House, 538 Great Horton Road, Bradford 7.

WE BUY New Valves for cash, large or small quantities, old types or the latest by return. Send details. Quotations by return. WALTON'S WIRELESS STORES, 15 Church Street, Wolverhampton.

WANTED.—Circuit for Echo Sounder, meter type. MIERS, Walton, Nr. Street, Somerset.

DAMAGED AVO METERS wanted. Models 7 and 8. Any condition. Any quantity. Send for packing instructions. HUGGETTS LTD., 2-4 Pawson's Road, West Croydon.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD
103 North Street, Leeds 7

FIRST-CLASS RADIO AND T/V COURSES... GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exm., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.I.E.R.E. Guide also gives details of range of diploma courses in Radio/TV Servicing, Electronics and other branches of engineering, together with particulars of our remarkable terms of

Satisfaction or refund of fee

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSES

CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)
(Dept. 849F), 148 HOLBORN
LONDON, E.C.1

PADGETTS RADIO STORE

OLD TOWN HALL
LIVERSEEDGE, YORKSHIRE
Telephone: Cleckheaton 2866

Special Offer. Ex R.A.F. Wave Meter, type W1649. Beautifully made in solid brass, all complete with slow-motion drive in wooden box. Valves are used but in good condition. 17/6, or new 30/-, plus post and packing 7/6.

Brand new TV Tubes. 14in., MW36/44, £2.0.0. 19 Set with outer case. Receiver section complete with valves.

Parts Removed. 500 micro-amp meter, all transmitter parts. Relay and 807 valve. Condition fair. No dry rot 10/-, Carr. 10/-.

Reclaimed Tubes. Six months' guarantee. AW43/80. 30/-. MW43/80. 30/-. MW43/69. 30/-. CRM172. 30/-. CRM142. 17/-. 12in. Tubes. 10/-. 17in. Tubes perfect but without guarantee. 17/- each. Carriage on any Tubes in G.B. 10/-.

Specially Selected Nearly New Valves. 6 months' guarantee.

PY33	6/-	ARP12	1/6	EL38	5/-
PCC84	5/6	ECL80	3/6	5U49	4/-
PCF80	5/6	ECC83	5/-	6K7	1/9
PL81	5/6	ECC82	1/3	6V6	1/9
807	5/-	EP91	2/-	185BT	8/6

Single Valves. Post 7d.

VALVE LIST

Ex. Single Valves.	Equipment, 3 months' guarantee.	Post 7d.	Post 2/6.
EF80	1/6	PCF80	2/-
ECL80	1/6	PCC84	2/-
EF91	9d.	PCL82	4/-
EB91	9d.	PCL83	3/-
EBF80	3/-	PCL85	5/-
ECC81	3/-	PZ30	5/-
ECC82	3/-	PY81	1/6
ECC83	4/-	PY82	1/6
EL84	5/-	PL81	4/-
EF50	1/-	PL86	5/-
EY86	5/-	PY33	5/-
6K25	5/-	6B8	1/6
6U4	5/-	6F1	1/-
6P25	5/-	6F14	5/-
KT36	5/-	10C2	5/-

Breaking up 19 Sets. Relays 100 ohm Coil 2/-. Post 2/6. 1 Doz. 26/-.

Post Paid. Jack Sockets, 7/6 doz. Post Paid. Toggle Switches, 7/6 doz. Post Paid.

Pointer Knobs, 7/6 doz. Post Paid. Top Grade Diodes, 3/6 doz. Post Paid. No duds.

Perfect Speakers. Removed from TV sets. Goodmans 7 x 4. 5/-.

Goodmans 8 x 5. 7/6. 6 x 4. and 5ins. 3/-.

Plus Post on any Speaker. 4/-.

New 12 inch Speakers, with built-in tweeter. 28/6. 3 or 15 ohm. Coil. 28/6. Post Paid.

New 24 volt Miniature Model Makers Motor will run from 6 volts. 6/6. Post Paid. Motors Single Phase Quarter H.P., 26/-.

Sixth H.P., 15/-.

Ex Washing Machines. Fully guaranteed. Plus Carriage 10/-.

Type 46 Set. Complete with valves. Send receive switch removed. 12/6. Post Paid.

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5	4/-	DK91	4/-	EF88	6/-	PY80	4/9
1R5	3/9	DK96	6/3	EP89	4/9	PY81	5/-
1T4	2/9	DL33	6/6	EL33	6/3	PY82	4/9
384	4/3	DL35	4/9	EL41	8/-	PY83	5/3
3V4	5/-	DL92	4/3	EL84	4/3	PY800	5/11
5V4G	7/9	DL94	5/-	EY31	5/11	R19	6/6
6F1	6/3	DL96	5/11	EY86	5/3	U25	3/9
6K7G	1/3	DY86	6/3	EZ40	5/6	U26	8/6
6K8G	3/3	DY87	6/3	EZ80	3/6	U191	10/-
6L18	7/3	EABC80	5/6	EZ81	4/-	U301	11/6
6V6G	9/-	EAF42	7/-	GZ92	8/9	U801	18/-
10C2	11/3	EB241	6/6	KT51	6/9	UABC80	5/-
10F1	9/6	EBF80	5/9	N78	14/6	UAF42	6/11
10P13	8/3	EBF89	5/9	PCC84	5/3	UBC41	6/6
20P2	10/3	ECC81	3/3	PCC89	9/9	UBF89	5/9
20P1	8/9	ECC82	4/6	PCF80	6/3	UCC84	7/9
20P3	8/9	ECC83	4/6	PCF82	5/9	UC085	6/-
20P4	12/6	ECC85	5/3	PCL82	6/3	UCP80	6/-
30P5	9/9	ECH35	5/9	PCL83	8/3	UCH42	8/6
30P4	11/6	ECH42	8/9	PCL84	7/3	UCH81	5/9
30P19	11/6	ECH81	5/-	PCL85	7/9	UCL82	6/9
DAC32	6/9	ECL86	5/9	PL36	8/6	UCL83	8/6
DAF91	8/9	ECL89	6/-	PL41	6/3	UF41	7/9
DAF96	5/11	ECL86	7/6	PL82	6/9	UF89	5/3
DF33	7/6	EF39	3/6	PL83	5/11	UL41	7/9
DF91	3/9	EF41	5/9	PL84	6/-	UL84	5/3
DF96	5/11	EP80	4/3	PY32	8/8	UY41	4/9
DK32	7/-	EP85	5/-	PY33	8/3	UY85	4/9

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON N.16

1/2 PRICE SPECIAL RADIO CHASSIS OFFERS




Hi-Fi CONTINENTAL STEREOGRAPHIC RADIOGRAM CHASSIS
Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Comes complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed automatic record changer. Complete £29 gns. (Units available separately if required. Chassis only, 21 gns.)
Special terms available of £10.6.6 deposit followed by 18 monthly payments of £1.7.3 (total H.P. of £34.17.0)+15/- P. & P. Send £11.1.6 now.



Imperial Hi-Fi STEREOGRAPHIC RADIOGRAM CHASSIS
The Imperial Stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons, controlling mono/stereo selection. GramLong-Medium-Short-FM-ON/OFF. The unit comes complete with two 10" elliptical loudspeakers plus a mono/stereo 4 speed automatic record changer. Complete £41.9.6. Chassis only, 29 gns.

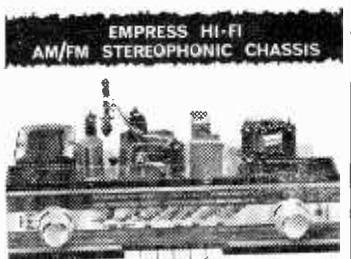Special terms available of £13.16.6 deposit followed by 24 monthly payments of £1.8.1.0 (total H.P. £48.8.6)+17/6 P. & P. Send £14.14.0 now.



Empress Hi-Fi AM/FM STEREOGRAPHIC CHASSIS
This most advanced radiogram chassis with automatic push button selection covers short, medium and long wavebands plus V.H.F./F.M. Offered complete with 2 10 x 6 speakers 4 speed Stereo/Mono autochanger only £35.19.6. Chassis only, 25 gns. Special terms available of £12 deposit followed by 18 monthly payments of £1.11.7. (total H.P. £40.8.6)+15/- P. & P. Send £12.15.0 now.

All Lewis Radio equipment including valves are fully guaranteed for one year free of charge. Send your cheque or P.O. today while stocks last to Dept. P.27.

LEWIS radio
LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14. Telephone: PAL 3733/9666


NO.2 NOW ON SALE

The new monthly all boat enthusiasts have always wanted

SALES OF NO. 1 PROVE IT! Practical BOAT OWNER new and excitingly different in its approach has already caught the imagination of everyone who loves 'messing about in boats'. Newcomers and old hands alike have welcomed it for its really practical help on every aspect of buying, building and maintaining every kind of small sailing and power craft. Make sure of this second issue today.



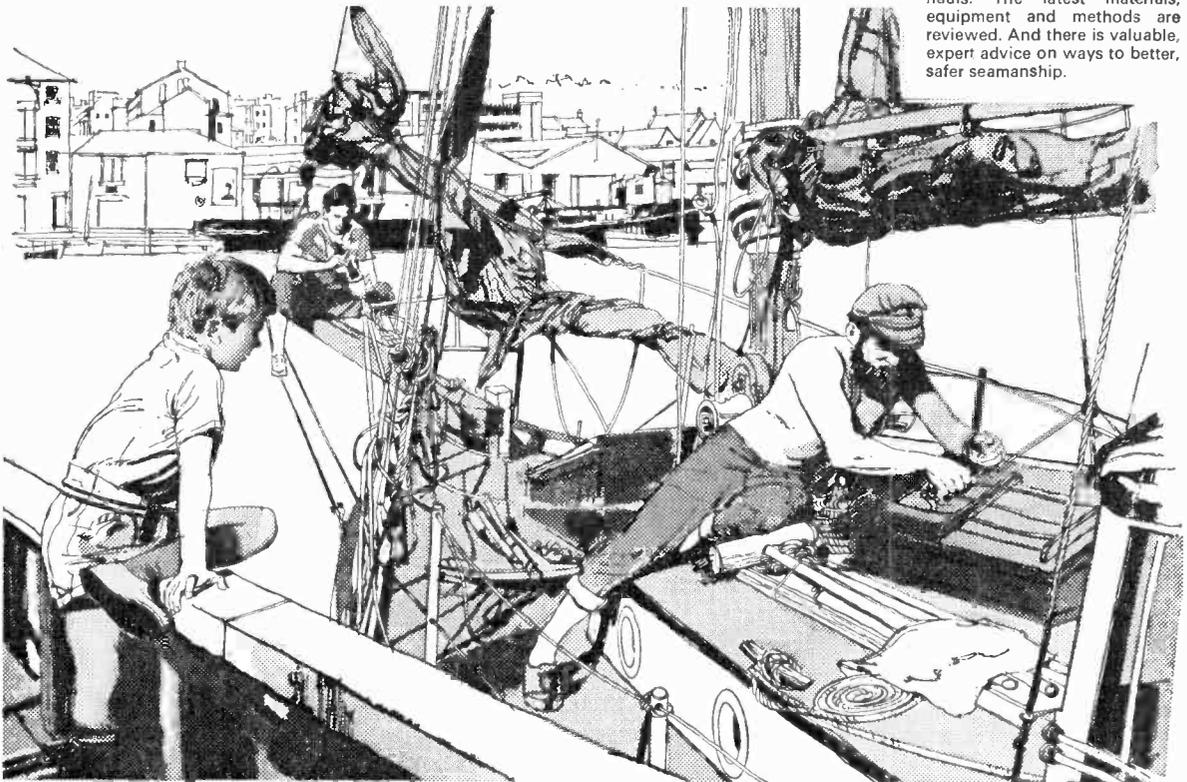Every month Practical BOAT OWNER gives step-by-step instructions, with many illustrations, on everything from minor repairs to major overhauls. The latest materials, equipment and methods are reviewed. And there is valuable, expert advice on ways to better, safer seamanship.



FREE! 2 SKIPPERS' SAFETY CHECK CARDS

Two more waterproofed, handy-size cards to keep in the cockpit for instant use.

- Recognition of Lights Part 1

- Recognition of Lights Part 2

More FREE cards in following issues



CONTENTS OF No. 2 INCLUDE:

TWO-STROKE TONE-UP A step-by-step guide for Stuart Turner owners.

A DINGHY RACK FOR YOUR CAR An easy-to-make roof rack that will carry your boat, or anything else.

ALL ABOUT PAINTING First of an encyclopaedic series on this all-important job: The Right Tools.

ALSO: An introduction to the steering compass ★ Gadgets to make ★ New chandlery ★ A woman's view of living aboard in winter ★ Useful techniques for home boat builders.

PRACTICAL Boat Owner


HELPS YOU GET THE BEST OUT OF BOATING

Monthly 3/6

RADIO CONSTRUCTOR

BUILD THIS ATTRACTIVE

TRANSISTOR V.H.F.
PORTABLE
RECEIVER

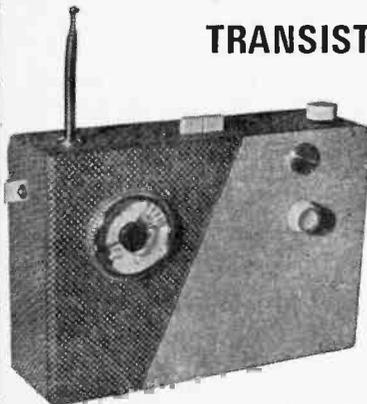

also featured
Radiogram Amplifier
Transistorised Grid
Dip Meter
Audio Frequency
Q Multiplier

Many other constructional articles

2/6 FEBRUARY ISSUE 2/6

From your newsagent or 3s. post paid from:
**DATA PUBLICATION LTD., 57 MAIDA VALE,
LONDON W. 9.**

17in.—£11.10.0


3 Star Guarantee
★ Tube ★ Valves
★ Components carr. 30/-

**TWO-YEAR GUARANTEE
EX-RENTAL TELEVISIONS**


FREE ILLUSTRATED
LIST OF TELEVISIONS

17" — 19" — 21" — 23"

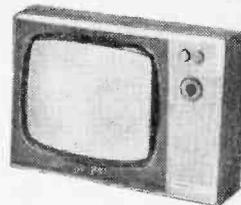WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY



LATEST RADIOGRAM CABINETS £9.10.0

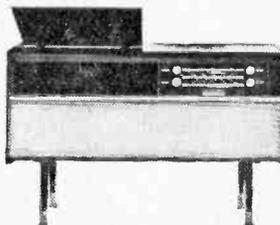

Superbly made and styled
in Veneered English
Walnut

Lift-up lid to changer and
record storage compartment
Position 8 x 5 in. twin Speakers
Dimensions: 40 x 16½ x 15½ in.
Legs 1 gn. Carr. 30/-
Other Models—Send for List

RECORD PLAYER CABINETS. 49/6.
Latest designed covered cabinets.
Takes any modern Autochanger.
P. & P. 7/6.

TRANSISTOR CASES 19/6 9½ x 6½ x
3½ in. P. & P. 2/6.

TV Turret Tuners, 2/6. New, less
valves. Slim models 5/- Press button
models 19/6. P. & P. 2/6.

TWO YEAR GUARANTEE

TUBES 100% REGUNDED

4in.—59/6. 17in.—79/6

21in. & ALL SLIMLINE TUBES
99/6 Carr. 10/6

EX MAINTENANCE TESTED TUBES

17in.—35/- 14in.—15/-

Carr. 5/- (not slimline)

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, E.12 ILF 6001-2-3

WORLD RADIO & TV HANDBOOK 1967, 32/-

by JOHANSEN, postage 1/3

Transistor Specs. and Subs. Handbook 1967 ed.
by Techpress. 22/6. P. & P. 1/-.
Radio Valve Data by W.W. new 8th ed. 9/6.
P. & P. 1/-.
V.H.F. for the Radio Amateur by C.Q. 28/-.
P. & P. 1/3.
Hi-Fi Year Book 1967. 15/- P. & P. 1/6.
R.S.G.B. Amateur Radio Call Book 1967 ed.
6/- P. & P. 8d.
R.S.G.B. Radio Amateur Examination
Manual 1967 ed. 5/- P. & P. 8d.
Transistor Pocket Book by Hibbeard. 25/-.
P. & P. 1/3.

Where possible 24-hour service guaranteed.

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT STREET,
LONDON, W.C.2

(Leicester Square Tube Station)

QUOTATIONS FOR COMPONENTS send your list of requirements for competitive quotation by return of post.

HEAVY DUTY RELAYS 9-14v. DC coil, single pole, switching up to 40 amps at low voltage, 2/6. P.P. 1/6. Discounts for quantities.

HI-K CERAMIC CAPACITORS (DISC) 500v. DC working, 1,000 pF 2/6 per dozen. P.P. 9d. 10,000 pF 3/6 per dozen. P.P. 9d.

SUBMINIATURE ELECTROLYTICS 100 mfd. 15v. brand new, at the fantastic price of 9/6 per dozen. P.P. 9d. Send for list of other bargains.

POTENTIOMETERS 5KΩ lin. 10KΩ lin. 100KΩ lin. 250KΩ lin. 1MΩ log. 2MΩ log. 2MΩ lin. 1/- each. P.P. 6d.

With double pole switch 500KΩ lin. 1MΩ log. 2/- each. P.P. 6d.

With single pole switch 10KΩ lin. 50KΩ lin. 2/- each. P.P. 6d.

Pre-set 250KΩ lin. 250KΩ log. 300KΩ lin. 2MΩ lin. 1MΩ lin. 1/- each. P.P. 6d.

FERROXUBE TOROIDS Leaflet on complete range available on request.

TOROID TRANSFORMERS for Inverter applications, etc. 20 watt version: 12v. input, 250v. 80mA output, 19/6. P.P. 4/6. 60 watt version: 12v. input, 300v. 200mA output, 39/6. P.P. 5/-. Toroid transformers also supplied to your requirements.

RESISTOR PACKS 100 well assorted values and types, mainly 1w. hy-stabs, but also some 1/10w. 1w. 2w. 1% to 10%. A super buy at 7/6. P.P. 1/6.

CAPACITOR PACKS 100 well assorted silver micas, ceramics, polyesters, papers, electrolytics, etc. 10/- P.P. 1/6.

VALVE HOLDERS B9A paxolin 2/- per dozen. P.P. 1/6.

UX7 10/- per dozen. P.P. 2/6.


HEADPHONES German made. 5 and 2,000 ohm versions. 20/- P.P. 2/-.

TRANSISTOR BARGAINS send for complete lists. Quotation by return for any type of transistor.

BRIAN J. AYRES & CO.

Dept. ED, 8 Hartfield Road Wimbledon, London S.W.19 Telephone: Wimbledon 6063

SOLDERING?—the complete answer!

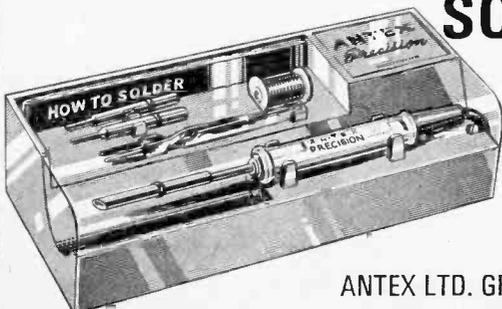

Made by ANTEX—makers of the finest precision soldering irons in the world, this Soldering Kit contains *everything* you need for successful soldering. Unique plastic "tool-box" format (with space for iron stowage *with* plug) keeps everything where you want it.

ANTEX LTD. GROSVENOR HOUSE, CROYDON, SURREY. MUNICIPAL 2774/5

**THE
PEMBRIDGE
COLLEGE
OF ELECTRONICS
FOR TRAINING
IN RADIO
AND TELEVISION**

**FULL-TIME COLLEGE COURSE
IN RADIO AND TELEVISION**

Our Course, of sixteen months' duration, provides a fundamental training for radio and television engineers. It includes theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Exactly half the time is spent on practical work and the course provides excellent practical experience on valve and transistor radio receivers and high-fidelity equipment and all well known makes of television receivers.

The Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Next Course commences 4th April, 1967.

To: **The Pembridge College of Electronics (Dept. P11)
34a Hereford Road, London, W.2.**

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name _____

Address _____

CMP 5

2 METRES 4

The thrills of VHF Amateur Radio! Complete Kit, 70-150 Mc/s, costs only 47/6 (by post, UK, 3/3 extra) also now available new transistor Short-Wave kit model TR2 10-180 metres. Ideal for beginners to Ham radio via simplified "Easy-Build" step-by-step instructions from 79/6. Write today enclosing a stamped addressed envelope for literature and full details. Overseas enthusiasts note we despatch to all parts of the world—local stamp OK for literature. "GLOBE-KING" (Regd.) precision standard products tried and trusted by Amateurs everywhere.

JOHNSONS (Radio)
St. Martins Gate, Worcester

WHEATSTONE BRIDGE KIT

Set of 18 x 1/4" Wirewound Resistors and 18 switches Measures 1Ω to 1MΩ. 70/6.

TRANSISTOR SQUARE WAVE GENERATOR
Useful for signal tracing or Morse practice. Variable amplitude. Parts to build 11/-.
300 Assorted 2 Watt Resistors, 1% to 20%, 13/6.

1% HIGH STABILITY RESISTORS
1/4 watt 1%, 2/- each. Full range 10Ω to 10mΩ. Selected to 1%, 6d. extra. Stock list available.

1% WIREWOUND RESISTORS
More stable than high stab carbon, and wound to any value 1Ω to 5kΩ, 3/3; to 20kΩ, 4/6. 1% acid 3d.
Circuits for Noughts and Crosses Machine, Demonstration Binary Adder/Subtractor, Analogue Multiplier/Divider, Football Pool Computer, Quadratic and Simultaneous Equation Solvers. Further details on request.

PLANET INSTRUMENT CO.

25 (W) DOMINION AVENUE, LEEDS 7.



396

£2
POST FREE

On your own **TRANSISTOR PORTABLE!**

- ★ Boosts Pirate and distant stations
 - ★ No Plugs—No Connections! Just place Dewtron Wave Trap near radio.
 - ★ Extends Battery life — reduces "fading".
 - ★ Use in car, caravan, without aerial. With PP3 battery (life several months).
- D.E.W. LTD., Dept. P.W., Ringwood Road, FERNDOWN, Dorset.

with the NEW Antex

PRECISION SOLDERING KIT

This is what the ANTEX Kit contains:

- Model CN240 15W Precision Iron with 3/16" bit, (used in electronic workshops and factories all over the world)
- Two spare Interchangeable Bits (5/32" and 3/32")
- Reel of resin-cored Solder
- Handy Heat Sink ● Cleaning Pad

BRING YOUR WORKSHOP UP-TO-DATE with the new ANTEX KIT

From electrical & radio shops, or if unobtainable locally apply direct to—

49/6

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

**ANTEX LTD. GROSVENOR HOUSE,
CROYDON, SURREY. MUNICIPAL 2774/5**

Broadway

ELECTRONICS

GARRARD 4 SPEED DECKS WITH CARTRIDGE:

Autochangers: AT6 Mk II £8.19.6.
Autoslim £5.5.0. AT60
£10.19.6. 3000, £8.8.0. 2000,
£6.19.6. 1000, £5.19.6. AT5—
Mono £6.10.0. P. & P. all changers
7/6.

SINGLE PLAYERS:

SP25 with cartridge stereo or
mono, £9.19.6. SRP 12, £4.5.0.
P. & P. 7/6.

CARTRIDGES:

Stereo: EV26, 25/- GP83, 15/-
Reuter, STD/2, 17/6. Mono: GC8,
15/- GC2, 15/- Sonotone, 2T/SS,
15/- GP67, 15/- P. & P. 1/-.

MICROPHONES:

Xtal Hand Mikes.

BM3 and 200C, 30/- P. & P. 2/-
Stand for same 9/6 & 12/6. P. & P.
1/9. ACOS Mike 45, 21/- ACOS
Mike 40, 18/6. Dyn, Mike DM-391,
22/6. CM21 Xtal, 12/6. CM20 Xtal,
9/6. Magnetic Hm 63C with remote
control switch, 15/- Telephone
Pick-up 10/6. P. & P. 1/- Xtal
Lapel Mike, 7/6. Guitar Mike,
12/6. P. & P. 6d.

BARGAINS IN TRANSISTORS:

AC127, AF114, 115, 116, 117,
118, 119, OC169, 170, 171, 172,
200, 202, 203, 204, 5/6.
OC72, 75, 82, 83, AAZ12,
BY38, BCZ11, 3/6. OC71, 81,
3/- R.F. Packs 1 OC44,
2 OC45 8/6. AF Packs 1
OC81D, 2 OC81 (Mullard),
8/6. A.F. Pack 1 GET119, 5/6.
GET113, Red Spot, 2/- OC26,
28, 29, 9/6. ORP12 Light Cell,
8/6. Diodes OA81, 2/3. OA91,
OA95, 1/9. P. & P. on above 6d.

TRANSISTOR ELECTROLYTICS:

1, 2, 4, 5, 8, 10, 16, 25, 32,
50, 100 mfd 15 volt working,
1/3. P. & P. 6d.
250 mfd DC 3/-, 500 mfd 12v
DC, 3/-, 500 mfd 50v DC, 5/-
P. & P. 1/-.

RESISTORS. ½ watt 10% from
3.3 ohm to 10 meg 5d. each.
4/- doz. P. & P. 6d.

EARPIECES WITH CORD AND
3.5 mm. plug, 8 ohm magnetic, 3/-
250 ohm, 4/-, 180 ohm with clip,
6/6. Xtal 4/- P. & P. 6d.

TRANSISTOR SPEAKERS 8 ohm
2in., 8/6; 3in. 10/6; 3½in. 12/6.
P. & P. 1/-.

PANEL LIGHTS, Neon 200-250v.
2/6. 6v. Red, Blue, Green, Yellow,
White (uses Lilliput bulbs) 3/- each.
P. & P. 6d.

PAPER CONDENSERS for Cross-
Over Units, 2 mfd. 2/6. P. & P. 6d.

92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON. S.W.17 Telephone BALham 3984

(four minutes from Tooting Broadway Underground Station)

SPEAKER ENCLOSURES
Tony Corner Cabinet 20 x 10 x
7in. takes 10 x 6in. speaker
covered in Rexine and Vynair,
45/- P. & P. 5/-.

Blake cabinet size 18 x 24½ x
9½in., fabric covered £4.10.0.
P. & P. 10/-.

Haydon, 16½ x 15 x 7½in. fabric
covered suitable for 12in.
speaker, 45/- P. & P. 7/6.

Haydon enclosure fitted with
12in. speaker and volume
control, £4.17.6. P. & P. 10/-.

Hi-Fi Bookshelf speaker en-
closure foam lined, cabinet
size 10½ x 5½ x 7½in. Teak
finish, £3.0.0. P. & P. 3/6.

Woofers for above £3.0.0. P. &
P. 2/6. Tweeter 12/6. P. & P.
1/6. Condenser for crossover
2/6. Terminals 2/6 pair. P. & P.
6d.

PLINTH Teak finish to match
above Hi-Fi speaker size
17½ x 14 x 4in. for Garrard
1000, 2000, 3000, AT60, SP25,
£2.17.6. P. & P. 4/6.

SPEAKERS:

Elac Heavy duty Ceramic
Magnets 11,000 line, 10in.
round 10 x 6in. 3 ohm or 15
ohm, 42/6. P. & P. 3/6. 8in.
round 15 or 3 ohm, 38/6. P. &
P. 3/6. E.M.I. 13½ x 8in. 15 or
3 ohm, 42/6. P. & P. 3/6.
E.M.I. Tweeter, 12/6. P. & P.
1/6. R.T.C. 12in. 20 watt 15
ohm, Ceramic magnet £5.5.0.
P. & P. 3/6. 8 x 4in Elliptical
30 ohm, 30/- P. & P. 3/6. All
other speakers supplied—
Goodmans, Bakers, W.B.,
Wharfedale, Eagle, Tripletone.

ROTARY SWITCHES


2 pole Mains Switch, 3/-, 1 pole
12 way, 2 pole 2 way, 3 pole 3 way,
3 pole 4 way, 4 pole 3 way, 3/6
each. P. & P. 6d.

PUSH BUTTON SWITCHES, 4
button, 2 banks of 6 S.P.C.O.,
1 bank of 5 S.P.C.O. 1 off button,
5/6. P. & P. 6d.

BATTERY CHARGER TRANS-
FORMERS AND RECTIFIERS 4
amp. GEC Rect., 15/- Heavy
Duty Transformer, 25/- P. & P.
3/6. 1 amp. Westinghouse contact
cooled rect., 7/6. Transformer 12/6.
P. & P. 3/-, Large Croc. Clips, 2/6
per pair, P. & P. 6d.

FERROX ROD AERIAL with
coils, 8 x ¾in., 8 x ½in. 5/6. 4 x ½in.
4/6. P. & P. 9d.

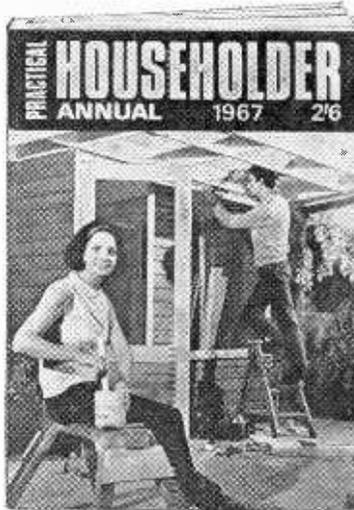Stockists of ● Eagle Products
● Goodmans ● W.B. ● Wharfe-
dale ● Bakers ● Tripletone
● Linear, all makes of ampli-
fiers and speakers supplied.
S.A.E. please. Trade terms to
bona fide dealers.



Get it Now!

YOUR GUIDE TO MAKING YOUR HOME BETTER, BRIGHTER, MORE EFFICIENT

Don't miss the 1967 PRACTICAL HOUSE-
HOLDER ANNUAL! It brings you masses
of new ideas for making your home more
attractive and efficient to live in... with
detailed instructions and clear how-to-
do-it illustrations that will enable you
to tackle any job like a professional.

Special Sections on:

HOME HEATING

All the latest developments in hot water central
heating, by perimeter heating and unit convec-
tors.

GUIDE TO HOME ELECTRICITY

A complete run-down for the handyman, with
diagrams, of domestic wiring circuits and how
they work.

HANDYMAN TOOLS

Invaluable information on hand and power
tools for the enthusiast.

OUTDOOR IMPROVEMENTS

How to build garden furniture—instructions
for building a summer house—stone, concrete
and brickwork around the house.

EASY HOME PLUMBING


How your hot water system works. Up to date
information on fittings for modern bathrooms.
Install your own shower.

PLAYTIME

Build for the children a complete outdoor play
unit of slide, shelter and sandbox and several
simple toys.

DECORATING

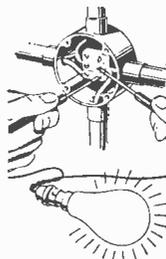Advice on long-lasting and attractive decora-
tions for the inside and outside of your home.



PRACTICAL HOUSEHOLDER ANNUAL 2/6


BIG DEMAND! MAKE SURE OF YOURS!




(14)



(12)

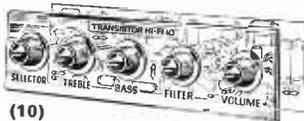

(10)

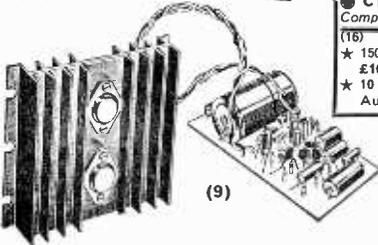

(9)

HENRY'S RADIO LTD.
303 EDGWARE RD., LONDON, W.2
PADdington 1008/9 (STD 01-723-1008)
Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday

12 AND 20 WATT MONO AND STEREO TRANSISTOR AMPLIFIERS

(9) **POWER AMPLIFIERS.** 12 watts RMS output. 100mV input. 30 c/s to 20 kc/s -1dB. 6-transistor Push-pull. Panel size 4 x 2½ x 1in. H/S 4 x 4in. (leaflet on request). MPA10/3 3-5 ohm spkr. £4.10.0, p.p. 2/6. MPA10/15 8-16 ohm spkr. £5.5.0, p.p. 2/6. (Mains unit 1 or 2 amplifiers, 59/6, p.p. 2/6).

The Finest High Fidelity at Unbeatable Prices

25 WATT AMPLIFIER
8-Transistor design. Push-pull output for 7½ to 16 ohm speaker. 150mV input. 30c/s to 20kc/s -1dB. For use with valve or transistor pre-amplifiers as item (10) above
PRICE BUILT £7.19.6 P.P. 3/-
(Mains unit 79/6, p.p. 2/6)

(13) MULTI-METERS SCOPE
PT34 1kV 39/6 EP30K 30kV £6.10.0
TP10 2kV 75/- EP50K 50kV £9.19.6
1T1-2 20kV 69/6 500 30kV £8.17.6
TP5S 20kV £5.19.6 EP100K 100kV £10.10.0
● **CT52 Scopes £22.10.0.** P.P. 10/-
Complete range of test equipment in stock

(16) NOMBREX TEST UNITS
★ 150 kc/s-350 mc/s RF Generator £10.10.0. All Transistor.
★ 10 c/s-100 kc/s Transistor. £16.19.6 Audio Generator.

(15) GARRARD BATTERY 2-SPEED TAPE DECK

Brand New with R/P head, erase/osc. head, tape cassette Specifications and osc. circuits. 2 speed 2-track 9 volt operated. List Price 13 9s. **£8.19.6** P. & P. 3/6

COMPONENTS AND EQUIPMENT. The largest range in the country. 8/6 buys 200-page catalogue with discount vouchers (see back page)

(10) **PREAMPLIFIERS.** 8 input selector. Treble, bass, volume, filter controls. 1½mV to 100mV inputs. Battery operated or from Mains Unit. Output up to 150mV RMS.

MP2 Mono 9½ x 2½ x 2in. £5.10.0, p.p. 2/6 (grey and gold front panel 8/6). SP4 Mono/Stereo, 9 x 3½ x 1½in. £10.19.6, p.p. 3/6 (front panel plate 12/6)
● ALL UNITS BUILT AND TESTED

(12) MW/LW QUALITY TRANSISTOR RADIO TUNER

Fully tunable superhet with excellent sensitivity and selectivity. Output up to ½ volt peak. Complete with front panel, etc. 9 volt operated. For use with any amplifier or tape recorder.

TOTAL COST £3.19.6 P.P. 2/6
TO BUILD

(14) VHF FM TUNER

Supplied as 2 Preassembled Panels, plus metal work Superhet design. 88-108 Mc/s. 9 volt operated. 6 Mullard Transistors. Total cost to assemble £12.17.6, p.p. 2/6

STABILISED POWER SUPPLY

Two outputs. 3.6 volt and 9.6 volt up to 250mA each. Transistorised and Zener stabilised. 110 to 250 volt mains input in case with leads. PRICE 67/6, p.p. 2/6.

(17) 5 WATT AMPLIFIER

6-Transistor Push-pull, 3 ohms. 6mV into 1K. 12-18V supply, 2½ x 2 x 1½in.

BUILT AND TESTED 69/6 P.P. 2/-
1½ watt version 59/6.

Matching Preamplifier, 6 Inputs, treble/bass/selector/volume controls. 6-10mV o/p. 9-18V supply. 79/6, p.p. 2/-.
For use with any Transistor Amplifier


(18) FMT41 FM TUNER. 6-transistor 3 diode design. Com- **£8.10.0** p.p. 2/-
pletely built and tested

(19) AMT31. Med. Wave Tuner Built ready to use. 79/5.

HR



(16)

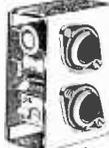

(17)



(13)



(15)

SEE BACK COVER FOR MORE ITEMS OF INTEREST



SUPPLIERS OF ELECTRONIC EQUIPMENT TO ...

* UNIVERSITIES
* COLLEGES OF TECHNOLOGY
* COLLEGES OF FURTHER EDUCATION & SCHOOLS
* ALL RADIO ENTHUSIASTS
OFFICIAL SUPPLIERS TO MANY EDUCATION AUTHORITIES
Usual Educational Discounts

OUR NEW 1966/67 illustrated catalogue NOW AVAILABLE
(send 1/- in stamps for your copy)

INCLUDES

Valves, Transistors, Transformers, Loudspeakers, Recording Tape, Coils, Resistors, Condensers, Potentiometers, Chassis, Rectifiers. Test meters, Microphones, Tools, Solder etc.

ALPHA RADIO SUPPLY CO

103 Leeds Terrace,
Wintown Street, Leeds 7
Telephone 25187

NEW RANGE U.H.F. AERIALS FOR BBC 2 (625) line transmissions

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays. 7 element. 35/-, 11 element. 42/6. 14 element. 50/-, 18 element. 57/6. **Wall Mounting with Cranked Arm.** 7 element. 60/-, 11 element. 67/-, 14 element. 75/-, 18 element. 82/6. **Roof Mounting with 2in. clamp.** 7 element. 42/6; 11 element. 55/-; 14 element. 62/-; 18 element. 70/-; **Chimney Mounting Arrays.** Complete. 7 element. 72/6; 11 element. 80/-; 14 element. 87/6; 18 element. 95/-; Complete assembly instructions with every unit. **Low Loss Cable.** 1/6 yd. U.H.F. Preamps. from 75/-; State clearly channel number required on all orders.

BBC · ITV · F.M. AERIALS

BBC (Band 1). Telescopic loft. 21/-; External S/D. 30/-; "H" £2.10.0.

ITV (Band 3). 3 Element loft array. 25/-; 5 element. 35/-; Wall mounting. 3 element. 35/-; 5 element. 45/-.

Combined BBC/ITV. Loft 1+3. 41/3; 1+5. 48/9; Wall mounting 1+3. 56/3; 1+5. 63/9; Chimney 1+3. 63/9; 1+5. 71/3.

VHF transistor pre-amps. 75/-.

F.M. (Band 2). Loft S/D. 12/6; "H". 30/-; 3 element. 52/6. External units available. Co-ax cable. 8d. yd. Co-ax plugs. 1/3. Outlet boxes. 4/6. Diplexer Crossover Boxes. 12/6. C.W.O. or C.O.D. P. & P. 5/-; Send 6d. stamps for illustrated lists.

Quotations for special arrays available on request

K.V.A. ELECTRONICS (Dept. P.W.)
27 Central Parade, New Addington
Surrey
LOD 2266

SPECIAL OFFERS ?

(No ... just normal Bothwell bargains)

H.F. SIRENS: Have you found another use for our powerful yet miniature high frequency horns? Already they are being used in burglar and fire alarms, and for all types of equipment where a clear penetrating sound is required. 1.5/4.5V D.C. only 3/6 each plus 1/- P. & P. per horn.

AERIAL WIRE: Pure copper, insulated; still available in 76 ft. reels at excellent price of 5/- plus 1/- P. & P.

RELAYS:

1. Miniature plug-in with 2 light duty c/o contacts. Coil 185 ohms. 41/18V. D.C. 15/-.
2. Miniature plug-in with 4 light duty c/o contacts. Coil 130 ohms. 9/15V. D.C. 18/9.
3. Heavy duty car alarm relay 6/12V. D.C. 3 heavy duty c/o contacts. 27/6. P. & P. on above items, 1/- each.
4. Base for item (2), 3/9 plus 6d. P. & P.

LOUDSPEAKERS: We carry a range of speakers to suit every application. Typical examples are:

1. Westwell 0.2W.: 8 ohm; 2½in. dia., 7/9.
2. Westwell 0.2W.: 8 ohm; 3in. dia., 9/6.
3. Richard Allan 1½in. 3 ohm with tweeter. 37/6 plus 3/- P. & P.

TEST METERS: ITI-2. A superb buy for the discerning engineer with a limited budget. 20K ohms/V.; with all the usual desirable features for testing and experimenting. A snip at 69/6 plus 3/- P. & P.

TEST LEAD KITS: Complete with plastic case. 6/9 plus 1/3 P. & P.

RECORD PLAYER AMPLIFIER: Powerful single valve amplifier (EI.84) with metal rectifier. Complete with volume and tone controls. 220/250V. A.C. only. 59/6 plus 3/- P. & P. And, of course, all Sinclair and Lander products always in stock.

Write or call now for our components list



BOTHWELL ELECTRIC SUPPLIES (Glasgow) LTD.
54 EGLINTON STREET
GLASGOW, C.S. Tel. 041 500TH 5904
Member of the Lander Group

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
 Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling

MINIMUM CHARGE 2/-. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
 Tel. LANGHAM 8403
 Open all day Saturday

0A2	6/-	6AF4	10/-	6FA8	11/-	10C1	12/-
0A3	10/-	6AF90	11/-	6F1	14/-	10C2	13/-
0B2	6/-	6AG5	2/6	6F4	30/-	10D1	7/-
0C8	6/-	6AG6	6/-	6F5	10/-	10D2	7/-
0D8	6/-	6AH6	10/-	6F6	5/-	10F3	8/-
0Z4A	5/-	6AK5	5/-	6F7	5/-	10F9	10/-
1A3	4/-	6AL5	3/-	6F8	5/-	10F18	9/-
1A5	5/-	6AM6	4/-	6F11	6/-	10L1	7/8
1A7GT	8/-	6AN8	10/-	6F12	4/-	10P13	15/-
1B3GT	8/-	6AQ4	5/-	6F13	6/6	10P14	15/-
1C5GT	5/-	6AQ5	5/6	6P14	15/-	11D3	7/-
1D6	8/-	6AR5	6/-	6F15	11/-	11D6	7/-
1D8	6/-	6AR8	6/-	6F17	6/-	12AC6	8/-
1G4GT	8/-	6ARR	17/6	6F18	7/8	12AD6	9/-
1G6GT	7/-	6AS5	5/-	6F23	10/-	12AR6	7/8
1H3GT	7/-	6AS6	8/-	6F24	12/-	12AL5	7/-
1L4	2/6	6AR75	15/-	6F25	12/-	12AQ5	7/-
1N5GT	8/-	6AT6	4/6	6F28	10/8	12AT6	5/-
1R4	6/-	6AU6	5/6	6H6	2/-	12AT7	4/-
1R5	6/-	6AU8	9/-	6J4	3/-	12AT8	6/-
1S4	5/-	6AV5GTA	4/-	6J6	4/-	12AV7	5/6
1S5	4/6	6AV6	11/-	6J8	3/6	12AV6	5/6
1T4	3/-	6AV6	5/-	6J7	5/-	12AV7	8/-
1T5GT	6/-	6AV8A	12/6	6K6	6/-	12AW6	20/-
1U4	5/-	6B4G	17/6	6K7GT	5/-	12AX7	6/-
1U5	6/-	6B8	7/-	6K5	8/-	12AY7	10/-
1Y2	10/-	6B8G	2/6	6K6G	6/-	12AY7	10/-
1X2B	7/-	6BA6	4/6	6L6G	7/6	12BA6	6/-
2C26A	7/-	6BA7	15/-	6L7	5/-	12B5E	6/6
2C34	7/8	6B8E	4/8	6L17	9/-	12B7	6/-
2C31	12/-	6BF6	6/-	6L18	6/-	12B7	6/-
2C34	12/-	6B77	15/-	6L19	5/-	12B7	6/-
2D21	6/-	6B6G6	16/-	6L19	5/-	12B7	6/-
2E24	40/-	6B16	7/6	6P25	12/-	12K5	5/-
2E36	22/6	6B16	7/6	6P28	12/6	12K7GT	7/-
3A4	4/-	6BK4	22/6	6Q5	15/-	12ATG	7/-
3A5	7/-	6B37A	9/-	6Q6	7/-	12ATG	7/-
3ANGT	8/-	6BL7GTA	8/-	6Q7	7/-	12A7	7/-
3A7	6/6	6B7	10/-	6A7	7/-	12B7	7/-
3B5	5/-	6BN6	7/6	6B7	8/-	12B7	7/-
3B8	40/-	6BQ7A	7/-	6B7	8/-	12B7	7/-
3D6	4/-	6B7	15/-	6B7	8/-	12B7	7/-
3E29	60/-	6BR8	5/-	6B7	8/-	12B7	7/-
3Q4	7/-	6B87	17/-	6B7	8/-	12B7	7/-
3Q5GT	6/6	6B7	17/-	6B7	8/-	12B7	7/-
3S4	5/-	6B7	10/-	6B7	8/-	12B7	7/-
3V4	6/-	6B7	10/-	6B7	8/-	12B7	7/-
4-65A	80/-	6B7	11/-	6B7	8/-	12B7	7/-
4E27	60/-	6C4	3/6	6B7	8/-	12B7	7/-
4TEA	8/-	6C5	8/-	6B7	8/-	12B7	7/-
4T8P	8/-	6C5GT	6/-	6B7	8/-	12B7	7/-
4X150A	100/-	6C8	4/-	6B7	8/-	12B7	7/-
4X250B	120/-	6C8	4/-	6B7	8/-	12B7	7/-
5R4G	9/-	6C8	4/-	6B7	8/-	12B7	7/-
5U4	5/-	6C8	4/-	6B7	8/-	12B7	7/-
5U5B	6/6	6C8	4/-	6B7	8/-	12B7	7/-
5U8	9/-	6C8	4/-	6B7	8/-	12B7	7/-
5V4G	8/-	6C8	4/-	6B7	8/-	12B7	7/-
5Y3GT	5/-	6C8	4/-	6B7	8/-	12B7	7/-
5Z3	7/8	6C8	4/-	6B7	8/-	12B7	7/-
5Z4G	7/8	6C8	4/-	6B7	8/-	12B7	7/-
6-30L2	8/8	6C8	4/-	6B7	8/-	12B7	7/-
6A8	8/-	6C8	4/-	6B7	8/-	12B7	7/-
6A8A	6/6	6C8	4/-	6B7	8/-	12B7	7/-
6A87	4/-	6C8	4/-	6B7	8/-	12B7	7/-
6AC3GT10/-	6/6	6C8	4/-	6B7	8/-	12B7	7/-
6AC7	4/-	6C8	4/-	6B7	8/-	12B7	7/-

First Quality Fully Guaranteed



ELECTRONIC VALVES

3011	5/6	872A	40/-	DF33	8/-	ECC84	6/6
30115	15/-	884	15/-	DF64	5/-	ECC85	5/-
30117	15/-	955	3/-	DF91	3/-	ECC86	7/-
30118	15/-	956	2/-	DF92	2/6	ECC88	8/-
30119	7/-	957	5/-	DF93	7/8	ECC91	8/6
30118	6/-	958A	4/-	DH63	6/-	ECC18	11/-
30119	13/-	959	8/-	DK32	8/-	ECC80	10/-
30115	15/-	991	7/-	DK40	11/-	ECC80	10/-
30115	15/-	1267	20/-	DK91	6/-	ECC82	7/6
30114	15/-	2050	12/-	DK92	8/-	ECC82	12/-
35A3	10/-	4313C	20/-	DK93	7/-	ECC86	8/6
35A5	10/-	3561	7/6	D133	6/8	ECH35	11/-
35B5	12/-	3564	8/-	D135	5/-	ECH42	9/6
35C5	6/6	3570	10/-	D168	10/-	ECH81	5/3
35D5	12/-	3578	10/-	D169	12/8	ECH83	7/6
35E5	5/-	3579	10/-	D191	5/-	ECH84	9/-
35V4	4/6	3571	12/-	D192	5/-	ECL90	7/-
35Z3	10/-	3573	10/-	D193	4/-	ECL81	7/6
35Z4	4/-	3514A	10/-	D194	6/-	ECL82	6/3
35Z4GT	8/8	3595	5/-	D195	7/-	ECL83	9/6
35Z5GT	5/6	3525GT	5/6	D196	7/-	ECL84	12/-
36A	6/6	3600	5/-	D197	7/-	ECL85	11/6
36B	6/6	3610	25/-	DM70	5/8	ECL86	11/6
36C	6/6	3620	25/-	DY30	8/-	ECL87	9/-
36D	6/6	3630	32/-	DY66	8/8	EY36	5/-
36E	6/6	3640	32/-	E880C	12/6	EY37A	8/-
36F	6/6	3650	30/-	E880C	10/-	EY38	8/-
36G	6/6	3660	27/6	E893	4/6	EY39	6/-
36H	6/6	3670	27/6	E893	4/6	EY40	6/-
36I	6/6	3680	27/6	E893	4/6	EY41	6/-
36J	6/6	3690	27/6	E893	4/6	EY42	6/-
36K	6/6	3700	27/6	E893	4/6	EY43	6/-
36L	6/6	3710	27/6	E893	4/6	EY44	6/-
36M	6/6	3720	27/6	E893	4/6	EY45	6/-
36N	6/6	3730	27/6	E893	4/6	EY46	6/-
36O	6/6	3740	27/6	E893	4/6	EY47	6/-
36P	6/6	3750	27/6	E893	4/6	EY48	6/-
36Q	6/6	3760	27/6	E893	4/6	EY49	6/-
36R	6/6	3770	27/6	E893	4/6	EY50	6/-
36S	6/6	3780	27/6	E893	4/6	EY51	6/-
36T	6/6	3790	27/6	E893	4/6	EY52	6/-
36U	6/6	3800	27/6	E893	4/6	EY53	6/-
36V	6/6	3810	27/6	E893	4/6	EY54	6/-
36W	6/6	3820	27/6	E893	4/6	EY55	6/-
36X	6/6	3830	27/6	E893	4/6	EY56	6/-
36Y	6/6	3840	27/6	E893	4/6	EY57	6/-
36Z	6/6	3850	27/6	E893	4/6	EY58	6/-
37A	6/6	3860	27/6	E893	4/6	EY59	6/-
37B	6/6	3870	27/6	E893	4/6	EY60	6/-
37C	6/6	3880	27/6	E893	4/6	EY61	6/-
37D	6/6	3890	27/6	E893	4/6	EY62	6/-
37E	6/6	3900	27/6	E893	4/6	EY63	6/-
37F	6/6	3910	27/6	E893	4/6	EY64	6/-
37G	6/6	3920	27/6	E893	4/6	EY65	6/-
37H	6/6	3930	27/6	E893	4/6	EY66	6/-
37I	6/6	3940	27/6	E893	4/6	EY67	6/-
37J	6/6	3950	27/6	E893	4/6	EY68	6/-
37K	6/6	3960	27/6	E893	4/6	EY69	6/-
37L	6/6	3970	27/6	E893	4/6	EY70	6/-
37M	6/6	3980	27/6	E893	4/6	EY71	6/-
37N	6/6	3990	27/6	E893	4/6	EY72	6/-
37O	6/6	4000	27/6	E893	4/6	EY73	6/-
37P	6/6	4010	27/6	E893	4/6	EY74	6/-
37Q	6/6	4020	27/6	E893	4/6	EY75	6/-
37R	6/6	4030	27/6	E893	4/6	EY76	6/-
37S	6/6	4040	27/6	E893	4/6	EY77	6/-
37T	6/6	4050	27/6	E893	4/6	EY78	6/-
37U	6/6	4060	27/6	E893	4/6	EY79	6/-
37V	6/6	4070	27/6	E893	4/6	EY80	6/-
37W	6/6	4080	27/6	E893	4/6	EY81	6/-
37X	6/6	4090	27/6	E893	4/6	EY82	6/-
37Y	6/6	4100	27/6	E893	4/6	EY83	6/-
37Z	6/6	4110	27/6	E893	4/6	EY84	6/-
38A	6/6	4120	27/6	E893	4/6	EY85	6/-
38B	6/6	4130	27/6	E893	4/6	EY86	6/-
38C	6/6	4140	27/6	E893	4/6	EY87	6/-
38D	6/6	4150	27/6	E893	4/6	EY88	6/-
38E	6/6	4160	27/6	E893	4/6	EY89	6/-
38F	6/6	4170	27/6	E893	4/6	EY90	6/-
38G	6/6	4180	27/6	E893	4/6	EY91	6/-
38H	6/6	4190	27/6	E893	4/6	EY92	6/-
38I	6/6	4200	27/6	E893	4/6	EY93	6/-
38J	6/6	4210	27/6	E893	4/6	EY94	6/-
38K	6/6	4220	27/6	E893	4/6	EY95	6/-
38L	6/6	4230	27/6	E893	4/6	EY96	6/-
38M	6/6	4240	27/6	E893	4/6	EY97	6/-
38N	6/6	4250	27/6	E893	4/6	EY98	6/-
38O	6/6	4260	27/6	E893	4/6	EY99	6/-
38P	6/6	4270	27/6	E893	4/6	EY100	6/-

EL22	15/-	KT32	6/6	PL302	13/-	U251	6/-
EL33	12/6	KT36	17/8	PL500	13/6	U281	12/-
EL34	9/6	KT41	7/6	PL15	15/-	U282	12/-
EL35	5/-	KT44	5/-	PL4	20/-	U301	11/-
EL36	8/8	KT45	15/-	PL25	15/-	U403	7/-
EL38	17/8	KT66	16/-	PL32	8/6	U404	5/-
EL41	8/6	KT67	45/-	PL33	8/6	U408	17/8
EL42	7/6	KT76	8/-	PL30	5/6	UA10	5/6
EL43	9/-	KT88	23/-	PL31	8/6	UA14	10/-
EL52	8/-	LP2	7/-	PL32	5/6	UB41	8/-
EL53	7/-	MH4	5/-	PL33	6/6	UBC41	9/-
EL54	4/3	MH41	9/-	PL34	8/6	UBC81	8/6
EL55	7/8	MHL4	5/-	PL35	11/-	UBF80	6/6
EL56	8/-	MS/PEN	8/-	PL36			

The following blueprints are available from stock. **Descriptive text is not available but the date of issue is shown for each blueprint. Send, preferably, a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.**

The Strand Amplifier } The PW Signal Generator }	(Oct. 1962) 5/-	The Celeste 7-transistor Portable Radio } The Spinette Record Player }	(June 1963) 5/-
The Berkeley Loudspeaker Enclo- sure } The Luxembourg Tuner }	(Dec. 1962) 5/-	Transistor Radio Mains Unit } 7 Mc/s Transceiver }	(June 1964) 5/-
The PW Troubadour } The PW Everest Tuner }	(June 1962) 7/6	The Citizen (December 1961) }	5/-
The PW Britannic Two } The PW Mercury Six }	(May 1962) 6/-	The Mini-amp (November 1961) }	5/-
Beginner's Short Wave Two S.W. Listener's Guide }	(Nov. 1963) 5/-	The PT Multimeter (October 1961) PT }	5/-
Beginner's 10-watt Transmitter Transmitting and Aerial Data }	(Dec. 1963) 5/-	The Beginner's Short Wave Superhet (Dec. 1964)	5/-
PW "Sixteen" Multirange Meter } Test Meter Applications Chart }	(Jan. 1964) 5/-	The Empire 7 Three-band Receiver (May 1965) }	5/-
		Electronic Hawaiian Guitar (June 1965) }	5/-
		Progressive SW Superhet (February 1966) }	5/-
		Beginners' 5-Band Receiver } Home Intercom Unit }	(Dec. 1966) 5/-

PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN
★ THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL ★
RADIO, TV OR AUDIO EQUIPMENT.

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) **We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

QUERY COUPON

This coupon is available until 3rd March, 1967 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, MARCH 1967



1967 CATALOGUE 200 PAGES PLUS!




COMPLETELY NEW EDITION — HUNDREDS OF NEW LINES

● Contains the largest and most comprehensive range of components and equipment available. Over 5,000 stock lines with more data, more information and illustrations. Hundreds of bargain lines. You cannot afford to be without a copy of this catalogue. Supersedes all previous editions. PRICE 7/6. p.p. 1/-

● 5 FREE VOUCHERS
Total value 10/- for use on purchases. Pays for catalogue after use.



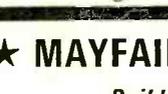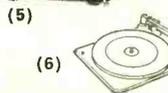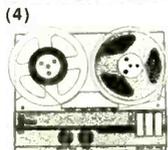● Unbeatable value — 200 packed pages — 10/- value discount vouchers ●



MARIOT TAPE HEADS
1 Track R/RP/3 Med z. 7/6. R/RP/1 High x, S/-, R/RP/1 High z + R/E/1 erase on block, 19/6. 4 Track L/R/S/P/2 High z 15/-, L/R/S/7 Med z. 19/6. L/E/S/9 erase, 12/6. Also H-R-R/P single track Rec/Play Med z. 6/6

DEAC RECHARGEABLE BATTERY
● 9.6 volt 225mA H 20/-, p.p. 1/6
DEAC CHARGER
To charge 3.6 volt and 9.6 volt packs. Fully mains isolated. 45/- P.P. 2/-
In moulded case.

(4) **BUILD A QUALITY 2 OR 4 TRACK TAPE RECORDER**
3-speed version using '363' decks
● TWO-TRACK. Deck £10.10.0. Martin Amplifier. £14.19.6. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 1200ft. tape, spare spool. **27 gns.** P.P. 15/-
● FOUR-TRACK. Deck £13.10.0. Martin Amplifier £15.19.6. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 1200ft. tape, spare spool. **30 gns.** P.P. 15/-
Today's Value £50.

(6) **GARRARD DECKS — BRAND NEW FULLY GUARANTEED**

1000 mono	£5 19 6	SP25 stereo	£10 19 6	401 less cart./arm	£27 10 0
AT5 mono	£9 9 6	SP25 Deram	£13 19 6	AT9 mono Mk. II	£5 19 6
2000 mono	£6 9 6	AT60 less cart.	£10 19 6	AT6 stereo Mk. II	£9 10 0
2000 stereo	£6 19 6	AT60 mono	£11 10 0	AT6 Deram	£11 19 0
3000 1 in stereo	£7 10 0	AT60 stereo	£11 19 6	Decadec Mk. II	£17 17 0
SP25 less cart.	£9 19 6	AT60 Deram	£14 19 6	A70 less cart.	£17 17 0
SP25 mono	£10 10 0	LA180 less cart.	£25 0 0	(P. and P. 5/- any type)	

All other makes of decks and cartridge in stock.

(7) **GLOBEMASTER MW/LW/SW PORTABLE RADIO TO BUILD**
Full 3-waveband tuning. Pushbutton wave-change. Superhet printed circuit design. Black-chromed cabinet 11 x 7 1/2 x 3 1/2 in. (SW 17-50 metres). Ear/Record sockets. 1 watt Push/Pull output. 6 Mullard Transistors.
TOTAL COST TO BUILD £7.19.6 P.P. 3/6

VALVE AMPLIFIERS AND TUNERS IN CABINETS
● SA100. 5+5 watt Stereo. 300mV Input watt version. Also Inc. FM Tuners, P.U's, etc. puts for Mag. Mic. optnl. **£15.15.0** P.P. 5/-
● SA200. 7+7 watt Stereo. 300mV Input watt version. Also Inc. FM Tuners, P.U's, etc. puts for Mag. Mic. optnl. **£25.10.0** P.P. 7/6
● AFM 200. AM/FM tuner to match SA100. **£30** P.P. 7/6
● AFM 200. AM/FM tuner to match SA200. etc. self-powered mains. **£30** P.P. 5/- (AFM100 and 200 may be used with any amplifier)

SUPPLIERS OF QUALITY COMPONENTS AND EQUIPMENT FOR MORE THAN 20 YEARS

SCR'S (THYRISTORS)
● 1 AMP SERIES WIRE LEADS
50 PIV 7/6 100 PIV 7/6
200 PIV 12/6 300 PIV 15/-
400 PIV (280V Rms) 17/6
100 PIV, 3 Amp Stud Type 8/6
400 PIV, 7 Amp (280V Rms) Stud Type 25/-
400 PIV, 3 Amp (280V Rms) Stud Type 26/-

FM STEREO DECODER
7 Mullard Transistors. Printed Circuit Design with Stereo Indicator. For use with any valve or transistor FM. Uses pot cores to Mullard design and ger. and silicon transistors.
Complete Kit Price **£5.19.6** P.P. 2/-

(5) **VHF FM TUNER TO BUILD**
87/105 Mc/s Transistor Superhet. Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3 1/2 x 2 1/2 in. Complete with dial plate. 5 Mullard Transistors (FM Decoder Kit £5.19.6. P.P. 2/-).
TOTAL COST TO BUILD £6.19.6 P.P. 2/6
(Cabinet Assembly 20/- extra)

TUNNEL DIODES
1mA 22/6; 5mA 15/-; 15mA 12/6.
Brand new at fraction of normal price. Free Specs. supplied.

TRANSISTOR CATALOGUE
Completely new 24-page 1967 edition. Hundreds of new types with details. The largest range available. Send 1/- for your copy.

(1) **REGENT-6 MW/LW POCKET RADIO TO BUILD**
6-Transistor superhet. Geared tuning. 6-Transistor speaker output. Moulded cabinet 5 x 3 x 1 1/2 in. Phone socket.
TOTAL COST TO BUILD 69/6 P.P. 2/-
Full tuning on both bands

HI-FI EQUIPMENT from stock: ARMSTRONG, GEAD, GOODMANS, LEAK, ROGERS, TRUVOX, ETC.
Complete range in stock. Send list of requirements for special price quote. Hi-Fi demonstration room open.

WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION.

OR BETTER STILL—BUY THE NEW 1967 CATALOGUE EVERYTHING YOU NEED IS LISTED.

"EXPLORER" (P.W. Jan. 1967) MW/VHF Receiver. All parts as specified (less chassis, etc.). 79/6. P.P. 2/6. Parts list on request.

HENRY'S RADIO LTD.
303 EDGWARE RD., LONDON. W.2
P.A. Ddington 1008/9 (STD 01-723-1008)
Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday

★ MAYFAIR PORTABLE ELECTRONIC ORGAN

Build the World's first All-Transistor Portable Electronic Organ Kit

- Plug-in printed circuits ● 170 transistors and devices ● 10 selected tone colours ● Fully sprung keyboard ● Vibrato ● 6 Octaves of generators ● Simple locked-in tuning ● 110/250 volt mains unit ● Cabinet size 30 1/2" x 15 1/2" x 9"
- Weight 35 lb. Cabinet with detachable legs, music stand and foot swell pedal
- Fully detailed building manual with photos, drawings and full circuits.

TO BUILD YOURSELF IN EASY STAGES. ALL PARTS SOLD SEPARATELY.

START BUILDING FOR AS LITTLE AS £5. BUILD THE MAYFAIR A SECTION AT A TIME.

SEE PAGE 879 FOR MORE ADVERTS

- * COMPLETE KIT 99 GNS. (CARR. 30/-).
- * HP FACILITIES AVAILABLE.
- * COMPLETE RANGE OF ORGAN COMPONENTS IN STOCK.

Detailed leaflet on request

Acclaimed by everyone

DESIGNED BY L. W. ROCHE



SEE FOR YOURSELF CALL IN FOR DEMONSTRATION