

# PRACTICAL WIRELESS

MAY  
1967

216

A MULTIPURPOSE  
**AUDIO SWITCH**




**SPECIAL**  
IN THIS ISSUE

A 70 cm Converter

3-Band  
Reflex  
Receiver


Simple  
Analogue  
Computer

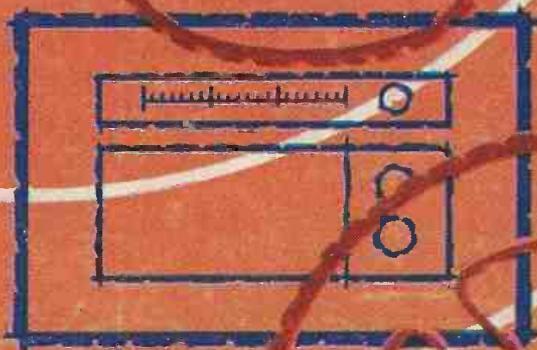



## SOLDERING EQUIPMENT

FOR  
THE  
RADIO  
CONSTRUCTOR

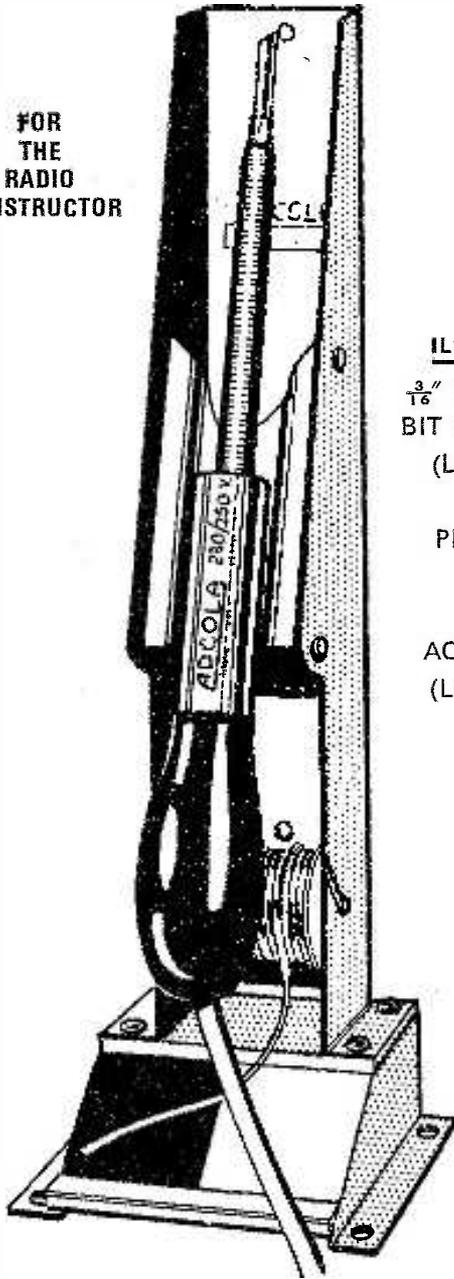

**ILLUSTRATED**  
 $\frac{3}{16}$ " DETACHABLE  
BIT INSTRUMENT  
(List No. 64)  
IN  
PROTECTIVE  
SHIELD  
WITH  
ACCESSORIES  
(List No. 700)


FOR CATALOGUES APPLY DIRECT

**ADCOLA PRODUCTS LTD.**  
**ADCOLA HOUSE**  
**GAUDEN ROAD,**  
**LONDON, S.W.4**

Telephones:  
MACaulay 0291/3

Telegrams: "SOLJOINT" LONDON SW4

## NOMBREX INSTRUMENTATION

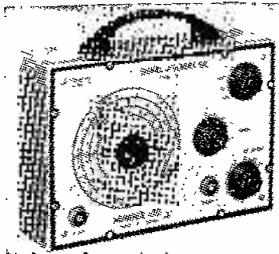

### WIDE RANGE TRANSISTORISED SIGNAL GENERATOR MODEL 27


- ★ Range 150Kc/s-350Mc/s
- ★ Direct Calibration
- ★ Mod. or Unmod. output
- ★ Accuracy better than 2% £10.18.9.

#### ALSO AVAILABLE

C. R. Bridge 62 .. ..	£9.8.9
Inductance Bridge 66 ..	£18.8.9
Power Supply Unit 61 ..	£6.16.6
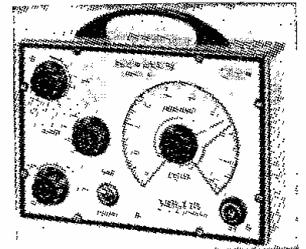
### WIDE RANGE TRANSISTORISED AUDIO GENERATOR 63

- ★ Range 10c/s-100Kc/s
- ★ Sine or Square Wave
- ★ Accuracy & Low Dist.
- ★ Calibrated Output £17.3.9



All prices include battery, post and packing

S.A.E. for Leaflet      Trade & Export Enquiries Invited      Prompt Delivery

## NOMBREX LTD INSTRUMENTS DIVISION

Estuary House, Camperdown Ter., Exmouth, Devon



for quick  
easy faultless  
soldering

Containing 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy reduces wear of copper soldering iron bits.




**SIZE 5  
HANDY SOLDER  
DISPENSER**  
Contains 12 ft.  
coil of 18 s.w.g.  
Ersin Multicore  
Savbit Alloy.  
2/6 each



**SIZE 15**  
21 ft coil of 60/40  
Alloy, 22 s.w.g. in  
a dispenser. Ideal  
for small compon-  
ents, transistors,  
diodes, etc.  
3/- each



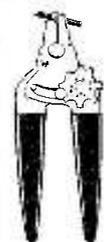**SIZE 12**  
Ideal for home  
constructors.  
Contains 102 ft.  
of 18 s.w.g. Ersin  
Multicore Savbit  
Alloy on a plastic  
reel. 15/- each



**BIB MODEL 8  
WIRE STRIPPER  
AND CUTTER**  
Strips insulation  
without nicking  
the wire, cuts  
wire and splits  
plastic twin flex.  
Plastic cushioned  
handles. 8/6 each

From Electrical or Hardware shops. If unobtainable write to:  
**Multicore Solders Ltd., Hemel Hempstead, Herts.**



# JASON

## ★ TAPE ★

We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT YOURSELF.

Standard Play		Long Play	
3in. 150ft. 2/3	3in. 225ft. 2/9	4in. 300ft. 4/6	4in. 450ft. 5/6
5in. 600ft. 7/6	5in. 900ft. 10/6	5 1/2in. 900ft. 10/6	5 1/2in. 1,200ft. 13/6
7in. 1,200ft. 12/6	7in. 1,800ft. 18/6	Double Play	
Triple Play		3in. 300ft. 4/-	4in. 900ft. 13/6
4in. 600ft. 8/-	5in. 1,800ft. 25/6	5in. 1,200ft. 15/-	5 1/2in. 2,400ft. 34/6
5 1/2in. 1,800ft. 19/6	7in. 3,600ft. 44/6	Quadruple Play	
7in. 2,400ft. 27/6	3in. 600ft. 8/6		

Postage 1/- reel.  
Post Free less 5% on three reels.

Quantity and Trade enquiries invited.  
NOTE. Large tape stocks at all branches.


## BARGAIN PARCELS

Including variable condensers, i.f. coils, loud-speaker plugs/sockets, knobs, pots, condensers, resistors, nuts, bolts, cabinet fittings, switches, transformer choke, rectifier, transistors at a small fraction of list value. Due to heavy demand we are now packing them in several sizes—TRY ONE.

3 lbs. (post 3/-)	9/-
7 lbs. (post 5/-)	17/6
14 lbs. (post 8/-)	29/-
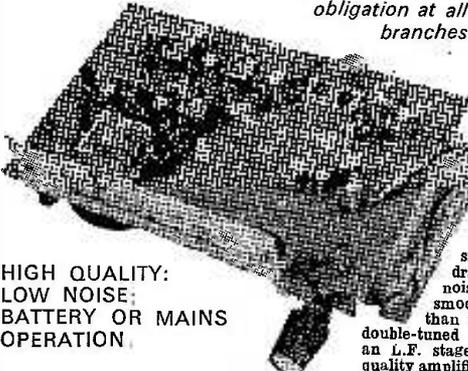
# Transistorised FM Tuner

CALLERS WELCOME Demonstration without obligation at all branches



HIGH QUALITY:  
LOW NOISE:  
BATTERY OR MAINS  
OPERATION

**TRANSISTORS GUARANTEED TOP QUALITY**  
Mullard Matched Output Kits OC81D and 2-OC81 .. 9/6  
R.F. Kits OC44, OC45 (2) 3 transistors .. 9/6

## GERMANIUM DIODES

General Purpose miniature detector A.V.C. etc. 6/6 doz. 8d.

Gold Bonded highest quality. Individually tested 9/6 doz. 1/-

## SILICON H.T. RECTIFIERS

Guaranteed performance. Top makes. Tested 250v. working. 120 mA (3 for 8/6) 2/9  
500 mA (3 for 19/6) 7/6

This beautifully compact 6 transistor machine (size 6 x 4 x 2 1/2 in.) will give quiet-er, more interference free reception. Months of use from a standard 9 volt battery or its small power requirements can be drawn from any amplifier. Low noise frequency changer with smooth 2 gang tuning feeding no less than three I.F. stages coupled to a double-tuned discriminator terminating in an L.F. stage giving ample output for all quality amplifiers.

## LATEST GARRARD

All Factory Fresh. All with cartridge. EV26 Ceramic Stereo cartridge fitted to any deck for 15/- extra.

SRP12 .....	£2.7.6
SP25 .....	£9.19.0
AUTOSLIM .....	£5.10.0
Model 1,000 .....	£6.5.0
Model 2,000 .....	£6.10.0
Model 3,000 .....	£8.10.0
AT60 .....	£9.19.0
A70 .....	£18.10.0
LAB80 .....	£24.19.0
401 .....	£29.19.0

## B.S.R. BARGAINS

TU14 .....	59/-
GU7 .....	85/-
UA14 .....	89/-
UA16 .....	99/-
UA25 SUPERSLIM .....	£5.10.0

## CARTRIDGES

G.C.2. Garrard Mono .....	16/-
EV26 Garrard Stereo Ceramic .....	24/-
EUPHONIC SUPER Ceramic Stereo Diamond 100mV Output .....	29/-

avoid disappointment

# ORDER NOW £8-10

AVOID AMPLITUDE DISTORTION WITH YOUR HI-FI AMP.

## STABILISED TRANSISTOR POWER SUPPLY

- VARIABLE 0—15V. AT 0—1 AMP.
- STABILISED FOR MAINS VAR. 210 - 250V.
- RIPPLE CORRECTED
- SHORT CIRCUIT PROTECTION
- HANDSOME STYLED CABINET

★ PRICE ONLY 6GNS.

## 10 WATT TRANSISTOR AMP

Consisting above stabilised power pack (can be used separately), with built-in pre-amp and controls driving two x OC26 main amp. in styled cabinet. New concept in value and design. 10 transistors, selection, vol. and tone controls equalisation.

PRICE 12GNS.

## ELPICO MONO PREAMPS

DPA15. Latest black/satin chrome finish multiple input channels selector bass and treble controls. Matches all pick-ups and mikes. Provision tape recording. 4 Gns. Normally 10 gns. our price

## Value in VALVES GUARANTEED 3 MONTHS BY RETURN OF POST

Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED. FREE TRANSIT INSURANCE. POSTAGE 1 valve 9d. 2-11 6d. per valve. Free over 12.

1L4	2/3	6K5GT	9/6	20P4	17/9	ECC88	9/6	GZ34	10/6	SP61	2/9
1R5	4/9	6L1	9/6	25L6GT	7/-	ECF80	7/9	KT61	12/-	TDD4	7/-
1S4	4/9	6L6G	8/6	25Z4G	7/-	ECF82	7/6	KT63	5/9	U14/18	7/6
1S5	4/6	6L18	7/9	30F5	9/-	ECH21	10/-	KT66	19/6	U85	9/6
1T4	3/6	6LD20	8/6	30FL1	9/9	ECH35	11/-	KT88	27/6	U86	9/6
2D21	5/6	6P25	12/-	30L15	11/6	ECH42	10/6	KTW61	5/9	U85	12/6
3A5	6/-	6P28	9/6	30P4	11/6	ECH81	6/9	KTW63	5/-	U37	11/-
3Q4	5/3	6Q7G	7/-	30P12	9/-	ECH83	7/9	KTZ63	7/-	U107	12/6
5U4G	6/-	6Q7GT	8/9	30PL1	11/-	ECL80	5/9	MU14	7/-	U191	12/6
5Y3GT	6/6	6SL7GT	6/9	35A5	9/6	ECL82	7/6	N87	9/6	U281	9/6
5Z4G	6/9	6SN7GT	6/9	35L6GT	8/6	ECL83	10/6	N78	13/-	U282	15/-
5Z4GT	9/6	6U4GT	9/6	35W4	6/6	ECL86	9/6	N108	13/-	U329	8/6
6X0L2	9/6	6V6G	4/9	35Z4GT	5/9	EF36	4/9	PC86	9/6	U801	19/6
6AB6	7/6	6V6GT	6/9	30L6GT	8/9	EF39	7/-	PC97	7/6	UABC80	6/9
6AK5	4/9	6X4	4/6	80	7/6	EF40	10/-	PC084	6/6	UAF42	7/9
6A45	5/-	6X5GT	5/-	185BTA	19/6	EF41	9/-	PC085	7/6	UB41	6/6
6A46	5/6	6X5GT	6/9	307	9/6	EF50	3/3	PC088	11/9	UBC41	8/9
6BA6	5/6	7B7	7/6	955	3/6	EF80	4/3	PC089	11/-	UBC81	6/9
6BE6	5/6	7C7	7/6	956	3/6	EF85	6/3	PC189	9/9	UBF80	7/6
6BH6	6/6	7C5	9/6	AZ31	3/6	EF86	7/6	PCF80	6/9	UBF89	7/6
6B16	6/6	7C6	7/6	CB131	19/6	EF89	6/6	PCF82	6/9	UBL21	10/9
6BR7	9/6	7E7	7/6	DAF96	7/6	EF91	3/6	PCF86	8/3	UC92	6/9
6BW6	7/6	7S7	14/6	DF96	7/6	EF183	8/-	PCL82	7/9	UC055	7/8
6BW7	5/-	7Y4	7/-	DK92	3/6	EF184	8/-	PCL83	9/6	UCF80	8/6
6C4	3/-	10C1	11/-	DL96	7/6	EL32	12/6	PCL84	9/6	UCJ22	8/6
6C5	5/6	10C2	12/6	DL92	6/6	EL33	12/6	PCL85	9/6	UCJ43	8/6
6C6	4/-	10F1	7/6	DL94	6/6	EL34	11/6	PCL86	9/6	UCJ81	7/6
6C9	11/-	10LD11	14/6	DL96	7/6	EL35	8/-	PL33	8/6	UCL82	8/-
6CD6G	17/-	10P13	9/6	EABC80	6/9	EL38	15/-	PL36	11/-	UCJ88	10/6
6D8	4/-	10P14	9/6	EAF42	8/-	EL41	9/9	PL35	9/6	UF41	9/6
6F1	6/6	12AT7	4/9	EB41	4/6	EL42	3/9	PL31	7/9	UF42	6/9
6F6G	5/-	12AU7	5/6	EB92	2/9	EL44	6/6	PL82	5/9	UF85	7/8
6F14	4/6	12AX7	6/-	EBC33	7/6	EMS0	7/-	PL83	6/-	UF89	6/9
6F18	7/6	12J7GT	9/-	EBC41	9/6	EM81	7/6	PL84	7/-	UL41	10/-
6F15	9/6	12K7GT	5/-	EBC91	6/9	EM84	7/9	PY31	7/8	UL44	14/6
6F28	3/-	12K8GT	9/6	EBF80	7/9	EY51	7/8	PY32	9/6	UL46	10/6
6F5G	4/-	12Q7GT	6/6	EBF89	7/-	EY88	7/6	PY33	7/6	UL84	6/6
6T5GT	6/6	14S7	14/6	EEL21	11/-	EY88	8/6	PY80	5/9	UM80	9/6
6T6	3/8	19AQ5	5/6	ECC40	9/6	EZ40	7/6	PY81	5/9	UY21	8/9
6T7G	5/6	20D1	8/9	ECC81	4/9	EZ41	3/6	PY82	5/6	UY41	7/-
6T7GT	9/6	20F2	9/6	ECC82	5/6	EZ80	5/6	PY83	5/9	UY85	5/6
6K7G	2/8	29L1	16/-	ECC83	6/6	EZ81	6/-	PY88	8/6	VR105	5/6
6K7GT	5/9	20P1	9/6	ECC84	7/-	FC4	3/-	PY800	7/-	VR150	5/-
6K9G	5/9	20P8	9/6	ECC85	5/9	GZ32	9/6	PZ30	9/6	X66	7/9

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone Linear Rogers, Truwoz, Ferrograph, Wharfedale, etc.


Post: 1 lb. 1/5, 1 1/2 lb. 2/6, 2 lb. 2/9, 4 lb. 3/3, 6 lb. 4/-, 14 lb. 5/6,

All Mail Orders to Brighton please

**LONDON** 10 Tottenham Court Road, W.1.  
Tel. MUSEUM 2639  
**BRIGHTON** Park Crescent Place  
Tel. 680722  
**PORTSMOUTH** 350-352 Fratton Road  
Tel. 22034  
**SOUTHAMPTON** 72 East Street  
Tel. 25351  
**WORTHING** 132 Montague Street  
Tel. 2535

# TECHNICAL TRADING

# THE *Adamin* DE-SOLDERING TOOL

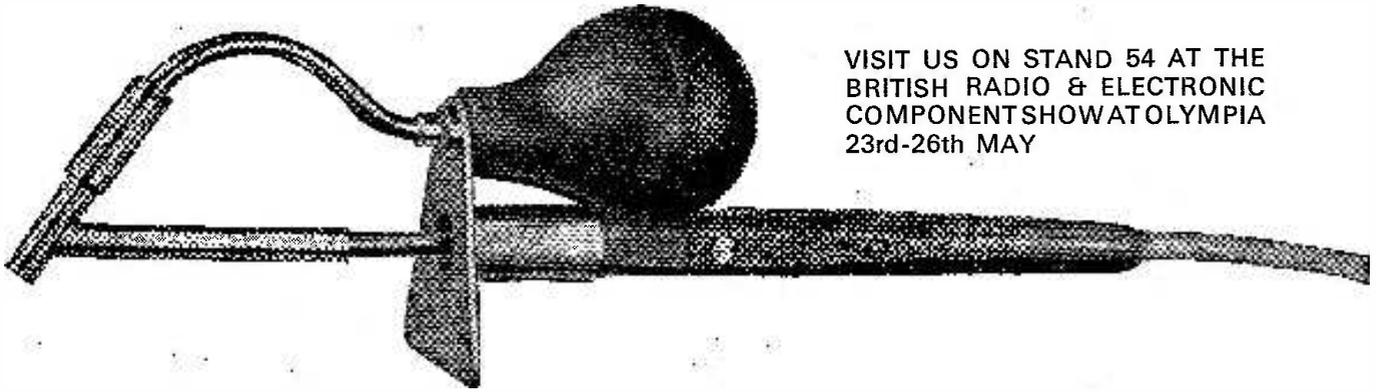

VISIT US ON STAND 54 AT THE  
BRITISH RADIO & ELECTRONIC  
COMPONENT SHOW AT OLYMPIA  
23rd-26th MAY

- Self-contained—does NOT require the use of air-lines or pumps
- Simple, light and inexpensive
- PERMABIT nozzle will not wear or become eroded by the solder
- Standard nozzle,  $\frac{5}{64}$  in. bore. Alternative,  $\frac{3}{64}$  in. bore
- Mains or low voltages

Please ask for free catalogue S.P.11

**LIGHT SOLDERING DEVELOPMENTS LTD.** 28 Sydenham Road, Croydon, CR9 2LL

Tel: CRO 8589, 4559

## OLRUS ELECTRONICS LTD.

PADDINGTON 1515

9 NORFOLK PLACE (off Praed St.) LONDON, W.2

### SCR-THYRISTORS

CRS105 1A 50PIV 7/6; CRS110 1A 100PIV 7/6; CRS120 1A 200PIV 12/6; CRS130 1A 300PIV 15/-; CRS135 1A 350PIV 16/-; CRS140 1A 400PIV 17/6; Unijunction 15/-; CRS305 3A 50PIV 8/6; CRS310 3A 100PIV 10/-; CRS320 3A 200PIV 13/6; CRS330 3A 300PIV 17/6; CRS350 3A 350PIV 18/6; CRS340 3A 400PIV 20/-; CR74 7A 400PIV 25/-.

### Field Effect Transistor

2N3819 18/-.

Moulded reed switch 14/-.  
Moulded magnet 5/-.  
Miniature Neon Lamp 1/3.  
Mains Panel Neon 3/-.

### CONTIL CASES

#### 21 SWG Steel

Smart electric blue finish with white panel—outside dimensions.

755	45/6	16127	98/6
867	47/6	161275	139/6
975	47/6	191010	133/-
1277	53/-	191010D	137/-

**DO IT YOURSELF**  
**SECTIONAL CASE**  
**AND CHASSIS**  
**S.A.E. FOR LEAFLET**

### TRANSFORMERS

230v Prim. 6-10-15-18-30v 2A 32/-  
230v Prim. 6-10-18v 1A 22/- + P.P. 5/-.

### EXPLORER KIT

AM/FM VHF RECEIVER  
Punched case and panel—2ADT 140+20C71 transistors—2 holders. £2.19.6 P.P. inc.

### SINCLAIR

Z12 Int. 12W Ampl. and Preamp Built 89/6  
PZ3 Trans. Mains Power Unit Built 79/6

Micromatic Built 79/6.  
Micro FM Kit 59/6.  
Micro FM Kit 25.19.6.  
Stereo 25 Preamp. and Control Unit Built 20.19.6 P.P. inc.

## TRANSISTORS - DIODES - ZENER - VALVES


FULLY GUARANTEED-FACTORY NEW. S.A.E. FOR FULL LIST. P.P. 2/- in £ 1/- min.

2N697	12/6	ASY26	6/6	NKT228	6/-	OAZ212	6/6	OCI70	5/-	PC88	11/-
2N1304	6/-	ASY28	6/6	NKT251	5/-	OAZ213	6/6	OCI71	6/-	PC97	7/6
2N2926	5/6	ASZ20	7/6	NKT255	6/6	OAZ222	9/6	OC200	7/6	PCC84	6/-
2N3819	15/-	ASZ21	12/6	NKT265	9/6	OAZ224	10/-	OC201	10/-	PCC89	11/-
2S002	10/6	ASZ23	30/-	NKT271	5/-	OAZ225	10/-	OC202	13/-	PCC189	11/-
2S003	9/6	BC107	7/6	NKT272	5/-	OAZ242	4/6	OC203	10/6	PCF80	7/-
2S004	9/6	BC108	5/-	NKT273	4/-	OAZ245	4/6	OC204	15/-	PCF86	8/6
2S012	20/-	BC109	7/6	NKT274	5/-	OAZ246	4/6	OC205	15/-	PCL82	7/6
2S012A	25/-	BCY31	13/6	NKT275	5/-	OAZ247	4/6	OC206	22/6	PCL83	8/6
2S013	20/-	BFY17	9/6	NKT277	5/-	OAZ290	9/6	ORP71	15/-	PCL84	7/6
2S013A	25/-	BFY51	8/6	NKT278	5/-	OAZ291	9/6	ORP12	3/6	PCL85	9/-
2S017	15/-	BFY53	7/6	NKT279A	4/-	OAZ292	9/6	DAF91	4/6	PCL86	8/6
2S018	17/6	BPY10	22/6	NKT304	8/-	OC16	20/6	DAF96	6/6	PL36	9/-
2S103	20/-	BSY27	9/6	NKT352	8/-	OC19	7/6	DF91	3/-	PL81	7/-
2S301	12/6	BSY51	7/6	NKT403	12/6	OC20	15/-	DF96	7/-	PL82	6/6
2S320	9/6	BSY53	7/6	NKT404	12/6	OC22	10/-	DK91	5/6	PL83	6/6
2S322	7/6	BSY95A	5/6	NKT453	12/6	OC23	12/6	DK92	3/-	PL84	6/6
2S323	10/6	BY100	4/6	NKT452	12/6	OC24	15/-	DK96	7/-	PL500	13/6
2S324	12/6	GBT7	5/-	NKT675	6/-	OC25	9/6	DL92	5/-	PY32	8/6
2S512	19/6	GBT8	8/-	NKT676	5/-	OC26	7/6	DL94	5/9	PY81	6/-
2S702	15/-	GBT16	7/6	NKT677	5/-	OC28	12/6	DL96	7/-	PY82	5/6
AC107	10/-	GBT20	10/-	NKT678	6/-	OC29	15/-	DY86	6/4	PY83	6/-
AC126	6/6	GBT88	5/-	NKT713	7/6	OC35	12/6	EBC41	7/6	PY88	7/3
AC127	7/6	GBT102	6/-	NKT773	6/-	OC36	12/6	EBC42	6/3	UBC41	7/6
AC127Z	9/6	GBT103	4/6	NKT777	8/-	OC41	6/-	EBC90	4/3	UBC81	7/6
AC128	6/6	GBT105	8/6	NKT0013	12/6	OC42	5/-	EBF89	6/9	UC085	6/6
AC176	7/6	GBT106	10/-	OA5	4/-	OC43	9/-	ECC81	4/-	UCH42	8/6
ACY17	8/6	GBT113	5/-	OA7	4/-	OC44	4/6	ECC82	5/-	UCH81	6/3
ACY18	5/6	GBT114	4/-	OA10	3/-	OC44M	5/6	ECC83	5/6	UCH82	7/3
ACY19	6/6	GBT115	9/-	OA47	3/-	OC45	3/6	ECC85	5/-	UL41	8/6
ACY20	5/-	GBT116	15/-	OA70	2/-	OC45M	4/-	ECC87	7/-	UL84	6/3
ACY21	6/-	GBT1571	5/-	OA73	2/6	OC46	5/3	ECC35	10/9	UY35	5/6
ACY22	3/6	GBT872	6/-	OA79	2/6	OC70	4/-	ECH42	9/-	U35	9/6
ADY28	4/6	GBT874	5/-	OA81	2/6	OC72	5/6	ECH81	5/2	U36	8/6
AD140	16/-	GBT875	6/-	OA85	2/6	OC73	7/6	ECH84	8/10	5Y4GB	6/6
AD149	16/-	GBT880	9/-	OA86	4/-	OC73	7/6	ECL60	7/-	5Y3GT	5/6
AD161	11/-	GBT882	9/-	OA90	3/6	OC75	6/-	ECL82	6/3	5Z4GT	3/-
AD182	11/-	GBT883	5/-	OA91	2/6	OC76	5/-	ECL86	9/-	6P23	10/-
AD1740	15/-	GBT885	5/-	OA95	3/6	OC77	3/-	EF80	5/-	6L6GC	7/6
AF102	13/-	NKT128	6/-	OA200	3/3	OC78	5/-	EF86	6/3	6SN7GTB	7/6
AF114	6/6	NKT142	8/-	OA202	4/3	OC78D	5/-	EF183	6/4	6V8GT	6/6
AF115	6/-	NKT211	6/-	OA210	7/6	OC81	5/-	EF184	6/4	6X5GT	6/-
AF116	6/6	NKT212	5/-	OA2111	9/6	OC81D	5/-	EL34	9/6	25L6GT	6/6
AF117	5/-	NKT213	6/-	OA2200	11/-	OC81M	5/-	EL41	8/6	30C15	10/-
AF118	10/-	NKT214	4/-	OA2201	10/-	OC81DM	5/-	EL44	4/9	30FL1	10/6
AF124	7/6	NKT216	7/6	OAZ202	8/6	OC81Z	9/-	EM84	7/9	30PL14	11/-
AF125	6/6	NKT217	8/-	OAZ203	8/6	OC82	6/-	EY51	7/-	30L15	11/-
AF126	6/-	NKT218	6/-	OAZ204	8/6	OC82D	5/-	EY86	6/6	30P12	9/-
AF127	6/-	NKT221	5/-	OAZ205	8/6	OC83	5/-	EZ40	7/6	30P19	13/-
AF139	12/6	NKT222	4/6	OAZ206	8/6	OC84	6/-	EZ86	5/6	30PL1	10/6
AF178	17/6	NKT223	6/-	OAZ207	9/6	OC122	15/-	EZ81	5/-	30PL13	12/-
AF186	12/6	NKT224	4/6	OAZ208	6/6	OC139	7/6	EZ90	4/6	35L6GT	6/-
AFY19	23/6	NKT225	3/6	OAZ209	6/6	OC140	9/6	GZ32	10/-	35Z6GT	5/6
AFZ11	17/-	NKT226	10/-	OAZ210	6/6	OC141	12/6	GZ34	10/-	50L6GT	6/6
AFZ12	12/6	NKT227	5/6	OAZ211	6/6	OC169	5/-	PC86	11/-		

# LASKY'S RADIO

# For the Finest Value and Service to HOME CONSTRUCTORS & ELECTRONICS ENTHUSIASTS

## TRANSISTOR PORTABLES

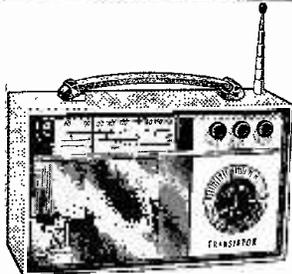

### THE SKYROVER De Luxe

7 transistor plus 2 diode superhet, 6 waveband portable receiver covering the full Medium Waveband and Short Waveband 31-94M and also 4 separate switched bandspread ranges, 13M., 16M., 19M and 25M., with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions. Superhet, 470 Kc/s. All Mullard Transistors and Diodes. Uses 4 U2 Batteries. 5in. Ceramic Magnet P.M. Speaker. 500 MW Output. Telescopic and Ferrite Rod Aerial. Tone Circuit with separate Tone Control. Volume Control. Tuning Control and Waveband Selector. In wood cabinet, size 11½ x 6½ x 3in. covered with washable material, plastic trim and carrying handle. Car aerial socket fitted.

Can now be built for **£8.19.6** Post 5/- extra

H.P. Terms: 60/- deposit and 11 monthly payments of 12/9. Total H.P.P. **£10.0.3.**

Four U2 batteries 3/4 extra.

### LONG WAVEBAND COVER FOR THE SKYROVER

A simple additional circuit provides coverage of the 1100/1950M. band (including 1500M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data.

Only 10/- extra Post Free.

This conversion is suitable for receivers that have already been constructed.

Data 2/6 extra: refunded if you purchase the parcel.

All components available separately.

## SINCLAIR SUPER MINIATURE KITS

Write for details of Package Deals

THE MICRO-6 miniature radio only 1½ x 1½ x 1½in.	£2 19 6
THE MICRO-FM (tuner/receiver)	£5 19 6
THE MICROMATIC World's smallest radio kit 1½ x 1½ x 1½	£2 19 6
THE MICROMATIC Ready built, tested and guaranteed	£3 19 6
THE Z-12 12 watt amp. and pre-amp., fully built	£4 9 6
PZ-3 power pack for Z-12	£3 19 6
STEREO 25 Pre-amplifier control unit fully built	£9 19 6

## SPECIAL INTEREST ITEMS

### NEW! LASKY'S CLEAR PLASTIC PANEL METERS


Precision made in Japan by HIOKI. Each meter boxed and fully guaranteed with all fixing nuts and washers. Sizes are of front panel. Add 1/6 Post on each.

Type KR-52 3 x 2½in. (illustrated)

1 mA DC	32/6	300 V DC	32/6
5 mA DC	32/6	500 µA	37/6
1 mA S Meter.....39/6			

Type MK-38A 2in. square		Type KR-65 3½ x 3in.	
1 mA DC	22/6	1 mA DC	36/-
5 mA DC	22/6	5 mA DC	35/-
300 V DC	22/6	300 V DC	35/-
55 µA	27/6	500 µA	42/6
1 mA S Meter	29/6	1 mA S Meter	39/6

Type MK-45A 1½in. square		Type MK-65A 3in. square	
1 mA DC	25/-	1 mA DC	36/-
5 mA DC	25/-	5 mA DC	35/-
300 V DC	25/-	300 V DC	35/-
500 µA	25/-	500 µA	39/6
1 mA S Meter	35/-	1 mA S Meter	37/6

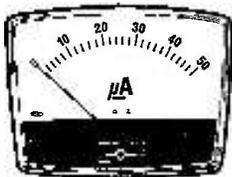

### NOW AVAILABLE! — JOYSTICK AERIALS

Revolutionary variable frequency antenna for transmission and reception. With a variable matching unit these antennae perform as a high 'Q' device at any selected Medium or Short waveband. Send for S.A.E. for descriptive leaflet.

VFA Standard	£4 15 0	Matching units	
VFA DeLuxe	£5 19 6	A.T.V. 3A	£3 12 6
		A.T.V. 4	£4 4 0
		A.T.V. 4/RF	£6 6 0

### INTERNATIONAL TAPE

Famous American Brand—Fully Guaranteed

3in. Message tape, 150ft.	2 6	5½in. Long play, 1200ft. Acetate	12 6
3in. Message tape, 225ft.	3 9	5½in. Standard play, 850ft. PVC	11 6
3in. Message tape, 300ft.	7 6	5½in. Long play, 1200ft. Mylar	15 0
3½in. Triple play, 600ft. Mylar	10 0	5½in. Triple play, 2400ft. Mylar	45 0
4in. Triple play, 900ft. Mylar	17 6	7in. Standard play, 1200ft. Acet.	12 6
5in. Double play, 1200ft. Mylar	15 0	7in. Standard play, 1200ft. Mylar	12 6
5in. Long play, 900ft. Acetate	10 0	7in. Long play, 1800ft. Mylar	19 6
5in. Standard play, 600ft. PVC	8 6	7in. Double play, 2400ft. Mylar	26 0
5in. Triple play, 1800ft. Mylar	35 0	7in. Long play, 1800ft. Acetate	15 0
5½in. Double play, 1800ft. Mylar	22 6	7in. Triple play, 3600ft. Mylar	50 0

P. & P. 1/- extra per reel. 4 reels and over Post Free

## CONSTRUCTORS BARGAINS

### SPECIAL PURCHASE—UHF/VHF TV TUNERS

Well known British makers surplus stocks. Now available for the first time to the Home Constructor. Add 2/6 Post and Packing on each.

#### TRANSISTORISED UHF MODEL

Metal case size 3½ (plus spindle) x 2½ x 1½in. Fully tunable with slow motion drive. Complete with two AF186 transistors. LASKY'S PRICE 25/6

#### VALVE UHF MODEL (illustrated)


In metal case size 4 x 6 x 1½in. Fully tunable—complete with PC86 and PC88 valves. LASKY'S PRICE 29/6 Without valves 12/6

#### TRANSISTORISED VHF TUNER

Sub-Miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case size 3 x 1½ x 2½in. LASKY'S PRICE 37/6
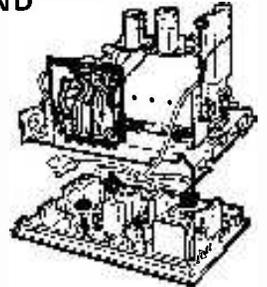
### BARGAIN—TV UHF TUNER AND IF AMPLIFIER PANEL

Model No. 89384 made by famous manufacturer as standard conversion unit to 625 line reception (BBC 2) for 19" and 23" 405 line (convertible model) Cosor, Philips, Scott and Stella television receivers. The units are boxed, brand new and fully guaranteed, complete with detailed conversion and operating instructions. To effect conversion on the sets mentioned above you need only a pair of pliers and a screwdriver! The units are fitted with 7 Mullard valves—PCF80 x 2, EF184, EF185, ECC82, PC86, PC88. Size of units: tuner 7½ x 4 x 8in., IF panel on 9 x 4½in. printed circuit board x 2½in. deep. Complete with all leads, screws, washers etc. Original Price £10.10.0.



LASKY'S PRICE 49/6 Post 5/-

### TREMENDOUS VALUE IF BOUGHT ONLY FOR THE VALVES AND COMPONENTS

## NEW—LASKY'S MINIATURE TRANSISTOR AMPLIFIER MODULES

Incorporating the very latest circuitry to provide high sensitivity and good quality in conjunction with extreme small size and compactness. High quality Newmarket transistors used throughout. All designed to operate on 9v. miniature battery.

Add 1/- on each for Post and Packing.


**TYPE LRPC 1.** 3 transistor. Input sens. 50mV. output 150mW output imp 40Ω, size 2 x 1 x 2½in. PRICE 27/6

**TYPE LRPC 2.** 5 transistor. Input sens. 1mV. output 330mW, output imp. 15Ω, size 2½ x 1½ x 2½in. PRICE 22/6

**TYPE LRPC 4.** 5 transistor, Input sens. 150mV, output 330mW, output imp. 15Ω, size 2½ x 1½ x 2½in. PRICE 22/6

**TYPE LRPC 5.** 6 transistor. Input sens. 8mV, output 3W, output imp. 3Ω, size 5½ x 1½ x 1in. PRICE 59/6

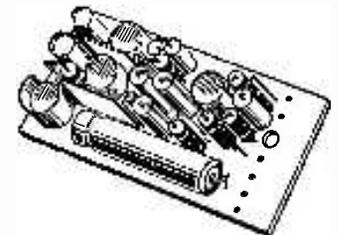**TYPE LRPC 6.** Tape record/playback amp. (for use with self oscillating erase head). Output 750mW, output imp. 8Ω. Size 4½ x 2 x 1in. PRICE 39/6



### VEROBOARD

High grade laminated board with copper strips bonded to it and pierced with holes.

<b>Boards</b>		<b>Accessories</b>	
42/1503 2½ x 5 in.	3/11	Terminal pins—pkt. of 50	3/-
43/1504 2½ x 3½ in.	3/3	Spot face cutter tool	7/8
45/1507 3½ x 5 in.	5/6	Pin inserting tool	9/6
46/1508 3½ x 3½ in.	3/11	Post 6d. per item extra.	
44/1505 3½ x 17 in.	15/6	Orders of 10/- and over post free.	

### GORLER UT 340 FM/VHF TUNING HEART

Permeability tuned—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case, size 3 x 2½ x 1½in. Circuit supplied.

LASKY'S PRICE 15/11 Post 2/- ECC85 valve 9/- extra.

### TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET S1, GET S5, GET S6 2/6; 873A, 874P 3/6; OC45, OC71, OC81D 4/6; OC44, OC70, OC76, OC81 5/6; (match pair 10/6); AF117, OC200 6/6; OC42, OC43, OC73, OC82D 7/6; OC201, OC204 15/-; OC205, PC206 19/6; OC28 24/6; OC75 8/-.

### TRANSFILTERS

by BRUSH CRYSTAL CO., Available from stock.

TO—01B 465 kc/s. ± 2 kc/s.	TO—02D 470 kc/s. ± 1 kc/s.	9/6 each Post 6d.
TO—01D 470 kc/s. ± 2 kc/s.	TF—01B 465 kc/s. ± 2 kc/s.	
TO—02B 465 kc/s. ± 1 kc/s.	TF—01D 470 kc/s. ± 2 kc/s.	

NOW AVAILABLE—OUR NEW BARGAIN BULLETIN. 24 foolscap pages packed with hundreds of bargains for the "ham" and service man—exclusive to Lasky's—plus full list of regular stock items. PRICE 6d. POST FREE.


207 EDGWARE ROAD, LONDON, W.2 Tel. PAD 3271  
118 EDGWARE ROAD, LONDON, W.2 Tel. PAD 9789  
33 TOTTENHAM CT. RD., LONDON, W.1 Tel. MUS 2605  
All the above branches open all day Saturday. Early closing Thursday.

42 TOTTENHAM CT. RD., LONDON, W.1 Tel. 01-580 2573  
152/3 FLEET STREET, LONDON, E.C.4 Tel. FLE 2833  
Both open all day Thursday. Early closing Saturday.

Mail Orders and correspondence to 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel.: STEPney Green 4821/2

## LASKY'S FOR SPEEDY MAIL ORDER SERVICE
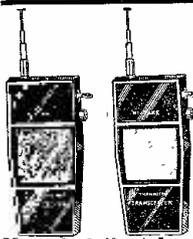
# FANTASTIC NEW 1967 BARGAINS FROM CONCORD



Frustrated Import Shipment  
OFFERED BELOW HALF PRICE TO CLEAR  
ALL TRANSISTOR 500 only  
PERSONAL TRANSCIEVER SETS

OUR PRICE **£6.19.6**

You've heard about them—You've read about them. NOW'S YOUR CHANCE TO OWN THEM. Highly sensitive two-way transistor transceiver sets have individual volume control and talk-listen switch. Telescopic aerial pulls in the voice from the other set over tremendous distances—no wires—a genuine transceiver as used by official bodies and forces. 500 sets only at **£6.19.6** plus 5/6 p. & p. (Batteries, leather cases, etc. 10/6 ex.). Money back if not delighted with the performance. These cannot be operated in U.K.

NO SOLDERING AMAZING CIGARETTE  
RADIO


ONLY **25/-**

Yes a perfectly ordinary packet of cigarettes! But watch your friends astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 cigarettes yet cleverly conceals highly sensitive, fully transistorised circuit (including battery). Even a young boy can assemble it under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file Mr. D. B. of Huddersfield, writes: "... I have fitted the parts in it and it is working wonderfully..." ALL PARTS including Semi-Conductors, ABC Plans, etc. **ONLY 25/-** plus 2/6 post, etc. Parts available separately.



Make 5 different  
TRANSISTOR  
RADIOS for

**39/6** No Experience Necessary

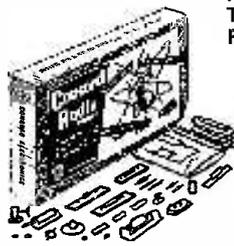


No soldering. Only 8 connections for first radio to work. Just look, you get Easy ABC Plans, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. **YES—EVERYTHING!** Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Complete course—originally **£6.** Now only **39/6** plus 4/6 Post etc.

NEW FULLY  
TRANSISTORISED  
PORTABLE RADIOS

with Full Variable waveband.  
NOW A FRACTION OF THE  
NORMAL PRICE

ONLY **34/6**

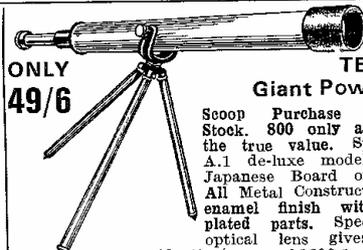WHY PAY MORE? All the latest refinements are packed into this new MULTI-STATION ALL Transistor radio—the internal aerial picks up even the remote stations and the powerful built-in speaker gives room filling volume. Individual tuning, confidence—packed (Personal earpiece and battery 4/6). Send **39/6** plus 4/6 p. & p.



ONLY **49/6**

New Lunar  
TELESCOPE  
Giant Power 40 x 40

Scoop Purchase of Limited Stock. 800 only at fraction of the true value. Special Grade A.1 de-luxe model—passed by Japanese Board of Inspection. All Metal Construction in white enamel finish with chromium plated parts. Special polished optical lens gives astounding magnification power of 1600-1 areas. Single draw focussing tube enables you to study the MOON, PLANETS & STARS. Focus on subjects miles away or just across the road. Brand new complete with collapsible tripod at unbelievable price of **only 49/6** plus 5/6 post and **SAFE PACKING**



Don't be put off by low price—we bought bankrupt stock.  
NAVAL (Pattern) BINOCULARS

40mm. O.G. lens

**45/-**



NO MORE TO PAY  
Telescopic draw tubes with smooth action centre focussing and inter-pupillary pivot. Takes you into space or just across the road. Save £ £ £—**ONLY 45/-**, incl. real

including real pigskin case. Superb area magnification of 15 times. Brand new. Grade A.2 de luxe model by leading optical manufacturer. Full size, metal construction, lightweight, precision ground and polished optical lenses for wide angle, needle sharp definition.


Profit from the credit squeeze  
Importers stock bought at miles  
below actual value

WIDE RANGE HIGH POWER  
MICROSCOPE only **37/6**


definition. 3 optically polished lenses on revolving turret, giving 100x, 200x and 300x magnification powers. Adjustable mirror light, reflector and tilting joint. Ideal for students, hobbyists, nature study, etc. Should last a lifetime—Passed by Japanese Board of Inspection.

not a penny more to pay. Grade A.1 De Luxe model, all metal construction in black crackle with plated parts. Accurate rack and pinion focussing gives crystal clear definition. Brand new in box, complete with set of slides **ONLY 37/6** + 3/6p & p money back guar.

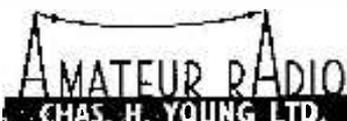CONCORD ELECTRONICS LTD. (Dept. P.W.37), 77 New Bond St., London, W.1  
Mail Orders only



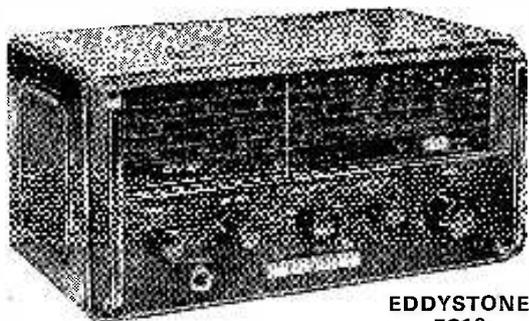The Sensational  
ALL-TRANSISTOR  
Communications Receiver



EDDYSTONE  
EC10

for use in the home, caravan, car or boat,  
H.P. facilities. **Only £48** Part exchanges

Write for brochure

170-172 CORPORATION STREET  
BIRMINGHAM 4  
Telephone: 021-236-1635

## TRANSISTORS

OC23	10/-	OC82	3/6
OC25	9/6	OC82D	3/6
OC26	9/6	OC84	5/6
OC28	11/-	OC169	4/6
OC35	12/6	OC170	4/6
OC36	12/6	OC171	6/-
OC38	12/6	OC200	7/6
OC44	3/6	AC126	3/6
OC45	3/6	AC127	3/6
OC46	4/-	AC128	3/6
OC70	3/6	AD170	15/-
OC71	3/6	AF114	5/3
OC72	3/6	AF115	5/-
OC75	3/6	AF116	5/-
OC76	4/-	AF117	4/6
OC78	4/-	AF118	4/6
OC78D	4/-	AF119	4/6
OC81	3/6	OA81	2/6
OC81D	3/6		

C.W.O., P.P. 2/- in £. Min. 1/-.

## RECORDING TAPES

3in. Standard	..	150ft.	3/11
3in. Standard	..	225ft.	4/11
3½in. Triple Play	..	600ft.	12/6
5in. Standard	..	600ft.	10/-
5in. Long Play	..	900ft.	14/6
5in. Double Play	..	1200ft.	15/6
5½in. Long Play	..	1200ft.	16/-
5½in. Double Play	..	1800ft.	22/6
7in. Standard	..	1200ft.	17/6
7in. Long Play	..	1800ft.	22/6
7in. Double Play	..	2400ft.	25/-

Four of the tapes or more are post free otherwise postage 1/6.

## SPOOLS

3in. spool	1/-	5½in. spool	2/-
3½in. spool	2/3	4in. spool	2/3
5in. spool	2/6	7in. spool	1/6

Postage and packing 6d. All items listed are cash with order.

## INTERCOM/BABY ALARM

Modernise your home or business with this new all transistor Intercom consisting of one master and one sub. Complete with all leads, battery and full instructions. Usually 5 gns.  
Our Price **49/6**. P.P. 2/-.

## TEST METERS

Pocket Test Meter D14  
Specifications: DC voltage 0-15 -150-1,000 volts (1,000 R/V). AC voltage 0-15-150-1,000 volts (1,000 R/V) DC current 0-150 milliamperes. Resistance 0-100 KΩ. Size: 57 x 93 x 30mm. Net weight 108 g. Only **39/-** Carr. 2/-.

Send 3d. stamp for catalogue containing  
Hi-Fi, Transistor Radios, Microphones, Autochangers, etc.  
to: MOORDOWN RADIO LTD., 941 WIMBOURNE RD.,  
MOORDOWN, BOURNEMOUTH. Tel 59866

# Build Your Own Heathkit Electronics

A kit for every interest—Home Workshop—Hi-Fi—Radio—Test—'Amateur'  
 Treat yourself to superb LW, MW entertainment with the  
**High-Performance Car Radio Kit. CR-1.**




Complete your motoring pleasure with this small, compact, high-performance car radio. It can be fitted to any make of car having 12 volt positive or negative earth system. Tastefully styled in neutral grey with matching black knobs and chrome trim to harmonise with any car colour scheme.

Features include:— Six transistor, 2-diode circuit. Completely pre-assembled and aligned tuning unit. High sensitivity, combined with wide range automatic gain control (AGC), minimises fading under weak reception conditions. Easy-tune dial. Push button long, medium, and tone selection.

The car radio is available for your convenience, in two separate units: RF Amplifier Kit CR-1T, £1.13.6 incl. P.T. IF/AF Amplifier Kit CR-1A, £11.3.6.

**TOTAL PRICE KIT (excluding loudspeaker) £12.17.0 incl. P.T.**  
 8 x 5in. Loudspeaker, Pt. No. 401-505, £1.16.1 incl. P.T.
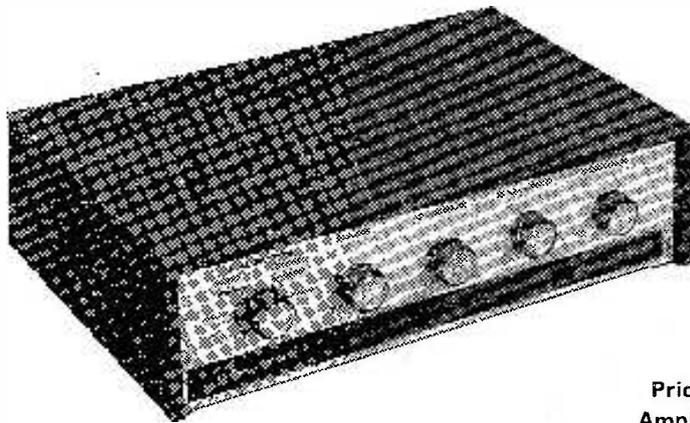
## The Transistor Amplifier you have been looking for!



### 3 + 3W Stereo Amplifier Kit, TS-23

Breaks the price barrier in transistor amplifier cost

Incorporates all the essential features for good quality reproduction from gramophone records, radio and other sources. Its many features include: 3 watts rms (15Ω) each channel. Good frequency response for outstanding fidelity. Compact slim-line styling. Ganged BASS, TREBLE and VOLUME controls. Six position SELECTOR switch for programme sources. Attractive perspex front panel, two-tone. 16 transistor, 4 diode circuit. Handsome fully finished walnut veneered cabinet. Outputs for 8 or 15 ohm loudspeakers. Printed circuit boards for free-standing or cabinet mounting. Size 3 $\frac{3}{8}$  x 13 x 8in. deep.

Prices Amplifier Kit **£17.15.0** Walnut veneered Cabinet  
 Amplifier kit & Cabinet **£18.19.0** separate **£2.0.0**


Hi-Fi performance from a "Mini" speaker kit with the 'AVON' BOOKSHELF SPEAKER SYSTEM



The challenge to our acoustic engineers was to design a speaker occupying the minimum space consistent with first class reproduction. The result of our efforts was the AVON, a compact unit of exceptional quality. Features two special speakers 6 $\frac{1}{2}$ in. BASS, 3 $\frac{3}{8}$ in. HF unit and cross over network. Good frequency response. Beautiful fully finished walnut veneered cabinet. Size only 7 $\frac{3}{4}$  x 13 $\frac{1}{4}$  x 8 $\frac{3}{8}$ in. deep. Supplied in two units. Can be built for a total price  
**KIT £13.16.0** incl. P.T.
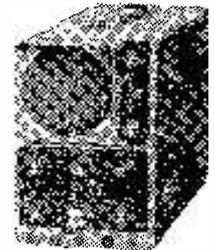
### A 3" Service Oscilloscope kit with outstanding features. Model OS-2

The attractively styled OS-2 is a compact, lightweight, portable and surprisingly versatile oscilloscope that fulfils many of the general requirements in Laboratories, Service Departments and Educational Training. It is ideal for use in production line testing where otherwise expensive equipment would be tied up on ordinary routine tests. The bandwidth of the OS-2 is from 2 c/s-3 Mc/s $\pm$ 3dB, this 'scope can therefore be used in applications ranging through audio, ultrasonic and radio frequencies. The time base operates from 20 c/s to 200 kc/s in four ranges and is self-synchronising.  
 Size 5 x 7 $\frac{3}{8}$  x 12in. deep. Weight 9 $\frac{3}{8}$  lb.



**KIT £23.18.0** Assembled **£31.18.0**  
 Optional extra. L/Cap Probe kit, PK-1. **KIT £3.12.6**

Many other models in wide range.  
 Prices quoted are Mail Order, retail prices in general 5% extra.  
 Full specification sheets of any model available upon request.

## FREE

BRITAIN'S LARGEST  
 ELECTRONIC KIT CATALOGUE  
 GET YOUR LATEST COPY NOW →

WHEN IN LONDON visit our  
**HEATHKIT CENTRE**  
 233 Tottenham Court Road, W1  
 Tel: MUSEum 01-636-7349  
 See a full range of British models and a selection of American Heathkit models.

## HEATHKIT

DAYSTROM LTD., Dept. PW-5  
 GLOUCESTER, ENGLAND

Please send me model(s) .....  
 for which I enclose £ ..... s ..... d post paid.  
 Please send me FREE British Heathkit Catalogue.

NAME .....  
 ADDRESS .....

**BRADFORD** Tel. 25349  
10 North Parade. (Half-day Wed.)  
**BRISTOL** 14 Lower Castle  
St. (Half-day Wed.) Tel. 22904  
**BIRMINGHAM** 30/31 Gt.  
Western Arcade, opp. Snow Hill  
Station. CENTral 1279. No half-day  
**DERBY** 26 Osmaston Rd.,  
The Spot (Half-day Wed.)  
Tel. 41361


**DARLINGTON** 13 Post  
House Wynd (Half-day Wed.)  
**EDINBURGH** 133 Leith  
Street (Half-day Wed.)  
Tel.: Waverley 5766  
**GLASGOW** 326 Argyle St.  
(No half-day) Tel.: CITY 4158  
403 Sauchiehall Street  
**HULL** 91 Paragon Street  
(Half-day Thursday) Tel.: 20505

**R.S.C.**  
HI-FI CENTRES LTD.

MAIL ORDERS TO: 102  
Henconner Lane, Bram-  
ley, Leeds 13. No C.O.D.  
under £1. Terms C.W.O.  
or C.O.D. Postage 4/6  
extra under £2. 5/9 extra  
under £5. Trade supplied.  
S.A.E. with enquiries

**LEICESTER** 32 High Street  
(Half-day Thurs.) Tel.: 56420  
**LEEDS** 5-7 County (Mecca)  
Arcade, Briggate (No half-day)  
Tel.: 28252  
**LIVERPOOL** 73 Dale St.  
(No half-day) Tel.: CENTral 3573  
**LONDON** 238 Edgware Road,  
W2 (Half-day Thurs.) Tel.: PAD  
1629. 96 High Holborn, WC1  
Tel.: HOL 9874 (Half-day Sat.)

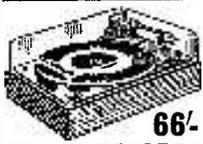**MANCHESTER** (No half-  
day) 60A-60B Oldham St.  
Tel.: CENTral 2778  
**MIDDLESBROUGH**  
106 Newport Road (Half-day  
Wednesday) Tel.: 47096  
**NEWCASTLE UPON TYNE**  
41 Blackett Street Opp Fenwicks  
Store (Half-day Wed.) Tel.: 21469  
**SHEFFIELD** 13 Exchange  
Street, Castle Market Bldgs.  
(Half-day Thursday) Tel.: 20716



**AUDIOTRINE PLINTHS**

for Record Playing units.  
Teak finish cut for Garrard  
1000, 2000, 3000, AT8 Mk 2,  
AT60, SP25 or Goldring  
GL68. Available with clear  
Perspex cover as illustrated  
£5.19.11. complete.

**66/- RECORD PLAYING UNITS**

Ready for plugging in to Amplifier or Tape Recorder.  
**RP2** Consisting of Garrard SP25 fitted Goldring  
CS9) high compliance ceramic Stereo/Mono  
ctgr with dmn'd stylus, above Only **19½ Gns.**  
plinth & cover. Normally £25. Carr. 15/-  
**RP3** As above but with Goldring Lenco GL68 Trans-  
cription unit and CS90 Cartridge. Normally  
over £33. Terms avail-  
able both units. Only **26½ Gns.**  
Carr. 15/-

**SPRING CLEARANCE SALE**

Send S.A.E. for list of brand new lines which  
must be cleared. Includes Record Playing  
Units, Amplifiers, Tape Decks, Cabinets etc.

**AUDIOTRINE HI-FI SPEAKER SYSTEMS**

Consisting of matched 12in. 12,000 line,  
15 ohm high quality speaker; cross-over  
unit and Tweeter. Smooth response  
and extended frequency range ensure  
surprisingly realistic reproduction.  
Standard 10 watt rating. Or **5 Gns.**  
Senior 20 watt inc. Fane  
122/10 speaker 7 Gns. Carr. 8/9. Carr. 6/9

please. HI-FI CATALOGUE NOW  
AVAILABLE price 3/3 post paid.  
Personal shoppers welcome. Open all day  
Sats. except High Holborn branch.

ALL LEADING MAKES OF HI-FI  
EQUIPMENT STOCKED Cash or Terms  
Full range Hi-Fi Furniture

**HI-FI LOUSPEAKER ENCLOSURES**

All types of pleasing modern design  
acoustically lined and ported and  
beautifully finished in light Teak or  
Walnut veneer. Credit terms available.  
**JES.** Size 16 x 11 x 8in. Gives  
pleasing results with 8in. Hi-  
Fi speaker. **£4.15.0**



**SES.** For optimum perform-  
ance with any Hi-Fi 8in.  
speaker. Size 22 x  
15 x 9in. Carr. 7/6 **£5.19.9**  
**SE10.** For 10in. Hi-Fi speaker  
with provision for tweeter.  
Size 24 x 15 x 9in. **£6.19.9**  
Carr. 10/-

**SE12.** For outstanding performance with  
any 12in. Hi-Fi speaker. Cut  
for tweeter. Size 24 x 20 x 10in. **8 Gns.**  
Carr. 10/-

NEW RANGE OF LINEAR  
HI-FI UNITS STOCKED

**HIGH FIDELITY LOUSPEAKER UNITS**

Cabinets of latest styling Satin Teak or Walnut,  
acoustically lined (and ported where appropriate).  
Credit Terms available on all units.

**MINI 8**

8 WATT rating. 3 or 15 ohm. Frequency  
response 50-13,000 c.p.s. Specially de-  
signed high flux 5in. speaker with low  
fundamental resonance. Handsome  
Teak veneered cabinet. **£6/19/11**  
9½ x 6½ x 7in. Carr. 7/6



**The DORSET**

Size 16 x 11 x 8in.  
Response 45-18,000 c.p.s. Rating 10  
watts. Fitted Audiotrine HF811D  
speaker. Impedance 3 or **£7/15/0**  
15 ohms. Carr. 7/6

**The DORCHESTER**

Size 24 x 15 x 10in. Fitted  
Audiotrine HF101D Speaker. Rating 12 watts.  
Impedance 3 or 15 ohms. Frequency  
Response 30-20,000 c.p.s. Carr. 15/- **12½ Gns.**

**The GLOUCESTER**

Size 24 x 20 x 8in.  
12in. High flux  
12,000 line speaker.  
Cross-over unit  
and Tweeter.  
Rating 10 watts.  
Smooth response  
40-20,000 c.p.s. Im-  
pedance 15 ohms. Carr. 15/- **12 Gns.**



**The BRONTE**

Size 22 x 15 x 9in.  
Fitted Wharfedale  
Super 8 R5SD or  
Audiotrine HF  
815D Speaker, with  
Roll surround and  
dual cone. Rating  
6/10 watts. Impe-  
dance 3 or 15 ohms.  
Carr. 15/- **12½ Gns.**

Tweeters R.A. 3 ohm or 15 ohm 25/9

**15 watt HI-FI TRANSISTORISED  
AMPLIFIER TYPE A15**

with integral pre-  
amp tone control  
stages. Output for 3,  
7.5 and 15 ohm spkrs.  
Kit includes Printed  
Circuit and all parts  
type semi-conductors.  
Heat sink and full wir-  
ing instructions or with printed circuit  
fully wired and tested 21/- extra. Frequency  
Response: ±1dB 20-20,000 c.p.s. Harmonic  
Distortion: 0.1%. Hum and Noise:  
-30dB. Sensitivity: 2mV. Bass Control:  
-9dB to -14dB at 40 c.p.s. Treble Con-  
trol: +8dB to -13dB at 10 Kc/s. Will  
operate from batteries giving 24v. Suit-  
able Power Pack Kit 47/9 or ready built 69/9




**R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER**

A complete set of parts for the construction of a unit giving 5 watts high quality  
output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable  
all crystal or ceramic stereo heads. Ganged Bass and Treble Controls. Provision  
is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83,  
ECC83, EL34, EL34, E791. Outputs for 2-3 ohm speakers. Point to point wiring  
diagrams and instructions supplied. Send S.A.E. for leaflet.  
Or supplied factory assembled with 12 months' guarantee for 11 Gns. Carr. 11/6 **£8.15.0**  
Terms: Dep. 36/- and 9 monthly payments 25/5 (Total £13.4.9).

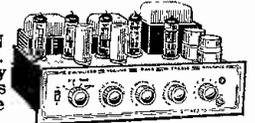**R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER**

PROVIDING 10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON  
EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE.  
Employing valves ECC83, ECC83, ECL86, ECL86, ECL86, E281. Frequency  
Response: +2dB 30-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 5 millivolts  
maximum. Harmonic Distortion: (each channel): 0.2%. ★Four-position tone  
compensation and Input Selector Switch. ★Stereo/Mono switch.  
★Will amplify direct from Tape Heads. ★Neon panel indicator. ★Handsome Perspex Frontplate.  
★Separate Bass "Lift" and "Cut" and treble "Lift" and "Cut" controls. Output transformers are high-  
quality sectionally wound to required specification. Output matching for 3 and 15 ohm spkrs. on 14 Gns.  
each channel. Complete set of parts, point-to-point wiring diagrams and instructions. Carr. 12/6  
Or factory assembled, tested and supplied with our usual 12 months guarantee.  
Or Deposit £3 and 9 monthly payments 43/2 (Total £22.4.6). Send S.A.E. for leaflet. Carr. 12/6 **19 Gns.**



**R.S.C. TFM1 TRANSISTORISED VHF/FM RADIO TUNER**

Total cost of parts  
with detailed wiring  
diagrams and instruc-  
tions. Carr. 10/- **12½ Gns.**  
Or factory built  
15 Gns. Or in Teak  
finished cabinet as  
illustrated 19 Gns.  
Terms: Deposit £5  
and 9 monthly pay-  
ments 39/-.  
Total £22.11.0.



★ High-sensitivity ★ 200-250v. A.C. Mains  
operation. ★ Sharp A.M. Rejection.  
★ Drift-free reception. ★ Output ample  
for any amplifier (approx. 500 m.v.).  
★ Simple alignment instructions. ★ Output  
available for feeding tuning meter.  
★ Output for feeding Stereo Multiplexer.  
★ Tuner head using Silicon Planar Tran-  
sistors. ★ Designed for standard 80 ohm co-axial input.  
Made to visually match our Super 15 and 30 amplifiers and of the same high  
standard of performance and reliability. The pre-wired tuning head facili-  
tates speed and simplicity of construction. Printed circuitry. Only first grade  
transistors and components used. Our latest product giving you the best at  
half the cost of comparable units. Stereo Multiplexer available.

**AUDIOTRINE HIGH FIDELITY  
LOUSPEAKERS**

Heavy cast  
construction.  
Latest high efficiency ceramic magnets.  
Dual Cone for extended frequency range.  
Plastic treated surround giving  
low fundamental resonance. Respon-  
se 40-18,000 c.p.s., Impedance  
3 or 15 ohms. Carr. 5/6.




HF811D 8in. 10 WATT 4 Gns.  
HF101D 10in. 12 WATT 5 Gns.  
HF100D 10in. 15 WATT £5.15.0  
HF121D 12in. 20 WATT £6.15.0  
HF127D 12in. 30 WATT 9 Gns.

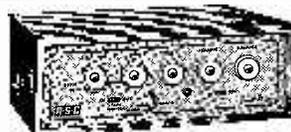**R.S.C. SUPER 15 HI-FI AMPLIFIER**

FULLY TRANSISTORISED 200/250v. A.C. Mains.  
OUTPUT 10 WATTS R.M.S. cont. into 15 ohms.  
15 WATTS R.M.S. cont. into 3-4 ohms.  
Maximum instantaneous Peak power output 28 watts.  
PRINTED CIRCUIT CONSTRUCTION.  
LATEST MULTILAYER TRANSISTORS. AD149, AD149,  
OC127, OC81Z, OC44, OC44, OC81Z, OC44, AC107.  
5 POSITION INPUT SELECTOR SWITCH  
EQUALISATION to Standard R.I.A.A. and C.C.I.R.  
Characteristics for Gram and Tape Heads.  
FULL TAPE MONITORING FACILITIES.  
SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or  
Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head  
2.5 mV. Radio/Aux or Ceramic P.U. 110 mV.  
FREQUENCY RESPONSE: ± 2dB 20-20,000 c.p.s.  
TREBLE CONTROL: +15dB to -14dB at 10 Kc/s.  
BASS CONTROL: +12dB to -15dB at 50 c/s. HUM LEVEL: -75dB.  
HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.25%.  
NEGATIVE FEEDBACK: 52dB.  
Complete Kit of parts with full constructional details and  
point to point wiring diagrams. Carr. 11/-  
Supplied factory built 15 Gns. Carr. 12/6. Terms: Deposit 49/- and 9  
monthly payments 33/9 (Total £17.12.9). Or fitted in beautiful Walnut or  
Teak veneered cabinet as illustrated, 4 Gns. extra.  
ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND  
SUPPLIED BY LEADING BRITISH MANUFACTURERS.

TECHNICAL  
SPECIFICATIONS COMPARE MORE  
THAN FAVOURABLY WITH SIMILAR  
AMPLIFIERS AT TWICE THE COST



11 Gns.


**R.S.C. SUPER 30 STEREO AMPLIFIER**

A DUAL CHANNEL VERSION OF THE SUPER  
15. Employing Twin Printed Circuits. Close tolerance  
Ganged Pots. Matched Components.  
CROSS TALK: -52dB at 1,000 c.p.s.  
CONTROLS: 5 position Input Selector, Bass Control,  
Treble Control, Volume Control, Balance Control, Stereo/  
Mono Switch, Tape Monitor Switch, Mains Switch.  
INPUT SOCKETS (Matched Pairs). (1) Magnetic P.U.  
(2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/  
Microphone. Operation of the Input Selector Switch  
assures appropriate equalisation.  
Rigid 18 s.w.g. Chassis. Size approx. 12in. Wide, 3in. High  
and 8in. Deep. Neon Panel Indicator. Attractive Facia  
Plate and Spun Silver Matching Knobs. Above facilities, etc., except for  
Ganging and Balance Control, apply also to Super 15.  
THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH  
ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic,  
Magnetic, Moving Coil, Ribbon) CURRENTLY AVAILABLE.  
SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY  
USING WITH FIRST RATE ANCILLARY  
EQUIPMENT. All required parts, point to point wiring  
diagrams and detailed instructions. Carr. 13/9  
Unit factory built 25 Gns. or deposit 83/9 and 9 monthly payments 56/9  
(Total £29.14.6). Fitted cabinet as Super 15 29 Gns. Carr. 15/- or Deposit  
£4.14.9 and 9 monthly payments 65/10 (Total £34.7.3). Send S.A.E. for leaflet.

18½ Gns.
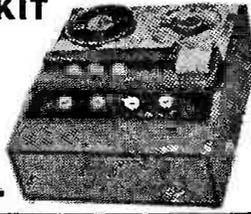
## AUDIOTRINE HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST: S.A.E. for leaflet.  
 CAN BE ASSEMBLED IN AN HOUR.  
 ONLY 4 PAIRS OF SOLDERED JOINTS PLUS MAINS. Incorporating the latest Magnavox 'Papedeck'. The Audiotrine High Quality Tape Amplifier with switched equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a handsome Portable Cabinet of latest styling finished dark grey leathercloth. Size 14 1/2 x 17 x 8 1/2 in. and circuit. Purchased separately would total approx. £34. Performance equal to units in the £50-£60 class. Deposit 26 1/2 Gns. 4 Gns. and 9 monthly payments 59/6 (Total 291 Gns.) 4 Track Model 3 Gns. extra. Carr. 19/6



LINEAR TAPE PRE-AMPLIFIER. Type LP/1 Switched Equalisation. Positions for Recording at 1 1/2 in., 3 1/4 in., 7 1/2 in. per sec. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier suitable most Tape Decks. Terms available. 10 1/2 Gns.

## R.S.C. 4/5 watt A5 HIGH GAIN AMPLIFIER

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P.U. heads and practically all "mikes". Separate Bass and Treble controls giving "lift" and "cut". Hum level 71dB down. Negative Feedback 15dB. Reserve power supply 300v 25 m.a., 6.3v 1.5 a. for Radio Tuner or Tape Pre-amp. For A.C. mains 200-250v. Speaker output 3 ohms. Complete in every detail with fully punched enamelled chassis, point-to-point wiring diagrams and instructions. Or assembled ready for use 6 Gns. plus 5/9 carr. £4.17.9

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp./Tone Control Stages. Performance figures equal to most expensive amplifiers available. Hum level -70dB. Frequency response +3dB 30-20,000 c/s. Specially designed sectionally wound ultra linear output transformer with 807 output valves. All first grade components. Valves EF86, EF86, ECC83, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 12 millivolts so that any kind of Microphone or Pick-up is suitable. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram. Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts 12 Gns. Carr. 12/6. Fully punched chassis, point to point wiring diagrams and instructions. 12 months guarantee for 15 Gns. If required perforated cover with carrying handles can be supplied for 21/- Send s.a.e. for leaflet. TERMS: Deposit 45/- and 9 monthly payments of 33/7 (Total £17.10.3).

## JASON VHF/FM TUNER | WIRELESS MICROPHONES

Complete with lapel mike. Complete kit with valves. £6.19.11 | Range up to one mile. Reception on any V.H.F. radio. These cannot be used in U.K. 10 Gns.

## R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP Two input sockets with associated controls allow mixing of "mike" and gram. etc. High sensitivity. Valves ECC83, ECC83, EL84, EL84. High quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE. Frequency response +3dB 30-20,000 c/s. Six negative feedback loops. Hum level -80dB. SENSITIVITY 23 millivolts. Suitable for Crystal or Ceramic P.U. all types "mikes". Comparable with the very best designs. For Musical Instruments such as String Bass, Electronic Guitars, etc. Reserve Power provides 300v. 30ma. and 6.3v. 1.5a. for Radio Tuner or Tape Pre-amp. Size approx. 12 x 9 x 7 1/2 in. For A.C. mains 200-250v. 50 c.p.s. Output for 4 and 15 ohm speakers. Kit complete to last nut. Chassis fully punched. Full instructions and point-to-point wiring diagrams (or factory built £11.15.0). Metal cover with 2 handles available for 21/-. TERMS ON ASSEMBLED UNITS: Deposit 36/6 and 9 monthly payments of 25/9 (Total £13.8.3). Send S.A.E. for illustrated leaflet of Cabinets, Speakers, Mikes, etc. £8.15.0

## R.S.C. BASS-REGENT 50 WATT AMPLIFIER

AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT For lead, rhythm, bass guitar and all other musical instruments. For vocalists, gram, radio, tape, and general public address. \* UNUSUALLY POWERFUL LOUDSPEAKER COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS a FANE 12in. 20 watt unit with extended frequency response. \* 4 Jack Inputs and two Volume Controls for simultaneous use of up to 4 pick-ups or "mikes". \* Cabinets covered in two-tone Rexine/Vynair with gold trimming. Fitted carrying handles. \* Separate Bass and Treble Controls giving "lift" and "cut". 49 1/2 Gns. Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at three times the cost. Carr. 30/- Or deposit £7.17.6 and 9 monthly payments of £5.10.10. (Total 55 Gns.)

## B20 MULTI-PURPOSE AMPLIFIER

especially suitable for Bass Guitar. Incorporating massive 15in. high flux loudspeaker. Rating 25 watts. Individual bass and treble controls. Two jack inputs separately controlled. Substantial cabinet attractively finished in Rexine and Vynair. Size approx. 24 x 21 x 11in. Send S.A.E. for leaflet. 29 1/2 Gns. Or Deposit £4.14.6 and 9 monthly payments of 66/- (Total £34.8.6). Carr. 17/6.

## LINEAR TREMOLO PRE-AMP UNIT

Suitable for use with any of our Amplifiers. Controls are Speed (frequency of interruptions), Depth (for 4 heavy or light effect), Volume and Switch. 4 Gns.

## R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50 c/s is available. Complete kit with diagram 47/9 or ready for use 59/11.

## SELENIUM RECTIFIERS F.W. (Bridged)

All 6/12 v. D.C. output. Max A.C. input 18 v. 1 a. 3/11. 2 a. 6/11. 3 a. 9/9. 4 a. 12/9. 6 a. 15/9. HEAVY DUTY SELENIUM RECTIFIERS 19/9 12v. 15 amps, F.W. (Bridged). Only

## LONDON-NEWCASTLE

New branches now open — see addresses

## R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. 15 ohm matching. Type C58, 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. 42 x 10 x 5in. Or Deposit 44/- and 9 monthly pmts 31/5 (Total £16.6.9) Carr. 10/- 14 Gns. Type C412, 40 watts. Fitted four 12in. 12,000 line 10 watt speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/- 21 Gns. Or Deposit £3.11.0 and 9 monthly payments of 46/7 (Total £24.10.3).

## 30 WATT HI-FI AMPLIFIER

for Guitar, Vocal or Instrumental Group A 4 Input, 2 volume control Hi-Fi unit with Separate Bass and Treble controls. Latest valves. Strong Rexine covered cabinet with carrying handles. Attractive black/gold perspex fascia. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. 17 Gns. Carr. 12/6 for leaflet. Deposit £3 and 9 monthly payments of 37/5 (Total £19.16.9).

## 12in. HIGH QUALITY L'SPEAKERS

In teak veneered cabinets. 10 Watt Model. Gauss 12,000 lines. 3 or 15 ohms. Carr. 7/6 £4.19.11 20 Watt Model. 15 ohm. Size 18x18x10in. Gauss 12,000 lines. Rexine covered £1 extra. Carr. 10/6 £7.19.11 Terms available on both.

## FANE HEAVY DUTY HI-FI SPEAKERS

12in. 20 watt. Type 122/10. Carr. 5/9 5 Gns.

## LOUDSPEAKERS

Limited number at fraction of list price 15 ohms. Impedance. Brand new, guaranteed. 12in. HEAVY DUTY 30 watts 7 Carr. 12/6 Normally £12 approx. 15in. EXTRA HEAVY DUTY 40-50 watts 11 Carr. 17/6 Normally £19 approx. GNS.

## R.S.C. GRAM AMPLIFIER KIT

3-4 watts output. Negative feedback. Controls: Vol. Tone and Switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc. supplied. Only 49/11.

## HIGH FIDELITY 12in. 10 WATT SPEAKERS

Flux Density 12,000 lines. Impedance 8 or 15 ohms. 59/11

## TRANSISTOR SALE

Mullard OC71, OC72, OC81, 2/11, OC44, OC45, 3/11, OC75, 7/9, AF117 6/9. Post 6d. for 3.

## R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED, Interleaved and Impregnated. Primaries 200-250v. 50 c/s. Screened. MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.	
250v., 60mA, 6.3v. 2a. ....	14/11
250-0-250v., 60mA, 6.3v. 2a. ....	15/11
FULLY SROUDED UPRIGHT MOUNTING	
250-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 3a. ....	19/9
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. ....	33/9
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. ....	33/9
300-0-300v. 130mA, 6.3v. 4a. c.t., 6.3v. 1a. ....	41/9
For Mullard 510 Amplifier	41/9
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. ....	33/9
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. ....	42/9
425-0-425v. 200mA, 6.3v. 4a., c.t., 6v. 3a. ....	67/9
425-0-425v. 200mA, 6.3v. 4a., 6.3v. 4a., 5v. 3a. ....	69/9
450-0-450v. 250mA, 6.3v. 4a. c.t., 6v. 3a. ....	79/9
TOP SROUDED DROP-THROUGH TYPE	
250-0-250v. 70mA, 6.3v. 2a., 0-5-6.3v. 2a. ....	19/9
250-0-250v. 100mA, 6.3v. 3.5a. ....	21/9
250-0-250v. 100mA, 6.3v. 2a., 6.3v. 1a. ....	22/9
350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. ....	23/9
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. ....	32/9
300-0-300v. 100mA, 6.3v. 4a., 0-5-8.3v. 3a. ....	32/9
300-0-300v. 130mA, 6.3v. 4a., 0-5-6.3v. 1a. ....	39/9
Suitable for Mullard 510 Amplifier	39/9
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. ....	32/9
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. ....	39/11
FILAMENT or TRANSISTOR POWER PACK Types	
6.3v. 1.5a 6/9, 6.3v. 2a 7/9, 6.3v. 3a 9/9, 6.3v. 6a 18/9, 12v. 1a 8/9, 12v. 3a or 24v. 1.0a 19/9, 0-9-18v. 1 1/2a. 15/9, 0-25-35-42v. 2a 27/9.	
CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. 13/11 2 1/2a. 16/11, 3a. 18/11, 5a. 21/11, 6a. 25/11, 8a. 31/11	
AUTO (Step Up/Step Down) TRANSFORMERS	
0-110/120v.-200-230-250v. 50-80 watts, 14/9 150 watts, 29/11, 250 watts, 49/9, 500 watts, 99/9	
OUTPUT TRANSFORMERS	
Standard Pentode 5,000Ω to 7,000Ω to 3Ω	7/9
Push-Pull 8 watts EL84 to 3Ω or 15Ω	11/9
Push-pull 10 watts 6V6 ECL86 to 3, 5, 8 or 15Ω	21/9
Push-pull EL84 to 3 or 15Ω 10-12 watt	19/9
Push-pull Ultra Linear for Mullard 510, etc.	35/9
Push-pull 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15Ω	29/9
Push-pull 20 watt high quality sectionally wound, EL34, 6L6, KT66, etc., to 3 or 15Ω fully shrouded	55/9
SMOOTHING CHOKES	
150mA, 7-10H, 250Ω 12/9. 100mA, 10H, 200Ω 9/11. 80mA, 10H, 350Ω 7/9. 60mA, 10H, 400Ω 4/11.	

## INTEREST CHARGES REFUNDED

on H.P. and Credit Sale Accounts settled in 3 months.

## CLEARANCE SALE !

WATKINS COPYCAT ECHO UNITS 19 1/2 Carr. 17/6 Listed £38.10.0. Brand new. VOX and LINEAR GUITAR AMPLIFIERS. Various models at half list price.

## POWER PACK KIT

Consisting of Mains transformer. Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250v. A.C. 22/11 mains. Output 250v. 60mA 6.3v. 2a Supplied with case in lieu of chassis 26/11. Or assembled 39/11.

## HEAVY DUTY BATTERY CHARGER KITS 6/12 v.

Consisting of Mains Trans. 200-250 v. Rectifier. Ammeter, Variable Charge Rate Selector, Panels, Plugs, Fuses and Holders. Fully punched stove enamelled case 4a 49/11 6a 69/11 Or assembled ready for use 10/- extra.



**"I am MORE THAN SATISFIED  
with my AMAZING JOYSTICK"**

REX LAWSON, LONDON, S.E.13

# JOYSTICK VFA SYSTEMS

The Joystick VFA system is a remarkable invention. Its unique quality of high performance at any selected frequency from 1 M/c. to 30 Mc/s.—particularly from difficult locations—has radically changed the attitude of both the licensed amateur and the shortwave listener towards their aerial problems.

Each Joystick VFA system is complete with a Joymatch matching unit suitable for your type of operation.

You cannot afford to ignore the potential of the Joystick VFA. The system is simple to use—the Joystick VFA will clip to a chimney, tree or mast, can be laid upon a pelmet, stood in the corner of a room. will even give a good account of itself in a basement.

You are strongly recommended to contact the Joystick factory immediately (or one of our agents) for a brochure with full details.

More Testimonials to Joystick Systems.


A3555 Nottingham: "2 to 3 S points up on my 20 mtr. long wire. Thank you for your prompt delivery".

L. Moore, Notts.: "Excellent Results".

U.K. Agents: G. W. Smith & Co. (Radio) Ltd., 3 Lisle Street, London, W.C.2. Stephens-James Ltd., 70 Priory Road, Liverpool, 4. Chas. H. Young, 170/172 Corporation Street, Birmingham, 4. R.S.C. (Manchester) Ltd., 326 Argyle Street, Glasgow, C.1 (and all branches) Swan & Co. Products Ltd., 247 Humber Ave., Coventry. Lasky's Radio (all branches), G3HSC, 45 Green Lane, Purley, Surrey. (Demonstrations by appointment).




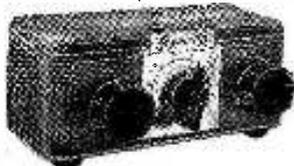Joymatch Type 3—General short wave coverage SWL (Junior model).



Joymatch Type 2A—General medium wave coverage extending over short wave spectrum.

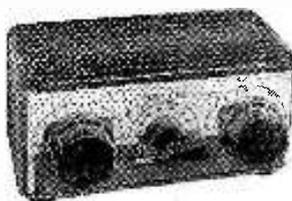U.S. PATENT  
No. 3274600.  
S. AFRICA PATENT  
No. 63/4389.  
UK and World Patents  
applied for.



Joymatch Type 3A—General short wave coverage for SWL. Bandswitched for amateur bands.

Post this coupon in the morning—without fail!

**PARTRIDGE ELECTRONICS LIMITED**

Caister House, Prospect Road, Broadstairs, Kent.

NAME..... Call sign.....

ADDRESS .....



PWD

**The safest, quick and handy  
connector for electrical  
appliances**
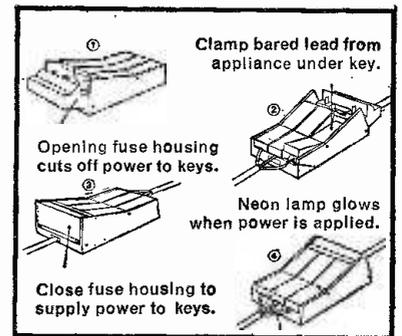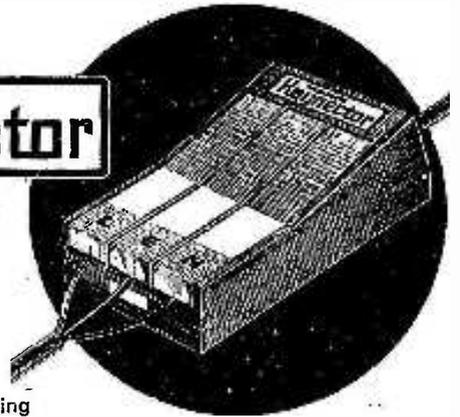
## MAINS Keynector

Measuring only 5in. x 3in x 1½in. the MAINS KEYNECTOR is made of non-combustible urea-formaldehyde. Designed in modern style and manufactured in attractive two-tone colour. The unit eliminates the need of terminating the mains input lead of any electrical instrument or appliance with a plug. Also enables more than one instrument or appliance to be connected in parallel and used simultaneously. In the workshop, the MAINS KEYNECTOR will prove invaluable to the experimenter and handyman.

Colour: **32/6**  
Duo-Green.  
Rating: 13 amp. inc. p.p.  
British and Foreign Patents pending.



**CYBERNAUT CONTROLS LTD.** (Ref. P.W.1)  
28-30 Rivington Street, London, E.C.2. Tel: 01-739 2763

## TELEVISION RECEIVER THEORY:

### Part I

A Textbook for Students and Technicians

G. H. HUTSON

35s. net

The first of two volumes which together provide a systematic course in television receiver theory, including a study of both positively and negatively modulated systems and embracing both valve and transistor circuitry.

## ELECTRICAL SCIENCE FOR ELECTRICAL INSTALLATION STUDENTS: Part I

J. A. MYERS

12s 6d. net

The first of two volumes written to cover the syllabus of Electrical Science for Electrical Installation Course "B" of the City and Guilds of London Institute.

## PROBLEMS IN ELECTRONICS

J. C. HIGGINS


40s. net

"... this is a useful compendium which will be of value to students and lecturers in technical colleges preparing for graduateship examinations."

**EDWARD ARNOLD**

41 Maddox Street, London, W.1.

# HEATHCRAFT

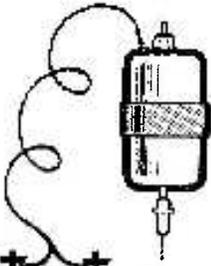

PAT. NO.  
980345

## Mini-Drill

**BATTERY OPERATED  
PRECISION MINIATURE DRILL**

SOME OF THE USES OF THE UNIQUE HEATHCRAFT MINI DRILL



PORTABLE, SHOCKPROOF, only 5" long, the Mini-Drill with its powerful miniature motor, works from a standard battery. With its specially designed MINI-TOOLS it enables many intricate jobs to be done not hitherto possible. Drills plastic, aluminium, brass, copper, gold, silver etc. **STANDARD** Mini-Drill with nylon holding bush, twist drill, mop, burr, abrasive, pencil brush, spear drill, full instructions 39/6 p.p. 1/6. **SUPER** Mini-Drill with extra power and interchangeable chuck, 69/6 p.p. 1/6. Guaranteed. Send cheque/P.O. or write for **FREE** leaflet. **JABERLAND TRADING CO. LTD.**, Dept. C., 148-150 Curtain Road, London, E.C.2.

## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS		1R5, 1B5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for 16/8. DAF96, DF96, DK96, DL96, 4 for 24/6															
1A7GT	7/6	10C2	11/6	DH77	4/-	EF92	3/3	PEN383	9/6	UCH81	6/-						
1H5GT	7/3	10F1	9/9	DH81	12/6	EF97	7/6	PFL20013/6	7/6	UCL82	7/-						
1N6GT	7/9	10P13	8/6	DK32	7/9	EF183	6/9	PL86	9/-	UCL83	8/8						
1R5	5/6	12AT7	3/9	DK91	5/6	EF184	6/-	PL81	6/9	UF41	8/-						
1B4	4/9	12AU6	4/9	DK92	8/-	EL33	6/6	PL82	6/6	UF80	7/-						
1B5	3/9	12AU7	4/9	DK96	6/6	EL41	3/6	PL83	6/-	UF89	5/9						
1T4	2/9	12AX7	4/9	DL33	6/9	EL42	7/9	PL84	6/3	UL41	8/9						
3A5	7/-	12K7GT	3/6	DL35	5/-	EL84	4/9	PL80	13/6	UL44	20/-						
3Q4	5/6	12K8GT	7/9	DL82	4/9	EM80	5/9	PL81	7/6	UL84	5/9						
3B4	4/9	20F2	10/6	DL94	6/-	EM84	6/9	PX25	7/9	UY21	8/9						
3V4	4/6	20L1	14/-	DL96	6/6	EM87	6/6	PY32	8/8	UY31	4/9						
5U4G	5/6	20P1	8/-	DY86	6/6	EY81	6/3	PY33	8/8	VP4B	11/-						
5V4G	7/9	20P2	9/-	DY87	6/6	EY86	6/-	PY80	5/3	VP4E	11/-						
5Y3GT	5/-	20P4	13/6	EABCS0	8/-	EZ40	6/3	PY81	5/3	W76	3/6						
5Z4G	7/-	25U4GT11/6	11/6	EAF42	8/-	EZ41	6/6	PY82	5/-	W77	3/6						
630L2	9/6	30C15	10/6	EB41	4/-	EZ80	4/6	PY83	5/9	Z77	3/6						
6A15	2/3	30C17	11/6	EB91	2/3	EZ81	4/6	PY88	7/3	Transistors							
6A15	3/6	30C18	9/9	EBC33	7/-	EZ82	9/-	PY800	6/6	AC107	10/-						
6A05	5/6	30F5	9/9	EBC41	8/-	KT61	6/6	PY801	6/-	AC127	7/6						
6A7B	4/-	30FL1	11/6	EBF50	5/9	N18	5/6	R19	7/6	AD140	15/6						
6B4A	4/6	30L15	11/-	EBF59	5/9	N78	14/9	R20	12/9	AF102	18/-						
6B8E	6/3	30L17	12/-	ECC81	3/9	PC86	9/-	U25	9/-	AF115	6/-						
6B36	4/9	30P4	11/6	ECC82	4/9	PC88	9/-	U26	8/9	AF116	6/6						
6BW6	7/3	30P12	9/9	ECC83	7/-	PC97	5/9	U47	8/6	AF117	5/-						
6F1	7/9	30P19	11/6	ECC84	6/3	PC90	8/9	U49	9/6	AF118	12/6						
6F13	3/6	30PL1	12/9	ECC85	5/6	PCC84	5/6	U52	4/6	AF124	9/-						
6F14	9/-	30PL13	13/3	ECC80	7/6	PCC89	9/3	U78	3/6	AF125	8/6						
6F23	9/9	35L6GT	6/3	ECC82	6/9	PCC89	9/3	U191	10/6	AF126	8/-						
6K7G	1/6	35V4	4/6	ECC86	9/-	PCF80	6/6	U301	11/9	OC22	10/-						
6K8G	4/3	35Z4GT	4/6	ECH35	6/-	PCF82	6/-	U801	16/3	OC25	9/6						
6K8GT	7/6	85A2	5/9	ECH42	9/-	PCF86	8/3	UAF42	7/9	OC26	6/9						
6L18	7/6	185BT	20/-	ECH81	5/-	PCF801	8/9	UBC41	6/9	OC44	4/3						
6Q7G	5/6	6063	12/6	ECH84	8/6	PCF802	9/6	UBF80	6/-	OC45	3/3						
6V6G	3/6	AZ31	9/-	ECL80	6/-	PCF805	9/9	UBF89	5/9	OC71	3/6						
6V6GT	6/6	B36	4/6	ECL82	6/3	PCL82	6/9	UBL21	9/-	OC72	4/9						
6X4	3/6	B729	10/-	ECL86	7/9	PCL83	8/6	UC92	5/6	OC75	5/9						
6X5GT	5/9	DAC32	7/3	EF39	3/9	PCL84	7/6	UCC84	7/9	OC81	3/6						
7B6	10/9	DAF91	3/9	EF41	6/3	PCL85	8/3	UCC85	6/6	OC81D	3/6						
7B7	7/-	DAF96	6/-	EF80	4/9	PCL86	8/6	UCF80	8/3	OC82	5/9						
7C5	9/6	DCC90	7/-	EF85	5/-	PEN44	6/9	UCF21	9/3	OC82D	5/-						
7C6	6/9	DF33	7/9	EF86	6/3	PEN38C15/-	UCH42	8/9		OC170	5/-						
7H7	5/6	DF91	2/9	EF89	5/-												
7Y4	6/6	DF96	6/-	EF91	3/6												

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. CRE 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

# TECHNICAL TRAINING in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- Institution of Electronics & Radio Engineers (Brit.I.R.E.)
- C. & G. Telecommunication Techns' Certs.
- C. & G. Supplementary Studies
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, signal generator and multimeter—all under expert tuition. Transistor Portable available as separate course.

## POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Interact House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.).....

NAME .....

ADDRESS .....

5.67

### INTERNATIONAL CORRESPONDENCE SCHOOLS

# VIKING TRANSISTOR

## 40-50 WATT AMPLIFIER

**OPERATING INSTRUCTIONS GENERAL.** An extremely reliable lightweight amplifier capable of giving 40-50 watts of undistorted sound, made possible by the use of the latest semi-conductors (transistors) and techniques which ensure space-age reliability under the most rugged conditions. It is designed as a general purpose amplifier particularly suitable for use with musical instruments that require exceptionally high treble response (not recommended for Bass Guitar). Tremolo facilities are available on Channel 1 only. **INPUTS—CONTROLS—CHANNEL 1 (Tremolo):** this contains two high gain input jack sockets controlled by Volume Control 1 which is mounted directly above the two sockets marked tremolo. **BASS 1:** gives a controlled boost to the lower frequencies on Channel 1 only. **TREBLE 1:** gives a controlled boost to the high frequencies on Channel 1 only. **TREMOLO:** this operates on Channel 1 only and the variations of intensity and speed of the Tremolo beat is adjusted by the controls **DEPTH** and **SPEED**. A socket is provided in the rear of the amplifier so that the Tremolo may be switched on and off by the use of a footswitch plugged into the socket. If you wish the Tremolo to be used without the foot-switch, this is possible as the footswitch is only used to short out the effect. **INPUTS AND CONTROLS—CHANNEL 2 (Normal):** this contains two high gain input jack sockets controlled by Volume Control 2 which is mounted directly above the sockets marked **Normal**. **TREBLE 2:** gives a controlled boost to the treble frequencies on Channel 2 only. **MAINS VOLTAGE:** fully adjustable, 200-250 volts, A.C. .50 cycles. **POWER OUTPUT:** 40-50 watts sine wave British rating. Very little distortion. **OUTPUT IMPEDANCE:** 3 ohms. Price 21 gns. plus £1 postage and packing.



**WOLSEY U.H.F. AERIAL AMPLIFIER,** two stage, gain 23 dB, noise factor 3 dB, power consumption 6 mA at 14 volts. Two AF186 transistors, complete with built-in power supply in metal case, list price 9 gns., our price 4½ gns. plus 2/6 postage and packing.

**MAINS TRANSFORMER,** primary 200/250 volt, secondary 425/425 volt. 250 mA, 6.3 volt 4 amp, 5 volt 3 amp; fully shrouded, chassis mounting. Price £2.5.0 plus 7/6 postage and packing. Auto transformer step-up-step-down, 240/110 volt 400 watt. Price £1.5.0 plus 7/6 postage and packing.


**MAINS TRANSFORMER 200/250 volt,** secondary 250/250 volt, 70 mA, 6.3 volt, 3 amp drop through. Price 12/6 plus 4/6 postage and packing. Elac 10 inch, 10,000 lines ceramic magnet, 3 or 15 ohms, 7 watt, £1.9.6 plus 4/6 postage and packing.



## POCKET MULTI-METER

Size 2½ x 2½ x 1½ in. Meter size 2½ x 1½ in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0.15, 0.150 0.1000. D.C. current 0.150mA. Resistance 0.100kΩ. Complete with test leads, battery and full instructions, 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

## 40W FLUORESCENT LIGHT KIT

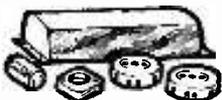

Incorporating GEC Choke size 8½ in. x 1½ in. x 1½ in., 2 bi-pin holders, starter and starter-holder. P. & P. 5/6. 11/6  
Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 11½ in. x 1½ in. x 1½ in., 2 bi-pin holders start and starter holder. P. & P. 6/6. 17/6

Twin 40W Choke instant start for 2 x 2ft. tubes 17/6. P. & P. 5/6.

## 3 to 4 Watt AMPLIFIER


3-4 watt Amplifier built and tested. Chassis size 7 x 3½ x 1½ in. Separate bass, treble and volume control. Double wound mains transformer, metal rectifier and output transformer for 3 ohms speaker. Valves ECC81 and 6V6. £2.5.0 plus 5/6 p. & p.

The above in Kit Form, £1.14.6 plus 5/6 p. & p.


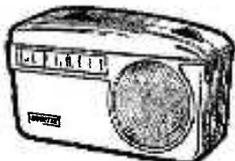
## "MUSSETTE" 6-Transistor Superhet Portable Radio

★ 2½" Speaker. ★ 6 Transistor Superhet Output 200mW. ★ Plastic Cabinet in red, size 4½" x 3" x 1½" and gold speaker louvre. ★ Horizontal Tuning Scale. ★ Ferrite Rod Internal Aerial. ★ IF 460 kc/s. ★ All components Ferrite Rod and Tuning Assembly mount on printed board. ★ Operated from PP3 Battery. ★ Fully comprehensive instructions and point-to-point wiring diagram. ★ Printed Circuit Board. ★ Tunable over medium and long waveband. ★ Car aerial and earpiece socket.



Price 39/6d. inc. carrying strap. Circuit Diagram 2/6 free with parts. P. & P. 8/6.

## RADIO & TV COMPONENTS (Acton) LTD

21c High Street, Acton, London, W3


Shop Hours 9 a.m.—6 p.m. Early Closing Wednesday

Goods not despatched outside U.K. Terms C.W.O. All enquiries Stamped Addressed Envelope
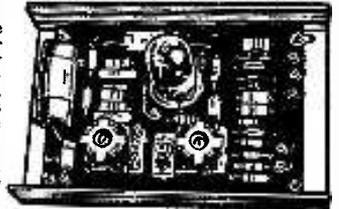
# MULTIPLEX DECODER

For receiving Stereo FM

Now is your chance to benefit in full from the new B.B.C. stereo transmissions with our Multiplex Decoder. Design features: Highly efficient Mullard vinkor pot cores. Two semi-conductor diodes. Double purpose valve. Printed circuit type construction high input impedance. Specification: Cross talk minus 26 dB at 1 kc/s. Input requirements 0.5—1.5 RMS. Stability plus or minus 0.1%. Voltage requirements H.T. 190—250 volts. D.C. at 5 mA, heaters 6.3 volts. A.C. at 300 mA. Self powered unit shortly available, price to be announced. Size 5½" x 3½" x 1". Fully built and tested.



Price £4.4.0 P. & P. 3/-



## Type E MOTOR


Small A.C. mains motor 230/250 volts complete with gearbox, 6 r.p.m. Price 15/- plus 4/- P. & P. Similar to above motor but without gearbox. Price 9/6 plus 3/- P. & P.

## Silicon Rectifiers

250 v. P.I.V. 750 milliamps. Six for 7/6, Post paid.
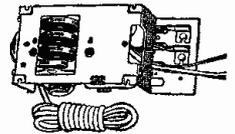
## TRANSISTORISED 1½ WATT AMPLIFIER

comprising 2AC 128, 20C 75 and 2 AA129 separate bass and treble volume controls. Complete with Power Supply AC mains 240 v. Size 7½" x 3½" x 2". Price 50/- plus 2/6 P. & P.



## POWER SUPPLY KIT

A.C. MAINS 200-250 V

Incorporating "C" core type mains transformer, full wave metal rectification and smoothing condenser. Smooth output 250 v. 250mA and 6.3v. 4 amp. for Heaters. 25/- P. & P. 9/6.




## FIRST QUALITY P.V.C. TAPE

5½" Std.	850ft.	9/-	5" L.P.	850ft.	10/6
7" Std.	1200ft.	11/6	3" T.P.	600ft.	10/6
3" L.P.	240ft.	4/-	5" T.P.	1800ft.	25/6
5½" L.P.	1200ft.	11/6	6½" T.P.	2400ft.	32/6
7" L.P.	1800ft.	18/6	7" T.P.	3600ft.	42/6
5½" D.P.	1800ft.	18/6	4" T.P.	900ft.	15/-

P. & P. on each 1/6, 4 or more post free

## EXTRACTOR FAN

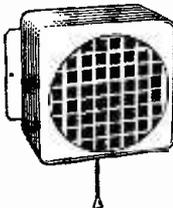

AC Mains 230/250 v. complete with pull switch. Size 6" x 6" x 4". Price 27/6 plus 5/- P. & P.


## GEC DOORBELL

Complete with mains transformer 240 v. AC & illuminated bell push. Price 12/6 plus 5/6 P. & P.



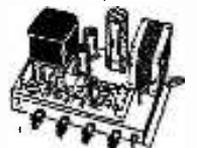
## 8-watt 4-valve PUSH-PULL AMPLIFIER & METAL RECTIFIER

Size: 9" x 6" x 1½". A.C. Mains, 200-250V 4 valves. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Output 8 watts at 5 per cent of total distortion. Separate bass and treble lift control. Two inputs, with controls for gram. and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested, £4.4.0. P. & P. 11/-, 8" x 5" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P.


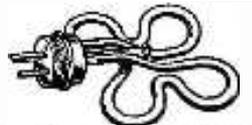
## GEC KETTLE ELEMENT

3,000W WITH AUTOMATIC EJECTION 200/240 v. Size of hole required 1½". List Price 32/-. Our PRICE 15/- P. & P. 1/6.




## NEW TRANSISTORISED SIGNAL GENERATOR

Size 5½" x 3½" x 1½". For IF and RF alignment and AF output 700 c/s frequency coverage 460 kc/s to 2 mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and Mussette. Built and tested. 39/6 P. & P. 3/6
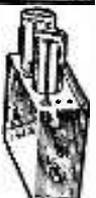
## CYLDON U.H.F. TUNER

Complete with PC88 and PC86 Valves. Full variable tuning. New and unused. Size 4½ x 5½ x 1½ in. Complete with circuit diagram. 35/- plus 3/6 P. & P.



Also at 323 EDGWARE ROAD, LONDON, W.2. Personal shoppers only. Early Closing Thursday. All orders by post to our Acton address.

# Elegant Seven Mk II A

## COMBINED PORTABLE and CAR RADIO

### SPECIAL OFFER

7" x 4" P.M. Speaker at no extra charge

Buy yourself an easy to build 7 transistor radio and save at least £10.0.0. Now you can build this superb 7 transistor superhet radio for under £4.10.0. No one else can offer such a fantastic radio with so many de luxe star features.


- ★ De luxe grey wooden size 12½" x 8½" x 3½".
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 11½" x 2".
- ★ High 'Q' ferrite rod aerial.
- ★ I.F. neutralization on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback.
- ★ Room filling output 350 mW.
- ★ Ready etched and drilled printed circuit board back printed for fool proof construction.
- ★ Fully comprehensive instructions and point-to-point wiring diagrams.
- ★ Car aerial socket.
- ★ Fully tunable over medium and long wave. 168-535 metres and 1250-2000 metres.
- ★ All components ferrite rod and tuning assembly mount on printed boards.
- ★ Full after sales service.
- ★ Parts list and circuit diagram 2s. 6d., free with parts.

**ONLY £4.4.0**

Plus 7/6 P. & P. Parts List and circuit diagram 2/6 FREE with parts.
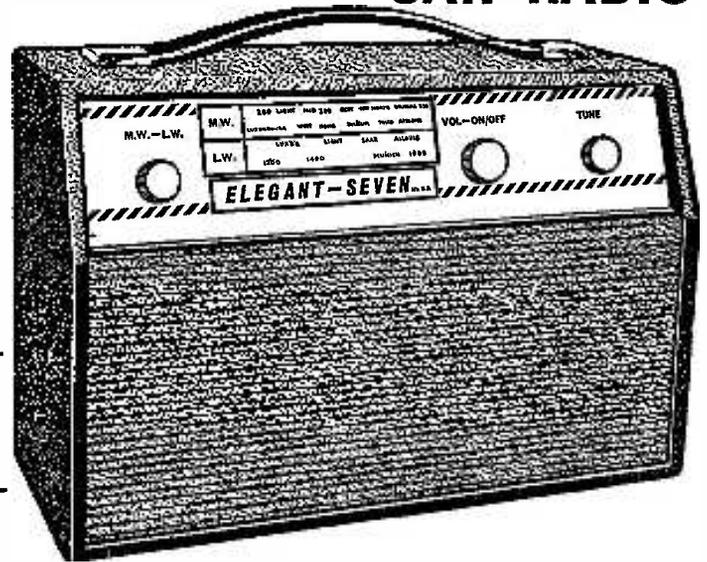
#### POWER SUPPLY KIT

To purchasers of 'Elegant Seven' parts, incorporating mains transformer, rectifier and smoothing condenser, A.C. mains 200/250 volts. Output 9v 100mA. 7/6 extra.



## RADIO & TV COMPONENTS (ACTON) LTD.

All orders by post to be sent to our Acton address

**323 EDGWARE ROAD, LONDON, W2**

Personal shoppers only. Early closing Thursday.

**21C HIGH STREET, ACTON, LONDON, W3**

OPEN 9 a.m.—6 p.m. INCLUDING SATS. EARLY CLOSING WED.  
GOODS NOT DESPATCHED OUTSIDE U.K. TERMS C.W.O.

All enquiries stamped addressed envelope

# FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 132-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio and Electronic Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Appointments Dept. and shows you how to qualify for five years promotion in one year.

### SATISFACTION OR REFUND OF FEE

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £30 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

- Radio
- Television
- Electronics
- Electrical
- Mechanical
- Civil
- Production
- Automobile
- Aeronautical
- Plastics
- Building
- Draughtsmanship
- B.Sc.
- City & Guilds
- Gen. Cert. of
- Education
- etc., etc.

#### PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc. A.M.I.E.R.E., City & Guilds Radio Amateur's Exam R.T.E.B. Certificate P.M.C. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

#### INCLUDING TOOLS!

This specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.



#### POST COUPON NOW!

- Please send me your FREE 132-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)
- NAME .....
- ADDRESS .....
- .....
- .....
- SUBJECT OR EXAM THAT INTERESTS ME ..... 344B

**BRITISH INSTITUTE OF ENGINEERING  
TECHNOLOGY**

344B, Aldermaston Court, Aldermaston, Berks.

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**

# WEYRAD

## COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values, details of which are given in the latest edition of the Constructors' Booklet priced at 2/-.

Oscillator Coil .....	P50/1AC (For OC45)	P50/1AC (For AF117).....	5/4
1st I.F. Transformer .....	P50/2CC (For OC45)	P51/1 (For AF117).....	5/7
2nd I.F. Transformer .....	P50/2CC (For OC45)	P51/2 (For AF117).....	5/7
3rd I.F. Transformer .....	P50/3CC (For OC45)	P50/3V (For AF117).....	6/-
Rod Aerial .....	RA2W.....		12/6
Driver Transformer .....	LFDT4/1 .....		9/6
Output Transformer.....	OPT1 .....		10/6
Printed Circuit.....	PCA1 .....		9/6

## I.F. TRANSFORMERS & COILS FOR VALVE CIRCUITS


Production of Tuning Coils (Type "H") and I.F. Transformers is being continued and details of these and our other components are given in an illustrated folder which will be forwarded on request with 4d. postage please.

## WEYRAD (ELECTRONICS) LIMITED


SCHOOL STREET, WEYMOUTH, DORSET
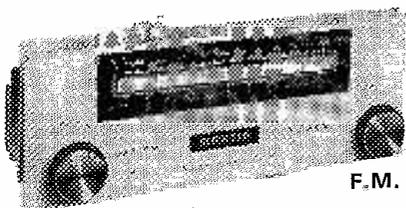
# PEOPLE PREFER MARTIN

FOR RELIABILITY, FOR QUALITY, FOR  
ADD-ON-ABILITY, FOR ECONOMY



F.M. TUNER

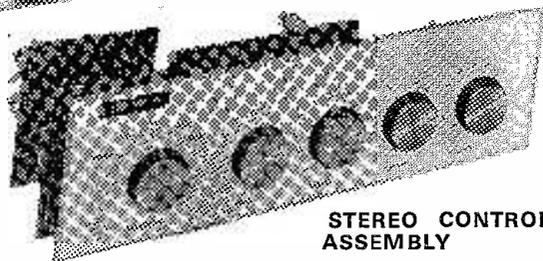

STEREO CONTROL ASSEMBLY

You can do so much with MARTIN kits. The system of using pre-fabricated transistorised units which can be interlinked in a variety of ways enables you to assemble the combination of your choice and then extend it unit by unit until you possess a full stereo gramophone and radio assembly. When new units are produced, they can be added to existing equipment very easily with the advantage that you can continue to use equipment you already have,

so that your installation is always up to date. Most important of all is the power and quality which MARTIN Audiokits give you. Their sturdy construction assures compactness without sacrifice to quality or efficiency. They offer excellent value, are very easily installed and will give years of unflinching service. That is why people prefer MARTIN—it's simple to instal, good to listen to, and looks completely professional.

## AMPLIFIER SYSTEMS • TUNERS • RECORDERS

MARTIN AUDIOKITS are available for Mono, and can be doubled up for stereo, or as complete stereo units. 3 ohm and 15 ohm systems are available. There is a special pre-amp for low output pick-ups and escutcheon panels to suit the arrangement you choose. The tuner is styled to match.

- 5-stage input Selector £2.7.6
- Pre-amp/vol. control £1.17.6
- Pre-amp/tone controls £3.2.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0
- FM Tuner £12.17.6

### MARTIN ELECTRONICS

154 High Street, Brentford, Middlesex

Please send Recordakit/F.M. Tuner/Audiokit  
Hi-Fi Leaflets. (Strike out items not wanted)

Name .....

Address .....

PW57


From Radio and Hi-Fi Stockists

**MARTIN ELECTRONICS LTD.** 154/5 HIGH STREET, BRENTFORD, MIDDLESEX. ISLeworth 1161/2

Trade enquiries invited
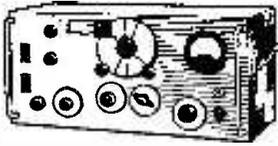
## MARCONI TEST EQUIPMENT

TF.144G STANDARD SIGNAL GENERATOR. 85 Kc/s.-25 Mc/s. 200/250 v. A.C. £25. Carr. 30/-  
 TF.501A V.H.F. SIGNAL GENERATOR. 10-310 Mc/s. 200/250 v. A.C. £32.10.0. Carr. 20/-  
 TF.195 M. BEAT FREQUENCY OSCILLATOR. 0-40 Kc/s. 200/250 v. A.C., £20. Carr. 30/-  
 All above offered in excellent condition fully tested and checked and offered at a fraction of original cost.



### 2-WAY RADIOS

Super quality. Brand new and guaranteed.

3 transistor £6.15.0 pr.  
 4 transistor £7.19.6 pr.  
 5 transistor £8.4.0 pr.  
 6 transistor £9.19.6 pr.  
 6 transistor De Luxe £17.10.0 pr.



10 transistor £22.10.0 pr.  
 13 transistor 500 MW £31.10.0 pr.  
 13 Trans. 1W £35.0.0 pr. Post extra.  
 These cannot be operated in U.K.

### SINCLAIR TRANSISTOR AMPLIFIERS


Z12 Amplifier 89/6; Z12 Power Pack 79/6; Stereo 25 Pre-Amplifier £9.19.6; Micro FM Radio Kits £5.19.6; Micro 6 Radio Kit 59/6; Micromatic Radio Kit 59/6; Ready built 79/6. Post paid.

### GARRARD RECORD PLAYERS

SRP12 Player mono £4.4.0; 1000 changer mono or stereo £5.19.6; 2000 changer mono or stereo £6.19.6; A50 Changer mono or stereo £7.10.0; 3000 Changer stereo £8.19.6; AT6 Mk II £9.19.6; SP25 Player mono or stereo £9.19.6; AT60 Changer mono or stereo £10.19.6; A70 less cartridge £19.19.0; LAB 80 Stereo £25.0.0; 401 Transcription 26 gns. Brand new and guaranteed. All plus post and packing 5/-.
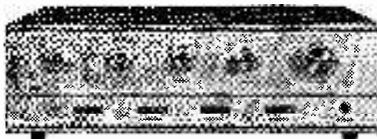
### LAFAYETTE HI-FIDELITY SOLID STATE STEREO AMPLIFIERS

Latest 1967 models now available. Outstanding performance from modern semi conductors. Provision for all types of inputs and outputs and comprehensive tone controls. Attractive metal cased free standing units.



Model LA-224T, 30 watt £25. Carr. 7/6. Model LA-60T, 60 watt £37.10.0. Carr. 7/6. DETAILS ON REQUEST

### LAFAYETTE MODEL HA-500 3SB/AM/CW 80 THROUGH 6 METRE RECEIVER



New outstanding Ham Bands only receiver covering the 80/40/20/15/10/6 metre bands. Incorporates 10 valves, product detector, two mechanical filters, S Meter, dual conversion on all bands, crystal calibrator, B.F.O., noise limiter, aerial trimmer, I.F.'s 2.608 Mc/s and 455 Kc/s. Output 8 ohms and 500 ohms. Operations 220/240 volt A.C. Supplied brand new and guaranteed with handbook. 42 gns. Carr. 10/- 100 Kc/s crystal 35/-.

### AVO CT.38 ELECTRONIC MULTIMETERS

A high quality instrument offered at a fraction of cost. Ranges A.C. and D.C. volts: 100 mV to 250 volt A.C. and D.C. current: 10µA to 1 amp. Waits: 50µW to 5 watts. Resistance: 4 ranges to 200 megohms. Operates on 110/200/250 v. A.C. 45/65 c/s. Supplied in guaranteed working order with all leads and R.F. probe. £25. Carr. 10/-.



### TRANSISTORISED TWO-WAY TELEPHONE INTERCOM.

Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.10.0. P. & P. 3/6.

### R.107 RECEIVERS

1.7-17.5 Mc/s. Mains or 12 volt D.C. operation. Perfect condition. £15. Carr. 30/-.

### SP.600JX RECEIVERS

Few only of these outstanding receivers 540 Kc/s-54 Mc/s. Cost over £500. Available in excellent condition £100.

### VARIABLE VOLTAGE TRANSFORMERS

Brand New—fully Shrouded. Input 230v. 50/60 c/s. Output 0-250 Volts.



1 Amp ..... £4.10.0  
 2-5 Amp ..... £5.7.6  
 5 Amp ..... £9.0.0  
 8 Amp ..... £13.10.0  
 10 Amp ..... £17.0.0  
 12 Amp ..... £19.10.0  
 20 Amp ..... £32.10.0  
 2-5 Amp Portable—Metal Case with Meter, Fuses, etc. £9.17.6.


### AMERICAN TAPE

First grade quality American tapes. Brand new. Discounts for quantities.

3in., 225ft. L.P. acetate ..... 4/-  
 3in., 600ft. T.P. mylar ..... 10/-  
 5in., 600ft. std. plastic ..... 8/6  
 5in., 900ft. L.P. acetate ..... 10/-  
 5in., 1,200ft. D.P. mylar ..... 15/-  
 5in., 1,800ft. T.P. mylar ..... 35/-  
 5in., 1,200ft. L.P. acetate ..... 12/6  
 5in., 1,800ft. D.P. mylar ..... 22/6  
 5in., 2,400ft. T.P. mylar ..... 45/-  
 7in., 1,200ft. std. mylar ..... 12/6  
 7in., 1,800ft. L.P. acetate ..... 15/-  
 7in., 1,800ft. L.P. mylar ..... 20/-  
 7in., 2,400ft. D.P. mylar ..... 25/-  
 7in., 3,600ft. T.P. mylar ..... 58/6  
 Postage 2/- Over £3 post paid.
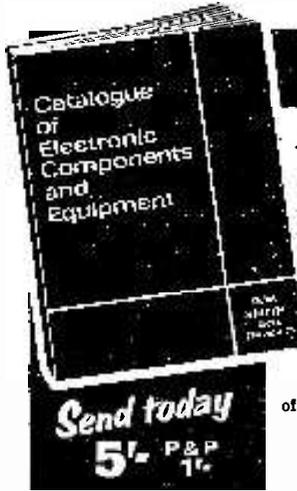
### CALLERS WELCOME!

Open 9 a.m. to 6 p.m. every day Monday to Saturday. Trade supplied. All items available as previously advertised.




# CATALOGUE

- ★ ELECTRONIC COMPONENTS
- ★ TEST EQUIPMENT
- ★ COMMUNICATIONS EQUIPMENT
- ★ HI-FI EQUIPMENT

We are proud to introduce our first comprehensive catalogue of Electronic Components and equipment. Over 150 pages fully illustrated, listing thousands of items many at bargain prices. Free discount coupons with every catalogue. Everyone in electronics should have a copy.
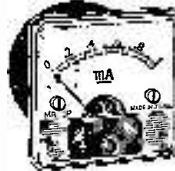
### CLEAR PLASTIC PANEL METERS

First grade quality, Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type MR, 38P, 1 21/32in. square fronts.



100-0-100µA	27/6	200mA	22/6	100V D.C.	22/6
500-0-500µA	22/6	300mA	22/6	150V D.C.	22/6
1-0-1mA	22/6	500mA	22/6	300V D.C.	22/6
1mA	22/6	750mA	22/6	500V D.C.	22/6
2mA	22/6	1A D.C.	22/6	750V D.C.	22/6
5mA	22/6	2A D.C.	22/6	15V A.C.	22/6
10mA	22/6	5A D.C.	22/6	50V A.C.	22/6
20mA	22/6	3V D.C.	22/6	150V A.C.	22/6
50µA	32/6	50mA	22/6	300V A.C.	22/6
100µA	29/6	100mA	22/6	500V A.C.	22/6
200µA	27/6	150mA	22/6	50V D.C.	22/6
500µA	25/-				
50-0-50µA	29/6				


POST EXTRA. Larger sizes available—send for lists.

### R209 MK. II COMMUNICATION RECEIVER

11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s. on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O. Aerial trimmer, internal speaker and 12 v. D.C. internal power supply. Supplied in excellent condition, fully tested and checked. £22/10/0. Carr. 20/-.



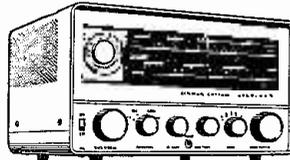
### LAFAYETTE HA-63 COMMUNICATION RECEIVER



Outstanding value. High-class 4 band receiver covering 550kc/s-31 Mc/s. Seven valves plus rectifier, RF stage, illuminated "S" meter, 1.5µV sensitivity. Electrical bandwidth on 80/40/20/15 and 10 metre bands. Slide rule dial, aerial trimmer. B.F.O., ANL, Output for phones or speaker. 115/220/240V. A.C. Brand new, guaranteed, with manual. 24 Gns. Carr. 10/-.
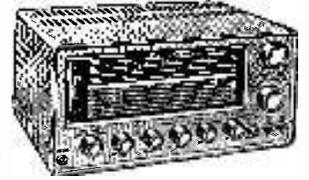
### LAFAYETTE KT-340 COMMUNICATION RECEIVER SEMI-KIT

Build this wonderful receiver and save pounds. Supplied semi completed, main components ready mounted, R.F. section already wired and aligned. Full and precise instructions supplied. Specification:— 8 valves+rectifier, 4 bands covering 550 kc/s-30 Mc/s. Incorporates 1 R.F. and 2 I.F. stages, 'Q' multiplier, B.F.O., A.N.L., 'S' meter, bandspread, aerial trimmer etc. Operation 115/230 V. A.C. Price 25 Gns. Carr. 10/-.




### HAM-1, 4 BAND COMMUNICATION RECEIVER



4 wavebands covering 535 kc/s. to 30 Mc/s. 5 valve superhet circuit. Incorporates S meter B.F.O., BANDSPREAD TUNING, BUILT-IN 4in. SPEAKER, FERRITE AERIAL AND EXTERNAL TELESCOPIC AERIAL. Operation 220/240 v. A.C. Supplied brand new with handbook. £16.16.0. Carr. 10/-.
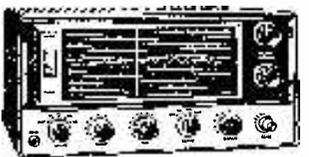
### NEW LAFAYETTE MODEL HA-700 AM/CW/SSB AMATEUR COMMUNICATION RECEIVER


8 valves, 5 bands incorporating 2 MECHANICAL FILTERS for exceptional selectivity and sensitivity. Frequency coverage on 5 bands 150-400 kc/s., 550-1,600 kc/s., 1.6-4.0 Mc/s., 4.8-14.5 Mc/s. 10.5-30 Mc/s. Circuit incorporates R.F. stage, aerial trimmer, noise limiter, B.F.O., product detector, electrical bandspread, S meter, slide rule dial. Output for phones, low to 2KΩ or speaker 4 or 8 ohms. Operation 220/240 volt A.C. Size 7in. x 15in. x 10in. Supplied brand new and guaranteed with handbook. 36 GNS. Carr. 10/- S.A.E. for leaflet.


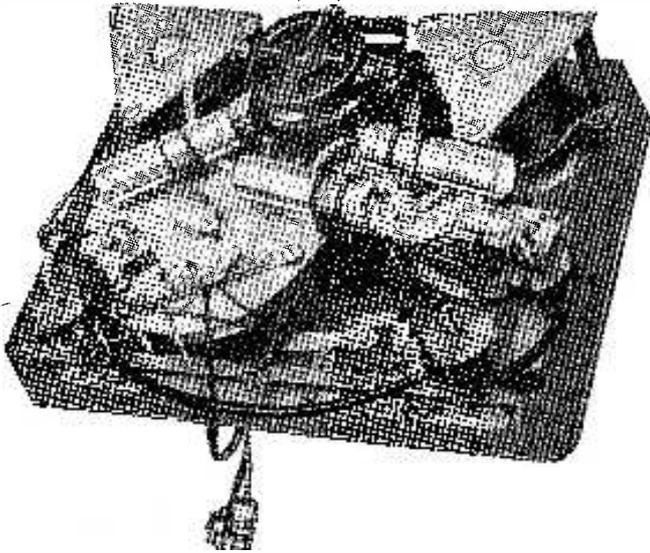
# G.W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155  
 Cables: SMITHEX LESQUARE  
 3-34 LISLE STREET, LONDON, W.C.2

Building first-class  
high fidelity  
equipment ?




## —then choose the superb Brenell Tape Deck

This is the deck for the demanding amateur and professional alike. 4 speeds, of course. 3 outer-rotor motors. Provision for 4 heads; unique, reliable braking system—instant stop without spillage. Pause control, superimpose switch, 1,200ft. per minute rewind. Reels up to 8 $\frac{1}{4}$ in. diameter. And the superb Brenell engineering in every detail.

A deck, in fact, to match the best in high fidelity electronics. **Prices from £38.**

See and hear them at the Audio Fair, London and the Brenell Mono/Stereo Hi-Fi Tape Link

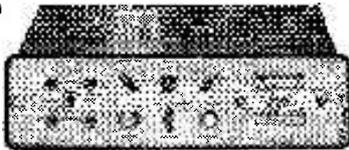A top-quality twin recording amplifier and twin playback preamplifier unit with A/B switching facilities. Ideal for use with the Brenell deck. **Price £46.** For technical specifications write to Brenell Publications Dept., Reference PW/5.




**BRENELL ENGINEERING CO. LTD.**  
231/5 LIVERPOOL ROAD, LONDON N.1. NOR8271 (5 lines)

# Household Heating Supplies LTD brings central heating price down

*you save £150 on  
D.I.Y installations!*

**OIL —  
GAS —  
SOLID FUEL**

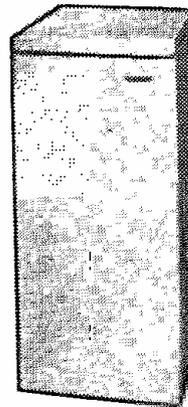

*Powell Duffryn  
G45 Gas Boiler*

You can do better than buy Central Heating at "frozen" prices—you can save at least £150 by doing-it-yourself—and you get FREE advice before and during installation.

Free delivery to your home. **NO DEPOSIT—5 YEARS TO PAY.** Branches at Croydon, Wood Green, Tottenham, Bedford, Manchester and Leicester.



To: Household Heating Supplies Ltd.  
7 Ilford Lane, Ilford. Essex ILF 5098/9  
Please send further details.

Name .....

Address .....

Telephone ..... P.W.5.67

# Why

## NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

FIRST FOR PERFORMANCE, QUALITY & PRICE!

BACKED BY OUR SUPER AFTER SALES SERVICE

"A wonderful range of transistor radios using first grade components guaranteed results."

### NEW ROAMER SEVEN Mk IV

7 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification ● Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS

FULLY TUNABLE ON ALL WAVEBANDS ● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned 7 x 4in. speaker. Air spaced ganged tuning condenser, Ferrite rod aerial for M. & L. Waves and telescopic aerial for S. Waves. Real leather-look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx.


The perfect portable and the ideal car radio. (Uses PP7 batteries, available anywhere.)

● EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, etc.

Total cost of parts now only


£5.19.6

P. & P. 5/6

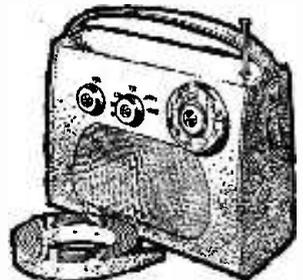

Parts Price List and easy build plans 3/- (Free with kit)

### NEW MELODY MAKER SIX

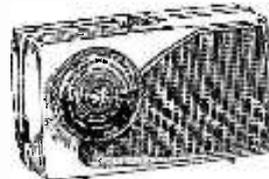


★ 8 stages. Six transistors and two diodes. Covers Medium and Long Waves and Extra Band for EASIER tuning of LUXEMBOURG etc. Top grade 3in. Loud-speaker for quality output. Two R.F. stages for extra boost. High Q 6in. Ferrite Rod Aerial. Approx. 350 Milliwatts push pull output. Handsome pocket size case with gilt fittings. Size 6 1/2 x 3 1/2 x 1 1/2. (Uses long-life PP6 battery). Carrying strap 1/6 extra.

This amazing receiver may be built for only

£3.9.6

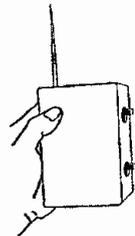P. & P. 3/6. Parts price list and easy build plans 2/- (Free with kit)



**QUICK CHECK TRANSISTOR TESTER.** Checks gain of R.F. and Audio Transistors. Also checks for noise level and duds. All parts ready to be assembled in attractive grey case with red grille, complete with Dial, Knobs, and Dynamic Speaker. Simple assembly instructions free with set of parts. 29/6, P. & P. 2/6.



**THE SIG-GEN.** A versatile Signal Injector. Something no constructor should be without. The ingenious device generates an audible signal through the Audio and R.F. ranges. With variable output. Telescopic Probe. Pocket size slim line case measures 4 1/2 x 3 1/2 x 1/2 in. Complete set of parts with full instructions. 19/6, P. & P. 2/-.

### NEW TRANSONA FIVE

Now with 3in. Speaker!

"Home, Light, A.F.N., Lux. all at good volume." G.P., Durham.

● 7 stages—5 transistors and 2 diodes


Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser volume control, new type fine tone super

dynamic 3in. speaker, etc. Attractive case. Size 6 1/2 x 4 1/2 x 1 1/2 in. with red speaker grille. (Uses 1289 battery, available anywhere.)

Total cost of all parts now only

42/6

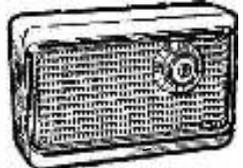P. & P. 3/6. Parts Price List and easy build plans 2/- (Free with kit)



### POCKET FIVE Now with 3in. Speaker!

● 7 stages—5 transistors & 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 3in. moving coil speaker, built into attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2 in. (Uses 1289 battery available anywhere.)

Total cost of all parts now only

42/6

P. & P. 3/6

Parts Price List and easy build plans 1/6 (Free with kit)



STOP PRESS!  
Pocket 5 med. and long wave version with miniature speaker.

29/6

P. & P. 3/-

### NEW ROAMER SIX

NOW, WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND !!

● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long Waves, Trawler Band and two Short Waves. Sensitive Ferrite rod aerial and tele-

scopic aerial for short waves. Top grade transistors. 3in. speaker, handsome case with gilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2 in. (Carrying strap 1/6 extra.)

★ EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, ETC.

Total cost of all parts now only

£3.19.6

P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)



### TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade 3in. speaker makes listening a pleasure. Push-pull output. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere). Carrying strap 1/- extra.

Total cost of all parts now only

59/6

P. & P. 3/6

Parts Price List and easy build plans 1/6 (Free with kit)



### MELODY SIX

● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering Medium and Long Waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. Ferrite rod aerial. Push-pull output. Wonderful reception of BBC, Home and Light, 208 and many Continental stations. Hand-


some leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2 in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

Total cost of all parts now only

£3.9.6

P. & P. 3/6

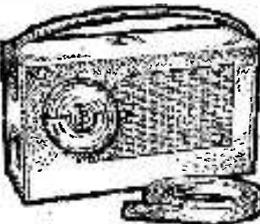Parts Price List and easy build plans 2/- (Free with kit)



### SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 R.F. Stages, push-pull output, 3in. speaker (will drive large speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses 9V battery, available anywhere.)

Total cost of all parts now only

£3.19.6

P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)



Callers side entrance Barratts Shoe Shop.

# RADIO EXCHANGE CO.

Open 9—5 p.m. Saturday 9—12-30 p.m.


61 HIGH STREET, BEDFORD Telephone: Bedford 52367

# LOOK!

**PRACTICAL!**

**VISUAL!**

**EXCITING!**

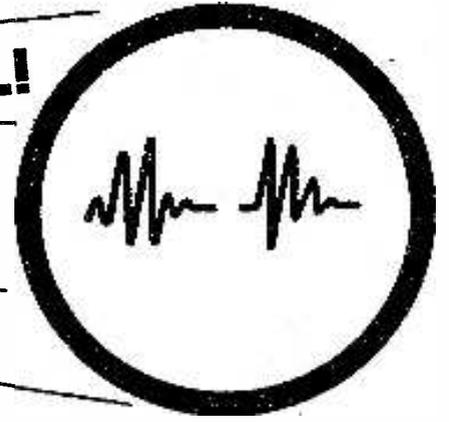


*a new 4-way method of mastering*

# ELECTRONICS

*by doing — and — seeing . . .*

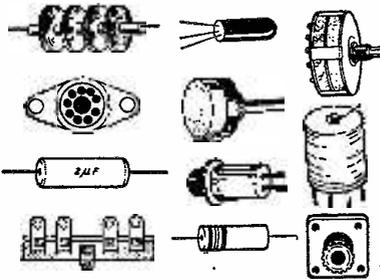
## 1 ▶ OWN and HANDLE a

complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



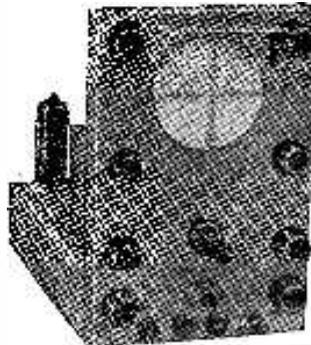
## 2 ▶ BUILD and USE

a modern and professional **CATHODE RAY OSCILLOSCOPE**



## 3 ▶ READ and DRAW and

**UNDERSTAND** **CIRCUIT DIAGRAMS**

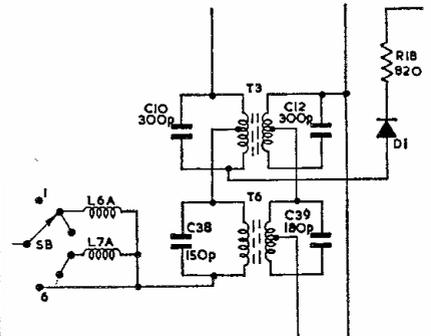

## 4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME ..... BLOCK CAPS

ADDRESS..... PLEASE PW5

# PRACTICAL WIRELESS

VOL 43 No 1

issue 723

MAY 1967

## TOPIC OF THE MONTH

### *Kitmanship*

OUR contributor Henry certainly touched an exposed nerve with his essay *To Kit or Not* in the March issue. The resulting correspondence, coupled with our own experience, indicates that a few of the kits currently being offered are shoddy affairs.

Principally kits are for the beginner and as such they must be easy to assemble and contain clear and concise assembly instructions. In fact some would tax the ingenuity of "advanced" constructors. Common complaints include wrong value resistors, faulty or sub-standard components, incorrect assemblage of components, misleading instructions, and so on. Substitute components also cause the home constructor a lot of trouble, particularly coils where the connections differ from the accompanying instructions. Identification problems are not, however, confined to coils, for we have had our attention drawn to unmarked resistors, capacitors, transistors and so on.

We know of one kit in which there were *fourteen* mistakes in the accompanying instructions. This is not good enough and must be stopped!

The gloom continues with the disquieting reports of abuses in "after-sales service" facilities which, if our informants are correct, are no more than rackets. Don't get us wrong, they are not all bad, but remember the old phrase *Caveat Emptor*—let the buyer beware.

It appears that the buyer of the more expensive kits gets the better deal, but this is no excuse for some of the rubbish we have heard of and seen. Even the cheapest kit of parts should be intact, and complete with easy-to-follow instructions. Often it is the youngster who buys these. He may have had to save weeks of pocket money to get one of these. It is a tragedy if he ends up with a heap of useless parts.

We strongly condemn sharp practice and will do our best to stamp it out. Any reader with a genuine complaint about goods or services from any *Wireless* advertiser, should send us clear and concise details. We will take up his case with the company concerned. Readers should, however, bear in mind that some of the "mail order" concerns handle very large quantities of kits and occasional packaging errors and delays are inevitable.

W. N. STEVENS—*Editor*

## NEWS AND COMMENT

Leader	17
News and Comment	18, 44
Practically Wireless <i>by Henry</i>	27
On the Short Waves <i>by John Guttridge and David Gibson, G3JDG</i>	28
New Books	32
The MW Column <i>by Alistair Woodland</i>	58

## CONSTRUCTIONAL

Multipurpose Audio Switch <i>by F. L. Thurston</i>	20
70cm Converter <i>by J. P. Billingham, G8AAC</i>	23
Beginner's 3-band Mains Receiver <i>by A. S. Carpenter</i>	40
A Simple Analogue Computer <i>by C. R. Bradley</i>	53
Add-on 500mW Amplifier <i>by Mike Fisher</i>	61

## GENERAL ARTICLES

Repairing Radio Sets, Part II <i>by H. W. Hellyer</i>	34
R/C Circuits with Gain <i>by K. T. Wilson</i>	46
Improving Cheap Tape Recorders, Part II <i>by W. S. Fowler, M.A.</i>	49

JUNE ISSUE WILL BE PUBLISHED ON MAY 5th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes London, W.C.2. Subscription rates, including postage: 36s. per year to any part of the world. © George Newnes Ltd., 1967. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

## Kits and Henry

I read with interest Henry's commentary about Kits in the March issue of PRACTICAL WIRELESS. A few months ago, I bought a kit from a firm who advertise in this magazine. It arrived short of the carrying strap and with a tuning dial the wrong size and with the scale reading in the wrong direction. The circuit diagram contradicted the instructions and the paxolin board on which the works were soldered, had to be wedged with cardboard. A short time later, I sent for another receiver from the same firm. This one was much worse! The parts were soldered to tag strips which were glued to a piece of cardboard. There was apparently no method of holding the battery still in the case and the back flew off the set at the slightest provocation. It has never worked and a letter to the firm concerned proved to be a waste of fourpence.

H. Boys.

Walsall,  
Staffordshire.

★ ★ ★

Henry's comments are only too true. I am a constructor of some experience and have built many sets for friends. I would hate to think of a newcomer tackling one of these kits for the first time—some of which, the firms claim, can be built in a matter of hours.

One more grouse I have is about so-called postage charges. You are charged say, 7s. 6d. and when the parcel arrives, it has stamps on it to the value of 3s. 6d.! The same is for valves. In some adverts, the postage charge is 6d. per valve, so if you order six valves, the postage charge is 3s. Why, then, when the package does arrive, does it have stamps to the value of 8d. on it?

A. H. Brough.

Leek,  
Staffordshire.

★ ★ ★

I agree with every word Henry says in "To Kit or Not". As a science teacher I had been approached by various pupils as to possible reasons why their kits did not work. This made me curious, so I sent away for a kit myself. The result was precisely the same as Henry's, with the final result that I returned it, paid the £1 fee, received a further demand for a further 15s., which being duly paid, brought back the chassis—but only working on one band! I wrote a letter to the firm saying that the so-called changes weren't made (I can recognise my own work) and that the so-called defective parts were their responsibility, seeing that they were selling the kit. This brought no reply at all!

C. Miller.

Maidstone,  
Kent.

# NEWS AND..

## VARIABLE CAPACITORS FOR PRINTED CIRCUITS AND VHF



Type CG80-01 is a miniature three-section, ganged capacitor designed for v.h.f. receivers. Each section has a capacity of from 2.5pF to 17pF. An internal gear and pinion drive gives a 3:1 reduction. High-grade ceramic posts insulate the stator from the frame, and the capacitor is 1.5in. long, 0.65in. wide and 0.85in. high overall.



Type S60-01, piston-type trimmer has an overall diameter of 0.25in. with 0.2in. fixing centres and is variable from 2pF to 25pF by means of a screwdriver slot in the rotor. It has a polystyrene dielectric, but for operation in extremes of temperature, a P.T.F.E. dielectric can be supplied. Wingrove and Rogers Ltd., Domville Road, Mill Lane, Liverpool 13.

## A.A. RADIO AT IDEAL HOME

The A.A. Linkline radiotelephone service (see News and Comment, page 732, February 1967 issue) was one of the main features of the Automobile Association's display at the Ideal Home Exhibition.

Direct contact between Olympia and the Linkline control centre at the A.A.'s Leicester Square headquarters was maintained and visitors to the A.A. stand were able to talk over the air and also listen to traffic information broadcasts and other messages being transmitted to Linkline users.

## 144th "COSMOS" SPUTNIK

The Soviet Union recently launched its 144th scientific earth satellite. Cosmos-144 was placed in a circular orbit at a distance from the earth's surface of 388 miles. In addition to scientific equipment the sputnik has a radio system for the accurate measurement of orbital elements and a radio telemetric system for transmitting data to earth concerning the function of instruments and apparatus.

## CURB ON LICENCE DODGERS

Under the terms of a Government Bill aimed at licence dodgers, published recently, TV dealers will be compelled to let the GPO know the names of customers buying or hiring sets.

It is estimated that the BBC loses £10M annually through people not obtaining licences.

Applicants for Road Fund Licences will also have to state whether or not their cars are fitted with radios.

Also under this Bill, the PMG Mr. Edward Short, will be able to prohibit the import or manufacture of certain wireless telegraphy apparatus, which, it is understood will include imported walkie-talkies and similar apparatus.

It is understood that dealers who do not comply with the requirement to furnish lists of purchasers will be liable to fines.

# ... COMMENT

## LOCAL RADIO IN THE NORTH AND MIDLANDS

The first three sites chosen for the BBC's experimental radio stations are at Leicester, Merseyside and Sheffield stated the Postmaster General recently. Merseyside includes Liverpool, Birkenhead and Wallasey. All stations will transmit on v.h.f. and have a range of 12 miles. They are expected to be on the air by the end of this year.

The BBC will build the stations at a cost of about £35,000 each and each station will have a staff of about 15. Running costs will be in the region of £1,000 per week.

Local output will be about four hours a day and will cover news, current affairs, local information and request programmes. After a transmission from his own studio, a station manager will then be able to switch over to one of the main BBC networks.

## ELECTRONICS PULL ASIDE IRON CURTAIN


Three years of negotiations have resulted in Plessey signing a 5-year agreement with Russia for the exchange of specialised knowledge and joint co-operation in the field of electronic equipment and components and automation.

Signed in Moscow recently with the Soviet State Committee for Science and Technology, the agreement is hoped to result in firm business within the next few months. Plessey will offer licensing agreements to the Russians and expect to be licensed for the sale of Soviet developments all over the world.

## ULTRASONICS HELP THE DOCTORS

The sound-visor, an instrument which transforms a reflected sound signal into a picture, making it possible to see in detail objects only a few tenths of a millimetre in size concealed in a mass of absolutely non-transparent substances, has been developed at the Institute of Acoustics of the USSR Academy of Sciences. The instrument is 200 times as sensitive as an X-ray machine in studying the human body. X-rays make it possible to discern the bone from the muscle but they cannot discern a tumour from a muscle. Scientists hope that tumours will be detected by the sound-visor.

## AVON BOOKSHELF SPEAKER

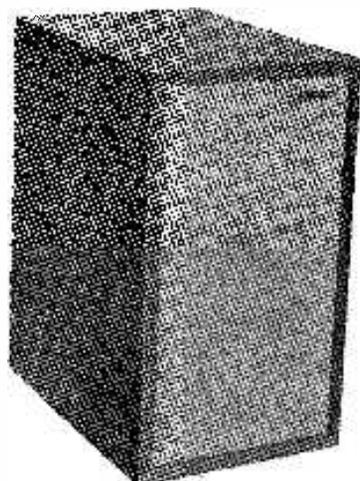

*Frequency response: 50c/s-19kc/s.  
Crossover frequency: 2kc/s.  
Power rating: 9W r.m.s. max.  
Nominal impedance: 15Ω.  
Speakers: 6½in. bass, 1⅜in. totally enclosed treble.  
Cabinet dimensions: 7½ x 13¼ x 8½in.  
Cabinet material: 12mm. high grade plywood with 1⅜in. aluminium alloy speaker mounting plate.  
Finish: Walnut veneer.  
Cross-over: Inductor-capacitor type.  
The walnut veneered cabinet kit costs £8 18s., and the loudspeakers and cross-over network kit cost £4 18s. Daystrom Ltd., Gloucester.*

## Phonetics and RAE

Mr. Haagensen may be glad to know that those who sat the Radio Amateurs' Examination in December, 1966, were confronted by this question: "How may the letters of the call sign be confirmed by radio-telephony? Give six examples of the recommended phonetic alphabet".

I might add that I have heard Czechoslovakia, Canada, America, Iceland, Sweden, Holland and many other countries in contact with British Amateurs, who varied their phonetical alphabet confirmations, and none of these countries seemed disturbed. Furthermore, the foreign countries varied their phonetical confirmations and I was able to comprehend all the callsigns.

All these countries were heard on 80m., using a 19 set and phones with a 67ft. long wire running 20 ft. from the ground NE SW. I can only suggest that Mr. Haagensen is slightly hard of hearing.

A. Barroclough.

Rotherham,  
Yorkshire.

★ ★ ★

I wonder how many Radio Hams Mr. Haagensen actually listened to? Surely he realises that there are many thousands of Hams who are active all over the world, all hours of the day and night, so how can he possibly judge all just by a few? I am not entirely in agreement with the NATO phonetic alphabet and I know it inside out, being a RAF Wireless Op and it is fine only if conditions are suited.

I was operating 5B4PC from 1962-65 and at time static was so bad that the NATO phonetics were truly useless. Here is an example of what I mean: Germany, Washington, Three, Santiago, Bravo, Ontario for the callsign GW3SBO is much clearer and understandable in the hissing static than Golf, Whiskey, 3, Sierra, Bravo, Oscar. There are many hams who agree with me—especially those who have missed the hissing Sierra or Oscar in a burst of static.

If I pass the RAE this year, I shall use phonetics which best suit the conditions I work under, until the NATO phonetic alphabet becomes compulsory.

W. F. Wright.

Sleaford,  
Lincolnshire.

## FILMSHOW TICKETS

Applications for Filmshow tickets—which are free—should be made to: Filmshow, Practical Wireless, Tower House, Southampton Street, London, W.C.2. A stamped addressed envelope must be included with all applications. See page 57.

More News and Comment on Page 44

# MULTIPURPOSE

# AUDIO SWITCH



F.L. THURSTON

Sound-operated switches are extremely useful devices and can be used in many applications, from saving tape (and thus extending the playing time) in recording machines . . . to burglar alarms. The multipurpose switch described in this article is quite sensitive and will operate—at normal conversation levels—at distances up to 30 feet.

One of the difficulties in designing a sound-operated switch with a high sensitivity hinges on the fact that long microphone leads are almost inevitable. Also, the microphone (which in the author's case is a low impedance loudspeaker) has to be matched into the amplifier section of the switch. A microphone transformer can be used for this, but with reservations. For example, if the "switch" is powered from the mains, pick-up by the microphone transformer from the mains transformer can cause the switch to be permanently "on". For this reason, another form of input matching was chosen: a grounded base transistor configuration, as shown in Fig. 1a. In this circuit, the input (from the "microphone") is fed directly into the emitter, with the base decoupled by C1. The emitter resistor can be omitted since a low impedance "microphone" is used as the pick-up. The other components in the circuit are included to give correct d.c. operating levels. Signal gain is approximately 100.

## Inter-stage Matching

Although the circuit shown in Fig. 1a has a reasonably high voltage gain, the problem comes when the gain has to be transferred to another stage. Should the following stage be a common

emitter amplifier, it will offer a fairly low impedance to the first stage: shown as  $R_z$  in Fig. 1a. As far as the signal is concerned,  $R_z$  is effectively in parallel with  $R_1$  the collector load, reducing its ohmic value (to the signal) to about  $800\Omega$ . This reduces the stage gain to about 8. The way to overcome this is to use an emitter follower as an inter-stage buffer. This has quite a high input impedance and does not load  $R_z$ . Figure 1b shows an emitter follower connected to the original circuit.


The temperature stability of the two circuits so far described is not very good: both circuits having small emitter resistors. It can be improved by adding a negative d.c. feedback loop from the emitter of Tr2 to the top of the Tr1 base chain—as shown in Fig. 1c. If the total resistance of  $R_3$ ,  $R_4$  is kept low, it can be made to serve as the emitter load of Tr2, making it possible to save in components without affecting the gain. The final development of this circuit is shown in Fig. 1d.

## Bootstrap Technique

One of the advantages of the emitter follower is that its output (which is taken from the emitter) is in the same phase and almost the same amplitude as the input signal applied to its base. The impedance levels are, of course, different.

Referring to Fig. 1d, note how the collector load of Tr1 is split into two parts.  $R_1$  forms the major load, while  $R_5$  acts as an "isolating" resistor, since the voltage appearing at the emitter of Tr2 approximates that at the collector of Tr1 and is fed back (via C2) to the junction  $R_1/R_5$ . Thus, similar a.c. signals appear at either end of  $R_1$ , and consequently only a small signal current flows through  $R_1$  when

Fig. 1: 'a' shows a simple grounded-base amplifier; 'b' the original circuit with an emitter-follower output; 'c' improved 'b' circuit with temperature compensation; 'd' the final development of this circuit.

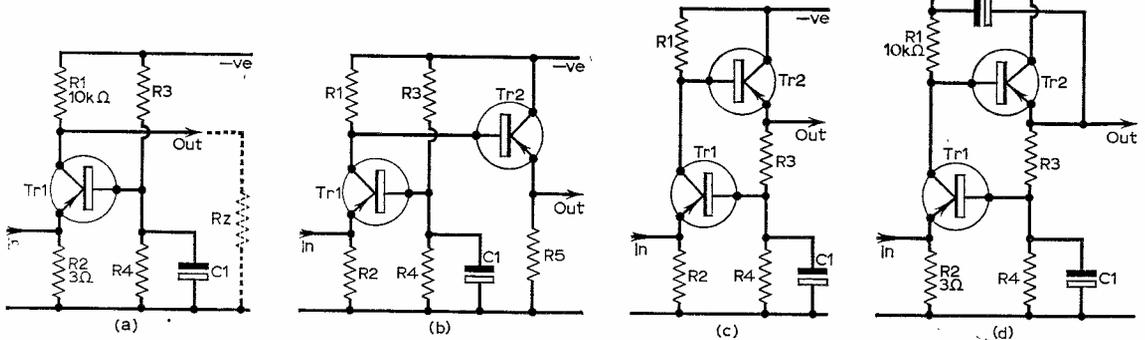

a given signal output is available. This enables the value of R1 to be increased by about ten times, hence, the 10kΩ looks like 100kΩ to a.c. signals and gives the circuit a voltage gain of the order of 500.

This method of increasing the ohmic value of R1 is known as Bootstrapping—it being analogous to the idea of a man lifting himself by his shoelaces. For this technique to work the signals appearing across R1 must come from isolated sources: putting a capacitor across R1 to isolate the ends will not work.

## Full Circuit

Looking at the full circuit diagram of the sound-operated switch, Fig. 2, you will see that Tr1 and Tr2 are wired in a similar fashion to the circuits in Fig. 1. The main collector load resistor being R2, with Bootstrapping being applied through R1, the "isolating" resistor. Potentiometer VR1 forms the major part of the emitter load and serves as a sensitivity control for the amplifier: R3 is simply a limiter and can be omitted if preferred.

The amplified signals appearing across the potentiometer are capacitively coupled by C3 into the base of Tr3, a conventional common emitter amplifier which further amplifies the signal. The output of this stage is rectified by D1/D2 (smoothed by C6/R9) and fed to a d.c. switching amplifier Tr4/Tr5. These two transistors are wired as a Super-Alpha pair and can be looked upon as an ultra-high-gain single transistor connected in a common emitter configuration. In the absence of an input

signal, no rectified or d.c. bias is available to the base of Tr4, so the combination transistor is cut-off. As soon as the bias condition changes (through the rectification of incoming signals) Tr4 is turned on. This shorts the base/collector junction of Tr5 and turns the transistor full on, energising the switching relay RLA. When the signal is removed, the transistors revert to their original condition.

The power requirements of the circuit are not critical, as the "switch" will function from a nine to twelve volt supply: either a battery or a mains power supply unit.

## Construction

All the components, excepting the "microphone" and the relay, are vertically mounted on a piece of Veroboard, which should be cut to the size (and the copper strips broken) in accordance with the information given in Fig. 3. Before assembly starts, it is as well to reduce the thickness of the mounting legs of the skeleton type potentiometer before trying to mount it, otherwise the "legs" will not go through the holes in the Veroboard. Remember to use heat shunts when soldering the semiconductors into circuit.

Once the Veroboard unit has been completed, check the circuitry, especially the electrolytic polarities, and check it again—a cross connection can easily cost a transistor. Now attach a "microphone", almost any three-ohm speaker will do, the relay and a power supply. The relay will probably operate when power is applied, but this is not important so long as it releases after a second or so.

## Circuit Modifications

The circuit shown in Fig. 2 switches off almost immediately the signal is removed. The unit can, however, be made to remain on for a few seconds after the input signal has been removed by increasing the value of C6. Should the constructor want the relay to be held on for a long time after the input signal is removed, a self-latching relay is needed. Fig. 4a

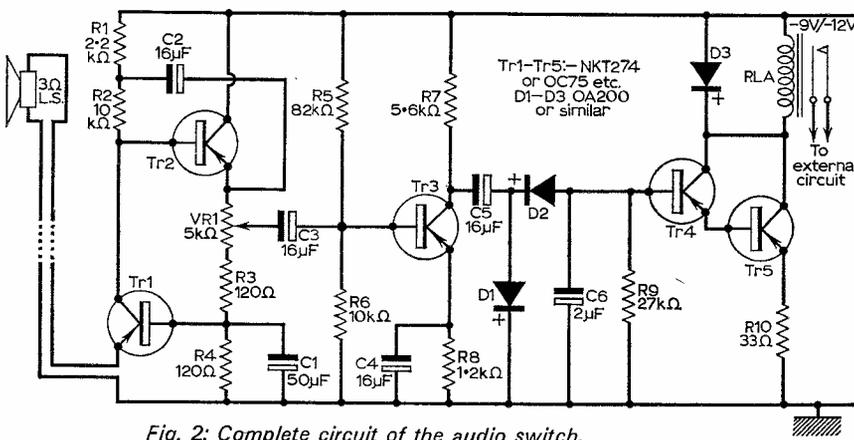


Fig. 2: Complete circuit of the audio switch.

shows that an additional pair of relay contacts are needed, which are normally open but, when the relay operates, close and connect the negative supply rail to the base of Tr4 (via Rx and S1). The exact value of Rx has to be found by trial and error: a good kicking-off point is 100kΩ. Switch S1 (a normally closed push-button type) is used to re-set the unit.

The basic audio switch can be operated from almost any a.c. signals, and in this context the "microphone" can be replaced by any low impedance transducer or pick-up. Thus, the unit can be activated by vibration, by changes in water pressure, changes in a magnetic field, and so on. Should the transducer or pick-up be a medium impedance device, the Tr1 and Tr2 circuitry should be replaced with a circuit identical to Tr3, except that the collector load should be replaced with a 5kΩ pre-set, which acts as a sensitivity control. A 1kΩ/16μF decoupling network should be wired in the negative supply lead between the two stages to prevent instability. It may be found that the sensitivity of the new circuitry does not match the former.

If the transducer or pick-up is a high impedance device (up to about 100kΩ) then Tr1 and Tr2 should be replaced by the circuit shown in Fig. 4b. In this circuit, Tr1 is wired as an emitter follower, with the input applied to its base and the output taken from the slider of the 5kΩ pre-set and fed into Tr2, a conventional common emitter amplifier. (The output from Tr2 collector is then fed on to C3 of Fig. 2.) Again a 1kΩ/16μF decoupling network is inserted to prevent instability. Should the transducer or pick-up be of ultra-high-impedance (1MΩ or greater), Tr1 and Tr2 should be replaced with the circuit shown in Fig. 4c, where Tr1 and Tr2 are wired as a Super-Alpha pair. Bootstrapping is applied to the base-bias network.

The "switch" may be built into existing equipment where it may, for example, be used to indicate the presence of a call signal at a receiver, or the presence of an input to a monitoring device. In

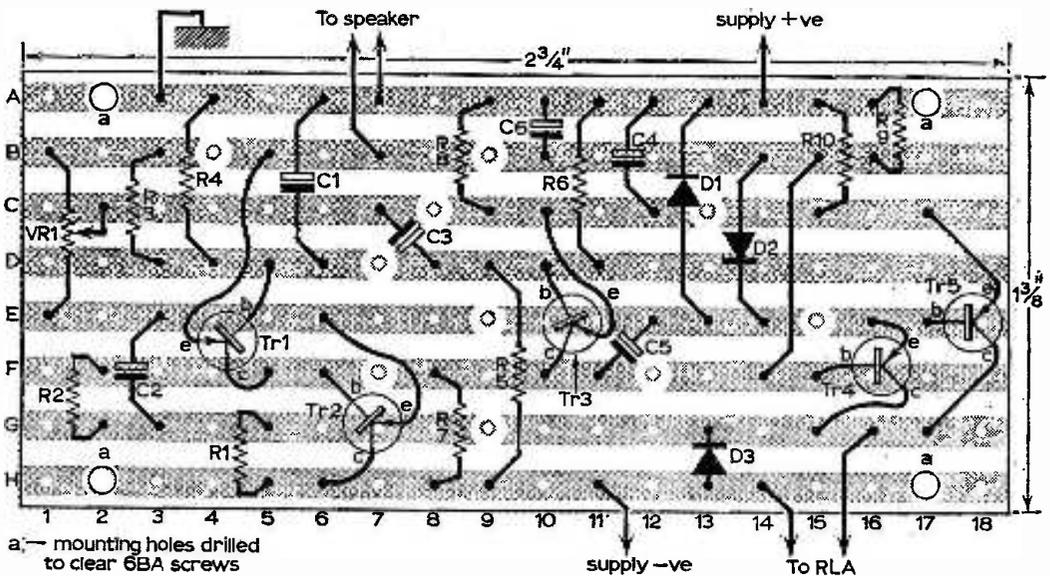


Fig 3: Layout and constructional diagram of the Veroboard panel.

these applications, if the "triggering" signal is of sufficient amplitude, the first three stages (Tr1 to Tr3) of the circuit can be omitted.

### ★ components list

#### Resistors:

R1	2.2kΩ	R6	10kΩ
R2	10kΩ	R7	5.6kΩ
R3	120Ω	R8	1.2kΩ
R4	120Ω	R9	27kΩ
R5	82kΩ	R10	33Ω

All 1/2W, 10% carbon  
VR1 5kΩ skeleton pre-set

#### Capacitors:

C1	50μF	C4	16μF
C2	16μF	C5	16μF
C3	16μF	C6	2μF

All sub-min. electrolytics 12VW, except C1 which may be 6VW.


#### Semiconductors:

Tr1 to Tr5 Newmarket NKT274, Mullard OC75 etc.  
D1, D2 Mullard 0A200, etc.

#### Miscellaneous:

Three-ohm loudspeaker; six-to-eight volt (600Ω or greater) relay; Veroboard, wiring, sleeving, etc.

Fig 4: 'a' shows a self-latching relay output for conditions where the switch must be held on after the activating signal is removed; 'b' a new input stage for use with high impedance inputs; 'c' a Super Alpha front end to cope with ultra-high impedance inputs.

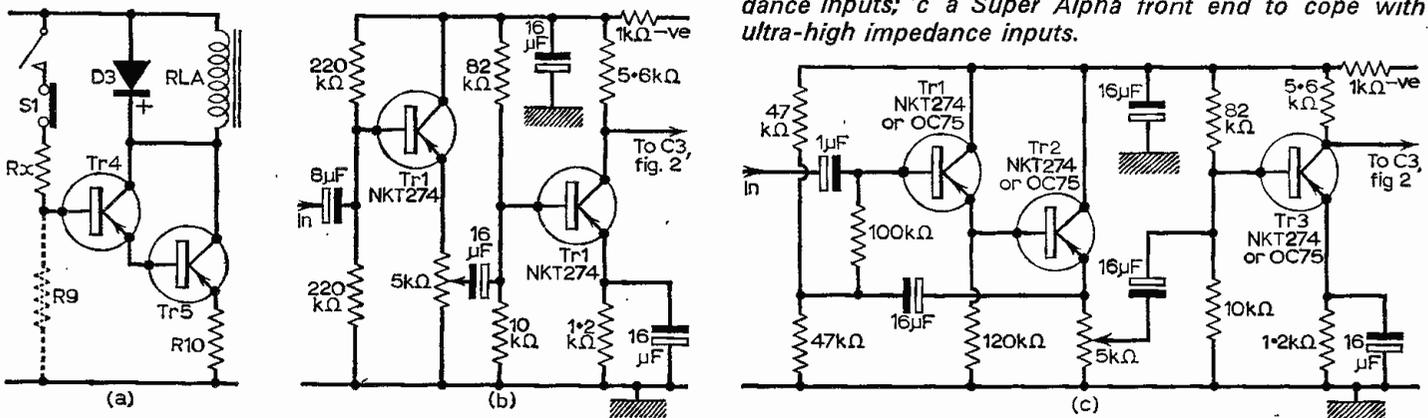


# 70cm converter

This three-valve, crystal-controlled, converter covers the frequency range 432 to 434Mc/s in the u.h.f. band and has an intermediate frequency output of 12 to 14Mc/s. This permits the converter to be used with almost any h.f. receiver, although a communications receiver is suggested for optimum results.

The converter does not have its own power supplies, however, if the main receiver cannot supply the necessary power for the three extra double-triode valves, a circuit for a stabilised p.s.u. is included in the article.

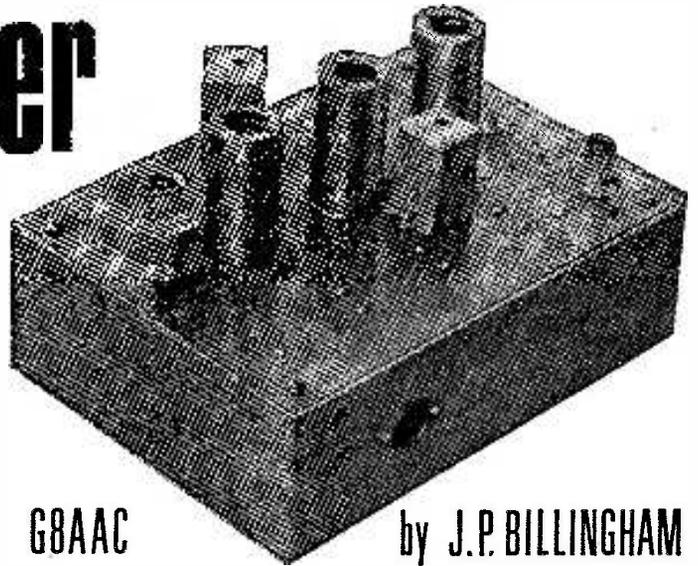Before describing the prototype, shown in Fig. 1, the author would like to point out, to more advanced readers, that a higher i.f. output is desir-



G8AAC

by J.P. BILLINGHAM

able, and suggests 22 to 25, 26 to 30Mc/s or even higher. Adopting a lower i.f. than used in the prototype will result in poor image rejection and a higher noise level.

## Circuit description

The input signal is taken directly to the input line L1 (tuned by TC1), which is connected to the grid of the first section of V1 — an E88CC double triode, operating as a cascode amplifier. This arrangement gives as much gain as a pentode stage, is just as stable, but is far less noisy. The amplified signal is coupled by C3 to the next tuned circuit L2, TC2 (the choke Ch2 provides adequate blocking to the r.f. signals). The r.f. amplifier is neutralised by Ch1, which has to be physically adjusted for optimum performance. If the choke has insufficient inductance, the stage will have a higher noise figure and may become unstable. Too much inductance will reduce the sensitivity of the converter.

The mixer stage of any converter is the most critical, for weak signals can be lost in a noisy mixer, and usually they are the most interesting. The traditional methods of mixing were investigated: multi-grid valves such as pentodes, hexodes, etc. were all ruled out by their high partition noise. Silicon diodes looked good at first sight with noise figures of 3 to 4dB, but

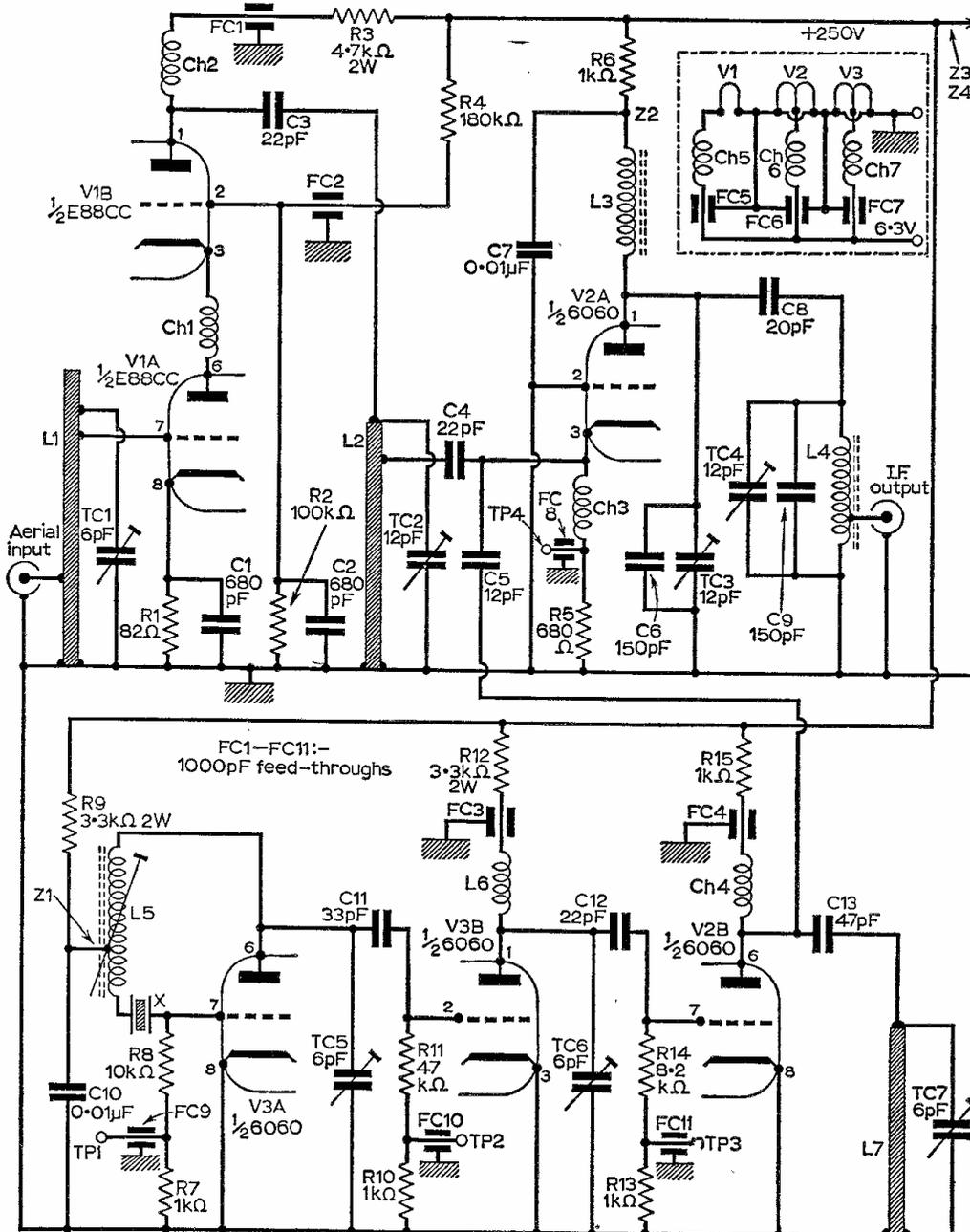


Fig. 1: Circuit diagram of the converter.

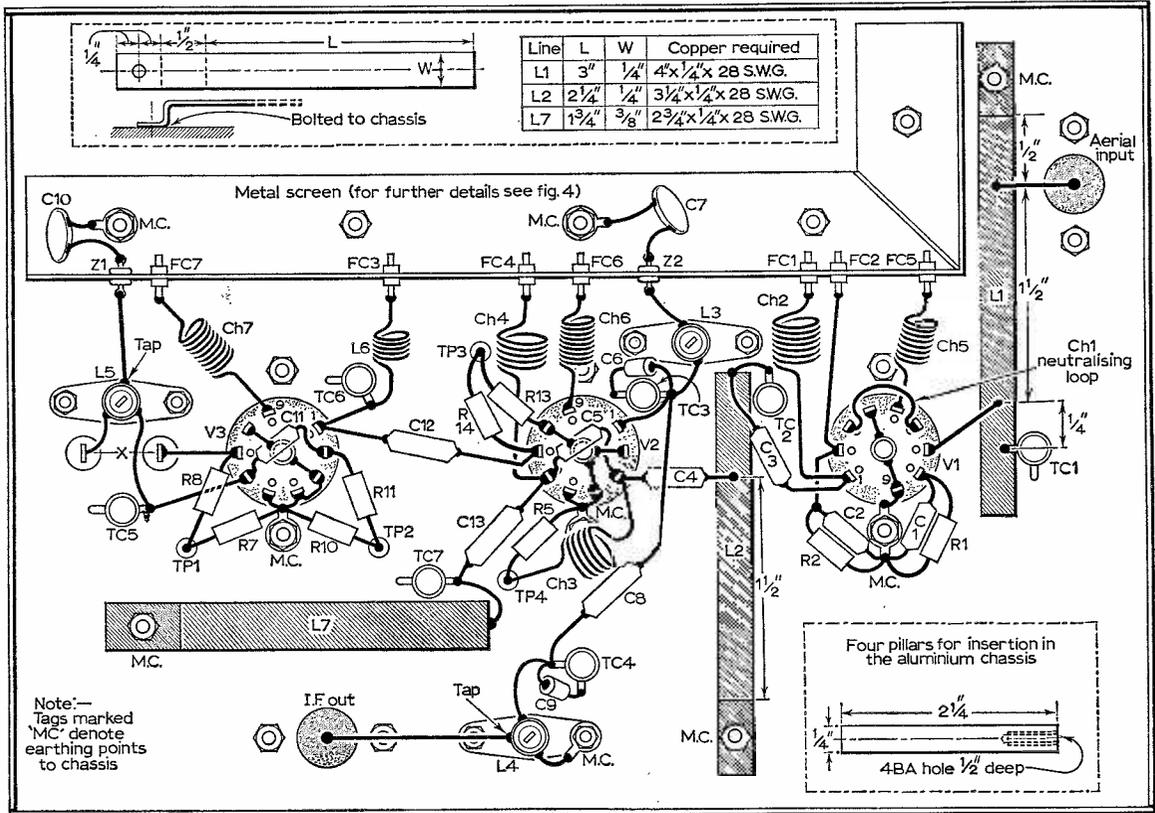


Fig. 2: Layout of the chassis—underside. Note: tapping points on the tuned lines are critical.

seemed less attractive when one considers they have a conversion loss of at least 6dB; thus, the signal to noise ratio is reduced by a minimum of 9dB, or nearly two S-points.

The grounded-grid triode was chosen as it provides a conversion gain and has only a slightly higher noise figure (6dB or more). Consulting the circuit diagram, it will be seen that the r.f. signal and local oscillator signals are capacitively coupled to the cathode of the mixer V2a by C4 and C5 respectively. The mixed signal is fed to a band-pass circuit which is broadly-tuned from 12 to 14Mc/s (L3, C6, TC3 coupled through C8 to L4, C9 and TC4). The i.f. output is taken from a low impedance tap on L4 to a 75Ω coaxial socket: the mixer current is monitored at TP4.

A crystal overtone frequency of 35Mc/s was chosen to keep the number of multiplier circuits to a minimum and to avoid TVI (television interference). The first link in this chain is a Squier overtone oscillator using V3a: the crystal is a miniature HC6/U, 35Mc/s third overtone. Coil L5 and TC5 form the resonant circuit for this stage; the ferrite slug for L5 determines the degree of feedback in the circuit, and TC5 permits the final tuning to be trimmed. Grid current is monitored at TP1.

The other half of V3 acts as a quadrupler, to raise the frequency to 140Mc/s—the anode of V3b is tuned by L6 and TC6, grid current is monitored at TP2. The final stage in the oscillator chain V2b trebles the frequency to 420Mc/s: the output is tuned by L7 and TC7, and grid current

is monitored at TP3.

A 12AT7 may be used in place of the 6060, but care must be taken as the input/output capacitances may differ, requiring adjustment of the tuned circuits.

### Construction

It is essential that all joints should be cleaned and that all the components should be mounted as rigidly as possible. Valve bases, lines, trimmers and so on should be soldered to the chassis. A 65-watt soldering iron is essential for this operation. However, as some constructors may not have a large iron, provisions have been made in the design for bolting components to the chassis—even feed-through capacitors.

Constructors may find it easier to fix all the bolt-on or solder-on components to the chassis before beginning wiring-up operations. When wiring-up, start with the oscillator chain, checking each stage before moving on to the next. Earth connections to the bases should be the first to be completed, followed by the components nearest the chassis.

So long as all the tuned circuits are constructed as suggested, only one resonance can be obtained for each of the tuned circuits in the oscillator chain. To align the first tuned circuit, pull the core of L5 out so it is flush with the base of the coil and adjust TC5 for maximum (negative) voltage on TP1—rising from a few millivolts to a few volts. The voltage on TP2 should also reach a similar level. Trimming capacitor TC6 is adjusted for

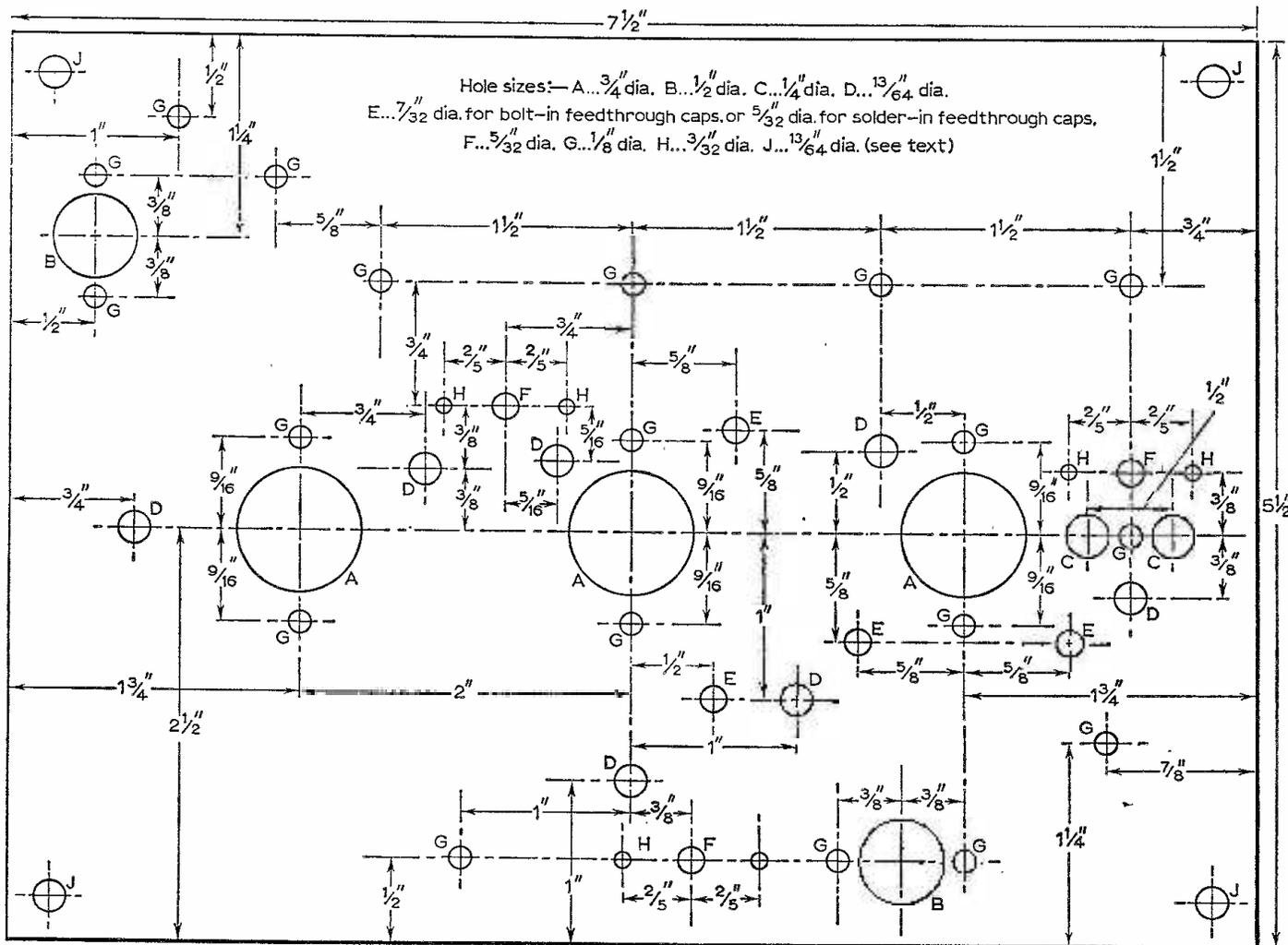


Fig. 3: Chassis drilling details (viewed from above).

maximum (negative) voltage at TP3. The 420Mc/s circuit is of sufficiently low "Q" to allow output over any part of the range of TC7.

The next step is to tune the i.f. output stage. To do this, one must hook the converter to a suitable receiver. The cores of L3 and L4 affect the "Q" of the circuits and trimmers TC3 and TC4 shift the frequency. The i.f. stage is correctly set when

converter noise can be heard throughout the 12 to 14Mc/s range on the main receiver.

Finally, the r.f. circuits should be tuned. Ideally this should be done with the aid of a locally generated signal. At first, the signal may have to be injected directly into the aerial socket, but as adjustments progress, stray radiations should be detected with little difficulty from a signal source some feet away.

Constructors living in the London area will find the beacon GB3GEC, located in Hammersmith and radiating several hundreds of watts on 431.5Mc/s, useful in setting up this converter.

If a u.h.f. source is not available, the r.f. circuits will have to be tuned to peak up on noise. This is quite difficult especially when two circuits have to be tuned. Harmonics from a lower frequency oscillator can be tuned quite easily.

Final adjustments can now be made, peaking up the r.f. and oscillator circuits. By now input signals


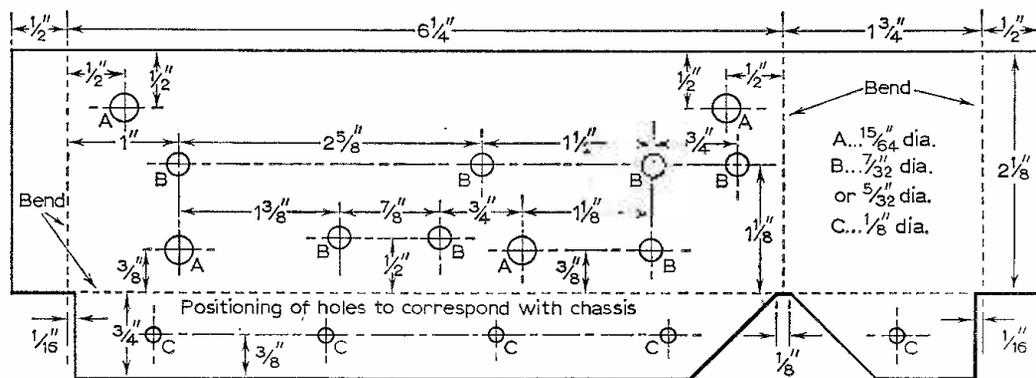


Fig. 4: Drilling and layout details for the screen panel.

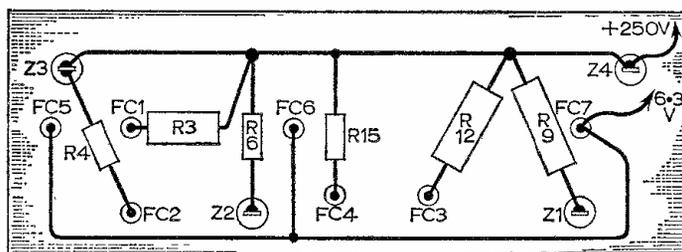

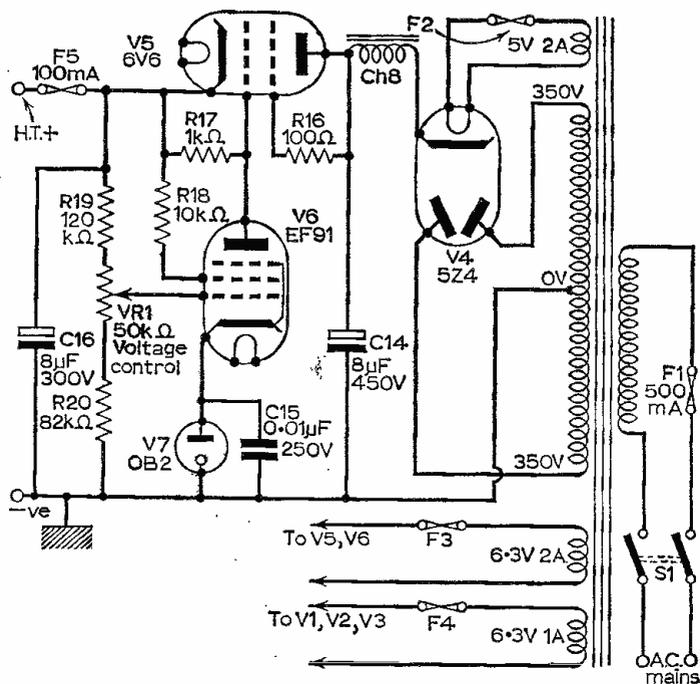


Fig. 5: Stabilised 250V power supply circuit suitable for the 70cm converter.

of 0.1μV should be readable.

One of the problems of using a converter is breakthrough, as it is difficult—to start with—to distinguish between u.h.f. and any signals being picked up by the aerial circuits of the main receiver. The best way to tackle i.f. breakthrough is to mount the converter and the main receiver (and power supplies if separate) all in a single metal cabinet. Connecting leads should be kept as short as possible, and all the equipment should be adequately earthed. An additional safeguard is to filter the power supplies.

An unstable r.f. stage and too much output from the local oscillator are the two most probable causes of instability. The cure for unstable r.f.

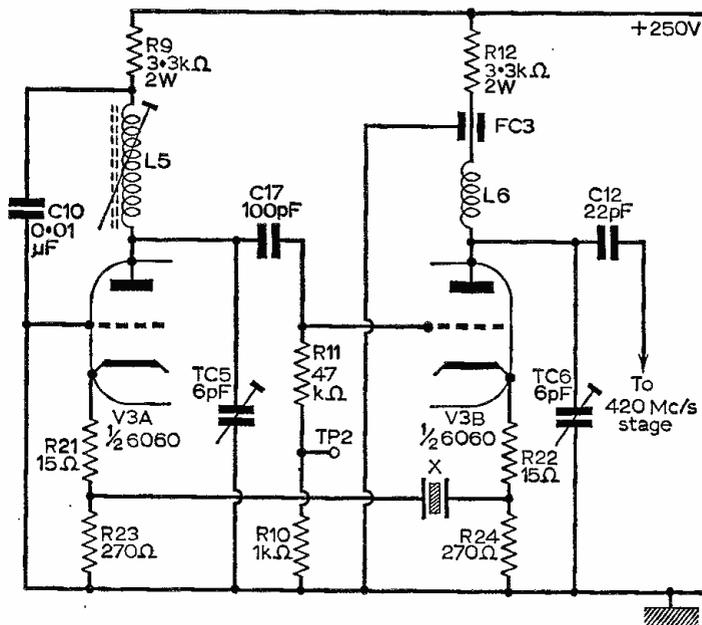


Fig. 6: Butler overtone oscillator. This circuit may well be an improvement on the existing oscillator, although the author has yet to try it.

stages is dealt with earlier in this article. The cure for the latter is to slightly detune either the 420Mc/s or the 140Mc/s oscillator stages. Another problem one may encounter is that of the received signal suffering a long period of oscillation, of the order of one cycle per second or so. This is cured by slightly reducing the capacitance of TC5 and then retuning the main receiver.

Table 1: Test Point Voltages

TP1	-0.5 to -2V
TP2	-0.5 to -2V
TP3	-0.5 to -2V
TP4	+4V rising to +4.5V with very strong signals.

### Future developments

An improvement over the prototype can be effected by mounting the i.f. coils above the chassis and using screening cans. Further modifications are being considered by the author, including the use of a Butler oscillator (see Fig. 6) which may improve the frequency stability. A better signal to noise ratio may be achieved by replacing the E88CC grounded-grid amplifier with an EC88, but this may entail additional underchassis screening.

### Practical Wireless Binders

A first class magazine deserves first class treatment. Store your copies of *Practical Wireless* with a new Easi-binder, specially designed to hold 12 copies of the new large size. It has a special pocket for storing those blueprints and data sheets too. Yours for 14s. 6d. from: Binding Dept., George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

Note. Please state the volume number required otherwise a blank cover will be sent.

#### Miscellaneous Items

- Chassis measuring 7½ x 5½ x 2½ in.
- Copper sheet 16 s.w.g. measuring 7½ x 5½ in.
- Copper sheet 20 s.w.g. measuring 9 x 2⅞ in.
- Copper sheet for L1, L2 and L7 (see Fig. 2).
- Skirted ceramic base for V3 and two p.t.f.e. bases for V1 and V2.

#### Coil Data:

- L3, ten turns of 30 s.w.g.
- L4, as L3, but tapped two turns from earthy end.
- L5, 19 turns 30 s.w.g., tapped four turns from crystal end.
- L6, five turns 22 s.w.g. airspaced ¼ in. diameter.

Note: L3-L5 are wound on Radiospares ¼ in. formers (Type 'A' cores are used.)

#### Chokes:

- Ch1, neutralising loop.
- Ch2, 4, nine inches of 22 s.w.g. wound ⅜ in. diameter, leaving ½ in. ends.
- Ch3, as Ch2, but using 12 in. of 22 s.w.g.
- Ch5, 7, as Ch2, but ¼ in. diameter.

#### Trimmers:

- TC1, 5, 6, 7 Mullard COOAEA/6E, 6pF.
- TC2, 3, 4 Mullard COOAEA/12E, 12pF.

# practically wireless

commentary by **HENRY**

**I**N my daily paper, not so long ago, I read of a magnificent scheme for abolishing Income Tax. Briefly, it consisted of slapping a 30 per cent tax on all goods and services. At almost the same time, the trade papers were bursting with the news that Retail Price Maintenance had gone with the wind. Those of us who still imagined that r.p.m. was something to do with rotation were due for a rude shock.

Price cuts of between 15 and 55 per cent on radio and electrical goods were announced by one multiple group of stores. Another had started slashing prices way



*You just grit your teeth*

back in the Christmas period, with the rather naïve excuse that "the windows of our 208 branches cannot be dressed in a day". Others, more cautious, reduced the mark-down on selected lines, principally washing machines and the larger appliances. One North-Country dealer reminded us wryly of the price-cut pioneers who had forced themselves out of business.

Readers of this column need no reminding of the consequences of price-cutting by the radio trade. Service is the first thing to go by the board. And when the purchaser of a bargain found that most of his saving was taken up

in subsequent repair charges it would be too late for him to have a rethink.

Of course, we are told that this is the age of the handyman. Do-it-yourself is the vogue. When your special offer, ridiculous reduction, must be disposed of, marked-down-bargain goes wrong it is pretty hopeless toddling round to the shop where you bought it. You just grit your teeth, fish out the snappily packaged toolkit that Aunt Ada sent for your birthday and thumb through a few back numbers of *PW* or *PT* in the hope of finding a crumb of information that might help.

Which may be all very fine for the regular reader who can distinguish a bootstrap from a locked-oscillator discriminator and who just happens to have the equivalent to an unidentifiable Japanese VDR in his ubiquitous, bottomless spares box.

Unfortunately for the electronics bargain-hunter, the parts most prone to breakdown are inevitably those specially produced for the manufacturer. Brackets, levers, pulleys, switches, drums or components of Lilliputian dimensions in spaces that forbid any conventional substitute. If it is any comfort, the Group Marketing Manager of one of our largest radio and TV makers forecast that more than half the 2.6 million radio sets expected to be sold in 1967 will be imported—most of them made in Hong Kong.

This does not deter some of our intrepid handymen, to judge by a sample of the equipment that lands on my workshop bench. Tape recorder belts fashioned from redundant garters, switch-springs made from twisted safety-pins, even a tarnished apostle spoon that did surprisingly effective duty as a clutch lever, all showed evidence of

abundant enthusiastic ingenuity.

The chap I always feel sorry for is he who slouches disconsolately up to the counter and waves a burned-out transformer under the salesman's nose. Even if he knew its rating, and could be supplied with an alternative, he would probably find it had to fit between a mini-gang capacitor and a paper-thin scale-plate. Footsore, dispirited, he travels on to the next shop, and probably ends up dreaming of white-coated assistants amid their gleaming banks of "bargains" sadly shaking their heads in unison.



*Under the salesman's nose*

With all the give-away gimmicks that operate, we may find it necessary to buy a bedroom suite to get the magnificent free-gift radio, or sign for a year's subscription to a paperback if we want a buckshee food mixer. Henry has dreams of opening one of those monster cereal packets one day to find it full of match-box intercoms with a single corn-flake nestling in the middle.

The joint managing director of Elliott Automation forecast that every home would have its own computer within ten years. I can't think what for—unless it is to work out what we have saved by snapping up these ex-RPM bargains. But what happens when the shoe-box computer goes wrong?

# ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times in GMT  
Frequencies in kc/s

## THE BROADCAST BANDS

by JOHN GUTTRIDGE

**F**IRST a plea to contributors. Most of the big stations send us their schedules regularly and there is no shortage of information about them. However, many stations keep no regular mailing lists, and information is scarce. We want more information on these harder stations.

Conditions are getting much better for DX now. With the high-power stations moving to the higher frequency bands the smaller low-powered stations in the lower band are not being blotted out nearly so much.

### AFRICA

**Congo:** *Radiodiffusion de la Republique Democratique du Congo* (B.P. 3171, Kinshasa) has French and other programmes from 1700-2200 on 7,205/9,775/11,795.

**Portuguese Guinea:** *Emisora Provincial de Guine* (Avenue da Republica, Bissau) is drifting from 5,040 to 5,044 when it has QRM from Togo on 5,047. Has also occasionally been heard on 5,017.

**Kenya:** *Voice of Kenya* (Box 30456, Nairobi). The home service on 4,885 (10kW) gives good reception in the evening until sign off at 2003 (2100 Saturdays).

**Morocco:** *Radiodiffusion Television Marocaine* (1 Pierre Parent, Rabat) has English on 7,225 at 1800-1900 and has been heard in English from 1830-1900 on 11,735.

**South Africa:** *Radio South Africa* (P.O. Box 8606, Johannesburg) has English at 0500-0512 on 7,270/9,525; 0645-0657 11,900/15,285; 2100-2155 11,900/15,285; 2200-2255 9,720/11,785/15,215.

### MIDDLE EAST

**Israel:** *Israel Broadcasting Authority* (Kol Yisrael, Broadcasting House, Jerusalem) is using 9,009/9,625/9,725 for its 2015-2030 and 2115-2130 English transmissions. Only announces 9,009/9,725.

**Lebanon:** *Radio Lebanon* (Ministry of Information, Beirut) now uses 11,940 for its African service from 1830-2030.

### ASIA

**Ceylon:** *Radio Ceylon* (P.O. Box 574, Colombo) has English for Europe from 0700-0815 on 15,330 and to South Asia from 0915-1030 on 17,830.

**China:** *Radio Peking* (Broadcasting Administration, Fu Hsin Men, Peking) has a Russian transmission at 1900 on 11,290. The U.S.S.R. jams many of these Russian transmissions from Peking. The jamming consists of over-modulated, distorted transmissions of the Radio Moscow Home service. Radio Peking's home service has been heard on 4,500 around 1530.

**Pakistan:** *Radio Pakistan* (Karachi) now uses 7,010/9,750 for its 1945-2030 English transmission to Europe.

### NORTH AMERICA

**U.S.A.:** *Voice of America* (U.S. Information Agency,

Washington, D.C. 20547) has dropped a number of frequencies from its schedules. English to Europe is now at 0300-0500 on 3,980/6,125/7,200/9,740; 0500-0715 as 0300 plus 6,040/1,196; 1400-1600 and 1800-2100 5,965/9,760/15,205/15,290; 1600-1800 as 1400 plus 1,196; 2100-2215 5,965/9,760/15,205/15,290/1,196 (not 2130-2200); 2215-2330 (to 2345 Sundays) 5,965/9,760/15,290/1,196. The Greenville transmitter has been heard signing on at 1900 on 9,710 with strong QRM from Radio Moscow.

*Radio New York, Worldwide*, WNYW (485 Madison Avenue, New York, N.Y.) now starts as DX programme at 1605 on Sundays and 2303 Saturdays.

### SOUTH AMERICA

**Brazil:** Frequency 11,925 listed as *Radio Bandeirantes* appears to be being used by *Agencia Nacional, La Voz de Brasil*.

*Radio TV Gaucha* (Casila Postale 1164, Porto Alegie) has moved PRC23 to 11,915. Reception is fair to good around 2200.

**Colombia:** *Radio Sutatenza* (Aereo 1770, Bogota) gives a good signal on HJEC 5,075 and HJEG 5,095 after 2230.

*Radio Nacional* (Apartado Nacional 1824, Bogota) has been signing off as early as 0100 over HJQC 4,955 recently.

### EUROPE

**Austria:** *Osterreichischen Reudfunk* (P.O. Box 700A, 1040 Vienna) has replaced 17,755 by 17,820 for its 1000-1130 transmission.

**Switzerland:** Swiss Broadcasting Corporation (CH 3000, Bern 16) has made some interim frequency changes until its summer schedule starts on May 7th. Frequencies affected for English programmes are 7,220 replaced by 9,665 at 1845; 9,670 replaced by 17,800 at 0700; 9,665 replaced by 17,830 at 1500; 5,965 replaced by 11,790 at 0115 and by 9,655 at 0500.

**U.S.S.R.:** *Radio Moscow* (Moscow) has English to North America at 2200-2230 on 9,760/9,680/9,620/9,570/7,250; 2300-2330 9,760/9,680/9,660/9,620/9,570/9,530/7,250/7,200; 0000-0030 9,760/9,680/9,660/9,610/9,570/9,530/7,310/7,250/7,200.

*Radio Vilnius* (Kanarskio g-ve 49, Vilnius) has English Sundays and Fridays 2100-2130 665/1,106/1,554 and 2230-2300 on 665/1,106/1,554/5,920/5,940/7,180/7,250.

**Vatican:** *Vatican Radio* (Vatican City) has English to the Philippines Tuesdays, Thursdays and Saturdays from 1155-1210 over the new frequencies 17,820/21,515.


Thanks this month go to A. B. Thompson, World Communications Club of Great Britain, A. E. Roxburgh, International Short Wave Club, Swiss Broadcasting Corporation, R. A. Miller, S. Shaw, Radio Sweden, and Radio New York, Worldwide.

# Peerless

## HI-FI BAFFLE SPEAKER SYSTEMS FOR MONO OR STEREO

The new Peerless systems are engineered to the high quality standards that have made Peerless pre-eminent in high-fidelity design over the past years. Our experience, together with the most careful selection of materials and strictest manufacturing controls, assure performance of highest quality.

All the speaker systems are mounted and wired on a front board covered with plastic fabric grille and ready for cabinet mounting. Standard impedance for PABS 2-8, 3-15 and 3-25: 8 ohms (3.2 ohms or 16 ohms on request). Standard impedance for PABS 2-10 and 4-30: 4 ohms (8 ohms or 16 ohms on request).

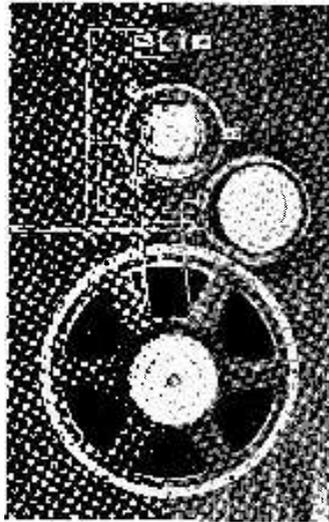

PABS 3-25

**PABS 4-30** (also available as KIT, see below). is a 3-way speaker system consisting of 4 speakers and crossover network. Max. Power Input: 30 Watts. Frequency Range: 30-18000 c.p.s. in 50 litres (1.75 cu. ft.) cabinet. Speakers: Woofer D 120 W special. Mid Range O 570 MRC. Tweeters 2 x MT 25 HFC. Crossover Frequencies: 500 and 3500 c.p.s. Dimensions (inside) for 50 litres cabinet: Approximately  $24\frac{13}{16} \times 13\frac{3}{8} \times 9\frac{1}{2}$  in. (630 x 340 x 234 mm). Brown coloured plastic fabric grille.

**PABS 2-8** (also available as KIT, see below). is a 2-way speaker system consisting of 2 speakers and crossover network. Max. Power Input: 8 Watts. Frequency Range: 50-18000 c.p.s. in 16 litres (0.57 cu. ft.) cabinet. Speakers: Woofer B 65 W. Tweeter MT 25 HFC. Crossover Frequency: 4000 c.p.s. Dimensions (inside) for 16 litres cabinet: Approximately  $15\frac{9}{16} \times 9\frac{3}{8} \times 6\frac{1}{2}$  in. (395 x 245 x 165 mm). Specify grey or golden coloured plastic fabric grille.


**PABS 2-10** (not available as KIT). is a 2-way speaker system consisting of 2 speakers and crossover network. Max. Power Input: 10 Watts. Frequency Range: 50-18000 c.p.s. in 6.5 litres (0.23 cu. ft.) cabinet. Speakers: Woofer O 525 WL. Tweeter MT 20 HFC. Crossover Frequency: 3500 c.p.s. Dimensions (inside) for 6.5 litres cabinet: Approximately  $9\frac{13}{16} \times 6\frac{1}{2} \times 6\frac{9}{16}$  in. (252 x 158 x 167 mm). Dark coloured plastic fabric grille.

**PABS 3-15** (also available as KIT, see below). is a 3-way speaker system consisting of 3 speakers and crossover network. Max. Power Input: 15 Watts. Frequency Range: 45-18000 c.p.s. in 30 litres (1.06 cu. ft.) cabinet. Speakers: Woofer P 825 W. Mid Range GT 50 MRC. Tweeter MT 20 HFC. Crossover Frequencies: 750 and 4000 c.p.s. Dimensions (inside) for 30 litres cabinet: Approximately  $20\frac{3}{8} \times 8\frac{3}{8} \times 10\frac{1}{2}$  in. (515 x 218 x 270 mm). Specify grey or golden coloured plastic fabric grille.

**PABS 3-25** (also available as KIT, see below). is a 3-way speaker system consisting of 3 speakers and crossover network. Max. Power Input: 25 Watts. Frequency Range: 40-18000 c.p.s. in 100 litres (3.5 cu. ft.) cabinet. Speakers: Woofer CM 120 W. Mid Range G 50 MRC. Tweeter MT 20 HFC. Crossover Frequencies: 750 and 4000 c.p.s. Dimensions (inside) for 100 litres cabinet: Approximately  $25 \times 15 \times 16\frac{1}{2}$  in. (635 x 380 x 412 mm). Specify grey or golden coloured plastic fabric grille.

## Peerless LOUDSPEAKER SYSTEMS IN KITS FOR MONO AND STEREO


If you want to spend a little extra time to establish your high-fidelity sound system and at the same time save money, you can get four of our PABS systems in KITS. A KIT system consists of speakers, crossover network, drawing of cabinet as well as mounting instruction, but without baffle. Standard Impedance for KIT 2-8, 3-15 and 3-25: 8 ohms (3.2 ohms or 16 ohms on request). Standard Impedance for KIT 4-30: 4 ohms (8 ohms or 16 ohms on request).

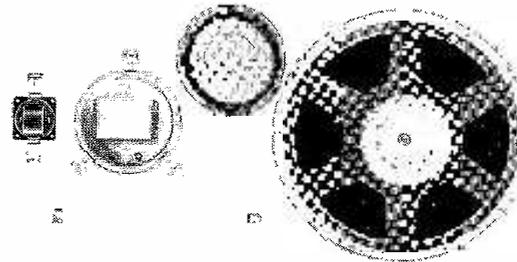

KIT 3-25
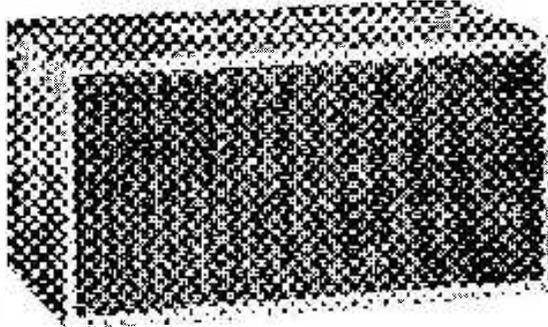
## Peerless HI-FI CABINET SPEAKERS FOR MONO AND STEREO

A trio of 2-way and 3-way compact speaker systems in oiled teak cabinets of bookshelf type, Danish design and technique at its very best. Standard Impedance: 4 ohms (8 ohms or 16 ohms on request). Infinite baffle type airtight enclosure, damped with "Rockwool".



MEDIUM SIZE SYSTEM 24-2

### COMPACT SYSTEM 6,5-2

is a 2-way speaker system in cabinet with dark coloured plastic fabric grille. Combines one special woofer ( $5\frac{1}{2}$  in.), one closed-back tweeter (2 in.) and a crossover network. Crossover Frequency: 3500 c.p.s. Frequency Range: 50-18000 c.p.s. Power Capacity: 10 Watts. Cabinet Size:  $10\frac{1}{2} \times 6\frac{9}{16} \times 8\frac{3}{8}$  in. (260 x 156 x 213 mm).

### MEDIUM SIZE SYSTEM 24-2

is a 2-way speaker system in cabinet with brown coloured plastic fabric grille. Combines one special woofer ( $6\frac{1}{2} \times 10\frac{1}{2}$  in. elliptical), one closed-back tweeter ( $2\frac{1}{2}$  in.) and a crossover network. Crossover Frequency: 3500 c.p.s. Frequency Range: 40-18000 c.p.s. Power Capacity: 10 Watts. Cabinet Size:  $19\frac{3}{8} \times 9\frac{3}{8} \times 10\frac{1}{8}$  in. (500 x 250 x 270 mm).

### MONITOR SYSTEM 50-4

is a 3-way speaker system in cabinet with brown coloured plastic fabric grille. Combines one special woofer (12 in.), one special mid range ( $5 \times 7$  in. elliptical), two closed-back tweeters ( $2\frac{1}{2}$  in.) and a crossover network. Crossover Frequencies: 500 and 3500 c.p.s. Frequency Range: 30-18000 c.p.s. Power Capacity: 30 Watts. Cabinet Size:  $25\frac{9}{16} \times 14\frac{9}{16} \times 11\frac{1}{2}$  in. (650 x 360 x 300 mm).

MADE BY

# PEERLESS FABRIKKERNE A/S

COPENHAGEN . DENMARK

Distribution in the U.K. by  
C. E. Hammond & Co. Limited — 90 High Street,  
Eton Windsor, Berkshire

Please send me details of Peerless


CABINET SPEAKERS     PABS     KITS

Mr. ....

Address .....

Post to C. E. Hammond & Co. Ltd., 90 High Street,  
Eton Windsor, Berkshire.

May/PW/1967

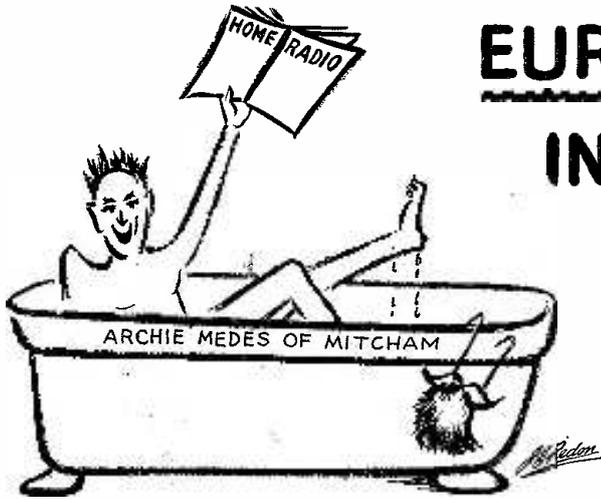

# EUREKA!!! I've found it!!!!

## IN THE HOME RADIO CATALOGUE

Our tame cartoonist (to whom all praise is due for his excellent illustrations) has made a psychological error this time! Nobody, but nobody, would be surprised at finding the electronic part they require in the Home Radio Catalogue. Quite the reverse... in fact they are surprised if they can't find a particular item in it! However, it seemed a pity not to use such a good cartoon.

You will be astonished at the vast range of items listed—6,000 of them, over 1,000 illustrated; but you will get used to it, leaping out of your bath only if you can't find just what you want.

The catalogue costs a modest 7/6, plus 1/6 postage and packing, and every copy contains 5 vouchers, each worth a shilling. With each catalogue is an easy-to-complete order form and an addressed envelope to post it in. Why wait? Send off the coupon today, with your P.O. or cheque for nine bob.

P.S. No—we don't supply a free false beard with every catalogue! Perhaps you didn't know that Archie Medes of Mitcham always takes off his beard before his ablutions.

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....

HOME RADIO LTD, Dept. PW, 187 London Rd, Mitcham, Surrey. CR4 2YQ

# R.S.T. VALVE MAIL ORDER CO.

144-146 WELLFIELD ROAD, STREATHAM, S.W.16

All valves  
brand new  
and boxed

Mon.—Sat. 9 a.m.  
—5.45 p.m.  
No Early Closing  
Open Daily to Callers  
Tel. STR 0199, 1649

OA2 5/3	6BE6 4/6	6K6GT 5/-	7R7 19/6	19AQ5 7/6	50L6GT 6/-	DF96 6/-	ECF80 7/-	EMS1 7/-	PCC189 10/-	S130 25/-	UMS0 7/-
OC3 5/-	6BH6 7/-	6K7M 5/-	7S7 17/9	20D1 10/-	75 5/-	DM77 3/6	ECF82 7/-	EM84 7/-	PCF80 6/6	SP4 9/-	UU6 13/6
LA7 7/9	6BJ6 7/-	6K7G 1/3	7Y4 7/6	20F2 11/-	78 4/6	DK32 7/9	ECH21 19/-	ESU15027/6	PCF82 6/-	SP41 1/6	UU7 13/6
LD5 6/-	6BQ7A 7/-	6K7GT 4/6	9BW6 8/-	20L1 15/-	80 5/-	DK91 5/-	ECH35 11/-	EY51 7/-	PCF84 8/-	SP61 1/-	UU9 8/-
1H5 7/6	6BR7 10/6	6K8M 8/6	10C1 9/-	20P4 17/-	85A2 3/6	DK92 3/6	ECH42 9/-	EY86 6/6	PCF86 6/6	SU25 19/6	UY21 7/6
1LD5 5/-	6BR8 7/6	6K8G 3/-	10C2 12/-	20P5 16/-	150B2 14/6	DK96 6/6	ECH81 5/3	EZ35 4/9	PCF801 9/9	SU2150 12/6	UY41 6/3
1N5GT 8/-	6BS7 16/9	6K8GT 8/3	10F1 14/-	25A6 6/6	150C4 12/6	DL66 15/-	ECH83 7/-	EZ40 7/-	PCF802 9/9	T41 9/-	UY85 5/-
1R5 5/-	6BW6 7/6	6K25 20/-	10F3 12/-	25L6GT 4/6	801 5/-	DL92 4/9	ECL50 6/6	EZ41 8/-	PCF805 10/9	TDD4 7/-	VMP4G 17/-
1S4 5/-	6BW7 8/6	6L1 9/6	10F9 9/9	25Y5 6/-	807 7/9	DL93 3/6	ECL82 6/6	EZ80 5/-	PCF806 12/-	U10 7/-	VP4B 27/6
1S5 3/3	6C4 3/-	6L6G 7/6	10F18 9/-	25Z4 6/3	813 80/-	DL94 5/9	ECL83 9/9	EZ81 5/-	PCF808 11/6	U14 7/-	VR105/30
1T4 2/6	6C5G 4/-	6L18 7/6	10L1 10/-	25Z5 7/-	866 10/-	DL95 6/6	ECL86 8/6	GZ30 8/6	PCL82 7/-	U19 30/-	VR150/30
3A4 3/6	6C6 3/9	6Q7G 5/6	10LD11 10/-	25Z6 11/-	954 4/-	DL96 6/-	EF9 20/-	GZ32 9/6	PCL83 8/6	U25 10/6	VR150/30
3Q4 3/6	6C8G 6/-	6Q7GT 9/-	10P13 14/-	28D7 5/-	1625 5/-	DM70 5/7	EF36 3/6	GZ34 10/-	PCL84 7/6	U26 10/6	VT25 5/-
3Q5 6/6	6CD6G 22/6	6SA7 7/6	11E3 27/6	30C1 6/6	4022AR 15/-	DY87 7/9	EF37A 7/6	KT36 22/6	PCL85 8/6	U78 3/6	VT25 29/-
3S4 4/9	6CH6 5/9	6SC7 6/6	12AT6 4/6	30CL5 11/6	5763 10/6	DY88 6/6	EF39 6/6	KT61 17/6	PCL86 8/6	U91 11/6	VT31 59/-
3V4 5/9	6CW4 12/-	6SG7 2/6	12AT7 3/9	30C17 12/-	7193 1/6	E88CC 12/-	EF41 8/6	KT66 20/-	PEN4A 20/-	U201 12/6	VU111 6/-
5R4G 8/9	6D6 2/9	6SH7 4/6	12AU6 5/9	30F5 13/-	7475 2/6	HA50 2/-	EF50 2/6	KT81 10/-	PEN4B 20/-	C301 13/-	VU120 12/6
5U4G 4/-	6E5 5/9	6SJ7 5/-	12AU7 4/9	30FL1 13/6	ATP4 1/9	EABCS0 5/9	EF80 5/6	KT88 27/6	PEN45 6/6	U403 6/6	VU508 30/-
5V4G 8/-	6F1 9/-	6SK7GT 4/9	12AX7 5/9	30L15 12/6	ATP5 7/-	EAF42 7/6	EF85 6/6	KTW61 4/3	PEN46 2/9	U801 18/6	WS1M 5/-
5Y3GT 5/-	6F5G 5/-	6SL7GT 4/9	12BA6 6/-	30L17 12/-	ATP7 4/6	EB41 4/6	EF86 6/6	KTZ41 8/-	PL36 9/-	UABC80 5/6	X79 41/-
5Z4G 8/-	6F6G 4/-	6SN7GT 4/-	12BE6 5/3	30P12 10/-	AU2 30/-	EB91 3/-	EF89 5/6	ML4 17/6	PL81 7/6	UAF42 8/9	XH1-5 5/-
6/30L2 11/3	6F8G 4/6	6SQ7 6/-	12C8GT 7/6	30P19 14/-	AU5 6/-	EBC33 7/-	EF91 3/3	ML6 12/6	PL82 6/6	UBC41 8/6	XP1-5 5/-
6A7 15/-	6F11 12/6	6U5G 7/6	12E1 19/6	30PL1 14/-	AZ1 3/9	EBC41 8/3	EF92 2/6	MSP4 12/6	PL83 6/6	UBC81 7/6	XSG1-5 10/-
6A8G 12/6	6F13 5/-	6V6G 8/-	12F5GT 2/3	30PL13 14/-	AZ31 7/9	EBC90 3/9	EF98 9/6	MU14 4/-	PL84 6/6	UBF80 5/9	Y63 7/6
6AC7 3/-	6F14 12/6	6V6G 3/6	12J7GT 7/3	30PL14 14/-	CB131 15/-	EBF80 6/6	EF183 6/6	MX40 12/6	PL500 14/6	UBF89 6/6	Tubes
6AK5 4/6	6F23 11/-	6V6GT 7/6	12K7GT 3/-	35A5 17/-	CL33 19/6	EBF89 6/6	EF184 6/6	N37 10/-	PX4 18/6	UCC84 8/6	3EG1 40/-
6AM5 2/6	6G6 2/6	6X4 3/6	12K8GT 8/-	35L6 4/6	CY31 10/-	EBL1 17/6	EL32 3/-	N78 15/-	PY33 8/6	UCC85 6/6	3FP7 12/6
6AM6 3/6	6H6 1/3	6X5G 4/9	12Q7GT 3/-	35Z3 10/-	DAC32 7/6	EBL21 10/6	EL33 17/6	N108 15/-	PY81 6/6	UCR80 8/6	5CP1 30/-
6AQ5 5/6	6J5M 6/6	6X5GT 7/6	12SA7 6/6	35Z4GT 3/9	DAC91 3/3	EBL31 27/6	EL34 9/6	NGT1 3/-	PY82 5/6	UCR42 8/6	CV1526 40/-
6ASTG 19/6	6J5G 2/6	7B6 11/-	12SG7 3/6	35Z5 5/6	DAF96 5/-	ECC81 3/9	EL41 8/6	NGT7 25/-	PY83 6/6	UCR81 6/6	ACR13
6AT6 3/9	6J5GT 4/6	7B7 7/-	12SH7 2/9	35Z6 5/6	DAC99 3/3	ECC82 4/9	EL42 7/6	OZ4 4/-	PY800 7/-	UCL82 7/6	£3.16.0
6AU6 6/-	6J6 3/-	7C5 10/-	12SK7 3/9	35Z7 5/6	DAF99 3/3	ECC83 5/9	EL43 8/6	PC86 9/-	PY801 7/-	UCL83 8/9	VCR97 35/-
6BSG 2/-	6J7M 8/6	7C6 8/-	12SR7 2/9	50B5 6/6	DF33 8/-	ECC84 5/6	EL49 5/6	PC88 9/-	R2 4/-	UF41 8/-	VCR517B
6B4G 10/-	6J7G 4/9	7D5 8/-	12SR7 5/-	50C5 5/9	DF91 2/6	ECC85 5/-	EL95 9/-	PC97 7/6	R19 7/-	UF89 6/-	£30/-
6BA6 4/6	6J7GT 8/6	7H7 5/-	14H7 9/-	50CD6G32/6	DF92 2/6	ECC88 7/-	EL180 20/-	PCC84 5/6	RG5/500	UL41 8/9	VCR517C
							EMS0 7/-	PCC89 10/-	59/-	UL84 6/-	£30/-

SPECIAL 24 HOUR SERVICE  
OBSOLETE TYPES A SPECIALITY  
QUOTATIONS FOR ANY VALVE NOT LISTED  
Postage 6d. per Valve C.W.O. No C.O.D.  
Send S.A.E. for list of 2,000 Types  
Manufacturers and Export Inquiries Welcome

Special 24 Hour  
Express Mail  
Order Service

SETS OF VALVES			
DAF96, DF96, DK96, DL96	...	...	Set of 4, 24/6
BRAND NEW TRANSISTORS			
AC127 8/-	OC25 11/-	OC71 4/6	OC81 4/-
AF114 7/-	OC28 16/-	OC72 6/-	OC81m/pr
AF115 7/-	OC35 9/6	OC75 6/-	OC82 12/6
AF116 7/-	OC44 4/6	OC76 6/-	OC81D 4/-
AF117 5/-	OC45 3/6	OC77 8/-	OC82 6/-
			OC200 8/-

PLEASE NOTE OUR NEW ADDRESS

**L**URID stories and 'orrible tales of goings on just below 28Mc/s have poured in this month. "They are allowed up to 100 watts and a 3 element beam" quotes one informant. "Up to 100mW with no licence and up to five watts with", reckons another. Many people sent in reports and received these stations on a wide variety of gear ranging from a simple t.r.f. to an AR88. The hand-picked "callsigns" are quite novel—"Rattlesnake", "Jack Rabbit", "Humpty Sumpty", "Colorado Batman", etc. Certainly the Citizens Band is humming and I forecast that it will hum even louder when the sunspot maximum gets nearer. Incidentally, I read that the GPO have recently said a very loud and emphatic "No" to a Citizens Band in this country. Ah well, looks like you'll just have to swot up the R.A.E. and get cracking on the slow morse transmissions on topband.

A fantastic month all round for reception. On topband GM's arriving at the home QTH in St. Albans loud and clear and on a.m. too. G3SED in Portsmouth was peaking so loud at one time I thought he was a local. His 160 metre antenna takes a bit of beating, a few hundred feet of wire in the form of an "inverted V", held up in the middle by—wait for it—a balloon! (So help me it's true.) He also has around a half square mile of earth mat to tune it against. (An' there's me with a mobile whip 8ft. 6in. tall—no justice these days.) Twenty has been going like the proverbial bomb, but let's keep that band for a while and take a peep l.f.

### 1·8/3·5/7·0

Not much on 1·8Mc/s reported this month but 80 has fared a little better.

**N. Flatman** (Suffolk), R1155, 68ft. end fed, logged these on 80 metre phone—CN8AW, K1ARD, K2DPA, K4KZZ, K5KFD, KØWFJ, OY7S, TI9AC, UA9BE, VE-1IE, 1UM, 2WM, 3ADX, 3HEW, VO1EG, VK1AF, 1FW, 4AJ, 9AU/M, VS9KRV, W-1HKK, 1FKJ, 3BFF, 4IML, 4SIB, 4YRW, WA2GSX, ZL-2GG, 3RJ, 4KE, 4LZ, 4OD, 3B1FX, 3C1-UA, UM, 5A4TK, 7XØAM.

**G. Watson** (Yorks), R1155, 10 Metre dipole plus a 19 set variometer, had a quick listen on 80 s.s.b. and heard—CN8AW, K3PHP, K4IUQ, LX1BW, OHØNF, UA2KBD (c.w.), 3B1FX, 3C3FJZ/P/SU, 9H1AR.

**N. Hembrey** (Sussex), EA12, 7ft. vertical rod at 30ft., reckons 80 is pretty lively. Unbelievers should peruse the following log, all s.s.b.—CN8AW, K-2RBT, 3UQU, 8DOC, 8YWG, MP4MAW, OY7ML, TI2NA, UA9BE, VE-1AFB, 1IE, 2WM, VP9FB, VS9ALV, VS9HRV, W1FZJ/KP4, W-1HAD, 3BMS, 3PHL, 9JLH, WA2KTI, 3C3FJZ/SU, 4X4AS, 5A1TK, 7XØAH, 9V1LP. A bit higher up on 7Mc/s, Norman logged—K7MNA, LX1BW, PI7AYJ, SV1BH, UF6FE, W3BMS, W4DQO, W8EZK, ZC4MO, ZD8RB, all s.s.b.

### 20 AND 15

If you don't hear much on these bands there's something wrong somewhere. Twenty is really back in the swing—but let's let the reports tell the story.

**H. Dearing** (Herts), Hammarlund Super Pro., 140ft. end fed. Twenty s.s.b.—JA-1AEA, 8BNK, 9KCE, KG6AA, KL7EBK, SV1BH, VKØCR, VK2AYT, VK3UQ, VK4SD, VK5MS, VK8OE, ZD3F, ZL3OS, ZL4BA, 5A1TE, 5A5TV, 7XØAH.

**C. Morris** (Worcs), 10 tube home brew (good lad!) s/het, indoor joystick, all s.s.b. on 20—CR4AJ, KG6FAE (Guam), KG6IJ, KG6SB (Saipan, Mariana Is.), KX6FD, VK9XI (Christmas Is.), VK3AHI/VK9 (Norfolk Is.), VP2GSM, VP8HZ (Falkland Is.), VP8IE (South Georgia Is.), VKØCR (Marquarie Is.), VQ8AX, VS9HRV, VU2WNV, ZK1AR, ZD3G, ZS3HT, ZS8L, 5U7AL.

**S. Cushworth** (Yorks), 52 RX, 132ft. l.w., 20 s.s.b.—CR6IF, HK2KO, HV1CN, PY4ASV, PY7AEW, VK2ID, VK3HW, YV5CMZ, 9K2WR.

**P. Cooper** (Mddx), CR45 (t.r.f.), 25ft. of wire "taped" to the ceiling, all s.s.b. on 20—CX3BR, DU1FH (Philippines), KG6ALV, KR6UL, KS6DO, MP4TBO, PY2CHM, PY7AKQ, TG9EP, VQ9AR, WAØPOG/P/KL7, WA6BMG, YV1BF, YV5CMQ, ZL1AIX, 3C3FJZ/P/SU, 5Z4AA, 9H1AN.

**R. Pearson** (Cleckheaton), BC 1147A, 140ft. l.w., on 15 a.m. and s.s.b.—EA5HW, EA9EJ, F2CD, HP9AJM, IIRMV, K2UTC, K4BZY, MP4BBA, OH2BR, SVØWL, UA9KCB, UT5OF, VO1HS, WA9BUI, ZC4MO, 3C1AFY, 4U1SU, 9G1DM.

**A. Darragh** (Berks), GC1U, 80ft. l.w., all s.s.b. on 15—AP8AD, BY2KU, CN8FF, CT1BB, CX8AAW, EL2AG, EP3AB, HI8XDA, HK4TA, JA-1JXU, 2ECG, 3FTB, 6CMI, 7MA, 9JX, KA2DO, KA3KGC, KP4BCL, KR6MB, KV4CX, OX3WX, PY2II, SVØWF, TF3EA, TU2AY, VK2FA, VP2GSM, VS9AFC, ZB2AM, ZC4RM, ZE1BS, ZS6BUY, 3B1IR, 3C3FGN, 3C5FO, 5A1TV, 9G1DY, 9H1R.

### 10 METRES

**D. Harvey** (Salop), Eddystone 730/4, 100ft. l.w., 10 metres all s.s.b.—CR6DX, K5AIQ/M, PY7EZ, VP5RB, VQ9AR, W-1/2/3/5/8/9/, YV5CMQ, ZL1AH, ZS4BV, 3C3FHO.

**D. Varley** (Notts), CR7OA + PR30, 20 metre folded capacitive loaded dipole. Ten metres, phone—CT3AS, K4QWM, OD5BZ, PY2CK, TG9EP, UB5CZT, W-1YRC, 2PH, 3POG, 8OCT, ZE1BR, 5A5TE.

**P. Baker** (S. Wales), HE30, 100ft. l.w., ten metres, all phone—CN8CS, CT2AC, EA8FG, EP3AM, KØIAF, LU1DAB, MP4BBA, OD5BZ, SVØWL (Crete), UA9MBM, UF6JAF, UL7HB, UW9DZ, VQ8BJ, W-1/2/3/4/5/8/9/Ø, XE2DDZ, ZC4GY, ZE2JA, ZS1BW, 3B1EJ, 5A1TK, 5N2AAF, 9G1DM, 9H1AM, 9J2RO.

### CONTESTS

Only one and that's on 15th-16th April on 70Mc/s. There's the transmitting part of the contest on the Saturday starting at 1800 and finishing Sunday at 1800. There's also a s.w.l. contest on 70Mc/s from 1800 on 15th April to 1800 on 16th April. Deadline for reports and logs this month is 20th April. What have you heard?



Books reviewed on this page are normally obtainable through any retail bookshop. In this instance, the information printed in heavy type should be quoted.

≡ **RAPID SERVICING OF TRANSISTOR EQUIPMENT**  
≡ By Gordon J. King. Published by George Newnes Ltd.  
≡ 151 pages, 8½ × 5½in. Hard covers. Price 30s.

**A** REMARKABLY good book. The author is to be congratulated for his fresh and stimulating treatment of what has almost become a hackneyed subject.

He makes no compromise. "*I have endeavoured*", he says "to discuss transistors, transistor circuits and their faults as though thermionic valves had never existed". This is the right approach, for more confusion has been caused by attempted parallels and analogies than ever by the faults themselves.

No time is wasted on fundamentals. In one concise chapter this essentially practical writer sets out the basic theory that we need to know before tackling transistor circuits. By Chapter 2, the reader is ready for preliminary circuit and transistor tests.

Throughout this book, the practical approach is paramount. We find such 'throwaway' remarks as: "*A good way of checking for capacitor leakage is to meter the Ic of the coupled stage . . . and, when connecting a meter, " . . . remember that the terminal resistance of any voltmeter is equal to the ohms/volt value multiplied by the fullscale voltage range selected.*" Small points, taken for granted by the practising technician, but for the beginner, or the service engineer whose training on valved equipment has produced the kind of mental blockage that needs careful handling, such tips are invaluable.

In Chapter 4, useful information on equalisation is included, plus some warnings about the interpretation of test results that again underline the essentially down-to-earth methods of this author.

Chapters 5 and 6 discuss fault-finding in r.f. circuits, and oscillator stages. Here again, we find the subject treated in a way that is both easily understood and technically efficient. The author has quite obviously sweated at the bench, repairing receivers with no more than his own basic knowledge to aid him.

In the seventh chapter we encounter transistor radios and hi-fi amplifiers as a whole. The treatment is less detailed than we would have liked; due, doubtless, to space restrictions. Full typical circuits are given, with component values.

Chapter 8, 'Practice of transistor equipment servicing' is actually a run-down on the various appropriate instruments, their use and application, and a few remarks on soldering and printed circuits.

With each chapter, a table of faults, their causes, and the tests to prove them, is appended, providing not only a useful reference but a summary of the foregoing information.

It is not often that we find a book of value both to the beginner and the practising technician, but this is one.—BRG.

≡ **ACOUSTICAL TESTS AND MEASUREMENTS**  
≡ By Don Davis. Published by Foulsham-Sams Technical Books.  
≡ 192 pages, 8½ × 5½in. Hard covers. Price 30s.

**I** NTEREST in audio, by both amateur and professional enthusiasts, too often ends at the hole where the sound comes out. Great trouble may be taken in loudspeaker enclosure design, in speaker placing, matching and general disposition, but the space into which the sound is projected is either taken for granted or simply accepted 'warts and all'.

Mr. Davis purports to write for the advanced technician, but his style of presentation and the plain good sense of the information he gives allows an appeal to any audio enthusiast.

His book abounds in the graphs and tables beloved by the academics. He details the work done on various halls, churches and stadiums. He tells us how to measure ambient noise, reverberation time, quietness (which is just as important as loudness) and sound distribution.

Why it is necessary to measure at all; why not trust our ears? The author tells us, with convincing detail. He goes on to describe some of the instruments needed to make these audio assessments, shows the various charts that are used "in the trade" and even gives a specimen survey report for the benefit of readers who may think of branching out into this highly specialised line.

For anybody who has listened to a hi-fi set-up in demonstration-room conditions, then heard the same equipment in the limited confines of a living-room, this book is a confirmation.—HWH.

≡ **LOUDSPEAKERS AND LOUDSPEAKER CABINETS**  
≡ By P. W. Van Der Wal. Published by Iliffe Books Ltd.  
≡ 107 pages. 8½ × 5½in. Price 15s

**T** HIS is the latest in the series of Philips paperbacks (P12) and is an English version of original Dutch material. A quick flip through gives the impression of a book packed with useful information and this is largely justified on closer inspection. Starting with the inevitable "How it Works" chapter, the author goes on to give notes on choosing a loudspeaker, important points in a sound installation, discussion on distortion and layouts of mono and stereo set-ups.

An important chapter deals with the frequently neglected factor of room acoustics and almost the whole second half of the book is devoted to enclosures, including a welcome chapter on how to build loudspeaker enclosures (practical carpentry hints) and 26 pages of plans for cabinets.

One possible criticism is that the 24 enclosures described all relate to Philips loudspeaker types. Perhaps this is natural in the circumstances but seeing that this is in effect a promotional project we think the price might have been lower!—CRR.

# stern-clyne ELECTRONIC CENTRES

MEMBER OF THE PANTIYA GROUP OF COMPANIES

MAIL ORDER & ALL ENQUIRIES TO: DEPT. PW, 3-5 EDEN GROVE, HOLLOWAY, LONDON, N.7. Tel. 01 607 8161

LONDON:  
18 Tottenham Court Road, W.1.  
23 Tottenham Court Road, W.1.  
309 Edware Road, W.2.  
109 Fleet Street, E.C.4.  
162 Holloway Road, N.7.

MUSEum 0095  
MUSEum 3451  
PADdington 6963  
FLEet Street 5312  
NORTH 7941


9 Camberwell Church Street, S.E.5.  
220 Edgware Road, W.2.

RODney 2875  
PADdington 5607  
CROYDON: 12 Suffolk House, George Street.  
MUNICIPal 3250  
BRISTOL: 26 Merchant Street, Bristol 1. Bristol 20261

LIVERPOOL: 52 Lord Street.  
MANCHESTER:  
20/22 Withy Grove, M/c 4.  
SHEFFIELD: 125 The Moor.  
NOTTINGHAM: Eastown House, Lincoln St.

Royal 7450  
Blackfriars 5379/5246  
Sheffield 29993  
Nottingham 45389

## INTERCOMS

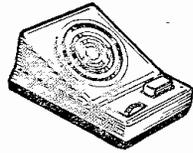

**LOW COST 54/6**  
**INTERCOM P. & P. 2/3**

Two station system for desk or wall mounting, also suitable as a Baby Alarm. Calling can be made from either station even if switch is in OFF position. Transistor circuit, output 50 mW. Size of each unit 3 x 2 x 4in. Uses one 9 volt battery. Complete with 66ft. connecting cable and fitted jack plugs, staples, fixing tape, battery and instructions.

### De-Luxe Intercom/ Baby Alarm

Superb professional compact transistor intercom. So sensitive—picks up normal breathing from several feet away. Powerful 3-transistor amplifier has 200m W output and operates from one 9 volt battery. Master station has Volume, On/Off and Listen/Talk Controls. Supplied with 66ft. connecting lead ready fitted with phono plugs, staples, location tape, battery and full instructions. Complete in attractive gift carton. **89/6 P. & P. 2/6.**



### DE-LUXE FOUR-STATION INTERCOM

Identical in style and presentation to the De-Luxe 2-station model described above, but complete with 4-station control master unit and 3 identical sub-stations complete with three, separate ready plugged, 66ft. long connecting leads.

**£7.19.6 P. & P. 5/-**


### EDEN 7-STATION INTERCOM

High grade Office Model Easily installed and maintained. Master Unit contains powerful, highly sensitive all-transistor amplifier and uses standard torch batteries. Control panel carries all switching and indicator lights to identify calling sub-station. System permits sub-stations to be called separately or simultaneously and for sub-stations to call Master Unit independently. All units are housed in attractively styled metal cases. Supplied complete with Master Station, six sub-stations all interconnecting cable, batteries and full instructions.



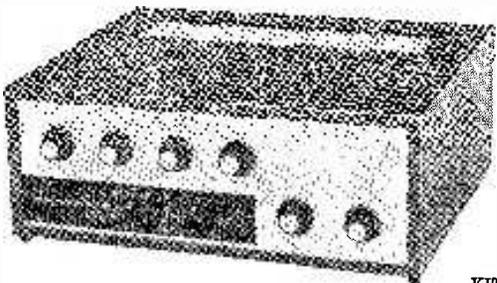**£18.18.0**

Terms: Deposit £6.0 and 12 monthly payments of £1.5.2. Total credit price £21.8.0. Carr. & Ins. 8/6.



## SULTAN Solid State Integrated Stereo Amplifier

**£29.8.0**

KIT OF PARTS:  
(LESS CASE)  
Terms: Deposit £9.16.0 and 12 monthly payments of £1.16.10. Total credit price £31.18.0.  
CASE ONLY £33.0.

ASSEMBLED AND TESTED INCLUDING CASE £39.18.0  
Terms: Deposit £13.6.0 and 12 monthly payments of £2.8.10. Total credit price £42.18.0. Carriage and Insurance 8/6.  
● Descriptive leaflet free on request.  
● Assembly Manual available separately 5/6 incl. P. & P.

The Stern-Clyne SULTAN represents a considerable advance in solid-state, high fidelity stereo amplifiers. Outstanding performance is allied to meticulous construction comprehensive facilities, installation simplicity and attractive functional styling.

SULTAN performance is a natural result of superb design incorporating the most advanced fully proved semi-conductors, and modular substage construction that permits searching quality control and precise matching at every stage of assembly. Particular attention has been given to the provision of all the additional input, output, and power take-off facilities ever likely to be required. The compact sized, craftsman finished teak veneer cabinet and restrained styling ensures unobtrusive, harmonious matching with almost any decor.

## stern-clyne's TREMENDOUS PRICE BREAKTHROUGH in NEW UNIVERSAL RECORDING TAPES

- TENSILIZED. prestretched, extra strong.
- Fully frequency spectrum response
- Guaranteed playing times

STERN-CLYNE make huge bulk purchases of recording tapes from the world's biggest manufacturers—and hand on the enormous price advantage to their customers. The quality is unequalled: Tensilized to ensure the most permanent type of base. Highly resistant to breakage, moisture, heat, cold or humidity. Highly polished, splice-free finish. Smooth output throughout entire audio range. Ideal for your most treasured recordings, cheap enough to use all the time.

Double-wrapped—distinctively boxed. Available in both P.V.C. and Polyester qualities.


TENSILIZED P.V.C.	
3in. 250ft. Long Play ..	5 6
5in. 600ft. Standard ..	8 6
5in. 900ft. Long Play ..	10 0
5 1/2in. 1,200ft. Long Play ..	12 6
7in. 1,200ft. Standard ..	12 6
7in. 1,800ft. Long Play ..	15 0
TENSILIZED POLYESTER	
3 1/2in. 600ft. Double Play ..	11 6
5in. 1,200ft. Double Play ..	15 0
5 1/2in. 1,800ft. Double Play ..	22 6
5 1/2in. 2,400ft. Triple Play ..	37 6
7in. 2,400ft. Double Play ..	25 0
7in. 3,600ft. Triple Play ..	50 0

**TRIPLE BARGAIN OFFER**  
3-Reel packs of 3in. Professional quality tape in self mailing boxes with fill-in address label on reverse. Works on all tape recorders. 250ft. per reel. Famous Audio Magnetic brand. **13/6**  
P. P & P. 1/6d.

### SEND FOR CATALOGUE

Send now for new 100-page Sound and Science Catalogue packed with unique items; profusely illustrated.

### COMMUNICATIONS RECEIVER CR 150

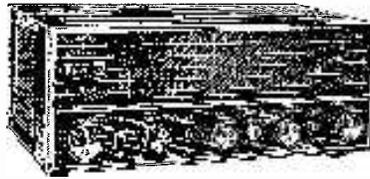

Now Only


**£19.10.0**

Deposit £6.10.0  
12 months £1.5.10  
Total credit Price £22.0.0  
Carriage and Insurance 18/-

New, advanced design provides fantastic sensitivity. Compact and attractive as a drawing-room radio but packed with communications engineering features to bring in the most distant stations loud and clear. Continuous coverage from 540 K to 30 Mc/s. takes in all broadcast bands, shipping, world-wide short wave and Ham radio. Built-in features include extra large tuning dial, extending rod aerial. "S" meter. B.F.O., Noise Limiter, extra quality loudspeaker, etc. Meticulously constructed, handsomely finished. Essential for superb reception but cheaper than many domestic radios. Size only 13 1/2 x 5 x 8in. Standard mains operation.

### New, bookshelf-size MEGAMITE Speaker System


**£8-19-6**  
carr. 7/6

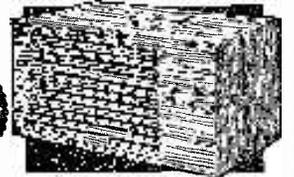

Features include:

- Full frequency range.
- Employs specially designed free-cone bass unit.
- Includes matching tweeter and crossover.
- Handles 10 watts output.

Special 5in. free-cone bass unit uses enormously powerful Feroba magnet to obtain the exceptional cone movement needed to get clean, deep-down bass response equal to much larger speaker performance. Matching 4in. tweeter and crossover is housed with bass unit in heavily lagged, handsome teak veneered cabinet, size only 13 x 7 x 8in. deep. Mounts vertically or horizontally. Ideal for modern hi-fi systems where clean, unobtrusive appearance with high performance is required.

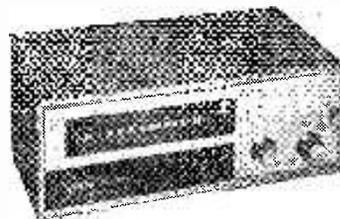

### SATURN VERITONE F.M. TUNER In Teak Cabinet

A mains operated solid-state tuner that provides superb reproduction of V.H.F./F.M. broadcasts. Specially designed to complement the SULTAN but it is also suitable for use with all amplifiers of the highest quality. Sensitivity is such that first class reception is assured in all areas where signal strength is greater than extraneous noise; low drift characteristic in conjunction with a highly effective AFC ensure a constant signal. Available as a compact shelf mounting unit in teak veneer cabinet or as a chassis mounted unit suitable for side-installation with existing equipment.

Terms: Deposit £9.2.0 and 12 monthly payments of £1.14.6. Total credit price £39.16.0. Carr. & Ins. 7/6.

**PRICE £27.6.0**

# repairing radio sets

## PART 2

H. W. HELLYER

In the first article of this series, Gordon J. King has compressed a wealth of technical information. My brief is to discuss the important mechanical aspects of servicing. Before we can do this, it is necessary to review the tools, instruments and other bench aids that are necessary, and others that are desirable though not indispensable. The emphasis is on tidy and methodical service procedure; hence the treatment of the subject which regards even the kitchen table workshop as a 'service department'.

Beginning at the beginning, we take a look at the basic tools of our trade or hobby.


## TOOLS

**T**OOLS are personal items. A toolkit is built up from humble beginnings, with experience proving the worth of some tools, modifying the use of others. One or two favourites will be to hand at all times; others are rarely needed. The following list is a suggestion of basic tools most often needed at the bench.
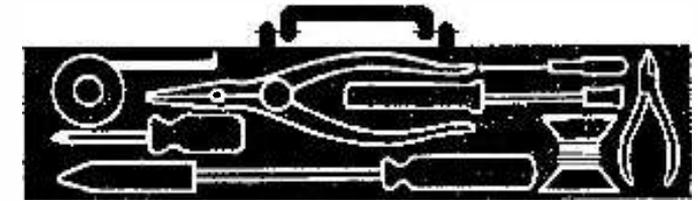
### ★ SCREWDRIVERS

At least three are needed of different lengths and blade size. A standard  $\frac{1}{4}$ in. blade type, with 8 to 10in. blade and straight taper; shorter type with broader blade, for tight wood-screws, etc.; a grub-screw driver.

Phillips type screwdriver and Posidrive tools are



commonly needed. There are two principal sizes, but tight chassis screws often need one of the larger types, with a cross-bar, such as used in cycle shops. The screwdrivers should preferably have insulated plastic handles. A number of makers market these especially for electrical work.

### ★ PLIERS


A large pair are essential with square, parallel jaws, a serrated circular section and strong edge cutting blade to deal with iron wire, bolt ends, chassis burrs. A pair of long-nosed "electrician's" pliers, with insulated handle and a smaller, flat-ended pair for delicate work are also recommended.

### ★ CUTTERS

Side and top-cutters of various styles and sizes are available. Choose a pair to suit one's hand and ensure that the blades have no gaps. Both types have their special uses. For transistor radio work, new types with small blades at the end of longer jaws are being produced and will be found handy in confined spaces.

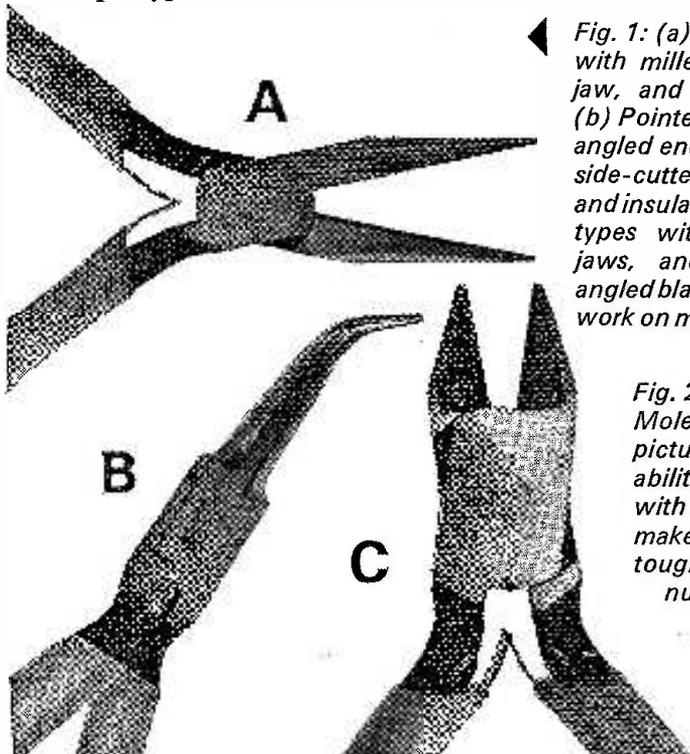
### ★ SPANNERS

Flat and box spanners covering the BA sizes



◀ Fig. 1: (a) Long-nosed pliers, with milled inner surface to jaw, and insulated handles. (b) Pointed-nosed pliers with angled end. (c) Conventional side-cutters, with snub jaws and insulated handles. Special types with longer, slimmer jaws, and with differently angled blades, are available for work on miniature equipment.

Fig. 2: The advantage of the Mole wrench or (in our picture) Guygrip tool is its ability to lock into place with a parallel grip. This makes it useful for releasing tough nuts without scarring nut, bolt or chassis. ▶

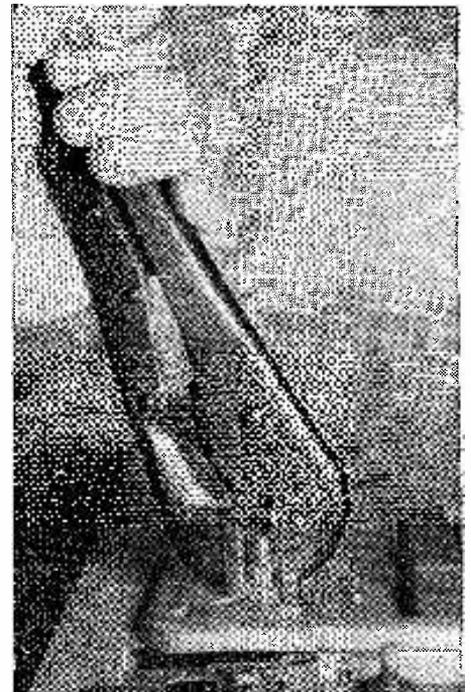

from 0 to 8 are needed most often. Box spanners with 6in. shanks and insulated handles for the "popular" sizes, 2 and 4BA will be found useful. Sets of spanners are available at reasonable prices, with angled tommy bar and separate ends. Nests of flat spanners (which should include the metric sizes for dealing with the growing number of imported sets) are also a great help. A small adjustable spanner of the "King Dick" variety and a larger Mole wrench or Guygrip tool will assist with odd sizes of nut and bolt.

## ★ WIRESTRIPPERS

These are great time-savers. The popular Bib model by Multicore Solders Ltd. is now available in a version with wire-gauge selector and insulated handles.

## ★ HACKSAWS

Even if no chassis work is undertaken, the "Junior" hacksaw will prove worth its modest cost, and a standard electrician's hacksaw, with tubular steel frame, extendable to 12in. blade length, is a very useful acquisition. Spare blades should be kept in the toolkit, protected by soft wrapping.

## ★ FILES

Principal requirements are 6 to 8in. flat, half-round and round files with bastard teeth. Second-cut and fine-toothed versions will be found handy, and a small triangular file is useful for some special work. A set of ward files, or "jeweller's" kit, will be an aid when dealing with transistorised equipment. At least one handle for each set of blades is desirable.

## ★ BENCH-VICE

Small vices (or vises) that clamp on the edge of a table are available quite cheaply, but a good bench vice is needed for any quantity of service

work, proving itself as clamp, support, pressure tool, and even anvil when required. Jaw protectors in aluminium, tin-plate and wood-block are an extra that can save time and trouble for special jobs.

## ★ SUNDRIES

For radio service work, certain additional tools have proved their worth, including tweezers, a magnifying watchglass, jeweller's screwdrivers and British and Metric Allen Key kits. Special tools for transistor work have been developed, and are worthy of note. A small camel-hair brush and a larger type such as a pastry brush or one-inch paint-brush will be found useful both on wired chassis and printed-circuit work.

Clamps fashioned from crocodile clips, extension prods, wire grips and other "home-made" items should be kept in the toolbox ready for use. A torch, or other form of small portable bench light is often needed, especially when working with printed circuit boards. An electric drill and hand-brace, with a selection of bits, completes the basic "hardware" tools.

Many of the foregoing items are to be found in kits of tools, especially combined for radio service work. These are held in neat cases and enable the user to keep his tools tidy and in constant review, to keep them from rubbing and chipping together, which quickly blunts cutting edges, and to carry them with him when working away from his base. Their extra cost is offset by their convenience.


## ★ SOLDER TOOLS

The most important item of a radio service toolkit is the soldering iron or gun. Three main sizes will be needed: a large, 100-watt type, for tin-plate and chassis work; a medium, general-purpose type, about 25 watts, of good quality, which can be left on for long periods without deterioration of the bit or overheating of the handle; and a miniature type suitable for transistor work, some

*Fig. 3: A small soldering iron is a vital tool. It should be kept clean and used only for its purpose—not to lever wires from tags, etc. Larger types are necessary for work on chassis connections, screen plates, lugs, etc.*



*Fig. 4: Switch-cleaners, greases, oils, freezers and other bench aids are now available in aerosol containers for easy application. The long, flexible nozzle allows the right amount of switch-cleaner to be applied in exactly the right place.*

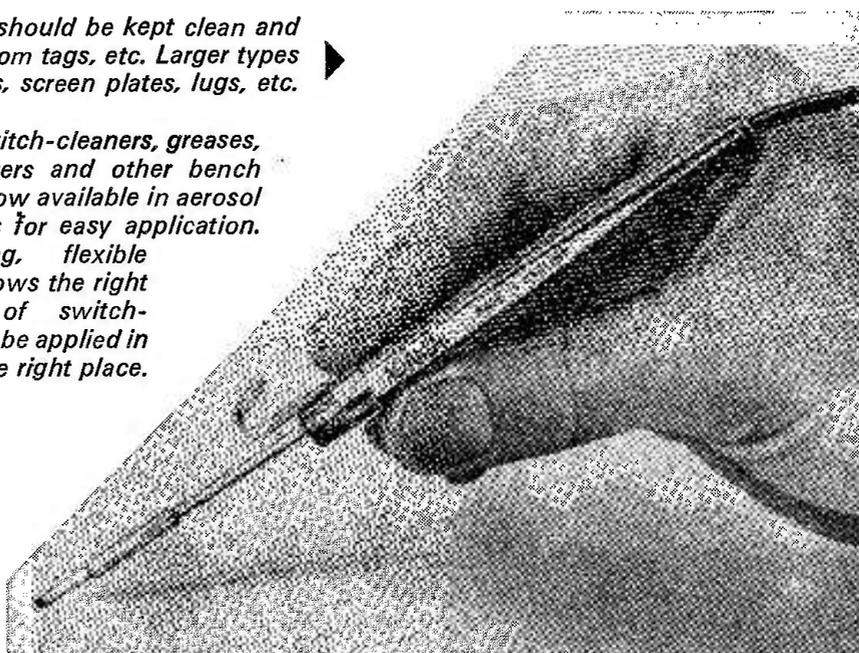

# repairing radio sets

of which are provided with shank guards to prevent the heat of the iron attacking closely-spaced components.

A solder gun is favoured by many engineers and hobbyists. The heat is applied only when the gun is activated by pressing a trigger or button. It is possible to apply more heat quickly in a small area of work but against this must be set the slightly heavier bulk of the tool compared with conventional electric soldering iron, shorter bit life (even though bits are more easily replaced, being mere loops of wire), and the waiting period of a couple of seconds while the bit heats up each time the tool is used. Some solder guns, and one or two conventional irons, have lamps mounted to throw a beam of light on the work at the tip. A few have solder dispensers.

Later versions, developed especially for dealing with printed circuits and multi-tag mountings, use aspirator techniques for drawing off the surplus solder as heat is applied. These can be a great asset for bench work that is likely to include a large number of transistor radios or other printed-circuit jobs. Some of the details of these tools will be dealt with more fully when we come to consider their applications.

## TEST GEAR

The depth of one's purse determines the amount and quality of test equipment that the workshop will contain. By following the constructional articles in *Practical Wireless*, *Practical Television* and *Practical Electronics*, a useful nucleus of test gear can be built at reasonable cost. (See Table 1.)

### ★ TEST METER

Basic requirement is a good test meter. This should preferably be a multimeter capable of measuring d.c. volts up to 1,000, current up to 100

microamps (with suitable ranges up to one or two amperes) plus resistance ranges capable of measuring both low ohms, (below 10) with accuracy, and from 1 to 20 Megohms also with a clear indication.

The sensitivity of the meter for radio work should not be less than 20,000 ohms/volt on d.c. A.C. measurements are less frequently required, and a 1,000 ohms/volt sensitivity may be adequate, as long as the ranges will cover 0—10 (for heater readings) and up to 500 volts for various mains and transformed input measurements.

Extending the ranges of such a meter is often a matter of adding probes with suitable resistance, and using series batteries to widen the ohms range coverage. The details of exact alterations should be available from the meter manufacturer where a commercial model is employed. Calculations that enable one to adapt instruments are fairly straightforward and will be found in several of the constructional articles that have appeared in these pages from time to time.

An important factor in choice of meter is the diversion of ranges. For example, transistor radio equipment will demand readings of 0 to 25 volts, with accurate determination of voltages as low as one-tenth of a volt. The most accurate readings are obtained in the middle third sector of a linear scale, and the instrument should be chosen with this point in mind. The marking of the scale is important, and provision of a knife-bladed pointer with rear mirror scale to avoid parallax error is extremely helpful for accurate work.


Some form of protective device is another aid that can save expensive repairs. Accidents happen in the best regulated circles! The form of cut-out used by Avo is well known and practically fool-proof, but all the leading meter manufacturers incorporate some form of meter protection and it is as well to become familiar with the instrument before committing oneself to any outlay. More will be said on this subject as the series of articles progresses.

Sensitivity of the meter was mentioned as a prime




A

Fig. 5: (a) A sensitive, robust meter like the Avo 9 is an asset for bench work and portable enough for field work. (b) A versatile small meter such as the Multiminor is indispensable for outside work.

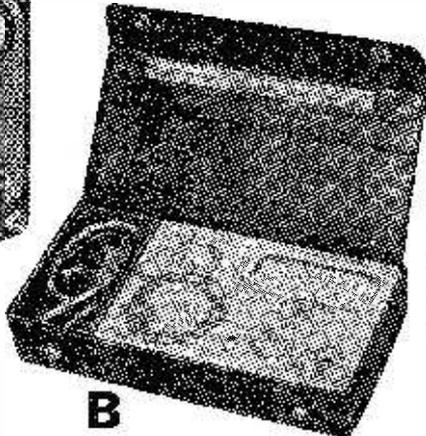

B

Fig. 6: Transistor testers are coming into more frequent use. The model illustrated makes "in-circuit" tests by balancing out the shunting effect of components in the transistor circuit. Measures collector voltage and current, current gain (Beta) and leakage current.

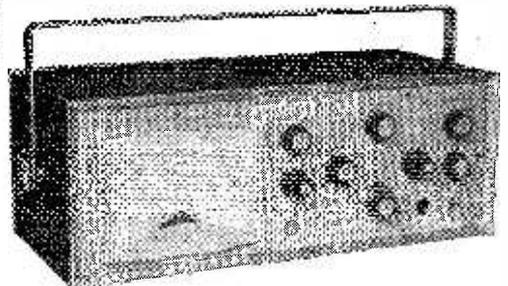

point. In this respect, the electronic testmeter scores. With a basic valve-voltmeter as its heart and an extremely high ohm/volt figure, it is a very efficient workshop instrument. For static work, its dependence on a power supply is no drawback. Many tests can be carried out with the valve-voltmeter that would be entirely misleading with less sensitive instruments.

Transistorised versions of electronic testmeters are now available, using battery supplies for field use. Some experience is needed in using this type of equipment, to avoid incorrect interpretation of results.

## ★ OUTPUT METER

Although the conventional multimeter can be used as an output meter, for more accurate results a correctly designed instrument is needed. Where a fair amount of audio work is undertaken, a good output meter comes high on the list of essentials. Output meters measure power and can be scaled directly in watts or decibels. Some interesting designs have been described in previous issues of *Practical Wireless*, and are worth further study.

## ★ SIGNAL INJECTORS

Signal injection can be carried out in one of several ways. For rough and ready tracing of the circuit—merely determining the signal path—a form of injector can be employed with no regulation of output, either as regards frequency or level.

A simple square-wave generator is a typical example, with frequencies in the audio range and sufficient output also in the intermediate and radio frequency bands to produce a noise at the output of the receiver. Several of these injectors are marketed, and constructional details of others have appeared from time to time. They are effective for rapid testing, enabling location of the fault to a particular section of the set. They do not permit quality testing, nor can they give more than a rough indication of stage gain. Nevertheless, such

instruments have their place, especially in field service, where their portability is a virtue.

## ★ SIGNAL GENERATORS

The signal generator, whether audio or r.f., modulated correctly, with a reasonably pure waveform and a regulated and calibrated output, is the instrument that the test bench is generally built around. The quality of the signal generator, which will be reflected in its cost, is based on the frequency accuracy, the stability, the pureness of the output waveform and the calibration of the output level.

The more ambitious types include crystal check frequencies as references and output monitoring, by a valve-voltmeter inbuilt and matched to the instrument, or by oscilloscope trace. Modulation should also be variable, although many standard service instruments employ a fixed modulation frequency and depth.

For frequency modulation alignment a sweep generator is needed, its output changing regularly in frequency over a determined band, again with controlled reference points which may be provided externally or be a built-in property.

The modulation frequency for a sweep generator is usually derived from an internal oscillator, but arrangements can be made to obtain this source from the timebase of an oscilloscope. It is in the combination of these two instruments that the most useful alignment set-up is obtained.

## ★ OSCILLOSCOPES

Oscilloscopes, giving a visual trace of the waveform being measured, have wide variations of specification. Basically, the oscilloscope is a voltage measuring device with an extremely high impedance loading to the circuit under test, presenting the least disturbance to it.

The cathode ray tube is one determining factor when choice is made; its size, persistence of the phosphor and sensitivity which limits spot size must be taken into consideration. Two other factors are


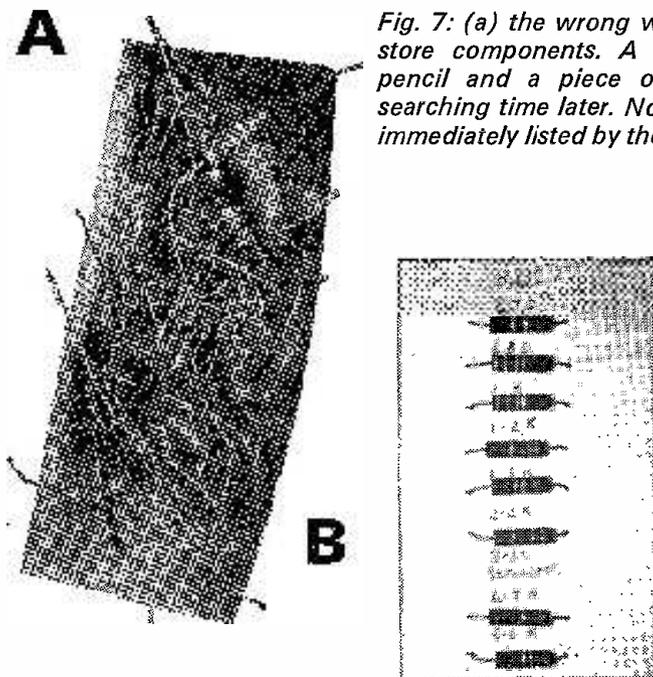


Fig. 7: (a) the wrong way, and (b) a better way to store components. A few minutes with marking pencil and a piece of card can save hours of searching time later. Note that replacements can be immediately listed by the obvious spaces on the card.

Fig. 8: Systematic storage of valves saves time and breakages. The Expanda-pack system used by Mullard can be adapted to make up a field kit, or used as a workshop storage system.

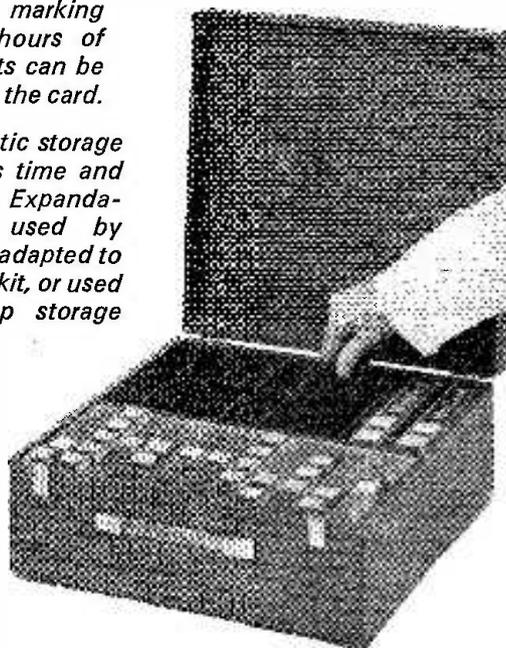

# repairing radio sets

the rise time and bandwidth of the Y-amplifier (or amplifiers, in the case of a double-beam instrument).

These two are linked, and limit the frequency response of the instrument. A greater bandwidth is needed for a faster rise-time, which would be needed for accurate display of a true square-wave signal. In practice some compromise is necessary and the frequency response of the Y-amplifier, falls off gradually at high frequencies giving a faster rise-time, while maintaining good overall response to prevent overshoot, which results in distortion of the trace.

The oscilloscope has an X-amplifier to permit expansion of the trace, to facilitate display of one or two cycles of the waveform in the viewing area of the tube. The repetition frequency of the time-base of the instrument must be equal to the frequency of the signal applied to the Y input to reduce the trace to one complete sine wave, which gives us another limiting factor.

Synchronisation of the timebase with the input frequency requires feedback of a small amount of test signal to the timebase under controlled conditions, which necessitates a "Sync" terminal, and if the amplitude of this test signal is made variable, a "Sync Control" will be fitted.

Further refinements are the synchronisation on either positive or negative waveforms, addition of repetitive triggering, with sensitivity control for this function and an inbuilt integrator for TV repair work. Some types have other facilities, such as a calibration output or a square-wave oscillator integral with the instrument. Choice of an oscilloscope depends both on the available funds and the work it is intended to do.

For comparison of signals and several special tests a twin beam oscilloscope is an advantage. This instrument has two Y-amplifiers, which may or may not be identical, and costs considerably more. Conversion of a single beam scope to a twin or split-beam type is possible by the addition of an external beam splitting unit. Details of these instruments, and their applications, will be found in the references listed in Table 1.

Applications of the instruments mentioned in the

**TABLE 1.—TEST GEAR**

A selective index of constructional articles on Test Gear, which have appeared in *Practical Wireless*, *Practical Television* and *Practical Electronics* during the past three years. (Where more than one successive article is involved, the symbol \* follows the initial month.)

## TEST METERS

"PW" Sixteen	Jan.	64	PW
Multitest with LCR Bridge	Aug.*	66	PW
Multirange Test Meter	Dec.	65	PE
Push-button Multimeter	Jan.	66	PW
Multimeter with electronic ohmeter	Sept.	64	PW
Simple multimeter	July	64	PW
A.C./D.C. volt-ohmmeter	May	65	PW
D.C. volt-amp-ohmmeter	June	65	PW
Comprehensive multimeter	June	65	PW
Direct reading frequency meter	April	66	PW
Add-on unit to increase sensitivity	Mar.	64	PT
Extending multimeter ranges	June*	64	PW
A.C. Millivoltmeter	Aug.	66	PE
Low-resistance ohmmeter	July	66	PT
Basic Moullin RF resonance voltmeter	Aug.	65	PW
Transistorised EHT voltmeter	Aug.	65	PT

## OSCILLATORS AND SIGNAL GENERATORS

AF/RF Signal Generator	May*	65	PW
Wide-range LF oscillator	Jan.	64	PW
Audio oscillator	April	65	PE
Audio oscillator with output meter	May	65	PE
Audio oscillator with valve-voltmeter	Nov.*	65	PE
Keyed audio oscillator	Mar.*	65	PW
Wien Bridge Transistorised audio osc.	Aug.	64	PW
Neon relaxation oscillator	Feb.	64	PW
Stable pulse generator	July	64	PT
UHF transistorised test oscillator	Nov.	65	PT
Grid Dip Oscillator	Feb.	66	PW
Colour Bar Generator	Feb.	65	PT

## SIGNAL INJECTORS AND TRACERS

Handy signal injector	Aug.	64	PW
-----------------------	------	----	----

Miniprobe signal injector	Jan.	66	PE
Widerange harmonic oscillator	April	66	PE
Simple noise generator	Sept.	64	PW
Pocket signal tracer	Mar.	64	PW
Inexpensive signal tracer	Mar.	64	PW
AF/RF signal tracer	Feb.	66	PE

## OSCILLOSCOPES, ETC.

Miniature oscilloscope	Nov.*	65	PW
Inexpensive oscilloscope	Mar.*	65	PE
Videoscope	Oct.*	64	PT
Videoscope modifications	June	65	PT
Oscilloscope from TV chassis	Feb.	66	PT
Oscilloscope amplifier	Mar.	65	PT
'Scope improvements	Sept.	65	PT
Probes (Test Gear Accessories)	Mar.*	64	PW
Beam switching unit	Aug.	66	PE
Electronic Gate trace doubler	April*	66	PE
Ellipse Generator	Aug.	66	PW

## BRIDGES, ETC.

Mutual and Self Inductance bridge	Aug.	65	PT
Inductance-Capacitance tester	Oct.	64	PW
"Ravenor" C-R bridge	Jan.	65	PT
R-C bridge	June	65	PE
Transistorised LCR bridge	Dec.*	65	PW
L-C Pico Meter	April	66	PT

## TRANSISTOR TESTERS

Simple transistor tester	Oct.	64	PW
Transistor and diode tester	Aug.	65	PE
Transistor tester	May	66	PE

**TABLE 2—BENCH AIDS**

A selective index of constructional and descriptive articles on Bench Aids which have appeared in *Practical Wireless*, *Practical Television* and *Practical Electronics* during the past three years. (Where more than one successive article is involved, the symbol \* follows the initial month.)

**POWER SUPPLY UNITS**

Stabilised power supply	July	66	PE
Compact power unit	Feb.	66	PE
Variable low-voltage d.c. supply	Dec.	64	PE
Basic stabilised power pack	Mar.	64	PW
Variable power supply—transistors	Jan.	64	PW
Transistor radio mains unit	June	64	PW
Regulated power for transistor receivers	July	65	PW
Stabilised 9 volts	June	65	PW
Stabilised 9 volts	June	66	PE
Low voltage battery pack	Aug.	65	PE
Thyristor power control unit	June	66	PE
D.C./A.C. Inverter	Feb.	65	PE
Low-powered d.c. inverter	Dec.	65	PW
A.C. mains voltage stabiliser	June*	65	PE
Mains voltage adjuster	Feb.	64	PW
Mains distribution panel	May	64	PW

**SUNDRY BENCH AIDS**

Attenuator unit	June	64	PW
Dummy aerials (test gear accessories)	Feb.	64	PW
Impedance matching unit	April	65	PE
Electrolytic tester	June	65	PT
CRT tester and rejuvenator	June	64	PT
Low voltage neon indicator	June	66	PW
Photocell circuits	Aug.	65	PW
Simple timing device	Jan.	65	PW
Photographic timer	Feb.	64	PW
Dual calibration standard	Nov.	64	PW
Light operated switches	Dec.	64	PW
Unit construction boards	May	64	PW
Making P-C boards	Feb.	64	PT
Making P-C boards	Mar.	66	PE
Heat sinks	Sept.	64	PW
Trimming tools	Mar.	64	PW
Practical service aids (tools, etc.)	Aug.	64	PT

previous notes, plus other less frequently used, aids to service, will be described at appropriate points in this series of articles.

**WORKSHOP TECHNIQUES**

Workshop techniques depend largely upon the equipment available and the scope of work to be carried out. Many of the aids to service are items which will not be on the general market—indeed, most engineers fashion tools and other aids for special purposes.

**★ IRONMONGERY**

Examples of these miscellaneous pieces of “ironmongery” are the heat shunts, soldering iron extensions for multiple tags, chassis clamps, solder brushes, trimming tools, angled tools and those with odd-shaped jaws. A collection can be built as needs arise.

Heat shunts can be made from crocodile clips with pads inserted or even “beds” of solder run between the jaws to form a smooth heat-conducting surface.

Iron extensions may be made from a twist of heavy-gauge copper wire formed to contact the tags to which heat must be applied, then wrapped at the free end around the iron bit.

Trimming tools are easily fashioned from plastic knitting needles and probes, printed-circuit hole cleaners, other aids to solder point manipulation and general purpose non-metallic blades fairly impervious to heat are easily whittled from small orange-sticks which can be purchased for a few coppers from any chemist.

**★ SPECIAL TOOLS**

Some special tools of frequent help are split-ended screwdrivers to release castellated nuts in confined spaces, angled flat and box spanners (the

last being angled at the tommy bar or clamp) and bent-end pliers.

Aerosol switch-cleaners that are not dangerous when used near plastics, etc., can now be obtained. In addition, an aerosol grease applier is marketed, which carries the light grease on a film of vapour and greatly aids application in previously inaccessible spots. Special fluids for cleaning of tape heads and guides and for tape lubrication are also obtainable and will speed service, where time is at a premium.

Jumper leads are devices that normally tend to clutter a service department. It is a great help to make up short leads with terminations to suit the jobs that are anticipated. To hang these neatly and in some order is the work of a few moments, but can save much time later. Similarly, attenuator pads, damping networks and matching devices can be ready-made and placed near to hand, correctly labelled for speedy selection.

**★ POWER SUPPLIES**

Power supply sources of many different kinds will be needed if any volume of work is undertaken. A fully comprehensive supply, adequately regulated, is a great asset, but tends to be both expensive and time consuming to construct.


It is a help to keep available small sources for the “popular” needs, such as transistor radios, pre-amplifiers, mixers and so on. These can be made up quite cheaply, and terminated in flyleads which allow testing to take place with the least inconvenience. A list of these bench aids is given in Table 2, which includes some of the other handy devices mentioned above.

The main supply to the bench should be isolated, for complete safety. An isolating transformer, ratio 1:1, or for a refinement, with selective voltage tapings to suit popular supply voltages, is not a cheap

—continued on page 46

# beginner's 3-ban

A.S. CARPEL

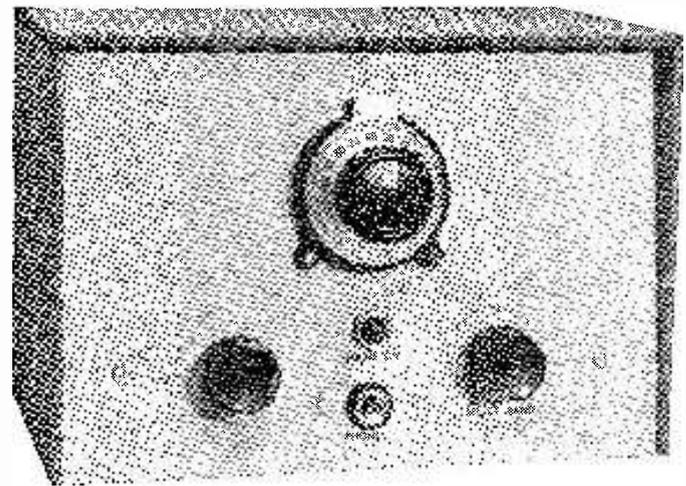

**T**HIS simple radio receiver can be built in 10–12 hours at a cost of approximately £4 10s., or less if the proverbial “junk box” is available, the valves may be purchased for about 2s. 6d. each. The receiver is a.c. mains powered and is completely safe to use at all times if built as described. All the coils are hand wound and easily copied. A few minor circuit changes mentioned later will enable the receiver to function in an alternative and even simpler mode. The receiver is of necessity a t.r.f. (tuned-radio-frequency) type and relies mainly on the use of variable positive feedback (regeneration) for sensitivity. This can, if not carefully adjusted, introduce instability, but the type of circuit chosen has the advantage of not affecting receiver tuning to any great extent.

## CIRCUITRY

The complete circuit diagram is given in Fig. 1. Signals from the aerial are inductively fed via coil LA to the valve grid choke RFC1 and pass via buffer valve V1 to the anode circuit. R.F. signals pass via C6 to the tuned grid circuit of V2, the

required signal being selected by means of VC1. Radio frequency chokes RFC1 and RFC2 function as loads for the signals. The cathode and grid 1 of V2 permit demodulation and audio frequency appears at the anode to be passed back via C9 and RFC1 to V1. Valve V1 now functions as a normal audio frequency amplifier and the signals selected may be heard when high impedance (4,000Ω) headphones are plugged in to socket J1. During this operation RFC1 and RFC2 function as filtering devices removing any unwanted r.f. from the

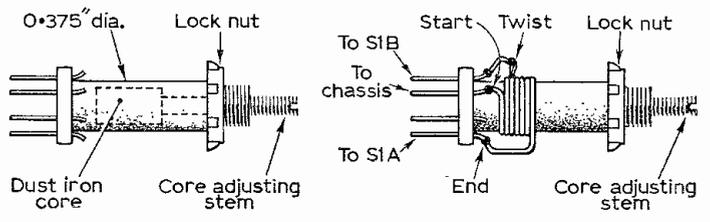


Fig. 2: Type of coil former used and method of winding.

audio signals. The phones are required to carry the direct current of V1 and are at h.t. potential; if this is objected to the “hot” (h.t.) end of RFC2 may be connected to the h.t. line via a 10kΩ resistor and socket J1 connected between chassis and the “hot” end of RFC2 via a 0.01μF d.c. blocking capacitor, leaving C4 *in situ*. The two chokes are seen to perform a double duty and must not be omitted.

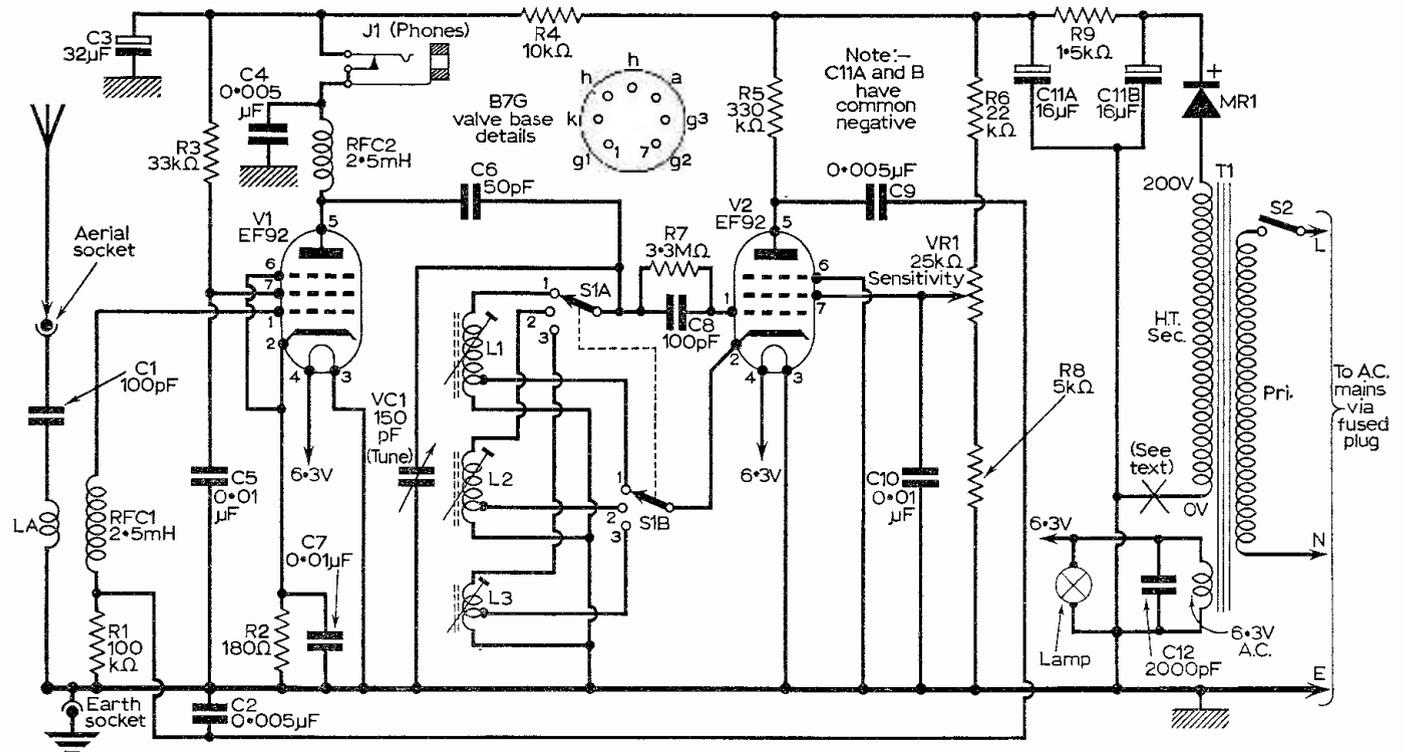


Fig. 1: Complete circuit of the reflex receiver.

# 1 mains receiver

VTEP

The relatively low sensitivity of the receiver is improved by including controllable regeneration around V2, the arrangement being that of an e.c.o. (electron-coupled-oscillator) with the valve cathode and grids 1 and 2 forming a triode. If VR1 is over-advanced V1 will oscillate and signal reception will be impossible; by keeping the stage at the edge of oscillation by adjustment of VR1, a high degree of sensitivity can be obtained and selectivity improved. When receiver tuning is changed VR1 must also be re-adjusted slightly. Since the grid circuit of V1 is untuned little r.f. gain results, the valve's purpose here is to act as a r.f. buffer and if V2 does break into oscillation such oscillations cannot reach the aerial and be radiated. The buffer stage also prevents the aerial from damping the tuned circuit. Powering of the receiver is simply and safely effected by utilising a small half-wave type mains transformer in conjunction with a contact-cooled rectifier and associated smoothing items.

## COILS

Coils are wound on 0.375in. dust-cored formers available from Denco Ltd., and three switched ranges are accommodated in the prototype receiver. The particular coil formers selected are designed to plug in to a noval valveholder and for a simpler band-changing system switch S1 may be omitted, a standard noval valveholder being mounted in-

Wire gauge swg enamelled	No. of turns (Total)	Tapping turns	Range in Mc/s
40	60	9	1.8-4.8
30	22	4	5.0-15.0
30	14	3	7.0-19.0
30	8	1.5	11.5-25.0

Table showing winding details of coils covering from 1.8Mc/s to 25Mc/s. Details are given in the text for a MW coil.

stead close to V2. Only three of the extra valveholder tags will be needed and the coil to be used will stand on the chassis upper surface conveniently placed for band-changing. Coil tuning is effected via VC1 coupled to a vernier reduction drive mechanism and direct driving, or the use of a larger value tuning capacitor, is not recommended. Various coil windings with details of ranges covered may be seen in the table and constructors may select as required remembering that the dust iron core fitted will permit of slight frequency variations.

Coil windings are secured by a layer of Sellotape or suitable adhesive. Each coil requires a tapping point connection and it is simplest to commence winding at the "earthy" end.


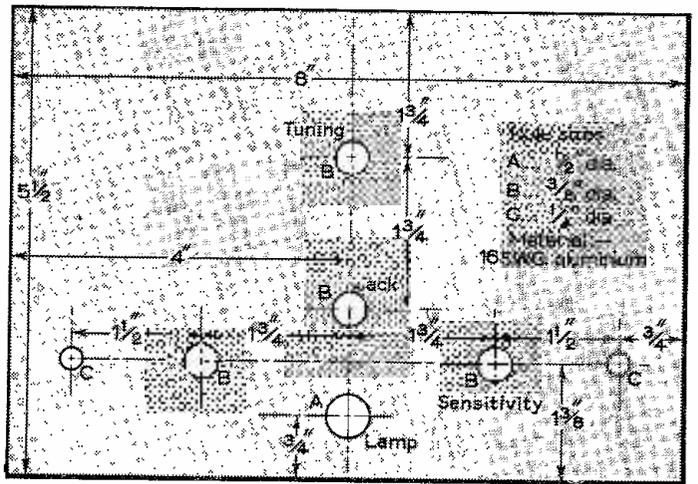
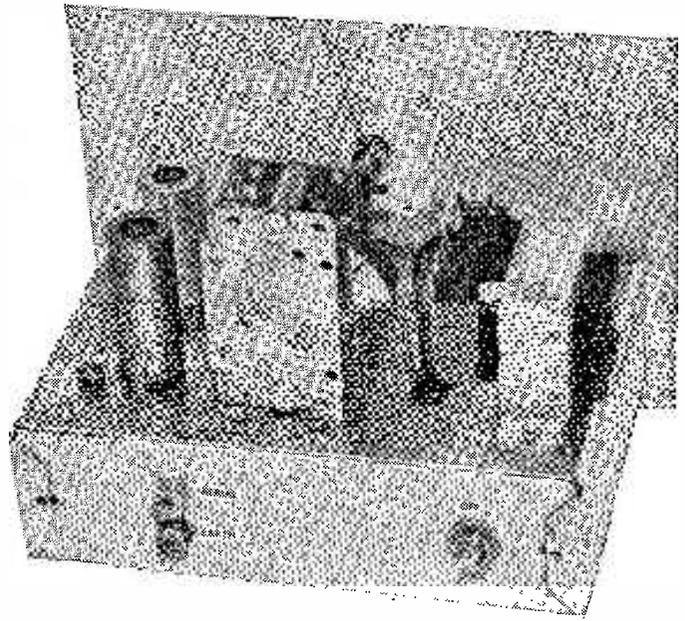


Fig. 3 (above): Front panel drilling details and dimensions. Fig. 4 (below): Layout of components above chassis and dimensions.

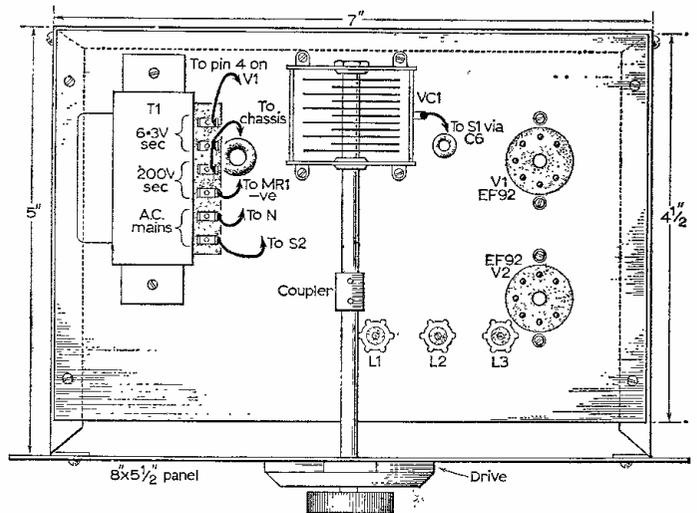

Referring to Fig. 2, solder one end of the wire, wind on the required number of turns, make the tap by twisting the wire, then add the remaining number of turns. Holding the complete winding firmly apply a layer of Sellotape, cut away excess wire, scrape off the enamel, then solder. Suitable enamelled copper wire may be easily salvaged from unwanted transformers, coils, chokes, etc., and the exact thickness is not unduly critical. The gauge

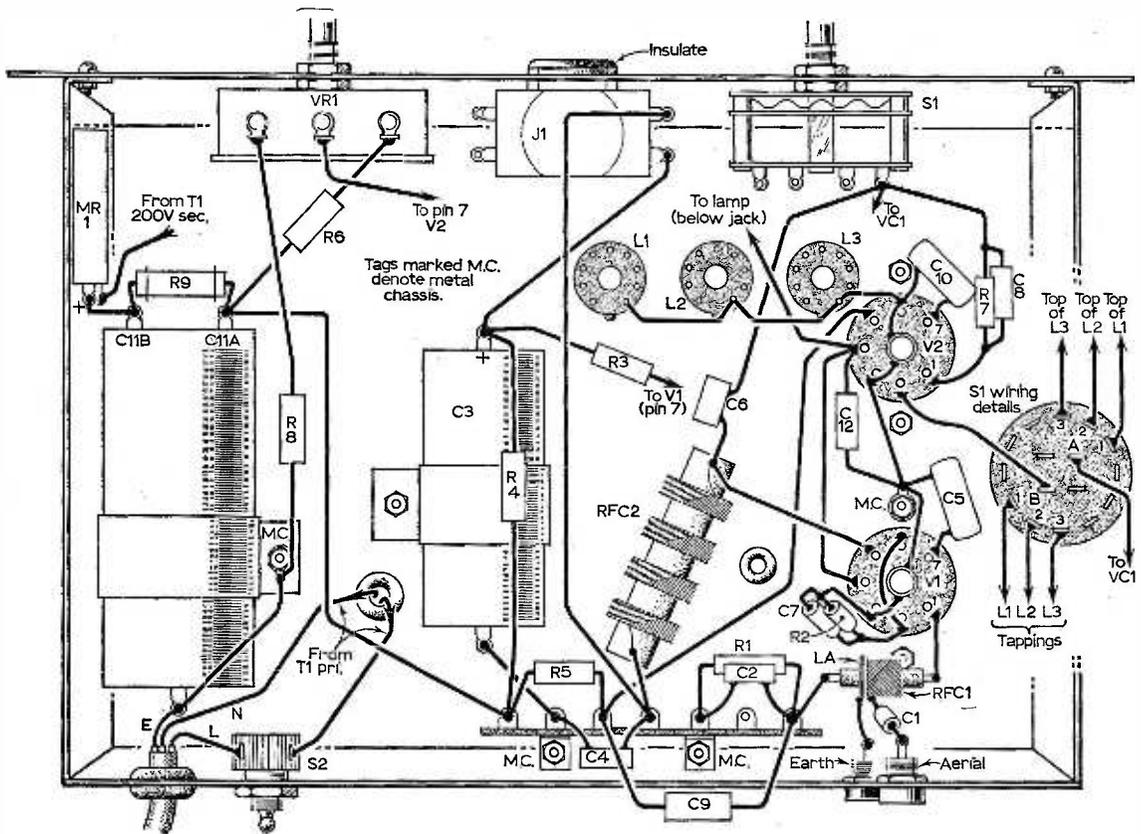


Fig. 5: Wiring and layout below chassis.

may be assessed by close winding some turns on to any dummy "former" and measuring the winding length with a ruler. The result may be compared with a book of "Wire Tables" but if a winding length of 0.5in. contains 36 turns the wire may be taken to be 30 swg.

Other ranges may be experimented with in addition to those shown in the Table and for Medium waveband coverage, 100 turns of fine wire—say 36 swg dsc—may be tried with a tapping at about 15–20 turns. Alternatively a commercial coil may be used; in this case some turns must be taken off carefully, the tapping made and the wire replaced as nearly as possible to its original form. If a commercial coil has a separate coupling winding, this and the main winding may be series-connected such that both windings are in the same direction; the junction of these two windings may then form the tapping point with the extremities going to chassis and S1A respectively.

### CONSTRUCTIONAL

Details of the front panel are given in Fig. 3, above- and below-chassis plans are detailed in Figs. 4 and 5. All the metal work is easily prepared using only a simple hand drill plus a few round and flat files. The chassis "box" is so bolted to the panel that the latter slopes slightly backwards; the chassis is a sectional type comprising of three sides plus a top plate. Choke RFC1 requires winding LA to be added (Fig. 6), this may consist of 20 turns of 36 swg dsc wire random wound over the "earthy"

end, in the case of a miniature ferrite type choke, or between two of the pies in a conventional type.

*Note:* Great care should be taken when fitting socket J1 for this must be completely isolated from the chassis and panel by means of insulating bushes or washers. Should J1 be in contact with

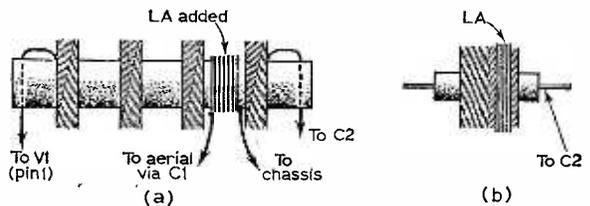


Fig. 6: Modifications made to RFC1.

the panel when the phones are plugged in the h.t. supply will be completely short-circuited to chassis and danger may result!

The tuning capacitor is not unduly critical and any small air-spaced variable of 150pF (maximum) may be used. Care should be taken with the wiring which should be rigid avoiding long, droopy leads.

### ALTERNATIVE CIRCUITRY

Although the layout is in no way super-critical the one shown in Fig. 5 has proved to be satisfactory and works out very well. The position of the mains switch for example is a matter of choice and it can be fitted anywhere to suit individual taste. Slight rearrangement to suit components to

hand will not alter the efficiency of the circuit to any real degree, although wide variation from the values of the components quoted is not advisable.

In Fig. 1 the receiver is a three-stage affair, viz., Buffer (V1), Demodulator (V2), Audio Amplifier (V1) but by making a few changes a simpler version is achieved. To simplify the design:— (1) Omit C1 and RFC1 (with LA) completely. (2) Omit capacitor C2 and connect the top of R1 together with the existing lead from C9 direct to V1 grid pin 1. (3) Lift the end of C6 connected to pin 5, V1 and connect it instead to the aerial socket.

The receiver will now function in two-stage mode, viz., Demodulator (V2), Audio Amplifier (V1). Some damping of the tuned circuit is likely to result due to the aerial and "dead spots" may be found on the dial but despite these disadvantages much of interest will be receivable. The effect of feeding the aerial, via C6, to the pole of S2B may also be tried and it might prove beneficial to connect a 15kΩ resistor across the Aerial/Earth sockets.

### TESTING

With no power applied the finished receiver should be checked with an ohmmeter to ensure that no direct short-circuit exists between the h.t. rail and the chassis and that except for the earthing pin, neither side of the mains supply plug is in connection with the chassis at either setting of S2. Particular attention in this respect should be given to socket J1 as mentioned earlier! If all is in order headphones may be plugged in, VR1 turned fully anti-clockwise, and aerial connected and also an earth if possible. The mains plug is then inserted and S2 closed whereupon both valves should glow. Signals should be heard when VR1 and VC1 are carefully adjusted but the detector valve should not be allowed to oscillate if at all possible since this will cause all signals to vanish! As VR1 is advanced towards its optimum point noise will be heard to increase and the improvement in sensitivity will become apparent; signals will seem to tune more sharply also. The h.t. rail voltage may now be measured and this should approximate to 230V d.c.

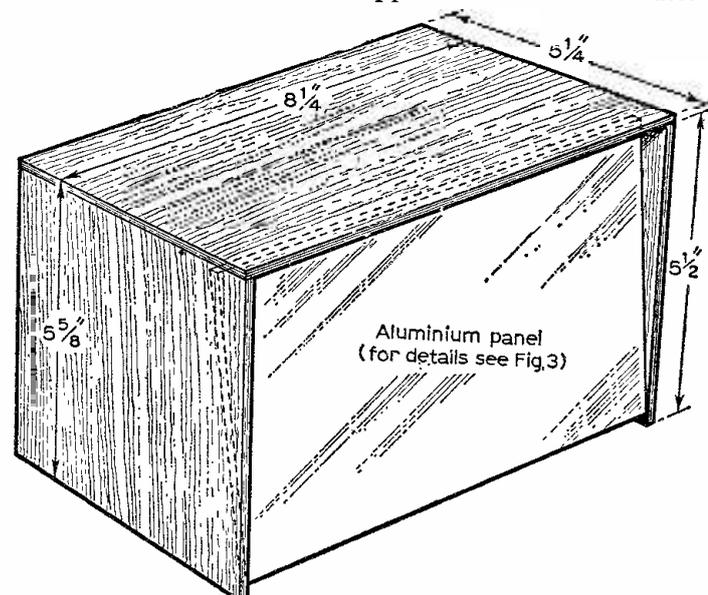


Fig. 7: Dimensions for a suitable cabinet. Details of the front panel are given in Fig. 3.

## ★ components list

### Resistors:

All 20% ½W except where stated

R1	100kΩ	R7	3·3MΩ
R2	180Ω	R8	5kΩ
R3	33kΩ	R9	1·5kΩ 1W
R4	10kΩ	VR1	25kΩ Potentiometer
R5	330kΩ		wire-wound
R6	22kΩ		

### Capacitors:

C1	100pF silver mica
C2	0·005 μF (5000pF) ceramic
C3	32μF, 350V D.C. electrolytic
C4	0·005μF (5000pF) ceramic
C5	0·01μF (10,000pF) ceramic
C6	50pF silver mica
C7	0·01μF (10,000pF) ceramic
C8	100pF silver mica
C9	0·005μF (5000pF) ceramic
C10	0·01μF (10,000pF) ceramic
C11	16+16μF, 350V d.c. electrolytic
C12	2000pF ceramic
VC1	150pF variable

### Rectifier:

MR1 Electrix Contact-cooled, 250V d.c. 50mA

### Valves:

V1/V2—EF92

### Chokes:

RFC1/RFC2 2·5mH

### Switches:

S1 4-pole, 3-way rotary (or 2-pole, 3-way)  
S2 Toggle type on/off, 250V d.c.

### Mains Transformer:

T1 Primary: 230V a.c. input.  
Secondaries: 0–200V 25mA, 6·3V 1A

### Drive:

Eagle Vernier type T-502.

### Chassis:

7 x 5 x 2in. Sectional type, plus panel 8 x 5½in.

### Miscellaneous:

Coil formers (3)—Denco 0·375in. diameter, Valve-holders (2) B7G, 6·5V 0·15A bulb, Lens and holder, Closed-circuit jack socket (Radiospares), Aerial and Earth sockets, Spindle coupler ½in., Spire clips (2), Grommets (3), 6BA nuts, bolts, washers, tags, material for casing, wire, solder, etc.

## CONCLUSION

To finalise the receiver fabricate a simple casing of faced hardboard, or paxolin. Grey-lacquer the panel and apply legends either by means of Letteraset symbols or transfers. The end product is an attractive little receiver capable of providing considerable pleasure. Do not expect "communications-type" efficiency however for after all the receiver uses but two valves and a handful of components! ■

## Mods for the R1155

I would like to put forward the following points which may prove useful to those using this set.

(A) The small metal panel formerly supporting the Meter Amplitude control can be replaced by one of insulating material on which can be placed a 50pF variable capacitor. The b.f.o. trimmer is then disconnected and the wires extended to the new control. The ease of operation on c.w. and s.s.b. is much enhanced.

(B) The rear portion of the b.f.o. box is cleared of components and a small bracket prepared to fit across it, on which are mounted the components of a Product Detector Stage, as in the April 1965 issue of *Practical Wireless*. This leaves the d.f. valve position next to the box vacant, one use for this valve base being a triode infinite impedance detector. The change-over switch from a.m. to s.s.b. is mounted on the front panel next to the wave range switch.

(C) A number of modifications such as adding an output stage, noise limiter, preamplifier stage Q-multiplier and valve type S-meter to replace the "magic eye" can be carried out very easily and neatly if all the d.f. components at the r.f. end of the chassis are removed and the wiring to the master switch and magic eye stripped off. The a.v.c. wiring to the Master Switch is re-routed to the Meter Balance position, where a DPST switch can be placed and the wires connected very conveniently. A metal panel 6in. x 5in. is now mounted vertically between the chassis and the main support bracket (this being countersunk so that the chassis will slide back into the case) next to the r.f. coils. The panel will accommodate four or five valves with B7G or B9A bases. According to the modifications being carried out, some may be horizontal and project over the tuning capacitor, or be fastened vertically to a bracket on the new panel. The exact mode of use will suggest itself to the constructor, but it will be found that all the wiring can be carried out conveniently, and above all, neatly. By this means also, the whole of the space beneath the chassis in this region will now be vacated. It is possible that a power supply could be fitted here, though most users have external PSU's.


By these means, considerable modifications can be made to the set without untidy wiring or interaction between stages.

**K. H. Ashcroft, B.Sc.,**

Wirral,  
Cheshire.

# NEWS AND..

## MIDGET FROM IKEGAMI

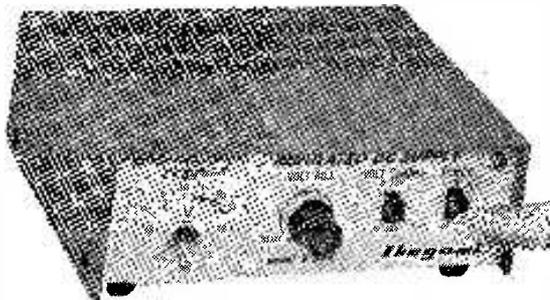

Claimed to be the smallest pack in the world, measuring 6 x 2 x 5in. and weighing less than 3lb. is the Ikegami regulated d.c. supply. Output voltage is d.c. 0-12V-24V. Output current is 0-400mA, regulation load is less than 30mV, temperature coefficient is 8mV per 1°C. Ripple is 3mV (p-p). The regulators are supplied with zip-carrying case. Price is £24 13s 6d. *Sole UK Agents, H. F. Collison (Goodwell Ltd.) High Street, Coleshill, Birmingham.*

## NORTHAMPTON MOVES—RHYL REVIVES

Due to the pressure of space, the Northampton Short Wave Radio Club, G3GWB, is moving to Kingsthorpe Community Centre, Kingsthorpe Hall, Northampton. Work is proceeding with the installation of transmitters on all bands up to 2m. Meetings will continue to be held on Thursdays at 7 p.m.

Sincere thanks are offered to Mr. T. Howard who has been the long-suffering host at the old Club Rooms at Duke Street.


The A.G.M. of the Flintshire Radio Society was held recently and after a dormant period of twelve months, the Club is commencing its 1967 programme with a new look.

The name has been changed to the Rhyl and District Amateur Radio Club and meetings are held at 8 p.m. on the second Tuesday of each month at the Rhyl Silver Band Rooms, off Windsor Street, Rhyl. Details from the Hon. Sec., A. Antley, GW3UTG, Fairholme, Fairfield Avenue, Rhyl. Tel. 1362.

## CANADA-BERMUDA PHONE CABLE

Cable and Wireless Ltd. and the Canadian Overseas Telecommunication Corp. recently announced their intention to provide a jointly-owned coax phone cable between Bermuda and Canada. Approximately 800 miles long, the new cable will have 480 circuits and a maximum capability of 640 telephone circuits.

## MULTI-WAVEBAND PORTABLE

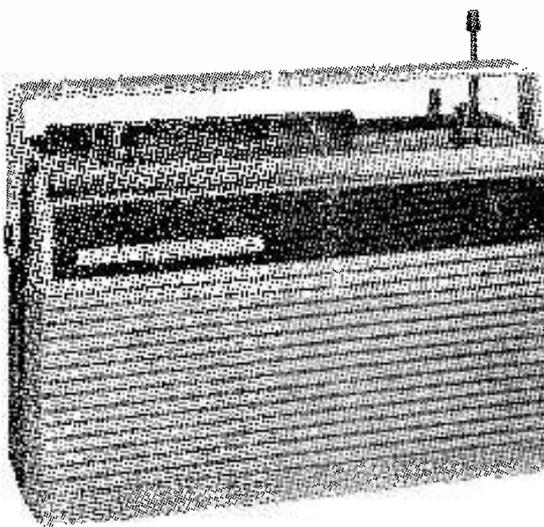


Recently announced is the 'Plein Feu', a de-luxe transistor portable from the French manufacturers Sonolor. It incorporates l.w., m.w. and four short wave bands. A car aerial socket with isolating switch is provided together with a tone control, telescopic aerial, dial light, 8 push-button controls and ear-phone/extension speaker socket. Recommended retail price is 23 guineas. Denham and Morley Ltd, 173/175 Cleveland St., London, W.1.

# ...COMMENT
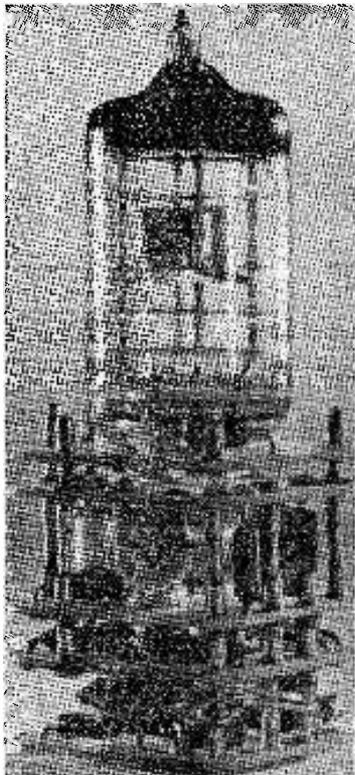
## RNLI GOES FOR BANTEX

Two new types of lifeboat, developed for the RNLI are being fitted with Bantex glass-fibre aerals. The first of these boats, a 48ft. 6in. class has recently been launched by Wm. Osborne of Littlehampton and represents a new self-righting design. Its electronic installation includes radar and maritime v.h.f. and u.h.f. communication with aircraft, plus echo sounder and direction finder. Mounted aft for radio telephone are twin 18ft. Bantex aerals built to withstand extreme conditions of high speed and severe weather.

The second type is a 44ft. boat built for high speed to the design of the U.S. coastguard vessel. For h.f. radio telephone they carry a single 18ft. aerial mounted on the fo'c'sle.



## LOW POWER MINI OSCILLATOR

A new temperature stabilisation technique employing a microelectronic circuit is embodied in a new range of miniature master oscillators announced recently by Marconi's Specialised Components Division. The oscillators which have a short term stability of 1 part in 100,000,000, have applications in airborne equipment and portable man-pack receivers.

The photograph shows the complete oscillator assembly removed from its aluminium case. At the top is the glass envelope containing the transistor can in which a crystal, microcircuit heater and a thermistor are housed. Beneath are the layers of printed circuit boards which make up the rest of the oscillator circuit. The trimmer which allows for 10 years of crystal ageing can be seen in the centre. The Marconi Company Limited, Chelmsford, Essex.

## FIRST IB CONVENTION FOR ROYAL LANCASTER

London and its newest hotel—the Royal Lancaster Hotel, Lancaster Gate, London, W.2, are to be the centre this year for the first International Broadcasting Convention, to be held from September 20 to 22, 1967. The Convention, organised jointly by the Electronic Engineering Association and the Royal Television Society, will comprise an exhibition of broadcasting equipment by leading manufacturers and a conference at which delegates can attend lectures by leading experts in all aspects of broadcasting.

## THIRD EDITION OF AVO MANUAL

Avo (MI Group) has produced the third edition of its Transistor Data Manual. This international reference book gives in-line data for more than 8000 transistors including those of Russian manufacture. A comprehensive list of transistor equivalents is included with commercial equivalents of Service transistors and connection diagrams. Copies of the manual are available from the Spares Department, Avo, Avocet House, Dover, Kent. Price in the U.K. postage paid is £2 5s.

## More on the R1155

The i.f. stages can be aligned without a signal generator by disconnecting the top cap of the frequency changer valve and poking the end of a few yards of insulated wire inside the first i.f. screening can. Broadcast signals from the Athlone 100kW transmitter on 566kc/s should be received without trouble and the i.f. transformers can be adjusted for peak output. This will align the i.f. strip to 566kc/s instead of 560kc/s but the error is only about 1% whereas many commercial signal generators have a calibration inaccuracy much worse than this.

U. Smith, G3UTI,

Darlington,  
Co. Durham.

## Ancient and Modern

Mr. A. W. Jenner P.W., February, 1967, asks for advice on Edison Cylinder reproduction.

The first essentials are a button stylus horizontally mounted i.e. tangentially to the cylinder and a pickup modified for response vertically and high lateral compliance. Considerable stylus pressure must be allowed for in the mounting.

The pickup, driven across the cylinder by the lead-screw should be free to move over two or three grooves to allow for shrinkage of old recordings.

Excellent recordings can also be made on these fascinating machines with far less trouble than cutting "acetate" discs.

If readers are seriously interested, I will reply in greater detail.

T. A. Bartlett, MBKS,  
Lusaka,  
Republic of Zambia.

## Simple Electronic Organ


I would like to thank people who have contacted me concerning my article on the construction of an electronic organ (page 657, P.W., January, 1967).

The use of a multivibrator circuit as the oscillator was satisfactory for the higher notes, but the lower notes lacked the deep bass quality which I wanted. I found (perhaps with the ear of faith) that the phase shift oscillator brought out the smooth deeper notes much better.

I now realise that using a 2½in. speaker was the main reason for failing to produce the most musical sounds. Since writing the article, however, I have been experimenting with methods of improving the tone without increasing the speaker size. The system which I find most satisfactory is to use the speaker as an "agitator" (as a reed in a clarinet) at the open end of a jam jar or tube of perspex which acts as a resonator.

J. M. Watt.

Northfield,  
Birmingham 31.

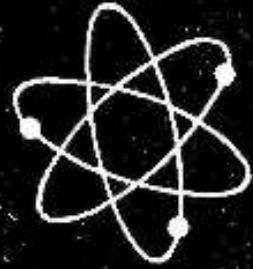

## R/C CIRCUITS WITH GAIN

K. T. WILSON

It is generally believed that resistance/capacitance circuits have less than unity gain: that is to say, the voltage or current out of such a circuit is less than that put into it. This might be thought to be true of all passive circuits—those which have no active components such as valves and semi-conductors. In fact, it is far from true. Take the transformer, for example, although it is a passive device, it can be arranged to give a good circuit gain.

The amount of gain from an R/C circuit is by no means comparable to what is possible from a transformer, but is sufficient for some purposes. The surprising thing is that gain is possible. However, to achieve gain, the R/C network has to be frequency conscious, has to be fed from a low impedance source and has to look into a high impedance—in just the same way a transformer has to achieve gain.

Analysis of the circuit given in Fig. 1 shows that the circuit will have zero phase shift at a given frequency. This frequency can be derived from the following formula:  $WT = \frac{1}{\sqrt{6}}$  where  $W$  is equal to  $2\pi f$  and  $T$  is equal to the product of the resistance and capacitance. At the resonant frequency the gain is approximately 1.03. Further examination of the circuit shows a strong resemblance to the somewhat familiar phase-shift oscillator. It is, in fact, of this class and the phase-shift is the reason for the gain. One may consider the circuit as an equivalent to the more conventional resonant circuit having inductive and capacitive elements.

If the circuit is so arranged that the output can be fed back to the input with zero phase shift, the circuit will oscillate at a given frequency—this can be found by the formula given earlier. It is also

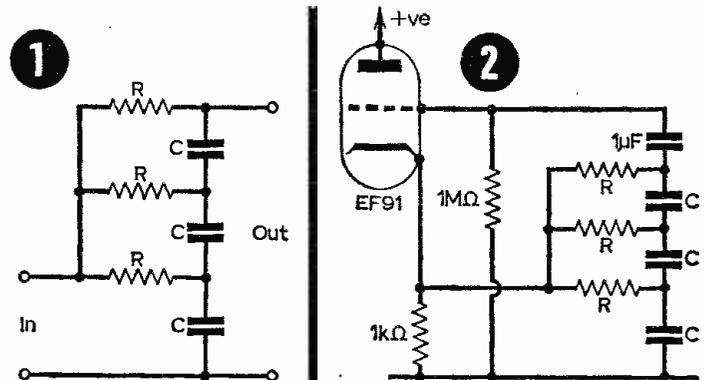


Fig. 1: At one specific frequency (depending upon the time constant  $CR$ ) it is possible to achieve gain with this arrangement.

Fig. 2: Cathode follower hooked to the basic Fig. 1 circuit for impedance matching, see text. Note: For 1,000c/s,  $R$  should be  $6.8k\Omega$  and  $C$   $0.01\mu F$ .

important that the output of the circuit looks into a high impedance and is fed from a low impedance source. This can be achieved using a cathode follower arrangement. Although the gain of the cathode follower is less than one (unity), the phase shift is zero, and the impedances are correct. The gain of the cathode follower can be arranged (using a high-slope valve) so that it is almost unity, and the coupling and biasing components selected not to introduce any further phase shift. If the slope of the selected valve is low, the circuit acts as a very selective amplifier, which 'rings' with a damped oscillation when a pulse is applied to its grid. The complete circuit is shown in Fig. 2. This circuit does not work with transistors, but might with F.E.T's although the author has not proved such a circuit.

## repairing radio sets

—continued from page 39

item, but should not be overlooked if work is anticipated on a.c./d.c. equipment, where one side of the mains supply is connected to the chassis of the test piece. Wrong connection can be harmful, even lethal, and it is wise to invest in safety.

### ★ SPARES

Store-keeping again depends on the amount of work anticipated. But whether one is running an economic workshop or simply pottering for amuse-

ment, systematic filing of service data, collecting of small spares and storing of larger ones makes life much easier.

Small items tend to get lost and damaged when tumbled haphazardly in the nearest cardboard box. In these days of increasing miniaturisation, valuable parts may be quite small and easily overlooked. A few moments spent in listing, filing and storing pay dividends later.

The foregoing may seem a counsel of perfection, but experience has shown that service work is so much a matter of applied logic that a logical approach to its practice is not only good economy but satisfying in itself.

To be continued

## DE LUXE PLAYERS

4-Speed Players 2-tone Cabinets 17 x 15 x 8 1/2 in. High Flux Loudspeakers and High Quality Amplifiers ready built. Quality output. Volume and Bass controls. Special instructions enable assembly in 30 minutes, only 5 wires to join. 12 months' guarantee.



### TO BUILD YOURSELF

Post 2/6 per item  
**PORTABLE CABINET**  
 As illustrated to fit standard player or autochanger. **69/6**  
**3 WATT AMPLIFIER**  
 Ready made and tested. With UCL82 triode pentode valve and **59/6** loudspeaker.  
**SINGLE PLAY UNITS**  
 BSR GU7 £4.19.6  
 Garrard SRP12 £4.19.6  
 Garrard SP25 £10.19.6  
 Philips AG101C £12. 9.6  
 Garrard A70 £19.19.6  
 Garrard LAB80 £24.19.6  
 Garrard 401 £29.19.6  
 Garrard Teak Wood Base WBL. Ready cut for mounting. 1000, 2000, 3000, SP25, AT60. **72/6**

**SUPERIOR AMPLIFIER**  
 Ready made and tested. Guaranteed better sound. Fully isolated AC Mains Transformer 4 watt output. ECL86 triode pentode valve. Volume and tone controls with knobs. Quality Loudspeaker **89/6**  
**AUTOCHANGE UNITS**  
 BSR Super Slim £5.19.6  
 Garrard 1000 £5.19.6  
 Garrard 2000 £6.19.6  
 Garrard 3000 £8. 9.6  
 Garrard AT60 with diecast turntable £10.19.6 **72/6**

**FULL WAVE BRIDGE SELENIUM RECTIFIERS:**  
 2, 6 or 12v. outputs, 1 1/2 amp, 8/9; 2 a. 11/3; 4 a., 17/6.  
**CHARGER TRANSFORMERS P. & P. 2/6 Tapped 200/250 v.**  
 for charging at 2, 6 or 12 v., 1 1/2 amps., 17/6; 2 amps., 21/-;  
 4 amps., 25/-. Circuit included. Amp meter 5 amp., 10/6.  
**WAVE-CHANGE SWITCHES WITH LONG SPINDLES.**  
 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way, 3/6 each.  
 1 p. 12-way or 4 p. 2-way, or 4 p. 3-way, 3/6 each.

**BARGAIN XTAL PICK-UP ARM** Complete with ACOS LP-78 Turnover Head and Stylus 20/-; Stereo 30/-  
**SPEAKER FRET** Tyran various colours, 52in. wide from 10/- ft.; 26in. wide from 5/- ft. Samples S.A.E.  
**EXPANDED METAL** Gold or Silver 12 x 12in. 6/-  
**NEW GARRARD GRAM MOTORS** 100-130v. A.C. 15/- pair for 200/250v. (in series), or 10/- each (Post 2/6).

## STELLA RECORD PLAYER AMPLIFIER

4 watt. 2 stage. 3 to 7 ohm. Neg. feed back. UCL82. UY85. 200-250v. A.C. tapped input. Chassis size 8 x 2 1/2 x 4in. high. Gold/Walnut knobs. Volume and Tone controls on separate Polished Wood Panel 6 x 2in. Brand new with makers' guarantee. Bargain price. Post 2/6 **78/6**

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350 v. . . . . 2/3	100/25 v. . . . . 2/-	8/600 v. . . . . 9/6	
4/350 v. . . . . 2/3	250/25 v. . . . . 2/6	16/600 v. . . . . 12/6	
3/450 v. . . . . 2/3	500/15 v. . . . . 3/-	18+16/500 v. . . . . 7/6	
16/450 v. . . . . 3/6	8+8/450 v. . . . . 3/6	32+32/450 v. . . . . 7/-	
32/450 v. . . . . 1/9	8+16/450 v. . . . . 3/6	50+50/350 v. . . . . 11/6	
25/25 v. . . . . 1/9	16+16/450 v. . . . . 4/3	60+100/350 v. . . . . 11/6	
50/50 v. . . . . 2/-	32+32/350 v. . . . . 4/3	100+200/275 v. . . . . 12/6	

### PAPER TUBULARS

350v.-0.1 9d., 0.5 2/6; 1 mfd. 3/-; 2 mfd. 150v. 3/-  
 500v.-0.001 to 0.05 9d.; 0.1 1/-; 0.25 1/6; 0.5 3/-  
 1,000v.-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1 2/6.

**E.H.T. CONDENSERS.** 0.001mfd., 7kV., 6/6; 20kV., 10/6.  
**SUB-MIN. ELECTROLYTICS.** 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mfd. 15v., 2/6; 500, 1000mfd. 15v., 3/6; 2,000mfd. 25v., 7/-  
**CERAMIC** 500v. 1 pF. to 0.01mfd., 9d. Disces 1/-  
**SILVER MICA.** Close tolerance (plus or minus ± pF.). 5 to 47 pF., 1/-; ditto 1% 50 to 800 pF. 1/-; 1,000 to 5,000 pF., 2/-  
**TWIN GANG.** 40-0° 208 pF. + 176 pF., 10/6; 365 pF., miniature, 10/-; 500 pF. standard with trimmers, 9/-; 500pF. midgeet less trimmers, 7/6; 500 pF. slow motion, standard 9/-; small 3-gang 500 pF. 15/8. Single "O" 365 pF. 7/6. twin 10/-  
**SHORT WAVE.** Single 10 pF., 25 pF., 50 pF., 75 pF., 100 pF., 160 pF., 5/6 each. Can be ganged. Couplers 9d. each.  
**TUNING.** Solid dielectric. 100 pF., 300 pF., 500 pF., 3/6 each.  
**TRIMMERS.** Compression ceramic 30, 50, 70 pF., 9d.; 100 pF. 150 pF., 1/3; 250 pF., 1/6; 600 pF., 750 pF., 1/9.  
**250v. RECTIFIERS.** Selenium 1/2 wa. 100mA 5/-; BY100 10/10  
**CONTACT COOLED** 1/2 wa. 60mA, 7/6; 85mA 9/6; Full wave 75mA 10/-; 150mA 19/6; T.V. rect. 10/-.

## MAINS TRANSFORMERS

	Post 2/6 each
250-0-250, 80 mA, 6.3 v. 3.5 a. Rectifier 6.3 v. . . . .	25/-
1a or 5 v. 2 a.; Ditto 350-0-350 . . . . .	29/6
MT.510 300-0-300 v. 120 mA, 6.3 v. 4a. . . . .	29/6
MINIATURE 200 v. 20 mA., 6.3 v. 1a. . . . .	10/6
MIDGEET 220 v. 45 mA., 6.3 v. 2 a. . . . .	15/6
HEATER TRANS. 6.3 v. 1 1/2 a., 8/6; 6.3 v. 4a. . . . .	10/6
Ditto tapped sec. 1.4 v., 2, 3, 4, 5, 6.3 v. 1 1/2 amp. . . . .	10/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. . . . .	25/-
1 a., 5, 10, 15, 20, 25, 30, 40, 45, 50, 55, 60 29/6; 2 a. 47/6.	
AUTO TRANSFORMERS 0-115-230 volt Input/Output. 150w 25/-; 500 w. 92/6; 1,000 w. 175/-.	

Tape Heads: Collaro 2 track 29/6 pair. B.S.R. 4 track 99/6.

## BAKER 12 in. STANDARD

The ideal High Fidelity Loudspeaker for high output at home or public address, etc. Built in concentric tweeter cone. Voice Coil impedance 15 ohms. Max. Power 20 watts. Bass Res. 40/50 cps. Flux 14,000 gauss. Voice Coil diameter 1 1/2 in. Response 40-14,500 cps. Chassis material Alcomax, overall dia. 12 1/2 in., overall depth 6in.



Price **£8** Post Free

CATALOGUE S.A.E.

**GROUP MODELS FOR VOCALS, BASS, LEAD and RHYTHM GUITARS**  
 30-10,000 cps. Voice Coils 15 ohms. Heavy Duty.

	'Group 25'	'Group 35'	'Group 50'
12in.	5gns.	12in. 8 1/2gns.	15in. 18gns.
25w.		35w.	50w.

**LOUDSPEAKERS P.M. 3 OHMS.** 2 1/2 in., 3 in., 4 in., 5 in., 7 in. x 4 in., 15/6 each; 8 in., 22/6; 6 1/2 in., 18/6; 10 in., 30/-; 12 in., 30/-; (15 ohms 35/-); 10 in. x 6 in., 30/-; 8 in. x 5 in., 21/-  
**E.M.I. Double Cone** 13 1/2 x 8 in., 3 or 15 ohm models, 45/-  
**Stentorian 10in.** HF1012, 25.10; 8in. HF812, 24.10; Crossover 35/-; Horn Tweeters 3-16 Kc/s. 10 w. 29/6; 20 w. 20 Kc/s. 99/6  
**JACK SOCKETS** Std. open-circuit 2/6, close circuit 4/6, Chrome Lead Socket 7/6. DIN 3-pin 1/3; Lead 3/6. Phono Plugs 1/-. Socket 1/-, Banana Plugs 1/-. Sockets 1/-  
**JACK PLUGS STANDARD.** Chrome 3/-, DIN 3-pin 3/6.

**DE LUXE TAPE SPLICER.** Cuts, trims, joins. For editing and repairs. With 3 blades. **14/6**

**4-CHANNEL TRANSISTOR MICROPHONE MIXER.** Add musical highlights and sound effects to recordings. Will mix microphone, records, tape and tuner with separate controls into single output. **59/6**

**PRIMO A.18 TRANSCRIPTION TONE ARM.** Complete with tracking template and two plug in shells suitable for mounting any cartridges. (Decca Deram Stereo Cartridges £4 extra). **5 gns**

**RETURN OF POST DESPATCH** Minimum P.P. Charge 1/6 unless otherwise stated. C.O.D. 5/- extra. Full List 1/- **CALLERS WELCOME**  
**RADIO COMPONENTS SPECIALISTS** 337 WHITEHORSE ROAD, WEST CROYDON  
 Written guarantee with every purchase. (Export—send remittance and extra postage, no C.O.D.) (Buses 133, 68 pass door). S.R. Stn. Selhurst. Tel. THO 1665

# Get these ALL-PURPOSE casuals!

**Trousers specially made for hard wear indoors and out**

Whether you're up and doing as a handyman or just at leisure you need these "WINWEAR" all-purposetrousers. In pure combed cotton and with superior tailoring they will give you years of service—plus comfort and fit.

**PRE-SHRUNK . DRIP DRY . TURN-UPS**  
**SELF-FITTING . PRACTICAL SIZE POCKETS**  
**BACK POCKET . ZIP FASTENING**  
**SANDY FAWN or LIGHT NAVY**

**POST NOW** To Mr. JOHN BEST, W.S.R. Ltd., (W.2.) 15-17, LONG ACRE, LONDON, WC. 99

Please send me the "WINWEAR" all-purpose trousers in size:  
 Waist.....ins. Inside leg.....ins.

**COLOUR SANDY FAWN**  **LIGHT NAVY**

I enclose  Postal Order  TICK ONE  Cheque 47s 6d. No.....

If sending cheque write name and address on back

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

WRITE IN BLOCK LETTERS (W.2.)

**ONLY 47'6 POST PAID**

**HOW TO ORDER**

Available in these sizes:  
**WAIST:** 30" 32" 34" 36" 38" 40" 42" 44" 46"  
**INSIDE LEG:** 29" 30 1/2" 32"

**COLOURS:** SANDY FAWN or LIGHT NAVY.

Write on coupon your waist and inside leg size, and tick colour required. Add your name and full postal address (in block letters) and send with remittance 47s 6d to:

**Mr. John Best, W.S.R. Ltd. (W.2), 15-17 Long Acre, London W.C.99**

Cheques or postal orders should be made payable to W.S.R. Ltd, and crossed " & Co." If sending cheque please write your name and address on back.

You are guaranteed money refunded if not completely satisfied, provided the garment is returned in absolutely new and unworn condition within 7 days of despatch to you. This offer does not apply in Eire or Overseas.

**QUALITY MEN'S WEAR BY W.S.R. LTD.**

## QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside table, tea, baby's food, etc. 19/6, post and insurance 1/6.



## 9 VOLT PRECISION MOTOR

Intended for driving battery operated tape recorders and record players. Laminated, 6 Pole Armature with Brush Gear and Rapid start switch. Normally 25/- . Our Price 7/6 plus post and insurance 1/6.



## MINIATURE WAFER SWITCHES

	Number of Positions				
	2	3	4	6	12
1 pole	3/6	3/6	3/6	3/6	3/6
2 pole	3/6	3/6	3/6	3/6	3/6
3 pole	3/6	3/6	3/6	3/6	3/6
4 pole	3/6	3/6	3/6	3/6	3/6

Any 12 switches ordered together 36/-.

## SILICON PLANAR TRANSISTORS

2N2926—general purpose type. Suitable for A.F. or H.F. up to 200 mcs, 3/- each or 4 for 10/-.

## GANGED POTS

Standard type and size with good length of spindle—made by Morganite. List price is 10/- each but if you act quickly you can have them at 12/- doz. (or 1/6 each if less than doz). Following values in stock all "lin"—5K + 5K—10K + 10K—100K + 100K—500K + 500K all new and unused. Post 2/8 on 1st doz. then 1/- per doz. 6 doz or more post free.



## ROLLER BEARINGS


You will find plenty of uses for these under anything which has to be moved, trolleys, sliding trays, etc. Made by Hoffman, approx. 2 1/2in. o.d. Offered at 4 for 10/-, post 4/6 + xtra.



Vacuum Cleaner Flex. Non-kinkable ribbed rubber, most pliable but very tough. 24/30 Cores. Normally 1/3 per yard, offered at 23 per 100 yard coil, post and insurance 8/6.

Sub Miniature Silicon Diodes. General purpose type with gold plated leads, 1/- each, 10/- per doz. Silicon Rectifier, equiv. BY100. 750 m.a. 400v., new, perfect. 6 for 21, post free.

## BUILDING SOMETHING?

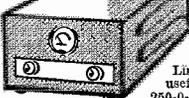

This may save you a lot of time and money. Ex

### Reditone Noise Limiter Unit

has most useful power pack with 250.0-250v 100 m.a. H.T. plus 2 x 6.3v. secondary windings and standard primary fused and with adjustment 200-250v. H.T. is provided by ZB280 rectifier and 4 smoothing condensers. The power unit is housed in the very nice laured metal cabinet, size approximately 10in. x 10in. x 7in., on the front is a 2in. flush moving coil meter scaled d.b. Also five pre-set controls behind a removable panel. Within the unit is a 10in. x 10in. chassis on which the power pack is mounted. There are also five wire holders, but a lot of clear space for anything you want to fit. Below the chassis there is an assortment of tag panels and components. All new and unused, offered for less than the value of the power pack alone, 49/6 plus 10/- carriage and insurance.


## SEMI-CONDUCTOR BARGAINS

Type	No.	Price	Type	No.	Price	Type	No.	Price
2N1727	15/-	MAT101	8/6	OC71	3/6			
2N1728	10/-	MAT120	7/9	OC72	5/6			
2N1742	25/-	BLAT121	8/6	OC75	6/6			
2N1747	25/-	AL5	5/-	OC76	5/6			
2N1748	10/-	OA10	6/-	OC77	7/6			
AC107	9/-	OA47	3/-	OC78	5/6			
AC127	9/-	OA70	3/-	OC78D	5/6			
ACY17	8/6	OA79	2/6	OC81	5/6			
ACY18	5/6	OA81	2/6	OC81D	5/6			
ACY19	8/6	OA85	2/6	OC82	5/6			
ACY20	5/6	OA90	2/6	OC83	5/6			
ACY21	6/-	OA91	2/6	OC84	5/6			
ACY22	4/6	OA200	3/6	OC189	9/6			
AF114	4/6	OC202	1/3	OC203	12/6			
AF115	7/6	OC23	10/-	OC170	5/6			
AF116	7/-	OC23	17/6	OC171	6/6			
AF117	5/-	OC24	15/-	OC200	9/6			
AF118	10/-	OC26	7/6	OC201	12/6			
AF139	12/6	OC28	15/-	OC202	12/6			
AF156	17/6	OC29	17/6	OC203	12/6			
AP212	15/-	OC35	15/6	OCPT1	15/-			
ASZ21	15/-	OC36	15/-	ORP12	8/6			
BC107	14/6	OC42	6/6	ORP60	5/6			
BY100	4/6	OC44	4/-	SB078	8/6			
BY213	7/6	OC45	3/6	SB205	8/6			
MAT100	7/9	OC70	4/-	SB251	10/-			

S.C.R.s (THYRISTORS) 7/6, 12 amp, 15/- 400 v. 100 v. 1 amp, 6/6, 3 amp, 17/6, 5 amp, 22/6, 25 amp, 23, 50 v. 1 amp, 6/6, 3 amp, 7/6, 10 amp, 10/- 25 amp, 30/-.

## THE VECTRONOME


## CAPSTAN DRIVEN TAPE RECORDER

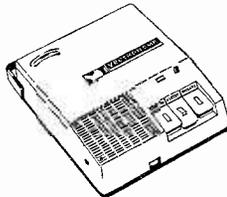


This is a truly portable self-contained instrument with built-in microphone and loudspeaker using a 7 transistor amplifier with P.P. output and suitable for operation from mains or by rechargeable batteries. Tape capacity is 25 minutes on easily change spools. A tape position indicator gives quick reference to any part of dictation. Recording level is automatically preset during dictation and can be adjusted to suit operator. Interlock prevents unintentional erasures. Tape speed controlled by fly wheel driven capstan. Very portable in neat case with carrying handle, overall size of which is approximately 9 1/2 x 7 1/2 x 2 1/2 in. with rechargeable main unit but less batteries. 25.19.6 (rather less than 1/3 original price). Postage and insurance 7/6. Unused and in perfect working order.
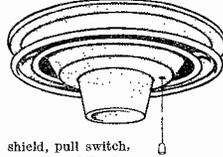
## HEAT AND LIGHT UNIT

Bring luxury to your bathroom—have comforting heat where you now only have light—all the parts to build full size (16in. diameter) model are now available—you will build it in an hour—12in. 750 watt circular silica glass encased element—opal bowl for up to 100 watt lamp—non-rust spin reflector—white enamelled base heat shield, pull switch, magnificent unit as sold normally at 44.5.0 only 49/6 plus 7/6 carr. and insurance.



## THIS MONTH'S SNIP

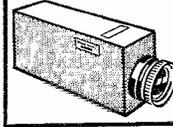

### Cine Camera for 19/6

16 mm. motorised (24 V. for 16 frames per second, contains film 1/8.5 triple anastigmatic lens and spool to carry 25ft. of film—probable cost around 25.0, brand new. P. & F. 6/6.



### EX-WD BARGAIN—Easily rebuildable to short wave radio

This is the 46 Receiver/Transmitter. It has a range of approx. 5 miles. Operates from dry batteries. Complete with six valves and in metal case. Size approx. 12in. x 6in. x 3 1/2in. Complete but less crystal, not tested nor guaranteed. 19/6 plus 4/6, post and insurance. Should not be operated as a transmitter in the U.K.

## SOLID STATE IGNITION

Big things are claimed of Electronic Ignition systems and if you would like to try for yourself a circuit was described in *Practical Electronics* (Sept., 1966). This requires a silicon controlled rectifier, four transistors and other components available as a kit. Price 26.15.0, post free.

## SUPERTONE G.C.V.

Saves you work—It's partly built!

Like its predecessors this latest Supertone has full fl performance—such as only a good wooden cabinet and very bifidus speaker can give, and due to its being partly built you will have it going in an evening. Note these features:


- All Mullard Transistors including 3 x AF117.
- Two-tone Cabinet, size 11 x 8 x 3 1/2 in.
- All circuit requirements—Push pull output—A.V.C. and feed back, etc.
- Printed circuit board all wired only connections, e.g. to Volume control W.C. Switch and Tuning Condenser.
- Pre-aligned IF stages complete with full instructions. Price only 23.19.6 plus 6/6 post and insurance.



## DRILL SPEED CONTROLLER

Correct speed electronically without loss of power. Complete kit, case, thyristor, rectifiers, wire wound pot, etc.

Only 19/6, plus 2/6 p. & p.

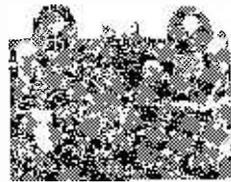

### 750mW TRANSISTOR AMPLIFIER

4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feedback loop—sensitivity 5 m/v. PRICE 19/6. Post and Insurance 2/6. Speakers 3in. 12/6; 5in. 13/6; 6 x 4in. 14/6.

## See in the Dark INFRA-RED BINOCULARS



These infra-red when fed from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lenses for T.V. cameras—light cells, etc. (details supplied) The binoculars form part of the Army night driving (Tabby) equipment. They are unused and believed to be in good working order but sold without a guarantee. Price 23.17.6, plus 10/- carr. and ins. Handbook 2/6.

## FLUORESCENT LIGHT KITS

Comprising choke, lampholders, starter and two chrome tube clips. 20 watt 19/6, 40 watt 11/6, Super Silent 40W 17/6, 80 watt 17/6, 65 watt 19/6. All 4/6 P. & P.

## THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouse, airing cupboard. Has spindle for pointer knob quickly adjustable from 30-80°F., 9/6, plus 1/- post. Suitable box for wall mounting, 6/-, P. & P. 1/-.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjust this from 50-550°F. Internal screw alters the setting so this could be adjustable over 30° to 1000°F. Suitable for controlling furnace, oven kiln, immersion heater or to make flame-start or fire alarm. 8/6, plus 2/6 post and insurance.

## SUPPRESSOR CONDENSER

Stop your drill or other appliances interfering with you or your neighbours' radio or television. Simple instructions given, 1/6 each. 12/- dozen.

## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500 mA (class B working). Takes the place of any of the following batteries: PL, PP3, PP4, PP5, PP7, PP9, and others. Kit contains: mains transformer-rectifier, smoothing and load resistor, 5,000 and 500 mfd. condensers. Zener diode and instructions. Real snip at only 14/6, plus 3/6 postage.

O-one Generator. Removes smells and creates an invigorating atmosphere. Ideal bedsteads, etc. Ready made in enamelled case 22/6, plus 4/6 post and insurance.

20W. Speaker (British Rating). This is a beautifully made Hi-fi reproducer with heavy duty 10,000 line magnet and 3in. voice coil, gives really fantastic results. In Saple Veneered enclosure, 27.15.0 plus 10/- carriage and insurance. Guitar model in fabric covered carrying case, 27.15.0. Either speaker supplied less enclosure, 24.19.6, plus 10/- carriage and insurance.

Twin Twisted 14/86 Flex Cable. Maroon cotton covered still the best for lighting drops, 50 yard coil, 15/- post 4/6.

PP3 Eliminator—play your pocket radio from the main! Save 4/6. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions. Only 6/6 + 1/- post.

## NO SOLDERING POCKET 3

Lots of fun to build and good results when finished—complete kit with detailed instructions and crystal earpiece batteries, 1/2d. extra — 25 value only 19/6, plus 3/- post & ins.

## SILICON RECTIFIERS

Tested and guaranteed

750mA	100v. 1/3	1 Amp	100v. 3/-
	200v. 1/6		200v. 3/-
	400v. 3/6		400v. 6/-
3A	100v. 3/6		
	200v. 5/-	10 Amp	100v. 9/6
	400v. 7/6		200v. 12/6
	600v. 9/6		400v. 14/6

Sub miniature glass encased—only approx. 3in. long wire ended.

750mA	50v. 1/6	100v. 2/6
	200v. 4/6	400v. 6/6

Where postage is not definitely stated as an extra then orders over 23 are post free. Below 23 add 2/6. Semi-conductors add 1/- post. Over 23 post free.

# ELECTRONICS (CROYDON) LIMITED

(Dept. P. W.) 102/3 TAMWORTH RD., CROYDON, SURREY (Opp. W. Croydon Stn.)

also at 266 LONDON ROAD, CROYDON, SURREY

# IMPROVING CHEAP TAPE RECORDERS

W. S. FOWLER M.A.

**L**AST month details were given for fitting an electric remote stop/start control to portable transistor recorders, and for varying the record and playback speed of the machine.

The amplifier section of a transistor tape recorder commonly consists of a four transistor circuit as shown in Fig. 3. As the signal from the tape head is only of the order of a few millivolts, a quite sensitive circuit is necessary and this readily lends itself to modification to increase the usefulness of the apparatus. As the amplifier alone is to be used, the stop/start jack previously described should be first inserted, in order to prevent the tape motor from operating unnecessarily.

## STRAIGHT AMPLIFIER

To use the tape recorder as a straight amplifier, the only modification required is to break the input circuit at point "X" in Fig. 3. Removal of the tape head cover usually reveals red and black leads connected to the record/playback head. The red lead should be broken and connected across the contacts of a miniature jack socket. The socket itself can be mounted at some convenient point on the cabinet, preferably choosing a non-metallic section, in order to avoid accidental short circuiting through the jack fixing nut.

When a jack plug is not inserted, the tape recorder circuit functions normally. Insertion of the jack disconnects the tape head and puts one of

the auxiliary circuits (shown in Figs. 4-8) into operation. The main function switch on the recorder is set at "playback".

An alternative method of tapping into the amplifier consists of using the existing microphone input socket. In this case the recorder is set to the "record" position and the loudspeaker muting connections are by-passed by fitting a small switch across the contact points. The speaker must normally be muted when recording from the microphone in order to avoid acoustic feedback which would result in howl.

Figure 4 shows a simple diode receiver circuit, using approximately seventy turns of 26 swg wire wound on to a 4 inch ferrite rod of  $\frac{3}{8}$  in. diameter. The OA81 diode is tapped off ten turns from the aerial end of the coil. Tuning is provided by a 500pF solid dielectric capacitor, connected in parallel with the tuning coil. This covers the medium wave band. The Light Programme on long wave can be brought in by shunting a fixed capacitor of about 0.002 $\mu$ F across the tuning coil.

Figure 5 shows an alternative form of tuner in which the station selection is achieved by moving the ferrite rod in or out of the coil former. Some of the early TV converters which used slug tuning provide useful components for cog and ratchet drive for the ferrite rod.

One of the difficulties of the simple diode circuit lies in the fact that the load is heavily damped by

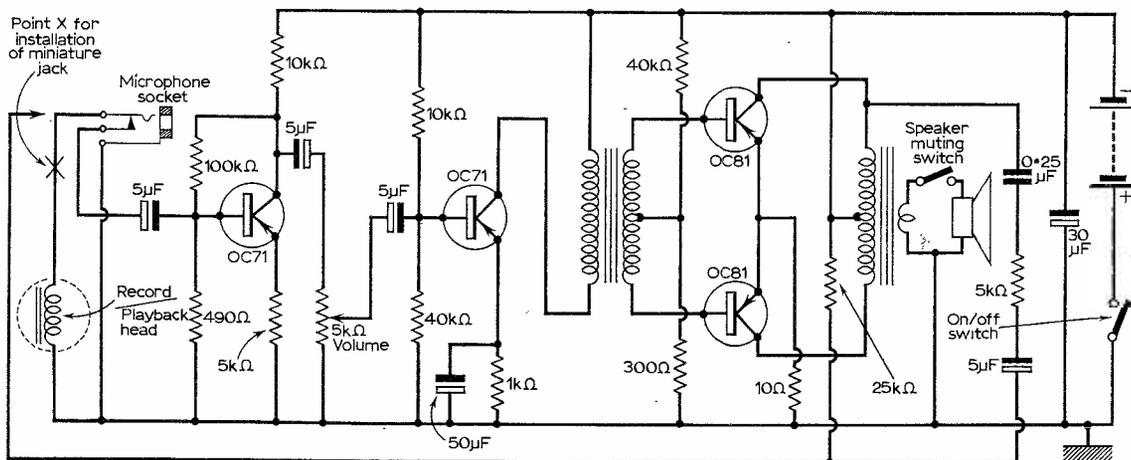


Fig. 3: Typical amplifier section of a transistor tape recorder.

the input side of the first transistor in the tape recorder amplifier. In poor signal areas this leads to loss of sensitivity and poor station selectivity.

Figure 6 shows a single transistor tuner circuit. The transistor is used first as an r.f. amplifier; the signal is then detected in the diode circuits and amplified, by reflexing, by the same transistor, before being fed, via the coupling jack, into the tape recorder amplifier.

The tuning coil consists of 76 turns of 26 swg wire wound on a five inch ferrite rod of  $\frac{3}{8}$  in. diameter. The bottom tap is taken ten turns from the "earthy" end of the winding. A good r.f. transistor such as the OC44 is essential here. The coil covers the medium waveband and once again, the Light Programme can be brought in on long wave by the parallel addition of a fixed capacitor of about 0.002—0.003  $\mu$ F.

If the power supply is to be separate, a miniature cell of the Mallory Mercury type may be used. The whole assembly can be arranged within very small dimensions, with the jack plug itself rigidly mounted to the assembly casing. It should be remembered that the proximity of metal reduces the efficiency

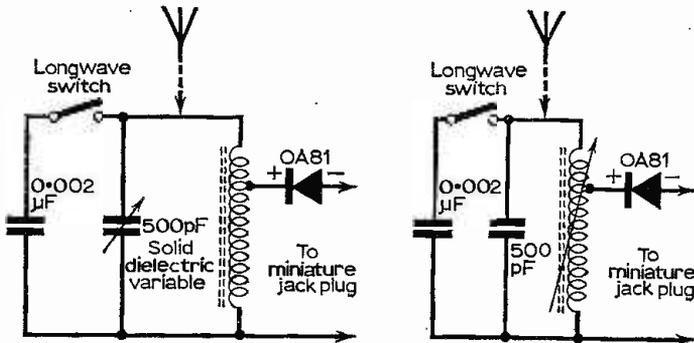


Fig. 4 (left): Simple capacity tuned radio jack.  
Fig. 5 (right): As Fig. 4 but permeability tuned.

of the ferrite rod considerably. Alternatively, in some tape recorders, the complete unit can be mounted inside the tape recorder case. The normal tape recorder amplifier battery supply can then be utilised to power the tuner.

Use of the remote electric stop-start control will enable the tape recorder motors to be brought into play, thus permitting the recording of the tuner signal, if required.

Figure 7 shows the utilisation of the recorder amplifier for baby alarm and intercom. purposes. The simple carbon "war surplus" mikes are very suitable for this purpose, and are energised via a bell battery and small step-up transformer. It is important to note that where long leads from the microphone are necessary these should be arranged on the low impedance side of the circuit (i.e. the step-up transformer should come directly next to the amplifier input). If this is not done, considerable hum and loss of volume will be caused.

An alternative to the carbon microphone is the miniature moving coil loudspeaker (see Fig. 8). Once again, the long leads must be kept on the low impedance side of the circuit. The moving coil speaker will serve well as a microphone and has the added advantage of not requiring an energising battery. The output is, however, considerably lower than from the carbon microphone.

Using the moving coil speaker, a two way intercom. can be built up by means of suitable switch-

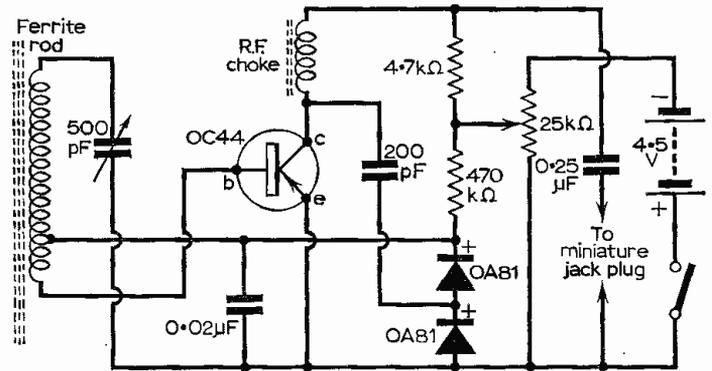


Fig. 6: Simple single transistor reflex tuner.

ing: the principal factor is the use of the moving coil speakers alternately as microphones and as loudspeakers.

## GRAMOPHONE AMPLIFIER

The tape recorder amplifier can readily be used as a gramophone amplifier by the connection of pick-up leads to a miniature jack plug which is then inserted into the jack socket already fitted at point "X" on Fig. 1.

An interesting variation is the adaptation of the tape recorder motor itself to provide a turntable drive for playing 45 r.p.m. records. By suitable adjustment of the potentiometer speed control previously described, most portable tape recorder drive motors can be adjusted to a speed of 45 r.p.m.

The right hand spool (take-up spool) is utilised as a miniature turntable, and the pick up itself is mounted on the left hand spool. Two empty three inch spools can be utilised to provide the "turntable" and the base for the pick-up arm. In order to ensure that the gramophone record clears the tape head assembly etc., one of the tape spools should be placed on the right hand spool drive base. The record is centred by gluing a 45 r.p.m. large diameter spindle on to the empty three inch spool, taking care that the centre holes are concentric (the tape recorder drive spindle usually protrudes far enough to ensure this).

The only other point which must be watched is that the direction of rotation of the gramophone


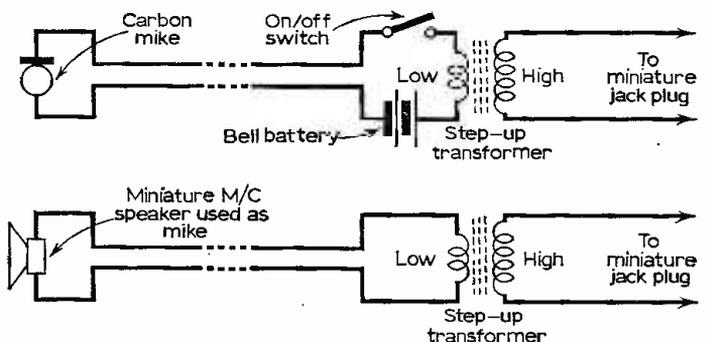


Fig. 7 (above): Input circuitry for carbon mike.  
Fig. 8 (below): Circuit for use with moving coil speaker.

record is the reverse of the normal tape drive (a record turns clockwise, but a tape spool take-up is anticlockwise). This is easily taken care of by reversing the polarity of the batteries with reference to the tape recorder motor. As these batteries are separate from the transistor battery supply, the operation of the amplifier is not affected. ■

# CODAR — QUALITY

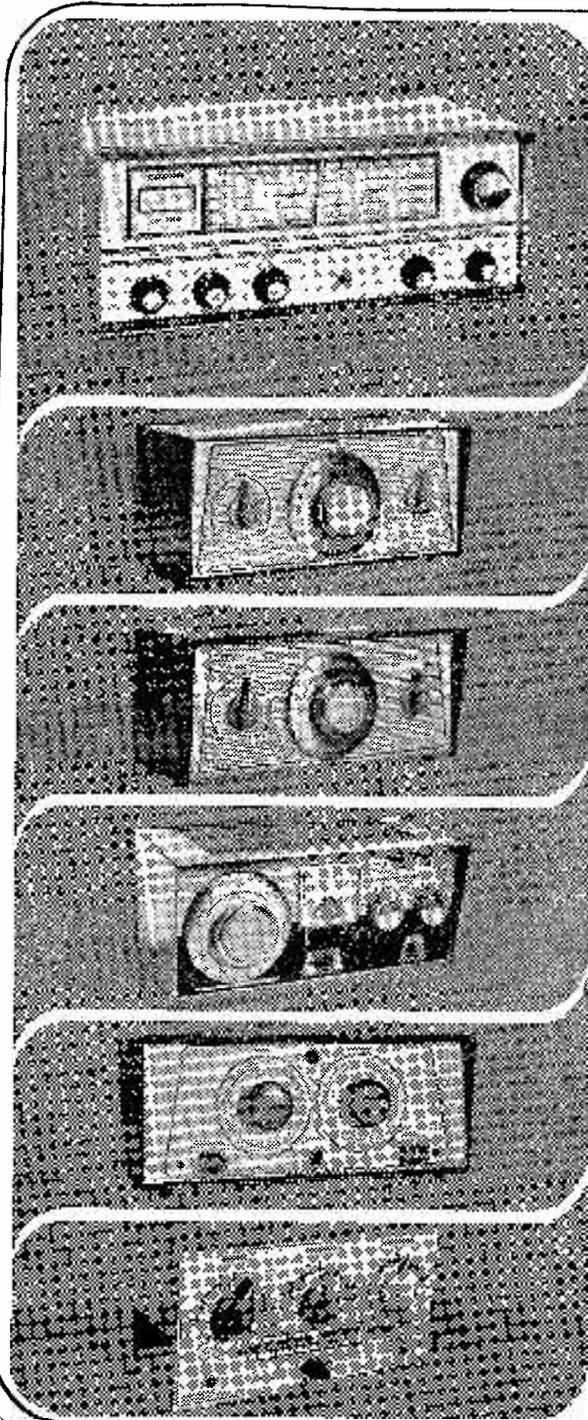

## ANOTHER CODAR TRIUMPH!

### THE CR.70A COMMUNICATION RECEIVER.

This completely new receiver sets a new high standard for performance and finish unequalled at the price, and is a worthy addition to the outstanding range of CODAR quality communication equipment. Frequency range: 560 Kc/s-30 Mc/s (540-10 metres) in four ranges; 560 Kc/s-1.5 Mc/s; 1.5 Mc/s-4.2 Mc/s; 4.2 Mc/s-11.5 Mc/s; 11.5 Mc/s-30 Mc/s. Slide rule scales for each band calibrated in frequencies plus an additional logging scale in degrees. Two speed vernier tuning control with reverse slow tune action. Unique aerial input stage exclusive to the CR.70A employing High 'Q' Air-spaced CODAR-COIL Inductor giving extremely high gain with low noise level. Panel aerial trimmer for peaking weak signals. Double tuned I.F. Iron cored transformers, 470 Kc/s with EF183 frame grid valve for maximum gain and selectivity. 5 valves (including two twin triodes) giving 7 valve line-up. Separate B.F.O. stage for CW and SSB reception. Calibrated signal strength 'S' meter, illuminated. Automatic Volume control. Panel phone jack for 'private' listening, 2-3 ohm output for external speaker. (Matching unit optional extra.) Superb styling, metal cabinet in the new Organosol Satin lustre finish. Size: 13" x 5½" x 7½". For A.C. 200/250v. Ready built. Not a Kit at the fantastic low price of £19.10.0. Carr. 7/6.

**CODAR R.F. PRE-SELECTOR MODEL P.R.30.** Considerably improves the performance of any superhet receiver over 1.5-30 Mc/s. Uses EF183 Frame Grid Valve, and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12mA H.T. 6.3 volts, 3 amp L.T. Size 8½ x 5 x 4in. Ready built, complete with cables, plugs and instructions, £5.10.0. Carr. 4/6. **MODEL P.R.30X.** Self powered model for 200-250v. A.C. Also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £7.4.0. Carr. 4/6.

**CODAR "Q" MULTIPLIER MODEL R.Q.10.** For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW, or SSB, B.F.O. Size 8½ x 5 x 4in. Power requirements 180-250v. H.T. at 5mA 6.3v. 3 amp L.T. Ready built complete with cables, plugs and instructions, £6.15.0. Carr. 4/6. **MODEL R.Q.10X.** Self powered version for 200-250v. A.C. and also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £8.8.0. Carriage 4/6.

**CODAR A.T.5, 12 WATT 2 BAND TRANSMITTER.** The newest most compact transmitter for fixed or mobile use on 160-80 metres. "The tiny TX with the BIG voice". Size only 8½ x 5 x 4in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR COIL Pi-net output, P.A. Plate current meter plus neon indicator. Plate-Screen modulator. AM/CW switch and Panel key jack. Plug changeover for 6 or 12 volts heater supply. Ready built £16.10.0. Carr. 4/6. **A.T.5 POWER SUPPLY UNITS.** For 200-250v. A.C. and 12v. Solid state for Mobile use, complete with all Transmitt/Receive changeover switching available.

**CODAR-KIT CR.45K MAINS T.R.F. SHORT-WAVE RECEIVER.** World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandsread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line-up: ECC81, EL84, EZ80. Size 12 x 5½ x 7in. **CODAR-KIT CR.45K** complete with valves, 3 coils (10-28, 25-75, 60-176 metres) and 11 page instruction manual, £9.10.0. Carr. 6/-. Extra coils 5/- each. Instruction manual only 4/- (credited on order). (Can also be supplied ready built—price on request).

**CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER** ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 39/6. Carr. 3/-. Extra coils 5/- each. Instruction manual only 2/- (credited on order). Electrical bandsread available. Provision to add 2 transistor amplifier.

Send 6d. in stamps for illustrated leaflets of the Codar range

• H.P. terms available

• World-Wide Mail Order Service



**CODAR RADIO COMPANY**  
BANK HOUSE, SOUTHWICK SQUARE  
SOUTHWICK, SUSSEX. Tel. 3149

G3IRE

G3HGQ

Canada: Codar Radio of Canada, Tweed, Ontario




### 10 TRANSISTOR TWO WAY RADIOS


Ultra sensitive superhet receiver with RF amplifier. 100mW output. Complete with telescopic aerial, leather carrying cases and batteries. A bargain at **£21.19.6**

(These cannot be operated in U.K.)

### 4 CHANNEL MICROPHONE MIXER

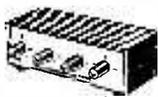

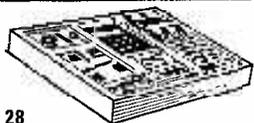Fully transistorised. Enables mixing of four separate signals—mike radio records etc. Complete with battery at the amazing low price of **42/6**



### EEK28. 28 PROJECT CONSTRUCTIONAL KIT

This advanced educational kit is excellent for beginners as well as the more advanced experimenter. Not even a soldering iron is needed. Complete with 60 page booklet giving full details of suggested circuits. **£6.10.0**



### 10 WATT HORN TWEETER

Brings true hi-fi reproduction to your system. Freq. response 1,500 to 18,000 cps. Crossover 3,000 cps. Sensitivity 104db/W. Impedance 16 ohm. Buy now while stocks last. **22/6**

Crossover Networks. CN.23—3ohm. 2 way 14/6; CN.216—16 ohm 2 way **14/6**

# RELDA RADIO LTD

(Dept. P.W.17) 87 Tottenham Court Road, London, W.1.


### FOR THE MOTORIST AND HOME HANDYMAN



Versatile home/auto tester for all electrical circuits in home and car. Measures AC Voltages 0—150, 0—300v. Resistance 0—1000 ohms. High resistance and leakage 1000 ohm 2 megohm. Current and power 0—15 amps 0—3KW. Car battery 0—75. 0—15 v. A must for only **£5.2.6.**
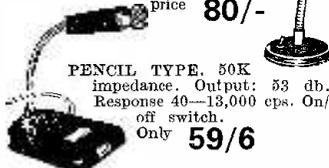
### MICROPHONE BARGAINS!

Gooseneck Dynamic Microphone. Dual impedance 600 ohm low/50K high. Output: 58 db. Response: 50—11,000 cps. With dual impedance on/off switch. Offered at well below regular price **80/-**




PENCIL TYPE. 50K impedance. Output: 53 db. Response 40—13,000 cps. On/off switch. Only **59/6**

### SEVEN-IN-ONE TESTER



Ideal for quick checks in the home or service dept. Supplied with batteries test leads and instructions. Featuring Resistance substitution in 5 ranges. Capacitance substitution in 5 ranges. R.F. Signal Generator 455 Kc/s. A.F. Signal Generator 400 c/s. D.C. and A.C. Voltmeter. 4 ranges; R.F. Field Indicator; 1—140 Mc/s. Unrepeatable at only **£5.10.0.**

### TT.144 DYNAMIC TRANSISTOR TESTER

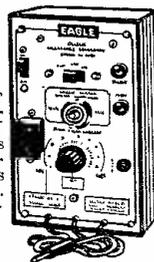

Tests in-circuit or out of circuit. Identifies PNP and NPN types. Indicates electrode open circuits, short circuits and current drain. Complete with instructions. **£4.10.0**

## ALL ITEMS SENT POST FREE

FOR FULL DETAILS OF THESE AND MANY OTHER ITEMS SEND FOR FREE COMPREHENSIVE CATALOGUE EAGLE NEWS AND ORDER FORM. ALL ITEMS AVAILABLE POST FREE AND COVERED BY 12 MONTHS' GUARANTEE.

CALLERS WELCOME AT OUR HI-FI SHOWROOM

### 72" SHIELDED CABLES

Fitted variety of plugs, sockets etc. for a variety of uses.

- CA. 1—Right Angle Jack plug/phone plug, 5/-.
- CA. 2—Right Angle Jack plug/alligator clips, 5/-.
- CA. 3—Right Angle Jack plug/Right Angle Jack plug, 7/6.
- CA. 4—Right Angle Jack plug/Spade Terminals, 5/-.
- CA. 5—Chrome phone plug/chrome phone socket, 5/-.
- CA. 6—Phonoplug/Alligator clips, 5/-.



### SUB-MINIATURE TRANSISTORISED PUSH-PULL AUDIO AMPLIFIERS

Ready built on printed circuit with full instructions. Ideal for building your own tuner, intercom, baby alarm, etc. 250 mW output 32/6; 1 watt output 42/6; 3 watt output 49/6.



### MCK.2. MORSE CODE KIT

Two station morse code kit supplied with instructions, 50ft. of connection wire and morse code charts. ONLY **27/6**

# THE PEMBRIDGE COLLEGE OF ELECTRONICS FOR TRAINING IN RADIO AND TELEVISION

## FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course, of sixteen months' duration, provides a fundamental training for radio and television engineers. It includes theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Exactly half the time is spent on practical work and the course provides excellent practical experience on valve and transistor radio receivers and high-fidelity equipment and all well known makes of television receivers.

The Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Next Course commences 5th September, 1967.

To: **The Pembridge College of Electronics (Dept. P11)**


**34a Hereford Road, London, W.2.**

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name \_\_\_\_\_

Address \_\_\_\_\_

CMP 5

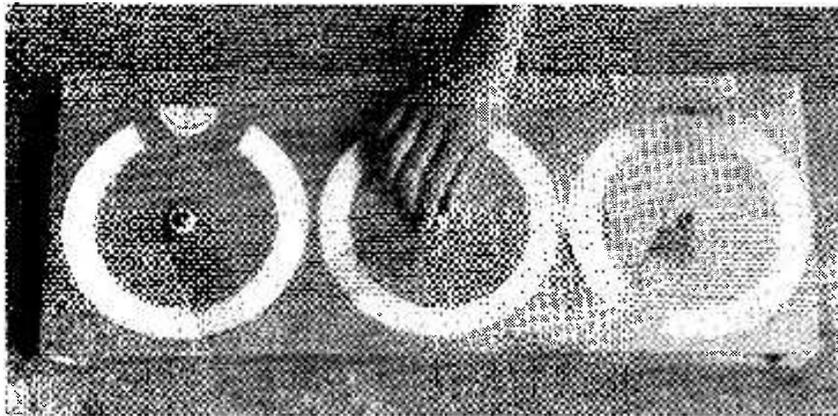

# A SIMPLE ANALOGUE COMPUTER

C. R. BRADLEY

COMPUTERS may be divided into two main classes, the *digital* and the *analogue*. Digital computers employ enormous numbers of interconnected switching circuits and in spite of modern advances in miniaturization by the use of semiconductors and printed circuits they are usually very large pieces of equipment.

Since they are composed mainly of switches with two positions, "ON" and "OFF", they can only deal with problems translated into an "ON/OFF" or two term "language" such as the *binary code*. Any number may be expressed in this code solely in terms of 0 (or "OFF") and 1 (or "ON"). Complex equipment is required to translate problems into binary code and to translate the answer produced by the computer into intelligible form. Needless to say, the tremendous expense of such equipment puts it beyond the range of the layman.

Analogue computers solve problems by electrically simulating the conditions of the problem. Their advantage over digital computers is that it is often unnecessary to convert the problem into a special form for the computer to handle. All this will be clear when the operation of a very simple and inexpensive analogue computer is considered.

The circuit diagram Fig. 1 shows a battery, a switch, a galvanometer and three linear potentiometers connected together. Each of the potentiometers is fitted with a pointer knob moving over a 0 to 10 scale. The operation of the computer is best seen by considering a simple multiplication sum, say  $6 \times 5$ . Firstly, the pointer on VR1 is set to 6. If the voltage supplied by the battery is X volts, then the voltage between the slider of VR1 and its lower end (and hence the voltage across VR2) is  $0.6X$  volts (the voltage drop across VR1 is linear). VR2 is now set to 5 and the voltage between its slider and lower end is therefore  $0.5 \times 0.6X$  volts, i.e.:  $0.3X$  volts.

VR3 is now adjusted until the galvanometer indicates zero current. At this "balance" point, the potentials at the sliders of VR2 and VR3 must be equal. The pointer reading on VR3 is therefore 3, and adding a nought to this gives the answer to our simple multiplication sum, i.e.:  $6 \times 5 = 30$ .

This demonstrates the computer's ability to

multiply; by a converse process it can divide. Example: To divide 8 by 2: Set VR3 to 8, set VR2 to 2 and adjust VR1 for zero deflection of the galvanometer. This is obtained at 4 which is the answer to the problem. In other words, all that has been done is to calculate  $4 \times 2 = 8$  in reverse.

So far only simple problems have been considered which one can do without a computer. However, a problem such as  $2.35 \times 9.2$  is a different matter, but the analogue computer will handle this problem just as easily. The correct answer is read out on VR3, viz.: 21.6 to 1 decimal place (actually read as 2.16 but seen to be obviously 1/10th too small).

The computer is not limited to manipulating numbers under 10; it can calculate  $2,350,000 \times 0.092$  just as easily. VR1 and VR2 are still set to 2.35 and 9.2 and the answer is still read as 2.16, but a moment's thought shows that it must actually be 216,000. (Alternatively:  $2,350,000 \times 0.092 = 2.35 \times 10^6 \times 9.2 \times 10^{-2} = 2.35 \times 9.2 \times 10^{6-2} = 21.6 \times 10^4 = 216,000$ ).

The computer is not limited by the *size* of numbers, but by the accuracy of the calibration of the potentiometers. The figure 5.2967 cannot be accurately set on a conveniently sized dial, the closest possible being 5.30.

## Construction

In practical form the computer employs eight-inch diameter dials for VR1, VR2 and VR3. This is large enough to give fairly accurate answers and easy reading. Any further increase in size would

Engraved line filled with ink

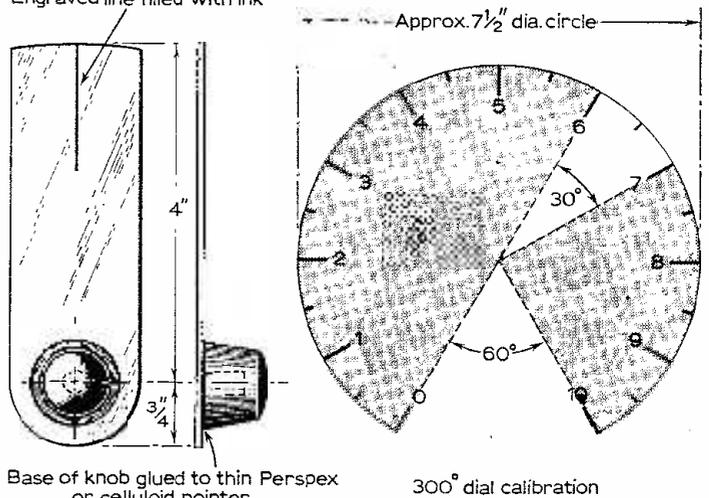


Fig. 2 (left): Suggested construction of the pointers.  
Fig. 3 (right): Dial suitable for a 300° potentiometer.

make the unit very bulky and would not greatly increase accuracy because the dials can only be calibrated to a certain accuracy and the potentiometers used will have a certain limiting resolution.

A simple "sandwich" construction is used consisting of two 12in. x 26in. pieces of  $\frac{1}{4}$ in. plywood separated by 1in. x 1in. x 2in. struts at each corner. Besides the three large potentiometer dials, the upper panel carries an on/off switch and the galvanometer. This is mounted on the lower surface of the panel and viewed through a semi-circular cutout.

## Potentiometer Values

If the pointer of VR1 is set to (say) 7 the voltage between its slider and lower end will only be exactly 0.7X if no current is drawn from it. If an appreciable current is drawn, more current will be flowing through the upper portion of the potentiometer than the lower and hence there will be a greater voltage drop across the upper portion than under no-load conditions. As VR2 must draw some current, the potential difference across it will always be slightly *below* that indicated on the pointer of VR1 because of this *loading error*.

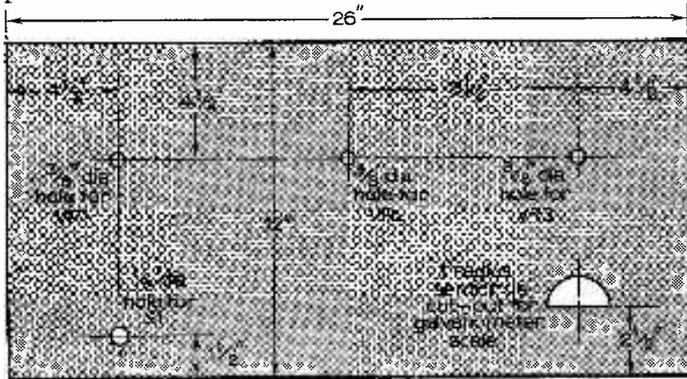



Fig. 4: Front panel layout used in the prototype.

Loading error can be minimised by using a low resistance potentiometer for VR1 (so that a large current flows through it and the current drawn by VR2 is very small in comparison) and a high resistance potentiometer for VR2 so that it draws only a small current. There is no loading error due to current drawn from VR2 or VR3 since, when the galvanometer indicates zero, no current is being drawn from either slider. VR3 should be low in value so that a small deviation from balance point will give a large galvanometer deflection.

Suitable values for VR1, VR2 and VR3 are 100 $\Omega$ , 5k $\Omega$ , and 100 $\Omega$  respectively, but these are not very critical (see components list). It is very important, however, to ensure that these are *linear* potentiometers and not the logarithmic type used in audio circuits. Large wirewound controls as used in Wheatstone bridge instruments may be used if available, although good results may be obtained from ordinary carbon potentiometers.
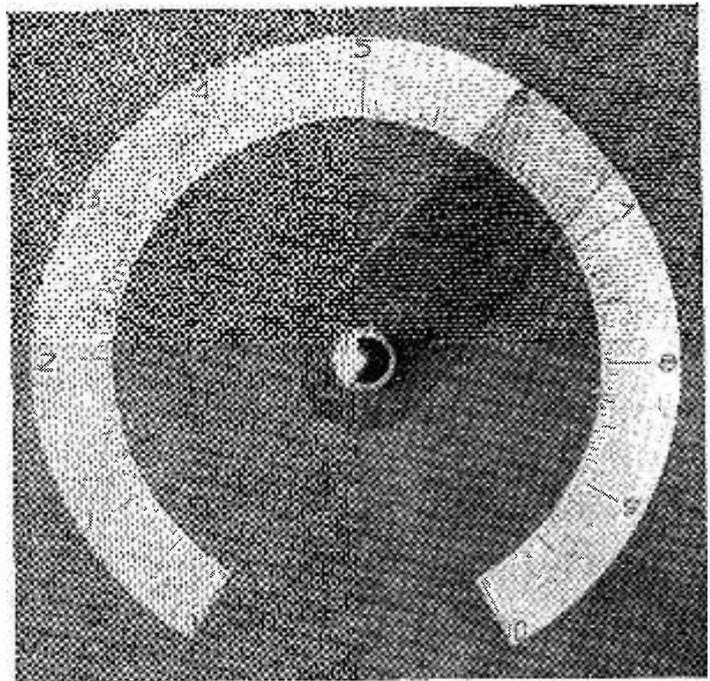
## Calibration

The easiest way to calibrate VR1, VR2 and VR3 is to measure their angles of rotation and mark off the divisions 0 to 10 using a protractor. Fig. 3 shows a dial for a 300° potentiometer; the angle between divisions in 300°/10, i.e.: 30°. The dial may be further subdivided into graduations of 0.1. This



Close-up of one of the dials.

dial is easily drawn on an 8in. diameter circle of paper which is glued to the control board.

A smart pointer knob for each of the potentiometers may be made by gluing an ordinary small knob to a shaped piece of celluloid or perspex (see Fig. 2). The pointer is completed by engraving a line as shown with a sharp needle and filling it with indian ink to show up against the paper scale. Such a calibration will be fairly accurate provided the potentiometers are precisely linear and the resistive track does not terminate well before the limit of revolution.

If an accurate ohmmeter is available, each potentiometer may be calibrated by actual measurement, i.e.: by marking "1" where the resistance on the lower side of the slider is 1/10th the total and so on.

Alternatively, if a *high resistance* voltmeter (20,000  $\Omega$ /V or greater) or valve voltmeter is avail-


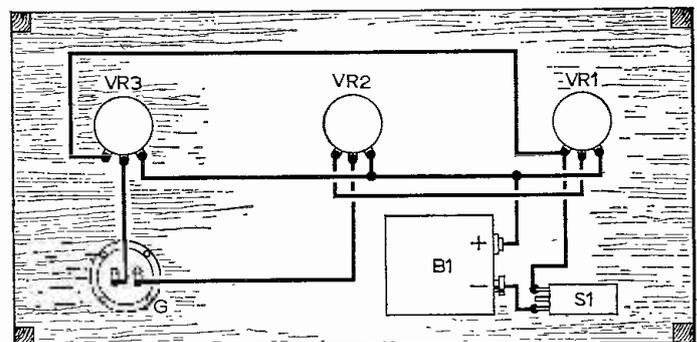


Fig. 5: Rear view of the front panel showing wiring.

able, calibration may be done by comparing the slider potential with an accurately measured voltage applied across the potentiometer.

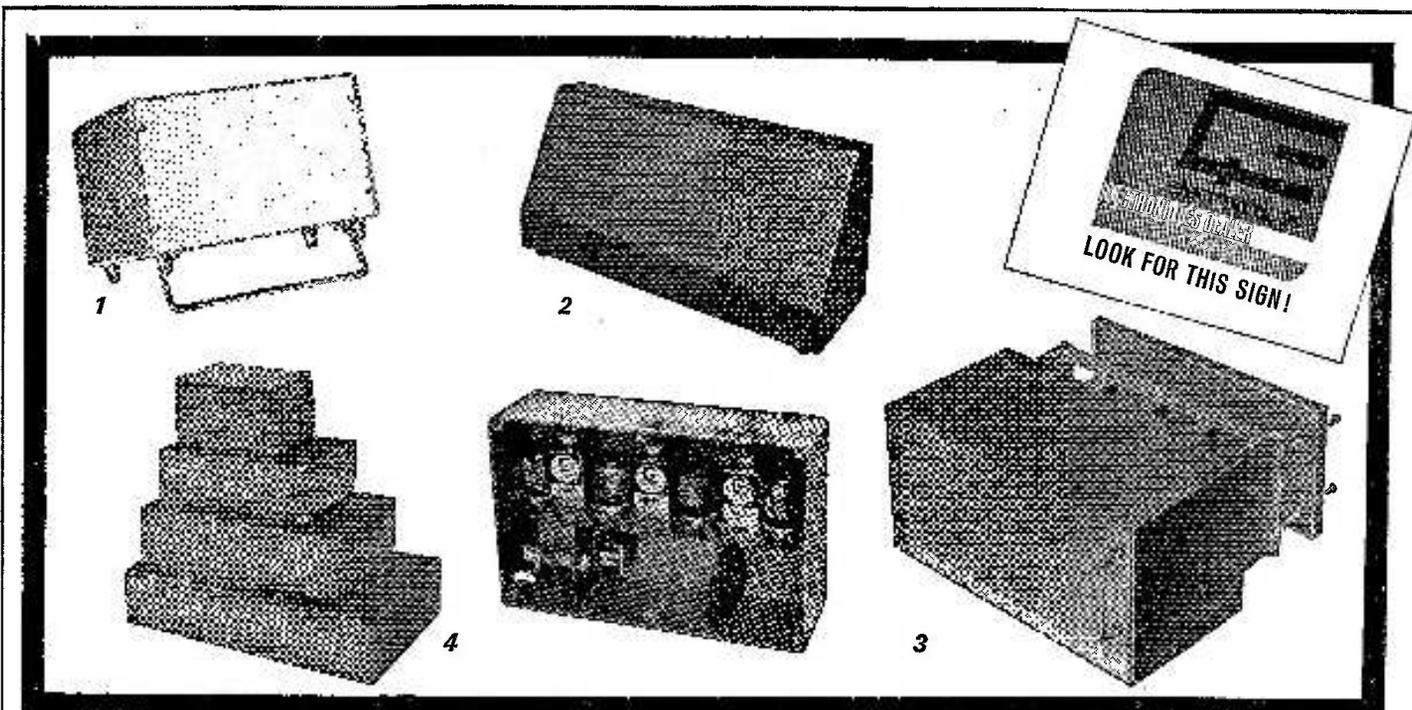The wiring of the unit is very simple. Any small 6 to 12 volt battery may be used as the battery voltage does not affect the answers obtained. A 100-0-100 $\mu$ A galvanometer is sensitive enough to give an accurate zero indication. If required, an even sharper indication may be obtained by raising the battery voltage and/or using a more sensitive galvanometer.



I should like a copy of the Electroniques Hobbies Manual. Enclosed is a cheque/P.O. for 10/6.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

P.W.5

## OBTAIN A PROFESSIONAL FINISH TO YOUR EQUIPMENT! Choose housings and equipment practice from the Electroniques catalogue.

With the new 600 page Hobbies Manual, you can obtain these—and over 11,350 other items—direct from Electroniques or through your Local Electroniques dealer! The service is fast; the choice is the most comprehensive ever offered. And the components, which are supplied by 85 leading manufacturers, meet every kind of need—whether the project is advanced or elementary!

### 1 For Small Electronic Assemblies

These attractive DATUM Dinkicases are available in four sizes ranging from 4" x 6" x 4" to 7" x 12" x 7". Grey hammer finish front and rear; panels front and rear grey/gloss enamel. A retractable leg can be supplied if required (as illustrated).

### 2 Sloping Panel Cases

These DATUM cases, by using the feet provided in alternative positions, can provide a narrow base (upright) case or a wide based case. Four sizes provide eight alternatives. Dark grey hammer finish cases; top panels grey gloss enamel. Dimensions from 12 $\frac{3}{8}$ " to 24 $\frac{3}{8}$ " inches width overall.

### 3 Modular Equipment Practice and Equipment Cases

Professional quality 19 inch equipment cases available for the amateur at competitive prices.

Symmetrical design allows panels fitted front and rear. Ideally suited for MCS 19 in. modular dossier system. A complete range of panels, sub-racks and system accessories is available. Stocked in seven sizes. Finish matches Dinkicases.

### 4 Diecast Boxes with unique slot guide system

These versatile diecast boxes are stocked in 5 sizes, to be used as screened sub-assemblies for complete equipments, test sets, and junction boxes, and they can be used as plug-in assemblies on the MCS board system. A special range of VEROBOARD is designed to fit the slot guides in the boxes, which will also fit DATUM Dinkicases. As used in our modular communication assemblies.

Send now for your Manual, on the coupon above, to this address: Electroniques (Prop. STC Ltd.) Edinburgh Way, Harlow, Essex. Telephone: Harlow 26777.



**electroniques**

High-grade components for amateur communications


### HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1

● Peak output in excess of 1 1/2 watts.  
 ● All standard British components.  
 ● Built on printed circuit panel, size 6 x 3in.  
 ● Generous size Driver and Output Transformers.  
 ● Output transformer tapped for 3 ohm and 15 ohm speakers.  
 ● Transistors (GET 114 or S1 Mullard OC81D and matched pair of OC81 o/p). ● 9 volt operation.  
 ● Everything supplied, wire, battery clips, solder, etc.  
 ● Comprehensive easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately.

**SPECIAL PRICE 45/-**. P. & P. 3/-.  
 Also ready built and tested, **52/6**. P. & P. 3/-.  
 A pair of TA1s are ideal for stereo.
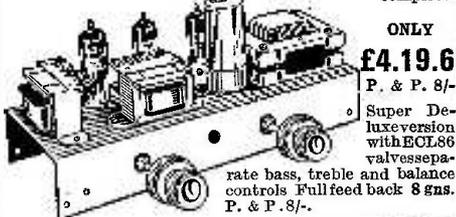
### STEREO AMPLIFIER

Incorporating 2 ECL86s and 1 EZ80, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



**ONLY £4.19.6**  
 P. & P. 8/-

Super De-luxe version with ECL86 valves separate bass, treble and balance controls. Full feedback 8 gns. P. & P. 8/-.

### 6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 8 1/2 x 2 1/2in.). ● 3 pre-aligned IF transformers ● High-gain Ferrite Rod aerial. ● All First-grade transistors ● Car aerial winding. ● Push-pull output ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time **ONLY 44.5.0**. P. & P. 2/6 (Circuit diagram 2/- Free with set of parts).

### 35 OHM SPEAKERS

Suitable for use with above. 2in. Goodmans' Ideal replacement for most pocket portables, 8/6; 3 1/2in. 12/6; 7 x 4in., 21/-; P. & P. 2/- per speaker.

### Portable CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2in. Suitable for above using 3 1/2in. speaker, 25/-; P. & P. 2/6.

### COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 IF transformers one oscillator coil one driver transformer and wound Ferrite aerial (med. long and car aerial coupling). 32/6 complete post 2/-, 6 transistor printed circuit board to match 8/6. Post 1/-. Circuit diagram 1/6 extra.

**MINIATURE PRECISION AIR-SPACED TWO GANG TUNING CONDENSER.** 176+176 p.F. size 1 1/2" x 1 1/2" d x 1 1/2" h with vanes open. Built in trimmers 5/-; P. & P. 1/-

**BRAND NEW TRANSISTOR BARGAINS**  
 GET 15 (Matched Pair) 15/-; V15/10p, 10/-; OC71 5/-; OC76 6/-; AF117 7/6.

Set of Mullard 6 transistors OC44, 2—OC45 OC81D matched pair OC81 25/-, ORP12 Cadmium Sulphide Cell 10/6.

### EDISWAN MAZDA

PXA101 6/6; XA103 6/6.  
 R.F.I. Pack: 1—PXA102 Mixer; 2—PXA101 I.F. Amp. (Equiv. OC44 and OC45) 10/6  
 R.F. 2 Pack: 2—PXA101 I.F. 1—PXA102 Osc. 1—PXA102 Mixer 12/6  
 L.F.6 Pack: Consisting of PXB113 Driver Matched pair. PX171 mounted complete with heat sinks (Equiv. OC81D and OC81) 12/6  
**ALL TRANSISTORS POST FREE.**

### TAPE DECKS

**B.S.R. MONARDECK** (Single speed) 3 1/2in. per sec. simple control, uses 5 1/2in. spools, £6.15.0 plus 7/6 carr. and ins. (Tapes extra).  
**LATEST COLLARO MAGNAVOX 363 TAPE DECK DE LUXE**, Three speeds, 2 track, takes up to 7in. spools. **10 gns.** Plus 7/6 Carr. & ins. on each (Tapes extra).

### PORTABLE TAPE RECORDER CASE

Beautifully made and expensively finished in dark grey heavy grade rexine. Satin Chrome metal grille front and chrome fittings. Speaker aperture 9" x 4". Overall size 15 1/2" w. x 15" d. x 7 1/2" h. Will take any standard tape deck or single record player. Limited number only. Worth at least 25. **OUR PRICE 49/6**. P. & P. 8/6. Brand new and unused.

**AGOS CRYSTAL MIKES.** High Imp. For desk or hand use. High sensitivity, 18/6. P. & P. 1/6.  
**TSL CRYSTAL STICK MIKE.** Listed at 45/-. Our price 18/6. P. & P. 1/6.

### QUALITY RECORD PLAYER AMPLIFIER

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3in. d. x 6in. h. Ready built and tested. **PRICE 69/6**. P. & P. 6/-.  
**ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit into cabinet below. **PRICE 89/6**. P. & P. 7/6.

### DE-LUXE QUALITY PORTABLE R/P CABINET

Uncut motor board size 14 1/2 x 12in. Clearance 2in below, 5 1/2in. above. Will take above amplifier and any B.S.R. or Garrard Autochanger or Single Player Unit (except AT60 and SP25) Size 18 x 15 x 8in. Price **£3.9.6**. Carr. 9/6.

### 4-SPEED PLAYER UNIT BARGAINS

All brand new in maker's original packing.  
**SINGLE PLAYERS**  
 B.S.R. TU/12 ..... £3.9.6 Carr. 5/6.  
 GARRARD SP25 De Luxe ..... £12.0.0 Carr. 5/6.  
 B.S.R. GU7 with unit mounted pickup arm. £4.18.8 Carr. 5/6.

### AUTO CHANGERS

Latest B.S.R. UA25 Super Slim ..... £6.2.6  
 GARRARD 1000 with special Hi-Fi cartridge ..... £6.19.6  
 GARRARD 2000 £7.10.0. GARRARD 3000 £5.15.0  
 GARRARD AT60. £10.10.0 Carr. 6/6 on each.  
 All the above units are complete with t/o mono head and sapphire styl or can be supplied with compatible stereo head for 12/6 extra.

### BRAND NEW CARTRIDGE BARGAINS!

AGOS GP87-1. Mono complete. List price 21/-. Our price 13/6. P. & P. 1/-.

### BRAND NEW 3 OHM LOUDSPEAKERS

5in., 12/6; 6 1/2in., 15/-; 8in., 22/6; 10in., 27/6; 7in. x 4in., 16/-; 10in. x 6in., 27/6.  
 E.M.I. 8in. x 5in. with high flux magnet, 21/-.  
 E.M.I. 1 1/2 x 8in. with high flux ceramic magnet, 42/- (15 ohm 45/-). P. & P. 5in. 2/-, 6 1/2 x 8in. 2/6, 10 x 12in. 3/6 per speaker.

### SPECIAL OFFER!

Limited number of 12in. 10 watt "R.A." Speakers: 3 ohm 25/-; 15 ohm 27/6. P. & P. 3/6.

**E.M.I. PLASTIC CONED TWEETERS**, 2 1/2in. 3 ohm. Limited number 12/6 each. P. & P. 1/6.

**BRAND NEW HEAVY DUTY 12in. SPEAKERS.** Response 45 c/s—13 Kc/s. 1 1/2in. voice coil. Available in 3 or 15 ohms. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. **LIMITED NUMBER ONLY. UNREPEATABLE** at 89/6. P. & P. 5/- Also 25 watt Guitar Model available at 25.5.0. And 35 watt Guitar Model 28.8.0.

### VYNAIR AND REXINE SPEAKER AND CABINET FABRICS.

Approx. 5 1/2in. wide. Usually 35/- yard. **OUR PRICE 18/6** per yard length. P. & P. 2/6 (min. one yd.) S.A.E. for samples.

### SPECIAL OFFER!

**GENUINE HIGH QUALITY TYGAN FABRIC.** 48in. wide. Our price 10/- per foot run. P. & P. 1/6. 30/- per yard run. P. & P. 2/6.

**SEMI SHROUDED DROP THRO' MAINS TRANSFORMER.** Tapped pri 200/250 v. Sec. 300-0-300 v. at 110mA. and 6.3 v. at 3 amp. (E/S screen). Stack size 3 1/2 x 3 1/2 x 1 1/2in. **30/-**. P. & P. 3/6.

**MAINS TRANSFORMER "R."** For transistor power supplies. Pri. 200/240 v. Sec. 9-v-9 v. at 500 mA. 11/-; P. & P. 2/6.

**MAINS TRANSFORMER.** For transistor power supplies. Tapped pri. 200-250 v. Sec. 40-0-40 at 1 amp (with electrostatic screen) and 6.3 v. at .5 amp for dial lamps etc. Drop thro mounting. Stack size 1 1/2 x 3 1/2 x 3 1/2in. 27/6. P. & P. 4/6.

**MATCHED PAIR OF 2 1/2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS.** Stack size 1 1/2 x 1 1/2 x 3 1/2in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/- P. & P.

**7-10 watt OUTPUT TRANSFORMERS** to match pair of ECL 86's in push-pull to 3 ohm output. **ONLY 11/-**. P. & P. 2/6.


### WELL-KNOWN MAKERS SURPLUS ONE TRANSISTOR PRE-AMP

Suitable for use with Medium or High Impedance mikes, guitars, gram pickups, tape decks etc.: For operation from 200/300 volt H.T. rail or 9 volt battery. Gain approx 14:1. Fully isolated input by Mu-Metal screened transformer. Size 4 1/2 x 1 x 1in. Ready built complete with full circuit diagram and instructions. **ONLY 15/-**. Post free.

**Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser.** 35/-; P. & P. 3/-.

**TWIN TELESCOPIC AERIAL.** Comprising two 3-section heavily chromed rods. Closed 12in. each extending to 32in. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, coax lead and plug. Suitable for F.M. or TV. 12/6. P. & P. 2/6.
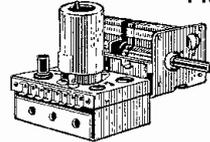
### SPECIAL HARVERSON OFFER! FM/AM TUNER HEAD



Beautifully designed and precision engineered by Dornier and Wadsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM connection. Prealigned FM section covers 86-102 Mc/s. I.F. output 10.7 Mc/s.

Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly! Limited number also available with precision geared 3:1 reduction drive, 30/-; P. & P. 3/-.

### MATCHED PAIR AM/FM I.F.'s

Comprising 1st I.F. and 2nd I.F. discriminator (465kc/s/10.7Mc/s). Size 1 x 1 1/2 x 2 1/2in. high. Will match above tuner head. 11/- pair. P. & P. 2/-.


### SPECIAL PURCHASE! TURRET TUNERS

By famous maker. Brand new and unused. Complete with PCC84 and PCF80 valves 34-38 Mc/s I.F. Biscuits for Channel 1 to 5 and 8 and 9. Circuit diagram supplied. **ONLY 25/-** each. P. & P. 3/9.

### GORLER F.M. TUNER HEAD

88-100 Mc/s, 10.7 Mc/s I.F. 15/- plus 2/- P. & P. (ECC85 valves 8/6 extra).

### 3-VALVE AUDIO AMPLIFIER MODEL HA34

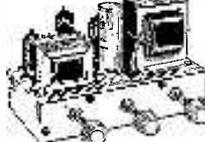


Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in. w. x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them **£4.5.0** complete with knobs, valves, etc., wired **£4.5.0** and tested for only **P. & P. 6/-**.
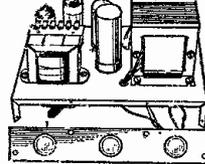
### HSL 'FOUR' AMPLIFIER KIT

A.C. Mains 200/250v., 4 watt, using ECC83, EL84, EZ80 valves.




● Heavy duty double-wound mains transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● Chassis size only 7 1/2in. wide x 4in. deep. Overall height 4 1/2in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves output transformer (3 ohms only) screened lead, wire, nuts, bolts solder etc. (No extras to buy). **PRICE 79/6**. P. & P. 6/-.

Comprehensive circuit diagram practical layout and parts list 2/6 (free with kit). *This kit although similar in appearance to HA34 employs entirely different and advanced circuitry.*
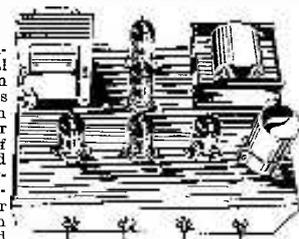
### 10/14 WATT HI-FI AMPLIFIER KIT

A Stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 8-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 1/6 (Free with part.) All parts sold separately. **ONLY 27.9.6**. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, **29.5.0**. P. & P. 8/6. Carrying case for above 28 6 P. & P. 7/6.



● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● Chassis size only 7 1/2in. wide x 4in. deep. Overall height 4 1/2in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves output transformer (3 ohms only) screened lead, wire, nuts, bolts solder etc. (No extras to buy). **PRICE 79/6**. P. & P. 6/-.

**NEON A.C. MAINS INDICATOR.** For panel mounting, cut out size 1 1/2 x 3/4 x 3/4in. deep inc. terminal. White case with lens giving brighter light. For mains 200/250v. 2/6 each. P. & P. 6d. (6 or more post free).

Open all day Saturday  
 Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHERRYWOOD 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Care must be taken not to damage the galvanometer by overload; when solving a problem it is a good plan to set the answer potentiometer to the approximate result expected before switching on. In this way the galvanometer will only carry a small current as the circuit is nearly in balance. Example: To multiply 2.95 by 8.30: Set VR1 and VR2 to 2.95 and 8.30. As the answer will clearly be approximately 24 (3 x 8), set VR3 to 2.4 and then switch on. The balance point and hence the

## ★ components list

VR1 50Ω to 500Ω linear carbon potentiometer  
 VR2 1kΩ to 10kΩ linear carbon potentiometer  
 VR3 50Ω to 500Ω linear carbon potentiometer  
 S1 Single pole single throw (SPST) switch  
 B1 Any small 6–12 volt battery  
 G Approx. 100–0–100μA galvanometer

Wood: Two pieces ½in. plywood, 12in. x 26in.  
 Four pieces 2in. x 1in. x 1in.

Three knobs

Perspex for knobs, wire, solder, screws etc.

answer is found very close to this at 2.45; the final answer is therefore 24.5 (to one decimal place).

Slide rule users will see that the scope of this simple computer may be greatly extended by the addition of further scales (e.g.: trigonometrical, logarithmic etc.) although these are beyond the scope of this article. Suffice to say that this simple computer should demonstrate just how uncomplicated analogue computers can be while still exceeding the brain's mental capabilities. ■

## CQ! CQ! CQ! CQ! CQ!

### CORRESPONDENTS WANTED

... someone of my own age (14½ yrs) who is interested in short-wave listening.—David Burdsall, 3 Poplar Drive, Whitburn, Nr. Sunderland, Co. Durham.

### ISSUES WANTED

... volumes 1 to 12 (1932–1938) either as loose copies or bound, but preferably in whole volumes with covers.—F. Allan Herridge, G3IDG, 96 George Street, Basingstoke, Hampshire.

... October, November, 1964 and April, November, 1965. These issues covered the 10–5 Rx.—M. D. Ellse, 86 Bennethorpe, Doncaster, Yorkshire.

... April 1965 which contained details of the Transistorised Solo Organ.—A. Sheldon, 12 Walker Street, Toll End, Tipton, Staffordshire.

... January 1964, July 1965, January 1966 and April 1966.—Cpl. Symes, REME Wing, T.E.R.A. Ty Croes Camp, Anglesey.

... July 1961 issue dealing with the 1392 v.h.f. Rx. I would swop any issue since 1945 for this.—J. A. Bird, 43 Manor Road, Bolehall, Tamworth, Staffordshire.

... April 1965 issue.—A. Rush, 5 Durham Road, S. Stanley, Co. Durham.

... January, February and March, 1966, and January, February and March 1967. C.O.D. or cash in advance.—M. Ivan Nicholls, 15a Iverson Road, Kilburn, London, N.W.6.

... July 1960 issue—D. Cole, 6 Alexandra Avenue, Newtown, Great Yarmouth, Norfolk.

... March 1966 issue dealing with Part 1 of 19 set mods.—T. R. Smith, 50b Aldershot Road, Guildford, Surrey.

... June 1965 (complete with blueprint) and September 1966 concerning the radio control Tx.—A. Scott, 83 Elmfield Avenue, Erdington, Birmingham 24.

### ISSUES FOR DISPOSAL

... Practical Wireless and Practical Television, complete issues from 1960 to 1966 inclusive.—H. Dodgson, 15 Chestnut Street, Parkinson Lane, Halifax, Yorkshire.

... February 1960, May, July, September, October, November and December 1963. 1964–1965 complete. January–September and November 1966 and January 1967.—J. Tring, Folyambe Terrace, Namartine Street, Nottingham.

**LAST CHANCE \* \* \* \* \***

**“PRACTICAL WIRELESS”**  
 and  
**“PRACTICAL TELEVISION”**  
**FILM SHOW**  
*(In collaboration with Mullard Ltd.)*

**Caxton Hall, Caxton Street, London, S.W.1.**  
*(Great Hall Site)*


**Friday, 14th April, 1967**  
 7.30 p.m. Sharp

**In the Chair: W. N. Stevens**  
 Editor: “Practical Wireless” and “Practical Television”

**see page 19.**

**NEXT MONTH**
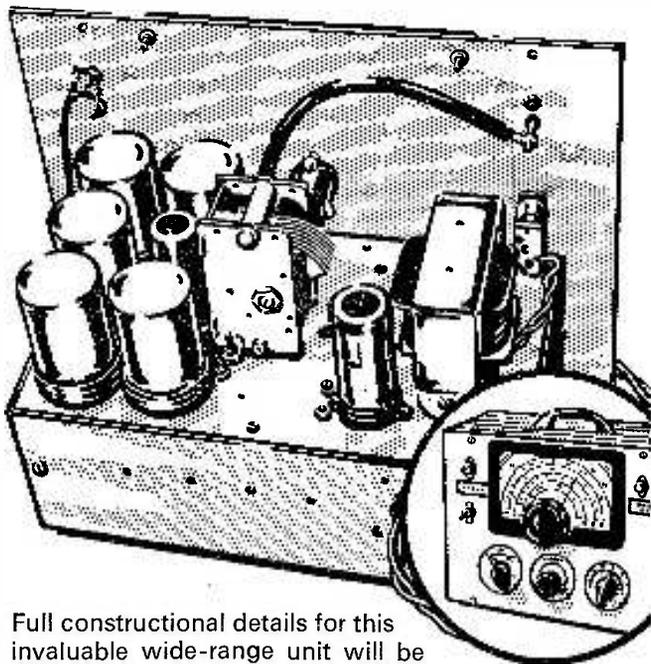
## How to make this **DUAL FUNCTION SIGNAL GENERATOR**



Full constructional details for this invaluable wide-range unit will be included in the June issue of *Practical Wireless*. Covering 200kc/s to 30,000kc/s, it can also be used to determine the resonant frequencies of unknown inductor/capacitor combinations.

### Other Constructional Features

#### **THE DENETTE — AN EASY-TO-MAKE RECEIVER FOR BEGINNERS**

Simple and efficient 3-waveband radio featuring low cost and high sensitivity.

#### **SUPER-SIMPLE TRANSISTOR TESTER**

Ultra-simple circuitry and very low cost. Will check p-n-p or n-p-n transistors for leakage (Ico), a.c. and d.c. gain. A must for every workshop and home experimenter.

# **PRACTICAL WIRELESS**

June issue — on sale May 5th

## **RESERVE YOUR COPY!**

# **THE MW COLUMN**

As we approach summer, reception of North America will become more difficult and there will be a noticeable swing to the more southerly regions. During the past few weeks, nothing of great interest has been heard from North America, only the more common ones like WNRC 660, WOR 710, WABC 770, WHDH 850, WABI 910, CJCH 920, CJON 930, CKBW 1000, KDKA 1020, WHN 1030, CBD 1110, WCAU 1210, WEZE 1260, WORK 1300, WAVY 1350, WPOP 1410, WMEX 1510, WKBW 1520 and WCKY 1530. CBA has been better received lately on 1070, after weeks when LR1 Radio el Mundo was the dominant station. CBN St Johns (Newfoundland) has at times been the strongest signal from North America (640).

WINS, the all-news station, on 1010 has been strongly received, as has CJCB on 1270. St. Pierre et Miquelon on 1375 is also strong still at times.

South America has been better and the log includes YVLL 670, HJAJ 760, ZFY 760, PJB 800, HJKC 850, WVKM 810 (often very good and the best from Puerto Rico), LR3 950, PRB9 1000, YVOZ 1020, LR1 1070, PRG3 1280, PJD2 1295.

Asia has been very poor and apart from the Russian Service Chinese station on 1525, the only ones heard by the writer have been Rajkot (India) 910 and Hanoi 1010—although other DX'ers have done better. Asiatic openings have been all too infrequent this season; last year you could hear several almost daily through the winter months.

With conditions changing we will have to look towards Latin America and we can hope for more from Central American and Caribbean areas. Some to look for are: TIRICA La Voz de Victor, Costa Rica (625), TIGPH 1505, YSS (El Salvador) 655, TGRR (Guatemala) 1120, 4V $\Sigma$ F (Haiti) 1035, Belize 835, Jamaica 750, Martinique (now heard consistently) 1310, XEOY (Mexico) 1000, XEJP 1150, YND Union Radio (Nicaragua) 675. If you want Panama, the best chance is HOL55 Radio Reforma on 1315, but it is usually weak. For Puerto Rico try WAPA 680, WKVM 810, WHOA 870, WRJS 1090, WUNO 1320 and WMDD 1480 (now consistent and good). In Surinam there is a choice of stations on 600 and 725, neither easy. Virgin Islands via WIVI on 970 is possible, but tough! St. Lucia, with Radio Caribbean is easy on 840; it has been consistent around 0030. A few more to search for are Chile on 1060, Peru on 854 and Uruguay (CX14 El Espectador 810 and CX16 Radio Carve 850). These are the best bets of a quite wide range of stations which should make an appearance in the next few weeks.

According to my files, about fifty readers asked for details of my medium wave loop aerial. I hope that by now you have all built them up and are getting results. I look forward to hearing from you all on what has been achieved!

**Alistair Woodland**

# For your Car and Casual Wear



**Superbly Tailored  
but at Ready-to-  
Wear Prices**



QUALITY means everything in men's wear, and the new season's Car Coat, Tweed Sports Jacket and Lovat Tailored Trousers shown here will always look "right", last for years and years. Select what you want for the months ahead and you can be sure of tailoring and cloth of high standard.

## THE "COASTA" CAR COAT

100% Coated Bri-Nylon Cloth. Super lightweight and quilted. Knitted Collar. With the new front-buttoned Yoke. Spacious pockets and in-breast pocket. Multi-coloured quality lining. In the new smoky black. Matching buttons. A high grade leisure jacket for car and every outdoor occasion. Price £6.19.6

## ALL-WOOL SCOTTISH TWEED SPORTS JACKET

Choose from two in tweed woven by Ballantyne of Peebles, Scotland. "MIDLOTHIAN" in traditional lovat green overcheck or "GRAMPIAN" in brown lovat overcheck. Fashionable centre vent at back. 3-button single breasted. Cross pockets and breast pocket. Inside pocket. A jacket of good taste. Price £7.19.6.

## STYLISH TERYLENE WOOL-WORSTED TROUSERS

In "YORK" lovat green or "CHESTER" brown lovat. Will tone with Car Coat or Sports Jacket, but available separately if desired. 55% Terylene, 45% Wool Worsted. Will not shrink or wrinkle. Self supporting and adjustable waistband. Turn-ups. Semi-cross side pockets and hip pocket. Button-fly. Long life guaranteed. Price £5.12.6.

## ★ HOW TO ORDER NO POSTAGE TO PAY

Choose garment or garments you wish to have and write or tick on coupon where required.

<b>"COASTA" CAR COAT</b>	SMALL	MEDIUM	LARGE
	(up to 36" chest)	(38"-40")	(42"-44")
<b>SPORTS JACKET</b>	CHEST SIZE:	34" 36" 38" 40" 42" 44"	
	COLOUR	"MIDLOTHIAN"	
		(lovat green overcheck)	"GRAMPIAN"
		(brown lovat overcheck)	
<b>TROUSERS</b>	WAIST SIZE:	30" 32" 34" 36" 38" 40" 42" 44"	
	INSIDE LEG:	29" 30" 31" 32" 33"	
	COLOUR:	"YORK" (green lovat)	
		"CHESTER" (brown lovat)	

Add your name and full address (in block letters) and send with remittance to:  
**Mr. John Best, W.S.R. Ltd. (W.1.) 15-17, Long Acre, LONDON, W.C.99.**

Cheques, postal orders and money orders should be made payable to W.S.R. Ltd. and crossed "& Co.". If sending cheque write name and address on back. You are guaranteed money refunded if not completely satisfied, provided garment or garments returned in absolutely new and unworn condition within 7 days of despatch to you. This offer does not apply in Eire or Overseas.

## ORDER BY POST NOW

To Mr. JOHN BEST, W.S.R. LTD. (W.1.), 15-17 Long Acre, London, W.C.99

Please send me Quality Men's Wear in sizes and colours as indicated:

**"COASTA" CAR COAT**    SMALL    MEDIUM    LARGE  
 £6.19.6 (Tick clearly the one required)           

**SPORTS JACKET**    CHEST SIZE:.....  
 £7.19.6    COLOUR: LOVAT GREEN (Tick one) BROWN LOVAT

**TROUSERS**    WAIST SIZE:..... Inside leg size.....  
 £5.12.6    COLOUR: LOVAT GREEN (Tick one) BROWN LOVAT

I enclose Postal Orders  
 Money Order, Cheque    Value £    s.    d. No.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

WRITE IN BLOCK LETTERS

(W.1.)

## GUARANTEED QUALITY MEN'S WEAR BY W.S.R. LTD.

**ELECTROLYTIC CONDENSERS**

·25µF .. 3 volt	5µF .. 50 volt	32µF .. 25 volt
1µF .. 15 volt	2µF .. 70 volt	40µF .. 3 volt
1µF .. 15 volt	6µF .. 12 volt	40µF .. 6.4 volt
1µF .. 40 volt	6µF .. 15 volt	50µF .. 6 volt
1µF .. 50 volt	6.4µF .. 40 volt	50µF .. 9 volt
1µF .. 350 volt	8µF .. 3 volt	64µF .. 2.5 volt
1-25µF .. 16 volt	8µF .. 6 volt	64µF .. 9 volt
2µF .. 3 volt	8µF .. 50 volt	64µF .. 10 volt
2µF .. 9 volt	10µF .. 6 volt	64µF .. 16 volt
2µF .. 10 volt	10µF .. 10 volt	64µF .. 40 volt
2µF .. 15 volt	10µF .. 12 volt	100µF .. 3 volt
2µF .. 70 volt	10µF .. 25 volt	100µF .. 6 volt
2µF .. 150 volt	13.5µF .. 4 volt	100µF .. 10 volt
2.5µF .. 16 volt	13.5µF .. 40 volt	100µF .. 12 volt
2.5µF .. 25 volt	16µF .. 16 volt	100µF .. 15 volt
3µF .. 3 volt	16µF .. 30 volt	150µF .. 12 volt
3µF .. 12 volt	16µF .. 150 volt	150µF .. 25 volt
3µF .. 25 volt	20µF .. 3 volt	200µF .. 3 volt
3-2µF .. 6 volt	20µF .. 6 volt	200µF .. 4 volt
3-2µF .. 6.4 volt	20µF .. 15 volt	250µF .. 2.5 volt
3-2µF .. 40 volt	25µF .. 6 volt	250µF .. 9 volt
3-2µF .. 64 volt	25µF .. 12 volt	250µF .. 15 volt
4µF .. 4 volt	25µF .. 25 volt	320µF .. 2.5 volt
4µF .. 12 volt	25µF .. 30 volt	500µF .. 2.5 volt
4µF .. 25 volt	30µF .. 6 volt	500µF .. 25 volt
4µF .. 100 volt	30µF .. 10 volt	750µF .. 2.5 volt
5µF .. 6 volt	30µF .. 15 volt	1000µF .. 18 volt
5µF .. 25 volt	32µF .. 1.5 volt	1000µF .. 6 volt

All at 1/- each 9/- per dozen. Mixed packet (our selection) 20 for 10/- 200/100µF 275 volt; 200/200µF 275 volt; 125/300/50µF 275 volt; 5/- each or 3 for 10/-.

**PAPER CONDENSERS**

·001µF .. 500 volt	·02µF .. 600 A.C.	·25µF .. 350 volt
·001µF .. 1000 volt	·02µF .. 350 volt	·5µF .. 150 volt
·002µF .. 500 volt	·1µF .. 350 volt	·5µF .. 350 volt
·005µF .. 750 volt	·1µF .. 750 volt	·5µF .. 500 volt

All at 15/- per 100 or mixed packet (our selection) 50 for 10/-  
**VERY SPECIAL VALUE! SILVER MICA, POLYSTYRENE, CERAMIC CONDENSERS**  
 Very well assorted. Mixed types and values. 10/- per 100.

**RESISTORS**

Very small 1/2 watt, 5% long leads, ideal for transistor work .. 10/- for 50  
 1/2 watt assorted values including printed circuit types .. 10/- for 100  
 1/2 watt to 3 watt mixed values and types .. 10/- for 100  
 To clear 10 meg. 1/8 watt resistors. £1 per 1,000. 55/- per 1000

**TRANSISTORS**

APZ 12 screened V.H.F. oscillator transistors, 5/- each. OC44, OC45 R.F. Transistors, 4/- each. OC81D 4/- each. OC 71 equivalent 1/- each. 28 per 100. Switching Transistors 45Y 22 (P.N.P.) or L.B.M. (N.P.N.) 6 for 10/- Car radio type Output Transistors type NKT 405 10/- each.

**TELEVISION VALVES BRAND NEW AND BOXED**

PCF80 .. 7/6	PCC84 .. 6/6	PCL83 .. 9/-
PCL84 .. 7/6	BY86 .. 6/-	PCL85 .. 7/6
PL36 .. 9/-	FCC89 .. 9/-	ECC82 .. 6/6
ECL80 .. 6/6	PCL82 .. 7/6	PY33 .. 9/-
PL51 .. 7/6	PY81 .. 6/-	

**COMPUTER DIODES.** Make excellent detectors, also suitable for keying electronic organs. 1/- each or 20 for 10/-.  
**BY100 TYPE TELEVISION H.T. RECTIFIERS.** SPECIAL PRICE 5/- each, 30/- doz.  
**ORP 12 light sensitive resistors** 9/- each.  
**TRANSISTOR BATTERY ELIMINATORS**—same size as PP9 30/-; PP6 20/-.  
**BATTERY CHARGERS,** with meter and fuse. 4 amp. 6/12 volt 55/- each.  
**SOLOIN MODEL 615 Slim Pencil-bit Soldering Irons** 25/- each.  
**WELLER DUAL-HEAT SOLDERING GUN,** 57/6.  
**NUTS, SCREWS and WASHERS,** very useful assorted packs, 6/- each.  
**WALKIE-TALKIES** (not for use in U.K.) £7.10.0 pair.

**MAGNETIC RECORDING TAPE.** British made, fully guaranteed.  
 Standard play. 3in., 150ft., 3/6; 5in., 600ft., 10/6; 5 1/2in., 900ft., 13/6; 7in., 1,200ft., 16/3.  
 Long Play. 3in., 225ft., 4/-; 5in., 900ft., 12/6; 5 1/2in., 1,200ft., 15/6; 7in., 1,500ft., 21/6  
 Double Play. 3in., 400ft., 6/6; 5in., 1,200ft., 20/-; 5 1/2in., 1,500ft., 28/-; 7in., 2,400ft., 34/-; 2 1/2in., 300ft., 6/6.  
 Triple Play Polyester. 3in., 600ft., 12/6; 4in., 900ft., 16/6.

**SIGNAL INJECTOR.** Parts and circuit to make 10/- only.  
**SIGNAL TRACER.** Parts and circuit to make 10/- only.  
**MOTOR CAR REV. COUNTER** (less 1mA meter). Parts and circuit to make 10/- only.  
**TRANSISTORS, COMPONENTS AND CIRCUIT.** To convert 1mA meter to 0 to 10 Meg. ohm meter 10/-.  
**TRANSISTORISED RUMBLE AND SCRATCH FILTER** (for improving reproduction of old records) all components and circuit 30/-.

**SINCLAIR.** All products in stock including latest version of MICRO-6. Worlds smallest radio, and only 59/6.

**NEEDLES FOR RECORD PLAYERS. HALF PRICE!** All types below at 3/6 each.  
 TCSLP; GC2LP; GCSLP; BF40LP; GP87LP; GP87; GP89; TCS StereoLP; Studio OLP. **CARTRIDGES.** Sonotone Mono 10/-, Acos 15/-, Acos Stereo Sapphire 12/6. Diamond 17/6. All complete with needles!

**LAPEL MICROPHONES.** Magnetic or Crystal 10/- each.  
**TAPE RECORDER MICROPHONES.** Fantastic value at 12/- each.  
**ACOS MIC.** 45 30/-, Many other both crystal and dynamic in stock.

**THIN CONNECTING WIRE.** 10yds 1/-; 100yds 7/6; 500yds 25/-; 1,000yds 40/-.

**LOUDSPEAKERS.** 12in. Richard Allen 37/6, 12in. Bakers Guitar 25.5.0.  
 3in., 4in., 5in. and 5 x 3in. all at 10/- each. 8 x 2 1/2in. 12/6. 2in. 80 ohm 7/6.  
**EARPIECES.** Magnetic or Crystal 5/- each.

**VEROBOARD.**  
 2 1/2in. x 5in. .. 3/11 Terminal Pins .. 50 for 3/-  
 2 1/2in. x 3 1/2in. .. 3/3 Spot Face Cutter .. 7/3  
 3 1/2in. x 5in. .. 5/6 Pin Insert Tool .. 9/6  
 3 1/2in. x 3 1/2in. .. 3/11 Special Offer, Cutter & 5 boards 2 1/2in. x 1in. 9/9


**ELECTRONICS DEALER, 600 PAGE CATALOGUE 10/6.**  
**ORDERS BY POST TO**

**G. F. MILWARD**  
**17 PEEL CLOSE, DRAYTON BASSETT, STAFFS.**

PLEASE INCLUDE POSTAGE COSTS

For customers in the Birmingham area, goods may be obtained from ROCK EXCHANGES, 281 ALUM ROCK ROAD, BIRMINGHAM 8.

**LATEST RADIOGRAM CABINETS £9.10.0**

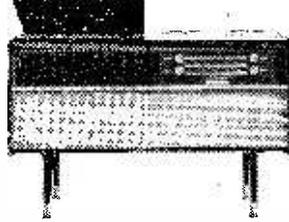


Superbly made and styled in Veneered English Walnut  
 Lift-up lid to changer and record storage compartment  
 Position 8 x 5in. twin Speakers  
 Dimensions: 40 x 16 1/2 x 15 1/2 in.  
 Legs 1 gn. Carr. 30/-  
 Other Models—Send for list



**RECORD PLAYER CABINETS, 49/6.** Latest designed covered cabinets. Takes any modern Auto-changer. P. & P. 7/6.  
**TRANSISTOR CASES 19/6** 9 1/2 x 6 1/2 x 3 1/2 in. P. & P. 2/6.  
**TV TURRET TUNERS, 2/6.** New, less valves. Slim models 5/-. Press button models 19/6. P. & P. 2/6.

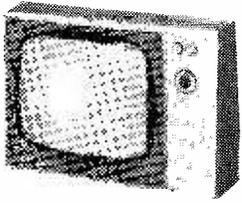**17in.—£11.10.0 TWO-YEAR GUARANTEE EX-RENTAL TELEVISIONS**

3 Star Guarantee  
 ★ Tube ★ Valves  
 ★ Components Carr. 30/-  
**FREE ILLUSTRATED LIST OF TELEVISIONS**  
 17"–19"–21"–23"  
 WIDE RANGE OF MODELS  
 SIZES AND PRICES  
 DEMONSTRATIONS DAILY



**TWO-YEAR GUARANTEED TUBES 100% REGUNNED**  
 14in.—69/6 17in.—89/6  
 21in. and ALL SLIMLINE TUBES 99/6  
 Carr. 10/6  
**EX MAINTENANCE TESTED TUBES**  
 17in.—35/- 14in.—15/-  
 Carr. 5/- (not slimline)

**DUKE & CO. (LONDON) LTD.**  
 621/3 Romford Road E.12 ILF 6001-2-3

**YOUR CAREER in RADIO & ELECTRONICS ?**

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates), the Grad. Brit. I.R.E. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:  
 NAME.....Block  
 ADDRESS.....Caps.  
 ..Please

5.87

**BRITISH NATIONAL RADIO SCHOOL**

# ADD-ON 500mW AMPLIFIER

BY MIKE FISHER

**M**ANY small transistor radios, record players, etc., give only a very limited maximum undistorted output, frequently in the order of a mere 60mW or less. The quality of reproduction from these small sets is frequently very poor, being due almost entirely to the use of very small built in speakers.

A satisfactory way of overcoming these problems is to feed the output of the unit into an external amplifier and speaker assembly, and in this way good quality at a reasonable volume level can be obtained from even the cheapest of sets. The unit to be described is designed for just this purpose, and will push up to 500mW or more into a 3 ohm speaker. The complete amplifier uses three transistors, measures 2½ in. x 2¼ in. x 1 in., and may thus be built into a very compact add-on unit complete with speaker or, in certain cases, may even be built into existing equipment. For ease of construction the unit is assembled on a piece of Veroboard panel, thus retaining all of the advantages of a printed circuit layout while at the same time involving none of the difficulties of marking out, etching, etc., which are involved in normal printed circuit practice.

## The Circuit: How It Works

The circuit of the unit is shown in Fig. 1, the design is exceptionally simple. The input is applied directly to VR1, a 10kΩ variable resistor which acts as the volume control. The signal is passed on from the volume control, via C1, to the base of

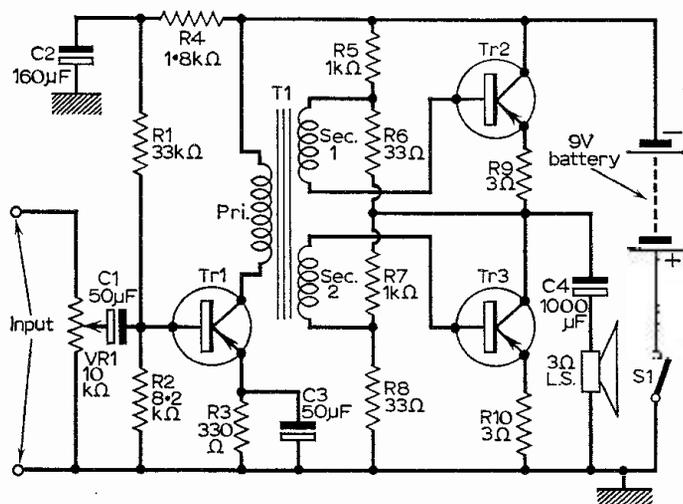


Fig. 1: Theoretical circuit diagram of the amplifier.

Tr1, which is connected as a common emitter amplifier with the primary of T1 as its collector load. R1 and R2 act as the base-bias voltage divider network of Tr1, and R3 is the emitter bias resistor, decoupled by C3 to give d.c. negative feedback over the stage, ensuring good thermal stability. To prevent a.c. instability, the base-bias network of Tr1 is decoupled from the rest of the circuit by R4—C2.

Test Point	Tr1	Tr2	Tr3
Collector	≈8.8	9.0	4.3-4.6
Base	1.0	4.4	0.15
Emitter	0.9	4.3-4.6	≈0.03

*Typical test voltages using a 9-volt supply. Nominal current with input shorted=8.5mA. Voltages measured with a 20,000Ω/V meter on the 10 volt range.*

Transformer T1 acts as the phase splitter for driving the two output transistors, Tr2 and Tr3, the secondary of the transformer being split into two equal windings which are connected in anti-phase. For practical purposes it can be considered that the voltage divider chain R5 to R8 consists of two sections of equal value, i.e., R5 and R6 form the upper section, and R7 and R8 make up the lower section, so that the junction of these two sections is at approximately half of the negative supply rail potential. Thus, each of the two output transistors can be considered as an independent amplifier operating from its own power supply equal to half the full negative rail voltage. Transistor Tr2 is wired as an emitter follower, with R5 and R6 as its base-bias network. The small emitter resistor, R9, is used for thermal stabilisation, and can be ignored, the true emitter load being the external speaker. This emitter follower gives unity voltage gain, and its output, taken from the emitter, is in phase with the input to its base. When an input signal is applied to the base of Tr2 via the secondary of T1, the transistor will conduct on negative half cycles only, and the output signal, of the same phase and form as the input, appears at low impedance at the emitter and is fed to the external speaker. When positive input signals arrive, the emitter-base junction of Tr2 is reverse biased and the transistor is cut off. Tr3, on the

other hand, is wired as a common emitter amplifier with 100 per cent. voltage negative feedback, thus giving unity voltage gain but with 180° phase shift between input and output, the output being taken from Tr3 collector. This transistor is also driven on by negative signals and cut off by positive ones, but the two windings of T1 are so arranged that when Tr2 is driven on, Tr3 is driven off; consequently, the outputs from Tr2 emitter and Tr3 collector complement each other, with the result that the two output transistors operate as a single-ended class-B push-pull amplifier.

The two small resistors, R6 and R8, in the base-bias networks of the output transistors, give a small amount of forward bias to these transistors, so that they conduct even when no input signal is applied. These no-signal currents are kept as small as possible, but must be large enough to prevent any appreciable degree of cross-over distortion. On the prototype, the total no-signal current of the unit was measured as 8.5mA.

The output of the unit is fed to the external speaker via C4. It should be noted that the speaker plays no active part in the operation of the unit, and that no damage results even if the speaker is disconnected. Because of this, the amplifier is suitable for use with any value of speaker impedance, above a couple of ohms, although the maximum available output power will be reduced as speaker impedances are increased. The full 500mW of output power is available when feeding into a 3Ω speaker load.

Although the unit is specifically designed for operation from a 9 volt supply, the circuit can be easily modified to work from any supply in the range of 6 to 18 volts.

## Building the Unit

The unit is wired up on a piece of Veroboard panel, cut from a standard sized sheet. Although the unit is quite small, the layout is not particularly "cramped", since all components are mounted vertically, and the novice can undertake construction with reasonable confidence.

Start construction by cutting the Veroboard panel to size, as shown in Fig. 2, and then break the copper strips where shown. Use a drill, pen-knife, or the special tool that is available for breaking the strips. Next, make the slots for holding the transformer; there are two of these slots, and they are made with the aid of a fret-saw fitted with a small metal cutting blade.

Start assembly of the unit by carefully positioning the transformer, T1, on the blank side of the board, as shown, and solder the leads and the two lugs to the copper strips on the other side. The leads are made of stiff wire, and will have to be bent slightly to fit into the correct holes; scrape the

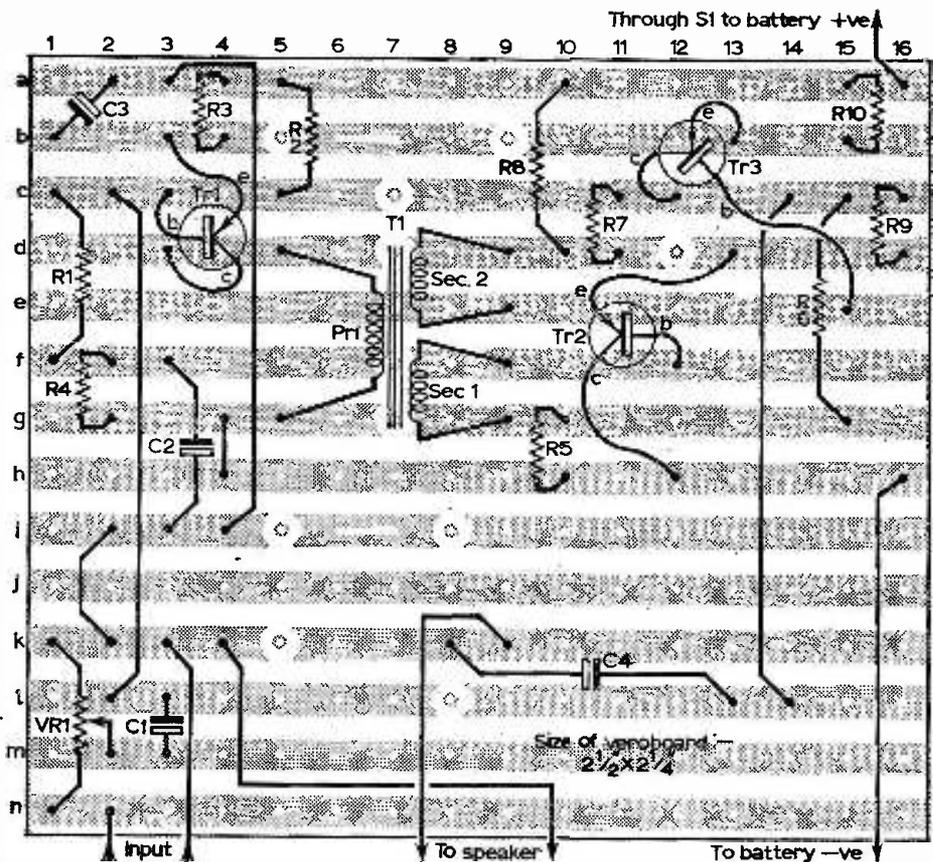


Fig. 2: Wiring diagram of the Veroboard.

varnish off the leads and lugs before attempting to solder them in position. Carefully file and trim the mounting legs of VR1, reducing their width until they fit in the holes in the Veroboard, and then mount and solder the component in position. Finally, wire up the rest of the components on the panel taking care to mount the electrolytics with their polarities as shown; use insulated sleeving where necessary; use heat-shunts when soldering the transistors in place.

When complete, the unit can be tested by shorting the input terminals and, with no external speaker fitted, connecting a 9 volt supply and checking the test voltages and currents as shown in the table. If satisfactory, the unit can now be given a functional check by connecting the external speaker and feeding a signal into the units input. The quality of reproduction should be good up to approximately 500mW r.m.s., with negligible cross over distortion. Distortion will be heard above approximately 500mW, as the amplifier is over-driven. It will be noticed from the circuit diagram that no negative feedback loops are used from output to input; the quality of reproduction is considered to be sufficiently good to make this practice unnecessary.

## Applications and Modifications

The unit is intended to be driven from the ear-phone jack of a small radio, etc., with which it is used; in such cases, the signal at the output jack is usually isolated from d.c. by either a blocking capacitor or transformer built into the radio, and the signal can thus be fed directly to VR1. As a safety precaution the input can be "double isolated" to d.c. by wiring a 50μF electrolytic between the top end of VR1 and the input terminal, the positive



# EVERYTHING YOU WANT IN STEREO EQUIPMENT at bargain prices

## STEREO AMPLIFIERS

### TRS — MULLARD 10-10

- 10 + 10 watts output
- For 3 and 15 ohm speakers
- Complete with valves

**£17.10.0**

(Carr. & pkg. 10/-)

Ready wired and tested, 50/- extra. (Ready built version only available at present)

This newest design from Mullard comprises integrated stereo pre-amp and amplifier with 10 watts output per channel. This is a very fine circuit, kitted by TRS to exact specification with top quality components. Features include ultralinear class B output on each channel with transformers tapped for 3 and 15 ohm speakers; bass, treble, volume and balance controls; switching for mono/stereo and speaker phasing; input switching; input sensitivity—210mV per section; H.T. and L.T. outlet for tuner. Pre-amp section metal shrouded. With escutcheon panel, pilot light indicator, knobs, plugs, etc. Size 11in. x 10 1/2in. x 4 1/2in. Ideal for use with Garrard Units offered below.

### SINCLAIR Z.12

Very good stereo is obtainable by using two of these famous integrated transistor amplifiers which can be used for 3, 5, 8 or 15 ohms speakers. Instructions included with the Z.12 enable you to use matched control circuits with all types of inputs for which we supply the necessary parts. Z.12 Amplifier as advertised in this journal.

**89/6**  
each

### SINCLAIR STEREO 25

De-luxe pre-amp ready built and ideal for two Z.12s **£9.19.6**

### PZ.3

Mains Power Unit **79/6**


### PEAK SOUND SA.8-8

14 transistor integrated stereo pre-amp and amplifier giving 17 watts output into two 5 ohm speakers. A fascinating kit to build, crammed with original features including "Shadow Template" and supply of Cir-kit. Complete down to wire and solder. With front panel, transistors and instructions. **£12.19.6** Mains power supply unit for SA.8-8 78/-

## TUNING UNITS
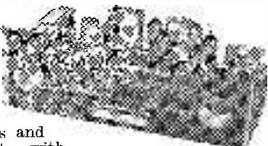
### 6 VALVE A.M./F.M. TUNER UNIT In Kit Form with or without Power Pack

Med. 190 m., 550 m., V.H.F.—86 Mc/s—103 Mc/s., 6 valves and metal rectifier. Self-contained power unit. Magic-eye, 3 push-button controls, on/off, Med., V.H.F. Diodes and high output sockets with gain control. Illuminated 2-colour perspex dial 1 1/2in. x 4 in. chassis size 1 1/2in. x 4in. x 5 1/2in. Strongly recommended for use with Mullard amplifiers. For A.C. mains 200/250 v. Unbeatable value. Complete kit, inc. Power Pack as illustrated, 11 gns. Carr. 7/6. Ditto less Power Pack, 10 gns. Carr. 7/6. Circuit and Construction details, 4/6. Free with kit.




### TRS FM STEREO DECODER

This outstanding kit is based on the highly successful Mullard design and uses 6 Transistors on a printed circuit size 5 1/2in. x 2 1/2in. A 2-stage transistor Stereo Beacon indicator is incorporated. Requires a 12v. supply. Basic Kit is suitable for use with Transistor equipment. With simple mods (data supplied with Kit) easily adapted for use with Valve Tuners and Amplifiers. Kit and assembly instructions complete with Mullard specified inductors Type WF2949 and WF2951. **£4.19.6** with coils **£5.5.0** pre-aligned Packing and postage either model 2/6.

### MULLARD FM DECODER COILS

Designed and made by Mullard. These inductors are as used in T.R.S. Decoder above. TYPE WF2949 and WF2951, each 25/-. Per pair 49/6. Post free.

### UNIQUE TAPE OFFER

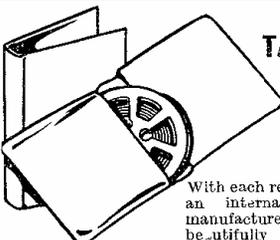

Professional Tape in Unique Library Wallets only from TRS

5" reel 900' **15/-** in wallet  
5 1/2" reel 1,200' **17/6** in wallet  
7in. reel, **22/6**  
1,800 ft. with wallet (p/p 1/6 per reel)

With each reel of this tape by an internationally famous manufacturer we give you a beautifully made wallet strongly made in simulated leather with stiff spring and space for a reel of tape each side. This is professional! full frequency quality tape with metalised leader/stop coils. These library wallets solve once and for all the problems of storing tapes efficiently and tidily.

## SINCLAIR

Micro FM seven transistor pocket tuner/ receiver kit as advertised in this journal. **£5.19.6**  
Micromatic six stage transistor receiver—the world's smallest. **Kit 59/6**  
Micromatic ready built and tested. **79/6**

### "CIR-KIT" INSTANT CIRCUITS

Enables you to produce "printed circuits" quickly and cleanly without chemical or elaborate processes. Kit No. 3 includes baseboard, processed copper strip and sheet as advertised. **15/-**

ENAMELLED COPPER WIRE—2 oz. reels. 14 g.-20 g. 3/-; 22 g.-28 g. 3/6; 30 g.-34 g. 4/3; 36 g.-38 g. 4/9; 39 g.-40 g. 5/- etc. TINNED COPPER WIRE. 16-22 g. 4/- 2 oz. BONDACOUST Speaker Cabinet Acoustic Wadding (lin. thick approx.) 18in. wide, any length cut, 6/- yard, 2/3 per foot. VEROBOARD—All sizes including 2 1/2in. x 5in. 3/8; 2 1/2in. x 3 1/2in. 3/-; 3 1/2in. x 5in. 5/2; 3 1/2in. x 3 1/2in. 3/8; 3 1/2in. x 17in. 12/6. All accessories and tools in stock. VOLUME CONTROLS. LOG and LINEAR. We carry very large stocks in the widest possible range of values, single and ganged. 5K-2 MΩ 3in. Spindles Morganite Midget Type 1 1/2in. diam. Guar. 1 year. LOG or LIN ratios less 8w., 3/6. D.P. Sw. 5/- Twin Stereo less Sw. 7/6. D.P. Sw. 9/6 (100k to 2 Meg. only). STEREO BALANCE CONTROLS. Log/Anti-Log 5KΩ. 10KΩ 1, 1, 2 Meg. 9/- each. ERSIN MULTICORE SOLDER. 60/40 4d. per yard. Cartons 6d., 1/-, 3/6 etc. WIREWOUND RESISTORS. 25 ohm to 10 K 5 w. 1/6. 10 w. 1/9. 15 w. 2/-. CONDENSERS Silver Mica. All values 2 pf to 1,000 pf. 6d. ea. Ditto ceramic 9d. Tub. 450 v. T.C.C., etc. .001 mfd to .01 10d. and 1/360 v. 10d. .02 MF to 0.1 MF. 500 v. 1/- .25 T.C.C. 1/9. 5 T.C.C. 2/-. CLOSE TOL. S/MICAS. 10% 5 pf. 500 pf. 9d. 600-5,000 pf. 1/- 1% 2 pf.-100 pf. 11d 100 pf.-250 pf. 1/2. 270 pf.-800 pf. 1/4. 800 pf.-5,000 pf. 2/-.

### FM TUNER FMT41

This is a six transistor FM Tuner of outstanding sensitivity and efficiency. It employs three stage of I.F. and double tuned discriminator. Suitable for mains or battery operation, this ready built tuner is exceptionally quiet in operation and it compares favourably in performance with far costlier units. Tunes from 88 to 108 mc/s. Complete on stepped metal chassis for easy mounting, and with horizontal scale and tuning control. Size 6in. x 4in. x 2in. **£8.10.0.**

### BARGAIN OPPORTUNITY

#### 7 valve AM/FM/RG Replacement Chassis

A superbly powerful, high performance instrument which makes the ideal way to modernise old equipment whilst retaining good cabinet work. Provides tuning on long, medium and F.M. wavebands with permeability tuning on F.M. Large clear dial with stations clearly named. A.V.C. good neg. feedback. Magic eye. Connections for speaker. P.U. and Tape outlet. 3 w output. A.C. 200/250 v. Circuit diagrams available. Aligned, tested and ready for use. (Carr. and ins. 8/6). S.A.E. brings full details **£13.19.6**

### THE 3d. WAY TO ECONOMY

— 3d. stamp brings you our latest 8-page printed bargain list for April.

## GARRARD UNITS & PLINTHS

LM.3000 R-cord Player with 9T.P. Stereo Cartridge. Limited number available. Brand new as from factory ..... 8 gns.  
AT.60 De-luxe Auto-changer. Die-cast turntable. Superbly engineered. Less cartridge ..... 9 1/2 gns.  
SP.25 De-luxe single player, Die-cast T/Table less cartridge. Packing and carriage on any one of above, 7/6 extra. Garrard Plinth. The ideal modern mounting for the Garrard Units offered here. Will readily suit any hi-fi set-up. Beautifully finished in Teak. Complete with contemporary drop-on plastic cover. Packing and carriage 5/- ..... 72/6  
Garrard Mono Cartridges from 15/-, Stereo from 25/-.

## TRS ALWAYS HAVE THEM!

Resistors in widest possible range of values and tolerances. Examples: 1% Hi-Stab 1/2 w. 10Ω-100Ω 2/-, 1% Hi-Stab 1/2 w. values over 100Ω each 1/6. 5% Hi-Stab 10Ω to 1 meg. 1/2 w. 5d. 1/4 w. 6d. 10% Hi-Stab 2-2 to 10 meg. 1/2 w. 5d. 1/4 w. 6d. 10% Standard 1/2 w., 1/4 w. 4d. 3/4 w. 6d. Send to TRS first for all you want!

## A UNIQUE TRANSFORMER SERVICE

We manufacture Transformers and Chokes of all types to stock or customer specification. Enquiries invited for prototype and small runs.

### HOW TO ORDER

Send cash, cheque or money order with order or pay C.O.D. Please mention "Practical Wireless". Packing and Carriage: unless stated add: 1lb. 1/-; 1lb. 1/9; 2lb. 3/6; 6lb. 5/-; 10lb. 6/6.

# TRS RADIO COMPONENT SPECIALISTS

Est. 1946

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

Phone: THO 2188

Daily 9.0 a.m. to 6.0 p.m.  
Wednesdays 1.0 p.m.

A few doors from Thornton Heath Stn. S.R. from Victoria

# BI-PAK SEMICONDUCTORS

8 RADNOR HOUSE  
93/97 REGENT STREET  
LONDON W1

★ VALUE PAKS for '67  
★ — NEW — UNTESTED —

PIV	LOW COST SILICON CONTROLLED RECTIFIERS (THYRISTORS) FACTORY TESTED				Free SCR Literature, Circuits, etc. with SCR orders or on request.
	1 AMP (TO-5 can)	7 AMP (STUD)	16 AMP (STUD)	30 AMP (STUD)	
25	7/6	7/6	10/6	30/-	
30	7/6	8/6	10/6	35/-	
100	8/6	10/-	15/-	45/-	
200	12/6	15/-	20/-	55/-	
300	15/-	20/-	25/-	80/-	
400	17/6	25/-	35/-	95/-	
500	—	30/-	45/-	—	
600	—	40/-	50/-	—	

**FREE** One 10/- Pack of your own choice free with orders valued £4 or over **FREE** LOGIC MODULES and/or, Gates, Memory Units, Timer Units, etc., details free **FREE**

**VALUE PAK 50** TRANSISTORS MIXED UNTESTED **10/-** | **10SCR's** UNMARKED, UNTESTED VOLTAGE RANGE 1 Amp 30-400 PIV **20/-**

3 OC139 Trans. NPN Mullard	10/-	3 High volt. AF Trans. PNP ACY17	15/-
2 Driit Trans. 2N1225 100 M/Cs PNP	10/-	5 Sil. Rect. 750mA 100 PIV TEXAS	15/-
6 Matched Trans. OC44/45/81/81D	10/-	3 BSY95A Sil. Trans. STC	15/-
4 OA10 Diodes Mullard	10/-	3 Sil. Trans. OC200 Mullard	15/-
15 Red Spot AF Trans. PNP	10/-	2 Sil. Power Rect. 6 Amp. 200 PIV BYZ18	15/-
15 White Spot RF Trans. PNP	10/-	1 AF139 GERM. Trans. 1500 M/Cs	15/-
4 Sil. Rects. 3A 100/400 PIV	10/-	1 Sil. Power Trans. 100 M/Cs TK 201A NPN	15/-
4 NPN Trans. OC139 2N1302, etc	10/-	6 Zener Diodes 3-15 volts. Mixed 400 mW	15/-
2 10 Amp. Sil. Rect. 50/100 PIV	10/-	5 OA5 Gold Bonded Diodes Mullard	15/-
8 Diodes 4 OA70, 4 OA79	10/-	1 2N1132 PNP PLANAR Trans. Sil.	15/-
1 5 AMP SCR 100 PIV	10/-	2 2N697 NPN PLANAR Trans. Sil.	15/-
3 Sil. Trans. 28303 PNP	10/-	4 GERM. Power Trans. eqvt. OC16 Mullard	15/-
5 GET884 Trans. Eqvt. OC44	10/-	1 UNIJUNCTION Trans. 2N2646 G.E.	15/-
10 Assorted Computer Diodes	10/-	2 Sil. Trans. 60VCB 200 M/Cs. ZT83/84	15/-
4 Zeners 5, 6.8, 10, 12 Volts	10/-	1 Sil. PLANAR Trans. BSY25 NPN 100 M/Cs	15/-
4 2G417 Trans. Eqvt. AF1116/117	10/-	1 Sil. Trans. IS104 150 M/Cs HFE 200 NPN	15/-
2 200 M/Cs Sil. Trans. BSY26/27	10/-	2 SCR's 50 PIV 1 Amp. TO-5 can	15/-
2 Bi-directional Trans. ASY66	10/-	1 Tunnel Diode IN3720 (TD-5) G.E.	15/-
4 High Current Trans. OC42 Eqvt.	10/-	1 2N2160 UNIJUNCTION Trans. TO-5 can	15/-
2 Power Trans. OC26/35	10/-	2 Sil. Rect. Type BY100 800 PIV Stud	15/-
5 Sil. Rects. 400 PIV 250mA	10/-	1 Tunnel Diode AEY II STC. 1050 M/Cs	15/-
3 OC71 Trans. Mullard	10/-	2 GERM. Power Trans. OC28/29	15/-
3 OC75 Trans. Mullard	10/-	2 ZENERS 25 watt 18 and 22 volts	15/-
3 NPN Sil. Trans. 70 M/Cs	10/-	6 Sil. Rect. Type BY100 800 PIV 550mA	20/-
1 Power Trans. OC20 100 Volts	10/-	8 Sil. Rect. 400 PIV 200/500mA	20/-
5 OA47 Gold Bonded Diodes	10/-	1 Transistor Manual by G.E. 648 pages	30/-
4 OA202 Sil. Diodes Sub-Min.	10/-	1 Silicon Controlled Rect. Manual G.E.	30/-
3 OC77 Trans. Mullard	10/-	25 Mixed Sil. & GERM. Trans. New Marked	30/-
8 OA81 Diodes CV448	10/-	40 Mixed Semiconductors New Marked	40/-
3 Sil. Rects PIV. 400 500 mA	10/-	1 Logic Module Handbook & Catalogue	17/6

GERM. SUB MIN.  
**120 DIODES 10/-**

ALL TYPES MIXED VOLTS  
**20 ZENERS 10/-**

SIL. NPN 200 M/Cs  
**25 Transistors 10/-**

1 Amp. GERM. up to 300 PIV  
**20 RECTIFIERS 10/-**

SILICON 200 mA  
**60 DIODES 10/-**

SILICON 750 mA TOP-HAT  
**16 RECTIFIERS 10/-**

**SILICON BRIDGE RECTIFIERS**  
NEW TESTED  
600 PIV 2 Amp. at 55°C.....25/- EACH  
800 PIV 2 Amp. at 55°C.....30/- EACH

A COMPLETE RANGE OF SILICON RECTIFIERS  
750 mA TO 25 Amp. 50-1000 PIV NOW IN STOCK.  
ASK FOR PRICE LIST.

Our vast stocks change daily with hundreds of Semiconductor bargains becoming available. Just send 2/6 to cover 3 months mailing of our latest stock lists, eqvt. charts, circuits, etc.

Minimum Order 10/-. CASH WITH ORDER PLEASE. Add 1/- postage and packing per Order. GUARANTEED by return postal service. Overseas add extra for Airmail.



# YOURS FREE FOR 7 DAYS

The New 'Picture - Book' way of learning

# BASIC

**ELECTRICITY (5 Vols)**  
**ELECTRONICS (6 Vols)**  
**ELECTRONIC CIRCUITS (2 Vols)**  
**INDUSTRIAL ELECTRICITY (2 Vols)**  
**SYNCHROS & SERVOMECHANISMS (2 Vols)**

You'll find it easy to learn with this outstandingly successful new pictorial method. The essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

## WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

... These books make interesting reading of a complicated subject ...  
V.L., Basingstoke.

... I am delighted with these marvellous manuals, so easy to follow, well done ...  
W.A., BUSHY

... I have found these manuals extremely clear and easy to understand ...  
L.L., YORK.

**POST NOW FOR THIS OFFER!**

**TO SELRAY BOOK CO.**  
**60 HAYES HILL, HAYES, BROMLEY, KENT**

Please send me **Without Obligation to Purchase**, one of the above sets on **7 Days Free Trial**. I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **Basic Electricity 70/-**. Cash Price or Down Payment of **15/-** followed by 4 fortnightly payments of **15/-** each. **Basic Electronics 82/-**. Cash Price or Down Payment of **15/-** followed by 5 fortnightly payments of **15/-** each. This offer applies to **UNITED KINGDOM ONLY**. Overseas customers cash with order.

Tick set required (only ONE set allowed on free trial).

**BASIC ELECTRICITY 70/-**  **BASIC ELECTRONICS 82/-**

**BASIC ELECTRONIC CIRCUITS 40/-**

**BASIC INDUSTRIAL ELECTRICITY 40/-**

**BASIC SYNCHROS & SERVOMECHANISMS 38/-**

**ALL PRICES INCLUDE POSTAGE**

Signature .....

(If under 21, signature of parent or guardian)

NAME .....

FULL POSTAL ADDRESS .....

BLOCK LETTERS BELOW

side of the capacitor being connected to VR1. If the amplifier is to be built into a small cabinet complete with speaker, VR1 may be replaced by a front panel mounted fully variable component of the same value; this component should preferably be complete with a ganged on/off switch.

The unit may be driven from any supply in the range of 6 to 18 volts, but in such cases the values of R6 and R8 will have to be adjusted to bring the total no signal currents of the amplifier within the approximate range of 8 to 12mA, the precise current value being the minimum that will give satisfactory operation without appreciable crossover distortion. As the operating voltage is increased, the maximum available output level will rise, and it may be necessary to use heat sinks on the two output transistors; the output transistors may become warm, but should not be allowed to become hot when driven at full output level for appreciable periods of time.

The completed amplifier panel can be mounted to a chassis, etc., by drilling two small holes in the panel to clear 6BA screws, which are pushed through the Veroboard from the blank side and bolted to the chassis, using small rubber grommets as spacers/insulators. If this modification is made, make sure that the screws do not short out any of the components, or the holes break any of the copper strips in places where the circuit operation will be effected.

## Low Impedance Preamplifiers

The sensitivity of the amplifier can be increased by incorporating a simple preamplifier into the design. The precise form of the preamplifier will depend on individual requirements, and four alternative types are shown in Figs. 3a to 3d.

### Less than 100Ω

If the input is to be fed from a very low impedance source, less than a hundred or so ohms, the preamplifier shown in Fig. 3a should be used. Here, Tr4 is wired as a grounded base amplifier, with the input fed via C5 to the emitter. The output of the grounded base amplifier is taken from R11, the Tr4 collector load. The input impedance of the main amplifier is very low, in the order of a few hundred ohms, and this impedance is effectively in parallel with the output impedance of the preceding stage, so that, if the output of Tr4 were fed directly to the main amplifier, the effective value of R11 would be greatly reduced and very little extra gain would be available. In Fig. 3a this snag is overcome by interposing emitter follower Tr5 between the output of Tr4 and the main amplifier, this emitter follower acting as a buffer and making considerable extra gain available. The final output of the preamplifier is taken from Tr5 emitter and fed, via C7, to the input of the main amplifier.

### 1000Ω Impedance

If the amplifier is to be fed from a medium impedance source, in the range of 1000 ohms or so, Fig. 3b should be used. Here, Tr4 is wired as a conventional common emitter amplifier, with the input signal fed to Tr4 base via C5. R11 and R12 are the base-bias resistors and R14 decoupled by C6 provides emitter bias, and R13 is the main


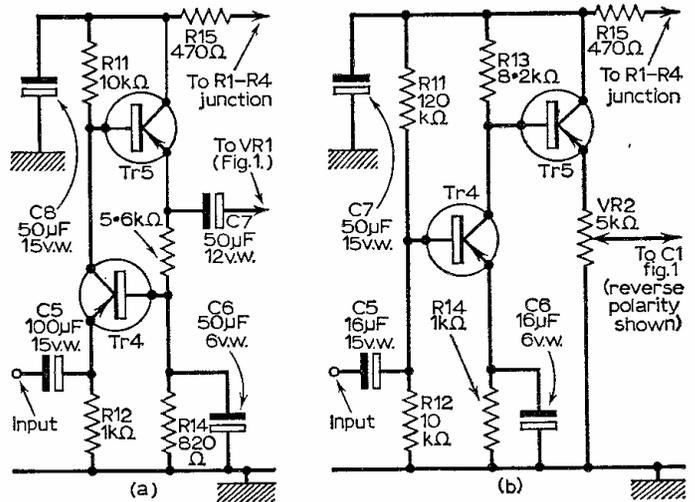


Fig. 3 (a): Preamp for use with low impedance input.  
 Fig. 3 (b): Circuitry for medium impedance inputs.  
 Fig. 3 (c): Super-alpha configuration for high impedance.  
 Fig. 3 (d): Very high input impedance preamp.

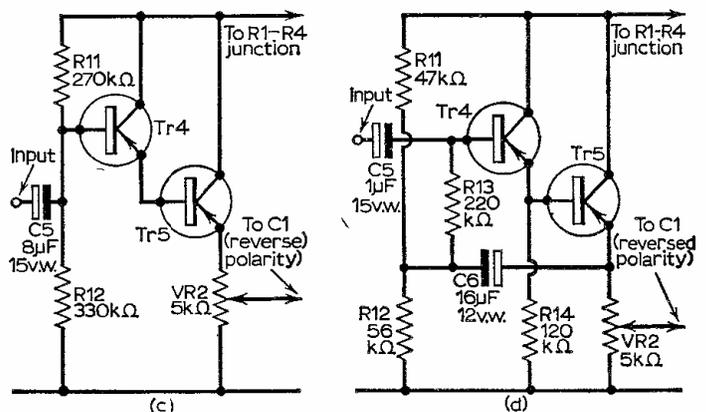

collector load of Tr4. An emitter follower, Tr5, is again used as a buffer between Tr4 and the main amplifier, but in this case variable resistor VR2 is used as the emitter load. The output of this stage is taken from the slider of VR2 and fed directly to C1 of Fig. 1. Note that in this case VR1 of Fig. 1 should be omitted from the circuit and the polarity of C1 should be reversed. In the cases of the two preamplifiers so far considered, decoupling networks R15—C7 or C8 are inserted in the negative supply lines to prevent instability.

## High Impedance Preamps

If the amplifier is to be driven from a high source impedance, the input signal will usually be of reasonable amplitude, and will not require additional voltage amplification, but will need to have its impedance matched to the low input impedance of the main amplifier without any significant loss of signal strength. In this case, one of the preamplifiers shown in Figs. 3c and 3d should be used.

### Up to 100kΩ

If the source impedance is in the order of 100kΩ or less, the circuit shown in Fig. 3c should be used. Here, transistors Tr4 and Tr5 are compound connected in the Super-Alpha or Darlington configuration, and may be regarded as a single transistor with a current gain equal to the product of the two individual transistor gains. This compound

## ★ components list

### Resistors:

R1	33k $\Omega$	} carbon 1/2 Watt 10%
R2	8.2k $\Omega$	
R3	330 $\Omega$	
R4	1.8k $\Omega$	
R5	1k $\Omega$	
R6	33 $\Omega$	
R7	1k $\Omega$	
R8	33 $\Omega$	
R9	3 $\Omega$	
R10	3 $\Omega$	
VR1	10k $\Omega$ sub-min pre-set skeleton type	

### Capacitors:

C1	50 $\mu$ F	} 15V sub-min electrolytic
C2	50 $\mu$ F	
C3	160 $\mu$ F	
C4	1000 $\mu$ F	

### Transistors:


Tr1	OC75
Tr2	OC81
Tr3	OC81

### Transformer:

T1	Radio spares type TT3 Ratio 3.6 : 1 + 1.
----	---
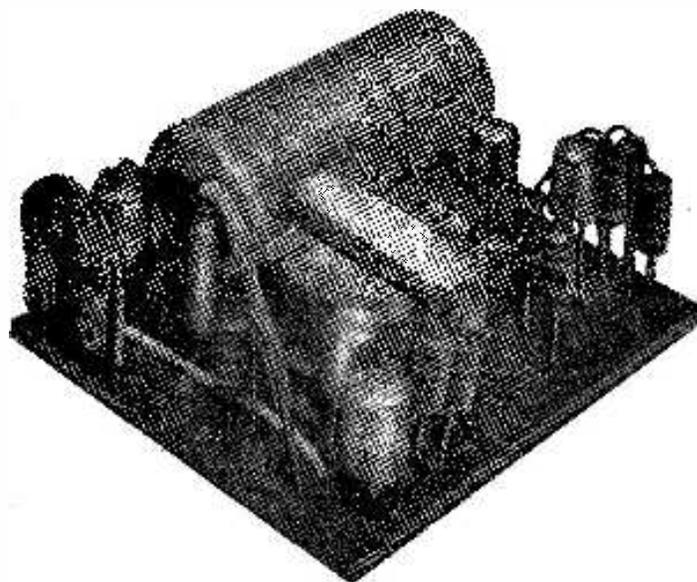
### Miscellaneous:

Veroboard, wire, sleeving, 9V battery, 3 $\Omega$  speaker, solder, etc.



General view of the completed main amplifier.

"transistor" is wired as an emitter follower, with R11 and R12 providing base-bias and VR2 as the main emitter load. The input signal to this circuit is applied to the base of Tr4 via C5, and the output is taken from the slider of VR2 and fed directly to C1 of Fig. 1. The input impedance of this preamplifier is in the order of 120k $\Omega$  when the unit is connected up to the main amplifier.

### 1M $\Omega$ and higher

If the source impedance of the input signal is very high, in the order of 1M $\Omega$  or so, as in the case of a crystal microphone, etc., the preamplifier shown in Fig. 3d should be used. Here, if R13, R14 and C6 are ignored, the circuit can be seen to be similar to that of Fig. 3c. In the case of 3c, however, the input impedance is limited by the shunting effects of the base-bias resistors, R11 and R12. In Fig. 3d these limitations are overcome by interposing an isolating resistor, R13, between the junction of R11 and R12 and the base of Tr4. The output signal, taken from the emitter of Tr5, is of the

same form and phase as the input, which is applied directly to Tr4 base, and a part of this output is taken from the Tr5 emitter and fed to the R11-R12 junction, so that, when an input signal is applied, similar signals appear at both ends of R13 and very little a.c. current thus flows in this resistor, which thus appears to a.c. as a very high impedance, in the order of a couple of Megohms, in spite of the fact that its real value is only 220 $\Omega$ . A very high input impedance to Tr4 base is thus obtained. This technique of artificially increasing the apparent value of a resistance is known as Bootstrapping, and it may be used to give effective input impedances of up to several hundred Megohms using normal germanium transistors.

Note that in the cases of the preamplifiers shown in Figs. 3c and 3d the outputs are fed directly to C1 of Fig. 1, which should have its polarity reversed, and that VR1 should be omitted from the circuit. Also note that additional decoupling networks are not required in the negative supply lines. ■

### TV AERIALS AND TRANSMISSION LINES

Design plus practical do-it-yourself dimensions.

#### 625 LINES ON 405

Thoughts on the structure of the TV signal

#### HOTTING UP A BAND III AERIAL

Simple modification to improve directivity

#### STORAGE TUBES FOR TELEVISION

A peep at slow-scan television techniques

all in

**PRACTICAL TELEVISION**

on sale April 21 Price 2s.

### PRACTICAL ELECTRONICS

MAY ISSUE

PRICE 2/6

ON SALE FRIDAY APRIL 14

CONSTRUCTION PROJECTS

LIGHT-OPERATED STOP WATCH

SCOOTER ALARM SYSTEM

ELECTRONIC BASS GUITAR

NEW SERIES


**ELECTRONIC COMPUTERS**

# THE WORLD'S SMALLEST RADIO

MEASURES ONLY  $1\frac{4}{5}$ " X  $1\frac{3}{10}$ " X  $\frac{1}{2}$ "

*Check it for yourself!*

AND CHECK THE PERFORMANCE TOO!

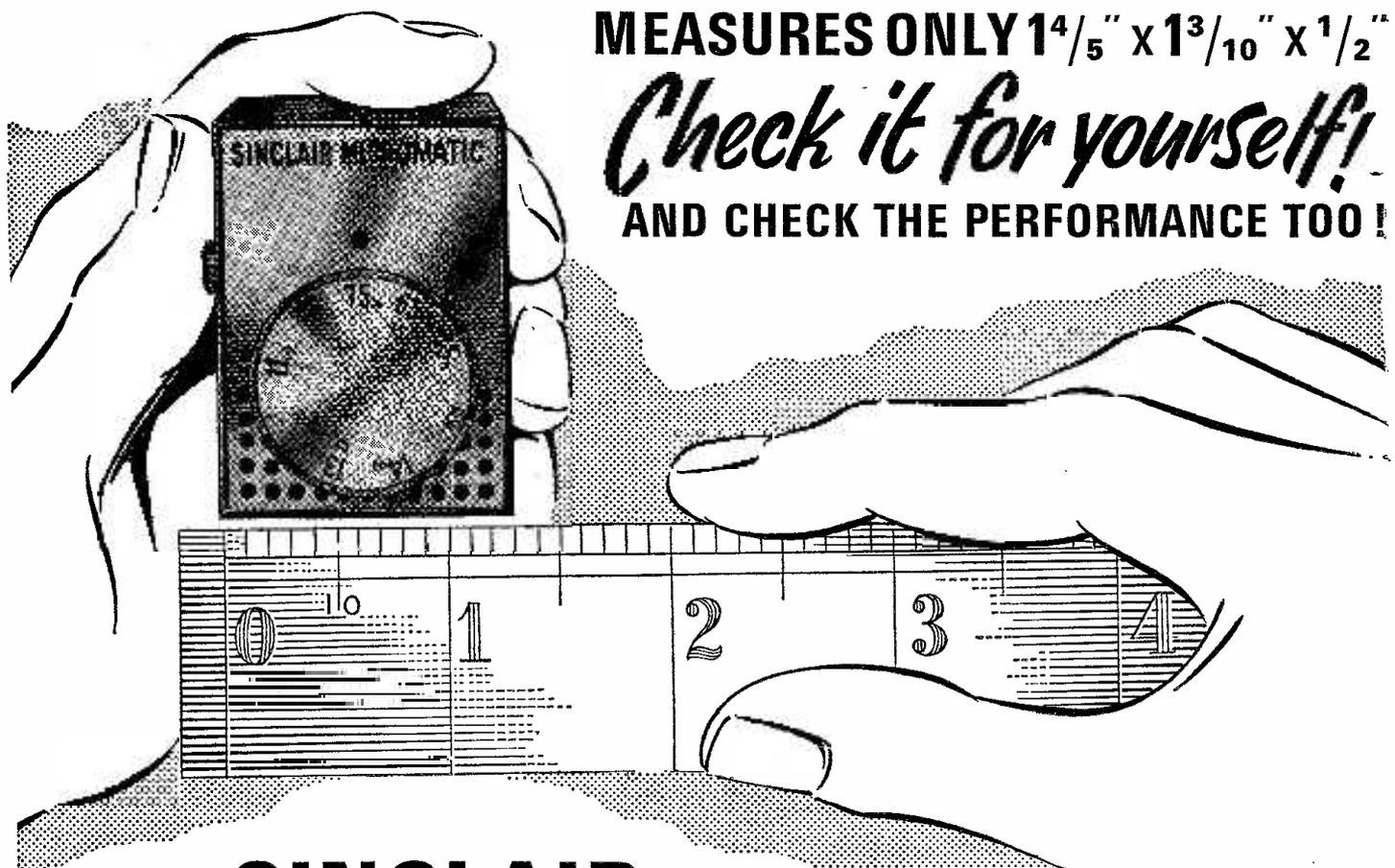

## SINCLAIR MICROMATIC

SIX STAGE  
TRANSISTOR  
RECEIVER

- ★  $1\frac{4}{5}$ in. x  $1\frac{3}{10}$ in. x  $\frac{1}{2}$ in.
- ★ CALIBRATED DIAL
- ★ BANDSPREAD TUNING
- ★ AMAZING POWER AND RANGE
- ★ GUARANTEED 5 YEARS

These are the facts—the Sinclair Micromatic is so small that its design brings it into the realm of real micro-electronics. Its performance and reliability are so good that it assures superb reception virtually anywhere. Its elegant styling inside and out make this a truly professional receiver, yet building the Micromatic is so simple that anyone can tackle it with complete confidence. Check these facts for yourself, and when you use your Micromatic, you will find it giving you the radio thrill of a lifetime.



### TECHNICAL DESCRIPTION

*In neat plastic case with aluminium front panel and calibrated aluminium tuning dial. Two stages of powerful R.F. amplification are followed by a double diode detector from which the tuned signal passes to a high gain three stage audio amplifier. Automatic Gain control counteracts fading from distant stations. The set is powered by two Mallory ZM.312 Cells obtainable anywhere for 1/7 each and giving approx. 70 hrs. working life. Inserting the earpiece plug switches the set on.*

ORDER FORM AND MORE SINCLAIR DESIGNS ON NEXT PAGES

IN THE SEALED "SEE FOR YOURSELF" KIT PACK

Complete kit of parts, including lightweight earpiece, instructions and solder.

**59/6**

Built, tested and guaranteed. Inc. earpiece all in case.

**79/6**

**sinclair**

SINCLAIR RADIONICS LTD, 22 Newmarket Rd., CAMBRIDGE

Telephone 52996 (STD Code OCA3)



# SINCLAIR STEREO 25 DE-LUXE PRE-AMP CONTROL UNIT

FOR USE WITH ANY GOOD STEREO SYSTEM

## TECHNICAL SPECIFICATIONS

Performance figures obtained using Stereo 25, two Z.12s and a PZ.3.

- **SENSITIVITY** for 10 watts into 1.5 ohms load per channel. Mic.—2mV into 50K ohms. Pick-up—3mV into 50K ohms; Radio—20mV into 4.7K ohms.
- **FREQUENCY RESPONSE** (M/c. and Radio)—25 c/s to 30 kc/s  $\pm 1$ dB extending to 100 kc/s  $\pm 3$ dB.
- **EQUALISATION**—Correct to within  $\pm 1$ dB on RIAA curve from 50 c/s to 20 kc/s.

## TONE CONTROLS

- Treble +12dB to -10dB at 10 kc/s.
- Bass +15dB to -12dB at 100 c/s.
- **SIZE**—6½in. x 2½in. x 2½in. overall, plus knobs.
- **FINISH**—Front panel sectioned in brushed and polished solid aluminium with solid aluminium knobs. Black figuring on front panel.

BUILT,  
TESTED AND  
GUARANTEED

£9.19.6

THE SINCLAIR STEREO 25 has been designed specially to ensure the highest possible standards of reproduction when used with two Z.12s or any other first class stereo power amplifier. Best possible components are used in the construction of this superb unit, whilst its appearance reflects the professional elegance characteristics of all Sinclair designs in hi-fi, radio and TV. The front panel of the Stereo 25 is in solid brushed and polished aluminium with beautifully styled solid aluminium control knobs. Mounting the unit is simple, and power is conveniently obtainable from the Sinclair PZ.3 which can also be used to supply two Z.12s to make a complete stereo assembly. Hi-fi enthusiasts seeking the ultimate in domestic listening will find all they want from this combination of Sinclair units. With a Micro-FM for tuner, they will have an installation to compare favourably with anything costing from four to five times as much.

*"I want to congratulate you on such a marvellous little receiver. I am very pleased with the results when connected to my tape recorder."*

D.M., Yeovil, Somerset


**A NEW SINCLAIR  
DESIGN—SEE  
PREVIOUS PAGE**

## SINCLAIR GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question.

## SINCLAIR MICRO-FM
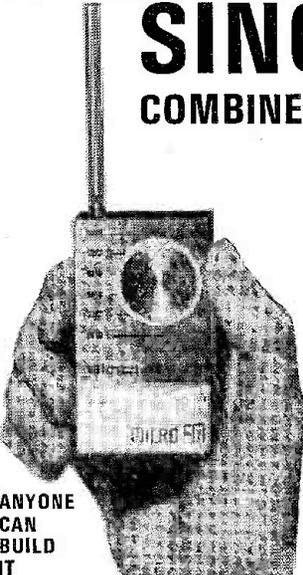
### COMBINED FM TUNER AND POCKET FM RECEIVER



ANYONE  
CAN  
BUILD  
IT

- 7 TRANSISTORS
- 
- NO ALIGNING
- 
- PULSE COUNTING  
DISCRIMINATOR
- 
- A.F.C.
- 
- TUNES 88-108Mc/s
- 
- SIZE—less than 3" x 1½" x ¾"

FM superhet using 7 transistors and 2 diodes. The R.F. amplifier is followed by a self-oscillating mixer and three stages of I.F. amplification which dispense with I.F. transformers and all problems of alignment. The final I.F. amplifier produces a square wave which is converted to produce the original modulation exactly. A pulse counting discriminator ensures better audio quality. One output is for feeding to amplifier or recorder and the other enables the Micro-FM to be used as an independent self-contained pocket portable. A.F.C. "locks" programme tuned in. Signal to noise ratio 30dB at 30 microseconds.

*Complete kit, including transistors, case, aerial, earpiece, etc.*


## £5.19.6

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS



SINCLAIR RADIONICS LTD, 22 Newmarket Rd., CAMBRIDGE

Telephone 52996 (STD Code OCA3)

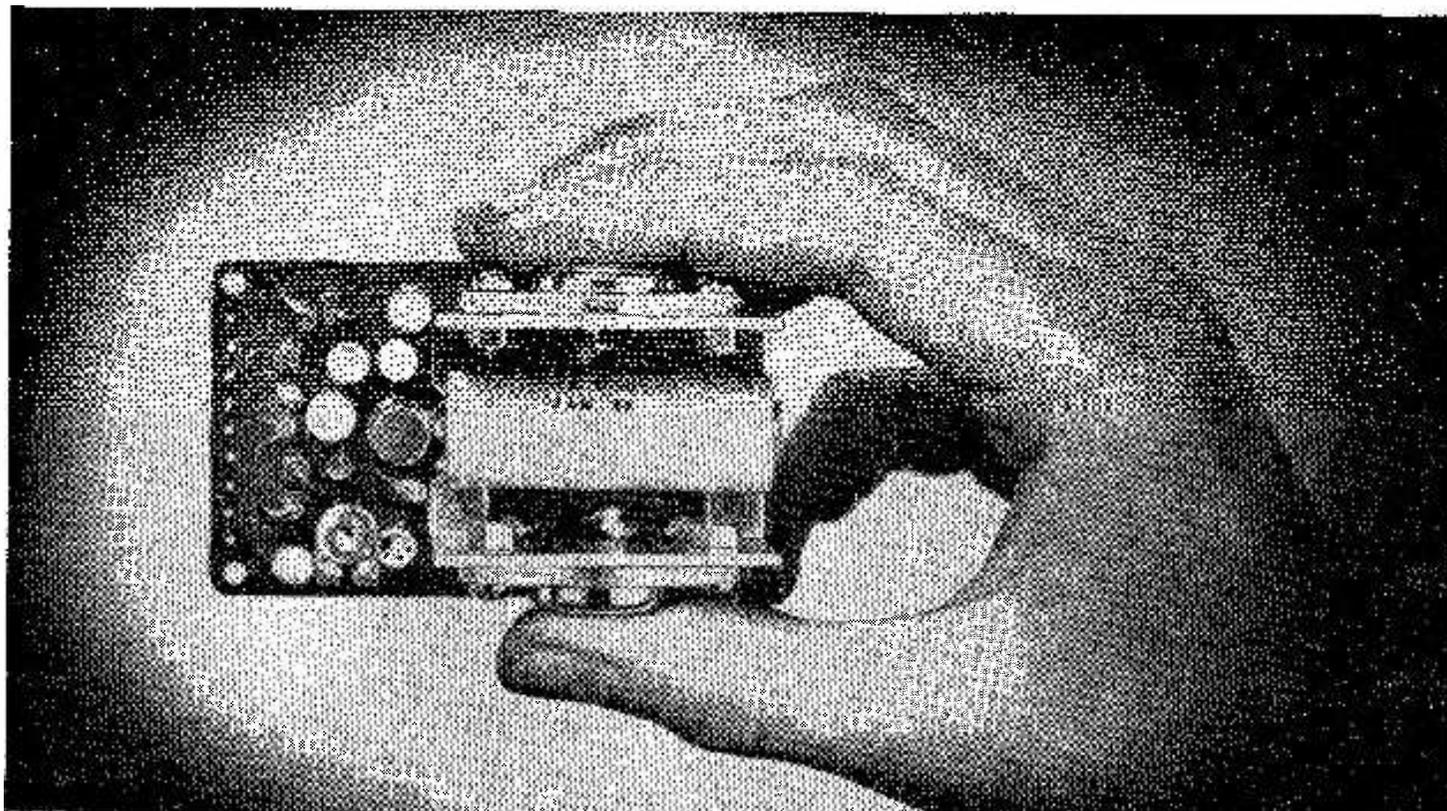

# Z.12 - THE WORLD'S MOST REMARKABLE AMPLIFIER

## for size

The Z.12 uses eight transistors measures 3in. x 1½in. x 1½in. and weighs 3 ounces.

## for power

A 12 watt R.M.S. continuous sine wave output (24w. peak) is obtainable from the Z.12. Music Power—15 watts (30w. peak). It can be used with loudspeakers from 3 to 15 ohm impedances. Two 3 ohm speakers may be used in parallel.

## for versatility

Designed essentially for use as a high fidelity unit the Z.12 can be used equally well with radio tuners such as the Sinclair FM, as a car radio, in an electric guitar system, for P.A. or intercom, in the lab., etc., etc. It will operate from 6 to 20V., D.C., and can be run ideally from a car battery.

## for reliability

Your Z.12 reaches you assembled, bench tested and guaranteed. The instructions supplied make installation simple; full details are included for wiring up control circuits.

## for value

Built tested and guaranteed the Z.12 costs only

PZ.3 Mains Power Unit 79/6

# 89/6

THE SINCLAIR Z.12 combined 12 watt amplifier and pre-amp is now the accepted standard for high fidelity units for constructors. It has ultralinear class B output with an input sensitivity of 2mV into 2K ohms. Frequency response—15-50,000c/s ± 1dB. Signal to noise ratio is better than 60dB. This brilliantly versatile amplifier comes to you ready built, tested and guaranteed, ready for use, and complete with comprehensive instructions manual for matching tone control circuits in mono and stereo (two Z.12s are required for the latter).

## WHAT Z.12 USERS WRITE

"I have recently bought a Z.12 and have been amazed at the power output from such a small unit. I use it for an electric guitar system and find that for small halls it is quite powerful enough."

J.R.F., Londonderry.

"I have for some time been running my Z.12 with a PZ.3 power supply and may I say that I am thoroughly delighted with the performance which in my opinion is better than that given out by . . . costing many times as much as my unit."

R.S.C., London, N.20.

"The whole assembly (two Z.12s, tone control circuits) works like a charm and is the envy of all who have listened to it."

P.C., Durban, S.A.

"I am the proud owner of a pair of those remarkable amplifiers Z.12. I was more than surprised to hear the splendid tone and volume. The thing that staggered me most of all is the small size of the Z.12. May I express my thanks."

C.R.R., St. Vincent, West Indies.

"It is wonderful to be able to hear my records properly (with the Z.12).

J.S.H.S., London, W.2.

"I have now had an opportunity of trying out the tuner with the Z.12 amplifier and my Quad speaker and am very pleased with the results.


H.A., London, N.6.

If you prefer not to cut this page, please quote P.W.5 when writing your order.

		<p>To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE</p>
		<p>Please send items listed below:</p> <p>NAME .....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>.....</p> <p>For which I enclose cash/cheque/money order</p> <p style="text-align: right;">PW.5</p>

**OUT NOW!**

# The Best Buy of the Year for Motorists

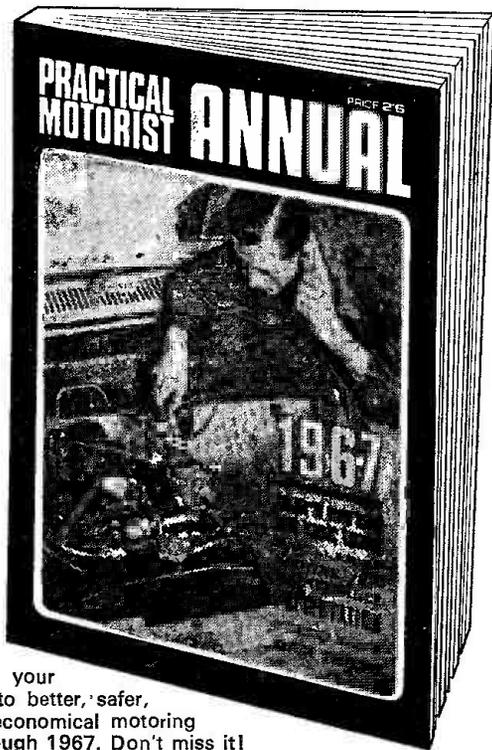

Here's your guide to better, safer, more economical motoring all through 1967. Don't miss it!

## GENERAL OVERHAUL AND BASIC TUNING

Step-by-step guides on overhauling engine, clutch, brakes, steering, suspension—how to obtain maximum performance from a standard engine.

## SERVICING ANCILLARIES

Full details for servicing distributor, starter motor, dynamo, water pump, carburettor, fuel pump—how to replace core plugs.

## ROUTINE MAINTENANCE

Typical adjustments fully explained, plus a comprehensive description of decarbonising and valve grinding techniques.

## INTERIOR AND EXTERIOR PRESERVATION

How to give your car a thorough cleaning from stem to stern—preparation and re-spraying of coach-

work—how to adjust doors—methods used to secure trim.

## ELECTRICS

How to find your way round a wiring diagram, fit electrical accessories, look after battery, check flashers, cure radio interference.

## ACCESSORIES REVIEWED


Examines a selection of the type of accessory that most motorists will want to fit into their car for added comfort and safety.

## CAR AND ACCESSORY TESTS

A detailed appraisal of some of the newer popular cars including some 'hot' models, plus comments on accessories we have tested.
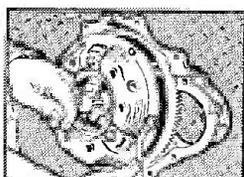
## TIPS FROM EXPERTS

A variety of useful wrinkles that will save time, money and trouble on the road and in the workshop, and make for better all-round motoring.



**BIG DEMAND! HURRY FOR YOUR COPY!**

**PRACTICAL MOTORIST ANNUAL** 2/6

Introducing . . . . .

THE NEW RICHARD ALLAN

# SARABANDE


RECOMMENDED RETAIL PRICE: £39.17.6

A magnificent triple speaker assembly containing a high flux 15" unit for no compromise bass,

and the new
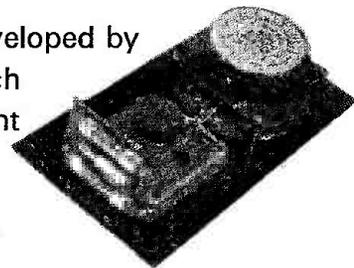
## MID RANGE & TWEETER MODULE

which has been developed by the same team which produced the brilliant High Fidelity Module.




THE SARABANDE OFFERS THE FINEST VALUE OBTAINABLE IN THIS PRICE RANGE OF LOUDSPEAKERS

*Richard Allan*

RICHARD ALLAN RADIO LTD., BRADFORD ROAD, GOMERSAL, CLECKHEATON, YORKS. TEL. CLECKHEATON 2442
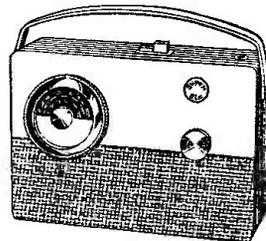
## The SUPER 6 LONG & MEDIUM WAVE TRANSISTOR RADIO



A quality radio available as a kit or ready-built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £21.12.0 commercial model.

★ All new parts. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit. ★ Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet 11 x 7½ x 3½in. ★ Vinyl covered in various colours. ★ 6 x 4in. speaker giving good bass and treble response. ★ Full instruction booklet, 2/-. Free with kit. ★ I.f. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately. Write for list, S.A.E. **COMPLETE KIT ONLY £4.0.0** P. & P. 5/- OR FULLY BUILT £6.7.6. Tax and Carr. Paid.

**NEW 6 PUSH-BUTTON STEREOGRAM CHASSIS.** M.W.; S.W.1; S.W.2; V.H.F.; Gram; Stereo Gram. Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6½in. high. Dial cream and red. 15 x 3in. 190-550M; 18-51M; 80-187M; VHF 86-100 Mc/s. Valves: ECC86, ECH81, EF89, 2 x ECL86, EM84 and Rect. Price £19.19.0, carr. paid or £6.13.0 deposit and 3 monthly payments of 58/6. Total H.P. price £20.15.6. Cream moulded escutcheon included.

## TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS — 2 or 4 TRACK (4 TRACK 25/- EXTRA)

Chassis 12½ x 5½ x 4½in. high. Plastic front panel "gold" finish—12½ x 4½in. 200-250 A.C. Record/Playback amp. switch; Off/On-Tone; Vol/Mic; Vol/Gram; Mic. Input; Gram. Input; Monitor; Speaker Sockets. Valves 6BR7; 12AX7; EM84; EL84; 6X4 Separate power pack. Complete amp. and power pack, £8.17.6. (8/- P. & P.). Rexine covered cabinet (tan) 15½ x 17 x 9½in. high with sloping front for amp; complete with two tweeter speakers, and special adapting brackets for Magnavox Deck—85/- (8/- carr.) 3 speed Magnavox 2 track tape deck £10.17.6; 4-track £12.15.0. Complete Recorders (with speed compensation) 2-track £29; 4-track £32 (carr. 25/-). Worth £10 more on normal retail prices.

## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants. Aldershot 2224  
(2 mins. from Station and Buses)  
CLOSED WEDNESDAY AFTERNOON  
CATALOGUE 9d.  
Bulk enquiries invited for Export.



# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/6d. per word (minimum order 18/-), box number 1/6d. extra. Semi-displayed setting £4. 12s. 6d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL WIRELESS, George Newnes Ltd., Tower House, Southampton Street, London, WC2, for insertion in the next available issue.

## SERVICE SHEETS

SERVICE SHEETS. 5,000 Models. 4/- each. 48 hour service. 59 Station Lane, Featherstone, Pontefract, Yorks.

SERVICE SHEETS. RADIO, TV. 5,000 Models. List 1/6. S.A.E. Enquiries. TELRAY, Maudling Bk., Preston.

SERVICE SHEETS for all makes, Radio, T/V, Tape Recorders, 1925-1966. Prices from 1/-. Catalogue 6,000 models 2/6d. Free fault-finding guide with all Sheets. Please send stamped addressed envelope with all orders/enquiries, HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS (75,000) 4/- each. Callers welcome. Always open. 5 South Street, Oakenshaw, Bradford.

RADIO TELEVISION over 8,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

## SERVICE SHEETS

4/- each, plus postage

We have the largest display of Service Sheets for all makes and types of Radios and Televisions, etc., in the country. Speedy service.

To obtain the Service Sheet you require please complete the attached coupon.

Name: .....

Address: .....

.....

.....

To: S.P. DISTRIBUTORS

35/36 Great Marlborough Street,  
London, W.1

Please supply Service Sheets for the following

Make: .....

Model No..... Radio/TV

Make: .....

Model No..... Radio/TV

Make: .....

Model No..... Radio/TV

I require the new 1967 List of Service Sheets at 1/6 each plus postage.

(please delete items not applicable)

enclose remittance of.....  
(which includes postage)

MAIL ORDERS ONLY (May) PW

## MISCELLANEOUS

CONVERT ANY TV SET into an Oscilloscope. Diagrams and instructions 12/6. REDMOND, 42 Dean Close, Portslade, Sussex.

## MISCELLANEOUS

(continued)

ALUMINIUM CHASSIS, PANELS, etc. Quick service, 'One-offs' welcome. Send sketch for quotation (stamp please). Trade supplied. FAIRISGRADES LTD., Barling, Nr. Southend, Essex.

### BERNIESOUND (AUDIO ENGINEERS)

Design-Build-Repair-Modify

All types of Electronic Equipment

For estimates write to:—

Mr. Brown, 1 Effie Place, London, S.W.6.

IDO (reformed Esperanto). More elegant, precise and easier; more likely to be officially adopted. Brit. Ido Soc., 31 Parkside Gardens, London, S.W.19.

## ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 6 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 3d. stamp.

## BOOKS & PUBLICATIONS

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—list free. WILLEN (Dept. 40), 61a Broadway, London, E.15.

## A Guide to Surplus Communication Receivers

A detailed guide to thirty-one receivers:—

AR88D	CR100	P104	R1132
AR88LF	CR150	R107	R1155
BC312	CR150/2	R109	R1392
BC342	CR150/3	R206	R1475
BC348	PCR	R208	TCS
BC453	PCR1	R209	52 set
BC454	PCR2	R216	HRO
BC455	PCR3	R220	Senior

7/6 P. & P. 1/-. Mail Order only to:

ADKINS, Dept. PW, 72 Courtenay Avenue,  
Harrow, Middlesex

## TAPE RECORDERS, TAPES, Etc.

TAPES TO DISC—using finest professional equipment 45 rpm—18/-. S.A.E. leaflet. DERROY, High Bank, Hawk Street, Carnforth, Lancs.

## SOUND RECORDINGS

A UNIQUE TAPE BUY! Top brand 7in. 2,400ft., 25/-; 5½in., 1,200ft. 15/-. P. and P. 1 at 2/-, 2 at 2/9, 3-6 at 3/6. Bargains in all sizes. S.A.E. for list. E. C. KINGSLEY AND CO. LTD., 93 Tottenham Court Road, London W.1., EUSton 6500.

## EDUCATIONAL

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

I.E.R.E., City & Guilds and R.T.E.B. exams. Specialised ICS home-study course will ensure success. For details of wide range of exam. and diploma courses in Radio, T.V. & Electronics, also new practical courses with kits, write to: ICS (Dept. 542), Parkgate Road, London, S.W.11.

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies during 1967. Grants available. Day and Boarding students. Stamp for prospectus. Wireless College, Colwyn Bay.

BECOME 'Technically qualified' in your spare time, guaranteed diploma and exam. home-study courses in radio, T.V. servicing and maintenance. T.T.E.B., City and Guilds, etc: highly informative 120-page Guide—free. CHAMBERS COLLEGE (Dept. 857K), 148 Holborn, London. E.C.1.

CITY & GUILDS (electrical, etc.) on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc., send for 132 page Handbook—FREE. B.I.E.T. (Dept. 168K) Aldermaston Court, Aldermaston, Berks.

## TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs) R.T.E.B., etc. Many unique diploma courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS DEPT. 541 PARKGATE ROAD  
LONDON, S.W.11.

## PUBLIC APPOINTMENTS

**TECHNICIANS/JUNIOR TECHNICIANS** required (a) experienced in electronics and preferably with ability in the use of machine tools for applied acoustics research laboratories, and (b) to do interesting work for research laboratories, including photographing and electronic assembly. Salary Junior Technician £366-£624 p.a., Technician £698-£1078 depending on qualifications and age. Application forms obtainable from Superintendent of Laboratories, Physics Department, Chelsea College of Science and Technology, Manresa Road, London, S.W.3. Tel. FLA 6421 ext. 28.

## SITUATIONS VACANT

**ARE YOU** Interested in Electronics? Do you want an interesting job making, testing and installing specialist sound equipment? If you do, write to the Managing Director, Stage-sound (London) Ltd., 11/12 King Street, Covent Garden, W.C.2.

**ALDERMASTON COURT POSTAL TRAINING** for B.Sc. (Eng) Part 1., A.M.I.E.R.E., A.M.S.E., City & Guilds, G.C.E., etc. prepares you privately for high pay and security as Technician or Technologist. Thousands of passes. For details of Exams & Courses in all branches of Engineering, Building, Electronics, etc. (including latest information on C.Eng.), write for 132-page handbook—FREE. Please state interest. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

**RADIO & TV Exam.** and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E., City & Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russell Street, Reading.

## SITUATIONS VACANT

(continued)

## RADIO TECHNICIANS

A number of suitably qualified candidates are required for permanent and pensionable employment (mostly in Cheltenham, but from time to time there are some vacancies in other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to candidates who can offer "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19—£747, at 25—£962 (highest age pay on entry) rising by four annual increments to £1,104.

Prospects of promotion to grades in salary range £1,032-£1,691. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

**Recruitment Officer (RT),  
Government Communications  
Headquarters  
Oakley, Priors Road  
CHELTENHAM, Glos.**

## SITUATIONS VACANT

(continued)

**FULL TIME ASSISTANT** experienced in handling components required. Retail shop. 5 day week. Please write giving age, experience salary required. **FRANK MOZER RADIO**, 5 Angel Corner Parade, Edmonton, N.18.

**BIDEFORD RELAY** require a qualified Relay Engineer. Good salary dependent upon experience in the Television Relay field. Clean driving licence essential. Apply to The Secretary, Bideford Relay Ltd., 26 Market Place, Bideford, Devon.

TV and Radio, City & Guilds, R.T.E.B., Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

## METAL WORK

**ALL TYPES** Metal Cabinets, Control Panels, Chassis, made to order. One-offs welcome. Send specifications, sketches, etc., to **HAWLEY SUPPLY CO. (ELECTRICAL) LTD.**, 5 Ethelbert Road, Hawley, Dartford, Kent.

**METAL WORK:** All types cabinets, chassis racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.** Chapman Street, Loughborough.

(continued on next page)

## MINISTRY OF TECHNOLOGY

### CAREER OPPORTUNITIES FOR THE SKILLED CRAFTSMAN

Opportunities exist for craftsmen in the Grade of Mechanic Examiner in both the Aeronautical Inspection Directorate and Electrical Inspection Directorate. The work will cover a wide range of electronic, electro-mechanical and mechanical equipment, and metallurgical work connected with the aircraft and electronics industries. There are vacancies in well-equipped laboratories at Bromley (Kent), Woolwich and Harefield (Middx.), and at firms' premises in London and the Home Counties.

<b>Qualifications</b>	A recognised apprenticeship or equivalent experience or training (including training in H.M. Forces).
<b>Pay and Prospects</b>	Greater London Area £17 8s. 0d. to £18 18s. 0d. for a five day 40-hour week. Overtime available in certain areas. Opportunities for promotion to higher grade posts with salaries up to £1,650 p.a. for men who possess or obtain the necessary qualifications, e.g. O.N.C. or C. & G. Final Cert. Time off allowed and fees paid for attending approved courses at Technical Colleges.
<b>Holidays</b>	2 weeks (80 hours) rising to 3 weeks (120 hours) after 5 years' service in the grade, plus 8½ days public holidays.
<b>General Information</b>	Paid sick leave scheme in operation.

Applications, giving brief details of apprenticeship and/or experience, and stating location preferred, to be sent to:

**MINISTRY OF TECHNOLOGY,  
E.I.D. (A.O./C.S.),  
"AQUILA", GOLF ROAD,  
BROMLEY, KENT.**

**FOR SALE**

**FOR SALE:** Philips Transworld De-luxe Portable Receiver L6X38T. Condition as new. Offers. J. DEANE, 36 Manor Court, Leamington Spa.

**FOR SALE**

(continued)

**FOR SALE,** Eddystone 770/R. 19 valve communication receiver. Coverage 19M/c. to 165M/c. Condition as new. Box No. 67.

**RECEIVERS & COMPONENTS**

**TRANSISTORS, UNMARKED, UNTESTED,** 40 for 10/-, p. and p. 1/-, 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc. (5,000 items), free. K. R. WHISTON (Dept. PRW), New Mills, Stockport.

**HAMMERITE**

**HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK**

**3/8 TIN • JUST BRUSH ON • WITHSTANDS 150° C. OIL, WATER ETC.**  
 2½ oz. tins .... 3/6      ½ gallon ..... 85/-\*  
 1 pint ..... 7/6      1 gallon ..... 58/-\*  
 1 pint ..... 15/-  
 Carriage: Orders up to 5/-, 9d.; up to 10/-, 1/9; over 10/-, 3/-. Colours: blue, silver, black or bronze. Return of post service, Monday to Friday.

From your component shop or direct from the manufacturer:  
**FINNIGAN SPECIALITY PAINTS (PW)**  
 Mickley Square, Stocksfield, Northumberland.  
 Tel. Stocksfield 2280.

**YUKAN 50 PROFESSIONAL THE YUKAN SELF-SPRAY HAMMER or BLACK WRINKLE (CRACKLE) finishes**

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/11 at our counter or 15/11, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.

**SPECIAL OFFER:** I can plus optional transferable snap-on trigger handle (value 3/-) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or P.O. for total amount to:

**YUKAN, Dept.**  
**307a EDGWARE ROAD, LONDON, W.2.**  
 Open all day Saturday Closed Thursday afternoons

Other Yukan Air Drying Aerosols include:  
 Zinc Chromate Primer  
 Clear Lacquer, Anti-Tarnish Gold and Metallic Finishes.

Dept. PW/5

**MORSE MADE EASY !**

**FACT NOT FICTION.** If you start right you will be reading amateur and commercial Morse within a month.

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune.

For full explanatory booklet enclose 8d. in stamps to: G3CHS/P.  
**45 GREEN LANE, PURLEY, SURREY**  
 S.T.D. 01-660.2896

**ANALOG COMPUTER**

Just think... with this desk-top mini-analog computer you can multiply and divide, take square roots or powers, and do log operations—simply by turning the dials and keeping your eye on the null meter. (And all this from a 1½ volt cell!) The Instruction Manual covers MAC-1's applications in electronics and physics, engineering and trigonometry.

Complete in kit form, MAC-1 is 3 gns— or £3 13s 6d built and ready for use. (For either please add 6s carriage.)

You would probably like more information: just send a 4d stamp to:

**I-COR SYSTEMS (File W2)**  
**18 Stamford Hill, London N.16**

**WANTED**

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

**VALVES WANTED**, brand new popular types boxed. **DURHAM SUPPLIES (C)**, 175, Durham Road, Bradford 8, Yorkshire.

**WE BUY** New Valves and Transistors. State price. **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

**WANTED:** Popular Brand New Valves. **R.H.S. Stamford House**, 538 Great Horton Road, Bradford 7.

**DAMAGED AVO METERS** wanted. Models 7 and 8. Any condition. Any quantity. Send for packing instructions. **HUGGETTS LTD.**, 2-4 Pawson's Road, West Croydon.

**WANTED NEW VALVES ONLY**

Must be new and boxed  
 Payment by return

**WILLIAM CARVIS LTD**  
 103 North Street, Leeds 7

**Radio—TV—Electronic Components**

**BARGAIN PRICES NEW TRANSISTORS**

OC44, OC45, OC71, OC72, OC81, OC81D, OC82, OC82D, all at 2/6 each. AF114, AF115, AF116, AF117, at 3/- each

BY100, 6/- each. B9A low loss v/holders at 1/6 per dozen.

Edgewise Volume Controls with Switch 5K, Jap Replacement, 3/6 each.  
 PP3 Battery Clips with Leads, 1/- each.  
 ½in. Iron Dust Cores, 1/- per dozen.  
 (P. & P. 6d.)

**HALSE RADIO**

61 Coppins Road, Clacton-on-Sea, Essex

**NEW 1,000 pf solder-in, feed-through capacitors.** 20 for 5/-. G3LXP, 68 Hughenden Road, St. Albans, Herts.

**R & R RADIO & TV SERVICE**

Dept. P.W.  
**MARKET STREET, BAGUP, LANCs.**  
 Telephone 465

**SALVAGE VALVES**

Tested before despatch

6F13	4/6	U329	5/-	30PL1	4/-	20P4	6/6
6L8	4/6	10P14	5/-	PL36	6/-	PCC84	4/-
EF90	1/6	20P5	6/6	PL82	3/6	PY81	8/6
ECC82	3/-	30P	7/-	U801	7/6	U301	6/-
ECL60	3/6	6F15	5/-	10F1	1/6	10P13	5/6
30P5	5/-	EB91	1/-	30FL1	5/-	20D1	2/-
PCP80	4/-	EP85	5/-	PY32	6/-	30P12	5/-
PL81	5/-	630L2	4/-	6U4GT	5/-	PY83	5/-
PZ30	5/-	20P8	6/-	EY86	4/-		

**Speakers.** Ex.T.V. 5in. round 6 x 4in., 3/6; 8in. round 8/-; post 2/-.

**Line Output Transformers** available. State set model No.

**Turret Tuners**, 8/- post 2/-.

**Scan Coils**, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

**150 NEW ASSORTED** Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous. ½-20 watt, 12/6. Post Free. **WHIT-SAM ELECTRICAL**, 18 Woodrow Close, Perivale, Middlesex.

**BARGAINS! BARGAINS!**

**Ex. Government Equipment**

**HRO'S, AR88's, 19 Sets** and equipment, **31 Sets, B44's. 88, 38 and 18 Sets** and miscellaneous Surplus Equipment.

**A. J. THOMPSON (Dept. P.W.)**

Eiling Lodge, Codicote, Hitchin, Herts.

Tel.: Codicote 242

**SPECIAL OFFER. GRUNDIG MA1. 2** Transistor Pre-amps for Tape Monitoring or Microphone Boosters, 47/6, post paid. **LIST PRICE 4 GNS. LEE ELECTRONICS**, 400 Edgware Road, Paddington 5521

**MINIFLUX 4-Track** stereophonic/monophonic record/playback heads. List Price 6 gns.—Special Offer 55/- each. **MINIFLUX 4-Track** stereophonic/monophonic Ferrite Erase Heads. List Price £3.10.0.—Special Offer 32/6 each, or supplied together (one of each) at £3.17.6. **SKN4 ½-track** stereophonic record/play heads for Transistor Circuits at 55/- each. Also available ½-track and full-track monophonic Ferrite Erase Heads. All heads complete with technical specifications. Send S.A.E. for details. **LEE ELECTRONICS**, 400 Edgware Rd., Paddington 5521.

**TRANSISTORS SPECIAL OFFER**

**1 watt S.T.C. 300 mc/s N.P.N. Silicon Planar Transistors**, limited stocks £1 for 6.

WITH DATA

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16, GET20.

4/- each. AF114, AF115, AF116, AF117, OC170 OC171.

5/- each. OC139, OC140, GET7, GET8, GET9, XC141, BY100, OA211.

BSY27 7/6 each OC20 10/- each

**ZENER DIODES**

All volts between 3.9v. and 26v. ¼w 3/6 each, 1.5w 5/- each, 7w 6/- each.

Send 6d. for full lists:— inc., S.C.R., Zeners.

**CURSONS**

78 BROAD STREET CANTERBURY, KENT

**RECEIVERS & COMPONENTS**  
(continued)

**STELLA NINE RANGE CASES** In Grey or Black Stelvetite Removable Back/Rubber Feet. All fitted with aluminium chassis. Cash refund if not suitable in any way:

- 4-Channel Audio Mixer. 7" x 3½" x 2", 10/3.
- 3-5 Mc/s Phone Transmitter. 8" x 6" x 4", 18/6.
- Transistor Tester. 6" x 3" x 2", 8/6.
- P. A. Pre-amplifier as Type D. 8½" x 3½" x 3½" x 2½", 14/6.
- Signal Generator Test Gear No. 2. 9" x 6" x 3", 22/-.
- Mighty Light. 8½" x 3½" x 3½", 15/6.
- Model Train Controller. 8½" x 5" x 3", 17/6.
- Linear Scale Cap Meter. 8½" x 5½" x 4", 18/6.
- The Explorer. 6½" x 4½" x 2½", 11/6.

Other sizes in stock. S.A.E.

**P.O. UNIT 1 x 3**

Each unit contains:

- 6—12 way Miniature Sockets.
- 2—12 way Miniature Plugs c/w Screen Lead.
- 1—6 way Miniature Socket.
- 1—2µF Condenser 250v. DC.W.
- 1—1µF Condenser 250v. DC.W.
- 1—Induction Coil P.O. No. 3/16.
- 1—Retardation Coil 400r.
- 1—Selenium Rectifier Type 280/LU658A.
- 1—Operators 4-pin Jack Socket.
- 3—6-pole Changeover Toggle Switch with spring return to "Off".
- 3—180Ω-3W Resistors.
- 3—12v Miniature Lilliput Screw Cap Lamp Holders with lamps and white plastic lens.
- 2—Metal Instrument Cases 5" x 5" x 4" plug in type.
- 1—Rack for Instrument Cases, horizontal or vertical mounting.
- 2—Humidity indicators.

ALL BRAND NEW IN SEALED CARTONS.  
20/- each, plus part post 5/-.

Assorted High Stab Resistors. 7/6, 100.

Assorted Syflex P.F. Condensers. 7/6, 100.  
Thin Pakolin Sheet, approx. 1/64" x 12" x 12", 6 sheets for 5/-.

White Plastic Sheet, approx. 1/32" x 6½" x 24" Suitable dials, insulation, case fronts, etc. 4 sheets for 5/-.

P.O. Relay 2000 ohm, 1B, 5/-, 1M, 1B, 6/-.

Plessey Plugs and Sockets, 12 way, 3/- pr., 6 way 5/- pr.

6 or 12 way screened cable to match, 3/- yd. Breast Mike, 6/-, Carbon Inserts, 1/6.

Small Component Boxes, 12/6, for 60 samples 6d. 100 volt Hand Generator, 7/6.

Modern lightweight Breast Mikes, Polythene fittings. New, 7/6, spare insert 2/6.

Type 3000 P.O. relay. New 6000 ohm coil, 2 sets of change-over, 8/6.

Printed circuit board, 11" x 5½" ideal for reuse with 28 diodes CV488 plus some high stab resistors, 10/- post paid.

Polystyrene capacitors 125 volts wkg., 120,000. Recent manufacture for computer co. Prices 6d. each, 5/- doz., 25/- per 100. Your choice of values stock up now and save pounds. FREE sample with lists of values.

Siemens High Speed Relay, S.P.C.O. 1,000 + 1,000 ohms, 6/-.

Small Sealed Relay 1,700 + 1,700 ohms S.P.C.O., 6/-.

P.O. Relay. 200 ohms 2 change over, 6/-.

Mains transformer output 350-0-350v at 100mA + 2 x 5v at 2A, 1 x 2v at 1A, 1 x 6.3v at 2a, 15/-.

Extra Small Rotary Transformer by Hoover, 12v in output 300 v suitable razors etc., with cooling fan new boxed. 10/-.

**E. R. NICHOLLS**

Mall Order and Retail Shop  
46 LOWFIELD ROAD  
OFF SHAW HEATH, STOCKPORT  
CHESHIRE

**RECEIVERS & COMPONENTS**  
(continued)

**TRANSMITTING VALVES**, 813 or 4B13, also 811-G.B., 3 Guildford Close, West Worthing, Sussex. Worthing 6151.

**WILSON ELECTRONICS**

- 2/- ea. AC126, 127, 128; 2G374B, S18T, S19T.
- 2/3 ea. OC81, 81D, 82, 82D, 2/6 ea. OC44, 45.
- 3/- ea. OC71, 72, 170; AC 126, 127, 128.
- 3/6 ea. AF115, 116, 117, 118, 119, 125, 127; AC107. 4/- ea. AF114, OC 171, 172. 7/- ea. OC23, 25, 26, 28. 8/6 ea. OC200. 11/- ea. AD140. 11/6 ea. OC35, 38.

20, BRADBOURNE AVE., WILFORD NOTTINGHAM

**BRAND NEW TELEVISION TUBES!**

2 YEAR GUARANTEE. VAST RANGE

- 12" £3; 14" £4 (not CRM141)
- 17" £5.15.6; 19" £6.17.6 etc. etc.

Carriage 12/-


Also British valves, lists free!

PHILIP H. BEARMAN, 6 Potters Road, New Barnet, Herts. Bar 1934/7873.

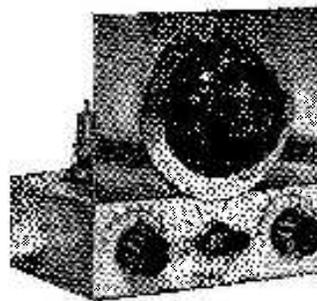**SEMICONDUCTOR SPECIAL**

AF139 12/6d., AF239 13/6d. Silicon Diodes 3/6d. per doz. Surplus BY100s 3/6d., 8 for £1. Surplus 2N706s 2/-d., 17/6d. doz. 5 Assorted 5 and 10A Thyristors £1. Post paid from J. C. WOODWARD, 94 Great Brickkiln Street, Wolverhampton, Staffs.

**H.A.C. SHORT-WAVE KITS**  
NEW RELEASE: MODEL "DX"



Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

**IMPROVED 1967 RANGE**


One-valve model "DX", complete kit—price 58/6 (Postage and packing 3/6.)

Customers say: "Definitely the best one-valve S.W. Kit available at any price." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form, etc., to:—

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1




**EQUIPMENT CABINETS OF DISTINCTION**

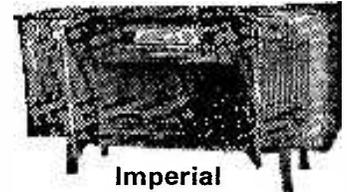

Imperial

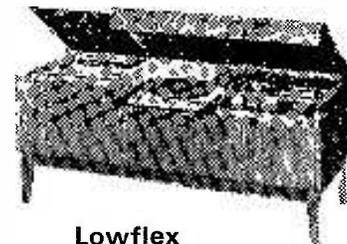- Illustrated in this advertisement are two fine cabinets from the Lewis Radio Range.
- These cabinets are just two of a really extensive range.
- Each one carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex



**FREE THE NEW LEWIS RADIO CATALOGUE**

Designed to assist your choice of Cabinet. The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE! Please send your FREE cabinet catalogue.

NAME .....

ADDRESS .....

..... (Dept. P57)  
Capitals please



100 Chase Side, Southgate, London N.14.  
Tel.: Palmer's Green 3733/9666



# BROADWAY ELECTRONICS

**GARRARD 4 SPEED DECKS WITH CARTRIDGE:**  
Autochangers: AT6 Mk II £8.19.6. Autoslim £5.5.0.  
AT60 £10.19.6. 3000. £28.3.0. 2000. £8.19.6. 1000.  
£5.19.6.

AT5—Mono £6.10.0.  
P. & P. all changers 7/6.

## SINGLE PLAYERS:

SP25 with cartridge stereo or mono, £9.19.6. SRP 12.  
£4.5.0. P. & P. 7/6.

## CARTRIDGES:

Stereo: BV26, 25/-, GP83, 15/-, Reuter, STD/2, 17/6.  
Mono: GCS, 15/-, GC2, 15/-, Scotlone, 2T/85, 15/-,  
GP67, 15/-, P. & P. 1/-.

## MICROPHONES:

Xtal Hand Mikes.  
BM3 and 200C 30/-, P. & P. 2/-, Stand for same  
9/6 & 12/6. P. & P. 1/9. ACOS Mike 45, 21/-, ACOS  
Mike 40, 18/6. Dm. Mike DM-301, 22/6. CM21 Xtal,  
12/6. CM20 Xtal, 9/6. Magnetic Hm 63C with remote  
control switch, 15/-, Telephone Pick-up 10/6. P. & P. 1/-.  
Xtal Lapel Mike, 7/6. Guitar Mike, 12/6. P. & P. 6d.

## SPEAKER ENCLOSURES

Tony Corner Cabinet 20 x 10 x 7in. takes 10 x 6in.  
speaker covered in Rexine and Ymar, 45/-, P. & P. 5/-.  
Blake cabinet size 18 x 24 1/2 x 9 1/2in., fabric covered  
£4.10.0. P. & P. 10/-.

Haydon, 16 1/2 x 15 x 7 1/2in. fabric covered suitable for  
12in. speaker, 45/-, P. & P. 7/6.

Haydon Enclosure fitted with 12in. speaker and  
volume control £4.17.6. P. & P. 10/-.

Hi-Fi Bookshelf speaker enclosure foam lined,  
cabinet size 10 1/2 x 5 1/2 x 7 1/2in. Teak finish, £3.0.0.  
P. & P. 3/6.

Woofer for above £3.0.0. P. & P. 2/6. Tweeter 12/6.  
P. & P. 1/6. Condenser for crossover 2/6. Terminals  
2/6 pair, P. & P. 6d.

PLINTH Teak finish to match above Hi-Fi speaker  
size 17 1/2 x 14 x 4in. for Garrard 1000, 2000, 3000,  
AT60, SP25, £2.17.6. P. & P. 4/6.

## SPEAKERS:

Blue Heavy duty Ceramic Magnets 11,000 line, 10in.  
round 10 x 6in. 3 ohm or 15 ohm, 42/6. P. & P. 3/6.  
8in. round 15 or 3 ohm, 38/6. P. & P. 3/6. E.M.I.  
1 1/2 x 8in. 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I.  
Tweeter, 12/6. P. & P. 1/6. R.T.C. 12in. 20 watt 15  
ohm Ceramic magnet, £5.5.0. P. & P. 3/6. 8 x 4in.  
Elliptical 39 ohm 30/-, P. & P. 3/6. All other  
speakers supplied—Goodmans, Bakers, W.B.,  
Wharfedale, Eagle, Tripletone.

## BARGAINS IN TRANSISTORS:

AC127, AF114, 116, 117, 118, 119, OC169, 170,  
171, 172, 200, 202, 203, 204, 5/6.  
OC29, 75, 82, 83, AAZ12, BY33, BCZ11, 3/6. OCT1,  
S1, 3/-, R.F. Packs 1 OC44, 2 OC45 8/6. AF Packs 1  
OC81D, 2 OC81 (Mullard), 8/6. A.F. Pack 1 GET119,  
5/6. GET113, Red Spot, 2/-, OC26, 25, 29, 9/6.  
ORP12 Light Cell, 8/6. Diodes OA81, 2/3. OA91,  
OA95, 1/6. P. & P. on above 6d.

## TRANSISTOR ELECTROLYTICS:

1, 2, 4, 5, 8, 10, 16, 25, 32, 50, 100mfd 15 volt working,  
1/3, P. & P. 6d.  
250 mfd DC 3/-, 500 mfd 12v DC, 3/-, 500 mfd 50v  
DC, 5/-, P. & P. 1/-.

RESISTORS 4 watt, 10%, from 3.3 ohm to 10 meg 5d.  
each. 4/- doz. P. & P. 6d.

**EARPIECES WITH CORD AND 3.5 mm. plug.** 8 ohm  
magnetic, 3/-, 250 ohm, 4/-, 180 ohm with clip, 6/6.  
Xtal 4/-, P. & P. 6d.

**TRANSISTOR SPEAKERS** 8 ohm 2in., 8/6; 3in.  
10/6; 3 1/2in. 12/6. P. & P. 1/-.

**PANEL LIGHTS**, 6v, Red, Blue, Green, Yellow.  
White (use 11input bulbs) 8/- each. P. & P. 6d.

**NEON PANEL LIGHTS** 200-250v, 3/- each. P. & P. 6d.

**PAPER CONDENSERS** for Cross-Over Units 2  
mfd, 2/6. P. & P. 6d.

## ROTARY SWITCHES

2 pole Mains Switch, 3/-, 1 pole 12 way, 2 pole 2 way,  
3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/6 each.  
P. & P. 6d.

**PUSH BUTTON SWITCHES**, 4 button, 2 banks of 6  
S.P.C.O., 1 bank of 5 S.P.C.O. 1 off button, 5/6.  
P. & P. 6d.

**BATTERY CHARGER TRANSFORMERS AND  
RECTIFIERS** 4 amp. GEC Rect., 15/-, Heavy Duty  
Transformer, 25/-, P. & P. 3/6. 1 amp. Westinghouse  
contact cooled rect., 7/6, Transformer 12/6. P. & P. 3/-.  
Large Croc. Clips, 2/6 per pair, P. & P. 6d.

**FERRUX ROD AERIAL** with coils, 8 x 1/2in. 5/6.  
4 x 1/2in. 4/6. P. & P. 9d.

Stockists of ● Eagle Products ● Goodmans ●  
W.B. ● Wharfedale ● Bakers ● Tripletone ●  
Linear, all makes of amplifiers and speakers supplied.  
S.A.E. please. Trade terms to bona fide dealers.

**92 MITCHAM ROAD, Tooting  
BROADWAY, LONDON, S.W.17**

Telephone BALham 3984

Closed all day Wednesday

(four minutes from Tooting Broadway  
Underground Station)

# NEW 1967 Edition WORLD RADIO TV HANDBOOK

32/- Postage 1/-

**TV FAULT FINDING** a Data Pub: 8/6.  
Postage 6d.

**SHORT WAVE LISTENING** by J.  
Vastenhoud. 12/6. Postage 1/-.

**HOW TO TEST ALMOST EVERY-  
THING ELECTRONIC** by J. Darr. 23/-.  
Postage 9d.

**LOUDSPEAKERS & LOUDSPEAKER  
CABINETS** by P. W. Van Der Wal. 15/-.  
Postage 1/-.

**QUESTIONS & ANSWERS ELEC-  
TRONICS** by C. Brown. 8/6. Postage 9d.

**RADIO VALVE DATA** Compiled "WW"  
8th ed. 9/6. Postage 9d.

**QUESTIONS & ANSWERS RADIO &  
TELEVISION** by H. W. Hellyer 8/6.  
Postage 9d.

**UNDERSTANDING TELEVISION** by  
J. R. Davies. 37/6. Postage 2/6.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS

of British and American Technical Books  
19-21 PRAED STREET  
LONDON W.2.  
Phone: PADDington 4185  
Closed Saturday 1 p.m.

## Laboratory Components

**Resistors**  
1W 10% High Stab. Class 1. Low Noise 3/- per Doz.  
**Capacitors**  
Min. Electrolytics, Ass or Single value 9/- per Doz.  
Polystyrene sub-min. 25V. 10% Ass. 6/- per Doz.

**Transistors**  
Matched Output Kit, OC81D+2 OC81 7/6 per set  
Germanium, Ass. PNP, NPN, AF Types 10/6 per doz  
Germanium Low Leakage, RF Types 12/- per doz.  
Type 1020, PNP, Germanium, AF, 50mW 8/- per Doz.  
Type 1021, PNP, Germanium, AF, 200mW 12/6 per Doz.  
Type 1024, PNP, Low Leakage, RF.  
4mc/s Typ.  
OC44, OC45, OC70, OCT1, ACY22, OC81D 2/8 each

**Power Transistors**  
(OC26 7/6) (OC25 8/6) (OC30 10/-)

For complete list of Laboratory Components send S.A.E.  
to:

**LABORATORY EQUIPMENT (ELEC)**  
38 Crawford St., London, W.1

All goods C.W.O. and P.P. 1/6

## AROUND THE WORLD



£2 POST FREE

On your own **TRANSISTOR PORTABLE!**  
★ Boosts Pirate and distant stations!  
★ No Plugs—No Connections! Just place  
Dewtron Wave Trap near radio.

★ Extends Battery life—reduces 'fading'.  
★ Use in car, caravan, without aerial.  
With PP3 battery (life several months).

D.E.W. LTD., Dept. P.W., Ringwood Road,  
FERNDOWN, Dorset.

## SPECIAL OFFERS! YOU CAN BENEFIT

**H.F. STRENS:** Have you found another use for our  
powerful yet miniature high frequency horns?  
Already they are being used in burglar and fire  
alarms, and for all types of equipment where a  
clear penetrating sound is required.  
1.5/4.5V. D.C. only 3/6 each plus 1/- P. & P. per horn.

**AERIAL WIRE:** Pure copper, insulated; still  
available in 76 ft. reels at excellent price of 5/- plus  
1/- P. & P.

## RELAYS:

1. Miniature plug-in with 2 light duty c/o contacts.  
Coil 185 ohms. 4 1/2/18V. D.C. 15/-.
2. Miniature plug-in with 4 light duty c/o contacts.  
Coil 130 ohms. 9/15V. D.C. 18/-.
3. Heavy duty car alarm relay 6/12V. D.C. 3  
heavy duty c/o contacts. 27/6.  
P. & P. on above items, 1/- each.
4. Base for item (2), 3/9 plus 6d. P. & P.

**LOUDSPEAKERS:** We carry a range of speakers to  
suit every application. Typical examples are:

1. Westwell 0.2W.; 8 ohm; 2 1/2in. dia., 7/9.
2. Westwell 0.2W.; 8 ohm; 3in. dia., 9/6.
3. Richard Allen 12in.; 3 ohm with tweeter. 37/6  
plus 3/- P. & P.

**TEST METERS:** ITL-2. A superb buy for the dis-  
cerning engineer with a limited budget. 20K. ohms/  
V.; with all the usual desirable features for testing  
and experimenting. A snip at 69/6 plus 3/- P. & P.

**TEST LEAD KITS:** Complete with plastic case,  
6/9 plus 1/3 P. & P.

**RECORD PLAYER AMPLIFIER:** Powerful single  
valve amplifier (EL84) with metal rectifier. Complete  
with volume and tone controls. 220/250V. A.C.  
only 69/6 plus 3/- P. & P.

And, of course, all Sinclair and Lander products  
always in stock.

Write or call now for our components list



**ROTHWELL ELECTRIC  
SUPPLIES (Glasgow) LTD.**  
54 EGLINGTON STREET  
GLASGOW, G.5. TEL. 041 5041 2904  
Member of the Lander Group

## NEW VALVES!

Guaranteed Set Tested  
24-HOUR SERVICE

1R5	5/6	DL35	4/9	EL33	6/3	PY81	5/-
1S5	3/9	DL92	4/3	EL41	8/8	PY82	4/9
1T4	2/9	DL94	5/-	EL54	8/8	PY83	5/3
834	4/8	DL96	5/11	EY51	6/11	PY800	5/11
874	5/-	DY86	6/3	EY86	5/3	PY801	5/11
5V40	7/6	DY87	6/3	EZ80	6/-	R19	6/6
6F1	6/3	EABCO8	5/6	BZ80	4/3	U25	9/6
6L8	7/3	EAF42	7/6	EZ81	4/6	U26	8/9
6V6G	3/6	EBC41	7/3	GZ82	8/9	U91	10/-
10C2	11/8	EBF80	5/9	KT61	6/3	U801	11/6
10F1	9/6	EBF89	5/9	N78	14/6	U801	15/-
10P13	8/3	EC83	8/3	PC900	8/-	UAF050	5/-
20P2	10/8	ECC82	4/6	PC084	5/8	UAF42	6/11
20P1	8/9	ECC83	4/6	PC089	9/9	UBO41	6/6
20P4	12/6	ECC85	5/3	PC189	8/3	UBF89	5/9
30P5	9/9	ECH35	5/6	PC080	6/3	UC084	7/9
30P4	11/6	ECH42	8/9	PC082	5/9	UC083	8/9
30P19	11/6	ECH81	5/-	PCL82	6/3	UC080	8/-
DAC82	6/9	ECH84	7/9	PCL83	8/3	UCH42	8/6
DAF91	3/9	ECL40	5/9	PCL84	7/3	UCH81	5/9
DAF96	5/11	ECL82	6/-	PCL85	7/9	UCL82	8/9
DF33	7/6	ECL86	7/6	PL86	9/-	UCL53	8/6
DF91	2/9	EPF9	3/6	PL81	6/3	UF41	7/9
DF96	5/11	EP41	5/9	PL82	6/9	UF89	5/6
DK32	7/-	EP80	4/3	PL83	5/11	UL41	7/9
DK91	5/6	EP85	5/-	PL84	6/-	UL54	5/3
DK96	6/3	EP86	6/-	PY32	8/3	UY41	4/9
DL33	6/6	EP89	4/9	PY33	8/3	UY35	4/9

Postage on 1 valve 9d. extra. On 2 valves or more,  
postage 6d. per valve extra. Any parcel insured against  
damage in transit 6d. extra. Office address, no callers.

## GERALD BERNARD

83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON N.16

FANTASTIC OFFER!!! Radiogram  
Chassis £8 10s. (. p. & p. 10/-). AM/  
FM 4 wave push keys Magic Eye.

Size 18in. x 9in. x 7in. approx.  
HARRISONS, 253 Camden High  
Street, London, N.W.1.

**Make sure of  
No 2**   
**OF THIS GREAT NEW 'PRACTICAL'**



Practical Decorating & Building  
**CARPORT/GARAGE** PRICE 5/-

PRESENTED FREE  
PRACTICAL DECORATING  
& BUILDING  
APRIL 1964

**PRACTICAL  
Decorating & Building**

**FREE!  
INSIDE**

**2** DOUBLE-SIDED  
DESIGN  
PLANS  
FOR BUILDING

**1** Carport/  
Garage

**2** Bedroom  
Floor-to-Ceiling  
Storage  
Unit

**EXTRA!**  
8-Page Supplement  
ALL ABOUT  
BRICKS & MORTAR

*Other Outstanding Features:-*  
**SELF-BUILD 4-BEDROOM HOUSE  
PUTTING IN A RING MAIN  
DECORATING A STEAMY KITCHEN  
RIDDING A ROOF OF PESTS**

**PRACTICAL  
Decorating & Building**

APRIL ISSUE OUT NOW 2/6


**NEW - ENLARGED - IMPROVED  
EXPERIMENTER'S  
PRINTED CIRCUIT KIT**

**BUILD 36 INTERESTING PROJECTS** on a **PRINTED CIRCUIT CHASSIS** with **PARTS** and **TRANSISTORS** from your **SPARES BOX**

**CONTENTS:** (1) 2 Copper Laminate Boards 4½" x 2½". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for building.

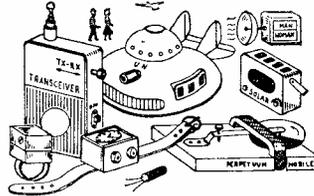**36 TRANSISTORISED PROJECTS**

A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 6 new circuits.



**EXPERIMENTER'S  
PRINTED CIRCUIT KIT  
8/6**

Postage & Pack. 1/6 (UK)  
Commonwealth:  
**SURFACE MAIL 2/-**  
**AIR MAIL 8/-**  
Australia, New Zealand  
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRIFLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World.


**3 SUBMINIATURE RADIO RECEIVERS**

Based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62" x .95" x .25". (11) Wristwatch Radio 1.15" x .80" x .55". (12) Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Seismic Car Alarm. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone - "Photophone".

**PHOTOELECTRIC KIT**

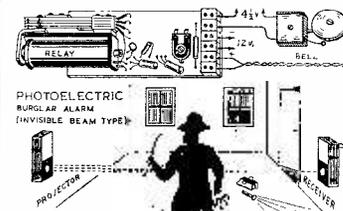**BUILD 12 EXCITING PHOTOELECTRIC DEVICES**

**CONTENTS:** 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Sensitive Photocell, Latching Relay, 2 Transistors, Condenser, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



**PHOTOELECTRIC KIT  
39/6**

Postage & Pack. 2/6 (UK)  
Commonwealth:  
**SURFACE MAIL 3/6**  
**AIR MAIL £1.0.0**

Australia, New Zealand,  
S. Africa, Canada & U.S.A.  
Also Essential Data Circuits  
and Plans for Building

**12 PHOTOELECTRIC PROJECTS.** (1) Steady-Light Photo-Switch/Alarm. (2) Modulated-Light Alarm. (3) Long-Range Stray-light Alarm. (4) Relay-Less Alarm. (5) Warbling-Tone Alarm. (6) Closed-Loop Alarm. (7) Projector Lamp Stabiliser. (8) Electronic Projector Modulator. (9) Mains Power Supply. (10) Car Parking Lamp Switch. (11) Automatic Headlamp Dipper. (12) Super-Sensitive Alarm.

**OPTICAL KIT** Everything needed (except plywood) for building: 1, Invisible-Beam Projector and 1 Photocell Receiver (as illustrated).

**CONTENTS:** 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (UK).

**LONG RANGE OPTICAL KIT 29/6 p.p. 1/6**


Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 50 Radio, Electronic and Photoelectric Projects. Assembled.

**EXPERIMENTAL ELECTRONIC KITS**

**YORK ELECTRICS, 333 York Rd., London S.W.11**
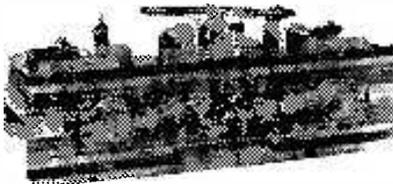
# 1/2 PRICE SPECIAL RADIO CHASSIS OFFERS

HI-FI CONTINENTAL  
STEREOPHONIC RADIOGRAM CHASSIS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Comes complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed automatic record changer. Complete 29½ gns. (Units available separately if required. Chassis only, 21 gns.)  
Special terms available of £10.6.6 deposit followed by 18 monthly payments of £1.7.3 (total H.P. of £34.17.0)+17/6 P. & P. Send £11.4.0 now.

## IMPERIAL HI-FI STEREOPHONIC RADIOGRAM CHASSIS



The Imperial Stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons, controlling mono/stereo selection, GramLong-Medium-Short-FM-ON/OFF. The unit comes complete with two 10" elliptical loudspeakers plus a mono/stereo 4 speed automatic record changer. Complete £41.9.6.  
Chassis only, 29½ gns.

Special terms available of £13.16.6 deposit followed by 24 monthly payments of £1.8.10 (total H.P. £48.8.6)+17/6 P. & P. Send £14.14.0 now.

## EMPRESS HI-FI AM/FM STEREOPHONIC CHASSIS



This most advanced radiogram chassis with automatic push button selection covers short, medium and long wavebands plus V.H.F./F.M. Offered complete with 2 10 x 6 speakers 4 speed Stereo/Mono autochanger only £35.19.6. Chassis only, 25½ gns. Special terms available of £12 deposit followed by 18 monthly payments of £1.11.7. (total H.P. £40.8.6)+17/6 P. & P. Send £12.17.6 now.

All Lewis Radio equipment including valves are fully guaranteed for one year free of charge. Send your cheque or P.O. today while stocks last to Dept. P.57.

**LEWIS radio**

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE  
LONDON, N.14. Telephone: PAL 3733/9666

## PADGETTS RADIO STORE

OLD TOWN HALL,  
LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

**Special Offer.** 19 Sets, Mark 3, in good clean condition. Parts removed. "B" set. 807 valve. TX section made U.S. Receiver bench tested. All that is required is a power pack. Price 35/- Carriage 10/-.

19 Sets in fair condition as above and also removed is the meter and Relay, 10/- Carriage 10/-.

46 Sets. New condition. Less Send/Receive switch, Crystal and Collis, 12/6 post paid.

46 Set Whip Aerial Sections. Nine for 2/- plus P.P. 2/6.

**EX RAF Wave Meter.** Type W1649. All complete with Slow Motion drive and six valves. Housed in wooden box. Used 17/6. New 30/- plus carriage B.R.S. 10/-.

**Silicon Rectifiers.** Top grade. Half amp 800 P.I.V., 3/- post paid; Half amp 400 P.I.V., 2/6 post paid; 5 amp 800 P.I.V., 5/- post paid; 5 amp 400 P.I.V., 4/- post paid; 5 amp 200 P.I.V., 2/6 post paid.

### VALVE LIST

Ex. Equipment, 3 months' guarantee.			
Single Valves. Post 7d.			
EF80	1/6	PCL82	4/-
ECL80	1/6	PZ30	5/-
EP91	9d.	PY81	1/6
EB91	9d.	PY82	1/6
EBF80	3/-	PL81	4/-
ECC81	3/-	PL36	5/-
ECC82	3/-	PY33	5/-
ECC83	4/-	6B8	1/6
EY86	5/-	6R1	1/-
EF50	1/-	6F14	5/-
6K25	5/-	10C2	5/-
6U4	5/-	10P13	2/6
6P25	5/-	10P14	5/-
KT36	5/-	20D1	3/-
PCF80	2/-	20L1	5/-
PCC84	2/-	20P1	4/-
		20P4	8/6
		U329	5/-
		U801	8/6
		U301	5/-
		U191	5/-
		U281	5/-
		U282	5/-
		U25	5/-
		ARP12	1/6
		EL38	5/-
		5U49	4/-
		6K7	1/9
		6V6	1/9
		185BT	8/6
		807	5/-

Top Grade Diodes, 3/6 doz. post paid.

Jap Earpiece. 3 or 5 m.m. plug. 1/11 post paid.

New 12in. Speaker with built-in tweeter. 3 or 15 ohm coil. 28/6 post paid.

Reclaimed Tubes. Six months guarantee. 17in., 30/-; 14in., 17/- plus carriage 10/-. All types.

Motors ex Washing Machines. 1 h.p. 1,400 revs. 230 volt, 26/- Carriage 10/-.

## ELECTRONICS GALORE! IN THE NEW dca CATALOGUE

THE CONVENIENT WAY TO SHOP  
FOR ALL YOUR ELECTRONIC  
NEEDS.

EVERYTHING FROM SINGLE COM-  
PONENTS TO COMPLETE EQUIP-  
MENT ALL AT BEST VALUE PRICES.

SEND 1/6d. NOW FOR YOUR  
COPY TO:—

Dept. PW/5

**dca ELECTRONICS LIMITED**  
28 UXBRIDGE RD., EALING, W.5

## NEW RANGE U.H.F. AERIALS FOR BBC 2 (625) line transmissions

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.  
**Loft Mounting Arrays,** 7 element, 35/-, 11 element, 42/6. 14 element, 50/-, 18 element, 57/6. **Wall Mounting with Cranked Arm,** 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. **Roof Mounting with 2in. clamp,** 7 element, 42/6; 11 element, 55/-; 14 element, 62/-; 18 element, 70/-, **Chimney Mounting Arrays, Complete,** 7 element, 72/6; 11 element, 80/-; 14 element, 87/6; 18 element, 95/-. Complete assembly instructions with every unit.  
**Low Loss Cable, 1/6 yd. U.H.F. Preamps.** from 75/-. State clearly channel number required on all orders.

## BBC · ITV · F.M. AERIALS



**BBC (Band 1).** Telescopic loft, 21/-, External S/D, 30/-, "H" £210.0.  
**ITV (Band 3).** 3 element loft array, 25/-, 5 element, 35/-. Wall mounting, 3 element, 35/-, 5 element, 45/-.

**Combined BBC/ITV.** Loft 1+3, 41/3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3.

**VHF transistor pre-amps,** 75/-.

**F.M. (Band 2).** Loft S/D, 12/6, "H" 30/-, 3 element, 52/6. External units available. Co-ax cable, 8d. yd. Co-ax plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & P. 5/-. Send 6d. stamps for illustrated lists.

Quotations for special arrays available on request

**K.V.A. ELECTRONICS (Dept. P.W.)**  
27 Central Parade, New Addington  
Surrey CRO OJB  
LODGE HILL 2266

## 4-STATION INTERCOM



£6/9/6

Solve your communication problems with this new 4-Station Transistor Intercom (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9v battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft. and other accessories. P. & P. 6/6.

## INTERCOM/BABY ALARM



Usually ~~£50.00~~  
Our Price ONLY

49/6

Modernise business or home with this new two-way Portable Transistor Intercom. Consisting of Master and Sub, in strong plastic cabinets, with chromium stands. Designed as a two-way instant communication system. Call/talk/listen from Master to Sub and Sub to Master. Operates on one 9v battery. Complete with 60ft wire and battery. P. & P. 2/6.

## Transistor TELEPHONE AMPLIFIER



Usually ~~£50.00~~  
Our Price ONLY

55/-

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. Indispensable in office/home. On/off switch. Volume Control. Operates on one 9v battery. P. & P. 2/6. Battery 2/6 extra. Full price refunded if returned in 7 days.


**WEST LONDON DIRECT SUPPLIES (PW5)**  
169 KENSINGTON HIGH STREET, LONDON, W.8.




(14)



(12)

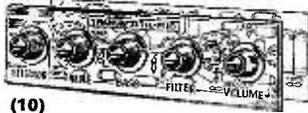

(10)

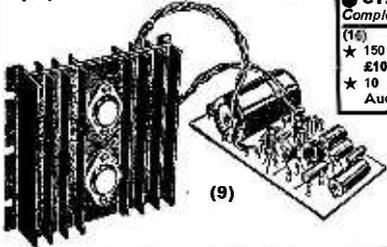

(9)

### HENRY'S RADIO LTD.

303 EDGWARE RD., LONDON, W.2  
PADdington 1008/9 (STD 01-723-1008)  
Open Mon. to Sat. 9-6. Thurs. 1 p.m.  
Open all day Saturday

## 12 AND 20 WATT MONO AND STEREO TRANSISTOR AMPLIFIERS

(8) **POWER AMPLIFIERS.** 12 watts RMS output. 100mV input. 30 c/s to 20 kc/s -1dB. 6-transistor Push-pull. Panel size 4 x 2½ x 1in. H/S 4 x 4in. (leaflet on request). MPA10/3 3-5 ohm spkr. £4.10.0, p.p. 2/6. MPA10/15 8-16 ohm spkr. £5.5.0, p.p. 2/6. (Mains unit 1 or 2 amplifiers, 59/6, p.p. 2/6)

**The Finest High Fidelity at Unbeatable Prices**

### 25 WATT AMPLIFIER

8-Transistor design. Push-pull output for 7½ to 16 ohm speaker. 150mV input. 30c/s to 20kc/s-1dB. For use with valve or transistor pre-amplifiers as item (10) above. **PRICE LISTED £7.19.6 P.P. 3/-** (Mains unit 79/6, p.p. 2/6)

### MULTIMETERS SCOPE

PT34 1KV 39/6 EP30k 30KV £6.10.0  
TP10 2KV 75/- EP50k 50KV £9.19.6  
TT1-2 20KV 69/6 500 30KV £8.17.0  
TP55 20kV £5.19.6 EP100k 100KV £10.10.0  
● **CT52 Scopes £22.10.0, P.P. 10/-.**

Complete range of test equipment in stock

### (16) NOMBREX TEST UNITS

★ 150 kc/s-350 mc/s RF Generator £10.10.0. All Transistor.  
★ 10 c/s-100 kc/s Transistor. £16.19.6 Audio Generator.

### (15) GARRARD BATTERY 2-SPEED TAPE DECK

Brand New with R/P head. erase/osc. head, tape cassette Specifications and osc. circuits. 2 speed 2-track 9 volt operated. List Price 13 gns.

**PRICE £8.19.6 P. & P. 3/6**

### COMPONENTS AND EQUIPMENT.

The largest range in the country. 8/6 buys 200-page catalogue with discount vouchers (see back page)

(10) **PREAMPLIFIERS.** 8 input selector. Treble, bass, volume, filter controls. 1½mV to 100mV inputs. Battery operated or from Mains Unit. Output up to 150mV

● **DETAILED BOOKLET ON REQUEST**  
MP2 Mono 9½ x 2½ x 2in. £5.10.0, p.p. 2/6 (grey and gold front panel 8/6).  
SP4 Mono/Stereo, 9 x 3½ x 1½in. £10.19.6, p.p. 3/6 (front panel plate 12/6)  
● **ALL UNITS BUILT AND TESTED**

### (12) MW/LW QUALITY

#### TRANSISTOR RADIO TUNER

Fully tunable superhet with excellent sensitivity and selectivity. Output up to ½ volt peak. Complete with front panel, etc. 9 volt operated. For use with any amplifier or tape recorder.

**TOTAL COST £3.19.6 P.P. 2/6 TO BUILD**

### (14) VHF FM TUNER

Supplied as 2 Preassembled Panels, plus metal work Superhet design. 88-108 Mc/s. 9 volt operated. 6 Mullard Transistors. Total cost to assemble £12.17.6, p.p. 2/6

### STABILISED POWER SUPPLY

Two outputs. 3.6 volt and 9.6 volt up to 250mA each. Transistorised and Zener stabilised. 110 to 250 volt mains input in case with leads. **PRICE 67/6, p.p. 2/6.**

### (17) 5 WATT AMPLIFIER

6-Transistor Push-pull, 3 ohms. 6mV into 1K. 12-18V supply, 2½ x 2 x 1½in.

**BUILT AND TESTED 69/6 P.P. 2/-**  
1½ watt version 59/6.


Matching Preamplifier, 6 inputs, treble/bass/selector/volume controls. 6-10mV o/put. 9-18V supply. 79/6, p.p. 2/-.  
For use with any Transistor Amplifier

(18) **FMT41 FM TUNER.** 6-transistor 3 diode design. Com- pletely built and tested **£8.10.0 P.P. 2/-**

(19) **AMT31, Med. Wave Tuner** Built ready to use. 79/6.



(16)

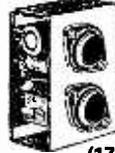

(17)



(15)



(14)

**SEE BACK COVER FOR MORE ITEMS OF INTEREST**

## BUILD YOUR CIRCUITS ON VEROBOARD

— the Universal Wiring Board — obtainable from your local Retailer

Retail enquiries to:

**NORMAN ROSE (ELECTRICAL) LTD.**  
8 ST. CHAD'S PLACE, GRAYS INN ROAD, LONDON, W.C.1

Technical enquiries to:

**VERO ELECTRONICS LTD.,** Chandler's Ford, Hampshire

## The most accurate pocket size CALCULATOR in the world

The 66 inch OTIS KING scales give you extra accuracy. Write today for free booklet, or send 75/- for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

**CARBIC LTD.** (Dept. PW1)  
54 Dundonald Road, London, S.W.19



## "GLOBE-KING"

2-4 Metres 10-180 Metres

ALL TRANSISTOR

AMATEUR VHF and SHORT-WAVE KITS

Send stamped addressed envelope for free copy interesting literature describing latest products: Unique VHF kit model SR2/P. 70-150 Mcs., 69/6 p.p. 4/-. Short-Wave kit model TR2. 79/6 p.p. 5/- "Mini-Amp" self-contained, cabinet size a mere 4½ x 3½ x 2½, 139/6 p.p. 4/-. Despatch: Within 21 days from receipt of order. Overseas enthusiasts send local stamp for literature and special postal charges for your particular country: Sole makers "Globe-King" (Regd.) products: Tel.: 24884; Est. 1943.

**JOHNSONS (RADIO)**  
St. Martins Gate, Worcester

## A.R.R.L. RADIO AMATEURS HANDBOOK 1967

New Edition 40/-. Postage 4/6


World Radio and TV Handbook 1967 by Johansen. 32/-. P. & P. 1/-.  
Transistor Specs. and Subs. Handbook 1967, ed. by Techpress 21/-. P. & P. 1/-.  
TV Fault Finding. New ed. by Data. 3/6. P. & P. 10d.  
Radio Valve Data by Wireless World. new 8th ed. 9/6. P. & P. 1/-.  
Guide to Broadcasting Stations. New ed. by Wireless World. 6/-. P. & P. 6d.  
How to Listen to the World. New 1967 ed. by Johansen. 26/-. P. & P. 1/-.  
Having Fun with Transistors by Buckwalter. 21/-. P. & P. 1/-.

Where possible 24-hour service guaranteed.

## UNIVERSAL BOOK CO.

12 LITTLE NEWPORT STREET  
LONDON, W.C.2

(Leicester Square Tube Station)

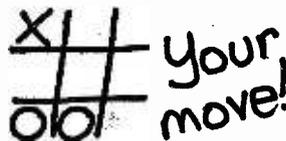

You must put your X to prevent the machine completing that row of O's. Then the machine will place its next O bang in the centre. Which leaves you well and truly beaten. Try it and see! This is just one of the ways our machine will win. Circuit, wiring diagram, instructions, 3/6d. Other circuits available are:—

Simple Analogue Computers.....4/6  
Simple Binary Adder/Subtractor.....3/6

**PLANET INSTRUMENT CO.**  
25 (W) DOMINION AVENUE, LEEDS 7

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel. PARK 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling

MINIMUM CHARGE 2/- No C.O.D. orders accepted

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel. LANGHAM 8403  
Open all day Saturday

0A9	6/-	6A8E	10/-	6F8G	5/-	10L1	7/6
0A3	10/-	6A85	5/-	6F81	6/-	10T13	15/-
0B2	6/-	6A85	3/-	6F12	4/-	10P14	15/-
0C3	6/-	6A86	4/-	6F13	6/6	11D3	7/-
0D3	6/-	6A87	10/-	6F14	15/-	11D5	7/-
0Z4A	5/-	6A94	5/-	6F15	11/-	12AC6	8/-
1A3	7/-	6A95	5/6	6F17	8/-	12AD6	9/-
1A5GT	5/-	6A85	6/-	6F18	7/6	12AE6	7/6
1A7	8/-	6A86	6/-	6F23	10/-	12AL5	6/-
1B3GT	8/-	6A85	17/6	6F24	12/-	12AQ5	7/-
1C5GT	5/-	6A85	5/-	6F25	12/-	12AT6	5/-
1D6	8/-	6A86	6/-	6F28	10/6	12AT7	7/-
1DSGT	6/-	6A79	15/-	6F28	6/-	12AT6	6/-
1G4GT	3/-	6A76	4/6	6F3	2/-	12AU7	5/6
1G6GT	3/-	6A76	5/6	6F4	9/-	12AV6	5/6
1H5GT	7/-	6A85	9/-	6F3	3/6	12AV7	8/-
1L4	2/6	6AV9GTA	6/7G	6F5	10/-	12AW6	20/-
1N3GT	3/-	6AV6	5/-	6K6G	6/-	12AX7	6/-
1R4	6/-	6AW8A	12/6	6K7GT	5/-	12AY7	10/-
1R5	6/-	6B4G	17/6	6K8	8/-	12BA6	6/-
1S4	5/6	6B8	7/-	6K8G	4/-	12BE6	5/6
1S5	4/6	6B8G	2/6	6L6GG	7/6	12BH7	6/-
1T4	3/-	6BA5	4/6	6L7	9/-	12BY7	10/-
1T5GT	6/-	6B7	15/-	6L17	9/-	12C7	6/-
1U5	6/-	6B86	4/6	6L18	6/-	12E1	20/-
1V5	6/-	6B87	6/-	6L20	5/-	12E5	8/-
1V2	10/-	6B87	15/-	6N7GT	7/-	12E7GT	7/-
1X2B	7/-	6B86G	18/-	6P25	12/-	12E8	8/-
2C26A	7/-	6B87	7/6	6P28	12/6	12G7G	4/-
2C34	7/6	6B87	7/6	6B8G	15/-	12H7	4/-
2C31	10/-	6B87	7/6	6B8G	15/-	12H7	4/-
2C34	12/-	6B87	7/6	6B8G	15/-	12H7	4/-
2D21	6/-	6B87	7/6	6B8G	15/-	12H7	4/-
2E26	22/6	6B86	7/6	6B8G	15/-	12H7	4/-
3A4	4/-	6B87	7/6	6B8G	15/-	12H7	4/-
3A5	7/-	6B87	11/-	6B8G	15/-	12H7	4/-
3A7	6/6	6B85	5/-	6B8G	15/-	12H7	4/-
3B7	5/-	6B87	17/-	6B8G	15/-	12H7	4/-
3B8	30/-	6B86	7/6	6B8G	15/-	12H7	4/-
3D8	4/-	6B87	10/-	6B8G	15/-	12H7	4/-
3E29	40/-	6B86	6/-	6B8G	15/-	12H7	4/-
3G4	7/-	6B87	11/-	6B8G	15/-	12H7	4/-
3Q5GT	6/6	6C4	4/-	6F8	8/6	20P3	12/-
3R4	5/-	6C5G1	6/-	6F8	7/6	20P4	13/-
3V4	6/-	6C8	4/-	6F8A	9/6	20P5	11/-
4F8A	4/-	6C8	15/-	6F8GT	6/6	20P6	12/-
4TSP	8/-	6C81	12/-	6X4	4/-	25Z4G	8/-
4X18A	5/-	6C86	5/-	6X5GT	6/6	25Z5	8/-
5R4Y	100/-	6C86GA17	6/6	6Y6G	9/-	25Z6GT	11/-
5U5E6	6/6	6C86	10/-	7B8	11/-	25D7	7/-
5U8	3/-	6C86	6/-	7B7	7/-	30A5	7/-
5V4G	6/6	6C86	11/-	7B8	8/-	30C1	6/6
5Y3GT	5/-	6C87	12/-	7C5	11/6	30C15	11/6
5Z3	7/6	6C87	11/-	7C7	5/-	30C18	11/6
5Z4G	7/6	6C87	11/-	7H7	8/-	30P5	10/-
6P80L2	8/6	6D5	8/-	787	22/-	30P12	14/-
6A8	8/-	6DK6	8/-	7Y4	8/-	30P13	6/-
6A84	6/6	6DQ8G	11/-	7Z4	8/-	30P14	13/-
6A87	4/-	6D8A	15/-	9B7	6/6	30L1	5/6
6AC7	4/-	6E5GT	8/-	10C2	13/-	30L15	15/-
6A7	10/-	6E8	11/-	10D1	14/-	30L17	15/-
6A7A	10/-	6E1	14/-	10F1	9/-	30P12	9/-
6A7F6	11/-	6E4	30/-	10F3	8/-	30P16	7/-
6A75	2/6	6E5G	3/-	10P9	10/-	30P16	6/6
6A7G	5/-	6E6G	5/-	10F18	9/-	30P19	13/-

## First Quality Fully Guaranteed



## ELECTRONIC VALVES

30P11	15/-	4318C	20/-	DK40	11/-	ECC88	8/-
30P113	15/-	5651	7/6	DK91	6/-	ECC81	3/6
30P114	15/-	5654	8/-	DK92	8/-	ECC189	11/-
30P115	15/-	5070	10/-	DK96	7/-	ECC804	10/-
35A5	10/-	3718	10/-	DL33	6/6	ECC80	13/6
35B6	12/-	5749	10/-	DL35	5/-	ECF80	7/-
35C5	6/6	5751	12/-	DL66	20/-	ECF92	7/6
35D5	12/-	5753	10/-	DL65	10/-	ECF83	6/6
35L6GT	6/-	5814A	10/-	DL69	12/6	ECF86	9/6
35P1	6/6	5823	5/-	DL91	5/-	ECH35	11/-
35Z3	10/-	6060	5/-	DL92	5/-	ECH42	9/-
35Z4G	4/-	6080	25/-	DL93	4/-	ECH51	5/6
35Z4GT	8/6	6146	25/-	DL94	6/-	ECH83	7/6
35Z5GT	5/6	6195	32/-	DL95	7/-	ECH84	9/-
35Z6	6/-	6298	60/-	DL96	7/-	ECL80	7/-
43U1	8/-	6380	10/-	DL98	30/-	ECL82	6/6
50A5	12/-	6939	45/-	DM70	5/6	ECL81	7/6
50B5	6/6	7551	30/-	DY30	8/-	ECL82	6/6
50C5	6/-	7588	22/6	DY86	6/6	ECL83	9/6
50CD6G27G	6/-	7895	22/6	EY80	8/-	ECL84	12/-
50L6GT	6/-	9002	5/6	E80	27/6	ECL85	11/6
52K1	7/-	9028	7/-	E82F	2/6	ECL86	9/-
55C0	30/-	9005	15/-	E83F	2/6	ECF56	5/-
55C6	45/-	A1820	20/-	E83CC	12/6	EF37A	8/-
55C8	13/-	AC/HL/DD	9/6	E90CC	10/-	EF39	30/-
58G	6/6	AC/HL	8/-	E92CC	7/6	EF40	9/-
58L	12/-	ADD	10/-	E180F	17/6	EF41	8/6
58L25	25/-	AC/TH1	8/-	E180F	17/6	EF42	11/-
58A3	7/6	AC/VP215	15/-	E180F	17/6	EF52	8/-
90A4G	46/-	AR	6/-	E180F	17/6	EF54	6/-
90A5	46/-	ARF12	3/6	E180F	17/6	EF55	6/6
90C1	12/-	AV6	6/-	E180F	17/6	EF56	6/6
90C2	25/-	AZ11	6/-	E180F	17/6	EF59	5/6
90C5	25/-	AZ12	9/-	E180F	17/6	EF91	4/-
11N7	30/-	AZ13	9/-	E180F	17/6	EF92	2/6
160B2	10/-	AZ14	9/-	E180F	17/6	EF93	4/6
150B3	5/-	AZ15	7/-	E180F	17/6	EF94	5/6
211	80/-	CB131	15/-	E180F	17/6	EF95	6/6
807	9/-	DA0	4/-	E180F	17/6	EF96	2/6
815	35/-	DAC2	7/6	E180F	17/6	EF98	10/-
832	20/-	DAF1	4/6	E180F	17/6	EF183	6/6
837	17/6	DAF2	8/-	E180F	17/6	EF184	6/6
866A	15/-	DAF3	8/-	E180F	17/6	EF189	8/-
872A	40/-	DAF5	6/6	E180F	17/6	EF204	21/-
884	15/-	DC08	7/-	E180F	17/6	EF811	12/-
955	3/-	DC09	7/-	E180F	17/6	EF812	10/-
956	2/-	DF3	8/-	E180F	17/6	EF813	10/-
957	5/-	DF4	5/-	E180F	17/6	EF814	12/-
958	15/-	DF5	8/-	E180F	17/6	EF815	12/-
959	8/-	DF6	5/-	E180F	17/6	EF816	12/-
991	7/-	DF7	6/-	E180F	17/6	EF817	12/-
1287	20/-	DH63	6/-	E180F	17/6	EL33	12/6
1290	12/-	DK32	8/-	E180F	17/6	EL34	9/6

EL35	5/-	KT32	6/6	PL34	6/6	U78	4/-
EL36	8/6	KT36	17/6	PL302	13/-	U191	11/-
EL38	17/6	KT41	7/6	PL500	13/6	U193	7/6
EL41	8/6	KT44	7/6	PL604	15/-	U281	6/-
EL42	7/6	KT45	15/-	PT15	15/-	U281	12/-
EL81	9/-	KT66	16/-	PX4	20/-	U282	12/-
EL82	8/-	KT67	45/-	PX25	15/-	U301	11/-
EL83	7/-	KT76	8/-	PY32	8/6	U403	7/-
EL84	4/6	KT88	23/-	PY33	8/6	U404	9/-
EL85	7/6	LP2	7/-	PY90	4/6	U801	17/-
EL86	8/-	MH4	5/-	PY81	6/-	UABC80	5/3
EL90	5/6	MH41	9/-	PY82	5/6	UAF42	9/-
EL91	2/6	MH4	5/-	PY83	6/-	UB41	10/-
EL95	8/-	MIA	8/-	PY85	8/-	UBC41	8/-
EL96	8/-	MS/PEN	8/-	PY201	11/-	UBC81	8/-
EL98	8/-	MS/PEN	7/-	PY800	6/-	UBF80	6/6
EL99	8/-	MS/PEN	7/-	PY801	6/-	UBF89	7/-
EL99	8/-	MS/PEN	7/-	PZ30	8/6	UBL21	10/-
EL99	8/-	MS/PEN	7/-	PZ21	5/-	UC92	6/-
EL99	8/-	MS/PEN	7/-	PZ25	5/-	UC94	8/-
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC95	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC96	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC97	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC98	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC99	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC100	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC101	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC102	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC103	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC104	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC105	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC106	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC107	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC108	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC109	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC110	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC111	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC112	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC113	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC114	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC115	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC116	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC117	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC118	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC119	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC120	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC121	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC122	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC123	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC124	8/6
EL99	8/-	MS/PEN	7/-	PZ30	5/-	UC125	8/6
EL99	8/-	MS					

The following blueprints are available from stock. Descriptive text is not available but the date of issue is shown for each blueprint. Send, preferably, a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

The Strand Amplifier ..	.. }	(Oct. 1962)	5/-	The Celeste 7-transistor Portable Radio ..	.. }	(June 1963)	5/-
The PW Signal Generator ..	.. }			The Spinette Record Player ..	.. }		
The Berkeley Loudspeaker Enclosure ..	.. }	(Dec. 1962)	5/-	Transistor Radio Mains Unit ..	.. }	(June 1964)	5/-
The Luxembourg Tuner ..	.. }			7 Mc/s Transceiver ..	.. }		
The PW Troubadour ..	.. }	(June 1962)	7/6	The Citizen (December 1961) ..	.. }		5/-
The PW Everest Tuner ..	.. }			The Mini-amp (November 1961) ..	.. }		5/-
The PW Britannic Two ..	.. }	(May 1962)	6/-	The Beginner's Short Wave Superhet (Dec. 1964)			5/-
The PW Mercury Six ..	.. }			The Empire 7 Three-band Receiver (May 1965) ..			5/-
Beginner's Short Wave Two S.W. Listener's Guide ..	.. }	(Nov. 1963)	5/-	Electronic Hawaiian Guitar (June 1965) ..	.. }		5/-
				Progressive SW Superhet (February 1966) ..	.. }		5/-
PW "Sixteen" Multirange Meter ..	.. }	(Jan. 1964)	5/-	Beginners' 5-Band Receiver ..	.. }	(Dec. 1966)	5/-
Test Meter Applications Chart ..	.. }			Home Intercom Unit ..	.. }		

★ PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL RADIO, TV OR AUDIO EQUIPMENT. ★

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

**QUERY COUPON**

This coupon is available until 5th May, 1967 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, MAY 1967










# 1967 CATALOGUE 200 PAGES PLUS!

COMPLETELY NEW EDITION — HUNDREDS OF NEW LINES REPRESENTS THE FINEST VALUE FOR THE PROFESSIONAL AND AMATEUR

● Contains the largest and most comprehensive range of components and equipment available. Over 5,000 stock lines with more data, more information and illustrations. Hundreds of bargain lines. You cannot afford to be without a copy of this catalogue. Supersedes all previous editions. PRICE 7/6, p.p. 1/-

● 5 FREE VOUCHERS  
Total value 10/- for use on purchases. Pay for catalogue after use.

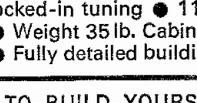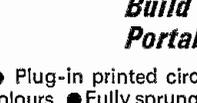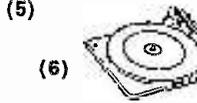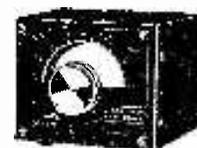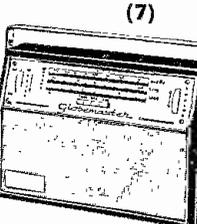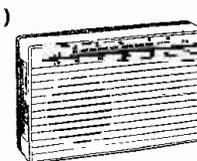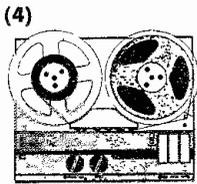● Unbeatable value — 200 packed pages — 10/- value discount vouchers ●



**MARRIOT TAPE HEADS**  
1/2 Track R/RP/3 Med z. 7/6. R/RP/1 High x, 8/-, R/RP/1 High z + R/E/1 erase on block, 19/6. 1/2 Track L/RPS/12 High z 15/-, L/RPS/7 Med z 19/6. L/ES/9 erase, 12/6. Also HR-RP single track Rec/Play Med z 6/6.

**DEAC RECHARGEABLE BATTERY**  
● 9.6 volt 225mA/H. 20/- p.p. 1/6  
**DEAC CHARGER**  
To charge 3.6 volt and 9.6 volt packs. Fully mains isolated **45/-** P.P. in moulded case. 2/-

(4) **BUILD A QUALITY 2 OR 4 TRACK TAPE RECORDER**  
3-speed version using '368' decks  
● TWO-TRACK. Deck £10.10.0. Martin Amplifier. £14.19.6. Cabinet and speaker 7 gns. Complete kits with FREE Tin. 1200ft. tape, spare spool **27 gns.** P.P. 15/- Today's Value £45  
● FOUR-TRACK. Deck £13.10.0. Martin Amplifier £15.19.6. Cabinet and speaker 7 gns. Complete kits with FREE Tin. 1200ft. tape, spare spool. **30 gns.** P.P. 15/- Today's Value £50.

(6) **GARRARD DECKS—BRAND NEW FULLY GUARANTEED**

1000 mono	£5 19 6	SP25 stereo	£10 19 6	401 less cart./arm	£27 10 0
AT5 mono	£8 9 6	SP25 Deram	£13 19 6	AT6 mono Mk. II	£8 19 6
2000 mono	£8 9 6	AT80 less cart.	£10 19 6	AT6 stereo Mk. II	£9 10 0
2000 stereo	£8 19 6	AT80 mono	£11 10 0	AT6 Deram	£11 19 0
3000 1 m stereo	£7 10 0	AT60 stereo	£11 19 6	Decadec Mk. II	£17 17 0
SP25 less cart.	£9 19 6	AT60 Deram	£14 19 6	AT7 less cart.	£17 17 0
SP25 mono	£10 10 0	LAB30 less cart.	£25 0 0	(P. and P. 5/- any type)	

All other makes of decks and cartridge in stock. List on request

(7) **GLOBEMASTER MW/LW/SW PORTABLE RADIO TO BUILD**  
Full 3-waveband tuning. Pushbutton wave-change. Superhet printed circuit design. Black-chromed cabinet 11 x 7 1/2 x 3 1/2 in. (SW 17-50 metres). Ear/Record sockets. 1 watt Push/Pull output. 6 Mullard Transistors. Booklet on request.  
**TOTAL COST TO BUILD £7.19.6** P.P. 3/6

**NEW!** **CAR MONO/STEREO AND MONO TAPE PLAYERS—TERRIFIC QUALITY**  
12 volt pos. or neg. earth operated. Uses Musicassettes. Either your own recording/ or EMI/Philips prerecorded tapes. Fits any car. Full range of controls bass/treble/ volume. Provides 30 mins. from one tape. Supplied complete with speakers, fixing kit, instructions and 50 min. prerecorded tape.  
Prices: Mono **26 gns.** Mono/Stereo **32 gns.** Leaflet on request. British Made.

Complete range of hi-fi equipment in stock. Demonstration room open. Latest stock list on request. Special prices.

**SCR'S (THYRISTORS)**  
● 1 AMP SERIES WIRE LEADS  
50 PIV .. 7/6 100 PIV .. 7/6  
200 PIV .. 12/6 300 PIV .. 15/-  
400 PIV (280V Rms) .. 17/6  
100 PIV, 3 Amp Stud Type .. 9/6  
400 PIV, 7 Amp (280V Rms) Stud Type 25/-  
400 PIV, 3 Amp (280V Rms) Stud Type 20/-

**FM STEREO DECODER**  
7 Mullard Transistors. Printed Circuit Design with Stereo Indicator. For use with any valve or transistor FM. Uses pot cores to Mullard design and ger. and silicon transistors. Leaflet on request.  
Complete Kit Price **£5.19.6** P.P. 2/-

(5) **VHF FM TUNER TO BUILD**  
87/105 Mc/s Transistor Superhet. Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3 1/2 x 2 1/2 in. Complete with dial plate. 5 Mullard Transistors (FM Decoder Kit £5.19.6. P.P. 2/-). Leaflets on request.  
**TOTAL COST TO BUILD £6.19.6** P.P. 2/6 (Cabinet Assembly 20/- extra)

(8) **TOURMASTER TRANSISTOR CAR RADIO**  
7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wave-change. R.F. stage. Supplied built, boxed, ready to use with Speaker and Baffle. Car fixing kit and manufacturers' current guarantee. Special Bargain Offer. Buy Now! Leaflet on request.  
List Price 15 gns. **£9.9.0** P.P. 3/6

**NEW!** VHF FM plus MW and Longwave Car Radio. 3 watts O/P. Pos. or neg. earth 12 volt. British Made. Complete with speaker, etc. **25 gns.**

**TUNNEL DIODES**  
1mA 22/6; 5mA 15/-; 15mA 12/6. Brand new at fraction of normal price. Free Specs. supplied.

**TRANSISTOR CATALOGUE**  
Completely new 24-page 1967 edition. Hundreds of new types with details. The largest range available. Send 1/ for your copy.

**INVERTOR KITS**  
12 volt input, output 230 volts a/c approx. 5A/s. Transistorised designs.  
● 15 watt .. 67/6, p.p. 3/6  
● 40 watt .. 97/6, p.p. 6/6

(1) **REGENT-6 MW/LW POCKET RADIO TO BUILD**  
6-Transistor superhet. Geared tuning. Push-pull speaker output. Moulded cabinet 5 x 3 x 1 1/2 in. Phone socket. P.P. 1/6  
**TOTAL COST TO BUILD 69/6**

**TINY TONE RADIO CONTROL**  
Miniature 27 Mc/s band, Radio Control Receiver. Size only 2 x 2 x 1/2 in. Sensitive 4 transistor design. Complete building instructions.  
**TOTAL COST TO BUILD 55/-** P.P. 1/6

**WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION. OR BETTER STILL—BUY THE NEW 1967 CATALOGUE. EVERYTHING YOU NEED IS LISTED.**

"EXPLORER" (P.W. Jan. 1967) MW/VHF Receiver. All parts as specified (less chassis, etc.). 79/6. P.P. 2/6. Parts list on request.

**HENRY'S RADIO LTD.**  
303 EDGWARE RD., LONDON. W.2  
PA Ddington 1008/9 (STD 01-723-1008)  
Open Mon. to Sat. 9-6. Thurs. 1 p.m.  
Open all day Saturday

## ★ MAYFAIR PORTABLE ELECTRONIC ORGAN

Build the World's first All-Transistor Portable Electronic Organ Kit

- Plug-in printed circuits ● 170 transistors and devices ● 10 selected tone colours ● Fully sprung keyboard ● Vibrato ● 6 Octaves of generators ● Simple locked-in tuning ● 110/250 volt mains unit ● Cabinet size 30 1/2" x 15 1/2" x 9"
- Weight 35 lb. Cabinet with detachable legs, music stand and foot swell pedal ● Fully detailed building manual with photos, drawings and full circuits.

TO BUILD YOURSELF IN EASY STAGES. ALL PARTS SOLD SEPARATELY.

Detailed leaflet on request

DESIGNED BY L. W. ROCHE

START BUILDING FOR AS LITTLE AS £5. BUILD THE MAYFAIR A SECTION AT A TIME.

- ★ COMPLETE KIT 99 GNS. (CARR. 30/-).
- ★ HP FACILITIES AVAILABLE.
- ★ COMPLETE RANGE OF ORGAN COMPONENTS IN STOCK.

● SEE FOR YOURSELF CALL IN FOR DEMONSTRATION



SEE PAGE 79 FOR FURTHER RANGE OF STOCK ITEMS

Britain's best-selling hi-fi transistorised units 12 and 25 watt systems, test equipment, AM and FM tuners, etc. The new 1967 catalogue (see above) contains details and illustrations of hundreds of other stock lines. Order your copy now!