

PRACTICAL WIRELESS

JUNE
1967

216

- * COVERS 5 RANGES
- * ALIGNS RECEIVERS
- * CHECKS TUNED CIRCUITS
- * CW or MCW
- * MAINS OPERATED



dual function
SIGNAL GENERATOR

ADCOLA
PRODUCTS LTD.
(Incorporated in England)

**SOLDERING INSTRUMENTS
 AND EQUIPMENT**

DESIGNED FOR
 THE AMATEUR'S
 RADIO STATION



ILLUSTRATED
 List No. 70 $\frac{1}{8}$ " BIT
 IN
 PROTECTIVE
 SHIELD
 List No. 68

for catalogue apply direct to:—
Sales and Service Dept.
ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4

Telephones **MACaulay 0291/3** Telegrams **SOLJOINT LONDON SW4**

JACKSON BROS.

(London) Ltd.

Invite you to see
 their latest designs of
**VARIABLE CAPACITORS
 DRIVES & TERMINALS**

At Stand No.

265


**R.E.C.M.F. EXHIBITION
 OLYMPIA
 23-26 MAY**

JACKSON BROS.
 (London) Ltd.



**KINGSWAY, WADDON,
 CROYDON. CR9 4DG**

NOMBREX INSTRUMENTATION

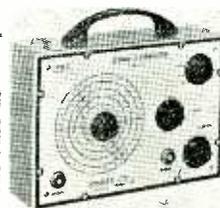

**WIDE RANGE
 TRANSISTORISED
 SIGNAL GENERATOR
 MODEL 27**


- ★ Range 150Kc/s-350Mc/s
 - ★ Direct Calibration
 - ★ Mod. or Unmod. output
 - ★ Accuracy better than 2%
- £10.18.9.

ALSO AVAILABLE

C. R. Bridge 62	£9.8.9
Inductance Bridge 66 ..	£18.8.9
Power Supply Unit 61 ..	£6.16.6

**WIDE RANGE TRANSISTORISED
 AUDIO GENERATOR 63**

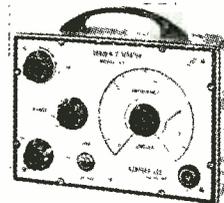- ★ Range 10c/s-100Kc/s
 - ★ Sine or Square Wave
 - ★ Accuracy & Low Dist.
 - ★ Calibrated Output
- £17.3.9



All prices include battery, post and packing

S.A.E. for Leaflet Trade & Export Enquiries Invited Prompt Delivery

NOMBREX LTD INSTRUMENTS DIVISION

Estuary House, Camperdown Ter., Exmouth, Devon

★ JASON TAPE ★

We offer you fully tensilised polyester/nylon and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. **TRY ONE AND PROVE IT YOURSELF.**

Standard Play		Long Play	
3in. 150ft. 2/3	3in. 250ft. 2/3	4in. 300ft. 4/6	4in. 450ft. 5/9
5in. 600ft. 7/6	5in. 900ft. 10/9	5 1/2in. 1,200ft. 13/6	5 1/2in. 1,800ft. 18/6
7in. 1,200ft. 12/6	7in. 1,800ft. 18/6	Double Play	
		3in. 300ft. 4/6	3in. 400ft. 5/6
		4in. 600ft. 8/6	4in. 800ft. 11/6
		5in. 1,200ft. 15/6	5in. 1,800ft. 21/6
		7in. 2,400ft. 27/6	7in. 3,600ft. 41/6
		Triple Play	
		3in. 900ft. 12/6	3in. 1,200ft. 16/6
		4in. 1,200ft. 16/6	4in. 1,800ft. 21/6
		5in. 1,800ft. 21/6	5in. 2,400ft. 27/6
		7in. 3,600ft. 41/6	7in. 5,400ft. 61/6
		Quadruple Play	
		3in. 600ft. 8/6	

Postage 1/- reel.
Post Free less 5% on three reels.

Quantity and Trade enquiries invited. **NOTE. Large tape stocks at all branches.**

BARGAIN PARCELS

Including variable condensers, i.f. coils, loud-speaker plugs/sockets, knobs, pots, condensers, resistors, nuts, bolts, cabinet fittings, switches, transformer choke, rectifier, transistors at a small fraction of list value. Due to heavy demand we are now packing them in several sizes—**TRY ONE.**

3 lbs. (post 3/-)	9/-
7 lbs. (post 6/-)	17/6
14 lbs. (post 8/-)	28/-

AVOID AMPLITUDE DISTORTION WITH YOUR HI-FI AMP.

STABILISED TRANSISTOR POWER SUPPLY

- VARIABLE 0—15V. AT 0—1 AMP.
- STABILISED FOR MAINS VAR. 210 - 250V.
- RIPPLE CORRECTED
- SHORT CIRCUIT PROTECTION
- HANDSOME STYLED CABINET

★ PRICE ONLY 6GNS.

10 WATT TRANSISTOR AMP

Consisting above stabilised power pack (can be used separately), with built-in pre-amp and controls driving two x OC26 main amp. in styled cabinet. New concept in value and design. 10 transistors, selection, vol. and tone controls equalisation.


PRICE 12GNS.

ELPICO MONO PREAMPS

DPA15. Latest black/satin chrome finish multiple input channels selector bass and treble controls. Matches all pick-ups and mikes. Provision tape recording. **4 Gns.** Normally 10 gns. our price

Transistorised FM Tuner

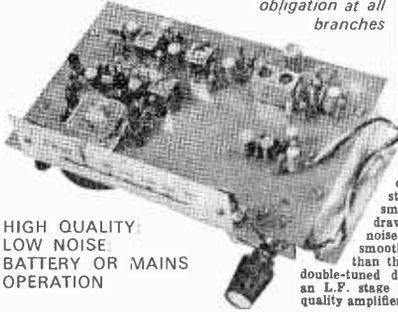CALLERS WELCOME *Demonstration without obligation at all branches*



HIGH QUALITY
LOW NOISE
BATTERY OR MAINS
OPERATION

TRANSISTORS GUARANTEED TOP QUALITY

Mullard Matched Output Kits OC81D and 2-OC81 .. 9/6
R.F. Kits OC44, OC45 (2) 3 transistors .. 9/6

GERMANIUM DIODES

General Purpose miniature detector A.V.C. etc. 6/8 doz. **8d.**
Gold Bonded highest quality. Individually tested 9/8 doz.

SILICON H.T. RECTIFIERS

Guaranteed performance. Top makes. Tested 250v. working. 120 mA **2/9**
(3 for 6/8)
500 mA **7/6**
(3 for 19/6)

This beautifully compact 6 transistor machine (size 6 x 4 x 2 in.) will give quiet, more interference free reception. Months of use from a standard 9 volt battery or its small power requirements can be drawn from any amplifier. Low noise frequency changer with smooth 2 gang tuning feeding no less than three I.F. stages coupled to a double-tuned discriminator terminating in an L.F. stage giving ample output for all quality amplifiers.

avoid disappointment

ORDER NOW £8-10

Value in VALVES GUARANTEED 3 MONTHS BY RETURN OF POST

Satisfaction or Money Back Guarantee on goods if returned unused within 14 days. ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED. FREE TRANSIT INSURANCE. POSTAGE 1 valve 9d. 2-11 6d. per valve. Free over 12.

1L4	2/3	6K8GT	9/8	30P4	17/9	ECG38	9/6	GZ34	10/8	SP81	2/9
1R5	4/9	8L1	9/8	25L8GT	7/-	ECF80	7/9	KT81	12/-	TTD4	7/-
1X4	4/9	8L6G	8/6	25Z4G	7/-	ECF82	7/6	KT63	5/9	UA14/18	7/6
1R5	4/6	8L18	7/9	30F5	9/-	ECH21	10/-	KT66	19/6	U25	9/6
1T4	3/-	8LD20	8/6	30FL1	9/6	ECH35	11/-	KT88	27/6	U28	9/6
3D21	5/6	8P25	12/-	30L15	11/6	EOH42	10/8	KTW61	5/9	U35	12/6
3A5	6/-	8P28	9/6	30P4	11/6	ECH31	6/9	KTW63	5/9	U37	11/-
3Q4	5/3	8Q7G	7/-	30P12	9/-	EOH33	7/8	RT263	7/-	U107	12/6
5U4G	6/-	8Q7GT	8/9	30PL1	11/-	ECL80	5/9	MU14	7/-	U119	12/6
5Y3GT	6/6	8SL7GT	6/9	35A5	9/6	ECL82	7/6	N37	9/6	U281	9/6
5Z4G	6/9	8SN7GT	6/9	35L6GT	8/6	ECL83	10/6	N78	13/-	U282	15/-
5ZAGT	9/6	8T4GT	9/6	35W4	6/6	ECL86	9/6	N108	13/-	U283	8/6
6X0L2	9/6	6V8G	4/9	35Z4GT	5/9	EP36	4/9	PC88	9/6	U301	19/-
6A8G	7/6	6V8GT	6/8	30L8GT	8/6	EP39	7/-	PC97	7/6	UABC80	8/6
6AK5	4/9	6X4	4/6	80	7/6	EP40	10/-	PC84	6/8	UAF42	7/9
6AQ5	5/-	6X5G	5/-	185BTA19/6	EP41	9/-	PC85	7/6	UB41	6/6	
6AT8	5/-	6X5GT	6/9	807	9/6	EP50	3/3	PC88	11/9	UB41	8/9
6BA6	5/6	7B8	11/6	856	3/6	EP80	4/3	PC89	11/-	UBC91	8/9
6BE6	5/6	7B7	7/6	955	3/6	EP85	6/3	PC189	9/9	UBF80	7/6
6BH6	6/6	7C5	9/6	AZ31	8/6	EP86	7/6	PCF59	6/9	UBF99	7/6
6B16	7/-	7C6	7/6	CB1.3	19/6	EP89	6/6	PCF82	6/9	UBL21	10/9
6BE7	9/6	7H7	7/6	DAF96	7/6	EP91	3/8	PCF88	8/3	UC92	8/9
6BW6	7/6	7S7	14/6	DF96	7/3	EP183	8/-	PCL82	7/6	UC95	7/3
6BW7	5/-	7Y4	7/-	DK92	8/6	EP184	8/-	PCL83	9/6	UCF91	7/6
6C4	3/-	10C1	11/-	DK92	8/6	EL32	5/-	PCL94	9/-	UCH20	9/6
6C5	5/6	10C2	12/6	DL92	6/-	EL33	12/-	PCL85	9/6	UCH42	8/6
6C3	4/-	10F1	7/6	DL94	8/6	EL34	11/6	PCL86	9/6	UCH81	7/-
6C9	11/-	10D11	14/6	DL96	7/6	EL35	8/-	PL33	9/6	UCL82	8/-
6D8G	17/-	10P13	9/6	EAPC80	6/9	EL38	15/-	PL36	11/-	UCL83	10/8
6D8	4/-	10P14	9/6	EAP42	8/9	EL41	9/9	PL38	12/6	UP41	9/6
6F1	6/6	12AT7	4/9	EB41	4/6	EL42	8/9	PL81	7/9	UF42	6/6
6F8G	5/-	12AU7	5/6	EB22	2/8	EL84	6/8	PL82	5/9	UF85	7/6
6F13	4/8	12AX7	6/-	ECB33	7/6	EM80	7/-	PL83	6/-	UF89	6/9
6F14	7/6	12TGT	9/-	EB041	9/6	EM81	7/6	PL84	7/-	UL41	10/-
6F15	9/6	12KGT	9/-	EB091	6/9	EM84	7/6	PT31	7/6	UL44	14/6
6F23	8/-	12K8GT	9/6	EBF80	7/9	EY51	7/6	PT32	9/6	UL46	10/6
6J5G	4/-	12Q7GT	6/6	EBF89	7/-	EY86	7/6	PT33	7/6	UL84	6/6
6J5GT	6/6	1487	14/6	EEL21	11/-	EY88	8/8	PY80	5/9	UM90	9/6
6J8	3/3	19A95	5/6	ECC40	9/6	EZ40	7/6	PY81	5/9	UY21	8/9
6J7G	5/6	20D1	8/9	ECC81	4/9	EZ41	8/6	PY82	5/6	UY41	7/-
6J7GT	9/6	20P2	9/6	ECC82	5/6	EZ80	5/8	PY83	5/9	UY85	5/6
6K7G	2/8	28L1	16/-	ECC83	6/-	EZ81	6/-	PY88	8/8	VR105	5/6
6K7GT	5/9	20P1	9/6	ECC84	7/-	FC4	8/-	PY80	7/-	VR150	5/6
6K8G	5/9	20P3	9/6	ECC85	5/9	GZ32	9/6	PZ30	9/6	X86	7/9

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone Linear Rogers, Truvox, Ferrograph, Wharfadele, etc.
Post: 1 lb. 1/5, 1 1/2 lb. 2/6, 2 lb. 2/9, 4 lb. 3/3, 6 lb. 4/-, 14 lb. 5/6, All Mail Orders to Brighton please

TECHNICAL TRADING

LONDON 10 Tottenham Court Road, W.1. Tel. MUSEum 8639

BRIGHTON Park Crescent Place Tel. 680722

PORTSMOUTH 350-352 Fratton Road Tel. 22034

SOUTHAMPTON 72 East Street Tel. 25851

WORTHING 132 Montague Street Tel. 2585

"SURPASSED ALL MY EXPECTATIONS"

M. I. CULLEN, CHELTENHAM

JOYSTICK VFA SYSTEMS

The Joystick VFA system is a remarkable invention. Its unique quality of high performance at any selected frequency from 1 Mc. to 30 Mc/s.—particularly from difficult locations—has radically changed the attitude of both the licensed amateur and the shortwave listener towards their aerial problems.

Each Joystick VFA system is complete with a Joymatch matching unit suitable for your type of operation.

You cannot afford to ignore the potential of the Joystick VFA. The system is simple to use—the Joystick VFA will clip to a chimney, tree or mast, can be laid upon a pelmet, stood in the corner of a room, will even give a good account of itself in a basement.

You are strongly recommended to contact the Joystick factory immediately (or one of our agents) for a brochure with full details.

More Testimonials to Joystick Systems.

"Quite an antenna this — ZL's, VK's and anywhere you like to mention". L. W. Hastings, Surrey.

U.K. Agents: G. W. Smith & Co. (Radio) Ltd., 3 Lisle Street, London, W.C.2. Stephens-James Ltd., 70 Priory Road, Liverpool. 4. Chas. H. Young, 170/172 Corporation Street, Birmingham, 4. R.S.C. (Manchester) Ltd., 326 Argyle Street, Glasgow, C.1 (and all branches). Swan & Co. Products Ltd., 247 Humber Ave., Coventry. Lasky's Radio (all branches). G3HSC, 45 Green Lane, Purley, Surrey. (Demonstrations by appointment).



Joymatch Type 3—General short wave coverage SWL (Junior model).

U.S. PATENT
No. 3274600.
S. AFRICA PATENT
No. 63/4389.
UK and World Patents
applied for.



Joymatch Type 2A—General medium wave coverage extending over short wave spectrum.



Joymatch Type 3A—General short wave coverage for SWL. Bandswitched for amateur bands.

Post this coupon in the morning—without fail!
PARTRIDGE ELECTRONICS LIMITED
Caister House, Prospect Road, Broadstairs, Kent.

NAME Call sign

ADDRESS

PWE

Adamin

MICRO SOLDERING INSTRUMENTS

New revised range

6 models

5 WATTS to 24 WATTS

- HIGH PERFORMANCE

325/400°C. Some models 450°C.

- MINIATURE

Overall lengths 6½ in. to 7½ in.

Maximum handle dia, 7/16 in.

- LIGHT

Weights from ¼ oz. to 1 oz. without flex

- RAPID HEATING

30 seconds to 2 minutes

- WIDE RANGE OF BITS

Tips 3/8 in. (-047) to ¼ in. dia.

ask for new colour catalogue

LIGHT SOLDERING DEVELOPMENTS LTD

28 Sydenham Road, Croydon, CR9 2LL

Telephone: 01-688 8589/4559



CODAR — QUALITY

ANOTHER CODAR TRIUMPH!

THE CR.70A COMMUNICATION RECEIVER.

This completely new receiver sets a new high standard for performance and finish unequalled at the price, and is a worthy addition to the outstanding range of CODAR quality communication equipment. Frequency range: 560 Kc/s-30 Mc/s (540-10 metres) in four ranges; 560 Kc/s-1.5 Mc/s; 1.5 Mc/s-4.2 Mc/s; 4.2 Mc/s-11.5 Mc/s; 11.5 Mc/s-30 Mc/s. Slide rule scales for each band calibrated in frequencies plus an additional logging scale in degrees. Two speed vernier tuning control with reverse slow tuning action. Unique aerial input stage exclusive to the CR.70A employing High 'Q' Air-spaced CODAR-COIL inductor giving extremely high gain with low noise level. Panel aerial trimmer for peaking weak signals. Double tuned I.F. Iron cored transformers. 470 Kc/s with EF183 frame grid valve for maximum gain and selectivity. 5 valves (including two twin triodes) giving 7 valve line-up. Separate B.F.O. stage for CW and SSB reception. Calibrated signal strength 'S' meter, illuminated. Automatic Volume control. Panel phone jack for 'private' listening. 2-3 ohm output for external speaker. (Matching unit optional extra.) Superb styling, metal cabinet in the new Organasol Satin lustre finish. Size: 13" x 5 1/2" x 7 1/2". For A.C. 200/250v. Ready built. Not a Kit at the fantastic low price of £19.10.0. Carr. 7/6.

CODAR R.F. PRE-SELECTOR MODEL P.R.30. Considerably improves the performance of any superhet receiver over 1.5-30 Mc/s. Uses EF183 Frame Grid Valve, and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12mA H.T. 6.3 volts. 3 amp L.T. Size 8 1/2 x 5 x 4 in. Ready built, complete with cables, plugs and instructions. £5.10.0. Carr. 4/6. **MODEL P.R.30X.** Self powered model for 200-250v. A.C. Also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £7.4.0. Carr. 4/6.

CODAR "Q" MULTIPLIER MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or selecting a signal on AM, CW, or SSB. B.F.O. Size 8 1/2 x 5 x 4 in. Power requirements 180-250v. H.T. at 5mA 6.3v. 3 amp L.T. Ready built complete with cables, plugs and instructions. £6.15.0. Carr. 4/6. **MODEL R.Q.10X.** Self powered version for 200-250v. A.C. and also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £8.8.0. Carriage 4/6.

CODAR A.T.5, 12 WATT 2 BAND TRANSMITTER. The newest most compact transmitter for fixed or mobile use on 160-80 metres. "The tiny TX with the BIG voice". Size only 8 1/2 x 5 x 4 in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR COIL Pi-net output. P.A. Plate current meter plus neon indicator. Plate-Screen modulator. AM/CW switch and Panel key jack. Plug changeover for 6 or 12 volts heater supply. Ready built £18.10.0. Carr. 4/6. **A.T.5 POWER SUPPLY UNITS.** For 200-250v. A.C. and 12v. Solid state for Mobile use, complete with all Transmit/Receive changeover switching available.


CODAR-KIT CR.45K MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandspread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned. ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line-up: ECC81, EL84, EZ80. Size 12 x 6 1/2 x 7 in. **CODAR-KIT CR.45K** complete with valves, 3 coils (10-28, 25-75, 60-176 metres) and 11 page instruction manual. £9.10.0. Carr. 6/-. Extra coils 5/- each. Instruction manual only 4/- (credited on order). (Can also be supplied ready built—price on request).

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER. ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 39/6. Carr. 3/-. Extra coils 5/- each. Instruction manual only 2/- (credited on order). Electrical bandspread available. Provision to add 2 transistor amplifier.

Send 6d. in stamps for illustrated leaflets of the Codar range

H.P. terms available

World-wide Mail Order Service

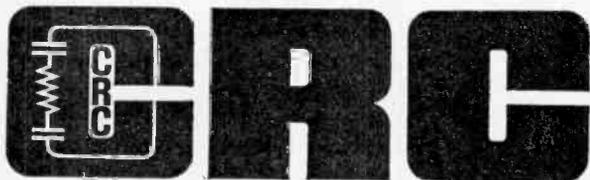

CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE

SOUTHWICK, SUSSEX. Tel. 3149

G3IRE

G3HGO

Canada: Codar Radio of Canada, Tweed, Ontario

R.S.T. VALVE MAIL ORDER CO.

144-146 WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.
—5.45 p.m.
No Early Closing
Daily to Callers
Tel. STR 0199, 1649

0A2 5/-	6BB6 4/6	6K6GT 5/-	7R7 19/8	19A95 7/6	50L6GT 6/-	DF96 6/-	ECF80 7/-	FM81 7/-	PCC189 10/-	8130 25/-	UM80 7/-
0C3 5/-	6BH6 7/-	6K7M 5/-	787 17/9	20D1 10/-	75 5/-	DH77 3/6	ECF82 7/-	EM84 7/-	PCF90 6/6	8P4 9/-	UU6 13/6
1A7 7/9	6BJ6 7/-	6K7G 1/3	7Y4 7/8	20F2 11/-	78 4/8	DK32 7/9	ECH21 19/-	ESU15027/6	PCF82 6/6	8P41 1/6	UU7 13/6
1D5 6/-	6BQ7A 7/-	6K7GT 4/6	9BW6 8/-	20L1 15/-	80 5/-	DK91 5/-	ECH35 11/-	EY51 7/-	PCF84 8/-	8P61 1/-	UU9 8/-
1H5 7/6	6BR7 10/6	6K8M 8/6	10C1 9/-	20P4 17/-	85A2 8/6	DK92 8/-	ECH42 9/-	EY86 6/6	PCF86 8/-	8U25 19/6	UY21 7/6
1LD5 5/-	6BR8 7/6	6K8G 3/-	10C2 12/-	20P6 16/-	150B2 14/8	DK96 6/6	ECH51 5/3	EZ25 4/9	PCF89 9/9	SU2150 12/6	UY41 6/3
1R5GT 8/-	6BR7 16/9	6K8GT 8/3	10F1 14/-	25A9 8/6	150C4 12/6	DL66 15/-	ECH83 7/-	EZ40 7/-	PCF802 9/9	T41 9/-	UY85 5/-
1R5 5/-	6BW6 7/6	6K25 20/-	10F3 12/-	25L8GT 4/6	801 5/-	DL92 4/9	ECL80 6/6	EZ41 8/-	PCF805 10/9	TDD4 7/-	VMP4G 17/-
184 5/-	6BW7 8/6	6L1 9/6	10F9 9/9	25Y5 6/-	807 7/9	DL93 3/6	ECL82 6/6	EZ80 5/-	PCF806 12/6	U10 7/-	VP4R 27/6
1R5 3/3	6C4 3/6	6L6G 7/-	10F18 9/-	25Z4 8/1	813 80/-	DL94 5/9	ECL83 9/-	EZ81 5/-	PCF808 11/6	U14 7/-	VR105/30
1T4 2/6	6C5G 4/-	6L18 7/6	10L1 10/-	25Z5 7/-	866 10/-	DL95 6/8	ECL86 8/9	GZ30 8/6	PCL82 7/-	U19 30/-	VR150/30
3A4 3/6	6C6 3/9	6Q7G 5/6	10LD11 10/-	25Z6 11/-	954 4/-	DL96 6/-	EP9 20/-	GZ32 9/6	PCL83 8/6	U25 10/6	VR150/30
3Q4 6/6	6C8G 3/9	6Q7GT 9/-	10P13 14/-	25D7 5/-	1625 5/-	DM70 5/-	FP36 3/-	GZ34 10/-	POL84 7/3	U26 10/6	VR150/30
3Q5 6/8	6C8G 3/9	6SA7 7/-	12A7 7/6	30C1 6/6	4022AR15/-	DY86 6/6	EP37A 7/6	KT36 22/6	PCL85 8/6	U78 3/6	VT25 29/-
384 4/9	6CD6G 22/6	68C7 6/6	12A7E 4/6	30C15 11/8	5763 10/8	EY87 7/9	EP39 6/-	KT61 17/6	PCL86 8/6	U191 11/6	VT31 59/-
3V4 5/9	6CH6 5/9	68G7 4/-	12A7T 3/9	30C17 12/-	7193 1/8	E880C 12/-	EP41 8/6	KT66 20/-	PEN44 20/-	U251 12/6	VU11 6/-
3R4G 8/9	6C16 5/9	68H7 2/6	12A7E 3/9	30F5 13/-	7475 2/8	EA59 2/-	EP50 2/-	KT81 10/-	PEN44 20/-	U301 13/-	VU120 12/6
5U4G 4/-	6CW4 12/6	68J7 5/9	12A7E 3/9	30F14 13/8	ATP4 1/9	EABC90 5/9	EP80 5/-	KT88 27/6	PEN45 6/-	U403 6/6	VU508 30/-
5V4G 5/-	6F1 9/-	68L7GT 4/9	12A7T 5/9	30L15 12/6	ATP5 7/-	EAF42 7/6	EP85 6/8	KTW61 4/3	PEN46 2/9	U801 18/6	W81M 5/-
5Y3GT 5/-	6F5G 4/-	68N7GT 4/-	12BA8 6/-	30L17 12/-	ATP7 4/8	EB41 4/6	EP86 6/3	KTZ41 8/-	PL36 9/9	UAB080 5/6	X79 41/-
5Z4G 8/-	6F6G 5/-	68N7GT 4/-	12BA8 6/-	30P12 10/-	AU2 30/-	EB91 3/-	EP89 5/6	M14 17/6	PL81 7/6	UAF42 8/9	XH1-5 5/-
6/301.2 11/3	6F8G 4/-	68Q7 8/-	12BB6 5/3	30P19 14/-	AU5 6/-	EBC23 7/-	EP91 3/3	M16 12/6	PL82 6/6	UBC41 8/6	XF1-5 5/-
6A7 15/-	6F9G 4/6	6U4GT 12/-	12CBGT 7/6	30P14 14/-	AZ1 8/9	EB04 8/3	EP92 2/8	M8P4 12/6	PL83 6/-	UBC81 7/6	XBG1-5 10/-
6A8G 12/6	6F11 12/6	6U5G 7/6	12E1 19/6	30P13 14/-	AZ31 7/9	EBC90 3/3	EP98 9/-	MU14 4/-	PL84 6/6	UBF80 5/9	Y63 7/6
6AC7 3/-	6F13 5/-	6V6M 8/-	12J5GT 2/3	30P14 14/-	CHL31 15/-	EBF80 6/6	EP183 6/6	MX40 12/6	PL500 14/6	UBF89 6/6	UBF89 6/6
6AK5 4/6	6F14 12/6	6V8G 3/6	12K7GT 7/3	35A5 17/-	CHC35 21/-	EBF83 7/-	EP184 6/6	N37 10/-	PX4 8/6	UCC84 8/6	3BG1 40/-
6AL5 3/-	6F23 11/-	6V8GT 7/-	12K7GT 3/-	35L6 5/9	CL33 19/6	EBF89 6/6	EL32 3/-	N78 15/-	PY33 8/6	UCC85 6/6	3FP7 16/6
6AM5 2/6	6G6 2/6	6X4 3/6	12K8GT 8/-	35W4 4/6	CY31 10/-	EBL1 17/6	EL33 17/6	N105 15/-	PY81 8/-	UCF80 8/6	5CP1 30/-
6AM6 3/3	6H6 1/3	6X5G 4/9	12Q7GT 3/-	35Z3 10/-	DAC32 7/8	EBL21 10/6	EL34 8/6	NGT1 3/-	PY82 5/6	UCH42 8/6	CV1526 40/-
6AQ5 5/6	6J6M 6/6	6X5GT 7/8	12S7 6/6	35Z4GT 3/9	DAF91 3/3	EBL31 27/6	EL41 8/8	NGT7 25/-	PY83 6/-	UCH81 6/3	ACR18 18/-
6AS7G 18/6	6J5G 2/6	7B6 11/-	12SGT 3/6	35Z5 5/8	DAF96 6/-	ECC81 3/9	EL42 7/6	OZ4 4/-	PY800 7/-	UCL92 7/6	23.16.0
6AT5 3/9	6J5GT 4/6	7B7 7/-	12SH7 2/9	37 5/-	DCC90 8/-	ECC82 4/9	EL84 4/6	PC86 9/-	RY801 7/-	UCL83 8/9	VCR97 35/-
6AU6 6/-	6J6 3/-	7C5 10/-	12S7 3/9	42 4/8	DF33 8/-	ECC83 5/9	EL90 5/8	PC88 9/-	R2 4/-	UF41 8/-	VCR157R
6B8G 2/-	6J7M 8/6	7C6 6/-	12S7 2/9	50B5 8/6	DF70 5/-	ECC84 5/6	EL95 6/-	PC97 7/6	R19 7/-	UF89 6/-	30/-
6B4G 10/-	6J7G 4/9	7D5 8/-	12SR7 5/-	50C5 5/9	DF91 2/8	ECC85 5/-	ELL80 20/-	PC884 8/6	RG51500 5/-	UL41 8/9	VCR517C
6BA6 4/6	6J7GT 8/6	7D7 5/-	14H7 9/-	50CD632/6	DF92 2/6	ECC88 7/-	EM80 7/-	POC89 10/-	58/-	UL84 6/-	30/-

SPECIAL 24 HOUR SERVICE
OBSOLETE TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
Postage 6d. per Valve C.W.O. No C.O.D.

**Special 24 Hour
Express Mail
Order Service**

SETS OF VALVES

DAF96, DF96, DK96, DL96 Set of 4. 2.4/6


BRAND NEW TRANSISTORS

AC127 8/-	OC25 11/-	OC71 4/6	OC81 4/-	OC82D 6/-
AF114 7/-	OC28 16/-	OC72 8/-	OC81m/pr	OC83 6/-
AF115 7/-	OC35 9/6	OC75 6/-	12/6	OC170 7/-
AF116 7/-	OC44 4/6	OC76 6/-	OC81D 4/-	OC171 8/-
AF117 5/-	OC45 3/6	OC77 8/-	OC82 6/-	OC200 8/-

Manufacturers and Export Inquiries Welcome

SEND S.A.E. FOR LIST OF 2,000 TYPES

surprise surprise

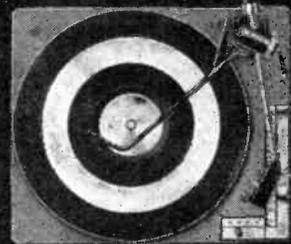

RUA UP EE or AC?

Just in case you don't get it—here's the translation... "Are you a University Professor, Electronics Engineer or Amateur Constructor?" All three types find life much easier with a Home Radio Catalogue to track down all the components they need. Incidentally, our cartoonist has been taking artistic licence again—our catalogue is such a necessity that everybody buys their own copy. Have you got yours? If not, all you have to do is to send the coupon with a cheque or P.O. for 9/- (7/6 plus 1/6 p. & p.), and your catalogue will come by return of post.

Just to remind you—the catalogue lists some 6,000 components with over 1,000 of them illustrated. With each catalogue you also get a Bargain List, a Bookmark, an Order Form and—just to make life really easy for you—an addressed envelope! Moreover every copy contains 5 vouchers, each worth one shilling if used as directed.



Please write your Name and Address in block capitals

NAME.....

ADDRESS

HOME RADIO LTD, Dept. PW, 187 London Rd, Mitcham, Surrey, CR4 2YQ

Perhaps you will be as surprised as the pundits when you hear the facts* about the BSR C1 ceramic cartridge "... another milestone on the public right-of-way to high fidelity"—said *The Gramophone*.

You could even be surprised to know that the BSR UA70 manual/automatic turntable unit is fitted with such a splendid cartridge and that its all round performance is equal to such high standards.

But maybe not... you could be one of those sensible people who knew all along that BSR don't just make a lot of autochangers but a lot of *very good* autochangers.

*If you'd like to read the independent test reports write to Arthur Nicholls at:

BSR Limited, Monarch Works, Old Hill, Staffordshire.



for better
sound reproduction

BSR UA70 SPECIFICATION

Turntable

Wow Less than .2%

Flutter Less than .06%

Long term speed variation

Less than .5%
(mains voltage $\pm 10\%$)

Rumble (ref.1kHz) —29 dB

Pick-up arm

Counterbalanced lightweight arm with calibrated tracking pressure control, integral cueing device and automatic lock.

Tracking pressure (depending on cartridge)
2 grams. min.

Cartridge

The now famous C1 ceramic

Compliance 5.2×10^{-6} cm/dynes

Frequency response 20-15,000 Hz

± 2 dB

Standard UA70 player £12.18.3*

C1 Ceramic Cartridge

sapphire stylus £2. 7.0*

diamond stylus £3. 1.9*

*Inc. P.T. surcharge

HI-FI AMPLIFIERS — TUNERS — RECORD PLAYERS

20+20
STEREO
AMP.
AA-22U



GARRARD
PLAYER
AT-60



TRANSISTOR MIXER. MODEL TM-1. A must for the tape enthusiast. Four channels. Battery operated. Similar styling to Model AA-22U Amplifier. Kit £11.16.6. Assembled £16.17.6

20+20W TRANSISTOR STEREO AMPLIFIER. Model AA-22U. Outstanding performance and appearance. 5 stereo inputs each channel, 20 transistor, 10 diode circuit. Kit £39.10.0 Assembled £57.10.0 (Cabinet £2.5.0 extra)

GARRARD AUTO/RECORD PLAYER. Model AT-60. less cartridge £14.12.10 With Decca Deram pick-up £19.7.4 incl. P.T. Many other Garrard models available, ask for Lists.

HI-FI MONO AMPLIFIER. Model MA-5. A general purpose 5W Amplifier with inputs for Gram., Radio. Modern functional appearance. Kit £11.9.6 Assembled £15.15.0

10W
POWER
AMP.
MA-12



9+9W
STEREO
AMP.
S-99



HI-FI MONO AMPLIFIER. Model MA-12. 10W output, wide freq. range, low distortion. Use with control units. Models UMC-1 (Mono) or USC-1 (Stereo). Kit £12.18.0 Assembled £16.18.0

CONTROL UNITS. Mono, UMC1. Kit £9.2.6. Assembled £14.2.6. Stereo, USC-1. Kit £19.19.0. Assembled £27.5.0.

DE LUXE STEREO AMPLIFIER. Model S-33H. De luxe version of the S-33 with two-tone grey perspex panel, and high sensitivity necessary to accept the Decca Deram pick-up. Kit £15.17.6 Assembled £21.7.6

HI-FI STEREO AMPLIFIER. Model S-99. 9+9W output. Ganged controls. Stereo/Mono, gram, radio and tape inputs. Push-button selection. Printed circuit construction. Kit £28.9.6 Assembled £38.9.6

POWER SUPPLY UNIT. Model MGP-1. Input 100/120V, 200/250V, 40-60 c/s. Output 6-3V 2-5A A.C. 200, 250, 270V, 120mA max. D.C. Kit £5.12.6 Assembled £7.2.6



ENJOY YOURSELF & SAVE MONEY

Finished models provide years of superlative performances

NEW!



HIGH PERFORMANCE CAR RADIO, CR-1. Superb LW/MW entertainment, wherever you drive. For 12V pos. or neg. earth systems. Tastefully styled to match any car colour scheme. Many special features. Send for details. Can be built for a total price Kit (less spkr) £12.17.0 incl. P.T. (6 x 4 LS £1.4.5 extra)

RADIOS



Oxford



UXR-1

"OXFORD" LUXURY PORTABLE Model UXR-2. Specially designed for use as a domestic or personal portable receiver. Many features, including solid leather case. Kit £14.18.0 incl. P.T.

TRANSISTOR PORTABLE. Model UXR-1. Pre-aligned I.F. transformers, printed circuit. Covers L.W. and M.W. Has 7" x 4" loudspeaker. Real hide case. Kit £12.11.0 incl. P.T.

JUNIOR EXPERIMENTAL WORKSHOP Model EW-1. More than a toy! Will make over 20 exciting electronic devices. incl.: Radios, Burglar Alarms, etc. 72 page Manual. The ideal present! Kit £7.13.6 incl. P.T.

TRANSISTOR STEREO FM TUNER. Elegantly designed to match the Stereo Amplifier, model AA-22U seen above. Many special features include built-in power supply. Available in two units sold separately, can be built for a TOTAL PRICE KIT (STEREO) £24.18.0 incl. P.T. Cabinet £2.5.0 extra. (MONO) version £20.19.0 Kit.

WHEN IN LONDON VISIT THE HEATHKIT CENTRE

233 Tottenham Court Road, W.1
We open MONDAY-FRIDAY 9 a.m.-5.30 p.m.
SATURDAY 9 a.m.-1.0 p.m.
Telephone No.: 01-636-7349

WHEN YOU ARE IN TOWN, WE HOPE YOU WILL VISIT US THERE

TEST INSTRUMENTS

Our wide range includes:

3" LOW-PRICED SERVICE OSCILLOSCOPE. Model OS-2. Compact size 5" x 7 3/8" x 12" deep. Wt. only 9 3/4 lb. "Y" bandwidth 2 c/s-3 Mc/s ±3dB Sensitivity 100mV/cm. T/B 20 c/s-200 kc/s in four ranges, fitted mu-metal CRT Shield. Modern functional styling. Kit £23.18.0 Assembled £31.18.0

5" GEN.-PURPOSE OSCILLOSCOPE. Model 10-12U. An outstanding model with professional specification and styling. "Y" band width 3c/s-4.5 Mc/s ± 3dB. T/B 10 c/s-500 kc/s. Kit £35.17.6. Assembled £45.15.0

DE LUXE LARGE-SCALE VALVE VOLTMETER. Model 1M-13U. Circuit and specification based on the well-known model V-7A but with many worth-while refinements, 6" Ernest Turner meter. Unique gimbal bracket allows operation of instrument in many positions. Modern styling. Kit £18.18.0 Assembled £26.18.0


VALVE VOLTMETER. Model V-7A. 7 voltage ranges d.c. volts to 1,500 A.C. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0-1Ω to 1,000MΩ with internal battery. D.C. input resistance 11MΩ. dB measurement, has centre-zero scale. Complete with test prods, leads and standardising battery. Kit £13.18.6 Assembled £19.18.6

MULTIMETER. Model MM-1U. Ranges 0-1.5V to 1,500V a.c. and d.c.; 150μA to 15A d.c.; 0-2Ω to 20MΩ 4 1/2" 50μA meter. Kit £12.18.0 Assembled £18.11.6

R.F. SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamentals and 200 Mc/s on harmonics. Up to 100mV output. Large accurate, calibrated dial scales. Factory wired and aligned coil and band switch assemblies. Ideal for the service shop. Kit £13.18.0. Assembled £20.8.0.

TV ALIGNMENT GENERATOR. Model HFW-1. Covers 3-6 Mc/s—220 Mc/s with 0-42 Mc/s max. sweep width. Stable all-electronic sweep circuit. Built-in marker oscillators—5 Mc/s crystal and 20 to 60 Mc/s variable. AGC circuit. Positive action return trace blanking. Kit £38.18.0. Assembled £49.15.0.

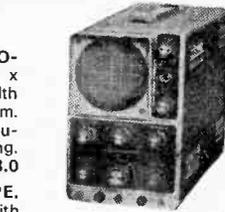TRANSISTOR POWER SUPPLY. Model IP-20U. Up to 50V, 1-5A output ideal for Laboratory use. Compact size. Kit £35.8.0 Assembled £47.8.9



OS-2




VVM, 1M-13U



V-7A



RF-1U

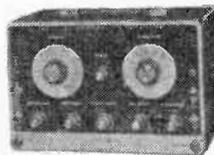

HFW-1

Prices and specifications subject to change without notice

VALVE TUNERS



TUNERS
← FM
AM/FM →

★ **HI-FI FM TUNER.** Model FM-4U. Covers 88-108 Mc/s. Fly-wheel tuning. Pre assembled and aligned. R.F. tuning unit (£2.15.0 incl. P.T.) with I.F. output of 10.7 Mc/s and I.F. amplifier unit, with power supply and valves (£13.13.0). For free standing or cabinet mounting. Total Kit **£16.8.0**

★ **HI-FI AM/FM TUNER.** Model AFM-1. Covers AM 16 to 50 200-550 and 900-2000 metres FM 88-108 Mc/s. Pre-aligned Tuning Heart (AFM-T1—£4.13.6 incl. P.T.) and I.F. amplifier (AFM-A1—£22.11.6). Printed circuit board, 8 valves. Built-in power supply. Total Kit **£27.5.0**


★ Models available in two units for your convenience.

MULTIPLEX DECODER. Model SD.1. Convert above models to stereo at low cost. Transistorised circuit. Self powered. Compact, matching unit. Kit **£8.10.0**. Assembled **£12.5.0**.

LATEST MODELS



STEREO AMPLIFIER, TS-23

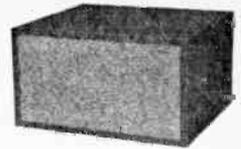

BOOK SHELF SPEAKER

Low-priced 3+3 watt TRANSISTOR AMPLIFIER. TS-23 Breaks the price barrier in quality stereo amplifier cost. Incorporates all the essential features for good quality reproduction from gram, radio and other sources. 3W rms (15Ω) each channel. Good frequency response. Modern, compact, slim-line styling. Ganged controls. 6 position selector switch. 16 transistor, 4 diode circuit. Walnut veneered cabinet, optional extra. Kit (Amplifier) **£17.15.0** Cabinet **£2.0.0** extra.

Good performance from a Mini speaker with the 'AVON' BOOKSHELF SPEAKER SYSTEM. Occupies the minimum space consistent with first class reproduction. Only 7½" x 13½" x 8½" deep. Two special speakers 6½" BASS, 3½" HF unit and crossover network. Kit **£4.18.0** incl. P.T. Walnut veneered, Fully finished cabinet, kit **£8.18.0**. TOTAL PRICE KIT **£13.16.0** incl. P.T.

Build Britain's Best Electronic Kits



No special kit-building skills or Electronic knowledge required

SPEAKER SYSTEMS



SSU-1

HI-FI SPEAKER SYSTEM. Model SSU-1. Ducted-port bass reflex cabinet "in the white". Two speakers. Vertical horizontal models with legs, Kit **£12.12.0** without legs, Kit **£11.17.6** incl. P.T.

The **BERKELEY SLIM-LINE SPEAKER SYSTEM**, fully finished walnut veneered cabinet for faster construction. Special 12" bass unit and 4" mid/high frequency unit. Range 30-17,000 c/s. Size 26" x 17" only 7½" deep. Modern attractive styling. Excellent value. Kit **£19.10.0** Assembled **£24.0.0**



Berkeley

COTSWOLD SPEAKER SYSTEMS. Outstanding performance for price. MFS: Size 36" x 16½" x 14" deep. Kit **£25.12.0** Assembled **£33.17.0** STANDARD: Size 26" x 23" x 14½" deep. Kit **£25.12.0** Assembled **£33.17.0**



Send for this Catalogue it's FREE

28 pages, many models in colour... Hi-Fi Audio, Radio... Amateur gear, Britain's largest selection of top quality, electronic kits.

Mail for your own copy Today! →

Deferred terms available in UK over £10
Prices quoted are Mail Order prices, retail prices slightly higher.


"AMATEUR" EQUIPMENT

80-10m TRANSMITTER. DX-40U. Power inputs 75W. C.W., 60W peak CC phone. Output 40W to aerial. Provision for VFO. Kit **£29.19.0** Assembled **£41.8.0**



DX-40U

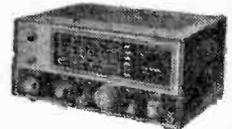AMATEUR BANDS RECEIVER Model RA-1. To cover all the Amateur Bands from 160-10 metres. Many special features, including: half-lattice crystal filter; 8 valves; signal strength "S" meter; tuned R.F. Amp. stage. Kit **£39.6.6** Assembled **£52.10.0**



RA-1

160-10M TRANSMITTER. Model DX-100U. Careful design has achieved high performance and stability. Completely self-contained. Kit **£81.10.0** Assembled **£106.15.0**

COMMUNICATIONS TYPE RECEIVER. Model RG-1. A high performance, low cost receiver for the discriminating listener. Frequency coverage: 600 kc/s-1.5 Mc/s and 1.7 Mc/s-32 Mc/s. Kit **£39.16.0** Assembled **£53.0.0**



GD-1U

GRID DIP METER Model GD-1U. Covers 1-8 to 230 Mc/s in 5 bands. Can be used as absorption wave-meter. Aligns IF stages traps, filters etc., etc. Compact size... can be held in one hand. Kit **£11.9.6**. Assembled **£14.9.6**. Coil set for ext. freq. to 350 kc/s 17/6 extra.

OUTSTANDING "AMATEUR" EQUIPMENT. Note lower prices. A wide range of American Amateur SSB equipment is now available in the U.K. Why not send for full details of range, for example:

FILTER TYPE SSB TRANSCEIVERS
Models for 80, 40 or 20 metre bands.
Model HW-12A (80M) **£53.10.0** Kit.
Model HW-32A (20M) **£53.10.0** Kit price inc. duty, etc.



80M Transceiver HW-12A

To DAYSTROM LTD, Gloucester. Tel. Glos. 20217.
Please send me FREE CATALOGUE YES/NO
Further details of model(s)

NAME

ADDRESS

DEPT. P.W.6


HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1

- Peak output in excess of 1 1/2 watts.
- All standard British components.
- Built on printed circuit board 6 x 3 in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 8 ohm and 15 ohm speakers.
- Transistors (GET 114 or 81 Mullard OC81D and matched pair of OC81 o/p).
- 9 volt operation.
- Everything supplied, wire, battery clips, solder, etc.
- Comprehensive easy to follow instructions and circuit diagram 1/6. (Free with Kit). All parts sold separately.

SPECIAL PRICE 45/- P. & P. 3/-.
Also ready built and tested, 52/6. P. & P. 3/-.
A pair of TA1s are ideal for stereo

STEREO AMPLIFIER

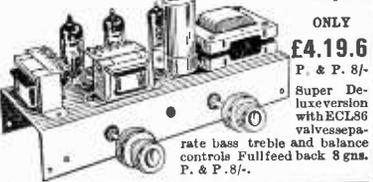Incorporating 2 ECL86s and 1 EZ80, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.



ONLY **£4.19.6** P. & P. 8/-
Super Deluxe version with ECL86 valves separate bass treble and balance controls Full feed back 8 gms. P. & P. 8/-.

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 5 1/2 x 2 1/2 in.). ● 3 pre-aligned I.F. transformers ● High-gain Ferrite Rod aerial. ● All First-grade transistors ● Car aerial winding. ● Push-pull output ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time ONLY £4.5.0. P. & P. 2/6 (Circuit diagram 2/-, Free with set of parts.)

35 OHM SPEAKERS

Suitable for use with above. 2in. Goodmans' Ideal replacement for most pocket portables, 8/6; 3 1/2in. 12/6; 7 x 4in. 21/-; P. & P. 2/- per speaker.

PORTABLE CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2 in. Suitable for above using 3 1/2 in. speaker, 25/-, P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers one oscillator coil one driver transformer and wound Ferrite aerial (med. long and car aerial coupling), 52/6 complete post 2/-. 6 transistor printed circuit board to match 8/6. Post 1/-. Circuit diagram 1/6 extra.

BRAND NEW TRANSISTOR BARGAINS

GET 15 (Matched Pair) 15/-; V15/10p, 10/-; OC71 5/-; OC76 6/-; AF117 7/6.
Set of Mullard 6 transistors OC44, 2-OC45 OC81D matched pair OC81 25/-, ORP12 Cadmium Sulphide Cell 10/6.

EDISWAN MAZDA

PXA101 6/6; XA103 6/6.
R.F.1. Pack: 1-PXA102 Mixer; 2-PXA101 I.F. Amp. (Equip. OC44 and OC45) 10/6
R.F. 2 Pack: 2-PXA101 I.F. 1-PXA102 Osc. 1-PXA102 Mixer 12/6
L.F.6 Pack: Consisting of PXB113 Driver Matched pair. PX171 mounted complete with heat sinks (Equip. OC81D and OC81) 12/6
ALL TRANSISTORS POST FREE.

LATEST COLLARO MAGNAVOX 383 TAPE DECK DE LUXE. Three speeds, 2 tracks, takes up to 7in. spools. 10 gms. plus 7/6 Carr. & ins. on each (Tapes extra).

PORTABLE TAPE RECORDER CASE

Beautifully made and expensively finished in dark grey heavy grade rexine. Satin Chrome metal grille front and chrome fittings. Speaker aperture 9" x 4". Overall size 16 1/2" w. x 15" d. x 7 1/4" h. Will take any standard tape deck or single record player. Limited number only. Worth at least 25. OUR PRICE 49/6. P. & P. 8/6. Brand new and unused.

ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity, 18/6. P. & P. 1/6
ACOS HIGH IMPEDANCE CRYSTAL STICK MIKES. Listed at 42/-. OUR PRICE 21/- P. & P. 1/6.

Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser. 35/- P. & P. 3/-.

NEON A.C. MAINS INDICATOR. For panel mounting, cut out size 1 1/2 x 1/2 in. deep inc. terminal. White case with lens giving brighter light. For mains 200/250v. 2/6 each. P. & P. 6d. (6 or more post free).

BRAND NEW T.V. U.H.F. TUNER AND SOUND AND VISION I.F. PANEL

By world famous maker. Suitable for use in conversion of TV sets to BBC2 (625 line reception). OFFERED (less valves) AT THE BARGAIN PRICE OF ONLY 27/6. Post paid. (The components are worth far more than our price for the complete unit and due to the very high value we regret that no correspondence can be entered into regarding this item).

QUALITY RECORD PLAYER AMPLIFIER

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC85, EL54, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3in. d. x 6in. h. Ready built and tested. PRICE 69/6. P. & P. 6/-.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 89/6. P. & P. 7/6.

DE-LUXE QUALITY PORTABLE R/P CABINET

Uncut motor board size 14 1/2 x 12in. Clearance 2in below. 5 1/2in. above. Will take above amplifier and any B.S.R. or Garrard Autochanger or Single Player Unit (except AT60 and 8P25) Size 18 x 15 x 8in. Price 23.9.6. Carr. 9/6.

4-SPEED PLAYER UNIT BARGAINS

All brand new in maker's original packing.

SINGLE PLAYERS	
B.S.R. TU/12	Carr. 5/6.
GARRARD 8P25 De Luxe	£12.0.0 Carr. 5/6.
B.S.R. GU7 with unit mounted pickup arm.	£4.16.8 Carr. 5/6.

AUTO CHANGERS

Latest B.S.R. UA25 Super 8lin.	£6. 2.6
GARRARD 1000 with special Hi-Fi cartridge	£6.16.6
GARRARD 2000	£7.10.0
GARRARD 3000	£8.15.0
GARRARD AT90	£10.10.0

Carr. 6/6 on each.
All the above units are complete with t/o mono head and sapphire stylus or can be supplied with compatible stereo head for 12/6 extra.

BRAND NEW CARTRIDGE BARGAINS!

ACOS GP 89/1 MONO CARTRIDGE. For E.P. and L.P. Complete with stylus. Only 18/6. P. & P. 1/-.

BRAND NEW 3 OHM LOUDSPEAKERS

5in., 12/6; 6 1/2in. 15/-; 8in. 22/6; 10in. 27/6; 7in. x 4in. 16/-; 10in. x 6in. 27/6.
E.M.I. 8in. x 6in. with high flux magnet, 21/-.
E.M.I. 1 1/2 x 3in. with high flux ceramic magnet, 42/- (15 ohm 45/-). P. & P. 5/6. 2/-, 6/- & 8in. 2/6, 10 & 12in. 3/6 per speaker.

SPECIAL OFFER!

Limited number of 12in. 10 watt "R.A." Speakers: 3 ohm 25/-; 15 ohm 27/6. P. & P. 3/6.

E.M.I. PLASTIC CONED TWEETERS. 2 1/2in. 3 ohm. Limited number 12/6 each. P. & P. 1/6.

BRAND NEW HEAVY DUTY 12in. SPEAKERS. Response 45 c/s - 15 Kc/s. 1 1/2in. voice coil. Available in 3 or 15 ohms. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE at 89/6. P. & P. 5/6. Also 25 watt Guitar Model available at 25.5.0. And 35 watt Guitar Model 28.8.0.

VYNAIR AND REXINE SPEAKER AND CABINET FABRICS.

Approx. 5 1/2in. wide. Usually 25/- yard. Our PRICE 13/6 per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

SPECIAL OFFER!

GENUINE HIGH QUALITY TYGAN FABRIC. 48in. wide. Our price 10/- per foot run. P. & P. 1/6. 30/- per yard run. P. & P. 2/6.

SEMI SHROUDED DROP THERO MAINS TRANSFORMER. Tapped pri. 270/350 v. Sec. 300-0-300 v. at 110ma. and 6.3 v. at 3 amp. (E/8 screen). Stack size 3 1/2 x 3 1/2 x 1 1/2 in. 30/- P. & P. 3/6.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240 v. Sec. 9-0-9 v. at 500 mA. 11/- P. & P. 2/6.

MAINS TRANSFORMER. For transistor power supplies. Tapped pri. 200/250 v. Sec. 40-0-40 at 1 amp (with electrostatic screen) and 6.3 v. at 5 amp for dial lamps etc. Drop thro mounting. Stack size 1 1/2 x 3 1/2 x 3 1/2 in. 27/6. P. & P. 4/6.


MATCHED PAIR OF 2 1/2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stack size 1 1/2 x 1 1/2 x 1 1/2 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/- P. & P.

7-10 watt OUTPUT TRANSFORMERS to match pair of ECL 86's in push-pull to 3 ohm output. ONLY 11/- P. & P. 2/6.

MINIATURE PRECISION AIR-SPACED TWO GANG TUNING CONDENSER. 1.76 + 176 p.F. size 1 1/2" w. x 1/2" d. x 1 1/2" with vanes open. Built in trimmers 5/- P. & P. 1/6.

TWIN TELESCOPIC AERIAL. Comprising two 3-section heavily chromed rods. Closed 12in. each extending to 32in. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, coax lead and plug. Suitable for F.M. or TV. 12/6. P. & P. 2/6.

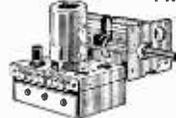SPECIAL HARVERSON OFFER! FM/AM TUNER HEAD



Beautifully designed and precision engineered by Dornier and Wadsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM connection. Prealigned FM section covers 86-102 Mc/s. I.F. output 10.7 Mc/s. Complete with EOC85 (8119) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/6. Order quickly! Limited number also available with precision geared 3:1 reduction drive, 30/- P. & P. 3/6.

MATCHED PAIR AM/FM I.F.'s Comprising 1st I.F. and 2nd I.F. discriminator (455kc/s 10.7Mc/s). Size 1 x 1 1/2 x 2 1/2 in. high. Will match above tuner head. 11/- pair. P. & P. 2/6.

SPECIAL PURCHASE! TURRET TUNERS

By famous maker. Brand new and unused. Complete with PCC84 and PCP80 valves 34-38 Mc/s I.F. Blecuits for Channel 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 25/- each. P. & P. 3/6.

GORLER F.M. TUNER HEAD

88-100 Mc/s, 10.7 Mc/s I.F. 15/- plus 2/- P. & P. (ECC85 valves 8/6 extra).

3-VALVE AUDIO AMPLIFIER MODEL HA34



Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates ECC83, EL54, EZ80 valves. Heavy duty, double wound mains transformer and output transformer and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, etc., wired and tested for only **£4.5.0** P. & P. 6/-

HSL 'FOUR' AMPLIFIER KIT

A.C. Mains 200/250v., 4 watt, using ECC83, EL84, EZ80 valves.




● Heavy duty double-wound mains transformer with electrostatic screen. ● Separate Bass, Treble and Volume controls, giving fully variable boost and out with minimum insertion loss. ● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ● Suitable for use with guitar microphone or record player. ● Provision for remote mounting of controls or direct on chassis. ● Chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in. ● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves output transformer (3 ohms only) screened lead, wire, nuts, bolts solder etc. (No extras to buy). PRICE 79/6. P. & P. 6/-.

Comprehensive circuit diagram, practical layout and parts list 2/6 (free with kit).

This kit although similar in appearance to HA34 employs entirely different and advanced circuitry.

10/14 WATT HI-FI AMPLIFIER KIT

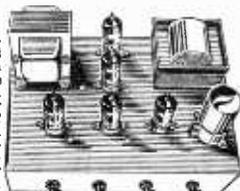

A Stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-16 Ohm speaker and 3 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 1/6 (Free with parts) All parts sold separately. ONLY 27.9.6 P. & P. 8/6. Also available ready built and tested complete with std. input sockets, 23.5.0. P. & P. 8/6. Carrying case for above 28/6 P. & P. 7/6.

Open all day Saturday
Early closing Wed. 1 p.m.
A few missions from South W imbeddon
Tube Stations.

HARVERSON SURPLUS CO. LTD.
170 HIGH ST., MERTON, S.W.19 CHerrywood 3985
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES
QUOTED APPLY TO U.K. ONLY
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.

Household Heating Supplies LTD brings central heating price down

you save £150 on D.I.Y installations!

**OIL —
GAS —
SOLID FUEL**



Powell Duffryn
G45 Gas Boiler

You can do better than buy Central Heating at "frozen" prices—you can save at least £150 by doing-it-yourself—and you get FREE advice before and during installation.

Free delivery to your home. NO DEPOSIT—5 YEARS TO PAY. Branches at Croydon, Wood Green, Tottenham, Bedford, Manchester and Leicester.



To: Household Heating Supplies Ltd.
7 Ilford Lane, Ilford, Essex ILF 5098/9
Please send further details.

Name

Address

Telephone P.W.6.67

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- Institution of Electronics & Radio Engineers (Brit.I.R.E.)
- C. & G. Telecommunication Techns' Certs.
- C. & G. Supplementary Studies
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, signal generator and multimeter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

6.67

INTERNATIONAL CORRESPONDENCE SCHOOLS

BRADFORD Tel. 25349
10 North Parade. (Half-day Wed.)
BRISTOL 14 Lower Castle
St. (Half-day Wed.) Tel. 22904
BIRMINGHAM 30/31 Gt.
Western Arcade, opp. Snow Hill
Station. CENTRAL 1279. No half-day
DERBY 26 Osleston Rd.,
The Spot (Half-day Wed.)
Tel. 41361

DARLINGTON 13 Post
House Wynd (Half-day Wed.)
EDINBURGH 133 Leith
Street (Half-day Wed.)
Tel.: Waverley 5766
GLASGOW 326 Argyle St.
(No half-day) Tel.: CITY 4158
403 Sauchiehall St. Tel.: 332-1572
HULL 91 Paragon Street,
(Half-day Thursday) Tel.: 20505

R.S.C.

HI-FI CENTRES LTD.

MAIL ORDERS TO: 102
Menconner Lane, Bram-
ley, Leeds 13. No C.O.D.
under 21. Terms C.V.O. 4/5
extra under £2. 5/9 extra
under £5. Trade supplies,
S.A.E. with catalogue now

LEICESTER 32 High Street
(Half-day Thurs.) Tel.: 56420
LEEDS 5-7 County (Mecca)
Arcade, Briggate (No half-day)
Tel.: 28252
LIVERPOOL 73 Dale St.
(No half-day) Tel.: Central 3573
LONDON 238 Edgware Road,
W2 (Half-day Thurs.) Tel.: PAD
1629. 96 High Holborn, WC1
Tel.: HOL 9874 (Half-day Sat.)

MANCHESTER (No half-
day) 60A-60B Oldham St.
Tel.: CENTRAL 2778
MIDDLESBROUGH
106 Newport Road (Half-day
Wednesday) Tel.: 47096
NEWCASTLE UPON TYNE
41 Blakett Street Opp Fenwicks
Store (Half-day Wed.) Tel.: 21469
SHEFFIELD 13 Exchange
Street, Castle Market Bldgs.
(Half-day Thursday) Tel.: 20716



66% RECORD PLAYING UNITS

Ready for plugging in to Amplifier or Tape Recorder.
RP2 Consisting of Garrard SP25 fitted Goldring
CS90 high compliance ceramic Stereo/Mono
plinth with diamond stylus above. Only **19½ Gns.**
RP3 As above but with Goldring Lenco GL68 Trans-
cription unit and CS90 Cartridge. Normally
over £33. Terms available
only **26½ Gns.**
Carr. 15/-

TAPE AMPLIFIERS 4-5 Watts Output
Suitable for use with Magnavox 363 Decks. Switched
equalization 20-2500 Hz A.C.
Originally 18 Gns. Size 11" x 21" x 6" **£6.19.11**

AUDIOTRINE HI-FI SPEAKER SYSTEMS
Consisting of matched 12in. 1200 line,
15 ohm high quality speaker; cross-over
unit and Tweeter. Smooth response
and extended frequency range ensure
surprisingly realistic reproduction.
Standard 10 watt rating. Or
Senior 20 watt rating. **5 Gns.**
122/10 speaker 7 Gns. Carr. 8/9. Carr. 6/9



please, HI-FI CATALOGUE NOW
AVAILABLE price 3/3 post paid.
Personal shoppers welcome. Open all day
Sats. except High Holborn branch.

ALL LEADING MAKES OF HI-FI
EQUIPMENT STOCKED Cash or Terms
Full range HI-FI Furniture

HI-FI LOUSPEAKER ENCLOSURES
All types of pleasing modern design
acoustically lined and ported and
beautifully finished in light Teak or
Walnut veneer. Credit terms available.
JES. Size 16 x 11 x 8in. Gives
pleasing results with 8in. Hi- **£4.15.0**
F1 speaker.

SE8. For optimum performance
with any Hi-Fi 8in.
speaker. Size 12 x **£5.19.9**
15 x 9in. Carr. 7/6

SE10. For 10in. Hi-Fi speaker
with provision for tweeter.
Size 24 x 15 x 9in. **£6.19.9**
Carr. 10/-

SE12. For outstanding performance with
any 12in. Hi-Fi speaker. **8 Gns.**
Carr. 10/-

NEW RANGE OF LINEAR
HI-FI UNITS STOCKED

HIGH FIDELITY LOUSPEAKER UNITS
Cabinets of latest styling Satin Teak or Walnut,
acoustically lined (and ported where appropriate).
Credit Terms available on all units.

MINI 8 8 WATT rating, 3 or 15 ohm. Frequency
response 50-13,000 c.p.s. Specially designed
high flux 5in. speaker with low
fundamental resonance. Handsome
Teak veneered cabinet. **£6/19/11**
8 x 8 x 7in. Carr. 7/6

The DORSET Size 16 x 11 x 8in.
Response 45-18,000 c.p.s. Rating 10
watts. Fitted Audiotrine HF811D
speaker. Impedance 3 or **£7/15/0**
15 ohms. Carr. 7/6

The DORCHESTER Size 24 x 15 x 10in. Fitted
Audiotrine HF101D Speaker. Rating 12 watts.
Impedance 3 or 15 ohms. Frequency **12½ Gns.**
Response 30-20,000 c.p.s. Carr. 15/-

The GLOUCESTER Size 24 x 20 x 8in.
12in. High flux
12,000 line speaker.
Cross-over unit
and 11 watt speaker.
Rating 10 watts.
Smooth response
40-20,000 c.p.s. Im-
pedance 15 ohms.
Carr. 15/- **12 Gns.**

The BRONTE Size 22 x 15 x 9in.
Fitted Wharfedale
Super 8 RSDD or
Audiotrine HF
811D Speaker with
Roll surround and
dual cone. Rating
6/10 watts. Im-
pedance 3 or 15 ohms.
Carr. 15/- **12½ Gns.**

Tweeters R.A. 3 ohm or 15 ohm 25/9

15 watt HI-FI TRANSISTORISED AMPLIFIER TYPE A15

with integral pre-
amp tone control
stages. Output for 3,
7.5 and 15 ohm spkrs.
Kit includes Printed
Circuit and all parts
type semi-conductors. **£4.12.9** Post
Heat sink and full wir-
ing instructions or with printed circuit
fully wired and tested 21/- extra. Frequency
Response: ±1dB 20-20,000 c.p.s. Harmonic
Distortion: 0.1%. Hum and Noise:
-30dB. Sensitivity: 2mV. Bass Control:
+8dB to -14dB at 40 c.p.s. Treble Con-
trol: +8dB to -13dB at 10 Kc/s. Will
operate from batteries giving 24v. Suit-
able Power Pack Kit 47/9 or ready built 69/9




R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER

A complete set of parts for the construction of a unit giving 5 watts high quality
output on each channel (total 10 watts). Sensitivity is 50 millivolts. Suitable
all crystal or ceramic stereo heads. Ganged Bass and Treble Controls. Provision
is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83,
ECC83, EL84, EL84, EZ81. Outputs for 2-3 ohm speakers. Point to point wiring
diagrams and instructions supplied. Send S.A.E. for leaflet.
Or supplied factory assembled with 12 months guarantee for 11 gns. **£8.15.0**
Carr. 11/6

R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER

PROVIDING 10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON
EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE.
Employing valves ECC83, ECC83, ECL86, ECL86, ECL86, EZ81. Frequency
Response: ±2dB 20-20,000 c.p.s. HUM Level: 65dB down. Sensitivity: 5 millivolts
maximum. Harmonic Distortion: (each channel): 0.2%. ★Four-position tone
compensation and Input Selector Switch. ★Stereo/Mono switch.
★Drift-free reception. ★Output meter. ★Neon panel indicator. ★Handsome Perspex Frontplate.
★Separate Bass "Lift" and "Cut" and treble "Lift" and "Cut" controls. Output transformers are high-
quality sectionally wound to required specification. Output matching for 3 and 15 ohm spkrs. on 14 Gns.
each channel. Complete set of parts, point-to-point wiring diagrams and instructions. Carr. 12/6
Or factory assembled, tested and supplied with our usual 12 months guarantee. Carr. 12/6
Or Deposit £3 and 9 monthly payments 43/2 (Total £22.4.6). Send S.A.E. for leaflet.

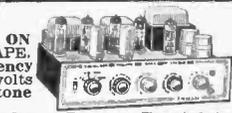

R.S.C. TFM1 TRANSISTORISED VHF/FM RADIO TUNER

Total cost of parts
with detailed wiring
diagrams and instruc-
tions. **12½ Gns.**
Carr. 10/-
Or factory built
15 Gns. Or in Teak
finished cabinet, as
illustrated 19 gns.
Terms: Deposit £5
and 9 monthly pay-
ments 39/-.
Total £22.11.0.



★ High-sensitivity ★ 200-250v. A.C. Mains
operation. ★ Sharp A.M. Rejection.
★ Drift-free reception. ★ Output meter
for any amplifier (approx. 500 m.v.).
★ Simple alignment (instructions). ★ Output
available for feeding tuning meter.
★ Output for feeding Stereo Multiplexer.
★ Tuner head using Silicon Planar Tran-
sistors. ★ Designed for standard 80 ohm co-axial input.
Made to visually match our Super 15 and 30 amplifiers and of the same high
standard of performance and reliability. The pre-wired tuning head facili-
tates speed and simplicity of construction. Printed circuitry. Only first grade
transistors and components used. Our latest product giving you the best at
half the cost of comparable units. Stereo Multiplexer available.

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS

Heavy cast
construction.
Latest high efficiency ceramic magnets.
Dual Cone for extended frequency range.
Plastic treated surround giving
low fundamental resonance. Response
3 or 15 ohms. c.p.s. Impedance
3 or 15 ohms. Carr. 5/6.

HF811D 8in. 10 WATT 4 Gns.
HF101D 10in. 12 WATT 5 Gns.
HF100D 10in. 15 WATT 25.15.0
HF121D 12in. 20 WATT 26.15.0
HF127D 12in. 30 WATT 9 Gns.




R.S.C. SUPER 15 HI-FI AMPLIFIER

FULLY TRANSISTORISED 200/250v. A.C. Mains.
OUTPUT 10 WATTS R.M.S. cont. into 15 ohms.
15 WATTS R.M.S. cont. into 9-4 ohms.
Maximum instantaneous Peak power output 23 watts.
PRINTED CIRCUIT CONSTRUCTION.
LATEST MULLARD TRANSISTORS. AD149, AD149,
OC127Z, OC81Z, OC44, OC44, OC81Z, OC44, AC107.
5 POSITION INPUT SELECTOR SWITCH
EQUALISATION to Standard R.I.A.A. and C.C.I.R.
Characteristics for Gram and Tape Heads.
FULL TAPE MONITORING FACILITIES.
SENSITIVITIES: Magnetic P.U. 4 mV. Crystal or
Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head
2.5 mV. Radio/Aux. or Ceramic P.U. 110 mV.
FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s.
TREBLE CONTROL: +15dB to -14dB at 10 Kc/s.
BASS CONTROL: +12dB to -15dB at 50 c/s. HUM LEVEL: -75dB.
HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.25%.
NEGATIVE FEEDBACK. 52dB.
Complete kit of parts with full constructional details and
point to point wiring diagrams. Carr. 11/-
Supplied factory built 15 Gns. Carr. 12/6. Terms: Deposit 49/- and 9
monthly payments 33/9 (Total £17.12.9). Or fitted in beautiful Walnut or
Teak veneered cabinet as illustrated. 11 Gns. extra.
ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND
SUPPLIED BY LEADING BRITISH MANUFACTURERS.

R.S.C. SUPER 30 STEREO AMPLIFIER

TECHNICAL
SPECIFICATIONS COMPARE MORE
THAN FAVOURABLY WITH SIMILAR
AMPLIFIERS AT TWICE THE COST

A DUAL CHANNEL VERSION OF THE SUPER
15. Employing Twin Printed Circuits. Close tolerance
Ganged Pots. Matched Components.
CROSS TALK: -52dB at 1,000 c.p.s.
CONTROLS: 5 position Input Selector, Bass Control,
Treble Control, Volume Control, Balance Control, Stereo/
Mono Switch, Tape Monitor Switch, Mains Switch.
INPUT SOCKETS (Matched Pairs). (1) Magnetic P.U.
(2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/
Microphone. Operation of the Input Selector Switch
assures appropriate equalisation.
Rigid 18 s.w.g. Chassis. Size approx. 12in. Wide, 3in. High
and 8in. Deep. Neon Panel Indicator. Attractive Facia
Ganging and Balance Control, apply also to Super 15.
THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH
ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic,
Magnetic, Moving Coil, Ribbon) CURRENTLY AVAILABLE,
SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY
USING WITH FIRST RATE ANCILLARY
EQUIPMENT. All required parts, point to point wiring
diagrams and detailed instructions. Carr. 13/9
Our factory built 25½ Gns. or deposit 83/9 and 9 monthly payments 56/9
(Total £23.14.6). Fitted cabinet as Super 15 29½ Gns. Carr. 15/- or Deposit
£4.14.9 and 9 mthly paymts 65/10 (Total £24.7.3). Send S.A.E. for leaflet.

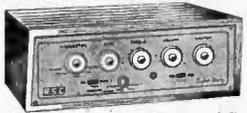

11 Gns.

18½ Gns.

AUDIOTRINE HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST: CAN BE ASSEMBLED IN AN HOUR. ONLY 4 PAIRS OF SOLDERED JOINTS PLUS MAINS. Incorporating the latest Magnavox Tape Deck. The Audiotrine High Quality Tape Amplifier with switched equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a handsome Portable Cabinet of 1st class styling finished dark grey leathercloth. Size 14 1/2 x 8 1/2 in. and circuit. Purchased separately would total approx. £34. Performance equal to units in the £50-£60 class. Deposit 4 gns. and 9 monthly payments 59/6 (Total 291 gns.) 4 Track Model 3 gns. extra. Carr. 19/6



26 1/2 Gns.

LINEAR TAPE PRE-AMPLIFIER. Type LP/1 Switched Equalisation. Positions for Recording at 1 1/2 in., 3 1/2 in., 7 1/2 in. per sec., and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier suitable most Tape Decks. Terms available. 10 1/2 Gns.

R.S.C. 4/5 watt A5 HIGH GAIN AMPLIFIER
A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P.U. heads and practically all "mikes". Separate Bass and Treble controls giving "lift" and "cut". Hum level 71dB down. Negative Feedback 15dB. Reserve power supply 300v 25 m.a., 6.3v 1.5 a. for Radio Tuner or Tape Pre-amp. For A.C. mains 200-250v. Speaker output 3 ohms. Complete in every detail with fully punched enamelled chassis, point-to-point wiring diagrams and instructions. Or assembled ready for use 6 gns. plus 5/9 carr. £4.17.9

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp/Tone Control Stages. Performance figures equal to most expensive amplifiers available. Hum level -70dB. Frequency response +3dB 30-20,000 c/s. Specially designed sectionally wound ultra linear output transformer with 1st, 2nd, 3rd, 4th, 5th, 6th, 7th, 8th, 9th, 10th, 11th, 12th, 13th, 14th, 15th, 16th, 17th, 18th, 19th, 20th, 21st, 22nd, 23rd, 24th, 25th, 26th, 27th, 28th, 29th, 30th, 31st, 32nd, 33rd, 34th, 35th, 36th, 37th, 38th, 39th, 40th, 41st, 42nd, 43rd, 44th, 45th, 46th, 47th, 48th, 49th, 50th, 51st, 52nd, 53rd, 54th, 55th, 56th, 57th, 58th, 59th, 60th, 61st, 62nd, 63rd, 64th, 65th, 66th, 67th, 68th, 69th, 70th, 71st, 72nd, 73rd, 74th, 75th, 76th, 77th, 78th, 79th, 80th, 81st, 82nd, 83rd, 84th, 85th, 86th, 87th, 88th, 89th, 90th, 91st, 92nd, 93rd, 94th, 95th, 96th, 97th, 98th, 99th, 100th, 101st, 102nd, 103rd, 104th, 105th, 106th, 107th, 108th, 109th, 110th, 111th, 112th, 113th, 114th, 115th, 116th, 117th, 118th, 119th, 120th, 121st, 122nd, 123rd, 124th, 125th, 126th, 127th, 128th, 129th, 130th, 131st, 132nd, 133rd, 134th, 135th, 136th, 137th, 138th, 139th, 140th, 141st, 142nd, 143rd, 144th, 145th, 146th, 147th, 148th, 149th, 150th, 151st, 152nd, 153rd, 154th, 155th, 156th, 157th, 158th, 159th, 160th, 161st, 162nd, 163rd, 164th, 165th, 166th, 167th, 168th, 169th, 170th, 171st, 172nd, 173rd, 174th, 175th, 176th, 177th, 178th, 179th, 180th, 181st, 182nd, 183rd, 184th, 185th, 186th, 187th, 188th, 189th, 190th, 191st, 192nd, 193rd, 194th, 195th, 196th, 197th, 198th, 199th, 200th, 201st, 202nd, 203rd, 204th, 205th, 206th, 207th, 208th, 209th, 210th, 211st, 212nd, 213th, 214th, 215th, 216th, 217th, 218th, 219th, 220th, 221st, 222nd, 223rd, 224th, 225th, 226th, 227th, 228th, 229th, 230th, 231st, 232nd, 233rd, 234th, 235th, 236th, 237th, 238th, 239th, 240th, 241st, 242nd, 243rd, 244th, 245th, 246th, 247th, 248th, 249th, 250th, 251st, 252nd, 253rd, 254th, 255th, 256th, 257th, 258th, 259th, 260th, 261st, 262nd, 263rd, 264th, 265th, 266th, 267th, 268th, 269th, 270th, 271st, 272nd, 273rd, 274th, 275th, 276th, 277th, 278th, 279th, 280th, 281st, 282nd, 283rd, 284th, 285th, 286th, 287th, 288th, 289th, 290th, 291st, 292nd, 293rd, 294th, 295th, 296th, 297th, 298th, 299th, 300th, 301st, 302nd, 303rd, 304th, 305th, 306th, 307th, 308th, 309th, 310th, 311st, 312nd, 313th, 314th, 315th, 316th, 317th, 318th, 319th, 320th, 321st, 322nd, 323rd, 324th, 325th, 326th, 327th, 328th, 329th, 330th, 331st, 332nd, 333rd, 334th, 335th, 336th, 337th, 338th, 339th, 340th, 341st, 342nd, 343rd, 344th, 345th, 346th, 347th, 348th, 349th, 350th, 351st, 352nd, 353rd, 354th, 355th, 356th, 357th, 358th, 359th, 360th, 361st, 362nd, 363rd, 364th, 365th, 366th, 367th, 368th, 369th, 370th, 371st, 372nd, 373rd, 374th, 375th, 376th, 377th, 378th, 379th, 380th, 381st, 382nd, 383rd, 384th, 385th, 386th, 387th, 388th, 389th, 390th, 391st, 392nd, 393rd, 394th, 395th, 396th, 397th, 398th, 399th, 400th, 401st, 402nd, 403rd, 404th, 405th, 406th, 407th, 408th, 409th, 410th, 411st, 412nd, 413th, 414th, 415th, 416th, 417th, 418th, 419th, 420th, 421st, 422nd, 423rd, 424th, 425th, 426th, 427th, 428th, 429th, 430th, 431st, 432nd, 433rd, 434th, 435th, 436th, 437th, 438th, 439th, 440th, 441st, 442nd, 443rd, 444th, 445th, 446th, 447th, 448th, 449th, 450th, 451st, 452nd, 453rd, 454th, 455th, 456th, 457th, 458th, 459th, 460th, 461st, 462nd, 463rd, 464th, 465th, 466th, 467th, 468th, 469th, 470th, 471st, 472nd, 473rd, 474th, 475th, 476th, 477th, 478th, 479th, 480th, 481st, 482nd, 483rd, 484th, 485th, 486th, 487th, 488th, 489th, 490th, 491st, 492nd, 493rd, 494th, 495th, 496th, 497th, 498th, 499th, 500th, 501st, 502nd, 503rd, 504th, 505th, 506th, 507th, 508th, 509th, 510th, 511st, 512nd, 513th, 514th, 515th, 516th, 517th, 518th, 519th, 520th, 521st, 522nd, 523rd, 524th, 525th, 526th, 527th, 528th, 529th, 530th, 531st, 532nd, 533rd, 534th, 535th, 536th, 537th, 538th, 539th, 540th, 541st, 542nd, 543rd, 544th, 545th, 546th, 547th, 548th, 549th, 550th, 551st, 552nd, 553rd, 554th, 555th, 556th, 557th, 558th, 559th, 560th, 561st, 562nd, 563rd, 564th, 565th, 566th, 567th, 568th, 569th, 570th, 571st, 572nd, 573rd, 574th, 575th, 576th, 577th, 578th, 579th, 580th, 581st, 582nd, 583rd, 584th, 585th, 586th, 587th, 588th, 589th, 590th, 591st, 592nd, 593rd, 594th, 595th, 596th, 597th, 598th, 599th, 600th, 601st, 602nd, 603rd, 604th, 605th, 606th, 607th, 608th, 609th, 610th, 611st, 612nd, 613th, 614th, 615th, 616th, 617th, 618th, 619th, 620th, 621st, 622nd, 623rd, 624th, 625th, 626th, 627th, 628th, 629th, 630th, 631st, 632nd, 633rd, 634th, 635th, 636th, 637th, 638th, 639th, 640th, 641st, 642nd, 643rd, 644th, 645th, 646th, 647th, 648th, 649th, 650th, 651st, 652nd, 653rd, 654th, 655th, 656th, 657th, 658th, 659th, 660th, 661st, 662nd, 663rd, 664th, 665th, 666th, 667th, 668th, 669th, 670th, 671st, 672nd, 673rd, 674th, 675th, 676th, 677th, 678th, 679th, 680th, 681st, 682nd, 683rd, 684th, 685th, 686th, 687th, 688th, 689th, 690th, 691st, 692nd, 693rd, 694th, 695th, 696th, 697th, 698th, 699th, 700th, 701st, 702nd, 703rd, 704th, 705th, 706th, 707th, 708th, 709th, 710th, 711st, 712nd, 713th, 714th, 715th, 716th, 717th, 718th, 719th, 720th, 721st, 722nd, 723rd, 724th, 725th, 726th, 727th, 728th, 729th, 730th, 731st, 732nd, 733rd, 734th, 735th, 736th, 737th, 738th, 739th, 740th, 741st, 742nd, 743rd, 744th, 745th, 746th, 747th, 748th, 749th, 750th, 751st, 752nd, 753rd, 754th, 755th, 756th, 757th, 758th, 759th, 760th, 761st, 762nd, 763rd, 764th, 765th, 766th, 767th, 768th, 769th, 770th, 771st, 772nd, 773rd, 774th, 775th, 776th, 777th, 778th, 779th, 780th, 781st, 782nd, 783rd, 784th, 785th, 786th, 787th, 788th, 789th, 790th, 791st, 792nd, 793rd, 794th, 795th, 796th, 797th, 798th, 799th, 800th, 801st, 802nd, 803rd, 804th, 805th, 806th, 807th, 808th, 809th, 810th, 811st, 812nd, 813th, 814th, 815th, 816th, 817th, 818th, 819th, 820th, 821st, 822nd, 823rd, 824th, 825th, 826th, 827th, 828th, 829th, 830th, 831st, 832nd, 833rd, 834th, 835th, 836th, 837th, 838th, 839th, 840th, 841st, 842nd, 843rd, 844th, 845th, 846th, 847th, 848th, 849th, 850th, 851st, 852nd, 853rd, 854th, 855th, 856th, 857th, 858th, 859th, 860th, 861st, 862nd, 863rd, 864th, 865th, 866th, 867th, 868th, 869th, 870th, 871st, 872nd, 873rd, 874th, 875th, 876th, 877th, 878th, 879th, 880th, 881st, 882nd, 883rd, 884th, 885th, 886th, 887th, 888th, 889th, 890th, 891st, 892nd, 893rd, 894th, 895th, 896th, 897th, 898th, 899th, 900th, 901st, 902nd, 903rd, 904th, 905th, 906th, 907th, 908th, 909th, 910th, 911st, 912nd, 913th, 914th, 915th, 916th, 917th, 918th, 919th, 920th, 921st, 922nd, 923rd, 924th, 925th, 926th, 927th, 928th, 929th, 930th, 931st, 932nd, 933rd, 934th, 935th, 936th, 937th, 938th, 939th, 940th, 941st, 942nd, 943rd, 944th, 945th, 946th, 947th, 948th, 949th, 950th, 951st, 952nd, 953rd, 954th, 955th, 956th, 957th, 958th, 959th, 960th, 961st, 962nd, 963rd, 964th, 965th, 966th, 967th, 968th, 969th, 970th, 971st, 972nd, 973rd, 974th, 975th, 976th, 977th, 978th, 979th, 980th, 981st, 982nd, 983rd, 984th, 985th, 986th, 987th, 988th, 989th, 990th, 991st, 992nd, 993rd, 994th, 995th, 996th, 997th, 998th, 999th, 1000th, 1001st, 1002nd, 1003rd, 1004th, 1005th, 1006th, 1007th, 1008th, 1009th, 1010th, 1011st, 1012nd, 1013th, 1014th, 1015th, 1016th, 1017th, 1018th, 1019th, 1020th, 1021st, 1022nd, 1023rd, 1024th, 1025th, 1026th, 1027th, 1028th, 1029th, 1030th, 1031st, 1032nd, 1033rd, 1034th, 1035th, 1036th, 1037th, 1038th, 1039th, 1040th, 1041st, 1042nd, 1043rd, 1044th, 1045th, 1046th, 1047th, 1048th, 1049th, 1050th, 1051st, 1052nd, 1053rd, 1054th, 1055th, 1056th, 1057th, 1058th, 1059th, 1060th, 1061st, 1062nd, 1063rd, 1064th, 1065th, 1066th, 1067th, 1068th, 1069th, 1070th, 1071st, 1072nd, 1073rd, 1074th, 1075th, 1076th, 1077th, 1078th, 1079th, 1080th, 1081st, 1082nd, 1083rd, 1084th, 1085th, 1086th, 1087th, 1088th, 1089th, 1090th, 1091st, 1092nd, 1093rd, 1094th, 1095th, 1096th, 1097th, 1098th, 1099th, 1100th, 1101st, 1102nd, 1103rd, 1104th, 1105th, 1106th, 1107th, 1108th, 1109th, 1110th, 1111st, 1112nd, 1113th, 1114th, 1115th, 1116th, 1117th, 1118th, 1119th, 1120th, 1121st, 1122nd, 1123rd, 1124th, 1125th, 1126th, 1127th, 1128th, 1129th, 1130th, 1131st, 1132nd, 1133rd, 1134th, 1135th, 1136th, 1137th, 1138th, 1139th, 1140th, 1141st, 1142nd, 1143rd, 1144th, 1145th, 1146th, 1147th, 1148th, 1149th, 1150th, 1151st, 1152nd, 1153rd, 1154th, 1155th, 1156th, 1157th, 1158th, 1159th, 1160th, 1161st, 1162nd, 1163rd, 1164th, 1165th, 1166th, 1167th, 1168th, 1169th, 1170th, 1171st, 1172nd, 1173rd, 1174th, 1175th, 1176th, 1177th, 1178th, 1179th, 1180th, 1181st, 1182nd, 1183rd, 1184th, 1185th, 1186th, 1187th, 1188th, 1189th, 1190th, 1191st, 1192nd, 1193rd, 1194th, 1195th, 1196th, 1197th, 1198th, 1199th, 1200th, 1201st, 1202nd, 1203rd, 1204th, 1205th, 1206th, 1207th, 1208th, 1209th, 1210th, 1211st, 1212nd, 1213th, 1214th, 1215th, 1216th, 1217th, 1218th, 1219th, 1220th, 1221st, 1222nd, 1223rd, 1224th, 1225th, 1226th, 1227th, 1228th, 1229th, 1230th, 1231st, 1232nd, 1233rd, 1234th, 1235th, 1236th, 1237th, 1238th, 1239th, 1240th, 1241st, 1242nd, 1243rd, 1244th, 1245th, 1246th, 1247th, 1248th, 1249th, 1250th, 1251st, 1252nd, 1253rd, 1254th, 1255th, 1256th, 1257th, 1258th, 1259th, 1260th, 1261st, 1262nd, 1263rd, 1264th, 1265th, 1266th, 1267th, 1268th, 1269th, 1270th, 1271st, 1272nd, 1273rd, 1274th, 1275th, 1276th, 1277th, 1278th, 1279th, 1280th, 1281st, 1282nd, 1283rd, 1284th, 1285th, 1286th, 1287th, 1288th, 1289th, 1290th, 1291st, 1292nd, 1293rd, 1294th, 1295th, 1296th, 1297th, 1298th, 1299th, 1300th, 1301st, 1302nd, 1303rd, 1304th, 1305th, 1306th, 1307th, 1308th, 1309th, 1310th, 1311st, 1312nd, 1313th, 1314th, 1315th, 1316th, 1317th, 1318th, 1319th, 1320th, 1321st, 1322nd, 1323rd, 1324th, 1325th, 1326th, 1327th, 1328th, 1329th, 1330th, 1331st, 1332nd, 1333rd, 1334th, 1335th, 1336th, 1337th, 1338th, 1339th, 1340th, 1341st, 1342nd, 1343rd, 1344th, 1345th, 1346th, 1347th, 1348th, 1349th, 1350th, 1351st, 1352nd, 1353rd, 1354th, 1355th, 1356th, 1357th, 1358th, 1359th, 1360th, 1361st, 1362nd, 1363rd, 1364th, 1365th, 1366th, 1367th, 1368th, 1369th, 1370th, 1371st, 1372nd, 1373rd, 1374th, 1375th, 1376th, 1377th, 1378th, 1379th, 1380th, 1381st, 1382nd, 1383rd, 1384th, 1385th, 1386th, 1387th, 1388th, 1389th, 1390th, 1391st, 1392nd, 1393rd, 1394th, 1395th, 1396th, 1397th, 1398th, 1399th, 1400th, 1401st, 1402nd, 1403rd, 1404th, 1405th, 1406th, 1407th, 1408th, 1409th, 1410th, 1411st, 1412nd, 1413th, 1414th, 1415th, 1416th, 1417th, 1418th, 1419th, 1420th, 1421st, 1422nd, 1423rd, 1424th, 1425th, 1426th, 1427th, 1428th, 1429th, 1430th, 1431st, 1432nd, 1433rd, 1434th, 1435th, 1436th, 1437th, 1438th, 1439th, 1440th, 1441st, 1442nd, 1443rd, 1444th, 1445th, 1446th, 1447th, 1448th, 1449th, 1450th, 1451st, 1452nd, 1453rd, 1454th, 1455th, 1456th, 1457th, 1458th, 1459th, 1460th, 1461st, 1462nd, 1463rd, 1464th, 1465th, 1466th, 1467th, 1468th, 1469th, 1470th, 1471st, 1472nd, 1473rd, 1474th, 1475th, 1476th, 1477th, 1478th, 1479th, 1480th, 1481st, 1482nd, 1483rd, 1484th, 1485th, 1486th, 1487th, 1488th, 1489th, 1490th, 1491st, 1492nd, 1493rd, 1494th, 1495th, 1496th, 1497th, 1498th, 1499th, 1500th, 1501st, 1502nd, 1503rd, 1504th, 1505th, 1506th, 1507th, 1508th, 1509th, 1510th, 1511st, 1512nd, 1513th, 1514th, 1515th, 1516th, 1517th, 1518th, 1519th, 1520th, 1521st, 1522nd, 1523rd, 1524th, 1525th, 1526th, 1527th, 1528th, 1529th, 1530th, 1531st, 1532nd, 1533rd, 1534th, 1535th, 1536th, 1537th, 1538th, 1539th, 1540th, 1541st, 1542nd, 1543rd, 1544th, 1545th, 1546th, 1547th, 1548th, 1549th, 1550th, 1551st, 1552nd, 1553rd, 1554th, 1555th, 1556th, 1557th, 1558th, 1559th, 1560th, 1561st, 1562nd, 1563rd, 1564th, 1565th, 1566th, 1567th, 1568th, 1569th, 1570th, 1571st, 1572nd, 1573rd, 1574th, 1575th, 1576th, 1577th, 1578th, 1579th, 1580th, 1581st, 1582nd, 1583rd, 1584th, 1585th, 1586th, 1587th, 1588th, 1589th, 1590th, 1591st, 1592nd, 1593rd, 1594th, 1595th, 1596th, 1597th, 1598th, 1599th, 1600th, 1601st, 1602nd, 1603rd, 1604th, 1605th, 1606th, 1607th, 1608th, 1609th, 1610th, 1611st, 1612nd, 1613th, 1614th, 1615th, 1616th, 1617th, 1618th, 1619th, 1620th, 1621st, 1622nd, 1623rd, 1624th, 1625th, 1626th, 1627th, 1628th, 1629th, 1630th, 1631st, 1632nd, 1633rd, 1634th, 1635th, 1636th, 1637th, 1638th, 1639th, 1640th, 1641st, 1642nd, 1643rd, 1644th, 1645th, 1646th, 1647th, 1648th, 1649th, 1650th, 1651st, 1652nd, 1653rd, 1654th, 1655th, 1656th, 1657th, 1658th, 1659th, 1660th, 1661st, 1662nd, 1663rd, 1664th, 1665th, 1666th, 1667th, 1668th, 1669th, 1670th, 1671st, 1672nd, 1673rd, 1674th, 1675th, 1676th, 1677th, 1678th, 1679th, 1680th, 1681st, 1682nd, 1683rd, 1684th, 1685th, 1686th, 1687th, 1688th, 1689th, 1690th, 1691st, 1692nd, 1693rd, 1694th, 1695th, 1696th, 1697th, 1698th, 1699th, 1700th, 1701st, 1702nd, 1703rd, 1704th, 1705th, 1706th, 1707th, 1708th, 1709th, 1710th, 1711st, 1712nd, 1713th, 1714th, 1715th, 1716th, 1717th, 1718th, 1719th, 1720th, 1721st, 1722nd, 1723rd, 1724th, 1725th, 1726th, 1727th, 1728th, 1729th, 1730th, 1731st, 1732nd, 1733rd, 1734th, 1735th, 1736th, 1737th, 1738th, 1739th, 1740th, 1741st, 1742nd, 1743rd, 1744th, 1745th, 1746th, 1747th, 1748th, 1749th, 1750th, 1751st, 1752nd, 1753rd, 1754th, 1755th, 1756th, 1757th, 1758th, 1759th, 1760th, 1761st, 1762nd, 1763rd, 1764th, 1765th, 1766th, 1767th, 1768th, 1769th, 1770th, 1771st, 1772nd, 1773rd, 1774th, 1775th, 1776th, 1777th, 1778th, 1779th, 1780th, 1781st, 1782nd, 1783rd, 1784th, 1785th, 1786th, 1787th, 1788th, 1789th, 1790th, 1791st, 1792nd, 1793rd, 1794th, 1795th, 1796th, 1797th, 1798th, 1799th, 1800th, 1801st, 1

NEWART

Dept PW5
30/32, SHUDEHILL MANCHESTER 4.
Telephone (061) 832 7710

FREE GIFT OFFER

OF A BRAND NEW WORLD FAMOUS EMI FISK SOLARISCOPE VALUE £2.2.0, WITH EVERY ORDER VALUE £5 AND OVER. THIS UNIQUE INSTRUMENT WHICH IS A BOON TO SHORT WAVE LISTENERS CLEARLY SHOWS THE AREAS OF DAYLIGHT AND DARKNESS ALL OVER THE EARTH AT ANY GIVEN HOUR.

MINI-MOTORS 3v to 4.5v operation. Ideal for mini-racing cars, models and toys. "Large" (1 1/2 x 7/10 x 1 1/2 in.): 3/11d. Medium (1 x 3/4 x 1 1/4 in.): 3/8d. Small (1/2 x 1/4 x 1 in.): 3/3d. P. & P. 9d. each.

BRAND NEW! Why use Sapphire Stylus in your record player when at very little extra cost you can have a first grade **GENUINE DIAMOND STYLUS** at 7/11d. plus 6d. P. & P. Available as replacements for the following popular types only at present: BSR.TC8LP; BSR.TC8 Stereo; BSR.TC8 LP/Stereo; Collaro Studio "O" LP/Ronette; Garrard GC8 LP; Acos GP 65/67LP; Ronette BF40/LP; Garrard GC2LP.

SPEAKERS. 12in. Round high quality British fitted tweeter cone. 6 watts available in 3Ω or 16Ω. Wonderful value at 29/6d. P. & P. 3/6d. 12in. Round B & A. 3Ω 25/6d. P. & P. 3/6d. 3in. Round best British make. 8/6d. P. & P. 1/6d.

TWEETER. 2 1/2in. Black plastic cone, round on Square Frame, E.M.I. 3Ω, 12/6d. plus 1/6d. P. & P. P.A. HORN Speaker, 8Ω, 15 watt 9 x 9in. Swivel mounting brackets, 25.5.0. Carr. Paid. Many other sizes and types available from 2in.

TRANSISTORS: Some popular types from our range: OC44 & OC45 3/8d. ea. OC71 3/8d. OC72 3/8d. OC81 & OC81D 2/- ea. OC169 3/8d. OC170 3/6d. AF117 4/- OC26 7/6. GET 8 5/8. General purpose (Approx. OC71) 1/- ea. Postage 6d. up to 3. Over 12 sent P. & P. paid.

MICROPHONES, LAPEL/HAND MIKE—1 1/4in. dia. Lapel Clip, ideal for tape recording. With lead. Very Sensitive. 7/6. P. & P. 1/-.

CRYSTAL HAND MIKE—Robust and Sensitive. Cream Plastic Case. Just the thing for tape recorders. 8/6. P. & P. 1/6.

ACOS MIC 40—World famous Desk Mike 12/9 x P. & P. 1/3

ACOS MIC 45—Hand Held Curved Hand Grip Crystal Mike 14/6 x P. & P. 1/6

ACOS MIC 90—"Stick" Type Crystal Mike 18/6 x P. & P. 1/6

ACOS Round Crystal Inserts, 1in. dia. 6/6; 1 1/2in. dia. 7/6. P. & P. on either, 6d.

DYNAMIC HAND/DESK TYPE. 50KΩ with cable and plug to suit most recorders, etc. 12/9. P. & P. 1/3.

TELESCOPIIC FLOOR STAND, HEAVY BASE. Standard thread. Suits above or any other mike. 49/6. Carr. & Pkg. 2/6.

TELEPHONE PICK-UP COIL. For recording or amplifying both sides of telephone conversation. Suction cup fitting to phone. With lead, 7/6. P. & P. 1/-.

INTER-COMM. DE-LUXE 2 WAY. Ideal for offices, workshops, theatres, etc. Highly efficient, safe **BABY ALARM.** No mains—works off PP3 battery, which lasts for months, obtainable everywhere. Buzzer call system, complete with leads, plugs, battery, in handsome carton. 68/-. P. & P. 2/6d.

PICK-UP ARM, 1 1/2lb weight, with T/O crystal cartridge and stylus for L.P. and 78 R.P.M. records on base with rest 27/8d. P. & P. 2/6d.

R.F. FIELD INDICATOR. Ideal for use with radio controlled models. Checks radiation from existing antenna. Tunes 1 to 250 Mc in 5 bands. Sensitive 200 mA meter movement, 5 section plug-in aerial. Phone jack and crystal earpiece for monitoring. No battery required. Powerful magnet for attaching to metal surfaces. Complete with instructions. 47/6d. P. & P. 2/6d.

4 TRANSISTOR SW AMPLIFIER. Size 2 1/2 x 2 1/4 x 1 1/4, 3, 8 or 15Ω output, 9 volt battery operated. Highly sensitive. Price (see battery) 52/6d. P. & P. 1/6d.

VERNIER DIALS—Rt standard 1in. spindle—approx. 8:1 ratio. Marked 0/100 through 1500. See red 5in. dia. 10/6d. Large 3in. dia. 12/-. Post on either 1/10.

MAINS TRANSFORMERS: 250/0/250 80mA, 6v and 6.3v at 2A Chassis MTG. 250v or 110v IN Size 4 x 3 1/2 x 2 1/2in. 21/- ea. P. & P. 2/-. **VOLTAGE DROPPING TRANSFORMER** 250v IN, 3.5v, 9v and 17v out at 4amps. Many uses. Ideal for Battery Chargers etc. 8 x 2 1/2 x 2 1/2, 22/6d. each. P. & P. 2/6d.

RECORD PLAYER DECKS, GARRARD. All latest models. All fitted Mono Cartridge. Stereo 10/- extra. Carr. & Pkg. all models 7/6d. but price inc. free gift.

SP25 De Luxe 4 speed single-player 29. 9.6

MODEL 1000 4 speed Auto-Change .. 25.19.6

AT6 MKIIA 4 speed De Luxe Auto-change 23.19.6

MODEL 2000 4 speed Auto-Change .. 27.10.0

B.S.E. Automatic Record-Change Decks—Latest Models.

UA 25—Very popular—4 speed. Capacity six 7", 10", 12" records. 25.19.6

UA 15 88—8in Design—first class 4 speed. Two-tone finish. 25.3.6.

UA 16/88D—As above, but with low mass pl/ arm reducing record wear and heavier 10in. t. t. Finished in Pearl Grey and Black. 26.18.6.

P. & P. on all above 7/6d. Price includes Free Gift.

Magnavox '368' Tape Decks. Latest Models. World famous. Made to highest standards. Size 13 1/2 x 11 x 5 1/2in. below book. For 200/250v. 57 cycles A.C. 3 speed, digit counter, plus auto controls. 7in. Reels. Every modern feature. Speeds 15, 3 1/2 and 7 1/2 i.p.m. With 1/4 track Brannin head 110.10.0. With 1/2 track Marriott heads 113.9.6. P. & P. 10/-. Price includes Free Gift.

PICK-UP CARTRIDGE REPLACEMENTS. STANDARD FIXING FOR MOST RECORD-PLAYER ARMS. ALL TUNER-OVER TYPES WITH STYLUS FOR L.P. & 78 R.P.M.

ACOS GP/67-A Mono, 12/6 ea. ACOS GP/91-1 Mono de luxe, 17/6 ea. ACOS GP/73-2 Stereo, 25/- ea. Postage and Packing 9d. each.

Finest Quality British made Mylar Recording Tape. Fully Guaranteed.

5in. Message .. 5/- 5 1/2in. 1200ft. Long Play .. 12/6

5in. 609 Standard Play .. 8/6 7in. 1800ft. Long Play .. 19/6

5 1/2in. 850 Standard Play .. 11/6 5in. 1200ft. Double Play .. 15/6

7in. 1290 Standard Play .. 12/6 5 1/2in. 1800ft. Double Play .. 22/6

5in. 900ft. Long Play .. 10/- 7in. 2400ft. Double Play .. 24/-

P. & P. 1/- per reel. Four reels and over post paid. N.A.—MYLAR based recording tape is of infinitely superior quality and far stronger than Acetate base tape.


POCKET MULTI-TEST METER. 1000Ω per volt. Volts 0/10/50/250/500/1000 AC and DC Current: 0-1-100-500mA. Resistance: 0-100kΩ. Complete with test leads, instructions. 27/6. P. & P. 1/6.

TERMS: Cash with order—No C.O.D. Orders totalling £5 and over sent carriage paid (excepting Record Player decks and Transmitters where carriage is shown). Guaranteed money refunded if goods returned perfect within 7 days of despatch.

REMEMBER THE NOVEL FREE GIFT EXCLUSIVE TO US!

Orders welcome—Very many more lines to choose from. Open 9.30 a.m.—6 p.m. Mon.—Sat.

COCKTAIL/STEREOGRAM CABINET £25

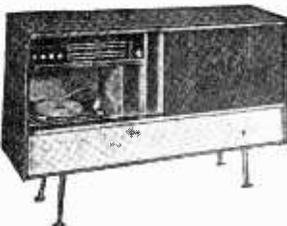

Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10in. elliptical speakers. Record storage space. Height 35 1/2in., width 52 1/2in., depth 14 1/2in. Legs 1 gn. extra.

OTHER MODELS, SEND FOR FREE LIST

RECORD PLAYER CABINETS, 49/6. Latest designed covered cabinets. Takes any modern Auto-changer. P. & P. 7/6.

TRANSISTOR CASES 19/6 9 1/2 x 6 1/2 x 3 1/2in. P. & P. 2/6.

TV TURRET TUNERS, 2/6. New, less valves, 511m models 5/-. Press button models 19/6. P. & P. 2/6.



17in.—£11.10.0 TWO-YEAR GUARANTEE EX-RENTAL TELEVISIONS

3 Star Guarantee
★ Tube ★ Valves
★ Components Carr. 39/-

FREE ILLUSTRATED LIST OF TELEVISIONS

17"—19"—21"—23"
WIDE RANGE OF MODELS
SIZES AND PRICES
DEMONSTRATIONS DAILY

TWO-YEAR GUARANTEED TUBES 100% REGUNNED

14in.—69/6 17in.—59/6


21in. and ALL SLIMLINE TUBES 99/6

Carr. 10/6

EX MAINTENANCE TESTED TUBES

17in.—35/- 14in.—15/-


Carr. 5/- (not slimline)

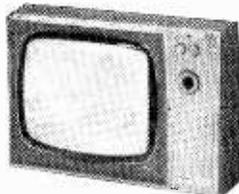

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, E.12 ILF 6001-2-3

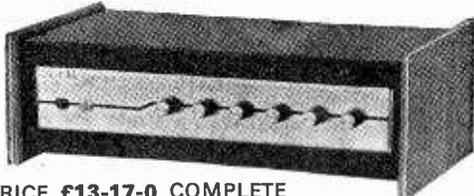VIKING STEREO 4 + 4 DE-LUXE HIGH QUALITY AMPLIFIER



PRICE £13-17-0 COMPLETE

A high quality stereo amplifier, built to meet the requirements of budget Hi-Fi. Elegant styled cabinet in black resin and woodgrained ends. Brushed aluminum panel, black and silver knobs. Quality components throughout. Ganged Bass and Treble controls, separate volume controls for each channel. Valves (Standard Model) 2 x ECL86 (De-Luxe Model) 1 x ECC83 (2) x ECL86. Output 3 ohms matching, suitable A.C. mains 230-240 volt. Cabinet size, 16 1/2in. high, 8 1/2in. depth. Full instructions and guarantee. Send for leaflet. S.A.E.

VIKING 10-12 A twelve watt amplifier for use on 230-240 volt A.C. Mains. Inputs suitable Microphone, Record Player, Tuner, Tape Recorder, etc. Printed circuitry. Five Mullard valves, reliable components. Front panel contains 2 Input Jacks, 2 Volume Controls, 1 Tone, Neon and On/Off switch. Designed to fit into same type and size cabinet as Stereo. Fully guaranteed. Send for leaflet. PRICE £8-19-6 PLUS 12/6 P.P.

VIKING X.P.15. A frustrated order offered at a fraction of cost (original price 39 gns.). 15 watts output. Suitable for 210-240 Volt A.C. mains. Attractive Black chassis with slotted Chromed steel top cover, size 15 x 7 1/2 x 7in. 4 Input Jacks, 2 volume controls, 2 tone. 5 Mullard valves. Fully guaranteed. Send for leaflet.

Price Complete £12.19.6 plus 12/6 P. & P. and Ins.

L.P. TAPE BARGAIN

5 1/2in. reels each containing 1200ft. of top quality polyester recording tape (limited quantity.)
Price 3 reels for 35/- P.P. free.

Terms: C.W.O., C.O.D. Money back guarantee.

VIKING (ELECTRONICS) LTD. 37 HILLSIDE, STONEBRIDGE, LONDON N.W.10

Telephone: ELG 3644

(MAIL ORDER ONLY)

Why

NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

FIRST FOR PERFORMANCE, QUALITY & PRICE!

BACKED BY OUR SUPER AFTER SALES SERVICE

"A wonderful range of transistor radios using first grade components guaranteed results."

NEW ROAMER SEVEN Mk IV

7 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification ● Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS

FULLY TUNABLE ON ALL WAVEBANDS

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned 7 x 4in. speaker. Air spaced tuned tuning condenser. Ferrite rod aerial for M. & L. Waves and telescopic aerial for S. Waves. Real leather-look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx.


The perfect portable and the ideal car radio. (Uses PP7 batteries. available anywhere.)

● EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, etc.

Total cost of parts now only

£5.19.6


P. & P. 5/6

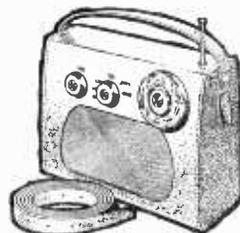

Parts Price List and easy build plans 3/- (Free with kit)

NEW MELODY MAKER SIX

★ 8 stages. Six transistors and two diodes. Covers Medium and Long Waves and Extra Band for EASIER tuning of LUXEMBOURG etc. Top grade 3in. Loud-speaker for quality output. Two R.F. stages for extra boost. High 'Q' 6in. Ferrite Rod Aerial. Approx. 350 Milliwatts push pull output. Handsome pocket size case with gilt fittings. Size 6 1/2 x 3 1/2 in. (Uses long-life PP6 battery). Carrying strap 1/6 extra.

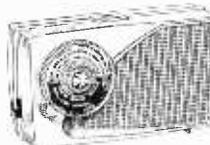

This amazing receiver may be built for only


£3.9.6

P. & P. 3/6

Parts price list and easy build plans 2/- (Free with kit).

QUICK CHECK TRANSISTOR TESTER.

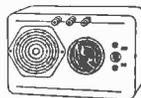Checks gain of R.F. and Audio Transistors. Also checks for noise level and duds. All parts ready to be assembled in attractive grey case with red grille, complete with Dial, Knobs, and Dynamic Speaker. Simple assembly instructions free with set of parts. 29/6. P. & P. 2/6.



THE SIG-GEN. A versatile Signal Injector. Something no constructor should be without. The ingenious device generates an audible signal through the Audio and R.F. ranges. With variable output. Telescopic Probe. Pocket size slim line case measures 4 1/2 x 3 1/2 x 1/2 in. Complete set of parts with full instructions. 19/6. P. & P. 2/-.

NEW TRANSONA FIVE

Now with 3in. Speaker!

"Home, Light, A.F.N., Lux. all at good volume." G.P., Durham.

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves. Incorporates Ferrite rod aerial, tuning condenser volume control, new type fine tone super dynamic 3in. speaker, etc. 1 x 1 1/2 in. with red speaker grille. (Uses 1289 battery available anywhere.)

Attractive case. Size 6 1/2 x 4 1/2 battery, available anywhere.)


● Extended M.W. band for easier tuning of Luxembourg etc.

Total cost of all parts now only

42/6

P. & P. 3/6

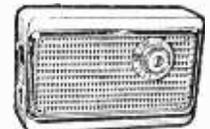Parts Price List and easy build plans 2/- (Free with kit)



POCKET FIVE Now with 3in. Speaker!

● 7 stages—5 transistors & 2 diodes


Covers Medium and Long Waves. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 3in. moving coil speaker, built into attractive black and gold case. Size 5 1/2 x 4 1/2 x 3/4 in. (Uses 1289 battery available anywhere.)

● Extended M.W. band for easier tuning of Luxembourg etc.

Total cost of all parts now only

42/6

P. & P. 3/-

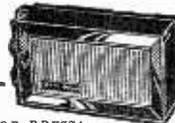

STOP PRESS!

Pocket 5 med. and long wave version with miniature speaker.

29/6

P. & P. 3/-

Parts Price List and easy build plans 1/6 (Free with kit)

NEW ROAMER SIX

NOW, WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND !

● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long Waves, Trawler Band and two Short Waves. Sensitive Ferrite rod aerial and telescopic aerial for short waves. Top grade transistors. 3in. speaker, handsome case with gilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2 in. (Carrying strap 1/6 extra.)



★ EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, ETC.

Total cost of all parts now only

£3.19.6

P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)

TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

A top performance receiver covering full Medium and Long Waves. High-grade 3in. speaker makes listening a pleasure. Push-pull output. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. (Uses PP4 battery available anywhere). Carrying strap 1/- extra.

● Extended M.W. band for easier tuning of Luxembourg etc.

Total cost of all parts now only

59/6

P. & P. 3/6


Parts Price List and easy build plans 1/6 (Free with kit)



MELODY SIX

● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering Medium and Long Waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. Ferrite rod aerial. Push-pull output. Wonderful reception of BBC, Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2 in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

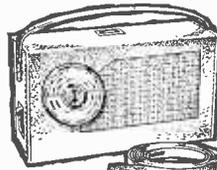

some leather-look pocket size case, only 6 1/2 x 3 1/2 x 1 1/2 in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

Total cost of all parts now only

£3.9.6

P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)

SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 R.F. Stages, push-pull output, 3in. speaker (will drive large speaker). Size 7 1/2 x 5 1/2 x 1 1/2 in. (Uses 9V battery, available anywhere.)



Total cost of all parts now only

£3.19.6

P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)

Callers slide entrance Barratts Shoe Shop.

RADIO EXCHANGE CO.


Open 9—5 p.m. Saturday 9—12.30 p.m.

61 HIGH STREET, BEDFORD Telephone: Bedford 52367

VIKING TRANSISTOR

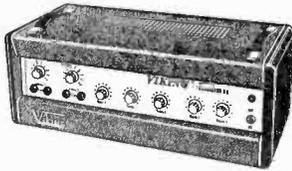40-50 WATT AMPLIFIER

OPERATING INSTRUCTIONS GENERAL. An extremely reliable lightweight amplifier capable of giving 40-50 watts of undistorted sound, made possible by the use of the latest semi-conductors (transistors) and techniques which ensure space-age reliability under the most rugged conditions. It is



designed as a general purpose amplifier particularly suitable for use with musical instruments that require exceptionally high treble response (not recommended for Bass Guitar). Tremolo facilities are available on Channel 1 only. **INPUTS—CONTROLS—CHANNEL 1 (Tremolo):** this contains two high gain input jack sockets controlled by **Volume Control 1** which is mounted directly above the two sockets marked tremolo. **BASS 1:** gives a controlled boost to the lower frequencies on Channel 1 only. **TREBLE 1:** gives a controlled boost to the high frequencies on Channel 1 only. **TREMOLO:** this operates on Channel 1 only and the variations of intensity and speed of the Tremolo beat is adjusted by the controls **DEPTH** and **SPEED**. A socket is provided in the rear of the amplifier so that the Tremolo may be switched on and off by the use of a footswitch plugged into the socket. If you wish the Tremolo to be used without the foot-switch, this is possible as the footswitch is only used to short out the effect. **INPUTS AND CONTROLS—CHANNEL 2 (Normal):** this contains two high gain input jack sockets controlled by **Volume Control 2** which is mounted directly above the sockets marked Normal. **TREBLE:** gives a controlled boost to the treble frequencies on Channel 2 only. **MAINS VOLTAGE:** fully adjustable, 200-250 volts, A.C. 60 cycles. **POWER OUTPUT:** 40-50 watts sine wave British rating. Very little distortion. **OUTPUT IMPEDANCE:** 3 ohms. Price 21 gns. plus 1/1 postage and packing.

WOLSEY U.H.F. AERIAL AMPLIFIER, two stage, gain 23 dB, noise factor 8 dB, power consumption 6 mA at 14 volts. Two AF186 transistors, complete with built-in power supply in metal case, list price 9 gns., our price 4 1/2 gns. plus 2/6 postage and packing.

MAINS TRANSFORMER, primary 200/250 volt, secondary 425/425 volt, 250 mA, 6.3 volt 4 amp, 5 volt 3 amp; fully shrouded, chassis mounting. Price £2.50 plus 7/6 postage and packing. Auto transformer step-up-step-down, 240/110 volt 400 watt. Price £1.50 plus 7/6 postage and packing.


MAINS TRANSFORMER 200/250 volt, secondary 250/250 volt, 70 mA, 6.3 volt, 3 amp drop through. Price 12/6 plus 4/6 postage and packing. Elac 10 inch, 10,000 lines ceramic magnet, 3 or 15 ohms, 7 watt, £1.96 plus 4/6 postage and packing.



POCKET MULTI-METER

Size 3 1/4 x 2 1/4 x 1 1/4 in. Meter size 2 1/4 x 1 1/4 in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0.15, 0.150 0.1000. D.C. current 0.150mA. Resistance 0.100kΩ. Complete with test prods, battery and full instructions, 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

40W FLUORESCENT LIGHT KIT

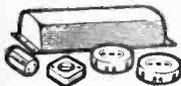

Incorporating GEC Choke size 8 1/2 in. x 1 1/2 in. x 1 1/2 in., 2 bi-pin holders, starter and starter-holder. P. & P. 5/6. **11/6**

Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 11 1/2 in. x 1 1/2 in. x 1 1/2 in., 2 bi-pin holders start and starter holder. P. & P. 6/6. **17/6**

Twin 40W Choke instant start for 2 x 2ft. tubes 17/6. P. & P. 5/6.


3 to 4 Watt AMPLIFIER

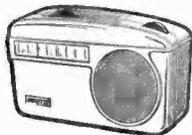3-4 watt Amplifier built and tested. Chassis size 7 x 3 1/2 x 1 in. Separate bass, treble and volume control. Double wound mains transformer, metal rectifier and output transformer for 3 ohms speaker. Valves ECC81 and 6V6. £2.50 plus 5/6 p. & p.
The above in Kit Form, £1.14.6 plus 5/6 p. & p.



"MUSETTE" 6-Transistor Superhet Portable Radio

★ 2 1/2" Speaker. ★ 6 Transistor Superhet Output 200mW. ★ Plastic Cabinet in red, size 4 1/2" x 3" x 1 1/2" and gold speaker louver. ★ Horizontal Tuning Scale. ★ Ferrite Rod Internal Aerial. ★ IF 460 kc/s. ★ All components Ferrite Rod and Tuning Assembly mount on printed board. ★ Operated from PP3 Battery. ★ Fully comprehensive instructions and point-to-point wiring diagram. ★ Printed Circuit Board. ★ Tunable over medium and long waveband. ★ Car aerial and earpiece socket.



Price 39/6d. inc. carrying strap. Circuit Diagram 2/6 free with parts. P. & P. 3/6.

RADIO & TV COMPONENTS (Acton) LTD


21c High Street, Acton, London, W3

Shop Hours 9 a.m.—6 p.m. Early Closing Wednesday
Goods not despatched outside U.K. Terms C.W.O.
All enquiries Stamped Addressed Envelope

8 VALVE STEREO RADIOGRAM CHASSIS

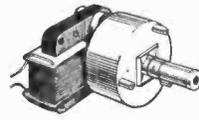3-4 WATTS PER CHANNEL
By Famous Manufacturer

Superb new 8-valve chassis covering long, medium and short waves on AM, also V.H.F. transmissions on FM, AM circuit's high sensitivity permits internal aerial for most stations. Well-known Goriier tuning heart in separate FM input. Tone and volume controls. Extra large illuminated dial. External AM and FM aerial inputs. Gram. pick-up socket. Standard 3 ohm speaker. 200/250 volts A.C. Size 17 x 7 x 5 1/2 in. deep. **£14.14.0**
P. & P. £1



Type E MOTOR


Small A.C. mains motor 230/250 volts complete with gearbox, 6 r.p.m. Price 15/- plus 4/- P. & P. Similar to above motor but without gearbox. Price 9/6 plus 3/- P. & P.

Silicon Rectifiers

250 v. P.I.V. 750 milliamps. Six for 7/6, Post paid.

TRANSISTORISED 1 1/2 WATT AMPLIFIER

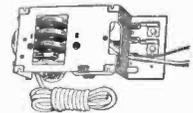
comprising 2AC 128, 20C 75 and 2 AA129 separate bass and treble volume controls. Complete with Power Supply AC mains 240 v. Size 7 1/4" x 3 1/4" x 2". Price 50/- plus 2/6 P. & P.



POWER SUPPLY KIT

A.C. MAINS 200-250 V

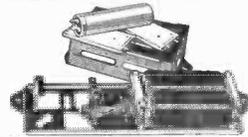Incorporating "C" core type mains transformer, full wave metal rectification and smoothing condenser. Smooth output 250 v. 250mA and 6.3v. 4 amp. for Heaters. 25/- P. & P. 9/6.



FIRST QUALITY P.V.C. TAPE

5 1/2" Std.	850ft.	9/-	5" L.P.	850ft.	10/6
7" Std.	1200ft.	11/6	3" T.P.	600ft.	10/6
3" L.P.	240ft.	4/-	5" T.P.	1800ft.	25/6
5 1/2" L.P.	1200ft.	11/6	5 1/2" T.P.	2400ft.	32/6
7" L.P.	1800ft.	18/6	7" T.P.	3600ft.	42/6
5 1/2" D.P.	1800ft.	18/6	4" T.P.	900ft.	15/-

P. & P. on each 1/6, 4 or more post free

EXTRACTOR FAN



AC Mains 230/250 v. complete with pull switch. Size 6" x 6" x 4". Price 27/6 plus 5/- P. & P.


GEC DOORBELL

Complete with mains transformer 240 v. AC & illuminated bell push. Price 12/6 plus 5/6 P. & P.



8-watt 4-valve PUSH-PULL AMPLIFIER & METAL RECTIFIER

Size: 9" x 6" x 1 1/4". A.C. Mains, 200-250V 4 valves. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Output 8 watts at 5 per cent of total distortion. Separate bass and treble lift control. Two inputs, with controls for gram. and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested, £4.4.0. P. & P. 11/-, 8" x 6" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P.

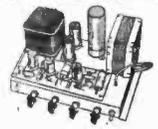

GEC KETTLE ELEMENT

3,000W WITH AUTOMATIC EJECTION
200/240 v. Size of hole required 1 1/8". List Price 32/- OUR PRICE 15/- P. & P. 1/6.



NEW TRANSISTORISED SIGNAL GENERATOR

Size 5 1/2" x 3 1/2" x 1 1/4". For IF and RF alignment and AF output 700 c/s frequency coverage 460 kc/s to 2 mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and Musette. Built and tested. **39/6** P. & P. 3/6

CYLDON U.H.F. TUNER

Complete with PC88 and PC86 Valves. Full variable tuning. New and unused. Size 4 1/2" x 5 1/2" x 1 1/4". Complete with circuit diagram. **35/-** plus 3/6 P. & P.



Also at 323 EDGWARE ROAD, LONDON, W.2. Personal shoppers only: Early Closing Thursday. All orders by post to our Acton address.

Elegant Seven Mk II A

COMBINED PORTABLE and CAR RADIO

SPECIAL OFFER


7" x 4" P.M. Speaker at no extra charge

Buy yourself an easy to build 7 transistor radio and save at least £10.0.0. Now you can build this superb 7 transistor superhet radio for under £4.10.0. No one else can offer such a fantastic radio with so many de luxe star features.

- ★ De luxe grey wooden size 12½" x 8½" x 3½".
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 11½" x 2".
- ★ High 'Q' ferrite rod aerial.
- ★ I.F. neutralization on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback.
- ★ Room filling output 350 mW.
- ★ Ready etched and drilled printed circuit board back printed for fool proof construction.
- ★ Fully comprehensive instructions and point-to-point wiring diagrams.
- ★ Car aerial socket.
- ★ Fully tunable over medium and long wave. 168-535 metres and 1250-2000 metres.
- ★ All components ferrite rod and tuning assembly mount on printed boards.
- ★ Parts list and circuit diagram 2s. 6d., free with parts.

ONLY **£4.4.0**

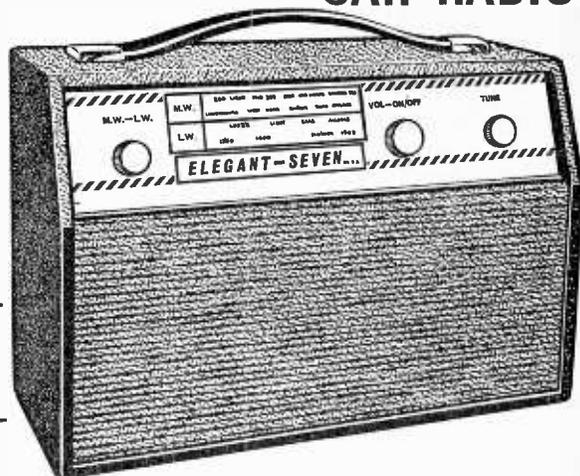Plus 7/6 P. & P. Parts List and circuit diagram 2/6 FREE with parts.



POWER SUPPLY KIT

To purchasers of 'Elegant Seven' parts, incorporating mains transformer, rectifier and smoothing condenser, A.C. mains 200/250 volts. Output 9v 100mA. 7/6 extra.

RADIO & TV COMPONENTS (ACTON) LTD.

All orders by post to be sent to our Acton address

323 EDGWARE ROAD, LONDON, W2

Personal shoppers only. Early closing Thursday.

21C HIGH STREET, ACTON, LONDON, W3

OPEN 9 a.m.—6 p.m. INCLUDING SATS. EARLY CLOSING WED.
GOODS NOT DESPATCHED OUTSIDE U.K. TERMS C.W.O.

All enquiries stamped addressed envelope

THE PEMBRIDGE COLLEGE OF ELECTRONICS FOR TRAINING IN RADIO AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course, of sixteen months' duration, provides a fundamental training for radio and television engineers. It includes theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Exactly half the time is spent on practical work and the course provides excellent practical experience on valve and transistor radio receivers and high-fidelity equipment and all well known makes of television receivers.

The Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Next Course commences 5th September, 1967.

To: **The Pembridge College of Electronics (Dept. P11)**
34a Hereford Road, London, W.2.
Please send, without obligation, details of the Full-time Course in Radio and Television.

Name _____

Address _____

CMP 5

stern-clyne

ELECTRONIC CENTRES

MEMBER OF THE PANTIYA GROUP OF COMPANIES

MAIL ORDER & ALL ENQUIRIES TO: DEPT. PW, 3-5 EDEN GROVE, HOLLOWAY, LONDON, N.7. Tel. NORTH 8161/5

LONDON:
15 Tottenham Court Road, W.1.
23 Tottenham Court Road, W.1.
389 Edgware Road, W.2.
109 Fleet Street, E.C.4.
162 Holloway Road, N.7.

MUSEum 0095
MUSEum 3451
PADdington 6963
FLEEt Street 5812
NORTH 7941

9 Camberwell Church Street, S.E.5.
CROYDON: 12 Suffolk House, George Street,
BRISTOL: 26 Merchant Street, Bristol 1.
LIVERPOOL: 52 Lord Street.

RODney 2875
Municipal 3250
Bristol 20261
Royal 7450

MANCHESTER:
20/22 Withy Grove, M/c. 4.
SHEFFIELD: 125 The Moor.
NOTTINGHAM: Eastown House, Lincoln St.

Blackfriars 5879/5246
Sheffield 29993
Nottingham 45889

SULTAN

solid-state integrated Stereo amplifier



The most advanced design in brilliant new kit form—so simplified you can build it to professional standards without specialized knowledge and with simple tools. Designed for kit builders from the beginning with a system of wiring that enables you to complete each solder joint as you proceed; nothing is soldered twice and there are no unfinished joints left waiting to be overcooked! SULTAN performance is a natural result of superb design incorporating the most advanced full proved semi-conductors, and modular substage construction that permits searching quality control and precise matching at every stage of assembly. Particular attention has been given to the provision of all the additional input, output, and power take-off facilities ever likely to be required. The compact sized, craftsman finished teak cabinet and restrained styling ensures unobtrusive, harmonious matching with almost any decor.

Sultan kit of parts **£29.8.0** Assembled and Tested **£39.18.0**
(Teak case only £3.3.0.) Carr. & Ins. 8/6 Carr. & Ins. 8/6


Terms: Kit of parts—Deposit £9.16.0 and 12 monthly payments of £1.16.10.
Total credit price £31.18.0.

Terms: Assembled and tested—Deposit £13.6.0 and 12 monthly payments of £2.8.10.
Total credit price £42.12.0.

- Descriptive leaflet free on request.
- Assembly Manual available separately 5/6 incl. P. & P.

SEND FOR CATALOGUE

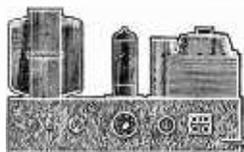A 1/- P.O. brings new 100-page Sound and Science Catalogue packed with unique items; profusely illustrated.



Designs by MULLARD
interpreted by STERN



5-10 POWER AMPLIFIER

One of the most famous amplifiers ever made—thousands are in use throughout the world. Superbly constructed to rigid Stern-Clyne requirements and conforming entirely to Mullard specification, including all specified components and brand new Mullard valves. Auxiliary power take-off for pre-amp and tuner (250 volts at 45 mA and 6.3 volts at 2 1/2 A) and gram mains supply on rear panel.

Kit of parts **£11.0.0** Assembled and Tested **£14.10.0**
Carr. & Ins. 6/6 Carr. & Ins. 6/6

2 VALVE PRE-AMPLIFIER

Specially designed by Mullard Research Laboratories for use with the 5-10 amplifier and one of the most compact pre-amplifiers available. Measuring only 9 1/2 x 2 1/2 x 4 1/2 in. deep. Input is provided for variable reluctance and crystal pick-ups with RIAA equalization, plus radio, sensitive microphone and tape reply direct, or from pre-amplifier. Controls: 6 position selector, volume on/off, wide range bass and treble. Powered direct by 5-10 amplifier.

Kit of parts **£6.6.0** Assembled and Tested **£9.10.0**
Carr. & Ins. 5/- Carr. & Ins. 5/-

COMBINED PRICES

5-10 Amplifier with 2-valve pre amplifier complete kit of parts £17.16.0.
Terms: Deposit £5.16.0 and 12 monthly payments of £1.4.2.

Total credit price £20.6.0

5-10 Amplifier and 2 valve pre-amplifier assembled and tested £8.19.0.
Terms: Deposit £8.0.0 and 12 monthly payments of £1.10.10.

Total credit price £26.10.0
Carr. & Ins. 10/-


RECORD PLAYERS at economical prices

BSR GU7 4-speed with mono cartridge	£3.19.6
GARRARD SRP22-4-speed with mono cartridge	£4.10.0
BSR UA50 Minichanger with XIM cartridge	£6.10.0
GARRARD 1000 Autochanger with GC8 cartridge	£6. 6.0
GARRARD 3000 Autochanger with 9TH/HC cartridge	£8.19.6
GARRARD SP25 with GP81 cartridge	£12.19.6
Carriage and Insurance on above 5/- extra	
GARRARD 401 Transcription Motor	£29.9.6
GOLDRING GL68 Transcription unit less cartridge	£19.16.0
GARRARD LAB80 MK2 Transcription Autochanger less cartridge	£30.7.2
GOLDRING GL70 Transcription unit less cartridge	£30.7.0
Carriage and Insurance on above 7/6 extra	

TERMS AVAILABLE ON ALL ORDERS OVER £15 IN VALUE

MERCURY

Brilliant new MODULAR HI-FI REPRODUCER

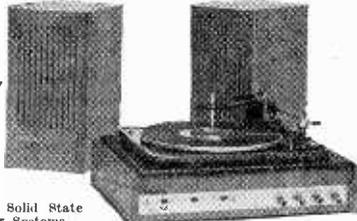

With Garrard Autochanger, Solid State Amplifier, Free-Cone Speaker Systems The Stern-Clyne Mercury is an important new approach to Hi-Fi sound reproduction in the home. One compact, modular system embodies the latest advances in solid-state amplifier design, loudspeaker system miniaturization, and pick-up cartridge development to provide superb stereo performance with exceptional installation facility. Combined Player Unit/Amplifier Console and identical speaker systems are superbly housed in matching teak veneer cabinets, specially designed to fit existing furniture or shelf space, and match any decor.

49 GNS.

TERMS:
Dep. £17.3.0 and 12 mthly. pymts. of £3.2.11. Total Credit Price £54.18.0.
Descriptive leaflet free on request.


MERCURY SYSTEM

AUTOCHANGER AND PICK-UP Garrard High-grade, Model 3000, specially equipped with high-compliance, ceramic cartridge fitted with Diamond stylus to ensure superb, wide range reproduction, and extremely low tracking weight.

AMPLIFIERS Identical, 5-watt, 7-transistor amplifiers designed round the latest, fully-proved semi-conductors. Each is independently constructed on a modular circuit board and subjected to searching inspection and precise matching at each stage of assembly.

LOUDSPEAKER SYSTEMS Bookshelf size, acoustically designed speaker system enclosure contain bass speakers and matching high frequency units with crossover network. Specially developed bass speaker employs enormously powerful magnet and free suspension cone to provide the full blooded bass response usually associated with much larger units.

STERNKIT FM1 TUNER

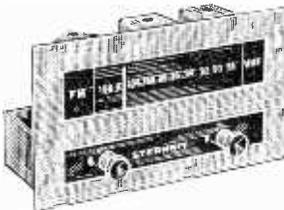

A new specially designed sensitive tuner for the amateur builder. Provides a stable, interference-free reception of BBC FM transmissions. High quality output signal ensures optimum performance from any Hi-Fi audio system. Reliable, easily aligned circuit includes RF stage and 2 IF noise limiting stages. Input sensitivity better than 100 microvolts for 40dB quieting. Power requirements 200 volts at 25mA, 6.3 volts at 1.5A.

Complete kit of parts **£7.9.6** Carr. & Ins. 4/-

Assembled and tested **£10.9.6** Carr. & Ins. 4/-

Optional power pack Type D kit **£2.15.0** Carr. 3/6 Assembly Manual only 3/- post free.

Assembled and tested **£3.10.0** Carr. 3/6 Descriptive leaflet free on request



39/6 TEST 7 Pocket Multimeter

Carr. 2/-

A really versatile instrument that makes a handy pocket-size tool. Measures AC or DC voltage in three ranges of 0-15-150-1000v. Resistance 0-1,000,000 ohms and Current 0-150mA. DC. Size only 3 1/2 x 2 1/2 x 1 1/2 in., with ingenious dial design providing a clear, easily read scale. Complete with battery and test leads.

EXCLUSIVE OFFER of Portable NOBILITY high quality recorders

Superbly styled, ruggedly constructed with features usually found only in more expensive instruments, including: separate motors for Rewind and Record/Play; "self-storing" remote control microphone in built-in housing, enclosed construction with integral handle that permits "any-attitude" recording, single master control for instant change of function. Four transistor amplifier gives 150 mW output into high grade dynamic speaker. Size: 10 1/2 x 8 1/2 x 2 1/2 in. Finished matt white/dark grey. Use anywhere for Note-taking, Idea Recording, Dictation, etc. Complete with microphone, batteries, 3 1/2 in. tape and spare spool in handsome gift box.



Only **£7.15.0**
Carriage 5/-

PRACTICAL WIRELESS

VOL 43 No 2

issue 724

JUNE 1967

Clause 7—No person shall make equipment undesirable to Government if new Act becomes law.

AT first glance, the changes to the Wireless Telegraphy Act outlined in the recently published Bill appear to be a bold attempt to remedy some long outstanding ills. Strong measures are suggested for dealing with TV licence dodgers and evaders of car radio licences. But the section dealing with illegal radio transmitting merits a much closer investigation.

This journal has long campaigned for action to resolve the ludicrous situation whereby it is perfectly legal to import, offer for sale and buy 27Mc/s walkie talkies and yet impossible to use them without breaking the law. The Board of Trade, the GPO and radio dealers have for years shrugged off responsibility with some agility.

In the new Bill, the PMG introduces provisions presumably to deal with this situation and that of radio bugging devices. Presumably, we say, because in the potentially explosive Clause 7 it states that "where it appears to the PMG to be expedient", the provisions should "apply to wireless telegraphy apparatus of any class or description" and that "no persons shall manufacture any apparatus of that class or description whether or not for sale".

This loose phraseology could be interpreted to cover any form of radio apparatus deemed to be "undesirable" and amounts virtually to a blanket control over the manufacture, importation, sale and *construction* of radio equipment of any type which the Government considers undesirable.

We do not say that the PMG intends to use the sweeping powers implicit in the seven sub-sections of Clause 7, nor even that he has considered them in detail, but the fact remains that if this Bill becomes law as it stands, these powers will not only be available to the present administration but to all future PMGs.

In seeking to deal with specific problems the PMG has wielded a bludgeon. If classification is difficult it would have been better to isolate the real objectives by making it illegal to sell or buy *any* transmitting equipment except on the production of a suitable transmitting licence. This way, innocent bystanders would not get involved. Unless, of course, the PMG has more sinister motives.

W. N. STEVENS—*Editor*

NEWS AND COMMENT

Leader	97
News and Comment	98, 122
Audio Fair Report	104
On the Short Waves <i>by John Guttridge and David Gibson, G3JDG</i>	129
Practically Wireless <i>by Henry</i>	133
New Books	145

CONSTRUCTIONAL

The "Denette" <i>by P. Matthews</i>	100
Keying the Ten-Five Tx <i>by A. S. Carpenter, G3TYJ</i>	103
Dual Function Signal Generator <i>by H. Webster</i>	115
Simple Transistor Tester <i>by G. A. Bobker</i>	120
Vibrato and Tremolo Units <i>by A. J. Bassett</i>	124
4-Channel Mixer/Amplifier <i>by F. L. Thurston</i>	134

GENERAL ARTICLES

Repairing Radio Sets, Part III <i>by Gordon J. King</i>	107
--	-----

JULY ISSUE WILL BE PUBLISHED ON JUNE 9th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes London, W.C.2. Subscription rates, including postage: 36s. per year to any part of the world. © George Newnes Ltd., 1967. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Kits a success

During the past eight years I have built kits supplied by seven of your regular advertisers and I cannot fault one of them. In all cases the instructions were clear and easy to follow.

I think those who make claims that their kits can be built in an hour are not helping their own cause. Who wants to build a kit in an hour anyway? It is a hobby and how much better to make the interest last for a few days at least. There are sure to be setbacks, then out comes the test-meter and the interest is extended further.

Most early efforts fail because of poor soldering, through getting resistor values mixed up and switch and coil connections wrong.

I do not grudge the charge of 6d. per valve, bearing in mind the cost to the retailer of cartons, corrugated paper, packer's wages, etc. I would give a vote of thanks to the firms who send me good valves promptly, cheaply and beautifully packed.

P. J. Plater.

Wallington,
Surrey.

★ ★ ★

Mr. A. H. Brough of Staffordshire (P.W. May issue) will probably find that most firms specify P. & P., and packing involves corrugated card, cartons and often stout cardboard boxes, also employment of a packer and checker, all of which has to be paid for to ensure adequate protection in transit.

A. Deverell.

Rickmansworth,
Hertfordshire.

U.S. Citizens' Band

After reading the column "Amateur Bands" in the May 1967 issue, it appears to me that there is some confusion concerning Citizens' Band licences in the United States. As an American now living in England, perhaps I can straighten out the situation.

A Citizens' Band licence may be issued to any U.S. citizen over the age of 18 with no exam. required. A fee of \$8.00 (£2 17s. 2d.) is charged, and the licence allows the bearer to transmit on the 27Mc/s band with a power not exceeding 5 watts. A call sign is assigned which usually consists of a three letter prefix followed by four numbers.


Any person, regardless of age, may use Citizen Band frequencies so long as the transmitter power does not exceed 100mW, and a vertical antenna of not more than 60 inches in length is used. No call signs are issued to these people, as they are not required to register with the Federal Communications Commission.

D. L. Potash.

Ambleside,
Westmorland.

NEWS AND..

VHF STEREO TRANSMISSIONS

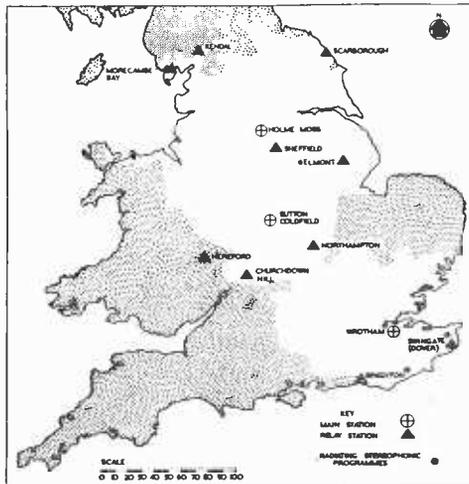


Work is in hand to extend the BBC stereophonic transmissions, at present radiated from Wrotham, Swingate and Brighton, to Sutton Coldfield and Holme Moss and certain relay stations fed from them, early in 1968. The unshaded part of the map indicates the areas in which satisfactory stereophonic reception should normally be obtained. In places where the field-strength is low, increased background noise may be heard on stereophonic programmes; improvements to the receiving aerial enable the noise level to be reduced.

ELECTRONICS CONFERENCE IN GREAT BRITAIN

A Technical Conference and Exhibition devoted to the engineers who build and produce electronic equipment will be held at Brighton in October 1968. This is the first such conference and exhibition ever to be held in this country or Europe.

Called NEP/CON-INTERNATIONAL it has for some time been held twice-yearly in the U.S., and will present a wide-ranging international technical programme. It will cover the most recently developed techniques such as printed circuitry, micro-miniaturisation, component and equipment manufacture etc. Talks will be given by leading engineers from the U.S., U.K. and Western Europe. Also there will be an exhibition where the latest components materials and machines will be on display.

SUB-MINIATURE METER

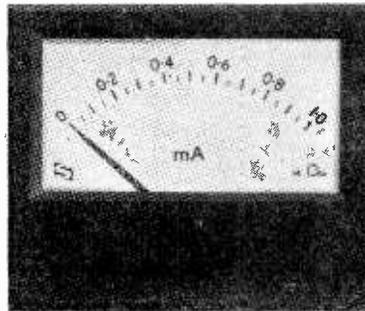

Sifam Electrical Instrument Co. Ltd., Woodland Road, Torquay, Devon, have introduced a new sub-miniature instrument in the "Director" series of moving-coil instruments.

The new "Director 14" is exceptionally compact, having an overall size of 1.92in. by 1.65in. with a scale length of 1.34in. It is flush mounting requiring a panel cutout of 1.5in. diameter.

The company emphasises that, despite its size, the instrument is a glazed-front, quality unit built to BS89: 1954 accuracies (i.e. ± 2.5 per cent of full-scale deflection). The case is made from a special reinforced plastic with a matt black finish, resulting in an elegant yet highly practical case style, which blends well with modern equipment panels.

... COMMENT

PANEL LIGHTS TO ELECTRIC ORGANS

From Henry's Radio Ltd. comes the 1967 Electronic Components, Equipment and High Fidelity Catalogue. This edition—now over 200 pages—is more comprehensive than those published in previous years and includes details of many new items supplied by Henry's, including their Mayfair Portable Electronic Organ.

Included in this issue are five free discount vouchers which when used enable the customer to obtain 2s. in the pound discount. It is also interesting to note that further discounts are allowed for equipment in the Hi-Fi section of the catalogue.

The price of the catalogue is 7s. 6d. plus 1s. postage and copies may be obtained from Henry's Radio Ltd., 303 Edgware Road, London, W2.



PIRATES—ALL OR NOTHING

Discussing the Marine and Broadcasting (Offences) Bill in the House of Commons recently, Mr. Ian Gilmour unsuccessfully suggested that the Government should restrict the scope and impact of some offences covered by the Bill. He maintained there was no reason why penalties should be imposed on scriptwriters and others who provided material for the pirates. He had not, however any objection to imposing penalties on those who ran the pirate stations. Answering, the Postmaster General, Mr. Edward Short, said to omit the clause from the Bill would enable the pirates to continue receiving advertising revenue, records and tapes, etc., from which they made up their programmes and attracted an audience. It would make the legislation almost ineffective. Publication of information about future programmes of the pirate stations is to be prohibited.

The Bill had been carefully drafted, Mr. Short told the House, to catch only things which served as advertisements. References to past broadcasts would not be affected by the Bill but references to future broadcasts would be. Also anybody in this country giving assistance to the pirates will be liable when the Bill becomes an Act.

Referring to Clause 6 of the Bill (Penalties and Legal Proceedings) Mr. Short moved an amendment to increase the maximum penalty for unlicensed transmitting from £100 to £400. He maintained that £100 was nothing more than petty cash to a successful pirate broadcaster.

ELECTRIC EYE HELPS TO TUNE



From Philips comes a new four waveband portable costing 19½ guineas. Included in the features is an "electric eye" tuning guide which doubles up as a battery condition tester. Another feature is a separate battery cartridge holding four U11 batteries which is released from the radio at the touch of a button. Wavebands covered are long, medium, short and f.m. Output is 380mW, and a telescopic aerial is provided for reception on v.h.f. and s.w. Cabinet measures 9½ x 5 x 1½ in. and is finished in black polystyrene with silver grille.

New members wanted

I am writing on behalf of the Sheffield Amateur Radio Club which urgently needs new members. Anyone interested in any aspect of radio, especially amateur radio and short wave listening would be most welcome at any of our meetings. These are held every Friday evening at 8.00 p.m. at 8 Sandbeck Place, Sheffield 11.

Anyone requiring further information or details on how to reach the club H.Q. should contact me at the address below.

G. Watson. 25 Underwood Road,
Woodseats,
Sheffield 8,
Yorkshire.

Well done Sirs

I am writing this letter to express admiration of two 60-year-old gentlemen whose letters appeared during 1965 stating that they had obtained their Amateur licences. These gentlemen fired my enthusiasm and I started to study for the RAE in October 1965 and passed in May 1966. I then started Morse practice and received my Pass slip recently.

I hope that this letter will encourage others, as I myself am 47 years of age.

All study was done at home from library books and guidance obtained from the RSGB Radio Amateurs' Examination Manual and a study of five years' examination papers. The Morse code was also self-taught by means of an oscillator and a tape recorder.

F. Woolliscroft.

Whitley Bay,
Northumberland.

The spirit of readers

You printed a request in your "CQ" column for me in the May issue of this journal and within hours of PRACTICAL WIRELESS being on sale I had a satisfactory reply. In fact, someone personally brought around the "wanted" magazines and many other readers wrote to me.

I. Nicholls.

Kilburn,
London, N.W.6.

U.K. Police State?

I would like to bring to the attention of other readers that if the Government gets its own way on the amendments to the Wireless Telegraphy Act, we shall be told what we can build and what we cannot. This is very wrong and I suggest readers in agreement with me write to the P.M.G. personally—Edward Short, M.P., House of Commons.

C. Rolls.



Highgate,
London, N.6.

[We are not very keen on the Government's proposals, for it covers virtually anything: see the Leader page for our views.]—Editor

More News and Comment on Page 122

THE DENETTE

P. MATTHEWS

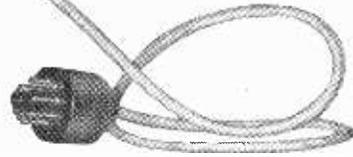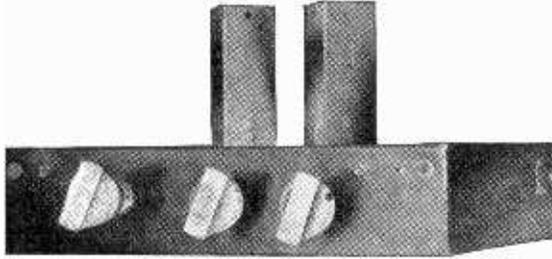

THE "Denette" is an easy-to-build receiver designed for use as a small mains portable. It is ideal for the kitchen or den where high quality sound reproduction is not essential. The controls on the prototype are tuning (which could be switched), volume, and fine reaction which is not required for local station reception. Both coarse reaction and tone are pre-set but could be brought out to separate controls on the front panel if desired. With a three foot piece of flex as an aerial the sensitivity is comparable to the average transistor portable, and in Northern Scotland the prototype receives Radio Luxembourg very well after dark.

The receiver contains very few components most of which are not critical, the circuit is thus ideal for experimentation. Both long and shortwave coverage can easily be added by the addition of

suitable coils and a wavechange switch. This modification is described later in detail. Although two modern miniature valves are specified using B9A valveholders, the older octal-based types such as the 6SL7 and 6V6 should function equally well. If these older valves are used then the valvebases should be wired accordingly, since the pin connections are different to the B9A base wiring shown in the circuit and layout diagrams.

CIRCUIT DESCRIPTION

The two-valve circuit contains three stages—detector, a.f. amplifier and output. The power supply unit (p.s.u.) is built on a separate chassis which enables it to be used to power other equipment.

The regenerative detector (V1A) has unusual input circuitry. The signal from the aerial is fed to a capacitive potential divider consisting of C1/C2, through the tuning coil L1 to the grid of V1A. The d.c. continuity between grid and chassis is established by the grid leak R2, and resistor R1 is wired between aerial and earth to prevent a charge building up on the aerial. Feedback is effected by L2 and TC1, the fine control being made by adjustment of VR1. Note that TC1 is insulated from the chassis. Slight detuning is evident because VCI is across the valve grid-to-cathode capacitance which alters slightly as the valve warms up. Detuning is also affected to some slight degree as the reaction is varied, but these effects are small and are thus ignored. The value of the anode load resistor R4 may be adjusted if regeneration cannot be readily obtained. Other methods of obtaining regeneration

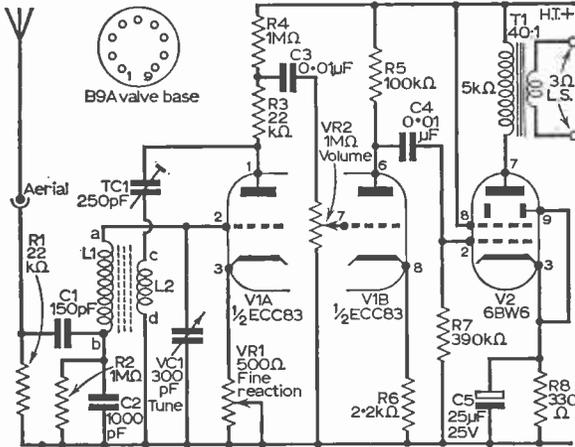


Fig. 1 (above): Circuit diagram of the Denette.

Fig. 2 (below): Suggested power supply circuit.

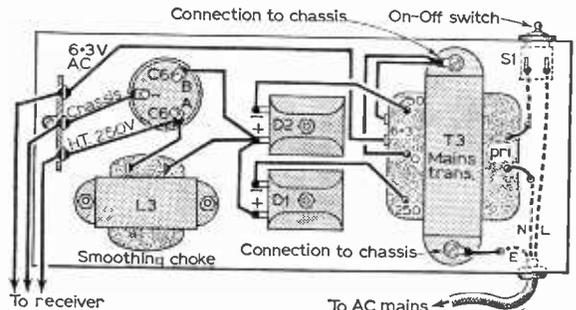
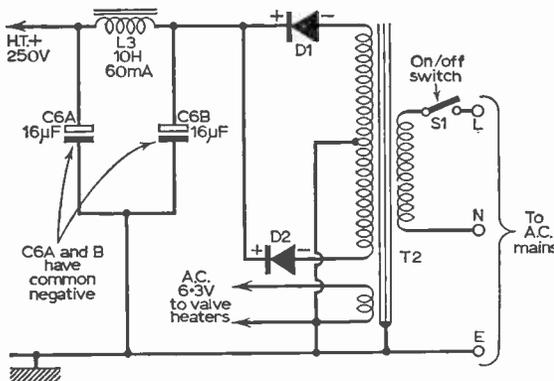


Fig. 3: Layout of the power supply shown in fig. 2.

are possible, however the method used works out very well. For those who like to experiment, the different "textbook" methods could be tried out.

From the junction of R3/R4 the detected signal passes via C3 and VR2 to the grid of the audio frequency (a.f.) amplifier V1B. This is an a.f. stage of conventional design other than the omission of the cathode by-pass capacitor usually wired in parallel with R6. In order to cut down the bass response when a miniature speaker is used, the cathode decoupling capacitor C5 may be reduced to 2 μ F. This will help prevent undue damage to the small speaker due to bass overloading. This step will not be necessary with the larger type of speaker. When using a small speaker, R8 could be increased to 1k Ω , this will limit the output and effect some economy.

POWER SUPPLY

The power unit is straightforward, using two contact-cooled metal rectifiers in a full-wave circuit. A valve, such as the EZ80, could be fitted in place of D1/D2, but this would require to be fed with 6.3 volts and would also contribute considerable heat. A double-wound mains transformer is strongly recommended and suitable types are readily obtainable from advertisers in this journal. It would be possible to make use of a miniature 220 volt 20/25mA mains transformer of the type used in tuners and preamps. In this case R8 should be increased to 1k Ω in order to reduce the current consumption.

MODIFICATIONS

Although the tuning capacitor VC1 gives satisfactory station separation on the medium and long wavebands, crowding occurs on the short waves. To combat this it is suggested that the s.w. band be split into two sections, and that the effective

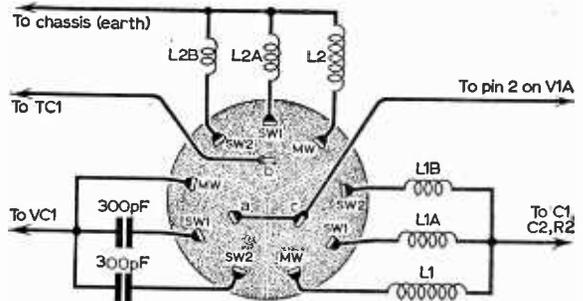


Fig. 6: Rear view of the wavechange switch for three-band coverage.

capacitance of VC1 be reduced. This latter suggestion can be easily performed by interposing a capacitor between VC1 and the junction of terminal a on L1, and pin 2 of V1A. By placing a fixed capacitor in series with VC1 in this way, the effective swing or tuning range of VC1 is restricted to a portion of the band. However, since this small portion of the band is now spread out over the entire 180° swing of VC1 instead of a few degrees, the stations received will be easier to tune. If the extra capacitor is made 300pF to start with, the constructor can experiment from there.

If band switching is required then a suggested method is shown in Fig. 6. As shown, the switch will give three-waveband coverage, the actual wavelengths covered depending on the coils used. Details for suitable coils are given later on.

Other worth-while modifications are a tone control and a socket for headphone reception. The simple top-cut control shown in Fig. 5 works well. The voltage rating of the capacitor between the anode and the headphone socket must be at least 1.5 times the nominal h.t. voltage. Do not fit a

Fig. 5 (below): Suggestions for the inclusion of a tone control and for using headphones. It would be unwise to use a capacitor of less than 400V working in the phones lead to the anode of the valve.

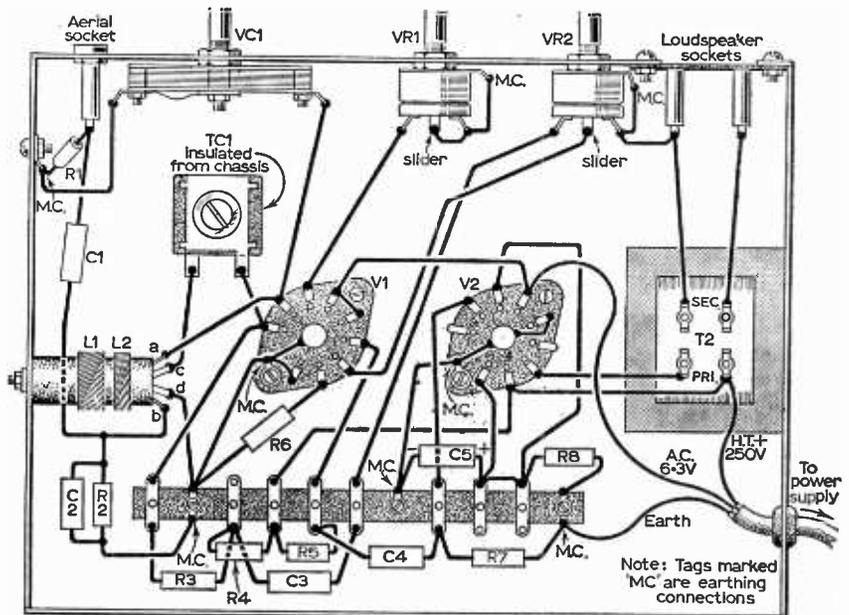
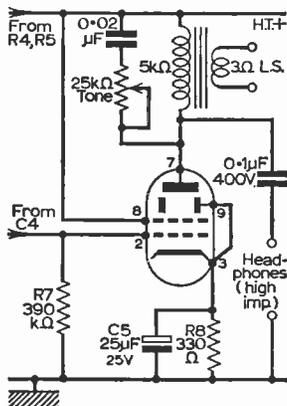


Fig. 4: Layout of components and wiring below chassis. Note that TC1 must be insulated from the chassis. This is essential for the circuit to function properly.

"normally closed" jack socket or this will short the signal to earth when the phones are removed.

CONSTRUCTION

The following procedure is recommended when all the parts, including the chassis have been obtained. Drill the chassis and mount all components securely. Wire up the power unit starting with the mains transformer. Wire the heaters of the valves with twisted leads and plug in both valves. After a careful check of the wiring switch on and note that the heaters inside the valves light up. If they do not, switch off immediately and re-check the wiring.

Switch off, unplug the valves and disconnect the power supply unit from the mains. Proceed with the wiring up of V2 starting with the output transformer working back to R7. Keep all leads as short as possible. Fit one end of C4 to pin 2 of V2

COIL	NO. OF TURNS	WAVEBAND
L1	45	} MW
L2	5	
L1a	12	} SW1
L2a	1-2	
L1b	5	} SW2
L2b	1-2	

The table shows details of the coils. The type of wire and former diameter are mentioned in the text.

and temporarily solder a wire to the other end. After checking the wiring plug in V2 only, connect the loudspeaker and switch on. After the valve has warmed up there should be a slight hum from the speaker, this should increase as the wire on C4 is touched. There should be no whistling or clicking nor any instability. If the stage is functioning properly switch off, remove the wire from C4 and unplug the valve.

Wire up V1B and fit one end of C3 to the volume control VR2. Check the wiring and plug in both valves. Repeat the test for V2. As the wire from C3 is approached a loud hum should be heard. If all is satisfactory switch off, unplug the valves.

Wire up V1A taking every care to keep connections short and direct. Unscrew TC1 to minimum capacitance and set VR1 to maximum resistance. Now check all wiring very carefully as this last stage is more complex. Plug in the valves and the aerial (2 or 3 yards of flex), then switch on. There should be no howling or whistling, if there is reduce the coupling i.e. the distance between L1 and L2. If preferred the number of turns on L2 may be reduced instead. Now screw up TC1 to the point where howling or whistling just commences. Tune in a station, backing down VR1 until oscillation has just stopped. This is the most sensitive position for the set. Retune VC1 if necessary and set the volume control to a convenient level. Switch off taking care not to touch the h.t. line without first discharging the capacitors C6a and C6b to chassis. Check all components to ensure that there has been no overheating. The receiver may now be enclosed in its cabinet.

COILS

The medium wave coil on the prototype consisted of 45 turns of 22s.w.g. enamelled copper

★ components list

Resistors:

R1	22k Ω	R5	100k Ω
R2	1M Ω	R6	2.2k Ω 10%
R3	22k Ω	R7	390k Ω
R4	1M Ω ½ watt	R8	330 Ω

Capacitors:

C1	150pF	C5	25 μ F 25V	} electrolytics
C2	1000pF	C6A	} 16 + 16 μ F	
C3	0.01 μ F	C6B		
C4	0.01 μ F			
TC1	250pF compression trimmer			
VC1	300pF variable, solid dielectric			

Valves:

V1	ECC83
V2	6BW6

Diodes:

D1	Contact-cooled metal
D2	rectifiers 250V 60mA

Potentiometers:

VR1	500 Ω	VR2	1M Ω
-----	--------------	-----	-------------

Inductors:

L1	} see text
L2	
L3	L.F. Choke 10H 60mA
T1	Output transformer ratio 40:1 suitable for mains pentode.
T2	Mains transformer 250-0-250V 60mA, 6.3V 3A.

Miscellaneous:

Two B9A valveholders, tagstrip, ¼in. coil former, chassis, nuts, bolts, solder, wire, 1 Pole 2 Way on/off switch, wire for coils.

COMPONENTS FOR MODIFICATIONS

Tone Control:

25k Ω potentiometer
0.02 μ F capacitor

Headphone Reception:

Normally open jack socket
0.1 μ F 400V capacitor

Wavechange:

3 Pole 3 Way rotary switch, Extra coil formers, Wire for coils, Two 300pF capacitors

wire pile wound, with L2, five turns, wound over the top. The former was ¼in. diameter fitted with an adjustable dust core. The former size is not critical except that the number of turns will need to be adjusted if the former is a different diameter to that specified. A long wave coil would require 140 turns for L1 and around 13 turns for L2. For short wave coverage less turns will be needed and if the wire used is thick enough no former will be required since the turns can be self-supporting. If the diameter is about one inch and the wire 16-20s.w.g. then between 5-12 turns for L1 and 1 or 2 turns for L2 will give coverage of 19-49 metres. These turns should be wound side by side on the same axis. ■

PRACTICAL ELECTRONICS

special project

★ MINIATURE R/C INSTALLATIONS ★

plus

★ CRO Trace Doubler ★

★ Video Pattern Generator ★

ON SALE MAY 12

SOME IMPRESSIONS OF THE 1967 INTERNATIONAL AUDIO FESTIVAL AND FAIR AT THE HOTEL RUSSELL, LONDON, MARCH 30 TO APRIL 2, AS SEEN BY THE P.W. TEAM.

Spread among the exhibition stands and hotel rooms were the static displays and live demonstrations of 96 exhibitors, an Aladdin's Cave for the audiophile. Readers familiar with the hustle and bustle of the Fair will appreciate the difficulty in seeing everything in the time available. The following notes are not intended as a comprehensive survey, but mainly impressions on trends.

Amplifiers, Tuners and Stereo

IN this field the steady migration towards semi-conductors continues. Some years ago, H. J. Leak, in his presidential address to the B.S.R.A. observed, that for power outputs of up to 15 watts per channel the valve could no longer compete with the transistor. At the Fair, transistor amplifiers in the hi-fi class were commonly offered with outputs of up to 110 watts, and although it is difficult to appreciate listening to this output in the average living room, it does indicate the advances in transistors. Most manufacturers were not content to state that the equipment was "fully transistorised" but plugged that they were silicon types. So it looks like the trend this year for amplifier enthusiasts is to acquire a "Silicon Solid Status".

The complexity of the units seems to grow each year. One can remember not so long ago being content with volume, treble and bass. Now one sees miniature Jodrell Bank-type front panels with Low-filter; High-filter; Equalisation; Input selector; Balance; Stereo reverse (should be interesting); Stereo left; Stereo right; Stereo left + right etc.

Stereo was very much in evidence and mostly solid state. The trend here was split right down the middle as regards units. Some were complete with amplifier, preamp and both speakers all in one package. Others had one or both speakers floating. Many speakers and indeed amplifiers were of the "bookshelf" type, usually in a matt wood. Listening to "Uranus" from the Planet Suite on stereo with large enclosures some 3ft. cube, and then on a couple of the small twelve inch bookshelf cabinets gave a vivid demonstration of the efficiency of the




smaller units. They did lack the roundness in the bass, but the reproduction nevertheless was exceptionally good.

Prices varied, but on the whole were high, some very high. Perhaps the common-sense way in buying would be to say—if I'm satisfied with the performance of cheaper equipment then it's pointless to spend more, but if I want the ultimate in quality and my ears can appreciate the difference, then I will pay for quality.

All things considered there was nothing really startling at this year's Audio Fair. Most of the units on show are already displayed in the dealers' windows and have been for some time. Summing it all up: Transistors now outnumbered valves. Stereo is becoming commonplace and trends indicate that before long it could well be stereo only, since the units can receive and/or play mono too. Prices are high but then so is performance, and there are more knobs to twiddle. Bookshelf units are advancing with the advance in the frequency response of smaller speakers.

Perhaps next year we will have vest pocket stereo, but we wonder how they'll fit all those controls in!

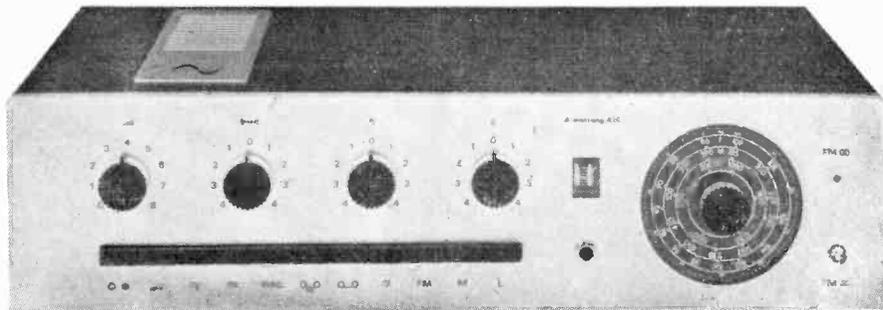The Armstrong 426 is an example of the growing complexity of audio units and the tendency towards "integration".



Tape Recorders

New trends this year in the tape recorder field were hard to find. The most noticeable was that more machines were making use of cassette loading. Also, we noticed fewer low-priced machines and more with comprehensive mixing and dubbing facilities. More are becoming available for vertical operation.

Philips, who pioneered the cassette-loading recorder market in the UK, released another battery-operated machine at the show—the EL 3302. Similar to its predecessors, it has almost double the audio output at 400mW, and an external loudspeaker socket. The price remains 27gns. Also from Philips come two mains-operated cassette-loading tape recorders—one stereo and one mono.

The range of Philips pre-recorded “Musicassettes” can be used on all of their cassette-loaded machines, and there are over 100 different mono/stereo Musicassettes available from the repertoires of EMI, Philips and Pye records.

Grundig's latest cassette-loading tape recorder, the C110, is also a mains-operated machine. Although it measures only $13\frac{3}{4} \times 9 \times 4\frac{1}{2}$ in., it has a two-watt push-pull amplifier and seven-inch elliptical speaker. Using the half-track recording system, it has a recording and play-back time (for DC90 tape) of approximately $1\frac{1}{2}$ hours. The technical specification gives a wow and flutter figure of better than $\pm 0.4\%$, a frequency range of 50c/s to 10kc/s, and a signal-to-noise ratio of better than 45dB. Grundig claim this machine to be virtually foolproof—click-in cassette loading, simple press-button controls, a green light to indicate the machine is switched on and a red warning light when the recording button is depressed. The price is 48gns.

Most of the four-track machines shown this year have comprehensive mixing facilities, permitting one to record on one channel while listening to the other. To permit this, three tape heads and independent and play-back amplifiers are necessary. An example is the Truvox R104 at 89gns. This machine, which has been on the market for some time now, has the facility aptly labelled *duo-play*.

The *Fidela* range of four-track tape desks and recorders from the Waltham Electronics Company of Geneva (handled in this country by Denham and Morley Ltd.) attracted a lot of attention for they were on show for the first time in this country. All of these are suitable for vertical or horizontal operation. The recorders have solid-state amplifiers and attractive specifications along with appropriate price tags—75 and 138gns. The tape decks are also expensive; Model 707 costs 119gns, but it comes complete with separate record and play-back amplifiers having a 30c/s to 22kc/s frequency response. The other deck, Model 780 at 145gns, also features adjustable bias for optimum performance with different types of tape.

Among the Telefunken exhibits were the Magnotophon 200 series of vertical and horizontal recorders. The 204E is a two-speed ($3\frac{1}{2}$ and $7\frac{1}{2}$ in.) stereo machine with a frequency range extending up to 18kc/s on the higher speed. This 106gn. machine has comprehensive mixing facilities.

Another semi-professional performance/stereo machine is the Tandberg Series 6x. This ‘x’ series is similar to earlier models, but incorporate an additional bias head, improved frequency response and




One of the Fidela vertical tape recorders shown for the first time at the Audio Fair.

signal-to-noise ratio—within 2dB from 20c/s to 25kc/s and a 62dB signal-to-noise figure on the fastest speed of $7\frac{1}{2}$ in./sec. Wow is less than 0.1% and crosstalk rejection is better than 60dB. Two and four-track recorders using this deck are offered at 115gns.

The newest model in the Uher range of professional recorders is the 1000 Report Pilot. With this machine, one can synchronise sound with film as well as reporting under professional conditions. Features of this £243 portable recorder include

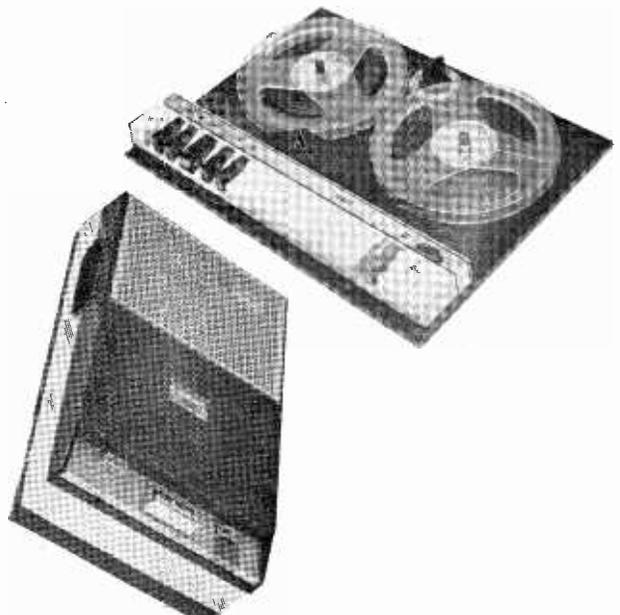Latest in the range of BSR popular tape decks—The TD20, available with a wide range of stereo or mono head arrangements.



One of the growing range of cassette tape recorders—the new Philips Model EL3302.

stroboscopic tape speed control and switchable equalisation. It has only one tape speed— $7\frac{1}{2}$ in./sec.

BSR's latest three-speed tape deck, the TD20, introduced at the end of last year, was prominently displayed. It is available in both stereo and mono versions with two or four-track heads. The control linkage has been improved and only requires the lightest pressure to operate the direct-action keys. Wow and flutter is claimed to be better than 0.15% on $7\frac{1}{2}$ in./sec., 0.25% on $3\frac{1}{2}$ in./sec., and better than 0.35% on $1\frac{1}{2}$ in./sec. It will take up to seven-inch reels and there is provision for a third head.

Tape Recorder Developments Ltd., who announced their first tape deck just over a year ago had on show seven variations of their TRD 1 deck, and silicon semiconductor electronic units to complete a hi-fi system—with any of the deck variations. As an indication to the type of deck, the wow and flutter specification is as follows: 0.04% at 30in./sec.; 0.05% at 15in./sec.; 0.08% at $7\frac{1}{2}$ in./sec.; 0.13% at $3\frac{1}{2}$ in./sec.; 0.2% at $1\frac{1}{2}$ in./sec.; and 0.35% at $\frac{1}{2}$ in./sec.

Tape Recorder Spares Limited had their usual wide range of pre-packed leads, plugs and accessories. Often it is not realised that this company deals with more than tape recorder accessories. In fact, they have a very wide range of connectors that could well solve many problems of the hi-fi and audio enthusiasts.

Microphones and Pickups

It is a very far cry from the carbon granules of yesteryear to the array of sophisticated microphones now available on the market; microphones of range and diversity to meet all requirements and depths of pocket.


One of the new developments noted at the Fair was a dynamic unit by AKG which combines two moving coil capsules, one covering high frequencies, one covering low frequencies. Philips also



A trend in speaker enclosures—the Celestion Ditton 3-element 15-watt system for bookshelf mounting.

had a unit with two moving coil units; this was a stereo type (Model EL179) in which the two m.c. units are detachable.

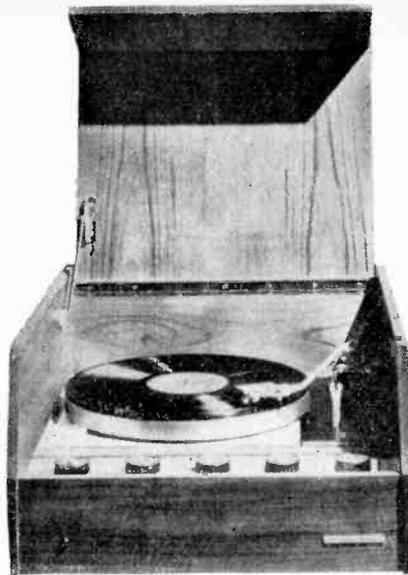Another interesting model was the Sennheiser unit which combines the directional properties of the gun microphone and the high performance of a condenser (or should we say capacitor?) micro-



Parmeko stereo record reproducer incorporating the latest in pickups—the Miniconic transistor cartridge.

phone. It is in fact, a transistorised r.f. condenser type.

It is impossible in this space to detail the many mentionable microphones on show, but those which attracted our attention included the new series of subminiature ribbon units by Lustraphone, the new Unisphere models by Shure which are based on the Unidyne dynamic cardioid type, the three new dynamic models from M.B. Mikrofonbau and the latest high-quality cardioid microphone from STC—who also showed for the first time the 4119 hyper-cardioid ribbon microphone.

Pickups, cartridges and gramophone decks, as to be expected, showed a general tendency to higher efficiency and slicker presentation. The most unusual exhibit was the new semiconductor stereo pickup introduced by Miniconic.

Insensitive to hum fields and turntable noise, the pickup is claimed to have a power output 40dB greater than a magnetic cartridge, 20dB greater than a ceramic cartridge. It functions by modulating the flow of d.c. provided by the amplifier power supply through a semiconductor strain gauge element (the resistance of which varies as the stylus is flexed) to produce signal current variations. In other words, energy is provided by an external source and not, as conventionally, by the record groove. The makers claim a frequency response of an octave below and two octaves above audible range, reduced record wear and chatter, a cleaner signal with increased dynamic range. The first British stereo equipment to incorporate this revolutionary pickup is the System 22 system marketed by Parmeko.

Also new at the Fair was the range of moving magnet stereo cartridges by Audio Technica, the new Studio 1000 range of amplifiers, tuners and speaker units by Braun and the *ffss* Mark 4 heads and cartridges by Decca. Focus of interest on the Garrard stand was their new Model 50 automatic turntable unit which incorporates pause and cue control, tubular pickup arm and calibrated force adjustment. ■

repairing radio sets

PART 3 GORDON J. KING

Having heard from H. W. Hellyer (last month) on the use and choice of tools and service equipment we now continue with fault symptoms in the "electronics" of the animal and thence to their diagnosis.

Part 1 investigated the first two or three stages of a typical valved receiver. These stages collectively are often referred to as front ends, being composed of r.f. amplifier (if the set has one), mixer and local oscillator. Modern a.m./f.m. sets have two front-ends, one for medium-frequency (and possible short-wave) a.m. and another for v.h.f./f.m.

FRONT-END NORMAL

Assuming that first tests failed to reveal any conclusive defect in the front-end, we can conclude that the mixer, or that section of the frequency changer, is delivering off-the-air signals converted to i.f. as they are tuned in by the set's dial. Something, then, is preventing these signals from reaching the detector and later stages. That is, assuming the symptom is the easy one of "no signals" or "set dead".

The best plan under these circumstances is to apply a modulated signal at the set's i.f. to the input of the first i.f. amplifier. A straightforward valved set usually has a single i.f. amplifier stage, a typical circuit being shown in Fig. 3—1.

Here the control (first) grid of the i.f. amplifier valve receives an i.f. signal from the secondary winding of the first i.f. transformer, whose primary


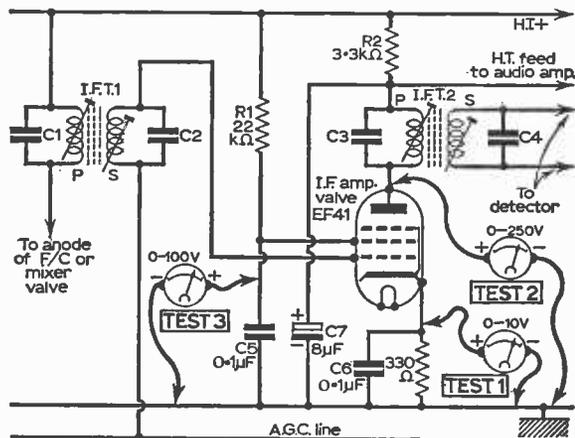


Fig. 3—1: Typical a.m.-only i.f. stage, showing three prime tests.

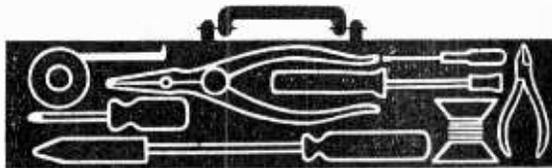

is loaded into the anode circuit of the mixer or frequency-changer valve. It should be understood that the nature of this testing for a "dead set" starts at the aerial input, works through to the frequency-changer, checks the local oscillator (as in Part 1) and then goes on to the i.f. stages, commencing at the input of the first i.f. amplifier valve (Fig. 3—1).

Assume that we have a signal generator and tune it to the set's i.f. (recent models 470kc/s, earlier models 465kc/s), then switch on the audio modulation and apply the signal to the control grid of the first i.f. valve. Signal continuity from this grid to the loudspeaker should give a modulated tone output. If there is no response the next move is to check the i.f. stage up to the detector input. If discontinuity remains, then the trouble is either in the detector or audio stages (to be considered in Part 5).

Useful first-action tests are (i) check that the i.f. valve heater is alight (change valve and/or check heater supply circuit if not) (ii) check the valve envelope for temperature with a hand (a "cold" valve—with heater alight—could indicate lack of anode and screen grid current) and (iii) try tapping the valve with the set running to establish the possible presence of internal inter-electrode shorts or open-circuits.

BASIC D.C. TEST

If these tests give no clues to the fault, a more scientific approach will be necessary. A good test for valve emission is to measure the voltage across the cathode resistor (see Test 1). A valve normally operating will yield about 2.2 volts d.c. across this resistor. A test voltage appears because the sum of the anode and screen-grid current passes through the cathode resistor, and this develops a voltage drop across it of magnitude depending (a) on the value of the resistor and (b) on the current value.

It is easy to find the cathode current (in mA) by dividing the voltage measured (in volts) by the value of resistance in kilohms (thousands of ohms). For example, 4 volts measured across 500Ω (0.5kΩ) signifies a current of 8mA.

If this first basic or "key" test indicates cathode current, we are sure that: (i) the valve has emission, (ii) its heater is aglow, (iii) the valve has both anode and screen grid voltage and (iv) the general d.c. conditions of the stage are reasonable—if not normal. A more exacting indication on the d.c. conditions can be obtained from a knowledge of the anode and screen grid (i.e., cathode) current of the valve in the circuit. Such operating parameters are

usually given in the service sheet, manual, or valve data book.

Abnormally low cathode current could mean (a) low emission valve, (b) low screen grid voltage, (c) low anode voltage or (d) reduced heater current. (This is often overlooked.)

To establish (a), **Tests 2 and 3** (see Fig. 3—1) would be made, and if the anode and screen grid voltages are reasonable (refer to service sheet, if possible), check the valve either by substitution (often the best way) or with a valvetester. Typical values are *anode 225 volts and screen grid 100 volts*.

So far we have established that the i.f. signal cannot be passed through the set from the control grid of the i.f. amplifier valve and, assuming Tests 1, 2 and 3 to be positive, that the d.c. conditions of the stage are reasonable.

There is a remote chance that the valve has some internal short or open-circuit which is failing to affect the d.c. conditions yet preventing the passage of signal. A sharp tap on the envelope of the valve with a screwdriver handle may prove something here; but valve substitution is much more conclusive a test in a case like this.

Some enthusiasts may not possess a signal generator or other equipment, yet may wish to try their hands at radio repairs. Where possible, therefore, suggestions based on instrument-less testing will be included. One instrument, however, is indispensable and that is a good quality multirange testmeter with a d.c. sensitivity not less than 10,000 ohms/volt (bearing in mind that low voltage and current readings may have to be made in transistor equipment).

Signal continuity in the i.f. stage can sometimes be proved by connecting an aerial to the control grid. This should pick up random signals in the i.f. band and reproduce them in the loudspeaker. Another dodge is connecting the contact points of a low-voltage electric buzzer between chassis and the control grid via a 100pF capacitor. The impulsive "signal" produced by the working buzzer contains many harmonic components well into the i.f. band, and signal continuity is revealed by a harsh buzz in the speaker. This, of course, also proves the detector and audio stages at the same time. Special transistor, pulse generating signal continuity test instruments are also available commercially, but there is nothing to beat a good modulated signal generator.

I.F. stage continuity can also be vaguely assessed by rubbing the tip of a screwdriver blade on the control grid pin of the i.f. valve while holding a finger in contact with the metal blade. Good response in the i.f. channel is then indicated by fairly loud crackles from the speaker when the test is performed.

DYNAMIC TROUBLE

We now assume that the d.c. conditions are normal, yet the signal fails to pass through the stage. This is often called "dynamic trouble", signal rather than d.c. A prime factor here is misalignment of the i.f. transformers. These are best checked—and aligned—by a modulated signal generator, as explained in Part 1 (April issue).

It will be recalled that the signal is applied to the signal grid of the frequency-changer valve (at fairly high level if the circuits are well out of

alignment) and then the *second* and first i.f. transformers adjusted—secondary and then primary—aiming for maximum output at the detector or audio stage.

ALIGNING THE I.F.'s WITHOUT INSTRUMENTS

It is possible to align the i.f.'s. without a signal generator, assuming that the front-end circuits are in alignment. The technique is first to bring the i.f. windings to exactly the same frequency, irrespective of the *actual* frequency. This can be done by "clicking" the screwdriver blade on the frequency-changer signal grid or by the use of a buzzer (as already explained) or other pulse-type harmonic generator and adjusting the i.f. trimmers or cores, one after the other, until maximum output is attained. The circuits will all be tuned to the *same* frequency, not necessarily the *correct* one.

Next, apply an aerial signal with the set tuned to the longwave Light Programme. Since the i.f.'s will most likely not be tuned to their correct frequency, the Light Programme will come in well off tune and possibly weakly, so full volume setting must be used.

The i.f.'s. can then be tuned nearer to the correct frequency by adjusting the main tuning so that the Light Programme can still be heard yet may still be off tune although closer to the actual 1,500 metre mark on the dial. The i.f.'s. should again be peaked in turn for maximum signal output and the process repeated until the i.f.'s. can be peaked with the tuning spot-on the station setting on the main dial. The i.f.'s. should then be in fairly reasonable alignment.


A dynamic fault can exist due to a short-circuit across one (or more) of the i.f. transformer windings. Note that an open-circuit, at least in the primary, would be brought to light by the d.c. testing earlier described. Typical trouble is a short across a trimmer (if used) or fixed parallel tuning capacitor (i.e., C1/2/3/4 in Fig. 3—1). A short can also occur across an internal tag panel, and such possibilities can only be examined by taking the screening can from the transformer. Incidentally, an open-circuit capacitor across a winding will be revealed during the alignment process by that particular tuned circuit failing to peak at the correct frequency.

If tuning is by a trimmer capacitor, the tendency towards maximum output will occur with the trimmer fully compressed (assuming that there is also a fixed trimmer), while if tuning is by dust-iron slug, the slug will be fully in the core and still not tuning the winding properly. Incorrect i.f.

★2 alignment aggravates adjacent channel interference effects, and these will be recognised from Symptom 2 on the record issued free with the April issue.

A fault typical of i.f. transformers is intermittency in the winding(s) or parallel capacitor. The primary winding (carrying h.t. current) is the one that often goes down in this way, but on some transformers leakage between primary and secondary is possible. Symptom 5 on the record typifies the noises

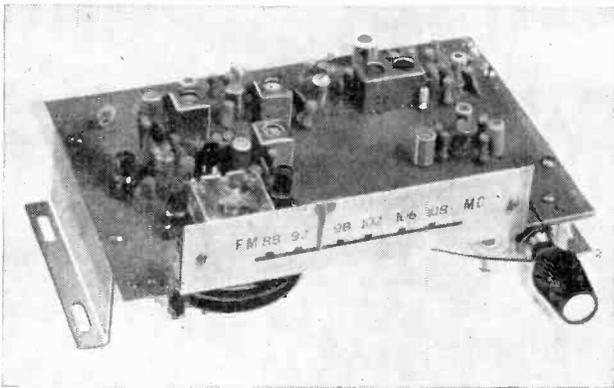★5 that can be expected from this trouble. To see whether the fault is in the first or second i.f. transformer, the control grid of the i.f. valve



FMT.41 Transistorised
FM Tuner


have
you...

WI.2. Transistorised
Wireless Intercom



seen
the

complete range of

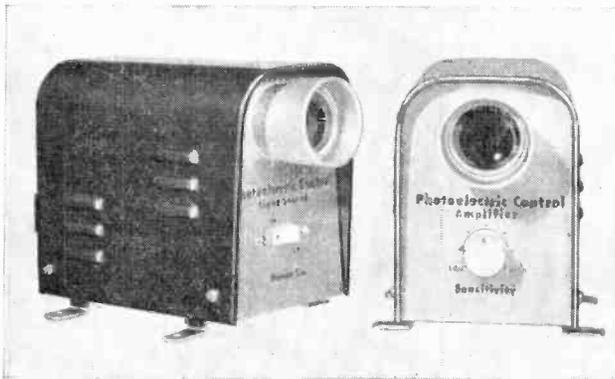

PEA.400. Photo Electric
Relay System



EAGLE
products

The "Eagle" Brand was launched 10 years ago. It was impossible to foresee that in such a short time the range would grow to cover over 500 items, all carrying the "Eagle" name. Whether you are interested in Hi-Fi, Amateur Radio, Do-it-Yourself projects or any field of Electronics, "Eagle" offer you the widest choice of sensibly priced products and by the end of the year we plan to increase our range to cover the formidable total of 700 items.

If you would like to study our entire range in the leisure of your home we will be delighted to send you our catalogue free of charge or why not ask your local dealer (there are over 6,000 "Eagle" stockists) to show you the latest "Eagle" Products today!


To: EAGLE PRODUCTS, Dept. PW.6,
Coptic Street, London, W.C.1.

Please send me catalogue of the entire "Eagle" range.

Name

Address

FANTASTIC NEW 1967 BARGAINS FROM CONCORD

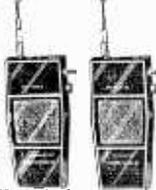

Frustrated Import Shipment
OFFERED BELOW HALF PRICE TO CLEAR
ALL TRANSISTOR 500 only
PERSONAL TRANSCIEVER SETS
£6.19.6

OUR PRICE
You've heard about them—You've read about them. NOW'S YOUR CHANCE TO OWN THEM. Highly sensitive two-way transistor transceiver sets have individual volume control and talk-listen switch. Telescopic aerial pulls in the voice from the other set over tremendous distances—no wires—a genuine transceiver as used by official bodies and forces. 500 sets only at **£6.19.6** plus 5/6 p. & p. (Batteries, leather cases, etc. 10/6 ex.). Money back if not delighted with the performance. These cannot be operated in U.K.

NO SOLDERING AMAZING CIGARETTE RADIO ONLY 25/-



Yes a perfectly ordinary packet of cigarettes! But watch your friends astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 cigarettes yet cleverly conceals highly sensitive, fully transistorised circuit (including battery). Even a young boy can assemble it under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bulging testimonial file Mr. D. B. of Huddersfield, writes: "... I have fitted the parts in it and it is working wonderfully..." ALL PARTS including Semi-Conductors, ABC Plans, etc. **ONLY 25/-** plus 2/6 post, etc. *Paris available separately.*



AUTHENTIC MARINE DIVERS' PATTERN AUTOMATIC DATE CHANGE
Gigantic Purchase at Fathoms below cost.

Made to highest possible marine spec. by Swiss maker.

79/11

Waterproof. 200ft. depth tested. 22 jewels (19 fully working, 4 subsidiary). Anti-magnetic stainless steel back, rotating time bezel. Calibrated tachometer scale, luminous dial & hands, centre sec. hand. 6 months' g'tee 79/11 + 4/7d. P. & P. (+ 7/6d. strap or 17/6 stainless steel bracelet.) **TEST on writ for 7 days free—money back g'tee.**

NEW FULLY TRANSISTORISED PORTABLE RADIOS
with Full Variable waveband. NOW A FRACTION OF THE NORMAL PRICE

ONLY 34/6

WHY PAY MORE? All the latest refinements are packed into this new **MULTI-STATION** ALL Transistor radio—the internal aerial picks up even the remote stations & the powerful built-in speaker gives room filling volume. Individual tuning, first-class reception. Purchase with confidence—packed in original manufacturers' cartons. (*Personal earpiece and battery 4/6*). Send **39/6** plus 4/6 p. & p.



Scoop Purchase by our Overseas Agent. Exact source cannot be disclosed due to drastically reduced price.



THE LATEST ALPHA HIGH POWERED SECRET AGENT CIGAR CASE BINOCULARS

Not repeatable at our price. **NOW ONLY 14/11**

The miniaturisation of modern technology and the increased activity of secret agents in every field have combined to produce these remarkably ingenious cigar case binoculars. At first glance the simulated leather case with plated fittings seems quite normal but press the button and **PRESTO!** the case springs quietly open to reveal a **POWERFUL** pair of lenses—rotates a concealed focusing wheel and you have an amazing pair of binoculars, not a toy—9 magnification areas. Limited number available in this country so rush your order. Send only **14/11**, plus 3/7 p. & p. for free home trial. *Full written guarantee—money refunded in full if not the most intriguing purchase of a lifetime.*

Make 5 different TRANSISTOR RADIOS for 39/6

No Experience Necessary

No soldering. Only 8 connections for first radio to work. Just look, you get **Easy ABC Plans**, Cabinet, Loudspeaker (alone 17/6), Earphone, 4 semi-conductors, Coils, Condensers, Resistor, Tuner, Switch, Screws, etc. **YES—EVERYTHING!** Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Complete course—originally



£8. Now only 39/6 plus 4/6 Post etc.



HIGH POWERED TRIPOD TELESCOPE ONLY 45/- NO MORE TO PAY

Advantageous Purchase Direct from Importer. **750** only at fraction of the true value. Special grade A.1 De Luxe model—passed by Japanese Board of Inspection. All Metal construction in **Black Crackle** finish with plated parts and simulated leather covering. Special polished optical lens gives astounding magnification power of 90x-1 areas. Single draw focusing tube enables you to study the **MOON, PLANETS & STARS.** Independent view finder permits you to focus on subjects miles away or just across the road. Brand new complete with collapsible tripod at unbelievable price of only **45/-** plus 5/- post and **SAFE PACKING.** Satisfaction or your money back.

CONCORD ELECTRONICS LTD. (Dept. P.W.38). 77 New Bond St., London, W.1
MAIL ORDERS ONLY

TRANSISTORS

OC23	10/-	OC82	3/6
OC25	9/6	OC82D	3/6
OC26	9/6	OC84	5/6
OC28	11/-	OC169	4/6
OC35	12/6	OC170	4/6
OC36	12/6	OC171	6/-
OC38	12/6	OC200	7/6
OC44	3/6	AC126	3/6
OC45	3/6	AC127	3/6
OC46	4/-	AC128	3/6
OC70	3/6	AD170	15/-
OC71	3/6	AF114	5/3
OC72	3/6	AF115	5/-
OC75	4/-	AF116	5/-
OC78	4/-	AF117	4/6
OC78D	4/-	AF118	4/6
OC81	3/6	AF119	4/6
OC81D	3/6	OAB1	2/6

C.W.O., P.P. 2/- in & Min. 1/-.

RECORDING TAPES

3in. Standard	.. 150ft.	3/11
3in. Standard	.. 225ft.	4/11
3½in. Triple Play	.. 600ft.	12/6
5in. Standard	.. 600ft.	10/-
5in. Long Play	.. 900ft.	14/6
5in. Double Play	.. 1200ft.	15/6
5½in. Long Play	.. 1200ft.	16/-
5½in. Double Play	.. 1800ft.	22/6
7in. Standard	.. 1200ft.	17/6
7in. Long Play	.. 1800ft.	22/6
7in. Double Play	.. 2400ft.	25/-

Four of the tapes or more are post free otherwise postage 1/6.

SPOOLS

3in. spool	1/-	5½in. spool	2/-
3½in. spool	2/3	4in. spool	2/3
5in. spool	2/6	7in. spool	1/6

Postage and packing 6d. All items listed are cash with order.

INTERCOM/BABY ALARM

Modernise your home or business with this new all transistor Intercom consisting of one master and one sub. Complete with all leads, battery and full instructions. Usually 5 gns.

Our Price 49/6. P.P. 2/-.

TEST METERS

Pocket Test Meter D14

Specifications: DC voltage 0-15 -150-1,000 volts (1,000 R/V). AC voltage 0-15-150-1,000 volts (1,000 R/V) DC current 0-150 milliamperes. Resistance 0-100 KΩ. Size: 57 x 93 x 30mm. Net weight 108 g. Only 39/- Cor. 2/-.

Send 3d. stamp for catalogue containing

Hi-Fi. Transistor Radios, Microphones, Autochangers, etc.

to: **Moordown Radio Ltd., 941 Wimbourne Road, Moordown, Bournemouth. Tel 59866**

YOUR CAREER in RADIO & ELECTRONICS?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the **Grad. Brit. I.E.R. Exam.**; the **RADIO AMATEUR'S LICENCE**; **P.M.G. Certificates**; the **R.T.E.B. Servicing Certificates**; etc. Also courses in **Television**; **Transistors**; **Radar**; **Computers**; **Servo-mechanisms**; **Mathematics** and **Practical Transistor Radio** course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. **Fullest details will be gladly sent without any obligation.**

To: **British National Radio School, Reading, Berks.**

Please send **FREE BROCHURE** to:

NAME.....Block

ADDRESS.....Caps.

.....Please

6.67

BRITISH NATIONAL RADIO SCHOOL

repairing radio sets

can be shorted direct to chassis. If the symptom persists, it is definitely not in the first i.f. transformer or in the front-end sections.

It may be a good idea to short out the secondary of the second i.f. transformer at this juncture to prove the audio section. If the noise effects cease, then the second i.f. transformer is almost certainly responsible. If they persist, the audio stages should be investigated (dealt with in Part 5).

If intermittency in the primary winding is responsible, it is often possible to "see" this in terms of a flickering pointer when the voltmeter is connected as for Test 2.

I.F. INSTABILITY

Oscillation in an i.f. stage can be brought about by incorrect i.f. alignment. Some sets are sensitive when the windings are peaked, and if they are the **★1** amplifier could change into an oscillator and produce the effect of Symptom 1 on the record. This kind of set requires so-called stagger-tuning in which one winding is detuned relative to the other on each transformer, but not sufficiently to reduce the sensitivity or to encourage adjacent channel interference.

Instability can also result from a bad valve (old valves with sprayed-on gold-coloured conductive coating were troublesome in this respect, but there are very few of these about now!) and from an open-circuit screen grid capacitor (C5 in Fig. 3—1).

An open-circuit in the cathode bypass capacitor (C6 in Fig. 3—1) will usually result in reduced sensitivity rather than instability owing to negative feedback effects. A set with an electrolytic in position C7 in the circuit could also go low-gain due to its open-circuit.

Other troubles that occur in the i.f. stage are (a) noise (Symptom 5) due to badly seating valves and/or dirty valve pins and faulty sockets, (b) burning resistors due to a shorting bypass capacitor **★5** (i.e., R1 would overheat due to C5 shorting, or R2 due to C7 shorting), (c) overloading due to **★4** an a.g.c. fault (Symptom 4) to be considered later and (d) intermittent operation due to a badly soldered connection, bad valve and poor connection of valve pins with its holder sockets. Valve bad seating can often be brought to light by wriggling the valve in its holder while the set is running.

A.M./F.M. I.F. STAGE

All that has so far been said applies equally to the i.f. stage employed in a.m./f.m. sets. From Part 1 it will be recalled that sets of this mode employ two i.f. transformers in series, one tuned to 470kc/s for a.m. and the other to 10.7Mc/s for f.m.

An i.f. stage typical in this respect is shown in Fig. 3—2. This shows that the basic d.c. parts of the circuit are almost identical to those in Fig. 3—1. The valve is a more modern version since it has to provide reasonable gain at 10.7Mc/s as well as at 470kc/s, and the voltages to be expected on a valve of this kind are shown on the diagram. Alignment of the a.m. transformers is performed first, and

these then present the correct impedance to the much higher frequency f.m. transformers, allowing their subsequent alignment.

The control grid of the valve is fed from the secondary windings of the first set of i.f. transformers (which are also in series with each other), and in some sets there is a switch to short out the primary of the first f.m. transformer when the set is set to a.m. working.

It may be remembered from Part 1 that on f.m. the a.m. mixer section of this kind of set works as an additional i.f. amplifier with the local oscillator section switched off. This gives another f.m. transformer, which is usually located in the v.h.f. tuner section (f.m. front-end).

Dynamic testing through this dual-type of i.f. amplifier follows the practices already described, and the fact that the circuit is normally responsive to two widely differing i.f. signals means that failure of one channel only cannot be caused by a valve fault or incorrect d.c. conditions. The reason is often related to misalignment of the affected channel or trouble in the appropriate i.f. transformer section.

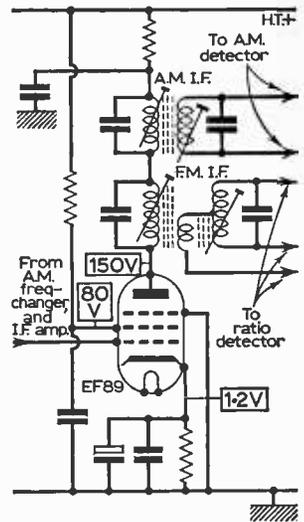


Fig. 3-2: This kind of i.f. stage is found in a.m./f.m. receivers.

DETECTOR AND A.G.C.

Now let us look at the detectors, starting with a.m. circuits. A detector a.g.c. circuit in common use is shown in Fig. 3—3. This employs a double diode-triode valve, but only the two diodes interest us at this time; the triode is used in the audio stages and will be considered in Part 5.

The detector is nothing more complex than a diode connected in series with the secondary winding of the second i.f. transformer, along with its

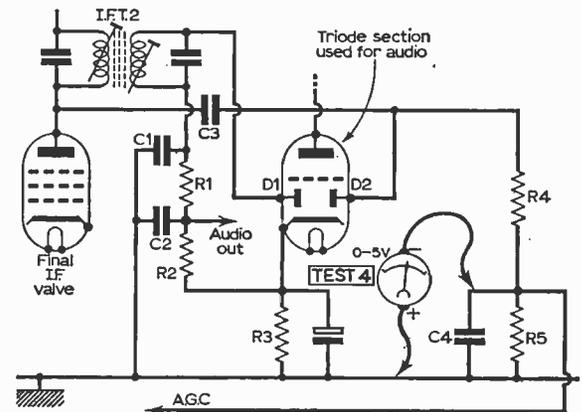


Fig. 3—3: An a.m. detector and a.g.c. circuit, showing a test for a.g.c.

load. It looks much more involved, however, when tied up in a complete circuit Fig. 3—3).

The detector diode is D1 and its load is R1 and R2 in series, with the bottom end returned to valve cathode instead of chassis. This is to avoid biasing the diode by the voltage dropped across the cathode resistor R3 when the triode is passing current. The audio signal thus appears across R1 and R2, and it is tapped-off at their junction. C1 and C2 are i.f. filter capacitors, taking away the residual i.f. signal, leaving only the audio component.

The i.f. signal from the anode of the final i.f. amplifier valve is passed to the second (a.g.c.) diode (D2) through the coupling capacitor C3. Rectified i.f. current thus flows through R4 and R5 and a d.c. voltage is developed across these resistors of a magnitude governed by the strength of the i.f. signal applied to the diode. This represents the a.g.c. bias, and since its full strength is not required a suitable level is tapped off the potential-divider R4/R5. This charges C4 and a time-constant is formed with R5. Residual i.f. signal is also bypassed by C4.

On the a.g.c. line therefore, is a negative potential (with respect to chassis) which is used as extra grid bias for the i.f. amplifier and frequency-changer (mixer section) valves. As the mutual-conductance (and hence stage gain) is determined by the amount of grid bias—the greater the bias the less the gain—the overall amplification of the signal circuits is automatically regulated by the strength of the signal. Rapid fading is also combated by the time-constant on the a.g.c. line.

FAULTY A.G.C.

One fault which can develop in the detector/a.g.c. stages, and cause bad overloading, is open-circuit of **★4** C3. This effect is clearly illustrated in Symptom 4 of the record and, apart from distortion due to “envelope distortion”, intermodulation troubles can occur on strong signals giving a background whistle accompaniment.

A conclusive a.g.c. test is shown in Fig. 3—3 at **Test 4**. Here a voltmeter is used to measure the actual a.g.c. voltage produced by the signal. There is no point in attempting this test with a voltmeter of less than 10,000 Ω /V sensitivity, however, for the meter would swamp the circuit and give virtually no reading even on a very strong signal. A reading up towards 5 volts should be obtained at the point indicated on the circuit on a strong signal.

In some sets the a.g.c. voltage is transferred to the control grids through very high (order of megohms) resistors, so even a highly sensitive meter would give very little reading at these points. A valve voltmeter or equivalent transistor instrument would, however, be suitable.

A noteworthy point of the a.g.c. circuit is that it is delayed. This comes about by the biasing given to the a.g.c. diode due to triode current flowing through the cathode resistor. Thus, the cathode is at some voltage positive with respect to D2 (since in this case D2 is returned to chassis through R4/5), and this means that D2 will not conduct until the signal reaches the delay level given by the bias. This means that the set's gain is always at maximum on weak signals.

The detector itself rarely develops faults except perhaps when an i.f. filter capacitor goes open-

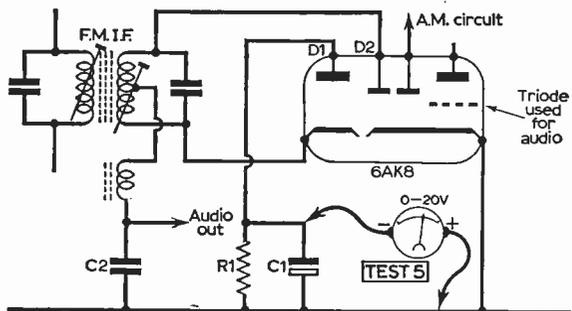


Fig. 3—4: The ratio-detector formed by two isolated diodes in a triple-diode-triode valve. A ratio detector test is shown.

circuit. This can aggravate instability and introduce whistles. Since the diodes are working at very low power they rarely fail, even though the triode may go low emission.

RATIO-DETECTOR

In a.m./f.m. sets, the detector valve is usually a triode (for audio) with *three* diodes, one with its own cathode and two using the common triode cathode. One of the diodes common to the triode cathode is used as an a.m. detector, which is often arranged to provide a.g.c. as well, while the other diode, in conjunction with that with its own cathode, is used in a ratio-detector for f.m., as shown in Fig. 3—4.

Here D1 has its own cathode and D2 a shared cathode. The ratio-detector circuit is formed by D2 anode going to one side of the ratio-detector transformer secondary and D1 cathode to the other side. D1 anode and D2 cathode are then connected across the d.c. load of the detector (as is conventional practice) comprising R1/C1. The audio is developed across C2 connecting to the third winding on the transformer. This looks a bit messy in this form but if it is worked out into a different pattern it will be found to conform to the ordinary ratio-detector circuit.

A good test for this kind of detector is to measure the voltage across the d.c. load, as shown by **Test 5** in the circuit. With a correctly working circuit, up to 20 volts will be measured across the load when the f.m. set is tuned to a strong transmission.

Difficult tuning and poor interference suppression is often caused by C1 of the load going down or becoming open-circuit. This would not be indicated by the test across the load and a new capacitor (about 4 μ F electrolytic) should be hooked on as a trial. Shorting C1 would, of course, prevent a voltage reading and certainly kill normal working of the detector.

If R1 goes high in value the effect is a sort of “overhang” on the f.m. tuning, it being difficult to establish quickly the correct tuning point.

This triple-diode-triode valve can cause a hum or buzz on f.m. only under certain fault conditions **★3** (not unlike the first interference effect in Symptom 3 of the record). The valve may not immediately be suspected since a.m. is invariably unaffected, but a substitution test soon shows that the valve is to blame.

To be continued

DENCO (CLACTON) LIMITED

**357-9 OLD ROAD
CLACTON-ON-SEA
ESSEX**

Telephone: Clacton 22807

In a piece of Electronic Equipment at Harvard University of America, London University of England, countless Equipments in our Fighting Services, Ships, Aircraft and Automation you will trace components being the handwork of our Craftsmen. In the records of some of our Country's Greatest Manufacturers of Electronic Equipments, which are reliable and World Renowned we are recognised for our Quality—Reliability and reasonable prices.

In many of the finest Home Constructor Technical Articles published by this Magazine and which for many years has encouraged the terrific growth of our Great Electronic Industry and Export Business, you will find mention of our products.

In these facts we take great pride. In the ownership of our products you may enjoy equal pride plus the guarantee of quality and long life.

Send 6d. in stamps for price list of components used in Articles or 2s. 6d. for comprehensive catalogue and please, the courtesy of an S.A.E. with all other queries.

MOVING COIL MULTIMETER TK 25 47/6
 0-100 v. A.C./D.C., ohms 0 to 1 k. etc.
 MOVING COIL MULTIMETER EP10K. 79/6
 0-1,000 v. A.C./D.C., ohms 0 to 3 meg. etc.
 MOVING COIL MULTIMETER EP20K. 99/6
 0-2,500 v. D.C. 20,000 ohms per volt. 0-1,000 v. A.C.
 Ohms 0 to 6 meg. 50 Microamps full scale.

NEW MULLARD TRANSISTORS

OC71 6/-; OC78 7/6; OC81D 6/-; OC81 6/-; AF115 8/-;
 AF114 8/6; OC44 8/-; OC45 8/-; OC171 9/-; OC170 8/6;
 AF117 7/-; OC28 12/6; AD140 15/-; OC35 15/-; Holders 1/8.

ARDEUTE TRANSISTOR TRANSFORMERS

D8055, 7.3 CT. 1 Push Pull to 8 ohms for OC78, OC81. 11/-
 D8034, 1.75: 1 CT. Push Pull Driver for OC78, OC81. 11/-
 D8068, 11.5: 1 Output to 8 ohms for OC78, OC81. 11/-

TRANSISTOR MAINS ELIMINATORS
 Famous "Power-Mite" 9 volt. Same size as PF9
 battery. Fully smoothed, 150mA. Full-wave circuit. 45/-

WEYRAD P50 — Transistor Coils

BA3W 6 in. Ferrite Aerial with car aerial coil... 12/6
 Spare Cores 6d.
 Driver Trans. LFDT4... 9/6
 Printed Circuit, PCA1... 9/6
 J.B. Tuning Gang... 10/6
 Weyrad Booklet... 2/-
 Osc. P50A1C... 5/4
 470 k/ohm L.F. P50/20C... 5/7
 Std L.F. P50/30C... 6/-

VOLUME CONTROLS

Long spindles. Midset Size 5 K. ohms to 2 Meg. LOG or L.M. 1/8 3/-. D.P. 5/-.
 STEREO L/8 10/6. D.P. 14/6.
 Ideal 625 lines yd.

80 Ohm Coax 6d yd.

Semi air-spaced Cable 40 yd. 17/6. 60 yd. 25/-
 FRINGE LOW LOSS 1/6
 Ideal 625 lines yd.

COAXIAL PLUG 1/-. PANEL SOCKETS 1/-. LINE SOCKETS 2/-.
 OUTLET BOXES. SURFACE OR FLUSH 4/6.
 BALANCED TWIN FEEDERS 1/- yd. 80 or 300 ohms.
 TELESCOPIC CHROME AERIAL. 6in. extends to 23in. 6/6.

TV REMOTE CONTROL

For PHILIPS 19TG111A, 191A, 195A, 142A, 23TG111A, 113A, 181A, 181A, STELLA FT1033A, 39A, 42A, 33A, ODSOR CT1910A, 21A, CT2310A, 21A, 31A, PHILIPS.
 Price 3 gns.
 Our Price 12/6 Post 2/6
 Brand New, includes 11ft. 7-way cable, MULLARD OAS1 2 pots, 3 switches, 5 resistors.



1967 GRAM CHASSIS Post 5/-



Three Wavebands: Five Valves: ECH81, EF89, Long. Med., Short. Gram. EB031, EL84, EZ80.
 12-month guarantee. A.C. 200-250 v. Ferrite Aerial 5 watts 8 ohms. Chassis 13 1/2 in. x 7 in. x 5 in. dial size 13 in. x 4 in. Two Pilot Lamps. Four Knobs. **£10.10**
 Aligned calibrated. Chassis isolated from mains
 De-LUXE STEREO GRAM CHASSIS, V.H.F., M.W., S.W.1. 19-50m. S.W.2. 60-180 m. Magic eye, push buttons, 6 valve + rect. AC only 200/250v. **£19.19**
 Size 15 x 7 1/2 x 6 in. high.

HIGH GAIN TV. PRE-AMPLIFIER BAND 1 B.E.C.
 Tunable channels 1 to 5. Gain 18dB. ECC84 valve. Kit price 32/6 or 55/- with power pack. Details 6d.
 BAND III I.T.A.—same price. Tunable channels 7 to 13. Band I or III. Coils and circuit only, 9/6. Chassis 4 1/8. B.E.C. Super Booster. UHF Transistor Model ready made 75/-

ALL PURPOSE TRANSISTOR PRE-AMPLIFIER
 Gain 14:1. 250v. or 9v. input. Ready built with Mn Metal input transformer for Mikes, Pick-Ups, Tuners
 Instructions and circuit supplied. Post 2/6. **15/-**

BLANK ALUMINUM CHASSIS 18 s.w.g. 2 1/2 in. sides, x 4 in., 5/6; 9 x 7 in., 6/6; 11 x 8 in., 8/6; 11 x 7 in., 7/6; 8 x 9 in., 9/6; 14 x 11 in., 12/6; 18 x 14 in., 15/-
ALUMINUM PANELS 18 s.w.g. 12 x 12 in., 5/6; 14 x 9 in., 4/6; 12 x 8 in., 3/6; 10 x 7 in., 2/6; 8 x 6 in., 2/-; 6 x 4 in., 1/6.
VALVE HOLDERS Int. Oct. 6d. Mazda Oct. 6d.; B7G, B8A, B8G, B9A Moulded 9d. Ceramic 10/- B7G, B9A cans 1/-
 Valve base plugs B7G, B8A, Int. Oct. 2/8.

THE INSTANT BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER



200/250 v. A.C. Leaflet S.A.E. Post 35/- 2/6

FM TUNER 88-108 Mc/s Six Transistor. Superhet. Ready built. Printed Circuit. Calibrated slide dial tuning. Size 6 x 4 x 2 1/2 in. £8.10

3-WATT QUALITY AMPLIFIER 4 Transistor Push-pull. Ready built, with volume control. 75/-

PRIMO A.18 TRANSCRIPTION TONE ARM. 5 gns. With tracking template and two plug-in shells. Moving Coil Stereo Diamond Cartridge 20-15,000 cps. 5 gns.

★**RADIO BOOKS★ (Postage 9d)**
 High Fidelity Speaker Enclosures and Plans... 5/-
 Transistor Superhet Commercial Receiver... 7/6
 Mullard Audio Amplifier Manual... 5/6
 Radio Valve Guide, Books 1, 2, 3 or 5... each 5/-
 Practical Radio Inside Out... 4/6
 Transistor Audio Amplifier Manual... 3/6
 Shortwave Transistor Receivers... 5/-
 Radio Communication 50/-
 International Radio Stations List... 2/6
 Modern Transistor Circuits, for Beginners... 7/6
 Sub-Minature Transistor Receivers... 5/-
 Wire-less World Radio Valve Data... 9/6
 At a glance Valve equivalents... 6/-

RESISTORS Preferred values, 10 ohms to 10 meg
 1/4 w. 1/4 w. 20% 4d.; 1/2 w. 8d.; 2 w. 1/-; 1/2 w. 10% 6d.
HIGH STABILITY. 1/4 w. 1% 2/-. Preferred values. 10 ohms to 10 meg. Ditto 5%, 10 ohms to 22 meg. 9d.
 5 watt } WIRE-WOUND RESISTORS { 1/6
 10 watt } 0.5 to 2.2 ohms 3/6
 15 watt } 10 ohms to 6,800 ohms { 2/-
 10K, 15K, 20K, 25K, 10W. MAINS DROPPERS. Midset. With sliders. 0.3 a., 1K. 0.2 a., 1.2 K., 0.15 a., 1.5 K. 6/- each.
LINE CORD 100 ohms ft. twin plus resistance 1/- ft.

WIRE-WOUND 3-WATT POTS. Miniature T.V. Valves 10 ohms to 30K, 3/6. Carbon 30 K, to 2 meg., 3/-

CRYSTAL MIKE INSERTS
 1 1/2 x 1 in. 6/6; ACO5 1 1/2 x 1 in. 8/6; BMS 1 x 1 in. 7/6
TANNOY CARBON MIKE with Switch... 5/6
HEADPHONES 2000 ohms 12/6. 4000 ohms 16/-.

BRAND NEW QUALITY EXTENSION LOUDSPEAKER
 In tough cream plastic cabinet with 20ft. lead and adaptors. For any transistor radio intercom, mains radio, tape recorder, etc 3 to 15 ohm matching. **30/-** POST 2/6




RETURN OF POST DESPATCH Minimum P.P. Charge 1/6 unless otherwise stated. C.O.D. 5/- extra. Full List 1/-.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON

Written guarantee with every purchase. (Export—send remittance and extra postage, no C.O.D.) (Buses 133, 68 pass door). S.R. Stn. Selhurst. Tel. THO 1665

YOURS FREE FOR 7 DAYS

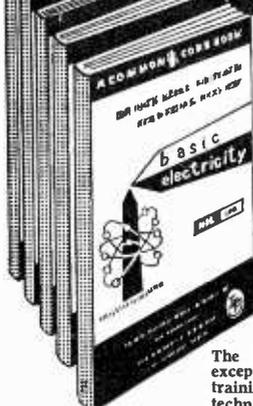

The New 'Picture - Book' way of learning BASIC ELECTRICITY (5 Vols) ELECTRONICS (6 Vols) ELECTRONIC CIRCUITS (2 Vols) INDUSTRIAL ELECTRICITY (2 Vols) SYNCHROS & SERVOMECHANISMS (2 Vols)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

... they make study a real pleasure... A.C., CAMBRIDGE.
 ... I must say how pleased I am with the simplicity of their explanations... C.G., JERSEY.
 ... I have passed my theory exam. on electronics with the help of your manuals... D.E.F., ELY.

POST NOW FOR THIS OFFER!

TO SELRAY BOOK CO. 60 HAYES HILL, HAYES, BROMLEY, KENT

Please send me Without Obligation to Purchase, one of the above sets on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 7 days or send the following amounts. Basic Electricity 70/-. Cash Price or Down Payment of 15/- followed by 4 fortnightly payments of 15/- each. Basic Electronics 82/-. Cash Price or Down Payment of 15/- followed by 5 fortnightly payments of 15/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order.

Tick set required (only ONE set allowed on free trial).
 BASIC ELECTRICITY 70/- BASIC ELECTRONICS 82/-
 BASIC ELECTRONIC CIRCUITS 40/-
 BASIC INDUSTRIAL ELECTRICITY 40/-
 BASIC SYNCHROS & SERVOMECHANISMS 38/-
ALL PRICES INCLUDE POSTAGE

Signature (If under 21, signature of parent or guardian)
 NAME
 FULL POSTAL ADDRESS

dual function SIGNAL GENERATOR



H. WEBSTER

NEXT to the multi-range testmeter probably one of the most useful items of equipment in the amateur workshop is a generator of signals covering a wide frequency spectrum. While such an instrument can be quite complex and costly, for most amateur requirements a simple, stable, modulated oscillator is sufficient for most purposes. With the aid of such an oscillator, alignment of receivers is easily carried out and the degree of uncertainty associated with trial and error methods eliminated. Apart from this prime function the signal generator is an invaluable aid to fault tracing in receivers.

The basic requirements of an oscillator suitable for alignment purposes are as follows. It should be stable and not require recalibration at frequent intervals. Changes in supply voltage should not have an adverse effect on the oscillator frequency. Radiation of energy other than by the output socket should be reduced to a minimum. Finally, the output of the oscillator should be controllable. Although none of these desirable features is easy to obtain and


is reflected in the relatively high cost of commercial instruments, nevertheless, by careful attention to screening and suitable choice of oscillator, it is possible to construct a generator which approaches these ideals.

The signal generator described in this article has been designed with these features in mind. As well as performing all the usual functions of the normal oscillator, a further valuable feature enables the experimenter to extend the scope of the instrument to inductance and capacitance testing. This aspect of the design will be dealt with briefly in the latter part of the article.

CIRCUIT DESCRIPTION


An examination of the circuit given in Fig. 1 will show that both the radio and audio frequency oscillators are of the "two terminal" type. In each case a double triode is employed, one section being used as a cathode follower and the other as a grounded grid amplifier. Energy in the correct phase is fed

Fig. 1: Circuit diagram of the signal generator including the power supply unit. The coupling capacitor C2 may require slight adjustment as described in the text.

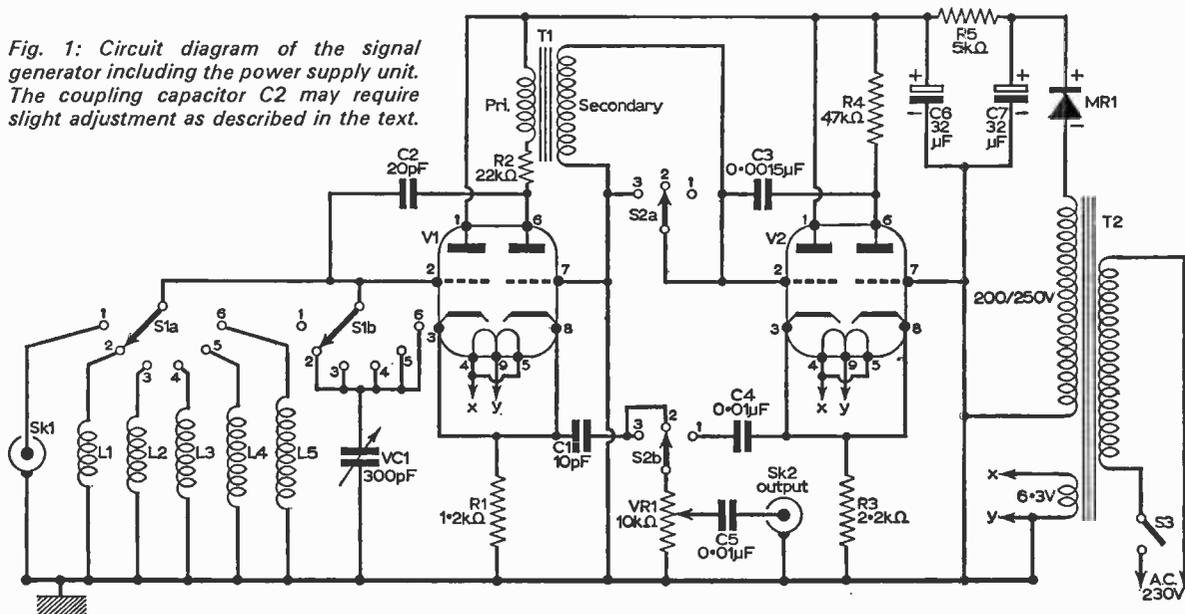






Dual function signal generator.
Figure 2

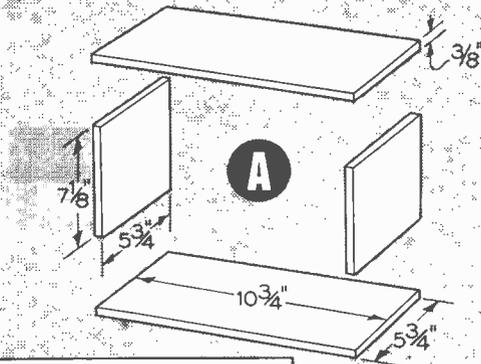- A:** Dimensions for a suitable cabinet.
- B:** Chassis drilling details.
- C:** Cardboard template for mounting coils.
- D:** Front panel drilling details.




Holes A $\frac{3}{4}$ " diameter
 Holes B $\frac{1}{4}$ " diameter
 Holes C 4 BA clearance
 Holes D 6 BA clearance

B

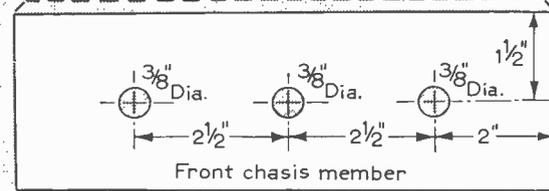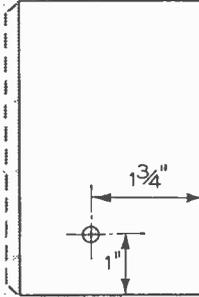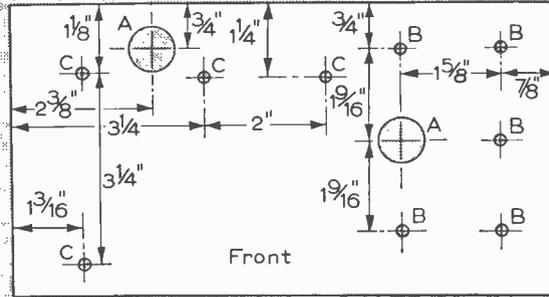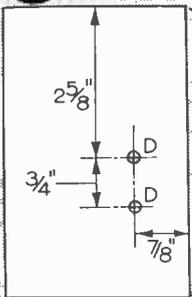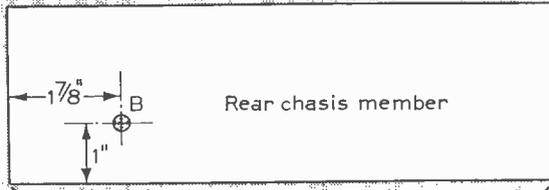


Holes A $\frac{1}{8}$ " diameter
 Holes B $\frac{1}{4}$ " diameter
 Template $\frac{3}{8}$ " diameter

C

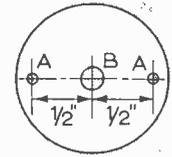

D

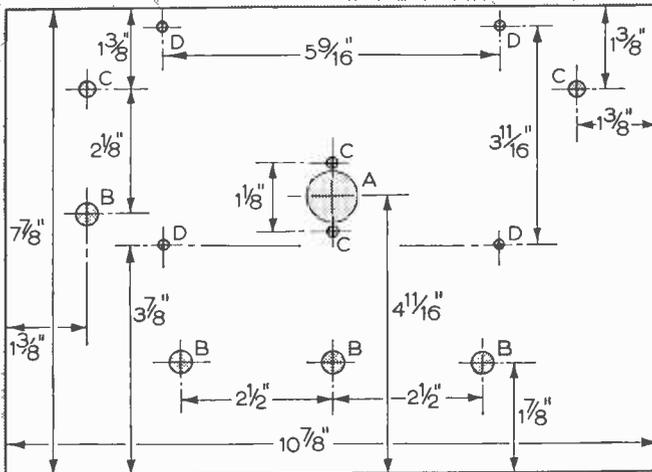Hole A $\frac{7}{8}$ " diameter
 Holes B $\frac{3}{8}$ " diameter
 Holes C 4 BA clearance
 Holes D 6 BA clearance



back from the second section of each triode into the grid circuit in such a way that continuous oscillation is maintained. The coupling capacitor, C2, between the anode of the section triode section of V1 and the grid of V1 is rather critical. Since valve and component tolerances vary somewhat, it may be found that some experiment is necessary to achieve optimum results. Generally a value between 10 and 50pF will be adequate. An indication that the value is too high will be shown by violent squegging.

Anode modulation of V1 is achieved by connecting the h.t. supply to V1 in series with the primary of the audio transformer T1. The audio component developed in the secondary of T1 is inductively transferred to the primary winding of the transformer. An audio signal for amplifier testing is taken from the cathode of V2. Selection of the desired signal, whether r.f., modulated r.f. or a.f. is by means of switch S2.

The frequency span of the generator is from 200kc/s to 30Mc/s. This range is covered using five inductors, L1 to L5, taken from the Denco range of iron cored coils. The screening cans supplied with these coils have been retained since they help materially in reducing extraneous radiation. Power requirements for the unit are quite modest and any small transformer with an output of 200-250 volts

at 20mA and 6.3 volts at 1 ampere is adequate. The specified audio transformer in the modulating section has a primary rated at 8mA and if any other type of transformer is substituted it must have a similar rating.

Although in the interests of compactness, miniature type valves have been specified, there is no reason why older types such as the octal based 6SN7 or 6SL7 should not be used. These two valves function perfectly satisfactorily in this circuit without any alteration in component values. Naturally the use of the larger octal valve holders will necessitate some chassis dimensions changes.

CONSTRUCTIONAL DETAILS

The generator is built on a 9in. x 5in. universal chassis. Full drilling and mounting details are given in Fig. 2. The front panel drilling dimensions given in Fig. 2D are applicable to the specified Eddystone dial. A flexible coupler is used to connect the epicyclic drive mechanism to the variable capacitor. When fitting the drive to the capacitor spindle care must be exercised in the alignment of the spindle and drive mechanism since slight misalignment will mar the smoothness of the drive system. Although many generators, both amateur and commercial, use a direct drive system, the use of a slow motion drive

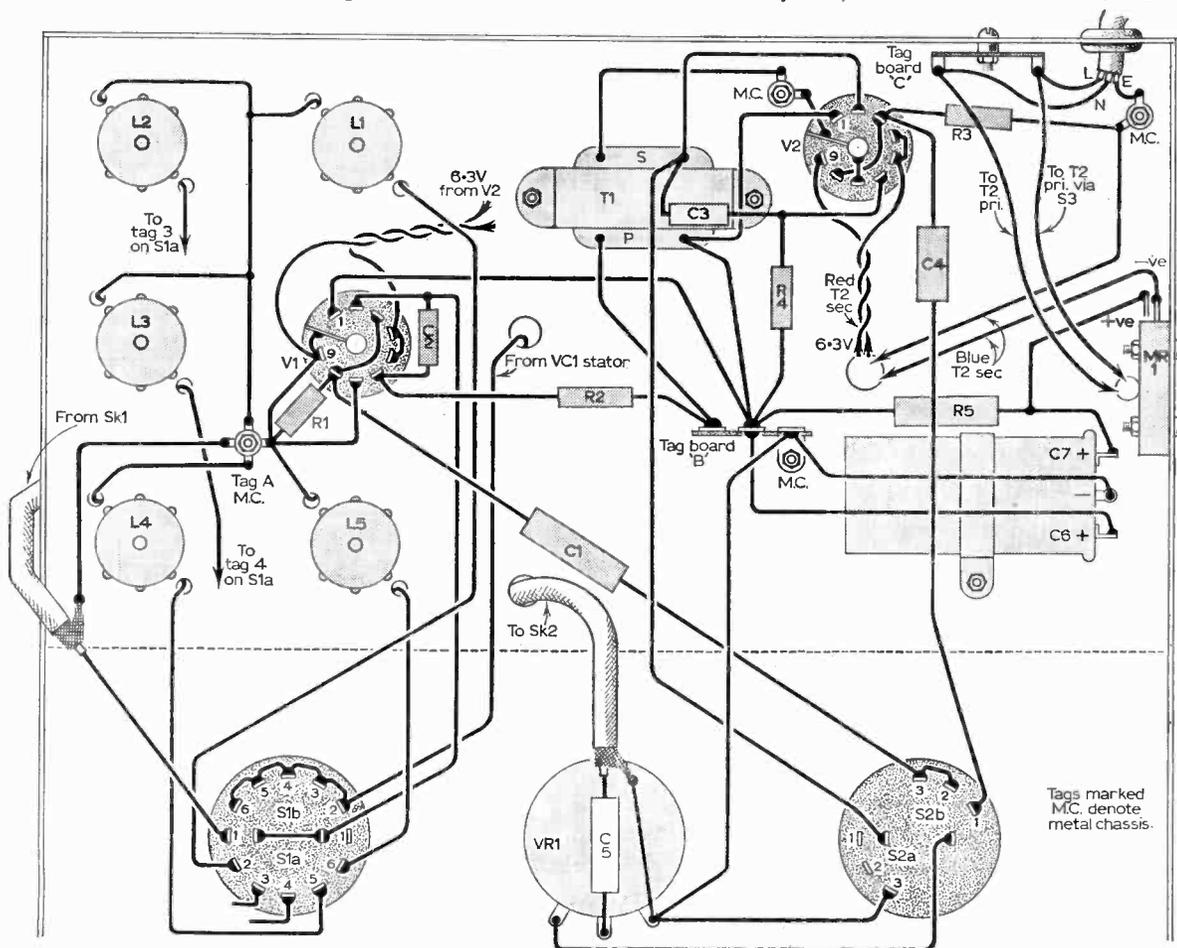


Fig. 3: Under chassis layout and wiring diagram. Note, tags marked MC are bolted directly to chassis.

enables more precise settings to be obtained.

The inductors, L1 to L5, together with the screening can lids are mounted ensuring that the holes in the chassis and can bases coincide. The cardboard template shown in Fig. 2C may be used to facilitate drilling of the chassis and can bases. Since the coil formers and associated plastic securing nuts are of polystyrene it is important that overtightening of the securing nuts is avoided.

When mounting the two valve holders, make sure that they are correctly orientated as shown in Figs. 3 and 4. The completely wired chassis is also shown in the same figures. On all coil ranges the primary windings are shorted out and connected via the earthy end of the grid coil to earth. It may be found on ranges 4 and 5 that the coils have wire ended terminations. If this is the case the grid wire must be insulated with a short length of sleeving before passing it through the chassis.

Wiring of the unit is straightforward although care must be exercised when soldering connections to the coil pins. Excessive and prolonged heating of the pins will lead to distortion of the polystyrene

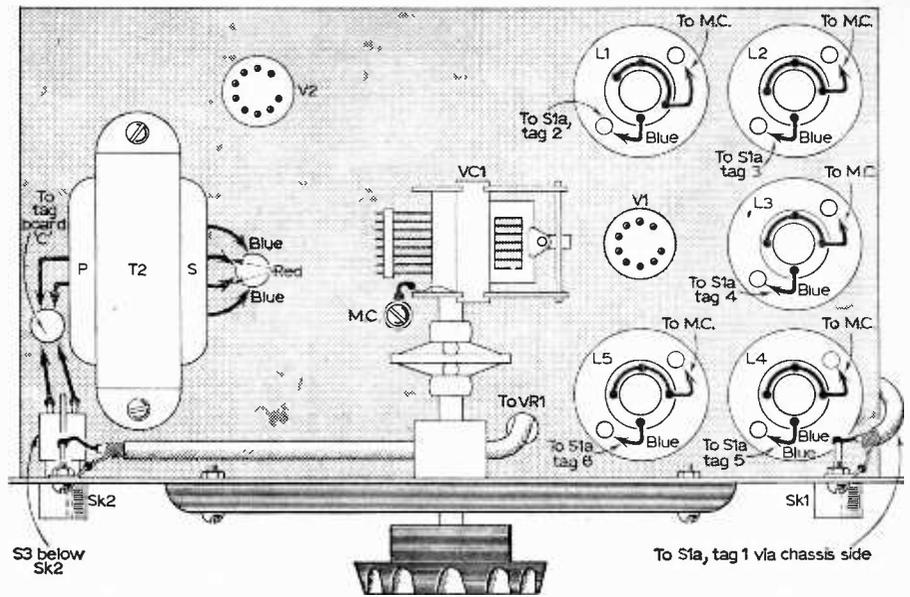


Fig. 4: Layout of components above chassis.

rear of the box is covered with a nominal 11in. x 8in. aluminium top plate taken from the universal chassis range. When covering the interior of the box with foil make sure sufficient overlap is allowed at the edges so that intimate contact between the front panel and back plate is obtained. This method of construction was adopted in the interests of cheapness, and a metal box would be preferable.

Calibration based on comparison with signals of known frequency has been given many times in PRACTICAL WIRELESS and although no attempt

TABLE 1

Range 1		Range 2		Range 3		Range 4		Range 5	
f kc/s	Dial	f Mc/s	Dial						
200	98	0.6	98	1.8	98	5.5	98	9	93
250	72	0.7	80	2.0	85	6.0	85	10	79
300	54	0.8	65	2.5	62	7.0	69	12	62
350	41	0.9	54	3.0	45	8.0	57	14	49
400	30	1.0	45	3.5	31	9.0	47	16	38
450	21	1.1	37	4.0	22	10.0	39	18	30
460	19	1.2	31	4.5	14	11.0	32	20	23
470	18	1.3	25	5.0	8	12.0	26	22	18
500	14	1.4	20	5.5	4	13.0	21	24	13
550	8	1.5	15	—	—	14.0	17	26	9
600	3	1.6	11	—	—	15.0	13	28	5
—	—	1.7	7	—	—	16.0	10	30	2
—	—	1.8	4	—	—	17.0	7	—	—

The table shows approximate dial readings against frequency. The coils should be adjusted as advised in the text in conjunction with Table 2.

formers. On completion of the wiring check the resistance between the h.t. line and chassis. A reading of approximately 500kΩ should be obtained. A much lower reading should be investigated and any obvious faults remedied.

The writer housed the instrument in a wooden box lined with aluminium foil. Constructional details are given in Fig. 2A and are self explanatory. The

will be made to give exhaustive details a brief description is given for the benefit of the newcomer.

The method requires a receiver, not necessarily accurately calibrated, covering a wide frequency range. After setting the receiver to a transmission of known frequency, the generator is adjusted to zero beat with the known frequency. By choosing an adequate number of frequencies for each band, a

graph may be drawn of frequency versus dial readings. Care must be exercised during this procedure since it is quite easy to confuse harmonics with the fundamental frequency. If a superhet receiver is used for calibration purposes, additional difficulties may arise, particularly on frequencies above approximately 10Mc/s. Simple superhets with an intermediate frequency of 450kc/s and without adequate selectivity prior to the mixer, will almost certainly suffer from second channel interference. As an example, consider a receiver of this type tuned to a known frequency of 15Mc/s. If, as is generally the case, the receiver oscillator is tuned to the higher frequency side of 15Mc/s, then in order to give an intermediate frequency of 450kc/s the receiver oscillator will be set at 15.45Mc/s. A little thought will show that a transmission on 15.90Mc/s

TABLE 2

Range	Frequency Range Mc/s	Core Turns
1	0.2— 0.6	5½
2	0.6— 1.8	6
3	1.8— 5.5	12½
4	5.5—17.0	12
5	9.0—30.0	20

For approximate calibration the coil cores are unscrewed to their fullest extent and then screwed in. The number of revolutions is shown in the table.

will equally give rise to an i.f. of 450kc/s. In terms of the generator calibration this means that when the generator is tuned from the low frequency end a first response will be obtained at 15Mc/s. Further tuning of the generator will give a further response when the generator frequency is 15.9Mc/s. In general terms, for each receiver setting on the high frequency ranges, two generator responses will be evident, one when the generator is set to the actual frequency, and a second in which the generator is set to this frequency plus twice the i.f. of the receiver. Although all this may appear rather formidable, in practice the actual calibration of the higher frequency ranges is quite simple and provided the foregoing is borne in mind, no real difficulty should arise. In any case, a graphical check will reveal any errors.

APPROXIMATE CALIBRATION

For those constructors who feel hesitant about this procedure and have no receiver covering the whole gamut of frequencies the following approximate calibration will enable them to make a start. The iron cores of each coil are gently unscrewed to their fullest extent. Do not apply undue force. The cores are then screwed back into the formers the number of complete turns shown in Table 2. The calibration chart shown in Table 1 is applicable to this procedure. If this method is adopted it is imperative that the specified coils are used and the wiring lay-out of Figs. 3 and 4 followed as closely as possible. It must be stressed that the foregoing method is of an approximate nature and is only intended as a preliminary aid to calibration and as a help to the constructor who has no suitable

★ components list

Resistors:

R1	1.2kΩ	R5	5kΩ 5 watt
R2	22kΩ	R6	400Ω
R3	2.2kΩ	R7	400Ω
R4	47kΩ	VR1	10kΩ carbon pot

All fixed resistors 1 watt except where otherwise specified

Capacitors:

C1	10pF	C4	0.01μF	C7	32μF
C2	20pF	C5	0.01μF	C8	200pF
C3	0.0015μF	C6	32μF	C9	400pF

Variable Capacitor:

VC1 300pF Jackson E1

Valves:

V1 ECC82 V2 ECC82

Inductors:

Chassis mounting types
 L1 Denco Maxi Q Yellow Range 1
 L2 Denco Maxi Q Yellow Range 2
 L3 Denco Maxi Q Yellow Range 3
 L4 Denco Maxi Q Yellow Range 4
 L5 Denco Maxi Q Yellow Range 5

RFC: See text

T1 Intervalve type 3:1 ratio
 Radiospares 8mA rating

Mains Transformer

T2 Osmabet 230v 45mA 6.3v 1A

Miscellaneous:

MR Metal rectifier contact cooled 250V 50mA
 B9A Skirted valve holders (2), B9A screens (2),
 Coax sockets (4), 2P 6W switch S1a, b; 2P 3W switch
 S2a, b; SPST switch S3, Universal chassis 9 x 5 x 3,
 Home Radio Aluminium panel 10½ x 7½ (2), Dial—
 Eddystone 598 (Stratton), Flexible shaft coupler;
 knobs, sleeving, coaxial cable, etc.

reference standard. More accurate calibration may be carried out at a later stage. When the finalised calibration has been completed the five scales of the dial may be marked in with indian ink.

DUMMY AERIAL

A suitable dummy aerial for use in conjunction with the signal generator during receiver alignment is given in Figs. 5 and 6. This dummy aerial is satisfactory for frequencies between 150kc/s and 2Mc/s. For the higher frequencies up to 30Mc/s the simple form shown in Fig. 7 is recommended.


In each case the dummy aerial may be mounted inside a discarded tobacco tin as shown in Fig. 5. The 20μH choke used in the medium frequency version consists of 70 turns of 34 gauge enamelled wire close wound on a ¼in. diameter former. The remaining details given in Fig. 5 are self explanatory.

A feature of the generator not generally available

—continued on page 142

SIMPLE TRANSISTOR

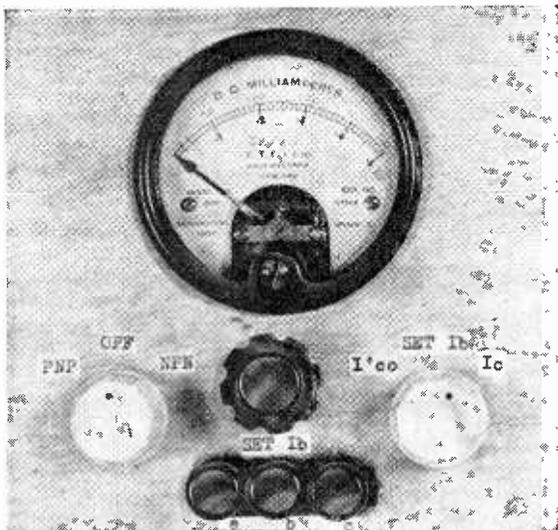Transistors are now readily available from various manufacturers' surplus units, and some of these are here enables some of the more useful transistor provide constructors with a very useful piece of



THIS design offers simplicity coupled with versatility. The tester will check p-n-p or n-p-n transistors for leakage (I'_{co}), a.c. and d.c. gain. The circuit has been arranged to minimise the switching and consequently enables the cheaper and more easily available types of switch to be used. By careful perusal of the advertisements in this magazine it could, at the time of writing, be built for about thirty shillings.

Circuit details

Having now discussed what it does and how much it will cost, let us turn to the question of how it works. Basically, a measured d.c. current is fed into the base of the transistor under test, and then the collector current is measured. The resistance of VR1 controls the base current, while R2 performs the function of preventing this current from

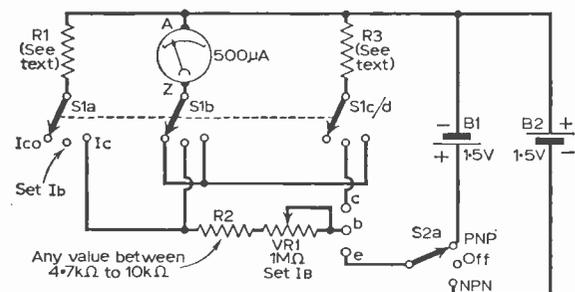


Fig. 1 (above): Basic circuit of the tester.

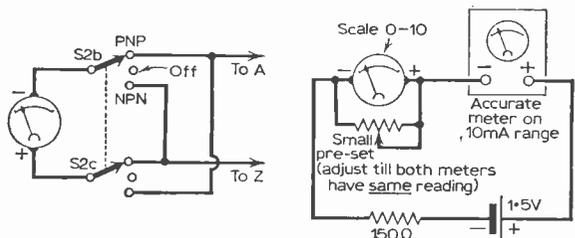


Fig. 2 (left): Modification for testing n-p-n transistors.

Fig. 3 (right): Calibration of the unit.

becoming excessive when VR1 is at its minimum value.

With the function switch S1 in the "Set I_b " position, the meter is connected in series with R2 and VR1, and thus measures the base current set by VR1. In the "Ic" position S1 switches R3 across the meter terminals to give it a full scale deflection (f.s.d.) of 10mA, thus enabling it to measure the collector current. In order to perform a leakage test, i.e., measure I'_{co} , S1 connects the supply voltage, with the base open-circuit.

To enable the tester to be used for both n-p-n and p-n-p transistors, the circuit of Fig. 1 is modified slightly by the addition of Fig. 2. The meter is

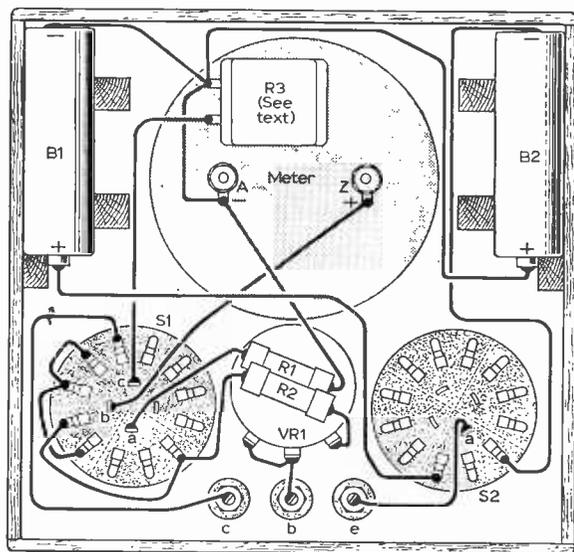


Fig. 4: Layout of the prototype tester. Compare this with the photograph in the heading on the right.

connected to points A and Z on Fig. 1 via the p-n/p-n-p-n switch S2. This enables both the meter and the supply to be reversed for testing n-p-n transistors (see Fig. 2).

Calculations

Resistor R1 should be equal to the meter's d.c. resistance, ± 20 per cent will be satisfactory, while R3 the 10mA shunt resistor *must* be made very accurate. Its precise value will depend on the meter used and its value may be calculated as follows:

$$R = \frac{\text{Meter's f.s.d.}}{\text{f.s.d. required} - \text{Meter's f.s.d.}} \times \text{Meter's resistance.}$$

ISTOR TESTER

BY G. A. BOBKER

sources quite cheaply. Others are obtainable in unmarked. The simple but efficient unit described has characteristics to be measured and it will thus stand up to gear at low cost. Construction is uncritical.

Example: Supposing we are using a meter having a f.s.d. of $500\mu\text{A}$ and a resistance of 250Ω . In order to give a f.s.d. of 10mA it would require a shunt resistor whose value will be:

$$R = \frac{500}{10,000 - 500} \times 250$$

This equation gives the value of R_3 as approximately 13.1Ω , therefore a preset potentiometer of some 25Ω will be ideal. To calibrate accurately, the meter is placed in series with another meter of known accuracy as shown in Fig. 3. As the shunt has to be very accurate it is switched in the tester by two of the switch contacts wired in parallel, S_{1c} and S_{1d} . This has the advantage of reducing the contact resistance of the switch.

As the leakage current of some a.f. output transistors can be as high as $450\mu\text{A}$, if a more sensitive meter is used then S_{1c}/S_{1d} should be arranged to switch in a $500\mu\text{A}$ shunt in the "I'co" position. The switch S_1 should be the normal 4-pole 3-way type. If fancy switches, or switches to hand are used, difficulty might be experienced if they are not of the "Break-before-make" type.

Construction

The cabinet was made from plywood fixed together with glue and panel pins, the finished case being covered with "Fablon" or "Contact". The final size of the case will be determined by the size of the meter used. The clips to hold the batteries were made from strips of brass pilfered from a defunct cycle-lamp battery, and these were fixed to the cabinet with Araldite. This is very easily achieved and is far superior to soldering wires direct to the battery cases.

The terminals used in the prototype were of the spring loaded variety and were obtained from surplus equipment. Alternative terminals can be

★ components list

Resistors:

R1 see text
R2 $4.7\text{k}\Omega$ – $10\text{k}\Omega$ see text
R3 $1\text{M}\Omega$ potentiometer
R4 see text

Switches:


S1 4 pole 3 way
S2 3 pole 2 way

Meter:

$500\mu\text{A}$ f.s.d.

Miscellaneous:

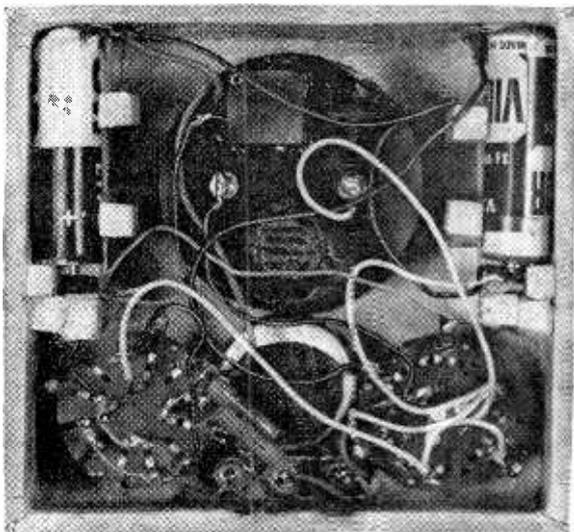Terminals, Batteries—2 penlight 1.5V, Materials for case, solder, wire etc.



made either from bolts or from three crocodile clips as shown in Fig. 5. Constructors may use their ingenuity as to terminals but whichever type is used they must provide good positive action holding the wires tightly. They should also be kept clean.

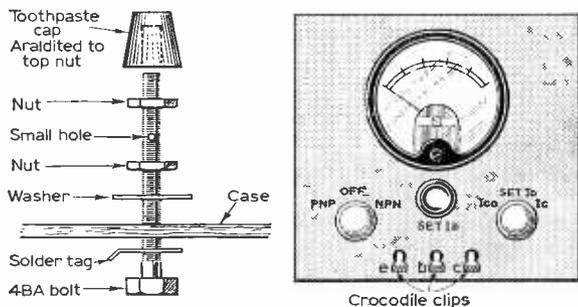


Fig. 5: Suggested approach to the problem of making suitable terminals, these may be modified bolts, or made from crocodile clips.

Using the tester

Set the p-n-p/n-p-n switch to the appropriate position and turn the function switch to the off position. (1) Connect the transistor to the terminals, switch to "I'co" and note the reading. (2) Switch to "Ib" and adjust "Set Ib" to give $20\mu\text{A}$ reading. (3) Switch to "Ic" and note the reading. Repeat (2) and (3) but this time using $I_b=40\mu\text{A}$. The d.c. gain is simply I_c divided by I_b . The small signal or a.c. gain is obtained from the readings noted in steps (2) and (3);

$$\text{A.C. gain} = \frac{\text{Change in } I_c \text{ in } \mu\text{A}}{\text{Change in } I_b \text{ in } \mu\text{A}}$$

Example: If $20\mu\text{A}$ gave 1.2mA , and $40\mu\text{A}$ gave 2.6mA then gain = $\frac{2600 - 1200}{40 - 20} = \frac{1400}{20} = 70$

If the meter scale is marked at the $20\mu\text{A}$ and $40\mu\text{A}$ positions then steps (2) and (3) are made very simple.

Let's Keep the Pirates

You have published many letters and articles in your pages against Pirate radio stations. One of the more recent letters dealt with the shortage of medium-wave channels. Has anyone ever looked to see how many channels are allocated to this country and how efficiently they are being used? It seems to me that using nine channels for the Home Service alone, is not doing things efficiently. Surely by using synchronised transmitters on one channel, we could release eight channels at once for other services. Any regional variations, few and short-lived as they are, could be accommodated on v.h.f.

The public has proved the demand for what the Pirates are providing. Why not let them provide it from land-based stations using channels already allocated to the UK?

R. E. Tinson.

Wilford,
Nottingham.

Comments from New Zealand

This is a somewhat belated reply to H. C. Pryse who wrote in the December issue of *PRACTICAL WIRELESS*, concerning his inability to obtain spares for his H.E.30 receiver. The Lafayette brand name is only one of many names used on this receiver which is made by the Trio Corporation, 6-5 Ichome Shibuya, Shibuya-KU, Tokyo, Japan, to which he may care to write.

Many amplifiers and receivers which are sold in the USA with American names on them are made in Japan and as to Mr. Pryse's inability to receive a reply from the Lafayette Co. I am in full sympathy with him. I find there are quite a few British firms including advertisers in *PRACTICAL WIRELESS* who do not answer my letters when I request information or catalogues. I get the impression that British firms are not interested in overseas orders!

S. Burrage.

Auckland,
New Zealand.

Ease of Pronunciation

There has been a certain amount of controversy over the last few months on the subject of changing cycles to Hertz. I personally do not care one way or the other since it is just as easy to write MHz as it is to write Mc/s.

The point that seems to be overlooked is the pronunciation of the new term. For example, Mc/s and kc/s are usually pronounced "Megs and Kaycees". The new terms MHz and kHz will now, I suppose, be pronounced "Megger hurts and Killer hurts."

V. E. Green.

Redditch,
Worcestershire.

NEWS AND..

EDDYSTONE RADIO FOR "EDDYSTONE" LIGHTHOUSE



The Eddystone Lighthouse has been presented with a transistorised receiver by Eddystone Radio Limited. This new receiver type EB35 will provide the lighthouse keepers with high quality reception on all the broadcasting frequencies in the long, medium, short and f.m. wave bands.

The receiver was presented at the lighthouse by Mr. A. C. Edwards, Director of Eddystone Radio Limited, and accepted, on behalf of Trinity House, by Principal Keeper Emerson. Mr. Edwards is seen here with Principal Keeper Emerson (centre) on the afterdeck of the Trinity House vessel *Stella* as the receiver was being delivered to the lighthouse. The Eddystone lighthouse and Smeaton's Stump can be seen in the background.

"CONTACT" FOR THE SWL

We have recently received a copy of "Contact", the monthly journal of the World Communication Club of Great Britain. It gives useful information for the SWL and contains articles of a nature that would also appeal to Hams.

The aims of the Club are: to interest more people in the international aspect of radio; to provide fellowship to all interested; to encourage and help DXers in their hobby and to learn more about the world we live in through the medium of short wave radio.

If anyone would like further information and details of membership of the Club, contact Mr. S. Green, 26 Tolhouse Street, Great Yarmouth, Norfolk.

ST. DUNSTAN'S CALLING

On Saturday, 8th April, a new callsign was heard on the amateur bands, GB3STD. This was the temporary callsign allocated to St. Dunstan's Holiday Home and Training Centre for men and women blinded on war service, when they held a weekend reunion of war-blinded radio Hams at their centre at Ovingdean near Brighton. The station was equipped with the very latest in amateur radio equipment. They had as their host, Lord Fraser of Lonsdale, St. Dunstan's Chairman who, despite his blindness, was one of the pioneers of amateur radio.

...COMMENT

HELP FOR WEATHER WATCHERS

A high-frequency communication system is to be supplied by The Marconi Company for the East African Meteorological Department. The system will use remotely controlled, self-tuning transmitters, and has been ordered through the World Meteorological Organisation in Geneva. It forms part of a general programme to improve and speed-up the transfer of weather information throughout the world for the World Weather Watch, an international study aimed at increasing the understanding of the fundamentals of meteorology.

The equipment will be installed at Nairobi in Kenya, at the Central Terminal for the clearance of meteorological information from Africa to the Northern Hemisphere. It will provide a greatly improved service from there to Offenbach, near Frankfurt, headquarters of the West German Meteorological Service which will disseminate the information received to the main meteorological telecommunications trunk circuit which runs through Offenbach. The transmission will also be received at Cairo where the information will be relayed to the Moscow World Weather Centre.


Two of the self-tuning transmitters will be installed at one of the East African Meteorological Depts. transmitting stations at Embakasi, just outside Nairobi.

SWEDISH DEALERS VISIT ENGLAND

The first of two parties of Swedish TV and radio dealers recently arrived in London. The visit has been arranged by Luxor Industri Aktiebolag, the largest Swedish-owned radio and TV manufacturer, and the Swedish Radio Dealers' Association. In all, 500 dealers from all over Sweden visited Britain for a combined educational and recreational trip.

Colour TV is expected to start in Sweden in 1970, and during the two visits the Swedish dealers studied British TV and had talks with the BBC and the ITA. They also met representatives of the Radio and Television Retailers' Association.

IMPROVEMENTS FROM AVO

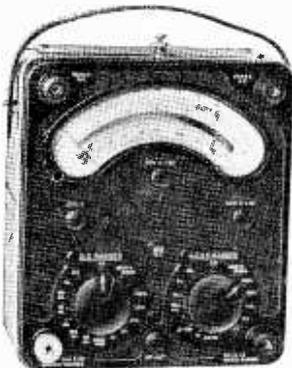

An improved version of its panclimatic Avometer is announced by Avo (MI Group). The new model, which has been granted Ministry of Defence approval (to specification DEF-155), is designated Avo multirange test set no. 1. It will replace the previous models 8SX, 9SX and 40SX which for some years have been extensively used in the Armed Services.

The new version, like its predecessors, is specially designed for use in conditions of extreme temperature or high humidity.

The Avo multirange test set no. 1 retains design features of earlier Avometers, including mechanical cut-out, movement reverse button and interlocked range switching. The five-inch scale has markings for both voltage and current measurements, with a separate scale for resistance measurements. Additional overload protection is provided by a fuse connected in series with the ohms range.

The instrument is supplied with an ever-ready carrying case, a pair of rubber-covered test leads, two spring clips and a pair of test prods.

Dah Di Dah Dit Dah Dah Di Dah

I think it ought to be publicised that the Postmaster-General will do all he can to assist in making alternative arrangements for the place and time for sitting the GPO Radio Amateurs' Morse Test for those who, because of their location, have a long way to travel to any of the officially designated centres.

From my own home in Workington, the nearest designated centres are Whitley Bay and Glasgow, 220 and 270 mile journeys respectively. Alternative arrangements were however made to take the test at Ambleside, 40 miles away, with the further suggestion that it could be taken in Workington but only at very short notice.

All readers working for the Morse Test, living in places remote from named Test centres should write to the GPO Radio Services Headquarters, where I have no doubt they will be given courteous consideration, and some easier-reached centre arranged.

A. G. Thorburn, G3WBT. Workington, Cumberland.

Useful Lists

I would like to congratulate Mr. H. W. Hellyer on his Repairing Radio Sets article in the May issue of PRACTICAL WIRELESS. The lists of Test Gear and Bench Aids that he gives on pages 38 and 39 are an invaluable aid and certainly save hunting through lots of old issues of the three "Practicals" for the article that you know is there but for the life of you, just cannot find! Many thanks H.W.H.

P. Keeling. Woodford Bridge, Essex.

Oh Henry!

I read with interest Henry's remarks on page 27 of the May issue of PRACTICAL WIRELESS regarding Retail Price Maintenance. I do not know how Henry can possibly say servicing will suffer because dealers may have to bring prices down to compete with the "big boys".

It is a fairly common fact that from manufacturer to consumer, the price of a product is nearly doubled. Part of this is taken by the wholesaler—about 10%—so where does the rest go? Why, to the retailer who cannot cut his prices to the man in the street because it will affect his servicing organisation. Already most servicing facilities are rather shoddy, so what have we got to lose?

A. Read.

Walthamstow, London, E.17.

VIBRATO & TREMOLO UNITS

by A. J. Bassett

LET us begin with a definition. "Tremolo" is a sound effect caused by rhythmic variations in the amplitude of a musical note or notes.

Another, radically different, effect is often confused with tremolo. This is "vibrato" i.e. rhythmic variations in the pitch of a musical note. Various amplitude-modulation devices now on the market are wrongly described as "vibrato" units. This is a gross inexactitude for a true vibrato effect can be achieved only by *frequency modulation* of the note.

Acoustic vibrato units are based upon the well-known "Doppler" effect; a note emitted at frequency "n" c/s by a moving object will have an apparent frequency "f" c/s when received by a moving or stationary auditor (e.g. listener or microphone).

The difference between "n" and "f" is the apparent shift in note frequency. This shift depends upon the velocity and direction of movement of both source and auditor. Similarly an apparent frequency-shift can be produced when a note from a stationary source is reflected from a moving object and the reflected sound waves received by a stationary auditor.

Thus arising from the "Doppler" effect we have three main acoustic means to an apparent change in pitch of a musical note radiated at a fixed frequency:

- (1) Moving source of sound
- (2) Moving auditor
- (3) Moving reflector of sound waves.


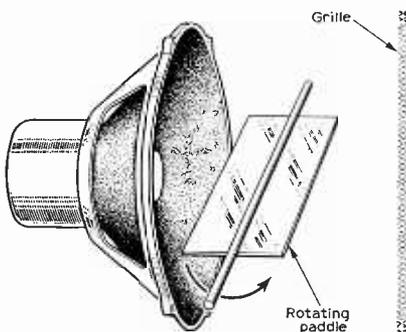


Fig. 1 (left): Rotating paddle method. The paddle may be polished or felt covered (see text).

Fig. 2 (right): Rotating loudspeaker device producing vibrato and tremolo effect.

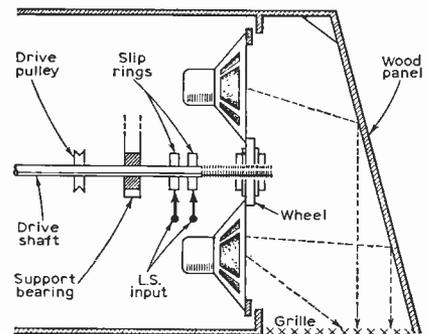

in a single installation and the paddles run at different speeds to produce an exhilarating "chorus" effect.

Best speed of rotation is in the region 100 to 300 r.p.m. for average use. The effect is best applied to the high and middle response speakers, large brass speakers being left alone.

Four main output loudspeakers are mounted in a "pitch" circle on a plywood wheel, which acts as a baffle. The wheel is driven silently round at about 80 r.p.m. Slip rings with multiple phosphor bronze brushes are used to make connections to the loudspeakers. Sound waves are guided outwards by means of a stout wooden panel as shown in Fig. 2. Destructive interference between waves of opposing phase contributes toward a tremolo effect, in addition to the vibrato effect which is the main feature of this device.

Echo Device

Here a real echo chamber is used. Once again, both vibrato and tremolo are produced, with the addition of echo and reverberation. In Fig. 3 a corner mounted loudspeaker (L) operating at a low level produces a complex pattern of direct and reflected sound-waves in the chamber. The sound is picked up by a rotating high-quality directional microphone (M). Because of the varying path-

The "loudspeaker paddle" method is shown in Fig. 1 where a wooden or metal paddle is rotated in front of the loudspeaker, producing a cyclic change in both pitch and amplitude. To enhance the tremolo effect, the paddle should be smooth and polished, thus promoting reflection of sound waves. If only vibrato is required, the paddle may be covered with felt.

There is no reason why several units should not function simultaneously at different speeds. Thus several loudspeakers may be fitted with paddles

lengths of the reflected and direct waves, a phase-shift effect emerges, which is sampled at various, angles by the microphone to produce a more or less intense vibrato effect. Tremolo is produced because some of the sound waves are stronger at different angles.

The degree of echo produced by such a chamber may be undesirable for certain types of music. This echo is determined by the length (S) of the chamber, which could be only 4ft. for minimum echo, though a length of 12ft. might be acceptable in

other instances. This is a subjective matter, and much depends upon the size and character of the main room or hall.

The chamber itself may be constructed in an unused passage or cellar from which extraneous noise is excluded. The walls are best constructed of concrete, brick, stone or heavy galvanised iron. The microphone is driven at about 300 r.p.m. from a silent-running electric motor using plastic or

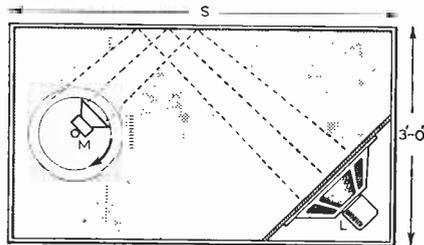


Fig. 3 (left): Echo chamber containing loudspeaker and microphone—only the microphone rotates.

Fig. 4 (right): Block schematic of complete system when using an echo chamber

rubberised gears. Its output passes to slip rings on its drive spindle where multiple phosphor-bronze brushes are used for smooth, electrically silent contact. Fig. 4 shows the block diagram of a circuit suitable for use with the echo chamber.

Electronic Units

In these days of fierce commercial competition, and the consequent production of cheap goods, discrimination suffers, and there is a general tendency to accept substitutes which can never really satisfy the enthusiast. Amongst the many items which fall victim to this trend, we find an important accessory to modern music; the "electronic vibrato unit". This unfortunate device has suffered to such a degree that there are very few genuine electronic vibrato units on the market, and none of the many "constructors' circuits" which the author has seen will give a genuine vibrato effect. The majority of vibrato units do in fact operate as amplitude-modulation devices. Some of these a.m. devices operate by means of screen-grid modulation of a pentode. A typical circuit is shown in


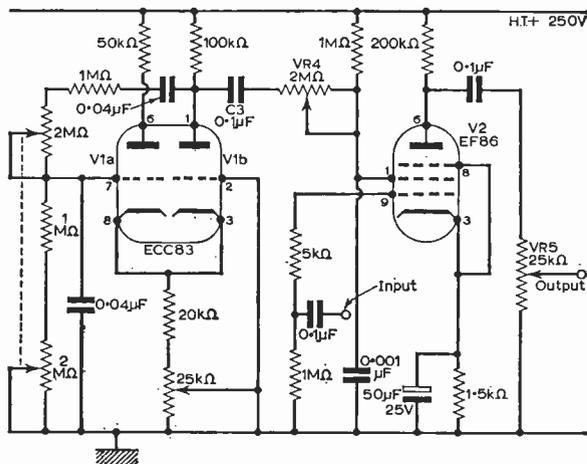


Fig. 5: Tremolo unit suitable for electric guitar or electronic organ.

Fig. 5. V1, a double-triode valve (ECC83) and its associated network form a low-frequency Wien-bridge oscillator, whose output is fed to the screen-grid of V2 via C3 and depth control VR4. The gain of V2 varies in sympathy with the changes in the voltage on its screen-grid, thus providing amplitude-modulation of the audio signal. VR5 is a gain control, which may be adjusted until the

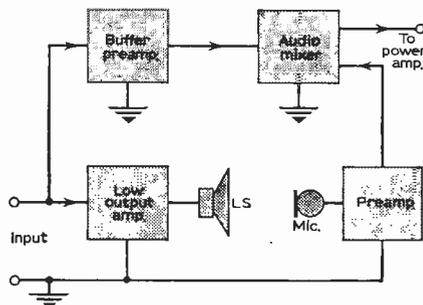

mean gain of the unit approximates unity. The output may contain, in addition to the input frequencies, traces of the tremolo frequency, but these are small and are usually not objectionable. This unit could not possibly produce frequency-modulation of any note it might receive from the pre-amp. A different approach is clearly needed.

We will now discuss a unit which does not rely upon acoustics; can be built fairly small, and which will produce a true vibrato effect; the basis of operation is a phase shift ladder network, whose theoretical diagram is shown in Fig. 6 together with associated amplifier circuits.

To each stage of the ladder is connected a capacitor plate P1, P2, - - - P6, these plates being arranged in a ring in the order given. Above this ring is placed a ring of thin sheet dielectric (e.g. perspex) pressed flat against the plates. A sliding pick-up plate P7 is arranged to run round on the dielectric, thus providing capacitive pickup of the audio signal, from each of the plates in the ring, in turn.

Because the phase of the signal is different at each stage of the ladder network, the output waveform derived from P7 is alternatively "compressed" and "expanded" with regard to the time axis. If the device is correctly adjusted by extra pads or dielectric where need be, amplitude-modulation is rendered negligible. The result is a frequency-modulated output derived from a constant frequency input.

Fig. 7 shows a rough sketch of a printed circuit board, showing arrangement of the capacitor plates P1—P6. It will be noticed that plates P2—P5 are split into different positions in the ring as shown. This aids in the production of a smooth output. An electric motor (not shown) drives the wiper plate P7 (not shown) over these plates to pick up the signal via the dielectric. Signal pickup from P7 is effected by a phosphor-bronze sliding contact. Speed of rotation of P7 is adjusted to about 300 r.p.m. for average use. The ladder network components shown are on the other side of the board. The paired capacitor plates are connected together by wires. The size of the printed circuit, etc., may be left to individual choice, but a pitch circle of 4 to 6 in. should be adequate for plates P1—P6, the

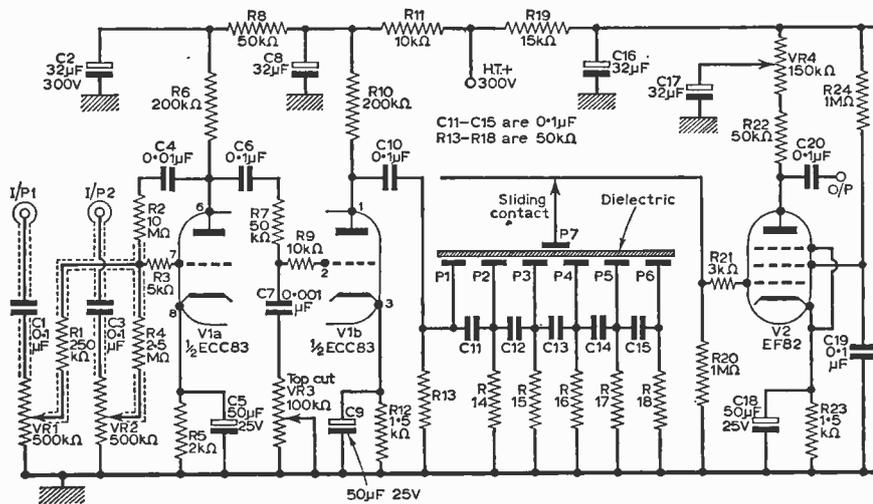


Fig 6: Phase-shift ladder network and associated amplifier—producing true vibrato effect. The component values in the ladder network may be varied (see text).

larger plates producing a better quality. The wiper plate P7 may be big enough to just cover one of these plates, or possibly a little shorter. This may be determined by subjective listening, or by the use of an oscilloscope to obtain good output waveform.

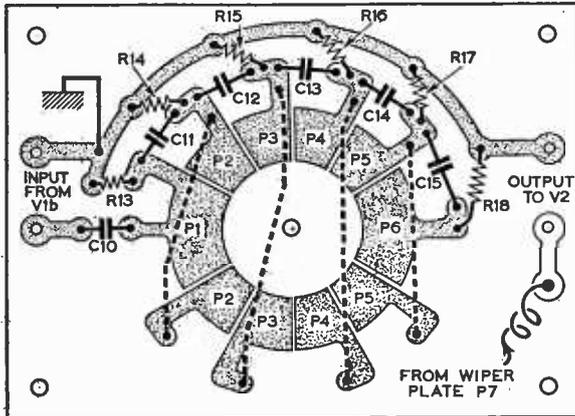


Fig. 7: Suggested layout of printed circuit board showing arrangement of the capacitor plates P1-P6.

Almost any small electric motor may be used provided the power is adequate to drive P7 against the small friction involved; however, a synchronous or regulated type is to be preferred. The motor should be geared down by non-metallic gears to avoid hum pick-up. Several modellers' motors are

available with suitable plastic multi-speed gearboxes, and these should be tested in the shop to ensure that they are reasonably silent-running.

The whole unit should be well shielded against external capacitive pick-up; special care being taken to shield the motor leads (use shielded twin cable), and the valves in separate compartments to avoid audio feedback.

V1 of Fig. 6 forms a preamplifier with high and low sensitivity inputs, and volume controls VR1, VR2. The top-cut tone control VR3 operates in conjunction with low-pass filter network R7, C7, R9. This is necessary to compensate for bass attenuation in the phase-shift network. The output from V1b is fed to the ladder network, and having passed to P7, is amplified by V2. VR4 is a gain control, which cuts down the voltage gain of V2, and will help combat any tendency to a.f. oscillation in this high-gain circuit. Output from V2 is fed to the main amplifier through C20.

The values of C11-C15 and R13-R18 may be varied to suit individual taste and the type of instrument to be used. Thus for bass instruments, a higher value of capacitor may be preferred.

With regard to the mechanical section of this unit, the constructor is not bound to use a printed circuit at all; thus the capacitor plates may be assembled in the form of a cylinder, inside which is a film of dielectric round which runs plate P7. In fact the whole design is quite flexible, and with care the constructor may build a vibrato and/or tremolo unit more suited to his purpose than many on the markets of today.



COLOUR IS COMING!

Yes—it won't be long now. And whether your interest is a practical one or purely academic, you'll want to freshen up your knowledge of what makes the PAL colour TV system tick.

Timed to finish around the time the colour service starts on BBC-2, a compact basic course in colour TV starts in the June issue. Make sure you get the full series by ordering your copies now!

(Note: The June issue, like all others, also contains all the regular features and many other articles which make Practical Television the best two shillings-worth on the market).

JUNE PRACTICAL TELEVISION IS OUT ON MAY 19th — — only 2s.

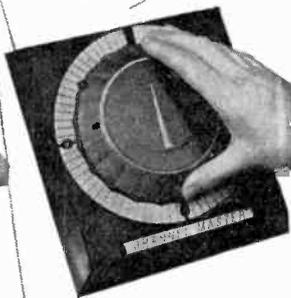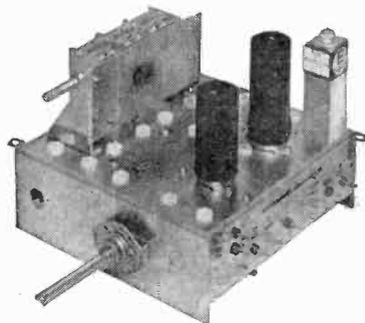1**TODAY'S MOST
ADVANCED
AERIAL
ROTATORS****2****BRILLIANT
VALVED
QOILPAX**

I should like a copy of the Electronics Hobbies Manual. Enclosed is a cheque/P.O. for 10/6.
NAME _____

ADDRESS _____

PW5

FROM THE ELECTRONICS HOBBIES MANUAL ...

1 AERIAL ROTATORS. This range of beam rotators and accessories offers more advanced features than any other on the U.K. market—and at a lower price. The rotators can aim an aerial to within one degree of the transmitter location. No guesswork, no irritating gear clicks—just precise fine adjustment through 365° with accurate repeatability. With both models the aerial is held in place in high winds with an ingenious stop-lock brake. **COMPASS MODEL** offering remote fingertip control and continuous direction indication—£12.12.0 plus 3/6 p&p.

AUTOMATIC MODEL (illustrated) offering remote control and facility to pre-set to desired location. A synchronised motor in the control unit gives continuous indication of aerial position—£17.17.0 plus 3/6 p&p.

2 VALVED QOILPAX. If you are building a communications receiver, (whether for general coverage or hambands), why not avoid all the headaches in the front end by purchasing one of our highly sensitive 'QOILPAX' tuners. Sensitivity is 1 μ V for 15dB S/N ratio, and second channel interference is exceptionally low. The high sensitivity RF stage is designed around an EF183 connected in a Miller compensating circuit, followed by an ECH81 triode heptode frequency changer, using oscillator circuits. These give optimum mixing conductance on each waveband without any pulling. Ideal also as a converter, feeding into existing receivers. General coverage and hambands versions are available, each with an IF output of 1620 Kc/s. All units are supplied completely wired, tested and aligned. Either model £12.12.0 each plus 4/- p&p.

FREE Aerial Supplement to the Electronics Hobbies Manual. This publication MG 222S1 supplementing the Manual lists our aerial rotators and wide range of J-Beam aeriels. Send for your copy today.

For the 600 page Electronics Hobbies Manual or further details of the products displayed on this page write to: Electronics (Prop. STC Ltd.) Edinburgh Way, Harlow, Essex. Telephone: Harlow 26777.



High-grade components for amateur communications

electronics

STEREO DYNAMIC MICROPHONE

A new outstanding stereo microphone excellent for pick-up of reverberation for full dimensional sound. Gives full 360° pick-up. Impedance 50Kohm Output—60db. Response 50-15,000 cps. With stereo/mono switch, desk stand, floor stand adaptor and cable.



A real bargain at **£4.19.6**



TRANSISTOR INTERCOM SYSTEM

Deluxe two way system for use in home, office, shop etc.—Ideal as a

baby alarm. Compact size, for table or wall mounting. Buzzer call system and volume on/off control. Supplied with cable and battery.

ONLY 49/6

EAGLE TT.144 DYNAMIC TRANSISTOR TESTER

Tests in-circuit or out of circuit. Identifies PNP and NPN types. Indicates electrode open circuits, short circuits and current drain. Complete with instructions.



£4.10.0

RELDA RADIO LTD

(Dept. P.W.18) 87 Tottenham Court Road, London, W.1.

EAGLE MATCHING HIGH FIDELITY AM/FM TUNER AND INTEGRATED STEREO AMPLIFIER

Beautifully styled in grey cabinets with silver front panel and knobs.


MODEL AFM.200



Covers 88-108Mc/s FM and 535-1605 Kc/s MW. Flywheel tuning, magic eye, automatic frequency control switch. Includes Multiplex socket for connection to multiplex adaptor.

PRICE £29.10.0

MODEL SA200

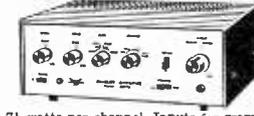

7½ watts per channel. Inputs for gram, tape, tuner, mike, aux. tape output socket. Separate volume controls for each channel. Separate bass and treble controls. Stereo/Mono selector. Stereo headphone socket. Impedance. 4, 8 or 16 ohms. **PRICE £25.10.0**

DUAL CONVERSION PROFESSIONAL COMMUNICATION RECEIVER



Frequency ranges. 160 metres (1.8-2 Mc), 80 metres (3.5-4 Mc), 40 metres (7.7-5 Mc), 20 metres (14-14.5 Mc), 15 metres (21-21.5 Mc), 10 metres (28-30 Mc), 6 metres (50-54 Mc). Incorporates Bandspread tuning, RF gain, RF Tuning, AF gain, Stand by/AM/SSB/CW switch, Selectivity switch, BFO, calibrator, AVC, ANL. Headphone jack, etc. etc. A really advanced receiver offering professional performance and appearance for the amateur enthusiast at a reasonable price—**ONLY £59.19.6**

ALL ITEMS SENT POST FREE

FOR FULL DETAILS OF THESE AND MANY OTHER ITEMS SEND FOR FREE COMPREHENSIVE CATALOGUE EAGLE NEWS AND ORDER FORM. ALL ITEMS AVAILABLE POST FREE AND COVERED BY 12 MONTHS' GUARANTEE.

CALLERS WELCOME AT OUR HI-FI SHOWROOM

9-TRANSISTOR TWO WAY RADIO

Professional type for powerful performance. Ultra sensitive superhet receiver with R.F. amplifier. Crystal control. Incorporate push to talk switches and volume controls. Complete with earphones, 45° telescopic aerials, batteries and leather carrying cases.



PAIR £19.19.6

(These cannot be operated in U.K.)



TRANSISTORISED SIGNAL INJECTOR

Covers AF and RF. Excellent for fault finding and servicing radios, TV, amps, tape recorders, cartridges, speakers etc. Complete with manual and battery. **SAVE TIME AND MONEY FOR ONLY 32/6**

EAGLE CRYSTAL SET KIT



Self-powered with private earphone. Supplied complete with instructions. **NOW 15/- ONLY**

EAGLE MODEL TD. 79 TAPE HEAD DEMAGNETIZER



Compact, easy to handle. Will remove magnetism from tape heads permitting improved recordings. Reduces harmonic distortion and noise level. Now at the reduced price of **85/-**.

GOODMANS HIGH FIDELITY MANUAL

A Guide to full listening enjoyment



The Manual is much more than a catalogue of Goodman's High Fidelity Loudspeakers—it contains informative articles, including advice on stereo, special beginners page, and full cabinet drawings. You'll find it interesting as well as informative.

The Perfect Combination MAXAMP 30

TRANSISTORISED STEREOPHONIC HIGH FIDELITY AMPLIFIER 15 + 15 watts • Silicon solid state • Integrated pre-amplifier Negligible distortion • **£49.10.0.**

STEREOMAX

MATCHING AM/FM STEREOPHONIC FM TUNER

Transistorised • Outstanding specification • Stereo de-coder (optional) **£60.0.0.** + £11.18.3. P.T. inc. Surcharge.

Both MAXAMP 30 and STEREOMAX have polished wood cases (10½" x 5½" x 7½" deep) in Teak or Walnut to order.

Full specifications of the Maxamp 30 and Stereomax are given in the High Fidelity Manual—send the coupon for your FREE copy—or pay an early visit to your Goodman's dealer.

FREE Please send 'Hi-Fi Manual' together with name and address of my nearest Goodman's dealer.

Name.....
Address.....

PW6

GOODMANS INDUSTRIES

AXIOM WORKS • WEMBLEY • MIDDLESEX. Tel: 01-902 1200
A Division of Radio Rentaset Products Ltd.

SERVICE VALVE AND SEMICONDUCTOR EQUIVALENTS

(RSGB)

5/6 Post Paid

This new edition has been enlarged to 64 pages, and now includes a much higher proportion of semiconductors. This book will enable the well-known tables of valves and semiconductors to be used with service types (CV, VT etc)

RADIO AMATEUR'S HANDBOOK

(ARRL)

44/- Post Paid (softbound)

52/- Post Paid (hardbound)

The 1967 edition has arrived from America and contains a large number of new circuits using the latest techniques. All the 648 pages cover the whole technical side of amateur radio from basic fundamentals to the latest receivers and single sideband transmitters.

TRADE ENQUIRIES WELCOME

Further details of other RSGB Publications and information about membership of the Society, including a free copy of the monthly RSGB Bulletin may be obtained on request from:

RADIO SOCIETY of GREAT BRITAIN, Dept. P.W.
28 LITTLE RUSSELL STREET, LONDON, W.C.1

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times in GMT
Frequencies in kc/s

THE BROADCAST BANDS

by JOHN GUTTRIDGE

ALBANIA: *Radio Tirana* (Rue Ismail Quemal, Tirana) European English schedule is 0630-0700 6,157 plus possibly 7,120; 1500-1530 1,214 (some reports say 7,265/1,277); 2000-2030 7,265; 2200-2230 7,265 (plus 1,310 in some reports). Non European English TX believed to be 0200-0300 9,715/7,265 and 0400-0430 7,265/9,390/1,310.

Radio Shkodra (Drejtoria e Radio Shkodres Shkoder) may just be heard at 1700-1930 on 8,217.

Andorra: *Radio Andorra* (c/o 82 Chelsea Manor Street, London, S.W.3) has been testing on 719 at 1800-0100 with a view to starting an external service beamed to the U.K.

Bulgaria: *Radio Sofia* (4 Boulevard Dragan Tsankov, Sofia) reported with new frequencies 11,930/11,955 for African English TX at 2105-2130.

France: O.R.T.F. (Maison de l'O.R.T.F., 116 Avenue du President Kennedy, Paris 16) has English 0515-0530 9,500/11,960; 1100-1115 17,850/21,650; 1300-1330 15,245/17,740/21,580; 1915-1930 15,245/9,700.

Germany: *Deutsche Welle* (Bruederstrasse 1, Postfach 344, 5 Koln) has made following changes in English TX: 1550-1620 11,765/15,435; 1100-1115 11,930/15,275/17,875; 1900-1910 11,925/15,380.

Westdeutschen Rundfunk Wallrafplatz 5, Koln) is to increase the power of its 1,586 TX to 800kW.

Radio Free Europe (1 Englisches Garten, Munchen) shows the new frequencies of 7,215 and 21,575 in its latest schedule.

Great Britain: BBC (CEXB, Bush House, London, W.C.2) using 25,750 for 1200-1300 Chinese TX.

Holland: *Radio Nederland* (P.O. Box 222, Hilversum) using 25,610 for some programmes. The 1600-1720 Sunday Happy Station session has been reported on 17,765/11,730 A special QSL is to be issued from April 28 to October 7 to commemorate the Canadian Expo 67 exhibition. A new picture series will then follow.

Hungary: *Radio Budapest* (Brody Sandor—S.U. 5—7, Budapest VIII) now uses 3,995/6,234/7,100/7,220/9,833 for the 2200-2230 English session.

Italy: R.A.I. (Viale Mazzini 14, Rome) has completely revised schedule. English is now aired as follows: 2135-2155 9,710/7,275/6,050; 0100-0120 11,810/9,575; 2200-2255 11,905/9,540/6,095; 0350-0410 17,770/15,310/11,905; 0425-0504 7,275/6,050; 2025-2045 9,575/7,235/6,130.

Monaco: *Trans World Radio* (Rue de la Poste 5, P.O. Box 141, Monte Carlo) has English 0630-0730; 7,295; 0730-0815 9,655/7,295. 0815-1000 Sunday, 1200-1245, 1430-1530 9,655. Frequencies are subject to confirmation.

Poland: *Radio Warsaw* (Warsaw). Revised European English schedule is: 1830-1857, 2130-2155 9,525/7,125;

1930-2000 9,525/7,285/7,125/1,502; 2030-2100 9,675/9,540; 2230-2300 9,540/7,285/1,502; 2303-2330 818.

Rumania: *Radio Bucharest* has new English transmission at 1200-1230 on 11,920/15,250 and 1300-1330 11,920/15,250/15,318. The 1500-1530 is now on 11,885/11,920/15,250.

Spain: *Radio Nacional de Espana* (General Yague 1, Madrid) has a new Hungarian TX at 1300 on 9,760.

Sweden: *Gothenburg Radio* (Omsala) reported testing at 0700, 1223 and 1715 on 11,820. Does anyone know anything about this station?

Radio Sweden (Box 955, Stockholm 1) now has English: 0900-0930 9,625/21,585; 1100-1130 9,625/15,240; 2015-2045 9,625/11,705; 1900-1930 11,705/17,840; 1230-1300 15,240/21,690; 2245-2315 9,620/11,705; 1400-1430 21,585/17,840; 0515-1545 17,840; 1600-1630 17,840/15,240; 0200-0230, 0030-0100 11,805; 0330-0400 11,705; 2330-2400 1,178.

Switzerland: *Swiss Broadcasting Corporation* CH 3000, Bern 16). The summer English schedule is: 0130-0315 6,120/9,535/11,715; 0515-0700 9,695/11,715; 0700-0900 (not Sundays) 6,135/9,535; 0700-0900 9,590/11,775/17,890; 0915-1030 15,305/21,520/17,830; 1115-1300 9,665/11,865; 1315-1500 15,235/17,775/21,520; 1515-1700 15,305/17,830/21,540; 1900-2045 9,665/11,865. Available transmitter powers are now 25/100/150/250 kW.

U.S.S.R.: *Radio Moscow* (Moscow) now broadcasts 24 hours a day in Chinese to China.

Radio Kiev (Ukrainiske Radio, Radio Centre, ul Khreshchatik 24, Kiev, Ukrainian SSR) has English to Europe Mondays, Thursdays and Saturdays at 1900-1930 6,020/6,040/9,640; 2230-2300 1,241. To North America on the same days 0030-0100 7,120/7,280/7,290/7,330/9,680; 0430-0500 7,250/7,290/7,330/9,600.

Yugoslavia: *Radio Belgrade* (70 Borisa Kidrica, Belgrade) has English 1530-1600 11,735/15,240/9,505; 1830-1900 6,100/7,200; 2200-2215 1,268/6100/7,200/9,505.

Clandestine: *Radiofonica Stamos i Foni*. This is a communist station with Greek programmes produced in East Germany and probably transmitted from Bulgaria. It can be heard 0510-0545 on 6,215 and 1730-1800 on 8,065.

Radio Portugal Libre transmits at 0700-0730 on 12,008; 1200-1230 11,510; 1900-1930 and 2115-2145 9,445.

Radio Espana Independiente transmits 0600-0700 6,950; 1300-1400 15,365; 1615-1800 9,430/10,130; 1800-2230 6,950/7,005/9,430.

Contributions came this month from Radio Sweden, R. J. Warner, A. E. Roxburgh, R. Severn, J. McDonald, J. W. Smith, D. S. Abbott, K. Proctor, W. E. Bartlett, D. Owen, J. Fitzgerald, and the Swiss Broadcasting Corporation.

WE will spend two minutes with heads reverently bowed in silence before pressing on. This token of mute sympathy is for the G3JDG receiver which passed peacefully away—just as ten metres was beginning to get interesting too. The mains “trany” has shorted itself out so it looks like I’m stuck with the t.r.f. until after Easter. Have you ever noticed how things always break down on a Sunday or a bank-holiday, when all the shops are shut? Prior to being struck “mains tranyles” however, things were going great guns and most bands appeared to be very busy. Ten metres has yielded VK stations at 5 and 7 on a.m. phone; fifteen has gone literally potty with signals at times and seems more consistently open these days; twenty has been, well twenty, lots of DX and quite good openings to the Pacific and Oceania. On seven megs lots of noise, commercials and DX too if you can stand the pace and have the skill to wrinkle them out. Eighty metres, well I didn’t do too well this month but others have sent in some very fine logs for 3-5 so it must be me. (More exciting confessions next month.)

LOW FREQUENCIES

Still very few people send logs for the l.f. bands. Everyone seems to stick h.f. where DX falls like ripe plums into the ears of anyone who cares to listen out. Some people are persistent however.

N. Henbry (Sussex), EA12, 20 metre dipole for 7mc/s, 7ft. vertical copper rod at 30ft. for all other bands. Norman really goes to town on the l.f. segments. On 80 s.s.b. he logged—FØAO/M, K1SLZ, K2DPA, K3UQU, K4SXT, K7UIT/9A1, KP4AST, TF3EA, TI2NA, VE1AHP, VE2BTS, VS9ALV, W1ZBT, W2ZPO, W3BMS, WA3DCG, W4SIB, 3A2MJC, 3AØAE, 3B1FG, 3C1UA, 3C2WM, 3C3FJZ/SU, 9H1AB. Up higher on 7Mc/s the log reads—CN8AW, CN8BV, GC8HT, K5OSH, PZICF, WB2CKS, W4OMW. It’s no good, I shall have to lay a long lead from Norman’s shack to my place to plug in a spare pair of phones.

L. Smith (Glasgow), 19 set (modified), 66ft. long wire went s.s.b’ing on forty and hooked—CN8AW, CN8BB, DJ4AX, DJ7QV, DL9ME, EP3AM, I1BAF, OE2EGL, PY6NW, UA3KBO, UB5KIW, YU3LB. Nearly all the reports this month were for the h.f. bands, so let’s turn the bandswitch to 20/15/10 and see what’s about.

HIGH FREQUENCIES

A. Darragh, QTH not stated so we’ll put him down as no fixed abode, GC1U, 100ft. long wire running N/S. On 20 s.s.b.—AC4AK, CE1FC, CE3TS, CP8OS, CT1BK, EP1BP, EP2BI, HI8LAL, HK4KL, HV3SJ, IS1KW, JA—1AEA, EZT, 4TRV, KC6BW, KH6BT, KL7BZ, KR5CUN, KR6UL, KS6BT, LU5AH, OX3LY, OX4AA, OY7S, PX1PA, TF3EA, TG2IA, TG8IA, TI2PAS, TU2DC, UA7JA, UA9FC, UF6KPA, UJ8KAA, UN1CC, U5ARTEK, VK—2ID, 3AUP, 4KS, 5LT, 6KK, 7SS, W4EFB/P/KH6, XE1FFA, XF1KB, YS1AG, ZL—1AI, 3BE, 3QH, ZS—2PD, 3FT, 6AJL, 6RA, VU2BX, 3A—ØAE, 2BS, 2MJ, 2RJC, 3B—1GL, 3C—3BVE, 5SV, 6ALX, 7ZU, 8AD,

4U1SU, 4X4MO, 5A1TV, 5A5TV, 5H3TG, 6Y5MJ, 9G1ND, 9H1A, 9M2DX, 9X5PB.

S. Porter (Surrey), has an R1155 with a 20 metre dipole. He reckons the best time to listen is around sunrise, and from 1800 onwards. His log for twenty includes—EL3D, KA6BFU, KP4CSV, KP4AXC, VK2NI, VK2ID, VL9UC, XE1CE, YV5BSL, 3A2KO, 4X4BL, 5A5TV, 7XØAH, 9X5A.

D. Clark (Bucks), progressive s/het plus PR30, 60ft. NW/SE, 20 s.s.b.—IS1DMN, K1EPG, K2AGZ, K3FGO, K4LZU, K5ZSX/MM, KG6AQQ, KL7EBK, KP4ID, KR6UL, OD5FA, OX4VT, SVØWII, TF3HS, VE1ACD, VE1AGH, VE3DJE, VK2AFD, VK3SX, W—1/2/3/4/5/9/Ø, WA8CH/MM, YN1JW, YV4AZ, ZE1AE, ZF1GC, ZL3UY, ZS1JM, 3A2CP, 5A1TG.

P. Baker (S. Wales), HE30, 120ft. l.w., heard these on 15 metres, mostly s.s.b. the rest a.m.—CN8FT, CR3KD, CR4BA, CR7BO, CR8AL, CT2AP, EA6BG, EA9EJ, EL6B, EP2RT, EP3AM, HC2SW, JA—1OYY, ITTL, 4AXW, 9JX, K6PIZ, KP4CQV, KV4CX, MP4—BBA, BGM, BGL, OA4TF, OD5BU, OX5AR, PY9AI, VE6QG/SU, SVØWL, TF2WKE, TI2RLJ, UA9DT, VE7PV, VK5HT, VS9ALV, WB2FBQ/MM, W6ITA, W7VSM, YS1TF, ZE6JL, ZL—3KA, 4JI, 4MZ, ZB1YR, 3C5HV, 3C6AJY, 4X4LL, 5A1TV, 5N2ABB, 7XØWW, 9G1EZ, 9H1X, 9U5BB.

J. Preece (Cheshire), PCR3, 60ft. l.w., 15 metres all a.m.—CN8CF, CO8RA, CR4EJ, CR6AU, CR7FM, EA9EJ, EP2RT, FG7XE, FM7WQ, HC2SW, HI8BGA, KG6AAY, LU5DZ, MP4BGL, OD5ET, PY1MGW, ST2SA, SV1DL, TF5TP, TJ8AC, VP6BW, WA5QQF, W6QBA, YV4ON, ZE6JE, 3C3GCO.

P. Knowles (Cheshire), CR45 plus PR30, 70ft. l.w., listened on ten metres a.m. for—CT1JW, EA3HL, K1ZFP, LA2XK, MP4BGM, UA3AWK, UB5EVW, VP7NP, W1DT, WB2QEH, ZS6RQ.

G. Taylor (Staffs), HE30, 135ft. l.w., ten metres a.m.—PJ3CL, VP6UN, XE1CT, 9Y4BS, on s.s.b.—CR7ER, DU1FH, EP2GI, FG7XL, HC1MF, JA2BVY, KV4EY, VK4TT, VP2MK, XW8AL, YV1EJ, ZE4JS, 5R8AS, 9LITL.

P. Allsop (Derby), GC1U, 66ft. l.w. all a.m. on ten metres—K1ZKD, K2BJR, K3HTZ, KØQMU/P, VE3CKM, W1UHY, W2BFZ, W3DJW, W5WS, W9MZM, XE2CJ, ZC4MO.

P. Elliott (S. Africa), 5 valve s/het, 105ft. l.w. logged these on phone on 10—CE6EZ, HBØWEE, KR6BF, KV4CX, KV4EY, MP4BBA, OD5EC, PY2PA, SVØWFF, VE6ALA, WA6UEK, YA5RG, YV1PP, YV3FBP, 3C3FDZ/P/SU, 4Z4AO, 5N2ABA, 5R8AS, 9H1HR, 9M2LO, 9V1NY.

WHERE AND WHEN

Contests and rallies are on the increase now that the warmer months are coming. In May there’s quite a few and my diary reads—7th, Thanet Mobile Rally at Ramsgate; 7th, 2 metre portable contest; 20th—21st, 1296Mc/s contest; 27th—28th, 432 Mc/s contest; 29th, Redbourne Fair (Herts) listen on 160; June 3rd—4th, National Field Day. Deadline for this month is 20th. The deadline for all logs in future will be the 20th of each month.

LASKY'S RADIO

For the Finest Value and Service to HOME CONSTRUCTORS & ELECTRONICS ENTHUSIASTS

TRANSISTOR PORTABLES



THE SKYROVER De Luxe

7 transistor plus 2 diode superhet, 6 waveband portable receiver covering the full Medium Waveband and Short Waveband 31-94M and also 4 separate switched band-spread ranges, 13M., 16M., 19M and 25M., with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions. Superhet, 470 Kc/s. All Mullard Transistors and Diodes. Uses 4 U2 batteries. 5in. Ceramic Magnet P.M. Speaker, 500 MW Output, Telescopic and Ferrite Rod Aerial. Tone Circuit with separate Tone Control, Volume Control, Tuning Control and Waveband Selector. In wood cabinet, size 11 1/2 x 6 1/2 x 3in. covered with washable material, plastic trim and carrying handle. Car aerial socket fitted.

LONG WAVEBAND COVER FOR THE SKYROVER

A simple additional circuit provides coverage of the 1100/1950M. band (including 1500M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data.

Only 10/- extra Post Free. This conversion is suitable for receivers that have already been constructed. Data 2/6 extra; refunded if you purchase the parcel. All components available separately.

Can now be built for **£8.19.6** Post 5/- extra

H.P. Terms: 60/- deposit and 11 monthly payments of 12/6. Total H.P.P. £10.0.3. Four U2 batteries 3/4 extra.

SPECIAL INTEREST ITEMS

NEW! LASKY'S CLEAR PLASTIC PANEL METERS

Precision made in Japan by HIOKI. Each meter boxed and fully guaranteed with all fixing nuts and washers. Sizes are of front panel. Add 1/6 Post on each.

Type KR-52 3 x 2 1/2in. (illustrated)
1 mA DC 32/6 300 V DC 32/6
5 mA DC 32/6 500µA 37/6
1 mA S Meter 39/6



Type MK-38A 2in. square	32/6	Type KR-55 3 1/2 x 3in.	36/-
1 mA DC	32/6	1 mA DC	35/-
5 mA DC	32/6	5 mA DC	35/-
300 V DC	37/6	300 V DC	42/6
50µA	29/6	500µA	42/6
1 mA S Meter	39/6	1 mA S Meter	38/6
Type MK-45A 1 1/2in. square		Type MK-65A 3in. square	
1 mA DC	25/-	1 mA DC	36/-
5 mA DC	25/-	5 mA DC	35/-
300 V DC	25/-	300 V DC	38/-
500µA	25/-	500µA	38/6
1 mA S Meter	35/-	1 mA S Meter	37/6

NOW AVAILABLE! — JOYSTICK AERIALS

Revolutionary variable frequency antenna for transmission and reception. With a variable matching unit these antennae perform as a high 'Q' device at any selected Medium or Short waveband. Send for S.A.E. for descriptive leaflet.

AERIALS (7' 6" Long)		Matching units	
VFA Standard	24 15 0	A.T.V. 3A	23 12 6
VFA DeLuxe	25 19 6	A.T.V. 4	24 4 0
		A.T.V./4RF	26 6 0

NEW INTERNATIONAL TAPE

FAMOUS AMERICAN MADE BRAND TAPE AT RECORD LOW PRICES IN CELLO WRAPPED BOXES FULLY GUARANTEED

3in. Message tape, 150ft.	9 6	5 1/2in. Long play, 1200ft. Acetate	12 6
3in. Message tape, 225ft.	8 9	5 1/2in. Standard play, 850ft. PVC	11 6
3in. Message tape, 300ft.	7 6	5 1/2in. Long play, 1200ft. Mylar	15 0
3 1/2in. Triple play, 600ft. Mylar	10 0	5 1/2in. Triple play, 2400ft. Mylar	45 0
4in. Triple play, 900ft. Mylar	17 6	7in. Standard play, 1200ft. Acet.	12 6
5in. Double play, 1200ft. Mylar	15 0	7in. Standard play, 1200ft. Mylar	12 6
5in. Long play, 900ft. Acetate	10 0	7in. Long play, 1800ft. Mylar	19 6
5in. Standard play, 600ft. PVC	8 6	7in. Double play, 2400ft. Mylar	26 0
5in. Triple play, 1800ft. Mylar	35 0	7in. Long play, 1800ft. Acetate	15 0
5 1/2in. Double play, 1800ft. Mylar	22 6	7in. Triple play, 3600ft. Mylar	50 0

1/- P. & P. 1/- extra per reel. 4 reels and over Post Free

CONSTRUCTORS BARGAINS

SPECIAL PURCHASE—UHF/VHF TV TUNERS

Well known British makers surplus stocks. Now available for the first time to the Home Constructors. Add 2/6 Post and Packing on each.

VALVE UHF MODEL (illustrated)

In metal case size 4 x 6 x 1 1/2in. Fully tunable—complete with PC86 and PC88 valves. LASKY'S PRICE 29/6 Without valves 12/6




TRANSISTORISED VHF TUNER

Sub-miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case size 3 1/4 x 2 1/2in. LASKY'S PRICE 37/6

TRANSISTOR FM TUNER CHASSIS

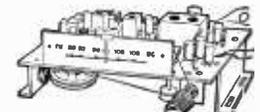
Fully tunable—range 88 to 108 Mc/s. Completely wired on printed circuit. 10.3 Mc/s. IP. 6 transistors and 3 diodes. Slow motion tuning drive. Size 6 1/2 x 4 x 2 1/2in. Operates from any 9v. D.C. source. Full data and circuit supplied.



LASKY'S PRICE £7.19.6 Post 5/- extra.

NEW—LASKY'S MINIATURE TRANSISTOR AMPLIFIER MODULES

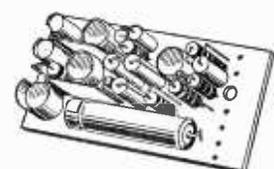Incorporating the very latest circuitry to provide high sensitivity and good quality in conjunction with extreme small size and compactness. High quality Newmarket transistors used throughout. All designed to operate on 9v. miniature battery. Add 1/- on each for Post and Packing.



TYPE LRPC 1. 3 transistor. Input sens. 50mV. output 150mW output imp 40Ω. size 2 x 1 x 1 1/2in. PRICE 27/6

TYPE LRPC 4. 5 transistor. Input sens. 150mV. output 330mW, output imp. 15 Ω, size 2 1/2 x 1 1/2 in. PRICE 22/6

TYPE LRPC 5. 6 transistor. Input sens. 8mV. output 3W, output imp. 3Ω, size 5 1/2 x 1 1/2 in. PRICE 59/6

SINCLAIR SUPER MINIATURE KITS

Write for details of Package Deals

THE MICRO-6 miniature radio only 1 1/2 x 1 1/2 x 1 1/2in.	£2 19 6
THE MICRO-FM (tuner/receiver)	£5 19 6
THE MICROMATIC World's smallest radio kit 1 1/2 x 1 1/2 x 1 1/2in.	£2 19 6
THE MICROMATIC Ready built, tested and guaranteed	£3 19 6
THE Z-12 12 watt amp. and pre-amp. fully built	£4 9 6
PZ-3 power pack for Z-12	£3 19 6
STEREO 25 Pre-amplifier control unit fully built	£9 19 6

VEROBOARD

High grade laminated board with copper strips bonded to it and pierced with holes.

Boards		Accessories	
42/1503 2 1/2 x 5 in.	3/11	Terminal pins—pkt. of 50	3/-
43/1504 2 1/2 x 3 1/2 in.	3/3	Spot face cutter tool	7/8
45/1507 3 1/2 x 5 in.	5/6	Pin inserting tool	9/6
46/1508 3 1/2 x 3 1/2 in.	3/11	Post 6d. per item extra.	
44/1505 3 1/2 x 17 in.	15/6	Orders of 10/- and over post free.	

GORLER UT 340 FM/VHF TUNING HEART

Permeability tuned—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case, size 3 x 2 1/2 x 1 1/2in. Circuit supplied. LASKY'S PRICE 15/11 Post 2/-, ECC85 valve 9/- extra.

TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET 81, GET 85, GET 86 2/6; 875A, 874P 3/6; OC45, OC71, OC81D 4/6; OC44, OC70, OC76, OC81 5/6; (match pair 10/6); AF117, OC200 6/6; OC42, OC43, OC73, OC82D 7/6; OC201, OC204 15/-; OC205, PC206 19/6; OC28 24/6; OC75 8/-.

TRANSFILTERS

by BRUSH CRYSTAL CO., Available from stock.

TO-01B 465 kc/s. ± 2 kc/s.	TO-02D 470 kc/s. ± 1 kc/s.	9/6 each Post 6d.
TO-01D 470 kc/s. ± 2 kc/s.	TF-01B 465 kc/s. ± 2 kc/s.	
TO-02B 465 kc/s. ± 1 kc/s.	TF-01D 470 kc/s. ± 2 kc/s.	

NOW AVAILABLE—OUR NEW BARGAIN BULLETIN. 24 foolscap pages packed with hundreds of bargains for the "ham" and service man—exclusive to Lasky's—plus full list of regular stock items. PRICE 6d. POST FREE.

207 EDGWARE ROAD, LONDON. W.2 Tel. PAD 3271
118 EDGWARE ROAD, LONDON. W.2 Tel. PAD 9789
33 TOTTENHAM CT. RD., LONDON. W.1 Tel. MUS 2605
All the above branches open all day Saturday. Early closing Thursday.


42 TOTTENHAM CT. RD., LONDON. W.1 Tel. 01-580 2573
152/3 FLEET STREET, LONDON. E.C.4 Tel. FLE 2833
Both open all day Thursday. Early closing Saturday.

Mail Orders and correspondence to 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel.: STerney Green 4821/2

LASKY'S FOR SPEEDY MAIL ORDER SERVICE




Eddystone high performance receivers

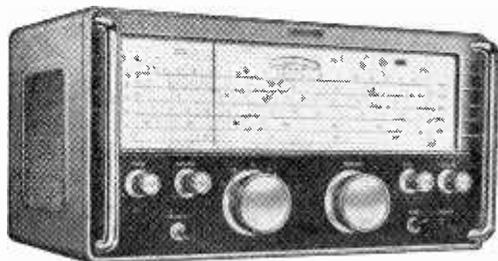

840C A.C or D.C Communications Receiver

An 8-valve receiver with gap free coverage from 480 kHz to 30 MHz providing excellent reception of broadcast programmes and from all major s.w channels including marine and international distress frequencies. The famous Eddystone extended band spread and logging scale is an essential feature. Being suitable for a wide range of a.c and d.c voltages and fully tropicalized, the receiver is suitable for use in any part of the world. £66.

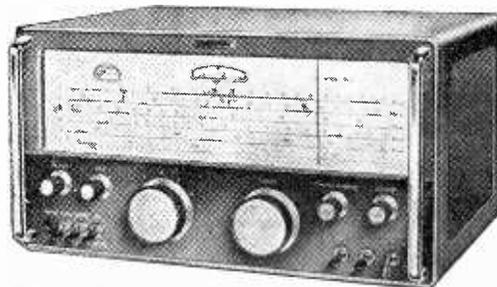


940 H.F Communications Receiver

An outstanding 13-valve receiver with two r.f and two i.f stages, silicon diode noise limiter circuit and high quality push-pull output. Built to a professional specification, facilities include provision for c.w, a.m, and s.s.b reception over the range of 480 kHz to 30 MHz in five bands. Suitable for 110/125 V and 200/250 V, 40-60 Hz a.c mains. £133.


Comprehensive information from your Eddystone distributor or: Eddystone Radio Limited (A MARCONI COMPANY)
Eddystone Works, Alvechurch Road, Birmingham 31. Telephone: Priory 2231 Telex: 33708 LTD/ED 46

PEOPLE PREFER MARTIN

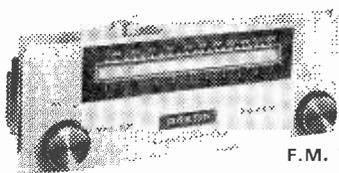FOR RELIABILITY, FOR QUALITY, FOR ADD-ON-ABILITY, FOR ECONOMY



F.M. TUNER

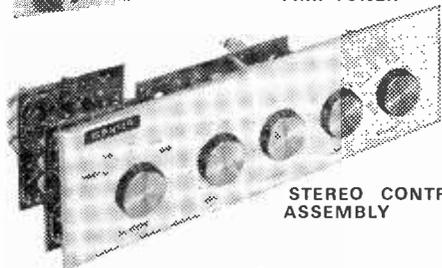

STEREO CONTROL ASSEMBLY

MARTIN AUDIOKITS are available for Mono, and can be doubled up for stereo, or as complete stereo units. 3 ohm and 15 ohm systems are available. There is a special pre-amp for low output pick-ups and escutcheon panels to suit the arrangement you choose. The tuner is styled to match.

You can do so much with MARTIN kits. The system of using pre-fabricated transistorised units which can be interlinked in a variety of ways enables you to assemble the combination of your choice and then extend it unit by unit until you possess a full stereo gramophone and radio assembly. When new units are produced, they can be added to existing equipment very easily with the advantage that you can continue to use equipment you already have,

so that your installation is always up to date. Most important of all is the power and quality which MARTIN Audiokits give you. Their sturdy construction assures compactness without sacrifice to quality or efficiency. They offer excellent value, are very easily installed and will give years of unflinching service. That is why people prefer MARTIN—it's simple to instal. good to listen to, and looks completely professional.

AMPLIFIER SYSTEMS • TUNERS • RECORDERS

- 5-stage input Selector £2.76
- Pre-amp/vol. control £1.17.6
- Pre-amp/tone controls £3.2.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0
- FM Tuner £12.17.6

MARTIN ELECTRONICS

154 High Street, Brentford, Middlesex

Please send Recordakit/F.M. Tuner/Audiokit Hi-Fi Leaflets. (Strike out items not wanted)

Name

Address

PW67

From Radio and Hi-Fi Stockists

Trade enquiries invited

MARTIN ELECTRONICS LTD. 154/5 HIGH STREET, BRENTFORD, MIDDLESEX. ISLeworth 1161/2

practically wireless

commentary by **HENRY**

THE price of newsprint is going up. Space must not be wasted. It is Henry's duty to utilise this column in a forthright, serious, progressive way. This was underlined by a letter on Page 821 of the March PRACTICAL WIRELESS. I.N.R.W. Newport accused the Editor of wasting space in comment; space that could have been better used for constructional articles. The sting of Mr. Newport's letter came in the tail. "*A far better policy would be to refuse advertised non-convertible 27 Mc/s walkie-talkie spreads unless boldly indicated as such.*"

The key-word is *boldly*. Our correspondent expects the advertisers to proclaim: "Buy it NOW—but use it NEVER." He may be right. It is scandalous that potentially illegal apparatus should be blatantly peddled for the innocent reader to be corrupted. What about those radio tuners for the front end of your hi-fi kit, feeding a tape recorder aren't they just a little naughty? Even the impeccable Mr. Molloy released the secret (Page 839, same issue) that the phone output of the R1155 was suitable to load a tape recorder. Shame on him!

We must draw the Editor's attention to another article that appeared in the same issue. A top-band transceiver is described by T. Simon.

Here the felony is compounded by an attractive cover picture

that even includes communications in foreign languages, aye, whisper it, from behind the Iron Curtain. What a gift to some potential George Blake.

The article bristles with law-breaking possibilities. In the first place, for only £15, our innocent is tempted to transmit. Or is it simply that the Editor is fanning another controversy on ham-licences and the anachronistic need to learn the Morse Code?

Let us look a little deeper at the article. Near the bottom of column 1, Mr. Simon tells us that in his area "... there is a strong break-through from the BBC at Brookmans Park (908 kc/s 2nd harmonic)". Who knows what else may break through, even using a well-peaked tank circuit. We may find ourselves clandestinely eavesdropping on the police, fire service, ambulances, even taxis. In a south-coast town even the dust-carts have two-way radio.

Further on we see two stages of modulation defended with the statement "... the QSO can be conducted in a confidential whisper with the mike gain half-way up." We have roamed the amateur bands and heard a few of those confidential whispers, thank you. It's a good job Mrs. Whitehead is only bothered about professional TV. What a fine hunting ground the ham-bands would provide for someone with a prurient mind.

True, Mr. Simon cares about

v.f.o. swishers and does his best to eliminate the beat note. He also uses frequency modulation the better to avoid t.v.i. Perhaps Mr. Newport would wonder darkly whether he has some ulterior motive — perhaps the family has demanded uninterrupted Coronation Street.

Yet the constructor still has to put 100pF across the mike to avoid BBC re-radiation. Tape recorder owners will recognise the phenomenon. Free radio programmes, lightly veiled in an innocent text. It's anarchy, that's what!

But Mr. N is more concerned with the advertisers. He worries about Swish not washing whiter than white noise. He forgets that we are conditioned to the blandishments of the adman and don't believe half of what we read, hear and see. Has he thought of the awful possibilities — the unsuspecting reader who buys and builds a kit that doesn't work, then offends the local litter-laws by throwing it out of the window? Or the student who chucks up his butcher's apron for a correspondence course and electrocutes himself with a 9V battery.

Somewhere a heart beats more strongly because Messrs. Super-Fi have advertised their home video tape link. What a prospect this conjures up! All your favourite programmes canned while you are out shopping, for a paltry ten quid an hour—or, as the advertisers say piously, much less when the demand steps up. To follow the argument through, we ought to ask for video tapes to apply for some kind of licence.

Henry stands aghast. The thought of such electronic sins being committed all round appalls him. Perhaps it is as well the price of newsprint is rising—there will be less room per issue for policy-bending letters.




The dust carts have two-way radios

4-CHANNEL

mixer/amplifier

F. L. THURSTON

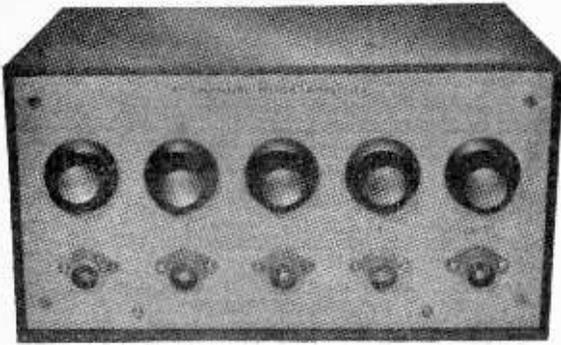

A DESIRABLE item in any audio enthusiast's list of "accessories" is a good quality mixer, to enable a number of inputs to be added together to give a single, complex, output signal. This four-channel mixer contains a 500mW power amplifier and makes the device very versatile and suitable for use either on its own as a multi-input, general purpose, power amplifier, or as a fairly conventional mixer capable of driving a speaker or a low impedance feeder line. Semiconductors are used in this high gain unit, which features good stability and quality with low noise and low inter-channel interaction.

BASIC DESIGN PRINCIPLES

A conventional "mixer" consists of some kind of combining circuit, followed by an amplifier which compensates for any attenuation which takes place in the adding process. In the unit we are considering here, an additional power amplifier "block" is provided so that the simplified block diagram of our unit is as shown in Fig. 1a.

Dealing first with the "mixer" part of the unit, a passive adder type is used, and is shown in basic form in Fig. 1b. Here, only two channels are shown; each input is applied across a variable resistor and a proportion of the input signal is tapped off at the slider and applied to a series circuit comprising either R1/R3 or R2/R3. Thus, the two input currents flow in the common resistor, R3. The output voltage developed across this resistor is proportional to the sum of the input signals. R3 may be made common to as many input signals as are required.

When this basic "mixer" circuit is redrawn as in Fig. 1c, it can be seen to be nothing more than a couple of potential divider circuits. The approximate values of input impedance, input-to-output attenuation, and inter-channel interaction can be established at a glance. Note that "worst case" values are shown, with VR1 and VR2 set for maximum sensitivity and with input 2 open circuit. In this case, the input impedance to input 1 is approximately 55k Ω , and, if 1 volt is applied, the attenuation will be such that 55mV will appear at the output, and inter-channel interaction will be such that 25mV will appear across input 2. Input impedance will vary with the setting of VR1, and will be at maximum (100k Ω) when VR1 is set for minimum sensitivity. The attenuation factor between VR1 slider and the output will be virtually constant.

The most important factor, as far as quality is

concerned, is the inter-channel interaction factor, as this will cause distortion between the inputs if it is high. In practice, this factor will depend on the setting of VR2 and the source impedance of the signal connected to input 2. Typically, when 1 volt is applied to input 1 and zero input is applied across input 2, from a 1k Ω source, and both VR1 and VR2 are set for maximum sensitivity, only 0.22mV will appear across input 2 and interaction


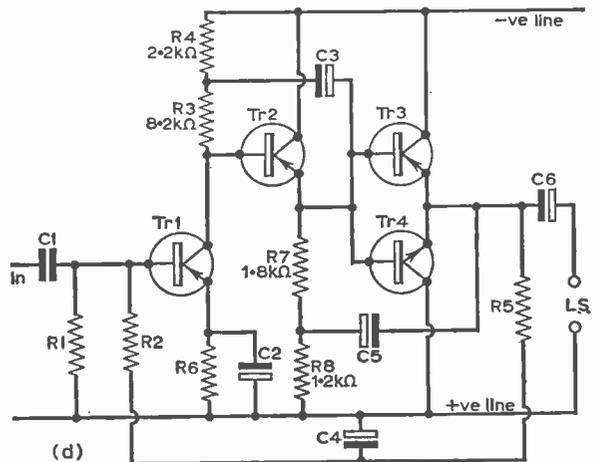
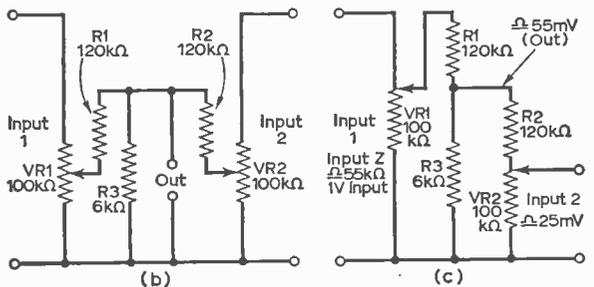


Fig. 1: 'a' block schematic of the mixer/amplifier; 'b' basic two-channel mixer; 'c' basic mixer re-drawn to show potential divider effect, with worst-case values; 'd' basic circuit of the amplifier section of the unit.

NEW MODEL 500. 30,000 o.p.v. With overload protection, mirror scale. 0/5/1/250/1,000/5,000V. A.C. 0/2.5/10/25/100/250/500/1,000V. D.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/50K/6 Meg./60. Meg Ω. £8/17/6. Post Paid.

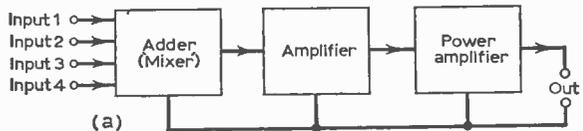PROFESSIONAL 20,000 o.p.v. LAB. TYPE MULTITESTER



With automatic overload protection, mirror scale. Ranges: 1/10/50/250/500/1,000 volts, D.C. and A.C. 0-500 μA, 10 mA, 250 mA. Current: 0/20 K, 200 K, 2 megohm. Decibels -20 to +20db. £5/10/0. P. & P. 2/6.

TE-900 20,000 VOLT GIANT MULTIMETER



6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000V. A.C. 0/2.5/12.5/10/50/250/1,000/5,000V. D.C. 0/50BA/110/100/500 mA 10 amp. D.C. 0/2K/20K/20 Megohm. £12/19/6. P. & P. 5/-.

MODEL ZQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A, B and Ic. Equally adjustable for checking diodes, etc. Spec. S: 0-7-0-9967, B: 5-200, Ic: 0-50 microamps, 0-5 mA. Resistance for diode 200Ω - 1 Meg. Supplied complete with instructions, battery and leads. £8/19/6. P. & P. 2/6.



*** TRANSISTORISED FM TUNER ***



6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6in. x 4in. x 3 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £8/19/6. P. & P. 2/6.

NOMBREX TRANSISTORISED EQUIPMENT. All Post Paid with Battery



Transistorised Audio Generator 10-100,000 c/s. Sine or square wave. £18/15/0. Transistorised Signal Generator 150 kc/s. 230 Mc/s. £10/10/0. Transistorised resistance capacity bridge 1Ω. 100 Meg. Ω. 1 pf. 100μF. £9. Transistorised Induction bridge 1μH-100H £18. Mains operated Transistor power supply unit, output 1-15 v. up to 100 mA. £8/10/0.

TE-65 VALVE VOLTMETER



High quality instrument with 28 ranges. D.C. volts 1.5-1,500 v. A.C. volts 1.5-1,500 v. Resistance up to 1,000 megohms. 220/240 v. A.C. operation. Complete with probes. P. & P. £15. P. P. 6/-. Additional Probes available: B.F. 35/-; H.V. 42/6.

TYPE 13A DOUBLE BEAM OSCILLOSCOPE BARGAIN!



A high quality instrument, offered at a fraction of original cost. Timebase 2 c/s-750 kc/s. Separate Y1 and Y2 amplifiers up to 5-5 Mc/s. Built-in callibrators at 100 kc/s and 1 Mc. Operation for 115/250v. A.C. Available in excellent condition, fully tested and checked. £22/10/0 Carr. 30/-

TE-20RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator. Operation 200/240 v. A.C. Brand new with instructions £12/10/0. P. & P. 7/6. S.A.E. for details.

LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 P.F. - 2,000 MFD. - 2 ohms 200 megohms. Also checks impedance turns ratio, insulation, 200/250 v. A.C. Brand New £15. Carr. 7/6.



TE22 SINE SQUARE WAVE AUDIO GENERATORS



Sine: 20 cps to 200 kc/s on 4 bands. Square: 20 cps to 30 kc/s. Output impedance 5,000 ohms, 200/250 v. A.C. Supplied brand new and guaranteed with instruction manual and leads, £15. Carr. 7/6.

ARF-100 COMBINED AF-RF SIGNAL GENERATOR



AF SINE WAVE 20 - 200,000 cps. Square wave 20-30,000 cps. O/P. HIGH IMP. 21 v. P.P. 600 Ω 2-8 v. P.P. TF. 100 kc/s-300 Mc/s.

Variable R.F. attenuation Int/Ext. Modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240 v. A.C. £27/10/0. Carr. 7/6.

F.M. WIRELESS MICROPHONE




94-104 Mc/s. Transistorised. Operates from 9 v. battery. Complete with additional secret-typing microphone. List £12.10.0. ONLY £7.10.0. P. & P. 2/6. These cannot be operated in U.K.

SILICON RECTIFIERS

200 v. P.I.V. 200mA.	2/8
200 v. P.I.V. 6 amp.	5/6
400 v. P.I.V. 3 amp.	7/8
1,000 v. P.I.V. 600 mA.	6/8
800 v. P.I.V. 500mA.	5/8
800 v. P.I.V. 5 amp.	7/6
400 v. P.I.V. 600mA.	5/8
70 v. P.I.V. 1 amp.	3/8
150 v. P.I.V. 165mA.	1/-
150 v. P.I.V. 25 amp.	19/6
700 v. P.I.V. 100 amp.	49/6
400 v. P.I.V. 3 amp. (S.C.R.)	10/-
100 v. P.I.V. 5 amp. (S.C.R.)	15/8
200 v. P.I.V. 5 amp. (S.C.R.)	15/8
400 v. P.I.V. 5 amp. (S.C.R.)	17/8

Discounts for quantities. Post extra

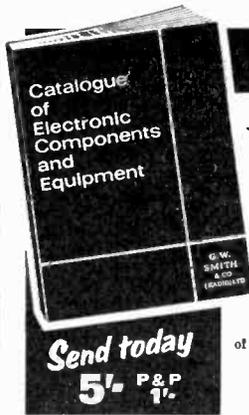

CATALOGUE

- ★ ELECTRONIC COMPONENTS
- ★ TEST EQUIPMENT
- ★ COMMUNICATIONS EQUIPMENT
- ★ HI-FI EQUIPMENT

We are proud to introduce our first comprehensive catalogue of Electronic Components and equipment. Over 150 pages fully illustrated, listing thousands of items many at bargain prices. Free discount coupons with every catalogue. Everyone in electronics should have a copy.

Send today 5/- P&P 1/-

CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type MK, 382, 1 21/52in. square fronts.




100-0-100μA	27/6	200mA	28/6	100V D.C.	22/6
500-0-500μA	22/6	300mA	22/6	150V D.C.	22/6
1-0-1mA	22/6	500mA	22/6	300V D.C.	22/6
1mA	22/6	750mA	22/6	500V D.C.	22/6
2mA	22/6	1A D.C.	22/6	750V D.C.	22/6
5mA	22/6	2A D.C.	22/6	15V A.C.	22/6
10mA	22/6	5A D.C.	22/6	50V A.C.	22/6
20mA	22/6	3V D.C.	22/6	150V A.C.	22/6
100μA	29/6	50mA	22/6	10V D.C.	22/6
100μA	27/6	100mA	22/6	30V D.C.	22/6
500μA	25/-	150mA	22/6	50V D.C.	22/6
50-0-50μA	29/6	50V D.C.	22/6	5V Meter 1mA	29/6

POST EXTRA. Larger sizes available - send for lists.

R209 MK. II COMMUNICATION RECEIVER

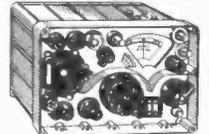11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s. on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O. Aerial trimmer, internal speaker and 12 v. D.C. internal power supply. Supplied in excellent condition, fully tested and checked. £15. Carr. 20/-.



LAFAYETTE HA-63 COMMUNICATION RECEIVER




Outstanding value. High-class 4 band receiver covering 550kc/s-31 Mc/s. Seven valves plus rectifier, RF stage, illuminated 'S' meter, 1.5μV sensitivity. Electrical bandspread on 80/40/20/15 and 10 metre bands. Slide rule dial, aerial trimmer. B.F.O., ANL, Output for phones or speaker. 115/220/240V. A.C. Brand new, guaranteed, with manual. 24 Gns. Carr. 10/-

LAFAYETTE KT-340 COMMUNICATION RECEIVER SEMI-KIT

Build this wonderful receiver and save pounds. Supplied semi completed, main components ready mounted, R.F. section already wired and aligned. Full and precise instructions supplied. Specifications: 8 valves - rectifier, 4 bands covering 550 kc/s-30 Mc/s. Incorporates 1 B.F. and 2 I.F. stages, 'Q' multiplier, B.F.O., A.N.L., 'S' meter, bandspread, aerial trimmer etc. Operation 115/230 V. A.C. Price 25 Gns. Carr. 10/-.




HAM-1, 4 BAND COMMUNICATION RECEIVER

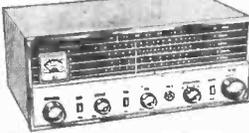

4 wavebands covering 535 kc/s to 30 Mc/s. 5 valve superhet circuit. Incorporates 8 meter B.F.O., BANDSPREAD TUNING, BUILT-IN 4in. SPEAKER, FERRITE AERIAL AND EXTERNAL TELESCOPIC AERIAL. Operation 220/240 v. A.C. Supplied brand new with handbook. £18.16.0. Carr. 10/-.

NEW LAFAYETTE MODEL HA-700 AM/CW/SSB AMATEUR COMMUNICATION RECEIVER

8 valves, 5 bands incorporating 2 MECHANICAL-FILTERS for exceptional selectivity and sensitivity. Frequency coverage on 5 bands 150-400 kc/s., 550-1,600 kc/s., 1.6-4.0 Mc/s., 4.5-14.5 Mc/s. 10.5-30 Mc/s. Circuit incorporates R.F. stage, aerial trimmer, noise limiter, B.F.O., product detector, electrical bandspread, S meter, slide rule dial. Output for phones, low to 2K Ω or speaker 4 or 8 ohms. Operation 220/240 volt A.C. Size 7 1/2in. x 15 1/2in. x 10in. Supplied brand new and guaranteed with handbook. 38 GNS. Carr. 10/- S.A.E. for leaflet.

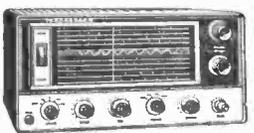

G.W. SMITH & CO (RADIO) LIMITED
 Phone: GERRARD 8204/9155
 Cables: SMITHEX LESQUARE
 3-34 LISLE STREET, LONDON, W.C.2



Want to train as a technician in aircraft or electronics?

Consider the Army.

If you're between 17 and 25 you can join the Army as a trainee technician . . . and take an 18-month technical training course. Soon you'll be up to City and Guilds standard. Six months after you've successfully completed your course you will be promoted to Corporal. From then on, it's up to you!

Today's Army has some of the most advanced equipment in the world: radio transmitters, closed-circuit TV, gunfire control equipment, radio transceivers, helicopters. You'll be training with them from the start. If you'd care to get on with it earlier in life, you can join as a Junior Entrant and start training as a technician or tradesman at 15.

Good pay!

This year every soldier in the Army is better off. Trainee Technicians get £477 a year from age 17—and all your food and lodgings are free. At the end of 18 months, your pay will go up automatically to £714; at the end of two years, to £805! From there, you'll be given every chance to work for promotion and *still* better pay.

WANT TO KNOW MORE? SEND OFF THE COUPON TODAY!

TO: ARMY CAREERS MP6(A), LANSDOWNE HOUSE, LONDON W.1
Please send me full details of how to become a Technician

NAME

ADDRESS

TOWN

COUNTY

DATE OF BIRTH

(You must be resident in the UK)

ELECTROLYTIC CONDENSERS

.25µF .. 3 volt	5µF .. 50 volt	32µF .. 25 volt
1µF .. 10 volt	5µF .. 70 volt	40µF .. 3 volt
1µF .. 15 volt	6µF .. 12 volt	40µF .. 6.4 volt
1µF .. 40 volt	6µF .. 15 volt	50µF .. 6 volt
1µF .. 50 volt	6.4µF .. 40 volt	50µF .. 9 volt
1µF .. 350 volt	8µF .. 3 volt	64µF .. 2.5 volt
1.25µF .. 16 volt	8µF .. 6 volt	64µF .. 9 volt
2µF .. 3 volt	8µF .. 50 volt	64µF .. 10 volt
2µF .. 9 volt	10µF .. 6 volt	64µF .. 16 volt
2µF .. 10 volt	10µF .. 10 volt	64µF .. 40 volt
2µF .. 15 volt	10µF .. 12 volt	100µF .. 3 volt
2µF .. 70 volt	10µF .. 25 volt	100µF .. 6 volt
2µF .. 150 volt	12.5µF .. 4 volt	100µF .. 10 volt
2.5µF .. 16 volt	12.5µF .. 40 volt	100µF .. 12 volt
2.5µF .. 25 volt	16µF .. 16 volt	100µF .. 15 volt
3µF .. 3 volt	16µF .. 30 volt	150µF .. 12 volt
3µF .. 12 volt	16µF .. 150 volt	150µF .. 25 volt
3µF .. 25 volt	20µF .. 9 volt	200µF .. 3 volt
3.2µF .. 6 volt	20µF .. 6 volt	200µF .. 4 volt
3.2µF .. 6.4 volt	20µF .. 9 volt	200µF .. 16 volt
3.2µF .. 40 volt	20µF .. 16 volt	250µF .. 2.5 volt
3.2µF .. 64 volt	25µF .. 6 volt	250µF .. 9 volt
4µF .. 4 volt	25µF .. 12 volt	250µF .. 15 volt
4µF .. 12 volt	25µF .. 25 volt	320µF .. 2.5 volt
4µF .. 25 volt	25µF .. 30 volt	500µF .. 4 volt
4µF .. 100 volt	30µF .. 6 volt	500µF .. 25 volt
5µF .. 6 volt	30µF .. 10 volt	640µF .. 2.5 volt
5µF .. 25 volt	32µF .. 15 volt	750µF .. 18 volt
	32µF .. 1.5 volt	1000µF .. 6 volt

All at 1/- each; 9/- per dozen. Mixed packet (four selection) 20 for 10/- 200/100µF 275 volt; 200/200µF 275 volt; 125/300/50µF 275 volt, 5/- each or 3 for 10/-.

PAPER CONDENSERS

.001µF .. 500 volt	.02µF .. 600 A C	.25µF .. 350 volt
.001µF .. 1000 volt	.02µF .. 350 volt	.5µF .. 150 volt
.002µF .. 500 volt	.1µF .. 350 volt	.5µF .. 350 volt
.005µF .. 750 volt	.1µF .. 750 volt	.5µF .. 500 volt

All at 15/- per 100 or mixed packets (four selection) 50 for 10/-.
VERY SPECIAL VALUE! SILVER MICA, POLYSTYRENE, CERAMIC CONDENSERS
Very well assorted. Mixed types and values. 10/- per 100.

RESISTORS

Very small 1/2 watt, 5% long leads, ideal for transistor work .. 10/- for 50
1/2 watt assorted values including printed circuit types .. 10/- for 100
55/- per 1000
1/2 watt to 3 watt mixed values and types .. 10/- for 100
55/- per 1000

To clear 10 meg. 1/4 watt resistors. £1 per 1,000.

TRANSISTORS

AFZ 12 screened V.H.F., oscillator transistors, 5/- each. OC44, OC45 R.F. Transistors, 4/- each. OC 8D 4/- each. OC 71 equivalent 1/- each, £3 per 100. Switching Transistors ASY 22 (P.N.P.) or I.B.M. (N.P.N.) 6 for 10/- Car radio type Output Transistors type NKT 405 10/- each.

TELEVISION VALVES BRAND NEW AND BOXED

PCF80 .. 7/6	PCC84 .. 6/6	PCL53 .. 9/-
PCL84 .. 7/6	EY86 .. 6/-	PCL55 .. 7/6
PL36 .. 9/-	PCCR9 .. 9/-	ECC82 .. 6/6
ECL80 .. 6/6	PCL89 .. 7/6	PY33 .. 9/-
PL81 .. 7/6	PY61 .. 6/-	

COMPUTER DIODES. Make excellent detectors, also suitable for keying electronic organs. 1/- each or 20 for 10/-.

BT100 TYPE TELEVISION H.T. RECTIFIERS. SPECIAL PRICE 5/- each, 30/- doz.

ORP 12 light sensitive resistors 9/- each.

TRANSISTOR BATTERY ELIMINATORS—same size as PP 30/-; PP 6 20/-.

BATTERY CHARGERS, with meter and fuse. 4 amp. 6/12 volt 55/- each.

SOLO MODEL 615 81mm Pencil-bit Soldering Irons 25/- each.

WELLER DUAL-HEAT SOLDERING GUN, 57/6.

NUTS, SCREWS AND WASHERS, very useful assorted packs, 6/- each.

WALKIE-TALKIES (not for use in U.K.) 27.10.0. pair.

MAGNETIC RECORDING TAPE. British made, fully guaranteed.

Standard play. 3in., 150ft., 3/6; 5in., 600ft., 10/6; 5 1/2in., 900ft., 13/6; 7in., 1,200ft., 16/3
Long Play. 3in., 235ft., 4/-; 5in., 900ft., 12/9; 5 1/2in., 1,200ft., 15/9; 7in., 1,800ft., 21/6
Double Play. 3in., 400ft., 6/8; 5in., 1,300ft., 20/-; 5 1/2in., 1,800ft., 23/-; 7in., 2,400ft., 34/-; 2 1/2in., 300ft., 6/9.
Triple Play Polyester. 3in., 600ft., 12/6; 4in., 900ft., 16/6.

SIGNAL INJECTOR. Parts and circuit to make 10/- only.

SIGNAL TRACER. Parts and circuit to make 10/- only.

MOTOR CAR REV. COUNTER (see 1in. meter). Parts and circuit to make 10/- only.

TRANSISTORS, COMPONENTS AND CIRCUIT. To convert 1mA meter to 0 to 10 Meg. ohm meter 10/-.

TRANSISTORISED RUMBLE AND SCRATCH FILTER (for improving reproduction of old records) all components and circuit 30/-.

SINGLAI. All products in stock including latest version of MICRO-6. World's smallest radio, and only 59/6.

NEEDLES FOR RECORD PLAYERS. HALF PRICES. All types below at 3/6 each.

TC8LP; GC2LP; GC8LP; BF40LP; GP67LP; GP37; GP69; TC8 Stereo LP; Studio OLP. CARTRIDGES, Sonotone Mono 10/-, Acos 15/-, Acos Stereo Sapphire 12/6. Diamond 17/6. All complete with needles!

LAPEL MICROPHONES. Magnetic or Crystal 10/- each.

TAPE RECORDER MICROPHONES. Fantastic value at 12/- each.

ACOS MIC. 45 30/-, Many other both crystal and dynamic in stock.

LEAD CONNECTING WIRE. 10yds 1/-; 100yds 7/6; 500yds 25/-; 1,000yds 40/-.

LOUDSPEAKERS. 12in. Richard Allen 37/6. 12in. Bakers Guitar 25.5.0.

30-, 4in., 5in. and 5 x 3in. all at 10/- each. 8 x 2 1/2in. 12/6. 2in. 8.0m 7/6.

EARPIECES Magnetic or Crystal 5/- each.

VEROBOARD.

2 1/2in. x 5in. .. 3/11 Terminal Pins .. 50 for 3/-

2 1/2in. x 3 1/2in. .. 3/5 Spot Face Cutter .. 7/6

3 1/2in. x 5in. .. 5/6 Pin Insert Tool .. 9/6

3 1/2in. x 3 1/2in. .. 3/11 Special Offer. Cutter & 5 boards 2 1/2in. x 1in. 9/9

ELECTRONICS DEALER 600 PAGE CATALOGUE 10/6.

ORDERS BY POST TO

G. F. MILWARD

17 PEEL CLOSE, DRAYTON BASSETT, STAFFS.

PLEASE INCLUDE POSTAGE COSTS

For customers in the Birmingham area, goods may be obtained from ROCK EXCHANGES, 281 ALUM ROCK ROAD, BIRMINGHAM 8.

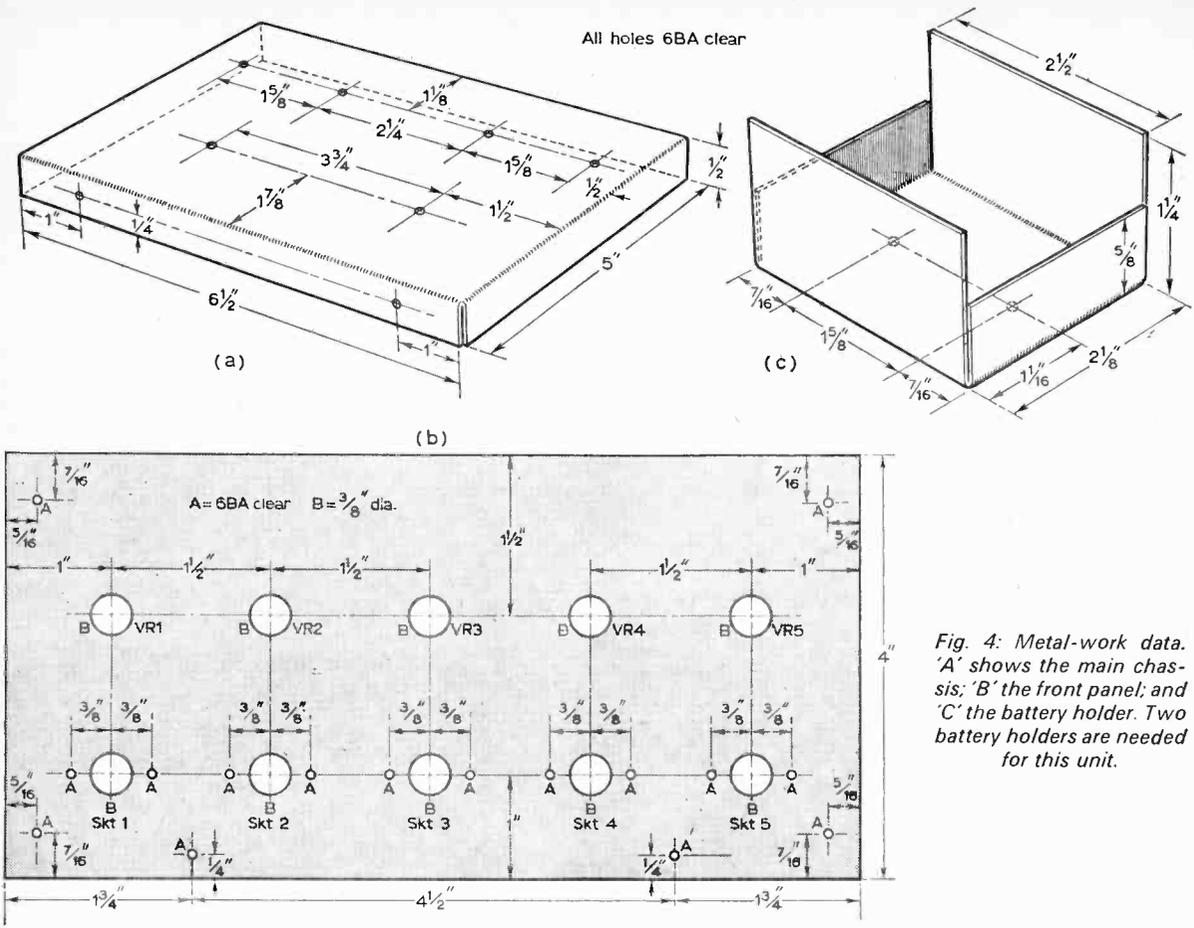


Fig. 4: Metal-work data. 'A' shows the main chassis; 'B' the front panel; and 'C' the battery holder. Two battery holders are needed for this unit.

value is set at about 10kΩ. It is possible to increase the effective value of the collector load without changing its real or d.c. value; referring to Fig. 1d, the signal at the emitter of Tr2 is of the same form and phase as the signal at Tr1 collector, but these two signals are effectively isolated from one another by the impedance transformation action of the emitter follower. In the diagram, Tr1 collector load is split into two parts, R3 and R4, and the signal appearing at Tr2 emitter is fed via C3 to the R3-R4 junction. Thus, when an input signal is applied to Tr1, similar a.c. signals appear at both ends of R3 and very little signal current flows in this resistor, which reacts as a high impedance, even though its resistive value is fairly low. In practice, the effective value of R3 may be increased to ten times its real value, giving consequent high gain. This technique of increasing the effective value of a resistance is known as "Bootstrapping".

The output signal at Tr2 emitter is direct coupled to the bases of Tr3 and Tr4, which are wired as a compound connected p-n-p/n-p-n emitter follower pair, giving unity voltage gain but a very low (virtually earth) output impedance, which is fed to the external speaker via C6. As in the case of Tr2, the Tr3-Tr4 emitter followers give an output that is of the same phase and form as their input signal (from Tr2 emitter), but the two signals are effectively isolated from one another by impedance transformation; the output signal from Tr3-Tr4 is

therefore used to Bootstrap the R7-R8 emitter load of Tr2, and to increase the effective input impedance of Tr2 and indirectly further increase the effective value of the collector load of Tr1.


The input impedance of an emitter follower is given (approximately) as the emitter load, R_L , times the β of the transistor, so that, in Fig. 1d, the effective value of the emitter load of Tr2 is dictated by the β s of Tr3 and Tr4 and the impedance of the speaker. The effective value of Tr1 collector load is dictated by this value times the β of Tr2. Since all impedance levels are interdependent throughout the circuit, the design automatically gives an optimum performance with whatever transistors are used.

The output transistors can be given a very high β by replacing the two individual transistors by Darlington or Super-Alpha-Pair connected transistors, in which case the effective collector load of Tr1 becomes so high that, on the prototype, voltage gains of 500 to 1,000 times are obtained when using a 15Ω speaker.

Note that direct coupling is used throughout the amplifier, and that the base-bias to Tr1 is obtained from the Tr3-Tr4 output via R1, R2, R5, so that a d.c. negative feedback loop is set up which fully stabilises the working points of all transistors used in the circuit. Also note that all signals from Tr1 collector onwards are in anti-phase with the input signal, so that any stray feedback will be degenera-

LOOK!

PRACTICAL!
VISUAL!
EXCITING!

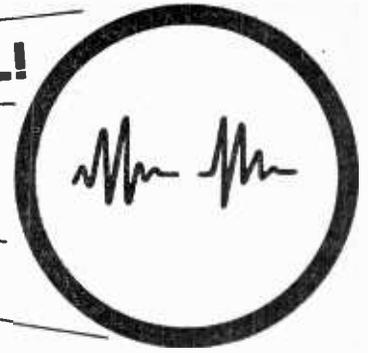


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing . . .


1 ▶ OWN and HANDLE a

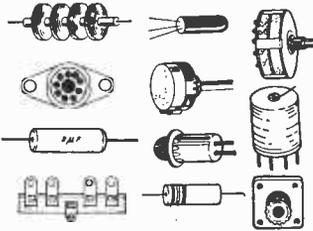complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 ▶ BUILD and USE

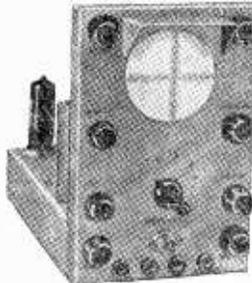a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 ▶ READ and DRAW and

UNDERSTAND
CIRCUIT DIAGRAMS

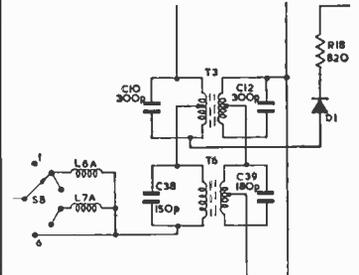

4 ▶ CARRY OUT OVER **40** EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
 - TRANSISTOR EXPERIMENTS
 - AMPLIFIERS
 - OSCILLATORS
 - SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
 - COMPUTER CIRCUIT
 - BASIC RADIO RECEIVER
 - ELECTRONIC SWITCH
 - SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
 - D.C. EXPERIMENTS
 - SIMPLE COUNTER
 - TIME DELAY CIRCUIT
 - SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME BLOCK CAPS


ADDRESS PLEASE PW6

BARGAIN OPPORTUNITIES



EXCLUSIVE TAPE OFFER

FREE LIBRARY WALLET WITH EVERY REEL

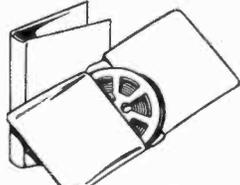

With each reel of this tape by an internationally famous manufacturer we give you a beautifully made wallet strongly made in simulated leather with space for a reel of tape each side. This is professional quality full frequency tape with metallised leader/stop foils. These library wallets solve once and for all the problems of storing tapes efficiently and tidily.

7" reel 1800' with wallet **22/6** 5" reel, 900' with wallet **12/6** 5 1/2" reel, 1200' with wallet **17/6**
p. & p. 1/6 per reel

TAPE AMPLIFIER

WITH 4 VALVES, FRONT PANEL, WIRED & TESTED **£6.5.0**

OUTSTANDING T.R.S. VALVE—Absolutely complete, mains powered amplifier for B.S.R. T.D.2 Deck. Supplied wired and tested. Facilities include mike/radio/F.U. inputs, playback switching, superimpose, magic eye, tone and volume controls, 3 D outlet and monitoring. With front panel and knobs. **£6.5.0**. (P. & P. 7/6) Contemporary styled 2-tone cabinet **39/6** (P. & P. to take above. Size 14 x 13 1/2 x 7 1/2 in.) **Detachable lid.**

T.R.S. MULLARD STEREO 10-10

Valve amplifier by T.R.S. to exact Mullard spec. Complete with pre-amp and o/p transformers tapped for 3 and 15 D. Bass, treble, volume, balance controls. Outlet for H.T. and L.T. for tuner. Switching for mono, stereo and speaker phasing. Shrouded pre-amp. Complete with phoskas, sockets, escutcheon, knobs, etc. **£17.10.0** At present supplied wired and tested. **£19.10.0**. Kit version available very shortly. (C/P 10/-)

7 VALVE AM/FM RG CHASSIS

A superbly powerful high performance instrument for the keenest enthusiasts. Provides tuning on long, medium and F.M. wavebands. 3 wave-band L/M/FM Permeability tuning on F.M. Large clear dia. A.V.C. good neg. feedback. Magic eye. 3 w. output. A.C. 200/250V. Circuit diagrams available. Aligned, tested and ready for use (Carr. and ins. 7/6). B.A.E. brings full details. **£13.19.6**

'CIR-KIT' INSTANT CIRCUIT

Indispensable for constructor. Enable you to produce "printed circuits" quickly and cleanly. Kit No. 3, inc. baseboard processed copper strip and sheet as advertised. 15/-.

TYGAN FRET or Vynair speaker fabric, 12 x 12in. 2/-; 12 x 18in. 3/-; 12 x 24in. 4/-, etc.

BONDACOUST Speaker Cabinet Acoustic Wadding, approx. 1in. thick, 18in. wide, any length cut, 2/3 1/2-/- yd.

EXPANDED ANODIZED METAL. Attractive gilt finish. 1/2 x 1in. diamond mesh 4/6 sq. ft. Multiples of 6in. cut. Max. size 4 x 3ft. 47/6 plus carr.

ENAMELLED COPPER WIRE—2 oz. reels. 14 g.-20 g. 3/-; 22 g.-28 g. 3/6; 30 g. 34 g. 4/3; 36 g.-38 g. 4/6; 39 g.-40 g. 5/-, etc.

TINNED COPPER WIRE—16-22 g. 4/- 2 oz.

VEROBOARD—All standard sizes including 2 1/2 in. x 5 in. 3/8; 2 1/2 in. x 3 1/2 in. 3/8; 3 1/2 in. x 5 in. 5/8; 3 1/2 in. x 7 1/2 in. 12/6. All accessories and tools in stock.

OUR MAY LIST

Is brimful of bargains and hard-to-find components. Send 3d stamp for free copy.

WE ARE APPOINTED STOCKISTS FOR ALL SINCLAIR AND PEAK SOUND PRODUCTS

TRS RADIO COMPONENT SPECIALISTS

Established 1946

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

Tel.: THO 2188. Hours 9 a.m.—6 p.m. 1 p.m. Wednesdays
A few doors from Thornton Heath Stn. (S.R. Victoria section.)

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 185, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for 16/9. DAF96, DF96, DK96, DL96, 4 for 24/6

1A7GT 7/6	10F1 9/9	DH81 12/6	EF97 7/6	PEN44 6/9	UCH42 8/9
1H5GT 7/3	10F13 8/6	DK32 7/9	EF183 6/6	PEN396C16/-	UCH81 6/-
1N5GT 7/8	12A7 3/6	DK81 5/6	EF184 5/9	PEN383 9/6	UC182 7/-
1R5 5/6	12A7 4/9	DK96 6/6	EL33 8/6	PFL20013/6	UC183 8/9
1R4 4/9	12A7 4/9	DK96 6/6	EL41 8/6	PL36 9/-	UF41 8/-
1R5 3/9	12AX7 4/9	DL33 6/6	EL42 7/9	PL81 6/9	UF80 7/-
1T4 2/9	12K8GT 7/8	DL35 5/-	EL84 5/-	PL82 6/9	UF89 5/9
3A5 7/-	20F2 10/6	DL92 4/9	EL90 5/-	PL83 6/-	UL41 8/9
3Q4 7/6	20L1 14/-	DL94 5/6	EL95 5/-	PL84 6/3	UL44 20/-
3R4 4/9	20P1 9/-	DL96 6/-	EM90 5/9	PL600 13/6	UL84 6/-
3V4 5/6	20P3 9/-	DY86 5/9	EM81 6/9	PX25 7/9	UY21 8/9
5U4G 4/6	20P4 13/6	DY87 5/9	RM84 6/3	PY31 6/9	UY41 5/6
6V4G 7/9	25Z4GT11/6	EABC80 6/-	EM87 6/6	PY32 6/9	UY85 4/9
6Y3GT 5/-	30C15 10/6	EAP42 8/-	EY51 6/3	PY33 8/6	VP4B 11/-
5Z4G 7/-	30C17 11/6	EB41 4/-	EY88 6/6	PY80 5/3	VP1321 21/-
6/30L2 9/6	30C18 10/3	EB91 2/3	EZ40 6/3	PY81 5/3	W77 3/3
6AL5 2/3	30F5 9/9	EBC33 7/-	EZ41 6/6	PY82 5/9	Z77 3/6
6AM6 3/6	30FL1 10/9	EB041 8/-	EZ80 4/6	PY83 5/9	Transistors
6AQ5 4/9	30L15 11/-	EBP80 6/-	EZ81 4/9	PY88 7/3	AC107 10/-
6AT5 4/9	30L17 10/9	EBP89 5/9	EZ82 9/-	PY800 5/9	AC127 7/6
6BA6 4/6	30P4 11/6	ECC81 3/9	KT61 6/6	PY801 6/-	AD140 15/6
6BE6 4/3	30P12 9/9	ECC82 4/9	N18 5/9	R19 7/6	AF102 18/-
6BJ6 6/9	30P19 11/6	ECC83 7/-	N78 14/9	R20 12/9	AF115 8/6
6BW6 7/3	30P11 12/9	ECC84 6/3	PC86 8/6	U25 9/6	AF116 9/6
6F1 7/9	30P13 13/3	ECC85 5/9	PC88 8/9	U26 8/9	AF121 8/6
6F13 3/6	30P14 13/9	ECC80 7/6	PC87 5/9	U47 9/6	AF118 12/6
6F14 9/-	35L6GT 6/3	ECCF82 6/9	PC900 8/6	U49 9/6	AF124 9/6
6F23 9/9	35W4 4/6	ECCF86 2/-	PC84 5/6	U52 4/6	AF125 8/6
6K7G 1/6	35Z4GT 4/6	ECH36 6/-	PC88 8/9	U78 3/6	AF126 8/-
6K90 4/3	35Z2 5/9	ECH42 8/-	PC180 8/6	U91 10/-	AF127 8/-
6K8GT 7/6	185BT 20/-	ECH81 5/-	PCF80 6/6	U301 11/9	OC22 11/-
6L18 6/-	6063 12/6	ECH84 8/6	PCF82 6/-	U801 16/3	OC25 9/6
6V6G 3/6	AZ31 9/-	ECL80 6/-	PCF85 8/9	UAC80 5/9	OC26 6/9
6V8GT 6/6	B36 4/6	ECL82 6/3	PCF80 10/6	UAP42 7/9	OC44 4/3
6X4 3/6	B79 10/9	ECL86 7/9	PCF81 8/9	UB41 6/9	OC45 3/3
6X5GT 5/9	DAC32 7/3	EP89 5/9	PCF802 9/6	UBF80 6/-	OC71 3/6
7B6 10/9	DAF91 3/9	EF41 6/3	PCF805 9/9	UBF89 5/9	OC72 4/9
7B7 7/-	DAF96 6/-	EP80 4/9	PCF806 11/9	UL21 9/-	OC75 5/9
7C5 9/6	DOC90 7/-	EP85 5/-	PCL82 6/9	UC92 5/6	OC81 3/6
7C8 6/9	DF33 7/9	EP86 6/6	PCL83 8/9	UC84 7/9	OC81D 3/6
7H7 5/6	DF91 2/9	EP89 5/-	PCL84 7/-	UC85 9/6	OC89 5/9
7Y4 6/6	DF96 6/-	EP91 3/6	PCL85 8/3	UC80 8/3	OC82D 5/9
10C2 11/6	DH77 4/-	EP92 8/3	PCL86 8/6	UCH21 9/3	OC170 5/-

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. CRE 7441

Postage on 1 valve 6d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

BUILD YOUR CIRCUITS

ON VEROBOARD

— the Universal Wiring Board — obtainable from your local Retailer

Trade enquiries to:

NORMAN ROSE (ELECTRICAL) LTD.
8 ST. CHAD'S PLACE, GRAYS INN ROAD, LONDON, W.C.1

Technical enquiries to:

VERO ELECTRONICS LTD.,
Industrial Estate, Chandler's Ford, Hampshire

DICTIONARY OF RADIO AND TELEVISION

W. E. Pannett, A.M.I.E.E.

This fully illustrated dictionary provides extended definitions of thousands of specialised words, terms, and abbreviations in use today in radio and television. Includes elementary terms and basic concepts, fundamental electrical and electronic terms; units, electronic devices, including valves and transistors; radio-telegraphy and radio-telephony; monochrome and colour television; sound and high fidelity reproduction; transmission lines waveguides; communication satellites; aerials; transmitters, etc.

380 pages, 220 line illustrations. 36s.

from all booksellers or 38s. by post.

NEWNES, Tower House, Southampton Street, W.C.2

tive, rather than regenerative, and very good circuit stability is thus obtained. Having cleared up the main details of the circuit, the final version of the completed unit can now be considered.

HOW THE CIRCUIT WORKS

The full circuit diagram of the completed unit is shown in Fig. 2. Here, the four inputs are applied to the variable resistors, VR1—VR4 via the coaxial sockets Sk1—Sk4 and the blocking capacitors C1—C4, and the input currents are added in R5 via R1—R4. If the output of the mixer, taken from across R5, were fed directly to the input of a common emitter amplifier the comparatively high input capacitance of the transistor would be effectively in parallel with R5 and would result in an increase in attenuation at the higher frequencies. This is overcome by feeding the output of the mixer to the base of emitter follower Tr1, which has a very low input capacitance.

The signal tapped off from the slider of VR5, the volume control, is fed, via C7, to the base of the common emitter amplifier, Tr2, which has its collector load, R10—R11, "bootstrapped" from the emitter of Tr3 via C10. The amplified signal at the emitter of Tr3 is fed to the base of the p-n-p Darlington-connected emitter follower pair Tr4/Tr7 and to the base of the similarly connected n-p-n pair, Tr5/Tr6. Diodes D1 and D2, and VR6, in the emitter of Tr3, are used to apply a degree of temperature compensated base-bias to the output transistors and so minimise any cross-over distortion which might otherwise occur. The very low impedance output at the emitters of Tr6/Tr7 is fed to the output socket, Sk5, and thence on to the external speaker, via C13. Bootstrapping is applied from Tr6/Tr7 emitters to the R14—R15 emitter loads of Tr3 via C12. Overall d.c. negative feedback is achieved via R8, R9, R19; decoupled via C11.

A 12 volt battery supply is used, and an output power of well over 0.5 watt is available when feeding a 15Ω speaker.

CONSTRUCTION

For ease of construction, the major part of the circuitry is wired up on a small piece of Veroboard. Start construction by cutting the panel to size, as shown in Fig. 3a, and breaking the copper strips where indicated. Now drill the two small mounting holes, to clear 6BA screws, where shown, and cut back the copper around them to eliminate risk of short circuits when the panel is secured to the main chassis.

Now solder all components, shorting links, and leads in position on the panel as shown in Fig. 3b. Note that all components, other than R7 and R13, are mounted vertically. Insulated sleeving should be used where there is any danger of short circuits occurring. Before attempting to fit VR1 in place, reduce the width of the three mounting legs, with the aid of a small file, so that they fit easily in the holes in the Veroboard. Particular care should be taken to ensure that all electrolytic capacitors are connected with the polarities shown. Heat shunts should be used when soldering all semiconductors in place.

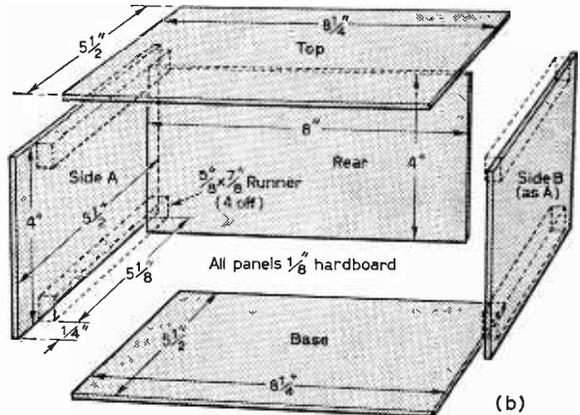
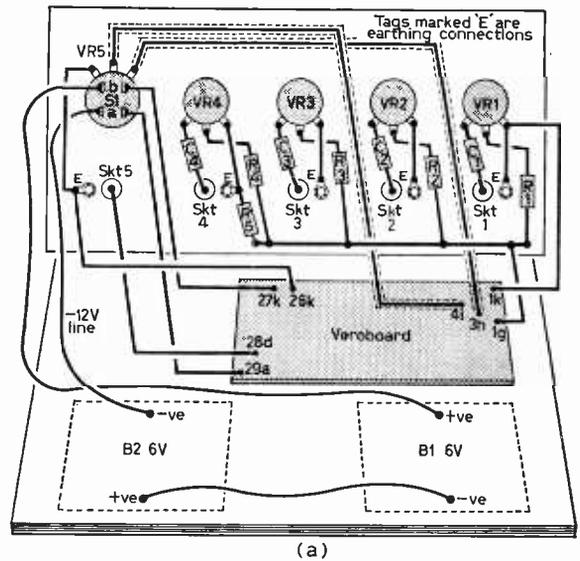


Fig. 5: 'a' shows the wiring details and 'b' cabinet details.

If preferred, D1 and D2 can be made from any scrap p-n-p germanium transistors, providing that the base-emitter junctions are intact, by cutting off the collector leads and soldering the resulting "diode" in place as shown.

When the assembly of the Veroboard panel is complete, double-check all wiring and make sure that no short circuits are occurring between the copper strips. If satisfactory, the circuit can now be given a functional check. Temporarily connect VR5 in place, set VR6 for minimum resistance, short the input to ground, and connect a 12 volt supply to the unit, taking care to monitor the supply current; the unit should draw about 8mA. Now connect a 15Ω speaker to the output, and check that there is no appreciable increase in mean current. If satisfactory, an input can be connected from a tuner, etc., and a functional check carried out; VR6 should be adjusted to give negligible cross-over distortion consistent with a low no-signal mean current, which should work out at about 10 to 12mA.

If the performance of the circuit is satisfactory, it should be run at fairly high volume for a few minutes, to make sure there is no tendency to thermal runaway. If there is any tendency to run-

away, the two output transistors (Tr6 and Tr7) should be fitted with heat sinks. Once these tests have been completed, the rest of the unit can be constructed.

Make up the main chassis, from light gauge aluminium, as shown in Fig. 4a, and cut and drill the front panel, from a medium gauge aluminium, as shown in Fig. 4b. If a battery supply is to be used, cut and drill and bend the two battery holders, from light gauge aluminium, as shown in Fig. 4c; the batteries are held in place by friction. Before assembling these components, carefully cover the outer face of the front panel with Fablon or a similar self-adhesive decorative plastic material; a material with a light wood-grained finish was used on the prototype. Cut away the surplus Fablon with a sharp knife. Now secure the five sockets, Sk1 to Sk5, and the five variable resistors, VR1 to VR5, in place on the front panel. Next, bolt the front panel to the main chassis, and wire up as shown in Fig. 5a. When wiring up is complete, secure the Veroboard panel to the main chassis by passing two 6BA screws through the Veroboard and the chassis, using the mounting holes provided, and interpose two small rubber grommets between the chassis and the panel to act as spacers/insulators.

The main construction can now be completed by bolting the two battery holders in place. The two batteries should now be fitted in place and the unit given a final and complete functional check. The cabinet can now be made up, as shown in Fig. 5b. This is an easy assembly to make, the sides, top, base, and rear being simply cut from hardboard and screwed or nailed to four short lengths of wood which hold the unit in a box shape. When the cabinet has been assembled, smooth off all rough spots with a file or sandpaper, and then cover the complete job with Fablon or a similar self-adhesive decorative plastic. Finally

★ components list

Resistors:

All $\frac{1}{2}$ watt, 10% carbon, except where otherwise stated.
 R1-R4 120k Ω , 5% hi-stab
 R5 8.2k Ω
 R6 47k Ω
 R7 56k Ω
 R8 10k Ω
 R9 22k Ω
 R10 2.2k Ω
 R11 8.2k Ω
 R12 1k Ω
 R13 1k Ω
 R14 1.2k Ω
 R15 1.2k Ω
 R16 470 Ω
 R17 470 Ω
 R18 470 Ω
 R19 33k Ω
 VR1-VR4 100k Ω variable
 VR5 5k Ω variable with built-in on/off switch (S1)
 RV6 500 Ω skeleton pre-set

Capacitors:

All sub-min. 15VW electrolytics
 C1 8 μ F
 C2 8 μ F
 C3 8 μ F
 C4 8 μ F
 C5 16 μ F
 C6 16 μ F
 C7 50 μ F
 C8 160 μ F
 C9 16 μ F
 C10 16 μ F
 C11 50 μ F
 C12 160 μ F
 C13 1000 μ F

Semiconductors:

Tr1 2G403 or NKT675
 Tr2 2G403 or NKT675
 Tr3 2G374 or NKT274
 Tr4 2G374 or NKT274
 Tr5 2N1304 or NKT713
 Tr6 2N1304 or 2N1306
 Tr7 2N1305 or 2N1307
 D1, D2 OA70
 (see text).

Miscellaneous:

Sk1-Sk5=Coaxial sockets. B1-B2=6 volt, type DT1 batteries. Veroboard, wire, sleeving, screened cable, nuts, screws, grommets, aluminium sheet, Fablon, etc. 15 ohm speaker.

secure the mixer/amplifier chassis in place with the aid of four small wood screws passed through the holes in the corners of the front panel, then mark the front panel with transfers or pressure sensitive lettering.

DUAL FUNCTION SIGNAL GENERATOR

—continued from page 119

in other types is the provision of an external socket to which the grid of the r.f. oscillator may be directly switched. Since the oscillator is of the two terminal type, oscillations may be set up in external coils without the use of tappings or separate feedback coils. What is perhaps more important is that

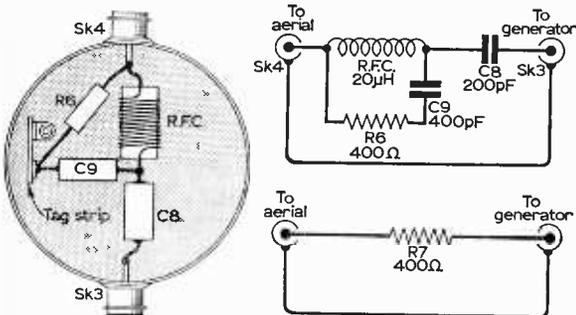


Fig. 5 (left): Layout of dummy aerial.

Fig. 6 (top right): Circuit of dummy aerial.

Fig. 7 (bottom right): Simplified dummy aerial.

oscillations may be set up in screened coils. Generally the presence of a screening can preclude the use of the more conventional grid dip oscillator technique. The author has found this facility to be of particular value when the resonance frequency of an unknown i.f. coil is required.

Let us suppose that an i.f. transformer in a receiver is suspect. The transformer is temporarily disconnected and one section connected via a short length of cable to the external socket of the generator. After switching the generator to this external coil, the signal emitted by the generator is picked up on a receiver. Let us assume that the i.f. transformer has a nominal resonant frequency of 470kc/s. A receiver set to the medium waveband will give a response in the neighbourhood of 940kc/s (319m), which is the second harmonic of 470kc/s. Although no account has been taken of the inevitable stray circuit capacitances, a response in this region is almost certain proof that at least one section of the transformer is functioning satisfactorily. The remaining section may be tested similarly. In the foregoing example it has of course been assumed that the i.f. transformer has its own built-in tuning capacitors. Further valuable uses to which the generator may be applied are coil matching and capacitor testing, details of which are given in the October 1964 issue of PRACTICAL WIRELESS.

FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 132-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio and Electronic Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Appointments Dept. and shows you how to qualify for five years promotion in one year.

SATISFACTION OR REFUND OF FEE

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £30 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

344B, Aldermaston Court, Aldermaston, Berks.

- Radio
- Television
- Electronics
- Electrical
- Mechanical
- Civil
- Production
- Automobile
- Aeronautical
- Plastics
- Building
- Draughtsmanship
- B.Sc.
- City & Guilds
- Gen. Cert. of Education
- etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc. A.M.I.E.R.E., City & Guilds Radio Amateur's Exam R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

This specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.



POST COUPON NOW!

Please send me your FREE 132-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)
 NAME
 ADDRESS

 SUBJECT OR EXAM THAT INTERESTS ME 344B

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

4-STATION INTERCOM

£6/9/6

Solve your communication problems with this new 4-Station Transistor Intercom (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Bureaux, Surgery, Schools, Hospitals, Office and Home. Operates on one 9v battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft. and other accessories. P. & P. 6/6.

INTERCOM/BABY ALARM

Usually ~~£6/6~~
Our Price ONLY **49/6**

Modernise business or home with this new two-way Portable Transistor Intercom. Consisting of Master and Sub, in strong plastic cabinets, with chromium stands. Designed as a two-way instant communication system. Call/talk/listen from Master to Sub and Sub to Master. Operates on one 9v battery. Complete with 60ft wire and battery. P. & P. 2/6.

Transistor TELEPHONE AMPLIFIER

Usually ~~£6/6~~
Our Price ONLY **55/-**

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. Indispensable in office/home. On/off switch. Volume Control. Operates on one 9v battery. P. & P. 2/6. Battery 2/6 extra. Full price refunded if returned in 7 days.

WEST LONDON DIRECT SUPPLIES (PW6)
169 KENSINGTON HIGH STREET, LONDON, W.8.

AMATEUR RADIO

G3NAP SPECIALISTS G3PQQ

STOCKISTS

Full range Lafayette Receivers, Partridge "Joystick" antennas and tuners. Eagle products. Electroniques manual and products. R.S.G.B. publications. Sommerkamp transmitters and receivers. Tokai transceivers (Amateur's licence required), Kw transmitters, receivers, etc. Contactor switchgear mobile equipment. Swan transceivers (Amateur's licence required), etc., etc. SAE Lists.

SWANCO PRODUCTS LTD.
247 HUMBER AVENUE
COVENTRY
Open all day Sat. Tel: COV. 22714

Laboratory Components

Resistors
1W 10% High Stab. Class 1 Low Noise 3/- per Doz.

Capacitors
Min. Electrolytics, Ass or Single value 9/- per Doz.
Polystyrene sub-min. 25V. 10% Ass. 6/- per Doz.

Transistors
1BC108 5/8 each
Matched Output Kit, OC81D+2 OC81 7/6 per set
Germanium. Ass. PNP, NPN, AF Types 10/6 per doz
Germanium Low Leakage, RF Types 12/- per doz.
Type 1020, PNP, Germanium, AF, 50mW 8/- per Doz.
Type 1021, PNP, Germanium, AF, 200mW 12/8 per Doz.
Type 1024, PNP, Low Leakage, RF.
4mc/s Typ. 17/6 per Doz.
OC44, OC45, OC70, OC71, ACY22, OC81D 2/3 each

Power Transistors
(OC26 7/6) (OC25 8/6) (OC30 10/-)

For complete list of Laboratory Components send S.A.E. to:
LABORATORY EQUIPMENT (ELEC)
38 Crawford St., London, W.1
All goods C.W.O. and P.P. 1/6

1967 EDITION RADIO AMATEUR HANDBOOK

40/- by ARRL Postage 4/-

BUILDING YOUR AMATEUR RADIO NOVICE STATION, by H. S. Pyle. 28/- Postage 1/-.

CAR RADIO SERVICING MADE EASY, by W. Lemons. 24/- Postage 1/-.

RADIO VALVE DATA, 8th edition. Compiled by "WW" 9/6. Postage 1/-.

WORLD RADIO TV HANDBOOK, 1967. 32/- Postage 1/-.

OUTLINE OF RADIO AND TELEVISION, by J. P. Hawker. 30/- Postage 2/-.

Inter GEC. TRANSISTOR MANUAL. 18/- Postage 2/-.

BASIC THEORY & APPLICATION OF TRANSISTORS. U.S. Dept Army. 10/- Postage 1/-.

RAPID SERVICING OF TRANSISTOR EQUIPMENT, by G. J. King. 30/- Postage 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
of British and American Technical Books

19-21 PRAED STREET
LONDON, W.2
Phone: PADdington 4185

new books



Books reviewed on this page are normally obtainable through any retail bookshop. In this instance, the information printed in heavy type should be quoted.

HOW TO LISTEN TO THE WORLD
Published by World Publications.
184 pages. 8½ x 5½in. Price 26s.

THIS is a new edition of a well established favourite. For those who have the previous edition there is little extra to be gained from purchasing this one. However, if you are a beginner and have had your appetite whetted by "PSE QSL" in the March PRACTICAL WIRELESS you will be helped considerably by this book.

Every aspect of DXing is covered both in theory and practice, and there are separate chapters on listening to various continents. For those with specialised interests there are chapters on learning languages by radio, listening to satellites and television DXing.

A good feature of the book is that every chapter is written by either a leading DXer or member of a short wave station's staff with the result that some good down-to-earth facts emerge. One slight disadvantage stems from this though in that inevitably there is a certain amount of overlap between chapters.

One disappointing feature is that the section How to write a report in Portuguese or Spanish is not in the latest edition. Even so a good buy for the beginner.—JMG.

HANDBOOK OF APPLIED MATHEMATICS
By E. E. Grazda, M. E. Jansson and W. R. Minrath.
Published by D. Van Nostrand Co. Ltd., 46 Victoria Street,
London, S.W.1. 1,119 pages. Size 7½ x 5½in. Price 80s.

THERE can be no doubt that the authors of this book have given value for money. In over a thousand pages they have covered a wide variety of fields. The problem is that if one recommends this book, to precisely whom can it fairly be offered. Starting with a general treatment of the various sections of mathematics the authors continue for the remaining 800-odd pages with the application of mathematics to various professions. For example, separate chapters are devoted to—Plumbing, Carpentry and Building, Brickwork, Print Shop, Accounting just to mention a few. For the layman it's a bit high up. The table headed "Coefficients of Transmission (U) of Pitched Roofs" might well prove too much for a layhandyman. On the other hand for the expert in a particular field, when he has read his chapter he will have another eight or nine hundred pages which are not applicable to his work.

As a person interested in mathematics as a whole, I found this book extremely interesting, and for those whose interests are parallel it would be a very useful addition to the bookshelf. Perhaps a better title would be "Applied Mathematician's Delight".—DLG.

NEWS FROM AROUND THE WORLD 1967
Published by O. Lund Johansen Ltd.
36 pages. 8½ x 6½in. Price 15s.

ONE of the fascinations of owning a short wave receiver is that when a new world trouble spot appears one can listen to the news from the spot. Alternatively you can hear the news from the various power centres and compare. To do this you need to know quickly when the country concerned has a news broadcast in a language you can understand and this is where this publication from the World Radio TV Handbook stable comes in with its listings of news broadcasts by both country and language.

For the DXer the book has a second use as an aid to the identification of stations. Whatever the language you can always tell the news broadcast. Reference to this book will show the stations transmitting news at the time concerned with the result that a process of elimination will enable the station to be identified.

One word of warning; although the times of news broadcasts are unlikely to vary greatly during the currency of this book the frequencies will. So don't pay too much attention to the frequency listings given.—JMG.

ABC'S OF ELECTRONIC TEST EQUIPMENT
By Donald A. Smith. Published by Foulsham-Sams Technical Books. 96 pages. 8½ x 5½in. Hard covers. Price 16s.

IF you buy your instruments ready-made, a book on applications will appeal more than this slim volume. If you are a kit-building enthusiast, the information given by a reputable kit firm should be more than adequate for your needs. There is little here to augment it, despite a neat plug for Heathkit in the preface. To whom then, should this book appeal? Perhaps the best way to expound is to describe its contents and leave readers to judge.

Chapter 1, predictably, describes the meter movement. Chapter 2 explains the Volt-Ohm-Milliameter, and the following chapter the basic design of the valve voltmeter. There is no mention of the later types of transistor millivoltmeter or high impedance meters and it seems obvious that this book has not been revised since the original publication in 1963. Transistor testers receive a very perfunctory treatment and valve testers are hastily skated over.

Perhaps the greatest disappointment is Chapter 6, where a description of signal tracers does not include a single buildable circuit, nor any sensible details of the use of this very handy instrument. The chapter on oscilloscopes is longer, and more fundamental, but reveals very little practical circuitry and virtually no practical application.

new books—continued

Vital specifications are hardly mentioned at all.

Of all things to find in a purported instrument book, we find Battery Eliminators in Chapter 8. With modern regulated and transistorised power supply units, this chapter is something of an anachronism, just as the final chapter, on signal generators, has not reached the state of considering f.m. generators, wavemeters and other modern necessities.

The author is an electronics development engineer in instrumentation and his aim has been to give those intending to service electronic equipment a 'thorough understanding of test and measuring instruments'. It is a mystery why the publishers did not allow him the space to do so.—*HWH.*

Catalogue Received

G. W. Smith & Co. (Radio) Ltd., 3—34 Lisle Street, London, W.C.2 have just published their first comprehensive Catalogue of Electronic Components and Equipments. It contains over 150 fully illustrated pages and lists items ranging from relays to table lamps and communications receivers to zener diodes and amateur equipment.

The cost of the Catalogue is 5s. plus 1s. postage, but discount coupons included in the Catalogue enable the cost to be retrieved with purchases.

G. W. Smith carry the complete Lafayette range and are agents for Codar, Partridge Aerials, TW Electronics, Green, and Contactor Switchgear. They offer after-sales service and spares for all imported radio equipment shown in their Catalogue.

KEYING THE TEN-FIVE TX

—continued from page 103

"C.W." and apply power to the transmitter. After a suitable warming up period has elapsed rotate the Function switch to "Net" whereupon the stabiliser should glow. Check the current as monitored by the externally connected testmeter; this should be in the range of 15-20mA. Check that V1 is oscillating and that drive is available.

Connect a dummy load to the transmitter aerial socket (Sk3) and rotate the Function switch to "Transmit". Load up to approximately 8W. Check the current reading monitored by the external meter and compare it with the earlier reading; if the two readings differ adjust the value of R9 slightly in an attempt to make them equal each other. In the prototype this necessitated making R9=4.7kΩ.

Later, the external meter may be removed and pin 7 of the OA2 tube returned direct to chassis. The meter should then be set to read 0-250V d.c. when a reading taken from between the R4/Ry junction and chassis should be 150V at both the "Net" and "Transmit" positions of the transmitter Function switch.

When these tests have been satisfactorily carried out the dummy load may be replaced with the station aerial and after adjusting the transmitter in the usual way a call may be put out in either c.w. or phone modes. It will then be found that the 10W maximum input available under phone conditions can be increased to approximately 15W of c.w. on "80" metres. ■

MAKE THIS TRANSFILTER PORTABLE



FULL DETAILS IN NEXT MONTH'S ISSUE

It's a 7-transistor receiver just right for the experimenter. Uses transfilters for the i.f. inter-stage couplings. Provides higher "Q", greater selectivity and more efficient matching than conventional i.f. transformers.

— ALSO —

CLASS D WAVEMETER

A popular ex-WD heterodyne wavemeter still obtainable at around £3. How it works, how it may be used and how to modify it for working from a 6V a.c. source or direct from a.c. mains.

AUDIO A.G.C. UNIT

How to construct a simple printed circuit in-line add-on unit to give automatic gain control facilities to existing P.A. systems, tape recorders, etc. Performance figures given.

Plus another article in The Repairing Radio Sets series and other constructional features.

PRACTICAL WIRELESS

July issue—on sale June 9th

RESERVE YOUR COPY NOW!

NEW BARGAINS

MOVING COIL METER. 2 1/2 in. flush mounting 5.0-5mA centre zero. 25/- each.

MOVING COIL METER. 2 1/2 in. flush mounting 250-0-250 micro amps, centre zero. 29/6 each.

50 OHM 50 WATT WIRE WOUND POT-METER. 8/8 each.

1 MEG MINIATURE. Pot-meter Morganite standard, 1/2 in. spindle 1/- each. 9/- per dozen.

1 MEG MINIATURE. Pot-meter Morganite pre-set screwdriver control. 9d. each. 6/- per dozen.

PRE-SET 100K by Welwyn with intricate bakelite knob. 1/- each. 9/- per dozen.

100K POT-METER. Miniature type with double pole switch and standard 1/2 in. spindle, by Morganite. 2/- each. 18/- per dozen.

25K POT-METER Standard size with double pole switch by Egan with full length 1/2 in. spindle 3/- each. 35/- per dozen.

BLANKET TEST GLASS. Enclosed, normally closed circuit with open should blanket overheats. 4/8 ea.

THERMAL RELAY. Can be used to delay the supply of HT while heaters warm up, or will enable 15 amp. loads to be controlled by miniature switches or relays. Regular list price over £2 price 7/8 each.

SIEMENS HIGH SPEED RELAY. Twin 1000 ohm coils. Platinum points changeover contacts—Ez equipment. 8/8 each.

ELECTROLYTIC CONDENSER. 500MF. 50 v working. 5/- each. 48/- per dozen.

FOOTSWITCH. Two snap-action switches in metal box with flex lead. Ideal to control tape-recorder, dark room lamp, etc., 18/6, plus 2/9 postage and insurance.

TOGGLE SWITCH BARGAIN. 10 amp. 250 v. normal one hole fitting 2/9 each, or 30/- per dozen.

ELECTRIC LOCK. 24 v. coil, but rewirable to other voltages. 4/8 each.

COMPRESSION TRIMMERS. Twin 100 pF. 1/- each. 8/- per dozen.

MINIATURE RELAY. American make. 630 ohm coil. 30/30 volt operation. 2 pole changeover. 3/- each. 30 per dozen.

PRECISION WHEATSTONE BRIDGE. Opportunity to build cheaply. 100K wire wound pot. 15 v. rating, only 5/-.

SHEET PAXOLIN. Ideal for transistor projects. 12 pencils each 5/-.

3 in. PM LOUSPEAKERS. 3 ohm, 12/6, 80 ohm, 13/6.

TRANSISTOR FERRITE SLAB AERIAL with medium and long wave coils, 7/8 each.

SLIDE SWITCH. Sub miniature double pole changeover. 2/- each. 18/- per dozen.

MAGSLEPS (Selsyns). American made transmitter and receiver. 27/6 each. post 4/8 for any one or the pair.

Vacuum Cleaner Flex. Non-kinkable ribbed rubber, most pliable but very tough. 34 1/2 Core. Normally 1/9 per yard, offered at £3 per 100 yard coil, post and insurance 8/6.

Sub-Miniature Silicon Diodes. General purpose type with gold-plated leads, 1/- each, 10/- per dozen.

MINIATURE WAFER SWITCHES					
Number of Positions					
	2	3	4	6	12
1 pole	3/6	3/6	3/6	3/6	3/6
2 pole	3/6	3/6	3/6	3/6	3/6
3 pole	3/6	3/6	3/6		
4 pole	3/6	3/6			

Any 12 switches ordered together 40/-.

SEMI-CONDUCTOR BARGAINS

Type	No.	Price	Type	No.	Price
2N127	15/-	MAT101	8/6	OC71	3/6
2N128	10/-	MAT120	7/9	OC72	5/-
2N1742	25/-	MAT121	8/8	OC75	6/-
2N1747	25/-	OA10	6/-	OC76	5/-
2N1748	10/-	OA10	6/-	OC77	7/-
AC107	9/-	OA47	3/-	OC78	5/-
AC127	9/-	OA70	2/-	OC78D	5/-
ACV17	8/8	OA79	2/8	OC81	5/-
ACV18	5/8	OA81	2/8	OC81D	5/-
ACV19	6/8	OA85	2/8	OC82	5/-
ACV20	5/8	OA90	2/8	OC83	5/-
ACV21	6/-	OA91	2/8	OC84	6/-
ACV22	4/8	OA200	3/6	OC139	8/8
AF114	7/-	OA202	4/3	OC140	12/6
AF115	6/8	OC101	10/-	OC170	5/-
AF116	7/-	OC23	17/6	OC171	6/-
AF117	5/-	OC24	15/-	OC200	9/-
AF118	10/-	OC26	7/8	OC201	12/6
AF139	12/6	OC28	15/-	OC292	13/6
AF186	17/8	OC29	17/8	OC293	12/6
AF212	15/-	OC38	12/6	OC171	15/-
ASZ21	15/-	OC36	15/-	ORP12	8/6
BC107	14/8	OC42	6/8	ORP60	5/-
BY100	4/8	OC44	4/-	SB078	8/8
BY213	7/8	OC45	3/8	SB305	8/8
MAT100	7/9	OC70	4/-	SB251	10/-

SILICON RECTIFIERS

Tested and guaranteed


750mA.	100v.	1/3	1 Amp.	100v.	3/-
	200v.	1/8		200v.	4/-
	400v.	3/8		400v.	6/-
8A	100v.	3/6	10 Amp.	100v.	9/8
	200v.	5/-		200v.	12/6
	400v.	7/8		400v.	14/8

Sub-miniature glass encased—only approx 1 1/2 in. long wire ended.

750mA	50v. 1/8	100v. 2/8
	200v. 4/8	

CASSETTE LOADED DICTATING MACHINE

Battery operated and with all accessories. Really fantastic offer a British made £31 outfit for only £8.19.6 brilliantly designed for speed and efficiency—cassette takes normal spools drops in and out for easy loading—all normal functions—accessories include—stethoscopic earpiece—crystal microphone has on/off switch—telephone pick-up—tape reference pad—DON'T MISS THIS UNREPEATABLE OFFER—SEND TODAY £8.19.6 plus 7/8 post and insurance. Footswitch 18/6 extra. Spare Cassettes £7/6 each, three for £1.

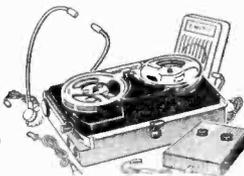

NOUGHTS AND CROSSES MACHINE. This machine, described in Sept. '65, is impossible to beat and will provide endless fun at home and considerable attraction (and profit) at charity do's and fetes, etc. It employs 19 switches and 9 bulbs and these and the other components necessary to make this are available. Price £4.10.0, post and insurance 3/6.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to max. Full power at all speeds by fingertip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance.

TWO NEW KITS

Multi-purpose Audio Switch, 5 transistors and all other components to make this ingenious unit described in last month's issue—only 48/6d. plus 2/9d. post and ins.

Analog Computer, all parts including centre zero galvanometer, perspex cursors, 8in. dials, to make the unit described in last month's issue. Available at 39/6d., plus 2/9d. post and ins.

THIS MONTH'S SNIP

An assortment of radio panel bulbs, all made by the famous Philips company. Their cost if bought retail would exceed 30/- . Offered as a parcel for 10/- post free. Parcel comprises 12 x 6-3V. -3A; 6 x 12V. -1A, 6 x 24V -05A; 6 x 12V. -6A, 6 x 6-3V -1A. All M.E.S. cap.

F.M. TUNER

of exceptional quality, giving really fantastic results with virtually no noise. Suitable for mains or battery operation. 6 transistors—three IF stages—double tuned discriminator. Complete, new, and built up all ready to work on chassis. Size 6 x 4 x 2 1/2 in. with tuning scale and slow motion drive. A £12.12.0 tuner for only £8.10.0.




SOLID STATE IGNITION

Big things are claimed of Electronic Ignition systems and if you would like to try for yourself a circuit was described in "Practical Electronics" (Sept., 1966). This requires a silicon controlled rectifier, four transistors and other components available as a kit. Price £6.15.0, post free.


OZONE AIR CONDITIONER

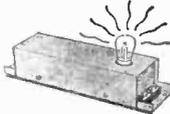For removing smells and generally improving oppressive atmosphere. In neat hammer finish box. Uses Philips ozone lamp and mains unit. Lamp easily replaceable. Only 39/8 plus 6/8 carr. and ins.



750mW TRANSISTOR AMPLIFIER

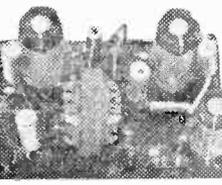
4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feed-back loops—sensitivity 5 m v. Price 19/6. Post and insurance 2/6. Speakers 3in. 12/6, 5in. 13/6, 6 x 4in. 14/6.



NOW INSTANT START

CIRCULAR FLUORESCENT

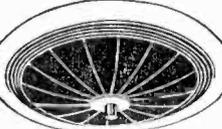Brings sunshine into your home. 150 watts of light but uses only 40 w. Beautiful fittings with glass, non-plastic centre, fluorescent tube and choke control. Made by Philips. Regular price £4.15.0. Special budget price 68/8, plus 8/6 c. and ins. Please state colour of glass centre, white, pink, blue, red, black, yellow or cream. Also whether normal or start, 99/8. 10/- carr. & ins.



MAIN TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500 mA (class B working). Takes the place of any of the following batteries: P11, P13, P14, P16, P17, P19, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, 6.000 and 600 mfd. condensers. Zener diode and instructions. Real snip at only 14/6, plus 3/6 postage.

9 VOLT PRECISION MOTOR

Intended for driving battery operated tape recorders and record players. Laminated, 6 Pole armature with Brush Gear and rapid start switch. Normally 25/- . Our Price 7/6, plus post and insurance 1/6.



SIMPLE RECEIVER FOR LOW VOLTAGE. A TRF transistor set powered from the Sun or a 1 1/2 v. cell. Suitable for children or others who forget to switch off. 4 N.P.N. silicon transistor diode and all other components necessary to build this circuit described in "Wireless World," Oct., are available as a kit. Price 19/8, plus 2/6 post and ins.

PHOTO-ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit, Laminated Boards and chemicals, Latching relay, Infra-red sensitive Photocell and Hood, 2 Transistors, cond., Terminal block, Plastic case. Essential data, circuits and P.C. chassis plans of 10 photo-electric devices including auto-car parking light, modulated light alarm. Simple invisible ray switch—counter—stray light alarm—warning tone electronic alarm—projector lamp stabiliser, etc., etc. Only 39/6, plus 2/- post and insurance.

HI-FI SPEAKER BARGAIN

12in. High fidelity loudspeaker. High flux permanent magnet type with either 3 or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 29/6. With built-in tweeter 35/-, plus 3/8 post and insurance.



Multi Purpose Neon Test Unit Robust, useful and instructive—tests insulation—capacity—continuity—resistor—voltage controls —also acts as signal injector and L.T. fault finder —kit comprises neon indicator—4-way water switch—ebonite tubes—resistors—condensers—terminals, etc. with diagram only 9/6, plus 2/- post and insurance.

PF3 Eliminator—play your pocket radio from the mainline Save £2. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions. Only 6/8, plus 1/- post.

SNIPERSCOPE

Famous war-time "cat's eye" used for seeing in the dark this is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the infra-red strike it. A golden opportunity for some interesting experiments. 7/8 each, post 2/-. Data will be supplied with kit, if requested.


HALF PRICE OFFER G.E.C. 13A Switched Sockets

Suitable for ring mains, etc. like the modern fused plug surface or sunk (flush) mounting type 4/9 each. 54/- 12/-.

12v. INVERTER Fully transistorised for operating a 20-watt fluorescent tube or other 20-watt mains device. Size 6 1/2 in. long by 1 1/2 in. 23.10.0. Post and insurance 3/-.

WATERPROOF HEATING ELEMENT 26 yards length 70W. Self-regulating temperature control 10/- post free.

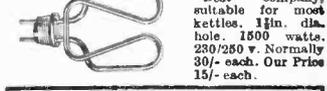KETTLE ELEMENT Made by famous "Best" company, suitable for most kettles. 1 1/2 in. dia. hole. 1500 watts. 230/250 v. Normally 30/- each. Our Price 15/- each.




Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free.

ELECTRONICS (CROYDON) LIMITED

(Dept. P. W.) 102/3 TAMWORTH RD., CROYDON, SURREY (Opp. W. Croydon Stn.)

also at 266 LONDON ROAD, CROYDON, SURREY

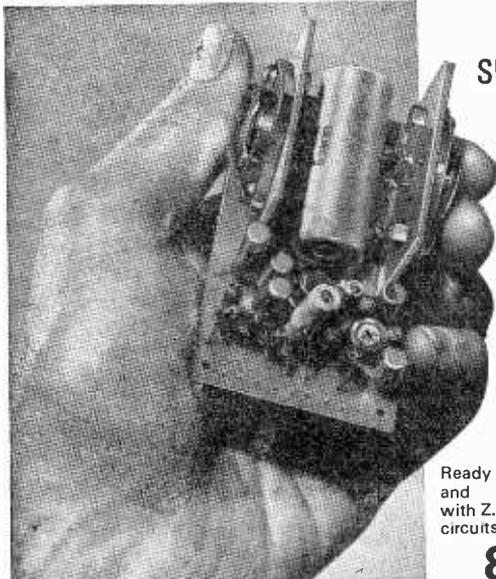

SINCLAIR

compact, powerful Z.12

COMBINED
12 WATT HI-FI
AMPLIFIER AND
PRE-AMP

12 WATTS R.M.S. OUTPUT CONTINUOUS SINE WAVE
(24 W. PEAK)

15 WATTS MUSIC POWER (30 WATTS PEAK)

The embodiment of power, efficiency and reliability, there has never been an amplifier to touch the Z.12 for adaptability and compactness. Nothing could be better than this fine amplifier for use with space-saving plinth-mounted motor and pick-up assemblies. Equally, the light weight of the Z.12 makes it the ideal guitar amplifier, particularly since it operates efficiently on any power supply between 6 and 20 V.D.C. The pre-amp of this 8-transistor masterpiece will accept the outputs of pick-up, radio and microphone, etc. Full details for matching, control and selector switching circuits are in the manual supplied with each unit. The Z.12 is now in use all over the world and is the accepted standard for all hi-fi needs.

MORE Z.12 USERS WRITE

"I must compliment you on your after-sales service. It is a pleasure to buy a product today and get the help that I have received."

E.E.W., Maidstone.

"I find the results after exhaustive tests very satisfactory. I consider that the performance is slightly superior to my valve equipment particularly as regards the reproduction of very low frequencies."

H.A. (Consulting Engineer), London, N6.

Ready built, tested and guaranteed, with Z.12 manual of circuits

89/6

- Frequency range—15–50,000 c/s \pm 1dB
- Ideal for use with a 12V car battery
- Can be used with 15, 7½ and 3Ω speakers. Two 3Ω speakers can be used in parallel

- Size 3 x 1½ x 1½in.
- Class B ultralinear output
- Input sensitivity—2mV into 2K ohms

SINCLAIR MICRO-FM

7 Transistor
combined
FM tuner-
receiver




Needs no
aligning when
built

This unique, superbly engineered FM superhet is the only set in the world which can be used both as an FM tuner and an independent FM pocket receiver just whenever you wish. Problems of alignment have been completely eliminated making the Micro-FM ready for use the moment you have built it. The pulse counting discriminator ensures best possible audio quality; sensitivity is such that the telescopic aerial included with the kit assures good reception in all but the very poorest reception areas. The Sinclair Micro-FM will give you all you want from a high quality FM unit. The case is elegantly styled in brushed and polished aluminium with spun aluminium slow motion tuning dial. SIZE—less than 3 x 1½ x ¾in.

7 Transistors, 2 diodes. Low I.F. obviates use of relatively large components and eliminates need for alignment after building. Set operates from a self-contained standard 9v. battery. A guaranteed Sinclair design. Complete kit inc. aerial, case earpiece and instructions

£5.19.6

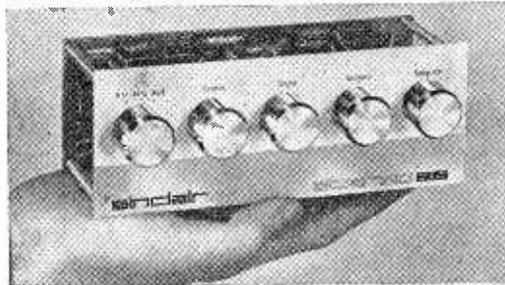

SINCLAIR STEREO 25

PRE-AMP AND
CONTROL UNIT

FOR USE WITH TWO Z.12s OR OTHER STEREO AMP

THE SINCLAIR STEREO 25 has been designed specially to ensure the highest possible standards of reproduction when used with two Z.12s or any other first class stereo power amplifier. Best possible components are used in the construction of this superb unit, whilst its appearance reflects the professional elegance characteristic of all Sinclair designs. The front panel of the Stereo 25 is in solid brushed and polished aluminium with beautifully styled solid aluminium control knobs. Mounting the unit is simple, and power is conveniently obtainable from the Sinclair PZ.3 which can also be used to supply two Z.12s to make a complete stereo assembly. Hi-fi enthusiasts seeking the ultimate in domestic listening will find all they want from this combination of Sinclair units. With a Micro-FM for tuner, they will have an installation to compare favourably with anything costing from four to five times as much.

Performance figures obtained using Stereo 25, two Z.12s and a PZ.3.

- **INPUTS** for P.U., Radio and Mic.
- **FREQUENCY RESPONSE** (Mic. and Radio)—25 c/s to 30 kc/s \pm 1dB extending to 100 kc/s \pm 3dB.
- **EQUALISATION** Correct to within \pm 1dB on R1A curve from 50 c/s to 20 kc/s.
- **CONTROLS** Volume, Treble, Bass, Volume, Input.
- **SIZE**—6½ x 2½ x 2½in. plus knobs.

SINCLAIR PZ.3 Transistorised A.C. mains power supply unit for two Z.12s with Stereo 25.

79/6


BUILT, TESTED AND
GUARANTEED
£9.19.6

★ Full service facilities available to all Sinclair customers



SINCLAIR RADIONICS LTD, 22 Newmarket Rd., CAMBRIDGE

Telephone OCA3-52996

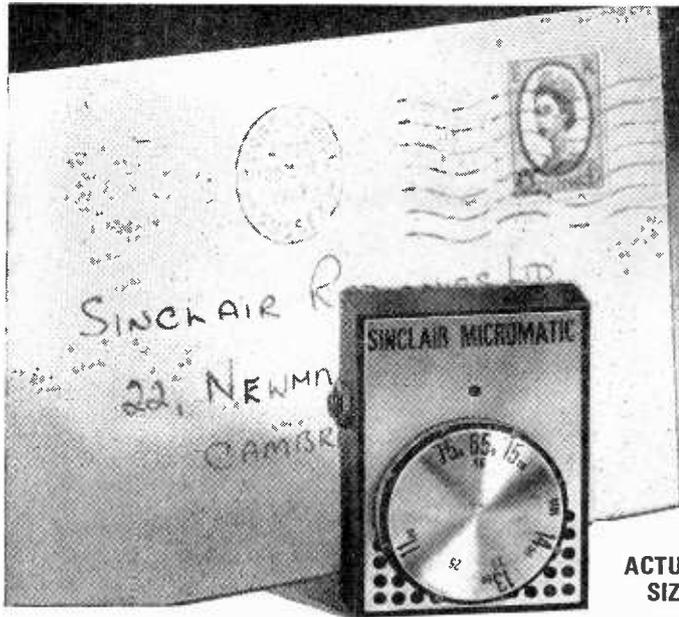

The most remarkable letter we have so far received

P.O. Box 43, PAKAKARIKI,
New Zealand.

27th February, 1967.

Thank you very much for the new Micromatic which arrived safely by Airmail. Our 13-year-old son is highly delighted. On the first evening he logged several New Zealand stations. These included our one and only "pirate", Radio Hauraki, stationed in the gulf of that name well over 400 miles north of here.

His biggest surprise was when 2CY, Canberra (10Kw) identified itself. Australia is more than 1,200 miles away! I tested the receiver within half a mile of 2YA and 2ZB (just north of Wellington). Selectivity remained perfect. Neither station swamped the other and the customary nul was evident when the ferrite aerial was end on to the transmitters.

In the metal coach of an electric train, the receiver functioned normally even under such noise producing conditions.

You have produced a radio receiver which has no equal. Its design size and performance are such that even you will not easily evolve a successor.

(Signed) Arnold S. Long

The original of this and countless other letters which enthusiasts send us can always be seen at our Cambridge offices.

SINCLAIR MICROMATIC

THE SMALLEST SET IN THE WORLD

- $1\frac{4}{5}'' \times 1\frac{3}{10}'' \times \frac{1}{2}''$
- NEW 6 STAGE CIRCUITRY
- AMAZING POWER AND RANGE
- BANDSPREAD
- IN KIT FORM OR READY BUILT

This British-made six stage transistor receiver is a fully fledged radio with all the features essential to reliable listening. It is smaller than anything you have ever used before, yet it gives good choice of programmes anywhere, is selective, powerful, dependable. When, after two or three months or so, the two batteries need replacing, new ones are easily obtainable from radio shops, Boots Chemists, etc. Good listening works out to under a halfpenny an hour. Whether you buy the

MICROMATIC in kit form or ready built, you will be the proud owner of a most elegantly styled set brimful of power and ready to keep you in touch with the world wherever you are — in modern town buildings, travelling, walking or anywhere else. The well prepared instructions manual makes building an assured success, and as with all Sinclair products, the MICROMATIC is fully guaranteed built or in kit form.

A SUPERB SPECIFICATION

This is a 6-stage receiver in which 3 special transistors are used in newly developed circuitry having two R.F. stages, a double diode detector and a powerful three stage A.F. amplifier, the output from which feeds into a specially matched high quality lightweight earpiece. The MICROMATIC has its own built-in ferrite rod aerial and uses vernier type tuning over the medium wave band. A.G.C. counteracts fading from distant stations. The beautifully styled case is faced with an artist designed aluminium front panel of outstanding elegance, with aluminium tuning dial to match.

Complete kit
in new "see-for-
yourself" quick
check pack,
instructions and
solder

59/6

Built, tested and
guaranteed with
ear piece and batts.

79/6

★ Full service facilities available to all Sinclair customers

USE THIS ORDER FORM FOR DELIVERY BY RETURN

SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE	
Please send	NAME
.....	ADDRESS
.....
for which I enclose cash/cheque/money
order value £.....s.....d.
	PW.6

Guarantee

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question.


NEW - ENLARGED - IMPROVED EXPERIMENTER'S PRINTED CIRCUIT KIT

BUILD 36 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4½" x 2½". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resistor. (5) Resolvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for building.

36 TRANSISTORISED PROJECTS

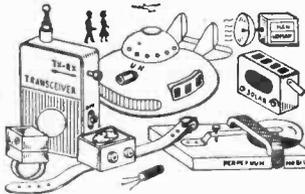A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 6 new circuits.



EXPERIMENTER'S PRINTED CIRCUIT KIT 8/6

Postage & Pack. 1/6 (UK)
Commonwealth:
SURFACE MAIL 2/-
AIR MAIL 8/-
Australia, New Zealand
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRIFLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World.


3 SUBMINIATURE RADIO RECEIVERS

Based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1-62" x .95" x .25". (11) Wristwatch Radio 1-15" x .80" x .55". (12) Ring Radio .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Seismic Car Alarm. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone - "Photophone".

PHOTOELECTRIC KIT

BUILD 12 EXCITING PHOTOELECTRIC DEVICES

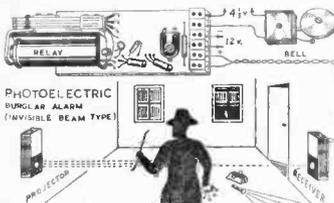CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Cadmium Sulphide Photocell, Latching Relay, 2 Transistors, Condenser, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT 39/6

Postage & Pack. 2/6 (UK)
Commonwealth:
SURFACE MAIL 3/6
AIR MAIL £1.0.0

Australia, New Zealand,
S. Africa, Canada & U.S.A.
Also Essential Data Circuits
and Plans for Building

12 PHOTOELECTRIC PROJECTS. (1) Steady-Light Photo-Switch/Alarm. (2) Modulated-Light Alarm. (3) Long-Range Stray-Light Alarm. (4) Relay-Less Alarm. (5) Warbling-Tone Alarm. (6) Closed-Loop Alarm. (7) Projector Lamp Stabiliser. (8) Electronic Projector Modulator. (9) Mains Power Supply. (10) Car Parking Lamp Switch. (11) Automatic Headlamp Dipper. (12) Super-Sensitive Alarm.

OPTICAL KIT Everything needed (except plywood) for building: 1, Invisible-Beam Projector and 1 Photocell Receiver (as illustrated).

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (UK).

LONG RANGE OPTICAL KIT 29/6 p.p. 1/6


Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 50 Radio, Electronic and Photoelectric Projects. Assembled.

Obtainable from your local supplier or direct from

"EXPERIMENTAL ELECTRONIC KITS"

Dep. YORK ELECTRICS, 333 York Rd., London S.W.11

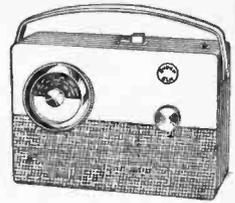The SUPER 6 LONG & MEDIUM WAVE TRANSISTOR RADIO



A quality radio available as a kit or ready-built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12.12.0 commercial model.

★ All new parts. ★ 6 transistors and diode. ★ 350mW output. ★ Superbet circuit ★ Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet 11 x 7½ x 3½in. ★ Vinyl covered in various colours. ★ 6 x 4in. speaker giving good bass and treble response. ★ Full instruction booklet, 2/-, free with kit. ★ I.f. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately. Write for list, S.A.E. COMPLETE KIT ONLY £4.0.0 P. & P. 5/- OR FULLY BUILT £6.7.6. Tax and Carr. Paid.

STEREO-AMPLIFIER 2 x 4 WATT

Valves ECC83, 2 x EL84, on printed circuit approx. 4 x 4in. Neg. feed back. Controls (Vol. or tone) on separate panel, 6½ x 2in. Separate power pack with rect., double wound mains trans., connection socket, etc. Supplied fully wired and tested with two O.P. transformers for 3-ohm speakers, only £5.10.0 (7/6 P. & P.). Two speakers, 8in., 3-ohm for 20/- each, post paid, if ordered with above Amp.

TAPE AMPLIFIER FOR MAGNVOX TAPE DECKS — 2 or 4 TRACK

Chassis 12½ x 5½ x 4½in. high. Plastic front panel "gold" finish—12½ x 4½in. 200-250 A.C. Record/Playback amp, switch; OR/On-Tone; Vol/Mic; Vol/Gram; Mic. Input; Gram. Input; Monitor; Speaker Sockets. Valves 6BR7; 12AX7; EM84; EL84; 6X4 Separate power pack. Complete amp. and power pack, £3.17.6. (6/- P. & P.). Resine covered cabinet (tan) 15½ x 17 x 9½in. high with sloping front for amp; complete with two tweeter speakers, and special adapting brackets for Magnavox Deck-85/- (8/- carr.) 3 speed Magnavox 2 track tape deck £10.17.6; 4-track £12.15.0. Complete Recorders (with speed compensation) 2-track £29; 4-track £32 (carr. 25/-). Worth £10 more on normal retail prices.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses) Aldershot B2240
CLOSED WEDNESDAY AFTERNOON
CATALOGUE 9d.

PRE-PAK SEMI-CONDUCTORS

DAVIS & WHITWORTH LTD.
BY 292-294 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
PHONE: SOUTHEND (0802) 46344

No.	DESCRIPTION	PRICE	TRANSISTORS PRICE
A1.	6—Silicon rectifiers BY100 type	20/-	4/-
A2.	10—Relays, mixed types and voltages	20/-	3/-
A3.	20—Mixed, marked and tested trans.	20/-	3/-
A5.	8—Sil. recs. 100-400P/PV, 0-5-1A	20/-	4/-
A6.	1—500 Mc/s epitaxial mesa. PNP 2N700	20/-	3/8
A8.	6—Sub. min. zeners, 3-16.15V, 400mW	20/-	3/8
A9.	1—2N174 real power trans. 80V, 150W	20/-	10/-
A13.	25—Assorted trans. and diodes, all new	20/-	5/-
A14.	4—2N601 p/trans. germ. 30V 10Mc/s	20/-	2/6
A15.	2—Power Comp. Pair. AD101/2	20/-	2/6
B1.	50—Unmarked, untested, trans., new	10/-	2/6
B2.	4—Solar cells, inc. Book of Instructions	10/-	5/-
B3.	4—OA5 gold bonded, diodes Mullard	10/-	10/-
B4.	20—Germ. diodes, 60P/V, 40Mc/s	10/-	10/-
B5.	7—Matched set, OC44, 45/81 D/81 + diode	10/-	5/-
B6.	15—Red spot AF. trans. or white spot RF.	10/-	2/6
B7.	2—60 watt power trans. 5Mc/s NPN	10/-	10/-
B8.	2—Power trans. OC28/35 type	10/-	2/6
B9.	1—Light sensitive cell, ORP12 type	8/-	2/6
B10.	10—60V trans. germ. FNE, latest type	10/-	2/6
B44.	1—Tunnel diode, APT1, 1000 Mc/s	10/-	2/6
B13.	7—BA115 G.B. diodes T.V. video	10/-	2/6
B15.	8—Bi-directional trans. ASY66	10/-	2/6
B20.	4—Assorted NPN trans., TO-6, TO-18	10/-	2/6
B21.	2—Sil. recs. 10 amp., 50-100P/V	10/-	2/6
B32.	4—1 amp. recs. 200/300 P/V	10/-	2/6
B33.	10—Germ. diodes, assorted types	10/-	2/6
B34.	8—Silicon diodes, assorted types	10/-	2/6
B35.	2—2 zener diodes 14W., 7 and 10 volts	10/-	2/6
B36.	10—Gold bonded, diodes, assorted	10/-	2/6
B42.	5—Switching trans. TK22C, STC.	10/-	2/6
B47.	10—Sil. stud. recs. unmarked, untested	10/-	2/6
B48.	5—Zener diodes, 5 volts, 1 watt.	10/-	2/6
C2.	1—Uni junction, 2N1260 or 2N2646	15/-	2/6
C4.	2—RF power trans., OC22 and BUY11.	15/-	2/6
D18.	1—ORP60 type light sensitive cell	5/-	2/6
AF114	4/-	2/6
AF115	3/-	2/6
AF116	3/-	2/6
AA117	4/-	2/6
AF118	3/8	2/6
AF119	3/8	2/6
AF178	10/-	2/6
BSY98A	5/-	2/6
GET102	2/6	2/6
OC211	2/6	2/6
NKT213	2/6	2/6
OC28	5/-	2/6
OC28	10/-	2/6
OC28	10/-	2/6
OC28	5/-	2/6
OC28	10/-	2/6
OC41	2/6	2/6
OC42	8/-	2/6
OC44	2/6	2/6
OC45	2/6	2/6
OC71	2/6	2/6
OC72	2/6	2/6
OC73	5/-	2/6
OC81	2/6	2/6
OC83	2/6	2/6
OC8D	4/-	2/6
OC139	2/6	2/6
OC149	5/-	2/6
OC170	3/-	2/6
OC217	4/-	2/6
OC290	5/-	2/6
OC201	3/-	2/6
2G301	2/6	2/6
2G339A	4/-	2/6
2G417	2/6	2/6
2N697	5/-	2/6
2N706	5/-	2/6

★ All our semiconductors have a written guarantee ★


FIRST EVER LOGIC KITS. Learn for yourself how computers work, even make one for yourself. Full instructions for a noughts and crosses machine, binary counters, timers, etc. L.1. 5 gns. L.2. 10 gns. No need to purchase both kits, you can start with L.2., which incorporates L.1. DETAILS FREE.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. For complete lists and subscription charts send 1/- in stamps, add 1/- post and packing. OVERSEAS ADD EXTRA FOR AIRMAIL.

'... designed to teach students and for this purpose should prove very useful' Industrial Electronics

MATHEMATICS for RADIO and ELECTRONICS TECHNICIANS

Dr. -Ing. Fritz Bergtold

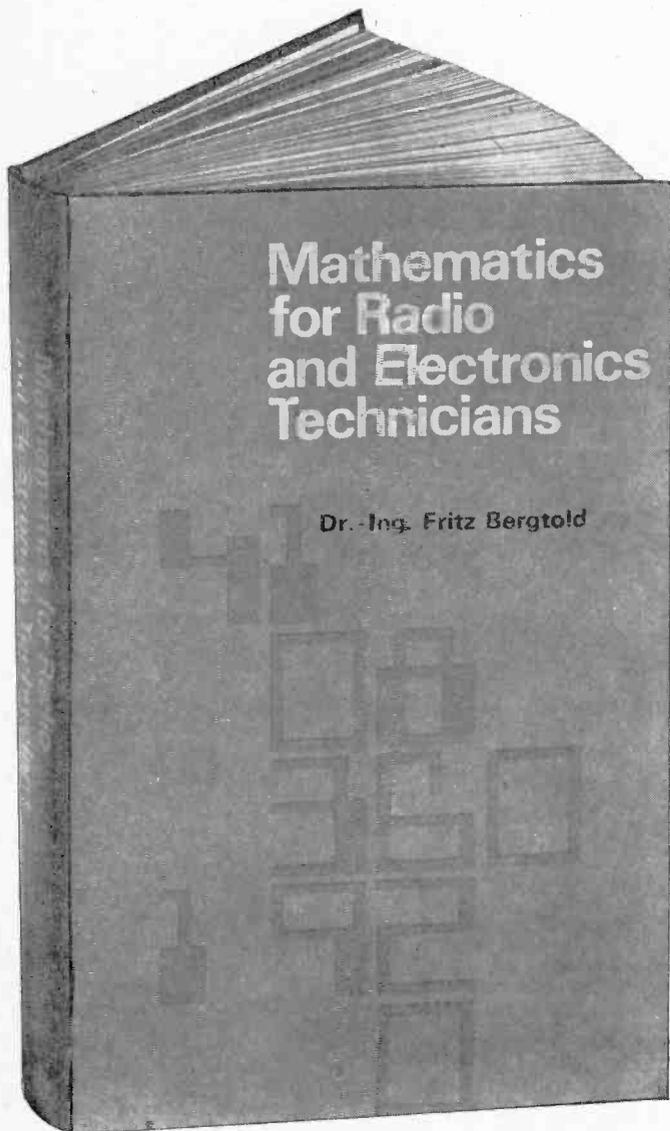

This book begins with the most simple equations and basic methods of calculations and gradually works its way through the various branches of mathematics which will be required by the radio and electronics technicians. The material is presented in an easy step-by-step method.

The subjects covered are involution, curves, arrangement, transformation and solution of equations, the slide rule, logarithms, the treatment of trigonometrical functions, Fourier and other series, differentiation and integration, polar co-ordinates and the Gaussian plane, vectors and calculation with complex values.

This teaching book will prove invaluable to all engaged or embarking on a career in radio and electronic engineering.

320 pages—266 figures, and numerous tables.

50s. from all booksellers or by post 52s. 6d. from George Newnes Ltd., Tower House, Southampton Street, London W.C.2.

NEWNES

Practical Wireless Classified Advertisements

EDUCATIONAL

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

I.E.R.E., City & Guilds and R.T.E.B. exams. Specialised ICS home-study course will ensure success. For details of wide range of exam, and diploma courses in Radio, T.V. & Electronics, also new practical courses with kits, write to: ICS (Dept. 542), Parkgate Road, London S.W.11.

BECOME 'Technically qualified' in your spare time, guaranteed diploma and exam. home-study courses in radio, T.V. servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

CITY & GUILDS (electrical, etc.) on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc., send for 132 page Handbook—FREE. **B.I.E.T.** (Dept. 168K) Aldermaston Court, Aldermaston, Berks.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs) R.T.E.B., etc. Many unique diploma courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS DEPT. 541 PARKGATE ROAD LONDON, S.W.11.

SITUATIONS VACANT

TV and Radio, City & Guilds, R.T.E.B., Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

RADIO & TV Exam. and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E., City & Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from **BRITISH NATIONAL RADIO SCHOOL**, Russel Street, Reading.

TRAINEE & skilled Service Engineers required by a large company dealing in the sale and manufacture of electronic and mechanical office machines. If your hobby is electronics and you would like to increase your knowledge and gain practical experience in the servicing of Dictating Machines and other electronic office machines why not write to our Technical Manager, Mr. Huddart at **OFFICE MACHINERY LTD.**, 17/23 Vale Royal, London, N.7 or telephone NORTH 7381.

RATES: 1/6 per word (minimum 12 words). Box No. 1/6 extra. Advertisements must be prepaid and addressed to **Advertisement Manager, "Practical Wireless", Tower House, Southampton St., London W.C.2.**

SITUATIONS VACANT

(continued)

ALDERMASTON COURT POSTAL TRAINING for B.Sc. (Eng) Part 1. A.M.I.E.R.E., A.M.S.E., City & Guilds, G.C.E., etc. prepares you privately for high pay and security as Technician or Technologist. Thousands of passes. For details of Exams & Courses in all branches of Engineering, Building, Electronics, etc. (including latest information on C.Eng.), write for 132-page handbook—FREE. Please state interest. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

RADIO TECHNICIANS

A number of suitably qualified candidates are required for permanent and pensionable employment (mostly in Cheltenham, but from time to time there are some vacancies in other parts of the UK, including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to candidates who can offer "O" level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19—£747, at 25—£962 (highest age pay on entry) rising by four annual increments to £1,104.

Prospects of promotion to grades in salary range £1,032—£1,691. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

**Recruitment Officer (RT),
Government Communications
Headquarters
Oakley, Priors Road
CHELTENHAM, Glos.**

METAL WORK

METAL WORK: All types cabinets, chassis racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.** Chapman Street, Loughborough.

LIGHT precision turning, screw-cutting, milling etc. Send sample or drawing for quotation, **J. K. MOLD**, 7 Wyvern Road, Moreton, Wirral, Cheshire. Phone ARRowebrook 8913.

SERVICE SHEETS

SERVICE SHEETS. RADIO, TV. 5,000 Models. List 1/6. S.A.E. Enquiries. **TELRAY**, Maudling Bk., Preston.

SERVICE SHEETS (75,000) 4/- each: please add loose 4d. stamp; callers welcome; always open. **THOMAS BOWER** 5 South Street, Oakenshaw, Bradford.

SERVICE SHEETS for all makes, Radio, TV, Tape Recorders, 1925-1967. Prices from 1/-, Catalogue 6,000 models 2/6d. Free fault-finding guide with all Sheets. Please send stamped addressed envelope with all orders/enquiries, **HAMILTON RADIO**, Western Road, St. Leonards, Sussex.

RADIO TELEVISION over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS

4/- each, plus postage

We have the largest display of Service Sheets for all makes and types of Radios and Televisions, etc., in the country. Speedy service.

To obtain the Service Sheet you require please complete the attached coupon

Name:

Address:

.....

To: **S.P. DISTRIBUTORS**

**35/36 Great Marlborough Street,
London, W.1**

Please supply Service Sheets for the following

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

I require the new 1967 List of Service Sheets at 1/6 each plus postage.

(please delete items not applicable)

I enclose remittance of (which includes postage)

MAIL ORDERS ONLY (June) PW

SOUND RECORDINGS

A UNIQUE TAPE BUY! Top brand 7in. 2,400ft. 25/-; 5 1/2in. 1,200ft. 15/-; P. and P. 1 at 2/-, 2 at 2/9, 3-6 at 3/6. Bargains in all sizes. S.A.E. for list. **E. C. KINGSLEY AND CO. LTD.**, 93 Tottenham Court Road, London W.1. EUSton 6500.

TAPE RECORDERS, TAPES, Etc.

TAPES TO DISC—using finest professional equipment 45 rpm—18/-. S.A.E. leaflet. **DEROY**, High Bank, Hawk Street, Carnforth, Lancs.

FOR SALE

MORSE MADE EASY !!

FACT NOT FICTION. If you start right you will be reading amateur and commercial Morse within a month. Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 w.p.m. in 4 weeks guaranteed.

For full explanatory booklet enclose 8d. in stamps to: G3CHS/P, 45 GREEN LANE, PURLEY, SURREY S.T.D. 01-660.2896

MINIFLUX 4-Track stereophonic/monophonic record/playback heads. List Price 6 gns.—Special Offer 55/- each. **MINIFLUX 4-Track stereophonic/monophonic Ferrite Erase Heads.** List Price £3.10.0.—Special Offer 32/6 each, or supplied together (one of each) at £3.17.6. **SKN4 1-track stereophonic record/play heads for Transistor Circuits** at 55/- each. Also available 1/2-track and full-track monophonic Ferrite Erase Heads. All heads complete with technical specifications. Send S.A.E. for details. **LEE ELECTRONICS, 400 Edgware Rd., Paddington 5521.**

ANALOGUE COMPUTER

Just think... with this desk-top Mini-Analog Computer you can multiply and divide, take square roots or powers, and do **log operations**—simply by turning the dials and keeping your eye on the null meter. (And all this from a 1 1/2 volt cell!) The Instruction Manual covers MAC-1's applications in electronics and physics, engineering and trigonometry.

Complete in kit form, MAC-1 is 3 gns.—or £3 13s 6d built and ready for use. (For either please add 4s 6d carriage.)

You would probably like more information: just send a 4d stamp to: **I-COR SYSTEMS (File PW3) 18 Stamford Hill, London, N.16**

TRANSISTORS SPECIAL OFFER

1 watt S.T.C. 300 mc/s N.P.N. Silicon Planar Transistors, limited stocks £1 for 6.

WITH DATA

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16, GET20.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171.

5/- each. OC139, OC140, GET7, GET8, GET9, XC141, BY100, OA211.

BSY27 7/6 each OC20 10/- each

ZENER DIODES

All volts between 3.9v. and 26v. 1/2w 3/6 each, 1.5w 5/- each, 7w 6/- each.

Send 6d. for full lists:— inc., S.C.R., Zeners.

CURSONS
78 BROAD STREET
CANTERBURY, KENT

FOR SALE
(continued)

COMPONENTS AT GIVE-AWAY PRICES: 92 Assorted resistors, condensers, valve holders, diodes, electrolytics, droppers, coils, pre-sets and plugs etc., etc., all brand new stock 10/- lot. **DIAMOND (MAIL ORDER) PRODUCTS, 204a FROGHALL LANE, HULL, EAST YORKSHIRE.**

HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK

3/8 TIN • JUST BRUSH ON • WITHSTANDS 150°C. OIL, WATER ETC.
2 1/2 oz. tins 3/6 1/2 gallon 85/-*
1/2 pint 7/6 1/4 gallon 58/-*
1 pint 15/- (* sent by road)
Carriage: Orders up to 5/-, 9d.; up to 10/-, 1/9; over 10/-, 3/-. Colours: blue, silver, black or bronze. Return of post service, Monday to Friday.

From your component shop or direct from the manufacturer:

FINNIGAN SPECIALTY PAINTS (PW)
Mickley Square, Stocksfield, Northumberland.
Tel. Stocksfield 2280.

YUKAN SELF-SPRAY HAMMER BLACK WRINKLE (CRACKLE)
Yukan Aerosol spraykit contains 16 oz. fine quality durable easy instant spray. No stone backing or dross. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/11 in our counter or 15/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Flat finish (12 oz. self-spray cans only) 13/- carriage paid.
SPECIAL OFFER: I can plus optional transferable snap-on trigger handle (value 5/-) for 18/11, carriage paid. Choose in 12 self-spray plain colours and primer. Motor car quality also available.
Please enclose cheque or P.O. for total amount to:
YUKAN, Dept.
307a EDGWARE ROAD,
LONDON, W.2.
Open all day Saturday. Closed Thursday afternoon.

Dept. PW/6

WANTED

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES, 55 Worcester Street, Wolverhampton.**

VALVES WANTED, brand new popular types boxed. **DURHAM SUPPLIES (C), 175 Durham Road, Bradford 8, Yorkshire.**

WE BUY New Valves and Transistors. State price. **A.D.A. MANUFACTURING CO., 116 Alfreeton Road, Nottingham.**

WANTED: Popular Brand New Valves. **R.H.S. Stamford House, 538 Great Horton Road, Bradford 7.**

DAMAGED AVO METERS wanted. Models 7 and 8. Any condition. Any quantity. Send for packing instructions. **HUGGETTS LTD., 2-4 Pawson's Road, West Croxson.**

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD
103 North Street, Leeds 7

RECEIVERS & COMPONENTS

PROFESSIONAL ELECTRONIC COMPONENTS

Send now S.A.E. for our first of many mail order lists which includes bargain offer in high quality hi-stab res. Don't miss getting on our mailing list now!

VAN-BEK ELECTRONICS
12 Market St., Altrincham, Cheshire

BARGAINS! BARGAINS!

Ex. Government Equipment

HRO'S, AR88's, 19 Sets and equipment, 31 Sets, B44's. 88, 38 and 18 Sets and miscellaneous Surplus Equipment.

A. J. THOMPSON (Dept. P.W.)

Eiling Lodge, Codicote, Hitchin, Herts.

Tel.: Codicote 242

SEMICONDUCTOR SPECIAL

AF139 12/6d., AF239 13/6d. Silicon Diodes 3/6d. per doz. Surplus BY100s 3/6d., 8 for £1. Surplus 2N706s 2/-d., 17/6d. doz. 5 Assorted 5 and 10A Thyristors £1. Post paid from J. C. WOODWARD, 94 Great Brickhill Street, Wolverhampton, Staffs.

TRANSISTORS SILICON PLANAR. AF & RF 2N706 to 100 Mc/s 3/-. 2N708, 400 Mc/s gain 6db at 100 Mc/s, 4/-. 2N2369, 650 Mc/s gain 7.5db at 100 Mc/s, 5/6. Diode SD10. Forward I 115 M/A PIV 30v. 3/-. R. A. IMPORT CO., 125 Balfour Road, Ilford. Data and Postage. 1/-.

TRANSMITTERS

Receivers, VHF, Wireless Intercom, Meters, Valves, Oscillators, UHF, Tuners, Transistors, Kits, Tools, Transformers, Transceivers, Switches, Test Sets, Telephones, Telescopic Aerials, Coils, Relays, Rectifiers, Microphones, Amplifiers, Speakers, Hi-Fi, Cables, Head Sets, Capacitors, Crystals, Filters, Registers, Plugs, Potentiometers, Mobile Transmitters, Morse Keys, Pick Ups, Chokes, Fire Alarms, FM Batteries, Communication Receivers, Compass, Antennas, Rotators, Aerials, Modules and lamps.

Send for free booklet and catalogue. Stamp please

P. J. PLOWMAN

Electronics Dealer
North Bradley House, Church Lane,
North Bradley, Trowbridge, Wilts.
Tel. 5306

RECEIVERS & COMPONENTS (continued)

TRANSISTORS, UNMARKED, UNTESTED, 40 for 10/-, p. and p. 1/-, 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc. (5,000 items), free. K. R. WHISTON (Dept. PRW), New Mills, Stockport.

TRANSMITTING VALVES, 813 or 4B13, also 811-G.B., 3 Guildford Close, West Worthing, Sussex. Worthing 6151.

BRAND NEW TELEVISION TUBES!


2 YEAR GUARANTEE. VAST RANGE
12" £3; 14" £4 (not CRM141)
17" £5.15.6; 19" £6.17.6 etc. etc.
Carriage 12/-

Also British valves, lists free!

PHILIP H. BEARMAN, 6 Potters Road,
New Barnet, Herts. Bar 1934/7873.

JOHN'S RADIO (Dept. B) OLD CO-OP, WHITEHALL ROAD DRIGLINGTON, BRADFORD

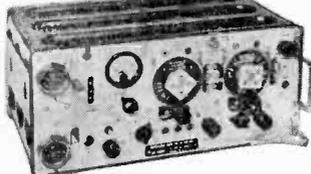FAMOUS ARMY SHORT-WAVE TRANSRECEIVER
MK. III




This set is made up of 3 separate units: (1) a two valve amplifier using a 6V6 output valve; (2) (some only, not built in the very latest models) a V.H.F. transceiver covering 229-241 Mc/s using 4 valves; (3) the main short-wave transmitter/receiver covering, in two switched bands, just below 2 Mc/s-4 Mc/s, and 4 Mc/s-8 Mc/s (approx. 160-37.5 metres) using 9 valves. For R.T., C.W. and M.C.W. The receiver is superheterodyne having 1 R.F. stage, frequency changer, two I.F. (465 Kc/s) signal detector, A.V.C. and output stage. A B.P.O. included for C.W. or single side-band reception. T.X. output valve 807, other valves octal bases. Many extras, e.g. netting switch, quick flick dial settings, squeel etc. Power requirements LT 12 volts, HT receiver 270 volts D.C., HT transmitter 500 volts D.C., size approx. 17 1/2 x 7 1/2 x 11 1/2. Every set supplied in new or as new condition in carton with book including circuits, only £4.10.0d., or Grade 2 slightly used 50/- carriage both 15/-.

A FULL KIT of brand new attachments for this set including all connectors, control box, headphones and mike, aerial tuning unit, co-axial lead etc. at only 45/- carriage 5/-.

WE MAKE A MAINS 200/250 VOLT POWER UNIT in louvered metal case to plug direct into set power socket to run (1) receiver, 70/- post 5/-.

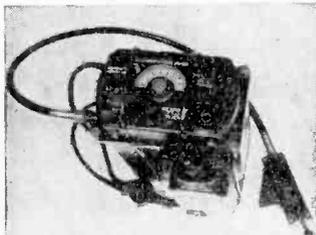(2) TX and RX, £8.10.0 post 7/6d. A charge of 10/- to unpack and test the receiver of these sets is made only if requested.

WALKIE-TALKIE MK III & CRYSTAL CALIBRATOR No. 9



This set is housed in a waterproof diecast aluminium case made by Murphy Radio for the Govt. having only reliability and quality in mind. Range 7.3-9 Mc/s, also on side of set is crystal calibrator No. 9 which gives pips on marks provided on the Tuning dial. Set uses a total of 5 valves power required L.T. 4 volts D.C., H.T. 100-175 volts D.C. Sets supplied in NEW or as new condition, boxed, only 50/- Carriage 10/-.

RECEIVERS & COMPONENTS (continued)

STELLA NINE RANGE CASES In Grey or Black Stolevite Removable Back/Rubber Feet. All fitted with aluminium chassis. Cash refund if not suitable in any way:

- 4-Channel Audio Mixer. 7" x 3 1/2" x 2". 10/3.
- 3.5 Mc/s Phone Transmitter. 8" x 6" x 4". 18/6.
- Transistor Tester. 6" x 3" x 2". 8/6.
- P.A. Pre-amplifier as Type D. 8 1/2" x 3 1/2" x 2 1/2". 14/6.
- Signal Generator Test Gear No. 2. 9" x 6" x 3". 22/-.
- Mighty Light. 8 1/2" x 3 1/2" x 3 1/2". 15/6.
- Model Train Controller. 8 1/2" x 5" x 3". 17/6.
- Linear Scale Cap Meter. 8 1/2" x 5 1/2" x 4". 18/6.
- The Explorer. 6 1/2" x 4 1/2" x 2 1/2". 11/6.

Other sizes in stock. S.A.E.

P.O. UNIT 1 x 3

Each unit contains:

- 6-12 way Miniature Sockets.
- 2-12 way Miniature Plugs c/w Screen Lead.
- 1-6 way Miniature Socket.
- 1-2µF Capacitor 250v. D.C.W.
- 1-1µF Capacitor 250v. D.C.W.
- 1-Induction Coil F.O. No. 3/16.
- 1-Retardation Coil 400r.
- 1-Selenium Rectifier Type 280/LU658A.
- 1-Operator 4-pin Jack Socket.
- 3-6-pole Changeover Toggle Switch with spring return to "OFF".
- 3-180r-3W Resistors.
- 3-12v Miniature Lilliput Screw Cap Lamp Holders with lamps and white plastic lens.
- 2-Metal Instrument Cases 5" x 5" x 4" plug in type.
- 1-Rack for Instrument Cases, horizontal or vertical mounting.
- 2-Humidity Indicators.

ALL BRAND NEW IN SEALED CARTONS.
20/- each, plus part post 5/-.

Assorted High Stab Resistors. 7/6, 100.

Assorted Syntex P.F. Condensers. 7/6, 100.
Thin Paxolin Sheet. approx. 1/16" x 12" x 12", 6 sheets for 5/-.

White Plastic Sheet, approx. 1/32" x 6 1/2" x 24"
Suitable dials, insulation, case fronts, etc. 4 sheets for 5/-.

P.O. Relay 2000 ohm. 1B. 5/-, 1M, 1B, 6/-.

Plessey Plugs and Sockets. 12 way, 3/- pr., 6 way 5/- pr.

6 or 12 way screened cable to match. 3/- yd.
Breast Mike. 6/-, Carbon Inserts, 1/6.

Small Component Boxes, 12/6, for 60 samples 6d.
100 volt Hand Generator, 7/6.

Modern lightweight Breast Mikes. Polythene fittings. New, 7/6, spare insert 2/6.

Type 3000 P.O. relay. New 6000 ohm coil, 2 sets of change-over. 8/6.

Printed circuit board, 11" x 5 1/2" ideal for reuse with 28 diodes CV488 plus some high stab resistors. 10/- post paid.

Polystyrene capacitors 125 volts wkg., 120,000. Recent manufacture for computer co. Prices 6d. each, 5/- doz., 25/- per 100. Your choice of values stock up now and save pounds. FREE sample with lists of values.

Siemens High Speed Relay, S.P.C.O. 1,000 + 1,000 ohms, 6/-.

Small Sealed Relay 1,700 + 1,700 ohms S.P.C.O., 6/-.

P.O. Relay, 200 ohms 2 change over. 6/-.

Mains transformer output 350-0-350v at 100mA + 2 x 5v at 2A, 1 x 2v at 1A, 1 x 6.3v at 2A, 15/-.

Extra Small Rotary Transformer by Hoover, 12v to output 300v suitable razors etc., with cooling fan new boxed. 10/-.

E. R. NICHOLLS

Mall Order and Retail Shop

46 LOWFIELD ROAD

OH SHAW HEATH, STOCKPORT

CHESHIRE

RECEIVERS & COMPONENTS (continued)

R & R RADIO

51, BURNLEY RD. RAWTENSTALL, ROSSENDALE
LANCS. TEL. ROSS 3152.

SALVAGE VALVES

Tested before despatch

6P13	4/6	1U99	5/-	80P11	4/-	PCC44	4/-
6L18	4/6	10P14	5/-	1P130	6/-	PY31	8/6
EP80	1/6	20P5	6/6	1P22	3/6	1301	6/-
ECC82	3/-	30P	7/-	1U501	7/6	10P13	5/6
ECL80	3/6	6P15	5/-	10F1	1/6	20D1	2/-
30P5	4/-	EH91	1/-	30P11	5/-	30P12	5/-
PCF80	3/-	Y85	7/-	PY32	6/-	Y88	5/-
1P181	5/-	80L2	4/-	614GT	6/-		
PZ30	5/-	20P3	6/-	EY86	4/-		

Speakers, Ex.T.V. 5in. round 6 x 4in., 3/6; 8in. round 6/-; post 2/-.

Line Output Transformers available. State set model No.

Turret Tuners. 8/- post 2/-.

Sean Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

WILSON ELECTRONICS

- 2/- ea. AC126, 127, 128, OC75, S18T, S19T.
- 2/3 ea. OC81, 81D, 82, 82D, 2/6 ea. OC44, 45.
- 3/- ea. OC71, 72, 170, AF117, 118, 119.
- 3/6 ea. AF115, 116, 125, 127, AC107.
- 4/- ea. AF114, OC171, 172.
- 7/- ea. OC23, 25, 26, 28.
- 8/6 ea. OC200, 11/6 ea., AD140, OC35, 38.

20 BRADBOURNE AVENUE, WILFORD,
NOTTINGHAM

300 m/W AMPLIFIER KITS

Comprising: Full instruction manual — Transformers — Printed circuit — Transistors — Resistors — Electrolytics — Potentiometer — Flex — Copper wire — and solder etc.
Price 35/- Post Free.

9-VOLT POWER PACK KITS

Comprising: Full instruction manual — Resistors — Transformer — Electrolytics — Mains lead — Flex — Printed circuit — Screws and nuts etc.
Price 27/6 Post Free.

Pocket-Size TRANSISTOR TESTER
Tests Transistors in or out of set — Tests both P.N.P. and N.P.N.
Price 30/- Battery and Post Free.

BROOK & HILL ELECTRONICS
695/697 SEVEN SISTERS ROAD
LONDON, N.15.
(50 yds from Wards Corner)

MISCELLANEOUS

ALUMINIUM CHASSIS, PANELS, etc. Quick service, 'One-offs' welcome. Send sketch for quotation (stamp please). Trade supplied. FAIRISGRADES LTD., Barling, Nr. Southend, Essex.

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swings.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 3d. stamp.

HEATHKIT

The World's Largest Manufacturer

of
ELECTRONIC KITS

We invite you to visit our
showrooms at

233 Tottenham Court Road, London, W.1

Telephone: 01-636-7349

Send for Free Catalogue, Dept. TC3

MISCELLANEOUS
(continued)

CONVERT ANY TV SET into an Oscilloscope. Diagrams and instructions 12/6. REDMOND, 42 Dean Close, Portslade, Sussex.

**INSTANT * *
ELECTRICITY
ANYWHERE!**



Wonderful for A.C. fluorescent lighting.

AMAZING NEW AMERICAN DYNAMOMETER UNIT which runs from any 12-volt CAR BATTERY and produces a **BIG ELECTRICAL OUTPUT** of 230/240 volts at 220 watts. Marvellous for TELEVISION, ELECTRIC DRILLS, MAINS LIGHTING and all Universal AC/DC mains equipment. **ONLY £12.10.0d.** plus 30/- carriage. Send stamped addressed envelope for illustrated details:—

SCIENTIFIC PRODUCTS (Dept. N), Onward Building (rear of Fleetwood Arms Hotel), Mount Street, Fleetwood, Lancs. Tel.: Fleetwood 3941
Open 7 days a week

BOOKS & PUBLICATIONS

SURPLUS HANDBOOKS

- 19 set Circuit and Notes .. 4/6 p/p 6d.
- 1155 set Circuit and Notes .. 4/6 p/p 6d.
- H.R.O. Technical Instructions .. 3/6 p/p 6d.
- 38 set Technical Instructions .. 3/6 p/p 6d.
- 46 set Working Instructions .. 3/6 p/p 6d.
- 88 set Technical Instructions .. 5/- p/p 6d.
- BC.221 Circuit and Notes .. 3/6 p/p 6d.
- Wavemeter Class D Tech. Instr. .. 3/6 p/p 6d.
- 18 set Circuit and Notes .. 3/6 p/p 6d.
- BC.1000 (31 set) Circuit and Notes .. 3/6 p/p 6d.
- CR.100/B.28 Circuit and Notes .. 8/6 p/p 9d.
- R.107 Circuit and Notes .. 5/- p/p 6d.
- AR.88D Instruction Manual .. 15/- p/p 1/6
- 62 set Circuit and Notes .. 4/6 p/p 6d.
- Circuit Diagram 3/- each post free. R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 set.

52 set Sender and Receiver circuits 5/- post free
Resistor colour code Indicator, 1/6 p/p 6d.

S.A.E. with all enquiries please.
Postage rates apply to U.K. only.

Mail order only to:

**INSTRUCTIONAL HANDBOOK
SUPPLIES**

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

**A.R.R.L. RADIO AMATEURS
HANDBOOK 1967**

New Edition 40/- Postage 4/6

- World Radio and T.V. Handbook 1967 by Johansen 32/- P. & P. 1/-
- Transistor Specs and Subs. Handbook 1967 by Techpress 21/- P. & P. 1/-
- Radio Valve Data 1967 ed. by Wireless World 9/6 P. & P. 1/-
- 101 Ways to use your Oscilloscope by Middleton 21/- P. & P. 1/-
- Computers, self taught through Experiments by Brayton 30/- P. & P. 1/-
- Amateur Radio Call Book 1967 by R.S.G.B. 8/- P. & P. 8d.
- Transistor Pocket Book by Hibberd 25/- P. & P. 1/3.

Where possible 24-hour service guaranteed.

UNIVERSAL BOOK CO.
12 LITTLE NEWPORT STREET
LONDON, W.C.2

(Leicester Square Tube Station)

**BROADWAY
ELECTRONICS**

GARRARD 4 SPEED DECKS WITH CARTRIDGE:
Autochangers: AT6 Mk II, 8/19.6. Autolim 45.5.0.
AT60 £10.19.6. 3000, 28.8.0. 2000, 28.18.6. 1000,
25.18.6.

AT5—Mono 28.10.0.
P. & P. all changers 7/6.
SINGLE PLAYERS:
SP25 with cartridge stereo or mono. 29.19.6. SRP 12,
24.5.0. P. & P. 7/6.

CARTRIDGES:
Stereo: EV26, 25/-, GP83, 15/-, Reuter, STD/2, 17/6.
Mono: GC8, 15/-, GC2, 15/-, Sonotone, 27/88, 15/-,
GP7, 15/-, P. & P. 1/-.

MICROPHONES:
Xtal Hand Mikes.
BM3 and 200C 30/-, P. & P. 2/- Stand for same
9/6 & 12/6. P. & P. 1/9. ACO8 Mike 45, 21/-, ACO8
Mike 40, 18/6. Dyn, Mike DM-391, 22/6. CM21 Xtal,
12/6. CM20 Xtal, 9/6. Magnetic Hm 65C with remote
control switch, 15/- Telephone Pick-up 10/6. P. & P.
1/- Xtal Lapel Mike, 7/6. Guitar Mike, 12/6. P. & P.
6d.

SPEAKER ENCLOSURES
Tony Corner Cabinet 20 x 10 x 7in. takes 10 x 6in.
speaker covered in Rexine and Vynair, 45/-, P. & P.
5/-

Blake cabinet size 18 x 24 x 9 1/2in., fabric covered
24.10.0. P. & P. 10/-

Haydon, 18 1/2 x 15 x 7 1/2in. fabric covered suitable for
12in. speaker, 45/-, P. & P. 7/6.

Haydon Enclosure fitted with 12in. speaker and
volume control 24.17.6. P. & P. 10/-

HI-FI Bookshelf speaker enclosure foam lined,
cabinet size 10 1/2 x 5 1/2 x 7 1/2in. Teak finish, 23.0.0.
P. & P. 3/6.

Wooler for above 23.0.0. P. & P. 2/6. Tweeter 12/6.
P. & P. 1/6. Condenser for crossover 2/6. Terminals
2/6 pair. P. & P. 6d.

PLINTH Teak finish to match above HI-FI speaker
size 17 1/2 x 14 x 4in. for Garrard 1000, 2000, 3000,
AT60, SP25, 22.17.6. P. & P. 4/6.

SPEAKERS:
Elae Heavy duty Ceramic Magnets 11,000 line, 10in.
round 10 x 6in. 3 ohm or 15 ohm, 42/6. P. & P. 3/6.

8in. round 15 or 3 ohm, 38/6. P. & P. 3/6. E.M.I.
13 1/2 x 8in. 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I.
Tweeter, 12/6. P. & P. 1/6. R.T.C. 12in. 20 watt 15
ohm Ceramic magnet 25.5.0. P. & P. 3/6. 8 x 4in.
Elliptical 30 ohm 80/- P. & P. 3/6. All other
speakers supplied—Goodmans, Bakers, W.B.,
Wharfedale, Eagle, Tripletone.

BARGAINS IN TRANSISTORS:
AC127, AF114, 115, 116, 117, 118, 119, OC169, 170,
171, 172, 200, 202, 203, 204, 5/6.

OC72, 75, 82, 83, A.4212, BY38, BC211, 3/8. OC71,
81, 3/-, R.F. Pack 1 OC44, 2 OC45 8/6, AF Packs 1
OC81D, 2 OC81 (Mullard), 8/6, A.F. Pack 1 GET119,
5/6. GET113, Red Spot, 2/-, OC26, 28, 29, 9/6.
ORP12 Light Cell, 8/6. Diodes OA81, 2/8. OA81,
OA95, 1/8. P. & P. on above 6d.

TRANSISTOR ELECTROLYTICS:
1, 2, 4, 5, 8, 10, 16, 25, 32, 50, 100 mfd 15 volt working.
1/8. P. & P. 6d.

250 mfd DC 3/-, 500 mfd 12v DC, 3/-, 500 mfd 50v
DC, 5/-, P. & P. 1/-

RESISTORS 1 watt 10% from 3.3 ohm to 10 meg 5d,
each, 4/- doz. P. & P. 6d.

**EARPIECES WITH CORD AND 3.5 mm. plug, 8 ohm
magnetic, 3/-, 250 ohm, 4/-, 180 ohm with clip, 6/6.
Xtal 4/-, P. & P. 6d.**

TRANSISTOR SPEAKERS 8 ohm 2in., 8/6; 3in.
10/6; 3 1/2in. 12/6. P. & P. 1/-

PANEL LIGHTS. 5v. Red, Blue, Green, Yellow,
White (uses Lilliput bulbs) 3/- each. P. & P. 6d.

NEON PANEL LIGHTS 200-250v. 3/- each. P. & P. 6d.
PAPER CONDENSERS for Cross-Over Units 2
mfd. 2/6. P. & P. 6d.

ROTARY SWITCHES
3 pole 3 way, 3 pole 4 way, 1 pole 12 way, 2 pole 2 way,
2 pole 3 way, 2 pole 4 way, 4 pole 3 way, 3/6 each.
P. & P. 6d.

PUSH BUTTON SWITCHES, 4 button, 2 banks of 6
S.P.C.O., 1 bank of 5 S.P.C.O. 1 off button 5/6.
P. & P. 6d.

**BATTERY CHARGER TRANSFORMERS AND
RECTIFIERS** 4 amp. GEO Rect., 15/-, Heavy Duty
Transformer. 25/-, P. & P. 3/6. 1 amp. Westinghouse
contact cooled rect., 7/6. Transformer 12/6. P. & P.
3/-, Large Croc. Clips, 2/6 per pair. P. & P. 6d.


FERROX ROD AERIAL with coils, 8 x 1/4in. 5/6.
4 x 1/4in. 4/6. P. & P. 9d.

Stockists of ● Eagle Products ● Goodmans ●
W.B. ● Wharfedale ● Bakers ● Tripletone ●
Linear, all makes of amplifiers and speakers supplied.
S.A.E. please. Trade terms to bona fide dealers.

**92 MITCHAM ROAD, Tooting
BROADWAY, LONDON, S.W.17**
Telephone BALham 3984
Closed all day Wednesday
(four minutes from Tooting Broadway
Underground Station)

**PRICE
SPECIAL RADIO
CHASSIS OFFERS**

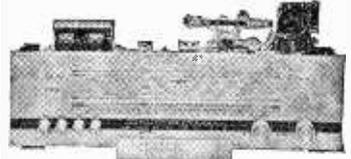**HI-FI KUBA ROYAL
STEREOPHONIC TUNER AMPLIFIER**



High Fidelity stereo/tuner amplifier. A four wave band tuner unit integrated with a powerful 16 watt high fidelity push-pull stereo amplifier. The most advanced comprehensive chassis yet designed. 8 Piano Key Selectors. Separate bass and treble controls. Full tape recording and play back facilities. Complete with a 4 speaker system (2-4in. tweeters, 2-10in. bass speakers) plus BSR 4 speed record changer. Model UAT0 with ceramic cartridge and diamond stylus. Fully guaranteed for one year including all valves.


Special Package offer only £74.5.0. (Chassis only 49/- Gns.)

Terms £24.15.0 deposit followed by 24 Monthly Payments of £2.11.7 (total H.P. £86.13.0) + 17/6 P. & P. Send £25.12.6 NOW.

For other stereophonic equipment see page 158.

**HI EQUIPMENT CABINETS
OF DISTINCTION**

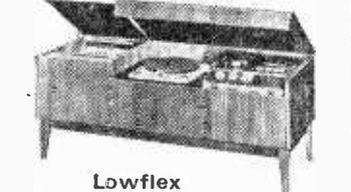- Illustrated in this advertisement is just one fine cabinet from the Lewis Radio Range.
- Each Lewis Radio Cabinet is carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex

**FREE THE NEW LEWIS
RADIO CATALOGUE**

Designed to assist your choice of Cabinet. The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE! Also available comprehensive range of stereophonic radiogram chassis and matching equipment. See page 158

Please send your FREE cabinet catalogue
Stereophonic equipment leaflets

NAME

ADDRESS

..... (Dept. P67)
Capitals please

LEWIS radio
LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14. Telephone: PA1 3733/9666

BI-PAK SEMICONDUCTORS

8 RADNOR HOUSE
93/97 REGENT STREET
LONDON W1

★ VALUE PAKS for '67
★ — NEW — UNTESTED —

PIV	LOW COST SILICON CONTROLLED RECTIFIERS (THYRISTORS) FACTORY TESTED		FACTORY TESTED		Free SCR Literature, Circuits, etc., with SCR orders or on request.
	1 AMP (TO-5 can)	7 AMP (STUD)	16 AMP (STUD)	30 AMP (STUD)	
25	7/8	7/8	10/6	35/-	
50	8/6	8/8	15/-	45/-	
100	12/6	15/-	20/-	55/-	
200	15/-	20/-	25/-	—	
300	17/6	25/-	35/-	80/-	
400	—	30/-	45/-	95/-	
500	—	40/-	50/-	—	
600	—	—	—	—	

FREE One 10/- Pack of your own choice (free with orders valued £4 or over) **FREE** LOGIC MODULES and/or, Gates, Memory Units, Timer Units, etc., details free **FREE**

VALUE PAK 50 TRANSISTORS MIXED UNTESTED **10/-** UNMARKED, UNTESTED VOLTAGE RANGE 1 Amp 50-400 PIV **10SCR's** **20/-**

3 OC139 Trans. NPN Mullard	10/-	3 High volt. AF Trans. PNP ACY17	15/-
2 Drift Trans. 2N1225 100 M/Cs PNP	10/-	5 Sil. Rect. 750mA 100 PIV TEXAS	15/-
6 Matched Trans. OC44/45/81/81D	10/-	3 BSY95A Sil. Trans. STC	15/-
4 OA10 Diodes Mullard	10/-	3 Sil. Trans. OC200 Mullard	15/-
15 Red Spot AF Trans. PNP	10/-	2 Sil. Power Rect. 5 Amp. 200 PIV BYZ13	15/-
15 White Spot RF Trans. PNP	10/-	1 AF139 GERM. Trans. 1500 M/Cs	15/-
4 Sil. Rects. 3A 100/400 PIV	10/-	1 Sil. Power Trans. 100 M/Cs TK 201A NPN	15/-
4 NPN Trans. OC139 2N1302, etc.	10/-	6 Zener Diodes 3-15 volts. Mixed 400 mW	15/-
2 10 Amp. Sil. Rect. 50/100 PIV	10/-	5 OA5 Gold Bonded Diodes Mullard	15/-
8 Diodes 4 OA70, 4 OA79	10/-	1 2N1182 PNP PLANAR Trans. Sil.	15/-
1 5 AMP SCR 100 PIV	10/-	2 2N697 NPN PLANAR Trans. Sil.	15/-
3 Sil. Trans. 2S303 PNP	10/-	4 GERM. Power Trans. eqvt. OC16 Mullard	15/-
5 GBT884 Trans. Eqvt. OC44	10/-	1 UNIJUNCTION Trans. 2N2646 G.E.	15/-
10 Assorted Computer Diodes	10/-	2 Sil. Trans. 60VCB 200 M/Cs ZT83/84	15/-
4 Zeners 5, 6.8, 10, 12 Volts	10/-	1 Sil. PLANAR Trans. BSY25 NPN 100 M/Cs	15/-
4 2G417 Trans. Eqvt. AF1118/117	10/-	1 Sil. Trans. 1B104 150 M/Cs HFE 200 NPN	15/-
2 200 M/Cs Sil. Trans. BSY26/27	10/-	2 SCR's 50 PIV 1 Amp. TO-5 can	15/-
2 Bi-directional Trans. ASY66	10/-	1 Tunnel Diode IN3720 (TD-5) G.E.	15/-
3 NPN Sil. Trans. 70 M/Cs	10/-	1 2N2160 UNIJUNCTION Trans. TO-5 can	15/-
1 Power Trans. OC20 100 Volts	10/-	2 Sil. Rect. 5 Amp. 400 PIV Stud	15/-
5 OA47 Gold Bonded Diodes	10/-	1 Tunnel Diode AEY 11 STC. 1050 M/Cs	15/-
8 OC71 Trans. Mullard	10/-	2 GERM. Power Trans. OC28/29	15/-
3 OC76 Trans. Mullard	10/-	2 ZENERS 25 watt 18 and 22 volts	15/-
3 NPN Sil. Trans. 70 M/Cs	10/-	6 Sil. Rect. Type BY100 800 PIV 550mA	20/-
1 Power Trans. OC20 100 Volts	10/-	8 Sil. Rect. 400 PIV 200/500mA	20/-
5 OA47 Gold Bonded Diodes	10/-	1 Transistor Manual by G.E. 648 pages	30/-
4 OA202 Sil. Diodes Sub-Min.	10/-	1 Silicon Controlled Rect. Manual G.E.	30/-
3 OC77 Trans. Mullard	10/-	25 Mixed Sil. & GERM. Trans. New Marked	30/-
8 OA81 Diodes CV448	10/-	40 Mixed Semiconductors New Marked	40/-
8 Sil. Rects PIV. 400 500 mA	10/-	1 Logic Module Handbook & Catalogue	17/6

Our vast stocks change daily with hundreds of Semiconductor bargains becoming available. Just send 2/6 to cover 3 months mailing of our latest stock lists, eqvt. charts, circuits, etc.

Minimum Order 10/-. CASH WITH ORDER PLEASE. Add 1/- postage and packing per Order. GUARANTEED by return postal service. Overseas add extra for Airmail.

GERM. SUB MIN.
120 DIODES 10/-

ALL TYPES MIXED VOLTS
20 ZENERS 10/-

SIL. NPN 200 M/Cs
25 Transistors 10/-

1 Amp. GERM. up to 300 PIV
20 RECTIFIERS 10/-

SILICON 200 mA
60 DIODES 10/-

SILICON 750 mA TOP-HAT
16 RECTIFIERS 10/-

SILICON BRIDGE RECTIFIERS
NEW TESTED
600 PIV 2 Amp. at 55°C..... 25/- EACH
800 PIV 2 Amp. at 55°C..... 30/- EACH

A COMPLETE RANGE OF SILICON RECTIFIERS 750 mA TO 25 Amp. 50-1000 PIV NOW IN STOCK. ASK FOR PRICE LIST.

TV TUBES REBUILT & RESCREENED

by Britain's largest
independent Tube
Rebuilder

SUFFOLK TUBES LTD.
1/3 Upper Richmond Road
Putney, London, S.W.15
Tel.: Vandyke 4304/5267

MIDLAND TUBES LTD.
467/483 Oldham Road
Manchester, 10
Tel.: Collyhurst 4412

BINARY ADDER/SUBTRACTOR

$$\begin{array}{r} 1011 \\ + 1100 \\ \hline 10111 \end{array} \quad \begin{array}{r} 1101 \\ - 0110 \\ \hline 0111 \end{array}$$

Above are two examples of calculations possible with our Binary circuit. This circuit uses switches and lamps only, and makes an excellent demonstration model for schools and training colleges. All parts are available at a reasonable cost. Full circuit, wiring diagram, price list and text explaining the Binary system—3/6d. post free.

PLANET INSTRUMENT CO
25(W) DOMINION AVENUE, LEEDS 7

Questions and Answers Series

Q. & A. on TRANSISTORS Clement Brown

Starting with the properties of semi-conductor materials, this book covers basic transistor circuits, transistors in radio receivers, high fidelity amplifiers and tape recorders and public address equipment. 96 pages. 60 line diagrams

Q. & A. on RADIO H. W. Hellyer

Starting with the fundamentals of electricity and sound and radio waves, this manual provides a thorough grasp of the principles of radio and television transmission and reception, with emphasis on modern practical techniques.

128 pages. 70 line diagrams.

Only 8s. 6d. each from all booksellers or in case of difficulty by post, 10s. from Newnes, Tower House, Southampton Street, W.C.2

Now available—
free revised catalogue
of the widest range of
Lenses, Prisms, Graticules, Flats etc.


from Dept. no. PW1

UNITED TECHNICAL SUPPLIES LTD

29 TOTTENHAM COURT ROAD LONDON W1

Phone: LAN 1118.7

UTS

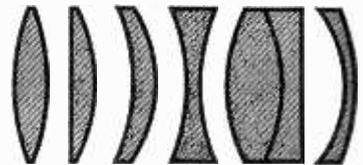

the how-to-do-it gardening weekly



Pricking out



Planting out



Disbudding Dahlias



Patio Gardening

HOME GARDENER experts really dig deep into a gardener's problems. They're all practical people with years of working experience behind them, and they cover the ground from the ordinary gardener's point of view, analysing the snags, putting you wise on the latest methods, showing you point by point and season by season, how to get the best possible results from everything you grow.

Every variety of Flowers, Fruit and Vegetables—HOME GARDENER covers the lot, with a wealth of how-to-do-it illustrations. If you want the very best from your garden, get this down-to-earth paper every week. It pays to read HOME GARDENER . . . in a big way.

HOME GARDENER

EVERY THURSDAY 7d. — PLACE A REGULAR ORDER WITH YOUR NEWSAGENT

PRICE SPECIAL RADIO CHASSIS OFFERS

HI-FI CONTINENTAL STEREOGRAPHIC RADIOGRAM CHASSIS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Comes complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed automatic record changer. Complete 29 gns. (Units available separately if required. Chassis only, 21 gns.)

Special terms available of £10.6.6 deposit followed by 18 monthly payments of £1.7.3 (total H.P. of £34.17.0) + 17/6 P. & P. Send £11.4.0 now.

IMPERIAL HI-FI STEREOGRAPHIC RADIOGRAM CHASSIS



The Imperial Stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons, controlling mono/stereo selection, Gram Long-Medium-Short-FM-ON/OFF. The unit comes complete with two 10" elliptical loudspeakers plus a mono/stereo 4 speed automatic record changer. Complete £41.9.6. Chassis only, 29 gns.

Special terms available of £13.16.6 deposit followed by 24 monthly payments of £1.8.10 (total H.P. £48.8.6) + 17/6 P. & P. Send £14.14.0 now.

EMPRESS HI-FI AM/FM STEREOGRAPHIC CHASSIS



This most advanced radiogram chassis with automatic push button selection covers short, medium and long wavebands plus V.H.F./F.M. Offered complete with 2 10 x 6 speakers 4 speed Stereo/Mono autochanger only £35.19.6. Chassis only, 25 gns. Special terms available of £12 deposit followed by 18 monthly payments of £1.11.7. (total H.P. £40.8.6) + 17/6 P. & P. Send £12.17.6 now.

All Lewis Radio equipment including valves are fully guaranteed for one year free of charge. For other Stereophonic Equipment and Cabinets, see page 155. Send your cheque or P.O. today while stocks last to Dept. P.67.

LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14. Telephone: PAL 3733/9666

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

Special Offer. 19 Sets, Mark 3, in good clean condition. Parts removed. 'B' set, 807 valve. TX section made U.S. Receiver bench tested. All that is required is a power pack. Price 35/-, Carriage 10/-.

19 Sets in fair condition as above and also removed is the meter and Relay. 10/-, Carriage 10/-.

46 Sets. New condition. Less Send/Receive switch, Crystal and Coils. 12/6 post paid.

46 Set Whip Aerial Sections. Nine for 2/- plus P.P. 2/6.

Ex RAF Wave Meter. Type W1649. All complete with Slow Motion drive and six valves. Housed in wooden box. Used 17/6. New 30/- plus carriage B.R.S. 10/-.

Silicon Rectifiers. Top grade. Half amp 800 P.I.V., 3/- post paid; Half amp 400 P.I.V., 2/6 post paid; 5 amp 800 P.I.V., 5/- post paid; 5 amp 400 P.I.V., 4/- post paid; 5 amp 200 P.I.V., 2/6 post paid.

VALVE LIST

Ex. Equipment, 3 months' guarantee. Single Valves. Post 7d.					
EF80	1/6	PCL82	4/-	20P4	8/6
ECL80	1/6	PZ30	5/-	U329	5/-
EF91	9d.	PY81	1/6	U801	8/6
EB91	9d.	PY82	1/6	U301	5/-
EBF80	3/-	PL81	4/-	U191	5/-
ECC81	3/-	FL36	5/-	U231	5/-
ECC82	3/-	PY33	5/-	U282	5/-
ECC83	4/-	6B8	1/6	U25	5/-
EY86	5/-	6F1	1/-	ARP12	1/6
EF50	1/-	6F14	5/-	EL38	5/-
6K25	5/-	10C2	5/-	5U49	4/-
6U4	5/-	10P13	2/6	6KT	1/9
6P25	5/-	10P14	5/-	6V6	1/6
KT36	5/-	20D1	3/-	185BT	8/6
PCF80	2/-	20L1	5/-	807	5/-
PCC84	2/-	20P1	4/-		

Top Grade Diodes, 3/6 doz. post paid.

Jap Earpiece, 3 or 5 m.m. plug, 1/11 post paid.

New 12in. Speaker with built-in tweeter, 3 or 15 ohm coil, 28/6 post paid.

Reclaimed Tubes. Six months' guarantee. 17in., 30/-; 14in., 17/- plus carriage 10/-, All types.

Motors ex Washing Machines, 1 h.p. 1,400 revs. 230 volt. 26/-, Carriage 10/-.

ELECTRONICS GALORE! IN THE NEW dca CATALOGUE

THE CONVENIENT WAY TO SHOP FOR ALL YOUR ELECTRONIC NEEDS.


EVERYTHING FROM SINGLE COMPONENTS TO COMPLETE EQUIPMENT ALL AT BEST VALUE PRICES.

SEND 1/6d. NOW FOR YOUR COPY TO:-

Dept. PW/6

dca ELECTRONICS LIMITED
28 UXBRIDGE RD., EALING, W.5

LISTEN TO THE WORLD on TELSTAR our

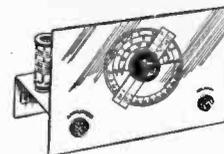

1-VALVE
SHORT WAVE
RADIO

Receives speech and music from all over the world. Price includes valve and one coil covering 40-100 metres. Can be extended to cover 10-100 metres. Can be converted to 2 or 3 valve and all-mains speaker use. **35/-** P. & P. 2/-
Total building costs
All parts available separately.

POCKET RADIO
Covers Medium waveband. No batteries needed. Complete with earpiece. **Only 12/6** P. & P. 2/-

MAINS POWER PACKS
The ideal economical and safe way of running any Transistor Radio, Record Player, Tape Recorder, Amplifier, etc. from A.C. Mains. The MAJOR "Power Plus" for 9v., 7.1v., 6v., 4.5v.; Single Output. P. & P. 2/6 **39/6**
For 9v. + 9v.; 6v. + 6v.; 4.5v. + 4.5v. Two separate outputs. P. & P. 2/6 **42/6**
Please state outputs required.
The BIJOU "Power Plus". For the smaller set using PP3 type battery. **17/6** P. & P. 2/6
All units are completely isolated from mains by double wound transformer ensuring 100% safety.

EASY TO BUILD SETS FOR THE CONSTRUCTOR
Crystal Radio with case. **8/6**
3-Transistor Set with speaker **37/6**
M.W. Tape Tuner for your recorder **20/-**
Supplied with easy to follow instructions. All parts available separately.
R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.), 11 Oliver Road, London, E17

"GLOBE-KING" 2-4 Metres 10-180 Metres

ALL TRANSISTOR
AMATEUR VHF and SHORT-WAVE KITS
Send stamped addressed envelope for free copy interesting literature describing latest products: Unique VHF kit model SR2/P. 70-150 Mcs., 69/6 p.p. 4/-, Short-Wave kit model TR2. 79/6 p.p. 5/-, "Mini-Amp" self-contained, cabinet size a mere 4 x 3 1/4 x 2 1/4", 139/6 p.p. 4/-. Despatch: Within 21 days from receipt of order. Overseas enthusiasts send local stamp for literature and special postal charges for your particular country: Sole makers "Globe-King" (Regd.) products: Tel.: 24864; Est. 1943.

JOHNSONS (RADIO)
St. Martins Gate, Worcester

GO AROUND THE WORLD
39/6
£2 POST FREE
Pat. App. For

On your own **TRANSISTOR PORTABLE!**

- ★ Boosts Pirate and distant stations
- ★ No Plugs—No Connections! Just place Dewtron Wave Trap near radio.
- ★ Extends Battery life — reduces 'fading'.
- ★ Use in car, caravan, without aerial. With PP3 battery (life several months).

D.E.W. LTD., Dept. P.W., Ringwood Road, FERNDOWN, Dorset.



SCR'S (THYRISTORS)

1 AMP SERIES WIRE LEADS

50 PIV	7/6	100 PIV	7/6
200 PIV	12/6	300 PIV	15/-
400 PIV (280V Rms)	1 Amp		17/6
100 PIV, 3 Amp Stud Type			9/6
400 PIV, 3 Amp (280V Rms) Stud Type	20/-		
400 PIV 5/7 Amp Stud Type	25/-		

27 Mc/s BAND RADIO CONTROL

Sub-miniature crystals, 17/6 each. Watched Pairs for superhet 35/- pair. (State 455 kc/s or 470 kc/s I.F.). Complete range of Recs. and Transmitter Kits In stock—see Catalogue.



HENRY'S RADIO LTD.

303 EDGWARE RD., LONDON, W.2
PA Ddington 1008/19 (STD 01-723-1008)
Open Mon. to Sat. 9-6, Thurs. 1 p.m.
Open all day Saturday

COMPONENTS AND EQUIPMENT

The largest range in the country, 8/6 buys 200-page catalogue with discount vouchers (see back page)

GARRARD DECKS—BRAND NEW FULLY GUARANTEED

1000 mono	£5 19 6	SP25 stereo	£10 19 6	401 less cart./arm	£27 10 0
AT5 mono	£6 9 6	SP25 Deram	£13 19 6	AT6 mono Mk. II	£8 19 6
2000 mono	£6 9 6	AT60 less cart.	£10 19 6	AT6 stereo Mk. II	£9 10 0
2000 stereo	£6 19 6	AT60 mono	£11 10 0	AT6 Deram	£11 19 0
3000 1 m stereo	£7 19 6	AT60 stereo	£11 10 0	Deccadec Mk. II	£17 17 0
SP25 less cart.	£9 19 6	AT60 Deram	£14 19 6	A70 less cart.	£17 17 0
SP25 mono	£10 10 0	LA680 less cart.	£25 0 0		

(P. and P. 5/- any type)
All other makes of decks and cartridge in stock

RADIO CONTROL RECEIVER

"TINYTONE" 27 mc/s band receiver. Printed circuit construction. Sensitive 4-transistor design. Size only 2in. x 2in. x 1/2in. Complete with circuit and Instructions. TOTAL COST 55/- P.P. TO BUILD 1/6 (Circuit etc. 1/3 separately).

REGENT-6 MW/LW

POCKET RADIO TO BUILD 6-Transistor superhet. Geared tuning. Push-pull speaker output. Moulded cabinet 5 x 3 x 1 1/2 ins. Phone socket. TOTAL COST 69/6 P.P. TO BUILD 2/-

MULTIMETERS/SCOPE

PT34	1kV 39/6	EP30k 30kV	£6.10.0
TP10	2kV 75/-	EP50k 50kV	£9.19.6
TT1-2	20kV 69/6	500 30kV	£8.17.6
		TP55 20kV	£5.19.6

CT 52 Scales £22.10.0. P.P. 10/-
Complete range of test equipment in stock

NOMBREX TEST UNITS

★ 150 kc/s—350 mc/s RF Generator £10.10.0. All Transistor.
★ 10 c/s—100 kc/s Transistor. £16.19.6 Audio Generator.

MW/LW QUALITY TRANSISTOR RADIO TUNER

Fully tunable superhet with excellent sensitivity and selectivity. Output up to 1/2 volt peak. Complete with front panel, etc. 9 volt operated. For use with any amplifier or tape recorder. TOTAL COST £3.19.6 P.P. TO BUILD 2/6

VHF FM TUNER

Supplied as 2 Preassembled Panels, plus metal work Superhet design. 88-108 Mc/s. 9 volt operated. 6 Mullard Transistors. Total cost to assemble £12.17.6, p.p. 2/6

STABILISED POWER SUPPLY

Two outputs. 3.6 volt and 9.6 volt up to 250mA each. Transistorised and Zener stabilised. 110 to 250 volt mains input in case with leads. PRICE 67/6, p.p. 2/6.

5 WATT AMPLIFIER


6-Transistor Push-pull, 3 ohms. 6mV into 1k. 12-18V supply, 2 1/2 x 2 x 1 1/2 in.

BUILT AND TESTED 69/6 P.P.

(optional mains units 54/-) 2/- 1 1/2 watt version 59/6. Matching Preamplifier, 6 inputs, treble/bass selector/volume controls. 6-10mV o/p. 9-18V supply. 79/6, p.p. 2/-.
For use with any Transistor Amplifier.

GARRARD BATTERY 2-SPEED TAPE DECK

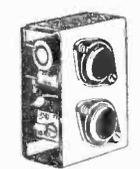Brand New with R/P head. erase/esc. head, tape cassette. Specifications and osc. circuits. 2 speed 2-track 9 volt operated. List Price 13 gns. P. & P. PRICE £8.19.6 3/6



NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5	5/-	DL92	4/3	EL41	8/-	PY81	5/-
1R5	3/9	DL94	5/6	EL94	4/3	PY82	4/9
1T4	2/9	DL96	5/11	PY61	5/11	PY83	5/3
8E4	4/3	DY86	5/6	EY86	5/3	PY800	5/9
5V4	7/6	DY87	5/6	EZ40	6/-	PY801	5/11
5V4G	5/9	EABCO80	5/6	EZ80	4/3	R19	6/8
6F1	6/3	EAFA2	7/6	EZ81	4/6	U26	9/3
6L18	6/-	EBC41	7/9	OZ22	3/9	U26	8/9
10C2	11/3	EBF80	5/9	KT61	6/3	U191	10/-
10P1	9/6	EBF89	5/9	N78	14/6	U301	11/6
10P13	8/3	ECC81	3/3	PC97	5/9	U801	16/-
20P2	10/3	ECC82	4/3	PC900	8/-	UABCO80	5/11
20P1	8/9	ECC83	4/3	PC884	5/3	UAFA2	6/11
20P4	12/6	ECC85	5/3	PC889	9/9	UBC41	6/8
30F5	9/9	ECH35	5/9	PC189	8/3	UBF89	5/9
30P4	11/6	ECH42	8/9	PCF80	6/3	UCC84	7/9
30P19	11/6	ECH81	5/-	PCF82	5/9	UCC85	6/-
DAC82	6/9	ECH84	7/9	PCL82	6/3	UCP80	8/-
DAP91	3/9	ECL40	5/9	PCL83	9/3	UCH42	8/8
DAP96	5/11	ECL82	6/-	PCL84	7/-	UCH81	5/9
DF33	2/9	ECL86	7/6	PCL85	8/3	UCL82	6/9
DF91	2/9	EP39	3/6	PL36	9/-	UCL83	8/6
DF96	5/11	EP41	5/9	PL81	6/3	UF41	7/9
DK32	7/-	EP80	4/3	PL82	6/9	UF89	5/6
DK31	5/-	EP85	5/-	PL83	5/11	UL41	7/9
DK96	6/3	EP88	6/-	PL84	6/-	UL84	6/-
DL33	4/9	EP89	4/9	PY32	8/3	UY41	4/3
DL35	4/9	EL33	6/3	YV33	8/3	UY85	5/9

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON N.16

PLEASE MENTION
"PRACTICAL WIRELESS"
WHEN REPLYING TO
ADVERTISEMENTS

NEW RANGE U.H.F. AERIALS FOR BBC 2 (625) line transmissions

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 35/-; 11 element, 42/6; 14 element, 50/-; 18 element, 57/6; Wall Mounting with Cranked Arm, 7 element, 60/-; 11 element, 67/-; 14 element, 75/-; 18 element, 82/6; Mast Mounting with 2in. clamp, 7 element, 42/6; 11 element, 55/-; 14 element, 62/-; 18 element, 70/-; Chimney Mounting Arrays, Complete, 7 element, 72/6; 11 element, 80/-; 14 element, 87/6; 18 element, 95/-; Complete assembly instructions with every unit.
Low Loss Cable, 1/8 vd. U.H.F. Preamps. from 75/-; State clearly channel number required on all orders.

BBC · ITV · F.M. AERIALS

BBC (Band 1). Telescopic loft, 21/-; External S/D, 30/-; "H" £2.10.0.
ITV (Band 3). 3 element loft array, 25/-; 5 element, 35/-; Wall mounting, 3 element, 35/-; 5 element, 45/-.
Combined BBC/ITV. Loft 1+3, 41/3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3.
VHF transistor pre-amps. 75/-.


F.M. (Band 2). Loft S/D, 12/6; "H", 30/-; 3 element, 52/6. External units available. Co-ax cable, 8d. vd. Co-ax plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & P. 5/-; Send 6d. stamps for illustrated lists.

Quotations for special arrays available on request

K.V.A. ELECTRONICS (Dept. P.W.)
27 Central Parade, New Addington
Surrey CRO OJB
LODGE HILL 2266

H.A.C. SHORT-WAVE KITS

NEW RELEASE: MODEL "DX"

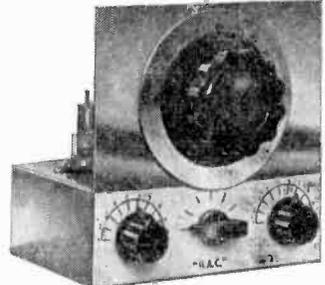

Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1967 RANGE

One-valve model "DX", complete kit—price 58/6 (Postage and packing 3/6).

Customers say: "Definitely the best one-valve S.W. Kit available at any price." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form,

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

Head Office and Warehouse
 44A WESTBOURNE GROVE
 LONDON W2
 Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
 85 TOTTENHAM COURT ROAD
 LONDON W1
 Tel. LANGHAM 8403
 Open all day Saturday

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling
 MINIMUM CHARGE 2/- No G.O.D. orders accepted

0A2	8/	6AG7	6/	6F9G	8/	10F3	8/
0A3	10/	6AH6	10/	6F8G	5/	10P9	10/
0B2	6/	6AK5	5/	6F7	5/	10F18	9/
0C3	6/	6AL5	3/	6F8G	5/	10L1	7/
0D3	6/	6AM6	4/	6F11	6/	10P13	15/
0Z3A	5/	6AN8	10/	6F12	4/	10P14	15/
1A3	4/	6AQ4	5/	6F13	6/	11D5	7/
1A5GT	5/	6AC5	5/	6F14	15/	11D5	7/
1A7GT	8/	6AR5	6/	6F15	11/	12AC6	8/
1B3GT	8/	6AR6	6/	6F17	6/	12AD6	6/
1C5GT	5/	6AR8	17/	6F18	7/	12AE6	7/
1D6	8/	6AB5	5/	6F23	10/	12A15	7/
1D8GT	6/	6AB6	6/	6F24	12/	12AQ5	7/
1G4GT	8/	6A87G	15/	6F25	12/	12AT6	5/
1G6GT	7/	6AT6	4/	6F28	10/	12AT7	4/
1H5GT	7/	6AUE	5/	6G8	10/	12AD6	6/
1N5GT	11/	6A8U	9/	6J4	9/	12A17	5/
1R4	8/	6AV6GTA	4/	6J6	3/	12AV6	5/
1R6	6/	6AV6	5/	6J7G	5/	12AV7	5/
1R4	5/	6AW8A12/8	6/	6K6G	6/	12AX7	6/
1R5	4/	6B4G	17/	6K7GT	5/	12AY7	10/
1T4	3/	6B8	7/	6K8	8/	12BA4	9/
1T5GT	8/	6B9	6/	6K9	4/	12BA6	6/
1U4	5/	6B8G	2/	6L6G	7/	12BB6	5/
1U5	6/	6BA7	5/	6L7	5/	12BB5	5/
1V2	10/	6BE6	4/	6L17	9/	12BV7	10/
1X2B	7/	6BFA	16/	6L18	6/	12C8	4/
2C34	7/	6BF7	15/	6LD20	5/	12E1	20/
2C51	10/	6B8A	7/	6N7GT	4/	12K7GT	7/
2CWC4	12/	6B3E	7/	6P28	12/	12K5	8/
2D21	6/	6BK4	22/	6Q64	15/	12Q7G	4/
2E26	22/	6BK7A	9/	6Q7	7/	12M7	4/
3A4	4/	6B17GTA	4/	6RAZ	4/	12NC7	4/
3A5	7/	6B17GTA	4/	6R7	9/	12NC7	4/
3A6	6/	6BNG	7/	6R5	7/	12RH7	4/
3B28	4/	6BQ7A	7/	6R7	7/	12RH7	4/
3D6	4/	6BR7	11/	6R8	7/	12R7	4/
3D9	2/	6BR8	5/	6R9	7/	12R7	4/
3E29	6/	6BR7	11/	6R8	7/	12R7	4/
3Q4	7/	6BWW	7/	6R7	7/	12R7	4/
3Q5GT	6/	6BWK	10/	6L7GT	8/	1487	18/
3R4	5/	6BZ6	6/	6N7GT	5/	20D1	9/
3Y4	8/	6BZ7	11/	6R7	7/	20P2	13/
4A5A	100/	6C4	3/	6R8	7/	20L1	13/
4B32	3/	6C6G	10/	6R8	7/	20P1	12/
4E27	6/	6C5GT	7/	6R8	7/	20P3	12/
4T8A	6/	6G6	4/	6R8A	9/	20P4	13/
4T8P	6/	6C9	11/	6VGT	6/	90C1	12/
4X150A	100/	6C31	12/	6X4	4/	90C2	25/
5R4GY	9/	6C86	5/	6Y5GT	5/	90C3	25/
5T4GB	6/	6C6G	10/	6Y6G	9/	11T7	30/
5U8	8/	6C1H	6/	7B7	7/	150B2	10/
5V4G	8/	6C1G	9/	7B8	8/	30C1	6/
5Y3GT	5/	6C16	11/	7C5	5/	30C15	11/
5Z3	7/	6C14	12/	7C6	6/	31A	35/
6A2G	7/	6C15	9/	7C7	5/	30C18	11/
6/30L2	8/	6C17	11/	7H7	8/	30F5	10/
6A8	8/	6D4	15/	787	22/	30F11	14/
6AB4	6/	6D6	3/	7Y4	8/	30F12	19/
6AD7	4/	6DK6	8/	7Z4	6/	30F13	6/
6AC5GT	10/	6C18	11/	8W6	6/	30F14	13/
6AC7	4/	6EGT	8/	10C1	12/	30L1	5/
6AP4	10/	6EA8	11/	10C2	13/	30L15	15/
6AP6G	11/	6F1	14/	10D1	7/	30L17	15/
6AG5	2/	6F4	30/	10P1	9/	30P12	9/

First Quality Fully Guaranteed



ELECTRONIC VALVES

30P16	7/	367	5/	DF91	3/	ECC84	6/
30P18	6/	388A	4/	DF92	2/	ECC85	5/
30P19	13/	959	8/	DF96	7/	ECC86	7/
30P11	15/	991	7/	DH63	6/	ECC88	8/
30P13	15/	1267	20/	DH101	7/	ECC91	3/
30P14	15/	2050	12/	DK32	8/	ECC93	11/
35A5	10/	551	7/	DK40	11/	ECC94	10/
35A4	4/	564	8/	DK91	6/	ECC97	13/
35B5	12/	5670	10/	DK92	8/	ECC98	9/
35C5	6/	5749	10/	DK96	7/	ECC99	9/
35D5	12/	5751	13/	DL33	6/	ECC103	12/
35L6GT	6/	5763	10/	DL26	5/	ECC106	9/
35W4	4/	5814	10/	DL66	20/	ECC107	11/
35Z3	10/	5965	5/	DL68	10/	ECC108	11/
35Z4G	4/	6060	5/	DL69	12/	ECC109	11/
35Z4GT	8/	6086	25/	DL91	5/	ECC109	11/
35Z5GT	5/	6146	25/	DL92	5/	ECC109	11/
42	6/	6159	32/	DL93	4/	ECC109	11/
41U7	8/	6197	20/	DL94	6/	ECC109	11/
50A5	12/	6238	30/	DL95	7/	ECC109	11/
50R5	6/	6386	30/	DL96	7/	ECC109	11/
50C5	6/	6939	45/	DM70	5/	ECC109	11/
50C6GT	7/	7551	4/	DR30	8/	ECC109	11/
51L6GT	6/	7596	22/	YR66	6/	ECC109	11/
52KU	5/	7895	22/	EBOCC	12/	ECC109	11/
12817GT	7/	9002	5/	EBOCC	12/	ECC109	11/
58C9	45/	9003	9/	EM70	7/	ECC109	11/
75C1	13/	9065	15/	EBOCC	8/	ECC109	11/
80	9/	9182	20/	E190F	17/	ECC109	11/
83A1	12/	AC/HL/D	1/	E192C	23/	ECC109	11/
85A1	25/	DD10	10/	EAG0	3/	ECC109	11/
85A2	7/	AC/HL	1/	EAC80	6/	ECC109	11/
85A3	5/	AC/HL	1/	EAC81	6/	ECC109	11/
90A6	4/	AC/TH1	8/	EAF42	8/	ECC109	11/
90A9	4/	AC/VP215	1/	EBC31	7/	ECC109	11/
90C1	12/	AR	6/	EBC41	8/	ECC109	11/
90C2	25/	ARP12	3/	EBC81	6/	ECC109	11/
90C3	25/	ATP25	9/	EBC90	4/	ECC109	11/
11T7	30/	AW6	5/	EBC91	5/	ECC109	11/
150B2	10/	AZ11	6/	EBC98	7/	ECC109	11/
30C1	6/	AZ12	9/	EBF43	8/	ECC109	11/
30C15	11/	AZ21	9/	EBF89	7/	ECC109	11/
31A	35/	AZ41	7/	EEL31	30/	ECC109	11/
30C18	11/	CB131	15/	EC86	12/	ECC109	11/
807	9/	DA90	4/	EC88	11/	ECC109	11/
811	40/	DA32	7/	EC90	2/	ECC109	11/
815	35/	DAF40	10/	EC91	5/	ECC109	11/
825	20/	DAF91	4/	EC92	6/	ECC109	11/
837	17/	DAF92	6/	EC95	17/	ECC109	11/
866A	14/	DAF96	6/	EC94	9/	ECC109	11/
872A	40/	DC90	7/	EC97	10/	ECC109	11/
884	15/	DC90	7/	EC98	11/	ECC109	11/
885	3/	DF33	8/	EC98	5/	ECC109	11/
956	2/	DF64	5/	ECC83	6/	ECC109	11/

TRANSISTORS

OC16	25/	OC8DM	5/	ACV19	6/	GET113	5/
OC23	15/	OC8S	5/	ACV20	5/	GET114	4/
OC24	17/	OC8A	5/	ACV21	6/	GET115	8/
OC25	9/	OC122	14/	ACV22	5/	GET116	12/
OC26	8/	OC139	8/	AD140	18/	GET875	9/
OC28	12/	OC140	10/	AD149	16/	GET880	12/
OC29	14/	OC170	6/	AF102	18/	MAT101	8/
OC35	12/	OC171	6/	AF114	8/	MAT120	7/
OC36	12/	OC176	6/	AF115	7/	MAT121	8/
OC42	5/	OC200	7/	AF116	7/	T1166	6/
OC43	9/	OC201	7/	AF117	6/	V30/30P20/	5/
OC44	5/	OC202	13/	AF118	14/	25309	5/
OC45	4/	OC203	10/	AF124	9/	26371A	5/
OC79	5/	OC204	10/	AF125	8/	26381	5/
OC71	5/	OC205	15/	AF126	8/	2N697	13/
OC72	5/	OC206	22/	AF127	8/	2N1134	37/
OC73	6/	OC107	10/	AF211	17/	29802	20/
OC75	6/	AC126	6/	AF212	12/	28003	20/
OC76	6/	AC127	6/	ASV26	6/	28004	20/
OC77	8/	AC128	8/	ASV28	6/	28005	20/
OC78	8/	AC176	7/	ASV29	6/	28006	20/
OC78D	5/	AC177	8/	ASZ21	15/	28012	140/
OC81M	5/	AC178	5/	GET1103	5/	28018	60/

SiC SILICON JUNCTION RECTIFIERS, HALF WAVE 3 AMPS D.C.

RS330	420 piv, 6/	RS390	840 piv, 9/
RS340	560 piv, 7/	RS400	960 piv, 9/
RS350	700 piv, 7/	RS380	1120 piv, 10/

TEXAS SILICON FULL-WAVE BRIDGE RECTIFIERS

1B90K10 100 piv, 2 amps, dimensions 1.4 x 1.4 x .6in. 25/-
 1B40K10 100 piv, 4 amps, dimensions 1.4 x 1.4 x .6in. 30/-
 1B100M10 100 piv, 10 amps, dimensions 2.1 x 2.1 x .1in. 35/-
 Postage 1/6 per rectifier.

MULTIMETERS

TYPE MF 15
 A.C. and D.C. voltage ranges:
 0.10-50-250-500-1000V.
 D.C. current ranges:
 500µA-10-100mA.
 Resistance ranges: 100Ω-1MΩ.
 The meter is also calibrated for Inductance (10-1000H), capacity (0.01µF) and output level measurements. Sensitivity 2000Ω/V. Accuracy ±2.5% for D.C. and ±4% for A.C. measurements.

Dimension: 5 1/2 x 3 1/2 x 1 1/2 in. Price £23.30.
 Type 108-T. 14 range precision portable meter. 5000 o.p.v. D.C. Volts: 2.5-10-50-250-500-2500V. A.C. Volts: 10-50-100-250-500-2500V. D.C. current 0.5-5-50-500mA Resistance 2000-20,000 ohms; 2-20 megohms. Power output calibration in A.C. for 500 ohms line. Complete with prods and batteries, £25.50. P. & P. 5/-.

Our new price list of Valves, Tubes and Semiconductor is now ready. In addition to listing prices of some 2,300 types it is a useful reference work giving: Valve and Tube Equivalents, Specification of Microwave Tubes, Cathode Ray Tubes and Semiconductors. Send S.A.E. (foolscap) now to get your copy free of charge.

WE REQUIRE KLYSTRONS

TYPE 723A/B and 2K25

Also Valves

4C35 5C22 and 8/3

30/- paid subject to test

HEADPHONES

DLR5. Low Impedance, balanced armature. Earpieces can be used as sound powered microphone, 10/-.
 No. 10 Assembly. Moving Coil Headphones with moving coil Hand Microphone fitted with press-to-talk switch. Rubber earpads. Cord terminated with army type 5-point moulded connector. Low impedance. Brand new, 20/- ea. Small quantity available if second hand assemblies, checked, in perfect order. 8/6 ea. P. & P. 3/6 per set.

CATHODE RAY TUBES

DGT-5	55/-	09J	80/-	48P31	200/-
DGT-6	80/-	3CP1	40/-	5B1P1	80/-
VCR138	50/-	4CP4	100/-	6CP1	40/-
VCR139A	30/-	4SP7	200/-	5UP7	80/-
09D	80/-	48P11	200/-	90EG4P	180/-

The following blueprints are available from stock. Descriptive text is not available but the date of issue is shown for each blueprint. Send, preferably, a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

The Strand Amplifier }	(Oct. 1962) 5/-	The Celeste 7-transistor Portable Radio }	(June 1963) 5/-
The PW Signal Generator }		The Spinette Record Player }	
The Berkeley Loudspeaker Enclosure }	(Dec. 1962) 5/-	Transistor Radio Mains Unit }	(June 1964) 5/-
The Luxembourg Tuner }		7 Mc/s Transceiver }	
The PW Troubadour }	(June 1962) 7/6	The Citizen (December 1961) }	5/-
The PW Everest Tuner }		The Mini-amp (November 1961) }	5/-
The PW Britannic Two }	(May 1962) 6/-	The Beginner's Short Wave Superhet (Dec. 1964)	5/-
The PW Mercury Six }		The Empire 7 Three-band Receiver (May 1965) ..	5/-
Beginner's Short Wave Two S.W. Listener's Guide }	(Nov. 1963) 5/-	Electronic Hawaiian Guitar (June 1965) }	5/-
PW "Sixteen" Multirange Meter }	(Jan. 1964) 5/-	Progressive SW Superhet (February 1966) }	5/-
Test Meter Applications Chart }		Beginners' 5-Band Receiver }	(Dec. 1966) 5/-
		Home Intercom Unit }	

★ PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL RADIO, TV OR AUDIO EQUIPMENT. ★

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 9th June, 1967 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, JUNE 1967

NEW SOLID STATE HIGH FIDELITY EQUIPMENT ★★★


IMPROVED PERFORMANCE · NEW STYLING · NEW MODELS · MONO & STEREO



MPA12+12
MPA25
MPA12/3
and
MPA12/15



MP3

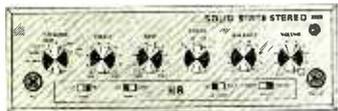

MPA12+12

MP3. Mono Preamplifier. All silicon low noise gener stabilised circuit. Full range of controls—fully equalised inputs for Xtal P.I., DW/Xtal Mic, Radio Tuners, Tape Head and Preamp Replay. Supplied built and tested, on metal chassis, complete with front Grey/Silver panel, Aluminium Knobs and Handhook. Output 250mV. Supply 12 to 60 volts, 3mA. Overall size 9 1/2 x 1 1/2 x 1 1/2. **MP3 Price £6.19.6, p.p. 3/-.**

SP6-2. Mono/Stereo Preamplifier. Uses 8 Silicon/Germanium devices, Zener stabilised. Completely new low noise design. Full range of controls and filters. Inputs for Magnetic/Xtal/Ceramic Cartridges, Radio Tuners, Tape Preamp., microphones, Tape Head, etc. Record output socket. Supplied built and tested on metal chassis with Grey/Silver front panel and matching knobs. Complete with Input Sockets and Handhook. Output 250mV per channel. Supply 9 to 60 volts 4mA. Overall size 12 x 3 1/2 x 3 1/2. **SP6-2 Price £14.19.6, p.p. 6/-.**

SP4. Mono/Stereo Preamplifier, as previously advertised. Complete with Front Panel and Knobs. Size 9 x 3 1/2 x 1 1/2. **SP4 Price £10.19.6, p.p. 3/-.**

MPA12/3 and MPA12/15. 12 watt Power Amplifiers for use with above preamplifiers. Improved response and performance with even lower distortion levels. MPA12/3 for 3 to 5 ohm speakers, 24/28 volt supply. MPA12/15 for 10 to 16 ohm speakers, 40/45 volt supply. Uses 8 silicon and germanium devices. Inputs 100mV for 12 wts. Response $\pm 1\pm 30$ c/s to 20 kc/s. THD 0.2% at 12 watts. High gain stable push-pull output designs. Built on to metal chassis as illustrated. Overall size 5 x 2 x 3 1/2 ins. Complete with handbook. **MPA12/3 Price £4.10.0, p.p. 2/6. MPA12/15 Price £5.5.0, p.p. 2/6.**

MPA12+12. Twin Amplifier for Mono/Stereo use with above preamplifiers. Consists of two matched MPA12/15 amplifiers—see above—on single chassis. Output for 10 to 16 ohm speakers. 40/45 volt supply. Overall size 10 x 2 x 3 1/2. **MPA12+12 Price £8.19.6, p.p. 4/-.**

MPA25. 25 watt Power Amplifier for use with above preamplifiers. New design and layout with improved response and overall performance. Output for 7 1/2 to 15 ohm speaker systems. Input 180mV for full output. Push-pull circuit uses 10 silicon and germanium devices. Supply 50/60 volts. Overall size 8 x 2 x 3 1/2. **MPA25 Price £7.10.0, p.p. 3/6.**

Choice of PREAMPLIFIER POWER AMPLIFIERS MAINS UNITS

MAINS UNITS.
110/240 volt 40/60 c/s input. AC/DC fused. Fully smoothed and isolated. Mu series has additional choke/capacitors filtering and panel voltage selectors. All types on metal chassis.
PS24/40. Output 24 and 45 volts 1 amp. for use with 1 or 2 MPA12/3, MPA12/15, or (1) MPA12+12. **Price 70/- p.p. 3/-.**
MU24/40. Choke smoothed. Output 24 and 45 volts 1 amp. for use with 1 or 2 MPA12/3 and MPA12/15 or (1) MPA12+12. **Price 87/6 p.p. 3/6.**
MU60. Choke smoothed. Output 50 volts 1 amp. for use with 1 or 2 MPA25. **Price 85/- p.p. 4/-.**

RECOMMENDED SYSTEMS	
MP3 + MPA12/15 + PS40	£14.12.6 p.p. 6/6
MP3 + MPA12/3 + PS24	£13.17.6 p.p. 6/6
MP3 + MPA25 + MU60	£13.5.0 p.p. 8/-
SP6-2 + (MPA12+12) + MU40 (or (2) MA12/15)	£28.5/6 p.p. 10/-
SP6-2 + (2) MPA12/3 + MU24	£28.15.0 p.p. 10/-
SP6-2 + (2) MPA25 + MU60	£33.5.0 p.p. 10/6
SP4 + (2) MPA12/15 + PS40	£24.0.0 p.p. 9/-
SP4 + (2) MPA12/3 + PS24	£22.15.0 p.p. 9/-
MP3 + (2) MPA12/15 + MU40	£20.17.6 p.p. 8/-
MP3 + (2) MPA12/3 + MU24	£19.7.6 p.p. 8/-


COMPLETE BROCHURE FREE ON REQUEST

THE FINEST VALUE IN HIGH FIDELITY — FULLY GUARANTEED CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

'EXPLORER' (PW Jan 1967) All parts (less chassis) 79/6 P.P. 2/6.
MULTI-BAND RX (PW April 1967). All parts £9.9.0. P.P. 4/-. Parts Lists on request.



NEW SCOOP CAR RADIO!

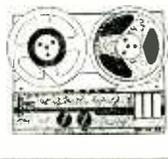

WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION.
OR BETTER STILL—BUY THE NEW 1967 CATALOGUE. EVERYTHING YOU NEED IS LISTED AND AVAILABLE FROM STOCK.

GLOBEMASTER MW/LW/SW PORTABLE RADIO TO BUILD
Full 3-waveband tuning. Pushbutton wave-change. Superhet printed circuit design. Black-chromed cabinet 11 x 7 1/2 x 3 1/2 in. (SW 17-50 metres). Ear/Record sockets. 1 watt Push/Pull output. 6 Mullard Transistors.
Handbook **TOTAL COST £7.19.6** P.P. on request **TOTAL BUILD 3/6**

TOURMASTER TRANSISTOR CAR RADIO—BRITISH MADE
7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wave-change. RF stage. Supplied built, boxed, ready to use with Speaker and Battery. Car fixing kit and manufacturers' current guarantee. Special Bargain Offer. Buy Now!
LIST PRICE 15 GNS. £7.19.6 P.P. Push button version **4/6** £11.19.6. P.P. 4/6.

BRITISH MADE STEREO TAPE PLAYER FOR CARS 32 gns.
Mono version 26 gns. also F.M. Med. wave/Low wave Car Radio 25 gns.

VHF FM TUNER TO BUILD LEAFLET ON REQUEST
87/105 Mc/s Transistor Superhet. Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3 1/2 x 2 1/2 in. Complete with dial plate. 5 Mullard Transistors plus 4 Diodes. (Cabinet Assembly 20/- extra).
TOTAL COST £6.19.6 P.P. **TO BUILD 2/6**

FM STEREO DECODER
7 Mullard Transistors. Printed Circuit Design with Stereo Indicator. For use with any valve or transistor FM. Uses pot cores to Mullard design and ger. and silicon transistors. Leaflet on request. As used by BBC and ITV.
£5.19.6 P.P. 2/- Complete Kit Price

BUILD A QUALITY 2 OR 4 TRACK TAPE RECORDER
3-speed version using '383' decks
● TWO-TRACK. Deck £10.10.0. Martin Amplifier. £14.19.6. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 1200ft. tape, spare spool. **27 gns.** P.P. Today's Value 24s.
● FOUR-TRACK. Deck £13.10.0. Martin Amplifier £15.19.6. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 200ft. tape, spare spool. **30 gns.** P.P. Today's Value 25s.

DEAO RECHARGEABLE BATTERY
● 9.6 volt 225mA/H 20/-, P.P. 1/6
DEAC CHARGER
To charge 9.6 volt and 9.6 volt packs. Fully mains isolated **45/-** P.P. in moulded case. 2/-
ALL ITEMS FULLY GUARANTEED

MAYFAIR PORTABLE ELECTRONIC ORGAN

Now available as
● Complete kit of parts
● Built and tested
● Prebuilt assemblies
Reverberation unit and recommended speakers and amplifiers in stock



Designed by L. W. Roche
Straightforward to build and tune—easy to play—fully guaranteed. All parts available separately—astounding value and performance.
● Plug-in printed circuits ● 170 transistors and devices ● 10 selected tone colours ● Fully sprung keyboard ● Vibrato ● 6 Octaves of generators ● Simple locked-in tuning ● 110/250 volt mains unit ● Cabinet size 30 1/2" x 15 1/2" x 9" ● Weight 35 lb. Cabinet with detachable legs, music stand and foot swell pedal ● Fully detailed building manual with photos, drawings and full circuits. **START BUILDING FOR AS LITTLE AS £5.**

COMPLETE RANGE OF ORGAN PARTS IN STOCK. FULLY DETAILED LEAFLET AND PRICE LIST ON REQUEST
H.P. FACILITIES AVAILABLE. TRADE/EXPORT SUPPLIED. Call for demonstration and play the Mayfair

RELAYS—MOTORS—SWITCHES—MINIATURE TRANSISTORS AND DEVICES
Complete range in stock all types for every purpose. Also panel and multi-meters, precision components, radio control crystals and parts, transistors, tuner diodes, thyristors, triacs, zeners, rectifiers and diodes. Everything you need for amateur and professional applications—see 1967 catalogue. The largest range in the country. Suppliers of quality components and equipment for over 20 years.

HR
LISTS AVAILABLE
(Incorporated in full catalogue)
● Transistors/Rectifiers/Scrs/Valves/
● Crystals/Zeners etc. 24 pages 1/-.
● 4 page Hi-Fi free stock list with discounts. All popular makes.
TUNNEL DIODES 1mA 22/6; 5mA 15/-; 15mA 12/6. Brand new at fraction of normal price. Free Specs. supplied.
HENRY'S RADIO LTD.
303 EDGWARE RD., LONDON W.2
PA Dington 1008/9 (ST1101-725 1008)
Open Mon. to Sat. 9-6, Thurs. 1 p.m.
Open all day Saturday

1967 CATALOGUE
Have you a copy? Fully detailed and illustrated. Over 200 pages of components, equipment, etc. Over 5000 stock items. Fully detailed and illustrated. PRICE 8/6, post paid. Five free discount vouchers, value 10/-, with every catalogue.
200 PAGES—PLUS!



SEE PAGE 159 FOR FURTHER RANGE OF STOCK ITEMS