

# PRACTICAL WIRELESS

DECEMBER  
1968


310

Special  
inside

**AUDIO SUPPLEMENT—No. 3**

**Servicing & Workshop Practice**

**5 STAGE MINI 3 RECEIVER**

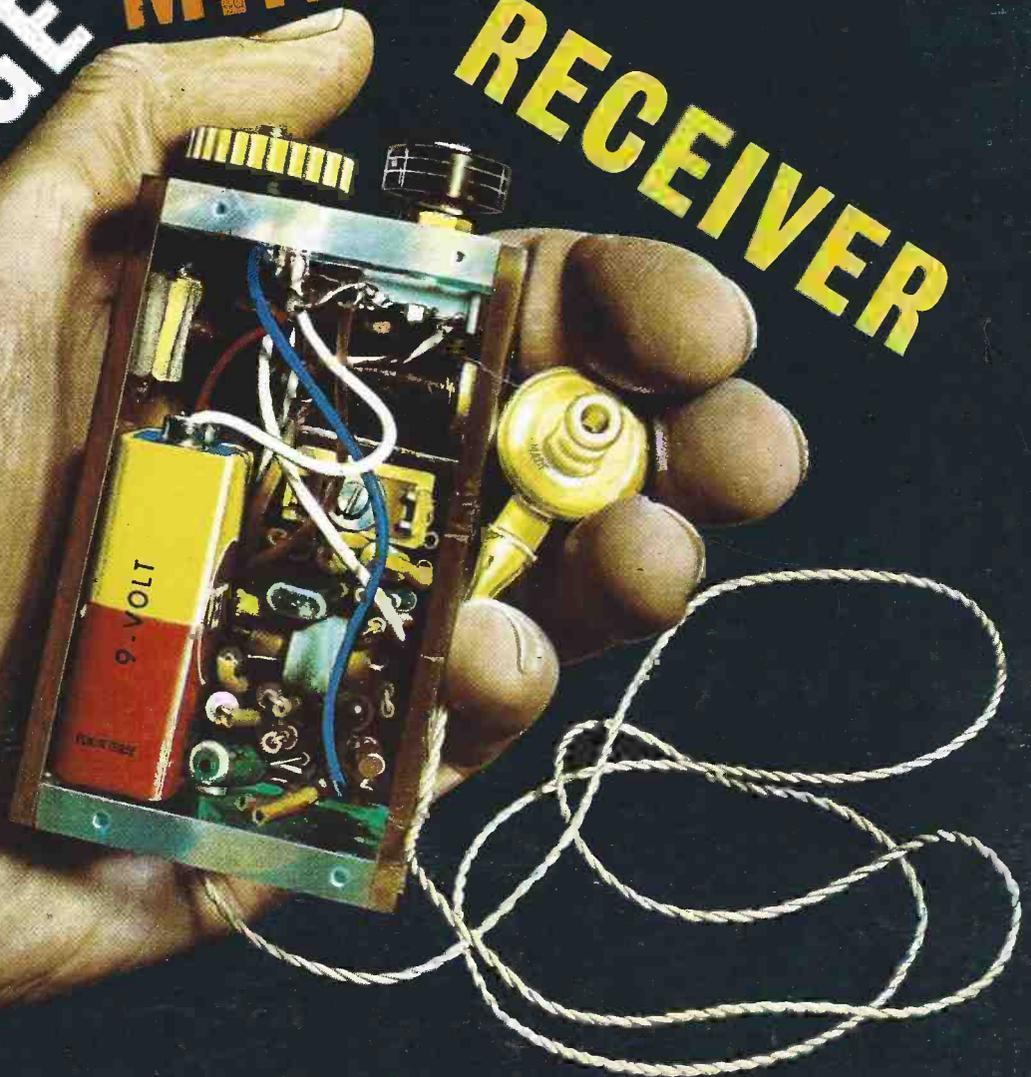

# ADCOLA

SOLDERING  
EQUIPMENT

## THE PEAK OF EFFICIENCY!



ILLUSTRATED

Model 64.  $\frac{3}{16}$ " Bit  
25 WATTS PRICE 36/-

**WIDELY USED BY INDUSTRY &  
THE DISCERNING ENTHUSIAST FOR RADIO,  
T.V. & PRINTED CIRCUIT WORK**

FROM YOUR LOCAL DEALER  
OR SEND DIRECT TO:-

**ADCOLA PRODUCTS LTD.,  
ADCOLA HOUSE,  
GAUDEN ROAD,  
LONDON. S.W.4.  
TELEPHONE 01-622-0291**

Send coupon for latest leaflet


Name	_____
Address	_____
	_____
	_____

# Lasky's Radio

## SPEAKERS
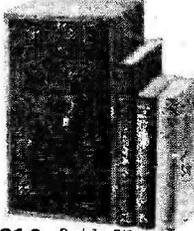
### FOSTER CRITERION HI-FI BOOKSHELF SPEAKER SYSTEM

This extremely high quality bookshelf speaker system by the world famous Foster Co. of Japan incorporates an acoustical suspension woofer and cone tweeter in a sealed infinite baffle enclosure with handsome oiled walnut finish. The performance of the Criterion is superior to many larger and far more expensive units and at Lasky's special purchase price is quite without equal. SPECIFICATION: Air suspension type 6 1/2 in. bass-midrange woofer with rolled cloth edge. 2 1/2 in. HF cone type tweeter. Frequency range 65-20,000c/s. Maximum power handling 15W. 8Ω impedance. Cabinet constructed from 3/4 in. laminate with oiled walnut veneer finish; size 13 1/2 x 7 1/2 in. square. Dark green woven acoustic gauze. Phono input at rear. List Price £12.10.0 each.




Lasky's Price £8.8.0 or 2 for £16 Post 1-7/6 2-12/6

## TEST EQUIPMENT
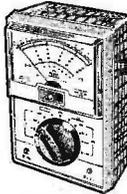
### TTC Model C-1000


A really tiny 1,000 O.P.V. pocket multi-tester with "big" meter performance. Precision 2 jewel meter movement. Hand calibrated to ±3% accuracy on full scale of d.c. ranges, 4% on a.c. ranges. 2 1/2 in. square meter. SPECIFICATIONS a.c./V ranges: 0-10, 50, 250, 1,000V at 1K/0. P.V. a.c./V ranges: 0-10, 50, 250, 100V at 1K/0. P.V. D.c. current: 0-1-100mA. Resistance: 0-100K/ohms (3,000 ohms centre scale). Decibels: -10 to +22dB. Operated on one penlight cell. Two colour buff/green case—size only 3 1/4 x 2 1/4 in. Click stop range selection switch. Ohms zero adjustment. Complete with test leads, battery and instructions with circuit data.



Lasky's Price 39/6 Post 2/6
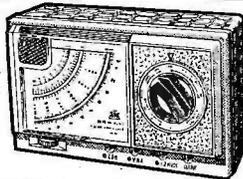
### TTC Model C-1051

A completely new design 20,000 O.P.V. pocket multimeter with mirror scale and built in thermal protection circuit. Exceptionally large easy to read meter with D'Aronval movement. Colour coded scales. Single positive click-in, recessed selection switch for all ranges. Ohms zero adjustment. Range spec AC volts: 0-5-30-300-1200 V at 10K/ohms/V DC volts: 0-3-15-150-300-1-2KV at 20K/ohms/V. Resistance: 0-60K-6megs. DC current: 0-60μA-300mA. Decibels: -20dB to +17dB. Hand calibration gives extremely high standard of accuracy on all ranges. Uses one 1 1/2 V penlight battery. Strong impact resistant plastic cabinet—size only 4 1/2 x 3 1/2 x 1 1/2 in. Two colour buff/green finish. Complete with test leads and battery. Original list price £5.5



Lasky's Price 75/- Post 2/6

## PHOTO ELECTRIC RELAY



TTC MODEL Q4001 Photo Relay System comprising "exciter" lamp and relay unit. Any interception of the light beam instantly triggers the relay which in turn will operate light, alarm bell or buzzer, electronic counter, heavy duty relay or electric motor. Many useful applications in the home, office, shop, factory, etc. Operates on 240V. A.C.; exciter lamp 12V. 20W. effective up to 15ft. in daylight or 50ft. at night. Very simple to install. In strong metal cases size (each) 6 x 4 1/2 x 3 1/2 in. Complete with mounting brackets wire and instructions.



Lasky's Price £7.19.6. Post 5/-

## NEW INTERNATIONAL TAPE

FAMOUS AMERICAN MADE BRAND TAPE AT RECORD LOW PRICES


3in. Message tape, 150ft. ....	2 8	5 1/2 in. Standard play, 850ft. PVC	11 6
3in. Message tape, 225ft. ....	3 9	5 1/2 in. Long play, 1200ft. Mylar	15 0
3in. Message tape, 300ft. ....	6 6	6 5/8 in. Triple play, 2400ft. Mylar	45 0
3 1/2 in. Triple play, 600ft. Mylar	10 6	7 in. Standard play, 1200ft. Acetate	12 6
4in. Triple play, 900ft. Mylar	17 8	7 in. Standard play, 1200ft. Mylar	12 6
5in. Double play, 1200ft. Mylar	15 0	7 in. Long play, 1800ft. Mylar	19 6
5in. Long play, 900ft. Acetate	10 0	7 in. Double play, 2400ft. Mylar	25 0
5in. Standard play, 600ft. PVC	8 6	7 in. Long play, 1800ft. Acetate	15 0
5in. Triple play, 1800ft. Mylar	35 0	7 in. Triple play, 3600ft. Mylar	50 0
6 1/2 in. Double play, 1800ft. Mylar	22 6		
6 1/2 in. Long play, 1200ft. Acetate	12 6		

P. & P. 1/- extra per reel. 4 reels and over Post Free. Special quotes for quantities.

## SPECIAL INTEREST ITEMS!
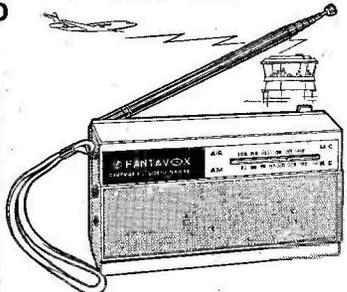
### NEW LASKY'S EXCLUSIVES FANTAVOX MODEL TV-1008 VHF AIRCRAFT BAND AND AM RECEIVER

The first pocket size Receiver of its type allowing you to "tune-in" anywhere to the entire air-to-ground, ground-to-air communications band covered by 108-137Mc/s in addition to all AM medium wave band cover of 535-1600Kc/s. An extremely sensitive 10-transistor and 2 diode, superhet circuit plus 1 variable capacitor and 1 thermister. Intermediate frequencies: AM-455 Kc/s; VHF-10.7Mc/s. Output power: 200mW. 2 1/2 in. Permanent Dynamic 8 ohm speaker, earphone also provided for "silent" listening. A built-in ferrite rod aerial is provided for AM reception and a fully directional telescopic antenna for VHF reception—the latter when collapsed neatly clips across the top of the set. Power is from 4-1.5V penlight cells and a Jack socket for connection to a suitable AC converter is also provided. The Model TV-1008 is extremely well made and finished in grey plastic with metallic blue speaker grille, chrome telescopic antenna; attached wrist strap is also provided. Size 6 1/2 x 3 1/2 x 1 1/2 in. Complete with batteries, magnetic earphone, instructions and circuit data.



Lasky's Price £11.10.0 P. & P. 5/-


### MIDLAND Model 10-502 VHF AIRCRAFT BAND CONVERTER

An entirely new item for the radio enthusiast bringing instant reception of the ground-to-air, air-to-ground waveband. For use with any standard AM or FM radio covering 535 to 1605Kc/s, 88 to 108Mc/s respectively—with an electrical conversion or connection required. The Model 10-502 (self powered by one 9V (PP3 type) battery) is merely placed close to the receiving set and then tuned over 110 to 136Mc/s which covers the whole aircraft communications band. Volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the vol. controls of each accordingly. The Model 10-502 has a smartly designed black plastic cabinet with brushed metal front panel and 1 1/2 in. chrome telescopic antenna, size only 4 x 2 1/2 x 2 1/2 in. (inc. knobs). Complete with battery and full instructions.



Lasky's Price 79/6 Post 3/6

## REMOTE CONTROL SWITCHING SYSTEM

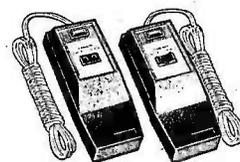

An extremely compact, simple to use and install remote switching system for use with a wide range of mains operated equipment. High frequency signal from the transmitter is relayed to the remote switching unit via the AC mains circuit in which the units are plugged—providing instant on/off—off/on control of appliance. Spec.: 3 transistor and 1 diode circuit. Frequency 190Kc/s (pre-set). Power 220/240V AC, 30/60c/s. Max. power of equip. to be switched—300W plastic cabinets size: 6 1/2 x 2 1/2 x 1 1/2 in., each with neon indicator lamp. Comp. with flex and instructions.

Lasky's Price £7.19.6 Post 5/-

## STEREO MOVING MAGNET CARTRIDGE Model AD-76K

Lasky's are first again with this new high compliance moving magnet stereo cartridge that really breaks the quality/price barrier. The performance of this cartridge is equal to others costing many 2's more and will bring out all the subtleties of the finest microgroove recordings and is suitable for use with all the latest high sensitivity amplifiers. SPECIFICATION: Diamond Stereo LP stylus. Compliance 10 x 10<sup>-6</sup> cm/dyne. Frequency response 20-20,000c/s. Channel separation 20dB. Output 7mV. Tracking pressure 2 grammes ±0.5grm. Standard 1/4 in. mounting. Total length (inc. pins) 1 1/2 in. Replacement Diamond stylus available. Fully guaranteed.



Lasky's Price 85/- Post 2/-

### Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271  
Open all day Saturday, early closing 1 p.m. Thursday

33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605  
Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel.: FLEet St. 2833  
Open all day Thursday, early closing 1 p.m. Saturday

### High Fidelity Audio Centres

42 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573  
Open all day Thursday, early closing 1 p.m. Saturday

118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789  
Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

## SPEAKER SYSTEMS



**THE CAXTON COLUMN**  
This is a column cabinet. Size 22½ x 5 x 6½ in., fitted with 3 speakers. This will handle 10 watts and will improve the quality of any tape recorder, or record player. Finished in wood grain cloth and sandstone Vynair. A real bargain at 59/6. P. & P. 10/6.



**THE IMP.** Extension Speaker Cabinet. Wedge shaped, size 7½ x 6½ in., fitted 7 x 4 in. speaker. Covered with attractive walnut with fawn Vynair front. Keyhole slot in back. Only 25/6. P. & P. 4/6




**DUO.** Wedge shaped Speaker Cabinet. Size 7½ x 7½ in., fitted 7 x 4 in. speaker. Covered in attractive two tone Vynair. Price 32/6. P. & P. 4/6.




**CLARENCE.** Extension Speaker Cabinet fitted 8 x 5 in. speaker. (3 ohms imp.) and volume control. Size 10½ x 8½ x 4½ in. Finished in black and grey Vynair. 45/-. P. & P. 4/6.

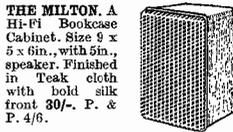
All cabinets are new and speakers are mounted on ½ in. chipboard baffles. All speakers are TV tested and hi flux magnet. All carefully tested before despatch.



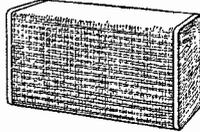**THE MILTON.** A Hi-Fi Bookcase Cabinet. Size 9 x 5 x 6 in., with 5 in. speaker. Finished in Teak cloth with bold silk front 30/-. P. & P. 4/6.




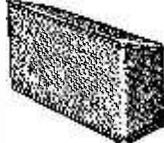**THE STEREO.** A superior extension speaker cabinet fitted with two 7 x 4 in. speakers. Size 16 x 9 x 8½ in. Finished in fawn Vynair with natural/teak ends. 23. P. & P. 5/-.



**THE SCOTT.** Table top or wall mounting speaker. Size 16½ x 10½ x 5½ in., tapered as illustrated. Fitted 13 x 8 in. speaker with volume control. Finished in teak cloth and contrasting Vynair. (Please state 3 or 15 ohm imp.) £4.5.0. P. & P. 7/6.

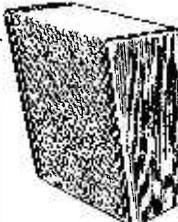with volume control. Finished in teak cloth and contrasting Vynair. (Please state 3 or 15 ohm imp.) £4.5.0. P. & P. 7/6.




**The Tennyson.** Wedge shape for table or wall mounting for 13½ x 16 x 8½ in. Cut out for 13½ x 8 in. speaker with port. Finished wood grain cloth and matching Vynair. £2.2.6 P. & P. 7/6.


**The Vernon.** Table top or wall mounting enclosure for 13½ x 8 in. speaker (Similar to The Scott illus. above). 27/6. P. & P. 8/-.

**The Haydon.** 16½ x 15 x 7½ in., wood grain cloth and contrasting Vynair covered suitable for 12 in. speaker, 72/6. P. & P. 9/-.

## SPEAKER ENCLOSURES

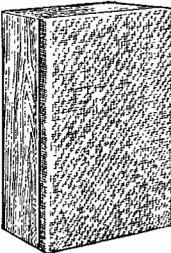

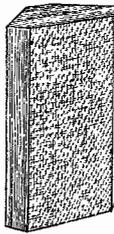**The Baker.** Size 8 x 15½ x 23½ in. Teak veneered top and sides. Fawn Vynair covered front. Cut out for 12 in. speaker and 8 in. tweeter with port and internal bass reflex board. Fitted rubber feet. £6.15.0. P. & P. 10/6.



**The Cowdrey.** Corner Cabinet in natural teak finish for 13½ x 8 in. speaker also cut out for tweeter, £3.15.0. P. & P. 8/6.

**SPEAKERS:** Elac Heavy duty Ceramic Magnets 11,000 line, 10 in. round, 10 x 6 in. 3 ohm, or 15 ohm, 43/6. P. & P. 3/6. 8 in. round 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I. 13½ x 8 in. 15 or 3 ohm 45/-. P. & P. 3/6. E.M.I. 8 in. tweeter, 15/-. P. & P. 1/6. E.M.I. 13½ x 8 in. fitted two 2 in. tweeters. 15 ohms, 77/6. P. & P. 4/6. E.M.I. 13½ x 8 in. (15 ohm) Hi Fi Quality, 45.19.6. P. & P. 4/6. E.M.I. Woofers, 8½ x 6½ in. square. 3 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 16/6. P. & P. 1/-. EAGLE Crossover units, 3 or 16 ohms, 14/6. P. & P. 1/-. Bakers 12 in., 25 watt, 15 ohm, £6.6.0. P. & P. 3/6. All other speakers supplied—Goodmans, Bakers, W.B., Wharfedale, Eagle, Tripletton.

**VYNAIR** Widths from 40 to 54 in., 16/6 yd. off roll. P. & P. 1/9. ¼ yard, 3/6. P. & P. 1/9. Send 1/- stamps for samples. **SPEAKER MATCHING TRANSFORMERS.** 3, 7, 15 ohms, 8 watt, 11/6. P. & P. 1/6.

**CARTRIDGE:** Reuter STD/2, 17/6. GPP1/1, 20/-. Mono Sonotone, 2TSS, 15/-. Acos GP67/2 high output, 18/6. P. & P. 1/-.

**MICROPHONES:** Xtal Hand Mikes. B1201 with stand, 54/6. P. & P. 3/6. ACOS Mike 46, 21/-. ACOS Mike 40, 19/6. Dyn. Mike DM-391, 40/-. CM21 Xtal, 12/6. Telephone Pick-up, 10/6. P. & P. 1/-. Xtal lapel Mike, 7/6. Guitar Mike, 12/6. P. & P. 1/-.

**TRANSISTOR ELECTROLYTICS:** 1, 2, 4, 5, 8, 10, 16, 25, 32, 50, 100 mfd 15 volt working, 1/3. P. & P. 1/-. 250 mfd DC, 3/-, 500 mfd 12v, 3/-. 500 mfd 25v DC, 3/6. P. & P. 1/-.

**EARPIECES WITH CORD** and 3-5 mm. plug. 3 ohm magnetic, 3/-. 250 ohm, 4/-. 180 ohm with clip, 6/6. Xtal. P. & P. 6d.

**TRANSISTOR SPEAKERS** 3 ohm 2 in., 3/6. 8 in., 10/6. 8 in., 12/6. P. & P. 1/-.

**FERROX RODS:** 6 x ½ in., 9/6; 4½ x ½ in., 2/-; 6 x ½ in., 2/6; 8 x ½ in., 3/-. P. & P. 1/-. each.

**FERROX RODS WITH COILS.** 4½ x ½ in., 3/6; 8 x ½ in., 5/6; P. & P. 1/-. each.

**ROTARY SWITCHES:** 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/6 each. P. & P. 1/-.

**PIANO KEY PUSH BUTTON SWITCHES,** 7 button inc. mains on off. 6 banks of 6 P.C.O., 8/6. P. & P. 1/-.

**SIEMENS CONTACT COOLED RECTIFIERS,** 250v. 350mA., 4/8. P. & P. 1/-.


**VACUUM CLEANER LEAD.** 7½ yds. twin cable with moulded 5 amp. two pin plug. 4/6. P. & P. 1/6.

# JACKSON

the big name in PRECISION components  
MINIATURE TUNING CAPACITORS

The Jackson 'O' range contains six basic types of different air-dielectric tuning capacitors with a wide variation of capacities available in each type. In addition, there are optional extras such as concentric-spindle slow-motion drives, built-in trimmers and plastic covers. The maximum capacitance per section ranges from 12, 18 or 24 pF for FM types to 420 pF for AM types.

TYPE "OO"

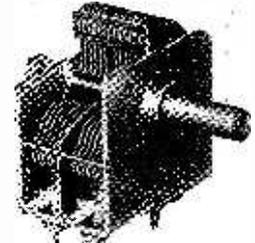

- ★ Type OO miniature twin capacitor at 12/6 each
- ★ Type OFM two-gang for FM at 12/9 each
- ★ Type O two-gang for AM at 12/9 each

Write for literature

**JACKSON BROS. (LONDON) LTD.** (Dept. P.W.)  
KINGSWAY-WADDON, CROYDON, CR9 4DG  
Phone Croydon 2754-5 (01-688) Grams: Walfilco, Croydon  
U.S. Office:—M. SWEDGAL  
258 Broadway, New York. N.Y. 10007

## TELEVISION BARGAINS

Due to Bulk Purchase we offer Ex Rental 12 channel T.V.s. Well maintained and tested. Tubes 100% guaranteed. Slimline 17" Peto Scott 732, Ultra V17/70, Regentone 7en 17, Cosser 874, Alba T44, F.M. all £8.0.0. each. 21" Ultra V21/70 £12.0.0. Semi slim 17" Alba T655, Regentone 7en 4 7en 8, Sobell T178, T179, Bush TV85, £7.0.0. each.

Many others available, all worth double  
Carriage £1 Terms C.O.D., C.W.O.

We stock all spares for most pre-1962 T.V.s

Send S.A.E. for price list to:

**D. WEBB**


58 Chanterlands Avenue,  
Hull, Yorkshire.  
Tel: Hull 43281 and 36016

## BROADWAY Electronics

92 MITCHAM ROAD, TOOTING BROADWAY,  
LONDON, S.W.17 Telephone 01-672 3984 (Closed all day Wednesday)  
(Few minutes from Tooting Broadway Underground Station)
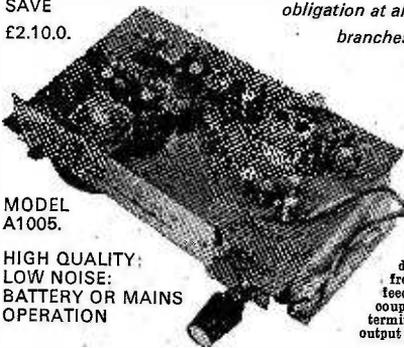
# Transistorised FM Tuner

CALLERS WELCOME Demonstration without obligation at all branches  
SAVE £2.10.0.



MODEL A1005.

HIGH QUALITY:  
LOW NOISE:  
BATTERY OR MAINS OPERATION

REDUCED PRICE DUE TO HUGE SALES

## STEREO DECODER

Model A1005M. Simple instructions to convert any FM tuner. Max input 100 m volts. Power supply 8-14 volts. Mains or batt. (5mA at 12V.) Output 1.5 x input. 4 transistors (2 each) 2SB-202; 2SB-186. 7 diodes IN34 (six) IN60 SAVE 34/- 5 Gns.

Keen offer if purchased with A1005 tuner making STEREO TUNER 11 gns.

This beautifully compact 6 transistor machine (size 6 x 4 x 2 1/2 in.) will give quieter, more interference free reception. Months of use from a standard 9 volt battery or its small power requirements can be drawn from any amplifier. Low noise freq. changer. Smooth 2 gang tuning feeding no less than three I.F. stages coupled to a double-tuned discriminator terminating in an L.F. stage giving ample output for all quality amplifiers.

£6.19.0  
(3 FOR £19)

### TRANSISTORS GUARANTEED TOP QUALITY

Mullard Matched Output Kits OC18D 12/6 and P-0051  
R.F. Kits OC44, OC45 (2) 3 transistors. 11/-

AF102	17/-	GET115	5/6	OC85	12/6
AF114	6/6	GET116	10/-	OC44	4/-
AF115	6/-	MAT121	3/6	OC45	3/6
AF116	6/6	OA5	3/-	OC71	4/-
AF117	5/-	OA10	6/-	OC72	5/-
AF127	6/-	OA79	2/6	OC73	7/6
AF186	16/-	OA81	2/6	OC74	7/6
BC107	7/6	OA90	2/6	OC81	5/-
BSY65	5/-	OA95	2/6	OC81D	4/6
FZA143	7/-	OA202	3/6	OC82D	5/-
GET111	3/6	OC19	18/6	OC170	5/6
GET113	4/-	OC29	6/-	OC171	6/-

SILICON RECTIFIERS  
Guaranteed performance. Top makes. Tested 250v. working.  
100mA 2/9 500mA (3 for 6/6) 5/- (3 for 12/6)

### BARGAIN PARCELS

Including variable condensers, i.f. coils, loudspeaker plug/socket, knobs, pots, condensers, resistors, nuts, bolts, cabinet fittings, switches, transformer chokes, rectifier, transistors at a small fraction of list value. Due to heavy demand we now pack them in several sizes—be amazed—try one now.

3 lbs. (post 3/-)	9/-
7 lbs. (post 5/-)	17/6
14 lbs. (post 6/-)	29/-



### FANTASTICALLY POPULAR TAPE

We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports TRY ONE AND PROVE IT YOURSELF.

Standard Play		Long Play	
3in. 150ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,500ft.	13/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,800ft.	25/-
5in. 1,200ft.	15/-	5 1/2in. 2,400ft.	34/-
5 1/2in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,400ft.	27/-	8in. Quadruple Play 600ft.	3/6

Postages 1/- each. Post Free less 5% on three reels. Quantity and Trade enquiries invited. NOTE. Large tape stocks at all branches.

### STEREO PORTABLE CABINETS

Latest black and silver metal finish. Consisting of centre cabinet size 16in. x 13in. x 5in. deep with lift up lid together with two 10 x 6 speaker cabinets which clip on ends of main cabinet size 4 1/2in. x 13in. x 5in. making overall size of 25 1/2in. x 13in. x 5in. High quality chrome fittings. Will take almost any autochanger or tape deck. Approx. half price at £3.19.0

### MONO PORTABLE CABINETS. B.S.R.

tape deck or single record player, new, attractive finish, hall price. 19/6

### AUTOCHANGE PORTABLE CABINETS.

As used on 18 gns. record player. Due to fortunate purchase we offer complete with motor board and all fittings 49/-

PLEASE NOTE. A wide range of cabinets to callers at all branches.

### 100 HI-STABS 9/-

1% to 5% 100Ω to 5MΩ.  
CO-AX. low loss. 6d. vd., 25 vds. 11/6; 50 vds. 22/-; 100 vds. 42/6. Plugs 1/3.

### 100 RESISTORS 6/6

SIZES—3 watt.  
MICROPHONE CABLE. Highest quality, black, grey, white, 9d. per yard.

### 100 CONDENSERS 9/6

Miniature Ceramic, Silver, Mica etc., 3pF to 5μF. LIST VALUE OVER 25.

### 25 ELECTROLYTICS 9/6

Assorted 2 to 500 mfd 6 to 400 volt. LIST VALUE OVER 25.

### 50 TAG STRIPS 7/6

Mixed sizes 2 to 15 way.

### 25 POTENTIOMETERS 9/6

Including with switch, long and short spindle, pre-sets, log and lin. unused. 1k-2MΩ.  
LIST VALUE APPROX. 24.

### CONNECTING WIRE 4/-

P.V.C. Bright Colours. Five 25ft. coils only.

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone, Linear, Rogers, Trivox, Ferrograph, Wharfedale, etc., etc.  
Post 1 lb. 1/6, 1 1/2 lb. 2/6, 2 lb. 2/9, 4 lb. 3/3, 6 lb. 4/-, 14 lb. 5/6.



# ★ GUARANTEED VALVES ★

BY RETURN OF POST—GUARANTEED 3 MONTHS

Satisfaction or Money Back Guarantee on goods if returned unused within 14 days  
ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED. FREE TRANSIT INSURANCE. POSTAGE 1 valve 9d. 2-11 6d. per valve. Free over 12

1L4	2/6	6E7GT	6/6	30FL1	14/-	EF89	7/6	EZ80	6/6	PZ20	8/6
1S4	2/6	6SL7GT	6/6	30L15	19/-	EC040	10/6	EZ81	7/-	SP61	4/6
2D21	6/-	6SN7GT	5/6	30L17	13/-	EC051	8/6	GZ32	10/-	TD14	8/6
3Q4	7/-	6U4GT	12/-	30P4	14/-	EC082	6/6	GZ34	10/-	UD14	18/6
504G	7/6	6V6G	5/-	30P12	12/-	EC083	6/6	KT61	13/-	U25	15/-
5Y3GT	6/6	6V6GT	7/6	30PL1	15/-	EC084	7/6	KT68	5/6	U26	16/-
5Z4G	7/6	6X4	4/6	30PL13	16/-	EC085	6/-	KT66	20/6	U35	13/6
5Z4GT	3/6	6X5G	5/6	30PL14	16/-	EC088	8/6	KTW61	6/9	U37	19/-
6/30L2	13/-	6K5GT	6/6	35A5	11/-	ECF30	8/6	KTW63	6/-	UI91	14/-
6AK5	5/6	7B6	11/6	35L6GT	3/6	ECF82	7/6	MU14	8/-	U981	8/6
6AQ5	6/-	7B7	7/6	35W4	5/6	ECH42	11/6	N37	10/6	U982	12/6
6AT6	5/6	7C5	16/-	35Z5	9/6	ECH31	7/-	N78	14/6	U301	13/6
6AU6	6/-	7C6	7/-	35Z4GT	8/6	ECL80	7/-	PC86	10/6	U404	7/6
6BA6	6/-	7H7	6/6	42	6/6	ECL82	7/6	PC88	10/6	U501	20/-
6BE6	6/-	7Y4	7/6	50L6GT	3/6	ECL83	10/6	PC97	8/6	UAC90	27/6
6BH6	7/6	10C1	9/-	80	8/6	ECL86	9/-	PC084	6/9	UAF49	9/6
6BJ6	7/6	10C2	12/-	185BTA20/6	6/6	EF39	7/-	PC085	7/-	UB41	9/6
6BR7	10/-	10F1	9/6	807	9/6	EF40	9/6	PC088	12/-	UBC41	9/6
6BR8	9/-	10F9	9/6	955	3/6	EF41	10/6	PC089	11/-	UBC81	9/6
6BW6	12/6	10L11	10/-	956	3/-	EF42	10/6	PC189	11/-	UBF80	7/6
6BW7	12/-	10P13	12/6	CL39	17/6	EF89	9/6	PCF82	6/6	UBF89	8/6
6C4	4/-	10P14	12/6	CY31	8/6	EF85	7/-	PCF83	6/6	UBL21	11/-
6C9	11/-	12A76	5/6	DAF91	5/-	EF86	8/6	PCF86	9/6	UC84	9/-
6F1	7/6	12A76	5/6	DAF96	7/6	EF89	7/-	PCF86	14/-	UCF90	9/6
6FG6	5/6	12A77	6/6	DF91	3/9	EF91	4/-	PCL82	7/9	UCH21	11/-
6F13	6/6	12A77	6/6	DF96	7/6	EF183	7/-	PCL83	9/9	UGH42	11/6
6F14	9/6	12BA6	5/6	DE91	6/6	EF184	7/-	PCL85	8/6	UCH31	7/6
6F15	9/6	12BE6	5/6	DL96	8/6	EL32	5/-	PCL86	9/6	UCL83	9/6
6F23	12/6	12J7GT	7/6	DK96	8/6	EL33	13/-	PCL86	9/6	UCL83	10/6
6F24	12/6	12K7GT	6/6	DL92	5/9	EL34	12/6	PL86	12/-	UF41	9/6
6F36	4/6	12K9GT	8/6	DL94	7/-	EL41	9/9	PL81	9/9	UF42	9/-
6J5GT	6/6	12Q7GT	6/6	DL96	8/6	EL42	10/6	PL82	7/6	UF80	8/6
6J7G	5/6	14S7	12/6	DM96	8/6	EL43	9/9	PL83	7/6	UF85	8/6
6J7GT	8/6	19A45	5/6	DY86	7/6	EL44	7/6	PL84	7/6	UF89	7/6
6K7G	3/6	20D1	9/-	DY87	7/6	EM80	7/6	PY31	7/6	UF89	7/6
6K7GT	5/6	20F2	9/6	EAB30	7/-	EM81	8/6	PY32	9/9	UL41	11/6
6K9GT	6/6	20L1	15/-	EB41	6/6	EM84	8/6	PY33	10/6	UL64	7/9
6L8	7/6	25L6GT	7/6	EB91	3/6	EM85	11/-	PY80	6/6	UM80	7/-
6LD20	7/6	25Z46	7/6	EB93	8/6	EM87	10/6	PY82	6/6	UT9	7/6
6P25	13/-	30C15	14/-	EB031	7/9	EY38	8/6	PY83	6/6	UY85	7/6
6Q7G	6/6	30G17	14/-	EBF80	7/6	EZ40	9/-	PY88	8/6	VR105	7/6
6Q7GT	8/9	30F5	14/-	EBF83	8/-	EZ41	9/-	PY800	9/-	VR150	7/6
								PY801	9/-	X86	7/6

## Tubes

HIGHEST QUALITY—COMPARE OUR PRICES

GUARANTEED

	6 Months	12 Months
MOST MULLARD.	12in. £2. 0.0	£3. 0.0
MAZDA, COSSOR.	14in. £2.10.0	£3.10.0
EMITRON, EMI.	15-17in. £3. 5.0	£4. 5.0
SCOPE, BRIMAR.	19in. £3. 5.0	£4. 5.0
FERRANTI TYPES PROCESSED IN OUR OWN FACTORY	21in. £3.15.0	£5.15.0
	23in. £3.15.0	£5.15.0

SATISFACTION GUARANTEED

NOTE: ALL TUBE ORDERS ONLY TO PORTSMOUTH BRANCH PLEASE

## JUST OUT — SEND NOW FOR FREE FLOG LIST No 3

Scores Special Bargains  
SEND S.A.E. OR CALL AT ANY BRANCH FOR YOURS

NAME .....

ADDRESS .....

Block Capitals Please .....PW12

CALLERS A very wide range of electronic components awaited you at all branches. Your enquiries welcomed.

LONDON 10 Tottenham Court Road, W.1. Tel. MUSeum 2639

PORTSMOUTH 350-352 Fratton Road. Tel. 22084


SOUTHAMPTON 72 East Street. Tel. 25851

BRIGHTON Park Crescent Place. Tel. 680722

All Mail Orders to Brighton with names and addresses in BLOCK CAPITALS please. (TV Tubes only Portsmouth).
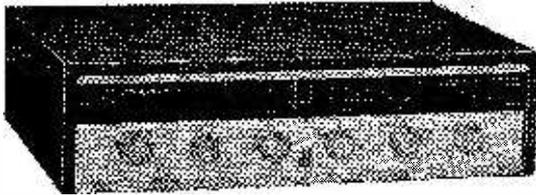
# Here's What's NEW from HEATHKIT in SOLID STATE RECEIVERS

AVAILABLE AS EASY TO BUILD KITS OR READY-TO-USE MODELS



Kit K/AR-14                      Ready to use A/AR-14  
**£54.0.0** P.P.                      **£75.0.0** P.P.  
 13/6                                      13/6  
 Cabinet £4.10.0. extra

## Top Value in a 30 Watt FM Stereo Receiver, AR-14

- 31 transistor, 10 diode circuit for cool, instant operation with the transparent, natural sound only transistors can deliver ●  $\pm 1$ dB, 15 to 50,000 Hz at 10 watts per channel continuous (20 watts total), 15 watts per channel IHF music power (30 watts total) ● Wide-band FM/FM stereo tuner plus two preamplifiers and two power amplifiers. ● Front panel stereo headphone jack. ● Compact—just  $3\frac{3}{8}$ " H x  $15\frac{1}{2}$ " W x 12" D. ● Custom install it in wall, your own cabinet, or use as a free standing unit. ● Build it in 20 hours.

Kit K/AR-14 (less cab.)                      kit **£54.0.0**, P.P. 13/6  
 A/AR-14 (less cab.)                      .. .. **£75.0.0**, P.P. 13/6  
 Cabinet extra: Teak or Walnut finish **£4.10.0**




Kit K/AR-17                      Ready to use A/AR-17  
**£39.0.0** P.P.                      **£59.0.0** P.P.  
 10/6                                      10/6  
 Cabinet £3.10.0. extra
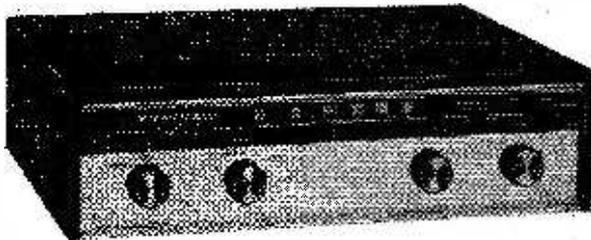
## Unbeatable Value in a 14 Watt FM Stereo Receiver, AR-17

- 28 transistor, 7 diode circuit for natural transparent sound, instant operation, long trouble-free life. ● 14 watts music power, 10 watts RMS from 25–35,000 Hz at  $\pm 1$ dB. ● Automatic stereo indicator light. ● Adjustable phase control for maximum separation. ● Complete front panel controls. ● Flywheel tuning. ● All critical circuits including FM "front-end" factory assembled and aligned. ● Circuit board assembly. ● Compact  $10\frac{3}{8}$ " D x 3" H x 12" W. ● Front panel stereo headphone jack.

Kit K/AR-14 (less cab.)                      .. kit **£39.0.0**, P.P. 13/6  
 A/AR-14 (less cab.)                      .. .. **£59.0.0**, P.P. 13/6  
 Cabinet extra: Teak or Walnut finish **£3.10.0**




Kit K/AR-27                      Ready to use A/AR-27  
**£22.10.0** P.P.                      **£32.0.0** P.P.  
 10/6                                      10/6  
 Cabinet £3.10.0 extra
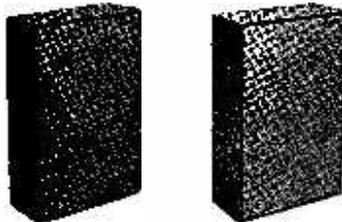
## A Quality Table Radio FM Mono Receiver, AR-27

- 13 transistor, 6 diode circuit for high-fidelity sound reproduction, long life, low heat, freedom from hum, and service-free operation. ● 7 watts music power. ●  $\pm 1$ dB, 25 to 60,000 Hz at 5 watts. ● Input connectors for phonograph and auxiliary signals. ● Complete front panel controls. ● Flywheel tuning. ● Preassembled and prealigned FM tuner, all other critical parts factory aligned. ● Easy, circuit board assembly. ● Compact bookshelf size. ● 3-way installation ... wall, free standing or in a suitable cabinet. ● 117 v. A.C. or 210/240 v. A.C., 50 Hz operation.

Kit K/AR-27 (less cab.)                      .. kit **£22.10.0**, P.P. 10/6  
 A/AR-27 (less cab.)                      .. .. **£32.0.0**, P.P. 10/6  
 Cabinet extra: Teak or Walnut finish **£3.10.0**



### BERKELEY LOUDSPEAKER SYSTEM

Use two for stereo. Best performance from a slim-line cabinet. Uses less than 1 sq. ft. of floor space. Available in Teak or Walnut finish.

Kit                                      Ready to use  
**£21.4.0** P.P.                      **£24.0.0** P.P.  
 13/6                                      13/6

CHOOSE A QUALITY  
 HEATHKIT LOUD-  
 SPEAKER SYSTEM  
 TO GET THE BEST  
 FROM YOUR AUDIO  
 SET-UP.



See how easy it is to build any Heathkit model. Purchase a manual only. British manuals 10/- each. American manuals £1 each incl. P.P. Price of manual deductible from kit if you buy later.

Showrooms: LONDON, Tottenham Ct. Rd. BIRMINGHAM, St. Martins Hse. GLOUCESTER Bristol Rd.

# HEATHKIT Models for Family Entertainment

OFFERS THE BEST IN SPECIFICATION AT LOWEST COST

## Latest STEREO TAPE RECORDER, STR-1

Fully portable—own speakers

Kit K/STR-1  
£58.0.0. P.P. 10/6

Ready-to-Use A/STR-1  
£72.0.0. P.P. 10/6

FOR THIS SPECIFICATION

$\frac{1}{2}$  track stereo or mono record and playback at  $7\frac{1}{2}$ ,  $3\frac{3}{4}$  and  $1\frac{5}{8}$ ips. Sound-on-sound and sound-with-sound capabilities. Stereo record, stereo playback, mono record and playback on either

channel. 18 transistor circuit for cool, instant and dependable operation. Moving coil record level indicator. Digital counter with thumbwheel zero reset. Stereo microphone and auxiliary inputs and controls, speaker/headphone and external amplifier outputs . . . front panel mounted for easy access. Push-button controls for operational modes. Built-in stereo power amplifier giving 4 watts rms per channel. Two high efficiency 8 x 5in. speakers. Operates on 230V a.c. supply.

Versatile recording facilities. So easy to build—so easy to use.

## Latest STEREO AMPLIFIER, TSA-12

12 x 12 watts output.  
Kit K/TSA-12  
£32.16.0. less cabinet. P.P. 10/6  
Cabinet £3.16.0. extra  
Ready-to-Use A/TSA-12  
£39.10.0. P.P. 10/6

FOR THIS SPECIFICATION

17 transistors, 6 diode  $\pm$  circuit. 1dB, 16 to 50,000 Hz at 12 watts per channel into 8 ohms. Output suitable for 8 or 15 ohm loudspeakers. 3 stereo inputs for Gram, Radio and Aux. Modern low silhouette styling. Attractive aluminium, golden anodised front panel. Handsome assembled and finished walnut veneered cabinet available. Matches Heathkit models TFM-1 and AFM-2 transistor tuners.

Full range power . . . over extremely wide frequency range. Special transformerless output circuitry. Adequately heat-sinked power transistors for cool operation—long life, 6 position source switch.

## RADIOS for Luxury Listening

### "OXFORD" PORTABLE UXR-2

This De-Luxe, 7 transistor, 3 diode portable radio covers long and medium wavebands with an easy-tune dial and uses battery-saving circuitry to ensure longer life and more hours of listening pleasure. Choice of Brown or Black real leather case.

Kit K/UXR-2 £15.10.0. P.P. 6/-  
Ready-to-Use A/UXR-2 £17.10.0. P.P. 6/-

### PORTABLE UXR-1

This luxury 6-transistor, 1 diode receiver covers long and medium wavebands. Its robust case is now available in real brown leather or choice of colours: Navy blue, coral pink, lime green (please state second choice).

Kit K/UXR-1 £12.8.0. colour case. P.P. 4/6  
Ready-to-Use A/UXR-1 £14.8.0. P.P. 4/6  
Kit K/UXR-1 £13.8.0. real leather. P.P. 4/6  
Ready-to-Use A/UXR-1 £15.10.0. P.P. 4/6


## Latest Portable Stereo Record Player, SRP-1

Automatic playing of 16, 33, 45 and 78 rpm records. All transistor—cool instant operation. Dual LP/78 stylus. Plays mono or stereo records. Suitcase portability. Detachable speaker enclosure for best stereo effect. Two 8in. x 5in. special loudspeakers. For 220-250V ac mains operation. Overall cabinet size  $15\frac{1}{8}$  x  $3\frac{3}{4}$  x  $10\frac{1}{2}$ in.

Compact, economical stereo and mono record playing for the whole family—plays anything from the Beatles to Bartok. All solid-state circuitry gives room filling volume.

Kit K/SRP-1 £28.6.0 incl. P.T. Ready-to-Use A/SRP-1 £35.4.0. P.P. 10/6

## High-performance CAR RADIO, CR-1

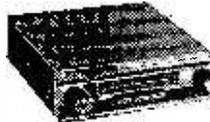

Superb long and medium wave entertainment wherever you drive. Complete your motoring pleasure with this compact outstanding unit.

8 Latest semi-conductors (6 transistors, 2 diodes). For 12 volt positive or 12 volt negative earth systems. Powerful output (4 watts). Pre-assembled and aligned tuning unit. Push-button tone and wave change controls. Positive manual tuning. Easy circuit board assembly.

Instant operation, no warm-up time. Tastefully styled to harmonise with any car colour scheme. High quality output stage will operate two loudspeakers if desired. Can be built for a total price.

Kit K/CR-1 (incl. speaker) £14.12.0. incl. P.T. P.P. 4/6  
Ready-to-Use A/CR-1 (incl. speaker) £19.12.0. incl. P.T. P.P. 4/6

## 'Mohican' General Coverage Receiver, GC-1U

Powerful 10 transistor, 5 diode circuit. Tunes 580 to 1550 kHz and 1.69 to 30 MHz in five bands. Bandspread on all bands. Fixed-aligned ceramic IF transistors for best selectivity. Pre-assembled and aligned 'front-end' for fast, easy assembly. Built-in 6 x 4in. speaker. Tuning meter for pin-point tuning. Completely self-contained for portability—can be operated on 230 volt AC with Model K/UBE-1. Kit £2.17.6. extra.

Kit K/GC-1U £38.8.0. Ready-to-Use A/GC-1U £46.8.0. P.P. 10/6

### OTHER MODELS FOR SW LISTENERS

Gen. Cov. Receiver RG-1 Kit	.. .. .	£39.16.0. P.P. 9/-
SW Receiver GR-64 Kit	.. .. .	£22.8.0. P.P. 9/-
SW Receiver GR-54 Kit	.. .. .	£50.2.0. P.P. 9/-



Oxford



UXR-1



**FREE!**

**CATALOGUE**

Describes 11 new and many more kits and components available for Stereo/All in One, the Beatles Record Players, The Airman, Amateur Radio, Sport, Motor, Test, Laboratory, Home and Hobby uses, comes with Heathkit money order coupon. Write to: DAYSTROM LTD., Gloucester, Tel. 29451

DAYSTROM LTD., Dept. PW12  
GLOUCESTER Tel. 29451

Enclosed is £ \_\_\_\_\_, plus packing and carriage.

Please send model (s) \_\_\_\_\_

Please send FREE Heathkit Catalogue.

Name \_\_\_\_\_ (Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_


Prices and specifications subject to change without notice.




<b>DULCI HI-FI AMP.</b> STEREO 7w X 7w MODEL 207 Usual price £19.19.0 Our big discount price <b>15½ guineas</b> plus 10/- p/p.	<b>RECORD PLAYER AMP.</b> As fitted to most popular record players. Our Bargain Price <b>59/6</b> only. Fully built and tested. EL84 output. 230-240V mains operated. 2 controls—vol.,—tone on flying lead. P/p. 3/6.	<b>"SOLENT"</b> Scandinavian style speaker system (teak). Full maker's guarantee. 12 watt output. Imp. 8-15 ohms. Woofer 6½" 10,000 gauss. Tweeter 3½" Frequency response 40 c/s- 20Kc/s. LIST PRICE 18 Gns. <b>OUR PRICE 11 GNS.</b> +10/- p/p.	<b>SONOTONE</b> 9TA-HC diamond 50/- plus 2/6 p/p.	● <b>BARGAIN—Speakers, Hi-Fi—The Baker Selhurst</b> Stalwart, 12in. round, 15 watt rating, 12,000 lines gauss, 3 or 15 ohms, response 40-13,000c/s. Bass resonance 40-50c/s, solid aluminium chassis. <b>Our price £4.19.6.</b> Brand new, 12 months' unconditional guarantee. P.P. 6/6. ● <b>BARGAIN—Speakers, Hi-Fi—The Baker Selhurst</b> Guitar Group 25, 12in. round, 25 watt rating, 12,000 lines gauss, 15 ohms, response 30-10,000c/s, solid aluminium chassis, heavy duty cone. <b>Our price £4.19.6.</b> Brand new, 12 months' unconditional guarantee. P.P. 6/6.																																	
<b>BARGAIN—CHANGER DECKS AT LOWEST PRICES EVER</b> <table border="1"> <tr> <td>Plinth WB1</td> <td>GARRARD 1025</td> <td>p/p. 7/6</td> <td><b>£8. 0.0</b></td> </tr> <tr> <td><b>£2.15.0</b></td> <td>GARRARD 2025</td> <td>p/p. 7/6</td> <td><b>£8.10.0</b></td> </tr> <tr> <td>Cover SPC1</td> <td>AT60 Mk. II</td> <td>p/p. 8/6</td> <td><b>£13. 0.0</b></td> </tr> <tr> <td><b>£2.15.0</b></td> <td>SP25 Mk. II</td> <td>p/p. 8/6</td> <td><b>£12.10.0</b></td> </tr> <tr> <td></td> <td>BSR UA25</td> <td>p/p. 7/6</td> <td><b>£6.15.0</b></td> </tr> </table>		Plinth WB1	GARRARD 1025	p/p. 7/6	<b>£8. 0.0</b>	<b>£2.15.0</b>	GARRARD 2025	p/p. 7/6	<b>£8.10.0</b>	Cover SPC1	AT60 Mk. II	p/p. 8/6	<b>£13. 0.0</b>	<b>£2.15.0</b>	SP25 Mk. II	p/p. 8/6	<b>£12.10.0</b>		BSR UA25	p/p. 7/6	<b>£6.15.0</b>	<b>BUDGET HI-FI SYSTEM</b> <b>YOU WON'T FIND A BETTER BARGAIN—ANYWHERE!</b> TELETON F2000 STEREO (MULTIPLEX) C AM-FM TUNER AMP. <b>£35.8.11</b> O <b>OUR PRICE</b> TELETON S1003 SPEAKER M ENCLOSURES (PAIR) <b>£9.13.6</b> L <b>59 GNS.</b> GARRARD SP25, SONOTONE 9TA, DIAM. P PLINTH TO MATCH <b>£22.1.4</b> E <b>FREE</b> TOTAL <b>£67.3.9</b> T <b>DELIVERY</b>															
Plinth WB1	GARRARD 1025	p/p. 7/6	<b>£8. 0.0</b>																																		
<b>£2.15.0</b>	GARRARD 2025	p/p. 7/6	<b>£8.10.0</b>																																		
Cover SPC1	AT60 Mk. II	p/p. 8/6	<b>£13. 0.0</b>																																		
<b>£2.15.0</b>	SP25 Mk. II	p/p. 8/6	<b>£12.10.0</b>																																		
	BSR UA25	p/p. 7/6	<b>£6.15.0</b>																																		
<b>EMI HI-FI SPEAKERS</b> 13 x 8in. <b>47/6</b> , p/p. 5/-, 13 x 8in. plus 2 twr. <b>57/6</b> , p/p. 7/6. 8 x 5in., 7 x 4in. <b>22/6</b> , p/p. 3/6. Catalogue, full spec. on request. Distributors for EMI Sound.	Beautiful oiled teak enclosure to suit EMI 13 x 8in. speakers. Retail value £8.15.0. Our low-low price <b>ONLY 99/6</b> plus 8/- p/p.	<b>FULL EAGLE RANGE TUNER UNITS,          AMPLIFIERS, MICROPHONES, SPEAKERS,          ACCESSORIES, etc. All less 15%.</b>																																			
<b>INTERNATIONAL MAGNETIC TAPE</b> <table border="1"> <thead> <tr> <th></th> <th>Standard</th> <th>Long Play</th> <th>Double Play</th> </tr> </thead> <tbody> <tr> <td>5"</td> <td>600ft. 10/-</td> <td>900ft. 13/6</td> <td>1200ft. 17/-</td> </tr> <tr> <td>5½"</td> <td>900ft. 13/6</td> <td>1200ft. 16/6</td> <td>1800ft. 21/-</td> </tr> <tr> <td>7"</td> <td>1200ft. 15/-</td> <td>1800ft. 17/6</td> <td>2400ft. 26/-</td> </tr> </tbody> </table>				Standard	Long Play	Double Play	5"	600ft. 10/-	900ft. 13/6	1200ft. 17/-	5½"	900ft. 13/6	1200ft. 16/6	1800ft. 21/-	7"	1200ft. 15/-	1800ft. 17/6	2400ft. 26/-	<b>BASF TAPE 33½ OFF</b> <table border="1"> <thead> <tr> <th></th> <th>Standard</th> <th>Long Play</th> <th>Double Play</th> </tr> </thead> <tbody> <tr> <td>5"</td> <td>600ft. 12/6</td> <td>900ft. 17/-</td> <td>1200ft. 27/6</td> </tr> <tr> <td>5½"</td> <td>900ft. 17/-</td> <td>1200ft. 21/6</td> <td>1800ft. 36/-</td> </tr> <tr> <td>7"</td> <td>1200ft. 21/6</td> <td>1800ft. 33/-</td> <td>2400ft. 52/6</td> </tr> </tbody> </table>				Standard	Long Play	Double Play	5"	600ft. 12/6	900ft. 17/-	1200ft. 27/6	5½"	900ft. 17/-	1200ft. 21/6	1800ft. 36/-	7"	1200ft. 21/6	1800ft. 33/-	2400ft. 52/6
	Standard	Long Play	Double Play																																		
5"	600ft. 10/-	900ft. 13/6	1200ft. 17/-																																		
5½"	900ft. 13/6	1200ft. 16/6	1800ft. 21/-																																		
7"	1200ft. 15/-	1800ft. 17/6	2400ft. 26/-																																		
	Standard	Long Play	Double Play																																		
5"	600ft. 12/6	900ft. 17/-	1200ft. 27/6																																		
5½"	900ft. 17/-	1200ft. 21/6	1800ft. 36/-																																		
7"	1200ft. 21/6	1800ft. 33/-	2400ft. 52/6																																		
POST & PACKING 2/-, OVER £5 FREE			<i>Thank you for reading our advertisement.</i>																																		
<b>S.B.E. Atlas House, Chorley Old Road, Bolton</b>				<b>BOLTON</b> <b>25881</b>																																	
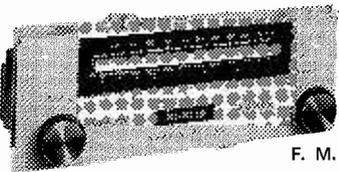
# MARTIN IS HIGH-FIDELITY

*The first and still the most satisfactory unit assembly system*



F. M. TUNER

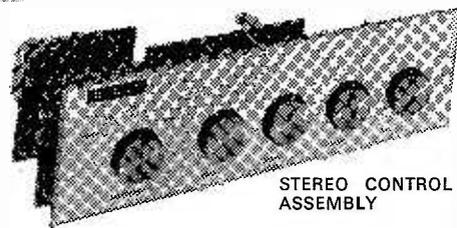

STEREO CONTROL ASSEMBLY

For many years now Martin Electronics have been producing highly efficient and dependable prefabricated module-type units for simple assembly into reasonably priced high fidelity systems. Many purchased at the time of the introduction of the Martin Audiokit system are in regular use to this day, completely justifying our claims for years of trouble-free service. No system gives you wider flexibility in the choice of units available than Martin and all equipment conforms precisely to stated specification. When new units

are introduced, they are designed for adding to those produced so far, making it easy and economical to extend and improve your existing Martin Audiokit set-up. Anyone can assemble Martin equipment with ease and the foreknowledge that when finished, he will be in possession of a true hi-fi assembly of the very best kind which looks and sounds completely professional in every way—and MARTIN AUDIOKITS remain as ever, the units that have true add-on ability.

## AMPLIFIER SYSTEMS • TUNERS • RECORDERS

**MARTIN HIGH-FIDELITY AUDIOKITS** cover the widest possible range of requirements. They are available for Mono, and can be doubled up for conversion to stereo, or as complete stereo units. 3 ohm and 15 ohm systems. Special pre-amp for low output pick-ups—escutcheon panels to suit the arrangement you choose. Tuner is styled to match.

- UNITS INCLUDE:
- 5-stage input selector
  - Pre-amp tone controls
  - 10 watt amp. (3 ohms)
  - 10 watt amp. (15 ohms)
  - Mains power supply
  - F.M. Tuner

**MARTIN ELECTRONICS**

154 High Street, Brentford, Middlesex  
 Please send Audiokit Hi-Fi/F.M. Tuner/Record-  
 akits Leaflets. (Strike out items not wanted)

Name .....

Address .....


PW12

Start by sending for leaflets at once Trade enquiries invited

**MARTIN ELECTRONICS LTD.** 154/5 HIGH STREET, BRENTFORD  
 MIDDLESEX. ISLeworth 1161/2

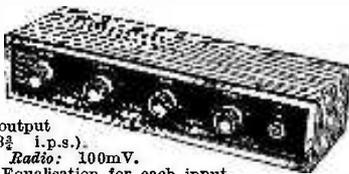
## THE CLASSIC

Controls: Selector switch Tape speed equalisation switch (3½ and 7½ i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 position rumble filter.



**Specification:** Sensitivities for 10 watt output at 1KHz. *Tape head:* 3mV (at 3½ i.p.s.). *Mag. P.U.:* 2mV. *Cer. P.U.:* 80mV. *Radio:* 100mV. *Aux.:* 100mV. *Tape/Rec. output:* 100mV. Equalisation for each input is correct to within ± 2dB (R.I.A.A.) from 20Hz to 20KHz. *Tone control range:* Bass ± 13dB at 60 Hz. Treble ± 14dB at 15KHz. *Total distortion:* (for 10 watt output) < 1.5%. *Signal noise:* < -60dB. A.C. mains 200-250v. Size 12½in. long, 4½in. deep, 2½in. high. Teak finished case. **Price 8 gns.** p. & p. free.

## THE DORSET (600mW output)

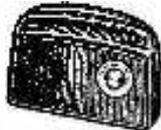

7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modularised and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

MAINS POWER PACK KIT: 9/6 extra.

PRICE £5.5.0 plus 7/6 p. & p. Circuit 2/6 FREE WITH PARTS.


## THE ELEGANT SEVEN MK. III (350mW output)

7-transistor fully tunable M.W.-L.W. portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

Price £4.9.6 plus 7/6 p. & p.

Circuit 2/6 FREE WITH PARTS.

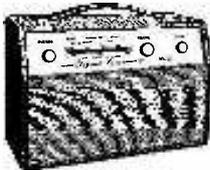


## X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

**Specifications:** *RMS Power Output* (into 3 ohms speaker): 10 watts continuous (sine wave), 13 watts music power. *Sensitivity* (for rated output): 1mV into 3K ohms (0-35 micro-amp). *Total Distortion* at 1KHz: at 5 watts 0.35%, at rated output 1.5%. *Frequency Response:* Minus 3dB points 20Hz and 40KHz. *Speaker:* 3-4 ohms (3-15 ohms may be used). *Supply voltage:* 24V d.c. at 800mA (6-24V may be used). **Control assembly:** including resistors and capacitors.

1. Volume: PRICE 5/-.
  2. Treble: PRICE 5/-.
  3. Comprehensive bass and treble: PRICE 10/-.
- The above 3 items can be purchased for use with the X101. **Power Supplies for the X101:**  
P101 M (for mono) 35/- plus 4/6 p. & p.  
P101 S (for stereo) 42/6 plus 4/6 p. & p.



Price 49/6 plus 2/6 p. & p.

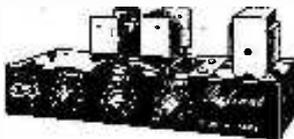

## THE RELIANT 10W SOLID-STATE HIGH QUALITY AMPLIFIER SPECIFICATIONS

**Output**—10 watts RMS Sine-wave  
13 watts RMS Music-power  
**Inputs**—1. xtal mic 10mV  
2. gram/radio 250mV  
**Tone Controls**—Treble control range ± 12dB at 10KHz  
Bass control range ± 13dB at 100Hz  
**Frequency Response**—(with tone controls central) Minus 3dB points are 20Hz and 40KHz.  
**Signal to Noise Ratio**—better than -60dB. **Transistors**—4 silicon Planar type and 3 Germanium type. **Mains input**—220-250V. A.C. Size of chassis—10" x 3½" x 2". A.C. Mains, 200-250V. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control for gram. and mike. Built and tested. 8" x 5" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P. **PRICE £5.5.0 plus 5/- P. & P.**

## THE VISCOUNT

Integrated High Fidelity Transistor Stereo Amplifier

**SPECIFICATIONS:** **Output:** 10 watts per channel into 3 to 4 ohms speakers (20 watts monoral). **Input:** 6 position rotary selector switch (3 pos. mono and 3 pos. stereo). **P.U., Tuner, Tape and Tape Rec.** Sensitivities: All inputs 100mV into 1-3M ohm. **Frequency response:** 40Hz-20 KHz ± 2db. **Tone controls:** Tone controls flat (Baxandall type), separate bass and treble controls. Treble 13db lift and cut at 15KHz. Bass 15db lift and 25db cut at 60Hz. **Volume controls:** Separate for each channel. **AC Mains input:** 200-240v. 50-60Hz. Size 12½ x 6 x 2½in. in teak-finished case. Built and tested. **PRICE 13½ Gns.** Postage & Packing 7/6 extra.

Goods not despatched outside U.K. Terms C.W.O. All enquiries Stamped Addressed Envelope

**RADIO & TV COMPONENTS (Acton) LTD**  
21c High Street, Acton, London, W.3.  
323 Edgware Road, London, W.2.  
All orders by post to our Acton address

## POCKET MULTI-METER

Size 3½ x 2½ x 1½in. Meter size 2½ x 1½in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000 D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test prods, battery and full instructions, 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 36 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.



## CYLDON U.H.F. TUNER

Complete with PC88 and PC86 Valves. Full variable tuning. New and unused. Size 4½ x 5½ x 1½in. Complete with circuits diagram. **35/-** p. & p. 3/6



## THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross over network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 gauss. Resonance 40-60 c/s. Frequency range 50c/s to 20kc/s. Size 13½ x 8½ x 4½ inches. By famous manufacturer. List Price £7. Our price 69/6 plus 5/- P. & P. Similar speaker to the above without tweeters in 3 and 15 ohm 39/6 plus 5/- P. & P.

## 600 mW FOUR TRANSISTOR AMPLIFIER

Features N.P.N. and P.N.P. complementary symmetrical output stage, 2½" x ¾" x ¾" Speaker. Output impedance 12 ohms frequency response 3dB points 90 c/s and 12 Kc/s. Price 19/6 plus 1/- P. & P. 7" x 4" Speaker to suit, 13/6 plus 2/- P. & P.

## 2½ watt ALL TRANSISTOR AMPLIFIER

AC mains 240V. Size 7" x 4½" x 1½". Frequency response 100 c/s—10 Kc/s Semi conductors, two OC 75's two AC 128's and two stabilizers AA129. Tone and volume controls on flying leads. £2.10.0 plus P. & P. 3/6. Suitable 8" x 5" 10,000 line high flux speaker, 18/6 plus 2/- P. & P.

Size 5½ x 3½ x 1½in. For IF and RF alignment and AF output 700 c/s frequency coverage 460 kc/s to 2 mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and Musette. Built and tested. **49/6** P. & P. 3/6.

## NEW TRANSISTORISED SIGNAL GENERATOR




## FIRST QUALITY P.V.C. TAPE

5½" Std.	850ft. .... 9/-	5" L.P.	850ft. .... 10/6
7" Std.	1200ft. .... 11/6	3" T.P.	600ft. .... 10/6
3" L.P.	240ft. .... 4/-	5" T.P.	1800ft. .... 25/6
5½" L.P.	1200ft. .... 11/6	5½" T.P.	2400ft. .... 32/6
7" L.P.	1800ft. .... 18/6	7" T.P.	3600ft. .... 42/6
5½" D.P.	1800ft. .... 18/6	4" T.P.	900ft. .... 15/-

P. & P. on each 1/6, 4 or more post free.

## 50 WATT AMPLIFIER A.C. MAINS 200-250V

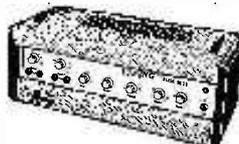


An extremely reliable general purpose valve amplifier—with six electronically mixed inputs. Suitable for use with: mics, guitars, gram, tuner, organs, etc. Separate bass and treble controls.

Price 27 gns.  
Plus 20/- p. & p.

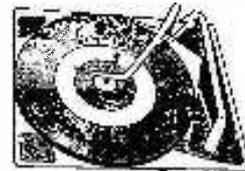
## RECORD PLAYER SNIP A.C. MAINS 240V

The "Princess" 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7" to 10" or 12". Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play. Post and insurance 7/6 extra.


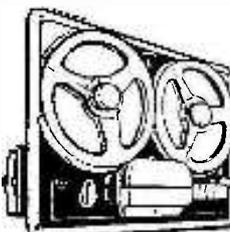
## ANTI-THIEF CAR BURGLAR ALARM


The Melguard Safermatic consists of an electrical device housed in small metal box 4" x 2" x 1½", which has been designed and developed to provide protection required by the average motorist at an economic cost. Using this system, an alarm and the immobilised condition is set automatically as soon as you park the car. Should you leave the key in the ignition, no one but you can drive the car away. Upon entering the vehicle the method of starting the car is by switching on the ignition, depressing two hidden switches, and simultaneously operating the starter. Location of the switches is known only to you. Should the alarm be set off it can be stopped by following the normal starting procedure. For 12V operation. List price 79/6, our price 29/6 plus 2 6 P. & P. Full easy-to-follow instructions supplied.



## MOTEK

3 Speed 2 track Tap Deck complete with heads, takes 7in. spool.  
Incorporating 3 motors.  
A.C. mains, 240 volts, listed at £21.0.0.  
**Our Price £9.19.6, plus 10/- P. & P.**
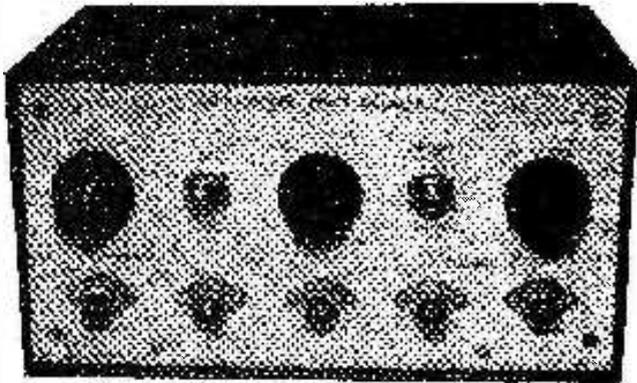
# Open the pages of The RADIO CONSTRUCTOR this month for . . . OSCILLOSCOPE TRACE DOUBLER



This 6 Transistor unit will give trace doubling for input waveforms up to 2 Mc/s or more. Two trace switching speeds are a feature of this design.

Also  
Low-value Capacitance Bridge.  
150 Watt Transmitter.  
Inexpensive Intercom System.

MANY OTHER ARTICLES

PLUS 2  
DETACHABLE DATA SHEETS

# RADIO CONSTRUCTOR

NOVEMBER ISSUE NOW ON SALE 3/-

# BI-PRE-PAK LTD

222-224 WEST ROAD, WESTLIFTON-ON-SEA, ESSEX  
PHONE: SOUTHEND (0802) 46344

## BRAND NEW PAK JUST RELEASED !!!

REPLACES OUR VERY POPULAR B39 PAK.  
Short Lead Components, all Brand New and Factory Marked  
mounted on Printed Circuit Panels.

Approximately:

- 80 TRANSISTORS AND DIODES
- 50 HIGH TOLERANCE RESISTORS
- 20 VARIOUS CAPACITORS

# 10/-

Please state when ordering Pak P.1. 2/6 Post and Packing  
with this pack.

### BRAND NEW PRE-PAKS

No.	Description	Price
B1	50 Unmarked Trans. Untested	10/-
B2	4 Solar Cells inc. Book of Instructions	10/-
B6	17 Red Spot AF Transistors	10/-
B6A	17 White Spot R.F. Transistors	10/-
B9	1 ORP12 Light Sensitive Cell	9/-
B53	25 Silicon Transistors 400 M/c	10/-
B54	40 Silicon Transistors NPN To5	10/-
B55	40 Silicon Transistors NPN To18	10/-
B56	40 Silicon Transistors NPN/PNP	10/-
B61	25 BSY26/7 Transistors new, untested	10/-
B62	25 BSY95a Transistors new, untested	10/-
B64	25 BFY50/1/2 Transistors new, untested	10/-
B65	25 BC107/8/9 Transistors new, untested	10/-
C2	1 Unijunction Transistor 2N2160	15/-
A3	25 Mixed Marked and Tested Transistors	20/-
A21	5 Power Transistors, one AD149, one OC26 and three more	20/-
	FEW LEFT 70 amp/400 p.i.v. SCR's	70/-


Transistors	Price
AC107	3/-
AC126	2/4
AC127	2/4
AF117	3/6
AC176	4/-
BC107-8-9	5/-
OC271	10/-
BSY95A	3/-
OC22	6/-
OC23	6/-
OC25	7/6
OC26	5/-
OC28	10/-
OC35	5/-
OC36	7/6
OC41	2/6
OC42	3/-
OC44	1/11
OC45	1/9
OC71	2/6
OC72	2/6
OC73	3/6
OC81	2/6
OC81D	2/6
OC83	4/-
OC139	2/6
OC140	3/6
OC170	3/-
OC171	4/-
OC200	5/-
OC201	8/-
2N1302 or 3	4/-
2N1304 or 5	5/-
2N1306 or 7	6/-
2N1308 or 9	8/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

Send for our FREE lists and catalogue of all our products. Check your own equivalent with our free substitution chart.

FIRST EVER LOGIC KITS. Learn for yourself how computers work, even make one for yourself. Full instructions for a noughts and crosses machine, binary counters, timers, etc. ENTIRELY NEW RANGE, Norkit Junior, £8, Norkit Senior, £16

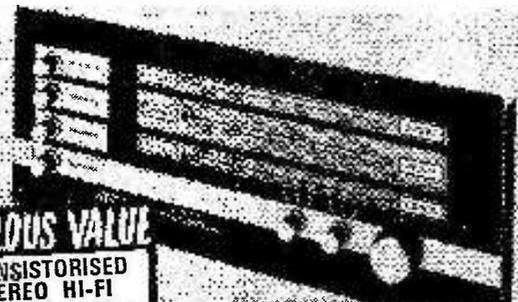NO CONNECTION WITH ANY OTHER FIRM MINIMUM ORDER 10/-.  
CASH WITH ORDER PLEASE, add 1/- post and packing.  
OVERSEAS ADD EXTRA FOR AIRMAIL



FABULOUS VALUE

### TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4 1/2" deep. 14 transistors plus 4 diodes, separate Bass and Treble - 10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL  
NO TECHNICAL KNOWLEDGE REQUIRED  
Only 27 Gns. + P&P 17/6

H. P. terms available. Deposit £7.1.9. & 12 monthly payments of 40/- (Total H. P. £31.1.9.). Send £7.19.3. today. Amplifier available separately at only 16 Gns.


### FANTASTIC BARGAIN OFFER!

### "TRANSCONTINENTAL" FULLY TRANSISTORISED STEREOPHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer - a complete radiogram at half normal price ONLY

10 Watts Total output  
17 Transistors & 10 diodes  
EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY  
H.P. available £9:2:6d deposit plus 18 monthly payments of £1:15:9d (Total H.P. £41:6:0)

Send £10 today

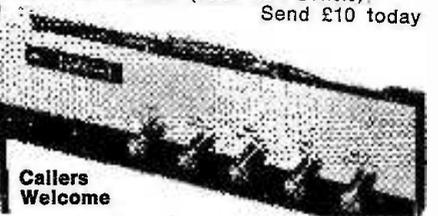

Callers  
Welcome

POST  
THIS  
COUPON  
NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name .....

Address .....

LEWIS radio 100 CHASE SIDE, SOUTHGATE, Dep. P1268  
LONDON, N.14. TELEPHONE PAL 3733/9666



# SENSATIONAL R.S.C. HIGH FIDELITY STEREO PACKAGE OFFERS

**"PACKAGE 3" 30 WATT SYSTEM**  
 ★ Goldring Transcription Turntable on Plinth  
 ★ Shure Magnetic Pick-up Cartridge  
 ★ Super 30 Amplifier in Teak veneer housing  
 ★ Pair of Stanton Loudspeaker Units  
 Special inclusive price. Fully wired units ready to "plug-in".  
**82 Gns.**  
**TERMS AVAILABLE ALL PACKAGE OFFERS**

Matched for optimum performance. Send for coloured brochure showing other money saving offers.

**"PACKAGE 2" 30 WATT SYSTEM**  
 ★ Garrard SP25 Mk II Turntable on Plinth  
 ★ Goldring CS90 Ceramic P.U. Cartridge  
 ★ Super 30 Amplifier in Teak veneer housing  
 ★ Pair of Stanton Loudspeaker Units  
 Special inclusive price. Fully wired units ready to "plug-in".  
**72 Gns.**

## AUDIOTRINE HIGH FIDELITY LOUSPEAKERS



Heavy cast construction. Latest high efficiency ceramic magnets. Treated Cone surround giving low fundamental resonance. "D" indicates Tweeter Cone providing extended frequency range. Impedance 3 or 15 ohms. Please state choice. Response 40-18,000 c.p.s. Exceptional performance at low cost. Prices include carriage.

HF501	5" 10W	59/9	HF120	12" 15W	69/9
HF801D	8" 8W	59/9	HF120D	12" 15W	79/9
HF811D	8" 10W	4 gns.	HF126	12" 15W	89/9
HF100D	10" 15W	59/9	HF126D	12" 15W	5 gns.



Illustrated with TFM1 Mk II Tuner fitted  
**EXTREMELY ATTRACTIVE AND VERSATILE PLINTHS**  
 finished in Satin Teak veneer. Tinted Perspex hinged cover with satin chrome handle.

## RECORD PLAYING UNITS

Money saving units. Ready to RP2 plug into Amplifier or Tape Recorder. Consisting of Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Mounted on Plinth. Perspex Cover 3 gns. RP3 extra. **19 Gns.**

As above but with Goldring Lenco GL88 Transcription unit and CS90 Cartridge. Perspex Cover 3 gns. extra. Inc. **24 1/2 Gns.**  
 Carr. ONLY

## "PACKAGE 1" 13 WATT SYSTEM

★ Garrard SP25 Mk II 4 speed Player Unit  
 ★ Goldring CS90 Ceramic P.U. Cartridge  
 ★ TA12 Amplifier in Teak veneer housing  
 ★ Pair of Dorset Loudspeaker Units  
 Special inclusive price.  
 Or Dep. £10 and 9 monthly payments £5.4.0. (Total £56.18.0.)  
 Perspex cover 3gns. extra. **49 1/2 Gns.**

## HIGH FIDELITY LOUSPEAKER UNITS

Cabinets of latest styling Satin Teak or Walnut acoustically lined (and ported where appropriate). Credit terms available on all units.

**DORSET** Size 16 x 11 x 9in. Response 45-18,000 c.p.s. Rating 8-10 watts. Fitted High flux 8in. Dual Cone **£8.19.9** speaker. Imp. 3 or 15 ohms.

**STANTON IIS** Size 18x11x10in. Rating 10 watts. Incorporating Fane 803B speaker with roll rubber surround and 15,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Response 30-20,000 c.p.s. Impedance 3 or 15 **16 Gns.** ohms. Givessmoothrealisticsound output. Inc. carr.

**GLOUCESTER** Size 25 x 16 x 10in. 12in. High flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Smooth response **12 1/2 Gns.** 40-20,000 c.p.s. Impedance 15 ohms.

## E2 EQUIPMENT CABINET

Size 17" wide 14" deep 11" high. Cut for TA12, Super 15, Super 30 and other amplifiers. "Hinged" perspex cover. Satin Teak veneer finish. **8 Gns.**  
 Price inc. carr.



**MOTOR BOARDS** cut for Garrard Turntables and many other units. Price **12/9**

## PLINTHS

for Record Playing units. Teak finish cut for Garrard **59/9** 1000.2000.

3000, AT6, AT80, SP25 or Goldring GL56. Available with clear Perspex cover. Perspex as ill. Inc. Carr. **6 Gns.** Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. **39/9**

**INTEREST CHARGES**  
**REFUNDED** on Credit Sales settled in 3 months.

## R-S-C-TA12 13 WATT STEREO AMPLIFIER

**FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL**  
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, "Mike" etc. 7 separate switched input sockets on each channel. ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250V A.C. mains ★ Frequency Response for 30-20,000 c.p.s. ★ 2dB Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (3) 100mV (4) 2mV ★ Handsome brushed silver finish Facia and Knobs. Complete kit of parts with full wiring diagrams and instructions. Factory built with 12 mth gntee **15 Gns.** Or Deposit £4.18.0 and 9 mthly pymts. 29/- (Total 17 Gns.). Or in Teak veneer housing **15 Gns.**



**AUDIOTRINE HI-FI SPEAKER SYSTEMS**  
 Consisting of matched 12in. 12,000 line 10 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Or Senior 15 watt inc. HF 128 **5 Gns.** 15,000 line Speaker **6 Gns.** Carr. 6/6

**HI-FI SPEAKER ENCLOSURES** Teak veneer finish. Modern design. Acoustically lined and ported. JES Size 16 x 11 x 9in. Gives pleasing results **4 Gns.** with any 8in. Hi-Fi speaker. SE8 For optimum performance with any 8in. **£4/19/9** Hi-Fi speaker. Size 22 x 15 x 9in. SE10 For excellent performance with 10in Hi-Fi speaker. **5 Gns.** Size 24 x 15 x 10in. SE12 For excellent performance with 12in Hi-Fi speaker. **6 Gns.** Size 25 x 18 x 10in.

**R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER**  
 ★ High-sensitivity ★ 200-250V. A.C. Mains operation. ★ Sharp A.M. Rejection. ★ Drift-free reception. ★ Tuner ample for any amplifier (approx. 500 m.v.). ★ Simple alignment instructions. ★ Output available for feeding tuning meter. ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicone Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. The pre-wired tuning head facilitates speed and simplicity of construction. Printed circuitry, only first grade transistors and components used. A quality product at considerably less than the cost of comparable units. Stereo version, all parts 18 gns. Carr. 10/-. Assembled 22 gns. inc. carr.

## R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER

200-250V. A.C. mains operated Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble "lift" and "cut" controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm speakers. Max. sensitivity 5mV. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. Carr. 7/6. Or factory built with 12 months guarantee. **6 Gns.**

Total cost of parts with detailed wiring diagrams & instructions. Carr. **12 1/2 Gns.**  
 Or factory built 18 gns. Or in Teak finished cabinet as illustrated 19 gns. Terms: Deposit £5 and 9 monthly payments £2. Total £23.

**R.S.C. SUPER 15 HI-FI AMPLIFIER** **SOLID STATE CONSTRUCTION**  
 SPECIFICATIONS COMPARABLE WITH UNITS COSTING CONSIDERABLY MORE  
 A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits. Close tolerance Ganged Pots. Matched Components. **CROSS TALK: -52dB** at 1,000 c.p.s.  
**CONTROL:** 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch. **INPUT SOCKETS (Matched Pairs):** (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of the Input Selector Switch assures appropriate equalisation. Rigid 18 s.w.g. Chassis. Size approx. 12in. wide, 3in. high and 8in. deep. Neon Panel Indicator. Attractive Facia Plate and Spun Silver Matching Knobs. Above facilities, etc., except for Ganging and Balance Control, apply also to Super 15.  
**THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon). CURRENTLY AVAILABLE SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT.** All required parts, point to point wiring diagrams and detailed instructions. Carr. 15/-.  
 Unit factory built 27 Gns. or deposit £8.8.0 and 9 monthly payments 68/9. (Total £31.8.3). Or in Teak veneer housing 30 Gns. Carr. 15/- or Deposit £8.2.6 and 9 monthly payments 64/- (Total £34.18.6). Send S.A.E. for leaflet.

## R.S.C. SUPER 30 STEREO AMPLIFIER

**FULLY TRANSISTORISED** 200/250V. A.C. Mains. **OUTPUT 10 WATTS R.M.S.** cont. into 15 ohms. **15 WATTS R.M.S.** cont. into 3-4 ohms.  
**LATEST TRANSISTORS:** NKT275, NKT276, NKT274, NKT713, NKT217, NKT217, NKT717, NKT403, NKT403.  
**5 POSITION INPUT SELECTOR SWITCH**  
**EQUALISATION** to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads.  
**FULL TAPE MONITORING FACILITIES.**  
**SENSITIVITIES:** Magnetic P.U. 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV.  
**FREQUENCY RESPONSE:** ±2dB 20-20,000 c.p.s.  
**TREBLE CONTROL:** +15dB to -14dB at 10 Kc/s. **NEG FEEDBACK:** 52dB.  
**BASS CONTROL:** +17dB to -15dB at 50 c/s. **HUM LEVEL:** -75dB.  
**HARMONIC DISTORTION** at 10 Watts 1,000 c.p.s. 0.1%. Complete Kit of parts with full constructional details and point to point wiring diagrams. Carr. 12/6.  
 Supplied factory built 151 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9). Or in Teak veneer housing as illustrated. 19 Gns.  
**ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING BRITISH MANUFACTURERS.**



**11 1/2 Gns.**

**R.S.C. SUPER 15 HI-FI AMPLIFIER** **SOLID STATE CONSTRUCTION**  
 SPECIFICATIONS COMPARABLE WITH UNITS COSTING CONSIDERABLY MORE  
 A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits. Close tolerance Ganged Pots. Matched Components. **CROSS TALK: -52dB** at 1,000 c.p.s.  
**CONTROL:** 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch. **INPUT SOCKETS (Matched Pairs):** (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of the Input Selector Switch assures appropriate equalisation. Rigid 18 s.w.g. Chassis. Size approx. 12in. wide, 3in. high and 8in. deep. Neon Panel Indicator. Attractive Facia Plate and Spun Silver Matching Knobs. Above facilities, etc., except for Ganging and Balance Control, apply also to Super 15.  
**THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon). CURRENTLY AVAILABLE SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT.** All required parts, point to point wiring diagrams and detailed instructions. Carr. 15/-.  
 Unit factory built 27 Gns. or deposit £8.8.0 and 9 monthly payments 68/9. (Total £31.8.3). Or in Teak veneer housing 30 Gns. Carr. 15/- or Deposit £8.2.6 and 9 monthly payments 64/- (Total £34.18.6). Send S.A.E. for leaflet.

**BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349

**BRISTOL** 14 Lower Castle St. (Half-day Wed.) Tel. 22904

**BIRMINGHAM** 30/31 Gt. Western Arcade opp. Snow Hill Station 021-236-1279 (Half-day Wed.)

**DERBY** 26 Osbaston Rd. The Spot (Half-day Wed.) Tel. 41361

**DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043

**EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. Waverley 5766

**GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. City 4158  
 403 Sauchiehall St. (Opp. Locarno) (Half-day Tues.) Tel. 332-1572

**HULL** 91 Paragon Street. (Half-day Thursday) Tel. 20505

**R.S.C.**  
 HI-FI CENTRES LTD.

32 High Street. (Half-day Thurs.) Tel. 56420 **LEICESTER**

5-7 County (Mecca) Arcade, Briggate (Half-day Wed) Tel 28252 **LEEDS**

73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 **LIVERPOOL**

238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**

98 High Holborn, WC1. Tel. HOL 9874 (Half-day Sat.)  
 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 **MANCHESTER**

106 Newport Rd (Half-day Wed) Tel. 47098 **MIDDLESBROUGH**

41 Blackett Street (Opp. Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**

13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

**MAIL ORDERS TO: 102 Hencorner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries please. Hi-Fi Catalogue 4/6.**

**Open all day Sats. except High Holborn**

## THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25 x 14 x 10in. Complete Kit  
★ Response 30-20,000 c.p.s. Impedance 15 ohms. **18 Gns.**  
★ Performance comparable with units costing considerably more. Consists of (1) 12in. 20 watt Bass unit with cast chassis, Roll rubber surround for ultra low resonance, powerful 2in. diam. pole pieces and ceramic magnet. (2) 3-way quarter section series crossover system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Measured weight of woolen acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions.  
**DEMONSTRATIONS AT ALL BRANCHES.**



## R.S.C. STEREO/20 HI-FI AMPLIFIER PROVIDING

10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL. SUITABLE FOR 'MIKE', GRAM, RADIO OR TAPE. (7) valves ECC83, (2) ECL86, (4) E281. Frequency Response: ±2dB 30-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 20 millivolts max. Harmonic Distortion: 0.2%. Four-position tone compensation and Input Selector Switch. ★Stereo/Mono switch. ★Neon panel indicator. ★Handsome Perspex Frontplate. ★Separate Bass and Treble controls. Output transformers are high quality sectionally wound. Outputs for 3 and 15 ohms speakers. Complete set of parts, point-to-point wiring diagrams and instructions. Or factory assembled with our usual 12 mths' entire 19 Gns. Or Dep. £4.10.0 and 9 monthly payments £2 (Total £22-10-0). Send S.A.E. for leaflet. Carr. 12/6

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp/Tone Control Stages. Performance figures equal to most expensive amplifiers. Hum level -70dB. Frequency response ±3dB 30-20,000 c/s. Sectionally wound output transformer. All first grade components. Valves EF86, EF86, ECC83, 607 607. Treble Bass and Treble Controls. Sensitivity 12 millivolts so that any kind of Microphone or Pick-up is suitable. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and 'Mike' can be mixed 300-250V 500/5 A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. Carr. 12/6

13 Gns. Twin-handled perforated cover 25/-. Supplied factory built with EL34 output valves. 12 months' guarantee for 16 gns. TERMS: Deposit £5.14.0 and 9 monthly payments of 28/9 (Total £18.12.9). Send S.A.E. for leaflet.

## R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT 'BUILT-IN' TONE CONTROL PRE-AMP. Two input sockets with associated controls allowing mixing of 'mike' and gram, etc. etc. High sensitivity. 5 valves—ECC83 (2), EL84 (2), E281. High quality sectionally wound output transformer. IND. BASS AND TREBLE CONTROLS. Frequency response ±3dB 30-20,000 c/s. Hum level -60dB. SENSITIVITY 23 millivolts. Suitable for Crystal or Ceramic PUS, all types etc. Size approx. 12 x 9 x 7in. For AC mains 200-250V, 50 cps. Output for 3 and 15 ohm spkrs. SAE for leaflet. Complete kit. 9 Gns. Full instructions and point-to-point wiring diagrams. Carr 11/6 (or factory built 12 Gns.) Twin handled metal cover 25/-. TERMS ON ASSEMBLED UNITS. Deposit £7/6 and 9 monthly payments of 22/-. (Total £14.5.6).

## RSC A11 TRANSISTORISED VERSION of above complete kit 9 Gns (Assembled 13 Gns)

## R.S.C. BASS-REGENT 50 WATT AMPLIFIER

An exceptionally powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape.

★ Two extra heavy duty 12in. Loudspeakers.  
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or 'mikes'. Bass and Treble controls.  
**49 1/2 Gns.** Carr. 30/- or dep. £7.17.6 and 9 monthly payments of 25.10.10. (Total 55 gns.). Send S.A.E. for leaflet.  
Also B20 Bass inc. 15in. 25w Spkr. 291 gns. G15 inc. 12in. 20w Spkr. 191 gns.

## R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BMI An all-dry battery miniator. Size 5x4x1/2 2in. approx. Completely replaces batteries supplying 1.5v. and 9v. where A.C. mains 200/250v. 50c/s. is available. Complete kit with diagram 47/9 or assembled 59/11.

SELENIUM RECTIFIERS (Bridged) All 6/12v. D.C. output. Max. A.C. input 18v. 1a. 3/11. 2a. 6/11. 3a. 9/8. 4a. 12/9. 6a. 15/8.

## R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250v. 50c/s. Screened.  
MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.  
250v., 60mA, 6.3v. 2a. 15/11  
250-0-250v. 100mA, 6.3v. 2a. 16/11  
FULLY SHROUDED UPRIGHT MOUNTING  
250-0-250v. 100mA, 6.3v. 2a., 0-5-6.3v. 3a. 21/9  
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. 35/9  
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. 35/9  
300-0-300v. 130mA, 6.3v. 4a., c.t., 6.3v. 1a. 43/9  
For Mullard 510 Amplifier. 43/9  
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. 35/9  
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. 45/11  
425-0-425v. 200mA, 6.3v. 4a., c.t., 5v. 3a. 69/9  
425-0-425v. 200mA, 6.3v. 4a., 6.3v. 4a., 5v. 3a. 75/-  
450-0-450v. 250mA, 6.3v. 4a., c.t., 5v. 3a. 85/9  
TOP SHROUDED DROP-THROUGH TYPE  
250-0-250v. 70mA, 6.3v. 2a., 0-5-6.3v. 2a. 21/9  
250-0-250v. 100mA, 6.3v. 3-5a. 23/9  
250-0-250v. 100mA, 6.3v. 2a. 6.3v. 1a. 24/9  
350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. 25/9  
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. 35/9  
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. 35/9  
300-0-300v. 130mA, 6.3v. 4a., 0-5-6.3v. 1a. 43/9  
Suitable for Mullard 510 Amplifier. 42/9  
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. 35/9  
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. 45/11  
FILAMENT or TRANSFORMER POWER PACK Types  
6.3v. 1.5a. 7/9; 6.3v. 2a. 8/9; 6.3v. 3a. 10/9; 6.3v. 6a. 21/9; 12v. 1a. 3/9; 12v. 3a. or 24v. 1.5a. 21/9; 0-9-18v. 1/2a. 17/9; 0-12-25-42v. 2a. 29/9.  
CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. 14/11; 2 1/2a. 17/9; 3a. 19/11; 5a. 23/9; 6a. 27/9; 8a. 33/9.  
AUTO (Step UP/step DOWN) TRANSFORMERS  
0-110/120v. 200-250-250v. 50-80 watts 15/9  
150 watts, 29/11; 250 watts 49/9; 500 watts 99/9  
OUTPUT TRANSFORMERS  
Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω .. 8/9  
Push-Pull 20 watts EL84 to 3 Ω or 15 Ω .. 12/9  
Push-Pull 10 watts 6V6 ECL56 to 3, 5, 8 or 15 Ω .. 22/9  
Push-Pull EL84 to 3 or 15 Ω 10-12 watts .. 21/9  
Push-Pull Ultra Linear for Mullard 510, etc. 38/9  
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω .. 38/9  
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω .. 59/9  
SMOOTHING CHOKES  
150mA, 7-10H, 250 Ω 12/9; 100mA, 10H, 200 Ω 10/9; 80mA, 10H, 250 Ω 8/9; 60mA, 10H, 400 Ω 7/11.

## R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair, ideal for vocalists and Public Address. 15 ohm matching. Type C48, 25-30 watts. Fitted four 8in. high flux 7 watt speakers. Overall size approx. 42 x 10 x 5in. Or deposit 65/- and 9 monthly pmts 24/9 (Total £18-17-9) Carr. 10/-  
Type C412, 40 watts, Fitted four 12in. 12,000 line 10 watt speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/- Or Deposit £3.13.0 and 9 monthly payments of 50/- (Total £26.3.0).



**15 Gns.**  
**22 Gns.**

## 30 WATT HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group  
A 2 input, 2 volume control Hi-Fi unit with Separate Bass and Treble controls. Peak rating 60 watts. Latest valves. Strong Rexine covered cabinet with handles. Attractive black/gold perspex facia. Neon indicator. For 200-250v. A.C. mains. 18 Gns. Carr. 10/- For 3 or 15 ohm speakers. Send S.A.E. 12/6 for leaflet. Deposit 3 gns. and 9 monthly payments of 39/8 (Total £21).



## 12in. HIGH QUALITY LOUDSPEAKERS

In Teak veneered or Rexine covered Cabinets  
10 Watt 12,000 lines **5 Gns.** 20 Watt 12,000 lines **8 Gns.**  
3 or 15 ohms 3 or 15 ohms



## LOUDSPEAKERS

Limited number of heavy duty units at fraction of list price. 15 ohms impedance. Brand new, guaranteed. Terms available over 28.  
HIGH FLUX | DUAL CONE | 12in. 30 watt Normally £6.19.9 over £14  
59/11 | £5.15.0 | Normally 9 gns.

## FANE 'POP' 100 LOUDSPEAKER

18" 100 Watt POST FREE  
Fantastic power handling. Guaranteed 2 years. **19 Gns.**

R.S.C. GRAM AMPLIFIER KIT. 4 watts output. Negative feedback. Controls: Vol., Tone and Switch. Mains operation 200-250V. A.C. Fully isolated chassis. Circuit etc. supplied. **49/11**

POWER PACK KIT Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250V. A.C. mains. Output 250v. 60mA 6.3v. 2a. Supplied with case **22/11** in lieu of chassis 26/11. or assembled 39/11.

## R.S.C. 4/5 watt

## A5 HIGH GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P.U. heads and most 'mikes'. Separate Bass and Treble controls. Hum level 7dB down. Negative Feedback 15dB. For A.C. mains 200-250v. Speaker output 3 ohms. Complete Kit with point-to-point wiring diagrams and instructions. **£4.17.9**



## CLEARANCE LINES

HIGH QUALITY 8" x 3" LOUDSPEAKERS 10000 Gauss 3 ohm only **12/9**  
EXTENSION 'SPEAKERS 29/9 EMI PLAYER T/TABLES  
Cabinet size 12 x 8 x 5in. with P.U. 4 speed. T/D cartridge. Limited number mail order only.  
Fitted high flux 6in. 5w. 3 ohm speaker. Mono **79/9** Stereo **89/9**

PHONE AMPLIFIERS Speak and listen with both hands free. Standard dry battery operated. Attractive black moulded case. **59/9**

1 WATT TRANSISTOR AMPLIFIERS for 3-5 ohm loudspeakers. Miniature size. Brand new boxed. **39/11**

PRINTED CIRCUIT KITS for making printed circuits. Complete with 72 square ins. laminated board and necessary fluids. **14/11**

J.B. VHF/FM DIAL & DRIVE ASSEMBLIES Complete with escutcheon. Size 7" x 4 1/2". Escutcheon 7 1/2" x 2 1/2". **ONLY 9/9**

TAPE RECORD/PLAYBACK AMPLIFIERS 4 watts output. Magic Eye Recording level indicator. For 3 ohm L/S. All normal facilities but less Facia Plate. (Normally 13 gns.). **£7.19.11**

MINI-8 HI-FI LOUDSPEAKER UNITS Teak veneered cabinet size 9 1/2 x 6 1/2 x 7 1/2 in. Max. power handling 8 watts 3 ohms or 15 ohms. Clearance Price **4 Gns**

HEAVY DUTY 15in. 40 WATT LOUDSPEAKERS in substantial Rexine/Vynair covered cabinet. **ONLY 14 Gns**

## STEREO/TEN HIGH QUALITY AMPLIFIER

5 watts high quality output on each channel. Sensitivity 50 millivolts. Suitable all crystal or ceramic stereo heads. Ganged Bass and Treble Controls. Valves ECC83 (2), EL84 (2), E281. For 2-3 ohm speakers. Assembled with 12 months' guarantee for **£11.19.6** Carr. 11/6

## VERDIK HIGH FIDELITY AMPLIFIERS

with separate pre-amplifier. Mullard 510 circuit. Limited number to clear by mail order only. Fully guaranteed. **12 gns**

## R.S.C. 6/12V CAR BATTERY CHARGERS

Complete kit of parts incl. Ammeter and Circuit.  
4 amp with variable charge rate selector **49/9**  
6 amp heavy with variable charge rate selector **69/9**  
All types 200-250v. A.C. mains. Ready built 10/- extra.

# Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the *fast*, modern way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new **TECHNATRON** Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING. The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 132-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 132-page book—'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 372B, Aldermaston Court, Aldermaston, Berkshire.

To: B.I.E.T., Dept. 372B, ALDERMASTON COURT, ALDERMASTON, BERKS.

I would like to know more about your Practical Radio & Electronics Course. Please send me full details and FREE 132-page book.

name.....

address.....

.....age.....



**ORGAN BUILDERS! SILICON N.P.N. TRANSISTORS, ALL INDIVIDUALLY TESTED IN PUBLISHED DIVIDER CIRCUIT! GOLD-PLATED LEADS FOR EASY SOLDERING!** Unbeatable value at 1/6 each or \$5.00 per 100.

**TRANSISTORISED FLUORESCENT LIGHT. 8 WATT 12in. TUBE.** Current drain only 700mA! Complete and tested \$2.19.6 only! Or in kit form: \*Case 10/-; \*Transistor 10/-; Lamp holders, pair 5/-; Condensers etc. 3/-; Transformer 13/6; Tube 8/-. \*Post Packing 5/-.

### TRANSISTORS

OC200, OC203, OC204 all at 2/- each.  
ASY22, 2N753, BSY28, BSY65, 2G344A, 2G345A, 2G371A, 2G378A, all at 1/6 each.  
Transistors similar to OC44, OC71 and OC72 all 1/- each.  
Unmarked, untested transistors 7/6 for 50.

**LIGHT SENSITIVE TRANSISTORS** (similar OCP71) 2/- each.  
30 watt transistors (ASZ17) 10/- each.

**DIODES.** Very low leakage. Make excellent detectors, also suitable for keying electronic organs. 1/- each. 20 for 10/-.

### RECTIFIERS

BY100.800 p.i.v. 2/6 each, 24/- per doz., \$7.10.0 per 100, \$50 per 1,000.  
BYZ13, 6 amp 400 p.i.v. available on same terms.

### MULLARD POLYESTER CAPACITORS. FAR BELOW COST PRICE!

0-001μF 400 volts	3d.	0-02μF 200 volts	3d.
0-0015μF 400 volts	3d.	0-15μF 160 volts	6d.
0-0018μF 400 volts	3d.	0-22μF 160 volts	6d.
0-0022μF 400 volts	3d.	0-27μF 160 volts	6d.
0-01μF 400 volts	3d.	1μF 125 volts	1/-

**VERY SPECIAL VALUE!** Small Silver-mica, Ceramic, Polystyrene Condensers. Well assorted. Mixed types and values. 10/- per 100.

**PAPER CONDENSERS,** mixed bags, 0-0001 to 0-5μF, 12/6 per 100.

**RESISTORS!** Give-away offer! Mixed types and values. 1 to 1 watt. 6/6 per 100, 55/- per 1,000. Individual resistors 3d. each. Also 1 to 3 watt Close Tolerance. Mixed values 7/6 100, 55/- 1,000.

**WIRE-WOUND RESISTORS.** 1 watt to 10 watts. Mixed bags only. 16 for 10/-

### RECORD PLAYER CARTRIDGES

ACOS GF67/3 Mono 15/- complete with needles.  
GF91/3 Stereo Compatible \$1.0.0 complete with needles.  
GF93/1 Stereo Ceramic \$1.5.0 complete with needles.  
GF94/1 Stereo Ceramic \$1.5.0 complete with needles.  
Small pick-up arms complete with cartridge and needle 10/- only.

**TRANSISTORISED SIGNAL INJECTOR KIT.** R.F./I.F./A.F. 10/- only.

**TRANSISTORISED SIGNAL TRACER KIT** 10/- only.

**TRANSISTORISED REV-COUNTER KIT** 10/-

### VEROBOARD

2 1/2in. x 1in.	0-15in. matrix	1/1	17in. x 2 1/2in.	0-15in. matrix	11/-
3 1/2in. x 2 1/2in.	0-15in. matrix	3/3	17in. x 3 1/2in.	0-15in. matrix	14/8
3 1/2in. x 3 1/2in.	0-15in. matrix	3/11	3 1/2in. x 2 1/2in.	0-1in. matrix	3/9
5in. x 2 1/2in.	0-15in. matrix	3/11	3 1/2in. x 3 1/2in.	0-1in. matrix	3/11
5in. x 3 1/2in.	0-15in. matrix	5/6	5in. x 2 1/2in.	0-1in. matrix	3/11
			5in. x 3 1/2in.	0-1in. matrix	5/6

Spot Face Cutter 7/6. Pin Insert Tool 9/6. Terminal Pins 3/6 for 36.

### MULTIMETERS. 20,000 ohms per Volt.

Ranges: A.C.: 1,000V, 500V, 100V, 50V, 10V.  
D.C.: 250ma, 25ma, 50μA.  
D.C.: 2,500V, 500V, 250V, 50V, 25V, 5V.  
Resistance: 0/60KΩ and 0/6MΩ.

Special price \$4.0.0 only.

### ELECTROLYTIC CONDENSERS

0-25μF	3 volt	4μF	25 volt	25μF	25 volt
1μF	6 volt	5μF	6 volt	30μF	6 volt
1μF	20 volt	6μF	6 volt	30μF	10 volt
1-25μF	16 volt	8μF	3 volt	50μF	6 volt
2μF	3 volt	8μF	12 volt	64μF	2-5 volt
2μF	350 volt	8μF	50 volt	64μF	9 volt
2-5μF	16 volt	10μF	6 volt	100μF	9 volt
3μF	25 volt	10μF	25 volt	320μF	4 volt
3-2μF	64 volt	20μF	6 volt	320μF	10 volt
4μF	4 volt	25μF	6 volt	400μF	6-4 volt
4μF	12 volt	25μF	12 volt		

All at 1/- each. 20 assorted (our selection) 10/-.

Orders by post to:

## G. F. MILWARD


DRAYTON BASSETT, NEAR TAMWORTH, STAFFS.

Please include suitable amount to cover post and packing. Minimum 2/- Stamped addressed envelope must accompany any enquiries.  
For customers in Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8.

# BARGAIN OPPORTUNITIES FROM


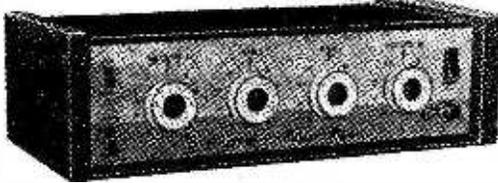
## TRS STEREO 4-4 a bargain in quality amplifiers



**AMPLIFIER KIT** £7.19.6 (pp. 3/6)  
**TRS POWER UNIT** £2.5.0 (p.p. 2/6)  
**TRS SIMPLEX CABINET** £11.7.6 (p.p. 2/6)  
 4 prs DIN plugs and sockets if purchased separately.  
 Complete kit inc. cabinet/power pack DIN plugs and socket.  
**£12.10.0** (post free)

Integrated 5 transistor stereo amp based on newly developed Mullard 4 watt modules and BC108 pre-amp. Suitable also for speakers from 3 to 15 ohms. With base and treble cut/boost. Response—80 to 14KHz—3dB. This excellently engineered layout requires only wiring between controls and modules. Complete with metal chassis and simplex teak-ended cabinet for instant assembly.



## A NEW DE-LUXE FM MONO/STEREO TUNER FROM TRS

This advanced design computable Hi Fi mono/stereo FM tuner comes in easy-to-assemble pre-fabricated units engineered to the highest standards of efficiency and performance. Valuable refinements include switchable A.F.C., automatic noise suppression, flywheel tuning, stereo indication light, excellent audio response. Sensitivity better than 5 microvolts. Stereo can be added later if so required. Inclusion of a world-famous Gurler I.F. amplifier ensures superb performance. Excellent chassis design made specially to fit the standard TRS Simplex cabinet system. Styled to match the TRS Stereo 4-4.

S.A.E. brings full details.

Total price (for mains operation) **£29.10.0** (corr. 10/-)

- A.F.C. & A.G.C.
- Noise Limiter
- Chassis Ready Built
- Pre-tuned

Kit to make MONO tuner inc. chassis and tuning assembly (p.p. 2/6) **15 gns.**  
 Add-on Stereo Unit (p.p. 2/6) **10 gns.**  
 Power Unit (p.p. 2/6) **£2.5.0**  
 Simplex Cabinet (p.p. 2/6) **£1.17.6**

## MAKE YOUR OWN BOOKSHELF SPEAKER

With a set of matched speakers and cross-over from TRS. Comprises modern style high efficiency 5in. bass unit with special cone assembly, X-over and 2 1/2in. tweeter **79/6**  
 (corr. 5/-).  
 A world-famous manufacturer. A genuine bargain for only

## GARRARD & E.M.I. PLAYING UNITS

**LM3000** Record Player with 9T.A. Stereo Cartridge. **£10.5.0**  
**AT.60** Mk. II De-luxe Auto-changer, die-cast turntable. Less cartridge. **£13.5.0**  
**SP.25** De-luxe single record player, die-cast turntable. Less cartridge. **£11.19.6**  
 Brand new in makers' cartons. Packing and carriage on any one of above 7/6.  
**GARRARD PLINTH WB.1** in fine Teak for any of above units. (Packing and carriage 5/-). **65/-**  
 Garrard clear-view rigid perspex cover (carriage 4/6). **62/6**  
**CARTRIDGES AVAILABLE TO PURCHASERS OF ABOVE PLAYER UNITS—STEREO.** Sonotone 9TA/H/C Ceramic with diamond 49/6  
 Decca Demam with diamond 92/6; MONO Acco GP91-1 21/-; Goldring Mx2M 26/6.  
**E.M.I. 4 SPEED PLAYER** Motor and 10 1/2 T/Table unit and free-mounting pick up arm with high quality T/O Cartridge. (p.p. 5/-). **69/6**

## FREE LIBRARY TAPE WALLETS

With each reel of this fine tape by an internationally famous manufacturer we give a well made wallet in simulated leather with space for a reel each side. This is professional quality full frequency tape with metalised leader/stop foils.  
 5 1/2in. reel, 1200ft., with wallet **17/6**  
 5in. reel, 900ft., with wallet, **12/6**  
 7in. reel, 1800ft., with wallet, **22/6**

## TRS MULLARD AMPLIFIERS

**STEREO 10-10** Kit with valves and passive control system **KIT—£17.10.0; BUILT £21.** (corr. either, 12/6)  
**2 + 2 VALVE PRE-AMP** Built, complete with valves, dial, etc. **13 gns.** (corr. 7/6)  
**5-10 MONO AMPLIFIER.** Basic Kit, with valves, etc.. **9 1/2 gns** Built, **11 1/2 gns.** (corr. 7/6 either).  
 Basic Kit with passive control system, **£11.19.6.** Built **£14.19.0** (corr. 7/6 either).  
**PRE-AMP 2 VALVE KIT** £6.12.6. Built **£8.10.0** (corr. 3/6 either)  
**BASIC 5-10 AMPLIFIER AND 2 VALVE PRE-AMP** Assembled, wired and tested, complete **£19.10.0** (corr. 10/-).  
 Send S.A.E. for leaflet giving full technical specifications on these world famous amplifiers.

## HERE'S A GREAT BARGAIN RECORD PLAYER AMPLIFIER

Ideal for building into a record player. 2 watts output with volume and tone controls. Double wound mains isolating transformer. E230 and E1122 valves. Stylish two-tone catchoon panel. Printed circuit assembly. Ready wired and tested for instant assembly. 32 matching o/p transformer. Recommended playing unit—E.M.I. unit at 69/6 above. Amplifier as described. **79/6**

## TRS Stereo Decoder

For reception of stereo broadcasts on your existing FM receiver. Based on Mullard design. 6 Transistors. Beacon indicator. All coils prechecked and aligned. (Carr. & Packing 2/6). **5 Gns.**

## TRS Power Supply Unit

Heavy duty, ready built mains power unit of great reliability and suitable for the heaviest demands without stress or fluctuation, very easy to mount. Size: 3 1/2 x 2 x 2in.  
**PU.12** giving 12V at 1.5A: **PU.24** giving 24V at 0.75A. Either model (p.p. 2/6) **45/-**

## WIRE WOUND RESISTORS—COATED TYPES

Stand. values 25 ohms—10000 ohms, 5w, 1/8, 10w, 1/8, 15w, 2/3. SPECIAL VALUES 15K—35K ohms 5w, 2/6.

**PRE-SET WIRE WOUND POTS.** Slotted Knurled Knob T.V. Type 25 ohms—30 Kohms 3/3, 50 Kohms 4/6. Ditto carbon track 50K—2 Meg. 3/3.

**SLIDER PRESETS** 1w, 10K 2-2 Meg. 2/- 10 ohms—5K 2/6.

**SKELETON PRESETS** for P/circuit use, 100 ohms—2.5 Meg. 2/-.

**STANDARD W/WOUND POTS.** Long Spindle. 100 ohms—50000 ohms each 6/-, 100,000 ohms each 6/9.

**VOLUME CONTROLS** 1 1/2in. dia. Long Spindles. Famous make. All values 5000 ohms—2 Megohms. Guaranteed 12 months. Log or Linear tracks. Less Sw. 3/6. DP Sw. 3/-. Log or Linear tracks, Centre Tapped 4 Megohm Log, 1 Megohm less Sw. 5/-. **TWIN GANGED STEREO** 1 1/2in. dia., Long Spindles. All values 5000 ohms to 2 Megohms less Sw., ea. 3/6. All values 100K to 2 Megohms with DP Sw., ea. 10/6.

## STEREO BALANCE CONTROLS

Log/Anti-Log 5K, 1/2 Meg., 1 Meg., 2 Meg. ea. 9/6.

**VEROBOARD**—All standard sizes including 2 1/2 x 5in., 3/8; 2 1/2 x 3 1/2in., 3/-; 3 1/2 x 5in., 5/2; 3 1/2 x 3 1/2in., 3/8; 2 1/2 x 17in., 12/6. All accessories and tools in stock.

**'GIR-KIT'** Adhesive copper strip for circuit building 60in. spool, 1 1/2in., 2/-.

## FOR 6d YOU CAN SAVE £ £ £

Send 6d. now to TRS for their latest bargain-priced lists of components, accessories, materials and equipments, including many hard to find items. 8 large pages, well printed. Send for your copy now.

**RESISTORS**—Modern ratings, full range 10 ohms to 10 megohms, 10%, 1/4 w., 4d. ea.: 5% Hi-Stab. 1/4 w., 6d. ea. (below 100 ohms and over 1 meg., 6d. ea.). 1% Hi-Stab. 1/4 w., 1/6 ea. (below 100 ohms, 2/- ea.).

**CONDENSERS** Silver Mica. All values 2 pf. to 1,000 pf. 6d. ea. Ditto ceramics 9d. Tub. 450v. T.G.C., etc. .001 mfd. to 0.1 mf./350 v. 10d. .02 mf. to 0.1 mfd. 500 v. 1/- .25 T.G.C. 1/9. 5 T.G.C. 2/-. **CLOSE TOL. 5/MICS.** 10% 5 pf.—500 pf. 8d. 600-5,000 pf. 1/-, 1% 2 pf.—100 pf. 9d. 100 pf.—500 pf. 11d. 375 pf.—5000 pf. 1/8.

**ALUM. CHASSIS.** 18g. Plain undrilled folded 4 sides, 2in. deep. 6 x 4in. 4/6; 8 x 6in. 5/9; 10 x 7in. 6/9; 12 x 6in. 7/6; 12 x 8in. 8/- etc.

**EXPANDED ANODISED METAL**—Attractive Gilt Finish 3/2in. x 1/2in. diamond mesh or finer mesh 5/- per sq. ft.

**VINAIR**—Latest I.C.I. speaker covering. Mottled Light Grey, Off-White, Fawn, Black, etc. 2/- per sq. ft.

**BONDACOUST**—Speaker Cabinet Acoustic Wadding. 18 in. wide, 2/3 per ft. 6/- per yard.

**ENAMELLED COPPER WIRE** in two ounce reels. 14-20 g. 3/-; 20-28 g. 3/6; 30-34 g. 4/3; 39-40 g. 5/-.

**ALWAYS IN STOCK AT KEENE'S PRICES.** Transistors, Coils, Switches, Valves, Speakers, Materials. See latest TRS lists. Please send S.A.E. with enquiries.

## 7-valve AM/FM/RG Chassis

A superbly powerful high performance instrument. Ideal for building into existing cabinet work, etc. Tunes over long, medium and F.M. wavebands. Excellent sensitivity. Permeability tuning on F.M. Large clear dial, A.V.C. good neg. feedback. Magic eye. 3W output. A.C. 200/250V circuit diagrams available. Supplied ready built and aligned. S.A.E. brings full details. **£13.19.6.** (Carr. 10/-)

## To Order

Send cash with order. Post and packing where not stated add 1/- per lb.; 1/9, 1lb; 3/6, 2lb; 3/-, 3lb; 6/6, 10lb; 8/-, 14lb; over 10/- To help speed your order, quote PW.12 when ordering.

# TRS RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

Established 1946  
 Tel.: 01-684 2188. Hours 9 a.m.—6 p.m. 1 p.m. Wednesdays  
 A few doors from Thornton Heath Stn. (S.R. Victoria section)

# R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m.

—5.45 p.m.

All valves brand new and boxed

Closed Sat. 1.30—2.30 p.m.  
Open Daily to Callers

Tel. 769-0199/1649

1A7 7/9	6BH6 7/6	6K6GT 5/-	7S7 30/-	20L1 17/-	78 5/-	DF96 6/9	ECF82 7/-	EM80 7/6	PC97 8/9	RG5/500	UF89 7/8
1D5 7/-	6BJ6 9/-	6K7M 5/9	7Y4 8/6	20P4 19/-	80 7/-	DH77 4/6	ECH21 12/6	EM81 7/9	PC84 6/3	80/-	UL41 9/8
1H5 7/-	6BQ7A 7/-	6K7S 2/-	9BW6 7/-	20P5 18/-	85A2 7/8	DK32 7/9	ECH35 11/-	EM84 7/6	PC89 11/-	S130 35/-	UL84 7/7
1LD5 5/-	6BR7 3/6	6K7GT 4/6	10C1 12/6	25A6 5/9	1502B 9/6	DK91 5/6	ECH42 11/-	ESU15020/-	PC189 11/6	SP4 8/-	UM80 6/-
1NE5GT 8/-	6BR8 5/6	6K8M 8/6	10C2 12/6	25L6GT 5/8	150C4 7/6	DK92 8/-	ECH81 5/9	EY51 7/6	PCF80 7/-	SP41 3/6	UU6 13/6
1R5 5/6	6BS7 16/9	6K8G 3/7	10F1 9/-	25Y5 6/-	801 6/-	DK96 7/9	ECH83 8/6	EY86 7/-	PCF82 6/-	SP61 3/6	UU7 13/6
184 5/-	6BW6 14/-	6K8GT 7/-	10F8 8/-	25Z4 6/3	807 7/-	DL66 15/-	ECL80 7/-	EZ35 4/6	PCF84 8/-	STV280/80	UU9 8/-
185 4/-	6BW7 14/-	6K25 20/-	10F9 9/9	25Z5 7/-	813USA	DL92 4/9	ECL82 7/-	EZ40 8/-	PCF86 9/-	85/-	UY21 9/8
1T4 3/-	6C4 2/9	6L1 9/6	10F18 9/-	25Z6 8/8	120/-	DL93 3/6	ECL83 10/3	EZ41 10/-	PCF89 10/-	SU25 19/8	UY41 7/-
3A4 3/6	6C5G 4/-	6L6G 7/6	10L1 8/-	25D7 5/-	813 75/-	DL94 5/9	ECL86 9/-	EZ80 5/6	PCF8012/10/-	SU2150 12/6	UY85 6/6
3Q4 6/6	6C6 3/9	6L18 5/-	10LD11 15/-	30C1 6/3	866A 13/6	DL95 6/6	ECL88 9/-	EZ81 5/6	PCF805 13/6	T41 15/-	VMP4G 17/-
3Q5 6/6	6C8G 6/-	6Q7G 8/6	10P13 15/6	30C15 13/6	954 4/6	DL96 7/6	ECL800	GZ30 10/-	PCF806 13/6	U10 7/6	VP4B 25/-
384 4/9	6CD6G 22/-	6Q7GT 8/6	11E3 42/-	30C17 14/-	1625 5/6	DM70 7/-	EF9 20/-	GZ32 9/6	PCF808 11/6	U14 7/6	VR105/30
3V4 5/9	6CH6 5/9	6SA7M 7/6	12AT6 4/6	30C18 13/6	4022AR 50/-	DY86 6/-	EF37A 7/-	GZ34 11/-	PCL82 7/9	U19 35/-	VR150/30
5R4GY 8/9	6CW4 12/-	6SC7 7/-	12AT7 3/9	30C19 13/6	7193 2/-	R88CC 12/-	EF39 6/-	KT36 17/6	PCL83 9/8	U25 13/6	VT25 15/-
5U4G 4/-	6D6 2/9	6SG7 5/-	12AUG 5/9	30C21 14/-	7475 14/-	RA50 2/-	EF41 10/-	KT61 20/-	PCL84 7/9	U26 13/6	VT31 80/-
5V4G 3/-	6E5 7/6	6SH7 3/3	12AU7 4/9	30C22 13/6	AG1 7/9	RABCS0 7/-	EF50 4/6	KT66 17/6	PCL85 9/8	U78 3/6	VT52 15/-
5Y3GT 5/6	6F6G 8/-	6S7 5/3	12AX7 6/3	30C23 13/6	ATP4 2/3	EAF42 10/-	EF80 5/6	KT81 35/-	PCL86 9/8	U91 13/6	VR105/30
5Z4G 6/9	6F6G 4/6	6SK7GT 4/9	12BA6 6/-	30C24 14/-	ATP5 7/7	EB41 10/-	EF85 6/6	KT81 (7C5)	PEN44 20/-	U95 16/3	VU111 7/6
6/30L2 13/-	6F8G 4/6	6SL7GT 4/9	12BE6 5/9	30C25 13/6	ATP7 5/6	EB91 3/-	EF86 6/9	KT88 27/6	PEN44 20/-	U95 16/3	VU120 12/6
6A7 15/-	6F11 7/-	6SQ7 6/6	12C8GT 4/6	30C26 13/6	AU2 30/-	EBC33 7/-	EF89 5/-	KTW61 10/-	PEN45 7/9	U403 6/6	VU508 35/-
6A8G 12/6	6F13 5/6	6U4GT 12/-	12E1 17/6	30C27 13/6	AU5 7/6	EBC41 9/9	EF91 3/6	KTZ41 6/-	PEN46 2/9	U404 11/9	W81M 12/6
6AC7 3/-	6F14 12/6	6U5G 7/6	12J7GT 7/-	30C28 13/6	AZ1 8/-	EBC90 4/6	EF92 2/6	ML4 17/6	PL36 10/-	U801 23/6	XH1-5 5/-
6AK5 4/6	6F23 13/6	6V6M 8/-	12K7GT 6/-	35A5 12/6	CBL31 15/-	EBF83 3/3	EF98 15/-	ML6 6/-	PL81 8/-	UABC80 6/3	XPI-5 5/-
6AL5 3/6	6F24 12/-	6V6G 4/6	12K8GT 8/-	35L6 5/9	CCH35 21/-	EBF89 6/6	EF184 6/6	MSP4 10/-	PL83 6/-	UABC41 8/6	Y63 7/6
6AM5 2/6	6F25 12/-	6V6GT 6/6	12Q7GT 4/6	35W4 4/6	CL33 20/-	EEL1 14/-	EL32 3/6	MU14 7/6	PL84 6/9	UBC81 8/3	Y63 7/6
6AM6 3/6	6F28 11/6	6X4 3/6	12SA7 6/6	35Z3 10/-	CY30 16/3	EEL21 11/-	EL33 12/6	MX40 12/6	PL500 15/6	UBF80 6/9	3EG1 50/-
6AQ5 6/-	6G6 2/6	6X5G 4/6	12SB7 3/6	35Z4GT 5/6	CY31 10/-	EEL31 27/6	EL34 10/6	N78 15/-	PX4 14/-	UBF89 7/3	3FP7 19/-
6AS7G 15/-	6H6 2/6	6X5GT 6/6	12SB7 3/6	35Z5 5/6	DAC32 7/-	EC90 2/9	EL41 10/6	N108 25/-	PY33 9/6	UCC84 8/6	5CP1 35/-
6AT6 4/6	6J5M 6/6	7B6 11/6	12SJ7 3/9	37 5/-	DAF91 4/9	ECC81 3/9	EL42 10/6	NGT1 3/6	PY81 6/6	UCC85 7/6	AC1526 40/-
6AUG 6/-	6J5G 2/6	7B7 7/6	12SK7 4/9	42 5/-	DAF96 6/9	ECC82 4/9	EL42 10/6	NGT7 55/-	PY82 6/6	UCF80 8/6	ACR13100/-
6B4G 15/-	6J5GT 4/6	7C5 15/-	12SR7 5/-	50B5 6/6	DDC90 12/6	ECC83 6/8	EL84 4/9	OA2 5/9	PY83 6/6	UCH42 10/6	VCR97 35/-
6B8G 2/-	6J6 3/6	7C6 15/-	14H7 9/6	50C5 6/3	DF33 8/-	ECC84 6/6	EL90 6/6	OC3 5/9	PY800 10/6	UCH81 6/9	VCR517B
6BA6 5/-	6J7M 7/6	7D5 8/-	19AQ5 5/-	50CD6G 31/-	DF70 7/-	ECC85 5/-	EL95 5/6	OZ4 4/6	PY801 10/6	UCL82 8/-	VCR517C
6BB6 5/-	6J7G 4/9	7H7 6/6	20D1 10/-	50L6GT 6/-	DF91 3/-	ECC88 7/-	ELL80 20/-	PC86 11/6	R2 7/6	UCL83 10/-	VCR517C
	6J7GT 6/6	7R7 17/6	20F2 14/-	75 7/-	DF92 2/6	ECF80 6/6	EM34 25/-	PC88 11/6	R19 7/9	UF41 10/-	46/-

**SPECIAL 24 HOUR SERVICE**

OBSOLETE TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Postage 6d. per valve.

C.W.O. No C.O.D.

Manufacturers and Export Inquiries Welcome

**Special 24 Hour Express Mail Order Service**

**SETS OF VALVES**


DAF91, DF91, DK91, DL92 or DL94 19/- the set  
DAF96, DF96, DK96, DL96 27/6 the set

**BRAND NEW TRANSISTORS**

AC127 7/6	OC25 11/-	OC71 4/6	OC81 4/-	OC82D 6/-
AF114 7/-	OC28 16/-	OC72 6/-	OC81D 4/-	OC83 6/-
AF115 7/-	OC35 11/6	OC75 6/-	OC81DM	OC170 7/-
AF116 7/-	OC44 4/6	OC76 6/-	6/-	OC171 8/-
AF117 7/-	OC45 4/-	OC77 8/-	OC82 6/-	OC200 7/6

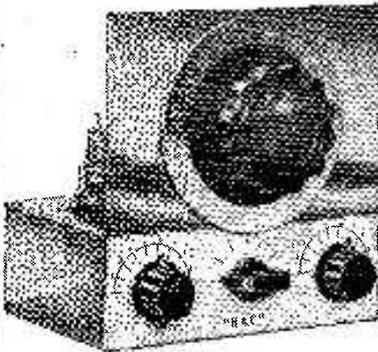**SEND S.A.E. FOR LIST OF 2,000 TYPES**

**H.A.C. SHORT-WAVE KITS**  
**WORLD-WIDE RECEPTION**



Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

**IMPROVED 1968 RANGE**

One-valve model "DX", complete kit—price 56/6 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

**"H.A.C." SHORT-WAVE PRODUCTS**  
29 Old Bond Street, London W.1

**AERIAL WIRE:** Coils of 25 yds., solid 2/3, plus 1/- P. & P

**TEST METERS:** Still available IT1/2 20 K ohms per volt, at £3.6.9, plus 3/- P. & P. Also stocked Taylor AVO T.M.K.

**TRANSFORMERS:** Instrument, 250 volt primary 250-volt secondary 6:3 volt 19/6, plus 3/9 P. & P. Charger, 4 amp for 6 or 12 volt, £1.2.6, plus 3/9 P. & P. Mains 250:0:250 sec 6:3 volt 60mA. 18/9, plus 3/9 P. & P.

**HIGH FREQUENCY HORNS:** 1½ to 4½ volt, ideal for alarm circuits. 3/6, plus 1/- P. & P.

**RELAYS:** 12 volt suitable for car alarm, heavy duty contacts, £1.1.9, plus 1/6 P. & P. Small relays for electronic uses, 130 ohm coil, 4 change over contacts operate 6 to 18 volt. 19/6, plus 1/- P. & P. iV-6V Relay, 1 NOC, 30 OHM, 5/-, plus 1/6 P. & P.

**EAR PIECES:** 3-5mm, 2-5mm magnetic, 2/6, plus 6d postage. 3-5mm, 2-5mm crystal, 5/6, plus 6d. postage

**LOUDSPEAKERS:** still available 8 ohm 2½in. 7/6, plus 1/- P. & P.

**VALVE HOLDERS:** B7g, B8a, B8g octal 6d., plus 6d. postage.

**COAX SOCKETS:** flush T.V. 6d., plus 6d. P. & P.

**PHONO PLUGS:** 5/- doz, plus 1/- P. & P.

**WAVE CHANGE SWITCHES:** 2 pole 6 way, 3/9, plus 1/- P. & P.

Many other items, please send stamp for free price list.



**BOTHWELL ELECTRIC SUPPLIES (Glasgow) LTD.**  
54 EGLINTON STREET,  
GLASGOW, C.5. Tel. 041 80Uth 2904

Member of the Lander Group

**NEW RANGE BBC 2 AERIALS**

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.  
**Loft Mounting Arrays,** 7 element, 37/6. 11 element, 45/-, 14 element, 52/6. 18 element, 60/-.  
**Wall Mounting with Cranked Arm,** 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6.  
**Mast Mounting with 2in. clamp,** 7 element, 42/6. 11 element, 55/-, 14 element, 62/-, 18 element, 70/-.  
**Chimney Mounting Arrays, Complete,** 7 element, 72/6. 11 element, 80/-, 14 element, 87/6. 18 element, 95/-.  
Complete assembly instructions with every unit. **Low Loss Cable,** 1/6 yd. U.H.F. Preamps from 75/-, State clearly channel number required on all orders.

**BBC - ITV AERIALS**



**BBC (Band 1),** Telescopic loft, 25/-, External S/D, 30/-, "H" £2.15.0.  
**ITV (Band 3),** 3 element loft array, 30/-, 5 element, 40/-, 7 element, 50/-, Wall mounting, 3 element, 47/6, 5 element, 52/6.  
**Combined BBC/ITV,** Loft 1+3, 40/-; 1+5, 50/-; 1+7, 60/-; Wall mounting 1+3, 57/6; 1+5, 67/6; Chimney 1+3, 67/6; 1+5, 75/-.  
**VHF transistor preamps,** 75/-.


**COMBINED BBC1 - ITV - BBC2 AERIALS** 1+3+9, 70/-, 1+5+9, 80/-, 1+5+14, 90/-, 1+7+14, 100/-.  
Loft mounting only. Special leaflet available.  
**F.M. (Band 2),** Loft S/D, 15/-, "H", 32/6. 3 element, 55/-, External units available. Co-ax cable 8d. yd. Co-ax plugs, 1/4. Outlet boxes, 5/-, Diplexer Crossover Boxes, 13/6. C.W.O. or C.O.D. P. & P. 5/- Send 6d. stamps for illustrated lists.

Callers welcomed - open all day Saturday

**K.V.A. ELECTRONICS (Dept. P.W.)**  
27 Central Parade, New Addington  
Surrey (CRO-OJB)  
LODGE HILL 2266
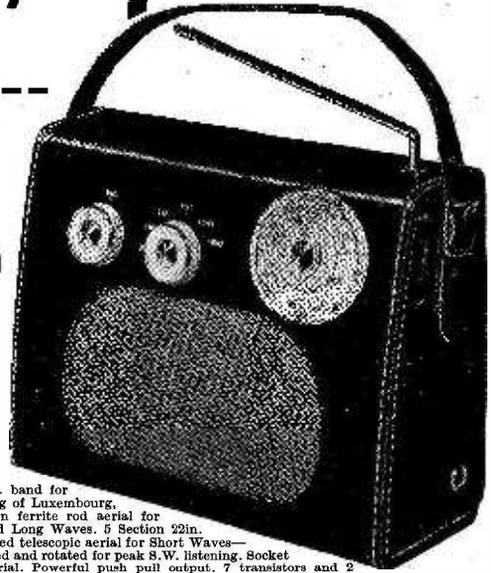
# Build yourself a quality transistor radio

guaranteed results  
backed by our  
after sales service!



## roamer seven mk IV

SEVEN WAVEBAND PORTABLE AND CAR RADIO WITH A SUPER SPECIFICATION GIVING OUTSTANDING PERFORMANCE!

7 FULLY TUNABLE WAVEBANDS—

MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.

### pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND (to 50 metres approx.) PORTABLE WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 5½ x 1½ x 3½in. Fully tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs  
**44'6** P. & P.  
3/6

Extra M.W. band for easier tuning of Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. 5 Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push pull output. 7 transistors and 2 diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker for rich-tone volume. Air spaced ganged tuning condenser. Separate on/off switch, volume control, wave change switches and tuning control. Attractive case with hand and shoulder straps. Size 9 x 7 x 4in. approx. First grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build with guaranteed results.


Total building costs  
**£5.19.6** P. & P.  
7/6 Personal Earpiece with switched socket for private listening 5/- extra.

Parts price list and easy build plans 3/- (Free with parts).
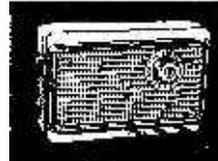
### transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND (to 50 metres approx.) PORTABLE WITH 3in. SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. Fully tunable. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. All first grade components. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs  
**47'6** P. & P.  
3/9

### super seven

THREE WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case size 7½ x 5½ x 1½in. with gilt fittings. The ideal radio for home, car or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 2 R.F. Stages, push pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Easy build plans and parts price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 5/- extra).



Total building costs  
**69'6** P. & P.  
4/6

### roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. World wide reception. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 5/- extra).



Total building costs  
**79'6** P. & P.  
4/6

## NEW LOOK melody six

TWO WAVEBAND PORTABLE

8 stages—6 transistors and 2 diodes. Covers Medium and Long Waves. Top quality 3in. Loudspeaker for quality output and also with Personal Earpiece with switched socket for private listening. Two R.F. stages for extra boost. High "Q". Ferrite Rod Aerial. Push-pull output. Handsome pocket size case with gilt fittings. Size 6½ x 4 x 2in. Easy build plans and parts price list 2/- (FREE with parts).



Total building costs  
**69'6** P. & P.  
4/3

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. Bedford 52367

I enclose £..... please send items marked

ROAMER SEVEN	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	SUPER SEVEN	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	MELODY SIX	<input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....

\* Callers side entrance Stylo Shoe Shop  
\* Open 10-1, 2.30-4.30 Mon-Fri. 9-12.30 Sat

# SEW PANEL METERS

Send S.A.E. for full lists. Other ranges available. Please include postage. Special quotations for quantities.



**CLEAR PLASTIC METERS**

**Type MR.38P. 1 1/2" x 3/4" square fronts.**

50μA	37/6	750mA	25/-
50-0-50μA	35/-	1 amp	25/-
100μA	35/-	2 amp	25/-
100-0-100μA	32/8	5 amp	25/-
200μA	32/6	3V. D.C.	25/-
500μA	37/6	10V. D.C.	25/-
500-0-500μA	26/-	20V. D.C.	25/-
1mA	25/-	50V. D.C.	25/-
1-0-1mA	25/-	100V. D.C.	25/-
2mA	25/-	150V. D.C.	25/-
5mA	25/-	300V. D.C.	25/-
10mA	25/-	500V. D.C.	25/-
20mA	25/-	750V. D.C.	25/-
50mA	25/-	15V. A.C.	25/-
100mA	25/-	50V. A.C.	25/-
150mA	25/-	150V. A.C.	25/-
200mA	25/-	300V. A.C.	25/-
300mA	25/-	500V. A.C.	25/-
500mA	25/-	8 meter IMA	39/6
		VU meter	39/6

**Type MR.45P. 2in. square fronts.**

50μA	42/6	10V. D.C.	27/6
50-0-50μA	39/6	20V. D.C.	27/6
100μA	39/6	50V. D.C.	27/6
100-0-100μA	35/-	300V. D.C.	27/6
500μA	29/6	15V. A.C.	27/6
1mA	27/6	300V. A.C.	27/6
5mA	27/6	8 meter IMA	35/-
10mA	27/6	VU meter	42/6
50mA	27/6	1 amp. A.C.*	27/6
100mA	27/6	5 amp. A.C.*	27/6
500mA	27/6	10 amp. A.C.*	27/6
1 amp	27/6	20 amp. A.C.*	27/6
5 amp	27/6	30 amp. A.C.*	27/6

**Type MR.52P. 2 1/2in. square fronts.**

50μA	59/6	100-0-100μA	45/-
50-0-50μA	49/6	500μA	42/6
100μA	49/6	1mA	37/6

## BAKELITE PANEL METERS

**Type MR.65. 3 1/2in. square fronts.**

25μA	67/6	500mA	32/6
50μA	45/-	1 amp	32/6
50-0-50μA	42/6	5 amp	32/6
100μA	42/6	15 amp	32/6
100-0-100μA	42/6	30 amp	32/6
500μA	39/6	50 amp	32/6
1mA	32/6	5V. D.C.	32/6
1-0-1mA	32/6	10V. D.C.	32/6
5mA	32/6	20V. D.C.	32/6
10mA	32/6	50V. D.C.	32/6
50mA	32/6	150V. D.C.	32/6
100mA	32/6	300V. D.C.	32/6

300V. D.C.	37/6	300V. A.C.	37/6
10mA	37/6	8 Meter IMA	39/6
50mA	37/6	VU Meter	59/6
100mA	37/6	1 amp. A.C.*	37/6
500mA	37/6	5 amp. A.C.*	37/6
1 amp.	37/6	10 amp. A.C.*	37/6
5 amp.	37/6	20 amp. A.C.*	37/6
10V. D.C.	37/6	30 amp. A.C.*	37/6
20V. D.C.	37/6		
50V. D.C.	37/6		

## Type MR.85P. 4 1/2in. x 4 1/2in. fronts.

50μA	69/6	15 amp.	49/6
50-0-50μA	59/6	30 amp.	49/6
100μA	59/6	20V. D.C.	49/6
100-0-100μA	59/6	50V. D.C.	49/6
200μA	55/-	150V. D.C.	49/6
500μA	52/6	300V. D.C.	49/6
500-0-500μA	49/6	15V. A.C.	49/6
1mA	49/6	300V. A.C.	49/6
1-0-1mA	49/6	8 meter IMA	55/-
5mA	49/6	VU meter	69/6
10mA	49/6	1 amp. A.C.*	49/6
50mA	49/6	5 amp. A.C.*	49/6
100mA	49/6	10 amp. A.C.*	49/6
500mA	49/6	20 amp. A.C.*	49/6
1 amp.	49/6	30 amp. A.C.*	49/6
5 amp.	49/6		


## Type MR.65P. 3 1/2in. x 3 1/2in. fronts.

50μA	65/-	50V. D.C.	39/6
50-0-50μA	52/6	150V. D.C.	39/6
100μA	52/6	300V. D.C.	39/6
100-0-100μA	49/6	15V. A.C.	39/6
500μA	45/-	50V. A.C.	39/6
1mA	39/6	150V. A.C.	39/6
5mA	39/6	300V. A.C.	39/6
10mA	39/6	500V. A.C.	39/6
50mA	39/6	8 meter IMA	45/-
100mA	39/6	VU meter	65/-
500mA	39/6	50mA A.C.*	39/6
1 amp.	39/6	100mA A.C.*	39/6
5 amp.	39/6	200mA A.C.*	39/6
10 amp.	39/6	500mA A.C.*	39/6
15 amp.	39/6	1 amp. A.C.*	39/6
20 amp.	39/6	5 amp. A.C.*	39/6
30 amp.	39/6	10 amp. A.C.*	39/6
50 amp.	39/6	20 amp. A.C.*	39/6
10V. D.C.	39/6	30 amp. A.C.*	39/6
20V. D.C.	39/6		



\*Moving iron, all other moving coil.


## NEW RANGE OF "SEW" EDGEWISE METERS

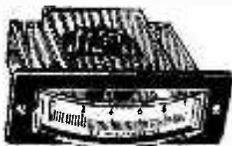

MODEL PE 70. Dimensions 3 1/2" x 1 1/2" x 2 1/2". deep overall. Available as follows:

50 microamp	57/6	500 microamp	49/6
50-0-50 microamp	55/-	1 milliamp	45/-
100 microamp	55/-	300 volt A.C.	45/-
100-0-100 microamp	52/6	VU meter	62/6
200 microamp	52/6	Post extra.	

## TE-200 RF SIGNAL GENERATOR

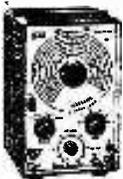

Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 7/6. Size 140 x 215 x 170 mm.

## T.M.C. 1000 SERIES KEY SWITCHES



Brand new with knobs as follows:

1 way, 2 c/o, 7/6; 1 way, 2 c/o 2h, 7/6; 1 way 4 c/o, 8/-; 2 way, 3m, 3m, 8/6; 2 way, 2 c/o, 2 c/o, 8/6. Post extra. Quantities available.

## NOMBREX TRANSISTORISED TEST EQUIPMENT

All Post Paid with Battery



Model 22. Power Supply 0-15V DC	£14.10.0
Model 30. Audio Generator	£19.10.0
Model 31. R.F. Signal Generator.	£12.10.0
Model 32. C.R. Bridge.	£10.10.0
Model 33. Inductance Bridge.	£20.0.0
Model 66. Inductance Bridge.	£18.0.0
Model 61. Power Supply.	£6.10.0


## TY75 AUDIO SIGNAL GENERATOR

Sine Wave 20 CPS-200 Kc/s. Square Wave 20 CPS-30 Kc/s. High and low impedance output. Output variable up to 8 volts. 220/240 volts A.C. Brand new with instructions. £16. Carr. 7/6. Size 210 x 150 x 120 mm.



CT.53 SIGNAL GENERATORS. 8-9-15-5 and 20-300 Mc/s. Output 1μV-100mV. Mains operated. Perfect condition less charts. £12.10.0. Carr. 15/-.

## AVO CT.38 ELECTRONIC MULTIMETERS

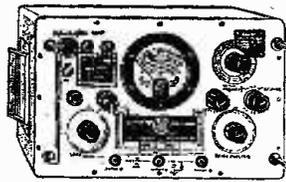

High quality 97 range instrument which measures A.C. and D.C. Voltage, Current, Resistance and Power Output. Ranges D.C. volts 250mV-10,000V. (10 megΩ-110 megΩ input). D.C. current 10μA-25 amps. Ohms: 0-1,000 megΩ. A.C. volt 100mV-250V (with R.F. measuring head up to 250 Mc/s) A.C. current 10μA-25 amps. Power output 50 micro-watts-5 watts. Operation 0/110/200/250V. A.C. Supplied in perfect condition complete with circuit lead and R.F. probe. £25. Carr. 15/-.

## TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2cps-750 Kc/s. Bandwidth 5-5 Mc/s. Sensitivity 38mV/CM. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.

## AM/FM SIGNAL GENERATORS



Oscillator Test No. 2. A high quality precision instrument made for the Ministry by Airmes. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9 1/2 in. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. 20/-.

## ADMIRALTY B.40 RECEIVERS

Just released by the Ministry. High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 650 Kc/s-30 Mc/s. I.F. 500 Kc/s. Incorporates 2 R.F. and 3 I.F. stages, band-pass filter, noise limiter, crystal controlled B.F.O., calibrator, O.F. output, etc. Built-in speaker, output for phones.



Operation 150/230 volt A.C. Size 19 1/2 x 19 1/2 x 16 1/2 in. Weight 11 1/2 lbs. Offered in good working condition. £22.10.0. Carr. 30/- With circuit diagrams. Also available B.41 L.F. version of above. 15 Kc/s-700 Kc/s. £17.10.0. Carr. 30/-.



## MARCONI CT44/TF956

AF Absorption Wattmeter

1 μ/watt to 6 watts: £20. Carr. 10/-.

## COSSOR DOUBLE BEAM OSCILLOSCOPES

Type 1035. General purpose. A.C. Coupled. £35 each. Carr. 30/-.



## AVOMETERS

Supplied in excellent condition, fully tested and checked. Complete with prods, leads and instructions.

Model 47A £9.19.6. P. & P. 7/6 each.


## CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. £5.19.6. Carr. 7/6. Or brand new with accessories. £7.19.6. Carr. 7/6.
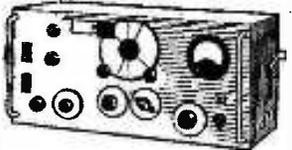
## MARCONI TEST EQUIPMENT

EX-MILITARY RECONDITIONED. TF.144G STANDARD SIGNAL GENERATORS. 85 Kc/s-25 Mc/s. £25. Carr. 30/- T.F.385 VIDEO OSCILLATOR 0-5 Mc/s. £45. Carr. 30/- T.F.195M BEAT FREQUENCY OSCILLATOR 0-40 Kc/s. 200/250V. A.C. £20. Carr. 30/- T.F.142E Distortion Factor Meter £20. Carr. 20/- All above offered in excellent condition, fully tested and checked. T.F.1100 VALVE VOLTMETER. Brand New, £50. T.F.1267 TRANSMISSION TEST SET, Brand New, £75. TF.1371 Wide Band Millivolt Meter. Brand New £50.



## Variable Voltage TRANSFORMERS



Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 50-60 cycles. Output full variable from 0-260 volts. Bulk quantities available. 1 amp. -£5.10.0; 2.5 amp. -£6.15.0; 5 amp. -£9.15.0; 8 amp. -£14.10.0; 10 amp. -£18.10.0; 12 amp. -£21.0.0; 20 amp. -£37.0.0.

## AMERICAN TAPE

First grade quality American tapes.

Brand new. Discount on quantities.	
3in. 225ft. L.P. acetate	3/6
3 1/2in. 600ft. T.P. mylar	10/-
5in. 600ft. std. plastic	8/6
5in. 900ft. L.P. acetate	10/-
5in. 1,200ft. D.P. mylar	15/-
5in. 1,800ft. T.P. mylar	22/6
5 1/2in. 1,200ft. L.P. acetate	12/6
5 1/2in. 1,200ft. L.P. mylar	16/-
5 1/2in. 1,800ft. D.P. mylar	2/6
5 1/2in. 2,400ft. T.P. mylar	39/6
7in. 1,200ft. std. acetate	12/6
7in. 1,800ft. L.P. acetate	15/-
7in. 1,800ft. L.P. mylar	20/-
7in. 2,400ft. D.P. mylar	25/-
7in. 3,600ft. T.P. mylar	45/-
Postage 2/- Over £3 post paid.	

## TAPE CASSETTES

C80-60 minutes	10/3
C90-90 minutes	14/3
Over £3 post paid.	

LUCAS 20/0/20 AMMETERS. Brand new boxed. Suitable car/motorcycle. 12/6. P. & P. 2/-.

EVERSHED VIGNOLES SERIES II 500 VOLT MEGGERS. Perfect condition £21. P. & P. 10/-.

DUBILIER NITROGEL CONDENSERS. Brand new. 8 mfd. 300V. 8/6. P. & P. 2/-; 2 mfd. 5,000V. 42/6. P. & P. 5/-.

## OMRON MK2 RELAYS



Brand New and Boxed. 24V. D.C. coils. 2 Pole changeover. 5 amp. contacts. 7/6 each. P. & P. 1/6.

## LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

0-20 Kc/s. Output 5 K or 500 ohms. 200/250 V. A.C. offered in excellent condition. £12.10.0. Carriage 10/-.

WS.88 TRANS/RECEIVERS. A and B sets available. Complete with valves. 39/6 each. P. & P. 4/6. Accessories available.

G. W. SMITH & CO (RADIO) LTD. 3-34 Lisle St., W.C.2. Also see oppo. page

# MULTIMETERS for EVERY purpose!

**LAFAYETTE DE-LUXE 100K $\Omega$ /VOLT "LAB TESTER."** Giant 6 $\frac{1}{2}$  in. scale. Built-in meter protection. 0/5/2-5/10/50/250/500/1,000 V.C. 0/3/10/50/250/500/1,000V A.C. 0/10/100 $\mu$ A/10/100/500mA/2-5/10A. 0/1K/10K/100K/1.0M/10M $\Omega$ . -10 to 49-4dB. £18.18.0. P. & P. 5/-.

**LAFAYETTE 57 Range Super 50k $\Omega$ /volt Multi-meter.** D.C. volts 125mV -1000V. A.C. volts 1-5V -1000V. D.C. current 25/1A-10 amp. Ohms 0-10meg $\Omega$ . dB -20 to +81 dB. Overload protection. £12.10.0. Carr. 3/6.

**NEW MODEL 500 30,000 O.P.V.** with overload protection. mirror scale 0/5/2-5/10/25/100/250/500/1,000V. D.C. 0/2-5/10/25/100/250/500/1,000V. A.C. 0/50/150/500mA. 12 amp. D.C. 0/60K/6 Meg./60 Meg. $\Omega$ . £8.17.6. Post paid.

**PROFESSIONAL 20,000 O.P.V. LAB. TYPE Multi-tester.** Automatic overload protection. mirror scale. Ranges: 1/10/50/250/500/1,000 volts. D.C. and A.C. 0-500 $\mu$ A, 10mA, 250mA. Current: 0/20K, 200K, 2 megohm. Decibels: -20 to +22dB. £5.19.6. P. & P. 2/6.

**MODEL TE-70.** 30,000 O.P.V. 0/2-5/10/25/100/250/500/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30/150/3/30/300mA. 0/16K/150K/1-6M/16 Meg.  $\Omega$ . £5.10.0. P. & P. 3/-.

**MODEL 2501.** 2,000 O.P.V. 0/10/50/500/2,500V. D.C. 0/10/50/500/2,500V. A.C. 0/2 Meg.  $\Omega$ . 0/250 mA. -20 to +38dB. 49/6, P. & P. 2/6.

**TE-900 20,000 $\Omega$ /VOLT GIANT MULTIMETER** mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2-5/10/250/1,000/5,000/20K/20 MEG. OHM. £15. P. & P. 5/-.

**MODEL AS-100D.** 100K $\Omega$ /VOLT. 5in. mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200V. D.C. 0/6/30/120/300/600V. A.C. 0/10 $\mu$ A/6/60/300mA/12 amp. 0/2K/200K/2M/300M $\Omega$ . -20 to +17dB. £12.10.0. P. & P. 3/6.

**MODEL AF-105.** 50k $\Omega$ /Volt. Mirror scale, built-in meter protection. 0/3/12/60/120/300/600/1,200V. D.C. 0/6/30/120/300/600/1,200V. A.C. 0/30 $\mu$ A/6/60/300mA/12 Amp. 0/10K/1M/10M/100M $\Omega$ . -20 to +17dB. £8.10.0. P. & P. 3/6.

**MODEL TE-12** 30,000 O.P.V. 0/2-5/10/25/100/250/500/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/60/150/6/60/600mA. 0/6K/600K/6 Meg./60 Meg. $\Omega$ . 50pF. 0-2 mfd. £5.18.6. P. & P. 3/6.

**MODEL TE-30.** 20,000 O.P.V. 0/10/50/100/500/1,000V. A.C. 0/5/25/50/250/500/1,000V. D.C. 0-50 $\mu$ A, 5/50/500mA. 0/6K/600K/6 K/6 meg. £4.17.6. P. & P. 3/-.

**MODEL PT-34.** 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/100/500mA. 0/6K/600K/6 K/6 meg. £3.9/6. P. & P. 1/6.

## UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kc/s-30 Mc/s. Incorporates variable BFO for CW/SSB reception. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6. **13 gns.**

## LAFAYETTE HA-700 AM/CW/SSB AMATEUR COMMUNICATION RECEIVER

8 Valves, 5 bands incorporating 2 MECHANICAL FILTERS for exceptional selectivity and sensitivity. Frequency coverage on 5 bands 150-400 Kc/s, 550/1,600 Kc/s, 1.6-4.0 Mc/s, 4.8-14.5 Mc/s, 10-5-30 Mc/s. Circuit incorporates B.F. stage, aerial trimmer, noise limiter, B.F.O. product detector, electrical band-pass, 8 meter, slide rule dial. Output for phones, low to 2k $\Omega$  or speaker 4 or 8 $\Omega$ . Operation 220/240V. A.C. Size 7 $\frac{1}{2}$  x 15 x 10in. Supplied brand new and guaranteed with handbook. 38 gns. Carr. 10/-, S.A.E. for leaflet.

## NEW LAFAYETTE SOLID STATE HA600 RECEIVER

5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE. 150 Kc/s-400 Kc/s and 550 Kc/s-30 Mc/s. F.E.T. front end & 2 mechanical filters. Huge dial & Product detector & Crystal calibrator. Variable BFO & Noise limiter. 8 Meter & 24 in. Bandpass. & 230V A.C./12V D.C. neg. earth operation. RF gain control. Size 15in. x 9in. x 8in. Wt. 15 lbs. EXCEPTIONAL VALUE £45. Carr. 10/-, S.A.E. for full details.

## TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550 Kc/s to 30 Mc/s, continuous and electrical bandspread on 10, 15, 20, 40 and 80 meters. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW & AM. Variable BFO & S meter & Sep. bandspread dial. IF 455 Kc/s & Audio output 1-5 W. Variable RF and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. £39.15.0. carr. paid. SPECIAL OFFER - Trio Communication Type Headphones. Normally £5.19.6. OUR PRICE £3.15.0 if purchased with receiver.

## LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 152-174 Mc/s. Fully tuned or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output 75 $\Omega$  aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. £37.10.0. Carr. 10/-.

## LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER

19 transistors, 8 diodes, IHF music power, 30W at 8 $\Omega$ . Response 30-20,000 c.p.s. at 1W. Distortion 1% or less. Inputs 3mV and 250mV. Output 3-16 $\Omega$ . Separate L and R. volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complementary metal case. Size 10 $\frac{1}{2}$  x 8 9/16 x 7 19/16in. Operation 115/230V. A.C. £28. Carriage 7/6.

## GARRARD DECKS

Brand new and guaranteed.

1900 mono	£6.60
1925 mono	£7.10.0
1925 stereo	£7.19.6
2025 TC less cartridge	£7.19.6
SP25 Mk. II less cartridge	£12.10.0
A70 Mk. II less cartridge	£12.12.0
LAB80 Mk. II less cart. with base	£27.10.0

Carr. 7/6 each.

Wooden Plinths for Garrard Series 1,000, 2,000, 3,000, etc., with perspex cover. £4.10.0. P. & P. 4/6.

## GARRARD TAP MOTOR

Brand new stock as used by famous manufacturer. 200/250V. A.C. Capstan motor 15/-, Fast Forward 10/6, Fast Rewind 10/6. P. & P. 3/-, Set of three motors £2/6. P. & P. 5/-.

## RECORDING HEADS

Router 1-track. As fitted to Collaro Mk. IV and Studio Decks. High imp. record playback, low imp. erase. Brand new. 19/6 pair. Minifix & track, record 12/6.

Cosmoord 1 Track Heads	65/-
High imp. record/playback	20/-
Low imp. erase	20/-
Marriott 1 Track Heads	65/-
High imp. record/playback	20/-
Low imp. erase	20/-

Post extra.

## ★ TRANSISTORISED FM TUNER ★

6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6 x 4 x 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6.7.6. P. & P. 2/6. Stereo multiplex adaptors 5 gns.

## HOSIDEN DHO4S 2-WAY STEREO HEADPHONES

Each headphone contains a 2in. woofer and a 3in. tweeter. Built in individual level controls 25-18,000 c.p.s. 6 $\frac{1}{2}$  imp. with cable and stereo plug. £5.19.6. P. & P. 2/6.

## AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

150 W.	£12.6. P. & P. 3/6.
300 W.	£27.6. P. & P. 3/6.
500 W.	£31.0. P. & P. 6/6.
1,000 W.	£5.10.0. P. & P. 7/6.
1,500 W.	£6.10.0. P. & P. 8/6.
3,000 W.	£7.10.0. P. & P. 12/6.
7,500 W.	£15.10.0. P. & P. 20/-.

## ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons

**VM.76 VALVE VOLTMETER**  
R.F. measurements in excess of 100 Mc/s and D.C. measurements up to 1000V, with accuracy of  $\pm 2\%$ . D.C. range 300 MV to 1 KV. A.C. range 300 MV to 300 V RMS. Resistance -02-500 M $\Omega$ . Price £72.

**VM.78 A.C. MILLIVOLT METER**  
Transistorised 1 MV-300V. Frequency 1 c/s to 1 Mc/s. Price £55.

**VM.79 UHF MILLIVOLT METER**  
Transistorised. A.C. range 10 MV-5V. D.C. current range 0.1 $\mu$ A-3mA. Resistance 1 ohm-10 megohms. Price £125.

**H1B AUDIO SIGNAL GENERATOR**  
15 c/s-50 Kc/s, sine or square wave. Price £30.

**J1B AUDIO SIGNAL GENERATOR**  
15 c/s-50 Kc/s. Price £30.

**J2B AUDIO SIGNAL GENERATOR**  
As per J1B except fitted with output meter. Price £35.

**TT1S TRANSISTOR TESTER**  
£37.10.0. Carriage 10/- per item.

## NO.76 TRANSMITTER

2-12 Mc/s. Crystal Controlled (not supplied). 807PA. Operation 12V. D.C. (Rotary transformer). 9 watts output. C.W. only. New condition. 72/6. Carr. 12/6.

## FIELD TELEPHONES TYPE L

Generator ringing, metal cases. Operates from two 1-5V. batteries (not supplied). Excellent condition. £4.10.0 per pair. Carr. 10/-.

## TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.6. P. & P. 3/6.

## INTERCOM/BABY SITTER

Transistorised Intercoms, ideal for home/office/workshop etc. 2-way buzzer call system. For desk or wall mounting. Supplied complete with connecting wire, batteries, instructions. 4 station £3.12.6. P. & P. 5/-.

## MODEL ZQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec: A: 0-7-0-9967. B: 5-200. Ico: 0-50 microamps. 0-5mA. Resistance for diode 200 $\Omega$ -1M $\Omega$ . Supplied complete with instructions, battery and leads. £5.19.6. P. & P. 2/6.

## CREED MORSE REPERFORATORS

TYPE 7W/3 200/240V. D.C. Brand new £15. Carriage 80/-.

# O.W. SMITH & CO. (RADIO) LIMITED

Phone GERRARD 8224/9135  
Cables: SMITHEX LESQUARE

3-34 LISLE STREET, LONDON, W.C.2

OPEN

9 a.m. to 6 p.m. every day Monday to Saturday. Trade supplied.

# CODAR CR.70A

## Communications Receiver 540-10 metres



The Codar CR.70A is an excellent general coverage communications receiver for the keen short wave listener. Very reasonably priced at just £19.10.0 the CR.70A is outstanding value for money. In four stable ranges, the receiver covers from 540 metres medium wave, right through the shipping and coastguard frequencies all the short wave and international amateur bands up to and including 10 metres, where the rapidly improving conditions that now prevail allow the regular reception of world-wide call-signs!

The CR.70A has a high 'Q' aerial input stage giving extremely high gain with low noise level. Double tuned, iron cored I.F. transformers produce high selectivity. Ready to plug into 200-250 volt A.C. mains, the CR.70A needs only your aerial and a 2-3 ohm loudspeaker. The cabinet measures only 13" x 5 1/2" x 7 1/2" and the control panel is finished in black and white with chrome trim knobs. Fully guaranteed for 12 months!

Buy your Codar equipment from your radio hobby store or direct from Codar. The order form will also bring fully descriptive leaflets (8d stamps appreciated).

STILL ONLY


# 19.10.0

Carriage 7/6 extra.


- \*Ideal for SWLs \*5 valves (inc. two twin triodes) giving 7 valve line-up
- \*Excellent on amateur and shipping frequencies
- \*Calibrated signal strength meter (illuminated)
- \*Automatic volume control
- \*Separate B.F. oscillator for morse and S.S.B. signals
- \*Two speed vernier tuning



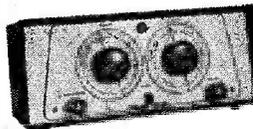
**T28 RECEIVER FOR 160 & 80 METRES AMATEUR BANDS**  
 9 transistors, bandspread 1.8-2Mc/s and 3.5-4Mc/s 12 volts, only 8" x 4" x 3 1/2". Ideal portable, mobile or home receiver. Efficient BFO, printed circuits. ONLY £15.17.6. Carr. 4/6.



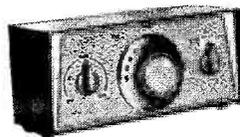**CR45 MAINS T.R.F. SHORT-WAVE RECEIVER**  
 World wide reception. \*Separate electrical band-spread. \*3 slow motion drives. \*Output 3 watts for 2/3 ohm speaker. \*Valves ECC81, EL84, EZ80. Size 12" x 5 1/2" x 7". CODAR-KIT CR.45K with 3 coils (10-28, 25-75, 60-176 metres). £9.15.0. Carr. 6/-, or ready built CR.45 £11.19.6. Carr. 6/-, Extra coils 5/4 each.



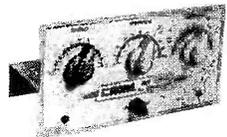**R.F. PRE-SELECTOR MODEL P.R.30**  
 1.5-30Mc/s  
 Provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Power requirements 100-250 volts 12mA H.T. 6.3 volts, .3 amp L.T. Size 8 1/2" x 5" x 4". Ready built complete with cables, plugs and instructions. £5.19.6. Carr. 4/6. Self-powered P.R.30x £7.19.6. Carr. 4/6.



**MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER**  
 \*Can be built in one evening. \*Complete with valve, one coil 25-75 metres and 4 page instruction manual. Price £2.4.6. Carr. 3/-. Extra coils 5/4

# CRC

**CODAR RADIO COMPANY**

BANK HOUSE, SOUTHWICK SQUARE, SOUTHWICK, SUSSEX. TEL: 3149  
 World-wide Mail Order Service

Please supply (tick as required)  
 I enclose cheque/M.O./P.O. value of £.....  
 8d stamp enclosed for leaflets

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

**POST ORDER FORM TODAY**

# PRACTICAL WIRELESS

VOL 44 No 8

Issue 742

DECEMBER 1968

## TOPIC OF THE MONTH

### No Title

**M**ANY writers say that finding a telling title for a piece of prose is the hardest part of the exercise. Certainly, with a good heading in front of you, the task becomes lighter, more purposeful, for the headlines contain the terms of reference for what follows. It's rather like the chicken and the egg teaser—what comes first, title or text?

One writer who adopts the title-first gambit is our columnist Henry. When we approached him to take on a regular feature he sat, pondered, then sprang to life with the suggestion "Practically Wireless". Very apt, he claimed: "practically" (in a practical manner), "wireless" (wireless), "by Henry" (one of my pet names used specifically by the wife when about to ask awkward questions). In effect, he went on, a column dealing with practical aspects of wireless written to provoke discussion and controversy.

And we fell for it, not realising that even the neatest of titles can boomerang owing to different connotations of the words. Consequently, Henry has had to endure the occasional quip that although his *critiques* are sometimes *practically wireless* they often don't make it. And last week, a reader suggested that Henry was none other than the proprietor of one of our well-known advertisers and was thus riding two horses at once!

But whatever the merits of the title, there is no doubt that the feature has done the job intended. Henry effects a deliberate light-hearted approach, but regular readers will know that underlying the humour lurk penetrating and shrewd thrusts born of an intimate knowledge of what goes on in the world of radio and electronics.

Alas, even the best of contributors have their black sides. Aided and abetted by his accomplice Pax (another pseudonym, not a new detergent), who has provided the illustrations, he has conspired to work in scurrilous (and libellous) digs at your editor which have been eliminated only by the utmost diligence.

This month, however, they have been allowed to get one through the censor, simply as a generous salute to the fact that they have now passed the 50 mark. Congratulations, and may the next 50 episodes be as entertaining. Finally, not having the genius(?) of Henry we were stuck for a title for this leader. Hence the title!

W. N. STEVENS—*Editor*.

## NEWS AND COMMENT

Leader	571
News and Comment	572
Letters to the Editor	601
Practically Wireless <i>by Henry</i>	605
On the Short Waves <i>by Christopher Danpure and David Gibson, G3JDG</i>	613

## CONSTRUCTIONAL

The Mini-3 <i>by R. F. Graham</i>	574
Absorption Wavemeter, Radiation Meter and Phone Monitor <i>by A. D. Taylor, GW8PG</i>	580
Pyramid All Purpose System, Part 4 T.R.F. Tuner and Gram Deck <i>by F. G. Rayer</i>	590
Practical Telephone Systems <i>by C. H. Moller</i>	606
Unijunction Transistor Circuits, Part 2 <i>by C. R. Bradley</i>	617

## OTHER FEATURES


P.W. Guide to Components, Part 1—Resistors <i>by M. K. Titman, B.Sc.(Eng.)</i>	577
Practical Guide to F.E.T.s <i>by K. Royal</i>	582
Audio Supplement	593

JANUARY ISSUE WILL BE PUBLISHED  
ON DECEMBER 8th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes Rand London. Subscription rates, including postage: 42s. per year to any part of the world. © George Newnes Ltd., 1968. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.


# NEWS AND COMMENT...

## NEW "BIB" TOOL

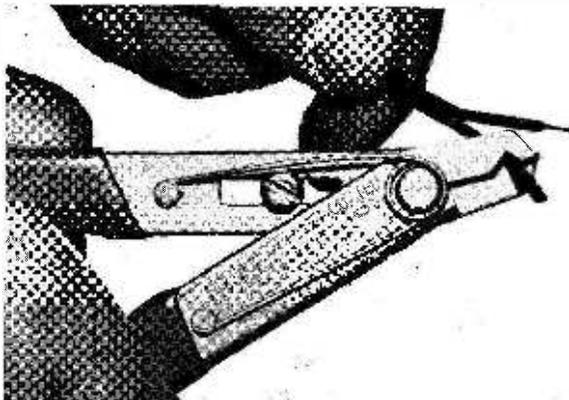

Multicore Solders Ltd., Hemel Hempstead, Herts., introduce their Model 6 Bib wire stripper and cutter. It enables insulation to be removed without nicking the wire and the aperture setting for different diameters is simply adjusted by a sliding screw set in one of the handles. This cutter also features two cutting positions—one for normal flex and the other for cutting wire after it has been connected to a tag or bolt. Price of the Model 6 is 8s 6d.

## MINIATURISING HI-FI

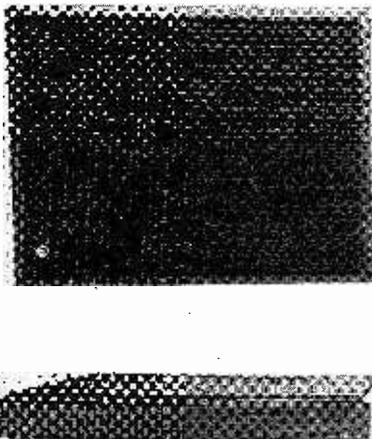

Oakland Trading Co. of London announce the new P.20 speaker unit.

The unit has an excellent response value within a frequency range of 40c/s to 20kc/s, but what is surprising is that the P.20, complete in a solid teak waterproof cabinet is only 21 inches deep. This will certainly enable the enthusiast to miniaturise his installation.

It has sensitivity rating of 85dB/M for 1W and a power capability of 20W peak (10W r.m.s.).


The P.20 measures 18 inches high by 14 inches wide.

Further details from: The Oakland Trading Company, 68 Lupus Street, London, S.W.1.

## BETTER RADIO 2 IN SCOTLAND

A substantial improvement in the signal strength of Radio 2 in parts of Southern Scotland is expected following the installation of four new broadcasting transmitters ordered recently from the Marconi Company by the BBC. The equipment radiates the Radio 2 signal in the medium waveband and provides a service to hundreds of thousands of listeners in Glasgow and Edinburgh areas.

## NEW SYNCHRONISER FOR TAPE AND FILM

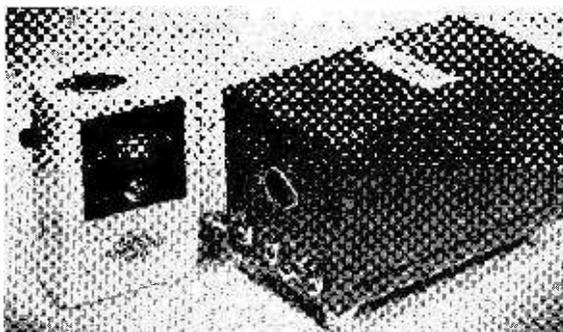

Now, with the introduction of new low-cost equipment from "Carol" Cinesound, recording anywhere in lip-sync precision with the movie film is possible and incredibly simple. The additional recording unit R.1 required is not much bigger than a packet of cigarettes.

This has been achieved by making two entirely separate, but compatible units, a Record Model R.1 and a Playback Model P.1.

The Record Model R.1 is battery operated. The Playback Model P.1 has its own mains operated power supply. These units will operate with most tape recorders, projectors and cameras.

You can film and record every shot with natural sound as it actually happens. Or, you can record at home using your projector with the Model R.1 to make precisely synchronised sound tracks.

The P.1 automatically generates a continuous tone when operating, and this tone is broken only when the camera or projector starts to operate. Editing, therefore, is extremely simple because if the tape recorder is allowed to run for a second or two before filming each shot, the sync. track can be subsequently monitored and the start and finish of the sound track to each shot located precisely.

Also, the camera produces its own synchronising track and therefore both spring-driven and electric cameras may be used at any normal film or tape speed. This is a truly versatile system requiring no special processing nor expensive special tape, but for those who prefer perforated tape, it may be used to form, in effect, a pre-recorded synchronising track.

Only a single modification is required to the camera and that is to provide a simple switch contact which will "make" once every frame to produce the necessary synchronising pulse. The total cost of Models R.1 and P.1 is only £19 16s. 3d.

# NEWS AND COMMENT...

## PUBLIC: FOR THE USE OF

Recently declassified by the USAF and US Navy is a RCA transistor which is said to provide an output of up to 800W at frequencies to 1Mc/s.

This device, which is still some way from being put on the market is reported to be based on new transistor technology and employs fused or laminated semiconductor materials. Ultrasonic cutting rather than photo-etching techniques are used and glass hermetic sealing is employed.

## SATELLITE POST

No, it's not beaming letters to a satellite and sending them round the world, Thailand have issued a postage stamp with a satellite pictured upon it. It is to mark the start of satellite communications in the country following the completion of an earth station by General Telephone & Electronics International. The stamp shows a yellow satellite against a sky of dark blue.

The ground station is also shown together with a section of S.E. Asia and along the top of the stamp, the words "satellite communications" are printed in English and Thai.

## CHANGES FOR AMATEUR U.H.F. BAND


The GPO have informed the RSGB that changes will be made to the British Amateur u.h.f. band which is at the moment 427 to 450Mc/s. The band will be split up into two segments—425 to 429Mc/s and 432 to 450Mc/s.

Under the 1959 Geneva Radio Regulations, this section of the frequency allocation is devoted on a primary basis to the radio-location service and on a secondary basis to the amateur service.

## 126 TRACK TAPE RECORDER GIVES 46 HOURS CONTINUOUS PLAYBACK

From Shield Laboratories Ltd., 44 Lullington Garth, Woodside Park, London, N.12, we have received details of a combined 4 waveband radio and 126 track tape recorder giving 46 hours of continuous unrepeated playback time, plus the facility of instantaneous track selection. This equipment incorporates a total of 27 transistors and 15 diodes. Covering V.H.F.—F.M./Long Wave/Medium Wave/Short Wave, with exclusive "Auton Control" to give precise station tuning. A 4 inch wide magnetic tape accommodates 126 separate tracks of 22 minutes each (length of time of a standard LP record). Each track is able to playback so that

## HOW ABANT THIS THEN?

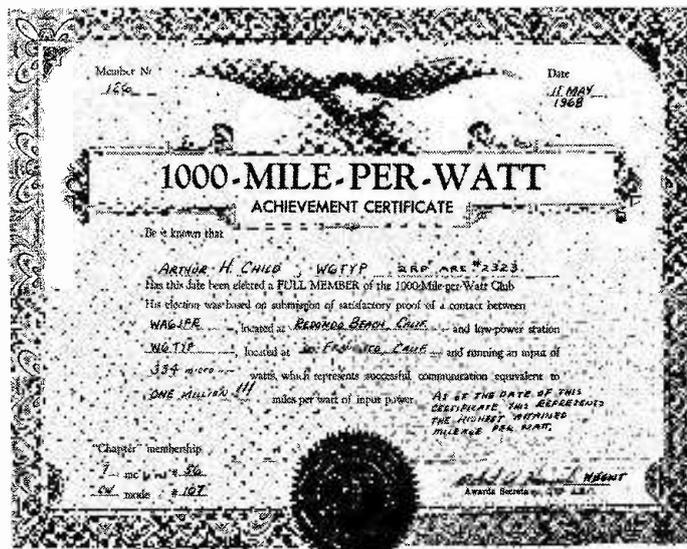

Partridge Electronics, makers of the "Joystick" aeriols, have forwarded a print of a certificate sent to them by Arthur Child, W6TYP of San Francisco. Using 354 microwatts, W6TYP established radio communication over 354 air miles, representing the distance of 1,000,000 miles per watt. He used a Joystick antenna to achieve this remarkable performance.

## SOLDERING TIPS FROM WELLER


With every Weller "Expert" soldering gun comes a useful booklet on soldering hints and tips. This booklet is fully illustrated. A comprehensive chart is included that shows the correct flux for various base metals, and this is followed up with the six golden rules of soldering.

you need not touch the machine for 46 hours. it automatically rewinds after each playback period. Tape speed 3 3/4 in./sec. frequency response 40-14 000c/s. Pause control. Automatic erase. Internal 10 inch wide range loudspeaker plus tweeter. Push-pull 10 watt r.m.s. audio output. External adapter (includes preamplifier) for microphone or record player and can be used as a radiogram or straight through amplifier. Cabinet size is 31 x 13 x 11 in. Further details from Shield Laboratories Ltd. 01-445-2825 (evening) or 01-445-0749 (day) 24 hour telephone answering service.

SCHAUB LORENZ


"MUSIC CENTRE"

MODEL 5001

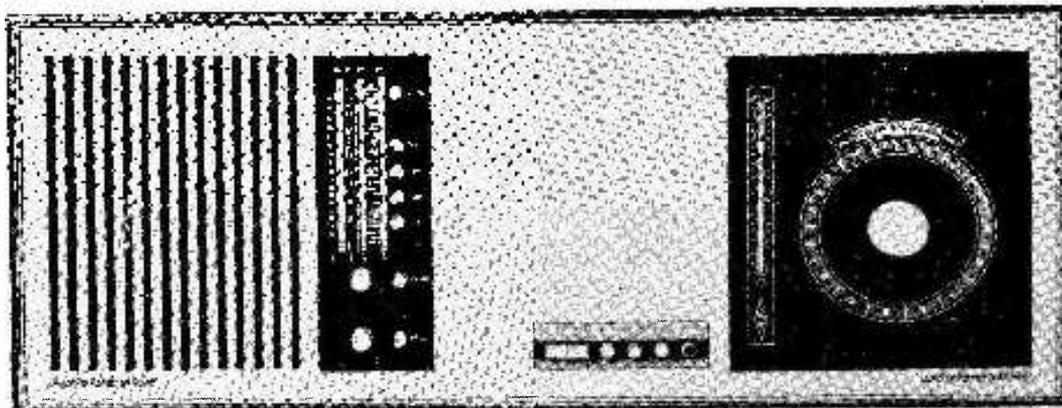

# THE MINI-3

R.F. GRAHAM

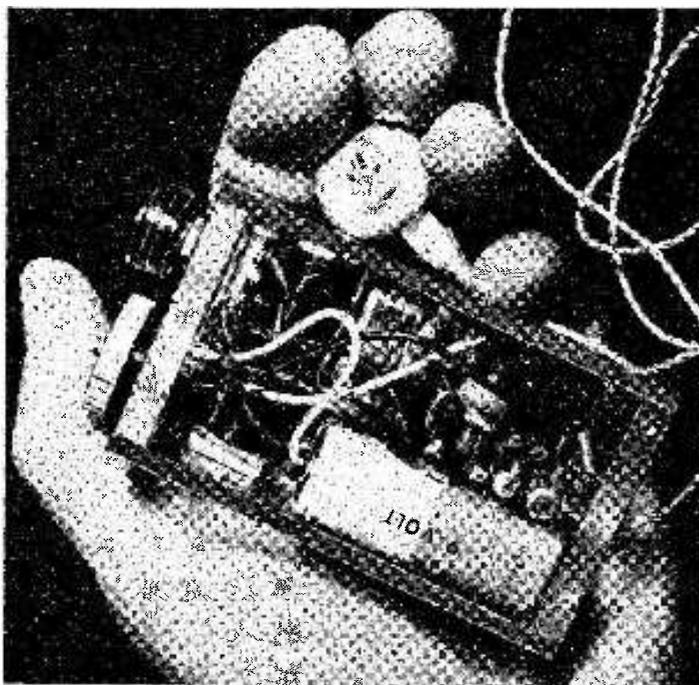

**T**HIS receiver uses a well tested circuit employing three transistors and two diodes in a five-stage reflexed circuit which gives very good headphone volume. The receiver, with a miniature 9V battery, occupies a case having internal dimensions of only  $1\frac{1}{2} \times 2\frac{1}{4} \times 1\frac{1}{4}$  in. External dimensions are of course a little greater depending on the thickness of material used. It could be accommodated in a box of different size and shape allowing something already to hand to be used: a metal box is unsuitable.

Figure 1 shows the circuit, with Tr1 acting as r.f. amplifier and also as audio amplifier after signal detection by D1 and D2. Tr2 and Tr3 are directly coupled audio stages, with Tr3 giving adequate output for all ordinary listening with a personal phone.

VR1 allows full control over regeneration which is very important for best sensitivity. The on/off switch is incorporated with VR1. VC1 is a compression type capacitor for small size. Its capacitance range is obtained over several turns of a small knob. A midget solid dielectric variable capacitor could be used instead.

Current drain is about 3mA from an ordinary miniature 9V battery, easily obtainable. The receiver also works satisfactorily with a 6V supply.

All the components except VC1, the aerial, L1, VR1 and C2 are assembled and wired on a small paxolin panel. When completed the panel is inserted in the case and connected with flying leads to VC1 and the other items just mentioned.

## Ferrite Aerial

The aerial input winding L1 is wound with 34 s.w.g. enamelled wire on a ferrite rod aerial  $1\frac{1}{8}$  in. long and  $\frac{3}{8}$  in. in diameter. A single layer of paper is first wound on the rod. The wire is secured near one end at point A, using adhesive. Fifty-four turns are wound side by side and a small loop is then twisted for the tapping. A further 12 turns are wound, continuing in the same direction, and the wire is fixed at B. The loop and coil ends are scraped and tinned.

If the case is not as shown (Fig. 4) and a longer rod can be accommodated this will increase signal pickup. Ferrite rod material cannot be sawn by ordinary means but is brittle and snaps easily: it can thus be gripped lightly in a vice with a little padding at the point where the break is wanted.

Ready-made windings (for superhet receivers) can generally be employed. The existing base coupling winding usually has very few turns and is removed or ignored. The main winding then furnishes the section from A to the tap and some thin insulated wire is used to add the turns required for the tap to B section. These turns may if necessary be on top of the existing coil, but must be in such a direction that A to B is effectively one continuous winding.

## Receiver Panel

The paxolin panel is only  $1\frac{1}{8} \times 1\frac{1}{8}$  in. so resistors etc. must be of the small size commonly used for small transistor receivers. The paxolin is  $\frac{1}{8}$  in. thick and the holes for leads were made with a  $\frac{1}{8}$  in. drill. The resistors, capacitors and diodes stand vertically. One lead passes down through a hole directly under the components, the other lead being covered with 1mm. sleeving and bent over to reach a second hole as shown in Fig. 2. D1, D2 and C4 are mounted with their positive ends on top so

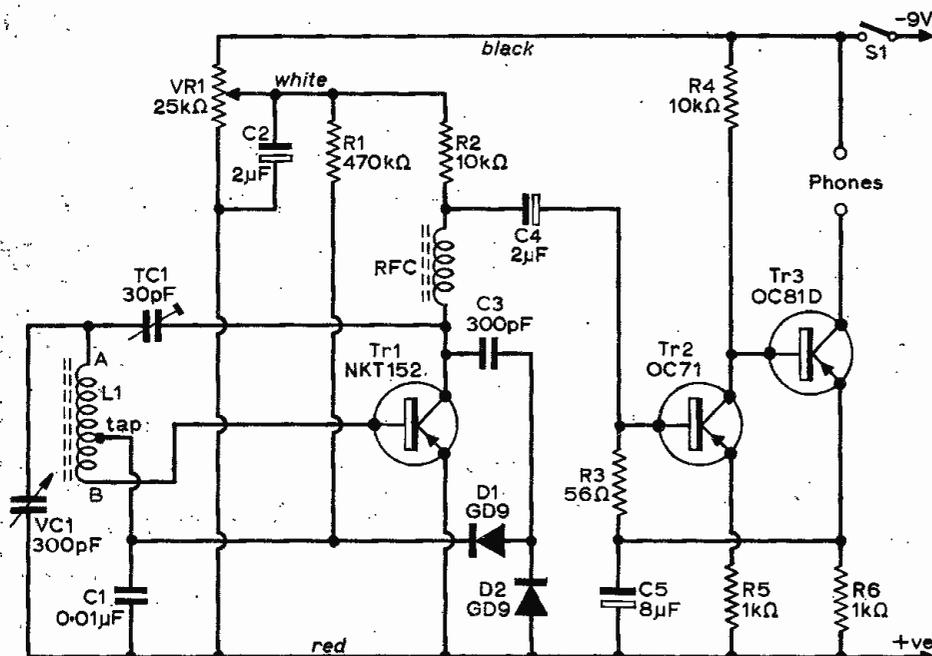


Fig. 1: Circuit diagram of the Mini-3. R3 is 56kΩ not 56Ω.

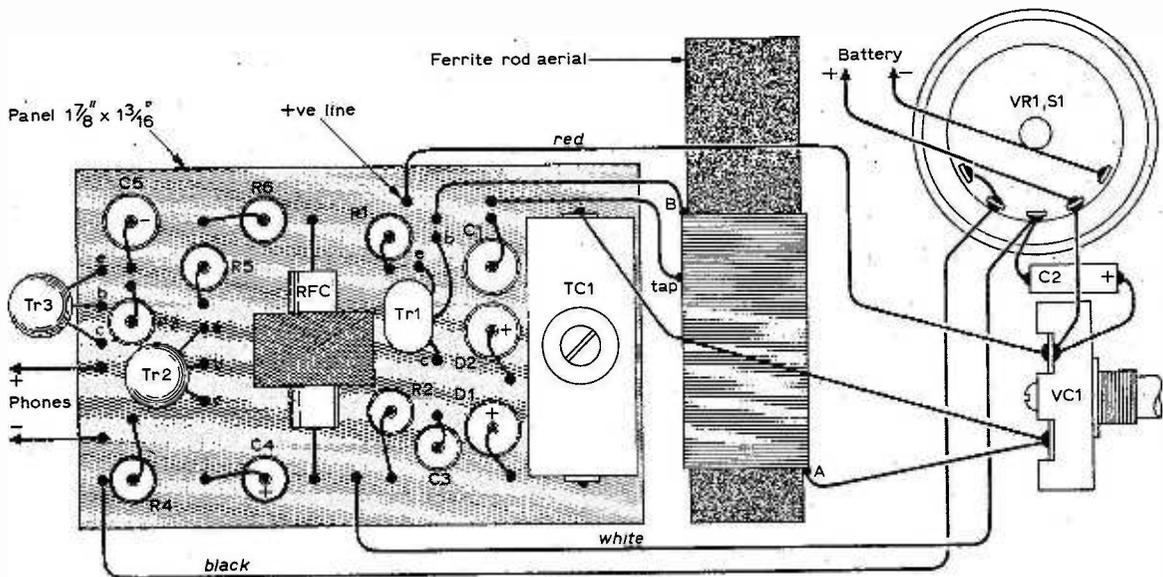


Fig. 2: Top view of paxolin board and connections to separately mounted components.

the negative ends emerge immediately under these components. C5 has its negative end uppermost.

Sleeving is also necessary on the transistor leads. The tops of the transistors are about  $\frac{1}{8}$  in. above the upper ends of the resistors etc. TC1 tags pass through slots made by drilling holes closely together, a central hole clearing the adjusting screw.

The panel is wired by turning it over and connecting as in Fig. 3. As there is little free space sleeving is used on nearly all wires. Transistor and diode connections must be soldered rapidly to avoid overheating. Unnecessary and lengthy heating of capacitors and resistors is also best avoided.

Pieces of thin insulated flex are soldered to the points indicated and will later be connected to VR1, VC1, and the aerial. If different colours are provided, as shown, this helps easy identification of the connections to be made later.

## Phones

Excellent results are obtained with a full-sized headset but a miniature personal phone is easily carried in the pocket with the receiver. Short wire ends were left projecting at the phones points as shown in Fig. 2. When the receiver is in its case, pass the phone leads through a small hole and solder them to these points, covering the joints with sleeving.

If the phones may be changed from time to time a miniature jacket socket can be fitted to the case. The circuit is suitable for medium or high impedance phones, but not for crystal earpieces.

## Other Components

VR1 is fixed to the outside of the box with an 8BA bolt, its five tags passing through holes. Should the material used for the box be too thick for the tags to pass right through, solder leads to the tags first, thread them through the holes, then fit VR1 in place.

VC2 is a compression type capacitor with fixing bush threaded for a 6BA bolt and is normally adjusted from the plates' side with a screwdriver. The bolt was removed and a longer one screwed in, the insulation and metal washers being kept as originally. A small disc or knob was then fixed on the free end of the bolt with lock nuts (a toothpaste tube cap can be used). Rotating the knob compresses or releases the plates of VC1 to alter its capacitance.

The ferrite rod was slightly shorter than the inside dimension of the box and was held with glue and a shaped slip of wood pushed between the box and one end of the rod.

The connections between the panel and other items in Fig. 2 can then be made. Figure 4 shows VC1 and VR1 in position; however, the various items could be rearranged to occupy different positions if this were more suitable for a box already available.

Leads were soldered directly to the battery. Alternatively the snap fasteners of an old battery

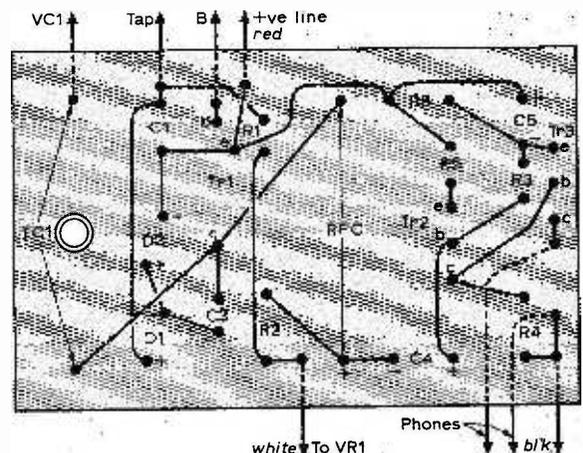


Fig. 3: Wiring on the underside of the panel.

could be used as connectors. If so remember to observe polarity as marked on the battery itself.

If a meter is placed in one battery lead the current drain should be zero with the receiver switched off and about 3mA when it is switched on, rising a little as VR1 is rotated. If a large current flows switch off at once and look for a wrong connection or short.

## Adjustments

Regeneration arises more easily towards the high frequency end of the waveband but should be possible over the whole band when TC1 is suitably adjusted. Unscrew TC1, set VR1 about one-third from zero (off) and screw down TC1 slightly until oscillation arises on tuning through a station near the h.f. end of the band (VC1 near minimum capacitance).

If TC1 is screwed down too far oscillation arises with only a small rotation of VR1 and best volume is not obtained. But if TC1 is not screwed down sufficiently no regeneration can be obtained at the l.f. end of the band (VC1 at full capacitance).

For normal use only rotate VR1 as far as proves necessary for the volume required. Turning VR1 too far (as if it were a volume control) will cause oscillation or loss of signals. VR1 should not be rotated more than about one-half to two-thirds of its movement from the off position. If VR1 is used for critical control of regeneration, in the usual way for a t.r.f. receiver with adjustable reaction or regeneration, the receiver will be very sensitive to weak signals.

An external aerial should not normally be needed. However a few feet of thin insulated wire as a throw-out aerial can be clipped to A.

## Case Construction

The box was made from clear Perspex, the ends being  $1\frac{3}{4} \times 1\frac{1}{4}$  in. and  $\frac{1}{4}$  in. thick. The sides were  $\frac{1}{8}$  in. material, each  $1\frac{1}{4} \times 3\frac{3}{8}$  in. Top and bottom were both  $3\frac{3}{8} \times 2$  in. This gives a case with internal dimensions of  $2\frac{7}{8} \times 1\frac{3}{4} \times 1\frac{1}{4}$  in. The top was held with four small screws passing through clearance holes into the ends.

## Tuning Range

With the ferrite-rod aerial described tuning covers the most important part of the medium wave band. Full coverage of this band is not achieved because the minimum capacitance of the 300pF compression

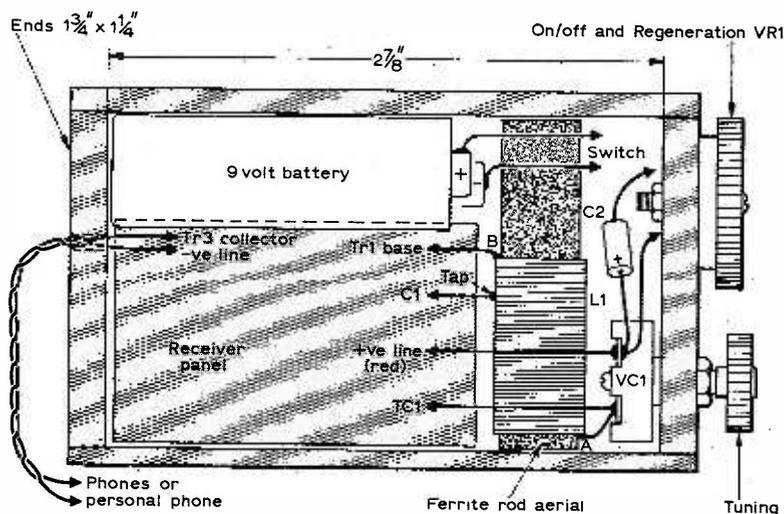


Fig. 4: Case dimensions and general assembly.

## ★ components list

### Resistors:

R1	470kΩ	R5	1kΩ
R2	10kΩ	R6	1kΩ
R3	56kΩ		All miniature 10%
R4	10kΩ	VR1	25kΩ with switch

### Capacitors:

C1	0.01μF miniature
C2	2μF 9V electrolytic
C3	300pF miniature
C4	2μF 6V electrolytic
C5	8μF 4V electrolytic
VC1	300pF compression capacitor
TC1	30pF trimmer

### Semiconductors:

Tr1	NKT152	D1	GD9
Tr2	OC71	D2	GD9
Tr3	OC81D		

### Miscellaneous:

R.F.C.	5mH or similar
L1	See text
	Paxolin board, wire, battery, etc.

capacitor is higher than the minimum capacitance of a conventional tuning capacitor.

In some parts of the country it may be felt desirable to tune to the low frequency end of the band. If so some turns should be added to the aerial winding. On the other hand should tuning to the high frequency end of the band be required a few turns can be removed from this winding.

**PRACTICAL TELEVISION**  
**IN THE DECEMBER ISSUE**  
**ON SALE NOVEMBER 22**

- ★ C.R.T. TESTER—Simple unit for *in situ* testing. Emission and leakage tests plus rejuvenation feature.
- ★ COLOUR SERVICING—Setting the grey-scale tracking and colour-drive controls. Also installation hints.
- ★ USING LENSES—A guide for the CCTV enthusiast.
- ★ TV RECEIVER TESTING—Tackling line output stage faults.

# P.W. GUIDE TO COMPONENTS

## PART 1

M. K. TITMAN, B.Sc. (Eng)

Component specifications are continuously changing as research leads to the introduction of new types. This series of articles will provide up-to-date information on the types of electronic component available for use in modern circuits. In each case the ideal performance of each type of circuit element will first be outlined and the various types available then compared to this. The information to be given on construction, tolerances, size and cost will guide the novice and expert alike in selecting the best component to use.

**R**ESISTORS are the most commonly used components in electronic circuits. They function as loads, potential droppers, current limiters, etc. Resistance is measured in ohms; kilohms and megohms being ohms multiplied by 1,000 and 1,000,000 respectively. Each resistor is marked by numerals or colour coded as shown in Fig. 1 and Table 1. A and B indicate the value, C is the multiplying factor in zeroes, and D the tolerance. In theory, a resistor should have a resistance exactly equal to the value printed or indicated on the body. In practice, however, they are selected or batch produced with various tolerances, e.g.  $\pm 10\%$  or  $\pm 1\%$ . In general the closer the tolerance the more expensive the component.

Ideally the resistance should not change with any external influence such as voltage, current, temperature, time, pressure, humidity, vibration, etc. In practice the resistance changes with all these parameters. The greatest resistance variation arises from temperature changes, and for this reason the maximum power dissipation of a resistor is limited. The reliability of a resistor increases enormously if the maximum power is limited to half the rated value.

### Tolerances and Standard Values

Tolerances and resistor standard values are also of paramount importance to the designer. Fixed resistors are only available in the standard values

TABLE 1: RESISTOR COLOUR CODING

Colour	Numeral	Colour	Numeral
Black	0	Green	5
Brown	1	Blue	6
Red	2	Violet	7
Orange	3	Grey	8
Yellow	4	White	9

shown in Table 2. The tolerance in the value sets the range of resistors available and the equipment designer must ensure that his design will operate using the standard values of resistor. In addition it must work over the full tolerance range for the resistors used. Thus a  $10k\Omega$  resistor with a  $\pm 10\%$  tolerance can have any value between  $9k\Omega$  and  $11k\Omega$ .

The various types of resistor available to the electronic designer are shown in Table 3. The table compares the various types for usage, value, power rating, tolerance, size and cost. Let us examine each type in turn, considering its advantages and disadvantages.

### Carbon Composition

Carbon composition resistors were one of the earliest forms of mass produced resistor and are formed as shown in Fig. 2. They are manufactured by compressing a granulated carbon composition into a cylindrical shape. The lead out wires are attached direct to the carbon and the whole resistor is then insulated by paint, granulated ceramic etc. These resistors are still the most commonly used general purpose resistor. They are cheap, reliable, small and have a low noise characteristic.

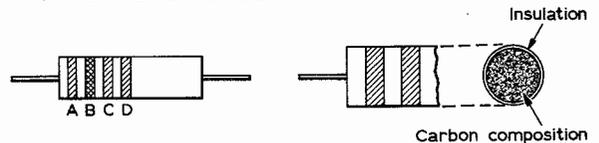


Fig. 1 (left): Colour coding. Fig. 2 (right): Carbon composition resistor.

The main disadvantage of carbon composition resistors is that the manufacturing process yields resistors with a large tolerance so that they are generally available with only 10% and 20% tolerances. Where they are available with closer

TABLE 2: STANDARD RESISTOR VALUES  
5% AND 10% RANGES

10%	5%	10%	5%	10%	5%
1.0	1.0	2.2	2.2	4.7	4.7
—	1.1	—	2.4	—	5.1
1.2	1.2	2.7	2.7	5.6	5.6
—	1.3	—	3.0	—	6.2
1.5	1.5	3.3	3.3	6.8	6.8
—	1.6	—	3.6	—	7.5
1.8	1.8	3.9	3.9	8.2	8.2
—	2.0	—	4.3	—	9.1

TABLE 3: COMPARISON OF TYPES OF RESISTOR AVAILABLE

Type	Usage	Range available	Power rating	Tolerance	Size	Cost each
Composition	General	4.7 Ω—22M Ω	1/10W—2W	10%, 20%	¼W 0.2in. diameter × 0.5in.	1d.—6d.
Carbon film	General Close Tolerance	4.7 Ω—22M Ω	1/10W—1W	1%—10%	¼W 0.2in. diameter × 0.5in.	5d.—9d.
Metal oxide	High stability	10 Ω—1M Ω	1/10W—1W	0.5%—5%	¼W 0.15in. diameter × 0.4in.	2s.—3/6d.
Metal film	High Stability and Semi Precision	1 Ω—2M Ω	1/10W—1W	0.05%—2%	¼W 0.15in. diameter × 0.4in.	2/6d.—5s.
Wire wound	General High Power	0.1 Ω upwards	1.5W upwards	5%—20%	3W 0.2in. diameter × 0.4in. 6W 0.5in. diameter × 1.125in.	2/6d. upwards
	Metering	All	—	0.001%—0.1%	¼in. diameter × 1in.	5s. upwards
Variable resistors	Carbon Linear or Log	100 Ω—2.2M Ω	¼W—5W	—	Printed circuit and panel mounting	5s. upwards
	Wire wound Linear, Log or Multi- turn	10 Ω—100k Ω	¼W—5W	—	Printed circuit and panel mounting	5s. upwards
	Rheostats	1 Ω—100k Ω	10W upwards	—	—	10s. upwards

tolerances these are selected from the 10% or 20% ranges. This has the effect of depleting the 10% or 20% ranges of values close to the marked value. Another disadvantage is that they tend to drift with time and temperature and therefore cannot be regarded as high stability resistors.

### Carbon Film Resistors

The carbon film resistor was developed as the need arose for resistors with greater stability and closer tolerance. They are more stable than composition resistors and are available in the tolerance ranges 1%, 2% and 5%. They are, therefore, more suitable for transistor circuits where closer tolerances are required, though a penalty is paid in increased cost.

They are manufactured by depositing a carbon film on to a cylindrical ceramic body as shown in Fig. 3. The ceramic body provides the rigidity and

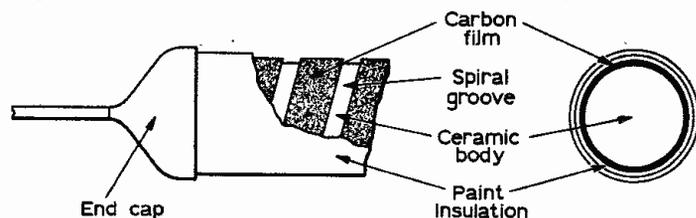


Fig. 3: Construction of the carbon film resistor.

has the same temperature coefficient as the carbon film. They are stable with time and temperature and withstand thermal shock. The exact resistance is formed by a spiral groove in the carbon film. This increases the length of track of the constant resistivity film, thus increasing its resistance. The wire connections are made to end caps fitted over the

ceramic body and the whole resistor is insulated by paint or lacquer.

The main disadvantage of the carbon film resistor is its decreased reliability compared with the composition resistor. The disconnection of the end caps in certain types has been a problem, although new types insulated with hard ceramic have solved this difficulty.

### Metal Oxide Resistors

Metal oxide resistors were developed to combine the high stability of carbon film resistors with the reliability of composition resistors. Thus metal oxide resistors form a semiprecision range of resistors with great stability, reliability and close tolerances. They also have lower noise levels than carbon resistors.

These advantages are outweighed in most commercial applications by their considerably increased cost, though for special circuits they are extremely useful.

They are formed by bonding metal oxide film on to a glass body and have a similar physical appearance to carbon film resistors. A spiral groove again sets the resistance value and the leads are connected by a band or cap. The whole body is insulated with a hard ceramic material.

### Metal Film Resistors

Metal film resistors are used where accuracy and stability are required, especially for low values. They are used as precision resistors for meter circuits and are available down to 1Ω with tolerances of 0.05%.

Construction is by vacuum deposition on a ceramic former resulting in a similar physical appearance to

Fig. 3. Connections are made to noble metal bands which give high stability and reliability. Insulation is by ceramic or epoxy material to give a strong resistant finish.

## Wire Wound Resistors

Wire wound resistors are utilised where the power dissipation is too great for normal resistors. They have wider tolerances and are dearer than carbon resistors but can dissipate more power. Usually the increased dissipation results in an increased surface temperature and care should be taken to ensure that surrounding circuit elements are not affected by this high surface temperature (which may be as high as 300°C).

Construction is shown in Fig. 4 and is by winding resistance wire on a heat resistant former. The resis-

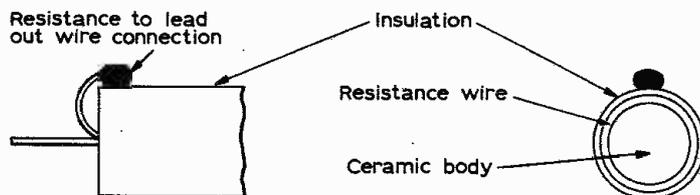


Fig. 4: Construction of a fixed wire wound resistor.

tance wire is welded or otherwise joined to the connecting wire to give a strong reliable connection. The body is then insulated by heat resistant ceramic material.

Precision wire wound resistors are used for meter shunts and standard resistances. These are wound and measured accurately and their power rating is derated to give great stability. In all cases wire having a low resistance-temperature coefficient is used.

Wire wound resistors are exclusively used below 1Ω and are readily obtained to 0.2Ω. They are reliable and are available up to 20W for printed circuit mounting. Size is determined mainly by power rating and maximum surface temperature. Reliability is increased if they are operated well below the rated power.

## Variable Resistors

Variable resistors or potentiometers are available in a wide variety of shapes, sizes and power ratings. Carbon or wire is again used as the basic resistance material, and in all cases a slider moves along a fixed resistance to give the variation in resistance.

Figure 5a shows a carbon printed circuit mounting potentiometer. A slider arm moves round a circular track of carbon when the spindle is rotated by the screwdriver slot. Figure 5b is a normal wire wound panel mounting potentiometer. Rotation of the spindle moves a slider across a coil of resistance wire. Similarly Fig. 5c is a printed circuit mounting multiturn wire wound potentiometer. As the adjusting screw is turned a slider moves along the screw thread and varies the resistance. Usually it is arranged to give 10 complete turns for the full range of resistance. Figure 5d is a precision helical potentiometer where 10 turns of the spindle give the complete range of resistance. This is used for precision resistance adjustments in equipment.

Both wire and carbon types are available in a logarithmic form in which the resistance varies logarithmically with rotation of the control spindle. This type is generally used for volume controls.

Carbon potentiometers give a smooth, infinitely

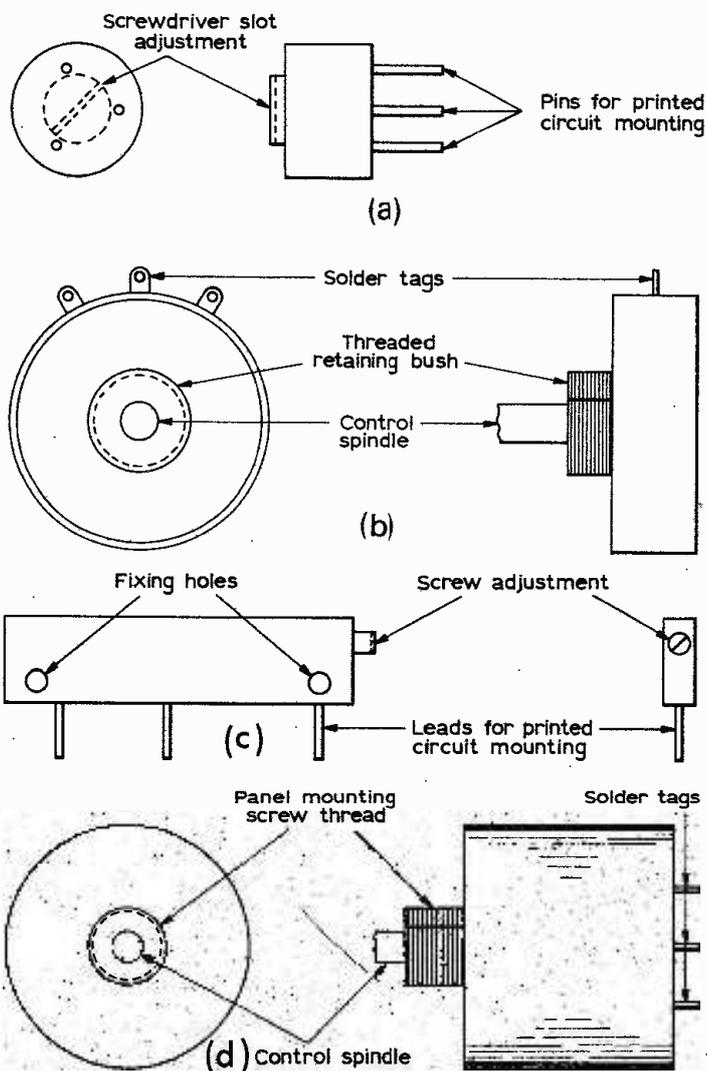


Fig. 5: (a) Printed circuit mounting potentiometer, (b) panel mounting potentiometer, (c) flat printed circuit multiturn potentiometer, (d) precision helical multiturn potentiometer.

variable variation of resistance, whilst wire wound potentiometers have step changes and are coarser. Carbon types tend to go noisy with usage whilst wire wound ones are more reliable. Failure in wire wound potentiometers is often due to breaks in contact between the slider and wire which gives an open circuit to the slider. In general, wire wound types are better where continual adjustments are made, whilst carbon types are preferable for smooth action or pre-set conditions.

## Future Trends

Trends will always be towards the ideal resistor. Further miniaturisation will occur and already 1/20W resistors smaller than match heads are available. Miniaturisation is in line with the trend for integrated circuits. For this purpose multiresistor thin film circuits have been developed. These will be useful mainly for the digital designer. Lower power dissipation in integrated circuit systems will lead to a further advance in the miniaturisation of resistors.

In the short term, however, carbon film resistors are unlikely to be ousted from their present position as the standard general purpose resistor for transistor circuits. Metal oxide and film resistors will be used for reliability and stability, and wire wound resistors will be further miniaturised for circuits where power dissipation is likely.

TO BE CONTINUED

# Absorption Wavemeter Radiation Meter and Phone Monitor

—FOR THE H.F. BANDS

by A. D. TAYLOR, GW8PG

**A**N absorption wavemeter is an essential instrument in any amateur station. It is the only type of wavemeter which does not itself generate harmonics, and as everyone who has studied for the R.A.E., will know it is always used during the first tests on a new transmitter to ensure that the output of the harmonic generator stages and the p.a. are at the correct frequencies. The instrument can also be used for the rough checking of receiver calibration.

Besides its use as a wavemeter, the instrument to be described can also be employed as a radiation meter when tuning the transmitter output circuit, and as an a.m. phone monitor. The design is so arranged that those readers who have to save up to buy the components can build the simple wavemeter circuit first and then add the other refinements later. The simple circuit alone will satisfy the GPO requirement that the station be equipped with an absorption wavemeter.

## THE CIRCUIT

Figure 1 shows the circuit of the instrument. Assume firstly that only the components to the left of the points marked X on the diagram have been wired.

If L1 is coupled to the p.a. tank coil of a transmitter and C1 is adjusted until the circuit resonates at the transmitter output frequency, power will be absorbed by the wavemeter tuned circuit. This will cause an r.f. current to flow in the circuit and lamp LP1 will glow, the maximum glow being obtained when the wavemeter is tuned to the same frequency as the transmitter. This system is quite adequate for checking the output frequency of the p.a. and the higher power stages in the exciter, but the energy

absorbed from low power stages may be insufficient to make the lamp glow. The sensitivity can be greatly increased by adding the components shown on the right of the points marked X on the diagram. When these components are added, if switch S1 is opened, thus removing the damping effect of the lamp from the circuit, the instrument becomes a sensitive diode demodulator, the output of which is applied to jack J1. If a 0-1mA or 0-500 $\mu$ A meter is plugged into J1 it will act as a sensitive indicator which will allow comparative readings to be taken. If a pair of headphones are jacked into J1 the quality of an a.m. phone transmission can be monitored.

## CONSTRUCTION

The coil L1 is wound on a 2½ in. length of 1 in. diameter paxolin tubing, though a stout cardboard tube of the same dimensions will be equally suitable. The wire used is 30 s.w.g. enamelled and the coil is secured to the chassis or box by means of two small "L" brackets fabricated from strips of brass or aluminium. It is important that the coil be mounted with the smallest winding (represented by the 6 turn tap) furthest from the chassis or box. The simplest and most inexpensive form of construction is the "L" shaped chassis made from a 4 × 6 in. sheet of aluminium as illustrated in Fig. 2(a). The chassis is provided with a wooden handle for convenience in use, a simple source of this item being a handle cut from a worn-out paint brush. A second but more expensive form of construction is to use a 4¼ × 3½ in. diecast box as shown in Fig. 2(b), and to provide it with a commercially made metal handle. Whichever method is adopted, the layout is in no way

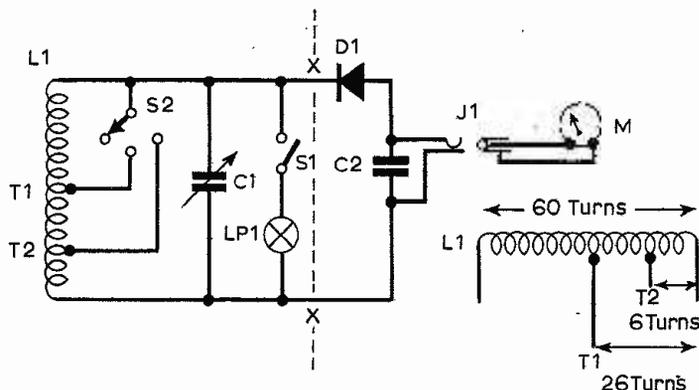


Fig. 1: Circuit diagram and coil winding details. L1 is wound on a 1 in. diameter former.

## ★ components list

C1	150pF variable (air spaced)
C2	2200pF 350V S.M.
D1	OA81 (Mullard)
S1	SPST switch
S2	1 pole 3 way switch
Meter	0-1mA milliammeter

Miniature jack socket and plug. Diecast box 4 x 3½ x 2⅝ in. (Electroniques). LP1 3.5V 0.1A bulb and holder. Small quantity of 30 s.w.g. enamelled wire.

critical and the wiring is very simple. When the wiring has been completed a scale should be cut from stiff card and three arcs should be drawn on it with a pair of compasses, one for each position of S2. The scale is then cemented on to the chassis above the spindle of C1 (Bostik is a suitable adhesive) and C1 is provided with a pointer type control knob. If the diecast box is used and a spare micro-ammeter is available this could be mounted permanently in the box, but the advantage of the jack-in meter is that it can be common to other instruments in the station such as a multi-range test meter.

## CALIBRATION

If a transmitter which has already been calibrated is available the wavemeter can be calibrated for the various amateur bands by tuning the transmitter to each band in turn, setting S1 so that the lamp is in circuit, setting S2 to the correct range, then adjusting C1 until LP1 glows at maximum brilliance. The setting then marked on the appropriate arc on the cardboard scale. Either pencil or a black ballpoint pen can be used. The method is illustrated in Figs. 3(a) and 3(b). If no transmitter is available two alternative methods can be used. A calibrated t.r.f. receiver can be tuned to the desired frequency

heterodyne receiver provided it is possible to loosely couple L1 to the local oscillator tuning coil and that the intermediate frequency of the receiver is known. The local oscillator normally operates on the h.f. side of the signal frequency, being separated from the signal frequency by an amount equal to the intermediate frequency. If, therefore, the receiver is tuned to a signal on 6,550kc/s the local oscillator will be tuned to a frequency equal to 6,550kc/s plus the intermediate frequency. If the i.f. is 456kc/s this will give 6,550 + 465 or 7,015kc/s. If under these conditions, L1 on the wavemeter is loosely coupled to the local oscillator coil on the receiver when the wavemeter is tuned near 7Mc/s violent "pulling" of the local oscillator will take place, this being indicated by movement of the received signal. It is thus possible to use this method for calibrating the wavemeter.

## USE

Once the wavemeter is calibrated it can be used to check the output frequency of any stage in a transmitter by means of the methods described in the previous paragraph, and these methods can also be used to provide rough calibration of a receiver.

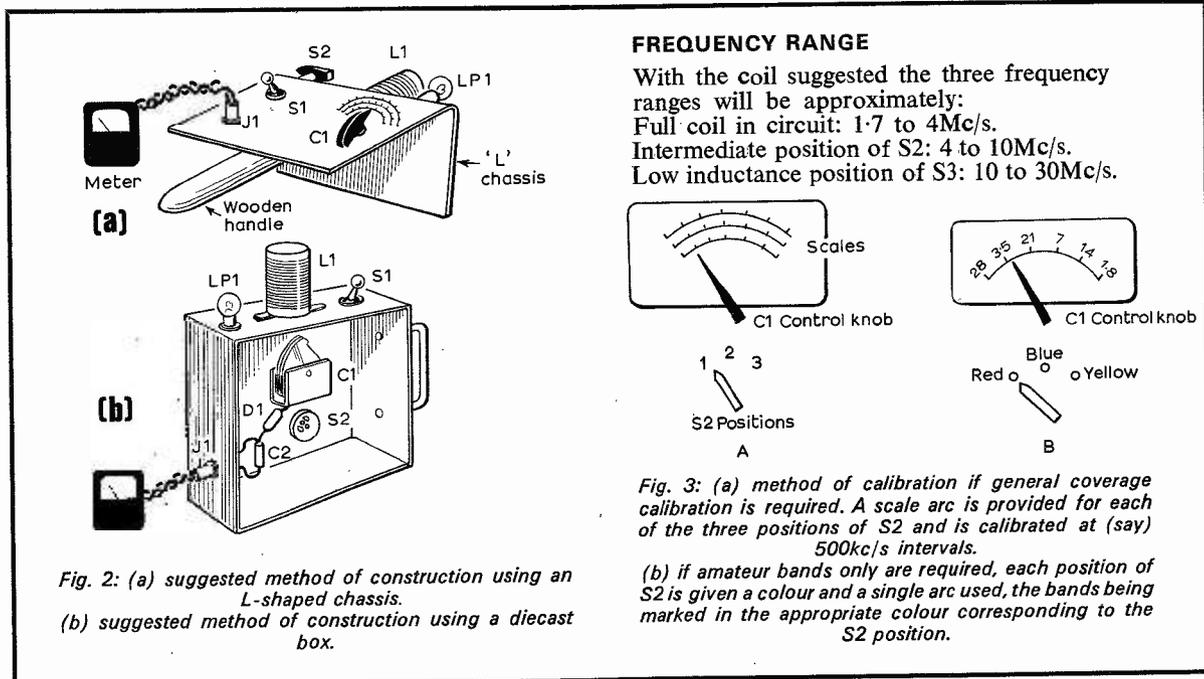


Fig. 2: (a) suggested method of construction using an L-shaped chassis.  
 (b) suggested method of construction using a diecast box.

Fig. 3: (a) method of calibration if general coverage calibration is required. A scale arc is provided for each of the three positions of S2 and is calibrated at (say) 500kc/s intervals.  
 (b) if amateur bands only are required, each position of S2 is given a colour and a single arc used, the bands being marked in the appropriate colour corresponding to the S2 position.

and the reaction control can be advanced until the detector begins to oscillate.


If L1 on the wavemeter is then loosely coupled to the detector grid coil by holding it two or three inches away, as the wavemeter is tuned close to resonance the detector will stop oscillating, re-starting again as the wavemeter is tuned away from resonance.

## ALTERNATIVE METHOD

A similar method can be used with a super-

For use as a radiation meter, a micro-ammeter is plugged into J1, LP1 is switched out of circuit and the instrument is tuned to the desired frequency and placed a few inches away from the aerial. It is then possible to tune the transmitter up by using the reading on the micro-ammeter, maximum reading corresponding to maximum r.f. output. With the wavemeter set up in this way the quality of an a.m. phone transmitter can be checked by unplugging the micro-ammeter and plugging a pair of headphones into J1. For best output these should be of the high impedance type.

# PRACTICAL GUIDE

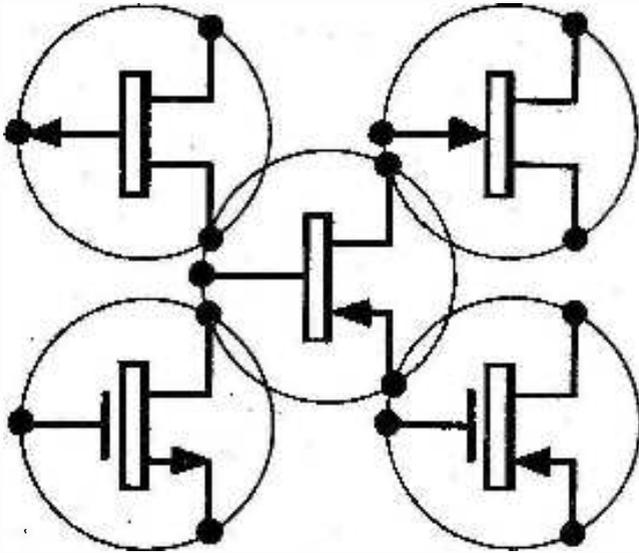

## TO F.E.T. S by K.ROYAL

THE field effect transistor (f.e.t. for short) differs in several ways from the more commonly used transistor that we have come to understand during the last decade. We know that the usual type of transistor possesses two "diode" p-n junctions—the emitter junction and the collector junction—and that two kinds of current carriers are involved in the working of the device. There is the *negative* carrier which is the electron and the *positive* carrier which is the hole. These are usually referred to as *n* and *p* carriers respectively, after their polarities. Depending on which way round the two junctions are arranged, we get either the p-n-p transistor or the n-p-n transistor. And since *two* kinds of current carriers are involved the usual type of transistor is known as a *bipolar* transistor.

The f.e.t. differs fundamentally from the bipolar transistor in that only *one* current carrier—either *n* or *p*—is involved in its working (that is one in type, not in quantity!), and for this reason the f.e.t. is often called a *unipolar* transistor. When a f.e.t. works with electrons it is called a *n-channel* type, and when holes are used it is called a *p-channel* type.

It will be recalled that a bipolar transistor has to be biased at its emitter/base junction for forward current conduction to secure collector current. This forward biasing means, of course, that the input impedance is intrinsically low, and a signal applied at the base may look into an impedance from about 500 to 50,000Ω, depending on the exact nature of the circuit. In other words, the bipolar transistor is current operated; that is, it needs signal current into its emitter/base junction to reflect a similar, but amplified, current into the collector circuit. There are schemes whereby the input impedance of a bipolar device can be raised—by feedback and by bootstrapping for example, but these are simply artifices that fool the input signal into thinking that it is looking into a high impedance circuit, where in actual fact the transistor remains a current operated device.

The opposite to current operation is voltage

operation. This means that the input impedance is truly very high and therefore passes virtually no current at all. A thermionic valve works like this when the input signal is applied between the control grid and cathode. The control grid functions on the electrostatic principle. It consists of a wire mesh across the path taken by the electrons flowing from the cathode to the anode. As its negative potential is increased (relative to the cathode) so some of the electrons arriving from the cathode are deflected back again (on the basis that like charges repel) and the number reaching the anode is reduced. The grid thus acts as an "electron tap", increasing or reducing the flow of electrons to the anode in accordance with its negative value. When it is very negative all the electrons are blocked and none pass to the anode. The valve is then biased to anode current cut-off. The control grid in effect performs its duty by "charging" to a certain potential, so the control action is almost completely divorced from current as such.

### Mode of Operation

While the input circuit of a bipolar transistor is essentially a semiconductor diode in forward conduction, the input of a f.e.t. appears to a signal either like a semiconductor diode in *reverse* conduction or like the control grid of a thermionic valve, depending on its exact nature. This brings us to the next important feature of the f.e.t., which is that it, too (like the thermionic valve) is voltage operated—the opposite to the bipolar transistor.

Let us consider the thermionic valve again for a minute. We know that if this is operated without grid bias the anode current will be abnormally high. We thus establish a valve circuit so that the control grid is biased negatively to yield the correct anode current for the application in hand. There is one type of f.e.t. that works in a similar manner; that is, the output current is high when the input is devoid of bias. The input, therefore, has to be biased in the same way as a thermionic valve to secure the required output current. This is known as a *depletion-type f.e.t.*

There is another kind—called an *enhancement-type f.e.t.*—that has biasing characteristics similar to those of a bipolar transistor. With this type there is no output current when the input electrode is without bias.

### F.e.t. Symbols

We must now have a look at the basic f.e.t. symbols and investigate the device electrodes. In a bipolar transistor, of course, we have emitter, base and collector electrodes; but in a f.e.t. the electrodes are correspondingly named *source*, *gate* and *drain*.

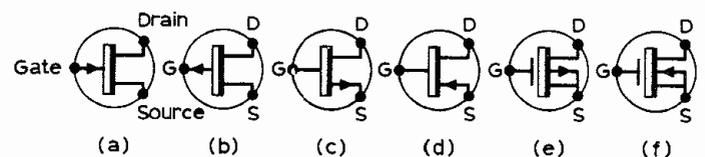



Fig. 1: F.e.t. symbols. (a) JGFET, n-channel depletion-type; (b) JGFET, p-channel depletion type; (c) JGFET, n-channel enhancement-type; (d) JGFET, p-channel enhancement-type; (e) IGFET, n-channel; (f) IGFET p-channel. It should be noted that in some literature slightly different symbols might be used, and in some IGFET symbols an arrowhead may not be included, in which case the device is generally assumed to be n-channel with the drain connected to a positive potential.

# LOOK!

**PRACTICAL!**

**VISUAL!**

**EXCITING!**

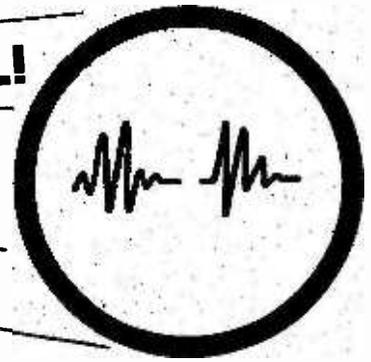

*a new 4-way method of mastering*

# ELECTRONICS

*by doing — and — seeing . . .*

**1** ▶ **OWN and HANDLE** a complete range of present-day **ELECTRONIC PARTS and COMPONENTS**

**2** ▶ **BUILD and USE** a modern and professional **CATHODE RAY OSCILLOSCOPE**

**3** ▶ **READ and DRAW and UNDERSTAND** **CIRCUIT DIAGRAMS**

**4** ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW for **BROCHURE**  
or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME..... BLOCK CAPS

ADDRESS..... PLEASE PW12

## TRANSISTORS

AC107	3/-	OC35	7/6
AC126	2/-	OC44	1/11
AC165	3/-	OC45	1/11
AC167	4/-	OC70	2/3
ACY19	3/9	OC71	1/11
ACY21	3/9	OC72	2/-
AF115	3/-	OC73	2/3
AF116	3/-	OC75	2/-
AF117	2/9	OC81	2/-
BFY18	4/6	OC82D	2/3
BFY51	4/-	OC140	5/-
BSY26	3/-	OC169	3/6
BSY28	3/9	OC170	2/2
BSY65	3/-	OC171	2/2
BSY95A	3/-	OC200	4/6
GET113	2/6	OC202	4/6
OA5	1/6	OC203	4/6
OA9	1/8	OC204	4/6
OA91	1/9	OC204	5/6
OC23	6/6	TK22C	1/6
OC25	5/-	2N706A	3/-
OC26	5/-	2N743	4/6
OC28	6/6	2N758	2/9

Crystal Diodes—6 for 2/6. (7d.).

## SILICON DIODE RECTIFIERS

750mA Series	
BY100 800 pV	2/6
400 pV	1/9
200 pV	1/4
Six Amp Series	
BYZ13 300 pV	3/6
BYZ12 600 pV	4/6
BYZ11 900 pV	5/-
BYZ10 1200 pV	5/6
Mullard Stack FW Bridge	
12A100 pV	39/6
THYRISTORS	
5 amp series	
100 pV	7/6
200 pV	9/-
300 pV	10/6
400 pV	12/-
10 amp series	
50 pV	10/-
100 pV	12/-
200 pV	16/-
100 amp series prices available on request.	

## Midget Electrolytic Conds. Wire Ends

At 6d. each	
0-8µF	25 volt
1µF	275 volt
2µF	150 volt
4µF	150 volt
640µF	2-5 volt
At 9d. each	
2µF	300 volt
4µF	12 volt
8µF	12 volt
10µF	25 volt
16µF	16 volt
30µF	10 volt
45µF	10 volt
80µF	6-4 volt
100µF	6 volt
125µF	4 volt
At 1/- each	
16µF	250 volt
50µF	10 volt
64µF	25 volt
100µF	12 volt
200µF	16 volt
320µF	10 volt

Also 8µF 350V 1/2, 25µF 25V 1/3 and 50µF 50V 1/9. Other electrolytics in current list. Postage, Packing and Insurance all above 7d. up to 3; 1/- from 4-11; 12 and over paid.

**2 GANG VAR. CONDENSER:** Mod., small, air-spaced, .0005 ea. sec. 4/6 (1/-).

**TRANSFORMERS:** Sub-min Output (3Ω for OC72 etc.) and Driver 2/6 each (6d.). Output 3Ω 5W 7000Ω for 6V6 (ex-equip. but perfect) 2/6 (1/9).

**PRINTED CIRCUIT PANELS:** Eight boards with minimum 30 Transistors, also Diodes, Capacitors, Resistors 8/- (2/-).

**TEST EQUIPMENT MULTITESTER:** 20,000Ω P. Volt D.C. 4½ x 3½ x 1½ in. D.C. volts 5, 25, 50, 250, 500 and 2.5k. A.C. volts 10, 50, 100, 500, 1000 at 10,000 p volt. D.C. current 0-50mA, 0-2.5 mA, 0-250mA. Res. 0-60kΩ, 0-6MΩ, 300Ω 30kΩ at centre scale. Cap. 100µµF to 0-01µF, 0-01µF to 0-1µF. —20 to +22dB. 67/6 (3/6), with prods. battery and instructions. Diode over-load protected.

**PANEL METERS:** 0-1mA, D.C. m/c 2in. sq. clear plastic 23/-; similar but 1-65 sq. in. fronts in 10, 50, 100, 150, 200, 300, 500mA, 1, 5 and 15 amp 24/-; "S" Meter 25/6; 500 microamps 25/6 (1/- each all types).

**DIAMOND STYLII:** Replacements for TC8LP, TC8/Stereo, TC8LP/Stereo, Studio 'O', BF40LP Ronette, GC2, GC8, GP65/7, all at 6/11 each. Also GP91-LP/8 at 12/6. **SAPPHIRE STYLII.** All these types at 2/11 GP91 at 6/- (6d. each all types). No 78 r.p.m. available in diamond or sapphire.

**PICK-UP CARTRIDGES** all with styli and standard replacement fittings Mono GP67/2 12/6. Newest Stereo GP93 22/-, Mono de Luxe GP91 16/-. Stereo Compatible (both mono and stereo) GP/91 SC 18/6. Ceramic Stereo Compatible, top quality for expensive outfits GP94 38/6 (all 1/-).

**FP3 ELIMINATOR (A.C.)** 17/6 (1/6); 2 stn. **INTERCOM**, comp. 52/6 (3/-).

**FOUR TRANSISTOR 3 WATT AMPLIFIER** 2½ x 2½ x 1½: 9v: 8Ω & 16Ω, excellent on 3Ω speakers; 45/6 (1/6). **Transr. TELEPHONE AMPLIFIER** 52/6 (1/6).

Extra High Torque **MINI-MOTOR**, 4½ to 12v, 1½ x ¾ in., 5/- (9d.).

Mech. **REV. COUNTER** to 999, long spindle, reset wheel, for T/recorders &c. 4/6 (1/-).

**BATTERY CHARGERS:** Small, sturdy, neat; 2 amp. 12v 35/-; 6v/12v 39/- (either 4/6) absolutely complete.

**RECORDING TAPE:** Finest quality British Mylar. **STANDARD:** 5in. 600ft 7/3, 5½in 850ft 8/3, 7in. 1200ft. **1 1/3. LONG PLAY** 5in. 900ft 10/-, 5½in 1200ft 11/3, 7in. 1800ft 18/- (1/3 reel). **MESSAGE TAPE**, 25ft LP Mylar 3/6 (9d.).

**MICROPHONES: CRYSTAL:** MIC40, Desk, 15/6; MIC45, curved hand grip 17/3; Stick "60" 20/3; Stick "39" 26/6 (1/6 each type). Cream plastic hand type 7/6, or with struct stand, switch and 2 leads with 2-5 & 3-5 plugs 11/-, or with single lead, no plugs, 8/9 (1/3 each type). Lapel (or hand) with clip 6/6 (1/-). Machined metal tapered stick type with neck cord & adaptor to fit standard floor stands, 25/- (1/6). **DYNAMIC:** Cream hand/table 14/- (1/-). **MS10** 50KΩ, 3½ x ¾ in. with Base, Adaptor and Neck Cord 27/6 (2/6). **MS11**, similar, but fixed on flexible Swan neck to switch-fitted base 42/6 (2/6). **PIEZO** 50KΩ black/chrome 2in. dia. x 1½ for stand use only. Standard inside thread 33/6 (1/6). All mikes supplied with leads.

**SPEAKERS:** 12in. round, fitted Tweeter, 6W, 3 or 15Ω (state which), 33/6 (4/6); 2½in. 3Ω 6/6 (1/-); 6 x 4 heavy duty 3Ω 13/6 (2/6) or for Stereo 30/- pair, post etc. paid; 8 x 3, 15Ω 13/6 (1/6); **HEADPHONES** High Res. 2000Ω ea. Earpiece 13/6 (1/6); Stereo Dyn 8-16Ω 63/- (3/-); **EARPIECES**, with lead etc., Min. Plug, Magnetic 1/6; Crystal 2/9 (either 6d.).

**AERIALS**—Car, telescopic, vandal proof; locks retracted, 2 keys and all fittings, 22/6 (2/6) For F.M. and all sets, telescopic 6 extn. 5½in.—22in. with swivel, 5/- (1/-). 7 extn. 5½in. to 32in. no swivel, screw hole in base, 6/6 (1/-).

**SWITCHES:** Standard toggle, metal, 250v 2A. One hole fixing: SPST 2/3. SPDT 2/9. DPST 3/-. DPDT 3/3. Slide types. Sub-min. DPDT 1/6 each. Small DPDT, 3 way, centre "off" 1/9. Reed magnetic on/off 1/9 (7d. each, all types).

**VIBRATORS:** 12V 4 pin, non-synch., 2/6; 6V, 6 or 7 pin, Synchronous, 10/- (1/- all types). **EDGE VOL. CONTROL:** 50K 1/- (6d.).

**MAINS NEON TESTER:** Fly leads 2/- (7d.). **PLUGS:** Std. Jack, plastic body 2/-, Screened 2/9, Sockets 1/6 (All 7d.). **VALVE HOLDERS:** B7G or B9A, Moulded 6d. (7d. up to 4, 1/- over 4). **CONNECTING WIRE:** 5 coils asstd. coils. each 5 yds. Solid Core 2/3. Flexible Core 2/6 (either 6d.). **PICK-UP WIRE:** Twin Super-thin Flex, Screened, Sheathed 1/9 yd. (6d.).

**CURRENT LIST** sent with all orders or free for S. A. Envelope—details of cable, wire, condensers, test equipment, tape recorder, sets, plugs, sockets, adaptors, tools and misc. items.

# FELSTEAD ELECTRONICS

(PW13)

LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Charges, which apply to G.B. and Eire only, are paid by us on orders value £5 and over. Overseas air or surface mail extra at cost.

**ERSIN**



**5 CORE SOLDER**

for quick,  
easy, reliable  
soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy also reduces wear of copper soldering iron bits.



**SIZE 5  
HANDY SOLDER  
DISPENSER**

Contains 10 ft. coil of 18 s.w.g. Ersin Multicore Savbit Alloy. 2/6 each.



**SIZE 15  
SOLDER  
DISPENSER**

Contains 21 ft. coil of 60/40 Alloy, 22 s.w.g. Ideal for small components, transistors, diodes, etc. 3/- each.



**SIZE 12**

Ideal for home constructors. Contains 90 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each.



**BIB MODEL 8  
WIRE STRIPPER  
AND CUTTER**

Strips insulation cleanly and quickly, fitted with unique 8 gauge wire selector. Plastic handles. 9/6 each.

From Electrical and Hardware shops. If unavailable, write to:  
**Multicore Solders Ltd., Hemel Hempstead, Herts.**



## RADIO TECHNICIAN TRAINING

IN THE

# RAAF

Vacancies exist in the Royal Australian Air Force for men who are interested in being trained in the Technical Radio fields. Applicants should be United Kingdom citizens resident in the U.K. aged between 18 and 33 years. Qualified personnel up to the age of 43 years are also invited to apply.

*Free passage to Australia is provided for families and pay commences from date of enlistment in London.*

Further information can be provided by writing or phoning:—

**RAAF CAREERS OFFICER (Dept. PW ) AUSTRALIA HOUSE  
STRAND, LONDON W.C.2 Telephone No: 01-836 2435**

as shown in Fig. 1. Here at (a) is given the symbol for a n-channel device and at (b) that for a p-channel device. It is noteworthy that in some literature the symbols differ slightly and the arrow-head may be found on the source electrode instead of on the gate electrode, as shown at (c) and (d), which are n-channel and p-channel symbols respectively. However, when the arrow-head is on the gate electrode, as in (a) and (b), the device is usually of the depletion-type, while when it is on the source electrode, as in (c) and (d), an enhancement-type is usually signified.

The high input impedance of a f.e.t. is a result either of the gate being isolated from the rest of the device by the reverse-biased diode effect or by a layer of insulation within the f.e.t. between the gate electrode and the channel. A device based on the reverse-biased diode effect is called a *junction-gate f.e.t.* (JGFET for short), while that embodying insulation in the gate electrode is called, as might well be expected, an *insulated-gate f.e.t.* (IGFET for short). All the symbols shown at (a), (b), (c) and (d) in Fig. 1 signify that the devices are of the junction-gate variety. Symbols for insulated-gate devices are given at (e) and (f) in Fig. 1, corresponding to n-channel and p-channel respectively. An alternative widely used name for the IGFET is the MOST or MOSTFET, which is derived from its layer construction with a metal gate, oxide insulating layer and semiconductor body—*t* for transistor of course!

Attention must now be drawn to the actual significance of the direction in which the arrow head on the symbol points. On each of the symbols on the left of the pairs in Fig. 1 the arrow points to the right. This is, in fact, the same direction in which the arrow on the emitter electrode of a n-p-n bipolar transistor points. Hence this signifies that the f.e.t. is a n-channel type (arrow pointing to the right, remember). Conversely on each of the symbols on the right of the pairs in Fig. 1 the arrow points to the left, which corresponds to the direction in which the arrow on the emitter electrode of a p-n-p bipolar transistor points, thus signifying that the f.e.t. is a p-channel type (arrow pointing to the left). As long as we remember the n-p-n and p-n-p arrow relationships on bipolar transistors, therefore, we can easily work out whether a f.e.t. is n-channel or p-channel from the symbol.

It is very important to know this because like the bipolar transistor the nature of the device determines the polarity that has to be applied to its electrodes. A p-n-p transistor requires a *negative* collector potential and similarly a *negative* potential is required by the drain of a p-channel f.e.t. Conversely, a n-p-n transistor requires a *positive* collector potential, as does the drain of a n-channel f.e.t.

### Summary of Principles

Before continuing let us summarise the foregoing aspects of the f.e.t. to clear the air a bit!

(1) A f.e.t. has a high or very high input impe-

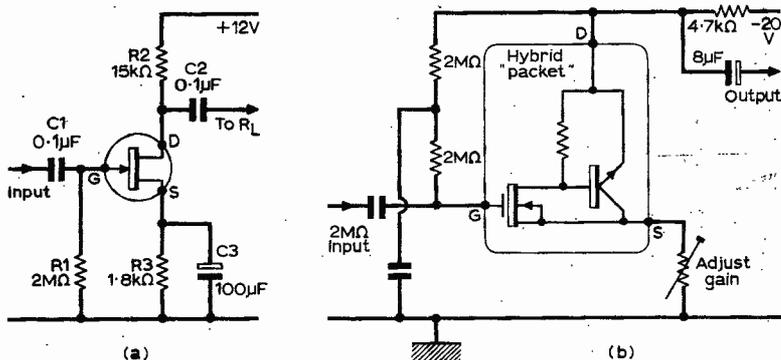


Fig. 2: (a) Simple a.f. amplifier using a JGFET of the depletion type; (b) hybrid "packet" in which a p-channel IGFET is integrated with a n-p-n bipolar transistor, giving a 2MΩ input impedance and medium output impedance with very high signal gain.

dance compared with the bipolar transistor, and in this respect is like a thermionic valve.

(2) It depends for its action on one kind of current carrier—electron or hole—as distinct from the two kinds required for the working of a bipolar transistor, and for this reason is sometimes called "unipolar"; when it uses electrons it is called a n-channel type (*n* standing for *negative* electrons) and when it uses holes it is called a p-channel type (*p* standing for *positive* holes).

(3) F.E.T.s are for either depletion- or enhancement-mode operation. A depletion-type has to be biased-off like a thermionic valve. The enhancement-type has to be biased-on like a bipolar transistor.

(4) There are two types of gate junction, one based on the reverse-biased diode effect called a junction-gate, and the other based on inbuilt insulation called an insulated-gate.

(5) The operating polarities of a n-channel f.e.t. are similar to those of a n-p-n bipolar transistor, while a p-channel type is connected to the supply in a similar manner to a p-n-p bipolar transistor.

### Basic Circuits

So far so good, now let us have a look at some circuits. The first thing we need to know when dealing with f.e.t.s is the variety—depletion or enhancement-type. We need to know this from the biasing point of view, of course. Circuit (a) in Fig. 2 shows a common-source voltage amplifier with an input impedance of 2MΩ (determined by the gate resistor R1), using a n-channel depletion-type f.e.t. Notice how closely this follows the triode valve amplifier circuit, where R1 would be the grid resistor, R2 the anode resistor, R3 the cathode resistor, C1 the input capacitor, C2 the output capacitor and C3 the cathode bypass capacitor. Since the f.e.t. is a depletion-type it has to be biased-off like a valve and, like a valved circuit, this is achieved by the voltage dropped across the source resistor R3, the value of which is selected to produce the required bias current for the application in hand, as determined, of course, by the type of f.e.t. used. A typical bias current in this circuit might be about 0.5mA, and this would be established by adjusting the value of R3, which is not uncommonly a preset.

The gain of a f.e.t. is signified in terms of *transconductance* ( $g_m$ ), or mA/V, as with a thermionic valve, while as we should know the parameter associated with bipolar transistors is *current gain* ( $h_{fe}$ ) or the change of

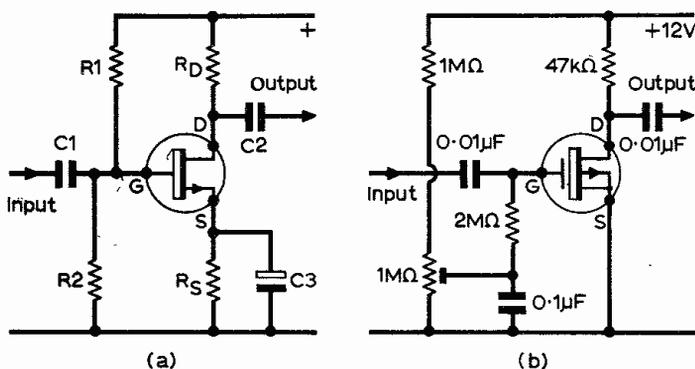


Fig. 3: (a) The biasing of a *n*-channel JGFET of the enhancement type; (b) alternative method of biasing an IGFET of the *n*-channel type.

output current with input current. Transconductance ( $g_m$ ), of course, relates to the voltage mode of operation of the f.e.t. Thus the gain is a measure of the change of drain current with gate input voltage. F.e.t.  $g_m$ s are not all that large, ranging from about 0.5 to 6 mA/V depending on how the device is operated; generally speaking the  $g_m$  increases with drain current. It is thus possible to vary the gain of a f.e.t. amplifier by varying the value of the resistance in the source circuit.

However, it should be noted that the voltage gain of a f.e.t. amplifier circuit in the typical RC coupled configuration will rise as the drain current falls. This is because the voltage gain of, say, the stage shown in Fig. 2(a) is equal to  $g_m R_L R_2 / (R_L + R_2)$ , where  $R_L$  is the resistance into which the stage is loaded, and because  $g_m$  is proportional to (drain current)<sup>1/2</sup> and  $R_2$  to  $1/(\text{drain current})$ .

While on the subject of f.e.t. gain it is worth noting that the medium value of f.e.t. output impedance lends itself admirably for connecting almost straight into a bipolar transistor input circuit, thereby giving the best of both worlds—a very high input impedance with medium f.e.t. gain times a considerable gain increase by the action of the partnered bipolar transistor. This sort of hybrid compatibility is nowadays often exploited in commercial equipment and Fig. 2(b) shows such an arrangement employing a f.e.t./bipolar “packet”. This gives a very high overall gain at a constant 2MΩ input impedance and at a medium output impedance.

Fig. 3(a) shows a simple a.f. amplifier using an enhancement-type f.e.t. This differs from Fig. 2(a) in the nature of the gate biasing. Here R1 and R2 form the gate potential-divider for biasing-on the device as with bipolar transistors.

Fig. 3(b) shows an alternative method of biasing, with the f.e.t. this time being an insulated-gate type of the *n*-channel variety. Sometimes the top 1M resistor is omitted. The bias is adjusted—to yield the required drain current—by regulating the variable (preset) resistor.

## Performance

In this sort of straightforward a.f. amplifier circuit the f.e.t. can produce voltage gains of up to 40 or so times and in addition to the high input impedance attribute the f.e.t. generally provides lower noise working than a bipolar transistor arranged for a similar input impedance. Moreover, f.e.t. amplifiers—both a.f. and r.f.—suffer less from the effects of overloading than similar amplifiers employing bipolar devices. One big problem of the bipolar transistor in such applications is that while the circuit can be arranged to provide the highest gain and least noise for a relatively small range of input

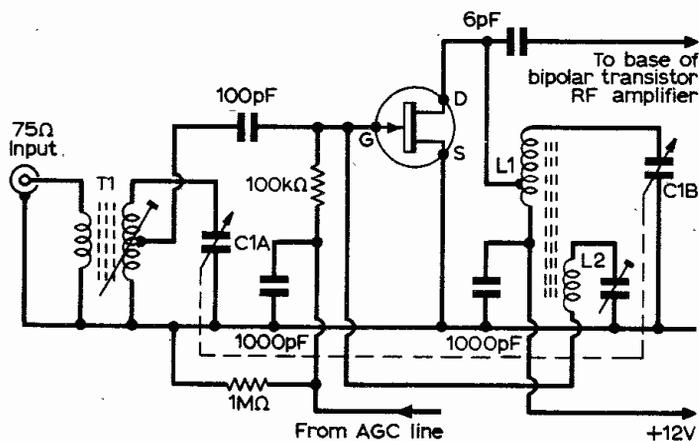


Fig. 4: JGFET arranged as a v.h.f. amplifier, tunable over Band II. The a.g.c. input is at the gate, via the 100kΩ and 1MΩ potential divider.

signal the occurrence of a signal—in band or spurious—rising above the dynamic limit rapidly pushes the amplifier into non-linearity, with a consequent rise in crossmodulation and intermodulation effects. The f.e.t. to a large extent combats these sorts of problems.

The transfer characteristic of a bipolar transistor is essentially exponential, while that of a f.e.t. is parabolic, following a square-law. That is the characteristic produced when input voltage is plotted against output current. The square-law characteristic of the f.e.t. can be useful in practical circuits for a.g.c. and manual gain control. These sorts of characteristics are already being exploited in audio equipment—for low-noise a.f. front ends with outstanding overload performance—and in radio tuners, especially of European and American designs, to produce f.m. sensitivities in the order of  $2\mu\text{V}$  for some -30dB of quieting, making it possible to get good off-air stereo reception with aerial signals hitherto considered impossibly low. The f.e.t. used in the front-end of the Vortexion CBL/7T tape recorder for example has a noise figure as low as 0.1dB, which is incredible in comparison with the near optimum noise figure of 2dB given by some of the best low-noise bipolar transistors.

## Typical Applications

Fig. 4 shows a circuit of a f.e.t. v.h.f. amplifier for a Band II (f.m.) tuner, using a *n*-channel device in the depletion mode. Again this is very similar to the triode valve counterpart, even to the extent of a.g.c. being applied at the input electrode

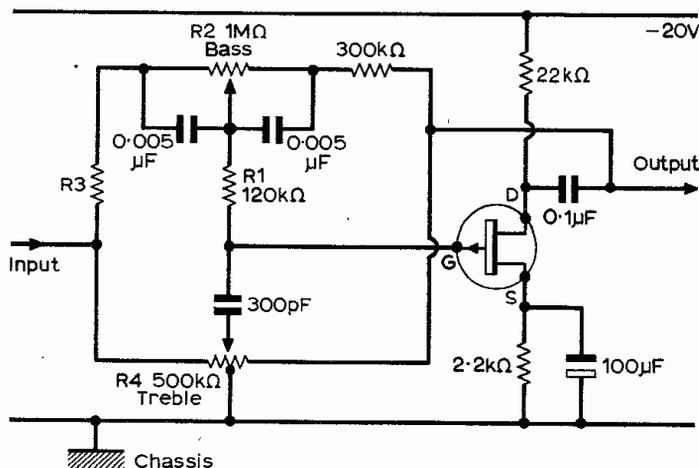


Fig. 5: A *p*-channel JGFET in a Baxandall tone control circuit.

### DE LUXE PLAYERS

PORTABLE CABINET As illustrated. To fit standard player or autochanger. **69/6**

RC5 AMPLIFIER 3 WATT. Ready made and tested with UCL82 triode pentode valve and loud-speaker. **59/6**

SUPERIOR AMPLIFIER. Ready made and tested. Better sound! Isolated AC Mains Transformer 3 watt output. ECL82 triode pentode valve. Volume and tone controls with knobs. **89/6**

Post 5/6 each item

**SINGLE PLAYERS MONO** AUTOCHANGERS MONO

Starr 9v. Battery	£2.19.6	B8R Superslim	£6.19.6
45trm Model	£2.19.6	B8R Transcription UA70	£12.19.6
EMI Junior	£6.19.6	Stereo/Mono	£12.19.6
Garrard SRP22	£6.19.6	Garrard AT60	£12.19.6

All fitted LP78 styli and pickup crystal complete.

**ALL LATEST GARRARD MODELS AVAILABLE**  
Send for our keenest quotation.



GARRARD TEAKWOOD BASE WB.1. Ready out for mounting 1000, 2000, 3000, SP25, AT60. **65/-**

GARRARD PRESPEX COVER SPC.1 for WB.1 EACH

PICK-UP ARM Complete with AGOS LP-78 Turnover GP67 and Stylus 25/-; GP67 15/-; Stereo Ceramic 35/-.

### CRYSTAL MIKE INSERTS

1 1/2 x 1/2 in. 6/6; ACOS 1 1/2 x 1/2 in. 3/6. BMS, 1" dia. 9/6

MOVING COIL MIKE with Remote Control Switch 19/6

### PORTABLE TRANSISTOR AMPLIFIER

Many uses, Intercoms, Baby Alarms, Guitar Practice, Telephones or Record Player Amplifier. ONE WATT OUTPUT

Wooden cabinet 12 x 8 x 4 in. Reziene covered two tone grey. Four transistors. 7 x 4 in. speaker. Volume control. Jack socket. Uses PP9 battery. **WORTH DOUBLE 79/6** Post 5/6.

OUR PRICE

### COLLARO BATTERY RECORD DECKS

4 speed model 9v. operated. Complete with pick-up fitted crystal cartridge. Plays 7, 10, 12 in. records. Fitted auto. stop and start. Ideal for use with above 69/6 POST transistor amplifiers. **OUR PRICE 69/6**

THE ABOVE GRANADA AMPLIFIER AND PLAYER DECK POST FREE IF PURCHASED TOGETHER.

### WEYRAD P50—TRANSISTOR COILS

RA2W 6in. Ferrite Aerial with car aerial coil. . . . .	12/6	Spare Cores . . . . .	6d.
Osc. P50/LAC . . . . .	5/4	Driver Trans. LFDT4. . . . .	9/6
1.F. P50/2CC 470 k/0s. . . . .	5/7	Printed Circuit, PCA1. . . . .	9/6
3rd L.F. P50/3CC . . . . .	6/7	J.B. Tuning Gang . . . . .	10/6
Telescopic Chrome Aerials 6in. extends to 23in. 5/-.		Weyrad Booklet . . . . .	2/-

### VOLUME CONTROLS

Long spindles. Midget Size 5K, ohms to 2 Meg. LOG or LIN. L/S 3/-, L/P 5/-, STEREO L/S 10/6, D.P. 14/6. 5K. S.P. Edge type, 5/-.

**80 Ohm Coax 8<sup>D</sup> yd.**

SEMI-AIR SPACED 40 yd. 20/-; 60 yd. 30/-

FRINGE LOW LOSS 1/6

Ideal 625 lines yd.

### VEROBOARD 0-15 MATRIX

2 1/2 x 5in. 3/8, 2 1/2 x 3 1/2in. 3/2, 3 1/2 x 3 1/2in. 3/8, 3 1/2 x 5in. 5/2.

EDGE CONNECTORS 16 way 5/-; 24 way 7/6.

PN5 36 per packet 2/4. PAGE CUTTERS 7/6.

S.R.P. Board 0-15 MATRIX 2 1/2in. wide 6d. per lin. 3 1/2in. wide 9d. per lin.; 5in. wide 1/- per lin. (up to 17in.).

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides 7 x 4in., 5/6; 9 x 7in., 6/6; 11 x 3in., 6/6; 11 x 7in. 7/6; 13 x 9in., 9/6; 14 x 11in., 12/6; 15 x 14in., 15/-.

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. 6/6; 14 x 9in. 5/6; 12 x 8 in. 4/6; 10 x 7 in. 2/6; 8 x 6 in. 2/6; 6 x 4 in. 1/6.

### Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key

1in. 16/-	1 1/2in. 17/6	1 1/2in. 19/6	1 1/2in. 24/-	2 1/2in. 44/3
1in. 16/-	1in. 19/6	1 1/2in. 20/6	1 1/2in. 29/-	2 1/2in. 57/3
1in. 16/9	1 1/2in. 19/6	1 1/2in. 21/6	2in. 39/-	1in. sq. 36/6

### 'SONOCOLOR' CINE RECORDING TAPE

5" reel, 900' with LP strobe markings, also cine light deflector-mirror for synchronisation. 14/- each.

Tape Spools 2/6. Tape Splicer 5/-. Leader Tape 4/6. Reuter Tape Heads for Collaro models 2 track 21/- pair. UNIVERSAL TAPE CASSETTES Type C60. OUR PRICE 14/-.

### 'THE INSTANT' BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER

200/250 v. A.C. Leaflet S.A.E. **35/-** Post 2/6.

RETURN OF POST DESPATCH Minimum Post and Packing charge 2/6. C.O.D. 5/- extra. Full list 1/-.

## RADIO COMPONENT SPECIALISTS

Written guarantee with every purchase. (Export—send remittance and extra postage, no C.O.D.)

### BARGAIN STEREO PARCEL

E.A.R. STEREO PLAYER CABINET suitable for B.S.R. Player Decks with 4 + 4 STEREO AMPLIFIER and TWO 6in. LOUDSPEAKERS BUILT INTO £13.19.6 CABINET AND LID. Post 10/6.

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350V .. 2/3	100/25V .. 2/-	8/800V .. 9/6	
4/350V .. 2/3	250/25V .. 2/6	16/800V .. 12/6	
8/450V .. 2/3	500/25V .. 4/-	16+500V .. 7/6	
18/450V .. 3/-	8+8/450V .. 3/6	32+32/250V 3/6	
32/450V .. 3/9	8+16/450V .. 3/9	50+50/350V 7/-	
25/25V .. 1/9	16+16/450V 4/3	60+100/350V 11/6	
50/50V .. 2/-	32+32/350V 4/6	3000/30V .. 8/6	

SUB.MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mF 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/-.

CERAMIC. 500V 1pF to 0.01mF. 9d. Discs 1/-.

### PAPER TUBULARS

350V-0-1 9d.; 0-5 2/8; 1mF 3/-; 2mF 150V 3/-.

500V-0-001 to 0-05 9d.; 0-1 1/-; 0-25 1/9; 0-5 2/6.

1,000V-0-001, 0-0022, 0-0047, 0-01, 0-02, 1/6; 0-47, 0-1, 2/6.

SILVER MICA. Close tolerance 1%, 5-500pF 1/-; 580-2,220pF 2/-; 2,700-5,600pF 2/6; 6,800pF-0-01, mid 6/- each.

TWIN GANG. "0-0" 208pF+176pF, 10/6; 365pF, miniature 10/1; 500pF standard with trimmers, 9/6; 500pF midget less trimmers, 7/6; 500pF slow motion, standard 9/-; small 3-gang 500pF 18/8. Single 40pF 365pF 7/8. Twin 10/-.

SHORT WAVE. Single 10pF, 25pF, 50pF, 75pF, 100pF, 160pF, 5/6 each. Can be ganged. Complete 9d. each.

TUNING. Solid dielectric. 100pF, 300pF, 500pF, 4/6 each.

TRIMMERS. Compression ceramic 30, 50, 70pF 1/-; 100pF, 150pF, 1/3; 250pF, 1/6; 800pF, 750pF, 1/9; 1000pF, 2/6.

### 250V RECTIFIERS. Selenium 1/2 wave 100mA 5/-; BY100 10/-.

CONTACT COOLED 1/2 wave 60mA 7/6; 85mA 8/6.

Full Wave Bridge 75mA 10/-; 150mA 19/8; 19V rect. 10/-.

RESISTORS. Preferred values, 10 ohms to 10 meg.

1w 1/2, 1w, 20w 3d., 1w 8d., 2w 1/-; 3w 10c 6d.

EIGHT STABILITY. 1w 1%, 10 ohms to 10 meg. 2/-.

Ditto 5%. Preferred values 10 ohms to 22 meg., 9d.

5 watt } 0-5 to 8-2 ohm 3w. 2/-  
10 watt } WIRE-WOUND RESISTORS 2/-  
15 watt } 10 ohms to 6,800 ohms 2/-

10K, 15K, 20K, 25K, 68K, 10W, 3/-

FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 8/8; 2a., 11/3; 4a., 17/6.

CHARGER TRANSFORMERS, P. & P. 5/-, Input 200/250v. for 6 or 12v., 1 1/2 amps., 17/6; 2 amps., 21/-; 4 amps., 30/-.

WIRE-WOUND 3-WATT POTS. T.V. Type. Values 10 ohms to 30K., 4/6

Carbon 30K to 2 meg. 4/6

WIRE-WOUND 4-WATT STANDARD SIZE POTS. LONG SPINDLE 50 OHMS to 100 K., 7/6

VALVE HOLDERS, MOULDED 9d.; CERAMIC 1/- EACH.

### NEW MULLARD TRANSISTORS 6/- each

OC71, OC72, OC81, OC44, OC45, OC171, OC170, AF117

REPANCO TRANSISTOR TRANSFORMERS

TT45. Push Pull Drive, 9.1 CT, 6/-; TT44 Output, CT8.1, 6/-.

TT49. Interstage 20:1, 6/-; TT52 Output 3 ohms, 4.5:1, 6/-.

TRANSISTOR MAINS POWER PACK. FAMOUS MAKE. FULLY SMOOTHED. FULL WAVE CIRCUIT **49/6**

9 Volt 500mA Size 5 x 3 x 2in.

TRANSFORMER ONLY. Size 2 1/2 x 1 1/2 x 1 1/2in. 9 volt 10/8.

### MAINS TRANSFORMERS

Post 5/- each

250-0-250 50 mA. 6.3v. 2a. Centre tapped . . . . .	19/6
250-0-250 80mA. 6.3v. 3.5a. 6.3v. 1a. or 5v. 2a. . . . .	30/-
350-0-350 80mA. 6.3v. 3.5a. 6.3v. 1a. or 5v. 2a. . . . .	35/-
300-0-300v. 120mA. 6.3v. 4a. C.T.; 6.3v. 2a. . . . .	45/-
MINIATURE 200v. 20mA. 6.3v. 1a. . . . .	12/6
MIDGET 220v. 45mA. 6.3v. 2a. . . . .	17/6
HEATER TRANS. 6.3v. 1 1/2a., 8/6; 6.3v. 4a. . . . .	12/6
Ditto tapped sec. 1.4v., 2, 3, 4, 5, 6.3v. 1 1/2 amp. . . . .	12/6
GENERAL PURPOSE LOW VOLTAGE, Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, and 30v. at 2a. . . . .	30/-
1 amp., 6, 8, 9, 10, 12, 16, 18, 20, 24, 30, 36, 40, 60 35/-	
3 amp., 0-12v. and 0-18v. . . . .	18/6
AUTO TRANSFORMERS 0-115-230v. Input/Output, 60w. 18/6; 150w. 30/-; 500w. 92/6; 1000w. 175/-.	

### COAXIAL PLUG 1/3. PANEL SOCKETS 1/3. LINE SOCKETS 2/-.

OUTLET BOXES. SURFACE OR FLUSH 4/6.

BALANCED TWIN FEEDERS 1/1. yd. 80 or 300 ohms.

JACK SOCKETS Std. open-circuit 2/6, closed circuit 4/6; Chrome Lead Socket 7/6. DIN 3-pin 1/6, 5-pin 2/-; Lead 3/6.

Phono Plugs 1/-. Phono Socket 1/-, 2-5mm, 3-5mm, 1/9

JACK PLUGS Std. Chrome 3/-; 2-5mm 1/9; 3-5 mm 2/6; DIN 3-pin 3/8; 5-pin 5/-.

WAVE-CHANGE SWITCHES WITH LONG SPINDLES. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 4/6 each.

1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way, 4/6 each.

Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 12/-, 2 water 17/-, 3 water 22/-.

Additional waters 5/- each water up to 12 max.

TOGGLE SWITCHES, sp. 2/6; sp. dt. 3/6; dp. 3/6; dp. dt. 4/6.

### 1968 GRAM CHASSIS

Post 6/-

Three Wavebands: Long, Med., Short, Gram. Five Valves: ECH81, EF89, EBC81, EL34, EZ80.

12-month guarantee. A.C. 200-250v. Ferrite Aerial 5 watts 3 ohm. Chassis 13 1/2in. x 7in. x 5in. dial size 13in. x 4in. Two pilot Lamps. Four Knobs. **£10.19**

Aligned calibrated. Chassis isolated from mains.

DE LUXE STEREO GRAM CHASSIS V.H.F., M.W. SW 18-50m. SW 60-180m. Magic eye, push buttons. **£19.19**

6 valve plus rect. Size 15 x 7 1/2 x 6in. high.

### BAKER MAJOR £8

30 14,500 c.p.s., latest double cone, woofer and tweeter cone together with a special BAKER magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms. Price £8, or Module kit. 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £10.19.6

LOUDSPEAKER CABINET WADDING 18in. wide, 2/6ft.

### BAKER "GROUP SOUND" SPEAKERS—POST FREE

'Group 25'	'Group 35'	'Group 50'
12in. 6 gns.	12in. 8 1/2 gns.	15in. 18 gns.
25w.	35w.	50w.

ALL MODELS "BAKER SPEAKERS" IN STOCK

E.M.I. Cone Tweeter 3 1/2in. square, 3-20k/s. 10W 17/6. Quality Horn Tweeters 2-18k/s. 10W 29/6. Crossover 16/6.

LOUDSPEAKERS P.M. 3 OHMS. 2 1/2in., 3in., 4in., 5in., 7 x 4in., 15/6 each; 8in 22/6; 6in 18/6; 10in 30/-; 12in. Double cone 3 or 15 ohm 35/-; 10 x 6in. 30/-; 8 x 6in. 21/-.

E.M.I. Double Cone 1 1/2 x 3in., 3 or 15 ohm models, 45/-.

SPECIAL OFFER: 8 ohm, 2 1/2in.; 80 ohm, 2 1/2in., 8in.; 25 ohm, 6 x 4in.; 35 ohm, 2 1/2in.; 15/6 EACH 15 ohm, 10 x 2 1/2in. 7 x 4in.

SPEAKER FRET Tygan various colours, 52in. wide, from 10/-; 26in. wide from 5/- ft. SAMPLES S.A.E.

EXPANDED METAL Gold or Silver 12 x 12in., 6/-.

### ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 ohms General Purpose . . . 19/6

H.R. HEADPHONES 2000 ohms Super Sensitive . . . 35/-

LOW RESISTANCE HEADPHONES 3-5 ohms . . . 35/-

DE LUXE PADDED STEREO PHONES 8 ohms . . . 79/6

### MINETTE AMPLIFIER

For all Record Players. A.C. Mains Transformer. Chassis size 7 x 3 1/2 x 4in. High. Valves ECL82, EZ80. Quality output 3 ohm matching. Bargain offer complete with engraved control panel, valves, knobs, volume and tone controls, wired and tested. 12 month guarantee. **79/6** Post 5/6

### ALL EAGLE PRODUCTS SUPPLIED AT LOWEST PRICES

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial, etc. **79/6**

BARGAIN DE LUXE TAPE SPLICER Cuts, trims, joins for editing and repairs. With 2 blades. **17/6**

BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. **59/6**

BARGAIN TRANSISTOR FM-LW-MW TUNER: 10 semi conductors. Calibrated tuning dial. 9v. operation. FM89-108 Mc/s; MW 190-560 metres. LW 850-2000 metres. Size 2 1/2 x 8 x 5 1/2in. **£14.19.6**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. **69/6**

40-PAGE EAGLE CATALOGUE 5/- Post Free

### RADIO BOOKS (Postage 9d.)

Practical Transistor Receivers . . . . .	5/-
Practical Stereo Handbook . . . . .	3/6
Supersensitive Transistor Pocket Radio . . . . .	3/6
High Fidelity Speaker Enclosures and Plans . . . . .	5/-
Radio Valve Guide, Books 1, 2, 3, or 4 ea. 5/- No. 6 ea. 6/-	
Practical Radio Inside Out . . . . .	4/6
Shortwave Transistor Receivers . . . . .	5/-
Transistor Communication Sets . . . . .	6/-
Modern Transistor Circuits for Beginners . . . . .	7/6
Sub-Miniature Transistor Receivers . . . . .	5/-
Wireless World Radio Valve Data . . . . .	9/6
At a glance valve equivalents . . . . .	10/6
Valves, Transistors, Diodes equivalents manual . . . . .	6/-
How to receive Foreign T.V. programmes on your set by simple modifications . . . . .	5/-

### SANGAMO 3 inch SCALE METERS

Various calibrations/movements. 500 Microamp; 1 Milliamper; 50-0-50 Microamp, etc. S.A.E. for list. **45/-**

POCKET MOVING COIL MULTIMETER. 0-1,000 AC/DC. ohms 0 to 100k, etc. **49/6**

SUPERIOR MOVING COIL MULTIMETER 0-2-500V D.C. 20,000 ohms per volt, 0-1,000V. A.C. Ohms 0 to 8 meg. 50 Microamps (Full list Meters S.A.E.) **99/6**


### BRAND NEW QUALITY EXTENSION LOUDSPEAKER

Black plastic cabinet, 20ft. lead and adaptors. For any radio, intercom, tape recorder, etc. 3 to 15 ohms. PRICE **30/-** Size: 7 1/2 x 5 1/2 x 3in. POST 2/6

CALLERS WELCOME 337 WHITEHORSE ROAD, WEST CROYDON

Buses 133, 68 pass door. S.R. Stn. Selhurst Tel. 01-684-1665

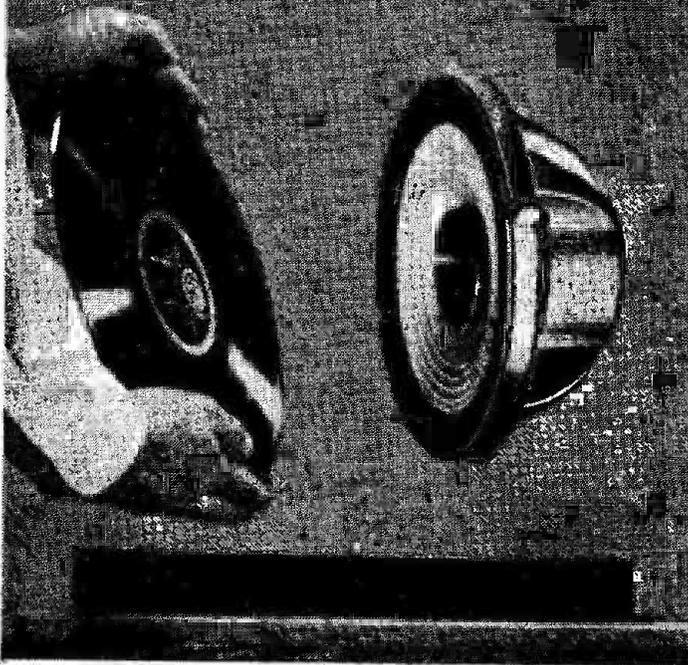Play through  
the TwinAxiette  
and listen  
to the difference!



# Goodmans

**Goodmans Loudspeakers Ltd.**

Axiom Works, Wembley, Middlesex. Telephone: 01-902 1200

Please send me FREE Goodmans High Fidelity Manual, which includes details of the TwinAxiette 8.

Name .....

Address .....

PW12

**Fabulous Value**

### STEREOPHONIC KUBA ROYAL RADIOGRAM

This radiogram chassis is offered complete with carefully matched loudspeaker system, two 10in. speakers, two 4in. Cone Tweeters and latest BSR UA70 Mono/Stereo record changer—a complete quality stereophonic radiogram at half normal price.


4 wavebands—AM/FM—8 piano keys control. 16 watts push-pull output—frequency response 30-20,000 cycles. **EASY TO INSTALL. NO TECHNICAL KNOWLEDGE REQUIRED.**

**ONLY £79.19.6.**

H.P. terms available. Deposit £20 and 24 monthly payments of £2/8 (total H.P. £95). Send £20 today or write for free leaflet.
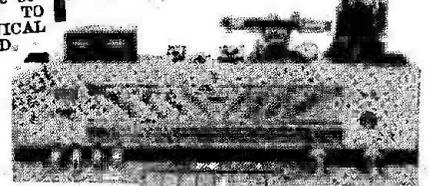
### Fantastic Bargain Offer

**KUBA IMPERIAL 666 STEREOPHONIC HI-FI RADIOGRAM CHASSIS**—complete with two 10in. x 6in. speakers and the latest BSR Mono/Stereo record changer—a complete radiogram at half normal price. 4 Waveband AM/FM chassis with the very latest printed circuitry—7 push button controls, 10 watts total output. Only **49½ Gns.** plus P. & P. 17/6. **EASILY FITTED. NO TECHNICAL KNOWLEDGE NECESSARY.** H.P. available £13.0.0 deposit plus 24 monthly payments 40/8 (total H.P. £61.16.0). Send £13.17.6 today.



CALLERS WELCOME

**POST THIS COUPON NOW!**

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name .....

Address .....

**LEWIS radio**

100 CHASE SIDE, SOUTHGATE, Dept. P1289, LONDON, N.14 TELEPHONE PAL 3733/9686

Become a

## COLOUR TELEVISION SERVICE ENGINEER

by taking a

## COLOUR TELEVISION SERVICING CORRESPONDENCE COURSE

with

**E. C. T. T.**

We specialise in Colour Television Training  
Practical Courses also held throughout the year  
Fees moderate Terms available

Write today for FREE information to:

**Electronic and Colour Television Training Ltd.,**  
Administrative Offices,  
45 Walton Road,  
East Molesey,  
Surrey.  
Telephone: 01-979-5553

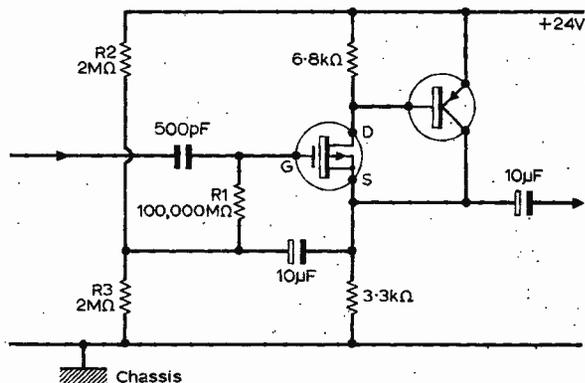


Fig. 6: Hybrid f.e.t./bipolar circuit with ultra high input impedance.

—the gate in Fig. 4. T1 is the aerial coupling transformer—which can also be arranged for 300Ω balanced input if required—and L1 is the drain tuned circuit, with L2 providing some neutralising feedback to the gate circuit. C1A and C1B are ganged.

Figure 5 shows a p-channel f.e.t. in the depletion mode operating in a typical audio application—in the Baxandall tone control circuit in fact. The bass and treble controls are rigged in the conventional network for this kind of circuit, while the f.e.t. is biased by the 2.2kΩ resistor in its source circuit. The electrolytic performs the same duty as such a capacitor in the cathode circuit of a valved amplifier (that is, bypassing audio and preventing degenerative feedback). The gate circuit is returned to chassis through the series combination of R1, R2, R3 and R4.

Finally, Fig. 6 shows a n-channel insulated-gate f.e.t. arranged to provide an extremely high input impedance—of 100,000 MΩ, fixed by the gate resistor R1—in conjunction with a p-n-p bipolar transistor for high gain, the base of this being d.c. coupled to the drain of the f.e.t. Gate biasing is handled by the potential divider R2 R3, while the 3.3kΩ resistor in the source circuit of the f.e.t. and the collector circuit of the bipolar transistor is the output load resistor. Incidentally the very high input impedance in this case is given by the nature of the f.e.t. which is a metal-oxide insulated-gate type. ■

## CORRIGENDA

### FET VOM—APRIL ISSUE

SW2 should have been listed in the components list as a 2-pole 3-way switch.

### SIMPLE SIGNAL GENERATOR AUGUST ISSUE

D1 can be a BY100 or any other silicon rectifier with a minimum rating of 800V p.i.v. and 50mA. In the components list C7 should be listed as 0.0047μF and not 0.0047pF.

### THREE TRANSISTOR RECEIVER AUGUST ISSUE

The following corrections should be made to the components list (page 248) for the third receiver in the series "Three Simple Receivers for Beginners":

Add R11 1kΩ and C8 10μF.

R10 should be 10kΩ and C7 100pF (ceramic or silver mica) as on the circuit.

The following amendments should be made to the above chassis layout (Fig. 8):

The resistor connected between C6 +ve and point "d" is R9. C7 is omitted: it should be shown connected between the +ve end of D1 and the lug on IFT2.

## PRACTICAL ELECTRONICS

### Electronic Games to build for Christmas

—Electronic Stockmarket

—Flip-flop "heads or tails"

### Door Chime

—Another printed board project.

DECEMBER issue on sale NOW

# Practical Gift

## FOR A PRACTICAL MAN!

**A** FULL-YEAR series of Practical Wireless issues delivered by post each month would be an ideal Christmas present. Why not give a subscription to a friend? He would certainly find the magazine just as interesting as you do and each issue would remind him of your good wishes.

But don't think too long—Christmas is very close. Act now and send your friend's name and address, together with your own and a remittance to cover each subscription to: Subscription Manager, Practical Wireless (Dept. Z), Tower House, Southampton Street, London, W.C.2. We will despatch first copies to arrive in time for Christmas, and send an attractive Christmas greetings card in your name to announce each gift.

RATES (including postage) for one year (12 issues) United Kingdom and Overseas £22.0.

To avoid disappointment, make sure of your own copy by placing a regular order NOW with your newsagent.

# PYRAMID ALL PURPOSE SYSTEM

By F. G. RAYER



## PART 4—TRANSISTOR T.R.F. TUNER and RECORD PLAYER DECK

WHEN the main need is reception of the stronger BBC transmissions, a t.r.f. tuner can give excellent results. Construction is much simpler than that of a superhet tuner, and the alignment difficulties sometimes experienced with the superhet circuit are absent.

The circuit diagram, shown in Fig. 1, has an AF117 as r.f. amplifier, followed by a diode detector, both stages being tuned by the ganged capacitor VC1/VC2. This provides medium wave coverage. It was decided not to incorporate full long waveband coverage, but by switching in capacitors C1 and C5 a small band around 1,500 metres can be tuned.

This method avoids the necessity of coil changing.

VR1 is the r.f. gain control, which is useful to avoid overloading if strong signals are present. Optional aerial terminals are provided to help obtain the best results with a variety of aerials.

Terminal "A" is used for a short extending telescopic aerial, or a short indoor wire. Terminal "B" is better for a somewhat longer aerial, such as a short outdoor wire, or an indoor aerial perhaps 15ft. or more in length. TC1 is adjusted for optimum results.

Terminal "C" is used for a longer aerial, or when maximum selectivity is needed. In all cases a good earth system improves reception, but is not essential.

Audio output is taken from detector diode D1. When the tuner is used with the amplifier described earlier, the amplifier volume control functions as the diode load. Should the tuner be used with other equipment, in which no such load is present, then a 5.6kΩ resistor should be connected across C6.

The tuner may of course be used with other amplifiers than the one mentioned earlier. It will also give excellent reception, used alone with medium or high impedance headphones. It would then run from a 4.5 or 6V battery. Current is otherwise drawn from the amplifier.

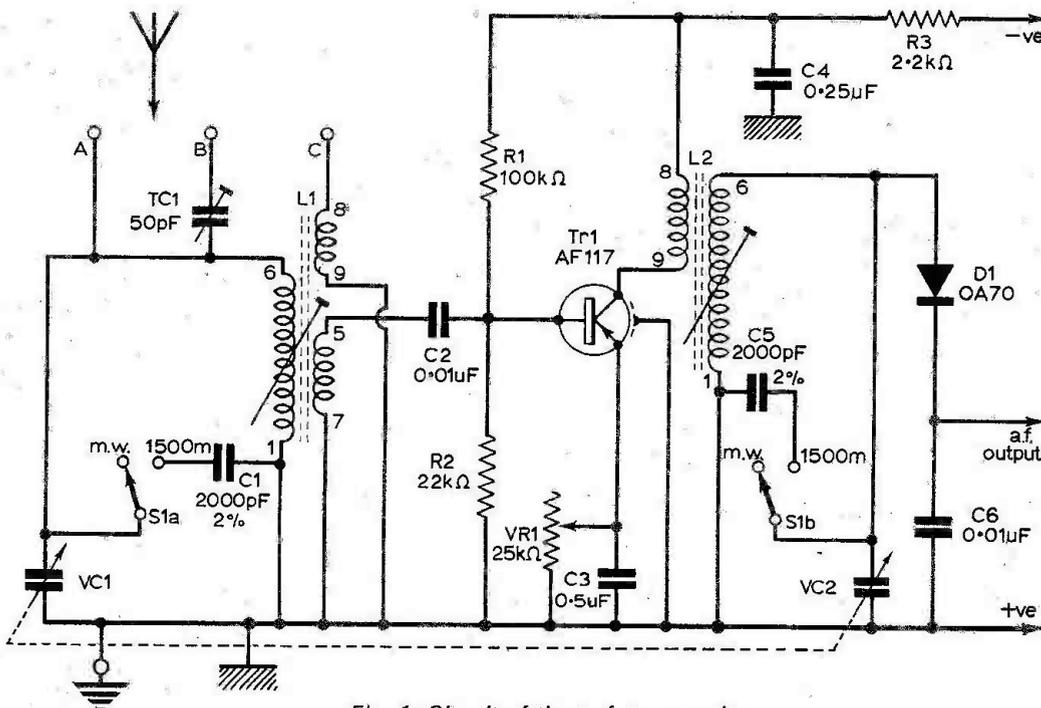


Fig. 1: Circuit of the t.r.f. tuner unit.

## Chassis, etc

As only a very small chassis is needed, this was made from a  $7 \times 3$  in. "Universal Chassis" runner. A 90-degree section is cut from each chassis flange  $1\frac{1}{2}$  in. from the end. The runner can then be bent to make a chassis  $4\frac{1}{2}$  in. wide,  $1\frac{1}{2}$  in. high, and 3 in. deep. This can be fitted into the cabinet specified in the components list, the chassis being cut away slightly at the front bottom corners, to clear the case flange.

Components are wired up as shown in Fig. 2. The coil canisters are used as screens, the lids being held to the chassis by the coils and a 6BA bolt with tag, which provides the "MC" or chassis points. Other leads pass down through holes in the chassis. When this wiring has been completed, the cans are screwed on over the coils.

A tag strip supports TC1, and provides tags A, B and C on which the aerial lead can be clipped.

## VC1/VC2 and Alignment

If dimensions are to be as given, VC1/VC2 should be as small as possible. That specified in the com-

ponents list is easily obtained, and has an integral ball drive. The drive is not essential, or could be added to a capacitor without drive. A maximum capacity of 300 to 500pF for each section will be satisfactory.

It was found that no trimmers were necessary, but should the tuning capacitor have trimmers, adjust them at the high frequency end of the m.w. band, for optimum performance.

With the circuit as in Fig. 1, place the switch in the 1500m position, set VC1/VC2 nearly fully closed, and adjust the coil cores from the underside of the chassis to tune in the BBC transmission. Then switch to medium waves, and if necessary make a compromise adjustment of the cores, for best reception around 400-500 metres.

As the second coil is loaded by the diode, losses of efficiency from slight mis-alignment are small. Should it become necessary to experiment with the tuned circuits 50pF trimmers should be fitted across VC1/VC2. Trim for best results with the tuning gang nearly fully open, and adjust the coil cores on medium waves for best results around 400-500m. Connect a 500pF or similar pre-set capacitor in

parallel with C1 and C5, and adjust these pre-sets for best reception at 1500m. It is also possible to use the coupling winding on the second coil to feed the diode. This increases selectivity.

## Under the Chassis

Most items are supported by a tagstrip as can be seen in Fig. 3. Transistor leads E (emitter), B (base), S (screen) and C (collector) are soldered to tags, and identified by the extra space between S and C wires.

For use with the amplifier described, take a flexible lead from R3. This is fitted with a plug to insert in the amplifier socket providing the battery negative supply.

The positive or chassis return circuit is completed by the outer brading of a co-axial lead, the inner lead carrying the audio frequency output, from the junction of D1 and C6.

With leads provided in this way, it is only necessary to plug in the co-axial connector and negative plug.

If m.w. coverage only is required, omit the switch, also C1 and C5.


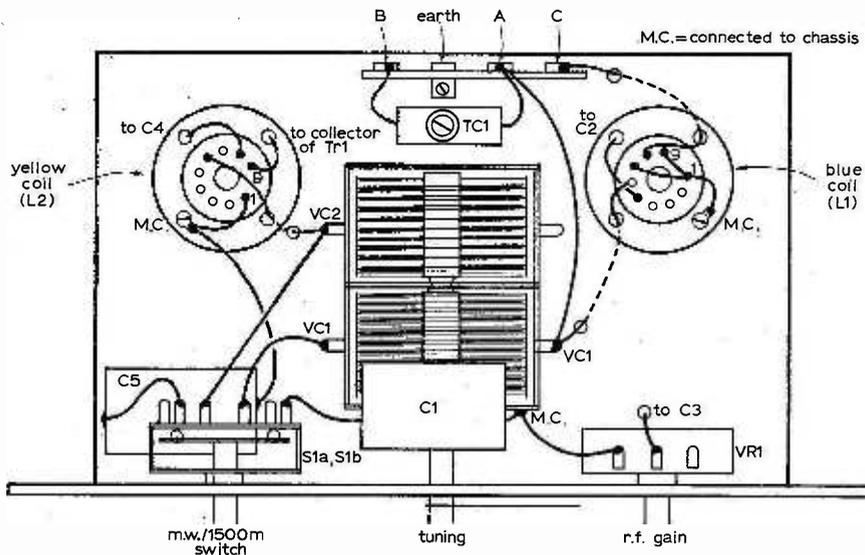


Fig. 2: Above-chassis layout. Fig. 3: Under-chassis layout.

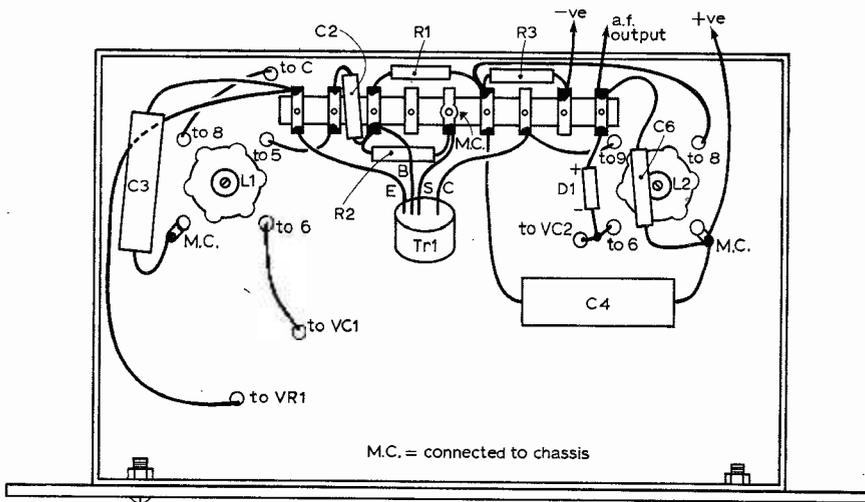

# THE RECORD PLAYER

This is battery operated, and intended for use with the "Pyramid" amplifier, or other transistor amplifiers of similar type. The turntable unit has a 9 volt motor and a PP9 battery gives long service. It has a 2-speed auto-stop mechanism, for 33 and 45 r.p.m. records, with a crystal pick-up.

For record playing with the "Pyramid" amplifier, it is only necessary to unplug the radio tuner or other equipment, and plug in a co-axial connector from the player.

## Case

This is of a simple type, constructed as shown in Fig. 4. Top and bottom consist of a 7 × 10in. piece of hardboard. Front, sides and back are  $\frac{3}{8}$ in. thick wood, sawn from 3in. wide boards. The lengths of these pieces would have to be changed slightly if the wood is not of this thickness.

A piece of cardboard or paper is cut with scissors to clear the motor mechanism, and used to mark the hardboard for sawing. All items are secured together with adhesive and panel pins, the hinged back being omitted.

When the adhesive is dry, edges and corners are

smoothed with a glasspaper block. Two small strips of wood keep the battery in place. Corner battens may be fitted at each corner to reinforce the cabinet.


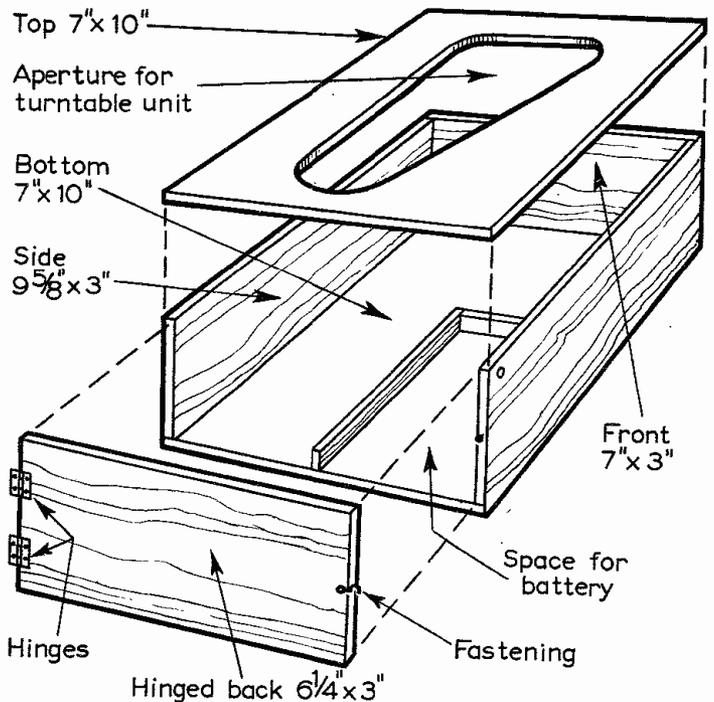


Fig. 4 (above): Case construction details

Fig. 5 (below): Motor and pickup connections

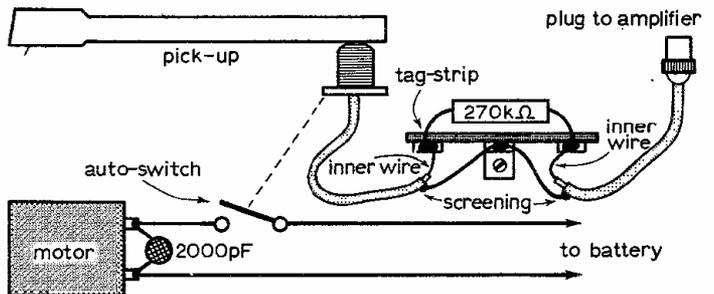

## ★ components list

### RECORD PLAYER UNIT

9V 33/45 r.p.m. turntable unit with crystal pickup; 270kΩ  $\frac{1}{4}$ -watt resistor; 2000pF disc ceramic capacitor; tagstrip, coaxial lead and plug.

Case: Top—hardboard 10 × 7in.  
 Bottom—hardboard 10 × 7in.  
 Front—7 × 3in.  
 Sides (2)— $9\frac{5}{8}$  × 3in. } All  $\frac{3}{8}$ in. wood  
 Back— $6\frac{1}{4}$  3in.  
 Hinges, etc.

### T.R.F. TUNER UNIT

Resistors: all 10%  $\frac{1}{4}$ -watt

R1 100kΩ R3 2.2kΩ  
 R2 22kΩ

Capacitors:

C1 2000pF 2% C4 0.25μF  
 C2 0.01μF C5 2000pF 2%  
 C3 0.5μF C6 0.01μF

TC1 50pF pre-set

VC1/VC2 Jackson 02 twin 365pF slow-motion, or similar

Semiconductors:

Tr1 AF117  
 D1 OA70 or similar

Miscellaneous:

VR1 25kΩ linear pot. Universal chassis single runner 7 × 3in. (Home Radio). Cabinet: Dinkicase 4 × 6 × 4in. (Electroniques). Coils: Blue and Yellow, Range 2, miniature transistor type (Denco). Knobs, tagstrips, 2-pole 2-way switch, etc.

## External Finish

The case is covered with one of the self-adhesive materials which can be obtained in many colours. All dust must be wiped off first. The case is placed upside down on a piece of material large enough to cover the front and sides also, with some overlap on to the bottom. It can then be cut to fit the corners, and the bottom is covered with a separate piece. The material is turned over inside the rear edges of the top, bottom and sides at the back.

The material is cut to suit the motor opening. The back is similarly covered, and fitted with two miniature hinges and a catch. It should be checked for size first, as it needs to be slightly under the dimensions given, to allow for the material.

Other finishes would be satisfactory, including bronze or other coloured "hammer finish" paint, which results in a metallic appearance.

Various ready-made record player cabinets are available, and often have a suitcase-type lid, which closes over the turntable. This type of cabinet is usually constructed by making a box deep enough for both lid and bottom. It is afterwards sawn round to produce the lid. Bottom and lid are finished off separately, and a panel for the motor is cut to fit

—continued on page 622



# AUDIO SUPPLEMENT

## No. 3 — SERVICING, TEST EQUIPMENT, WORKSHOP PRACTICE

**I**N the previous sections of this supplement we have considered the standard and parameters of audio equipment, and discussed some of the theory from which these figures may be derived. To conclude this brief look at the audio field we must outline a few of the tests that may be carried out to prove the validity of those figures. Audio in general, high fidelity in particular, is a very subjective art. Ultimately, much depends on the judgement of our own ears. But instruments can narrow the field of investigation for us, and will often reveal subtle factors of deviation which our ears refuse to distinguish, or to which our hearing has become accustomed. The aim, then, is objectivity.

Equally important, in practice, is the matter of impedance matching, avoidance of poor joints and hum loops, and correct siting of the ancillary parts of the equipment. The room or space in which a recording is made, and that place where the result will be reproduced, affects the sound we shall hear, and our relationship with the microphone or loudspeaker system and the acoustics of the room have all to be taken into account.

In fact, both the subjective and the objective assessment of audio equipment have to be made together, and we shall endeavour, in this section, to treat both aspects in a practical manner, as the relevant points arise.

### Microphones

Beginning at the input end of the audio chain, it is necessary to consider the type (and number) of microphones, the siting—in accordance with room acoustics and the type of signal we are going to record—and the matching to the following links of the chain.

Types of microphone were dealt with fairly comprehensively in the section on transducers. Comparative sensitivities and outputs have been covered and some idea of how the standards are derived was also touched upon. It should be stressed, however, that choice of microphone depends as much on the signal expected and the room acoustics as on "cold-blooded" efficiency. The ribbon microphone is perhaps the most versatile in the hands of an experienced user (an unfortunate phrase, for the last thing one wants to do is to handle a ribbon mike while recording!). It is not the most sensitive, but its extended upper frequency range, good response characteristics and selective polar diagram allow careful siting to produce good results, where other units, although having greater output voltages for the same sound pressure applied to them, will not be so selective, nor have such a good signal-to-noise ratio.

The use of an inbuilt transformer to raise the very low impedance of the ribbon unit to a line impedance

suitable for matching to a preamplifier also enables us to get sufficient sensitivity to load most high fidelity input stages. But the impedance is still low enough for long lines to be used without the danger of hum pickup or the attenuation of the high frequencies by the self-capacity of the cable. For this purpose, a balanced type of connection is often used.

High quality cable is needed for a balanced input, to avoid cable noise with movement, due to the changing capacity which causes temporary imbalance. As with all balanced systems (and this includes the 300-ohm type of aerial feeder for f.m. radio inputs), preservation of balance is vital. Any cable damage will lead to hum and other noise level increase, and poor joints are even more intolerable than with single-screened systems.

The microphone can be regarded as a type of generator with a reactive shunt and series element. As low impedance devices, such as ribbon and moving coil microphones, will generally match into a pre-amplifier with greater source impedance, most of the signal generated will be fed to the preamp. The safeguard against noise is partly built-in by this factor. Where a microphone has a fairly level frequency response, extending well into the higher regions, sharp peaks will not be troublesome and the problems of acoustic feedback are lessened. Add to this the polar diagram advantage of the ribbon microphone, which allows siting with a preference for the signal and exclusion of unwanted sounds such as reflections and we can see why the reduction in sensitivity is easily offset by an improvement in acoustical efficiency. The improvement can, in practice, be too great! Where a ribbon unit is sited too close to the sound source, some bass attenuation may be required. Speakers who like to kiss the microphone should not use ribbon units.

Moving coil microphones are extremely versatile, more robust, and often give a higher output. They are the largest branch of the microphone family, and range over a wide price. By careful arrangement of the mounting and housing, a favourable response curve and polar diagram can be obtained.

Where more than one microphone is used, either as a stereo input set-up or as a combined mono input to a mixer and preamplifier, care must be taken to ensure that the two units are in phase. Normally, the polarity of microphones will be marked, or the connections arranged so that leads cannot be crossed. Where this is not the case, or where some doubt arises through the use of dissimilar units, some experiment will be needed. The cancellation effects of out-of-phase connection will give rise to some quite unmistakable distortions, especially when the two units are sited at equal distance from the sound source.

Stereo siting can be either "co-incident" with the microphones placed close together, usually one above the other, and angled outwards to cover the sound field, or widely spaced to give a broad coverage. Each system has its advantages.

Reflected sounds can be troublesome, and a very "live" acoustic needs great care with microphone siting. Some "damping" can help—even a coat hung over a chair may reduce the unwanted reflection sufficiently to enable good recordings to be made! Room furnishings can be re-arranged, doors and windows opened to break up the reflecting areas—so long as this does not of itself introduce unwanted noise. A microphone in the centre of a flat table is often a failure. Even the most careful padding of the table top will not reduce the reflections, and the solution may be to raise the microphone or site it nearer a corner. It is in such small matters that the difference between success and failure lies.

Room acoustics will have less effect if the microphone is near the sound source. This seems obvious, but is too often disregarded when a wide sound source is to be captured. Some reverberation may be helpful to obtain "presence", and more than one microphone can be used; one sited to get the best direct sound, the other shielded as much as possible from the direct sound, and arranged to pick up the reverberations.

Ceramic and crystal units (piezo-electric), are general with cheaper audio systems, not usually employed when high fidelity is the aim. This is not to say that good quality piezo-electric devices are non-existent. But, generally, the attraction is cheapness, and some precaution is necessary to obtain the best results.

These are high impedance devices, thus limiting the length of connecting lead. The equivalent circuit is a voltage source in series with a capacitor. This works into an essentially resistive load, fairly high, but seldom as high as the microphone. As the capacitive element has a high reactance at low frequencies, any resistive damping at the input of the preamplifier will result in bass loss. This means that high impedance matching is necessary, and the possibility of hum and noise pickup is a further limitation.

Exact tests are beyond the scope of all but the best laboratories. Comparison tests and that prime tool—

experience—are the standby of the average workshop.

Servicing should be limited to the checking of continuity and inter-connections. A low resistance reading will be obtained with ribbon and moving coil units, and a faint crackle will be heard as the ohmmeter is connected. Crystal units will register an open-circuit, but as the connection is made and broken, again, a faint click should be audible.

Most common cause of faults is cable breakage, and this will nearly always be at the point of greatest flexing—where the cable enters plug or microphone, or is twisted and clamped within the housing.

## Gramophone Pickups

Some of the most precise test and adjustment procedures in audio work centre about the gramophone pickup. With stylus playing weights down to a couple of grams and stylus tip radii less than 0.0007in., some delicate setting up may be needed to get the best possible reproduction. We are not so much concerned here with the pickup cartridge, but with the combination of cartridge and arm and their relationship to the disc.

Figure 1 shows the sort of calculation that has to be made, for example, when mounting a pickup arm on a motor board. This precision is needed to take care of tracking angle, offset angle and sidethrust.

Because the cutting stylus is chisel shaped and tracks in a parallel fashion across the disc when this is being made, some attempt is needed to encourage the reproducing stylus to follow the same path. There have, in fact, been a few mechanisms based on diametric rather than pivoted movement, but mechanical considerations other than pure direction of stylus movement have offset any advantage that may have been gained. To achieve optimum results, a pivoted arm of infinite length would be needed. The longer the arm, the less the tracking error, but again, other considerations intervene. The angle of the plane of stylus vibration relative to the groove varies and second harmonic distortion is generated. Offsetting the head in relation to the plane of the arm reduces the "angle-of-attack" and the distortion. Allowing the tracking curve to "overhang" the centre of the disc reduces the distortion still further.

Distortion is inversely proportional to linear groove

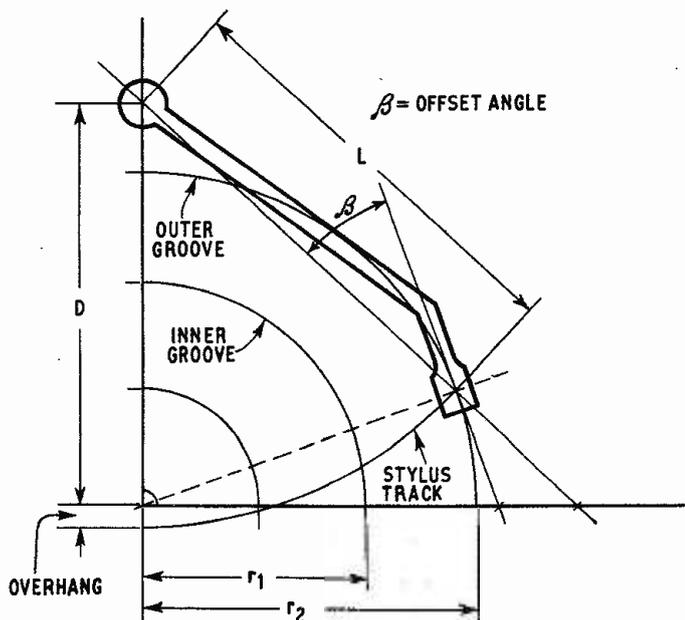


Fig. 1: Pick-up arm constants—horizontal plane.

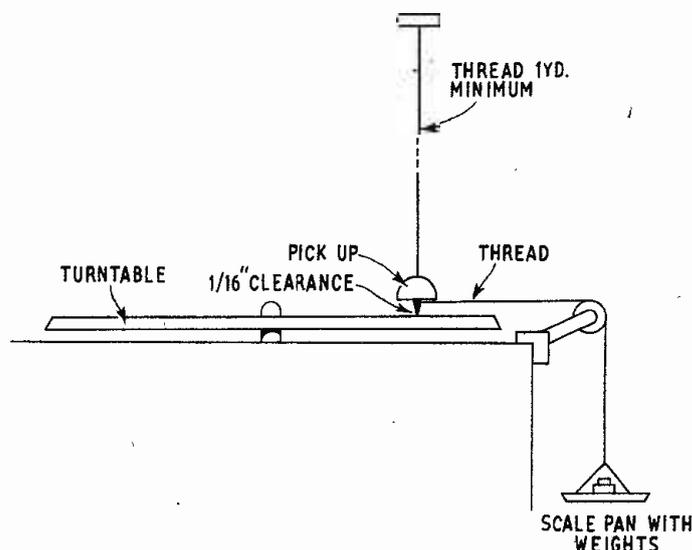


Fig. 2: Method of measuring back bearing friction.

velocity. A greater angle error on the outer grooves than the inner grooves of a disc can be tolerated. Some compromise is required. Distortion tends to be greatest at the lower reproducing speeds nearer the centre of the record: this is unfortunately the section of the recording likely to contain the greatest amplitude variations, musical climaxes, etc., and the offset angle for minimum tracking error may not be the best for minimum distortion.

Referring to Fig. 1, the formulae for overhang,  $D$ , and offset angle,  $\beta$ , are as follows:

$$D = \frac{r_1^2}{L \left( \frac{L}{4} \left( 1 + \frac{r_1}{r_2} \right)^2 + \frac{r_1}{r_2} \right)} \text{ inches}$$

$$\beta = \frac{r_1 \left( 1 + \frac{r_1}{r_2} \right)}{L \left( \frac{L}{4} \left( 1 + \frac{r_1}{r_2} \right)^2 + \frac{r_1}{r_2} \right)} \text{ radians}$$

where  $L$  is the arm length from pedestal pivot to stylus point,  $r_1$  the radius of the innermost groove and  $r_2$  of the outer groove. The offset angle  $\beta$  is in radians. In the example given, the arm length of  $7\frac{1}{2}$  in. and offset angle of  $24\frac{1}{2}$  degrees gives an overhang of 0.56 in. and a total distortion figure of below 2 per cent.

To aid mounting of arms, pivot-to-spindle length is often worked out by the arm manufacturer and stated in his specifications. Templates are frequently provided and should always be adhered to where available. If the cartridge to be fitted substantially alters the stylus point position from the type recommended by the arm supplier, some compensation will be needed. Pivot-to-stylus dimension is the most important single factor in pickup-arm mounting. Some adjustment of cartridge position is often provided.

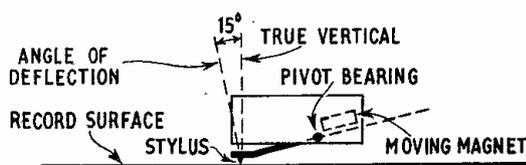


Fig. 3: Pick-up constants—vertical plane.

Adjustment of sidethrust and of stylus angle will also be found. A force tending to push the pickup toward the spindle exists and the stylus will bear more heavily on the inner wall of the groove, producing distortion especially on stereo recordings. High compliance cartridges require more compensation, and a weighted pivot, thread and weight or magnetic system will be employed to compensate for the varying forces. Stylus angle has now been standardised at 15 degrees, as shown in Fig 3, and where adjustment is provided this rake should be maintained in the playing position. For this to be accurate, the level of the arm must also be checked, so that it is horizontal in the playing position. The tendency of the pick-up arm to "skate" inwards expressed in a formula,  $F = 300w \tan a$  (dynes), where  $w$  is the playing weight in grams and  $a$  the angle from tangency. Without going too deeply into the geometry of the system, we can see that an increase in playing weight may be called for unless some anti-skating device is used. Increased in playing weight results in rapid groove deformation and loss of high frequencies, which may be "rubbed off" even at the first playing.

Friction due to the back bearing is another factor to

be taken into account. It may not have any compensating adjustment, but during service every effort should be made to reduce its effect. To measure this friction, a set-up such as in Fig. 2 may be needed, with thin thread suspending the head so that the stylus just fails to contact the disc. Then the second thread runs from pickup, over the pulley to the scale pan; the head is tapped gently until it starts to move in its normal direction. The amount of weight needed to start it moving back toward the outer edge is approximately equal to the amount of extra playing weight needed to compensate for back friction.

Some arms are balanced on blade edge, some on needle point, some "float" in gimbals, some are clamped in ball-bearing races: all have arguments in their favour. All can be adjusted by the user to achieve a point of balance, and with the aid of a simple stylus pressure gauge, the actual force can be measured. To balance, simply ensure horizontal mounting with a spirit level. Then turn the weight adjustment on the arm to zero, disconnect or remove the bias corrector, with the power off, switch to Play and set the lowering device to free the pickup arm. Then adjust the back weight until the arm is just hovering horizontally and can be gently pushed inward from the edge of the disc without seesawing. Clamp the weight, reset the compensator and set the weight adjustment to that recommended for the cartridge in use. When in doubt, err on the *slightly* heavy side: more damage to disc and stylus is done by a light loading, with the high compliance cartridges currently in use, than by over-balancing the playing weight.

Pickup arm raising and lowering devices can now be fitted independently, and there are one or two good ones to choose from. Whatever type is fitted should allow a dropping movement independent of the operator, whose action only "triggers off" the lowering device.

As important as the adjustments for correct weight and forces is the necessity to keep your records scrupulously clean. Dusty and sticky deposits in the disc groove, even the inherent dust that develops when the stylus first plays a new disc, can give much the same symptoms as mistracking—a high frequency distortion. Unfortunately, a damaged record may have the same symptoms. The clue is that increase of playing weight temporarily will cure the "dirt" problem but make no improvement to the gritty sound of a damaged record. The stylus itself can be cleaned with a drop of alcohol, taking care with this as some kinds of cleaner are solvents for the adhesive that secures the jewelled point.

The disc itself can be cleaned with a preener, a dustbug that tracks in front of the stylus, or the use of an antistatic cloth. An antistatic turntable mat is a great help in the exclusion of dust, and careful record storage will complete the necessary precautions. Discs should be in dustproof containers, such as polythene sleeves turned 90 degrees within cardboard sleeves, stacked upright and supported lightly, not flat and under pressure.

## Radio Tuners

From the audio point of view, these can be regarded as a plain signal source, and the guiding parameters are those relating to radio receivers. British Standards B.S.4054:1966 can be used as a criterion, and the American equivalent IHFM-T-100 is all that is needed as a secondary reference. Factors to be regarded are harmonic distortion, signal-to-noise ratio and the rejection figure for exclusion of weaker stations, where f.m. signals are being received. As high fidelity is our

guide word, we shall not regard a.m. tuners as more than an unavoidable extra!

The tuning range should include the specified bands, 87.5–108Mc/s for v.h.f., which includes shipping, police and aero services. Actual broadcasts are confined to 88.1–97.1Mc/s. For a.m. purposes the wavebands to be covered should be Long: 2,000–1,053 metres (150)–285kc/s, Medium: 571–187 metres (525–1,605kc/s) and Short: 50–11.5 metres (6–26Mc/s). There will be units that offer restricted coverage; others that have press-button selection of a limited number of stations. Choice will depend on one's listening tastes. Other factors may be more important than an extended range. If this is the prime factor, then a communications receiver will be more suitable than the average tuner—though very high quality exceptions exist, at a price!

Tuner sensitivity is expressed in microvolts at aerial input to produce the rated output (in the case of f.m. tuners, for the degree of "quieting"), and at a specified signal-to-noise ratio. American standards give a 30dB figure for the latter, and British standards are more exacting at 40dB. For stereo purposes, considerably more sensitivity is required, as we have already seen. Care must be taken when choosing or testing to allow for future development if one is operating in an area still served only by the mono signal. Pilot tone rejection is another factor that can trap the unwary, especially where the aim is tape recording. Additional 19 and 38kc/s filters may prove to be required.

Such filters can affect the frequency response adversely, and this must be taken into account when checking this specification, which is one of the "quality" factors of f.m. tuner performance. In theory it should be possible to obtain a frequency response from zero to well above the audio range, with plus or minus one or two decibel variation over the whole band. In practice, de-emphasis reduces the limits, and pilot tone considerations will further cut down response, so that a figure of 15kc/s may be regarded as adequate.

Automatic frequency control circuits vary between the token and the sophisticated, and testing has to take into account the drift to be expected over a period of use. In some designs it is necessary to render these circuits inoperative while carrying out preliminary alignment.

Because a wide pass-band is used, and peaking of intermediate frequency stages of the f.m. tuner is not possible, there is generally some reluctance to attempt re-alignment. Although this may be advisable unless the circuits are known to be badly out of tune, nevertheless, there is no mystique about f.m. tuner alignment, only the need for greater care. To be absolutely accurate, one should use a wobulator (frequency modulated signal generator) and oscilloscope, but much can be accomplished with an a.m. signal generator covering the appropriate frequency band, a meter, and knowledge of the circuitry.

The usual procedure is to detune the final winding of the i.f. transformer chain, secondary of the pre-detector stage, and connect a meter across the detector load. The exact point of connection depends on the type of discriminator circuit. This can be either a balanced or unbalanced ratio detector or the popular Foster-Seeley configuration. An amplitude limiter circuit will almost certainly precede the detector and care must be taken to keep the generator input as low as possible to avoid limiting and misleading Megger indications—i.e. flattened "peaks". Peaking the i.f. stages too sharply will impair the h.f. response, and some detuning may help if trials are being made.

A good "rough test" of response curve symmetry can be made by slowly swinging the tuning through a fairly strong station, with the a.f.c. disconnected or switched "off". When on tune, the signal should be clear and the indicator at peak; at either side there should be a lower level but undistorted area and then a distorted area, usually quite sharp, where the signal is being rectified on the non-linear portion of the discriminator curve. Asymmetry indicates the need for re-alignment: too small a clear area indicates the need for some detuning or damping.

When aligning the r.f. end of the tuner, always check sensitivity at both ends of the f.m. band. This is a prime failing with some cheap tuners, and little can be done to improve them. The actual transmissions can be used for these tests, provided the i.f. stages have been aligned satisfactorily. Again, some reduction of signal may be needed in areas of high signal strength to avoid the masking of the limiting action, which is one of the fundamental advantages of f.m. reception in excluding amplitude variations, and much interference.

Alignment with "scope and wobulator" is more satisfactory as the response curve can be viewed and the immediate effect of any adjustment can be seen.

## Amplifiers

The audio amplifier is the heart of the system and requires the most stringent testing. Various parameters, specifications, input and output matching and some kinds of distortion have been described.

Frequency response and the overall gain characteristic is the first consideration. Unless the response is flat within specified limits and extends over the audio band, with correct "slope" at the ends of the curve, there is

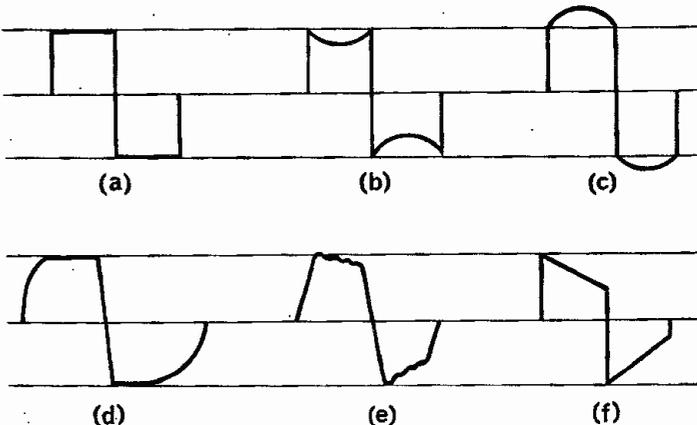


Fig. 4: Square-wave testing of amplifier: (a) square-wave input, (b) low frequency loss, (c) low-frequency boosted, (d) high frequency roll-off, (e) high frequency boosting causes ringing, (f) low-frequency phase shift.

no point in making further tests. But in this respect it must be remembered that we are concerned now with the basic amplifier and not the equalised and corrected preamplifier circuits. As we saw in previous sections, the amplifier must correct for non-linearity in the signal presented to it. We must also be able to test this correction, to ensure that a normal signal from a transducer will come out at the other end as a "flat" output. Tone controls are another matter, and should be treated separately, after the tests for true frequency response are made.

First step is to check the specifications. Although the audio spectrum may be considered to extend from 20c/s to 20kc/s, not all amplifiers have a sensibly flat response as ambitious as this. Some are deliberately

limited in the interests of stability and noise reduction, especially in the case of some less expensive transistorised units.

Frequency response is measured in decibels, giving the relative gain to a standard output for a standard input at a set frequency. This should be stated in the specifications; where it is not, take the rated output as the standard, and the test frequency as 1kc/s, with the specified input as that for the unequalised input of the amplifier—usually the “auxiliary”, “radio”, “diode” or “tuner” input. Tone controls should be in the “flat” position, scratch, rumble and noise filters set so that no compensation is introduced and loudness controls out of circuit. Gain controls are set at maximum for all tests unless otherwise specified.

With stereo amplifiers, balance controls which are intended to have a frequency “roll-off”, should be in the null position for response tests. Remember that balance controls will normally introduce an earlier roll-off at the top end of the frequency spectrum than would be indicated for monophonic amplifiers.

Tests are made with a measured input from an audio generator, the output of the amplifier being monitored by an output meter and, if possible, an oscilloscope across a load resistor equivalent to the rated load of the loudspeaker. The output meter can be a direct reading type of instrument, or a simple a.c. meter whose voltage reading can be converted to power by a normal Ohm’s law formula, i.e.  $\text{Power} = V^2/R$ . The resistor should be non-inductive.

For preliminary tests, the loudspeaker can be left in circuit. A signal is injected to produce a 1-watt output at 1kc/s and the dB reading noted. Further signals may now be injected at spot frequencies over the specified range and variations from the noted standard can be tabulated, or entered on a graph to give a “picture” of the frequency response. Remember, this is a frequency response test and not a power response, so the input level must be adjusted to keep the output below any level which may result in distortion, hence the 1-watt preliminary standard. If in doubt, make a further set of readings to produce a lower output and compare the two sets.

Frequency response should be smooth. Peaks may indicate instability—although some amplifiers have a deliberate peak at around 2kc/s.

Square wave testing, where a suitable signal generator and an oscilloscope are available, is a quick and effective way of revealing the frequency response defects in an amplifier. A theoretical square wave has zero rise time and will look like Fig. 4. In practice, this is never achieved; there must be a finite time from the instant of the rise commencing and the reaching of peak output. Bandwidth limitation accentuates this “slope”. The relationship between the high frequency limit and rise time will be found from the

$$0.35$$

equation:  $f = \frac{0.35}{t_r}$  where  $f$  is the

frequency at which the top end of the band has rolled off by 3dB and

$t_r$  is the rise time. A really good oscilloscope is needed to show the true square wave from a high fidelity amplifier, and its horizontal axis should be calibrated in time. Wide-band d.c. scopes are most useful in this application.

Figure 4 also shows the various distortions of the square wave that will be produced by defects in the amplifier. They may be regarded as clues rather than proofs, and can greatly speed investigations.

We mentioned earlier the need for correct assessment of the equalised preamplifier when testing response curves the equipment as a whole. The principal correction to be noted is that for gramophone cartridge inputs. In these days of high-grade ceramic cartridges, and quite inexpensive magnetic types, it is not at all unusual to find amplifiers with switched correction for different types of curve. The curve shown in Fig. 5 is the RIAA recording curve which is the American standard. If we assume that a record amplifier has been designed to give a signal at the constant-velocity record head, and a uniform signal is applied to this amplifier, with the curve shown, the resulting groove will have constant amplitudes up to 500c/s, limiting the groove swing at low frequencies. Constant-velocity mode is used from 500 to 2120c/s, with the groove swing decreasing as the frequency rises. Above 2120c/s the constant-amplitude mode is again used to allow the high frequencies to overcome record noise.

Use of this recording curve for a constant-velocity cartridge requires a compensating curve as in Fig. 5 in the playback amplifier to produce a level response. To check this, an equipment setup as in Fig. 6 is used. First the output from the signal generator is fed to the “flat” input—the auxiliary socket—and then an attenuated input fed to the phono socket. Both signal and earth return leads are switched to avoid hum loops. With the switch at Aux., feed in a 30c/s input and turn


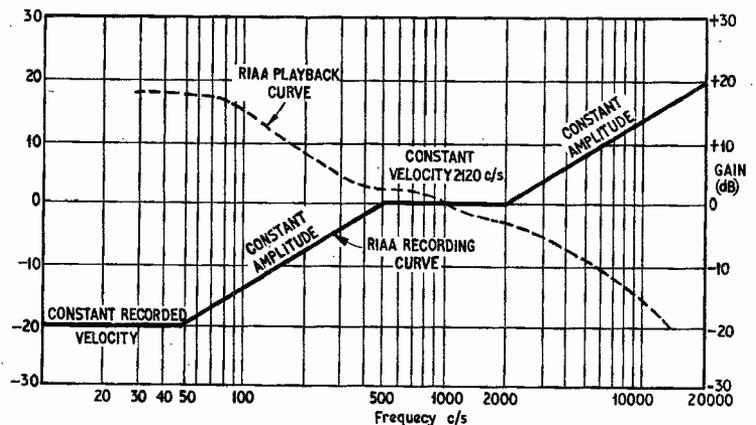


Fig. 5: RIAA recording—playback curve.

Fig. 6: Setup for measuring phase-shift, with an oscilloscope.

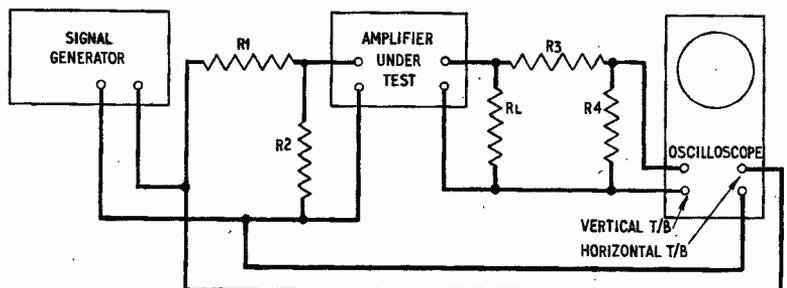

up the gain to distortion point, then back off slightly and note the output meter reading. Feed a 1kc/s signal to the pickup input and set the generator input for an output reading 20dB or so below the previous reading and take this as the 0dB level. Make other measurements relative to this figure. A curve similar to Fig. 5 should be produced.

Constant-amplitude cartridges may be used, and these match, in theory, into the linear input. But the equivalent circuit of such a cartridge is a voltage source in series with a resistor, as we have already seen. Losses at low frequencies are determined by the load resistor. A load impedance of a couple of megohms may be needed to prevent loss of bass. In such cases, a network such as that shown in Fig. 7 may be required to match a constant-amplitude device into a constant velocity, i.e. corrected phono-input. The roll-off of the preamplifier will approximately cancel the high-frequency boost given by the network. At the lower end, the curve equalises the output from the cartridge. The dummy load resistor,  $R_2$ , can be chosen to produce the required output to match the sensitivity of the preamplifier.

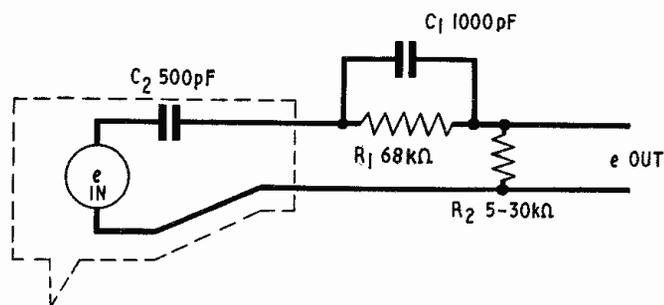


Fig. 7: Matching network for constant amplitude cartridge into pre-amp with constant velocity equalisation.

## Distortion

Measurement of distortion in amplifiers is a highly sophisticated task, requiring quite expensive instruments. But much can be done with normal bench apparatus and a knowledge of the conditions. Regarding first non-linear distortion, such as harmonic and intermodulation distortion, we can sum up the conditions by producing a transfer characteristic for the amplifier, as in Fig. 8. This shows the resultant waveform of two applied sinewaves. In practice, of course, the amplifier seldom handles pure sinewaves, but carries intelligence which is a combination of many sinewaves, with their sum and difference effects. These last are the intermodulation products, and are accentuated by any non-linearity in the amplifier's response. By applying two sinewaves and measuring the intermodulation, some idea of the amplifier linearity is gained. This is a recognised laboratory method.

The effect of harmonic distortion varies as the proportions of the harmonics differ. Harmonics up to and including the sixth are not discordant in small quantities, but above this, especially the 7th, 9th, 11th, 13th, 14th, 17th, 18th and 19th harmonics, severe dissonances occur with even quite small amplitudes of the unwanted frequency. This is why a relationship between bandwidth and distortion is needed, to demonstrate which order of harmonics is causing the distortion. Overall harmonic distortion figures alone can be misleading. For example: with a 15kc/s bandwidth, harmonic distortion of 0.8% will be just noticeable. As much as 1.5% could be tolerated by most people, but 2% or more would probably be objection-

able. If we now restrict the bandwidth of the amplifier to 3.75kc/s, as would be done by a speech/music switch, selecting "speech", the figures alter drastically. Harmonic distortion can rise to 1.2% before it becomes perceptible, is still tolerable well over 5% and only becomes really objectionable at 12% or more. Hence the compression methods employed when relaying telephone conversations.

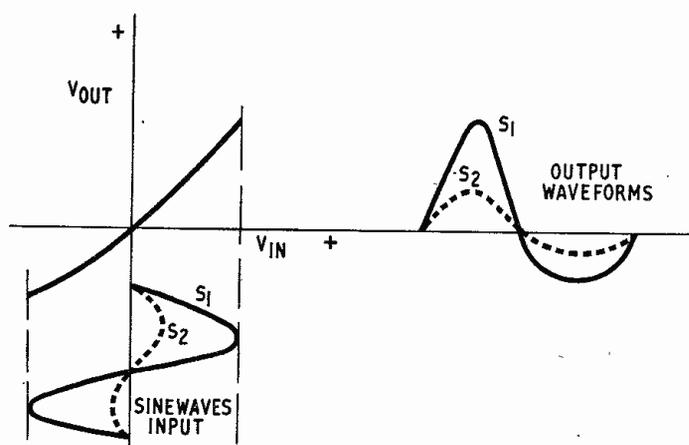


Fig. 8: Transfer characteristic of a typical amplifier, showing effect of intermodulation distortion.

At a point on the bandwidth/distortion relationship curve, intermodulation distortion becomes more unpleasant. This is principally because the intermodulation products are not harmonically related to the original signal. The frequencies produce continuing discords. The ear is itself non-linear and dissonant frequency components produce violent effects on the hearing as volume increases. But volume alone is not the cause of the unpleasantness. A volume whose sound level consists of pure signal plus distortion may be unbearable, but is not so when the distortion is removed and the sound level brought to the same amount as before.

The transfer characteristic of an amplifier will differ in slope and shape at different frequencies. Intermodulation and harmonic distortion although both related to the transfer function, are not directly related to each other and should be measured separately.

In practice we measure the effects of, rather than the amount of, non-linearity. Distortion can be caused by inherent curvature in the characteristics of valves or transistors, non-linearity in transformers, push-pull stage mis-matching (with even harmonic distortion the greater culprit), and crossover distortion, particularly with transistorised Class B push-pull stages where biasing alters due to falling power supplies. Measurements of harmonic and intermodulation distortion can be divided into single signal methods for harmonic and overall distortion and double signal measurements for intermodulation. A distortion meter is necessary to separate signal from distortion without causing misleading results.

There are two approved methods of measuring intermodulation distortion. The argument applied here is that single-frequency tests alone do not reveal a true picture of non-linearity, and a measurement of intermodulation distortion gives a better assessment of the amplifier's performance. The two methods are (a) Comite Consultatif International Telephonique, and (b) the type of test employed by the Society of Motion Picture and Television Engineers. Differing results are obtained, and the method must be stated when specifications are given.

In the CCIF method, two sinewaves of equal ampli-

tude are applied, the frequencies being close together (10 to 20% difference is usual). A peak reading voltmeter monitors output, a low-pass filter rejects the original signals and distortion is read by the second meter. The reading is of peak intermodulation distortion, and omits odd order intermodulation products and some sum components, which are also stopped by the low pass filter. It is therefore most useful for upper frequency band testing. The most important practical precaution is to avoid making the two frequencies so close that the difference frequency is below the frequency response (3dB point) of the amplifier.

Method (b) uses two test tones widely separated in frequency and the amplitude of the low frequency tone is four times that of the high frequency tone. Normally 1kc/s and 10kc/s would be the test tones employed. The band-stop filter (high pass) prevents the low-f tone getting to the measuring meter, while the carrier frequency high-f, is passed to a conventional carrier-level meter, a demodulator and finally a low-pass filter, the resultant amplitude of the demodulated signal being the intermodulation product.

Power output of an amplifier should be stated with regard to other specifications, as we have already discussed at some length. Having determined what the actual power output should be, from the quoted specifications, measurements should be made with suitable test equipment. An undistorted input, sine-wave, squarewave or modulated signal, is fed to the "flat" input and an output voltage across a restrictive load equivalent to the loudspeaker load. Refinements are the oscilloscope to view the waveform and a distortion meter to make a direct reading of the harmonic distortion level. Continuous sinewave power is then calculated simply by dividing the square of the a.c. voltage by the resistance of the load.

As the amplitude of a sinewave varies throughout the cycle, the average value of power output, (because maximum voltage is equal to r.m.s. voltage  $\times \sqrt{2}$ ) will be the square of the r.m.s. voltage divided by the resistance.  $P_{av} = E_{rms}^2/R$ . Similarly, peak power, which would be the output if the amount of power developed at the peak of the sine wave were to be extended through the complete cycle, is twice the average sine-wave power output.

But amplifiers are not designed to deliver sinewave power alone. Indeed, a continuous sinewave of any size through many transistor amplifiers would damage them. Square wave testing may help show up many of the defects, while still enabling a power test to be made. If an audio frequency square-wave is fed to the amplifier and the gain turned up until as near a rectangular shape is displayed on the oscilloscope, then the peak-reading voltmeter connected across the output, the power can be calculated from:  $P_{(peak)} = E_{max}^2/R$ . But as most meters are designed to indicate peak-to-peak voltages, and  $E_{p-p}$  is  $2E_{max}$ , the peak power will then be the square of the peak-to-peak reading divided by four times the load resistance.

Music power measurement assumes no change in power supply voltage with signal level, and tests should include a laboratory type regulated power supply to ensure this condition. The resultant power reading (sine-wave) is the IHF power rating, and will be higher than the original sinewave power. Peak IHF or peak music power is twice the former figure (which explains the need for caution when accepting manufacturers' claims for output power). By the same code, precautions are needed when checking power rating of transformerless transistorised amplifiers, whose power output

increases inversely with the resistance of the output-load. A lower resistance (or lower impedance loudspeaker) than specified should never be used to attempt to get better figures.

Testing amplifier sensitivity is a different matter from checking the power output. We are now concerned with the level of input needed to produce the rated power, which will be the level at a certain percentage of distortion. If there are no definitions of the power rating, we take it that the power figure is this rated output. Thus, a 10-watt amplifier that requires 150mV at 1kc/s, at the auxiliary input to produce 10 watts of output power can be said to have a sensitivity, at that output of 150mV, to measure this, suitable test equipment should be utilised.

With the gain control at maximum and all other controls set for linear amplification, a 1kc/s input is applied and the generator output set so that the rated output appears across the load. Output power is derived from the square of the output voltage reading divided by the load resistance. The input voltage is then the sensitivity. Do not confuse output power with sensitivity. Two dissimilar amplifiers with the same "sensitivity" rating may be deceptively different from that expected. One has to determine what input is needed for the same rated output power, when the lower powered unit may well turn out to be the more sensitive. This can be important when we need to consider the amplifier's safeguard against overload.

Phase distortion is considered very important by some authorities. As an amplifier stage shifts the signal through 180 degrees, the deviation from a linear phase shift will cause non-linearity. All frequency components will not be shifted by the same amount. Some delay is caused by capacitive and inductive elements of the amplifier circuit. This becomes more evident with complex waveforms, and depends on harmonic content.

Other amplifier tests include those for hum and noise, for parasitic oscillation, and for overload. While these figures may not always be specified, the tests for them can be made with the foregoing bench rigs, and by using commonsense interpretations of the measured ratings.

With stereo amplifiers, the separation between the two channels becomes an important rating. There should be as little leakage as possible from one channel to the other, for any input or output condition. The appropriate test equipment should be used, taking care to keep the unmeasured channel correctly loaded, then throwing the change-over switch so that the output on the channel with no input is read—the dB difference between the two output readings being the separation. Always reverse and retest.

## Tape Recorders

Much of the testing previously outlined will apply also to tape recorder amplifiers, with the added problem of recording bias and erase current, which can affect distortion, output level, and residual noise. Some idea of the way in which this occurs is seen from the simplified diagram, Fig. 9. Correct adjustment of bias amplitude, correct frequency, and a good sinewave form are all needed to ensure distortion ratings within the maker's specifications. Erasure should be clean, with residual tape noise again below the dB figure stated, and this will only be gained when the erase current is adequate—all other factors being in order.

The azimuth setting of the record and playback heads is important for good frequency response and

adequate output. Test tapes have been produced with bands of "white noise"—i.e. combination of all frequencies within set portions of the audio spectrum at equal amplitude—which sound like a hiss with a pronounced low level rumble when properly reproduced. By tilting the head for maximum output, the

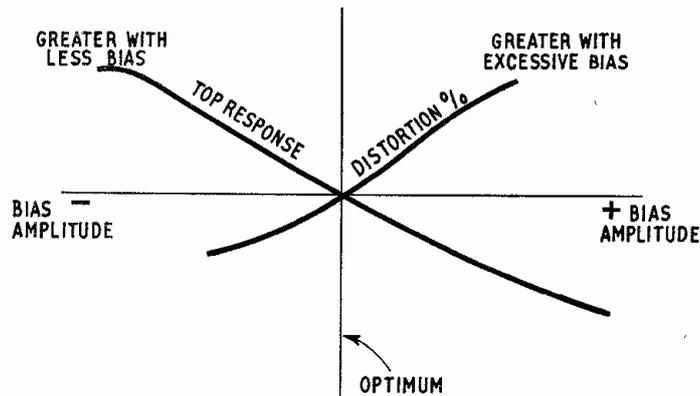


Fig. 9: Bias setting is important for tape recorder adjustment.

correct azimuth can be obtained. Aurally, the rumble aids alignment, and by using a tape with a portion of track erased, height and setting of tape heads can be checked.

As we saw when considering other transducers, the

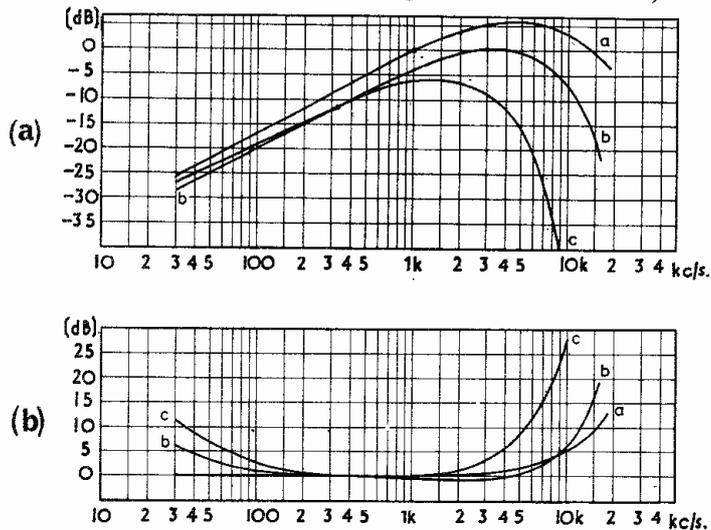


Fig. 10: (a) Frequency response of combined record playback head with 100kc/s bias, recorded with constant a.f. current at 1kc/s, and at three speeds, 19, 9.5, and 4.75cm/s, a, b, c. (b) Recording current boost required with combined heads to obtain the curves of (a).

response of the tape amplifier is not flat. Figure 10 shows the response curves, which are different at different speeds, and (b) shows the recording current boost needed to obtain these curves.

Mechanical considerations enter into matters when we check tape recorders. Unless the mechanism is correct, work on the amplifiers is useless. Regular and accurate speed is vital. Variation from the speed regularity at a low rate (wow) causes an objectionable wobble of the test tone, or the programme, and at a high rate (flutter) a harshness becomes apparent.

Wow and flutter percentages can be derived by making tests with a frequency modulated derivation of the input signal, carefully limited and detected. Special

meters for the purpose are available, and lately a model has appeared on the market at less than £50.

## Loudspeakers

There is little we can do when testing except ensure that the maker's ratings are not despoiled. Principal factor is the efficiency, and Fig. 11 shows a typical graph of relationship between the power input to a loudspeaker and the sound pressure that is actually produced—a concept that has to be grasped before any assessment of loudspeaker quality can be made. Doubling the power to a loudspeaker only increases the sound by 3dB, which is hardly noticeable to the ear—but this also depends on the frequency at which the test is made and the power level at which we commenced—as we demonstrated at the outset of this supplement. It often pays to use a higher efficiency speaker (one with greater flux density) and employ a lower power.

Room acoustics have to be taken into account also, and this again is a subject which exceeds our present terms of reference. Reverberation times differ greatly for different rooms and for different placing of loudspeakers in the rooms, even for different placement of furniture. Room dimensions affect the resonances, and apart from avoiding rooms in which the dimensions coincide, to give marked resonances, there is little we may wish to do structurally.

Table of room dimension ratios (Volkman) for optimum listening conditions:—

Type of room	Height	Width	Length
Small	1	1.25	1.6
Medium	1	1.6	2.5
Large	1	1.25	3.2

It is worth noting that most of the room changes made to aid heat preservation, double-glazing, plaster-board ceiling on builders' insulation board, wood-block floors with part carpeting, clinker or breezeblock walls in place of brick and plasterboard, all improve acoustic

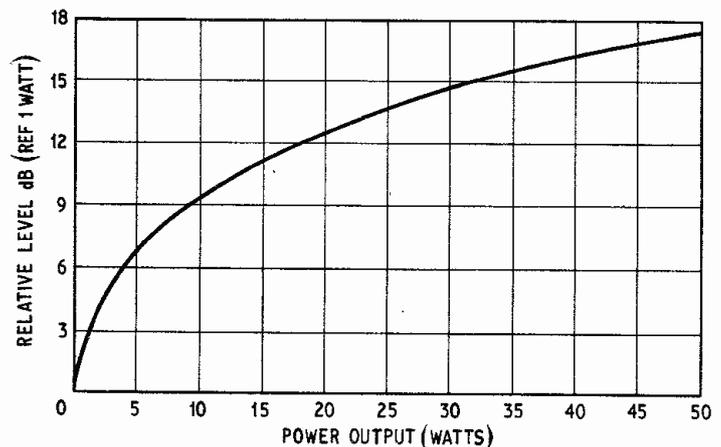


Fig. 11: Loudspeaker efficiency. Graph showing relationship between power input and sound pressure, reference 1 watt.

conditions. But these are incidentals to our present survey; the scope of this audio supplement was intended to aid understanding of audio matters and to facilitate testing. Articles on various aspects of audio will appear from time to time in the main body of the magazine and the supplement can be regarded as a preparation to a better appreciation of these, as well as a source of reference.

# LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents.

## Another Son of Silence...

I have had the same experience as A. Trowbridge—always “instant silence” on trying out each transistor set I make. Decided to make up the transistor tester as described in an earlier issue. Tested the transistors I had used and found that three of them had “gone for a Burton”. Whereupon I felt like going out for a “Johnnie Walker”. The latest of the silent sets is the Reflex Front End for 1.6 to 5Mc/s, but I managed to coax some sound out of it in the way of motor-boating. Perhaps a penny of some sort will drop some day but in the meantime, like Mr. Trowbridge, it's back to valves.—D. Smith (Stockport).

## ... and a Dad

As a “Dad of Constant Silence” how encouraged I was to read Mr. Trowbridge's letter (October). No longer need I feel alone in my shame as we all sit in frozen immobility with breath held while I try to distinguish whether it is a station I hear in the headphones or my hair growing.

I have tried simple circuits—crystal, transistor and one-valve from many sources, including the otherwise incomparable PW, and the only faintly audible signal I ever heard was an intimate mixture of at least two broadcast stations obtained with a 3in. dia-tapped coil, one OA81 and headphones only.

However, I've never tried a large super set and if Mr. Trowbridge is really tiring of his, I'll gladly send him my 3in. home-wound coil in exchange for one of his super sets—and pay the carriage.—D. Hannaford (Brighton).

## Some advice...

Regarding A. Trowbridge's letter may I suggest he perseveres with transistors. After many false starts I finally achieved success on two PW designs for transistors. The first was the single transistor receiver (June '68). Having achieved results on this I decided to try the 300mW transformerless amplifier (June '66). Much to my surprise\* this worked as an excellent straight amplifier using a crystal mike. The next step was to couple the receiver to the amplifier. This was completed successfully and I now have an excellent little receiver. Both units

provided great interest, and excellent experience in my transistor construction.—J. A. Ennis (Saltash). \*Thanks for the back-handed compliment!—Ed.)

## ... and comfort

I am writing to comfort those poor readers who think that they are very unlucky with their equipment. I decided to build a really good portable record player, with 6 watts output, a 10×6in. speaker, and a good deck. The amplifier turned out to be the best audio oscillator I have ever come across. Adjusting the bass, treble and volume controls provided any noise from a motor bike to a VC10. I discovered that this was due to the fact that the whole thing was earthed at the wrong place on the right electrical wire. Why that should matter beats me.

After that, the reputable deck developed a nasty habit of engraving extra grooves on records, at 90 degrees to the existing ones. As if that wasn't enough, the loudspeaker has developed an intolerable “fuzzing” when anything was played through it. Just in case I could replace that, the cabinet warped horribly.

Have I made my point? No? Well, I mended a 30 watt bass amplifier not very long ago, and an output valve exploded (how?) not long afterwards. The amp always did smoke a bit, but exploding!? May be I should take up stamp collecting...—R. Sterry (Reading).

## Subject for discussion

How naïve can a reader be, when he thinks that amateurs ought to concentrate on radio for a subject to talk about on the air? The idea is to communicate, mainly. The most boring operators are those that describe in detail what they did, heard, constructed, etc. But somebody who can cure my warts at 70 miles or so on 80, is the man for me. And a good curry recipe is worth all the agony I suffered in an evening class for the R.A.E.!

“Giggles and squeaks”, how awful. Has R. Meachim ever thought of the Invalid and Bedfast Net and its wonderful work; some of the members even guffaw and laugh out loud. The devils; they should be discussing micro-wave circuits in solemn and porten-

tous voices. As a short-wave listener since 1928 and a licensed amateur since 1964 I advise R. Meachim of London, N.12 to keep off the air, he will only be a bore of the worst kind.—Zach Nichols (Ickenham).

★ ★ ★

In reply to Mr. Meachim's letter (September), I think that he is in the minority of S.W.Ls. when he finds radio amateurs a bunch of irresponsible gigglers. A licensed amateur is at liberty to talk on any subject of which he, or the person or persons with whom he is in contact, has had direct experience, provided that the message is not of a business, advertisement or propaganda nature or on behalf of any social, religious or commercial organisation.

Mr. Meachim states (and quite correctly), that the purpose of a licence is for the self-training and advancement of radio knowledge of the licensee. This somewhat stuffy concept goes back to the days of the early amateurs whose only purpose was to improve radio communication; these were the forerunners of radio today, but now, few amateurs do any original experimenting. Today, an amateur can operate within the terms of his licence, enjoy amateur radio, and advance his knowledge of radio and operating technique very little. Amateur radio is not an apprenticeship to becoming a professional wireless operator; it is a hobby in its own right, and as such does not have to be taken too seriously.

As to the implication that amateurs are irresponsible, all I can say is that Mr. Meachim has not opened his eyes (or ears) to the rest of the world. Most amateurs are courteous and always willing to fit in with others, and they also keep their equipment in good order, well aware of the dangers it could cause to other services. I could hardly see irresponsible people forming such a useful and able body of men as the Radio Amateurs Emergency Network.

On the same page was a letter by a Mr. Curtis attributing a large part of his success in the R.A.E. to listening to “the intelligent discussions on the 80 metre amateur band”. If Mr. Meachim does not like the subjects discussed, he

should remember he has not been asked to listen!—**H. Dearing**, A 5554 RSGB (*Waltham Cross*).

## Polarity poser

I have always understood that the terms Negative and Positive referred to the direction of electron progression but I'm rather puzzled by the marking of those terminals, of either battery or rectifier diode which are connected to the anode load resistors and so to the anodes.

We are assured that the connection at the earth end of the cathode bias resistor is negative, and the other end positive because of the voltage drop across it, that the cathode is negative in respect to the anode, and the anode end of the anode load resistor is negative in respect to the h.t. supply end. A chain of positive to negative connections.

But what happens when we get to the h.t. battery or rectifier diode. We connect the positive end of the load resistor to the positive terminal of the battery and the negative terminal to the negative connection to the cathode resistor. Is this merely a persistence of the old positive-to-negative flow of current?—**H. C. Loxley** (*Warwick*).

## How Solid is Solid?

Mr. Gibbins gave an adequate definition in his letter (PW Oct. 68) of the term solid state as one of the three phases of matter—solid, liquid and gaseous states. But he did not draw the conclusions necessary when the term is applied to electronics.

Most electronic apparatus consist of both active (valves, transistors, etc) and passive (resistors, capacitors, etc.) components. The term "solid state" is applied to an apparatus when the conduction process present in the active devices involves the motion of charge carriers within the solid state of matter (i.e. a transistor). An electronic valve involves the motion of charge carriers in a cloud of other charges—space charge—and this phenomenon is conduction in the gaseous state. A valved equipment could well be called "gaseous state".

I do not at all go along with Mr. Gibbins' deduction that the term solid state is incorrectly applied.

There are doubtless liquid and even gaseous semi-conductors (in the broadest meaning of the word) but those that technology uses in the construction of active devices are exclusively solid state, and thus we can rationally apply the term solid state to electronic equipment.—**P. Goodhart** (*London, W.4.*)

## Re-activating Mercury Cells

The article which appears in the October issue contains a number of inaccuracies. The author states that "cells in good condition give a useful life of two or three days and thus cost 1s. 0d. to 1s. 6d. per day to run". The useful life depends entirely on the current drain placed upon the battery powering the device and a cost per day figure is therefore meaningless.

Some hearing aids using Mallory RM675H cells, with drains of around 0.5mA, will last for more than 300 hours which on a basis of 10 hours per day use will give 30 days of service.

Mr. Stott goes on to state that "many (cells) are not sold in good condition and that their useful life is accordingly shorter". We at Mallory take great pains to ensure our cells are sold in good condition and the useful life of our product is uniformly consistent. With this emphasis on quality the shelf-life of our batteries is at least two years and their condition does not deteriorate during this period.

Later in the article it is stated that "when new, the mercury cell should have a voltage of 1.4V and has a reputed life of 35-40mA". The most popular hearing aid cell—the RM675H—has a capacity of 160mA so that if the current drain is 1mA it will give 160 hours of service, over four times the life quoted by Mr. Stott.

We appreciate the possibility of re-activating hearing aid cells but would like to point out there are many difficulties and dangers in so doing. When a voltage of more than 1.7V is applied to the terminals of a cell, the electrochemical system contained therein will generate gas and there is a strong possibility of explosion. The number of "cycles" possible is also very limited, while this is aggravated by the fact that recharging and even re-activation

is virtually impossible once the cell is discharged to any appreciable extent.—**Dr. A. Gilmour** (*Manager of Engineering, Europe Mallory Batteries Ltd*).


## The Author Replies:

I have had no opportunity to test all hearing aids on the British market. *Which* (January 1968 issue) says the battery life of the fourteen hearing aids tested by them (with one exception) varied from 20 to 90 hours. The exception used secondary cells. There is a wide difference between an average life of 55 hours and Dr. Gilmour's 160 hours.


The Royal National Institute for the Deaf says batteries "last anything from one a day to one a week" (*Hearing Aids* p. 10 Q. 40). At one a day the present costs can amount to 17s. 6d. a week. Only one make seems to claim a battery life of 300 hours, which the makers say is achieved by the use of a special circuit; the price of the hearing aid is greatly enhanced accordingly. The "cost per day" figure may be meaningless to Dr. Gilmour, but it is what matters to the user, and I think in view of the foregoing my estimate of the *practical* cost per day was not unreasonable.

Dr. Gilmour does not say what are the "difficulties" of charging mercury cells. So far as "dangers" are concerned I refer to this twice in my article: in paragraph 11 I point out that the voltage used in commercial "chargers" is 3V. Has he objected to the sale of these chargers which are still being sold at 38s. 6d.? I also point out that the number of cycles is limited (paragraph 14). But even two cycles are worthwhile with mercury cells at 2s. 6d. By implication Dr. Gilmour says that 1.7V may safely be applied to a RM675H type cell. I have never suggested that more than 1.5V should be used; where then is the danger?

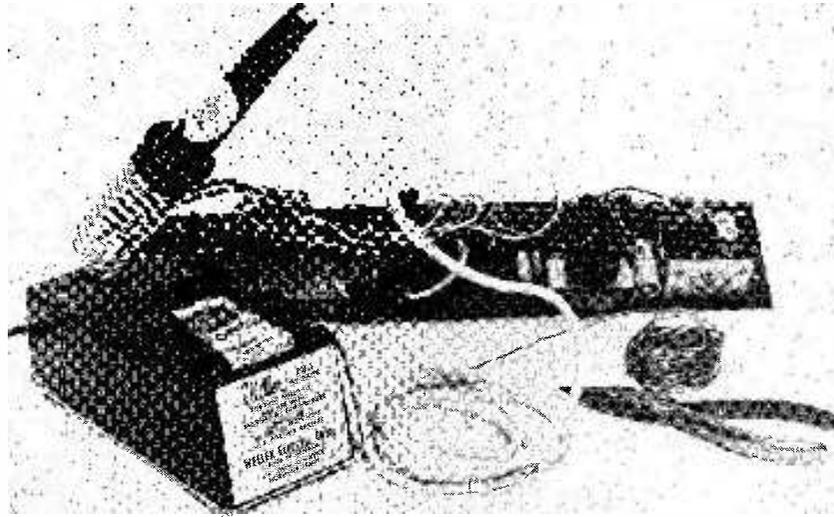So far as accidents are concerned I happen through an oversight to have left six mercury cells in boosters for a period of over three months. The state of the Leclanché cells tested on an ex-WD battery tester (which draws a fairly heavy current) is still "good for all purposes". There is no visible damage to the mercury cells.—**L. B. Stott** (*Lincolnshire*).



## Jack Peters uses a Weller at work

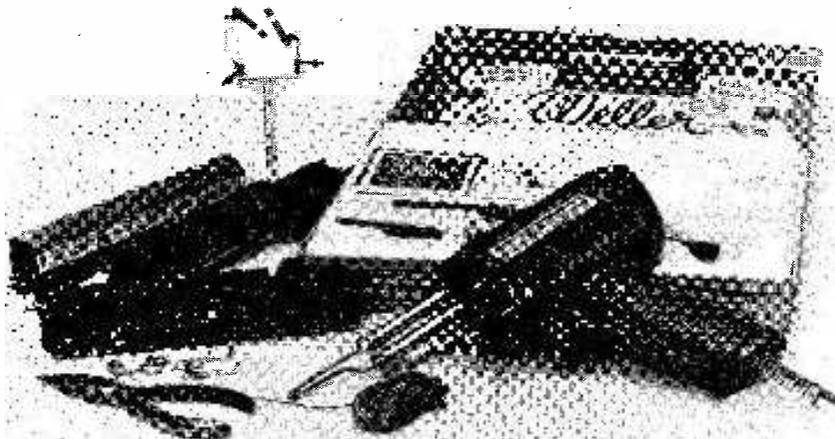

## and at home!

Jack Peters knows the quality and reliability of the Weller soldering equipment he uses during the day—so he naturally chooses Weller for all the soldering jobs around the house. The same technical know-how and perfection go into both.

The world's widest range of quality soldering tools offers:

**TEMPERATURE CONTROLLED IRONS** with iron plated tips which control temperature without limiting

performance. For mains or low voltage.

**RAPID SOLDERING GUNS.** Instant heat models. Just reach for the solder . . . 4 seconds and the job's done.

**LOW INITIAL COST.** The range of Marksman Irons—25, 40, 80, 120 & 175 watt,—all have pretinned nickel plated tips.

There's a Weller soldering tool for every job and every pocket. Send for full details of our range.

# Weller Electric Limited

REDKILN WAY · HORSHAM · SUSSEX. Telephone: 0403 61747

# RADIONIC

LEARN AS YOU BUILD

AT HOME

THE EXCITING WAY

Clear, simple, versatile, this rugged system can build almost any electronic circuit. Ideal for the experimenter; the teacher; and the complete beginner. Already used by well over 1,500 schools in the U.K.

Selected by the Council of Industrial Design for all British Design Centres. Featured in Sound and Television broadcasts.

Beautifully engineered; battery operated; no soldering; no prior knowledge needed. Results guaranteed by our technical department. People say:

- "I can only describe the results as brilliant, absolutely brilliant."
- "You have opened up a new world."
- "Nothing could paint the picture clearer than building these sets."
- "The kit has been used by my son (aged 10) with complete success."
- "Most impressive—a stroke of genius whoever devised it."

**UNIQUE!** Our "No soldering" printed circuit board for superhet portable. Simply insert components and tighten nuts.

- No. 1 Set £7.10.0. 14 Circuits (Earphone)
  - No. 2 Set £9.0.0. 20 Circuits (Earphone)
  - No. 3 Set £13.10.0. 22 Circuits (7" x 4" Loudspeaker Output)
  - No. 4 Set £18.10.0. 26 Circuits (incl. 6-transistor and reflex superhets)
- ELECTRONICS KIT: 30 plus circuits £19.7.0.** (Prices Post Free)


Full details from:

**RADIONIC PRODUCTS LIMITED**


STEPHENSON WAY, THREE BRIDGES  
CRAWLEY, SUSSEX

Tel. CRAWLEY 27028

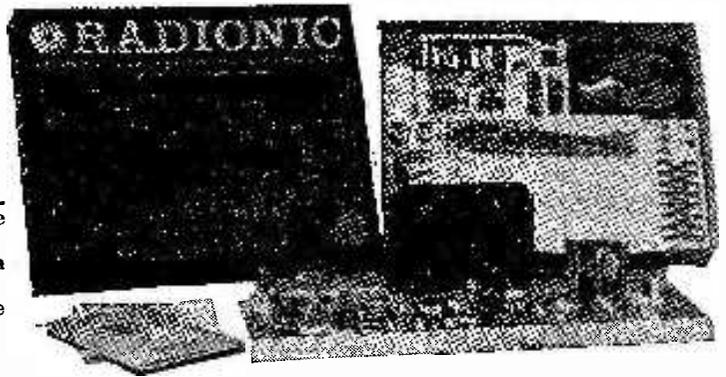
## RADIO & ELECTRONIC INSTRUCTIONAL SYSTEM



A No. 4 SET and 6-TRANSISTOR SUPERHET

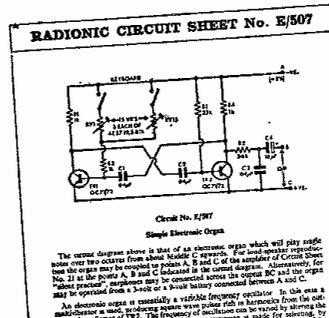

Theoretical Circuit

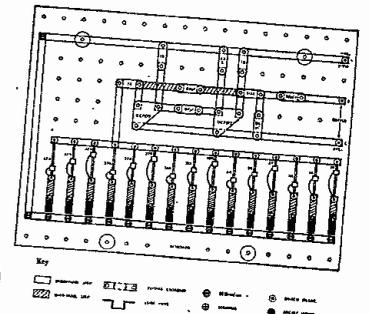

Practical Layout

# FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 132-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio and Electronic Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Appointments Dept. and shows you how to qualify for five years' promotion in one year.

**SATISFACTION OR REFUND OF FEE**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £30 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

- Radio
- Television
- Electronics
- Electrical
- Mechanical
- Civil
- Production
- Automobile
- Aeronautical
- Plastics
- Building
- Draughtsmanship
- B.Sc.
- City & Guilds
- Gen. Cert. of Education
- etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, etc. A.M.I.E.R.E., City & Guilds Radio Amateur's Exam R.T.E.B. Certificate P.M.C. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS

This specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.



### POST COUPON NOW!

■ Please send me your FREE 132-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

■ NAME.....

■ ADDRESS.....

■ .....

■ .....

■ SUBJECT OR EXAM THAT INTERESTS ME..... 344B

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

344B, Aldermaston Court, Aldermaston, Berks.

## THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

# practically wireless

commentary by **HENRY**

IT can hardly have escaped the notice of vigilant readers that the publication date of this issue falls very near that red-letter day of all anarchists, November the Fifth.

Anarchy is very much the fashion nowadays—so who do we want to blow up? No, you can come out from under that table, Mr. Editor. No point in wasting our fireworks. There is already an effigy hanging in the market place: the Postmaster-General, no less.

Mr. Stonehouse has said he is likely to be the last PMG. At the rate of turnover this office has seen of late, perhaps this possibility of a settled administration is to be welcomed. But before we throw our hats (stovepipe?) over the hedges, let us take heed of the implied threat in the turning of a much abused public service into a commercial company.

"We could make four times the profit," boast that famous non-entity, A. Spokesman. That's as may be. Four times the profit simply means, to us, that what we paid indirectly is likely to be extorted directly, by higher prices all round for those services we have come to regard as our right. We have felt the thin end of this wedge already, with the infamous two-tier postal service.

Looked at from any point of view, our postal service can be proved one of the best in the

world. The sheer bulk of deliveries, our modern dependence on paperwork, is what has brought about the need for streamlining the system. It is only logical to attempt a sorting of the wheat from the chaff. More important mail has to be shunted through quickly; less vital fodder can wait. At the same time, some price increase was inevitable. *Ergo*, raise the stamp levy on the faster stream—but what a jumping cracker that idea turned out to be!

The trouble, ironically, was lack of communications. That guy for all seasons, the Public Relations Officer, appears to have smouldered over the presentation rather than bursting it upon a public eager to hear of progress, but reluctant to stomach change! Any good businessman could have explained that the right approach was to offer a faster service at a higher rate, and quash utterly any suggestion of holding back the mails in order to achieve—or maintain—the upper tier.

No wonder one newspaper, in an inspired leader, announced a number of mythical two-tier services, including a new £6 television licence that would enable viewers to see programmes while they were transmitted, whereas the old £5, second-class, licence would allow us to watch the Epilogue at 7 a.m.

Who's joking? In these days of near perfect videotape, we are practically getting canned TV now. About the only programmes that appear "live" are boring discussions that could as easily be slotted into those advertisement spaces the lordly Doctor tries hard not to admit he has toyed with.

As an afterthought—why use postage stamps at all? Now that envelopes are to be standardised, could not they be segregated by colour or shape, or a metallic mar-



*Dependence on paperwork*

ker, to achieve the same object at less capital costs?

Hastily retreating from that bonfire, lest the philatelists ignite it beneath me, let's dial a number or two on the telephone service. To judge from the vitriolic comment in some evening papers, it is nothing but a guessing game with numbers. Those of us who have depended upon it for years, and have seen the services in other countries, will realise that what we already have is getting near the best.

We are not speaking now of the offshoot services: dialling a different pop tune every night and all day Sunday, or asking for recipes that Jimmy Young has overlooked. The telephone service covers a mass of communication engineering that helps keep the wheels of commerce and industry turning. The PCM system alone is a "first" of which Britain can be proud—or will be, when exchanges like the experimental "Empress" on test at Kensington gain a wider public ear.

Henry's damp squib seems to have backfired. I have been praising the PMG with faint damns, which is not what was intended. A glance at recent editorials will show that the radio fraternity—at least, *our* sector of it—has little to thank the stonewalling gentleman and his ilk for.



*Come out from under that table, Mr. Editor.*

# PRACTICAL telephone SYSTEMS

C.H.MOLLER

**O**FTEN the need arises in the house or office for a simple, cheap and efficient means of communication between two points. This could in its simplest form be merely two loudspeakers from old radio sets connected together. Whilst this may be satisfactory in quiet surroundings, more often than not a louder output is required. This can be obtained in one of two ways. An amplifier of some sort may be used, or a carbon microphone and battery driving an earphone.

The tendency in commercial home intercom systems at the moment is to employ a transistor amplifier with two loudspeakers and a press-to-speak switch to change the direction of amplification. The author has experimented with this type of system and found that in certain cases it is undoubtedly preferable, though in the majority of cases it may be very much simpler to use a carbon microphone as is used on large telephone networks.

These can be obtained very cheaply on the surplus market and yet the number of circuits available to the home constructor for using them seems very limited. As a result the author has designed a number of circuits employing surplus equipment which with slight modification to cater for individual needs should fit most applications.

## Using standard handsets

The first system was devised for use over short distances using standard handsets. The constructor can easily make quite attractive stands for the telephone at great saving, as handsets are very much cheaper than complete desk telephones. The range of this system is rather limited because of the use of d.c. signalling. As lamps take a relatively large current the battery voltage will soon become unreasonably high to maintain a reasonable lamp brightness and an alternative method should be used.

Figure 1a shows the basic operating conditions

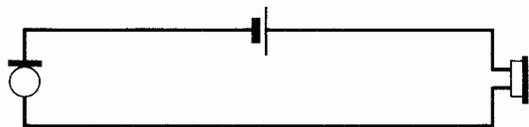


Fig. 1(a): Basic circuit for one-way communication using a carbon microphone and earpiece.

for one-way communication with a carbon microphone and earphone. For a  $1\frac{1}{2}$ V battery the quiescent current should be between 5—25mA depending on the quality of the carbon microphone. The second circuit (Fig. 1b) shows its adaptation for two-way conversation.

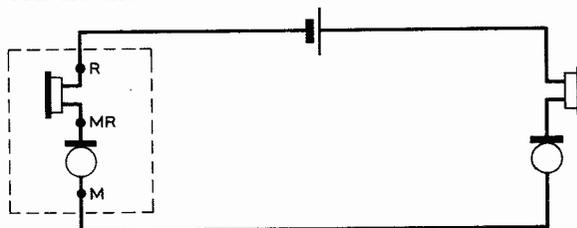


Fig. 1(b): Modification of the circuit shown in Fig. 1(a) for two-way conversation using two handsets. R is receiver connection, M microphone connection, MR common connection.

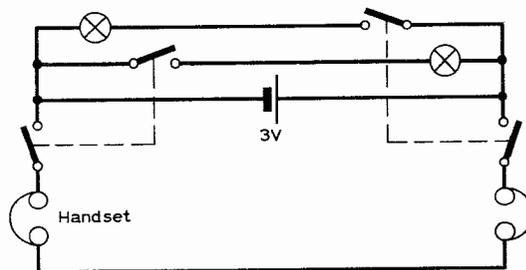


Fig. 2: Practical version of the previous circuit using a lamp calling system operated by switches.

Figure 2 shows a practical application of the circuit incorporating a lamp calling system. If bells are used instead of lamps a break switch will have to be incorporated at each end to silence the bell when the telephone has been answered.

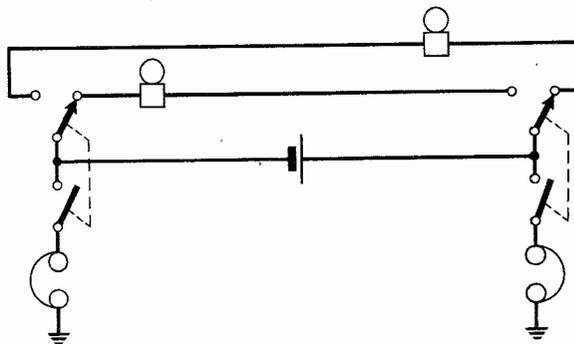


Fig. 3: A further modification, using a bell calling system.

Whilst the circuit of Fig. 3 is primarily designed for only two telephones it is possible to operate it on a "master-and-slave" principle, although if this is desired an automatic selecting system will probably prove more convenient.

## A simple handset stand

A suitable telephone handset stand can be made in about half an hour from a piece of Perspex approximately  $12\frac{1}{2} \times 4 \times \frac{1}{8}$  in. The Perspex should be warmed gently (too rapid warming will result in blistering) over a gas flame or electric heater and

# Ordering Components is **FUN!**



**A bargain  
at 7/6  
plus 3/- p&p.**



**with THIS  
Catalogue  
in your hands!**

Ever had trouble locating a particular piece for your project? Ever wasted time thumbing through confusing price lists? Ever been foot-weary and frustrated tramping round the shops?

Sigh no more. Just sink into an armchair and enjoy life with a Home Radio Catalogue!

Pick your parts. Grab your pen. Make for a letter-box. Your chosen items will be with you almost before you can get back to that armchair!

This Catalogue really is a *must* if you're interested in Radio and Electronics. It has 256 pages, over 7,000 items listed, over 1,300 illustrations. With each catalogue we supply a Book Mark giving Electronic Abbreviations, an Order Form and an Addressed Envelope. All this for only 7/6 plus 3/- post and packing. By the way, every catalogue contains 5 vouchers, each worth 1/- when used as directed. Send the coupon today with your cheque or P.O. for 10/6.

*Please write your Name and Address in block capitals*

Name.....

Address.....

Home Radio (Mitcham) Ltd., Dept. PW, 187 London Rd., Mitcham  
CR4 2YQ

# RADIO COMMUNICATION HANDBOOK

The Fourth Edition of the famous RSGB Amateur Radio Handbook is available at last

This is the LARGEST EDITION yet produced, running to 832 pages, containing dozens of designs for receivers, transmitters, test equipment, V.H.F. gear, aerials and filters. Early chapters cover the theory of radio and design of equipment. The book is well illustrated, and there is even a special fold-out sheet for two particularly large circuits of a receiver and a transceiver. It is a British publication, and therefore all the components specified can be obtained in this country.

A guide to its contents can be gleaned from the chapter titles: Principles, Valves, Semiconductors, H.F. Receivers, V.H.F. Receivers, H.F. Transmitters, V.H.F. Transmitters, Keying and Break-in, Modulation, Single Sideband, RTTY and Frequency Modulation, Propagation, H.F. Aerials, V.H.F. Aerials, Noise, Mobile, Power Supplies, Interference, Measurements, Operating, RSGB and the Radio Amateur.

Price **63s.** plus an extra 6s. to cover the cost of postage and a tough container.

RADIO SOCIETY OF GREAT BRITAIN

Dept. PW, 35 Doughty Street, London, W.C.1.

Fully guaranteed  
Individually packed  
**VALVES**

PERSONAL CALLERS WELCOME

Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.


MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. Orders up to 10/-, 1/-; 10/- to 2/-; over 2/-, 2/- per 1/-; over 23 post free. C.O.D. 4/- extra



ALL valves guaranteed

brand

AC/HL 6/-	ECF82 6/8	KT76 7/-	TP22 5/-	VR105/30 6/-	1C5GT 6/-	3E29 50/-	5U4G 4/6	6AK8 5/9	6F12 4/-	12AT7 4/-	78 5/-
ARF3 3/-	ECH35 11/-	KT88 27/-	TP25 5/-	VR150/30 6/-	1D8GT 6/-	3Q4 3/-	5V4G 7/6	6AL5 7/-	6F13 5/-	12AV6 6/8	80 5/6
ARF12 3/6	ECH42 10/-	KTZ63 7/-	TT11 3/-	VU39 6/-	1G6GT 6/-	3Q5GT 6/-	5X4G 8/6	6AL5W 3/-	6F14 5/-	12AV7 6/8	81 9/-
AR8 5/-	ECH81 8/6	L63 6/-	TT15 55/-	W118 10/-	LLA 2/6	3B4 5/9	5Y3GT 5/6	6AM5 2/6	6F23 14/9	12AU7 4/3	83 14/-
ARTP1 6/-	ECH83 5/6	MH41 3/-	TTB31 45/-	W119 9/-	LLA6 6/-	3V4 6/6	5Y3WGB 6/-	6AM6 3/6	6F32 3/-	12AT7WA 84	84 5/-
ATP4 2/3	ECL80 7/-	MHLD6 7/6	TZ40 60/-	X65 5/-	LLC6 7/-	4D1 4/-	5Y3WGTB 6/8	6AN5 2/6	6F33 20/-	12AX7 5/6	85A2 7/6
AZ31 9/-	ECL82 6/-	ML6 6/-	TZ020 4/-	X66 7/6	LLH4 4/-	5A173G 5/-	6AX5 20/-	6AX5 20/-	6G6G 2/8	12AY7 10/-	282A 100/-
BD78 40/-	ECL86 10/-	N34 3/-	TZ20 16/-	X76M 7/-	LR5 6/-	5A174G 5/-	6AX5W 9/-	6AX5W 9/-	6H6GT 1/8	12AY7 10/-	307A 5/6
BL63 10/-	EF36 3/4	N78 15/-	U12/14 7/-	X118 3/-	LS4 5/-	5B251M40/-	6AS6 6/-	6AS6 6/-	6H6M 3/-	12BA6 6/-	310C 25/-
B2134 16/-	EF37A 8/-	OA2 6/-	U15 9/-	X145 8/-	LS5 4/6	5B251M35/-	6AT6 4/6	6AT6 4/6	6J4WA 12/-	12BB6 5/8	350B 8/-
BT35 55/-	EF39 6/-	OB2 6/-	U25 14/6	Y63 6/8	IT4 3/-	5B251M15/-	6AG7 8/-	6AG7 8/-	6J5 7/-	12BH7 8/8	357A 7/-
BT45 150/-	EF40 9/-	OB3 7/-	U26 14/6	Y65 4/-	2A3 5/-	5B251M40/-	6AG7 8/-	6AG7 8/-	6J5GT 5/8	12C8 3/-	368A 5/-
BT83 35/-	EF41 10/-	OC3 6/-	U27 3/-	Z800U 28/-	2D21 4/6	5B251M35/-	6AG7 8/-	6AG7 8/-	6J5GT 5/8	12E1 17/-	368AS 30/-
CV102 3/-	EF42 10/-	OD3 6/-	U28 4/6	Z801U 25/-	3A4 4/-	5R4WG 27/8	6AH6 10/-	6AH6 10/-	6J6 3/8	12E18 3/-	392A 27/8
CV103 4/-	EF50 4/6	OZ4A 5/-	U29 14/6	Z900T 12/-	3B7 5/-		6AJ7 2/-	6AJ7 2/-	6J6W 6/-	12F7GT 6/8	408C 30/-
CV315 (matched pair) 120/-	EF50 4/6	P41 7/-	U30 14/6	Z901U 12/-	3B7 5/-		6AK5 5/6	6AK5 5/6	6J7G 5/8	12K5M 10/-	446A 8/-
	EF85 6/8	PABOC80 7/6	U31 14/6	LB22 30/-	3D3 3/-		6AK7 6/-	6AK7 6/-	6J7M 8/-	12QGT 6/8	703A 30/-
	EF86 6/8	PC86 10/3	U32 14/6				6AK8 8/-	6AK8 8/-	6K6GT 8/-	12R7GT 4/6	705A 20/-
	EF89 5/6	PC97 9/-	U33 14/6				6K7 6/-	6K7 6/-	6K7GT 4/9	12S67 3/4	715B 60/-
	EF91 3/6	PC90 8/3	U34 14/6				6K7GT 4/9	6K8G 4/9	6K8GT 7/3	12SH7 3/4	717A 3/-
	EF92 2/6	PC84 8/3	U35 14/6				6K8G 4/9	6K8GT 7/3	6K25G 15/-	12SL7GT 7/6	803 30/-
	EF93 2/6	PC89 9/6	U36 14/6				6K8GT 7/3	6K8GT 7/3	MAT100 7/8	12SL7GT 7/6	807 9/-
	EF94 2/6	PC88 8/3	U37 14/6				6K8GT 7/3	6K8GT 7/3	MAT101 8/8	12SL7GT 7/6	808 8/-
	EF95 5/6	PC87 8/3	U38 14/6				6K8GT 7/3	6K8GT 7/3	MAT102 8/8	12SL7GT 7/6	813 75/-
	EF183 7/-	PC82 8/3	U39 14/6				6K8GT 7/3	6K8GT 7/3	MAT103 8/8	12SL7GT 7/6	815 35/-
	EF184 6/-	PC81 8/3	U40 14/6				6K8GT 7/3	6K8GT 7/3	MAT104 8/8	12SL7GT 7/6	829B 50/-
	EF185 6/-	PC80 8/3	U41 14/6				6K8GT 7/3	6K8GT 7/3	MAT105 8/8	12SL7GT 7/6	830B 4/-
	EF186 6/-	PC79 8/3	U42 14/6				6K8GT 7/3	6K8GT 7/3	MAT106 8/8	12SL7GT 7/6	832A 45/-
	EF187 6/-	PC78 8/3	U43 14/6				6K8GT 7/3	6K8GT 7/3	MAT107 8/8	12SL7GT 7/6	843 5/-
	EF188 6/-	PC77 8/3	U44 14/6				6K8GT 7/3	6K8GT 7/3	MAT108 8/8	12SL7GT 7/6	866A 14/-
	EF189 6/-	PC76 8/3	U45 14/6				6K8GT 7/3	6K8GT 7/3	MAT109 8/8	12SL7GT 7/6	884 10/-
	EF190 6/-	PC75 8/3	U46 14/6				6K8GT 7/3	6K8GT 7/3	MAT110 8/8	12SL7GT 7/6	954 4/7
	EF191 6/-	PC74 8/3	U47 14/6				6K8GT 7/3	6K8GT 7/3	MAT111 8/8	12SL7GT 7/6	955 2/6
	EF192 6/-	PC73 8/3	U48 14/6				6K8GT 7/3	6K8GT 7/3	MAT112 8/8	12SL7GT 7/6	956 2/-
	EF193 6/-	PC72 8/3	U49 14/6				6K8GT 7/3	6K8GT 7/3	MAT113 8/8	12SL7GT 7/6	957 5/-
	EF194 6/-	PC71 8/3	U50 14/6				6K8GT 7/3	6K8GT 7/3	MAT114 8/8	12SL7GT 7/6	958A 4/-
	EF195 6/-	PC70 8/3	U51 14/6				6K8GT 7/3	6K8GT 7/3	MAT115 8/8	12SL7GT 7/6	991 6/-
	EF196 6/-	PC69 8/3	U52 14/6				6K8GT 7/3	6K8GT 7/3	MAT116 8/8	12SL7GT 7/6	1622 17/-
	EF197 6/-	PC68 8/3	U53 14/6				6K8GT 7/3	6K8GT 7/3	MAT117 8/8	12SL7GT 7/6	1625 6/-
	EF198 6/-	PC67 8/3	U54 14/6				6K8GT 7/3	6K8GT 7/3	MAT118 8/8	12SL7GT 7/6	1629 4/6
	EF199 6/-	PC66 8/3	U55 14/6				6K8GT 7/3	6K8GT 7/3	MAT119 8/8	12SL7GT 7/6	2051 5/-
	EF200 6/-	PC65 8/3	U56 14/6				6K8GT 7/3	6K8GT 7/3	MAT120 8/8	12SL7GT 7/6	4043C 35/-
	EF201 6/-	PC64 8/3	U57 14/6				6K8GT 7/3	6K8GT 7/3	MAT121 8/8	12SL7GT 7/6	4313C 20/-
	EF202 6/-	PC63 8/3	U58 14/6				6K8GT 7/3	6K8GT 7/3	MAT122 8/8	12SL7GT 7/6	5676 10/-
	EF203 6/-	PC62 8/3	U59 14/6				6K8GT 7/3	6K8GT 7/3	MAT123 8/8	12SL7GT 7/6	5678 10/-
	EF204 6/-	PC61 8/3	U60 14/6				6K8GT 7/3	6K8GT 7/3	MAT124 8/8	12SL7GT 7/6	5696 6/-
	EF205 6/-	PC60 8/3	U61 14/6				6K8GT 7/3	6K8GT 7/3	MAT125 8/8	12SL7GT 7/6	5704 9/-
	EF206 6/-	PC59 8/3	U62 14/6				6K8GT 7/3	6K8GT 7/3	MAT126 8/8	12SL7GT 7/6	5726 7/-
	EF207 6/-	PC58 8/3	U63 14/6				6K8GT 7/3	6K8GT 7/3	MAT127 8/8	12SL7GT 7/6	5933 22/6
	EF208 6/-	PC57 8/3	U64 14/6				6K8GT 7/3	6K8GT 7/3	MAT128 8/8	12SL7GT 7/6	6057 10/-
	EF209 6/-	PC56 8/3	U65 14/6				6K8GT 7/3	6K8GT 7/3	MAT129 8/8	12SL7GT 7/6	6080 5/6
	EF210 6/-	PC55 8/3	U66 14/6				6K8GT 7/3	6K8GT 7/3	MAT130 8/8	12SL7GT 7/6	6084 7/-
	EF211 6/-	PC54 8/3	U67 14/6				6K8GT 7/3	6K8GT 7/3	MAT131 8/8	12SL7GT 7/6	6085 8/-
	EF212 6/-	PC53 8/3	U68 14/6				6K8GT 7/3	6K8GT 7/3	MAT132 8/8	12SL7GT 7/6	6089 27/8
	EF213 6/-	PC52 8/3	U69 14/6				6K8GT 7/3	6K8GT 7/3	MAT133 8/8	12SL7GT 7/6	6146 28/-
	EF214 6/-	PC51 8/3	U70 14/6				6K8GT 7/3	6K8GT 7/3	MAT134 8/8	12SL7GT 7/6	8013A 35/-
	EF215 6/-	PC50 8/3	U71 14/6				6K8GT 7/3	6K8GT 7/3	MAT135 8/8	12SL7GT 7/6	8020 30/-
	EF216 6/-	PC49 8/3	U72 14/6				6K8GT 7/3	6K8GT 7/3	MAT136 8/8	12SL7GT 7/6	9001 3/6
	EF217 6/-	PC48 8/3	U73 14/6				6K8GT 7/3	6K8GT 7/3	MAT137 8/8	12SL7GT 7/6	9002 4/6
	EF218 6/-	PC47 8/3	U74 14/6				6K8GT 7/3	6K8GT 7/3	MAT138 8/8	12SL7GT 7/6	9008 8/6
	EF219 6/-	PC46 8/3	U75 14/6				6K8GT 7/3	6K8GT 7/3	MAT139 8/8	12SL7GT 7/6	9004 2/6
	EF220 6/-	PC45 8/3	U76 14/6				6K8GT 7/3	6K8GT 7/3	MAT140 8/8	12SL7GT 7/6	9006 2/6
	EF221 6/-	PC44 8/3	U77 14/6				6K8GT 7/3	6K8GT 7/3	MAT141 8/8	12SL7GT 7/6	9007 2/6
	EF222 6/-	PC43 8/3	U78 14/6				6K8GT 7/3	6K8GT 7/3	MAT142 8/8	12SL7GT 7/6	9008 2/6
	EF223 6/-	PC42 8/3	U79 14/6				6K8GT 7/3	6K8GT 7/3	MAT143 8/8	12SL7GT 7/6	9009 2/6
	EF224 6/-	PC41 8/3	U80 14/6				6K8GT 7/3	6K8GT 7/3	MAT144 8/8	12SL7GT 7/6	9010 2/6
	EF225 6/-	PC40 8/3	U81 14/6				6K8GT 7/3	6K8GT 7/3	MAT145 8/8	12SL7GT 7/6	9011 2/6
	EF226 6/-	PC39 8/3	U82 14/6				6K8GT 7/3	6K8GT 7/3	MAT146 8/8	12SL7GT 7/6	9012 2/6
	EF227 6/-	PC38 8/3	U83 14/6				6K8GT 7/3	6K8GT 7/3	MAT147 8/8	12SL7GT 7/6	9013 2/6
	EF228 6/-	PC37 8/3	U84 14/6				6K8GT 7/3	6K8GT 7/3	MAT148 8/8	12SL7GT 7/6	9014 2/6
	EF229 6/-	PC36 8/3	U85 14/6				6K8GT 7/3	6K8GT 7/3	MAT149 8/8	12SL7GT 7/6	9015 2/6
	EF230 6/-	PC35 8/3	U86 14/6				6K8GT 7/3	6K8GT 7/3	MAT150 8/8	12SL7GT 7/6	9016 2/6
	EF231 6/-	PC34 8/3	U87 14/6				6K8GT 7/3	6K8GT 7/3	MAT151 8/8	12SL7GT 7/6	9017 2/6
	EF232 6/-	PC33 8/3	U88 14/6				6K8GT 7/3	6K8GT 7/3	MAT152 8/8	12SL7GT 7/6	9018 2/6
	EF233 6/-	PC32 8/3	U89 14/6				6K8GT 7/3	6K8GT 7/3	MAT153 8/8	12SL7GT 7/6	9019 2/6
	EF234 6/-	PC31 8/3	U90 14/6				6K8GT 7/3	6K8GT 7/3	MAT154 8/8	12SL7GT 7/6	9020 2/6
	EF235 6/-	PC30 8/3	U91 14/6				6K8GT 7/3	6K8GT 7/3	MAT155 8/8	12SL7GT 7/6	9021 2/6
	EF236 6/-	PC29 8/3	U92 14/6				6K8GT 7/3	6K8GT 7/3	MAT156 8/8	12SL7GT 7/6	9022 2/6
	EF237 6/-	PC28 8/3	U93 14/6				6K8GT 7/3	6K8GT 7/3	MAT157 8/8	12SL7GT 7/6	9023 2/6
	EF238 6/-	PC27 8/3	U94 14/6				6K8GT 7/3	6K8GT 7/3	MAT158 8/8	12SL7GT 7/6	9024 2/6
	EF239 6/-										

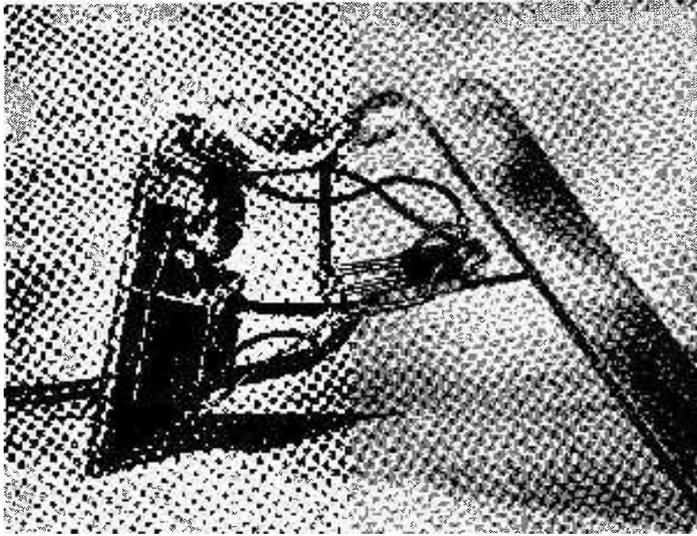

Telephone handset stand made from a sheet of Perspex. The switching follows the circuit shown in Fig. 3.

bent at the lowest temperature possible. It should then be quenched in cold water for at least a minute, maintaining the Perspex in the required position for as long as possible. Drilling should be done after bending, as holes will cause lines of weakness along which the Perspex will tend to bend.

The contacts are obtained directly from GPO type plunger switches. It is necessary to put a small piece of Perspex or Paxolin ( $\frac{1}{2} \times \frac{1}{4} \times \frac{1}{8}$  in.) between the two sets of contacts. Glue this into place. The screw should also be glued on to the top of the top contact. Mount the whole contact assembly on a piece of heavy metal strip spaced from it by another small piece of Perspex. On the prototype units two standard mushroom feet were glued in the instep for the handset to rest on, ensuring rather more silent operation than otherwise.

The finished units have a pleasing appearance despite the visibility of the contacts etc. inside the unit. No doubt however the more inventive constructor could devise a means of producing side pieces for the units. I found it difficult to bend the Perspex with sufficient accuracy to enable a standard template for cutting out the sides to be made, i.e. each side piece had to be made individually.

### High-impedance battery circuit

In general the designing of circuits is much simplified by the use of a completely different basic audio circuit (Fig. 4). In this the battery, which normally has a very low impedance, is made to have a high impedance to audio signals by the choke, whilst still supplying the current to drive the carbon microphones. In practice the choke is often a relay coil which may then be used for signalling purposes as well.

The circuit shown in Fig. 5 utilises both the choke

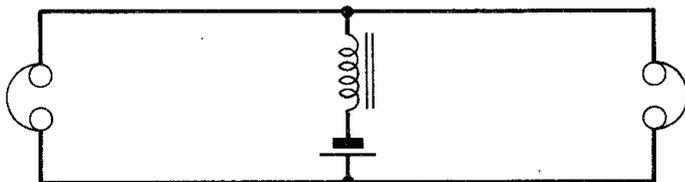


Fig. 4: Basic audio circuit with choke in series with battery.

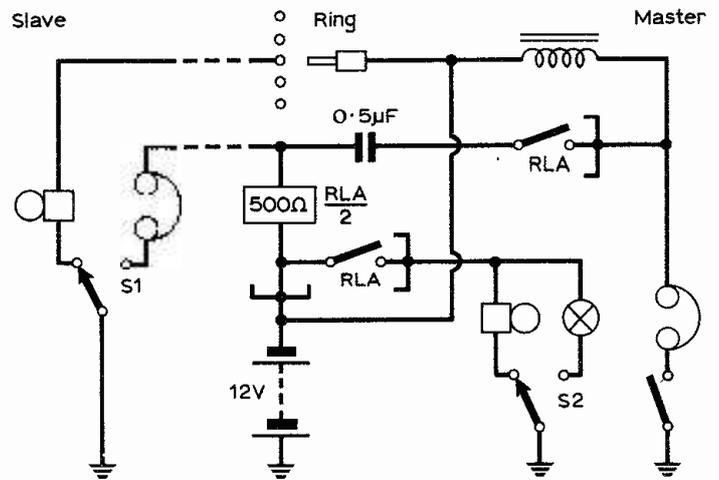


Fig. 5: Practical circuit based on the system shown in Fig. 4 and incorporating a relay ringing system. This arrangement requires an operator or master station.

d.c. circuit principle and a relay ringing system, but requires an operator or master station and only provides for one conversation at a time. Master-to-slave, slave-to-master and slave-to-slave operation are possible.

### Operation of master-slave circuit

When any one of the slave stations operates S1 (this may be either a toggle switch or, preferably, a switch operated by the weight of the telephone handset) the relay RLA associated with that particular station will operate, owing to the d.c. circuit now existing through the handset, and close both the relay contacts. The lower contact provides the current to ring the master bell. When the master answers, i.e. operates S2, his d.c. circuit is made via the choke and the speech circuit is completed through the  $0.5\mu\text{F}$  capacitor. The slave station can then ask the master station to ring the number desired, which is done simply by inserting the calling plug in the appropriate socket. When the other slave station answers the operation is repeated, but as all the speech circuits go to a common point, i.e. the master, there is no need of further connection. When the two sub-stations have finished their conversation the light on the master station will go out, reminding the operator to disconnect the calling signal if he has not already done so.

Because it is very simple this system suffers from a few inherent disadvantages. There is first no privacy in the system at all; that is to say a person at any station is at liberty to lift his receiver and overhear any conversation that happens to be going on at the time. Secondly it only allows for one conversation at a time. Despite this it is a very simple system that is quite reliable and quite cheap to build.

### Using standard desk telephones

The need often arises to provide communication between two points at short notice. Whilst rigging up systems as so far described can be a relatively lengthy business, if two standard desk telephones are available and only two telephones are required the job can be done very quickly.

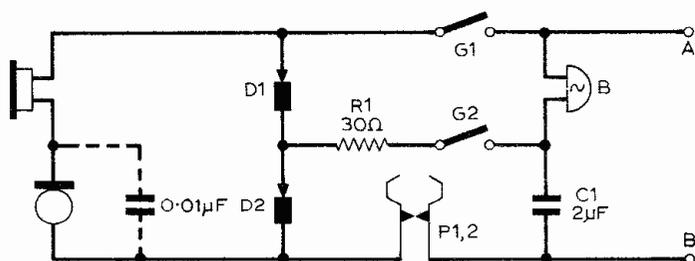


Fig. 6: Basic desk telephone set circuit.

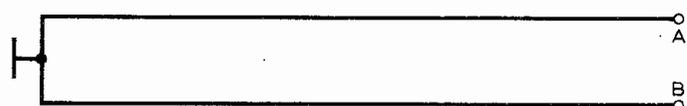


Fig. 7: Shorthand way of showing the circuit of Fig. 6.

The basic circuit of a desk telephone is shown in Fig. 6. Figure 7 shows a shorthand form of this. G1 and G2 are contacts normally open when the handset is on its rest and make when it is removed. D1 and D2 are "off-normal" contacts on the dial assembly and are normally open. As soon as the dial is moved away from its normal position these two contacts make. P1 and P2 are the pulse contacts, which are normally closed but break a number of times on the return of the dial, equal to the number dialled.

## Dialling

When the handset is removed G1 and G2 make. G1 completes a d.c. loop to the exchange via the handset and operates RLA (Fig. 8). (In a large exchange the operation of RLA will probably set off a train of equipment to provide the subscriber with a free line.) The dial is then turned, making D1 and D2, and on the return stroke P1 and P2 break the d.c. circuit the appropriate number of times and release RLA for short pulses. These may be used to operate selecting equipment although in this automatic circuit no dialling is necessary. R1 and C1 act as spark suppression for the pulse contacts; R1 also prevents the magneto bell tinkling during dialling.

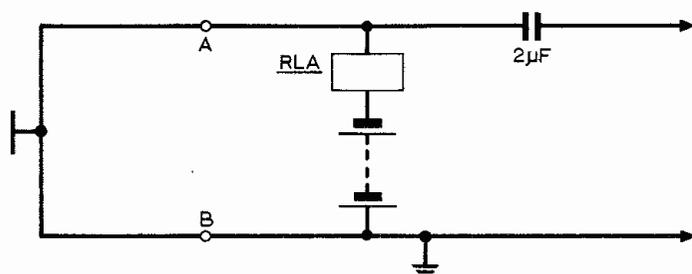


Fig. 8: When the handset is lifted G1 and G2 (Fig. 6) close operating relay RLA at the exchange.

When the other subscriber has been selected an a.c. ringing signal is sent down the line and via C1 operates the magneto bell. This is a bell, usually with two gongs, which rings when fed with about 20V at 15mA a.c. of about 16—50c/s. Normally they are set for 25c/s and will not work well at any other frequency. This can easily be remedied by applying the appropriate ringing signal to A and B and moving the two gongs closer together or farther apart until the point at which most satisfactory operation is found.


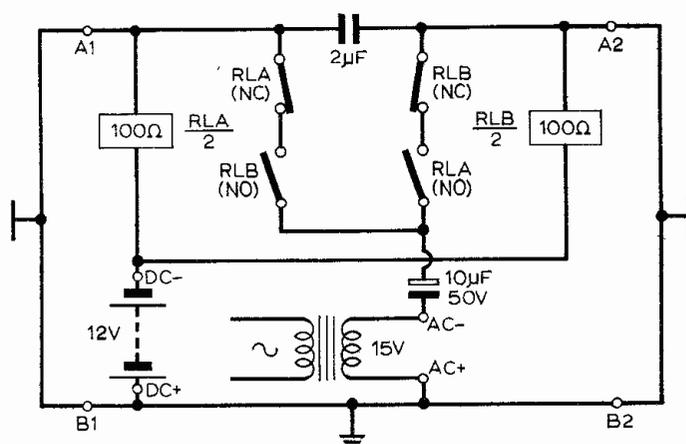


Fig. 9: Circuit for two-way communication using a pair of standard desk telephones.

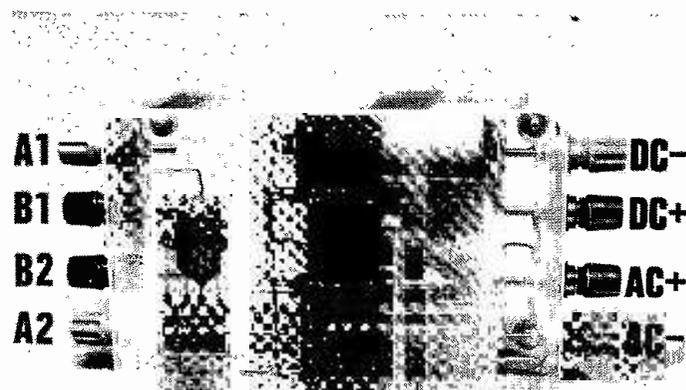

The author's interchange unit incorporating RLA, RLB and the 2µF and 10µF capacitors. The housing is a plastic lunch box.

Many telephones have modifications to the arrangement depicted in Fig. 6. For example some have small transformers to prevent one hearing too much of one's own voice in the earpiece. These coils may be left in providing that this does not cause too severe impedance mismatching with other telephones. If removing the coils, take care! The 30Ω resistor R1 is often carefully concealed in the form of a non-inductive winding in the transformer. If need be this may be satisfactorily replaced by a 33Ω 1W carbon resistor. Also an 0.01µF capacitor may be incorporated in the casing of the 2µF capacitor and will probably be connected across the carbon microphone. This is to prevent long lines from picking up stray r.f. and may be left in.

## Two-way desk telephone circuit

Figure 9 shows the basic arrangement for operating two standard desk telephones. This needs only one wire for each telephone and is fairly independent of the resistance of the wires etc. If required as a field telephone it may be run off a car accumulator and two hand-ringing generators (one at each end). At home it may be run off a train transformer (suitably smoothed) or a bell transformer. Used in this way it can make a very compact and neat unit. The author has had this system working for a long time at home and it has been very satisfactory.

The relays used are the GPO 3000 type, having a 100Ω coil and one make and one break contact. ■

# COMMUNICATION RECEIVER


## TYPE T.R.G.D.X./20.C.

Brand new fully transistorised Communications Receiver. Specifications: 4 complete ranges 550 Kc/s to 30 Mc/s. covering all amateur bands, shipping and trawler bands, and broadcast bands. A highly efficient double tuned superhet, comprising R/F aerial tuning section, A.V.C. and built-in B.F.O. for C.W. or SSB reception. Ideal for fixed or mobile reception. Operates from standard 9 volt battery, provided that its internaly. Gives over 1 watt audio output. With speaker and headphone output. Hammer finished robust steel case of pleasing modern design with all controls on well set-out front panel. Size approx. 9 x 7 x 6 in. British manufacture. Due to huge purchase we can offer these excellent receivers at less than half their normal worth. Complete with handbook £16.10.0. Carr. and ins. 15/-. Headphones if required 17/6 per pair. p. & p. 2/6.

### AERIAL TUNER UNITS

for TX/RX use. Will load almost anything. Calibrated control dial. Housed in compact steel case. Ideal for all radio amateurs and S.W.L.'s. 25/-, p. p. 7/6.

### HEAT LIGHT SPEED CONTROL Unit

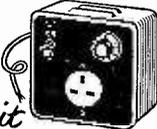

An Electronic unit capable of controlling electrical equipment up to 3,000 watts capacity. Fingertip control of all a.c./d.c. electrical equipment. Suitable for all types of lighting arrangements. Incandescent lamps. Spot lamps. Arc lamps. Floodlights. Makes an ideal dimming unit. Ideal for controlling all types of electric drills and up to 2 h.p. electric motors for all applications. Ideal for all types of electric heaters. Suitable for lathes and power tools. Contains the latest electronic switching devices and associated thyristor circuitry. Size 6 x 5 x 2 in. Louvered metal case in pleasing hammer finish. Attractive front panel with matching socket and controls. Suggested price 25 gns. Huge purchase enables us to offer them at £8.19.6, carriage and insurance 10/-. C.O.D. if required.

### MORSE PRACTICE OSCILLATOR SET

Complete with "Hints on Learning morse" manual. Fully Transistorised. 18/6, p. & p. 3/6.

### TRAWLER TOP BAND RECEIVER KIT

This wonderful little set will provide hours of listening pleasure. Listen to the thrilling sound of an SOS at sea. Super for listening to the Hams at work. A printed circuit layout makes it simple to build in a short time. Fully comprehensive instructions. Employs the latest components and transistors. Complete down to the last detail. An ideal project for beginners. Price 65/- Post 5/-.

### MINIATURE MOVING COIL SPEAKERS

1 1/2 in. diameter. Only 3/6 each, p. & p. 1/6. Two for 3/6 post free. Four for 15/- post free.

### 12V. MULTI-PURPOSE Switching Relay



One of the most versatile relays ever made. Operates from 6 volt or 12 volt A.C. or D.C. Consists of one pair of heavy duty D.P.D.T. contacts which are ideal for switching up to 20 amps. Plus many low current switching contacts. Metal base-plate. Ebonite terminal block. Ideal for aerial changeover units. Car or house burglar alarms, model railways etc. Worth nearly £3 each. Size only 3 x 2 x 2 in. approx. Special price of 17/6 each, p. & p. 2/6. Two for 30/-, post free

### TRANS/RECEIVERS AIR/SEA/RESCUE TYPE

Must be dismantled or exported. Complete with mike/speaker aerial. Work up to 100 miles. Cost Govt. over £40 each. £2.10.0 per set, 10/- P. & P. 2 sets £5, post free.

### LOUDSPEAKER UNIT SALE

Famous manufacture Sin. Moving Coil 10 watt Loudspeakers. In Wooden Cabinets. Not brand new but in good condition. Only 50/- each, p. & p. 10/-. Two speakers for £4.10.0, post free.

### IMPEDANCE MATCHING UNITS

These unique pieces of equipment will match a high impedance output to a low impedance load such as speaker or headphones. Also will match a low impedance output to a high impedance load. Ideal for all types of matching, radios, microphones, pickups, guitars etc. In a compact plastic case. Only 17/6 each, p. & p. 2/6. Two unit for 30/-, post free.

### MINIATURE TRANSISTORISED B.F.O. UNIT

This is a miniature transistorised B.F.O. unit (tunable) that will enable your set to receive C.W. or S.S.B. reception. Compact. Single hole fixing. This small unit will fit anywhere. Ideal for all Ex-Govt. Communication Receivers and most Commercial Types. Complete with fitting instructions. 49/6, post free.

### MOVING COIL HEADPHONES AND MICROPHONES

Brand new in makers' cartons, 25/-, p. & p. 5/-.

### 40 METRE BAND RECEIVER

These excellent receivers were made for the Civil Service. It will cover the complete 40 M. Amateur band, Aircraft, and Marine and other Government Stations. It is a 4 valve superhet and works from standard dry batteries. Built in a robust metal case size 10 x 6 x 4 in. Half moon calibration tuning dial. Phone or speaker output. Not new but in excellent condition. £3.10.0. Carriage 10/-. Few only.

### AIRCRAFT POLICE BAND BROADCAST REC.

Listen to the thrills of Aircraft. Pilots and airports at work also Police, Fire, ambulance, Taxis and Civil Depts. Ideal 2 metre Ham Bands. A fully transistorised receiver covering 97-150 Mc/s V.H.F. broadcasts. Robust louvered steel stove enamelled cabinet of hammer finish. Size 6 x 4 x 4 in. Operates from a 9 volt battery that fits inside. Speaker or headphone output. Simple to use. Worth over £15. Our Price £3.10.0 carriage and insurance 10/-. C.W.O. or C.O.D.

### PARACHUTES

Again we have pulled off another scoop purchase. Brand new parachutes direct from the War Dept. Must have cost over £25 each. Highest quality manufacture. 1ft dia. giving over 100 sq. ft. in area. Complete with cords, etc. Thousands of uses. Over 10,000 already sold. Unobtainable elsewhere at the ridiculous price of 50/- each, p. & p. 10/-. or two for 25/-, post free. Six for £12.10.0, post free. £22.10.0 a dozen, post free.

### 10 HENRY (60 m.a.) SMOOTHING CHOKES

Only 2/6 each, p. & p. 1/- Four for 7/6, p. & p. 1/-.

### HANDY 2WAY TALKIE-PHONE SET

A Two-way Intercom Set. Ideal for all 2-way communication, indoor/outdoor use, home/office use. They will work up to great distances. No G.P.O. licence required. Made to high standard Government specifications. As used by Tank Commanders. The complete set ready to use. nothing more to buy. Batteries supplied. Bargain offer to Practical Wireless Readers. The Set £2.10.0, p. & p. 10/-.

### RUN TELEVISION-LIGHTING DRILLS ETC-ETC from a 12 Volt CAR BATTERY



POWER CONVERTER (De-luxe model). 12 volt D.C. input gives a 240 volt, 300 watt output enabling you to run all your AC/DC equipment and fluorescent lighting. Thousands of uses. Provides a portable Power Supply. Contained in attractive louvered steel case. Complete with leads and clips and full instructions. As supplied to Hospitals and Universities. Recommended price over £30. Our Price £5.19.8, carriage and insurance 15/-. Not to be confused with Heavy Duty Dynamotor units.

### COLLAPSIBLE AERIAL IN 5 SECTIONS

A fully adjustable highly efficient whip aerial. Made to exacting specifications. Copper plated sections. Brass base. An ideal aerial for TX/RX use. Easily adaptable for cars, scooters, walkie talkies etc. Brand new in makers' boxes. Only £1 each, post and packing 2/6. Two aerials for 35/-, post free.

### KHORD

Introducing the range of KHORD audio products we proudly present the "Symphony" loudspeaker unit. This unit is a high class high fidelity economical price. Size 24 x 14 x 10 in. Hand made contemporary veneered teak or light oak cabinet, with matching Vynair front. Incorporating the fabulous Wharfedale drive unit. An 8m speaker with dual cone, roll surround. Freq. response 48-20,000 c/s. Rating 6/10 watts. Ideal for all Hi-Fi arrangements. Price only 11 gns., carriage 17/6. If purchasing 2 units at once £21. Carriage 30/-. We welcome Trade enquiries.

### 3 WATT TRANSISTOR AMPLIFIERS

Operate from a 9 volt battery. Size only 3 x 2 x 1 1/2 in. Highly sensitive. Worth £4.10.0. Our price 55/-, p. & p. 5/-.

### TOP BAND TRANSMITTER

A fully transistorised compact transmitter for Licensed Amateur use. Fully portable. Suitable for mobile use. Fully Tunable 1.8 to 2 mc/s. Contains R/F output meter. Price £12.10.0, carriage 10/-. G.P.O. Licence required.

### HANDY POWER PACK KIT

Consists of Mains Transformer, Silicon Rectifier, Electrolytics, and choke etc. Also Robust chassis and full circuit and instructions. Input 200/250v. AC. Output 250v. 75mA. plus 6.3v. at 2 amps. Only £2/6, p. & p. 7/6. Assembled 32/6 p. & p. 7/6.

### KHORD 15 WATT AMPLIFIER

Hi-Fi Transistorised Amplifier. Inputs for Mic. P.U. Tape. Tuner, etc. Separate Bass and Treble controls. Output for 3 and 15 ohm speakers. Suitable for Microphone, or Guitar, pickup, Gram, Radio, or tape. Freq. response 40-50,000 c.p.s. -3dB Hum Level. Operation from standard AC mains. Size approx 10 x 3 x 5 in. Ideal for P.U. or Hi-Fi. Brand new and ready to use. Another Scoop Purchase. Only £11.10.0, Carriage 15/-. Worth Double.

### SCOOP PURCHASE TRANSFORMER SALE

Build purchase enables us to offer the following transformers at a ridiculously low price. Made by a famous manufacturer and fully tested and guaranteed. CHARACTER TRANSFORMERS. 0-9-15 volts. 2 amp. 9/6 each, p. & p. 2/6. Two for 17/6 post free. TRANSISTOR POWER PACK TYPES. 6.3v at 2 amps. 5/6 each, p.p. 2/-, 12 volt at 2 amp. 12/8 each, p.p. 2/6.

### SHIPPING BAND RECEIVER

Listen to the thrills of an SOS at sea. Hear the worlds shipping at work. Covers the complete maritime and trawler band. Attractive hammer finished case approx. 7 x 5 x 5 in. A neat little superhet. Fully transistorised. 9 volt battery fits inside. Speaker or headphone output. Brand new direct from the makers. Price only £8.10.0 carriage and insurance 10/-.

Callers welcome at this address:

**GLOBE SCIENTIFIC LTD**  
DEPT. P.W.18, 24 CAWOODS YD., MILL STREET, LEEDS, 9.

# Opportunity of a lifetime!

## Big price reductions on top quality knights-kits


Easy to build. Designed to highest specifications. Unbeatable quality and superb performance guaranteed.




**KG980 Solid-State Stereo FM Receiver Kit**  
Silicon transistors. Control facilities for phono and tape. Extra-wide power bandwidth and response. 240V. 50Hz AC. Kit £55. 3. 6. Teak case extra £5. 15. 6. (inc. P.T.) Tuning heart extra £7. 19. 0. (inc. P.T.)



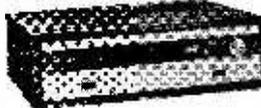**KG765A Solid-State Stereo FM-AM Tuner**  
Frequency response 1dB. 20-20,000 Hz. Hum and noise (7m.) 55dB down. Outstanding in weak signal areas. Kit £34. 14. 2. Teak case extra £5 (inc. P.T.) Tuning heart extra £10. 15. 4. (inc. P.T.)



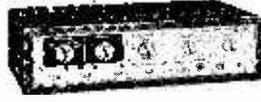**KG795 Stereo Tuner**  
F.M. ± 1dB. 30-15,000 Hz. Hum and noise better than -50dB. Tuning range 88-108 MHz. Channel separation 30dB or more at 1kHz. Kit £34. 14. 2. Teak case extra £5. 7. 6. (inc. P.T.) Tuning heart extra £6. 16. 0. (inc. P.T.)



**KG854 Stereo Amplifier**  
Advanced design. 14 transistors. 2 silicon diodes. Full controls. Response ± 1dB. 20-25,000 Hz. Kit £42. 9. 0. Teak case extra £5 (inc. P.T.)



**KG964 Stereo FM-AM Receiver**  
For the perfectionist. Powerful 64-Watt-1HF Amplifiers. 46 semi-conductors. Full controls. Factory assembled FM Front-end, FM-AM IF Circuits, transformers and coils. Response ± 1dB. 20-20,000 Hz. Hum and noise 55dB. Kit £52. 6. 4. Teak case extra £8. 10. 7. (inc. P.T.) Tuning heart extra £20. 1. 4. (inc. P.T.)



**KG790 Stereo AM-FM Tuner**  
22 Transistors. 14 diodes. Response ± 2dB. 50 Hz to 15 kHz. Hum and noise -60dB. Range 87.5 to 109.5 MHz. Kit £55. 18. 2. Teak case extra £8. 9. 6. (inc. P.T.) Tuning heart extra £20. 1. 4. (inc. P.T.)



**21 Circuit Transistor Lab. Kit**  
Complete with headphones and photocell. Great fun and instructive. Enables you to broadcast through any nearby radio; turn electric equipment on and off just by speaking! Kit £7. 19. 6. (inc. P.T.)



**KG275A CdS Exposure Meter Kit**  
Takes accurate readings even in moonlight. Covers ASA Speed Ratings 6 to 12,000; shutter settings 1/4,000 second to 30 minutes. Cine settings 4 to 128 frames per sec. Incident or reflected light readings. Kit £10. 7. 6. (inc. P.T.) Hard case £2. 8. 3. (inc. P.T.) extra. Soft case £1. 6. 5. (inc. P.T.) extra.

Easy credit facilities available, ask for details.

### 12 Hobbies Sections New 960 page Hobbies Manual - over 12,000 units & components for dozens of Hobbies 16/6

Please send me: Free Knight-Kits brochure   
The new Electronics Hobbies Manual. (16/6)   
Enclosed is a cheque/postal order for 16/6 (which includes the 5/- pp) made payable to Electronics (Prop. STC) Ltd.

Name.....  
Address.....

**knight-kit** Quality built-in, built up by you.

Electronics (Prop. STC) Ltd., PW5, Edinburg Way, Harlow, Essex.



# NEW MART

Dept. No. V8  
30/32, Shudehill 15, Whitechapel  
Manchester 4 Liverpool  
Tel. 061-832 7710 Tel. 051-236 0738

FREE GIFT OFFER OF A BRAND NEW WORLD FAMOUS E.M.I. FISK SOLARISCOPE VALUE £22.0 WITH EVERY ORDER VALUE £5 AND OVER THIS UNIQUE INSTRUMENT WHICH RECORDS SHORT WAVE LISTENERS CLEARLY SHOWS THE AREAS OF DAYLIGHT AND DARKNESS ALL OVER THE EARTH AT ANY GIVEN HOUR

SEND FOR A FABULOUS COLOUR ILLUSTRATED SOUND AND SCIENCE CATALOGUE. 88 PAGES CRAMMED WITH PICTURES AND INFORMATION ON ALL THE LATEST ELECTRONIC AND SCIENTIFIC GADGETS, ACCESSORIES AND EQUIPMENT. ONLY 1/6. P. P. 1/- FULL PRICE OF CAT. CREDITED ON EVERY ORDER OF 30/- & over.

**SYNCHRONISE your TAPE RECORDER** with your **SLIDE PROJECTOR** with an **ORTOSLIDE UNIT**. Fits any tape recorder, 2 or 4 track. Can be fitted in minutes. List Price £8.17.6. Our Price ONLY 59/11 P. P. 2/- Send S.A.E. for Leaflet.

**PICK-UP CARTRIDGE REPLACEMENTS** (for all Record Players) ACOS GP/67-2 MONO 17/6. ACOS GP/73-2 STEREO 30/-, ACOS GP/91-1 MONO-DE-LUXE 21/-, SONOTONE STA CERAMIC STEREO 37/6. SONOTONE 9 TAHC CERAMIC 48/6. COLLEGE SCUI STEREO CRYSTAL 49/11. BSR SXIM STEREO CRYSTAL 48/6. PHILIPS GP316 39/11. MONO and STEREO ACOS GP93 STEREO 45/- P. P. 9d.

**Finest Quality British made MYLAR Recording Tape. Fully Guaranteed. In Cartons.**

3in. 225ft. Message .....	5/6	5 1/2in. 1200ft. Long Play .....	15/6
5in. 600ft. Standard Play .....	10/6	5 1/2in. 1200ft. Double Play .....	15/6
5 1/2in. 850ft. Standard Play .....	13/-	5 1/2in. 1800ft. Double Play .....	23/6
7in. 1200ft. Standard Play .....	16/3	7in. 2400ft. Double Play .....	27/6
5 1/2in. 900ft. Long Play .....	13/3	Leader tape various colours .....	2/-

F. & P. 1/- per reel. Future sales over post paid. Tape splices 17/6 plus P. P. 1/-

**POCKET MULTI-TEST METER.** 1000Ω per volt. Volts 0/10/50/250/500/1000 A.C. and D.C. Current: 0-1-100-500mA. Resistance: 0-100kΩ. Complete with test prods, instructions. 39/6. P. P. 1/6. De-Luxe Model, mirror scale, 49/6 plus P. P. 1/6.

**MULTITESTER**—Pocket size: with built in meter protection. Wide angle, jewelled, meter movement. 20,000 Ω per volt D.C. 10,000 Ω per volt A.C. ● 19 ranges—0.25, 25, 50, 250, 500, 2500 volts D.C. 0.10, 50, 100, 500, 1000 volts A.C. ● 0-50/1A-2.5mA-50mA D.C. 0-5000 Ω-6 megohms. 10µA/0-0.01 mA. ● —30 to +22dB. Mirror Scale. Complete in cloth-lined leather case with carry strap and test leads. Exceptional value at £4.11.6 P. P. 3/6.

**TRANSISTORS:** Some popular types from our range; OC44 and OC45 3/6 each. OC71 2/9. OC72 3/6. OC81 and OC81D 3/- each. OC169 3/9. OC170 3/6. AF117 4/-. OC26 7/6. GETS 5/9. General purpose Approx. OC71 1/- each.

**NEW HIGH FREQUENCY TRANSISTORS.** Similar ST140 4/-; ST141 6/-, both capable of operating up to 700 Mc/s. ALSO MAT100 7/9. MAT101 8/6. MAT120 7/9. MAT121 8/6. AD1140 15/- All transistors post. 6d. up to 3. Over 12 sent P. P. paid.

**BATTERY ELIMINATORS,** replacement for PP9, 29/11 P. P. 2/-; PP8, 19/11 P. P. 1/6.

**MINI-MOTORS** 3V to 4.5V operation. Ideal for mini-racing cars, etc. "Large" (1 1/8 x 7/16 x 1 1/2 in.) 3/11. Medium (1 x 3/8 x 1 1/4 in.) 3/8. P. P. 9d.

**GENUINE DIAMOND STYLUS** at 7/11 plus 6d. P.P. as replacements for the following popular types: BSR TUBS—BSR TUBS STEREO—BSR TUBS LP STEREO—DOLLAR STYDIO (4") LP/SONITE—GARRARD G69 LP—ACOS GP65/67 LP—RONETTE SP401L—GARRARD G69 LP. Sapphire also available at 3/11 each.

**SPEAKERS.** 12in. round high quality British fitted tweeter cone, 6 watts, in 3Ω or 15Ω, 45/-, P.P. 3/6. ROUND 12in. R. & A. 3Ω, 35/-, P.P. 3/6. Many other speakers available. 8in. 3 or 15Ω, 29/6. 10in. 3 or 15Ω, 35/6. 10 watt bass speaker by E.M.I. 12in. x 8in. 15Ω, 39/11. With double tweeter. Very sensitive. 79/11. P. P. 3/6.

**TWEETER.** 2 1/2in. Black plastic cone. Square Frame, E.M.I. 3Ω, 12/6, plus 1/6 P. P. 1/6.

**MICROPHONES LAPEL/HAND MIKE**—1 1/2in. dia. Lapel Clip, ideal for tape recording. Very sensitive. 7/6. P. P. 1/- Similar but stick type AM4, 14/6.

**CRYSTAL HAND MIKE.** Robust and sensitive. Cream plastic case. Just the thing for tape recorders, 8/6. P. P. 1/6. Similar with built-in stand, 10/6.

**STUDIO CRYSTAL MIKE.** Professional, Omni-directional, providing features usually only available at many times the price. Sensitivity—50dB. Response—50-12,000 c.p.s. Black Plastic with punched chromium case, swivels, stand-holder and shielded cable. Only 48/-, P. P. 2/- The stand below fits this mike (as well as many others). ACOS MIC 40—World famous Desk Mike. 18/6 plus P. P. 1/3.

**ACOS MIC 45**—Splendid Curved Hand Grip Crystal Mike, 18/3 plus P. P. 1/6.

**ACOS MIC 60**—"Stick" Type Crystal Mike, 21/3 plus P. P. 1/6.

**ACOS 39-1**—High Quality Stick Mike. High Impedance, 39/- plus P. P. 1/6.

**ACOS ROUND Crystal Mike** insert, 1 1/2in. dia., 7/6. P. P. 6d.

**TELESCOPIC FLOOR STAND HEAVY BASE.** Standard thread, ext. to 4ft. 7in. 49/6. Carriage and Packing 4/6. Desk stand for stick mikes, 7/6.

**SIREN MODULES.** Encapsulated solid state circuit. Only requires 3 Ω speaker, switch and battery (9v.) to complete. Give screaming siren note. Special half price offer. List 25/-, Our price 12/6, p.p. 1/-. Make ideal burglar alarm or warning system.

**INTER-COMMS—DE LUXE TRANSFORMER** PHILIPS "WOKIPHONE" 2-Way With cable. Uses PP5 batt. List Price 6 gns. OUR PRICE 59/11 P. P. 2/-

**AMPLIFIER.** Compact for use in mains portable grams 6 1/2 x 2 1/2 x 5 1/2 in., vol. and tone controls attached by fly leads, over 2 watts output, 59/6. P. P. 4/6.

**4 TRANSISTOR 3W AMPLIFIER.** Size 2 1/2 x 2 1/2 x 1 1/2 in., 3, 8 or 15Ω output, 9 volt battery operated. Highly sensitive. Price (less battery) 52/6. P. P. 1/6.

**NEW MODEL FIELD STRENGTH METER.** Range 1 to 200 mV, 23 P. P. 2/-

**NEW MODEL HI-FI 3-WAY VALVE CROSSOVER NETWORK.** 63/- P. P. 2/-

**LATEST MODEL RESISTANCE SUBSTITUTION BOX.** From 15Ω to 10,000 Ω low range. 15kΩ to 10MΩ high range. £2 P. P. 2/- (with leads)

**HI-FI TWEETER** 15 Ω 10 watts Mod. CT10. Spec. 1,500 Ω, 16,000 c/s sensitivity 104dB. 31/6. P. P. 2/-

**CAR REAR SEAT AUTO SPEAKER KIT** with wire and switched junction box. For instant select. P. P. 3. or both. Suitable for all cars. 22/6. P. P. 3/6

**CAPACITANCE SUBSTITUTION BOX.** Range from .0001 mfd to 22 mfd, complete with leads. 25/-, P. P. 2/-

**ALL PURPOSE TEST LEAD KIT** for the radio amateur, with leads, test prods, spare terminals and croc clips. 12/6. P. P. 1/6.

**ARET DYNAMIC MICROPHONE DM155** 50k imp. black crackle finish, with wind-shield. Very robust, ideal for outside use. £13.5. P. P. 3/6

**GUITAR CONTACT MICROPHONE** clips into instrument output. 12/6. P. P. 1/6.

**HI-FI STEREO HEADPHONE** 15 Ω impedance. For hi-fi amplifiers and tape recorder monitoring. Complete with leads and stereo jack plug £4.15.0. P. P. 4/6.

**VERNIER DIALS.** Universal mounting for standard 1/2 in. drives, 2in. diam. x 1in deep, 10/6. 2 1/2 in. diam. x 1 1/2 in., 13/-, P. P. 1/6.

TERMS. Cash with order. No C.O.D. Order total £5 and over sent carriage paid (excepting record player decks where carriage is shown). Guaranteed money refunded if goods returned perfect within 7 days of despatch.

# ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times GMT  
Frequencies in kc/s

## THE BROADCAST BANDS by CHRISTOPHER DANPURE

**W**ELL, the cold winter days are with us again, and here are this month's propagation predictions for the main circuits to the U.K.

**West Africa:** 0800-1400 25, 21, 17 and 15Mc/s; 1400-1600 25, 21, 17, 15 and 11Mc/s; 1600-1800 25, 21, 17, 15, 11 and 9Mc/s; 1800-2000 21, 17, 15, 11, 9, 7, 6, 5 and 4Mc/s; 2000-2200 17, 15, 11, 9, 7, 6, 5 and 4Mc/s; 2200-2400 15, 11, 9, 7, 6, 5, 4 and 3Mc/s; 2400-0600 11, 9, 7, 6, 5, 4 and 3Mc/s; 0600-0800 15, 11, 9 and 7Mc/s.

**South Africa:** 0800-1400 25, 21 and 17Mc/s; 1400-1600 25, 21, 17 and 15Mc/s; 1600-1800 25, 21, 17, 15 and 11Mc/s; 1800-2000 21, 17, 15, 11, 9, 7 and 6Mc/s; 2000-2200 17, 15, 11, 9, 7, 6 and 5Mc/s; 2200-0200 15, 11, 9, 7, 6 and 5Mc/s; 0200-0400 11, 9, 7 and 6Mc/s; 0400-0600 11 and 9Mc/s; 0600-0800 15Mc/s only.

**East Africa:** 0800-1400 25, 21, 17 and 15Mc/s; 1400-1600 25, 21, 17, 15, 11 and 9Mc/s; 1600-1800 21, 17, 15, 11, 9, 7 and 6Mc/s; 1800-2000 17, 15, 11, 9, 7, 6 and 5Mc/s; 2000-0200 11, 9, 7, 6 and 5Mc/s; 0200-0400 11, 9, 7 and 6Mc/s; 0400-0600 11 and 9Mc/s; 0600-0800 21, 17 and 15Mc/s.

**South Asia:** 0600-1000 25, 21, 17 and 15Mc/s; 1000-1200 25, 21, 17, 15 and 11Mc/s; 1200-1400 25, 21, 17, 15, 11 and 9Mc/s; 1400-1600 21, 17, 15, 11, 9, 7, 6, 5, 4 and 3Mc/s; 1600-1800 15, 11, 9, 7, 6, 5, 4 and 3Mc/s; 1800-2000 11, 9, 7, 6, 5, 4 and 3Mc/s; 2000-2200 11, 9, 7, 6, 5 and 4Mc/s; 2200-0200 9, 7, 6, 5 and 4Mc/s; 0200-0400 9, 7, 6 and 5Mc/s; 0400-0600 11 and 9Mc/s.

**South East Asia:** 0600-1200 25, 21, 17 and 15Mc/s; 1200-1400 25, 21, 17, 15, 11 and 9Mc/s; 1400-1600 25, 21, 17, 15, 11, 9, 7, 6, 5 and 4Mc/s; 1600-1800 17, 15, 11, 9, 7, 6, 5 and 4Mc/s; 1800-2000 11, 9, 7, 6, 5 and 4Mc/s; 2000-2200 11, 9, 7, 6 and 5Mc/s; 2200-2400 11, 9, 7 and 6Mc/s; 2400-0400 9Mc/s only; 0400-0600 weak signals on 9Mc/s.

**North East Asia:** 0800-1100 25, 21, 17, 15 and 11Mc/s; 1100-1200 17, 15 and 11Mc/s; 1200-0200 11 and 9Mc/s; 0200-0600 11Mc/s only; 0600-0800 15 and 11Mc/s.

**Australia (via Asia):** 0600-0800 21Mc/s only; 0800-1000 25, 21 and 17Mc/s; 1000-1200 21, 17 and 15Mc/s; 1200-1400 21, 17, 15, 11 and 9Mc/s; 1400-1600 17, 15, 11, 9, 7, 6, 5 and 4Mc/s; 1600-1800 15, 11, 9, 7, 6, 5 and 4Mc/s; 1800-2000 11, 9, 7 and 6Mc/s; 2000-2200 9Mc/s only; 2200-0600 circuit closed.

**West Coast of South America (North of Chile):** 1200-1400 25, 21 and 17Mc/s; 1400-1800 25 and 21Mc/s; 1800-2000 25, 21 and 17Mc/s; 2000-2200 17 and 15Mc/s; 2200-2400 15 and 11Mc/s; 2400-1000 11 and 9Mc/s.

### HAPPY EVENT!

On November 18th, the "Happy Station" programme of *Radio Nederland* celebrates 40 years of short wave bands broadcasting. This programme is today still

produced and presented every Sunday by Edward Startz and is believed to be the longest running short wave radio programme.

The secret of its popularity is that it keeps politics out of the programme, and just plays music for all tastes, and at the end of each programme there is a mailbag with answers to listeners' letters. On November 17th there is a special anniversary programme, so be sure to listen, as there is a special QSL card for the 40 years' celebration, and also a special leaflet has been issued telling in brief about the history of the Happy Station programme.

You can hear the Happy Station every Sunday in the British Isles and Western Europe at the following times, 1030-1150 GMT on 11,730 or 9,715, 6,020 and 5,980 and from 1430-1550 GMT on 6,020.

Now on to this month's DX-tips.

### EUROPE

**Sweden:** Starting November 3rd, *Radio Sweden* transmits its morning programmes to Europe from 0930 onwards on 6,065, English is at 1100-1130.

**Switzerland:** The evening programme to the British Isles from the Swiss Shortwave Service, Berne, is now heard on 9,665 and 6,015 from 1930-2030.

### AUSTRALASIA

**Papua:** *Radio Milne Bay* with 250 watts is now on 3,235 in English and Pidgin from 0700-1200 and 1700-2000.

### AFRICA

**Angola:** *Emissora Oficial*, Luanda, now operates on 4,820 with 100kW from 0500-0745 and 1855-2400, on Sunday mornings does not close until 0200.

**Somali Rep:** *R. Somali*, Hargeisa, now operates on the new frequency of 11,675, heard recently around 1500.

### CARIBBEAN AREA

**Haiti:** *Radiodiffusion Haitienne* has been heard on a new frequency of 5,075 at 2330.

### SOUTH AMERICA

**Chile:** *La Voz de Chile*, Santiago, has been heard on 6,150 in parallel with 9,690 at 0400.

**Uruguay:** *Radio Oficial*, SODRE, has been heard again on 15,272, transmits daily from 1130-0230.

Many thanks for tips this month to Sweden calling DX-ers. Deadline this month is **November 10th, 73.**

**T**HE autumn has arrived—thank goodness. With any luck the summer doldrums should leave us and the bands can get cracking.

Twenty metres has, of course, proved its worth being almost a 24 hour band. Early mornings are the time to catch Pacific DX—VK and ZL, with the smaller islands coming in quite consistently, VR6 and KH6, KB6 etc.

Top band, after faithful service as a favourite talk-in band for summer mobiles, can now get down to the more serious business of the winter transatlantics. You'll need to be able to read c.w. for these but the call signs are usually sent very slowly—5 w.p.m. Listen around band edge from 1-800 to 1-805kc/s for W and/or K stations

Ten metres, definitely the biggest disappointment, has stirred a little. Openings to Africa have appeared and even a South American path opened up on a couple of occasions. There are a number of local G nets on ten, so it might be worth a listen to keep up to date with local Ham news. Leicester has such a net and, so I hear, does Hatfield in Hertfordshire.

No news of any exotic expeditions have come in. **J. Moore** (Leicester) queries LG5LG heard in QSO with FOJH. He called himself "Ernie" and claimed to be at a children's home in a "small Scandinavian state" (probably Earls Court!).

**K. Proctor** (Yorks.) says that for anyone with time and patience to spare, he recommends 40 metres. The DX is certainly there, as I've mentioned before, and the band should improve now the colder weather is here.

## LOGS

**Ken**, G8APJ (E.10) noted my remarks *re* two metres and promptly sent in a log. He doesn't specify the gear or the antenna but it should be pretty good judging by the log—DL0ER, F5NS, F9FT, F9NL, GW5BI, GW8UM, ON4RY, PA0AFG, PA0CML, PA0VVH. Ken tells of G3PFM hearing an EA3 on the band.

**M. Pasek** (Notts.), QP166 into an HRO, wire "X" beam for 7Mc/s logged this bunch on 40 between 0600 and 0730, all s.s.b.—CM2DC, CO2FA, HK6BMS, PY1CLI, VK2AGW, WK2BKL, VK3-AHT, VK3XM, ZL1AGD, ZL1AQ, ZL2AAG, ZL3DD, 8P6AN(c.w.). On 80, his best were—ZL2BCG and ZL3RK, both s.s.b.

**K. Proctor** (Yorks.), HA500 plus pre-selector, 20ft. base—loaded vertical (homebrew) plus a.t.u. winkled out these on 40 s.s.b.—CT1GD, CT2AP, CE3DM, CN8AW, EA3JE, ET3USA, HB9AIW, I1IJ/P—IP1 (zone 33) OX3DX, PY7LAV, TL8BD (at 5 and 9 plus 15dB), VK3OZ, VP2KF, YV4QB, YV5CIL, ZC4MO, ZS1JA, 3A2MJC, 4X4TB, 5A5XO (a.m.), 4U1ITU, 8P6BH, 9M2DQ, 9Q5EP, 9Y4KR, 9Y4TO. A very f.b. log and certainly beats my best on 40. Any other braves like to have a go?

## 20, 15 and 10

The old favourites, 15 and 20, have supplied a steady stream of DX for the past few months.

**J. Moore** (Leicester), CR100/2 plus 60ft. end fed, says his station cost him about £14, so listening in on 14Mc/s makes it a quid-a-meg? Pickings from the s.s.b. log—CE3FI, EP2DA, FOHI/FC/M, HB0LL, HB0AAI, G3ODO/KL7, HC4WM, HS3HB, JA2BTV, JX1DM (Jan Meyen—I hope!), K1FNA/KG6, KH6BX, KL7GCK, KP4AST, PY2BNQ, TG9AG, VE3EQK, VE4CN, VK2LT, VK2APP, VK3BM, VK4DO, VK5WO, VK7RX, VQ8CS (Mauritius), VR6TC, ZL2AAG, ZL4BX, 3V8AA, 4A1FFC, 4X4YL.

**S. Mummery** (Bromley) has attained the ripe old age of 13. He roams 20 metres with a B34 and a 66ft. end fed. Not content with this he logs stations to wit—CR4AJ, CT1TU, EA4DO, EI7AY, HB0LL, IP1OK, KH6BX, KZ5TI, LX1SL, TF2WKP, VK2AFN, VK3AOF, VK3AOV/P, VK4GY, VK5XW, VK7SM, VP9MI, VR6TS, VS9MB, ZB2AY, ZL1DAS, ZL2ABY, ZL3DO, 4U1ITU, 4X4YP, 5A3IJ.

**P. Baker** (S. Wales), HE30, 150ft. long wire, shovelled up a nice haul on 15 metres—CE1DF, CE0AE, CO2FM, CP6HI, CR4BC, CR5SP, CR9AK, CT2AV, DUIFH, EA9AQ, EL2B, EP3AM, HB0AAI, HK2RB, HK0BKX (San Andres) HL9KW, HP1CT, HR6EB, HV3SJ, KA1IJ, KG4AM, KH6BX, KP4BCL, KR6KN, KV4DB, LU1DAB, MP4MBC, OA4NG, OX3DX, PX1YY, SV0WN, TJ1AL, TU2BQ, VK2AGW, VE7LB, G3UHR/VO2, VK9DS, VP2DAJ, VP8JH (South Orkneys), VQ9DH (Seychelles Islands), VR1L, VR2CC, VR6TC, VS5AT (Brunei), VS6DR, VS9MB (Maldives), VU2DKZ, XW8AX, YS1XEE, ZD3D, ZD5V, ZD8Z, ZE1CS, ZP5KN, 3V8AA, 4A1WF, 5A1TG, 5H3JL, 5N2ABF, 5Z4LG, 6W8AL, 7Q7AM, 8P6CC, K0BAC/8P6, 8R1P, 9G1DM, 9J2BC, 9K2BC, 9M2DQ, 9Y4GS, 9V1NY. You should have seen his log for twenty!

**W. Thomas** (Worcester) sends in the best 10 metre log. Yes, there are signals there. Bill used a BC348 with an RF24 plus 50ft. end fed to hook—CR6KI, OD5CS, ZE1CB, XE2JA, ZS1JA, 9G1FL, all on a.m. On s.s.b.—CR6JI, CR7IC, CX8DM, ET3USA, HS1AF, KV4AD, KZ5AO, LU3DTV, LU7CK, VP8JC, ZD7DI, ZD9BE, ZS2LM, ZS5LB, ZS6BCI, 4A1WS, 5Z4AA, 7Q7WW, 9J2BK, 9K2BV. If you didn't do quite so well on ten don't worry—I listened at just the wrong times too.

## CONTESTS

Six contests chalked up on my shack wall. November 9th—10th, R.S.G.B. 7Mc/s DX Phone Contest; 9th—11th, ARRL SSB Phone Contest; 16th—17th, second 1-8Mc/s Contest; 16th—18th, ARRL SS Contest (c.w.); 23rd—24th, CQ WW DX Contest (c.w.); December 1st, fourth 70Mc/s c.w. contest.

Please drop me a line if you hear anything of interest. Deadline this month is the 18th.

**NEW—FIELDMASTER CASSETTE TYPE TUNER PACK.**

The best of its type! Uses 4 top grade transistors.



Fits in place of tape cassette and converts recorder to radio reception. Covers full medium wave, battery operated. Highly sensitive circuit. £4.19.6. P. & P. 2/6.

**FEW ONLY—MAGNAVOX 4 TRACK TAPE DECKS** £16.19.6. Carr. 12/6.

**NEW—ADASTRA "DOUBLE 5" STEREO AMPLIFIER.**


10 transistor circuit. Volume, Treble, Bass, On and Off Balance controls. Inputs for magnetic and ceramic cartridges, tuner and microphone. Output 5 watts per channel. Complete with operating booklet. £12.19.6. P. & P. 4/6.

**"ADASTRETTA" 2/3 watt Record Player Amplifier.** EC182 and E280 valves. Output imp 3/5 ohms. Easy to fit into cabinet. Separate control panel with on/off, volume and tone controls. Complete with instructions £4.7.6. P. & P. 4/6.

**NEW—7 TRANSISTOR RADIO KIT.** Complete kit with all parts and easy to follow instruction book. Covers full medium wave. Speaker and earpiece. Attractive case 7 1/2 x 2 1/2 x 1 1/2 in. with carrying strap. 79/6. P. & P. 3/6.

**SHIRA 6SD MULTI-TESTER 20,000 o.p.v.** DC Voltage: 5-250 0.5-2500-5000-25K (20,000 ohms per Volt). AC Voltage: 10-50-100-500-1000 Volts (10,000 ohms per Volt). DC Current: 0-50A, 0-2-5mA, 0-250mA. Resistance: 0-6K, 0-6mg (300 ohm and 30K at center scale). Capacitance: 10P to -0.01F. -0.01F to -1F. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 x 1 in. 69/6. P. & P. 3/6.

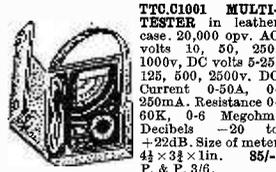**TTC1001 MULTI-TESTER** in leather case. 20,000 opr. AC volts 10, 50, 250, 1000v. DC volts 5-25, 125, 500, 2500v. DC Current 0-50A, 0-250mA. Resistance 0-60K, 0-6 Megohm. Decibels -20 to +22dB. Size of meter 4 1/2 x 3 1/2 x 1 in. 85/- P. & P. 3/6.



**GARRARD DECKS**

1025 Stereo/mono cart.	£7.19.6
2025 Stereo/mono cart.	£8.19.6
3000/S Stereo/mono cart.	£9.19.6
3000/D Stereo Diamond cart.	£10.19.6
SP25 less cart.	£11.19.6
SP25 Deram Stereo cart.	£17. 4.6
AT60 less cart.	£13.19.6
AT60 Deram Stereo cart.	£19. 4.8
AP75 less cart.	£22.11.6
SL75 less cart.	£34.18.9
SL95 less cart.	£44. 6.9

All plus P. & P. 12/6.

**NOW OPEN—OUR NEW Hi-Fi Demonstration Room**  
 • Recording Tape Bar  
 • Scientific Centre—wonderful selections of Microscopes, Binoculars, Telescopes.  
 At 18 Tottenham Court Rd., W 1

**NEW STEREO/MONO HEADPHONES**

**SDH-7.** Soft rubber earpieces with slide switch for mono/stereo listening and ind. vol. controls. Impedance 8-16 ohm. Freq. response 25-15,000 cps. With lead and stereo plug. £8.6.0. P. & P. 3/6.



**STEREO HEADPHONES**

**GI111.** With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000cps. With lead and stereo plug. £3.10.6. P. & P. 3/6.

**SINCLAIR 212 12 watt integrated amp and pre-amp.** Size 8 x 1 1/2 x 1 1/2 in. Built with manual £4.9.6. P. & P. 3/6.

**STEREO HEADPHONE JUNCTION BOX.** Enables headphones to be used with any amplifier. Incorporates amplifier leads, speaker terminals, jack socket and speaker/headphones switch. 29/6. P. & P. 2/-.



**NEW TRANSISTOR MODULES.**

**E.1311. PHONO PRE-AMPLIFIER.** Size 2 x 1 x 1/2 in. built-in R.I.A.A. Characteristics enabling low output to 1 volt. Input 100K ohm; Gain: 28dB; Max. output: 3; Max. Input: 50mV; Distortion: 0-15% (at 1v level). Powersupply: 9-12v. 29/6. P. & P. 2/-.

**E.1312. TAPE PRE-AMPLIFIER.** Incorporating N.A.R.T.B. curve characteristics, this amplifies tape head signals up to 1 volt within the frequency range of 30Hz-15KHz. Input imp 100Kohm; Gain: 26dB; Max. output: 2v; Max. Input: 50mV; Distortion: 0-15% (at 1v level); Powersupply: 9-12 volts. 29/6. P. & P. 2/-.

**E.1313. MICROPHONE PRE-AMPLIFIER.** Enables a low output microphone to be used with an amplifier or radio. Input imp. 100K ohms; Gain: 28dB; Max. output: 3v; Max. input: 50mV; Distortion: 0-15% (at 1v level); Freq. res. 10Hz-50KHz. Power supply: 9-12v. 29/6. P. & P. 2/-.

**E.1314. POWER AMPLIFIER.** When used in conjunction with E.1311, E.1312 and E.1313, units this amplifier module produces about 300mW output for speaker connection (8-16 ohms), without necessity for an output transformer. Input imp: 1,000 ohms; Gain: 20dB; Output: 300mW; Distortion: 3% (at 200mW output level). Freq. res. 50Hz-10KHz. Power supply: 9v Current 30mA at no signal, 80mA at max. output. 29/6. P. & P. 2/-.


**E.1315. ELECTRONIC ORGAN TONE OSCILLATOR.** Used in conjunction with an organ keyboard, variable resistances and a 9v power supply, this module acts as the oscillator unit for an electronic organ. Tone Frequency: 200-1,000Hz; Output: 30mV; Current: 15mA. 25/- P. & P. 2/-.

**E.1316. MORSE CODE OSCILLATOR.** A transistorised morse code oscillator (buzzer) to be used in conjunction with an operating key. Suitable for direct connection to a loudspeaker. Tone freq. 400Hz; Power output: 60mW; Power supply: 3-9v. Current: 45mA. 25/- P. & P. 2/-.

**E.1317. WIRELESS CODE OSCILLATOR/TRANSMITTER.** Can be used with an ordinary AM radio receiver for modulated signal transmissions, and for bench trouble shooting when servicing. Trans. Freq: 400Hz-30MHz; Tone freq: 400Hz; Power supply: 9v DC. Current: 35mA. 25/- P. & P. 2/-.

**E.1318. DUAL LAMP FLASHER.** A switch module for electronically alternating two miniature bulbs, 6V, 100-200mA. Ideal for models, toy boats and planes, displays, warning and security devices, communication signals, etc. Flasher time: 1/2 sec; Power supply: 6v DC. Current: 150mA; Lamp: 6V-150mA. 25/- P. & P. 2/-.

**COMPACT 2-WAY INTERCOMS.**

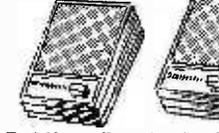

For table or wall mounting. Smart two tone grey cases size 3 1/2 x 1 1/2 x 2 1/2 in. Complete with lead, staples and 9v battery. 49/6. P. & P. 3/6.




**AC/DC CONVERTER.** Enables transistor equipment to be operated from AC mains. 6/9 12v output selector switch and on/off switch. Grey case size 4 x 2 1/2 x 2 in. complete with mains lead, connecting leads and instructions. 59/6. P. & P. 3/6.




**CIRCUIT 10 watt Amplifier.** Size only 1 x 0-4 x 0-2 in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. 1 Guaranteed 5 years. ONLY 59/6. P. & P. 1/6.

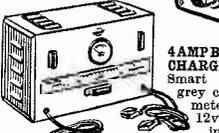**NEW—VHF AIRCRAFT BAND CONVERTOR.** When placed within lin. of a MW band radio full coverage of VHF Aircraft Band 108-135Mc/s. can be obtained. All transistor, 9v battery operation fully tunable. 18 1/2 in. x 7 section telescopic aerial. Size 4 x 2 1/2 x 1 1/2 in. 79/6. P. & P. 3/6.



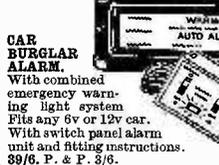**4 AMP BATTERY CHARGER.** Smart hammer grey case 13 1/2 in. meter, 6v and 12v switch. Includes safety fuses and heat vents. Complete with 5ft. three core mains lead, 5ft. red and black battery leads with heavy duty crocodile clips. 59/6. P. & P. 4/6.



**CAR BURGLAR ALARM.** With combined emergency warning light system. Fits any 6v or 12v car. With switch panel alarm unit and fitting instructions. 39/6. P. & P. 3/6.



**NEW TRANSISTOR CHECKER.** For measuring alpha, beta, and Ico factors of transistors also for checking germanium and silicon diodes. Internal 9v. battery. Wide reading scale. Moulded case size 7 x 4 1/2 x 3 1/2 in. Ranges: Alpha 0-7-0-9987; Beta 0-300; Ico 0-50A-5,000A. Diode Test: Forward and reverse internal resistance. Resistances: 200 ohm-1 megohm. Complete with connectors and instruction booklet. £7.19.6. P. & P. 3/6.

**EAGLE TT.144 TRANSISTOR TESTER.** Tests in-circuit or out of circuit. Identifies PNP and NPN types. Indicator lamp provides positive information on the following tests: Electrode open circuits and current drain. Provides reliable GO-NO-GO tests at practical collector currents of from 5mA-50mA or more on power transistors. With accessories and instructions. Size 3 1/2 x 6 1/2 x 2 1/2 in. £4.19.6. P. & P. 3/6.

**"HI-TEN" LOUSPEAKER**

British made full range 10in. unit handles up to 10 watts. Ceramic magnet. Freq. response: 40-10,000 cps. Imp: 15 ohms. Flux density: 10,000 lines. 49/6 P. & P. 4/6.



**S-DeC BREAD BOARD**



Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. 29/6 P. & P. 2/6.




**9 in 1 ELECTRONIC KIT** Build nine different projects from one basic kit—no mechanical knowledge required. Build a Police Siren, Metronome, Morse Code Amplifier, Electronic Massager, W/T Transmitter, Radio Telephone, One transistor Radio, Two-transistor radio, Electronic Music Kit. Completely safe-operated on 9v. EP3 battery. Complete with simple step by step instructions. ONLY 69/6 P. & P. 5/-.



**SOLDERING GUN** With interchangeable tips, extension barrels, comfortable grip with trigger control, "U" shaped 3 1/2 in. bit to minimise wear. Light beam is automatically directed on to end of bit when ON/OFF trigger is in use. Complete with 2-pin plug 230-250 volts. Spares available. 85 watt element. 49/6 P. & P. 2/6.



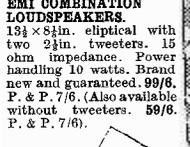**"ADASTRA" SOLDERING IRON.** 30 watt. Employs its protective cover as a handle. AC 230/250v. Adjustable bit. With 4ft. lead. Spares available. 12/6 P. & P. 2/6.



**EMI COMBINATION LOUSPEAKERS.** 13 1/2 x 8 1/2 in. elliptical with two 2 1/2 in. tweeters. 15 ohm impedance. Power handling 10 watts. Brand new and guaranteed. 99/6. P. & P. 7/6. (Also available without tweeters. 59/6. P. & P. 7/6).

**LIND AIR (OPTRONICS) LTD.**

18 Tottenham Court Road, London, W.1. Tel: 01-580 2255.  
 25 Tottenham Court Road, London, W.1. Tel: 01-580 7679.  
 53 Tottenham Court Road, London, W.1. Tel: 01-580 4534.  
 Open 9-6 pm Monday to Saturday Open Thursday until 7 pm.

ALL MAIL ORDERS  
 To Dept. PW1268  
 53 Tottenham Ct. Rd.,  
 London, W.1.

# PEAK SOUND

## ES.10-15 LOUDSPEAKER

As described in  
"Wireless World"  
and much praised  
by Hi Fi News,  
October.



## A revolutionary advance in design logic

In the Peak Sound ES.10-15, low priced components are combined in an original way to produce a loudspeaker so startlingly good that it has no difficulty in comparing with speakers costing six or seven times as much. Mr. P. J. Baxandall, world recognised for his work on tone control systems, designed and describes this speaker in "Wireless World" August and September Issues, and Peak Sound are privileged to offer the designer-approved assembly exact to specification.

Response 60-14,000Hz (100-10,000 ± 3dB). Loading up to 10 watts R.M.S.; Impedance 15 ohms. Performance is characterised by exceptional clarity and definition at all frequencies. Both size and cost make the ES.10-15 ideal for stereo. Full, simple assembly instructions with each speaker.

Equaliser assembly **£1.16.0**  
Special loudspeaker unit **£1.18.0**  
Purchase tax **8,1**  
Pack-flat Cabinet (18 x 12 x 10in.) in natural Afrormosia Teak, all parts cut and drilled. **£6.15.0**

# £10.17.1

Carr. paid in UK

Cross-over choke for using ES.10-15 with additional woofer £1.2.6.

## HI FI NEWS, REVIEWING THE ES.10-15 SAYS

"The immediate impression was of a thoroughbred speaker, smooth and effortless and unbelievable that there was not a tweeter. Voices were uncannily real. Congratulations Peter Baxandall and to Peak Sound for making this kit available."

Peak Sound products include "Cir-Kit" adhesive copper strip for circuit building; a new super high fidelity 10 watt amplifier for the constructor etc. from dealers, or in cases of difficulty please send direct. Trade enquiries invited.

### PEAK SOUND (HARROW) LTD.

32 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY  
Telephone EGHAM 5316

TO PEAK SOUND

Please send

for which I enclose £.....s.....d

NAME

ADDRESS

Block letters please

PW12

# FIRST CLASS PRECISION TOOL THE HEATHCRAFT Mini-Drill

WITH 6 MINI-TOOLS FOR  
precision drilling  
grinding, polishing  
etching, cutting  
gouging, shaping

**SUPER MODEL** 5in. long.

Powered by a 9/12 volt external battery, completely portable, shockproof. Indispensable for printed circuits, model making, precision engineering, car maintenance, optical work and every job where a tool with exceptional accuracy, power and speed is required. Fully guaranteed. STANDARD Mini-Drill with smaller motor 39/6 p & p 1/6.

C.W.O. to: Dept. L2  
Heathcraft Metal Products Ltd  
54 Poland St., London W.1.

ONLY  
**79'6**  
P&P 16



## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!


**SETS** 1R5, 1R5, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for 17/6. DAF96, DF96, DK96, DL96, 4 for 28/-.  
1R5, 1R5, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for 17/6. DAF96, DF96, DK96, DL96, 4 for 28/-.

O2A	4/6	12AX7	4/9	DK96	7/-	EL42	9/9	PEN36C15/-	UCC85	6/6	
1A7GT	7/-	12K8GT	7/6	DL35	5/-	EL84	4/9	PFL20012/-	UCR80	8/3	
1H5GT	7/-	20F2	10/6	DL92	5/9	EL90	5/-	PL36	9/6	UCH42	9/9
1N5GT	7/6	20L1	16/9	DL94	5/9	EL95	5/-	PL81	7/3	UCH81	8/6
1R5	4/6	20E3	14/9	DL96	7/-	EM80	6/9	PL82	6/6	UCL82	7/6
1R5	4/6	20F4	16/6	EL36	5/6	EM81	8/9	PL83	6/6	UCL83	8/9
1T4	2/3	2E4GT11/6		DY87	5/9	EM84	6/3	PL84	6/3	UF41	8/9
3R4	5/9	30C1	6/9	EABCS0	6/6	EM87	7/6	PL500	12/-	UF80	7/-
3V4	5/9	30C15	13/6	EAF42	8/6	EY51	7/-	PL504	12/6	UF85	6/9
6U4G	4/6	30C17	12/6	EB91	2/3	EY86	6/3	PL508	15/-	UF89	6/3
6Y3GT	5/9	30C18	9/-	EBC83	7/6	EZ40	7/6	PM54	7/9	UL41	9/6
6Z4G	7/6	30F6	12/-	EB041	7/-	EZ41	7/6	PX35	10/6	UL44	20/-
6/30L2	12/6	30FL1	12/6	EBF80	6/6	EZ80	4/6	PY32	10/-	UL84	6/6
6AL5	2/3	30FL4	12/6	EBF89	6/3	EZ81	4/9	PY33	10/-	UM84	7/6
6AM6	2/6	30L1	6/-	ECC81	3/9	KT81	8/9	PY80	5/3	UY41	7/-
6AQ5	4/9	30L15	14/-	ECC82	4/9	KT81	15/-	PY81	5/3	UY85	5/9
6AT6	4/-	30L17	18/-	ECC83	7/-	N76	14/9	PY82	5/-	VP4B	10/6
6AT6	4/6	30P4	12/-	ECC84	5/6	PABC80	7/3	PY83	5/9	V1921	21/-
6BA6	5/6	30P12	11/-	ECC85	4/9	PC86	9/6	PY88	6/3	Z77	8/6
6BE6	4/3	30P19	12/-	ECC804	12/6	PC88	9/6	PY800	6/9	Transistors	
6B3E	6/9	30PL1	12/6	ECR80	7/-	PC96	8/6	PY801	6/9	AC107	3/6
6BW8	13/-	30PL13	14/6	ECF82	6/9	PC97	8/6	R19	6/6	AC127	2/-
6C4	2/9	30PL14	15/-	ECI35	6/6	PC900	8/3	R20	12/6	AD140	7/6
6F13	3/6	36L6GT	8/-	ECH42	10/6	PC884	6/-	TH21C	9/9	AF102	18/-
6F14	9/-	35W4	4/6	ECH81	5/9	PC885	6/6	U25	13/-	AF115	3/-
6F23	12/6	36Z4GT	5/-	ECH84	6/9	PC888	9/9	U26	12/-	AF116	3/-
6K7G	2/6	6063	12/6	ECL80	6/9	PC889	10/6	U47	13/6	AF117	3/6
6K8G	4/3	AZ31	9/-	ECL82	6/9	PCC189	9/9	U49	13/6	AF124	7/6
6L15	6/-	B38	4/9	ECL83	9/-	PCF80	6/9	U52	4/6	AF125	3/6
6V6G	3/6	B729	12/6	ECL86	8/3	PCF82	6/-	U78	3/6	AF126	7/-
6V6GT	6/6	CCR35	10/-	EF39	3/9	PCF86	9/3	UI91	12/6	AF127	3/6
6X4	3/6	CL83	18/6	EF41	9/6	PCF800	13/6	U301	13/6	OC22	5/-
9X5GT	5/9	DAC32	7/-	EF50	4/6	PCF801	7/-	U801	18/-	OC26	5/9
7B6	10/9	DAF91	4/3	EF85	5/6	PCF802	9/6	UABC80	6/3	OC44	2/3
7C7	7/-	DAF96	6/-	EF86	6/3	PCF805	9/-	UAF42	9/6	OC45	2/3
7C5	15/-	DF83	7/9	EF89	5/3	PCF8011/6		UB41	6/6	OC71	2/3
7C6	6/9	DF91	2/9	EF91	3/6	PCF80812/6		UB041	7/9	OC72	3/6
7Y4	6/6	DF96	6/-	EF188	5/9	PCL82	7/-	UB831	7/-	OC75	2/-
10F1	15/-	DH77	4/-	EF184	5/9	PCL83	9/-	UBF80	6/-	OC81	2/3
10P18	15/6	DH81	10/9	EH90	6/3	PCL84	7/8	UBF89	6/9	OC81D	2/3
12AT7	3/9	DK82	7/-	EL33	8/9	PCL85	3/3	UBL21	9/-	OC82	2/3
12AU6	4/9	DK92	9/3	EL34	5/6	PCL86	8/6	UC92	5/-	OC82D	2/6
12AU7	4/9	DK92	9/3	EL41	9/6	PEN44	12/6	UCC84	7/9	OC170	2/9
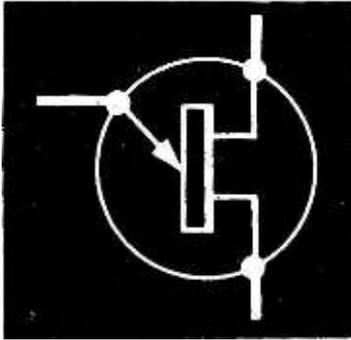
## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage In Transit 6d. extra.



# UNIJUNCTION TRANSISTOR CIRCUITS

C.R. BRADLEY

## PART 2

LAST month the basic operation of the unijunction transistor was described and some simple, practical circuits based on the use of the unijunction transistor as a relaxation oscillator were given. Some further practical circuits using unijunction transistors are featured this month.

### Calling Systems

The circuit in Fig. 7 was found useful in a large sub-divided house to enable the occupants to recognise their own particular door buzzer tones. A unijunction transistor Tr1 is used in a buzzer circuit which draws about 1/30th the power of a conventional bell or buzzer. Each occupant's bell-push on the front door produces a different toned buzz. The circuit could also be used in a house to identify callers at the front, back (and side) doors. Again layout is not critical and batteries or the mains power supply may be used. The preset potentiometers are adjusted to give four distinctly different tones.

The circuit in Fig. 8 is a door buzzer system which

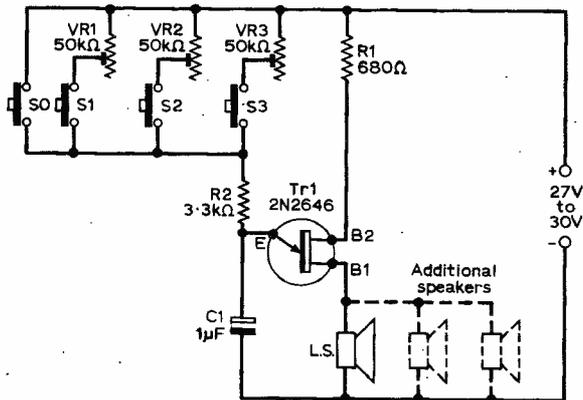


Fig. 7: Multitone calling system. VR1-VR3 are adjusted to give different pitched buzzes.

### ★ components list

R1	680Ω ¼W
R2	3.3kΩ ¼W
VR1-VR3	50kΩ skeleton presets
C1	1μF 30V electrolytic
S0-S3	Door bell-pushes
LS	3-15Ω speaker, any size
Tr1	2N2646 or equivalent
Battery or mains power supply	

was installed in a block of flats at a considerable saving over a conventional bell system. There is no limit to the number of speakers in the system. As

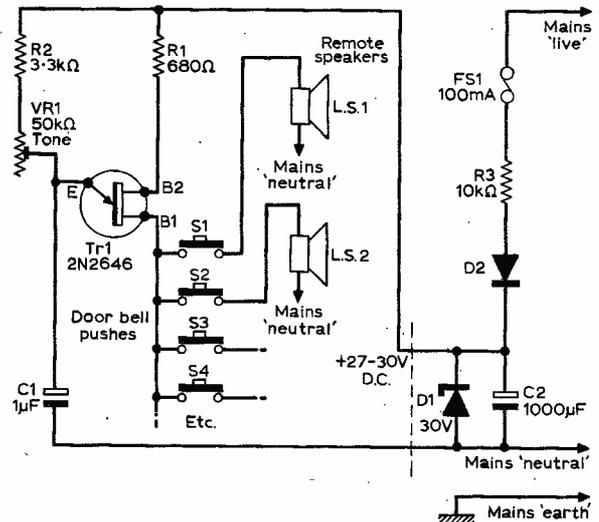


Fig. 8: Multispeaker buzzer system. Note importance of safety precautions in text if using the non-isolated power supply shown.

### ★ components list

R1	680Ω ¼W
R2	3.3kΩ ¼W
R3	10kΩ 5W
VR1	50kΩ skeleton preset
C1	1μF 30V paper or electrolytic
C2	1000μF 30V electrolytic
D1	30V 1W zener diode
D2	400V p.i.v. silicon diode
S1-S3 etc.	Bell push-switches
LS1, LS2 etc.	3-15Ω remote speakers
FS1	100mA
Tr1	2N2646 or equivalent
Fuseholder, wire, etc.	

this was a permanent installation a very simple non-isolated power supply was used. Capacitor C2 is trickle charged through R3 and D2 up to a potential of 30V when the zener diode conducts away further current. If this power supply is used it *must* be connected to the mains with the polarity as shown or the wiring will become dangerously "live".

Ensure that all exposed metal associated with the

buzzer system is earthed. Note that each speaker is returned to mains neutral. This is an economy on wire as only single core cable is required to connect each speaker to the circuit. A testmeter or neon screwdriver should be used to ensure that no connection is made to the live side of the mains.

If R3 is increased to 33kΩ 5W and C2 reduced to 500μF then the power supply will only hold enough charge to drive the circuit at full volume for a few seconds. One must then wait a few seconds before the buzzer can be used at full volume again. This feature of decaying volume would prevent annoying over use of the buzzer by callers.

### Timing Circuits

If the values of C and R in Fig. 2 are both large one can obtain extremely low frequency oscillation. For example if C is 1,000μF and R is 100kΩ the circuit will fire about once every 3 minutes. If C is a good quality electrolytic used well within its voltage rating (for low leakage current) then the period will remain constant. Supply voltage changes and temperature variation have little effect on the period. For this reason the unijunction is excellent for use in timing circuits in which it acts as a one-shot oscillator.

### Photographic Timer

The circuit in Fig. 10 is a photographic timer which will switch on an enlarger for a preset period of 1 second to 1 minute. The operation is as follows: S1 ("on") is pressed to open and the relay de-energises. C1 now charges slowly through R1 and VR1, the latter having been set for the required period. During this time the enlarger lamp draws current through the relay contacts RL2. When C1 reaches

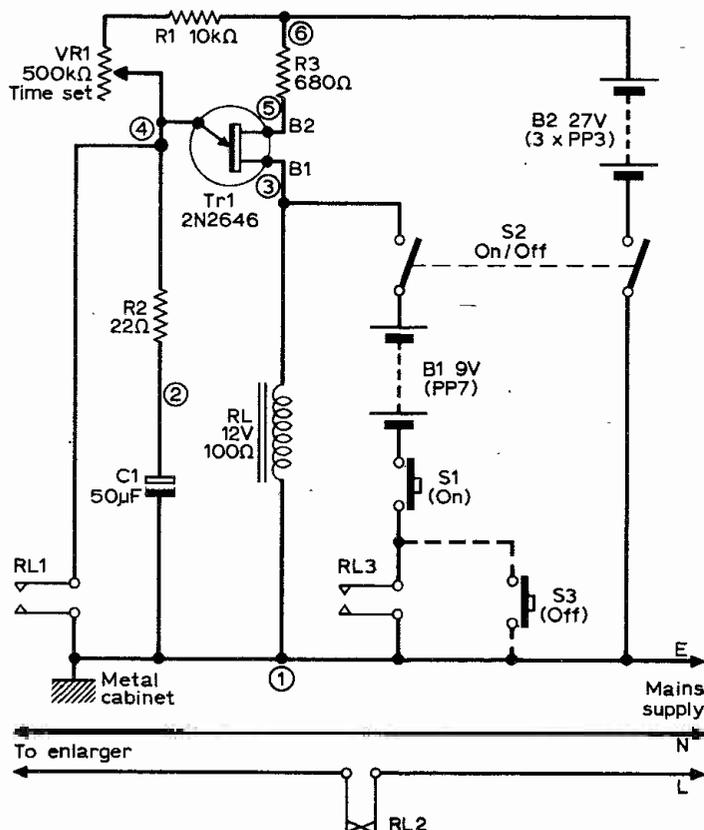


Fig. 10: Photographic enlarger timer. Pressing S1 de-energises the relay for a time set by VR1. While the relay is de-energised the enlarger is on.

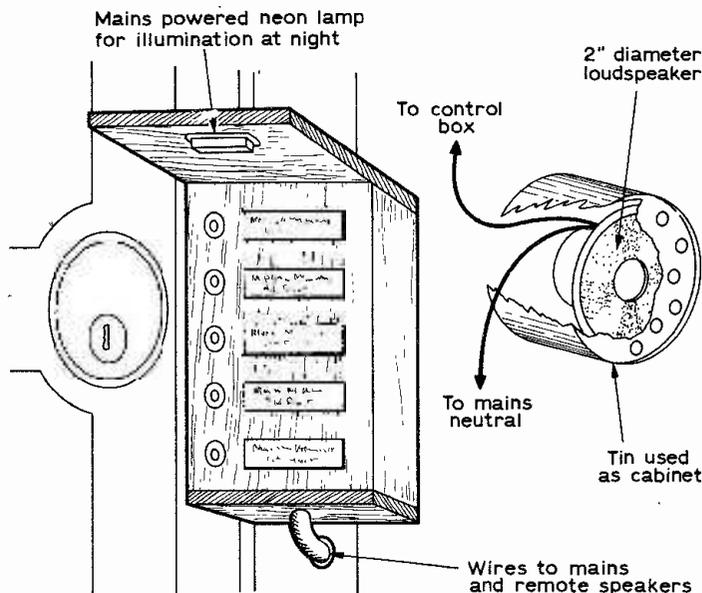


Fig. 9: Constructional details of the multispeaker buzzer system.

the unijunction firing voltage it discharges through the unijunction and the relay, causing the relay to energise. Once the relay is energised it is held closed by B1 until S1 is opened to start another timed period. When the relay is energised the contacts RL1 discharge C1 to ensure that it has zero charge at the start of each timing period.

R2 limits the peak discharge current through the unijunction. It may be reduced if the relay does not close properly. VR1 should be an ordinary logarithmic track potentiometer wired to give increasing period with clockwise rotation. This gives a better spaced scale than a linear type would. The scale is very non-linear but can be calibrated easily using a stopwatch. The maximum period may not be exactly 1 minute but will probably be within 2-3 seconds of this. For most photographic purposes this will not matter. Similarly, the minimum period may not be 1 second

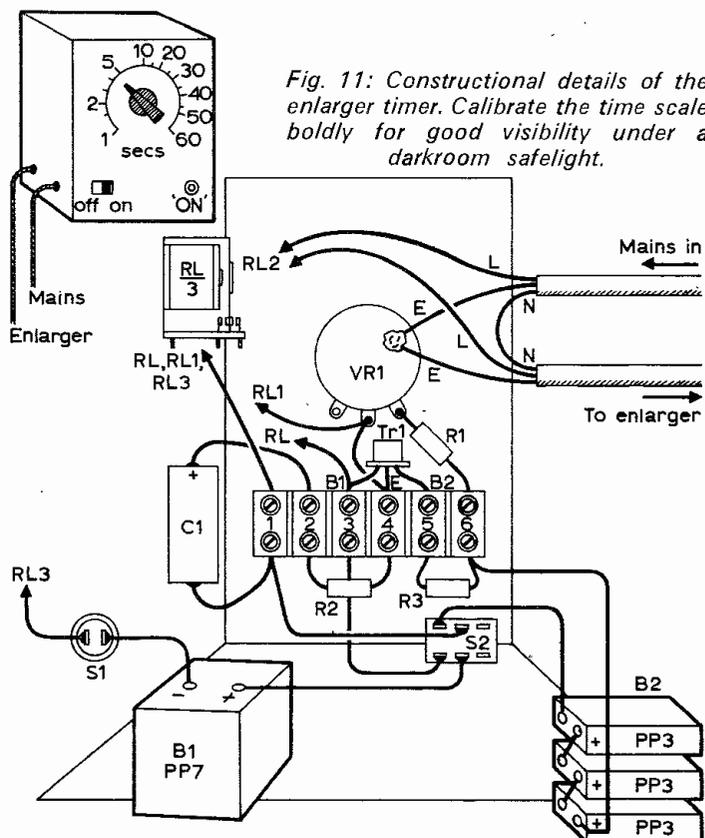


Fig. 11: Constructional details of the enlarger timer. Calibrate the time scale boldly for good visibility under a darkroom safelight.

# Wharfedale High Fidelity single unit speaker - Super 8



The Super 8 is a single, wide spectrum loudspeaker unit. The massive magnet gives it very high sensitivity and it will give a much louder and purer sound volume than ordinary speakers.

It is simplicity itself to install in a home-built cabinet, needing no special skills.

The Super 8 will transform the results from your radio or radiogram. The sound of your television set can be greatly enhanced by using the Super 8 with a Wharfedale transformer.

Installed in your car, you will achieve a wonderful depth of sound from a normal car radio.

The Super 8 is a real high fidelity loudspeaker and gives a response from 20 Hz to 20,000 Hz in a good enclosure.



**RANK WHARFEDALE LTD.**  
**IDLE, BRADFORD, YORKS.**

**Multi Purpose Neon Test Unit.** Robust, useful and instructive, tests insulation, capacity, continuity, resistor, volume controls, also acts as signal injector and L.T. fault finder, kit comprises neon indicator, 4-way water switch, chonite tubes, resistors-condensers, terminals, etc., with diagram, only 9/6, plus 2/- post and insurance.

**5 Push Switch.** One push operates mains on/off switch, the other four operate various on/off and change-over switches. 2/6.

**A.E.I. Fractional H.P. Motor.** 200/250 v. 50/60 c.p.s. enclosed, continuous rating 1/40 h.p., ex. equip. Perfect order, 19/6, plus 4/6.

**Experimenting with ultra violet?** Philips U.V. lamp, 19/6; holder and control gear 19/6.

**G.E.C. Black Light Tube** for experiments and special lighting effects—40 watt 2ft. tubes only, 14/6 each; holders and control gear, 19/6, plus 4/6 post.

**Clock Motor.** 230v. 50 cps synchronous—self starting, 6/6.

**Pentode Output Transformer.** Standard size, 40-1, ex-equipment but OK, 4/8 each, 48/- doz. Post paid.

**E.H.T. Condenser.** 0-1 mfd. 5 kv, 8/6 each.

**Neon Mains Tester,** 1/3 each, 12/- doz.

**Flood Lamp Control.** Our dim and full switch is ideal for controlling photo flood lamps; it gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances can be arranged where used in pair or where circuit can be split exactly in half. Technically the switch is known as a double-pole change over with off. Our price 4/6.

**Sub-Minature Silicon Diodes.** General purpose type with gold-plated leads, 1/- each or 7/6 per dozen.

**Message Tapes.** 225ft. Tape on 3in. spools, normally 4/6 each, we offer 4 tapes for 12/6.

**White Circular Flex.** Ideal for lighting drops, twin made by BICC. Usually 8d. yd., 100 yd. coil for 30/-, plus 6/- postage.

**Edgewise Control.** Morganite, as fitted many transistor radios, 2K or 5K with switch, 2/6 each or 24/- per dozen.

**12V Inverter.** Full transistorised for operating a 20-watt fluorescent tube, size 6in. long x 1 1/2 x 1 1/2. £3.10.0. Post and insurance 3/-.

**Silicon Rectifier.** Equiv. BY100 750mA 400V., 10 for 20/-.


**Miniature Pickup** for 7in. records made by Cosmo-code, crystal cartridge with sapphire stylus only 3/9 or 35/- dozen.

**Telesopic Aerial** for radio or transmitter, chrome plated, 6 section extends from 7 1/2in. to 47in., 7/6 each, 54 per dozen.

**Midget Neons** for mains indicators, etc., 1/3 each or 12/- dozen.

**Compression Trimmers.** Twin 100pF, 1/- each; 9/- per dozen.

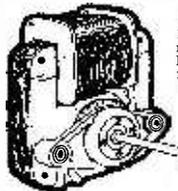**3in. PM Loudspeaker.** 3 ohm, 12/6; 80 ohm, 12/6.



### MAINS MOTOR


Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.

### WORKSHOP or REFRIGERATOR ?

Many readers will have found to their dismay that the loft, garage or shed, which they so carefully converted into a workshop, is just a refrigerator in the winter—it can't be used, because it never gets warm until it is time to finish. The answer is "RADIANT ZONE HEATING". Benefit from this type of heating is immediate and low in cost. Our Radiant Zone Heaters (made by the famous Philips Company) are internally mirrored glass tubes with built in 500 watt heat and light elements. Four of these over the average size bench is all you need and will cost only about 4d. an hour to run. Ideal also under typists' desks. Keeps legs and knees warm, no matter how mini the "mini". Price is 27/6, post and insurance 4/6 on one or any quantity.

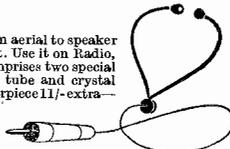
### RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. 29/6—twin stethoscope instead of earpiece 11/- extra—post and ins., 2/9.


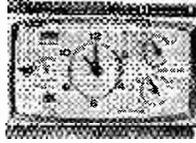
### ELECTRIC CLOCK WITH 20 AMP SWITCH

Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another timer or alarm—this may be set in minutes up to 4 hours. At the end of the period a bell will sound. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



### DEAC RECHARGEABLE BATTERY

3-6V-600mA hr.—size 1 1/2 x 1 1/2 in. dia. really powerful will deliver 1 amp for 1/2 hour. Regular price 33/6 each—our price 19/6 each unused but ex-equipment.

**Precision Wheatstone Bridge.** Opportunity to buy cheaply. 100K wire wound pot. 15W rating, only 5/-.

**Sheet Paxolin.** Ideal for transistor projects. 12 panels each 5in. x 8in., 5/-.

**Transistor Ferrite Slab Aerial** with medium and long wave coils, 7/6 each.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. With enquiries please.

**Rotary Cam Operated Switch.** 12 positions each of which close a separate pair of contacts except the last which leaves them all open. Contacts rated at 250V 16 amps, 15/- each.

**Rotary Cam Operated Switch.** 4 positions: 1st position all contacts open; 2nd contact 1 closed; 3rd contacts 1 and 2 closed; 4th contacts 1, 2 and 3 closed. Contact rated 250V 16 amps, 8/6 each.

**Under Carpet Heating Element.** Waterproof plastic covered element 12 yds. long, 900 watt, 19/6 each.

**Breast Microphone.** Fine American made dynamic type, adjustable on breast plate with neck straps, 7/6, post 4/6.

**Circular Fluorescent.** 22 watt, 9in. diam. tube complete with choke, starter, holders and chrome clips, 29/6, post, etc., 4/6.

**Midget Relay** twin 250 ohm coils, size approx. 1 1/4in. x 1in. x 1in. 4 pairs changeover contacts, 7/6 each.

**P.O. Type Relay.** Twin 200 ohm coils, size approx. 3in. x 2in. x 3in. 4 pairs changeover contacts, 8/6 each.

**Printed Circuit Board, Edge Connector,** solder terminations, 32 contacts, standard spacing for veroboard, etc. 6in. long but easily cut, 7/6 each, 30/- doz.

**1,000V Fire Spiral,** replacement for most fires, 1/3 each, 12/- doz.

**50 ohm 50 watt Wire Wound Pot-meters,** 8/6 each. 1 Meg Miniature. Pot-meter Morganite standard 3in. spindle 1/- each; 9/- per dozen.

**1 Meg Miniature.** Pot-meter Morganite preset screwdriver control. 9d. each; 8/- per dozen.

**Pre-Set 100K** by Welwyn with intricate bakelite knob, 1/- each; 9/- per dozen.

**100K Pot-Meter.** Miniature type with double pole switch and standard 3in. spindle, by Morganite, 2/- each; 18/- per dozen.

**Blanketstat Glass.** Enclosed, normally closed. Circuit will open should blanket overheat, 4/6 each.

**Thermal Relay.** Can be used to delay the supply of HT while heaters warm up, or will enable 15A loads to be controlled by miniature switches or relays. Regular list price over £2, price 7/6 each. Siemens High Speed Relay. Twin 1,000 ohm coils. Platinum points changeover contacts—Ex equipment, 8/6 each.

**Toggle Switch Bargain.** 10A 250V normal one hole fitting 2/9 each; or 30/- per doz.

**Electric Lock.** 24V coil, but rewindable to other voltages, 4/6 each.

## ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CR0-2TH

# YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fulllest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAME ..... Block

ADDRESS ..... Caps.

Please 12/88

## BRITISH NATIONAL RADIO SCHOOL

17in.—£11.10.0  
19in. SLIMLINE  
SOBEL—24 Gns.


**TWO-YEAR GUARANTEE**  
**EX-RENTAL TELEVISIONS**

**FREE ILLUSTRATED LIST OF TELEVISIONS**


17"-19"-21"-23"  
WIDE RANGE OF MODELS  
SIZES AND PRICES  
DEMONSTRATIONS DAILY

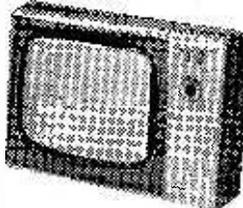**TWO-YEAR GUARANTEED TUBES 100% REGUNNED**

14in.—69/6 17in.—89/6  
21in. and ALL SLIMLINE TUBES 99/6  
EXCHANGE BOWLS. Carr. 10/6  
EX. MAINTENANCE TESTED TUBES  
17in.—35/-, Carr. 5/- (not slimline)



### COCKTAIL/STEREOGRAM CABINET £25

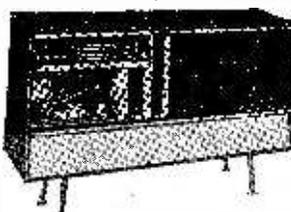

Polished walnut veneer with elegant glass fronted cocktail compartment, padded. Position for two 10in. elliptical speakers. Record storage space. Height 35 1/2in., width 52 1/2in., depth 14 1/2in. Legs 1 gn. extra.

**OTHER MODELS. SEND FOR FREE LIST**

**TRANSISTOR CHASSIS D1 49/6**

6 Transistors, LW/MW. Brand New. Famous British Manufacturer.

(LESS SPEAKERS). Dia. 7 1/2" x 3 1/2". P. & P. 4/6.

**TRANSISTOR CASES 19/6.** Cloth covered, many colours. Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 4/6. Similar cases in plastic 7/6.

**TRANSISTOR RECORD PLAYER CABINETS 19/6.** Dim. 11" x 14 1/2" x 5 1/2". P. & P. 7/6.

**SINGLE PLAYER CABINETS 19/6.** P. & P. 7/6.

**AUTO CHANGERS £8.19.6.** Garrard 3000 with sonotone 9T. A.C. D/S stereo cartridge.

**STRIP LIGHT TUBES 3/9** each. 11" (284 mm.) 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting etc. 6 for £1. P. & P. free.

**DUKE & CO. (LONDON) LTD.**

621/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

exactly due to component tolerances. If a precise range of 1 second to 1 minute is required it may best be obtained by trying different components for R1, VR1 and C1. (Adjust R1 to vary the minimum period.) Doing this, one will discover the very wide tolerance allowed between electrolytic capacitors and the extreme non-conformity of potentiometer tracks! However, once calibrated the circuit will give very accurately reproducible timed periods.

A fairly high current is required to hold the relay closed and this is why a separate battery is used for this. 9V should be sufficient to operate the relay. If not a 12V battery can be used. When S2 is "off" the timer is out of action. The enlarger will remain on indefinitely when S1 is held pressed.

For safety reasons it is best to build the timer in an earthed metal cabinet, as darkrooms are likely to be humid. A further push-button switch S3 ("off") may be incorporated to interrupt a timed period if desired (see Fig. 10).

## ★ components list (ENLARGER TIMER)

R1	10k $\Omega$ $\frac{1}{4}$ W
R2	22 $\Omega$ $\frac{1}{4}$ W
R3	680 $\Omega$ $\frac{1}{4}$ W
VR1	500k $\Omega$ log. pot.
C1	50 $\mu$ F 30V or above electrolytic
B1	9V PP7
B2	27V 3 x PP3
RL	12V 100 $\Omega$ miniature relay with 3p.d.t. contacts
S1	Press-to-open switch
S2	D.P.S.T. on/off switch
S3	Press-to-close switch (if required)
Tr1	2N2646 or equivalent
Metal cabinet, terminal block, large pointer knob, wire, etc.	

## Colour Timer

A more complex photographic timer built for amateur colour print work (Paterson Pavele process) will be described briefly. The complete circuit without

constructional details is shown in Fig. 12. The timer is designed to do the following: (1) Switch on the enlarger for three separately set times (successive exposures through red, green and blue filters). (2) Give an audible signal at the end of three different preset periods of 3, 1 and 2 minutes (developer, stop and bleach-fix bath times).

The operation with S3 in positions 1, 2 and 3 (red, green and blue) is clearly the same as the timer already described. VR1, VR2 and VR3 determine the red, green and blue exposures respectively. At the start and finish of each period a click is heard from the internal speaker.

For the three chemical bath times S3 is set to position 4 ("chem") and the appropriate preset period set by S5. To start the period (when the colour print is first immersed in the bath) S1 is pressed as before. The relay opens and the "chem" neon indicator lights (but not the enlarger). C3 is slowly charged through R4 and VR4, VR5 or VR6, and D1. After a minute or more the unijunction emitter reaches the firing potential. The unijunction fires and C2 is discharged by the diode D1. As the charge in C2 is insufficient to energise the relay, the circuit now oscillates as a relaxation oscillator with C2 as the capacitive timing element. A warning buzz is heard from the loudspeaker.

S4 ("off") is pressed to return the timer to normal (relay energised). S4 can also be used to interrupt a timing period. Relay contacts RL1 and RL2 discharge the timing capacitors between timing periods; R5 protects RL1 against excessive discharge current from C3.

It is important to note that the battery negative line is connected to the live side of the mains. For

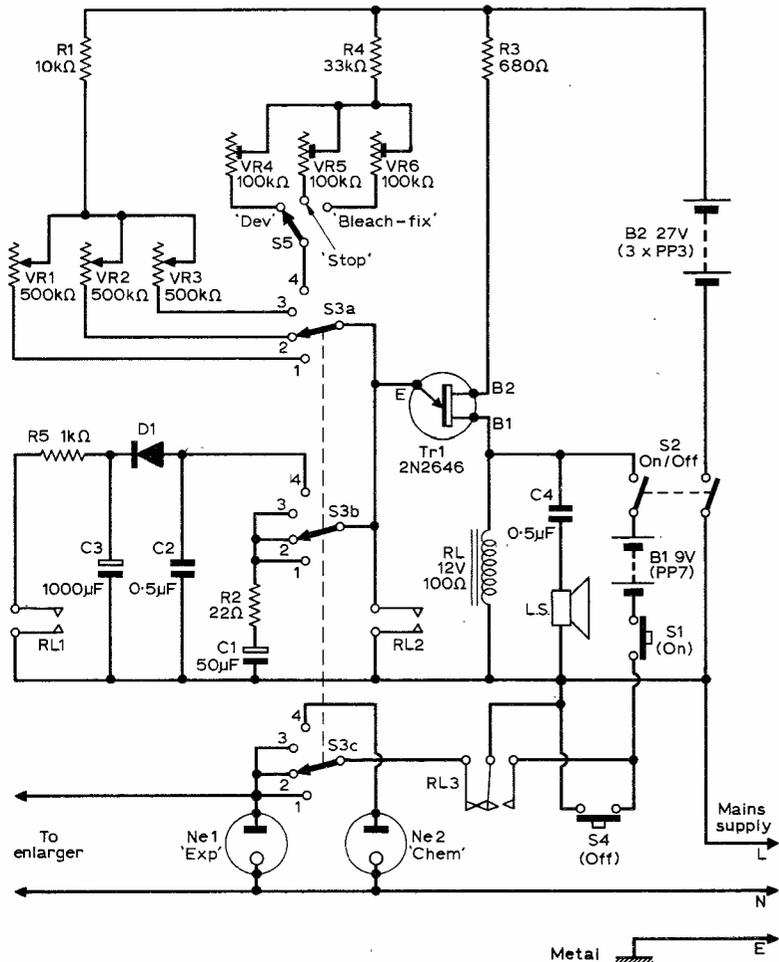


Fig. 12: Colour photographic timer. S3 settings: (1) Red exposure, set by VR1; (2) green exposure, set by VR2; (3) blue, exposure, set by VR3; (4) audible chemical bath time warning, three different preset periods set by S5.

safety the circuit must be wired inside an *earthed* metal cabinet to which no other connection is made. In this respect the author made a mistake which might be instructive; the 27V supply is provided by three PP3 batteries which are metal cased. These were taped to the inside of the earthed metal cabinet without a second thought. When the instrument was first plugged in, fuses blew! Mains voltage had occurred across the internal case insulation of the PP3 batteries, which had been unable to withstand it. The remedy, of course, was to insulate the batteries from the cabinet. But there is a more important lesson to be drawn. Had the cabinet not been earthed it would have become dangerously "live" without blowing fuses. ■

## ★ components list

R1	10kΩ ¼W
R2	22Ω ¼W
R3	680Ω ¼W
R4	33kΩ ¼W
R5	1kΩ ¼W
VR1-VR3	500kΩ log. pots
VR4-VR6	100kΩ skeleton presets
C1	50µF 30V electrolytic
C2	0.5µF paper
C3	1000µF 30V electrolytic
C4	0.5µF paper
D1	Germanium diode
B1	9V PP7
B2	27V 3 x PP3
Ne1, Ne2	Mains neon indicators
LS	Small 3-15Ω speaker
RL	12V 100Ω miniature relay with 3p.d.t. contacts
Tr1	2N2646 or equivalent
S1	Press-to-open switch
S2	D.P.S.T. on/off switch
S3	Rotary 3p.4t. switch
S4	Press-to-close switch
S5	Rotary s.p.3t. switch
Metal cabinet, three pointer knobs, etc.	

## PYRAMID SYSTEM — continued from page 592

inside the bottom portion, and rests on strips. Hinges, a catch, and carrying handles can then be screwed on.

## Motor and Pickup

Leads from the motor and switch are fitted with battery clips, this circuit being separate from other connections as shown in Fig. 5. The motor is started by lifting the arm and moving it outwards. When the record is played movement of the pickup automatically operates the on/off switch, stopping the motor.

A screened lead descends through the pick-up arm mounting, and this is brought to a tagstrip, which anchors the impedance compensating resistor, and external lead. The external lead has a plug to match the amplifier input socket.

With a low impedance pick-up, the resistor is reduced in value, or omitted. The value shown is for the usual type of popular crystal pickup. Lowering the value increases volume, but pickup matching deteriorates. The amplifier tone control is adjusted for most satisfactory results.

TO BE CONTINUED

## NEXT MONTH IN P.W.

### THE SOLID STATE

To mark the 21st anniversary of the advent of the transistor, this article provides a simple account of exactly how semiconductor devices work, from the simplest diodes to the more complex components coming into use at the present time.

### SUBMINIATURE HEARING AID AMPLIFIER

Designed around an integrated circuit, this amplifier is built on a simply etched printed board measuring only  $1\frac{1}{8} \times \frac{3}{4}$  in. Alternative uses are as a miniature audio preamp or stereo preamp.

### REPAIRING RADIO SETS

What to do when confronted with an unknown set. This feature tells how to diagnose faults when no data is to hand, covering both valve and transistor receivers.

### PYRAMID SUPERHET TUNER

Three-waveband (515–1545kc/s, 1.67– 5.3 Mc/s and 5–15Mc/s) tuner with five tuned circuits in the i.f. strip to provide high gain and selectivity. For use with the Pyramid amplifier or, with one small modification, to drive any other amplifier.

### CAPACITANCE BRIDGE

Build this simple piece of test equipment for the measurement of unknown capacitor values.

### P.W. COMPONENTS GUIDE

The second feature in this series deals with the wide variety of types of capacitors available today, with practical advice on the best type to use for a given job.

**PRACTICAL  
WIRELESS**

All in the JANUARY issue on  
sale DECEMBER 5th



**ORDER YOUR COPY NOW!**


Sinclair launch their System 2000 range with coils. They have become an integral part of the amplifier, tuner and speaker shown here. The tuner and amplifier are separate units which may be mounted together for convenience. Each is complete in itself and may be used with existing high fidelity equipment. The System 2000 uses new components and ingenious construction in ways which reduce costs, increase performance and improve reliability. For example, look at the circuits of most F.M. tuners and you will find that they vary very little. Look at the System 2000 tuner. You will notice the absence of conventional

provision for plug-in remote and switched tuning units (available separately). The amplifier and loudspeaker are equally outstanding and well worth comparing for yourself. Ask your dealer for a demonstration or write or ring us for a leaflet.

- System 2000 35 watt integrated Stereo Amplifier 29 gns
- System 2000 F.M. Tuner 25 gns plug in stereo decoder gns
- System 2000 8-ohm loudspeaker 1 gns

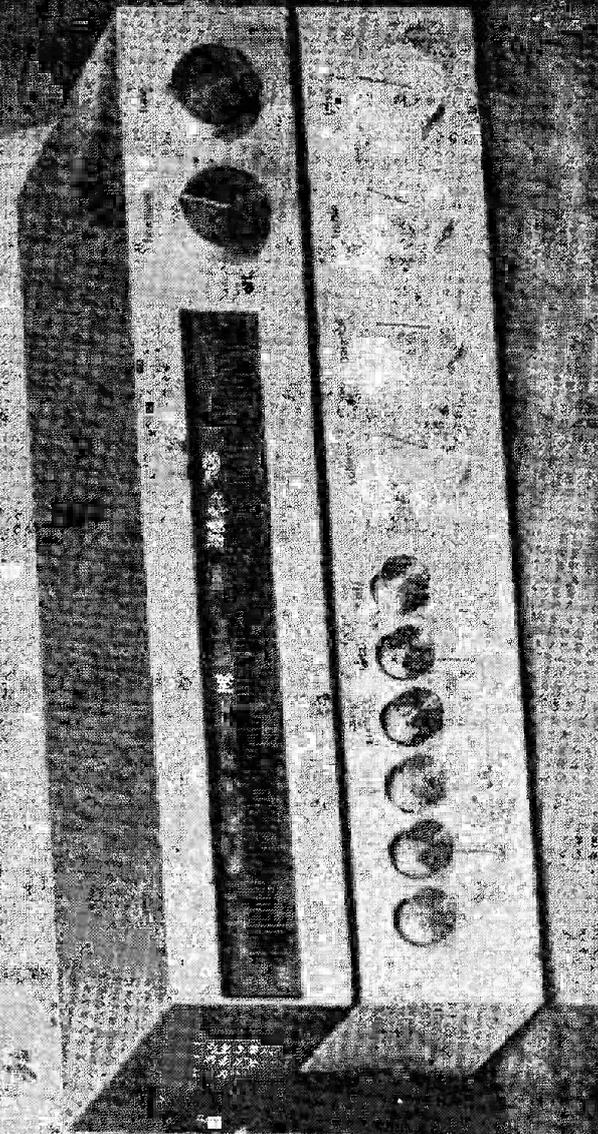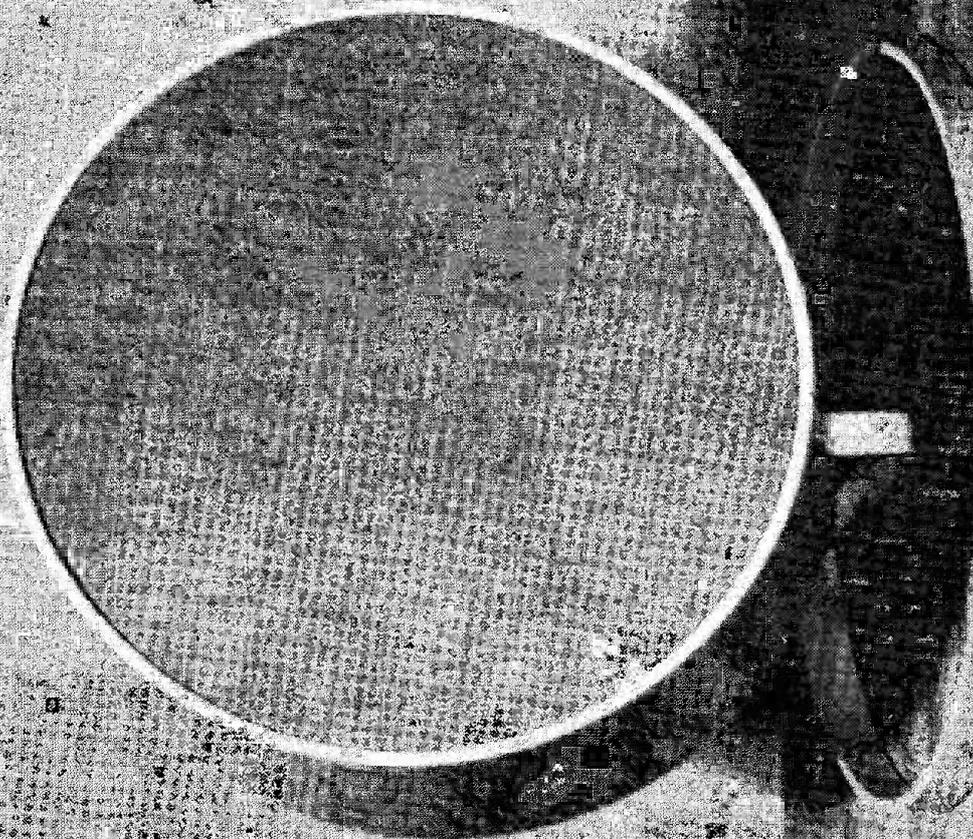Sinclair Radionics Limited, 22, Newmarket Road, Cambridge. Tel Cambridge 52996



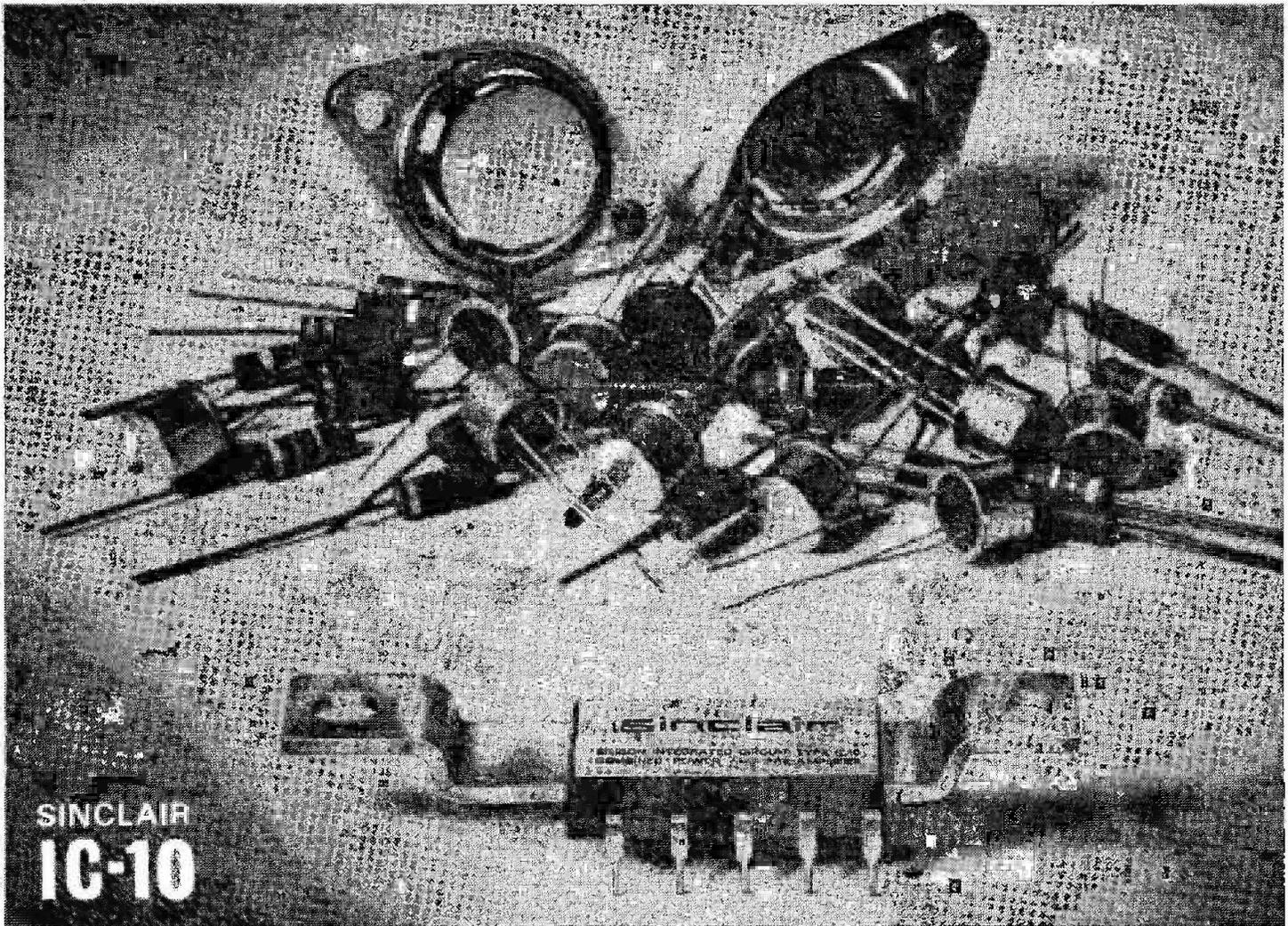

## the world's most advanced high-fidelity amplifier

The Sinclair IC-10 is the World's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, which has an output power of 10 Watts, is a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick. This tiny chip contains 13 transistors (including two power types), 2 diodes, 1 zenor diode and 18 resistors, all of which are formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins.

Monolithic I.C.'s. were originally developed for use in computer and space applications where their extraordinary toughness and reliability were even more important than their minute size. These same advantages make them ideal for linear applications such as audio amplifiers, but hitherto they have been confined to low power applications. The IC-10 thus represents a very exciting advance. Not only is it far more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most

important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of the usual tone and volume controls and a battery or mains power supply. However, the IC-10 is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc.

The photographic masks required for producing monolithic I.C.'s. are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. So we are able to sell the IC-10 at a price far below that of the components for a conventional amplifier of comparable power. At the same time, we give a 5 year unconditional guarantee on each IC-10 knowing that every unit will work as perfectly as the original and do so for a lifetime.

**sinclair**

**SINCLAIR RADIONICS LTD, 22 Newmarket Rd. Cambridge. Tel: OCA3-52731**

# 10 WATT MONOLITHIC INTEGRATED CIRCUIT AMPLIFIER

## ■ Specifications

Power Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz $\pm$ 1dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5 mV.
Input impedance	Adjustable externally up to 2.5 M ohms for above sensitivity.

## ■ Circuit Description


The circuit diagram of the IC-10 is shown on the right. The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. The output stage operates in class AB with closely controlled quiescent current which is independent of temperature. A high level of overall negative feedback is used round both sections and the amplifier is completely free from cross-over distortion at all supply voltages. Thus battery operation is eminently satisfactory.
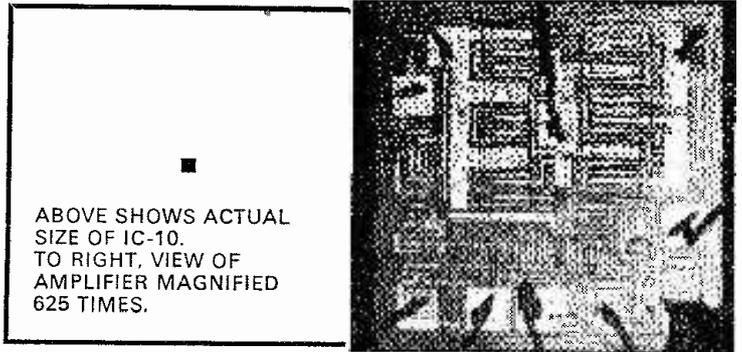
## ■ Construction


The monolithic I.C. chip is bonded onto a gold plated area on the heat sink bar which runs through the package. Wires are then welded between the I.C. and the tops of the pins which are also gold plated in this region. Finally the complete assembly is encapsulated in solid plastic which completely protects the circuit. The final device is so rugged that it can be dropped thirty feet on to concrete without any effect on performance. The circuit will also work perfectly at all temperatures from well below zero to above the boiling point of water.



**SINCLAIR RADIONICS LIMITED,**  
22 NEWMARKET ROAD, CAMBRIDGE  
Telephone OCA3-52731



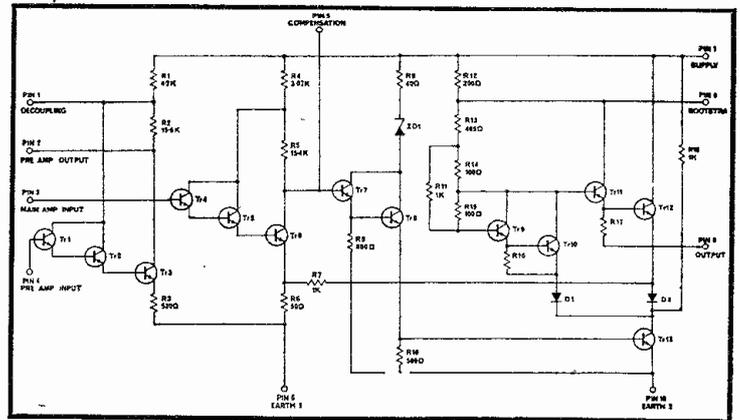
ABOVE SHOWS ACTUAL SIZE OF IC-10. TO RIGHT, VIEW OF AMPLIFIER MAGNIFIED 625 TIMES.


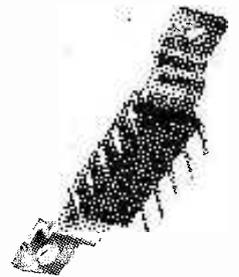
## ■ Applications

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity uses. These include public address, loud-hailers, use in cars, inter-com., stabilised power supplies, electronic organs, oscillators, volt meters, tape recorders, solar cell amplifier, radio receivers.

The transistors in the IC-10 have cut off frequencies greater than 500 MHz so the pre-amp section can be used as an R.F. or I.F. amplifier making it possible to build complete radio receivers without any additional transistors.



**SINCLAIR**  
**IC-10**

*The complete IC-10 with the manual and 5 year guarantee costs just*

**59¢**  
**POST FREE**

**ORDER FORM AND MORE SINCLAIR DESIGNS OVERLEAF**




# SINCLAIR Q.14

## low-priced high fidelity speaker

- Handles up to 14 watts
- 60-16,000 Hz
- 8 ohms impedance
- Ideal for IC-10 or Z.12

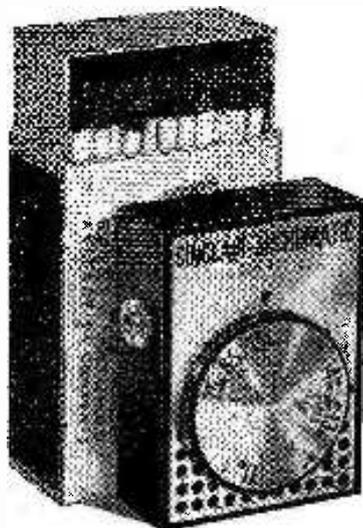**£7.19.6**


It costs a quarter of what you would expect to pay for a good stereo speaker system when you choose Q.14s. This is the result of research and experimentation in materials and careful design to make the Q.14 an instrument so outstandingly good that experts, reviewers and the public alike are unanimous in their praise for it. The Q.14 measuring only  $9\frac{3}{4}$ " square on its face by  $4\frac{3}{4}$ " deep. Its unusual contours permit it to be positioned where no ordinary speaker could be used to advantage. Black matt finish with aluminium bar trim keep this speaker pleasantly in conformity with modern design trends.



# SINCLAIR MICROMATIC
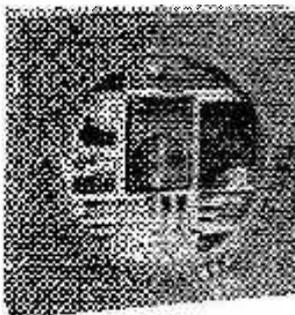
## the smallest radio set in the world

- $1\frac{4}{5}$ " x  $1\frac{3}{10}$ " x  $\frac{1}{2}$ "
- Tunes over medium waves
- Plays anywhere



The Sinclair Micromatic is available ready built or in kit form. This latter now comes in a convenient new presentation pack complete down to a generous free supply of solder. The moulded polystyrene interior enables you to check the contents in an instant, and helps to make building even easier and surer. Now, the Micromatic is better than ever—more powerful and better sounding to assure superb listening. Selectivity is better than many larger sets. Whether you build it, or buy your Micromatic ready built, it is the best and the smallest personal radio in the world—and it's British. In elegant aluminium fronted black case with slow motion tuning.


Complete kit inc. magnetic ear-piece and instructions. **49/6** Ready built & tested **59/6**

Mallory Mercury Cell RM.675 (2 needed) each 2/9.

# SINCLAIR Z.12
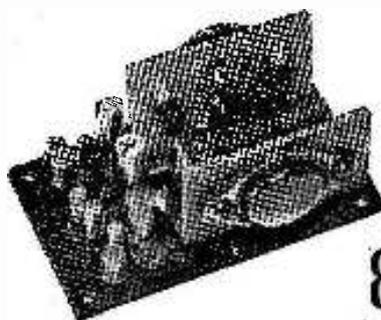
## INTEGRATED 12 WATT HI-FI AMP AND PRE-AMP

- Size  $3$ " x  $1\frac{3}{4}$ " x  $1\frac{1}{2}$ "
- Suitable for car battery operation
- For all high quality audio applications



**89/6**

15 to 50,000 Hz  $\pm 1$  dB, using ultralinear Class B output. Input sensitivity —2mV into 2k $\Omega$  OUTPUT—12 WATTS R.M.S. CONTINUOUS SINE WAVE (24 w. PEAK), 15 WATTS MUSIC POWER (30 w. PEAK). Suitable for 3-15 $\Omega$  loudspeakers. Two 3 $\Omega$  speakers may be used in parallel. **READY BUILT, TESTED AND GUARANTEED.**

# SINCLAIR PZ.4 STABILIZED POWER SUPPLY UNIT

A heavy duty A.C. mains power supply unit delivering 18 v. D.C. at 1.5A. Designed for Sinclair IC-10 or 4 assemblies using two Z.12s and stereo 25 unit. Ready built. **99/6** and tested.

ORDER FORM BRINGS PROMPT DELIVERY SENT TO YOU POST PAID

To: SINCLAIR RADIONICS LIMITED 22 NEWMARKET ROAD, CAMBRIDGE.  
Please send POST FREE

NAME.....  
ADDRESS.....

For which I enclose cash/cheque/money order.

PW.1268

### SINCLAIR GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full at once and without question. Full service facilities available to all purchasers.



SINCLAIR RADIONICS LIMITED  
22 NEWMARKET ROAD  
CAMBRIDGE OCA3-52731

# BI-PAK SEMICONDUCTORS

500 CHESHAM HOUSE,  
150 REGENT ST., LONDON, W.1.

**KING OF THE PAKS** Unequalled Value & Quality  
**SUPER PAKS** BRAND NEW—UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

PAK NO.	Description	Price
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 Watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1182	10/-
U12	12 Silicon Rectifiers EPOXY 500mA up to 800 PIV	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 2SL04	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ18 Type up to 600 PIV	10/-
U19	80 Silicon NPN Transistors like BC108	10/-
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	10/-
U21	30 A.F. Germanium alloy Transistors 2G800 Series & OC71	10/-
U22	10 1-Amp Glass Min. Silicon Rectifiers High Volts	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-Amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1 Amp SCR's TO-5 can up to 600 PIV CR51/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil. Planar NPN trans. low noise 2N8707	10/-
U32	25 Zener diodes 400mW DO-7 case mixed Vts. 3-18	10/-
U33	15 Plastic case 1 Amp silicon rectifiers W4000 series	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

### FULLY TESTED

AC107	3/6
AC128-7-8	2/6
AF116-117	3/6
AF139	10/-
AL102	15/-
BC107-3-9	5/-
BFY60-51-52	7/6
BSY26-7	3/6
BSY28-9	4/6
BSY96-95A	4/6
OC22-25	5/-
OC28-35	7/6
OC28-29	7/6
OC44-45	1/9
OC71-81	1/8
OC72-75	2/6
OC81D-82D	2/6
OC82	2/6
OC140	5/-
OC170	2/6
OC171	3/6
OC201	7/6
OPF12-60	8/6
OCF71	8/6
OA5-10	1/9
OA47	2/-
OA70	1/3
OA79	1/9
OA81-85	1/8
OA91	1/8
OA95	1/9
OA200	3/-
OA202	3/6
ON696-7	5/-
2N706	3/6
2N708	5/-
2N710	5/-
2N2646	15/-
2N2712	5/6
2N2926	2/6
MAT100-101	3/-
MAT120-121	3/6
ST140	3/-
ST141	4/-

### SIL. RECTS TESTED

PIV 750mA 3A 10A 30A	
50 1/- 2/9 4/3 9/6	50
100 1/3 8/3 4/6 15/-	100
200 1/8 4/- 4/9 20/-	200
300 5/8 4/6 8/6 25/-	300
400 2/6 5/6 7/6 25/-	400
500 3/- 6/- 8/6 30/-	500
600 3/3 6/9 9/- 37/-	600
800 3/6 7/6 11/- 40/-	800
1000 5/- 9/3 12/6 50/-	1000
1200 6/6 11/6 15/-	1200

### TESTED SCR's

PIV 1 AMP 7A 16A 30A	
25 25 7/6 80/-	25
50 7/6 8/6 10/6 35/-	50
100 8/6 10/- 15/- 45/-	100
200 12/6 15/- 20/- 55/-	200
300 15/- 20/- 25/-	300
400 17/6 25/- 35/- 80/-	400
500 30/- 40/- 45/- 95/-	500
800 40/- 50/-	800

### INTEGRATED CIRCUITS

I.C. Operational Amplifier with zener output.  
**Type 701C.** Ideal for P.E. projects. 8 Lead TO-5 case. Full Data. Our Price 12/6 each. 5 off 11/- each. Large qty prices quoted for.  
**Fairchild Epoxy TO-5 8 Lead. I.C.**  
uL900 Buffer 10/6  
uL914 Dual Gate 10/6  
uL923 J.K. Flip-Flop 14/-  
I.C. Data Circuits etc. 1/8  
Mullard I.C. Amplifiers  
TAA243 ORP.AMP. 70/-  
TAA263 Min AF Amp 18/6  
TAA293 G.P. Amp 26/-  
RCA CA3020 Audio Amp 30/-

### PRINTED CIRCUITS

**EX-COMPUTER**  
Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/- Plus 2/- P. & P.

### UNIUNION

U746, Eqt. 2N2646, 7/6	
Eqvt. TI843	

### FET's

2N3810	10/-
2N3820	25/-

### AD161-162 NPN-PNP Comp. Pair 12/6 pr.

2SO34..... 15/- ea.

### TRANSISTOR EQUIVALENT BOOK

52 pages of Cross References for transistors and diodes. Types include British, European, American and Japanese. Specially imported by BI-PAK 10/- each.

**PLEASE NOTE.**—To Avoid any further Increased Postal Charges to our Customers and enable us to keep our "By lined our Despatch Order Department and we now request you to send all your orders together with your remittance. Direct to our Warehouse and Despatch Department, postal address:—BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS. Postage and Packing 8411 1/- per order. Minimum Order 10/-.

# DUXFORD ELECTRONICS

97/97a MILL ROAD, CAMBRIDGE (PW)

CAMBRIDGE (0223) 63687

MINIMUM ORDER VALUE 5/-

C.W.O. Post and Packing 1/-

DISCOUNT 10% over £2  
15% over £5

**CERAMIC DISC CAPACITORS** (Hunts). 500V ±20%; 100, 220, 330pF -20% +80%; 470, 680, 1000pF, 5d. each.

**ELECTROLYTIC CAPACITORS** (Mullard). -10% to +50%.

Subminiature (all values in µF)					
4V	8	32	64	125	250
6.4V	6.4	25	50	100	200
10V	4	16	32	64	125
16V	2.5	10	20	40	80
25V	1.6	6.4	12.5	25	50
40V	1	4	8	16	32
64V	0.64	2.5	5	10	20
Price	1/6	1/3	1/2	1/-	1/1

Small (all values in µF)					
4V	800	1,250	2,000	3,200	5,000
6.4V	640	1,000	1,600	2,500	4,000
10V	400	640	1,000	1,600	2,500
16V	250	400	640	1,000	1,600
25V	160	250	400	640	1,000
40V	100	160	250	400	640
64V	64	100	160	250	400
Price	1/6	2/-	2/6	3/-	3/6

### POLYESTER CAPACITORS (Mullard)

Tubular 10%, 160V: 0-01, 0-015, 0-022µF, 7d. 0-033, 0-047µF, 8d. 0-068, 0-1µF, 9d. 0-15µF, 11d. 0-22µF, 1/-, 0-33µF, 1/3, 0-47µF, 1/6, 0-68µF, 2/3, 1µF, 2/8.  
400V: 1,000, 1,500, 2,200, 3,300, 4,700pF, 6d. 6,800pF, 0-01, 0-015, 0-022µF, 7d. 0-033µF, 8d. 0-047µF, 9d. 0-068, 0-1µF, 11d. 0-15µF, 1/2, 0-22µF, 1/6, 0-33µF, 2/3, 0-47µF, 2/8.  
Modular, metallised, P.C. mounting, 20%, 250V: 0-01, 0-015, 0-022µF, 7d. 0-033, 0-047µF, 8d. 0-068, 0-1µF, 9d. 0-15µF, 11d. 0-22µF, 1/-, 0-33µF, 1/3, 0-47µF, 1/6, 0-68µF, 2/3, 1µF, 2/9.

**POLYSTYRENE CAPACITORS:** 5%, 160V (unencapsulated): 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF, 5d. 1,000, 1,500, 2,200pF, 6d. 3,300, 4,700, 5,600pF, 7d. 6,800, 8,200, 10,000pF, 8d. 15,000, 22,000pF, 9d. 1%, 100V (encapsulated): 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820pF, 1/-, 1,000, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 4,700pF, 1/3, 5,600, 6,800, 8,200, 10,000, 12,000, 15,000pF, 1/6, 18,000, 22,000, 27,000, 33,000, 39,000pF, 1/9, 0-047, 0-056µF, 2/-, 0-068, 0-082, 0-1µF, 2/3, 0-12µF, 2/9, 0-15, 0-18µF, 3/-, 0-22µF, 4/-, 0-27, 0-33µF, 5/-, 0-39µF, 5/9, 0-47µF, 6/3.

**JACK PLUGS** (Screened): Heavily chromed, 1/4in. Standard: 2/9 each. Side-entry: 3/3 each. Standard (Unscreened): With black, grey, white, red, blue, green or yellow covers, 2/3 each.

**JACK SOCKETS** (1/4in. Plug): With black or white bezel and chrome nut, 2/9 each. Available with: Break/Break, Make/Break, Break/Make, Make/Make contacts.

**POTENTIOMETERS** (Carbon): Long life, low noise. 1W at 70°C. ±20% ≤ 1M, ±30% > 1M. Body dia., 1/4in. Spindle, 1/8in. × 1/4in., 2/3 each. Linear: 100, 250, 500 ohms, etc., per decade to 10M. Logarithmic: 5k, 10k, 25k, etc., per decade to 5M.

**SKELTON PRE-SET POTENTIOMETERS** (Carbon). Linear: 100, 250, 500 ohms, etc., per decade to 5M.

Miniature: 0-3W at 70°C. ±20% ≤ 1M, ±30% > 1M. Horizontal (0-7in. × 0-4in. P.C.M.) or Vertical (0-4in. × 0-2in. P.C.M.) mounting, 1/- each.

Submin. 0-1W at 70°C. ±20% ≤ 1M, ±30% > 1M. Horizontal (0-4in. × 0-2in. P.C.M.) or Vertical (0-2 × 0-1in. P.C.M.) mounting, 10d. each.

**RESISTORS** (Carbon film), very low noise. Range: 5%, 4-7 to 1MΩ 10%, 10Ω to 10MΩ.

1W (10%), 1 1/2d. (over 99, 1 1/2d.), 100 off per value 12/-  
1W (5%), 2d. (over 99, 1 1/2d.), 100 off per value 13/9  
1W (10%), 2d. (over 99, 1 1/2d.), 100 off per value 13/9  
1W (5%), 2d. (over 99, 2d.), 100 off per value 15/6

**SEMI-CONDUCTORS:** OA5, OA81, 1/9, OC44, OC45, OC71, OC81, OC81D, OC82D, 2/-, OC72, 2/3, OC170, OC171, 2/6, AF115, AF116, AF117, 3/-, OC73, 3/3, OC140, 4/3.

**SILICON RECTIFIERS** (0-5A): 170 P.I.V., 2/9. 400 P.I.V., 3/-, 800 P.I.V., 3/3, 1,250 P.I.V., 3/9, 1,500 P.I.V., 4/-.

**SWITCHES** (Chrome finish, Silver contacts): 3A 250V, 6A 125V. Push Buttons: Push-on or Push-off (with white, black, green or red buttons) 5/-, Toggle Switches: SP/ST, 3/3, SP/DT, 3/6, SP/DT (with centre position), 3/9, DP/ST, 4/3, DP/DT, 5/-.

**PRINTED CIRCUIT BOARD** (Vero).  
0-15in. Matrix: 3 1/2in. × 2 1/2in., 3/3. 5 1/2in. × 2 1/2in., 3/11. 3 1/2in. × 3 1/2in., 3/11. 5in. × 3 1/2in., 5/6.

0-1in. Matrix: 3 1/2in. × 2 1/2in., 4/-, 5in. × 2 1/2in., 4/6. 3 1/2in. × 3 1/2in., 4/6. 5in. × 3 1/2in., 5/3.

**RECORDING TAPE** (Finest quality MYLAR—almost unbreakable). Standard Play: 5in. 600ft., 7/6; 5 1/2in. 850ft., 10/6; 7in. 1200ft., 12/6. Long Play: 3in. 225ft., 4/-; 5in. 900ft., 10/6; 5 1/2in. 1200ft., 13/-; 7in. 1800ft., 18/-.

SEND S.A.E. for MAY, 1968 CATALOGUE

# Want to get going in a career as a technician? Join the Army

**2 years from now you could be earning over £15 a week, all found, as a qualified technician. Qualified in a career that'll set you up for life.**

If you're between 17 and 25 you can join the Army as a trainee technician and get started on a 15-month course in aircraft, electronics or instruments. About eight months after successfully completing the course, you'll get promotion to Corporal. And from there on it's up to you. The sky's the limit.

**The equipment** you'll be working with—whether it is radio transmitters, transceivers, closed-circuit T.V., gunfire control equipment or helicopters—is the most advanced of its kind anywhere. And you'll be training with it from the start.

**The pay** As a trainee technician you can get as much as £9 a week (clear) from the age of 17½—food and accommodation free. After about 15 months this rises to nearly £14 on passing a trade test and, after about 2 years and promotion to Corporal, to over £15. After that, there's every chance of more promotion and still more pay.

And don't forget that in the Army, besides moving fast in a worthwhile career, you've every opportunity for travel, action, sport and excitement, too!

**SEND OFF THE COUPON FOR ALL THE FACTS**

TO: ARMY CAREERS MP6(A), LANSDOWNE HOUSE,  
BERKELEY SQUARE, LONDON W.1  
*Please send me full details of how to become a technician.*

NAME.....

ADDRESS.....

TOWN.....

COUNTY.....

DATE OF BIRTH.....

(You must be resident in the UK) M70994102

# S-DeC BREADBOARDING

- Fast, reliable, solderless circuit assembly
- Contacts last indefinitely
- Use ordinary components again and again
- Test *all* the circuits in the magazines

This breadboard is used professionally by development engineers throughout the world. Over 80% of current production is exported.

A booklet of projects is included with each kit giving construction details for a variety of circuits such as amplifiers, oscillators, VHF transmitter, radio, etc.

**S-DeC Kit:** One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "S-DeC Projects" giving construction details for a variety of circuits. 29/6d retail.

**4-DeC Kit:** Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "S-DeC Projects" all contained in a strong, attractive, plastic case. Ideal for the professional user. £5.17.6 retail.

AVAILABLE FROM LEADING SUPPLIERS

or in case of difficulty from

**S.D.C. PRODUCTS (Electronics) LTD**

THE CORN EXCHANGE, CHELMSFORD, Essex

Telephone: Chelmsford (OCH 5) 56215



We put  
**23,340**  
cigarettes

in our Budget  
combination storage  
unit!

Think what you could  
put in it!

Storage. Lots of it, for a thousand things you stock; replacement parts; light bulbs; cameras; anything up to 7 x 8 x 10½ in. Safety drawer-stops as 'standard'. Smooth guide runners thro'out. All in a compact 3ft. 6in. high, 2ft. 11in. wide, 1ft. deep area. Ready assembled, in stove enamelled green or grey. With 18 handy, 6 large, 8 king-sized drawers. At £15 19s. worth every penny! See the rest of the N. C. Brown range!



£15.19s

BRAND NEW  
range from  
on mail order



**N.C. BROWN LTD.**


pacesetters in storage equipment

Send your FREE BROCHURE  or Send  (how many) Budget Storage Units at £15. 19s. In green or grey.

NAME .....  
ADDRESS .....  
Dept. PW Eagle Steelworks, Heywood, Lancs. Tel: 69018  
London: 25-27 Newton St., W.C.2. Tel: 01-405 7931

# FREE! Handyman's reference booklet

in a durable wallet for constant use!

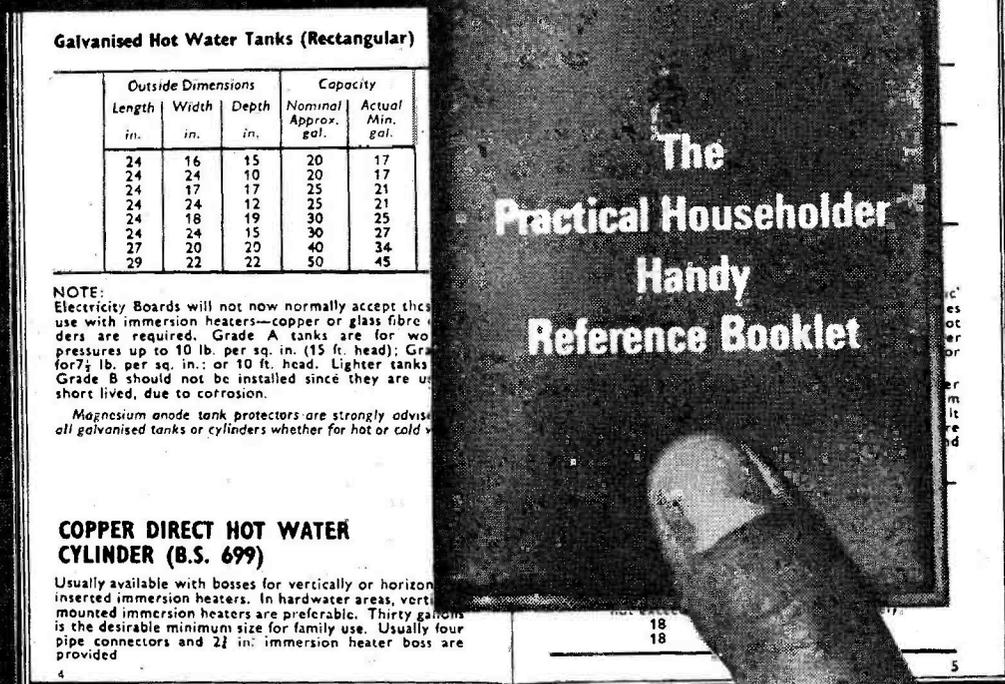

16 pages packed with the at-a-glance data that every handyman needs, including tabulated details for piping, plumbing, water tanks and cisterns—spreading capacities of paints and distempers—wallpaper measurements—concrete facts and figures—floor tiles—wood screw gauges—timber sizes—fuel storage space. Complete in a neat open-flat wallet with transparent cover for easy reference. It will give vital information on many jobs around the house. Get yours in PRACTICAL HOUSEHOLDER now!

**Plus** HOW TO ADD £1,000 TO THE VALUE OF YOUR HOUSE. More ideas to bring your home into the luxury class—including how to transform an old-type fireplace into a stylish contemporary affair... how to give your kitchen the full modernising treatment.

**PRACTICAL HOUSEHOLDER** DECEMBER

OUT NOW 2/-

# TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets and Manufacturers' Manuals for most makes and types of Radios, Tape Recorders and Televisions.

Please complete order form below for your Service Sheet to be sent by return. To:

## OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND LONDON WC2

Make	Model	Radio/TV

1968 List available at 2/- plus postage

If list is required indicate with X

From .....  
Address .....

enclose remittance of .....  
(and a stamped addressed envelope)  
s.a.e. with enquiries please  
**MAIL ORDER ONLY (December PW)**

**NEW! EXCITING! ADD STEREO EFFECTS**



**TO YOUR LISTENING...**

with a Dewtron "NEW DIMENSIONS" 3-Dimensional effects amplifier. Gives Big Hall Stereo effect to any radio, tape, etc. PLUS fully adjustable echo, vibrato and tone. 9 volt model, 8 gns. Speaker, 25/- extra. 6/12V car model, 10 gns. incl. speaker. Post and ins. 5/- either model. Write now—right now.

D.E.W. LTD.,  
P.W., RINGWOOD ROAD, FERNDOWN, DORSET

**PLEASE MENTION "PRACTICAL WIRELESS" WHEN REPLYING TO ADVERTISEMENTS**

### EAGLE MULTIMETERS

EP30K, 120/-, p.p. 4/6; EP10KN, 108/-, p.p. 4/6; EP20KN, 90/-, p.p. 3/-; EP30KN, 150/-, p.p. 4/6; EP50LN, 210/-, p.p. 4/6, details on request.

High Stability Resistors 1%  $\pm$ W, 2/- Full standard range plus many multimeter values. 5%  $\pm$ W, 4d. Full stock list on request.

0-50 microamp level meters, 15/-, post 1/-.

High Res. Phones, 2,000  $\Omega$ , 15/-, p.p. 1/-.

Multimeter ITI-2, 20,000 o.p.v. d.c., 0-5, 25, 50, 250, 2,500V d.c., 10, 50, 100, 500, 1,000V a.c.; 0-50  $\mu$ A, 0-2.5mA, 250mA; 0-60k $\Omega$ , 0-6M $\Omega$  capacity and dB ranges, 87/-, post 3/-.

Postage extra, cash with order.

**PLANET INSTRUMENT CO.**  
25(W) DOMINION AVENUE, LEEDS 7


Est. 1943 **JOHNSONS** Tel: 24864

VHF and Short-Wave kits for the Amateur enthusiast and constructor. For 2 and 4 metres, the unique two transistor model SR2/P, 70-150Mc/s, 69/6, p.p. 4s. New super 5V all-wave, all-band kit, also "Mini-Amp" self-contained, cabinet, size a mere 4½ x 3½ x 2½. Write today, enclosing a stamped addressed envelope for interesting free literature, and details, direct to

**JOHNSON'S (RADIO)**  
St. Martin's Gate, Worcester

# YOURS FREE FOR 7 DAYS
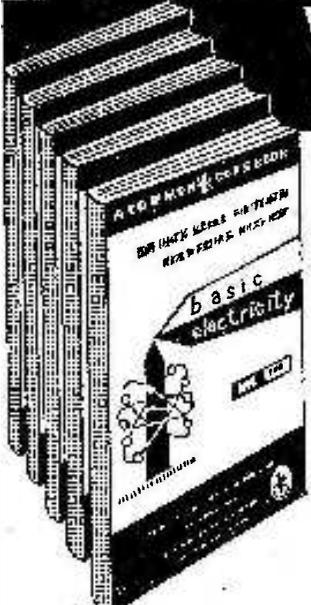
## The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)



You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

**TO TRY IT, IS TO PROVE IT**

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

**WHAT READERS SAY**

"May I take this opportunity to thank you for such enlightening works and may I add, in terms, easily understood by the novice." L. W. M., Birmingham.

"I find that the new pictorial method is so easy to understand, and I will undoubtedly enjoy reading the following five volumes: thank you for a wonderful set of books." C. B., London.

"Please accept my admiration for producing a long felt want in the field of understanding Electronics." S. B. J., London.

"The easiest set of manuals it has been my pleasure to study." J.P.P., Taunton.

A TECH-PRESS PUBLICATION

**POST NOW FOR THIS OFFER!!**

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 15/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY  BASIC ELECTRONICS

Prices include Postage and Packing.

Signature .....  
(If under 21 signature required of parent or guardian)

NAME .....  
BLOCK LETTERS

FULL POSTAL ADDRESS .....

# BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government

38 CHALCOT ROAD, LONDON, N.W.1

Telephone Primrose 9090

ALL GOODS LISTED BELOW, ACTUALLY IN STOCK, ALL GOODS ARE NEW, BEST QUALITY MANUFACTURE ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE, PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS & REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE.

0A2	6/-	6D3	7/6	12A66	7/6	78	4/9	DL92	4/9	RF89	4/9	LZ329	6/6	R16	34/11	VU120	12/-	BA129	2/6	OA81	1/9
0B2	6/-	6D6	3/-	12A76	4/6	35A2	8/6	DL94	5/6	RF91	3/8	MHD4	8/3	R17	17/6	VU120A12/-		BA130	2/-	OA85	1/6
0Z4	4/3	6E5	7/6	12A77	3/9	90AG	87/6	DL96	7/-	RF92	2/6	MHL4	12/6	R18	9/6	VU133	7/-	BCY10	5/-	OA86	4/6
1A3	4/6	6F1	8/9	12A78	4/9	90AV	67/6	DL98	9/6	RF94	5/6	MHLD6	7/6	R19	6/6	W42	10/6	BCY12	5/-	OA90	2/6
1A5	5/-	6FG	4/-	12A79	4/6	90CG	34/-	DM70	6/-	RF95	4/6	MU12/14/4		RK34	7/6	W61M	24/6	BCY33	4/6	OA91	1/9
1A7GT	7/6	6FGM	12/6	12A80	4/6	90CV	33/6	DM71	7/6	RF97	10/-	MX40	12/6	SPI3C	12/6	W63	10/6	BCY34	5/6	OA182	3/6
1CL	5/6	6F12	3/3	12A81	6/-	90C1	16/-	DW4	350	RF98	10/6	N78	33/4	SP42	12/6	W76	5/9	BCY38	5/6	OA200	1/-
1C2	7/9	6F13	3/6	12A82	4/6	150B2	14/6	DW4/500		EF183	5/6	N108	26/7	SP61	3/3	W77	2/6	BCY39	4/6	OA202	2/-
1C3	7/-	6F14	15/-	12A83	9/9	150C2	6/-			EF184	5/9	N152	7/3	TDD4	3/3	W78M	6/6	BCZ11	3/6	OA210	9/6
1C5	4/9	6F15	9/6	12BA6	6/-	161	15/-			EF804	20/5	N339	25/-	TH4B	10/-	W101	26/2	BC107	4/6	OA211	13/6
1D5	6/9	6F17	12/6	12BE6	5/9	185BT	35/-	DY86	5/9	EH90	6/8	N359	7/3	TH233	7/-	W107	7/-	BC108	3/6	OA2200	12/6
1D8	9/6	6F18	7/6	12BH7	6/-	301	20/-	DY87	5/9	EL32	3/8	P61	2/6	TP22	5/-	W729	10/-	BC109	4/6	OA2201	12/6
1FD1	6/-	6F23	12/3	12E1	17/-	302	16/6	EB0F	24/-	EL33	12/-	PABC80	7/8	TP25	5/-	X24	16/6	BC113	5/-	OA2202	9/6
1FD9	3/9	6F24	11/9	12F5GT	2/6	303	15/-	EB3F	24/-	EL34	9/6	PC86	9/6	TP2620	3/9	X41	10/-	BC115	3/6	OA2203	9/6
1G6	6/-	6F25	11/9	12G7GT	6/6	305	16/6	EB8CC	12/-	EL35	10/-	PC88	9/6	TY36F	12/2	X61	5/9	BC116	5/6	OA2204	9/6
1HSGT	7/-	6F28	10/6	12K5	10/-	306	13/-	E180CC	8/-	EL36	8/6	PC95	8/3	UAF42	9/6	X64	12/6	BC118	4/6	OA2205	9/6
1L4	2/6	6F32	3/-	12K7GT	5/9	807	11/9	E180F	17/6	EL37	17/3	PC97	7/9	UBA4	6/6	X65	5/-	BD119	9/6	OA2206	9/6
1LD5	5/-	6G6G	2/6	12K8GT	7/6	956	2/-	EA50	1/6	EL41	9/3	PC900	8/3	UBC41	7/6	X66	7/6	BFY50	4/6	OA2207	10/6
1LN5	5/-	6H6GT	1/9	12Q7GT	8/9	1821	10/6	EA76	13/-	EL42	9/9	PC84	6/-	UBC81	7/-	X67M	7/6	BFY51	4/6	OA2210	7/6
1N8GT	7/9	6J5G	3/9	12S4GT	4/6	5783	10/6	EABC80	6/-	EL43	8/6	PC85	6/6	UBF80	5/9	X81M	29/1	BFY52	4/6	OA2213	7/6
1P1	7/6	6J5GT	4/6	12S7GT	4/6	6060	5/6	EA91	3/6	EL44	8/6	PC88	9/6	UBF89	6/9	X101	29/1	BF159	5/6	OA2214	7/6
1P10	4/9	6J6	3/6	12S8GT	4/6	7193	10/6	EA94	2/6	EL45	7/6	PC89	9/6	UBL21	2/6	X109	29/1	BF163	4/6		
1P11	5/6	6J7G	4/9	12S9GT	4/6	7475	4/-	EB4	4/6	EL46	8/6	PC89	9/6	UC92	5/6	Y63	5/-	BF167	2/6		
1R5	5/6	6K7GT	6/6	12S9GT	4/6	A1834	20/-	EB41	7/6	EL47	9/3	PC90	8/6	UC92	5/6	Y65	5/-	BF173	2/6		
1S4	1/6	6K8GT	5/6	12S9GT	4/6	ACO44	14/-	EB91	2/6	EL48	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF180	13/6		
1R5	3/9	6K7G	2/6	12S9GT	4/6	AC2PEN		EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
1T4	2/9	6K7GT	4/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
1U4	5/9	6K8G	3/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
1U5	5/3	6K8GT	7/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
2A7	12/6	6L6GT	7/9	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
2D13C	7/-	6L1	19/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
2D21	5/6	6L18	5/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
2X2	4/9	6L19	5/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
2A4	3/6	6L20	6/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
3A5	10/-	6NDT	8/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
3B7	5/-	6P1	12/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
3D6	3/9	6P25	12/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
3Q4	6/6	6P26	12/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
3QSGT	6/-	6P28	12/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
3E4	4/9	6Q7G	9/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
3V4	5/6	6Q7GT	8/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
4D1	3/9	6R7G	7/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
5R4GY	8/9	6S4GT	7/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
5U4G	4/9	6S4GT	7/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
5V4G	7/6	6S4GT	7/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
5Y3GT	5/6	6S7G	3/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
5Z3	3/-	6S7G	3/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
5Z4G	6/9	6S7G	3/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6/30L2	12/6	6SK7GT	4/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6A8G	5/6	6SL7GT	4/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6A9G	3/6	6SN7GT	4/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AG7	5/9	6S87	3/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6A75	3/6	6U4GT	12/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AK5	4/6	6U5G	5/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AK6	6/6	6U7G	7/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AK8	6/6	6V6G	3/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AL5	2/3	6V6GT	6/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AM4	16/6	6X4	3/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AM5	2/6	6X5GT	12/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AM6	3/3	6Y7G	12/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AQ5	4/9	7A7	12/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AR6	20/-	7AN7	6/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AT6	4/-	7B6	10/9	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AU6	5/-	7B7	7/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6AV6	5/6	7C6	6/6	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-	BF185	8/6		
6B8G	2/6	7D6	15/-	12S9GT	4/6	AC2PEN	19/6	EB91	2/6	EL49	8/6	PC92	8/6	UC92	5/6	Y65	5/-				

# TECHNICAL TRAINING

## in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

## POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS


12/68

INTERNATIONAL CORRESPONDENCE SCHOOLS
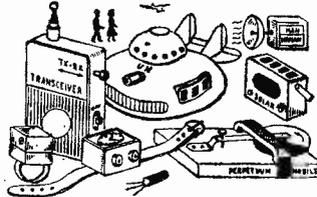
## PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Match-box Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Snipcut. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.




### EXPERIMENTER'S PRINTED CIRCUIT KIT 8/6

Postage & Pack. 1/6 (UK)  
Commonwealth:  
SURFACE MAIL 2/-  
AIR MAIL 8/-  
Australia, New Zealand  
South Africa, Canada.

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photo-cell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 design yet offered to the Home Constructor anywhere in the World. (10) 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (11) Postage Stamp Radio. Size only 1.62" x .95" x .25". (12) Wristwatch Radio 1.15" x .80" x .55". (13) Ring Radio 70" x 70" x .65". (14) Bacteria-powered Radio. Runs on sugar or bread. (15) Radio Control Receiver. (16) Transistor P/P Amplifier. (17) Intercom. (18) 1-valve Amplifier. (19) Bell. (20) Ultrasonic Switch Alarm. (21) Guided Missile. (22) Perpetual Motion Machine. (23) Metal Detector. (24) Transistor Tester. (25) Human Body Radiation Detector. (26) Man/Woman Discriminator. (27) Signal Injector. (28) Pocket Transceiver (Licence required). (29) Constant Volume Intercom. (30) Remote Control of Models by Induction. (31) Inductive-Loop Transmitter. (32) Pocket Triple Reflex Radio. (33) Wristwatch Transmitter/Wire-less Microphone. (34) Wire-less Door Bell. (35) Ultrasonic Switch Alarm. (36) Stereo Pre-amplifier. (37) Quality Stereo Push-Pull Amplifier. (38) Light-Beam Telephone "Photophone". (39) Light-Beam Transmitter. (40) Silent TV Sound Adapter. (41) Ultrasonic Transmitter. (42) Thyristor Drill Speed Controller.
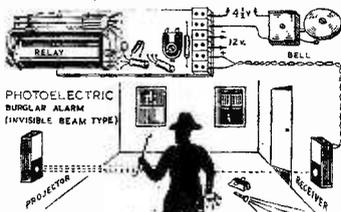
## PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Condensers, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



### PHOTOELECTRIC KIT 39/6

Postage and Pack. 2/6 (UK)  
Commonwealth:  
SURFACE MAIL 3/6  
AIR MAIL £1.0.0  
Australia, New Zealand,  
S. Africa, Canada and U.S.A.  
Also Essential Data Circuits  
and Plans for Building

12 PHOTOELECTRIC PROJECTS. (1) Steady-Light Photo-Switch/Alarm. (2) Modulated-Light Alarm. (3) Long-Range Stray-Light Alarm. (4) Relay-less Alarm. (5) Warning-Tone Alarm. (6) Closed-Loop Alarm. (7) Projector Lamp Stabiliser. (8) Electronic Projector or Main Power Switch. (9) Main Power Switch. (10) Car Parking Lamp Switch. (11) Automatic Headlamp Dipper. (12) Super-Sensitive Alarm.

### INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, performance data, etc. Price 19/6. Postage and Pack. 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

### JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc. for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (UK). Commonwealth 2/-; Air Mail 4/-.

### JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver. Price 10/6. Postage and Pack. 1/6 (UK). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

### PHOTOELECTRIC PARKING LAMP SWITCH

Turns your light on at dusk, off at dawn, automatically. Never forgets. Protects your car. Saves the Battery. Miniature construction. Simply user: in the parking lamp lead. Price: 27/6. Post & Packing (U.K.) 2/6 (12 volts only).

### ELECTRONIC MAINS LAMP DIMMER

Varies lamp brightness from nothing to full 100 watt maximum. Ideal for Parties, TV watching, Children's bedroom etc. Just mount on the wall in place of on-off switch. Price: 59/6. Post & Packing 2/6.

## YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

## DRY JOINT TESTER

The most reliable way of testing for a dry joint is to measure the resistance between the component lead and the printed circuit board. Our kit for doing this comprises a large scale (3in.) moving coil meter, a variable resistance for adjusting zero setting, and a wiring diagram with instructions. The only additional items you will need are a battery, some wire, a pair of test rods. Price 19/6, postage and insurance 2/6.

## MINIATURE WAFER SWITCHES

4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment.



## WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 10/- post free.

## BLANKET SWITCH

Double pole with neon let into side so luminous in dark, ideal for dark room light or for use with waterproof element—new plastic case. 5/6 each. 3 heat model 7/6.



## PHOTO-ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit. Laminated Boards and chemicals. Latching relay. Infra-red sensitive Photocells and Hood, 2 transistors, cond., terminal block. Plastic case. Essential data, circuits and P.C. chassis plans of 10 photo-electric devices including auto. car parking light, modulated light alarm, simple invisible ray switch—counter—stray light alarm—warbling tone electronic alarm—project lamp stabiliser, etc., etc. Only 39/6, plus 2/- post and insurance.

**PP3 ELIMINATOR.** Play your pocket radio from the mains! save 5s. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions, only 6/6 plus 1/- post.



## BECKASTAT

This is an instant thermostat, simply plug your appliance into it and its lead into wall plug. Adjustable setting for normal air temperatures. 13A loading. Will save its cost in a season 19/6. Post and ins. 2/9.



## KETTLE ELEMENT

230/240V 1500 watt. Made by Best for kettles with 9/16 in. dia. hole including: Best, Besco, Chalfont, Davidson, Dimplex, Grafton, Hawkins, Jurymaid, Morroware, Monogram, Pifco, Revco, Towen, Swan, Normality 32/6. Our price 15/- plus 2/6 post.



## QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. 19/6, post and insurance 1/6. 12v. car model also available.



## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

## THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knobs. Quickly adjustable from 30-30°F. 9/6 plus 1/- post. Suitable box for wall mounting, 5/-, P. & P. 1/-.

Type "B" 15 amp. This is a 17in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-550°F. Internal screw alters the setting so this could be adjustable over 30° to 1000°F. Suitable for controlling furnace, oven kiln immersion



heater or to make flame-start or fire alarm, 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point, 2/8 amps. Has many uses one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (16 yds. 10/-) is wound round the pipes. 7/6. P. & P. 1/1.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 7/6, plus 1/- post.

Type "F". Glass encased for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/-, plus 2/- post and insurance.




## DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance. Or available made up 25/-, plus 2/6 post.



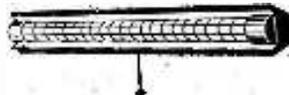
## INFRA-RED HEATERS

Make up one of these latest type heaters. Ideal for bathroom, etc. They are simple to make from our easy-to-follow instruction—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watts element, all parts, metal casing, as illustrated, 19/6, plus 4/- post and insurance. Pull switch 3/- extra.



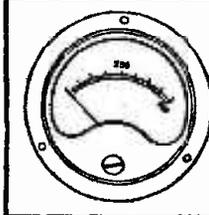
## 2 1/2" MOVING COIL METER

Meters are always being needed and they are jolly costly when you have to buy them in a hurry. So it's sensible to take advantage of this offer: 2 1/2in. (3" o.d.) flush mounting moving coil meters only 8/6 each. These are scaled 0-300mA. but once the internal shunt is removed the i.s.d. is usually about 10mA so you can make it into almost anything by adding shunts or series resistors. These are Ex. W.D. of course but are all new and unused. Price only 8/6 each plus 2/6 post. 12 or more post free.



## FLUORESCENT LIGHTING SNIP

### THE TWENTYLITE

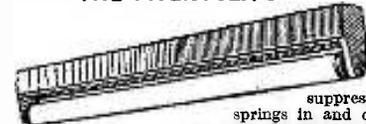

A Fluorescent lighting unit made by the famous Atlas company, with super silent polyester filled choke and radio suppressed starter. The tube springs in and out and the whole unit is beautifully made and finished white enamel. Amazingly economical. If left on all the time costs only one penny per day (uses 1/2 unit). Measures 2ft. long. Is ideal in Kitchen, Bedroom, Hallway, Porch, Loft, etc. Don't miss this amazing offer, 39/6 with tube. Assembled ready to install. Postage and Insurance 6/6 extra.

## THIS MONTH'S SNIP

### TIMED SWITCH

For keeping an electrical circuit closed for a time period of up to ten minutes. Made by a very famous company for switching washing machines, but equally suitable for any appliance lamp or heater up to 13 amp. Special snip price 9/6 post free if ordered with other lightweight items totalling £5. Otherwise add 2/9 post and insurance.

## HI FI BARGAIN

**FULL FI 12 INCH LOUDSPEAKER.** This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address.

Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S.—Cone Moulded fibre—Freq. response 30,10,000 c.p.s.—specify 8 or 15 ohms—Main resonance 60 c.p.s.—Chassis Diam. 12in.—12 1/2in. over mounting lugs—Baffle hole 11in. diam.—Mounting holes 4, holes 1/2in. diam. on pitch circle 1 1/2in. diam.—Overall height 5 1/2in. A £6 speaker offered for only £8.98 plus 7/6 p & p. Don't miss this offer.



## BATTERY OPERATED TAPE DECK

With Capstan control. This unit is extremely well made and measures approx. 6 x 5 x 2in. deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4 1/2 volts. Supplied complete with 2 spools ready to install. Record, Replay head is the sensitive M4 type intended for use with



transistor, amplifier. Price 89/6. Post and insurance 4/6.

## BARGAIN OF THE YEAR

### MICRO-SONIC

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2in.—complete with soft leather zipped bag. Specification:—Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency: 465 Kc/s, or 455 Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type.

In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new, 19/6 plus 2/6 post and ins., less batteries. Everlasting batteries 7/- pair.



Spring coil leads as fitted to telephones, 4 core 2/6 each. 3 core 2/- each.

**Indicator lamp.** Panel mounting, consists of neon lamp in red plastic lens with resistor in leads for mains operation. 2/8 each. 24/- dozen.

**Appliance switch double pole 16A 230v rating** spindle for pointer knob control, 3/6.

**0005 tuning condenser for crystal or transistor radio, 24/- dozen.**

**16mm Zoom Lens** for closed circuit TV camera, brand new, £7.5 (Half current price list.)

**Bulkhead Aerial lead** out two cone shaped porcelain insulators with OBA brass rod through centre fitted terminals 9/6.

**18V Blower heavy duty motor** with centrifugal blower coupled to one end, ideal for car heater, 12/6, plus 4/6 post.

## COPPER CLAD ELEMENT

1250 watts—4ft. long but bent to U shape, ideal for overhead heater—just mount reflector above 12/6 each, plus 4/6 post. £6 doz. post paid.

## BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching the blanket on for varying time periods, thus giving a complete control from off to full heat. Also suitable for controlling the temperature of any other appliances using up to 1 amp. Listed at 27/8 each, we offer these while our stock lasts at only 12/6 each.

0-1mA Full Vision Moving Coil Meter. 2in. sq. full vision. 19/6 plus 2/- post.

0-500mA 3in. Flush Mounting Moving Coil Meter 10/-.

**G.E.C. Black Light Tube** for experiments and special lighting effects—40 watt 2ft. tubes only 14/6 each, holders and control gear 19/6 plus 4/6 post.

You never need buy another battery for your transistor radio. Stupendous offer this month—a 6-9V Nickel Cadmium battery stack together with a mains operated charger which you mount on the back of your set. The mains flex unplugs so the set remains completely portable. Offered for less than the cost of the batteries alone. ONLY 29/6 plus 3/6 post.

Experimenting with Ultra Violet? Philips UV lamp 16/6, holder and control gear 19/6 plus 4/6 post. Double pole push to test switch. Spring return 10 amp. 250V. 2/9 each. 30/- doz.

**A.E.I. FRACTIONAL H.P. MOTOR.** 200/250v. 50/60 c.p.s. enclosed, continuous rating 1/40 h.p., ex. equipt. Perfect order 19/6 plus 4/6.

## FLUORESCENT CONTROL KITS


Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. 19/6. Kit B—30-40 w. 19/6. Kit C—80 w. 19/6. Kit D—125 w. 22/-. Kit E—85 w. 19/6. Kit MF1 is for 6in., 9in. and 12in. miniature tubes, 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MF1 8/6 on first kit then 3/6 on each two kits ordered.

## REED SWITCH

Suitable for dozens of different applications, such as burglar alarms, conveyor belt switching. These are simply glass in cased switches which can be operated by a passing permanent magnet coil. A special buy enables us to offer these at 2/6 each, or 24/- a dozen. Suitable magnets are 1/- each.
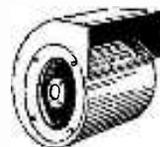
## CENTRIFUGAL FAN

**CENTRIFUGAL BLOWER** or extractor by Torrington, very low noise but large capacity air flow, designed for central heating and air conditioning; ideal also for fume extraction over cooker, duct type outlet, 200-250 v. 50 C.F.S. motor. £3.19.6. post and insurance 7/6.



## 16 RPM GEARED MOTOR

Made by Smith's Electrics, these are almost silent running, but are very powerful. They operate from normal to 240V. mains and the final shaft speed is 16 r.p.m. 15/-, Post & ins. 2/9.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

# ELECTRONICS (CROYDON) LIMITED

(Dept. P.W.) 266 LONDON ROAD, WEST CROYDON CRO 2TH

also at 102/3 TAMWORTH ROAD, CROYDON, SURREY

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 2s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL WIRELESS, George Newnes Ltd., 15/17 Long Acre, London, WC2, for insertion in the next available issue.

## SERVICE SHEETS

SERVICE SHEETS. RADIO, TV. 5,000 Models. List 1/6. S.A.E. Enquiries. TELRAY, 11 Maudland Bank, Preston, Lancs.

SERVICE SHEETS. RADIO, TELEVISION, TAPE RECORDERS, 1925-1968 by return post, from 1/- with free fault-finding guide. Catalogue 6,000 models 2/6. Please send stamped addressed envelope with all orders/enquiries. HAMILTON RADIO, 54w London Road, Bexhill, Sussex.

SERVICE SHEETS (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. THOMAS BOWER, 5 South Street, Oakenshaw, Bradford.

RADIO, TELEVISION over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

## C. & A. SUPPLIERS

### SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS)

Only 5/- each, plus S.A.E.

(Uncrossed P.O.'s please, returned if service sheets not available.)

71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post) Please state make and model number alternative.

Mail order only.

SERVICE SHEETS—Radio, T.V., Players, Grams., Tape Recorders, from 1/- . Send for lists 1/- (s.a.e.). Fountain Press, 46-47 Chancery Lane, London, W.C.2.

## EDUCATIONAL

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV., automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. CHAMBERS COLLEGE (Dept. 857K), 148 Holborn, London, E.C.1.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

## EDUCATIONAL

(continued)

### TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541, INTERTEXT HOUSE, LONDON, SW11

(continued page 637)

## BOOKS & PUBLICATIONS

### SURPLUS HANDBOOKS

19 set Circuit and Notes .. 6/6 p/p 6d.  
1155 set Circuit and Notes .. 6/6 p/p 6d.  
H.R.O. Technical Instructions .. 5/6 p/p 6d.  
38 set Technical Instructions .. 5/6 p/p 6d.  
46 set Working Instructions .. 5/6 p/p 6d.  
88 set Technical Instructions .. 7/- p/p 6d.  
BC.221 Circuit and Notes .. 5/6 p/p 6d.  
Wavemeter Class D Tech. Instr. .. 5/6 p/p 6d.  
18 set Circuit and Notes .. 5/6 p/p 6d.  
BC.1000 (31 set) Circuit and Notes .. 5/6 p/p 6d.  
CR.100/B.28 Circuit and Notes .. 10/- p/p 9d.  
R.107 Circuit and Notes .. 7/- p/p 6d.  
AR.88D Instruction Manual .. 18/- p/p 6d.  
62 set Circuit and Notes .. 6/6 p/p 6d.  
Circuit Diagram 5/- each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 set.  
52 set Sender and Receiver circuits 7/6 post free

Resistor colour code indicator 2/6 p/p 6d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

### INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,  
28 TALBOT GARDENS, LEEDS 8

## WANTED

### WANTED NEW VALVES ONLY

Must be new and boxed  
Payment by return

WILLIAM CARVIS LTD  
103 North Street, Leeds 7

WANTED: New valves, transistors etc.; state prices. E.A.V. Factors, 202 Mansfield Road, Nottingham.

## WANTED

(continued)

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S WIRELESS STORES, 55 Worcester Street, Wolverhampton.

WANTED: Popular Brand New Valves. R.H.S. Stamford House, 538 Great Horton Road, Bradford 7.

DAMAGED Avo Meters, Models 7 and 8, Damaged Meggers, any quantity. Send for packing instructions. HUGGETT'S LTD., 2/4 Pawson's Road, West Croydon.

VALVES WANTED, brand new popular types boxed. DURHAM SUPPLIES, 367c, Kensington Street, Bradford 8, Yorkshire.

WANTED NEW VALVES, televisions, radiograms, transistors, etc. STAN WILLETTS, 37 High Street, West Bromwich, Staffs. Tel: WES 0186.

WE BUY New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

## ELECTRICAL



Run all your transistor equipment direct from A.C. mains.

The most economical way of running Transistor Radios, Hi-Fi Equipment, Record-Players, amplifiers etc. No more expensive batteries to buy. All the units are contained in an attractive case with a full set of accessories.

Mk 1 Model—replaces all 9 volt batteries, i.e. PP3, PP4, PP5, PP6, PP7, PP9 and all equivalents, or all 6 volt batteries, i.e. PP1 and PP8. (Please state which voltage). Now only 30/-, p.p. 7/6. Mk. 2 Model. This unique model has three outputs—6 volts, 7½ volts and 9 volts and is ideal for cassette tape-recorders, price only 55/-, p.p. 5/- . Extra lead with DIN plug for Cassettes 6/6. Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

Mark III. This unit is the same as the Mk. 2 version above with the added refinement that all the outputs are STABILISED making the unit most suitable for running Hi-Fi and Test Gear direct from the mains. Only 75/-, p.p. 5/- . All units available from dept PW, Globe Scientific Ltd, 22-24 Cawoods Yard, Mill St, Leeds 9.

## ELECTRICAL (continued)

**240 VOLT  
ELECTRICITY  
ANYWHERE**



**MOST BRILLIANT PERFORMANCE EVER**  
from 12 volt Car Battery

**BRILLIANT HEAVY DUTY 240 volt AMERICAN DYNAMOTOR** with BIG 220 WATT OUTPUT. Marvellous for TELEVISION, ELECTRIC DRILLS, MAINS LIGHTING and ALL UNIVERSAL AC/DC MAINS EQUIPMENT. Marvellous for Fluorescent lighting. Thousands of uses. Tremendous purchase of this model makes fantastically low price possible.  
ONLY £4.19.6 each plus 10/6 delivery. C.O.D. with pleasure. **MONEY BACK** if not DELIGHTED. Please send s.a.e. for full illustrated details. (Dept. PW) **STANFORD ELECTRONICS** Rear Derby Road, North Promenade, BLACKPOOL, Lancs.

## MISCELLANEOUS

**BUILD IT** in a DEWBOX quality cabinet. 2in. x 2½in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**RHYTHM MODULES.** Build your own rhythm box—simply, cheaply. Realistic sound guaranteed. S.A.E. for details. D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset.

## ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 3d. stamp.

## INTEGRATED CIRCUITS

CA 3018 (June issue) 26/-  
CA 3020 (May issue) 31/-

All types of Digital and Linear Integrated Circuits supplied.

MAIL ORDER ONLY C.W.O. P. & P. 9d.

**ANDOR ELECTRONICS LTD.**  
7 Hindley Street, Stockport

## 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed 65/- POST PAID

**BIG BARGAIN PARCELS ONLY**  
**OF COMPONENTS** 10/-

**SALOP ELECTRONICS** POST PAID  
9a Greyfriars Road,  
Coleham, Shrewsbury S.A.E. for lists

## AERIALS

### Enthusiasts THE T.M.P. EXPERIMENTAL AERIAL KIT

A unique collection of alloy elements, dipoles, booms, clamps, mast reflectors, nuts & bolts, cables even a compass! etc., to make up various experimental aerials to cover all bands.

This includes TV transmissions, SW for the radio amateur, VHF for BBC FM. Amateurs on 2 and 4 MTrs, Aircraft, Police etc., UHF for experiments on BBC 2 and Ultra High Frequencies. These Kits can be used indoor or outdoor. Robust construction with simplified detailed plans for easy assembly.

The Wonder T.M.P. Kit costs only 89/6—no extra for carriage.

Despatched to any address in UK within 7 days.

**TUBULAR METAL PRODUCTS**  
7 LOWESMOOR TERRACE,  
WORCESTER

## SITUATIONS VACANT

**ENGINEERS.** A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C. Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

**RADIO** and tape recorder testers and trouble shooters required. Canteen, excellent rates of pay. 8.00 a.m. to 5.00 p.m. 5-day week. Elizabethan Electronics Limited, Crow Lane, Romford, Essex. Phone: Romford 64101.

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

(continued page 637)

## FOR SALE

**SEE MY CAT.** for this and that. Tools, materials, mechanical and electrical gear—lots of unusual stuff. This Cat. is free for the asking. **K. R. WHISTON** (Dept. PWC), New Mills, Stockport.

## MINIFLUX HEADS

Special offer SKN4 ½-track stereo record/playback head (list 8 gns.). Special offer 55/-. Miniflux LF6-0 self oscillating half-track mono erase head, list £3.10.0. Offered at 22/6. VLF4 ½-track ferrite erase head, list £4.5.0. Offered at 32/6. S.A.E. for full lists.

## LEE ELECTRONICS

400 EDGWARE ROAD. PADDINGTON 5521.

Boxes of B.A. Nuts and Bolts, all Brand new and high grade machine cut items, invaluable to all Service men, experimenters etc. Bolts include 2.BA, 4.BA and 6.BA up to 2" long, various heads, mainly brass, approx. 3—400 items per box, our Special Price 7/6d. plus 2/-d. Post and Packing. **WALTON'S WIRELESS STORES**, 55a Worcester Street, Wolverhampton, Staffs.

**HIGH GLOSS METALLIC  
HAMMERED ENAMEL  
MAKES FANTASTIC  
DIFFERENCE TO PANELS**

—say hundreds of enthusiastic users  
'Crackle' pattern appears like magic on wood and metal. No undercoat. Air dries 15 min. to hard glossy finish. Heat, liquid and scratch-proof. Lt. and Dk. Blue; Bronze; Silver; Green; Black. Send NOW for free list, or 8/- (+ 1/6 post and packing) for trial ½pt. tin, colour samples and instructions.

**BRUSH  
OR SPRAY-ON**

*Hammerite*

**FINNIGAN SPECIALITY PAINTS**, Dept. P.W.  
STOCKSFIELD (Tel. 2280), Northumberland

## MORSE MADE EASY !!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 3d. stamp for explanatory booklet to:

**63CBS/P, 45 GREEN LANE, PURLEY, SURREY**

**PRACTICAL WIRELESS** copies for sale. All issues from August 1950, excluding Dec. 1951, July 1952, May 1956, April 1957, June 1958, April 1958, August 1959. What offers. Box No. 83.

## FOR SALE (continued)

**5 TON FACTORY CLEARANCE.** Radio, TV, elec. components in 27s. 6d. mixed parcels. Post free. Example: resistors, condensers, pots, speakers, coax, coils, fibre washers, valves, over a dozen different types, tuning knobs, grommets, sleeving, IFS, Paxolin, wire, rectifiers. Lots of other items. Pot luck. Postal order to—P. L. Newton, 16 Shallcross Crescent, Hatfield, Herts.

## RECEIVERS & COMPONENTS

### STELLA NINE RANGE CASES

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

**LIST OF PRICES AND SIZES**  
which are made to fit Standard Alloy Chassis

Width	Depth	4" Height		6" Height		7½" Height	
		£	s d	£	s d	£	s d
6½"	3½"	10	0	12	6	14	6
6½"	4½"	11	6	14	6	16	6
8½"	3½"	12	6	16	0	17	9
8½"	6½"	17	9	1	1	6	1
10½"	7½"	1	3	0	1	8	0
12½"	3½"	17	9	1	1	9	1
12½"	5½"	1	2	3	1	7	0
12½"	8½"	1	8	9	1	14	6
14½"	3½"	1	0	6	1	5	0
14½"	9½"	1	15	0	2	4	9
16½"	6½"	1	11	0	1	17	0
16½"	10½"	1	19	3	2	10	0

Cases—Post 4s. 6d.

**CHASSIS** in Aluminium, Standard Sizes with Gusset Plates  
Sizes to fit Cases. All 2½" Walls.

s d		s d		s d	
6" x 3"	5 6	10" x 7"	8 6	14" x 3"	7 3
6" x 4"	5 9	12" x 3"	6 9	14" x 9"	14 6
8" x 3"	6 6	12" x 5"	7 6	16" x 6"	10 9
8" x 6"	7 9	12" x 8"	10 9	16" x 10"	16 0

Chassis—Post 3s. 0d.

## E. R. NICHOLLS

Manufacturer of Electronic Instrument cases

**46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE**

Tel: STOCKPORT 2179

Printed circuit capacitors, tubular ceramic 3-3 pf and 500 pf 6/- per 100.

Disc ceramic P.C., .01 mf 500 vw (erie) approx 7/16" dia. 10/- per 100.

Disc ceramic wire ended .01 mf 12 vw. 3/- doz.

Hunts 1 mf. 350 vw. P.C. mounting approx ½" dia x 1" long 14/6 per 100 post paid.

Mixed bag silver mica and ceramics approx 150 10/- 80 pf small silver mica ideal for transistors 4/- per 100.

Double gang pots. 500k + 500k in 1" dia., 250k + 250k log. long spindles 3/- each.

Slider pots. 250k, 2 meg. 2/6 per doz.

Transistor driver and output transformers suit OCS1s etc. reduced to 5/6 pair. (approx 1 watt rating) 500 m/w 4/- pair.

Transistor .1 mf 50 vw. 3/- doz.

Transistor electrolytics 2 mf 6vw, 4 mf 64vw, 20 mf 6 vw, 50 mf 6 vw, 100 mf 6vw, 6d each. 100 mf 9vw, 150 mf 12 vw, 350 mf 9 vw, 8d each. 400 mf 15 vw, 500 mf 9 vw, 9d each. 1000 + 1000 mf 18 vw can neg. 2/-, 1000 mf 50 vw 4/- each.

Smoothing capacitors, 100 + 100 + 50 mf 275 vw, 100 + 300 + 100 + 16 mf 4/- each.

Small M.W. ferrite aerials 2½" long 3/- each.

Goodmans 4" sq. loudspeakers brand new boxed 15 ohm imp. 11/6 post paid.

Polystyrene capacitors 1000 pf 5000 pf 30 vw. 5% 10, 25, 36, 60, 110, 250, 375, 470, 820 pf 125 vw. 2½ and 5% 33, 100, 120, 137, 1000 pf 350 vw. all 2/6 doz.


Manufacturers surplus transistorised stereogram chassis M.W. LW. FM. send for list of full details.

MAIL ORDER ONLY S.A.E. FOR LISTS  
POSTAGE up to £1 + 1/6, £1 to £2 + 2/3, up to £5 + 3/6, over £5 free.

**A J H ELECTRONICS**  
59 Waverley Road . The Kent  
Rugby . Warwickshire

# SURPLUS BARGAINS

(EX GOVT.)

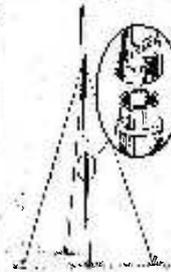

### 35FT AERIAL MASTS

Seven 5ft. 8in. interlocking sections of 2in. diameter heavy gauge steel tube, complete with swivel base calibrated in degrees, nine nylon guy lines and ground spikes. Finished olive green. £16. Carr. 30/-

**70FT. MAST.** 14 sections as above with 12 nylon guy lines and spikes plus block and tackle, £32.10.0. Carr. 50/-

### MAKE YOUR OWN AERIAL MAST

5ft. 8in. sections as above 20/- per section. Carr. 3/- each. Nylon guy lines with semi-automatic tensioner. 37ft. 7/6 each; 50ft. 8/6 each; 60ft. 10/- each. P. & P. 2/- each. Swivel base 30/- Carr. 10/- Ground spikes 4/6 each. P. & P. 1/6 each.

**TELESCOPIC AERIAL MASTS.** Tubular steel copersised spray finish, ring cam locking on each section provides for full or any height required. Suitable all fixings and base locations. Bottom section 1 1/2in. diameter. 20ft. 4 section. Closed 5ft. 9in. Weight 16lb. 70/- Carr. 15/- 20ft. 4 section plus 12ft. whip. Weight 17lb. 80/- Carr. 15/- 34ft. 6 section. Closed 6ft. 6in. Weight 20lb. 90/- Carr. 15/-

**HALLICRAFTERS R19H/TRC1 A.M.** 16 valve double conversion superhet. Crystal controlled 70-100 Mc/s. Direct crystal frequency. Size 19" x 12" x 7". 115v. A.C. Internal speaker and outlet socket for external speaker. Many other refinements. Circuit included. £25. Carr. 30/-

**100 SETS OF AB101/TRC1 MAST EQUIPMENT.** With guys and ancillary parts. £25 per set (ex warehouse)

**MURPHY B40 NAVAL RECEIVERS.** Tested £25. Carr. 30/- Untested as received from Ministry £12.10.0. Carr. 30/- **B41 RECEIVERS.** Tested £15. Carr. 30/- Untested as received from Ministry £10.10.0. Carr. 30/-

**COLLINS (U.S.A.) RECEIVERS.** 7 valve superhet (Int. Octal Valves). Exceptionally stable for SSB. Frequency coverage 1.5-12 Mc/s. Power required 250v. D.C. 80mA. 12v. A.C. 1.25A. Excellent condition. LAST FEW £8.10.0. Carr. 15/-

ALL 19 SET EQUIPMENT IN STOCK.

## A.J. THOMPSON (Dept. P.W.)

"EILING LODGE", GODICOTE, HITCHIN, HERTS.  
Phone: GODICOTE 242

Hours of business Monday to Friday 8-5. Sat. 8-12.  
Prices correct at time of press but subject to increase

Terms of business: C.W.O. Minimum orders value £3.3.0. Carriage charges apply to Mainland only.  
(IT'S CHEAPER IF YOU CALL AND COLLECT)


**BARGAIN TRANSISTORS.** Good Audio Types, 5 for 5/-, 10 for 8/-. All New, Tested. Post 6d. J. BLACKER, 221 Loughborough Road, LEICESTER.

**MINIATURE ELECTROLYTICS,** 15 Volt 2 6 8, 10, 15, 20, 30, 40, 50, 100 mfd., 8/6 per dozen, 30 for £1. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield 8.

**COMPONENTS AT GIVE AWAY PRICES.** Digital Counters, Rev Counters, Thyristors, Transistors, Valves, Tool Bags, Track Heads, Recording Tape, Aerials, Intercoms, Microphones, Micro Switches etc. 6d. stamp only to **DIAMOND MAIL ORDER PRODUCTS, PROSPECT HOUSE, CANAL HEAD, POCKLINGTON, YORK. NO4 2NW.**

**SIGNAL INJECTOR.** Transistorised square wave generator probe, British Made, only 19/6, P & P 1/6 S A E for details and lists **WILSIC ELECTRONICS LTD., 6 Copley Road, Doncaster, Yorks.**

## WE ARE BREAKING UP COMPUTERS

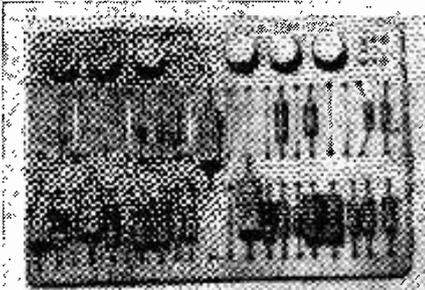

**COMPUTER PANELS** (as shown) 2 x 4in. 8 for 10/- Post free with min. 30 transistors. 100 for 65/- + P. & P. 6/6; 1,000 for £30 + carr.  
**NPN GERMANIUM TO5 1 WATT POWER TRANSISTORS** on small heat sink on 2 x 4in. panel. 5 for 10/-, P. & P. 1/6.  
**PANELS** with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/-  
**POWER TRANSISTORS** sim. to 2N174 ex eqpt. 4 for 10/-, P. & P. 1/6.  
**POWER TRANSISTORS** sim. to 2N174 on FINNED HEAT SINK (10D) 4 for £1. P. & P. 3/-  
**LONG ARM TOGGLE SWITCHES** ex eqpt. SPST 13/6 doz. DPDT 22/6 doz. DPST 17/- doz. P. & P. ALL TYPES 2/- doz.  
**TRANSISTOR COOLERS** TO5 7/6 doz, TO3 18/- doz. P. & P. 9d  
**OVERLOAD CUT OUTS.** Panel mounting in the following values . . . 5/- each 1, 1 1/2, 2, 3, 4, 5, 7, 8 amp.  
**MINIATURE GLASS NEONS.** 12/6 doz.  
**NEW MIXED DISC CERAMICS.** 150 for 10/-, P. & P. 1/-  
**LARGE CAPACITY ELECTROLYTICS** 1 1/2in. diam. Screw terminals. All at 6/- each + 1/6 each P. & P.  
1,500mF, 150V d.c. wkg; 4,000mF, 72V d.c. wkg; 5,000mF, 55V d.c. wkg; 6,300mF, 72V d.c. wkg; 16,000mF, 25V d.c. wkg; 25,000mF, 12V d.c. wkg.

**KEYTRONICS, 52 Earls Court Road, London, W.8. Mail order only.**

## SEMICONDUCTOR BARGAINS

1S130	2/6	AF117	5/-	BYZ10	9/-
1S132	2/6	ASZ21	4/6	BYZ11	7/6
2N696	5/-	ASY26	4/6	BYZ12	6/-
2N697	5/-	ASY27	8/6	BYZ13	5/-
2N706	3/-	ASY28	6/6	NKT261	4/6
2N706A	3/-	BC107	3/6	NKT262	4/6
2N1302	4/6	BC108	3/6	NKT264	4/6
2N1304	5/6	BC109	3/6	NKT405	15/-
2N1305	5/6	BCY34	4/6	NKT713	5/6
2N2220	5/-	BCY70	6/6	NKT781	6/-
2N2369A	8/-	BCY71	10/6	OC23	8/-
2N2905	8/-	BCY72	6/6	OC28	7/6
2N2905A	8/-	BFX13	6/6	OC35	7/6
2N2926	3/6	BFX29	15/-	OC36	7/6
2N3053	7/6	BFX84	8/-	OC44	7/6
2N3055	19/6	BFX85	10/-	OC45	2/6
2N3702	4/-	BFX86	8/-	OC71	2/6
2N3704	4/6	BFY50	5/6	OC72	2/6
2N3705	4/6	BFY51	4/6	OC75	3/-
2N3706	4/6	BFY52	5/6	OC81	4/-
2N3707	4/-	BSX19	5/6	OC170	6/-
2N3819	10/-	BSY26	4/-	OC171	6/-
AC107	6/-	BSY27	4/-	OC200	5/6
ACY17	5/-	BSY28	4/-	OC201	5/6
ACY18	5/-	BSY29	4/6	OC202	8/6
ACY19	5/-	BSY38	4/6	OCF71	8/6
ACY20	4/-	BSY39	4/6	OA81	1/6
AD140	8/-	BSY40	4/6	OA91	1/6
AD149	8/-	BSY95A	4/-	OA202	2/-
AR114	5/-	BY100	4/6		

**A. MARSHALL & SON (LONDON) LTD.**  
28 Cricklewood Broadway, London NW.2  
Telephone: 01-452 0161

**WHARFEDALE UNIT 3.** This amazing Hi-Fi Speaker Kit complete with ready-to-assemble Cabinet to Wharfedale specifications. Send stamp for details to:

**EATON AUDIO FITMENT**  
Dept. W.  
Leopold Street, Long Eaton, Nottingham.

**MONITOR 74, 17/6, Indicator 95, 17/6,** carriage 12/6 each. Monitor 100, 30/-, carriage £1. All with tubes etc., waveform generators type 51, mains operated, 30/-, carriage £1. S.A.E. for list. **NOYCE, High Laws, Silloth, Cumberland.**

# ELECTROVALUE

## RAPID MAIL ORDER SERVICE

### MINI TRANSISTORS MIGHTY SPECIFICATIONS

2N4285 PNP hFE 35-150 at 10mA IT 7MHz min.  
2N4286 NPN 30V hFE over 100 at 10µA to 1mA IT 280MHz typical.  
2N4289 PNP 60V hFE over 100 at 100µA to 1mA IT 170MHz typical.  
2N4291 PNP 40V hFE over 100 at 100mA, complementary driver/output.  
2N3794 NPN 40V hFE over 100 at 100mA, complementary driver/output.  
2N4292 NPN 30V UHF, N.F. 6dB max at 100MHz. IT 570MHz typical.  
B5001 Power, 14.3W at 100°C base temp. Insulated base. T066 size. 35V, hFE over 100 at 0.5A.

Prices: 2N4285 to 2N4292, 2N3794, 3/3d; B5001 13/6.

**RECTIFIERS:** 100V PIV 1/2A type TS1, 2/-; 400V PIV 1/2A type TS4, 2/9. 850V PIV 1/2A type BY238, 3/9; 1000V PIV 1.5A type 1N5054, 3/11.

FOR FURTHER DATA on the above semiconductors and many others, see our catalogue, price 1/- only, post free.

### BRAND NEW TRANSISTORS for immediate delivery

2N1302	4/-	2N3704	4/-	BFY51	5/-
2N1303	4/-	2N3705	3/8	BSX20	4/6
2N1304	4/-	2N3819	10/-	MFF105	8/-
2N1805	4/-	ACY22	3/3	NKT403	14/10
2N2646	12/11	ACY40	3/6	NKT405	15/-
2N2926R	2/8	AD161	8/-	OA47	1/9
2N2926b	2/6	AD162	8/-	OA90	1/3
2N2926y	2/8	ASY28	6/6	OA91	1/3
2N2926z	3/-	BC148	4/9	OA95	1/3
2N3053	5/6	BC149	3/9	OA99	3/-
2N3055	16/6	BC149	4/9	D29A4	7/-
2N3391A	5/6	BFX85	8/3	BC107	2/9
2N3702	4/-	BFX88	7/9	BC108	2/6
2N3703	3/9	BFY50	5/3	BC109	2/9

### ★ SUPER QUALITY NEW RESISTORS

Carbon film high stab, low noise:  
1W 10% 1Ω to 3.3Ω, 1/10 doz., 14/6 per 100.  
1W 5% 3.9Ω to 1MΩ, 1/10 doz., 14/6 per 100.  
1W 10% 4.7Ω to 10MΩ 1/9 doz., 13/6 per 100.  
1W 5% 4.7Ω to 10MΩ 2/2 doz., 17/- per 100.  
1W 10% 4.7Ω to 10MΩ 4d each, 8/3 doz., 25/10 per 100.

1/6 less per 100 if ordered in complete 100's of one ohmic value. Please state resistance values required.

**★ QUALITY CARBON SKELETON PRE-SETS:** 100Ω, 250Ω, 500Ω, 1KΩ, 2KΩ, 2.5KΩ, 5KΩ, 10KΩ, 20KΩ, 25KΩ, 50KΩ, 100KΩ, 200KΩ, 250KΩ, 500KΩ, 1MΩ, 2MΩ, 2.5MΩ, 5MΩ, 10MΩ. Available in horizontal or vertical mounting, 1/- each.

**EVERYTHING BRAND NEW. NO 'SURPLUS' SEND 1/-** for our catalogue containing data on 200 up-to-date semiconductors available from stock, as well as many other components, also transistor equivalents table. Invaluable to every serious experimenter and designer. Everything at best possible prices.

**★ COMPONENT DISCOUNTS:** 10% over £3, 15% over £10.

Post and Packing: 1/- under £1, free over £1.

Stores Telephone No. EGHAM 5533

**ELECTROVALUE** Dept. PW.11  
6 MANSFIELD PLACE, ASCOT, BERKSHIRE

**SPECIALISTS IN READY TO ASSEMBLE** Speaker Enclosures from bookshelf to the larger 3 speaker system models. Satisfaction assured. Send S.A.E. for details. **EATON AUDIO FITMENTS, Dept. W1, Leopold Street, Long Eaton, Nottingham.**

**COMPLETE RANGE of Amateur, Aircraft, Communications receivers.** Chassis, panels, meters, cabinets, microphones, etc. **Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.**


### MICROMINIATURE MICROPHONES

Sensitive dynamic type. Will pick-up rustle of newspaper from 30 feet. Size 9 mm. x 9 mm. x 3.5 mm. Impedance 1 KΩ.

ONLY 28/6 Post free—C.W.O.

SHOWN FULL SIZE **MICRO DATA SYSTEMS**  
30 BAKER ST., LONDON, W.1

**RECEIVERS & COMPONENTS**  
(continued)

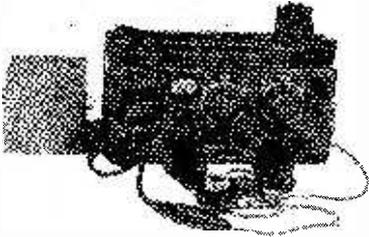


**TRANS/RECEIVER TWO TWO**

This is one of the latest releases by the govt. of an extremely recent R/T set covering 2-5Mc/s in two switched bands, containing 13 valves (3 BL22s in TX output) which can be used for more CW or R/T. Also has netting trimmer, BFO, RF and AF controls, switched meter for checking all parts of set, size 17 x 8 x 12 in. Power required LT 12V D.C., HT 325V D.C. Supplied brand new and boxed with headphones and mike also two spare valves and circuit of set. Few only at £5.10.0, carr. 50/- New plug in power supply made by us for either 12V D.C. input £3.10.0 or 200/250V A.C. £3.17.6.

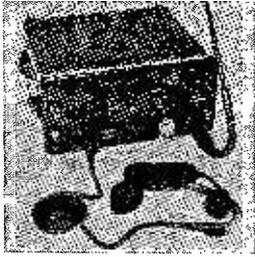**V.H.F. TRANS/RECEIVER**

THIS IS THE AFV VERSION WHICH CONTAINS A SQUELCH CIRCUIT USING 3 MORE VALVES MAKING A TOTAL OF 18. EVERYTHING ELSE AS BELOW.

This is a modern self contained tunable V.H.F. low powered frequency modulated trans/receiver for E.T. communication up to 8-10 miles. Made for the Ministry of Supply at an extremely high cost by well-known British makers, using 15 midjet B.G. 7 valves, receiver incorporating R.F. amplifier. Double



superhet and A.F.C. Slow motion tuning with the dial calibrated in 41 channels each 200 kc/s apart. The frequency covered is 39 mc/s-48 mc/s. Also has built-in Crystal calibrator which gives pips to coincide with marks on the tuning dial. Power required L.T. 4 1/2 volts, H.T. 150 volts, tapped at 90 volts for receiver. Every set supplied complete with valves and crystals. New in carton, complete with adjustable whip aerial, and circuit. Price £4.10.0, carriage 10/-

**JOHN'S RADIO**

OLD CO-OP, WHITEHALL ROAD, DRIFHLINGTON, BRADFORD. Tel: DRIFHLINGTON 2732

**RECEIVERS & COMPONENTS**  
(continued)

**BARGAIN PARCELS** of new surplus Electronic Components, 3/-, 5/-, 10/-, post free. **DOLPHIN ELECTRONICS**, 5 Pooles Way, Briar Close, Burntwood, nr. Lichfield.

**150 NEW ASSORTED** Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous, 1-20 watt, 12/6 Post Free. **WHITSAM ELECTRICAL**, 33 Drayton Green Road, West Ealing, W.13.

**METAL WORK**

**METAL WORK:** All types cabinets, chassis, racks etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

**PLEASE  
MENTION  
PRACTICAL  
WIRELESS  
WHEN REPLYING  
TO  
ADVERTISEMENTS**

**EDUCATIONAL**  
(continued)

**LEC**

**RADIO AND TELEVISION SERVICING  
RADAR THEORY AND MAINTENANCE  
TELECOMMUNICATIONS**

This private College provides efficient theoretical and practical training in the above subjects. One-year day courses are available for beginners and shortened courses for men who have had previous training.

Write for details to:

The Secretary, London Electronics College, 20 Penywern Road, Earls Court London, S.W.5. Tel. 01-373-8721

**SITUATIONS VACANT**  
(continued)

**RADIO OPERATORS, PREFERABLY WITH PMG2 CERTIFICATE, REQUIRED IMMEDIATELY FOR DUTY ON METEOROLOGICAL OFFICE OCEAN WEATHER SHIPS.**

Salary Scale £871-£1,353 per annum according to age, plus £157 overtime allowance. Free food and accommodation provided on board ship. Applicants must be natural born British Subjects. Full details from Shore Captain, Ocean Weather Ship Base, Great Harbour, Greenock. Telephone: Greenock 24291.

**PADGETTS RADIO STORE**

OLD TOWN HALL,  
LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

**SPECIAL OFFER OF TV SETS**  
Just off Rental. 12 Channels.  
Bush TV 85, £38.0.0.

Sets tested with good tubes, cabinets fair, could do with cleaning out.  
Carriage £1. Passenger train double rate.

**NEW BOXED REBUILT TV TUBES**

Type MW43/69. Top grade, not a second. 12 months guarantee. 47/- Carriage 12/-.  
New TV Tubes with slight glass fault. All types 19in. and 17in., 50/-, Carriage 12/-. 12 months guarantee. Reclaimed TV Tubes with six months guarantee. 17in. type AW43/88, AW43/80, 40/-, MW43/69, 30/-, 14in. types 17/-, All tubes 12/- carriage.

Speakers Removed from TV Sets. All PM and 3 ohms. 5in. round and 8 x 5in., 6/6. Post and Packing 3/6. 6in. round 3/-, P/p 3/-. 6 for 24/-, post paid. 7 x 4in., 5/-, Post and packing 3/-. 6 for 24/-, post paid. 7 x 4in., 5/-, P/p 3/-. 6 for 24/-, post paid. 5in. round, 3/-, P/p 3/-. 6 for 24/-, post paid. Slot speakers 8 x 2 1/2in., 5/-, P/p 3/-. 6 for 30/-, post paid.

Special Sale of ex-W.D. Gear. R.A.F. Tube Unit, Type 286, just like the 62A Unit. Fitted with VCR97 Tube. Mu-metal screen, full of EF50 valves, complete with outer case. Grade I, 27/-, Grade II, 22/-, Both units 10/- carriage each.

Bush TV 53. 14in. 12-Channel tested, with good tube, cabinets fair, £5.0.0, carriage 15/-, passenger train double rate.

Untested Pye, K.B., R.D.G., Ekco 17in. TV Sets. Bush 17in. TV Sets 50/- each, carriage 15/-, Passenger train double rate.

VCR97 Tube complete with mu-metal screen 10/-, p. & p. 5/-.

Top Grade Mylar Tapes, 7in. Standard, 11/6, 7in. Long Play, 14/-, 7in. Double Play, 19/6, 5in. Standard 7/9, 5in. Long Play, 10/-, plus post on any tape 1/6.

**VALVE LIST**

Ex. Equipment. 3 months' guarantee

Single Valves Post 7d., over 3 Valves p. & p. paid. 10P1, EF80, EB91, ECL80, EF50, PY82, PZ30, 20P3. All at 10/- per dozen, post paid.

ABP12	1/6	PL81	4/-	6U4	5/-
EB85	3/	PY33	5/-	6V6	1/9
EBF85	3/	PY81	1/6	6P28	5/-
EBF80	3/	PY82	1/6	10C2	5/-
ECC81	3/	PZ30	5/-	10P13	2/6
ECC82	3/	R19	5/-	183BT	3/6
ECC83	4/-	U25	5/-	20D1	3/-
ECL80	1/6	U191	5/-	20L1	5/-
EF50	1/	U281	5/-	20P1	5/-
EF80	1/6	U282	5/-	20P3	2/6
EF91	6/6	U301	5/-	20P4	3/6
EY81	2/6	U329	5/-	30PLL	5/-
EY88	5/-	U251	5/-	30P4	5/-
KT36	5/-	U801	3/6	30P12	5/-
PCC84	2/-	6B8	1/8	30F5	2/6
PCF80	2/-	6B7	2/6	30FL1	5/-
PCL82	4/-	6K7	1/6	6/30L2	5/-
PCL83	5/-	6K25	5/-	50CD6	6/-

**NEW VALVES!**

Guaranteed Set Tested  
24-HOUR SERVICE

IR5	4/9	DL86	6/6	EY88	6/-	PL504	12/6
IR5	4/8	DY86	5/8	EZ80	8/9	PY32	3/6
IT4	2/9	DY87	5/6	EZ81	4/6	PY83	9/6
384	5/9	EABC80	5/9	KT61	8/3	PY81	5/-
3V4	5/6	EBC41	6/9	N78	14/6	PY82	4/9
524G	6/6	EBF80	5/9	PAB080	7/-	PY83	5/3
6AQ5	4/6	EBF89	5/9	PC86	9/3	PY83	6/-
6L8	6/-	ECC81	3/9	PC88	9/3	PY800	6/6
12KSGT	7/-	ECC82	4/3	PC97	7/8	PY801	6/6
20F2	10/-	ECC83	4/9	PC900	8/-	R19	6/3
30C18	8/9	ECC85	4/9	PCC84	5/9	U25	12/9
30PL1	12/3	ECH35	5/6	PCC89	8/9	U26	11/9
30P4	11/-	ECH42	9/9	PCC189	8/6	U191	12/8
30P19	11/-	ECH81	5/3	PCF80	6/3	ULABC80	5/6
30PL1	12/3	ECL80	6/3	PCF82	5/9	UBC41	7/6
CCL35	9/9	ECL82	6/3	PCF801	6/9	UBF89	6/3
CL33	18/6	ECL83	8/9	PCF805	8/9	UCC84	7/9
DAC82	6/9	ECL86	7/6	PCL82	6/6	UCC85	6/-
DAF91	4/3	EF89	3/6	PCL83	8/9	UCF80	3/-
DAF96	5/11	EF80	4/9	PCL84	7/-	UGL42	9/6
DF33	7/6	EF85	5/-	PCL85	8/-	UGH81	6/-
DF91	2/9	EF86	6/3	PCL86	8/-	UCL82	6/9
DF96	5/11	EF89	4/9	PFL20012	-	UCL83	9/6
DK32	6/9	EF182	5/9	PL36	9/3	UP41	9/6
DK81	4/9	EF184	5/6	PL81	7/9	UP89	5/11
DL96	6/6	EL33	8/3	PL82	6/9	UY41	5/9
DL35	4/9	EL41	9/3	PL83	6/-	UL84	5/9
DL92	5/9	EL84	4/6	PL84	6/-	UY41	6/6
DL94	5/6	EY51	6/9	PL500	12/-	UY85	5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

**GERALD BERNARD**

83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON, N.16



## Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full time 16 month College Diploma Course which gives a thorough fundamental training for radio and television engineers, starts on 1st January 1969.

The Course includes theoretical and practical instruction on Colour Television receivers and is recognised by the Radio Trades Examination Board for the Radio and Television Servicing Certificate examinations. College Diplomas are awarded to successful students.

The way to get ahead in this fast growing industry—an industry that gives you many far-reaching opportunities—is to enrol now with the world famous Pembridge College. Minimum entrance requirements: 'O' Level, Senior Cambridge or equivalent in Mathematics and English.

To: The Pembridge College of Electronics  
(Dept. PW5), 34a Hereford Road, London, W.2

Please send, without obligation, details of the Full-time Course in Radio and Television.

NAME.....

ADDRESS .....

# Adamin

## MODEL 15



### MICRO SOLDERING INSTRUMENT

- **EXTREME VERSATILITY**  
Range of 8 interchangeable bits, from 3/64" (.047") to 3/16", including new non-wearing PERMATIPS.
- **ULTRA-SMALL SIZE**  
Length 7 1/8". Weight 1/2 oz.  
Max. handle dia. 7/16".
- **EXTRA-HIGH PERFORMANCE**  
Heating time 90 secs. Max. bit temp. 390°C. Loading 15 watts — equals normal 30/40 watt iron.
- **ALL VOLTAGES**

The ADAMIN range includes five other models (5, 8, 12, 18 and 24 watts), Thermal Strippers (PVC and PTFE) and a De-soldering Tool. Please ask for colour catalogue A/10.

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL  
Telephone 01-688 8589 and 4559



**TRANSISTOR POWER OUTPUT STAGE** on P.C. Board (with diagram). 5 1/2 in. x 2 in. x 1 1/2 in. high. Tested and working. OC7L, OC81D and 2 x OC81 and Heat Sinks. With O.P. Trans. for 35 ohm speaker. Requires 5K Pot, Speaker and 9v. supply. Price **£27/6** Post paid. 5K Log Pot + Switch 4/-, 8 in. x 2 1/2 in. 35 ohm. Speaker 16/6.

**1 1/2 W MAINS GRAMOPHONE AMPLIFIERS**, EZ80, ECL82, O.P. Transformer (3 ohm). Vol./On-off and Tone Control. Double wound mains transformer. 2 1/2 x 2 1/2 in. x 2 1/2 in. separate but wired to chassis. 4 in. x 2 1/2 in. x 4 1/2 in. over valves, 65/- post paid including 6 1/2 in. Speaker. (52/6 less speaker.)



**NEW F.M. TUNER**. Range 87 to 107 MHz Attractively finished metal container with cast front 3 catches. Case size 13 in. x 7 in. x 3 1/2 in. high. Mains transformer. Metal Rectifier and Valves ECC85, EF89, EF80, ECC82 as cathode follower. EM84 tuning indicator, 2 x AF117 and 2 diodes. A really fantastic performer. Price **£17.17.0**, tax paid and carr. paid or with Stereo Decoder. **£25**. Terms available this item.

**2 x 4 WATT STEREO AMPLIFIER**. Printed circuit. Separate power pack and separate control panel. Metal rectifier. ECC83 and 2—EL84. Negative feedback. Vol., bass, treble each channel. Muting switch and on/off. Printed circuit 4 1/2 in. x 4 1/2 in. Power Pack 7 1/2 x 4 1/2 in. x 3 1/2 in. and control panel 4 in. x 5 in., with output transformers for 3-ohm speakers on power pack. **£5.10.0** (7/6 P. & P.).

**TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS**  
— 2 or 4 TRACK



Chassis 12 1/2 x 5 1/2 x 4 1/2 in. high. Front panel "gold" finish—12 1/2 x 4 1/2 in. 200-250 A.C. Record/Playback amp. switch On/Off; Tone; Vol./Mic.; Vol./Gram; Mic. Input; Gram. Input; Monitor; Speaker Socket Valves 6BR7; 12AX7; EM84; EL84; 6X4 Separate power pack, 2 Track **£8.19.6**; 4 Track **£10.4.0** (6/- post each). Rexine covered cabinet (tan) 15 1/2 x 17 x 9 1/2 in. high with sloping front for amp; complete with two tweeter speakers, and special adapting brackets for Magnavox Deck 85/- (8/- carr.) 3 speed Magnavox 4 track tape deck. Type 853. **£16.10.0**, carr. paid. 2 x 2 Stereo deck **£20**.

**"SUPER SIX" L.W. and M.W. TRANSISTOR RADIO KIT**, Mark 2. Complete set parts **£4.2.6** (5/- post). PP6 batt. 2/9 extra. Instructions and list 2/- (free with kit), Superhet; ferrite rod; wooden cab. 9 1/2 x 7 1/2 x 3 in. Celestion 4 1/2 in. speaker, 6 transistors. diode, etc.

**SPEAKERS IN CABINETS**. 20 x 15 x 6 1/2 in. Finished Vynair and Rexine, various colours. With E.M.I. 13 x 8 in. 3 or 15 ohm speaker 90/-; with 12 in. Elac 15-ohm 15W speaker. **£8.10.0** (post 10/- on either). Top quality speakers 6 x 4 in. (3 or 15 ohm), 14/6; 5 in. (3-ohm), 12/6; 4 1/2 in. (3 or 10 ohm), 12/6d.; 7 x 3 1/2 in. (3 ohm), 16/6; 13 x 8 in. (3 or 15 ohm) 41/- (post 3/8) all others post 1/6 each. 12 in. heavy duty Elac Loud-speaker 15 ohm, 20 watt, **£6.6.0**, carr. paid.

**8 W. PEAK PUSH-PULL OUTPUT AMPLIFIER**, 200-250 Volts A.C. EZ80, ECC83. 2—EL84, Bass, treble. vol/on-off, **£7.17.6** (post paid). Size 12 x 3 1/2 x 5 in. high. For Record Player, Radio Tuner, etc.




**RADIOGRAM CHASSIS** unused but very slightly tarnished. Size 13 1/2 x 5 1/2 x 7 in. Dial 13 x 4 in. gold and brown. Controls beneath dial, Tone, Volume/on/off, MW/LW/ Gram Tuning. Ferrite rod aerial. Valves UY85 rect., UCL82, UBF89, UCH81. Limited quantity. **£7.7.0**, carr. paid.

**EX GOVERNMENT AVO METER**, Model 7. Excellent condition, fully checked, with leather carrying case. List price new over **£29**. Our price **£18**. Carr. paid.

**GLEAR PLASTIC PANEL METERS D.C.** Type KA/38C. 1 1/2 in. sq. 50 microA 30/-, 500 microA 27/6; 1mA (S-meter) 27/6; 3mA 27/6; 100mA 25/-; 300V 27/6. Post 1/6d.

**6 PUSH-BUTTON STEREOGRAM CHASSIS**

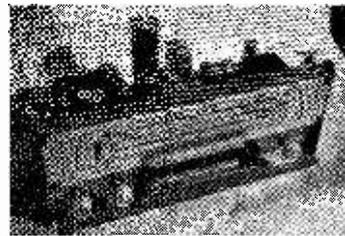

M.W.; S.W.1; S.W.2; V.H.F.; Gram; Stereo Gram Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6 1/2 in. high. Dial silver and black 15 x 3 in. 190-550M; 18-51M; 50-137M; VHF 86-100 Mc/s. Valves: ECC85, ECH81, EF89, 2x ECL86, EM84 and Rect. Price **£19.19.0**, carr. paid or **£6.13.0** deposit and 5 monthly payments of 56/6. Total H.F. price **£20.15.6**. With Stereo Decoder fitted **£7.10.0** extra.

**GLADSTONE RADIO**

66 ELMS ROAD, ALDERSHOT, Hants.  
(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240  
CLOSED WEDNESDAY AFTERNOON. CATALOGUE 6d.  
ALL ITEMS FULLY BUILT UNLESS OTHERWISE STATED  
1/- in the £ discount on orders over £10.

**4-STATION INTERCOM**

**£7/15/0**

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

**WIRE-LESS INTERCOM**

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 12 gns. P. & P. 9/6 extra.

**INTERCOM/BABY ALARM**

Originally 6 gns. OUR PRICE ONLY **59/6**

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

**Telephone AMPLIFIER**

Why not boost efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

**WEST LONDON DIRECT SUPPLIES (P/W12)**  
169 KENSINGTON HIGH STREET, LONDON, W.8.

**ALPHA**

IT'S A MUST  
OUR  
CATALOGUE  
JOIN THE  
THOUSANDS  
OF SATISFIED CUSTOMERS  
SEND NOW FOR

**OUR NEW 1968/69**  
illustrated catalogue  
NOW AVAILABLE  
(send 2/- in stamps for your copy)

Catalogue contains prices and details of Amplifiers — Hi-Fi Tuners — Loudspeakers — Pick-ups — Playing Decks — Microphones — Test Meters — Hand Tools — Valves — Soldering Irons — Tape Recording Accessories etc.

**OFFICIAL SUPPLIERS TO MANY  
EDUCATION AUTHORITIES AND  
RESEARCH ESTABLISHMENTS**

Usual Educational Discounts

**ALPHA RADIO SUPPLY CO**  
103 Leeds Terrace, Leeds 7. Tel: 25187

**MAINS UNITS for all types of TRANSISTOR EQUIPMENT**

The ideal, economical and safe way of running Transistor Radios, Record Players, Tape Recorders, Amplifiers etc. from A.C. Mains. All units are completely isolated from mains by double wound transformer ensuring 100% safety.

**PLUS-3  
MAINS UNIT**

Provides three separate switched output voltages 6v., 7 1/2v. and 9v. DC. Attractive case with indicator light, mains lead output socket, plug and lead. Size 4 1/2 x 3 1/2 x 2 1/2 in. (Extra lead with DIN plug for Cassette Recorders 7/6)

**57/6** P. & P. 2/6

**POWER PLUS  
MAINS UNIT**

For Cassette Tape Recorders using 7 1/2v. Complete with DIN plug for recorder power socket. Can also be supplied for a 6-volt output complete with suitable plug. (Please state make, model and voltage required.)

**45/-** P. & P. 2/6

**MAINS UNIT for FI-CORD 202A  
TAPE RECORDER** P. & P. 5/- **£4.15.0**

**MAJOR POWER PLUS  
MAINS UNITS**

For single outputs, 9v, 6v, 39/6. P. & P. 2/6.  
For two separate outputs, 9v + 9v, 6v + 6v. 42/6. P. & P. 2/6.  
(Please state outputs required.)

**R.C.S. PRODUCTS (RADIO) LTD.**  
(Dept. P.W.), 31 Oliver Road, London, E.17

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel. PARK 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office  
When sending cash with order, please include 2/6 in £ for postage and handling  
MINIMUM CHARGE 2/-. No C.O.D. orders accepted.

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel. LANgham 8403  
Open all day Saturday

0A2	6/-	6AG7	6/9	6BQ7A	7/-	6K25	15/-
0A3	8/6	6AH6	10/-	6BR7	18/-	6L1	12/-
0B2	6/-	6AJ5	9/-	6BR8	12/6	6L6GT	8/6
0B3	6/-	6AJ8	5/3	6BS7	25/-	6L7	6/-
0C3	6/6	6AK5	5/6	6BW6	13/6	6L12	5/-
0D3	6/-	6AK6	11/8	6BW7	12/-	6L18	6/-
OM10	11/-	6AL6	3/-	6BZ6	6/-	6LD20	5/6
LAX2	12/-	6AL7GT		6BZ7	10/-	6N7GT	6/6
1B3GT	7/-			6C4	5/6	6P1	11/6
1C3GT	5/-	6AM4	22/-	6C5GT	6/6	6P25	13/-
1G4GT	3/-	6AM5	5/-	6C6	4/-	6P28	12/-
1H5GT	3/-	6AM6	4/-	6C8G	7/-	6Q7	7/-
1L4	3/-	6AM8	8/-	6C9	17/3	6SA7	7/-
1R5	5/-	6AN8	10/-	6CB6	5/-	6SG7	6/-
1S4	6/-	6AQ5	6/-	6CDB6A		6SH7	4/6
1S5	4/6	6AQ6	10/-		22/-	6SJ7	7/-
1T4	4/-	6AR5	6/-	6CG7	8/-	6SL7GT	6/-
1U4	6/-	6AR6	8/-	6CH6	11/-	6SN7GT	5/6
1U5	8/6	6AS5	6/6	6CL6	9/-	6SQ7	7/-
1V2	9/-	6AS6	7/-	6CL8	15/-	6SR7	7/-
1X2B	7/-	6AS7G	15/-	6CU6	12/-	6SS7	3/-
1Z2	25/-	6AT6	4/6	6CW4	12/-	6T8	6/-
2C26A	8/-	6AU4GT		6CY5	7/-	6U4GT	12/-
2C40	8/-			6D3	7/6	6V8	6/-
2C51	8/-	6AU6	5/-	6D4	17/6	6V6GT	6/-
2CW4	12/-	6AU8	10/-	6DC6	13/6	6X4	4/6
2D21	6/-	6AV5GT		6DK6	8/-	6X5GT	5/-
2E26	27/6			6DQ6B	11/-	6X8	11/-
2X2	5/-	6AV6	5/6	6DS4	15/-	6Y6G	11/6
3A3	11/-	6AW8A	11/-	6DT6	8/-	6Y5	13/6
3A4	4/-	6AX4GT		6EA8	11/-	6Y4	9/-
3B28	40/-			6EW6	12/-	6Z4	7/6
3Q4	7/6	6AX5GT		6F6GB	6/6	9BW6	7/-
3S4	6/6			6F7	9/-	9D2	3/6
3V4	6/6	6AX7	10/-	6F11	6/-	9D7	9/-
5AN8	11/-	6B4G	15/-	6F13	6/6	10C1	13/-
5R4GV	10/-	6B8G	2/6	6F14	12/-	10C2	10/-
5U4G	5/6	6BA6	4/-	6F15	11/-	10D2	2/-
5U4GB	7/-	6BA7	15/-	6F17	9/-	10F1	18/-
5U8	8/-	6BC5	3/6	6F18	7/6	10F9	10/-
5Y3GT	5/6	6BE6	4/6	6F23	15/-	10F18	7/6
5Z3	8/-	6BF6	9/-	6F24	13/-	10L1	7/6
5Z4G	7/-	6BF7	12/-	6F25	14/-	10LD11	10/-
5Z4GT	7/6	6BG6G	11/-	6F28	13/-	10P13	12/-
6R0L2	14/-	6BH6	8/-	6F28	11/-	10P14	16/-
6ASG	5/6	6B76	8/-	6GK6	12/-	12AC6	7/-
6AB4	6/6	6BK4	20/-	6GW6	11/-	12AD6	6/-
6AB7	4/-	6BK7A	9/-	6J4	9/-	12AL5	7/6
6AC5GT		6BL7GT		6J5GT	5/6	12AQ5	7/-
	12/-			6J7	3/6	12AT6	4/6
6AC7	4/-	6BN6	7/6	6J7	8/-	12AT7	6/-
6AD4	15/-	6BN8	8/-	6K6GT	9/-	12AU6	5/-
6AF4A	9/-	6BQ6GT		6K7G	2/6	12AU7	5/9
6AG5	3/-			6K23	9/-	12AV6	5/6

First Quality Fully Guaranteed



ELECTRONIC VALVES

12AX7	5/6	30C15	14/-	90CG	25/-	DL68	13/-
12B4A	9/6	30C17	15/-	90CV	25/-	DL96	7/-
12BA6	6/-	30C18	14/-	150B2	11/-	DM70	6/-
12BA7	6/-	30F5	18/-	150B3	10/-	DM160	8/-
12BE6	6/-	30FL1	15/-	807	9/-	DY86	6/-
12BH7	6/-	30FL12	17/6	811A	30/-	DY87	6/6
12BT6	4/6	30FL13	8/-	812A	60/-	DY802	9/-
12BY7	10/-	30FL14	14/6	813	75/-	E88CC	12/6
12DQ7	10/-	30L1	6/-	837	15/-	E180F	17/6
12E1	20/-	30L15	18/-	866A	14/-	EAF80110	
12E14	52/6	30L17	16/-	884	10/-	EABC80	6/-
12K5	10/-	30P12	15/-	1805	7/6	EBC33	8/-
12K8	8/-	30P19	14/-	5670	10/-	EBC41	8/6
12Q7GT	5/6	30PL1	15/-	5751	11/-	EBC81	6/-
12SA7GT	8/-	30PL13	17/6	5763	12/-	EBF80	7/6
12SC7	4/6	30PL14	17/-	5840	20/-	EBF83	8/-
12SG7	6/-	35A5	10/-	5886	40/-	EBF89	6/-
12SK7	6/6	35B5	12/-	6080	27/6	EEL1	12/-
12SQ7	7/6	35C5	6/6	6146	27/6	EEL31	24/-
13D3	5/9	35D5	12/-	6197	20/-	ECC34	8/-
19AQ5	6/-	35L6GT	8/-	6360	25/-	ECC40	10/-
20CV	62/6	35W4	4/6	6939	40/-	ECC70	17/-
20D1	9/-	35Z3	10/-	7360	30/-	ECC81	6/-
20L1	18/-	35Z4G	4/-	7551	30/-	ECC82	5/9
20P1	10/-	35Z5GT	6/-	7581	22/6	ECC83	5/6
20P3	12/-	50A5	12/-	7586	22/6	ECC84	5/6
20P4	18/-	50B5	12/-	7591A	20/-	ECC85	5/-
20P5	19/-	50C5	6/-	7895	22/6	ECC86	8/-
25BQ6GT		50L6GT	7/6	AZ31	9/-	ECC88	7/6
		53KU	13/6	CCH35	9/-	ECC89	11/-
25C5	9/-	75C1	8/-	CY31	7/-	ECC91	3/6
25CUG	12/-	80	7/-	DAF96	7/-	ECC97	14/-
25L6GT	6/6	83A1	12/6	DF96	7/-	ECF50	6/6
25Z4G	6/-	85A2	7/6	DH81	10/-	ECF82	6/6
25Z5	8/-	85A3	7/6	DH101	9/-	ECF83	14/-
25Z6GT	11/-	90AG	46/-	EK92	8/8	ECF86	9/6
30A5	7/-	90C1	12/-	EK96	7/6	ECF80482	

ECH35	11/-	ELL80	15/-	PCF80014		U25	14/6
ECH42	10/-	EM34	15/-	PCF801	9/-	U26	14/6
ECH81	5/3	EM71	12/6	PCF802	9/-	U31	8/-
ECH83	8/-	EM80	7/-	PCF80514		U33	30/-
ECH84	9/-	EM81	7/6	PCF80612		U76	4/-
ECL80	7/-	EM84	7/-	PCF80814/6		U81	10/-
ECL81	7/6	EM87	10/-	PCL80	15/-	U281	8/-
ECL82	6/-	EN32	30/-	PCL81	9/-	U282	8/-
ECL83	10/-	EN91	6/-	PCL82	7/-	U301	11/6
ECL84	10/-	EY51	7/6	PCL83	9/6	U403	8/-
ECL85	10/6	EY80	8/6	PCL84	8/-	U404	5/-
ECL86	8/-	EY81	7/-	PCL85	8/6	UABC80	6/-
ECLL800		EY83	10/-	PCL86	8/6	UAF42	9/6
		EY84	9/6	PCL88	17/-	UBC41	8/6
EF9	8/-	EY86	6/6	PCL80017/6		UBC81	8/6
EF37A	8/-	EY87	8/-	PCL80115		UBF80	6/6
EF39	8/-	EY88	8/-	PEN45	6/6	UBF89	7/-
EF40	9/-	EZ40	7/6	PEN45DD		UBL1	8/6
EF41	9/-	EZ41	8/6		12/-	UC92	6/-
EF42	13/-	EZ80	5/-	PEN383	9/-	UC85	7/-
EF54	10/-	EZ81	5/-	PEN384	9/-	UCF80	9/6
EF55	12/-	GZ32	9/6	PEN453DD		UCH21	9/6
EF80	4/6	GZ33	13/6		10/-	UCH42	9/6
EF83	9/6	GZ34	10/-	PF86	10/-	UCH81	6/6
EF85	6/6	HL42DD		PF818	14/-	UCL81	10/-
EF86	6/-			PFL20013		UCL82	7/-
EF89	5/-	KT66	20/-	PL33	8/-	UCL83	9/6
EF91	4/-	KT68	29/-	PL36	10/-	UF9	10/-
EF92	7/6	MH4	7/6	PL38	18/-	UF41	9/6
EF93	4/-	MH41	9/-	PL81	7/6	UF42	10/-
EF94	5/-	MLA	9/-	PL83	8/-	UF43	10/-
EF95	5/-	MSFENT		PL83	7/-	UF80	7/-
EF96	3/6			PL84	6/6	UF85	7/3
EF183	6/-	N78	19/-	PL500	13/6	UF89	7/-
EF184	6/6	PABC80	7/6	PL504	15/-	UL41	9/6
EF804	20/-	PABC80	11/-	PY31	5/-	UL84	6/6
EH90	7/-	PC88	11/-	PY32	10/-	UM4	10/-
EK90	4/6	PC95	7/6	PY80	5/6	UM84	7/-
EL34	9/6	PC97	8/-	PY81	5/6	U8	7/-
EL36	8/6	PC900	8/9	PY82	5/6	UU9	7/6
EL41	9/6	PC84	8/-	PY83	6/6	UY21	9/6
EL42	10/-	PC85	7/6	PY88	7/6	UY41	7/-
EL81	9/-	PC88	11/-	PY800	9/-	UY82	9/6
EL82	8/-	PC89	9/6	QU37	27/-	UY85	6/-
EL83	7/6	PC8189	10/-	SP41	5/6	VU111	8/6
EL84	4/6	PC805	16/-	SP61	5/-	VUL33	8/-
EL86	8/-	PC806	16/-	TP22	10/-	W76	7/-
EL90	6/-	PC880015		TP21	35/-	W107	7/-
EL95	5/-	PCF80	6/6	TP22	35/-	W729	10/-
EL860	22/-	PCF82	6/3	T22	35/-	X65	9/-
EL500	17/-	PCF84	8/-	U19	40/-	X69	15/-
EL821	10/-	PCF86	8/6	U20	12/-	Z759	25/-
EL822	17/-	PCF87	15/-	U22	8/-	Z803U	15/-

## INTEGRATED CIRCUIT AMPLIFIERS

RCA Type CA3020  
Integrated Circuit Audio Amplifier in TO5 encapsulation (size of a small transistor), equivalent to seven n-p-n silicon transistors, 3 diodes and 11 resistors. Power output 550mW. Total harmonic distortion 1%. Will operate on voltage from 3 to 9 volts. 30/- plus 2/- p.p.

## 10-watts STUD MOUNTED ZENER DIODES

4-7V, 5-1V, 5-6V, 6-2V, 6-8V, 7-5V, 8-2V, 9-1V, 11-0V, 12-0V, 15-0V, 16-0V, 18-0V, 2-00V, 24-0V, 27-0V, 30-0V, 33-0V, 36-0V, 43-0V, 47-0V—all at 6/6.

SPECIAL OFFER OF SILICON RECTIFIERS  
1N5054; 1,000 p.i.v., 1.5 Amp. miniature wire ended epoxy encapsulated. 4/8 each  
(We apologise for misprint in the November issue where price was shown as 3/6.)  
For orders of 12 or more. 3/8 each

## LOW and MEDIUM CURRENT THYRISTORS

3/40, 400 p.i.v. 3 amp, stud mounted. Gate voltage 3-0v. at 20mA max. 7/6  
BLUE SPOT, 200 p.i.v. 5 amp, stud mounted. Gate voltage 3-25v. at 120mA max. 12/6  
GREEN SPOT, 400 p.i.v. 5 amp, stud mounted. Gate voltage 3-25v. at 120mA max. 17/6

## HIGH CURRENT THYRISTORS

CR80-021A, 80 amps, 25 p.i.v. 23/-  
CR100-151A 30/-  
CR100-201A, 100 amps, 200 p.i.v. 35/-  
CR100-215A, 100 amps, 250 p.i.v. 40/-  
CR100-301A, 100 amps, 300 p.i.v. 45/-  
CR100-351A, 100 amps, 350 p.i.v. 50/-  
CR100-401A, 100 amps, 400 p.i.v. 55/-  
CR100-501A, 100 amps, 500 p.i.v. 75/-

## AVALANCHE SILICON RECTIFIERS

Type RA508AF, 960 p.i.v. at 6 amps, max., stud mounted. 10/6

## DRY REED INSERTS

Glass dry reed inserts approx. 1/16 in. dia. x 1 in. long with axial leads. One "make" contact of 100mA capacity at 50V. Can be operated by permanent magnet or 30-50 Amp-turns relay coils. PRICE 18/- per doz. post free.

## CURRENT PRODUCTION CATHODE RAY TUBES

2AP1—2in. screen. EHT 500 to 1000V. Typical sensitivity at 500V. X—220mm/V; Y—260mm/V. USM11 Base. Overall length 7 1/2 in. 40/-  
3BP1—3in. screen. EHT 1500V. Typical sensitivity X—150mm/V; Y—200mm/V. B14A Base. Overall length 10 1/2 in. 55/-  
5CP1A—DG13-2—5in. screen, with P.D.A.; EHT 4000 and 2000V. Typical sensitivity X—275mm/V; Y—325mm/V. B14A Base. Overall length 15 1/2 in. 100/-  
All the above tubes have 6-3V heaters and are suitable for general oscilloscope to use.

## GERMANIUM POINT CONTACT DIODES

CG4E—CV448 2/-; OA5 8/-; OA6 4/-; OA7 4/-; OA47 2/6; OA70 2/-; OA79 2/3; OA81 1/9; OA85 1/6; OA90 2/-; OA91 2/-; OA95 2/-.

## OUR NEW 1968/1969 CATALOGUE IS NOW READY

THE TECHNICAL INFORMATION SECTION HAS BEEN FURTHER EXPANDED TO INCLUDE MORE DETAILS OF SEMICONDUCTORS. PLEASE SEND S.A.E. (Quarto Size) FOR FREE CATALOGUE.

# PRACTICAL WIRELESS

## blueprints

The following blueprints are available from stock. Descriptive text is not available but the date of issue is shown for each blueprint. Send, preferably, a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

The Strand Amplifier .. .. } The PW Signal Generator .. .. }	(Oct. 1962)	5/-	Transistor Radio Mains Unit .. .. } 7 Mc/s Transceiver .. .. }	(June 1964)	5/-
The Berkeley Loudspeaker Enclosure .. .. } The Luxembourg Tuner .. .. }	(Dec. 1962)	5/-	The Citizen (December 1961) .. .. .		5/-
The PW Britannic Two .. .. } The PW Mercury Six .. .. }	(May 1962)	6/-	The Mini-amp (November 1961) .. .. .		5/-
Beginner's Short Wave Two S.W. Listener's Guide .. .. }	(Nov. 1963)	5/-	The Beginner's Short Wave Superhet (Dec. 1964)		5/-
The Celeste 7-transistor Portable Radio .. .. . } The Spinette Record Player .. .. }	(June 1963)	5/-	The Empire 7 Three-band Receiver (May 1965) ..		5/-
			Electronic Hawaiian Guitar (June 1965) .. .. .		5/-
			Progressive SW Superhet (February 1966) .. ..		5/-
			Beginner's 5-Band Receiver .. .. . } Home Intercom Unit .. .. }	(Dec. 1966)	5/-

★ PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL RADIO, TV OR AUDIO EQUIPMENT. ★

# PRACTICAL WIRELESS

## query service

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) **We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

### QUERY COUPON

This coupon is available until 6th December, 1968 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, DECEMBER 1968

# ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

## SOLID STATE-HIGH FIDELITY AUDIO EQUIPMENT

Audio Equipment developed from Dinsdale Mk.II—each unit or system will compare favourably with other professional equipment selling at much higher prices.


COMPLETE SYSTEMS FROM **£15.5.0**

THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

All units available separately.

SEND FOR 16 PAGE BROCHURE (No. 21) TODAY!

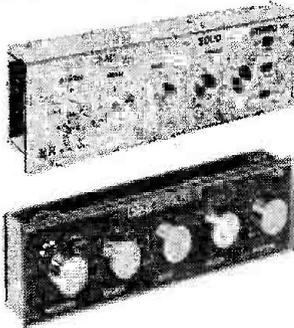DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



## Acclaimed by everyone THE MAYFAIR ELECTRONIC ORGAN



A completely new development in portable electronic musical instruments and a new field for the home constructor. The 'MAYFAIR' produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Supplied as a kit of parts which includes 165 transistors, printed circuit panels, special fully sprung and depth of touch adjusted keyboard, attractive vinyl covered cabinet with carry handle. A complete detailed and illustrated construction manual is provided with circuits and full parts list. Cost can be spread by purchasing the components packet by packet. All parts supplied are fully guaranteed. Full after sales service.


A new source of construction for the keen electronics fan either amateur or professional. Once built the 'MAYFAIR' will then provide years of enjoyable entertainment. **TOTAL COST 99 Gns.**

ORGAN COMPONENTS We carry a comprehensive stock of organ components for TRANSISTOR AND VALVE FREE PHASE designs.

Deferred terms available. COMPLETE KIT Deposit £29.19.0. 12 monthly payments of £7. TOTAL £113.19.0.

BUILT AND TESTED Deposit £36.8.0 & 12 monthly payments of £9. Total £144.8.0. EXPORT ENQUIRIES INVITED

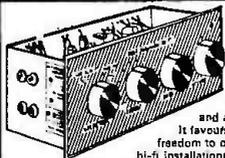Ask for BROCHURE 9 Call in. See it and play it yourself.



## TRANSISTOR AMPLIFIER

INTEGRATED 7 WATT AMPLIFIER & PREAMPLIFIER—MA7 With full Bass Treble and Volume Controls

A brilliant new design suitable for home or portable installations. For use with magnetic and crystal/ceramic cartridges, radio tuners, microphones, tape head replay and auxiliary inputs. Output is for 3 to 16 ohm speakers. It favours the user in so many ways—with fantastic power, with far greater adaptability, with freedom to operate it from batteries or mains power supply unit (the new PS.20 is ideal for this), hi-fi installations, electronic guitars and organs, P.A. installations, intercom, systems, etc. This true 7-watt amplifier is supplied ready built, tested and guaranteed.

For complete listening satisfaction. FOR ONLY £8/10/0 P.P. 4/-.

(OPTIONAL MAINS UNIT PS.20 62/2, P.P. 3-.) Illustrated Brochure No. 12.



## BRITISH MADE CAR RADIOS

A fine precision engineered car radio that's perfect company for long hours on the road. So easy to install and operate—and the price is exactly right. Has quick push-button operation for immediate station selection and choice of Medium or Long wave frequency. Manual tuning facilities. Push-button control. Output of 31 watts ensures crisp, top quality sound even at high motoring speeds. Price includes 7" x 4" speaker, full accessories and instructions.

POSITIVE OR NEGATIVE EARTH EASI-TUNE £12.10.0. pp. 4/6

£10.10.0. pp. 4/6

AUTOBAHN MANUAL as the EASI-TUNE, but with a single MW/LW Push Button.

CAR AERIALS \* 3-Section Single Hole Wing or Boot Mounting 19/6

Brochure 15

Multi Section fully disappearing type with locking device, single hole mounting 35/- Post free with Car Radio or pp. 2/6 separately.

## BUILD THESE PRACTICAL DESIGNS

	LIST
I.C.F.M. TUNER	£5.2.6. 40B
Switched F.M. Tuner	£3.17.6. 39B
Fluorescent Camping Light	£3.2.6. 43

Let us have your enquiries for parts for current PW and PE designs. S.A.E. PLEASE.



## NEW MODELS NOMBREX TRANSISTORISED Test Equipment

MODEL	£ s. d.	No.
22 Power Supply	14 0 0	22
30 Audio Generator	19 10 0	24
31 R.F. Generator	12 10 0	25
32 C.R. Bridge	10 10 0	26
33 Inductance Bridge	20 0 0	29

Send for descriptive Illustrated Brochure.



## DO IT YOURSELF MW/LW PORTABLE

New printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local and Continental stations. **TOTAL COST £6.19.6.** P.P. 4/6 TO BUILD Send for Brochure 1



## MULLARD 1 WATT AMPLIFIER WITH VOLUME CONTROL

Suitable 7x4 inch 3 ohm speaker 17/6 Ideal for Portable Record Players. Inter-Comms. Baby Alarms etc. 45/- pp. For 9 Volts operation. 45/- 3/6d.

## ITS SO EASY TO BUILD TO PROFESSIONAL STANDARDS

To get the best out of your MAGNAVOX STUDIOMATIC DECK Type 363, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board, together with necessary transformers, switches, control knobs—in fact everything needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER, which, when built, will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED.



TWO TRACK Deck, Amplifier, Cabinet and Speaker. Complete kits with MICROPHONE 7 in 1,200 ft. tape, spare spool. Today's Value £55. OUR PRICE 26 gns. FOUR-TRACK Deck, Amplifier, Cabinet and speaker. Complete kits with MICROPHONE 7 in 1,200 ft. tape, spare spool. Today's Value £60. OUR PRICE 39 gns. P.P. 22/6 ALL UNITS AVAILABLE SEPARATELY. Both models ASK FOR BROCHURE 6.

## VHF FM SUPERHET TUNER MKII

\*5-MULLARD TRANSISTORS & 4 DIODES \* 300 Kc/s BANDWIDTH \* PRINTED CIRCUIT CONSTRUCTION \* HIGH FIDELITY REPRODUCTION MONO AND STEREO \* MATCHES AUDIO MK II EQUIPMENT A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and with the decoder stereophonic broadcasts. There is no doubt about it—VHF FM gives the the real sound. Excellent stability economically priced. **TOTAL COST £6.19.6. DECODER £5.19.6. (CABINET 20/- EXTRA) ASK FOR LEAFLET 3.**



TRANSISTORS, RECTIFIERS, ZENERS, SCR'S TUNNEL DIODES, FIELD EFFECT TYPES, VALVES, CRYSTALS

## New 1968 32-page Booklet

Price 1/- Post Paid Circuits with Data, Details and Prices of over 2000 different types. This booklet is a must for every enthusiast. MANUFACTURERS — DISTRIBUTORS. We also publish a QUANTITY, SEMI-CONDUCTOR BULLETIN. Please write to us for your copy.

## NEW—MALLORY LONG LIFE MERCURY BATTERIES 50% OFF LIST PRICES

\* RM12 1.35 volts 3600 m/ah OUR PRICE 5/- each size 2" x 3" dia. \* RM625 10.35 volts 350 m/ah Pack of 8. Size 2 1/2 x 1 1/2 dia. OUR PRICE 10/- each. Easily split into eight 1.35v cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required. QUANTITY QUOTATIONS WRITE OR PHONE EXTN. 2.

## TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1968 LIST OF 1000 types available from stock. Send for your FREE COPY TODAY. (List No. 36) S.C.R.'s from 5/- Field Effect Transistors from 9/6 Power Transistors from 5/- Diodes and Rectifiers from 1/6

## GARRARD DECKS




BRAND NEW All below list price

	£ s. d.
2025 Mono/Stereo	.. .. . 8 19 6
300 LM with STAHC	.. .. . 9 19 6
SP25 MK II	.. .. . 12 12 0
LAB80 Mk II	.. .. . 25 0 0
AT60	.. .. . 10 19 6
AT60 Mk II	.. .. . 13 19 6
40 Mk II	.. .. . 11 10 0
3500 Mono/Stereo	.. .. . 27 15 0
401	.. .. . 21 10 0
AP75	.. .. . 13 10 0
SL55	.. .. . 16 19 6
SL65	.. .. . 32 10 0
SL75	.. .. . 39 10 0
SL85	.. .. . 13 13 0

Send for Illustrated brochures 16, 17 Complete range of accessories available
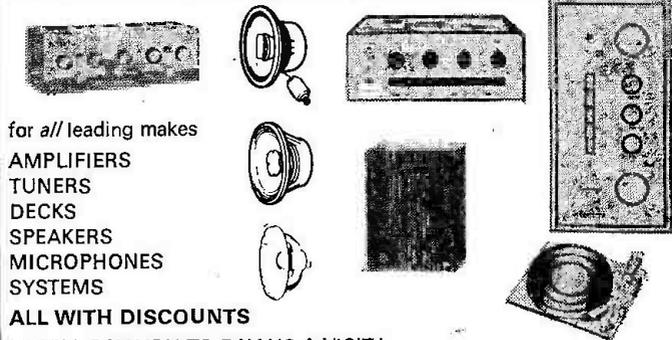
## Hi-Fi equipment to suit EVERY POCKET

Ask for Hi-Fi- Stock List Leaflet 16.17 VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE RD



for all leading makes AMPLIFIERS TUNERS DECKS SPEAKERS MICROPHONES SYSTEMS ALL WITH DISCOUNTS IT WILL PAY YOU TO PAY US A VISIT!

## Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1968)


The most COMPREHENSIVE—CONCISE—CLEAR—COMPONENTS CATALOGUE

Complete with 10/- worth discount vouchers FREE WITH EVERY COPY.

- \* 32 pages of transistors and semi-conductor devices, valves and crystals.
- \* 200 pages of components and equipment.
- \* 65 pages of microphones, decks and Hi-Fi equipment.

6,500 ITEMS 300 BIG PAGES

Send today 8'6 Post Paid

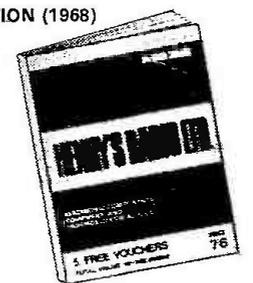

# HENRY'S RADIO LTD



OPEN MON.—SAT. 9 a.m.—6 p.m.; THURS. 9 a.m.—1 p.m.

303 Edgware Road, London, W.2. Mail Order Dept. all types of Components, Organ Dept. (01) 723-1008 9 309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-6963