

PRACTICAL WIRELESS

MAY
1969

310


BUILD THIS TRANSISTOR TESTER



ALSO INSIDE
PULSE CIRCUITS
IN OPERATION



**Soldering
Instruments**

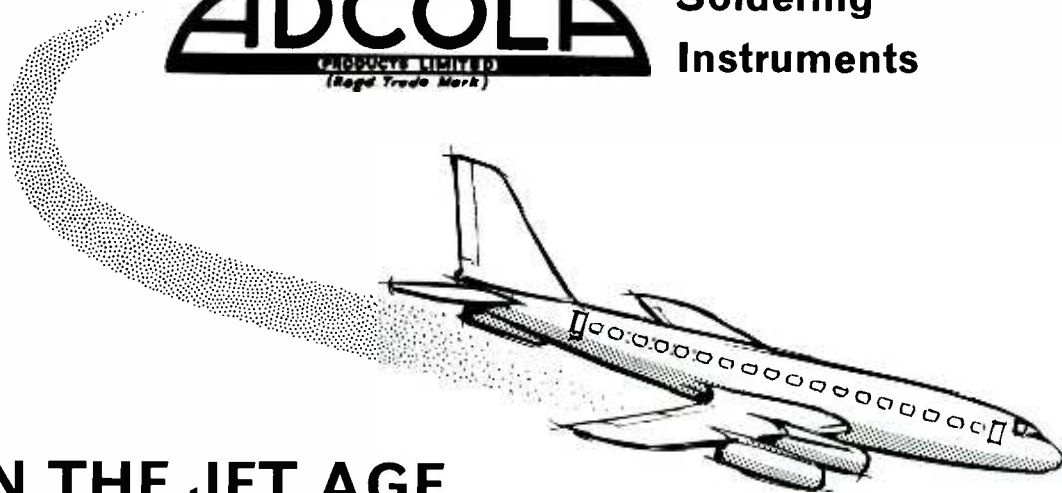

IN THE JET AGE.....

**EFFICIENCY AND RELIABILITY,
AND CONSISTANT, SUSTAINED PERFORMANCE
ARE BASIC REQUIREMENTS.**

**ADCOLA SOLDERING INSTRUMENTS MEET THESE NEEDS
AND GO ON MEETING THEM, DAY AFTER DAY, YEAR AFTER YEAR,
WITH UNFAILING REGULARITY.**

**LEADING MANUFACTURERS THROUGHOUT THE WORLD LIKE THIS,
THEY ALSO LIKE THE QUICK SERVICE WHEN REPLACEMENTS
DO BECOME NECESSARY. SO THEY SPECIFY ADCOLA.**

WHY DON'T YOU!

**AVAILABLE FROM SHOPS EVERYWHERE
OR DIRECT FROM**

**SALES & SERVICE DIVISION,
ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4.**

TELEPHONE 01-622 0291

**SEND COUPON
FOR LATEST LEAFLET**

NAME	_____
ADDRESS	_____

P.W.167	_____

Lasky's Radio

LASKY'S RADIO ESTABLISHED OVER
36
YEARS

SKYROVER Mk II



COMMUNICATIONS RECEIVER

A completely new short wave receiver exclusive to Lasky's, at a real economy price. Four valve line up using one each 6BE6, 6BA6, 6AV6 and 6AR5 valves, gives highly sensitive reception and powerful gain. Switch selected 8W frequency range cover: 1.5 to 30 Mc/s in three separate bandspread ranges and full 500-1,400 Kc/s. Vernier reduction

AM medium waveband cover in one range 500-1,400 Kc/s. Vernier reduction drive tuning with fine hair line cursor. Controls include volume on/off, BFO, Band selector. Power on indicator lamp. External antenna connections and mains fuse at rear. 8 ohms internal speaker plus standard 5mm jack socket for phones on front. For 220/240V AC mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9 1/2 x 6 1/2 x 5 1/2 ins. complete with mains lead and full instructions.

LASKY'S
PRICE


£17.15.0

Post
5/-

TRIO

MODEL 9R-59DE

Brief spec.: 4 band receiver covering 550 Kc/s to 30 Mc/s continuous and electrical band spread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. Special features: SSB-CW, ANL, Variable BFO, 8 meter Sep. band spread dial, IF frequency 455 Kc/s, Audio output 1-5W, Variable RF and AF gain controls. For use on 110/250V A.C. Mains. Beautifully designed control layout finished in light grey with dark grey case, size 7 1/2 x 15 x 10 in. Weight 19 lbs. Fully guaranteed, complete with instruction manual and service data.

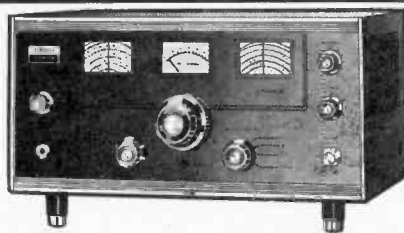

LASKY'S
PRICE

£42.0.0

Car. FREE

TWO BAND PUSH BUTTON TRANSISTOR CAR RADIO MODEL CR-62

A high quality all transistor superhet car radio that really breaks the quality/price barrier. A unique feature of this set are the four M/W band station preselection buttons which you yourself set to your own four favourite stations—this is in addition to full M/W band cover over 535-1805 Kc/s and full L/W band cover over 150-300 Kc/s (IF frequency 455 Kc/s). Externally adjustable aerial trimmers ensure maximum output. Six transistor (including one drift type) and one diode circuit provides powerful 2W output. The set is adjustable for use on either positive or negative ground 12V systems (external line fuse fitted). Standard mounting size 6 1/2 x 5 1/2 x 2 1/2 in.—front panel (in. larger all round—finished in anodised aluminium with black push buttons. Complete with mounting brackets, full installation instructions and 2 baffle boards (for round or elliptical speaker). Fully guaranteed.



LASKY'S
PRICE

£9.19.6

Post 5/-
8 x 4 in. dynamic speaker 17/6 extra—
Post FREE

MANUAL TUNING MODEL OF CR-62 AVAILABLE. £7.19.6.
SPECIAL OFFER—LOCKING CAR AERIAL Model 83003 five section 43" extension heavy chrome telescopic wing mounting type with unique locking device to protect the antenna when closed. Complete with mounting bracket, lead and plug and two "keys". LASKY'S SPECIAL PRICE 39/6 Post. Free with the CR-62. Post Sep. 2/6.

WIEN

FMX-1917 AM/FM STEREO TUNER AMP

A new solid state AM/FM Multiplex tuner Amplifier offering excellent quality and pleasing design at a price you can afford. Brief spec.: 18 transistors, 9 germanium diodes, 1 variable diode and 1 silicon rectifier. Single ended push pull amplifier—output 5W RMS per channel into 8 ohms. Frequency response 30c/s to 12 Kc/s. Frequency range: FM—88 to 108Mc/s, AM—535 to 1605Kc/s. Stereo separation 15dB at 100 µV input. External FM aerial; built-in ferrite rod antenna for AM. Controls: Balance, Mode, Tone, Vol./on-off, tuning. Input for ceramic phono pick-up. Powered by 220/250V A.C. 50/60c/s. Extremely well made oiled walnut cabinet with large clear tuning dial (black/grey/silver trim). Size 14 x 8 1/2 x 5 1/2 in.



LASKY'S
PRICE

£29.0.0

Carriage FREE

"COMPACT" STEREO AMP

Lasky's 5 x 5 watt 'Compact' integrated stereo amp, with unique provision for record deck to be mounted in the top of the cabinet. Employing 10 silicon transistors and 4 diodes the amplifier delivers up to 5 watts per channel RMS into 15 ohm speakers, with negligible distortion. Bass, treble, balance and volume controls plus mono/stereo mode switch. Inputs suitable for medium output ceramic cartridges, radio or tape input, plus tape record output.



The top of the amplifier will accept any turntable up to 13 x 15 in. The stereo 'Compact' is of very slim proportions with distinctive blue/silver front panel, teak side panels and top (motor board) covered in black leather grain P.V.C. Size 14 1/2 x 3 1/2 x 14 in. For 220/240V A.C. This is certainly the ideal basis for a low cost home stereo 'Compact' system—see Package offer below.

LASKY'S PRICE

£21.0.0

Post 7/6

SUGGESTED PACKAGE DEAL

Lasky's "Compact" amplifier.
2 Foster FCS-104 speakers.
Garrard 2028TC with stereo cartridge.

£42

Post 15/-
Perspex cover 70/- extra

MIDLAND Model 10-502 VHF AIRCRAFT BAND CONVERTER

An entirely new item for the radio enthusiast bringing instant reception of the ground-to-air, air-to-ground waveband. For use with any standard AM or FM radio covering 535 to 1605 Kc/s, 88 to 108Mc/s respectively—with no electrical conversion or connection required. The Model 10-502 self powered by one 9V (PP3 type) battery is merely placed close to the receiving set and then tuned over 110 to 135Mc/s which covers the whole aircraft communications band. Volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the vol. controls of each accordingly. The Model 10-502 has a smartly designed black plastic cabinet with brushed metal front panel and 18 in. chrome telescopic antenna, size only 4 x 2 1/2 x 2 1/2 in. (inc. knob). Complete with battery and full instructions.



LASKY'S
PRICE

79/6

Post 3/6

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 3271

Open all day, 9 a.m.—6 p.m. Monday to Saturday

33 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-636 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel.: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centres

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2573

Open all day, 9 a.m.—6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2 Tel.: 01-723 9789

Open all day Saturday, early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117).....	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117).....	5/7
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117).....	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117).....	6/-
Rod Aerial	RA2W.....		12/6
Driver Transformer	LFDT4/1.....		9/6
Output Transformer	OPT1.....		10/6
Printed Circuit	PCA1.....		9/6

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	7/6
T41/2E	2nd I.F. Transformer	7/6
T41/3T	3rd I.F. Transformer	10/6
T41/3T	B.F.O. Coil	10/6

Details of these and our other components are given in an illustrated folder which will be supplied on request with 4d. postage please.

WEYRAD (ELECTRONICS) LIMITED
SCHOOL STREET, WEYMOUTH, DORSET

FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble - 10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED

Only **28 Gns.** + P & P 17/6

H. P. terms available. Dep. £9.16.0 & 12 monthly payments of 36/9 (Total H.P. £31.17.0). Send £10.13.6 today.

Amplifier available separately at only 17 Gns.

FANTASTIC BARGAIN OFFER!

"TRANSCONTINENTAL"

FULLY TRANSISTORISED STEREOPHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer - a complete radiogram at half normal price **ONLY 34 1/2 GNS.** 17/6

10 Watts Total output
17 Transistors & 10 diodes

EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY

H.P. available £12.1.6 dep. plus 18 monthly payments of 32/- (Total H.P. £40.17.6).

Send £12.19.0 today.

Callers Welcome

POST THIS COUPON NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name

Address

LEWIS radio 100 CHASE SIDE, SOUTHGATE. Dep. P569 LONDON, N.14. TELEPHONE PAL 3733-9668

F.A.L. Phase 32

You must hear this superb unit



15 + 15 WATT HIGH FIDELITY OUTPUT

Recommended Retail Price **ONLY 35 Gns.**

SOLID STATE STEREO AMPLIFIER

- ★ *Excellent performance*
- ★ *High grade components and transistors*
- ★ *Impressive technical specification*
- ★ *Attractive appearance*
- ★ *Modest cost*

Housed in Teak veneered Cabinet, Switched selection of Mic., Mag. P.U., Ceramic P.U., Radio Tuner, Tape Rec.

Available from your local Hi-Fi Dealer

Wholesale and Retail enquiries to Manufacturers

FUTURISTIC AIDS LTD, 103 Henconner Lane, Leeds 13

SEND S.A.E. FOR FULLY DESCRIPTIVE LEAFLET

VALUABLE NEW HANDBOOK **FREE** TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

RADIO ENGINEERING

Advanced Radio — Gen.
Radio — Radio & TV
Servicing — TV Eng. —
Telecommunications — Sound
Recording — Automation —
Practical Radio — Radio
Amateurs' Exam.

ELECTRICAL ENG.

Advanced Electrical Eng. —
Gen. Electrical Eng. —
Installations — Draughts-
manship — Illuminating Eng.
— Refrigeration — Elem.
Electrical Science — Elec-
trical Supply — Mining Elec.
Engineering.

CIVIL ENGINEERING

Advanced Civil Eng. — Gen.
Civil Eng. — Municipal
Eng. — Structural Eng. —
Sanitary Eng. — Road Eng.
— Hydraulics — Mining
Water Supply — Petrol Tech.

ELECTRONIC ENG.

Advanced Electronic Eng. —
Gen. Electronic Eng. —
Applied Electronics — Prac.
Electronics — Radar Tech. —
Frequency Modulation —
Transistors.

MECHANICAL ENG.

Advanced Mechanical Eng. —
Gen. Mechanical Eng. —
Maintenance Eng. — Diesel
Eng. — Press Tool Design —
Sheet Metal Work — Welding
— Eng. Pattern Making —
Inspection — Draughtsman-
ship — Metallurgy — Pro-
duction Eng.

AUTOMOBILE ENG.

Advanced Automobile Eng. —
Gen. Automobile Eng. —
Automobile Maintenance —
Repair — Automobile Diesel
Maintenance — Automobile
Elec. Equipment — Garage
Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS IN-
CLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRU-
MENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B.,
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT.
OF EDUCATION, ETC.

British Institute of Engineering Technology

453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT
CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theore-
tic Course for beginners in
Radio, T.V., Electronics, Etc
A.M.I.E.R.E. City & Guilds
Radio Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS

The specialist Elec-
tronics Division of
B.I.E.T.
NOW offers you a
real laboratory train-
ing at home with
practical equipment.
Ask for details.

B.I.E.T.

You are bound to benefit from reading
"ENGINEERING OPPORTUNI-
TIES", and if you are earning less than
£30 a week you should send for your
copy *now*—FREE and without
obligation.

POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING
OPPORTUNITIES." I am interested in (state subject,
exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT TO CUT THIS PAGE



THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

TRANSISTORS etc.

AC107	3/-	OC35	7/6
AC126	2/-	OC44	2/0
AF115	3/-	OC45	2/0
AF116	3/-	OC70	2/3
AF117	2/6	OC71	2/-
BFY18	4/6	OC72	2/2
GET113	2/6	OC73	2/3
OA5	1/6	OC75	2/2
OA9	1/8	OC81	2/-
OA81	1/6	OC81D	2/-
OA85	1/6	OC82D	2/3
OA91	1/6	OC140	5/-
OC23	6/6	OC169	3/6
OC23	6/6	OC170	2/2
OC25	5/-	OC171	2/2
OC26	5/-	OC202	4/6
OC28	6/6	TK22C	1/6

Crystal Diodes—6 for 2/6. (7d.).

Also 81uF 350V 1/2, 25uF 25V 1/3 and 50uF 50V 1/8. Other electrolytics in current list. Postage, Packing and Insurance all above 7d. up to 3; 1/- from 4-11; 12 and over paid.

2 GANG VAR. CONDENSER: Mod., air-spaced, .0005 ca. sec. 5/- (1/-).

TRANSFORMERS: Sub-min Output (3Ω for OC72 etc.) 2/6 (6d.).

MULTIMETER: 20,000 Ω/V D.C., 10,000 Ω/V A.C. 0-5/25/50/250/500/1K volts D.C. ● 0-10/50/100/500/1K volts A.C. ● 0-50/1A/2-5mA/250mA D.C. ● 0-6KΩ/6 meg Ω ● 10μuF-0.01mfd./1mfd. ● —20 to +22dB. ● Case. ● Complete with test leads and instructions. ● Over-load protected 1969 model with every refinement. £4.75 (2/6).

JUNIOR MODEL at 95/- (1/6) 1000 Ω/V described in free list.

SOLDERING IRON. Slim Mod. British High speed, 8in., all parts replaceable, fully guaranteed for professional, radio and general D.I.Y. use. 18/6 post free. **GUN TYPE.** Built in transformer for instant power, 46/- (4/6).

DIAMOND STYLII Replacements for BSR TC8LP, TC8 STEREO, and TC8LP/STEREO; COLLARO "O"; RONETTE BF40LP; GARRARD GC2LP and GC8LP; ACOS GP65/67; all at 7/6 each (6d.).

ACOS GP91 BT/LP; BSR 8T4 and 8T9; SONOTONE 9TA and 9TAC; PHILIPS 43306. All at 15/6 (6d.).

SAPPHIRE all the above 7/6 types only, also ACOS GP37 at 3/3 each (6d.). ACOS GP91 at 6/9 (6d.). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES. all fitted Styl and Standard fittings. Mono GP67/82, 13/6. ● Mono de Luxe GP91/2, 17/-, ● Stereo Compatible—Mono which also plays Stereo records monaurally with min. wear, GP91/8C, 19/6. ● Latest Stereo GP93, 22/-, ● Ceramic Stereo, top quality hi-fi cartridge, GP94, 25/6 (all 1/-). New **MOVING MAGNET STEREO TYPE.** 4 coil, 4 pole, diamond stylus at £4.12.6 (post etc. paid). Full details in list of this, the lowest price high quality cartridge available.

PP3 ELIMINATOR (A.C.) 17/6. (1/6) **TWO STATION TRANS. INTER-COM.** Excellent baby alarm. Instant, easy fitting. All you require 52/6 (3/-).

FOUR TRANSISTOR 3 WATT AMPLIFIER 2 1/2 x 2 1/2 x 1 1/2; 9V: 8Ω and 16Ω, excellent on 3Ω speakers; 45/6 (1/6).

TELEPHONE AMPLIFIER, transistorised, batt. op. Fitted in seconds—leaves both hands free when phoning 52/6 (1/6).

Extra High Torque **MINI-MOTOR**, 4 1/2 to 12V. 1 1/2 x 1/2 in. 5/- (9d.). 9,000 r.p.m. Mech. REV. COUNTER to 999, reset wheel, for T/records etc. 4/6 (1/-).

BATTERY CHARGER 8V, 8 amp, sturdy, neat; 2 amp. 12V 85/- 6V/12V 29/- (4/6 either type). Larger British 6V and 12V with meter, fuse, etc. 42/6 (6/-). All absolutely complete (4/6 either type).

RECORDING TAPE: Finest quality British Mylar. **STANDARD:** 5in. 600ft. 7/8, 5 1/2in. 850ft. 8/8, 7in. 1200ft. 11/8. **LONG PLAY** 5in. 900ft. 10/-, 5 1/2in. 1200ft. 11/8, 7in. 1800ft. 18/-, (1/3 reel). Other types in our list.

MICROPHONES—CRYSTAL. MIC91. Desk, 18/3; MIC45, curved hand grip 17/8; Stick "60" 20/3; Stick "39" 26/6 (1/6 each type). Cream plastic hand type 7/6, or with "strut" stand, switch and 2 leads with 2-5 and 3-5 plugs 11/-, Lapel (or hand) with clip 6/6 (1/-).

25in. finished metal tapered stick type with neck cord and adaptor to fit standard floor stands, 14/- (1/6). **DYNAMIC:** Cream hand/table 14/- (1/-). MB10 50KΩ, 3 1/2 x 1/2 in. with Base, Adaptor and Neck Cord 37/6 (2/6). MB11, similar, but fixed on flexible Swan neck to switch-fitted base 42/6 (2/6). PIZZO 50KΩ black/chrome 2in. dia. x 1 1/2 for stand use only. Standard inside thread 33/6 (1/6).

CARDIOM DYNAMIC OMNI-DIRECTIONAL: Professional types now available to all at really sensible prices. Extremely handsome with every possible new feature making for perfection in sound amplification. For use in or out of doors—full details in our list. Both wire-mesh screen types. For stand mounting: "Square" type, 308, £5.10.0 (5/-).

"Ball Type" with built-in vol. control, on/off switch and optional hi/lo impedance (50kΩ or 600Ω), £5.17.6 delivered free. An exactly similar mike bearing a world famous name is sold at over twice this price. All mikes are supplied with leads.

SPEAKERS: 12in round, fitted Tweeter, 6W, 3 or 15Ω (state which), 35/6 (5/6); 2 1/2in. 80Ω British, 5/- (1/-); 2 1/2in. 3Ω 6/6 (1/-); 6 x 4 heavy duty 3Ω 15/6 (3/6) or for Stereo 22/6 pair, post etc. paid. 2 1/2 x 3 1/2 in. 8/6 (1/-). **HEADPHONES** High Res. 2000Ω ca. Earpiece 18/6 (1/6); Stereo Dyn 8-16Ω 63/- (3/-); **EARPIECES** with lead etc., Min. Plug Magnetic 1/6; Crystals 2/6 (either 6d.).

MICROPHONE INSERTS: Diameter 1-75in. or 0-9in either size 5/6 (6d.).

AERIALS, Car Types: Telescopic, vandal proof, locks retracted, 2 keys and all fittings, 22/6 (2/6) Motorised, 12V, 5 section, complete £7.10.0 (5/-).

FOR ALL PORTABLES AND F.M. SETS. Telescopic 5 section 5/-22in. with swivel, 5/-, 7-Section 5 1/2-32in., no swivel, screw hole in base, 6/6. ● 10-section 6 1/2-47 1/2in., no swivel, screw hole in base, 12/6 (1/- all sizes).

SWITCHES: Standard toggle, metal, 250V 2A. One hole fixing: SPST 2/3, SPDT 2/6. DPST 3/-, DPDT 3/6. Slide types. Sub-min. DPDT 1/6 each. Small DPDT 3 way, centre "off" 1/6. Reed magnetic on/off 1/6 (7d. each, all types). Rotary Switches etc. in list.

VIBRATORS: Famous makes only. 12 volt 4 pin non-synch 2/6. 12 volt 7 pin synch 10/- 6 volt 7 pin synch 10/- (1/- each, all types).

MAINS NEON TESTER: Fly leads 2/- (7d.). Pocket screwdriver type 3/6 (6d.). **PLUGS:** 8d. Jack, plastic body 2/- Screened 2/6. Sockets 1/6 (all 7d.). **VALVE HOLDERS:** B7G or B9A, Moulded 6d. (7d. up to 4, 1/- over 4). **CONNECTING WIRE:** 5 coils asstd. coils, each 5 yds. Solid Core 2/3. Flexible 2/6. Super thin for transistor wiring etc. 3/- (6d. all types, per 6 coils). **PICK-UP WIRE.** Twin Super thin Fly. Screened, Sheathed, 1 1/2 yd. (6d. up to 6 yds., over 6 yds. post free). **TWIN MIKE CABLE:** 1 1/2 yd. (up to 6 yds. 8d., over post free). **SINGLE MIKE CABLE:** 7d. yd. (up to 6 yds. 8d., over post free). Both flexible, screened and sheathed. ● **FEEDER CABLE:** Twin 1/8 in. "fig. 8", 80Ω, or flat 300Ω transparent polythene insulated, either 6d. per yd. (as mike cable).

CURRENT LIST: Sent with all orders or free for a.s.e. details of cable, croc., clips and leads, Continental dtp page for Grundig, Telefunken equipment, etc., dials, plugs and sockets, panel meters, record players and tape recording accessories, rectifiers, relays, wire wound resistors, test equipment, test prods, tape recorder, special transistors, portable sets, car radio, more switches and other components, tools, Verboord, etc., etc. If interested in surplus equipment and units please say so. This advertisement cancels all previous ones and lists supplied prior to March 31st, 1969.

TERMS: Cash with order only. No C.O.D. or call service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted. Charges apply to G.B. and Eire only. Overseas air or surface mail extra at cost. S.A.E. please for all enquiries.

FESTEAD ELECTRONICS

(PW18)

LONGLEY LAKE, GATLEY, CHADDLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or call service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted. Charges apply to G.B. and Eire only. Overseas air or surface mail extra at cost. S.A.E. please for all enquiries.

www.americanradiohistory.com

TELEVISION BARGAINS

Due to Bulk Purchase we offer Ex Rental 12 channel T.V.s. Well maintained and tested. Tubes 100% guaranteed. Slimline 17" Peto Scott 732, Ultra V17/70, Regentone 7en 17, Cossor 874, Alba T44, F.M. all £8.0.0 each. 21" Ultra V21/70 £12.0.0. Semi slim 17" Alba T655, Regentone 7en 4 7en 8, Sobell T178, T179, Bush TV85, £7.0.0 each.

Many others available, all worth double

Carriage £1 Terms C.W.O.

We stock all spares for most pre-1962 T.V.s

Send S.A.E. for price list to:


D. WEBB

58 Chanterlands Avenue,

Hull, Yorkshire.

Tel: Hull 43281 and 36016


RADIO COMMUNICATION HANDBOOK

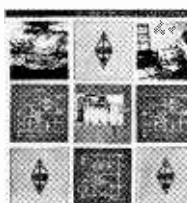

amateur radio circuit book



amateur radio techniques

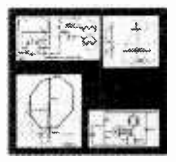

Radio Communication Handbook

832 pages of everything in the science of radio communication. The Handbook's British origin ensures easy availability of components. The standard work in its field. 69s post paid

Amateur Radio Circuits Book

Dozens of clear, concise circuit suggestions with the basic constructional details. 120 spiral bound pages lie flat when open for convenience. 11s 6d post paid

Amateur Radio Techniques

All the good ideas are here. An anthology of the famous "Technical Topics" column from RADIO COMMUNICATION. Fascinating reading and an invaluable information source. 13s 6d post paid

All these and many more, plus free details of the

RADIO SOCIETY OF GREAT BRITAIN


from
35 DOUGHTY STREET, LONDON, WC1

- ALL ITEMS OFFERED ARE FULLY GUARANTEED AND BACKED BY COMET.
- OPENING HOURS, OPEN DAILY UNTIL 5.30 p.m. (8.0 p.m. THURS. AND FRI. EVENINGS) AND 5.0 p.m. SATURDAY.
- COMPLETE FREE PRICE LIST CONTAINING OVER 500 ITEMS ON REQUEST.

Comet Discount Warehouse DELIVERY Comet guarantee that all prices quoted are genuine. All items offered are available at time of offer.
Reservoir Road, Clough Road, Hull. Tel. 42363 Add 9/- for post and packing on all orders.

Here's a Selection of Models from the FREE HEATHKIT CATALOGUE

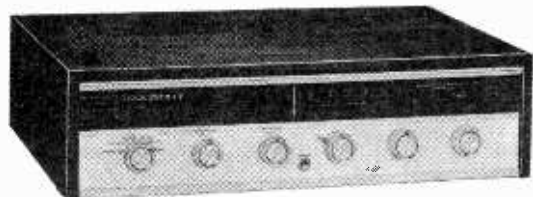
AVAILABLE AS EASY TO BUILD KITS OR READY-TO-USE MODELS



Kit K/AR-14 Ready to use A/AR-14
£54.2.0 P.P. 14/- **£76.12.0** P.P. 14/-
Cabinet £4.10.0. extra



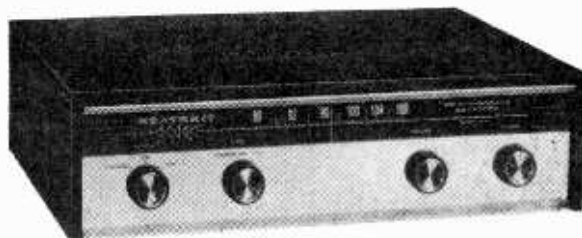Kit K/AR-17 Ready to use A/AR-17
£39.2.0 P.P. 11/- **£60.4.0** P.P. 11/-
Cabinet £3.10.0. extra



Kit K/AR-27 Ready to use A/AR-27
£22.12.0 P.P. 11/- **£32.14.0** P.P. 11/-
Cabinet £3.10.0 extra



BERKELEY LOUDSPEAKER SYSTEM

Use two for stereo. Best performance from a slim-line cabinet. Uses less than 1 sq. ft. of floor space. Available in Teak or Walnut finish.

Kit Ready to use
£21.4.0 P.P. 14/- **£24.0.0** P.P. 14/-

CHOOSE A QUALITY
HEATHKIT LOUD-
SPEAKER SYSTEM
TO GET THE BEST
FROM YOUR AUDIO
SET-UP.

Top Value in a 30 Watt FM Stereo Receiver, AR-14

● 31 transistor, 10 diode circuit for cool, instant operation with the transparent, natural sound only transistors can deliver ● $\pm 1\text{dB}$, 15 to 50,000 Hz at 10 watts per channel continuous (20 watts total). 15 watts per channel IHF music power (30 watts total) ● Wide-band AM/FM stereo tuner plus two preamplifiers and two power amplifiers. ● Front panel stereo headphone jack. ● Compact—just $3\frac{3}{4}''$ H x $15\frac{1}{2}''$ W x $12''$ D. ● Custom install it in wall, your own cabinet, or use as a free standing unit.

Kit K/AR-14 (less cab.) kit £54.2.0. P.P. 14/-
A/AR-14 (less cab.) £76.12.0. P.P. 14/-
Cabinet extra: Teak or Walnut finish £4.10.0

Unbeatable Value in a 14 Watt FM Stereo Receiver, AR-17

● 28 transistor, 7 diode circuit for natural transparent sound, instant operation, long trouble-free life. ● 14 watts music power, 10 watts RMS from 25–35,000 Hz at $\pm 1\text{dB}$. ● Automatic stereo indicator light. ● Adjustable phase control for maximum separation. ● Complete front panel controls. ● Flywheel tuning. ● All critical circuits including FM "front-end" factory assembled and aligned. ● Circuit board assembly. ● Compact $10\frac{3}{8}''$ D x $3''$ H x $12''$ W. ● Front panel stereo headphone jack.

Kit K/AR-17 (less cab.) kit £39.2.0. P.P. 11/-
A/AR-17 (less cab.) £60.4.0. P.P. 11/-
Cabinet extra: Teak or Walnut finish £3.10.0

A Quality Table Radio FM Mono Receiver, AR-27

● 13 transistor, 6 diode circuit for high-fidelity sound reproduction, long life, low heat, freedom from hum, and service-free operation. ● 7 watts music power. ● $\pm 1\text{dB}$, 25 to 60,000 Hz at 5 watts. ● Input connectors for phonograph and auxiliary signals. ● Complete front panel controls. ● Flywheel tuning. ● Preassembled and prealigned FM tuner, all other critical parts factory aligned. ● Easy, circuit board assembly. ● Compact bookshelf size. ● 3-way installation ... wall, free standing or in a suitable cabinet. ● 117 v. A.C. or 210/240 v. A.C., 50 Hz operation.

Kit K/AR-27 (less cab.) kit £22.2.0. P.P. 11/-
A/AR-27 (less cab.) £32.14.0. P.P. 11/-
Cabinet extra: Teak or Walnut finish £3.10.0

A welcome awaits you at the Heathkit shops and showrooms
Retail shops with showrooms and Hi-Fi demonstration facilities at:—

The London Heathkit Centre, 233 Tottenham Ct. Rd., W.1.
The Birmingham Heathkit Centre, 17-18 St. Martins Hse., Bull Ring.
There is a showroom with Hi-Fi demonstration facilities at the Daystrom Factory, Bristol Rd., Gloucester.

★ Goods may be purchased at the retail shops at prices slightly higher than the advertised mail order price.
★ Orders may be placed at the retail shops for mail order despatch from the factory at mail order prices.

There's Something for Everyone in the HEATHKIT Electronic Range . . .



STEREO TAPE RECORDER, STR-1

A complete stereo system including speakers in one compact Transportable. Versatile recording facilities. Powerful output, 4 watts rms per channel.

Kit K/STR-1 £59.4.0 P.P. 11/-



STEREO AMPLIFIER, TSA-12

Fully transistorised. Fantastic performance at lowest cost. Many exceptional features.

Kit K/TSA-12 £32.16.0 P.P. 10/6
Cabinet £3.16.0 extra



PORTABLE VOM, IM-17

The latest solid-state circuit, plus rugged polypropylene case. For homeowners, hobbyists, service.

Kit K/IM-17 £13.12.0 P.P. 6/-



RF SIGNAL GENERATOR, RF-1U

100kHz to 200MHz in six bands. The specification is outstanding for price. A dependable service instrument.

Kit K/RF-1U £13.18.0 P.P. 6/-



VALVE VOLTMETER, V-7A

Popular size, 7 AC, DC, ohms range. Popular price.


Kit K/V-7A
£14.16.0 P.P. 4/6



HIGH PERFORMANCE CAR RADIO CR-1

Latest transistor circuit gives powerful output, 4 watts. For 12v pos or 12v neg earth systems.

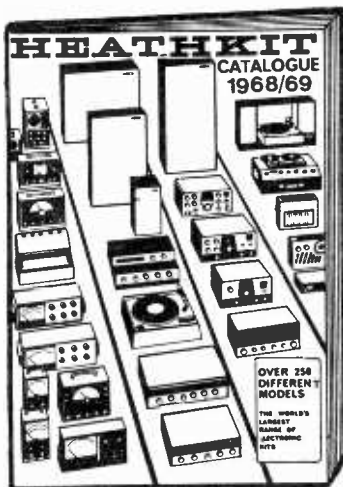Kit K/CR-1 (less speaker)
£13.11.3 P.P. 4/6 LS £1.2.9 extra



Send for the
FREE
Catalogue
and see for yourself, Today!

This catalogue describes these and many more kits and ready-to-use models for Stereo/Hi-Fi, Domestic Radio, Record Players, Amateur Radio, Short Wave, Test Instruments, Educational, Home Workshop, all at significant savings.



STEREO RECORD PLAYER, SRP-1

A complete stereo system including speakers in one compact portable. Plays mono or stereo records. Cool, crisp, bold sound.

Kit K/SRP-1 £28.12.0 P.P. 11/-



4 BAND RECEIVER, GR-64

Offers you the exciting world of shortwave at low-cost. Modern styling.

Kit K/GR-64 £22.8.0 P.P. 9/-



UXR-1



UXR-2

TRANSISTOR PORTABLES

UXR-1. The popular choice. Many de-luxe features.

Kit K/UXR-1 leather £13.14.0 P.P. 4/6

Kit K/UXR-1 colour case £12.14.0 P.P. 4/6

UXR-2. For clean, bold sound. Rugged leather case in black or brown.

Kit K/UXR-2 £15.16.0 P.P. 6/-

To
DAYSTROM LTD., Dept. PW-5, GLOUCESTER, GL2-6EE.

Please send me FREE CATALOGUE ☐

NAME

ADDRESS

Prices and specifications subject to change without notice

Aerial Wire: Coils of 25 yds. solid core, 2/3 plus 1/- P. & P.

Battery Eliminators for Transistor Supplies. 9v., 7½v., 6v., 29/6 plus 2/6 P. & P.

Condensers: Large range available from 6d. each.

Coax Sockets: Flush, 6d. plus 6d. P. & P.

Cartridges: Acos GP67/2G, 14/9; BSR TC8H, 30/-; TC8M, 28/6; X1M Inserts, 22/8, etc.

Ear Pieces: 2-5µ/m or 3-5µ/m Mag., 2/6 plus 1/- P. & P. 2-5µ/m or 3-5µ/m Crystal, 5/6 plus 1/- P. & P.

High Impedance Horns: 1½ to 4½ volt, ideal for alarms, 3/6 plus 1/- P. & P.

Loudspeakers: Large range. 2in. 8 ohm, 7/6; 4in. 8 ohm, 12/6; 5in. 8 ohm, 16/6 plus 2/- P. & P.

Transistors: Full range, i.e. OC44, OC45, OC71, OC82, 2/6; OC35, 9/-; Fet.MPF103, 9/6.

Transformers: 12 volt battery charger, £12.6. 250-0-250 volt 60mA, 18/9; 0-250 with 6-3 volt, 19/6 plus 3/6 P. & P.

Relays: 12 volt suitable for car alarm, 21/-; 6 volt AC, 28/6; 240 volt AC, 27/6 plus 3/- P. & P.

Ex. Govt. Panel Meters: 0-SM/A, 17/6; 0-300V AC/DC, 25/6 plus 2/7 P. & P.

Many other items, please send S.A.E. for free price list.



BOTHWELL ELECTRIC SUPPLIES (Glasgow) LTD.
54 EGLINTON STREET,
GLASGOW, G.5. Tel. 041 SOUTH 2904

Member of the Lander Group

4-STATION INTERCOM



£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideal suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

WIRE-LESS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price 12 gns. P. & P. 9/6 extra.

INTERCOM/BABY ALARM



65/-

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.



59/6

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days. WEST LONDON DIRECT SUPPLIES (P/W5) 189 KENSINGTON HIGH STREET, LONDON, W.8.

NEW RANGE BBC 2 AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 37/6.
11 element, 45/-; 14 element, 52/6; 18 element, 60/-.
Wall Mounting with Cranked Arm, 7 element, 80/-; 11 element, 87/-; 14 element, 75/-; 18 element, 82/6.
Roof Mounting with 2in. clamp, 7 element, 42/6.
11 element, 55/-; 14 element, 62/-; 18 element, 70/-.
Chimney Mounting Arrays, Complete, 7 element, 72/6.
11 element, 80/-; 14 element, 87/6; 18 element, 95/-.
Complete assembly instructions with every unit. Low Loss Cable, 1/8 yd. U.H.F. Preamps from 75/-. State clearly channel number required on all orders.

BBC - ITV AERIALS



BBC (Band 1). Telescopic loft, 25/-; External S/D, 30/-; "H", £215.0.
ITV (Band 3). 3 element loft array, 30/-; 5 element, 40/-; 7 element, 50/-.
Wall mounting, 3 element, 47/6.
5 element, 52/6.
Combined BBC/ITV. Loft 1+3, 40/-; 1+5, 50/-; 1+7, 60/-; Wall mounting 1+3, 57/6; 1+5, 67/6; Chimney 1+3, 67/6; 1+5, 75/-.
VHF transistor preamps, 75/-.

COMBINED BBC1 - ITV - BBC2 AERIALS 1+3+9, 70/-; 1+5+9, 80/-; 1+5+14, 90/-; 1+7+14, 100/-.
Loft mounting only. Special leaflet available.
F.M. (Band 2). Loft S/D, 15/-; "H", 32/6.
3 element, 55/-; External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/4.
Outlet boxes, 5/-; Diplexer Crossover Boxes, 13/6. C.W.O. or C.O.D. P. & P. 6/-.
Send 6d. stamps for illustrated lists.

Callers welcomed - open all day Saturday

K.V.A. ELECTRONICS (Dept. P.W.)

40-41 MONARCH PARADE
LONDON ROAD, MITCHAM,
SURREY 01-648 4884

AIRCRAFT-PLUS GENERAL V.H.F. TELECOMMUNICATIONS BAND REC.

Listen to the thrills of aircraft, pilots and airports at work. Also Civil Depts., Fire and Ambulance services. Also taxis, Gas and Electricity services. Ideal for receiving 2 metre amateurs. Gives super reception within the range of all transmissions. A fully transistorised receiver covering 87-145Mc/s VHF broadcasts. Robust attractively finished metal cabinet size approx. 7 x 7 x 3in. Operates from a 9 volt internal battery. Speaker or earphone output. Price only £8.19.6, carr. and ins. 10/6.

COMMUNICATION RECEIVER TYPE T.R.G.D.X./20.C.

Brand new fully transistorised Communications Receiver. Specifications: 4 complete ranges 550 Kc/s to 30 Mc/s, covering all amateur bands, shipping and trawler bands, and broadcast bands. A highly efficient double tuned superhet, comprising R/F aerial tuning section, A.V.C. and built-in B.F.O. for C.W. or SSB reception. Ideal for fixed or mobile reception. Operates from Standard 9 volt battery, provided that fits internally. Gives over 1 watt audio output. With speaker and headphone output. Hammer finished robust steel case of pleasing modern design with all controls on well set-out front panel. Size approx. 9 x 6 x 6in. British manufacturer. Due to huge purchase we can offer these excellent receivers at less than half their normal worth. Complete with handbook £16.10.0. Carr. and ins. 15/-; Headphones if required 17/6 per pair, p. & p. 2/6.



TELEPHONE BARGAIN

The Bargain of the year. Standard type desk telephone complete with dial and cord. Not new but in good condition. Only 15/- each, p.p. 5/-; Two for 30/- post free. Four for 50/- post free. Limited stocks.

RUN YOUR 19 SET TX and RX FROM THE MAINS

We make an excellent power supply unit. Simply plug into your 19 set, and the transmitter and receiver is fully operational. Brand new in attractive louvered steel case. Operates from 200/250V A.C. Only £6.10.0 carr. and ins. 10/-.

AIR/SEA TRANS/REC. RESCUE

Compact V.H.F. Trans./Rec. Fits in the pocket. Consists of Mike/Speaker, amplifier, aerial, transmitter and receiver. Were made to operate up to 100 miles depending on terrain. Operates from dry batteries. Completely self-contained. Cost Govt. over £50 each. Regulations state must not be operated in UK so please mention "For Diamanting purposes only" when ordering. Price £210.0 each, p. & p. 10/-; Two sets for £50.0, post free. Four sets £8, carriage free. Bulk sale of 10 sets £15, carriage £1. Export enquiries invited.



NEW SHOP NOW OPEN at

SCOOP PURCHASE TRANSFORMER SALE

Bulk purchase enables us to offer the following transformers at these ridiculously low prices. Made by a famous manufacturer and fully tested and guaranteed. Charger Transformers, 0-9-15V 2A, 8/6 each, p. & p. 2/6. Two for 17/6, post free. Transistor Power Pack Type 6-3V at 2A, 7/6 each, p. & p. 2/6. 12V at 2A, 12/6 each, p. & p. 2/6.

MINIATURE MOVING COIL SPEAKERS 1½in. diameter. Only 3/6 each, p. & p. 1/6. Two for 8/6 post free. Four for 15/- post free.

38 BRIDGEND, MEADOW LANE, LEEDS 1

Open 9-0am—5-30 pm daily and all day Saturday

Callers please bring copy of advert for special opening offer, a de-luxe soldering iron for only 8/6, should be 27/6

RUN TELEVISION-LIGHTING DRILLS ETC-ETC from a 12 VOLT CAR BATTERY

POWER CONVERTER (De-luxe model). 12 volt D.C. input gives a 240 volt, 300 watt output enabling you to run all your AC/DC equipment and fluorescent lighting. Thousands of uses. Provides a portable Power Supply. Contained in attractive louvered steel case. Complete with leads and clips and full instructions. As supplied to Hospitals and Universities. Recommended price over £30 Our Price £24.10.0, carriage and insurance 10/-; Not to be confused with Heavy Duty Dynamometer units.


GLOBE SCIENTIFIC LTD
DEPT. P.W. 24 CAWOODS YARD,
MILL STREET, LEEDS 9

Build yourself a quality transistor radio

backed by our
after sales service!

roamer seven mk IV SEVEN WAVEBAND PORTABLE

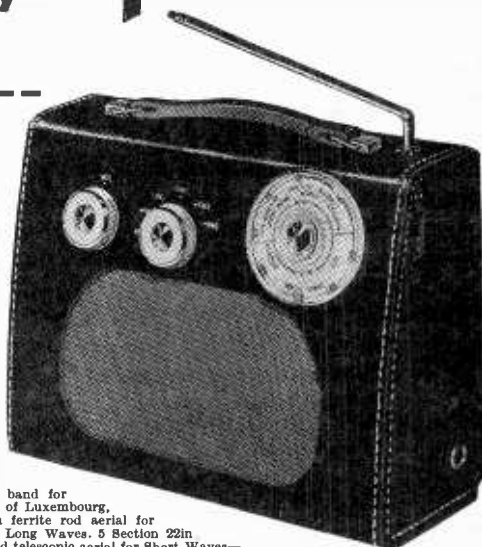SEVEN TUNABLE WAVEBANDS—
MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.



pocket five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND (to 50
metres approx.) PORTABLE
WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. All first grade components—7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
44'6 P. & P.
3/6

Extra M.W. band for easier tuning of Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. 5 Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push pull output. 7 transistors and 2 diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker for rich-tone volume. Air spaced ganged tuning condenser. Volume on/off control wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. First grade components. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build.

Total building costs
£5.19.6 P. & P.
7/6 Personal Earpiece with switched socket for private listening 5/- extra.

Parts price list and easy build plans 3/- (Free with parts).

transona five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND (to 50
metres approx.) PORTABLE
WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½in. x 1½in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. All first grade components. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
47'6 P. & P.
3/9

NEW LOOK melody six

TWO WAVEBAND PORTABLE

8 stages—6 transistors and 2 diodes. Covers Medium and Long Waves. Top quality 3½in. Loudspeaker for quality output and also with Personal Earpiece with switched socket for private listening. Two R.F. stages for extra boost. High "Q". Ferrite Rod Aerial. Push-pull output. Handsome pocket size case with gilt fittings. Size 6½ x 4 x 2½in. Easy build plans and parts price list 2/- (FREE with parts).



Total building costs
69'6 P. & P.
4/3

super seven

THREE WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive case size 7½ x 5½ x 1½in. with gilt fittings. The ideal radio for home or outdoors. Covers Medium and Long Waves and Trawler Band. Special circuit incorporating 2 R.F. Stages, push pull output, ferrite rod aerial, 7 transistors and 2 diodes, 3in. speaker (will drive larger speaker) and all first grade components. Easy build plans and parts price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 5/- extra.)



Total building costs
69'6 P. & P.
4/6

roamer six

SIX WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. All top grade components, 9 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts). (Personal Earpiece with switched socket for private listening 5/- extra.)



Total building costs
79'6 P. & P.
4/6

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. Bedford 52367

I enclose £..... please send items marked

ROAMER SEVEN	☐	ROAMER SIX	☐
TRANSONA FIVE	☐	SUPER SEVEN	☐
POCKET FIVE	☐	MELODY SIX	☐

Parts price list and plans for

Name

Address

PW5

* Callers side entrance Stylo Shoe Shop

* Open 10-1, 2.30-4.30 Mon-Fri. 9-12.30 Sat

BI-PAK SEMICONDUCTORS

500 CHESHAM HOUSE,
150 REGENT ST., LONDON, W.1.

KING OF THE PAKS SUPER PAKS

Unequalled Value & Quality
BI-PAK NEW—UNTESTED
SEMICONDUCTORS

Satisfaction GUARANTEED In Every Pak, or money back.

PAK NO.	DESCRIPTION	10/-
U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 Watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U12	12 Silicon Rectifiers EPOXY BY126/127	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 2S104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	30 Silicon NPN Transistors like BC108	10/-
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	10/-
U21	30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
U22	10 1-Amp Glass Min. Silicon Rectifiers High Volts	10/-
U23	30 Madt's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-Amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like 1N914 Micro-min	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1 Amp SCR's TO-5 can up to 600 PIV CRSI/25-600	20/-
U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
U31	20 Sil. Planar NPN trans. low noise 2N3707	10/-
U32	25 Zener diodes 400mW DO-7 case mixed Vits. 3-18	10/-
U33	15 Plastic case 1 Amp silicon rectifiers W4000 series	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

FULLY TESTED

AC107	3/6
AC126-7-8	2/6
AF116-117	3/6
AF139	10/-
AL102	15/-
BC107-8-9	5/-
BFY50-51-52	7/6
BSY26-7	3/6
BSY28-9	4/6
BSY95-95A	4/6
OC22-25	5/-
OC26-35	5/-
OC28-29	7/6
OC44-45	1/6
OC71-81	1/6
OC72-75	2/6
OC81D-82D	2/3
OC82	2/6
OC140	5/-
OC170	2/6
OC171	3/6
OC201	7/6
ORP12-60	8/6
OC71	8/6
OA5-10	1/9
OA7	2/6
OA70	1/3
OA79	1/9
OA81-85	1/6
OA81	1/3
OA85	1/9
OA200	3/-
OA202	3/6
2N696-7	5/-
2N706	3/6
2N708	5/-
2N180	15/-
2N2646	5/6
2N2712	2/6
2N2926	2/6
MAT100-101	3/6
MAT120-121	3/6
ST140	3/6
ST141	4/-

SIL. RECTS TESTED

PIV 750mA 3A	10A 30A
50 1/- 2/8	4/8 8/8
100 1/3 3/3	4/8 15/-
200 1/9 4/-	4/9 20/-
300 2/3 4/8	6/8 22/-
400 2/6 5/8	7/8 25/-
600 3/- 6/-	8/8 30/-
800 3/3 6/8	9/- 37/-
1000 3/6 7/8	11/- 40/-
1200 5/- 9/3	12/6 50/-
1500 6/8 11/8	15/-

PRINTED CIRCUITS

EX-COMPUTER
Packed with semiconductor and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/-. Plus 2/- P. & P.

UNIJUNCTION

UT46	Eqvt. 2N2846	7/6
Eqvt. TI843		
FET's		
2N3819		10/-
2N3820		25/-
MPP105		8/-
AD161-162	NPN-PNP	
Comp. Pair	12/6 pr.	
28034		15/- ea

TRANSISTOR EQUIVALENT BOOK

52 pages of Cross References for transistors and diodes, types include British, European, American and Japanese. Specially imported by BI-PAK 10/- each.

PLEASE NOTE.—To Avoid any further Increased Postal Charges to our Customers and enable us to keep our "By lined our Despatch Order Department and we now request you to send all your orders together with your remittance, Direct to our Warehouse and Despatch Department, postal address:—BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS. Postage and Packing Still 1/- per order. Minimum Order 10/-.

ERSIN



for quick,
easy, reliable
soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required. Ersin Multicore Savbit Alloy also reduces wear of copper soldering iron bits.



SIZE 5 HANDY SOLDER DISPENSER

Contains 10 ft. coil of 18 s.w.g. Ersin Multicore Savbit Alloy. 2/6 each.



SIZE 15 SOLDER DISPENSER

Contains 21 ft. coil of 60/40 Alloy. 22 s.w.g. Ideal for small components, transistors, diodes, etc. 3/- each.



SIZE 12

Ideal for home constructors. Contains 90 ft. of 18 s.w.g. Ersin Multicore Savbit Alloy on a plastic reel. 15/- each.



BIB MODEL 8 WIRE STRIPPER AND CUTTER

Strips insulation cleanly and quickly, fitted with unique 8 gauge wire selector. Plastic handles. 9/6 each.



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

MARTIN

IS HIGH FIDELITY

plus

ADD-ON-ABILITY

THRILLING POWER

DEPENDABILITY

GENUINE ECONOMY

How would you like to start with a simple amplifier, say, and add to it until it became a fully stereo twenty watt amplifier with FM tuner and facilities to take the most sensitive low output pickups ever made? With Martin Audiokits it's easy, for with these superbly engineered all-transistor prefabricated units, success is built in from the start and you build to your own preferred plan. IT'S A MONEY SAVING SCHEME, TOO.

Details from:

● Trade enquiries invited.

MARTIN ELECTRONICS LTD., 155 High St., Brentford, Middlesex. ISLeworth 1161

To MARTIN ELECTRONICS, 155, High Street, Brentford, Middlesex.

I have not had your leaflets before. Please send them on
AMPLIFIERS ☐ FM TUNER ☐ RECORDAKITS ☐
(Tick as required)

NAME

ADDRESS

WP5

TECHNICAL TRAINING

*in radio television
and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.)

NAME

ADDRESS

5/69

INTERNATIONAL CORRESPONDENCE SCHOOLS

WIRECOMP ELECTRONICS

SPRING SALE

BRAND NEW EMI Emitape

Famous British made tape—brand new and perfect in makers sealed cartons.

Type 88/4	300ft 4" Standard List price 11/-	SALE PRICE 7/6
Type 88/6	600ft 5" Standard List price 21/10	SALE PRICE 13/6
Type 881/9	900ft 5½" Standard List price 28/10	SALE PRICE 15/-
Type 88/12	1,200ft 7" Standard List price 36/2	SALE PRICE 19/6

Post 1/- per reel. Orders of 6 reels and over POST FREE.

Philips Moving Coil Mic. Inserts

Type EL.6081/04. Self contained complete with diaphragm. 50 ohms imp. Size: ¾in. dia. x 1½in. long. Brand new in protective case.

SALE PRICE 19/6 P. & P. 1/-

Siemens Moving Coil Mic.

Brand new hand or desk mic. with remote control switch. 500 ohms. imp. Size: 3 x 2 x 1in. complete with 7ft. screened cable and 5 pin DIN plug.

SALE PRICE 55/- P. & P. 2/-

Tape Rec. Position Indicators

3 digit type with reset. Surface mounts on deck with two screws or with special clip provided. Couples to tape spool by flexible cable (included).

SALE PRICE 29/6 P. & P. 2/6

3 digit type with reset as used on many famous tape decks. Flush mounting type. Size: 1½in. wide x 1 x 1½in. Driven from take-up spool.

SALE PRICE 4/6 P. & P. 1/-

WHARFEDALE BARGAINS

Reflex Baffle Extension Speaker

6in. L/speaker unit in polished walnut veneered wood cabinet, size 10 x 8 x 4in. Volume control fitted. 1½-5 ohms imp. Complete in maker's carton with 5ft. flex.

List price 76/11 **SALE PRICE 45/-** P. & P. 3/6

Wharfedale Super 3

3in. H.F. unit—accepted as one of the finest tweeters ever made. Cloth surround. Max power cap. 6W RMS. Freq. range 1Kc to 20Kc/s. 6-8 ohms imp.

List price £6.8.3 **SALE PRICE 69/6** P. & P. 5/-

Wharfedale Super 5

5in. Mid/high range unit. 1in. aluminium voice coil. Max. power capacity 6W RMS. Frequency range 400c/s to 17Kc/s. 10-15 ohms impedance.

List price £6.14.5 **SALE PRICE £4.9.6** P. & P. 5/-

Wharfedale "Truqual"

Constant impedance volume control. Provides attenuation from 0 to -24dB in 5 steps plus OFF. For 1½ to 5 ohm speaker systems. Flush mounting.

List price 20/- **SALE PRICE 7/6** P. & P. 2/6

100's and 100's of Other Bargains

There's something for everyone in our vast stocks of new, shop soiled and first-class reconditioned equipment—

COME AND LOOK TODAY (Open 6 days a week!)

PERSONAL CALLERS TO:

48 TOTTENHAM CT. RD., W.1

Tel. 01-636 0647


MAIL ORDERS TO:

378 HARROW ROAD, PADDINGTON, LONDON, W.9

PLEASE NOTE: Owing to increased handling charges —
MINIMUM Mail Order value £1 (including postage).

LIND-AIR OPTONICS LTD

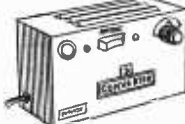See our vast range of
Electronic Components
at our new
Component Centre
25 Tottenham Court Road



Battery
Eliminator. En-ables
transistor
equipment
to be oper-ated
from AC
mains. 6/9/
12v. output
selector switch and on/off switch. Case size
4 x 2 1/2 x 2 1/2 in. complete with mains lead, con-
necting leads and instructions. 59/6. P. &
P. 3/6.

GARRARD DECKS



8RP22 less cartridge.....	25. 9.6
1025 Stereo/Mono with cart.....	27.19.6
2025 Stereo/Mono with cart.....	28. 9.6
3000S Stereo/Mono with cart.....	29.19.6
3000D Stereo/Mono with cart.....	210.19.6
SP25 less cartridge.....	210.19.6
SP25 with Decca Deraam cart.....	217. 4.6
SL55 less cartridge.....	212. 9.6
SL55 with Decca Deraam cart.....	218.14.6
Covers for above.....	22.10.0
Bases for above.....	23. 0.0
AP75 less cartridge.....	218.19.0
SL75 less cartridge.....	228.19.6
SL95 less cartridge.....	238.19.6
Bases for above.....	24.19.6

SPECIAL OFFER
SP25 less cart., with base..... 213. 2.6
P. & P. Decks 12/6, Cover 4/6, Base 4/6.
P. & P. Deck/Cover/Base 17/-

EMI COMBINATION LOUDSPEAKERS

13 1/2 x 8 1/2 in. elliptical with
two 2 1/2 in. tweeters. 15 ohm
impedance. Power handling
10 watts. Brand new and
guaranteed. 99/6. P. & P. 7/6.
(Also available without
tweeters. 59/6. P. & P. 7/6.)

"HI-TEN" LOUDSPEAKER

British made full range 10 in.
unit handles up to 10 watts.
Ceramic magnet. Freq. re-
sponse: 40-10,000 cps. Imp:
15 ohm. Flux density: 10,000
lines. 49/6. P. & P. 4/6.



SOLDERING GUN

Comfortable grip with
trigger control. T-
shaped 3 1/2 in. bit to mini-
mise wear. Light beam is
automatically directed on
to end of bit when ON/OFF
trigger is in use. 230-250 volts. 85
watt element. 49/6. P. & P. 3/6.

"ADASTRA" SOLDERING IRON

30 watt. Employs its protective cover
as a handle. AC 230/250v. With 4ft.
lead. 12/6. P. & P. 2/6.

NEW-VHF AIRCRAFT BAND CONVERTOR

When placed within 1 in.
of a MW band radio full
coverage of VHF Air-
craft Band 108-136Mc/s
can be obtained. All
transistor. 9v battery
operation. Fully tunable
15 1/2 in. x 7 in. section tele-
scopic aerial. Size 4 x 2 1/2
x 1 1/2 in. 70/6. P. & P. 3/6.

13-5 watts per channel. Free standing unit
with black crackle case and satin alloy
front panel. Specification: Frequency
range 30c/s to 20Kc/s (+3dB). Harmonic
distortion 2% at 10 watt (1Kc). Cross talk
45dB at 1Kc/s. Signal to noise ratio 60dB.
Inputs: Aux. 100mV, Phono 3mV, Tuner
150mV, Tapehead 4mV. Tone controls:
Treble 10Kc/s at +10dB. Loudness
(medium frequency cut). Output im-
pedance 8 ohms. Mains operates. Size
4 1/2 x 6 1/2 x 12 1/2 in. Price £28.5.0. P. & P. 9/6.

STEREO AMPLIFIERS

ORAL STEREO AMPLIFIER MODEL
TS-135. SOLID STATE. 13 TRANSISTORS.



DULCI STEREO AMPLIFIER MODEL 207



8 watts per channel. Integrated high fidelity
transistor Stereo amplifier. An attractive
free standing unit with provision for
mounting in equipment cabinet. Finish
Dark Grey vinyl simulated leather grain.
Front panel satin alloy. Specification:
Sensitivity, Radio/Tape 100mV into
1Mohm. Phono 100mV into 1Mohm. 3
position selector on front panel. Frequency
response: 40c/s to 16Kc/s +2dB. Separate
bass and treble controls with boost and cut.
balance control. Mono/Stereo Function
switch (both channels work in parallel).
Normally £23.2.0. LIND-AIR PRICE
£19.19.0. Plus P. & P. 9/-.

8-DeC BREAD BOARD



Solderless breadboard panels, for fast re-
placement of components. Includes
Single DeCs. One 8-DeC with Control
Panel, Jig and Accessories for solderless
connections to controls, etc., with booklet
"Projects on 8-DeC" giving construction
details for a variety of circuits. 29/6.
P. & P. 2/6.
4-DeC KIT. Four 8-DeCs with two Control
Panels, Jigs and Accessories and the book-
let "Projects on 8-DeC" all contained in a
strong attractive plastic case. Ideal for the
professional user. £5.17.6. P. & P. 3/6.

SPECIAL PURCHASE!

DE-LUXE STEREO HEADPHONES



With soft rubber
earpieces. Impedance
8-16 ohms. Frequency
response 23-13,000cps.
With lead and stereo
plug. Only 59/6. P. & P. 3/6.

NEW STEREO/MONO HEADPHONES

8HD-7. Soft rubber
earpieces with slide
switch for mono/
stereo listening and
ind. vol. controls.
Impedance 8-16 ohm
Freq. response 25-
15,000cps. With lead
and stereo plug.
£6.6.0. P. & P. 3/6.



HI-TONE RECORDING TAPE

BRITISH MADE. TOP QUALITY			
J1001	3"	Long Play PVC	225ft. 5/6 P. & P. 1/2.
J1002	3"	Triple Play Poly	600ft. 10/6 P. & P. 1/2.
J1003	5"	Long Play PVC	900ft. 10/- P. & P. 1/8.
J1004	5"	Double Play Poly	1200ft. 15/- P. & P. 1/8.
J1005	5"	Long Play PVC	1200ft. 12/6 P. & P. 2/-.
J1006	5"	Double Play Poly	1800ft. 22/6 P. & P. 2/-.
J1007	7"	Standard Play PVC	1200ft. 12/6 P. & P. 2/6.
J1008	7"	Long Play PVC	1800ft. 17/6 P. & P. 2/6.
J1009	7"	Double Play Poly	2400ft. 25/- P. & P. 2/6.
J1010	7"	Triple Play Poly	3600ft. 50/- P. & P. 2/6.

NEW TRANSISTOR MODULES

- E.1311. PHONO PRE-AMPLIFIER.** Size 2 x 1 1/2 in. Built-in R.I.A.A. characteristics enabling low output magnetic pick-up cartridges to be amplified up to 1 volt. Input 100Kohm: Gain 28dB: Max. output 3v: Max. input 50mV: Distortion 0.15% (at 1v level). Power supply 9-12v. 29/6. P. & P. 2/-.
- E.1313. MICROPHONE PRE-AMPLIFIER.** Enables a low output microphone to be used with an amplifier or radio. Input imp. 100Kohms: Gain 28dB: Max. output 3v: Max. input 50mV: Distortion 0.15% (at 1v level). Freq. response 10Hz-50KHz. Power supply 9-12v. 29/6. P. & P. 2/-.
- E.1318. DUAL LAMP FLASHER.** A switch module for electronically alternating two miniature bulbs. 6V, 100-200mA. Ideal for models, toy boats and planes, display signals, etc. Flasher time 1 sec: Power supply 6v DC: Current 150mA: Lamp 6v 150mA. 25/- P. & P. 2/-.
- E.1315. ELECTRONIC ORGAN TONE OSCILLATOR.** Used in conjunction with an organ keyboard, variable resistances and a 9 volt power supply, this module acts as the oscillator unit for an electronic organ. Tone Frequency: 200-1,000Hz: Output 80mW: Current 15mA. 25/- P. & P. 2/-.
- E.1314. POWER AMPLIFIER.** When used in conjunction with E.1311, E.1312 and E.1313 units this amplifier module produces about 300mW output for speaker connection (8-16 ohms), without necessity for an output transformer. Input imp. 1,000 ohms: Gain 20dB: Output 300mW: Distortion 3% (at 300mW output level). Freq. res. 50Hz-10KHz. Power supply 9v. Current 20mA at no signal, 80mA at max. output. 29/6. P. & P. 2/-.
- E.1317. MINIATURE MORSE TRANSMITTER.** Will transmit to any adjacent AM Receiver, also makes a useful oscillator for trouble shooting. Audio tone 400c/s. Radio frequency range 400c/s to 30Mc/s. Power supply 9v DC. Current 35mA. 25/- P. & P. 2/-.
- E.1312. TAPE PRE-AMPLIFIER.** Incorporating N.A.R.T.B. curve characteristics, this amplifies tape head signals up to 1 volt within the frequency range of 30Hz-15KHz. Input imp. 100Kohm: Gain 25dB: Max. output 2v: Max. input 50mV: Distortion 0.15% (at 1v level). Power supply 9-12 volts. 29/6. P. & P. 2/-.
- E.1316. MORSE CODE OSCILLATOR.** A transistorised Morse code oscillator (buzzer) to be used in conjunction with an operating key. Suitable for direct connection to a loudspeaker. Tone freq. 400Hz: Power output 80mW: Power supply 3-9v: Current 45mA. 25/- P. & P. 2/-.

Visit our Brand New
Hi-Fi Demonstration Room.
Tape Bar, Scientific Show of
Microscopes, Binoculars,
Telescopes also Watches at
18 Tottenham Court Road

COMPACT 2-WAY INTERCOMS



For table or wall mounting. Smart tone
grey cases size 3 1/4 x 1 1/2 x 2 1/2 in. Complete
with lead, staples and 9v battery. 65/-
P. & P. 3/6.

LIGHT DIMMER AND SWITCH

600 watts. 250 v
Fully suppressed
complete with
control knob and
fully assembled,
less casing. Will fit
most electrical
fittings. Uses 4
silicon rectifiers,
2 transistors and
1 thyristor. Many
other uses. £3.15.0
P. & P. 2/-.

MODEL MAKER'S MOTOR
No. 15RN. Voltage 11-5v.
Current 400mA. Torque
12g-cm. Body size
1 1/2" long x 1 1/2" dia.
Shaft 3/16" long x
1/16" dia. Ideal for
small models and
toys. 5/6 each.
P. & P. 1/3. 3 for 15/- P. & P. 6/6.

NEW TRANSISTOR CHECKER
For measuring alpha,
beta and Ico factors of
transistors also for check-
ing germanium and sil-
icon diodes. Internal 9v.
battery. Wide reading
scale. Moulded case size
7 x 4 1/2 x 3 1/2 in. Ranges:
Alpha 0.7-0.9967: Beta
0.300: Ico 0.50-5,000A.
Diode test: forward and
reverse internal resistance. Resistance:
200 ohm-1 megohm. Complete with con-
nectors and instruction booklet. £7.19.6.
P. & P. 3/6.

SHIRA 62D MULTI-TESTER 20,000 o.p.v.
DC voltage: 5-25-50-250-
500-2.5K (20,000 ohms per
volt). AC Voltage: 10-50-
100-500-1000 volts (10,000
ohms per volt). DC Cur-
rent: 0.50uA, 0.2-5mA, 0-
250mA. Resistance: 0-6K,
0-6M (300 ohm and 30K
at centre scale). Capacitance: 10pf. to .001
mfd., .001uF to .1uF. Decibels: -20 to
+22dB. Size 4 1/2 x 3 1/2 x 1 1/2 in. Complete with
case 77/- P. & P. 3/6.

TTC C1001 MULTITESTER in leather case.
20,000 o.p.v. AC volts
10, 50, 250, 1,000.
DC volts 5-25, 125,
500, 2500v. DC Current
0.50uA, 0.250mA
Resistance 0-60K, 0-6
Megohm. Decibels -20
to +22dB. Size of
meter 4 1/2 x 3 1/2 in.
85/- P. & P. 3/6.



CIRCUIT 10 watt Amplifier. Size only 1 x
0.4 x 0.2 in. A true hi-fi amplifier complete
with manual giving details of a wide range
of applications and instructions. (Guan-
teed 5 years. ONLY 59/6. P. & P. 1/6.

LIND-AIR OPTONICS LTD
18, 25 & 53 TOTTENHAM COURT, LONDON W.1.
Telephone: 01-580 2255/4532/7679
Shops open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

ALL
MAIL ORDERS
To Dept. PW569,
54a Tottenham
Court Road,
London, W1.

THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size, only 25 x 14 x 10in. Complete Kit
- ★ Response 30-20,000 c.p.s. Impedance 15 ohms. **19 Gns.**
- ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in high flux middle range speaker. (4) High efficiency tweeter. (5) Measured weight of woollen acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions.

DEMONSTRATIONS AT ALL BRANCHES.



R.S.C. STEREO/20 HI-FI AMPLIFIER PROVIDING 10/14 WATT

ULTRA LINEAR PEAK PUSH-PULL OUTPUT ON EACH CHANNEL. SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE. (7) valves ECC83, (2) ECL86, (4) E221. Frequency Response: ±2dB 30-20,000 c.p.s. Hum Level: 65dB down. Sensitivity: 30 millivolts max. Harmonic Distortion: 0.2%. ★ Four-position tone compensation and Input Selector Switch. ★ Stereo/Mono switch. ★ Neon panel indicator. ★ Handsome Perspex Frontplate. ★ Separate Bass and Treble controls. Output transformers are high quality sectionally wound. Outputs for 3 and 15 ohm speakers. Complete set of parts, point-to-point wiring diagrams and instructions. Or factory assembled with our usual 12 mths' antee 18gns. Or Dep. £4.10 and 9 monthly payments £22 (Total £22.10.0). Send S.A.E. for leaflet.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI

AMPLIFIER Highly sensitive. Push-Pull high output, with Pre-amp/Tone Control Stages. Performance figures of factory built units: Hum level -70dB. Frequency response ±3dB 30-20,000 c.p.s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 mV so that almost any kind of Microphone or Pick-up is suitable. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250V. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. Carr. 12/6. **14 Gns.** Twin-handled perforated cover £7/6. Supplied factory built with EL34 output valves. 12 months' guarantee for 17 gns. TERMS: Deposit £5.14.0 and 9 monthly payments of £1/3 (Total £19.15.3). Send S.A.E. for leaflet.

R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with associated controls allowing mixing of "mike" and gram. etc. and high sensitivity. 5 valves—ECC83 (2), EL84 (2), E221. High quality sectionally wound output transformer. IND. BASS AND TREBLE CONTROLS. Frequency response ±3dB 30-20,000 c.p.s. Hum level -60dB. SENSITIVITY 40 millivolts. Suitable for Crystal or Ceramic PUS. all types "mikes". For Musical Instruments such as String Bass, Electronic Guitars etc. Size approx. 12 x 9 x 7in. For A.C. mains 200-250V. 50 c/s Output for 3 and 15 ohm spkrs. SAE for leaflet. Complete kit. **9 Gns.** Full instructions and point-to-point wiring diagrams. Carr. 11/6 (or factory built 12 Gns.). Twin handled metal cover £7/6. TERMS ON ASSEMBLED UNITS. Deposit £7/6 and 9 monthly payments of £2/-. (Total £14.5.6).

RSC A11 TRANSISTORISED VERSION of above complete kit 9 Gns (Assembled 13 Gns)

R.S.C. BASS-REGENT

50 WATT AMPLIFIER

An exceptionally powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape.

★ Two extra heavy duty 12in. Loudspeakers. ★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls.

52 Gns. Carr. 30/- or dep. £10.1.9 and 9 monthly payments of £5.11.9. (Total 57.1 gns.). Send S.A.E. for leaflet. Also B20 Bass Inc. 15in. 25w Spkr. 29g gns. £15 inc. 12in. 20w Spkr. 19g gns.

R.S.C. BATTERY/MAINS

CONVERSION UNITS

Type BM1 An all-dry battery eliminator. Size 5x4x4 2in. approx.

Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250V. 50c/s is available. Complete kit with diagram 49/11 or assembled 59/11

SELENIUM F.W. RECTIFIERS (Bridged)

All 6/12V. D.C. output. Max. A.C. input 18v. 1a. 3/11. 2a. 8/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.

BLACKPOOL AGENT APPOINTED O. & C. ELECTRONICS 227 CHURCH ST.

R.S.C.
HI-FI CENTRES LTD.

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair, ideal for vocalists and Public Address. 15 ohm matching. C57 15 watts inc. five 7 x 4in. speakers £7.19.11. Type C48S, 30 watts. Fitted four 3in. high flux 8 watt speakers. Overall size approx. 42 x 10 x 5in. Or deposit £5/- and 9 mthly pmts 34/9 (Total £18.17.9) Carr. 10/- **16 Gns.** Type C412S, 50 watts. Fitted four 12in. 11,000 line 15 watt speakers. Overall size 56 x 14 x 9in. approx. Carr. 15/- **24 Gns.** Or Deposit £4.13.6 and 9 monthly payments of 52/6 (Total £28.5.0).

30 WATT HI-FI AMPLIFIER

for Guitar, Vocal or Instrumental Group A 2 or 4 input, 2 vol. control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold perspex facia. Neon indicator. For 200-250V. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 3 Gns. and **18 Gns.** Carr. 9 mthly payments of 39/8 (Total £21).



12in. HIGH QUALITY LOUDSPEAKERS

In Teak or Afrormosia veneered Cabinet. 15 Watt 1,000 lines 20 Watt 10,000 lines 30r13ohms Carr.7/6 **£5.15.0** 30r13ohms Carr.9/9 **£8.19.9**

LOUDSPEAKERS

Limited number of heavy duty units at well below list prices. Brand new, guaranteed. Terms available over £8. Carr. 10/- extra.

12in. 30 watt 6-8 ohms Normally approx. £12	15 ohms Impedance Normally £10.10.0	15in. 40 watt 15 ohms Extra heavy 10 Gns. duty
£6.19.9	£6.19.9	

FANE 'POP' 100 LOUDSPEAKER

18" 100 Watt
Fantastic power handling. Guaranteed 2 years. POST FREE **19 Gns**

ARMSTRONG UNITS CLEARANCE

Stereo Amplifier 222 **Our Price £25**
AM/FM Tuner-Amp 227M **Our Price £25**

POWER PACK KIT Consisting of Mains transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250V. A.C. mains. Output 250V. **24/11**
60mA 6.3v. 2a. Supplied with case in lieu of chassis 28/11. Or assembled 39/11.

CLEARANCE LINES

HIGH QUALITY 8" x 3" LOUDSPEAKERS 10000 Gauss 11/9
3 ohm only Post 2/-

14 WATT HI-FI AMPLIFIERS

High sensitivity. Two separate Jack inputs. Two vol. controls for mixing purposes. Separate Bass and Treble Controls. Valves ECC83, ECL86, ECL86, E220. Output for 15 ohm Loudspeaker. 200-250V 50 c.p.s. A.C. mains operation. Size approx. 8 x 8 x 6in. Factory built and fully guaranteed. Limited number to clear at **£7-19-11** Carr. 10/-

EXTENSION 'SPEAKERS 29/9

Cabinet size 12 x 8 x 5in. attractive grey lizard skin finish. Fitted high flux 5 watt 3 ohm speaker.

EMI PLAYER TURNTABLES

with P.U. 4 speed. Turnover cart-ridge. Limited number. **59/9** Mono **69/9** Stereo

PHONE AMPLIFIERS

Speak and listen with both hands free. Standard dry battery operated. Attractive black moulded case. **59/9**

1 WATT TRANSISTOR AMPLIFIERS

loudspeakers. Miniature size. Brand new boxed. for 3-5 ohm Post 2/- **37/9**

PRINTED CIRCUIT KITS

for making printed circuits. Complete with 72 square ins. laminated board and necessary fluids. Post 2/9 **12/9**

J.B. VHF/FM DIAL & DRIVE ASSEMBLIES

Complete with escutcheon. Size 7" x 4". Escutcheon 7" x 2" Post 2/9 **ONLY 9/9**

TAPE RECORD/PLAYBACK AMPLIFIERS

4 watts output. Magic Eye Recording level indicator. For 3 ohm L/S. All normal facilities. Less Facia plate. For 200/250 A.C. mains. Carr. 8/6. **£8.15.0**

HEAVY DUTY 15in. 40 WATT LOUDSPEAKERS

in substantial Rexine/Vynair covered cabinet. Carr. 15/- **14 Gns.**

MINI-8 HI-FI LOUDSPEAKER UNITS

Teak veneered cabinet, size approx 10 1/2 x 6 1/2 x 7 1/2in. Peak power handling 8 watts or 15 ohms. **59/11**

JASON VHF/FM TUNER DESIGNS

All parts FMT1 5 Gns. FMT2 £6.19.11. JTV2 9 1/2 Gns. Please state channel

STEREO/TEN HIGH QUALITY AMPLIFIER

5 watts high quality output on each channel. Sensitivity 50 millivolts. Suitable all crystal or ceramic stereo cartridges. Ganged Bass and Treble Controls. Valves ECC83 (2), EL84 (2), E221. Output rating is peak. For 2-3 ohm speakers. Assembled with 12 months' guarantee Carr. 11/6 **£11.19.6**

R.S.C. 6/12V CAR BATTERY CHARGERS

Complete kit of parts incl. Ammeter and Circuit.

4 amp with variable charge rate selector	49/9
6 amp heavy duty with variable charge rate selector	69/9

All types 200-250V. A.C. mains. Ready built 10/- extra.

SENSATIONAL R.S.C. HIGH FIDELITY STEREO PACKAGE OFFERS

"PACKAGE 3" 30 WATT SYSTEM
 ★ Goldring Transcription Turntable on Plinth
 ★ Shure Magnetic Pick-up Cartridge
 ★ Super 30 Amplifier in cabinet
 ★ Pair of Stanton Loudspeaker Units
 Special inclusive price, Fully wired, plus small units ready to "plug-in". Carr. 25/- P.T. surcharge
TERMS AVAILABLE ALL PACKAGE OFFERS

85 Gns.

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround giving low fundamental resonance. "D" indicates Tweeter Cone providing extended frequency range 40-15,000 c.p.s. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost. Prices include carriage.

HF100D 10" 5W	57/9	HF120 12" 15W	69/9
HF801D 8" 8W	57/9	HF120D 12" 15W	79/9
HF810D 8" 10W	4/4	HF125 12" 15W	89/9
HF102D 10" 8W	58/9	HF125D 12" 15W	5 Gns.

HIGH FIDELITY LOUDSPEAKER UNITS
 Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled woolen damping. Ported where appropriate. Credit terms available.

DORCHESTER Size 16 x 11 x 9in. Appr. Range 45-15,000 c.p.s. Rating 9-10 watts. Fitted High flux 13 x 8in. Dual Cone spkr. Imp. 3 or 15 ohms

STANTON III Size 18x11x10in. Rating 10 watts. Incorporating Fane 803b speaker with roll rubber cone surround and 15,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 30-20,000 c.p.s. Imp. 16 Gns. realistic sound output.

GLOUCESTER Size 25 x 16 x 10in. High flux 12,000 line speaker. Cross-over unit and Tweeter. Rating 10 watts. Frequency range 40-20,000 c.p.s. Impedance 15 ohms.

E2 EQUIPMENT CABINET
 Size 17" wide 14" deep 11" high. Cut for TA12, Super 15, Supers and other amplifiers. Hinged perspex cover. Satin Teak or Afrormosia veneer finish. Price inc. carr.

MOTOR BOARDS cut for Garrard Turntables and many other units. Price **12/9**

R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER

200-250v. A.C. mains operated Frequency Response 30-20,000 c.p.s. ±2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble controls. 3 input sockets for Mike, Gram, Radio/Tape. Input selector switch. Output 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 21 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams. Complete kit of parts with full wiring diagrams. Carr. 12/6. Or factory built with 12 months guarantee. 8 Gns.

R.S.C. SUPER 15 HI-FI AMPLIFIER

FULLY TRANSISTORISED 200/250v. A.C. Mains. OUTPUT 10 WATTS R.M.S. cont. into 15 ohms. 15 WATTS R.M.S. cont. into 3-4 ohms. TRANSDUCERS, 9 different types of high quality by leading manufacturers. 5 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads. FULL TAPE MONITORING FACILITIES. SENSITIVITY: Magnetic 4 mV. Crystal or Ceramic P.U. 400 mV. Microphone 4.5 mV. Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV. FREQUENCY RESPONSE: ±2dB 20-20,000 c.p.s. TREBLE CONTROL: +15dB to -14dB at 10Kc/s. NEGFEEDBACK: 52dB. BASS CONTROL: +17dB to -15dB at 50 c/s. HUM LEVEL: -75dB. HARMONIC DISTORTION at 10 Watts 1,000 c.p.s. 0.2% Complete Kit of parts with full constructional details and point to point wiring diagrams. Carr. 12/6. Supplied factory built 154 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9). Or in Teak or Afrormosia veneer housing as illustrated. 19 Gns. ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING MANUFACTURERS.

Matched for optimum performance. Send for coloured brochure showing other money saving offers.



Illustrated with TFMI Mk II Turner fitted
EXTREMELY ATTRACTIVE AND VERSATILE PLINTHS
 finished in Teak or Afrormosia veneer. Tinted Perspex "hinged" cover with satin chrome handle.

RECORD PLAYING UNITS
 Money saving units. Ready to plug into Amplifier or RP2 Tape Recorder. Consisting of Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Mounted on Plinth. Inc. Perspex cover. Carr. 22 Gns. 15/- Plus 8/7 P.T.

RP3 Goldring Lenco GL68 Transcription unit and CS90 Cartridge. Supplied with Perspex Cover. Carr. 21/- Inc. P.T. s'charge

R.S.C. PLINTHS for Record Playing units. Teak finish cut for Garrard 3000, AT6, AT80, SP25 or Goldring GL68. Available with clear Perspex cover or as illustrated. Inc. Carr. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/9



3000, AT6, AT80, SP25 or Goldring GL68. Available with clear Perspex cover or as illustrated. Inc. Carr. 6 Gns. Perspex cover sold separately at 3 Gns. Limited number of covers slightly damaged but repaired by makers. 39/9

INTEREST CHARGES REFUNDED on Credit Sales settled in 3 months.

R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

Total cost of parts with detailed wiring diagrams & instructions. **14 Gns.** Carr. 12/6. Or factory built 164 Gns. Or in Teak finished cabinet as illustrated 184 Gns. Terms: Deposit 25 and 9 monthly payments £22. Total £23.

R.S.C. SUPER 30 STEREO AMPLIFIER

A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits High quality German For Matched Components. CROSS TALK: -52dB at 1,000 c.p.s. CONTROL: 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch. INPUT SOCKETS (Matched Pairs). (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone. Operation of the Input Selector Switch assures appropriate equalisation. Rigid 18 s.w.g. Chassis. Size approx. 12in. wide, 3in. high and 8in. deep. Neon Panel Indicator. Attractive Facia Plate and Spun Silver Matching Knobs. Above facilities. etc., except for Gangs and Balance Control, apply also to Super 15. THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon). CURRENTLY AVAILABLE SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions. Carr. 15/- Unit factory built 28 Gns. or deposit £7.5.0 and 9 monthly payments 56/3. (Total £32.13.3). Or in veneered housing 31 Gns. Carr. 15/- or deposit £7.3.6 and 9 monthly payments 64/- (Total £35.19.6). Send S.A.E. for leaflet.

"PACKAGE 2" 30 WATT SYSTEM
 ★ Garrard SP25 Mk II Turntable on Plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ Super 30 Amp. in cabinet. **75 Gns.** Carr. 25/-
 ★ Pair Stanton Speaker Units
 Special inclusive price. Fully wired units ready to "plug-in". P.T. surcharge

"PACKAGE 1" 15 WATT SYSTEM
 ★ Garrard SP25 Mk II 4 sp player unit on Plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge
 ★ TA12 Amplifier in cabinet
 ★ Pair of Dorchester Loudspeaker Units
 Special inclusive price. **49 1/2 Gns.** Plus small P.T. s'charge

Or Dep. £10 and monthly payments £5.4.0. (Total £56.18.0.) Perspex cover 3 Gns. extra.

10 W HIGH FIDELITY AMPLIFIERS
 LINEAR L10 Separate Pre-amp and Main Amp. Matched to Magnetic P.U. To clear **10 Gns.**

R-S-C TA12 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL. Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV Output rating I.H.F.M. ★ Handsome brushed silver finish facia plate and knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 mth gntee **16 Gns** or Deposit **£4.16.0** and 9 mthly pymts **31/6** (Total **£18.19.6**) Or in Teak or Afrormosia veneer housing **19 Gns**. Dep. **£4.19.0** and 9 mthly pymts **39/-**. (Total **£22.10.0**)

AUDIOTRINE HI-FI SPEAKER SYSTEMS
 Consisting of matched 12in. 12,000 line 10 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **5 Gns.** Or Super 15 watt inc. HF 125 15,000 line Speaker 6 Gns. Carr. 6/6 Carr. 5/9

HI-FI SPEAKER ENCLOSURES Teak or Afrormosia veneer finish. Modern design. Acoustically lined and ported. Inc. carr. JES Size 16 x 11 x 9in. Pressurised. Gives **4 Gns.** SE8 For optimum performance with any 8in. **5 Gns.** HI-FI speaker. Size 22 x 15 x 9in. SE10 For outstanding results SE12 For exclnt prfmanc with 12in HI-FI with 10in HI-FI spkr **£5.10.0** Size 24 x 15x10in. **6 Gns.** Size 25 x 16 x 10 1/2 in.

R.S.C. SUPER 15 HI-FI AMPLIFIER

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349
BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street
BIRMINGHAM 30/31 Gt. Western Arcade opp. Snow Hill Station 021-236-1279 (Half-day Wed.)
DERBY 26 Osmaston Rd. The Spot (Half-day Wed.) Tel. 41361
DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
EDINBURGH 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
GLASGOW 326 Argyle St. (Half-day Tues.) Tel. City 4158
 403 Sauchiehall St. (Opp. Locarno) (Half-day Tues.) Tel. 332-1572
HULL 91 Paragon Street. (Half-day Thursday) Tel. 20505

R-S-C
 HI-FI CENTRES LTD.

MAIL ORDERS TO: 102 Henconner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries please. Open all day Sat.


32 High Street. (Half-day Thurs.) Tel. 56420 **LEICESTER**
 5-7 County (Mecca) Arcade, Briggate (Half-day Wed) Tel 28252 **LEEDS**
 73 Dale St. (Half-day Wed.) Tel. CENtral 3573 **LIVERPOOL**
 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**
 60A Oldham Street (Half-day Wed.) Tel. CENtral 2778 **MANCHESTER**
 106 Newport Rd (Half-day Wed) Tel. 47096 **MIDDLESBROUGH**
 41 Blackett Street (Opp. Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

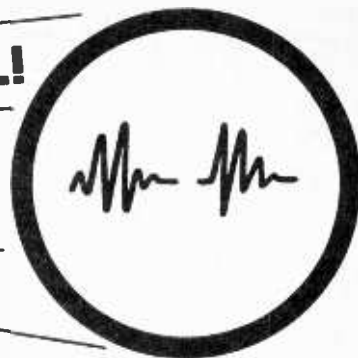


a new 4-way method of mastering
ELECTRONICS
by doing — and — seeing . . .

1

**OWN and
HANDLE a**

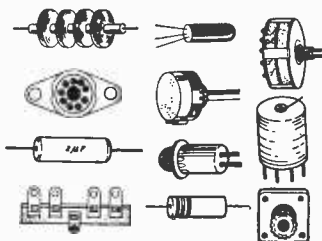
complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



2

**BUILD
and USE**

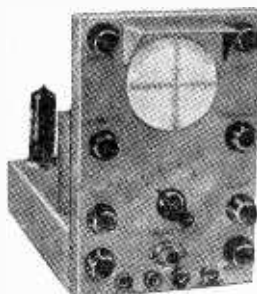
a modern and professional **CATHODE RAY OSCILLOSCOPE**



3

**READ and
DRAW and**

**UNDERSTAND
CIRCUIT DIAGRAMS**

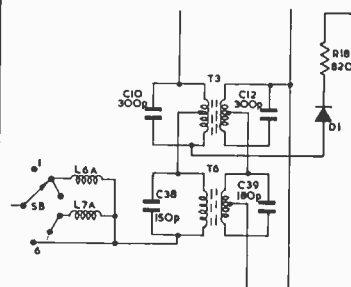

4

CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- | | | |
|--------------------------|--------------------------|------------------------|
| ● VALVE EXPERIMENTS | ● PHOTO ELECTRIC CIRCUIT | ● A.C. EXPERIMENTS |
| ● TRANSISTOR EXPERIMENTS | ● COMPUTER CIRCUIT | ● D.C. EXPERIMENTS |
| ● AMPLIFIERS | ● BASIC RADIO RECEIVER | ● SIMPLE COUNTER |
| ● OSCILLATORS | ● ELECTRONIC SWITCH | ● TIME DELAY CIRCUIT |
| ● SIGNAL TRACER | ● SIMPLE TRANSMITTER | ● SERVICING PROCEDURES |

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE

**POST NOW
for
BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW 5

PRACTICAL WIRELESS

VOL 45 No 1

Issue 747

MAY 1969

TOPIC OF THE MONTH

Seven Ages (so far)

ACCORDING to what we hear, there are seven ages of man. If this is true, it doesn't apply to readers of P.W. who—to our knowledge—range from seven to seventy, or thereabouts. But if it is impossible to split readers into seven ages, an attempt could be made with the subject itself.

There are still a few readers who can remember Age 1, the dawn period when you had to *make* most, if not all, of the components before wiring could begin. The next generation of enthusiasts was luckily able to buy most of the bits and pieces and was no doubt considered rather effete by the old guard!

Later on, in Age 3, the purists were even more affronted because complete units, including communications receivers, could be obtained. The rot had set in. For Age 4 let us nominate the immediate post-war years when the flood of surplus equipment swamped the stores and found its way into thousands of radio dens.

The next generation (Age 5) grew up in the kit era. There had been kits before, but now they proliferated and if you could solder a joint you could become a member of the fraternity. The pace accelerates to Age 6 when printed circuits and transistors burst on the scene simplifying construction and bringing in real miniaturisation for the first time. The present generation (Age 7) sees modules and ICs beginning to make an impact.

At each of these stages in the evolution of the radio hobby, it was perfectly understandable for the preceding generation to shake its collective head and remark that "things are not like they used to be" and "Today everything's far too easy". Yet, the hobby continues to flourish!

One strong reason why this should be so is that radio fans are usually very adaptable and fired with curiosity. Thus, even today there is room for experiment and ingenuity, and this cannot be better exemplified than by a new series of articles we have commissioned under the generic heading of *TAKE 20*. Each part will describe a constructional project using 20 or less components and costing 20 or less shillings to build. Turn to page 49 for the first instalment.

W. N. STEVENS—*Editor*.

NEWS AND COMMENT

Leader	17
News and Comment	18
MW Column <i>by C Molloy</i>	25
On the Short Waves <i>by Christopher Danpure and David Gibson, G3JDG</i>	26
CQ CQ CQ CQ CQ CQ	32
Practically Wireless <i>by Henry</i>	43
Letters to the Editor	65

CONSTRUCTIONAL

Comprehensive Transistor Tester <i>by J. A. Jebb</i>	20
Combined Loudspeaker and S-meter <i>by F. G. Rayer</i>	24
P.W. Double-12, Part 2 <i>by Hal Moorshead</i>	35
Calibration Oscillator <i>by R. F. Graham</i>	46
Take 20 <i>by Julian Anderson</i>	49
Integrated Circuit Stereo Amplifier <i>by L. McNamara, B.Sc.</i>	61

OTHER FEATURES


Basic Semiconductor Technology, Part 1 <i>by M. F. Docker, M.Sc.</i>	28
Pulse Circuits in Operation, Part 1, <i>by I. J. Kampel</i>	40
P.W. Guide to Components, Part 5, Transistors, <i>by M. K. Titman, B.Sc.</i>	44
Aerials, Part 2 <i>by A. J. Whittaker</i>	50
Satellite Earth Station, Part 2 <i>by Richard Collins</i>	57

JUNE ISSUE WILL BE PUBLISHED
ON MAY 9th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", IPC Magazines Ltd., Tower House, Southampton Street, London, W.C.2. Phone: 01 836 4363. Subscription rates, including postage: 42s. per year to any part of the world. © IPC Magazines Ltd., 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

NEWS AND COMMENT...

"MOXEY" PISTOL-GRIP HAND DRILL

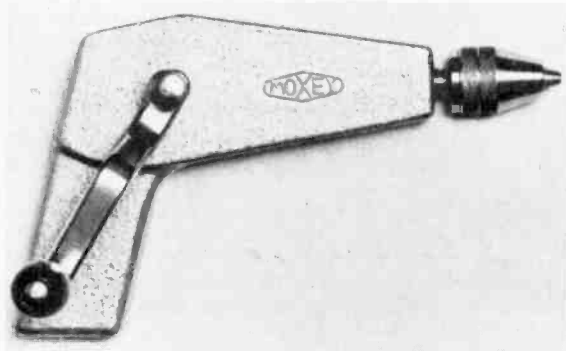

Main feature of the new pistol-grip hand drill made by the Moxey Manufacturing Co., is the enclosed gear mechanism. This eliminates the chance of pinching your fingers on the open cogwheel which is a disadvantage of so many hand drills on sale today. The gears of the Moxey drill are hidden in the aluminium casing and the $3\frac{3}{8}$ in. driving handle is made to come off for easy storage.

The drill is named after Bernard A. Moxey, aged 39, a Herts. toolmaker who set up on his own in 1953. Now, after having made millions of parts for other firms he has embarked upon manufacture of a finished product of his own design.


The drill measures $8\frac{1}{2}$ in. from the chuck tip to the handle extremity and weighs 18oz. The casing may be opened for lubricating the moving parts but the makers claim they are not likely to require lubrication for some years.

The Moxey drill is available at ironmongers stores and departmental stores and costs 32s. 6d.

THANET MOBILE RALLY

On 18th May the Thanet Radio Society Mobile Rally will be held at Ramsgate, Kent. An added attraction this year is the SRN-4 hovercraft at nearby Pegwell Bay. Further details, send s.a.e. to Dick Trull, G3RAD, Hon. Treasurer and P.R.O., 1 Approach Road, Broadstairs, Kent.

TANDBERG HI-FI SYSTEM 15

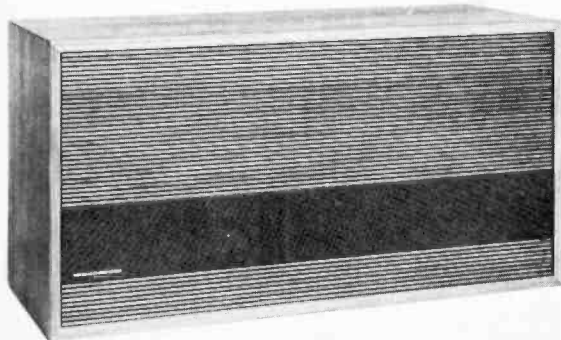

The Hi-Fi System 15 comprises a 12in. woofer, a 5in. midrange and a 2.5in. tweeter. The impedance is 4 Ω and the handling capacity is 30W. The speaker is available in teak and a rosewood version will be available shortly. Price (teak) is £40 19s.

MULLARD FILMSTRIP ON INTEGRATED CIRCUITS

New from the Mullard Educational Service is a 36-frame, 35mm. colour filmstrip called "Integrated Circuits". It acts as an introduction to the subject for students of semiconductor technology and for those with a wider interest in electronics. Although an elementary knowledge of semiconductors is desirable, it is not essential and the notes provided with the filmstrip can easily be edited to suit varying audience levels.

Also available as a set of slides mounted in 35mm. frames, the film is obtainable from The Slide Centre Ltd., Portman House, 17 Broderick Road, London, S.W.17. The cost is £2 for the filmstrip and £2 10s. for the slides. Good value as a club investment.

DRY JOINT LOCATOR



Techmation Ltd. announce their dry-joint locator. It is manufactured in the UK by Davian Instruments Ltd. and is basically a linear-scaled ohmmeter of variable sensitivity which is normally preset. By using a high current to measure low resistances, any dry joints show up as the current tends to accentuate the resistance of the joint. On any resistance greater than 4 times f.s.d. (including o/c) an active protection circuit reduces the current from its preset value to about 10–15mA total. In order to protect both meter and circuitry under test, the maximum applied voltage is limited to less than 1V.

A good soldered joint should have a resistance of less than 50m Ω and dry joints normally have a resistance greater than 0.5 Ω . Any joint of greater resistance than 0.1 Ω is a potential source of trouble and should be re-soldered.

Other possible applications of the unit are: investigation of earth loops and return paths, relay contacts, measurement of contact resistance, determination of wire lengths etc.

The price of the battery-powered version is £17 excluding batteries. The mains version is £19 10s. and post and packing are 7s. 6d. extra. Techmation Ltd., 58 Edgware Way, Edgware, Middlesex.

NEWS AND COMMENT...

OFF-THE-SHELF "MINIS"



A new off-the-shelf range of miniature power transformers has recently been introduced by The Belclere Co. Ltd. Outputs range from 3.0-3V to 20.0-20V and each transformer delivers up to 600mW. Standard construction is p/c pin mounting, varnish impregnated, but clamped versions with or without electrostatic screen are also available.

Prices start at less than 10s. each for quantity, and "specials" using the same frame size can also be designed and supplied.

Full details are available from The Belclere Company Ltd., 385/387 Cowley Road, Oxford. Tel.: Oxford 77266.

KNIGHT-KIT REDUCTIONS

The Electroniques new list of Knight-Kit prices shows a reduction—in many cases up to or exceeding 20%. Electroniques say that they have been able to do this because of their record 1968 sales figures.

RADIO AMATEUR LEADS AFRICA EXPEDITION



David Dunn, GW3XRM, aged 25 and a senior design draughtsman with Hydraulic Machinery (G.B.), is off on an 8-month trans-Africa safari. He and his team will study the reliability of low-powered short wave radio communications and carry out geological investigations of the Rift Valley area of East Africa.

David (pictured) will make daily QSOs en route with a radio operator based at Cardiff University. Both the university and Students' Union have provided grants for the provision of the radio gear which is installed on the ex-Army Commer cross-country truck the team purchased for £100 to take them on their 12,000 mile journey. He has also applied for licences to transmit from each country the team visits.


ANNUAL DINNER FOR SUTTON & CHEAM

The Sutton & Cheam Radio Society announce their 21st Annual Dinner and Ladies' Festival to be held at The Crown Inn, Morden, Surrey, (just by Morden station at end of Northern Line Underground) on Saturday, 12th April 1969. Reception at 6.30p.m.

The President of the RSGB, Mr. J. W. Swinnerton, G2YS, has kindly accepted their invitation to attend as guest of honour, and it is expected that a number of other well-known personalities in the field of Amateur Radio will be present.

A really first-class evening, including cabaret, is planned and a heavy demand for tickets is anticipated. Please contact Roy Scott, G2CZH, 140 Seymour Avenue, Morden, Surrey, as soon as possible for bookings, at 35s. per person, and further information.

"CHIP" CAPACITORS

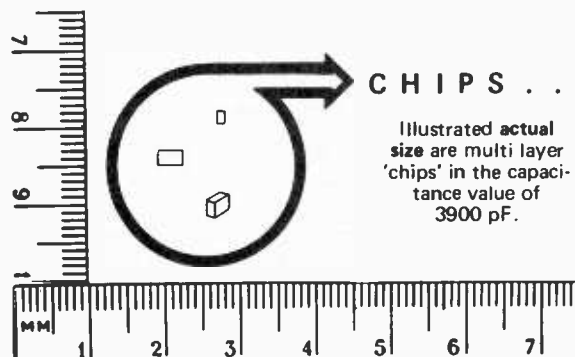

From The Radio Resistor Company Limited comes a new range of multi-layer capacitor "chips" for incorporation into integrated circuits. Available in a wide range of capacitance values to order these new capacitors can be supplied with or without tin-plated electrodes.

In addition, the range is also available as complete components with radial terminations and synthetic-coated finish in a capacitance range of from 470pF to 47,000pF.


Tolerance on capacitance on both types is $\pm 20\%$ and $\pm 10\%$; Working voltage is 63V d.c.; Loss factor is equal to or less than 25×10^{-3} .

These multi-layer capacitors are manufactured by Rosenthal Isolatoren G.m.b.H. for whom The Radio Resistor Company Limited, 9-11 Palmerston Road, Wealdstone, Harrow, Middlesex, are the sole UK representatives.

MULLARD DATA HANDBOOK 1969

The 1969 Mullard Data Handbook gives abridged data on the extensive range of Mullard valves, picture tubes, semiconductors and components used in the consumer electronics industry.

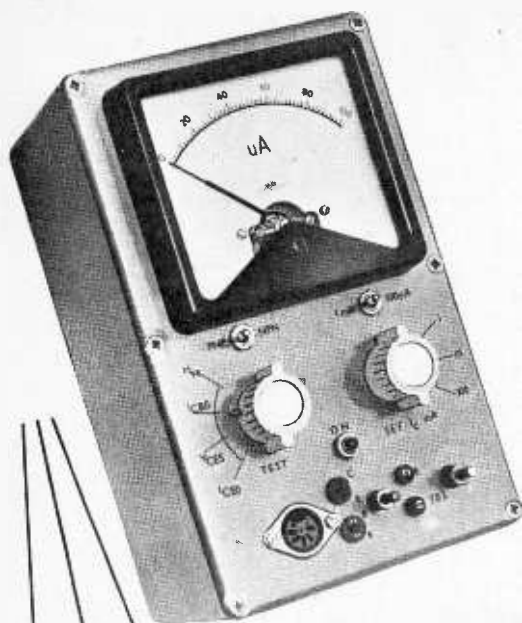Each product has been printed on different coloured pages to facilitate quick reference, and although some of the earlier devices are not listed due to lack of space the handbook will prove invaluable to the serviceman or the amateur constructor. The cost of the handbook is 3s. 6d.



the collector circuit shown in Fig. 3, in order to ascertain that the I_c is not too great. This is an indication of the construction of the device under test, i.e., whether it is silicon or germanium. (The I_{ceo} value is also a guide, but this can be confused if the device is faulty). This test also applies to diodes.

Establishing β . This parameter enables us to set up a reasonable I_c when the device is in use, and is consequently of great importance. The circuit in Fig. 4 will evaluate β , and can be set up on the bench. The variable resistors are used to set I_c and I_b to a reasonable level. β is given by ΔI_c by definition. If ΔI_b

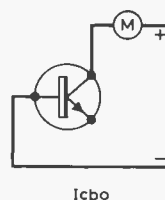


Fig. 2: Test for I_{cbo} .

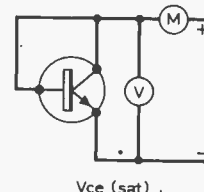


Fig. 3: Test for $V_{ce} (sat)$.

a comprehensive transistor tester

THE specification sheet of a particular transistor may, at first sight, seem a little forbidding, and perhaps give the impression that the evaluation of a transistor is a difficult task. The important parameters are, I_c for a certain I_b , the bottoming voltage, and the serviceability of the junctions. These quantities are related to β (also known as H_{fe}), $V_{ce} (sat)$ and I_{ceo} .

Basic Tests

The transistors considered will all be n-p-n types, for the sake of argument, that is, wired with collector to positive.

Test for I_{ceo} . This is essentially an insulation test of both the junctions, see Fig. 1. A good silicon transistor will have $I_{ceo} < 0.1 \mu A$. A good germanium transistor has I_{ceo} about $0.1 mA$, but this varies from device to device, and also depends on the temperature (I_{ceo} doubles for every $10^\circ C$. rise, and even on the intensity of light illumination at the time of testing.)

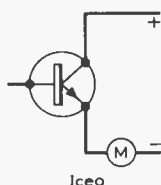


Fig. 1: Test for I_{ceo} .

Test for I_{cbo} . Again an insulation test, but this time over only one junction. I_{cbo} is always $< 20 \mu A$, even for germanium transistors, see Fig. 2.

Test for $V_{ce} (sat)$. This is a measure of the turn-on voltage of the transistor. It will be about $0.7V$ for silicon and $0.2V$ for germanium. A meter is included in

β is linear in I_c , then $\beta =$

$$\frac{I_c + I_{ceo}}{I_b} \quad \text{Since } I_{ceo} \text{ is usually } < 1/10 I_c, \text{ then}$$

$$\beta \approx \frac{I_c}{I_b}$$

The tests described so far give a fairly good indication of the nature of the device, its gain, and whether it is in working order. In order to perform these tests quickly, a small unit has been constructed, which simplifies testing, and embodies several desirable features. Many commercial, and the majority of home-designed testers employ a technique which, though very simple, has one main draw-back. This technique is described in the circuit shown in Fig. 5.

The base of the transistor under test is fed from a constant current source, usually a high-value resistor. Depending on β a current is set up in the collector, which is then measured. This is unfortunate, as the value of β at a specified I_c is normally required, not β at a certain I_b , as this test gives.

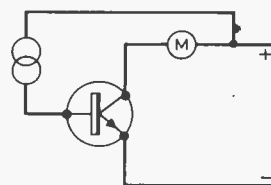


Fig. 4: Circuit for establishing β .

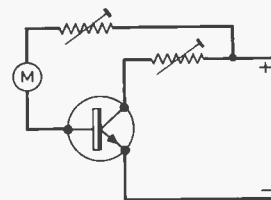


Fig. 5: A common method of transistor testing which has disadvantages described in the text.

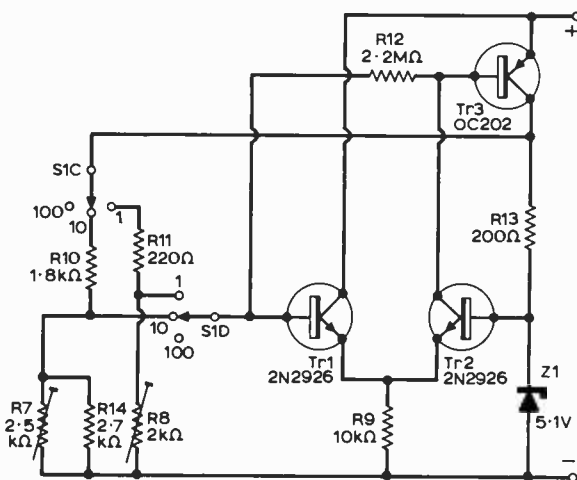


Fig. 6: The circuit for the 1mA and 10mA constant current source.

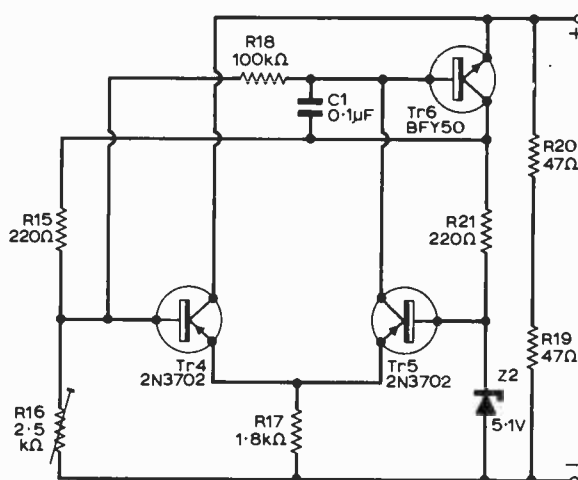


Fig. 7: The circuit for the 100mA constant current source.

The Circuit

The unit described in this article has a constant current source in the collector circuit, and a meter in the base circuit. The constant current source is switchable to 1mA, 10mA, and 100mA, and the meter is shunted from 100μA to 1mA by independent switch, and 10mA by switch ganged to the 100mA range.

There are two separate constant current sources used in the instrument, one providing 1mA and 10mA, the other 100mA: Fig. 6.

The differential amplifier formed by Tr1 and 2 drives a series transistor Tr3, which is of opposite polarity to Tr1 and 2. In the 1mA and 10mA circuits, the series transistor is an OC203, an obsolete p-n-p junction type. The differential pair are 2N 2926 green (the green refers to the gain grouping), with a gain of approximately 250. The OC203 was chosen because of its low leakage current and its gain, which is substantially constant over 1mA–10mA. A germanium OC81D was tried and worked, but the specimen used was a glass-encapsulated one, and its I_{ceo} was greatly affected by changes in temperature and ambient light conditions, resulting in poor stability. There is a fair amount of switching to be done to change 1mA to 10mA, but stability considerations made this essential.

The 100mA range was designed round a BFY 50, n-p-n transistor, with a maximum dissipation of 800mW. A heat flag was originally fitted but this proved unnecessary. P-N-P transistors are required in the differential pair, and 2N 3702's were used for reasons of availability and price. One disadvantage

Common transistor symbols and abbreviations

BV_{CBO}	Collector-base breakdown voltage	$I_{CBO}(\max)$	Maximum collector-base cut-off current with emitter open-circuit
CB	Common-base circuit	$I_{CM}(\max)$	Maximum peak collector current
C_{cb}	Collector-base capacitance	I_E	Emitter current
CC	Common-collector circuit	I_{EBO}	Emitter-base leakage current, collector open-circuit
CE	Common-emitter circuit	I_F	Forward current
c_{ob}	Maximum common-base output capacitance	I_R	Reverse current
c_{tc}	Collector depletion capacitance	$P_C(\max)$	Maximum collector dissipation
f_T	Transition frequency	$P_{tot}(\max)$	Maximum total dissipation
h_{fe}	Small signal common-emitter signal current gain with output short-circuited to a.c.	T_{amb}	Ambient temperature
h_{FE}	Large signal common-emitter signal current gain with output short-circuited to a.c.	T_c	Case temperature
h_{FEL}	Large signal current amplification factor	T_j	Junction temperature
I_B	Base current	$T_j(\max)$	Maximum junction temperature
I_C	Collector current	V_{BE}	Base-emitter voltage
$I_{C(AV)}\max$	Maximum mean collector current	V_{CB}	Collector-base voltage
I_{CBO}	Common-base collector-base current with emitter open-circuit (leakage current)	$V_{CBM}(\max)$	Maximum peak collector-base voltage
		$V_{CB}(\max)$	Maximum collector-base voltage
		V_{CE} , etc.	Collector-emitter voltage, etc., as for collector-base voltages
		$V_{CE(sat)}$	Collector-emitter voltage for saturated (fully conducting) operation
		V_F	Forward voltage
		V_R	Reverse voltage

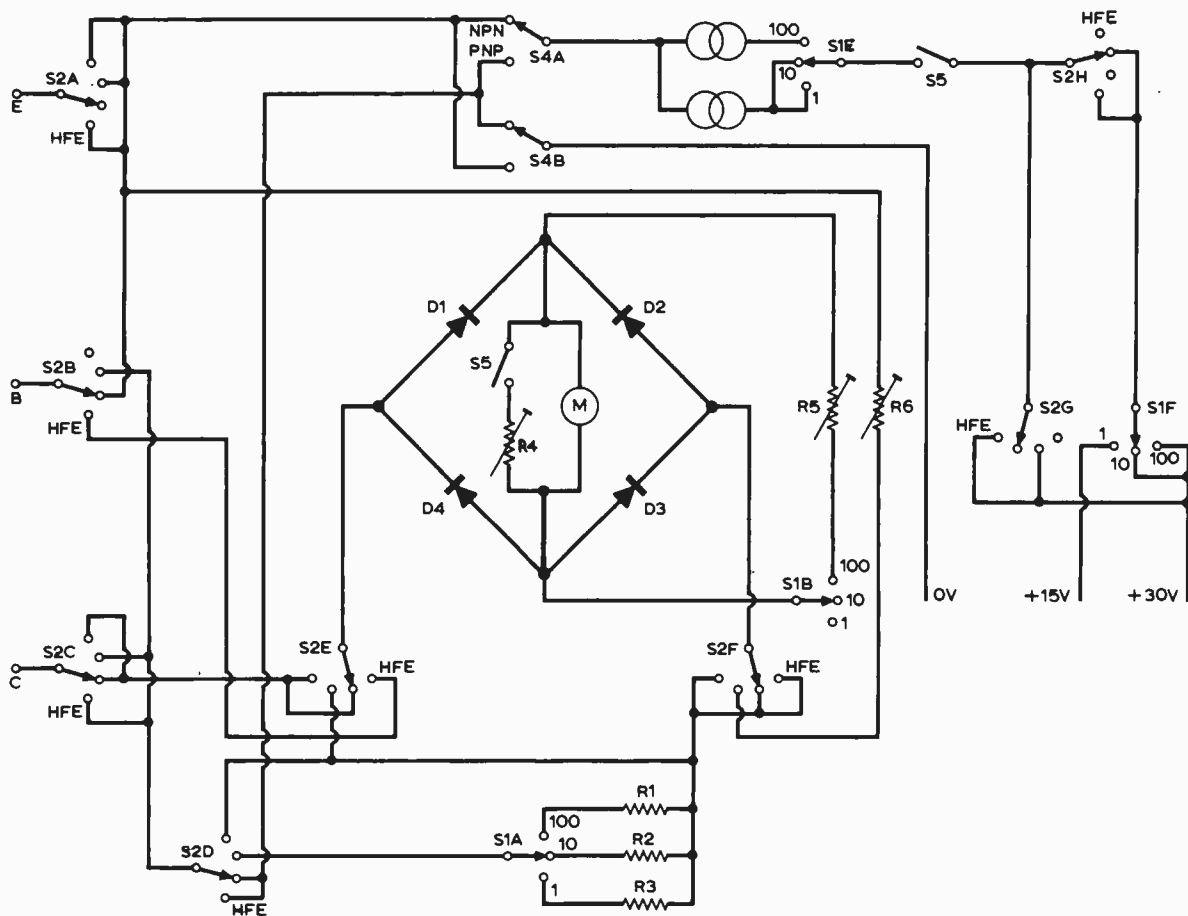


Fig. 8: The complete circuit of the transistor tester. The constant current sources are shown as two interlocking circles.

of these is that the gain varies from between approximately 10 at $100\mu\text{A}$ to 60 at 10mA , however, the stability of the circuit is quite adequate.

The switch used to change the constant current circuit (Sw1) is ganged to others which alter the meter shunts. Most transistors which will take 100mA I_c have a gain of between 10–100, so a meter shunted to 10mA gives a useful scale. This only applies to this range, and an independently switched 1mA shunt is employed on other ranges. Transistors with a gain of 10–1000 may be tested at 1mA or 10mA .

After some weeks of usage, it was noticed that the tester often showed a transistor to be excessively leaky, even when it worked satisfactorily in practical circuit. This was traced to the rather high value of battery voltage used. Since the leakage currents are quite small, the constant current supplies will not operate and the full 30V will be placed across the device under test. Accordingly, the circuit was modified so that, when Sw2 was set to I_{ce0} or I_{cb0} , the setting of Sw1 determines the battery voltage applied. Setting Sw1 to 1mA gives a voltage of 15V , setting to 10mA or 100mA gives 30V . For the $V_{ce}(\text{sat})$ and H_{fe} tests, voltage is always 30V .

The switch Sw1 selects the test required, also the type of metering required (current or voltage).

To obviate the need for extra poles on the polarity switch, a bridge rectifier was placed around the meter. This was most convenient, and introduced no non-

linearity on the current ranges, but on the $V_{ce}(\text{sat})$ range, it was found that no useful reading was obtained. This was attributed to the non-linear current/voltage characteristic of the diodes. The solution to the problem lies in the introduction of an off-set voltage of just enough strength to turn on the diodes. This is effected by the insertion of a resistor in series with the transistor under test, having such a value that the meter just begins to register a reading when the appropriate current from the constant current source is passed with collector and emitter terminals shorted.

When a transistor is inserted, $V_{ce}(\text{sat})$ is added to the off-set voltage and can be measured on the meter. Three resistors are required, one for each I_c range, and these are switched by the current switch Sw2. Owing to variations in diode characteristics, the value of resistor cannot be predicted accurately, but for the 1mA it is a good start to try $1\text{K}\Omega$ and then 4.7K , 3.9K , 3.3K and 2.7K in turn, in parallel with this, with collector and emitter shorted. The other current ranges decrease the resistor value by $1/10$ each time.

This test does not give a very accurate voltage check (within about 10%), but it is good enough to distinguish 0.2V from 0.7V , and hence decide on the structure of an unknown transistor.

The H_{fe} test connects collector and emitter to the constant current source, and base to the metering system. At 1 and 10mA , current ranges of $100\mu\text{A}$ and

1mA are satisfactory for Hfe up to 500 and down to about 2. However, at 100mA, the problem is different, owing to the relatively small range of Hfe encountered in transistors that will take this current without damage. Most fall within the range 10-100, i.e., a 1mA or 100μA meter system is not satisfactory.

It was decided that 10mA would be an appropriate sensitivity, and that a pole on the current range switch could be utilised to bring in the appropriate resistor.

This has the advantage that it is now more difficult to grossly overload the meter through using the high-current range. Overloading is possible, of course, on the 10mA range, if the meter is set at 100μA.

Next Month the article will be concluded with full constructional and comprehensive operating details.

★ components list

Resistors:

R1	see text	R12	2.2MΩ
R2	see text	R13	220Ω
R3	see text	R14	2.7kΩ
R4	150Ω preset pot.	R15	220Ω
R5	15Ω preset pot.	R16	2.5kΩ preset pot.
R6	10kΩ preset pot.	R17	1.8kΩ
R7	2.5kΩ preset pot.	R18	100kΩ
R8	2kΩ preset pot.	R19	47Ω
R9	10kΩ	R20	47Ω
R10	1.8kΩ	R21	220Ω
R11	220Ω		

Semiconductors:

Tr1 and 2	2N2926G	Z1 and 2	BZY88
Tr3	OC202	D1, 2, 3 and 4	OA47
Tr4 and 5	2N3702		
Tr6	BFY50		

Miscellaneous:

C1 0.1μF; Meter, 100μA movement, 1kΩ coil resistance; SW1 Six pole, three way switch; SW2 Seven pole, four way; Batteries to give 30 Volts, 100mA; Veroboard; Eddystone diecast box type 6827P; two miniature toggle switches; transistor sockets as discussed in text.

RECENT PROPOSALS FOR COMMERCIAL RADIO

Two days before last month's publication date Paul Bryan M.P., the Opposition spokesman on broadcasting made a speech which was very much in line with our last leader. As the consequences of this may alter broadcasting in this country greatly we are publishing the main proposals made in the speech without comment.

THE "pirate" radio stations showed that people want commercial radio in addition to the B.B.C. programmes. The Government are determined to stop us having it. A Socialist Government will always prefer the B.B.C. monopoly, over which it has some measure of control. The Post Office conveniently asserts that the technical problems of establishing many more radio stations are very great. No independent experts agree with them.

The next Conservative Government will set up 100 or more local commercial radio stations. These will come under the general supervision of the I.T.A., which is already highly skilled and experienced in the control of broadcasting programmes and of advertising. The Independent Television Authority would become the Independent Broadcasting Authority and would be responsible, in co-operation with Local Authorities, for the selection of programme contractors and for the transmission of programmes.

There would be a limit to the number of stations available to any one contractor. The levy money paid by the station contractors could profitably be put to use locally on all the social and cultural activities which are, at present, starved for funds, such as the repertory theatre, playing fields, swimming baths, etc. Local newspapers should be allowed to take a financial interest, but not a controlling financial interest, in local radio. This would not only compensate for the advertising revenue they may lose, but their news-gathering facili-

ties would be a great help to the radio station.

The Government's local radio experiment has been a completely irresponsible venture. These stations were certain to have some programme success, for they are well run and have no competition and who is to say if a programme is a success when only a quarter of the homes can hear it?


But typically, the Labour Government never faced the problem of who would pay for local radio. The last P.M.G. but two, Mr Short, told us that the money for the stations would be raised "locally but not through the rates", and that it would be wrong for the B.B.C. to pay, except in the experimental stages, and then only the cost of actually setting up the stations. In any event, and precisely as we Conservatives warned the Government, practically no money has been raised locally except through the rates and the B.B.C. has had to pay much more than was intended.

Local Authorities will not go on paying for the stations and it would be wrong if they did. I do not favour a system of finance which smacks of sponsorship. What does a Local Authority do when the station it subsidises is over-critical of its doings?

As Lord Hill has rejected raising funds by advertisement and the Postmaster General has said that the B.B.C. ought not to pay for local radio from its general licence revenue, and sufficient money is not forthcoming locally, the experiment is heading for a totally foreseeable financial collapse. ■

combined loudspeaker and S-meter

F. G. RAYER

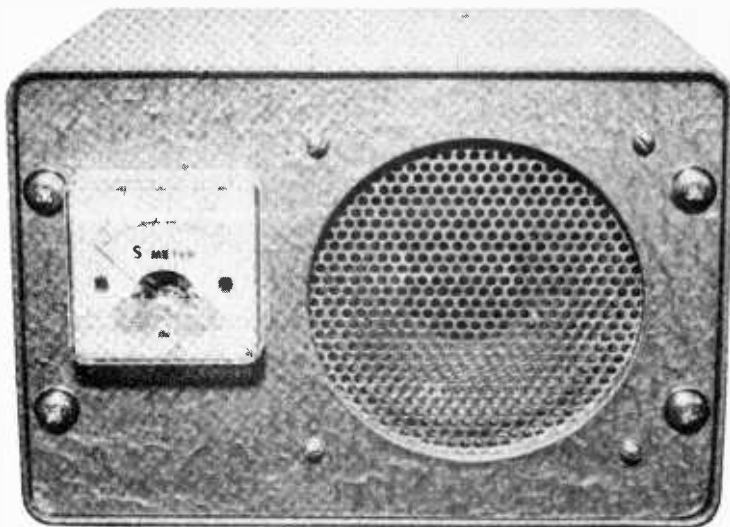

MANY commercial communications receivers have no internal speaker or S-meter, and most users find that they have to provide these themselves. They can easily be combined in a neat and compact unit, and with receivers such as the Eddystone 640, 740, 750 and 888A, the S-meter connection can simply be made via an octal plug in the rear socket provided. With other receivers however, such as the CR100, an internal connection will have to be made.

A ready-calibrated S-meter was fitted in the unit shown, this simply being a 1mA moving coil meter, with an appropriate scale. It is therefore possible to use an ordinary 1mA meter, or a 500 μ A, 250 μ A, or 100 μ A instrument. The latter can provide increased sensitivity, if required, but means that the scale will have to be calibrated by the constructor.

The speaker fitted was a 3 $\frac{1}{2}$ in. moving coil unit, and this allowed everything to fit in a 6 $\times$ 4 $\times$ 4 "Dinkicase". There is, of course, no reason why this size speaker has

to be used, and it might be possible merely to fit the S-meter in an existing speaker cabinet.

Figure 1 is the circuit used, but Fig. 2 may be more convenient with some receivers. Both employ a bridge arrangement in which the meter reads zero for minimum signal strength, the reading rising as signal strength increases.

Cathode Circuit

The meter is connected to the cathode of a valve which receives automatic gain control bias (generally an i.f. stage). R1 and R2 form a potential divider, with VR1 for zero adjustment. With no signal present, VR1 is adjusted so that the voltage drop across the cathode resistor R_k equals that in the lower part of the resistor network, so no voltage is present across the S-meter.

When a signal is present, a.g.c. bias reduces cathode current. Current through R_k falls, resulting in a smaller voltage drop in R_k. The meter negative terminal thus moves negative, giving a reading. Movement of the meter pointer depends on the a.g.c. voltage, and thus on the strength of the received signal.

R2 needs to be similar to R_k in value, and can be 330 Ω for many valves of the 6K7 and similar type, but should be 68 Ω for the 6BA6. R2 can be omitted if VR1 is adjusted carefully, a portion of VR1 then substituting for R2.

Anode Operated

In Fig. 2, C1 and R1 may be present. If not, these or similar values can be fitted. When anode current falls (with increased signal strength) reduced voltage drop in R1 results in the application of a positive voltage to the meter.

In both circuits VR1 need not be 500 Ω . VR1 should be wire-wound, and preferably not over about 2k Ω , or its adjustment becomes critical.

Should values in a receiver be such that VR1 does not allow the meter to read zero, with no signal input, this can be corrected by changing R1 or R2 in Fig. 1, or R2 and R3 in Fig. 2. Actual values are not too important, provided the circuit can be balanced for no voltage across the meter, with no signal.

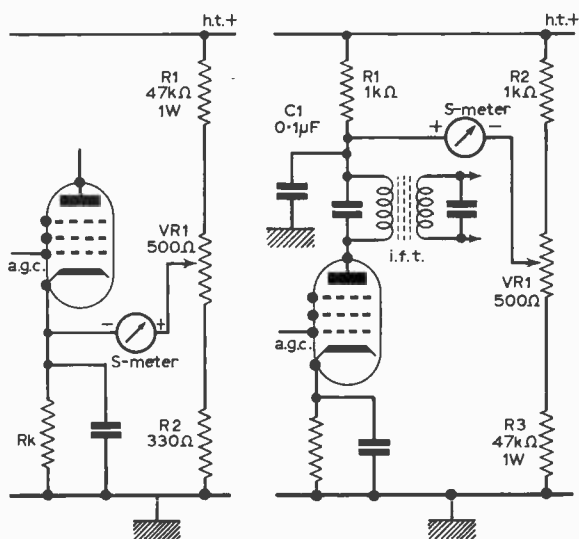


Fig. 1: (Left), An S-meter operated from the cathode circuit of the last i.f. amplifier

Fig. 2: (Right). An S-meter connected to the anode circuit.

The sensitivity of either circuit may be reduced by placing a resistor in series with the meter. A pre-set will allow adjustable sensitivity.

Construction

The few components can be fitted in any suitable case, similar to Fig. 3. The speaker circuit is quite separate to that for the S-meter, and it is wise therefore to colour code the flexible leads for the latter: red for h.t. positive, green for cathode (or C1, Fig. 2) and black for chassis return.

For the Eddystone receivers mentioned, connections can be to an octal plug or the base of an old octal valve. Viewing this plug from the pins, and counting clockwise from the key-way, take red to pin 1, green to pin 2, and black to pin 8. As a series diode is present, set the meter pointer mechanically a little below zero. Short receiver aerial to earth, and adjust VR1 for zero on the meter.

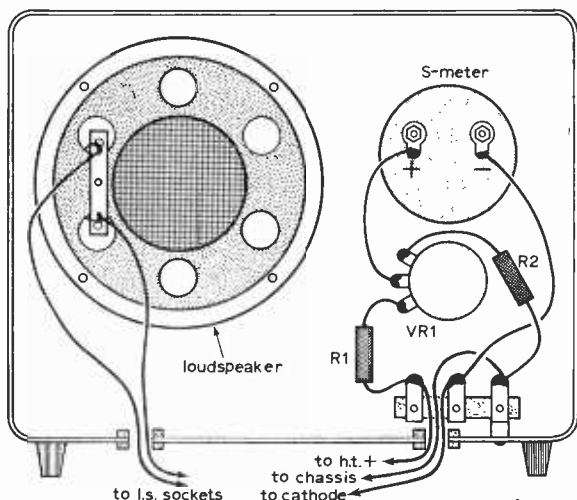


Fig. 3: The wiring in the box used by the author.

With other receivers, locate the cathode or h.t. side of an i.f.t. in a stage controlled by a.g.c. bias, and connect as in Fig. 1 or Fig. 2. If the unit needs to be readily detached, any convenient means could be used, such as a valve base, B7G miniature plug or 3-pin plug, and socket to match.

CQ! CQ! CQ! CQ! CQ! CQ!

APPARATUS REQUIRED

... pressure roller for a Walter 101 tape recorder.—D. Burke, 51 Carna Drive, Glasgow, S.4.
... an X79 radio valve. All the normal sources have been tried with no success.—E. Pennington, 4 Northdown Road, Longfield, Kent.

CORRESPONDENTS WANTED

... anyone using an Eddystone S640 with an interest in s.s.b.—H. Bolwell, Ivanhoe, Lodge Lane, Wrexham, Nr. Bristol.
... someone of about my own age (15½) who simply adores physics.—M. McNally, 17 Crosslees Park, Thornliebank, Glasgow, Scotland.
... any female (16-18) who is interested in any form of radio, electronics, organic chemistry or any other science.—W. Gunn, 9 Brannen Terrace, Dornoch, Sutherland-shire, Scotland.
... anyone of my own age (15) who shares my interests in semiconductor circuitry and amateur radio in general.—D. Hogon, 4 Priors Croft, Walthamstow, London, E.17.

TAPESENDERS WANTED

... any English-speaking female of my own age (15). My tape recorder is a Philips four-track with speeds of 1½ and 3½ i.p.s. Maximum reel size is 7in. My interests are radio, tape recording, electronics, and pop records.—S. Isherwood, 3 York, Nr. Langho, Blackburn, Lancashire.
... any female about my own age (15). I have a HMV recorder with four tracks, and a speed of 3½ i.p.s. Spool size is up to 5½in. I am interested in electronics, music and photography.—M. McCluskey, 23 Woodley Grove, Ormesby, Teesside.

THE MW COLUMN

WHEN the writer expressed the hope earlier in the season that a fall in sunspot activity might lead to improved conditions on the medium waves he was hardly prepared for what followed. December and January brought the finest North American DX for several years. Joe Stephenson of Hull reports: "On New Year's Eve CBA (1070) was interfering with Paris at 2100hrs GMT—at midnight on the 3rd January WOWO (1190) in Fort Wayne, Indiana was a fantastic S8-S9." Other items from Joe's log include CFCY (630) Charlottetown, Prince Edward Island; WJR (760) Detroit; WHAS (840) Louisville, Kentucky; WABI (910) Bangor, Maine; WCFL (1000) Chicago; WTIC (1080) Hartford, Connecticut; KMOX (1120) St. Louis; WWVA (1170) Wheeling, West Virginia; WGAR (1220) Cleveland; CKCW (1220) Moncton, New Brunswick; ZBM1 (1235) Hamilton, Bermuda; CKBL (1250) Matane, Quebec; CKOY (1310) Ottawa; WEGP (1390) Presque Isle, Maine; WENE (1430) Endicott, N.Y.; WPTR (1540) Albany, N.Y.; WQXR (1560) New York City. Joe uses a Hammarlund SP600, a TV aerial and an aerial tuning unit.

The writer's best catch came from the Caribbean when he heard St. Vincent (705) in the Windward Islands close down at 0218hrs GMT on December 19th. This station is only 500 watts and it verified with a quite specific but rather unattractive QSL card. Although the good conditions of mid-winter ended with a fadeout in February the indications are that we are 'over the hump' and we can look forward to some good DX as sunspot activity continues to decrease.

Traditionally, medium wave DXing is a winter occupation to be abandoned as the days lengthen, though in actual fact the hobby can be pursued throughout the year. North American stations are often audible in midsummer for about an hour before sunrise. Static from local thunderstorms can be troublesome but QRM from Eastern Europe is much less severe than in winter since this area is in daylight. DX from East and South Africa is often possible in May and June. South Africa has been heard on 782 and 1286 between 0200 and 0300hrs.; Mozambique on 917; Dar es Salaam, Tanzania on 638.

It is from South America though that the bulk of summertime DX is obtained. This continent is, of course, having its winter during this period. From June to September for about 2 hours before sunrise is the time to look for YVKS (750) *Radio Caracas*, Venezuela; HJKC (850) Bogota, Colombia; CX16 (850) *R. Carve*, Montevideo; PRA3 (860) Rio de Janeiro; CX20 (930) *R. Montecarlo*, Montevideo; PRF4 (940) *R. Journal*, Rio; LR3 (950) *R. Belgrano*, Buenos Aires; OAX4U (1010) *R. America*, Lima, Peru; LS10 (1030) *R. Libertad*, Buenos Aires. When conditions are favourable some remarkably strong signals can be heard.

CHARLES MOLLOY

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times GMT
Frequencies in kc/s

THE BROADCAST BANDS by CHRISTOPHER DANPURE

HERE we are in the month of April, with the good DX conditions which come with spring. But the only problem I find is that directly the h.f. bands of 25, 21 and 17Mc/s stay open later at night, we get swamped by *R. Free Europe* in Lisbon with 250RW blotting out all we have gained with better conditions. Still that's the way the conditions play, it all comes back to the need for frequency control by an international committee to halt the chaos before it goes too far.

Next on the list comes the month's propagation conditions as prepared by Cable and Wireless of London.

South Africa: 0800-1400 25, 21 and 17Mc/s; 1400-1700 25, 21, 17 and 15Mc/s; 1700-1800 25, 21, 17, 15 and 11Mc/s; 1800-2000 21, 17, 15, 11 and 9Mc/s; 2000-2200 17, 15, 11, 9, 7, 6 and 5Mc/s; 2200-0200 15, 11, 9, 7, 6 and 5Mc/s; 0200-0400 9, 7, 6, 5 and 4Mc/s; 0400-0600 11, 9 and 7Mc/s; 0600-0800 21, 17 and 15Mc/s.

South Asia: 0800-1200 21, 17 and 15Mc/s; 1200-1400 21, 17, 15 and 11Mc/s; 1400-1600 21, 17, 15, 11 and 9Mc/s; 1600-1800 15, 11, 9, 7 and 6Mc/s; 1800-2000 15, 11, 9, 7, 6 and 5Mc/s; 2000-2200 11, 9, 7, 6, 5 and 4Mc/s; 2200-2400 11, 9, 7, 6, 5, 4 and 3Mc/s; 2400-0200 9, 7, 6 and 5Mc/s; 0200-0400 11 and 9Mc/s; 0400-0600 15 and 11Mc/s; 0600-0800 17 and 15Mc/s.

South East Asia: 0800-1200 21 and 17Mc/s; 1200-1400 21, 17 and 15Mc/s; 1400-1600 21, 17, 15, 11 and 9Mc/s; 1600-1800 17, 15, 11, 9 and 7Mc/s; 1800-2000 15, 11, 9, 7, 6 and 5Mc/s; 2000-2200 11, 9, 7, 6 and 5Mc/s; 2200-2400 11, 9 and 7Mc/s; 2400-0200 9Mc/s only; 0200-0400 11Mc/s only; 0400-0600 15Mc/s only; 0600-0800 17Mc/s only.

North East Asia: 0800-1400 17 and 15Mc/s; 1400-1800 11Mc/s only; 1800-2000 11 and 9Mc/s; 2000-2200 11 and 9Mc/s; 2200-0200 circuit closed; 0200-0400 11Mc/s only; 0400-0600 circuit closed; 0600-0800 15Mc/s only.

E. Australia via Asia: 0800-1000 21Mc/s only; 1000-1200 17Mc/s only; 1200-1400 15Mc/s only; 1400-1600 15 and 11Mc/s; 1600-1800 11 and 9Mc/s; 1800-2000 11, 9 and 7Mc/s; 2000-2200 11 and 9Mc/s; 2200-2400 11Mc/s only; 2400-0800 circuit closed.

West Coast of South America (North of Chile): 1200-1600 21 and 17Mc/s; 1600-2000 21, 17 and 15Mc/s; 2000-2200 17, 15 and 11Mc/s; 2200-2400 15, 11, 9 and 6Mc/s; 2400-0600 11, 9, 6, 5, 4 and 3Mc/s; 0600-0800 15, 11, 9 and 6Mc/s; 0800-1000 11 and 9Mc/s; 1000-1200 15 and 11Mc/s.

Now what information have we next for the DX-tips? Firstly, *Radio Nederland* has a very useful DX Information Catalogue listing all the free publications which interest DX-ers that *R. Nederland* publish. The address is *R. Nederland*, English Section, P.O. Box 222, Hilversum, Holland. *R. Nederland* have also issued a special Red, White and Blue QSL card for the full

operation and opening on their relay base at "Bonaire Noord". Reports on the new transmissions from Bonaire in May will be QSL'd by the new card first, before the Lopik reports receive the new card, if any are left. So now down to those DX-tips.

AFRICA

Ethiopia: *Radio Voice of the Gospel*, station ETLF, is now on the following schedule: 0300-0425 11,730; 0330-0425 9,680; 0430-0555 15,400; 0445-0525 15,180; 0530-0555 11,890; 1230-1300 17,760 or 17,815; 1300-1510 15,315; 1330-1625 15,400; 1515-1555 15,315; 1600-1710 6,065; 1630-1655 11,770 or 11,735; 1700-1755 9,695; 1715-2015 11,910; 1800-1900 9,705; 1900-1945 15,410.

South Africa: There have been last minute alterations to *Radio R.S.A.* transmissions, the last published details are correct except for these transmissions: 0956-1050 now 21,535, 17,825 and 15,220, and 1156-1250 now 17,825, 15,220 and 11,900.

PACIFIC AREA

Australia: *R. Australia's* booster station at Darwin is now on the following test transmissions with reduced power of 100kW on beam 300° directed to Central S.E. Asia. 0030-1000 Sundays only on 15,355 in English, Mon.-Sat. from 0830-1000 only in English on 15,355, daily from 1000-1130 in Indonesian on 6,050 and 1130-1330 in Mandarin and Vietnamese on 9,650. The other alterations to Shepperton and Lyndhurst transmissions, is now the 1000-1212 service on 9,580 to N.E. Asia stops at 1100 and the East Coast N. American service from 1212-1315 now starts at 1112-1215 on 11,710 and 9,580. And the Mid-Pacific service from 0830-1212 now runs on 7,205 instead of 7,190.

EUROPE

Fed. Rep. Germany: The *Deutsche Welle* at Cologne has had a complete shuffle of all its transmissions from the Jülich transmitters. In brief, the German transmissions are now only 2 hours 10 minutes' duration instead of 2 hours 55 minutes. There is now a daily Japanese service and the Chinese and English broadcasts have been extended. The English transmissions are now: 0120-0200 on 11,965 and 9,545; 0130-0250 on 9,735, 6,185 and 6,130; 0345-0405 on 9,545 and 7,290; 0435-0555 on 11,945, 9,545 and 6,145; 0600-0630 on 17,845, 15,275 and 11,785; 0920-1020 on 21,560, 17,845, 17,740 and 11,795; 1045-1055 on 15,315, 11,905 and 9,605; 1700-1735 on 17,875 and 15,275; 1900-1910 on 17,790, 15,405 and 11,795 and then 2100-2200 on 15,275, 9,765 and 7,290. The new Japanese service is transmitted from 1120-1220 on 21,580, 17,705 and 15,275.

Well that's all the space we have, so remember those DX-tips to be in by 18th April, good DX-ing and 73s.

MIXED conditions seem to be the verdict for this past month on the amateur bands, but on the whole very satisfying for those who persisted. Twenty metres has become almost a 24-hour band although there were times when one seemed ear-deep in EU stations all calling CQ DX.

Fifteen has really come into its own and provided some juicy prefixes. It hasn't stayed open as long as 20 and at the time of writing it opens around 0700 and fades at 2100. Its stable-mate, 10 metres, has been a bit of a disappointment. The first part of the month saw 10 as a very slow starter but it did make the effort later. It opened about the same time as 15 but seemed to close an hour or so earlier.

A very excellent month for the 1.f. sections, and there was quite a lot of activity on 40, 80 and 160. A number of W stations have been prominent on 160, while on 80 and 40 some sleuths have detected some very nice DX.

A good tip for all bands is to listen during that twilight time when the band is just starting to close. Very often one can catch some very good DX about this time although it is admittedly usually weak, and certainly c.w. offers the best bet for hooking something really good.

Reports tell tales that the infamous Citizens' Band is peaking very well. Tune from 27 to 28Mc/s for interesting dialogue and quite startling revelations. Rumours that ZL stations are peaking on 80 at 0730 but my receiver just won't confirm this.

A number of letters query how to send in reports. Just for the record here's the basic requirements: date, time (GMT), frequency, call-sign, mode (c.w./s.s.b./a.m.), gear in use, aerial and last but most important—call-signs in alphabetical order please; it makes it so much easier.

LF LINGERINGS

A 5RV aerial entwined around the rhubarb and the loan of an AR88LF add up to a log from **David Pick** (Leicester). He confesses to passing R.A.E. (welcome to the club OM) and to great concentrations on c.w., meanwhile his s.s.b. log for 160 reads—EI4AN, GC3UJE, GD6IA, GI6TK, GM3YCB, GW3UCB, HB9CM, HB9T.

P. Tones (Dorset) has a B40 and a quarter-wave aerial for 160. His efforts to read c.w. resulted in sigs from—DL9KRA, HB9CM, K1LMO, K2GNC, K4WUY, KV4FZ, OK1AES, OK1ATP, OK1FAB, OK2BOB, OK3BU, OL6AKP, W2CRS, W2EQS, W2FJ, W3DPJ, W3EOP, W3FE, W3IN, W3TV, W8AH, WA3EPT, WA8EMJ.

"Why are 80 metre logs so sparse in your columns?" **W. Wright** (Staffs) writes this query and promptly furnishes a log to prove what's about. He claims that there's plenty of DX on the band and he's logged—CO2DC, CT2AP, CT2AS, EL8J, F9UC/FC, HI7VDC, HK3AIS, HP1JC, K1CEC, K2DPA, K3NPV, K3UZE, K8HZU, KP4CL, KZ5WH, KZ5JQ, LA2PH/MM, OD5BA, OHØNC, PJ7JC, SL7AY/MM, UH8AE, U18LM, VE1IARY, VE2AFM, VE3BSU, VO1FX, VP7NH, VP9BK, W1BL, W1BGD/2, W2LV, W3MSK, W4IHK, WA8LEO, XE1ZB, XE3EB, YV5ANF, ZD8Z, ZL4AK, 4X4UF, 6Y5CC, 6Y5DW, 9E3USA,

9H1BL. The receiver is an RG-1 and the aerial a 180ft. end fed.

N. Thornley (Northampton) plans to be 14 years old in one year's time. He is passing the time with an R107 plus 80ft. end fed. Rewards for his labours on 80 metres include—CM2DC, CT1LN, F9UC/FC, HV3SJ, K3UZE, KZ5RP, KZ5WH, VE1AMJ, VE3DJE, VE8RCS (Ellesmere Island), VO1FX, W51OU, XE1KB, XE3EB, ZL2BCG, 4X4GV. Cor, wish I was 13 and had an R107.

Mock GCEs and Christmas are said to have seduced **D. Henbry** from proper care and listening on his HA500. Still, the 7ft. rod aerial at 30ft. is still standing faithfully to attention and during a weak moment David confesses to hearing—CR6GA, K6AHE, KR6JD, PY1CAD, OD5EJ, PY2PA, PY7VKZ, W6KG, W6QV, ZD8Z, ZL1ATS, ZL3LE, 4X4VL, 6W8DY, 9J2VX.

HF HAPPENINGS

After reading David Henbry's log for 40 I thought I stood a good chance with my 20 metre bests. However, I can't even boast of these coz **S. Mummery** presented me with this basket of goodies all on 20 s.s.b.—CR6LF, EP3AM, H18LA, JA5HB, OY7S, PJ2PJ, PZ1BG, VK3AKP, VK6MN, VK9BJ, XE3AT, XE1EA, YV5ANF, ZF1GC, ZL1KN, ZL3JO, ZP5KN, ZS1YF, ZS5KAL, ZS6BJ, 5A5TS, 5R8AS, 6Y5GB, 8P6CV. I'd just sipped my gripe water when I saw his log for 15—JA1KXY, OD5AT, OHØNI, PY2CYT, SVØWN, TF5TP, VK2EK, VK2XT, VK5BB, WA5EQN/MM (China Seas), YV1EL, YV5CMQ, ZC4HS, ZL2KD, 4X4RW. The mode was s.s.b. and the receiver a B34.

L. Bousher (near Swansea), has been reported as "at it" on 20 s.s.b. Thirty feet of wire and an R1155 is all that stood between him and—CN8GE, CN8MJ, CR6IV, EA6BI, EL8J, ET3REL, JA2BTU, MP4TCF, OA8RT, OX5BA, OY7Z, PY7ASQ, PZ1BG, SU1IM, TF2WLM, VE1KG, VE3BZK, VE7IL, VE8RCS, VK2AVA, VK6XW, VP8KD, VS6DR, YA5RG, ZB2AY, ZC4TK, ZD9BE, ZE1BP, ZL1AXB, ZL4BX, ZS3HF, ZS6OY, 3A2CO, 5A4TF, 5H3KJ, 6W8DY, 9G1GD, 9H1M, 9K2CF, 9L1HT, 9X5AA.

D. Honeywood (Surrey) CR300/1, dipole, 20—JA1JBB, TF2WLM, VK2AVA, VK2XQ, VK3MO, VK4HR, ZL1AHT, ZL5VK, 3A2CL, 5N2ABG.


J. Moore (Leicester) CR100/2, 60ft. end fed, claims that the following are only radiating one sideband on 15—CO8RA, CP5DM, CR8AH, EA6AR, HC2HM, H13AGS, H1KKS, K6SHA, MP4MBB, TF2WLM, VE6AAV, VK2FA, VK3VK, VK5GF, XE1LLS, YA1HD, ZD3D, 9Y4EH.

HERE AND THERE

Quite a few happenings in April. On the 6th is the ARMS mobile meeting at Lydd Airport in Kent; 12th-13th, 4 metre contest; 20th, North Midlands mobile rally at Drayton Manor Park in Staffs; 26th, VHF/UHF convention at the Winning Post Hotel, Whitton, near Twickenham; 27th, The Belle Vue Convention at Manchester. May 3rd-4th, 2 metre portable contest. That's all for now, and bcnu all again next month.

BASIC SEMICONDUCTOR TECHNOLOGY

PART ONE

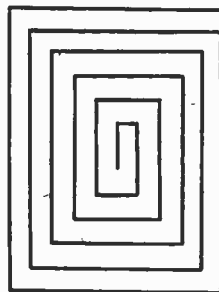

by M.F. DOCKER, M.Sc.

EVERY material is composed of submicroscopic particles called atoms. Some materials contain only a single type of atom, these substances being called elements. Other materials, called compounds, contain several types of atom combined to form molecules. No matter how much a compound is chemically refined it will still contain the same ratio of atoms of the different elements of which it is composed. The molecule thus contains a certain fixed number of each type of atom; for example a water molecule contains two hydrogen atoms and one oxygen atom.

The atom has been shown to contain various elementary particles—electrons, protons, neutrons and others which will not be of concern to us in these articles. The electron has a very small mass, 9×10^{-28} gram, and a negative charge of 1.6×10^{-12} e.s.u.; the proton has a mass 1,840 times that of the electron and a charge equal to that of the electron but of opposite sign. The neutron has a mass equal to that of the proton but carries no charge.

Figure 1 shows a model of an atom of helium which has two electrons encircling a nucleus composed of two protons and two neutrons. The nucleus

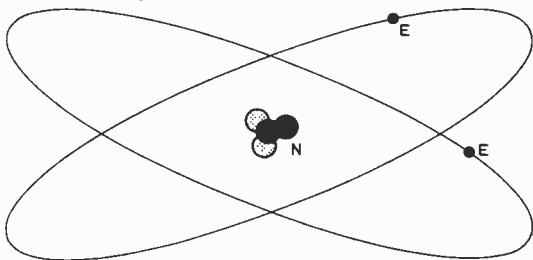


Fig. 1: Representation of a helium atom, showing the electrons *E* in orbit around the nucleus.

thus has a charge of plus two which is precisely balanced by the negative charge on the electrons, leaving the whole atom electrically neutral. The mass of one helium atom is equal to four times that of the proton, neglecting the masses of the electrons.

Many atoms can be shown to have masses which differ although they are chemically the same. These are isotopes of one element, having the same atomic structure as each other except that the number of neutrons is different. Thus hydrogen has three isotopes; hydrogen, deuterium and tritium; having one neutron, two and three neutrons respectively. As the chemical properties of the atom are determined mainly by the electrons, and as *their* number remains unchanged from isotope to isotope, the properties of isotopes of the same element are virtually the same as each other.

The electrons of an atom move in orbits around the nucleus. They are not clearly defined paths, such as planetary orbits, but more regions in which the electrons may be expected to be found. Another finding of modern atomic theory is that the electrons are arranged into certain groups called shells. Those atoms that have just sufficient electrons to completely fill a shell are particularly stable. Examples of these are helium, neon and argon. These substances do not form compounds easily.

Electrovalent Bonding

In atoms not containing the "magic" numbers of electrons it is the electrons which are not in a full shell that account for most of the properties of the atom. Thus sodium with one excess electron combines with chlorine which has seven excess electrons to form sodium chloride. In this case the sodium donates its excess electron to the chlorine atom, leaving itself positively charged; the chlorine atom accepts one electron to make up a complete group of eight electrons, the chlorine atom then having a net charge of minus one. Since one electron has changed hands the sodium and chlorine are both said to have valencies of unity. Other atoms have valencies of 2, 3, 4 and 5.

This type of atomic bonding is called electrovalent bonding. Other types of bonding are possible, the most important being covalent bonding where two or more atoms share electrons in order to make up the full shells which give a stable atomic structure. This occurs in hydrogen which has one electron per atom: two atoms combine to form a single hydrogen molecule, the electrons being shared between the two atoms to give a stable structure with the first shell, which contains two electrons, being filled.

Crystal Structure

Most inorganic substances have a crystalline structure. The atoms of which the crystal is composed are bound together by covalent forces. For example carbon which has a valency of four forms a well known crystal, the diamond structure, in which each atom is surrounded by four other atoms. Each carbon atom has four electrons in its outer shell and shares one from each of its neighbours to make up the stable structure with eight electrons in the outer shell. Figure 2 shows the arrangement of the atoms in the diamond structure. Many other elements such as germanium and silicon have similar structures.


The outer shell of electrons is called the valence shell for reasons which should by now be obvious.

—continued on page 31

Mullard DATA BOOK for 1969

Get up-to-date with the latest Mullard Data Book—just published. It contains details of current Mullard valves, picture tubes, semiconductors and components for Radio, TV, Audio and HiFi applications. Each section, colour coded for quick reference, includes comparables and equivalents information plus details of the latest devices in the replacement market.

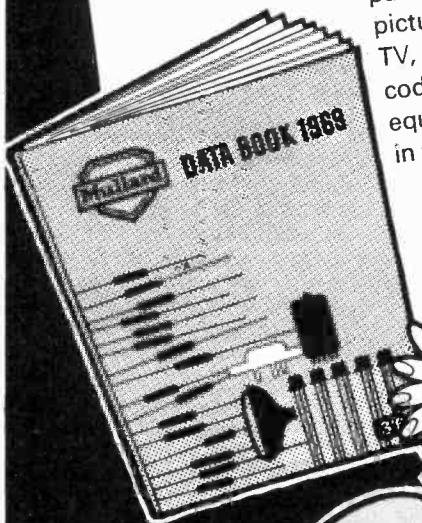Quick! Buy your copy from your local TV retailer
or send 3/6 plus 9d for postage and
packing direct to Mullard Ltd.



Mullard

Mullard Limited, Distributor Sales Division, Mullard House, Torrington Place, London WC1.

CED72

BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government

38 CHALCOT ROAD, LONDON, N.W.1

Telephone Primrose 9090

ALL GOODS LISTED BELOW, ACTUALLY IN STOCK. ALL GOODS ARE NEW. BEST QUALITY MANUFACTURE ONLY, AND SUBJECT TO MAKERS' FULL GUARANTEE, PLEASE NOTE THAT WE DO NOT SELL ITEMS FROM USED EQUIPMENT NOR MANUFACTURERS' SECONDS AND REJECTS, WHICH ARE OFTEN DESCRIBED AS "NEW AND TESTED" BUT HAVE A SHORT AND UNRELIABLE LIFE.

O42 5/9	6D3 7/6	12AD6 6/-	77 6/6	DLS10 9/6	EF95 4/6	MHL4 12/6	R12 6/9	VT61A 7/-	ASY29 10/-	O447 2/-
O82 6/-	6D6 3/-	12AE6 7/6	78 4/8	DM70 6/-	EF97 10/-	MHL5D 7/6	R16 34/11	VT501 3/-	BA102 9/8	O470 3/-
O24 4/8	6E5 7/8	12AT6 4/8	85A2 9/8	DM71 7/6	EF98 10/-	MU12/14/-	R17 17/8	VU111 7/3	BA115 2/8	O473 3/-
IA3 4/8	6F1 9/8	12AT7 3/8	90AG 6/8	DW4/350	EF183 6/-	MX40 12/6	R18 9/8	VU12 12/8	BA19 2/8	O479 1/8
IA5 5/-	6F6G 4/-	12AU6 4/8	90AV 6/8	DW4/500	EF184 6/-	N78 38/4	R19 9/8	VU120A12/8	BA20 2/8	O481 1/8
1ATG7 7/-	6F6M 12/8	12AU7 4/8	90CA 34/-		EF184 20/5	N108 27/4	R20 11/9	VU133 7/-	BA210 2/8	O485 1/8
IC1 5/8	6F12 3/3	12AV6 5/8	90CV 38/8		EH90 6/6	N152 7/8	RK34 7/8	W42 14/10	BCY10 5/-	O486 4/8
IC2 7/9	6F13 3/8	12AV7 8/8	90CI 18/8	DY86 5/6	EL32 3/8	N308 17/8	SP4 9/8	W63 10/8	BCY12 5/-	O490 2/8
IC3 7/-	6F14 15/-	12AX7 4/8	150B2 14/6	DY87 5/6	EL33 12/-	N339 25/-	SP13C 12/8	W76 9/8	BCY13 5/-	O491 1/8
IC5 4/9	6F15 9/8	12AY7 9/9	150C2 5/9	E80F7 24/-	EL34 9/8	N359 7/3	SP42 12/8	W77 2/8	BCY34 4/8	O4182 2/8
1D5 6/9	6F17 12/8	12BA6 6/8	301 20/8	E83T 24/-	EL35 10/8	N389 12/8	SP61 3/8	W81M 6/8	BCY38 5/8	O4200 1/8
1D6 9/8	6F18 7/8	12BA6 5/8	302 18/8	E89CC 6/8	EL36 8/8	P61 2/8	TDD4 8/8	W101 28/8	BCY39 4/8	O4202 2/8
1FD1 6/-	6F23 13/8	12BH7 6/8	303 15/-	E18HCC 8/-	EL37 17/3	PABC80 7/8	TH4B 10/8	W107 7/8	BCZ11 3/6	O4210 9/8
1FD9 3/9	6F24 11/9	12E1 17/8	306 18/6	E180F 17/6	EL41 9/8	PC86 9/8	TH233 7/-	W229 10/8	BC107 4/8	O4211 13/8
1G6 6/-	6F25 11/8	12F5GT 2/6	306 18/8	EA50 1/8	EL42 9/8	PC88 9/8	TP22 5/-	X24 16/8	BC108 3/6	O4220 12/8
1H5GT 7/-	6F28 10/8	12JGT 6/8	807 11/8	EAB76 13/-	EL41 8/-	PC95 8/8	TP25 5/-	X41 10/8	BC109 4/3	O4230 10/8
1L4 2/6	6F32 3/-	12K5 10/-	956 2/-	EAB8C0 6/8	EL43 6/8	PC97 8/8	TP26 20/9	X61 5/8	BC113 5/8	O4232 9/8
1LD5 5/-	6G6G 2/8	12K7GT 5/8	1821 10/8	EAC91 3/-	EL44 9/8	PC98 8/8	UAB8C0 5/8	X63 5/8	BC115 3/8	O4233 9/8
1LN5 6/-	6H6GT 1/8	12K8GT 7/8	5763 10/8	EAF42 8/8	EL45 7/8	PC94 8/8	UAF42 9/8	X64 12/6	BC116 5/8	O4234 9/8
1P1 7/-	6J5GT 4/8	12Q7GT 4/6	6060 10/8	EB34 7/8	EL46 8/8	PC85 6/6	UB41 6/8	X65 5/8	BC118 4/8	O4235 9/8
1P10 4/8	6J6 3/-	12S4GT 6/8	7138 10/8	EB41 4/8	EL49 2/6	PC88 9/8	UBC41 7/8	X66 7/8	BD119 8/8	O4236 9/8
1P11 5/8	6J7G 4/8	12S7GT 3/8	A1834 20/-	EB91 2/8	EL45 5/8	PC88 9/8	UBC81 7/8	X76M 7/8	BFY60 4/8	O4237 10/8
1R5 5/8	6J7GT 6/8	12SH7 3/8	AC2PEN	EB91 2/8	EM71 14/-	PC88 9/8	UBF80 5/8	X81M 30/8	BFY51 4/8	O4238 10/8
1R4 4/8	6K6GT 5/8	12S7GT 4/8	AC2PEN	EB91 2/8	EM80 6/8	PC88 9/8	UBF89 9/8	X89 18/8	BFY52 4/8	O4239 10/8
1R5 3/8	6K7G 2/8	12S8GT 4/8	AC2PEN	EB91 2/8	EM81 6/8	PCF82 8/8	UBL21 9/8	X109 28/8	BF154 5/8	O4244 5/8
1T4 2/9	6K7GT 4/8	12S9GT 3/8	AC2PEN	EB91 2/8	EM84 6/8	PCF84 8/8	UC92 5/8	Y83 5/8	BF159 5/8	O4245 16/8
1U4 5/8	6K8G 3/8	12S7GT 4/8	AC2PEN	EB91 2/8	EM85 11/-	PCF86 9/8	UC94 8/8	Y85 10/8	BF163 4/8	OC19 25/-
1U5 6/8	6K8GT 7/8	12Y4 2/-	AC2PEN	EB91 2/8	EM97 7/8	PCF80 7/8	UC95 8/8	Z63 4/8	BF180 12/8	OC22 5/8
2A7 12/8	6L1 19/8	13D1 5/8	19/8	EBL21 11/-	EY81 7/8	PCF802 9/8	UCF80 8/3	Z77 3/8	BF181 8/8	OC23 5/8
2D13C 7/8	6L6GT 7/8	13D3 9/8	AC2PEN	EC92 8/8	EY83 8/8	PCF806 12/8	UCF89 9/8	Z399 25/8	BF182 8/8	OC24 5/8
2D21 5/8	6L7 12/8	14H7 9/8	19/8	EC93 12/6	EY84 7/8	PCF808 12/8	UCH42 9/8	Z729 6/8	BTX34/400	OC25 5/-
2X2 4/8	6L8 12/8	14S7 15/8	AC2PEN	EC94 11/-	EY86 6/8	PCF81 9/8	UCL82 7/-			OC26 5/8
3A4 3/6	6L19 19/8	18 12/8	AC2PEN	EC97 4/8	EY87 6/8	PCF82 7/8	UCL83 10/8			OC28 5/8
3A5 10/-	6LD20 8/8	19 10/8	AC2PEN	EC98 10/8	EY88 7/8	PCF83 9/8	UCF41 9/8	20225 10/8	BY105 10/8	OC30 8/-
3B7 5/8	6N7GT 6/8	19A05 4/8	AR3P 7/8	EC99 10/8	EY89 8/8	PCF84 7/8	UCF42 6/8	20227 10/8	BY106 10/8	OC31 8/-
3D6 3/8	6P1 12/8	19Q1 40/-	ATP4 2/8	EC92 6/8	EZ35 6/8	PCF85 8/8	UP80 6/8	202369A 4/3	BY234 4/3	OC36 7/8
3D4 6/8	6P25 12/8	20D1 13/8	AZ1 8/8	EC93 15/6	EZ40 7/3	PCF86 8/8	UP85 6/8	202369A 4/3	BY236 4/3	OC38 11/8
3Q5GT 7/8	6P26 12/8	20D4 20/5	AZ31 8/8	EC93 4/8	EZ41 7/3	PCF88 15/8	UP86 9/8	2023121 50/8	BY236 4/3	OC41 10/8
384 4/8	6P28 25/8	20F2 14/8	AZ41 7/8	EC93 29/1	EZ42 4/8	PCF89 15/8	UP89 6/8	2023703 4/3	BY238 4/3	OC42 6/8
3Y4 5/8	6Q7G 6/8	20L1 13/8	B36 4/8	EC93A 29/6	EZ51 4/8	PCF90 15/8	UP90 6/8	2023708 20/8	BY239 20/8	OC43 23/8
4D1 3/8	6Q7GT 8/8	20P1 17/8	B39 6/8	EC94 9/8	EZ52 4/8	PCF91 15/8	UP91 6/8	2023709 20/8	BY240 20/8	OC44 24/8
5R4GY 9/8	6RTG 7/8	20P3 18/8	B729 12/8	EC94 12/8	EZ53 4/8	PCF92 15/8	UP92 6/8	2023710 20/8	BY241 20/8	OC45 24/8
5U4G 4/8	6R4GT 7/8	20P4 18/8	E133 10/8	EC94 12/8	EZ54 4/8	PCF93 15/8	UP93 6/8	2023711 20/8	BY242 20/8	OC46 24/8
5V4G 7/8	6R4T 7/8	20P5 18/8	CK506 6/8	EC94 12/8	EZ55 4/8	PCF94 15/8	UP94 6/8	2023712 20/8	BY243 20/8	OC47 24/8
5Y3GT 8/8	6R4GT 6/8	25A6G 7/8	CL4 19/8	EC94 12/8	EZ56 4/8	PCF95 15/8	UP95 6/8	2023713 20/8	BY244 20/8	OC48 24/8
5Z3 8/8	6R6G 7/8	25L6G 5/8	CL33 18/8	EC94 12/8	EZ57 4/8	PCF96 15/8	UP96 6/8	2023714 20/8	BY245 20/8	OC49 24/8
5Z4G 6/8	6R7 7/8	25Y5 6/8	CV8 10/8	EC94 12/8	EZ58 4/8	PCF97 15/8	UP97 6/8	2023715 20/8	BY246 20/8	OC50 24/8
6J3012 12/8	6R7 6/8	25Y6 8/8	CV8 10/8	EC94 12/8	EZ59 4/8	PCF98 15/8	UP98 6/8	2023716 20/8	BY247 20/8	OC51 24/8
6A8G 5/8	6R7GT 6/8	25Z4G 7/8	CV8 10/8	EC94 12/8	EZ60 4/8	PCF99 15/8	UP99 6/8	2023717 20/8	BY248 20/8	OC52 24/8
6AC7 3/8	6R7GT 6/8	25Z5 7/8	CV8 10/8	EC94 12/8	EZ61 4/8	PCF100 15/8	UP100 6/8	2023718 20/8	BY249 20/8	OC53 24/8
6AG5 3/8	6R7GT 6/8	25Z6G 7/8	CV8 10/8	EC94 12/8	EZ62 4/8	PCF101 15/8	UP101 6/8	2023719 20/8	BY250 20/8	OC54 24/8
6AJ5 3/8	6R87 3/8	30C1 6/8	CV8 10/8	EC94 12/8	EZ63 4/8	PCF102 15/8	UP102 6/8	2023720 20/8	BY251 20/8	OC55 24/8
6AK5 4/8	6U4GT 12/8	30C15 13/8	CV8 10/8	EC94 12/8	EZ64 4/8	PCF103 15/8	UP103 6/8	2023721 20/8	BY252 20/8	OC56 24/8
6AK6 6/8	6U5G 5/8	30C17 12/8	CV8 10/8	EC94 12/8	EZ65 4/8	PCF104 15/8	UP104 6/8	2023722 20/8	BY253 20/8	OC57 24/8
6AK8 6/8	6U7G 7/8	30C18 12/8	CV8 10/8	EC94 12/8	EZ66 4/8	PCF105 15/8	UP105 6/8	2023723 20/8	BY254 20/8	OC58 24/8
6AL5 2/3	6V6G 3/8	30F5 13/8	D63 5/8	EC94 12/8	EZ67 4/8	PCF106 15/8	UP106 6/8	2023724 20/8	BY255 20/8	OC59 24/8
6AM4 16/8	6V6GT 8/8	30FL1 15/8	D77 2/8	EC94 12/8	EZ68 4/8	PCF107 15/8	UP107 6/8	2023725 20/8	BY256 20/8	OC60 24/8
6AM5 2/8	6X4 3/8	30FL12 16/8	DAC32 7/8	EC94 12/8	EZ69 4/8	PCF108 15/8	UP108 6/8	2023726 20/8	BY257 20/8	OC61 24/8
6AM6 3/8	6X5GT 8/8	30FL13 8/8	DAF91 3/8	EC94 12/8	EZ70 4/8	PCF109 15/8	UP109 6/8	2023727 20/8	BY258 20/8	OC62 24/8
6AQ5 4/8	6Y6G 8/8	30FL14 12/8	DAF96 9/8	EC94 12/8	EZ71 4/8	PCF110 15/8	UP110 6/8	2023728 20/8	BY259 20/8	OC63 24/8
6AR5 2/8	6Y7G 12/8	30FL15 12/8	DC90 10/8	EC94 12/8	EZ72 4/8	PCF111 15/8	UP111 6/8	2023729 20/8	BY260 20/8	OC64 24/8
6AT6 4/8	7A7 12/8	30L15 13/8	DD4 10/8	EC94 12/8	EZ73 4/8	PCF112 15/8	UP112 6/8	2023730 20/8	BY261 20/8	OC65 24/8
6AU6 5/8	7A7 6/8	30L17 13/8	DDT4 8/8	EC94 12/8	EZ74 4/8	PCF113 15/8	UP113 6/8	2023731 20/8	BY262 20/8	OC66 24/8
6AV6 5/8	7B6 10/8	30P4 12/8	DF33 7/8	EC94 12/8	EZ75 4/8	PCF114 15/8	UP114 6/8	2023732 20/8	BY263 20/8	OC67 24/8
6B9G 2/8	7B7 7/8	30P4MR	DF72 8/8	EC94 12/8	EZ76 4/8	PCF115 15/8	UP115 6/8	2023733 20/8	BY264 20/8	OC68 24/8
6B4G 4/8	7C6 6/8	30P4 12/8	DF91 2/8	EC94 12/8	EZ77 4/8	PCF116 15/8	UP116 6/8	2023734 20/8	BY265 20/8	OC69 24/8
6B8E 4/8	7D6 15/8	30P12 13/8	DF96 6/8	EC94 12/8	EZ78 4/8	PCF117 15/8	UP117 6/8	2023735 20/8	BY266 20/8	OC70 24/8
6B8G 20/5	7H7 5/8	30P19 12/8	DF97 10/8	EC94 12/8	EZ79 4/8	PCF118 15/8	UP118 6/8	2023736 20/8	BY267 20/8	OC71 24/8
6BH6 7/8	7R7 12/8	30P1L 15/8	DH30 15/8	EC94 12/8	EZ80 4/8	PCF119 15/8	UP119 6/8	2023737 20/8	BY268 20/8	OC72 24/8
6BJ6 6/8	7R7 20/8	30P1L15 15/8	DH63 6/8	EC94 12/8	EZ81 4/8	PCF120 15/8	UP120 6/8	2023738 20/8	BY269 20/8	OC73 24/8
6BQ5 4/8	7V7 5/8	30P1L14 15/8	DH76 4/8	EC94 12/8	EZ82 4/8	PCF121 15/8	UP121 6/8	2023739 20/8	BY270 20/8	OC74 24/8
6BQ7A 7/8	7Y4 6/8	30P1L15 15/8	DE77 2/8	EC94 12/8	EZ83 4/8	PCF122 15/8	UP122 6/8	2023740 20/8	BY271 20/8	OC75 24/8
6BR7 6/8	7Z4 4/8	35A5 15/8	DE81 4/8	EC94 12/8	EZ84 4/8	PCF123 15/8	UP123 6/8	2023741 20/8	BY272 20/8	OC76 24/8
6BR8 8/8	9BW6 7/8	35D5 11/8	DH101 25/-	EC94 12/8	EZ85 4/8	PCF124 15/8	UP124 6/8	2023742 20/8	BY273 20/8	OC77 24/8
6B8T 16/8	9D7 9/8	35L6GT 8/8	DH107	EC94 12/8	EZ86 4/8	PCF125 15/8	UP125 6/8	2023743 20/8	BY274 20/8	OC78 24/8
6RW6 12/8	10C1 12/8	35W4 4/8	16/11	EC94 12/8	EZ87 4/8	PCF126 15/8				

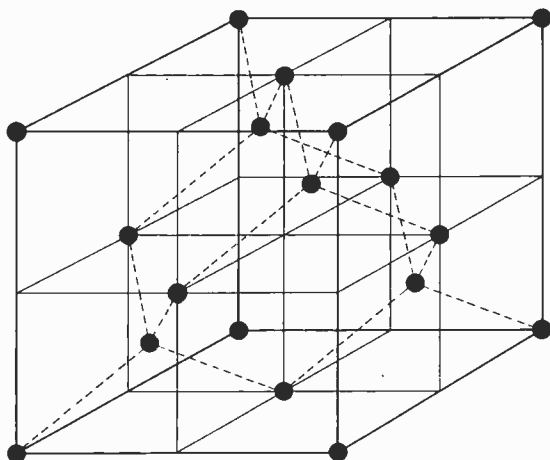


Fig. 2: Crystal structure of diamond. Each atom has four near neighbours as can be seen for those inside the crystal lattice structure.

Electrons in this shell are attached to the atom by electrostatic forces. If one of the electrons receives sufficient energy it may be able to reach the next highest band, the conduction energy band. The use of the term energy band calls for some explanation.

Energy Bands

When two systems having the same energy states, such as two pendula, are brought together they interfere with each other and the energy level is split into two. Thus in a crystal the energy levels which are discrete in the atom are split into millions of levels all close together. These constitute the energy bands of which more will be heard and which are illustrated in Fig. 3.

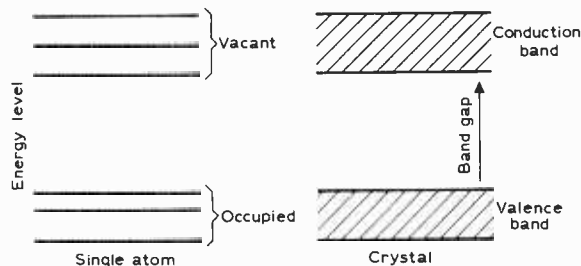


Fig. 3: Energy levels in a semiconductor atom and in semiconductor crystal.

These bands are separated in semiconductors and insulators, the difference in energy between the valence and conduction bands being called the energy band gap. In germanium the band gap is 0.67eV. (One electron-volt, or eV, is the energy that an electron gains when it is accelerated by a potential difference of one volt. About 3×10^{19} or three times ten million, million, million electron volts are required to warm one gram of water by one centigrade degree.)

The separation of these bands determines the conducting nature of a given material. In insulators the separation is large, the band gap being several eV wide. In order to lift these electrons from the valence to the conduction band a potential difference of several volts would thus have to exist across each atom. If this situation existed the insu-

lator would break down. In metals either there is no band gap, the valence and conduction bands being in contact, or else the valence band is only half full. A third alternative as seen in copper is that both these conditions are present. These three circumstances each lead to a high conductivity.

In semiconductors the band gap is quite small as mentioned previously for germanium. In this case thermal vibrations in the crystal lattice can lead to the excitation of electrons to the conduction band. This results in a small current flowing through the crystal when a field is applied to the sample. However the number of electrons liberated depends almost entirely on the thermal vibrations and not on the applied field. So when a voltage is applied across the crystal a current flows which does not vary with voltage. However it does depend on the temperature, being called *temperature-saturated current*. The number of electrons increases exponentially with temperature, the saturated current increasing similarly. This accounts for the reverse leakage currents experienced in solid-state diodes and transistors (Icbo).

n- & p-type Semiconductors

If an atom of phosphorus or another pentavalent element is introduced into a pure or "intrinsic" semiconductor crystal such as germanium there will be one electron which cannot enter into the covalent bonding. This electron will be only weakly bound to the atom since the presence of the surrounding atoms will substantially modify the local electrostatic fields, lowering the attraction by about a factor of ten. This electron thus requires only a small fraction of an electron volt to lift it to the conduction band, and this is easily supplied by heat in the crystal. Such an atom is called a donor atom and gives rise to a local donor state in the crystal. The material so formed is said to be doped with phosphorus and to be an n-type semiconductor.

Conversely if an atom having only three valence electrons such as aluminium is introduced into the lattice there will be a vacancy which can easily be filled by an electron from the valency band. Such an atom is called an acceptor atom. As before, the energy required to fill this acceptor state is very small. However a difference is apparent. Since electrons move from the valence band into these acceptor states these latter states must be near to the valence band rather than to the conduction band. The various states and energy bands are shown in Fig. 4. The vacancies result in electrons

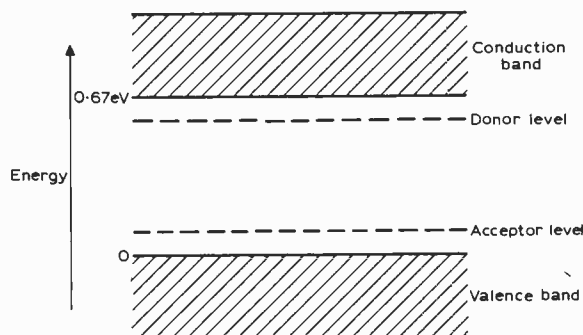


Fig. 4: Acceptor and donor energy levels.

moving from the valence band to fill them. These electrons leave behind them holes. The states into which the electrons move are called acceptor states. A material doped with aluminium is said to be a p-type semiconductor.

Hole conduction can be likened to the movement of cars in a circle of parking meter spaces, where the cars represent the valence electrons and the spaces the holes. If there are only a certain number of meter bays and they are all full no movement of cars can occur since no car is allowed to move into a bay which already contains a car. However if one car leaves the circle a bay becomes vacant and the cars can proceed around the circle step by step. It is obvious that the hole or vacant bay seems to move in the opposite direction to that in which the electrons or cars move.

Electrical conduction in a semiconductor can be due to movement of electrons in the conduction band or else to the movement of holes in the valence band. Conduction can occur by both holes and electrons in the same sample of material. When this occurs the current carrier which is in the majority is called the *majority carrier*, the other being called the *minority carrier*.

The simple addition of p- and n-type dopants in equal quantities will not result in an equal part of the conduction being shared by the holes and electrons. Compensation is said to occur, electrons from the donor states filling the vacancies in the acceptor states. This mechanism only occurs efficiently at low levels of doping.

Measuring Semiconductor Properties

When semiconducting substances are manufactured it is necessary to know certain of their physical properties. Such things as resistivity, type of doping (that is whether the crystal is p- or n-type) and the band gap of the intrinsic material need to be measured.

The resistivity of a sample of a semiconductor is measured by making use of Ohm's law. Two probes, P1 and P2 in Fig. 5, from a source of

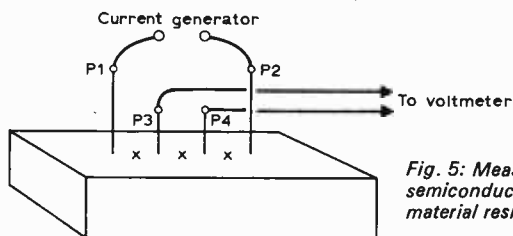


Fig. 5: Measuring semiconductor material resistivity.

current are placed on the surface of the sample. Two further probes, P3 and P4, are placed on the surface of the sample and coupled to a valve voltmeter. The resistivity of the sample can be shown to be proportional to the ratio of the measured voltage and current. This method overcomes the difficulties encountered because of contact potentials.

Hall Effect

The Hall effect is very important in measurements on semiconductors and will be briefly described. As is well known a wire carrying a current is deflected when in a magnetic field. This effect is used in

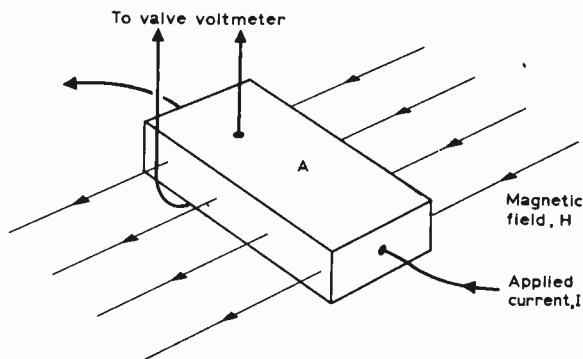


Fig. 6: Demonstration of the Hall effect.

moving-coil, galvanometers. The same effect occurs when electrons flowing in a semiconductor are subjected to a magnetic field. In Fig. 6 the electrons would be deflected upwards towards face A. The electrons which accumulate near to this face set up an electric field which opposes the electron motion since the top surface becomes negative. An equilibrium situation is thus developed, the Hall voltage being measured with the valve voltmeter.

Holes are deflected in the same way. However as they have a positive charge the Hall voltage is of opposite polarity. Thus by measuring the voltage developed it is possible to determine if the conduction is due to holes or electrons.

The Hall effect has many other applications. Among these are the use for measuring magnetic field strengths and as a multiplying device in computers.

Other Properties

As mentioned previously the number of carriers excited to the conduction band varies exponentially with temperature. As the conductivity is proportional to the number of carriers this too varies exponentially. By measuring the temperature dependance of the conductivity of the material the band gap can be calculated.

The degree to which a semiconductor needs to be purified can be judged from the fact that at room temperature intrinsic germanium contains only one electron-hole pair per thousand million atoms. So in order to be able to study the intrinsic behaviour of germanium a purity of one part in 10^9 is required.

In silicon with the wider band gap of 1.1eV a purity of one part in 10^{12} is required. This refinement is not possible and other techniques are required to obtain intrinsic behaviour. The methods used in the purification of semiconducting material will be discussed in Part 2.

TO BE CONTINUED


CORRIGENDA

January issue—Simple Capacitance Bridge

In the multivibrator circuit certain component values were inadvertently transposed: R1 and R4 should be 2.2k Ω and R2 and R3 10k Ω .

SOLDER ON WITH

A N T E X

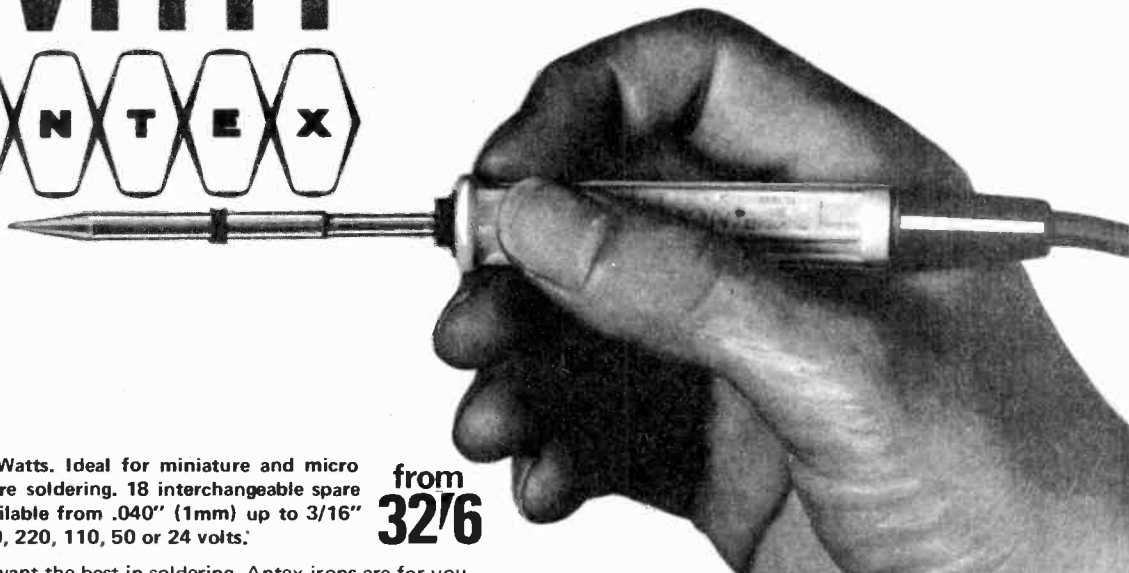

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts.

from **32/6**

If you want the best in soldering, Antex irons are for you. Pin point precision, fingertip control, interchangeable bits that slide over the elements and do not stick, sharp heat at the tip, reliable elements and full availability of spares. World-wide users, both enthusiasts and professionals solder with Antex. It's time you joined them.

Antex soldering irons are stocked by quality electrical dealers, or order direct from Antex by sending Cash. A free colour catalogue will be supplied on request.

A N T E X

PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon
Telephone : Plymouth 67377/8. Telex 45296. Giro No.258 1000



Model CN 240/2
15 watts - 240 volts

Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

31/6

Complete precision soldering kit



This kit—in a rigid plastic "tool-box" — contains everything you need for precision soldering.

- Model CN 15 watts miniature iron, fitted 3/16" bit.
- Interchangeable spare bits 3/32", 1/8", 3/16".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron
- Space for stowage of lead and plug

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

From Electrical and Radio Shops or send cash to Antex.

49/6



G 18 watts. Ideal for miniature work on production lines. Interchangeable spare bits, 3/32", 1/8", 3/16", and 1/4". For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16". For 240, 220, 110 or 24 volts. from 35/6.



ES 25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4". Ideal for high speed production lines. For 240 220, 110, 24 or 12 volts. from 35/6.



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32". Very high temperature iron. Available for 240, 220, 110, 24 or 20 volts. from 42/6. Spare bits and elements for all models and voltages immediately available from stock.

- ☐ Please send me the Antex colour catalogue
☐ Please send me the following irons

Quantity Model Bit Size Volts Price

.....
.....
.....

To: Antex, Mayflower House, Plymouth, Devon

I enclose cheque/P.O./cash value

NAME

ADDRESS

WP 3 Telephone:

VARIABLE VOLTAGE TRANSFORMERS



50
AMPS



1/2 AMP
£3.10.0.



PORTABLE TYPE
£9. 5. 0.

INPUT 230/240v. A.C. 50/60—
OUTPUT VARIABLE 0-290v.

BRAND NEW
Keenest prices in the country. All
Types (and Spares) from 1 to
50 amp. from stock.

SHROUDED TYPE
1 amp, £5.10.0 2-5 amps, £6.15.0
4 amps, £9.0.0. 5 amps, £9.15.0
8 amps, £14.10.0. 10 amps, £18.10.0
12 amps, £21.0.0. 15 amps, £25.0.0
20 amps, £27.0.0. 37-5 amps, £72.0.0
50 amps, £92.0.0.

OPEN TYPE (Panel Mounting)
1/2 amp, £3.10.0. 1 amp, £5.10.0
2 1/2 amps, £6.12.6.

PORTABLE TYPE
1-5 amp. portable fitted metal case,
voltmeter, lamp, switch, etc. £9.5.0.
Similar to above 2-5 amp. £11.7.6.

100 WATT POWER RHEOSTATS (NEW)

AVAILABLE IN THE FOLLOWING VALUES

1 ohm, 10 a.; 5 ohm, 4-7 a.; 10 ohm, 3 a.; 25 ohm,
2 a.; 50 ohm, 1-4 a.; 100 ohm, 1 a.; 250 ohm,
7 a.; 500 ohm, 45 a.; 1,000 ohm, 280 mA;
1,500 ohm, 230 mA; 2,500 ohm, 2 a. Diameter 3 1/2 in. Shaft length
7 1/2 in., dia. 1 1/2 in. All at 27/6 each. P. & P. 1/6.
50 WATT. 1/5/10/25/50/100/250/500/1,000/1,500/2,500/ohm, 21/-.
P. & P. 1/6.
25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 ohm, 14/6.
P. & P. 1/6.

200/250v AC HORSTMAN 20A TIME SWITCH

2 on/off every 24 hours at any pre-set time.
Fitted in metal case. 36 hr. spring reserve.
Used but fully tested. Fraction of maker's
price. £3.19.6 plus 4/6 P. & P.
Available with solar dial, on request.



INSULATED TERMINALS

Available in red, white, yellow, black, blue
and green. New 17/- per doz. 2/- P. & P.

230/250v. A.C. SOLENOID

Heavy duty type, approx. 3 lbs. pull. Price
17/6 plus 2/6 P. & P.

12/24V. D.C. SOLENOID

Approx. 8 oz. push. Price 8/6 plus 1/6 P. & P.

PARVALUX TYPE SD 19 230/250 VOLTS A.C.

REVERSIBLE GEARED MOTOR.
30 r.p.m., 40lb. ins. Position of drive
spindle adjustable to 3 different angles.
Mounted on substantial cast aluminium
base. Ex-equipment. Tested and in first
class running order. A really powerful
motor offered at a fraction of makers'
price. 6 GNS. P. & P. 10/-.

CONSTANT VOLTAGE TRANSFORMER

Input 185-250 v. A.C. Output 230 v. A.C.
Capacity 250 watt. Attractive metal case.
Fitted red signal lamp. Rubberfeet. Weight 17lb.
Price £11.10.0. P. & P. 15/-.

SELENIUM BRIDGE RECTIFIERS

30 volt 3 amp., 11/-, plus 2/6 P. & P.
30 volt 5 amp., 16/-, plus 2/6 P. & P.

L.T. TRANSFORMERS

All primaries 220-240 volts.

Type No.	Sec. Taps	Price	Carr.
1	30, 32, 34, 36 v. at 5 amps.	£4.5.0	6/6
2	30, 40, 50 v. at 5 amps.	£6.5.0	6/6
3	10, 17, 18 v. at 10 amps.	£4.10.0	4/6
4	6, 12 v. at 20 amps.	£5.17.6	6/6
5	17, 18, 20 v. at 20 amps.	£6.12.6	6/6
6	6, 12, 20 v. at 20 amps.	£6.5.0	7/6
7	24 v. at 10 amps.	£4.15.0	5/6
8	4, 6, 24, 32 v. at 12 amps.	£6.10.0	6/6

DOUBLE WOUND VARIABLE L.T. TRANSFORMER

Input 230 v. A.C. OUTPUT CONTINUOUSLY
VARIABLE 0-36 v. A.C.
0-36 v. at 5 amp. £9.12.6. P. & P. 8/6.
0-36 v. at 20 amp. £21.0.0. P. & P. 15/-.

LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cad-
mium Sulphide Photocell, Relay,
Transistor and Circuit, etc., 6-12
volt D.C. op. price 25/- plus 2/6
P. & P. ORP 12 including circuit,
10/6 each, plus 1/- P. & P.

A.C. MAINS MODEL Incorporates Mains
Transformer. Rectifier and special relay with
3, 5 amp mains c/p contacts. Price inc. circuit
47/6 plus 2/6 P. & P.

LIGHT SOURCE AND PHOTO

CELL MOUNTING

Precision engineered
light source with focussible
lens assembly and ventilated
lamp housing, to take MBC bulb. Separate
photo cell mounting assembly for ORP 12
or similar cell. Both units are single hole
fixing. Price per pair £21.5.0. P. & P. 3/6.

MINIATURE UNISELECTOR SWITCH

3 banks of 11 positions plus
homing bank. 40 ohm coil.
24-36 v. D.C. operation.
Tested. 22/6, plus 2/6 P. & P.

COMPACT HEAVY DUTY 6v. D.C. RELAY

2 change over, 30 ohm coil. 7/6 each. P. & P. 1/6.
3 for 22/-, Post paid.

NICKEL CADMIUM BATTERY. Sintered

Cadmium Type 1-2 v. 7AH. Size height 3 1/2 in.,
width 2 1/2 x 1 1/2 in. Weight approx. 13 oz. Ex-
R.A.F. Tested. 12/6. P. & P. 2/6.

A.C. CONTACTOR

2 make + 2 break (or, 2 c/o).
15 amp. contacts. 230/240V.
A.C. operation. Brand new.
Price 22/6 plus 1/6 P. & P.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type
Xenon white light flash tube. Solid state
timing and triggering circuit. 230/250v. A.C.
operation.

ECONOMY KIT. Flash rate 1-36 flash per
second. All components including Uni-
junction, thyristor, tube and circuit. £5/5/0
plus 3/6 P. & P.

INDUSTRIAL KIT. Flash rate 1-80 f.p.s.
Ideally suitable for schools, laboratories,
etc. Incorporates double wound transformer
which isolates both tube and timing circuit
from mains. Stabilized timing circuit and
higher power tube. £8/8/0 plus 6/- P. & P.
4 1/2 in. **POLISHED REFLECTOR.** Ideally
suited for above Strobe kits. Price 8/6 post
paid. Regret NOT sold separately.

RELAYS

Bulk purchase enables us to offer the follow-
ing new **SIEMENS, PLESSEY**, etc. mini-
ature plug in relays complete with base, at
a fraction of maker's price.

Coil	Voltage	Contacts	Price
280	6-12	2 c/o	14/6
280	9-18	4 c/o	15/6
700	12-24	2 c/o	12/6
700	16-24	4 c/o	15/6
700	16-24	4M 2B	12/6
1250	20-40	2 c/o H.D.	12/6
2500	30-50	2 c/o H.D.	12/6
5800	50-70	4 c/o	16/-
9000	40-70	2 c/o	16/-

H.D. — Heavy Duty. POST PAID

'AVO' METER MODEL 7

Supplied fully checked and tested
on all ranges and in excellent
condition. Complete with bat-
teries and leads. Price £13.10.0.
P. & P. 7/6. Avo Leather Car-
rying Case 30/-, Regret not supplied
separately.



TAPE

We offer you fully tensilized polyester/mylar and
P.V.C. tapes of identical quality hi-fi, wide range
recording characteristics as top grade tapes. Quality
control manufacture. They are truly worth a few
more coppers than acetate, substandard, jointed or
cheap imports. TRY ONE AND PROVE IT YOURSELF

Standard Play		Long Play	
8in. 150ft.	2/3	8in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
8in. 600ft.	7/6	8in. 900ft.	10/6
6 1/2in. 900ft.	10/6	6 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
8in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	8in. 1,800ft.	25/-
6 1/2in. 1,200ft.	15/-	6 1/2in. 2,400ft.	34/-
7in. 1,800ft.	21/6	7in. 3,600ft.	44/-
8in. 2,400ft.	27/6	8in. 3,600ft.	54/-

Postages 1/- reel.

Post Free less 5% on three reels.

Quantity and Trade enquiries invited.

NOTE: Large tape stocks at all branches.

TUBES

Highest Quality—
Compare Our Prices

Carr. & Ins.	GUARANTEED
12/6	6 Months 12 Months
14in.	£2.10.0 £2.10.0
17in. & 19in.	£3. 5.0 £4. 5.0
21in. & 23in.	£3.15.0 £5.15.0

SATISFACTION GUARANTEED

Most Mullard, Mazda, Concor, Emulon, Emiscope,
Brimar, Ferranti types processed in our own factory.
NOTE: ALL tube orders only to Portsmouth branch
please.

NEW and SPECIAL Lines at the keenest prices

AM/FM STEREO MULTIPLEX RECEIVERS
18 transistors, 9 diodes, 1 variable diode, 2 silicon
Rectifiers. Push-pull Stereo Amplifiers. FM Stereo
Separation 15dB. AM Medium Wave 180-550 Metres.
Power output 10W R.M.S., 230/240V A/C Mains.
Beautiful wooden plinth case—approximately
15" (w) x 8" (h) x 8" (d). Controls: Function Switch,
Balance, Base/Treble Control, Volume, Tuning, Fine
tuning. Special purchase enables us to offer these superb
machines of famous make at a ridiculously low price.
Unrepeatable offer at a fraction of list price... only
26 GNS. POST FREE.

SHARP RD504 Mains Battery Tape Recorder, List 36 gns	28 gns
HITACHI Marine D/F Receivers SW/MAR/MW/LW	27 gns
GARRARD 1025 Changers with Stereo Cartridge	£8 10s
JASON 18in. Discast full range twin cone Speakers	£4 10s
AJAX Mains/Battery, AM/FM larger Radio	12 gns
WELESMEERE AM/FM High Sensitivity Black Leather	7 gns
HITACHI WH837E All-Wave, full size. Excellent Short Wave	13 gns
HI-FI By Leak, Wharfedale, Goodmans, WB, Dulci, Arona, Teleton, etc., etc.	

All items previously
advertised
available. Huge Hi-
Fi and Component
stocks at all branches.
Please call
and view without
obligation.



RETAIL BRANCHES:

LONDON. 10 Tottenham Court Rd. (MUS 2639)
PORTSMOUTH. 350-352 Fratton Road
(Tel. 22034)
SOUTHAMPTON. 72 East Street (Tel. 25851)
BRIGHTON. 5 Queen's Road (Tel. 23975)

MAIL ORDER WAREHOUSE:


Devonian Court, Park Crescent Place, Brighton.
(Tel. 680722)

BARGAIN PARCELS

Including variable condensers, i.f. coils, loudspeaker
plug/sockets, knobs, pots, condensers, resistors, nuts,
bolts, cabinet fittings, switches, transformer chokes,
rectifier, transistors at a small fraction of list value
Due to heavy demand we now pack them in several
sizes—be amazed—try one now.
8 lbs. (post 8/-) 9/-
7 lbs. (post 5/-) 17/6
14 lbs. (post 9/-) 29/-

SERVICE TRADING CO

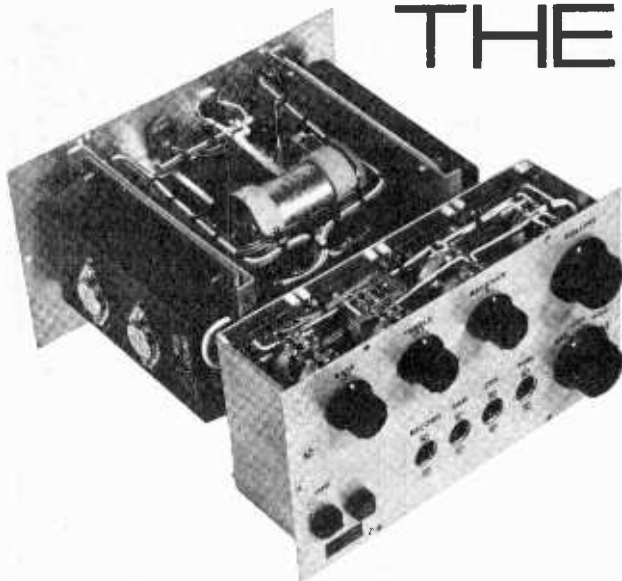All Mail Orders—Also Callers—Ample Parking Space
57 BRIDGMAN ROAD, LONDON, W.4 Phone 995 1560
SHOWROOM NOW OPEN CLOSED SATURDAY
Personal callers only
9 LITTLE NEWPORT STREET
LONDON, WC.2. Tel. GER 0576



THE P.W. DOUBLE-12 HI-FI AMPLIFIER

HAL MOORSHEAD

PART 2

Last month details were given on the construction of the preamplifier and tone control panels. This month we are dealing with the completion of the preamplifier as a complete unit and the metalwork for the whole unit.

HAVING built up the preamplifier and tone control panels, these have now to be mounted together with the input sockets and controls into a complete unit. For those wishing to use the preamplifier with an existing power amplifier or one of another design this unit will be all that is required apart from a supply of 20V; this can generally be taken from the main amplifier power supply.

As the photographs of the unit show, all the controls are mounted on the front panel enabling the preamplifier to be permanently fitted into a cabinet. The four panels described last month are fitted vertically behind this front panel, bolted to another panel forming the back of the unit. They are arranged so that the tags on the boards are in close proximity to the variable pots controlling the treble, bass, volume and balance. The other ends of the panels have the contact pins for the selector switch inputs and the power supply.

The matching resistors for the input circuit are mounted on the actual input plugs. An additional plug is incorporated with the three inputs; this is a low level output from the preamplifier unit for feeding into a tape recorder or external amplifier, the output to this plug is not controlled by the volume control.


The P.W. Double-12 is not provided with a mono/stereo switch, a feature often provided on stereo amplifiers. This facility is not required as any

mono input, such as an a.m. radio tuner or standard record player input will be fed to the preamplifier by means of a DIN plug. Where the input is mono all that is necessary is to fit a jumper wire inside the plug paralleling the inputs. The actual plugs chosen were the Philips 5-pin or DIN type, these having become almost universal for this kind of equipment.

In order to bring all the active controls to the front panel, the on/off switch and the indicator neon are also mounted on the front.

Layout of the preamplifier unit

Figure 1 shows a block diagram of the connections for the preamplifier as this is fairly involved and mistakes can easily be made. After having made up

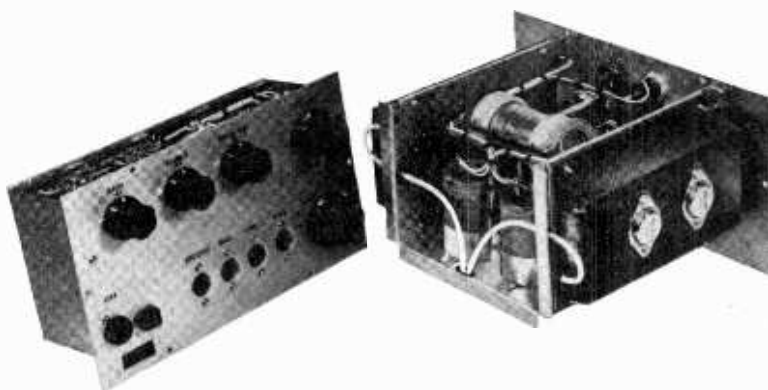

The two sections of the completed amplifier before being bolted together.

the metal work for this unit mount the necessary items on it, that is the on/off switch, the input and output sockets, the selector switch and the variable pots. Potentiometers are sold with spindles of varying lengths and it is advisable to cut these to the required length before mounting them as cutting spindles *in situ* can damage the equipment. Clasp the spindle firmly in a vice and cut with a sharp

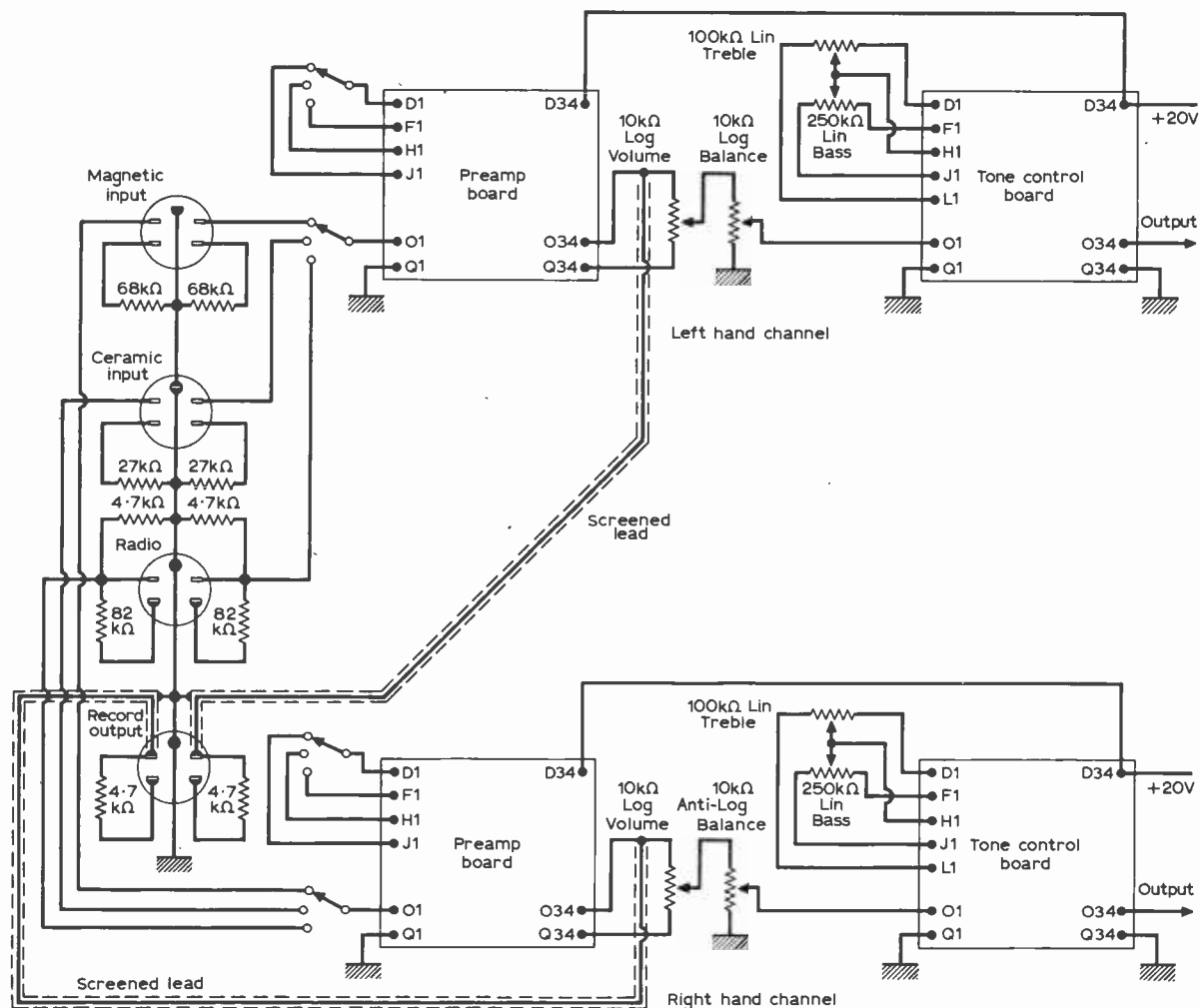


Fig. 1: Schematic diagram showing the interconnection of the panels. The DIN sockets are viewed from the rear and note that the balance control should be wired so that the chassis connection for one of the sections is fed from the left hand tag (viewed from the front) and in the other case from the right hand tag. It does not matter which section of the balance control is used for which channel.


★ components list

Balance control—10kΩ double gang, one section log., the other anti-log.


Two 4.7kΩ, $\frac{1}{4}$ watt miniature resistors.

Four DIN input sockets; knobs; Mains switch toggle; indicator neon; Eight way tag strip (if used as a separate unit); 6BA nuts and bolts; screened lead.

Metalwork as shown.

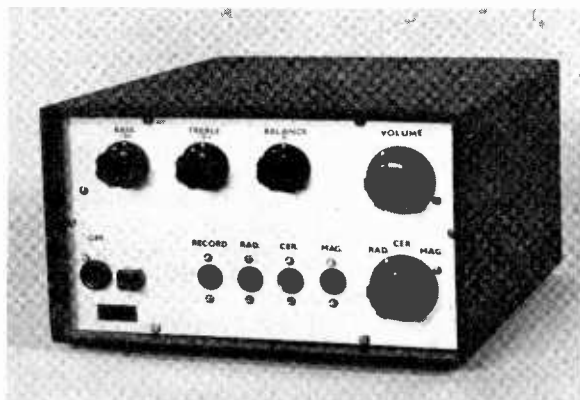

Front view of the completed amplifier.

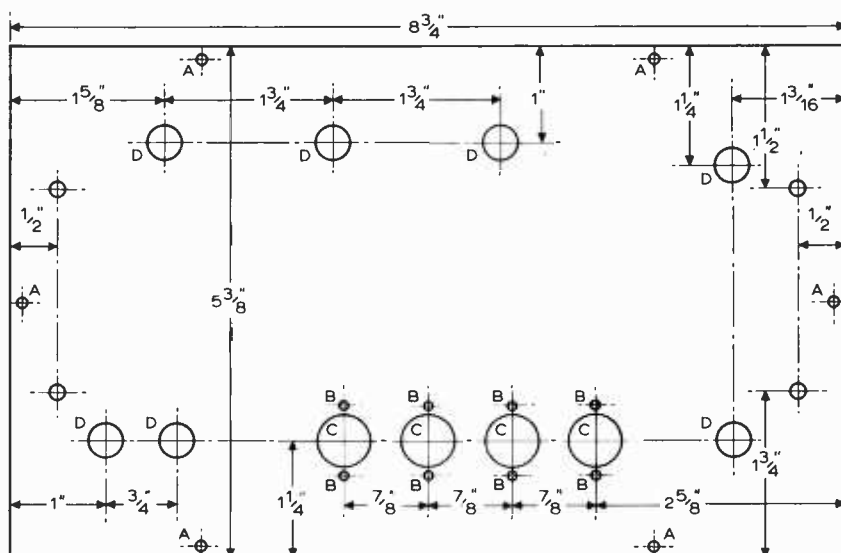

Holes A..... $\frac{1}{8}$ " dia. suitably located for fixing panel to cabinet. C..... $\frac{9}{16}$ " dia.
B.....6BA clearance located to mount DIN sockets. D..... $\frac{3}{8}$ " dia.

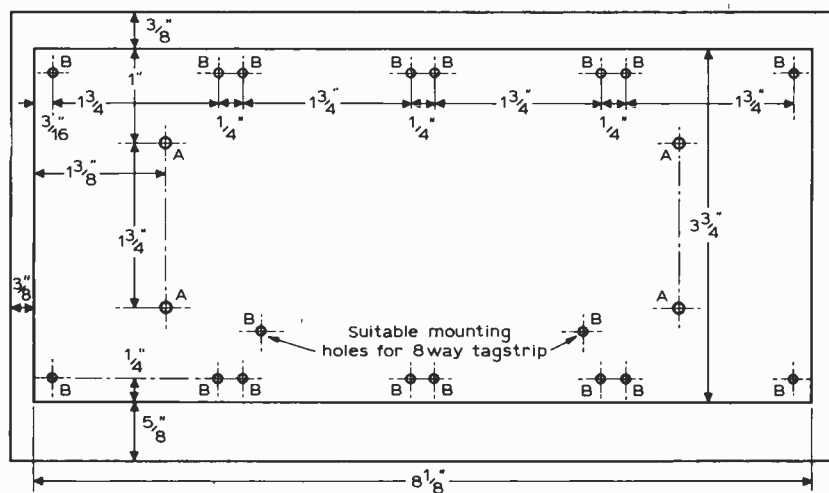
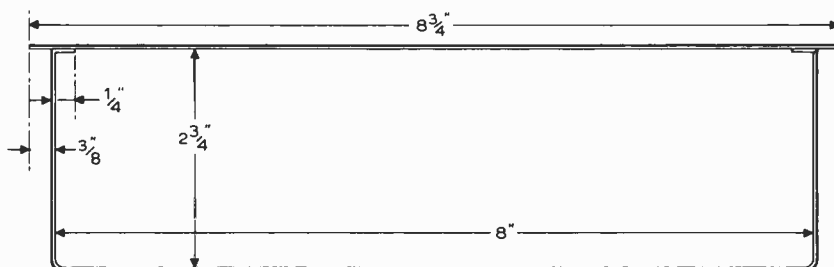


Fig. 2: The metalwork details for the preamplifier section.

hacksaw, finally filing off the rough edges. The actual length of spindle will depend upon the knobs chosen, but about $\frac{3}{4}$ in. should be right. Arrange the pots in such a way that the contacts are facing upwards.

A small solder tag should be fitted to one of the bolts holding the DIN plugs and a bus-bar threaded

through the pins as shown. The attenuating resistors are mounted on the DIN plugs, their chassis connections being taken to the bus-bar.

The feeds from the input sockets are taken to the selector switch as shown in the diagram. In turn the output from the switch is fed to the preamplifier panels which are mounted behind the selector switch.

It is advisable firstly to do the necessary wiring between those points on the front panel and to also solder the wires which will later lead to the boards, this will save at least fixing both ends of the inter-connecting wires when the unit is assembled.

Mounting the boards


The preamplifier and tone control boards should next be mounted on the back panel. Each of these are held by means of four 6BA screws half an inch long, quarter-inch tubular spacers support the panels themselves and prevent the connecting pins from touching the chassis.

For those wishing to use the preamplifier by itself it is suggested that an eight way tag strip is mounted on the back of the rear panel to which the wires of the mains, supply voltage and outputs may be taken; if the preamplifier is to be used with the main amplifiers and power supply suggested this will not be required as the leads will connect directly to points on the other chassis. Screened leads are only necessary for the final outputs from the tone control panels and on the feeds from the top of the volume control to the low level output. In wiring the unit it is strongly recommended

that wire of several different colours is used; this will greatly help in reducing mistakes.


The secret of wiring such a unit is to work logically, starting at the input and working through to the output and once the job is done leave it for a couple of hours and start with a fresh mind and follow through the sequence again.

Fig. 3: The metalwork for the centre section which should be bent as shown in the photograph on page 35. This section will hold the power amplifiers and power supply in the completed unit.

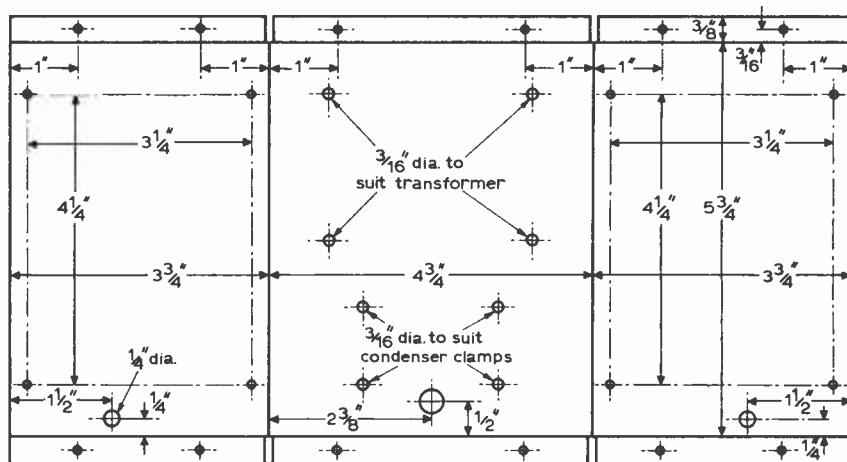


All unmarked holes $\frac{1}{8}$ dia.

Fig. 4: Details of the drilling required for the back panel. The loudspeaker sockets fit into the $\frac{5}{8}$ in. diameter holes. The power amplifier fuses fit into the two centre $\frac{3}{8}$ in. holes while the top two $\frac{3}{8}$ in. holes are used for the mains input lead and the mains fuse.

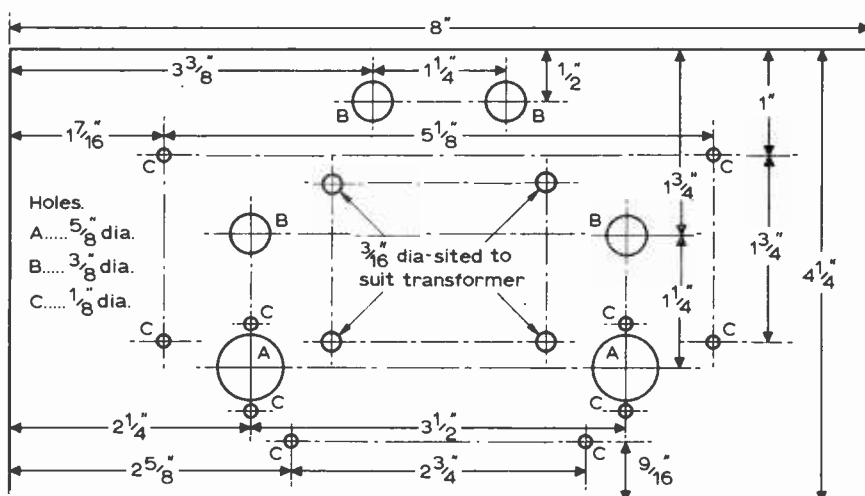

The metalwork

As mentioned before, the design of the metalwork has been kept as simple as possible. Aluminium sheet, 16 s.w.g., should be used which is available from component suppliers, it can easily be cut using metal shears. All holes should be carefully marked and drilled, the resulting scurf being removed by a countersink bit. Chassis bending can easily be done in a vice although the aluminium should be protected from the jaws by sandwiching between card-board.

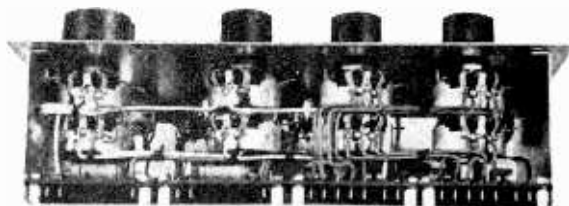

Top view of the completed preamplifier section.


PRACTICAL WIRELESS have made arrangements with H. L. Smith and Co. Ltd. of 287/289 Edgware Road, London W.2, to supply the basic metalwork, as specified complete with the six holes of over $\frac{3}{8}$ in. diameter already punched for 26/2d plus 4s 6d p. & p. All that is necessary is to drill the smaller holes detailed in the drawings.

Next month, the final article will deal with the construction of the main amplifiers, the power supply and a suggested design for a cabinet.

HERE'S YOUR LINE-UP FOR NEXT MONTH'S PRACTICAL WIRELESS

A COMPREHENSIVE AUDIO MIXER

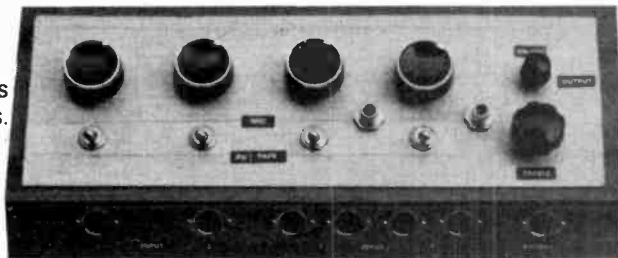Most small audio mixers have very limited applications and the audio enthusiast has to resort to hookups of attenuators, transformers and other devices to match sources to inputs. The P.W. mixer to be described next month provides comprehensive facilities so that almost anything can be plugged into it without alteration. Facilities are also provided for monitoring the composite signal.



TRANSISTOR POWER OUTPUT STAGES


Transistor amplifiers look simple enough, but once you deviate from a published circuit design not only can performance be disappointing but components can be easily damaged. This article explains the peculiarities of various output circuits.

P.W. DOUBLE-12

The final article in this series deals with the building of the power amplifiers and power supply. Together with the preamplifier (for which you will find completion details in this issue), the unit described next month will build up into a complete hi-fi system *at a considerable saving over ready built units.*

A SLIMLINE SUPERHET

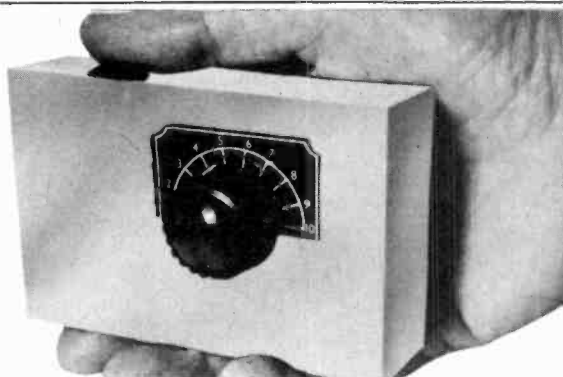This simple medium wave superhet receiver using just four transistors and two i.f. transformers is designed to feed a personal earpiece or headphones. Measuring only $4\frac{1}{2} \times 3 \times 1$ in., it is easy to build and full wiring instructions are given.



PRACTICAL WIRELESS

3/- June issue
on sale Friday May 9

ORDER YOUR COPY NOW!

A NEW SERIES - BY I. J. KAMPEL

THIS is the first in a short series of articles dealing with the theory behind the operation of pulse circuits. All the familiar, and some of the not-so-familiar circuits are discussed in a detailed analysis. The descriptions of how these circuit elements function should be of great assistance to the beginner with a basic knowledge of semiconductors as practical illustrations of how semiconductors work together in switching circuits. These basic building blocks are frequently taken for granted, perhaps not considered worthy of detailed appraisal, but an intimate knowledge of how such circuits operate must lead to improved design techniques in even modest pulse circuitry. Since saturation switching plays such an important role in pulse circuitry, this subject will be dealt with before more practical pulse circuits are discussed.

voltage approaches the line voltage since only minimal voltage is developed across the load by this small leakage current.

To take two examples, a germanium transistor having a leakage current of $5\mu\text{A}$ at a line voltage of 10V might have an effective saturation resistance of only 4Ω . The impedance in the ON state is thus 4Ω , and in the OFF state it is determined by the leakage current and the line voltage, since $V_{CE\text{ sat}}$ may be considered negligible compared with V_{CC} , the line voltage. The OFF state impedance is $10/(5 \times 10^{-6}) = 2\text{M}\Omega$. Therefore,

$$\text{off-to-on ratio} = \frac{10}{4 \times 5 \times 10^{-6}} = 0.5 \times 10^6$$

If we consider a typical silicon transistor, the saturation resistance will be higher, but the leakage current will be lower, and a similar ratio results. Taking a silicon

pulse circuits in oper

The ultimate aim in switching circuits is to obtain a means of effectively switching between the two states of zero impedance and infinite impedance, upon the application of electrical stimuli. The electromechanical switch, the relay, gives the closest approximation to this as is possible, since it switches between contact resistance, perhaps milliohms, to a true open-circuit. The relay thus has an infinite off-to-on impedance ratio.

Whilst a useful off-to-on impedance ratio is obtainable with a relay, there are many applications where a relay is quite impracticable, due to its severe limitations. As an electromechanical unit with moving parts it is subject to wear and has a limited lifetime. The mechanical parts limit its speed of operation, the unit is bulky, and it is also expensive. The transistor on the other hand provides an inexpensive form of switching which is silent, fast, reliable, with almost infinite lifetime, and it is also very small. It is true that a transistor cannot have an infinite off-to-on impedance ratio, but more than adequate ratios are obtainable.

When a transistor is overdriven in terms of base current, and made to bottom, the collector voltage drops to $V_{CE\text{ sat}}$, usually of the order of one or two hundred millivolts for a typical silicon transistor. The normal emitter-base voltage for a silicon transistor is six to seven hundred millivolts, indicating that when a transistor is saturated the collector voltage is *below* the base voltage, i.e. the transistor is driven into a state where the normally reverse-biased collector-base junction is now forward-biased.

When a transistor is cut off, only the leakage current I_{CBO} flows through the collector load, and the collector

transistor with a leakage current of 100nA at $V_{CC} = 10\text{V}$, and a saturation resistance of 200Ω ,

$$\text{off-to-on ratio} = \frac{10}{0.1 \times 10^{-6} \times 200} = 0.5 \times 10^6$$

Similar ratios are thus possible with silicon and germanium transistors. Power transistors have lower saturation resistances but higher leakage currents.

From the above considerations it is seen that transistors make useful switches, and switching speeds may be over a thousand times better than with high speed relays. The mode of switching will normally be common emitter, for in the common base mode, a current almost as large as the current to be controlled in the collector must be applied to switch. In common emitter the necessary switching current is reduced by the factor of the transistor's current gain, h_{FE} , and a small current in the base can control a much larger current in the emitter-collector circuit.

Figure 1.1 shows the output characteristics of a typical silicon transistor, and a load line is drawn for a line voltage of 20V , not exceeding the maximum power rating, while another load line passes through the region where the power rating is exceeded. We shall consider the former initially, R_{L1} . Point A represents the upper limit for the transistor to be in the OFF state, where $I_B = 0$. If a small negative bias is applied to the base of an n-p-n transistor (or positive bias for a p-n-p transistor), this will cause a negative current $I_B = I_{C0}$ to flow, and the transistor is switched into a more definite OFF state.

Point B on load line R_{L1} represents a point in the ON state where the transistor is non-saturated since the

effective collector-emitter voltage is seen to be 6V, and in fact the transistor in this state, with a base current drive of $250\mu\text{A}$, dissipates a power of $50 \times 10^{-3} \times 6 = 300\text{mW}$. Point C on the load line represents the transistor in saturation, and it will be seen that here the power dissipation is very small since the collector-emitter voltage is very small. With this particular load resistance, any base current in excess of about $400\mu\text{A}$ will drive the transistor hard into saturation.

The maximum power dissipation curve plotted on the diagram indicates the area on the graph which should not be exceeded by the load line in normal operation. In the case of a fast switching operation, there are situations where it is quite acceptable to exceed this power curve, however. First of all consider point E on this new load line, R_{L2} . This point represents the transistor operating with a base current drive of $350\mu\text{A}$ at a collector current of nearly 70mA , i.e. the power dissipation is in excess of the maximum rating throughout the period of the ON state. Point E must never be used therefore. Point F, however, is slightly different.

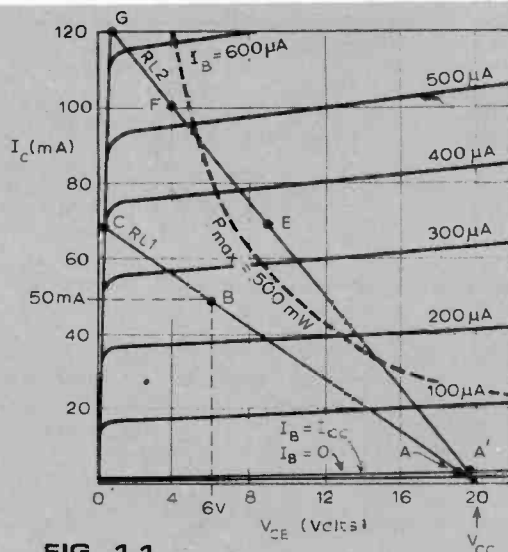


FIG. 1.1



ation part one

saturation switching

Although the load line intersects the limiting power curve, the operating point is within the power limit. It is possible to operate a switching transistor in this mode, but careful design is necessary, since the switching time is critical—the transistor must not spend any great time in the region of the load line where the power rating curve is exceeded. Where switching from point A to point F occurs rapidly, this is acceptable.

Point G indicates another saturated point for the transistor on R_{L2} , and provided that switching occurs rapidly, although the load line exceeds the maximum power rating, the transistor should not dissipate excessive power, since most power is dissipated during the switching operation. A base current greater than about $800\mu\text{A}$ would be required to switch the example transistor into definite saturation with load R_{L2} . In the design of such circuits, the duty cycle of the pulse must be carefully considered.

Switching Speed

The switching speed of a transistor is considered when an ideal square wave, or step function is applied to the base, in Figure 1.2. The voltage applied to the base is shown in (a). For a transistor to repeat this step function precisely it would have to have an infinite bandwidth, since a perfect step function with a vertically rising edge is made up from the harmonics of an infinite number of frequencies. To switch the transistor on fast, the base current is overdriven, that is to say, referring to the saturated position of point C in Figure 1.1, instead of

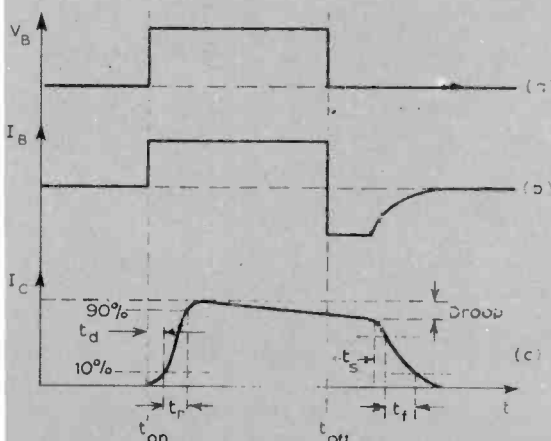


FIG. 1.2

applying minimum base current for saturation, namely $350\mu\text{A}$, $500\mu\text{A}$ or more are driven into the base. The base current resulting from a given emitter-base voltage will vary with transistor spreads, and to take up this spread it is usual to use a constant current source to switch the base current. The transistor cannot have infinite bandwidth, and hence follow the step function exactly since it takes a finite time for the transit of carriers, and minority carriers have to be swept out of the base region before switch-off is complete.

Figure 1.2 shows how a transistor will respond to a step function input. As the base voltage rises at t_{on} so the base current immediately responds, rising to the programmed constant current level. Since carriers must travel across the base region before a collector current can flow, a turn-on delay results, and collector current does not immediately respond. Electrons travelling to the collector all have their own individual paths through the lattice structure, some short paths, some long, some undergoing many collisions, others few. There is thus a delay in the rise time before anything like a constant and maximum current can flow. (The rise time is defined as the time taken for the current to rise from 10% to 90% of its maximum value). The delay time is measured from the beginning of the input pulse to the 10% point of rise, and is denoted t_d in the figure.

Since the transistor is driven into saturation, the collector now will emit electrons into the base region, just as the emitter does normally. This has the effect of flooding the base region with minority carriers, and before the transistor can be turned off, all these excess carriers, the *stored base charge*, have to be removed. When the step function reaches its falling edge, for a finite delay time, the *storage time*, the base region rich in minority carriers supports the original collector current and there is no instantaneous response to the switch-off at the base. Again the time interval over which the last carriers leave the collector is drawn out as they follow dissimilar paths, and the *fall time* results (90 to 10%). The stored charge due to the minority carriers in the base region causes the base to go negative at the switch-off point until the minority carrier storage has ceased. This is shown in (b). By driving a reverse current into the emitter-base, in fact overdriving in the reverse direction, the switch-off time may be improved, just as overdriving speeded up the switch-on time.

Overdriving to turn a transistor sharply on may, in certain circumstances, dissipate too much power in the

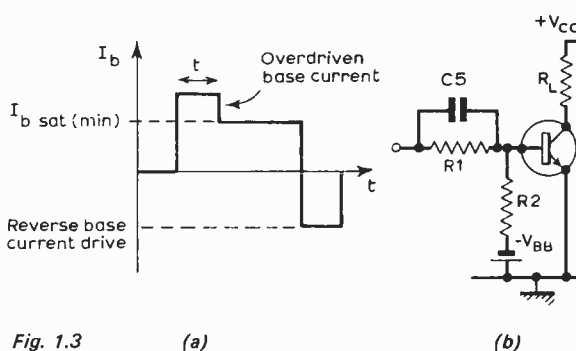


Fig. 1.3

transistor if excessive overdrive is employed for too long a period. To get over this problem and yet still maintain a high overdrive current, the ideal input to the emitter-base is shown in Figure 1.3a. The forward current is seen to be a step function, driving initially up to the overdrive value, remaining at this level until the transistor is in the ON state, then dropping to $I_{b\text{sat}}(\text{min})$ to maintain the saturation, but at reduced power dissipation.

Such a waveform can be approached by the use of a speed-up capacitor, and in Figure 1.3b a speed-up capacitor C_s is chosen such that the current through it takes up the difference between the required overdrive current, and the minimum base current for saturation, $I_{b\text{sat}}(\text{min})$. The battery V_{bb} in Figure 1.3b holds the transistor cut off when no pulse is supplied at the input, thus ensuring that only I_{CBO} flows through R_L and that switching is substantially between V_{ce} and $V_{ce\text{sat}}$ at the collector.

If the input voltage is sufficiently large in order that the voltage dropped across $R1$ is large compared to V_{BE} , substantially constant current will be driven into the emitter-base circuit.

In Part Two of this series, the multivibrator family will be considered. The precise operation of various forms of multivibrator will be explained, and a method of speeding up the inherently slow rising edge will be discussed.

TO BE CONTINUED

PRACTICAL TELEVISION—MAY

★ VIDEO AMPLIFIERS

Video amplifiers are required to operate over a frequency range from d.c. to 6MHz: details are given of the problems involved in obtaining this wide bandwidth and the circuit techniques used.

★ PROGRAMME PRODUCTION

An account of the processes involved from the acceptance of an idea through to the final broadcast stage.

★ FOCUS ON AGC

Many new a.g.c. techniques have been introduced with the advent of hybrid and transistorised models: these are fully described and illustrated.

★ UHF AERIALS

The special problems of aerials for use at u.h.f. are outlined and details given of practical systems.

PLUS CHECKING AUDIO STAGES, POWER SUPPLY AND CONSTRUCTIONAL DETAILS OF THE VIDEOSCOPE, AND ALL THE REGULAR FEATURES

ON SALE APRIL 18th

practically wireless

commentary by HENRY

MY mate Bob is a practical man. He says. Not for him the involved calculations on a bench-side jotting pad to prove the profundities of some designer's quirk. He does not waste his time with deep diagnosis, conjuring the whys and wherefores of a burned-out resistor.

Bob is a practical man: he belongs to the "suck-it-and-see" brigade. And, like many another hardworking technician, he achieves a very fair proportion of successes.

Before I get a heap of textbooks heaved at my head, let me state that this measure of success is not merely because the empirical method is superior to logical progression in fault-finding. Nor that I believe experiment to be a good idea when equipment breaks down for no obvious reason. In these days of direct-coupled transistor amplifiers, where a faulty component sets up a domino-effect chain of disasters, guesswork can have catastrophic results. One does not even connect the test-meter without offering up a silent invocation.

In his first few months with us, Bob made some overeager bloomers that looked too much

like guesswork. At odd moments we could see him racking his brains for possible solutions, and it was as well that he did not have too much pride to ask for guidance. Only in that way can experience be built up—and too often a failure in the workshop happens because some engineer has become "bogged down" in a mess of dead-ends.

Of course, here and there we come across the old hand whose experience, like moss on a boulder, has so encrusted the basic man that he is incapable of taking in anything new. This is the type of chap who derides transistors because—he avers—they are noisy, untrustworthy, too vulnerable, cannot be replaced without major surgery, and are as likely to be swept under the bench with the rubbish as put back neatly into store. He says: "You know where you are with valves." What he really means is that he simply cannot grasp the concept of holes and barriers.

There is a danger nowadays that the new men will take the opposite view, forgetting that there are still many fields where valved equipment can do a better job. Worse still, the characteristics of the later devices are being taken for granted. "Suck-it-and-see" is a dangerous philosophy when a complicated piece of electronic gear is on the bench.

And as technology scoots along breathlessly we can rely much less often on experience. Almost daily, the engineer is confronted (confounded?) with a circuit that incorporates some new technique.

Sceptics may think Henry unduly alarmist. Some of my colleagues in the Society of Service Managers have already seen the red light. They are pressing ever more vehemently for increased industrial training. We cannot,



An élite of engineers

they say, allow the technician to gravitate into a dead-end groove. The more science becomes the province of the specialist, the more is there a need for the chap in the workshop to learn his groundwork thoroughly. And be better supervised.

Readers in the radio repair trade will have seen the change that colour TV has brought. An élite of engineers is growing up, trained by the manufacturer, flushed with the novelty of it all, keen as can be. Despite all the foolproofing that a designer can dream up, there will always be room for the technical man with a diagnostic flair and a good solid grounding in the fundamentals. There is less time today to gather that moss of experience.

Despite all, there will always be room for blokes like Bob, who have a keen nose for the possible fault and a good memory for symptoms. We could do with a few more in the editorial office, answering readers' queries. Although I sometimes feel an inspired omniscience would be more useful, with letters that begin: "My receiver went dead last Saturday. What do you think can be wrong?"



A heap of textbooks at my head.

P.W. GUIDE TO COMPONENTS

PART 5

M. K. TITMAN, B.Sc. (Eng)

TRANSISTORS are used extensively as amplifying components in electronic circuits and have almost displaced thermionic valves in this role. Only in the specialist fields of high frequency power circuits and high voltage circuits are transistors unable to meet the circuit requirements. Nevertheless it is entirely possible that solid state circuits will in time replace the valve even in these fields.

Transistors are three terminal amplifying devices of semiconductor material. Semiconductor material with the required electrical characteristics is obtained by adding impurities to pure silicon or germanium crystal structures. By suitable choice of the chemical element used as the impurity an excess of positive charges or negative charges is established in the material. This results in the two basic forms known as p-type or n-type material respectively (p-type with an excess of positive charges—holes, and n-type with an excess of negative charges—electrons).

When a single junction is formed between a p-type and an n-type semiconductor the resulting structure is known as a p-n junction, and has the properties of a diode. A two junction structure as shown in Fig. 1 has amplifying properties—providing the centre or base region is very thin. Two basic forms of amplifier are possible, the p-n-p transistor or n-p-n transistor. The structure and circuit symbols for each type are shown in Figs. 1 and 2 respectively.


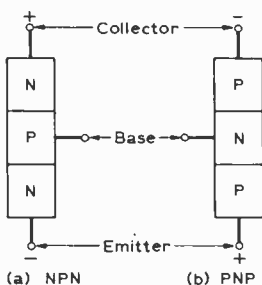


Fig. 1 (left): Basic transistor construction

Fig. 2 (below): Standard transistor symbols.

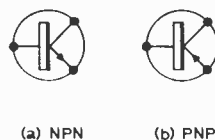

In order to understand the reason for the methods used in transistor construction let us examine further the mechanism by which amplification is achieved. Figure 3 illustrates the diode properties of each junction individually and clearly the transistor appears as a back-to-back diode combination as shown in Fig. 3(c). When a voltage is connected between the collector and emitter no conduction can take place. However if the base region is very thin then conduction across the base-emitter junction obtained by biasing the base with respect to the emitter results in current flow between collector and emitter. This can be regarded in the n-p-n configuration shown as due to electrons flowing into the base region and thereby establishing a conduction path

between collector and emitter. In order to make the base-emitter junction conduct it must be forward biased and this is achieved by applying bias to overcome the natural junction barrier potential of 0.2-0.3V for germanium transistors and 0.6-0.75V for silicon.

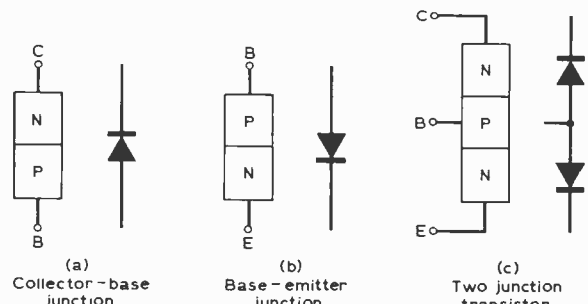


Fig. 3: N-P-N transistor junction characteristics.

Once this barrier voltage has been overcome a small increase in the voltage between the base and emitter will drastically increase the collector-emitter current flow. The relationship between base-emitter voltage and collector current for a germanium transistor is shown in Fig. 4 and it can be seen that a change of 25mV results in an emitter current change of 4mA giving an effective gm of 160mA/V. Therefore a very small base-emitter voltage change—once the barrier voltage is overcome—gives a change in collector current which when passing through a suitable load resistor results in a large voltage change. Hence the transistor has voltage amplification properties due to its capacity for current or power gain.

The mechanism of operation depends on current gain because current flow into the base produces current flow from collector to emitter and this is the reason for


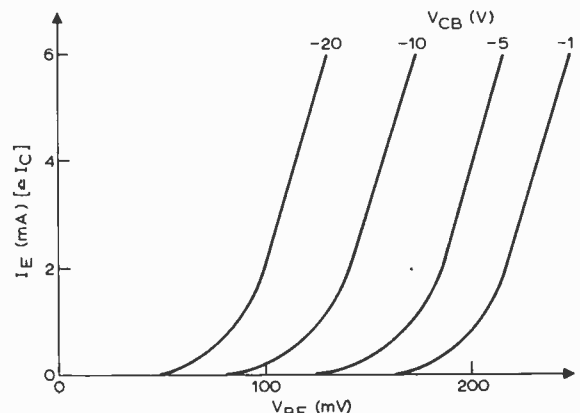


Fig. 4: Base-emitter voltage/emitter current characteristics.

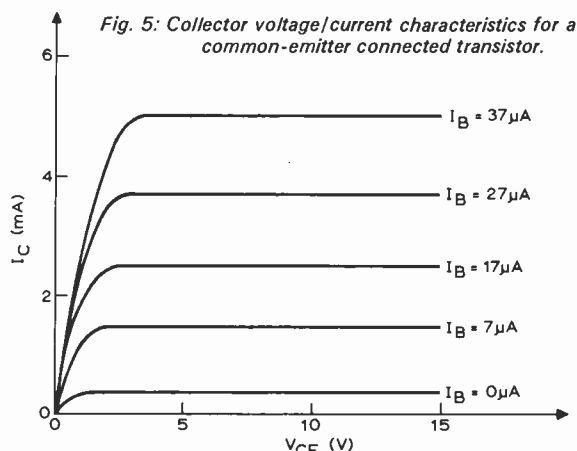

the designation of transistors as current-operated devices. However as we have seen from Fig. 4 the transistor can equally be regarded as voltage-operated.

The relationship between collector current and collector-emitter voltage is shown in Fig. 5 and it will be noticed that the general shape of the curves of constant base current resembles very closely those of pentode valve characteristics. This feature of base current operation further explains the term "current-operated" for transistors though this expression has tended to produce a psychological barrier for those more familiar with valve operation. In fact amplification is achieved in the same way and the transistor and valve amplifiers shown in Fig. 6 are analogous.

A small positive increase at the base (in the case of an n-p-n transistor) or grid results in an increase in collector or anode current and produces a change in collector or anode voltage. Polarities, phasing and operation of the amplifiers shown is identical—it is only the voltage levels and impedances that differ.

As transistor characteristics are basically given in terms of current it is usual for the current gain, which is change in collector current for change in base current, to be quoted. The current gain approximates to the values given for h_{fe} , α' or β in transistor characteristics. The gm can however be determined and is defined as the change in base-emitter voltage for a given change in collector current. This corresponds to the slope of the characteristic shown in Fig. 4.

Having briefly covered the method of operation of transistors of the basic p-n-p or n-p-n two-junction structure, let us now examine how this structure is manufactured in practice and the advantages and limitations of different forms of construction.

Alloy Junction Transistors

Transistors first became commercially available with the alloy junction form of construction and well-known examples of this type are the OC70 series. Initially germanium was used as the base material as its melting point of 950°C is lower than silicon (1,400°C) and it is therefore easier to work with.

The transistors from 1950 were germanium p-n-p types made from n-type material formed by purifying germanium to an impurity concentration of 1 part in 10^8 and then adding arsenic or antimony to give the n-type characteristic. The single crystal material was cut and diced into chips 0.1in. square and 0.005in. thick. The two junctions were then formed by alloying beads of p-type impurity—normally indium—to both sides of the chip as shown in Fig. 7.

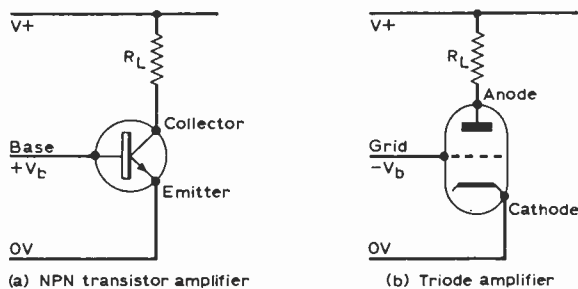


Fig. 6: Comparison of simple transistor and valve amplifiers.

Alloying was achieved by heating the indium pellets to their melting point at which stage a solid bond was obtained and some of the indium diffused into the n-type slice to give p-type material. The depth of penetration was determined by the time and temperature and thus the base thickness was controlled.

The transistor characteristics of all transistors are determined by base thickness, material, impurity concentrations, resistivity etc., and by using the alloying technique fairly wide tolerances occurred. As a result useful transistors of like characteristics are obtained by individual selection within acceptable limits. Thus each production line produces a range of transistors such as the OC70, OC71 and OC72, and the yield of each type differs. The cost of each type of transistor therefore is largely determined by the numbers required and the production yield.

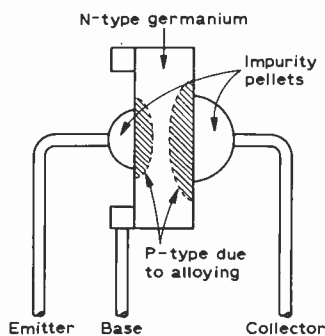


Fig. 7: Alloy junction transistor construction.

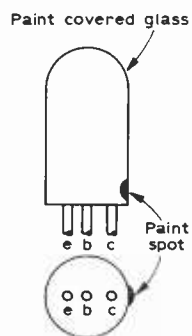


Fig. 8: Glass encapsulation.

Silicon alloy junction transistors, which are still produced in fairly large quantities, utilise aluminium as the p-type impurity to alloy with the silicon slice. N-P-N transistors were more difficult to produce and like silicon more expensive than the p-n-p germanium transistor. With n-p-n transistors this was due to the use of arsenic or antimony as the n-type impurity which had to be alloyed to lead to make the pellets.


The finished transistor slices of the early transistors were encapsulated in glass, as shown in Fig. 8, after soldering the lead-out wires to the centre slice and the two pellets. The glass formed an efficient hermetic seal and was coated with paint to prevent light penetration to the junction. The device was marked with its designation and the collector lead indicated by a coloured paint spot.

Glass encapsulations however are not efficient for heat dissipation, although grease is inserted to give additional conduction between the chip and the glass, and later devices used metal containers of the same basic shape.

—continued on page 54

CALIBRATION OSCILLATOR

R. F. GRAHAM

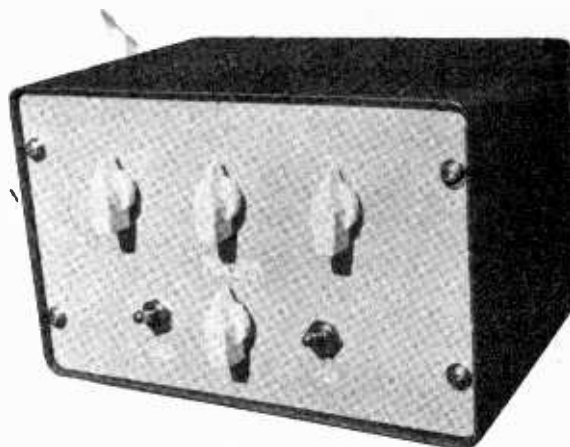

A CALIBRATION oscillator of this type provides calibration signals at a large number of fixed frequencies, so that the tuning scales of receivers and other equipment can be marked. The actual frequencies available fall into three ranges, as follows:

5Mc/s and its multiples 10, 15, 20, 25 and 30Mc/s, to provide signals at 5 megacycle intervals from 60 to 10 metres.

1Mc/s and multiples to give signals at 1, 2, 3, 4, 5, 6, 7Mc/s etc., permitting calibration at 1 megacycle intervals from 300 to 10 metres.

100kc/s and multiples for calibration of medium waves from 500 kilocycles to 1,500 kilocycles (600 to 200 metres) and for short wave bands where required. A typical use is calibrating at 1,800, 1,900 and 2,000kc/s for the 160M amateur band, or 3,500, 3,600, 3,700 and 3,800kc/s for the 80M band.

In such equipment, crystals are generally employed. In view of the cost of these, inductors are used instead, with a combination of fixed and pre-set capacitance in parallel. These circuits are set on frequency with the aid of the 200kc/s BBC Radio 2 (1,500M) transmission, and the National Physical Laboratory 5Mc/s signals. There is no great difficulty in obtaining an accuracy far higher than that which can be observed on the tuning scales of any general coverage communications type or other receiver.

Figure 1 is the calibration oscillator circuit. The pentode section of the ECF80 has cathode feedback from the taps on coils L1, L2 and L3, with electron coupling to the anode output circuit. This gives isolation of the tuned circuits, and quite a large r.f. output.


The ECF80 triode section is an audio oscillator, allowing tone modulation when required. This gives ready identification of the calibration oscillator output.

Power can generally be borrowed from the receiver. If not, a small power pack, giving 6.3V at 0.43A, and about 10mA at 220V, will be required.

Harmonic Output

Figure 2 shows some of the outputs available from the calibration oscillator, and will help to clarify the way in which it is used. The fundamental outputs 5Mc/s, 1Mc/s and 100kc/s (0.1Mc/s) and multiples of them will be heard on a receiver. The multiples grow progressively weaker, the upper frequency limit depending either on the coverage of the receiver, or its sensitivity. The outputs of 5Mc/s, 1Mc/s, 100kc/s and their multiples, are selected by the calibration oscillator bandswitch. With a typical communications receiver, all can be heard up to 30Mc/s.

Fig. 1: Complete circuit of the calibration oscillator.

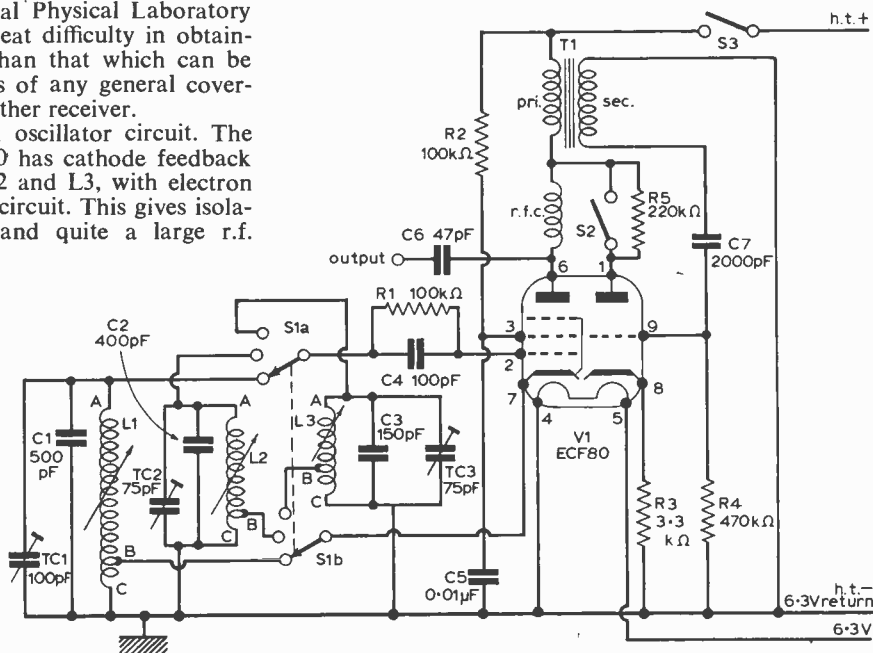

The harmonics may be used for trimming and aligning purposes, or to correct errors in dial readings of a ready-made receiver. When dealing with the h.f. bands, first check at 10, 15, 20, 25 and 30Mc/s, for positive identification of these frequencies by the 5Mc/s oscillator harmonics. Appropriate 1Mc/s points can then be located by tuning up and down from the 5Mc/s multiples, as required.

With a completely uncalibrated receiver, a similar method is used. First mark the receiver scales at 5Mc/s intervals, omitting the numbering if not known. The 1Mc/s coil is then switched in, and lighter marks made at 1Mc/s intervals. This gives a scale similar to a portion of Fig. 2, but without numbers. It is now necessary to identify *one* frequency on each receiver band, and to count up and down from this, to fill in all marks on that band. This is generally easy, but the following notes may be useful.

The National Physical Laboratory signals on 2.5Mc/s and 5Mc/s identify these frequencies. Amateurs will be heard on the low frequency side of the 2Mc/s mark in the 1.8-2.0Mc/s band. Amateurs also use 3.5-3.8Mc/s, so will be heard a little l.f. of a 4Mc/s mark, and this and other bands can be calibrated by counting the 100kc/s signals between 1Mc/s markings already put on the receiver scale.

For higher frequency ranges, identification can if wished be from amateur bands. Since one 5Mc/s mark will be 15Mc/s, a 1Mc/s harmonic l.f. of this will be 14Mc/s, and the 20M amateur band is 14-14.35Mc/s. Another 5Mc/s harmonic is 20Mc/s, and a mark 1Mc/s h.f. of this will be 21Mc/s, or the l.f. end of the 15M or 21-21.45Mc/s amateur band.

For medium waves, mark the dial at 100kc/s intervals throughout the tuning range. Identify one mark by noting its relationship to a BBC transmission or any other station. Then count up and down from this, writing in the frequencies, as for the short wave bands.

Construction

This should be rigid. Figure 4 is under the chassis, and Fig. 5 above the chassis. Each coil has a parallel fixed capacitor, and smaller pre-set or variable control for narrow frequency adjustment around the wanted spot frequency. If coils and capacitors are as shown, the correct frequencies can easily be found. Except for this, there is no need that capacitor values are exactly as shown, so it might be possible to utilise trimming and other capacitors already to hand.

Various intervalve coupling transformers and tapped output transformers will produce an audio tone. A single tapped winding, such as available on an output transformer, can be used by taking the tapping to h.t. positive (switch). One outer tag then

goes to the triode anode (via modulation switch) and the other outer tag to C7. Transistor type transformers are unsuitable. If no oscillation is obtained by using a transformer having two windings, reverse connections to one winding.

Inductors

These are wound on $\frac{1}{4}$ in. diameter formers having adjustable cores. The smallest coil L3 has 20 turns of 24 s.w.g. enamelled wire, side by side. Begin at A, Fig. 3, the start of all coils being as near the tagged ends of the former as possible. Bare and tin the wire, thread it through the pin A, and solder at the tip. Tapping B is a loop, and C is the end of the winding. For L3, tapping B is five turns from earthed end C. All turns are in the same direction. Pressure should not be exerted on the pins while they are hot.

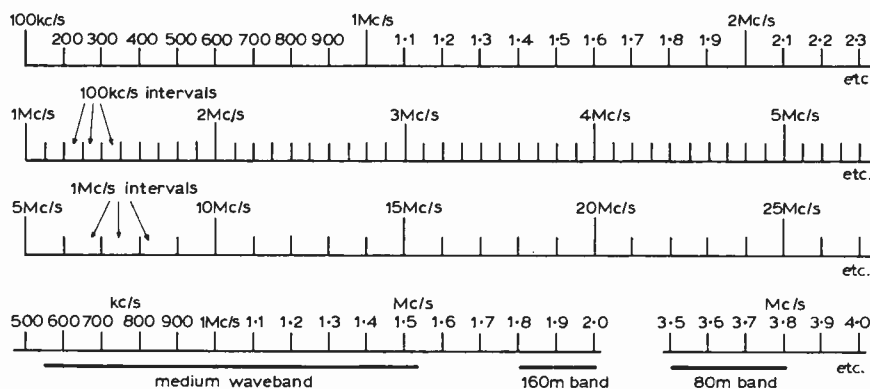


Fig. 2: Chart showing output frequencies of calibration oscillator.

L2 has 58 turns of 34 s.w.g. enamelled wire side by side, tapped at eight turns from C.

The large coil L1 has 500 turns of 36 s.w.g. enamelled wire, tapped at 50 turns from C. Cut two discs about 1in. in diameter from paxolin or hardboard. Punch or make $\frac{1}{4}$ in. diameter holes so these discs are a push fit on the former. They are cemented as in Fig. 3, with $\frac{1}{4}$ in. winding space between them.

End A passes through a small hole in the upper disc, near the former. Wind on 450 turns, then make a loop and place sleeving on it. The loop goes through pin B, and is soldered. A further 50 turns are then wound on, in the same direction, and the coil finished at C.

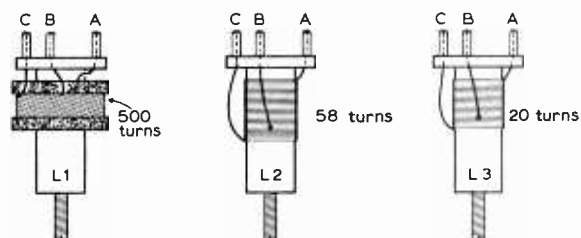


Fig. 3: Coil winding details.

Windings are lightly cemented in place. The coils are held by 6BA nuts, which are tightened after adjusting the cores.

An insulated socket is provided for the output lead. Enough coupling can be obtained on some frequencies by placing the output lead near the aerial socket of the receiver, or near a short insulated wire connected to the aerial socket. With portables, place the lead near the receiver.

Oscillator Calibration

The 100kc/s signal should first be checked by tuning in Radio 2 on 200kc/s on any available receiver, and rotating the coil core of L1 so that the calibration oscillator harmonic falls on the same frequency, with VC1 about half closed. Then lock the core.

Short wave conditions vary, but listening on one or two occasions should enable the "tick" of the NPL signal to be located on 5Mc/s. If necessary, first identify 1Mc/s or 300M in the medium wave band by using the 100kc/s harmonic, and tune the 1Mc/s circuit L2 to this. A 1Mc/s harmonic will then be 5Mc/s, and will show where to tune for the NPL signal.

When the 5Mc/s NPL signal is found, both the 1Mc/s and 5Mc/s circuits L2 and L3 are tuned to zero beat with this. The 100kc/s circuit L1 may also be checked on this frequency, but *after* tuning to Radio 2 as described.

Check that four 1Mc/s marker signals are obtained between each 5Mc/s marker signal and the next, every fifth 1Mc/s harmonic naturally falling on the 5Mc/s harmonics. In the same way, nine 100kc/s marker signals will be found between each 1Mc/s signal and the next, the tenth 100kc/s harmonic falling on 1Mc/s, and so on (Fig. 2).

Put dots on the panel to show tuning positions for the calibration oscillator controls. The equipment should be placed in a cabinet. Before accurate and permanent calibration of a receiver, switch on the oscillator in advance, and correct its circuits against the NPL signal on 5Mc/s, if necessary.

Receiver Calibration

When the calibration oscillator unmodulated harmonic falls near a radio transmission (e.g., Radio 2) a heterodyne note is heard. This falls in frequency as the difference between the two signals is reduced. With modulation off, tune for "zero beat".

A heterodyne is best heard when the two signals are reasonably similar in strength. For example, tight coupling on 200kc/s can swamp the receiver so that the Radio 2 signal is scarcely audible.

When heterodyning the calibration oscillator with a transmission or with a signal generator or v.f.o. for calibration purposes, the receiver is merely to

—continued on page 54

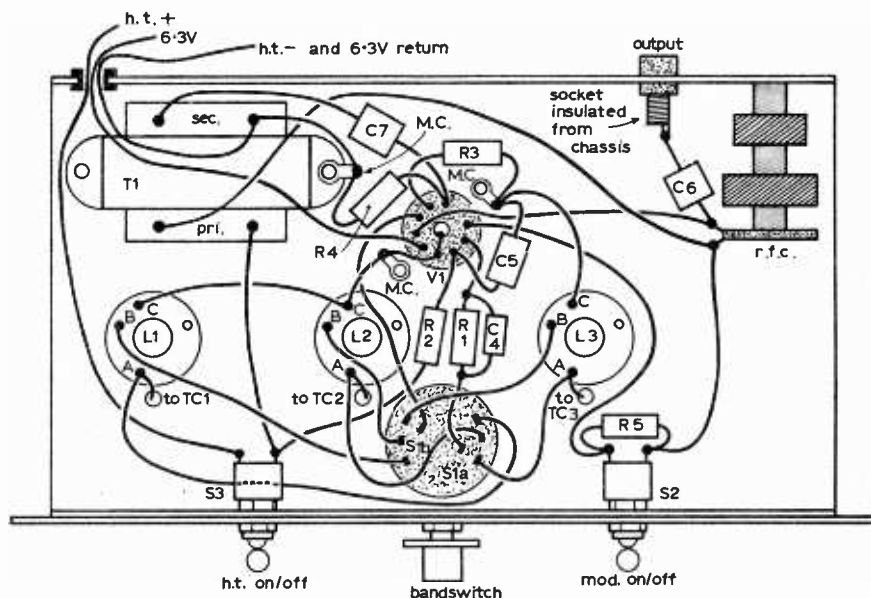


Fig. 4: Under-chassis wiring details.

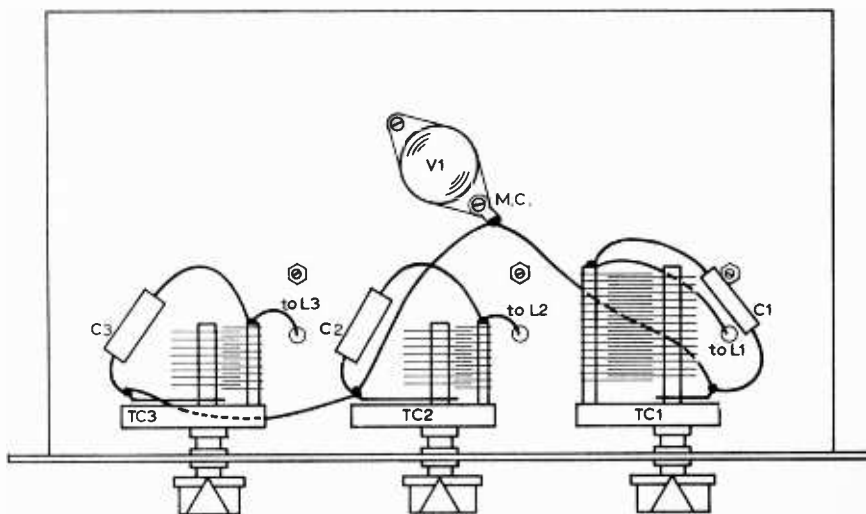


Fig. 5: Above-chassis view.

TAKE 20

JULIAN ANDERSON

A SERIES OF SIMPLE TRANSISTOR PROJECTS, EACH USING LESS THAN TWENTY COMPONENTS AND COSTING UNDER TWENTY SHILLINGS TO BUILD.

NEARLY all the amplifiers described for the constructor are for a specific purpose, either for a record player radio or tape-recorder. Again nearly all of them amplify the input to at least 350 milliwatts and do their best to faithfully reproduce the signal but these amplifiers are relatively complicated (at least compared to the design about to be described) and not inexpensive, especially as several use transformers.

The two-transistor amplifier described in this article could hardly be simpler, it certainly isn't Hi-Fi (even using that term in its present adulterated term) and it hasn't much of an output, nevertheless it has plenty of uses. Being very simple and also being capable of being made very small it is ideal for adding to miniature radios and other equipment. With no modifications it is ideal as an audio signal tracer and by adding a detector diode and smoothing capacitor it may also be used as an r.f. signal tracer.

THE CIRCUIT

The signal is fed to the base of Tr1 via C1, this ensures that whatever the input, the d.c. working conditions of the first transistor are unaffected. The output from Tr1 appears across R2 and is coupled directly to the base of Tr2 and in turn the output appears across the loudspeaker coil. R1 is connected between the collector and base of Tr1 and not only provides the correct working voltage but applies both a.c. and d.c. feedback. To provide the correct working voltage at the emitter of Tr2 a resistor is inserted in the emitter circuit of this transistor as it is conducting all the time a voltage is developed across R3. However the conductivity of Tr2 varies with the signal and so will the voltage, making it necessary to "iron out" the fluctuations, this is done by C2.

By using a speaker of 75Ω impedance an output transformer is unnecessary. Speakers of this impedance are very common in the smaller diameters (2in. etc.).

CONSTRUCTION

The construction is absolutely straightforward and layout is not at all important, a suggested arrangement is shown in Fig. 2. A volume control is not shown on the board but this could easily be included as could the diode and smoothing capacitor when required as an r.f. signal tracer. The transistors used are an OC71 and an OC81 but almost all germanium P-N-P transistors could be substituted—and have

No.1 a two transistor amplifier ★ components list

Resistors:

R1 120kΩ

R2 4.7kΩ

R3 330Ω

VR1 5kΩ with switch.

Capacitors:

C1 5μF

C2 32μF

C3 100μF

Tr1 OC71, Tr2 OC81—see text.

Loudspeaker, 75Ω impedance. Veroboard 1½ x 1½ in. 9 volt battery, PP3 etc.

Extra components for r.f. signal tracer, C1, 1,000pF, C2 0.01μF, Diode OA79 etc.

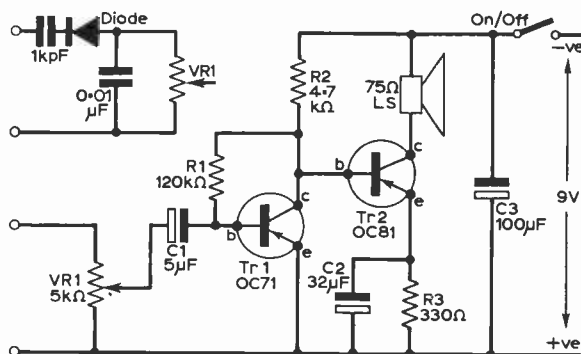


Fig. 1: The circuit of the two transistor amplifier.

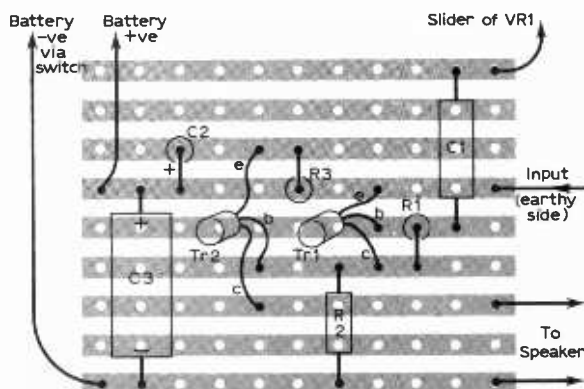


Fig. 2: The component layout; note that none of the copper strips need be broken.

been by the author. An output transistor should be used in place of the OC81 as small signal types can get a bit hot and fail. Only a very small signal is needed at the input to provide an audible output and so by inserting a high value resistor (about 1MΩ) it can be used to trace fairly high impedance signals.

AERIALS

A. J. WHITTAKER

PART 2—TRANSMITTER AERIALS (CONTINUED)

LAST month we discussed some of the basic principles of the radiation of radio waves from a dipole aerial. In this article we shall continue our investigation by examining the simple dipole and the Marconi quarter-wave aerials.

Radiation Height

Radiation height depends upon the current distribution in the aerial. It may be approximately linear, or sinusoidal. See Fig. 2.1 below.

The effect is to make the aerial effectively shorter because the amount of power radiated is reduced. In practice the power radiated is indicated by "metre amperes" which is equal to the radiation height multiplied by the r.m.s. current flowing in the aerial wire = $L_r I$.

The power radiated from a dipole, using L_r in the equation, is given by,

$$P = \frac{320\pi^2 L_r^2 I^2}{\lambda^2} \quad R_r = \frac{320\pi^2 L_r^2}{\lambda^2}$$

Where,

L_r = radiation height = $K \times$ physical height

K = aerial form factor (see below)

λ is the wavelength in metres.

The radiation resistance of a dipole, R_r , may be derived by expressing the physical height in terms of the wavelength λ in use. If the dipole height is $\lambda/2$, putting $\lambda = 4L$ and $L_r = 2L/\pi$ (form factor) we have,

$$R_r = \frac{320\pi^2 4L^2}{16L^2\pi^2} = 80 \text{ ohms.}$$

This value is typical for all half wave aerials erected above the ground and provides an empirical rule for estimating radiated power.

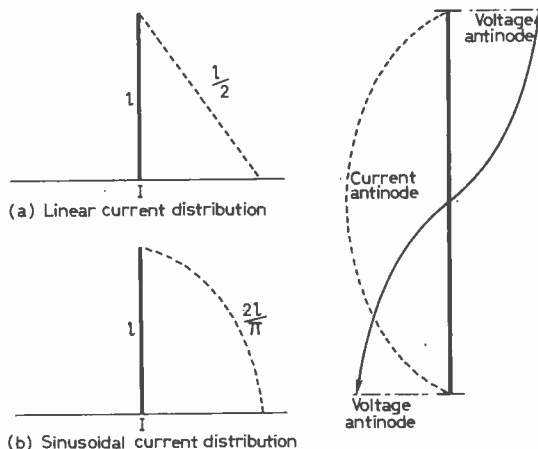


Fig. 2.1

Fig. 2.2

Figure 2.2 below illustrates the voltage and current patterns in a simple dipole aerial. Nodes of voltage or current are points of minimum amplitude. Anti-nodes are points of maximum voltage or current.

The aerial impedance (Z) is the ratio of r.m.s. volts/r.m.s. current at any point and is thus a minimum in the centre, being typically 80 ohms. The aerial system, equivalent to a series resonant circuit, is current fed at the centre, and is said to be excited at its natural or fundamental frequency.

Marconi Quarter-wave Aerial

The fundamental frequency of the aerial in Fig. 2.3, is four times its physical length. This may be compared with an organ pipe with the top closed, producing a note of four times the length of the pipe.

As there is a current antinode at the base of the aerial, this is a convenient point to fix a current meter. This is usually of the thermocouple type, its purpose being to monitor the aerial current when tuning the system. The aerial is in tune when the meter shows maximum reading.

Figure 2.4 shows the voltage and current wave patterns on a quarter-wave Marconi aerial with a current meter fixed at the current anti-node point.

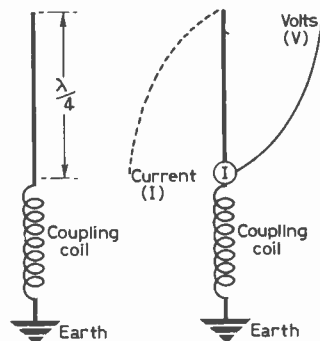


Fig. 2.3

Fig. 2.4

Figure 2.5 shows the radiation pattern from a Marconi quarter-wave aerial. $P O P_1$ represents the earth line and as this is not a perfect conductor, it absorbs energy from the passing wave front causing a forward tilt. This assists the wave to follow the earth's curvature (i.f. waves only, 30-300kc/s).

The power radiated from a Marconi quarter-wave aerial is given by,

$$P = \frac{160\pi L_r I}{\lambda}$$

Again putting $\lambda = 4L$ and $L_r = 2L/\pi$ (form factor) we have


$$\text{Radiation resistance } R_r = \frac{160\pi^2 4L^2}{16L^2\pi^2} = 40 \text{ ohms.}$$

*Fine design
superlative
performance*

P.W. DOUBLE 12

As described in this month's Practical Wireless
*Top line integrated hi-fi stereo
amplifier featuring*

PEAK SOUND "CIR-KIT"

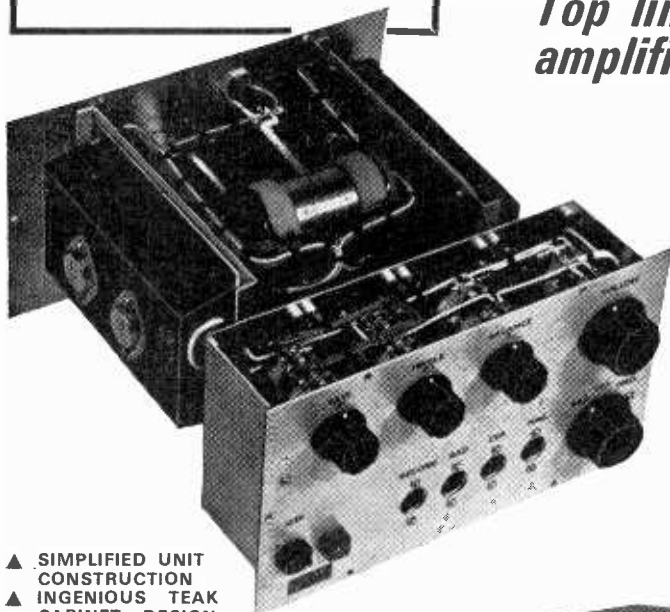

- ▲ SIMPLIFIED UNIT CONSTRUCTION
- ▲ INGENIOUS TEAK CABINET DESIGN
- ▲ PROFESSIONAL IN EVERY WAY AND MONEY SAVING TOO!

This is your "P.W. Double 12" shopping list

As you follow through stage by stage with P.W. these are the Peak Sound kits you will require. They are exact to specification. Transistors included.

2 Spools of "Cir-Kit" at 2/- each	4	0
2 Pre-amp and tone control kits	4	15 0
4 3½in x 2in "Cir-Kit" matrix boards	7	0
2 PA.12-15 Power Amplifier Kits	7	19 0
2 Heat Sink assemblies	12	0
1 PS.45K 45 volt power supply kit	4	10 0
1 Pack-flat afrormosia teak finished Cabinet kit	2	12 6
5 Controls as specified	2	0 0

TOTAL COST £22 19 6

Metal work (make or buy), knobs, plugs and sockets, fuses etc. allow £3.0.0.

Go to your Dealer NOW

for your authentic Peak Sound Kits. In case of difficulty, please send direct, giving the name and address of your usual supplier where possible and add 11/- postage for complete assembly, or 5/6 if without power pack.

TRADE ENQUIRIES INVITED

PEAK SOUND (HARROW) LTD., 32 ST JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, Phone EGHAM 5316

Peak Sound are indeed proud to be associated with this superb P.W. design and that so much of it is made possible because of Peak Sound products and design techniques. Basically, the "P.W. Double 12" demonstrates the value of using "Cir-Kit" in modern circuit board units either for single or prototype examples, but in this instance, Peak Sound have contributed much more to the success of this project. This includes the remarkable power amplifiers, the power pack and the ingeniously styled cabinet which almost assembles itself, it is so simple to build. Read about the "P.W. Double 12" in this issue right now. Then when you build this exciting new design be sure you do it with authentic, exact-to-specification Peak Sound kits as described.



▲ Abridged specification

Formation—Two pre-amp panels, two tone control panels, two power amplifier modules, power supply unit on chassis, housed within teak finished cabinet.

Controls—Bass and treble cut and lift based on Baxandall circuitry/Volume/Balance/ Rotary selector.

Input Sensitivity—Magnetic P.U. (per channel) 2.5mV into 68kΩ. Ceramic P.U.—25mV into 27K. equalised for flat response. Radio/Aux. 60mV.

HIGH OVERLOAD FACTOR ON ALL INPUTS.

Frequency Response—20Hz to 30KHz ± 1dB overall,



"Cir-Kit" is at the heart of building this fine design. Made from almost 100% pure copper with unique adhesive backing, it is the superb circuit builder for all requirements. In 5" spools, 1/8" wide, 2/- each.

"CIR-KIT" makes it possible!

Output—12 watts per channel into 15Ω (8Ω speakers may be used).

Negative Feedback—43dB over each section.

Power required—45V D.C (supplied by built-in power unit).

Cabinet—Afrormosia teak finish, pack-flat, easy to build kit. Size 9½ x 5½in. high x 9½in. deep.

Transistors—Ultra low noise in pre-amp and tone control stages.

PERFORMANCE CHARACTERISTICS, PARTS REQUIRED, ETC., SEE OTHER PAGES IN THIS ISSUE

THESE PEAK SOUND PRODUCTS WILL HELP



PA.12-15 POWER AMPLIFIER

As specified for "P.W. Double 12" and available ready built complete with heat sink for mounting directly into position as described, but can also be used in other applications. Also available as a kit less heat sink and board.

Built **£5.19.6**

Kit (less heat sink, board and "Cir-Kit") **79/6**

Heat sink and baseboard assembly **10/-**
Please add 2/6 p/p either model if ordered direct, or 5/- for two.

ES. 10-15 BAXANDALL SPEAKER

This easy to build loudspeaker provides genuine hi-fi standards by the use of unique equalising principles. Frequency response 60-14,000Hz (100-10kHz ± 3dB). Easy-to-build kit including 18 x 12 x 10in cabinet.

(Carr. 11/6). Leaflet available.



£9.17.6

+ £1.2.1 P/Tax

Where

L_r =radiation height= $K \times$ physical height (K =form factor).

R_r =radiation resistance.

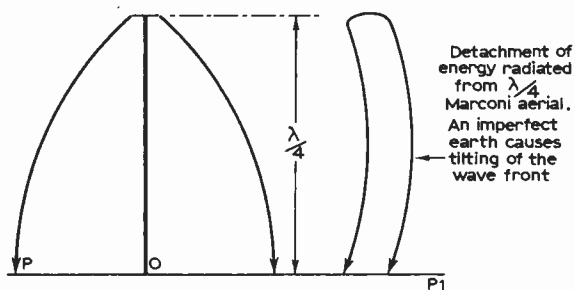


Fig. 2.5

Image Aerials

Figure 2.6 shows the image of a dipole aerial suspended above the ground on a mast. As in the case of optical reflection from a mirror the effect of the ground in the neighbourhood of the aerial system may be assessed by replacing the ground by an image of the aerial, from which half of the total energy is radiated. The total radiation field is then calculated by assessing the joint field so produced by the aerial and its image.

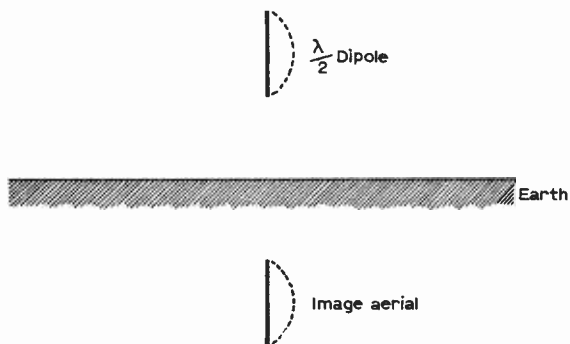


Fig. 2.6

Aerial Impedance and Tuning Arrangements

The measurement and tuning of a Marconi quarter-wave aerial may be done by fixing volt and ammeters at appropriate points in the circuit. Figure 2.7 shows the general arrangement. The aerial is in tune when the ratio V/I is a minimum. The value of this ratio gives the aerial impedance (Z_1) and is typically 40 ohms.

In the case of the half-wave aerial, end fed, the circuit at the feed point is tuned for maximum V/I ratio. This gives the aerial base resistance which is typically 3500 ohms. Figure 2.8 shows the circuit with the voltage and current meters in place.

Aerial Capacitance

If we add an extension to our quarter-wave aerial and bend this over so as to form an inverted L shape, we will increase the capacitance of the aerial. The parallel or top part of the wire forms an additional capacitor plate. The effect of this is to increase the current flowing in the vertical wire and so increase the effective height. The form of the voltage and current distribution in such an aerial system is given below, Figs. 2.9a and b.

The "T" aerial gives much the same results but is a slightly better radiator and has slight directional properties. Its form is given below, Fig. 2.10b.

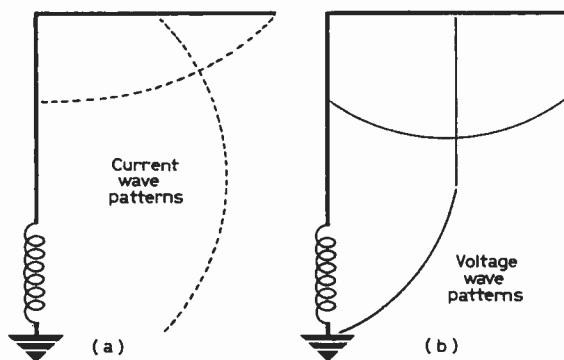


Fig. 2.9

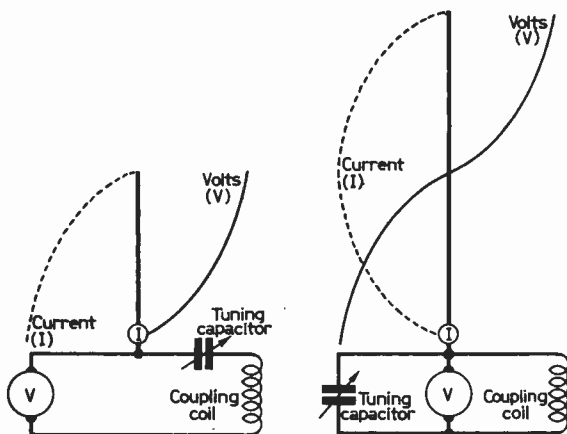


Fig. 2.7

Fig. 2.8

Aerial Form Factor

Aerial form factor (AFF) refers to T and L shaped aerials where the current distribution in the vertical part is no longer sinusoidal and it is impossible to arrive at an estimate of the power radiated. However, it is possible to arrive at a factor by which the actual height may be multiplied in order to obtain the *effective or radiation height*. This is the AFF given in the tables, which give a good approximation for the effective height for fixed ground stations.

The symbol used for effective or radiation height is L_r , and in the case of the dipole, it refers to the mean value of current flowing in the length of the aerial system concerned.

The AFF of the inverted "L" aerial, when the vertical and horizontal members are equal in length, gives a ratio of $L_r/l=1$, whence the $AFF=0.904$ (see table below).

For the "T" aerial the horizontal or top part is twice

the length of the vertical part. Figure 2.10 (a and b) shows the general arrangement of the two aerial systems.

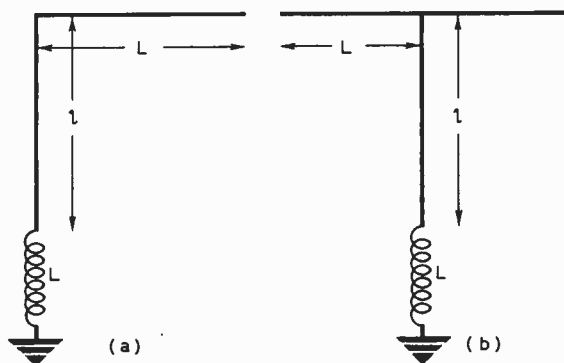


Fig. 2.10

Table of Aerial Form Factors

$\frac{L}{7}$	AFF	$\frac{L}{7}$	AFF
0.0	0.639	1.5	0.940
0.1	0.696	2.0	0.958
0.2	0.741	3.0	0.979
0.3	0.777	4.0	0.987
0.4	0.806	5.0	0.993
0.5	0.830	6.0	0.996
0.6	0.850	7.0	0.998
0.7	0.867	8.0	0.999
0.8	0.881	9.0	0.999
0.9	0.893	10.0	1.0
1.0	0.904	—	—

Aerial Capacity

All l.f. (30kc/s–3000kc/s) aerials are of necessity of the large capacity type and they are either of “L” or “T” form or earthed quarter-wave types. This is because (a) radiation resistance (R_r) is proportional to the square of the effective height. This is made large by erecting the aerial system as high as possible and by attaching a horizontal member, forming either an “L” or “T” shape, thereby increasing the capacity (σ) which makes the effective height nearly equal to the actual height. (b) The greater the capacity of the aerial the less inductance will be required to tune the aerial thus lowering the oscillatory potential and the less likely to brush discharge.

To increase the aerial capacity, a number of parallel wires are added in the horizontal plane well separated, usually about 3ft. apart.

The simple Hertzian dipole aerial system and variations thereof are generally used for v.h.f. communication, the range being little more than optical distance depending upon a number of factors, such as aerial height, nature of terrain between transmitter and receiver.

References

Admiralty Handbook *Wireless Telegraphy*.
Short Wave Wireless Communication.

TO BE CONTINUED

PART 3 WILL DESCRIBE DIPOLE AERIALS AND THE CONSTRUCTION OF A V.H.F. F.M. AERIAL

CALIBRATION OSCILLATOR

—continued from page 48

compare signals from the two sources, and exact tuning of the receiver has no bearing on calibration.

Exact alignment of circuits, or calibration, is best obtained with the modulation off. In these circumstances, the harmonic will be heard as an unmodulated carrier, with the receiver b.f.o. switched on.

With the modulation switch S2 closed, the audio tone will be heard accompanying all harmonics, and this is occasionally useful.

★ components list

Resistors:

R1	100k Ω $\frac{1}{2}$ W	R3	3.3k Ω $\frac{1}{2}$ W
R2	100k Ω 1W	R4	470k Ω $\frac{1}{2}$ W
		R5	220k Ω $\frac{1}{2}$ W

Capacitors:

C1	500pF silver mica
C2	400pF silver mica
C3	150pF silver mica
C4	100pF silver mica
C5	0.01 μ F 250V
C6	47pF mica
C7	2000pF paper, mica or ceramic
TC1	100pF air spaced variable
TC2	75pF air spaced variable
TC3	75pF air spaced variable

Miscellaneous:

R.F.C. Osmor QC1 all-wave r.f. choke; three Type CR22 $\frac{1}{2}$ in. dia. formers and cores (Home Radio, Mitcham); T1 Type TIV3 1:3 transformer (Home Radio, Mitcham); ECF80; B9A valveholder; Chassis 4in. x 6 $\frac{1}{2}$ in. x 2in; 5in. x 8in. x 5in. Dinkicase (Electroniques); two-pole three-way rotary switch S1a, b; Four small pointer knobs; Two toggle on/off switches S1, S2; Tagstrip, wire, etc.

When dealing with a superhet whose design or frequency coverage results in strong second channel indications, these can be identified in the usual manner. Avoid swamping or overloading the receiver with the lower order harmonics, as this may give confusing results. To calibrate a v.f.o. or signal generator, tune in the wanted calibration oscillator harmonics on a receiver, tune the v.f.o. or signal generator to zero beat, and mark its scale. ■

P.W. GUIDE TO COMPONENTS

—continued from page 45

Alloy transistors suffer one major drawback and this is due to the alloy process. In the process the base thickness cannot be controlled accurately enough to give very thin base regions. As the frequency response depends largely on this thickness alloy transistors are limited to operation below approximately 10Mc/s.

As a result of this limitation and with the improvement of diffusion techniques the drift transistor was subsequently introduced. This uses the mesa form of construction.

TO BE CONTINUED

CODAR CR.70A

Communications Receiver 540-10 metres




The Codar CR.70A is an excellent general coverage communications receiver for the keen short wave listener. Very reasonably priced at just £21 the CR.70A is outstanding value for money. In four stable ranges, the receiver covers from 540 metres medium wave, right through the shipping and coastguard frequencies all the short wave and international amateur bands up to and including 10 metres, where the rapidly improving conditions that now prevail allow the regular reception of world-wide call-signs! The CR.70A has a high 'Q' aerial input stage using exclusive CODAR COIL air space inductor. Double tuned, iron cored I.F. transformers produce high selectivity. Ready to plug into 200-250 volt AC mains, the CR.70A needs only your aerial and a 2-3 ohm loudspeaker. The cabinet measures only 13" x 5 1/2" x 7 1/2" and the control panel is finished in black and white with chrome trim knobs. Fully guaranteed for 12 months! New model has separate direct output socket for feeding tape recorder, Hi-Fi equipment, etc.


20 gns.

Carriage 7/6 extra

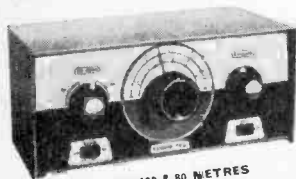
*Ideal for SWLs *5 valves (inc. two twin triodes) giving 7 valve line-up *Excellent on amateur and shipping frequencies *Calibrated signal strength meter (illuminated) *Automatic volume control *Separate B.F. oscillator for morse and S.S.B. signals *Two speed vernier tuning *Separate output for recording etc.



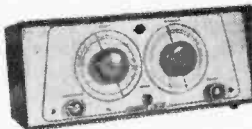T21 RECEIVER FOR 160 & 80 METRES AMATEUR BANDS
8 transistors, bandspread 1.8-2Mc/s and 3.5-4Mc/s 12 volts, only 8" x 4" x 3 1/2". Ideal portable, mobile or home receiver. Efficient BFO, printed circuits. ONLY £15.17.6. Carr. 4/6.



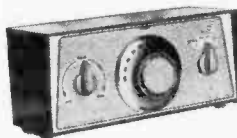CR45 MAINS T.R.F. SHORT-WAVE RECEIVER
World wide reception. *Separate electrical band-spread. *3 slow motion drives. *Output 3 watts for 2/3 ohm speaker. *Valves ECC81, 6L84, EZ80. Size 12" x 5 1/2" x 7". CODAR-KIT CR.45K with 3 coils (10-26, 25-75, 60-176 metres). £9.15.0. Carr. 6/-, or ready built CR.45 £11.19.6. Carr. 6/- Extra coils 5/4 each.



R.F. PRE-SELECTOR MODEL P.R.30
1.5-30Mc/s
Provides up to 20dB gain plus substantial image rejection. Improved signal/noise ratio and selectivity. Power requirements 180-250 volts (2mA H.T. 6.3 volts, 3 amp L.T. Size 8 1/2" x 5" x 4". Ready built complete with cables, plugs and instructions. £5.19.6. Carr. 4/6. Self-powered P.R.30x £7.19.6. Carr. 4/6.



MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER
*Can be built in one evening. *Complete with valve, one coil 25-75 metres and 4 page instruction manual. Price 22.4.6. Carr. 3/- Extra coils 5/4.

CRC

CODAR RADIO COMPANY

BANK HOUSE, SOUTH-WICK SQUARE, SOUTHWICK, SUSSEX. TEL: 3149
World-wide Mail Order Service

Please supply
(tick as required)
☐ I enclose cheque/
M.O./P.O. value of
£.....

☐ 5d stamp enclosed
for leaflets

NAME _____
ADDRESS _____

POST ORDER FORM TODAY

SPEAKER SYSTEMS

THE CAXTON COLUMN
This is a column cabinet. 23½ x 6½ x 5½ in. wide, fitted with 3 speakers. This will handle 10 watts and will improve the quality of any tape recorder, or record player. Finished in wood grain cloth and sandstone Vynair. A real bargain at 59/6. P. & P. 10/6.

THE IMP. Extension Speaker Cabinet. Wedge shaped, size 7½ x 6½ in. fitted 7 x 4 in. speaker. Covered with attractive walnut with fawn Vynair front. Keyhole slot in back. Only 25/6. P. & P. 4/6.

DUO. Wedge shaped Speaker Cabinet. Size 7½ x 7½ in. fitted 7 x 4 in. speaker. Covered in attractive two tone Vynair. Price 32/6. P. & P. 4/6.

CLARENCE. Extension Speaker Cabinet fitted 7 x 4 in. speaker. (3 ohms imp.) and volume control. Size 10½ x 8½ x 4½ in. Finished in black and grey Vynair. 45/- P. & P. 4/6.

All cabinets are new and speakers are mounted on ½ in. chipboard baffles. All speakers ex TV reconditioned but magnet. All carefully tested before despatch.


THE MILTON. A Hi-Fi Bookcase Cabinet. Size 9 x 5 x 6 in., with 5 in. speaker. Finished in Teak cloth with bold silk front 30/- P. & P. 4/6.

THE STEREO. A superior extension speaker cabinet fitted with two 7 x 4 in. speakers. Size 16 x 9 x 8½ in. Finished in fawn Vynair with natural/teak ends. 28. P. & P. 5/-.


THE SCOTT. Table top or wall mounting Speaker. Size 16½ x 10½ x 5½ in., tapered as illustrated. Fitted 13½ x 8 in. Speaker with volume control. Finished in black cloth with matching grey Vynair. (Please state 3 or 15 ohm imp.) 24.5.0. P. & P. 7/6.

SPEAKER ENCLOSURES

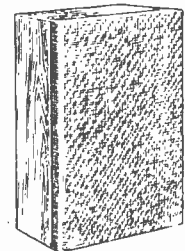NOTE:—Speaker enclosures can only be supplied with speakers see below for ideal types:



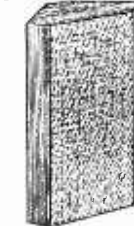The Baker. Size 8 x 15½ x 23½ in. Teak veneered top and sides. Fawn Vynair covered front. Cut out for 12 in. speaker and 3 in. tweeter with port and internal bass reflex board. Fitted rubberfeet. 26.15.0. P. & P. 10/6.



The Cowdrey. Corner Cabinet in natural teak finish for 13½ x 8 in. speaker also cut out for tweeter. 28.15.0. P. & P. 8/6.

SPEAKERS: Elac Heavy duty Ceramic Magnets 11,000 line, 10 in. round, 10 x 6 in. 3 ohm, or 15 ohm, 48/6. P. & P. 3/6. 8 in. round 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I. 13½ x 8 in. 3 ohm 48/6. P. & P. 3/6. E.M.I. 3 in. tweeter, 17/6. P. & P. 1/6. E.M.I. 13½ x 8 in. fitted two 2 in. tweeters. 15 ohms 70/6. P. & P. 4/6. E.M.I. 13½ x 8 in. (15 ohm) Hi-Fi Quality. 25.19.8. P. & P. 4/6. E.M.I. Woofers, 6½ x 6½ in. square, 8 ohm, 50/6. P. & P. 4/6. E.M.I. Crossover, 18/6. P. & P. 1/- EAGLE Crossover units, 3 or 16 ohms, 16/- P. & P. 1/- Bakers 12 in., 25 watt, 15 ohm, 26.6.0. P. & P. 3/6. All other speakers supplied—Goodmans, Bakers, W.B., Wharfedale, Eagle, Tripletone.

TEAK PLINTH AND PERSPEX DUST COVER for SP25 etc. 25.5.0. P. & P. 5/- VYNAIR Width from 40 to 64 in., 17/6 yd. off roll. P. & P. 1/9. 4 yd. 9/- P. & P. 1/9. Stamp for samples.

SPEAKER MATCHING TRANSFORMERS. 3, 7, 15 ohms, 8 watt, 11/6 P. & P. 1/6.

MICROPHONES: Xtal Hand Mikes. B1201 with stand, 54/6. P. & P. 3/6. ACOS Mike 45, 21/- ACOS Mike 40, 18/6. Dyn. Mike DM-391, 30/- CM21 Xtal, 12/6. Telephone Pick-up, 10/6. P. & P. 1/- Xtal lapel Mike, 7/6. Guitar Mike, 12/6. P. & P. 1/-.

FERRON RODS: 6 x ½ in., 2/6; 4½ x ½ in., 2/-; 6 x ½ in., 2/6; 8 x ½ in., 3/- P. & P. 1/- each.

FERRON RODS WITH OILS: 4½ x ½ in., 3/6; 8 x ½ in., 6/6; P. & P. 1/- each. **ROTARY SWITCHES:** 2 Pole Mains Switch, 3/-; 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3 pole 6 way, 6 pole 1/-.

PIANO KEY PUSH BUTTON SWITCHES. 7 button inc. mains on off. 6 banks of 6 P.C.O.s, 8/6. P. & P. 1/-.


BROADWAY Electronics

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 Telephone 01-672 3984 (Closed all day Wednesday) (Few minutes from Tooting Broadway Underground Station)

PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4½" x 2½". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet (Printed Circuits for Amateurs. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.

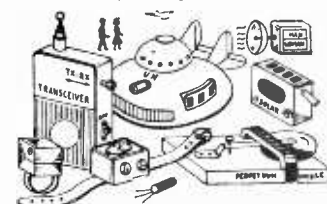

EXPERIMENTER'S PRINTED CIRCUIT KIT

8/6

Postage & Pack. 1/6 (UK)

Commonwealth:
SURFACE MAIL 2/-
AIR MAIL 8/-
Australia, New Zealand
South Africa, Canada.

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio, etc. (8) "TRIFLEXOR" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Controller anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62" x .96" x .25". (11) Wristwatch Radio 1.15" x .80" x .55". (12) Ring Radio .70" x .70" x .95". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Wire-less Door Bell. (33) Ultrasonic Switch/Alarm. (34) Stereo Preamplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller.

YORK ELECTRICS

333 YORK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

B-PRE-PAK LTD

222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
PHONE: SOUTHEND (0702) 46344

SPECIAL OFFER

Stock Clearance of Manufacturers Rejects. Limited Number UHF/VHF Tuner Units. Consisting of: 2 AF186 Transistors, Tuning Condensers, Coils and Comps etc.

Price 5/- each

Post and Packing U.K. 2/6.

BRAND NEW PRE-PAKS

No.	Price
B1 50 Unmarked Trans. Untested	10/-
B2 4 Solar Cells Inc. Book of Instructions	10/-
B3 17 Red Spot AF Transistors	10/-
B4 17 White Spot RF Transistors	10/-
B9 1 ORP12 Light Sensitive Cells	10/-
B53 25 Silicon Transistors 400 M/c	10/-
B54 40 Silicon Transistors NPN To18	10/-
B55 40 Silicon Transistors PNP To18	10/-
B56 40 Silicon Transistors NPN/PNP	10/-
B61 25 BSY28/7 Transistors new, untested	10/-
B82 25 BSY95A Transistors new, untested	10/-
B84 25 BFY50/1/2 Transistors new, untested	10/-
B85 25 BC107/8/9 Transistors new, untested	10/-
B86 100 Germ. Min. Diodes, untested	10/-
C3 1 Unijunction Transistor 2N2160	10/-
A3 25 Mixed Marked and Tested Transistors	20/-
A21 5 Power Transistors, one AD149, one OC26 and three more	20/-

Transistors	Price
AC126	2/4
AC127	2/4
AC176	1/6
AD149	10/-
ASV29	10/-
BC107-8-9	4/6
BC171	2/6
BC172	2/6
BC173	2/6
OC78	2/6
OC79	2/6
OC26	2/6
OC28	2/6
OC29	2/6
OC44	1/11
OC45	1/8
OC71	2/6
OC72	2/6
OC110	2/6
OC140	2/6
OC261	2/6
OC271	2/6
2N108	2/6
2N109	2/6
2N4284	2/6
2N4285	2/6
2N4286	2/6
2N4287	2/6
2N4288	2/6
2N4289	2/6
2N4290	2/6
2N4292	2/6
2N3055	2/6

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

Send for our FREE lists and catalogue of all our products. Check your own equivalent with our free substitution chart.

Matched Set. NPN/PNP AD161-AD162 10/- PR. Complementary Set. NPN/PNP Germ. trans. Pak F.3 2/6 PR.

NO CONNECTION WITH ANY OTHER FIRM MINIMUM ORDER 10/- CASH WITH ORDER PLEASE, add 1/- post and packing. OVERSEAS ADD EXTRA FOR AIRMAIL

SATELLITE EARTH STATION

RICHARD COLLINS REPORTS... PART 2

GOONHILLY 2—TECHNICAL CHARACTERISTICS

A brief summary of the general technical characteristics of Goonhilly 2 operating to Intelsat III—F2 is as follows:

Aerial Gain: Gain at 4165MHz (TV receive) 60dB; Gain at 6390MHz (TV transmit) 63dB; Beamwidth at 4GHz approximately 11 min. arc; Side lobe level at 6GHz is greater than 33dB lower than main lobe level with 1 degree arc away from main lobe.

Aerial G/T: Noise Temperature at 4165MHz and 30° elevation 55 deg. k; G/T at 4165MHz and 30° elevation 42.6dB/deg. k.

Aerial Tracking: Aerial steerability (a) Azimuth: 96 deg. 53 min. to 295 deg. 18 min. E. of N. Tracking rate is up to 5 deg./min. (b) Elevation: 0 deg. 14 min. to 43 deg. 55 min. Tracking rate is up to 2.5 deg./min.

Tracking modes: Autotrack, manual velocity, manual position, tape control.


System Bandwidth: Nominally 500MHz. (a) Transmit: 5900MHz to 6437MHz; (b) Receive: 3685MHz to 4225MHz.

Polarisation: Circular.

Equivalent Isotropically Radiated Power: Up to 93dBW at 6390MHz (TV transmit). This is equivalent to 1kW transmitter output power. Power stability is better than ± 0.1 dB. Frequency accuracy is generally within 40kHz of nominal at 6GHz.

Modulation: Frequency modulation is used throughout. The deviations used are: (a) Television 23MHz peak-peak; (b) Telephony 630kHz rms test tone for 132 channels, 410kHz rms test tone for 60 channels, 250kHz rms test tone for 24 channels.

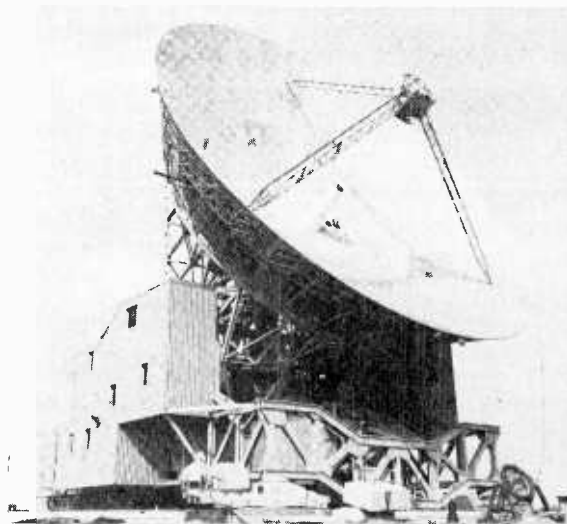Normal CCIR pre-emphasis is used for both TV and Telephony.




The No. 2 aerial.

Microwave Link

A microwave radio link from Goonhilly extends the satellite circuits to the International Telephone Services Centre in London. In the central building at Goonhilly the circuits are rearranged at baseband frequencies into units of 24, 60 or 132 channels as dictated by traffic requirements. Each baseband unit then modulates an intermediate frequency of 70MHz in the modulator section of the equipment provided by GEC-AEI (Electronics) Ltd. Also injected into the circuit at this point are a 60Hz continuity pilot, an energy dispersal signal to restrict the level of intermodulation products during light traffic loading and engineering service channels at sub-baseband frequencies. Intersite coaxial cables transmit the modulated i.f. carriers to the equipment on the aerial, where they are converted individually to their assigned frequencies on the GHz band. All carriers are then combined at low power level before amplification, in two stages, by common wideband travelling-wave-tube amplifiers. The output stage has a maximum capability of 8-10W but in order to restrict the power of unwanted intermodulation products it will not normally be loaded above 1.5W. A second transmitter which serves as a reserve for the telephony system can be used alternatively for television transmissions.

Parametric Amplifier

The very weak signals from the satellite in the 4GHz band are amplified by a three-stage parametric amplifier, cooled in a closed-circuit, gaseous-helium refrigeration system followed by a tunnel-diode amplifier. The four stages have an overall gain of 40dB over the 500MHz band assigned for the down path from the satellite. At the output of the common amplifier the individual carriers are separated by a

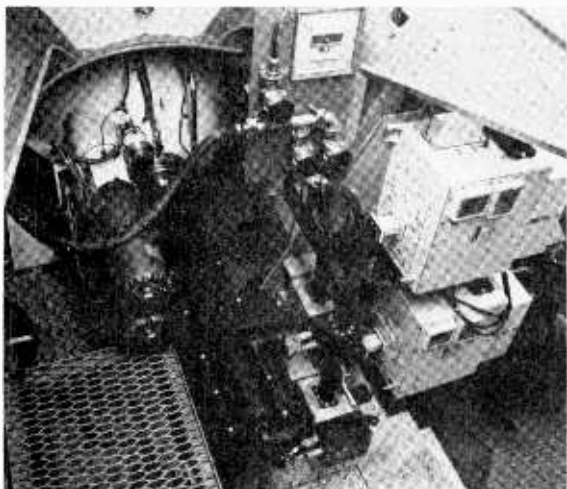

First stages of the receiving system, housed in a cabin directly behind the centre of the aerial dish. The two cryogenic enclosures can be seen as white boxes with waveguide network leading to them from aerial horn feed at dish vertex.

selective branching network converted in frequency to 70MHz and extended individually by coaxial cables to the feedback demodulators in the main building. Here supervision is effected by monitoring the synchronising pulses.

The main and standby parametric amplifiers are mounted in separate containers inside the low-noise receiver cabin. This cabin has a movable floor which remains horizontal at any aerial altitude and is readily accessible for maintenance. Each container is completely removable for servicing without affecting the other.


Wideband TWTs

The transmitter uses wideband travelling wave tubes to provide a final peak saturation power output of 10kW, but in normal operation this power is limited to about 1kW to ensure that intermodulation between carriers is virtually eliminated and to avoid overloading the satellite.

The gain of each of the TWT stages is of the order of 30dB throughout the entire civil satellite communications band of 5,952MHz to 6,425MHz.

Two TWT amplifier stages are employed in series to provide a high power output capable of transmitting three separate telephony carriers, giving the capacity for up to 400 telephone channels. The standby transmitter can be used simultaneously to provide a television videocarrier and separate sound channels in addition to the telephony channel on the main transmitter.

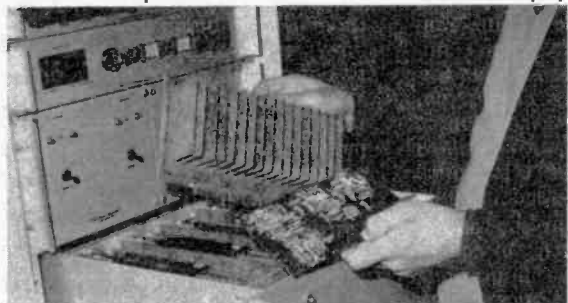Extensive provision of switched redundant equip-




A logic board—old style and new. 156 of the old ones are equal to the unit held in the technician's right hand. Here the "i.c." comes into its own again.



This is the logic equipment for the steering of Aerial No. 2. Technician John Austin is seen here inspecting one of the logic board modules.



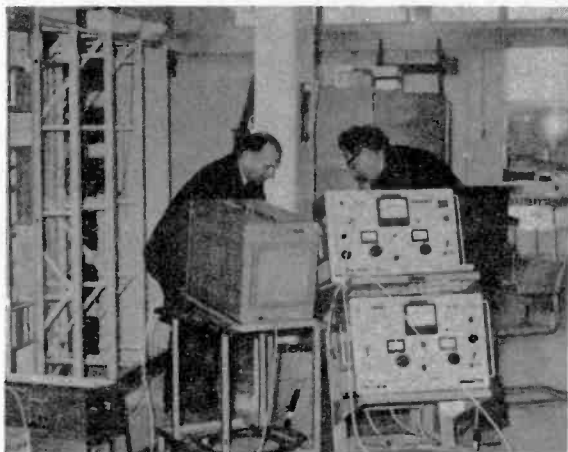The consul in the control tower for Aerial No. 1 which can be seen through the window in the background. Visibility is normally better than this but our reporter chose the one day Cornwall had snow for his visit to Goonhilly.



Here some of the Station engineers are repairing logic faults on the changeover equipment on the microwave link gear.

ment in the system and the comprehensive control facilities will ensure a high standard of reliability and enable maximum economy of operational manpower to be achieved.

Satellite tracking

The satellite is tracked using a beacon signal which it transmits itself. The signal from this beacon is separated from the communication carrier signals in the waveguide branching network and fed into the tracking receiver.

The tracking signal itself is derived from the rotation of the horn feed at the vertex of the dish to produce a conical scanning motion of the beam at the beacon frequency only. This conical motion, only 0.4 minutes of arc off centre, produces a modulation of the received beacon signal which reduces to zero when the beam is pointing directly at the satellite.

Key position

The Goonhilly Downs Post Office Radio Station has played an important part in the experimental and operational phases of satellite communications. With the completion of No. 2 aerial and the further modifications to the No. 1 aerial, it occupies a key position in the world-wide satellite communication network.

The latest developments in this field combine the high quality formerly available over submarine cables with the information handling capacity possessed by microwave links.



NEW NAME & Trade Mark



HOME RADIO (COMPONENTS) LTD

Formerly Home Radio (Mitcham) Ltd.



NEW ADDRESS & Phone No.

234-240 • LONDON ROAD • MITCHAM • SURREY • CR4 3HD

Telephone: 01-648-8422

Only 500 yds. from our old premises—but now we have much more space, much more stock!



NEW CATALOGUE



New catalogue? Well—yet another edition of the "old faithful" that for over eleven years has presented to an ever-growing army of enthusiasts the latest and best radio and electronic components. This latest edition is no exception to our policy of making every new edition better and bigger than the one before! It has no less than 330 pages, lists over 8,000 items, illustrating over 1,500 of them. With each catalogue you get a 30-page Price Supplement, a bookmark giving electronic abbreviations and an order form. All for only 8/6d plus 3/6d post, packing and insurance. Incidentally every catalogue contains 6 vouchers, each worth 1/- when used as directed.

POST THIS COUPON NOW

with your cheque or P.O. for 12/-




Please write your Name and Address in block capitals

Name

Address

I enclose 12/- for Components Catalogue
HOME RADIO (Components) LTD. Dept. PW,
234-240 London Road, Mitcham, Surrey, CR4 3HD

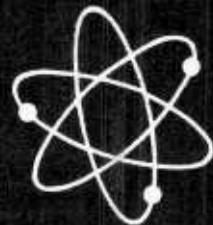**...but still the same old
SUPERLATIVE SERVICE**



AN INTEGRATED CIRCUIT STEREO AMPLIFIER

L. McNAMARA B.Sc.

THE G.E. (USA) audio amplifier I.C. type PA 222 was introduced to readers of this magazine in the article by A. J. McEvoy in the August 1968 issue, page 260. On that occasion the writer centred his attention on the circuitry of the unit, describing in detail the technical design features. It is now proposed to report on a fully developed practical application of this interesting component, a stereo amplifier with one PA222 in each channel.

The amplifier is intended for use on batteries (e.g. two PP9s in series, giving 18V) and to accept the signal from a crystal type gram pickup. That application implies a high-impedance input to the amplifier, and therefore a special preamp. stage before each PA222. (If the earlier article is consulted, it will be noted that the PA222 alone was found perfectly adequate for use from a medium-impedance source, or with a radio tuner; however, a matching stage is essential with a high-impedance source.)

In the prototype it was decided to employ an integrated circuit in the preamp. stage also, so that the complete project would be as up to date as possible, a true reflection of the state of the art as available to the amateur constructor in 1969.

A suitable I.C. for this application was found in the R.C.A. CA3036, which observant readers will identify as a development of the four transistor CA3018, introduced in the June 1968 issue of PRACTICAL WIRELESS.

The theory in brief

Since the theory of operation of each of the types of I.C. incorporated in this project has been dealt with in detail recently, only a brief résumé will be given for the benefit of new readers. First, the CA 3036. Assembled, like all monolithic I.C.s to date, on a silicon substratum, this unit is a variant of the CA3018 in that the four transistors are employed as two "super alpha pairs". It is common knowledge that this configuration implies a very high input impedance. Better still, the lower output impedance of the unit matches closely the requirements of the common emitter stage which forms the input element of the PA222.

It is worth noting an advantage of the CA3036 in this particular application (see Fig. 1) since both transistor pairs are formed simultaneously by the same process in the same crystal of silicon, it follows that they must be perfectly matched, to an accuracy much higher than is easily obtained with discrete transistors. The advantage in a stereo pre-amplifier, where one pair acts for each channel, is obvious. Similarly, the PA222s are manufactured under closely controlled conditions, so that as long as similar loudspeakers are used in the audio system, a balance control may be omitted.

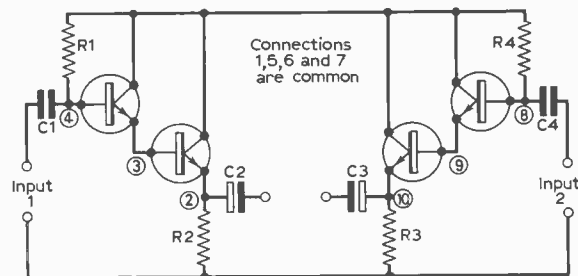


Fig. 1: The circuit associated with the pre-amplifier. The four transistors are in the I.C. CA3036.

The PA222 is a 1-watt audio amplifier housed in an 8-lead dual in-line epoxy package, and fitted to a heatsink tab to increase the permissible dissipation of the output transistors. For a full understanding of the operation of the unit it is advisable to consult the previous article, but the basic outline is quite simple.

In Fig. 2 it can be seen that Tr1 is a conventional common emitter amplifier, directly coupled to the phase splitter Tr2. Careful examination of the transistor pairs Tr4 and Tr5, and Tr3 and Tr6 will reveal the essential symmetry in their operation. Receiving opposite phases of the audio signal from the phase splitter, they amplify in class B as super alpha pairs in series connected single ended push-pull. There is then a high power, low impedance signal appearing at the emitter of Tr5, matching into a 25Ω loudspeaker. The diode serves to limit crossover distortion, and a.c. and d.c. feedback systems are provided.

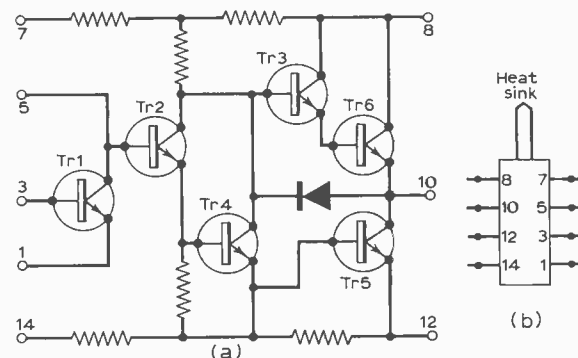


Fig. 2: (a) The internal circuit of the output stage PA222. (b) The connections to the I.C. package.

A complete stereo system requires not only high gain with matching to signal source and loudspeaker with symmetry between the two channels, but also tone and volume controls to match the characteristics of the system to the tastes of the listener. All

these elements are incorporated in the block diagram of the system, Fig. 3. It will be observed that the CA3036 preamplifier stage, which requires a power supply of 9V, is connected to the battery through a voltage dropper resistor.

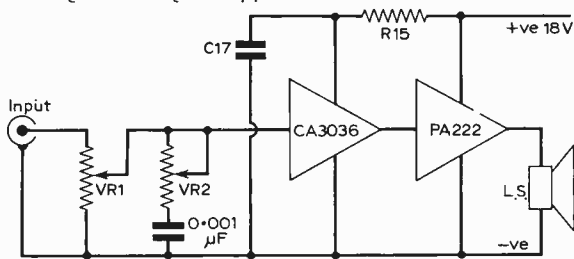


Fig. 3: Block diagram of each channel.

This component, with the associated capacitor C17, also serves to decouple the preamplifier from any variation in the voltage supply or audio leakage on the h.t. line; these effects could be quite marked otherwise, as there will be a considerable dependence of current consumption on volume level due to the class B mode of operation of the amplifier. Mention has already been made of the possible omission of a balance control on this amplifier, due to the high degree of symmetry between the two channels. Only one component may differ between the two, and that is the resistor in the collector circuit of the first transistor in each PA222, between pins 5 and 7 on the package.

This component is specified by the manufacturer on the basis of tests during manufacture, to choose the optimum operating conditions for the individual component. Since all the transistors in a PA222 are direct coupled, this resistor sets the currents drawn by each of them, and hence the whole operating conditions of the amplifier channel. Use of the appropriate value will ensure equal performance from each channel. The resistor will be 68kΩ, 100kΩ or 150kΩ, the value recommended is stamped on the epoxy shell.

Nonetheless it would be better if two PA222s could be obtained for which the same value is specified. In that case the channels will be completely identical from pick up cartridge to loudspeaker, so that a balance control to equalise the outputs should be unnecessary. Should one be

desired, though, it may take the form of a 5kΩ linear potentiometer, preferably wirewound, replacing R2 and R3 in the preamp. section. The slider should be earthed, while the other two are joined to the emitters of the transistors of the super alpha pair through 1.5kΩ resistors. Since the output of the preamp. is developed across these emitter resistors, a variation in the ratio of the two emitter resistors implies a variation in the relative amplitudes of the signals developed across them, and hence a "balance control" effect.

Since the completed unit can be made very small, mounting in a record player or other system should pose no difficulties; however, in view of the high input impedance, the same precautions as are employed with valve amplifiers are advisable to minimise hum pickup. Whereas a low impedance transistor amplifier can be used with quite long runs of unscreened cable without difficulty, it is advisable in this case to use screened leads from volume and tone controls if the amplifier is to be more than a few inches from the controls.

The constructor who completes this project can be satisfied that it is one of the most up-to-date devices available in terms of the components used; and further he will notice one of the chief advantages of the integrated circuit, that it permits the assembly of quite complex systems with the maximum assurance of success, since all active elements are carefully matched by the manufacturer, with close adherence to specifications. The variations, with resultant openings for malfunctions, which are associated with a similar project using discrete components, are all but eliminated. In short, commercial standards of quality control are assured, yet the constructor can still say: "I built it myself."

★ components list

Resistors:

R1 2.2MΩ	R9 10Ω
R2 4.7kΩ	R10 10Ω
R3 4.7kΩ	R11 See text
R4 2.2MΩ	R12 22Ω
R5 22kΩ	R13 180Ω
R6 See text	R14 10Ω
R7 22Ω	R15 8.2kΩ
R8 180Ω	

VR1 3MΩ log. twin gang. VR2 1MΩ lin. twin gang.
(See text for balance control; R2 and R3 are 1.5kΩ with a 5kΩ linear wirewound potentiometer.)

Capacitors:

C1 0.04μF	C10 125μF
C2 10μF	C11 0.001μF
C3 10μF	C12 10μF
C4 0.04μF	C13 0.001μF
C5 0.001μF	C14 10μF
C6 10μF	C15 0.001μF
C7 0.001μF	C16 125μF
C8 10μF	C17 1000μF
C9 0.001μF	

Miscellaneous:

IC 1 CA3036, R.C.A. } Available from
IC 2 and 3 PA222, G.E.(USA) } Henry's Radio
Loudspeakers, two identical, 25Ω impedance. On/off switch, printed circuit board, wire, etc.


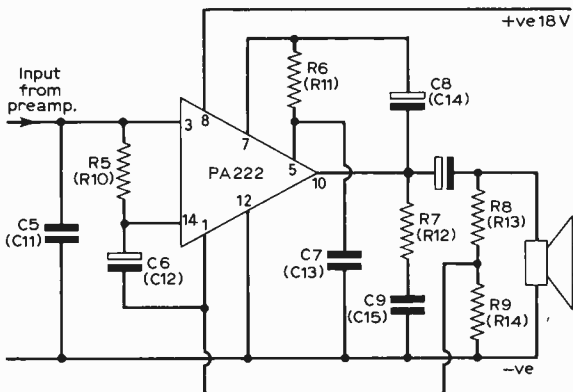


Fig. 4: The circuitry associated with each output stage. The component numbers in brackets refer to the other channel. The unmarked capacitor between Pin 10 and the loudspeaker is C10 (16).

RADIO STETHOSCOPE

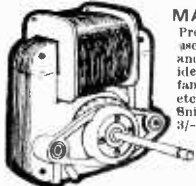Easiest way to fault find—traces signal from aerial to speaker—when signal drops you've found the fault. Use it on Radio, T.V., amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. 29/6—twin stetho-set instead of earpiece. 11/- extra—post and ins. 2/9.



MAINS MOTOR

Precision made — as used in record decks and tape recorders—ideal also for extractor fans, blower, heater, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered. 12 and over post free.



ROTISSERIE MOTOR

Very powerful 7 r.p.m., operates from standard A.C. mains. 29/6, plus 3/6 p. & p.



230 VOLT SOLENOID

1in. stroke. Size 2 1/2in. x 2in. x 1 1/2in. 14/6, postage 2/9.



SNIPERSCOPE

Famous war-time "cat's eye" used for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up like a cathode ray tube when the electrons released by the infra-red strike it. A golden opportunity for some interesting experiments. 7/6 each, post 2/6. Data will be supplied with cells, if requested.

MAINS TRANSFORMER SNIP

Making a power pack for amplifier or other equipment? These transformers have normal mains primaries (230/40 v.) and isolated secondaries two types (1) 12 v. 500 mA. at 8/6; (2) 15 v. 500 mA. at 8/6.



SPRING COIL LEADS

as fitted to telephones. 4 core 2/6 each, 3 core 2/- each.



PP3 ELIMINATOR. Play your pocket radio from the match save £s. Complete component kit comprises 4 rectifiers—minus dropper resistances, smoothing condenser and instructions, only 6/6 plus 1/- post.

AC FAN

Small but very powerful mains motor with 6 1/2in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6, post 4/6. Mounts from back or front with 4BA screws.



TRANSISTOR SET CASE

Very modern cream cabinet, size 5 1/2 x 3 1/2in. with chrome handle, tuning knob and scale. Price 4/6 plus 2/- postage. Printed circuit board for this case 2/6.



SOIL WARMING ELEMENT. 30 yards, heavy PVC covering. 12/6.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

ELECTRIC TIME SWITCH



Made by Smiths these are AC mains operated, NOT CLOCKWORK ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours. 5 amp changeover contacts will switch circuit on or off during these periods. 59/6, post and ins. 4/6. Additional time contacts 10/- pair.

VARYLITE

Will dim fluorescent or incandescent lighting up to 600 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob £3.18.6.




NICAD RECHARGEABLE BATTERIES



3-6V 300mA size 1 1/2 x 1 1/2in. dia. type ref. DKZ500 really powerful will deliver 1 amp for 2 hours. Regular price 32/6 each, price 16/6 each. New and guaranteed. Other voltages available, single cell 1-2V 6/8, 5 cell 6V 29/6.

ELECTRIC CLOCK WITH 20 AMP SWITCH

Made by Smiths these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another timer or alarm—this may be set in minutes up to 4 hours. At the end of the period a bell will sound. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 45/-, less than the value of the clock alone—post and insurance 2/9.

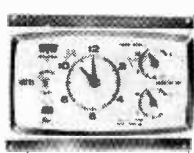

THIS MONTH'S SNIP

Recording Tape

Quadruple tape on 3in. spool giving 800ft. Of the finest quality by very famous maker. Especially suitable for message tapes and portable equipment. Regular price 36/- per spool. Our price 7/6 plus 2/9 p. & p. or 3 for 22/6 post paid.


HI FI BARGAIN

FULL FI 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi loud and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—specific 3 or 15 ohms—Main resistance 60 c.p.s.—Chassis Diam. 12in. x 12in. on mounting lugs—Baffle hole 11in. diam. Mounting holes 4, holes—1in. diam. on pitch circle 1 1/2in. diam.—Overall height 5 1/2in. A 65 speaker offered for only £3.9.6 plus 7/6 p. & p. Don't miss this offer. 16in. 50 watt £7.19.6.



DRILL CONTROLLER

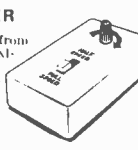Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6 plus 2/6 post and insurance. Or available made up 29/6, plus 2/6 post.



PROCESS TIME CONTROLLER



Made by Smiths, motorised and mains driven, enables 13A circuit to be started up to 18 hours in advance and to stay on for a period from 15 minutes to 3 hours. Totally enclosed in metal box with glass front and chrome surround. 49/6 plus 4/6 post and ins.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

REED SWITCH

suitable for dozens of different applications, such as burglar alarms, conveyor belt switching. These are simply glass encased switches which can be operated by a passing permanent magnet coil. A special buy enables us to offer these at 2/6 each, or 24/- a dozen. Suitable magnets are 1/- each.

MOVING COIL METER BARGAIN

Panel meters are always being needed and they are jolly costly when you have to buy them in a hurry—so you should take advantage of this offer: 2in. moving coil flush mounting meters only 9/6. These are actually R.F. meters and cost about £2 each but if you don't want them for R.F. then all you have to do is to remove the thermocouple and you will have a 2-3 ma. meter which you can make into almost anything by adding shunts or series resistor. New and unused.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/6. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

Multi Purpose Neon Test Unit. Robust, useful and instructive, tests insulation, capacity, continuity, resistor, volume control, also acts as signal injector and L.T. fault finder. Kit comprises neon indicator, 4-way wafer switch, ebony tubes, resistors—condensers, terminals etc., with diagram. Only 9/6, plus 2/- post and insurance.

Tuning Condenser. solid dielectric .0005mfd. variable 2/6 each. 24/- dozen.

A.E.I. Fractional H.P. Motor. 200/250 v. 50/60 c.p.s. enclosed, continuous rating 1/40 h.p., ex. equip. Perfect order, 19/6, plus 4/6.

Experimenting with ultra violet? Philips U.V. lamp. 16/6; holder and control gear 19/6.

G.E.C. Black Light Tube for experiments and special lighting effects—40 watt 2ft. tubes only 14/6 each; holders and control gear. 19/6, plus 4/6 post.

Clock Motor. 230v. 50 c.p.s. synchronous—self starting. 6/6.

Pentode Output Transformer. standard size, 40-1, ex-equipment but OK. 4/3 each. 43/- doz. Post paid.

E.H.T. Condenser. 0-1 mfd. 5 kV. 8/6 each.

Neon Mains Tester. 1/3 each. 12/- doz.

Flood Lamp Control. Our dim and full switch is ideal for controlling photo flood lamps; it gives two lamps in series, two lamps full brilliance and lamps off. Similar control of other appliances can be arranged where used in pair or where control can be split exactly in half. Technically the switch is known as a double-pole change over with off. Our price 4/6.

Sub-Miniature Silicon Diodes. general purpose type with gold-plated leads. 1/- each or 7/6 per dozen.

Measure Tapes. 25ft. Tape on 3in. spools normally 4/- each. we offer 4 tapes for 12/6.

White Circular Flex. ideal for lighting drops, twin made by BICC. Usually 8d. yd., 100 yd. coil for 30/-, plus 6/- postage.

Edgewise Control. Mergantite, as fitted many transistor radios. 2K or 5K with switch. 2/6 each or 24/- per dozen.

12V Inverter. Full transistorised for operating a 20-watt fluorescent tube, size 6in. long x 1 1/2 x 1 1/2. Post and insurance 3/6.

Silicon Rectifier. Epimix BY100 750mA 400V. 10 for 20/-.

Miniature Pickup for 7in. records made by "omnicode". crystal cartridge with sapphire stylus only 3/9 or 36/- dozen.

Headphones. EA. With unused and perfect, low resistance. Single with headband 4/6. Double with headband 8/6.

Midget Neons for mains indicators, etc., 1/8 each or 12/- dozen.

Compression Trimmers. Twin 10uF. 1/- each; 9/- per dozen.

3in. PM Loudspeakers. 4 ohm. 12/6; 8 ohm. 13/6.

Rotary Cam Operated Switch. 12 positions each of which close a separate pair of contacts except the last which leaves them all open. Contacts rated at 250V 16 amps. 15/- each.

Rotary Cam Operated Switch. 4 positions: 1st position all contacts open; 2nd contact 1 closed; 3rd contacts 1 and 2 closed; 4th contacts 1, 2 and 3 closed. Contact rated 250V 16 amps. 8/6 each.

Pocket Test Meter. measures AC volts (3 ranges), DC Volts (3 ranges), ohms, milliamps. ideal to carry around. Complete with instructions and test leads. 39/6 plus 2/6 p. & p.

Breast Microphone. Fine American made dynamic type, adjustable on breast plate with neck straps. 7/6, post 4/6.

Circular Fluorescent. 22 watt, 9in. diam. tube complete with choke, starter, holders and chrome clips. 29/6, post, each, 4/6.

Midget Relay twin 250 ohm coils, size approx. 1 1/2in. x 1in. x 1in. 4 pairs changeover contacts. 7/6 each.

Printed Circuit Board, Edge Connector, solder terminations. 32 contacts, standard spacing for veroboard, etc. 6in. long but easily cut. 7/6 each. 80/- doz.

1.000W Fire Spiral. replacement for most fires, 1/3 each, 12/- doz.

50 ohm 50 watt Wire Wound Pot-meters. 8/6 each.

1 Meg Miniature. Pot-meter Mergantite standard 1in. spindle 1/- each; 9/- per dozen.

1 Meg Miniature. Pot-meter Mergantite preset screwdriver control. 9d. each; 8/- per dozen.

Pre-Set 100K by Welwyn with intrinsic bakelite knob. 1/- each; 9/- per dozen.

100K Pot-Meter. Miniature type with double pole switch and standard 1in. spindle, by Mergantite. 2/- each; 18/- per dozen.

Battery Motor 1 1/2in. long, 1in. dia., operates from 3V upwards, reversible, speed variable by changing voltage or resistance 4/6 each, 50/- doz.

Thermal Relay. Can be used to delay the supply of HT while heaters warm up, or will enable 15A loads to be controlled by miniature switches or relays. Regular list price over £2. price 7/6 each.

Siemens High Speed Relay. Twin 1.0 ohm coils. Platinum points change-over contacts—Ex equipment. 8/6 each.

Toggle Switch Bargain. 10A 250V normal one hole fitting 2/9 each; or 30/- per doz.

Electric Lock. 24V coil, but rewindable to other voltages. 4/6 each.

ELECTRONICS (CROYDON) LTD
Dept PW 266 London Road, Croydon CRO-2TH
Also 102/3 Tamworth Road, Croydon

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:

NAME Block

ADDRESS Caps.

..... Please
5/69

BRITISH NATIONAL RADIO SCHOOL

Field-effect Transistors at Realistic Prices

2N 3819 N-channel. RF Amplifier. Low Noise.	10/- each (5 or more 9/6 each)
2N 3820 P-channel. Complement to 2N 3819.	17/6 each (5 or more 16/3 each)
2N 3823 N-channel. V.H.F. Amplifier.	33/6 each (5 or more 28/6 each)
BFW 10 N-channel. V.H.F. Amplifier.	45/- each (5 or more 39/- each)
MPF 102 N-channel. V.H.F. Amplifier.	8/- each (5 or more 7/6 each)
MPF 103 N-channel. AF Amplifier.	7/9 each (5 or more 7/3 each)
MPF 104 N-channel. AF Amplifier.	7/9 each (5 or more 7/3 each)
MPF 105 N-channel. AF Amplifier/Switch.	7/9 each (5 or more 7/3 each)
MFE 2094 N-channel. AF Amplifier/Switch.	31/8 each

All of the above items are Ex-stock delivery at 31/8/68.

All components offered for sale are guaranteed to be brand new first grade items only. All items are subject to the guarantee terms of their individual manufacturer, where applicable.


M. R. CLIFFORD & COMPANY (PW)
Component Stockholding Services
66, Old Oscott Lane,
Great Barr, Birmingham, 22A.

Terms: C.W.O. MAIL ORDER ONLY. (Nett monthly a/c to approved accounts).
Suppliers to: Government and Educational Establishments, H.M. Forces, etc.
Please add 2/- postage and packing per order.

SILICON TRANSISTORS. EX-STOCK—many others available.

BC 107 3/6	BC 172 3/2	2N 697 5/-	2N 3704 3/8
BC 108 3/-	BC 173 3/9	2N 706 2/6	2N 3705 3/2
BC 109 3/6	BC 182L 4/-	2N 706A 3/2	2N 3706 3/7
BC 115 10/-	BC 183L 3/3	2N 2926 2/6	2N 3707 3/10
BC 116 12/-	BC 184L 4/9	2N 3053 6/-	2N 3708 2/6
BC 167 3/-	BFY 50 5/3	2N 3054 15/6	2N 3709 2/4
BC 168 2/6	BFY 51 4/4	2N 3055 21/-	2N 3710 2/7
BC 169 2/9	BFY 52 5/3	2N 3391A 7/-	2N 3711 3/-
BC 170 3/-	BFY 53 4/4	2N 3702 3/6	2N 3793 3/3
BC 171 3/8	BSY 95A 3/9	2N 3703 3/2	2N 4292 3/3

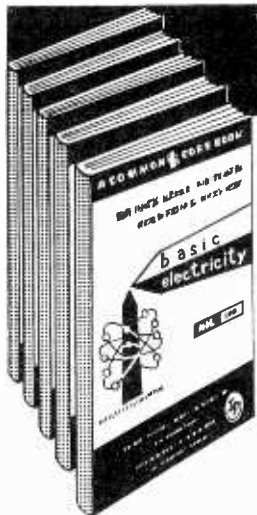We are also an Electronics Agency (960 page Catalogue 16/6 post free)



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

"They certainly confirm everything your readers say about them and I am more than delighted with them. They will be of great value to me in my job as Hospital maintenance electrician." A. B., Birmingham.

"I am entirely satisfied with the books, they are everything you claim them to be." S.S., Cardiff.

"An extremely marvellous set of books." C.B., London

A TECH-PRESS PUBLICATION

POST NOW FOR THIS OFFER!!

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts, BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 15/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY ☐ BASIC ELECTRONICS ☐

Prices include Postage and Packing.

Signature (If under 21 signature required of parent or guardian)

NAME
BLOCK LETTERS

FULL POSTAL
ADDRESS

LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents.

My mistake

I was very surprised that my letter was so badly taken, but I realise that this was due to my being very ambiguous. I apologise to Mr. Parkinson, Mr. Thompson and Mr. Kojminihi for misleading them, but I must thank Mr. K. Smith for his obvious understanding of the matter.

I have every intention of getting a full licence, but unfortunately I did not take the wise course used by G3XJB, that of getting his Ticket before taking his "O" Levels (may I wish him and all the rest of us who may be concerned the very best of luck in the exams), but I sincerely hope to alter this soon, and hope to take the RAE next summer. If I pass I sincerely hope he will NOT remove his PA valve as he threatens.

As Mr. Smith so accurately puts it (ESP?) our headmaster has a strong tendency to put school studies "next to God" (several of my friends had been "advised" to discontinue their extra curricular studies, lest it interfere with their work, and lessen their chances of success in the summer), and our Physics teachers weren't over-enthusiastic about the idea of starting an Amateur Radio Club, although they are willing to give us whatever help they can. It is at such places that I consider the Novices' Licence would be of very great use, as the club can be operated during the lunch hour and after school, and as such is a perennial project.

Pupils who would not otherwise have the opportunity of experiencing Amateur Radio at its best can do so, and by adding a few suitable rules, e.g. make the Morse test compulsory for all people wanting to transmit, it should be possible to sort the "weeds from the flowers". Also, as the RAE is basically a cross between the "O" and "A" levels in Physics, I see no reason why the pupils should not get their Ticket gradually. It is also my firm belief that the one subject complements the other, which is why I consider Amateur Radio to be a hobby with many useful "side-effects".

I am therefore wholly in favour of the Novices' licence, or anything similar, if it is used in this way. I do NOT think that it should be run on the same lines as the "great" American Citizens Band.—C. Williams A5376 (Staffordshire).

"AA" licence

I note that the argument(s) about the once proposed "Beginner's" Licence still goes on. I have once put it to you that a return to the pre-war "Artificial Aerial" Licence would be a good thing and you were kind enough to reply saying that you had already approached the then PMG on this subject with little avail. May I now suggest that a "Beginner's" Licence could take the same form as that as for a Driving Licence? If an enthusiast who, although capable of constructing a Tx but is not yet ready for the RAE could enroll the aid (either through his club or otherwise) of a licensed "Ham" to watch over him whilst working the rig then the problem would become easier. I have personally constructed a 40 watt rig and three friends with current licences are all prepared to work it "Stroke A". This means that when (or IF) I get a ticket I shall have all the "gen" at my finger tips. The "L" driver, if he fails his first test goes on until he does pass. Why not in radio?

I should make it quite clear that although I have built a Tx it is not ready to go on the air—this contravenes GPO regulations, or so I believe.—H. W. Boyett, BRS 30526 (Sussex)

Nothing false about this

Reading through previous copies of PRACTICAL WIRELESS I came across, in the Amateur Bands column, a note about false logs. Mr. Gibson also mentioned a report received on something like an OC71 into three OC72s being impossible.

I obtain good reception of the Amateurs with my receiver which is a crystal set into a one-transistor amplifier stage into a four-stage amplifier. To crown it, I use a Band III television aerial and the central heating system as an earth.—B. Beord (Hampshire).

An appeal

I would like to appeal for copies (no matter how old) of PRACTICAL WIRELESS, *Practical Electronics* and any other radio magazines for use by children in the Nunthorpe County Modern School, Middlesbrough.

I am sure that many readers will be pleased to encourage this interest

and hope the children will receive as much enjoyment from reading the old magazines as their original owners did when they were new.—G. M. Bartram, Head of Science Department (Nunthorpe County Modern School, Middlesbrough).

From the Opposition Benches

I am heartily sick of reading letters from people who want transmitting licences without the trouble of taking a Morse test, and would like to express an opinion from the Opposition Benches.

Far from abolishing this test, the required speed should be raised to 20 w.p.m. for, as you are well aware, the issue of a licence is not only for one's pleasure but also to enable one to train oneself to become a radio operator in the service of his country should a national emergency arise.

The crowd of "Big Jessies" who natter on for hours on the mike and never touch a key once they have got their ticket are doing nothing at all towards this end for if "telephonists" are ever required in a hurry, female voices are far more suitable for this purpose and furthermore, women could be trained to do the job in a matter of hours.

I would like to see telephony of all kinds totally abolished from 15, 20, 40 and 80m and restricted to 70cms, 2m, 10 and 160m only. This would not only leave the DX bands clear for the *real* radio operators but might also solve the problem of non-activity on 70cms and 2m and prevent these being taken from us for that reason.—W. Morris, G4HU (Cheshire).

An old friend

I was looking through some old pre-war radio magazines and QSLs the other day, when I came across a photograph of BRS 1724 and his short wave outfit. I guess the picture was taken between 1932 and 1934. It has the name F. C. Holwill, Dartmouth, impressed on the bottom of it (I expect this is the name of the photographer).

I should like to locate BRS 1724 if possible and send the photograph to him as he might be interested in it.—F. G. Sadler (19 Kithurst Crescent, Goring-by-Sea, Sussex).

LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents.

The fictitious "hole"

While I thoroughly appreciate B. R. Meredith's predicament concerning the fictitious "hole", (P.W. March 1969), might I suggest that it stems from our inability to sufficiently express abstract ideas in our all-too-concrete language. To start with, the concept of energy moving and expressing mass is impossible to conceive in anything but mathematical reasoning. So we build up a theory of particles we can hold in our imagination. It is easy to think of orbits each capable of maintaining fixed energy levels, which when filled constitute a perfect electrical balance. (Where our "concrete" particle is, three dimensionally, during its transit from one orbit to another when it radiates or absorbs its quantum of energy is just as hard to understand as our "hole". Does it momentarily cease to exist in our space, or is it a fault inherent in the picture.) It is when this balance of charges is disturbed that we experience electrical phenomena. The presence of extra electrons we choose to call a negative charge. Extra gaps appearing in an orbit we call positive.

We find no difficulty discussing a hole in our bank balance as an overdraft, making it a tangible reality. Negative figures in everyday life are added together or moved from one record to another with such ease that no one needs to explain the movement of these deficiencies.

When the particle has been classified as a negative though, by reasoning, its deficiency, a minus negative, can only become positive. The fault of reasoning is therefore one of nomenclature. Were electrons classified as positive, their deficiencies, or "holes" would be negative and no one need ever make the mistake of imagining they are "nothings which are current carriers".—L. G. A. Green (*Peterborough*).

Ouch!

I am writing to ask whether or not it is possible to publish articles of a more intellectual nature in both your PRACTICAL WIRELESS and Practical Electronics magazines. Do you have to treat all your readers like blithering idiots, because I am sure a child with an IQ of minus 2

could understand your magazine in its present form.

I am sorry to be so blunt, but it seems to me that all your articles are of a descriptive nature, why? I can only conclude by saying that I think that one of your authors in a recent issue has just guessed the values of the components used in his simple circuit.

I appreciate the fact that these magazines are for the Practical application of electronics as the names suggest, but this does not mean "spoon-feeding" the readers.

—M. Floyd (*Berks.*)

[Really, Mr. Floyd! Fancy associating with —2 IQ morons by reading P.W. If you want the intellectual stuff try The New Statesman.—Editor.]

Hello, hello, hello!

Reference G3WVR and his echo effects on the air.

It seems to me that the average Amateur of today forgets two things as quickly as possible once he has obtained his licence. First, Licence Conditions, and secondly c.w. The latter is understandable the former unforgivable.

If this "Wet behind the ears" Amateur requires to experiment in this manner I suggest that he gives up the idea of ever becoming an Amateur, throws away that B.Sc., lets his hair grow, takes drugs, and joins one of those ill-mannered "groups", who, I feel sure, will appreciate his efforts to produce peculiar sounds. Those of us who can still carry out experiments in the true sense, and have long and enjoyable QSOs (both on the key and mic.) have no time for this type in our ranks.—B. J. Clark, G3BEC (*Hon. President, Yeovil Amateur Radio Club*).

All you need is willpower

Having followed with interest the "battle" in your columns between those advocating a "Beginner's Licence" and their critics, I feel I should offer my opinion. I am one of the many schools' pupils who are about to sit "O" Level Examinations: consequently it is necessary that I revise as much as five years' work. Nevertheless I have found adequate time to pass the RAE and the GPO Morse test—with which I might add that I am all in favour—and take out an Amateur Sound Licence (A), while keeping up a

fairly reasonable standard both at school, and at various out-of-school activities. Living in "the wilds" as I do, I have been unable to join a radio club and benefit from its advice and guidance. My studies for the RAE were therefore with the aid of the usual text-books, and also occasional visits to an experienced and very helpful Amateur.

Armed with a licence, then, I began hesitantly to operate—and ran into most of the well-known problems—TVI, aerial loading, shortage of cash, to mention but a few, and above all, inexperience. However, having solved some of these, I made my first contacts on c.w. I believe that were it not for the compulsory Morse test, many people would ignore c.w. as a mode of transmission, and in doing so completely sacrifice an efficient, simple, interesting, and—most important—cheap means of communication.

In my experience, limited though it may be, there should be no reason why someone with sufficient will power and enthusiasm should not pass with relative ease the RAE and the GPO Morse test, even when bound by inevitable commitments and examinations.

I think Amateur Radio is a marvellous hobby. It is one of the few pastimes which is enjoyable, relaxing and yet educational in so many ways.—D. M. Holburn—15 G3XZP (*Wolsingham, Co. Durham*)


[We must now close the subject of the Beginner's Licence, so no more letters on that subject please.—Editor]

Stop press

The author of the article "A Six Transistor F.M. Tuner," part 2 of which appeared in the March issue, has asked us to publish this additional note on alignment:

In isolated cases the tolerance of the capacitors in the oscillator tuned circuit may be such that some difficulty may be found in tuning the i.f. end (Radio 2) owing to insufficient capacitance. The simple way to overcome this is to increase the inductance of L4 by screwing in a dust iron core. The core should be made vibration proof by using either a core locking compound, or a thin piece of rubber band screwed in with the core.

Sinclair

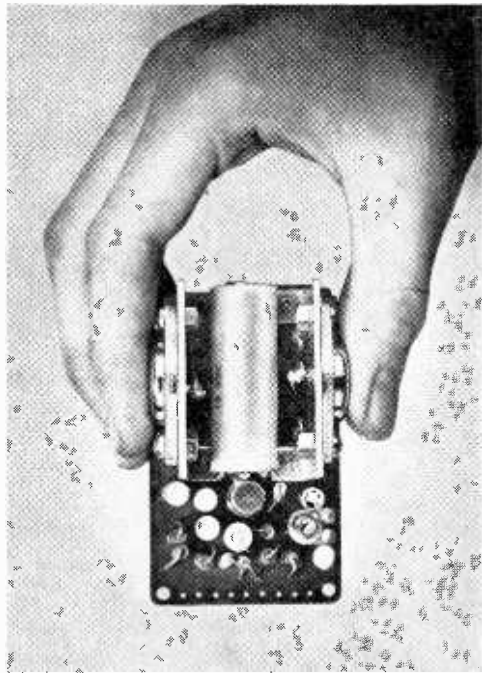

Z.12 - for all you want from any amplifier

The Z.12 is a most versatile integrated amplifier and pre-amp in which power, compactness and true high-fidelity standards are combined within a unit of very modest price. The most widely used unit of its kind in the world, the Z.12 has an output of 12W R.M.S. continuous sine wave (24W peak) or 15W music power (30W peak). It has Class B ultralinear output which can be fed into any loud-speaker from 3 to 15 ohms. (Two 3 ohm speakers can be used in parallel.) Frequency response—15 to 50,000Hz $\pm$ 1dB; input sensitivity—2mV into 2 kilohms. The Z.12 will operate from any power source between 6 and 20V d.c. As such,

a car battery or the PZ.4 are eminently suitable, giving much wider than usual scope in the applications to which the Z.12 may be put. As well as hi-fi, these include systems for P.A. electronic guitars, organs, intercom systems, laboratory, education or industry. You will find the Z.12 in use in such instances again and again. The Sinclair Z.12 is supplied ready built, tested and guaranteed complete with manual of circuits and instructions for matching it to your precise requirements. Two may be used in stereo when, with the Stereo 25 and PZ.4 together with two Q.14s, you will have an ideal high fidelity assembly.


89/6

Q.14 - the unique loudspeaker

New materials and original design techniques have been used to produce a speaker of fantastic quality at a most attractive price. Experts and reviewers have enthusiastically endorsed its performance. The shape and size of the Q.14 make it far more adaptable to its environment than is the case with conventionally styled speakers so that it is much easier to position this speaker in the room in which it is to be heard. The Sinclair Q.14 has a substantially flat frequency response

from 60 to 16,000Hz and outstandingly good transient response. It will comfortably handle up to 14W loading and is positively brilliant in stereo. Measuring 9 $\frac{1}{2}$ in. square by 4 $\frac{1}{2}$ in. deep, this loudspeaker is finished in matt black with solid aluminium bar trim.

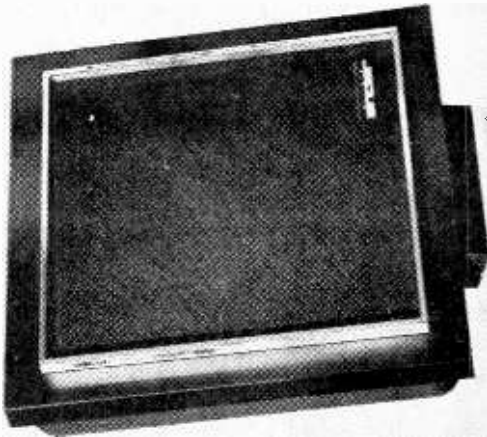Try the Q.14 in your own home without delay. If you are not delighted with it, your money, including cost of return postage to Sinclair, will be refunded immediately.



£7.19.6

Stereo 25 de-luxe pre-amp/control unit

This is a very elegantly styled unit, which, although designed basically for use with the Z.12, is readily adaptable for use with any high quality power amplifier system. The switched input selector allows for Pick-up, Radio and Auxiliary and there are controls for bass cut and lift, treble cut and lift, volume and stereo balance. P.U. input is equalised to R.I.A.A. curve

from 50 to 20,000Hz $\pm$ 1dB and the instructions manual provided gives matching details for pick-ups, shows how to connect up, etc. The front panel of the Stereo 25 is finished in brushed and polished aluminium embellished in black. The control knobs are in solid aluminium to match. Size 6 $\frac{1}{2}$ x 2 $\frac{1}{4}$ x 2 $\frac{1}{2}$ in. plus knobs. Supplied built, tested and guaranteed.

£9.19.6

PZ.4 - stabilised power supply unit

Designed specially to meet the power requirements for an assembly of two Z.12s and the Stereo 25, this heavy duty transistorized power supply unit has stabilised output of 18V d.c. at up to 1.5A. It is for a.c. mains operation 200/250V.

Supplied built, tested and guaranteed.

99/6

SINCLAIR MICROMATIC

Whether you buy your micromatic in kit form or built ready for use, you must not deny yourself the thrill of owning this fantastically small British receiver. Smaller than a matchbox, it has power range and selectivity that must be experienced to be believed. The high quality magnetic earpiece supplied with the set ensures excellent reproduction indoors and out. The Micromatic tunes over the medium waveband and has A.G.C. to counteract fading from distant stations. Bandpass tuning makes reception of Radio 1 easier; in fact you will find this set performing in some cases where other sets cannot be heard at all. The Micromatic is housed in a neat black case given an elegantly modern appearance by the attractive aluminium front panel and matching tuning control.

Kit in fitted pack with magnetic earpiece, instructions and free solder.

49/6

Built, tested and guaranteed, inc. magnetic earpiece.

59/6

Mallor Mercury Cell type RM.675 (2 required) 2/9 each

YOUR SINCLAIR GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us your money will be refunded in full at once and without question. For details of our guarantee available to all purchasers.

Goods sent post free in U.K. and Overseas by surface mail. Air-freight charged at cost.

Please send POST FREE


NAME

ADDRESS

For which I enclose cash/cheque/money order

PW5.69

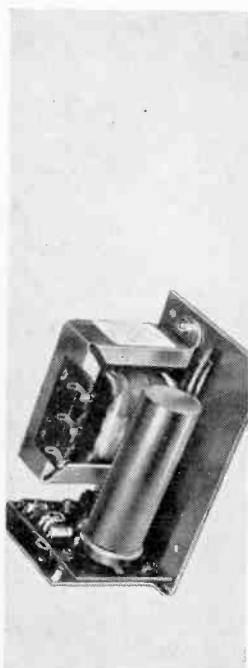SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE OCA-3 52731



The world's smallest personal radio

sinclair

ORGAN BUILDERS! SILICON N.P.N. TRANSISTORS TESTED AND APPROVED BY DESIGNER FOR USE IN "PRACTICAL ELECTRONICS" ORGAN CIRCUIT—1/6 each or £5 per 100.

LATEST LIST OF TRANSISTOR STOCK. ALL BRAND NEW AND TO MANUFACTURERS SPECIFICATIONS

NKT11 9/3	NKT402 19/3	BFX86 6/8	2N2221 8/8
NKT12 7/3	NKT403 16/-	BFX87 8/-	2N2221A 10/-
NKT13 5/-	NKT404 19/3	BFX88 7/3	2N2222 10/9
NKT124 8/6	NKT405 14/9	BFY50 5/-	2N2222A 12/6
NKT125 5/9	NKT406 13/3	BFY51 4/6	2N2297 9/3
NKT126 5/-	NKT420 40/-	BFY52 5/-	2N2368 4/6
NKT135 5/-	NKT451 13/3	BFY53 4/6	2N2369 4/6
NKT137 6/8	NKT452 12/8	BFY90 29/6	2N2389A 5/-
NKT210 5/9	NKT453 8/-	BSX19 4/6	2N2483 8/6
NKT211 5/-	NKT603F 6/6	BSX20 4/6	2N2484 10/9
NKT212 5/-	NKT613F 7/3	BSX60 16/6	2N2220A 10/9
NKT213 6/8	NKT674F 4/6	BSX61 10/-	2N2904 10/9
NKT214 4/6	NKT677F 5/8	BSY95A 3/9	2N2904A 12/-
NKT215 5/-	NKT713 5/-	2N686 5/-	2N2905 15/6
NKT216 10/-	NKT717 8/-	2N697 5/-	2N2905A 18/-
NKT217 10/9	NKT734 5/-	2N706 3/-	2N2906 12/6
NKT219 5/-	NKT736 6/6	2N706A 3/-	2N2906A 13/3
NKT223 5/9	NKT773 4/6	2N708 4/6	2N2907 14/-
NKT224 4/6	NKT781 5/-	2N709 11/8	2N2907A 20/9
NKT225 4/6	NKT10419 5/-	2N914 5/-	2N3053 5/9
NKT229 5/-	NKT10519 5/9	2N918 11/6	2N3055 20/9
NKT237 7/3	NKT10339 6/6	2N929 7/3	2G345 4/-
NKT238 4/6	NKT10439 7/3	2N930 8/-	2G371 4/-
NKT239 5/8	NKT12329 11/6	2N1131 8/8	2G378 4/-
NKT240 4/6	NKT12429 14/-	2N1132 10/-	OC22 10/-
NKT241 4/6	NKT13329 5/-	2N1302 4/6	OC204 6/-
NKT242 3/-	NKT13429 5/-	2N1303 4/6	OC44 6/-
NKT243 14/-	NKT13529 22/3	2N1304 5/-	OC45 6/-
NKT244 3/-	NKT16229 11/6	2N1305 5/-	ASZ17 10/-
NKT245 3/9	NKT20329 12/6	2N1306 6/6	
NKT261 3/9	NKT20339 8/6	2N1307 6/6	Quantity
NKT262 3/9	BC107 4/6	2N1308 8/6	Discount:
NKT264 3/9	BC108 3/-	2N1309 8/6	25/49 5%
NKT271 3/9	BC109 4/6	2N1613 5/9	50/59 10%
NKT272 3/9	BCY55 70/-	2N1711 6/8	100/299 15%
NKT273 3/9	BCY70 5/3	2N1893 12/6	300/999 20%
NKT274 3/9	BCY71 8/-	2N217 7/3	1,000 25%
NKT275 3/9	BCY72 4/6	2N217A 15/6	
NKT281 5/-	BDY20 22/3	2N2218 8/6	
NKT302 16/6	BFX29 11/6	2N2218A 10/-	
NKT304 13/3	BFX30 13/3	2N2219 10/9	
NKT351 11/6	BFX84 6/8	2N2219A 12/6	
NKT401 18/-	BFX85 8/-	2N2220 7/3	all one type

UNMARKED TRANSISTORS (tested) similar to:
2N753 1/6, BSY28 1/6, BSY65 1/6, OC44 1/6, OC71 1/-, OC72 1/-.
LIGHT SENSITIVE TRANSISTORS (similar to OC71) 2/- each.
ORP2 CADMIUM SULPHIDE LIGHT-SENSITIVE RESISTORS 9/- each.

GIANT-SIZE SELENIUM SOLAR CELLS—PRODUCE UP TO 6mA AT 6 VOLTS FROM DAYLIGHT! 67mm. diameter 10/- each.
50mm. x 37mm.. 2 for 10/-.

MULLARD POLYESTER CAPACITORS FAR BELOW COST
PRICE: 0.001µF 400V 3d., 0.0015µF 400V 3d., 0.0018µF 400V 3d., 0.0022µF 400V 3d., 0.01µF 400V 3d., 0.15µF 160V 6d., 0.22µF 160V 6d., 0.27µF 160V 6d., 1µF 125V 1/-.

RECORD PLAYER CARTRIDGES, COMPLETE WITH NEEDLES
GP67/2 Mono 15/-, GP91/3 Compatible £1, GP93/1 Crystal Stereo 25/-, GP94/1 Stereo Ceramic 25/-.

TRANSISTORISED SIGNAL INJECTOR KIT 10/-.
SIGNAL TRACER KIT 10/-. **CAR REV. COUNTER KIT 10/-.**

VEROBOARD

21 x 1" 0.15 matrix 1/3 5 x 3" 0.15 matrix 5/8 31 x 3" 0.1 matrix 4/9
31 x 2" 0.15 matrix 3/3 17 x 2" 0.15 matrix 11/- 5 x 2" 0.1 matrix 4/7
31 x 3" 0.15 matrix 3/11 17 x 3" 0.15 matrix 14/8 5 x 3" 0.1 matrix 5/6
5 x 2" 0.15 matrix 3/11 31 x 2" 0.1 matrix 4/2

Spot Face Cutter 7/6. Pin Insert Tool 9/6. Terminal Pins 3/6 for 36.
Special Offer! Spot Face Cutter and 5 24 x 1" boards. 9/9 only

PAPER CONDENSERS. Mixed bags 0.001µF to .5µF. 12/6 per 100.
SILVER-MICA. Ceramic, Polystyrene Condensers. Well assorted.
Mixed types and values. 10/- per 100.

RESISTORS. Mixed types and values, 1 to 1 watt. 6/6 per 100. 55/- per 1,000. Wire-wound resistors. 1 watt to 10 watts. Mixed values. 20 for 10/-.
TRANSISTORS. Mixed, unmarked, mainly O.K. 7/6 for 50.

12 VOLT TRANSISTORISED FLUORESCENT LIGHTS. HALF NORMAL PRICE.

8 Watt 12" tube. Reflector type £2.19.6. 15 watt 18" Batten type £3.19.6.
IDEAL FOR CAMPING OR CARAVAN HOLIDAYS! A BRIGHT LIGHT FOR VERY LITTLE CURRENT!

ELECTROLYTIC CONDENSERS

0.25µF 3 volt	4µF 4 volt	10µF 25 volt	64µF 9 volt
1µF 6 volt	4µF 12 volt	20µF 6 volt	100µF 9 volt
1µF 20 volt	4µF 25 volt	25µF 6 volt	330µF 4 volt
1.25µF 16 volt	6µF 6 volt	25µF 12 volt	330µF 10 volt
2µF 3 volt	6µF 6 volt	25µF 25 volt	400µF 6.4 volt
2µF 350 volt	8µF 3 volt	30µF 6 volt	All at 1/- each.
2.5µF 16 volt	8µF 12 volt	30µF 10 volt	20 assorted
3µF 25 volt	8µF 50 volt	50µF 6 volt	(our selection)
3.2µF 64 volt	10µF 6 volt	64µF 2.5 volt	10/-

Orders by post to:

G. F. MILWARD, DRAYTON BASSETT, NEAR TAMWORTH. STAFFS.

Please include suitable amount to cover post and packing. Minimum 2/-. Stamped addressed envelope must accompany any enquiries.

For customers in Birmingham area goods may be obtained from Rock Exchanges, 231 Alum Rock Road, Birmingham 8.


LINEAR RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors.

LTA15 15 WATT AMPLIFIER

HIGH FIDELITY OUTPUT SWITCHED INPUTS FOR GRAM, 'MIKE', TAPE, AND RADIO

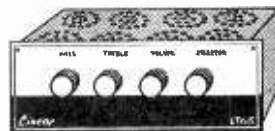Frequency Response 10-40,000 cps—3dB. Bass Control+18dB to—16dB at 40cps. Treble Control+17dB to—14dB at 14Kcs. Hum and Noise—80dB. Harmonic Distortion 0.2% at rated output. Output for 3-8-15 ohm Loudspeakers.




Recommended 17 gns
Retail Price
Size 9½ x 3½ x 5½ in.

PTA30 HI-FI PUBLIC ADDRESS AMPLIFIER

A SUCCESSOR TO OUR POPULAR CONCHORD 30 WATT UNIT

Input Sensitivity 2 mv (max.)
Output 30 watts.

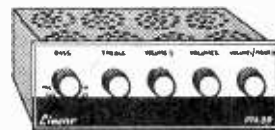Output Terminals or Loudspeaker or combination of Speakers with total impedance between 3 ohms and 30 ohms. Three individually controlled Jack Inputs for mixing purposes. Housed in fully enclosed stove enamelled steel case. Controls Vol. (1) Vol. (2) Vol. (3) with mains switch, Treble 'lift' and 'cut'. Bass 'lift' and 'cut'.



Recommended 21 gns
Retail Price
Size 12 x 3½ x 6in.

AN IDEAL UNIT FOR VOCAL AND INSTRUMENTAL GROUPS, SUITABLE FOR ANY KIND OF 'MIKE' AND INSTRUMENT PICK-UP, ALSO FOR RADIO, TAPE OR GRAM.

If required an attractive wood cabinet with Satin Teak veneer finish can be supplied for any model. Prices from **70s.**

Please send a stamped addressed envelope for full descriptive details of above units, also **TUNER/AMPLIFIERS STEREO and MONO.**

AVAILABLE FROM YOUR LOCAL HI-FI DEALER

Wholesale and Retail enquiries to:

LINEAR PRODUCTS LTD, Electron Works, Armley, Leeds

Fabulous Value

STEREOPHONIC KUBA "ROYAL" RADIOGRAM

This radiogram chassis is offered complete with carefully matched loudspeaker system, two 10in. speakers, two 4in. Cone Tweeters and latest BSR UA79 Mono/Stereo record changer—a complete quality stereophonic radiogram at its half normal price.

4 wavebands—AM/FM—8 piano keys control 8 watt push-pull output per channel—frequency response 30-20,000 cycles. EASY TO INSTALL. NO TECHNICAL KNOWLEDGE REQUIRED.

ONLY £79.19.6.

H.P. terms available. Deposit £26.13.2 and 24 monthly payments of 55/- (total H.P. £93.7.2) Send £21.10.8 today or write for free leaflet.

Fantastic Bargain Offer

KUBA "IMPERIAL 666" STEREOHONIC HI-FI RADIOGRAM CHASSIS—complete with two 10in. x 6in. speakers and the latest BSR Mono/Stereo record changer—a complete radiogram at half normal price. 4 Waveband AM/FM chassis with the very latest printed circuitry—7 push button control, 12 watts total output. Provision for stereo decoder. Only **49½ Gns.** plus P. & P. 17/6. **EASILY FITTED, NO TECHNICAL KNOWLEDGE NECESSARY.** H.P. available £17.6.6 deposit plus 24 monthly payments 36/2 (total H.P. £60.14.6). Send £18.4.0 today.

CALLERS WELCOME

POST THIS COUPON NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name

Address

LEWIS radio

100 CHASE SIDE, SOUTHGATE, Dept. P569A, LONDON, N.14
TELEPHONE 01-888 3788/8886

EXCLUSIVE PURCHASE!

PORTABLE AMPLIFIER UNIT

BY WELL-KNOWN BRITISH MAKER

A luxury unit at a bargain price. Only 35/- P. & P. 4/6. Designed as a Telephone Amplifier but can be used in many different ways—a booster amplifier for transistor radios, a baby alarm, intercom, paging system etc., etc. High gain four transistor amplifier unit housed in attractive leatherlike covered wooden cabinet with upward facing 3in. high flux P.M. speaker covered by neat plastic grille. Fitted 3-5mm jack socket and volume/on/off control. Size 7 x 4 1/2 x 3 1/2 in. Operates on standard PP6 or VT6 battery. Supplied complete with telephone pick-up induction coil fitted suction pad, lead and 3-5mm jack plug.

OUR SPECIAL PRICE... 35/- P. & P. 4/6.

Or as above with 3-5mm plug and DLRS unit for use as sensitive microphone for baby alarms, communication systems etc. Will operate over distances of up to 200ft. or more when connected with twin flex or bell wire.

PRICE 40/- P. & P. 4/6
(Batteries and flex not included.)

BRAND NEW 3 OHM LOUDSPEAKERS

5in. 14/-; 6in. 18/6; 8in. 27/-; 7 x 4in. 18/6; 10 x 6in. 27/6. E.M.I. 8 x 5in. with high flux magnet 21/-; E.M.I. 13 1/2 x 5in. with high flux ceramic magnet 42/- (15 ohm 45/-). E.M.I. 13 x 5in. with two built-in tweeters and crossover network 3 or 15 ohms 4 gns. P. & P. 5in. 21/-; 6 1/2 x 8in. 2/6, 10 & 12in. 3/6 per speaker.

BRAND NEW 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly 45.10.0. P. & P. 5/-; Guitar models: 25w. 45.0.0 35w. 48.0.0. E.M.I. 13in. 3 1/2w. HEAD DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3 or 15 ohm, 35/-; P. & P. 3/6.

35 OHM SPEAKERS
3in. 12/6; 7 x 4in. 21/-; P. & P. 2/- per speaker.

VYNAR AND REXINE SPEAKERS AND CABINET FABRICS app. 54in. wide. Usually 35/- yd., our price 13/6 yd., length. P. & P. 2/6 (min. 1 yd.). S.A.E. for samples.

LATEST COLLARO MAGNAVOX 363 STEREO TAPE DECK. Three speeds 4 track, takes up to 7in. spools. 218.10.0. Carr. 10/-.

QUALITY PORTABLE TAPE RECORDER CASE. Brand new. Beautifully made. Only 49/6. P. & P. 8/6. Dual Purpose Bulk Tape Eraser and Tape Head Demagnetiser 35/-; P. & P. 3/-.

ACOS CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity. 18/6. P. & P. 1/6.

ACOS HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE 21/-; P. & P. 1/6.

NEW S.T.C. TYPE 25 MINIATURE RELAYS—12 volt. 4 s/p. c/o contacts. 1 amp rating. Coil resistance 185 ohms. Size approx. 1 1/4 x 1 1/2 in. high. 10/- each. P. & P. 1/6.

Also some similar above but coil resistance 5,800 ohms 48 volt operation. 8/- each. P. & P. 1/6.

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF + 146pF. Fitted with trimmer and 5:1 integral auto motion. Suitable for nominal 470 kc/s I.P. Size approx. 2 1/4 x 1 1/4 in. Only 8/6. P. & P. 2/6.

TRANSFORMER BARGAINS

MAINS TRANSFORMER. Primary 200-240V two separate 1/2 wave secondaries giving approx. 16V at 1 amp and 20V at 1.2 amp; secs. can be connected in series for 36V at 1.5 amp. Ideal for transistor power supplies. Drop through mounting. Stock size 2 1/2 x 3 1/4 x 1in. 15/-; P. & P. 6/-.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. 11/-; P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 2/6.

MATCHED PAIR OF 2 1/2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS. Stock size 1 1/4 x 1 1/4 x 1in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/-; P. & P.

7-10 watt OUTPUT TRANSFORMERS to match pair of ECL86's in push-pull to 3 ohm output. ONLY 11/-; P. & P. 2/6.

BRAND NEW MAINS TRANSFORMERS for Bridge Rectifier. Pri. 240V. AC. Sec. 240v. at 50mA and 6.3v. at 1.5 amp. Stock size 2 1/4 x 2 1/4 in. 10/6. P. & P. 3/6. (Special quotations for quantities).

HIGH GRADE COPPER LAMINATE BOARDS
8 x 6 x 1/16 in. FIVE for 10/- P. & P. 2/-.

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class HI-FI Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Clr-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response 3-31B. 20-20,000 c/s. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 6 amp. PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0. All Post Free. Circuit diagram, construction details and parts list (free with kit) 1/6. (S.A.E.).



SPECIAL PURCHASE!

E.M.I. 4-SPEED PLAYER
Heavy 9in. metal turntable. Low flutter performance 200/250 v. shaded motor (90 v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. LIMITED NUMBER ONLY 63/- P. & P. 6/6.

4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. E.M.I. MODEL 999 Single Player with unit mounted pick-up arm and mono cartridge. £5.5.0. B.S.R. UA25 with latest mono compatible cart. £6.10.0. All plus Carriage and Packing 6/6. LATEST GARRARD MODEL 5. All types available 1000 SP25, 3000, AT80 etc. Send S.A.E. for latest Bargain Prices! PLINTH UNITS cut out for Garrard Models 1000, 1025, 2000, 3000, AT60, SP25. With rigid perspex cover. OUR PRICE 5 gns. complete. P. & P. 8/6.

LATEST RONETTE T/O STEREO/COMPATIBLE

CARTRIDGE for EP/LP/80/80/78. Only 32/6. P. & P. 2/-; LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/-; P. & P. 2/-; SONOTONE 9TAHC compatible Stereo Cartridge with diamond stylus 50/-; P. & P. 2/-.

QUALITY RECORD PLAYER AMPLIFIER MKII



A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7" w. x 3" d. x 6" h. Ready built and tested. PRICE 75/-; P. & P. 6/-.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

DELUXE QUALITY PORTABLE R/P CABINET MKII
Output motor board size 14 x 12in. clearance 2in. below. 6in. above. Will take above amplifier and any B.S.R. or GARRARD autochanger or Single Player Unit except AT60 and SP25. Size 18 1/2 x 5 1/2 x 8in. PRICE 79/6. P. & P. 9/6.

FM/AM TUNER HEAD

Beautifully designed precision engineered by Dornier & Wadsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM conversion. Prealigned FM section covers 86-102 Mc/s. I.P. output 10-7 Mc/s. Complete with ECC85 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-; GORIER F.M. TUNER HEAD. 88-100 Mc/s. 10-7 Mc/s. I.P. 15/- plus 2/6 P. & P. (ECC85 valves, 8/6 extra)

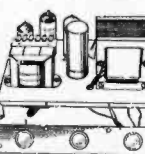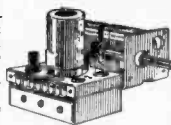

speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only 44.5.0. P. & P. 6/-.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched Pair) 15/-; V1510/10. 10/-; OCT1 5/-; OCT6 6/-; AF117 7/6.

Set of Mullard 6 transistors OC44, 2-OC45, AC128D, matched pair AC128 25/-; Mullard LPH3 Audio Transistor Pack AC128D and matched pair AC128 12/6; ORP12 Cadmium Sulphide Cells 10/6. All post free.

SPECIAL OFFER!


A great opportunity to purchase a first class GENERAL PURPOSE, HIGH GAIN, HIGH SENSITIVITY PORTABLE AMPLIFIER. Completely self contained and can be used for a variety of purposes, i.e. Intercom, Baby Alarm, Booster unit for transistor radios etc., also ideal for classroom unit etc. Works perfectly with our special offer ACOS Stick Microphone (21/-). Output 100mW. Uses standard 9 volt battery. Smart two tone carrying case size 12 x 4 x 9in. fitted standard input jack socket, volume controls, 7 x 4in. speaker. Completely built and tested, brand new with full maker's guarantee.



Only 79/6 Post free

STEREO AMPLIFIER

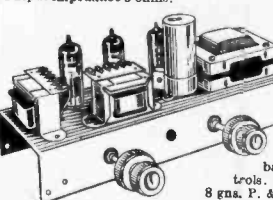Incorporating 2 ECL86s and 1 E280, heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete. Output impedance 3 ohms.




ONLY £5.9.6

P. & P. 8/-
Super Deluxe version with ECL86 valves, sep. bass and treble and balance controls. Full feedback. 8 gns. P. & P. 8/-.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1

- Peak output in excess of 1 1/2 watts.
- All standard British components.
- Built on printed circuit panel size 6 x 3in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 3 ohm and 15 ohm speakers.
- Transistors (GET114 or 81 Mullard AC128D) and matched pair of AC128 o/p. ● 9 volt operation.
- Everything supplied, wire, battery clips, solder, etc.
- Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 45/-; P. & P. 3/-.

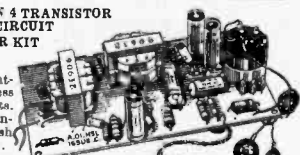

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, E280 rectifier and ECL86 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7" wide x 8" deep x 6" high overall. AO mains 200/240v. Supplied absolutely brand new completely wired and tested with valves and good quality output transformer. LIMITED NUMBER ONLY.


OUR ROCK BOTTOM BARGAIN PRICE

49/6

P. & P. 6/-

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good life and cut. Valve line-up 2EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY 57.9.6. P. & P. 8/6. Also available ready built and tested complete with std. Input sockets, 59.5.0. P. & P. 8/6.

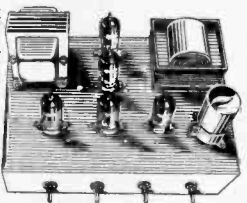

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon
Tube Station

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Please write clearly

PLEASE NOTE: P. & P. CHARGES
QUOTED APPLY TO U.K. ONLY.
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.

R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m.
—5.30 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Callers

Tel. 788-0199/1649

1A7 7/9	6BQ7A 7/-	6K7G 2/-	9BW6 7/-	20P5 20/-	80 7/6	DF96 7/6	ECF80 6/8	EM80 7/8	PC97 8/8	RG5/50080/-	UF99 7/6
1D5 7/8	6BR7 17/-	6K7GT 4/6	10C1 12/6	25A6 6/8	85A2 7/8	DH77 4/8	ECF82 6/8	EM81 8/8	PC88A 6/8	S130 40/-	UL41 12/-
1H5 7/8	6BR8 12/6	6K8M 11/6	10C2 12/6	25B6 7/-	150B2 11/8	DK32 7/8	ECF84 6/8	EM84 7/8	PC89 10/8	SP4 8/-	UL44 7/-
1LD5 6/8	6BR7 25/-	6K8G 3/-	10F1 14/9	25Y6 6/-	150C4 8/8	DK91 6/-	ECF85 11/6	ESU15020/-	PC189 10/8	SP41 3/6	UM80 5/6
1N5GT 6/8	6BW6 14/8	6K8GT 7/-	10F3 15/-	25Z4 6/8	801 8/8	DK92 9/-	ECF86 7/8	EY51 7/8	PCF80 6/8	SP61 3/6	U6 13/6
1R5 6/8	6BWT 13/-	6K8 12/-	10F8 8/-	25Z5 8/8	807 9/-	DK96 7/8	ECF87 5/8	EY86 7/8	PCF82 6/8	STV280/80	U7 13/6
184 5/8	6C4 6/-	6L1 12/-	10F18 8/-	25Z6 8/8	813USA	DL66 25/-	ECF88 3/8	EZ35 6/8	PCF84 8/-	55/-	U9 8/8
185 4/6	6CSG 5/8	6L6G 7/9	10L1 8/-	25Z7 9/8	120/-	DL92 6/8	ECF89 3/8	EZ40 8/8	PCF86 9/8	SU25 19/-	U9 8/8
1T4 4/6	6C6 3/8	6L18 6/-	10L11 10/6	30C1 6/8	813 80/-	DL93 4/-	ECF90 3/8	EZ41 9/8	PCF88 9/8	SU2160 12/8	U9 8/8
3A4 4/6	6CSG 6/8	6Q7G 6/-	10P13 13/6	30C15 15/-	866A 15/-	DL94 6/8	ECF91 3/8	EZ42 9/8	PCF90 9/8	T41 17/6	U9 8/8
3Q4 7/9	6CD6G 24/-	6Q7GT 8/6	11E3 70/-	30C17 16/-	954 5/8	DL95 7/8	ECF92 3/8	EZ43 9/8	PCF92 9/8	U10 7/8	U9 8/8
3Q5 7/8	6CH6 7/8	6SA7M 7/-	12A7 6/-	30C18 15/-	1625 6/8	DL96 7/8	ECF93 3/8	EZ44 9/8	PCF94 9/8	U11 7/8	U9 8/8
384 6/8	6CWA 12/-	6SCT 7/-	12A7 6/-	30F5 17/-	4022AR87/-	DM70 6/-	ECF94 3/8	EZ45 9/8	PCF96 13/8	U12 7/8	U9 8/8
3V4 6/8	6D6 3/8	6SCT 6/-	12A7 6/-	30FL1 10/-	5763 12/-	DY86 6/-	ECF95 3/8	EZ46 9/8	PCF98 13/8	U13 7/8	U9 8/8
6R4GY 10/8	6E5 7/8	6SCT 3/8	12A7 6/-	30FL12 19/-	7193 2/-	DY87 8/8	ECF96 3/8	EZ47 9/8	PCF99 13/8	U14 7/8	U9 8/8
5U4G 4/6	6F1 12/6	6SCT 6/-	12A7 6/-	30FL14 15/8	7475 14/-	DY88 8/8	ECF97 3/8	EZ48 9/8	PCF99 13/8	U15 7/8	U9 8/8
5V4G 5/8	6F5G 8/-	6SCT 6/-	12A7 6/-	30L15 17/-	AS1 7/9	DY89 8/8	ECF98 3/8	EZ49 9/8	PCF99 13/8	U16 7/8	U9 8/8
5Y3GT 6/8	6F6G 5/-	6SCT 6/-	12A7 6/-	30L17 17/-	ATP4 2/3	DY90 8/8	ECF99 3/8	EZ50 9/8	PCF99 13/8	U17 7/8	U9 8/8
5Z4G 7/-	6F9G 5/8	6SCT 6/-	12A7 6/-	30P12 16/-	ATP5 12/-	DY91 8/8	ECF99 3/8	EZ51 9/8	PCF99 13/8	U18 7/8	U9 8/8
6/30L2 15/-	6F11 6/8	6SCT 6/-	12A7 6/-	30P19 15/-	ATP7 8/8	DY92 8/8	ECF99 3/8	EZ52 9/8	PCF99 13/8	U19 7/8	U9 8/8
6A7 15/-	6F13 6/8	6SCT 6/-	12A7 6/-	30P11 18/-	AU2 80/-	DY93 8/8	ECF99 3/8	EZ53 9/8	PCF99 13/8	U20 7/8	U9 8/8
6A8G 12/6	6F14 12/6	6SCT 6/-	12A7 6/-	30P13 18/6	AU5 8/8	DY94 8/8	ECF99 3/8	EZ54 9/8	PCF99 13/8	U21 7/8	U9 8/8
6A7 4/6	6F23 16/-	6SCT 6/-	12A7 6/-	30P14 15/-	AZ1 8/-	DY95 8/8	ECF99 3/8	EZ55 9/8	PCF99 13/8	U22 7/8	U9 8/8
6AK5 5/8	6F24 14/-	6SCT 6/-	12A7 6/-	35A5 11/6	AZ31 10/-	DY96 8/8	ECF99 3/8	EZ56 9/8	PCF99 13/8	U23 7/8	U9 8/8
6AL5 4/8	6F25 14/-	6SCT 6/-	12A7 6/-	35A6 11/6	CB131 18/-	DY97 8/8	ECF99 3/8	EZ57 9/8	PCF99 13/8	U24 7/8	U9 8/8
6AM5 2/8	6F26 14/-	6SCT 6/-	12A7 6/-	35A7 11/6	CB131 18/-	DY98 8/8	ECF99 3/8	EZ58 9/8	PCF99 13/8	U25 7/8	U9 8/8
6AM6 3/8	6G6 2/6	6SCT 6/-	12A7 6/-	35W4 4/6	CB131 18/-	DY99 8/8	ECF99 3/8	EZ59 9/8	PCF99 13/8	U26 7/8	U9 8/8
6AQ5 6/8	6H6 3/6	6SCT 6/-	12A7 6/-	6X23 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ60 9/8	PCF99 13/8	U27 7/8	U9 8/8
6A87G 18/-	6J5M 9/-	6SCT 6/-	12A7 6/-	6X24 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ61 9/8	PCF99 13/8	U28 7/8	U9 8/8
6AT6 4/8	6J5G 4/8	6SCT 6/-	12A7 6/-	6X25 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ62 9/8	PCF99 13/8	U29 7/8	U9 8/8
6AUG 6/8	6J5GT 5/8	6SCT 6/-	12A7 6/-	6X26 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ63 9/8	PCF99 13/8	U30 7/8	U9 8/8
6B4G 20/-	6J6 8/8	6SCT 6/-	12A7 6/-	6X27 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ64 9/8	PCF99 13/8	U31 7/8	U9 8/8
6B8G 20/-	6J7M 8/8	6SCT 6/-	12A7 6/-	6X28 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ65 9/8	PCF99 13/8	U32 7/8	U9 8/8
6BA6 5/8	6J7G 8/8	6SCT 6/-	12A7 6/-	6X29 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ66 9/8	PCF99 13/8	U33 7/8	U9 8/8
6BE6 5/8	6J7GT 7/8	6SCT 6/-	12A7 6/-	6X30 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ67 9/8	PCF99 13/8	U34 7/8	U9 8/8
6BH6 9/8	6K6GT 5/8	6SCT 6/-	12A7 6/-	6X31 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ68 9/8	PCF99 13/8	U35 7/8	U9 8/8
6B6 9/-	6K7M 6/8	6SCT 6/-	12A7 6/-	6X32 10/-	CB131 18/-	DY99 8/8	ECF99 3/8	EZ69 9/8	PCF99 13/8	U36 7/8	U9 8/8

SPECIAL 24 HOUR SERVICE

OBsolete TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Express postage 9d. per valve.

Ordinary postage 6d. per valve. C.W.O. No C.O.D.

Complete range of T.V. Tubes available from £4.5.0.

Manufacturers and Export Inquiries Welcome

Special 24 Hour

Express Mail

Order Service

SETS OF VALVES

DAF91, DF91, DK91, DL92 or DL94 20/- plus postage
DAF96, DF96, DK96, DL96 25/- plus postage


TRANSISTORS

AC127 7/6	OC25 11/-	OC71 4/6	OC81 4/-	OC82D 6/-
AF114 7/-	OC28 10/-	OC72 6/-	OC81D 4/-	OC83 6/-
AF115 7/-	OC36 11/8	OC75 6/-	OC81DM 4/-	OC170 7/-
AF116 7/-	OC44 8/8	OC76 8/-	OC82 6/-	OC171 8/-
AF117 6/8	OC45 4/-	OC77 8/-	OC82 6/-	OC200 7/6

SEND S.A.E. FOR LIST OF 2,000 TYPES

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

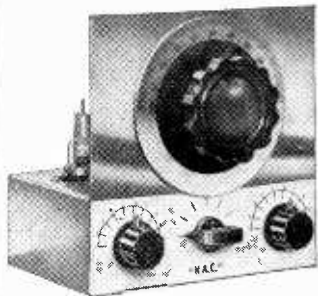

Famous for over 30 years for Short-Wave Equipment of quality, "H.A.C." were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1969 RANGE

One-valve model "DX", complete kit—price 56/8 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits still available, including the famous model "K" (recommended by radio clubs). All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

Est. 1943 **JOHNSONS** Tel: 24864

VHF and Short-Wave kits for the Amateur enthusiast and constructor. For 2 and 4 metres, the unique two transistor model SR2/P, 70–150Mc/s, 75/6, p.p. 4s. New super 5V all-wave, all-band kit, also "Mini-Amp" self-contained, cabinet, size a mere 4½ x 3½ x 2½. Write today, enclosing a stamped addressed envelope for interesting free literature, and details, direct to

JOHNSON'S (RADIO)
St. Martin's Gate, Worcester

SPECIAL FRINGE AREA BBC-2 & COLOUR TV AERIAL



Unbeatable Offer

ONLY 45/-

(Carr. 5/-)

For loft or roof fixing. Complete with mounting arm. State Channel required or nearest transmitter. Hundreds sold. Special low-loss co-axial cable 2/3 yd. Socket 2/6.



SPEAKER BARGAIN!

Famous English 12in. high flux, heavy cone, 10 watts speaker with built-in tweeter, excellent bass response, 15 ohms.

(P. & I. 5/6) **39/6**

ELECTRAMA

Dept. 93, 1 George St., Hailsham, Sussex

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets and Manufacturers' Manuals for most makes and types of Radios, Tape Recorders and Televisions.

Please complete order form below for your Service Sheet to be sent by return. To:

OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1969 List now available at 2/- plus postage

If list is required indicate with X


From
Address

enclose remittance of
(and a stamped addressed envelope)
s.a.e. with enquiries please
MAIL ORDER ONLY (May PW)

THE CLASSIC

Controls: Selector switch Tape speed equalisation switch (3½ and 7½ i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 position rumble filter.

Specification: Sensitivities for 10 watt output at 1KHz. Tape head: 3mV (at 3½ i.p.s.). Mag. P.U.: 2mV. Cer. P.U.: 80mV. Radio: 100mV. *Max.*: 100mV. *Tape/Rec. output*: 100mV. Equalisation for each input is correct to within ± 2dB (R.I.A.A.) from 20Hz to 20KHz. *Tone control range*: Bass ± 13dB at 60 Hz. Treble ± 14dB at 15KHz. *Total distortion*: (for 10 watt output) <1.5%. *Signal noise*: <-60dB. A.C. mains 200-250V. Size 12½in. long, 4½in. deep, 2½in. high. Teak finished case. **Price 8½ gns.** + 7/6 p. & p. Built and Tested

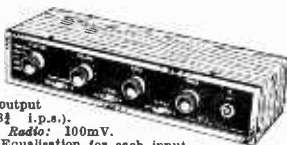

THE DORSET (600mW output)



7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modularised and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

MAINS POWER PACK KIT: 9/6 extra.

PRICE £5.5.0 plus 7/6 p. & p. Circuit 2/6 FREE WITH PARTS.

THE ELEGANT SEVEN MK. III (350mW output)

7-transistor fully tunable M.W.-L.W. portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

Price £4.9.6 plus 7/6 p. & p.

Circuit 2/6 FREE WITH PARTS.



X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: *Power Output* (into 3 ohms speaker) 10 watts. *Sensitivity* (for rated output): 1mV into 3K ohms (0-33 microamp). *Total Distortion* at 1KHz. at 5 watts 0-35%, at rated output 1-5%. *Frequency Response*: Minus 3dB points 20Hz and 40KHz. *Speaker*: 3-4 ohms (3-15 ohms may be used). *Supply voltage*: 24V d.c. at 800mA (6-24V may be used).

Control assembly: including resistors and capacitors.

1. Volume: PRICE 5/-.

2. Treble: PRICE 5/-.

3. Comprehensive bass and treble: PRICE 10/-.

The above 3 items can be purchased for use with the X101.

Power Supplies for the X101:

P101 M (for mono) 35/- plus 4/6 p. & p.

P101 S (for stereo) 42/6 plus 4/6 p. & p.



Price 49/6
plus 2/6 p. & p.

THE RELIANT MK II

10W SOLID-STATE HIGH QUALITY AMPLIFIER

SPECIFICATIONS

Output—10 watts

Inputs—1. xtal mic 10mV

2. gram/radio 250mV

Frequency Response—(with tone controls central) Minus 3dB points are 20Hz and 40KHz. *Signal to Noise Ratio*—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220 - 250V. A.C. Size of chassis—10½" x 4½" x 2½". A.C. Mains, 200-250V. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control for gram. and mike. Built and tested. 8" x 5" speaker to suit price 14/6 plus 1/6 P. & P. Crystal mike to suit 12/6 plus 1/6 P. & P.

Reliant Mark II. 6½ gns. plus 7/6 p. & p.

In teak finished case.



THE VISCOUNT

Integrated High Fidelity Transistor Stereo Amplifier

SPECIFICATIONS: Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monaural). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo). P.U., Tuner, Tape and Tape Rec. Sensitivities: All inputs 100mV into 1-8M ohm. Frequency response: 40Hz-20KHz ± 2db. Tone controls: (Baxandall type), separate bass and treble controls. Treble 13db lift and cut at 15KHz. Bass 15db lift and 24db cut at 60Hz. Volume controls: Separate for each channel. A.C. Mains input: 200-240V. 50-60Hz. Size 12½ x 6 x 2½in. In teak-finished case. Built and tested

PRICE 13½ Gns. Postage & Packing 7/6 extra.

Goods not despatched outside U.K. Terms C.W.O. All enquiries Stamped Addressed Envelope

RADIO & TV COMPONENTS (Acton) LTD
21c High Street, Acton, London, W.3.

All orders by post to our Acton address
323 Edgware Road, London, W.2.



POCKET MULTI-METER

Size 3½ x 2½ x 1½in. Meter size 2½ x 1½in. Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000 D.C. current 0-150mA. Resistance 0-100KΩ. Complete with test prods, battery and full instructions. 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.

CYLDON 4 TRANSISTOR U.H.F. TUNER

Brand new. Complete with circuit diagram.

£2.10.0 plus 1/- p. & p.

THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss cross over network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 gauss. Resonance 40-60 c/s. Frequency range 50c/s to 20Kc/s. Size 13½ x 8½ x 4½ inches. By famous manufacturer. List Price £7. Our price 74/6 plus 5/- P. & P. Similar speaker to the above without tweeters in 3 and 15 ohm 44/6 plus 5/- P. & P.

B.S.R. TD-2 TAPE DECK

This tape deck takes 5½in. spools complete with two-track heads. Size 13½in. long by 5½in. wide. £8.19.6 plus 7/6 p. & p.

2½ watt ALL TRANSISTOR AMPLIFIER

AC mains 240V. Size 7" x 4½" x 1½". Frequency response 100 c/s—10 Kc/s. Semi conductors, two OC 75's two AC 128's and two stabilizers AA129. Tone and volume controls on fly.ing leads. £2.10.0 plus P. & P. 3/6. Suitable 8" x 5" 10,000 line high flux speaker, 18/6 plus 2/- P. & P.



FIRST QUALITY P.V.C. TAPE

5½"	Std.	850ft.	11/6	5"	L.P.	850ft.	12/-
7"	Std.	1200ft.	13/-	3"	T.P.	600ft.	12/-
3"	L.P.	240ft.	5/6	5"	T.P.	1800ft.	27/-
5½"	L.P.	1200ft.	13/-	5½"	T.P.	2400ft.	34/-
7"	L.P.	1800ft.	20/-	7"	T.P.	3600ft.	44/-
5½"	D.P.	1800ft.	20/-	4"	T.P.	900ft.	16/6

P. & P. on each 1/6.

50 WATT AMPLIFIER A.C. MAINS 200-250V



An extremely reliable general purpose valve amplifier—with six electronically mixed inputs. Suitable for use with: mics, guitars, gram, tuner, organs, etc. Separate bass and treble controls. Output impedance 3, 8 and 15 ohms.

Price 27 gns. Plus 20/- p. & p.

RECORD PLAYER SNIP A.C. MAINS 240V

The "Princess" 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7" to 10" or 12". Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play. Post and insurance 7/6 extra.




CAR TRANSISTOR IGNITION SYSTEM

(by famous manufacturer)

For 6 volt or 12 volt positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers etc.). **PRICE £4.19.6.** (post and packing 5/- extra).

3 + 3 watt STEREO AMPLIFIER

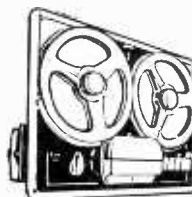Available shortly. A.C. mains 240 volt in teak finished case. Size 10½" long x 4½" wide x 2½" deep. **Price 9 gns.** plus 7/6 p. & p.



MOTEK

3 Speed 2 track Tape Deck complete with heads, takes 7in. spool.

Incorporating 3 motors.

A.C. mains, 240 volts, listed at £21.0.0.

Our Price £9.19.6, plus 10/- P. & P.



Interested in cutting your motoring costs?

You can save a considerable amount of money by tackling some of the car maintenance jobs yourself and the **PRACTICAL MOTORIST ANNUAL** is designed specially to help you. Authoritative articles and step-by-step instructions show you how to maintain the engine, ignition, cooling, carburation, transmission, suspension and steering, brakes, tyres, bodywork, electrics, etc., and give advice on simple tuning.


With holidays in mind there is a most helpful section on camping and caravanning.

EVERY MOTORIST NEEDS THE PRACTICAL

motorist annual

Now on sale 3/6

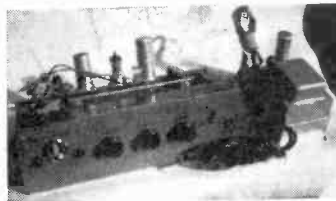TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS — 2 or 4 TRACK




Chassis 12½ x 5¼ x 4½in. high. Front panel alum and black—12½ x 4½in. 200-250 A.C. Mains Trans. Off/On-Tone; Vol./Mic.; Vol./Gram.; Mic. Input; Gram. Input; Monitor; Valves 6BR7, ECC83, EM84, EL84 and Rect. 2 Track £10.10.0; 4 Track £12 (12/6 p. & p.). Ready for bolting direct to Magnavox deck. 3 speed Magnavox 4 Track tape deck, Type 368. £16.10.0 curr. paid. 2 x 2 Stereo deck £20.

FULLY BUILT STEREO AMPLIFIER. 2 x 3 watts, mains trans., metal rect., 2 x UCL82, 2 o.p. trans. for 3 ohm, vol/on-off, tone, balance, chassis type with 3 controls on front. 11 x 3½ x 4in. high. £6 (8/- p. & p.).

8W. PEAK PUSH-PULL OUTPUT AMPLIFIER. 200-250V A.C. EZ80, ECC83, 2—EL84, Bias, treble, vol/on-off, £7.17.6 (post paid). Size 12 x 3½ x 5in. high. For Record Player, Radio Tuner, etc. Mains Trans. o.p. trans. for 3 ohm.



6 PUSH-BUTTON STEREOGRAM CHASSIS

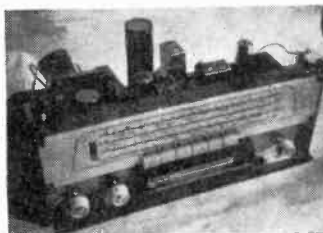

M.W.: S.W. 1: S.W. 2: V.H.F. Gram.: Stereo Gram.: Vol.: Tone: Mains Trans.: 200-250 Volts, 2 o.p. for 3 ohm. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6½in. high. Dial silver and black 15 x 3in. 190-550M. 18-51M. 60-187M. VHF 86-100 Mc/s. Valves: ECC83, ECH81, EF89, 2x ECL86, EM84 and Rect. Price £18.19.0, curr. paid. With Stereo Decoder fitted £7.10.0 extra.

GLADSTONE RADIO


66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses).

FULL GUARANTEE

Aldershot 22240

CLOSED TUESDAY AND WEDNESDAY.

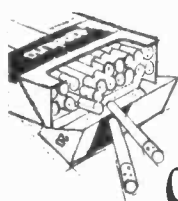

We put
23,340
cigarettes

in our Budget
combination storage
unit!

Think what you could
put in it!

Storage. Lots of it, for a thousand things you stock; replacement parts; light bulbs; cameras; anything up to 7 x 8 x 10½in. Safety drawer-stops as 'standard'. Smooth guide runners thro'out. All in a compact 3ft. 6in. high, 2ft. 11in. wide, 1ft. deep area. Ready assembled, in stove enamelled green or grey. With 18 handy, 6 large, 8 king-sized drawers. At £17 5s. worth every penny! See the rest of the N. C. Brown range!



£17 5s.

Carriage free
on mainland



N.C. BROWN LTD.

pacesetters in storage equipment

Send your FREE BROCH-
URE ☐ or Send ☐ (how
many) Budget Storage Units
at £17. 5s. in green or
grey.

NAME
ADDRESS

Dept. PW Eagle Steelworks, Heywood, Lancs. Tel. 69018
London: 25-27 Newton St., W.C.2. Tel. 01-405 7931

NEW PRICES ON NEW COMPONENTS

RESISTORS

High stability, carbon film, low noise. Capless construction, molecular termination bonding.

Dimensions (mm.): Body: $\frac{1}{4}$ W; 8×2.8
 $\frac{1}{2}$ W; 10×4.3

Leads: 35

10% ranges; 10 Ohms to 10 Megohms (E12 Renard Series).

5% ranges; 4.7 Ohms to 1 Megohm (E24 Renard Series).

Prices—per Ohmic value.

	each	10 off	25 off	100 off
$\frac{1}{4}$ W 10%	2d.	1/6	3/3	10/4
$\frac{1}{4}$ W 5%	2½d.	1/9	3/8	11/8
$\frac{1}{2}$ W 10%	2½d.	1/9	3/8	11/7
$\frac{1}{2}$ W 5%	3d.	2/-	4/-	12/10

CAPACITORS

Subminiature Polyester film. Modular for P.C. mounting. Hard epoxy resin encapsulation. Radial leads.

± 10% tolerance. 100 Volt Working.

Prices—per Capacitance value (µF)

	each	10 off	25 off	100 off
0.001, 0.002, 0.005.				
0.01, 0.02	6d.	4/3	8/4	30/-
0.05	8d.	6/-	12/6	41/8
0.1	10d.	7/1	15/6	51/-
0.2	1/2	10/-	20/10	68/6
0.5	2/-	17/6	37/6	125/-

Polystyrene film, Tubular, Axial leads. Unencapsulated. ± 5% or ± 1pf tolerance. 160 Volt Working.

Prices—per Capacitance value (µF)

	each	10 off	25 off	100 off
10, 12, 15, 18, 22, 27, 33,				
39, 47, 56, 68, 82, 100, 120,				
180, 220, 270, 330, 390	5d.	3/7	7/9	24/-
470, 560, 680, 820, 1,000,				
1,500	6d.	4/-	8/8	26/8
2,200, 3,300, 4,700, 5,600	7d.	5/-	10/10	33/4
6,800, 8,200, 10,000, 15,000	8d.	6/-	13/-	40/-
22,000	9d.	6/9	18/-	45/4

Polystyrene film, Tubular, Axial leads. Professional Grade. Hard Epoxy Resin encapsulation.

± 1% tolerance. 100 Volt Working.

Prices—per Capacitance value (µF)—except where stated.

	each	10 off	25 off	100 off
100, 120, 150, 180	1/3	10/2	21/2	64/6
220, 270, 330, 390, 470,				
560, 680, 820	1/3	10/8	23/1	71/-
1,000, 1,200, 1,500,				
2,200, 2,700	1/6	13/10	29/11	92/-
3,300, 3,900, 4,700, 5,600	1/9	14/1	31/-	96/-
6,800, 8,200, 10,000, 12,000	1/9	15/2	32/10	101/-
15,000, 18,000	2/-	15/11	34/9	107/4
22,000, 27,000	2/3	17/3	37/10	115/-
33,000, 39,000	2/6	20/1	43/6	133/9
47,000, 56,000	2/9	22/1	47/10	147/4
68,000	3/-	24/9	53/8	165/4
82,000	3/3	26/1	56/6	173/9
0.1 µF	3/6	27/5	59/4	182/8
0.12 µF	3/9	30/3	65/10	202/-
0.15 µF	4/3	34/2	73/7	228/-
0.18 µF	5/-	37/10	81/11	252/3
0.22 µF	6/-	47/-	101/10	313/4
0.27 µF	6/9	53/9	116/8	358/4
0.33 µF	7/3	58/10	126/11	390/-
0.39 µF	7/9	65/-	140/10	433/4
0.47 µF, 0.5 µF	9/9	75/2	137/7	500/-

POTENTIOMETERS (Carbon)

Miniature, fully enclosed, rear tags, carbon brush wiper. Long life, low noise. Body dia., $\frac{1}{2}$ in. Spindle, $\frac{1}{16}$ in. $\frac{1}{4}$ W at 70°C. ± 20% below $\frac{1}{2}$ M, ± 30% over $\frac{1}{2}$ M. Lin. 100 ohms to 10 Megohms. Log. 5 Kohms to 5 Megohms.

Prices—per ohmic value

	each	10 off	25 off	100 off
Miniature (0.3W)	1/-	8/9	18/9	66/8
Subminiature (0.1W)	10d.	7/1	14/7	46/8

SKELETON PRE-SET POTENTIOMETERS (Carbon)

High quality pre-sets suitable for printed circuit boards of 0.1in. P.C.M. 100 ohms to 5 Megohms (Linear only). Miniature: 0.3W at 70°C. ± 20% below $\frac{1}{2}$ M, ± 30% above $\frac{1}{2}$ M. Horizontal (0.7in. × 0.4in. P.C.M.) or Vertical (0.4in. × 0.2in. P.C.M.). Subminiature: 0.1W at 70°C. ± 20% below 2.5M, ± 30% above.

Prices—per ohmic value

	each	10 off	25 off	100 off
Miniature (0.3W)	1/-	8/9	18/9	66/8
Subminiature (0.1W)	10d.	7/1	14/7	46/8

JACK PLUGS

$\frac{1}{2}$ in. Type P1. Standard. Screened. Heavily chromed.

$\frac{1}{2}$ in. Type P2. Standard. Unscreened. Unbreakable moulded cover.

$\frac{1}{2}$ in. Type SE/P1. Side-entry version of P1 plug.

3.5 mm. Type P5. Standard. Screened. Aluminium cover.

3.5 mm. Type P6. Standard. Unscreened. Unbreakable moulded cover.

	each	10 off	25 off	100 off
P1	3/-	26/8	62/6	233/4
P2	2/6	23/4	54/2	200/-
SE/P1	3/6	30/10	66/8	280/-
P5	2/2	19/2	43/9	158/4
P6	1/8	15/-	33/4	116/8

JACK SOCKETS

$\frac{1}{2}$ in. Type S.5 Standard. Moulded body. Chrome insert.

3.5 mm. Type S.6. Specification as above.

Available with make/make, make/break, break/break, break/make contacts.

	each	10 off	25 off	100 off
S.5	2/9	25/-	56/8	216/8
S.6	1/6	13/4	33/4	100/-

ELECTROLYTIC CAPACITORS (Mullard). -10% to +50%.

Subminiature (all values in µF)

	each	10 off	25 off	100 off
4V	8	32	64	125
6.4V	6.4	25	50	100
10V	4	16	32	64
16V	2.5	10	20	40
25V	1.6	6.4	12.5	25
40V	1	4	8	16
64V	0.64	2.5	5	10
Price	1/4	1/3	1/2	1/-

Small (all values in µF)

	each	10 off	25 off	100 off
4V	800	1,250	2,000	3,200
6.4V	640	1,000	1,600	2,500
10V	400	640	1,000	1,600
16V	250	400	640	1,000
25V	160	250	400	640
40V	100	160	250	400
64V	64	100	160	250
Price	1/6	2/-	2/6	3/-

POLYESTER CAPACITORS (Mullard)

Tubular 10%, 160V: 0.01, 0.015, 0.022 µF. 7d. 0.033, 0.047 µF. 8d. 0.068, 0.1 µF. 9d. 0.15 µF. 11d. 0.22 µF. 1/-, 0.33 µF. 1/3, 0.47 µF. 1/6, 0.68 µF. 2/3, 1 µF. 2/8.

400V: 1,000, 1,500, 2,200, 3,300, 4,700pF. 6d. 6,800pF. 0.01, 0.015, 0.022 µF. 7d. 0.033 µF. 8d. 0.047 µF. 9d. 0.068, 0.1 µF. 11d. 0.15 µF. 1/2, 0.22 µF. 1/6, 0.33 µF. 2/3, 0.47 µF. 2/8.

Modular, metalised, P.C. mounting, 20%, 250V: 0.01, 0.015, 0.022 µF. 7d. 0.033, 0.047 µF. 8d. 0.068, 0.1 µF. 9d. 0.15 µF. 11d. 0.22 µF. 1/-, 0.33 µF. 1/5, 0.47 µF. 1/8, 0.68 µF. 2/3, 1 µF. 2/9.

SEMICONDUCTORS: OA5, OA81, 1/9. OC44, OC45, OC71, OC81, OC81D, OC82D, 2/-, OC70, OC72, 2/3. AC107, OC75, OC170, OC171, 2/6. AF115, AF116, AF117, ACY19, ACY21, 3/3. OC140, 4/3. OC200, 5/-, OC139, 5/3. OC25, 7/-, OC35, 8/-, OC23, OC28, 8/3.

SILICON RECTIFIERS (0.5A): 170 P.I.V., 2/9. 400 P.I.V., 3/-, 800 P.I.V., 3/3. 1,250 P.I.V., 3/9. 1,500 P.I.V., 4/-, (0.75A): 200 P.I.V., 1/6. 400 P.I.V., 2/-, 800 P.I.V., 3/3. (6A): 200 P.I.V., 3/-, 400 P.I.V., 4/-, 600 P.I.V., 5/-, 800 P.I.V., 6/-.

SWITCHES (Chrome finish, Silver contacts): 3A 250V, 6A 125V. Push Buttons: Push-on or Push-off 5/-. Toggle Switches: SP/ST, 3/6. SP/DT, 3/9. SP/DT (with centre position) 4/-. DP/ST, 4/6. DP/DT, 5/-.

PRINTED CIRCUIT BOARD (Vero).

0.15in. Matrix: 3 $\frac{1}{2}$ in. × 2 $\frac{1}{2}$ in., 3/3. 5 $\frac{1}{2}$ in. × 2 $\frac{1}{2}$ in., 3/11. 3 $\frac{1}{2}$ in. × 3 $\frac{1}{2}$ in., 3/11. 5in. × 3 $\frac{1}{2}$ in., 5/6.

0.1 Matrix: 3 $\frac{1}{2}$ in. × 2 $\frac{1}{2}$ in., 4/-, 5in. × 2 $\frac{1}{2}$ in., 4/6. 3 $\frac{1}{2}$ in. × 3 $\frac{1}{2}$ in., 4/6. 5in. × 3 $\frac{1}{2}$ in., 5/3.

SEND S.A.E. FOR 1969 CATALOGUE

DUXFORD ELECTRONICS (PE)

97/97A MILL ROAD, CAMBRIDGE

Telephone: CAMBRIDGE (0223) 63687

(Visit us—at our new Mail Order, Wholesale and Retail Premises)

MINIMUM ORDER VALUE 5/-

C.W.O. Post and Packing 1/6

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 2s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., 15/17 Long Acre, London, WC2, for insertion in the next available issue.

SITUATIONS VACANT

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc. on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. write for 132-page Handbook—FREE. Please state subject. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 137K), Aldermaston Court, Aldermaston, Berks.

ENGINEERS. A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C. Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Drafts., Building, etc. For full details write for FREE 132 page guide: BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY. (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

SERVICE ENGINEERS—we are an old established electronics company, but headed by a young management team and we need you to help us. Age is no barrier to a high salary as you will find out when you join us. If you have experience in T.V., Radio or Hi-Fi Service and want a job that looks ahead phone Michael Adler at 01-636 9606.

EDUCATIONAL

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV., automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies in September and January. Grants available. Day and Boarding students. Stamp for prospectus. Wireless College, Colwyn Bay.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.
ICS, DEPT. 541, INTERTEXT HOUSE, LONDON. SW11

EDUCATIONAL

(continued)

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. CHAMBERS COLLEGE (Dept. 857K), 148 Holborn, London, E.C.1.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

BOOKS & PUBLICATIONS

AUDIO. America's foremost journal. Year's subscription 50/-. Specimen copy 4/6. All American radio journals supplied—list free. Willen (Dept. 40), 61a Broadway, London E.15.

GOVT. SURPLUS WIRELESS EQUIPMENT HANDBOOK

This useful Handbook gives detailed information and circuit diagrams for British and American Government Surplus Receivers, Transmitters and Test Equipment etc.; also contained are some suggested modification details and improvements for the equipment. Incorporated in this revised edition is a surplus/commercial cross referenced valve and transistor guide. This book is invaluable to radio enthusiasts, radio clubs, universities and laboratories. The latest edition priced at 35/- per volume plus 5/- p & p is obtainable only from us at

GILTEXT (LEEDS) LTD

Dept. P.W., 24 Stansfield Chambers, Gt. George Street, Leeds 1.

s.a.e. with all enquiries, please. Extra postage for foreign orders.

SURPLUS HANDBOOKS

19 set Circuit and Notes	6/6 p/p 6d.
1155 set Circuit and Notes	6/6 p/p 6d.
H.R.O. Technical Instructions	5/6 p/p 6d.
38 set Technical Instructions	5/6 p/p 6d.
46 set Working Instructions	5/6 p/p 6d.
88 set Technical Instructions	7/- p/p 6d.
BC.221 Circuit and Notes	5/6 p/p 6d.
Wavemeter Class D Tech. Instr.	5/6 p/p 6d.
18 set Circuit and Notes	5/6 p/p 6d.
BC.1000 (31 set) Circuit and Notes	5/6 p/p 6d.
CR.100/B.28 Circuit and Notes	10/- p/p 9d.
R.107 Circuit and Notes	7/- p/p 6d.
AR.88D Instruction Manual	18/- p/p 6d.
62 set Circuit and Notes	6/6 p/p 6d.
Circuit Diagram 5/- each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.824, 22 set.	

52 set Sender and Receiver circuits 7/6 post free

Resistor colour code indicator 2/6 p/p 6d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

SERVICE SHEETS

SERVICE SHEETS. RADIO, TV. 5,000 Models. List 1/6. S.A.E. Enquiries. TELRAY, 11 Maudland Bank, Preston, Lancs.

RADIO, TELEVISION over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS (1925-1969) for TELEVISIONS, RADIOS, TRANSISTORS, TAPE RECORDERS, RECORD PLAYERS, etc., by return post, with free fault-finding guide. Prices from 1/-. Over 8,000 models available. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

SERVICE SHEETS (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. THOMAS BOWER, 5 South Street, Oakenshaw, Bradford.

C. & A. SUPPLIERS

SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS)

Only 5/- each, plus S.A.E.

(Uncrossed P.O.'s please, returned if service sheets not available.)

71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post) Please state make and model number alternative.

Mail order only.

WANTED

DAMAGED AVO METERS, Models 7 & 8, any quantity. Send for packing instructions. HUGGETT'S LTD., 2/4 Pawsons Road, West Croydon.

NEW VALVES WANTED. Popular TV and Radio types. Best cash price by return. DURHAM SUPPLIES, 367c Kensington Street, Bradford. 8, Yorkshire.

WANTED NEW VALVES, televisions, radio-grams, transistors, etc. STAN WILLETTS, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

WANTED (continued)

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S WIRELESS STORES, 55 Worcester Street, Wolverhampton.

WANTED: Popular Brand New Valves. R.H.S. Stamford House, 538 Great Horton Road, Bradford 7.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD
103 North Street, Leeds 7

WANTED: New valves, transistors etc.; state prices. E.A.V. Factors, 202 Mansfield Road, Nottingham.

WE BUY New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

FOR SALE

£6,000 IN VOUCHERS GIVEN AWAY. See free Catalogue for details. Tools, materials, mechanical, electrical, thousands of interesting items. WHISTON, Dept. VW, New Mills, Stockport SK12 4HL.

THE IDEAL Panel Mounting Meter Movement for any Sensitive Test Meter etc. 200 Micro Amp F.S.D. 4 1/2 in. x 4 1/2 in. In clear plastic case. Our special price only 39/6d. P. & P. free. Limited number only. WALTON'S WIRELESS STORES, 55A Worcester Street, Wolverhampton, Staffs.

YUKAN SELF-SPRAY 50 PROFESSIONAL PAINT
NEW! AIR DRYING

Get these air drying **GREY HAMMER**
NOW! OR **BLACK WRINKLE**
(CRACKLE) Finishes

Yukan Aerosol spraykin contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 16/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt Finish (12 ozs. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 19/11 carriage paid. Choice of 13 self-spray paint colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct.

Depot M/4 **YUKAN**, 307A, EDGWARE ROAD, (S.W.)
We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.
Open all day Saturday. Closed Thursday afternoons.

FOR SALE (continued)

PRECISION POTENTIOMETERS

Multi-turn, continuous or ganged from 25/-; carbon from 2/-. Also resistors, mains rectifiers, synchros, geared motors, chokes, capacitors, meters, microswitches, semiconductors. 6d. stamp catalogue. F. HOLFORD & CO., 6 Imperial Square, Cheltenham.

TOP TRADE DISCOUNTS FOR ALL COMPONENTS VALVES TUBES TRANSISTORS

Free Trade Catalogue
Engineers & Service Dealers Only
WILLOW VALE
THE SERVICE DEPT.
WHOLESALE, 4 The Broadway, Hanwell, London, W.7
01-567 5400/2971

MORSE MADE EASY !!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 8d. stamp for explanatory booklet to:
68CH8 (BOX 11), 45 GREEN LANE, PURLEY, SURREY

ELECTRICAL

240 VOLT ELECTRICITY ANYWHERE

MOST BRILLIANT PERFORMANCE EVER
from 12 volt Car Battery

BRILLIANT HEAVY DUTY 240 volt AMERICAN DYNAMOTOR with BIG 220 WATT OUTPUT. Marvellous for TELEVISION, ELECTRIC DRILLS, MAINS LIGHTING and ALL UNIVERSAL AC/DC MAINS EQUIPMENT. Marvellous for Fluorescent lighting. Thousands of uses. Tremendous purchase of this model makes fantastically low price possible.

ONLY £4.19.5 each plus 10/6 delivery. C.O.D. with pleasure. **MONEY BACK** if not DELIGHTED Please send s.a.e. for full illustrated details.

(Dept. PW) **STANFORD ELECTRONICS**
Rear Derby Road, North Promenade, **BLACKPOOL, Lancs.**
Open 7 days a week

MISCELLANEOUS

RHYTHM MODULES. Build your own rhythm box—simply, cheaply. Realistic sound guaranteed. S.A.E. for details. D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset.

BUILD IT in a DEWBOX quality cabinet. 2in. x 2 1/2 in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

UFO DETECTOR CIRCUITS, data. 10s. (refundable). Paraphysical Laboratory (UFO Observatory), Downton, Wilts.

YOUR CALL SIGN ENGRAVED. White Letters Black Plate 6 x 1 1/2 in. 5/6. 2 x 1 1/2 in. Badge Pin, 4/-. Post Free. C.W.O. Workshops for Disabled, Northern Road, Cosham, Portsmouth. PO6 3EP.

ELECTRONIC SOUND and musical devices required for exploitation. Adequate finance available. Projects developed to pre-production stage required. Royalty payments guaranteed. Box 87

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

RECEIVERS & COMPONENTS

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous, 1-20 watt, 12/6 Post Free. **WHITSAM ELECTRICAL**, 33 Drayton Green Road, West Ealing, W.13.

BAKER & BAINES

for Television and F.M. Aerials

Examples of prices: FM dipole 21/-, H 38/-, BBC dipole 30/-, X 38/-, H 42/-, 3 ele 89/-, ITA 3 ele 28/-, 5 ele 34/-, 8 ele 47/6, 11 ele 57/6, Combined BBC/ITA 1 + 5 45/-, H + 5 89/-, X + 5 75/-, BBC2 8 ele 29/-, 14 ele 37/-, 18 ele 54/-, 22 ele 83/-.

All types generally available including accessories—prices include mounting clamps and postage.
11 Dale Crescent, New Tupton, Chesterfield.

(continued on next page)

TELEVISION TUBES

Large stocks of television tubes, London's leading wholesale suppliers, all tubes complete with guarantee card. By return despatch. Terms: Cash with order, s.a.e. all enquiries.

14in. types. AW36/20, AW36/21, AW36/80, MW36/24, CRM141, CRM144, CME1402 etc.	£4 17 6
17in. types. MW43/80, MW43/80, CRM173, CME1702 MW43/69 CRM172, AW43/88, AW43/89, CME1703, CME1705 etc	£4 17 6
19in. types. AW47/90, AW47/91, CME1901, CME1903, CME1902, C19AH	£4 19 6
21in. types. AW53/88, AW53/89, CME2101, CME2303	£6 12 0
MW53/80, AW53/80, MW53/20, CRM211/2	£8 18 10
23in. types. AW59/90, AW59/91, CME2301, CME2303	£6 12 0
23in. Twin Panel. CME2306, A59-16W	£13 1 0
23in. Panorama. A59/11W etc.	£12 0 0
19in. Twin Panel. A47-13W, CME1906 etc.	£10 1 0
19in. Panorama. A47/11W etc.	£9 0 0

We stock all types of tubes.

Large stocks of valves, transistors components. L.O.P.T.'s, Electrolube, Servisol switch cleaner, Multicore solder. Service Tools.

WILLOW VALE ELECTRONICS LTD.

The Service Dept. Wholesalers, 4 The Broadway, Hanwell, London, W.7. Tel: 01-567 2971/5400
CATALOGUE TRADE ONLY. S.A.E. Please

RECEIVERS & COMPONENTS (continued)

SIGNAL INJECTOR. Transistorised square wave generator probe, British Made, only 19/6, P & P 1/6 S A E for details and lists WILSIE ELECTRONICS LTD., 6 Copley Road, Doncaster, Yorks.

BRAND NEW ELECTROLYTICS, 15 Volt, 1, 2, 5, 6, 8, 10, 15, 20, 30, 40, 50, 100 mfd. 7/6 dozen, postage 1/-. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield 8.

TINY TRANSISTOR RELAY for model control, light switches, experiments etc. Only 1in. square, 330Ω coil, 30/- post free. H. R. RADIO, 174 Bramall Lane, Sheffield. S2 4RF.

POWERFUL HI FI AMPLIFYING EQUIPMENT. Kilowatt Racked Amplifiers £195, unvalued £145. 30 watt for Rack Mounting £15. Leak TL12 Amplifiers with Pre-amp Mixers £18. Electrostatic Speakers Acoustical Mfg. £35. Voigt Corner Horns with P.M. units £12. Williamson 10 watt by Rogers £10. All perfect. Sold subject Buyer's collection, after inspection/demonstration. Reduction for bulk purchase. **WIRED COLOUR VISION LTD.** 8 Milfield Road, Whickham, Newcastle upon Tyne. Telephone Whickham 887351.

COMPLETE RANGE of Amateur, Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

OFFERS FOR R155 RECEIVER. Write: SELECTRON, 22 Spencer Road, Acton, London W.3.

Stella Nine Range Cases

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES which are made to fit Standard Alloy Chassis

Width	Depth	4" Height £ s. d.	6" Height £ s. d.	7 1/2" Height £ s. d.
6 1/2"	3 1/2"	12 6	15 0	18 0
6 1/2"	4 1/2"	13 6	18 0	1 0 0
8 1/2"	3 1/2"	15 0	1 0 0	1 1 0
8 1/2"	4 1/2"	1 1 0	1 6 6	1 11 3
10 1/2"	3 1/2"	1 1 0	1 6 6	1 11 0
10 1/2"	4 1/2"	1 8 0	1 14 0	1 17 6
12 1/2"	3 1/2"	1 16 0	2 3 0	2 7 3
14 1/2"	3 1/2"	1 5 0	1 11 6	1 14 0
14 1/2"	4 1/2"	2 3 0	2 15 0	2 18 6
16 1/2"	3 1/2"	1 18 6	2 6 3	2 11 6
16 1/2"	4 1/2"	2 10 0	3 5 0	3 11 9

Cases—Post 4s. 6d. per order.
Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases All 2 1/4" Walls

6" x 3"	6" x 4"	8" x 3"	8" x 4"	10" x 3"	10" x 4"	12" x 3"	12" x 4"	14" x 3"	14" x 4"
5 s. d.	5 s. d.	5 s. d.	5 s. d.	5 s. d.	5 s. d.	5 s. d.	5 s. d.	5 s. d.	5 s. d.
10" x 7"	12" x 3"	12" x 3"	12" x 3"	12" x 3"	12" x 3"	12" x 3"	12" x 3"	12" x 3"	12" x 3"
10 s. d.	10 s. d.	10 s. d.	10 s. d.	10 s. d.	10 s. d.	10 s. d.	10 s. d.	10 s. d.	10 s. d.

Chassis—Post 3s. 0d. per order.
Discounts available on quantities.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases
46 LOWFIELD ROAD
STOCKPORT - CHESHIRE
Tel: 061-480 2179

RECEIVERS & COMPONENTS (continued)

ELECTROVALUE

Everything brand new
and exactly as specified

BARGAINS IN NEW TRANSISTORS

All power types supplied with free insulating sets.

2N696	5/6	2N3705	3/5
2N697	6/-	2N3706	3/5
2N706	3/5	2N3707	4/-
2N1132	13/-	2N3709	2/9
2N1302	4/-	2N3709	3/
2N1303	4/-	2N3710	3/3
2N1304	4/-	2N3711	3/11
2N1305	4/-	2N3711	2/16
2N1306	6/9	2N3714	2/11
2N1307	6/9	2N3819	6/-
2N1308	6/9	2N4005	4/9
2N1309	3/9	2N4005	4/-
2N1613	6/9	2N4006	4/3
2N1711	7/4	2N4011	4/6
2N2147	13/6	2N4062	4/5
2N2218	11/6	2N4066	2/11
2N2369A	6/9	2N4296	2/11
2N2646	6/9	2N4299	2/11
2N2924	6/-	2N4291	2/11
2N2925	6/9	2N4292	2/11
2N2926/R	2/9	2N4443	2/11
2N2926/O	2/9	40362	12/6
2N2926/Y	1/9	40362	18/9
2N2926/G	2/3	AC126	4/6
2N3053	3/9	AC128	6/-
2N3054	15/6	AC176	6/3
2N3055	16/6	AC177	6/3
2N3391A	3/9	AC177	2/3
2N3702	3/6	ACY40	3/6
2N3703	3/6	AD149	17/6
2N3704	3/9	AF124	7/6

AF127	7/-	BC168	9/-
AF166	20/-	BC169	2/3
BS041	13/6	BD121	13/6
BC107	3/6	BF194	7/-
BC108	3/-	BF194	12/3
BC109	3/6	BF194	8/3
BC126	6/3	BF194	7/9
BC126	13/-	BF194	4/9
BC147	4/3	BF194	4/3
BC148	3/3	EC401	4/-
BC149	4/3	M481	2/7
BC167	2/3	M481	8/1

NKT271	4/3	UA45	1/3
NKT274	4/3	UA300	2/6
NKT275	2/1	UA302	2/-
NKT405	14/10	OC71	5/6
NKT454	14/6	OC71	8/3
NKT405	18/-	P346A	6/9
NKT791	6/-	T1560	6/6
OA47	1/9	T1561	6/6
OA90	1/8	T81	1/9
OA91	1/8	T84	2/3

RESISTORS
1W, 5%, 1/10 doz. 14/6 per 100. 4.7Ω to 1MΩ
1W, 10%, 1/9 doz. 13/6 per 100. 4.7Ω to 10MΩ
1W, 5%, 2/2 doz. 17/- per 100. 4.7Ω to 10MΩ
1W, 2% tin oxide Electroval TR5. 10d each, 9d each for 25 to 99, 10Ω to 1MΩ.

MYLAR FILM CAPACITORS 100 100V
-001, -002, -005, -01, -02, -03, -05, 5d ea. 1μF 7d ea.
CERAMIC DISC CAPACITORS 20% TOLERANCE
500V wkg: 1000pF, 2000pF, 5000pF. 4d ea.
50V wkg: -01μF, -02μF, -05μF. 4d ea.

MINIATURE ELECTROLYTICS
5μF, 10μF, 25μF, 50μF all 10 volts, 9d ea.
5μF, 10μF, 25 volts, 9d ea.
25μF, 50μF, 25 volts 1/- ea.

PEAK SOUND PRODUCTS
PA12-15 Amplifier kit \$3.19.6 net
P8/45/K Power Supply kit \$4.19 net
KP/P2 Pre-amp kit \$1.70 net
KP/C2 Tone filter kit 19/6 net
Accessories: heat sink, matrix board and Cir-Kit for PA12-15, 12/-
Mono volume controls 2/6.
Mono tone controls 5/-
Stereo volume and balance controls 17/-
Stereo tone controls 17/-
Input selector switch 4/9

ALL GOODS BRAND NEW—NO SURPLUS
1988 CATALOGUE now ready. Send 1/6 for your copy.

COMPONENT DISCOUNTS
10% on total order over \$3.00. 15% on total order over \$10.00, unless stated otherwise.

POSTAGE AND PACKING on orders up to \$1, add 1/-; over, post free in U.K.

OVERSEAS ORDERS WELCOMED. Carriage charged at cost.

ELECTROVALUE

Dept. P.W.4

38A St. Judes Road, Englefield Green, Egham, Surrey.
Telephone: Egham 5533 (STD 0784-3)

RECEIVERS & COMPONENTS (continued)

BRAND NEW SEMICONDUCTORS

IN914	2/-	ACV07	8/6	BF194	8/6	MPF106	8/-
18020	3/6	ACY17	5/-	BFX29	12/6	NKT261	4/6
18021	4/-	ACY18	5/-	BFX34	8/-	NKT264	4/6
2N706	3/6	ACY19	5/-	BFX85	10/-	NKT40315/-	
2N706A	3/6	ACY20	4/-	BFY50	4/6	NKT40515/-	
2N1302	4/6	AD149	8/-	BFY51	4/6	NKT781	6/-
2N1303	4/6	AF114	5/-	BFY52	4/6	OC28	6/6
2N1304	4/6	AF116	5/-	BSX19	5/6	OC35	6/6
2N1305	5/6	AF117	5/-	BSX20	5/6	OC36	6/6
2N16014/-		ASY26	4/6	BSY26	4/-	OC44	3/-
2N2220	8/-	ASY28	5/6	BSY27	4/-	OC45	2/6
2N2694A	5/-	BC107	3/6	BSY28	4/-	OC71	2/6
2N2646	11/6	BC108	3/6	BSY38	4/6	OC72	2/6
2N2926	3/6	BC109	3/6	BSY39	4/6	OC81	4/-
2N3053	6/6	BCY70	5/6	BSY40	5/6	OC200	5/6
2N3055	15/-	BCV71	9/-	BSY85A	5/6	OC201	5/6
2N3702	4/-	BCY72	5/-	BY100	4/6	OC202	8/6
2N3707	4/-	BF180	8/6	MPF102	8/6	OC271	8/6
AC187	12/-	BF181	8/6	MPF103	7/-	OA81	1/6
AC188	12/-	BF184	7/6	MPF104	7/6	OA202	2/-

Send 6d. stamp for complete list. Over 1,000 types Semiconductor in stock. Capacitors, Resistors and Pots also available.

A. MARSHALL & SON (London) LTD.,
28 Cricklewood Broadway, London, N.W.2.
01-452 0181/2/3

WE ARE BREAKING UP COMPUTERS

EX COMPUTER PRINTED CIRCUIT PANELS
2in x 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc.

Our price, 10 boards 10/- P. & P. 2/-. With a guaranteed minimum of 35 transistors.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. 100 boards 65/- P. & P. 6/6. With a guaranteed minimum of 350 transistors.

PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/- P. & P. 2/-.

NPN GERMANIUM T051 WATT POWER TRANSISTORS on small heat sink, on 2in x 4in panel. 5 for 10/- P. & P. 2/-.

POWER TRANSISTORS sim. to 2N174 ex eqpt., 4 for 10/- P. & P. 2/-.

POWER TRANSISTORS sim. to 2N174 ON Finned Heat Sink (10D) 4 for £1, P. & P. 3/-.

LONG ARM TOGGLE SWITCHES ex eqpt. SPST 13/6 doz., DPST 15/- doz. P. & P. all types 2/- doz.

ORGAN BUILDERS' SPECIAL 500 T018 TRANSISTORS on panels. £4, P. & P. 6/-.

OVERLOAD CUT OUTS. Panel mounting in the following values... 5/- each, 2, 3, 4, 5, 7, 8 amp. P. & P. 1/6.

MINIATURE GLASS NEONS, 12/6 doz. P. & P. 1/6.
150 PIV. 10 amp. **BRIDGE RECTIFIERS** on FINNED HEAT SINK. 12/- + 2/- P. & P. ea.

LARGE CAPACITY ELECTROLYTICS
4 1/2in, 2in diam. Screw terminals.
All at 6/- each + 1/6 each P. & P.
4,000mF 72V d.c. wkg.
10,000mF 25V d.c. wkg.
6,600mF 45V d.c. wkg.
1,500mF 150V d.c. wkg.
16,000mF 25V d.c. wkg.
25,000mF 12V d.c. wkg.

KEYTRONICS, 52 Earls Court Road
London, W.8. Mail order only

AERIALS

Enthusiasts THE T.M.P. EXPERIMENTAL AERIAL KIT

A unique collection of alloy elements, dipoles, booms, clamps, mast reflectors, nuts & bolts, cables even a compass! etc., to make up various experimental aerials to cover all bands.

This includes TV transmissions, SW for the radio amateur, VHF for BBC FM. Amateurs on 2 and 4 Mtrs, Aircraft, Police etc., UHF for experiments on BBC 2 and Ultra High Frequencies. These Kits can be used indoor or outdoor. Robust construction with simplified detailed plans for easy assembly.

The Wonder T.M.P. Kit costs only 89/6—no extra for carriage.

Despatched to any address in UK within 7 days.

TUBULAR METAL PRODUCTS
7 LOWESMOOR TERRACE,
WORCESTER

MOBILE S.W. LISTENERS

The Halson Mobile Antenna for
**AMATEUR RECEIVING and
TRANSMITTING**

The most efficient mobile All-Band Whip on the market. COILS FOR ALL BANDS. Complete with one coil £6.17.6, plus 3/6. Extra coils £3.17.6, plus 3/6.

From leading amateur radio stores or
direct from the manufacturers:

HALSON ELECTRICAL SERVICES
Dover Road, off Ansdell Road,
Blackpool.

ACCURATE HOLES IN BRASS, STEEL, ALUMINIUM, FIBRE PLASTIC

It's easy with-
Tompkins
hole
punch

FROM 1/16" AT
13/6
TO 3" DIA. AT 120/-

Used and trusted by engineers, mechanics, plumbers etc. Cuts most materials down to 16-gauge mild steel. A boon for the handyman who needs accurate tools. Available in sizes from 1/16" to 3" dia. at 120/-.

Send now for full details of specifications to:
TOMPKINS AND LONGMAN LIMITED
237 Gipsy Road, West Norwood, London, S.E.27

GENUINE BARGAIN YOU CAN'T AFFORD TO MISS GARRARD SP25 MkII

- ★ Fitted Sonotone 9TA Cartridge
- ★ Mounted on Plinth Perspex cover
- ★ Connected ready to plug in
- ★ Guaranteed

★ ONLY **19 Gns** TODAY'S VALUE **£26**

Cash with order only
Mail Order Dept.

D. T. WICKS & CO.

49 North Station Road, Colchester,
Essex. Tel: Col. 78807 (U.K. only)

We guarantee your satisfaction

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5 4/9	DY86 5/6	EZ80 3/9	PL500 12/9
1R5 4/3	DY87 5/6	EZ81 4/6	PL504 13/3
1T4 2/9	EABC80 5/9	KT61 8/3	PY32 10/-
384 5/9	EBG41 8/-	KT66 15/9	PY33 10/-
3Y4 5/6	EBF80 6/-	N78 14/6	PY81 5/-
6A4Q5 4/6	EBF89 5/9	PABC80 6/9	PY82 5/-
6L18 6/-	ECC81 3/9	PC86 10/3	PY83 5/3
30C18 8/9	ECC82 4/3	PC88 10/3	PY88 6/-
30FL1 12/6	ECC83 4/9	PC97 7/9	PY800 7/3
30FL12 14/3	ECC85 5/6	PC900 8/-	PY801 6/6
30FL14 10/3	ECC85 5/6	PC934 6/3	R19 5/3
30P4 11/6	ECC82 10/6	PC989 9/9	U25 12/9
30P19 11/6	ECC81 5/9	PCC189 11/6	U26 11/6
30PL1 12/6	ECC80 7/3	PCF80 6/3	U191 12/3
CH35 9/9	ECL82 6/3	PCF82 5/9	UABC80 5/9
CL33 17/6	ECL83 5/9	PCF801 6/9	UBC41 8/3
DAC32 6/9	ECL86 7/6	PCF805 8/9	UBF85 6/3
DAF91 4/3	EF39 3/6	PCF808 10/3	UCR4 7/9
DAF96 8/3	EF80 5/9	PCL82 6/9	UCR85 6/-
DF33 7/6	EF85 5/-	PCL83 8/9	UCF80 8/-
DF91 2/9	EF86 6/3	PCL84 7/-	UCH42 9/6
DF96 5/11	EF89 4/9	PCL85 8/9	UCH81 6/9
DK32 6/9	EF183 5/9	PCL86 8/3	UCL82 6/9
DK91 4/9	EF184 5/6	PFL200 12/-	UP41 9/6
DK96 6/6	EL33 8/3	PL36 9/9	UF89 6/6
DL35 4/9	EL41 10/3	PL81 7/-	UL41 10/3
DL82 5/9	EL84 4/6	PL82 6/9	UL84 6/9
DL94 5/6	EY81 7/3	PL83 6/9	UY41 6/6
DL96 6/9	EY85 6/6	PL84 6/9	UY85 5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

ADD NEW EXCITING STEREO EFFECTS TO YOUR LISTENING



with a Dewtron "NEW DIMENSIONS" 3-Dimensional effects amplifier. Gives Big Hall Stereo effect to most radios, tapes, etc. PLUS fully adjustable echo, vibrato and tone. 9 volt model, 8 gns. Speaker, 25/- extra. 6/12V car model, 10 gns. incl. speaker. Post and ins. 5/- either model. Write now—right now.

D.E.W. LTD.
P.W., RINGWOOD ROAD, FERNDOWN, DORSET

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDE, YORKS.
Tel. Cleckheaton 2866

Indicator Unit type 26

Size 12 x 9 x 9 in. with outer case. Fitted with 2 1/2" tube C.R.T. type CV1526. Nine B7C valves. Clean condition, but not tested. 32/6, p. & p. 10/-.

Lumulator and Secant Gear Unit. Delight for the model maker. 12/6, p. & p. 8/6.

Silicon Rectifier 500mA, 800 P.I.V. No diodes. 2/6, post paid. 24/- per dozen, post paid.

Jap Ear Piece. Magnetic 8 ohm. Small and large plug. 1/11, post paid.

Reclaimed TV tubes with six months guarantee. 17in. type AW43/88, AW43/80, 40/-; MW43/69, 30/-; 14in. types, 17/-; All tubes, 12/- carriage.

Speakers removed from TV sets. All PM and 3 ohms. 8in. round and 8 x 5in., 6/6, p. & p. 3/6.

6in. round, 3/-, p. & p. 3/-; 6 for 24/-, post paid.

6 x 4in., 3/-, p. & p. 3/-; 6 for 24/-, post paid.

7 x 4in., 5/-, p. & p. 3/-; 6 for 34/-, post paid.

5in. round, 3/-, p. & p. 3/-; 6 for 24/-, post paid.

Slot Speakers, 8 x 2 1/2in., 5/-, p. & p. 3/-; 6 for 30/-, post paid.

Untested 12-channel 14in. TV sets, 20/-, carriage 15/-. Passenger train double rate.

Untested Pye, KB, RDG, Ekco 17in. TV sets. Bush 17in. TV sets, 50/- each, carriage 15/-.

Passenger train double rate.

VALVE LIST

Ex Equipment. 3 months' guarantee

Single Valves Post 7d., over 3 Valves p. & p. paid. 10P1, EF80, EB91, ECL80, EF50, PY82, PZ30, 20P3. All at 10/- per dozen, post paid.

ABP12 1/8	PCL83 5/-	6BW7 2/6
EB91 9d.	PL36 5/-	6K7 1/9
EF85 8/-	PL38 6/-	6U4 5/-
EBF80 2/-	PL81 4/-	6V6 1/9
ECC81 3/-	PY33 5/-	6P28 5/-
ECC82 3/-	PY81 1/6	10P13 2/6
ECC83 4/-	PY82 1/6	185BT 8/6
ECL80 1/8	PZ30 5/-	20D1 3/-
EF50 1/-	U191 5/-	20P1 5/-
EF80 1/8	U281 5/-	20P3 2/6
EF91 9d.	U282 5/-	30PL1 5/-
EY51 2/6	U301 5/-	30P13 5/-
EY86 5/-	U329 5/-	30F5 2/6
PC84 2/-	U251 5/-	30FL1 5/-
PCF80 2/-	6B8 1/8	630L2 5/-
PCL82 4/-		

PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING TO
ADVERTISEMENTS

10w AMPLIFIER

SSAR3. 10W. PUSH-PULL OUTPUT. TW99 OUTPUT TRANSFORMER. 4 VALVE: EF94, ECC81, EL90 (2). FULLY CONSTRUCTED ON CHASSIS. NEW AND BOXED WITH CIRCUIT DRAWING. 22.10.0. P. & P. 10/-.

MIXER UNITS. Type 18. H.F. M.F. L.F. Valve V882. 10/-, P. & P. 2/6.

FLEXIBLE METAL TUBING. Galvanised. 1/2in. int. diam. 35/-, 100ft. P. & P. 7/6.

FIELD TELEPHONES TYPE "F". 32/6. P. & P. 7/6.

CHASSIS UNIT. 13 valves: ECC82 (5), EB91 (6), EF91 (2). 60 Resistors. Capacitors etc. Valve Cans and Bases. Multicon Plugs. 22/-, P. & P. 6/-.

RESISTORS. Mixed parcel of 200. 20/-, P. & P. 2/6.

RESISTORS. Variable. Mixed parcel of 30. 20/-, P. & P. 2/6.

TRANSFORMERS. 6STR 894. Pri. 220-230-250V. Secondary 6-3V (2a), 300-350-390V (35mA), 80-90-100V (10mA). 30/-, P. & P. 5/-.

8STR073. Primary 220-230V. Secondary 35V (0-5a), 6-3V (2a), 225-0-225V (27mA) 25/-, P. & P. 5/-.

S.A.E. FULL LIST

STATUS SUPPLIES

STATUS HOUSE, WILKINSON AVENUE, BLACKPOOL

AMAZING MINI-DRILL



FOR PRECISION
**MODEL
WORK**

+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL Super Kit (extra power, interchangeable chuck) 79/6, p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money ref. g'tee.

MERLIN SUPPLY CO.

Dept. PW2D, Nailsea, Bristol BS19 2LP

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling

MINIMUM CHARGE 2/6. No C.O.D. orders accepted.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANGHAM 8403
Open all day Saturday

OA2	6/-	6AJ8	5/8	6BW6	13/6	6L12	5/-
OA3	8/6	6AK5	5/-	6BW7	12/-	6L18	5/-
OB2	6/-	6AK6	11/6	6B26	6/-	6LD20	5/8
OB3	6/-	6AL5	8/-	6B27	10/-	6N7GT	6/8
OC3	6/6	6AM4	22/-	6C4	5/8	6P1	11/6
OD3	6/-	6AM5	5/-	6C6GT	6/6	6P25	13/-
OM10	11/-	6AM6	4/-	6C6	4/-	6P28	12/-
1AX2	12/-	6AM8	8/-	6C8G	7/-	6Q7	7/-
1B3GT	7/-	6AN8	10/-	6C9	17/8	68A7	7/-
1C5GT	6/-	6AQ5	6/-	6CB8	5/-	68G7	7/-
1O4GT	8/-	6AQ8	10/-	6CD6GA	22/-	68H7	4/8
1R5GT	7/-	6AR5	6/-	6CG7	7/-	68J7	7/-
1L4	3/-	6AR6	6/-	6CH8	11/-	68L7GT	6/-
1R5	6/-	6AS5	6/6	6CL6	9/-	68N7GT	6/8
1R4	5/-	6AS6	7/-	6CL8	15/-	68R7	7/-
1B5	4/6	6AT6	4/6	6CU6	12/-	68S7	3/-
1L4	4/4	6AU4GTA	6/-	6CW4	12/-	6T8	6/-
1U5	8/6	6AV5GTA	10/-	6CY5	7/6	6U4GT	12/-
1V2	9/-	6AV6	5/-	6D3	7/6	6U8	6/-
1X2B	7/-	6AV8	10/-	6DC6	13/6	6V6GT	6/-
1Z2	25/-	6AV9GTA	10/-	6DK6	8/-	6X4	4/8
2C28A	8/-	6AY6	5/6	6DKE	8/-	6X6GT	6/-
2C40	8/-	6AW8A11/-	6/-	6DKE6	11/-	6X8	11/-
2C51	8/-	6AX4GTB	8/-	6D84	16/-	6V6G	11/8
2C6W4	12/-	6AX5GT	8/-	6D78	7/6	6X5	13/6
2D21	6/-	6AX6GT	8/-	6E78	11/-	7X4	9/-
2E26	27/6	6AX7GT	12/6	6E8W6	12/-	7Z4	7/6
2X2	5/-	6AX8	10/-	6F6GB	6/8	9BW6	7/-
3A3	11/-	6BAX7	10/-	6F7	9/-	9D2	3/6
3A4	4/-	6BAX8	15/-	6F11	6/-	9D7	6/8
3B28	40/-	6B8G	2/6	6F13	9/8	10C2	10/-
3Q4	7/6	6BA6	4/-	6F14	12/-	10D2	8/-
3B4	6/-	6BA7	15/-	6F15	11/-	10F1	18/-
3V4	6/6	6BC5	3/6	6F17	9/-	10F9	10/-
4B32	80/-	6BE6	4/6	6F18	7/8	10F18	7/8
5R4G10	6/6	6BF6	15/-	6F23	15/-	10L1	7/6
5U4G	6/6	6BF8	15/-	6F24	13/-	10LD11	10/-
5U4G6	7/-	6BF9	15/-	6F25	14/-	10P13	12/-
5U8	8/-	6BG6G	11/-	6F28	13/-	10P14	16/-
5Y3GT	5/6	6BH6	8/-	6GK6	12/-	12AC8	7/-
5Z3	8/-	6BK6	8/-	6GK6	12/-	12AD6	6/-
5Z4G	7/-	6BK8	20/-	6GW6	11/-	12AL5	7/6
6B0L2	14/-	6BL7GA	9/-	6J4	4/-	12AQ5	7/-
6A8G	5/6	6BL7GA	9/-	6J5GT	5/8	12AT6	4/6
6A84	6/6	6B6	11/-	6J6	3/6	12AT7	6/-
6A87	4/6	6B6	7/6	6J7	8/-	12A7C	6/-
6AC7	4/6	6B8	8/-	6K6GT	9/-	12A7D	6/-
6AD4	15/-	6BQGT	7/6	6K7	7/6	12A7E	6/-
6A65	9/-	6BQ7A	7/6	6K25	15/-	12A7F	6/-
6AG7	6/6	6B7	16/-	6L1	12/-	12A7G	6/-
6A76	10/-	6BR8	12/6	6L6GT	7/6	12B2A	6/-
6A75	9/-	6B87	25/-	6L7	6/-	12B2B	6/-

First Quality Fully Guaranteed



ELECTRONIC VALVES

Combined effect of increase in Purchase Tax and S.E.T. and Import restrictions forced us to introduce an increase of 1d. per shilling which must be added to the total of each order.

12BH7	6/-	30FL1	15/-	807	9/-	DY86	6/-
12BT6	4/8	30FL12	17/6	811A	30/-	DY87	6/6
12BY7	10/-	30FL13	8/-	812A	60/-	DY802	9/-
12CU6	12/-	30FL14	14/6	813	75/-	E55L	52/6
12DQ7	10/-	30L1	6/-	837	15/-	E23F	20/-
12E1	20/-	30L15	16/-	866A	14/-	E23F	20/-
12E14	52/6	30L17	16/-	884	10/-	E88C	22/-
12K5	10/-	30P12	15/-	8670	10/-	E88C	18/8
12K8	8/-	30P14	14/-	5751	11/-	E130L	100/-
12Q7GT	6/-	30P15	15/-	5753	12/-	E180F	17/8
12S7GT	6/-	30P13	17/6	5886	40/-	EAF80110/-	6/-
12S7GT	6/-	30P14	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P15	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P16	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P17	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P18	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P19	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P20	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P21	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P22	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P23	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P24	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P25	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P26	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P27	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P28	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P29	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P30	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P31	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P32	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P33	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P34	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P35	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P36	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P37	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P38	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P39	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P40	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P41	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P42	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P43	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P44	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P45	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P46	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P47	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P48	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P49	17/6	6080	27/8	EAB80	8/-
12S7GT	6/-	30P50	17/6	6080	27/8	EAB80	8/-

ECF86	9/6	EL821	10/-	PCF86	8/6	U25	14/6
ECF86	9/6	EL822	17/-	PCF87	15/-	U26	14/6
ECF86	9/6	EL823	17/-	PCF88	15/-	U27	14/6
ECF86	10/-	EL824	15/-	PCF80014/		U28	8/6
ECF86	10/-	EL825	15/-	PCF801	9/6	U33	80/-
ECF86	8/6	EL826	12/6	PCF802	9/6	U76	4/6
ECF86	8/6	EL827	12/6	PCF802	9/6	U77	10/6
ECF86	8/6	EL828	12/6	PCF80612/		U81	8/6
ECF86	8/6	EL829	12/6	PCF80612/		U82	8/6
ECF86	8/6	EL830	12/6	PCF80614/		U83	8/6
ECF86	7/6	EL831	10/6	PCF80614/		U84	8/6
ECF86	7/6	EL832	10/6	PCF80614/		U85	8/6
ECF86	7/6	EL833	10/6	PCF80614/		U86	8/6
ECF86	7/6	EL989	10/6	PCF80614/		U242	8/6
ECF86	7/6	EL990	10/6	PCF80614/		U243	8/6</

PRACTICAL WIRELESS

blueprints

The following blueprints are available from stock. Descriptive text is not available but the date of issue is shown for each blueprint. Send, preferably, a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, I.P.C. Magazines, Tower House, Southampton Street, London, W.C.2.

The Strand Amplifier .. } (Oct. 1962) 5/-
The PW Signal Generator .. }

The Berkeley Loudspeaker Enclosure .. } (Dec. 1962) 5/-
The Luxembourg Tuner .. }

The PW Britannic Two .. } (May 1962) 6/-
The PW Mercury Six .. }

Beginner's Short Wave Two .. } (Nov. 1963) 5/-
S.W. Listener's Guide .. }

The Celeste 7-transistor Portable Radio .. } (June 1963) 5/-
The Spinette Record Player .. }

Transistor Radio Mains Unit .. } (June 1964) 5/-
7 Mc/s Transceiver .. }

The Citizen (December 1961) 5/-

The Mini-amp (November 1961) 5/-

The Beginner's Short Wave Superhet (Dec. 1964) 5/-

The Empire 7 Three-band Receiver (May 1965) .. 5/-

Electronic Hawaiian Guitar (June 1965) 5/-

Progressive SW Superhet (February 1966) 5/-

Beginner's 5-Band Receiver .. } (Dec. 1966) 5/-
Home Intercom Unit .. }

★ PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL RADIO, TV OR AUDIO EQUIPMENT. ★

PRACTICAL WIRELESS

query service

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

QUERY COUPON

This coupon is available until 9th May, 1969 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, MAY 1969


ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

SOLID STATE-HIGH FIDELITY AUDIO EQUIPMENT

Mono or Stereo Audio. Equipment developed from Dinsdale Mk.II—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM £15.5.0

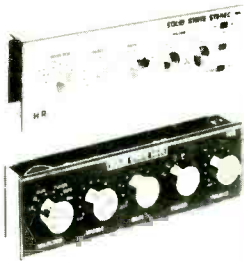THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS



All units available separately.

SEND FOR FREE BROCHURE (No. 21) TODAY! DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



MA7 MONO £8.10.0

OR THE STEREO POST PACKING 5/- EITHER MODEL

INTEGRATED TRANSISTOR AMPLIFIERS MA66 12 WATTS STEREO

We are pleased to offer two new designs with the choice of either mono or stereo systems. These BRITISH DESIGNED UNITS favour the user in so many ways— with fantastic power and quality with far greater adaptability, with freedom for battery or mains operation.

MA66 £16.10.0 OPTIONAL MAINS UNIT PS20 62/6d. p.p. 4/-

For complete listening satisfaction choose either the—

Illustrated leaflets 12 and 14 FREE on request.



DO IT YOURSELF MW/LW PORTABLE

New printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local and Continental stations.

TOTAL COST £6.19.6. P.P. 4/6 TO BUILD Send for Brochure 1



NEW MODELS NOMBREX TRANSISTORISED Test Equipment

MODEL	PRICE	Leaflet
29s Gen.	£ 21 0 0	No. 25
29x Xtal RF Gen.	29 10 0	25
30 Audio Generator	19 10 0	24
31 R.F. Generator	12 10 0	25
32 C.R. Bridge	10 10 0	26
33 Inductance Bridge	20 0 0	25

ELECTRONIC ORGANS KITS TO BUILD YOURSELF AND COMPLETE UNITS.

THE MAYFAIR

A completely new development in portable electronic musical instruments and a new field for the home constructor. The "MAYFAIR" produces a multitude of the most pleasing sounds with a wide range of tone colours suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Supplied as a kit of parts which includes 165 transistors, printed circuit panels, special fully sprung and depth of touch adjusted keyboard, attractive vinyl covered cabinet with carry handle.

Deferred terms available.
COMPLETE KIT
Deposit £29.19.0.
12 monthly payments of £8.
Total £44.8.0
TOTAL £112.19.0



BUILT AND TESTED
Deposit £36.8.0 and
12 monthly payments of £8.
Total £44.8.0
THE MAYFAIR
99 GNS. Brochure 9

THE GROSVENOR

THE GROSVENOR is designed for the more ambitious musician and has a much wider range than most commercial organs. It comprises 2-4 octave (49 note) keyboards and a thirteen note pedal board. It has four pitches (i.e. 8th, 4th, 2nd, 1st) on the upper or solo keyboard, three pitches (i.e. 16th, 8th, 4th) on the lower or accompaniment keyboard, two pitches (i.e. 16th, 8th) on the pedal board. Variable sustain on the solo keyboard and variable vibrato on both keyboards. It has 15 voices in the solo tone-forming unit, 10 voices in accompaniment tone-forming unit and 4 voices in the pedal tone-forming unit. All components and sections are available separately including the OAK CASE at £65.18.0.

THE GROSVENOR
Kits from £220.
Terms available
Brochure 9B

PRACTICAL ELECTRONICS - ELECTRONIC ORGAN KIT

We are able to supply parts as described in this issue. Details on request.
ORGAN COMPONENTS. Complete range in stock. 49 and 81 note keyboards.
• 2 to 5 amp Gold Contacts • Collis and Chokas • Reversion Springs and Units. • Stop Tabs and Assemblies. • Pedal Boards. • Rhodium and Gold Clad Wire. Also printed circuits, etc. Complete ranges for Transistorised Organs. Ask for new Price List with Details. Leaflet 9B

All enquiries to: ORGAN DEPT. Mr. EVANS



QUALITY CAR RADIOS

A precision engineered car radio that is perfect company for long hours on the road. Has quick push button operation for immediate station selection and choice of Medium or long wave frequency. Output of 3½ watts ensures crisp top quality sound even at high motoring speeds. Includes full accessories and instructions.
POSITIVE/NEGATIVE EARTH PRICE £12 12 0 pp. 4/6
MANUAL as above £8 19 6. but with single MW/LW Push Button

MULLARD 1 WATT AMPLIFIER

PORTABLE TRANSISTOR UNIT with volume control. Many uses. Intercoms. Baby Alarms. Guitar Practice. Telephone or Record Player Amplifier.
Optional Resine covered Wood cabinet 12 x 9 x 4 12 6
7 x 4 in speaker 17/6
Uses 7PB battery



45/- pp 3/6d

Ask for Leaflet 2

BUILD A QUALITY TAPE RECORDER

To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre amplifier which comes to you assembled on its printed circuit board—in fact every thing needed down to the last screw. For MAKING A SUPERB TAPE RECORDER which when built, will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED.



2 Track 36 gns.
P.P. 22/6 either model.
Kit comprises: Deck Amplifier. Cabinet and speaker, with MICROPHONE 7 in 1 200 Hz tape, spare spool. ALL UNITS AVAILABLE SEPARATELY
ASK FOR BROCHURE 6

VHF FM SUPERHET TUNER MKII

5-MULLARD TRANSISTORS & 4 DIODES - 300 Kc/s BANDWIDTH - PRINTED CIRCUIT CONSTRUCTION - HIGH FIDELITY REPRODUCTION MONO AND STEREO
A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and with the decoder stereophonic broadcasts. There is no doubt about it—VHF FM gives the real sound. Excellent stability economically priced.
TOTAL COST £8.19.6
DECODER £5.19.6 (CABINET 20/-)
ASK FOR LEAFLET 3.



NEW—MALLORY LONG LIFE MERCURY BATTERIES

50% OFF LIST PRICES
*RM12 1.35 volts 3600 mAh OUR PRICE 5/- each
Size 2 1/2 x 1 1/2 in. dia. *RM25 10.35 volts 300 mAh
Pack of 8. Size 2 1/2 x 1 1/2 in. dia.
OUR PRICE 10/- each
Easily split into eight 1.25v cells
These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required.

QUANTITIES AVAILABLE

TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1969 LIST OF 1000 types. Send for your FREE COPY TODAY (list 36)

S.C.R.'s from 5/-
Field Effect Transistors from 9/6
Power Transistors from 5/-
Diodes and Rectifiers from 1/6

GARRARD RECORD DECKS




BRAND NEW All below list price

	£ s. d.
2025 Mono/Stereo	8 8 0
3000 LM with 9TAHC	9 9 6
SP25 Mk II	11 19 0
AT70 Mk II	13 10 0
3500 Mono/Stereo	12 19 6
401	28 10 0
AP75	19 0 0
SL55	11 19 6
SL65	14 14 0
SL75	29 0 0
SL95	35 0 0
A70 Mk II	12 12 0

Send for New 8-Page Brochures
Complete range of accessories available

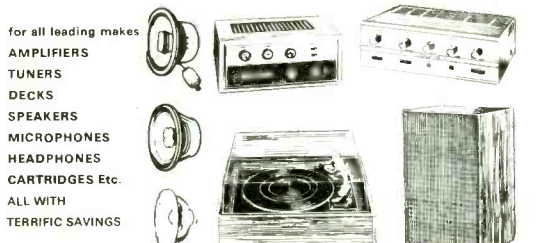VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE ROAD, AND SAVE UP TO £25 ON SEPARATE UNITS OR THE SYSTEM OF YOUR CHOICE



IT WILL PAY YOU TO PAY US A VISIT! COMPLETE SYSTEMS FROM £48—SAVE £12.10.0
SEND FOR NEW 8-PAGE ILLUSTRATED HI-FI LIST 16/M.

Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1969)

The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE

Complete with 10/- worth discount vouchers FREE WITH EVERY COPY
• 32 pages of transistors and semi-conductor devices, valves and crystals.
• 210 pages of components and equipment.
• 70 pages of microphones, decks and Hi-Fi equipment.

6,500 ITEMS

320 BIG PAGES

Send today 7/6 Post etc 2/-



HENRY'S RADIO LTD

OPEN MON.-SAT. 9 a.m.-6 p.m. THURS. 9 a.m.-1 p.m.

303 Edgware Road, London, W.2. Mail Order Dept. all types of Components, Organ Dept. (01) 723-1008/9
309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-6963