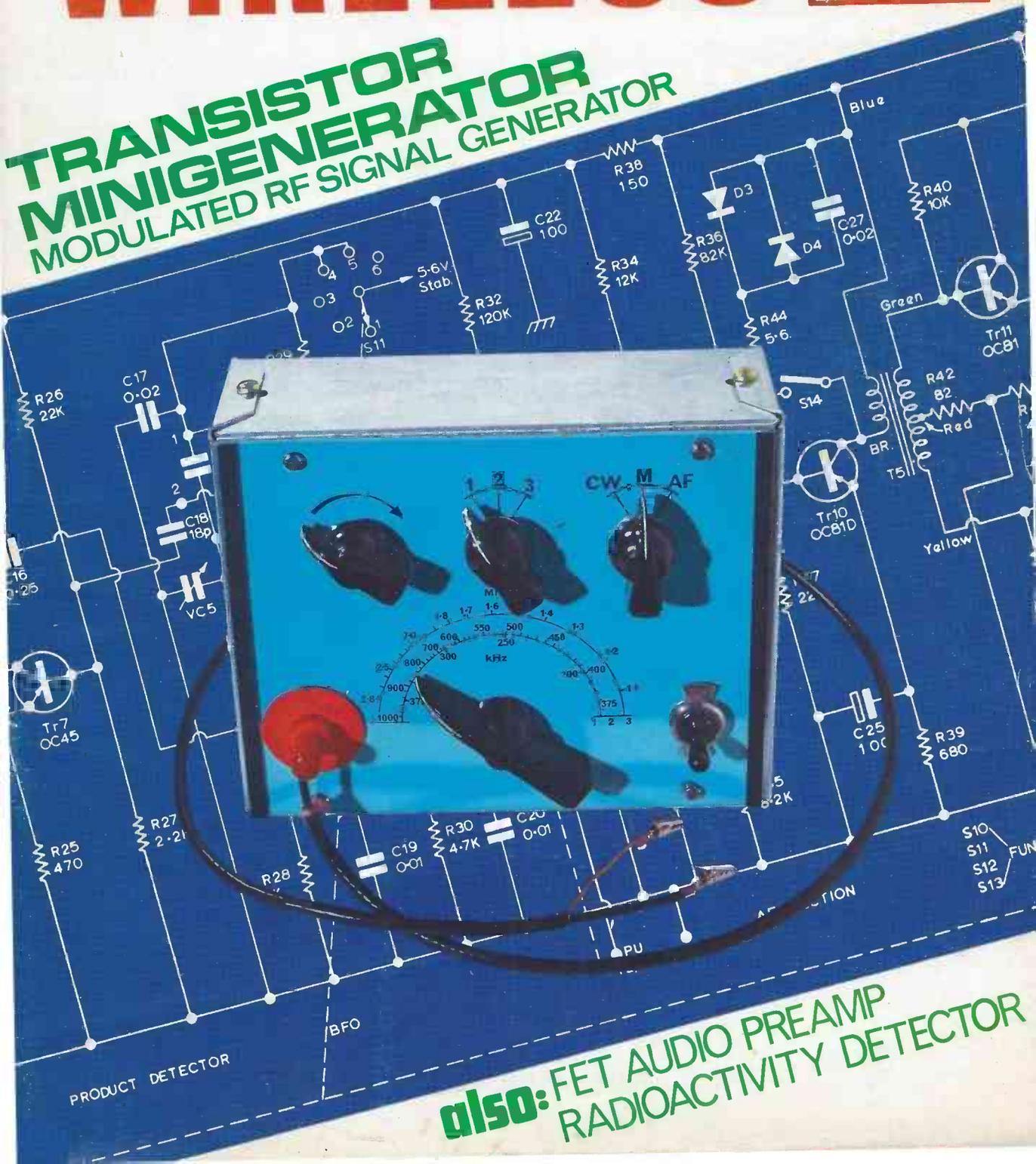


# PRACTICAL WIRELESS

APRIL 1970

3/6

## TRANSISTOR MINI GENERATOR MODULATED RF SIGNAL GENERATOR



also: FET AUDIO PREAMP  
RADIOACTIVITY DETECTOR

**Head Office and Warehouse**  
**4A WESTBOURNE GROVE**  
**LONDON W2**  
**Tel. PARK 5641/2/3**

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling

MINIMUM CHARGE 2/6. No C.O.D. orders accepted

PLEASE NOTE THAT THE VALVES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN

**Retail Shop**  
**65 TOTTENHAM COURT ROAD**  
**LONDON W1**  
**Tel. LANGHAM 8483**  
**Open all day Saturday**

0A2	6/6	6AW8A	11/1	6F15	11/-	10F18	8/-
0A3	9/-	6BA6	4/6	6F18	8/1	10L1	6/-
0B2	6/6	6BE6	5/-	6F22	6/6	10LD11	11/-
0B3	10/-	6BF5	15/6	6F23	15/6	10P13	11/-
0C3	7/-	6BF6	9/-	6F24	13/6	10P14	20/-
0D3	6/-	6BG6G	12/-	6F25	15/-	12AR5	10/-
1B3GT	7/6	6BH6	8/6	6F26	7/1	12AC6	7/6
1L4	3/6	6B16	8/6	6F28	14/-	12AD6	7/6
1R4	6/6	6BK4	21/-	6F29	6/6	12AL5	8/6
1R5	7/-	6BK7A	10/-	6F30	7/1	12AQ5	5/-
184	5/6	6BL8	7/-	614	9/6	12AT6	5/-
185	5/6	6BN5	8/6	615GT	6/1	12AT7	6/6
1T4	4/6	6BN6	8/6	617	8/6	12AU6	5/6
1U4	6/6	6BQ5	5/-	6K6GT	10/-	12AU7	6/6
1U9	9/6	6BQ7A	7/6	6K7	6/6	12AV6	6/6
1V2	9/6	6BR7	17/6	6K8G	6/6	12AV7	9/-
1X2B	7/6	6BR8	13/-	6K23	10/-	12AX7	7/6
2D21	6/6	6BS7	28/-	6K25	15/-	12AY7	13/6
3A5	10/-	6BW6	16/-	616GT	9/-	12BA4	10/-
3Q4	8/-	6BW7	13/6	617	6/6	12BA6	6/6
3S4	7/-	6BX6	5/-	618	6/6	12BA7	6/6
3V4	8/-	6BZ6	6/6	61D20	6/6	12BE6	6/6
3R4G	11/-	6C2GT	7/6	6N7GT	7/6	12BH7	7/6
3U4G	6/-	6C5GT	7/6	6P1	12/-	12B7	10/-
3U4GB	7/6	6C9	17/3	6P28	12/6	12BY5	10/-
3V4G	8/-	6CA4	5/6	6Q7	7/6	12K7G	7/6
3Y3GT	6/-	6CA7	10/6	6R7G	7/6	12Q7G	5/-
3Z1	9/-	6CB6	5/6	6S2	8/-	12S2C	7/6
3Z4G	8/6	6CDB6A	23/-	6S4A	11/-	12S2G	7/6
3Z4GT	8/6	6CDB6A	23/-	6S7	7/6	12S2H	7/6
6/30L2	15/-	6CG7	9/-	6S7G	6/6	12S17	5/6
6AB4	6/6	6CH6	11/-	6S17	7/6	12S2K	8/6
6AF4A	9/6	6CL6	10/6	6SK7	6/6	12S17GT	8/6
6AG7	7/6	6CW4	12/6	6SL7GT	6/6	12SN7GT	8/6
6AH6	10/-	6C5	8/-	6SN7GT	6/6	12S07	8/6
6A18	5/6	6C7	12/-	6S07	8/6	12S07	6/6
6AK5	6/6	6C8	12/-	6S17	7/6	12S07	6/6
6AK6	11/6	6DC6	13/6	618	6/6	20D1	9/6
6AL3	8/6	6DK6	8/6	614GT	12/6	20L1	20/-
6AL5	3/6	6DQ6B	12/-	618	7/6	20P1	10/-
6AM5	5/6	6DS4	15/-	6V6GT	6/6	20P3	12/-
6AM6	4/6	6E8	11/-	6X4	5/6	20P4	20/-
6AQ5	6/6	6EH7	6/6	6X5GT	5/6	20P5	20/-
6AQ6	10/-	6E7	7/6	6X8	11/-	20C5	9/6
6AR5	6/6	6EWE	12/-	6Y6G	12/6	21S6GT	7/6
6AR6	6/6	6F1	14/-	6W6	8/6	21Z6G	7/6
6AS7	16/-	6F6G	5/6	10D2	10/-	21Z6GT	12/-
6AT6	5/6	6F11	6/6	10D1	8/6	30A5	8/6
6AU6	5/6	6F12	4/6	10D2	8/6	30A3	8/6
6AV6	6/-	6F13	7/6	10F1	18/-	30C6	6/6
		6F14	12/-	10F9	10/-	30C15	15/-

## First Quality Fully Guaranteed



## ELECTRONIC VALVES

30C17	16/-	811A	30/-	DY802	10/-	ECH84	9/-
30C18	15/-	812A	30/-	E51	55/-	ECL80	9/-
30F5	17/-	86A	14/-	E10L	90/-	ECL81	6/6
30FL1	15/-	6080	27/6	E180F	10/-	ECL82	6/6
30FL12	10/6	6146	30/-	EAB C80	6/6	ECL83	12/6
30FL13	10/6	6146B	47/6	EAF42	10/-	ECL84	11/-
30FL14	15/6	6267	6/6	EBC33	9/-	ECL85	10/6
30L1	7/-	6360	25/-	EB41	10/6	ECL86	8/6
30L15	17/-	6919	42/-	EB90	5/6	EF37A	9/-
30L17	17/-	7199	15/-	EB81	8/6	EF39	8/6
30P12	16/-	7360	36/-	EB91	6/-	EF40	10/-
30P18	7/6	7586	25/-	EBF80	8/6	EF41	12/6
30P19	15/-	9002	6/6	EBF83	8/6	EF42	14/-
30PL1	15/6	9003	10/6	EBF89	6/6	EF55	13/6
30PL13	18/-	A231	18/-	EEL31	25/-	EF80	5/6
30PL14	17/-	A230	12/-	EEL38	10/6	EF84	8/6
35A3	11/-	CBL1	16/-	EC86	12/6	EF85	7/6
35A5	11/-	CBL31	17/-	EC88	12/6	EF86	6/6
35B5	13/-	CY31	17/-	EC90	6/6	EF89	5/6
35C5	7/6	DAF11	11/-	EC92	6/6	EF91	4/6
35D5	13/-	DAF91	5/6	EC93	9/6	EF92	7/6
35L6GT	9/6	DAF92	9/6	EC94	11/-	EF93	4/6
50C14	17/-	DAF96	7/6	EC95	11/-	EF94	5/6
50C15	17/-	DL1	17/6	EC98	6/6	EF95	6/6
50C16	17/-	DL2	17/6	EC99	6/6	EF96	4/6
50C17	17/-	DL3	17/6	EC99	6/6	EF97	10/6
50C18	17/-	DL4	17/6	EC99	6/6	EF98	10/6
50C19	17/-	DL5	17/6	EC99	6/6	EF99	10/6
50C20	17/-	DL6	17/6	EC99	6/6	EF99	10/6
50C21	17/-	DL7	17/6	EC99	6/6	EF99	10/6
50C100	17/-	DL86	17/6	EC99	6/6	EF99	10/6

EL42	11/6	N78	21/-	PL82	9/-	UABC80	6/9
EL81	10/6	PC86					

# VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

## On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

## WHICH OF THESE IS YOUR PET SUBJECT?

**RADIO ENGINEERING**  
Advanced Radio — Gen. Radio — Radio & TV Servicing — TV Eng. — Telecommunications — Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

**ELECTRICAL ENG.**  
Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Supply — Mining Elec. Engineering.

**CIVIL ENGINEERING**  
Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining Water Supply — Petrol Tech.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power? B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

British Institute of Engineering Technology  
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

## THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.**

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy *now*—FREE and without obligation.



## POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME .....

ADDRESS .....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**

# HENRY'S RADIO LTD.

# ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES

## TO BUILD YOURSELF

- \* PW Stereo Decoder (Reprint 45A 1/6d). £5 15 0 pp. 3/6  
OR with optional power supply £7 7 0
- \* PE Spring Line Reverberation Unit (Reprint 46A 1/6d). £11 5 0 pp. 6/6
- \* Repaco 15 watt Inverter Kit £3 7 6 pp. 5/-
- \* Repaco 40 watt Inverter Kit £4 17 6 pp. 7/-
- \* Tiny Tone Radio Control Receiver (Reprint 18A 1/6d). £2 15 0 pp. 3/-
- \* Henry's MW/LW Tuner (Brochure No. 5 FREE) £3 19 6 pp. 3/6
- \* PW Switched FM (Reprint 1/-). £3 17 6 pp. 3/6

**MOST PARTS IN STOCK FOR PRACTICAL WIRELESS AND ELECTRONICS PUBLISHED CIRCUITS. ALL INTEGRATED CIRCUITS IN STOCK—LEAFLET 36A OR LATEST CATALOGUE FOR COMPLETE LIST.**

## HENRY'S RADIO Fully Illustrated CATALOGUES

**A**  
ALL TYPES OF ELECTRONIC COMPONENTS  
TEST EQUIPMENT  
KITS  
BUILT UNITS



**B**  
HIGH FIDELITY & GENERAL AUDIO EQUIPMENT CATALOGUE

### COMPREHENSIVE CLEAR CONCISE CATALOGUES

A. Over 300 pages fully detailed and illustrated with more than 6,000 stock items. Everything for amateur and professional use. Complete with 5 vouchers. 10/- value, for use with purchases.

ORDER AS CATALOGUE A PRICE 7/6 pp.2/-  
B. New audio and high fidelity catalogue. 120 pages containing ideas and equipment for every application. Special low prices for all leading makes. Plus 12/6 extra discount voucher. Over 40 recommended Stereo Systems.

**WHY NOT SEND AWAY TODAY!**

ORDER AS CATALOGUE B PRICE 5/- pp.1/-  
CONTINUALLY IMPROVED AND REVISED.

## INTEGRATED CIRCUITS



BP1010	3 watt Amp	25/-	SL702C	Amplifier	29/6
MC1304	Stereo Decoder	55/-	µL900	Buffer	10/-
TAD100	AM Radio	47/6	7L914	4in. Gate	11/-
PA237	2 watt Amp	37/6	µ910		10/-
PA234	1 watt Amp	20/-	IC10	Amplifier	59/6
PA230	Pre-amp	22/6	TAD110	AM/FM Radio	59/6
MC1303	Stereo Pre-amp	52/6	CA3028	Osc/Mixer	24/6
LA709C	Amp	22/6	CA3036	Dual Dar	18/6
SL403	3 watt Amp	49/6	CA3020	Amplifier	27/6
TA A263	Amp	15/-	CA3018	Array	22/6
			CA3014	FM	29/6

**TRANSUCERS.** Type 1404 for LF Communication with Circuit £5 18 0 pair  
Complete List and Details of all Integrated Circuits No.36A Free on request

## BUILD A QUALITY 4 TRACK TAPE RECORDER



To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything for making a superb Tape Recorder. You need no experience or technical skill to bring this about.  
**THE INSTRUCTIONS MANUAL MAKES BUILDING EASY, AND SUCCESS IS ASSURED.** Kit comprises Deck, Amplifier, Cabinet and speaker, with microphone, 7in. 1200ft tape, and spare spool.  
**ASK FOR BROCHURE 6. TODAY'S VALUE £60. PRICE 39 gns pp. 22/6. NOTHING ELSE TO BUY.**

## GARRARD DECKS

* SP25 mk. II	L/C	£11 19 6
* SP25 mk. II	9TAH/C	£14 5 0
* SP25 mk. II	Mag. Cart.	£16 0 0
* 2025TC	9TAH/C	£8 19 6
* 3000LM	9TAH/C	£9 19 6
* AT60 mk. II	L/C	£13 10 0
* AT60 mk. II	9TAH/C	£15 15 0
* AT60 mk. II	Mag. Cart.	£17 10 0
† AP75	L/C	£17 17 0
† AP75	AT21 Cart.	£25 12 6
† SL75	L/C	£29 0 0
† SL75	AT21	£36 17 6


\* Plinth/Cover 95/- pp. 5/- Deluxe £8 10 0 pp. 5/-  
† Plinth/Cover £8 pp. 5/-  
Deluxe £8 10 0 pp. 5/-  
**COMPLETE LIST 16/17 ON REQUEST WITH SPECIAL LOW PRICES WITH CHOICE OF CARTRIDGE.**



(Carriage etc. 7/6).  
† Plinth/Cover £8 pp. 5/-
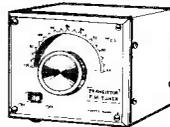
## BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO & STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.  
**PARTS TOTAL COST £6 19 6 DECODER £3 19 6**  
**ASK FOR BROCHURE No. 3 (FOR STEREO)**




## HENELEC 5-5 STEREO AMPLIFIER

Excellent low priced British designed Stereo Amplifier for use with Record Decks, Tuners, 16 transistor mains operated. Output 5+5 watts for 8-15 ohm speakers. Black, silver and wood finish, size 13in x 3in x 6in.  
**PRICE £13 10 0 pp. 7/6 (Leaflet on request).**  
Complete Stereo System 5-5.  
Garrard 2025 TC stereo, 5-5 Amplifier, Plinth/Cover, Two 10 watt speakers with tweeters in polished cabinets. Size 18" x 11" x 7"  
Usual price £49 10 0. **OUR PRICE £39 10 0 pp. 20/-**. ASK FOR BROCHURE 13




**HENRY'S STOCK EVERY TYPE OF COMPONENT YOU NEED — A CATALOGUE IS A MUST!**

## NEW FOR 1970

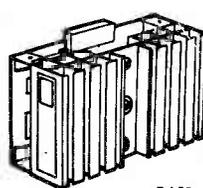

PA25  
(25 watts RMS)

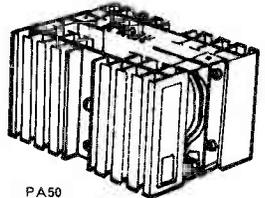

PA50  
(50 watts RMS)

## SILICON POWER AMPLIFIERS WITH DIRECT COUPLED, SYMMETRICAL OUTPUT

### \* HENELEC 'PA25' POWER AMPLIFIER

This silicon design from Henry's Radio uses complementary transistors in the symmetrical output stage direct coupled to a loudspeaker of 8 ohms impedance or higher. Power output is 25 watts RMS with an 8 ohms load, or 12 watts for 15 ohms. Over a frequency range of 15Hz-25kHz 3db. Cool running is assured by the use of generously dimensioned black anodised heatsinks. Price £27 10 0

### \* HENELEC 'PA50' POWER AMPLIFIER

Basically similar to the 'PA25' the 'PA50' will deliver 50 watts RMS to a 3-4 ohm load. Extra power is handled by complementary triplet circuits using the latest PNP and NPN silicon power transistors. As a result of extra heatsinking the 'PA50' runs as cool as the 'PA25'. Price £29 10 0

### \* HENELEC MU442 POWER SUPPLY

Designed to run one or two 'PA25's or one 'PA50' the MU442 connects to the amplifiers by means of plug-on harnesses. No soldering is required to connect up the system. Audio input plug and speaker plug go to the panel of the MU442. Price £6 0 0


\* SEND FOR FREE BROCHURES

## AMPLIFIERS IN STOCK

* 1 watt Mullard	£2 5 0	† PA25 25 watt	£27 10 0
* PA7 7 watt	£3 12 6	* PA50 50 watt	£29 10 0
* MPA12/3 12 watt	£4 10 0	* 100 watt PA	£49 10 0
* MPA12/15 12 watt	£5 5 0	Z30 Sinclair	£4 9 6
* MPA25 25 watt	£7 10 0	Stereo 60	£9 19 6
* MA7 7 watt Amp/Preamp	£8 10 0	P25	£4 19 6
* M466 Stereo Amp/Preamp		* Leaflets available on request.	
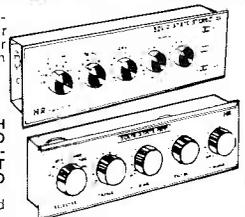
## AUDIO EQUIPMENT

Mono or Stereo Audio equipment developed from Dinsdale Mk. II—each unit or system will compare favourably with other professional equipment selling at much higher prices.  
**COMPLETE SYSTEMS AND MIXERS** from £11 12 6 to £38 17 6 (all units available separately).  
**THE FINEST VALUE IN LOW COST HIGH FIDELITY — CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS, 7, 12 and 25 WATT AMPLIFIERS, STEREO AND MONO PREAMPLIFIERS AND MODULES.**  
\* SEND FOR BROCHURES No. 12/14 and 21 TODAY!



# HENRY'S RADIO LTD.

Mail Order Dept, Electronic Components and Equipment, and Electronic Organ Dept.  
303 EDGWARE ROAD, LONDON W2.  
Telephone: 01-723 1008/9  
Open Mon-Sat, 9am-6pm, Thurs, 9am-1pm

High Fidelity and Audio Centre  
309 EDGWARE ROAD, LONDON W2.  
Telephone: 01-723 6963  
Open all day Saturday.

# ADCOLA

PRODUCTS LIMITED  
(Regd Trade Mark)

## THE RELIABLE SOLDERING INSTRUMENT!



SEND COUPON FOR LATEST LEAFLET

**ADCOLA PRODUCTS LTD**  
**ADCOLA HOUSE**  
**GAUDEN ROAD**  
**LONDON SW4**  
Telephone 01-622 0291/3

NAME .....

ADDRESS .....

.....

.....

PW177

## JACKSON BROTHERS


have acquired the manufacturing rights of

# WAVEMASTER
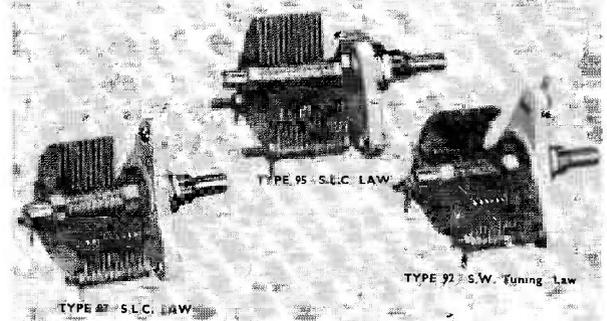
### VARIABLE CAPACITORS



'Wavemaster' variable capacitors have brass vanes and a single ceramic end plate. All have .248" spindles, extended both ends for ganging by means of our Universal Couplings. All are designed for S.W. working and for one hole fixing. 6mm spindles to order if required. Various capacitances. Largest vane packs 300 pF .017 air gap, 50 pF 0.64 air gap.




<p><b>Type 87</b> <b>S.L.C. Law</b> Plain bearings <math>\frac{3}{8}</math>" fixing bush front area <math>1\frac{1}{2}</math>" w. x <math>1\frac{7}{8}</math>" h.</p>	<p><b>Type 95</b> <b>S.L.C. Law</b> Ball bearings <math>\frac{7}{8}</math>" dia. fixing bush front area <math>1\frac{7}{8}</math>" w. x <math>1\frac{1}{2}</math>" h.</p>	<p><b>Type 92 Modified</b> <b>S.L.C. Law</b> (S.W. Tuning) Plain bearings <math>\frac{3}{8}</math>" dia. fixing bush front area <math>1\frac{1}{2}</math>" w. x <math>1\frac{7}{8}</math>" h.</p>
---	---	---

## JACKSON BROTHERS (London) LTD

Kingsway, Waddon, Croydon, CR9 4DG. 'Phone: 01-688 2754-5  
U.S. Office:- M. Swedgal, 258 Broadway, New York. N.Y. 10007
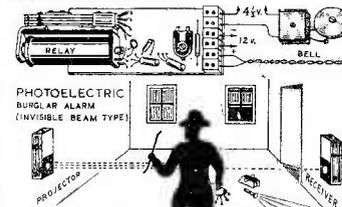
## PHOTOELECTRIC KIT

**CONTENTS:** 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



### PHOTOELECTRIC KIT 39/6

Postage and Pack. 2/6 (UK)  
Commonwealth:  
SURFACE MAIL 3/6  
AIR MAIL £1.0.0  
Australia, New Zealand,  
S. Africa, Canada and U.S.A.  
Also Essential Data Circuits and  
Plans for Building  
10 Advanced Designs

### INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

**CONTENTS:** 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

### LONG RANGE INVISIBLE BEAM OPTICAL KIT

**CONTENTS:** As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

### JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

**CONTENTS:** Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

### JUNIOR OPTICAL KIT

**CONTENTS:** 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.

Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

## YORK ELECTRICS

335 BATTERSEA PARK RD., LONDON S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

# COMPLETE STEREO SYSTEM

FOR ONLY **39 GNS**  
CARRIAGE 35/-



The Premier Stereo System "ONE" consists of an all transistor stereo amplifier. Garrard 2025 T/C auto manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on off, stereo mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.19.6 Carr. 7/6.)

### SPECIAL OFFER CARTRIDGES

SHURE		
	List Price	Premier Price
M3D	£8.10.6	£6.19.6
M44-5	£14.9.1	£10.10.0
M44C	£12.19.5	£9.9.0
M44E	£17.8.4	£13.19.6
M55E	£20.15.1	£15.15.0
M75-5	£17.8.4	£13.19.6
M75E	£25.18.10	£21.0.0

AUDIO TECHNICA		
	List Price	Premier Price
A.T.33.7 stereo	£10.14.3	£7.19.6
A.T.75 stereo	£22.0.0	£15.0.0
A.T.7X elliptical	£25.0.0	£18.0.0

Post and Packing 1/6 each

### "NOVA" 505 TRANSISTOR STEREO AMPLIFIER

A superb stereo amplifier offering every facility for the hi-fi enthusiast. Output 5 watts per channel. Frequency Response 40-20,000 Hz. 3dB Inputs for radio, P.U. Ceramic, P.U. Magnetic Tape. Separate bass and treble controls, Volume and Balance controls, Mono Stereo Switch. Also features headphone socket and tape output. Teak case with attractive illuminated front panel. Size 14 1/2 x 9 1/2 x 3 1/2 in. A.C. 200/250V.



WONDERFUL VALUE  
AT ONLY 18 Gns. Carr. 10/-

### PICK-UP CARTRIDGES AT MONEY SAVING PRICES!

GOLDRING G900 (Stereo)	£8.19.6
SONOTONE STARCD (Stereo)	£2.15.0
ACOS GP91 1SC (Mono compatible)	£1.13.5
ACOS GP93-1 (Stereo)	£2. 5.7
ACOS GP94 (Stereo)	£2.14.8
B R R X3M (Mono compatible)	£1.16.5
B R R X3H (Mono compatible)	£1.16.5
RONETTE 106 (Stereo)	£1.15.0
RONETTE 106 (Stereo)	£1.15.0

All complete with mounting brackets and instructions. Post and Packing 1/6 each.

### WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

All leading makes available including Rogers, Armstrong, Dulci, Wharfedale, Goodmans, Goldring, Shure, etc., etc.

### PREMIER STEREO SYSTEM "TWO"

As system 'ONE' above but with Garrard SP25 Carriage 35/- **45 Gns.**

### ALBA UA100D ALL TRANSISTOR STEREO TUNER AMPLIFIER



Covers Long, Medium and Short Waves plus VHF/FM with built in stereo decoder and A.F.C. Output 16 watts r.m.s. per channel into 8 ohms (distortion less than 0.3%). Response 20Hz-20kHz. Inputs for Magnetic and ceramic p.u. and Tape. Tape outlet socket. Tuning, Volume, Bass, Treble and Balance controls. Push button selector. Black leatherette top, teak ends and brushed aluminium front panel.

PREMIER £67.11.6 Carriage 12/6.



### E.M.I. 13 x 8in. HI-FI SPEAKERS

Fitted two 2 1/2 in. tweeters and crossover network. Impedance 3 and 15 ohms. Handling capacity 10 watts. Brand new.

99/6 P. & P. 7/6

Also available without tweeters

49/6 P. & P. 7/6

### PREMIER STEREO SYSTEM "THREE"

Nova 505 Amplifier (as above), £18.18.0. Garrard SP25, £11.19.6. Sonotone STARCD, £2.15.0. Teak base and cover, £5.10.0. Pair of 3-Unit Hi-Fi Enclosures fitted E.M.I. Speakers, £26.5.0. Total cost if purchased separately, £65.7.6.

PREMIER PRICE 55 Gns. Carriage 35/-

### VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2 1/2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono inputs output. Attractive teak wood grain finish case.



MONO MODEL 59/6 STEREO MODEL 69/6 P. & P. 2/6.

### VERITAS V-313 TAPE HEAD DEFLUXER

A must for all tape users! Tape heads become permanently magnetized with constant use: this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds.



34/6 P. & P. 1/6.

### SANYO M48M Cassette Tape Recorder

A truly compact lightweight recorder size 8 x 4 1/4 x 2 1/2 in. 5 transistors and 1 diode. AC Bias. 2 1/2 in. speaker. Record level indicator. Earphone socket. Complete with carrying strap, remote control microphone with pouch and tape cassette. Output 300mW. Operates on 4 U11 batteries.



PRICE £21

P. & P. 7/6

### TWO STATION TRANSISTOR INTERCOMS.

Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home, office, factory, etc.



65/- P. & P. 4/-

### TAPE CASSETTES



C60 (60 min.) 7/6  
THREE FOR 21/-  
C90 (90 min.) 12/6  
THREE FOR 34/-  
C120 (120 min.) 17/6  
THREE FOR 51/-  
P. & P. 1/-.



### CASSETTE HEAD CLEANER

Removes unwanted deposits from delicate tape heads. Fits all cassette recorders.

11/6 P. & P. 1/-.



### "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped-attractively boxed.

LP3 3'	250'	P.V.C.	5/8	LP6 51'	1200'	P.V.C.	12/6
TT3 3'	450'	POLYESTER	7/8	DT6 61'	1800'	POLYESTER	22/6
DT3 3 1/2'	600'	POLYESTER	1 1/8	TT6 61'	2400'	POLYESTER	37/6
SP6 5'	600'	P.V.C.	8/8	SP7 7'	1200'	P.V.C.	13/6
LP6 5'	900'	P.V.C.	10/8	DT7 7'	2400'	POLYESTER	25/-
DT6 5'	1800'	POLYESTER	1 1/8	TT7 7'	3600'	POLYESTER	50/-

TAPE SPOOLS 3' 1/-, 5', 5 1/2', 7' 1/8, TAPE CASES 5', 7' 2/6.  
Post and Packing 3' 1/-, 5', 5 1/2', 1/6, 7' 2/6. (3 reels and over Post Free).

# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



# Kinver for Components

## LINEAR INTEGRATED CIRCUITS

High Performance operational Amplifiers, Texas Type SN72709N 21/- each  
This device is electronically similar to MIC709, MC709C,  $\mu$ A709C, N5709A etc.,  
supplied complete with specification sheet

Also in stock:

PA230	21/-	CA3012	26/3	FAA293	21/8
PA234	23/-	CA3020	27/6	FAA310	32/-
PA237	34/-	CA3028A	28/-	FAA320	13/5
PA246	57/-	CA3028B	37/6	SL403A	49/6 net
CA3000	54/9	CA3029	26/3	IC-10	59/6 net
CA3001	79/6	CA3035	30/-	D13T1	10/8
CA3011	20/-	FAA231	56/8	2N5306	11/6

Add 1/- to the above i.e. s. for data sheets if required (1/9 with SL403A, free with IC-10).  
Other data sheets (apart from IC-10) may be purchased separately at 1/6 per sheet,  
post free.

### 1 WATT AMPLIFIER MODULE TYPE PCM1

This amplifier unit is a printed circuit module incorporating the popular and well tried  
PA234 i.c. amplifier. The unit is a complete AUDIO AMPLIFIER and requires no  
external components, you simply connect an 18 volt power supply and a 15 or 16 ohm  
speaker or head phone, even the supply smoothing capacitor and the output capacitor  
are included! The overall dimensions, including capacitors, are 2 1/4 in. x 3 in. x 7/16 in.  
The input for 1 watt output at 1 kHz is typically 300mV into 100 kohms.  
This unit is available at only 36/- net, complete with descriptive leaflet or 70/- net per  
pair. Send for free leaflet.

### SILICON TRANSISTORS FOR HIGH QUALITY EQUIPMENT

BC107	3/3	BD123	24/3	T1P32A	23/-	2N3055	15/9
BC108	3/-	BDY20	24/3	T1S44	1/9	2N3702	3/6
BC109	3/3	BF184	7/6	T1S49	2/6	2N3703	3/3
BC158	7/6	BF194	7/-	T1S50	3/9	2N3704	3/9
BC182L	3/2	BFX29	10/4	2N696	4/9	2N3705	3/4
BC183L	2/5	BFX84	6/8	2N697	5/-	2N3707	4/5
BC184L	3/2	BFX85	8/8	2N706	3/3	2N3708	2/-
BC212L	3/9	BFY50	5/-	2N1132	10/9	2N3819	9/-
BC213L	3/9	BFY51	4/6	2N2906	13/-	2N3820	18/9
BC214L	4/-	BFY52	5/-	2N2924	4/4	2N3826	5/11
BCY70	5/4	BSY95A	3/11	2N2925	5/3	2N4058	4/6
BCY71	10/4	MJ481	27/3	2N2926	3/-	2N4059	3/5
BCY72	4/6	MJ491	32/11	2N3053	6/8	2N5457	9/9
BD121	17/3	T1P31A	17/-				

### COMPONENTS CATALOGUE—2/- post free (Inland)

P & P 1/6 inland, overseas at cost (min. 10/-). Cash with order please, discounts may  
be deducted as follows: order over £5—10% order over £10—15%. Trade orders—  
net 30 days.

Please send SAE with enquiries. CALLERS WELCOME Open 9.00 a.m.—12.50 p.m.,  
2.00 p.m. to 5.00 p.m. Weekdays and Saturday mornings 9.00 a.m.—12.50 p.m.

**ELECTRONICS LTD**  
**Kinver**

STONE LANE KINVER  
STOURBRIDGE, WORCS  
Telephone: KINVER 2099

## Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full time 16 month College Diploma  
Course which gives a thorough fundamental  
training for radio and television engineers,  
starts on 15th April 1970.

The Course includes theoretical and practical  
instruction on Colour Television receivers and is  
recognised by the Radio Trades Examination  
Board for the Radio and Television Servicing  
Certificate examinations. College Diplomas are  
awarded to successful students.

The way to get ahead in this fast growing industry  
—an industry that gives you many far-reaching  
opportunities—is to enrol now with the world  
famous Pembridge College. Minimum entrance  
requirements: 'O' Level, Senior Cambridge or  
equivalent in Mathematics and English.

To: The Pembridge College of Electronics  
(Dept. PW12), 34a Hereford Road, London, W.2

Please send, without obligation, details of the  
Full-time Course in Radio and Television.

NAME .....

ADDRESS .....

## 20 Solid State

### Projects for The Home

R. M. Marston

From light-operated switches to metal detection  
and photographic timers, the versatile circuits in  
this manual will prove invaluable to the enthusiast.  
The author reflects the present-day state of semi-  
conductor technology in his choice of devices.  
Triacs and silicon controlled rectifiers are included  
with integrated circuits unijunction transistors  
and field effect transistors, not to mention the  
more familiar silicon planar bipolar transistors.

Cased 592 02867 4 105 pages 54 illustrations 28s

Limp 592 02872 0 18s


Available from leading booksellers or:

**The Butterworth Group**  
88 Kingsway London WC2



# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

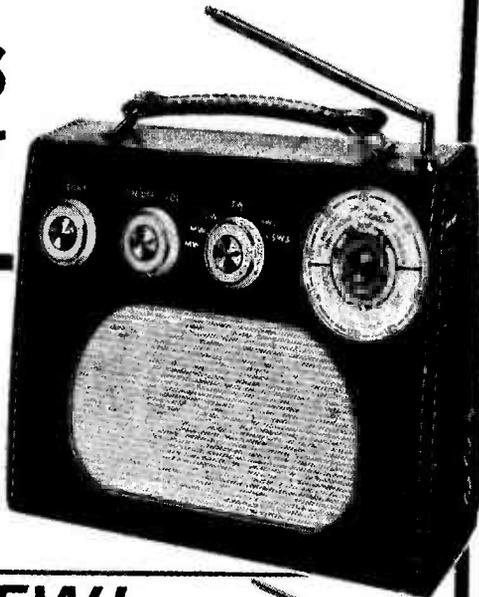

## NEW! roamer eight mk1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 23in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total Building Costs

**£6.19.6**

Parts Price List and Easy Build Plans 5/- (FREE with parts).

P & P 7/6.


## roamer seven mkIV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Five Section 23in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak B.W. listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.

Total building costs

**£5.19.6**

P & P 7/6

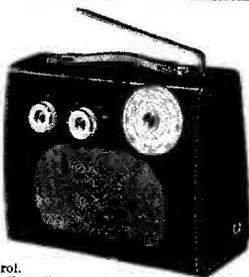

## NEW! trans eight

SIX WAVEBAND  
PORTABLE WITH  
3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.

Total building costs

**89'6**


P & P 5/6


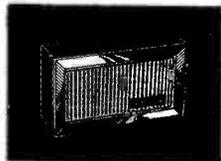
## pocket five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND PORTABLE  
WITH SPEAKER AND EARPIECE

Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker, also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

**44'6**

P. & P.  
3/6

## transona five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND PORTABLE  
WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

**47'6**

P. & P.  
3/9

## roamer six

SIX WAVEBAND PORTABLE  
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long Waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 8 stages—5 transistors and 3 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/-. (FREE with parts).



Total building costs

**79'6**

P. & P.  
4/6

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....

\* Callers side entrance Stylo Shoe Shop

\* Open 10-1, 2.30-4.30 Mon-Fri. 9-12 Sat

PW.16

# Complete stereo system – £29-10

The new Duo general-purpose 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION—

Impedance 10 ohms. It incorporates Goodmans high flux 6" x 4" speaker and 2 1/2" tweeter. Teak finish 12" x 6 1/2" x 5 1/2". 4 guineas each. 7/6d. p. & p.

Type 2 as type 1. Size 17 1/2" x 10 1/2" x 6 1/2". Incorporating 10 1/2" x 6 1/2" bass unit and 2 1/2" tweeter 3 ohms impedance £6-6-0 plus 15/- p. & p.

Garrard Changers from £7 19 6d. p. & p. 7/6d.

Cover and Teak finish Plinth £4 15 0d. 7/6d. p. & p.

The items illustrated can be purchased together for £29-10.

The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

SPECIFICATION—

R.M.S. power output: 3 watts per channel into 10 ohms speakers.

INPUT SENSITIVITY: Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.

CONTROLS: 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.

STONE CONTROL: Treble lift and cut. Separate on/off switch. A preset balance control.

*Duetto*

Integrated Transistor Stereo Amplifier

£9-10

plus 7/6d. p. & p.



The above 5 items can be purchased together for £29.10 + £1.10.0 p. & p.

## The Classic

£9 plus 7/6 p. & p.



Controls: Selector switch Tape speed equalisation switch (3 1/2 and 7 1/2 i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 position rumble filter.

Specification: Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape head: 3mV (at 3 1/2 i.p.s.). Mag. P.U.: 2mV. Cer. P.U.: 80 mV. Tuner: 100mV. Aux.: 100mV. Tape/Rec. output: Equalisation for each Input is correct to within ±2dB (R.I.A.A.) from 20Hz to 20KHz. Tone control range: Bass ±13dB at 60Hz. Treble ±14dB at 15KHz. Total distortion: (for 10 watt output) <1.5%. Signal noise: <—60dB. A.C. mains 200-250v. Built and tested. Size 12 1/2 in. long, 4 1/2 in. deep, 2 1/2 in. high. Teak finished case.
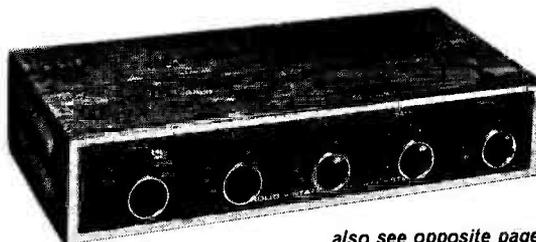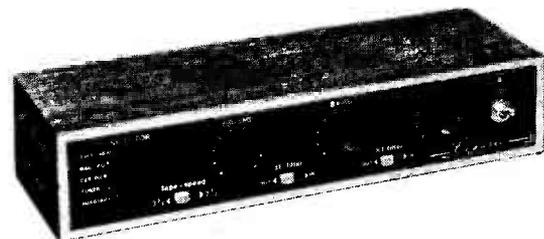
## The Viscount

£14.5 plus 7/6 p. & p.

Integrated High Fidelity Transistor Stereo Amplifier. Specification—Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monaural). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo), P.U., Tuner, Tape and Tape Rec. out. Sensitivities: All inputs 100mV into 1-8M ohm. Frequency Response: 40Hz-20KHz ±2dB. Tone Controls: Separate bass and treble controls; treble, 13dB lift and cut (at 15KHz); Bass, 15dB lift and 25dB cut (at 60Hz). Volume Controls: Separate for each channel. A.C. Mains Input: 200-240V. 50-60Hz. Size, 12 1/2" x 6" x 2 1/2" in teak finished case. Built and tested. VISCOUNT MARK II for use with magnetic pick-ups specification as above. Fully equalised for magnetic pick-ups. Suitable for cartridges with minimum output of 4mV/cm/sec. at 1kc. Input impedance 47k. £15.15 plus 7/6 p. & p.



also see opposite page



## SPECIAL OFFER!

Complete stereo system comprising BALFOUR 4-speed autoplayer with stereo head, 2 Duo speaker systems, size 12 in. x 6 1/2 in. x 5 1/2 in. Plinth (less cover) and the DUETTO stereo amplifier. All above items

£25 plus 22 p. & p.

## NEW COMPLETE HI-FI STEREO SYSTEM - £41

comprising SP 25 Garrard Mk II with diamond cartridge, or 2025 TC, Viscount Mk I amplifier, two type 2 speakers, plinth and cover

£41 plus £2-10-0 p. & p.



### The ELEGANT SEVEN Mk. III (350mW Output)

7 transistor fully tunable M.W.-L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.  
MAINS POWER PACK KIT: 9/6 extra.

Circuit 2/6  
FREE WITH PARTS.

Price £4.9.6 plus 7/6 P. & P.

### The DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. superhet portable—with baby alarm facility. Set of parts. The latest modified and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

Price £5.5.0 plus 7/6 P. & P.

MAINS POWER PACK KIT: 9/6 extra



Circuit 2/6  
FREE WITH PARTS.



### EXTRACTOR FAN

A.C. mains 230/250v. complete with pull switch. Size: 6 x 6 x 4in.

Price 27/6 plus 7/6 P. & P.


### X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: Power Output (into 3 ohms speaker) 10 watts. Sensitivity (for rated output): 1mV into 3K ohms (0.33 microamp). Total Distortion at 1KHz at 5 watts, 0.35%, at rated output 1.5%. Frequency Response: Minus 3dB points 20Hz and 40KHz. Speaker: 3-4 ohms (3-15 ohms may be used). Supply voltage: 24V. DC. at 800mA (6-24V. may be used).

Price 69/6 plus 2/6 P. & P.

Control assembly: including resistors and capacitors. 1. Volume: PRICE 5/-. 2. Treble: PRICE 5/-. 3. Comprehensive bass and treble: PRICE 10/-. The above 3 items can be purchased for use with the X101.

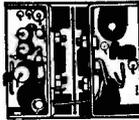Power Supplies for the X101: P101 M (for mono) 35/- plus 4/6 p. & p. P101 S (for stereo) 42/6 plus 4/6 p. & p.



### CAR TRANSISTOR IGNITION SYSTEM

by famous manufacturer

For 6 volt or 12 volt positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers, etc.).

Price £4.19.6 plus 5/- P. & P.

### 50 WATT AMPLIFIER

A.C. Mains 200-250V



Price £28.10

plus 20/- p. & p.  
3 & 4 300mV at 1m. Suitable for most high output instruments (gram, tuner, organ, etc.). Input sensitivity relative to 10w output. TONE CONTROLS ARE COMMON TO ALL INPUTS. Bass Boost +12dB at 60Hz. Bass Cut -13dB at 60 Hz. Treble Boost +11dB at 15 KHz. Treble Cut -12dB at 15 KHz. With bass and treble controls central -3dB points are 30 Hz and 20 KHz. POWER OUTPUT: For speech and music 50 watts rms. 100 watts peak. For sustained music 45 watts rms. 90 watts peak. For sine wave 38.5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3.2% at 1KHz. Total distortion at 20 watts 0.15% at 1KHz. Output to match into 8 or 15 ohms speaker system. NEGATIVE FEEDBACK 20dB at 1KHz. SIGNAL TO NOISE RATIO 60dB. MAINS VOLTAGES adjustable from 200-250V. A.C. 50-60 Hz. A protective fuse is located at the rear of unit. Output impedance 3, 8 and 15 ohms.


### B.S.R. TD-2 TAPE DECK

Takes 5 1/2in. spools, fitted with B.S.R. 1/2 Track Heads. Size 13 1/2in. long by 8 1/2in. wide.

Price £8.19.6 plus 7/6 P. & P.
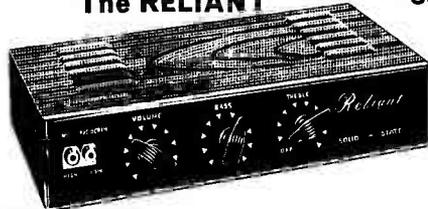
### The RELIANT

SOLID STATE  
GENERAL  
PURPOSE  
AMPLIFIER



#### SPECIFICATIONS

Output—10 watts  
Inputs—1. -xial mic 10mV Tone Controls—Treble control range ±12dB at 10 KHz.  
2. -gram/radio 250mV

Bass control range ±13dB at 100Hz

Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10 1/2" x 4 1/2" x 2 1/2". For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from gram and mike. Built and tested.

#### RELIANT Mk. I

As above less teak case  
£5.15 plus 7/6 P. & P.

#### RELIANT Mk. II

In teak finished case.  
£6.16 plus 7/6 P. & P.

### RECORD PLAYER SNIP

The "Princess", 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7" to 10" or 12". Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play. Post and ins. 7/6 extra.

ONLY £5.19.6 plus 7/6 P. & P.



A.C. Mains 240V



### POCKET MULTI-METER

Size 3 1/2 x 2 1/4 x 1 1/4in. Meter size 2 1/4 x 1 1/4in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. volts 0-15, 0-150, 0-1,000 D.C. current 0-150mA Resistance 0-100KΩ Complete with test prods, battery and full instructions.

42/6 plus 3/6 P. & P.

FREE GIFT for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter

### 40W FLOURESCENT LIGHT KIT



Incorporating GEC Choke size 8 1/2 x 1 1/2 x 1 1/2in. 2 bi-pin holders starter and starter-holder. P. & P. 5/6. 11/6

Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 1 1/2 x 1 1/2 x 1 1/2in. 2 bi-pin holders, start and starter holder. P. & P. 6/6. 17/6

### THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss crossover network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 gauss. Resonance 40-60 c/s. Frequency range 50c/s to 20Kc/s. Size 13 1/2 x 8 1/2 x 4 1/2in. By famous manufacturer.

List price £7 OUR PRICE 74/6 plus 5/- P. & P.


Similar speaker to the above without tweeters in 3 and 15 ohms 44/6 plus 5/- P. & P.

### PYE CAR RADIO

Push Button Tuning Heart

This PRESTOLOK 5 station Push-Button Tuner Heart with Manual Over-ride is an ideal basis for a quality AM car radio. Size 6 1/2 x 4 1/2 x 2 1/2".

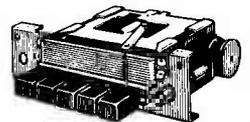As illustrated but without knobs.  
25/- plus 3/- P. & P.



### QUALITY MAINS TRANSFORMER

Input 250 volts. OUTPUT (All RMS values) 4 windings of 11.5 volts connected in series total 46 volts at 4.5 amps (conservatively rated). The following combinations may be used. 1. 23-0-23 volts. 2. 46 volts.

Both of these above voltages are commonly used in medium to high powered transistor amplifiers, power supplies, etc.

Price 35/- plus 7/6 P. & P.



TERMS C.W.O.  
All enquiries S.A.E.

RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED

Goods not despatched outside UK  
**RADIO & T.V. COMPONENTS (ACTON) LTD**  
21c High Street, Acton, London W.3.  
Also at 323 Edgware Road, London W.2.  
ALL ORDERS BY POST TO OUR ACTON ADDRESS

### FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	2/6	OC200	3/6
AC128	2/6	OC201	7/6
AC176	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF114	4/-	2N1302-3	4/-
AF115	3/6	2N1304-5	5/-
AF116	3/6	2N1306-7	6/-
AF117	3/6	2N1308-9	9/-
AF239	12/6	2N3819 FET.	9/-
AF186	10/-	2N3844A	5/-
AF139	10/-		
BFY50	4/-	Power	
BSY25	7/0	Transistors	10/-
BSY26	3/6	OC20	10/-
BSY27	3/-	OC23	10/-
BSY28	3/-	OC25	8/-
BSY29	3/-	OC26	5/-
BSY95A	3/-	OC28	7/6
OC41	2/6	OC35	5/-
OC44	2/6	OC36	7/6
OC45	2/6	AD149	10/-
OC71	2/6	ALY1-10	30/-
OC72	2/6	2N3055	15/-
OC73	3/6	2S034	10/-
OC81	2/6	Diodes	
OC81D	2/6	AA42	2/-
OC83	4/-	OA91	2/-
OC139	2/6	OA79	1/9
OC140	3/6	OA81	1/9
		IN914	1/6

### NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits, Data and Circuits of types, supplied with orders.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
B82	10	OC45, OC81D and OC81 Trans Mullard glass type.	10/-
B83	200	Trans. Makers rejects. NPN/PNP. Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
B66	150	High quality Germ. Diodes. Min. glass type.	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types.	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN, PNP, equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes. Mixed voltages.	10/-
H5	16	1 Amp. Plastic Diodes, 50-1,000 Volts. 6 large, 10 small	10/-
H6	40	250mW. Zener Diodes DO-7 min. Glass Type. AV. 40% Good.	10/-

### NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries .3 to .5 volt, .5 to 2 ma.	10/-
B77	2	AD161-AD162 NPN/PNP Trans Comp. Output, Pair.	10/-
B79	4	1N4007 Sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Plastic.	10/-
B81	10	Reed Switches, mixed types, large and small.	10/-
B89	2	SSP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45.	10/-
B92	4	NPN, Sil. Trans. AO6 BSX20 2N2369 500 MHz, 360mW.	10/-
B93	5	GET113 Trans. equiv. to ACY17 to ACY21 PNP Germ.	10/-
B96	5	2N3136 PNP Sil. Trans. TO-18. HFE 100-300 I.C. 600mA. 200MHz.	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NK271, etc.	10/-
B99	200	Capacitors, Electrolytics, paper silver mica, etc. Post and packing, this Pak 2/6.	10/-
H4	250	Mixed Resistors, Post and packing 2/-.	10/-
H7	40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-

**FREE!** Packs of your own choice up to the value of 10/- with orders over £4.

### RETURN OF THE UNBEATABLE P.1. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

**P1** PLEASE ASK FOR PAK P.1. 2/- P. & P. on this Pak **ONLY 10/-**


Complementary Set. NPN/PNP Germ. trans., Pak F.3. **2/6 PAIR**

**P.O. RELAYS 8 FOR 20/-**  
Various Contacts and Coil Resistances. Post & Packaging 5/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.

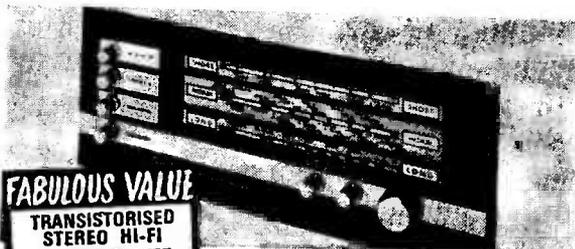NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order OVERSEAS AND EXTRA FOR AIRMAIL.



### FABULOUS VALUE

#### TRANSISTORED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistored amplifier which comes complete with 2-10" x 8" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble - 10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL  
NO TECHNICAL KNOWLEDGE REQUIRED  
Only **28 Gns.** + P&P 17/6  
Credit terms available, first monthly payment £3.8.2 followed by 9 monthly payments of £3.6.2. (Total "Credit Sale" Price £33.1.8). Send £4.3.8 today.

### FANTASTIC BARGAIN OFFER!

#### "TRANSCONTINENTAL" FULLY TRANSISTORED STEREO PHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer - a complete radiogram at half normal price **ONLY**

10 Watts Total output **£36.10.0** P&P 17/6  
17 Transistors & 10 diodes

EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY  
Credit Terms available. First monthly payment £4.2.2 followed by 9 monthly payments of £4.2.2. (Total "Credit Sale" Price £41.1.8). Send £4.19.8 today.



Callers Welcome

## BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board— obtainable from your local Retailer

Trade enquiries to:  
**NORMAN ROSE (ELECTRICAL) LTD.**  
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:  
**VERO ELECTRONICS LTD.**  
Industrial Estate, Chandler's Ford, Hants

## H.A.C. Electronic Kits

### DID YOU KNOW?

That we have specialized in the supply of kits for the Amateur Constructor for over 35 years. (Established 1934.)

That we now have available a full range of Complete transistor kits with comprehensive instruction manual, for constructing—Radios—Resistance Bridge—Lightmeter—Electronic Counter—Voltmeter—80 metre Converter, etc. etc. (Details for 40 different electronic circuits are available.) Complete kits from 54/-. Fully guaranteed. Illustrated brochure upon application. send S.A.E. please.

H.A.C. Products, 29 Old Bond Street, London W.1.

**POST THIS COUPON NOW!**

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name: \_\_\_\_\_  
Address: \_\_\_\_\_

**LEWIS radio** 180 CHASE SIDE, SOUTHGATE, DEP. P470 LONDON, N.14, TELEPHONE PAL 3733/9666

# COMET

Hi-Fi DISCOUNT WAREHOUSES

- All items offered are brand new, latest models in manufacturers' sealed cartons. Fully guaranteed with after-sales service.
- Complete Free price list of over 800 items on request.



Open Daily to the public from 9 a.m. Closed Tuesday 1 p.m.  
Mon. & Sat. 5-30 p.m. Open until 8 p.m. Wednesday, Thursday & Friday.

	Rec. Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>		
ARENA 210 Amplifier	£34 10 0	£22 0 0
ARMSTRONG 521	£52 0 0	£42 19 6
DULCI 207	£25 0 0	£17 0 0
DULCI 207M	£30 0 0	£20 19 0
GOODMANS Maxamp	£54 0 0	£41 19 0
LEAK Stereo 30 Plus	£53 0 0	£42 19 6
LEAK Stereo 30 Plus In teak case	£59 10 0	£47 19 6
LEAK Stereo 70	£65 0 0	£49 19 6
LEAK Stereo 70 In teak case	£69 10 0	£53 19 6
LINEAR LT.66	£18 18 0	£14 19 6
PHILIPS RH 591	£73 0 0	£56 1 0
PHILIPS RH 590	£49 0 0	£37 12 6
PHILIPS RH 580	£26 0 0	£19 19 6
QUAD 33 Pre-amplifier	£43 0 0	£35 19 6
QUAD 303 Main Amplifier	£55 0 0	£46 19 6
ROGERS Ravensbourne	£59 10 0	£48 19 6
ROGERS Ravensbourne In teak case	£64 0 0	£52 13 6
ROGERS Ravensbrook	£44 0 0	£32 19 6
ROGERS Ravensbrook In teak case	£49 0 0	£39 19 6
SINCLAIR 2000	£39 0 0	£29 19 6
TELETON 200E	£28 7 6	£21 15 6
TRUVOX TSA.200	£54 12 0	£37 19 6

	Rec. Retail Price	Comet Price
<b>TUNERS</b>		
ARENA F211 with decoder	£39 10 0	£33 19 6
ARMSTRONG 523 AM/FM	£52 9 0	£44 19 6
ARMSTRONG 524 FM	£40 4 6	£34 19 6
ARMSTRONG M8 decoder	£9 10 0	£7 19 6
DULCI FMT.7 FM	£22 1 0	£17 19 6
DULCI FMT.7 Stereo	£31 0 0	£25 5 0
GOODMANS STEREO MAX	£32 10 5	£21 19 0
LEAK Troughline with MPX	£51 10 6	£39 19 6
LEAK Stereofetic Chassis	£56 11 0	£48 19 6
LEAK Stereofetic In teak case	£64 14 4	£54 19 6
PHILIPS RH 690	£39 0 0	£33 2 6
QUAD Stereo FM	£51 0 0	£41 19 6
ROGERS Ravensbourne Tuner with Decoder	£61 17 9	£52 12 6
SINCLAIR 2000	£26 14 6	£19 4 6
TRUVOX FM 200/IC with decoder	£60 11 10	£39 19 6

	Rec. Retail Price	Comet Price
<b>TUNER/AMPLIFIERS</b>		
ARENA 2400 with MPX	£90 6 0	£79 19 6
ARENA 2600 with MPX	£97 0 0	£89 0 0
ARENA T1000F with MPX	£72 9 0	£59 19 6
ARENA T900 with MPX	£303 9 0	£258 0 0
ARMSTRONG 525	£87 16 9	£78 19 6
ARMSTRONG 526	£98 15 6	£79 19 6
ARMSTRONG 127	£43 19 6	£37 19 6
(Teak Case for 127)	£3 17 0	£3 19 0
GOODMANS 3000	£77 14 7	£66 19 6
PHILIPS RH781	£74 19 6	£63 14 6
PHILIPS RH790	£125 0 0	£106 4 6
PHILIPS RH 691	£53 0 0	£37 0 0
TANDBERG System	£75 18 0	£59 19 6
TELETON F.2000	£51 0 0	£37 19 0
TELETON TATI	£133 0 0	£85 0 0

	Rec. Retail Price	Comet Price
<b>COMPLETE HI-FI SYSTEMS</b>		
TELETON MX.900	£64 13 2	£48 19 6
TELETON R.8000	£60 19 6	£49 19 6
TELETON CMS 300	£105 15 0	£79 19 6
TELETON CMS.400	£126 0 0	£99 0 0
GOODMAN 3000 Stereo suite	£140 9 0	£111 0 0
MARCONI Unit 4	£74 10 0	£60 17 6
WYNDSOR SYSTEM	£59 19 6	£49 19 6
VIDEORAMA	£42 19 6	£35 0 0

	Rec. Retail Price	Comet Price
<b>SPEAKERS</b>		
ARENA HT 21	£10 10 0	£9 5 0
ARENA HT 7	£19 19 0	£17 0 0
ARENA HT 10	£22 1 0	£18 19 6
ARENA HT 20	£32 11 0	£26 19 6
ARENA HT 28	£75 15 0	£65 19 6
B & W DM3	£63 0 0	£53 6 0
B & W P2H	£94 10 0	£81 5 0
B & W DM1	£32 0 0	£23 19 6
CELESTION Ditton 10	£21 3 2	£17 5 0
CELESTION Ditton 15	£29 0 0	£22 19 6
DULCI AS 3	£8 6 0	£6 19 6

	Rec. Retail Price	Comet Price
<b>GOODMANS</b>		
Majesta	£57 0 0	£48 19 6
Maximo	£20 7 9	£15 19 6
Maximo II	£20 12 0	£24 19 6
Magnum-K	£20 2 0	£31 19 6
Miramba	£24 0 1	£19 19 6
Mambo	£22 5 6	£18 11 0
3005 (pair)	£25 0 0	£21 0 0
KEF Celeste	£29 0 0	£22 10 0
KEF Concord	£43 10 0	£33 19 6
LEAK Sandwich	£43 10 0	£34 19 6
LEAK Mini-Sandwich	£29 15 0	£23 19 6
LOWTHER L.I.P. with PMO Special Price	£23 10 0	
QUAD Electrostatic	£66 0 0	£53 19 6
TRUVOX LS200	£22 7 3	£15 19 6
<b>WHARFEDALE Speakers</b>		
Alredale	£69 10 0	£57 14 0
Denton	£18 0 0	£13 19 6
Super Linton	£21 10 0	£17 19 6
Malton	£29 10 0	£23 19 6
Dovedale 3	£39 10 0	£29 19 6
Rosedale	£55 0 0	£43 19 6
UNIT 3 Speaker Kit	£10 19 6	£8 19 6

Most types of chassis, speakers, cross over networks, etc., available ex-stock.

**THE GOODMAN 3000 MUSIC AUDIO SUITE**  
A complete Audio Suite with Stereo Radio, complete with Speakers, Turntable and magnetic cartridge. All Wired and ready to go. Beautifully finished in Teak. Rec. Retail Price £140.9.0. **COMET PRICE £111.0.0.**

## CARTRIDGES

	Rec. Retail Price	Comet Price
<b>TURNTABLES</b>		
ARENA SP25 with base, cover and cartridge	£30 19 0	£24 19 6
GARRARD SP. 25 MK II	£15 11 4	£11 19 6
GARRARD AP. 75	£23 16 0	£17 19 6
GARRARD SL. 55	£13 17 9	£11 12 6
GARRARD SL. 65B	£19 6 5	£14 9 6
GARRARD SL. 75B	£35 12 4	£28 19 6
GARRARD SL. 95B	£45 9 1	£37 19 6
GARRARD 40	£31 14 2	£25 19 6
GARRARD SL. 72B	£30 2 0	£24 19 6
GARRARD 3500 with GKS Cartridge	£15 15 0	£11 19 6
GOLDRING GL 69	£25 1 6	£21 5 0
GOLDRING 69P	£33 11 9	£28 19 6
GOLDRING GL. 75	£36 8 2	£27 19 6
GOLDRING 75P	£46 18 8	£38 0 0
GOODMANS 3025	£37 14 9	£32 19 6
<b>GOLDRING COVERS for 69P and 75P</b>		
THORENS TD. 125	£4 4 3	£3 6 0
THORENS 125 AB	£75 17 8	£59 19 6
THORENS 125 AB	£120 3 11	£99 19 6
THORENS TD 150	£29 9 1	£24 19 6
THORENS TD 150B	£33 13 0	£26 19 6
THORENS 150A MK II	£43 12 7	£32 19 6
THORENS 150AB MK II	£47 8 7	£40 19 6
THORENS TD 126/II	£46 15 10	£39 19 6

Bases, plinths and covers stocked.

## HI-FI STEREO TAPE DECKS AND TAPE RECORDERS

	Rec. Retail Price	Comet Price
AKAI 150D	£130 2 4	£109 0 0
AKAI X-360	£230 0 0	£200 0 0
AKAI X-360 D deck	£290 0 0	£243 0 0
AKAI 1710	£109 0 0	£89 19 6
AKAI 1800	£158 0 0	£133 0 0
AKAI 1800SD	£199 0 0	£167 0 0
AKAI 4000 D deck	£37 10 0	£31 19 6
TRUVOX PD 120 deck	£114 15 3	£79 0 0
MARCONI 4218 Stereo tape Recorder	£89 11 2	£69 19 6
MARCONI 4238 4-track tape Recorder	£58 11 0	£49 19 6
TRUVOX R52 & R54 3-speed 2-track	£77 5 1	£52 2 0

Tandberg also available

	Rec. Retail Price	Comet Price
<b>PICKUP ARMS</b>		
GOLDRING Lenco L75	£12 6 6	£10 19 6
GOLDRING Lenco G65	£7 13 6	£6 19 6
SME 3000 with S2 shell	£31 6 3	£24 19 6
SME 3012 with S2 shell	£33 7 3	£26 19 6

	Rec. Retail Price	Comet Price
<b>CHASSIS</b>		
Goodmans Axiote 8	£7 2 1	£5 13 6
Goodmans Twinxlatte 8	£8 0 7	£6 14 0
Goodmans Axiom 10	£8 0 0	£6 14 0
Goodmans Axiom 201	£12 10 0	£9 7 6
Goodmans Axiom 301	£17 16 0	£13 6 6
Goodmans Axiom 51	£11 6 0	£8 9 6
Goodmans Axiom 61	£16 7 0	£12 5 6
Goodmans Axiom 81	£27 12 0	£20 14 9
Goodmans Axiom 91	£31 5 0	£23 9 6
Goodmans Axiom 91/100	£34 17 0	£26 2 0
Goodmans ARU 180	£37 17 8	£28 19 6
Goodmans ARU 280	£37 17 8	£28 19 6
Goodmans ARU 480	£5 8 5	£4 1 3
Goodmans ARU 172	£37 17 8	£28 19 6
Goodmans Trebox 100	£7 9 0	£5 11 6
Goodmans Trebox 5K/20KL	£8 8 0	£6 8 0
Goodmans Mixax	£34 4 0	£26 2 0
Goodmans Attenuator	£3 1 4	£2 6 0
Goodmans Crossover Networks XO/950/5000	£8 8 7	£6 6 0
Goodmans Crossover Networks XO/950	£6 7 9	£4 15 9
Goodmans Crossover Networks XO/5000	£2 6 0	£1 14 6
Wharfedale 8" Bronze/RS/DD	£4 8 0	£3 13 6
Wharfedale Super 8/RS/DD	£7 12 0	£6 6 0
Wharfedale Super 10/RS/DD	£12 14 0	£10 19 6
Wharfedale VMT 1 Matching Transformer	16 9	13 6

	Rec. Retail Price	Comet Price
<b>CARTRIDGES</b>		
Goldring G65 Pick-up Arm	£7 16 1	£6 4 6
Goldring L75 Transcription Arm	£12 10 10	£10 0 0
Goldring 800 Cartridge	£13 0 0	£10 7 6
Goldring 800H	£10 13 9	£8 19 6
Goldring 800E	£18 17 1	£15 0 0
Goldring 800 Super E	£26 0 1	£20 15 0
Goldring CS90 Stereo Ceramic Cartridge	£5 4 0	£4 3 0
Goldring CS91/E	£7 16 1	£6 4 6
Ortofon SL 15E	£29 12 11	£23 12 11
Ortofon 2X 15K	£7 0 0	£5 5 4
Shure M3DM	£7 8 3	£6 6 3
Shure N3D	£5 11 2	£4 6 8
Shure M31E	£12 19 5	£10 6 0
Shure N31E	£9 5 3	£7 6 6
Shure M32E	£12 0 11	£9 12 0
Shure N32E	£8 6 9	£6 13 0
Shure M32-3	£11 2 4	£8 17 6
Shure N32-3	£6 9 8	£5 3 6
Shure M44-5	£11 2 4	£8 17 6
Shure N44-5	£7 8 3	£6 6 0
Shure M44-7	£10 3 10	£8 5 0
Shure N44-7	£6 9 8	£5 3 6
Shure M44-C	£10 3 10	£8 5 0
Shure N44-C	£6 9 8	£5 3 6
Shure M44E	£14 16 6	£11 16 6
Shure N44E	£10 3 10	£8 5 0
Shure M55E	£16 13 6	£14 13 6
Shure N55E	£11 2 4	£8 17 6
Shure M75G	£17 12 1	£14 0 0
Shure N75G	£9 5 3	£6 17 6
Shure M75-6	£16 13 6	£13 6 0
Shure N75-6	£8 6 9	£6 13 0
Shure M75EJ	£24 1 9	£19 4 6
Shure N75EJ	£11 2 4	£8 17 6
Shure M75EJ-95G	£27 15 11	£22 3 0
Shure N75E	£12 19 5	£10 6 0
Shure V15-11	£40 15 3	£32 19 6
Shure VN15E	£16 13 6	£14 13 6
Shure V15-11-7	£38 18 3	£31 0 0
Shure VN7	£14 16 6	£11 16 6

# COMET Hi-Fi DISCOUNT WAREHOUSES

Reservoir Road, Clough Road, Hull. Tel 407906  
68a Armley Rd (Artist St) Leeds LS12 2EF Tel 32055

Customers are welcome to call personally.  
Ample Car Parking facilities

Comet guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press.  
Add 9/- for post and packing on all orders. Make cheques, Money Orders payable to "COMET"

# R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

- \* Super 30 Amplifier (30 watt) in veneered housing
- \* Goldring Transcription Turntable on Plinth
- \* Shure or Goldring Magnetic Pick-up Cartridge
- \* Pair of Stanway II Loudspeaker Units

Special total price. Four fully wired units ready to "plug-in". Carr. 30/-  
**86 Gns.**  
 TERMS AVAILABLE ALL PACKAGE OFFERS

Matching as recommended for optimum performance. Send for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.

- \* Super 30 amplifier (30 watt) in veneered housing
- \* Garrard SP25 Mk II Turntable on Plinth
- \* Goldring CS90 Ceramic P.U. Cartridge with diamond stylus
- \* Pair Stanway II Speaker Units

Four fully wired units ready to "plug-in". Special total price **76 Gns.** Carr. 30/-  
 \* TA12 Amplifier (13 watt) in veneered housing  
 \* Garrard SP25 Mk II 4 sp. player unit on plinth  
 \* Goldring CS90 Ceramic P.U. Cartridge **53 Gns**  
 \* Pair of Dorchester Loudspeaker Units  
 Special total price Carr. 25/-  
 Or Dep. £10.0.3 and 9 mthly. payments **£5.15.5** (Total 59 gns.). Transparent plastic cover 3 gns. extra.

## AUDIOTRINE HIGH FIDELITY LOUSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 15 ohms. Please state choice. Except Max. performance. \*  
 Prices include carriage.  
 HF100D 10" 15W £4.19.9  
 HF510L 5" 10W 49/9 HF120 12" 15W 75/9  
 HF801D 8" 8W 59/9 HF120D 12" 15W 89/9  
 HF811D 8" 10W 4 gns. HF126 12" 15W £5.5.0  
 HF102D 10" 10W 65/- HF126D 12" 15W £5.15.0

EXTREMELY ATTRACTIVE PLINTHS finished in Teak or Afrormosia veneer. Trans. plastic cover.

## RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover Ready to plug into Amplifier or Tape recorder.  
**RP2C** Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. **23 Gns.**  
**RP5C** Garrard 2025 Auto Unit fitted Garrard GCS 23 Stereo Cartridge with diamond tip. Plinth & Cover as RP2C. inc. carr. **15 Gns.**  
 Other types available with Magnetic cartridges and with alternative design plinths. Limited Number of CLEARANCE LINES in leading makes of Hi-Fi equip. at Branches only

As above but with Garrard 3000 Autochanger (fitted Sonotone 9 TA Cartridge) in lieu of SP25 or Dep. £9 and 9 monthly payments. **£5.4.9** (Total £56.2.9). Transp. plastic cover 3 gns. extra inc. carr. Carr. 25/- **47 1/2 Gns.**

## R.S.C. TA12 MKII 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED. SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL. Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, 'Mike' etc. \* 3 separate switched input sockets on each channel  
 \* Separate Bass and Treble controls  
 \* Slide Switch for mono use  
 \* Speaker Output 3.5 ohms or 200-250V A.C. mains  
 \* Frequency Response 30-20,000 c.p.s.—2dB \* Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise—70dB \* Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV. Output rating I.H.F.M. \* Handsome brushed silver finish Facia and Knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 mthly payments **13 1/2 Gns.**  
 Dep. £5.10.6 and 9 monthly payments **£2.1.7** (Total £24.4.9).



## HIGH FIDELITY LOUSPEAKER UNITS

Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. credit terms available.

**DORCHESTER** Size 16 x 11 x 9 in. Appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High Flux 13x8 in. Dual cone spkr. Imp. 3 or 15 ohms. Carr. 7/6

**STANWAY II** Size 20x10x19 in. approx. Rating 10 watts. Inc. Fane 13x8 in. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.**

## R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER



200-250V. A.C. mains operated. Frequency Response 30-20,000 c.p.s.—2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble

'lift' and 'cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **7 Gns.** Carr. 7/6  
 Or factory built with 12 months' guarantee. **£8.19.9**

## R.S.C. PLINTHS

for Record Playing units, cut for Garrard 1025, 2025, 3000, AT60, SP25 etc. Inc. Carr. **6 Gns.**  
 Available **5/9** with trans. plastic cover. **6 Gns.**

## INTEREST CHARGES REFUNDED

On Credit Sales settled in 3 months.

**LINEAR L10 HIGH FIDELITY 10W AMPLIFIER** with separate Pre-amp. Magnet P.U. matching. To clear **10 Gns.**

## THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

\* Moderate size, only 25 x 14 x 10 in. Complete Kit **20 Gns.**  
 \* Response 30-20,000 c.p.s. Impedance 15 ohms  
 \* Performance comparable with units costing considerably more. Consists of (1) 12 in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5 in. high flux middle range 'speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £5.10.6 and 9 monthly payments 39/- (Total £23.1.0). DEMONSTRATIONS AT ALL BRANCHES

## R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

\* High-sensitivity. \* 200-250V. A.C. Mains operation. \* Sharp A.M. Rejection. \* Drift-free reception. \* Output ample for any amplifier (approx. 500 m.v.). \* Output for feeding Stereo Multiplexer. \* Tuner head using silicon Planar Transistors. \* Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. Printed circuitry. A quality product at considerably less than the cost of comparable units. Factory built 18 gns. Or in Teak finished cabinet as illustrated 21 gns. Terms: Deposit £6.1.0 and 9 monthly payments. 2 gns. Total £24.19.0. Stereo version, 23 gns. All prices include carriage.

## R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1 An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram 52/6 or assembled 3 Gns.  
**R.S.C. SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER**  
 Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. Carr. 12/6  
 or factory built 15t Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9) or in Teak or Afrormosia veneered housing. 19 Gns.

# R.S.C. SUPER 30 MKII HIGH FIDELITY STEREO AMPLIFIER

High Grade Components Specifications comparable with units costing considerably more.

TRANSISTORS 9 high quality types in each channel.

OUTPUT 10 Watts R.M.S. continuous into 15Ω (per channel). 15 Watts R.M.S. continuous into 3Ω.


INPUT SENSITIVITIES Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5 mV.

FREQUENCY RESPONSE ± 2 dB. 10-20,000 c.p.s.

TREBLE CONTROL +17 dB to -14 dB at 10 Kc/s.

BASS CONTROL +17 dB to -15 dB at 50 c/s.

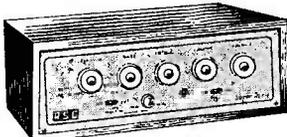HUM LEVEL -80 dB.  
 HARMONIC DISTORTION 0.1% at 10 watts 1,000 c.p.s.



FACIA PLATE Attractive design in rigid Perspex. Spun silver finish matching control knobs as available.

## COMPLETE KIT OF PARTS Carr. 15/- 22 Gns.

Point to point wiring diagrams and detailed instructions. Eminently suitable for use with any make of Pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first-rate ancillary equipment. UNIT FACTORY BUILT 29 Gns. With 12 mths. guarantee. or Deposit £7.5.0 and 9 monthly payments 58/9 (Total £33.13.9) or in Teak or Afrormosia veneer housing 32 Gns. Carr. 15/-. Terms: Deposit £7.3.6 and 9 monthly payments of 66/- (Total £37.2.0). Send S.A.E. for leaflet.

## PARTRIDGE "JOYSTICK" SHORT WAVE AERIALS AND TUNERS AT ALL BRANCHES (S.A.E. for full list)

**BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349

**BLACKPOOL** (Agent) O. & C. Electronics, 227 Church Street

**BIRMINGHAM** 30/31 Gt. Western Arcade 021-236-1279 (Half-day Wed.)

**DERBY** 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361

**DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043

**EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. Waverley 5766

**GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. CITY 4158

**HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: 102 Henconner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or G.O.B. Postage 4/6 extra under £2. 5/6 extra under £5. Trade supplied. S.A.E. with enquiries.  
 Branches open all day Sat. MAIL ORDERS MUST NOT BE SENT TO SHOPS

32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**

5-7 County (Mecca) Arcade, Brigzate (Half-day Wed.) **LEEDS** Tel. 28252

73 Dale St. (Half-day Wed.) Tel. CENTral 3573 **LIVERPOOL**

238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**


60A Oldham Street (Half-day Wed.) Tel. CENTral 2778 **MANCHESTER**

106 Newport Rd. (Half-day Wed.) Tel. 47096 **MIDDLESBROUGH**

41 Blackett Street (Opp. Fenwick's Store) **NEWCASTLE UPON TYNE** Tel. 21469

13 Exchange Street (Castle Market Bldg.) **SHEFFIELD** (Half-day Thursday) Tel. 20716

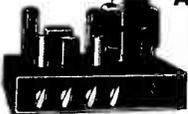
### R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive, Push-Pull high output with Pre-amp Tone Control Stages. Performance features of factory built units: Hum level — 70dB. Frequency response  $\pm 3\text{dB}$  30-20,000/c/s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC81, 80T, 80T, C234. Separate Bass and Treble Controls. Sensitivity 36mV. Suitable for high impedance microphones. Crystal or Ceramic P.U.'s. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape, Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls to that two separate inputs such as Gram and "Mike" can be mixed. 200-250v, 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. **15 Gns.** Carr. 1/26

Twin-handled perforated cover 27/6. Supplied factory built with EL34 output valves. 12 months' guarantee for 18 Gns. TERMS: Deposit  $\pounds 6.3.0$  and 9 monthly payments of 34/- (Total  $\pounds 21.9.0$ ). Send S.A.E. for leaflet.
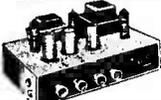
### R.S.C. All HIGH FIDELITY 12-14 WATT AMPLIFIER



PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with mixing facilities High sensitivity, 5 valves. Independent Bass and treble controls. Frequency response  $\pm 3\text{dB}$  30-20,000 c/s. Hum level — 60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High impedance "mikes".

For Musical Instruments etc. Std. AC mains. For 3 & 15 ohm speakers. SAE for leaflet. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 11/6. Twin handled metal cover 27/6. Price Factory built 13 1/2 Gns. or Deposit 99/6 and 9 monthly payments of 26/- (Total  $\pounds 16.13.6$ ). R.S.C. All HI TRANSISTORISED VERSION of above complete kit 9 Gns. (Assembled 13 Gns.)

### 30 WATT HI-FI AMPLIFIER

FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP. A 2 or 4 input, 2 vol. control HI-FI unit with Separate Bass and Treble controls. B.V.A. valves. Peak output rating. Strong Resine covered cabinet with handles. Attractive black/gold perspex fascia. Neon indicator. For 200-250v, A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit 8 gns. and 9 monthly payments of 39/8 (Total 22 gns.) **19 Gns.** 12/6



### FANE ULTRA HIGH POWER LOUSPEAKERS

All power ratings are R.M.S. continuous. 2 years' guarantee. High Flux ceramic magnets. Heavy cast chassis. All prices carr. free

<b>'POP' 100</b> 18" 100 Watt 14,500 gauss 8/15Ω	<b>'POP' 60</b> 15" 60 Watt 14,000 gauss 15Ω	<b>'POP' 50</b> 12" 50 Watt 14,000 gauss 15Ω	<b>'POP' 30C</b> 12" 25 Watt Dual cone 15Ω
<b>21 GNS.</b>	<b>12 GNS.</b>	<b>10 GNS.</b>	<b>£5-19-9</b> Carr. free

### FANE LOUSPEAKERS

12" 25 Watt Dual cone 15Ω **£5-19-9** Carr. free

F.A.L. P.A. AMPLIFIERS PHASE 29 GNS. PHASE 50 100 59 GNS. S.A.E. for leaflets.

### R.S.C. COLUMN SPEAKERS

Covered in two-tone Resine/Vynair, ideal for vocalists and Public Address. 15 ohm matching. C57 15 watts inc. five 7 x 4in. speakers  $\pounds 7.19.11$ . TYPE C485 25/30 WATTS. Fitted four Rin. high flux 8 watt speakers. Overall size approx 42 x 10 x 5in. **16 Gns.** Carr. 10/-

Or deposit 67/- and 9 monthly payments 34/9 (Total  $\pounds 18.19.9$ ). TYPE C4125, 50 WATTS. Fitted four 12in. 11,000 line 15 watt speakers. Overall size 56 x 14 x 9in. approx. **15 Gns.** Carr. 15/-

Or Deposit  $\pounds 5.17.6$  and 9 monthly payments of 54/6 (Total  $\pounds 30.7.0$ ).



### R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primaries 200-250v, 50c/s. Screened MIDGET CLAMPED TYPE 24" x 24" x 24in.

250-0-250v, 6.3v, 2a.	17/11
250-0-250v, 60mA, 6.3v, 2a.	18/11

FULLY SHROUDED UPRIGHT MOUNTING

200-0-250v, 60mA, 6.3v, 2a.	24/9
250-0-250v, 100mA, 6.3v, 4a.	33/9
300-0-300v, 100mA, 6.3v, 4a.	39/9
300-0-300v, 130mA, 6.3v, 4a.	47/11
350-0-350v, 100mA, 6.3v, 4a.	39/9
350-0-350v, 150mA, 6.3v, 4a.	47/9
425-0-425v, 200mA, 6.3v, 4a.	89/9
425-0-425v, 200mA, 6.3v, 4a.	93/9
450-0-450v, 250mA, 6.3v, 4a.	99/9

TOP SHROUDED DROP-THRU TYPE

250-0-250v, 70mA, 6.3v, 2a.	23/9
250-0-250v, 100mA, 6.3v, 3.5a.	27/9
250-0-250v, 100mA, 6.3v, 2a.	28/9
350-0-350v, 80mA, 6.3v, 2a.	29/11
250-0-250v, 100mA, 6.3v, 4a.	39/9
300-0-300v, 100mA, 6.3v, 4a.	39/9
300-0-300v, 130mA, 6.3v, 4a.	46/9

Suitable for Mullard 510 Amplifier

350-0-350v, 100mA, 6.3v, 4a.	39/9
350-0-350v, 150mA, 6.3v, 4a.	46/11

FILAMENT OR TRANSISTOR POWER PACK Types

6.3v, 1.5a, 8/9; 6.3v, 2a, 9/9; 6.3v, 3a, 13/9; 6.3v, 6a, 22/9; 12v, 1v, 9/11; 12v, 3a, or 24v, 1.5a, 23/9; 0.9-18v, 1.1a, 19/11; 0.12-2.5-4.2v, 2a, 31/9	
---	--

CHARGE TRANSFORMERS 0.9-15v, 1.1a, 18/9; 2.1a, 19/11; 3a, 21/11; 5a, 25/11; 6a, 29/9; 8a, 36/9

AUTO (Step UP/step DOWN) TRANSFORMERS 0-110/120v, 200-230-250v, 50-80 watts 19/9  
150 watts, 33/6; 250 watts 49/9; 500 watts 105/-

OUTPUT TRANSFORMERS

Standard Pentode 1000 Ω or 7,000 Ω to 3 Ω	8/9
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω	14/9
Push-Pull 10 watts 6V6 ECL86 to 3, 5, 8 or 15 Ω	24/9
Push-Pull EL84 to 3 or 15 Ω 10-12 watts	23/9
Push-Pull Ultra Linear for Mullard 510, etc.	39/9
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15 Ω	35/9
Push-Pull 20 watt high quality sectionally wound EL84, 6L6, KT66 etc. to 3 or 15 Ω	59/9

SMOOTHING CHOKES - 150mA, 7-10H, 250 Ω 12/9; 100mA, 10H, 200 Ω 10/9; 80mA, 10H, 350 Ω 8/9; 60mA, 10H, 400 Ω 4/11.

SELENIUM RECTIFIERS F.W. (Bridged) All 6/12v, D.C. output. Max. A.C. input 18v. 1a, 4/3, 2a, 6/11, 3a, 9/9, 4a, 12/9, 6a, 15/9.

### HIGH QUALITY LOUSPEAKERS

In Teak or Afrmosia veneered Cabinets

L13 13" x 8" 10 Watt 10,000 lines	<b>£4-19-9</b>
3 or 15 ohms.	Carr. 7/6
L12 12" 20 Watt 10,000 lines	
15 ohms.	Carr. 8/9

**£8-19-9**

### R.S.C. BASS-REAGENT 50 WATT AMPLIFIER

An exceptionally powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak O-P rating.

★ Two extra heavy duty 12in. Loudspeakers.

★ Four Jack inputs and Two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls.

**55 Gns.** Carr. 30/- or dep.  $\pounds 13.4.9$  and 9 monthly payments of  $\pounds 5.11.9$ . (Total  $\pounds 60$  gns.) Send S.A.E. for leaflet.

G100 100 watt peak output with Pr. speaker columns and a Bass Unit (Six 12" and Two 15" Speakers). 99/ gns.

# YOURS FREE FOR 7 DAYS

## The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 vols.) ELECTRONICS (6 vols.)



You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

**WHAT READERS SAY**

... played an important part ...  
These Manuals have played an important part in my career ... K.W., West Drayton.

... a sound basis ...  
These books create a sound basis on which to build a successful future ... R.G., Lowestoft.

... well set out ...  
I am well pleased with the series. Everything is well set out in self-explanatory diagrams ... D.D., West Ham.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY  BASIC ELECTRONICS

Prices include Postage and Packing.

Signature \_\_\_\_\_  
(If under 21 signature required of parent or guardian)

NAME \_\_\_\_\_  
BLOCK LETTERS

FULL POSTAL ADDRESS \_\_\_\_\_

A TECH-PRESS PUBLICATION

**POST NOW FOR THIS OFFER !!**


# HENRY'S RADIO LTD.

ELECTRONIC COMPONENTS AND EQUIPMENT  
303 EDGWARE ROAD LONDON W.2 01 723 1008 9  
Open Monday to Saturday 9am to 6pm - Thurs 1pm  
Open all day Saturday.


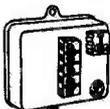
## \*EXPERIMENTORS MODULE

Brand new STC time delay electronic units. Relay output. Adjustable 3-15 secs. 9-12 volt operated. Supplied complete with uses and circuits **STC Module Price 35/-** or 3 for 99/-.



## \*MULTIMETER

Return of a popular model. 2000ohms/V 0/10/50/500/1000V ac/dc. 0/50uA. 0/10/250mA d.c. 0/10/100kΩ/1MΩ resistance. dB and capacitance scales. Size 5 x 3 1/2 x 1 1/2" Robust and easy to use. Complete with leads, batteries and instructions **THL32a. Price £2/6** p.p. 2/8. Leather case—Price 22/6.



## \*GRID DIP METER

All transistor grid dip meter, absorption and osc. detector. Frequency range 440 kc/s to 280Mc/c in 6 coils. Uses 3 transistors plus diode with 500uA meter. Internal battery. **TE 15 Price £11.10.0** p.p. 3/6.



## \*MULTI-METER 20KΩ/V



Popular model but with extra scale range 20,000 ohms per volt. 0/5/25/50/250/500/2500V d.c. 0/10/50/100/500/1000Va.c. 0/50uA, 0/2/250mA. Resistance 0-5kΩ and 6MΩ. Also dB scales and capacitance. **200M. Price 7/6** p.p. 2/-.  
Leather case, Price 15/-.

# FREE

16 PAGE BROCHURE COVERING LOW COST TEST EQUIPMENT FULLY DETAILED AND ILLUSTRATED. OVER 50 UNITS DETAILED ASK FOR PUBLICATION 'T' - REMEMBER IT'S FREE!


## \*SINE/SQUARE WAVE AUDIO GENERATOR

Provides audio output on 4 bands. Sine wave 200c/s to 2000c/s, output up to 7V; square wave 60c/s to 30kc/s, 7V p.p. Distortion under 2%. Output impedance 1kΩ. Variable output amplitude control. Supplied with leads and instructions. A.C. mains operated. **TE22. Price £16.10.0.** Carriage, etc., 10/-.



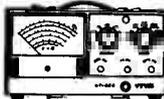
## \*LOW COST VACUUM TUBE VALVE VOLTMETER

New Model Multi-Range and easy to use. DC and AC. Volts 0/1/5/15/50/150/500/1500. AC p-p 0/4.2/14/42/140/420/1400/4200. Resistance 0.2 ohm to 1000 Megohm—7 ranges. dBm scales—20 to +25 dBm. Input impedance: DC 11 Meg, AC ±5 Meg. Response: ±1dB 20c/s to 5 Mc/s. Complete with probe and handbook. Size 10 1/2" x 5 1/2" x 4 1/4". **VT550 Price £16.10.0** p.p. 7/6.




**BUILD YOURSELF A QUALITY RADIO**

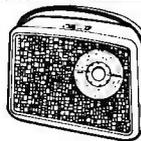

New printed circuit design with full power output. Fully tuneable on both mw/lw. bands. 7 Mullard transistors. Fitted 5" speaker. Room Filling Power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered front. All local and continental stations. Complete detailed instructions. **TOTAL COST £8.19.6** p.p. 4/8. Ask for Leaflet No. 1.
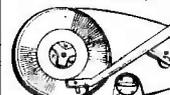
## \*SCOOPI! STAAR RECORD PLAYER

Deck plays 33, 45, 78, R.P.M. records. 9 volt operated, with mono cartridge. **BRAND NEW...** as illustrated.



Price 59/6. p.p. 3/6. Send for leaflet No. 2



**MULLARD 1 WATT AMPLIFIER**  
Portable Transistor Unit—ideal for intercoms, Baby Alarms, Telephone, Record Players or Guitar Practice. 9 Volt 5 transistors with volume control, output 3 ohms. Ideal for use with **STAAR RECORD DECK. Price 45/-**, p.p. 2/6.

## \*FIELD STRENGTH METERS



5-ranges 1-250 Mc/s. Fitted 200uA meter. Earphone output. Calibrated tuning scales. **FL30HA Price 7/6** p.p. 2/-.  
Also non calibrated type peaking F/S Meter **F81 Price 45/-** p.p. 2/6

## \*TRANSISTOR CHECKER

Complete capacity for checking all transistors npn and pnp for alpha, beta and leakage. Also diodes complete with leads and instructions. **ZQM-2. Price £5.19.6** p.p. 3/6.



## \*SIGNAL INJECTOR AND TRACER





New model for checking all audio and RF up to VHF. Simple to use. Battery operated. Output approx. 1kc/s, 1.4V pp. Harmonics up to VHF. **SE250B Price 35/-** p.p. 1/6.  
\* Matching Signal Tracer. **SE500 Price 2/6** p.p. 1/-.

**ALL PARTS IN STOCK TO BUILD THE INTEGRATED CIRCUIT DESIGNS APPEARING IN PRACTICAL WIRELESS AND ELECTRONICS. ASK FOR QUOTATIONS—SEE LATEST CATALOGUE EDITIONS.**
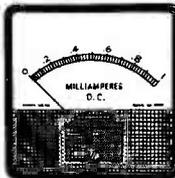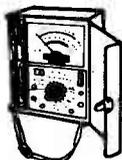
## \*50,000 OHMS PER VOLT MULTIMETER

Recommended quality instrument with mirror scale and overload protection. 0/0.3/3/12/60/120/300/600/1200V d.c. 50kΩ/V; 0/6/30/120/300/600/1200V a.c. 10kΩ/V; 0/30uA 6/300mA, 0/12A; resistance 0/10kΩ/1/10/100MΩ. Meter movement 20uA. Polarity reversing switch. Complete with batteries, leads and instructions. **AF103, Price £8.10.0** p.p. 2/6. Leather case 28/6.



## \*QUALITY PANEL METERS (D.C. RANGES)

33 Series. Face size 42 x 42mm (1 1/2 in. x 1 1/2 in). 50uA, 37/6; 10uA, 35/-; 200uA, 32/6; 600uA, 27/6; 1mA, 5mA, 10mA, 50mA, 100mA, 500mA, 25/- each; 10V, 20V, 50V, 100V, 300V, and 500V, 25/- each; 1A and 5A, 25/- each. "S" meter, 1mA, 29/6; VU meter, 37/6.  
65 Series. Face size 86 x 78mm (3 3/8 x 3 1/8 in). 50uA, 62/6; 100uA, 52/6; 200uA, 47/6; 500uA, 45/-; 1mA, 5mA, 10mA, 500mA, 37/6 each. "S" meter, 1mA, 42/6. Other ranges and sizes in stock. Leaflet No. 33.

## \*10 in I TEST UNIT

A NEW DESIGN TESTS MOST CIRCUITS Model SE400 Price £9.10.0




\*AC/DC Volts (4K/Volt) 0/15/50/150/500. \*Resistance 0/10K/100K/1 Meg. \*Five values resistance and capacitance substitution. \*RF F/S Meter 1 to 140 Mc/s \*DC Ammeter 0/500mA. \*455/700kc/s RF Generator \*400c/s Audio Generator. Size 7 1/2" x 3 3/4" x 3 1/4"

**COMPONENTS** UK'S LARGEST STOCKISTS  
ASK FOR QUOTES—SEE LATEST CATALOGUE

**HENRY'S FAMOUS CATALOGUES—SEE BACK COVER FOR DETAILS**
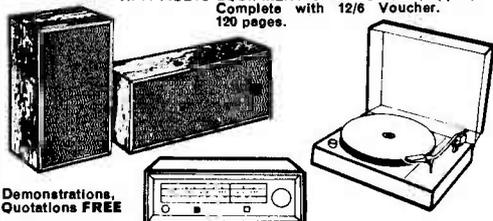
## HI-FI equipment to suit EVERY POCKET

HI FI AUDIO EQUIPMENT CATALOGUE 5/- pp. 1/-.  
Complete with 12/6 Voucher.  
120 pages.



Demonstrations. Quotations FREE

VISIT OUR HI-FI CENTRE AT 309 EDGWARE ROAD, for all leading makes of AMPLIFIERS, TUNERS, DECKS, SPEAKERS, MICROPHONES, TEST EQUIPMENT. ALL WITH DISCOUNTS—IT WILL PAY YOU TO PAY US A VISIT. AUDIO SYSTEMS £40-£300 TO SUIT. SEND FOR BROCHURE 16/17.

## ELECTRONIC ORGANS

- ★MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT.
- ★TEAK VENEERED CABINETS FOR ALL MODELS.
- ★49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE.
- ★KITS AVAILABLE IN SECTIONS AS REQUIRED.
- ★HP and CREDIT SALE FACILITIES. WHEN IN LONDON CALL IN AND TRY FOR YOURSELF.



FREE 16 PAGE ORGAN BROCHURE COVERING ORGANS IN KIT FORM AND READY BUILT—WRITE OR PHONE TO ORGAN DEPT. ASK FOR PETER ELVINS.

# BRAND NEW FULLY GUARANTEED TRANSISTORS & DEVICES

1N4001	2/-	2N4211	25/-	80M	50/-	CRS150	8/-	OA9	3/-
1N4002	2/3	2N4292	35/-	RA110	5/-	CRS155	8/6	OA10	4/-
1N4003	2/6	2N431	15/-	RAV31	3/-	CRS160	9/6	OA27	2/-
1N4004	3/-	4062	15/6	BC107	3/-	CRS305	6/-	OA70	2/-
1N4005	3/6	25001	10/-	BC108	2/9	CRS310	6/-	OA71	2/-
1N4006	4/-	25002	10/6	BC109	3/-	CRS320	7/6	OA73	2/-
1N4007	5/-	25003	10/6	BC113	3/-	CRS330	7/6	OA74	2/-
1N4009	1/6	25004	9/6	BC116	3/-	CRS340	10/-	OA79	2/-
1N4148	1/6	25005	15/-	BC118	7/6	CRS400/396	4/-	OA81	2/-
1N4785	10/-	25012	25/-	BC124	5/-	CRS025AF	4/-	OA82	2/-
2G10	12/6	25012A	22/6	BC135	6/-			OA86	4/-
2G240	49/6	25013	20/-	BC136	7/-	CRS25025	15/-	OA90	2/-
2G301	4/-	25013A	25/-	BC137	8/-	DD088	3/9	OA91	1/6
2G302	4/6	25017	15/-	BC138	8/-	DD088	6/-	OA95	1/6
2G303	5/-	25018	17/6	RCY30	5/6	DD190	12/6	OA200	1/9
2G306	7/6	25020	50/-	RCY31	8/6	DD226A	7/6	OA202	2/-
2G309	6/-	25025	60/-	RCY32	5/6	DD267A	3/9	OA210	2/6
2G339A	3/-	25026	100/-	RCY34	6/-	DK10	1/6	OA211	9/6
2G371	4/6	25034	12/6	RCY38	7/6	DD3200	7/6	OA220	11/-
2G374	5/6	25036	25/-	RCY39	5/6	FST10	3/6	OA221	10/6
2G381	5/-	25102	10/-	BCY40	10/-	FST21	3/-	OA230	8/6
2G382	5/-	25103	12/6	BCY42	5/-	FST30	3/-	OA234	8/6
2G378A	4/6	25104	12/6	BCY43	6/-	FST40	3/-	OA235	8/6
2G383	5/-	25101	7/6	BCY70	4/-	FST38	6/-	OA236	8/6
2G304	4/6	25131	6/-	BC211	7/6	FST05 AF	3/-	OA207	9/6
2G305	5/-	25132	7/6	BC147	5/9	GET102	6/-	OA208	6/6
2N404	4/-	25303	10/-	BC148	2/9	GET103	4/6	OA209	6/6
2N456	15/-	25304	12/6	BC149	2/9	GET105	4/6	OA210	6/6
2N458	20/-	25305	15/-	BF152	6/-	GET106	10/-	OA211	6/6
2N503	9/6	25320	9/-	BF182	5/6	GET107	5/-	OA212	6/6
2N599	12/6	25321	6/-	BF194	3/6	GET113	5/-	OA213	6/6
2N601	3/6	25322	7/6	BF195	3/6	GET114	4/-	OA222	9/6
2N696	4/6	25323	10/-	BTY79/100R	15/-	GET116	10/-	OA225	9/6
2N697	5/-	25324	12/6	BT102/500R	15/-	GET120	5/-	OA231	9/6
2N698	8/6	25501	8/6			GET121	5/-	OA232	9/6
2N708	1/6	25502	8/6	BD119	12/6	GET880	9/6	OA241	4/6
2N706A	2/6	25503	9/6	BD124	12/6	GET882	6/-	OA224	7/6
2N707	12/6	25512	9/6	BEV3000	5/-	GET883	5/-	OA225	7/6
2N711	7/6	25701	8/6	BF115	5/-	GET885	5/-	OA226	7/6
2N712	7/6	25724	50/-	BF154	8/-	GET887	4/-	OA228	7/6
2N721	11/-	25731	8/6	BF158	6/-	GET890	6/6	OA234	7/6
2N743	4/-	25732	8/6	BF159	12/-	GET890	6/6	OA237	7/6
2N744	6/-	25733	9/6	BF163	8/-	GET896	4/6	OA244	4/6
2N753	5/-	25743	50/-	BF167	5/-	GET897	4/6	OA245	4/6
2N865A	12/6	25745A	30/-	BF171	6/-	GET898	4/6	OA246	4/6
2N914	4/6	AA129	4/-	BF180	7/6	GET899	2/6	OA247	4/6
2N916	4/6	AA178	8/6	BF181	7/6	JK10A	15/-	OA272	4/6
2N918	7/6	AA179	2/-	BF190	6/-	JK10B	12/6	OA270	7/6
2N919	4/-	AA172	5/-	BF198	5/-	JK11B	9/6	OA291	7/6
2N920	5/-	AA122	4/-	BFY17	6/-	JK20A	15/-	OA292	7/6
2N923	8/6	AA123	4/-	BFY18	5/-	JK60A	2/6	OC10	10/-
2N930	7/6	AA127	2/-	BFY19	5/-	JK601B	15/-	OC19	7/6
2N1090	6/-	AC126	5/-	BFY20	12/6	MT100	5/-	OC20	19/6
2N1091	6/6	AC127	5/6	BFY21	5/-	MT101	5/-	OC22	9/6
2N1131	6/6	AC127Z	12/6	BFY31	4/6	MT120	5/-	OC23	12/6
2N1132	8/6	AC128	5/-	BFY32	5/-	MT121	6/-	OC24	12/6
2N929	4/6	AC129	4/-	BFY51	4/-	MT124	5/-	OC25	12/6
2N1304	5/-	AC154	3/-	BFY64	8/6	NKT72	5/-	OC26	5/-
2N1305	5/-	AC169	3/6	BFY10	20/-	NKT128	6/-	OC28	12/6
2N1306	5/-	AC170	3/6	BFY11	22/6	NKT132	5/-	OC29	12/6
2N1307	5/-	AC187	5/-	BPY10	19/6	NKT211	5/-	OC35	10/-
2N1308	6/-	AC188	6/-	BSX20	4/-	NKT212	4/-	OC36	12/6
2N1309	5/-	AC197	4/-	BSX21	4/-	NKT213	4/-	OC41	5/6
2N1420	18/6	ACY18	4/-	BSX76	4/-	NKT214	4/-	OC42	6/6
2N1483	9/6	ACY19	5/-	BSY27	4/-	NKT216	5/-	OC43	8/-
2N1613	9/6	ACY20	4/-	BSY28	4/-	NKT217	5/-	OC46	4/6
2N1613	9/6	ACY21	4/6	BSY29	5/-	NKT218	5/-	OC44	4/6
2N2147	17/6	ACY22	3/6	BSY50	5/-	NKT221	5/6	OC45	3/6
2N2160	15/-	ACY28	3/6	BSY51	5/-	NKT222	5/6	OC46M	3/6
2N2160	15/-	ACY29	3/6	BSY52	5/-	NKT223	5/6	OC47	3/6
2N2287	25/-	ACY36	5/-	BSY64	5/-	NK1224	4/6	OC57	12/-
2N2297	9/6	ACY39	9/6	BSY65	5/-	NK1225	3/6	OC58	12/6
2N2404	7/6	AD140	11/-	BSY66	5/-	NK1226	10/-	OC59	13/-
2N2646	10/6	AD140	11/-	BSY67	5/-	NK1227	5/6	OC71	2/6
2N2784	10/-	AD149	12/6	BSY99	4/6	NK1251	5/-	OC72	6/6
2N2904	8/6	AD170	7/6	BSY95	3/-	NK1261	5/-	OC73	6/6
2N2905	10/-	AD162	7/6	BTY42	18/6	NK1265	9/6	OC74	6/6
2N2925	4/-	ADT140	10/-	BTY79/400R	35/-	NK1271	5/-	OC75	6/6
2N2926	2/6	ADZ12	29/6	BTY84	12/6	NK1272	5/-	OC76	5/6
2N3011	7/6	AEY11	10/-	BTY86	15/-	NK1273	5/-	OC77	8/6
2N3043	5/-	AEY12	12/6	BUY10	12/6	NK1274	5/-	OC78	5/6
2N3044	12/6	AEY12	12/6	BUY11	18/6	NK1275	5/-	OC78D	2/6
2N3055	15/-	AF102	15/-	BY108	3/6	NK1277	5/-	OC79	5/6
2N3133	6/-	AF114	6/6	BY109	3/6	NK1278	5/-	OC81	5/-
2N3136	6/-	AF118	6/6	BY103	4/6	NK1279A	4/-	OC81D	4/-
2N3142	7/6	AF116	6/6	BY126	5/-	NK1281	6/-	OC81M	5/-
2N3212	15/-	AF117	5/-	BY210	10/6	NK1282	6/-	OC82	7/6
2N3233	30/-	AF118	5/-	BY211	9/6	NK1283	15/-	OC82D	3/6
2N3238	10/-	AF125	5/-	BY212	8/6	NK1284	9/6	OC82D	3/6
2N3278	9/6	AF128	4/-	BY213	5/-	NK1289	8/6	OC83	5/-
2N3702	3/6	AF127	4/-	BY215	20/-	NK1291	10/-	OC84	5/-
2N3703	3/6	AF139	6/6	BY216	12/6	NK1452	7/6	OC122	10/-
2N3704	4/-	AF128	9/6	BY288CV4	4/-	NK1453	6/-	OC123	10/-
2N3705	3/6	AF181	8/6	BY288CV4	4/-	NK1454	6/-	OC124	10/-
2N3707	4/-	AF186	9/6	BY288CV4	4/-	NK1455	6/-	OC125	10/-
2N3709	3/6	AF199	3/6	BY288CV4	4/-	NK1456	6/-	OC126	10/-
2N4291	3/-	AF211	8/-	BY288CV4	4/-	NK1457	6/-	OC127	10/-
2N4315	6/6	AF212	10/-	BY288CV4	4/-	NK1458	6/-	OC128	10/-
2N3794	2/6	ASV26	5/6	BY288CV4	4/-	NK1459	6/-	OC129	10/-
2N4292	3/-	ASV27	7/6	BY288CV4	4/-	NK1460	6/-	OC130	10/-
2N3711	9/6	ASV28	6/6	BY288CV4	4/-	NK1461	6/-	OC131	10/-
2N3730	10/-	ASV29	6/-	BY288CV4	4/-	NK1462	6/-	OC132	10/-
2N3731	12/6	ASV30	5/-	BY288CV4	4/-	NK1463	6/-	OC133	10/-
2N3818	10/-	ASV31	3/6	BY288CV4	4/-	NK1464	6/-	OC134	10/-
2N3820	19/6	ASV31	8/-	BY288CV4	4/-	NK1465	6/-	OC135	10/-
2N3823	17/6	ASV36	9/6	BY288CV4	4/-	NK1466	6/-	OC136	10/-
2N4058	5/6	TA4263	15/-	BY288CV4	4/-	NK1467	6/-	OC137	10/-
2N4061	4/-	ASV86	6/6	CP404	12/6	MPF104	7/6	OC171	9/6
2N4286	3/-	ASV21	8/6	CRS105	5/-	MPF105	8/-	ORP12	9/6
2N4288	3/-	ASV23	20/-	CRS110	5/-	OAS	3/-	ORP60	8/6
2N4289	3/6	AU110	19/6	CRS120	7/6	OA7	4/-		
2N4290	3/-	AU101	30/-						

Send for Free Copy of 1970 Transistor List (36) of a 1,000 Types Today!

INTEGRATED CIRCUITS	
BP1010	25/-
CA3014	29/6
CA3018	22/6
CA3020	29/6
CA3028A	23/6
CA3036	18/6
IC10	59/6
PA230	23/6
PA234	20/-
PA237	37/6
PA424	39/6
PA436	79/6
PA246	52/6
MC1304	55/-
TAD100	45/-
TA4263	15/-
UL903	49/6
UL900	10/-
UL910	10/-
UL914	12/6

DISCOUNTS  
10% on 12+ and 15% on 25+ any one type

QUANTITY PRICES 100+

Phone 01-723-0401 Ex. 4.

Post/Packing add 2/6 on your order.

# HENRI'S RADIO

Mail Order Dept. Components Dept.  
303 EDGWARE ROAD, LONDON W2  
Telephone 01-723 1008 9

Conds 10µf 150v tantalum 4 for 3/-. Paper conds tubular by Seimens 20µf 400v 6/-, 16µf 400v 5/-, 4µf 800v 5/-, H.V. conds. 1µf 1.6Kv 3/6, .05µf 2.5Kv 3/6, Plug & Sk 28-way with cover 4/6, Swts 2p 6w min 3/-. Toggle 2p c/o 3 for 5/-. Inst 2p 22w 2b with knob 7/6, Ledex coil 1K 3p 11w 3b 11/6, Meters 1 to 5 mA edgewise scale 0 to 2000yds 10 div 20/-, 500 µA scale 0 to 2 2A OSD 20/-, Control panel with 6x1 meg, 8x100K & 1K min type 15/6, Min panel fuse holders take 4in fuses 3 for 5/-. Pot Cores type LA.66 wound 3/6 ea, Yax Swts 6p 11w 6b with 27 1% resistors 12.6, 4p 12w 4b with 29 x 1%

# Lasky's

## SCOOP Garrard 3000

**CUSTOM UNIT** BY FAMOUS BRITISH MANUFACTURER

A deluxe custom styled and built record player unit made by world famous British manufacturer. The unit incorporates the renowned Garrard 3000 four speed autochanger with lightweight tubular pick-up arm FITTED WITH SONOTONE STA STEREO CARTRIDGE with diamond stylus. The beautifully made plinth is finished in richly figured teak veneer with tinted perspex panels in the lid and with attractive charcoal grey "mirror" insert panel on front. All metal trim parts are satin chrome. Blackleather grain underside. The lid allows the player to operate fully automatically when closed and has snap action "stay" when raised. Mains socket and 5 pin DIN audio output socket are at rear. Overall size 15 1/4 x 7 1/4 x 14 in.

**LASKY'S SPECIAL PRICE £16.15.0** Post 15/-




## AUDIO-TECHNICA

## Garrard
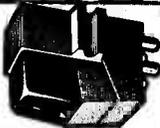
### SPECIAL OFFER

**AT-35X** Stereo magnetic cartridge with elliptical diamond stylus. Frequency response 20-25 kHz  $\pm$  2 dB. Channel separation 30 dB. Output 5mV. List Price £24.4.3.



**LASKY'S PRICE £17.10.0** Post Free

Also available AT-35 stereo magnetic cartridges with either 0.5 or 0.7 mil diamond stylus assemblies. List Price £18.10.0. Lasky's Price £13.10.0. Post Free.

**AT-33** Stereo magnetic cart.—frequency response 20-20 kHz with 0.7 mil diamond stylus. Output 5mV. List £10.14.3.

**LASKY'S PRICE £7.19.6**

## ADC 40 PRECISION PICK-UP ARM

The ADC 40 Mk II is a complete low inertia arm with side thrust compensator and anti-drag lead out arrangement. Single thrust ball bearings used at four points. Accurately machined walnut non-resonant arm. Adjustable counterweight. Plug-in head shell accommodates nearly all cartridges. Easy installations. Built-in arm rest. Arm length 10 1/2 in. overall. Pivot to stylus tip 9 in. Rear overhang 1 1/2 in.



List Price £19.1.6

**OUR PRICE £8.19.6** Post 3/6

## INTERNATIONAL

MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in. Message tape, 150ft. ....	2 6	5 1/2 in. Long play, 1200ft. Mylar ...	15 0
3in. Message tape, 225ft. ....	3 0	5 1/2 in. Triple play, 2400ft. ....	35 0
3in. Message tape, 300ft. ....	7 0	7in. Standard play, 1200ft. ....	12 6
3 1/4 in. Triple play, 600ft. Mylar ...	10 0	7in. Acetate ..... ..	12 6
5in. Double play, 1200ft. Mylar ...	15 0	7in. Standard play, 1200ft. ....	12 6
5in. Long play, 900ft. Acetate ...	10 0	7in. Mylar ..... ..	12 6
5in. Standard play 600ft. ....	8 6	7in. Long play, 1800ft. Mylar ...	15 0
5 1/2 in. Double play 1800ft. Mylar ...	22 6	7in. Double play, 2400ft. Mylar ...	25 0
5 1/2 in. Long play 1200ft. Acetate ...	15 0	7in. Long play 1800ft. Acetate ...	15 0
5 1/2 in. Standard play 900ft. Acetate ...	12 6	7in. Triple play 3600ft. Mylar ...	50 0

P. & P. 1/- extra per reel, 4 reels and over Post Free. Special quotes for quantities.

## USA MADE CASSETTES

AT LASKY'S BUDGET PRICES

C80 7 1/2 each post 1/-	38/- post 2/-	65/- post 3/-
C90 12 1/2 each post 1/-	57/- post 2/-	115/- post 3/-
C120 17 1/2 each post 1/-	88/- post 2/-	168/- post 3/-

## metro sound

CASSETTE HEAD CLEANER

This ingenious device enables the delicate recording heads and drive system of your Cassette Recorder to be cleaned without damage. Just slip in the cassette like any other cassette and run through once. Only takes moments to remove all dirt and oxide deposits.

**LASKY'S PRICE 10/8** POST 1/- EACH

## SP.25 Mk II



THE U.K.'s MOST POPULAR

### HI-FI TURNTABLE

4-speed single record playing deck features include heavy precision-built turntable, pick-up arm bias compensation, calibrated stylus-force adjustment, cueing device. After play, the arm automatically rises, returns to rest and switches off motor. Finish: dark green polychromatic and silver.



**LASKY'S PRICE £11.19.6**

SP. 25 Mk.11 with A.D.76K Stereo Magnetic Cartridge £15.0.0.

### OTHER GARRARD UNITS FROM STOCK AT LASKY'S EXCLUSIVE PRICES.

AUTOCHANGERS	3000 complete with 9TAHC stereo cartridge .....	£3 10 0
SL72B .....	SL95B .....	£3 10 0
SL72B .....	1025 with stereo cartridge .....	£3 10 0
AT80 Mk II .....	SL95B .....	£40 0 0
2025TC with stereo cartridge .....	SL75B .....	£32 0 0

**SINGLE PLAYERS**  
AP 75, £15.19.6 AP75 with AD76K mag. cart., £21.19.6. 401 Transcription Unit, £29.9.0

### BASES AND COVERS FOR GARRARD UNITS


Type WB1 and WB3 for models AT80 Mk II, 2025TC, 3000, SL65B 1025, SP25 Mk II Price £3.12.6. WB5 £5.12.6. Type WB4 for models SL72B, SL75B, SL95B Price £3.12.6. Perspex covers: SPC1 for WB1, £3.14.1. SPC4 for WB4 and WB5 (allows unit to be played with the cover in place)—price £4.5.6.

### PACKAGE DEALS

AP75 complete with AD76K Stereo magnetic cartridge, teak plinth and perspex cover	<b>£30.0.0</b>	Post 10/-
SP25 Mk II complete with AD76K cartridge, teak plinth and perspex cover	<b>£19.0.0</b>	Post 7/6
1025 complete with J2185 stereo ceramic cart., teak plinth and perspex cover	<b>£11.19.6</b>	Post 7/6

Post on Garrard units: 6/- extra—except AP75, SL75B, SL95B and 401 7/6 extra Post on bases and covers 5/- extra.

## SKYROVER mkII

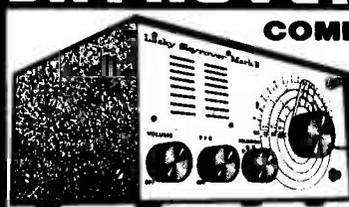

### COMMUNICATION RECEIVER

A short wave receiver, exclusive to Lasky's, at a real economy price. Four valve line up using one each 6BE6, 6BA6, 6AV6 and 6AR5 valves gives highly sensitive reception and powerful gain. Switch selected SW frequency range cover: 1.5 to 30 MHz in three separate band-spread ranges and full AM medium wave band

cover in one range 550-1,600KHz. Reduction drive tuning with hair line cursor. Controls include volume on/off BFO. Band selector. Power-on indicator lamp. External antenna connections and mains fuse at rear. Internal speaker plus standard 5mm jack socket for phones on front. For 220/240V a.c. mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9 1/2 x 5 1/2 x 5 1/2 in. Complete with mains lead and full instructions.


### THE IDEAL BEGINNERS RECEIVER

**LASKY'S PRICE £13.13.0**

Post 5/-
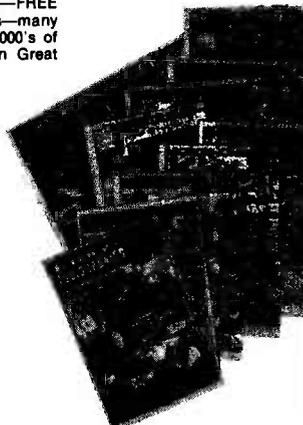
# Audio Tronics 70

The 1970 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 28 tabloid pages—many in full colour—are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast. Electronics Hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package deals). Tape recording and audio accessories PLUS Lasky's amazing money saving vouchers worth over £25. All goods are available by Mail Order—bringing the benefits of shopping at Lasky's to you in the comfort of your home.




**SEND TODAY**

Your name, address and 2/- for postage only and inclusion of your name on our regular mailing list.

**DON'T MISS THIS MONTH'S**

**VOUCHER WORTH 30/- !**

## sinclair Project 60

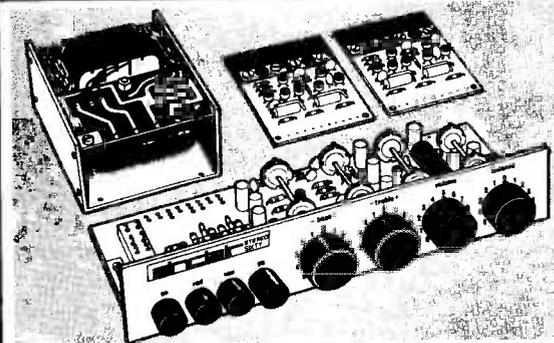

Project 60 is a range of modules which connect together to form a complete stereo amplifier. The modules are: 1. Z-30 high gain power amp. 2. Stereo-60 pre-amp, control unit. 3. The PZ-5 unswitched and PZ-6 stabilised power supplies. A complete system comprises two Z-30's, one Stereo-60 and a PZ-5 or PZ-6.

### STEREO 60 SPECIFICATION

Input sensitivities: Radio up to 3mV. Magnetic Pick-up 3mV: correct to R.I.A.A. curve  $\pm 1\text{dB}$ ; 20 to 25,000Hz. Ceramic Pick-up up to 3mV. Auxiliary up to 3mV. Output: 1 volt. Signal to noise better than 70dB. Front panel: brushed aluminium with black knobs and controls. Size:  $8\frac{1}{2} \times 1\frac{1}{2} \times 4\text{in}$

**£9.19.6** post 3/6

### Z-30 SPECIFICATION

Power output: 15 w. R.M.S. into 8 ohms using a 35 volt supply. Frequency response: 30 to 300,000Hz  $\pm 1\text{dB}$ . Distortion: 0.02%. Signal to noise: better than 70dB. Input sensitivity: 250mV into 100 K ohms. Loudspeaker imp. 3 to 15 ohms. Power requirements: from 8 to 35V DC (The Z30 will operate from batteries if required) - Size:  $3\frac{1}{2} \times 2\frac{1}{4} \times 1\frac{1}{2}\text{in}$ .

**89/6** post 3/6

30V unswitched - sufficient to drive two Z-30's and a Stereo 60 for domestic applications.

**PZ5** 35V stabilised - ideal for driving two Z-30's and a Stereo 60 for low efficiency speakers.

**99/6** Post: 2/6

**PZ6** 35V stabilised - ideal for driving two Z-30's and a Stereo 60 for low efficiency speakers.


**£7.19.6** Post 2/6

**PACKAGE PRICE** For Stereo 60, two Z-30 and one PZ-5 **£21.10.0** Post 10/-

# EXCLUSIVE

## FOSTER "Criterion" MkII
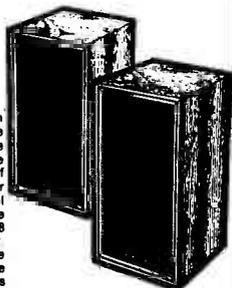
### HIGH FIDELITY 2 SPEAKER TWO WAY BOOKSHELF SPEAKER SYSTEM



Another high quality sub-miniature booksheft system from Foster. The "Criterion" MkII is a sealed infinite baffle type enclosure using 5 1/2 in. bass/mid-range woofer with rolled cloth edge and a 2 1/2 in. HF cone type tweeter. The compact cabinet is constructed of 1/2 in. laminate with handsome oiled walnut veneer finish and black woven acoustic gauze-front panel with satin chrome edge insert. SPEC: Frequency range 90-20,000Hz. Power Handling 10 watts. Impedance 8 ohms. HF crossover. Screw Tag connections at rear. Size 12 1/2 x 7 3/4 x 6 1/4 in. The performance of the "Criterion" is superior to many larger and more expensive units and at Lasky's exclusive price offers absolutely unbeatable value.

LASKY'S PRICE **£9.10.0** or **£17.10.0** Post 1-7/6 2 for 2-10/-

## SONICS AS-57

### ELEGANT BUDGET PRICED BOOKSHELF SPEAKER SYSTEMS

The AS-57 is a real space saver. This fine booksheft high-fidelity speaker system will provide good quality sound anywhere in your home at remarkably low cost. Designed for use where space is at a premium, the AS-57 system is ideal for the small apartment or isolated listening area. The special high efficiency 5x7 in. full range speaker has a frequency range of 70-18,000 Hz with a peak handling capacity of 10 watts. Imp. 8 ohms. Finish: oiled walnut. Size: 5 1/4 x 15 1/4 x 8 1/4 in. (May be used upright or longways).


LASKY'S PRICE **£15** per PAIR Post 10/-

# SPECIAL OFFER

## THIS MONTH ONLY SUPERB—WHARFEDALE
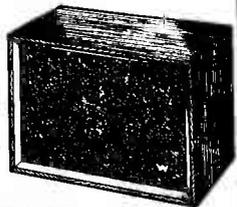
### DENTON

A compact system sold in matched pairs for a perfectly balanced stereo system. Each Denton contains an 8 in. bass unit with 3 in. H.F. pressure unit, coupled by a Wharfedale cross-over network. Rated input 15 watts maximum. Frequency response 65-17,000Hz. Impedance 4/8 ohms. Cabinet 9 1/4 x 14 x 8 3/4 in. These most attractive units are available in oiled teak and are small enough to blend in with most surroundings.



LIST PRICE NORMALLY £36 PAIR

**OUR PRICE £33 PAIR** Post 15/-

## MIDLAND 10-502 VHF AIRCRAFT BAND CONVERTER

An entirely new item for the radio enthusiast bringing instant reception of the ground-to-air, air-to-ground waveband. For use with any standard AM or FM radio covering 535 to 1605 Kc/s. 88 to 108Mc/s respectively—with no electrical conversion or connection required. The Model 10-502 self powered by one 9V (PP3 type) battery is merely placed close to the receiving set and then tuned over 110 to 135Mc/s which covers the whole aircraft communications band. Volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the vol. controls of each accordingly. The Model 10-502 has a smartly designed black plastic cabinet with brushed metal front panel and 16 in. chrome telescopic antenna, size only 4 x 2 1/2 x 2 1/2 in. (inc. knobs). Complete with battery and full instructions.



**LASKY'S PRICE 72/6** Post 2/6

# Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2

Tel 01 723 3271

High Fidelity Audio Centres

33 TOTTENHAM CT. RD., LONDON, W.1

Tel 01 636 2605

42-45 TOTTENHAM CT. RD., LONDON, W.1

Tel 01 580 2573

Open all day, 9 a.m.—6 p.m. Monday to Saturday

Open all day, 9 a.m.—6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4

Tel 01 353 5812

118 EDGWARE ROAD, LONDON, W.2

Tel 01 723 9789

152/3 FLEET STREET, LONDON, E.C.4

Tel 01 353 2833

Open all day Saturday, early closing 1 p.m. Thursday

Open all day Thursday, early closing 1 p.m. Saturday

Open all day Saturday, early closing 1 p.m. Thursday


ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1



Tel.: 01-790 4821



# peak sound englefield

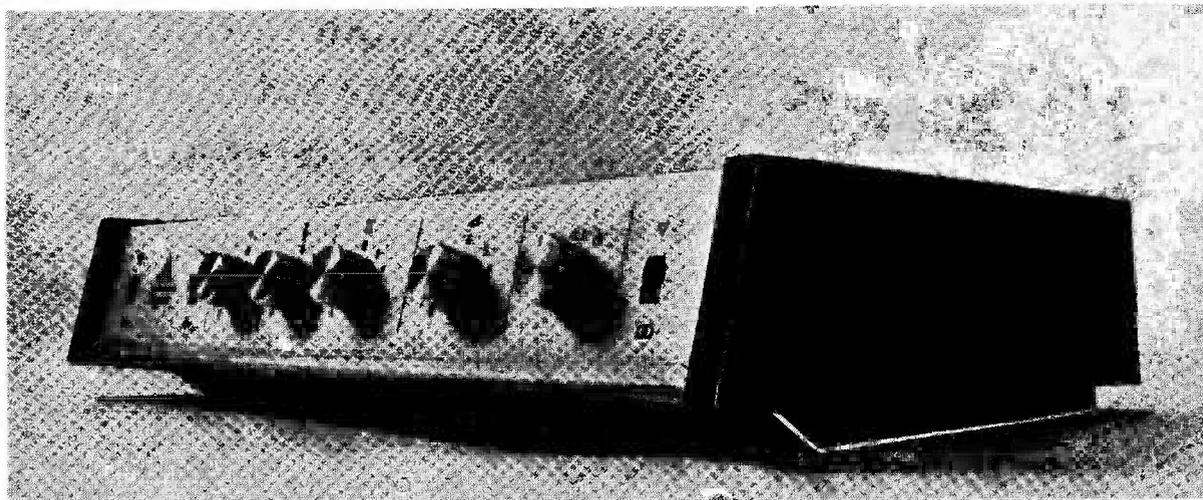

developed out of the highly successful PW. 12+12 and now in complete kit form to save you still more

The Peak Sound Englefield is a system offering great flexibility whilst providing cost-performance ratios which have never been bettered in high fidelity. Here top-flight circuitry is housed in a cabinet of elegantly original styling which is both beautiful and completely practical front and back. Now we carry design standards further by offering a 12+12 watt version completely in kit form. The resultant specification surpasses that even of the original PW.12+12 which again was based on Peak Sound design. In this Englefield kit, printed circuit boards are supplied for you to mount the components on. Standards of input sensitivity and overload factor on all channels as well as filter performance are all improved. By giving you the satisfaction of building the Englefield this way, you save considerably and finish with a completely professionally styled instrument. Go to your dealer and start building now, or send direct for delivery by return in case of difficulty.

### and this is the Peak Sound Specification Guarantee

Peak Sound guarantee that their equipment meets all specifications as published by them and that these are written in the same terms as used in equipment reviews appearing in this and other leading British hi-fi journals. Audio output powers are quoted at continuous sine wave power in terms of Root Mean Square values (R.M.S.) into stated loads at stated frequencies.

### The specification that tells you everything (See guarantee)

Using two Peak Sound PA. 12-15's, driven simultaneously at 1 KHz from 240-V. mains supply.  
 Output per channel: 11 watts into 15Ω; 14 watts into 8Ω.  
 Frequency bandwidth: 10Hz to 45 KHz for 1dB at 1 watt.  
 Total Harmonic Distortion at 1 KHz at 10 watt into 15Ω—0.1%.  
 Input sensitivities: Mag. PU.3.5 mV. R.I.A.A. equalized into 68KΩ; Tape, 100mV linear into 100KΩ; Radio, 100mV linear into 100KΩ.  
 Overload factor: 29dB on all input channels.  
 Signal/noise ratio: —65dB on all inputs.  
 Vol. control at max.  
 Controls: Volume, Treble, Bass, Low-pass Filter, Mono/Stereo: On/off; Balance.  
 Complete kit of parts including cabinet assembly, knobs, transistors, well-prepared instructions and wire to length, colour coded and stripped at ends as well as built-in mains power supply. (Post free in U.K.)

£33.2.0

Englefield assembly as above, but in easy-to-put-together modules. (Post free in U.K.)

£38.9.0

Peak Sound ES.10-15 BAXANDALL LOUD-SPEAKER. Fantastic performance and value. Ideal with your Englefield. Cabinet 18"x12"x10" natural teak finish. Ready built—18½ gns. Parts available separately for building yourself with appreciable saving. Leaflet on request.

## peak sound

PEAK SOUND (HARROW) LTD., SAINT JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY. Egham 5316

To Peak Sound, Saint Judes Road, Englefield Green, Egham, Surrey  
 Details of Englefield systems, please and.....  
 Name .....  
 Address .....  
 PW4  
 Write your stockist's name and address in margin below and cut out with coupon if necessary

**CAR LIGHT FLASHERS**



Heavy duty light flasher employs a condenser discharge principle operating on electro mechanical relay. (As inset). Housed in strong plastic case. Flashing rate between 60-120 per minute. 12V DC operation. Maximum load 6 amps. Size 2-11/16in. dia. x 4in. Supplied brand new at a fraction of original cost. 6/6 each P. 2/6. (\$ for 17/6 P. F. 4/6).

**CLASS D WAVEMETERS**



A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. Attractive 7/6. Or brand new with accessories. £7.19.8. Carr. 7/6.

**CLASS D WAVEMETERS NO. 2**

Crystal controlled. 1.2-19 Mc/s. Mains or 12V. D.C. operation. Complete with calibration charts. Excellent condition. £12.10.0. Carr. 30/-.

**R209 MK II**

**COMMUNICATION RECEIVER**  
11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O., aerial trimmer, internal speaker and 15v. D.C. internal power supply. Supplied in excellent condition fully tested and checked £15.0.0. Carr. 20/-

**TYPE 13A DOUBLE BEAM OSCILLOSCOPES**




An excellent general purpose D/B oscilloscope. T.B. 3 K/s. Bandwidth 5-6 Mc/s. Sensitivity 38mV/C.M. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.



**MARCONI T/44/TF956 AP Absorption Wattmeter**  
1 μwatt to 6 watts. £20. Carr. 10/-.

**GEARED MAINS MOTORS**

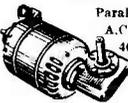


Paralux type 8D19 230/250V. A.C. Reversible. .30 r.p.m. 40 lb./ins. Complete with capacitor. Excellent condition. 99/6. Carr. 10/-.

**TO-3 PORTABLE OSCILLOSCOPE**



3in. tube. Y amp. Sensitivity 0.1v p-p/C.M. Bandwidth 1.5 cps-15 MHz. Input imp. 2 meg Ω 25pF. X amp. sensitivity 0.9v p-p/C.M. Bandwidth 1.5 cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale 140 x 216 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. £37.18.8 Carr. 10/-.

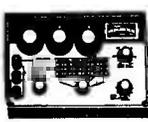**TRANSORISED L.C.R. A.C. MEASURING BRIDGE**



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 10-11.1 meg Ω 6 Ranges ±1%. L. 11.1 HENRY'S 6 Ranges -2%. C. 10pF ±1110mF. 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 6 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 1/2 in. £20. P. & P. 5/-.

**UNR-30 4-BAND COMMUNICATION RECEIVER**

Covering 550 Kc/s-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6. **13 gns.**





**TRIO JR-310 New Amateur Band 10-80 Metre Receiver in stock. £77.10.0.**



**LAFAYETTE SOLID STATE HA800 RECEIVER**  
5 BAND AM/OW/SSB AMATEUR AND SHORT WAVE 150 Kc/s-400 Kc/s and 550 Kc/s-30 Mc/s B.F.T front end & 2 mechanical filters. Heterodyne dial. Product detector. Variable BFO. Noise limiter. 8 meter. 24in Bandspread. 230V. A.C./18V. D.C. neg. earth operation. RF gain control. Size 15in. x 9 1/2in. x 8 1/2in. Weight 18 lb. EXCEPTIONAL VALUE. \$45. Carr. 10/-, S.A.E. for full details.

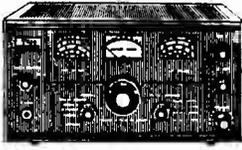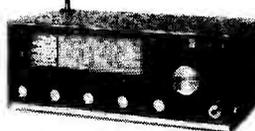**UR-1A SOLID STATE COMMUNICATION RECEIVER**

4 bands covering 550 Kc/s-30 Mc/s continuous. Special features are use of FET transistors. 5 meter. built in speaker and telescopic aerial. variable BFO for SSB reception. noise limiter. bandspread control. sensitivity control. Output for low impedance headphones. Operation 220/240 volt A.C. or 12 volt D.C. Size 12 1/2in x 4 1/2in x 7in. Excellent value. ONLY £24 carr. 7/6.



**TRIO COMMUNICATION RECEIVER MODEL 9R-59DE**  
4 band receiver covering 550 Kc/s to 30 Mc/s continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit, 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. IF 455 Kc/s. Audio output 1.5 W. Variable RF and AF gain controls. 115/200V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. £42. carriage paid. **TRIO COMMUNICATION TYPE HEADPHONES.** Normally £5.19.6. OUR PRICE £3.15.0 if purchased with above receiver.

**TRIO JR. 500SE 10-80 Metre Receiver £69.10.0**

**TRIO TS 510 AMATEUR TRANS-CEIVER with speaker and mains P.S.U. £218. IN STOCK!**




**RCA COMMUNICATIONS RECEIVERS AR88D**  
Latest release by ministry BRAND NEW in original cases. 110-250V. A.C. operation. Frequency in 6 Bands. 555 Kc/s-32 Mc/s continuous. Output impedance 2-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price £27.10.0. Carr. £2.

**LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER**

A completely new transistorised receiver covering 152-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. £27.10.0. Carr. 10/-.



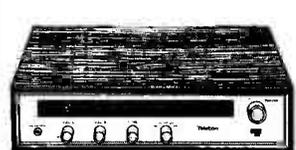**TELETON CR-10T AM/FM STEREO TUNER AMPLIFIER**



A new model from Telenon. 31 solid state devices. 4+4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600KHz FM 88-108MHz. Automatic FM Stereo reception. Stereo Indicator. Controls: Tuning, function selector, Tone and R & L volume controls. AFC switch. Stereo headphone socket. Size 13 1/2 x 3 1/2 x 9 1/2 approx. PRICE £34.0.0. Carr. 7/6.

**CLEAR PLASTIC PANEL METERS**

First grade quality Moving Coil panel meters. Type MR 38P. 1 1/2in. square fronts.

500-0-500μA	£27/6	50mA	£27/6	150V. D.C.	£27/6
1mA	£27/6	100mA	£27/6	300V. D.C.	£27/6
1-0-1mA	£27/6	100mA	£27/6	500V. D.C.	£27/6
2mA	£27/6	200mA	£27/6	750V. D.C.	£27/6
5mA	£27/6	300mA	£27/6	15V. A.C.	£27/6
10mA	£27/6	500mA	£27/6	150V. A.C.	£27/6
50-0-50μA	£27/6	750mA	£27/6	3V. D.C.	£27/6
100-0-100μA	£27/6	1 amp	£27/6	10V. D.C.	£27/6
200μA	£25/-	5 amp	£27/6	20V. D.C.	£27/6
500μA	£40/-	20mA	£27/6	100V. D.C.	£27/6

FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET

**Variable Voltage Transformers**

Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 50-60 cycles. Output full variable from 0-250 volts. Bulk quantities available. 1 amp. -£13.0.0; 2 1/2 amp. -£15.0.0; 5 amp. -£18.0.0; 8 amp. -£14.10.0; 10 amp. -£18.10.0; 12 amp. -£21.0.0; 20 amp. -£27.0.0.

**CRYSTAL CALIBRATORS NO. 10**



Small portable crystal controlled wavemeter. Size 7 x 7 1/4 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V. D.C. 0.3A. Excellent condition. 99/6. Carr. 7/6.

**TE-40 HIGH SENSITIVITY A.C. VOLTMETER**

10 meg. input 10 ranges: .01-1/003-1/1-3/15/10/30/100/300V. R.N.S. 4cps. 1-2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.10.0. Carr. 5/-.



**LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS**

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/250V. A.C. Supplied in perfect order. £12.10.0. Carr. 10/-.

**TE-65 VALVE VOLTMETER**



High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17.10.0. P. & P. 6/-. Additional probes available: R.F. 35/-; H.V. 42/6.

**COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES**

D.C. coupled. Band width 1Kc/s. Perfect order. £25. Carr. 30/-.

**AM/FM SIGNAL GENERATORS**

Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmeec. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt. A.C. Size 12 x 8 1/2 x 4in. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. 20/-.

**EDDYSTONE VHF RECEIVERS Model 770R. 19-165 Mc/s. Excellent condition. £150.**

**PLESSEY SL-423A 3 watt Integrated Amplifier Circuit 40/6 Post Paid.**



**TE-16A Transistorised Signal Generator.** 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. £7.19.6. P. & P. 4/-.


**HOSIDEN DH-08S DE-LUXE STEREO HEADPHONES**



Features unique mechanical 2 way units and fitted adjustable level control. 8 ohm impedance. 30-20,000cps. Complete with spring lead & stereo jack plug. £7.19.6 P. & P. 2/6

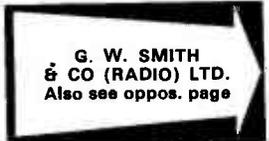**AUTO TRANSFORMERS**

0/115/230V. Step up or step down. Fully shrouded. 150 W. £2. 8.6. P. & P. 3/6. 300 W. £2.19.6. P. & P. 4/6. 500 W. £4.10.0. P. & P. 6/6. 1,000 W. £6.10.0. P. & P. 7/6. 1,500 W. £7.19.6. P. & P. 8/6. 7,500 W. £15.10.0. P. & P. 20/-.



**G. W. SMITH & CO (RADIO) LTD. Also see oppo. page**

**ARF-100 COMBINED AF-RD SIGNAL GENERATOR**



**A.F. SINE WAVE**  
20-200,000 c/s.  
Square wave 20-80,000 c/s. O/P. **HIGH IMP.** 21V.  
P/P 800Ω 3.5V. P/P. **T.F. 100 Kc/s-300 Mc/s.** Variable R.F. attenuation int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V. A.C. £32.10.0. Carr. 7/6.

**TE-20D RF SIGNAL GENERATOR**



Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator. audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 7/6. Size 140 x 215 x 170 mm.

**PEAK-SOUND PRODUCTS.** Full range of Amplifiers, Kits, Speakers in stock.

**TV75 AUDIO SIGNAL GENERATOR**

Sine Wave 20c/s to 200 kc/s. Square Wave 20c/s to 30kc/s. High and low impedance output. Output variable up to 6 volts. 220/240 volts A.C. Size 210 x 150 x 120 mm. Brand new with instructions. £18. Carr. 7/6.



**MARCONI TFI45E DISTORTION FACTOR METERS.** Excellent condition. Fully tested. £20. Carr. 15/-.

**LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER**

2 pF-2000 mF. 2 ohms 200 meg. ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New. £17.10.0 Carr. 7/6.



**MODEL ZQM TRANSISTOR CHECKER**

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec.: A: 0.7-0.9967. B: 5-200. Test 100 microamps 0-5mA. Resistance for diode 200Ω-1MΩ. Supplied complete with instructions, battery and lead. £5.19.6. P. & P. 2/6



**ADVANCE TEST EQUIPMENT**

Brand new and boxed in original sealed cartons

**J1B. AUDIO SIGNAL GENERATOR.** 15 c/s to 50 Kc/s. Sine wave. Output 600 ohms of 5 ohms. £30.0.0.  
**VM79. UHF MILLIVOLT METER.** 100 Kc/s to 1,000 Mc/s. A.C. 10 mV to 3v. D.C. 10 mV to 3v. Current 0.01 uA to 0.3 mA. Resistance 1 ohm to 10 megohm. £125.0.0.


**TT15. TRANSISTOR TESTER.** Full range of facilities for testing PNP or NPN transistors in or out of circuit. £37.10.0. Carriage 10/- per item.

**HOSIDEN DHO4S 2-WAY STEREO HEADSETS**



Each headphone contains a 2 1/2 in. woofer and a 1 in. tweeter. Built in individual level controls. 8Ω imp. 25-18,000c/s with cable and stereo plug. £5.19.6. P. & P. 2/6.

**AVOMETER MOVEMENTS**

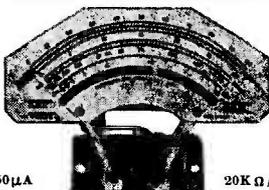

50μA 20KΩ/V

Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multimeter. Brand New & Boxed. 59/6. P. & P. 3/6.

The latest edition shows full details of a comprehensive range of H.F. COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. ... **SEND NOW - ONLY 7/6**

**GARRARD**

FULL CURRENT RANGE OFFERED BRAND NEW AT FANTASTIC SAVINGS

2025 stereo	£7.19.6	AP75	£16.19.6	SL55 with Sonotone	
2025T/C stereo	£8.17.6	SL75	£23.19.6	9TAMCD	£12.10.0
3000 stereo	£9.19.6	SL75B	£29.9.0		
SP25 Mk II	£11.9.6	SL95B	£35.9.0		
SL35	£11.12.6	A70/11	£11.19.6		
SL65B	£14.19.6	401	£26.10.0		

Carriage 7/6 extra each item.

**TEAK PLINTHS & PERSPEX COVERS**

- For SP25, SL65, SL55, 3000, 2025 T/C 2025, 1000. £4.10.0
- For AP75, SL75, SL95 £7. 9.6.
- For SP25 etc. to operate with lid in place £6.19.6. Carriage 7/6 extra each type. Full range of Garrard accessories available.



**LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER**

19 transistors, 8 diodes, 18W music power, 30W at 8Ω. Response 30-20,000 ± 2dB at 1W. Distortion 1% or less. Inputs 5mV and 250mV. Output 2-16Ω. Separate L and R volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complementary metal case. Size 10 1/2 x 3 9/16 x 7 13/16 in. Operation 115/230V. A.C. £24. Carriage 7/6.

**MULTIMETERS for EVERY purpose!**

**TE-51. NEW 20,000Ω/VOLT MULTIMETER** with overload protection and mirror scale. 0.6/30/120/1,200V. A.C. 0.9/30/60/300/600/3,000V. D.C. 0-60μA/12/300mA. D.C. 0/60K/6 meg. ohm. 92/6. P. & P. 2/6.

**MODEL AS-100D. 100K Ω/VOLT.** 5in. mirror scale. Built-in meter protection. 0.3/12/60/120/300/600/1,200V DC 0.1/6/30/120/300/600V AC. 0.10/10μA/6/60/300 mA/12 amp. 0.2K/200K/2M/200MΩ. -20 to +17.6. £12.10.0. P. & P. 3/6.

**MODEL TE-90 50,000 OPV** mirror scale overload protection. 0.3/12/60/300/600/1200 v. D.C. 0.6/30/120/300/1200V. D.C. 0.3/6/60/600mA. D.C. 16K/160K/1.6/16meg Ω. -20 to +63dB. £7.10.0. P. & P. 3/-.

**MODEL TE-70. 30,000 OPV.** 0.3/15/60/300/600/1200V DC. 0.6/30/120/300/600/1200V. A.C. 0.10/10μA/6/60/300mA/12amp/160K/1.6/16Meg. Ω. £5.10.0. P. & P. 3/-.

**MODEL FT-84.** 1,000 OPV. 0.10/150/250/500/1,000V AC and DC. 0.1/100/500mA DC. 0.100K Ω. 59/6. P. & P. 1/6.

**TE-800 20,000Ω/VOLT GIANT MULTIMETER** mirror scale and overload protection. 6in. full view meter. 3 colour scale. 0.2/8/10/250/1,000/5,000 v. A.C. 0.25/12.5/10.50/250/1,000/5,000V. D.C. 0.5/0.5μA/1/10/100/500 mA/10 amp. D.C. 0.2K/200K/20 MEG. OHM. £15. P. & P. 5/-.

**MODEL TE-10A. 20kΩ/VOLT** 5/25/50/250/500/2,500V. D.C. 10/50/100/500/1,000 v. A.C. 0.750μA/2.5mA/250mA. D.C. 0.6K/6 meg. ohm. -20 to +22dB. 10-0, 100mFd. 0-100-0-1mFd. 69/6. P. & P. 2/6.

**LAFAYETTE 57 Range Super 50KΩ/Volt Multi-meter.** D.C. volts 12 mV -1000V. A.C. volts 1.5V -1000V. D.C. current 25μA-10 amp. Ohms 0-10 meg Ω -20 to +81 dB. Overload protection. £12.10.0. Carr. 3/6.

**MODEL TE-80. 20,000 O.P.V.** 0.10/50/100/500/1,000V A.C. 0.8/25/50/250/500/1,000V D.C. 0-50μA. 0.5/500mA. 0.6K/60K/600K/6meg. £4.17.6. P. & P. 3/-.

**MODEL TE-12** 20,000 O.P.V. 0.10-6/30/120/600/1,200/3,000/6,000V. D.C. 0.6/30/120/600/1,200V. A.C. 0.8/60μA/6/60/600mA. 0.6K/600K/6meg/60 Meg. Ω. 50P.F. 0.2mFd. £5.19.6. P. & P. 3/6.

★ **TRANSISTORISED FM TUNER** ★

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £4.7.6. P. & P. 2/6. Stereo multiplex adaptors 99/6.



**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £8.19.6. P. & P. 3/6.




**SINCLAIR EQUIPMENT**

Project 60 range of new models now in stock. 230 Amplifier 99/6. STEREO 60 Control Unit £9.19.6. P25 Power Supply £4.19.6. P26 Power Supply £7.19.6. O16 Speakers £2.19.6. All Post Paid.

**SPECIAL PACKAGE OFFER!**  
2x 230 Amplifiers. Stereo 60 and P25 Power Supply. £19 Carr. 7/6 or with 2x O16 Speakers. £35 Carr. 7/6.  
Micromatic Radio Kit 49/6  
Micromatic Radio Built 59/6  
SINCLAIR IC/10 IN STOCK 59/6  
2000 Amplifier £23.10.0 Carr. 7/6  
Neoteric Amplifier £42.10.0 Carr. 7/6


**ECHO HS-606 STEREO HEADPHONES**

Wonderfully comfortable. Light-weight adjustable vinyl headband. 6ft. cable and stereo jack plug. 25-8,000 c/s. 6 ohm imp. 67/6. P. & P. 2/6.

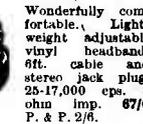

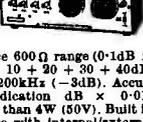**TE111. DECADE RESISTANCE ATTENUATOR**

Variable range 0-111dB Connections. Unbalanced T and Bridge T. Impedance 600Ω range (0-1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.06dB. - Indication dB x 0.01. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 0/-.



**RECORDING HEADS**

**GOSWORTHY** 4-track heads. High imp. record/playback 65/- Low imp. erase 80/-.  
**MARRIOTT** 4-track heads. High imp. record/playback 65/- Low imp. erase 80/-.  
Post extra.

**AMERICAN TAPE**

First grade quality American tapes. Brand new. Discount on quantities.  
3in. 255ft. L.P. acetate ..... 8/6  
3 1/2 in. 600ft. T.P. mylar ..... 15/-  
3 1/2 in. 600ft. std. plastic ..... 8/6  
5in. 900ft. L.P. acetate ..... 10/-  
5in. 1,200ft. D.P. mylar ..... 15/-  
5 1/2 in. 1,200ft. L.P. acetate ..... 13/6  
6 1/2 in. 1,200ft. L.P. mylar ..... 15/-  
6 1/2 in. 1,800ft. D.P. mylar ..... 22/6  
6 1/2 in. 2,400ft. T.P. mylar ..... 39/6  
7in. 1,200ft. std. acetate ..... 12/6  
7in. 1,800ft. L.P. acetate ..... 15/-  
7in. 1,800ft. L.P. mylar ..... 20/-  
7in. 2,400ft. D.P. mylar ..... 25/-  
7 1/2 in. 3,600ft. T.P. mylar ..... 45/-  
Postage 2/- Over £3 post paid.

**TAPE CASSETTES**


Top quality in plastic library boxes.  
C60 60 min 8/6. 3 for 24/-  
C90 90 min 12/6. 3 for 36/-  
C120 120 min 15/6. 3 for 43/-  
Cassette Head Cleaner 11/3. Post Extra.

**G.W.SMITH & CO. (RADIO) LTD**

All Mail Orders to -  
147, Church Street, London, W.2  
Tel: 01-262 6562  
(Trade supplied)  
3, LISE STREET, LONDON, W.C.2 Tel: 01-437 8204  
31, LISE STREET, LONDON, W.C.2 Tel: 01-437 9155  
131, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)
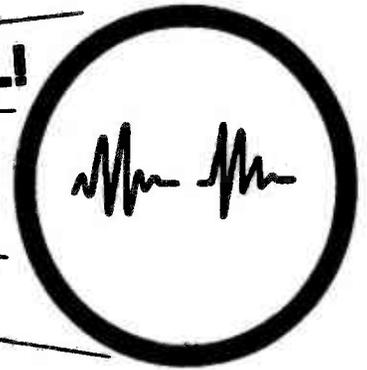
# LOOK!

**PRACTICAL!**  
**VISUAL!**  
**EXCITING!**




*a new 4-way method of mastering*  
**ELECTRONICS**  
*by doing — and — seeing . . .*

**1**

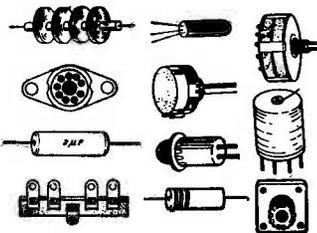**OWN and HANDLE a**


complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



**2**

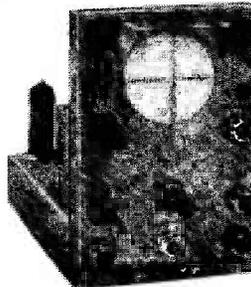**BUILD and USE**


a modern and professional **CATHODE RAY OSCILLOSCOPE**



**3**

**READ and DRAW and**

**UNDERSTAND CIRCUIT DIAGRAMS**

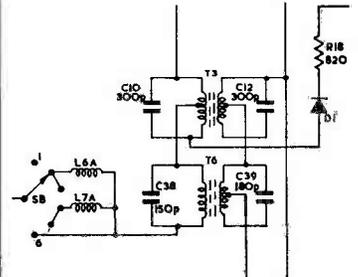

**4**

**CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
  - TRANSISTOR EXPERIMENTS
  - AMPLIFIERS
  - OSCILLATORS
  - SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
  - COMPUTER CIRCUIT
  - BASIC RADIO RECEIVER
  - ELECTRONIC SWITCH
  - SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
  - D.C. EXPERIMENTS
  - SIMPLE COUNTER
  - TIME DELAY CIRCUIT
  - SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW1

# PRACTICAL WIRELESS

VOL 45 NO 12

Issue 758

APRIL 1970

## TOPIC OF THE MONTH

### Behind the times

**W**HAT on earth are the BBC and the Government up to? Having decided to open twenty local radio stations by the Autumn and twenty more within the next few years, and having found accommodation for them in Band II, the Minister of Posts and Telecommunications decides that these stations will also operate partly on m.w.

A government decision in the face of BBC opposition? Certainly not, for Ian Trethowen, managing director of BBC Radio, "warmly welcomes" the Minister's decision. The justification for using m.w. channels is said to be the shortage of suitable car radios and lack of v.h.f. portables. This is largely nonsense, although our set makers have been somewhat tardy in producing v.h.f. car radios.

But who can blame them for this, when the BBC still clings pathetically to a.m. For if the BBC is not seen to be convinced that v.h.f.-f.m. radio is the medium of today then how can set makers and the general public be swayed?

The BBC has been bold enough to set a target for the phasing out of 405-line v.h.f. television and this, of course, has given the industry and the public clear guide lines. What we need is a similar declaration on the future of sound broadcasting. As it is, the grandiose BBC plan of "Broadcasting in the Seventies" could be construed as meaning the *Eighteen Seventies!* Not to labour the point, our sound broadcasting is twenty years or so behind the times. Whereas, after the war, Europe and the USA in particular, put their faith in v.h.f.-f.m. we have largely dragged our heels, seemingly reluctant to take the final decisive plunge.

The local stations will use a.m. only during daylight, so that the best those without v.h.f. receivers will have is half a service. This is futile and half baked! So much so, that one can be excused for suspecting ulterior motives. And the only one we can think of at the moment is that the BBC and/or the Government have agreed to establish squatters rights on the two m.w. channels to thwart pirate and/or commercial stations from setting up house.

Whatever the case, the decision to use m.w. part of the time is a negative one and not in the interests of the development of sound broadcasting in this country.

W. N. STEVENS—*Editor.*

**MAY ISSUE WILL BE PUBLISHED ON APRIL 3**

## NEWS AND COMMENT

Leader	931
News and Comment	932, 933
MW Column by <i>C. Molloy</i>	941
Practically Wireless by <i>Henry</i>	942
On the Short Waves by <i>Malcolm</i> <i>Connah and David Gibson,</i> <i>G3JDG</i>	945
Letters to the Editor	961

## CONSTRUCTIONAL

Transistor Minigenerator by <i>R. F. Graham</i>	934
I.C. of the Month, Sanken Audio Amplifiers by <i>L. A. J. Ireland</i>	938
FET's and their Uses, Part 2 by <i>T. Snowball</i>	949
Electronic Thermometer by <i>C. R. Bradley</i>	952
FET Preamp by <i>W. T. Morris,</i> <i>B.Sc., Ph.D.</i>	956
Audio Noise Limiter by <i>R. F. Graham</i>	960
Radioactivity Detector by <i>L. McNamara</i>	964
Take 20, Lie Detector by <i>Julian Anderson</i>	970
General Coverage Receiver, Part 2 by <i>F. G. Rayer, G3OGR</i>	973

## OTHER FEATURES

Repairing Transistor Radios, Part 2 by <i>V. Capel</i>	954
Sums plus Circuits equals Understanding by <i>Leslie Moore</i>	958
Medium Wave DXing by <i>Charles Molloy</i>	962
What do you know about Meter Shunts? by <i>H. A. Cole,</i> <i>C.Eng., M.I.E.R.E.</i>	966
P.W. Guide to Components, Part 16 by <i>M. K. Titman, B.Sc.</i>	981

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

# NEWS... NEWS... NEWS...

## Brema figures

Colour television deliveries to the Trade continued to rise during November (when three channel colour broadcasts officially began) according to the Economic and Statistical Division of the British Radio Equipment Manufacturers' Association. 28,000 colour sets were delivered, bringing the total for the period January-November to 129,000 sets.


On the other hand, for the sixth month running deliveries of monochrome sets fell below the comparable month for 1968—165,000 monochrome sets were delivered in November, 9% below November 1968 (181,000).

The slight recovery in deliveries of radiograms has continued and for the third month in a row deliveries for the month have improved on the same month for 1968—deliveries in November were 25,000 as against 24,000 in November 1968.

No end to the fall in deliveries of radios (67,000) and car radios (20,000) was experienced in November; for the period January to November the figures continue to be 28% and 15% respectively below 1968.

These estimates are net figures of deliveries by manufacturers to the home market on firm and other accounts including those to specialist rental and relay companies.

## A trio from Trio

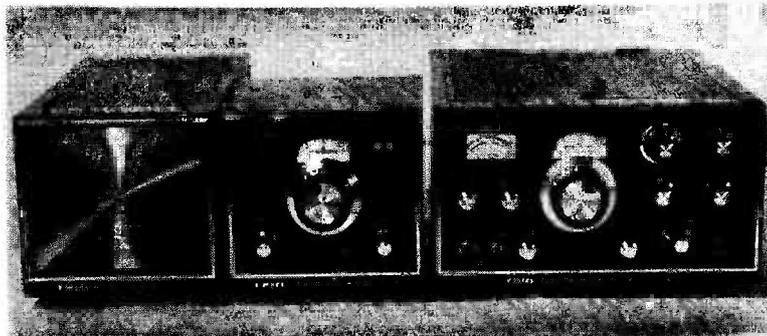

At the November 1969 R.S.G.B. Exhibition, Trio (B. H. Morris & Co. (Radio) Ltd.) introduced a new transceiver—the TS510 together with a companion v.f.o. and power supply/speaker unit.

The TS-510 Transceiver, on the right of the picture, employs a high-frequency crystal filter and covers all Ham bands from 3.5 to 29.7MHz. Both Rx and Tx sections employ the dual conversion configuration. The receiver is a dual-conversion superhet in which the r.f. and local oscillator are independently tuned. A selectivity switch is provided for s.s.b. and c.w. modes and the a.g.c. circuit features signal strength meter indication independent of r.f. gain adjustment. Type of emission is s.s.b. (A3J), c.w. (A1). Rated input: 160W at 3.5-21 MHz, 120W at 28MHz. The transceiver uses 14 valves, 2 f.e.t.s, 13 transistors and 29 diodes. Dimensions: 13 x 7 x 13½ in.

Stability is assured in the v.f.o. type 5D through the use of two f.e.t.s plus two other transistors. This unit is equipped with the same precision double-gear drive as the TS-510 transceiver which tunes a 25kHz range in one rev. Crystal controlled operation permits spot channel communication and built-in RIT circuit permits slight shifting of receive/transmit frequencies when desired. Frequency range on 80m is 3.5-4.1 MHz; 40m 7.0-7.6MHz; 20m 14.0-14.6MHz; 15m 21.0-21.6MHz; 10m (A) 28.0-28.6MHz; 10m (B) 28.5-29.1MHz; 10m (C) 29.1-29.7MHz.

The PS 510 power supply speaker unit measures 7½ x 9 x 12 in. approx. Further details may be obtained from B. H. Morris & Co. (Radio), 84-88 Nelson Street, London, E.1, or your nearest amateur radio equipment stockist.



The new President, Dr. Saxton

## The present and past

Dr. J. A. Saxton, DSc., PhD, CEng, FIEE, FInstP was installed as the 36th President of the Radio Society of Great Britain on January 16th.

Dr. Saxton, before, during and after the last war, was working on propagation studies and research in radio meteorology. He was appointed Deputy Director of the Radio Research Station in 1960 and in 1964 to 1966, he held the post of Deputy Director of the U.K. Scientific Mission and scientific counsellor at the British Embassy, Washington, U.S.A. Upon returning to the U.K., Dr. Saxton was appointed Director of the Radio & Space Research Station.



Immediate Past President, J.W. Swinnerton.

# NEWS... NEWS... NEWS...

## Oh to be in Finland

Christmas in Helsinki, Finland, was made a little livelier in 1969 due to the medium of TV. Finnish people were shocked when a pornographic film was shown over the air. Apparently the film was meant to be a closed-circuit test picture but it was put out on the air because a technician did not pull the right switch!

## Bromsgrove move

The Bromsgrove & District Amateur Radio Club, G3VGG, (Club Spot February) now meet at the Royal Oak pub, Catshill, Bromsgrove. Meetings are held the second Friday of the month at 8 p.m.

## Mobile radio systems

A conference on "Mobile Radio-communication Systems" is to be held from June 30th to July 2nd. The conference which is being organised by the Society of Electronic and Radio Technicians will be held at Brunel University, Uxbridge.

The conference will deal principally with vehicular and personal mobile systems. The increase of this field of communication, makes the subject of very wide interest not only to those already operating such systems but also to those contemplating such a step. The conference will cover all aspects of mobile radio-communication including propagation problems, system planning and design, statutory requirements and manufacturer and user experience.

This will primarily be a non-residential conference although hostel accommodation has been reserved for those delegates who are unable to travel to and from Uxbridge each day. The registration fee including lunch and refreshments each will be £7 7s. 0d. for members of the Society and £10 10s. 0d. to non-members.

Further information and registration forms may be obtained from: *The Conference Secretary, Society of Electronic and Radio Technicians, Faraday House, 8-10 Charing Cross Road, London, W.C.2.*

## Lasky's Hi-fi centre



Europe's biggest Hi-Fi and audio centre was officially opened in London recently. The Chairman of the company which operates the 5,000 sq. ft. store, Mr. Harry Lasky told over 150 electronics company guests from all over the world, "Our customers will have the choice of more than 10,000 items of equipment—that is the biggest selection outside the USA."

The centre in Tottenham Court Road, W.1. contains a demonstration studio where customers, with the aid of a custom-built comparator, can instantly compare the latest Hi-Fi installations exactly as they will sound in their own homes. Experts staff the new centre and they will plan a 'customised' system to suit the home and pocket of the prospective customer.

Mr. Lasky said, "Our new centre is designed to cater for the absolute beginner as well as the enthusiast with thousands of pounds to spend and it is an important landmark in the continuous process of introducing Hi-Fi to an ever-widening circle of the public."

The address of the new centre is: 42-45 Tottenham Court Road, London, W.1. Another Hi-Fi audio centre is at 118 Edgware Road, London, W.2. and the seven-branch group headquarters is 3-15 Cavell Street, London, E.1.

The photograph shows the Lasky demonstration studio which enables customers to make a balanced comparison of equipment.

## Motorola semiconductor data book


Motorola have just announced the availability in the U.K. of the fourth edition of 'The Semiconductor Data Book'. The price is £3 (plus 6s. postage) and it is available through the Modern Book Co., 19 Praed Street, London, W.2.

This latest edition has been enlarged (it now includes 2,160 pages) and the format has been redesigned to make it easier to retrieve data. Instead of a number of product categories, dis-

crete device specifications are presented in alphanumeric sequence in three major sections, namely: '1N' numbered devices, '2N' and '3N' numbered devices, and devices with Motorola house numbers. Also included is a 50-page section of selection guides which enable application needs to be directly related to semiconductor device numbers. Furthermore, the Data Book lists all EIA registered 1N, 2N and 3N devices along with their short-form specifications.

In all, more than 12,700 types are listed together with details of their characteristics.

# transistor

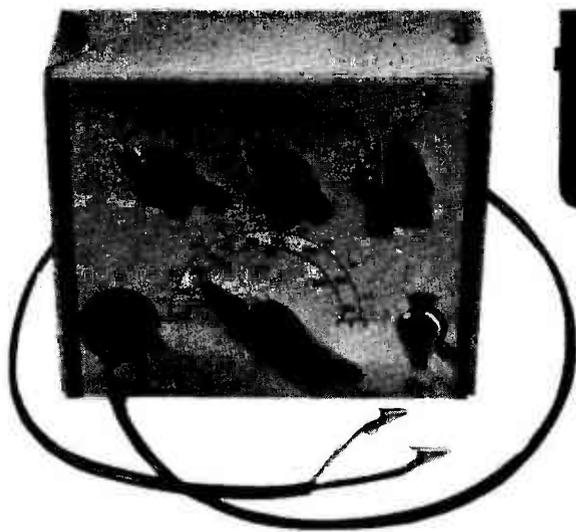

**A** SIGNAL generator is extremely useful for trimming, aligning and testing receivers, and testing amplifiers. The transistor signal generator described here is of small size, and has three tuned ranges:

- (1) 190-375kHz (approx. 1600-800 metres).
- (2) 375-1000kHz (approx. 800-300 metres).
- (3) 1.1-2.8MHz (approx. 275-105 metres).

These frequencies are available as c.w., or modulated with an audio tone. In addition, the audio tone is available, for amplifier and audio circuit checks. The ranges cover 470kHz, 1.6MHz and similar intermediate frequencies, as well as medium and long waves, while harmonics can be used for higher frequencies.

## Circuit Details

Figure 1 is the circuit, Tr1 being the audio oscillator, with feedback from primary to secondary of the transformer T1. Tr2/Tr3 are in the r.f. oscillator circuit, tuned by VC1. S3/S4 is a 2-pole switch, selecting coils L1, L2 or L3, for the required band.

S1/S2 is a further 2-pole switch. When S1 is at "C.W." the base of Tr1 is shorted to the positive line, cutting off Tr1. Tr2/Tr3 then provide an unmodulated r.f. signal, via C7, S2, and R9. With S1/S2 in the "Mod" position, Tr1 oscillates at audio frequency, and modulates Tr2/Tr3 due to the a.f. impedance of C2/R10. This gives an audible r.f. signal. With S1/S2 at "A.F." Tr2 base is shorted and moved positive, while a.f. from C4 is taken by S2 to R9. In all cases VR1 is an attenuator, and C8 gives d.c. isolation of external circuits.

Each kind of output signal—c.w., modulated, or a.f.—has its own particular uses, described later.

The coils L1, L2 and L3 are of fixed inductance, and manufactured to a high degree of accuracy. So provided VC1 is the capacitor listed, band coverage and calibration can be expected to agree well with that given. If wished, individual calibration can be made in the way described.

## Panel and Case

The completed generator is  $5 \times 6 \times 2$  in. and the case is made from "universal chassis" members. The box has a  $5 \times 6$  in. front, and sides  $5 \times 2$  in., top and bottom being  $6 \times 2$  in.

Sides, top and bottom are flanged, so they can be fitted later. This allows all construction and wiring to be done with the front and bottom only fitted together as in Fig. 2. Holes should be punched in

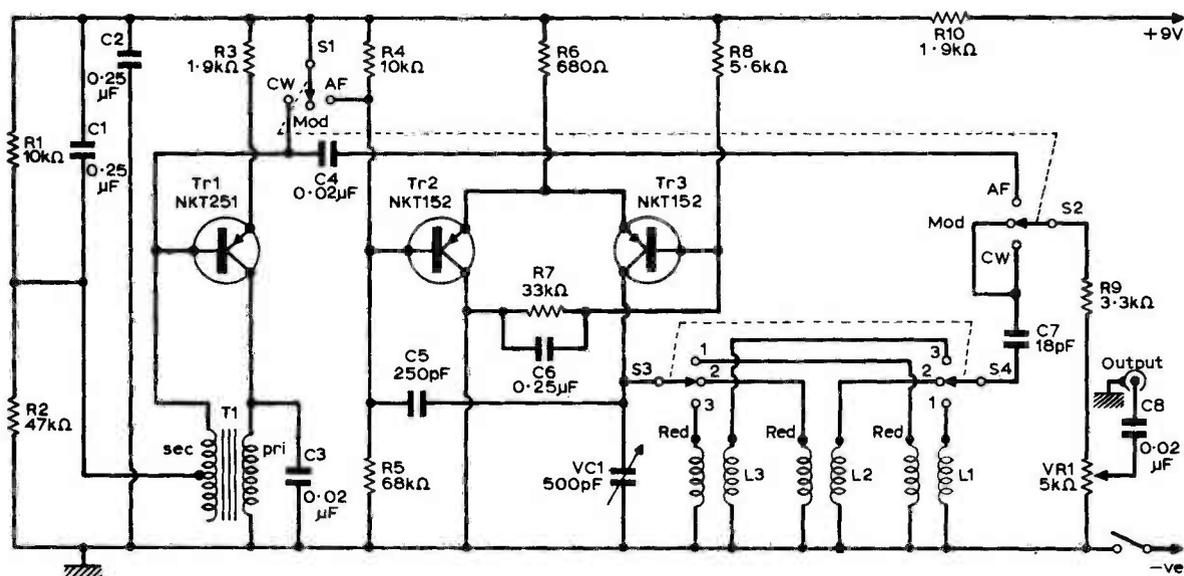


Fig. 1: Complete circuit of minigenerator

# mini generator

R. F. GRAHAM

the front for VC1, the switches, output socket, and VR1. VC1 is bolted to the bottom runner, which is then fixed to the panel. A countersunk bolt with extra nuts is passed through the panel and a hole in the top corner of the frame of VC1, the tag MC being locked here.

L1, L2 and L3 are held with countersunk bolts, through the panel and base into the mounting strips. The socket for C8 provides an output insulated from the metal.

The items in Fig. 2 are wired as shown, with sleeving on all leads. Note that the circuit has a negative earth (metal box), not positive as in much transistor equipment.


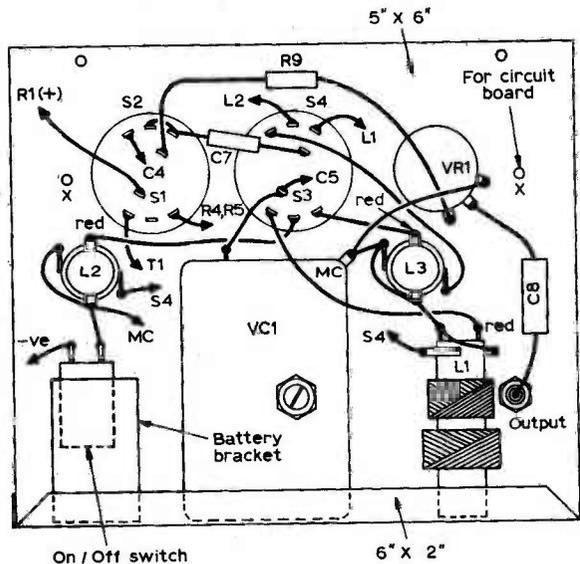


Fig. 2: Major component layout and wiring

The other components are assembled on a paxolin panel  $5 \times 1\frac{1}{2}$  in., as in Fig. 3. The holes X-X of the circuit board match holes X-X in the metal panel, Fig. 2. Countersunk bolts pass through the panel, and are locked here. Extra nuts are put on the bolts, and the finished circuit board can then be put into place, and held with further nuts, resting behind VR1 and the rotary switches.

The transformer is a driver type for OC81D/2xOC81, and if a different transformer is fitted, it may be necessary to reverse connections to one winding, to obtain audio oscillation.

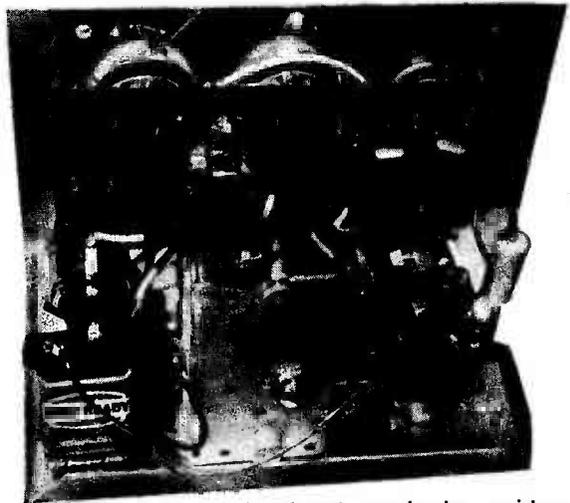Wiring of the circuit board should be quite straightforward. Take thin red flex from R10, for the battery positive connection. Leave flying leads from the points shown, for S1, S2, etc.



The circuit board is placed nearly in position, and the leads cut and soldered to S1, S2 and S3. The MC or negative connection is to the tag at VC1, and metal cabinet. The board can then be pushed right on the bolts, and held with nuts, leaving a little space between it and the tags of the switches.

## Case

The generator can be tested before finishing the case, by setting the switch to "Mod" and swinging VC1 on Range 2, when an audio tone should be heard in a nearby receiver on medium waves.

Elastic holds a PP3 9V battery to a bracket behind the on/off switch. Current drain is about 2-3mA at "Mod" with about  $4\frac{1}{2}$ V working voltage due to drop in R10. The back is held in position with self-tapping screws.

## Calibration

By fitting the specified coils and tuning capacitor VC1, coverage about as listed can be expected. The pointer knob is fully clockwise with VC1 closed, so goes a little beyond the mark at the other end of the scales.

## CALIBRATION POINTS

Range 1	°	Range 2	°	Range 3	°
180 kHz	179	375 kHz	169	1.1 MHz	166
200 "	147	400 "	149½	1.2 "	143½
250 "	95	450 "	123	1.3 "	127
300 "	58	500 "	99	1.4 "	112
350 "	27½	550 "	82	1.5 "	98
375 "	14½	600 "	68	1.6 "	87
		700 "	56½	1.7 "	76½
		800 "	42	1.8 "	67½
		900 "	24	2.0 "	51
		1000 "	3	2.5 "	30
				2.8 "	13

The frequency markings are copied on the card, before finally adding the perspex, and knobs. If the scales are to be individually calibrated, first put frequency markings directly against the pointer position, then add the perspex later.

For individual calibration of the scales, one of several methods can be used, according to the equipment available. The brief details following should be helpful.

**With Signal Generator.** If a calibrated generator can be borrowed, tune it to various frequencies, tune in the signal with a receiver, and adjust the Mini-generator tuning to the same frequency and mark its scale.

**With Calibrated Receiver.** If an accurately calibrated receiver is to hand, set this at various frequencies, tune the Minigenerator to the same frequencies, and mark its scales. This is the easiest and most accurate method when harmonic pips from a 100kHz crystal marker are available to give exact receiver tuning throughout.

**With Uncalibrated (or poorly calibrated) Receiver.** Tune in the BBC on 200kHz. Tune Minigenerator to same frequency, and mark 200kHz. Leave Mini-generator tuning untouched, and tune receiver to harmonic heard on 400kHz. Leave receiver tuning untouched, tune Minigenerator to 400kHz, and mark its scale. Repeat the procedure each time for 600kHz, 800kHz, 1,000kHz, etc., up to 1,400kHz for a MW receiver, and up to 2,800kHz (2.8MHz) for an all-wave receiver.

**Use of Harmonics.** Tune the receiver to a known high frequency, such as MSF, or 2,000kHz derived from the 200kHz BBC transmission as mentioned. Leave the receiver tuning, and tune the Mini-generator progressively towards lower frequencies. Harmonics will then be heard when a multiple falls on 2,000kHz (or other chosen frequency). As example, on 1,000kHz (x2), 500kHz (x4), 400kHz (x5), and so on. This allows calibration over 400-500kHz, for intermediate frequencies.

## ★ components list

### Resistors:

R1	10k $\Omega$	R6	680 $\Omega$
R2	47k $\Omega$	R7	33k $\Omega$
R3	1.9k $\Omega$	R8	5.6k $\Omega$
R4	10k $\Omega$	R9	3.3k $\Omega$
R5	68k $\Omega$	R10	1.9k $\Omega$

All resistors 10%  $\frac{1}{2}$  watt  
VR1 5k  $\Omega$  linear pot.

### Capacitors:

C1	0.25 $\mu$ F 150V
C2	0.25 $\mu$ F 150V
C3	0.02 $\mu$ F 150V
C4	0.02 $\mu$ F 150V
C5	250pF silver mica
C6	0.25 $\mu$ F 150V
C7	18pF silver mica
C8	0.02 $\mu$ F 350V

VC1 Jackson 500pF variable, Home Radio Cat. No. VC5.

### Semiconductors:

Tr1	NKT251
Tr2	NKT152
Tr3	NKT152

### Miscellaneous:

L1, L2, L3. C083A, C083G, C083F, Home Radio;  
5 x 6 x 2in. Universal chassis CU13, Home Radio;  
Two 2-pole 3-way rotary switches; On/off toggle switch; T1 Type RS.T/T6, Home Radio; KN9 type knob; PK4 insulated socket; PK3 plug; BTS33 perforated eyelet board, Home Radio; PP3 battery; sleeving; bolts; etc.

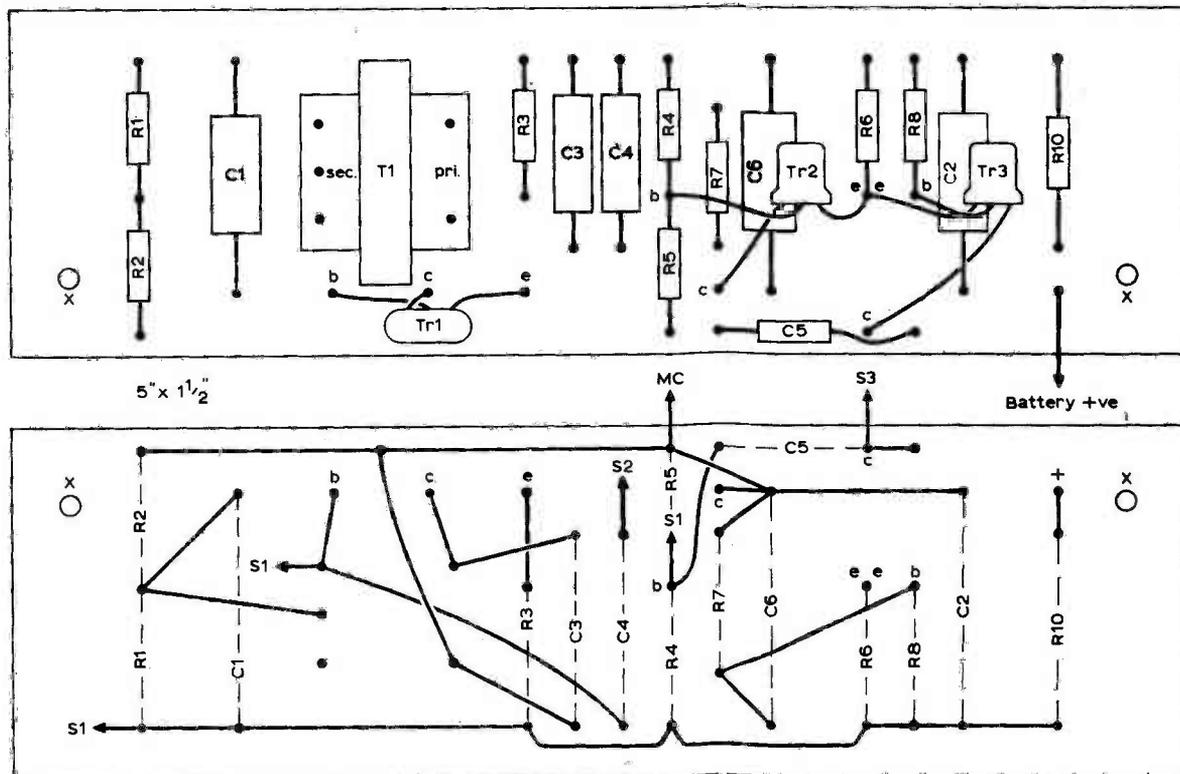


Fig. 3: Circuit board component layout and wiring

## Generator Output

The c.w. output resembles that of a transmitter during a silent interval in programmes. It will heterodyne with another c.w. signal (as from a crystal marker) or can be heard with a receiver having a b.f.o. It operates a tuning meter or indicator. It is used for critical alignment.

The modulated output has an audio tone accompanying the r.f., so can be tuned in with any receiver, and heard with the loudspeaker.

The a.f. output is used for audio circuit tests only, by injecting a.f. into various amplifier points, working backwards from the loudspeaker. When signals cease, the last coupling circuit or stage introduced is the one at fault.

## To Align I.F.T.'s

Set the generator to the wanted intermediate frequency. Should the i.f.t.'s be badly out of alignment, work backwards from the detector, dealing with them in turn. Then inject at the mixer base or signal grid, and check all i.f.t. cores. With all such work, keep signal strength well down. Output can be checked with a meter in one battery lead, with push-pull transistor receivers, or with an a.f. meter, or by watching the a.v.c. voltage.

## Checking Band Coverage

To adjust a receiver band coverage, set oscillator trimmers at the h.f. end of each band, and coil inductance at the l.f. band ends. In this way each band can be adjusted to have the wanted frequency range.

## R.F. Alignment

To adjust aerial or r.f. circuits for best results, deal with each band separately, in the manner described for the receiver. This usually requires that trimmers are set for best results near the h.f. end of a band, and coil inductances are adjusted near the l.f. end of each band.

## Coupling

Coupling from the signal generator to a receiver should always be very loose. With portables, a short lead can be plugged into the generator output socket, and placed near the receiver or its ferrite aerial. For other receivers, connect a short lead to the aerial socket, and place this near the generator output lead, or lightly twist the insulated wires together.

## Use of Harmonics

There are two main uses for the harmonic outputs of the signal generator. Such outputs are on multiples of the frequency to which the generator is tuned. For example, if the generator is tuned to 1MHz, a signal will be heard on 1MHz, 2MHz, 3MHz, 4MHz, and other multiples, the limit depending on receiver sensitivity. If the generator were tuned to 1MHz, a home-built receiver could thus be tuned from 1MHz upwards, and its scales marked to indicate 2MHz, 3MHz, etc. In this particular case, the 0.5MHz points could be found as harmonics of 0.5MHz, or 500kHz, if wanted.

Harmonics also allow exact calibration of small frequency bands. As example, if the generator is tuned to 200kHz, harmonics will appear on multiples of this. Those on 1,800kHz and 2,000kHz would set the limits of the 1.8-2.0MHz amateur band.

With a completely uncalibrated receiver, harmonics may if needed be identified by using the generator on two frequencies. As example, if all 1MHz points are marked, but not known, 5MHz can be identified by tuning the generator to 2.5MHz, as the 2nd harmonic falls on 5MHz. Or 6MHz could be identified from 2MHz on the generator (3rd harmonic), which would also give 4MHz as 2nd harmonic. When one frequency has been identified in a receiver tuning range, the remaining 1MHz points can be counted up and down from this.

## Audio Circuits

These are tested by injecting a.f. With some equipment, an earth return is required, from equipment chassis to generator case. The earth terminal allows this.

Tests should not be made on a.c./d.c. equipment having a live chassis.

Where little or no amplification is available, the full generator output will be wanted. But when tests bring into circuit one or more amplifier stages, output must be reduced with the generator potentiometer VR1, to avoid overloading the output or other stages in the receiver or amplifier. ■

# **PRACTICAL TELEVISION** *in the APRIL issue*

## **STROBE-TRIGGER TIMEBASE UNIT**

For detailed design work and TV experimentation strobe-trigger operation of the oscilloscope is necessary. This unit has been designed for use with the PTV Videoscope MV3. An output is available from the master multivibrator so that the unit can be used as a general-purpose squarewave signal generator.

## **REGULAR LONG-DISTANCE RECEPTION**

There are many areas where satisfactory signals can be obtained from more than one ITA or BBC transmitter, giving a worthwhile increase in the programmes available. The conditions necessary for reliable long-distance reception are examined, with an account of how to decide on its practicability in a given area.


## **EHT MULTIPLIERS**

EHT multipliers of the simple ladder variety have been in use for some time now in monochrome receivers. A slightly different configuration provides considerable advantages in colour receivers. A full account is given of these advantages and the basic operation of this type of circuit.

PLUS—Servicing the

**BUSH-MURPHY TV161U-V191OU SERIES**

**On Sale MARCH 20th price 3s. 6d.**

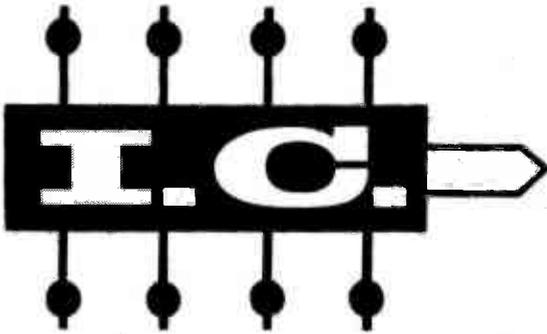

# OF THE MONTH

L.A.J. IRELAND

Number 6

## The Sanken SI-1020A/50A Audio Amplifiers

**J**APANESE electronic firms have always been quick to follow on the heels of their American and European counterparts and the same trend is becoming evident in the world of microcircuits. Lately the Sanken Electric Co. of Tokyo has introduced two rather advanced hybrid i.c.'s one of which can give an audio output power in excess of 50 watts. A very attractive feature of the units is that they comprise virtually the complete amplifier, the only external components required being a power supply, loudspeaker of  $8\Omega$  impedance and coupling capacitor. They provide therefore an ideal beginners project in electronics since with so few components involved, success is virtually guaranteed and a first-class hi-fi amplifier obtained.

A look at Fig. 1 shows that the amplifier itself is fairly orthodox and straight forward in design. The common emitter input stage Tr1, provides a typical input impedance of  $70k\Omega$  and degeneration from the output can be applied across its emitter resistor via pin 3 of the i.c. The signal is then r.c. coupled to Tr2 which acts as a driver for the complementary pair Tr3 and Tr4 and these in turn are direct coupled to the power output stage. Provision is made for the inclusion of a ripple filtering circuit in the 1020A version which is not included in the 1020A.

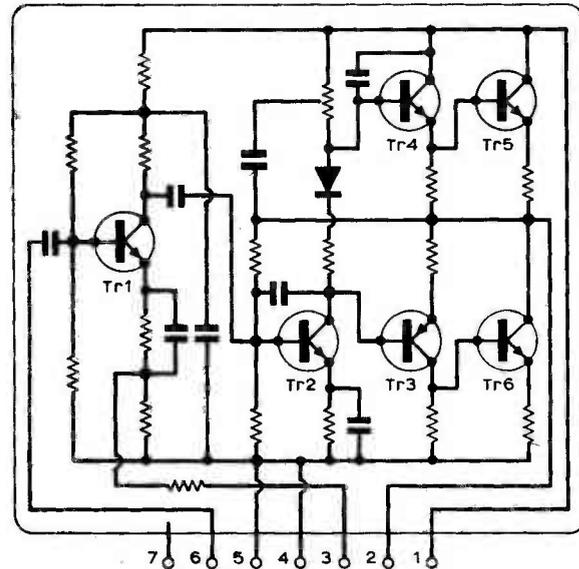


Fig. 1: Circuit of the SI-1020A

Characteristic	Symbol	SI-1020A	SI-1050A
Supply Voltage	$V_{cc}$	48V	62V
Maximum Continuous Output Power (distortion < 0.5%)	$P_o$ max (rms)	25W	50W
Voltage Gain	$G_v$	30dB typ.	30dB typ.
Frequency Range (output 1W)		20Hz—100kHz	20Hz—100kHz
Input Impedance	$Z_{in}$	$70k\Omega$ typ.	$70k\Omega$ typ.
Output Impedance	$Z_{out}$	$0.2\Omega$ typ.	$0.2\Omega$ typ.
S/N Ratio		90dB typ.	90dB typ.
Idling Current		30mA typ.	30mA typ.

CONDITION :  $25^\circ\text{C}$  ambient, 1kHz,  $R_L=8\Omega$

Electrical characteristics of the two amplifiers

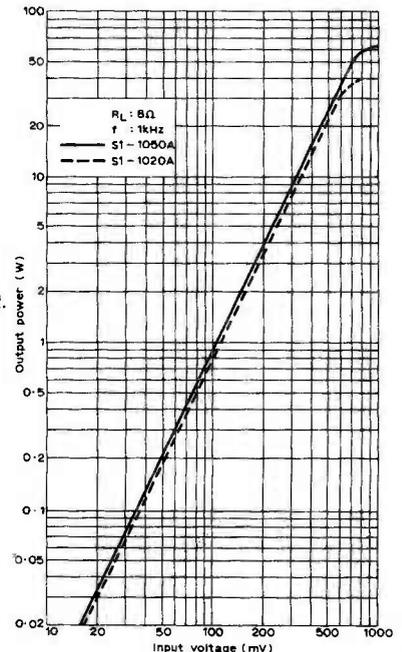


Fig. 2: Graph showing required signal input for a given power output.

*Sign here!!*

for your  
miniature  
soldering  
iron.

CN 15 Watts. Ideal for miniature and micro  
miniature soldering. 18 interchangeable spare  
bits available from .040" (1mm) up to 3/16"  
For 240, 220, 110, 50 or 24 volts.

from  
**32/6**



Model CN 15 watts miniature iron, fitted with 3/32" bit. Interchangeable spare bits 1/8", 3/16" and 1/4" available. For 240, 220, 110, 50 or 24 volts. 32/6



Model CN 15 watts miniature iron, fitted with 1/4" bit. Interchangeable spare bits 3/32", 3/16" and 1/8" available. For 240, 220, 110, 50 or 24 volts. 32/6




Model CN 15 watts miniature iron, fitted with 1/4" bit. Interchangeable spare bits 3/32", 3/16" and 1/8" available. For 240, 220, 110, 50 or 24 volts. 32/6



Model CN 15 watts miniature iron, fitted with 1/4" bit. Interchangeable spare bits 3/32", 3/16" and 1/8" available. For 240, 220, 110, 50 or 24 volts. 32/6

**Complete precision soldering kit**

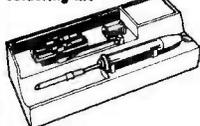

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box"—contains

- Model CN 15 watts miniature iron, fitted with 3/32" bit. Interchangeable spare bits 1/8", 3/16", 1/4"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**



**Model CN 240/2**  
15 watts - 240 volts

Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.

**31/6**



**PRECISION MINIATURE SOLDERING IRONS**

Antex, Mayflower House, Plymouth, Devon.  
Telephone: Plymouth 67377/8.  
Telex: 45296, Giro No. 2581000.

Please send me the Antex colour catalogue

Please send me the following irons

Quantity Model Bit Size Volts Price

.....  
.....  
.....

I enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

PW4

# BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government

38 CHALCOT ROAD, LONDON, N.W.1

Telephone 01-722-9090

EXPRESS POSTAL SERVICE, SAME DAY DESPATCH BY FIRST CLASS MAIL.

All goods are offered subject to the standard three month guarantee.

NO EXPORT ORDERS

OA2 5/9	6E5 7/6	12AC6 7/1	90AV 67/6	EA50 1/6	EL83 6/9	PCC89 9/6	UBCR1 7/1	W101 26/2	BA115 2/8	OA47 2/1
OB2 4/6	6F1 8/9	12AD6 7/6	90C3 34/1	EA76 13/1	EL84 4/9	PCC189 10/6	UBF80 5/9	W107 7/1	BA116 5/1	OA70 3/1
OZ4 6/6	6F6G 4/1	12AE6 7/6	90CV 33/6	EABC80 6/1	EL85 7/6	PCC805 13/9	UBF89 6/9	W729 10/1	BA129 2/6	OA73 3/1
IA3 4/6	6F6M 12/6	12AT6 7/6	90CV 33/6	EAC91 3/1	EL86 8/3	PCC806 13/6	UBR21 10/1	X24 16/6	BA130 2/1	OA79 1/9
1A5 7/3	6F12 3/3	12AT7 3/9	90C19 16/6	EAF42 8/9	EL95 5/3	UBC92 5/6	UC29 5/6	X61 5/9	BA131 2/1	OA81 1/9
1A6 7/3	6F13 3/6	12A16 4/9	130C2 5/9	EB34 3/1	EM80 7/1	PCF82 6/3	UC84 8/1	X61 5/9	BCY12 1/6	OA85 1/6
1C1 5/6	6F15 10/1	12A17 4/6	301 20/1	EB41 4/6	EM81 7/6	PCF84 8/1	UC85 4/6	X63 5/6	BCY33 5/1	OA86 4/1
1C2 9/1	6F18 7/6	12A18 5/6	302 16/6	EB91 2/3	EM84 6/6	PCF86 9/1	UCF80 8/3	X64 12/6	BCY34 4/6	OA90 2/6
1C3 7/1	6F23 13/3	12A17 8/1	303 15/1	EB41 4/6	EM85 11/1	PCF87 16/1	UCH21 9/1	X65 5/1	BCY38 5/1	OA91 1/9
1C5 4/9	6F24 11/9	12AX7 4/6	305 16/6	EBC81 5/6	EM87 7/6	PCF800 13/1	UCH42 13/1	X66 7/6	BCY39 4/6	OA95 1/9
1D5 6/9	6F25 13/1	12AY7 9/9	306 13/1	EBC90 4/1	EY51 7/6	PCF801 7/1	UCH81 6/6	X101 30/6	BCZ11 3/6	OA200 1/1
1D6 9/6	6F26 5/3	12BA6 6/1	807 11/9	EBC91 5/6	EY81 7/1	PCF802 9/1	UCR82 7/1	X109 26/1	BCI07 4/1	OA202 2/1
1FD1 6/6	6F28 14/1	12BE6 5/9	956 2/1	EFB80 6/9	EY83 8/3	PCF805 11/6	UCL83 10/1	X119 6/6	BCI08 3/6	OA210 1/6
1FD9 4/3	6F29 6/6	12BH7 6/1	1821 10/6	EFB83 2/1	EY84 7/6	PCF806 11/6	UFL8 10/1	X719 5/9	BCI13 5/1	OA211 13/6
1G6 6/1	6F30 6/1	12E1 17/1	5763 10/1	EFB89 6/3	EY86 6/6	PCF808 12/6	UJ46 12/6	Z749 13/3	BCI15 3/1	OA2200 12/1
1H5GT 7/1	6F32 3/1	12J5GT 2/6	6060 5/6	EBL21 11/1	EY87 6/6	PCF82 7/6	UF80 6/9	Z777 3/3	BCI16 5/1	OA2201 10/6
1L4 2/6	6H6GT 1/9	12J7GT 6/6	7193 10/6	EC33 12/6	EY88 7/6	PCF83 9/1	UF85 6/9	Z152 4/6	BCI18 4/6	OA2202 9/1
1LDS 5/1	6J5G 3/9	12K5 10/1	7475 4/1	EC54 6/1	EY91 3/1	PCF84 7/6	UF86 9/1	Z219 16/1	BD119 9/1	OA2203 9/6
1LNS 8/1	6J5GT 4/6	12K7GT 5/9	A1834 20/1	EC70 4/9	EZ35 5/1	PCF85 9/1	UF89 6/9	Z719 4/6	BFY50 4/1	OA2204 9/1
1N5GT 7/9	6J6 3/1	12O7GT 7/6	A2134 10/1	EC86 12/6	EZ40 7/6	PCF86 8/6	UL41 10/6	Z729 6/3	BFY51 4/1	OA2205 9/1
1U4 7/1	6T7G 4/9	12S4GT 6/9	A3042 15/1	EC88 12/6	EZ80 6/6	PCF88 11/6	UL46 12/6	Z759 4/5	BFY52 4/1	OA2206 9/1
1F10 5/9	6T7GT 6/6	12S7 3/1	AC2PEN/	EC92 4/6	EZ80 6/6	PCF88 11/6	UL84 6/6	Z759 4/5	BFY54 3/1	OA2207 10/6
1P11 5/9	6K7G 2/1	12S7 3/1	DD 19/6	EC93 15/6	EZ81 4/9	PCF801 15/1	UM80 6/6	Z759 4/5	BFY59 5/1	OA2210 7/1
1R5 5/6	6K7GT 4/6	12SH7 3/1	AC2PEN/	EC93 31/6	EZ90 4/3	PEN45 7/1	URIC 10/6	Z759 4/5	BFY63 4/1	OA2211 7/1
1S4 4/9	6L1 19/6	12S7 4/6	DD 19/6	EC93 31/6	EW4 12/6	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2212 16/6
1S5 4/3	6L6GT 7/9	12S7 4/6	AC6PEN 4/9	EC94 29/6	FC4 12/6	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2213 16/6
1T4 2/9	6L7 12/6	12S7GT 7/6	AC/PEN (5)	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2214 16/6
1U2 4/3	6L8 12/6	12S7GT 7/6	AC/PEN (7)	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2215 16/6
2A7 12/6	6L18 6/1	14S7 15/1	AC/PEN (7)	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2216 16/6
2D13C 7/1	6L19 19/1	18 12/6	AC/PEN (7)	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2217 16/6
2D21 5/6	6LD12 6/1	19A05 4/9	AC/TH10/	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2218 16/6
2X2 4/9	6LD20 9/6	19H1 40/1	AC/TP 19/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2219 16/6
3A4 3/6	6N7GT 6/6	20D1 13/1	AC/TP2 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2220 16/6
3A5 10/1	6P1 12/1	20D4 20/5	AC/TP2 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2221 16/6
3B3 5/1	6P5 4/1	20S2 14/1	AC/TP2 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2222 16/6
3D6 3/6	6P25 12/1	20L1 13/1	AZ1 8/1	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2223 16/6
3Q4 6/6	6P26 12/1	20P1 17/6	AZ31 9/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2224 16/6
3Q5GT 6/1	6P28 25/1	20P3 18/1	AZ41 7/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2225 16/6
3S4 5/9	6P12 6/1	20P4 18/6	B36 6/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2226 16/6
3V4 5/9	6Q7G 6/1	20P5 18/6	B39 6/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2227 16/6
4D1 3/9	6Q1T 8/6	25L6GT 5/6	B79 5/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2228 16/6
5R4G 5/9	6R7G 7/6	25S2 14/1	B729 12/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2229 16/6
5U4G 5/6	6R7 11/1	25Y5G 8/6	BL6 10/1	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2230 16/6
5V4G 7/6	6SA7GT 7/1	25Z4G 6/1	CL33 18/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2231 16/6
5Y3GT 5/6	6SA7 7/1	25Z5 7/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2232 16/6
5Z3 8/1	6S7GT 6/6	25Z6G 8/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2233 16/6
630L2 12/6	6S7 6/1	30C1 6/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2234 16/6
630L3 12/6	6S17 3/3	30C15 12/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2235 16/6
6AC3 3/1	6SK7GT 4/6	30C18 7/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2236 16/6
6AG5 3/6	6SN7GT 4/6	30F5 16/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2237 16/6
6AJ5 8/6	6SQ7GT 7/6	30F11 15/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2238 16/6
6A18 5/9	6S57 3/1	30F11.2 16/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2239 16/6
6AK5 5/6	6G4GT 12/1	30F11.3 16/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2240 16/6
6AK6 6/6	6V6G 3/6	30F11.4 16/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2241 16/6
6AK8 4/1	6X4 4/3	30L1 6/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2242 16/6
6AL5 2/3	6X3GT 5/1	30L1.5 13/9	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2243 16/6
6AM6 3/6	6Y6G 8/1	30L1.7 15/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2244 16/6
6AQ5 5/6	6Y7G 12/6	30P4 12/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2245 16/6
6AR6 20/1	6Z1 12/6	30P4MR 17/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2246 16/6
6AT6 4/1	7AN7 6/3	30P12 13/9	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2247 16/6
6AU6 5/1	7B6 10/9	30P18 6/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2248 16/6
6AV6 5/6	7B7 7/1	30P19 12/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2249 16/6
6B8G 2/6	7C6 6/1	30P11.5 12/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2250 16/6
6B6A 4/6	7D6 15/1	30P11.5 15/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2251 16/6
6B6E 4/9	7E1 7/6	30P11.6 15/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2252 16/6
6B6G 2/6	7H7 12/1	30P11.5 15/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2253 16/6
6B6H 7/6	7Y7 5/1	35A3 9/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2254 16/6
6B6J 8/6	7V4 6/6	35A5 15/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2255 16/6
6BQ5 4/9	7Z4 4/6	35D5 12/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2256 16/6
6BQ7A 7/1	8B76 7/1	35L6GT 8/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2257 16/6
6BR4 6/6	9D7 4/6	35L6GT 8/6	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2258 16/6
6BR8 8/1	10C1 12/6	35Z3 10/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2259 16/6
6B8T 16/6	10C2 10/1	35Z4GT 4/9	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2260 16/6
6B8V 12/9	10C4 6/6	35Z5GT 6/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2261 16/6
6B9W 11/1	10D1 8/1	42 5/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2262 16/6
6B9X 4/6	10D2 14/7	43 10/1	CV6 10/6	EC94 9/6	GZ30 7/1	PEN45 7/1	URIC 10/6	Z759 4/5	BFY73 7/6	OA2263 16/6
6BZ6 6/1										

A diagram of the complete amplifier together with a suitable power supply is given in Fig. 3. The 1A fuse (2A in the case of the 1050A model) in series with the power supply provides adequate protection in the event of a short-circuit of the loudspeaker terminals. The units themselves are capable of withstanding a short-circuit of the output terminals for 5 seconds under all operating conditions and so the fuse will blow before any damage is done. The metal housing in which the amplifier is mounted provides sufficient heat dissipation and in addition it can be directly bolted to the chassis or case without the need for insulating washers as it is electrically insulated from the i.c. itself. The 1020A measures approx. 3.15in. x 1.8in. and the 1050A 3.9in. x 1.6in. approx. overall.

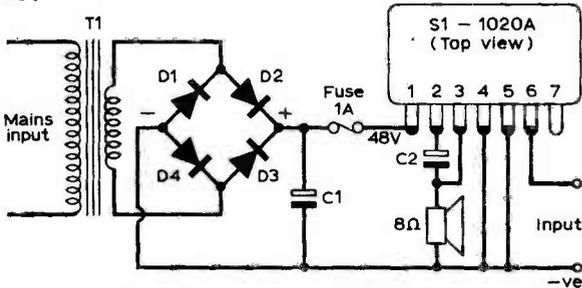


Fig. 3: Circuit of suitable power supply

Two very attractive features of the units are their frequency response, 20Hz. to 30kHz., and harmonic distortion of less than 0.5% at the full output power levels and with a signal to noise ratio of greater than 90dB. they should fill the requirements of the most discerning hi-fi enthusiast. One slight disadvantage however, especially if the units are to be put to mobile use is the rather high operating voltage required but even here idling current has been reduced to a mere 30mA which ensures economical battery operation.

## ★ components list

### Capacitors :

- C1 4000 $\mu$ F 60V (70V for 1050A)
- C2 2000 $\mu$ F 30V (40V for 1050A)

### Miscellaneous :

- D1-4 60V 1A (70V 2A for 1050A)  
(Henry's Radio Type RS32AF)
- T1 Transformer (Henry's Radio Type MT104AT)
- IC Type SI-1020A or SI-1050A  
(Photain Controls Ltd., Randalls Road, Leatherhead, Surrey)

The signal input levels required for various power outputs can be derived from Fig. 2.

At the present state of the art, these are the most powerful i.c.'s available and provide the obvious answer to anyone requiring a rugged and miniature audio power amplifier.

**NEXT MONTH:** The RCA 3052 i.c., comprising four separate amplifiers, will be reviewed. It is ideal for use ahead of the SI-1020A or SI-1050A amplifier reviewed above. ■

# THE MW COLUMN

CONDITIONS on the band this winter have been the best for several years. Especially noticeable were the number of Far East stations logged in the afternoons—China on 940, 1000, 1230 and 1290kHz, Taiwan on 750 and 1200. Ryukyu islands on 1178 and 1360, South Korea on 1190. Calcutta 1130kHz was a regular for several weeks. Near East stations logged were Bagdad 760, Teheran 895 and 1325, Kabul 1280, Kuwait 1345 and at night the Indians—Rajkot 1070 and Jabalpur 1180. North American DX was almost unbroken all winter. The writer started the year with a fine logging of *KOMO Seattle* on 1000kHz from 0740 to 0800 Hrs GMT on the 2nd January. Earlier the same morning *WVOV Huntsville Alabama* on the same frequency was heard doing an equipment test at 0630. Other DX includes *CBF Montreal* 690kHz, a Newfoundland relay station on 740, *WJR Detroit* 760, *WWL New Orleans* on 870, *CBM Montreal* 940, *WCFL Chicago* 1000, *CFRB* 1010 in Toronto, *KMOX St. Louis* on 1120, *WBT Charlotte North Carolina* 1110, *WOAI* 1200 in *San Antonio Texas*. Some of the best North American DX occurs in the spring and autumn. Stations that have been logged in this country are *KOMO* 1000kHz in *Seattle*, *KING* 1090 also in *Seattle*, *KNX* 1070 *Los Angeles*, *KEX* 1190 *Portland Oregon*, *KFBK* 1530 in *Sacramento, California*.

The Caribbean area is often heard well at this time of year. After midnight, look for *CMGN* 720kHz *Radio Rebelde* in *Colon, Cuba*, *St. Vincent* in the *Windward Islands* on 705, *Port Maria, Jamaica*, on 750 with the call *JBC*, *ZFY Radio Demerara, Georgetown, Guyana*, 760, *ZBVI Roadtown, Tortola, British Virgin Islands* on 780, *PJB Trans World Radio Bonaire Netherlands Antilles* on 800 (an easy one), *4VEC 'La Voix Evangelique'* 830kHz *Cap Haitien, Haiti* in French and English, *Radio Belize, British Honduras* on 834, *Radio Caribbean* 840 *Castries, St. Lucia* in English and French, *Radio Antilles* 930 in *Montserrat, Leeward Islands* in French and English, *TIFC 'The Lighthouse of the Caribbean'* 1075kHz in Spanish and English, *WBMJ* 1190kHz in *San Juan Puerto Rico* with pop music and English announcements, *PJD2 'The Gospel Voice of the Eastern Caribbean'* 1295kHz in *St. Martin, Netherlands Antilles* in Dutch and English. A new station is *Radio Anguilla* on 1505kHz with a power of 500 watts.

The new 1000kW station at *Beida, Libya*, is now on the air on 1124kHz and has been heard in North America. Another powerful North African is *Azilal Morocco* on 209kHz on the Long Waves. This station is the only African on this band and it can be heard in Spanish, French and English as well as in Arabic. The Spanish station audible at sunset on 1140 is *ECS11 Radio Centro Madrid* which has moved from 1394kHz. Another member of the same network is *ECS13, La Voz de Ciudad Real*, currently on 1145kHz.

CHARLES MOLLOY

# practically wireless commentary by HENRY

Just playing  
about!

I DO not know Mr. Matthews. And he knows Henry only by the odd effusions he occasionally picks up in this column. Odd, it would seem, is hardly a strong enough term. My informant is Mrs. Matthews, whose bus-top confidences to Mrs. Henry sparked off the idea for this month's contribution.

You see, Mr. Matthews is one of our unsung electronic heroes—a radio enthusiast, an avid constructor, a lonely wielder of the soldering iron who does not believe in flaunting his merits abroad. In the privacy of his own two-up, two-downer, he struggles with the intricacies of transistor testers, knocks up a record player for his younger daughter, modifies the family radio set and will one day provide his doted-on grandson with a personal communications receiver.

Henry would never have heard of him if it were not for his distressing tendency to drop hot solder on the tufted living-room carpet. One can almost hear the whoops of commiseration as the two ladies swapped horror stories.

*'It's just the same in our house! Once he gets his nose into that book, and spreads his wires all over the floor, there's no stopping him.'*

That book, as you will have guessed, is *Practical Wireless*, which, if the ladies get the emancipation they are militating for

and rule our lives in deadly earnest, will soon join the Fahrenheit 451 list of banned, subversive literature. And what will Henry do then, poor thing?


Well, I'll tell you what he may do. He may join Mr. Matthews and others of like bent in the formation of a radio-dabblers underground movement. One of the basic rules is that members shall have suffered at least a single eviction from what they thought was going to be a snug den, to a draughty corner of the potting shed or equivalent.

The ladies, bless them, just do not understand. Poor Mr. Matthews, I am told, has suffered the final indignity of having his precious equipment jocularly dismissed as 'toys'. He is 'permitted' to play at set hours, in carefully circumscribed places, so long as he does not make too much noise. That he still manages to derive a great deal of fun from his hobby is as much a tribute to his sense of humour and tolerance as to the well-known attraction of the electron. A few spots of solder on the Cyril Lord are a small price to pay for such peace of mind that our hobby can give—and, after all, flourishing pliers and tin-snips does not drag us away from the family hearth. That is surely a plus-point, madam?

Reading this, Mr. Matthews will realise I am joking—having mastered the initial shock of my intrusion into his privacy. Indeed, I would not have known about him at all—though he, apparently, has the advantage of me—were it not for his wife's very obvious pride in her lord and master's prowess.

The fact that a chap can string two wires together and make an invisible power give voice smacks something of witchcraft and we all know how superstitious the hausfrau can be.

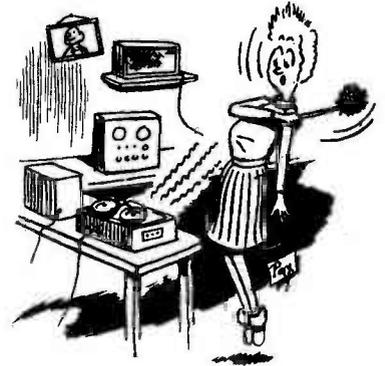Mrs. Henry, for example, has little regard for my prowess as a



*"Programmed to yell 'don't touch me!'"*

gardener. She prefers to remember the time I uprooted a corner of dormant 'busy-lizzie' in the belief I was ridding the world of convolvulus rather than the bird-activated pea-protector that very nearly was successful. Only the switching time of an OC71 was the best we could do in those days...

But the communications corner of my den still scares her. In this last refuge, from which I am still winkled when the approach of visitors demands I turn it back into the spare bedroom, I can at least be sure of some isolation. I believe my advantage stems from the time Joe and I were experimenting with an intriguing—and probably quite illegal—voice-operated CQ switch, and Mrs. H. was interrupted in the middle of a private tidying-up session by the clicking of relays and a disembodied Joe asking: 'Hallo there, are we together?'

It would not be much trouble for Mr. Matthews and me to collaborate in the design of a series of proximity switches that could activate a solenoid-switched tape recorder programmed to yell 'Don't touch me!' loud and clear. Now that would be a toy worth having. Even better than that electronic shoehorn (bootstrapped circuit, of course) that young Bob has promised to make me.



*"My informant is Mrs. Matthews"*

# DISCOSOUND

## NEW DISCOSOUND PRE-4



**DISCOSOUND** announce a new range of high quality modular pre-amps, and main amplifiers which offer a wide range of facilities to suit all types of applications.

**Model Pre-4.** This is a four channel fully mixable pre-amp, with separate treble, bass and master volume controls, and is completely self powered. All four inputs are by standard jack socket on the front panel with the addition of inputs 3 and 4 being duplicated on the back panel, with two paralleled outputs also featured for versatility in use.

**Specification:**

Inputs.	Vol. 1. 10 mv at 50k Ohms	} Other Impedances can be made to special order.
	Vol. 2. 10 mv at 50k Ohms	
	Vol. 3. 50 mv at 500k Ohms	
	Vol. 4. 50 mv at 500k Ohms	

Frequency Response: 30—20,000 HZ  $\pm$  3db.

Signal/Noise Ratio: -65db.

Bass: continuously variable 20db. at 100 HZ.

Treble: continuously variable 20db. at 10 KHZ.

Output: variable up to 1 volt RMS at 25k Ohms.

Size: front panel 12 $\frac{1}{2}$  x 5 $\frac{1}{4}$  cut out required 11 $\frac{1}{2}$  x 4 $\frac{1}{4}$ .

Completely built and tested.

**PRICE £18.0.0 inc. P. & P.**

## NEW DISCOSOUND 70 MAIN AMPLIFIER

This is a 70 watts RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features, full automatic overload protection against short or open circuits. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound PRE-4, or can be used with any other high quality pre-amp control unit.

**Specification:**

Power Output: 70 watts RMS into 8 Ohms.

Frequency response: 20—20,000 Hz  $\pm$  2db.

Harmonic distortion: less than 0.5% at 70 watts RMS.


Input Impedance and Sensitivity: 700 mv at 20-30k Ohms.

Size: 7" x 9" x 6".

Completely built and tested on steel Chassis.

**PRICE £30.0.0 inc. P. & P.**

## DJ 30L PSYCHEDELIC LIGHT CONTROL UNIT

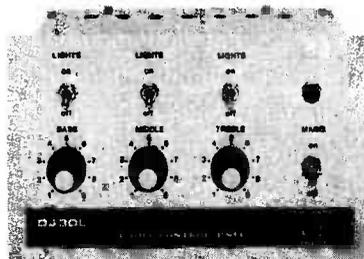


3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation.

Completely built and tested.

**PRICE £37.10.0 inc. P. & P.**

## NEW DJ 70S INTEGRATED MIXER-AMPLIFIER

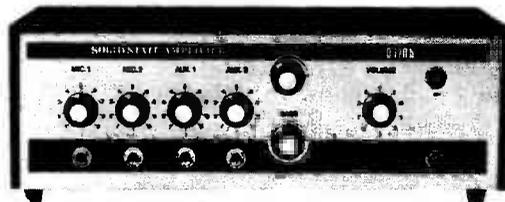

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output, a frequency response that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs etc., or anywhere that high quality high output is required.

**SPECIFICATION**

Power output	70 watts R.M.S. $\pm$ 1db at 8 ohms
Frequency response	30-20,000 HZ $\pm$ 3db.
Signal/noise ratio	Better than -65db at full output.
Harmonic distortion	Less than 1% at full output.
Inputs 1 & 2 -MTC	8 mV at 50k ohms.
3 & 4 -AUX	50 mV at 1 meg ohm.
50 or 600 ohm mic	Inputs can be ordered at extra cost to special order.
Bass	Continuously variable 20db at 100HZ.
Treble	Continuously variable 20db at 10KHZ.
Size	15 $\frac{1}{2}$ in x 5in x 6in.

**PRICE £55.0.0 inc. P. & P.**

Also available DJ105S 30 watt P.A. Amplifier. Similar specification to above.

**PRICE £35.0.0 inc. P. & P.**

For full details of these and all Discosound Products write direct to:—

**DISCOSOUND, 122 BALLS POND ROAD, LONDON, N.1. Tel: 01-254 5779**

Full money back guarantee if returned within 10 days.


All Discosound Products are guaranteed for 12 months.

Demonstrations given at any time.

# MARCH ISSUE

# RADIO CONSTRUCTOR

## "DISCOVERY" - BEGINNER'S RECEIVER

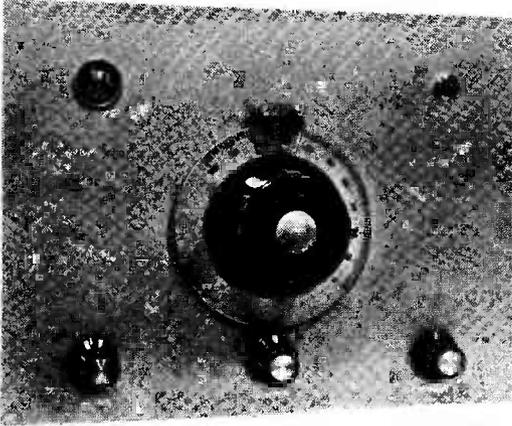

Written especially for the beginner, this 2-valve, 4-stage design - ECC83, ECL82 - has an integral power supply (BY100 silicon rectifier) and features a grounded-grid input stage. An efficient reaction circuit with absence of "dead spots" is a feature of the design. Coverage is from 30 to 1.7MHz (approx), also the medium wave-band.

### FREE

A four-page art paper cut-out colour supplement featuring Workshop Plans, Circuit, Point-to-Point Wiring Diagram and Testing Tables for this receiver.

### PLUS

## SPECIAL WORKSHOP EQUIPMENT OFFER

OTHER CONSTRUCTIONAL PROJECTS  
DATA SHEET 36  
SUPPORTING FEATURES

# THE RADIO CONSTRUCTOR

ON SALE NOW 3/-

Copies may also be obtained direct from the Publishers—3s. 6d. including postage. Published by:

DATA PUBLICATIONS LTD.,  
57 MAIDA VALE, LONDON, W.9.

### TRANSISTORS etc.

AC107	3/-	OC35	9/-
AC126	2/-	OC44	2/-
AF115	3/-	OC45	2/-
AF116	3/-	OC70	2/3
AF117	2/9	OC71	2/-
BF18	4/6	OC72	2/2
BF51	4/-	OC73	2/9
GET113	2/6	OC75	2/2
OA5	1/6	OC81	2/-
OA9	1/8	OC81D	2/-
OA47	1/9	OC82D	2/3
OA81	1/6	OC140	5/-
OA85	1/6	OC169	3/6
OC23	6/6	OC170	2/6
OC25	6/-	OC171	2/2
OC26	7/6	OC202	4/6
OC28	8/6	TK22C	1/6

### SILICON DIODE RECTIFIERS

BY100	800 piv	2/10
500mA	250 piv	1/9
Avalanche	1/4 A	
	1200 piv	4/-
5A Amp Series		
BVZ13	300 piv	3/6
BVZ12	600 piv	4/6
BVZ11	900 piv	5/-
BVZ10	1200 piv	5/6
Mullard Stack FW		
Bridge		
12A	100 piv	39/6 (3/-)

### THYRISTORS

5 amp series		
100 piv		7/6
200 piv		9/-
300 piv		10/6
400 piv		12/-
800 piv		25/-
100 amp series		
50 piv		10/-
100 piv		12/-

### Midget Electrolytic Conds. Wire Ends

At 6d. each		
0.8µF		25 volt
4µF		150 volt
640µF		2.5 volt
At 9d. each		
3µF		350 volt
4µF		12 volt
8µF		12 volt
16µF		16 volt
30µF		10 volt
100µF		6 volt
125µF		4 volt

### At 1/- each

16µF		250 volt
50µF		10 volt
100µF		12 volt
100µF		25 volt
200µF		10 volt
320µF		10 volt

Crystal Diodes—6 for 2/6 (7d)

100 amp series prices available on request.

2000 MFD. 30V 5/6  
1500 MFD. 30V 4/6

Additional Transistors—AF147 and AF150, 24V. Larger envelope, 4 leads, collective current 10mA, gain 70—4/- each. AF149—gain 225—4/6 each. Also 8µF 350V 1/2, 25µF 25V 1/3 and 50µF 50V 1/9. Other electrolytics in current list. Postage, packing and insurance all above 1/- up to 11/- and over charges paid. 2 GANG VAR. CONDENSER: Mod., air-spaced, .0005 ea. sec. 5/- (1/-), 3 GANG, 7/6 (1/6). SUB-MIN. TRANSFORMER: Output (3Ω for OC72 etc) 2/9 (Up to six 1/-). MULTIMETER: 20,000 Ω/V D.C., 10,000 Ω/V A.C. 0-25/50/500/1K volts D.C. 0-10/50/100/500/1K volts A.C. 0-50µA/2.5mA/250mA D.C. 0-6K Ω/6 meg Ω. 0-10µF-100mfd/1mfd. 0-20 to +22dB. Complete with test leads and instructions. Overload protected 1970 model with every refinement. £4.10.0 (2/6). JUNIOR MODEL at 47/6 (2/6). 1000Ω/V described in free list.

SOLDERING IRON. Slim Mod. British High speed, 84W in., all parts replaceable, fully guaranteed for professional, radio and general D.I.Y. use, 19/6 (1/6).

DIAMOND STYLI Replacements for BSR TC8LP, TC8/S and TC8LP/STEREO; COLLARO "O"; RONETTE BF40LP; GARRARD GC2LP and GC8LP; ACOS GP65/67; all at 7/6 each (1/-). ACOS GP73 and GP91; BSR ST4 and ST9; SONOTONE 9TA, 9TA and 9TAHC; PHILIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304), all at 13/6 (1/-).

SAPHIRE all the above 7/6 types only, also ACOS GP37 at 3/3 each (1/-). ACOS GP91 at 7/6 (1/-). No other types at present, and no 78 rpm available in any type.

PICK-UP CARTRIDGES All fitted Styli and Standard fittings. Mono GP67/2, 15/-; Stereo compatible—Mono which also plays Stereo records monaurally with min. wear, GP91SC, 21/-; latest Stereo GP93, 24/6. Ceramic Stereo, top quality for expensive outfits, GP94, 30/- (all 1/-).

RF ELIMINATOR (A.C.) 17/6 (1/6). TWO STATION TRANS. INTER-COM. Excellent battery alarm. Instant, easy fitting with leads, plug and battery. All you require 52/6 (3/-). TRANSISTORISED AMPLIFIERS, 3 watt, 9V operation, 45/6 (1/6); 7½ watt, 6 trans. 24V operation 47/6 (2/6).

Extra High Torque MINI-MOTOR, 4½ to 12V, 1¼ x 7/16 in. 5/- (1/-), 9,000 r.p.m. SUBSTITUTION BOXES. Capacitance 25/6 (1/6). Resistance 32/6 (1/6). Both full range and complete. Full details in list.

TEST PROBES: Flexible, unbreakable 24in. Red and Black leads, thin 4¼ in. prods, 1¼ in. plugs 4/9 (1/-). CROC. CLIPS: Plated with screw, or with red/black handles, 6d. each, 5/- doz. (1/-).

RECORDING TAPE Finest quality British Mylar. STANDARD: 3in. 600ft. 7/3, 5¼ in. 1200 ft. 11/3, 7in. 1800ft. 18/- (1/3 reel). Still the finest quality and value obtainable.

MICROPHONES—CRYSTAL MIC91. Desk, 16/3; MIC45, curved hand grip 17/6; Stick "60" 20/3; Stick "39" 26/6 (1/6 each type). Cream plastic hand type 7/6, or with "strut" stand, switch and 2 leads, with 2.5 and 3.5 plugs 12/6 (1/2). Label (for hand) with clip 6/6 (1/2). Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands, 25/- (1/6). DYNAMIC: Cream hand/table 15/6 (1/6). MS10 50K Ω. 3¼ x 7/16 in. with Base. Adaptor 37/6 (2/6). MS11, similar but on flexible Swan neck to switch-fitted base 42/6 (2/6). DN 160, uni-directional pencil type all metal, for hand or stand use at new low price of £3.13.6 (1/6).

CARDIOID DYNAMIC (DYNAMIC) DIRECTORS: Two high successful mikes "SQUARE" 208, £5.10.0. "BALL" type, 209, with 50K/600 ohms imp., £5.17.6 (either type 5/-). Full details in list.

MICROPHONE INSERTS: Diameter 1.75in. or 0.9in., either size 5/6 (1/2).

SPEAKERS: 12in. round, fitted Tweeter, 6W, 3 or 15Ω (state which), 37/6 (5/6); or for stereo, 80/- per pair (charges paid); 2½ in. 30 6/6 (1/2); 6x4 heavy duty 3D 14/6 (3/6) or for Stereo 34/6 pair (charges paid). Limited quantity powerful 2½ in. PM transistor replacement speaker, high ohms, excellent 5/9 (1/6).

EARPIECES with lead and min. jack plug, magnetic 1/9. Crystal 4/9 (up to 3 for 1/- on either). State if 2.5mm. or 3.5mm. plug required. (Crystal 3.5mm. only.)

AERIALS, Car Types: Telescopic, vandal proof, locks retracted, 2 keys and all fittings, 22/6 (2/6). Motor driven, 12V, 5 section, complete £7.10.0 (5/-).

FOR ALL PORTABLES and P.M. SETS. 7-Section 3½-32in., no swivel, screw hole in base, 6/6. 10-section 6½-47½ in., no swivel, screw hole in base, 12/6.

DISAPPEARING 8 section, swivel fixing assembly, 6½-33in. 10/-; New 6 section 5¼-25¼ in., screw hole in base, no swivel 4/- (1/- all sizes).

SWITCHES: Standard toggle, metal, 250V 2A. One hole (fixing): SPST 2/3, SPDT 2/9, DPST 3/-, DPDT 3/3. Slide type, Sub-min. DPDT 1/6 each. Small DPDT 3 way, centre "off" 1/9. Reed magnetic on/off 1/9 (up to three, 1/-; 1d each all additional). Rotary Switches etc. in list.

VIBRATORS: Famous makes only, 12 volt 4d pin non-synch. 4/6. 12 volt 7 pin synth. 12/6 (1/6 each either type). No other types available.

MAINS NEON TESTER: Fly leads 2/-, Pocket screwdriver type 3/6. PLUGS: Std. Jack, plastic body 2/3. Screened 3/-, VALVE HOLDERS: B7G or B9A, Moulded 6d. (all above, 1/- up to three).

CONNECTING WIRE: 5 coils assid. coils, each 5 yds. Solid Croc 2/6. Flexible 3/-, Super thin for transistor wiring etc. 3/- (1/- all types per 5 coils). PICK-UP WIRE: Twin Super thin Flex, Screened, Sheathed, 1/3 yd. (6d. up to 6 yds., over 6 yds. post free). TWIN MIKE CABLE: 1/3 yd. SINGLE MIKE CABLE: 8d. yd. Both flexible, screened and sheathed. (Up to 3 yds. 8d., each additional yard 1d. extra.)

R.F. FIELD INDICATOR, 5-band with antenna, monitoring crystal earpiece, visible indicator etc. 48/6 (1/6). Details in list.

RETRACTABLE FLEXIBLE LEADS. Space saving "Curly", many uses in car and home; with phono plug each end, 6ft., 4/6; 12ft., 7/9; With phono plug one end, phono socket at other, 6ft., 5/-; 12ft., 8/6 (1/- each all types).

CAR RADIO: Splendid new All-British dash-mounting radio using Mullard transistors and circuit. M. and L. wave. Separate speaker and baffle. Absolutely complete for + or - chassis, £11.11.0 (6/6). A huge success since introduction.

CURRENT LIST: Set with order, free for s.a.e. details of cable, croc. clips and leads, Continental din plugs for Grundig, Telefunken equipment, etc., dials, plugs and sockets, panel meters, record player and tape recording accessories. Battery chargers, test equipment, terminals, special transistors, portable sets, more switches and other components, Veroboard etc., in this advertisement cancels all previous ones and lists supplied prior to Feb. 28th, 1970.

## FELSTEAD ELECTRONICS

(PW29) LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK6 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 3/- plus carriage cannot be accepted, and a minimum charge of 1/- is now made. Charges apply to G.B. and Eire only. Overseas orders welcomed. Air or surface mail at cost. Sent at buyer's risk, unregistered and uninsured unless specified and min. insurance/fee. of 3/2 sent. S.A.E. please for all enquiries, otherwise regret cannot be replied to.

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

This month I have enough DX News and logs to fill several pages so I will start with:—

**Peter Giles** of Wolverhampton has a Heathkit RG-1 and a 70 foot end-fed aerial which enabled him to send in the following log:—

11855 *S. Arabia* in English from 0430 to 0530  
 11970 *R. Lebanon* in English from 0230 to 0300  
 15105 *WIBS* in English (weak signal), 1945 to 2130  
 17705 *Havana*, Cuba in English from 2010 to 2138  
 17920 *UAR* in English from 1315 to 1430.

**N. G. Pope** of Chesterfield also heard the Saudi Arabian station in English on 11855 but at the earlier time of 1716-1730.

Mr. Pope also mentions that the *Voice of Denmark* will continue to broadcast in Danish in accordance with the following schedule:—

On 15165 at 0730-0815, 0945-0950, 1130-1155, 1200-1245, 1330-1345, 1400-1445, 1730-1815, 1830-1915 and 2100-2145 also on 9520 from 0100-0145.

The station will only answer letters and reports which are written in Danish.

**Mr. T. R. Gibbs** of Swindon sent me his log which included: *Radio Portugal* on 17895 and 21495 at 1350-1415; *Radio Australia* on 9570 at 2100-2130 and *All India Radio* on 7215, 11775 and 15435 at 2200-2230.

**Michael R. Preston** of London, NW11 used his HMV Domestic and 12 metre wire to send in one of the best logs this month:—

9540 *R. Lubumbashi*, Katanga, Congo in French at 2200  
 9605 *Athens* at 1832  
 11925 *Tashkent* at 1400.

Michael also mentions that *Radio Finland* now uses 11755 instead of 11805 in all transmissions including English from 1800-1830 which is also on 9550 and 15185. Another news item from Michael says that *Radio New Zealand* plans to increase its power from 7.5 to 20kW.

**Robert Hanstock** of Sheffield sent me the English schedule of *Radio Belgrade* which reads:—

1530-1600 on 9620, 11735 and 15240; 1830-1900 on 6100 and 2000-2030 on 7200 and 9620.

Another good log came from **Mr. R. Ellis** of Stroud with his Hammarlund receiver and 49 metre 'V' dipole:—

7250 *Vilnius, Lithuania* from 2230 to 2300  
 11855 *S. Arabia*, good signal from 1830 to 1900  
 15150 *Radio Kuwait*, 55455 from 1600-1615  
 15180 *ETLF* in English sign on at 1600  
 15255 *HCJB*, Ecuador, 54343 from 1900 to 1915  
 17750 *Karachi*, Pakistan, 44344 from 1500 to 1511  
 17850 *Bucharest*, Rumania, 44233 from 1315 to 1330.

**Kevin Goulding** of Bath informs me that the

Times in GMT • Frequencies in kHz

## THE BROADCAST BANDS

Malcolm Connah

World Radio-TV Handbook Co. Ltd. (see December 1969 issue) has changed its address to: Søjlilveje 44, 2650 Hvidovre, Denmark.

### Africa

**Sierra Leone:** The latest schedule from Radio Sierra Leone indicates that all transmissions are on the frequency of 3316 (10kW) and the hours of broadcasting are: 0600-0930, 1245-1330 and 1545-2300 Monday to Friday; 0600-1000 and 1200-2330 on Saturday and 0600-2230 on Sunday.

**South Africa:** Radio RSA continues to broadcast in English to the U.K. from 1756 to 1850 on 15250 and 21480 but has dropped the frequency of 17795.

### Asia

**Nepal:** Radio Nepal signs on at 0120 on 7105 and 11970 and also at 1220 on 7165 and 11970, the power used is 5 or 100kW.

**Mongolia:** According to a new programme schedule from Radio Ulan Bator the station now broadcasts in English from 1220 to 1250 on 15445 and 17785 and also from 2200 to 2230 on 9540 and 11860.

**Qatar:** Radio Qatar is now using the new frequencies of 5150, 6135, 9550, 9770 and 11710. This should make reception easier as the station used to be on the very crowded channel of 9570 only.

**South Vietnam:** Radio Vietnam in Hue broadcasts in Vietnamese on 9667 until sign off at 1500, this station is not listed in the World Radio-TV handbook.

### Oceania

**Australia:** Radio Australia has a new broadcast in English for the Pacific area on 15140 from 0900 to 1400. The station is also testing the frequency of 11920 between 2000 and 2055.

**Gilbert and Ellice Islands:** Radio Tarawa can be heard on 4912.5 and the following schedule is given:—

English and Vernaculars from 1845 to 2000 Monday to Saturday and in English from 0700 (0630 on Sunday) to 0745 daily.

**New Zealand:** Radio New Zealand has been picked up in England between 0700 and 0845 with fair strength on 11780.

**Tahiti:** Radio Tahiti, Papeete has been heard around 0600 on 11825 with strong interference from several adjacent stations.

Many thanks to all of you who sent in your logs for the benefit of the other readers, I hope that you will continue to do so and will be joined by many other contributors.

73 and good DX until the next time.

# THE AMATEUR BANDS

David Gibson, G3JDG

IT has been one of those months on the amateur bands. Such a mixture of logs and contradictions that it's difficult to decide just what is what.

One s.w.l. claims that the l.f. bands have been very good and appeared to be getting better towards the end of the month. Another tells harrowing tales of evenings spent listening to long slices of noise, and at times even the arrival of a solitary European station was enough to cause a minor celebration.

The same tale has been repeated at the other end of the spectrum. Some have described ten metres as an r.f. cemetery while others have praised its service in the interests of amateur radio. Perhaps some of us have listened at the wrong times.

At the home QTH, the l.f. bands, forty metres and below, have appeared reasonable. Hoards of W stations have been heard s.s.b.-ing to each other and a number of EUs have been logged both calling and working Oceania, although it must be confessed that VK stations and the like could not be received and so don't count.

In the v.h.f. region we scooped an all-time record—two logs received. One exponent of these frequencies threatens to listen on seventy centimetres. Any one doing anything with lasers yet?

P. Knisely (Surrey) informs of two more stations now active from Anguilla, VP2EQ and VP2EM. Owls may care to QRX on twenty and fifteen from midnight on most nights.

John Morris, G3ABG, sends details of the Worked All Britain award. Interesting to note that there are certificates for s.w.l.s. Interested enthusiasts, and sheepskin hunters, should drop John a line at 24 Walhouse Street, Cannock, Staffs.

P. Flatman (Suffolk), NCX100 plus PR30 pre-selector, admits to plundering 80. The swag includes: CN8HD, EA6BG, OHØNC (Aaland Is.), VE1IE, VO1FG, W2HBW, 4X4GV, all s.s.b.

Pearls of wisdom from Pat Johnson regarding the where and when on 80. For W/VE/VO, any time after 2300 up until 0800. Best DX frequencies are 3-790 and 3-80MHz. Pat advises to QRX for LA5KG or ON4UN and listen to their QSOs. He also reckons that the best EU DXers seem to favour a half-wave vertical with ground radials. So if you can plant a 130 odd feet of vertical in your back yard, you're in business. Pat used an Eagle RX60, PR30, a.t.u. and 35ft end fed running N/S, or a 70ft wire running N/E-S/W for s.s.b. sigs from: CN8MN, EA5JK, HK3WO, K1KTH, K2ADY, K3UZE, K4JY, LX1GP, OA8V, OJØMR (Market Reef, between Aaland Is. and Sweden), OY2Z, TA3RF, UW9AF, VE1BU, VE3AYS, VO1CC, VS6DO, W1CF, W3AGM, W4OKL, W9WIB, WB2LWH/VP9, YV4UA, 4S7PB.

J. Jackson (Leeds), TCS13, a.t.u. plus "wire in the loft" detected 80 metre s.s.b. from: CN8MN, CR4BC, HK3WO, KV4FZ, OJØMR, TA3RF, UW9AF, VE1AUC, VE2MY, VE3HJ, VO1CV, VP2VI, WA1AIM/P/VO2, W1FZ, W2PV, W4AQW, W5IOU, YV4UA. He also logged YT3OV, a special Yugoslavian station.

Stephen Champion (Herts) has an R1155 with a 60ft end fed. He claims that 80 is packed with EUs but that the DX is there for the patient. Stephen's

best were HK3WO and VK3MV.

Tom Maxwell (Lanarkshire) CR7OA and 18ft end fed had a long, lingering lugfull on fifteen and twenty. Rewards include: CN8MN, CR6IS, CT2AK, EA3JE, IT1TTH, KV4FZ, LX1BA, OK4PI/MM, PY4AS, PY8OL, TF2WLM, TI2JCC, UB9KAG, UNIKAM, VE3GKH, VO9JJ, VP2AA, VR6GX, YV4WT, ZB2BV, ZP5CF, ZS6AJS, 3V8AL, 6Y5GB, 8R1U, 9K2CM, all on 20 s.s.b.

David Robbins (Warwick), CR7OA, 60ft of mains cable "looped vertically up to 20ft." (The Electricity Board shall hear of this!) The following procession passed through the hoop on 15 s.s.b.: CN8HD, CN8HL, CR4BB, CT2AT, HC1MG, IS1LIO, JX3DH, KP4RK, KV4FZ, OJØMR, PY4AKR, TF2WKL, TF3HS, TU2BB, VP2AA, W6-QI, YDK, YWQ, ZFN, FDR, HGU, ZB2BY, ZL3JC, ZS6BRK, 4X4AX, 4X4FC, 4Z4HG, 9H1BL, 9Q5SN, 9X5SP.

N. Richardson (Bucks) CR7OA, PR30, 30ft end fed at 18ft, queries RA3BCF claiming to be in Moscow. His best on ten metres s.s.b. were: CR6LX, KV4AD, UV3DN and ZS6HR.

John Moore (Leicester) is eavesdropping on two metres. A home brew (good lad) G3BKQ f.e.t. convertor into a CR100/2 tuning 24-9-26-9MHz is fed with a 6-element Yagi indoors. (What happens when you want to have a bath, OM?) Signals bearing the a.m. label received from: G3GJY, G3JXN, G3PYG/A (near Sheffield), G8CB, G8BPO, G8BRT/P (near Sheffield), G8BYW/P (Derbyshire). Two independent squeaks of s.s.b. heard from G3OCH and G6NB.

"Tell Glyn Richards he isn't the only 2 metre fan in G.B.," says L. Coombes who lives in Cwmbran. (I don't know either, it's certainly not near St. Albans.) Listening on an Interceptor 1880 raised: G3YRN, G8AFA, G8DCK, GW3IJE, GW5NF, GW8CCA. The antenna is an inverted L about 75ft long.

Quite an active month for contest enthusiasts. March 7-8th BERU contest; 7-8th ARRL phone contest; 21-22nd ARRL c.w. contest; April 5th 80 metre QRP contest.

A special one on March 28-19th April is the IARC propagation research contest, which is a phone only one. Don't forget that it's nearly mobile rally time. The first in my diary is the North Midlands Rally on 19th April. Listen for a talk-in station at all these rallies on topband. For the c.w. types, National Field Day this year will be on the 6-7th of June. Just time to get a bit of practice in on the key. ■

## BINDERS AND INDEX

Don't let your copies of PRACTICAL WIRELESS become torn and dirty: hard-cover binders are available at 14s. 6d. from:


**BINDING SECTION,  
IPC MAGAZINES, LTD.,  
SOUTHAMPTON STREET,  
LONDON, W.C.2.**

Indexes to Vol. 43, 1967-8, are also available at 1s. 6d.

These prices include post and packing.

## MONO TRANSISTOR AMPLIFIER

### HSL.700

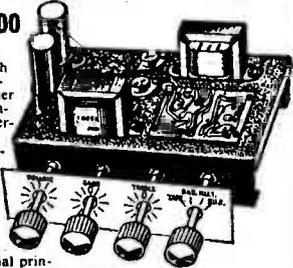

A really high fidelity mono-audio amplifier with performance characteristics to suit the most discriminating listener. A 6 transistor circuit with integrated pre-amplifier assembled on special printed sub panel. AD161-AD162

operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for AC mains 200/240V. Controls: Bass, Treble, Volume/on/off. Function selector for PU, PU2 Tape, Radio. The HSL.700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 9 1/2 x 5 1/2 x 4 1/2 in. high. Sensitivity: PU1-50mV/v. 56K input impedance. PU2-110mV/v. 1 meg input impedance. Tape-110mV/v. 1 meg input impedance. Radio-110mV/v. 1 meg input impedance.

Output power measured at 10Kc-2 watts RMS into 3 ohms. 5.8 watts RMS into 15 ohm. Overall frequency response 30 c/s-18 Kc/s. Continuously variable tone controls: Bass, +8db to -12db at 100c/s. Treble, +10db to -10db at 10Kc/s. The HSL.700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front escutcheon panel, long spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions.

Our Special Price **£719.6** P. & P. 7/6.

### LOUDSPEAKER BARGAINS

3in. 3 ohm 16"/v. & 3in. 3 ohm 27/6. P. & P. 6/-, E.M.I. 8 x 5 in. 3 ohm with high flux magnet 26/-, P. & P. 4/-, E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet 42/- (15 ohm 45/-), P. & P. 6/-. E.M.I. 13 x 8in. 3 or 15 ohm with two inbuilt tweeters and crossover network 4 gns. P. & P. 6/-  
**BRAND NEW, 12in. 15w. H/D Speakers, 3 or 15 ohms.** Current production by well-known British maker. Now with Hifux ceramic ferrobar magnet assembly £5.10.0. P. & P. 7/6  
**Guitar models:** 25w. £6.0.0. 35w. £8.0.0. E.M.I. 34in. **HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each: 15 ohms 18/6 each. P. & P. 2/6.  
**12in. "RA" TWIN CONE LOUDSPEAKER.** 10 watts peak handling. 3 or 15 ohm 37/6. P. & P. 6/-  
**35 OHM SPEAKERS** P. & P. 1/6  
**3in. 14/-, P. & P. 18/6**  
**8 OHM MOVING COIL SPEAKERS**  
**High Flux Magnet.** 2in. dia. 12/- each. P. & P. 1/6.

### BALANCED ARMATURE EARPHONE

Approx 70 ohm impedance. Can be used as ultra sensitive mike or speaker. ONLY 3/6. P. & P. 1/6.  
**CRYSTAL MIKES.** High imp. for desk or hand use. High sensitivity. P. & P. 1/6  
**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE 21/-, P. & P. 1/6.  
**HIGH IMPEDANCE DYNAMIC STICK MIKES.** High sensitivity. 39/6. P. & P. 2/6.

### PYE MICROSWITCHES S/P. C/O.

Lever roller action Rating 250v. AC at 5 amps. Size approx 1 x 3 x 4in. 4/- each. P. & P. 6 or more post free).  
**HONEYWELL MICROSWITCHES S/P. C/O.** Push button action. Rating 250v. AC at 15 amps. Size approx 1 1/2 x 3 x 4in. 5/- each. P. & P. 1/6 (6 or more post free).

### TELESCOPIC AERIALS WITH SWIVEL JOINT.

Can be angled and rotated in any direction. 12 section Heavy Chrome. Extends from 7in. to approx. 5 1/2 in. Maximum diameter 7in. 10/- each. P. & P. 1/6. 6 section Lacquered Brass. Extends from 6in. to 22 1/2 in. approx. Maximum diameter 7in. 5/- each. P. & P. 1/6.

### BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.

Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60 half wave at 1 amp. or 10-0-10-20-20-0-30-30v. at 2 amps full wave. Size 3in. long x 3 1/2 in. wide x 3in. deep. P. & P. 3/6.  
**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. 11/-, P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/6. P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 12/6. P. & P. 2/6.  
**BRAND NEW! PARMEKO MAINS TRANSFORMERS.** Primary 110v-250v. Secondary 330-0-330v. 100mA and 6.3v. at 2 amps. 6.3v. at 2 amps and 6.3v. at 1 amp. Conservatively rated. Fully impregnated Electrostatic screen. Suitable for vertical or drop through mounting. Overall size 4 1/2 x 3 1/2 x 3 1/2 in. Weight 8lb. Limited number only at 37/6. P. & P. 8/-  
**HIGH GRADE L.A.M.I.N.A.T.E. BOARDS** 8 x 6 x 1/4 in. Lined for 10/-, P. & P. 2/-

## SPECIAL OFFER!!

Your opportunity to acquire a first class HI-FI LOUDSPEAKER SYSTEM at an extremely moderate price!

Beautifully made teak finish enclosure with most attractive Tygan front. Size 16 1/2" high x 10 1/2" wide x 6 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 3" bass unit, two 10c.F. tweeter units and a crossover. Power handling 10 watts. Available 3 or 15 ohm impedance.

**OUR PRICE WHILE LIMITED STOCKS LAST 8 GNS**  
 Carriage 10/-

## TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp. with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speaker from 3 to 15 ohms. Compact design. All parts supplied including drilled metal work. Kit-Cir board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response ±3dB. 20-20,000 c/s. Bass boost approx. 10 to +12dB. Treble cut approx. 10 to -16dB. Negative feedback 18dB over main amp. Power requirements 25V at 6 amp.  
**PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0.** All Post Free.  
 Also available STEREO 10+10. As above but 10 watts per channel. **PRICES: AMPLIFIER KIT £12; POWER PACK KIT £3.10.0.**

Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.).

### Official stockists of all PEAK SOUND HI-FI EQUIPMENT

including the P.W. DOLBY 12 STEREO AMPLIFIER as featured in Practical Wireless April, May and June issues. Component pack as specified. Total cost £23.5.6 Plus P. & P. 1/6. (Excluding metalwork, knobs, plugs and sockets and fuses).

### SPECIAL PURCHASE!

**E.M.I. 4-SPEED PLAYER**  
 Heavy 8 1/2 in. metal turntable. Low flutter performance 200/2500. Shaded motor (90v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with 1/0 styli for LP/78. ONLY 63/-, P. & P. 6/6.

### QUALITY RECORD PLAYER AMPLIFIER MKII

A top quality record player amplifier employing heavy duty double wound mains transformer. ECC83, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE 75/-, P. & P. 6/-  
**ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6  
**DELUXE QUALITY PORTABLE R/P CABINET MKII.** Uncut motor board size 14 1/2 x 12in. clearance 2in. below. 5 1/2 in. above. Will take above amplifier and any B.S.R. or CARARAC changer. or Single player device AT60 and SP25. Size 18 x 15 x 6in. PRICE 79/6. P. & P. 9/6.


### 3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis. Size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc. wired and tested for only £4.15.0. P. & P. 6/-  
**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-

**BRAND NEW TRANSISTOR BARGAINS, GET 15 (Matched Pair) 15/-; V15/10 10/-; OC71 5/-; OC76 6/-; AF117 3/6; 2G339 (NPN) 3/-.**  
 Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 25/-; ORP12 Cadomium Sulphide Cells 10/6. All post free.  
**VYNAIR and REXINE SPEAKER AND CABINET FABRICS.** Approx. 5 1/2 in. wide. Usually 35/- yard. **OUR PRICE 15/-** per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

**POWERFUL COMPACT Motor for 6-9v.** Battery operation approx. 25 mA. Made originally for "Staar" and "Greeneco" record player decks. Built in constant speed device. Ideal for models. Overall size approx. 1 1/4 x 1 1/4 x 7/8 each. P. & P. 1/6 (3 or more Post Free).

## DE LUXE STEREO AMPLIFIER

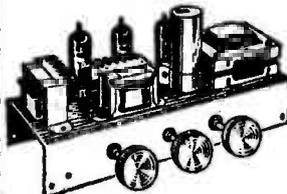

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving quiet smoothing with negligible hum.

Valve line up:- 2 x ECL86 Triode Pentodes. 1 x E280 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dust valve control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. **PRICE 8 gns.** P. & P. 8/-

### 4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. B.S.R. UA25 with latest mono compatible cart. £6.19.6. All plus Carriage and Packing 6/6

**LATEST GARRARD MODELS.** All types available 1025, 2025, SP25, 3000, AT60 etc. Send S.A.E. for latest Prices!

**PLINTH UNITS** cut out for Garrard Models. 1025, 2025, 3000, AT60, SP25. With integrated plastic cover. **OUR PRICE 5 gns.** complete. P. & P. 8/6

**SONOTONE 2539** High output Stereo Cartridge. T/0 stylus for Stereo/LP/78. Complete with universal mounting bracket. List Price 48/7. **OUR PRICE 25/-.** P. & P. 1/6

**SONOTONE 9TAHC** compatible Stereo Cartridge with diamond stylus 50/6. P. & P. 1/6

**AC128D RONETTE T/0 STEREO/COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. 32/6. P. & P. 2/-  
**LATEST RONETTE T/0 MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only 30/-, P. & P. 2/-

### HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

Type TA1  
 ● Peak output in excess of 1 1/2 watts  
 ● All standard British components  
 ● Built on printed circuit panel size 6 x 3in.  
 ● Generous size Driver and Output Transformers.  
 ● Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (GET114 or S1 Mullard AC128D and matched pair AC128 25/-) 9 volt operation. ● Everything supplied, wire, battery clips, solder, etc. ● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately.  
**SPECIAL PRICE 45/-.** P. & P. 3/-  
 Also ready built and tested. 52/6. P. & P. 3/-

### HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer. E280 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3 1/2 in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. **FEW ONLY.**  
**OUR ROCK BOTTOM BARGAIN PRICE 55/-** P. & P. 6/-

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished mono-audio amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate input for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. ONLY £7.9.6. P. & P. 8/6. Also available ready built and tested complete with sid. input sockets. £9.5.0. P. & P. 8/6.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open all day Saturday  
 Early closing Wed. 1 p.m.

**HARVERSON SURPLUS CO. LTD.**


170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 9385

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

A few minutes from South Wimbledon Tube Station.

# FRANCIS OF WOOD GREEN

where the cost of Hi-Fi comes down  
HAVING TROUBLE GETTING THE  
RIGHT PLUG?

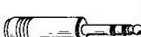- |  |                                   |       |   |
|--|-----------------------------------|-------|---|
|  | Pack 107 5 Pin Din .....          | 4/-d. |  |
|  | Pack 108 3 Pin Din .....          | 3/6d. |  |
|  | Pack 135 1/2 Jack .....           | 5/-d. |  |
|  | Pack 130 1/2 Jack Stereo .....    | 9/6d. |  |
|  | Pack 103 Loudspeaker Plug .....   | 3/-d. |  |
|  | Pack 100 Phono Plug .....         | 1/3d. |  |
|  | Pack 230 3 pin Socket .....       | 4/6d. |  |
|  | Pack 236 5 pin Socket .....       | 6/-d. |  |
|  | Pack 234 Loudspeaker Socket ..... | 6/-d. |   |
- Special express delivery service 6d. per unit postage.  
Send S.A.E. for complete list of plugs, sockets,  
drive belts, ready-made leads etc.



**GARRARD SP25 Mark II**  
Single record playing unit.  
Features include cue and pause  
and automatic pick-up return and  
switch off.

**£11.9.6** plus 10/-  
carriage

Wired with mains cable and 5ft.  
twin screened stereo cable,  
5 pin plug. 10/6 extra.

AP75 Complete with base and  
cover £25 plus 15/- extra.




**E.M.I. 20W MATCHED  
SPEAKER SET 305**

recommended £12.0.0  
our price

**£6.19.6**

plus 7/6 post, packing.

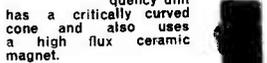13.5" x 8.125" elliptical  
woofer coupled to a  
coaxially mounted  
3.125" high frequency  
choke and condenser  
dividing network. The  
high fre-  
quency unit  
has a critically curved  
cone and also uses  
a high flux ceramic  
magnet.



**ALSO  
E.M.I. 450 SPEAKER**  
our price **65/-** plus 7/6  
carriage

**PLINTH AND COVER** unbeatable value

Suitable for AT60; SP25; 3000;  
2500; 3500. Superb finish.  
Spindle can be left in position  
with cover on. Cover of natural  
smoke tint perspex.  
Also available for AP75; SL99;  
SL75 £6.17.6 plus 10/- carr.

**95/-**

plus 10/- p.p

**REPLACEMENT STEREO  
DIAMOND STYLI**

8TA 9TA 9TAHC all at  
GP91 ST4 ST9 **15/-**  
EV26 GC8 each  
others on request p.p. 1/6

**COUNTDOWN  
SPEAKER**

teak cabinet

**£12** insurance  
& carr. 7/6

A speaker of  
outstanding speci-  
fications and  
technical merit.  
Solid teak cabinet size: 14" x 10"  
x 6". Originally designed for use  
with our Countdown stereo  
budget system but now available  
separately.



**CASSETTE  
HEAD  
CLEANER**

**11/3** Plus  
2/6  
p & p

Removes de-  
posits from  
the recording head with  
a non-abrasive polishing action. Fits  
all compact cassette recorders and  
playback units



**SONOTONE CARTRIDGES**

(Fitted diamond styli)  
Ceramic. (list price  
82/-)

Sensitivity: 9TA **47/6**  
80mV 9TAHC 55mV/  
cm/sec rms minimum plus

at 45° at 1,000Hz measured 2/6 p. & p.  
on Decca SXL2057

**RONETTE 105 STEREO CARTRIDGE**  
Saphire (78) Diamond (LP) **25/-** p & p  
Recommended price **£3.15.0.**

**ARENA F210 AMPLIFIER** £28 plus 10/-  
Normally £36.15.0. Our price

A smart purpose built and decor styled all-  
round monaural/stereo amplifier constructed  
in accordance with the Arena modular system.  
ARENA F211 Tuner. Stereo Decoded tuner available  
at £36 plus 10/- p. & p.



**MAGNETIC (Diamond styli)  
CARTRIDGE** Our price

Today's value **£8. 95/-**  
Stylius replace-  
ment is simple plus  
and can be car- 2/6 p & p  
ried out without removing  
the cartridge. Fully guar-  
anteed.



**NAGRA**

We are the  
specialists  
for this—"The  
finest portable tape  
recorder in the world".

**J. J. FRANCIS**  
(WOOD GREEN) LTD  
123 ALEXANDRA ROAD, HORNSEY,  
LONDON, N.8. Tel: 01-888 1662

ERSIN



5 CORE SOLDER

**for fast, easy,  
reliable soldering**

Contains 5 cores of non-corrosive  
flux, instantly cleaning heavily  
oxidised surfaces. No extra flux  
required.

**SAVBIT ALLOY  
ALSO REDUCES  
COPPER BIT WEAR.**

Economically packed for  
general electrical  
and electronic  
soldering. 75ft.  
18 gauge on  
plastic reel.  
Recommended  
retail price 15/-



**THIN GAUGE  
SOLDER,  
ESSENTIAL FOR**

soldering small components  
and thin wires. High tin  
content, low  
melting point,  
60/40 alloy, 170ft.  
22 gauge on  
plastic reel.  
Recommended  
retail price 15/-



**A RANGE OF  
SOLDERS IN HANDY  
DISPENSERS.**

REF. ALLOY SWG

4A	60/40	18	3/-*
Size 5			
(Il-	Savbit	18	3/-*
ustra-			
ted)			
15	60/40	22	4/-*

\*Recommended Price



**INVALUABLE FOR STRIPPING  
FLEX, THE NEW AUTOMATIC  
OPENING BIB WIRE STRIPPER  
AND CUTTER,**

easily  
adjustable for all  
standard  
diameters. Plastic  
covered handles  
can also be used  
as wire cutter.  
Recommended  
retail price 8/6

From Electrical and Hardware shops. If unobtainable, write to:  
Multicore Solders Ltd., Hemel Hempstead, Herts.

## YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man  
in every field of Electronics today—both in the U.K. and  
throughout the world. We offer the finest home study  
training for all subjects in radio, television, etc., especially  
for the **CITY & GUILDS EXAMS** (Technicians' Certifi-  
cates); the Grad. Brit. I.E.R. Exam.; the **RADIO  
AMATEUR'S LICENCE**; P.M.G. Certificates; the  
R.T.E.B. Servicing Certificates; etc. Also courses in Tele-  
vision; Transistors; Radar; Computers; Servo-mech-  
anisms; Mathematics and Practical Transistor Radio course  
with equipment. We have **OVER 20 YEARS'** experience  
in teaching radio subjects and an unbroken record of  
exam. successes. We are the only privately run British  
home study College specialising in electronics subjects only.  
Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send **FREE BROCHURE** to

NAME ..... Block

ADDRESS ..... Caps.

Please  
1/70

**BRITISH NATIONAL RADIO SCHOOL**



# FET'S AND THEIR USES

T. SNOWBALL

## PART 2

LAST MONTH THE PARAMETERS OF F.E.T.'S WERE DISCUSSED TOGETHER WITH A TESTER SUITABLE FOR DETERMINING THESE. THE SECOND PART DESCRIBES A NUMBER OF CIRCUITS USING F.E.T.'S.

### F.E.T. CASCADE WITH TRANSISTOR AS A PRE-AMP FOR CRYSTAL OR CERAMIC PICK-UP

A very useful combination that presents a high input impedance and low output impedance suitable for other transistor stages and provides gain is shown in Fig. 7.

The output transistor is set at a collector current of 0.5mA if the output is at plus 8V and  $R_1 + R_2$  is 16k $\Omega$ . As it is a feedback amplifier, putting in a signal of 0.1V means that for the circuit to be satisfied, 0.1V must be fed back to the source from  $R_2$ . If 0.1V occurs across  $R_2$ , then the current change must be  $0.1/R_2$ , and to the voltage across  $R_1 + R_2$  must be  $0.1/R_2 \times (R_1 + R_2)$ ; so this voltage, which is the output voltage, will be  $\frac{R_1 + R_2}{R_2}$  times the input voltage,

or in the other words the gain is  $\frac{R_1 + R_2}{R_2}$  . . . . . (11)

$$\text{Gain} = \frac{15 + 0.68}{0.68} = 20$$

Taking a typical MPF103 with a  $V_p$  of 3V at a bias of 2.5V,  $I_D$  will be about 100 $\mu$ A.  $I_{DSS}$  will be about 3mA. Thus from (3)

$$g_m = \frac{2 \times 3}{3} \left( 1 - \frac{2.5}{3} \right) = 0.34 \text{mA/V}$$

The output impedance will be much lower than in Fig. 6 because the  $g_m$  is multiplied by the transistor gain, say times 50.

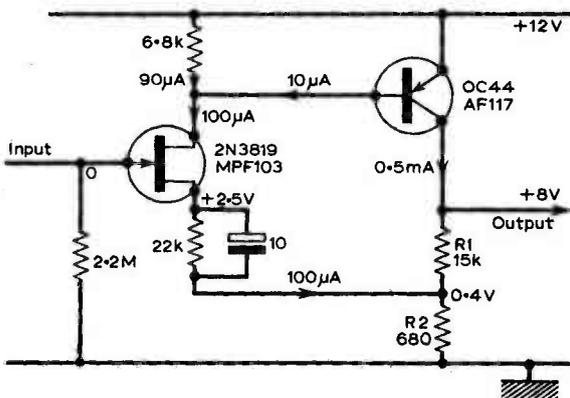


Fig. 7: A high input impedance/low output impedance preamplifier.

$$R_{out} = \frac{15000}{1 + (15 \times 0.34 \times 50)} = \frac{15000}{250} = 60\Omega$$

And input impedance is of course 2.2M $\Omega$ .

At 0.5mA  $I_C$  for the output transistor plus the 0.1mA through the f.e.t. only 0.4V is produced across the 680 $\Omega$  resistor, so the rest of the f.e.t. bias of 2.5V must be made up by a source resistor in the f.e.t. This is 2.1V at 100 $\mu$ A i.e.. approximately 22k $\Omega$  which must be by-passed by a capacitor to prevent negative feedback. The 100 $\mu$ A drain current must not be allowed to go into the transistor base, which with a gain of 50 will only need about 10 $\mu$ A. This gives a value of drain resistor equal to 6.8k $\Omega$  but this may need adjustment to set the output voltage at approximately 8V.

### Hi-Fi- TONE CONTROL

Figure 8 shows a Hi-Fi tone control circuit which gives up to  $\pm 15$ dB of bass and treble control. It is a big improvement over ordinary circuits because most of the capacitors are a tenth of the normal value, these being the most bulky items and so a much smaller unit is possible.

Once again an N-channel f.e.t. is used, source bias is chosen to set the f.e.t. at a low value of  $I_D$  to allow a high drain resistor for good gain. At present N-channel f.e.t.'s are the most common and cheapest. For instance, taking a Newmarket type NKT0213 with a typical  $V_p$  of 1V and  $I_{DSS}$  of 0.4mA, if we bias it at 100 $\mu$ A from equation (2)

$$V_{gs} = 1.0 \left( 1 - \sqrt{\frac{0.1}{0.4}} \right) = 0.5V$$

$$\therefore R_{source} = \frac{V_{GS}}{I_D} = \frac{0.5}{0.1} \approx 4.7k\Omega$$

If the supply voltage is 12V and we let the drain voltage be 3V then  $R_L = \frac{9}{0.1} \approx 82k\Omega$

Then from (3)

$$g_m = \frac{2 \times 0.4}{1} \left( 1 - \frac{0.5}{1} \right) = 0.4 \text{mA/V}$$

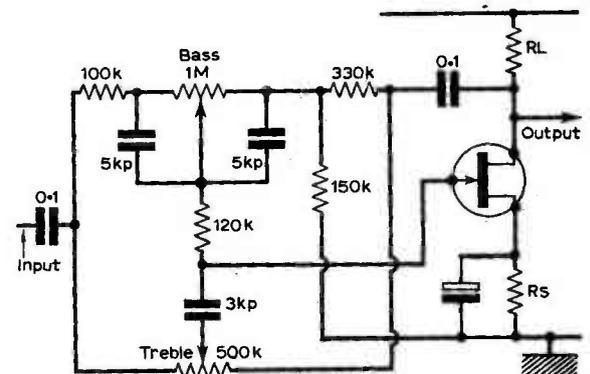


Fig. 8: A hi-fi tone control—see text.

So gain from (7) =  $0.4 \times 82 = 33$

This figure of 33 is the inherent gain of the stage but the feedback tone controls reduce this to a low level at middle frequencies and the gain is used to give the treble and bass boost.

## F.E.T. VOLTMETER

If f.e.t.'s are used to drive a meter, then a voltmeter with a very high input impedance will result.

For instance, Fig. 9 shows a voltmeter with  $20M\Omega$  input impedance on all ranges, using a  $100\mu A$  meter. In this circuit the tester should be used to get two f.e.t.'s matched so that, at the drain current used, the gate bias is within 10 per cent.

Using a 9V battery and a potential divider which sets the gate of the right hand f.e.t. at +3V with respect to the negative terminal of the battery, is the starting point of design.

If 1mA is chosen as a useful operating current, then measuring  $V_{GS}$  on typical Motorola MPF103's will give a bias of about 1V. Thus the sources should sit at about +4V. With the zero set pot. at its mid-position of  $2.5k\Omega$ , then to make 1mA flow the fixed source resistor must be  $1.5k\Omega$ .

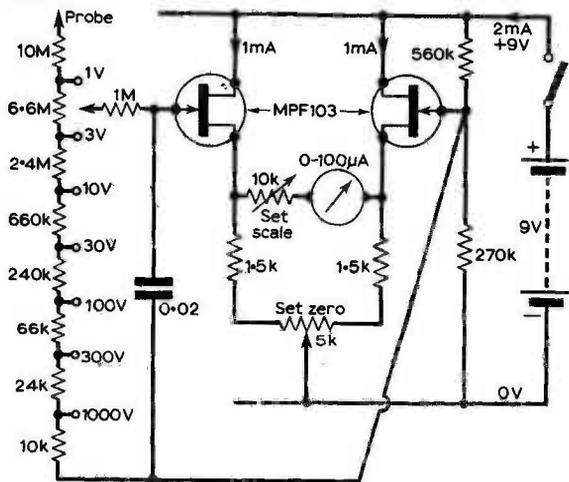


Fig. 9: F.E.T. voltmeter circuit.

These sums shown here are to enable the constructor to redesign the circuit should he not have f.e.t.'s of similar ratings.

Setting-up procedure consists of adjusting the set pot. for zero meter reading with the scale pot. set at zero resistance.

Then apply a known test voltage on the correct range and adjust the scale pot. to correct meter reading; this is a pre-set adjustment and should not require changing again.

This meter drifts very little with temperature, time or battery voltage down to about 6V, due to the long tailed pair circuit configuration.

In passing it should be mentioned that due to the high impedances involved, pick-up can be troublesome and it is suggested that a metal box be used for construction and a screened lead for the probe.

## SENSITIVE F.E.T. MILLIVOLTMETER

If the constructor does not wish to use a sensitive  $100\mu A$  meter or requires greater sensitivity, then the addition of two transistors as amplifiers will allow the use of a 1mA meter with a sensitivity of 30mV f.s.d.

Figure 10 shows such a circuit with an input impedance fixed only by the input attenuator, which can be as high as  $50M\Omega$ .

The circuit will be recognised as a doubling up of Fig. 7 with some extra complications.

The meter used is made up to  $100\Omega$  resistance, which means that 100mV is required to give f.s.d. The  $2.7k\Omega$  and  $1.5k\Omega$  resistors give a gain of 2.8 times but the shunt of  $18k\Omega$  and the gain set pot. means this can be increased and set accurately to times 3.3 so the input signal required for f.s.d. is only 30mV.

This sensitivity can be reduced to read any higher voltage in a similar manner to the earlier circuit. But in order to reduce the effects of amplifier drift, it is recommended that the first set of range switching to say 1V, is carried out by inserting series resistors in the meter circuits. The test meter runs from three 9V batteries and consumes about 6.5mA. The f.e.t.'s can be selected on the meter for matched  $V_{GS}$  at an  $I_D$  of 1mA. The lower f.e.t. is used as a constant current source for the amplifier. If the voltage on the drain of an f.e.t. is varied, then the current through it will not vary by more than a few per cent, as long as the voltage is greater than  $V_p$ . In this case the tester is used to select an f.e.t. with an  $I_{DSS}$  equal to 6mA and it is put in the circuit with  $V_{GS} = 0$ , or simply gate and source strapped together, so now variations of battery voltage will not change the current fed to the amplifier. Should it prove difficult to get an f.e.t. with the correct  $I_{DSS}$ , then select one with greater than 6mA and insert a source resistor as calculated from Fig. 5a to give an  $I_D$  of 6mA.

The transistors should be silicon types but are not critical as regards frequency response.

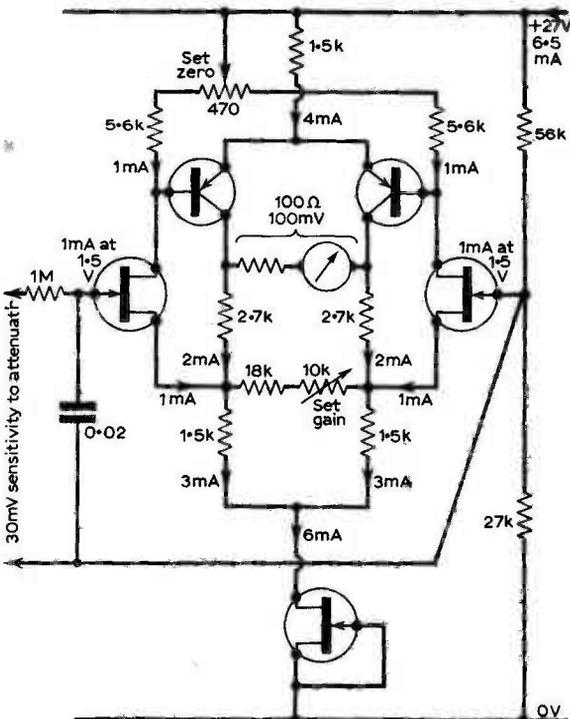


Fig. 10: Circuit for a sensitive f.e.t. voltmeter.

## TAPE PRE-AMPLIFIER

In replaying tapes, the aim of the amplifier is to present a high impedance at least ten times the head reactance and if possible, upon switching on, not

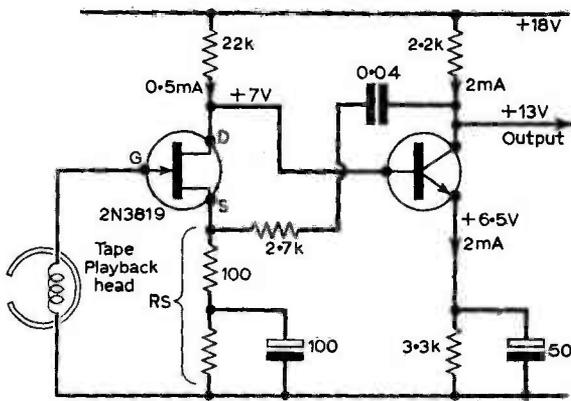


Fig. 11: Tape preamplifier equalised for 3½ i.p.s. The transistor should be shown as a 2N2926.

introduce any capacitor charging currents or d.c. into the head circuit, because these will cause noise to be impressed on the tape.

Most normal transistor circuits inevitably do cause charging currents to flow, however they can be made high impedance enough with some trouble; but an f.e.t. pre-amplifier gets around all these troubles. The tape head can be fed directly into the gate, and so no capacitors are involved; also the high input impedance is unquestioned.

Figure 11 shows a circuit with 120μS equalisation for normal 3½in. recorded tapes.

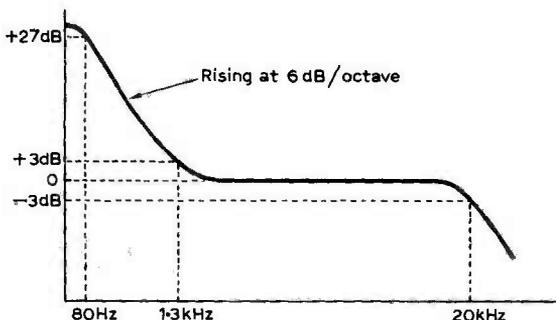


Fig. 12: The equalisation curve used in Fig. 11.

The f.e.t. is run at an  $I_D$  of 0.5mA and  $R_S$  is calculated from the tester measured characteristics as in Fig. 5a. The 2.7kΩ and 100Ω resistors give a medium to high frequency gain of 27 times, while the capacitor in series with the 2.7kΩ gives the low frequency rising characteristic as needed for tape replay, as shown in Fig. 12.

The time constant should be 120μS for normal 3½in. tapes, so with the 2.7kΩ resistor

$$CR = 120 \times 10^{-6}$$

$$\therefore C = \frac{120}{2.7 \times 10^3} \mu F \approx 0.04 \mu F$$

The rest of the voltages and currents as calculated are all shown on the circuit diagram.

## MAGNETIC PICK-UP PRE-AMPLIFIER

Shown in Fig. 13 is a pre-amp for a high fidelity magnetic pick-up cartridge.

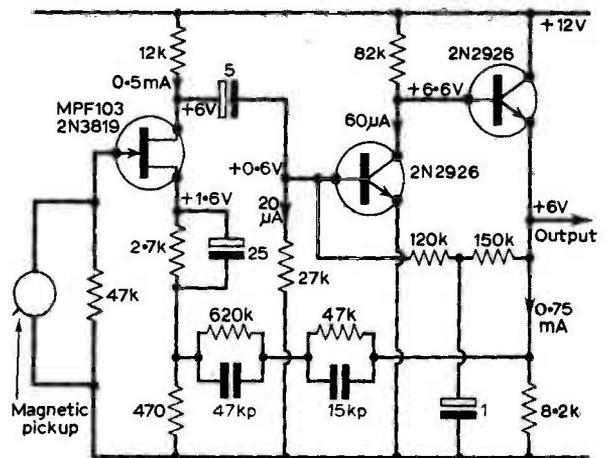


Fig. 13: Preamplifier for a hi-fi magnetic pick-up cartridge.

Here the f.e.t. is used to present a very high input impedance and then a resistor is put across the input to match the pick-up in use. Otherwise with a normal transistor circuit one would have to design a high input impedance, say 100kΩ circuit and then put a resistor in parallel to bring it down to the correct value; this would be all right if the input impedance could be relied upon to stay constant over the audio band and also be constant from unit to unit despite transistor variations; however the f.e.t. overcomes all these problems.

The f.e.t. is biased at 0.5mA as previously discussed, followed by a grounded emitter stage to give some more gain, and an emitter follower to provide low output impedance and to drive the equalisation components which feed back into the source to give the correct play characteristics. The transistor pair are coupled together in a d.c. feedback configuration with the a.c. signal removed by the 1μF capacitor.

The circuit gives a gain of 100 at 1kHz with an output swing of about 2V r.m.s., enough to fully drive any normal power amplifier, response is within ±1dB of the RIAA characteristic from 20Hz to 20kHz. Output impedance is less than 1kΩ.

Design voltages and currents are shown on the circuit diagram.

The previous notes should now have given a good idea of how to use f.e.t.'s to their best advantage, but we finish now with the warning that they are, especially m.o.s.f.e.t.'s, rather fragile as regards stray voltages in handling, and it is recommended that plug-in sockets be used whenever possible and leave the f.e.t.'s out of circuit whenever soldering.

## ARE YOU BUILDING THE P.T.V. SINGLE - STANDARD RECEIVER ?

- ★ Latest Mullard 20in tube
- ★ Stabilised e.h.t.
- ★ Flywheel sync.
- ★ Noise-cancelled sync. separator
- ★ Clamped black level
- ★ Isolated chassis

FULL CONSTRUCTIONAL DETAILS STARTING IN THE MARCH ISSUE OF

**PRACTICAL TELEVISION**  
ON SALE NOW

# AN ELECTRIC THERMOMETER

THE temperature of a piece of intrinsic semiconductor material determines the number of electrons and 'holes' (spaces left in the structure by departed electrons) available for electric conduction. Therefore the resistance of the material depends on temperature. A thermistor is a component consisting simply of two leads joined by a piece of suitable semiconductor material. The instrument to be described measures the temperature-dependent resistance of a thermistor designed specifically for thermometer use and displays the corresponding temperature on a meter. The electric thermometer possesses several features which make it more versatile than the ordinary mercury- or alcohol-in-glass types, viz:

(i) The temperature-sensitive thermistor is connected to the measuring instrument by ordinary twin flex and may be almost any distance from it. This makes the thermometer suitable for many remote temperature sensing applications.

(ii) A meter scale is generally easier to read than the engravings on a glass thermometer.

(iii) The piece of semiconductor material in the specified thermistor is roughly the size of a pinhead. This means that the thermistor has a small heat capacity and can follow a rapidly changing temperature, and that temperature readings can be taken without delay.

(iv) The thermistor is small enough for insertion in many otherwise inaccessible places, although it is rather fragile.

## THERMISTOR

The thermistor specified is a Mullard Varite VA3705 which has a miniature glass bead construction. For general use it can be mounted in a holder made from a hexagonal shape ballpoint pen ('BIC') case (Fig. 1.). The pen cap is used to protect the fragile 'business end' of the thermistor when not in use. Twin flex is connected to the thermistor leads as shown using plastic sleeving to insulate them. This must be done carefully as the leads are fragile. Individual thermistors vary somewhat, but average values of resistance for the VA3705 are:  $6.8\text{k}\Omega$  at  $25^\circ\text{C}$ . ( $77^\circ\text{F}$ .),  $700\Omega$  at  $90^\circ\text{C}$ . ( $194^\circ\text{F}$ .) i.e: resistance decreases with increasing temperature.

## CIRCUIT

The circuit of the thermometer is shown in Fig. 2. B1 and B2 are two small dry cells connected in series to give about 3 volts. Current passes through current limiting resistor R1 and through zener diode D. The zener diode operates in its reverse breakdown condition so that the voltage drop across it is virtually constant (2.4 volts). This ensures the voltage supply to the thermistor is constant in spite of battery wear. The current passing through the thermistor is

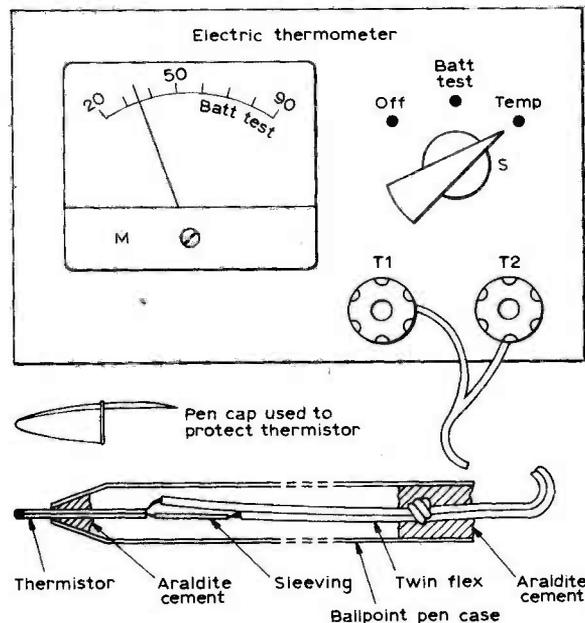


Fig. 1: (top) panel layout (bottom) probe construction

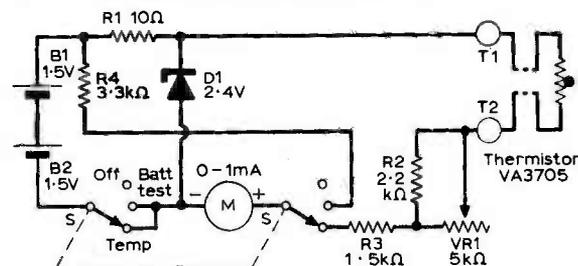


Fig. 2: Circuit of thermometer

measured by meter M which can be directly calibrated in temperature. VR1 is part of the current limiting resistance in series with the thermistor and is preset to give full scale meter deflection (1mA) at 90°C. (194°F.). When S is in the BATT TEST position, the battery voltages under load can be checked on the meter. The dissipation constant of the VA3705 is about 1mW/°C which means that the heating effect of the current passed through it will not introduce an inaccuracy greater than ±1°C.

## CONSTRUCTION

The instrument can be constructed in any convenient cabinet and the few components wired direct. The front panel carries rotary switch S, insulated terminals T1 and T2 and 1mA moving coil meter M, which can be any cheap surplus meter, as large as possible for easy reading. VR1 is mounted inside the cabinet as it only has to be set once; it can be any type of potentiometer, a salvaged volume control from a defunct transistor radio will suffice. The author made a simple holder for the two U12 cells (B1 and B2) from a matchbox, a scrap of metal and two drawing pins (Figs. 3a, 3b).

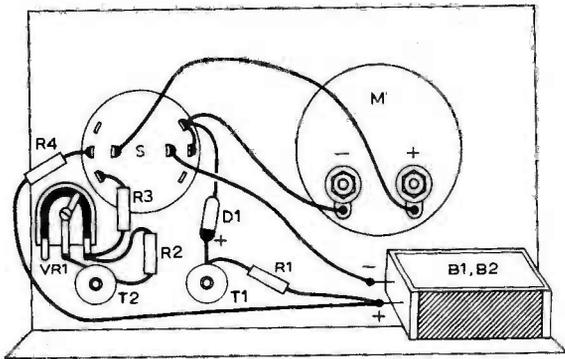


Fig. 3a: Panel wiring

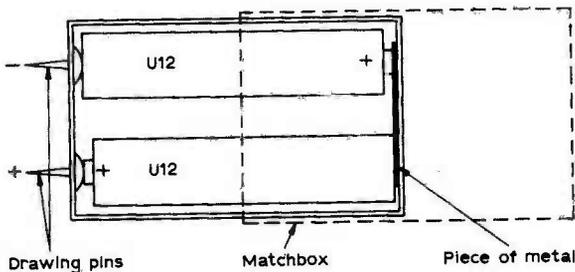


Fig. 3b.: Battery holder

## CALIBRATION

The instrument is easily calibrated using an ordinary mercury thermometer. With VR1 set to maximum resistance, connect the probe to T1 and T2 and place it in water heated to exactly 90°C. (194°F.) as measured with the mercury thermometer. Adjust VR1 for 1mA deflection and use a dab of glue or wax to fix it in this position. Now place the probe in water, cooled to exactly 20°C. (68°F.) and note the meter reading. Now plot these two readings

on a graph (Fig. 4). As the temperature coefficient of the thermistor is linear between these two limits, the two plots have only to be joined by a straight line to provide a complete calibration graph. If a clinical thermometer is available it can be used to provide a third calibration point at 36.7°C. (98°F.).

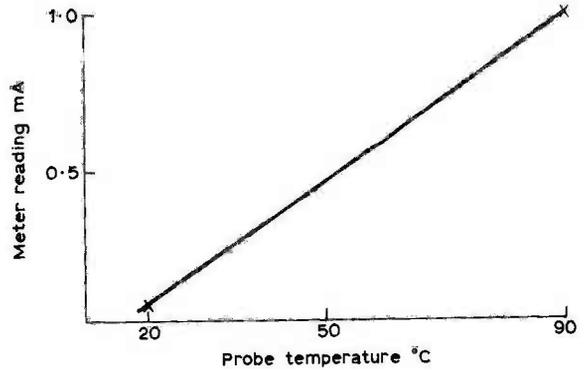


Fig. 4: Construction of graph

## ★ components list

### Resistors:

- R1 10 Ω ½W 10%
- R2 2.2k Ω ½W 10%
- R3 1.5k Ω ½W 10%
- R4 3.3k Ω ½W 10%

D 2.4V 1W zener diode

M 1mA f.s.d. moving coil meter

VR1 5k Ω pre-set pot.

S Two-pole three-way rotary switch

B1, B2 Ever Ready U12 cells

Thermistor Mullard VA3705

The graph can be used to calibrate the meter scale directly, if desired. Open the meter unit carefully and away from dust to avoid damage to the movement. A piece of paper suitably calibrated in degrees centigrade and/or fahrenheit is then slipped under the needle and glued in place. Mark the scale with a green area above 0.80mA. When the needle fails to reach this area on BATT TEST, the batteries should be replaced. If the thermistor is damaged and has to be replaced, the temperature calibration must be repeated.

## USE

The instrument is now complete and will continue to give accurate measurements provided the thermistor temperature does not pass outside the range 20°C. (68°F.) to 90°C. (194°F.). The author's original use for the instrument was measuring transistor heat sink temperatures. Merely touching the probe tip to the heat sink was found to give fairly accurate readings. Overall accuracy of the instrument is better than ±1.5°C. if a good thermometer is used for calibration. The procedures for converting degrees fahrenheit to centigrade and the reverse are as follows: To convert degrees F. to degrees C., subtract 32 from the F. value, multiply by 5 and divide by 9; to convert degrees C. to degrees F., multiply by 9, divide by 5, and then add 32 to the result. Degrees Kelvin or Absolute are degrees centigrade plus 273 degrees. ■

# REPAIRING TRANSISTOR RADIOS

V. CAPEL

## PART 2

**I**N the last part we saw that speed is essential in repairing the cheaper transistor radios if an economic job is to be done. Whatever short cuts may suggest themselves in diagnosis and repair should be used even though these may not always be considered to be good practice with more conventional jobs.

Distortion and no-signal faults were dealt with, but now we will consider the symptom of low sensitivity. Almost any stage could give rise to this, but rarely the output stage as faults here generally produce distortion as well. Before getting too involved though, as with other faults, always check the battery first. Although more usually producing distortion, many modern circuits allow the battery voltage to fall to quite low levels before distortion sets in, but sensitivity is bound to suffer.

A quick check can be made by detuning the set and turning up the volume full. A fairly strong background hiss would suggest that the audio circuits were in order and that the trouble probably lay in an early stage, the mixer or the first i.f. A too silent background would indicate that the fault was in the latter stages.

The most usual causes of low sensitivity are mechanical damage, faulty transistors or mis-alignment. Of the first, a broken ferrite rod is perhaps the most frequent example. A visual examination will soon reveal this. When replacing, make sure that the diameter is the same as well as the length.

In cases where the ferrite rod has broken free from its mounting not only can the fine connecting wires be broken away from the print as described in the previous issue, but the coils themselves can sustain damage. The long-wave coil, being layer wound often suffers with other sharp components digging in and penetrating several layers. This may cause a complete open-circuit or a short-circuit of several turns. This short can be reflected into the medium wave windings and cause low sensitivity on both bands.

Faulty transistors can be diagnosed by voltage readings and shunting a replacement across the suspect as described before. Some idea as to the operation of the i.f. stages can be obtained by detuning each i.f. transformer in turn. There should be a sharp tuning peak in each case with the possible exception of the last one which may be damped by the detector. If it is possible to rotate the core with very little drop in volume, then the associated stage would appear to be faulty. Sometimes a stage may be completely inoperative yet low-volume results can still be obtained due to stray coupling from a preceding stage. Thus the signal 'jumps' the offending stage. Where a good peak is obtained, there is unlikely to be a fault in that part of the circuit. Restore each coil to its correct tuning point before dealing with the next.

Coming back to the ferrite rod aerial again, the

aerial coils may simply be loose on the rod and therefore out of their optimum position. Aligning and sealing will bring back the sensitivity to normal.

Mis-alignment can come about in many ways. Portable radios are obviously subject to more shock and stress than others, hence there is plenty of opportunity for coils to become loose and slip as well as coil cores to turn. If the few quick checks we have outlined here fail to come up with the answer, try re-aligning. Not only may an alignment cure the trouble, but if a circuit fault exists, aligning will often reveal it, as something does not tune up which should do.

Conventional alignment procedure calls for the use of signal generator and output meter, but the simple circuits we are dealing with here do not require these. As we have seen, speed is all important and it is quite possible to do an alignment in just a few minutes without wasting time setting up an array of equipment, by using broadcast signals and the ear. Results are little inferior to those obtained when doing it 'properly', if at all.

## ALIGNMENT

As with more conventional methods, the first step is to align the i.f.'s. A broadcast transmission should be chosen that is weak in order to avoid a.g.c. action, but it should be steady. One of the more distant BBC Home services will usually serve the purpose. Volume should be turned down to a fairly low level as the ear is more sensitive to volume changes at lower levels.

It can be assumed that the i.f. coils are already near the correct i.f. frequency, or perhaps all except one that has been affected by a fault condition which is now cleared. If it is suspected that all or most of the coils are some way out, as would be the case if the receiver had been tampered with, then a signal generator would have to be used to align to the correct i.f. frequency.

Normally though, the broadcast signal can be used. So starting with the last i.f., the cores are tuned for maximum volume. With a weak station there will be a background hiss due to the local oscillator, and as this is steady, it is often easier to listen to this for making the adjustments rather than the programme content which of course will be varying.

In most cases all i.f. coils will be peaked, but there are some that are stagger tuned. These are usually in the better type of receiver, and stagger tuning is rarely if ever found in the types we are discussing. If stagger tuned coils are peaked, then instability will most likely result. The adjustments should be repeated, especially if it was found that one coil was some way out of tune.

Now we come to the oscillator. Circuits differ widely at this point, but with the simpler portable, differences are not so great as to affect alignment much. Most circuits employ a single oscillator coil

### QUICK ALIGNMENT SEQUENCE FOR RADIOS WITHOUT L.W. OSCILLATOR TRIMMER

Tune to:	Adjust:
Weak m.w. station	3rd i.f. transformer for max. volume 2nd i.f. transformer for max. volume 1st i.f. transformer for max. volume then repeat procedure.
Radio 2, 1,500m. Radio 3, 464m. BBC West, 206m. or Radio 1, 247.	Oscillator coil for compromise dial setting Oscillator gang trimmer for correct dial setting then repeat procedure
Weak l.w. station	L.W. aerial coil for max. volume
Radio 3, 464m. or nearby weak station BBC West 206m. or nearby weak station	M.W. aerial coil for max. volume Aerial gang trimmer for max. volume then repeat procedure

### QUICK ALIGNMENT SEQUENCE FOR RADIOS WITH L.W. OSCILLATOR TRIMMER

Tune to:	Adjust:
Weak m.w. station	3rd i.f. transformer for max. volume 2nd i.f. transformer for max. volume 1st i.f. transformer for max. volume then repeat procedure
Radio 3, 464m. BBC West, 206m. or Radio 1, 247m.	Oscillator coil for correct dial setting Oscillator gang trimmer for correct dial setting then repeat both procedures
BBC 2, 1,500m.	L.W. Oscillator trimmer for correct dial setting
Weak l.w. station	L.W. aerial coil for max. volume
BBC 3, 464m. or nearby weak station BBC West, 206m. or nearby weak station	M.W. aerial coil for max. volume Aerial gang trimmer for max. volume then repeat procedure

for both wavebands. As it stands, it works the medium waveband, and for the long waveband an additional capacitor is switched in. In some cases a trimmer is switched in as well, and the alignment procedure depends on whether this trimmer is present or not.

The first thing to do then, is to look for a trimmer apart from the two appearing on the gang tuning capacitor. Sets having a bandspread medium waveband in addition to the normal medium wave, will have extra trimmers in which case they will have to be identified. This can be done by giving each a slight turn back and forth and seeing which band is affected. Oscillator trimmers tune sharply whereas aerial trimmers are flat.

Going back to the straightforward two-waveband job, if the separate long wave trimmer is present, we start with the medium wave. Tune in a station at the low frequency end of the scale (gang at maximum capacitance), the Third programme on 464 metres is suitable. Adjust the oscillator coil core to bring the station to the correct point on the scale. Now tune to the other end of the band and tune in


a suitable station, the West Home Service on 206 metres or Radio One on 247 metres. Adjust the oscillator trimmer on the gang for correct scale calibration. Repeat both adjustments if necessary.

Switching now to the long wave, tune in the Light programme on 1500 metres and adjust the long wave trimmer.

If there is no long wave trimmer, we start on the long wave. Tune in the Light programme and adjust the oscillator coil core to give correct scale reading. Then we switch to the medium wave and check that the Third programme or other station at the l.f. end comes in the right place. If it does not, the coil is adjusted to give a compromise between the two. With this type of set, scale markings are not very precise purposely. Next the h.f. end of the medium wave is aligned using the West programme or Radio One with the oscillator gang trimmer as in the previous case. A check will then have to be made on both l.f. end of medium wave and long wave and a re-adjustment made if needed. In practice, it will be found that the gang trimmer has very little effect on the long waveband.

Finally, the aerial circuits are lined up. Weak stations are best for this, if the ones used for oscillator alignment are weak they can be used, but if not, others nearby should be found. On the long wave, all that is required is to slide the long wave aerial coil (the largest, most likely layer wound) along the ferrite rod for maximum volume. The medium wave is aligned with the medium wave aerial coil at the l.f. end, then the aerial trimmer on the gang capacitor is used to line up the h.f. end. It is useful to remember that with both oscillator and aerial circuits, induction is used to tune the l.f. and capacitance to tune the h.f. end of a waveband.

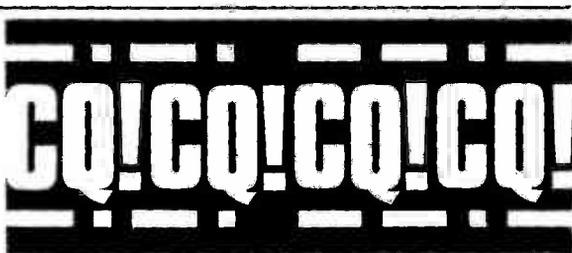
All that is needed now is to seal the coils on the rod by melting wax over them and so complete an economical repair. ■




#### ISSUES WANTED

- ... any issues of P.W. containing circuits, constructional articles on electronic musical instruments, particularly the P.W. Electronic Organ published in the 1950's.—D. E. Bray, 104 Fulmerston Road, Thetford, Norfolk.
- ... October 1966, November 1966 and all the issues of P.W. that had information on the RAE (1964'65).—C. J. Bourne, 111 Woodhouse Lane, Bishop Auckland, Co. Durham.
- ... October 1962 issue of P.W. containing part 2 of the Tudor valve receiver.—M. J. Dorby, 268 Canley Road, Coventry, Warwickshire, CV5 6AP.
- ... the following issues of P.W.: Jan./Dec. inclusive 1964, Jan./Aug. inclusive 1965, Nov./Dec. inclusive 1965, Jan./June inclusive 1966, August 1966. Also the following issues of P.E.: Jan./Oct. inclusive 1966, Dec. 1966, Jan., Feb., April, May and July/Dec. inclusive 1967. All preferably including blueprints.—D. L. Edwards, 18 Parkdale Crescent, Worcester Park, Surrey.
- ... January 1967 issue of P.W. containing Explorer Rx.—S. Marklew, 4A George Street, Worswell, Nr. Barnsley, W. Yorks.
- ... the periodical with the article about the conversion of WS 38 to top band.—Alan Carter, Rosemary, Shakepear Avenue, Langdon Hills, Basildon, Essex.
- ... June 1965 issue of P.W.—N. Taylor, 21 Tower Mill Road, Millfield Estate, Bungay, Suffolk.
- ... April 1966 issue of P.W. dealing with mods to the 19 set.—Thomas Smith, 50b Aldershot Road, Guildford, Surrey.
- ... July 1963 issue of Practical Wireless and the September 1967 issue of Wireless World.—S. Sætheren, Box 336, N-3101 Tonsberg, Norway.
- ... the issue of P.W. containing the article on the Colour Organ.—4269206 S.A.C. Swift D.G., 'B' (S.C.S.) R.A.F. Stanbridge, Leighton Buzzard, Beds.
- ... the issue of P.W. containing E. J. Wotton's t.r.f. receiver. I think it was February 1961.—V. Reed, 25 Aclington, Ashford, Kent.
- ... the issues that covered the article on the 19 set conversion for 1.8 to 2MHz.—B. W. F. Mainprize, Vine Cottage, Exminster, Exeter.
- ... the September 1957 issue of Practical Wireless and the circuit diagram of the 266 indicator unit.—Paul Dorrington, 383 Spen Lane, Leeds, 16, Yorks.
- ... October and November 1964 issues of P.W.—John McGregor, 20 Lorton Close, Mirehouse, Whitehaven, Cumberland.

# F.E.T. PREAMP

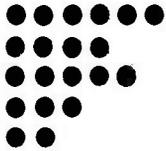

W.T. MORRIS B.Sc., Ph.D.

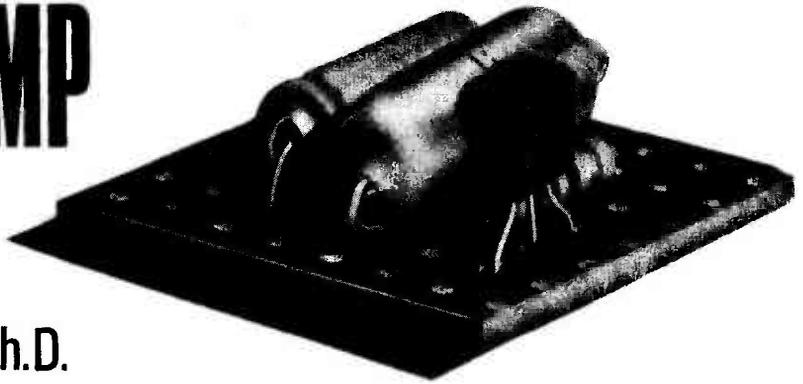

THE matching of ceramic and crystal pickups to transistorised amplifiers often presents a problem to the constructor. The outputs of these transducers, in common with those of crystal microphones, most valve pre-amplifiers and valve f.m. tuners, must be fed into amplifiers with input impedances of  $1M\Omega$  or higher in order to achieve good bass response and a low background noise level. This requirement is easily met with valved amplifiers, but not with most transistorised designs, which have input impedances of a few kilohms only. Remedies such as inserting a high resistance in series with the amplifier input are generally unsatisfactory, since most of the signal is lost, especially the treble frequencies, and the signal to noise ratio is usually very poor.

The achievement of high input resistances with "ordinary" bipolar transistors, even silicon types, demands a fairly complex circuit (see Fig. 1), and even then noise levels can be high, particularly if "cheap" transistors of doubtful origin are used.

Field Effect Transistors (f.e.t.'s) offer an ideal solution to this problem. They have an extremely high input impedance and a very low noise level when driven from a high impedance source such as a ceramic or crystal cartridge. Also, their cost is now low enough to make them a most attractive proposition for the Hi-Fi enthusiast and experimenter. Figure 2 shows a simple circuit using an N-channel f.e.t. Note that this requires a positive voltage supply, like an n-p-n transistor. The input impedance is over  $2M\Omega$ , as recommended by the manufacturers of such cartridges as the "Deram" 9TAHC, CS90 etc. The performance of the circuit is excellent.

The high frequency response extends into the radio-frequency range. (A roll-off at ultrasonic frequencies above 20KHz can be arranged if required simply by adding a resistor R1 of  $330k\Omega$  to  $1M\Omega$  as close as possible to the pre-amp. input). Distortion is very low, rising to one per cent only at signal levels of 1.5V to 2V r.m.s. Noise is so low as to be virtually unmeasurable: this feature alone makes the slight extra cost of f.e.t.'s seem worthwhile!

The output voltage of the pre-amp. is typically nine-tenths of the input, i.e. there is a ten per cent loss of voltage. However, it is *current* gain that we require here, and this is of the order of 1,000 times. In conjunction with the f.e.t. pre-amp., the 300mV maximum output of a typical valve f.m. tuner would appear as about 250mV into the load of  $2k\Omega$  provided by the input of a transistor power amplifier. In other words, the *current* output of the tuner,  $0.3/2 \times 10^6$  amps., i.e.  $0.15\mu A$ , is amplified by the

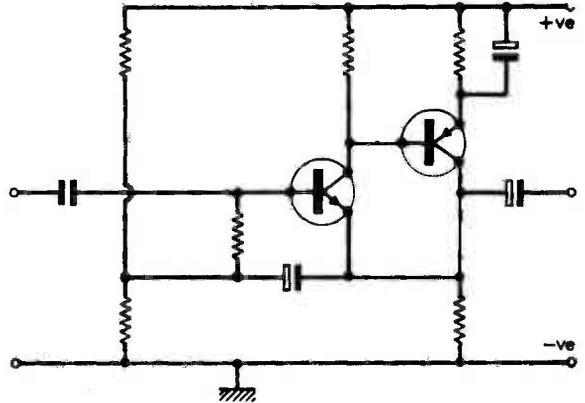


Fig. 1: The circuit configuration necessary for achieving a high impedance using bipolar transistors.

f.e.t. pre-amp. to a current of  $0.25/2 \times 10^8$  amps., i.e.  $0.125mA$ , a current gain of 800 times! Without the aid of the f.e.t. pre-amp., the f.m. tuner could supply only a few millivolts to the power amplifier; bass frequencies would be lost, and there would probably be a high level of background noise.

## CONSTRUCTION

The pre-amp. is readily accommodated on a piece of 0.15in. matrix "Veroboard", 8 holes (about  $1\frac{1}{2}$ ins.) square. Figure 3 gives a convenient layout. Connect the resistors first, then the capacitors, and lastly, the f.e.t. Do not shorten the leads of the transistor, and observe the usual precaution of gripping them with pointed-nosed pliers or crocodile clip while soldering. to avoid overheating the transistor. All connec-

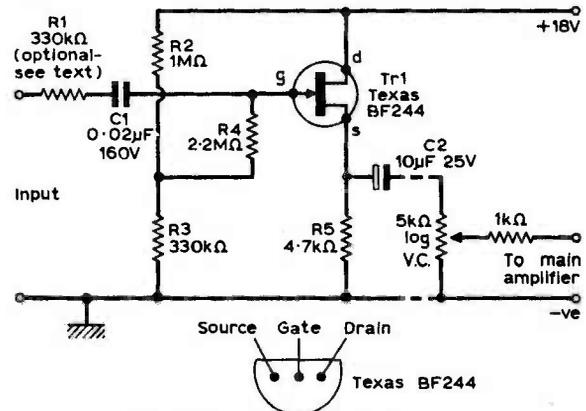


Fig. 2: The circuit of the f.e.t. preamp.

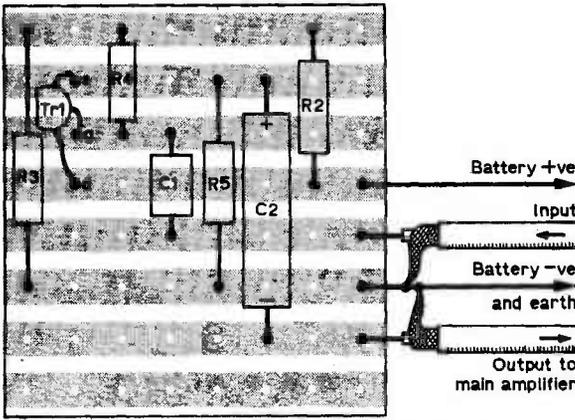


Fig. 3: The component layout on Veroboard.

tions to the pre-amp. can be made using the spare row of holes at the edge of the board remote from the f.e.t., again, of course, completing the job quickly to avoid overheating the components. Note that if an f.e.t. different from the one suggested is tried in the circuit, the base connections may not be in the same order as given in Fig. 2, the correct connections for the particular type must of course be known with certainty if an expensive mistake is to be avoided!

The values of the capacitors are not critical. Any value between  $0.01\mu\text{F}$  and  $0.1\mu\text{F}$  will do for C1: miniature polyester types with voltage ratings of 100V to 400V are especially suitable. C2 should not be less than  $8\mu\text{F}$  to avoid any loss of bass: on the other hand there is nothing to be gained by using values above  $25\mu\text{F}$  for audio signals. A voltage rating of 25V is adequate for C2.

## POWER SUPPLY

A negative-earth power supply of 18V to 24V at 1 to 2mA is required. The exact value of the current drain will depend on the particular f.e.t., but the circuit is designed to compensate to a large extent for transistor variations. Two 9V batteries connected in series can be used, and large types such as the PP9 will have a very long life even when supplying current to a pair of pre-amps. in a stereo set-up. If a mains power pack is used, it must be very well smoothed, and decoupling capacitors of  $1,000\mu\text{F}$  are recommended if the main amplifier's power supply is used. (Before attempting to use the main amplifier's power pack, check that it is of the correct polarity, i.e. it *must* be positive, with the negative line earthed.)

## CONNECTION AND MOUNTING

Input and output connections should be made with screened microphone lead, the input lead being kept short to avoid hum pick-up. The pre-amp. fits


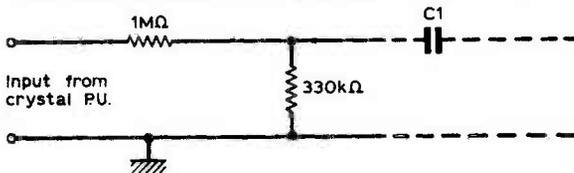


Fig. 4: The circuit of the attenuator necessary when high output cartridges are used. The actual value of the unmarked resistor will depend upon the attenuation required.

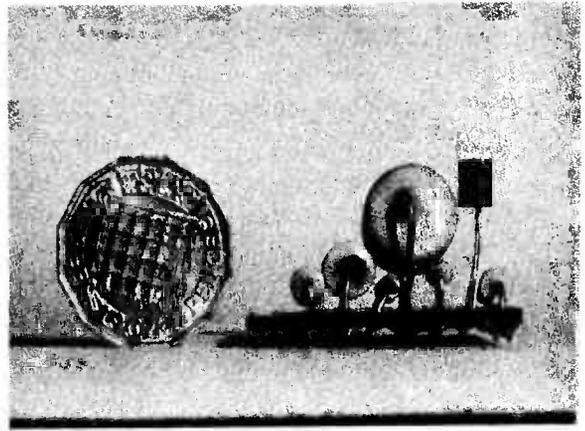

When built on a small piece of Veroboard the complete unit is very small.

neatly into a matchbox, and an ideal mounting position is near the tag-strip under a record-player deck. The output lead can be up to 20ft. long, and likewise there is no restriction on the length of the battery leads. If hum is troublesome, it can usually be cured by wrapping the matchbox in aluminium cooking foil, and earthing the foil.

The circuit given in Fig. 2 will handle signals of at least 1.5V r.m.s., and will therefore accept the outputs of low and medium-output cartridges. Some crystal cartridges, however, give more than 250mV per cm per sec recorded velocity (i.e. maximum outputs of more than 2.5V r.m.s. are possible). In such cases, an attenuator should be fitted as shown in Fig. 4. This will be necessary only if the output of the cartridge is quoted as being 200mV/cm/sec or more. The use of a volume control, a 1 or  $2\text{M}\Omega$  log. potentiometer, across the input is also possible: if this is done the pre-amp. must be positioned as close to the volume control as possible to minimise loss of treble frequencies. It is normally preferable to place the volume control across the output of the pre-amp., i.e. across the input of the power amplifier, a 5 or  $10\text{k}\Omega$  log. potentiometer being suitable.

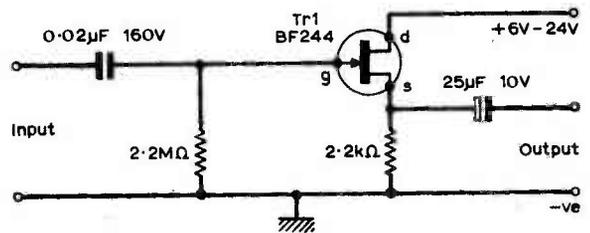


Fig. 5: An even simpler circuit for an f.e.t. preamp.

## A SIMPLER CIRCUIT

The even simpler circuit of Fig. 5 can be used with lower supply voltages, down to 6V if required. However, the current drain varies widely according to the particular f.e.t. sample, and if the current is found to be less than 0.7mA, the attenuator of Fig. 4 will be necessary even with low-output cartridges (50-80mV/cm/sec), though not with f.m. tuners and crystal microphones. The circuit of Fig. 5 is therefore ideal for use with these latter sources, and has the advantage of being insensitive to quite large amounts of ripple on the power supply.

SUMS

plus

CIRCUITS

equals

UNDERSTANDING

# PART 1

LESLIE MOORE

**B**UILDING electronic circuitry can be an extremely interesting and worthwhile past time. The functions of many of these circuits can be explained in simple terms, provided a basic knowledge of component operation has been attained. More complex circuits, however, cannot be described so precisely and an alternative exact method must be found.

Mathematics can provide a means of describing a circuit function, can be used to determine exactly how a circuit will operate under all conditions and must be used in design techniques, again, assuming an understanding of component operation with, of course, the availability of relevant component data.

The aim of this series is to introduce the reader to several basic mathematical theorems and explain the applications of these theorems to electronic circuitry.

## Algebraic Manipulation

One of our aims should be to be able to predict the operation of a circuit given any necessary manufacturer's design data for the components used. A simple example of the use of algebraic manipulation is in the determination of the gain of a thermionic triode amplifier stage, of which a circuit diagram and an equivalent circuit are shown in Fig. 1.1. The equivalent circuit considers the operation of the amplifier under signal conditions. Internal resistances of the h.t. power supply are assumed negligible compared with other resistances in the circuit, hence the effective signal output voltage is developed across  $R_L$ . The value  $r_a$ , or "anode resistance" is the effective resistance of the valve under given bias conditions, and  $\mu$ , or "amplification factor," is the ratio by which the valve will amplify a signal applied to the grid.

Quantities  $r_a$  and  $\mu$  are supplied in manufacturer's data, but they can be measured. Voltage gain of the amplifier,  $A$ , is defined as output voltage,  $V_o$ , divided by input voltage,  $V_g$ , or:-

$$A = \frac{V_o}{V_g}$$

The valve is represented by a voltage generator in the equivalent circuit, producing a voltage of  $\mu V_g$ . Therefore the amplifier output voltage will only be a fraction of  $\mu V_g$ . Considering Kirchoff's law (explained in detail later) which states that the sum of potentials in a circuit is zero, then :

$$-V_a - V_o + \mu V_g = 0$$

$$\text{or } \mu V_g = V_a + V_o \dots \dots \dots (1)$$

This equation is obtained from: the equivalent circuit because of the potential directions (indicated by arrows). A simple rule is :

Follow current direction in the circuit. For all those potential arrows opposing current flow, subtract; for all those in the same direction as the current, add.

From Ohm's Law

$$V_a = i_a r_a \dots \dots \dots (2)$$

$$\text{and } V_o = i_a R_L \dots \dots \dots (3)$$

substitute equations (2) and (3) in equation (1) gives  $\mu V_g = i_a r_a + i_a R_L$

Because both  $r_a$  and  $R_L$  are multiplied by  $i_a$ , this equation may be re-written as

$$\mu V_g = i_a (r_a + R_L) \dots \dots \dots (4)$$

Now, we wish to determine a relationship between  $V_o$  and  $V_g$ .

Equation (3) states that  $V_o = i_a R_L$  and equation (4) states that  $\mu V_g = i_a (r_a + R_L)$ .

To obtain a relationship for  $V_g$  alone, we divide both sides of equation (4) by  $\mu$  to give

$$V_g = \frac{i_a (r_a + R_L)}{\mu} \dots \dots \dots (5)$$

By dividing equation (3) by (5) the required result:

$$\frac{V_o}{V_g} = \frac{i_a R_L \mu}{i_a (r_a + R_L)}$$

or, because the effect of  $i_a$  cancels:-

$$\frac{V_o}{V_g} = \frac{\mu R_L}{r_a + R_L} = A \text{ (Voltage gain of the amplifier)}$$

From the above example it can be seen that algebraic manipulation can be broken down into three parts which are:

- (1) Developing an equivalent circuit to represent a circuit under its working conditions.
- (2) Deriving equations from the equivalent circuit.
- (3) Manipulating the derived quantities into the required form.

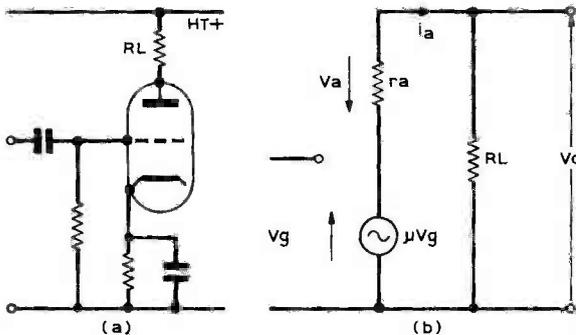


Fig. 1.1 (a) Typical amplifier circuit.  
(b) Equivalent circuit.

Firstly, a familiarity with electronic components and their principles of operation is an important factor. Numerous text books give many standard equivalent circuits, but a good understanding of how these are obtained will prove to be an asset.

Secondly, the derivation of equations from an equivalent circuit requires a knowledge of the more common network theorems, a précis of which is given here:

(1) OHM'S LAW:

The voltage  $V$ , developed across a resistance  $R$ , is directly proportional to the current  $I$ , flowing through that resistance. (see Fig. 1.2).

(2) KIRCHOFF'S LAWS, of which there are two:

(A) The sum of the currents flowing into a junction must equal the currents flowing away from it. (see Fig. 1.3 (a) ).

(B) As before, the total sum of potentials in a circuit is zero. (see Fig. 1.3 (b) ).

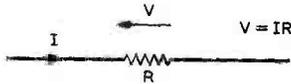


Fig. 1.2: Ohm's Law.

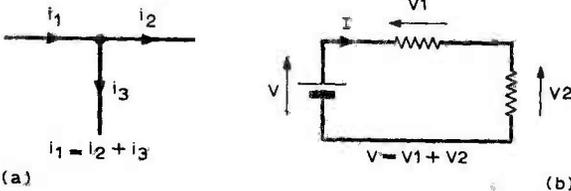


Fig. 1.3: (a) Kirchhoff's Law A.  
(b) Kirchhoff's Law B.

(3) METHOD OF MESH CURRENTS:

Derived from Kirchoff's Laws but, in fact, can provide a simpler solution to complex problems.

(4) THEVENIN'S THEOREM:

This is used for determining the current flowing in a branch of a network and is applied in the following manner:

- Make a break in the branch in question.
- Determine the voltage which would appear across the break.
- Reduce all sources of e.m.f.'s. (or voltages) to zero and replace them by their internal resistances.
- Determine the impedance looking into the break.
- Divide the result of (b) by the result of (d) to give branch current.

An example of the use of Thévenin's Theorem is given in Fig. 1.4.

Example:

Determine the current  $i_2$  shown in Fig. 1.4(a)

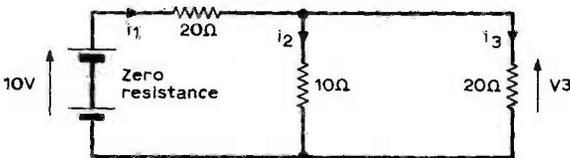


Fig. 1.4: (a) Current  $i_2$  unknown.

Step (a)

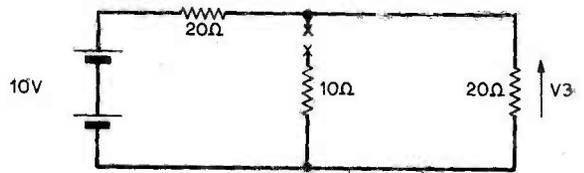


Fig. 1.4: (b) Make a break in the branch.

Step (b) There is now no current in the 10Ω resistor so the voltage looking into the break is equal to  $V_3$

$$V_3 = \frac{20}{20+20} \times 10 \text{ Volts} = 5 \text{ volts.}$$

Step (c)

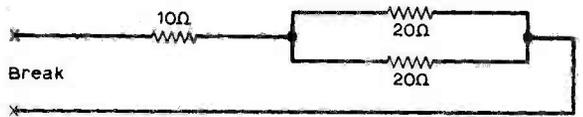


Fig. 1.4: (c) Determine the resistance looking into the break, voltages reduced to zero.

Step (d)

$$\text{Resistance} = 10\Omega + \frac{20 \times 20}{20+20} = 20\Omega$$

Step (e)

$$i_2 = \frac{5}{20} = \frac{1}{4} \text{ Ampere (250mA)}$$

(5) NORTON'S THEOREM

This is similar to Thévenin's Theorem but uses equivalent constant current generators.

Such a list could be used to include many more complex theorems, however, if those mentioned were understood completely they would provide a good background to enable the formation of mathematical equations from circuitry.

Thirdly, the manipulation of equations obtained. This may be broken down into three logical steps:—

- What is the problem, or what is to be found?
- Which pieces of information are required to solve the problem?
- How should the equations be manipulated to give this information?

To demonstrate them consider the further example of a transistor amplifier stage using the standard hybrid parameter equivalent circuit as shown in Fig. (1.5).

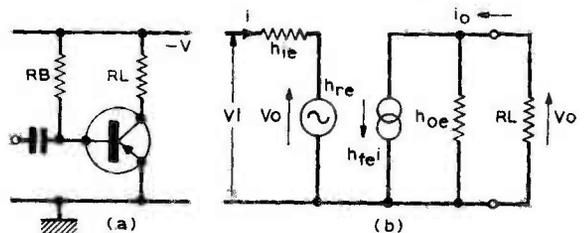


Fig. 1.5 (a) Typical amplifier circuit.  
(b) Equivalent circuit neglecting biasing resistor.

From the equivalent circuit which employs voltage and current generators to represent the inherent characteristics of the transistor, the following equations may be derived.

$$V_i = ih_{ie} + h_{re} V_o \dots\dots\dots(1)$$

$$V_o = -i_o R_L \text{ (due to current direction)} \dots\dots(2)$$

$$i_o = ih_{fe} + V_o h_{oe} \dots\dots\dots(3)$$

Note that the units of  $h_{oe}$  are those for conductance or the inverse of resistance.

Suppose we wish to know the input resistance of the circuit (i.e. at a frequency where capacitive components have negligible reactance to the signal). From Ohm's Law, the input resistance to the circuit is given by the relation:

$$r_i = \frac{V_i}{i}$$

Equation (1) gives an equation containing both  $V_i$  and  $i$ , but  $V_o$  is also present. Therefore we must substitute other quantities to give a relation between input resistance and other circuit constants: From equation (2) we have

$$V_o = -i_o R_L$$

and from equation (3)

$$i_o = h_{fe} i + V_o h_{oe}$$

Substituting for  $i_o$  in (2) gives

$$\begin{aligned} V_o &= -R_L (h_{fe} i + V_o h_{oe}) \\ \therefore V_o (1 - R_L h_{oe}) &= -R_L h_{fe} i \\ \therefore V_o &= \frac{-R_L h_{fe} i}{(1 + R_L h_{oe})} \dots\dots\dots(4) \end{aligned}$$

Substituting equation (4) in equation (1) gives

$$\begin{aligned} V_i &= ih_{ie} - \frac{R_L h_{fe} h_{re} i}{1 + R_L h_{oe}} \\ \therefore V_i &= i \left( h_{ie} - \frac{R_L h_{fe} h_{re}}{1 + R_L h_{oe}} \right) \quad (1) \\ \text{or } \frac{V_i}{i} &= r_i = h_{ie} - \frac{R_L h_{fe} h_{re}}{1 + R_L h_{oe}} \end{aligned}$$

Thus giving the relationship required.

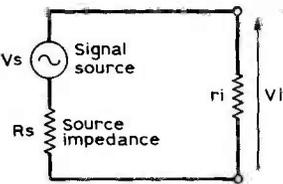


Fig. 1.6: Determination of true input voltage,

Fig. 1.6 shows the importance of being able to determine an amplifier input resistance. All signal sources will have an output impedance which can be represented as a series impedance with the source. The actual amplifier input voltage  $V_i$ , will then be only a fraction of the signal source voltage  $V$ .

Then the amplifier input voltage will be given by:

$$V_i = \frac{r_i}{R_s + r_i} V$$

The usefulness of algebraic manipulation applied to circuits does not end here. It is hoped, however, that these examples have served as a good introduction and that further articles will help give a complete picture of how mathematics can become another tool of the enthusiast.

**TO BE CONTINUED**

# AUDIO LIMITER

**R. F. GRAHAM**

FOR short wave reception and personal listening, headphones are frequently used. The output stage of communications type and other receivers will provide enormously more volume than required, so that almost continuous manipulation of the audio gain control is required. Even then, while tuning or listening, bursts of interference, or powerful transmissions, can be very uncomfortable when searching for weaker signals.

This discomfort, and the need for much adjustment of the receiver volume control, can be eliminated by the audio limiter circuit in Fig. 1. Audio is taken from the usual phone outlet of the receiver.

The series resistor R1 limits power reaching the diodes with very strong signals. The diodes conduct to clip positive and negative audio peaks, the residual amplitude depending largely on the diode resistors R2 and R3. The potentiometer VR1 allows a suitable signal level to be taken off for the phones.

The components may be wired on a small panel, or in a box, with twin leads and a jack plug to provide the audio input from the receiver. The phone jack plug is inserted in a socket on the limiter.

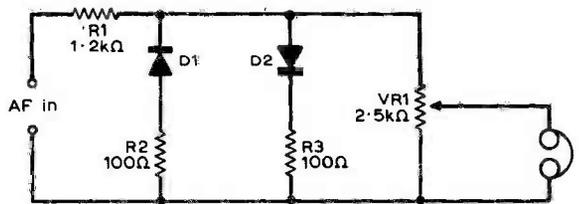


Fig. 1: Limiter for high impedance headphones.

Tune in a signal, adjust the receiver volume control until distortion commences, and turn it back somewhat from this point. VR1 is then adjusted for the required headphone volume. It will then be found that headphone volume does not increase if the receiver gain control is advanced, though there is a deterioration in audio quality due to the clipping action. For most signals the receiver volume control can be left in a suitable middle position, giving enough volume with weak transmissions, without serious loss of quality on strong transmissions. The circuit also limits some types of static and similar interference.

Values in Fig. 1 were for high impedance phones. Values could easily be modified if necessary. D1 and D2 were GD9 or OA91 diodes. Others are suitable.

Where output is taken from an extension circuit attached to the secondary of a speaker transformer, and the speaker is out of use, a 10Ω or similar 1-watt resistor may be connected across the a.f. input points, this provides some loading to reduce a.f. peak voltages in the transformer primary. ■

# LETTERS

The Editor does not necessarily endorse the views expressed by correspondents.

## Space signals

I cannot agree with Mr. R. Hall, Cornwall that we shall not receive signals from other planets. We can, and do receive signals from the planet Jupiter.

Unintelligible signals, but signals nevertheless, which can be picked up on any domestic receiver, which covers the 21 to 14 metres band.

Electrical or magnetic storms in the atmosphere of Jupiter are thought to be the cause of the signals received.

Other rich sources are the Crab Nebula, and the galaxy Andromeda.

The simplest form of radio telescope could be a television set with directional aerial, steerable and used when the local stations are off the air.

For those who would like to take up this absorbing branch of radio, there are excellent text books in your local libraries, giving constructional details of receivers which are quite easy to construct and operate, together with details of galaxies to search, frequencies, etc.

Who knows, some day or night, we may receive the kind of signals, from many light years away, to reawaken us to revise our whole concept of life as we know it.—E. Furlong (*Cheshire*).

## Points of view

After reading the letter in your December issue from Mr. E. W. Baigent on the "old days," I became rather dissatisfied with putting "supplied components into holes in a printed circuit board." It seems that construction today is a rather automatic process—I wonder how many of your readers would ever dream of modifying any of your circuits other than by changing slightly the odd capacitance or resistance value. It seems that individuality is a thing of the past—I am no exception to this.

I find it rather harder to agree with his other points, however. One of the greatest and most constantly overlooked needs in electronics is that of standardisation, ("Practically Wireless" No.

63, December issue). In the case of "c.p.s.," what would that mean to a Frenchman or a German? Once established, the use of a name tends to become international and readily understandable to many more people.

As for the new colour coding, this is another example of international standardisation. The colours now coming into use are of necessity a compromise. Though the use of red for live would have been very desirable from our point of view, quite a large number of Continental firms had until recently been using red for earth! In any case, brown is not very far removed from red, and if we remember that on mains wires, the only two-tone wire is the earth, it takes very little adjustment to adapt ourselves to the new system.

The case for the Hertz is very debatable, I agree, but the new wiring takes into account people's lives, no mean commodity, in this country and abroad; we should be glad to have at last an acceptable compromise, and think before we shout.—A. L. McLeish (*Durham*).

## What, no chips?

Much has been written on the subject of Integrated Circuits (Chips) and I would like to add my own comments.

Having purchased one with the intention of making a record player amplifier, I was amazed at the difficulty of setting it up. One is obliged to experiment with component values and to add this and that to prevent instability. Really, it is reminiscent of tinkering with a regenerative receiver to make it operate correctly!

The small physical size of these chips seems to me to be of no advantage as they need quite a few added external components including large electrolytic capacitors.

Cost-wise too, there is no advantage. For the cost of constructing a 5W mono amplifier using a "chip," I am able to build the P.W. Double 12 in mono which gives 12W (both powers in r.m.s.). I refer to constructing the respective chassis without cabinet

trimmings etc. If the integrated circuit amplifier goes wrong, I have to purchase a new chip but if my P.W. Double 12 packs in, I pay, at the most, a few shillings for a new component.

I do not think "chips" pose any threat to our fascinating hobby and to those constructors like myself, who like to build equipment from scratch.—Frank Casson (*Teesside*).

## No Denial!

Re Mr. R. Hall's letter in the January issue, I well remember that towards the end of the active career of Marconi, the newspapers reported that when he was cruising on his yacht 'Electra' in the Mediterranean, some mysterious long wave signals were being received by him. The reports were really quite reserved. Their general tone was: 'where do the peculiar wireless signals received by Marconi, come from?' A few went further and mentioned the possibility of Mars!

Though Marconi did not actually claim they *did* come from Mars, he in no way said they did not! "He would investigate further."—A. Trowbridge (*Middlesex*).

## PRACTICAL WIRELESS QUERY SERVICE

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

# MEDIUM WAVE DXING

CHARLES MOLLOY

**I**NTEREST has been growing recently in the medium waves. DXers who look for something different, something more exacting or who are simply curious to sample local broadcasting from other parts of the world are turning to the 'broadcast band'. The medium waves do offer a real challenge. In Europe the main problem is interference: several hundred stations broadcast on unauthorised frequencies or use excessive power. Many are on the air 24 hours a day, so the band is never quiet after dark. Directional aerials help to counteract the problem. Loop antennas, based on the frame aerial that was popular in the early days of radio are now standard equipment for the majority of MW DXers. The second problem is knowing the right time to listen. Most parts of the world, with the exception of Australasia, can be logged at some time of the year. The hobby is not seasonal and is not restricted to the winter months. All that is required for success is a path of darkness between transmitter and receiver and of course, favourable propagation conditions. Broadly speaking the best DX to be had in the UK will be trans-equatorial in summer and from the northern hemisphere in winter. The Far East is only heard in winter while stations in East and South Africa are usually only logged in summer. There is no lack of stations, in fact there are many more of them on the medium waves than on all of the Short Wave broadcast bands put together—over 5000 in the United States alone. Canada, United States, Caribbean, Central and South America, Africa, Near East, India, China and Japan, have all been logged on numerous occasions by DXers in this country.

## PROPAGATION

The medium waves are used almost exclusively for local broadcasting, propagation being by ground wave. During the daytime the sky wave is absent since high angle radiation is absorbed by the lowest part of the ionosphere—the 'D' layer. This layer disappears at sunset enabling refraction from higher regions to take place; even vertical radiation is returned. The sky wave interferes with the ground wave to produce severe fading in areas where the two are comparable in strength. As distance increases from a MW transmitter, an area is reached where selective fading and distortion occur after dark limiting the useful night-time range of the transmitter. The ground wave diminishes in strength as the distance from the transmitter increases and finally it disappears. Beyond this point after dark, only the sky wave can be received, we are now out of the normal service range of the transmitter and the signal is becoming DX.

Anti-fading aerials are used by large numbers of medium wave transmitters. This type of aerial, which is a vertical, puts out maximum signal at low angles to the horizon and minimum signal at high angles. The reduction in high angle radiation reduces the amount of sky wave into the service area, con-

sequently fading decreases and the night-time range is extended. Low angle radiation is of great interest to the DXer. It enters the ionosphere at a shallow angle and can travel up to 1500 miles in a single hop after reflection by the 'E' layer. Often it continues for thousands of miles in successive hops when propagation is favourable. Conditions on the medium waves are more variable than on the short waves, a factor which frequently causes disappointment to the newcomer. Persistence and patience are the qualities required of the MW DXer. If you do not hear North America at the first attempt then try again a few days later. If conditions are poor they are unlikely to remain so for long.

## AERIALS

No serious MW DXer would be without a loop (Fig. 1). This type of aerial is directional, maximum pick-up is along the plane of the windings, minimum pick-up is along a line at right angles to the windings. The depth of the null (degree of signal suppression) depends on the electrical balance of the windings so it is important that they should be symmetrical. The loop is very simple to use. Tune in a station on the receiver, peak it with the loop tuning control and rotate the loop for optimum reception. Frequently it is possible to null-out different stations on the same frequency e.g. on 1070kHz CBA in Canada can sometimes be heard free of interference if the null is pointing towards LR1 in Buenos Aires and similarly LR1 can be heard with CBA nulled-out. There are additional benefits to be had from a loop. Static is reduced, in early summer when much of it comes from thunderstorms to the south, it can be eliminated when listening to the west. Overloading and cross-modulation are reduced leading to the unlikely, but quite correct, claim that audio quality is sometimes better when using a loop. Direction finding can be a help to station identification. Turn the loop until the unidentified station disappears, when its direction will be along a line at right angles to the windings. The 40in. loop is a compromise between pick-up and convenience. A larger loop will have greater pick-up. Alternative sizes can be constructed using approx. 100ft. of plastic covered wire of about 22 s.w.g. for the main winding which should be wound to a whole number of turns. If the loop will not tune to the h.f. end of the band there are too many turns. If it will not tune to the l.f. end then add turns or increase the value of the tuning capacitor.

If anyone has space to erect a long wire aerial several wavelengths long he will find it is directional along the length of the wire and the pick-up will be far greater than that of a loop. DXers in New Zealand achieve remarkable results using long wires. Few of us in this country will have the space for this type of aerial and it is doubtful if one would be of value in the presence of strong QRM. No-one should be deterred from DXing on the medium waves through lack of an outside aerial. The

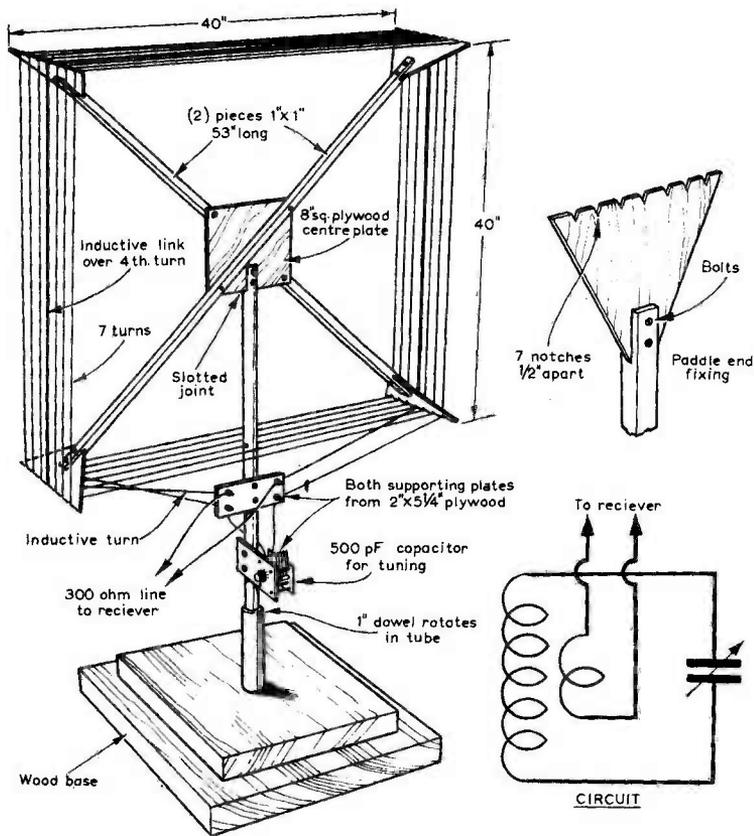


Fig. 1: The loop aerial.

ordinary TV aerial gives excellent results when used in conjunction with a good earth at the receiver. Connect the inner wire of the co-ax downlead to the aerial socket and earth the outer braiding. In some locations better results will be obtained by using the co-ax outer as the aerial.

## DXING

Winter is the time of year for Asiatic stations and there are three periods of the day when reception is possible. The first is in the afternoon from approx. 1500hrs to 1700hrs GMT. Stations heard recently include Taiwan on 750kHz; Bagdad (760); Teheran (895); Iran (985); Anwei, China (940); Peking (1000); Calcutta (1130) in English 1530 to 1600hrs; Philippines (1140); VOA, Okinawa (1178); Korea (1190); Kabul, Afghanistan (1280); China (1290); Teheran (1325); Kuwait (1345). The second period is in the evening from 2000hrs onwards:—Saudi Arabia (588); Jerusalem (677); Aleppo, Syria (746); Amman, Jordan (800); Beirut (836); Bagdad (908); Damascus (957); Diyakir, Turkey (1061); Haifa (1205). The last period is after midnight when stations in India are sometimes logged. The easiest is Rajkot 1070kHz but others have been heard on 910, 1020, 1060, and 1330.

North Americans can be heard throughout the year. In summer those along the east coast of Canada and the United States are audible for an hour before sunrise and are usually free of interference since the greater part of Europe is in daylight at this time. During the winter stations from this area appear regularly after 2300hrs GMT, the time when most Europeans sign-off for the night. If conditions are favourable the following should be heard between 2300hrs and midnight:—WOR (710) and

WINS (1010) in New York City; WHDH (850) Boston; CBH (860) Halifax, Nova Scotia; CJON (930) St John's, Newfoundland; CBA (1070) Moncton, New Brunswick; WBAL Baltimore on 1090. More stations appear as the night progresses but at 0300hrs when Eastern Europeans sign-on QRM starts to become troublesome. The following may be heard during this period—WNBC (660), WABC (770), WCBS (880), WHN (1050), and WNEW (1130) all in New York City; CHER (950) Sydney, N.S.; CHNS (960) Halifax; KDKA (1020) Pittsburg; WOWO (1190) Fort Wayne, Indiana; WKBW (1520) Buffalo N.Y.; WCKY (1530) Cincinnati Ohio.

South American stations are at their best in summer. From June to September (when it is winter in the southern hemisphere) during the two hours before sunrise, look for stations from the deep south and the east of the continent such as CX16 (850) *Radio Carve*, Montevideo Uruguay; PRF4 (940), PRE8 (980) and PRE3 (1180) *Radio Globo*, Rio de Janeiro; PRB9 (1000) *Radio Record* in Sao Paulo; CB106 (1060) *Radio Minería* in Santiago de Chile; OAX41 (1320)

*Radio Cronica* Peru. These are but a few of the stations that can be heard and sometimes they come roaring in, especially the Brazilians.

In winter, the Caribbean area and parts of South America are heard regularly after midnight including YVKS (750) *Radio Caracas* Venezuela; Jamaica also on 750 in English; Georgetown, Guyana (760); PJB (800) Bonaire; WKVM (810) in Spanish, and WBMJ (1190) in English of San Juan, Puerto Rico; *Radio Caribbean* (840) St. Lucia in French; *Radio Belize* (835) British Honduras; LR3 (950) *Radio Belgrano* and LR1 (1070) *Radio el Mundo*, both in Buenos Aires; HJHN (960) Barranquilla, Colombia; PJD2 (1295) St Maartin (in Dutch and English).

During the late evening in winter look for the following West Africans:—Tenerife, Canary Islands on 620 and 894; Monrovia, Liberia (629); *Radio Sahara* (656) in Spanish Sahara; Dakar (764) in Senegal; Luanda, Angola (1088); Conakry, Guinea (1403); Funchal, Madeira (1529). Conakry broadcasts in French and is often quite strong at 2300hrs. In summer, the following have been logged from East and South Africa between 0200 and 0400hrs:—Dar es Salaam, Tanzania (638); Lourenco Marques, Mozambique (917); Kitwe, Zambia (1070); Pretoria (1268); Johannesburg (1286).

Medium wave stations in Europe are spaced 9kHz apart while in other parts of the world, including North America, they are usually on 'channels' 10kHz apart. Co-incidence occurs every 90kHz, namely on 620, 710, 800, 890, 980, 1070, 1160, 1250, 1340, 1430, 1520 and exceptionally, 1570kHz. This set-up is significant; if a European DXer wants to listen to North America he will find it easier if he listens on those sections of the band

—continued on page 965

# radioactivity DETECTOR

L. McNamara



THE high voltage required to operate geiger tubes in portable equipment is usually obtained from h.t. batteries. This article describes a method for operating one of these tubes from a 7.5V battery and eliminates the need for rather large and cumbersome power supplies. The pulses produced by the radioactive particles are heard as "clicks" in the loudspeaker or, if the constructor so wishes, they can be fed into a scaler and counted in this way.

Referring to the circuit diagram, Fig. 1, it can be seen that basically the design consists of a static inverter followed by a voltage doubler circuit to give the high tension required to operate the tube. The inverter is an astable multivibrator with regeneration provided by R3 and R4. The primary of the transformer forms the load for Tr1 and Tr2 while resistors R1 and R2 ensure that the transistor leakage current is kept to a minimum.

For correct operation of the tube 400V is required. If the voltage is too low the tube will fail to trigger when a radioactive particle enters it. If on the other hand it is too high a continuous discharge will take place. To control this voltage a 100Ω pre-set resistor was inserted between one terminal of the battery and the inverter and this can be adjusted to give the correct operating voltage on the tube.

Whenever a radioactive particle enters the tube it ionises some of the gas particles. The negative ions produced in this way will move towards the anode while the positive ions move to the cathode. Some of these charged particles accelerated by the high voltage will collide with other gas molecules causing further ionisation and so a rapid discharge of the tube follows. This pulse is taken from across R5 and fed via C3 to the transistor amplifier. R6 acts as a buffer resistor to limit the current drawn from the geiger tube. If too much current were drawn then the voltage across C2 would drop below 400V with the result that if a number of particles

were to follow in quick succession some would fail to register.

The super alpha pair Tr3 and Tr4 further increase the input impedance of the amplifier and biasing resistors were found to be unnecessary as the input pulse was of a sufficiently high amplitude to bias the transistors on. In the absence of a pulse no current flows through Tr3 and Tr4. Consequently the voltage across R7 will be virtually zero and this ensures that Tr5 is biased off and so no current flows through the loudspeaker. When the tube is triggered the negative going pulse biases Tr3 and Tr4 on, and the current flowing through them causes a voltage drop across R7 which in turn biases Tr5 on and this gives rise to a 'click' in the loudspeaker.

Some constructors may find the pulse amplifier

## ★ components list

### Resistors:

R1	470 Ω	R5	2.2M Ω
R2	470 Ω	R6	330k Ω
R3	2.2k Ω	R7	4.7k Ω
R4	2.2k Ω	VR1	100 Ω preset

### Capacitors:

C1	0.1 μF 250V	C3	0.05 μF 250V
C2	8 μF 450V		

### Semiconductors:

Tr1	2N2926	Tr4	OC81
Tr2	2N2926	Tr5	2N2926
Tr3	OC81	D1, D2	BY100

### Miscellaneous:

Geiger tube type CV2247 (G5H)†; Loudspeaker 30 Ω to 80 Ω type; Transformer type MT98, primary 0-250V, secondary 9.0-9V†; copper laminate printed circuit board etc.

† Available from Henry's Radio Ltd.

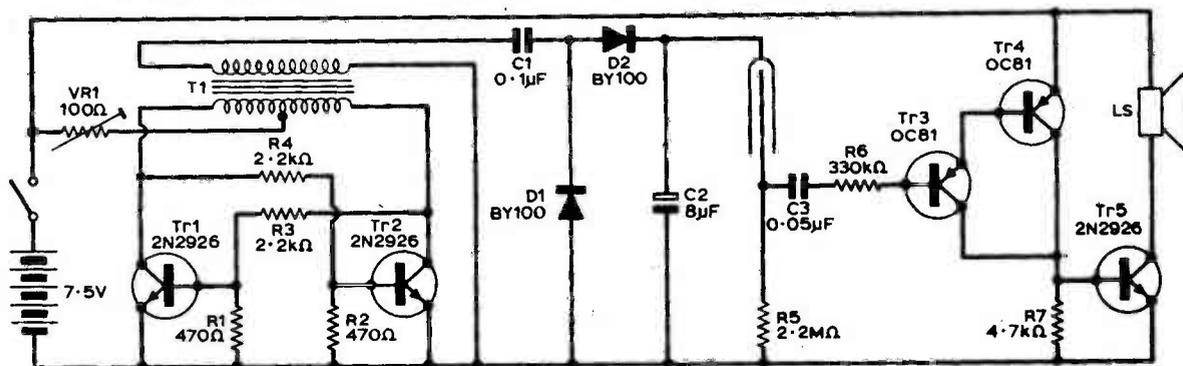


Fig. 1: Circuit of the radioactivity detector.

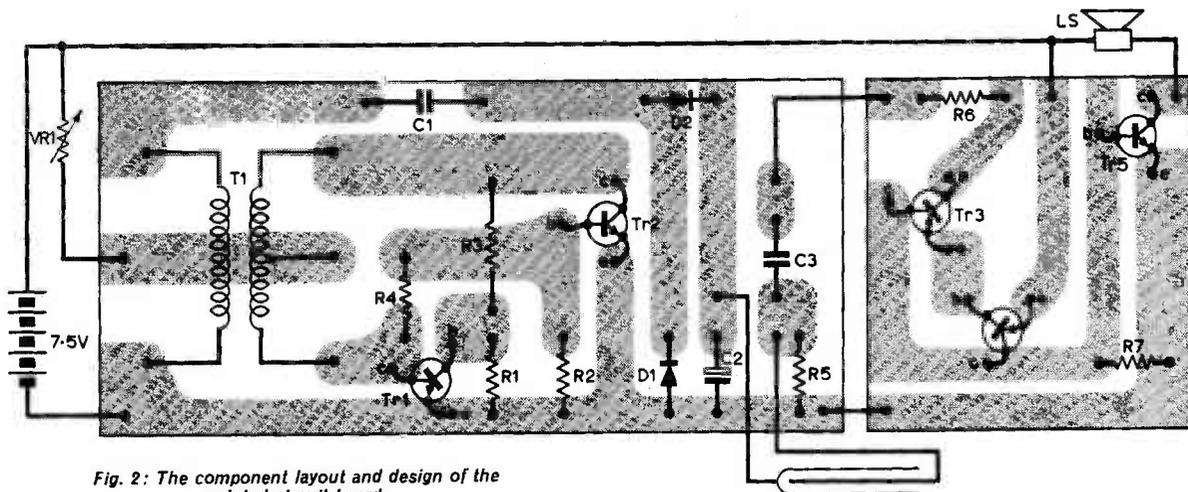


Fig. 2: The component layout and design of the printed circuit board.

unnecessary, especially if they may wish to operate the unit to drive a scaler or an earphone. Consequently the prototype was built on two separate printed circuit boards and Fig. 2 shows the layout pattern which should be painted on a copper laminate board and etched in a solution of ferric chloride.

When the unit is switched on for the first time a

meter should be inserted in the battery leads to monitor the current drawn. It should be in the region of 25mA. VR1 can then be adjusted to give the correct operating voltage. The background radiation with the type of tube specified should give a count of approximately 40 per minute but this will vary considerably depending upon the location. ■

## MEDIUM WAVE DXING

— continued from page 963

where the North American channels are clear of Europeans. For Example, CBA (1070) cannot usually be heard until Paris II signs-off at 2300hrs. On the other hand CJON, St John's Newfoundland on 930kHz can often be heard earlier in the evening since the nearest European frequencies (and QRM) are 926 and 935. Schedules of European stations are important. Many Europeans close down late on Saturday nights but have shorter broadcasting hours on a Sunday. Most, including the BBC, sign-on late on Sunday mornings and many sign-off early on Sunday evenings as well.

DX signals on the medium waves nearly always suffer from slow cyclic fading. The fast fluttery type of fading that can be counted in 'fades per minute' is seldom encountered by the MW DXer. If two stations are heard simultaneously on a channel, it will be found that their relative strengths are changing continually. If the DXer is patient (and lucky) he may hear each station in the clear for a short while during a fade of the other one.

## RECEIVERS

It is not necessary to own an expensive communications receiver to DX on the medium waves, especially if a loop is used. Both the R1155 and the PCR receiver are satisfactory. Good sensitivity and selectivity are desirable but freedom from overloading and cross-modulation are of paramount importance and in this respect oldish ex-service equipment excels. The AR88D and the CR100 are popular with MW DXers in this country. The writer uses a CR100 and a BC314, the latter being an i.f. version of the well known BC312. It covers 150kHz to 1500kHz in 4 bands and the i.f. is only 90kHz which gives good selectivity without a crystal filter. The MN26C is similar and more readily available but unfortunately does not have a tuning scale as it was designed for remote control.

Modern communications receivers perform well on

the medium waves but beware of double or triple conversion as some are prone to spurious on this band. It is not unknown for modern receivers to have their performance degraded on the MWs, probably to make them suitable for entertainment purposes. If in doubt examine the circuitry and look for damping resistors in the r.f. and mixer stages.

When tuning across the band, switch off the a.g.c. otherwise weak stations close to strong ones may be overlooked. In order to protect the ears use an audio limiter of the type connected between the receiver and headphones.

## REFERENCES

There are a number of specialist publications that provide news and information about the MWs. Broadcasting Stations of the World Part 2 published by the US Government Printing Office, Washington D.C. 20402, lists by frequency all broadcasting stations in the range 150kHz to 28MHz except for those in the USA. World Radio and TV Handbook, published annually in Denmark but available in bookshops in the UK, lists MW stations throughout the world as well as containing a mine of information of use to the general DXer. Medium Wave News, the club Magazine of the Medium Wave Circle appears eight times a year and contains recent loggings, station news and information on loops and receivers. Further information can be had from the editor, Ken Brownless, 7 The Avenue, Clifton, York YO3 6AS. For readers in the United States there are the International Radio Club of America, 5421 Clinton Court, Englewood, Colorado 80110 USA and the National Radio Club of America, PO Box 99, Cambridge Mass. 02138 USA. Both clubs specialise in the MWs.

Peak MW DX occurs in years when solar activity is low and since we are currently on a declining part of a sunspot cycle, further outlook is good. Several years of good and improving conditions lie ahead and will no doubt attract many newcomers to the oldest DX band, the medium waves. ■

# WHAT DO YOU KNOW ABOUT METER SHUNTS?

## PART 1

H.A. COLE, C. ENG., M. I. E. R. E.

IT is presumed that many readers could set about calculating separate shunt resistor values for a multi-range milliammeter but one wonders how many could do the same thing for a universal shunt? Where does one start? What value should be chosen for the shunt? And having selected a value, how does one then go about calculating the various sections of the shunt?

This article hopes to clear up these points and enable the reader to calculate both types of shunt.

### The basic ammeter

The great majority of indicating meters used in testmeters are of the moving coil type where a coil of very fine wire is wound over a drum-shaped former and suspended between the poles of a permanent magnet (the pole pieces are specially shaped to fit the contour of the drum). When current is passed through the coil a magnetic field is set up around it which interacts with that from the permanent magnet. The interaction is such that the drum carrying the coil is forced to rotate, hence the name 'moving coil' for this type of meter.

Two small coil springs, one at each end of the drum, provide a partial restraining force against the rotation and hold the drum stationary when the deflecting force produced by the interaction of magnetic fields exactly balances that of the two springs. The springs also serve to conduct the current into and out of the coil. A very thin lightweight pointer is attached to one end of the drum so that it rotates with it, and a graduated scale positioned behind the pointer enables the deflection to be measured.

The amount of coil current required for the pointer to reach full scale deflection (f.s.d.) depends, other factors being equal, upon the number of turns in the coil. A coil with many turns may, for example, require only  $25\mu\text{A}$  for f.s.d., whereas a coil consisting of much fewer turns may require  $10\text{mA}$  or more to produce the same deflection. Meters requiring very little current for f.s.d. are said to have a high sensitivity, whereas those requiring larger currents (about  $1\text{mA}$  or more) are considered to be low sensitivity types. High sensitivity meters e.g.,  $50\mu\text{A}$  f.s.d., have coil resistances of the order of  $1,000\text{--}2,000\Omega$ , whereas low sensitivity types e.g.,  $10\text{mA}$ , are of the order  $50\text{--}100\Omega$ . The difference is in the number of turns and the gauge of wire used in the construction of the moving coil; the thinner the wire and the greater the number of turns, the higher the resistance.

For multi-range testmeter applications of the moving coil meter, it is desirable to be able to use the same basic meter to measure a wide range of currents. To do this one must first select a meter which has an f.s.d. suitable to the smallest range of currents to be covered by the testmeter. For example, if the lowest range on the test-

meter is to be  $0\text{--}100\mu\text{A}$ , then one must use a meter whose f.s.d. is not greater than  $100\mu\text{A}$ . The next step is to provide means for bypassing that portion of the current to be measured which is in excess of the meter f.s.d. For example, for a  $100\mu\text{A}$  meter to indicate  $1\text{mA}$  ( $1,000\mu\text{A}$ ) full scale, it is necessary to by-pass  $900\mu\text{A}$ . By-passing current in this way is called shunting, and is achieved by connecting a resistor of appropriate value in parallel with the meter; such resistors are called *shunts*.

Shunting in practice can be achieved by either of two methods. In the first a separate shunt resistor is used for each current range to be covered by the meter, and the appropriate shunt selected by a switch. In the second method a single shunt resistor is permanently connected across the meter and tapped at intervals along its length so as to provide the required amount of shunting for the ranges to be covered; this form of shunt is known as a *universal shunt*.

### The separate shunt method

Assume a  $50\mu\text{A}$  moving coil meter (a very popular choice) which has a coil resistance of  $1,000\Omega$ , and that this meter is to be used in a testmeter having d.c. ranges of  $0\text{--}200\mu\text{A}$ ;  $0\text{--}1\text{mA}$ ;  $0\text{--}25\text{mA}$ ;  $0\text{--}100\text{mA}$  and  $0\text{--}500\text{mA}$ . For the first range it is necessary to provide a  $150\mu\text{A}$  shunt so that only  $50\mu\text{A}$  is allowed to flow in the meter (remember, ALWAYS ensure that not more than  $50\mu\text{A}$  is allowed to flow in the meter, no matter what range is to be covered.) The required arrangement is shown in Fig. 1. ( $R_s$  is the shunt resistor and  $R_m$  is the meter coil resistance). The total current ( $I_t$ ) applied through the input terminals of the testmeter divides so that  $50\mu\text{A}$  flows in the meter,  $I_m$ , and  $150\mu\text{A}$  flows in the shunt,  $I_s$ . Now to derive a simple but very useful formula which can be used to calculate the value of  $R_s$  for any values of  $I_t$ ,  $I_m$  and  $R_m$ .

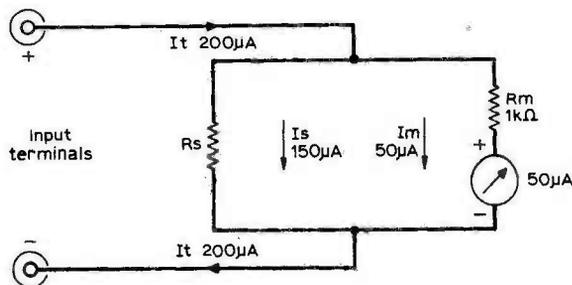


Fig. 1 Simple meter shunt

Referring to Fig. 1, since  $I_m$  flows through  $R_m$  then a voltage ( $V_m$ ) will be developed across  $R_m$  equal to  $I_m \times R_m$  i.e.,

$$V_m = I_m \cdot R_m \text{ (by Ohm's law) } \dots \dots \dots (i)$$

Now, since  $R_s$  is connected in parallel with  $R_m$ , then  $V_m$  must also appear across  $R_s$  and therefore the current in  $R_s = I_s = \frac{V_m}{R_s}$  or, by substituting for  $V_m$  from equation (i),  $I_s = \frac{I_m \cdot R_m}{R_s}$  Transposing for  $R_s$ :

$$R_s = \frac{I_m \cdot R_m}{I_s} \dots \dots \dots (ii)$$

Now, since  $I_s = I_t - I_m$ , one may substitute  $I_t - I_m$  for  $I_s$  so that the equation becomes;  $R_s = \frac{I_m \cdot R_m}{I_t - I_m}$

Now divide top and bottom of this equation by  $I_m$ :

$$R_s = \frac{\frac{I_m}{I_m} \times R_m}{\frac{I_t}{I_m} - \frac{I_m}{I_m}} = \frac{R_m}{\frac{I_t}{I_m} - 1}$$

Finally, since the ratio  $\frac{I_t}{I_m}$  is really the multiplying factor of the f.s.d. of our basic meter, call this factor 'N' and write the equation as:

$$R_s = \frac{R_m}{N - 1} \dots \dots \dots (iii)$$

Now to use this equation to calculate the value of  $R_s$  for the  $105\mu A$  shunt in Fig. 1 (some may prefer to use equation (ii), which is equally valid, by substituting  $I_m = 50\mu A$  and  $I_s = 150\mu A$ ).

Since  $N = \frac{200\mu A}{50\mu A} = 4$ , then  $R_s = \frac{1,000}{4 - 1} = 333\Omega$

Summarising, in order to use the  $50\mu A$  meter to indicate  $200\mu A$  at f.s.d. (range 1), one must provide a shunt resistor ( $R_{s1}$ ) of  $333\Omega$ .

Now consider the requirements of the second range ( $I_{mA}$ ), making use of equation (iii):

$$N = \frac{1mA}{50\mu A} = \frac{1,000\mu A}{50\mu A} = 20$$

$$R_{s2} = \frac{R_m}{N - 1} = \frac{1,000}{20 - 1} = 52.6$$

$$R_{s2} = 52.6\Omega$$

For range 3 (25mA),

$$N = \frac{25mA}{50\mu A} = \frac{25,000\mu A}{50\mu A} = 500$$

$$R_{s3} = \frac{1,000}{500 - 1} = \frac{1,000}{500} = 2 \text{ (ignoring 1 in the denominator because it is so small compared to 500).}$$

$$R_{s3} = 2\Omega$$

For range 4 (100mA),

$$N = \frac{100,000}{50} = 2,000 \text{ and } R_{s4} = \frac{1,000}{2,000} = 0.5$$

$$R_{s4} = 0.5\Omega$$

An important point should be noted at this stage, and that is the fact that since 100mA is 100 times 1mA, then 100 times as much shunt current is required for the 100mA range as was required for the 1mA range. Therefore, since current is inversely proportional to resistance ( $I = V/R$ ), then a 100mA shunt will be 100 times smaller in value than a 1mA shunt. Having already calculated  $R_{s2}$  for 1mA and found it to be  $52.6\Omega$  the value of  $R_{s4}$

for 100mA will be  $\frac{52.6}{100} = 0.526\Omega$  or, approximately

$0.5\Omega$ . This agrees well with the value obtained for  $R_{s4}$  using equation (iii).

Next calculate  $R_{s5}$  for range 5 (500mA) using equation (iii), or determine its value by observing that 500mA is 5 times greater than 100mA, and therefore  $R_{s5}$  (for 500mA) will be 1/5th of the value of  $R_{s4}$  (for 100mA),

i.e.,  $R_{s5}$  for 500mA =  $\frac{0.5}{5} = 0.1\Omega$ . Checking this answer by using equation (iii);  $N = \frac{500,000}{50} = 10,000$ ,

$$\text{therefore } R_s = \frac{1,000}{10,000} = 0.1\Omega.$$

$$R_{s5} = 0.1\Omega.$$

Fig. 2 shows a suitable arrangement for incorporating the shunts just calculated to provide the desired ranges on the testmeter.

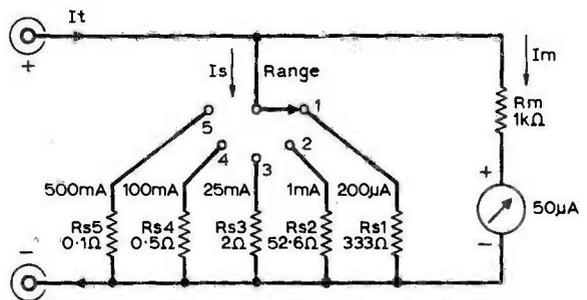


Fig. 2: Final circuit using separate shunts

The big disadvantage with this type of circuit is the contact resistance introduced by the switch. This may not be very important with a new good quality switch but after a period of use the contacts of most switches become dirty causing an increase in the resistance between the contacts, thus introducing measurement errors. The problem is not very important on the lower current ranges because the shunt resistors associated with these ranges are usually so large compared with the contact resistance that its effect may be ignored. On the high-current ranges, however, this is not the case and the contact resistance is comparable in value with that of the shunt (we have just shown that a shunt of only  $0.1\Omega$  is required for the measurement of 500mA).

The problem of contact resistance may be alleviated considerably by artificially increasing the resistance of the meter ( $R_m$ ). From equation (iii), the shunt resistance

is directly proportional to  $R_m$  ( $R_s = \frac{R_m}{N - 1}$ ), so if we

increase the value of  $R_m$  then the value of  $R_s$  can be increased in the same proportion. Achieving this will not only reduce the importance of contact resistance but it will also avoid the need for fractional ohmic values of shunt resistance (it is never a simple matter to produce, or obtain, resistor values of less than  $1\Omega$ ). To illustrate how this can be done, take the same  $50\mu A$ ,  $1,000\Omega$  meter, and deliberately increase its resistance tenfold i.e., make  $R_m = 10k\Omega$ ; by connecting a  $9k\Omega$  resistor in series with it. Now repeat the testmeter design procedure, using equation (iii), for the same current ranges of  $200\mu A$ ; 1mA; 25mA; 100mA and 500mA.

For range 1 (200 $\mu$ A).

$$N = 4, \text{ therefore } R_{s1} = \frac{10,000}{4-1} = 3,333\Omega.$$

$$R_{s1} = 3,330\Omega$$

For range 2 (1mA).

$$N = 20, \text{ therefore } R_{s2} = \frac{10,000}{20-1} = 526\Omega$$

$$R_{s2} = 526\Omega \text{ and so on.}$$

It will be noticed that the values of  $R_{s1}$  and  $R_{s2}$  are now ten times greater than what they were when  $R_m$  was 1,000 $\Omega$ . In other words, multiplying  $R_m$  tenfold has enabled us to multiply the shunt resistor values tenfold also. This means that  $R_{s5}$  for 500mA is now 1 $\Omega$  instead of 0.1 $\Omega$ , and this is a standard value which can be obtained without great difficulty. The same applies to the 100mA range;  $R_{s4}$  is now 5 $\Omega$  instead of 0.5 $\Omega$ , which again is readily obtainable. The values of  $R_{s1}$ — $R_{s5}$  are now large enough, except perhaps for the 500mA range, to make contact resistance of the switch negligible.

All this sounds very convenient, so what are the snags? The big snag is that the effective resistance of the testmeter i.e., the resistance which would be measured between the two input terminals, is now much larger than it previously was, and this resistance may introduce errors into measurements, particularly when measuring large currents derived from low voltages. To demonstrate this, consider the simple circuit shown in Fig. 3.

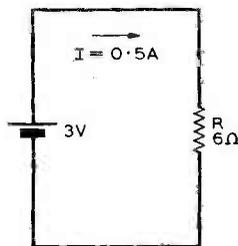


Fig. 3: Simple circuit.

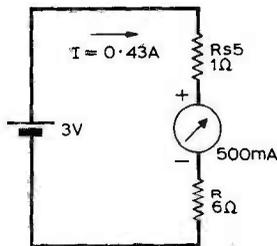


Fig. 4: Effect of adding meter

A 3V battery is connected across a 6 $\Omega$  resistor (this could be a torch bulb, for instance) causing a current of 500mA to flow ( $I = 3V/6\Omega$ ). Now connect the testmeter, switched to the 500mA range, in series with this circuit so as to measure the current flowing and we shall be adding a resistance of about 1 $\Omega$  to the circuit (this is the calculated value of  $R_{s5}$  for 500mA; we can neglect the value of  $R_m$  which is 10k $\Omega$  because it is so large compared with  $R_{s5}$ ). The circuit now appears as shown in Fig. 4 and the current ( $I$ ) now equals

$$\frac{3V}{R_{s5} + R} = \frac{3}{7} = 0.43A \text{ (430mA).}$$

This is the current which will be indicated on the meter, although it is known that the *true* circuit current without the meter in circuit is really 500mA. The presence of the meter has therefore introduced an error of

$$\frac{500-430}{500} \times 100\% = 14\%$$

and this is quite substantial!

Now consider what would happen using the testmeter fitted with the original value of  $R_{s5}$  for 500mA i.e., 0.1 $\Omega$ . The circuit current would now be

$$I = \frac{3V}{6\Omega + 0.1\Omega} \times 10^3 \text{mA} = 491 \text{mA.}$$

## NEXT MONTH IN

# PRACTICAL WIRELESS

### F.M. STEREO DECODER

With the ever increasing interest in the B.B.C.'s stereo broadcasts on the v.h.f. band, it is natural that the demand for stereo equipment is also on the increase. One of the most important items in the stereo set-up is the decoder. The author describes the construction of an inexpensive unit, which nevertheless has an excellent performance. A indicator lamp is included to indicate the presence of a stereo transmission. Full constructional details and wiring diagrams are included.

### AERIALS FOR MOBILES

With that long warm summer to look forward to the mobile enthusiast will be going over his gear to see how he can best improve it after the mediocre results of last season. But whatever the equipment in use it is not much good if the weakest link in the chain, the aerial system, is not up to scratch.

Fred Judd, G2BCX, a very experienced 'mobileer' describes various practical arrangements and methods to ensure that the aerial system is really tuned up 'on the nose'.

### A 3-BAND TRF-4 RECEIVER

Not the usual 3 band set but incorporating band spread coverage of the h.f. end of the medium wave band where the 'pop' stations are to be found, not forgetting the future m.w. local stations, and including the interesting radio amateur's Top Band.

In addition the BBC's Radio 2 service on I.w. plus continuous extended m.w. coverage from 150 to 620m. Full constructional details in the April issue.

### PLUS THE REGULAR FEATURES AND OTHER CONSTRUCTIONAL ARTICLES.

May issue on sale April 3rd. 3/6

The measurement error is now

$$\frac{500-491}{500} \times 100\% = 1.8\%$$

this is still significant but much more acceptable.

The price to pay for high meter resistance is reduced measurement accuracy—especially on the high-current ranges. It is interesting to note here that the AVO model 7, which has a 1mA (effective) indicating meter, is much more suitable for measuring low-voltage high-currents than is the AVO model 8, which has a 50 $\mu$ A (effective) indicating meter. This is because the effective resistance of the model 7 is lower than that of the model 8, due to the lower resistor values used for the current shunts (the 1 amp shunt on the model 7 is about 0.14 $\Omega$ , whereas the equivalent shunt on the model 8 is about 0.5 $\Omega$ .)

TO BE CONTINUED

# 4! brings you a mountain of components at manufacturers' prices

The serious amateur should never be without this comprehensive price list and guide to semiconductors and electronic components from RCA, IR, SGS, Emihus, Semitron, Keyswitch, Plessey, Morganite, Litesold and others (together with manufacturers' application data) which you can buy direct from us at *manufacturers' prices* e.g. **IN914 1/3d.**  
 **IN916 1/11d.**  **2N697 4/5d.**  **2N706 2/3d.**  **2N706A 2/9d.**  **2N929 5/8d.**  
 **2N1613 4/8d.**  **2N3011 9/1d.**  **2N3053 6/2d.**  **2N3055 15/9d.**  **3N140 15/3d.**  **BFY50 4/8d.**  **BFY51 3/9d.**  **BSY27 18/-**  
 **BSY95A 3/3d.**  **C407 4/6d.**  **CA3012 18/3d.**  **CA3014 25/6d.**  **CA3020 25/9d.**  **OA200 1/9d.**  **OA202 1/11d.**



## Build the NEW Mainline Audio Amplifier kits - UP TO 70 WATTS

The result of the combined resources of SGS and RCA, these quasi circuits set new standards in quality and performance. Each kit is complete with circuit diagram, all semiconductors, resistors, capacitors and printed circuit board.

<b>12A</b> .....	<b>£7. 0. 0.</b>
<b>25A</b> .....	<b>£8. 5. 0.</b>
<b>40A</b> .....	<b>£9. 0. 0.</b>
<b>70A</b> .....	<b>£10.10. 0.</b>

Any two will make an outstanding stereo equipment.



To: Mainline Electronics Limited, Thames Avenue, Windsor, Berkshire

- I enclose 4/-. Please send me your price list and guide   
 I am interested in ..... Amp Mainline Audio Amplifier Kits. Please send me full data   
 I am interested in receiving data on preamplifier & power supply kits

NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_

(A member of the ECS Group of Companies)

PW4/70

# TAKE 20

JULIAN ANDERSON

**A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build.**

**A**SSUMING that the reader has a multimeter, this month's project should cost no more than five shillings since it consists simply of a single transistor with no associated components "pepping up" the performance of the resistance range on a multimeter.

Lie detectors are not very accurate pieces of equipment but they do work in a vague sort of way using a very simple principle and they provide endless hours of fun. The principle of simple lie detectors is that the skin resistance of a person varies with changes of emotion. These changes can easily be measured and are surprisingly rapid especially when the emotion is fear.

Many readers will know that a reading of skin resistance can be obtained using the high resistance range on a multimeter simply by holding the probes, one in each hand. The actual resistance varies enormously—between about 20k $\Omega$  and 300k $\Omega$  but under most conditions the resistance is between 100k $\Omega$  and 250k $\Omega$ . Cheaper multimeters will certainly show a reading for this sort of resistance but it will almost certainly be at the extreme end of the scale and to observe changes of about 5 per cent is very hard.

It is however very easy to increase the sensitivity of the meter just by connecting a transistor's collector and emitter to the meter and taking the probes from the base and collector. The battery inside the meter (1.5V in most cases with additional 9V or 15V ones in the better types) provides the supply voltage and it will quickly be seen from Fig. 1 that a very high resistance in the base-collector circuit of the transistor brings about a greater current flow through the meter and thus effectively registers a lower resistance. Note that the positive connection to a meter is actually the negative connection to the battery and so the connections to the transistor are made in what appears to be the wrong way around.

A silicon n-p-n transistor should be used (so here the meter positive lead goes to the emitter) and a 2N2926, BC109 or BC169 or any similar type is ideal. These transistors have very low leakage and very high gain and will bring the meter reading to the centre portion of the scale.

The same circuit is also applicable for measuring very high resistances or checking insulation. Using the circuit shown most meters will give a decent reading for 20M $\Omega$ —something quite outside the scope of most meters. Your scale will of course bear no relationship to the resistance being measured but it is a relatively easy matter to plot points on a graph using known resistances for calibration.

The transistor itself should be mounted on solder tags fixed to a small panel of perspex or polythene. The resistance of wood or similar sorts of material

## No. 12 LIE DETECTOR

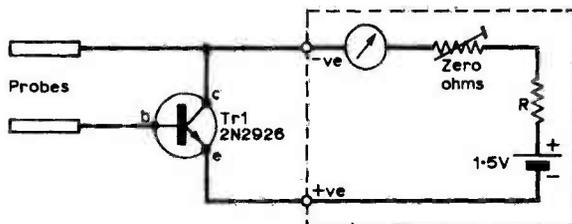


Fig. 1: The circuit of the lie detector. The components inside the dotted line are those within the multimeter itself.

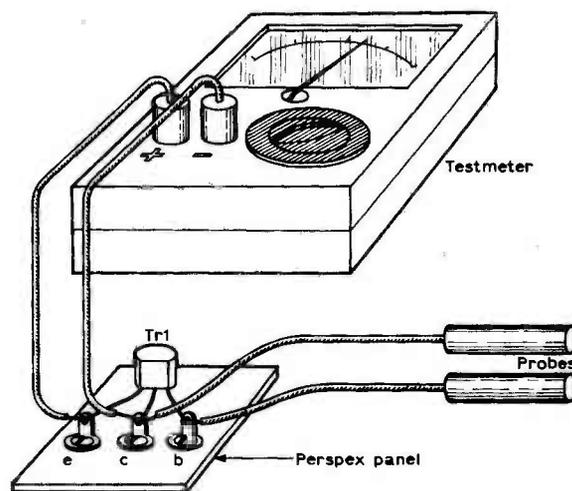


Fig. 2: The connections to the transistor.

will upset the readings. The hand held probes can be made from brass or copper rod and when used these should be firmly held.

The use of the lie detector can be very amusing and provide hours of fun at parties. There is an admirable solution to the inevitable sceptic who mocks the test—pour your drink over his hands! The surprise itself should be enough to produce the reaction but what he will probably not know is that the liquid will improve the probe contact and increase the reading. (Use water with a little salt in for this emergency measure—it looks quite like gin or vodka and after all you don't want to waste your drink do you!)

Next month's *Take 20* project is a two transistor radio. The circuit is designed specifically for miniaturisation by the constructor.

# Never Built a Kit Before?

Why not prove how easy it is the HEATHKIT way.  
Build one of these beginner kits.



- GUITAR PRACTICE AMPLIFIER
- ELECTRONIC METRONOME
- AMBASSADOR SPEAKERS
- AUTO-TUNE-UP METER
- AIRCRAFT MONITOR RECEIVER
- CAR RADIO
- TECHNICIANS LOW-COST 'VVM'
- SEVERN AM/FM RADIO
- FABULOUS STEREO HI-FI COMPACTS
- STEREO RECORD PLAYER
- D.I.Y. SPEAKER SETS
- GENERATORS
- POWER SUPPLIES
- D.I.Y. RADIOGRAM PACKS
- MANY OTHER MODELS TOO NUMEROUS TO MENTION

Send for this  
**FREE Catalogue**  
and see for yourself, Today!



A Schlumberger Company

DAYSTROM LTD  
GLOUCESTER  
GL2-6EE

TO DAYSTROM LTD, GLOUCESTER GL2-6EE

Please send me my free copy of the 1970 HEATHKIT CATALOGUE

NAME .....

ADDRESS .....

51/4

# Adamini

## MODEL 15



### MICRO SOLDERING INSTRUMENT

- **EXTREME VERSATILITY**

Range of 8 interchangeable bits, from 3/64" (.047") to 3/16", including long-life PERMATIPS.

- **ULTRA-SMALL SIZE**

Length 7 7/8". Weight 1/2 oz. Max. handle dia. 7/16".

- **EXTRA-HIGH PERFORMANCE**

Heating time 90 secs. Max. bit temp 390°C. Loading 15 watts — equals normal 30/40 watt iron.

- **ALL VOLTAGES**

The ADAMINI range includes five other models (5, 8, 12, 18 and 24 watts), Thermal Strippers (PVC and PTFE) and a De-soldering Tool. Please ask for colour catalogue A/10.

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL  
Telephone 01-688 8589 and 4559




## THE RSGB AMATEUR RADIO CALL BOOK

1970 edition containing 120 pages.

Complete up to date listing of all amateur stations in the U.K. and Eire together with much operating information including beam headings and list of prefixes.

7s 3d post paid

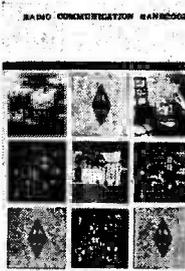

over

# 20,000

copies sold

Now in its second printing

### Radio Communication Handbook

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. The standard work in its field.

69s post paid

### THE VHF-UHF MANUAL

By George Jessop, G6JP

A complete manual for frequencies above 30 MHz. Covers aerials, receivers, transmitters and test equipment. The first book of its kind outside the USA.

23s post paid

Obtainable from:

**RADIO SOCIETY of GREAT BRITAIN**  
35 DOUGHTY STREET, LONDON, WC1



### RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors.



#### LT55 6 WATT AMPLIFIER

A HIGH FIDELITY UNIT PROVIDING EXCELLENT RESULTS AT MODEST OUTPUT LEVELS.

Sensitivity 5 mv (max).

Frequency Response 30-20,000 cps—2dB Harmonic Distortion 0.5% at 1,000 cps Output Rating I.H.F.M. Input Sockets for "Mike," Gram and Radio Tuner/Tape Recorder. Suitable for speakers 3-15 ohms.

Recommended Retail price **£10**

Size 9 1/4" x 2 3/4" x 3 1/4" in.

Controls (5) Volume, Bass, Treble, Mains Switch, Input Selector Switch.

#### LT66 12 WATT STEREO AMPLIFIER

A TWIN CHANNEL VERSION OF THE LT55 PROVIDING UP TO 6 WATTS I.H.F.M. HIGH FIDELITY OUTPUT ON EACH CHANNEL.

Switched Input Facilities Socket (1) Tape or crystal PU (2) Radio Tuner (3) Ceramic PU Microphone.

Controls (6) Volume, Bass, Treble, Balance, Mains Switch, Input Selector Switch. Stereo/Mono Switch.

Face Plate Rigid Perspex with black/silver background and matching black edged knobs with spun silver centres.



Recommended Retail price **18 gns**

Size 12" x 3 1/2" x 6 1/2" in.

If required an attractive wood cabinet with veneer finish can be supplied for any model.

Prices from **70s.**

PLEASE SEND A STAMPED ADDRESSED ENVELOPE FOR FULL DETAILS OF ABOVE UNITS AVAILABLE FROM YOUR LOCAL HI-FI DEALER

Wholesale and Retail enquiries to:

**LINEAR PRODUCTS LTD, Electron Works, Armley, Leeds**

# UNIT BUILT

# GENERAL COVERAGE RECEIVER

SSB • CW • AM  
550kHz to 30MHz

F. G. RAYER  
G30GR

Continued from last month

**F**IXING holes for the drive are located with the paper template included with it. The S-meter is fitted to the right, Fig. 4. Holes are punched to take the controls under the chassis, as in Fig. 5.

An aperture is cut in the chassis to take the flywheel and drive. Holes are positioned for aerial and earth sockets, etc., and under each section of the ganged capacitor. Each coil needs a  $\frac{1}{4}$  in. dia. hole and they will be placed as in Fig. 5.

The chassis flanges are fixed to the panel with chromed bolts, the bottom of the chassis being  $\frac{1}{8}$  in. higher than the bottom of the panel, to allow for the cabinet flange.

Leads are soldered to the bottom tags of the variable capacitor, and passed down through the holes mentioned. Capacitor and drive spindles are carefully lined up and joined with a flexible coupling. Spaces or extra nuts are needed under the capacitor, to raise it.

Space is left for a PP9 battery, Fig. 4. When the audio panel is completed, it is fitted a little clear of the chassis as in Fig. 4. This is done with two bolts with extra nuts. One bolt also provides the earth return connection from amplifier positive to chassis.

The i.f. and S-meter amplifier panel is secured with two small brackets, Fig. 4. This allows all cores and underneath wiring to be reached, with short connections where necessary. Positive is returned to the chassis at a bracket.

The small b.f.o. and produce detector panel is also fixed with two brackets, Fig. 4. The b.f.o. coil

core is reached from the underside, so it is necessary to have a short adjusting tool, or make one from a strip of paxolin or insulated rod.

## Bandswitch

This has a mechanism with moving stop, which is placed to give four positions. The three wafers are placed with their identification marks all the same way, and are threaded on the shaft. The screwed rods are then put in, with spacers allowing the wafers to come approximately as in Fig. 5.

Each wafer is three-pole four-way, and the switch cannot work if any is reversed, or has its rotating section wrongly placed on the shaft. If there is any doubt about its operation, this will be clarified by examining a wafer, and checking with a meter, with the switch in each of its four positions in turn. Also test the receiver with the three coils for one band only actually connected, with the switch in the appropriate position.

The front wafer is S1, S2 and S3. S3 is nearest the chassis, and wired to VC1 (and VC4). Tr1 base goes to S2 as in Fig. 5. The remaining section is S1, used for aerial.

The central wafer is S4, S5 and S6. Tr1 collector goes to S4, Tr2 emitter to S5, Fig. 5, and again the tag nearest the chassis has a short lead through to VC2.

The rear wafer is S7, S8 and S9, Tr2 emitter and collector going to S8 and S7, positioned as in Fig. 5, with a short lead from VC3 to the remaining section S9, near the chassis. This allows short leads where required.

## Coils, etc.

These are positioned as in Fig. 5, for short leads on the h.f. ranges, while keeping similar coils well separated. The wiring is largely duplicated from one band to the next, as follows:

**Blue (Aerial) Coils.** 1 and 9 joined on all, and to chassis. 7 joined on all, and to C1. C1 goes directly from S.W.1, pin 7, to chassis, Fig. 5. S1 tags, S2 tags and S3 tags are then wired in sequence to 8, 5 and 6, of S.W.1, S.W.2, S.W.3 and M.W. coils.

**Yellow (Mixer) Coils.** All tags 1 to chassis. Tags 8 joined and to C3. Tags 7 joined and to C5 at S.W.1, Fig. 5. S4, S5 and S6 then go to 9, 5 and 6. for each range, as before.

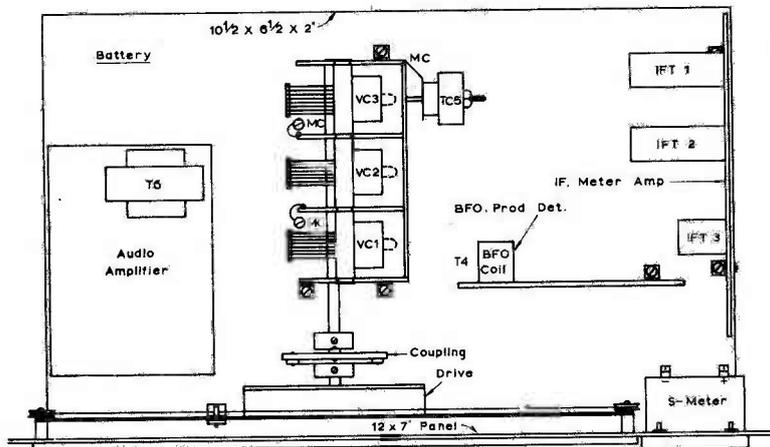


Fig. 4: Layout of main components on the top of the receiver chassis.

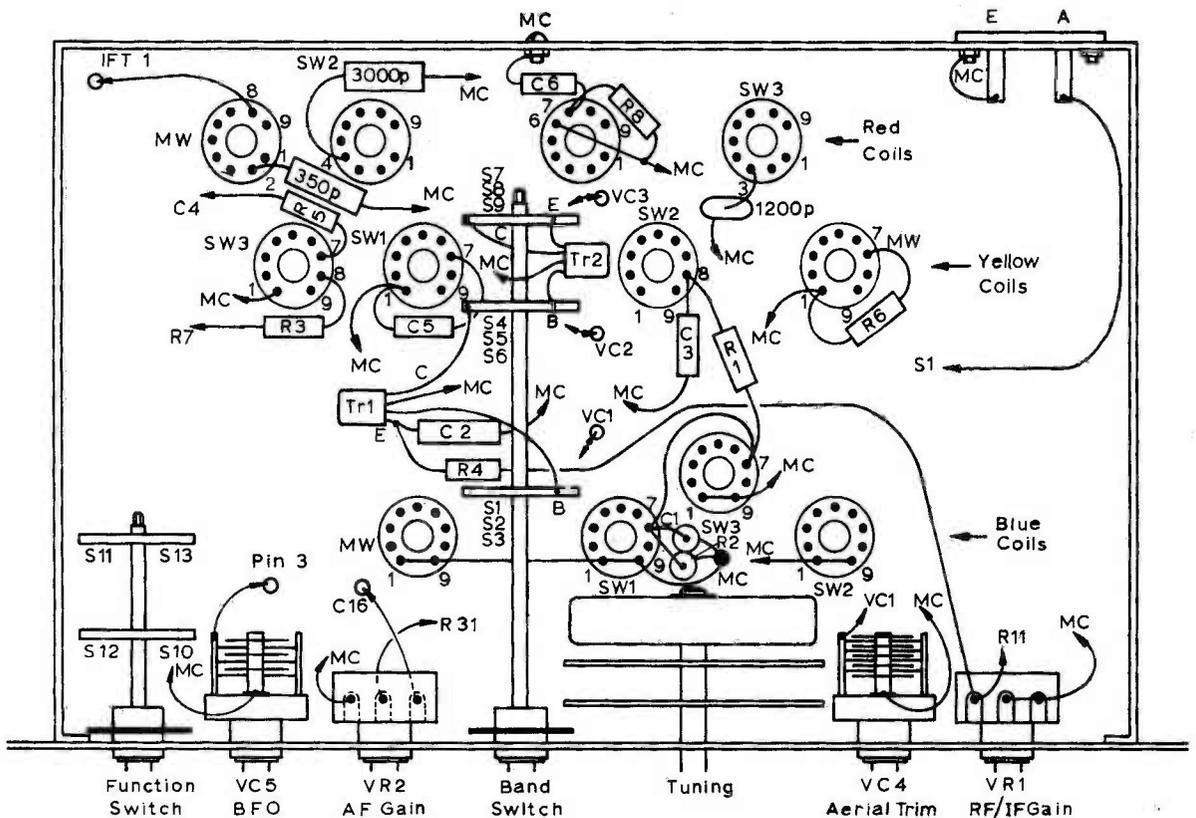


Fig. 5: Layout and part wiring of components on the chassis underside.

**Red (Oscillator) Coils.** Tags 8 joined, and to 2 on i.f.t.1. Tags 7 to C6 at S.W.1 (Fig. 5). S7, S8 and S9 to tags 9, 5 and 1. Padders as described, and in Fig. 5.

Chassis returns for S.W.1 and S.W.2, including those via capacitors C1, C5 and C6, *must* be very short and direct. For these ranges, 20 s.w.g. connections are suggested, with 26 s.w.g. for the lower frequency coils. Different colours of 1mm sleeving will help identify the leads.

Coils were placed to allow a screen between blue and yellow types, but this was found unnecessary. Shorting type wafers to earth all unused windings are not available in the three-pole type. Small absorption effects were found to arise at about 12, 17 and 24MHz. Since 12MHz is available on both S.W.1 and S.W.2, this may be neglected. The others would be cured by using shorting wafers. This would require more wafers, as they are only available in two-poles per wafer type. Alternatively, the offending coils could be placed in the cans supplied by the maker, for screening.

Tr1 and Tr2 are close to their connecting points, and with each the shield lead goes to the chassis. Actual wires are emitter, base, shield, collector, in line and with extra spacing for the collector lead.

Individual mixer coil trimmers are not shown in Fig. 5 for clarity. These are soldered directly from

pin 1 to pin 6 on each yellow coil, the plate adjacent to the adjusting screw-head going to 1 (chassis).

## Constructional Points

Amplifiers and product detector with b.f.o. are assembled on insulated eyelet board having holes at 0.2in. centres. Plain board could be drilled to suit.

Some 26 s.w.g. tinned copper or similar wire may be used throughout, with 1mm sleeving. It is helpful to identify external and other connections by colour, and to use red for chassis (positive) and black for

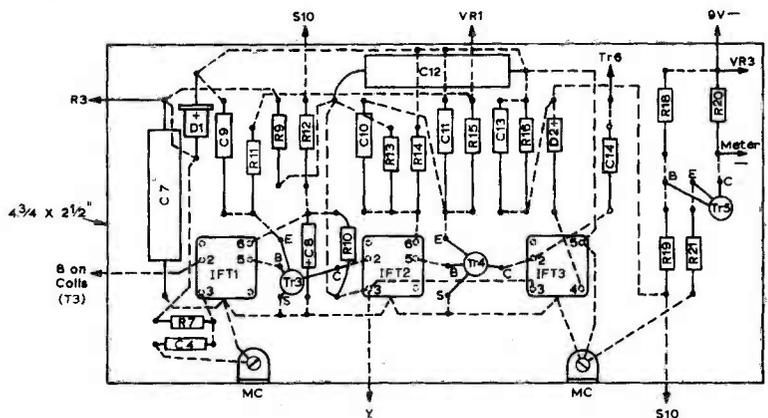


Fig. 6: I.F. amplifier and meter amplifier board.

## BSR 4-SPEED SUPERSLIM MODEL UA25 RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. Size 13 1/2" x 11 1/2" x 1 1/2". Above motor board 3 pins below 2 pins. AC 200/250v.



**MONO £5.19.6 STEREO £6.19.6** Post 5/6  
**PRICE PRICE**  
 BSR UA70 Stereo/Mono Transcription £12.19.6  
 Auto Changer. Calibrated Stylus Pressure.  
 BSR Minichanger UA50 Stereo/Mono. Size 12" x 8 1/2". AC 200/250v. Post 5/6. £7.19.6

**GARRARD PLAYERS** with Sonotone 9TA Cartridges. Stereo Diamond/Mono Sapphire. SP25 MK II £14.19.6. AT90 MK II £14.19.6. Model 3000 £12.19.6. Post 5/6.  
**RECORD PLAYER PORTABLE CABINET** Space for amplifier and autochanger. Post 5/6. **75/-**  
**RCS DE-LUXE 3 WATT AMPLIFIER.** Ready-made and tested. A 2-stage unit using triode pentode valve, giving 3 watt output. Tone and volume controls. Isolated mains transformer. With knobs, loudspeaker and valves ECL82, EZ50. Frequency response 50-12,000 cps. Sensitivity 200mV. Post 5/6. **89/6**

**GARRARD TEAKWOOD BASE WB.1.** Ready cut out for mounting 1025, 3000, SP25, AT90, etc. **77/6**  
**GARRARD PLASTIC COVER SPEC.1** for WB.1 BASE. Durable tinted attractive appearance. **77/6**  
**EMI PICK-UP ARM.** Complete with mono cartridge 29/8.  
**EMI JUNIOR 4 SPEED RECORD PLAYER** Mains operated motor, turntable and pick up complete. Post 5/6. **59/6**  
**EMI PICK UP CARTRIDGES**  
 GP94 55/-, GP95 45/-, GP91 30/-, GP97 19/6, ACOS L.P. only 10/8. All standard fixing complete with stylus.

**CRYSTAL MIKE INSERTS**  
 1 1/2" dia. 6/6. ACOS 1 1/2" dia. 12/6. BMS, 1" dia. 9/6

## PORTABLE AMPLIFIER

Portable mini p.a. system. Many uses - ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive finish covered cabinet, size 15 x 9 x 4 1/2", with powerful 7 x 4 in. speaker and four transistor one watt power amplifier. Uses PP9 battery. Brand new in Makers' carton with full makers' guarantee. World famous make.



Only **75/-** Post 5/-

**WEYRAD P50 - TRANSISTOR COILS**  
 RASV Ferrite Aerial 12/8 Spare Cores ..... 6d.  
 OSC. P50/LAC ..... 5/4 Driver Trans. LEDT4 ..... 8/6  
 I.F. P50/CO 470 kc/s ..... 5/7 Printed Circuit, PCA1 ..... 9/8  
 S.E.P. P50/PCO ..... 8/- J.M. Tuning Gans ..... 10/8  
 P51/L P51/H ..... 5/7 Weyrad Booklet ..... 2/-  
 P51/S, 6/- Telescopic Aerials 6in. to 23in. 5/-  
 Ferrite Rod 8 x 1/4 in. 6 x 1/4 in. 5/-

**VOLUME CONTROLS** 80ohm Coax 8d. yd.  
 Long spindles. Midget Size 5 ohms to 2 Meg. LOG on LIN. L/S 3/-. D.P. 5/-  
**STEREO L/S 10/6, D.F. 14/6**  
 Edge 5K. P.P. Transistor, 5/-  
**WIRE-WOUND 3-WATT POTS.** Small type with small knob. Values 10 Ω to 30 K. **4/6**  
**WIRE-WOUND 3-WATT STANDARD SIZE POTS.** LONG SPINDLE. 10 OHMS to 100 K. **7/6**

**VEROBOARD 0-15 MATRIX** 2 1/2" x 5in. 3 1/2" x 3 1/2". 3 1/2" x 3 1/2". 3 1/2" x 5in. 5/2.  
**EDGE COIL** 15 way 5/-, 24 way 7/6.  
**PIN 36 per packet 3/4. PAIR CUTTERS 7/6.**  
 S.E.B.P. Board 0-15 MATRIX 2 1/2 in. wide 6d. per lin., 3 1/2 in. wide 9d. per lin.; 5in. wide 1/1 per lin. (up to 17in.).  
**W.R.P. undrilled 1/4 in. Board 10" x 8in. 3/-.**

**BLANK ALUMINIUM CHASSIS.** 18 s.w.g. 2 1/2 in. sides, 7 x 4 in., 6/-; 11 x 8 in., 7/6; 11 x 7 in., 9/8; 13 x 9 in., 10/6; 15 x 14 in., 15/-; 9 x 7 x 2 in., 9/6; 14 x 11 x 8 in., 14/6.  
**ALUMINIUM PANELS** 18 s.w.g. 12 x 12 in., 6/6; 14 x 9 in., 6/6; 18 x 9 in., 4/6; 10 x 7 in., 3/6; 8 x 6 in., 2/6; 5 x 4 in., 1/6.  
**1 1/2 in. DIAMETER WAVE-CHANCE SWITCHES.** 2 p. 2-way, or 2 p. 8-way, or 3 p. 4-way 4/6 each. 3 p. 12-way or 4 p. 2-way, or 4 p. 2-way 4/6 each. 1 inch DIAMETER Wave-Change "MAKISS" 1 p. 12-way, 2 p. 8-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 12/6, 2 water 18/-, 3 water 24/-, 4 water 30/-, 5 water 36/-.  
**TOGGLE SWITCHES,** sp. 2/6; sp. 2/6; sp. 2/6; dp. 3/6; dp. 4/6

**ALL PURPOSE HEADPHONES**  
 H.R. HEADPHONES 200 ohms Super Sensitive ..... 35/-  
 LOW RESISTANCE HEADPHONES 3-4 ohms ..... 39/6  
 DE LUXE PADDED STEREO PHONES 8 ohms ..... 79/8

**"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER**



200/250 v. A.C. Leatler S.A.E. Post 2/8 **42/6**  
 Minimum Post and Packing 2/6. RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK.

# RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON

List 1/- Written guarantee with every purchase. (Export: Remit cash and extra postage). Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-884-1665

★ ALL PURPOSE TRANSISTOR PEE AMPLIFIER BRITISH MADE ★  
 9-12v. and 200-300v. D.C. operation. Size 1 1/2" x 1 1/2" x 1 1/2". Response 15 cps. to 25 Kc/s. 25 db gain. For use with valve or transistor equipment. Full instructions. **17/6 each**

**NEW TUBULAR ELECTROLYTICS** CAN TYPES  
 2/350V .. 2/3 100/25V .. 2/- 16+120/500V 11/-  
 4/350V .. 2/3 250/25V .. 2/6 80+40/500V 7/-  
 8/450V .. 2/3 500/25V 4/- 60+100/550V 11/6  
 16/450V 3/- 8+3/450V 3/6 32+32+250V 3/6  
 32/450V 3/9 8+16/450V 3/9 32+32/450V 6/6  
 25/25V 1/9 16+16/450V 4/3 32+32+32/350V 8/6  
 50/50V 2/- 32+32/350V 4/6 100+50+50/350V 9/6

**SUB-MIN. ELECTROLYTICS** 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250mF 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/-  
**CERAMIC** 500V 1pF to 0.01mF, 9d.  
**PAPER** 350V-0.1 9d., 0.5 2/6; 1mF 3/-; 2mF 150V 3/-  
 500V-0.001 to 0.05 9d.; 0.1/-; 0.25 9d.; 0.5 3/-  
 1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1, 2/6.  
**SILVER MICA.** Close tolerance 1%, 5-500pF 1/-; 560-2,200pF 2/-; 2,700-5,500pF 3/6; 8,500pF-0.01, mica 6/-, each.

**TWIN GANG.** "0-0" 208pF+176pF, 10/6; 365pF, miniature 10/6; 500pF standard with trimmers, 12/6; 600pF midget less trimmers, 7/6; 500pF slow motion, standard 9/-; small 3-gang 500pF 19/8. Single "0" 305pF 7/6. **TWIN 10/6.**  
**SHORT WAVE.** Single 10pF, 25pF, 50pF, 75pF, 100pF, 160pF, 200pF, 10/6.  
**TRIMMERS.** Solid dielectric. 100pF, 300pF, 500pF, 7/- each. TRIMMERS. Compression 30, 50, 70pF, 1/-; 100pF, 160pF, 1/3; 250pF, 1/4; 600pF, 760pF, 1/4; 1000pF, 2/6.  
**RECTIFIERS CONTACT COOLED** 1/4 watt 60mA 7/6; 80mA 9/6. **SILICON BZ13 6/-; BY100 10/-.**  
 Full wave Bridge 75ma 10/-; 150ma 10/6; TV rect. 10/-.  
**NEON PANEL INDICATORS** 250v. AC/DC Red. Amber 4/6.  
**RESISTORS.** Preferred values, 10 ohms to 10 meg. 1/2 w., 1 w., 20% 2d.; 1 1/2 w., 8d.; 2 w., 1/-; 1 w., 10% 6d.  
**HIGH STABILITY.** 1/2 w., 1% 10 ohms to 10 meg., 2/-; Ditto 5%. Preferred values 10 ohms to 22 meg., 9d.  
**WIRE-WOUND RESISTORS** 5 watt, 10 watt, 15 watt, 10 ohms to 100K. 2/- each; 21 watt, 1 ohm to 8.2 ohms. 2/-.

**BRAND NEW TRANSISTORS 6/- EACH.**  
 OC71, OC72, OC81, OC44, OC45, AF117.  
**MAT 100 7/8; MAT 101 7/8; MAT 120 7/8; MAT 121 8/6.**  
**REPANCO TRANSISTOR TRANSFORMERS.**  
 TT45. Push Pull Drive, 9:1 CT, 6/-; TT46 Output, CT8:1, 6/-.  
 TT49. Interstage, 4:5:1, 6/-; TT52 Output 3 ohms, 20:1, 6/-.  
**TT23 4 PAIR 10 watt Amp. Transformers and circuit 35/-.**

**TRANSISTOR MAINS POWER PACKS. FULL WAVE**  
 9 volt 500mA. Size 4 1/2 x 2 1/2 in. Metal case. **49/6**  
 Cracks in. Output terminals. On/off switch.  
 Half Wave 9 volt 500mA. Size 2 1/2 x 1 1/2 in. Snap terminals 32/6  
 9 volt 500mA. TRANSFORMER ONLY. 2 1/2 x 1 1/2 in. 10/6

**MAINS TRANSFORMERS** Post 5/- each  
 250-0-250 50 mA. 6.3 v. 2 amps, centre tapped 19/6  
 250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 35/-  
 350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 35/-  
 300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 6.3 v. 2 a. 45/-  
**MINIATURE** 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 12/8  
**MIDGET** 220 v. 45 mA. 6.3 v. 3 x 2 1/2 in. 17/6  
**HEATER TRANS.** 8.3 1 1/2 a., 10/6; 6.3 v. 4 a. 15/6  
 Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1 amp. 15/6  
**GENERAL PURPOSE LOW VOLTAGE.** Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. 35/-  
 1 amp., 8, 10, 12, 15, 20, 24, 30, 35, 40, 45, 60, 80, 85/-  
**AUTO. TRANSFORMERS** 0-110-230 v. Input/Output, 60w. 18/6; 150w. 35/-; 500w. 95/-; 1000w. 195/-  
**CHARGER TRANSFORMERS.** Input 200/250v for 6 or 12v., 1 amp., 22/-; 4 amp., 35/-  
**FULL WAVE BRIDGE CHARGER RECTIFIERS:**  
 6 or 12v. outputs, 1 amp. 89/6; 2 amp. 113/6; 4 amp. 17/6.

**COAXIAL PLUG 1/8, PANEL SOCKETS 1/8. LINE 3/6.**  
**OUTLET BOXES, SURFACE OR FLUSH 4/6.**  
**BALANCED TWIN FEEDERS 1/2 yd. 80 ohms or 300 ohms.**  
**JACK SOCKET 8d.** open-circuit 2/6, closed circuit 4/6;  
 Chrome Lead Socket 7/6. Phone Plug 1/2. Phone Socket 1/2.  
**JACK PLUGS 8d.** Chrome 3/6; 3 1/2 mm Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/8; 6-pin 2/-; DIN SOCKETS Lead 3-pin 3/6; 6-pin 5/-; DIN PLUGS 3-pin 3/6; 5-pin 6/-; VALVE HOLDERS, 9d.; CERAMIC 1/6; GANS 1/-.

**E.M.I. 13 1/2 x 8in. LOUSPEAKERS**  
 With flared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. Speech coil, 3 or 15 ohm. **45/-**  
 Recommended Teak Cabinet Size 16 x 10 x 8in. **94/6**  
 Also with twin tweeters 3 or 8 or 15 ohms. 10 watt. **79/6**

**MINI-MODULE LOUSPEAKER KIT**  
 10 WATT 65/- CARRIAGE 5/-  
 Triple speaker system combining on ready cut baffle. 3 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm. **TEAK VENEERED BOOKSHELF ENCLOSURE.** 16 x 10 x 9 in. Modern Scandinavian. **94/6** Post 5/- fluted front design for Mini-Module.

## ALL MODELS "BAKER SPEAKERS" IN STOCK BAKER 12in MAJOR £8



30-14,500 c.p.s., 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 cps. Rated 20 watts. Voice coils 3 or 8 or 15 ohms.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and **£10.19.6** instructions.

**BAKER "GROUP SOUND" SPEAKERS - POST FREE**  
 "Group 25" 18in 25 watt **6gns.** "Group 35" 12in 35 watt **8gns.** "Group 50" 15in 50 watt **8gns.** "Group 50" 18in 50 watt **18gns.**

**TEAK HI-FI SPEAKER CABINETS.** Fluted wood front. For 10 or 12in round Loudspeaker ..... £5.10.0.  
 For 18 x 8in or 8in round Loudspeaker ..... £4.14.6.  
 For 10 x 8in or 6in round Loudspeaker ..... £3.18.6.  
**LOUDSPEAKER CABINET WADDING** 18in wide, 2/6in.

Goodmans Tweeter 3in 3 ohm 35/-, EMI 29/8 8 ohm 17/6. Horn Tweeters 2-18Kcs, 10W 15 ohm 2/6. Crossover 16/6. **LOUDSPEAKERS P.M. 3 OHMS.** 2 1/2in, 3in, 4in, 5in, 6in, 8 x 3in, 7 x 4in, 17/6 each; 6in 22/6; 8 x 6in, 21/-; 8 x 2 1/2in 21/-; 10 x 6in, 30/-; 10in, or 12in. Double cone 3 or 15 ohm 39/6.  
**SPECIAL OFFER:** 80 ohm, 2 1/2in, 21in, 35 ohm, 3 in, 25 ohm, 15/6 EACH 6 x 4in; 8 x 6in. 15 ohm. 7 x 4in; 8 x 6in.  
**8in LOUSPEAKER UNITS** 3 ohm 27/6; 15 ohm 30/6. ELAC 8 in. De Luxe Ceramic 3 ohm 45/-; 15 ohm 50/-, 8in LOUSPEAKER. **TWIN OHM 3** 3 ohm 25/-, 5 in. WOODER, 3 watts max. 20-10,000 cps. 8 or 15 ohm 39/6. **OUTPUT TRANS.** EL84 etc. 4/8; **MIKE TRANS.** 50m. 3/8. **SPEAKER COVERING MATERIALS.** Samples Large S.A.E.

## THE FAMOUS "MULLARD 510" £16.19.6 Post 10/6



Main power, amplifier and 2 valve pre-amplifier. Silver grey facia panel. Volume, treble, bass controls. Function switch: Radio, Tape 1, Tape 2, Mio, Gram L.P., Gram 78. Tape output socket. Valves: 2 x EL84, 3 x EY88. 1 x 6X8, 1 x EZ81. Ultra linear Parmeko output transformer. 20 db negative feedback, 10 watts r.m.s. mono, 3 and 15 ohm output. Brand new. Guaranteed.

## ALL EAGLE PRODUCTS SUPPLIED AT LOWEST PRICES. ILLUSTRATED EAGLE CATALOGUE 5/- Post free.

**BARGAIN AM TUNER.** Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **79/6**  
**BARGAIN DE LUXE TAPE SPLICER.** Cuts, trims, joins for editing and repairs. With 3 blades. **22/6**  
**BARGAIN 4 CHANNEL TRANSISTOR MIXER.** Add musical highlights and sound effects to recordings. With mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **59/6**  
**BARGAIN FM TUNER 88-108 Mc/s.** Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. **£9.10.0**  
**BARGAIN 3 WATT AMPLIFIER.** 4 Transistor Push-Full Ready built, with volume control. 9v. **69/6**

★ RADIO BOOKS ★ (Postage 9d.)  
 Practical Transistor Receivers ..... 5/-  
 Practical Radio Inside Out ..... 4/6  
 Super-sensitive Transistor Pocket Radio ..... 3/8  
 Radio Valve Guide, Books 1, 2, 3, or 4 ..... 5/- No. 5 ..... 6/-  
 T.V. Fault Finding 405/625 lines ..... 2/6  
 Short Wave Transistor Receivers ..... 5/-  
 Transistor Communication Sets ..... 7/6  
 Modern Transistor Circuits for Beginners ..... 2/6  
 Sub-Minute Transistor Receivers ..... 2/6  
 Radio Valve Guide, Books 1, 2, 3, or 4 ..... 5/- No. 5 ..... 6/-  
 International Radio Stations Guide ..... 2/6  
 Transistor Circuits for Radio Controlled Models ..... 7/6  
 Valves, Transistors and Diodes equivalents Manual ..... 10/6

**3 inch MOVING COIL METERS BRITISH MADE**  
 Various calibrations/movements. 500 Microamp. 1 Milliamp; 50-0-50 Microamp. etc. S.A.E. for list. **37/6**

**MAINS ELECTRIC MOTORS** (120v. or 240v. AC). Size 2 1/2 x 2 1/2 x 1 1/2 in. Clockwise 1,800 r.p.m. off load. Heavy duty 4 pole 500mA. Spindle 3/4 x 3/80. **BARGAIN 17/6 EACH**  
 PRICE 3 for 50/-; 6 for 99/-.

CALLERS WELCOME. 975

## AUDIO EFFECTS

5 SHAW LANE, HALIFAX YORKS

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.  
**AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT.** No fuss, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco plug in coils 2T. 0.5 to 1.54 Mhz 3T. 1.67 to 5.3 Mhz 4T. 0.5 to 15 Mhz 5T. 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 9 volt battery. Easy step by step instructions. Complete Kit. £8.19.6 plus 5/6 P. P. & Ins. Extra ranges 12/- per range.

**POWER CONTROLLER.** Power at your finger tips. Not merely half wave control but full wave. A single variable control goes from zero to full power. Uses latest 15 amp 3kW triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions £6.9.6. Ready built £9.4.6 plus 5/6 P. P. & Ins.  
**REVERBERATION AMPLIFIER.** Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2" x 3 1/2" x 4 1/2". £10.4.0 plus 6/- P. P. & Ins.

**VOX SWITCH.** The most advanced operated switch is ideal for mobile TX work, tape recorder, switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 42/6. Ready built, tested and guaranteed. 62/6, plus 2/6 P. P.

**METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive black and white polythene case, 37/6 post paid.

**MORSE OSCILLATOR.** PC board, transistors, high stab. components, battery carrier, car piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 25/- post paid.

**STRAIGHT FROM THE PRESS.** Latest Mullard manual: Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi Tape, etc. etc. 32/6 post paid.

**JUST ARRIVED IN STOCK.** Texas transistors. Complementary symmetry. Driver, NPN, PNP output. The set of three ONLY 6/6 post paid.

Free lists with every order. For lists only send 1/6 (deductible from first order).

## NEW VALVES!

Guaranteed and Tested  
24-HOUR SERVICE

1R5	5/8	DL96	7/-	EY31	7/6	PL504	13/3
1R5	4/3	DY88	4/0	EY86	6/3	PY32	10/-
1T4	2/0	DY87	4/0	EZ80	4/3	PY33	10/-
3R4	5/0	PABC80	5/0	EZ81	4/6	PY81	5/-
3V4	6/0	EBC33	7/0	KT61	9/3	PY82	5/-
6/30L2	11/6	EBC41	6/3	KT86	16/6	PY83	5/6
6AQ5	4/3	EFB80	6/0	N78	17/-	PY88	9/6
6V80	3/-	EFB89	5/6	PABC80	6/0	PY800	6/6
26L6GT	4/6	ECC81	3/6	PC88	10/3	PY801	6/6
30PL1	13/6	ECC82	4/-	PC88	10/3	R19	6/3
30PL12	14/3	ECC83	4/0	PC97	8/3	U25	12/0
30P4	11/6	ECC86	5/0	PC980	7/-	U26	11/6
30P19	11/6	ECH85	5/6	PC94	4/3	U19	12/-
30PL1	13/6	ECH81	5/0	PC98	8/11	U193	8/6
30PL13	14/11	ECL90	6/6	PCF80	5/11	U251	14/-
6CH35	13/-	ECL82	6/3	PCF801	6/6	U301	10/-
CL33	17/6	ECL83	8/-	PCF802	8/0	U329	14/6
DAF91	6/3	ECL86	7/6	PC92	6/6	UABC80	6/-
DAF91	4/3	EP7A	6/0	PC97A	9/0	UBC41	3/3
DAF96	6/0	EF89	4/6	PCL84	7/-	UBF89	6/3
DF33	7/6	EF80	4/6	PCL85	8/6	UC85	7/3
DF91	2/0	EF85	4/0	PCL98	8/-	UC81	6/-
DF96	6/0	EF86	6/3	PFL20011	-	UCL82	6/0
DE32	6/0	EF89	4/0	PL36	9/3	UP41	10/6
DE31	5/6	EF83	6/0	PL41	8/-	UL41	6/-
DK96	7/3	KT184	5/3	PL82	5/0	UL41	10/3
DL35	4/0	EH80	6/-	PL83	6/3	UL84	6/3
DL92	5/0	EL33	9/3	PL84	6/-	UY41	7/-
DL94	6/6	EL84	4/0	PL500	12/0	EY85	5/3


Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any insured parcel against damage in transit 6d. extra. Office address, no callers.

## GERALD BERNARD

83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON, N.16

## H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

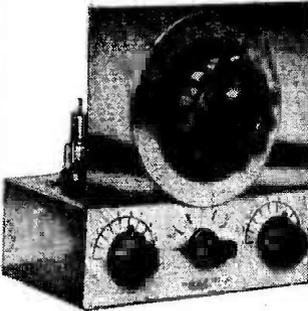

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

### IMPROVED 1970 RANGE

One-valve model "DX", complete kit—price 56/0 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve B.W. Kit available at any price. America and Australia received clearly as good volume." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other B.W. kits including the famous model "K" and "K plus" (illustrated above.) All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1

## 1,750 COMPONENTS FOR 65/- ??

YES, QUITE TRUE.  
READ ON

### BUMPER BARGAIN PARCEL

We guarantee that this parcel contains at least 1,750 components. Short-leaded on panels, including a minimum of 350 transistors (mainly NPN & PNP germanium, audio and switching types—data supplied). The rest of the parcel is made up with: Resistors 5% or better (including some 1%) mainly metal oxide, carbon film, and composition types. Mainly 1/2 & 1/4 watt . . . diodes, miniature silicon types OA90, OA91, OA95, IS130, etc. . . capacitors including tantalum, electrolytics, ceramics & polyesters . . . inductors, a selection of valves . . . also the odd transformer, trimpot, etc., etc. . . . These are all miniature, up to date, professional, top quality components. Don't miss this, one of our best offers yet!! Price, 65/-, Post and Packing 6/6 U.K., New Zealand 20/- post and packing. Limited stocks only.

## KEYTRONICS, PW

52 Earls Court Road, London, W8  
Tel. 01-478 8499

MAIL ORDER ONLY. Retail and Trade supplied. Export enquiries particularly welcome.

BY RETURN SERVICE

S.A.E. for list of other goods.

## PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDEGE,  
YORKS. Tel. Heckmondwike 4285

AW48-80 TV Tubes good picture—no guarantee £1 plus 12/- carriage

Aircraft Sighting Head with Gyro Unit. Condition Fair 18/6, carriage B.R.S. 12/-.

Small 12-way Plug and Socket, 1/6 each p.p. 1/-, 15/- per doz. p.p. 3/6. Ex unit.

Panel of 19 mixed pots. 5/- post paid. Ex unit. Panels of Resistors and Condensers 8/- per doz., post paid. Ex unit.

Bombight-Computers containing a large selection of gears. A delight for The Model Maker. 55/- carriage paid.

Complete untested 17 inch TV Sets 12 channel 50/-, 15/- carriage.

Small Sub Chassis containing small 12-way Plug and socket. Few Resistors and Condensers 5/-, p. p. 1/6.

Speakers removed from T.V. Sets. All PM and 3 ohm. 6in. round 3/-, p. & p. 3/-; 6 for 24/-, post paid 6x4in. 3/-, p. & p. 3/-; 6 for 24/-, post paid. 5in. round 3/-, p. & p. 3/-; 6 for 24/- post paid. 7x4in. 5/-, p. & p. 3/-; 6 for 34/- post paid. Slot Speakers 8x2in. 5/-, p. & p. 3/-; 6 for 30/- post paid.

Reclaimed T.V. Tubes, with 6 months' guarantee 17in. Type AW43/80. AW43/88 40/-, MW43/69 30/-, 14in. Type 17/-, All Tubes 12/- carriage.

Silicon Rectifier 500mA 800 PIV, 2/6 post paid. 24/- per dozen, post paid.

Jap Earpiece. Magnetic 8 ohm. Small and Large Plug 1/11 post paid.

G.P. Diodes 3/6 per dozen, post paid.

Top Grade Mylar Tapes, 7in Standard 11/6, 7in. Long Play 14/-, 5in. Standard 7/9, 5in Long Play 10/-, plus post on any tape 1/9.

VALVE LIST—Ex Equipment, 3 months' guarantee. Single Valves Post 7d., over 3 Valves p. & p. paid

ARP12	1/6	PCL82	4/-	6B8	1/8
EB91	9d	PCL83	5/-	6BW7	2/6
EF85	3/-	PL36	5/-	6K7	1/9
EFB80	3/-	PL38	6/-	6U4	5/-
ECC81	3/-	PL81	4/-	6P28	5/-
ECC82	3/-	PY33	5/-	10P13	2/6
		PY81	1/6	185BT	8/6
ECC83	4/-	PY82	1/6	20D1	3/-
ECL80	1/6	PZ30	5/-	20P1	5/-
EF50	1/-	U191	5/-	20P3	2/6
EF80	1/6	U281	5/-	30P11	5/-
EF91	9d	U282	5/-	30P12	5/-
EY86	5/-	U301	5/-	30F5	2/6
PCC84	2/-	U329	5/-	30FL1	5/-
PCF80	2/-	U251	5/-	6/30L2	5/-

Est. 1943 **JOHNSONS** Tel: 24864

New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

**JOHNSON'S (RADIO)**

St. Martin's Gate, Worcester

Please mention

**PRACTICAL  
WIRELESS**

when replying to  
advertisements

negative circuits.

Short pieces of sleeving will also identify transistor leads when these are fitted. Black is suggested for base, yellow for emitter, and red for collector.

**I.F./Meter Amplifier.** This is the largest unit, shown in Fig. 6. It mounts vertically by two brackets used as chassis return. Figure 6 shows the "top" of the board, with i.f.t.s, resistors, etc. Wiring under the board is shown with broken lines.

It is convenient to fit the i.f.t.s first, with central holes to reach the cores later. All the cans are earthed. If each component and lead is marked with coloured pencil as fitted and soldered it will be easily clear what has been done, and nothing is likely to be omitted.

Later, leads are passed through the chassis to the function switch, 8 on oscillator coils, and other items as shown. A check should be made against Fig. 2 as required. R18 to R21, Tr5 and the meter may be omitted until later.

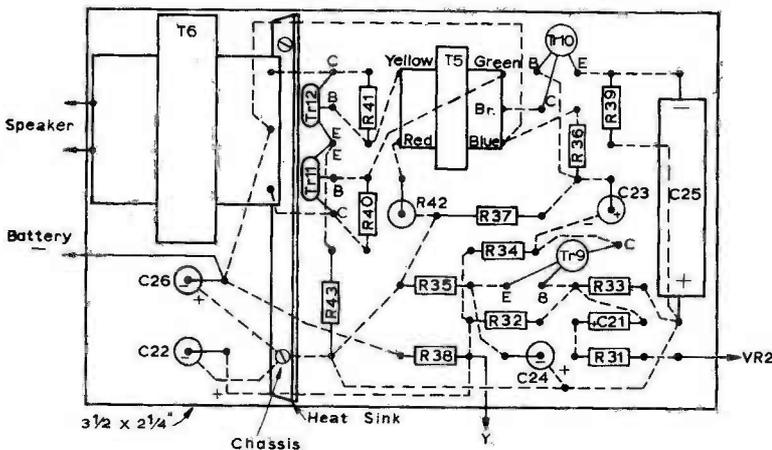


Fig. 7: The audio amplifier board.

**Audio Amplifier.** Figure 7 shows components and wiring. The heatsink is fixed with two 1/4 in. or similar bolts, and a tag under one nut serves as chassis return. Extra nuts are put on, and the finished board can then be clamped to the chassis, with a little clearance.

Tr11 and Tr12 occupy clips bolted to the heat-sink. The connections given for T5 are for the particular transformer listed, and if an alternative is fitted, the maker's data should be followed.

A black flexible lead with negative battery clip runs from C26. The lead Y supplies the i.f. amplifier. VR2 slider runs to R31.

The whole amplifier can be tested by taking an audio input to R31, with battery positive as earth return.

If the receiver is to be temporarily or permanently used for ordinary a.m. reception (speech, music) only, VR2 can be fed from diode D2 via a capacitor, as described.

**Product Detector and B.F.O.** Connections are shown in Fig. 8. The completed panel again mounts vertically on brackets, and is placed to allow quite short leads from C14 and VC5. A hole is necessary under the b.f.o. coil to reach its core.

The circuit provides a.m. detection when the b.f.o. is off, and the function switch breaks this circuit.

Tr6 and Tr7 run from the reduced voltage available from Y at the i.f. amplifier. The b.f.o. receives the regulated supply from the 5.6V Zener diode. When the completed panel is fixed in place, remove the temporary coupling capacitor used to give a.m. reception from D2, if previously fitted.

## IF Alignment

The intermediate frequency is 465kHz. If a signal generator is available, loosely couple it to the base of Tr2, and rotate all the cores for best results with a 465kHz input. A c.w. signal will operate the meter, so i.f.t. cores can be adjusted for best meter reading. Input should be kept well down.

With a modulated signal from the generator, adjustments can be for maximum audio output, with gain controls at maximum; or for maximum battery current, shown by a meter in one lead. Input must again be kept well down.

If no generator is available, a stable signal should be tuned in (such as a BBC transmission, with a very short aerial). The five cores are then carefully adjusted for best results.

A properly shaped core adjusting tool is best employed for the i.f.t.s. Final alignment should be with a weak signal. These cores are then left and need no further adjustment.

## BFO

With VC5 half closed, and the b.f.o. switched on, a strong heterodyne should be heard when the b.f.o. coil core is rotated with a tool. Ignore any weak whistles produced at other core settings, and place the core so that it is at the central or zero beat position. A whistle, which rises in pitch, will then be heard if VC5 is opened or closed. During these adjustments, a

steady carrier should be present, from a signal generator or transmission.

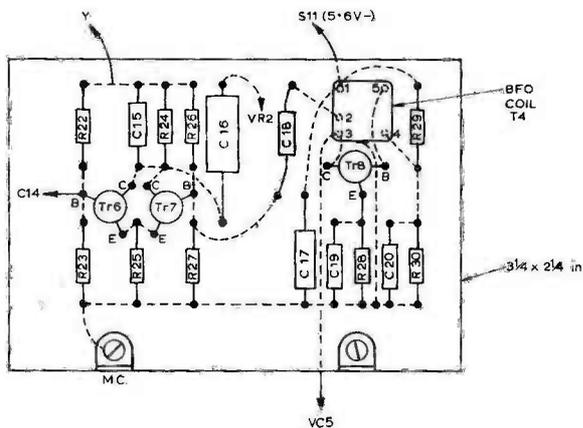


Fig. 8: Product detector and b.f.o. board.

## RF, Mixer and Osc

It is necessary to describe adjustments to only one range, as each range is dealt with separately.

TC5 is about two-thirds or so closed. Its setting primarily determines band limits at the high frequency end of the band. The red coil core is adjusted to obtain a suitable band limit at the low frequency end of the band.

The coils are normally packed with the brass screws set right in, so it is as well to unscrew them all so that roughly  $\frac{1}{2}$  in. of 6BA rod projects, to begin.

Set VC4 (aerial trimmer) about half closed, and rotate the cores of blue and yellow coils for best results, near the l.f. end of the band (ganged capacitor nearly fully closed). Tune to the h.f. end of the band, this time adjusting the yellow coil trimmer for best results.

Repeat these adjustments, as necessary, for suitable band coverage, and best performance. VC4 will not need continuous adjustment, when the blue cores are suitably placed, but this trimmer is helpful when changing aerials, or bringing up weak signals.

## Notes on Operating

The dial reads 0-500, to log particular s.w. transmissions, etc. s.w. reception, especially on the h.f. bands, varies greatly from hour to hour, daily, and has seasonal and other variations.

For normal reception, put the function switch to a.m. with a.v.c. When very strong transmissions overload early stages, VR1 must be turned back. VC4 is simply peaked for best results, and should never be fully open or fully closed.

In some cases manual control of r.f. gain only is required, and 3rd and 4th positions of the switch provide this, the latter with the b.f.o. on. In the 4th position, s.s.b. and c.w. do not control gain via the a.v.c. circuit. In the 5th position, these signals provide a.v.c. bias.

With the switch in the 5th position, c.w. and s.s.b. can be resolved over a considerable level of signal strengths. Rotating VC5 one way or the other, from the central or zero position, will resolve an s.s.b. signal, the direction of rotation depending on whether upper or lower sideband is being transmitted. With exceptionally strong or local signals, gain must be reduced with VR1.

With c.w., the b.f.o. acts as a pitch control, and may also be above or below the carrier frequency, as giving best results.

In all cases VR2 controls volume, and it is as well to keep current peaks down to 30-40mA or so, which should give ample output.

S14 can be closed during noisy static conditions, or when wearing headphones. The limiting is fairly heavy, to avoid blasting on phones.

VR3 should originally be set at about its middle position, with VR1 at maximum gain. With no aerial, and no signal tuned in, adjust VR3 for zero on the S-meter. If wished, VR3 can be made up from one or more resistors in series with a potentiometer of lower value, though using 5k $\Omega$  as shown is not too critical when adjusting zero.


For very long distance reception, one of the numerous external short wave aerials of improved type may be used—a dipole, doublet, tuned end-fed wire, etc.

For general results, any end connected wire may be taken to the aerial socket. It will probably be


found that a long wire is best avoided for medium and low frequencies.

A telescopic 30in. or similar aerial, fixed to the case but insulated from it, will give very good results over medium and high frequencies, though naturally not with extremely remote stations. A flying lead from the aerial can be taken to the aerial socket, or directly to the fixed section of VC1.

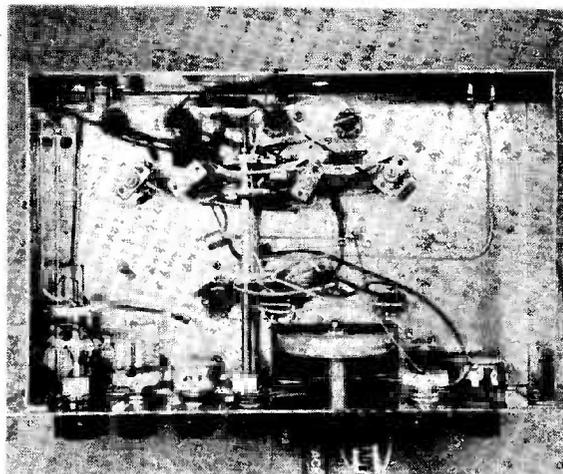With some frequencies and transmissions, adding an earth will bring about no significant improvement. With other signals (such as weak Top Band amateurs) adding an earth will increase volume very considerably.



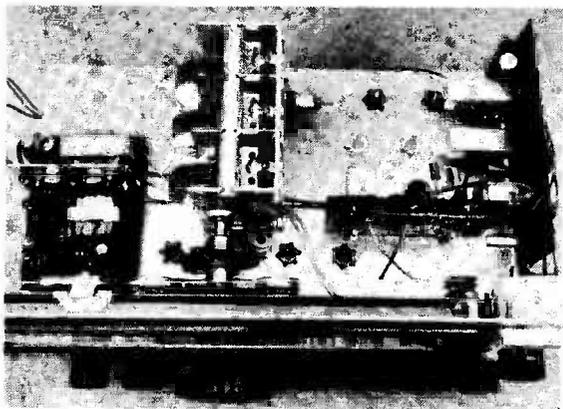Photographs show underside and above views of the complete receiver.



## Other Points

R38 and R9 are chosen to drop just over 3V with a current slightly in excess of 10mA. Since D1 maintains 5.6V, 3.4V must be dropped with a 9V supply. The fairly high resistor values are to help reduce current lost through D1.

Though the values shown should prove satisfactory with 10% resistors and some variation in the actual controlled voltage of D1, a stabilised supply may no longer be obtained, when the battery voltage falls even slightly. If so, R9 should be slightly reduced. Battery drain, with no signal, should be about 20-25mA, with VR1 at maximum. ■

# ELECTROVALUE

Everything brand new and to specification • Large stocks • Good service

## RESISTORS :

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82Ω-220KΩ	E12	18	16	15
CC	1/8W	5%	4.7Ω-830KΩ	E24	2.5	2	1.75
C	1/4W	10%	4.7Ω-10MΩ	E12	2.5	2	1.75
C	1/2W	5%	4.7Ω-10MΩ	E24	3	2.5	2.25
MO	1/2W	2%	10Ω-1MΩ	E24	9	8	7
C	1W	10%	4.2Ω-10MΩ	E12	6	5	4.5
WW	1W	10% + 1/20Ω	0.22Ω-3.3Ω	E12	15d all quantities		
WW	3W	5%	12Ω-10KΩ	E12	15d all quantities		
WW	7W	5%	12Ω-10KΩ	E12	18d all quantities		

Codes : C = carbon film, high stability, low noise.  
MO = metal oxide, Electrofil TR5, ultra low noise.  
WW = wire wound, Plessey.

Values : E12 denotes series: 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and their decades.  
E24 denotes series: as E12 plus 1.1, 1.3, 1.6, 2, 2.4, 3, 3.6, 4.3, 5.1, 6.2, 7.5, 9.1 and their decades.  
Prices are in pence each for quantities of resistors of same ohmic value and power rating NOT mixed values.  
(Ignore fractions of one penny on total resistor order.)

## COLVERN 3 WATT WIRE-WOUND POTENTIOMETERS :

10KΩ, 15Ω, 25Ω, 50Ω, 100Ω, 150Ω, 250Ω, 500Ω, 1KΩ, 1.5KΩ, 2.5KΩ, 5KΩ, 10KΩ, 15KΩ, 25KΩ, 50KΩ. Price only 5/6 each.

## CARBON TRACK POTENTIOMETERS : Double wiper ensures minimum noise level.

Long plastic spindles. each  
Single gang linear: 220Ω, 470Ω, 1K etc. to 2.2MΩ 2/6 Log/Anti-log: 10K, 47K, 1MΩ only 8/6  
Single gang log: 4K7, 10K, 22K, etc. to 2.2MΩ 2/6 Dual anti-log: 10K only 8/6  
Dual gang linear: 4K7, 10K, 22K etc. to 1MΩ 8/6 Any type with 1 amp. double pole mains switch extra 2/3  
Dual gang log: 4K7, 10K, 22K etc. to 2M2Ω 8/6

FETS n-channel low cost general purpose 2N5163, 25 volt, only 5/- each.  
Audio/f.f. Texas 2N3819 8/6, Motorola 2N5459 (MPF103) 9/9 each, Motorola 2N5457 (MPF103) 9/9 each.

NEW PLESSEY INTEGRATED CIRCUIT POWER AMPLIFIER TYPE SL403A. Only 48/6 nett. Operates with 18V power supply. Sensitivity 20mV into 20MΩ, 3 watts into 7.5Ω. Applications data with two or more. PE Nov. 69 Stereo Amplifier kit less metal work £11/18/- NET complete.

## 30 WATT BAILEY AMPLIFIER COMPONENTS :

Transistors for one channel £7/5/6 list, with 10% discount only £6/11/0.  
Transistors for two channels £14/11/0 list, with 15% discount only £12/7/5.  
Capacitors and resistors for one channel list £2.  
Printed circuit board free with each transistor set.  
Complete unregulated power supply kit £4/17/6 mono or stereo, subject to discount.  
Complete regulated power supply kit £9/5/- subject to discount. Further details on application.

## SINCLAIR IC.10 Integrated Circuit Amplifier and Pre-amplifier.

This remarkable monolithic integrated circuit amplifier and pre-amp now available from stock. The equivalent of 13 transistor/18 resistor circuit plus 3 diodes and the first of its kind ever. It is d.c. coupled and applicable to an unusually wide range of uses as detailed in the manual provided with it. As advertised, post free 59/6 NET.

## CARBON SKELETON PRE-SETS.

Small high quality, type PR: Linear only, 100Ω, 220Ω, 470Ω, 1KΩ, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1MΩ, 2M2, 5M, 10MΩ vertical or horizontal mounting, 1/- each.

S-DeCs put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC only 30/6 post free. Compact T-DeC, increased capacity, may be temperature-cycled T DeC only 51/- post free. Full range available.

## CAPACITORS: All new stock

High ripple current types:  
2000µF 25V 7/4; 2000µF 50V 11/4; 5000µF 25V 12/6; 5000µF 50V 21/11; 1000µF 100V 16/3; 2000µF 100V 28/9; 5000µF 70V 36/-; 5000µF 100V 58/3; 1000µF 50V 8/2; 2500µF 64V 15/5; 2500µF 70V 19/6.

### Medium electrolytics

Axial leads: Values (µF/V):  
50/50 2/-; 100/25 2/-; 100/50 2/6; 250/25 2/6; 250/50 3/9; 500/25 3/9; 1000/10 3/3; 500/50 4/6; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-; 3030/25 2/6.

### Small electrolytics

Axial leads: 5/10, 10/10, 25/10, 50/10 1/- each, 25/25, 47/25, 100/10, 220/10 1/3 each.

## PEAK SOUND ENGLEFIELD KITS

Brilliant new styling and available in two forms: Stereo 15 watts per channel in kit form with complete amplifier and pre-amplifier modules and power supply. Build it 12 + 12 or 25 + 25. Output per channel into 15Ω, 12 watts R.M.S. Price £38/9/- net

25 WATTS PER CHANNEL. As above but Output per channel into 15Ω, 25 watts R.M.S. Price £58/15/- Net. Brief specification: Total harmonic distortion 0.1%. Inputs: Magnetic, Ceramic, Tape, Radio. Signal to noise ratios: Better than 60dB all inputs. O/load factor 28dB all channels.

ENGLEFIELD CABINET to house either above assemblies (as illustrated) 46 Net. OTHER PEAK SOUND PRODUCTS AS ADVERTISED.

## MULLARD Sub-min electrolytic C426

range: Price 1/3 each. Axial leads. Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/48/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5µF/V.

Wavechange switches: 1P 12W; 2P 6W; 3P 4W; 4P 3W long spindles, 4/9 each.  
Slider switches, double pole double throw 3/- each.

## BARGAINS IN NEW TRANSISTORS

All power types supplied with free insulating sets

2N696	5/6	2N5192	25/-
2N697	5/6	2N5195	28/3
2N706	2/9	4036	12/6
2N1132	9/9	40362	16/-
2N1302	4/-	AC126	6/6
2N1303	4/-	AC127	6/-
2N1304	4/6	AC128	6/-
2N1305	4/6	AC176	11/-
2N1306	6/9	ACY22	3/9
2N1307	6/9	ACY40	4/-
2N1308	8/9	AD140	19/-
2N1309	8/9	AD149	17/6
2N1613	6/-	AD161	16/-
2N1711	7/-	AD162	comp. pr.
2N2218	9/3	AF118	16/6
2N2147	18/9	AF124	7/6
2N2369A	5/3	AF127	7/-
2N2644	10/9	BA102	9/-
2N2924	4/-	BC107	2/9
2N2925	4/6	BC108	2/6
2N2926R	2/3	BC109	2/9
2N2926O	2/3	BC147	3/6
2N2926Y	2/3	BC148	3/3
2N2926G	2/3	BC149	3/6
2N3053	5/6	BC153	10/-
2N3054	14/3	BC154	11/-
2N3055	16/-	BC157	3/9
2N3391A	6/3	BC158	3/6
2N3702	3/6	BC159	3/9
2N3703	3/3	BC167	2/6
2N3704	3/9	BC168	2/6
2N3705	3/5	BC169	2/3
2N3706	3/3	BC177	6/3
2N3707	4/-	BC178	5/8
2N3708	3/-	BC179	6/-
2N3709	3/-	BD121	18/-
2N3710	3/6	BD123	24/3
2N3711	3/11	BF178	10/6
2N3904	7/6	BFX29	10/9
2N3906	7/6	BFX85	8/3
2N3731	24/-	BFX88	6/9
2N4058	5/3	BSX20	3/9
2N3325	10/9	BFY50	4/6
2N3794	3/3	BFY51	4/3
2N4284	3/3	MJ480	21/-
2N4286	3/3	MJ481	27/-
2N4289	3/3	MJ491	30/-
2N4291	3/3	P346A	4/6
2N4292	3/3	V405A	7/9
2N4410	4/9	NKP403	15/6
		NKP405	15/-

MAIN LINE AMPLIFIER KITS as advertised. Prices Net. Authorised dealer.

## COMPONENT DISCOUNTS :

10% on orders for components for £5 or more.  
15% on orders for components for £15 or more.  
(No discount on net items.)

## POSTAGE AND PACKING :

Free on orders over £2.  
Please add 1/6 if order is under £2.  
Overseas orders welcome; carriage charged at cost.

# ELECTROVALUE


(Dept. PW. 4) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY.

Telephone: Egham 5533 (STD 0784-3)

Open 9 — 5.30 Sats. 1 p.m.

# F.A.L. 'PHASE 50'

## Public Address Amplifier

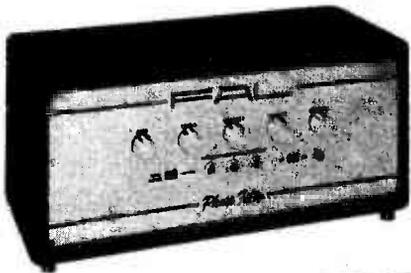

A superb solid state A.C. Mains unit for vocal and Instrumental groups and General Public Address use.

# 29 Gns

Recommended Retail price

- ★ 50 Watts Output (Peak Rating)
- ★ High Sensitivity
- ★ Output matching for speakers from 3-30 ohms
- ★ 3 separately controlled inputs
- ★ Separate Bass and Treble Controls
- ★ Frequency Response 22c.p.s. to 30Kcs.

SEND S.A.E.  
FOR FULLY  
DESCRIPTIVE  
LEAFLET

Available from your local Dealer  
Wholesale and Retail enquiries to Manufacturers  
**FUTURISTIC AIDS LTD, 103 Henconner Lane, Leeds 13**

## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED

**SETS** 1R5, 1R5, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for 1R5, DAF96, DF 96, DK96, DL96, 4 FOR 27/-.

0Z4	4/8	12X8GT	7/8	DK32	7/8	EF183	5/9	PCF808	14/9	UBC41	9/-
1A7GT	7/8	12SN7GT	7/8	DK91	5/9	EF304	6/8	PCL82	7/8	UBF80	5/9
1H6GT	7/8			DK92	8/8	EF390	6/8	PCL83	10/-	UBF89	6/9
1N5GT	7/9	19BG6G17/8		DK98	7/3	EL33	9/8	PCL84	7/8	UCB84	7/-
1R5	5/9	20F2	13/8	DL35	5/-	EL34	9/8	PCL86	9/-	UCB85	7/8
1R5	4/8	20F3	11/9	DL92	5/9	EL41	11/-	PCL86	8/8	UCF80	7/8
1T4	2/9	20P4	18/8	DL94	6/9	EL84	4/9	PEN44	18/8	UCH42	12/-
3R4	5/9	25L6GT	5/-	DL96	7/8	EL90	4/8	PFL200	11/9	UCH81	6/8
3V4	6/9	25U4GT11/8		DY86	5/9	EL650	12/8	PL36	9/9	UCL82	7/8
5Y3GT	5/9	30C1	6/8	DY87	5/9	EM80	7/8	PL81	3/9	UCL83	11/9
5Z4G	7/8	30C15	13/-	EABC80	6/8	EM81	7/8	PL81A	3/9	UF41	10/8
6/80L2	12/-	30C17	18/-	EAP42	10/-	EM84	6/9	PL82	6/8	UF80	7/-
6AL5	2/8	30C18	14/-	EB91	2/8	EM87	7/8	PL83	9/8	UF85	6/9
6AM3	2/8	30P5	12/-	EB33	8/-	EY1	7/9	PL84	5/8	UF89	6/9
6AQ5	4/8	30PL1	13/9	EB34	9/8	EY26	6/8	PL600	15/-	UL41	10/9
6AT6	4/-	30PL12	14/8	EBF80	6/9	EZ40	5/-	PL504	13/8	UL44	20/-
6AU6	4/8	30PL14	14/9	EBF89	6/8	EZ41	5/-	PL508	23/8	UL84	7/-
6BA6	4/8	30L1	6/8	ECC81	3/9	EZ80	4/8	PM84	7/8	UM84	6/8
6BE6	4/9	30L15	14/-	ECC82	4/9	EZ81	4/9	PX25	10/8	UY41	7/8
6BJ6	8/8	30L17	15/8	ECC83	7/-	GZ32	3/9	PY32	10/-	UY85	5/9
6BW6	13/-	30P4	12/-	ECC85	5/-	GZ34	9/9	PY33	10/-	VP4B	10/-
6F13	3/8	30P12	12/9	ECC91	3/-	KT61	9/9	PY81	5/8	W119	7/-
6F14	9/-	30P19	12/-	ECC94	12/-	KT66	16/9	PY82	5/8	Z77	3/9
6F23	14/8	30PL1	12/9	ECP80	6/8	N78	17/8	PY88	5/8	Transistors	
6F25	12/-	30PL13	15/8	ECP82	8/-	PABC80	7/-	FY88	5/8	AC107	3/8
6J6	3/-	30PL14	16/8	ECH35	6/-	PC86	10/8	PY800	7/8	AC127	2/8
6K7G	2/8	35L6GT	8/8	ECH42	13/8	PC88	10/8	PY801	6/8	AD140	7/8
6K8G	2/9	35W4	4/8	ECH81	5/8	PC86	8/8	R19	6/8	AF116	3/8
6L18	6/-	35Z4GT	5/-	ECH83	8/8	PC97	8/8	R20	12/8	AF118	3/-
6SN7GT	4/8	6083	12/8	ECH84	7/8	PC900	7/8	U26	12/-	AF117	4/8
6V6G	3/8	AC/VP2	10/-	ECL80	7/-	PC84	6/8	U26	12/8	AF125	3/8
6V8GT	8/8	AZ31	8/8	ECP82	6/9	PC85	6/-	U47	12/8	AF127	3/8
6X4	4/8	B729	12/8	ECL83	8/8	PC88	9/-	U49	12/8	OC26	5/8
6X5GT	5/9	CCH35	13/8	ECL86	8/-	PC89	10/8	U78	4/3	OC44	2/8
7B7	7/-	CL33	13/8	EF37A	6/8	PC189	11/8	U191	12/8	OC45	2/8
7C6	6/9	CY31	6/9	EF39	4/9	PCF80	6/8	U193	8/8	OC71	2/8
10F1	14/-	DAC32	7/8	EF41	10/9	PCF82	6/8	U251	14/8	OC72	2/8
10F18	7/-	DAF91	4/8	EF80	4/8	PCF86	12/-	U301	10/8	OC75	2/8
10F18	12/-	DAF96	7/8	EF85	5/8	PCF200	13/8	U323	14/8	OC81	2/8
12A7T	3/9	DF33	7/9	EF86	6/8	PCF800	13/8	U301	13/8	OC81D	2/8
12AU6	4/9	DF91	2/9	EF89	5/3	PCF801	6/9	UAB30	6/8	OC82	2/3
12AU7	4/9	DF96	7/8	EF91	2/9	PCF802	9/-	UAF42	10/8	OC82D	2/8
12AX7	4/9	DE77	4/8	EF94	4/8	PCF805	14/-	UB41	6/8	OC170	2/8

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra

HOME RADIO (Components) LTD. Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD. Phone 01-648 8422



## Why live the HARD way?

## We're making life EASY for you!

We've never seen the sense in wasting time and energy tramping round the shops trying to locate components for radio and electronic projects—especially when the British weather turns it into a battle worse than a lone journey across Antarctica! That's why we issue the Home Radio Components Catalogue which for many years has enabled thousands of enthusiasts to order by post. We've built up a mail-order service which for speed and efficiency is second to none. But recently we've gone a step further in making life easy for you. Now you need not even walk round to the post box. With our Credit Account Service you can just telephone—any time of day or night, week-ends included! If your call comes out of shop hours a recording machine takes your message for us to deal with when we open next day. For full details just drop us a line or phone 01-648 8422.

After you have availed yourself of the service for 12 months we regularly send an up-to-date catalogue—FREE.

If you've not already got a Home Radio Catalogue, send the coupon with cheque or P.O. for 12/- (8/6 plus 3/6 P. & P.). Even if you don't intend to use our Credit Account Service you certainly need the catalogue—it has 350 pages, lists over 8,000 components and has over 1,500 illustrations!



Please write Name and Address in block capitals

NAME .....

ADDRESS .....

HOME RADIO (COMPONENTS) LTD., Dept. PW,  
234-240 London Road, Mitcham, Surrey, CR4 3HD

# P.W. GUIDE TO COMPONENTS

PART 16

M. K. TITMAN, B.Sc. (Eng)

## INTEGRATED CIRCUITS

**A**N integrated circuit may be defined as a multi-element circuit module constructed and encapsulated in such a way that the individual elements cannot be isolated by normal bench techniques. They can be divided into various groupings categorised by the constructional methods employed in manufacture. Figure 1 illustrates diagrammatically the basic groupings.

The two basic categories of integrated circuits are thin film circuits—which contain no active semiconductor devices—and semiconductor circuits which contain active semiconductor components. Two methods of construction are used to produce semiconductor integrated circuits and these are known as monolithic and hybrid integrated circuits. Hybrid circuits consist of many discrete circuit elements, such as diode and transistor chips bonded to a header and interwired, whilst monolithic circuits consist of a single silicon die with both active and passive components diffused into the surface.

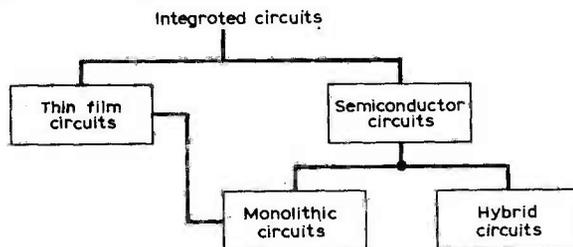


Fig. 1: Basic groupings of integrated circuits.

At present the great majority of integrated circuits available commercially are of monolithic construction, as this form is best suited to mass production techniques. Thin film and hybrid circuits are usually manufactured to suit a particular requirement and are more suitable for small production runs. For example, a manufacturer of, say, missiles would use hybrid or thin film circuits for special applications such as i.f. amplifiers, whilst for switching or logic functions standard monolithic logic circuits would be used. The i.f. amplifiers would be built to the manufacturer's requirements of performance, and in all probability could not be used by other manufacturers.

It follows therefore that the majority of integrated circuits available are of monolithic construction. However thin film techniques are used in monolithic construction for the formation of end connections, resistors and capacitors.

### Thin Film Circuits

Thin film circuits are manufactured by depositing layers of metals or metallic compounds on to the surface of a high resistivity substrate to form resistor combinations, capacitors or inductors. A typical thin film circuit is shown diagrammatically in Fig. 2. Three types of substrate are in common use: glass, ceramic and glazed ceramic. When compatible thin film circuits are deposited on monolithic silicon structures then the substrate is a layer of oxidised silicon.

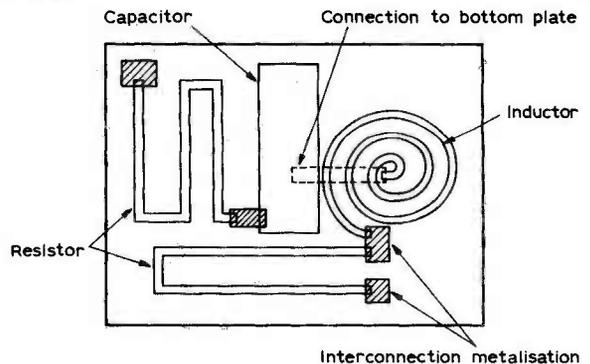


Fig. 2: Typical thin film circuit.

The required materials are deposited on to the substrate by a variety of methods of which the most common are vacuum evaporation, sputtering, gas plating and silk screening. Silk screen layers are deposited in the required pattern by the actual process whereas in all the other processes further work is required, patterning being achieved by a photographic (photoresist) and etching system.

Perhaps the most common deposition system is vacuum evaporation and this is used for gold, silver, aluminium and nichrome (NiCr). The pure metals are used for capacitor plates, inductor windings, and connections and interwiring—whilst nichrome forms the basis of most thin film resistors. Vacuum evaporation is achieved by the evacuation of a glass bell-shaped chamber and rapidly heating the material to be deposited by an electric current through a separate filament. The substrate is positioned near the material, which vaporises, and

collects part of the condensate as a thin film over its surface. Subsequent etching then produces the required pattern to give the desired characteristics.

Cathode sputtering is used to deposit tantalum to form resistors or oxidised to form capacitors. In this case deposition is due to bombardment of a tantalum cathode by high energy inert gas particles (often Argon). The substrate is placed at the anode of a highly evacuated jar and the released tantalum atoms are attracted by a high d.c. (or occasionally a.c.) potential difference between anode and cathode. The tantalum atoms impinge on the substrate and adhere, thus building a thin film on to the surface.

Gas plating is used for the production of films of silicone dioxide ( $\text{SiO}_2$ ), aluminium silicate ( $\text{Al}_2\text{O}_3\text{SiO}_2$ ) and aluminium oxide ( $\text{Al}_2\text{O}_3$ ), which are used as dielectric layers for capacitors. The chemical reactions are complex and depends upon either hydrogen reduction or thermal decomposition of compounds. The compound in vapour form is passed over the heated substance and decomposition or a chemical reaction takes place to leave the required dielectric layer.

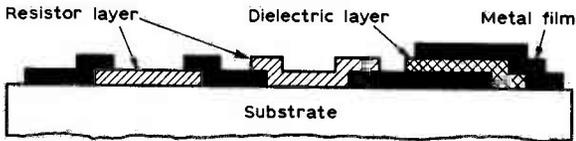


Fig. 3: Cross section of thin film circuit.

We have seen how resistors, capacitors and inductors may be formed and Fig. 3 shows a cross section through a typical thin film surface. Only passive components, however, can be produced by these techniques and although passive filters, attenuators etc. are often required system flexibility is limited. In order to combat these limitations transistor chips, which are manufactured separately, can be bonded to the surface of the film. Wire interconnections are used and hence extremely flexible circuits can be produced. A typical thin film r.f. amplifier is shown in Fig. 4.

Now ideally all-integrated circuits should display the same characteristics as equivalent discrete component circuits, but in practice, because of the close proximity of components, parasitic capacitive and inductive effects are present. These parasitic effects require careful consideration in the initial design.

Another problem resulting from the close proximity of components is leakage paths along the surface of the substrate. Substrates are specifically chosen to reduce surface leakage and these effects are further reduced by careful layout. One considerable advantage of thin film circuits lies in the close component tolerances and wide range of values which can be achieved.

## Hybrid Circuits

Hybrid semiconductor circuits are formed by bonding discrete components to a header and interwiring with wire. A typical hybrid circuit is shown in Fig. 5. The header forms part of a TO-5 size transistor case with 10 leads. The discrete transistor chips are usually normal production line transistors whilst the capacitors, resistors and inductors are specially produced to fulfill the circuit requirements.

Interwiring with gold wire is carried out by hand using special micromanipulators and microscopes. This form of fabrication results in an expensive component. However, the yield is high because each component is tested prior to assembly. Hybrid

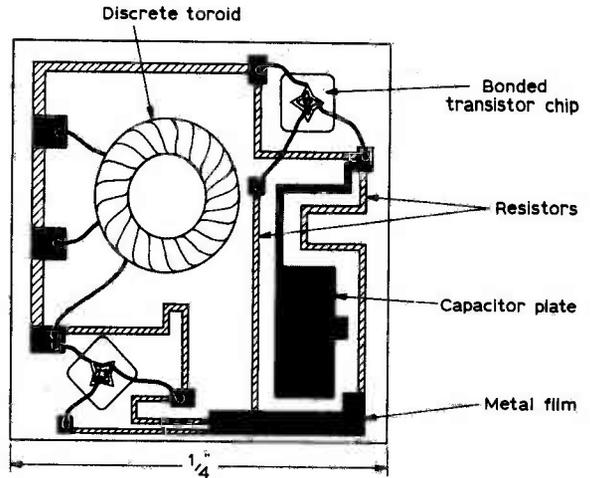


Fig. 4: Some of the components of a thin film r.f. amplifier.

circuits are therefore similar to conventional circuits except that fabrication is carried out in a micro-miniature assembly. Development is thus considerably simplified as breadboard models can be constructed and the layout tested without investing in costly processes. Because each component is manufactured separately the flexibility of the system is considerable, since every transistor can be chosen for individual characteristics and no component relies on the characteristics of other components. Thus hybrid construction is the costliest production system as a result of the non-automatic assembly techniques but requires considerably less development time to produce.

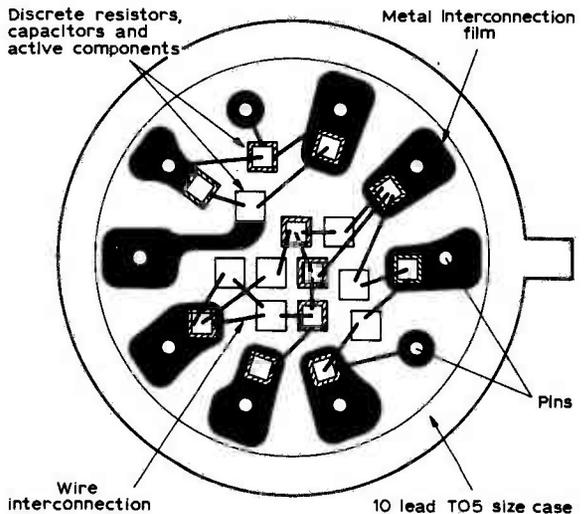


Fig. 5: Hybrid integrated circuit.

Hybrid circuits therefore are particularly suitable for small quantity requirements and production runs. Because of the flexibility, elaborate and close

## DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with call push button, connectors and master inter-com. Simply plugs together. Originally sold at £10. Special snip price 49/6, plus 3/6 postage.



## 5A, 3 PIN SWITCH SOCKETS

An excellent opportunity to make that bench dis board you have needed or to stock up for future jobs. This month we offer 6 British made (Hicraft) bakelite flush mounting shuttered 5A switch sockets for only 10/- plus 3/6 post and ins. (20 boxes post free).

## TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for GBA screw. 7/6 HUCKLED MODEL FOR F.M. 9/6.

## PHILIPS TRIMMER

0-30 pf an old design but one which has never been bettered. 1/- each, 10/- doz. £4.0.0 per 100.

## PP3 BATTERY ELIMINATOR

Run your small transistor radio from the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 8/6 each.

## TOGGLE SWITCH

3 amp 250v. with fixing ring. 1/6 each 15/- doz.

## DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything plus full instructions. 19/6 plus 2/6 post and insurance. Made up model 37/6 plus 2/6 p. & p.

## 230 VOLT SOLENOID

1/2in. stroke. Size 2 1/2in. x 2in. x 1 1/2in. 14/6, postage 2/9.

## 13 AMP FUSED SWITCH

Made by G.E.C. For connecting water heater etc. into 13 amp ring main. Flush type 3/6 each 30/- doz. Metal boxes for surface mounting 1/6 each 15/- doz.

## MICRO SWITCH

5 amp. changeover contacts. 1/9 each 18/- doz. 15 amp Model 2 each or 21/- doz.

## ISOLATION SWITCH

20 amp D.P. 250 volts. Ideal to control Water Heater or any other appliance. Neon indicator shows when current is on. 4/6 48/- per dozen.

## SUPPRESSOR CONDENSER TCC

.1 mfd. 250v. A.C. working, metal cased with fixing lugs. 1/9 each 18/- doz.

## 15/20 AMP CONNECTORS

Polythene insulated 12-way strip. 2/6 each 24/- doz.

## MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters etc. New and perfect. Snip at 9/6. Postage 3/- for first then each one ordered. 12 and over post free.

## 0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits. 2/6 each. 24/- doz.

250V AC working condensers for power factor correction, motor starting etc. 3 mfd. 6/6 each, 6.5 mfd. 8/6 each, 8 mfd. 9/6 each.

3 amp battery charger kit comprises copper backed circuit board, 3 amp mains transformer, regulator resistors and smoothing condenser 29/6 inc. wiring diagram, post & ins. 4/6.

## VARIAC CONTROLLERS

With these you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to dim lighting. We offer a range of these, ex-equipment but little used and in every way as good as new. Any not so, will be exchanged or cash refunded. Any not so, 2 amp £4.19.6, 5 amp £7.19.6, 8 amp £12.19.6, 10 amp £15.19.6. Note: Some of these are panel mounting types



## HOUR COUNTERS

If you wish to know how long your equipment has been switched on then this is what you need. Counts running time up to 9999 hours. 50 c/s mains operation. 49/6 plus 3/6 post & insurance. Resettable type 69/6 plus 3/6 post & insurance.



## 24 HOUR TIME SWITCH

Mains operated. Adjustable Contacts give 2 on/off periods per 24 hours. Contracts rated 15 amps. repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 with Perspex cover, plus 3/6 postage and insurance. a real snip which should not be missed.




## DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets and on/off switch with supplied complete with 7 feet of heavy cable. neon warning light in metal box. Takes standard 13 amp fused plugs 39/6 wired up, ready to work plus 4/6 post & insurance.
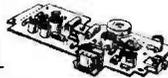
## 1 WATT AMPLIFIER & PREAMP

5 transistors—highly efficient, made for use with tapehead G4 but equally suitable for microphone or pick up—limited quantity 29/6 Full circuit diag. also shows tape controls 5/-



## THIS MONTHS SNIP

### 1 HOUR MINUTE TIMER

Made by famous Smiths company, these have a large clear dial, size 4 1/2 x 3 1/2, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch 22/6



## VARYLITE

Will dim incandescent lighting up to 600 watts from full brilliance to about 1/2. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mount on surface. Price complete in heavy plastic box with control knob £3.19.6.

## MINIATURE EXTRACTOR FAN

Beautifully made by famous German Company. PAPST System. 230/240 A.C. Mains operated, size 3 1/2in. x 3 1/2in. Made for instrument cooling but ideal to incorporate in a cooker hood, etc. 65/-

## STANDARD WAFER SWITCHES

Standard Size 1 1/2 wafer—silver plated 5 amp contact standard 1/2 spindle 2in. long—with locking washer and nut.

Poles	2 way	3 way	4 way	5 way	6 way	8 way	10 way	12 way
1 pole	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
2 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
3 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
4 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
5 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
6 poles	5/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
7 poles	6/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
8 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
9 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
10 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
11 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6
12 poles	10/6	10/6	10/6	10/6	10/6	10/6	10/6	10/6

## 15, 30 & 100 WATT H-FI SPEAKERS

FULL FI 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—Sensitivity 3 or 15 ohms—Mains resonance 60 c.p.s.—Chassis Diam. 12in.—12 1/2in. over mounting lugs—Baffle hole 1 1/2in. Diam.—Mounting holes 4. holes—3/4in. diam. on pitch circle 1 1/2in. diam.—Overall height 5 1/2in. A £6 speaker offered for only £3.19.6 plus 7/6 p. & p. Don't miss this offer. 15in. 25 watt £7.19.6 18in. 100 watt £19.10.0.

## 3kW TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 79/6. Postage and insurance 6/6. Don't miss this.

Where postage is not stated then orders over £3 are post free. Below £3 add 2/9. Semi-conductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

## MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 3/6 each. 36/- dozen, your assortment



## WATERPROOF HEATING ELEMENT

26 inches length 70W. Self-regulating temperature control. 10/- post free.

## BLANKET SWITCH

Double pole with neon let into side so luminous in dark, ideal for dark room light or for use with waterproof element, new plastic case 5/6 each, 3 heat model 7/6.



## COPPER CLAD ELEMENT

1250 watts—4ft. long but bent to U shape, ideal for overhead heater—just mount reflector above. 12/6 each, plus 4/6 post. £6 doz. post paid.

## HEAT & LIGHT LAMP

275W. internally mirrored bulb, with b.c. end for plugging into lamp holder. 19/6 each plus 4/6 post and insurance.

## TUBULAR HEAT & LIGHT LAMP

Philips 500W. 29/6 plus 4/6 post and insurance.

## ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



## THERMOSTATS

Type "A" 15 amp. for controlling room heaters, greenhouses, drying cupboard. Has spindle for pointer knobs. Quickly adjustable from 30-80°F. 9/6 plus 1/- post. Suitable box for wall mounting. 5/-, P. & P. 1/-

Type "B" 15 amp. This is a 17in. long rod type made by the famous Synvic Co. Spindle adjusts from 30-55°F. Internal screw alters the setting so this could be adjustable over 30° to 1000°F. Suitable for controlling furnace, oven, kiln, immersion heater or to make flame-stat or fire alarm. 8/6 plus 2/6 post and insurance.

Type "D". We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amps. Has many uses one of which would be to keep the loft pipes from freezing. If a length of our blanket wire (16 yd 10/-) is wound round the pipes. 7/6. P. & P. 1/-

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperatures from 16, plus 1/4 post. This "E" Glass enclosed for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemists' baths of all types. Adjustable over range 50° to 150°F. Price 18/- plus 2/- post and insurance.

## RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kits comprises two special transistors and all parts including probe tube and crystal earpiece. 29/6—twin stetho- set instead of earpiece 11/- extra—post and ins. 2/9.



## BECKASTAT

This is an instant thermostat, simply plug your appliance into it and its lead into wall plug. Adjustable setting for temperatures. 13A loading Will save its cost in a season. 19/6. Post and insurance 2/9.



## MAINS TRANSFORMER SNIP

Making a power pack for amplifier or other equipment? These transformers have normal mains primaries (230/240v.) and isolated secondaries two types (1) 12v. 500mA. at 8/6; (2) 15v. 500mA at 8/6.



# ELECTRONICS (CROYDON) LTD

Dept PW 266 London Road, Croydon CRO-2TH  
Also 102/3 Tamworth Road, Croydon

# TECHNICAL TRAINING

## *in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

*Many diploma and examination courses available, including expert coaching for:*

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

**Examination Students coached until successful**

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

#### INTERNATIONAL CORRESPONDENCE SCHOOLS

EST. 1891

Dept. 171, Intertext House, Stewarts Road, London, S.W.8.  
Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam).....

NAME .....


ADDRESS.....

4/70

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

# BETTER Bargains Service FROM TRS
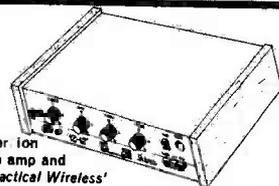
## BUILD THIS FINE VERSION OF THE PW.12-12 WITH A TRS KIT



T.R.S. have produced their own kit version of this outstanding combined stereo amp and pre-amp. It conforms precisely to *Practical Wireless'* excellent circuit but is styled for a flatter, more conventional cabinet which will be available shortly. Kit includes two-tone front panel and control knobs, components and transistors.

Inputs—Mag. P.U. (R.I.A.A.) 2.5mV into 68 Kohms; Ceramic P.U. and Radio; Response 20Hz to 30KHz  $\pm$  1dB. Output—12 watts per channel. R.M.S. into 15 ohms.

Kit complete, less cabinet **£24.10.0** (Carr. 7/6) *Power Amplifier & Pre-amp Kits available separately. S.A.E. brings list.*

## AMPLIFIERS

Styled and kitted by T.R.S., using quality components, including valves or transistors as necessary and excellent instructions. Backed by T.R.S. service.

**MULLARD 5-10.** Basic kit (requires pre-amp). Input Sensitivity—40mV; Response 20Hz-15KHz  $\pm$  1dB; Output 10 watts R.M.S. at 3 or 15 ohms. KIT **£10.0.0**. BUILT **£13.0.0** (Carr. either, 7/6).

**MULLARD 2 VALVE PRE-AMP.** Switching for 5 inputs; base/treble/volume controls, etc. Sensitivity at Input—4mV max. Into 80K-1 Megohms; Response 20-25,000Hz  $\pm$  1dB. KIT **£6.10.6**. BUILT **£9.10.0** (Carr. either 5/6).

**MULLARD 10-10 STEREO AMPLIFIER.** Input sensitivity—210mV per channel; Response 12Hz-35KHz  $\pm$  3dB; 10 watts R.M.S. output per channel into 3 or 15 ohms. KIT **£18.0.0**. BUILT **£22.10.0** (Carr. either 12/6).

Basic Kit (no panel or controls) **£17.0.0**. Built **£21.0.0**. Pre-amp must be used here.

**MULLARD 2+2 STEREO PRE-AMP** with same characteristics per channel as mono pre-amp (+ balance). BUILT **£13.10.6** (Carr. 7/6).

**T.R.S. 4+4 ECONOMY STEREO.** Modular assembly. With cabinet power supply and Din plugs. 4 watts per ch. into 8-15 $\Omega$  **£12.10.0** (Carr. 7/6).

**50 & 100 WATT R.M.S. VALVE AMPLIFIERS** for mic., P.A. and instruments, etc. 4, 8/15 $\Omega$  output. Available shortly.

## TUNERS

**T.R.S. 6 VALVE AM/FM.** Self-powered, large scale; push-buttons. Magic eye. Med. Wave and F.M. Diode output per tape. COMPLETE KIT **£12.10.0** (Carr. 7/6).

**T.R.S. FM TUNER.** Transistors, Inter-station suppression, A.F.C. etc. Modular assembly, Modules, chassis, drive etc. come to **£15.15.0** (Carr. 7/6)

Cabinet to match T.R.S. 4+4 **£1.17.6** (Carr. 2/6)  
Power supply **£2.5.0** (Carr. 3/-)  
Decoder for Stereo **£10.10.0** (Carr. 2/6)

## GRAMO UNITS & PLINTHS

**GARRARD SP.25 MK. II.** Manual: Arm and 10 $\frac{1}{2}$ in. die-cast t/table, cueing device, etc. less cartridge. Brand new in maker's carton **£12.7.6**.

**GARRARD LM.2025.** With Sonotone 9TA/HC Stereo Cartridge and lift control **£10.10.6** (Carr. 7/6)

Garrard WB.1 Plinth **£3.12.0** (Carr. 5/-)

Garrard CLEARVIEW Cover SCP.1 **£3.7.6** (Carr. 4/6)

Garrard Scandinavian Type Plinth **£5.5.0** (Carr. 5/-)

## ALWAYS IN STOCK

Resistors in all values; wire-wound resistors; volume controls log or linear, 10K-2meg. Mono 3/6 (with switch 5/-). Stereo 8/6 (with switch, certain values 10/6). Log/antilog balance controls 3/6, capacitors and electrolytics; Vinal speaker covering 48in.—30/- yd; Bondacoust 18in. x 1in. thick 7/- yd; Veroboard; Cir-Kit; valves; transistors, Sinclair products, etc., etc. S.A.E. with enquiries please.

# TRS

**RADIO COMPONENTS  
70 BRIGSTOCK ROAD,  
THORNTON HEATH,  
SURREY**

Open Sats.  
Close early Weds.

1 min. Thornton Heath  
Stn. (Southern)

Phone:  
01-684 2188

tolerance circuits can be achieved. Hybrid construction is consequently rarely used for general purpose mass produced devices.

## Monolithic

The vast majority of integrated circuits available to the amateur are of monolithic construction as this construction is best employed for mass production. Initial design is difficult and costly whilst the actual manufacture is reasonably economic and hence economically priced units are possible only for large demand circuits.

The fabrication of most monolithic structures combines the planar epitaxial transistor process and thin film technology. Only thin film materials and processes which do not damage the basic structure or impurity concentrations, can be employed, and such films are known as compatible thin films. Let us now examine the steps involved in the fabrication of a circuit using both p-n-p and n-p-n transistors. Most other components are manufactured during one or more of these stages.

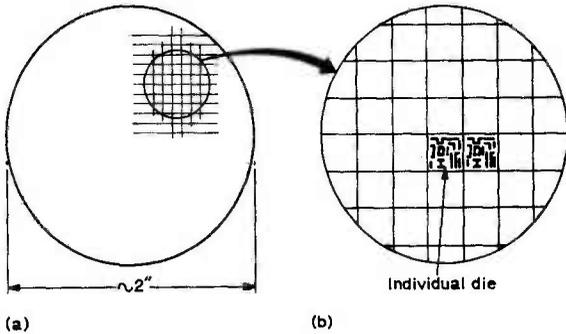


Fig. 6: Monolithic integrated circuit wafer. (a) wafer, (b) enlargement showing dice.

The starting point consists of a p- or n-type silicon wafer such as that illustrated in Fig. 6(a). Fig. 6(b) shows how ultimately the wafer will be subdivided to give individual dies. We will consider only one of the dies and it should be appreciated that in each process perhaps 10-20 wafers each with 100-200 individual integrated circuits are treated simultaneously. In consequence true mass production is carried out in processes which require laboratory standards of accuracy, measurement and cleanliness.

Initially a p-type impurity is diffused into the surface of the basic n-type slice to give the cross section shown in Fig. 8(a). At the end of the diffusion steam is passed over the wafer and forms a layer of silicon dioxide on the surface. The surface is coated with photoresist and the areas to be diffused next masked with an extremely accurate photographic mask. The photoresist is set by exposing the wafer to ultra-violet light and the silicon dioxide is then etched off where the diffusion is required, since diffusion does not penetrate the silicon dioxide layer. The resulting structure is shown in Fig. 8(b).

The second diffusion is known as the isolation diffusion since the areas which are to become components—in this case a p-n-p and an n-p-n transistor—are masked by silicon dioxide. The diffusion is of n-type impurity and is of such a depth as to penetrate through to the n-type substrate, thus forming islands of p-type in the basic n-type sub-

strate as illustrated by Fig. 8(c). At the end of this diffusion a layer of silicon dioxide is again formed to give the structure of Fig. 8(d). The collector of the p-n-p transistor has now been formed by the original p-type diffusion and is isolated from other components by the n-type substrate. This isolation is only effective providing the resultant p-n junction is reverse biased. In consequence an n-type substrate is always electrically connected to the most positive supply voltage and a p-type one to the most negative supply voltage.

In order to reduce the number of diffusions to a minimum it would now seem logical to diffuse the n-type base of the p-n-p transistor and the collector of the n-p-n transistor simultaneously. Unfortunately this is not possible as the impurity concentrations required differ considerably. The n-p-n collector is masked and etched to remove the silicon dioxide. Great care is taken in the alignment of the mask since the final characteristics depend on physical dimensions as well as impurity concentrations. Alignment is aided by instruments but final adjustments are carried out by eye. The n-type diffusion is carried out and a further silicon dioxide layer formed to give the structure shown in Fig. 8(e).

Further masking and diffusions produce the p-n-p transistor base shown in Fig. 8(f) and then by simultaneous p diffusions the p-n-p emitter and n-p-n base shown in Fig. 8(g). The final n diffusion completes the two-transistor structure shown in Fig. 8(h). The interconnecting to other components is carried out by a further mask and etch of the silicon dioxide and the formation of a thin film (often aluminium) interconnection pattern.

Figure 7 shows the schematic of the structure which has been fabricated. Clearly isolation can only be maintained if the isolation diodes  $D_i$  are reverse biased. Also it will be noted in Fig. 8(h) that the substrate and n-p-n transistor form a p-n-p-n structure (or thyristor) which would fire to the

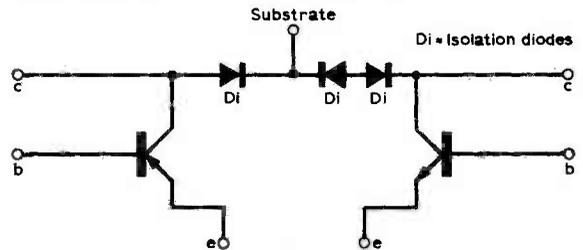


Fig. 7: Schematic of fabricated structure.

saturated condition unless reverse biased. In addition parasitic effects of leakage current, capacitance and inductance are present and these will be discussed later.

## Resistors

As far as possible resistors are formed of semiconductor material usually during the resistive base diffusion which results in medium resistivity semiconductor. Occasionally the low resistivity emitter diffusion is used for low value resistors. Fig. 9 illustrates the structure of such a resistor. Isolation is again achieved by reverse biased pn-junctions. Resistor values of from  $100\Omega$  to  $30k\Omega$  with tolerances of  $\pm 10\%$  can be achieved by this method.

Compatible thin film resistors are manufactured from nichrome, tin oxide, tantalum, aluminium,

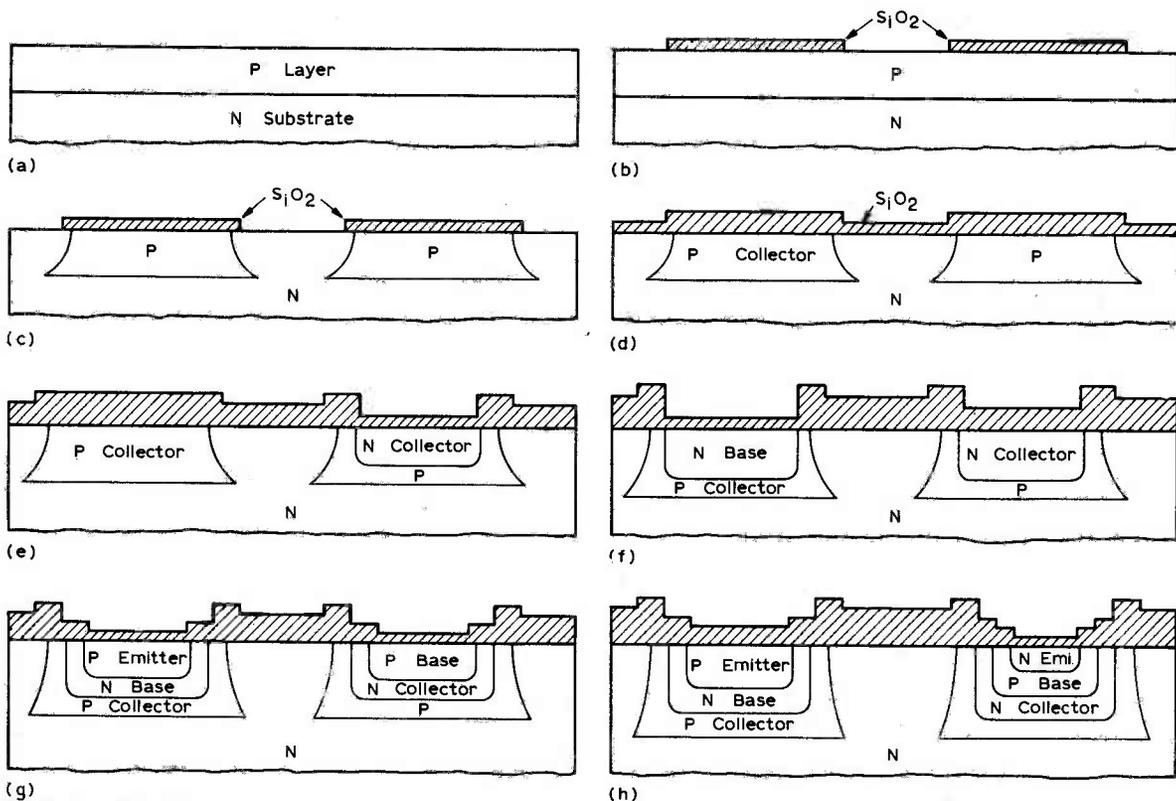


Fig. 8: (a) portion of starting wafer, (b) silicon dioxide masked for transistors, (c) isolation diffusion n type, (d) silicon dioxide grown after diffusion, (e) collector of n-p-n transistor formed, (f) base diffusion of p-n-p transistor, (g) simultaneous p type base and emitter diffusion (h) final n type emitter diffusion.

chromium and nickel. Values from  $20\Omega$  to  $3M\Omega$  can be achieved with tolerances of  $\pm 5\%$ . In all cases the power and voltage ratings are severely limited and are  $3mW$  per square mil maximum power and  $20V$  maximum voltage drop.

of  $2.5pF/mil$  and  $0.3$  to  $0.5pF/mil$  respectively. Tolerances generally are  $\pm 20\%$  and maximum voltage ratings of  $20-50V$ . Q factors vary from  $10-100$  and practical maximum capacitance values are  $1000pF$  or  $5000pF$  for tantalum oxide.

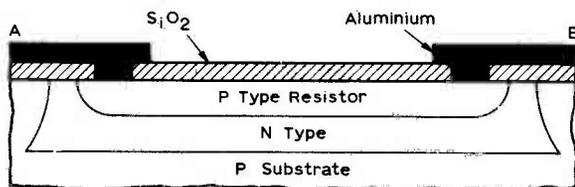


Fig. 9: Diffused resistor structure.

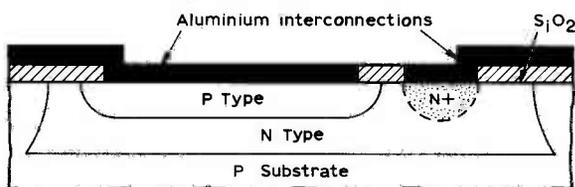


Fig. 10: Diffused capacitor structure.

## Capacitors

Wherever possible capacitors are fabricated from reverse biased diodes and such a structure is illustrated in Fig. 10. However as the isolation of such diodes is achieved by reverse biased junctions considerable parasitic capacitance is present. Where necessary silicon dioxide dielectric capacitors are fabricated to overcome this disadvantage. Silicon dioxide capacitors have the added advantages that they are non-polar and their capacitance is constant with bias voltage.

Thin film capacitors of tantalum oxide and aluminium are also used and give capacitance values

## Inductors


Inductors with practical values of inductance and Q are the most difficult components to produce. Despite the considerable research devoted to inductors it is true to say that their value as an integrated circuit component is severely limited. The maximum practical inductance is limited to  $4\mu H$  with Q factors of  $1-5$  in monolithic structures or  $30-50$  in thin film fabrications.

**TO BE CONTINUED**

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-236 8080. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia, Malawi and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2 5s 0d. PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.


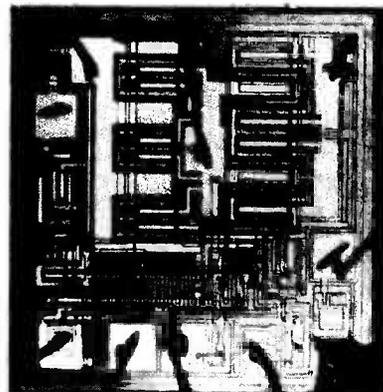
## MONOLITHIC INTEGRATED CIRCUIT HIGH FIDELITY AMPLIFIER AND PRE-AMP



### the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output of 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 Zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required as part of the process of producing monolithic I.C.s are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. This enables us to cover every IC-10 with the Sinclair guarantee of reliability.

#### ■ SPECIFICATIONS

Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz $\pm 1$ dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5mV.
Input impedance	Adjustable externally up to 2.5 M ohms.

#### ■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

#### ■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.


SINCLAIR

**IC.10** with  
IC.10 manual **59/6**

POST FREE

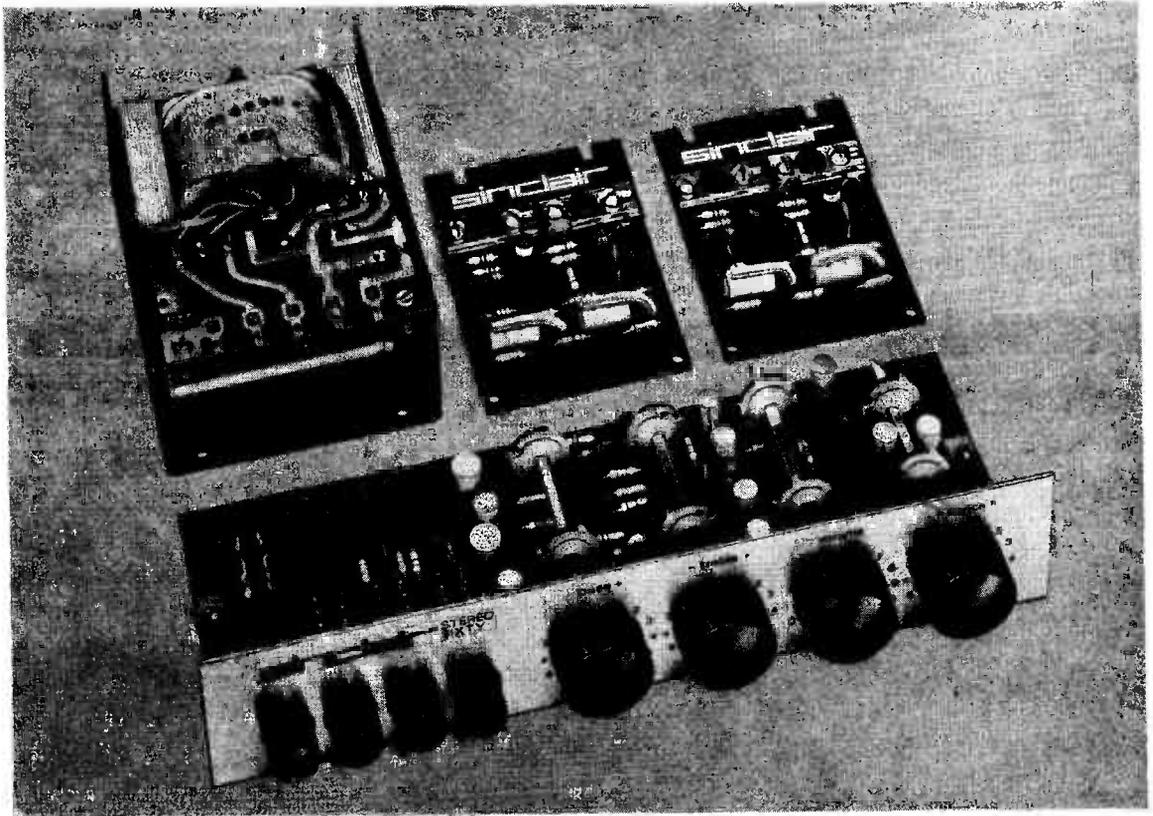**sinclair**

**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD · CAMBRIDGE  
Telephone 0223 52731



## Project 60 an exciting alternative

The buyer of an amplifier today has a remarkably wide variety to choose from. It is unlikely that a purchaser would have real difficulty in finding a unit that met all his requirements, although the price might not be as low as could be wished. The only snags are that one's needs can change and that the technically correct amplifier may be physically inconvenient. If you are confident that there is an amplifier available, of the right size and price, which will meet all your needs for the foreseeable future, then that is your best buy. If not, however, we can offer you another possibility which we believe to be an exciting alternative approach. That alternative is **Project 60**.

Project 60 is a range of modules which connect together simply to form a complete stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare with it in overall performance.

The modules are: **1.** The Z-30 high gain power amplifier, which is an immensely flexible unit in its own right. **2.** The Stereo 60 preamplifier and control unit. **3.** The PZ.5 and PZ.6 power supplies. A complete system comprises two Z-30's, one Stereo-60 and a PZ-5 or PZ-6. The power supplies differ in that the PZ-6 is stabilised whilst the PZ-5 is not. This means that the former should be used where the highest possible continuous sine wave rating is required. In a normal domestic application there will not be a significant difference between using either power unit unless loudspeakers of very low efficiency are being used.

In view of the very high performance of an amplifier system built with Project 60 modules, the cost may seem surprisingly low. There are two reasons for this: Firstly, we are the largest producers of this type of module in Europe and we are able therefore to use highly efficient production methods. Secondly, you are not paying for a cabinet which you may not require anyway.

All you need to assemble your system is a screwdriver and a soldering iron. No technical skill or knowledge whatsoever is required and, in the unlikely event of you hitting a problem, our customer service and advice department will put the matter right promptly and willingly.

Project 60 modules have been carefully designed to fit easily into virtually every type of plinth or cabinet to provide a complete unit of great compactness. Only holes have to be drilled into the wood of the plinth and any slight slips here will be covered completely by the aluminium front panel of the Stereo 60. The Project 60 manual gives all the instructions you can possibly want clearly and concisely.

Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future. We shall shortly be introducing additional modules which will include a comprehensive filter unit, a stereo F.M. tuner and an even more powerful amplifier for very large systems. These and all other modules we introduce will be compatible with those shown here and may be added to your system at any time.

# sinclair

**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD, CAMBRIDGE


Tel: 0223 52731


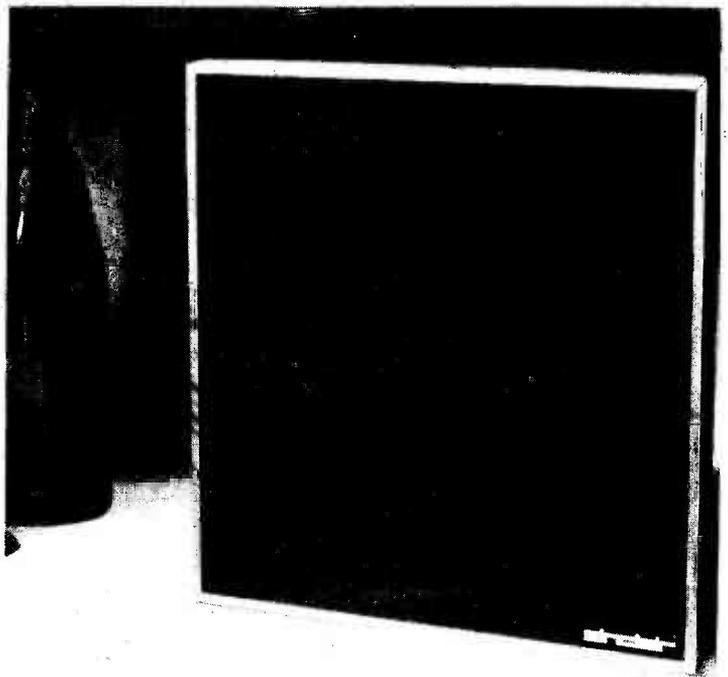
# SINCLAIR Q.16

new elegance in an  
outstanding loudspeaker

All the superb features which went to make the Sinclair Q.14 have been incorporated in the new Q.16 which gives an exciting new opportunity for you to match your Sinclair equipment with modern decor. Employing the same well proven acoustic system in which materials, processing and styling are used in such a radical and successful departure from conventional design, the new Q.16 presents an entirely new appearance with its attractive teak surround and all-over special cellular foam front chosen as much for its appearance as for its ability to pass all audio frequencies without loss. The Q.16 is compact and slim. Its new styling makes it eminently suitable for shelf mounting, but it is no less versatile than its famous predecessor. Listen to a pair of Q.16s in stereo and marvel at the standards of quality and clarity they give.



The Q.16 will handle loading up to 14 watts R.M.S. and presents an 8 ohm impedance to the amplifier output. Frequency response extends from 60 to 16,000Hz with exceptional smoothness. A specially designed driver system is used in a sealed and contoured pressure chamber to ensure good transient response at all frequencies. Size: 9 $\frac{1}{2}$ " square  $\times$  4 $\frac{1}{2}$ " deep from front to back.

## £8.19.6

POST FREE

# SINCLAIR MICROMATIC

The world's most  
successful miniature  
radio



**SPECIFICATIONS**—Size: 1 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{4}$ "  $\times$   $\frac{1}{2}$ " (46  $\times$  33  $\times$  13mm). **Weight incl. batteries:** 1 oz. (28-35gm) approx. **Tuning:** Medium wave band with bandspread at higher frequency end. **Earpiece:** Magnetic type. **Case:** Black plastic with anodized aluminium front panel, spun aluminium dial.

Complete kit incl. earpiece, case, solder and instructions in fitted pack.

Ready built, tested and guaranteed, with earpiece.

Mallory Mercury Cell RM675 (2 req.) 2/9 each

49/6

59/6

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation much easier than with many larger sets. The plug-in magnetic earpiece which matches exactly with the output provides wonderful standards of reproduction.

Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wrist-watch, and dependable under the severest listening conditions.

### SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

## sinclair

### SINCLAIR RADIONICS LIMITED

22 NEWMARKET ROAD, CAMBRIDGE

Tel: 0223 52731

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE  
Please send

NAME

ADDRESS

For which I enclose cash/cheque/  
money order

PW 370

**MARCONI CR 150/2** double Superhet receiver 1-5-22Mc/s AM/CW/SSB operation Xtal Filter, BFO fast/slow motion tuning 'S' Meter, etc. Good condition. Tested and working. Separate power pack required. £22.10.0 P.P. 30/-

**R200 RECEIVER, AM/CW/FM, 1-20Mc/s.** Four bands, Vernier tuning. 12 volt DC Input. Tested and working. £13.10.0 P.P. £1

**COMPUTER BOARDS.** Min 30 transistors and diodes and res. etc. 10 boards, 10/- and P.P. 2/6; 25 boards 22/6 and P.P. 4/6.

**HEADPHONES.** Chamois padded, low impedance. Moving coil, magnetic microphone, new ex W.D., rare type, limited stock. 25/- per pair and 3/6 P.P.

**AERIALS.** new condition, extending to 11ft fully open; whip type; 12/6 and P.P. 3/6. Whip aerials, 12ft collapsible type; used condition 10/- and P.P. 3/6 Bases for above 5/- and 2/6 P.P.

**BARGAIN PARCELS.** 14 lb. 29/- and 6/6 P.P.; 28 lb. 55/- and 12/6 P.P.; 56 lb. 90/- and 25/- P.P. Contain Pots, Res., Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value saves £££. LUCKY DIP SERVICE.

**FURHILL BEAT FREQUENCY OSCILLATOR.** 0-10Kc/s, 110/250 volt. Good condition; complete with spares. £5.10.0 and 25/- P.P.

**VHF RECEIVER TYPE 715,** less crystal 60-100Mc/s, can be operated on 2 or 4 meters or made tunable 12 volt input; not tested, complete with valves and speaker. £3.0.0 and £1 P.P.

**VIBRATOR POWER SUPPLY TYPE 69** by BCC for 69 T/R. Small compact 12V Input gives 250V DC at 80mA and 12V output. Good condition. 25/- and 7/6 P.P.

**MOBILE POWER UNITS** by PYE for the C12 T/R. Power output is 400V DC at 140mA and 300V DC at 100mA. Good condition. £3.10.0 and £1 P.P.

**INSULATION TESTERS.** Bench or fieldwork; speed clutch; new condition, complete with leather case; 500V, 500 megohms. £20 and 12/6 P.P. Also 1000V 1000 megohms with case. £23 and 12/6 P.P.

**CRYSTALS AS NEW.** Hc6U 5,345; 5,055; 5,030; 4,945; 4,875; 4,840; 4,785; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s and 10 x J 485 Kc/s. All at 10/- and 1/6 P.P.

**METERS/MOVING COIL EX EQUIPMENT.** Good condition; all from 0-10mA, 30mA, 50mA, 100mA, 500mA. All 2 1/2 in. round. 10/- ea and 5/- P.P. from 15 amp DC, 20 amp DC, 40 amp DC. All 2 in. round. 10/- ea and 5/- P.P.

**SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS.** 10% tolerance 1/4 & 1/2 watt. Preferred values in packets of 10. Our price 10/- per 100, 10/- per 200, 27/- per 300, 50/- at 42/6. Our selection. P.P. 1/6 per 100 and 6d per 100.

# A. H. THACKER

Radio Dept.

HIGH ST., CHESLYN HAY, Nr. WALSALL, STAFFS.

## 6 PUSH-BUTTON STEREOGRAM CHASSIS



M.W.: S.W.1.: S.W.2.: V.H.F.:  
Gram: Stereo Gram; Vol:  
Tone: Mains Trans: 200-  
250 Volts; 2 o.p. for 3 ohm  
Also operates with two  
speakers on Radio. Chassis  
size: 15 x 7 x 6 1/2 in. high. Dial  
silver and black 15 x 3 in. 190-  
550M: 18-51M: 60-187M:  
VHF 86-100 Mc/s. Valves:  
ECC85, ECH81, EF89, 2 x  
ECL86, EM84 and Rect.  
Price £19.19.0, carr. paid.  
With Stereo Decoder fitted  
£8 extra.

## STEREO AMPLIFIER type HV— 2 x 3 Watts

Fully built. On off. sep. vol. and tone each channel 12 x 4 1/2 x 6 in. high. EZ80, 2 x ECL86; for 3 ohm speakers, double wound main trans; fixing flanges and base plate, suitable for crystal cart, tuner etc. £6.10.0 (8/- p. x p.)



## STEREO AMPLIFIER type RC— 2 x 3 Watts

Fully built. 2 x UCL82, metal rect; ganged vol. and tone cont; on-off. balance. 11 x 3 1/2 x 4 in. high. Double wound mains trans. with supporting brackets. For 3-ohm speakers. £6 (8/- p. & p.).



## MONO GRAM CHASSIS 3 WATT

3 Wave band long-med-short. Gram., 200-250v AC Ferrite aerial. Chassis 13 x 7 x 5 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH81 EF89, EBC81, EL84, EZ80. Price £10.12.6. (7/6 p. & p.) Output trans. for 3-ohm speaker.



**BAKERS' Selhurst Speakers.** 12 in., cast frame, 3, 8 or 15 ohm (state which). Group 25 (25 watt) for guitars, etc. £6.6.0; Stalwart 45-13,000 cps, 15W £6.6.0; de Luxe Mk2 dual cone 25-16,000cps. 15W £9 (all carr. paid) less 10% for 2 speakers.

## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240 CLOSED WEDNESDAY. S.A.E. for enquiries please.

# Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new  
TECHNATRON Outfit! No mathematics.

No soldering—but you learn the practical way.

Now you can learn basic Radio and Electronics at home—the fast, modern way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new TECHNATRON Self-Build Outfit take the mystery out of the subject—make learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING. The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a teaching Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book—'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 372B, Aldermaston Court,  
Aldermaston, Berkshire.

To: B.I.E.T., Dept. 372B, ALDERMASTON COURT,  
ALDERMASTON, BERKS.

I would like to know more about your  
Practical Radio & Electronics Course. Please  
send me full details and FREE 164-page book.

name.....

address.....

age.....



# LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 1/2 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.



**COWDREY FIVE.** Specially designed Corner Cabinet 20 1/2 x 13 x 7 1/2 in. deep. Finished in natural teak veneers with Vynair front. Fitted rubber feet. Five speaker units 15 ohms. Impedance handles 15 watts). £4.6.0 P. & P. 8/6 each.



**ADAstra DOUBLE 5** stereo solid state amplifier housed in handsome cabinet veneered in natural teak. Size 11 1/2 x 8 x 5 1/2 in. 10 Transistors—power output 5 watts peak per channel. 220-240V AC. Output impedance 12 to 15 ohms (our Cowdrey speaker system eminently suitable). Smart blue escutcheon. £14.14.0. P. & P. 10/6.





**CAXTON COLUMN.** This is a column cabinet 23 1/2 x 5 1/2 x 5 1/2 in. deep finished in black or wood grain cloth with blue Vynair front. Keyhole slot for wall mounting. Fitted with three speaker units, 9 ohms impedance. Handles 8 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at 59/6d. P. & P. 10/6d. each.

**ELF.** An extension speaker of quality 9 x 5 1/2 x 3 1/2 in. deep veneered in natural teak with smart gold and brown Vynair front trimmed in white. Fitted with 3 ohm speaker unit mounted on 1/2 in. baffle. Exceptional value 37/6d. P. & P. 3/9d. each.



**SCOTT.** This elegant tapered cabinet 10 1/2 x 15 x 5 1/2 in. deep is attractively finished in black cloth with striped grey Vynair front. Suitable for table or for wall mounting. Fitted with 13 1/2 x 8 in. speaker unit and volume control. 3 or 15 ohms Impedance—please state impedance required. £4.5.0. P. & P. 7/6d each. Fitted with E.M.I. 13 x 8 in. speaker unit and twin tweeters. 15 ohms Impedance, capacity 10 watts. 30/- extra.

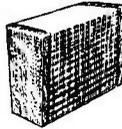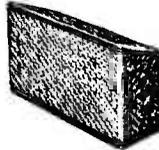

**IMP.** Wedge shaped extension speaker 7 1/2 x 6 1/2 x 4 in. (max.). Covered in walnut wood grain cloth with foam Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only 25/6d. P. & P. 3/9d. each.

**SPEAKERS:** Elac Heavy duty Ceramic Magnets 11,000 line, 10in. round, 10 x 6in. 3 ohm or 15 ohm, 48/6. P. & P. 3/6. 8in. round 15 or 3 ohm, 42/6. P. & P. 3/6. E.M.I. 13 1/2 x 8in. 3 ohm, 45/-, 15 ohm 48/6. P. & P. 1/6. E.M.I. 3 in. tweeter 17/6. P. & P. 1/6. E.M.I. 1 1/2 x 8in. fitted two 2 1/2 in. tweeters. 15 ohm 77/6. P. & P. 4/6. E.M.I. 1 1/2 x 8in.

(15 ohm) Hi-Fi quality £5.10.6. P. & P. 4/6. E.M.I. Woofers. 6 1/2 x 6 1/2 in. square, 8 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 16/6. P. & P. 1/- EAGLE Crossover units 3 or 10 ohms, 16/- P. & P. 1/-. Bakers 12in., 25 watt 15 ohm £6.8.0. P. & P. 3/6.

**TEAK PLINTH AND PERSPEX DUST COVER** for SP25 etc. £5.5 0 P. & P. 5/-.

**VYNAIR** Widths from 40 to 54in., 17/6 yd. off roll. P. & P. 1/9. 3 yard, 9/- P. & P. 1/9. Send 1/- stamps for samples.

**SPEAKER MATCHING TRANSFORMERS.** 3, 7, 15 ohms, 8 watt, 13/6. P. & P. 1/6.

**MICROPHONES:** Xtal Hand Mikes. B1201 with stand, 54/6. P. & P. 3/6. Dyn. Mike DM-391, 30/- CM21 Xtal, 12/6. Telephone Pick-up, 10/6. P. & P. 1/- Xtal lapel Mike, 7/6. Guitar Mike, 12/6. P. & P. 1/-.

**FERROX RODS:** 6 x 1/2 in., 2/6; 4 1/2 x 1/2 in., 2/-; 6 x 1/2 in., 2/6; 8 x 1/2 in., 4/9. P. & P. 1/- each.

**FERROX RODS WITH COILS,** 4 1/2 x 1/2 in., 3/6; 8 x 1/2 in., 5/6. P. & P. 1/- each.

**ROTARY SWITCHES:** 1 pole 12 way, 2 pole 2 way, 3 pole 3 way, 3 pole 4 way, 4 pole 3 way, 3/6 each. P. & P. 1/-.

**TRANSISTOR SPEAKERS** 8 ohm 2 in., 8/6, 3 in., 10/6. P. & P. 1/-.

**CARTRIDGES.** Stereo: Sonotone 9TA H/C Diamond, 47/6. Ronette S105 Medium Output, 28/6. S106 High Output, 28/6. Acos GP93/1 Sapphire, 37/6. GP94/1 Sapphire, 39/6. GP81 Diamond, 42/- GP91 Stereo Compatible (High, Medium or Low Output), 25/- TA800 converts Philips AG3301, AG3306 to B.S.R. SX1H. Plug-in head complete with cartridge, 50/- TA700 equivalent to B.S.R. SX1M, 35/- Japanese equivalent to B.S.R. TC8s, 35/- P. & P. 1/6.

Mono: Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 15/- B.S.R. TC8H Jap. equivalent, 26/- Sonotone 2TSS, 15/- P. & P. 1/6.

**EARPIECES WITH CORD** and 3.5mm. plug, 8 ohm magnetic, 3/- 250 ohm, 4/- 180 ohm with clip, 6/6. Xtal. P. & P. 6d.

**PIANO KEY PUSH BUTTON SWITCHES.** 7 button inc. mains on off. 6 banks of 6 P.C.O., 8/6. P. & P. 1/-.

**BROADWAY Electronics** (Few minutes from Tooting Broadway Underground Stn)

92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 01-672 3884 (Closed all day Wednesday)

CANCELS PREVIOUS LIST

# WIRECOMP ELECTRONICS

## LONDON'S LEADING BARGAIN SPECIALISTS

### FOR THE RADIO • HI-FI & ELECTRONICS ENTHUSIAST

Special displays of radios, recorders, record decks, tuners, amps, meters, speakers, etc., etc. ALL faulty or damaged needing repair—**AT GIVE AWAY PRICES!**

100's of component bargains from our easy to see and choose from self service racks.

100's OF OLD TYPE VALVES — from 2/- each  
ASSORTED TRANSISTORS 9d each. 7/6 per doz

Huge stocks of shop soiled and reconditioned second hand radios, record players, tape recorders, etc.

## SPOT CASH PART EXCHANGES

WE OFFER THE HIGHEST RATES IN LONDON

There's something for everyone  
**COME AND LOOK TODAY (Open 6 days a week!)**  
ALL THESE ITEMS ARE AVAILABLE TO CALLERS ONLY


PERSONAL CALLERS TO:  
48 TOTTENHAM CT. RD., W.1 Tel. 01-636 0847

## M. & B. RADIO

38 BRIDGE END, LEEDS 1

Telephone: 0532-35649

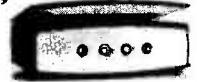**STEREO CABINETS.** A beautifully finished polished wood cabinet supplied in original carton. Size approx. 22 x 16 x 8in. New 47/6 plus 6/6 carriage.



**TELEMETERS.** A well finished cabinet containing lots of useful items for the constructor. Endless tape unit and tape head, 2 motors, auto and mains transformers, miniature valve I.F. strip etc. Ideal for modifying or stripping. 77/6 plus 7/6 carr.



**STETHOSCOPE HEADSETS.** Brand New. Ideal for stereo or mono. Low impedance. 27/6 plus 3/6 pp.

**MICROPHONES.** Radiotelephone type, used. 5/- plus 2/- pp.

**TRANSISTORISED 2 METER CONVERTERS.** Please state preference of I.F. frequency when ordering. £7.15.0 plus 5/- pp. 4 metre models available at the same price. VHF Marine band model £8.5.0 plus 5/- pp.

**12V TRANSISTOR INVERTERS.** 12vdc input. 275vdc at 150mA output. Size of aluminium case 1 1/2" x 2 1/2" x 4" approx. Size of transformer approx. 1 1/2" x 2" x 2". £3.5.0 plus 5/- pp.

**2 to 3 WATTS INTEGRATED CIRCUITS.** Tested c/w circuit. £1 plus 1/- pp.

**60 UNTESTED TRANSISTORS** 5/- plus 1/- pp.

**60 UNTESTED DIODES** 2/6 plus 1/- pp.

**BYX25 800R Silicon diodes** 300 pIV 16amps on heat sink 5/- plus 1/- pp. 455Kc/s FM

Transistorised I.F. strips. Faulty usually low in gain but new. 6 transistors. 12/6 plus 1/- pp.

**USED TESTED VALVES.** OQVO3/10 6/-, 6AQ5/EL90 3/-, 6BJ6 1/6, 6BH6 1/6, 12AX7/ ECC83 2/6, 5U4 6/-, ECF80 2/- All plus 1/6 pp.

**AERIAL CHANGE OVER RELAYS** 6v, 12v or 50v 4/- plus 1/6 pp.

**UHF Coaxial AERIAL CHANGE OVER RELAYS.** BNC Sockets. 27/6 plus 2/6 pp.

**BRAND NEW HEADPHONES.** A well known make of headset which combines quality with comfort. Mono or Stereo. 54/- plus 4/- pp.

**PLEASE NOTE NEW ADDRESS. NO CONNECTION WITH FIRM PREVIOUSLY AT THIS ADDRESS**

**LIST OF OTHER EQUIPMENT PLEASE SEND 6d. PLUS S.A.E.**



# R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM S.W.16

Mon.—Sat. 9 a.m.  
—5.30 p.m.  
Closed Sat. 1.30—2.30 p.m.  
Open Daily to Callers

Tel. 769-0199/1649

IA7 7/9	6BR8 12/6	6K7GT 4/6	10C2 12/6	25L6GT 7/1	15B22 11/6	DK32 7/9	ECH35 11/6	EY31 7/6	PCC189 10/6	R2 7/6	UF41 10/6
ID5 7/6	6B87 25/-	6K8 2/9	10F1 14/9	25Y5 6/-	15C04 9/6	DK91 6/-	ECH42 13/-	EY86 7/6	PCF80 6/9	R19 7/9	UF89 7/6
ILD5 6/1	6BW7 14/6	6K8M 11/6	10F3 18/-	25Z4 6/3	801 9/6	DK92 9/6	ECH81 5/9	EZ35 6/-	PCF82 6/6	RG5/50080/-	UL41 12/-
IN5GT 8/-	6A4 13/-	6K8GT 3/-	10F9 10/6	25Z5 8/-	807 9/6	DK96 7/9	ECH83 8/6	EZ40 9/6	PCF84 8/-	S130 4/0	UL84 7/-
IS5 6/6	6C5G 5/-	6K25 15/-	10L1 8/6	25Z6 8/6	813USA 12/6	DL22 25/-	ECL80 7/6	EZ41 9/6	PCF86 9/-	SP4 8/0	UM80 5/6
IS4 5/6	6C6 3/9	6L1 12/-	10LD11 10/6	30C1 6/9	813 12/6	DL93 4/-	ECL83 10/3	EZ81 5/6	PCF801 9/9	SP61 3/6	UU6 21/-
IS5 4/6	6C8G 6/-	6L6G 7/9	10P13 13/6	30C15 15/-	866A 15/-	DL94 6/6	ECL86 9/-	GY501 5/6	PCF805 15/-	STV280/8/0	UUR 21/-
IT4 4/-	6CD6G 24/-	6L18 6/-	11E3 7/9	30C17 16/-	954 5/3	DL95 7/9	ECLL80 30/0	GZ30 10/-	PCF806 13/-	SU25 95/-	UY9 8/3
3A4 4/-	6C8H 7/6	6Q7G 6/-	12AT6 4/9	30C18 15/-	1625 6/6	DL96 7/6	ECLL80 30/0	GZ32 10/-	PCF808 15/9	SU25 19/6	UY21 9/6
3Q4 7/9	6C9A 13/6	6Q7GT 8/6	12AT7 6/-	30F15 17/-	4022AR 67/-	DM70 6/-	EF9 20/-	GZ34 11/-	PCL82 7/9	SU2150 12/6	UY41 8/6
3Q5 6/3	6D6 3/9	6SA7M 7/6	12AU6 5/9	30F11 15/-	5763 12/-	DY86 6/-	EF37A 7/6	HN309 20/-	PCL83 10/3	T41 17/6	UY85 6/6
3S4 6/3	6E5 7/6	6SC7 7/6	12AU7 5/9	30FL12 19/-	7193 2/-	DY87 6/6	EF39 8/-	KT36 18/-	PCL84 8/6	TTDD 8/6	VMP4017/-
3V4 6/9	6F1 12/6	6SG7 7/6	12AX7 6/3	30FL14 15/6	7475 14/-	E88CC 12/6	EF41 10/-	KT61 17/6	PCL85 9/3	U10 7/6	VP48 25/-
3V4GY 10/6	6F5G 8/-	6SH7 3/3	12BA6 6/-	30L15 17/-	A61 9/6	EA50 3/6	EF30 5/6	KT66 30/-	PCL86 9/3	U14 7/6	VR105/300/6-
3U4G 5/6	6F6G 5/-	6SI7 6/-	12BE6 6/3	30L17 17/-	ATP4 2/3	EABC80 6/6	EF85 4/6	KT81 35/-	PD500 29/-	U19 35/-	VR150/306/-
3V4G 8/6	6F8G 5/6	6SK7GT 4/6	12C8GT 5/-	30P12 16/-	ATP7 8/6	EB41 10/-	EF86 6/6	KT81 (7C5) 35/-	PEN44 20/-	U26 15/6	VT25 15/-
5Y3GT 6/-	6F11 6/6	6SL7GT 6/6	12E1 20/-	30P19 15/-	AU2 80/-	EB91 10/-	EF89 5/6	KT88 34/-	PEN45 7/6	U91 13/9	VU120 12/6
5Z4G 7/6	6F13 6/6	6SN7GT 5/6	12G1 20/-	30PL1 16/-	AU5 8/9	EBCC3 8/6	EF91 3/6	KTW41 12/6	PEN46 4/9	U251 16/3	VU508 35/-
6/30L2 15/-	6F14 12/6	6SOT 7/6	12J2GT 6/6	30PL13 18/6	AZ1 10/-	EBCC9 4/9	EF98 15/-	ML4 17/6	PEN46 4/9	U251 16/3	VU508 35/-
6AT 15/-	6F23 12/6	6U4GT 12/6	12K7GT 7/6	30PL14 15/-	AZ31 10/-	EBF80 7/6	EF183 6/6	ML6 17/6	PL81 8/0	U301 12/6	W81M 13/6
6AR 12/6	6F24 12/6	6V6M 12/6	12K8GT 8/6	35A5 11/6	CB131 16/6	EBF80 7/6	EF183 6/6	ML6 17/6	PL82 8/6	U408 7/6	XPI-5 5/-
6AC7 4/-	6F25 15/-	6V6M 12/6	12Q7GT 6/-	35L6 9/6	CH35 15/-	EBF83 9/6	EF184 7/6	MSB4 7/6	PL83 7/6	U801 15/6	XSG1-5/10/7
6AK5 5/-	6F28 14/-	6V6M 12/6	12S7 3/9	35Z4GT 8/6	CY30 12/6	EBL1 14/-	EL32 12/6	MX40 12/6	PL84 7/6	UABC80 6/6	Y6 7/6
6AM5 4/6	6F32 2/9	6V6GT 6/6	12SA7 4/6	35W4 4/6	CL33 20/-	EBL2 12/6	EL34 10/6	N78 19/-	PL500 14/6	UAF42 10/6	Tubes
6AM6 3/6	6G6 2/6	6X4 4/6	12SG7 6/6	35Z3 10/-	CV450 25/-	EBL3 27/6	EL38 22/6	N108 25/-	PL508 29/-	UBC41 9/3	3EB1 65/-
6AQ5 6/3	6H6 3/-	6X5G 4/6	12SH7 3/9	35Z5 6/6	CY31 8/6	EBL3 27/6	EL41 11/6	NGT1 3/6	PL509 29/-	UBC81 9/3	3FP7 29/-
6AS7G 16/6	6I5M 9/6	6X5GT 6/6	12SK7 4/6	35Z5 6/6	DA32 7/6	EC90 5/6	EL41 11/6	NGT1 3/6	PL802 16/6	UBF80 7/6	5CP1 55/-
6AT6 4/6	6F4G 6/6	6Y7 7/6	12SK7 4/6	35Z5 6/6	DA32 7/6	EC90 5/6	EL41 11/6	NGT1 3/6	PL802 16/6	UBF80 7/6	5CP1 55/-
6AU6 5/-	6J5GT 5/6	7B7 1/6	12SR7 5/6	42 6/6	DA39 4/6	EC82 9/6	EL84 4/6	OA2 14/-	PK4 14/-	UBF89 7/6	ACV1526 65/-
6BA6 20/-	6J6 3/6	7C5 22/6	14H7 9/6	50B5 6/6	DAF96 7/6	EC82 9/6	EL84 4/6	OA2 14/-	PK4 14/-	UBF89 7/6	ACV1526 65/-
6BSG 2/-	6J7M 8/6	7C6 15/-	19AQ5 5/-	50C5 6/6	DCC90 20/-	EC83 6/3	EL95 6/6	OC3 5/6	PY33 10/9	UC84 8/6	ACV1526 65/-
6BA6 5/-	6J7G 7/6	7D5 8/6	20D1 10/5	50CD6G31/-	DF33 8/-	EC84 5/6	ELL80 20/-	OZ4 4/6	PY81 5/9	UC85 7/6	VCR91 100/-
6BE6 5/-	6J7GT 7/6	7H7 6/6	20F2 14/-	50L6GT 8/-	DF70 9/6	EC85 5/6	EM34 21/-	PC86 11/6	PY82 5/3	UCF80 8/6	VCR97 45/-
6BI6 6/6	6K6GT 5/6	7R7 13/-	20L1 20/-	75 9/6	DF91 4/6	EC88 7/6	EM80 7/6	PC88 11/6	PY83 7/6	UCH2 10/6	VCR517B 46/-
6B16 9/6	6K7 2/9	7S7 43/-	20P1 20/-	80 7/6	DF92 3/6	EC88 7/6	EM81 8/3	PC97 8/9	PY500 18/6	UCH81 7/6	VCR517C 46/-
6BQ7A 7/6	6K7M 6/6	7Y4 8/6	20P5 20/-	80 7/6	DF96 3/6	EC88 7/6	EM82 8/6	PC84 7/6	PY800 9/6	UCH82 7/6	VCR517C 46/-
6BR7 17/-	6K7G 2/-	8W6 7/6	25A6 5/9	85A2 7/3	DH77 4/9	ECH21 12/6	ESU150 20/-	PCC89 10/6	PY801 9/6	UCH83 10/6	46/-

Manufacturers and Export Inquiries Welcome  
OBsolete TYPES A SPECIALITY  
QUOTATIONS FOR ANY VALVE NOT LISTED  
Express postage 9d. per valve.  
Ordinary postage 6d. per valve. C.W.O. No C.O.D.  
Tube postage 7/6 each

Special Express Mail Order Service

### TUBES

14 inch	84 0 0
17 inch	84 0 0
19 inch	86 0 0
21 inch	86 10 0
23 inch	812 0 0
27 inch	88 0 0

### SETS OF VALVES

DAF91, DF91, DK91, DL92 or DL94 ... 19/- plus postage  
DAF96, DF96, DK96, DL96 ... 27/6 plus postage

### TRANSISTORS

AC127 5/-	OC25 7/6	OC71 3/0	OC81 4/-	OC82D 3/0
AF114 5/-	OC28 12/6	OC72 4/6	OC81D 3/0	OC83 4/6
AF115 5/0	OC35 6/3	OC75 4/6	OC81DM 3/0	OC170 5/6
AF116 4/6	OC44 4/6	OC76 3/0	OC82 3/0	OC171 6/-
AF117 4/6	OC45 4/6	OC77 8/6	OC82 3/0	OC280 5/6

SEND S.A.E. FOR LIST OF 3,000 TYPES

## SURPLUS EX GOVT. BARGAINS



AMPLIFIER RF NO. 2 MK III. Increases output of 19 set to 25 watts. Brand New. 12v operation. D.C. Power Units 50/-, Carr. 10/-, 12/24V A.C. Power Units with Vibrator MK II No. 2, 70/-, Carr. 10/-

H/MIC SETS. Used 15/-, New 22/6. P. & P. 5/- Mains P.S.U.'s for 19 TM/RC £6.15.0. Carr. 10/-, R.F. Antenna Tuner (ATU) 25/-, P. & P. 5/-.

**FEW ONLY!**  
No. 19 MK III CANADIAN TRANSCEIVERS  
Rebuilt as new. Complete station with all connectors, headset, varemeter, control box and aerials.  
£22.10.0. Carr. 50/-

B.41 RECEIVER. LF Version of B.40. Coverage 15Kcs—700Kcs. Mains Operation. As received from Ministry. £8.10.0. Carr. 30/-, Tested, working £15. Carr. 30/-



R.209 MK II COMMUNICATION RECEIVERS. 11 valve. Covers 1-20 Mc/s. 4 bands. A.B.F.M. P.W. 12v D.C. Internal Power Supply. Tested. £13.10.0. Carr. 15/-

TELESCOPIC MASTS. 20ft. Closes to 5ft. 9in. 70/-, Carr. 15/-, 34ft. Ditto 80/-, Carr. 15/-, 35FT. AERIAL MASTS. Seven 2in. dia. sections. Interlock 8in. Complete with base. Nylon Guys. £12.10.0. Carr. 50/-, TELE 'F' FIELD TELEPHONES. Communication up to 10 miles. Tested with batteries. £5.15.0 pair. Carr. 20/-, LIVINGSTONE LAB TRANSISTOR AMPLIFIER. 50 watts R.M.S. Size 144 x 9 x 4in. With mains p.s.v. Size 16 x 9 1/2 x 6in. 22 Gns. Carr. 20/-

A.J. THOMPSON (Dept. P.W.)

"Eiling Lodge," Codicote, Hitchin, Herts.  
Phone: Codicote 242

C.W.O. Carriage charges apply to mainland only

## NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.  
Loft Mounting Arrays, 7 element, 40/-, 11 element, 47/6, 14 element, 55/-, 18 element, 62/6. Wall Mounting with Cranked Arm, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. Mast mounting with 2in. clamp, 7 element, 42/6, 11 element, 55/-, 14 element, 62/-, 18 element, 70/-, Chimney Mounting Arrays, Complete, 7 element, 72/6, 11 element, 80/-, 14 element, 87/6, 18 element, 95/-, Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Preamps from 75/-, State clearly channel number required on all orders.

### BBC - ITV AERIALS

BBC (Band 1), Loft, 25/-, External S/D, 30/-, "H" £21.5.0. ITV (Band 3), 3 element loft array, 30/-, 5 element, 40/-, 7 element, 50/-, Wall mounting, 3 element, 50/-, 5 element, 55/-, Combined BBC/ITV, Loft 1 + 3, 40/-, 1 + 5, 50/-, 1 + 7, 60/-, Wall mounting 1 + 3, 60/-, 1 + 5, 70/-, Chimney 1 + 3, 70/-, 1 + 5, 80/-, VHF transistor pre-amps, 75/-.

COMBINED BBC1 - ITV - BBC2 AERIALS 1 + 3 + 9, 70/-, 1 + 5 + 9, 80/-, 1 + 5 + 14, 90/-, 1 + 7 + 14, 100/-, Loft mounting only. F.M. (Band 2), Loft S/D, 17/6, "H", 35/-, 3 element, 57/6. External units available. Co-ax cable 8d. yd. Co-ax plugs, 1/6. Outlet boxes, 5/-, Diplexer Crossover Boxes, 17/6. C.W.O. & C.O.D. P. & P. 6/6. Send 6d. stamps for illustrated lists.

Callers welcomed — open all day Saturday

K.V.A. ELECTRONICS (Dept. P.W.)  
40-41 MONARCH PARADE  
LONDON ROAD, MITCHAM,  
SURREY DT1-648 4884

## 4-STATION INTERCOM



Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 9 connecting wires each 66ft. and other accessories. P. & P. 7/6.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way loud and clear communication. On/off switch and volume control. Price £11.19.6. P. & P. 8/6 extra.

## INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/8. P. & P. 4/6.

### Transistor TELEPHONE AMPLIFIER

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/8 extra. P. & P. 3/8. Full price refunded if not satisfied in 7 days. WEST LONDON DIRECT SUPPLIES (P/W) 169 KENSINGTON HIGH STREET, LONDON, W.8.

# BI-PAK SEMICONDUCTORS

500 CHESHAM HOUSE, REGENT STREET, LONDON W.1.

## NEW LOW PRICE TESTED S.C.R.'s

1 A (TO-5 case)	3 A (TO-66 case)	7 A (TO-48 case)	16 A (TO-48 case)	30 A (TO-48 case)	PIV each	each
50	4/6	5/-	9/6	10/6	25	20/-
100	5/-	6/6	10/6	12/6	50	23/-
200	7/-	7/6	11/6	15/-	100	28/-
400	8/6	9/6	13/6	18/6	200	32/-
600	10/6	11/6	15/6	25/-	400	35/-
800	12/6	14/-	18/-	30/-	800	80/-

## PRINTED CIRCUITS EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/- Plus 2/- p. & p.

**TRANSISTOR EQVT. & SPECIFICATION BOOK** (German publication). A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- ea.

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 5/- ea.

Sil. trans. suitable for P.E. Organ, Metal TO-18 Eqt. ZTX300 1/- each. Any Qty.

120VCB NIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND120, 1-24, 3/6 each. TO-5 NPN 25 up 3/- each.

**PLEASE NOTE.** To avoid any further Increased Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organized and streamlined our Dispatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Dispatch Department, postal address: **BI-PAK SEMICONDUCTORS, Dispatch Dept., P.O. BOX 6, WARE, HERTS.** Postage and packing still 1/- per order. Minimum order 10/-.

## SIL. RECTS. TESTED

PIV 750mA	3A	10A	30A
50	1/-	2/9	4/3
100	1/3	3/3	4/8
200	1/9	4/-	4/9
300	2/3	4/6	6/6
400	2/6	5/6	7/6
500	3/-	6/-	8/6
600	3/3	6/9	9/-
800	3/6	7/6	11/-
1000	3/-	9/3	12/6
1200	6/6	11/6	15/-

## TRIACS

VBOM (TO-1)	2A (TO-66)	6A (TO-8)	10A (TO-8)
100	14/-	15/-	22/6
200	17/6	20/-	28/-
400	20/-	25/-	35/-

VBOM=Blocking voltage in either direction.

2N3055 115 WATT SIL. POWER. NPN. OUR PRICE 12/6 EACH.

**FULL RANGE OF ZENER DIODES** VOLTAGE RANGE 2-16V. 400mV (DO-7 Case) 2/6 ea. 1-5W (Top-Hat) 3/6 ea. 10W (SO-10 Stud) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

**BRAND NEW TEXAS GERM. TRANSISTORS** Code and Guaranteed. Pak No. EQVT  
 T1 8 2G371A OC71  
 T2 8 2G374 OC75  
 T3 8 2G374A OC81D  
 T4 8 2G381A OC81  
 T5 8 2G382T OC82  
 T6 8 2G344A OC44  
 T7 8 2G345A OC45  
 T8 8 2G378 OC78  
 T9 8 2G398A 2N1302  
 T10 8 2G417 AF117  
 All 10/- each pack

# SUPER PAKS

NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and Quality

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.

- U1 120 Glass Sub-min. General Purpose Germanium Diodes 10/-
- U2 60 Mixed Germanium Transistors AF/RF ..... 10/-
- U3 75 Germanium Gold Bonded Diodes sim. OA5, OA47 10/-
- U4 40 Germanium Transistors like OC81, AC128 ..... 10/-
- U5 60 200mA Sub-min. Sil. Diodes ..... 10/-
- U6 40 Silicon Planar Transistors NPN sim. BSY95A, 2N706 10/-
- U7 16 Silicon Rectifiers Top-Hat 750mA up to 1,000V 10/-
- U8 50 Sil. Planar Diodes 250mA OA/200/202 ..... 10/-
- U9 20 Mixed Volts 1 watt Zener Diodes ..... 10/-
- U11 30 PNP Silicon Planar Transistors TO-5 sim. 2N1132 10/-
- U13 30 PNP-NPN Sil. Transistors OC200 & 2S104 ..... 10/-
- U14 150 Mixed Silicon and Germanium Diodes ..... 10/-
- U15 30 NPN Silicon Planar Transistors TO-5 sim. 2N697. 10/-
- U16 10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV 10/-
- U17 30 Germanium PNP AF Transistors TO-5 like ACY17-22 10/-
- U18 8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV 10/-
- U19 30 Silicon NPN Transistors like BC108 ..... 10/-
- U20 12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV 10/-
- U21 30 AF Germanium alloy Transistors 2G300 Ser. & OC71 10/-
- U23 30 Madt's like MAT Series PNP Transistors ..... 10/-
- U24 20 Germanium 1-amp Rectifiers GJM up to 300 PIV. 10/-
- U25 25 300Mc/s NPN Silicon Transistors 2N708, BSY27. 10/-
- U26 30 Fast Switching Silicon Diodes like IN914 Micro-min. 10/-
- U28 Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc.. 8 Assorted Pieces 20/-
- U29 10 1-amp SCR's TO-5 can up to 600 PIV CRS1/25-600 20/-
- U31 20 Sil. Planar NPN trans. low noise Amp 2N3707. 10/-
- U32 25 Zener diodes 400mW D07 case mixed Volts, 3-18. 10/-
- U33 15 Plastic case 1 amp Silicon Rectifiers 1N4000 series 10/-
- U34 30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4 ..... 10/-
- U35 25 Sil. Planar trans. PNP TO-18 2N2906 ..... 10/-
- U36 25 Sil. Planar NPN trans. TO-5 BFY 50/51/52 ..... 10/-
- U37 30 Sil. alloy trans. SO-2 PNP, OC200 2S322 ..... 10/-
- U38 20 Fast Switching Sil. trans. NPN, 400 Mc/s 2N3011 10/-
- U39 30 RF Germ. PNP trans. 2N1303/5 TO-5 ..... 10/-
- U40 10 Dual trans. 6 lead TO-5 2N2060 ..... 10/-
- U41 30 RF Germ. trans. TO-1 OC45 NKT72 ..... 10/-
- U42 10 VHF Germ. PNP trans. TO-1 NKT667 AF117. 10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

## I.C. AMPLIFIER



Identical encapsulation and pin configuration to the following: SL402-3, IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each.

## AD161 NPN

## AD162 PNP

**MATCHED COMPLEMENTARY PAIRS OF GERM-POWER TRANSISTORS.** For mains driven output stages of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 12/6 PER PAIR.

## UNIUNION


UT46. Eqt. 2N2646. Eqt. T1543. BEN3000 25-99 5/- EACH 100 UP 4/-

**NPN Silicon PLANAR** BC107/8/9, 2/- each 50-99, 1/10 100 up, 1/8 each, 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

**NPN DIFFUSED SILICON PHOTO-DUODIODE** TYPE 15701 (2N2175) or Tape Readout, high switching and measurement indicators, 50V, 250mW. OUR PRICE 10/- EACH. 50 OR OVER 8/6. EACH. FULL DETAILS.
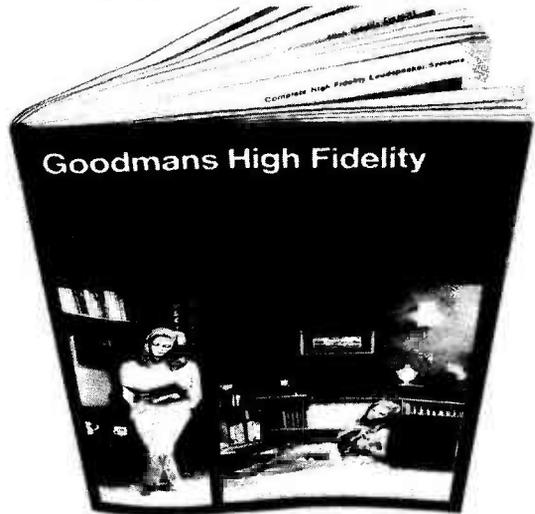
## FET'S

2N 3819 ..... 8/-  
 2N 3820 ..... 25/-  
 MPF105 ..... 8/-



## Let us give you the facts

From cover to cover Goodman's Manual is packed with fascinating articles on Stereo; a beginners guide to High Fidelity; Stage-built Systems; complete details of Goodman's High Fidelity Audio products. 28 pages you can't afford to miss... and it's yours FREE!

Please send me a free copy

Name \_\_\_\_\_  
 Address \_\_\_\_\_ PW4/70

**Goodmans Loudspeakers Limited**  
 Axiom Works, Wembley, Middlesex, Tel: 01-902 1200

# ALL MOTORISTS ARE KEEN TO CUT COSTS

2,973,000\* do something about it they read

# PRACTICAL MOTORIST

The most widely read motoring monthly every month

2/6

THE NATIONAL READERSHIP SURVEY JULY '68 - JUNE '69

# SEMICONDUCTORS

BRAND NEW AND FULLY GUARANTEED

1N914	1/6	2N2906	6/-	ACY28	4/-	BD121	17/6	MJ481	27/6
1N916	1/6	2N2906A	8/-	AD140	8/-	BD123	21/6	MJ490	22/6
1S021	4/-	2N2923	4/-	AD149	11/6	BD124	12/-	MJ491	29/6
1S025	5/-	2N2924	4/-	AD161	7/6	BF115	5/-	MPP102	8/6
1S113	3/-	2N2925	3/6	AD162	7/6	BF117	10/6	MPP103	7/6
1S120	2/6	2N2926	3/6	AF114	5/-	BF167	5/6	MPP104	7/6
1S121	2/6	.. Green	3/-	AF116	5/-	BF173	7/6	MPE105	6/-
1S130	2/6	.. Yellow	2/9	AF117	5/-	BF180	7/6	NKT0013	8/6
1S131	2/6	.. Orange	2/9	AF118	12/6	BF181	6/6	NKT216	7/6
1S132	2/6	2N3011	12/6	AF124	4/6	BF184	7/6	NKT217	8/6
1S44	2/-	2N3053	6/6	AF125	4/6	BF194	5/-	NKT261	4/-
2C301	4/-	2N3054	12/6	AF126	4/-	BFX12	4/6	NKT262	4/-
2C302	4/-	2N3055	15/-	AF127	3/6	BFX13	4/6	NKT264	4/-
2C303	4/-	2N3102	3/6	AF139	7/6	BFX29	12/6	NKT271	4/-
2G371	3/-	2N3703	4/6	AF181	8/6	BFX35	19/6	NKT272	4/-
2N696	4/6	2N3704	4/6	AF186	11/-	BFX43	8/6	NKT275	4/-
2N697	5/-	2N3705	4/-	AF239	7/6	BFX44	8/6	NKT281	5/6
2N698	4/6	2N3706	4/6	ASY26	5/6	BFX48	7/6	NKT403	15/-
2N706	2/6	2N3707	4/-	ASY27	8/6	BFX84	9/6	NKT404	12/6
2N706A	2/6	2N3708	3/6	ASY28	5/6	BFX85	7/6	NKT405	15/-
2N708	4/6	2N3709	3/6	ASY29	5/6	BFX86	6/6	NKT405	15/-
2N929	5/6	2N3710	4/-	ASZ20	7/6	BFX87	6/6	NKT613	6/6
2N930	7/6	2N3711	4/-	ASZ21	7/6	BFX88	5/-	NKT674	5/-
2N1090	6/6	2N3819	9/-	BA102	6/6	BFY10	4/6	NKT677	5/-
2N1091	6/6	2N3820	23/6	BAX13	1/6	BFY17	4/6	NKT713	5/-
2N1131	6/6	2N3906	7/6	BAX16	1/9	BFY18	4/6	NKT773	5/-
2N1132	6/6	2N4058	5/6	BAY31	1/6	BFY19	4/6	NKT781	6/-
2N1302	3/6	2N4059	5/-	BAY38	3/6	BFY20	12/6	NKT20329	8/6
2N1303	3/6	2N4060	5/-	BC107	3/6	BFY41	10/-	NKT80111	15/6
2N1304	4/6	2N4061	4/6	BC108	3/6	BFY43	12/6	NKT80112	19/6
2N1305	4/6	2N4062	4/6	BC109	3/6	BFY51	4/6	OA5	2/6
2N1306	5/-	2N4254	8/6	BC113	4/6	BFY52	4/6	OA9	2/-
2N1307	5/-	2N4255	8/6	BC116	12/6	BFY76	8/6	OA70	1/6
2N1308	6/-	2N4284	3/6	BC118	6/6	BFY77	11/6	OA73	2/-
2N1309	6/-	2N4285	3/6	BC125	11/-	BFY90	12/6	OA79	1/9
2N1307	5/6	2N4286	3/6	BC126	11/-	BSX19	3/6	OA81	1/6
2N1613	5/6	2N4287	3/6	BC147	3/6	BSX20	3/6	OA85	1/6
2N1711	6/6	2N4288	3/6	BC148	3/6	BSY11	7/6	OA90	1/6
2N1889	6/6	2N4289	4/6	BC149	3/6	BSX26	10/6	OA91	1/6
2N1893	8/6	2N4291	3/6	BC167	3/6	BSX27	10/6	OA95	1/6
2N2102	15/-	2N4292	3/6	BC168B	3/6	BSX28	13/6	OA200	2/-
2N2147	14/6	40361	12/6	BC168C	3/9	BSX29	6/6	OC26	6/6
2N2148	12/6	40362	14/6	BC169B	3/6	BSX29	6/6	OC28	8/6
2N2160	12/6	3N128	18/6	BC169C	3/9	BSY26	4/-	OC29	15/6
2N2193	5/6	3N140	19/6	BC182L	5/-	BSY27	4/-	OC35	6/6
2N2193A	5/6	3N141	21/6	BC212L	5/-	BSY39	4/6	OC44	4/-
2N2194A	5/6	3N142	16/6	BCY30	5/6	BSY39	4/6	OC45	2/6
2N2217	6/6	AAZ13	2/-	BCY31	5/6	BSY38	4/6	OC71	2/6
2N2218	6/6	AAZ15	2/6	BCY32	7/6	BSY39	4/6	OC72	2/6
2N2219	6/6	AAZ17	2/6	BCY33	4/-	BSY40	6/6	OC75	4/6
2N2220	5/-	AC107	6/6	BCY34	4/6	BSY51	8/6	OC83	4/6
2N2221	5/-	AC126	4/-	BCY38	6/6	BSY52	9/-	OC84	5/6
2N2222	6/6	AC127	5/-	BCY39	7/6	BSY54	10/6	OC81	4/6
2N2368	5/-	AC128	4/-	BCY40	6/6	BSY95A	2/6	OC83	4/6
2N2369	5/-	AC176	5/-	BCY42	3/-	BY100	4/6	OC81D	4/6
2N2369A	5/6	AC187	12/-	BCY43	3/-	BY10	5/6	OC84	5/6
2N2399	4/6	AC188	12/-	BCY54	7/6	BY10	5/6	OC139	6/6
2N2540	4/6	AC126	4/-	BCY38	6/6	BY11	7/6	OC150	6/6
2N2646	11/6	ACY18	5/-	BCY71	4/6	BY12	6/-	OC200	6/6
2N2904	8/-	ACY19	5/-	BCY72	4/-	BYZ12	6/-	OC201	7/6
2N2904A	8/-	ACY20	5/-	BDY20	25/6	BYZ13	5/-	OC202	18/6
2N2905	8/-	ACY21	5/-	BD116	35/-	MJ480	20/6		
2N2905A	8/-	ACY22	4/-						

<b>MULLARD INTEGRATED CIRCUITS</b>	
FCH211 Hexuple DTL Inverter Gate	28/6
FC1221 Triple 3 Input DTL Inverter	28/6
FC1101 3 Input JK Flip Flop	36/-
TAA241 Operational Amplifier	47/6
TAA243 Operational Amplifier	47/6
TAA 263 Linear AF Amplifier	18/6
TAA 300 Linear A.F. Amp	47/6
TAA320 Most LF Pre-amplifier	15/6
TAA 350 Wide-band Lim. Diff. Amp	45/-
<b>SPEAKERS (3 ohm)</b>	
10in. x 6in. 37/6,	
9in. x 4in. 23/6,	
8in. x 5in. 19/6,	
7in. x 4in. 15/6,	
5in. x 3in. 12/6,	
3in. 9/6, 5in. 14/6	
8in. 27/6, 12in. 39/6.	
Post and Packing 2/9	
<b>THERMISTORS</b>	
R53 (STC)	25/6
K151 (IK)	2/6
All various Muirard Thermistors in stock.	
SEND 6d. STAMP FOR CATALOGUE	
P.P. for Components 1/6 per order.	
<b>VEROBOARD</b>	
2 1/2in. x 3 1/2in.	3/6
2 1/2in. x 5in.	4/3
3 1/2in. x 3 1/2in.	4/3
3 1/2in. x 5in.	5/6
2 1/2in. x 17in.	12/6
3 1/2in. x 17in.	16/-
Cutter 9/-	
<b>RESISTORS</b>	
1/2 watt 5% .4d.	
1 watt 10% .6d.	
2.5 watt 5% 1/6	
5 watt 5% 2/-	
10 watt 5% 2/6	

**A. MARSHALL & SON**  
 28 CRICKLEWOOD BROADWAY, LONDON N.W.2  
 01-452 0161/2/3 CALLERS WELCOME

Post & Packing U.K. only, 1/6. Europe 10/-, Commonwealth (Air) 13/-



Become a  
**RADIO  
 TECHNICIAN**

and work at  
 the nerve centres  
 of civil aviation

The National Air Traffic Control Service of the Board of Trade needs Radio Technicians to install and maintain the very latest electronic aids at Civil Airports, Air Traffic Control Centres, Radar Stations and specialist establishments. Vacancies exist in various parts of the United Kingdom.

This is responsible demanding work (for which you will get familiarisation training) involving communications, computers, radar and data extraction, automatic landing systems, and closed-circuit television. It offers excellent prospects with ample opportunities to study for higher qualifications in this fast-expanding field.

If you are 19 or over, with at least one year's practical experience in telecommunications, fill in the coupon now. Preference will be given to those having ONC or qualifications in Telecommunications.

Salary: £985 (at 19) to £1,295 (at 25 or over); scale maximum £1,500 (higher rates at Heathrow). Some posts attract shift-duty payments. The annual leave allowance is good and there is a non-contributory pension scheme for established staff.

Complete this coupon for full details and application form:  
 To: A. J. Edwards, C.Eng., M.I.E.E., M.I.E.R.E., Room 705, The Adelphi,  
 John Adam Street, London WC2 marking your envelope 'Recruitment'

Name.....  
 Address.....

PW/B3

Not applicable to residents outside the United Kingdom.

**NATCS** National Air Traffic Control Service

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 10s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

## MISCELLANEOUS

### ALBIONS APRIL BARGAINS



**SPEAKER CABINETS**  
Beautifully finished in teak veneer with attractive front cloth.  
Measure 16in x 8in x 6in.  
ONLY 67s 6d each; pp. 7s 6d.

Single Mic Cable, 6d yard, post/pack. 7d+1d yd. Toggle Switches, DPDT 3s; SPST 2s 3d. DIN plugs, 3 pin 2s 9d; 5 pin 3s 9d. Standard bakelite barrel plugs 2s 6d. POST: up to 3, 1s and thereafter 1d each. Eagle 4 channel Mic mixer 52s 6d; 3 watt, 4 trans' audio amp'. Ready built 63s. POST: both 3s 6d.

UP TO 50 Watts WITH FAL. Yes, the fantastic FAL phase 50 PA Amplifier can give up to 50 Watts of rich sound. Suitable for use with Tape, Records, Mic, or even Bass Guitar, incorporating three mixed inputs, Bass and Treble controls, New and Guaranteed 12 months. ONLY 29 gns. post and packing free, or as exclusively offered by us with two 25 watt Bass Guitar speakers, ONLY 35 gns. post and packing £1. SAE leaflet.

Send for free lists of Electronic equipment and components, Amps, Tuners, Cables, Gadgets, etc.

**ALBION ELECTRONICS SUPPLIES**  
Dept. 3, 16 Albion Rd., Birchington, Kent

## THE NEW

### ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 26 Maude Street, Darlington, Durham. Send 4d. stamp.

**NOTES ON USE OF TV FOR UFO Detection.** Optical Detector Circuits, 8s 6d. Radar & Electronic Publications, "Highlands," Needham Market, Suffolk.

**EXPRESS ROTARY SWITCHES.** Switches for Mullard audio circuits, also switches made to customers own specifications. For details and price list, write or phone to 189 Edgware Road., London W.2. Tel. 01-723 4455.

### 6 OR 12 VOLT FLUORESCENT LIGHTS

12 in. 8 Watt tube ample light for caravan, tent etc. Fully transistorised, low battery drain. Unbeatable at £2.19.6 post paid.

or in kit form 50/-

### 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed 65/- POST PAID

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop, Shrewsbury, Shropshire S.A.E. for list

**BUILD IT** in a DEWBOX quality cabinet. 2in. x 2½in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

## MISCELLANEOUS

(continued)

## Be well-equipped

You need not worry about the painful and lingering minor burns that occur from time to time in leisure pursuits if you keep BURNENZE close to hand. This unique new scientific aerosol cools and anaesthetizes. BURNENZE takes the heat out of a burn in just 8 seconds, then controls the blistering and pain that steal skill from nimble fingers. Be well-equipped—buy BURNENZE, from chemists.

Potter & Clarke Ltd Croydon CR9 3LP



**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond, Surrey.

**MUSICAL MIRACLES.** Send S.A.E. for details of Rhythm Modules, versatile bass-pedal unit, self-contained with unique effects, kits for waa-waa pedals. Also new 50µA meters, 25/- post paid. HURRY! D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

**JOURNAL OF PARAPHYSICS** Russian experiments: telekinesis ("mind-over-matter"); brainwaves actuate electronic relays; transistor UFO detectors; finger-vision; hyperspace; time-reversal; tachyons ("faster than light") etc. S.A.E. for list. 20s. for back issues. Paraphysical Laboratory, Downton, Wilt.

## FOR SALE

**YUKAN SELF-SPRAY** SO PROFESSIONAL THE YUKAN AEROSOL WAY

Get these NOW! air drying **GREY HAMMER** OR **BLACK WRINKLE (CRACKLE)** finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 18/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray can only) 15/11 carriage paid.

**SPECIAL OFFER:** I can plus optional transferable snap-on trigger handle (value 5/-) for 18/11 carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

Dept: M-YUKAN, 307a, EDGWARE ROAD, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and leading Industrial Organizations—We can supply you too.

Open all day Saturday. Closed Thursday afternoons.

**500 I.T.A. CONVERTED TUNERS,** 3/- for sample. Limited Quantity of new Boxed Television Valves 7/6 ea. SAE for list. E. Graley, 15 Roskell Road, Liverpool 25.

## FOR SALE

(continued)

## MORSE MADE !! EASY

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-680 2896 send 8d. stamp for explanatory booklet to: **GSCHS (BOX 11), 45 GREEN LANE, FURLEY, SURREY**

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

## WANTED

**SERVICE SHEETS AND MANUALS PURCHASED.** Highest prices paid. Sultan Radio, 29 Church Road, Tunbridge Wells, Kent. Phone T.W. 22093.

**VINTAGE RADIO.** 1930 era. ANY condition. Privately. 25 High Street, Olney, near Bucks.

**CASH PAID** for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS,** 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

**CIRCUIT,** kit or complete tuner for TV Sound. Transistorised. REES, Brendon Carlton Road, South Godstone, Surrey.

## WANTED NEW VALVES ONLY

Must be new and boxed  
Payment by return

**WILLIAM CARVIS LTD.**  
103 North Street, Leeds 7

**WE BUY** New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

**WANTED NEW VALVES,** televisions, radiograms, transistors, etc. **STAN WILLETT,** 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES,** 55 Worcester Street, Wolverhampton.

**ARMY SURPLUS** throat microphones, any quantity; any condition. J. Laycock, Music Department, University, Nottingham.

## METAL WORK

**METAL WORK:** All types cabinets, chassis, racks etc. to your specifications. **PHILPOTTS METAL WORKS LTD.,** Chapman Street, Loughborough.

## ELECTRICAL

**240 VOLT  
ELECTRICITY  
ANYWHERE**



**BEST EVER 200/240 VOLTS "MAINS"  
SUPPLY FROM 12 VOLT CAR BATTERY**

Exclusive World Scoop Purchase. The fabulous Mk. 2D American Heavy Duty Dynamo Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested, only £4.19.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details. Dept. FW STANFORD ELECTRONICS, Rear Derby Road, North Promenade, Blackpool, Lancashire.

## SERVICE SHEETS

**SERVICE SHEETS (1925-1970)** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 1/- Over 8,000 models available. Catalogue 2/6. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex.

**SERVICE SHEETS.** Radio, TV etc. 8,000 models. List 2/-. S.A.E. enquiries. TEL-RAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS (75,000)** 5/- each: please add loose 4d. stamp: callers welcome; always open. THOMAS BOWER, 5 South Street, Oakenshaw, Bradford.

**RADIO, TELEVISION** over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

## TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

## OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND  
LONDON WC2

Make	Model	Radio/TV

1970 List now available at 2/- plus postage

If list is required indicate with X

From .....

Address .....

enclose remittance of .....

(and a stamped addressed envelope)  
s.a.e. with enquiries please

**MAIL ORDER ONLY (February PW)**

## SERVICE SHEETS

(continued)

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,  
RECORD PLAYERS, TRANSISTORS,  
STEREOGRAMS, RADIOGRAMS,  
CAR RADIOS)

Only 10/- each, plus large S.A.E.

(Uncrossed P.O. s please, original  
returned if service sheets not available.)

**C. CARANNA**  
71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of  
Service Sheets (strictly by return of post).  
Please state make and model number  
alternative.

Free TV fault tracing chart or TV list on  
request with order.

Mail order only.

## AERIALS

**BBC**, dipole 30s; H 42s; 3 ele 89s. ITA, 3 ele 26s; 5 ele 34s; 8 ele 47s 5d; 11 ele 57s 6d. ITA doubles 8 ele 112s; 11 ele 140s; 13 ele 159s. Combined BBC/ITA D 5 45s; D 8 52s; H 5 69s; X 5 75s. Combined loft special, D 5 with loft pole and fixings 37s. UHF aerials BBC/ITA, 14 ele 37s; 18 ele 54s; 22 ele 63s; Double 22 ele 142s. Co-ax loss at 1s 3d and 2s 3d. co-ax plugs 1s 4d. Diplexers-Triplexers-Matched UHF/VHF Diplexers, Poles, lashings, clamps, couplers, etc. Postage paid on all aerials. Extra on accessories. Please state channels when ordering.

## BAKER and BAINES

11 Dale Crescent, Tupton, Chesterfield.

"**WORLD ECORD** winning Aerial" Joystick—The Stick that does the Trick! All bands MW, SW, 7ft 6in long. Free brochure: Partridge Electronics (PW) Ltd., Broadstairs, Kent.

## BOOKS & PUBLICATIONS

### SURPLUS HANDBOOKS

19 set Circuit and Notes ... 6/6 p/p 6d.  
1155 set Circuit and Notes ... 6/6 p/p 6d.  
H.R.O. Technical Instructions ... 5/6 p/p 6d.  
38 set Technical Instructions ... 5/6 p/p 6d.  
48 set Working Instructions ... 5/6 p/p 6d.  
88 set Technical Instructions ... 7/- p/p 6d.  
BC.221 Circuit and Notes ... 5/6 p/p 6d.  
Wavemeter Class D Tech. Instr. ... 5/6 p/p 6d.  
18 set Circuit and Notes ... 5/6 p/p 6d.  
BC.1000 (31 set) Circuit and Notes ... 5/6 p/p 6d.  
CR.100/B.28 Circuit and Notes ... 10/- p/p 6d.  
R.107 Circuit and Notes ... 7/- p/p 6d.  
AR.58D Instruction Manual ... 18/- p/p 6d.  
62 set Circuit and Notes ... 6/6 p/p 6d.  
Circuit Diagram 3/- each post free, R.1116/A, R.1294/A, R.1355, R.F. 24, 25 and 26, A.1154, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22 set.  
52 set Sender and Receiver circuits 7/6 post free

Colour code Indicator 2/6 p/p 6d.

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

**INSTRUCTIONAL HANDBOOK  
SUPPLIES**

DEPT. PW, TALBOT HOUSE,  
28 TALBOT GARDENS, LEEDS 8

## RECEIVERS & COMPONENTS

**EMSAC FOR ANTENNA SYSTEMS AND CONVERTERS.** Please send s.a.e. for details of 2 metre converters, antennas and transmatchers for receiving and transmitting. ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD., Highfield House, West Kingsdown, Kent. Tel. W.K. 2344.

## BARGAIN PARCELS

Any 5, 9/-; 10, 14/-; 100, £5.10.0 from the following:  
ECC82, ECL80, EF80, EF85, EF183, EBF89, EB91, EY86, PCC84, PCC89, PCF80, PCL82, PCL83, PCL84, PL36, PL81, PY33, PY81, PY82, U191, 6-30L2, 30FL1, 30F5.

## U.H.F. AERIAL BOOSTER

Transistorised, cavity tuned, high-gain. All uhf channels. Complete with battery and lead. 69/-, p. & p. 1/-, VELCO ELECTRONICS, 62 Bridge Street, Rambottom, Bury, Lancs.

## NEW VHF KIT

Receives Television Sound, Ambulances, Aircraft, Radio 2, 3 and 4 on VHF, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. The Kit comes with easy to follow instructions and circuit. Powered by 9v Battery. Complete with built-in Jack Plug Socket for use with Earphones or Amplifier.

ONLY 57/- P. & P. FREE U.K. ONLY.

Postal Orders, Cheques to:

Dept. P.W.7,

Galleon Trading Co., 298A Lodge Lane, Romford, Essex.

**150 NEW ASSORTED** Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hy-stab, Vitreous, 1-20 watt, 15/- Post Free. WHITSAM ELECTRICAL, 33 Drayton Green Road, West Ealing, W.13.

**COMPLETE RANGE** of Amateur Aircraft, Communications receivers, Chassis, panels, meters, cabinets, microphones, etc. Stephens, James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

**BRAND NEW ELECTROLYTICS**, 15/16 volt 0.5, 1, 2, 5, 8, 10, 20, 30, 40, 50, 100, 200 mfd. 8s per dozen, postage 1s. The C.R. Supply Co., 127 Chesterfield Road, Sheffield 8.


**TO HELP THE HOME CONSTRUCTOR.** Heathkit now make available our surplus Resistors, Capacitors, etc. at Bargain prices. Send for lists. E. Moyle, Daygarn Ltd., Gloucester.

**AUDIOSCAN-HI-FI** loudspeaker systems for the home constructor, cabinet kits, new range of Peerless speakers, speaker kit systems and cross-over networks, BAF wadding and all necessary components. Free speaker fabric samples on request. Send 9d in stamps to: AUDIOSCAN, Dept. P.W., 4 Princes Square, Harrogate, Yorks.
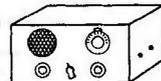
## AT LAST!!! CRYSTAL CLEAR RESOLUTION OF S.S.B.

A highly sensitive receiver specially designed for the amateur bands on 20-40-80-160 metres.

Build in 10 hrs.  
Tune in to world  
S.S.B. or A.M.  
Coils assembled  
and metred  
before despatch



Plug-in coils  
9 Transistors  
Tunable Aerial  
coils  
Push/pull output  
to 3in  
loudspeaker

Designed for the novice constructor. Capable of reception previously only obtainable on very expensive equipment. Kit includes the 3in. speaker, an aluminium chassis and coils for 80 metre reception, assembly instructions with circuit diagram. 18 Guineas

Coil assemblies for 20, 40, 160 metres for amateur wavebands. 30/- each

Coil assemblies for commercial, shipping, aircraft wavebands 30/- each

**RADIO RAVONICS**  
BINGLEY ROAD, CROSSROADS, KEIGHLEY, YORKS.

**RECEIVERS & COMPONENTS**  
(continued)

**Stella Nine Range Cases**

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

**LIST OF PRICES AND SIZES**  
which are made to fit Standard Alloy Chassis

Width	Depth	4" Height		6" Height		7 1/2" Height	
		s. d.	s. d.	s. d.	s. d.	s. d.	s. d.
6 1/2"	3 1/2"	12	6	15	0	18	0
6 1/2"	4 1/2"	13	6	18	0	1	0
8 1/2"	3 1/2"	15	0	1	0	1	0
8 1/2"	6 1/2"	1	1	6	6	1	11
10 1/2"	7 1/2"	1	8	6	15	6	18
12 1/2"	3 1/2"	1	1	6	6	1	11
12 1/2"	6 1/2"	1	8	0	14	0	17
12 1/2"	8 1/2"	1	16	0	3	0	2
14 1/2"	3 1/2"	1	5	0	1	11	6
14 1/2"	9 1/2"	2	3	0	2	15	9
16 1/2"	6 1/2"	1	18	6	2	6	3
16 1/2"	10 1/2"	2	10	0	3	5	0

Cases—Post 4s. 6d. per order.  
Discounts available on quantities.

**CHASSIS in Aluminium, Standard Sizes, with Gusset Plates**

Sizes to fit Cases. All 2 1/2" Walls

s. d.	s. d.	s. d.	s. d.
6" x 3"	5 6	10" x 7"	8 6
6" x 4"	5 9	12" x 3"	6 9
8" x 3"	6 6	12" x 5"	7 6
8" x 6"	7 9	12" x 8"	10 9

Chassis—Post 3s. 0d. per order.  
Discounts available on quantities.

**E. R. NICHOLLS**

Manufacturer of Electronic Instrument Cases  
46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE  
Tel: 061-480 2179

**5,000 TRANSISTORS.** Similar BCY 71. Unmarked and untested. 20 for 25/- or 30 for £5. P & P 1/- and 2/-, respectively. S. E. Ward, 20 Shadwell Road, North End, Portsmouth, Hants.

**A. J. H. ELECTRONICS**

59 Waverley Road, The Kent, Rugby Warwickshire. Tel. Rugby 71066

**P. C. RECEIVER BOARDS**

PCR.1. 6 transistors OC44, 2/OC45, OC81D, 2/OC81, but less the audio transistors i.e. OC81D, & 2/OC81, double tuned 1st. IF. transformerless output approx 1/2 watt to 8 ohm speaker will work with any impedance, size 8 1/2 x 3" less ferrite aerial, tuning capacitor, etc. similar to item previously advertised with data 25/- each.

PCR.2. 7 transistors 3/AF117, 2/AC127, 2/AC128, 1/2 watt output to 5 ohm speaker, size 3 1/2" x 7 1/2" IF. & audio complete, no osc. coil, tuning capacitor, ferrite aerial, etc. requires 9v supply, modern board with miniature components, 35/- each with circuit.

PCR.3. 6 transistors OC44, 2/OC45, OC81D, 2/OC81, transformerless output approx 400 milliwatts requires 6v battery, edgewise volume control, & osc. coil on this board, 3" x 5" as used in pocket portables no details or circuit 25/- each.

All boards as new and unused  
25p post postage stamp type ceramic compression trimmers 6d each 5/- doz. (new) Screw in type car distributor & coil suppressors 6d each (new).

PUSH-PULL output transformers to match EL84s to 15 ohm speaker with negative feedback winding only 9/- each.

Postage add 1/6 MAIL ORDER ONLY

**RECEIVERS & COMPONENTS**  
(continued)

**JEF ELECTRONICS**

New Full Specification Devices

Integrated Circuits complete with data:  
GE PA230 Audio Preamplifier 18/6d  
GE PA234 1W Audio Amplifier 17/6d  
GE PA237 2W Audio Amplifier 32/6d  
Plessey SL402A Preamp & 2W Amp 42/-  
MEL 11 Photo Darlington Amp 9/6d

High quality low cost transistors:  
GE 2N5172 NPN 200mW 1/9d; ME 0412 PNP 200mW 3/9d; TI 2N4059 PNP 250mW 3/6d; MUL BFX86 NPN 800mW 6/-; MUL BD124 NPN 15W 12/-; S 2N3055 NPN 115W 14/6d.

Triacs for full wave power control:  
RCA 40669 8A 400V 24/-; RCA 40583 Trigger Diode 5/3d.

Plastic rectifiers for power supplies:  
IN 4820 1.5A 400V Si Rectifier 2/6d;  
W005 1A 50V full wave bridge Si 7/6d;  
PD40 2A 400V full wave bridge Si 15/-.  
C.W.O. P. & P. 1/- per order.  
York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail order only

**TRANSFORMERS.** Rewound, prototypes and specials made to order. Reasonable charges. S.A.E. please. Ratcliffe, 18 Beech Avenue, Thongsbridge, Huddersfield, Yorks.

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/- P. & P. 1/6. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/- P. & P. 1/6.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for 20/- P. & P. 5/-.

**LARGE CAPACITY ELECTROLYTICS**  
4000MFD 72V } 7/6 ea. P & P 1/6  
16000MFD 12V }  
or £3.10/0 per doz. Carr. 10/-.

**250 MIXED RESISTORS** 12/6  
1/4 & 1/2 watt

**150 MIXED HI STABS** 12/6  
1/4, 1/2 & 1 watt 5% & better.

**EXTRACTOR/BLOWER FANS (PAPST)**

100 CFM 2800 RPM 4 1/2 in x 4 1/2 in x 2 in. Ideal for kitchen extraction, instrument cooling, etc., etc. 50/- each. P. & P. 5/-.

**DIODES** EX EQPT. SILICON

10 AMP 150 PIV 4 for 10/- P. & P. 1/6  
20 AMP 150 PIV 4 for 20/- P. & P. 1/6  
35 AMP 400 PIV 4 for 45/- P. & P. 1/6

**EX COMPUTER "MEMORY" CORE STORE PLANES**

160 bits £1 P. & P. 2/- ideal for experiments.  
4,000 bits £4 P. & P. 4/- demonstrations, etc.  
10,000 bits £8 P. & P. 8/-

**BARGAIN RELAY OFFER**

Single pole change over silver contacts. 25v to 50v. 2.5klt coil. 8 for 10/- P. & P. 1/-

**KEYTRONICS** mail order only  
52 EARLS COURT ROAD,  
LONDON W8 01 478 8499

**RECEIVERS & COMPONENTS**  
(continued)

Build the Prac. Electronics (Vol 4/11-12) RHYTHM GENERATOR

Fabulous with electronic organ or guitar 5 sounds & 12 rhythms, each in choice of 3 percussion patterns. For simpler and neater construction use our un drilled PRINTED CIRCUIT (14 1/2 in x 5 1/2 in) with layout diagram and instructions. Price 29/6d. C.W.O. inc. U.K. postage from: ALMARY DESIGNS, 12 Lattimore Road, Wheathampstead, Herts.

**CONSTRUCTOR'S BARGAIN PACK**

containing 10 PNP germ. transistors, 10 sil. diodes, 3 ex-computer panel (dozens of useful components), 2 reed switches, 50 mixed resistors (1 to 1 watt), 25 condensers. All components brand new (diodes and transistors untested, not guaranteed.) Unbelievable value at 22/6+2/6 p.p. SATISFACTION GUARANTEED OR MONEY BACK. Brand new headphones complete with heavy duty hand mike. To clear at only 15/-+5/- p.p. 6 new ARP12 valves—6/- post free, 12—10/- post free. Carbon microphone inserts 3—3/-+1/- p.p. 6—6/- post free. 12—10/- post free.

MEPPEN-WALTER MAIL ORDER  
12 GLEDHOW PARK DE., LEEDS LS7 4JT

**Cathode Ray Tubes—Full 2 years guarantee**  
—Mail order only, 14in, £6; 17in, £6; 19in, £7 15; 21in, £7 15s; 23in, £9; Twin panel 19in, £12; 23in, £15 7s 6d; Ringuard 19in, £10 9s; 23in, £13 14s. Carriage 12s 6d. Insurance 5s. Television Valves—Most valves available Brand New for extra performance, three months guarantee. 15% off standard price. UHF Signal Boosters—High gain transistor pre-amplifiers from 75s; postage 3s. These units are powered by small 9v battery. Mains unit available from 117s 6d. Please state channel when ordering.

BAKER and BAINES,  
11 Dale Cres., Tupton, Chesterfield.

**SITUATIONS VACANT**

**Trainee Radio Technicians**

A Progressive Career in the Field of Radio and Electronics

Applications are now invited for an intensive training course of two years, leading to appointment as a fully qualified RADIO TECHNICIAN, with further prospects of progression to the Telecommunication Technical Officer Class.

Generous Pay and Conditions while under training.

Candidates must be over 16 and under 21 years of age as at 7 September, 1970, on which date training commences.

Minimum educational qualifications required are passes at GCSE 'O' Level in English Language, Mathematics and Physics (already held or expected to be obtained in the Summer, 1970). Equivalent passes in Scottish or Northern Ireland Certificates and CSE Grade 1 passes are also acceptable.

Closing date for receipt of applications: 27 February, 1970.

Apply for full details and application form to:—

The Recruitment Officer (TRT/37),  
Government Communications Headquarters,  
Oakley, Priors Road,  
Cheltenham, Glos.  
GL52 5AJ

**ENGINEER** required to carry out repairs on stereophonic amplifiers—valve and transistor. Initiative could lead to better things without having qualifications. Why not ring BATTERSEA 3245 Ex 50 or 54 for an interview.

**SITUATIONS VACANT**  
(continued)

**ENGINEERS, A TECHNICAL CERTIFICATE** or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. Write for 132 page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept 137K), Aldermaston Court, Aldermaston, Berks.

**PLEASE MENTION  
"PRACTICAL WIRELESS"  
WHEN REPLYING TO  
ADVERTISEMENTS**

**APPOINTMENTS**

**TECHNICAL OFFICER**  
Home Office Police Scientific  
Development Group

Unestablished vacancy for a Technical Officer Grade III with knowledge and experience of workshop practice and electronic equipment. The successful candidate will work in the equipment section, which is concerned with assessment, trials and development of a wide range of equipment for police use, and will carry out construction, modification and test work in co-operation with police officers. The post is based initially in Central London, but the section will move to Sandridge, near St Albans, later in the year.

Qualifications: Ordinary National Certificate or evidence of an equivalent standard of technical education, together with a five year apprenticeship and at least three years' practical experience. Salary: £1355 (age 25)—£1485 (age 28 or over on appointment)—£1675

Applications should be made to the Principal Establishment Officer (T.O.), Room 324, Home Office, Whitehall, London, S.W.1 by 31st March 1970

**EDUCATIONAL**

LEC

**RADIO AND TELEVISION SERVICING  
RADAR THEORY AND MAINTENANCE  
TELECOMMUNICATIONS**

This private College provides efficient theoretical and practical training in the above subjects. One-year day courses are available for beginners and shortened courses for men who have had previous training.

Write for details to:  
**The Secretary, London Electronics College, 20 Penywern Road,  
Earls Court, London, S.W.5. Tel. 01-373-8721**

**BECOME** "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. **CHAMBERS COLLEGE** (Dept. 857K), 148 Holborn, London, E.C.1.

**CITY & GUILDS** (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. **B.I.E.T.** (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

**RADIO OFFICER** training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

**TRAIN FOR SUCCESS  
WITH ICS**

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how ICS can help you in your career.  
**ICS, DEPT. 541 INTERTEXT HOUSE,  
STEWARTS ROAD, LONDON. SW8**

**CAREERS IN  
SCIENCE AND  
ENGINEERING**

Exciting and rewarding opportunities in these fields are almost unlimited

Write now for details of the following courses offered by:-

**BOURNEMOUTH COLLEGE  
OF TECHNOLOGY**

**UNIVERSITY OF LONDON  
EXTERNAL DEGREES**

**B.Sc. General (Hons.)** — Mathematics, Physics, Chemistry, Botany, Zoology, Statistics

**B.Sc. (Eng.) (Hons.)**—Electrical (including Electronics)

These courses are suitable for both men and women

Study by the Sea in Britain's foremost international and cultural resort.

For prospectus apply to:  
**The Principal, Room 46,  
College of Technology,  
Lansdowne, Bournemouth  
BH1 3JJ. Tel: B.20844**

# Practical Householder annual

128 informative pages packed with money-saving ideas on home improvement and maintenance. Expert advice on tiling a fireplace, building a swimming-pool, fitting an underfloor ventilated fire, installing central heating from a room heater, and a beginners' guide to bricklaying and working in concrete.



Hurry for your  
copy, price 3/-