

# PRACTICAL WIRELESS

JUNE  
1970

3/6

## LIGHT BEAM TELEPHONE



**also:-**

WIDE-RANGE LF SIGNAL GENERATOR  
CONVERTER FOR 10/15m. BANDS  
160/80m. TRANSMITTER/RECEIVER

# ADCOLA Soldering Instruments add to your efficiency

## ADCOLA 64 for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*  
Standard temp. 360°C at 23 watts.  
Special temps. from 250°C—410°C

### \*Additional Stock Bits (illustrated) available

#### COPPER

- B 38**  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE
- B 14**  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE
- B 24**  $\frac{1}{16}$ " — 4.75 mm SCREWDRIVER FACE
- B 12**  $\frac{3}{16}$ " — 4.75 mm EYELET BIT
- B 58**  $\frac{1}{4}$ " — 6.34 mm CHISEL FACE

#### LONG LIFE

- B 42 LL**  $\frac{3}{16}$ " — 4.75 mm CHISEL FACE
- B 38 LL**  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE
- B 14 LL**  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE
- B 44 LL**  $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



**ADCOLA PRODUCTS LTD.,**  
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

\* Write for price list and catalogue


# JACKSON

the big name in **PRECISION** components

## MINIATURE TUNING CAPACITORS

The Jackson 'O' range contains six basic types of different air-dielectric tuning capacitors with a wide variation of capacities available in each type. In addition, there are optional extras such as concentric-spindle slow-motion drives, built-in trimmers and plastic covers. The maximum capacitance per section ranges from 12, 18 or 24 pF for FM types to 420 pF for AM types.

### TYPE "OO"

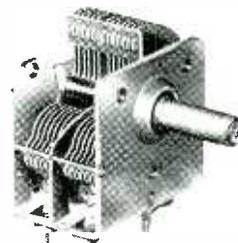


- ★ Type OO miniature twin capacitor at 12/6 each
- ★ Type OFM two-gang for FM at 12/9 each
- ★ Type O two-gang for AM at 12/9 each

Write for literature

**JACKSON BROS. (LONDON) LTD.** (Dept. P.W.)  
KINGSWAY-WADDON, CROYDON, CR9 4DG  
Phone Croydon 2754-5 (01-688) Grams: Walfilco, Croydon  
U.S. Office:—M. SWEDGAL  
258 Broadway, New York, N.Y. 10007
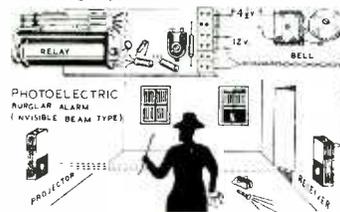
## PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



### PHOTOELECTRIC KIT 39/6

Postage and Pack. 2/6 (UK)  
Commonwealth:  
SURFACE MAIL 3/6  
AIR MAIL £1.0.0  
Australia, New Zealand,  
S. Africa, Canada and U.S.A.  
Also Essential Data Circuits  
and Plans for Building  
10 Advanced Designs

### INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

### LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

### JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Photo-transistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

### JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-Red Filter, 1 amholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit. Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

## YORK ELECTRICS

335 BATTERSEA PARK RD., LONDON S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

# COMPLETE STEREO SYSTEM

FOR ONLY

# 39 GNS

CARRIAGE 35/-




**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on off, stereo mono switch. Brushed aluminium front panel Black metal case with teakwood ends: Size 12 x 5½ x 3¼in. high (Amplifier available separately if required £14.19.6. Carr. 7/6.)

## PREMIER STEREO SYSTEM "TWO"

As system 'ONE' above but with Garrard SP25.

**PREMIER PRICE 45 Gns. Carr. 35/-**


## TELETON SAQ203E STEREO AMPLIFIER

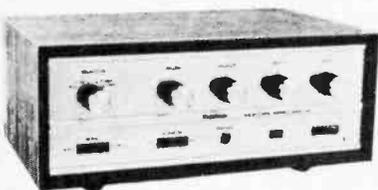

A small but powerful amplifier designed for stereo hi-fi reproduction. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble, Stereo/Mono slide switch. Stereo headphone socket. Attractive oiled walnut cabinet with brushed aluminium front panel. List Price £28.7.0

**OUR PRICE 22 Gns. P. & P. 10/-**
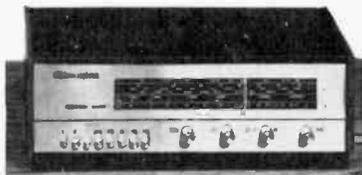
## ALBA UA100D ALL TRANSISTOR STEREO TUNER AMPLIFIER



Covers Long, Medium and Short Waves plus VHF/FM with built in stereo decoder and A.F.C. Output 16 watts r.m.s. per channel into 8 ohms (distortion less than 0.3%). Response 20Hz-20kHz. Inputs for Magnetic and ceramic p.u. and Tape. Tape outlet socket. Tuning, Volume, Bass, Treble and Balance controls. Push button selector. Black leatherette top, teak ends and brushed aluminium front panel.

**PREMIER PRICE £67.11.6 Carrage 12/6.**

## "NOVA" 505 STEREO AMPLIFIER



A superb stereo amplifier offering every facility for the hi-fi enthusiast. Output 5 watts per channel. Frequency response 40-20,000 Hz ± 3dB. Inputs for radio, P.U. Ceramic, P.U. Magnetic Tape. Separate bass and treble controls. Volume and Balance controls, Mono Stereo Switch. Also features headphone socket and tape output. Teak case with attractive illuminated front panel. Size 14½ x 9½ x 3¼in. A.C. 200/250V.

**WONDERFUL VALUE AT ONLY 18 Gns. Carr. 10/-**

## PREMIER STEREO SYSTEM "FOUR"

Teleton SAQ203E Amplifier (as above)	£23.2.0
Garrard SP25	£11.19.6
Shure M3D	£6.19.6
Teak base and cover	£5.10.0
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers	£26.5.0
<b>Total cost if purchased separately</b>	<b>£78.16.0</b>

**PREMIER PRICE 65 Gns. Carr. 35/-**

## PREMIER STEREO SYSTEM "FIVE"

Alba UA100D Tuner/Amplifier	£67.11.6
Garrard SP25	£11.19.6
Shure M3D	£6.19.6
Teak base and cover	£5.10.0
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers	£26.5.0
<b>Total cost if purchased separately</b>	<b>£118.5.6</b>

**PREMIER PRICE £110 Carr. 35/-**

## VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2½in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono inputs. Attractive teak wood grain finish case.



**MONO MODEL 59/6 STEREO MODEL 69/6 P. & P. 2/6.**

## VERITAS V-313 TAPE HEAD DEFLUXER

A must for all tape users! Tape heads become permanently magnetized with constant use: this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds.



**34/6 P. & P. 1/6.**

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped-attractively boxed.

LP3 3" 250' P.V.C.	5/6	LP6 6½" 1200' P.V.C.	12/6
TT3 3" 450' POLYESTER 7/6		DT6 6½" 1800' POLYESTER 22/6	
DF3 3½" 600' POLYESTER 11/6		TT6 6½" 2400' POLYESTER 37/6	
SP3 5" 600' P.V.C.	8/6	SP7 7" 1200' P.V.C.	12/6
LP5 5" 900' P.V.C.	10/-	LP7 7" 1800' P.V.C.	15/-
DT5 5" 1200' POLYESTER 15/-		DT7 7" 2400' POLYESTER 25/-	
<b>TAPE SPOOLS 3" 1/-, 5", 5½", 7" 1/9,</b>		<b>TT7 7" 3600' POLYESTER 30/-</b>	

Post and Packing 3" 1/-, 5", 5½", 1/6, 7" 2/- (8. reels and over Post Free).




## PREMIER STEREO SYSTEM "THREE"

Nova 505 Amplifier (as above)	£18.18.0
Garrard SP25	£11.19.6
Sonotone 9TAHCD	£2.15.0
Teak base and cover	£5.10.0
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers	£26.5.0
<b>Total cost if purchased separately</b>	<b>£65.7.6</b>

**PREMIER PRICE 55 Gns. Carr. 35/-**
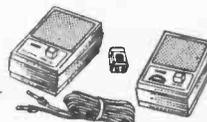
## TWO STATION TRANSISTOR INTERCOMS.

Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home office, factory, etc.



**65/- P. & P. 4/-**

## TAPE CASSETTES

C60 (60 min.)	7/6
<b>THREE FOR 21/-</b>	
C90 (90 min.)	12/6
<b>THREE FOR 36/-</b>	
C120 (120 min.)	17/6
<b>THREE FOR 51/-</b>	

P. & P. 1/-.



## CASSETTE HEAD CLEANER

Removes unwanted deposits from delicate tape heads. Fits all cassette recorders.

**11/6 P. & P. 1/-**

# PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1 Tel: 01-636 3451



# Laskys

## SCOOP Garrard 3000

**CUSTOM UNIT** BY FAMOUS BRITISH MANUFACTURER

A deluxe custom styled and built record player unit made by world famous British manufacturer. The unit incorporates the renowned Garrard 3000 four speed autochanger with lightweight tubular pick-up arm **FITTED WITH SONOTONE 1TA STEREO CARTRIDGE** with diamond stylus. The beautifully made plinth is finished in richly figured teak veneer with tinted perspex panels in the lid and with attractive charcoal grey "mirror" insert panel on front. All metal trim parts are satin chrome. Black leather grain underside. The lid allows the player to operate fully automatically when closed and has snap action "stay" when raised. Mains socket and 5 pin DIN audio output socket are at rear. Overall size 15 1/2" x 7 1/2" x 14in.



**LASKY'S SPECIAL PRICE £16.15.0**

Post 15/-

## AUDIO-TECHNICA Garrard

### SPECIAL OFFER

**AT-35X** Stereo magnetic cartridge with elliptical diamond stylus. Frequency response 20-25 kHz  $\pm 2$  dB. Channel separation 30 dB. Output 5mV. List Price £24.4.9.



**LASKY'S PRICE £17.10.0** Post Free

Also available AT-35 stereo magnetic cartridges with either 0.5 or 0.7 mil diamond stylus assemblies. List Price £18.10.0.

Lasky's Price £13.10.0. Post Free.

**AT-33** Stereo magnetic cart.—frequency response 20-20 kHz with 0.7 mil diamond stylus. Output 5mV. List £10.14.3.

**LASKY'S PRICE £7.19.6**

## ADC 40 PRECISION PICK-UP ARM


The ADC 40 Mk II is a complete low inertia arm with side thrust compensator and anti-drag lead out arrangement. Single-thrust ball bearings used at four points. Accurately machined walnut non-resonant arm. Adjustable counter-weight. Plug-in head shell accommodates nearly all cartridges. Easy installations. Built-in arm rest. Arm length 10 1/2 in. overall. Pivot to stylus tip 9 in. Rear overhang 1 1/2 in.



List Price  
**£19.1.6**

**LASKY'S PRICE**  
**£8.19.6** Post 3/6

## Audio Development

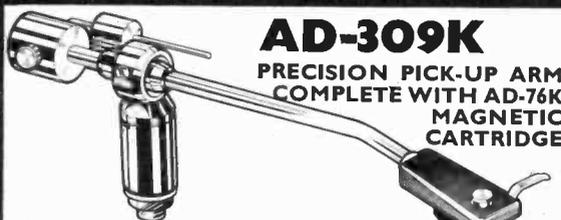

**AD-309K**  
PRECISION PICK-UP ARM  
COMPLETE WITH AD-76K  
MAGNETIC  
CARTRIDGE

The new AUDIO DEVELOPMENT precision counter-balanced pick-up arm—ready fitted with the outstanding AD-76K magnetic cartridge is constructed of brass throughout, heavily chrome-plated; uses needle and miniature ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard 1/4 in. mounting centres and is finished in black enamel with chrome lifting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm.; needle to pivot length 223mm.; offset angle 24°; overhang 10mm. Requires single 1/4 in. dia. mounting hole.

**LASKY'S PRICE £9.19.6** Post 3/6


## AUDIO DEVELOPMENT AD-76K

Stereo magnetic cartridge with diamond stylus  
Frequency response 20-20,000Hz. 5mV output  
Replacement diamond stylus Model JS-P1 38/6

**90/-** Post Free

## SP.25 Mk II

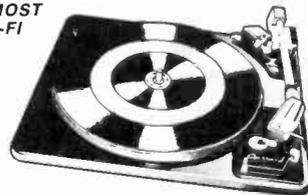**THE U.K.'s MOST POPULAR HI-FI TURNTABLE**



4-speed single record playing deck features include: heavy precision-built turntable, pick-up arm bias compensation, calibrated stylus-force adjustment, cueing device. After play, the arm automatically rises, returns to rest and switches off motor. Finish: dark green polychromatic and silver.

**LASKY'S PRICE £11.19.6**

SP. 25 Mk. II with A. D. 76K Stereo Magnetic Cartridge £15 10 0

### OTHER GARRARD UNITS FROM STOCK

AUTOCHANGERS			
SL72B	£25 0 0	SL65B	£15 10 0
2025TC with stereo cartridge	£8 17 6	1025 with stereo cartridge	£8 10 0
3000 complete with 9TAHC stereo cartridge	£9 19 6	SL95B	£40 0 0
		SL75B	£32 0 0

**SINGLE PLAYERS**  
AP 75, £16.10.0 AP75 with AD76K mag. cart., £21.10.0. 401 Transcription Unit, £20.0.0

### BASES AND COVERS FOR GARRARD UNITS

Type WB1 and WB5 for models 2025TC, 3000, SL65B, 1025, SP25 Mk II Price WB1 £3.16.6, WB5 £5.12.6. Type WB4 for models SL72B, SL75B, SL95B Price £5.12.6. Perspex covers: SPC1 for WB1, £3.14.1. SPC4 for WB4 and WB5 (allows unit to be played with the cover in place)—price £4.8.0.

### PACKAGE DEALS

AP75 complete with AD76K Stereo magnetic cartridge, teak plinth and perspex cover **£30.0.0** Post 10/-  
SP25 Mk II complete with AD76K cartridge, teak plinth and perspex cover **£19.0.0** Post 7/6  
1025 complete with J2105 stereo ceramic cart., teak plinth and perspex cover **£11.19.6** Post 7/6

Post on Garrard units: 8/- extra—except AP75, SL75B, SL95B and 401 7/6 extra. Post on bases and covers 5/- extra.

### SPECIAL OFFER—BSRUA-15

4 speed autochangers with modified tubular tone arm. Comp. with stereo cart. £46.19.6 Post 5/-

## SKYROVER Mk II

### COMMUNICATION RECEIVER



A short wave receiver, exclusive to Lasky's, at a real economy price. Four valve line up using one each 6BE6, 6BA6, 6AV6 and 6AR5 valves, gives highly sensitive reception and powerful gain. Switch selected SW frequency range cover: 1.5 to 30 MHz in three separate band-spread ranges and full AM medium waveband

cover in one range 550-1,600kHz. Reduction drive tuning with hair line cursor. Controls include volume on/off, BFO, Band selector, Power-on indicator lamp. External antenna connections and mains fuse at rear. Internal speaker plus standard 5mm jack socket for phones on front. For 220/240V a.c. mains operation. Strong metal cabinet finished in grey crackle with anodised silver front panel. Size 9 1/2 x 5 1/4 x 5 1/4 in. Complete with mains lead and full instructions.

### THE IDEAL BEGINNERS RECEIVER

**LASKY'S PRICE ONLY £13.13.0**

Post 5/-

# Audio Tronics 70

The 1970 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 28 tabloid pages—many in full colour are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and HI-FI enthusiast. Electronics Hobbyist, Servicemen and Communications Ham. Over half the pages are devoted exclusively to every aspect of HI-FI (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories. All the goods shown are available from any of our branches or by Mail Order to any address in the U.K. or Overseas—bringing the benefits of shopping at Lasky's to you in the comfort of your home. plus Lasky's amazing money saving vouchers worth over £25.00.



**SEND TODAY**  
Send: Your name, address and 2/0 for the post only and inclusion of your name on our regular mailing list  
**THIS MONTHS**

**VOUCHER WORTH 40/-!**

## EXCLUSIVE

### FOSTER "Criterion" MkII HIGH FIDELITY BOOKSHELF SPEAKER

Another high quality bookshelf system from Foster. The "Criterion" MkII is a sealed infinite baffle type enclosure using 5 1/2 in. bass/mid-range woofer with roiled cloth edge and a 2 1/2 in. HF cone type tweeter. The compact cabinet is constructed of 1/2 in. laminate with handsome oiled walnut veneer finish and black woven acoustic gauze—front panel with satin chrome edge insert. SPEC: Frequency range 30-20,000Hz. Power Handling 10 watts. Impedance 8 ohms. HF cross-over. Screw Tag connections at rear. Size 12 1/2 x 7 1/2 x 6 1/2 in. The performance of the "Criterion" is superior to many larger and more expensive units and at Lasky's exclusive price offers absolutely unbeatable value.




LASKY'S PRICE **£9.10.0** or **£17.10.0**  
1—7/6  
2—10/-

## SONICS AS-57

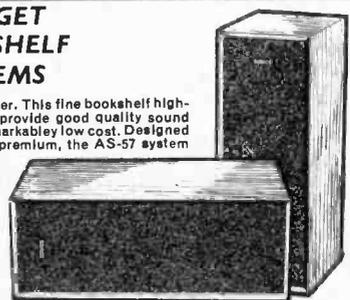
### ELEGANT BUDGET PRICED BOOKSHELF SPEAKER SYSTEMS

The AS-57 is a real space saver. This fine bookshelf high-fidelity speaker system will provide good quality sound anywhere in your home at remarkably low cost. Designed for use where space is at a premium, the AS-57 system is ideal for the small apartment or isolated area. The special high efficiency 5 x 7 in. full range speaker has a frequency range of 70-18,000 Hz with a peak handling capacity of 10 watts. Imp. 8 ohms. Finish: oiled walnut. Size: 5 1/2 x 15 1/2 x 8 1/2 in.



LASKY'S PRICE **£15** per PAIR Post 10/-

# JUST ARRIVED DIGITAL CLOCK SCOOP!

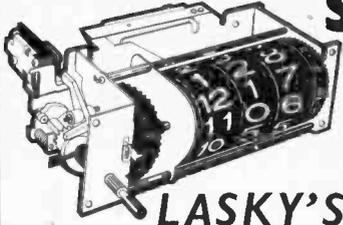

## LASKY'S FIRST AGAIN!

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER
- SILENT OPERATION SYNCHRONOUS MOTOR

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light etc. at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning.

The clock measures 4 1/2 W x 1 1/4 x 3 1/2 (overall from front of drum to back of switch). SPEC: 210/240V AC, 50Hz operation; switch rating 250V. 3A. Complete with instructions. HUNDREDS OF APPLICATIONS FOR THE ELECTRONICS HOBBYIST.

LASKY'S PRICE **£6.19.6** POST 3/6  
SPECIAL QUOTATIONS FOR QUANTITIES

## COLOUR + SOUND DJ LIGHT CONTROL UNITS



These two psychedelic light control units may be fed from the speaker output of the Amplifier although drawing virtually no signal themselves, they are suitable for connection across a 60 watt max. amplifier. The signal is fed to a thyristor light control unit. (In the case of the DJ30L, the signal is split 3 ways, bass, middle, and top, to independent

thyristor circuits). Independent Intensity controls and lights-on override switches are provided. Outputs are to 5A 2 pin sockets on the back of the instrument. Main on/off switches and pilot lights are provided. Specs: DJ10L. Single channel thyristor control. 1000 watts max. light output. Input level equivalent to 60 watts RMS into 15 ohms, or similar voltage. 220-250V. 50-60 Hz. Size 6 x 6 x 5 1/2 in. DJ30L. 3 channel thyristor control (built-in cross-over). 1000 Watts max. light output. Per channel (de-rate to 600 watts per channel when all three channels are used simultaneously) 220/250V. 50-60 Hz. Size 6 x 10 x 5 1/2 in. Complete with instructions. Both units are panel mounting with brushed aluminium front panel.

DJ 10L **£19.10.0** Post 3/6  
DJ 30L **£37.10.0** Post 5/-

NEW EAGLE LIGHT CONTROL UNIT  
NOW AVAILABLE **£11.19.6** Post 3/6

## NEW BRANCH

We have pleasure in announcing the opening of yet another Lasky's Audio, Electronics and HI-FI Centre— **109 FLEET STREET, E.C.4.** Here you will find the customarily wide range of everything for the audio, HI-FI and tape recording enthusiast, electronics hobbyist and communications ham. An especially comprehensive range of high fidelity equipment is presented for easy comparison. We look forward to welcoming you at our newest city branch.

# Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271  
33 TOTTENHAM CT. RD, LONDON, WIP 9RB. Tel: 01-636 2605  
Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5822  
152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833  
Open all day Thursday, early closing 1 p.m. Saturday

HIGH FIDELITY AUDIO CENTRES  
42-45 TOTTENHAM CT. RD, LONDON, WIP 9RD. Tel: 01-580 2753  
Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789  
Open all day Saturday early closing 1 p.m. Thursday



ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821



### FABULOUS VALUE

#### TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED

Only **28** Gns. + P & P 17/6  
Credit terms available, first monthly payment £3.6.2 followed by 9 monthly payments of £3.6.2. (Total "Credit Sale" Price £33.1.8). Send £4.3.8 today.

### FANTASTIC BARGAIN OFFER!

#### "TRANSCONTINENTAL" FULLY TRANSISTORISED STEREOPHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price **ONLY**

10 Watts Total output **£36.10.0** P & P 17/6  
17 Transistors & 10 diodes

EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY  
Credit Terms available. First monthly payment £4.2.2 followed by 9 monthly payments of £4.2.2. (Total "Credit Sale" Price £41.1.8). Send £4.19.8 today.



Callers Welcome

POST THIS COUPON NOW!

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name

Address

**LEWIS radio** 100 CHASE SIDE, SOUTHGATE, Dep. P670 LONDON, N.14. TELEPHONE 634 3733/9666

## Kinver for Components

### SILICON TRANSISTORS FOR HIGH QUALITY EQUIPMENT

BC107	3/3	BD123	24/3	TIP32A	23/-	2N3055	15/9
BC108	3/-	BDY20	24/3	T1844	1/8	2N3702	8/6
BC109	3/3	BF184	7/6	T1849	2/6	2N3703	3/3
BC158	7/6	BF194	7/-	T1850	3/9	2N3704	3/9
BC182L	3/2	BFX29	10/4	2N696	4/9	2N3705	3/4
BC183L	2/5	BFX84	6/8	2N697	5/-	2N3707	4/-
BC184L	3/2	BFX85	8/8	2N706	3/3	2N3708	2/5
BC212L	3/9	BFY50	5/-	2N1132	10/9	2N3819	9/-
BC213L	3/9	BFY51	4/6	2N2906	13/-	2N3820	18/9
BC214L	4/-	BFY52	5/-	2N2924	4/4	2N3826	5/11
BCY70	5/4	BRV95A	3/11	2N2925	5/3	2N4058	4/6
BCY71	10/4	MJ481	27/3	2N2926	3/-	2N4059	3/5
BCY72	4/6	MJ491	32/11	2N3053	6/8	2N4427	9/9
BD121	17/3	TIP31A	17/-				

### 1 WATT AMPLIFIER MODULE TYPE PCMI

This amplifier unit is a printed circuit module incorporating the popular and well tried FA234 i.c. amplifier. The unit is a complete AUDIO AMPLIFIER and requires no external components, you simply connect an 18 volt power supply and a 15 or 16 ohm speaker or head phone, even the supply smoothing capacitor and the output capacitor are included! The overall dimensions, including capacitors are 2 1/2" x 3" x 1/2". The input for 1 watt output at 1kHz is typically 300mV into 100 kohms.

This unit is available at only 36/- net complete with descriptive leaflet or 70/- net per pair. Send for free leaflet.

### ELECTRONIC COMPONENTS IN THE WEST MIDLANDS

A wide range of components are available from stock for CALLERS, including the following:  
**RESISTORS** (includes 5% 1 watt, High stable at only 2d. each in 100+ quantities of MIXED values of your choice in the E 12 series from 10 ohm to 10 Mohm)  
**CAPACITORS** (includes Polyester, polystyrene, metallised film, miniature electrolytics, silver mica).  
**SEMICONDUCTORS**, (includes Integrated circuits, transistors, diodes, rectifiers).  
**PLUS ALL** the usual components such as plugs & sockets, pots, Veroboard, etc.

### WE ARE AN INTERNATIONAL RECTIFIER SEMICONDUCTOR CENTRE

Mail order, 1/6 P & P per order inland, Overseas at cost, min. 10/- . Open 9.00 a.m. to 12.50 p.m. 2.00 p.m. to 5.00 p.m. Weekdays, 9.00 p.m. to 12.50 p.m. Saturdays. Please note, we will be closed for annual holiday from June 1 to June 6 inclusive.

**ELECTRONICS LTD**  
**Kinver**

STONE LANE KINVER  
STOURBRIDGE WORCS  
Telephone: KINVER 2099

# Peerless

PEERLESS FABRIKKERNE A/S  
COPENHAGEN · DENMARK

### HIGH FIDELITY LOUDSPEAKER KIT SYSTEMS FOR THE HOME CONSTRUCTOR

#### KIT 2-8

Max. Power Input ..... 10 watts.  
Frequency Range .... 50-18,000 Hz in  
0.57 cu. ft. cabinet.

Woofer ..... B 65 W.  
Tweeter ..... MT 25 HFC  
Cross-over Frequency .... 4000 Hz.  
Delivered with components for  
dividing network and drawing for  
cabinet.

Price ..... **£6-14-0** incl. tax.

#### KIT 3-25

Max. Power Input ..... 25 watts.  
Frequency Range .... 40-18,000 Hz in  
3 1/2 cu. ft. cabinet.

Woofer ..... CM 120 W.  
Mid-range ..... G 50 MRC.  
Tweeter ..... MT 20 HFC  
Cross-over Frequencies 750 & 4000 Hz.  
Delivered with ready-wired cross-over  
network and cabinet leaflet.

Price ..... **£15-17-6**

#### KIT 3-15

Max. Power Input ..... 15 watts.  
Frequency Range .. 45-18 000 Hz in  
1.06 cu. ft. cabinet.

Woofer ..... P 825 W.  
Mid-range ..... GT 50 MRC  
Tweeter ..... MT 20 HFC  
Cross-over Frequencies 750 & 4000 Hz.  
Delivered with components for  
dividing network and cabinet leaflet.

Price ..... **£12-9-5** incl. tax.

#### KIT 20-2

Max. Power Input ..... 30 watts.  
Frequency Range .... 40-20,000 Hz in  
0.7 cu. ft. cabinet.

Woofer ..... L 825 WG.  
Tweeter ..... MT 225 HFC  
Cross-over Frequency .. 2500 Hz.  
Delivered with ready-wired cross-over  
network and cabinet handbook.

Price ..... **£12-12-6** incl. tax.



KIT 3-25

TO: P. F. & A. R. HELME, Dept, PW6, SUMMERBRIDGE,  
HARROGATE, YORKS.

(sole U.K. distributors)

Please send me details on the Peerless kit system .....

Name .....

Address .....

Peerless Fabrikkerne A/S have over 35 years of experience in acoustics and they are today the largest loudspeaker factory in Scandinavia.

# COMET

Hi-Fi DISCOUNT WAREHOUSES

- All items offered are brand new, latest models in manufacturers' sealed cartons. Fully guaranteed with after-sales service.
- Complete Free price list of over 800 items on request.



Customers Welcome  
Open Daily to the public from 9 a.m. Closed Tuesday 1 p.m.  
Mon. & Sat. 5-30 p.m. Open until 8 p.m. Wednesday & Friday.

	Rec. Price	Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>			
ARENA 210 Amplifier	£34	13 0	£28 0 0
ARMSTRONG 521	£52	0 0	£42 19 6
DULCI 207	£25	0 0	£17 0 0
DULCI 207M	£30	0 0	£20 19 0
GOODMANS Maxamp	£54	0 0	£44 19 6
LEAK Stereo 30 Plus	£53	0 0	£43 19 6
LEAK Stereo 30 Plus in leak case	£59	10 0	£47 19 6
LEAK Stereo 70	£65	0 0	£53 19 6
LEAK Stereo 70 in leak case	£71	10 0	£57 19 6
LINEAR LT.66	£18	18 0	£15 19 6
PHILIPS RH 591	£73	0 0	£56 1 6
PHILIPS RH 590	£49	0 0	£37 12 6
PHILIPS RH 590	£26	0 0	£19 19 6
PHILIPS 580	£26	0 0	£12 19 6
PHILIPS 590	£49	0 0	£37 12 6
PHILIPS 591	£73	0 0	£55 19 6
QUAD 33 Pre-amplifier	£43	0 0	£37 19 6
QUAD 303 Main Amplifier	£55	0 0	£47 19 6
ROGERS Ravensbourne	£59	10 0	£48 19 6
ROGERS Ravensbourne in leak case	£64	0 0	£52 13 6
ROGERS Ravensbrook	£44	0 0	£36 19 6
ROGERS Ravensbrook in leak case	£49	0 0	£38 19 6
ROGERS Ravensbrook (Chassis)	£45	0 2	£39 19 6
ROGERS Ravensbrook (Chassis) in leak case	£51	5 3	£42 19 6
SINCLAIR 2000	£30	9 0	£24 19 6
TELETON 203E	£28	7 6	£21 15 6
TRUVOX TSA.200	£54	12 0	£35 19 6

	Rec. Price	Retail Price	Comet Price
<b>TUNERS</b>			
ARENA F211 with decoder	£39	10 0	£33 19 6
ARMSTRONG 523 AM/FM	£52	9 0	£44 19 6
ARMSTRONG 524 FM	£40	4 6	£34 19 6
ARMSTRONG M8 decoder	£9	10 0	£7 19 6
DULCI FMT.7 FM	£22	1 0	£17 19 6
DULCI FMT.75 Stereo	£31	0 0	£25 5 0
GOODMANS stereomax	£82	10 5	£71 19 6
LEAK Trougline with MPX	£51	10 6	£39 19 6
LEAK Stereofetic Chassis	£59	18 0	£51 19 6
LEAK Stereofetic in leak case	£67	3 6	£57 10 0
PHILIPS RH 690	£39	0 0	£33 2 6
PHILIPS 690	£39	0 0	£32 19 6
QUAD Stereo FM	£51	0 0	£39 19 6
ROGERS Ravensbourne Tuner with Decoder	£61	17 9	£52 12 6
SINCLAIR 2000	£26	14 6	£19 4 6
TRUVOX FM 200/IC with decoder	£60	11 10	£39 19 6

	Rec. Price	Retail Price	Comet Price
<b>TUNER/AMPLIFIERS</b>			
ARENA 2400 with MPX	£90	6 0	£69 19 6
ARENA 2600 Stereo AM/FM with MPX	£111	6 0	£94 0 0
ARENA 2700 Stereo FM with MPX decoder	£105	0 0	£85 0 0
ARENA T1500F with MPX	£72	9 0	£59 19 6
ARENA T9000 with MPX	£303	9 0	£258 0 0
ARMSTRONG 525	£87	16 9	£66 19 6
ARMSTRONG 526	£98	15 6	£79 19 6
ARMSTRONG 127	£43	19 9	£37 19 6
(Teak Case for 127)	£3	17 0	£3 10 0
GOODMANS 3000	£77	19 7	£69 19 6
PHILIPS RH781	£74	19 6	£63 14 6
PHILIPS RH790	£125	0 0	£106 4 6
PHILIPS RH 691	£83	0 0	£70 10 6
TANDBERG SolvSuper	£75	18 0	£55 19 6
TELETON F.2000	£51	0 0	£37 19 6
TELETON 7AT1	£133	0 0	£85 6 6
TELETON R.4200	£51	15 0	£42 19 6
TELETON CR/10T	£39	0 0	£29 19 6

	Rec. Price	Retail Price	Comet Price
<b>COMPLETE HI-FI SYSTEMS</b>			
METROSOUND Stereo 1010	£77	6 4	£65 19 6
TELETON MX.950	£64	13 2	£48 19 6
TELETON R.8000	£60	19 6	£49 19 6
TELETON CMS 300	£105	15 0	£79 19 6
TELETON CMS.400	£126	0 0	£89 0 0
MARCONI unit 4	£77	9 0	£66 19 6
GOODMAN 3000 suite	£140	9 0	£117 0 0
WYNDSOR System	£59	19 6	£49 19 6
VIDEORAMA	£42	19 6	£35 0 0

	Rec. Price	Retail Price	Comet Price
<b>CARTRIDGES</b>			
Goldring 800 Cartridge	£13	0 0	£10 7 6
Goldring 800H	£10	13 9	£8 10 6

	Rec. Price	Retail Price	Comet Price
Goldring 800E	£18	17 1	£15 0 0
Goldring 800 Super E	£26	0 1	£20 15 0
Goldring G850	£6	10 0	£5 10 0
Goldring CS90 Stereo Ceramic Cartridge	£5	4 0	£4 3 0
Goldring CS91/E	£7	16 1	£6 4 6
Pickering V15 AC2	£8	8 0	£6 19 6
Ortofon SL 15E	£29	12 11	£23 12 11
Ortofon 2X 15K	£7	0 0	£5 5 4
Shure M30M	£7	8 3	£6 8 3
Shure N3D	£5	11 2	£4 8 8
Shure M31E	£12	19 5	£10 6 0
Shure N31E	£9	5 3	£7 8 6
Shure M32E	£12	0 11	£9 12 0
Shure N32E	£8	6 9	£6 13 0
Shure M32-3	£11	2 4	£8 17 6
Shure N32-3	£6	9 8	£5 3 6
Shure M44-5	£11	2 4	£8 17 6
Shure N44-5	£7	3 8	£6 8 3
Shure M44-7	£10	3 10	£8 5 0
Shure N44-7	£6	9 8	£5 3 6
Shure M44-C	£10	3 10	£8 5 0
Shure N44-C	£6	9 8	£5 3 6
Shure M44E	£14	16 6	£11 16 6
Shure M44E	£13	9 8	£10 12 0
Shure M55E	£16	13 6	£14 13 6
Shure N55E	£11	2 4	£8 17 6
Shure M75G	£17	12 1	£14 0 0
Shure N75G	£9	5 3	£8 17 6
Shure M75-6	£15	13 6	£13 6 0
Shure N75-6	£8	6 9	£6 13 0
Shure M75EJ	£24	1 9	£19 4 6
Shure N75EJ	£11	2 4	£8 17 6
Shure M75E-95G	£27	15 11	£22 3 6
Shure N75E	£12	19 5	£10 6 6
Shure V15-11	£40	15 3	£32 19 6
Shure VNT5E	£16	13 6	£14 13 6
Shure V15-11-7	£38	18 3	£31 0 0
Shure VNT	£14	16 6	£11 16 6

	Rec. Price	Retail Price	Comet Price
<b>TURNABLES</b>			
ARENA SP25 with base, cover and Pickering magnetic cartridge	£30	19 0	£24 19 6
GARRARD SP. 25, MK II	£15	11 4	£11 19 6
GARRARD AP. 75	£23	15 0	£17 19 6
GARRARD SL 55	£13	3 10	£12 0 0
GARRARD SL 65B	£19	6 5	£14 9 6
GARRARD SL 75B	£35	12 4	£28 19 6
GARRARD SL 95B	£45	9 1	£37 19 6
GARRARD 401	£31	14 2	£26 10 0
GARRARD SL 72B	£30	2 0	£24 19 6
GARRARD 3500 with GKS Cartridge	£15	15 0	£11 19 6
GOLDRING GL 69	£25	1 6	£21 5 0
GOLDRING 69P	£33	11 9	£28 19 6
GOLDRING GL 75	£36	8 2	£27 19 6
GOLDRING 75P	£46	18 8	£38 0 0
GOLDRING COVERS for 69P and 75P	£4	4 3	£3 8 0
GOODMANS 3025	£37	14 9	£32 19 6
PHILIPS 228	£19	19 6	£16 19 6
PHILIPS GA 146	£29	19 6	£24 19 6
PHILIPS 217	£22	0 9	£27 4 0
PHILIPS 202 Electronic	£64	0 0	£54 0 0
THORENS TD. 125	£75	17 8	£59 19 6
THORENS 125 AB	£120	3 11	£99 19 6
THORENS 150A MK II	£43	12 7	£32 19 6
THORENS 150AB MK II	£47	8 7	£40 19 6
THORENS TD. 124/II	£46	15 10	£39 19 6
Bases, plinths and covers stocked.			

	Rec. Price	Retail Price	Comet Price
<b>SPEAKERS</b>			
ARENA HT 27	£18	18 0	£13 19 6
ARENA HT 28	£17	0 0	£12 19 6
ARENA HT 21	£10	10 0	£9 5 0
ARENA HT 7	£19	19 0	£17 0 0
ARENA HT 10	£22	1 0	£18 19 6
ARENA HT 20	£32	11 0	£26 19 6
ARENA HT 26	£78	15 0	£65 19 6
B & W DM3	£63	0 0	£53 6 0
B & W P2H	£94	10 0	£81 5 6
B & W DM1	£32	0 0	£25 19 6
CELESTION Dilton 10	£21	3 2	£17 5 0
CELESTION Dilton 15	£29	0 0	£22 10 0
DULCI AS 3	£8	8 0	£6 19 6
GOODMANS Majesta	£57	0 0	£48 19 6
GOODMANS Maxim	£20	7 9	£15 19 6

	Rec. Price	Retail Price	Comet Price
<b>GOODMANS Mezzo II</b>			
GOODMANS Magnum-K	£30	18 0	£24 19 6
GOODMANS Mirimba	£40	2 0	£31 19 6
GOODMANS Mambo	£24	0 1	£19 19 6
GOODMANS 3005 (pair)	£22	5 6	£18 11 6
KEF Celeste	£25	0 0	£21 0 0
KEF Concord	£29	0 0	£22 10 0
LEAK Sandwich	£43	10 0	£33 19 6
LEAK Mini-Sandwich	£45	10 0	£36 19 6
LOWTHER L.I.P. with PH6	£29	15 0	£23 19 6
PHILIPS RH 481	£11	0 0	£9 2 6
PHILIPS RH 482	£18	0 0	£14 18 6
QUAD Electrostatic	£66	0 0	£55 19 6
TRUVOX LS200	£22	7 3	£15 19 6
<b>WHARFEDALE Speakers</b>			
Alredale	£69	10 0	£57 14 0
Dornton	£19	0 0	£14 19 6
Super Linton	£22	10 0	£18 19 6
Melton	£29	10 0	£23 19 6
Dovedale 3	£39	10 0	£29 19 6
Rosedale	£59	10 0	£48 19 6
<b>WHARFEDALE</b>			
UNIT 4 Speaker Kit	£11	19 6	£9 19 6
UNIT 5 Speaker Kit	£16	0 0	£13 10 0
UNIT 5 Speaker Kit	£23	10 0	£19 19 6
Most types of chassis, speakers, cross over networks, etc., available ex-stock.			

	Rec. Price	Retail Price	Comet Price
<b>CHASSIS SPEAKERS</b>			
Goodmans Axielte 8	£7	2 1	£5 13 6
Goodmans Twnaxlette 8	£8	0 7	£6 8 0
Goodmans Axlom 10	£8	8 0	£6 14 0
Goodmans Axlom 201	£12	10 0	£9 7 6
Goodmans Axlom 301	£17	18 0	£13 8 6
Goodmans Audlom 51	£11	6 0	£8 8 6
Goodmans Audlom 61	£16	7 0	£12 5 6
Goodmans Audlom 81	£27	12 0	£20 14 0
Goodmans Audlom 91	£21	5 0	£23 8 6
Goodmans Audlom 91/100	£23	17 0	£26 9 6
Goodmans ARU 180	£3	17 8	£2 18 6
Goodmans ARU 280	£3	17 8	£2 18 6
Goodmans ARU 480	£5	8 5	£4 1 3
Goodmans ARU 172	£3	17 8	£2 18 6
Goodmans Trebox 100	£7	9 0	£5 11 6
Goodmans Trebox 5K/20K	£8	8 0	£6 6 0
Goodmans Midax	£11	4 0	£8 8 0
Goodmans Attenuator	£3	1 4	£2 6 0
Goodmans Crossover Networks XO/950/5000	£8	8 7	£6 6 0
Goodmans Crossover Networks XO/950	£6	7 9	£4 15 9
Goodmans Crossover Networks XO/5000	£2	6 0	£1 14 6
Wharfedale 8" Bronze/RS/DD	£4	8 0	£3 13 6
Wharfedale Super 8/RS/DD	£7	12 0	£6 6 0
Wharfedale Super 10/RS/DD	£12	14 0	£10 10 0
Wharfedale WMT			
Matching Transformer		16 9	13 6

	Rec. Price	Retail Price	Comet Price
<b>HI-FI STEREO TAPE DECKS AND TAPE RECORDERS</b>			
AKAI 150D	£130	2 4	£109 0 0
AKAI X-360	£339	0 0	£284 0 0
AKAI X-360 D deck	£290	0 0	£243 0 0
AKAI 1710	£109	0 0	£89 19 6
AKAI 1800	£158	0 0	£133 0 0
AKAI 1800SD	£199	0 0	£167 0 0
AKAI 4000 D deck	£87	10 0	£71 19 0
TR			

# Complete stereo system — £29-10

The new Duo general-purpose 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

## Type 1 SPECIFICATION:—

Impedance 3, 8 or 10 ohms (please state requirement) high flux 6" x 4" speaker and 2½" tweeter. Teak finish 12" x 6½" x 5½". 4 guineas each. 7/6d. p. & p.

Type 2 as type 1. Size 17½" x 10½" x 6½". Incorporating 10½" x 6½" speaker and 2½" high frequency speaker 3 ohms impedance £6-6-0 plus 15/- p. & p.

Garrard Changers from £7.19.6d. p. & p. 7/6d.  
Cover and Teak finish Plinth £4.15.0d. 7/6d p. & p.

The items illustrated can be purchased together for £29-10.

The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

## SPECIFICATION:—

R.M.S. power output: 3 watts per channel into 10 ohms speakers. INPUT SENSITIVITY. Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.

CONTROLS: 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.

TONE CONTROL: Treble lift and cut. Separate on/off switch. A preset balance control.

*Duetto*

Integrated Transistor Stereo Amplifier plus 7/6d. p. & p.

**£9-10**



The above 5 items can be purchased together for £29.10 + £1.10.0 p. & p.

## The Classic

**£9** plus 7/6 p. & p.

Controls: Selector switch Tape speed equalisation switch (3½ and 7½ i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 position rumble filter.

Specification: Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape head: 3mV (at 3½ i.p.s.). Mag. P.U.: 2mV. Cer. P.U.: 80mV. Tuner: 100mV. Aux.: 100mV. Tape/Rec. output: Equalisation for each input is correct to within ±2dB (R.I.A.A.) from 20Hz to 20KHz. Tone control range: Bass ±13dB at 60Hz. Treble ±14dB at 15KHz. Total distortion: (for 10 watt output) <1-5%. Signal noise: <-60dB. A.C. mains 200-250v. Built and tested. Size 12½in. long, 4½in. deep, 2½in. high. Teak finished case.



## The Viscount

**£14.5** plus 7/6 p. & p.

Integrated High Fidelity Transistor Stereo Amplifier. Specification—Output: 10 watts per channel into 3 to 4 ohms speakers (20 watts monaural). Input: 6 position rotary selector switch (3 pos. mono and 3 pos. stereo), P.U., Tuner, Tape and Tape Rec. out. Sensitivities: All inputs 100mV into 1-3M ohm. Frequency Response: 40Hz-20KHz ±2dB. Tone Controls: Separate bass and treble controls; treble, 13dB lift and cut (at 15KHz); Bass, 15dB lift and 25dB cut (at 60Hz). Volume Controls: Separate for each channel. A.C. Mains Input: 200-240V. 50-60Hz. Size, 12½" x 6" x 2½" in teak finished case. Built and tested.

VISCOUNT MARK II for use with magnetic pick-ups specification as above. Fully equalised for magnetic pick-ups. Suitable for cartridges with minimum output of 4mV/cm/sec. at 1kc. Input Impedance 47k. £15.15 plus 7/6 p. & p.



also see opposite page



## SPECIAL OFFER!

Complete stereo system comprising BALFOUR 4-speed autoplayer with stereo head, 2 Duo speaker systems, size 12in. x 6½in. x 5½in. Plinth (less cover) and the DUETTO stereo amplifier. All above items

**£25** plus £2 p. & p.

## NEW COMPLETE HI-FI STEREO SYSTEM - £41

comprising SP 25 Garrard Mk II with diamond cartridge, or 2025 TC, Viscount Mk I amplifier, two type 2 speakers, plinth and cover

**£41** plus £2-10-0 p. & p.



### The ELEGANT SEVEN Mk. III (350mW Output)

7 transistor fully tunable M.W.-L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.  
Price £55.0 plus 7/6 P. & P.


Circuit 2/6  
FREE WITH PARTS.

### The DORSET (600mW Output)

7-transistor fully tunable M.W.-L.E. superhet portable—with baby alarm facility. Set of parts. The latest modernised and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

Price £55.0 plus 7/6 P. & P.

MAINS POWER PACK KIT: 9/6 extra

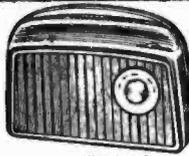

Circuit 2/6  
FREE WITH PARTS



### EXTRACTOR FAN

A.C. mains 230/250v. complete with pull switch. Size: 6 x 6 x 4in.

Price 27/6 plus 7/6 P. & P.


### X101 10W SOLID-STATE HI-FI AMP WITH INTEGRAL PRE-AMP

Specifications: Power Output (into 3 ohms speaker) 10 watts. Sensitivity (for rated output): 1mV into 3K ohms (0.33 microamp). Total Distortion at 1KHz at 5 watts, 0.35%, at rated output 1.5%. Frequency Response: Minus 3dB points 20Hz and 40KHz. Speaker: 3-4 ohms (3-15 ohms may be used). Supply voltage: 24V. DC. at 800mA (6-24V. may be used).

Price 69/6 plus 2/6 P. & P.

Control assembly: Including resistors and capacitors. 1. Volume: PRICE 5/-. 2. Treble: PRICE 5/-. 3. Comprehensive bass and treble: PRICE 10/-. The above 3 items can be purchased for use with the X101

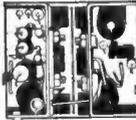Power Supplies for the X101:  
P101 M (for mono) 35/- plus 4/6 p. & p.  
P101 B (for stereo) 42/6 plus 4/6 p. & p.



### CAR TRANSISTOR IGNITION SYSTEM


by famous manufacturer

For 6 volt or 12 volt positive earth systems. Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers, etc.).

Price £4.19.6 plus 5/- P. & P.

### 50 WATT AMPLIFIER

A.C. Mains 200-250V

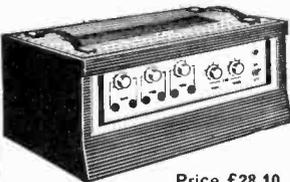

Price £28.10

plus 20/- p. & p. or guitars. Channels 3 & 4 300mV at sensitivity relative to 10w output. TONE CONTROLS ARE COMMON TO ALL INPUTS. Bass Boost +12dB at 60Hz. Bass Cut -13dB at 60Hz. Treble Boost +11dB at 15 KHz. Treble Cut -12dB at 15 KHz. With bass and treble controls central—3dB points are 30 Hz and 20 KHz. POWER OUTPUT: For speech and music 50 watts rms. 100 watts peak. For sustained music 45 watts rms. 90 watts peak. For sine wave 38.5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3.2% at 1KHz. Total distortion at 20 watts 0.15% at 1KHz. Output to match into 8 or 15 ohms speaker system. NEGATIVE FEEDBACK 20dB at 1KHz. SIGNAL TO NOISE RATIO 60dB. MAINS VOLTAGES adjustable from 200-250V. A.C. 50-60Hz. A protective fuse is located at the rear of unit. Output impedance, 3, 8 and 15 ohms.

### B.S.R. TD-2 TAPE DECK


Takes 5 1/2 in. spools, fitted with B.S.R. 1 Track Heads. Size 13 1/2 in. long by 8 1/2 in. wide.

Price £8.19.6 plus 7/6 P. & P.

TERMS C.W.O.  
All enquiries S.A.E.

### The RELIANT
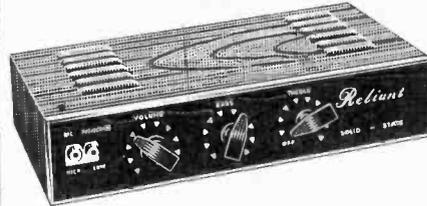
### SOLID-STATE GENERAL PURPOSE AMPLIFIER



#### SPECIFICATIONS

Output—10 watts  
Inputs—1. xtal mic 10mV Tone Controls—Treble control range ±12dB at 10KHz.  
2. gram/radio 250mV  
Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10 1/2" x 4 1/2" x 2 1/2". For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from gram. and mike. Built and tested.

#### RELIANT Mk. I

As above less teak case  
£5.15 plus 7/6 P. & P.

#### RELIANT Mk. II


In teak finished case.  
£6.16 plus 7/6 P. & P.

### RECORD PLAYER SNIP

A.C. Mains 240V

The "Princess", 4-speed automatic record changer and player engineered with the utmost precision for beauty, long life, and trouble free service. Will take up to ten records which may be mixed 7" to 10" or 12". Patent stylus brush cleans stylus after each playing and at shut off, the pick-up locks itself into its recess, a most useful feature with portable equipment—other features include pick-up height adjustment and stylus pressure adjustment. This truly is a fine instrument which you can purchase this month at only £5.19.6 complete with cartridge and ready to play. Post and ins. 7/6 extra.

ONLY £5.19.6 plus 7/6 P. & P.

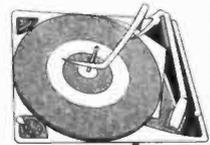

### POCKET MULTI-METER




Size 3 1/2 x 2 1/4 x 1 1/2 in. Meter size 2 1/4 x 1 1/2 in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. volts 0-15, 0-150, 0-1,000 D.C. current 0-150mA Resistance 0-100K Ohm Complete with test leads, battery and full instructions.

42/6 plus 3/6 P. & P.

FREE GIFT for limited period only, 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter

### 40W FLUORESCENT LIGHT KIT

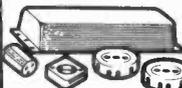

Incorporating GEC Choke size 8 1/2 x 1 1/4 in. 2 bi-pin holders, starter and starter-holder. P. & P. 5/6. 11/6

Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 1 1/4 x 1 1/4 x 1 1/2 in. 2 bi-pin holders, start and starter holder. P. & P. 6/6 17/6

### THREE-IN-ONE HI-FI 10 WATT SPEAKER

A complete Loud Speaker system on one frame, combining three matched ceramic magnet speakers with a low loss crossover network. Peak handling power 10 watts. Impedance 15 ohms. Flux density 11,000 gauss. Resonance 40-60 c/s. Frequency range 50c/s to 20Kc/s. Size 13 1/2 x 8 1/4 x 4 1/2 in. By famous manufacturer.

List price £7 OUR PRICE 74/6 plus 5/- P. & P.

Similar speaker to the above without tweeters in 3 and 15 ohms 44/8 plus 5/- p. & p.


### PYE CAR RADIO

Push Button Tuning Heart

This PRETOLOCK 5 station Push-Button Tuner Heart with Manual Over-ride is an ideal basis for a quality AM car radio. Size 6 1/2" x 4" x 2".

As illustrated but without knobs.

25/- plus 3/- P. & P.

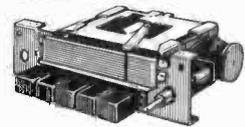


### QUALITY MAINS TRANSFORMER

Input 250 volts. OUTPUT (All RMS values) 4 windings of 11.5 volts connected in series total 46 volts at 4.5 amps (conservatively rated). The following combinations may be used. 1.23-0-23 volts. 2.46 volts.

Both of these above voltages are commonly used in medium to high powered transistor amplifiers, power supplies, etc.

Price 35/- plus 7/6 P. & P.

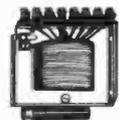

Goods not despatched outside UK

## RADIO & T.V. COMPONENTS (ACTON) LTD.

21c High Street, Acton, London W.3.

Also at 323 Edgware Road, London, W.2.

ALL ORDERS BY POST TO OUR ACTON ADDRESS

RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED

# HENRY'S RADIO LTD.

ELECTRONIC COMPONENTS AND EQUIPMENT  
303 EDGWARE ROAD, LONDON W.2. 01-723 1008 9.  
Open Monday to Saturday 9am to 6pm (Thurs 1pm)  
Open all day Saturday.



## ★ EXPERIMENTERS MODULE

Brand new STC time delay electronic units. Relay output. Adjustable 3-15 secs. 9-12V operated. Supplied complete with uses and circuits. STC Module Price 35/-, or 3 for 90/-



## ★ MULTIMETER

Return of a popular model. 2,000 ohms/V 0/10/50/500/1,000V a.c./d.c. 0/50μA. 0/10/250mA d.c. 0/10/100kΩ/1MΩ resistance. dB and capacitance scales. Size 5in. x 3½in. x 1½in. Robust and easy to use. Complete with leads, batteries and instructions. THL33a. Price 82/6, p.p. 2/6. Leather case. Price 22/6



## GRID DIP METER

All transistor grid dip meter, absorption and osc. detector. Frequency range 440 kc/s to 280Mc/s in 6 coils. Uses 3 transistors plus diode with 500μA meter. Internal battery. TE15 Price £11.10.0. p.p. 3/6.



## ★ RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-500Mc/s on 6 bands. Directly calibrated. Variable RF attenuator, audio output. Xtal socket for calibration. 220/240V. a.c. Brand new with instructions. Size 140 x 215 x 170mm. TE20D Price £15 p.p. 7/6




## ★ MULTIMETER 20Ω/V

Popular model but with extra scale range 20,000 ohms per volt. 0/5/25/50/250/500/2,500V d.c. 0/10/50/100/500/1,000V a.c. 0/50μA, 0/2/250mA. Resistance 0-6KΩ and 6MΩ. Also dB scales and capacitance. 200M. Price 77/6 p.p. 2/-.  
Leather case, Price 15/-


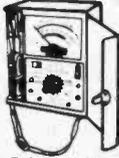
## ★ 50,000 OHMS PER VOLT MULTIMETER

Recommended quality instrument with mirror scale and overload protection. 0/0.3/3/12/60/120/300/600/1,200V d.c. 50kΩ/V; 0/6/30/120/300/600/1,200V a.c. 10kΩ/V; 0/30μA/6/60/300mA. 0/12A; resistance 0/10kΩ/10/100MΩ. Meter movement 20μA. Polarity reversing switch. Complete with batteries, leads and instructions. AF105, Price £8.10.0. p.p. 2/6. Leather case 28/6



**FREE** 16 PAGE BROCHURE COVERING LOW COST TEST EQUIPMENT FULLY DETAILED AND ILLUSTRATED. OVER 50 UNITS DETAILED ASK FOR PUBLICATION 'T' - REMEMBER IT'S FREE!

## ★ SINE/SQUARE WAVE AUDIO GENERATOR

Provides audio output on 4 bands. Sine wave 20c/s to 200kc/s, output up to 7V; square wave 60c/s to 30kc/s, 7V p-p Distortion under 2%. Output impedance 1kΩ. Variable output amplitude control Supplied with leads and instructions. A.C. mains operated. TE22. Price £16.10.0. Carriage, etc. Also TE22D (matching TE20D) Price £17. p.p. 10/-.



## ★ LOW COST VACUUM TUBE VALVE VOLTMETER

New model Multi-Range and easy to use: d.c. and a.c. Volts 0/1/4/5/15/50/150/500/1,500, a.c. p-p 0/4/2/14/42/140/420/1,400/4,200. Resistance 0.2 ohm to 1,000 Megohm—ranges. dBm scales -20 to +25dBm. Input impedance: d.c. 11 Meg. a.c. ±5 Meg. Response: ±1dB 20c/s to 5Mc/s. Complete with probe and handbook. (Size 10½in. x 5½in. x 4½in.) VT650 Price £17. p.p. 7/6



New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mc/s. Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered fronts. All local and continental stations. Complete detailed instructions. Total cost £6.19.6. p.p. 4/6. Ask for Leaflet No. 1.

## BUILD YOURSELF A QUALITY RADIO



## SCOOP! STAAR RECORD PLAYER

Deck plays 33, 45, 78, r.p.m. records, 9V operated, with mono cartridge. BRAND NEW... as illustrated. Price 59/6 p.p. 3/6. Send for leaflet No.2



Head-phones Quality stereo phones DHO2S only 45/- p.p. 3/-




## MULLARD 1 WATT AMPLIFIER

Portable Transistor Unit—Ideal for Intercoms, Baby Alarms, Telephone, Record Players or Guitar Practice. 9V 5 transistors with volume control, output 3 ohms. Ideal for use with Staar Record Deck. Price 45/-, p.p. 2/6
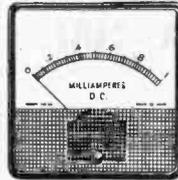
## ★ QUALITY PANEL METERS (D.C. RANGES)

38 Series. Face size 42mm x 42mm (1½in. x 1½in.). 50μA, 37/6; 100μA, 35/-; 200μA, 32/6; 500μA, 27/6; 1mA, 5mA, 10mA, 50mA, 100mA, 500mA, 25/- each; 10V, 20V, 50V, 100V, 300V, and 500V; 25/- each; 1A and 5A, 25/- each. "S" meter, 1mA, 29/6 VU meter, 37/6. 65 Series. Face size 86mm x 78mm (3½in. x 3¼in.). 50μA, 62/6; 100μA 52/6; 200μA, 47/6; 500μA, 45/-; 1mA 5mA, 10mA, 500mA, 37/6 each. "S" meter, 1mA, 42/6. Other ranges and sizes in stock. Ask for list. ref. No. 33



## ★ 10 in 1 TEST UNIT

A new design tests most circuits. Model SE400. Price £9.10.0.

\*A.c./d.c. Volts (4K/Volts) 0/15/50/150/500.  
\*Resistance 0/10K/100K/1 Meg.  
\*Five values resistance and capacitance substitution.  
\*RF F/S Meter 1 to 140Mc/s.  
\*455/700Kc/s RF Generator.  
Size 7½in. x 3½in. x 1½in.  
\*D.c. Ammeter 0/500mA.  
\*400c/s Audio Generator.



**COMPONENTS** UK'S LARGEST STOCKISTS ASK FOR QUOTES—SEE LATEST CATALOGUE 356 pages Price 7/6 p.p. 2/-

**HENRY'S FAMOUS CATALOGUES—SEE BACK COVER FOR DETAILS**

## GARRARD TURNTABLES

GOLDRING - BSR - GARRARD ALWAYS EXTRA BARGAINS FOR CALLERS AT OUR 309 EDGWARE RD. STORE

Credit Sale (Callers Only) For purchases from the 309 Store from £30



3000 LM	9TAHC DIAM	£9 15 0
3500	Ceramic Stereo	£8 10 0
Decadecc Deram		£12 19 6
		£18 10 0

## ★ NOTE THESE SPECIAL PRICES WITH DIAMOND STYLUS CARTRIDGES ★

Cartridge Model	Less Cartridge	9TAHC Diam.		AT21 or M3DM		AT66 AT21X*		AT33 Deram*		G800	J2203 800SE*		CS91E Ceramic							
		£	s	d	£	s	d	£	s		d	£	s	d	£	s	d			
SP25 Mk II	11	9	6	13	12	0	0	10	15	0	0	21	0	0	19	0	0			
AP75	17	15	0	19	15	0	0	25	10	0	0	27	0	0	25	10	0			
GL75P	46	0	0	—	—	—	—	53	10	0	0	55	10	0	70	0	0			
GL69P	35	0	0	37	0	0	0	42	10	0	0	44	10	0	59	0	0			
MA70	12	10	0	14	10	0	0	20	0	0	0	—	—	16	10	0	20	0		
AT60 Mk II	13	10	0	15	15	0	0	21	7	6	19	0	0	17	12	6	21	10	0	
GL75	33	0	0	35	0	0	0	40	10	0	0	42	10	0	40	0	0	40	10	0
SL72B	25	0	0	27	0	0	0	32	10	0	0	34	0	0	29	0	0	32	10	0
SL75B	31	0	0	33	0	0	0	33	10	0	0	40	10	0	35	0	0	38	10	0
SL95B	39	0	0	41	0	0	0	46	10	0	0	48	10	0	43	0	0	46	10	0
SL65B	15	19	6	18	0	0	0	23	10	0	0	20	10	0	19	15	0	23	10	0
GL69	23	0	0	25	0	0	0	30	10	0	0	32	10	0	47	0	0	30	10	0

Plinth/covers Model 50, 2025, 3000, 3500, SP25 99/6 p.p. 6/- (Note GL69P and GL75P complete with plinth/covers). 2025, 3000, 3500, SP25, SL65B, SL72B, SL75B, SL95B Deluxe type-(state model) £8.10.0. p.p. 7/6.

Complete range in stock. 100 watt Discoamp/Preamp £85, 35 watt £35, 70 watt £50. Also separate 70 watt power amplifier £35, preamplifier £22. All with 4 Inputs—full mixing etc.

DISCOTHEQUE AND PUBLIC ADDRESS EQUIPMENT

# BRAND NEW FULLY GUARANTEED TRANSISTORS & DEVICES

1N4001 2/-	2N2991 3/-	1M1 1/6	CRS1730 8/-	OA9 3/-
1N4002 2/3	2N4292 3/-	BA110 5/-	CRS135 8/6	OA10 4/-
1N4003 2/6	40361 12/-	BAY31 2/-	CRS140 9/6	OA47 2/-
1N4004 3/-	40362 13/6	BC107 3/-	CRS305 6/-	OA70 2/-
1N4005 3/6	25001 10/-	BC108 3/-	CRS310 6/-	OA71 2/-
1N4006 4/-	25002 10/6	BC109 3/-	CRS320 7/6	OA73 2/-
1N4007 5/-	25003 9/6	BC113 6/-	CRS330 8/6	OA74 2/-
1N4009 1/6	25004 9/6	BC116 6/-	CRS340 10/-	OA79 2/-
1N4148 1/9	25005 15/-	BC118 7/6	CRS400/40 39/6	OA81 2/-
1N4785 10/-	25012 25/-	BC134 7/6	CRS5025AF 4/-	OA85 2/6
2G211 12/6	25017 22/6	BC135 6/-		OA86 4/-
2G240 49/6	25013 20/-	BC136 7/-	CRS25025 15/-	OA90 2/6
2G301 4/-	25013A 25/-	BC137 8/-	DD008 3/9	OA91 1/6
2G303 4/6	25017 15/-	BC138 8/-	DD058 4/-	OA95 1/6
2G303 4/6	25018 17/6	BCY30 5/6	DD190 12/6	OA200 1/9
2G306 7/6	25020 50/-	BCY31 8/6	DD26A 7/6	OA202 2/6
2G308 7/6	25024 50/-	BCY32 10/6	DD262A 3/9	OA210 6/-
2G309 4/-	25021 60/-	BCY33 5/-	DK110 1/6	OA211 9/6
2G339A 3/-	25026 100/-	BCY34 6/-	DT3250 7/6	OA2200 11/-
2G371 4/6	2G374 5/6	BCY36 7/-	FST171 3/-	OA2201 10/-
2G374 5/6	25036 25/-	BCY39 8/6	FST20 3/6	OA2202 8/6
2G381 5/-	25102 10/-	BCY40 10/-	FST21 3/-	OA2203 8/6
2G383 6/-	25103 12/6	BCY42 5/-	FST30 3/-	OA2204 8/6
2G382A 4/6	25104 12/6	BCY43 5/-	FST31 4/-	OA2205 8/6
2G383 5/-	25131 7/6	BCY70 4/-	FST38 6/-	OA2206 8/6
2G394 4/6	25132 6/-	BCZ11 7/6	FST305 AF 3/-	OA2207 8/6
2G395 5/-	25102 7/6	BC147 3/9	GET102 4/6	OA2208 6/6
2N404 4/6	25303 10/-	BC148 2/9	GET103 4/6	OA2209 6/6
2N456 15/-	25304 12/6	BC149 4/-	GET104 4/6	OA2210 6/6
2N458 20/-	25305 15/-	BF152 6/-	GET106 10/-	OA2211 6/6
2N503 9/6	25320 9/-	BF182 6/6	GET110 5/-	OA2212 6/6
2N509 12/6	25321 6/-	BF184 3/6	GET113 3/-	OA2213 6/6
2N601 3/6	25322 7/6	BF195 3/-	GET114 4/-	OA2214 6/6
2N606 4/6	25323 10/-	BTY79/100R 15/-	GET115 9/-	OA2215 6/6
2N697 5/-	25324 12/6		GET120 5/-	OA2219 9/6
2N698 8/6	25501 8/6	BT102/500R 15/-	GET122 5/-	OA2220 9/6
2N706 1/6	25502 8/6		GET127 4/6	OA2238 9/6
2N706A 2/6	25503 9/6	BD119 12/6	GET128 6/-	OA2241 4/6
2N707 12/6	25513 9/6	RD124 12/6	GET182 4/6	OA2242 4/6
2N708 3/-	25701 8/6	BEN3000 5/-	GET183 5/-	OA2244 7/6
2N710 7/6	25702 11/6	BF15 5/-	GET185 5/-	OA2245 7/6
2N711A 7/6	25704 8/6	RF154 8/-	GET189 6/-	OA2248 7/6
2N721 11/-	25731 8/6	BF158 6/-	GET189 6/-	OA2244 7/6
2N743 4/6	25732 8/6	RF159 12/-	GET189 6/-	OA2242 4/6
2N747 4/6	25733 9/6	RF163 8/-	GET189 6/-	OA2244 4/6
2N753 5/-	25743 50/-	BF167 5/-	GET189 6/-	OA2245 4/6
2N865 12/6	25745A 30/-	BF173 4/-	GET189 6/-	OA2246 4/6
2N914 4/6	AA129 2/6	BF180 7/6	GET189 6/-	OA2247 4/6
2N916 4/6	AA178 8/6	BF181 7/6	JK10A 15/-	OA2272 4/6
2N918 7/6	AA171 2/-	BF300 6/-	JK10B 12/6	OA2290 7/6
2N919 5/-	AA172 6/-	BF308 8/6	JK11B 9/6	OA2291 7/6
2N920 5/-	AA173 6/-	BF317 6/-	JK20A 15/-	OA2292 7/6
2N922 8/6	AAZ13 2/6	BFY18 5/-	JK60A 19/6	OC16 10/-
2N930 7/6	AAZ17 2/-	BFY19 5/-	JK600B 15/-	OC19 7/6
2N1090 6/-	AC126 5/-	BFY20 12/6	MAT100 5/-	OC20 19/6
2N1091 6/6	AC127 5/6	RFY50 5/-	MAT101 4/6	OC22 9/6
2N1131 6/-	AC128 5/6	BFY41 4/6	MAT120 5/-	OC23 12/6
2N1132 6/-	AC128 5/6	BFY52 5/-	MAT121 6/-	OC24 12/6
2N9929 4/6	AC153 4/6	BFY53 4/6	NKT124 5/-	OC25 7/6
2N1303 6/-	AC164 4/6	BFY64 8/6	NKT125 4/6	OC26 5/-
2N1304 5/-	AC169 3/-	BL10 20/-	NKT128 6/-	OC28 12/6
2N1305 5/-	AC176 5/6	BL11 22/6	NKT142 8/-	OC29 12/6
2N1306 5/-	AC177 5/6	BFY10 19/6	NKT142 8/-	OC35 10/6
2N1307 5/-	AC188 6/-	BSX20 4/-	NKT212 4/-	OC36 12/6
2N1308 6/-	AC177 5/6	BSX21 5/-	NKT213 5/-	OC41 5/-
2N1309 5/-	AC178 5/6	BSX26 4/-	NKT214 4/-	OC42 5/-
2N1420 18/6	AC19 5/-	BSY27 4/-	NKT216 5/-	OC43 8/-
2N1483 9/6	ACY20 4/-	BSY28 5/-	NKT217 8/-	OC44 4/-
2N1613 7/6	ACY21 4/-	BSY29 5/-	NKT218 5/-	OC45 4/-
2N1617 17/6	ACY22 3/6	BSY30 5/-	NKT221 5/6	OC45 3/6
2N2160 15/6	ACY28 3/6	BSY31 5/-	NKT222 4/6	OC45M 3/6
2N2180 15/6	ACY34 3/6	BSY33 5/-	NKT223 4/6	OC46 5/6
2N2287 25/-	ACY36 5/-	BSY44 5/-	NKT224 4/6	OC57 12/-
2N2297 9/6	ACY39 9/6	BSY65 5/-	NKT225 3/6	OC58 12/6
2N2484 4/6	AD140 10/6	BSY66 5/-	NKT226 4/6	OC59 13/6
2N2646 10/6	AD140 10/6	BSY67 5/-	NKT227 5/6	OC70 3/6
2N2784 10/-	AD149 12/6	BSY95A 4/6	NKT228 6/-	OC71 3/6
2N2904 2/6	AD161 6/6	BSY95 3/6	NKT228 6/-	OC72 5/6
2N2905 10/-	AD162 7/6	BTY42 18/6	NKT261 5/-	OC73 6/-
2N2925 4/-	ADT140 10/6	BTY79/400R 35/-	NKT265 9/6	OC74 6/-
2N2926 3/6	ADT140 10/6		NKT271 5/-	OC75 5/-
2N3011 7/6	AD121 29/6	BTY84 12/6	NKT272 5/-	OC76 5/-
2N3053 5/-	AEY11 20/6	BTY88 15/-	NKT273 4/-	OC77 8/6
2N3054 12/6	AEY12 20/6	HUY10 12/6	NKT274 5/-	OC78 5/-
2N3055 15/-	AF102 15/-	HUY11 18/6	NKT275 5/-	OC78D 2/6
2N3133 6/-	AF114 6/6	BY100 3/6	NKT277 5/-	OC79 4/6
2N3136 6/-	AF115 6/6	BY103 4/6	NKT278 5/-	OC81 5/-
2N3142 7/6	AF116 6/6	BY114 5/-	NKT279A 4/-	OC81D 4/-
2N3232 15/6	AF117 5/-	BY126 5/-	NKT301 4/-	OC81M 4/-
2N3233 15/6	AF118 12/6	BYX2400 9/3	NKT302 4/-	OC81M 4/-
2N3235 30/-	AF124 6/-	BYZ10 10/-	NKT352 8/6	OC81Z 7/6
2N3228 10/6	AF125 5/-	BYZ11 9/6	NKT403 15/6	OC82 8/6
2N3238 9/6	AF126 6/-	BYZ12 8/6	NKT404 9/6	OC82D 5/6
2N3702 3/6	AF127 6/-	BYZ13 5/-	NKT449 8/6	OC83 5/-
2N3703 3/6	AF139 4/-	BYZ15 20/-	NKT451 8/6	OC84 5/-
2N3704 4/-	AF178 8/6	BYZ16 12/6	NKT452 7/6	OC122 10/6
2N3705 3/6	AF181 8/6	BZY88C3V3 4/-	NKT453 6/-	OC123 10/6
2N3707 4/-	AF186 9/6	BZY88C4V7 4/-	NKT454 6/-	OC139 5/-
2N3709 3/6	AF239 5/-	BZY88C5V6 4/-	NKT455 6/-	OC140 7/6
2N3710 3/-	AFY19 22/6	BZY88C5V1 4/-	NKT457 5/-	OC141 15/6
2N4291 3/6	AFZ11 8/-	BZY88C6R4 4/-	NKT458 5/-	OC169 5/-
2N3135 6/-	AFZ12 10/6	BZY88C7V5 4/-	NKT459 5/-	OC170 5/-
2N3794 2/6	ASY26 5/6	BZY88C8V2 4/-	NKT473 6/-	OC171 6/-
2N4292 3/6	ASY27 7/6	BZY88C9V1 4/-	NKT477 8/-	OC200 5/-
2N3711 3/6	ASY28 6/6	BZY88C9V 4/-	NKT12329 7/6	OC201 9/6
2N3710 10/-	ASY29 6/-	BZY88C9V2 4/-	NKT12429 9/6	OC202 12/6
2N3731 12/6	ASY36 5/-	BZY94C10 4/-	NKT13329 4/6	OC203 7/6
2N3810 8/-	ASY50 3/6	BZY94C11 4/-	NKT20329 11/6	OC204 8/6
2N3820 19/6	ASY51 8/-	BZY94C12 4/-	NKT35219 10/6	OC205 12/6
2N3823 17/6	ASY67 9/6	BZY94C15 4/-	NKT35219 10/6	OC206 15/6
2N4058 5/6	ASY73 15/-	BZY94C16 4/-	MPF103 7/6	OC207 9/6
2N4061 4/-	ASY86 6/6	CP404 12/6	MPF104 7/6	OCPT1 19/6
2N4286 3/-	ASZ21 8/6	CRS105 5/-	MPF105 3/6	ORP12 9/6
2N4288 3/-	ASZ23 20/-	CRS110 3/-	OA7 4/-	ORP60 8/-
2N4289 3/6	AUY10 19/6	CRS120 7/6		
2N4290 3/-	AU101 30/-			

Send for Free Copy of 1970 Transistor List (36) of a 1,000 Types Today!

**INTEGRATED CIRCUITS**

BP1010 25/-	PA424 59/6
CA3014 29/6	PA246 52/6
CA3018 22/6	MC1304 55/-
CA3020 29/6	TAD100 45/-
CA3028A 23/6	TA263 15/-
CA3036 18/6	SL403 49/6
IC10 99/6	UL900 10/-
PA230 23/6	UL910 10/-
PA234 20/-	UL914 12/6
PA237 37/6	

**DISCOUNTS**  
10% on 12+ and 15% on 25+ any one type

**QUANTITY PRICES 100 +**  
Phone 01-723-0401 Ex. 4.

Post/Packing add 2/6 on your order.

# TECHNICAL TRAINING

## in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

# NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

## POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
EST. 1891

Dept. 171, Intertext House, Stewart's Road, London, S.W.8.

Please send me the ICS prospectus—free and without obligation. (state Subject or Exam).....

.....

NAME .....

ADDRESS.....

6/70

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

# R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

★ Super 30 Amplifier (30 watt) in veneered housing  
 ★ Goldring Transcription Turntable on Plinth  
 ★ Shure or Goldring Magnetic Pick-up Cartridge  
 ★ Pair of Stanway II Loudspeaker Units  
 Special total price Four fully wired units ready to "plug-in". Carr. 30/-

TA12 Amplifier (13 watt) in veneered housing. Garrard 3000 4sp. Autochanger unit on plinth. Sonotone 9TA P.U. cartridge. Pair of Dorchester Loudspeaker units  
 Special Total Price **47½ Gns.** Carr. 25/-

Matching as recommended for optimum performance. Send for coloured brochure showing other money-saving offers.

★ Super 30 amplifier (15 + 15 watt) in veneered housing  
 ★ Garrard SP25 Mk II Turntable on Plinth  
 ★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus  
 ★ Pair Stanway II Speaker Units  
 Four fully wired units ready to "plug-in". Special total price **76 Gns.** Carr. 30/-



EXTREMELY ATTRACTIVE PLINTHS finished in Teak or Afrormosia veneer. Trans plastic cover.

● TA12 Amplifier (13 watt) in veneered housing  
 ● Garrard SP25 Mk II 4 sp. player unit on plinth  
 ● Goldring CS90 Ceramic P.U. Cartridge  
 ● Pair of Dorchester Loudspeaker Units. **53 gns.**  
 Special total price Carr. 25/-  
 Or Dep. £10.0.3 and 9 monthly payments £5.15.5 (Total £59 gns.). Transparent plastic cover 3 gns. extra.  
**TERMS AVAILABLE ALL PACKAGE OFFERS**

## AUDIOTRINE HIGH FIDELITY LOUSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. "L" indicates Roll Rubber cone surround. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost.

HF501L	5"	10W	49/9	HF120	12"	15W	79/9
HF801D	8"	3W	54/3	HF120D	12"	15W	89/9
HF102D	10"	10W	67/11	HF126	12"	15W	£5.5.0
HF100D	10"	15W	£4.19.9	HF126D	12"	15W	£5.15.0
HF105DL	10"	10W	6 gns.				

## HIGH FIDELITY LOUSPEAKER UNITS

Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or fitted acoustic damping. Ported where appropriate, credit terms available.



**DORCHESTER** Size 16 x 11 x 9 in. approx. Range 45-15,000 c.p.s. Batting 8-10 watts. Fitted High flux 13x8 in. Dual Cone speaker. Imp. 3 or 15 ohms. **£8.19.9** Carr. 7/6

**STANWAY II** Size 20x10x9 1/2 in. approx. Rating 10 watts. Inc. Fane 13x8 in. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.**

## R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER



200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s.

Separate Bass and Treble controls. 3 input sockets for Mike, Gram and ceramic. Radio or Tape. Input selector switch. Output for 3-15 ohm speakers. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 3 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **7 Gns.** Carr. 7/6  
 Or factory built with 12 months' guarantee. £8.19.9

## RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amplifier or Tape recorder.

**RP2C** Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Carr. 9/6 **23 Gns.**

**RP5C** Garrard 2025 Auto Unit fitted Garrard GCS 23 Stereo Cartridge with diamond tip, Plinth & Cover as RP2C **15 Gns.**

Other types available with Magnetic cartridges and with alternative design plinths.

Limited Number of CLEARANCE LINES in leading makes of Hi-Fi equipment at Branches only

## R.S.C. PLINTHS



for Record Playing units cut for Garrard 1025, 2025, 3000, AT60, SP25 etc. **3 gns.**

Available with trans. plastic cover. Carr. free **6 gns.**

**INTEREST CHARGES REFUNDED**  
 On Credit Sales settled in 3 months.

## LINEAR L10 HIGH FIDELITY LOW AMPLIFIER 10 Gns.

with separate Pre-amp Magnetic P.U. matching. To clear

## R.S.C. TA12 MKII 13 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV. Output rating I.H.F.M. ★ Handsome brushed silver finish Facia and Knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 months guarantee 17 Gns or Deposit £5.2.8 and 9 monthly payments 34/- (Total £20.8.6). Or in Teak or Afrormosia veneer housing 20 1/2 Gns. Dep. £5.10.8 and 9 monthly payments £21.7 (Total £24.4.9).



## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Or Senior 15 Watt inc. HF126 15,000 line Speaker £6.15.0. Carr. 6/6 **£5.15.0** Carr. 5/9

## HI-FI SPEAKER ENCLOSURE

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 5/- per enclosure  
**JES** Size 16 x 11 x 9 in. Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. **£4.15.0**  
**SEB** For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9 in. Ported enclosure. Gives pleasing results with any 8in. Hi-Fi speaker. **£5.15.0**  
**SE10** For outstanding results SE13 For excellent performance with 12in. Hi-Fi speaker and Tweeter. **£6.19.9**  
 Size 24x15x10in. Sp'dr. **£5.19.6** Size 25 x 16 x 10 1/2 in.

## THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25x14x10in. COMPLETE KIT **20 Gns**  
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms Carr. 12/6  
 ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £5.10.8 and 9 monthly payments 39/- (Total £23.1.0).  
**DEMONSTRATIONS AT ALL BRANCHES**



## R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

★ High-sensitivity. 200-250v. A.C. Mains operation. ★ Sharp A.M. Reception ★ Drift-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed for standard 80 ohm coaxial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. Printed circuitry. A quality product at considerably less than the cost of comparable units. Factory built 18 gns. Or in Teak finished cabinet as illustrated 21 gns. Terms: Deposit £6.1.0 and 9 monthly payments. 2 gns. Total £24.19.0. Stereo version, 23 1/2 gns. Carr. 10/6 extra



# R.S.C. SUPER 30 MKII HIGH FIDELITY STEREO AMPLIFIER

High Grade Components Specifications comparable with units costing considerably more.

**TRANSISTORS** 9 high quality types in each channel.  
**OUTPUT** 10 Watts R.M.S. continuous into 15Ω (per channel). 15 Watts R.M.S. continuous into 2Ω.  
**INPUT SENSITIVITIES** Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5 mV.  
**FREQUENCY RESPONSE** ± 2 dB. 10-20,000 c.p.s.  
**TREBLE CONTROL** +17 dB to -14 dB at 10 Kc/s.  
**BASS CONTROL** +17 dB to -15 dB at 50 c/s.  
**HUM LEVEL** -80 dB.  
**HARMONIC DISTORTION** 0.1% at 10 watts 1,000 c.p.s.



Employing Twin Printed Circuits. 200/250v. A.C. mains operation. **CROSS TALK** 62 dB at 1,000 c.p.s.  
**CONTROLS** 5 Position Input Selector. Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.  
**INPUT SOCKETS** (1) P.U. (2) Tape Amp. (3) Radio. (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).  
**CHASSIS** Strong Steel construction. Approx. 12 x 3 x 8 in.

**FACIA PLATE** Attractive design in rigid plastic silver background black lettering. Silver finish matching control knobs as available.  
 Eminently suitable for use with any make of pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first rate ancillary equipment.

**COMPLETE KIT OF PARTS** Point to point wiring diagrams 22 gns. and detailed instructions. Carr. 15/-  
**UNIT FACTORY BUILT** 29 gns. With 12 months guarantee.  
 Or Deposit £7.5.0 and 9 monthly payments 58/9 (Total £23.13.9) or in Teak or Afrormosia veneer housing 82 Gns. Carr. 15/- Terms: Deposit £7.3.8 and 9 monthly payments of 66/6 (Total £37.2.0). Send S.A.E. for leaflet.

## R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1 An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram 62/6 or assembled 3 gns.

## SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER

Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. **12 1/2 Gns.** Carr. 12/6  
**OR FACTORY BUILT** 16 1/2 Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.9) or in Teak or Afrormosia veneered housing. 19 gns.

## PARTRIDGE "JOYSTICK" SHORT WAVE AERIALS AND TUNERS AT ALL BRANCHES (S.A.E. for full list)

- BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL** (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM** 30/31 Gt. Western Arcade 021-236-1279 (Half-day Wed.)
- DERBY** 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. City 4158
- HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: 102 Henconner Lane, Bramley, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £5. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries. Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS

- 32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) **LEEDS** Tel. 28252
- 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 **LIVERPOOL**
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. **LONDON** PAD 1629
- 60A Oldham Street (Half-day Wed.) **MANCHESTER** Tel. CENTRAL 2778
- 106 Newport Rd. (Half-day Wed.) **MIDDLESBROUGH** Tel. 47096
- 41 Blakett Street (Opp Fenwick's Store) **NEWCASTLE UPON TYNE** Tel. 21469
- 13 Exchange Street (Castle Market Bldgs.) **SHEFFIELD** (Half-day Thursday) Tel. 20716

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive. Push-Pull high output, with Pre-amp. Tone Control Stages. Performance figures of factory built units: Hum level -70dB. Frequency response  $\pm$  3dB 30-20,000c/s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 607, 607, GZ34. Resonant Bass and Treble Controls. Sensitivity 36mV. Suitable for high impedance microphones. Crystal or Ceramic P.U.'s. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor

Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 60w A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. **15 Gns.** Carr. 12/6. Twin-handled perforated cover £7/6. Supplied factory built with EL34 output valves. 12 months' guarantee for 18 gns. TERMS: Deposit £8.8.0 and 9 monthly payments of 34/- (Total £21.9.0). Send S.A.E. for leaflet.

## R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER



PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with mixing facilities High sensitivity, 5 valves. Independent Bass and treble controls. Frequency response  $\pm$  3dB 30-20,000 c/s. Hum level -80dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes".

For Musical Instruments etc. Std. A.C. mains. For 3 & 15 ohm spkrs. **91 Gns.** SAE for leaflet. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 11/6. Twin handled metal cover £7/6. Price factory built 134 gns. or Deposit 99/8 and 9 monthly payments of 28/- (Total £16.13.6). RSC A11 TRANSISTORISED VERSION of above complete kit 9 Gns. (Assembled 13 Gns.)

## 30 WATT HI-FI AMPLIFIER

FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP A 4 input, 2 volume control Hi-Fi unit with Separate Bass and Treble controls. B.V.A. valves. Peak output rating. Strong Resine covered cabinet with handles. Attractive black/gold face panel. Neon Indicator. For 200-250v. A.C. mains. For 3 or 15 ohm **19 Gns.** Carr. 12/6. Send S.A.E. for leaflet.



Dep. 5 gns. & 9 monthly payments of 39/8 (Total 22 gns.)

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 years' guarantee. High flux ceramic magnets. Heavy cast chassis. All prices carr. free

<b>'POP' 100</b> 18" 100 Watt 14,500 gauss 8/15Ω <b>21 GNS.</b>	<b>'POP' 60</b> 15" 60 Watt 14,000 gauss 8/15Ω <b>12 GNS.</b>	<b>'POP' 50</b> 12" 50 Watt 14,000 gauss 15Ω <b>10 GNS.</b>
---	---	---

## FANE LOUDSPEAKERS

**'POP' 30C**  
12" 25 Watt  
Dual cone 15Ω  
**£5-19.9**  
Carr. free

F.A.L. P.A. AMPLIFIERS PHASE 50 **29 GNS.**  
S.A.E. for leaflets.

PHASE 100 **59 GNS.**

## R.S.C. COLUMN SPEAKERS

Covered in two-tone Roxine/Vynair. ideal for vocalists and Public Address. 15 ohm matching.



**TYPE C485 25/30 WATTS.** Fitted for 8in. high flux 8 watt speakers. Overall size approx. 42 x 10 x 5in.

**16 Gns.** Carr. 10/-

Or deposit 67/- and 9 monthly payments 34/9 (Total £18.19.0).

**TYPE C4125 50 WATTS.** Fitted for 12in. 11,000 line 15 watt speakers. Overall size 56 x 14 x 9in. approx.

**26 Gns.** Carr. 12/6

Or Deposit £5.17.6 and 9 monthly payments of 54/6 (Total £30.7.0)

## HIGH QUALITY LOUDSPEAKERS

In Teak or Afrormosia veneered Cabinets

**L13 13" x 8" 8-10 Watt**  
10,000 lines 3 or 15 ohms. Carr. 7/6

**Type L12 12" 20 Watt**  
10,000 lines 15 ohms. Carr. 8/9

## R.S.C. BASS-REGENT 50 WATT AMPLIFIER



A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram. radio, tape. Peak Output rating.

Two extra heavy duty 12in. Loudspeakers. Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls.

**55 Gns.** Carr. 30/- or dep. £18.4.9 and 9 monthly payments of £5.11.9. (Total 604 gns.) Send S.A.E. for leaflet.

G100 100 watt peak output with Fr. speaker columns and a Bass Unit (Six 12" and Two 15" Speakers). 994 gns.

## SURPLUS EX GOVT. BARGAINS



**AMPLIFIER RF NO. 2 MK III.** Increases output of 19 set to 25 watts. Brand New. 12v operation. 76/-, Carr. 15/-

No. 19 set New £10.10.0 Carr. Paid. All Ancillary Equipment available. 12v D.C. Power Units 50/-, Carr. 10/-, 12/24v D.C. Power Units with Vibrator MK II No. 2. 70/-, Carr. 10/-.

H/MIC SETS. Used 15/-, New 22/6. P. & P. 5/-, Mainna P.S.U.'s for 19 TM/RC £8.15.0. Carr. 10/-, R.F. Antenna Tuner (ATU) 25/-, P. & P. 5/-.

**FEW ONLY!** No. 19 MK III CANADIAN TRANSCEIVERS. Rebuilt as new. Complete station with all connectors, head-set, variometer, control box and aerials. £22.10.0. Carr. 50/-

**B.41 RECEIVER.** LF Version of B.40. Coverage 15Kc/s-700Kc/s. Mains Operation. As received from Ministry. £8.10.0. Carr. 30/-, Tested, working £18, Carr. 30/-.



**B.209 MK II COMMUNICATION RECEIVERS.** 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW. BFO. 12. D.C. Internal Power Supply. Tested. £13.10.0. Carr. 15/-.

**HALLICRAFTER RH9 4 metre Receiver.** Ex TAL controlled double conversion £12.10.0. Carr. 20/-.

**TELESCOPIC MASTS.** 20ft. Closes to 5ft. 9in. 70/-, Carr. 15/-.

**35FT. AERIAL MASTS.** Seven 2 in. dia. sections. Interlock 8in. Complete with base. Nylon Guy. £12.10.0. Carr. 50/-.

**TELE 'P' FIELD TELEPHES.** Communications up to 10 miles. Tested with batteries. £5.15.0. pair, Carr. 20/-.

**RETIREMENT.** All stocks to be cleared. Many bargains for callers only. 9-5 Mon-Fri. 8-12 Sat.

**A.J. THOMPSON (Dept. P.W.)**

"Elting Lodge," Codicote, Hitchin, Herts. Phone: Codicote 342

## UNREPEATABLE PRE STOCKTAKING OFFER SAVE NEARLY 20%

LATEST NEW & IMPROVED "JULIETTE" NA5018A COMMUNICATIONS RECEIVER (with AFC and BFO) 5 BAND MAINS/BATTERY SOLID STATE PORTABLE RECEIVER



LIST PRICE £44.17.6  
**OUR PRICE 34 gns.** (cash only) + 9/- p/p Limited quantity

- AM Band: Full Medium wave cover
- Marine Band: Shipping, Ham, SW, etc.
- FM/VHF: Radios 2, 3, 4; TV Sound, Public Services, etc.
- Aircraft (improved sensitivity): Airlines and (ground Control) ● PS (High VHF Band): TV Sound, Fire, Ambulance, etc., Taxis, Shipping

Fuel Boards, Oil Rigs, Gas and Electric Boards, Local Hams, Industrial and Commercial Mobiles, etc. (DEPENDENT ON LOCALITY). FEATURES:— 4" Dynamic PM Speaker. Directional telescopic VHF aerial. Internac Ferrite rod aerial. Illuminated Dial. size 9 1/2" x 5 1/2" x 4". Weight 5 1/2 lbs. Impressive and sturdy design in Chrome and Black Leather. Ultra sensitive 18 transistor circuit. Earpiece and Socket. Leather carrying and shoulder straps. Batteries incl.

RETAIL TRADERS SUPPLIED Enquiries to wholesale dept. STOCKTON PARTNERS (DEPT. P.W.) BRIGHOWGATE, GRIMSBY, LINCOS. Tel: 0472 58815/64196 Imports, Wholesale Electronic Equipment Distributors

## LOOK AT THESE PRICES

**CARTRIDGES**  
Acos GP67-2, GP91-38C 22/6; Acos GP93-1 26/8; Acos GP94-1 22/6; Sontonec 9TAHC 39/6; All above in makers cartons; Japanese Stereo 16/-.

**1 WATT AMPLIFIER**  
Complete with volume control, rectifier, smoothing etc, fully transistorised, **OUR PRICE 27/6**

**PLUGS & SOCKETS**  
Phono plugs, red, white, yellow, green, grey, blue, black 11d 9/- per doz; Coaxial plugs, aluminium 1/6; Coaxial couplers 1/-; 2 pin DIN plugs 3/6; 3 pin DIN plugs 3/6; 5 pin DIN plugs 8/6; 2 pin, 3 pin DIN sockets 1/6; wandler Plugs 8d; sockets 8d; Banana plugs 1/1, sockets 1/-; 3.5mm J/Plugs 1/6 & 2/6; Standard J/Plugs with solder terminals 2/- & 3/-; Side Entry J/Plugs black and chrome 4/9; Insulated J/sockets, o/cct 3/3, c/cct 3/6.

**ELECTROLYTIC CAPACITORS**  
4uF, 150v 9d; 8uF 500v 3/-; 8uF 12v 10d; 8uF + 8uF 450v 4/3; 10uF 150v 9d; 12uF 25v 9d; 16uF 450v 2/9d; 16uF + 16uF 450v 4/3; 30uF 10v 9d; 50uF 10v 9d; 100uF 9v 9d; 100uF 12v 9d; 150uF 12v 9d; 320uF 9v 1/-; 1500uF 30v 3/9; 2000uF 30v 4/2; 5000uF 25v 10/-; 10,000uF 25v 15/-; 20,000uF 30v 21/-.

**MICROPHONES**  
Acos Mic 45 22/6; Acos Mic 60 19/11; Planet CM70 30/-; Hand Mike 15/-; Shure 201 25; Shure 444 £10.10.0.

**VALVES**  
PY81 7/2; PCL82 7/9; EF183 9/-; EF184 9/-.


**GEORGE FRANCIS (Dept PW),**  
93 Balderton Gate, Newark, Notts.  
Telephone: Newark 4783.

# RADIO CONSTRUCTOR

**FREE** CUT-OUT ART SUPPLEMENT  
of WORKSHOP PLANS

Full Working Diagrams including  
Printed Circuit Board Layout

**SOLID-STATE DISTORTION METER**

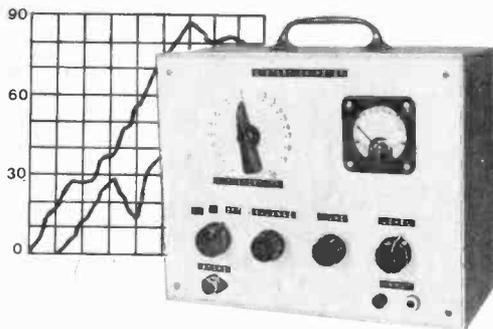

Copies may also be obtained direct from the  
Publishers—4/- including postage.  
Published by:

**DATA PUBLICATIONS LTD.,**  
57 MAIDA VALE, LONDON, W.9.

## MAY ISSUE

### ON SALE NOW 3/6

OTHER CONSTRUCTIONAL PROJECTS  
INCLUDE

- C.R.O. Beam Switching Unit
- Electronic Siren Module
- Neon-L.D.R. A.F. Oscillator


NEW SERIES  
"UNDERSTANDING TAPE RECORDING"

**PLUS**

★ **EXCLUSIVE MOTORING** ★  
**OFFER**

(Maserati Air Horns, etc.)

THE  
**RADIO CONSTRUCTOR**

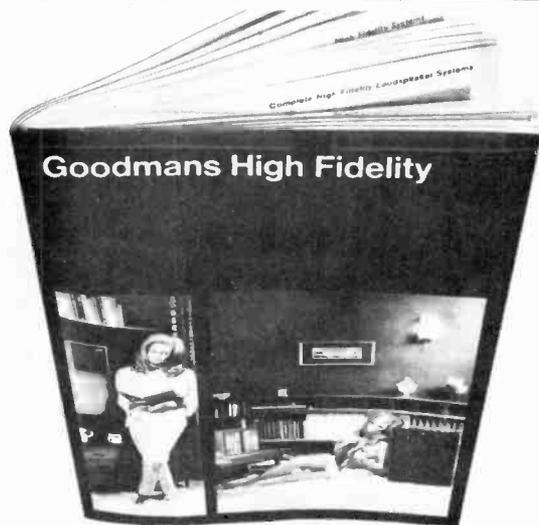

**Let us give you the facts**

From cover to cover Goodman's Manual is packed with fascinating  
articles on Stereo; a beginners guide to High Fidelity; Stage-built  
Systems: complete details of Goodman's High Fidelity Audio products.  
28 pages you can't afford to miss . . . and it's yours FREE!

**Please send me a free copy**

Name \_\_\_\_\_

Address \_\_\_\_\_

PW/670



**Goodmans Loudspeakers Limited**

Axiom Works, Wembley, Middlesex. Tel: 01-902 1200

## LINEAR

**RANGE OF SOLID STATE  
A.C. MAINS AMPLIFIERS**


Employing only

high grade components and transistors.

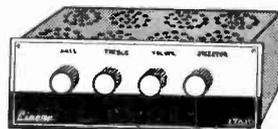**LTA 15 WATT AMPLIFIER**

**HIGH FIDELITY OUTPUT  
SWITCHED INPUTS FOR  
GRAM, 'MIKE', TAPE,  
AND RADIO**

Frequency Response 10-40,000  
cps-3dB. Bass Control+17dB  
-10-16dB at 40cps. Treble Control-  
17dB to-14dB at 14Kcs. Hum and  
Noise-80dB. Harmonic Distortion  
0.2% at rated output. Output for  
3-8-15 ohm Loudspeakers.



Recommended **£18. 10. 0.**  
Retail Price  
Size 9½ x 3½ x 5½ in. approx.

**PTA30 HI-FI  
PUBLIC ADDRESS  
AMPLIFIER**


**A SUCCESSOR TO OUR  
POPULAR CONCHORD  
30 WATT UNIT**

Input Sensitivity 2 mv (max.)

Output 30 watts.

Output Sockets for Loudspeaker or  
combination of Speakers with total  
impedance between 5 ohms and 30  
ohms. Three individually controlled  
Inputs for mixing purposes. Housed in fully enclosed stove enamelled  
steel case. Controls Vol. (1) Vol. (2) Vol. (3) with mains switch, Treble 'lift',  
and 'cut', Bass 'lift' and 'cut'.

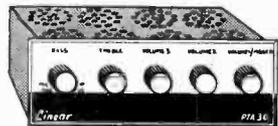**AN IDEAL UNIT FOR VOCAL AND INSTRUMENTAL GROUPS,  
SUITABLE FOR ANY KIND OF 'MIKE' AND INSTRUMENT  
PICK-UP, ALSO FOR RADIO, TAPE OR GRAM.**



Recommended **£23.**  
Retail Price  
Size 12 x 3½ x 6 in. approx.

If required an at-  
tractive wood cabi-  
net with veneer  
finish can be sup-  
plied for any  
model.  
Prices from **70s.**

Please send a stamped addressed envelope for full descriptive  
details of above units, also TUNER/AMPLIFIERS STEREO and  
MONO.

AVAILABLE FROM YOUR LOCAL HI-FI DEALER  
Wholesale and Retail enquiries to:

**LINEAR PRODUCTS LTD,**  
Electron Works, Armley, Leeds

# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

## NEW! roamer eight mkl WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total Building Costs

**£6.19.6**


Parts Price List and Easy Build Plans 5/- (FREE with parts).

P & P 7/6.


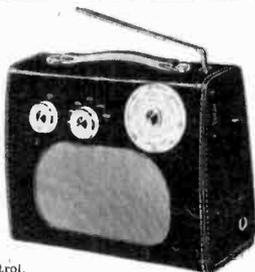
## roamer seven mklV

SEVEN FULLY TUNABLE WAVE-BANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Five Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.



Total building costs

**£5.19.6**

P. & P. 7/6

## NEW!

### trans eight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.



Total building costs

**89'6**

P & P 5/6

## pocket five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND PORTABLE  
WITH SPEAKER

Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

**44'6**

P. & P.  
3/6

## transona five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND PORTABLE  
WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 8½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

**47'6**

P. & P.  
3/9

## roamer six

SIX WAVEBAND PORTABLE  
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/-. (FREE with parts).



Total building costs

**79'6**

P. & P.  
4/6

\* Callers side entrance Stylo Shoe Shop

\* Open 10-1, 2.30-4.30 Mon-Fri. 9-12 Sat

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD, Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....

PW.18

### CAR LIGHT FLASHERS



Heavy duty light flasher employs a condenser discharge principle operating on electro mechanical relay. (As inset). Housed in strong plastic case. Flashing rate between 60-120 per minute. 12V DC operation. Maximum load 6 amps. Size 2-11/16in. dia. x 4in. Supplied brand new at a fraction of original cost. 6/6 each. P. P. 2/6. (3 for 17/6. P. P. 4/6).

### CLASS D WAVEMETERS




A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. £5.19.8. Carr. 7/6. Or brand new with accessories. £7.19.8. Carr. 7/6.

### CLASS D WAVEMETERS No. 2

Crystal controlled. 1.2-19 Me/s. Mains or 12V. D.C. operation. Complete with calibration chart. Excellent condition. £12.10.0. Carr. 30/-.
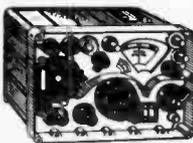
### R209 MK II COMMUNICATION RECEIVER

11 valve high grade communication receiver suitable for tropical use. 1.90 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O., aerial trimmer, internal speaker and 12V. D.C. internal power supply. Supplied in excellent condition. Fully tested and checked £15.0.0. Carr. 20/-.



### TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5.5 Mc/s. Sensitivity 33mV/cm. Operating voltage 0/110/200/250V. A.C. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe leads, etc. £25. Carrage 30/-.



### MARCONI T/44/TF956

AF Absorption Wattmeter

1 μ/watt to 6 watts. £20. Carr. 10/-.

### SOLARTRON CD 711S2

Double Beam Oscilloscopes

D.C. to 9 Mc/s. Perfect order 665. Carr. 50/-

(Few available less C.R.T.) £25 Carr. 50/-


### TO-3 PORTABLE OSCILLOSCOPE



3in. tube. Y amp. Sensitivity 0.1v p-p/cm. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0.5v p-p/cm. Bandwidth 1.5 cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHz.

Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 14 lb. 220/240V. A.C. Supplied brand new with handbook. £37.10.0. Carr. 10/-.
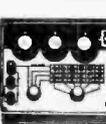
### TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE




A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1-111 meg Ω 6 Ranges ±1% L.1 μ H - 111 HENRYs 6 Ranges -2% C. 10pF ± 1110mFd. 6


Ranges ±2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2in. £20. P. & P. 5/-.
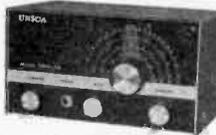
### UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kcs-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6. **13 gns.**



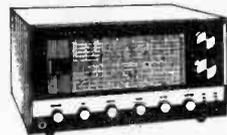TRIO JR.310 New Amateur Band 10-80 Metre Receiver in stock. £77.10.0.



### LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER

Six bands 3-5.4, 7-7.3, 14-14.85, 21-21.45, 29-29.7, 50-54Mc/s. Initial conversion on all six bands. 2 x 455 Kc/s mechanical filters. FET front end. Product detector, variable BFO. 100Kc/s crystal calibrator. 'B' Meter. Huge slide rule dial. Operation 230V AC or 12V DC. Size 15 x 9 1/2 x 8 1/2 in. Complete with instruction manual. £57.10.0 Carr. Paid. 100Kc/s crystal 39/6 extra.

### UR-1A SOLID STATE COMMUNICATION RECEIVER

4 bands covering 550 Kcs-30 mc/s continuous. Special features are use of FET transistors. 8 meter, built in speaker and telescopic aerial, variable BFO for SSB reception, noise limiter, bandspread control, sensitivity control. Output for low impedance headphones. Operation 220/240 volt A.C. or 12 volt D.C. Size 12 1/2 in. x 4 1/2 in. x 7 in. Excellent value. ONLY £24. Carr. 7/6.



### TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550 Kc/s to 30 Mc continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW ● ANL ● Variable BFO ● 8 meter ● Sep. bandspread dial ● IF 455 Kc/s ● Audio output 1.5 W. ● Variable RP and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. £42. carriage paid. TRIO COMMUNICATION TYPE HEADPHONES. Normally £5.19.6. OUR PRICE £3.15.0 if purchased with above receiver.

TRIO JR. 500SE 10-80 Metre Receiver £69.10.0



TRIO TS 510 AMATEUR TRANS-CEIVER with speaker and mains P.S.U. £180 IN STOCK!

### RCA COMMUNICATIONS RECEIVERS AR88D


Latest release by ministry BRAND NEW in original cases. 110-230V. A.C. operation. Frequency in 6 Bands. 635 Kc/s-32 Mc/s continuous. Output impedance 2.5-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price £65.0.0. Carr. £2.

### LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

A completely new transistorised receiver covering 162-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. £37.10.0. Carr. 10/-.


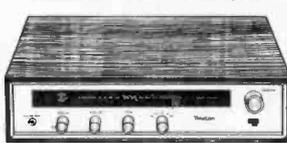
### TELETON CR-10T AM/FM STEREO TUNER AMPLIFIER



A new model from Teleton. 31 solid state devices. 4 + 4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600KHz FM 88-108MHz. Automatic FM Stereo reception. Stereo Indicator. Controls: Tuning, function selector, Tone and R & L volume controls. AFC switch. Stereo headphone socket. Size 13 1/2 x 3 1/2 x 9 1/2 approx. PRICE £34.0.0. Carr. 7/6.

### CLEAR PLASTIC PANEL METERS



First grade quality Moving Coil panel meters. Type MR 38P. 1 1/4 in. square fronts.

500-0-500μA	27/6	50mA	27/6	150V. D.C.	27/6
1mA	27/6	100mA	27/6	300V. D.C.	27/6
1-0-1mA	27/6	300mA	27/6	500V. D.C.	27/6
2mA	27/6	200mA	27/6	750V. D.C.	27/6
5mA	27/6	150mA	27/6	15V. A.C.	27/6
10mA	27/6	50mA	27/6	50V. A.C.	27/6
750mA	27/6	3V. D.C.	27/6	150V. A.C.	27/6
1 amp	27/6	10V. D.C.	27/6	300V. A.C.	27/6
100-0-100μA	35/-	20V. D.C.	27/6	500V. A.C.	27/6
200μA	35/-	5 amp	27/6	8 meter 1mA 22/-	
500μA	40/-	20mA	27/6	100V. D.C.	27/6
				VU meter	42/-

FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET

### Variable Voltage TRANSFORMERS

Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 50-60 cycles. Output fully variable from 0-230 volts. Bulk quantities available. 1 amp.-£5.10.0; 2.5 amp.-£6.15.0; 5 amp.-£8.15.0; 8 amp.-£14.10.0; 10 amp.-£18.10.0; 12 amp.-£21.0.0; 20 amp.-£37.0.0.



### CRYSTAL CALIBRATORS NO. 10



Small portable crystal controlled wavemeter. Size 7 x 7 1/2 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V. D.C. 0.3A.

Excellent condition. 89/8. Carr. 7/6.

### TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0.1/0.03-1/3/1/8/10/30/100/300V. R.N.S. 4cps-1.2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instruction manual. Operation 230V. A.C. £17.10.0. Carr. b/-.



### LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/250V. A.C. Supplied in perfect order. £12.10.0 Carr. 10/-.

### TE-65 VALVE VOLTMETER



High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance 200/240V. A.C. operation. Complete with probe and instructions. £17.10.0. P. & P. 6/-.

Additional probes available: R.F. 35/-, H.V. 42/6.

### COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.C. coupled. Band width 1Kc/s. Perfect order. £25. Carr. 30/-.




### AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airtec. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1μV-100V. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. 20/-.

EDDYSTONE VHF RECEIVERS Model 770R. 19-165 Mc/s. Excellent condition. £150.

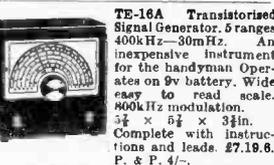PLESSEY 8L403A 3 watt Integrated Amplifier Circuit 49/6. Post paid.



TE-16A Transistorised Signal Generator: 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 8 1/2 x 3 1/2 in. Complete with instructions and leads. £27.19.8. P. & P. 4/-.

### HOSIDEN/DH-085 DE-LUXE STEREO HEADPHONES

Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead & stereo jack plug £17.19.6. P. & P. 2/6.



### AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded. 150 W. £2. 2/6. P. & P. 3/6. 300 W. £2.19.6. P. & P. 4/6. 500 W. £4.10.0. P. & P. 6/6. 1,000 W. £6.10.0. P. & P. 7/6. 1,800 W. £7.19.6. P. & P. 8/6. 7,500 W. £15.10.0. P. & P. 20/-.



G. W. SMITH & CO (RADIO) LTD. Also see oppo. page

### ARF-100 COMBINED AF-RD SIGNAL GENERATOR



**A.F. SINE WAVE**  
20 - 200,000 c/s.  
Square wave 20 - 30,000 c/s. 0.1V.  
**HIGH IMP.** 21V.  
P/P 600 Ω 3.8V. P/P  
TF 100 Kc/s-300  
Mc/s. Variable R.F.

attenuation Int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V. A.C. £32.10.0. Carr. 7/6.

### TE-20RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-260 Mc/s on 6 bands.



Directly calibrated Variable R.F. attenuator. Operation 200/240V. A.C. Brand new with instructions. £15.0.0. P. & P. 7/8, S.A.E. for details.

**PEAK-SOUND PRODUCTS.** Full range of Amplifiers, Kits, Speakers, in stock.

### TE22 SINE SQUARE WAVE AUDIO GENERATORS



Sine: 200c/s to 200 Kc/s on 4 bands. Square: 200c/s to 20Kc/s. Output impedance 5,000 ohms. 200/250V. A.C. Supplied brand new and accompanied with instruction manual and leads. £16.10.0. Carr. 7/6.

**MARCONI TP142E DISTORTION FACTOR METERS.** Excellent condition. Fully tested. £20. Carr. 15/-.

### LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mFd  
2 ohms 200 meg-ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New £17.10.0. Carr. 7/6.



### TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPB-1 MHz. Input imp. 2 meg Ω 25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 v a.c. Supplied brand new with handbook. £22.10.0. Carr. 10/-.



### ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons

**JTB AUDIO SIGNAL GENERATOR.** 15 c/s to 50 Kc/s. Sine wave. Output 600 ohms or 5 ohms £30.0.0.

**VM79. UHF MILLIVOLT METER.** 100 Kc/s to 1,000 Mc/s. A.C. 10mV to 3v. D.C. 10 mV to 3v. Current 0.01 uA to 0.3 mA. Resistance 1 ohm to 10 megohm. £125.0.0.

**TT18. TRANSISTOR TESTER.** Full range of facilities for testing PNP or NPN transistors in or out of circuit. £37.10.0. Carrage 10/- per item.

### HOSIDEN DHO45 2-WAY STEREO HEADSETS



Each headphone contains a 2in. woofer and a 1in. tweeter. Built in individual level controls. 8 Ω imp. 25-18,000c/s with cable and stereo plug. £5.19.6. P. & P. 2/6.

### AVOMETER MOVEMENTS



50μA 20K Ω/V  
Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multimeter. Brand New & Boxed. 69/6. P. & P. 3/6.

# Latest Catalogue

The latest edition giving full details of a comprehensive range of Hi FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. Over 230 pages, fully illustrated and detailing thousands of items - many at bargain prices. **FREE DISCOUNT COUPONS VALUE 10/-.**



SEND NOW - ONLY 7/6 P & P 1/-

Note: 4th Edition now printing - reserve your copy now!

# GARRARD

FULL CURRENT RANGE OFFERED BRAND NEW AT FANTASTIC SAVINGS

1025 stereo	£7.19.6	AP75	£16.19.6	SL55 with Bonotone	
2025T/C stereo	£9.17.6	SL75	£25.19.6	9TAHCD	£12.10.0
3000 stereo	£9.19.6	SL75R	£25.0.0		
SP25 Mk II	£11.9.6	SL95B	£25.0.0		
SL55	£11.12.6	A70/11	£11.19.6		
SL65B	£14.19.6	401	£25.0.0		
SL72B	£25.0.0				

Carrage 7/6 extra each item.

**TEAK PLINTHS & PERSPEX COVERS**

- For SP25, SL65, SL55, 3000, 2025 T/C 2025, 1000. £4.10.0
  - For AP75, SL75, SL95 £5.19.6.
  - For SP25 etc. to operate with lid in place £5.19.6.
- Carrage 7/6 extra each type. Full range of Garrard accessories available.



### LAFAYETTE LA-224T TRANSISTOR STEREO AMPLIFIER



10 transistors, 8 diodes. 1HF music power, 30W at 8 Ω. Response 30-20,000 ± 2dB at 1W. Distortion 1% or less. Inputs 3mV and 250mV. Output 3-16 Ω. Separate L and R. Volume controls. Treble and bass control. Stereo phone jack. Brushed aluminium, gold anodised extruded front panel with complementary metal case. Size 10 1/2 x 3 9/16 x 7 15/16in. Operation 115/250V. A.C. £24. Carrage 7/6.

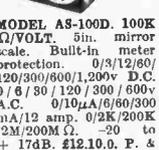
## MULTIMETERS for EVERY purpose!



**TE-51. NEW 20,000 Ω/VOLT MULTIMETER** with overload protection and mirror scale. 0/5/80/120/1,200v. A.C. 0/3/30/60/300/600/3,000v. D.C. 0.60μA/12/300mA. D.C. 0/80K/6 meg. ohm. 92/8. P. & P. 2/6.



**TE-90 20,000 Ω/VOLT MULTIMETER** mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000/25,000/100/500/1,000 v. A.C. 0/50μA/2.5mA/250mA D.C. 0/50μA/110/100/500mA/10 amp. D.C. 0.02K/200K/20 MEG. OHM. £15. P. & P. 5/-.



**MODEL AS-100D. 100K Ω/VOLT. 5in. mirror scale.** Built-in meter protection 0/3/12/60/120/300/600/1,200v D.C. 0/8/30/120/300/600v A.C. 0/10μA/6/60/300 mA/12 amp. 0/2K/200K/2M/2000M Ω. -20 to +174B. £12.10.0. P. & P. 3/6.



**MODEL TE-10A. 20k Ω/Volt 5/25/50/250/500/2,500v. D.C. 10/100/500/1,000 v. A.C. 0/50μA/2.5mA/250mA D.C. 0/9K/6 meg. ohm. -20 to +22dB. 10.0, 100mFd. 0.100-0.1mFd. 69/6. P. & P. 2/6.**




**MODEL TE-90 50,000 Ω/Volt mirror scale overload protection 0/3/12/60/300/600/1200v. D.C. 0/6/30/120/300/600mA. D.C. 0/8/60/600 mA. D.C. 16K/160K/1.6/16 meg Ω. -20 to +634B. £7.10.0. P. & P. 3/-.**



**MODEL TE-70. 30,000 Ω/V. 0/3/15/60/300/600/1300v D.C. 0/6/30/120/600/1200v A.C. 0/30μA/3/30/300mA. 0/16K/160 K/1.6M/16 Meg. Ω. £5.10.0. P. & P. 3/-.**



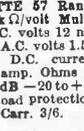**MODEL TE-80. 20,000 Ω/V. 0/10/50/100/500/1,000 v. A.C. 0/5/25/50/250/500/1,000 v. D.C. 0-50μA, 5/50/500mA. 0/6 K/60 K/600 K/6 meg Ω. £4.17.6. P. & P. 3/-.**



**MODEL TE-12 20,000 Ω/V. 0/0.6/6/30/120/600/1,200/3,000/6,000v. D.C. 0/6/30/120/600/1,200v. A.C. 0/60μA/6/60/600mA. 0/6K/600K/6Meg/60 Meg. Ω 50pF. 0.2mF. £5.19.6. P. & P. 3/6.**



### ★ TRANSISTORISED FM TUNER ★



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 x 2 1/2in 3 I. F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6.7.6. P. & P. 2/6. Stereo multiplex adaptors 99/6.

### TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection, 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.6. P. & P. 3/6.



### SINCLAIR EQUIPMENT

Project 60 range of new models now in stock  
Z30 Amplifier 89/6  
STEREO 60 Control Unit £9.19.6  
P25 Power Supply £4.19.6  
P26 Power Supply £7.19.6  
O16 Speakers £29.19.6  
All Post Paid  
SPECIAL PACKAGE OFFER!  
2 x Z30 Amplifiers Stereo 60 and P25 Power Supply £19. Carr. 7/6  
or with 2 x O16 Speakers £35 Carr. 7/6  
Micromatic Radio Kit 49/6  
Micromatic Radio Built 59/6  
SINCLAIR 1C/10 IN STOCK 59/6  
2000 Amplifier £23.10.0 Carr. 7/6  
Neoteric Amplifier £42.10.0 Carr. 7/6

### ECHO HS-606 STEREO HEADPHONES



Wonderfully comfortable. Lightweight adjustable vinyl headband. 6ft. cable and stereo jack plug. 25-17,000 cps. 8 ohm imp. 67/6 P. & P. 2/6.

### TE11. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: ±0.05dB. ±Indication dB x 0.1. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 5/-.



### RECORDING HEADS

COSMOCORD 1-track heads. High imp. record/playback 65/- Low imp. erase 20/-  
MARRIOTT 1-track heads. High imp. record/playback 65/- Low imp. erase 20/-  
Post extra.

### AMERICAN TAPE

First grade quality American tapes. Brand new. Discount on quantities.  
3in. 225ft. L.P. acetate ..... 8/6  
3 1/2in. 600ft. T.P. mylar ..... 10/-  
5in. 600ft. std. plastic ..... 8/6  
5in. 900ft. L.P. acetate ..... 10/-  
5in. 1,200ft. L.P. mylar ..... 15/-  
5 1/2in. 1,200ft. L.P. acetate ..... 12/6  
5 1/2in. 1,200ft. L.P. mylar ..... 18/6  
5 1/2in. 2,400ft. T.P. mylar ..... 22/6  
7in. 1,200ft. std. acetate ..... 12/6  
7in. 1,800ft. L.P. acetate ..... 15/-  
7in. 1,800ft. L.P. mylar ..... 20/-  
7in. 2,400ft. T.P. mylar ..... 25/-  
7in. 3,600ft. T.P. mylar ..... 45/-  
Postage 2/- Over £3 post paid.

### TAPE CASSETTES

Top quality in plastic library boxes.  
C60 60 min 8/8, 3 for 24/6  
C90 90 min 12/8, 3 for 36/6  
C120 120 min 18/-, 3 for 43/6  
Cassette Head Cleaner 11/8. Post Extra.

# G.W. SMITH & CO. (RADIO) LTD


All Mail Orders to -  
147, Church Street, London, W.2  
Tel: 01-262 8562 (Trade supplied)  
3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

# LOOK!

**PRACTICAL!**

**VISUAL!**

**EXCITING!**

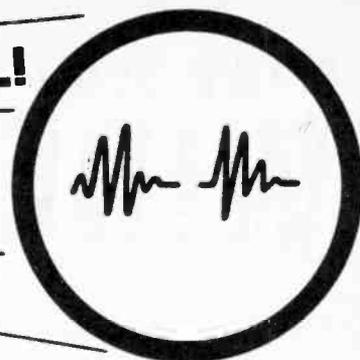


*a new 4-way method of mastering*

# ELECTRONICS

*by doing — and — seeing . . .*

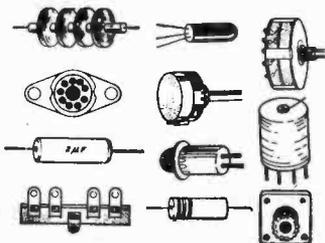
## 1 ▶ OWN and HANDLE a

complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



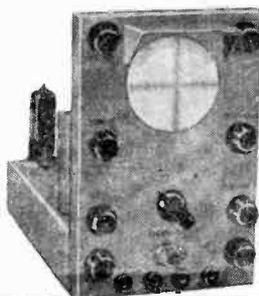
## 2 ▶ BUILD and USE

a modern and professional **CATHODE RAY OSCILLOSCOPE**



## 3 ▶ READ and DRAW and

**UNDERSTAND** **CIRCUIT DIAGRAMS**

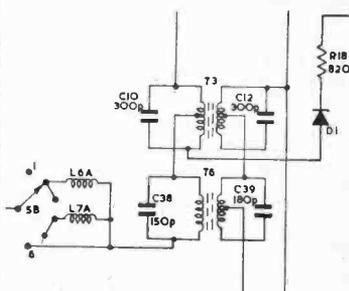

## 4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
  - TRANSISTOR EXPERIMENTS
  - AMPLIFIERS
  - OSCILLATORS
  - SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
  - COMPUTER CIRCUIT
  - BASIC RADIO RECEIVER
  - ELECTRONIC SWITCH
  - SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
  - D.C. EXPERIMENTS
  - SIMPLE COUNTER
  - TIME DELAY CIRCUIT
  - SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW5

# PRACTICAL WIRELESS

VOL 46 NO 2

Issue 760

JUNE 1970

## TOPIC OF THE MONTH

### LO, HI or MID?

FOR a good many years, a number of people (including the present writer) have argued the case for establishing a British standard for hi-fi equipment. Nothing, however, has been done in this direction in the UK and manufacturers wishing to put a label on their audio products are forced to quote the German DIN specifications.

The trouble is that progress has caught up with, and passed, requirements so that to many enthusiasts the fact that a piece of equipment meets the DIN45 500 specification is not so much a guarantee of high quality but rather an assurance that the equipment is not of low quality. The DIN specifications were drawn up several years ago and while they may have been adequate at the time are now sadly out of date as a criteria of top quality audio. Today they could reasonably be interpreted as being the minimum requirement of anything with any pretensions to quality and that any equipment below this specification is poor indeed.

This, of course, is the result of technical progress made in the past few years, and it leaves open to question current terminology. With the advent of really high quality audio equipment, the term "hi-fi" became part of the language, with inferior products dismissed contemptuously as "lo-fi" and other similar derisory terms. Around "hi-fi" grew up a certain mystique, which was encouraged not only by elements in the manufacturing world but by purist audio enthusiasts. The term became, as it were, the "in" thing.

But this barrier (which is based partly on snobbery) is becoming dissipated, due mainly to the vast improvements made in ordinary "domestic" audio equipment, which, once far removed from the real high quality equipment, has placed good quality sound reproduction within reach of most families. In other words, the gap in narrowing. And this has led to another frightful term, unfortunately gaining favour, namely "mid-fi".

So, what is the answer? The DIN45 500 standard (once hi-fi) is nowadays reckoned to be mid-fi by British thinking. The mid-fi of today, equivalent to the hi-fi of yesterday, will no doubt be the lo-fi of tomorrow. Do we abandon all labels, or set up a British audio standard which is subject to revision every few years? Or do we forget the whole mess and just sit back and enjoy listening to music?

W. N. STEVENS—*Editor.*

**JULY ISSUE WILL BE PUBLISHED ON JUNE 5**

## NEWS AND COMMENT

Leader	105
News . . . News . . . News . . .	106
On the Short Waves by Malcolm Connah and David Gibson, G3JDG	124
MW Column by Charles Molloy	132
Practically Wireless by Henry	142

## CONSTRUCTIONAL

Wide-Range L.F. Signal Generator by T. J. Melville	108
I.C. of the Month, National Semiconductors LM 100 by L. A. J. Ireland	112
Take 20, Record Player Amplifier by Julian Anderson	114
Light Beam Telephone by J. Thornton Lawrence	128
Mains Connector by B. Hunter	136
10 or 15 Metre Converter by C. Drinkwater	137
Transmitter/Receiver for the L.F. Bands by F. G. Rayer, G3OGR	145

## OTHER FEATURES

Going Hi-Fi by R. Hindle	115
Sums plus Circuits equals Understanding Part 3 by Leslie Moore	119
Aerials for Mobiles Part 2 by F. C. Judd, G2BCX	126
Superconductivity by I. R. Sinclair	133
P.W. Guide to Components Part 18 by M. K. Titman, B.Sc.	153

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

## Eliminators



Recently announced by *RCS Products Ltd., 11 Oliver Road, Walthamstow, London, E.17*, is a unit which enables a cassette tape recorder or portable radio to be used from a car battery supply. It is said to be particularly useful to people who have to make "notes" whilst driving or to people who want to just listen to music. Operating from the car supply it is possible to turn the volume up fully without any drain on a recorder's internal batteries.

Units can be supplied to deliver 6V, 7.5V or 9V. When ordering, the manufacturers ask if readers will state the make of recorder or radio and type of plug required on the unit lead. Price is 35s. plus 2s 6d. p.p.

## Mini Space Dishes

GEC-AEI (Electronics) have been awarded a substantial contract by the Ministry of Defence (Navy), for the development of a small shipborne satellite communications terminal (SCOT) to operate through the Skynet system, and provide secure communication links between small ocean-going warships and the U.K. The dish aerial, only 3½ feet in diameter, will be the smallest ever used in satellite communications.

While designed as part of the Skynet system, SCOT will be capable of operation through the American Defence Communication Satellite system should the need arise. More significantly, terminals as small, reliable and cheap as these could open the way for a large expansion in satellite communications for other purposes, both military and civil. SCOT is seen to have a considerable export potential.

## Police Equipment

The police forces of three of the states of the Federal Republic of Germany have recently installed fingerprint facsimile transmission equipment manufactured by Muirhead Limited of Beckenham, Kent.

Fingerprint photographs can now be transmitted within minutes between the Bundeskriminalamt in Wiesbaden and the Landeskriminalamter in Dusseldorf (Nordrhine/Westphalia), Stuttgart (Wuttenburg), and Hannover over normal telephone lines.

With this equipment a fingerprint picture 8 inches square when scanned at a density of 7.54 lines/mm (190 lines/inch) can be transmitted with extremely high definition in 14 minutes. The picture received is fully processed inside the receiver.

## Dynatron Phones



Dynatron Radio Limited feel confident that the use of high quality Stereo Headphones for personal listening will very soon become as popular here in the U.K. as they have been for some time past in the U.S.A., Canada and Scandinavia, and accordingly have equipped their range of radiograms and audio separates for 1970/71 with a jack socket to enable every item in their range to have stereo headphones connected.

The quality of sound obtainable through their new Stereo Headphones type S.P.2 which are suitable for use with their range of products is said to be quite equal to high quality Stereo Loudspeaker Systems. Price is £7 10s.

## Bedfast Club

Would readers of *Practical Wireless* like to help in the good work done by the Radio Amateur Invalid & Bedfast Club?

They would be grateful for any foreign stamps, which will be sorted and packeted and sold at the International Radio Engineering and Communications Exhibition to be held in London later this year, all proceeds going to R.A.I.B.C. funds.

Stamps need not be soaked off, but should have their backing paper cut to leave a generous margin on all sides. The address to which they should be sent is:

*Allan Herridge, G3IDG, 96 George Street, Basingstoke, Hants.*

Should there be a large response, it may not be possible to acknowledge individually, but donors may rest assured that all offerings, whether large or small, will be equally appreciated.


Readers may also be interested to know that the Bedfast Club, founded in 1954, now has 365 disabled licensed amateur and short-wave listener members in 12 countries.

## Low-cost scope

*Mitre Electronic Products of 22 Powis Terrace, London. W.11*, have introduced a new oscilloscope type EA0669-2 at only £29 15s. 0d. Features include: 2½ in. diameter tube; d.c. to 100kHz Y-amplifier bandwidth; calibrated Y attenuator giving deflection sensitivities of 100mV/cm., 250mV/cm., 1V/cm., 2.5V/cm., 10V/cm., and 25V/cm.; a.c. or d.c. input coupling; automatically synchronised timebase with four ranges (plus off) from 100mS/cm. to 10µS/cm.



## Receiver Kit

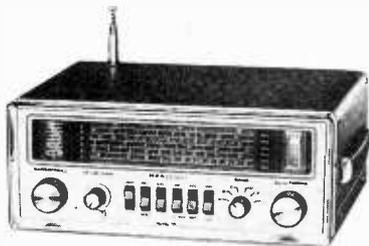

The GR-78 General coverage Receiver recently announced by Heath Company provides a.m., c.w. and s.s.b. coverage from 190kHz to 30MHz in six switch-selected bands. The all solid-state circuit employs Field Effect Transistors in the r.f. section and four ceramic i.f. filters. The ceramic i.f. filters eliminate the need for alignment. Built-in bandspread tuning can be calibrated for either the short-wave broadcast or amateur radio bands, and a switchable 500kHz crystal calibrator insures accurate dial calibration.

This receiver comes complete with a rechargeable nickel-cadmium battery pack with a built-in charging circuit. Wiring options permit operation from either 120 or 240V a.c., and 12V d.c. This receiver incorporates switched a.v.c. and an automatic noise limiter. Additional features include headphone jack, built-in speaker, external antenna terminals, receiver muting for use with a transmitter and a front panel relative signal strength meter.

Styled in Heath charcoal wrinkle finish with grey, black and chrome accents, the unit measures only 4½ in. H x 11½ in. W x 8½ in. D and weighs only 11lbs. The Kit GR-78 costs £68 18s. Daystrom Ltd., Heathkit Division, Gloucester. Telephone 0GL2 29451.

## Price changes


The prices in the Codar Radio advertisement on page 53 of the May issue are incorrect. The following are the revised prices: **T28** £16 10s., carriage 4s. 6d. **CR45** ready built £13 10s., carriage 10s. **Preselector PR30** £6 10s., carriage 4s. 6d. **PR30X** £8 10s., carriage 4s. 6d. **Mini Clipper 55s.**, carriage 3s.

## Chesterfield R.S.

The above Society met at its Headquarters at Hunloke Adult Education Centre, off Derby Road, on the 11th February. Twenty members were present and after the conclusion of the normal business, two extremely interesting films were shown from the Mullard Film Library, entitled: "Mirror in the Sky" and "Girdle round the Earth."

Other events have included a talk on colour television on the 11th March by Mr A. Barsby and a talk and demonstration on transistor principles by Mr G. C. Oxley on the 25th March.

## P.C. Boards

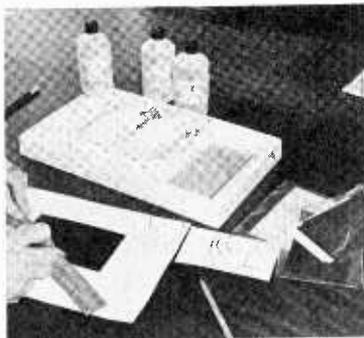

Circuitrite Ltd. have achieved a breakthrough in printed circuit design by developing a process by which electrically conductive patterns can be produced by direct application of a special pen to selected areas.

A Circuitrite "pen" containing a special chemical is applied directly to specially prepared materials which are subsequently immersed in a metal reducing solution. Since the chemical provides a catalytic surface to the selected areas only, the chemical reduction of metal is confined to those areas—even when the whole material is immersed in the reducing solution. In this way an electrically conductive pattern can be drawn directly on to the substrate without the necessity for etching or removing conductive material from unrequired areas.

Further details may be obtained from *Circuitrite Limited, c/o Haven Green, Ealing, London, W.5.*

## Engineer appointment

Phil Keene (44) at present an Engineer at the BBC's studios in Glasgow, has been appointed Engineer for BBC Radio Derby.

Mr Keene joined the BBC in December 1941 as an Engineering trainee in London. For the past eighteen years he has lived and worked in Glasgow.

## Thanet R.S.

Meetings of the above Society are held at Hilderstone House, Broadstairs each Friday at 7.30 p.m. except when the South East UHF/VHF Group hold their meetings. Further gen from *Dick Trull, G3RAD, 1 Approach Road, Broadstairs, Kent.*

## 2-hour Cassette

The range of Scotch magnetic tape cassettes has been expanded to include a two-hour version. A feature of this new Philips-compatible cassette—the Scotch C-120—is an improved shim material which offers reliability while eliminating tape binding and jamming.

The Scotch C-120 cassette, which retails at a recommended price of 33s. 6d., utilises Scotch Dynarange low-noise magnetic tape, which provides good high-frequency response while offering complete compatibility with slow (1½ i.p.s.) recording speed. As with the other cassettes in the range (the Scotch C-60 which gives 60 minutes recording and the Scotch C-90 giving 90 minutes) the new cassette is supplied in a durable hinged plastic case designed to protect the tape and provide easy storage.



# A WIDE-RANGE L.F. SIGNAL GENERATOR


**T**HE SIGNAL GENERATOR to be described is a sine-wave oscillator employing a Wien bridge feedback network, and the frequency coverage is from 15Hz to 1.5MHz in five ranges. The circuit uses the minimum of components consistent with reliable operation, and is easy to build and use. However, it is as well to say right away that if a really good output waveform is required, high quality components *must* be used throughout, particularly in the case of the ganged tuning potentiometers. The theoretical harmonic distortion of the instrument is under 1 per cent.

If the constructor needs only a general-purpose signal generator, and does not, for instance, wish to make distortion measurements on audio amplifiers, economies can be made. Using readily available components, an inexpensive dependable instrument can still be built.
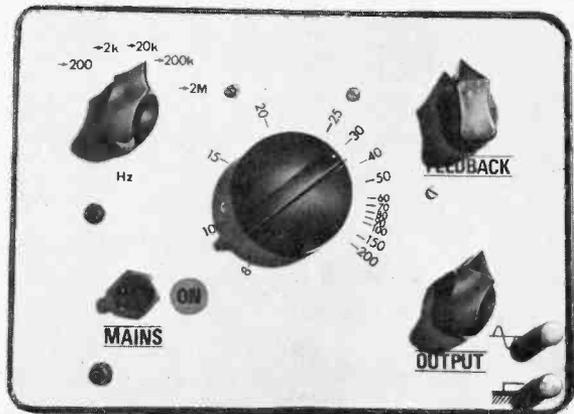
## Operation

The theoretical operation of the system is illustrated in Fig. 1. In its most elementary form, the oscillator is an amplifier with a resistance-capacitance network providing positive feedback between output and input. R-C networks are, of course, frequency selective; so the amount of feedback available reaches a peak at one particular frequency ( $f$ ). If the gain of the amplifier, and hence the positive feedback, were not controlled in some way, the waveform of the oscillations would be an indescribable monstrosity, with only peaks in amplitude corresponding to  $f$ . Very careful regulation of the amplifier's gain is therefore essential, and so a negative feedback loop is added to the circuit.

This loop cuts the gain of the amplifier down to the point where oscillation can only just be sustained;



## T. J. MELVILLE

thus regeneration can only occur at  $f$ , the frequency at which the Wien bridge permits the maximum amount of positive feedback, and the output is a sine wave.

In a circuit such as this, it is usual to make the components in the two halves of the Wien bridge of equal value, to simplify design calculations, and to enable variable tuning to be employed. Therefore,  $R=R_1=R_2$ ,  $C=C_1=C_2$  and the frequency of

oscillation is calculated from the formula  $f = \frac{1}{2\pi CR}$

the units being hertz, farads and ohms. Varying either  $C$  or  $R$  alters the frequency, and in this design,  $C$  is varied decade-fashion to provide "coarse" tuning for the instrument, and  $R$  is varied by potentiometers for the "fine" tuning.

In Fig. 1,  $R_3$  and  $R_4$  constitute a potential divider between the amplifier's output and earth. An accurately determined portion of the output voltage is fed back to the input from this, but in reverse phase. Consequently, the gain of the amplifier is drastically reduced. Given that  $C_1=C_2$  and  $R_1=R_2$ , the forward gain has to be cut to times 3.

The amplifier used in the signal generator is a simple two-stage circuit. The first stage comprises  $Tr_1$  and  $Tr_2$  (of Fig. 2) connected as a Darlington pair and has a high input impedance. This has to be high to prevent the lowish impedance of the bridge from being shunted. The second stage is a common-emitter amplifier with a small collector load to provide a low output impedance.

## Practical details

Since the gain requirement is so low, a wide range of bipolar transistors can be used in this circuit, germanium or silicon, npn or pnp. (Note: if pnp types are used, the power supply lines and electrolytic capacitors will need to be reversed in Figs. 2 and 4).

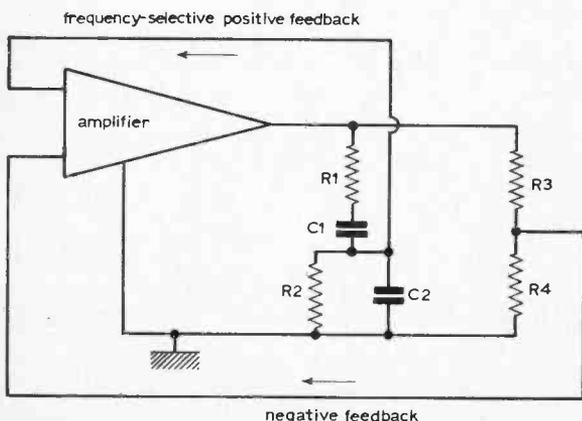


Fig 1: Block diagram of Wien bridge oscillator.

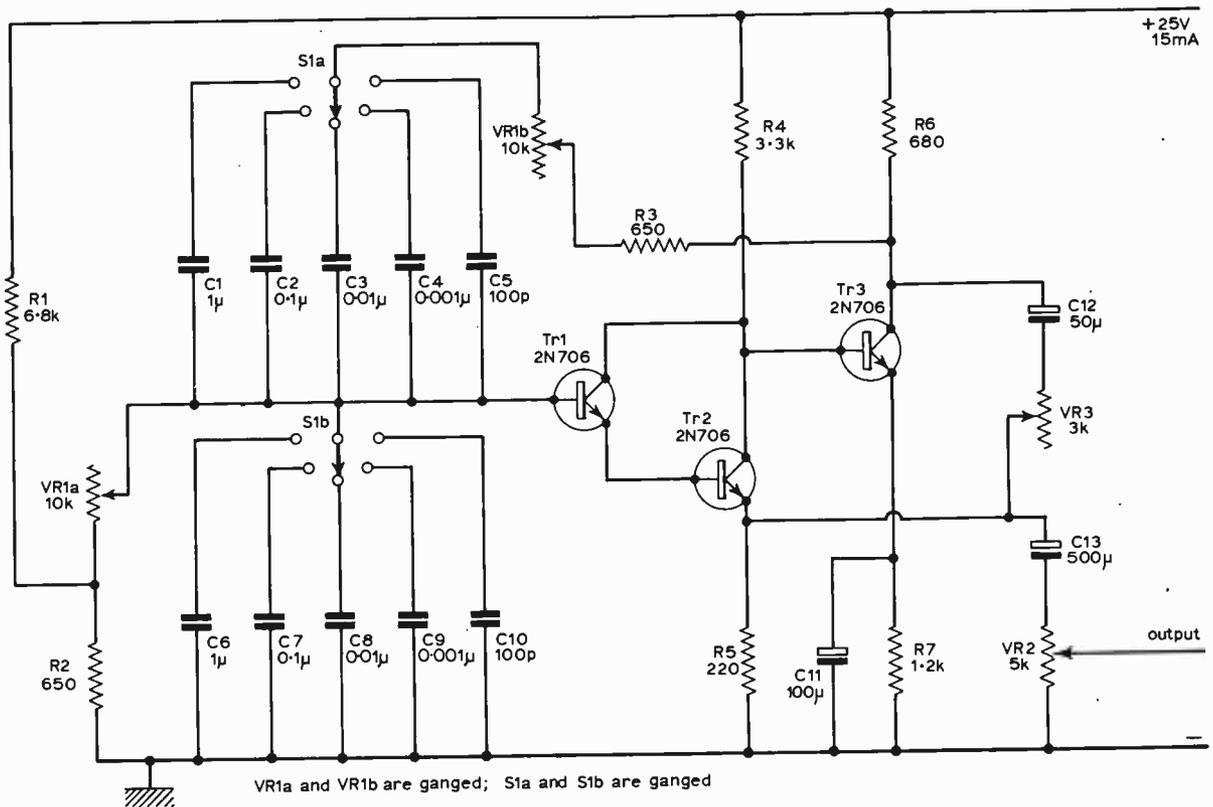



Fig. 2: Circuit of signal generator based on Wien bridge oscillator.

However, if the instrument is required to operate on the top range, transistors with a high cut-off frequency are essential. The types specified have an  $F_T$  of 200MHz, which enables the scale calibration to remain unchanged for all ranges. If poorer devices were used (eg.  $F_T$  about 10MHz) a modified scale would be needed for the 1.5MHz range at least.

After extensive experimenting, the author finally opted for "untested" 2N706's, which, at a few pence each, are the most economical choice. Silicon planar transistors with their low leakage ( $I_{cbo}$ ) offer the further advantage that the operation of the instrument is substantially unaffected by large changes in supply voltage or ambient temperature.

To move on to the actual circuit diagram (Fig.2), R3 and VR1b correspond to R1 in Fig.1, and R2 and VR1a to R2.; C1-5 of Fig.2 are C1 of Fig.1, and C6-10 are C2. From the formula quoted above, the theoretical range of the instrument is 14.950Hz to 2.453MHz, but as should be clear from Fig. 3,

Fig. 3: Typical dial calibration showing cramping at top end of scale when using linear-track potentiometers.

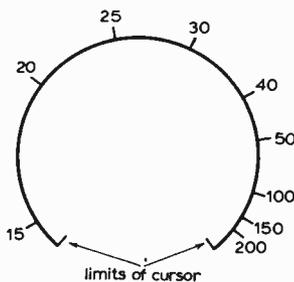

the scale above the 150 mark is too cramped for accurate calibration. Consequently, the nominal top frequency of the instrument is taken to be 1.5MHz.

The scale follows a more or less logarithmic course, and this admittedly unfortunate fact is principally due to the use of linear-track potentiometers for VR1. Anti-log types would improve the situation considerably, if reliably matched anti-log, or indeed matched log pots were available. The so-called logarithmic carbon pots that are offered by retailers are, of course, nothing of the sort. They merely have their track divided into two, one part being low-resistance and linear, and the other high-resistance and linear. To try and use a "matched" ganged pair of these in the present application is definitely not possible.

Ganged carbon pots usually claim to be matched to within 2dB, a figure which appears admirably low, but to the author at least, an unqualified decibel rating is more or less meaningless. He can only assume 2dB matching means a mismatch of up to +25%, -20%. From tests made on such components, however, this would appear to be a too pessimistic view.

Figure 3 illustrates the behaviour of VR1 in the prototype, which does, in fact, use a ganged carbon pot, and this probably makes the calibration more "logarithmic" than it should be. For the best possible results, ganged wire-wound potentiometers must be used. Suitable types are available from Colvern Ltd, Spring Gardens, Romford, Essex.

Negative feedback is derived from the collector of Tr3 and taken to the emitter of Tr2 via the

potential divider comprising VR3 and R5+VR2 (=R3 and R4 of Fig.1). VR3 varies the amount of feedback applied, so that the user can obtain the best waveform from the oscillator at any frequency. With VR3 at minimum resistance, the forward gain will be too low for oscillation to commence. The user should back off the control just to the point where it does occur.

The typical output level with VR3 correctly set and with VR2 at maximum is around 700mV, but variations of up to 10% can be expected due to mismatching in the bridge and the reduced efficiency of the amplifier at extreme frequencies.

At this point, the author must introduce Fig.4. This is a modified version of the original circuit employing a thermistor to give automatic gain control. It is ideal for those who do not like having an excess of knobs to twiddle, and who want a constant 1V output (VR2 can then be accurately calibrated). But the use of a thermistor has disadvantages. First, its dual roles of giving a constant output voltage and regulating the gain of the amplifier are not necessarily compatible. Consequently, the hi-fi constructor is advised to retain VR3 to get the best waveform, and not to worry too much about the output voltage.

The maximum dissipation of the only thermistor suitable is 3mW, which means that the careless must be very careful with their soldering irons and heat sinks. Also, its purchase would almost double the cost of the instrument. If the thermistor is to be used, a small pre-set potentiometer (about 1k $\Omega$ ) may have to be wired in series or parallel with it (experimenting will decide which) in order to get the best results. Once adjusted, this potentiometer should of course be left alone, since continued twiddling would invalidate the use of the thermistor in the first place.

### Using the Frequency Meter

The capacitors C1-10 should be close-tolerance types, and can be checked with the frequency meter described in PW May 1970, even if the signal generator to be used for the testing signal is the present design and still under construction. Although the output waveform will doubtless be rather nasty, the signal generator will function with capacitors that are quite badly mismatched. By judicious manipulation of VR1 and the f.s.d. pre-set control in the frequency meter, a considerable overlap of ranges is possible.

If, for example, two 0.1 $\mu$ F  $\pm$ 20% capacitors are temporarily wired in for C2 and C7 in the signal generator (and if oscillation occurs), 1 $\mu$ F, 0.1 $\mu$ F and 0.01 $\mu$ F capacitors can be accurately checked with the frequency meter. As the latter does not contain a 100pF capacitor, two of these will need to be purchased.

If the constructor has already built the frequency meter, calibration of the scale for VR1 is no problem at all: some might not consider it even necessary. There is surely nothing more tedious than inscribing scales and dials, especially if they are cramped at one end. This constructor for one invariably gets an acute attack of Calibrator's Cramp! On the prototype of the signal generator, only one scale was found to be necessary, calibration for the bottom range being correct for the top range. Though as the latter (if included) cannot be checked against

the frequency meter, a radio set should be called into use.

### Construction

The instrument must be housed in a metal case or box, and screened leads used for output connections. The reason for this is simply to avoid r.f. radiation from the instrument. Readers may well think that operating the oscillator at 1kHz, say, is unlikely to interfere with anyone's radio reception. It won't, as long as the output waveform is kept sinusoidal.

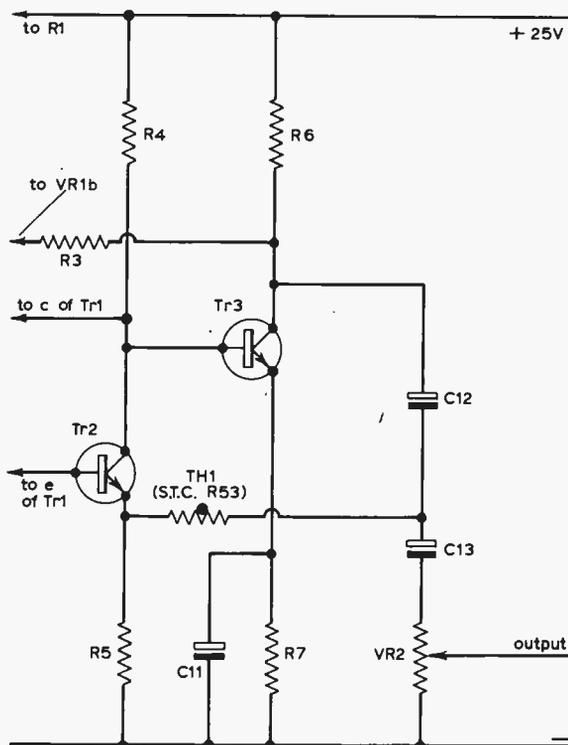


Fig. 4: Modified circuit using a thermistor to provide a.g.c.

Most of the components are accommodated (vertically) on a Veroboard module. (See Figs.5 and 6). Layout is not critical, though wiring between the module and the other bits and pieces should be short, direct and rigid to minimise stray capacitances.

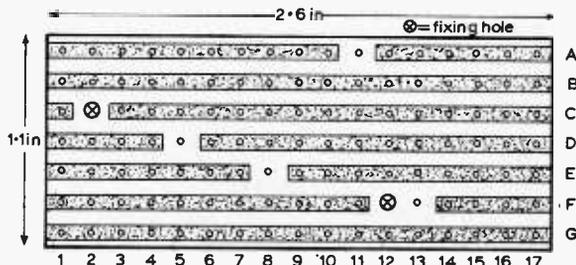


Fig. 5: Circuit board shown actual size.

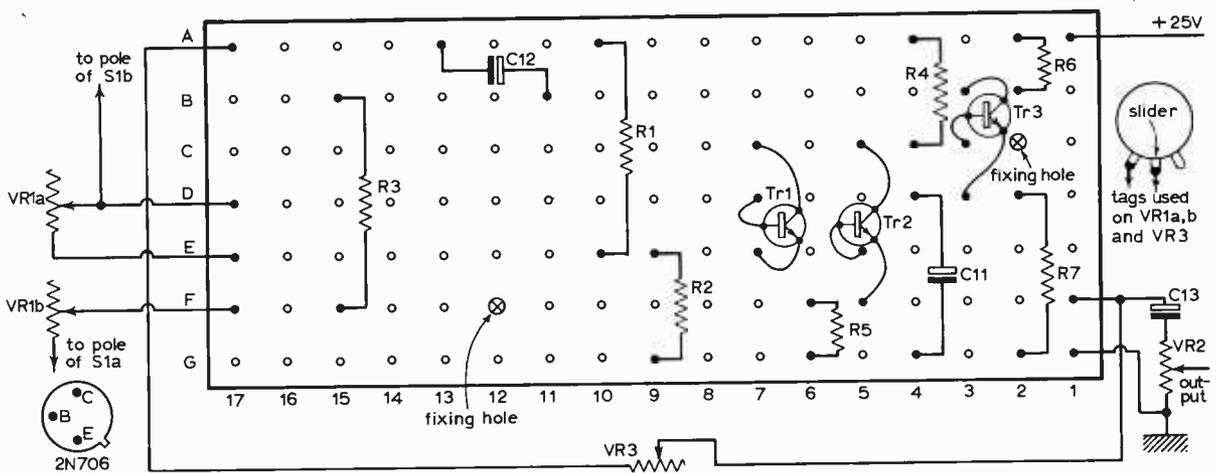


Fig. 6: Enlarged view of circuit board showing location of components.

This is particularly important if the top range is to be included. The tuning capacitors C1-10 are mounted on a group board, and this should have more than the required minimum of ten parallel pairs of tags, to allow room for padding capacitors, if necessary.

## ★ components list

### Resistors

R1	6.8k $\Omega$	VR1a/b	10k $\Omega$ linear ganged
R2, 3	650 $\Omega$ $\pm$ 1%	VR2	5k $\Omega$ linear
R4	3.3k $\Omega$	*VR3	3k $\Omega$ linear
R5	220 $\Omega$		
R6	680 $\Omega$		
R7	1.2k $\Omega$		

### Capacitors

C1-10	see Table 1
C11	100 $\mu$ F 6V electrolytic
C12	50 $\mu$ F 25V electrolytic
C13	500 $\mu$ F 3V electrolytic

### Semi-conductors

Tr1, 2, 3 2N706

### Miscellaneous

\*TH1 Thermistor type R53 (Fig. 3: only)  
Veroboard, 2 pole 5 way switch, metal case,  
insulated terminals, group board for C1-20.

### Power Supply

\*Transformer 18-25V at 20mA \*see text  
\*Capacitor 2000 $\mu$ F 25V  
\*Four silicon diodes 50 p.i.v. 50mA(OA200, OA202)  
On-off switch, group board for diodes.

## Power supply

Figure 7 illustrates a suitable power supply for mains operation of the instrument. There is a lot to be said for powering the equipment from batteries if this is feasible, since a ripple-free supply is essential. However, the power needed is at least 20V at 15mA, so readers may consider a mains supply more practicable.

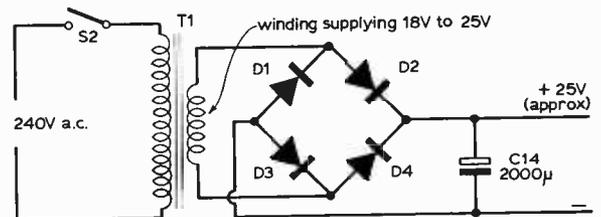


Fig. 7: Circuit of suggested power supply unit.

The mains transformer and smoothing capacitor will need to be of modest dimensions if they are to be housed in the same portable case as the rest of the circuitry. The author in fact used a miniature 120V transformer, with a 12k $\Omega$  resistor as a voltage dropper (on the mains side), and certainly a resistor of this size helps the smoothing considerably.


If miniature silicon diodes such as the OA200 (or "untested" equivalents) are used for the rectifiers, it should be noted that they have a high forward resistance at 15mA or so, compared to the more orthodox types of rectifier diodes. Consequently, if one's transformer gives out 25V a.c., the output from the rectifier bridge will still be only 25-30V d.c. (It should be about 36V with a large capacitance reservoir). The maximum operating voltage of the signal generator is about 30V, but the rating of the smoothing capacitor will normally limit this to 25V.

The author used a box 9 x 6½ x 1½ in to house his instrument. A large front panel area is needed, if the controls are to be comfortably spaced out, and the depth will largely be determined by the size of the mains transformer or battery used.

Table 1

Values for C1-10 (all  $\pm$ 1%) and ranges covered

C1, C6=1 $\mu$ F	15-150Hz
C2, C7=0.1 $\mu$ F	150Hz-1.5kHz
C3, C8=0.01 $\mu$ F	1.5-15kHz
C4, C9=0.001 $\mu$ F	15-150kHz
C5, C10=100pF	150kHz-1.5MHz

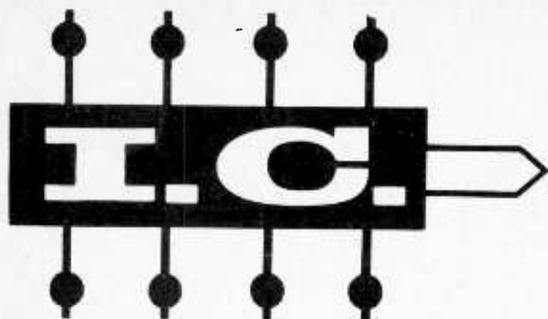

# OF THE MONTH

L.A.J. IRELAND

Number 8

LM100 Voltage Regulator

**A** FEATURE of the present phase of integrated circuit development is the increasing number of special-purpose linear units becoming available, and this month one such application is discussed, the question of precision voltage regulators.

Here the close matched characteristics of monolithic active elements is particularly useful. Operation is by comparison of the voltage delivered to the load at any instant with a stabilised reference voltage, with any deviation being amplified and applied to the actual regulating element.

In a given case this may be either a series or parallel element; the former procedure places the control transistor in series with the load, so that its d.c. resistance (dependent on the bias applied by the deviation amplifier) forms a potential divider, together with the load, across the unregulated supply voltage, while the latter method divides the output current between the load and a transistor in parallel with it, the transistor being biased so that the total current drawn remains constant despite fluctuations of the load.

regulated output which supplies the comparison signal to match the fixed reference voltage.

"Line regulation," that is, the variation of output voltage as the input unregulated voltage fluctuates, is better than 0.05% per volt, while load regulation, or the variation in voltage as the current drawn from the regulator changes from its minimum to its maximum limit, is 0.1%. Further, a current limiting feature is built in, so that the circuit is self-protecting against output short circuits.


The only obvious limitation on the usefulness of this device is the low value of permitted output current which can be drawn from the regulated output, 12 mA. This is due to the fact that a high current transistor requires a relatively large junction area, while in the LM100 the whole circuit occupies a chip of silicon only 38 mils. square. However, if the output of the circuit is used as the base current of an external discrete transistor, a current of 200mA. is available, or even several amps. if a power transistor is used.

## Operation of the LM100

Now to examine the actual device and its application in detail. In use, the reference voltage is compared with a fraction of the output voltage; therefore to allow the maximum range of permissible output voltages, the reference should be as low as possible. Further, on the stability of the reference depends the maintenance of the preset output voltage as temperature drift occurs.

In the LM100 the basic reference is provided by the zener D1; 6.3 volts appears across this element when supplied with current from the constant current source Q2. However, it has a positive temperature drift, amounting to 7mV/°C at the output of the emitter follower buffer transistor. This is compensated for by the negative drift of Q7, so that the definitive reference voltage of approx. 1.8V. at the junction of R1 and R2 is stable to within 0.3% over an extended temperature range (-55°C to +125°C).

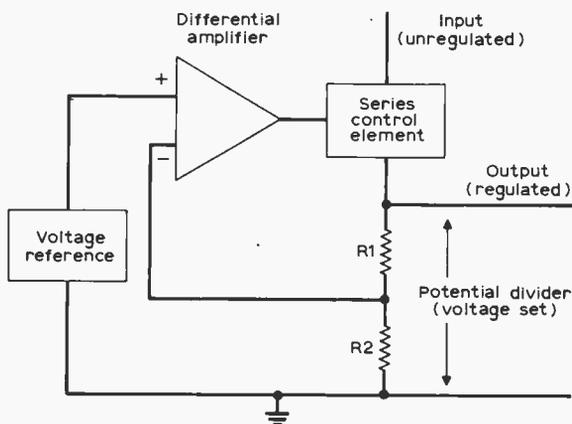The deviation or error amplifier is basically a single stage differential pair (Q8 and Q9) followed by a Darlington output circuit, Q11 and Q12. If, however, an external transistor with a higher current rating is to be employed, access to the collector of Q12 is provided to supply the base drive, with R8 already in place to act as an emitter-base resistor for




Block diagram of a series regulator.

The standard voltage regulator is the National Semiconductors type LM100. This is a "positive" regulator, in that the negative line is common to both the input (unregulated) and output circuits. It can accept an input voltage of up to 40V and provide an output of from 2 to 30V, the precise value being determined by a potential divider across the

the transistor; when used "straight" pins 2 and 3 are shorted, eliminating this resistor from the circuit.

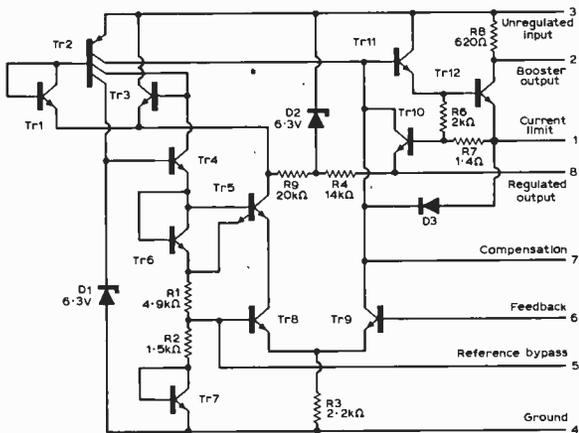Q10 is responsible for the current-limiting function. At a level determined by an external resistor, Q10 is biased on, reducing the drive to Q11 of the Darlington pair. The emitter-base voltage of Q12 also affects the bias of Q10, and with the difference in temperature drift between these two transistors due to the difference in current density in their emitter junctions, the current limit for operation of Q10 drops as the temperature rises.




Complete circuit of the LM100.

The amateur will probably prefer to use the commercial variant of the LM100 circuit, having little need for the extended temperature range which can be traded off against unit cost. The LM200 operates from  $-25^{\circ}\text{C}$  up to  $+85^{\circ}\text{C}$  and cheaper still is the LM300, further restricted in temperature and also in input voltage (30 rather than 40). However, all three have the same internal layout, and the degree of regulation achieved is similar.
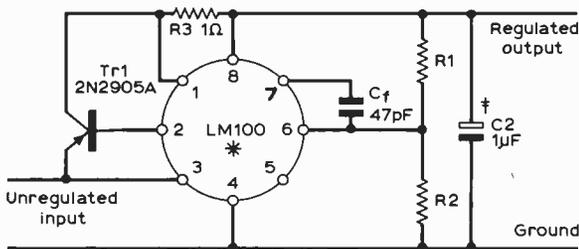
## Applications

As for amateur applications, two will be mentioned to indicate possibilities. Standard transistor radios, tape recorders, etc. have a current consumption dependent on audio output level, since they commonly employ a class B arrangement. Should it be desired to operate such a device from, say, a 12 volt car battery, a simple dropper resistor in series




\*Base diagram is top view

†Solid tantalum


With an external transistor stabilised outputs up to 200mA can be obtained.

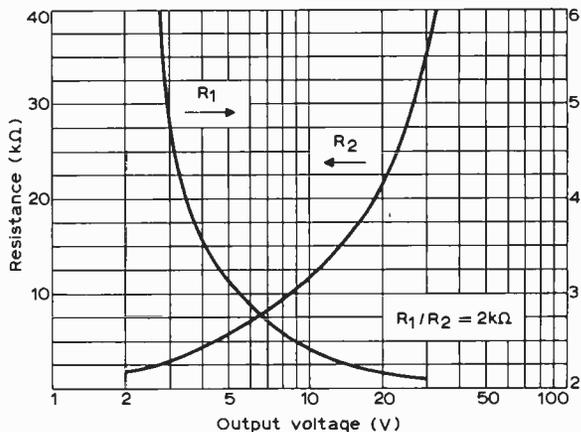would not provide the 6 or 9 volts required, as by Ohm's law the voltage drop would be current dependent.



Optimum values of  $R1/R2$  as a function of the output voltage.

An LM100 type regulator, however, with a suitable external transistor, would be ideal as a source of stabilised d.c. for such a load. In another field, every constructor has at some time desired a variable d.c. power supply unit to replace batteries when experimenting or developing transistor circuits. If pin 6 is supplied from the slider of a 50kΩ potentiometer, an LM100 is a very fine continuously variable power supply; further, with the current limit facility, should there be a fault in the experimental circuit no excessive current can be drawn, so that not only is the regulator protected, but also the equipment under test.

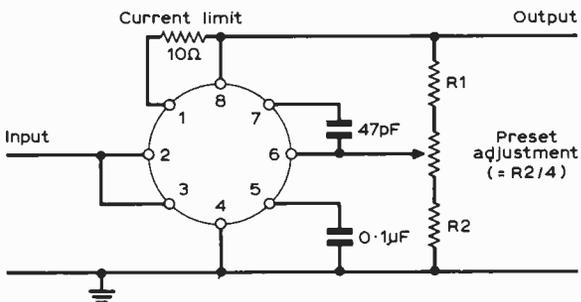

Circuit to provide a continuously variable output.

Already, too, there is news of improved regulator circuits on the way, which will not require external transistors to carry a useful current; G.E. (U.S.A.) are working on a PA264 with a 5 watt capability, similar in appearance to the PA246 audio amplifier already mentioned in these pages. Motorola are introducing an MC1461 with a reported 10 watt dissipation, in a new can with integral heat sink; and from National a negative regulator (LM104) is expected. So perhaps in the future a return to this month's theme will be called for; meanwhile the "simple" positive regulator can be usefully investigated and applied.

The LM300 can be obtained from the Semiconductor Marketing Co. Ltd., 140 High St., Egham, Surrey.

# TAKE 20

JULIAN ANDERSON

**A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build**

THERE must be many constructors who have purchased record players and have added ready built amplifiers to these. Our project for this month is for such an amplifier for those who may wish to build their own and save money. Although designed for use with a record player, the amplifier has, of course, uses in several other fields. It is extremely simple and should be very quickly built and this, together with the fact that it should cost well under 20s., makes it an ideal project for the raw beginner.

There should be no problem in obtaining the components from almost any supplier, though by shopping around it is usually possible to save quite a bit.

Output from the amplifier is about 750mW, which is of course very small by current standards, but this sort of volume is more than adequate for normal use. The quality is very acceptable and although far from being in the Hi-Fi category, it is unlikely to be the main cause of poor quality when used with a cheap record player using a crystal pickup on 45 r.p.m. discs. It should be the ideal companion for one of the cheap battery operated turntables.

## THE CIRCUIT

Crystal pickups have a high output but also have a high impedance and for best matching should be connected to a load of at least 500k $\Omega$ . VR1, nominally 1M $\Omega$ , could in fact be any value between 500k $\Omega$  and 2M $\Omega$ . Although the volume control presents a high impedance to the pickup, the amplifier has a very much lower impedance input and it will be seen that when the volume control is at maximum the input impedance of the first stage causes a mismatch. In fact in this position the tone *does* alter because of this. However this is not objectionable and while theoretically it is bad practice, it has been left like this for simplicity.

C1, 0.5 $\mu$ F is rather lower than one would expect to see but in the prototype no improvement was gained by increasing the value.

Tr1 acts as a straightforward amplifier with R1 providing the base bias and R2 acting as the collector load. We have made considerable use of the transistor used here, the BC169C, in previous circuits and will do so in future. It is a plastic encapsulated, high gain, low noise silicon transistor costing around 2s 6d. (It has two further features to recommend it, neither of which are made use of in this circuit, of handling an appreciable collector current and having a high frequency cut-off). In this circuit we are using it for its high gain.

Tr2 is a germanium PNP type power transistor and in the circuit is "inverted" so to speak. The base is

## No. 14 RECORD PLAYER AMPLIFIER

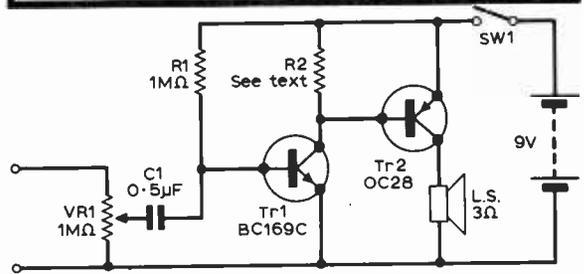


Fig. 1: The circuit of the record player amplifier. In the prototype R2 was 39 $\Omega$ .

## ★ components list

R1	1M $\Omega$ 10%, $\frac{1}{2}$ watt
R2	39 $\Omega$ 10%, $\frac{1}{2}$ watt, see text
VR1	1M $\Omega$ log. pot. with switch.
C1	0.5 $\mu$ F
Tr1	BC169C
Tr2	OC28
L.S.	3 $\Omega$ type, 6in. diameter or larger.
Battery	9V, PP9 etc.

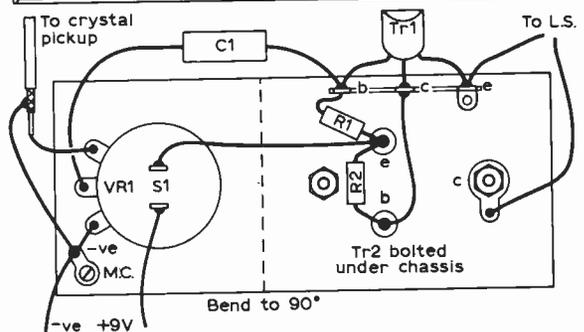



Fig. 2: The layout on a small aluminium chassis. Note that the power transistor, Tr2, should be insulated from the chassis in the usual way.

directly coupled to the collector of Tr1 and the loudspeaker acts as the collector load.

The value of R2 is critical for it sets the quiescent current through Tr2. If its value is high excessive current is drawn leading to short battery life; if too low it causes "clipping" and severe distortion. Its value should be chosen so that it is the lowest that does not cause clipping on maximum output on the peaks of the signal. In the prototype 39 $\Omega$  was the final value chosen but in earlier mock-ups it was 56 $\Omega$  and 100 $\Omega$ . One could use a preset here but trial and error selection is just as good. If one has a testmeter it will be found that the quiescent current is around 30mA using the best value.

Since the quiescent current for Tr2 is passing through the speech coil of the loudspeaker it is important that a decent sized one is used. Speakers under about 6in. diameter will sound dreadful operated from this amplifier as the biased speech coil causes it to operate at an unfavourable point; this effect is not noticeable on larger diameters. ■

# GOING HI-FI

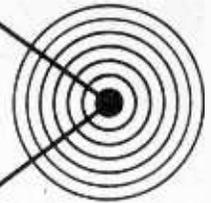

R. HINDLE

**T**HERE is a minimum specification that should be met before the tag Hi-Fi is attached to an installation but there are often signs of misuse of the term and there is no widely accepted definition. Specifications can be in technical terms such as power output, degree of distortion, frequency range and so on but, although these factors are important, they cannot tell the whole story because, firstly, they do not cover the whole chain of reproduction; and, secondly, the environment (e.g., the type of room and its furnishings) has a profound effect on the result.

The overall system involves one or more sources of signal—a radio tuner, a record player or a tape deck, or a combination of those—an amplifier and a speaker system. Maybe present needs are thought not to call for equipment capable of stereo reproduction (resulting in doubling up the amplifier and speaker systems) to qualify as Hi-Fi, but the time when this must be insisted upon is surely coming.

The Hi-Fi enthusiast is also unlikely to accept into his world any equipment built as a single unit; he has good reasons for his belief that high fidelity in reproduction can be achieved only by the use of speakers separate from other equipment.

## COMPARING EQUIPMENT

The usual advice given to purchasers of Hi-Fi equipment is to go where they can hear comparisons between a wide range of models. This is good theoretical advice but it is not really practicable. This is because it is quite impossible to carry in one's mind a sufficient impression of successive permutations and combinations of equipment for the mutual comparison to be valid. Even if this were not so it would not be possible to make a reliable, final choice without taking into account the environment, so that the ultimate tests would have to be made in the user's own room.

Is the equipment, in fact, to be stereo or mono? The answer these days surely must be stereo; even though the full aim may not be realised immediately

and the intention is to reproduce in mono for the time being everything to be bought at this time must be suitable for a stereo ensemble.

## INPUTS

Next, specify all the input sources that are likely to be needed, not just now but during the lifetime of the equipment. Almost certainly there will be a record player, perhaps in the first place using a cheaper, ceramic cartridge but later to acquire a more expensive cartridge which will not only give a much smaller signal but will also have a different characteristic.

So the amplifier must have two suitable input facilities if it is intended to progress from a cheaper to a more expensive cartridge. Typical input sensitivities looked for would be around:—

100/200mV for ceramic cartridges

2/4mV for magnetic cartridges.

A stereo cartridge in either variety would be chosen. This will play either mono or stereo records but the mono cartridge would not deal with stereo records.

There is also likely to be a need to budget for a radio tuner (typically giving 200mV). Perhaps also a tape deck is to be used. In practice it is extremely unlikely that a modern amplifier will be deficient in these input facilities or in the provision of the necessary equalisation circuits to compensate for standard characteristics now adopted for the input signals. Not all operate equally well with regard to the input overload characteristic and this is very significant. The input sensitivity previously referred to indicates the input signal to give rated output, and if there is more input signal than rated the volume control can be set lower so that the output circuits are not overloaded. However, the volume control is unlikely to be in the input circuit itself but will follow the low noise first stage and consequently its adjustment cannot prevent the input stage from overloading.



*"go where they can hear comparisons"*

Having determined the input characteristics needed, any amplifier unsuitable on this account can be rejected on the basis of considering the technical specifications given in the manufacturer's literature and in technical reviews. The rest can be surveyed without further consideration of input requirements and demonstrations can be taken using a single, high quality input device—probably a pickup cartridge because of the ease and speed with which a range of different sounds can be demonstrated using records.

## THE BUDGET

There is the question of cost and it is pointless to produce a short list of possibles only to find that none can be fitted into one's budget, though most people finish up by paying more than they had originally intended. If a complete outfit is to be purchased about a third of the total money available should be spent on the amplifier and about another third on the speakers, leaving a third for a motor, pickup arm and cartridge; the proportion will change if a tuner or tape deck is also to be included.

The important consideration is that the quality of the various units should be compatible. However, it is perhaps worth bearing in mind that amplifier design is probably nearer perfection than other links in the chain and a good choice now is going to be acceptable for a long time.

## POWER OUTPUT

Power output from the amplifier is worthy of thought. Advertisements give one the impression that power needs are increasing all the time and figures up to hundreds of watts are seen. But first make sure that the watts are genuine. Only ratings of continuous sine wave output (or so called r.m.s.) should be accepted for comparison and if interesting amplifiers are not specified in this way (read the small print to make sure), ask for a conversion of the specification provided into continuous sine wave form.

Practically the whole of one's listening is done at the level of a fraction of a watt, so why bother about high output? The truth is that it is not so important as one might imagine, but it does come into its own on the occasional peaks that contribute so much to the overall satisfaction derived from listening to music.

Probably many people can get by with some 3 to 4 watts per channel, but musically it is unlikely to be satisfying. Ten watts per channel will be a great improvement and most people will be content. An increase to 20/25 watts per channel will be worth while, but it is doubtful whether any further increase will be an advantage in most cases.

Speakers vary in acoustic efficiency and therefore have a bearing on power output needed. The smaller units are less efficient and need more power input for a given noise but are rated at lower maximum power input than the larger more efficient speakers. The larger units are commonly rated at 25 watts and if fed by power up to their full rating will give a very healthy volume.

It is not necessary to be overstrict in comparing amplifier peak output ratings with speaker power ratings—the figures need not necessarily be identical.

Speakers with a higher rating than the amplifier are obviously acceptable and even if they have a somewhat lower rating it need be no cause for concern. Speaker impedance varies as frequency varies and so matching to amplifiers is not an exact science.

However, one should choose speakers with a nominal impedance equal to that specified by the makers of the amplifier. This impedance is commonly 8 ohms with modern transistor amplifiers but there are variations, for instance 16 ohms as commonly used for valve amplifiers. If an amplifier is to be bought for use with existing speakers and if perhaps the preferred amplifier specifies an impedance differing from that of the speakers caution is called for.

Small increments in power output are quite unnoticeable. An increase from, say, 10 to 12 watts (other things, and particularly distortions, being equal) will be pointless. Increases by a factor 2 are necessary to make an impression of greater power.

## DISTORTION

Having dealt with input and output, what goes on in the middle? In the process there will be the inevitable production of distortion and this is specified in relation to output. For modern amplifiers a total harmonic distortion at full rated output of 1% is mediocre; the better amplifiers will have a figure of 0.1% or less. Since the greater part of one's listening time involves output at a fraction of a watt, distortion at these low levels can be very annoying.


The intending purchaser should look for a specification of low level distortion, ideally in the form of a graph or a statement covering a range of output levels rather than a specification at a single output level. The surest way of avoiding this unpleasant rise in distortion at lower outputs is to use Class A output in which case there is an intrinsic fall in distortion at lower levels; such amplifiers sound distinctly better than most and are as good as the best of Class B amplifiers.

Frequency response is unlikely to be inadequate in these days. It should, and generally does, extend from below 40Hz to above 20kHz without significant deviation from level response. However, this is usually measured at comparatively low power levels and it is important to know if the frequency range is held at higher powers—this is often called the power bandwidth. A satisfying statement by the makers of a well-known amplifier is "Frequency response maintained up to full power (25Hz—25kHz  $\pm 0.5$ dB)."

## CONTROLS

Finally the controls provided should be considered. There must be an input selector for the various inputs chosen. A switch is needed to ring the changes between stereo and mono, in the latter case permitting either left hand or right hand input to be used or for the two to be combined into a single signal. Volume, bass and treble tone controls are needed in each channel for stereo—ganged controls with single knobs are preferred and this makes a balance control essential.

—continued on page 150

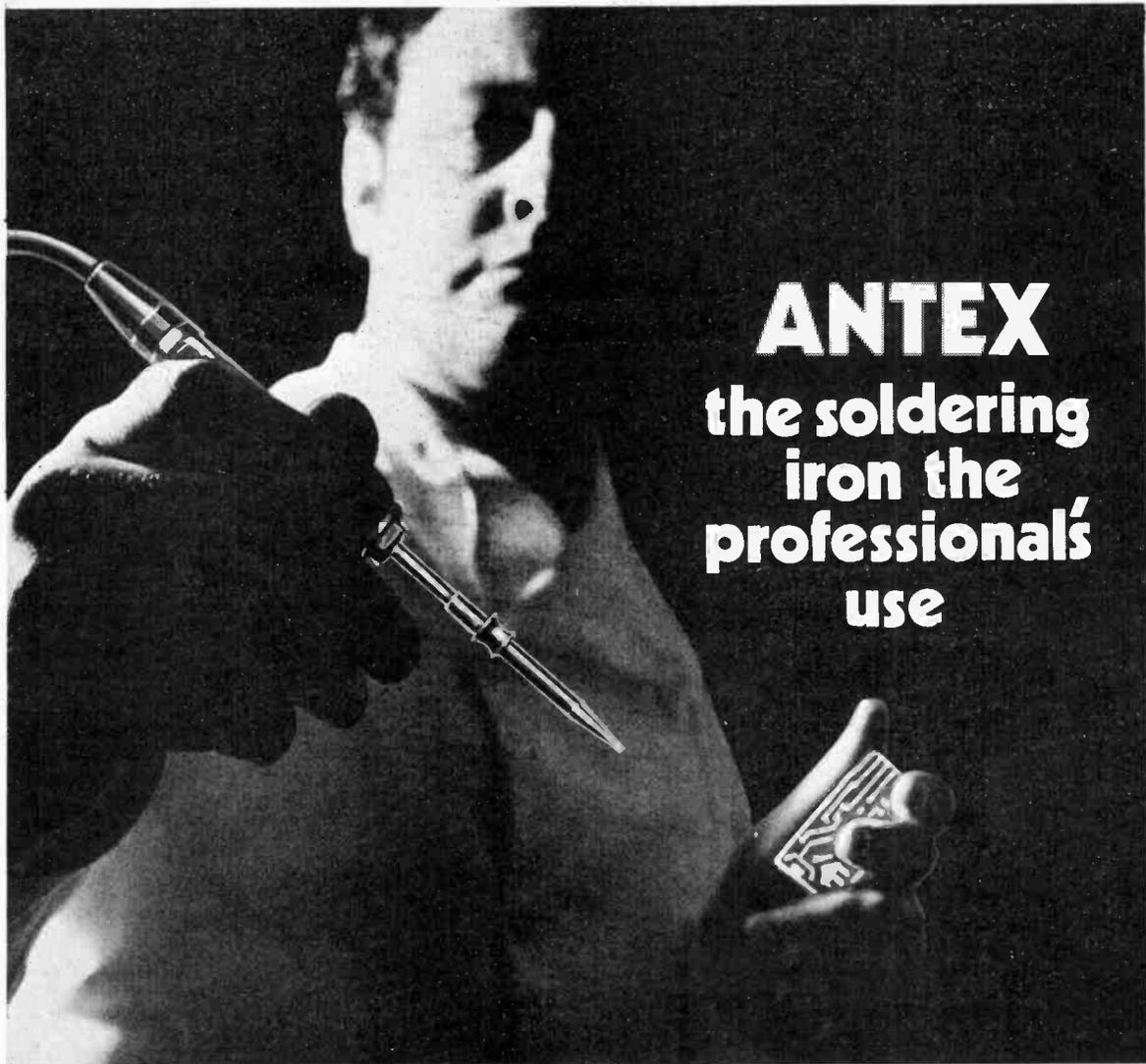

# ANTEX

## the soldering iron the professionals' use



G 18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From 35/-




ES 25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From 35/-



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From 42/6 Spare bits and elements for all models and voltages immediately available from stock.

### Complete precision soldering kit

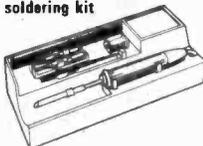

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits 1/8", 3/16"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**



Model CN 240/2  
15 watts - 240 volts  
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **31/6**



### PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.  
Telephone: Plymouth 67377/8.  
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |

enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

..... P.W.6

# BENTLEY ACOUSTIC CORPORATION LTD.

Suppliers to H.M. Government. 38 CHALCOT ROAD, LONDON, N.W.1 Telephone 01-722-9090

EXPRESS POSTAL SERVICE, SAME DAY DESPATCH BY FIRST CLASS MAIL  
ALL GOODS ARE NEW, BEST QUALITY MANUFACTURE ONLY, AND SUBJECT TO MAKER'S GUARANTEE

0A2	5/9	6D6	3/-	10P14	20/-	77	10/8	E83P	24/-	EL34	10/8	PC88	10/3	SP42	12/8	VT501	3/-	ASY27	8/8	MAT120	7/9
0B2	4/6	6E5	7/8	10P18	6/8	78	4/9	E88CC	12/-	EL37	17/3	PC95	8/3	SP61	3/3	VU111	7/3	ASY28	6/8	MAT121	8/6
0Z4	4/6	6P1	12/6	10P12	7/-	85A2	4/9	E180C	8/-	EL41	11/-	PC97	8/6	TH48	10/-	VU120	12/8	ASY29	10/0	OAS	5/8
1A5	4/8	6P6A	5/-	12A6	12/8	85A3	4/9	E180F	19/-	EL42	10/8	PC98	7/6	TH233	7/-	VU120A12	10/0	B1181	10/0	OAS	2/8
1A8	4/8	6P6M	12/8	12A6C	7/8	90A0	8/7/8	E182CC	22/6	EL61	10/8	PC98A	6/3	TP22	11/-	VU133	7/-	BA102	9/0	OAI0	8/8
1A7GT	7/8	6P12	3/3	12A16	7/6	90A9	3/7/8	E450	1/6	EL83	7/8	PC98B	6/6	TP23	6/9	W63	10/8	BA103	9/0	OAI1	8/8
IC10	5/6	6P13	3/8	12A18	12/6	90G0	3/7/8	E473	1/5	EL84	4/8	PC98C	9/9	TP28	9/9	W76	3/9	BA104	11/0	OAI2	8/8
IC2	9/9	6P15	10/-	12A19	4/8	90V4	8/7/8	E480C	6/8	EL85	7/8	PC98D	9/6	UAB0C	6/8	W77	2/6	BA105	2/6	OAI3	7/8
IC3	7/8	6P18	7/8	12A27	3/9	9801	16/6	E4C91	3/-	EL86	4/8	PCC189	10/8	UAF42	10/3	W81M	13/8	BA130	2/6	OAI7	1/9
ICG	4/9	6P25	14/3	12A28	4/9	19012	14/6	E4F42	10/-	EL91	4/8	PCC805	13/9	UB41	6/8	W101	26/8	BCY10	5/0	OAI9	1/9
ID5	7/6	6F24	12/8	12A27	4/8	160C2	5/9	EB34	3/-	EL95	5/3	PCC806	15/6	UBC41	9/-	W107	8/8	BCY12	5/0	OAI5	1/8
ID6	9/6	6F25	13/-	12A28	5/8	301	20/9	EB41	4/6	EM80	7/8	PCC800	13/9	UBC81	7/-	W729	12/8	BCY33	6/0	OAI6	4/8
1PD1	4/6	6F26	5/3	12A27	9/9	302	18/8	EB81	2/3	EM81	7/8	PCF80	10/8	UBF80	5/8	X24	13/8	BCY34	4/8	OAI9	2/8
IPD9	6/8	6F28	14/3	12A27	9/9	305	16/8	EB81	6/8	EM85	11/8	PCF82	6/3	UB89	6/9	X41	10/0	BCY38	4/8	OAI0	1/9
IO6	6/9	6F29	10/-	12A27	9/9	305	16/8	EB81	6/8	EM85	11/8	PCF84	8/-	UBL21	9/-	X61	5/9	BCY39	4/8	OAI5	1/9
IH5GT	7/-	6F30	6/7	12A16	6/7	306	13/8	EB89	4/8	EM87	7/8	PCF86	12/9	UC92	5/8	X63	6/8	BCZ11	3/6	OAI20	1/8
IL4	2/8	6F32	3/-	12B28	5/9	807	11/9	EB91	5/6	EY51	7/8	PCF87	16/9	UC94	8/8	X64	12/8	BCZ10	4/7	OAI21	1/8
ILD6	6/9	6G06	15/-	12B17	6/7	956	2/-	EBF80	6/9	EY81	7/7	PCP200	13/3	UC95	7/8	X65	10/0	BCZ10	3/6	OAI21	8/6
ILN6	8/9	6H60T	8/-	12K1	17/7	1821	10/8	EBF83	8/8	EY83	11/8	PCP800	13/8	UCF90	8/3	X66	10/0	BCZ11	5/0	OAI11	13/6
IPN0T	7/9	6J50	4/9	12J50T	2/8	6763	10/8	EBF89	6/8	EY84	10/0	PCP801	7/7	UCI01	7/7	X109	25/8	BCZ15	3/6	OAZ20012	1/8
IP10	6/9	6J50T	4/9	12J50	10/8	6966	10/8	EBL1	10/8	EY85	6/8	PCP802	9/7	UCH42	12/8	X119	6/6	BCZ18	4/6	OAZ2010	10/8
IP11	6/8	6J76	4/9	12K74T	6/9	7476	14/8	EC53	12/8	EY87	6/6	PCP805	14/8	X198	6/6	X199	6/6	BCZ18	4/6	OAZ2010	10/8
1R5	5/6	6K7	6/6	12Q70T	5/8	A1834	20/8	EC54	10/8	EY88	8/8	PCP806	11/8	UC28	7/7	Z63	4/9	BD159	9/0	OAZ203	9/8
1R4	4/9	6K7G	2/2	12BA078	1/8	A2134	19/8	EC68	12/8	EZ35	5/8	PCP808	14/8	UC48	10/8	Z159	4/8	BFY50	4/8	OAZ204	9/8
1R5	4/8	6K7	4/8	12B07	5/8	A3042	15/8	EC88	12/8	EZ40	7/8	PCP82	7/3	UF41	10/8	Z389	16/8	BFY51	4/8	OAZ205	9/8
1T4	2/9	6K8A	4/8	12B47	4/8	AC/PEP	19/8	EC89	12/8	EZ41	8/8	PCP85	10/8	UF42	9/8	Z719	4/8	BFY52	4/8	OAZ206	9/8
1T4	2/9	6L1	18/8	12B47	4/8	AC/PEP	19/8	EC92	6/8	EZ42	8/8	PCP86	10/8	UF43	9/8	Z729	6/3	BFY54	5/0	OAZ207	10/8
2A7	12/8	6L80T	7/9	12B47	4/8	AC/PEP	19/8	ECC32	4/6	EZ43	8/8	PCL84	7/6	UF85	6/9	Z749	14/8	BFY55	5/0	OAZ208	10/8
2D13C	7/9	6L7	12/6	12K87	4/9	DD	19/8	ECC33	31/8	EZ90	4/3	PCL86	8/6	UF89	6/9	Z759	4/8	BFY63	4/8	OAZ213	7/8
2D21	6/6	6L12	5/6	12BQ78	1/8	AC/PEP	19/8	ECC34	29/8	FC4	12/8	PCL88	15/8	UL41	10/8	UL41	10/8	BFY70	7/8	OAZ224	16/8
2X2	4/9	6L18	8/8	1417	7/8	AC/PEP	19/8	ECC40	11/8	GW4500	6/8	PCL800	15/8	UL46	12/8	INT124	10/8	BFY81	8/8	OAI21	5/8
3A4	3/8	6L19	27/8	1487	15/8	AC/PEP	19/8	ECC41	3/8	GZ32	5/7	PCL801	15/8	UL47	6/8	PN615	6/6	BFY85	8/8	OAI22	5/8
3A5	10/8	6L20	6/8	18	14/8	AC/PEP	19/8	ECC42	6/8	GZ32	5/7	PCL802	15/8	UM80	6/8	2N966	10/6	BTX34	400	OC25	5/8
3B7	3/8	6L20D	9/8	19A05	4/8	AC/PEP	19/8	ECC43	4/8	GZ33	12/8	PEN45	7/7	URIC	10/8	2N1756	10/0	OC25	5/8	OC25	5/8
3D6	3/9	6N74T	6/8	19H1	40/8	ACTH110	10/8	ECC44	6/8	GZ34	10/8	PEN45DD	7/7	US7	7/8	2N147	17/7	BY100	3/6	OC26	5/8
3Q4	7/8	6P1	12/8	20D1	13/8	ACTP	19/8	ECC45	5/8	GZ37	14/8	UL4	16/8	UT8	14/8	2N2987	4/8	BY101	3/6	OC28	9/8
3Q64T	6/8	6P16	4/9	20J4	20/5	ARK3	7/8	ECC46	8/8	H30	3/8	PEN46	4/7	UT9	7/8	2N2989	4/3	BY102	3/6	OC29	9/8
3R4	5/8	6P25	12/8	20P2	14/8	ATP4	2/3	ECC47	8/8	H30C9	3/8	PEN45DD	7/7	UL12	4/9	2N2993	7/8	BY104	3/6	OC38	7/8
3Y4	8/8	6P28	15/8	20P3	12/8	AC/PEP	19/8	ECC48	3/8	H31C	4/8	PEN44	19/8	UY19	9/8	2N3053	6/8	BY126	3/6	OC36	7/8
4D1	3/9	6P28	25/8	20P1	17/6	AZ51	9/6	ECC49	8/8	H32	6/8	PEN44	19/8	UY21	9/8	2N3121	60/0	BY127	3/6	OC37	7/8
BR4C	10/8	6P12	6/8	20P3	18/8	AZ41	10/6	ECC50	12/8	HL41	3/9	PEN/DD	UY41	7/8	2N3703	3/9	BY220	30/0	OC41	10/8	
5T4G	5/6	6Q7G	6/8	20P4	18/8	B36	6/6	ECC51	27/8	HL41DD	19/8	4020	17/8	UY85	5/9	2N3709	4/9	BY210	30/0	OC42	19/8
5T4C	7/6	6Q7GT	8/8	20P5	20/8	B319	6/3	ECC52	6/8	HL42DD	19/8	PFZ00	11/9	UY10	9/8	2N3866	20/9	BY212	5/8	OC43	23/8
5Y30T	5/6	6R7G	7/7	25L60T	8/8	B719	6/8	ECC53	6/8	HLR2	10/8	PL36	9/6	UY14	7/8	2N3988	10/0	BY213	5/8	OC44	2/8
823	9/8	6R7G	7/7	25L60T	8/8	B719	6/8	ECC54	6/8	HLR2	10/8	PL36	9/6	UY15	15/8	2832	10/0	BY215	5/8	OC44PM	8/8
3Z4G	7/8	6R7AT	7/7	25Y41	8/8	BL63	10/8	ECC55	6/8	HYR2	16/8	PL81	9/8	UY17	5/8	AA129	3/8	BY218	35/0	OC45	2/8
6/30L2	12/8	6R7A	7/7	25Y40	6/7	CL33	18/8	ECC56	12/8	W3	5/8	PL81A	10/8	UY34	3/6	AA129	3/8	OG12E	4/8	OC46	8/8
6A8G	6/8	6R7C	6/8	25Z6	8/8	CV6	10/8	ECC57	12/8	IW4350	5/8	PL82	6/8	UY2	7/8	AA129	3/8	OG44	4/8	OC46	3/8
6AC7	3/8	6R7G	7/7	25Z6A	8/8	CV43	10/8	ECC58	5/8	IW4350B	5/8	PL83	6/8	UY25	13/8	AA129	3/8	OG44	4/8	OC46	3/8
6A9G	4/8	6R7H	7/7	30C1	6/8	CV21	12/8	ECC59	12/8	K78	34/8	PL84	6/8	UY26	13/8	AA129	3/8	OG44	4/8	OC46	3/8
6AJ5	8/8	6R7I	6/8	30C2	13/8	CV28	12/8	ECC60	12/8	K78	34/8	PL85	6/8	UY27	13/8	AA129	3/8	OG44	4/8	OC46	3/8
6AK5	5/8	6R7J	4/8	30C17	18/8	CV18	10/8	ECC61	8/8	K741	19/8	PL86	6/8	UY28	13/8	AA129	3/8	OG44	4/8	OC46	3/8
6AK5	5/8	6R7K	4/8	30C14	14/8	CY31	7/8	ECC62	8/8	K742	20/8	PL87	6/8	UY29	13/8	AA129	3/8	OG44	4/8	OC46	3/8
6AK6	6/8	6R7L	7/8	30F5	16/8	D1	1/3	ECC63	7/8	K761	12/8	PL88	6/8	UY30	13/8	AA129	3/8	OG44	4/8	OC46	3/8
6AK8	6/8	6R7M	4/8	30P1	13/9	D41	10/8	ECC64	8/8	K762	12/8	PL89	6/8	UY31	13/8	AA129	3/8	OG44	4/8	OC46	3/8
6AL6	2/8	6U4GT	12/8	30P2	15/8	D63	5/8	ECC65	9/8	K763	5/8	PL90	27/8	UY32	7/8	AA129	3/8	OG44	4/8	OC46	3/8
6AM6	3/8	6U7G	10/8	30P12	12/8	DAC32	7/8	ECC66	12/8	K764	12/8	PL91	27/8	UY33	7/8	AA129	3/8	OG44	4/8	OC46	3/8
6AQ5	5/8	6R7N	8/8	30P13	8/8	DAC91	8/8	ECC67	8/8	K765	12/8	PL92	15/8	UY34	13/8	AA129	3/8	OG44	4/8	OC46	3/8
6AR6	20/8	6X4	4/3	30P14	14/8	DAP96	6/8	ECC68	11/8	K788	34/8	PY31	6/8	UY49	11/9	AA129	3/8	OG44	4/8	OC46	3/8
6AT6	4/8	6X5GT	5/8	30L1	6/3	DOU90	10/8	ECC69	10/8	K7W61	12/8	PY32	10/8	UY52	5/8	AA129	3/8	OG44	4/8	OC46	3/8
6AU6	5/8	6Y6G	8/8	30L12	13/9	DU4	10/8	ECC70	30/8	K7W62	12/8	PY33	10/8	UY53	5/8	AA129	3/8	OG44	4/8	OC46	3/8
6AV6	5/8	6Y7H	12/8	30L17	16/8	DF33	7/9	ECC71	12/8	K7W63	6/8	PY34	10/8	UY54	5/8	AA129	3/8	OG44	4/8	OC46	3/8
6BBG	2/6	6Y81	12/8	30P18	16/8	DF91	2/9	ECC72	12/8	K7W64	6/8	PY35	10/8	UY55	5/8	AA129	3/8	OG44	4/8	OC46	3/8

**SUMS****plus****CIRCUITS****equals****UNDERSTANDING****PART 3****LESLIE MOORE****TRIGONOMETRY**

**F**OR a full understanding of circuit operation and relevant mathematical treatment, a few trigonometrical exercises should be dealt with, so a few simple definitions are required for further work. Consider the right angled triangle shown in Fig. 3.1.

Definitions of trigonometrical ratios are:—

$$\text{Sine of angle A} = \frac{a}{c} \text{ (written as } \sin A \text{).}$$

$$\text{Cosine of angle A} = \frac{b}{c} \text{ (written as } \cos A \text{).}$$

$$\text{Tangent of angle A} = \frac{a}{b} \text{ (written as } \tan A \text{).}$$

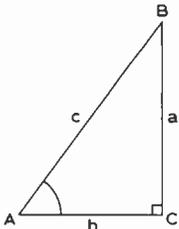


Fig. 3.1.

These relationships are valid only for right angled triangles. The sinusoidal waveforms discussed in the last article are in fact graphs of angle sines against angle, and as trigonometrical tables exist which give us angles for given sines, cosines and tangents, the above relationships are of importance.

Further information of use to us is given in Pythagoras' Theorem which states that for a right angled triangle:

$$c^2 = b^2 + a^2 \text{ (with reference to fig. 3.1.)}$$

e.g. when  $a = 4$ ,  $b = 3$ .

$$c^2 = 4^2 + 3^2 = 16 + 9 = 25$$

$$c = \sqrt{25} = 5$$

In this particular case:

$$\sin A = \frac{4}{5} = 0.8$$

$$\cos A = \frac{3}{5} = 0.6$$

$$\tan A = \frac{4}{3} = 1.33$$

The size of angle A can be found from any of the trigonometrical tables mentioned. In this case angle  $A = 53^\circ 8'$  (53 degrees 8 minutes).

These few facts are of use in determining out of phase angles in a.c. circuits as will be seen later.

**Sinusoidal waves**

The sine wave is the basic alternating waveform we use. Figure 3.2 shows one cycle of a waveform and indicated are several values of importance.

1. **R.M.S.** or root mean square value is the voltage/current normally quoted. This is the value which must be used for determining power in a circuit.
2. **Average value** is the mathematical average of the waveform obtained by dividing the waveform's bounded area by its base length.
3. **Peak value** which should be known when considering electronic circuitry so that "bottoming" of a transistor and exceeding diode peak-inverse voltage limits may be avoided.
4. **Peak-peak value**, twice the peak value, is used when determining useful amplifier gain graphically.

The base of a waveform can be graduated in units of time or angle. e.g. A frequency of 1Hz will have a waveform of 1 second periodic time. One complete cycle which occurs in the periodic time, can also be considered as  $360^\circ$  of angular rotation. From this consideration waveform amplitudes may be obtained for each angle using sinusoidal tables.

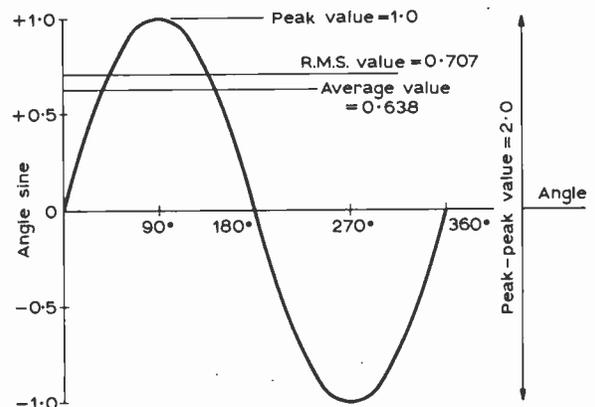


Fig. 3.2: Typical sine wave and four methods of defining its value.

## Reactive Components

Inductive and capacitive components have "reactance" in a.c. circuits and it is the reactance value which gives us most useful information.

Capacitance is the property which exists between two conducting surfaces held apart by an insulating material or "dielectric".

The value of capacitive reactance is determined by the formula:

$$X_C = \frac{1}{2\pi fC} \Omega$$

where  $f$  = frequency in Hz.

$C$  = capacitance in Farads.

$X_C$  = capacitive reactance in ohms.

A capacitor in an a.c. circuit has the effect of producing a current out of phase with the applied voltage. Figure 3.3 gives an example. Values of current and voltage can be calculated using Ohm's law, however, phase change should be taken into account.

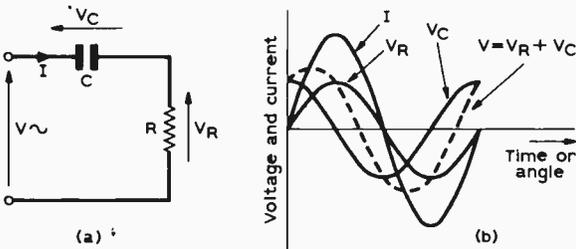


Fig. 3.3a: CR series circuit.  
3.3b: Voltage and current wave forms.

Only resistive components in an a.c. circuit will consume power, therefore they are known as "real" components. Reactive components, however, absorb no power and are known as "imaginary" components.

Vector representation utilises real and imaginary components as different axis on a graph, each current, voltage, or impedance being represented as a single straight line. Purely real components are drawn along the horizontal axis and purely reactive components are drawn along the vertical axis. Any component which is not purely reactive or resistive is drawn at a relevant angle to the horizontal plane.

The representative straight lines, known as vectors, are drawn to scale, e.g. 1 inch represents 1 volt in magnitude. It should be noted that all vectors should represent the same type of component value, rms values are normally used.

Figure 3.5 (a) shows a CR circuit with all voltages and current marked. A vector diagram for this circuit has been constructed in Fig. 3.5 (b).

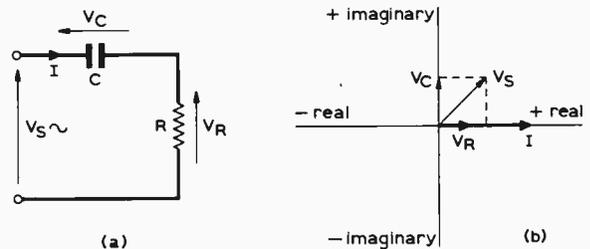


Fig. 3.5a: CR series circuit.  
3.5b: Vector diagram for CR circuit.

Inductance is due to the build up of magnetic fields around a coil of wire. An alternating current in the coil produces an alternating magnetic field which tries to oppose the flow of current. This opposition to current flow is termed inductive reactance and is determined from the formula:

$$X_L = 2\pi fL \Omega$$

where  $L$  is the inductance in henries

$X_L$  is the inductive reactance in ohms.

Inductance in an a.c. circuit gives a phase shift in the opposite direction to that of capacitance. This is demonstrated in Fig. 3.4.

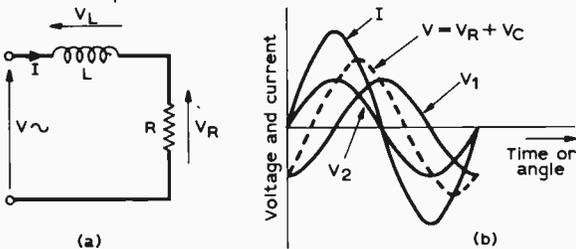


Fig. 3.4a: LR series circuit.  
3.4b: Voltage and current waveforms.

Supply current to a series circuit is common to both R and C components and therefore taken as reference vector. Resistive volt drops are in phase with current, hence  $V_R$  is a real component. Voltage across a capacitor is out of phase with current by  $90^\circ$ , and as current reaches a maximum value  $90^\circ$  after the voltage, voltage is shown on the plus reactive scale.

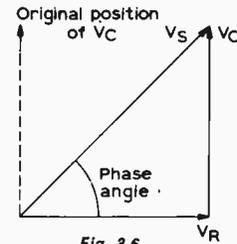


Fig. 3.6.

Supply voltage to the circuit can now be determined by adding resistive and reactive volt drops vectorially.

The reconstruction of the voltage vectors in Fig. 3.6 and as can easily be seen, supply voltage and its angle with supply current can be measured.

Having drawn the diagram, from comparison with the introduction of this article, we can determine a method for calculating phase angle and supply voltage.

Tangent of the phase angle is given by the ratio

$$\frac{V_C}{V_R}, \text{ and by Ohm's law:}$$

$$V_C = I_S X_C \text{ and } V_R = I_S R$$

Tangent of phase angle (often written as  $\tan \phi$ ) is given by:

$$\tan \phi = \frac{I_S X_C}{I_S R} = \frac{X_C}{R}$$


Phase angle can be obtained accurately directly from trigonometrical tables.

## Calculation of phase angle

Phase angle is determined from resistive and reactive values in a circuit. This can be most easily demonstrated by representing voltage drops by the method of vectors.

# DISCOSOUND

## DJ DISCO-AMP

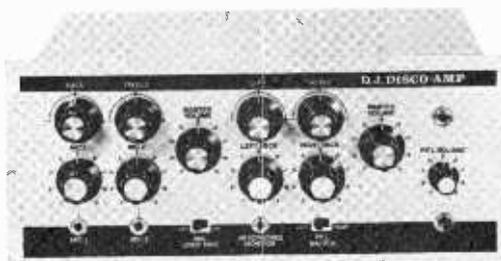

The DJ Disco-amp has been designed specifically for use with discotheques and has many exclusive features not normally found on P.A. amplifiers. The unit will be of use to the professional D.J. as well as in clubs and mobile discotheques.

The pre-amp section features independent inputs and volume controls for two mics with separate bass, treble and master volume, plus two independent inputs and volume controls for turntables, again with separate bass, treble and master volume controls.

A complete Pre-fade listen (P.F.L.) cueing monitor section is also featured with separate input for headphones (either stereo or mono) with an independent volume control for headphone monitoring, and a P.F.L. switch, so that either turntable can be monitored for accurate cueing up of records. A mic over-ride switch is also added which cuts the music volume by half so that mic announcements may be made over the music without altering the volume controls.

The power amplifier section has an output of 70 watts R.M.S. into 8 ohms and has elaborate protection against thermal, short or open circuit. The unit is designed for panel mounting.

### SPECIFICATION

Output power	70 watts R.M.S. $\pm$ 1db at 8 ohms.
Frequency response	30-20,000 Hz $\pm$ 3 db.
Harmonic distortion	Less than 1% at full output.
Signal/noise ratio	Better than - 65db.
Speaker impedance	8-16 ohms.
HeadPhone impedance	8-16 ohms.
Bass control	Variable 20 db at 100 Hz.
Treble control	Variable 20db at 10 kHz.
Inputs:	Mic 1 & 2 5 mV at 50 K ohms.
turntable	1 & 2 100mV at 1 meg ohm.


50 ohm or 600 ohm mic inputs may be ordered at extra cost.  
Size: Front Panel 16 $\frac{1}{2}$ " x 7". Cut out 15 $\frac{1}{2}$ " x 6". Fuses: A.C. 1.5 amp (B.S.) mounted on back panel.

**PRICE £85.0.0 inc. P & P.**
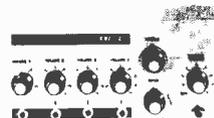
## DISCOSOUND PRE-4

This is a four channel fully mixable pre-amp, with separate treble, bass and master volume controls, and is completely self powered. All four inputs are by standard jack socket on the front panel with the addition of inputs 3 and 4 being duplicated on the back panel, with two paralleled outputs also featured for versatility in use.


Frequency response: 30-20,000 Hz  $\pm$  3db.  
Signal/Noise Ratio: -65db.  
Size: front panel 12 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " cut out required 11 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ ".  
Completely built and tested.



**PRICE £18.0.0 inc. P & P.**

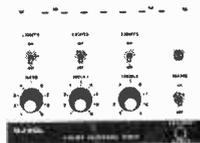
## DJ 30L PSYCHEDELIC LIGHT CONTROL UNIT

3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation.  
Completely built and tested



**PRICE £37.10.0 inc. P & P.**

## DJ 70S INTEGRATED MIXER-AMPLIFIER

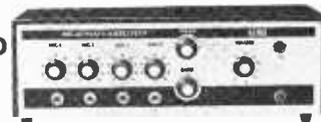

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls. Plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70 watts R.M.S.) a frequency response (30-20,000 Hz  $\pm$  3db) that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs etc., or anywhere that high quality high output is required. Size: 15 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ ".

**PRICE £55.0.0 inc. P & P.**

Also available DJ105S 30 watt P.A. Amplifier. Similar specification to above.

**PRICE £35.0.0 inc. P & P.**

## DISCOSOUND 70 MAIN AMPLIFIER

A 70 watts RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response: 20-20,000 Hz  $\pm$  2db. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound PRE-4, or can be used with any other high quality pre-amp control unit. Size: 7" x 9" x 6".  
Completely built and tested on steel Chassis.

**PRICE £30.0.0 inc. P & P.**

For full details of these and all Discosound Products write direct to:—

**DISCOSOUND, 122 BALLS POND ROAD, LONDON, N.1. Tel: 01-254 5779**

Full money back guarantee if returned within 10 days.  
All Discosound Products are guaranteed for 12 months.  
Demonstrations given at any time.

**Fully guaranteed  
Individually packed  
VALVES**

Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves, U.K. Orders up to 10/-, 1/-; 10/- to £1 2/-; over £1, 2/- per £1; over £3 post free. C.O.D. 4/- extra

**TRANSISTORS, ZENER DIODES etc.**



**ALL valves guaranteed**

CY21	7/-	EF36	3/6	OB2	7/6	OA5	2/6	OC29	16/-	OC172	7/6	3FR5	6/6	AF118	10/-	CR83/20	10/6	6P25	11/-	19AQ5	7/9	5933	22/6
DAF96	7/9	EF37A	7/-	PABC80	7/6	OA10	6/6	OC35	8/6	OC200	6/6	3N128	17/8	AF139	10/-	CR83/30	11/6	68A7	7/6	19G3	7/9	6057	10/-
DF96	7/6	EF39	6/6	PC97	9/-	OA70	2/-	OC38	8/6	OC201	7/6	3N139	35/6	AF178	12/6	CR82/025	15/-	68A7GT	6/6	19G6	20/-	6060	7/6
DK96	7/6	EF40	10/-	PC900	9/6	OA71	2/-	OC44	4/6	OC206	10/-	3N140	19/6	AFY19	22/6			68C7	13/-	19H4	85/-	6064	7/6
DL92	6/6	EF41	12/6	PC984	6/6	OA79	1/6	OC45	2/6	IN21	3/6	3N154	19/-	ASV26	5/6	CR83/40	12/6	68C7GT	6/6	20P4	17/-	6065	13/6
DL94	6/6	EF80	5/6	PCF89	9/6	OA81	1/6	OC70	2/6	IN21B	5/6	3N159	29/6	3AW19	5/6	GET103	4/6	68G7	6/-	25L6GT	7/3	6080	27/6
DM70	6/6	EF83	9/7	PC189	11/6	OA200	1/6	OC71	2/6	IN25	1/6	6FR5	9/6	BC107	3/6	GET116	8/-	68H7	7/6	30C15	15/-	6146	28/-
DM71	7/6	EF85	6/6	PC890	15/-	OA210	7/6	OC73	11/-	IN70	4/6	12P80	14/9	BC108	4/6	BD918	5/8	68J3GT	6/6	30C17	16/-	8020	35/-
DY66	6/6	EF86	6/6	PCF82	9/6	OA211	9/6	OC75	4/6	IN70-7257/8	7/6	28303	10/-	BCY10	9/6	SD928	6/6	68K7	7/6	30C18	15/-	9001	3/-
DY87	6/6	EF89	5/6	PCF84	9/6	OA2200	11/6	OC78	5/6	IN746A	4/6	40584	27/6	BCY12	7/6	SD948	6/6	68L7GT	6/6	30C19	16/-	9002	4/6
DY802	9/9	EF91	3/6	PCF82	9/6	OA2201	10/-	OC81	4/6	series	4/6	40585	27/6	BFY51	4/6	SD968	7/8	68N7GT	6/6	30P11	18/-	9003	10/-
E88CC01		EF92	7/6	PCF86	10/6	OA2202	10/-	OC82	5/6	OC81D	4/6	40586	27/6	BFY52	4/6	SD968	7/8	68Q7	7/9	30P12	18/6	9004	2/6
		EF95	5/6	PCF200	15/6	OA2206	4/6	OC82DM	5/6	IN823A	25/6	40668	27/6	BB05	7/6	V405A	7/9	68Q7GT	7/9	30P13	9/3	9006	2/6
		EF96	5/6	PCF201	15/6	OA2208	4/6	OC82	5/6	IZMT10	6/6	40669	29/6	BB1	9/6	Z Range		68Q7GT	7/9	30P14	15/6		
		EF183	9/6	PCF201	15/6	OA2213	6/6	OC83	4/6	IZT15	12/6	AC127	4/6	BU100	35/-	3/6 ca.		68Q7GT	7/9	30P15	17/-	C.R. Tubes	
		EF184	7/6	PCF801	9/6	OA2213	6/6	OC83B	3/6	IZT15	12/6	AC128	6/6	BY213	5/6	Z2A range		68Q7GT	7/9	30P16	17/-	VCR81	22/6
		EF802	9/6	PCF802	9/6	OA2225	10/-	OC84	4/6	2N1306	6/6	AC176	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF83	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF84	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF85	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF86	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF87	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF88	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF89	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF90	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF91	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF92	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF93	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF94	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF95	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EF96	6/6	PCF806	14/6	OC16	15/-	OC122	10/-	2N1307	6/6	AC178	7/6	BYZ16	15/6	Z3B range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL85	8/6	PCL83	13/-	OC28	5/6	OC140	8/6	2N3053	6/6	AD149	11/6	CR81/20	9/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL86	8/6	PCL84	8/6	OC28	5/6	OC140	8/6	2N3054	12/6	AD161	7/6	CR81/30	10/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL90	6/6	PCL85	9/6	OC28	5/6	OC170	5/6	2N3055	15/6	AD162	7/6	CR81/35	11/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6	OC171	6/6	P100	12/6	AF117	4/6	CR81/40	12/6	ZL range		68Q7GT	7/9	30P19	14/-	VCR817B55	
		EL96	7/6	PCL86	9/6	OC28	5/6																

It is now also obvious that supply voltage magnitude can be determined using Pythagoras' theorem.

$$\text{then } V_S^2 = V_C^2 + V_R^2$$

$$\text{therefore } V_S^2 = I_S^2 X_C^2 + I_S^2 R^2$$

$$\text{therefore } V_S = \sqrt{I_S^2 X_C^2 + I_S^2 R^2} \\ = I_S \sqrt{X_C^2 + R^2}$$

The term  $\sqrt{X_C^2 + R^2}$  is the circuit impedance,  $Z$ .

It seems then, that by using a few simple calculations useful information may be obtained for resistive-reactive networks. Unfortunately not all circuits are quite so simple to work with and other techniques have been utilised to handle them.

## j Notation

Complicated vector diagrams can be solved by a series of small calculations which take up time.

j notation can be used to represent vectors mathematically and so eliminate some of the more tedious work.

The vector diagram axis of real and imaginary terms is used. Positive and negative real axis are graduated with real numbers whereas positive and negative imaginary axis terms are prefixed with +j and -j terms.

Although j has the meaning of a vector of unity magnitude at 90° from the reference, j also has the numerical value of being the square root of -1.

The following table lists vector positions in terms of j.

Angle	0° or 360°	90°	180°	270° or -90°
j notation	(j) <sup>0</sup> =1 or j <sup>4</sup> =1	j	j <sup>2</sup> =-1	j <sup>3</sup> =-j

Any vector lying at some angle between axis has two components, real and imaginary. Figure 3.7 shows a vector which can be written as 2 + j1.

There are a few rules which should be obeyed when manipulating j items, but these are best demonstrated in an example.

Figure 3.8 shows a parallel circuit. Circuit impedance in j items is given by:—

$$Z = \frac{-jX_C(R + jX_L)}{R - jX_C + jX_L} \\ = \frac{X_C X_L - jX_C R}{R + j(X_L - X_C)}$$

If  $R = 10 \Omega$ ,  $X_L = 5 \Omega$ ,  $X_C = 10 \Omega$

$$\text{then } Z = \frac{50 - j50}{10 + j5}$$

This term is rather cumbersome, so to produce an impedance term which can be easily handled the lower term of the fraction (or denominator) must be made into a real number. This is done simply by multiplying both numerator and denominator by a term which contains the denominator's real part and the opposite sign of its imaginary part.

$$Z = \frac{50 - j50}{10 + j5} \cdot \frac{10 - j5}{10 - j5} \\ = \frac{500 - j250 - j500 - 250}{100 - j50 + 50 + 25} \\ = \frac{250 - j750}{125} \\ = 2 - j6 \Omega$$

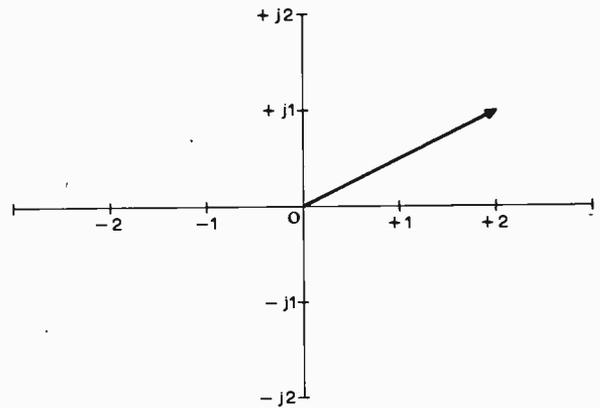


Fig. 3.7: Relating vectors to j notation.

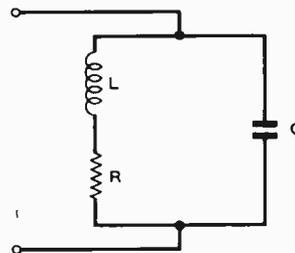


Fig. 3.8: Parallel tuned circuit to demonstrate use of j notation.

## Polar Representation

A further method of representing vectors can often prove useful, especially when vectors are to be multiplied or divided. This involves representing each vector by its magnitude and angle.

e.g. (I)  $A \angle X$ ; (II)  $B \angle Y$ ; (III)  $C \angle Z$

where A, B and C are the vector magnitudes (or lengths) and X, Y and Z are the vectors' angles.

Rules for multiplying are:

Multiply magnitudes and add angles.

Rules for dividing are:

Divide magnitudes and subtract angles. (It should be noted that we cannot add and subtract vectors when represented by their polar forms.)

Conversions from j notation to polar form are often made necessary. Suppose the term  $D + jE$  is to be converted to  $A \angle X$ . Using rules discussed previously,  $A^2 = D^2 + E^2$ .

$$A = \sqrt{D^2 + E^2}$$

$\tan X = \frac{E}{D}$ , therefore angle X, can be obtained from

trigonometrical tables.

## Applications

Numerous applications for this type of calculation include the determination of lower and upper half power points of amplifiers, calculations involving filter networks and attenuators, determination of oscillator operating frequency and accurate measuring bridge calculations.

Application of some of the theorems mentioned here will be discussed later in the series.

**TO BE CONTINUED**

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

**T**HE FIRST report this month is another excellent one from **Geoffrey Gilham**, ISWL G-10056, of London S.E.12. Geoff's equipment includes an Eddystone EC10 and a TRIO 9R59D.

4820 *HRVC*, Honduras with classical music at 0215.

4940 *R. Yaracuy*, Venezuela with Ident. at 0227

4960 *R. Sucre*, Venezuela with news at 0200

5020 *Trans. Caldas*, Colombia at 0704

9560 *R. Australia* with DX News at 0730

11650 *R. Pakistan*, Dacca at 1500

11920 *Abidjan*, Ivory Coast with Eng. news at 1830

15105 *BBC*, Ascension Island relay, Ident. at 0915

15365 *RNE*, Canary Islands with Ident. at 0105

**Chris Stacey** of Tunbridge Wells has a Lafayette HA-700 with a Joystick antenna and A.T.U. and he sent me the following log:

7295 *Athens*, Greece at 1412-1445

7306 *Polish Pathfinders* at 1530-1555

9009 *Israel Broadcasting Auth.* at 2045-2127

17810 *R. Nederland*, Bonaire in Dutch at 1955-030

**Roy Patrick** of Derby has an impressive line-up of equipment including an Eddystone 840, Hallcrafters S×24, Codar Preselector and various aerials and seems to have been concentrating on Middle-Eastern stations:

7155 *R. Amman*, Jordan in English at 2015

9667 *R. Damascus*, Syria in English at 2030-2100

17820 *R. Ankara*, Turkey in English at 1415

Roy also reports that *Radio Iran* will have a 250kW shortwave transmitter on the air very soon.

**T. R. McKirdy**, ISWL GM-13209, of Hamilton used a TRIO 9R59D, RF Preselector and a 66ft dipole at 18ft to send in a log which included:

5975 *VOA*, Okinawa with Science of Medicine at 0240

6050 *HCJB*, Ecuador with Religious Service at 0930

9630 *CBC*, Canada with Ident, in English at 1615

11720 *VOA Tangier* with 'Jazz Hour' at 2340

15040 *R. Peking* with news in English at 0000

21535 *NHK*, Japan in English at 0820.

**Ray Hounslow** of Carlton near Bedford has a Hallcrafters S-76 and sent in the following items:

The *Windward Islands Broadcasting Service (WIBS)* transmits with a power of 5kW at 0245-0315 on a frequency of 11970. The QSL card is a bit drab but it is worth the effort.

The *Broadcasting Service of the Kingdom of Saudi Arabia* uses 11855 at 0615-0645 with a power of 50kW.

**John W. Smith** of Anstruther, Fife has, once again, made good use of his Eddystone 840C and Joystick to hear several interesting stations:

Times  
in GMT

Frequencies  
in kHz

## THE BROADCAST BANDS

Malcolm Connah

6255 *Schulungssender des Osterreicheschen Bundesheeres* at 1830-1900

15080 *All India Radio* at 1850

15155 *R. Dif. de Sao Paulo*, Brazil at 2145

15155 *ELWA*, Liberia sign off at 2230

15160 *R. Ankara*, Turkey at 2210

15370 *R. Tamois and Tupi*, Brazil (33443) at 2200

21455 *Voice of Nigeria* (44444) at 0705

John also reports that a new QSL card will be issued to mark the 25th anniversary of the International Service of *CBC*, Canada.

### Africa

**Malagasy Republic:** According to a recent schedule from the IV network of *R.T.V. Malagasy* there is a programme in English on Tuesdays, Thursdays and Saturdays and in French on Mondays at 1700-1715. The programme, titled "QSL Service," is followed by a musical programme until close down at 1730 on 17730 with a power of 100kW.

### Asia

**Afghanistan:** *Radio Afghanistan*, Kabul broadcasts in German at 1730 and English at 1800 on new frequencies of 9530 and 11790.

**Ceylon:** The Commercial Service of *Radio Ceylon* in English now starts at 0100 on frequencies of 9720 and 15120.

**Indonesia:** The *Voice of Indonesia* is now using the frequency of 11710 and broadcasts news in English to the United Kingdom at 1915.

**Philippines:** *Radio Veritas*, Manila is broadcasting test transmissions on 15170 and 11830 from 0530 to 0630 and from 1100 to 1400.

### South America

**British Honduras:** *Radio Belize* has increased power from one to five kilowatts on its shortwave channel of 3300 and broadcasts until close down at 0600.

**Ecuador:** A note received from *HCJB*, Quito says that in order to receive a QSL from them the following details *must* be given:— date, time, frequency in MHz (only 5kHz variance is allowable and metre band only is not acceptable), name of programme and items that would identify the programme. If an airmail reply is required three International Reply Coupons must be enclosed.

**El Salvador:** *YSS, Radio Nacional*, El Salvador is to broadcast in English and French. The programmes will be transmitted Monday to Saturday at 0300-0330 and on Sunday at 0030-0100 and consist of news items in Spanish, French and English. The frequent cems used will be 5980 and 9555.

All reports, preferably in frequency order, should arrive at 58 Kensington Gardens, Cranbrook, Ilford, Essex by the 17th of each month.

# THE AMATEUR BANDS

## David Gibson, G3JDG

**E**VEN listeners with cloth ears must have had themselves a ball this past month. All bands from 1.8MHz to 144MHz have been humming and, judging by the logs received, plus the remarks accompanying them, the resultant happy lug-holes are in a state of high jubilation.

**L. Bunnewell** (Norwich) claims that there is no achievement in receiving DX if you use a commercial receiver, and that it is the receiver and not the operator which should get due credit. (How many photographers do you know who make their own cameras, OM?) Any readers agree with this, or have any other ideas?

**D. Henbry** (Sussex), KW77, 7ft. vertical at 30ft. is back in the r.f. saddle again and sends in a fantastic all-band log. Down among the spurious and curious on 80 metres his ears beheld the wonders of: CN8HL, CR4BC, CR4BB, CT2AP, HC2GG, HK3WO, HP1JC, HS5ABD, KZ5AE, KZ5NR, MP4BFO, TI9CF (Cocos Is.), VP5NB, VP5TH, VP7NY, VS6DO, W5JV, W9FIU/KS4, WA1AIM/VO2, XE1CE, XE1KS, YV4UA, ZM1BAZ, ZM2GL, ZL2BCG, ZL4NH, 3A2MJC, 4X4UF, 9L1RP, 9Y4MM. (Cor! It's better than my log for 20 metres.)

On 40 metres David logged: CE3RR, CO2DC, CO2FA, CP1GN, EA8BZ, HBØLL, HI7CAF, HK1BWC, HT1HF, KZ5NR, OA4NLA, PY7PYQ, PZ1AH, TF5TP, TG8IA, TI2CAP, VP2VI, VP9GE, XE1BR, YV4CH, ZL3JC, 4X4KT.

**D. Isaac** (S. Wales), 9R-59DE, 60ft. end fed, caught this bunch red-handed on 80 as they crossed the Welsh border: CT2AT, HC2GG, HK3WO, K3UZE, K5KLA, K8UDI, KP4CL, OA4NLA, PY7VIZ, VE3TC, W2JKI, W3GM, W4BVV, W5IOU, W5QWF, XE1CE, XE2IH, YV4UA, YV5TS, ZL4NH, ZM3GQ, ZM3LE, 4X4UF.

**J. Moore** (Leicester), CR100/2, 60ft. end fed, reports happenings on the lower frequencies. 160—EI4AN, GI3TLT, GM3LIB, GM3NVU. 80—CT2AK, HV3SJ, K1BXL, KP4CL, VO1DE, W1CBU, WA1JFX, W2NIN, XE1KS, YV5BTS, ZC4CV. 40—K2BQI, PY7BFN, W2IUY, WA2BVU, W3ZKH/P/3, ZM3RK, 6W8DY. All this lot on s.s.b.

An urgent message for the chemistry master at Sir Thomas Rich's School, Gloucester. Messrs. **Anderson, Davies** and **Apperley** are holding sneaky listening sessions on your HRO plus 80ft. end fed. On 15 metres this trio logged: CN8HD, EP2EX, G3CGD, VE3ACD, W6ARJ, W6NWU, W8LIC, W9KHW, YA1HD, YT2FVW, 3Z6AAT, 4X4DK, 4Z4BG, 9H1BI. Well done lads—back to the tuck shop.

**D. Robbins** (Warks), CR70A, 60ft end fed, got these on s.s.b with the help of his b.f.o.: AX4PX, CN8HD, CR4BB, ET3USA, G3RTU/4X4, IS1LMN, JA6JNQ, JA6KCY, JX3MN, LU9DZ, PY7AF, VS6DA, VS6BE, ZC4HS, ZD9BM (Tristan da Cunha), ZL3BJ, ZS6AO, 5H3JR, 5H3KJ/A (Zanzibar), 9E3USA, 9G1GD. All these on 15 metres. On 20 s.s.b.—AX6RU, CE6DP, CP1GT, FP8CSV, HI8UD, HV3SJ (Vatican), JX3MN, JX4DN, JW3XK, KL7EBK, KP4FS, KZ5EK, LU1DM, DU6DLN, LU8AFB, LU9DDH, MP4QBK,

PY4ATG, PY6AG, PZ1AP, TI9CF, TR8DG, VK3MO, VP2AA, VP2GLE, YV1ABO, ZP5AA, 4U1ITU, 5Z4LW, 8R1U, 9L1RP, 9Y4MM, 9Y4PL.

**T. Maxwell** (Lanarkshire), CR70A, 18ft. end fed sent a thin slip of paper with a fat log. Fifteen s.s.b.: CT1GD, EA6BJ, ET3REL, HPØLL, HR2HHP, JAØENB, JA3TXN, JA8AHH, JR1DDQ, JW1CI, KZ5MP, OD5GD, PAØWEJ/SM/MM, SVØWP, VE5MW, VE6AJS, WB6UZF, YO9CN, ZM2NY, ZS6RO, 4U1ITU, 4X4RW, 6Y5ET, 7P8AB, 9Q5NW, 9U5CR.

**K. Webb** (Bucks), CR45, 12ft. whip antenna, says Vive la t.r.f. and promptly shows what can be heard. His log for 15 reads: AX3AKP, EA6BN, EA8FS, FP8CT, HR2WTA, JX3MN, KL7YM, KP4BBK, KR6HS, KV4GN, LU8FLO, PY2PA, SV1AR, VE1FN, VEØNA, VP2VI, VK3ZL.

**A. Markham** (Essex), 9R-59DE, 33ft. end fed, received these on 10 metres: AX3ACR, AX6BDO, AX6NM, HK5NE, JA1LBR, KH6QR, KZ5KZ, VE6UM, YV5CIL, ZE3JO, ZE4JG, 6Y5GB, 9J2PU, 9Q5RH.

**A. Crooks** (Leicester), RA1, PR30, 45ft. end fed logged FM7WR (Martinique) on 10 metres a.m. On s.s.b. Andy logged: CE3RR, CE8AA, CR7GC, CR7IK, EP2BI, HR1EMM, K6QVT, KP4ZC, LU2DAW, MP4QBK, OA4J, PY3APH, PY8JL, RA1AKZ (U.S.S.R.), SV1DA, VE2DMG, VE6AJD, VE6ANO, VP7DL, VP8KD, VP8KL, VU2OLK, W5RMC, W6GU, W7KPK, WØDQ, WA6FOY, WA6UAG, WB6SMG, XW8BP, ZE1BS, ZP5OJ, 5N2AAF, 7Q7LZ, 9G1GD, 9H1BX, 9J2WS.

**J. Stevenson** (Surrey) is working on a collapsible 3-element 2 metre beam which can be dragged off the roof and hidden under the bed when the landlord is in. Mind how you turn over in bed OM, or you'll get more dB's than you bargained for. John has constructed the CQ-2 with certain modifications. His present antenna is a simple dipole made from 14 s.w.g. wire and he reports many fairly local signals. His main criticism of 2 metres is the overall standard of modulation. "Class C a.f. stages don't do much for R5 copy", he says. (Down you mutinous G8's.)

**G. Richards** (Isle of Wight) says, "Tell L. Coombs that I have declared war on him". Glyn has a 4 over 4 slot-fed yagi, JXK converter into a Mohican receiver tuning 28-30MHz. Stations in the 70-110 mile range received on 144MHz include—GW8ASA, GW3MFY, G2JF, G2DRT. From further afield—G3EGK (Leicester) and G6CW (Nottingham) both on s.s.b.

**N. Richardson** (Bucks), 5-element yagi (hand-rotated), Garex converter, PR30 plus CR70A as tuneable i.f. Nicholas reports some good openings and his log includes signals from—G2DQI, G2MR, G2BVV, G3HRH, G3KPB, G3MJW, G3NJV, G3RJC, G3SLJ, G8LT, G8ASR/A, G8BBB, G8BSH, G8BIC/P, G8CAF, G8CLX.

Goings on in May include: May 2nd. - 3rd., 144MHz contest; 10th., Ealing and District A.R. Mobile Rally at Hanwell, London, W. 7.; 17th. D/F event at Grimsby; 17th., Northern Mobile Rally; 30th., and 31st., 70cm. contest; June 6th., and 7th., National Field Day.

Please remember that logs must reach me by the 18th. of the month and should be in alphabetical order. Several logs received last month arrived on the 20th. and were too late to be included. Summer is aerial weather so how about trying a new aerial this year and let me know how you get on?

# AERIALS FOR MOBILES

F. JUDD G2BCX

Continued from last month

## Matching the Aerial to the Transmitter

One of the problems which many mobile operators find difficult to overcome is that of matching the aerial to the transmitter which is most important if maximum power is to be transferred into the aerial. As all loaded aerials for the h.f. bands are resonant to a quarter-wavelength they are current fed. A ten watt transmitter should put at least 0.3 to 0.4A into the aerial. However, this is only

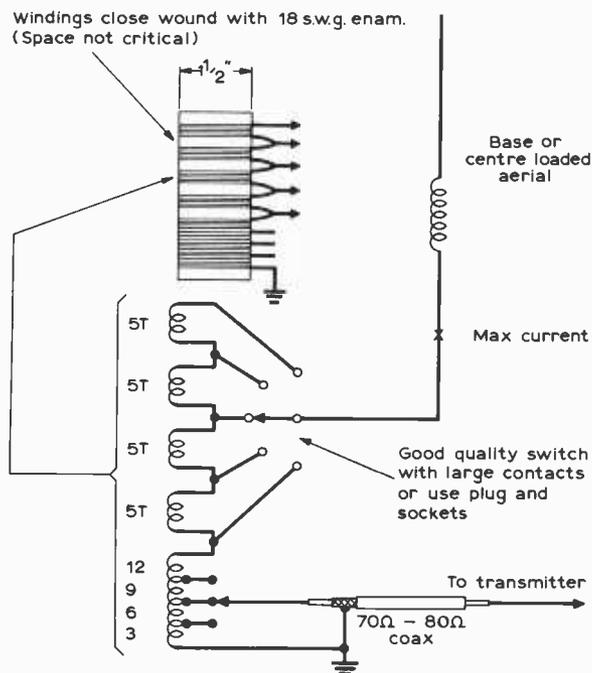


Fig. 11: Wide range matching system.

a rough guide and the aerial resonance should be adjusted until no further increase in aerial current can be obtained. There is also the problem of maintaining resonance over the whole of the band and which is closely bound with matching. The transmitter output must in the first instance be of low impedance, i.e., from a pi-network or link coil coupling. From here the aerial can be fed by a co-axial cable of 70 to 80Ω impedance. Unfortunately the feed impedance of loaded aerials is usually much lower than that of a full quarter-wave aerial and because of their low efficiency accurate matching is important.

A simple method is that shown in Fig. 11 which can be adapted to all the h.f. bands. The method provides not only accurate matching but also allows the aerial to be set to resonance over the band. The total amount of inductance in series with the feed to the aerial itself must be sufficient to maintain resonance at the lowest working frequency. As the sections of inductance are switched out the aerial will resonate at higher frequencies. Some operators use a coil with a sliding contact but these are difficult to obtain and/or make. Normally a mobile operator will work over a fairly narrow frequency band to avoid constant retuning of the aerial. Another method of tuning the aerial so as to be able to cover the whole band is to use a ferrite slug as illustrated in Fig. 12. The aerial and the matching inductance should be adjusted to resonate at the high frequency end of the band. Resonance at the lower frequencies is obtained by sliding the ferrite further into the coil. This method should only be used for the lower frequency bands of 1.8 and 3.5MHz.

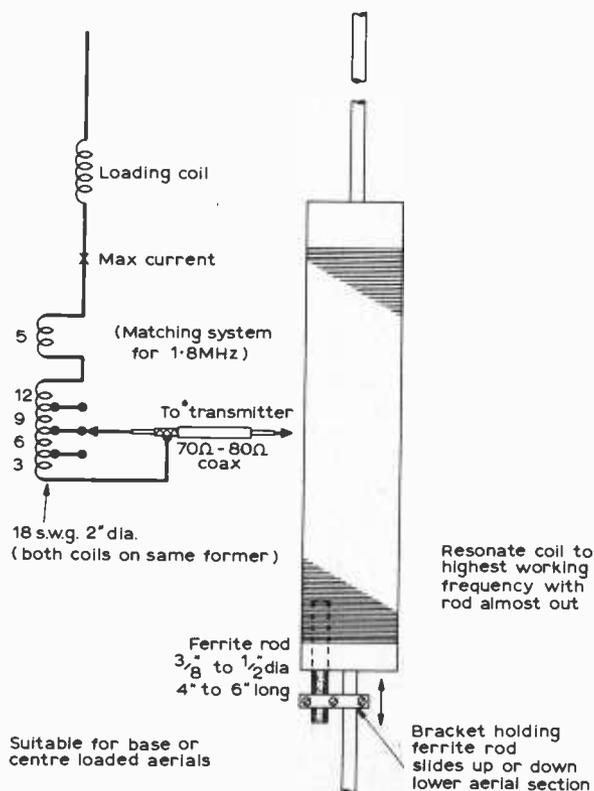


Fig. 12: Ferrite rod system for the i.f. bands

## Capacity Hats

The capacity hat is rarely used now for low frequency aerials since it would have to be fairly large to produce any worthwhile reduction in coil inductance. Capacitive elements above the loading coil can, however, be used to tune the aerial to resonance over an appreciable proportion of the low frequency bands 1.8 and 3.5MHz. A fairly simple arrangement is shown in Fig. 13 and consists of two rods, one fixed and one moveable. Each rod should be about 12 in. long and  $\frac{1}{4}$  in. diameter brass or copper. When the two rods are in line the capacity is minimum and as they are spread apart to form a 'V' the capacity increases. Both rods are in contact with the whip section above the coil and with each other.

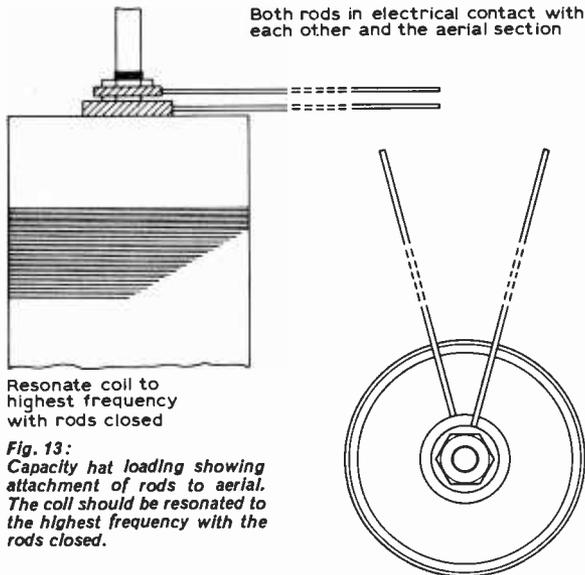


Fig. 13: Capacity hat loading showing attachment of rods to aerial. The coil should be resonated to the highest frequency with the rods closed.

## Ground Wave Field Strength at 1.8MHz

The most popular amateur band for mobile operation is 1.8MHz on which propagation is predominantly ground wave. Field strength is therefore very much influenced by the ground over which the wave travels and particularly by built up areas. In open flat country transmitting ranges of up to 100 miles are possible but in rolling country this can soon be reduced to 30 miles or so. In heavily built up areas the range may well be limited to 10 miles or less. This is assuming a reasonably

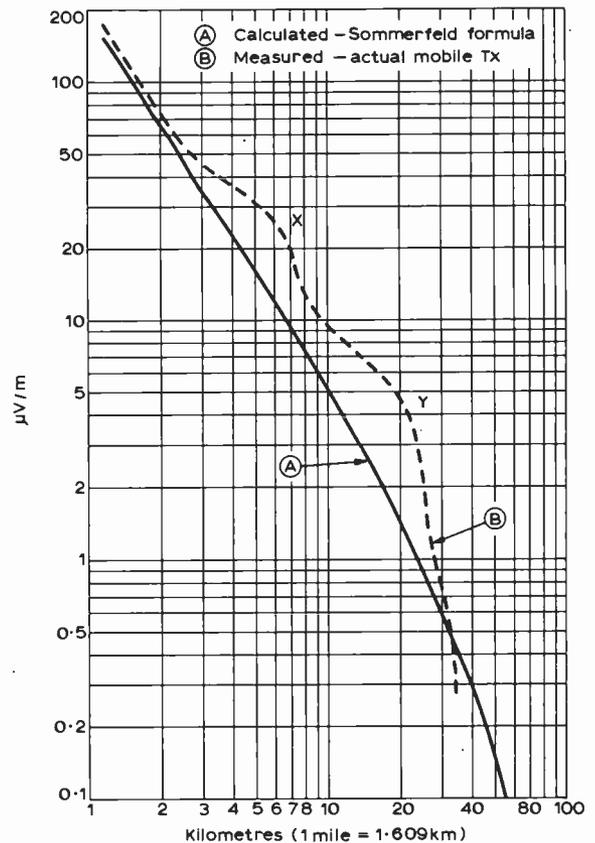


Fig. 14: Ground wave measurements on 1.8MHz.

efficient mobile aerial, a transmitter input power of around 10 watts and that the receiving station also has a good aerial. Mobile to mobile ranges will normally be much less. A few years ago the writer carried out a series of field strength/distance checks with a 1.8MHz mobile transmitter (1). These were made over fairly flat country and compared favourably with field strength/distance calculated by the Sommerfeld formula.

The calculated and measured field strengths/distance are given in Fig. 14. The small increases in measured signal strength at X and Y were due to an increase in the height of the ground over which the mobile station was travelling.

(1) *Ground Wave Propagation at 1.8MHz* by F. C. Judd, A.Inst.E. R.S.G.B. Bulletin, December, 1960.

### P.W. BINDERS

Preserve your copies of Practical Wireless. Don't let them become torn and dirty—buy a hard-cover binder for 14s. 6d. from:

Binding Department,  
IPC Magazines Limited,  
Tower House,  
Southampton Street,  
London, W.C.2.

Price includes post and packing

### P.W. INDEX

The Index to Volume 44 (May 1968 to April 1969) is now available, price 1s. 6d. Copies may be obtained from:

P.W. Index Department,  
IPC Magazines Limited,  
Carlton House,  
Great Queen Street,  
London, W.C.2.

Price includes post and packing

# A LIGHT BEAM TELEPHONE

J. THORNTON LAWRENCE

The light beam telephone provides a convenient method of short range point-to-point communication, without the use of wires, which does not involve transmission and reception on frequencies requiring a Post and Telecommunications Licence.

Basically, the transmitter consists of a lamp which is amplitude (brightness) modulated by the voice signal to be transmitted. The lamp is mounted in an optical system, so as to produce a parallel beam of light, which is directed at the receiver. The receiver consists of a phototransistor mounted in a similar optical system to the transmitter.

The resultant audio frequency currents in the phototransistor, produced by the received light, are amplified to a level suitable to operate an earphone. By using a transmitter and receiver at both ends, a two way speech link may be established.

## Technical Considerations

When the light source consists of a filament lamp, the thermal inertia, i.e. the time taken for the filament temperature to follow rapid changes of the applied current, causes the higher audio frequencies to be severely attenuated. To counteract this effect it is necessary to provide frequency compensation in the amplifier circuits, having an opposite characteristic which rises at the higher audio frequencies, in an attempt to produce a relatively level response.

The compensation is done in the coupling and de-coupling circuits in the transmitter and at the receiver. The effect is to produce an overall frequency response which is within 3dB over the range, 300-3000Hz, normally required for good voice communication.

## Circuit Description

The circuit of the transmitter is shown in Fig. 1. The direct energising current for the carbon microphone M1 is provided by R1. The resultant a.f. signal voltage developed across R1 is coupled by C1 to the base of Tr1. Tr1 and Tr2 are connected as a 'Darlington pair' with the transmitter lamp LP1 connected in the collector circuit. R2, R3 and VR1 provide an adjustable potential divider which enables the operating current of Tr1 and Tr2 to be varied, so that the brightness of the transmitter lamp may be set to the level which gives the best modulation characteristics.

The necessary rising high frequency response is provided by the time constant of the coupling capacitor C1 and the potential divider resistors, and by negative current feedback at low frequencies by C2 and R5. H.T. line de-coupling is provided by C3.

In the receiver, Fig. 2., a.f. signals are developed across R7, the collector load resistor of the phototransistor Tr3. The signals are coupled via C4 to the base of Tr4. Tr4 and Tr5 comprise a direct coupled

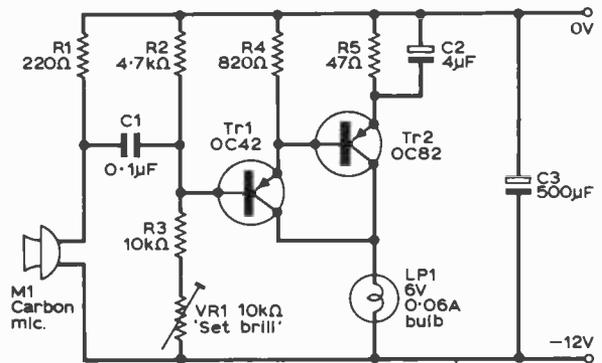


Fig. 1: Circuit of transmitter.


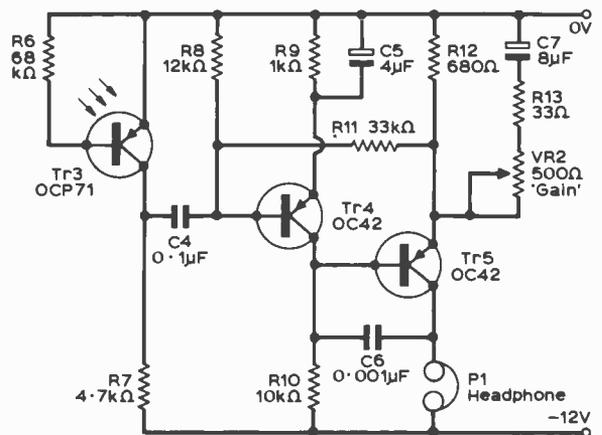


Fig. 2: Circuit of receiver.

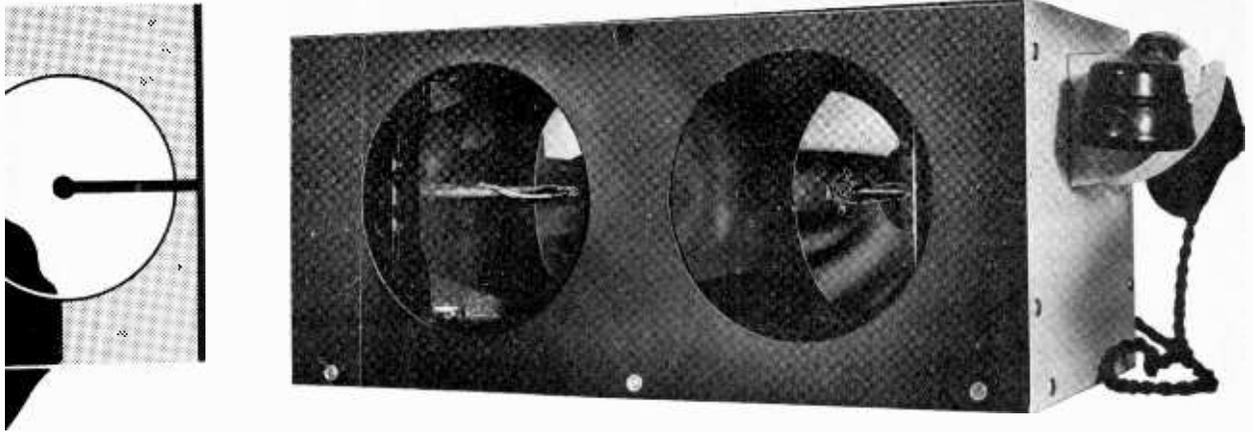

amplifier. D.C. stabilisation of the operating conditions is provided by current shunt feedback from R11 and R8 to the base of Tr4. A rising high frequency response is produced by C4 and R7 also by C5 and R9.

For good signal to noise ratio the rising high frequency response has to be restricted to the required passband, this is done by C6 which provides voltage shunt feedback to reduce the gain of Tr5 at frequencies beyond about 8kHz.

Amplified a.f. currents in the collector circuit of Tr5 are fed to the earphone in the telephone handset. An a.f. gain control is provided by VR2 which forms part of the a.f. feedback loop with R11 to the base of Tr4. The overall measured frequency response is shown in Fig. 3.

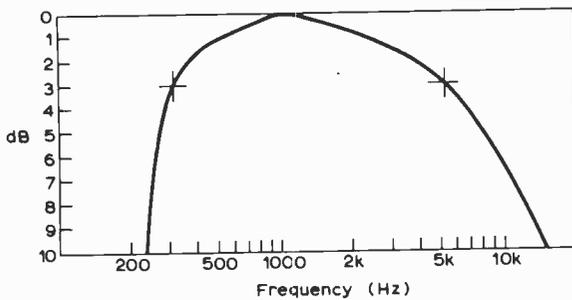


Fig. 3: Frequency response of receiver.

## The Optical System

A number of experimenters have used different types of optical systems having varying beam widths and efficiencies. For the best results it is important to have a parallel beam of light from the transmitter to the receiver. The optics required to produce a near-parallel beam would normally be quite expensive.

The optics used in this system are built from four Mullard optical projector units, salvaged from old projection-type television receivers, such as Decca 1000, Ferranti 20T4, Peto Scott 169 and Philips 1700A series etc.

The Mullard optical unit contains a precision concave mirror, which is part of the Schmidt optical system and capable of giving a remarkably parallel beam of light. The focal length of the concave

mirror is about 9.5 cms giving an equivalent aperture of about f1.8. The lamp in the transmitter is positioned so that its filament is at the focal point of the mirror and at the receiver a similar arrangement has the phototransistor at the focal point.

## Construction

Construction of the unit is not critical, and the layout shown in the photographs is just one possible arrangement. Each Mullard optical unit frame is stripped of all hardware except the concave mirror and its fixing clips. Two units are bolted together feet-to-feet with an aluminium plate sandwiched between, to act as an optical screen. Aluminium plates are also fitted over the aperture left by removing the corrector lens.

The transmitter lamp and the receiver phototransistor are mounted on suitable brackets at the focal point of the mirror (about 9.5 cms out from the centre). Due to the very narrow beam width that can be obtained it is essential to have an optical sight attached to the units to facilitate correct alignment of both stations.

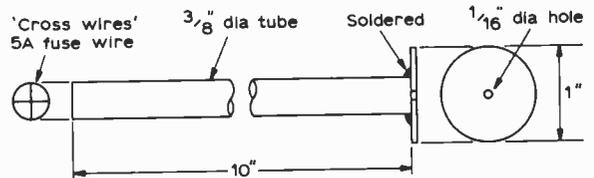


Fig. 4: Constructional details of optical sight.

The construction of the sight is shown in Fig. 4 and consists of a brass tube with a small aperture at the eye end and cross-wires at the remote end. The sight is attached by clips at the top junction of the optical unit feet and is packed into its correct position as described in the setting-up instructions.

The optical units may conveniently be bolted to a baseboard and the complete light beam telephone may be cased-in to prevent accidental damage to the components and to afford some protection against direct sunlight and the weather, when used for portable work outdoors.

## Modified Construction

The original set of Light Beam Telephones were built some years ago and since that time, it has become increasingly difficult to obtain redundant Mullard optical units.

A very satisfactory alternative to the Mullard unit is the metal reflector from a car headlamp. This type of reflector can be found on most pre-1955 British cars and on current production cars of Continental manufacture. One of the easiest headlamps to modify are those found on Volkswagen vans. The reflector is readily removable and has an excellent lampholder on which the lamp or phototransistor can be mounted. These and similar types can be purchased from most car breakers for about 10s each.

It may be possible to use headlamps with surface silvered glass reflectors, but the front glass would have to be removed to avoid diffusion of the beam.

A suitable mounting arrangement is shown in Fig. 5. Here the reflector is mounted on the front


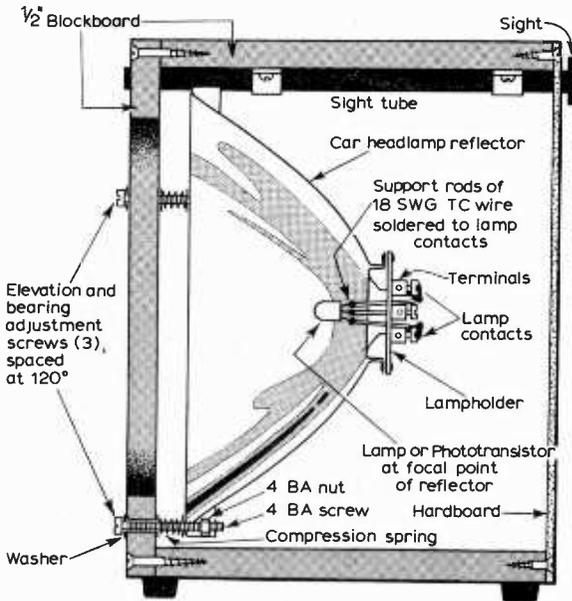


Fig. 5: Alternative construction using headlamp mirrors.

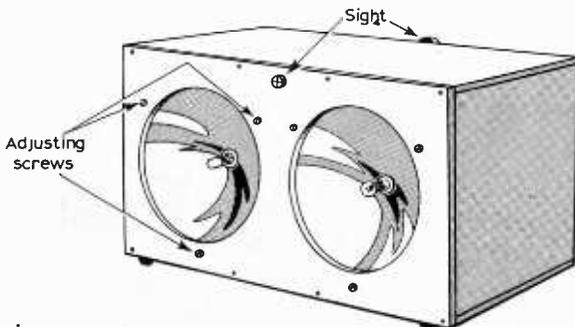

General view of modified unit.

## ★ components list (for one unit only)

### Resistors

R1	220Ω
R2	4.7kΩ
R3	10kΩ
R4	820Ω
R5	47Ω
R6	68kΩ
R7	4.7kΩ
R8	12kΩ
R9	1kΩ
R10	10kΩ
R11	33kΩ
R12	680Ω
R13	33Ω
VR1	10kΩ preset
VR2	500Ω variable

All ½ watt 10% carbon

### Capacitors

C1	0.1μF	125V	Paper/polyester
C2	4μF	15V	Electrolytic
C3	500μF	15V	Electrolytic
C4	0.1μF	125V	Paper/polyester
C5	4μF	15V	Electrolytic
C6	0.001μF	125V	Paper/polyester

### Semiconductors

Tr1	OC42	Mullard or 2N1303 T.I.
Tr2	OC82	Mullard
Tr3	OCP71	Mullard
Tr4	OC42	Mullard or 2N1303 T.I.
Tr5	OC42	Mullard or 2N1303 T.I.

### Miscellaneous

M1 and P1	Standard telephone handset.
LP1	6V 0.06 amp m.e.s. pilot lamp.
2	Mullard optical units (see text)
	Miscellaneous screws, nuts, aluminium plates, lampholder etc.

panel by three long 4BA screws. The reflector has clearance holes drilled in its edge at 120 degree spacing and corresponding holes are drilled in the front panel. The long screws pass through the front panel, through three compression springs, through the reflector and are held in place by three 4BA nuts which wedge in the return flange of the reflector. The screws are tightened sufficiently to compress the springs and adjustment of elevation and bearing can be made from the front of the unit by adjusting the appropriate screws.

The phototransistor or lamp is mounted on short support rods of 18 s.w.g. tinned copper wire which are soldered to the lampholder contacts. This enables the original terminals to be used for connections.

The setting up instructions for the lamp and phototransistor in the Mullard unit apply similarly to the car headlamp reflectors. However, the fact that the reflectors can be tilted individually means that the sights on both units should be aligned on each other first, then the reflectors adjusted for correct alignment of the beams.

## Circuit Board

The photographs show a prototype unit in which the transmitter and the receiver units were constructed on separate circuit boards.

In the final version the two boards were combined on a single board consisting of a piece of Veroboard 5½ x 2½in. of 0.15x0.15in. matrix.

The board contains all the components with the exception of the gain control, the lamp and the phototransistor.

Details of the circuit board are given in Figs. 6 and 7. The board should be mounted as close to the phototransistor as possible in order to reduce the lead lengths. The gain control is mounted at the rear of the chassis at the same end as the circuit board.

### Setting up

The easiest way to adjust and align the units is to set them up at each end of a fairly long room or corridor, facing each other, parallel and level.

Set the 'SET BRILL' control on one unit for near maximum brightness of the lamp and fix a piece of white paper over the opposite receiver unit aperture.



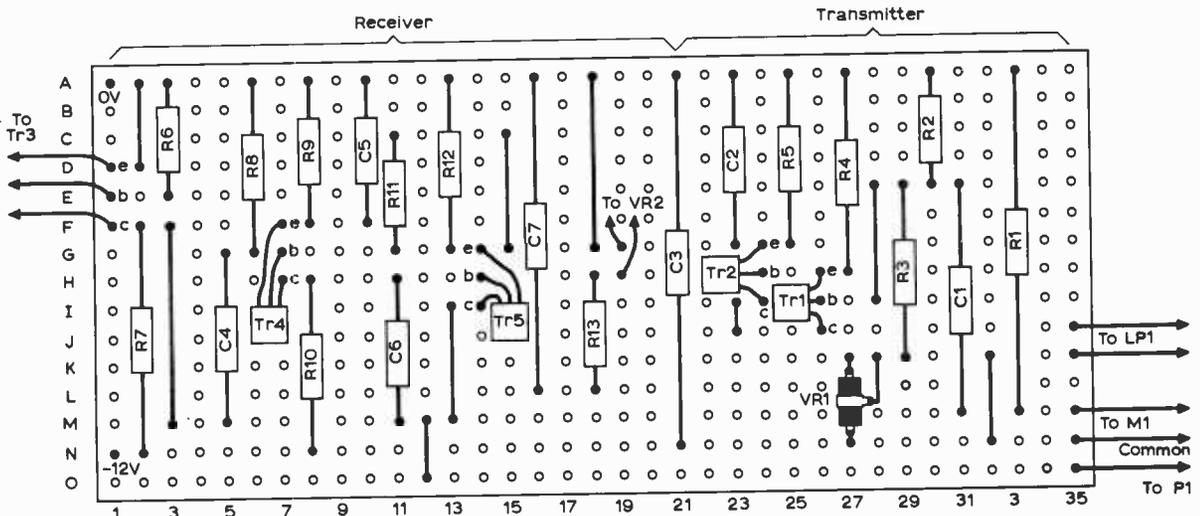
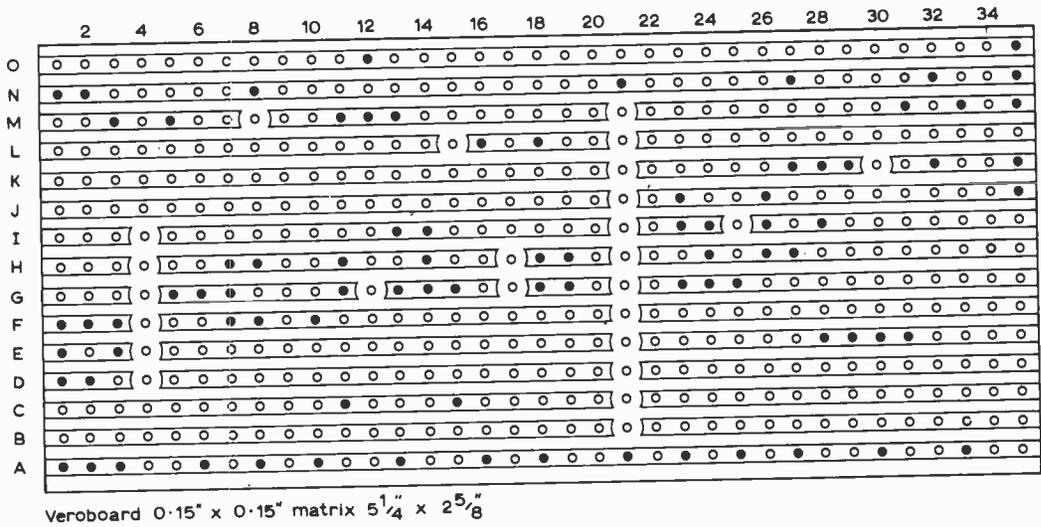


Fig. 6: Basic circuit board for combined transmitter and receiver.  
 Fig. 7: bottom: Top of board showing component layout.

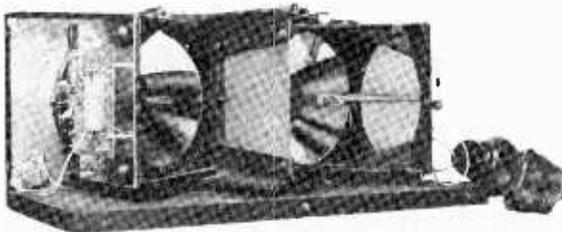

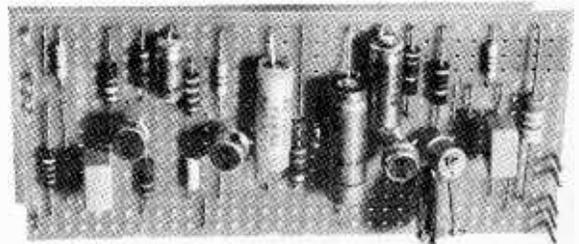View of prototype unit showing receiver circuit board.



Completed circuit board. Compare with Fig. 7.

# THE MW COLUMN


Darken the room or corridor and adjust the position of the transmitter lamp to obtain an even parallel beam, focussed on the paper and centred on the axis of the receiver optical unit. Remove the paper and adjust the position of the phototransistor for maximum illumination of its sensitive area.

Re-set the 'SET BRILL' control on the transmitter for about half full brightness and with a sound signal, e.g. voice or 'ticking clock', check the control setting for best modulation. If necessary make a final adjustment to the phototransistor position to give maximum audio volume.

The setting-up procedure for the other channel should now be carried out, but care should be taken not to move either unit or the original alignment will be upset. When both channels are fully operational, the optical sights on each unit should be aligned by packing the sight within its fixing clip so that the cross-wire on each is correctly sighted on the end of the sight of the other unit.
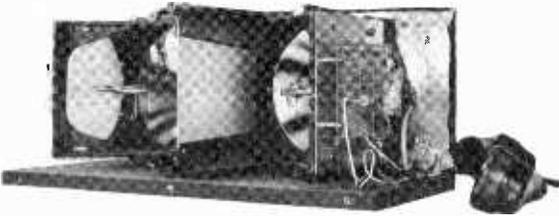
## Operation

A range of several hundred feet should be obtained under normal daylight conditions, providing the sun is not shining directly into either receiver unit. An extended front cowl will normally overcome this problem, if it arises.



View from transmitter end of prototype unit.

At night the range will be increased to several hundred yards or more in very dark conditions. The gain control may be adjusted to suit the particular operating conditions.

## Note

The concave mirrors are surface silvered and care should be taken to avoid damaging or marking the surface. If the mirror requires cleaning, this may be done by very gentle rubbing with a small pad of cotton wool slightly moistened with Stergene, diluted in accordance with the maker's instructions for cleaning glass.

Other sources of suitable reflectors, in order of suitability, include Aldis signalling lamps, aircraft runway landing lights, and projector lamp-house reflectors. The successful operation of the system depends on having a well focussed beam and good alignment.

Finally, should it be found necessary to use head-lamp reflectors great care must be taken in removing any front glass to avoid injury to the hands. If necessary wrap the reflector unit in a cloth and then tap the glass gently with a hammer until it breaks. ■

WEST AFRICAN stations are usually at their best at this time of year. Listen from sunset onwards, preferably using a loop aerial since DX is to the south while any interference will probably be from the east. Conakry 1403kHz is invariably a good signal after 2300 hrs GMT—it was logged in Germany recently on a transistor portable! Listen for French announcements and African style music and singing. Dakar 746kHz in Senegal also signs off at midnight and has similar programming. Try after Sottons goes off the air at 2300 hrs (except on Saturdays). More difficult stations from this area include ELBC 629kHz in Monrovia Liberia which signs off at 0045 hrs with announcements in English; *Radio Abidjan* 1240kHz in the Ivory Coast in French; CQA 759kHz on the Portuguese island of Sao Tome in the Gulf of Guinea. Further south in Angola, CR6RZ on 1088kHz is sometimes heard in Portuguese after BBC4 on the same channel finishes for the night. Among easier stations in the north are *Radio Sahara* 656kHz in Spanish Sahara with close-down at midnight and Tenerife 620kHz in the Canary Islands which signs off at 0100 hrs. *The Voice of Morocco* 1232kHz in Tangiers is usually strong and can be heard quite late in the evening, broadcasting in Arabic or French.

The continued improvement in conditions on the medium waves since the maximum of the current sunspot cycle is illustrated in an interesting letter from Chris Pearson of Bolton Lancashire. Chris made his first attempt at MW DX on the 13th and 14th February using a domestic receiver and a 60ft aerial. During the period 2300 to 0130 GMT he logged CFCY 630kHz in Charlottetown Prince Edward Island; *WOR* 710 in New York City; *CHER* 950 Sydney Nova Scotia; *WINS* 1010 N.Y.C.; *CBA* 1070 Sackville New Brunswick; *WBAL* 1090 Baltimore; *WCAU* 1210 in Philadelphia; *WGAR* 1220 Cleveland. A very good beginning Chris. North American stations can still be heard from 0230 GMT until sunrise in May.

Sunset is a profitable time for the MW DXer. Before European QRM becomes too troublesome it is often possible to pick-out quite rare stations. Khania 1511kHz in Crete is one that has been logged at sunset during May. Although part of Greece, Crete is generally regarded as a separate country for DX purposes. Another 'DX Country' in this area is Rhodes in the Dodecanese Islands. In spite of QRM the *VOA Rhodes* on 1259kHz is occasionally logged. From the Persian Gulf the BBC Eastern Relay, *Radio Mazirah* 1410kHz in Sharjah, Trucial Oman, was heard regularly last summer in Arabic and Hindi up to sign off at 2115hrs. Further east, Urumchi 1525kHz in the Sinkiang Province of Western China beams programmes westward and can be heard quite clearly during the evening in Russian, in spite of jamming. Urumchi is one of a small number of high power MW stations intended for other than domestic or medium range reception; it's power is believed to be in the region of 2000kW.

CHARLES MOLLOY

# SUPERCONDUCTIVITY

I. R. SINCLAIR

OF all the surprising effects which research in physics has uncovered in the 20th century, effects which include transistor action, lasers, parametric amplification and many others which have affected communications, one of the strangest to influence electronics must be superconductivity. It had, of course, been known that all good conductors decreased in resistance as they were cooled, and also that, contrary to what might be expected, the resistance then became constant for most materials at low temperatures.

By "low" in this context, we mean temperatures at which most gases are frozen solid, and to measure such temperatures we use a scale of temperature called the Kelvin or Absolute scale. We shall have to become used to this scale, as it is now internationally recognised as a standard, and will soon be the only scale of temperature taught in schools. The familiar term "degree" will disappear, to be replaced by the "Kelvin," and the temperature of "nought" Kelvin will be the absolute zero of temperature.

There are no temperatures below zero on the Kelvin scale, as we have very convincing evidence that it is impossible to have colder temperatures, and in practice we can only approach to within a few hundredths of a Kelvin to zero temperature. The zero of the Kelvin scale is at  $-273.16^{\circ}$  on the Celsius (often wrongly called Centigrade, even by the BBC) scale on which water freezes at  $0^{\circ}$  and boils at  $100^{\circ}$ .

On the Kelvin scale, water freezes at  $273.16^{\circ}\text{K}$ , oxygen at  $91^{\circ}\text{K}$  and nitrogen at  $79^{\circ}\text{K}$ . Incidentally, if you think that this is another new fangled continental measurement, the scale was originated by Lord Kelvin in 1854, and has been in use since that time.

## Research

By 1933, it was known that certain metals, in particular lead and tin, showed a sudden drop in resistance at temperatures of only a few Kelvin. Such temperatures could only be attained in baths of liquid helium, which is the last gas still to be liquid as the temperature approaches absolute zero, and the discovery must have seemed to readers of the newspapers of the time (if they troubled to report it) a useless piece of pure research with no practical significance.

It has great significance now. When lead is cooled, the resistance starts to fall very noticeably at about  $7^{\circ}\text{K}$  and by the time  $4^{\circ}\text{K}$  has been reached, the boiling temperature of liquid helium, the resistance of the lead is only a millionth of a millionth ( $10^{-12}$ )

of its value at the freezing point of water. The **transition temperature** at which such metals suddenly drop in resistance varies from one metal to another; for tin it is  $3.7^{\circ}\text{K}$ , for mercury it is  $4.1^{\circ}\text{K}$ , and so on.

Much of the work which has been done on superconductivity has been aimed at finding alloys whose transition temperatures are higher than those of pure metals; the highest known at the time of writing is about  $22^{\circ}\text{K}$ . There is even a faint prospect of finding non-metallic substances which may be superconducting at ordinary room temperatures.

## The Superconductivity State

To form any idea about what happens when materials become superconducting, we must use the modern theory of solids (see "The Solid State" in *Practical Wireless*, December 1968 and January 1969). This theory pictures a solid as an arrangement of positively charged nuclei surrounded by electrons of various energies arranged in groups or **bands**. The transfer of electrons from one band to a higher energy band can be arranged by providing the electrons with energy in the form of heat, light, or other radiation, sufficient to cause the transfer.

In many substances there are gaps between the bands, meaning that no electron can ever have values of energy corresponding to the gaps. If these gaps are wide, the transfer of electrons may never take place under any conditions which we can arrange, if the gaps are narrow, the transfer may be easy.

Insulators are materials whose highest energy band in use is filled with electrons, and whose next empty band is a large energy gap away. Insulators become conducting only at very high temperatures when some electrons transfer to the empty band and become free to move from the region of one nucleus to others.

Semiconductors have a smaller band gap, so that conductivity increases rapidly as the material is heated because of the easy transfer of electrons into a vacant band, leaving behind holes which can also act as conductors. Metals have overlapping bands, and electrons can move easily at normal temperatures. In this case the effect of heating is to move too many electrons into higher band regions, so causing what amounts to a traffic jam and **raising** resistance.

If we could examine an atom of a substance, we might find that the energies of the electrons were carefully graded in steps of energy which formed into bands only when atoms were forced to live close together, as when a gas is condensed into a

solid. In each step of energy, a maximum of two electrons can only ever be found, distinguished from each other by their "spin," that is they appear to spin in opposite directions.

We should not take this too literally, because we cannot observe this spin, nor can we imagine any axis around which an electron should be spinning, but there is a sound basis for the idea of electron spin, not least in the explanation of magnetism, and spin is as good an idea as any to describe the difference between electrons which appear to be identical in every other respect.

As a metal is cooled, electrons of opposite spin in different energy levels appear to team up to form pairs (called Cooper Pairs) which have identical energy values, a situation which never exists at higher temperatures. These pairs with identical energy values stay together and move together without any interference from the rest of the particles forming the material.

## An Analogy

The nearest thing which we know to this in everyday electronics is series resonance. Suppose we call an inductor a "resistor with clockwise spin"—expressing the idea that the voltage across the inductor is  $90^\circ$  ahead of the current through it. Since the voltage across a capacitor is  $90^\circ$  behind the current through it, we could call a capacitor a "resistor with anti-clockwise spin," and we might not be surprised if we found that the combination of an inductor and a capacitor had, under certain circumstances of energy (frequency) practically no resistance.

We cannot press this similarity very far, however, for nothing in electronics prepares us for the idea that all pairs of electrons will have the same energy and will move together. It is as if tuning one resonant circuit in a vast tuned amplifier caused all the other circuits to come into resonance at the same time.

The idea is not entirely unfamiliar, because the action of a laser depends on electrons moving from one energy level to another in a large number of atoms together. In the laser, however, the "sync. pulse" which causes the electrons to move in step is the light ray travelling to and fro along the laser tube or rod; in the superconductor, the "sync. pulse" seems to be the vibrations (called **phonons**) of the nuclei of the atoms of the solid which in certain substances reach the correct frequency for stimulating the pairing of electrons at the transition temperature.

When a substance becomes superconducting, an energy gap appears which did not previously exist in the substance, and the paired electrons are all in a band which is just below this gap. If the paired superconducting electrons are given enough energy to travel across this gap into another energy band, they can no longer contribute to superconduction, and they "unpair" rapidly.

If enough energy is put in, by heating above the transition temperature, or by the application of strong magnetic fields, then the energy gap disappears and superconduction stops.

The ability of superconduction to be switched on and off in this way is the principle behind the use of superconducting wire in computer memories. For

some other purposes, the destruction of superconductivity by magnetic fields is a disadvantage, and alloys have been developed (for winding electromagnets) in which the magnetic field for the breakdown of superconductivity is very large.

## The Josephson Effect

We have seen that superconducting electron pairs cause other electron pairs to move in the same way and have the same energies. The situation is similar to the hypothetical case of a set of oscillators being brought to the same frequency by a sync. pulse applied to one oscillator, the others being very closely coupled.

We know also that if the coupling between the oscillators in our imaginary case were made loose, it would be most unlikely that they would pull into line so willingly, but what happens when we loosen the coupling between electrons in a superconductor?

The way in which we can do this is by inserting an insulator between two portions of superconductor. If the insulator is "thick" to the extent of several thousand atoms, then the conditions existing in one superconductor have no relation to the conditions existing in the superconductor on the other side of the insulator; there is no synchronisation.

If, on the other hand, the insulator is very thin, perhaps one or two atoms in extent, the superconductivity is unaffected by the insulator. We say that the superconducting electrons have tunneled through the insulator, implying that there has been a superconducting current in an insulator.

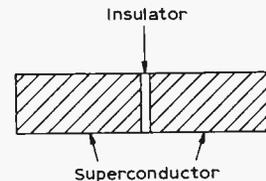


Fig. 1: The Josephson Junction

The effects which can be produced in these sandwich constructions of superconductor-insulator-superconductor (Fig.1) were discovered by a research student, B. D. Josephson, in 1962. He found that the current flowing in an insulator-superconductor junction, now called a Josephson Junction, was expressed by a comparatively simple formula which involved the steady voltage across the junction, the alternating voltage applied, the frequency of this alternating current, the charge on the superconducting electron pair, and a well known constant called Planck's Constant which appears in any description of energy levels, and can be crudely described as being the atom of energy.

We can obtain several solutions to the Josephson equation by filling in values for the voltages which we can adjust. If, for example, we have no voltages, direct or alternating, across the junction, the equation predicts a steady flow of current. Such a current, flowing without an applied voltage is a superconducting current, and shows that the junction is behaving as a superconductor.

If a steady voltage only is applied, the solution

of the equation is now an oscillating current whose frequency is equal to 483.6MHz for every microvolt applied. This appears to be a very simple way of generating very high frequencies, with the frequency easily varied by varying the voltage applied.

When alternating voltage alone is applied to the junction, the results are not particularly interesting, a current at the applied frequency; but when both alternating and direct voltage are applied together, the output is a direct current whose amplitude is proportional to the frequency of the alternating voltage, plus a series of harmonics of the alternating voltage. This implies that a Josephson Junction can be used as a detector, even at extremely high frequencies.

## Superconductivity Switches

Up until now, switching with superconductor materials has been done by the principle mentioned earlier that the superconducting state can be destroyed by added energy. It turns out, however, that a Josephson Junction is much easier to switch. At low currents, the junction is superconducting and has zero voltage across it, at higher currents the junction conducts by electron tunnelling and has about 1mV across it.

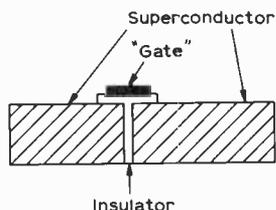


Fig. 2: Josephson Junction with gate.

Adding a third electrode, a strip of lead carrying a control current, makes a more satisfactory arrangement similar in construction to a mosfet (Fig.2). A flip-flop has already been constructed (Ref.1) which has a switching time of less than 0.8ns ( $1000\text{ns}=1\mu\text{s}$ ).

## The Future

To my mind, the whole future of the Josephson Junction depends on the achievement of superconductivity at higher temperatures. The use of any device which depends on supplies of liquid helium for its operation is inevitably going to be restricted to applications for which absolutely nothing else will do.

If we reach the stage where the developments in superconductive materials and the developments in electrical cooling (by Peltier-Thomson junctions) overlap in their temperature range, then the Josephson Junction may suddenly become the big growth industry in electronics. Until then we only watch and wait.

### References:

1. Matisoo, J., "The Tunnelling Cryotron," *Proc. Inst. Elect. Electronics Engrs.* 1967, 55, pp 172-180.
2. Solymar, L., "Josephson Junctions," *"Electronics & Power,"* Aug. 1968, p. 316.

## NEXT MONTH IN

# PRACTICAL WIRELESS

### REVERBERATION UNIT

All lovers of good music, be it classical or 'pop', will appreciate the importance of 'reverb' on the end product as it comes from their speaker systems.

This unit can be added quite simply to any existing amplifier chain and it will provide the necessary reverberation effect with adjustable time delay. Tape recording enthusiasts can also put the unit to good use when re-recording those old discs and tapes.

### NOVEL SIGNAL INJECTOR

A two transistor signal generator complete with power supply can hardly be described as novel. But when it is built into the handle of a small screwdriver, such as is carried around by every radio enthusiast in his top pocket, then it IS novel!

### LIGHT OPERATED SWITCH

This 3 transistor unit built into a clear plastic box can be sited indoors or outside and will operate a lamp or relay when darkness falls. The heart of the unit is a photoconductive cell that costs around 10s. Incidentally, the three transistors together will hardly break the bank at 9s!

**PLUS THE REGULAR "TAKE 20" AND "I.C. OF THE MONTH" FEATURES AND OTHER CONSTRUCTIONAL ARTICLES AND FEATURES**

**Don't miss your copy of the July issue of Practical Wireless —on sale 5th June—price 3s. 6d.**

# MAINS connector

B. HUNTER

WHEN setting up a workshop, the author was careful to provide mains sockets for all the common types of plugs in use so that plugs would not have to be changed on apparatus being serviced. This method worked well until equipment arrived without plugs or when testing newly constructed apparatus which did not yet have a plug. Fitting plugs was time consuming and so some method of connecting the bare wires to the mains was desired so the author decided to construct the mains connector described here. Using this, apparatus without plugs may be quickly connected to the mains and the bare wires are completely covered and safe.

The connector consists of a base to which three crocodile clips are fixed. These clips are connected to the mains supply and provide *Live*, *Neutral* and *Earth* connection to the wires from the apparatus. The clips are completely covered by the top and sides of the connector so that the user is protected from electric shock whilst the unit is closed. It seemed a pretty safe bet that at some time or other, the user would open the top whilst the unit was still live and possibly receive quite a shock, so a means of cutting off the supply when the unit was opened was required. The simple addition of a micro-switch provided this facility. The micro-switch is in the live side of the mains, the normally open contacts being used so that the switch is closed when the top of the unit is closed.

A mains neon may be fitted if thought necessary, and by adding the neon after the micro-switch, a visual indication of the unit switching off when the top is opened is obtained. This is an added safety feature in the unlikely event of the micro-switch failing to break the supply.

The unit was constructed from  $\frac{1}{4}$  in. Perspex which was glued together with 'Araldite'. The size of the unit is, of course, in no way important. The sizes given in Fig. 1 may be changed to suit individual taste.

The bolts in the crocodile clips should be removed and the end of the clip shown in Fig. 2 should be broken off. The clips are held to the base by bolts which fit through the holes shown in Fig. 1. These holes should be countersunk so that the heads of the bolts sit well below the surface of the perspex. The clips are screwed to the base with countersunk bolts, solder tags being fitted underneath the clips. The clips are already tapped for 6BA bolts, so it is not necessary to use nuts on the bolts. When the clips are tightened, the heads of the counter-sunk bolts should be completely covered with 'Araldite' because these are connected to the mains when in use.

The sides are cut out as in Fig. 1, slots being filed as in the diagram to accommodate the wires. The sides are then glued to the top so that they are out of the way when the unit is opened.

The micro-switch should be bolted to one of the sides so that the switch operates just as the top is

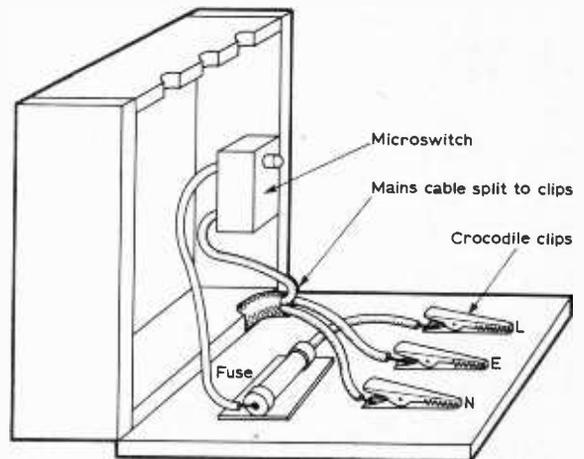
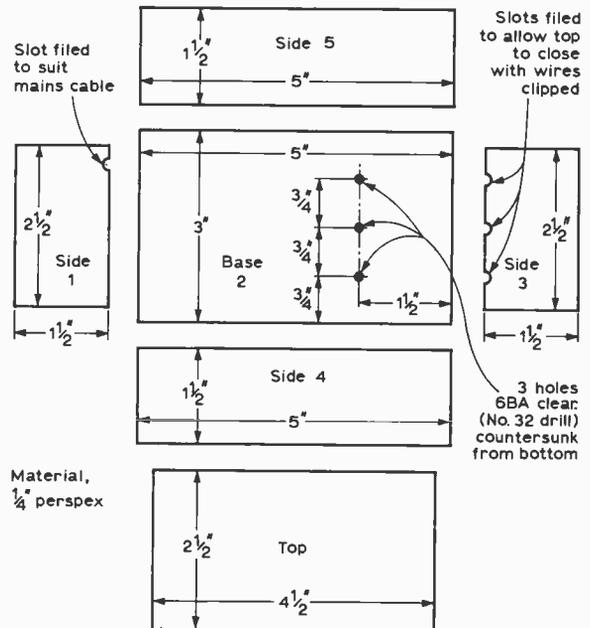


Fig. 1: The constructional details of the mains connector.

opened. It is best to construct the box then fit the switch so that the position of it can be adjusted for correct operation. If the unit is fitted with a 13 amp plug, this will already be fused, but it is a good idea to fit one inside the unit for ease of replacement.

When the glue on the sides has set (up to 3 days—see instructions on Araldite packet), a hinge should be fitted on side 1 and the base 2.

When the plastic work is complete, the three-core mains cable should be fitted through the slot in side 1 and held in place with a cable clip. The black (neutral) lead from the mains cable should go to the

—continued on page 141

# 10 OR 15 METRE CONVERTER

C. DRINKWATER

**T**HERE are many good receivers in use which do not cover the 15 and 10 metre bands, and this article is intended to provide a relatively cheap unit which is both useful to the more experienced and instructional to the beginner. The tuning depends upon the main set, and bandspread or a good length of tuning scale is needed for the 2.5—3.5MHz i.f. No crystal or tuning gang is employed in the converter, and it is suggested that the beginner start with the 15 metre version to gain experience, before tackling the 10 metre version.


The omission of crystal control does cause oscillator drift, but this was not found troublesome, even for s.s.b. once the unit has settled down after switching on. Results obtained have been surprisingly good, and it is recommended that the beginner should read and act upon one of the many articles covering aerials although an unmatched long wire will work quite well. Ten metres is more prone to ignition interference, and if the location is near a busy road the answer is a good aerial or a limiter on the main set, or both in a particularly bad spot.

## The circuit

R.F. is tuned by L2/TC1, coupled to the base of amplifier Tr1 by L3, aerial coupling by L1. Output is coupled to mixer stage by L4, tuned by L5/TC2, and coupled to Tr2 by L6. T:3 is a Colpitts circuit—h.f.c., C8, L8, TC3 with C9 to base—operated above signal frequency, and coupled via L7 to mixer Tr2 emitter. As the oscillator is at a fixed frequency, a variable i.f. is obtained via C5; e.g. on 15 metres, 24.5MHz will mix with an incoming signal of 21.0MHz to give an i.f. of 3.5MHz, signal of 21.5MHz will give i.f. of 3.0MHz etc. On 10 metres, 31.5MHz with 28.0MHz gives 3.5MHz i.f., with 28.5MHz gives 3.0MHz, etc. It will be found that the tunable i.f. range extends beyond 2.5-3.5MHz, but results may be erratic due to the fixed front end.

It is desirable to fit a lid to the box to minimize breakthrough of local TV or v.h.f. stations, and to prevent the local oscillator from interfering with domestic TV. Note the position of C7 in Fig. 2 to prevent radiation from the battery leads. The battery was fitted externally to avoid disturbing the wiring accidentally, and to reduce the effects of changing characteristics. The battery life should be extremely long since little current is drawn.

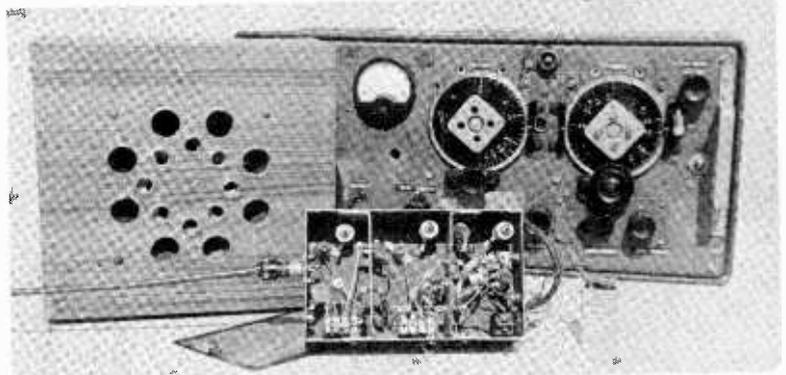The h.f.c. used was the "56UH" type found in common use on those computer panels which most good "junk-shops" seem to have. Note the use of



*The underside of the completed Converter.*

AF115 transistors for 15 metres, and AF114 for 10 metres. These will in fact work either way round, but it was found to be more stable and with better gain if used as indicated. If used transistors are to be fitted, be certain that they are of known good quality. Many fruitless hours can be spent when all that is wrong is a transistor of unknown response failing at these higher frequencies.

Cx is only to bring the oscillator into the range required, and if it is over 5pF it will probably be better to rewind the coil, although it can be as much as 10pF. Usually the ends of the coil have come away in fitting and as this will cause a weaker oscillator, it is better to rewind.

## Construction

The original was made in a box of heavy-gauge tinplate, soldered at all edges, but the second unit was constructed in a die cast box, easily obtained although the screens had to be made—see Fig. 2 for dimensions. Rubber sleeves were used to deaden any vibration on the leads passing to other compartments, as a tendency was found for the unit to be microphonic. Drill the  $\frac{1}{8}$ in. holes for these at a depth of  $\frac{1}{8}$ in., two in each screen, and a larger one for the battery leads. Apply a little Bostik or Evo-Stik to the sleeves and push them in and allow to set. A short length of 18-gauge tinned copper wire is then carefully pushed through and the ends formed into a tight loop to form an anchoring point for the various components either side. Drill the larger holes for the co-ax. input and output sockets switch S1 and the smaller holes for mounting the trimmer capacitors and fit these components.

If it is possible to get enough heat from the soldering iron without over-heating everything else, it is better to solder all points marked MC to the chassis direct. Solder tags can be used, but fit a non-slip washer on the screw first, then fix the tag on a

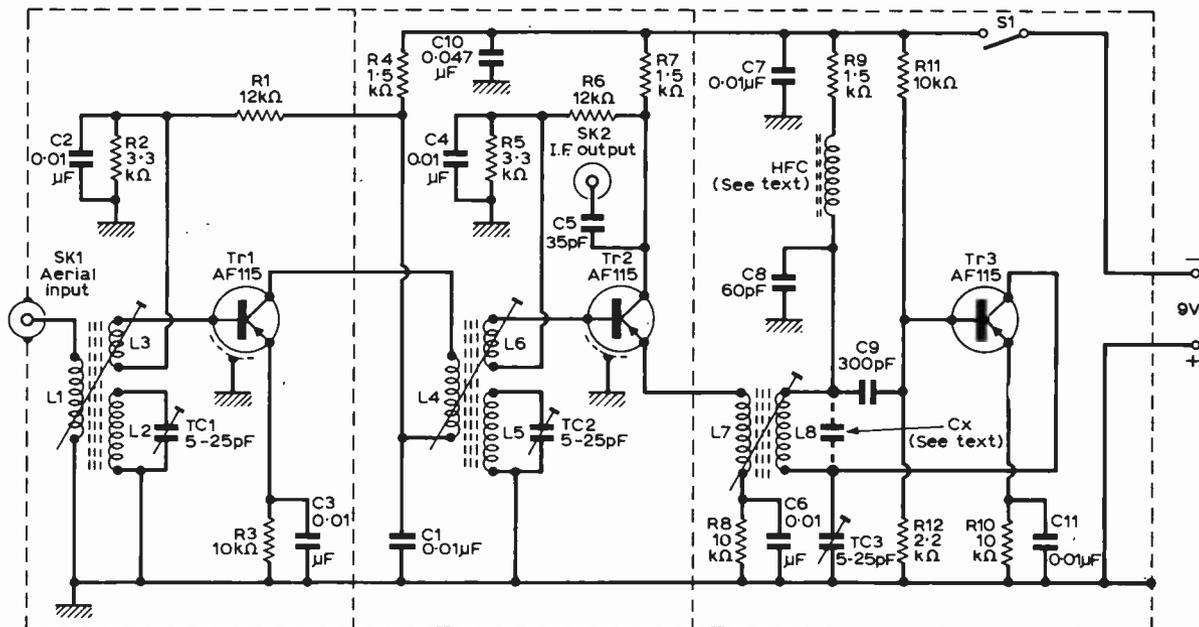


Fig. 1: The circuit of the converter. Coil winding details are given below.

cleaned surface as tightly as possible, bending up the end to allow the wire to be pushed through for soldering. It is important that these are good chassis contacts.

Fit the four-way tag strips about half the depth of the box to allow room for the transistors to be fitted last of all. Fix the coils to the chassis and wire in all components. Some of the components are intended to be self supporting, a check with Fig. 2 will show which. Keep the leads as short as possible, and stick to the layout as near as components will allow, particularly in the oscillator section as this affects frequency. If a lid is fitted drill holes to allow access to the coils and trimmers, as the lid causes a considerable shift in frequency when in place.

Check wiring carefully on completion, make sure transistors are fitted correctly before fitting battery, and ensure battery positive is connected to chassis.

### Alignment without signal generator

Switch on main set and tune to 3.0MHz, connect aerial and connect converter. Set dust cores extending half-way out and trimmers halfway open. Swing main set tuning for some indication of life. The aim is to get the band central on 3.0MHz i.f., this can be done if care is taken. The newcomer at this point needs some information on what he is listening for; briefly, once the amateurs can be heard, the "Calling CQ on 10" etc., will soon establish where you are. The bands consist of amateur a.m., amateur s.s.b., commercial a.m.,

with various c.w., telegraphy, etc., to either side. If you hear the "Citizens-Band" you are too low for ten metres, they are around 27.0MHz and you should be around 28.0MHz.

Centre up the band by means of the oscillator trimmer capacitor adjusting the dust core on the 15 metre version until the right spot is found. Do this slowly, as little movement shifts the frequency a lot. Peak up L5 and L2 at this point, re-adjusting L8 to keep the band central on 3.0MHz until no improvement can be made. Tune to a signal on 2.5MHz i.f. and adjust TC2, TC1, but do not adjust the oscillator.


Remember, the 10 metre band is liable to fold up

### COIL DATA AND CONSTRUCTION

Coil	Turns 10metres	Turns 15metres	Positioning	Wire
L2	10	13	Wind on first, close wound	22 gauge enam.
L1	3	4	Over L2 opposite direction	22 gauge DCC
L3	1½	2½	Over L1 lower end, same direction as L2	22 gauge enam.
L5	9½	12	as L2	as L2
L4	3	4	as L1	as L1
L6	1½	2½	as L3	as L3
L7	4	5	For 10 metres, wind L8 on dust core, with L7 over and opposite. For 15 metres, wind L8 on former first, with L7 over and opposite direction	22 gauge DCC 22 gauge enam.
L8	8	11		

Use ¼in. x ¼in. plastic formers with ⅜in. long dust cores with fine thread; be sure they are h.f. type. Use quick setting cement; hold in jig while setting. Wind coils tightly. Keep ends straight and do not allow them to open out when fitting.
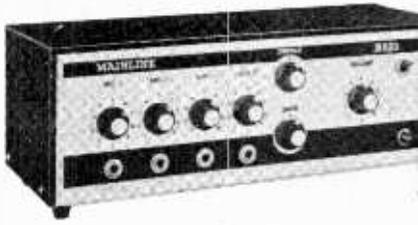
# Mainline set the NEW standard in amplifiers



Mainline 70ABD £64.0.0.



Mainline 70AB power amplifier £35.0.0.



Mainline Pre-4 mixer pre-amp control unit £24.0.0.

## Mainline 70ABD

The 70ABD is a fully integrated Preamplifier and Power Amplifier to the specifications of the Pre-4 and 70AB. Size  $6\frac{1}{2}'' \times 15\frac{1}{2}'' \times 4\frac{3}{4}''$ .

**Recommended Retail Price £64.0.0.**

## Mainline 70AB power amplifier

The MAINLINE 70AB is a high fidelity power amplifier, which is in every respect one of the finest units available on the market today, regardless of price. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit, and we can guarantee that it is virtually indestructible. Allied to this is the very high power output (70 watts RMS) a frequency range that is superb, and distortion well below 1% even at full output. The unit is suitable for use in discotheques, groups, P.A., etc., or anywhere that high quality, high output is required. Coupled to our Pre-4 Control Unit the results are quite remarkable. The Mainline 70AB main amplifier can be used with any other good quality control unit.

### Specification

**POWER OUTPUT** 70 watts RMS  $\pm 1$  db at 8 OHMS.  
**FREQUENCY RESPONSE** 20-20,000 HZ  $\pm 1$  db.  
**SIGNAL/NOISE RATIO** -70 db at full output.  
**HARMONIC DISTORTION** less than 5% at full output.

**INPUT SENSITIVITY** 700 mV at 20-30 K OHMS.  
**SIZE** 7" x 9" x 6 1/4".  
**A.C. FUSE** 1.5 amps (British Standard).

**Recommended Retail Price £35.0.0.**

## Mainline Pre-4 mixer pre-amp control unit

The MAINLINE Pre-4 is a high quality control unit, which has been designed specifically for use where mixing facilities are essential, and features many facilities not normally found on control units of this type.

The unit has four individual inputs each with its own gain control, plus separate bass, treble and master volume controls, for versatility in use. Inputs 3 and 4 are duplicated on the back panel so that if the unit is panel mounted the two auxiliary inputs (which are suitable for P.U. Tuners, Tape-recorders, etc.) may be connected from the rear. As the Pre-4 is self-powered it can be used with any other Power Amplifier, but has been designed basically as the control unit for our MAINLINE 70AB Amplifier Module.

### Specification

**INPUTS VOL. 1** 8 mV at 50K OHMS (mic).  
**VOL. 2** 8 mV at 50K OHMS (mic).  
**VOL. 3** 50 mV at 500K OHMS (aux).  
**VOL. 4** 50 mV at 500K OHMS (aux).  
 50 OHM and 600 OHM Mic inputs may be ordered at £2.0.0, extra per input.  
 1 or 2 meg OHM aux inputs may be ordered at no extra cost.  
**FREQUENCY RESPONSE** 30-20,000 HZ  $\pm 3$  db.

**SIGNAL/NOISE RATIO** Better than -65 db.  
**HARMONIC DISTORTION** Less than 5% at 1 volt.  
**BASS** Continuously variable 20 db at 100 HZ.  
**TREBLE** Continuously variable 30 db at 10 KHZ.  
**SIZE** 12 1/2" x 6" x 4 1/4".  
**CUT OUT REQUIRED** 11 1/4" x 5".  
**FUSE** 60 ma internally mounted.

**Recommended Retail Price £24.0.0.**



**5** stops you paying through the nose for your components

You could be paying too much for your semiconductors and electronic components. One *sure* way of saving money is to buy RCA, IR, SGS, Emihus, Semitron, Keyswitch, Plessey, Morganite, Litesold devices (together with manufacturers' application data) direct from us.

## For example :- PLESSEY SL403A

As described in *Practical Electronics*



Integrated Circuit (Dual in Line Package) Audio Amplifier incorporating its own Pre-Amplifier. A Class A-B Power Amplifier stage capable of delivering up to 3.5 Watts RMS. The SL403A can be used to form the basis of a simple Audio Amplifier using a minimum of external components. Complete with Data Sheet. 44/- each.

## Build the NEW Mainline Audio Amplifier Kits - up to 70 watts



The results of the combined resources of SGS and RCA, these Universal Quasi Complementary Symmetry Amplifier kits use rugged NPN Hometaxial base output transistors and provide full power to beyond 20 KHz.

The all silicon circuit with nine transistors and eleven diodes provides outstanding performance for the most stringent requirements of Hi-fi equipment manufacturers.

Each kit is supplied complete with all semiconductors, resistors, capacitors, P.C. board and heat sink.

- 12A ..... £7. 0. 0.
- 25A ..... £8. 5. 0.
- 40A ..... £9. 0. 0.
- 70A ..... £10. 10. 0.

Any two will make an outstanding stereo equipment.

To: **MAINLINE ELECTRONICS LIMITED, THAMES AVENUE, WINDSOR, BERKSHIRE.**

- Please send me ..... Mainline Pre-4 mixer pre-amps control unit(s)
- Please send me ..... Mainline 70AB power amplifier(s)
- Please send me ..... Mainline 70ABD integrated pre-amp and power amplifier(s)

- I am interested in ..... Amp Mainline Audio Amplifier kits.
- Please send me ..... kits  Please send further data
- Please send me your price-list guide. I enclose 5/-
- Cash or cheques with orders please.
- I would like further data on pre-amplifier and power supply kits before I order.

Name \_\_\_\_\_

Address \_\_\_\_\_

A member of the ECS Group of Companies

PW 6/70

# SOLDERING IRONS?

Whatever your particular application we are almost certain to have just the tool for the job.

ADAMIN—featherweight instruments with the slip-on bits and the big performance.

LITESOLD—the best-selling seven-model range of top-quality 'conventional' irons.

THERMOSTATIC CONTROL? The new LITESTAT instruments are surely the most advanced available — at not so advanced prices.

You ought to get the whole story. Ask for catalogues L10. Free.

**LIGHT SOLDERING DEVELOPMENTS LTD**  
**28 Sydenham Road, Croydon, CR9 2LL**  
**Telephone: 01-688-8589 & 4559**



## BAKER 12in. MAJOR £8

The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

Major Module 30-17,000 cps with tweeter, crossover, baffle £10.19.6  
 19 x 12 1/2 in. and instructions.

Send 4d Stamp for Further Details

**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

## A GUIDE TO AMATEUR RADIO

By Pat Hawker, G3VA

Fourteenth edition. 100 pages.

The new edition of this indispensable aid to all who want to know more about amateur radio. Designed to assist the newcomer to this unique hobby. Revised and expanded.


8s 10d post paid

RADIO COMMUNICATION HANDBOOK

over

# 20,000

copies sold

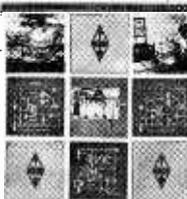

Now in its second printing

## Radio Communication Handbook

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. The standard work in its field.

69s post paid

## THE VHF-UHF MANUAL

By George Jessop, G6JP

A complete manual for frequencies above 30 MHz. Covers aerials, receivers, transmitters and test equipment. The first book of its kind outside the USA.

23s post paid

Obtainable from:

**RADIO SOCIETY of GREAT BRITAIN**  
 35 DOUGHTY STREET, LONDON, WC1


## H.A.C. Electronic Kits

### DID YOU KNOW?

That we have specialized in the supply of kits for the Amateur Constructor for over 35 years. (Established 1934.)

That we now have available a full range of Complete transistor kits with comprehensive instruction manual, for constructing—Radios—Resistance Bridge—Lightmeter—Electronic Counter—Voltmeter—80 metre Converter, etc. etc. (Details for 40 different electronic circuits are available.) Complete kits from 54/-. Fully guaranteed. Illustrated brochure upon application. send S.A.E. please.

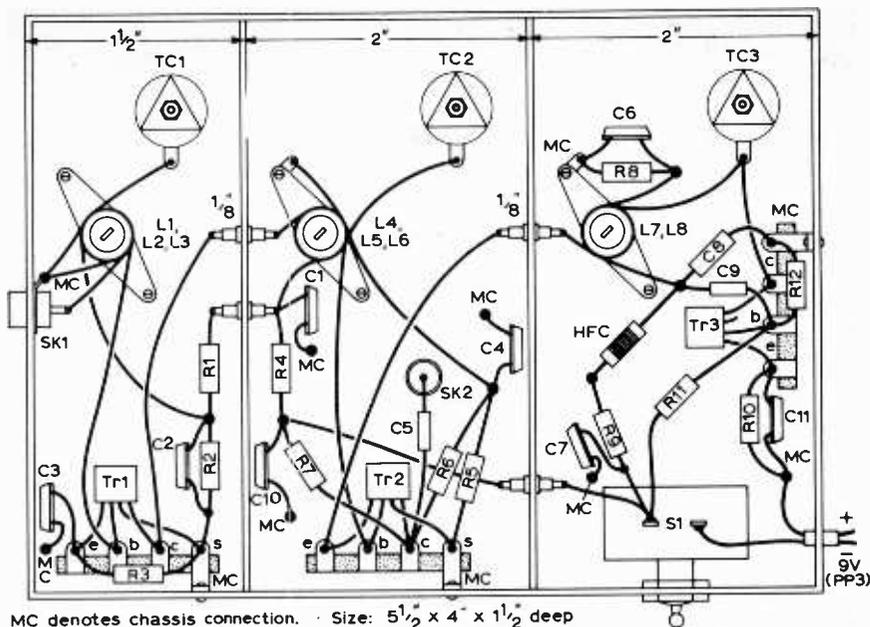H.A.C. Products. 29 Old Bond Street. London W.1.



MC denotes chassis connection. Size:  $5\frac{1}{2} \times 4 \times 1\frac{1}{2}$  deep

Fig. 2: The component layout.

much quicker than the 15 metre band, and good DX is more likely to occur during daylight. On 15 it does continue for several hours after sunset, with s.s.b. coming in from the daylight side.

### Alignment using a signal generator

**15-Metre version.** Set main tuning at 3.0MHz i.f., feed in 21.5MHz via an one turn loop fitted to the test lead held over L5. Adjust L8 and TC3 together, a little at a time until signal is heard. Place loop

### ★ components list

#### Resistors

R1	12kΩ	R7	1.5kΩ
R2	3.3kΩ	R8	10kΩ
R3	10kΩ	R9	1.5kΩ
R4	1.5kΩ	R10	10kΩ
R5	3.3kΩ	R11	10kΩ
R6	12kΩ	R12	2.2kΩ

All resistors  $\frac{1}{4}$ W, 10% types.

#### Capacitors:

C1	0.01μF disc ceramic	C6	0.01μF disc ceramic
C2	0.01μF disc ceramic	C7	0.01μF disc ceramic
C3	0.01μF disc ceramic	C8	60pF silver mica
C4	0.01μF disc ceramic	C9	300pF silver mica
C5	35pF ceramic	C10	0.047 disc ceramic

Cx—see text.

TC1, TC2, TC3—5–25pF concentric trimmers.

#### Miscellaneous

Tr1, Tr2, Tr3: AF115 for 15 metres, AF114 for 10 metres; coils—see data box; coil formers; 3 off 4-way tag strips; on-off switch; metal chassis; 2 off co-ax sockets, etc.

over L2, adjust L5 for maximum whilst re-adjusting TC3. Adjust L2,, reducing signal by removing loop until no further gain is obtained. Set main tuning to 2.5MHz and feed in 22.0MHz via loop to L2, adjust signal generator if needed to final signal, peak up TC2 and TC1.

**10-Metre version.** L8 is not adjustable. Using TC3, adjust to receive 28.5MHz on 3.0MHz main tuning, coupling as for 15 metre version, and adjusting L5, L2. Set to receive 29.0 MHz, around 2.5MHz on main tuning, peak up on TC2, TC1. If Cx is needed, see end of circuit description, it should not be more than 10pF. ■

### Mains Connector

—continued from page 136

crocodile clip on the left, and the green (earth) lead should go to the middle clip. The red (live) lead should go first through the micro-switch then the fuse and on to the right-hand crocodile clip. The fuse-holder may be fitted in any convenient position inside the unit. A fuse-holder as used in television and radio sets should be used, indeed the one used in the authors unit was stripped from an old set.

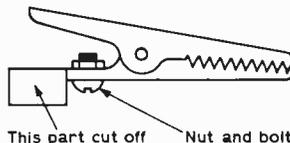


Fig. 2: The modification to the crocodile clips.

As was stated earlier, a mains neon may be fitted in any convenient position and should be wired between the live and neutral clips.

A 5 amp fuse should be the largest that should be required in the unit. If the workshop mains fuses are 5 amp then the fuse in the unit should be smaller so that this fuse will blow before the main fuse. The three crocodile clips should have identifying letters beside them so that confusion as to which clip is which does not arise. These letters (L, N, E) may be painted on, or 'Instant Lettering' may be used, the latter giving a neater appearance.

The author's model was made from perspex because some scrap perspex was available, but there is no reason why wood or any other insulating material should not be used, providing it has physical strength. Although Araldite was used for bonding the perspex together, perspex cement might possibly make a neater job.

The unit has been in use for some months now and has proved extremely useful by eliminating the annoyance of fitting plugs. ■

# practically wireless commentary by HENRY

No. 69  
Sin of  
Omission

ONCE upon a time—oh, long before *then*—manufacturers of 'wireless' equipment took great pride in not only making a good product but also a good 'image' by which to foster its sales. Slogans abounded. Individual makes were as instantly recognisable by their style as by their name. And there was a similar sense of company pride about the brochures and handbooks that accompanied the equipment.

In the springtime turnout that Mrs. Henry employs to remind the rest of the menage of her superiority, we came across some of these old handbooks and nostalgically leafed through them. What struck us immediately was not the amount of information they contrived to pack into the board-like pages but the significance of the technical data they had left out.

Wavebands were mentioned—in metres of course, and only occasionally in cycles. Hertz hadn't come along then. Now and again a power output figure would be quoted. One took it for granted, these being British and the need for dissimulation not yet having arisen, that these watts were r.m.s. It was never manifest.

Curiously, although practically every radio set on the market used one of three distinct intermediate frequencies (more by convention

than agreement), the i.f. was almost always stated. It was one of the things that the user could do little about, but we presumed that some advertising mogul had opined that this pearl of wisdom gave comfort and all his rivals followed suit.

After which it comes as no surprise to read in a recent audio publication that the HMV 'little dog' has been adopted by several different countries.

The ironic comment on that is that the dog was a bitch and the original gramophone that the artist painted was a cylinder type, not the better-known horn. Anyway, says Joe, the animal should have been a cat, which does appear to make much more note of recorded sound.

But it is not my intention to knock the advertising boys—this time. Henry is more concerned with the omission of vital information from these 'come-on' compilations. Technical data, mostly.

Quite often, we are called upon to match odd pieces of equipment—some, very odd—and have recourse to the precious 'user's handbook' for connections, impedances and sensitivities. Said user may have bought an amplifier or tape recorder and now wishes to record the rumblings of his ancient radiogram and perhaps replay the recordings through its massive 'super-mellow' loudspeakers.

Can we find the notes we want in that lavish publication? Can we heck! Connections may be given, but impedances are never more than 'high' or 'medium' and sensitivity quotes are as elusive as the Greek calends. This is so commonly the case that we are nowadays resigned to 'suck-it-and-see', more scientifically known as 'empirical performance testing.'

As a variant on this theme, we have to answer off-the-cuff telephone enquiries. 'What sort of microphone do you think I should buy to play my Whizzispool?'



Opulent brochures given away to small boys.

cries the distraught owner. We are expected to know, and this is one reason that the files of service information are right there above the head of the bloke who answers the workshop phone. (And sometimes on it when he pulls too desperately).

But whoever is responsible for the compilation of the average service sheet does not live in Kedar's tents. He believes that the buyer of product X is never going to purchase anything from maker Y. It is inevitably taken for granted that matching of items from X's stable will be in order, so nobody bothers to quote the figures, on the circuit diagram or on the specification sheet that accompanies it.

We could name at least five firms with this obnoxious sin of omission, and yet three of them publish opulent sales brochures, given away to small boys at exhibitions, that contain all this and much besides.

Not British companies—oh no! These are either too good, or so completely out of touch that their service data is a smudged sheet of blotting paper with half the components wrongly rated. At least, you know where you are with them. Up the creek, oarless. The culprits are Continental and Japanese organisations whose determined efforts to improve their 'image' make the effusions of their advertising almost believable.


All together now, lie down in the driveways of that bright new factory and shout: 'Come on makers—we want data.'



'What sort of microphone should I buy...?'
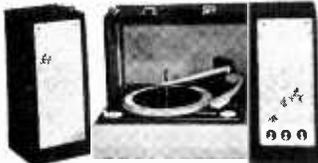
# Never Built a Kit Before?

Why not prove how easy it is the HEATHKIT way.  
Build one of these beginner kits.



**Stereo Record Player**  
Exciting Sound — Budget Price  
Kit: K/SRP-1 - - £27.6.0  
Carr. 11/-



**Automobile  
Tune-up  
Meter**  
For D.I.Y. Car Mechanics  
Kit: K/ID-29 - - £17.8.0  
Carr. 5/-



108-136  
MHz  
Portable  
**Aircraft Monitor  
Receiver**  
Kit: K/GR-98 - - £27.12.0  
Carr. 5/-



**Economy SW Receiver**  
World-wide Recept on  
1 to 30 MHz plus 550-1620 KHz  
Kit: K/GR-64 - - £24.16.0  
Carr. 9/-




**Deluxe Car Radio**  
Heathkit Value—Powerful Output  
Kit: K/CR-1 (Less  
Speakers) £12.12.0  
Carr. 5/-



**Technician's  
Versatile  
'VVM'**  
7AC, 7DC,  
7 ohm ranges  
Kit: K/IM-18U - - £16.14.0  
Carr. 5/-

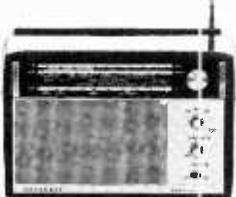**'SEVERN' AM/FM Radio**  
Beautiful Looks — Luxury Sound



Kit: K/SEVERN - - £18.18.0  
Carr. 5/-

**Portable 'VVM'**  
For Hobbyists — Householders



Kit: K/IM-17 - - £14.8.0  
Carr. 6/-

**Modellers  
Low-cost  
Tachometer**  
Uses reflected  
ambient light  
Kit: K/GD-69 - - £11.0.0  
Carr. Paid.



Many more kits to choose from in the 1970 Catalogue



A Schlumberger Company

**DAYSTROM LTD.**  
GLOUCESTER GL2 6EE

★ Please rush me a copy of your Free Catalogue

NAME.....

ADDRESS..... POST CODE.....

51/6

# BI-PAK SEMICONDUCTORS

500 CHESHAM HOUSE, REGENT STREET, LONDON W.1.

**NEW LOW PRICED TESTED S.C.R.'s.**

	1A	3A	7A	16A	30A
(TO-5)	(TO-66)	(TO-48)	(TO-48)	(TO-48)	(TO-48)
PIV	each	each	each	each	PIV
50	4/6	5/-	9/6	10/6	25
100	5/-	6/6	10/6	12/6	50
200	7/-	7/6	11/6	15/-	100
400	8/6	9/6	13/6	19/6	200
600	10/6	11/6	15/6	25/-	400
800	12/6	14/-	18/-	30/-	800

**PRINTED CIRCUITS EX-COMPUTER**  
Packed with semiconductors and components. 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/- Plus 2/- p. & p.

**TRANSISTOR EQVT. & SPECIFICATION BOOK** (German publication). A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- ea.

**2N2060 NPN SIL. DUAL TRANS. CODE D1899 TEXAS.** Our price 5/- ea.

**120VCB NIXIE DRIVER TRANSISTOR.** Sil. BSX21 & C407, 2N1893 FULLY TESTED AND CODED NDI20. 1-24. 3/6 each. TO-5 NPN 25 up 8/- each.

**PLEASE NOTE.** To avoid any further increased Postal Charges to our Customers and enable us to keep our "By Return Postal Service" which is second to none, we have re-organised and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 6, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-.

**SIL. RECTS TESTED**

PIV	750mA	3A	10A	30A
50	1/-	2/9	4/3	9/6
100	1/3	3/3	4/6	15/-
200	1/9	4/-	4/9	20/-
300	2/3	4/6	6/6	22/-
400	2/6	5/6	7/6	25/-
500	3/-	6/-	8/6	30/-
600	3/3	6/9	9/-	37/-
800	3/6	7/6	11/-	40/-
1000	5/-	9/3	12/6	50/-
1200	6/6	11/6	15/-	55/-

**TRIACS**

VBO	2A	6A	10A
(TO-1)	(TO-66)	(TO-88)	
100	14/-	15/-	22/6
200	17/6	20/-	28/-
400	20/-	25/-	35/-

VBO = Blocking voltage in either direction.

**2N3055 115 WATT SIL. POWER. NPN. OUR PRICE 12/6 EACH**

**FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-16V. 400mV (DO-7 Case) 2/ea. 1-5W (Top-Hat) 3/6 ea. 10W. (80-10 Stand) 5/- ea. All fully tested 5% tol. and marked. State voltage required.**

**BRAND NEW TEXAS GERM. TRANSISTORS**

Pak No.	EQVT
T1	8 2G371A OC71
T2	8 2G374 OC75
T3	8 2G374A OC81D
T4	8 2G381A OC81
T5	8 2G382T OC82
T6	8 2G344A OC44
T7	8 2G345A OC45
T8	8 2G378 OC78
T9	8 2G389A 2N1302
T10	8 2G417 AF117

All 10/- each pack

# SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and Quality Satisfaction GUARANTEED in Every Pak, or money back.

**Pak No.**

U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RP	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
U4	40 Germanium Transistors like OC51, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	30 Silicon Planar Transistors NPN sim. BBY95A, 2N706	10/-
U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Voits 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 2B104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	25 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	25 Silicon NPN Transistors like BC108	10/-
U20	12 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 AF Germanium alloy Transistors 2G300 Ser. & OCT1	10/-
U23	30 Mad's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min.	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U29	10 1-amp SCR's TO-5 can up to 600 PIV CR81/25-600	20/-
U31	30 Sil. Planar NPN trans. low noise Amp 2N3707	10/-
U32	25 Zener diodes 400mW D07 case mixed Voits, 3-18	10/-
U33	15 Plastic case 1 amp Silicon Rectifiers IN4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2B302/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY 50 51/52	10/-
U37	30 Sil. alloy trans. 80-2 PNP, OC200 2B322	10/-
U38	20 Fast Switching Sil. trans. NPN. 400 Mc/s 2N3011	10/-
U3	25 BF Germ. PNP trans. 2N1303/5 TO-5	10/-
U40	10 Dual trans. 6 lead TO-5 2N2060	10/-
U41	30 RF Germ. trans. TO-1 OC46 NKT72	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code NoB. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

# I.C. AMPLIFIER



Identical encapsulation and pin configuration to the following: BL402-3, IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of delivering up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each.

**AD161 NPN AD162 PNP MATCHED COMPLEMENTARY PAIRS OF GERM-POWER TRANSISTORS.** For mains driven output stages of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 12/6 PER PAIR.

**UNIJUNCTION UT46.** Eqv. 2N2646 Eqv. TIS43. BEN3000 5/6 EACH 25-89 5/- 100 UP 4/-

**NPN Silicon PLANAR BC107/8/9, 2/- each 50-99, 1/10 100 up, 1/8 each, 1,000 off, 1/6 each. Fully tested and coded TO-18 case.**

**NPN DIFFUSED SILICON PHOTO-DUODIODE TYPE IS701 (2N1275) or Tape Readout, high switching and measurement indicators, 50V, 250mV. OUR PRICE 10/- EACH. 50 OR OVER 8/6. EACH. FULL DETAILS.**

**FET'S**

2N 3819	8/-
2N 3820	25/-
MPF105	8/6

## 1,750 COMPONENTS FOR 65/- ??

YES. QUITE TRUE. READ ON

### BUMPER BARGAIN PARCEL

We guarantee that this parcel contains at least 1,750 components. Short-leaded on panels, including a minimum of 350 transistors (mainly NPN & PNP germanium, audio and switching types—data supplied). The rest of the parcel is made up with: Resistors 5% or better (including some 1%) mainly metal oxide, carbon film, and composition types. Mainly 1/2 & 1 watt 1% diodes, miniature silicon types OA90, OA91, OA95, IS130, etc. capacitors including tantalum, electrolytics, ceramics & polyesters. Inductors, a selection of values. Also the odd transformer, trimpot, etc. etc. These are all miniature, up to date, professional, top quality components. Don't miss this, one of our best offers yet! Pric. 65/-, Post and Packing 6/6d U.K. New Zealand 20/- post and packing. Limited stocks only.

## KEYTRONICS, PW

52 Earls Court Road, London, W8 Tel. 01-478 8499

MAIL ORDER ONLY. Retail and Trade supplied. Export enquiries particularly welcome.

BY RETURN SERVICE S.A.E. for list of other goods.

## DIAMOND STYLII

Replacements for BBR TC8LP, TC8ST, TC8LP/ST (Compatible), Collaro "O", Ronette BF40, Garrard GC2 and GC8, Acos GP65/67 all at 7/6d. each (1/-d.) ACOS GP73 and GP91, BBR 874 (873, 878), 875 (876), Sonotone 8TA, 9TA, 9TAHC, Philips AG3306, 3066, 3068, 3101, 3302, 3304) all at 15/- each (1/-d.).

**DOUBLE DIAMOND** (Second Diamond in place of the 78 stylus—doubles life) for 874, (873, 875) 878 (9), 9TA, 9TAHC, 3306, GP91 (for GP92, 93 and 94 cartridges), GP918C for GP918C cartridges, all at 30/- (1/-d.) Each stylus packed in individual case.

**CARTRIDGES** Replacements for GP67/9. 15/-: GP918C, 21/-: GP93 (Stereo), 24/6: GP94 (Stereo Ceramic) 38/6. (1/-). All fitted two sapphire styli.

**DIAMOND CARTRIDGES** fitted with a Diamond Stylus on the LP and/or Stereo side (the 78 side is sapphire fitted). For GP918C, (DIA918C) 30/-: GP93 (DIA93) 35/-, GP94 (DIA 94) 50/- (All 1/- each). SONOTONE 9TAHC 55/- (1/-)

## RECORDING TAPE PINEBT QUALITY

British Mylar—best value anywhere.

**STANDARD 5"** 600, 7.3, 5 1/2" 900, 10 1/2" 1200, 11 1/2" 1800 5" 900, 10" 5 1/2" 1200, 11 1/2" 1800, 18" (1/3 per reel).

**NEW ENLARGED LIST** with most of our usual popular lines and many new items including Transistors, B.D.R.'s and other devices, 10 types of extension aerials for P.M., & ordinary portables and car-radios from 4/- to £7.10.0, Microphones, Boldering Irons, Super-thin pickup wire, three types of connecting wire, single and twin mike cable, plugs and numerous small but useful items, phones, earpieces, VALVES, Meters, etc. etc. LIST SENT FREE ON RECEIPT OF S.A.E. (Overseas, post free)


**ANNUAL HOLIDAYS. NO ORDERS RECEIVED AFTER MAY 19TH. WILL BE DEALT WITH UNTIL JUNE 8th.**

## FELSTEAD ELECTRONICS (PW31)

LONGBLEY LANE, GATLEY, CHEADLE, CHESHIRE SKK 4EE

Cash with order only. No C.O.D. or Caller service. Post, packing and Insurance charges are shown in brackets after all items, and apply to GB/Eire only. Min. Charge 1/- S.A.E. for enquiries please.

## DIMMASWITCH

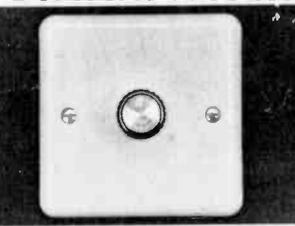

The DIMMASWITCH is an electronic dimmer capable of controlling from 40-600 watts of incandescent lighting at mains voltages from 200/250V at 50 Hz. The DIMMASWITCH has the same dimensions (3 3/8" x 3 1/2") as a standard switch and is intended as an alternative fitting, finished in Ivory, with a contrasting control knob. Two models of the DIMMASWITCH are now available, each incorporating an on/off switch, and at 10/- less in each case a kit is produced to enable a competent constructor to self build the DIMMASWITCH. Both models are available with either clockwise or anti-clockwise dimming and internal tuning may be provided at an additional cost of 2/- in each case, or 2/6d. for the kit.

**MODEL DS500/2**—utilises an advanced design of triggering circuit to enable smooth fade up from zero—£3 12s. 6d. Similar to competitive products at £5 5s.

**MODEL DS500/2/P**—a DIMMASWITCH incorporating a newly patented on/off control enabling the lamp to be switched on and off at any brilliance setting by push/pull action of the knob—£3 18s. All models give control from zero to maximum and use RCA and Mullard components and semi-conductors, and comply generally with the recommendations of B.S. 800.

Ideal for T.V. viewing and for children's night lights, etc.

Please send C.V.O. to:—


## DEXTER & COMPANY

ULVER HOUSE, 19 KING STREET, CHESHIRE CHI 2AH Tel. Chester 25883

As supplied to H.M. Government Departments, Hospitals, etc.

# TRANSMITTER / RECEIVER

F.G. RAYER G30GR

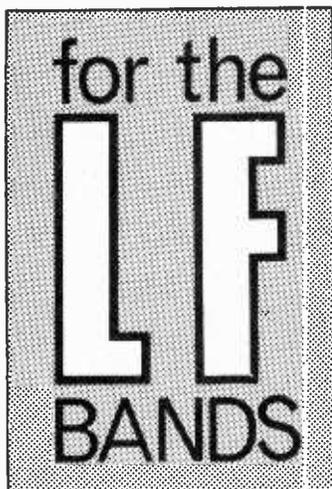

**T**HIS equipment incorporates all the required circuitry for transmission and reception, and with internal power pack and speaker, offers a neat "one box" station for regular use, or for /A (alternative address) working. The equipment described runs the full permitted power (10 watts) on the 160m band, and can easily be modified to cover 80m. Anyone who has used a transmitter at this relatively low power level will have found that results are generally surprisingly good. Many receiver S-meters are calibrated at about 6db per S-point, so if 150W input gives an S9 contact, 10W input will give about S7, which ought to be quite acceptable.

Fig.1 is the complete circuit, and brief notes on the function of each stage will make its working clear.

## Circuit

**Transmitter RF Section.** V1 is a Vackar type v.f.o. tuned by VC1 and covering 1.8-2.0MHz. The voltage regulator VR provides 150V for V1 and the screen grid of the buffer V2. L2 is broadly resonant, and V2 drives the power amplifier V3, the test point 'G' being provided to check grid current. The p.a. tank coil L3, with tuning and loading capacitors, allows V3 to be matched to most ordinary aerials.

**Audio and Modulator Section.** V4A/V4B is a high-gain microphone amplifier giving full modulation from a crystal microphone V5 with the primary of transformer T1 provides anode and screen modulation of V3. When receiving V5 drives the loadspeaker.

**Receiver RF Section.** V6 is a tuned r.f. amplifier, followed by the mixer V7. V8 is the i.f. amplifier, a diode giving detection and AGC bias for all stages. VR1 is the receiver r.f. gain, and VR2 the audio gain control.

**Power Supply.** This delivers about 120mA at 300V

on 'transmit', reduced to 220V on 'receive'. It is not absolutely necessary that the voltage is reduced when receiving, but this was found helpful in obtaining cooler running over long periods by avoiding the heat of series dropping resistors.

## Switching

Change-over of all required circuits is achieved with a 2-way 8-pole rotary switch. It is possible to change some circuits slightly so that fewer poles are needed, as described later. The functions of each pole are given below, and this should be checked when wiring.

**Section 1:** In the 'transmit' position T this applies h.t. to v.f.o. V1, and the buffer V2. In the 'receive' position R, h.t. is taken to r.f. mixer and i.f. stages, V6, V7 and V8.

**Section 2 and 3.** These contacts allow the same meter to be used to show PA anode current and to operate as a dip type tuning meter on reception. Section 2 supplies h.t. to either the p.a. anode, or to the receiver. Section 3 takes h.t. directly from the h.t. line, via S1, for reception, or from the modulator V5 for transmission. The main advantage of this method is that a 50mA meter can be used for both functions without any shunts having to be made up.

**Section 4.** On transmit this switches the aerial to the p.a. tank circuit L3 and to the receiver aerial coil L4 on receive.

**Section 5.** On transmit input to V5 is from the microphone amplifier V4B and from the receiver gain control VR2 on receive.

**Section 6.** This connects the anode of V5 to the anode (via meter) and screen grid circuits of V3 to modulate the latter when transmitting.

**Section 7.** This closes only on receive to bring in the speaker.

**Section 8.** This opens during reception converting the power supply to choke input to reduce the h.t. voltage without resorting to dropping resistors.

Net. This switch is temporarily closed while receiving to put h.t. on the v.f.o. and buffer stages so that the v.f.o. can be tuned to the frequency on which transmission will be wanted. Stray r.f. coupling into the receiving operates the tuning meter thus

indicating when the v.f.o. and receiver are tuned to the same frequency.

It may be found more convenient to make this switch a spring loaded one rather than a toggle switch.

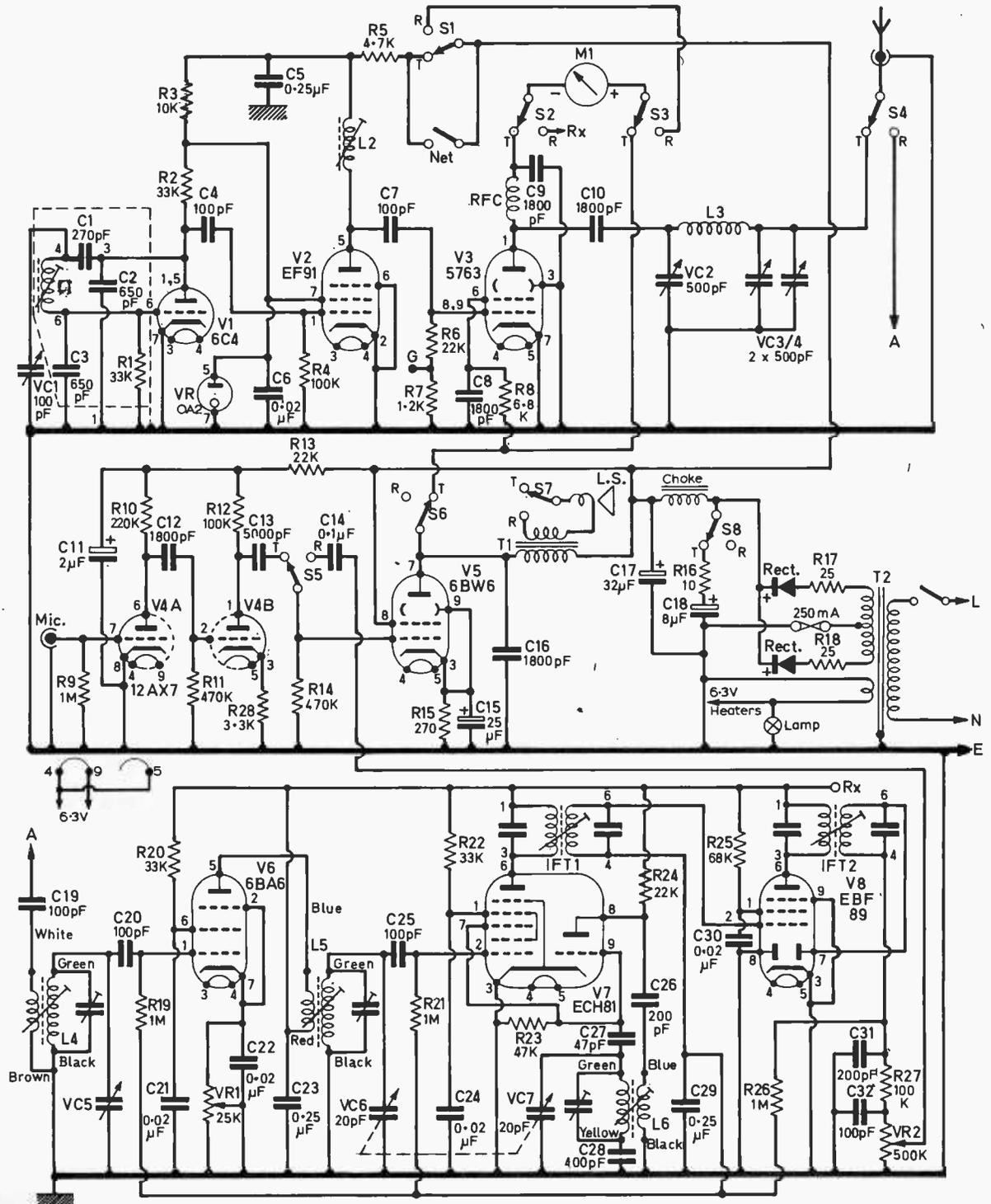


Fig. 1: Complete circuit diagram of the transmitter/receiver and power supply.

## BSR 4-SPEED SUPERSLIM MODEL UA25 RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. Size 13 1/4" x 11 1/4" x 4 1/4". Above mono board 3 1/2" in. below 2 1/2" in. AC 200/250V.



MONO BOARD 3 1/2" in. below 2 1/2" in. AC 200/250V. PRICE £5.19.6 POST 5/6. BSR UA70 Stereo/Mono Transcription £12.19.6. Auto Changer. Calibrated Stereo Pressure. BSR Minichanger UA50 Stereo/Mono. Size 12 x 8 1/2 in. AC 200/250V. Post 5/6.

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond/Mono Sapphire. SP25 Mk II £14.19.6. AT80 Mk II £14.19.6. Model 3000 £12.19.6. Post 5/6. RECORD PLAYER PORTABLE CABINET Space for amplifier and autochanger. Post 5/6. RCS DE-LUXE 3 WATT AMPLIFIER. Ready made and tested. A 2-stage unit using triode pentode valve, giving 3 watts output. Tone and volume controls. Isolated mains transformer. With knobs, loudspeaker and valves ECL82, EZ80. Frequency response 50-12,000 cps. Sensitivity 200mV. Post 5/6. 89/6

GARRARD TEAKWOOD BASE WB.1. Ready cut out for mounting 1025, 3000, SP25, AT80, etc. 77/6. GARRARD PLASTIC COVER SP.1 for WB.1 BASE. Durable limited attractive appearance. 77/6

EMI PICK-UP ARM. Complete with mono cartridge 29/6. EMI JUNIOR 4 SPEED RECORD PLAYER. Mains operated motor, turntable and pick up complete. Post 5/6. 59/6

HI-FI PICK UP CARTRIDGES GP94 55/-; GP93 45/-; GP91 30/-; GP67 19/3; ACOS L.P. only 10/6. All standard finish complete with stylus.

### CRYSTAL MIKE INSERTS

1 1/2" dia. 6/6. ACOS 1 1/2" dia. 12/6. BM3. 1 1/2" dia. 9/6

## PORTABLE AMPLIFIER

Portable minip.a. system. Many uses - ideal for Parties, or as a Baby Amplifier, Intercom - Telephone or Record Player Amplifier, etc. Attractive roxine covered cabinet, size 12 x 9 x 4 1/2 in., with powerful 7 x 4 in. speaker and four transistor one watt power amplifier. Uses P79 battery. Brand new in Makers' carton with full makers' guarantee. World famous make.



Only 75/- Post 5/-

WEYRAD P50 - TRANSISTOR COILS EA2/Ferrite Aerial 12/6 Spare Cores 9/6. O.C. P50/AC 1/4 Drive Trans. LED7A 6/6. I.F. P50/CO 470 kc/s 5/7 Printer Circuit. PC41 9/6. 3rd I.F. P50/3CC 6/- J.B. Tuning Gun 10/6. P51/1 or P51/2 5/7 Weyrad Booklet 2/- P51/3 6/-; Telescopic Aerials 6in. to 23in. 6/- Ferrite Rod 8 x 1/2 in. 4/- 6 in. 6/-

### VOLUME CONTROLS

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 3/6. D.P. 5/- STEREO L/S 1 1/2". D.P. 5/- Edge 5K. P. Transistor, 5/6. Ideal 625 lines

### 80ohm Coax 8d. yd.

BRITISH AERIAL/TE AERIAL-AIR SPACED 40 yd. 20/- 60 yd. 30/- FRINGE LOW LOSES 1/6 yd. Ideal 625 lines

### WIRE-WOUND 3-WATT POTS.

Small type with small knob. Values 10 to 30 K. Carbon 30 K to 2 meg. 5/-

### WIRE-WOUND 3-WATT STANDARD SIZE POTS.

LONG SPINDLE. 10 OHMS to 100 K. 8/-

### VEROBORD 0.15 MATRIX

1 1/2 x 5in. 3/8. 2 1/2 x 3 1/2. 3 1/2 x 3 1/2. 3/8. 3 1/2 x 5in. 5/2. FINS 3p per packet 3/4. FACE CUTTERS 7/6. E.B.P. Board 0.15 MATRIX 2 1/2 in. wide 6d. per lin. 3 1/2 in. wide 9d. per lin. 5in. wide 1/- per lin. (up to 17in.). E.B.P.F. undrilled 4in. Board 10 x 8in. 3/-

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 in. sides. 7 x 4in., 6/-; 11 x 8in., 7/6; 11 x 7in., 9/6; 13 x 9in., 10/6; 15 x 14in., 15/-; 9 x 7 x 2in., 8/6; 14 x 11 x 2in., 14/6. ALUMINIUM PANELS 18 s.w.g. 12 x 12in. 6/6; 14 x 9in. 6/6; 12 x 8in. 4/6; 10 x 7in. 3/6; 8 x 6in. 2/6; 6 x 4in. 1/6. 1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 1/6 each. 1 p. 2-way, or 4 p. 2-way, or 4 p. 3-way 1/6 each. 1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way. 1 wifer 12/-, 2 wifer 15/-, 3 wifer 24/-, 4 wifer 30/-, 5 wifer 38/- TOGGLE SWITCHES. sp. 2/6; sp. dt. 3/6; dp. 3/6; ip. dt. 4/6

ALL PURPOSE HEADPHONES H.B. HEADPHONES 2000 ohms Super Sensitive 35/- LOW RESISTANCE HEADPHONES 3-5 ohms 39/6 DE LUXE PADDED STEREO PHONES 8 ohms 79/6

### "THE INSTANT"

BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER



200/250 v. A.C. Leadline S.A.E. 42/6 Post 2/6

★ ALL PURPOSE TRANSISTOR PRE AMPLIFIER BRITISH MADE ★ Response 25 c.p.s. to 25 Kc/s. 26 db gain. For use with valve or transistor equipment. Full instructions. 17/6 each Brand new. Guaranteed. Details S.A.E.

NEW TUBULAR ELECTROLYTICS CAN TYPES 2/350V 2/8 100/25V 2/- 16 + 18/500V 11/- 4/350V 2/8 200/25V 2/8 50 + 50/350V 7/- 5/350V 2/8 500/25V 3/- 80 + 100/350V 11/6 16/450V 2/8 8 + 16/450V 3/- 32 + 32/250V 3/8 32/450V 4/- 8 + 16/450V 4/- 32 + 32/450V 6/8 25/25V 2/- 16 + 16/450V 5/- 32 + 32 + 32/350V 8/6 50/50V 2/- 32 + 32/350V 6/- 100 + 50 + 50/350V 8/6 SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 2/-; 600, 1000mF 12V 3/6; 2000mF 25V 7/- CERAMIC 1pF to 0.01mF, 9d. Silver Mica 2 to 5000pF, 9d. PAPER 350V-0.1 9d. 0.6 2/8; 1mf 3/-; 2mf 150V 3/- 50V-0.001 to 0.05 9d. 0.1 1/-; 0.25 1/6; 0.47 5/6. 1.00V-0.001-0.002, 0.0047, 0.01, 0.02, 1/8; 0.047, 0.1, 2/8. SILVER MICA. Close tolerance 1%, 5-500pF 1/-; 580-2,200pF 2/-; 2.700-5,600pF 3/6; 6,800pF-0.01, mfd 6/8; etc. TWIN GANG. "0-0" 20pF + 176pF, 11/-; 365pF, miniature 11/-; 500pF standard with trimmers, 15/-; 500pF midsize trimmers, 8/-; 500pF slow motion, standard 9/-; smallest 3-gang 500pF 22/- Single "0.385pF 8/- TWIN 11/- SHORT WAVE. Single 10pF, 25pF, 50pF, 75pF, 100pF, 150pF, 200pF, 10/8 each. TUNING. Solid dielectric, 100pF, 300pF, 500pF, 7/- each. TRIMMERS. Compression 30, 50, 70pF, 1/- 100pF, 150pF, 1/8; 250pF, 1/8; 600pF, 750pF, 2/-; 1000pF, 2/6. RECTIFIERS CONTACT COOLED 1wave 60mA 7/6; 85mA 9/6. SILICON BYZ13 8/-; BY100 10/- Full wave Bridge 75mA 10/-; 150mA 19/6; TV rectis. 10/- NEON PANEL INDICATORS 250v. AC DC Red. Amber 5/- RESISTORS. Preferred values, 10 ohms to 10 meg. 1/2 w. 1/2 w. 1 w. 20% 3d. 1 1/2 w. 8d. 2 w. 1/-; 1 w. 10% 6d. HIGH STABILITY. 1/2 w. 1% 10 ohms to 10 meg. 2/- DHTO 5%. Preferred values 10 ohms to 22 meg. 9d. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K. 2/- each; 2 1/2 watt 1 ohm to 2 ohms. 2/-

## Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key 1in. 16/- 1in. 17/6 1in. 18/6 1in. 24/- 2 1/2 in. 44/3 1in. 16/- 1in. 19/6 1in. 20/6 1in. 22/- 2 1/2 in. 57/3 1in. 16/9 1 1/2 in. 19/6 1 1/2 in. 21/6 2in. 39/- 1in. sq. 36/8

TRANSISTOR MAINS POWER PACKS. FULL WAVE 9 volt 500mA. Size 4 1/2 x 2 1/2 in. Metal case. 49/6 Cracks finish. Output terminals. On switch. 44/3 Half Wave 9 volt 50mA. Size 2 1/2 x 1 1/2 in. Snap terminals 32/6 9 volt 500mA. TRANSFORMER ONLY. 2 1/2 x 1 1/2 x 1 1/2 in. 60/6

## MAINS TRANSFORMERS

250-0-250 50 mA. 6.3 v. 2 amp, centre tapped 19/6 250-0-250 80 mA. 6.3 v. 2.5 a. 6.3 v. 1 a. or 8 v. 2 a. 38/- 350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 39/- 300-0-300 v. 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. 45/- MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 15/- MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 17/8 HEATER TRANS. 6.3 v. 1 a. 10/6; 6.3 v. 4 a. 15/6 DHTO tapped sec. 1.4 v. 2.5 a. 3.5 a. 6.3 v. 1 amp. 15/6 GENERAL PURPOSE LOW VOLTAGE. On switch. Outputs 3, 4, 5, 8, 9, 10, 12, 15, 18, 24 and 30 v. 2 a. 38/- 1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, 38/- AUTO TRANSFORMERS 0-115-230 v. Input/Output, 60w. 18/6; 150w. 38/-; 500w. 25/-; 1000w. 21/2 CHARGER TRANSFORMERS. Input 200/250V for 6 or 12v. 1 1/2 in. 24/-; 4 amp. 38/- FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 8/-; 2 amp. 11/-; 4 amp. 17/-

COAXIAL PLUG 1/3, AMP. SOCKETS 1/3. LINE 3/6. OUTPUT BOXES. 8 pin. 4/6. BALANCED TWIN FEEDERS. 7/-; 80 ohm or 300 ohms. JACK SOCKET Std. open-circuit 8/6, closed circuit 4/6; Chrome Lead Socket 7/6. Phono Plugs 1/-; Phono Socket 1/-; JACK PLUGS Std. Chrome 3/6; 3 1/2 mm Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/6; 6-pin 2/- DIN SOCKETS Lead 3-pin 3/6; 6-pin 5/-; DIN 3-pin 3/6; 6-pin 5/- VALVE HOLDERS. 9d.; CERAMIC 1/-; CANS 1/-

## E.M.I. 13 1/2 x 8in. LOUSPEAKERS

With flared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. Speech coil, 3 or 15 ohm. Also with twin tweeters. Complete with crossover, 3 or 8 or 15 79/6 ohms. 10 watt. Recommended Teak Cabinet Size 16 x 10 x 8 in. £5

Triple speaker system combining on ready cut haffle. 1 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 16 x 10 x 9 in. Modern Scandinavian fluted front design for Mini-Module. £5 Post 5/-

## MINI-MODULE LOUSPEAKER KIT

10 WATT 65/- CARRIAGE 5/-

Triple speaker system combining on ready cut haffle. 1 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 16 x 10 x 9 in. Modern Scandinavian fluted front design for Mini-Module. £5 Post 5/-

## ALL MODELS "BAKER SPEAKERS" IN STOCK

## BAKER 12in MAJOR £8



30-14,500 c.p.s. 12in double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Moddle kit, 30-17,000 c.p.s. with tweeter, crossover, haffle and instructions. £10.19.6

BAKER "GROUP SOUND" SPEAKERS-POST FREE "Group 25" 12in 25 watt 6gns. "Group 35" 12in 35 watt 8 1/2 gns. "Group 50" 15in 50 watt 18gns.

TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 10 or 12in round Loudspeakers. £9.0.0. For 15 x 8in or 8in round Loudspeakers. £5.0.0. For 10 x 8in or 8in round Loudspeakers. £4.0.0. LOUSPEAKER CABINET WADDING 18in wide. 2/6it

Horn Tweeters 2-16kc/s, 10W 8 ohm 29/6. De Luxe Horn Tweeters 2-18 Kc/s, 15W, 18 ohm 69/6. EMI Plastic Cone 2 1/2 in 8 ohm 17/6; Crossovers 3 or 8 or 15 ohm 18/6. SPECIAL OFFER! 80 ohm 2 1/2 in. dia.; 35 ohm 3 in. 25mm. 3in. dia.; 6 x 4in.; 8 x 3in.; 8 x 5in. 17/6 EACH 15 ohm, 7 x 4in.; 8 x 5in. 3in. 2 1/2 in. 3in. 5in. 5 x 3in. 7 x 4in. LOUSPEAKERS P.M. 3 OHMS. 6in 22/6; 8 x 5in. 21/-; 8 x 2in. 21/-; 8in 35/-; 10 x 6in 50/- 5in. WOOFER 8 watts max. 20-10,000 cps. 8 or 15 ohm 39/6. ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm 50/- 8in LOUSPEAKER. TWIN CONE 15 ohm 35/- RICHARD ALLAN 10 of 12in Twin cone 3 or 15 ohm 39/6. OUTPUT TRANS. EL84 etc. 5/- MIKE TRANS. 50:5 5/- SPEAKER COVERING MATERIALS. Samples Large S.A.E.

## THE FAMOUS "MULLARD 510"

£16.19.6 Post 10/6



Main power amplifier and 2 valve pre-amplifier. Silver grey lacia panel. Volume, treble, bass controls. Function switch: Radio, Tape 1, Tape 2, Mic, Gram LP, Gram 78. Tape output socket. Valves: 2 x EL84, 3 x EP88. 1 x EC83B, 1 x EZ81. Ultra linear Parmeko output transformer. 20 db negative feedback. 10 watt mono. 3 and 15 ohm output. Brand new. Guaranteed.

## ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES. ILLUSTRATED EAGLE CATALOGUE 5/- Post free.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. 79/6 BARGAIN DE LUXE TAPESPLICER Cuts. trims, joins for editing and repairs. With 3 blades. 22/6 BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add music, highlights and sound effects to recordings. With mic Microphone, records, tape and tuner with separate controls into single output. 9 volt. 59/6 BARGAIN FM TUNER. 88-108 Mc/s Six Transistor. Printed Circuit. Calibrated slide dial tuning. £9.10.0 Walnut Cabinet. Size 7 x 5 x 4 in.

FM STEREO MULTIPLEX ADAPTOR 99/6

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. 69/6

### ★ RADIO BOOKS ★ (Postage 9d.)

Practical Transistor Receivers 4/6 Practical Radio Inside Out 5/6 Super-sensitive Transistor Pocket Radio 3/6 Radio Valve Guide. Books 2, 3, or 4 ea. 5/- No. 5 ea. 6/8 Short Wave Finding 405/625 Lines 8/6 Thru-Wave Transistor Receivers 6/6 Transistor Communication Sets 6/6 Sub-Miniature Transistor Receivers 6/6 Wireless World Radio Valve Data 10/- International Radio Stations Guide 2/6 Transistor Circuits for Radio Controlled Models 7/6 Valves, Transistors and Diodes equivalents Manual 10/6

3 Inch MOVING COIL METERS BRITISH MADE Various calibrations/movements. 500 Microamp; 1 Milliamper; 60-0-60 Microamp. etc. S.A.E. For list. 37/6

## MAINS ELECTRIC MOTORS

(120v. or 240v. AC). Size 2 1/2 x 2 1/2 in. Clockwise 1,200 r.p.m. of load. Heavy duty 4 pole 50mA. Spindle 1/2 x 3/20. BARGAIN 17/6 EACH PRICE 3 for 50/-; 6 for 90/-




Minimum Post and Packing 2/6. RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME. RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, WEST CROYDON Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) List 1/- Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-884-1665

# M. & B. RADIO

38 BRIDGE END, LEEDS 1

Telephone: 0532-35649

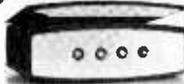**STEREO CABINETS.** A beautifully finished polished wood cabinet supplied in original carton. Size approx. 22 x 16 x 8in. New 47/6 plus 6/6 carriage.



**TELEMETERS.** A well finished cabinet containing lots of useful items for the constructor. Endless tape unit and tape head, 2 motors, auto and mains transformers, miniature valve I.F. strip etc. Ideal for modifying or stripping. 77/6 plus 7/6 carr.



**STETHOSCOPE HEADSETS.** Brand New. Ideal for stereo or mono. Low impedance. 27/6 plus 3/6 pp.

**MICROPHONES.** Radiotelephone type, used. 5/- plus 2/- pp.

**TRANSISTORISED 2 METER CONVERTERS.** Please state preference of I.F. frequency when ordering. £7.15.0 plus 5/- pp. 4 metre models available at the same price. VHF Marine band model £8.5.0 plus 5/- pp.

**12V TRANSISTOR INVERTERS.** 12vdc input. 275vdc at 150mA output. Size of aluminium case 1 1/2" x 2 3/4" x 4" approx. Size of transformer approx. 1 1/2" x 2" x 2". £3.5.0 plus 5/- pp.

**2 to 3 WATTS INTEGRATED CIRCUITS.** Tested c/w circuit. £1 plus 1/- pp.

**60 UNTESTED TRANSISTORS 5/- plus 1/- pp.**

**60 UNTESTED DIODES 2/6 plus 1/- pp.**

**BYX25 800R Silicon diodes 800 Div 16amps on heat sink 5/- plus 1/- pp.**

**455Kc/s FM Transistorised I.F. strips.** Faulty usually low in gain but new. 6 transistors. 12/6 plus 1/- pp.

**USED TESTED VALVES.** 6AQ5/EL90 3/-, 6BJ6 1/6, 6BH6 1/6. 12AX7/ECC83 2/6, 5U4 6/-, ECF80 2/-.

**Aerial change over relays 6v, 12v or 50v 4/- plus 1/6 pp.**

**UHF Coaxial Aerial change over relays.** BNC Sockets. 27/6 plus 2/6 pp.

**BRAND NEW HEADPHONES.** A well known make of headset which combines quality with comfort. Mono or Stereo. 54/- plus 4/- pp.

**PLEASE NOTE NEW ADDRESS. NO CONNECTION WITH FIRM PREVIOUSLY AT THIS ADDRESS**

**LIST OF OTHER EQUIPMENT PLEASE SEND 6d. PLUS S.A.E.**



# BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board—  
obtainable from your local Retailer

Trade enquiries to:  
**NORMAN ROSE (ELECTRICAL) LTD.**  
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:  
**VERO ELECTRONICS LTD.**  
Industrial Estate, Chandler's Ford, Hants

FREE LIST!  
SEND S.A.E.  
FOR BUMPER FLOG  
LIST

FANTASTICALLY POPULAR  
★ JASON TAPE ★

We offer you fully tensilized polyester mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports **TRY ONE AND PROVE IT YOURSELF!**

## TECHNICAL TRADING

BARGAIN SPRING  
SALES AT ALL  
BRANCHES

- ★ LONDON (MUS 2639)
- ★ 10 Tottenham Court Road
- ★ PORTSMOUTH (Tel. 22034)
- ★ 358-362 Fratton Road
- ★ SOUTHAMPTON
- ★ 72 East Street (Tel. 25851)
- ★ BRIGHTON (Tel. 23975)
- ★ 8 Queen's Road

Standard Play		Long Play	
3in. 150ft.	1/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 3/4in. 900ft.	10/6	5 3/4in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,800ft.	28/-
5in. 1,200ft.	15/-	5 3/4in. 2,400ft.	34/-
5 3/4in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,100ft.	27/-	Quadruple Play	
		3in. 600ft.	8/6

Postages 1/- reel.  
Post Free less 5% on three reels.  
Quantity and Trade enquiries invited.

All mail orders to DEVONIAN COURT, PK. CRES. PLACE, BRIGHTON (Tel 880722)

# the BIG one . . .



**350**  
pages  
**8,000**  
components  
**1,500**  
illustrations

The **HOME RADIO CATALOGUE** is the complete answer to the problem of tracking down components. This Catalogue, one of the largest ever compiled, is a must if you are interested in Radio and Electronics. With each catalogue is a Book Mark giving Electronic Abbreviations, an Order Form and Addressed Envelope. All for only 12/6 (8/6 plus 4/- Post, Packing and Insurance). In addition every catalogue contains 6 vouchers, each worth 1/- when used as indicated.

And for users of our catalogue . . . a **CREDIT ACCOUNT SERVICE** to simplify and speed up your orders

You can now order components just by picking up a telephone any time of day or night, **Sundays included!** No need to bother with postal orders, cheques, registering envelopes every time you order. Prepaid envelopes and order forms are provided and only one payment is required each month. So simple—8,000 items as near to you as your telephone. Write for details or 'phone 01-648 8422.

Send the  
Coupon with  
cheque or P.O.  
for 12/6

The price of 12/6 applies only to catalogues purchased by customers residing in the U.K.

Please write your Name and Address in block capitals

Name.....

Address .....

**HOME RADIO (Components) LTD.,**  
Dept. PW, 234-240 London Road, Mitcham, CR4 3HD



## ★ sectional components list ★

### RF Section

L1, C1, C2, C3, R1 incorporated in VFO2 coil (Electroniques).  
 C4 100pF mica  
 C5 0.25 $\mu$ F 350V  
 C6 0.02 $\mu$ F 500V disc ceramic  
 C7 100pF mica  
 C8 1800pF 1kV disc ceramic  
 C9 " " " "  
 C10 " " " "  
 VC1 100pF air spaced variable  
 VC2 500pF " " "  
 VC3/4 2x500pF or similar ganged capacitor  
 R2 33k $\Omega$  1W R6 22k $\Omega$  1W  
 R3 10k $\Omega$  3W R7 1.2k $\Omega$   $\frac{1}{2}$ W  
 R4 100k $\Omega$   $\frac{1}{2}$ W R8 6.8k $\Omega$  2W  
 R5 4.7k $\Omega$  2W  
 L2 Denco "Blue" Range 2  
 L3 65 turns 22 s.w.g. enam. on 1in. former  
 V1 6C4. B7G holder with shield  
 V2 EF91. " " " "  
 V3 5763. B9A holder " "  
 VR OA2 voltage regulator. B7G holder  
 RFC 2.6mH 60mA RF choke

### Audio Section

C11 2 $\mu$ F 350V C14 0.01 $\mu$ F 150V  
 C12 1800pF disc C15 25 $\mu$ F 25V  
                   ceramic C16 1800pF 1kV disc  
 C13 5000pF mica                   ceramic  
 R9 1M $\Omega$   $\frac{1}{2}$ W R13 22k $\Omega$   $\frac{1}{2}$ W  
 R10 220k $\Omega$   $\frac{1}{2}$ W R14 470k $\Omega$   $\frac{1}{2}$ W  
 R11 470k $\Omega$   $\frac{1}{2}$ W R15 270 $\Omega$  1W  
 R12 100k $\Omega$   $\frac{1}{2}$ W R28 3.3k  $\frac{1}{2}$ W  
 V4A/V4B 12AX7 B9A holder with shield  
 V5 6BW6 B9A holder  
 T1 80-100mA type pentode matching transformer  
 Speaker: WB 2/3 ohm  $\frac{3}{4}$ in. or similar

### Power Supply

Choke Parmeko 120mA 5H  
 R16 10 $\Omega$  1W  
 R17 25 $\Omega$  1W  
 R18 25 $\Omega$  1W

C17 32 $\mu$ F 450V  
 C18 8 $\mu$ F 450V  
 Rectifiers, 2x5E-05  
 250mA fuse and holder  
 T2 Parmeko P2931, 250/0/250V 150mA, 6.3V 4A

### Receiver Section

C19 100pF mica C26 200pF mica  
 C20 100pF " C27 47pF mica  
 C21 0.02 $\mu$ F 500V disc C28 400pF silver mica  
                   ceramic                   (padder)  
 C22 0.02 $\mu$ F disc C29 0.25 $\mu$ F 150V  
                   ceramic C30 0.02 $\mu$ F 500V disc  
 C23 0.25 $\mu$ F 350V                   ceramic  
 C24 0.02 $\mu$ F 500V disc C31 200pF mica  
                   ceramic C32 100pF mica  
 C25 100pF mica  
 R19 1M $\Omega$   $\frac{1}{2}$ W R24 22k $\Omega$  1W  
 R20 33k $\Omega$  1W R25 68k $\Omega$  1W  
 R21 1M $\Omega$   $\frac{1}{2}$ W R26 1M $\Omega$   $\frac{1}{2}$ W  
 R22 33k $\Omega$  1W R27 100k $\Omega$   $\frac{1}{2}$ W  
 R23 47k $\Omega$   $\frac{1}{2}$ W

VR1 25k $\Omega$  linear pot V7 ECH81 B9A holder  
 VR2 500k $\Omega$  log pot V8 EBF89 B9A holder  
 V6 6BA6 B7G holder  
 L4 1.8MHz bandsread aerial coil } Types 1-8/46  
 L5 " " mixer " } Electroni-  
 L6 " " osc. " } ques

1FT1/2 Denco 1FT11/465  
 VC5 50pF air spaced tuning  
 VC6/7 2-gang 20pF or similar

### Miscellaneous

Metal cabinet with panel 15x9x8in. (H. L. Smith & Co.,  
 287/9 Edgware  
 Road, W.2.)  
 13x8x2 $\frac{1}{2}$ in. chassis Type 1 " "  
 Pair 4in. Type C panel brackets " "  
 50mA miniature meter: 8-pole 2-way rotary switch:  
 Two DL50A ball drives with flange for pointer (Home  
 Radio, Mitcham): Two co-axial sockets: (Micro-  
 phone and, aerial). Knobs, etc. Panel fitting lamp  
 holder. 6.3V lamp. 2-SPST toggle switches.

**Regulator VR.** This provides 150V for V1 and the screen grid of V2 with the power supply as given. If a 250v or similar supply is to be utilised, and VR fails to strike when switching to transmit, R3 can be reduced to about 6.8k $\Omega$  or R5 to 2.2k $\Omega$ .

**Buffer-amplifier.** The anode coil L2 of V2 is a medium-wave type broadcast band coil, with primary removed. Due to the low parallel capacitance, this can be tuned to about 160 metres. When first setting up the transmitter, connect a milliammeter between test point G and chassis with positive to chassis. Set the v.f.o. to about 1.9MHz and adjust the core of L2 for maximum grid current. This should be about 3mA, falling off only slightly towards 1.8MHz and 2.0MHz. R7 is included so that grid current can be measured without disconnecting R6.

**RF Power Amplifier.** The supply is 300V, so an anode current of 30mA on the panel meter represents an input of 9 watts. If the equipment is later used on 80m, the current can be 40mA, or about 12 watts.

**TO BE CONTINUED**

### Going HI-FI —continued from page 116

A bass filter might be needed to suppress rumble from the motor and treble filters can help to take roughness and background noise out of reproduction and these should be provided with switches to bring them in and out at will.

Loudness controls are controversial. These vary the frequency response with sound volume to counteract the variations in sensitivity of the ear to different frequencies at different volume levels. However, a switch separate from the volume control, to reduce volume and adjust tone appropriately (sometimes called a "quiet" switch) is most useful.

If a cheaper cartridge is to be used for the time being it would be as well to include this in the demonstration and if at all possible the demonstration should take place in one's own home. At least, by eliminating most of available equipment from individual consideration on the lines given above, the demonstration required has been reduced to manageable proportions with reasonable hope of a conclusive result. ■

### MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 3/6 each. 26/- dozen, your assortment.

**WATERPROOF HEATING ELEMENT**  
26 yards length 70W. Self-regulating temperature control. 10/- post free.

### MICRO SWITCH

5 amp. changover contacts, 1/9 each, 18/- doz. 15 amp Model 2/- each or 21/- doz.



### TOGGLE SWITCH

3 amp 250v. with fixing ring. 1/6 each, 15/- doz.

### CONSTRUCTORS PARCEL

1. Plessey miniature 2 gang tuning condenser with built in trimmers and wave gang switch. 2. Ferrite slab aerial with coils to suit the above tuning condenser. 3. Circuit diagram giving all component values for 6 transistor circuit covering full medium wave and the long wave band around Radio 2. The three items for only 7/6d which is half of the price of the tuning condenser alone.

### 10 AMP 24V BATTERY CHARGER

Ideal unit for garage, boat station etc. £22.10.0d. each plus carriage and cost.

### BEHIND THE EAR DEAF-AID

Made by a very famous maker. Thoroughly overhauled, cleaned and re-conditioned. Guaranteed 6 months. Regular price around £50. Our price £10.

### ISOLATION TRANSFORMERS 200-250 Mains

A must if you work on mains equipment. Prevents accidents and shocks even in damp conditions. Input and output separately screened by connection block. 100 watt £3.10.0. 250 watt £5.

### SLOW MOTION DRIVES

For coupling to tuning condensers etc. One end in. shaft, the other end fits a 1/4 in. shaft with grub screws. Price 4/6 each 48/- dozen.

### LARGE PANEL MOUNTING MOVING COIL METERS

Size 6in. x 4in. Centre zero 200-0-200 micro amp made by Sangamo Weston. Regular price probably £8. Our price 59/6. ditto but 100-0-100 79/6.

A.C. Ammeter 0-5 amps. flush mounting—moving iron. Ex equipment but guaranteed perfect 29/6.

### CIRCUIT BOARDS

Heavy copper on 3/32 paxolin sheet ideal for making power packs etc. as sheet is very strong and thick enough to allow copper to be cut away with hacksaw blade. 5in. x 5in. 1/6 each. 15in. x 5in. 4/6d. each.

6KV Auto-transformer in ventilated sheet steel case—tapped 110v-140v-170v-200v-230v. Ex equipment but guaranteed perfect £19.10.0. carriage at cost.

### PP3 BATTERY ELIMINATOR

Run your small transistor radio from the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 9/6 each.



### REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature. 1in. long x approximately 1/4in. diameter. Will make and break up to 1A up to 300 volts. Price 2/6 each. 24/- dozen.

Standard. 2in long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each. 18/- per dozen.

Flat. Flat type. 2in. long, just over 1/16in. thick, approximately 1/4in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 9/6 each. £3 per dozen.

Small ceramic magnets to operate these reed switches 1/9 each. 15/- dozen.

### 0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- doz.



### SUB-MINIATURE MOVING COIL MICROPHONE

as used in behind the ear deaf aids Acts also as earphone size only 1/4in. x 1/4in. Regular price probably £3 or more. Our price 19/6. Note these are ex-equipment but if not in perfect working order they will be exchanged.

### INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade chips, definitely not sub-standard or seconds. The ICs are all single silicon chip General Purpose Amplifiers. Regular price of each is well over £1 each. Full circuit details of the ICs are included and in addition you will receive a list of 50 different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only £1 post paid; or List and all data 10/- post free. Credited when you order IC's value of 30/- and upwards.



### 24 HOUR TIME SWITCH

Mains operated. Adjustable Contacts give 2 on/off per 24 hours. Contracts rated 15 amps, repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 39/6 with Perspex cover, plus 3/6 postage and insurance, a real snip which should not be missed.

### DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets and on/off switch with neon warning light (in metal box). Takes standard 13 amp fused plugs Supplied complete with 7 feet of heavy cable. 39/6 wired up ready to work plus 4/6 post & insurance.

5 amp model 34/6 plus 4/6 p. & i.  
15 amp model 45/- plus 4/6 p. & i.

### THIS MONTHS SNIP

#### REPAIRABLE RADIOS

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 1 1/4 in.—complete with soft leather zipped bag. Specification:— Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency: 465 Kc/s or 455 Kc/s. For output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. These radios require attention. Circuit diagram is not available. Price only 24/6 plus 2/6 post and insurance rechargeable batteries 8/6 post. Plug in mains charge 12/6.



#### VARIABLE CONTROLLERS

With these you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to dim lighting. We offer a range of these, ex-equipment but little used and in every way as good as new. Any not so, will be exchanged or cash refunded.  
2 amp £4.19.6. 6 amp £9.10.0. 8 amp £12.19.6. 10 amp £15.19.6.



#### 15, 30 & 100 WATT HI-FI SPEAKERS

FULL BT 12 INCH LOUDSPEAKER. This is undoubtedly one of the finest loudspeakers that we have ever offered. Produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwell—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—Specify 3 or 15 ohms—Mains resonance 60 c.p.s.—Chassis Diam. 12in.—12in. over mounting lugs—Baffle hole 1 1/4 in. Diam.—Mounting holes 4, holes—1/4 in. diam. on pitch circle 1 1/4 in. diam.—Overall height 5 1/4 in. A £6 speaker offered for only £3.19.6 plus 7/6 p. & p. Don't miss this offer. 15in. 25 watt £7.19.6 18in. 100 watt £19.10.0.



#### THE 5.5 WATT STEREO AMPLIFIER

Made by one of our most famous makers for a de-luxe player. This amplifier has a quality of reproduction much better than average. Using a total 16 transistors and a generously sized mains power pack. Controls include bass, treble, balance and volume. Suitable for 8-16 ohms impedance speakers with crossovers for tweeter mid-range and bass thus giving option of 1, 2 or 3 speakers per channel. Offered at about one third of its original price only £9.19.6d. plus 6/6d post and insurance.

#### 1 HOUR MINUTE TIMER

Made by famous Smiths company, these have a large clear dial, size 4 1/2 x 3 1/2, which can be set in minutes up to 1 hour. After preset period by the bell rings. Ideal for processing, a memory jogger or for adding simple lever, would operate motor-switch 22/6.



A.C. Condensers—these make good voltage droppers for working low voltage appliances from AC mains—the big advantage being there is no heat. Also useful in power factor correction, motor starting and in DC circuits where reverse voltage is encountered.

1.5 mfd 400v 3/6	5 mfd 570v 9/6	12 mfd 250v 11/8
2 mfd 440v 4/6	6.25 mfd 250v 8/6	15 mfd 250v 13/6
3.4 mfd 440v 6/6	8 mfd 250v 9/6	20 mfd 275v 16/6
3.5 mfd 225v 6/6	8 mfd 440v 11/6	

Gro-lux Lighting. Special tubes give light rich in U.V. and other rays necessary for plants and fish kept indoors away from natural sunlight. 12in. 8 watt tube 22/6—control kit comprising choke and starter—tube ends and clips—starter holder and diagram 19/6—post and insurance 3/6 on either or 4/6 on both items.



#### VARYLITE

Will dim incandescent lighting up to 600 watts from full brilliance to out. Fitted on M.K. flush plate, same size and fixing as standard wall switch so may be fitted in place of this, or mounted on wall. Price complete in heavy plastic box with control knob £3.19.6.

### NEED A SPECIAL SWITCH

Double Leaf Contact. Very slight pressure closes both contacts, 13/8 each, 12/- doz. Plastic push-rod suitable for operating, 1/- each, 9/- doz.



50-Way Connector Block. Heavy duty block, size 2 1/4 in. x 2 1/4 in. x 1 1/4 in. approximately. Each of the 50 ways has a multi cable inlet and outlet designed for easy connection. Also, each way has 2 test sockets and a disconnecting plug. Ideal for inserting ammeter or other device without breaking circuit, offered at 69/6 each, which is only a fraction of the regular price, postage and insurance 5/6.

Under-floor Heating Cable. 200ft. lengths, suitable for dissipating 1,000 watts at 80 volts. Join three in series to make a 240 volt mains operated element of 3kW. Price 20/- per length, 4/6 post on any quantity.

3-Core Leads. Heavy duty 23/36, average length 5ft. 10/- per dozen lengths, plus 4/6 P. & I.

Paper Motors. Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. 30/- each.



Instrument Knobs. 1/4 in. dia. head with 1/4 in. shank for flatted 1/4 in. spindle, 9d. each, 8/- dozen. Ditto but with metal disc, 1/- each, 11/- dozen.

Midget Output Transformer. Ratio 140:1. Size approx. 1 1/4 in. x 1/2 in. x 1/2 in. primary impedance 450 Ω. Connection by flying leads. 4/6 each 48/- doz.

Midget Output Transformer. Ratio 80:1. Size approx. 1 1/4 in. x 1/2 in. x 1/2 in. Primary impedance 132 Ω. Printed circuit board connection. 5/6 each. £3 doz.

4-Gang Air Spaced Tuning Condenser for AM/FM circuits. AM rf section 200 pf ac section 80 pf both with trimmers.—FM rf section 9.5 pf ac section 11.2 pf—integral slow motion drive 9/6 each.

Mains Connector. A quick way to connect equipment to the mains safely and firmly—L, N, and E, coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7.029 cables. 12/6 each



#### DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6, plus 2/6 post and insurance. Made up model also available 37/6 plus 2/6 p. & p.



#### ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled—so it is extremely accurate. The small dial enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 39/6, less than the value of the clock alone—post and insurance 2/9.



#### MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 19/6, plus 3/6 postage.

**ELECTRONICS (CROYDON) LTD**  
Dept. PW, 266 London Rd., Croydon CP0-2TH  
Also 102/3 Tamworth Road, Croydon

# R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.  
—5.30 p.m.  
Closed Sat. 1.30—2.30 p.m.  
Open Daily to Callers

Tel. 769-0199/1649

1A7	7/9	6BR8	12/6	6K7GT	4/6	10C1	20/-	25L6GT	7/-	150B2	11/6	DK32	7/9	ECH35	11/6	EY86	7/-	PCF80	6/9	PY801	9/6	UCL83	10/-
1D5	7/6	6B8T	25/-	6K8	2/9	10C2	12/6	25Y5	6/-	150C4	9/6	DK91	6/-	ECH42	13/-	EZ35	6/-	PCF82	6/8	R2	7/8	UF41	10/6
1H5	7/6	6BW6	14/6	6K8M	11/6	10E1	14/9	25Z4	6/3	801	9/6	DK92	9/-	ECH81	5/9	EZ40	9/-	PCF84	8/-	R19	7/9	UF89	7/8
1LD5	6/-	6BW7	13/-	6K8G	3/-	10F3	18/-	25Z5	8/-	807	9/-	DK96	7/9	ECH83	8/6	EZ41	9/6	PCF86	9/-	R45/500	80/-	UL41	12/-
1N5GT	8/-	6C4	5/-	6K8GT	7/-	10F9	10/8	25Z6	8/6	813USA	1200/-	DL66	25/-	ECL80	7/-	EZ80	5/6	PCF801	9/9	5130	40/-	UL34	7/-
1R5	6/-	6CG5	5/-	6K25	15/-	10F18	8/-	28D7	9/3		75/-	DL93	4/-	ECL83	10/3	GY501	15/-	PCF805	15/-	BP41	3/6	U07	21/-
1B4	5/6	6C6	3/9	6L1	12/-	10L1	8/-	30C1	6/9	813	15/-	DL94	6/9	ECL86	9/-	GZ30	10/-	PCF806	13/-	BP61	3/6	U06	21/-
1S5	4/6	6C8	6/-	6L6	7/9	10LD11	10/6	30C15	15/-	866A	5/3	DL95	7/9	ECLL80030	20/-	GZ32	10/-	PCF808	15/6	RTV280	80/-	U08	21/-
1T4	4/-	6CDG6	24/-	6L18	6/-	10P13	13/6	30C17	16/-	954	5/3	DL96	7/8	EF9	20/-	GZ34	11/-	PCF82	7/9	85	UT9	8/3	
3A4	4/-	6CG6	7/6	6Q7G	6/-	11E3	7/6	30C18	15/-	1625	6/8	DL97	DM70	8/-	EF37A	7/-	HM309	20/-	PCL53	10/3	8U35	13/6	
2Q4	7/9	6CW4	13/6	6Q7GT	8/6	12A7E	4/9	30F5	17/-	40Z2AR	67/-	DM70	8/-	EF37A	7/-	HM309	20/-	PCL54	8/6	8U2150	12/6	U41	8/6
3Q5	7/-	6D6	3/9	6SA7M	7/-	12AT7	6/-	30FL1	15/-	5763	12/-	DT86	6/-	EF39	5/6	KT86	18/-	PCL54	8/6	8U2150	12/6	U41	8/6
3B4	6/3	6E5	7/8	68C7	7/-	12AU7	5/9	30PL14	15/6	7475	14/-	E88CC	12/-	EF50	5/-	K766	30/-	PCL56	9/3	TDD4	8/6	VMP4G	17/-
3V4	6/9	6F1	12/6	68G7	6/-	12BL7	6/-	30PL16	17/-	A61	9/6	EA50	3/6	EF80	4/6	KT81	35/-	PD500	29/10	U10	7/6	VP4B	25/-
5U4G	5/6	6F6G	5/-	68J7	6/-	12BA6	6/-	30L17	17/-	ATP4	2/3	EACB80	6/6	EF85	7/-	KT81 (7C5)	PEN44	20/-	U14	7/6	VR105/30	6/6	
5V4G	8/-	6F8G	5/6	68K7GT	4/9	12BE6	6/3	30P4	22/6	ATP5	12/-	EAF42	10/-	EF86	6/6	KT88	34/-	PEN45	7/-	U25	15/6	VT25	15/-
5Y3GT	6/-	6F11	6/6	68L7GT	6/-	12C8GT	6/-	30P12	16/-	ATP7	8/6	EB41	10/-	EF89	5/6	KT88	34/-	PEN45	7/-	U26	15/6	VT31	80/-
5Z4G	7/-	6F13	6/6	68N7GT	5/6	12E1T	20/-	30P19	15/-	AU2	80/-	EB91	3/-	EF91	3/6	KTW61	12/6	PEN46	4/-	U26	15/6	VT31	80/-
6/30L2	15/-	6F14	12/6	68Q7	7/6	12F5GT	2/6	30PL1	16/-	AU5	8/9	EB33	6/6	EF92	2/6	KTZ41	6/-	PL36	10/9	U78	4/6	VI111	8/9
6A7	15/-	6F23	16/-	6U4GT	12/-	12J7GT	6/6	30PL13	18/6	AZ1	8/-	EB41	9/9	EF98	15/-	ML4	17/6	PL81	9/6	U191	13/9	VU120	12/6
6A8G	12/6	6F24	14/-	6U5G	7/9	12K8GT	7/6	30PL14	15/-	AZ31	10/-	EB90	4/9	EF183	6/6	ML6	7/6	PL82	8/6	U251	16/3	VU508	35/-
6ACT	4/-	6F25	15/-	6V6M	12/-	12K8GT	8/-	35A5	12/6	CBL31	16/-	EBF90	7/6	EF184	7/6	MSP4	10/-	PL83	7/6	U301	12/6	VB11	13/6
6AK5	5/-	6F28	14/-	6V6G	4/6	12Q7GT	6/-	35L6	9/-	CCH35	15/-	EBF83	9/-	E132	3/6	MU14	7/6	PL84	7/6	U403	6/6	XE1-5	5/-
6AM6	4/6	6F32	2/9	6V6GT	4/6	12R7	8/-	35W4	4/6	CL3	6/6	EBF89	6/6	EL33	12/6	MX40	12/6	PL500	14/6	U404	7/6	XP1-5	5/-
6AM6	3/6	6G6	3/6	6X4	4/6	128G7	6/-	35Z3	10/-	CV450	25/-	EBL1	14/-	EL34	10/6	N78	18/-	PL504	10/6	U801	23/6	XBG1-5	110/-
6AQ5	6/3	6H6	3/-	6X5G	4/6	128H7	3/6	35Z4GT	8/6	CV30	12/6	EBL12	12/-	EL38	22/6	N108	25/-	PL508	29/-	UACB80	6/6	Y63	7/8
6A8TG	15/-	6J5M	9/-	6X5GT	6/-	128J7	3/9	35Z5	6/-	CV31	8/6	EY11	27/6	EL41	11/-	NGT1	3/6	PL509	29/-	UAF42	10/6	Y63	7/8
6AT6	4/9	6J5G	4/-	7B6	11/6	128K7	4/9	37	6/6	DAC32	7/-	EC90	5/-	EL42	11/6	NGT7	55/-	PL802	16/6	UCB41	9/3	3E01	65/-
6AU6	5/-	6J6GT	5/6	7B7	7/8	128R7	5/-	42	6/6	DAF91	4/6	ECC81	6/-	EL44	4/9	OA2	6/-	PX4	24/-	UCB91	9/3	3PT	29/-
6E4G	20/-	6J6	3/6	7C3	22/6	14H7	9/6	50B5	6/6	DAF66	7/8	ECC82	5/6	EL93	6/6	OC3	5/-	PX25	27/6	UBF80	7/-	SCP1	55/-
6B5C	2/-	6J7M	8/6	7C4	15/-	19AQ5	5/-	60C5	6/3	DCC90	20/-	ECC83	6/3	ELL80	20/-	OZ4	4/6	PY33	10/9	UBF89	7/8	CV1526	65/-
6BA6	5/-	6J7G	6/-	7D6	8/-	20D1	10/-	60CD6G	31/-	DP33	8/-	ECC84	5/6	EM34	18/-	PC86	11/6	PY81	5/9	UCB4	8/6	ACR1311	60/-
6BE6	5/-	6J7GT	7/6	7B7	6/6	30F2	14/-	60L6GT	8/-	DP70	9/-	ECC85	5/6	EM80	7/8	PC88	11/6	PY82	5/3	UCB5	7/8	VCB97	45/-
6BH6	9/-	6K6GT	8/-	7R7	13/-	20L1	20/-	75	9/6	DP91	4/-	ECC88	7/8	EM81	10/-	P87	9/9	PY83	7/-	UCB8	8/6	VCB517B	8/6
6BQ6	9/-	6K7	1/9	787	45/-	20P4	20/-	78	5/-	DP92	3/6	ECP56	6/6	EM84	7/8	PCB84	6/6	PY500	18/6	UCH42	10/6		46/-
6Q7A	7/-	6K7M	6/6	7Y4	8/8	20F5	20/-	80	7/6	DP96	7/6	ECP82	6/6	ESU150	20/-	PCB89	10/6	PY500	18/6	UCH81	7/-	VCB517C	46/-
6BR7	17/-	6K7G	2/-	8BW6	7/-	25AG	5/9	85A2	7/3	DR77	4/9	ECH21	12/6	EY51	7/8	PCB189	10/6	PY800	8/6	UCL82	7/6		46/-

Manufacturers and Export Inquiries Welcome

OBsolete TYPES A SPECIALTY

QUOTATIONS FOR ANY VALVE NOT LISTED

Express postage 9d. per valve.

Ordinary postage 6d. per valve. C.W.O. No C.O.D.


Tube postage 7/6 each

Special Express Mail Order Service

## VALVES & TRANSISTORS

2G414	6/0	AC12R	4/6	AF118	12/-	OA10	3/-	OC36	8/6	OC77	8/-	OC122	12/6
2N1305	5/0	AC178	6/2	BC108	3/6	OA79	1/9	OC44	4/-	OC78	3/-	OC123	4/6
2N1417	16/6	ACY18	4/-	BC109	3/6	OA81	1/6	OC45	3/3	OC78D	3/3	OC139	7/6
2N2369A	4/-	ACY27	5/-	BFY51	6/-	OA91	1/6	OC46	3/-	OC79	3/-	OC140	6/6
2N2696	6/3	ACY28	4/-	BFY96	12/6	OA202	2/-	OC58	12/6	OC81	4/-	OC141	12/3
2N2926	3/-	ACY39	12/6	BY100	4/6	OA242	4/6	OC70	3/6	OC81DM	3/-	OC169	6/7
2N3765	4/-	AD149	12/-	GETP14	4/-	OA2246	4/6	OC71	3/6	OC81M	3/-	OC171	6/7
2N3819	8/-	AD161	7/6	G3TM	6/6	OC16	15/0	OC72	4/-	OC82	3/-	OC172	7/6
AC127	3/6	AD162	7/6	G3TM	6/6	OC19	8/6	OC73	7/3	OC82D	3/6	OC200	5/6
		AK127	4/6	NK724	4/9	OC28	12/6	OC75	4/6	OC83	4/6	OC201	8/6
		AF117	4/6	NK713	7/6	OC85	6/3	OC76	3/6	OC84	4/9	OC202	8/6
						OC86	8/6	OC78	3/6	OC114	7/6	OC203	6/-

SEND S.A.E. FOR LIST OF 3,000 TYPES

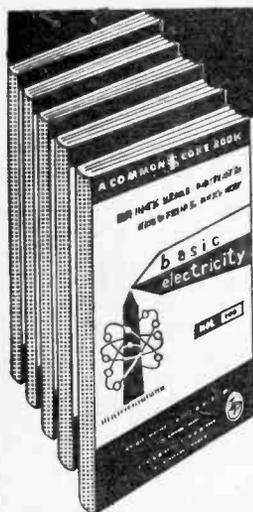

# YOURS FREE FOR 7 DAYS

## The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-style drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

### WHAT READERS SAY

'Everything is clearly set out ...'

... I am well pleased with this pictorial system. Everything is clearly set out in diagrams, ... L.P., Co. Armagh.

'... very pleased with the set ...'

... I was very pleased with the set of Basic Electronics. Please send Basic Electricity ... D.W., Margate.

'... how understandable your books are ...'

... Pleased to say how understandable your books are, I now have a sound knowledge of the subject ... A.A., Hull.

A TECH-PRESS PUBLICATION

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY 75/- Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. BASIC ELECTRONICS 90/- Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY  BASIC ELECTRONICS

Prices include Postage and Packing.

Signature \_\_\_\_\_  
(If under 21 signature required of parent or guardian)

NAME \_\_\_\_\_  
BLOCK LETTERS  
FULL POSTAL ADDRESS \_\_\_\_\_

POST NOW FOR THIS OFFER!!

# P.W. GUIDE TO COMPONENTS

PART 18

M.K.TITMAN, B.Sc. (Eng)

## INTEGRATED CIRCUITS

(continued)

### Linear I.C.'s

THE term linear integrated circuit is applied to all non-digital devices. Originally they were d.c. amplifier circuits used in analogue computers for differentiation, integration etc., and were consequently required to have precise and linear characteristics. Now the term is used loosely and includes many specialist devices.

The d.c. amplifiers produced utilise fully the advantages of matched pair operation in long tail pair circuits. Again in order to minimise resistive elements active constant current generators are used. Consequently the amplifiers—such as the operational amplifier shown in Fig. 18—are extremely stable in terms of temperature and drift. This basic configuration is used for many applications such as a.f., i.f., r.f. and wideband amplifiers.

### Special Circuits

Many specialist circuits are now available such as audio amplifiers, power control circuits, motor control circuits, i.f. strips and complete receiver circuits which only require the addition of tuned circuits and controls. Most of these circuits are the control devices for power stages and are rarely designed as complete devices. The power limitations restrict the output stages, although 5W audio amplifiers are available in integrated circuit form. Table 2 gives a list of some of the devices available together with costs, parameters and applications.

### Summary and Future Trends

We have seen how integrated circuits are fabricated and investigated some of their advantages and disadvantages. Perhaps the greatest advantage is reliability and simplicity of design. When using circuit blocks, design time is reduced and all the layout

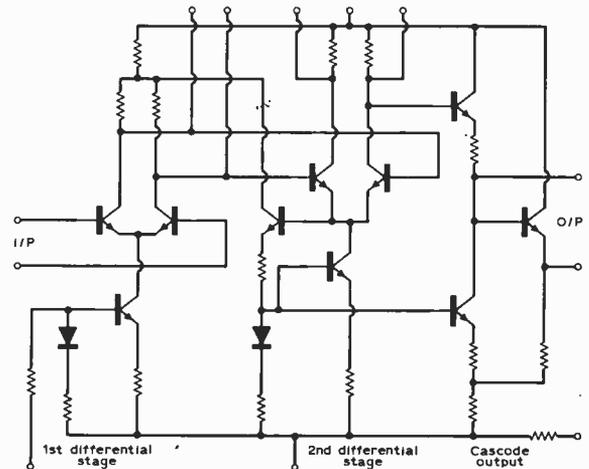


Fig. 18: Typical linear integrated circuit.

and interaction difficulties solved. They are still new and consequently the full potential has yet to be realised. Undoubtedly the very basis of electronics will change through the widespread use of integrated circuits since multi-element, complex devices will become feasible and perhaps commonplace. Undoubtedly as the range widens designers will increasingly operate simply as systems engineers, building circuits with integrated circuit "bricks". It is because they are the devices of the future that it is important they are understood, just as it is important to be aware of the many devices which are available.

With this final article the series "PW Guide to Components" comes to an end. The series which began in December 1968 has covered the whole range of components used in the field of electronics from simple resistors to the latest in integrated circuits. It is hoped that the series has proved of some worth to our readers. ■

**Table 2: Parameter and Cost of Some Linear Integrated Circuits**

Device, designation and circuit function	Parameters	Cost	Supplier
Operational amplifier: High gain, linear d.c. amplifier for critical applications	Open loop V gain 3,000 to 75,000 Zin 15 k $\Omega$ to 2M $\Omega$ Common mode rejection 75-100dB	50/- to £5 upwards to £25	Most
Wideband Amplifier: Wideband d.c. and video amplifiers	Frequency d.c. to 2 or 5MHz Power gain about 50dB Signal to noise about 70dB Power output about $\frac{1}{2}$ W	20/- to 50/- upwards to £10	Most
R.F. amplifiers: R.F. and I.F. amplification	Voltage gain about 25dB Frequency d.c. to 40MHz	30/- to 50/- upwards to £17	Most
I.F. Amplifiers: A.M. and F.M. I.F. amplifiers and discriminators	Voltage gain 60-70dB at 4.5 MHz Noise figure about 8.5dB A.F. output level about 200mV	12/6 to 30/-	Most
Audio amplifiers: Direct low output to speakers or to drive p.a. stage	Voltage gain about 20-50 Power output about 0.5-5W Bandwidth about 500 KHz	£2 to £6	Most
Pre-amplifiers: Low level audio stages, f.e.t. input	Bandwidth from 20Hz—10kHz to d.c.—500kHz	12/6 to 30/- upwards to £15	Most
Differential amplifiers: General purpose with Darlington input stages and cascode output	Differential voltage gain 60-150 Bandwidth d.c. to 0.2 up to 2MHz	30/- to 50/- upwards to £10	Most
Diode and transistor Arrays: General purpose circuits with matched diodes or transistors	Signal diodes 1-8pF, 0.73V Transistors V <sub>CE</sub> about 15V I <sub>cm</sub> about 50mA h <sub>FE</sub> about 60	Approx. 20/-	Most
Receiver semiconductors: All semiconductors in receiver or transmitter; a.m. or f.m., and i.f. and 10MHz amplifier	R.F. range 10-30MHz I.F. 100-500kHz Amp. gain 50dB	Approx. 50/-	Mullard
Optoelectronic amplifier: Gallium arsenide diode and photodiode interface	Computer and communications	—	T.I.
Phase control: Module for controlling phase switching of triacs and thyristors	Gate current 2A peak Supply 8.5V Input—feedback or manual	Approx. £4	G.E.
Voltage regulator: Error amplifiers for controlling d.c. power supplies	D.C. voltages to 15V direct	20/- to £5	Most
Zero switch module: Thyristor and triac controller switching at zero volts only	Zero line voltage sensing, output to 15A, 240V triac	Approx. £5	G.E.
Complementary unijunction: Monolithic complement of p-emitter unijunction	Frequency 100kHz Stability + 0.6% Voltage (V <sub>bb</sub> ) 30V max.	Approx. 30/-	G.E.

### BLUEPRINT SERVICE

We would like to draw readers' attention to the fact that the BLUEPRINT SERVICE has been discontinued and therefore no further BLUEPRINTS are available.


### QUERY COUPON

This coupon is available until 5th June 1970 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, JUNE 1970

# New for Project 60


## Active Filter Unit

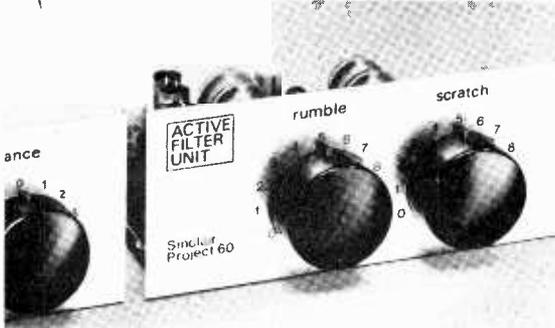

The Sinclair Active Filter Unit is a new addition to our Project 60 range of high fidelity modules and is designed to complement the other modules in the range. Its performance is such, however, that users of other amplifier systems might well consider adding it to their assemblies.


The purpose of a filter unit is to reject frequencies above (scratch) or below (rumble) a specific cut off frequency when these frequencies contain unwanted interference. The Sinclair A.F.U. is unique in that the cut off frequency is continuously variable for both the scratch and rumble units and, as the attenuation in the rejection band is rapid (12dB per octave), the removal of interference can be achieved with less loss of the wanted signal than has previously been possible.

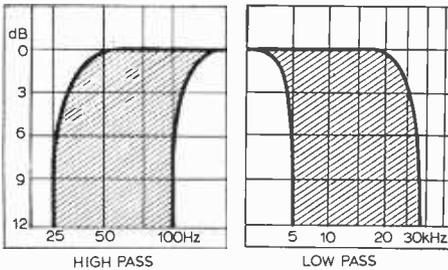Each channel of the A.F.U. has an overall gain of unity and, as the input impedance is high and the output impedance is low, it may be connected between the pre-amplifier and power amplifier sections of any amplifier. Both amplitude and phase distortion have been made quite negligible by the careful design and the large amount of negative feedback employed.



HIGH PASS

LOW PASS

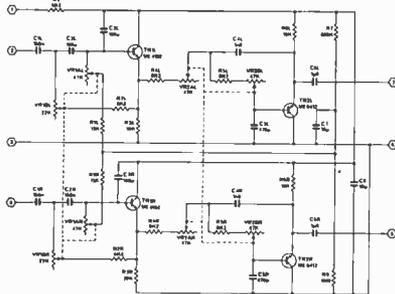

## Specifications

Designed for connection between the Stereo 60 pre-amplifier and two Z-30 or Z-50 power amplifiers.

Employs two Sallen & Key type active filter stages, the first being a rumble (high pass) filter and the second a scratch (low pass) filter. The two stages use complementary transistors to minimise distortion.

Supply voltage 15 to 35V Current 3mA max.

Gain at 1kHz, filters flat 0.98 (—0.2dB)

H.F. cut off (—3dB) variable from 28kHz to 5kHz

H.F. filter slope 12dB/octave

L.F. cut off (—3dB) variable from 25Hz to 100Hz

L.F. filter slope 12dB/octave

Distortion at 1kHz (35v supply) 0.02% at rated output (250mV R.M.S.)

Frequency response, flat position, 35Hz to 20kHz—1dB  
25Hz to 28kHz—3dB

Built, tested and guaranteed **£5.19.6**

## Z-50 FORTY WATT R.M.S. (80 WATT PEAK) HIGH FIDELITY POWER AMPLIFIER

The Z-50 has been designed for applications requiring higher output power than the Z-30. The maximum supply voltage is raised to 50 Volts and the output power is **40 watts continuous R.M.S. in to 3 or 4 ohms and 30 watts continuous into 8 ohms.** The Z-50 is otherwise identical to the Z-30 in design and specification, the increased power being obtained by using much higher current power transistors used well within their rated limits.

The Z-50 is, of course, compatible with the other Project 60 modules, such as the Stereo 60, and since the price is only 20/- higher than that of the Z-30, customers may like to consider the advantages of buying two Z-50's for their systems now in case higher power is required later.

Where the full output power is not required the Z-50 may be used with the PZ-5 or PZ-6 but for the full output power the PZ-8 should be used. This unit is a stabilised power supply providing 45 volts at up to 3 amps. It is supplied without mains transformer as it is designed for use with a readily available "Radiospares" unit.

Z-50 built, tested and guaranteed **£5.9.6**


PZ-8 **£5.19.6**



SINCLAIR  
Z-50

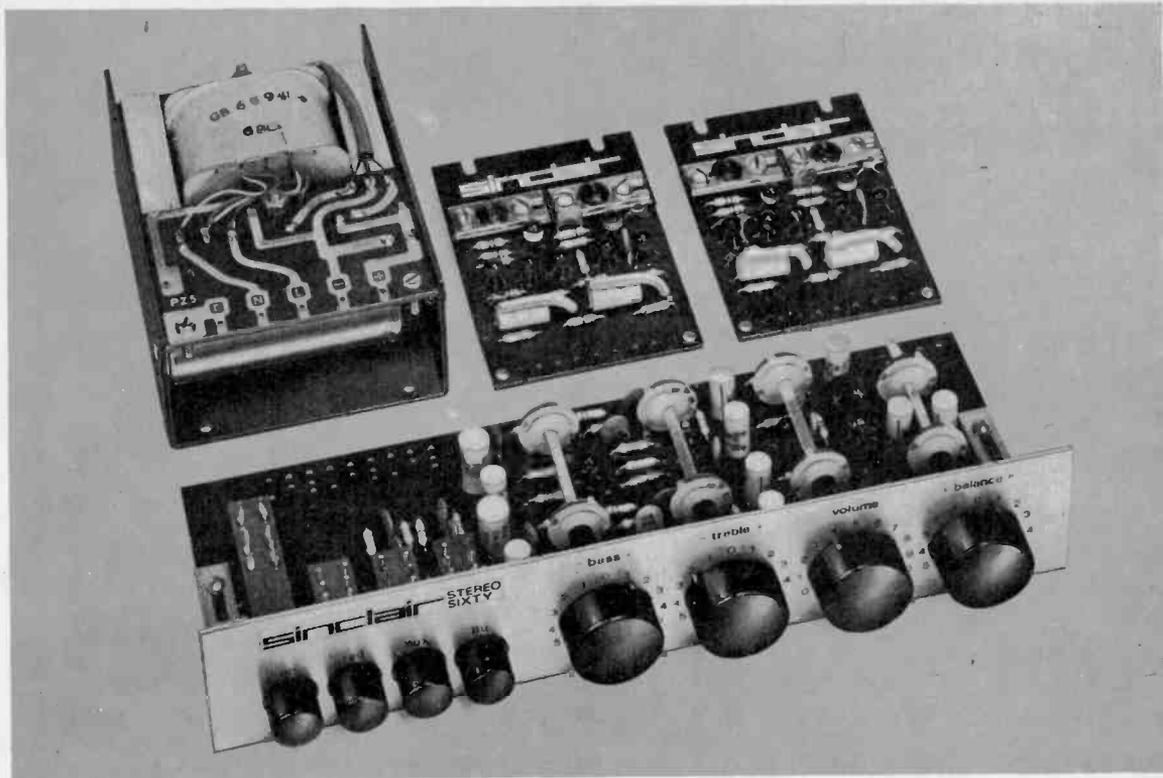**sinclair**

**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD, CAMBRIDGE  
Tel: 0223 52731



## Project 60 an exciting alternative

It is not likely that anyone purchasing an amplifier today would have difficulty in finding one that met all his requirements, although the price might not be as low as could be wished. But one's needs can change, also the technically correct amplifier may be physically inconvenient. If there is an amplifier available, of the right size and price, to meet all your needs for the foreseeable future, then that is your best buy. If not, we offer a possibility which we believe to be an exciting alternative approach. That alternative is Project 60.

Project 60 now comprises a range of modules which connect together simply to form a complete stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare in overall performance. Now with the addition of three new modules to the range, the constructor has choice of assemblies with either 20 or 40 watts output per channel, with or without filter facilities.

The modules now are: 1. The Z-30 and Z-50 high gain power amplifiers, each of which is an immensely flexible unit in its own right. 2. The Stereo 60 pre-amplifier and control unit. 3. The Active Filter unit with both high and low audio frequency cut-offs. 4. The PZ-5 and PZ-6 power supplies. A complete system could comprise, for example, two Z-30's, one Stereo-60, and a PZ-5. The P-Z6 is stabilised and should be used where the highest possible continuous sine wave rating is required. An A.F.U. may

be added later. In a normal domestic application, there will be no significant difference between using PZ-5 or PZ-6 unless loudspeakers of very low efficiency are being used, in which case the PZ-6 will be required. For assemblies using two Z-50's there is the new PZ-8 stabilised supply unit to ensure maximum performance from these amplifiers.

All you need to assemble your Project 60 system is a screwdriver and soldering iron. No technical skill or knowledge whatsoever is required and, in the unlikely event of you hitting a problem, our customer service and advice department will put the matter right promptly and willingly. Project 60 modules have been carefully designed to fit into virtually all modern plinth or cabinets and only holes need be drilled into the wood of the plinth to mount the control unit. Any slight slip here will be covered by the aluminium front panel of the Stereo 60. The Project 60 manual gives all the buildings and operating instructions you can possibly want, clearly and concisely. Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future as the latest additions to the range show. A stereo F.M. tuner is next to come. These and all other modules we introduce will be compatible with those already available and may be added to your system at any time. And because Sinclair are the largest producers of constructor modules in Europe, Project 60 prices are remarkably low.

# sinclair

**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD, CAMBRIDGE

Tel: 0223 52731

# Z.30 TWENTY WATT R.M.S. (40 WATT PEAK) HIGH FIDELITY POWER AMPLIFIER

The Z.30 is a complete power amplifier of very advanced design employing 9 silicon epitaxial planar transistors. Total harmonic distortion is incredibly low being only 0.02% at full output and all lower outputs. As far as we know, no other high fidelity amplifier made can match this specification, no matter what the price. Thus you can be utterly certain that your Project 60 system will do full justice to your other equipment however good it may be. The Z.30 is unique in that it will operate perfectly, without adjustment, from any power supply from 8 to 35 volts. It also has sufficient gain to operate directly from a crystal pickup. So in addition to its use in a high fidelity system you can use a Z.30 to advantage in your car or a battery operated gramophone for your children, for example. These, and many other applications of the Z.30 are covered in the manual of circuits and instructions supplied with every Z.30 high fidelity power amplifier.

## SPECIFICATIONS

**Power output**—15 watts R.M.S. into 8 ohms using a 35 volt supply; 20 watts R.M.S. into 3 ohms using a 30 volt supply.

**Output**—Class AB.

**Frequency response:** 30 to 300,000 Hz  $\pm$  1dB.

**Distortion:** 0.02% total harmonic distortion at full output into 8 ohms and at all lower output levels.

**Signal-to-noise ratio:** better than 70dB unweighted.

**Input sensitivity:** 250mV into 100Kohms.

**Damping factor:** > 500.


**Loudspeaker Impedances:** 3 to 15 ohms.

**Power requirements:** From 8 to 35 V.d.c. (The Z.30 will operate ideally from batteries if required.)

**Size:** 3½ x 2¼ x ½ inches.
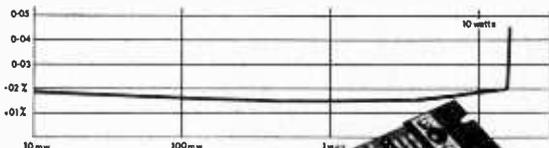
## APPLICATIONS

Hi-fi amplifier; car radio amplifier; record player amplifier fed directly from pick-up; intercom; electronic music and instruments; P.A.; laboratory work etc. Full details for these and many other applications are given in the manual supplied with the Z.30.



Power versus distortion curve of Sinclair Z.30 amplifier

**Z.30**  
Built, tested and guaranteed, with circuits and instructions manual

# 89/6

# STEREO 60 PRE-AMPLIFIER AND CONTROL UNIT

The Stereo 60 is a stereo preamplifier and control unit designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout and great attention has been paid to achieving a really high signal-to-noise ratio and excellent tracking between the two channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs. The tone controls are also very carefully designed and tested.

## SPECIFICATIONS

• Input sensitivities—Radio—up to 3mV  
Magnetic Pickup—3mV; correct to R.I.A.A. curve  $\pm$  1dB; 20 to 25,000 Hz. Ceramic Pickup—up to 3mV;  
Auxiliary—up to 3mV.

• Output—250mV

• Signal-to-noise ratio—better than 00dB.


• Channel matching—within 1dB.

• Tone controls—TREBLE + 15 to -15dB. at 10 KHz; BASS + 15 to -15dB at 100Hz.

• Power consumption 5mA.

• Front panel—brushed aluminium with black knobs and controls.


• Size 8¼ x 4 ins.

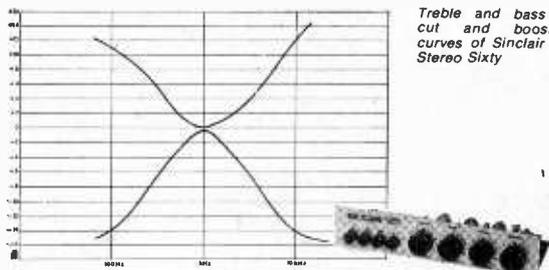

Treble and bass boost curves of Sinclair Stereo Sixty

Ready for immediate installation **£9. 19s. 6d.**

# SINCLAIR MAINS POWER SUPPLY UNITS

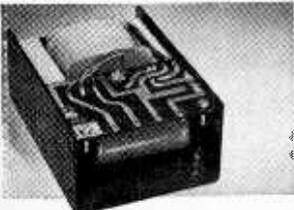

**PZ-5** 30 volts unstabilised—sufficient to drive two Z.30's and a Stereo 60 for the majority of domestic applications. **£4.19.6**

**PZ-6** 35 volts stabilised—ideal for driving two Z.30's and a Stereo 60 when very low efficiency speakers are employed. **£7.19.6**

**PZ-8** 45 volts power supply unit for use with Z.50 amplifiers (less mains transformer) **£5.19.6**

## GUARANTEE

If at any time within 3 months of purchasing Project 60 modules from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for services thereafter. No charge for postage by surface mail. Air-mail charged at cost.

### BUILDING A PROJECT 60 ASSEMBLY



The illustration here shows quite clearly how easily Project 60 can be contained in one of today's slim, modern plinths. Very little space is required to house these Sinclair units, and within the space of the motor plinth, you can install a stereo amplifier of the very highest quality. If, for example you have already put together an assembly as illustrated here, adding the Active Filter Unit would be very easy.

IC.10 MICROMATIC AND Q.16. Please see next page

**TO: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE**

Please send

NAME .....

ADDRESS .....

.....

.....

For which I enclose cash/cheque/ money order

PW 670





### FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	3/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF114	4/-	2N1302-3	4/-
AF115	3/6	2N1302-5	5/-
AF116	3/6	2N1306-7	9/-
AF117	3/6	2N1308-9	9/-
AF239	12/6	2N3819 FET.	9/-
AF186	10/-	2N3844A	5/-
BF139	10/-	Power	
BFY50	4/-	Transistors	
BSY25	7/6	OC20	10/-
BSY26	3/-	OC23	10/-
BSY27	3/-	OC25	8/-
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	7/6
BSY95A	3/-	OC35	5/-
OC41	2/6	OC36	7/6
OC44	2/6	AD149	10/-
OC45	2/6	AU710	30/-
OC71	2/6	2N3055	15/-
OC72	2/6	2S034	10/-
OC73	3/6	Diodes	
OC81	2/6	AAV42	2/-
OC81D	2/6	OA91	2/-
OC81	4/6	OA79	1/9
OC139	2/6	OC81	1/9
OC140	3/6	IN914	1/6

**FREE!** Packs of your own choice up to the value of 10/- with orders over £4.

### RETURN OF THE UNBEATABLE P.1. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

**P1 PLEASE ASK FOR PAK P.1.**  
2/- P. & P. on this Pak **ONLY 10/-**

### NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits. Data and Circuits of types, supplied with orders.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
B82	10	OC45, OC81D and OC81 Trans. Mullard glass type.	10/-
B83	200	Trans. Makers rejects. NPN/ PNP, Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
B66	150	High quality Germ. Diodes. Min. glass type.	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types.	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN, PNP, equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes. Mixed voltages.	10/-
H5	16	1 Amp. Plastic Diodes, 50-1,000 Volts. 6 large, 10 small	10/-
H6	40	250mW. Zener Diodes DO-7 min. Glass Type. AV. 40% Good.	10/-

### NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries .3 to .5 volt, .5 to 2 ma.	10/-
B77	2	AD161-AD162 NPN/PNP Trans Comp. Output, Pair.	10/-
B79	4	IN4007 Sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Plastic.	10/-
B81	10	Reed Switches, mixed types, large and small.	10/-
B89	2	5SP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45.	10/-
B92	4	NPN. Sil. Trans. AO6 BSX20 2N2369 500 MHz. 360mW.	10/-
B93	5	GET113 Trans. equiv. to ACY17 to ACY21 PNP Germ.	10/-
B96	5	2N3136 PNP Sil. Trans. TO-18, HFE 100-300 I.C. 600mA. 200MHz.	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NK271, etc.	10/-
B99	200	Capacitors, Electrolytics, paper silver mica, etc. Post and packing, this Pak 2/6.	10/-
H4	250	Mixed Resistors, Post and packing 2/-.	10/-
H7	40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-

Complementary Set. NPN/PNP Germ. trans., Pak F.3. **2/6 PAIR**

**P.O. RELAYS** 8 FOR Various Contacts and Coil Resistances. Post & Packaging 5/- **20/-**


### ★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order OVERSEAS AND EXTRA FOR AIRMAIL.

## H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

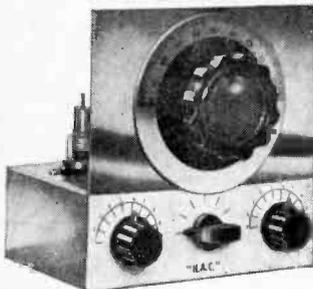

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hms, etc.

#### IMPROVED 1970 RANGE

One-valve model "DX", complete kit—price 56/6 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits including the famous model "K" and "K plus" (illustrated above.) All orders despatched by return. (Mail order only.) Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1

## 4-STATION INTERCOM



£7/15/0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft. and other accessories. P. & P. 7/6.

#### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way loud and clear communication. On/off switch and volume control. Price £11.19.6. P. & P. 8/6 extra.

## INTERCOM/BABY ALARM



OUR PRICE ONLY 3 gns.

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 60ft. connecting wire. Battery 2/6. P. & P. 4/6.



59/6

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days. WEST LONDON DIRECT SUPPLIES (P/W4) 169 KENSINGTON HIGH STREET, LONDON, W.8.

## MAINS UNITS for all types of TRANSISTOR EQUIPMENT

The ideal, economical and safe way of running Transistor Radios, Record Players, Tape Recorders, Amplifiers etc. from A.C. Mains. All units are completely isolated from mains by double wound transformer ensuring 100% safety.

### PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v, 7½v, and 9v, DC, attractive case with indicator light, mains lead output socket, plug and lead.

Size 4½ x 3½ x 2½ in. (Extra lead with DIN plug for Cassette Recorders 7/6)



57/6 P. & P. 2/6



### POWER PLUS MAINS UNIT

for transistor equipment using 7½v. Complete with DIN plug for power socket. Can also be supplied for a 6-volt output complete with suitable plug. (State make, model and voltage required.)

45 - P. & P. 2/6

NOW AVAILABLE—UNIT FOR USE WITH 12v CAR BATTERY as featured this issue. Suitable for running transistor radios etc. (State output reqd. - 6v, 7½v or 9v) Price 35/- including fused lead P. & P. 2/6

### MAJOR POWER PLUS MAINS UNITS

For single outputs, 6v, 9v, 12v, 18v, 39/6. For two separate outputs, 4½v + 4½v, 6v + 6v, 9v + 9v. 42/6. P. & P. 2/6 per unit. (Please state outputs reqd.)



**R.G.S. PRODUCTS (RADIO) LTD.**  
(Dept. P.W.), 31 Oliver Road, London, E.17

# ELECTROVALUE

## RESISTORS:

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	18	16	15
C	1/8W	5%	4.7 Ω-330K Ω	E24	2-5	2	1.75
C	1/4W	10%	4.7 Ω-10M Ω	E12	2-5	2	1.75
C	1/2W	5%	4.7 Ω-10M Ω	E24	3	2-5	2-25
MO	1/2W	2%	1.0 Ω-1M Ω	E24	9	8	7
C	1W	10%	4.2 Ω-10M Ω	E12	6	5	4-5
WW	1W	10% +1/20 Ω	0.22 Ω-3.3 Ω	E12	15d all quantities		
WW	3W	5%	12 Ω-10K Ω	E12	15d all quantities		
WW	7W	5%	12 Ω-10K Ω	E12	15d all quantities		

## Codes:

C = carbon film, high stability, low noise.  
MO = metal oxide, Electroal TR5, ultra low noise.  
WW = wire wound, Plessey.

Values: E12 denotes series: 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2 and their decades.  
E24 denotes series: as E12 plus 1.1, 1.3, 1.6, 2.2, 2.4, 3.3, 3.6, 4.3, 5.1, 6.2, 7.5, 9.1 and their decades.

Prices are in pence each for quantities of resistors of same ohmic value and power rating NOT mixed values. (Ignore fractions of one penny on total resistor order.)

## COLVERN 3 WATT WIRE-WOUND POTENTIOMETERS:

10 Ω, 15 Ω, 25 Ω, 50 Ω, 100 Ω, 150 Ω, 250 Ω, 500 Ω, 1K Ω, 1.5K Ω, 2.5K Ω, 5K Ω, 10K Ω, 15K Ω, 25K Ω, 50K Ω. Price only 5/6 each.

## CARBON TRACK POTENTIOMETERS: Double wiper ensures minimum noise level. Long plastic spindles.

Single gang linear: 220 Ω, 470 Ω, 1K etc. to 2-2M Ω	each	2/8
Single gang log: 4K7, 10K, 22K, etc. to 2-2M Ω	"	2/8
Dual gang linear: 4K7, 10K, 22K etc. to 1M Ω	"	8/6
Dual gang log: 4K7, 10K, 22K etc. to 2M2 Ω	"	8/6
Log/Anti-log: 10K, 47K, 1M only	"	8/6
Dual anti-log: 10K only	"	8/6
Any type with 1 amp. double pole mains switch	extra	2/8

FETS n-channel low cost general purpose 2N5163, 25 volt, only 5/- each. Audio/ r.f. Texas 2N3819 8/6. Motorola 2N5459 (MPF105) 9/9 each.

NEW PLESSEY INTEGRATED CIRCUIT POWER AMPLIFIER TYPE SL403A. Only 48/8 nett. Operates with 18V power supply. Sensitivity 20mV into 20M Ω, 3 watts into 7-5 Ω. Applications data with two or more. PE Nov. 69 Stereo Amplifier kit less metal work £11/18/- NET complete.

## 30 WATT BAILEY AMPLIFIER COMPONENTS:

Transistors for one channel £7/5/6 list, with 10% discount only £6/11/0.  
Transistors for two channels £14/1/0 list, with 15% discount only £12/7/5.  
Capacitors and resistors for one channel list £2.  
Printed circuit board free with each transistor set.  
Complete unregulated power supply kit £4/17/6 mono or stereo, subject to discount.  
Complete regulated power supply kit £9/5/- subject to discount. Further details on application.

**CAPACITORS: All new stock**  
High ripple current types:  
2000µF 25V 7/4; 2000µF 50V 11/4;  
5000µF 25V 12/8; 5000µF 50V;  
2111; 1000µF 100V 16/3; 2000µF 100V 28/9; 5000µF 70V 36/-;  
5000µF 100V 58/3; 1000µF 50V 8/2; 2500µF 64V 15/5; 2500µF 70V 19/6.

**Medium electrolytics**  
Axial leads: Values (µF/V): 50/50 2/-; 100/25 10/10, 25/10, 50/10  
2/-; 100/50 2/6; 250/25 1/- each, 25/25, 47/25, 100/10, 220/10 1/8 each.

**Small electrolytics**  
Axial leads: 5/10, 10/10, 25/10, 50/10  
1/- each, 25/25, 47/25, 100/10, 220/10 1/8 each.

**MULLARD Sub-min electrolytic C426 range:** Price 1/3 each. Axial leads. Value<sup>8</sup> (µF/V): 0.6/4/4; 1/40; 1.6/25; 2.5/16; 2.5/6/4; 4/10; 4/40; 5/6/4; 6.4/6.4; 6.4/2/5 8/4; 8/40; 10/2.5; 10/16; 10/6/4; 12.5/25; 16/40; 20/16; 20/6/4; 25/6.4; 25/2/5; 32/10; 32/40; 32/6/4; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6/4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5µF/V.

Wavechange switches: 1P 12W; 2P 6W; 3P 4W; 4P 3W long spindles, 4/9 each.  
Slider switches, double pole double throw, 3/- each.

Suppliers of PEAK SOUND, SINCLAIR MAIN LINE PRODUCTS, etc., as advertised. Also large stocks of all types of transistors, etc.

## COMPONENT DISCOUNTS:

10% on orders for components for £5 or more.  
15% on orders for components for £15 or more.  
(No discount on net items.)

## POSTAGE AND PACKING:

Free on orders over £2.  
Please add 1/6 if order is under £2.  
Overseas orders welcome; carriage charged at cost.

# ELECTROVALUE

DEPT. PW. 6

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY, Hours 9-5.30. Sat. 10 p.m. Telephone Egham 5533 (STD 0784-3) Telex: 264475

## EX-RENTAL TELEVISIONS

### TWO-YEAR GUARANTEE


17" SLIMLINE 405 only £11 10 0

19" SLIMLINE 405/625 39 Gns.

Carriage and Insurance 30/-

FREE ILLUSTRATED LIST OF TELEVISIONS

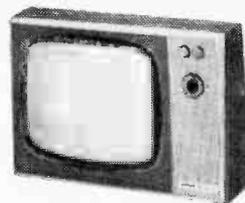17"-19"-21"-23"  
WIDE RANGE OF MODELS, SIZES AND PRICES  
DEMONSTRATIONS DAILY



### TWO-YEAR GUARANTEED TUBES 100% REGUNNED

Slim Line Tubes 110" 17" and 19" 109/6, 21" and 23" 129/6.  
Normal Tubes 70" and 90" 17" 99/6, 21" 119/6, 14" and other sizes 79/6.

**SPEAKERS 10", 21" 8Ω, 31" 25Ω, 4" 10Ω, 3" x 5" 8Ω, 7" x 4" 3Ω, 8" x 3" 3Ω. BRAND NEW. P. & P. 2/-.**

### RECORD PLAYER CABINET 49/6

Transistors: Mullard matched output kit 7/6, OCB1D-2 OCB1S. P. & P. FREE.

Transistor Radio Cases: 4 for £1. Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 9/6.

Ferrite Rods 3/6: 6" and 8" complete with LWMW Coils. P. & P. FREE.

STRIP LIGHT TUBES 3/9 each. 11" (284mm). 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffuse lighting, etc. 6 for £1. P. & P. free.



Cloth covered. Size 16 1/2" x 14 1/2" x 7 1/2". Takes any modern auto-changer. P. & P. 7/6.

(DUKE & CO. LONDON) LTD.

621/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

## VALVES

SAME DAY SERVICE  
NEW! TESTED! GUARANTEED

SETS 1R5, 1R5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL84. Set of 4 for 18/6, DAF96, DF 96, DK96, DL96, 4 FOR 27/-.

OZ4	4/8	12K8GT	7/3	DK91	5/9	EF184	5/6	PCL82	7/3	UBF90	5/9
1A7GT	7/8	19BGG17/8	DK92	8/6	EH90	6/3	PCL83	12/-	UBF89	6/9	
1HG7T	7/3	20P2	13/6	DK96	7/3	EL33	9/6	PCL84	7/6	UCB84	7/-
1NSGT	7/9	20P3	11/9	DL55	5/-	EL34	9/6	PCL85	9/-	UCB85	7/8
1R5	5/9	20P4	18/6	DL92	5/9	EL41	11/-	PCL86	8/3	UCF80	7/3
1R5	4/3	25L6GT	5/-	DL94	6/3	EL84	4/9	PENA	12/6	UCH42	12/6
1T4	2/9	26U4GT11/8	DL96	7/3	EL90	4/6	FEL200	11/9	UCH81	6/8	
3V4	5/9	30C1	8/6	DY86	5/9	EL500	12/6	FL36	9/9	UCL82	7/-
384	6/3	30C15	13/-	DY87	5/9	EM80	7/6	PL81	8/9	UCL83	11/9
6Y3GT	5/9	30C17	18/-	EAB80	6/6	EM81	7/6	PL81A	10/6	UF41	10/6
5Z4G	7/6	30C18	14/-	EAF42	10/-	EM84	6/9	PL82	6/6	UF80	7/-
6Y30L2	12/-	30F5	16/-	EB91	2/3	EM87	7/6	PL83	6/6	UF85	6/9
6AL5	2/3	30FL1	14/-	EB92	8/6	EY61	7/3	PL84	6/6	UF89	6/9
6AM6	2/9	30FL12	14/6	EB94	8/6	EY86	6/6	PL500	13/-	UL41	11/9
6AQ5	4/6	30FL14	14/6	EB90	6/9	EZ40	8/-	PL504	13/6	UL44	20/-
6AT6	4/-	30L1	6/6	EBF89	6/3	EZ41	8/-	PL508	23/6	UL84	7/-
6AU6	4/6	30L15	14/-	ECC81	3/9	EZ80	4/6	PM84	7/6	UM84	6/6
6BA5	4/6	30L17	15/6	ECC82	4/9	EZ81	4/9	PX25	12/-	UY41	7/6
6BE6	4/9	30P4	12/-	ECC83	7/-	GZ32	8/9	PY32	10/-	UY85	6/9
6B6	8/8	30P12	13/6	ECC85	5/-	GZ34	9/9	PY33	10/-	V4B	10/-
6BW6	4/9	30P19	12/-	ECC91	3/-	KT61	9/9	PY81	5/3	W77	3/6
6CG6	4/9	30PL1	14/9	ECC80A	12/-	KT66	16/9	PY82	5/3	W119	7/6
6F13	3/6	30PL13	17/6	ECC80	6/6	N78	17/6	PY83	5/3	Z77	2/9
6F14	9/-	30PL14	16/6	ECC82	6/6	PABC80	7/-	PY88	6/9	Transistors	
6P23	14/3	35L6GT	8/6	ECH35	6/6	PC86	10/3	PY800	7/6	AC107	3/6
6P25	13/3	35W4	4/6	ECH42	13/6	PC88	10/3	PY801	7/6	AC127	2/6
6J5G	4/9	35Z4GT	5/-	ECH81	5/9	PC96	9/6	R19	6/6	AD140	7/6
6J6	4/9	60S3	12/6	ECH83	8/3	PC97	8/6	R20	12/6	AF115	3/-
6K7G	2/8	60T	9/-	ECH84	7/6	PC900	7/6	U25	13/-	AF116	3/6
6K8G	2/8	AC/VP210/-	ECL80	7/-	PCC84	6/6	U26	12/-	AF117	4/6	
6L18	6/-	AZ31	9/6	ECL82	6/9	PCC85	6/6	U47	13/6	AF125	3/6
6SN7GT	4/3	B729	12/6	ECL83	8/6	PCC88	9/-	U49	13/6	AF127	3/6
6V6G	3/3	OCH35	13/6	ECL86	8/6	PCC89	10/6	U78	4/6	OC81	2/6
6V6GT	6/6	CL33	18/6	EF37A	6/6	PCC89	11/6	U91	12/6	OC44	2/6
6X4	4/3	CV31	6/6	EF39	4/9	PCF80	6/6	U93	8/6	OC45	2/3
6X5GT	5/9	DAC32	7/3	EF41	10/9	PCF82	6/6	U251	14/6	OC71	2/6
10F1	14/-	DAF91	4/3	EF80	4/6	PCF86	10/6	U301	10/6	OC72	2/6
10P18	7/-	DAF96	7/3	EF85	6/3	PCF800	13/6	U329	14/6	OC75	2/6
10P13	12/-	DF33	7/9	EF86	6/3	PCF801	6/9	U801	19/6	OC81	2/6
12AT7	3/8	DF91	2/9	EF89	5/3	PCF89	11/6	UAFB80	6/6	OC82	2/6
12AU6	4/8	DF94	7/3	EF91	2/9	PCF805	14/6	UAFC40	10/3	OC8D	2/3
12AU7	4/8	DH77	4/8	EF94	4/6	PCF806	12/9	UB41	6/6	OC82D	2/6
12AX7	4/8	DK32	7/8	EF183	5/9	PCF808	14/9	UB41	9/6	OC170	4/6


## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.
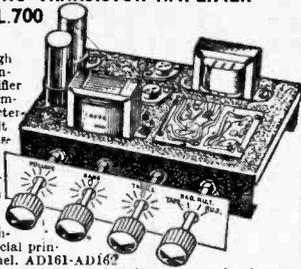
## MONO TRANSISTOR AMPLIFIER HSL 700

A really high fidelity mono-aural amplifier with performance characteristics to suit the most discriminating listener.



6 transistor circuit with integrated pre-amplifier assembled on special printed sub-panel. AD181-AD182 operating in asymmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phono input sockets. Full wave bridge rectifier power supply for AC mains 200-240v. Controls: Bass, Treble, Volume/on/off. Function selector for P.U.I., P.U.Z., Tape, Radio. The HSL 700 is strongly constructed on rigid steel chassis bronze hammer enamel finish, size 9 1/2 x 5 x 4 1/2 in. high. Sensitivity: P.U.I.-50mV, 56K input impedance. P.U.Z.-110mV, 1 meg input impedance. Tape.-110mV, 1 meg input impedance. Radio.-110mV, 1 meg input impedance. Output power measured at 1Kc.-8.2 watts RMS into 3 ohms. 5.8 watt RMS into 15 ohm. Overall frequency response 30 c/s-18 Kc/s. Continuously variable tone controls: Bass, +8db to -12db at 100c/s. Treble, +10db to -10db at 10Kc/s. The HSL 700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front enclosure panel, four spindles (can be cut to suit your housing requirements) full circuit diagram and operating instructions.

Our Special **£7.19.6** P & P. 7/6

### LOUDSPEAKER BARGAINS

5in. 3 ohm 15/7 x 5in. 3 ohm 21/-, P. & P. 4/-, 10 x 6in. 3 ohm 27/8, P. & P. 6/-, E.M.I. 8 x 6in. 3 ohm with high flux magnet 26/-, P. & P. 4/-, E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet 42/- (16 ohm 45/-), P. & P. 6/-. E.M.I. 13 x 8in. 3 or 15 ohm with two built tweeters and crossover network 4 gns. P. & P. 6/-.

**BRAND NEW**, 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly £5.10.0. P. & P. 7/6. Guitar models: 25w. £8.0.0, 35w. £8.0.0. E.M.I. 3 1/2in. **HEAVY DUTY TWEETERS**. Powerful ceramic magnet. Available in 3 or 8 ohms 15/- each; 15 ohms 18/6 each. P. & P. 2/6.

12in. **"BA" TWIN CONE LOUDSPEAKER**. 10 watts peak handling, 3 or 15 ohm 37/8, P. & P. 6/-.

### 35 OHM SPEAKERS

3 1/2in. 14/-, P. & P. 2/6; 7 x 4in. 21/-, P. & P. 4/-.

**BALANCED ARMATURE EARPHONE**. Approx 70 ohm impedance. Can be used as ultra sensitive mike or speaker. **ONLY 8/6**. P. & P. 1/6.

**CRYSTAL MIKES**. High imp. for desk or hand use. High sensitivity, 18/6, P. & P. 1/6.

**EIGH IMPEDANCE CRYSTAL STICK MIKES**. OUR PRICE 21/-, P. & P. 1/6.

**HIGH IMPEDANCE DYNAMIC STICK MIKES**. High sensitivity, 39/6, P. & P. 2/6.

**HONEYWELL MICROSWITCHES**. 8/P. C/O. Push button action. Rating 250v. AC at 15 amps. Size approx. 1 1/2 x 1 1/2 x 1/2 in. 5/- each. P. & P. 1/- (6 or more post free).

**SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG**. 400pF + 146pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 k/c/s I.F. Size approx. 2 1/2 x 1 1/2. **Only 8/6**. P. & P. 2/6.

**TELESCOPIC AERIALS WITH SWIVEL JOINT**. Can be angled and rotated in any direction. 12 section Heavy Chrome. Extends from 7in. to approx. 56in. Maximum diameter 1/2in. 10/- each. P. & P. 1/6. 6 section Lacquered Brass. Extends from 6in. to 22 1/2in. approx. Maximum diameter 1/2in. 5/- each. P. & P. 1/-.

### TRANSFORMER BARGAINS!

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS**. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp. or 10-0-10. 20-0-20. 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price 32/6, P. & P. 6/-.

**MAINS TRANSFORMER**. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500mA. 11/-, P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/8, P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6, P. & P. 3/6. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 22/6, P. & P. 2/6.

**BATTERY CHARGER TRANSFORMERS**. 200/240v. input. Non-pull output for 6 or 12v. batteries 3 amps. Size approx. 3 1/2 x 2 1/2. Brand New. Price 21/-, P. & P. 5/-.

**HIGH GRADE COPPER LAMINATE BOARDS**. 8 x 6 x 1/4 in. FIVE for 10/-, P. & P. 2/-.

Open all day Saturday  
Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

## SPECIAL OFFER!!

Your opportunity to acquire a first class HI-FI LOUDSPEAKER SYSTEM at an extremely moderate price!  
Beautifully made teak finish enclosure with most attractive Tyeann front. Size 18 1/2" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 15 ohm impedance.

**OUR PRICE WHILE LIMITED STOCKS LAST 8 Gns.**  
Carriage 10/-

### TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class HI-FI Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work. Circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Freq. response ±3db. 20-20,000 c/s. Bass boost approx. to +12db. Treble cut approx. to -15db. Negative feedback 18dB over main amp. Power requirements 230v at 4 gns. **PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £3.0.0.** All Post Free. Also available STEREO 10 + 10. As above but 10 watts per channel. **PRICES: AMPLIFIER KIT £12; POWER PACK KIT £3.10.0.** Circuit diagram, construction details and parts list (free with kit) 1/8 (S.A.E.).

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER


For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. Can be operated from 9-15v. battery supply or direct from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 17/6. P. & P. 2/6.



**SPECIAL PURCHASE!**  
**E.M.I. 4-SPEED PLAYER** (heavy duty) 9 1/2in. metal turntable. Low flutter performance 200/200v. shaded motor (90v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. **ONLY 63/-**. P. & P. 6/6.

**QUALITY RECORD PLAYER AMPLIFIER MK II**  
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. **PRICE 75/-**. P. & P. 6/-.

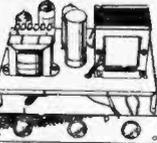**DELUXE QUALITY PORTABLE R/P CABINET MK II**  
Uncut motor board size 14 1/2 x 12in. clearance 2in. below. 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE 79/6**. P. & P. 9/6.



### 3-VALVE AUDIO AMPLIFIER H3A MK II


Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£4.15.0**. P. & P. 6/-.

**HSL "FOUR" AMPLIFIER KIT**. Similar in appearance to H3A above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-.

### HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound mains transformer, EZ80 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. **FEW ONLY**  
**OUR ROCK BOTTOM 55/-** P. & P. BARGAIN PRICE 6/-

## DE LUXE STEREO AMPLIFIER

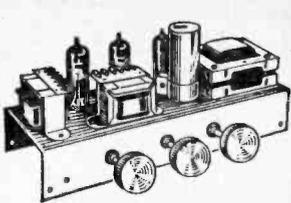

A.C. mains 200-240 v. U a l i n g heating duty fully isolated double mains transformer with full wave rectification giving a q u a l e smoothing with negligible hum.

Valve line up: -2 x ECL86 Triode Pentodes, 1 x EZ80 as full wave rectifier. Two dual potentiometers are provided for base and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for the full output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. **PRICE 8 gns. P. & P. 8/-**.

### 4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. **LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER**. With latest mono compatible cartridge £6.19.6. Carr. 6/6. With stereo cartridge £7.19.6. Carr. 6/6. **LATEST GARRARD MODELS**. All types available 1025, 2025, SP25, SP50. AT60 etc. Send S.A.E. for latest Prices! **PLINTH UNITS** cut out for Garrard Models, 1025, 2025, 2000, 3000, AT60, SP25. With transparent plastic cover. **OUR PRICE 5 gns. complete. P. & P. 8/6**.

**LATEST ACOS GP91/1SC** mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. 30/- P. & P. 1/6.

**SONOTONE 2539** High output Stereo Cartridge. T/O stylus for Stereo/LP/78. Complete with universal mounting bracket. List Price 48/7.

With stereo cartridge £25/-, P. & P. 1/6. **SONOTONE 9TABC** compatible Stereo Cartridge with diamond stylus 50/-, P. & P. 2/-.

**LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. 32/6. P. & P. 2/-.

**LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE** for EP/LP/78 mono or stereo records on mono equipment. **Only 30/-**. P. & P. 2/-.

### HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT

**Tape TA1**  
● Peak output in excess of 1 1/2 watts.  
● All standard British components.  
● Built on printed circuit panel size 6 x 3in.  
● Generous size Driver and Output Transformers.  
● Output transformer tapped for 3 ohm and 15 ohm speakers.  
● Transistors (GET114 or S1 Mullard AC128D and matched pair of AC128 o/p).  
● 9 volt operation.  
● Everything supplied, wire, battery clips, solder, etc.  
● Comprehensive easy to follow instructions and circuit diagram 2/6 (Free with Kit). All parts sold separately.

**SPECIAL PRICE 45/-**. P. & P. 3/-.  
Also ready built and tested, 52/6. P. & P. 3/-.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monoaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 2/6 (Free with parts). All parts sold separately. **ONLY 27.9.6**. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, £9.5.0. P. & P. 8/6.

**BRAND NEW TRANSISTOR BARGAINS**. Get 15 (Matched pair) 15/-; V15/10p 10/-; OC71 5/-; OC76 6/-; AF117 3/6; 2G339 (NPN) 3/-.  
Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 25/-; ORP12 Cadmium Sulphide Cells 10/6. All post free.

**VYNAID AND REXINE SPEAKER AND CABINET FABRICS**. Approx. 54in. wide. Usually 35/- yard. **OUR PRICE 15/-** per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 10s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

## MISCELLANEOUS

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond, Surrey.

**BUILD IT** in a DEWBOX quality cabinet. 2in. x 2 1/2in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

## TOP TRANSISTORS

ACY22 1/9	OC45 1/9	ZTX300 1/9
BC108 1/9	OC71 1/9	2N706 1/9
BFY51 1/9	OC200 1/9	2N2926 1/9
BFY52 1/9	OC201 1/9	2N3708 1/9

All the above types are available at 16 for £1. Brand New. Individually Tested. MONEY BACK GUARANTEE.

P & P 1/-.

J. M. KING (Z),  
17 BUCKRIDGE, PORTPOOL LANE,  
LONDON, E.C.1.

**500 ITA CONVERTER TUNERS** 3/- for sample.—E. Graley, 15 Roskell Road, Liverpool 25 OLN.

**PARAPHYSICAL LABORATORY.** Downton, Wilts. Telekinesis. Magazines. Send S.A.E. for list. Samples 20s.

**SERVICE FOR THE AMATEUR** electronic enthusiast. Are you building equipment requiring a transformer? If so, send for an immediate quotation, or s.a.e. for our comprehensive price list. Also available on request, enamelled copper wire price list.—Banner Transformers, 84 Old Lansdowne Rd, West Didsbury, Manchester, 20.

## PHOTO ELECTRIC SWITCH KIT

Light cell, transistor, relay etc. Elegant case in hammer finish 5 1/2" x 2 1/2" x 4 1/2" fitted with light hood. Ideal counter alarm, Dawn/Dusk switch, etc. **35/-** Post Paid.

## 6 OR 12 VOLT FLUORESCENT LIGHTS

12 ins. 8 Watt tube ample light for caravan, tent etc. Fully transistorised, low battery drain. Unbeatable at **65/6** post paid.

Or in kit form **57/6**

## 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **72/6** POST PAID

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop, Shrewsbury, S.A.E. for lists  
Shropshire

**MUSICAL MIRACLES!** Drum, Cymbals, Waa-Waa and Fuzz modules. New unique effects units, Percussion etc. Good waa-waa kits 49/-. Famous "Mister Bassman" bass pedal unit. Also bargain components list of reset switches etc. Send S.A.F. NOW!—D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.

## MISCELLANEOUS

(continued)

### DO-IT-YOURSELF PRINTED CIRCUIT KITS

AMAZING VALUE! Each pack contains

- ★ P. C. Boards (assorted sizes)
- ★ Eichant
- ★ Resist
- ★ Etching Tank
- ★ Full instructions

Price 16/- and 30/- (extra large). C.W.O. CLIFFORD ELECTRONICS, (Dept. P.W.) 177 Watford Road, Harrow, Middx.

**"FLAME FROM THE AIR"** A revolutionary cigarette lighter that has no wick, flints or moving parts: uses no petrol, gas or batteries; cannot be blown out. Awarded Gold Medal Luxembourg International Trades Fair, 39/6 + 2/6 pp from JW Exports, (Dept. MO2), 44 Earls Court Road, Kensington, London W.8.

## THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

**NOTES ON USE** of TV for UFO Detection. Optical Detector Circuits, 8s 6d. Radar & Electronic Publications, "Highlands," Needham Market, Suffolk.

**EXPRESS ROTARY SWITCHES.** Switches for Mullard audio circuits, also switches made to customers own specifications. For details and price list, write or phone to 189 Edgware Road., London W.2. Tel. 01-723 4455.

## AERIALS

### BAKER AND BAINES

BBC dipole 30/-, H 42/-, 3 ele 89/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/5, 11 ele 57/6, ITA doubles 8 ele 112/-, 11 ele 140/-, 13 ele 159/-, Combined BBC/ITA D+5 45/-, D+8 52/-, H+5 69/-, X+5 75/-, Combined Loft Special D+5 with loft pole and fixings 37/-, UHF Aerials BBC-ITA 14 ele 37/-, 18 ele 54/-, 22 ele 63/-, Double 22 ele 142/-, CO-AX low loss at 1/3 and 2/3, Co-Ax plugs 1/4.  
Diplexers—Triplexers—Matched UHF/VHF Diplexers. VHF/UHF Pre Amps 75/-  
Poles, Lashings, Clamps, Couplers, etc. Postage Paid inland on aerials. Extra on accessories. Please state channels when ordering.

11 Dale Cres., Tupton, Chesterfield.

## HI-FI EQUIPMENT

**SHURE MAGNETIC CARTRIDGES.** Manufacturers pack, brand new, post free, M3DM £4.19.6, M44/5/7 £7.10.0, M44E £8.17.6, M55E £9.17.6, M75/6 Type 2 or M75G Type 2 £12.5.0, M75EJ £15.15.0, M75E Type 2 £16.10.0, GOLDRING G 800 £7.17.6, GARRARD SP.25 £10.17.6, AP.75 £16.10.0, P. & P. 7/6, Complete Hi-Fi Stereo System normally 57gns. Our price 39gns. P. & P. 27/6 Mayware & Co. 38 Achilles Road, London, N.W.6. Mail Order only.

## FOR SALE

## MORSE MADE !! EASY

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognize the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 8d. stamp for explanatory booklet to: 680HS (BOX 11), 46 GREEN LANE, PULLEY, SURREY

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**YUKAN SELF-SPRAY** SO PROFESSIONAL THE REGULAR AEROSOL WAY

Get these NOW! air drying **GREY HAMMER** OR **BLACK WRINKLE** (CRACKLE) Finishes

Yukan Aerosol spraykit contains 16 oz. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/6! at our counter or 16/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Max finish (12 oz. self-spray cans only) 13/11 carriage paid.

**SPECIAL OFFER:** I can plus optional transferable snap-on trigger handle (value 5/-) for 18/11 carriage paid. Choice of 13 self-spray paint colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

Dept: M-YUKAN, 307A, EDGWARE ROAD, Dept. M-YUKAN, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations.—We can supply you too.

Open all day Saturday, Closed Thursday afternoons

**TO CLEAR.**—Sets of over 35 useful components from ex. adm. amplifier panels, sub chassis, rectifiers, condensers, diodes, resistors, James plugs, valve holders, etc. Only 3/- plus 1/6 P&P. Also valves CV2127, CV455, CV4055, CV4024, 2/6 each or 6 for 10/-.—Greene, Fieldings, Poulner, Ringwood, Hants.

**TX. (10 WATTS INPUT) RX.** 150m-80m-40m. Mains or 12v. £12 two for £20 o.n.o. G8CER 5, Quiney Way, Oadby, Leicestershire. Vintage Valves. And New.

**JENNINGS ORGAN.** two manual. A.R.C.O. pedal board. Suit enthusiast. A bargain at £100. Madens Organ Centre, 487 Sheffield Road, Chesterfield. Phone 5404.

**ALL KINDS OF EVERYTHING** for sale to Irish readers. Write for price list, plus Bargain page. Toner Electronics, Lismore Park, Waterford. Phone 3048.

## WANTED

**CASH PAID** for New Valves. Payment by return. WILLOW VALE, ELECTRONICS. 4 The Broadway, Hanwell, London. W.7. 01-567/5400-2971.

**WE BUY** New Valves and Transistors. State price: A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

**WANTED**  
(continued)

**WANTED NEW VALVES ONLY**  
Must be new and boxed  
Payment by return  
**WILLIAM CARVIS LTD.**  
103 North Street, Leeds 7

**WANTED NEW VALVES**, televisions, radiograms, transistors, etc. **STAN WILLIAMS**, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

**SERVICE SHEETS AND MANUALS PURCHASED.** Highest prices paid. Sultan Radio, 29 Church Road, Tunbridge Wells, Kent. Phone T.W. 22093.

**SERVICE SHEETS**

**SERVICE SHEETS** (1925-1970) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 1/- Over 8,000 models available. Catalogue 2/6. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex.

**SERVICE SHEETS.** Radio, TV etc. 8,000 models. List 2/-. S.A.E. enquiries. **TELRAY**, 11 Maudland Bank, Preston.

**TRADER SERVICE SHEETS**

5/- each plus postage

We can supply **Trader Service Sheets** for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

**OAKFIELD ENTERPRISES LIMITED**

30 CRAVEN STREET, STRAND  
LONDON WC2

Make	Model	Radio/TV

1970 List now available at 2/- plus postage

If list is required indicate with X

From .....

Address .....

enclose remittance of .....

(and a stamped addressed envelope)  
s.a.e. with enquiries please

**MAIL ORDER ONLY** (February PW)

**SERVICE SHEETS**  
(continued)

**LARGE SUPPLIER OF SERVICE SHEETS**

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 10/- each, plus large S.A.E.

(Uncrossed P.O.'s please, original returned if service sheets not available.)

**C. CARANNA**

71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

**RADIO, TELEVISION** over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

**SERVICE SHEETS** (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. **THOMAS BOWER**, 5 South Street, Oakenshaw, Bradford.

**RECEIVERS & COMPONENTS**

**RECEIVERS & COMPONENTS**  
(continued)

**A. J. H. ELECTRONICS**  
59 Waverley Road, The Kent, Rugby Warwickshire. Tel. Rugby 71066

**P. C. RECEIVER BOARDS**

PCR.1, 6 transistors OC44, 2/OC45, OC81D, 2/OC81, but less the audio transistors (i.e. OC81D, & 2/OC81, double tuned list. IF transformerless output approx 1/2 watt to 8 ohm speaker will work with any impedance, size 8 1/2 x 3" less ferrite aerial, tuning capacitor, etc. similar to item previously advertised with data 25/- each.

PCR.2, 7 transistors 3/AF117, 2/AC127, 2/AC128, 1/2 watt output to 5 ohm speaker, size 3 1/2" x 7 1/2" IF. & audio complete, no osc. coil, tuning capacitor, ferrite aerial, etc. requires 9v supply, modern board with miniature components, 35/- each with circuit.h

PCR.3, 6 transistors OC44, 2/OC45, OC81D, 2/OC81, transformerless output approx 400 milliwatts requires 6v battery, edgewise volume control, & osc. coil on this board, 3" x 5" as used in pocket portables no details or circuit 25/- each.

All boards as new and unused  
250 pf postage stamp type ceramic compression trimmers 6d each 5/- doz. (new) Screw in type car distributor & coil suppressors 6d each (new).

PUSH-PULL output transformers to match EL84s to 15 ohm speaker with negative feedback winding only 9/- each.

Postage add 1/6 **MAIL ORDER ONLY**

**A CORNUCOPIA OF COMPONENTS!** Scarce valve, selected T.V. components, Speakers, Cabinets. Computer panels—long leads NOT printed circuits. Transistors, resistors—new and recovered. State requirements. S.A.E. (F.S.) for details. **MAIL-MART**, 6 Eastbourne Road, Pevensey Bay, Sussex.

**LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS**

All cabinets are new and carefully designed acoustically with speakers mounted on 1/2 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.



**CAXTON COLUMN.** This is a column cabinet 23 1/2 x 5 1/2 in. deep finished in black or wood grain cloth with blue Vynair front. Key-hole slot for wall mounting. Fitted with three speaker units, 9 ohms impedance. Handles 3 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at 59/6d. P. & P. 10/6d. each.

**SPEAKERS:** Elac Heavy duty Ceramic Magnets 11,000 line, 10in. round, 10 x 8in, 3 ohm or 15 ohm, 48/6. P. & P. 3/6. 8in. round 15, 42/8. P. & P. 3/6. E.M.I. 13 1/2 x 8in. 3 ohm, 45/-. 15 ohm 48/6. P. & P. 1/6. E.M.I. 3in. tweeter 17/6. P. & P. 1/6. E.M.I. 13 1/2 x 8in. fitted two 2 1/2 in. tweeters. 15 ohm 77/6. P. & P. 4/6. E.M.I. 13 1/2 x 8in. (15 ohm) Hi-Fi quality £5.19.6. P. & P. 4/6. E.M.I. Woofers, 6 1/2 x 6 1/2 in. square, 8 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 16/6. P. & P. 1/-. EAGLE Crossover units 3 or 16 ohms, 17/4. P. & P. 1/-. Bakers 12in., 25 watt 15 ohm £6.6.0. P. & P. 3/6.

**VYNAIR** Widths from 40 to 54in., 15/- yd. off roll. P. & P. 1/9. 1/2 yard, 8/-. P. & P. 1/9. Send 1/- stamps for samples.

**SPEAKER MATCHING TRANSFORMERS.** 3, 7, 15 ohms, 8 watt, 13/6. P. & P. 1/6.

**CARTRIDGES:** Stereo: Sonotone 9TA H/C Diamond, 47/6. Ronette S105 Medium Output, 28/6. S106 High Output 28/6. Acos GP93 1 Sapphire, 37/6. GP94 1 Sapphire, 39/6. GP81 Diamond, 42/- GP91 Stereo Compatible (High, Medium or Low Output), 25/- TA800 converts Philips AG3301, AG3306 to B.S.R. SX1H. Plug-in head complete with cartridge, 56/-. TA700 equivalent to B.S.R. SX1M, 35/- Japanese equivalent to B.S.R. TCS8, 35/- P. & P. 1/6. Mono: Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 15/- B.S.R. TC8H Jap. equivalent, 26/- Sonotone 2TSS, 15/- P. & P. 1/6.

**EARPIECES WITH CORD** and 3.5mm. plug, 8 ohm magnetic, 3/- 250 ohm, 4/- 180 ohm with clip, 6/6. Xtal. P. & P. 6d.

**PIANO KEY PUSH BUTTON SWITCHES.** 7 button inc. mains on off. 6 banks of 6 P.C.O., 8/6. P. & P. 1/-.

**INSTANT HEAT.** Soldering gun!  
Save £ £ £'s by tackling intricate soldering jobs yourself! All-purpose soldering gun gives **INSTANT HEAT** Save electricity. Automatic spotlight makes work easier. Spare solder bits only 2/6 each (P. & P. 5d.). Money ref. guarantee.



Only **39/6**  
5/- p.&p.

**BROADWAY ELECTRONICS** (Nr. Tooting Broadway Underground Stn)  
92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 01-672 3984 (Closed all day Wed.)

**RECEIVERS & COMPONENTS**  
(continued)

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/- P. & P. 1/6. With a guaranteed minimum of 35 transistors. Transistor data included.

**SPECIAL BARGAIN PACK.** 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. Transistor data included.

**PANELS** with 2 power transistors sim. to OC28 on each board + components. 2 boards (4x OC28) 10/- P. & P. 1/6d.

9 OAS, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13" x 4".  
4 for 20/- P. & P. 5/-.

**EX COMPUTER "MEMORY" CORE STORE PLANES**

160 BITS £1 P. & P. 2/-  
4,000 BITS £4 P. & P. 4/-  
10,000 BITS £8 P. & P. 8/-


**250 MIXED RESISTORS**  
½ & ¼ watt 12/6 P. & P. 1/6

**DIODES EX. EQPT SILICON**

10 AMP 150 PIV 4 for 10/-  
20 AMP 150 PIV 4 for £1  
35 AMP 150 PIV 4 for 45/- P. & P. 1/-

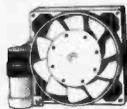**EXTRACTOR / BLOWER FANS (Papst)**

100 c.f.m. 4½" x 4½" x 2"  
2800 r.p.m.  
50/- ea. P. & P. 5/-



**RELAY OFFER**

Single pole changeover silver contacts 2" x 6" x 7" 2.5 KΩ coil operates on 25 to 50v 8 for 10/- P. & P. 1/6

**KEYTRONICS**

**LT/STEP DOWN TRANSFORMER**  
PRI 0, 200, 215, 230, 245v  
SEC 1, 0.10.25v 4A  
SEC 2, 0.115v 2A  
30/- P. & P. 6/- Quantity available

**12V 4A POWER SUPPLY**

Extremely well made by Frako GMBH in West Germany with constant voltage mains transformer, tapped input from 115 to 240V full wave rectification and capacitor smoothing. Size 9 x 6 x 5. Weight 11lbs. These units are brand new unused and fully guaranteed. Makers price believed to be around £80.

**OUR PRICE £9.10.0** Carr. 10/-

**150 HIGH STABS ½, ¼ and 1 Watt**  
5% and Better 12/6d. P. & P. 1/6

**LARGE CAPACITY ELECTROLYTICS**

1500 Mfd 150v  
4000 Mfd 72v  
5000 Mfd 36v 7/6 each  
16000 Mfd 12v P. & P. 1/6d.  
£3 10 0 Doz. P. & P. 10/-

**EXTENSION TELEPHONES**

19/6 Ea. P. & P. 5/-  
35/- for 2 P. & P. 7/-



These phones are extensions and do not contain bells.

**MAILING ADDRESS**

52 EARLS COURT ROAD, LONDON W8  
WAREHOUSE & DISPATCH  
01 478 8499

**VALVE BARGAINS**

Any 5, 9/-; 10, 14/-; 100, £5 10s from the following:

ECC82, ECL80, EF85, EF183, EBF89, EB91, EY86, PCC84, PCC89, PCF80, PCF86, PCL82, PCL83, PCL84, PL36, PL81, PY33, PY81, PY82, PY800.

**AERIAL BOOSTERS 59/-**

Three types of High Gain Transistorised pre-amplifiers all at the same price  
UHF 625 Type L45, Tunable over the complete UHF Stations  
VHF 405 Type L12 with Separate Tuning for Band 1 and Band 2. Please state channel numbers

FM UHF RADIO PRE-AMPLIFIER SAE for Full Details. All complete with battery and leads, 7 day money back guarantee if not satisfied

VELCO ELECTRONICS, 62 BRIDGE ST., RAMSBOTTOM, BURY, LANCS.

**Stella Nine Range Cases**

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

**LIST OF PRICES AND SIZES**  
which are made to fit Standard Alloy Chassis

Width	Depth	4" Height		6" Height		7½" Height	
		£ s. d.	£ s. d.	£ s. d.	£ s. d.		
6½"	3½"	12	6	15	0	18	0
6½"	4½"	13	6	18	0	1	0
8½"	3½"	15	0	1	0	1	0
8½"	6½"	1	0	2	6	1	1
10½"	7½"	1	8	1	5	1	8
12½"	8½"	1	0	1	6	1	1
12½"	5½"	1	8	0	14	0	17
12½"	8½"	1	16	0	2	3	0
14½"	3½"	1	5	0	1	11	6
14½"	9½"	2	3	0	2	15	9
16½"	6½"	1	18	6	2	6	3
16½"	10½"	2	10	0	3	5	0

Cases—Post 4s. 6d. per order.  
Discounts available on quantities.

**CHASSIS in Aluminium, Standard Sizes, with Gusset Plates**

Sizes to fit Cases. All 2½" Walls

	s. d.	s. d.	s. d.	s. d.	
6" x 3"	5 6	10" x 7"	8 6	14" x 3"	7 3
6" x 4"	5 9	12" x 3"	6 9	14" x 9"	14 6
8" x 3"	6 6	12" x 5"	7 6	16" x 6"	10 9
8" x 6"	7 9	12" x 8"	10 9	16" x 10"	16 0

Chassis—Post 3s. 0d. per order.  
Discounts available on quantities.

**E. R. NICHOLLS**

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE  
Tel: 061-480 2179

**JEF ELECTRONICS**

New Full Specification Devices

Integrated Circuits complete with data:

GE PA230 Audio Preamplifier 18/6d  
GE PA234 1W Audio Amplifier 17/6d  
GE PA237 2W Audio Amplifier 32/6d  
Plessey SL402A Preamp & 2W Amp 42/-  
MEL 11 Photo Darlington Amp 9/6d  
Connectors for GE I.C.'s 7/-

High Quality low cost transistors:  
GE 2N5172 NPN 200mW 1/9d; ME 0412  
PNP 200mW 3/9d; TI 2N4059 PNP 250mW  
3/6d; MUL BFX86 NPN 800mW 6/-; MUL  
BD124 NPN 15W 12/-; S 2N3055 NPN  
115W 14/6d.

Triacs for full wave power control:  
RCA 40669 8A 400V 24/-; RCA 40583  
Trigger Diode 5/3d.

Plastic rectifiers for power supplies:  
1N 4820 1.5A 400V SI Rectifier 2/6d;  
W005 1A 50V full wave bridge SI 7/6d;  
PD40 2A 400V full wave bridge SI 15/-.  
C.W.O. P. & P. 1/- per order.

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail order only

**EMSAC FOR ANTENNA SYSTEMS AND CONVERTERS.** Please send s.a.e. for details of 2 metre converters, antennas and transmatchers for receiving and transmitting.  
**ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD.,** Highfield House, West Kingsdown, Kent. Tel. W.K. 2344.

**150 NEW ASSORTED** Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hytstab, Vitreous, ¼-20 watt, 15/- Post Free.  
**WHITSAM ELECTRICAL,** 33 Drayton Green Road, West Ealing, W.13.

Free and Illustrated Lists of all types of Hi-Fi equipment; Tuners, Amps, etc. Electronic equipment, components, and gadgets at lowest prices from:  
**ALBION ELECTRONICS SUPPLIES, D/3,** 16 Albion Road, Bircnington, Kent.

**R. & R. RADIO (P.W.1)**  
51, Burnley Road, Rawtenstall,  
Rossendale, Lanc's. BB4 8EW.

EB91 2/- EBF89 3/6 ECC82 3/-  
ECL80 3/- EF80 2/- EF85 3/-  
EF183 3/6 EY86 4/- PCC84 3/-  
PCC89 4/- PCF80 3/- PCL83 4/-  
PCL82 4/- PCL84 5/- PL36 5/-  
PL81 5/- PY33 5/- PY81 3/6  
PY82 3/- U191 4/6 6BW7 3/-  
30F5 3/6 30P12 4/- PY800 3/6

All valves guaranteed 3 months. Post one valve 9d over six post paid. Quotations given for any items required, S.A.E. please.

**BRAND NEW ELECTROLYTICS 15/16V**  
0.5, 1, 2, 5, 8, 10, 20, 30, 40, 50,  
100 mfd. 8.5d. postage 1s. The C.R.  
Supply Co., 127 Chesterfield Rd., Sheffield,  
8.

## RECEIVERS & COMPONENTS

(continued)

### NEW MODEL V.H.F. KIT MK2

Our latest Kit improved design and performance plus extra Amplifier Stage receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4 etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

ONLY 68/- P. & P. FREE U.K. ONLY.

Postal Orders, Cheques to:

Dept.P.W.

Galleon Trading Co., 298A Lodge Lane, Romford, Essex.

**COMPLETE RANGE** of Amateur Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

**COMMUNICATIONS RECEIVERS:** Ex-Govt. bargains in the £10 to £20 range, including: R209, PCR2, CR300, B40, B41, Murphy HF/MF, and others. Write or phone for details. P. R. GOLLEDGE, G3EDW, Glen Tor, Torrington, Devon. 08-052 2411.

**AUDIOSCAN-HI-FI** loudspeaker systems for the home constructor, cabinet kits, new range of Peerless speakers, speaker kit systems and cross-over networks, BAF wadding and all necessary components. Free speaker fabric samples on request. Send 9d in stamps to: AUDIOSCAN, Dept. P.W., 4 Princes Square, Harrogate, Yorks.

## BOOKS & PUBLICATIONS

### TAPE RECORDING YEAR BOOK

COMPLETELY NEW NINTH EDITION WITH COMPREHENSIVE CATALOGUE SECTION AND ARTICLES BY EXPERTS

PRICE 10/6d. from

7 ALVERSTONE AVENUE, EAST BARNET, HERTS.

### SURPLUS HANDBOOKS

19 set Circuit and Notes .. 7/0 p/p 9d.  
1155 set Circuit and Notes .. 7/0 p/p 9d.  
H.R.O. Technical Instructions .. 6/0 p/p 9d.  
38 set Technical Instructions .. 6/0 p/p 9d.  
46 set Working Instructions.. 6/0 p/p 9d.  
88 set Technical Instructions .. 7/0 p/p 9d.  
BC.221 Circuit and Notes .. 6/0 p/p 9d.  
Wavemeter Class D Tech. Instr. .. 6/0 p/p 9d.  
18 set Circuit and Notes .. 6/0 p/p 9d.  
BC.1000 (31 set) Circuit and Notes .. 6/0 p/p 9d.  
CR.100/B.28 Circuit and Notes .. 10/6 p/p 1/-  
R.107 Circuit and Notes .. 7/0 p/p 9d.  
AR.88D Instruction Manual .. 18/6 p/p 9d.  
62 set Circuit and Notes .. 7/0 p/p 9d.  
Circuit Diagram 5/6 each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624. 22 set.  
Colour Code Indicator.. 2/8 p/p 6d.  
52 set Sender and Receiver circuits 8/- post free

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

**INSTRUCTIONAL HANDBOOK SUPPLIES**

DEPT. PW, TALBOT HOUSE, 28 TALBOT GARDENS, LEEDS 8

## EDUCATIONAL

**BECOME** "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. CHAMBERS COLLEGE (Dept. 857K), 148 Holborn, London, E.C.1.

## EDUCATIONAL

(continued)



## TELEVISION

This private College provides efficient theoretical and practical training in Radio and TV Servicing. One-year day courses, commencing in Sept., January and April, are available for beginners, and shortened courses for men who have had previous training. Write for free prospectus to:—

London Electronics College, Dept. LX/4, 20 Penywern Road, Earls Court, London, S.W.5 Tel. 01-373 8721

## TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs) R.T.E.B., etc. Many non-exam courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON. SW8

**CITY & GUILDS** (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc. send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

**RADIO OFFICER** training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

## APPOINTMENTS

## CAREERS IN SCIENCE AND ENGINEERING

Exciting and rewarding opportunities in these fields are almost unlimited

Write now for details of the following courses offered by —

## BOURNEMOUTH COLLEGE OF TECHNOLOGY

### UNIVERSITY OF LONDON EXTERNAL DEGREES

B.Sc. General (Hons.)—Mathematics, Physics, Chemistry, Botany, Zoology, Statistics

B.Sc. (Eng.) (Hons.)—Electrical (including Electronics)

These courses are suitable for both men and women.

Study by the Sea in Britain's foremost international and cultural resort.

For prospectus apply to:

The Principal, Room 69, College of Technology, Lansdowne, Bournemouth, BH1 3JJ. Tel. B.20844

## SITUATIONS VACANT

# Radio Operators

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1971 and in subsequent years.

Specialist training courses lasting approximately nine months, according to the trainee's progress, are held at intervals. During training a salary will be paid on the following scale:—

Age	£800 per annum
21	855
22	890
23	925
24	965
25 and over	965

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade 1 scale:—

Age	£965 per annum
21	1025
22	1085
23	1145
24	1215
25 (highest age point)	1215

then by six annual increases to a maximum of £1,650 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad. Applicants must normally be under 35 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or PMG qualifications.

Interviews at intervals throughout the year. Application forms and further particulars from:—

**RECRUITMENT OFFICER, Government Communications Headquarters,**

Oakley, Priors Road, CHELTENHAM, Glos. GL52 5AJ

Tel: No. Cheltenham 21491 Ext 2270

**ENGINEERS, A TECHNICAL CERTIFICATE** or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Drafts., Building, etc. For full details write for FREE 132 page guide: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. Write for 132 page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept 137K), Aldermaston Court, Aldermaston, Berks.

## METAL WORK

**METAL WORK:** All types cabinets, chassis, racks etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

## ELECTRICAL

**240 VOLT  
ELECTRICITY  
ANYWHERE**



**BEST EVER 200/240 VOLTS "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY**

Exclusive World Scoop Purchase. The fabulous Mk. 2D American Heavy Duty Dynamo Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. **Brand New and Fully Tested, only £4.10.6.** plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details. **Dept. PW STANFORD ELECTRONICS,** Rear Derby Road, North Promenade, Blackpool, Lancashire.

## PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDEGE,  
YORKS. Tel. Heckmondwike 4285

Amplifier Units Type A1413. Complete with Valves Type 5Z4 and 6V6GT. 230-250 Volt 50 cycles. Transformer Class Condition. Untested 25/-. Carriage B.R.S. 15/-

Air Mileage Units complete with 24 volt Motor and Gears etc. Clean condition. Untested, less Relay 15/-. Carr. B.R.S. 12/-

Special Sale of New C.V. Valves. Removed from units. 12 months Guarantee. P/P on any Valve 9d.

CV138 2/- CV140 2/- CV455 2/- CV284 1/- CV287 1/- CV345 1/- CV455 2/- CV136 2/-

Speakers P.M. All 3 ohm. Perfect condition, removed from TV sets. P/P on any Speaker 4/- 6 inch Round 3/-, 5 inch Round 3/-, 8 x 5 Elliptical 6/-, 7 x 4 Elliptical 5/-, 6 x 4 Elliptical 3/-, Slot Speakers 8 x 24 Elliptical 3/-

AW43/80 T.V. Tubes. Good Picture. No Guarantee £1. Plus carriage 15/-

Reclaimed T.V. Tubes with 6 months Guarantee 17" Type AW43/80, AW43/88. £2 each. MW43/69 30/- All Tubes 15/- carriage.

Silicon Rectifiers. 500 MA. 800 P.I.V. 2/6 or 24/- Per doz. Post Paid.

Jap Earpieces. Magnetic. 8 ohms. Small or Large Plug. 1/11 Post Paid.

Top Grade Mylar Tapes 7 inch Long Play 14/-, 7 inch Standard 11/6. 5 inch Standard 7/9. 5 inch Long Play 10/-. Post on any Tape 1/9.

Panel of 19, mixed Parts 7/6 Post Paid. Ex Units. Panels of Resistors and Condensers. 9/- Post Paid Ex Units.

Complete Untested 17 inch T.V. Sets 12 Channel 50/- carriage £1.

Aircraft Sighting Head, with Gyro Unit. Condition Fair. 18/6. Carriage B.R.S. 12/-

**VALVE LIST—Ex. Equipment, 3 months' guarantee. Single Valves Post 7d., over 3 Valves p. & p. paid**

ARP12	1/6	PCL82	4/-	6B8	1/6
EB91	9d	PL36	5/-	6BW7	2/6
EBF80	3/-	PL81	4/-	6U4	5/-
ECC81	3/-	PY81	1/6	10P13	2/6
ECC82	3/-	PY33	5/-	20D1	3/-
EF50	1/-	PY82	1/6	20P1	5/-
EF91	9d	PZ30	5/-	20P3	2/6
EY86	5/-	U191	5/-	30PL1	5/-
PCC84	2/-	U251	5/-	30F5	2/6
PCF80	2/-				

## NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors. Loft Mounting Arrays, 7 element, 40/-, 11 element, 47/6, 14 element, 55/-, 18 element, 62/6. Wall Mounting with Cranked Arm, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6, 11 element, 55/-, 14 element, 62/-, 18 element, 70/-. Chimney Mounting Arrays, Complete, 7 element, 72/6, 11 element, 80/-, 14 element, 87/6, 18 element, 95/-. Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Preamps from 75/- State clearly channel number required on all orders.

## BBC - ITV AERIALS



BBC (Band 1). Loft, 25/- External S/D, 30/-. "H" £2.15.0. ITV (Band 3). 3 element loft array, 30/-, 5 element, 40/-, 7 element, 50/-, Wall mounting, 3 element, 50/-, 5 element, 55/-, Chimney 1 + 3, 70/-; 1 + 5, 80/- VHF transistor pre-amps. 75/-

**COMBINED BBC1 - ITV - BBC2 AERIALS** 1 + 3 + 9, 70/-, 1 + 5 + 9, 80/-, 1 + 5 + 14, 90/-, 1 + 7 + 14, 100/- Loft mounting only.

F.M. (Band 2). Loft S/D, 17/6. "H", 35/-, 3 element, 57/6. External units available. Co-ax. cable 8d. yd. Co-ax. plunks, 1/6. Outlet boxes, 5/-, Diplexer Crossover Boxes, 17/6. C.W.O. or C.O.D. P. & P. 6/6. Send 6d. stamps for illustrated lists.

Callers welcomed — open all day Saturday

**K.V.A. ELECTRONICS (Dept. P.W.)**  
40-41 MONARCH PARADE  
LONDON ROAD, MITCHAM,  
SURREY 01-648 4884

Est. 1943 **JOHNSONS** Tel: 24864

New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

**JOHNSON'S (RADIO)**  
St. Martin's Gate, Worcester

Please mention

**PRACTICAL  
WIRELESS**

when replying to  
advertisements

## NEW VALVES!

Guaranteed and Tested  
24-HOUR SERVICE

IR5	5/6	DL94	5/9	EL84	4/9	PL504	13/3
185	4/3	DL96	7/-	EY51	7/-	PY32	10/-
1T4	2/9	DY86	5/3	EBY6	6/3	PY33	10/-
384	5/9	DY87	5/3	EZ80	4/6	PY81	5/-
3V4	5/9	EABC80	5/9	EZ81	4/6	PY82	5/-
6/30L2	11/6	EBCC33	7/9	KT61	9/3	PY83	5/6
6AQ5	4/3	EBCC41	9/3	KT66	18/6	PY88	6/6
6V6G	3/-	EBF80	6/-	N78	17/-	PY800	7/7
28L6GT	4/6	EBF89	5/9	PABC80	6/9	PY801	6/9
30FL1	13/9	ECC81	3/6	PC86	10/3	B19	6/3
30FL12	14/3	ECC82	4/-	PC88	10/3	T35	12/9
30P4	4/3	ECC86	7/6	PC900	7/7	U28	11/6
30P19	11/6	ECC85	5/-	PCC84	6/3	U191	12/-
30PL1	14/6	ECH35	5/6	PC889	8/11	U193	8/6
30PL13	16/9	ECH81	5/9	PCF80	5/11	U261	14/-
ECC35	13/-	ECL80	6/6	PCF801	6/9	U301	10/-
CL33	17/6	ECL82	6/3	PCF802	6/9	U329	14/-
DA32	6/9	ECL83	6/6	PC882	6/9	U330	6/6
DAF31	4/3	ECL86	7/6	PCL83	11/9	UBC41	8/3
DAF96	6/9	EF37A	6/-	PCL84	7/-	UF89	6/3
DF33	7/6	EF39	4/6	PCL85	8/6	UCC85	7/3
DF91	2/9	EF80	4/6	PCL86	8/6	UCH81	6/6
DF96	6/9	EF85	5/9	PFL200	11/-	UCL82	6/9
DK32	6/9	EF88	6/3	PL36	9/3	UF41	10/8
DK61	6/6	EF89	4/9	PL81	15	UFB39	8/-
DK92	8/3	EF183	5/6	PL82	5/9	UL41	11/9
DK96	7/3	EF184	5/3	PL83	6/9	UL14	6/3
DL35	4/9	EH90	6/-	PL84	6/-	UY41	7/7
DL92	5/9	EL33	9/3	PL600	12/9	UY85	5/8

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any insured parcel against damage in transit 6d. extra. Office address, no callers.

## GERALD BERNARD

83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON, N.16

## AUDIO EFFECTS

5 SHAW LANE, HALIFAX YORKS

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

**AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT.** No fuss, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco plug in coils 2T. 0.5 to 1.54 Mhz 3T. 1.67 to 5.3 Mhz 4T. 5.0 to 15 Mhz 5T. 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 9 volt battery. Easy step by step instructions. Complete Kit. £8.19.6 plus 5/6 P. P. & Ins. Extra ranges 12/- per range.


**POWER CONTROLLER.** Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3Kw triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions £6.9.6. Ready built £9.4.6 plus 5/6 P. P. & Ins. **REVERBERATION AMPLIFIER.** Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2" x 3 1/2" x 4 1/2". £10.4.0 plus 6/- P. P. & Ins.

**VOX SWITCH.** This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 42/6. Ready built, tested and guaranteed. 62/6, plus 2/6 P. P. **METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive black and white polythene case, 37/6 post paid.

**MORSE OSCILLATOR.** PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 25/- post paid. **STRAIGHT FROM THE PRESS.** Latest Mullard manual: Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi Tape, etc. etc. 32/6 post paid.

**JUST ARRIVED IN STOCK.** Texas transistors. Complementary symmetry. Driver. NPN. PNP output. The set of three ONLY 6/6 post paid. Free lists with every order. For lists only send 1/6 (deductible from first order).

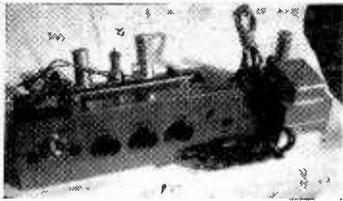**AMPLIFIER FOR MAGNAVOX TAPE DECKS — 4 TRACK**



Chassis 12½ x 5½ x 4½ in. high. Plastic front panel finished in Black and "Silver". 200-250 A.C. Record/Playback amp. switch; Off/On-Tone. Vol./Mc.; Vol./Gram; Mic. Input; Gram. Input; Valves 6BR7; 12AX7; EM84; EL84 and EZ80. Separate Output Transformer (Already wired to amp). PRICE £12 (10/- P. & P.). 3-ohm speaker 7" x 4" 16/- extra.

**STEREO AMPLIFIER type HV—2 x 3 Watts**

Fully built. On off. sep. vol. and tone each channel 12 x 4½ x 6 in. high. EZ80. 2 x ECL86; for 3 ohm speakers, double wound main trans; fixing flanges and base plate, suitable for crystal cart, tuner etc. £6.10.0 (8/- p. x p.)



Superior version — separate base, treble & vol each channel with mono/stereo switch 15/- extra

**STEREO AMPLIFIER type RC—2 x 3 Watts**

Fully built. 2" x UCL82, metal rect; ganged vol. and tone cont; on-off, balance. 11 x 3½ x 4 in high. Double wound mains trans, with supporting brackets. For 3-ohm speakers. £6 (8/- p. & p.).



**MONO GRAM CHASSIS 3 WATT**

3 Wave band long-med-short. Gram., 200-250v AC Ferrite aerial. Chassis 13 x 7 x 5 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH81 EF89, EBC81. EL84, EZ80. Price £10.12.6. (7/6 p. & p.) Output trans. for 3-ohm speaker.

NEW TAPE AMPLIFIER for 4 track B.S.R. Deck TD2. Mains and output Trans. 10" x 6" x 4" overall. Rect; ECC83, EL84. Mike and Gram inputs. £7.5.0 (10/- P. & P.). For 3-ohm speaker.

**GLADSTONE RADIO**

66 ELMS ROAD, ALDERSHOT, Hants. (2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240 CLOSED WEDNESDAY. S.A.E. for enquiries please.

**SEMICONDUCTORS**

BRAND NEW AND FULLY GUARANTEED

1N914	1/6	2N2906	6/-	ACY28	4/-	BD121	17/6	MJ481	27/6
1N916	1/6	2N2906A	6/8	AD140	8/-	BD123	21/6	MJ490	22/6
18021	4/-	2N2923	3/6	AD149	11/6	BD124	12/-	MJ491	29/6
18025	5/-	2N2924	3/6	AD161	7/6	BF115	5/-	MFF102	8/6
18113	3/-	2N2925	3/6	AD162	7/6	BF117	10/6	MFF103	7/6
18120	2/6	2N2926	3/6	AF114	5/-	BF167	5/8	MF104	7/6
18121	2/6	" Green 3/6		AF116	5/-	BF173	7/6	MFI05	7/6
18130	2/6	" Yellow 2/9		AF117	5/-	BF180	7/6	NKT0013	8/6
18131	2/6	" Orange 2/9		AF118	12/6	BF181	6/6	NKT216	7/6
18132	2/6	2N3011	12/6	AF124	4/6	BF184	7/6	NKT217	8/6
1844	2/-	2N3053	5/8	AF125	4/6	BF194	5/-	NKT261	4/-
2G301	4/-	2N3054	12/6	AF126	4/6	BFX12	4/6	NKT262	4/6
2G302	4/-	2N3055	15/-	AF127	3/6	BFX13	4/6	NKT263	4/6
2G303	4/-	2N3702	3/6	AF139	5/6	BFX29	12/6	NKT271	4/6
2G371	3/-	2N3703	4/6	AF181	8/6	BFX30	9/-	NKT272	4/6
2N696	4/-	2N3704	4/6	AF186	11/-	BFX35	19/6	NKT274	4/-
2N697	5/-	2N3705	4/6	AF239	7/6	BFX43	8/6	NKT275	4/6
2N698	4/6	2N3706	4/6	AF256	5/6	BFX44	8/6	NKT281	5/6
2N706	2/6	2N3707	4/-	ASV27	8/6	BFX54	7/6	NK403	15/-
2N708	2/6	2N3708	3/6	ASV28	5/6	BFX85	8/6	NKT404	12/6
2N708	4/-	2N3709	3/6	ASV29	5/6	BFX86	6/6	NKT405	15/-
2N929	5/6	2N3710	4/-	ASZ20	7/6	BFX87	6/6	NKT613	6/6
2N930	7/-	2N3711	4/-	ASZ21	7/6	BFX88	5/-	NKT674	5/6
2N1090	6/6	2N3819	9/-	BA102	6/6	BFY10	4/6	NKT677	5/6
2N1091	6/6	2N3820	22/6	BAX13	1/6	BFY17	4/6	NKT713	5/-
2N1131	5/6	2N3821	8/6	BAX19	1/6	BFY18	4/6	NKT773	5/-
2N1132	6/6	2N4058	5/6	BAY31	1/6	BFY19	4/6	NKT781	6/6
2N1302	3/6	2N4059	5/-	BAY38	3/6	BFY20	12/6	NKT20529	8/6
2N1303	3/6	2N4060	5/-	BC107	3/6	BFY41	10/-	NKT801115/6	
2N1304	4/6	2N4061	4/6	BC108	3/6	BFY43	12/6	NKT801219/6	
2N1305	4/6	2N4062	4/6	BC109	3/6	BFY50	4/6	NKT801322/6	
2N1306	5/-	2N4234	8/6	BC113	3/6	BFY21	4/6	CA5	2/-
2N1307	5/-	2N4255	8/6	BC116	12/6	BFY22	4/6	CA9	2/-
2N1308	6/-	2N4284	3/6	BC118	6/6	BFY76	8/6	CA70	1/6
2N1309	6/-	2N4285	3/6	BC125	11/-	BFY77	11/6	CA73	2/6
2N1607	5/6	2N4286	3/6	BC126	11/-	BFY90	12/6	CA79	1/6
2N1613	5/-	2N4287	3/6	BC147	3/6	B8X19	3/6	CA81	1/6
2N1711	6/6	2N4288	3/6	BC149	3/6	B8X20	3/6	CA85	1/6
2N1889	6/6	2N4289	3/6	BC149	3/6	B8X21	7/6	CA90	7/6
2N1893	8/6	2N4291	3/6	BC167	3/6	B8X26	10/6	CA91	1/6
2N2102	15/-	2N4292	3/6	BC168B	3/6	B8X27	10/6	CA95	1/6
2N2147	14/6	40361	12/6	BC168C	3/6	B8X28	6/6	CA200	2/-
2N2148	12/6	40362	12/6	BC169B	3/6	B8Y29	18/6	CA202	2/6
2N2149	12/6	3N128	18/6	BC169C	3/6	B8Y26	4/6	OC26	6/6
2N2193	3/6	3N140	4/6	BC182L	4/6	BSV22	4/6	OC28	10/6
2N2193A	5/6	3N141	21/6	BC212L	5/-	BSV28	4/6	OC29	15/-
2N2194A	5/6	3N142	16/6	BCY30	5/6	BSV29	4/6	OC35	6/6
2N2217	5/6	AA213	2/-	BCY31	5/6	BSV38	4/6	OC36	6/6
2N2218	8/6	AA215	2/6	BCY32	7/6	BSY39	4/6	OC44	4/-
2N2219	9/6	AA217	2/6	BCY33	4/-	BSY40	6/6	OC45	2/6
2N2220	5/6	AC138	6/-	BCY34	4/6	BSY51	9/6	OC71	2/6
2N2221	5/-	AC126	4/6	BCY38	4/6	BSY52	9/6	OC72	2/6
2N2222	6/6	AC127	5/-	BCY39	7/6	BSY53	8/6	OC75	4/6
2N2368	5/-	AC128	4/6	BCY40	6/6	BSY54	10/6	OC81	4/6
2N2369	3/-	AC176	5/-	BCY42	3/-	BSY96A	2/6	OC83	4/6
2N2389A	5/6	AC187	12/-	BCY43	3/6	BY100	4/6	OC81D	4/6
2N2389B	4/6	AC138	12/6	BCY45	7/6	BY151	5/6	OC82	4/6
2N2640	4/6	ACY17	5/-	BCY70	4/6	BYZ10	9/-	OC139	6/6
2N2646	11/6	ACY18	5/-	BCY71	8/6	BYZ11	7/6	OC140	6/6
2N2904	9/-	ACY19	5/-	BCY72	4/-	BYZ12	6/-	OC200	6/6
2N2904A	8/-	ACY20	5/-	BDY20	25/6	BYZ13	5/-	OC201	7/6
2N2905	8/-	ACY21	5/-	BD116	35/-	MJ480	20/6	OC202	10/6
2N2906A	9/-	ACY22	4/-						

**YOUR CAREER in RADIO & ELECTRONICS ?**

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME ..... Block

ADDRESS ..... Caps.

Please 1/70

**BRITISH NATIONAL RADIO SCHOOL**

**PLESSEY INTEGRATED CIRCUITS**

8L402A	42/6
8L403A	49/6
Data Sheets	2/-

**MULLARD INTEGRATED CIRCUITS**

TAA241 Operational Amplifier	47/6
TAA243 Operational Amplifier	47/6
TAA 263 Linear AF Amplifier	15/6
TAA 300 Linear A.F. Amp	47/6
TAA 320 Most LF Pre-amplifier	15/6
TAA 350 Wide-band Lim	
Df. Amp	45/-
Data Sheets 1/-	

**SPEAKERS (3 ohm)**

10in. x 6in. 27/6	4
9in. x 4in. 23/6	4
8in. x 5in. 19/6	5
7in. x 4in. 15/6	6-4
5in. x 3in. 12/6	8
3in. 9/8, 5in. 14/8	8
8in. 27/6, 12in. 39/6	8

Post and Packing 2/9

**THERMISTORS**

R53 (STC)	25/6
K151 (1K)	2/6
Various Mullard Thermistors in stock.	

Send 2/6 for new comprehensive catalogue. P.P. for Components 1/6 per order.

**THYRISTORS**

1 AMP: 50V 8/-, 100V 5/6, 200V 7/-, 400V 9/6.  
3 AMP: 50V 8/-, 100V 7/8, 200V 9/-, 400V 10/6.  
ZENERS: 1 1/2 WATT 2-7-33V 4/6.  
400m/w 3-0-33V 4/-, 1 Watt. 2-4v-200v 7/6.

**INTEGRATED CIRCUITS—R.C.A.**

CA3005 30/-, CA3011 20/-, CA3012 25/-, CA3013 30/-, CA3014 30/-, CA3018 25/-, CA3019 25/-, CA3020 27/6, CA3021 42/6, CA3022 35/-, CA3023 32/6, CA3026 27/6, CA3028 A25/-, CA3028B 35/-, CA3035 35/-, CA3036 20/-, CA3039 A25/-, CA3046 25/-, CA3048 52/6, CA3051 25/-.

**FAIRCHILD**

L900, 914 11/-, L923 14/-, L701C 17/6, L702C 45/-, L709C 27/6.

**G.E. INTEGRATED CIRCUITS**

PA230 27/6, PA234 26/6, PA237 45/-, PA246 57/6.  
Data Sheet 1/-.

**Presets std., horiz. or vert. Potentiometers. Log/Lin**

MFD	V	Price	MFD	V	Price	MFD	V	Price
1	40	1/9	25	10	1/8	200	6-4	1/6
2	15	1/6	25	50	1/8	250	25	2/8
2	350	2/-	32	15	1/8	250	50	3/9
2-5	16	1/9	32	450	5/6	320	10	1/6
4	15	1/6	40	6-4	1/8	400	16	2/9
4	40	4/9	40	16	1/8	500	6	2/8
4	350	2/3	50	12	1/8	500	25	3/9
5	15	1/6	50	25	1/8	500	50	4/9
6-4	6-4	1/9	50	50	2/-	640	16	3/8
8	18	1/8	64	25	1/8	1000	16	4/8
8	40	1/8	80	6-4	1/8	1000	25	5/8
8	450	3/-	80	16	1/8	1000	50	7/8
10	15	1/6	100	6-4	1/8	2000	25	5/8
10	25	1/6	100	12	1/6	2000	50	12/6
12-5	25	1/9	100	25	2/-	2500	25	9/6
16	18	1/8	100	50	2/8	5000	25	12/6
25	6-4	1/8	125	4	1/8	6000	50	19/6

**VERBOARD**

2 1/2in. x 3 1/2in.	3/6	4/-
2 1/2in. x 5in.	4/6	4/8
3 1/2in. x 3 1/2in.	4/3	4/9
3 1/2in. x 5in.	5/6	5/8
2 1/2in. x 17in.	12/6	
3 1/2in. x 17in.	16/-	21/6

**RESISTORS**

1/2 watt 5%. 4d.  
1 watt 5%. 5d.  
1 and 1/2 watt 5%. 5d.  
2 watt 5%. 1/6.  
5 watt 5%. 2/-.  
10 watt 5%. 2/6

**A. MARSHALL & SON**

28 CRICKLEWOOD BROADWAY, LONDON N.W.2  
01-452 0161/2/3 CALLERS WELCOME

Post & Packing U.K. only 1/6. Europe 5/-, Commonwealth (Air) 13/-

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel. PARK 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office  
When sending cash with order, please include 2/6 in £ for postage and handling  
MINIMUM CHARGE 2/6. No C.O.D. orders accepted

PLEASE NOTE THAT THE VALUES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel. LANGHAM 8403  
Open all day Saturday

First Quality Fully Guaranteed



ELECTRONIC VALVES

OA2	6/6	6AV6	8/-	6F18	8/-	10F9	10/-
OA3	9/-	6AW8A	11/-	6F22	8/6	10F8	8/6
OB2	6/6	6BE6	5/6	6F23	15/6	10L1	8/-
OB3	10/-	6BE5	4/6	6F24	13/6	10LD11	11/-
OC3	7/-	6BF5	16/-	6F25	15/-	10P13	11/-
OD3	6/6	6BF6	9/-	6F26	7/-	10P14	20/-
1B3GT	7/6	6BG6G	12/-	6F28	14/-	12AB5	10/6
1L4	3/6	6BH6	8/6	6F29	8/6	12AC6	7/6
1R4	6/6	6BJ6	10/-	6F30	7/-	12AD6	7/6
1R5	7/6	6BK4	7/6	6F4	9/6	12A15	8/-
1R8	5/6	6BL4	7/6	6J5GT	6/-	12A25	8/-
1R5	6/-	6HN5	8/6	6J7	8/6	12A26	5/6
1T4	4/6	6KN4	8/-	6KN4	10/-	12A27	6/6
1U4	6/-	6RQ5	5/6	6K7	6/6	12A28	5/6
1U5	9/6	6RQ7A	7/6	6K8G	9/-	12A27	6/-
1V2	9/6	6R18	12/-	6K23	10/-	12AV6	6/-
1X2B	7/6	6B8	26/-	6L25	15/-	12AV7	9/-
2D21	6/6	6BW6	16/-	6L6GT	9/-	12AX7	6/-
3A4	4/-	6BW7	13/6	6L7	6/6	12AY7	13/6
3B28	42/6	6BX6	5/-	6L18	6/-	12B4A	10/-
3BP1	55/-	6BZ6	6/6	6LD20	6/6	12BA6	6/6
3Q4	8/-	6C4	6/-	6NTG7	7/-	12BA7	6/6
3R5	7/-	6C5GT	7/-	6P1	12/-	12BE6	6/6
3V4	8/-	6CA4	5/6	6P25	21/-	12BH7	6/6
5R4G Y	11/-	6CA7	10/6	6P28	12/6	12BY7	10/-
5U4G	6/-	6CB6	5/6	6Q7	7/6	12K5	10/6
5U4G B	7/6	6CDBGA	6/6	6R7	7/-	12K7GT	7/-
6V4G	8/-	6C7	23/-	6S2	8/6	12L7G	5/6
6Y3GT	6/-	6C7G	11/-	6S4A	8/-	12M7G	5/6
6Z3	8/6	6CH6	11/-	6S47	7/6	12N2G	7/-
6Z40T	8/-	6CL6	10/-	6S67	6/6	12N87	5/6
6/30L2	15/-	6CW4	12/6	6S7	7/6	12N87	5/6
6A4	6/6	6CY5	8/-	6R67	6/6	12N87	5/6
6A4A	9/6	6C7	12/-	6BL7GT	6/6	12N87GT	8/-
6A7	7/6	6D	6/6	6B7GT	6/6	12N87GT	8/-
6A8	10/-	6DC6	13/6	6R67	8/-	12N87	6/6
6A18	5/6	6DK6	8/6	6R7	7/6	12N87	6/6
6AK5	6/-	6DQ6	12/-	6T8	6/6	1487	16/-
6AK6	11/6	6D84	15/-	6U4GT	12/6	20D1	9/-
6AL3	8/6	6E2A	11/-	6U8	7/-	20L1	20/-
6AL5	3/6	6E17	6/6	6V6GT	6/6	35Z5GT	7/6
6AM5	5/6	6E18	6/6	6X	5/-	20P3	20/-
6AM6	4/6	6E18	6/6	6X	5/-	20P4	20/-
6AQ5	6/6	6E1	14/-	6X8	11/-	20P5	20/-
6AR5	10/-	6F5	8/-	6Y6G	12/-	25C5	9/-
6AR6	6/6	6F6G	5/-	7Y4	12/-	25L6GT	7/6
6AS7	16/-	6F13	7/6	10C2	10/-	25Z4G	8/6
6AT6	5/-	6F14	12/-	10D1	8/-	30A5	8/6
6AU6	5/-	6F15	11/-	10P1	18/-	30A5E	8/6
						30C1	6/6

30L15	15/-	90CV	25/-	DJ70	6/6	ECF83	15/-
30C17	16/-	807	9/6	DY70	12/-	ECF86	12/6
30C18	15/-	811A	30/-	DY86	6/6	ECF80430/-	
30F5	17/-	812A	65/-	DY87	7/-	ECH42	13/-
30FL1	15/-	813	75/-	DY802	10/-	ECH81	5/9
30FL12	18/6	866A	14/-	E58L	55/-	ECH83	8/6
30FL13	10/6	5042	12/6	E86C	9/-	EM80	8/6
30FL14	15/6	6980	27/6	E130L	8/6	EM84	9/-
30L1	7/-	6146	30/-	E180F	19/-	EM84	7/6
30L15	17/-	6146G	47/6	EABC80	6/6	EM87	11/-
30L17	17/-	6267	6/6	EAF42	10/-	EN91	6/6
30P12	18/-	6380	25/-	EBF33	9/6	ECL84	11/6
30P18	17/-	6938	42/-	EBF39	9/6	ECL85	10/6
30P19	15/-	7189	15/6	EBC81	6/6	ECL86	8/6
30PL1	18/6	7260	36/6	EBC81	6/6	ECL86	8/6
30PL13	18/-	7586	25/6	EBC91	6/6	EF39	8/-
30PL14	17/6	9002	6/6	EBF80	8/6	EF40	10/-
35A3	10/-	9003	10/-	EBF83	8/6	EF41	12/6
35A3	11/-	AZ31	10/-	EBF89	8/6	EF42	14/-
35B3	13/-	AZ30	12/-	EC53	10/6	EF40	9/6
35C5	7/-	CB1	16/6	EC53	10/6	EF83	10/6
35L6GT	9/6	CB13	17/-	EC88	12/-	EF85	7/-
35W4	5/-	DAF41	11/-	EC92	6/6	EF86	6/6
35Z3	11/-	DAF91	5/6	EC93	6/6	EF89	5/6
35Z4G	5/-	DAF92	9/6	EC95	17/-	EF91	4/6
35Z5GT	7/6	DAF96	7/6	EC96	4/6	EF92	7/6
50A5	13/-	DF98	7/6	EC98	4/6	EF94	5/6
50B5	7/-	DK40	10/6	EC82	6/6	EF95	6/6
50C5	7/-	DK91	7/-	EC83	6/6	EF97	10/6
50C6G330/-		DK92	9/-	EC84	6/6	EF98	6/6
50L6GT	8/-	DK96	8/6	EC85	5/6	EF98	6/6
83A1	19/-	DL91	5/6	EC88	8/6	EP90	20/-
85A2	7/6	DL92	7/6	EC89	8/6	EP90	20/-
90A9	48/-	DL93	4/-	ECC91	4/-	EP804	20/-
90AV	48/-	DL94	8/-	ECC91	4/-	EP811	15/-
90C1	12/-	DL95	8/-	ECC98	7/-	EP812	15/6
90CG	25/-	DL96	7/6	ECF82	7/-	EP814	13/6
						EC90	5/-

EL34	10/6	KT66	27/6	PL36	11/-	U801	20/-	
EL36	9/6	KT88	33/-	PL81	9/6	UA8C80	6/9	
EL41	11/-	N78	21/-	PL82	9/6	UAF41	10/-	
EL42	11/6	PABC80	8/-	PL83	8/-	UAF42	10/6	
EL81	10/-	PC86	11/6	PL84	7/6	UB41	11/-	
EL83	8/3	PC88	13/6	PL302	15/-	UB41	8/6	
EL85	5/6	PC97	8/6	PL50	15/-	UBC81	8/6	
EL85	8/6	PC900	9/6	PL504	16/-	UBF80	7/3	
EL86	8/6	PC84	7/6	PL508	17/6	UBF89	7/6	
EL90	6/6	PC85	8/-	PL509	30/-	UBL1	10/-	
EL91	5/6	PC88	12/-	PL801	16/-	UBL21	12/-	
EL95	7/6	PC88	10/6	PL802	14/-	UC99	6/6	
EL96	25/-	PC88	11/6	PM84	9/6	UC85	9/6	
EL98	17/-	PC805	17/-	PM81	5/6	UCF80	10/6	
EL99	17/-	PC806	17/-	PY33	12/6	UCH21	11/-	
EL180	15/-	PC80015/-		PY80	6/6	UCH42	13/-	
EM34	10/-	PC80	6/6	PY81	6/6	UCH43	12/6	
EM71	12/6	PC82	6/6	PY82	6/6	UCH81	6/6	
EM80	8/6	PC84	9/6	PY83	7/6	UCL81	11/-	
EM81	8/6	PC87	7/6	PY88	8/6	UCL82	7/6	
EM84	7/6	PC80015/-		PY200	20/6	UCL83	12/-	
EM87	11/-	PC8010	10/-	PY800	10/6	UF9	11/6	
EN91	6/6	PC802	10/6	PY801	10/6	UF11	10/6	
EY51	8/6	PC805	15/-	PZ30	7/6	UF41	10/6	
EY80	9/6	PC806	13/6	QVQ02-6		UF42	12/6	
EY81	8/6	PC808	15/6	PCF808	15/6	UF82	11/6	
EY83	11/-	PC120014		PC120014		QVQ03-10	UF80	7/6
EY86	8/6	PC181	10/6	PC181	10/6	UF85	8/6	
EY87	8/6	PC182	7/6	PC182	7/6	UF89	7/6	
EY88	8/6	PC183	13/6	PC183	13/6	UL41	12/-	
EZ35	5/6	PC184	8/6	PC184	8/6	UL84	6/6	
EZ40	9/6	PC185	9/6	PC185	9/6	UM84	4/6	
EZ41	9/6	PC186	8/6	PC186	8/6	UM84	4/6	
EZ42	5/6	PC187	17/6	PC187	17/6	UY11	11/6	
EZ43	5/6	PC188	17/6	PC188	17/6	UY11	11/6	
EZ44	5/6	PC189	17/6	PC189	17/6	UY11	11/6	
EZ45	5/6	PC190	17/6	PC190	17/6	UY11	11/6	
EZ46	5/6	PC191	17/6	PC191	17/6	UY11	11/6	
EZ47	5/6	PC192	17/6	PC192	17/6	UY11	11/6	
EZ48	5/6	PC193	17/6	PC193	17/6	UY11	11/6	
EZ49	5/6	PC194	17/6	PC194	17/6	UY11	11/6	
EZ50	5/6	PC195	17/6	PC195	17/6	UY11	11/6	
EZ51	5/6	PC196	17/6	PC196	17/6	UY11	11/6	
EZ52	5/6	PC197	17/6	PC197	17/6	UY11	11/6	
EZ53	5/6	PC198	17/6	PC198	17/6	UY11	11/6	
EZ54	5/6	PC199	17/6	PC199	17/6	UY11	11/6	
EZ55	5/6	PC200	17/6	PC200	17/6	UY11	11/6	
EZ56	5/6	PC201	17/6	PC201	17/6	UY11	11/6	
EZ57	5/6	PC202	17/6	PC202	17/6	UY11	11/6	
EZ58	5/6	PC203	17/6	PC203	17/6	UY11	11/6	
EZ59	5/6	PC204	17/6	PC204	17/6	UY11	11/6	
EZ60	5/6	PC205	17/6	PC205	17/6	UY11	11/6	
EZ61	5/6	PC206	17/6	PC206	17/6	UY11	11/6	
EZ62	5/6	PC207	17/6	PC207	17/6	UY11	11/6	
EZ63	5/6	PC208	17/6	PC208	17/6	UY11	11/6	
EZ64	5/6	PC209	17/6	PC209	17/6	UY11	11/6	
EZ65	5/6	PC210	17/6	PC210	17/6	UY11	11/6	
EZ66	5/6	PC211	17/6	PC211	17/6	UY11	11/6	
EZ67	5/6	PC212	17/6	PC212	17/6	UY11	11/6	
EZ68	5/6	PC213	17/6	PC213	17/6	UY11	11/6	
EZ69	5/6	PC214	17/6	PC214	17/6	UY11	11/6	
EZ70	5/6	PC215	17/6	PC215	17/6	UY11	11/6	
EZ71	5/6	PC216	17/6	PC216	17/6	UY11	11/6	
EZ72	5/6	PC217	17/6	PC217	17/6	UY11	11/6	
EZ73	5/6	PC218	17/6	PC218	17/6	UY11	11/6	
EZ74	5/6	PC219	17/6	PC219	17/6	UY11	11/6	
EZ75	5/6	PC220	17/6	PC220	17/6	UY11	11/6	
EZ76	5/6	PC221	17/6	PC221	17/6	UY11	11/6	
EZ77	5/6	PC222	17/6	PC222	17/6	UY11	11/6	
EZ78	5/6	PC223	17/6	PC223	17/6	UY11	11/6	
EZ79	5/6	PC224	17/6	PC224	17/6	UY11	11/6	
EZ80	5/6	PC225	17/6	PC225	17/6	UY11	11/6	
EZ81	5/6	PC226	17/6	PC226	17/6	UY11	11/6	
EZ82	5/6	PC227	17/6	PC227	17/6	UY11	11/6	
EZ83	5/6	PC228	17/6	PC228	17/6	UY11	11/6	
EZ84	5/6	PC229	17/6	PC229	17/6	UY11	11/6	
EZ85	5/6	PC230	17/6	PC230	17/6	UY11		

# VALUABLE NEW HANDBOOK **FREE** TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

**On 'SATISFACTION or  
REFUND of FEE' terms**

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

**WHICH OF THESE IS  
YOUR PET SUBJECT?**

**RADIO ENGINEERING**  
Advanced Radio — Gen.  
Radio — Radio & TV  
Servicing — TV Eng. —  
Telecommunications— Sound  
Recording — Automation —  
Practical Radio — Radio  
Amateurs' Exam.

**ELECTRICAL ENG.**  
Advanced Electrical Eng. —  
Gen. Electrical Eng. —  
Installations — Draughts-  
manship — Illuminating Eng. —  
Refrigeration — Elem.  
Electrical Science — Electri-  
cal Supply — Mining Elec.  
Engineering.

**CIVIL ENGINEERING**  
Advanced Civil Eng. — Gen.  
Civil Eng. — Municipal  
Eng. — Structural Eng. —  
Sanitary Eng. — Road Eng.  
Hydraulics — Mining —  
Water Supply — Petrol Tech.

**ELECTRONIC ENG.**  
Advanced Electronic Eng. —  
Gen. Electronic Eng. —  
Applied Electronics — Prac.  
Electronics — Radar Tech. —  
Frequency Modulation —  
Transistors.

**MECHANICAL ENG.**  
Advanced Mechanical Eng. —  
Gen. Mechanical Eng. —  
Maintenance Eng. — Diesel  
Eng. — Press Tool Design  
Sheet Metal Work — Welding  
— Eng. Pattern Making —  
Inspection — Draughtsman-  
ship — Metallurgy — Pro-  
duction Eng.

**AUTOMOBILE ENG.**  
Advanced Automobile Eng. —  
Gen. Automobile Eng. —  
Automobile Maintenance —  
Repair — Automobile Diesel  
Maintenance — Automobile  
Elec. Equipment — Garage  
Management.

**"WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS IN-  
CLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRU-  
MENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.**

Which qualification would increase your earning power?  
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B.,  
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,  
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT.  
OF EDUCATION, ETC.

**British Institute of Engineering Technology**  
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

## THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT  
CAREER - GUIDANCE

**PRACTICAL  
EQUIPMENT**

Basic Practical and Theoretic Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

**INCLUDING  
TOOLS**

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.**

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy *now*—FREE and without obligation.



**POST NOW!**

TO B.I.E.T., 453A, ALDERMASTON COURT,  
ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).


NAME .....

ADDRESS .....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**
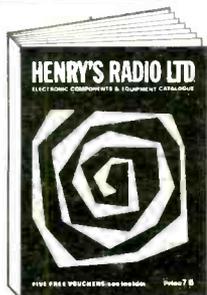
# HENRY'S RADIO LTD. ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES



## NEW CATALOGUE REPRINT

350 PAGES FULLY DETAILED AND ILLUSTRATED. COMPONENTS & EQUIPMENT—AUDIO/HIGH FIDELITY. Complete with 5 x 2/- Discount vouchers for use with picture.

PRICE 7/6 p.p. 2/-

### BUILD A QUALITY 4 TRACK TAPE RECORDER



To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDAKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything for making a superb Tape Recorder. You need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY, AND SUCCESS IS ASSURED. Kit comprises: Deck, Amplifier, Cabinet and speaker, with microphone, 7in. 1200ft tape, and spare spool. TODAY'S VALUE £60. ASK FOR BROCHURE 6. PRICE 39 gns. pp. 22/6. NOTHING ELSE TO BUY.

- #### AMPLIFIERS IN STOCK
- PA7 7 watt £3 12 6
  - MPA12 3 12 watt £4 10 0
  - MPA12 15 12 watt £5 5 0
  - MA7 7 watt Amp £8 10 0
  - Preamp Mono £16 10 0
  - MA66 Stereo Amp £16 10 0
  - Preamp £16 10 0
  - PA25 25 watt £9 10 0
  - PA50 50 watt £9 10 0
  - Leaflets available on request.

#### SINCLAIR STEREO 60


Two Z30, PZ5 and Stereo 60 (usually £23.18.0)

**PRICE £19**

(ADD £2 for PZ6 in place of PZ5).

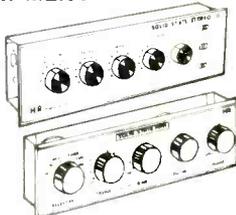
### MONO STEREO UNIT EQUIPMENT

Mono or Stereo Audio equipment developed from Dinsdale Mk. II—each unit or system will compare favourably with other professional equipment selling at much higher prices. COMPLETE SYSTEMS AND MIXERS from £11 12 6 to £38 17 6 (all units available separately). THE FINEST VALUE IN LOW COST HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE YOURSELF POUNDS. 7, 12 and 25 WATT AMPLIFIERS, STEREO AND MONO PREAMPLIFIERS AND MODULES. SEND FOR BROCHURES No. 12/14 21 TODAY!



**HENRY'S STOCK EVERY TYPE OF COMPONENT YOU NEED — A CATALOGUE IS A MUST!**  
ALSO SEE EARLIER PAGES FOR MORE ADS.

## HI-FI equipment to suit EVERY POCKET

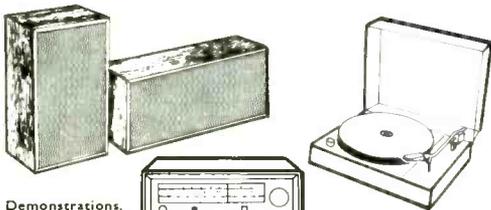

Demonstrations, quotations FREE

\* Credit Terms (CALLERS) For Purchases at ONLY For 309 Branch only From £30\*

VISIT OUR HI-FI CENTRE AT 309 EDGWARE ROAD, for all leading makes of—AMPLIFIERS, TUNERS, DECKS, SPEAKERS, MICROPHONES, TEST EQUIPMENT. ALL WITH DISCOUNTS—IT WILL PAY YOU TO PAY US A VISIT. AUDIO SYSTEMS £40-£300 TO SUIT. SEND FOR STOCK LIST 16/17.


### BUILD THIS VHF FM TUNER

5 MILLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO & STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. PARTS TOTAL COST £6 19 6 DECODER £5 19 6 ASK FOR BROCHURE No. 3 (FOR STEREO)


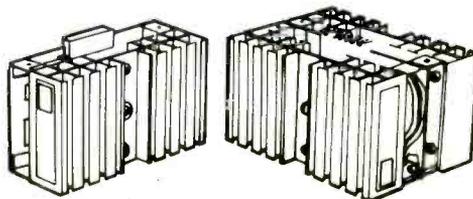
### HENELEC 5-5 STEREO AMPLIFIER

Excellent low priced British designed Stereo Amplifier for use with Record Decks. Tuners. 16 transistor mains operated. Output 5+5 watts for 8—15 ohm speakers. Black, silver and wood finish, size 13in x 3in x 6in. PRICE £13 10 0 pp. 7/6 Complete Stereo System 5-5. Garrard 2025 TC or 3000LM with 9TAHC Diam. Ceramic cartridge. 5-5 Amplifier, Plinth Cover, Two 10 watt speakers with tweeters in polished cabinets. Size 18" x 11" x 7". Usual price £50.0.0. OUR PRICE £39 10 0 pp. 20/- ASK FOR BROCHURE 13



PA25 (25 watts RMS)

PA50 (50 watts RMS)

### SILICON POWER AMPLIFIERS WITH DIRECT COUPLED, SYMMETRICAL OUTPUT

- HENELEC 'PA25' POWER AMPLIFIER  
This silicon design from Henry's Radio uses complementary transistors in the symmetrical output stage direct coupled to a loudspeaker of 8 ohms impedance or higher. Power output is 25 watts RMS with an 8 ohms load or 12 watts for 15 ohms, over a frequency range of 15Hz—25kHz 3dB. Cool running is assured by the use of generously dimensioned black anodised heatsinks. Input 700mV 15K ohm. Price £7 10 0
- HENELEC 'PA50' POWER AMPLIFIER  
Basically similar to the 'PA25' the 'PA50' will deliver 50 watts RMS to a 3-4 ohm load. Extra power is handled by complementary triplet circuits using the latest PNP and NPN silicon power transistors. As a result of extra heatsinking the 'PA50' runs as cool as the 'PA25'. Price £9 10 0
- HENELEC MU442 POWER SUPPLY  
Designed to run one or two 'PA25's' or one 'PA50' the MU442 connects to the amplifiers by means of plug-on harnesses. No soldering is required to connect up the system. Audio input plug and speaker plug go to the panel of the MU442. Price £6 0 0
- SEND FOR FREE BROCHURES No.: 24/25


Transistors, integrated circuits, test equipment, Garrard and Goldring turntables all at special save money prices—See our adverts on earlier pages of this magazine.  
16 Page Testgear Catalogue Ref T/33  
10 Page Record Player Decks List Ref 16/17  
Semiconductor Price List Ref. 36.

**FREE SEND NOW!**
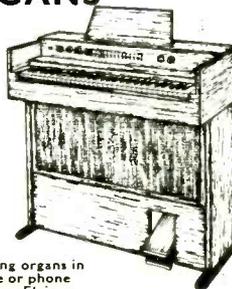
### ELECTRONIC ORGANS

CALL IN and SEE THE NEW MODELS!

- ★ MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT
- ★ TEAK OR WALNUT VENEERED CABINETS FOR ALL MODELS
- ★ 49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE
- ★ KITS AVAILABLE IN SECTIONS AS REQUIRED
- ★ HP and CREDIT SALE FACILITIES



**FREE** 16 page organ brochure covering organs in kit form and ready built—write or phone to ORGAN DEPT. Ask for Peter Elvins.

# HENRY'S RADIO LTD.

Mail Order Dept, Electronic Components and Equipment, and Electronic Organ Dept.  
303 EDGWARE ROAD, LONDON W2.  
Telephone: 01-723 1008/9  
Open Mon-Sat. 9am-6pm, Thurs. 9am-1pm

High Fidelity and Audio Centre  
309 EDGWARE ROAD, LONDON W2.  
Telephone: 01-723 6963  
Open all day Saturday.