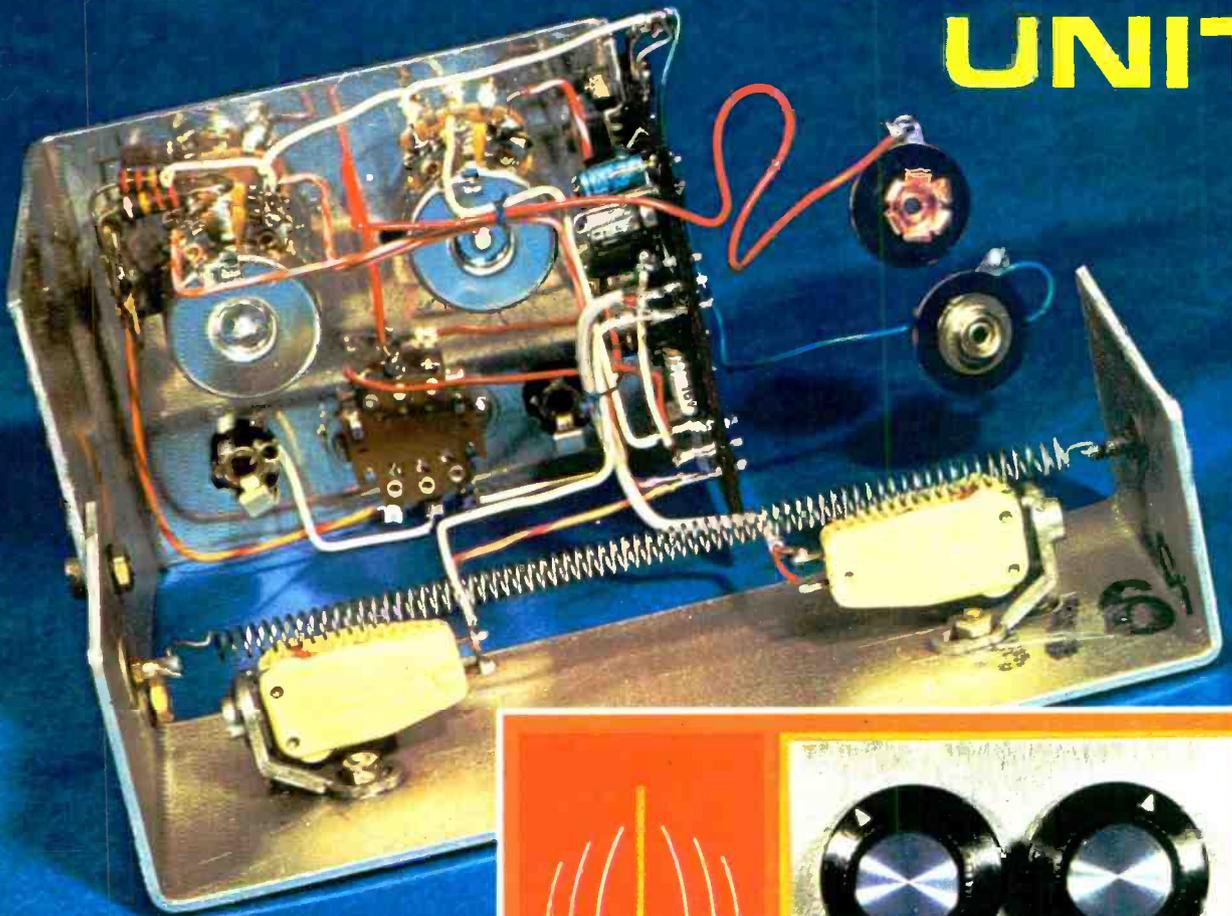


PRACTICAL WIRELESS

JULY
1970

3/6

REVERBERATION UNIT



also:-

LIGHT OPERATED SWITCH
NOVEL SIGNAL INJECTOR

ADCOLA Soldering Instruments add to your efficiency

ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{3}{16}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{3}{16}$ " — 4.75 mm EYELET BIT

B 58 $\frac{3}{16}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{3}{16}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{3}{16}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



* Write for price list and catalogue

ADCOLA PRODUCTS LTD.,
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

SEMICONDUCTORS

BRAND NEW AND FULLY GUARANTEED

1N914	1/8	2N2906	6/-	ACV28	4/-	BD123	21/6	MJ490	22/6
1N916	1/8	2N2906A	6/6	AD140	8/-	BD124	12/-	MJ491	28/6
18021	4/-	2N2923	3/6	AD149	11/6	BF115	5/-	MPF102	7/6
18025	1/-	2N2924	3/6	AD161	7/6	BF117	10/6	MPF103	7/6
18113	2/-	2N2925	3/6	AD162	7/6	BF167	5/6	MPF104	7/6
18120	2/-	2N2926	3/6	AF114	5/-	BF173	7/6	MPF105	7/6
18121	2/-	Green	3/-	AF116	5/-	BF180	7/6	NKT0013	8/6
18130	2/6	Yellow	2/9	AF117	5/-	BF181	7/6	NKT216	7/6
18131	2/6	Orange	2/9	AF118	12/6	BF184	7/6	NKT217	8/6
18132	2/6	2N3011	12/6	AF124	4/6	BF194	5/-	NKT261	4/-
1844	2/-	2N3053	5/6	AF125	4/6	BFX12	4/6	NKT282	4/-
2G301	4/-	2N3054	12/6	AF126	4/-	BFX13	4/6	NKT264	4/-
2G302	4/-	2N3055	15/-	AF127	3/6	BFX29	12/6	NKT271	4/-
2G303	4/-	2N3702	3/6	AF139	7/6	BFX30	9/-	NKT272	4/-
2G371	3/-	2N3703	4/6	AF181	8/6	BFX35	19/6	NKT273	4/-
2N696	4/-	2N3704	4/6	AF186	11/-	BFX43	8/6	NKT275	4/-
2N697	5/-	2N3705	4/-	AF239	7/6	BFX44	8/6	NKT281	5/6
2N698	4/6	2N3706	4/6	ASV26	5/6	BFX44	7/6	NKT403	15/6
2N706	2/6	2N3707	4/-	ASV27	8/6	BFX45	9/-	NKT404	12/6
2N706A	2/6	2N3708	3/6	ASV28	5/6	BFX46	8/6	NKT405	15/6
2N708	4/-	2N3709	3/6	ASV29	5/6	BFX47	6/6	NKT406	15/6
2N929	5/6	2N3710	4/-	ASZ20	7/6	BFX48	5/-	NKT674	5/-
2N930	7/-	2N3711	4/-	ASZ21	7/6	BFY10	4/6	NKT677	5/-
2N1090	6/6	2N3819	9/-	BA102	6/6	BFY17	4/6	NKT713	5/-
2N1091	6/6	2N3820	23/6	BAX13	1/6	BFY18	4/6	NKT773	5/-
2N1131	5/6	2N3820	7/6	BAX16	1/9	BFY19	4/6	NKT781	6/6
2N1132	6/6	2N4058	5/6	BAY31	12/6	BFY20	12/6	NKT8029	8/6
2N1302	3/6	2N4059	5/-	RAY38	3/6	BFY41	10/-	NKT80115/6	6/6
2N1303	3/6	2N4060	5/-	BC107	3/6	BFY43	12/6	NKT801219/6	6/6
2N1304	4/6	2N4061	4/6	BC108	3/6	BFY50	4/6	NKT801322/6	6/6
2N1305	4/6	2N4062	4/6	BC109	3/6	BFY51	4/6	OA5	2/6
2N1306	2/6	2N4254	6/6	BC113	6/6	BFY52	4/6	OA9	2/6
2N1307	5/-	2N4255	8/6	BC116	12/6	BFY76	6/6	OA70	1/6
2N1308	6/-	2N4284	3/6	BC118	6/6	BFY77	11/6	OA73	2/6
2N1309	6/-	2N4285	3/6	BC125	11/-	BFY90	12/6	OA79	1/6
2N1507	5/6	2N4286	3/6	BC126	11/-	B8X19	3/6	OA81	1/6
2N1513	5/-	2N4287	3/6	BC147	3/6	B8X20	3/6	OA85	1/6
2N 711	6/6	2N4288	3/6	BC148	3/6	B8X21	7/6	OA90	1/6
2N1589	6/6	2N4289	3/6	BC149	3/6	B8X22	10/6	OA91	1/6
2N1893	8/6	2N4291	3/6	BC167	3/6	B8X27	10/6	OA95	1/6
2N2102	15/-	2N4292	3/6	BC168B	3/6	B8X28	6/-	OA200	2/-
2N2147	14/6	40361	12/6	BC168C	3/6	B8Y29	13/6	OA202	2/-
2N2148	14/6	40362	14/6	BC169B	3/6	B8Y26	4/-	OC26	10/6
2N2160	12/6	3N128	13/6	BC169C	3/6	B8Y27	4/-	OC28	10/6
2N2193	5/6	3N140	19/6	BC182L	4/6	B8Y28	4/6	OC29	15/-
2N2193A	5/6	3N141	21/6	BC212L	5/-	B8Y29	4/6	OC35	6/6
2N2194A	5/6	3N142	16/6	BCY30	5/6	B8Y38	4/6	OC36	6/6
2N2217	5/6	AZ13	2/-	BCY31	5/6	B8Y39	4/6	OC44	4/6
2N2218	6/6	AZ15	2/6	BCY32	7/6	B8Y40	6/6	OC45	2/6
2N2219	6/6	AZ17	2/6	BCY33	4/-	BSY51	8/6	OC71	2/6
2N2220	5/-	AC107	6/-	BCY34	4/6	BSY52	9/-	OC72	2/6
2N2221	5/-	AC126	4/6	BCY38	4/6	BSY53	8/6	OC75	4/6
2N2222	6/6	AC127	5/-	BCY39	7/6	BSY54	10/6	OC81	4/6
2N2368	5/-	AC128	4/6	BCY40	6/6	BSY95A	2/6	OC83	4/6
2N2369	5/-	AC176	5/-	BCY42	3/-	BY100	4/6	OC811	4/6
2N2369A	5/6	AC187	12/6	BCY43	5/6	BY116	5/6	OC84	5/6
2N2539	4/6	AC188	12/6	BCY54	7/6	BVZ10	9/-	OC139	6/6
2N2540	4/6	ACV17	5/-	BCY70	4/6	BVZ11	7/6	OC140	6/6
2N2646	11/6	ACV18	5/-	BCY71	8/6	BVZ12	6/-	OC200	6/6
2N2904	8/-	ACV19	5/-	BCY72	4/-	BVZ13	5/-	OC201	7/6
2N2904A	8/-	ACV20	8/-	BDY20	25/6	MJ480	20/6	OC202	10/6
2N2905	8/-	ACV21	5/-	BDJ21	17/6	MJ481	27/6	OCPT1	12/6
2N2905A	9/-	ACV22	4/-						

PLESSEY INTEGRATED CIRCUITS

SL402A	42/6
SL403A	49/6
Data Sheets	2/-

MULLARD INTEGRATED CIRCUITS

TAA241 Operational Amplifier	47/6
TAA243 Operational Amplifier	47/6
TAA 263 Linear A.F. Amplifier	15/6
TAA 300 Linear A.F. Amp	47/6
TAA 320 Most LF Pre-amplifier	15/6
TAA 350 Wide-band Lim	45/-
Diff. Amp	45/-
Data Sheets 1/-	

SPEAKERS (3 ohm)

10in. x 6in. 37/6	4	15	1/6	40	6	4	1/6	400	16	2/6
9in. x 4in. 23/6	4	40	9/6	40	16	1/6	500	6	2/6	
8in. x 5in. 19/6	4	350	2/3	50	12	1/6	500	25	3/6	
7in. x 4in. 15/6	5	15	1/6	50	25	1/6	500	50	4/6	
5in. x 3in. 12/6	6	4	1/6	1/9	50	50	2/-	640	16	3/6
3in. 9/6, 5in. 14/6	8	18	1/6	80	16	1/6	1000	25	5/-	
5in. 27/8, 12in. 39/6	8	450	3/-	100	6	4	1/6	1000	50	8/6
Post and Packing 2/9	10	15	1/6	100	12	1/6	2000	25	8/6	
	12	5	25	1/9	100	25	2/-	2000	50	12/6
	16	18	1/6	100	50	2/6	2500	25	9/6	
	25	6	4	1/8	125	4	1/6	5000	25	12/6
	25	10	1/6	200	6	4	1/9	5000	50	19/6

THERMISTORS

R53 (STC)	25/6
K151 (1K)	2/6
Various Mullard Thermistors in stock.	

Send 2/6 for new comprehensive catalogue. P.P. for Components 1/6 per order.

THYRISTORS

1 AMP: 50V 5/-, 100V 5/6, 200V 7/-, 400V 9/6.
3 AMP: 50V 6/-, 100V 7/6, 200V 8/-, 400V 10/6.
ZENERS: 1 1/2 WATT 2.7-33V 4/-, 1 WATT 3.9-100V 7/6, 400mW 3.0-33V 4/-, 1 WATT 2.4V-200V 7/6.

INTEGRATED CIRCUITS—R.C.A.

CA3005 30/-, CA3011 20/-, CA3012 25/-, CA3013 30/-, CA3014 30/-, CA3018 25/-, CA3019 25/-, CA3020 27/6, CA3021 42/6, CA3022 35/-, CA3023 32/6, CA3026 27/6, CA3028 42/6, CA3029 B 35/-, CA3029B 35/-, CA3036 20/-, CA300 84/-, CA3046 25/-, CA3048 32/6, CA3051 25/-, FAIRCHILD) L900, 914 11/-, L923 14/-, L701C 17/6, L702C 45/-, L709C 27/6.

G.E. INTEGRATED CIRCUITS

PA250 27/6, PA234 28/6, PA237 45/-, PA246 57/6. Data Sheet 1/-.

Presets std., horiz. or vert.

Potentiometers, Log/Lin 3/8 each
Twin-ganged Pots Log and Lin. 7/6

MFD	V	Price	MFD	V	Price	MFD	V	Price	
1	40	1/6	25	25	1/6	200	16	2/6	
2	15	1/6	25	50	1/6	250	25	2/6	
2	350	2/-	32	15	1/6	250	50	3/6	
2	5	1/6	32	450	5/6	320	10	1/6	
4	15	1/6	40	6	4	1/6	400	16	2/6
4	40	9/6	40	16	1/6	500	6	2/6	
4	350	2/3	50	12	1/6	500	25	3/6	
5	15	1/6	50	25	1/6	500	50	4/6	
6	4	1/6	50	50	2/-	640	16	3/6	
8	18	1/6	64	25	1/6	1000	16	4/6	
8	40	1/6	80	16	1/6	1000	25	5/-	
8	450	3/-	100	6	4	1/6	1000	50	8/6
10	15	1/6	100	12	1/6	2000	25	8/6	
12	5	25	1/9	100	25	2/-	2000	50	12/6
16	18	1/6	100	50	2/6	2500	25	9/6	
25	6	4	1/8	125	4	1/6	5000	25	12/6
25	10	1/6	200	6	4	1/9	5000	50	19/6

VERBOARD

2 1/2in. x 3 1/2in.	3/6	4/-
3 1/2in. x 5in.	4/3	4/6
3 1/2in. x 3 1/2in.	4/3	4/6
3 1/2in. x 5in.	5/6	5/6
2 1/2in. x 17in.	12/6	21/6
3 1/2in. x 17in.	16/-	
Cutter 9/-		

RESISTORS

2 watt 5%, 4d.	
1 watt 5%, 6d.	
1/2 watt 5%, 1/6	
5 watt 5%, 2/6	
10 watt 5%, 2/6	

A. MARSHALL & SON

28 CRICKLEWOOD BROADWAY, LONDON N.W.2
TELEX 21492 01-452 0161/2/3 CALLERS WELCOME
Post & Packing U.K. only 1/6. Europe 5/-. Commonwealth (Air) 13/-

Laskys

SCOOP Garrard 3000

CUSTOM UNIT BY FAMOUS BRITISH MANUFACTURER

A deluxe custom styled and built record player unit made by world famous British manufacturer. The unit incorporates the renowned Garrard 3000 four speed autochanger with lightweight tubular pick-up arm **FITTED WITH SONOTONE 9TA STEREO CARTRIDGE with diamond stylus.** The beautifully made plinth is finished in richly figured teak veneer with tinted perspex panels in the lid and with attractive charcoal grey "mirror" insert panel on front. All metal trim parts are satin chrome. Blackleather grain underside. The lid allows the player to operate fully automatically when closed and has snap action "stay" when raised. Mains socket and 5 pin DIN audio output socket are at rear. Overall size 15 1/2" x 7 1/2" x 14 in.




LASKY'S SPECIAL PRICE £16.15.0 Post 15/-

SONICS AS-57

ELEGANT BUDGET PRICED BOOKSHELF SPEAKER SYSTEMS

The AS-57 is a real space saver. This fine bookshelf high-fidelity speaker system will provide good quality sound anywhere in your home at remarkably low cost. Designed for use where space is at a premium, the AS-57 system is ideal for the small apartment or isolated area. The special high efficiency 5 x 7 in. full range speaker has a frequency range of 70-18,000 Hz with a peak handling capacity of 10 watts, Imp. 8 ohms. Finish: oiled walnut. Size: 5 1/2" x 15 1/2" x 8 1/2 in.

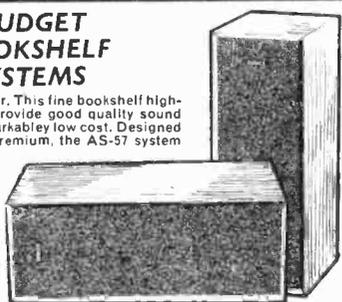


LASKY'S PRICE £15 per PAIR Post 10/-

Garrard



SP.25 Mk II

THE U.K.'s MOST POPULAR HI-FI TURNTABLE

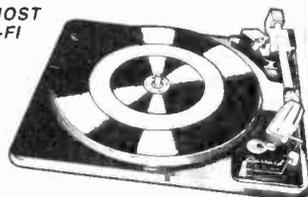

4-speed single record playing deck features include heavy precision-built turntable, pick-up arm bias compensation, calibrated stylus-force adjustment, cueing device. After play, the arm automatically rises, returns to rest and switches off motor. Finish, dark green polychromatic and silver.

LASKY'S PRICE £11.19.6

SP.25 Mk.11 with A.D.76K Stereo Magnetic Cartridge £15.10.0

OTHER GARRARD UNITS FROM STOCK

AUTOCHANGERS

SL72B	£25 0 0	SL65B	£15 19 6
2025TC with stereo cartridge	£8 17 6	1025 with stereo cartridge	£6 19 6
3000 complete with 9TAHC stereo cartridge	£9 19 6	SL95B	£40 0 0
		SL75B	£32 0 0

SINGLE PLAYERS

AP 75, £18.10.0 AP 75 with AD76K mag. cart., £21.10.0. 401 Transcription Unit, £28.0.0

BASES AND COVERS FOR GARRARD UNITS

Type WB1 and WB5 for models 2025TC, 3000, SL65B 1025, SP25 Mk II Price WB1 £3.16.6, WB5 £5.12.6. Type WB4 for models SL72B, SL75B, SL95B Price £5.12.6. Perspex covers: SPC1 for WB1, £3.14.1. SPC4 for WB4 and WB5 (allows unit to be played with the cover in place)—price £4.8.0.

PACKAGE DEALS

AP75 complete with AD76K Stereo magnetic cartridge, teak plinth and perspex cover	£30.0.0	Post 10/-
SP25 Mk II complete with AD76K cartridge, teak plinth and perspex cover	£19.0.0	Post 7/6
1025 complete with J2185 stereo ceramic cart., teak plinth and perspex cover	£11.19.6	Post 7/6

Post on Garrard units 6/- extra—except AP75, SL75B, SL95B and 401 7/6 extra. Post on bases and covers 5/- extra.

SPECIAL OFFER—BSR-UA-15


4 speed autochangers with modified tubular tone arm. Comp. with stereo cart. £6.19.6. Post 5/-.

FANTAVOX

TPC-2

SOLID STATE COMPACT CASSETTE RECORDER

A Lasky's STAR BARGAIN this beautifully made compact cassette recorder and play back machine offers tremendous performance and value. **BRIEF SPEC:** 6 transistor and 1 thermister circuit. Constant speed capstan drive system. A.C. bias recording. PM magnet erase. 2 1/2 in PM Dynamic speaker. Economical operation on 4 x 1.5V (U-2 type) batteries. **SPECIAL FEATURES:** Absolutely foolproof operation. Piano key controls. Powerful volume with recessed control. Handsome impact resistant cabinet finished in black with satin aluminium and ivory trim. Size 5 1/2" x 5 1/2" x 2 1/2". Jack sockets for remote control microphone, earpiece and external 6V battery pack (or A.C. adaptor). **COMPLETE WITH** Remote control Dynamic microphone, earpiece removable carrying strap, batteries, full instructions and three C-60 cassettes

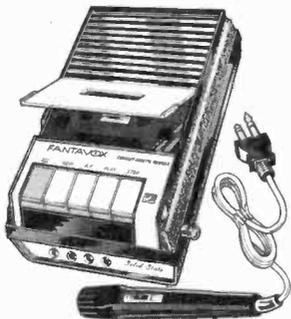

LASKY'S PRICE £17.10.0 Post 5/-

USA MADE CASSETTES

AT LASKY'S BUDGET PRICES

C60 7/6 each post 1/-	35/- post 2/-	65/- post 3/-
C90 12/6 each post 1/-	57/6 post 2/-	115/- post 3/-
C120 17/6 each post 1/-	85/- post 2/-	165/- post 3/-

5 for 10 for

The 1970 edition of Lasky's famous Audio-Tronics catalogue is available FREE on request. The 28 tabloid pages many in full colour are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics Hobbyist, Servicemen and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories plus Lasky's amazing money saving vouchers worth over £25.

SEND TODAY. Send: Your name, address and 2/- for the post and inclusion of your name on our regular mailing list.

THIS MONTH'S VOUCHERS WORTH 50/-

Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271
 33 TOTTENHAM CT. RD, LONDON, W1P 9RB. Tel: 01-636 2605
 Open all day, 9 a.m. - 6 p.m. Monday to Saturday
 129 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812
 152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833
 Open all day Thursday, early closing 1 p.m. Saturday

HIGH FIDELITY AUDIO CENTRES
 42-45 TOTTENHAM CT. RD, LONDON, W1P 9RD. Tel: 01-580 2573
 Open all day, 9 a.m. - 6 p.m. Monday to Saturday
 118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789
 Open all day Saturday early closing 1 p.m. Thursday



ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

R + TV

RADIO & TV COMPONENTS (Acton) Ltd.

21c High Street, Acton, London W.3.

Also at 323 Edgware Road, London, W.2.


ALL ORDERS BY POST TO OUR ACTON BRANCH

Terms C.W.O.

All enquiries S.A.E.

Complete Stereo System £41

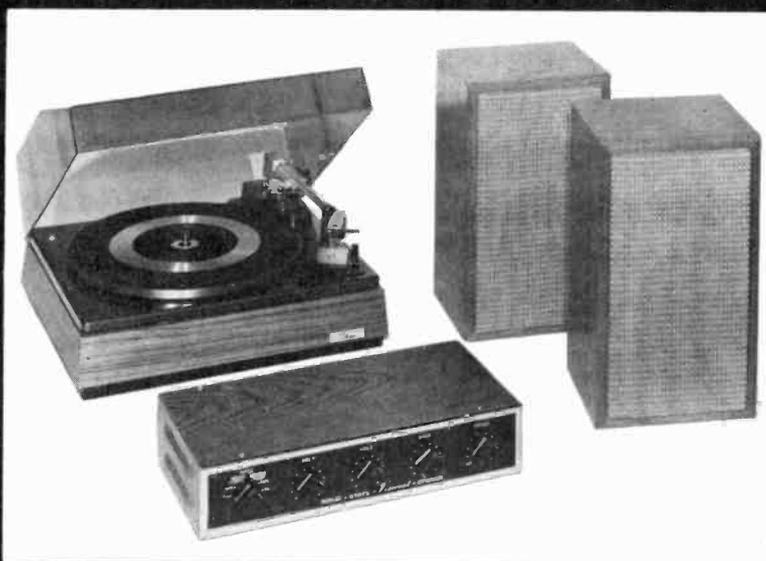WITH
F.E.T.
FIELD EFFECT TRANSISTORS
AMPLIFIER



This superb stereo system is a real price break through. It comprises the VISCOUNT F.E.T. amplifier on which full details are given below, the famous Garrard SP 25 Mk II (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers. Measuring 17½ in x 10½ in x 6½ in, the Duo type 2 speakers are beautifully finished in teak veneer with matching vynair grills. They incorporate a 10½ in x 6½ in drive unit and high frequency speaker, both of which are of 3 ohms impedance. The Duo speaker system is also available separately at £6.6.0 each, plus 15/- p. & p.

Complete stereo system £41 plus £2.10. p. & p.



MkII (MAG P.U.) £15.15 plus 10/- p. & p.

Specification same as Mk I, but with the following inputs. Mag. P.U. CER. P.U. Tuner. Spec. on Mag. P.U. 3mV at 1kHz input impedance 47K. Fully equalised to within ±1db RIAA. Signal to noise ratio—65db (vol. max)


The Viscount F.E.T. Mk I £14.5 plus 7/6 p. & p.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

Specification—Output per channel 10 watts r.m.s. Frequency bandwidth 20 Hz to 20 kHz + 1db at 1 watt. Total distortion at 1 kHz at 9 watts 0.5% Input sensitivities CER. P.U. 100mV into 3 meg ohms. Tuner 100mV into 100K ohms. Tape 100mV into 100K ohms. Overload Factor Better than 26db.

Signal to noise ratio—70db on all inputs (with vol. max). Controls—6 position selector switch (3 pos. stereo and 3 pos. mono). Separate volume controls for left and right channels. Bass + 14db at 60 Hz. Treble (with D.P.S. on/off) + 12db at 10 KHz.

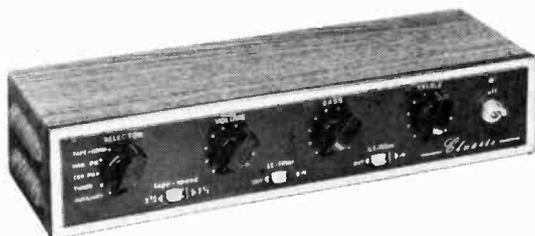Tape recording output sockets on each channel. Size 12½ in x 6 in x 2½ in. in teak-finished case. BUILT & TESTED.



The Classic £9.10. plus 7/6 p. & p.

Controls: Selector switch Tape speed equalisation switch (3½ and 7½ i.p.s.). Volume. Treble. Bass. 2 position scratch filter and 2 position rumble filter.

Specification: Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape head: 3mV (at 3½ i.p.s.). Mag. P.U.: 2mV. Cer. P.U.: 80mV. Tuner 100mV. Aux.: 100mV Tape/Rec. output: Equalisation for each input is correct to within ± 2dB (R.I.A.A.) from 20Hz to 20KHz. Tone control range: Bass ± 13dB at 60Hz. Treble ± 14dB at 15KHz. Total distortion: (for 10 watt output) < 1.5%. Signal noise: < -60dB. A.C. mains 200-250v. Built and tested. Size 12½ in long, 4½ in deep, 2½ in high. Teak finished case.



Duetto

Integrated Transistor Stereo Amplifier **£9.10** plus 7/6 p. & p.

The Duetto is a good quality amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

SPECIFICATION:—

R.M.S. power output: 3 watts per channel into 10 ohms speakers.

INPUT SENSITIVITY: Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 80dB at 1Kc/s.

CONTROLS: 4-position selector switch (2 pos. mono and 2 pos. stereo) dual ganged volume control.

TONE CONTROL: Treble lift and cut. Separate on/off switch. A preset balance control.


THE DUO SPEAKER SYSTEM

Similar in design to those on the previous page the 2-way speaker system is beautifully finished in polished teak veneer, with matching vynair grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION:—

Impedance 3, 8 or 10 ohms (please state requirement). It incorporates Goodmans high flux 6in x 4in speaker and 2½in speaker. Teak finish 12in x 6½in x 5½in. 4 guineas each. 7/6 p. & p.

THE RELIANT

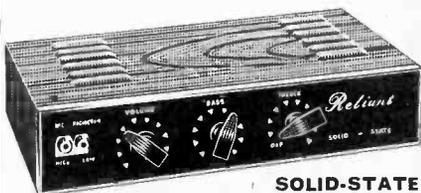

SOLID-STATE GENERAL PURPOSE AMPLIFIER

SPECIFICATIONS

Output—10 watts. Output impedance—3 to 4 ohms. Inputs—1. xtal mic 10mV Tone Controls—Treble control range ±12dB at 10KHz.

2. gram/radio 250mV. Base control range ±13dB at 100Hz. Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10½in x 4½in x 2½in. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from gram. and mike. Built and tested.


RELIANT Mk. I

As above less teak case
£6.10 plus 7/6 P. & P.

RELIANT Mk. II

In teak finished case
£7.5 plus 7/6 P. & P.

50 WATT AMPLIFIER

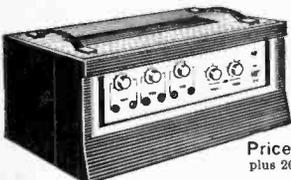

A.C. Mains 200-250V

Price **£28.10** plus 20/- p. & p.

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

TECHNICAL SPECIFICATIONS

3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. SENSITIVITIES AND INPUT IMPEDANCES. Channels 1 and 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars. Channels 3 and 4 300mV at 1m. Suitable for most high output instruments (gram, tuner, organ, etc). Input

sensitivity relative to 10w output. TONE CONTROLS ARE COMMON TO ALL INPUTS. Bass Boost +12dB at 60Hz. Bass Cut—13dB at 60Hz. Treble Boost +11dB at 15 KHz. Treble Cut—12dB at 15 KHz. With bass and treble controls central—3dB points are 30 Hz and 20 KHz. POWER OUTPUT: For speech and music 50 watts rms. 100 watts peak. For sustained music 45 80 watts peak. Total distortion at rated output 3.2% at 1KHz. Total distortion at 20 watts 0.15% at 1KHz. Output to match into 8 or 15 ohms speaker system. NEGATIVE FEEDBACK 20dB at 1KHz. SIGNAL TO NOISE RATIO 60dB. MAINS VOLTAGES adjustable from 200-250V A.C. 50-60Hz. A protective fuse is located at the rear of the unit. Output-impedance 3, 8 and 15 ohms.



The ELEGANT SEVEN Mk. III (350mW Output)

7 transistor fully-tunable M.W.—L.W. superb portable Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 9/6 extra.

Price **£5.5.0** plus 7/6 P. & P.

Circuit 2/6 FREE WITH PARTS



The DORSET (600mW Output) Price £5.5.0 plus 7/6 P. & P.

Circuit 2/6 FREE WITH PARTS

7-transistor fully tunable M.W.—L.W. superb portable—with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in.

MAINS POWER PACK KIT: 8/6 extra

QUALITY MAINS TRANSFORMER

Input 250 volts. OUTPUT (All RMS values) 4 windings of 11.5 volts connected in series total 46 volts at 4.5 amps (conservatively rated). The following combinations may be used. 1. 2. 3. 999. 1000.


Both of these above voltages are commonly used in medium to high powered transistor amplifiers, power supplies, etc.

Price **35/-** plus 7/6 P. & P.

LIQUIDATED STOCK

DANSETTE

TOURISTE MK3 CAR RADIO

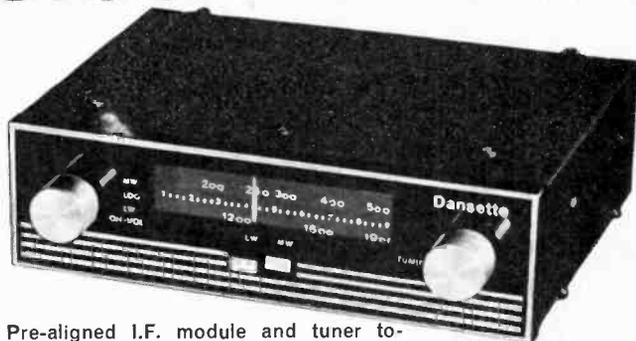

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensures excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts.

Originally sold complete for £15.4.6.


SET OF PARTS **£6.6.0** plus 7/6 P. & P.

Speaker, baffle and fixing kit 25/- extra plus 4/- P. & P.

See top of previous page for address

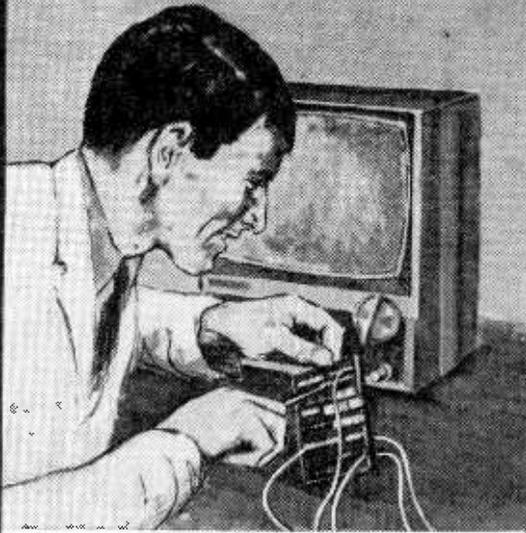Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.





Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics.

The next full-time 2 year College Diploma Course which gives a thorough fundamental training for radio and television engineers starts on 2nd September, 1970.

The course includes theoretical and practical instruction on Colour Television receivers and is designed to cover the syllabus of the new City and Guilds Radio, Television and Electronics Technicians' Course. Pembridge College diplomas are awarded to successful students.

The way to get ahead in this fast growing industry—an industry that gives you many far-reaching opportunities—is to enrol now. Minimum entrance requirements 'O' Level, Senior Cambridge or equivalent in Mathematics and English.

**To: The Pembridge College of Electronics
(Dept. PW14), 34a Hereford Road, London,
W.2**

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.


NAME.....

ADDRESS.....

newbury

SOUND EQUIPMENT

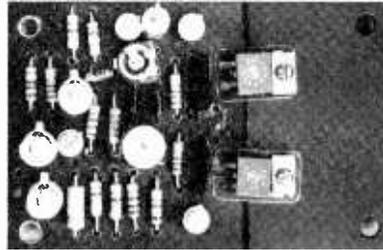PRESENT THE LATEST MODULE
THE **6T2 — 20 WATTS (RMS)**
AMPLIFIER WITH INTEGRAL PRE-AMP.



This amazing unit measures only 3 1/4" x 2 1/4" yet will deliver up to 25 Watts speech and music from a circuit using the latest R.C.A. plastic output transistors

- CONTINUOUS POWER 20 WATTS INTO 4 OHMS
16 WATTS INTO 8 OHMS
- 10-30,000 Ht @ 10 WATTS ± 1dB
- LESS THAN 0.25% DISTORTION @ 100mW & 15W
- POWER GAIN 80dB INPUT 40mV into 10 Kiloohms

ABSOLUTE SATISFACTION GUARANTEED

86/- + 2/6 p. & p. 35VOLT SUPPLY FOR TWO 6T2
MODULES 86/- + 4/6 p. & p.

**ALSO !! FIVE ENCAPSULATED CIRCUITS
AT LESS THAN £1 EACH !**

BRAND NEW FULLY GUARANTEED AND TESTED MODULES

POWER AMPLIFIER MODULE 19/6 500mW maximum output, 200mW for less than 5% distortion. Power gain 50dB. Input 40mV into 400 ohms. 3-15 ohms load. Frequency response 35-45,000Hz ± 2dB.

Type 3TI
Ideal for intercoms, baby alarms, record-players, etc. 9-12V operation.

ORGAN MODULE 17/6
Type 3TN
Will make the ideal basis for either monophonic or polyphonic organs. Can be used as a divider, locking in to the correct frequency. Will drive a loudspeaker or can be fed into tone circuits, amplifiers, etc.

Frequency range 30-6000Hz.
Power into 80 ohms loudspeaker 100mW, 9V operation.

MULTI-PURPOSE PRE-AMPLIFIER 19/6
Type 3TO
For use with the 3TI, or as an impedance matcher, high gain pre amp, headphone amplifier, etc. It may be used as an oscillator or high fidelity preamplifier using the requisite feedback loops.

Input impedance and gain fully variable up to 500 kiloohms and 40dB. Output impedance 300 ohms. Will deliver 30mW into 15 ohms. Frequency response 20-35,000Hz ± 2dB. Supply voltage 6-24V. Noise level—60dB.

DUAL-VOLTAGE PRE-AMPLIFIER 17/6
Type ITO
For increasing the input sensitivity of low gain valve or transistor amplifiers. A high smoothing factor makes operation direct from H.T. lines possible.

Gain 20-26dB. Input impedance 50 kiloohms. Frequency response 30-45,000Hz ± 2dB. Supply voltages 9-24 and 200-500.

TACHOMETER MODULE 18/9

Type 2TN
For 4 or 6 cylinder, 6 or 12V positive or negative earth vehicles. Will operate 200 microamp to 1mA meters on 12V and 200-500 microamp meters on 6V. Suitable meters from 57/6. This module will provide linear readings up to 10,000 r.p.m. if your car can provide the signal!

Please send S.A.E. with enquiries. We welcome your problems!!
All orders to:—
NEWBURY SOUND EQUIPMENT,
21 Lancaster Court,
Lancaster Ave., London, S.E.27
Cash with order plus 1/- p. & p.
Please cross all cheques and P.O.s.
Quantity discounts. Trade enquiries welcomed.
Callers by appointment.

COMET

Hi-Fi DISCOUNT WAREHOUSES

- All items offered are brand new, latest models in manufacturers' sealed cartons. Fully guaranteed with after-sales service.
- Complete Free price list of over 800 items on request.



Customers Welcome
Open Daily to the public from 9 a.m. Closed Tuesday 1 p.m.
Mon. & Sat. 5-30 p.m. Open until 8 p.m. Wednesday, Thursday & Friday.

	Rec. Price	Retail Price	Comet Price
STEREO AMPLIFIERS			
ARENA 210 Amplifier	£34	£13 0	£28 0 0
ARMSTRONG 521	£52	0 0	£42 19 6
DULCI 207	£25	0 0	£17 0 0
DULCI 207M	£30	0 0	£20 19 6
GOODMANS Maxamp	£54	0 0	£44 19 6
LEAK Stereo 30 Plus	£53	0 0	£43 19 6
LEAK Stereo 30 Plus in teak case	£59	10 0	£47 19 6
LEAK Stereo 70	£65	0 0	£53 19 6
LEAK Stereo 70 in teak case	£71	10 0	£57 19 6
LINEAR LT.66	£18	0 0	£15 19 6
PHILIPS RH 591	£17	0 0	£15 19 6
PHILIPS RH 590	£49	0 0	£37 12 6
PHILIPS RH 580	£26	0 0	£19 19 6
QUAD 33 Pre-Amplifier	£43	0 0	£38 19 6
QUAD 303 Micro Amplifier	£57	3 0	£48 19 6
ROGERS Ravensbourne	£59	10 0	£48 19 6
ROGERS Ravensbourne (cased)	£64	0 0	£52 13 6
ROGERS Ravensbrook	£44	0 0	£38 19 6
ROGERS Ravensbrook (cased)	£49	0 0	£36 19 6
SINCLAIR 2000	£30	9 0	£24 19 6
TELETON 203E	£28	7 6	£21 15 6
TRUVOX TSA, 200	£54	12 0	£35 19 6

	Rec. Price	Retail Price	Comet Price
TUNERS			
ARENA F211 with decoder	£39	10 0	£33 19 6
ARMSTRONG 523 AM/FM	£52	9 0	£44 19 6
ARMSTRONG 524 FM	£40	4 0	£34 19 6
ARMSTRONG M8 decoder	£9	10 0	£7 19 6
DULCI FMT.72M	£22	1 0	£17 19 6
DULCI FMT.75 Stereo	£31	0 0	£25 5 0
GOODMANS Stereomax	£82	10 5	£71 19 6
LEAK Troughline with MPX	£51	10 6	£39 19 6
LEAK Stereofelic Chassis	£59	18 0	£51 19 6
LEAK Stereofelic in teak case	£67	3 0	£57 10 0
PHILIPS RH 690	£39	0 0	£33 2 6
QUAD Stereo FM	£51	0 0	£39 19 6
ROGERS Ravensbourne Tuner with Decoder	£61	17 9	£52 12 6
ROGERS Ravensbrook	£45	0 2	£39 19 6
ROGERS Ravensbrook (cased)	£51	5 3	£42 19 6
SINCLAIR 2000	£26	14 6	£19 4 6
TRUVOX FM 2001C with decoder	£60	11 10	£39 19 6

	Rec. Price	Retail Price	Comet Price
TUNER/AMPLIFIERS			
ARENA 2400 with MPX	£90	6 0	£71 19 6
ARENA 2600 Stereo AM/FM with MPX	£111	6 0	£94 0 0
ARENA 2700 Stereo with MPX	£105	0 0	£85 0 0
ARENA T1500F with MPX	£72	9 0	£59 19 6
ARENA T9000 with MPX	£303	9 0	£258 0 0
ARMSTRONG 525	£97	18 9	£86 19 6
ARMSTRONG 526	£98	15 6	£79 19 6
ARMSTRONG 127 (Teak Case for 127)	£43	19 9	£37 19 6
GOODMANS 3000	£37	17 0	£30 10 0
PHILIPS RH781	£74	19 6	£63 14 6
PHILIPS RH790	£125	0 0	£106 4 6
PHILIPS RH691	£83	0 0	£70 10 6
TANDBERG SoluSuper	£75	18 0	£55 19 6
TELETON F.2000 with MPX	£51	0 0	£37 19 6
TELETON 7A.T1 with MPX	£133	0 0	£85 0 0
TELETON R4200 with MPX	£51	15 0	£42 19 6
TELETON CR/107 with MPX	£39	0 0	£29 19 6

	Rec. Price	Retail Price	Comet Price
CARTRIDGES			
GOLDRING 800 Cartridge	£13	0 0	£10 7 6
GOLDRING 800H	£10	13 9	£8 10 6
GOLDRING 800E	£18	17 1	£15 0 0
GOLDRING 800 Super E	£26	0 0	£20 15 0
GOLDRING CS90 Stereo	£5	4 0	£4 3 6
GOLDRING CS81/E	£7	16 1	£6 4 6
GOLDRING G850	£6	10 0	£5 10 0
PICKERING V15 AC2	£8	8 0	£6 19 6
ORTOPON SL15E Transformer	£29	12 11	£23 12 11
SHURE M3DM	£7	0 0	£5 4 6
SHURE N3D	£7	8 3	£6 8 3
SHURE N3E	£5	11 2	£4 8 8
SHURE M31E	£12	0 11	£9 9 0
SHURE N31E	£9	5 3	£7 8 6
SHURE M32E	£11	2 4	£8 15 0

	Rec. Price	Retail Price	Comet Price
SHURE			
SHURE N32E	£8	6 9	£6 13 0
SHURE M32-3	£10	3 10	£7 19 6
SHURE N32-3	£6	9 8	£5 3 6
SHURE M44-5	£11	2 4	£8 17 6
SHURE N44-5	£7	8 3	£6 8 3
SHURE M44-7	£10	3 10	£8 5 0
SHURE N44-7	£6	9 8	£5 3 6
SHURE M44-C	£10	3 10	£8 5 0
SHURE M44E	£12	0 11	£9 19 6
SHURE M44E	£10	3 10	£8 5 0
SHURE M55E	£12	19 5	£10 19 6
SHURE N55E	£11	2 4	£8 17 6
SHURE M75E	£17	12 1	£14 0 0
SHURE N75G	£9	5 3	£8 17 6
SHURE M75-6	£16	13 6	£13 6 0
SHURE N75-6	£8	6 9	£6 13 0
SHURE M75EJ	£19	9 1	£16 10 0
SHURE N75EJ	£11	2 4	£8 17 6
SHURE M75E-95G	£12	19 5	£10 19 6
SHURE N75E	£12	19 5	£10 19 6
SHURE V15-11	£40	15 3	£32 19 6
SHURE VN15E	£16	13 6	£14 13 6
SHURE V15-11-7	£33	18 3	£31 0 0
SHURE VN7	£14	16 6	£11 16 6
SHURE M75E	£21	6 2	£17 19 6
SHURE M75E/D19	£23	3 3	£18 19 6

	Rec. Price	Retail Price	Comet Price
TURNTABLES			
ARENA SP25 with base, cover	£22	1 0	£17 19 6
GARRARD SP.25 Mk II	£15	11 4	£10 19 6
GARRARD AP.75	£23	16 0	£17 19 6
GARRARD SL.55	£13	7 9	£11 12 6
GARRARD SL.65B	£19	6 5	£14 9 6
GARRARD SL.75B	£35	12 4	£28 19 6
GARRARD SL.95B	£49	9 1	£37 19 6
GARRARD 401	£31	14 2	£26 10 0
GARRARD SL.72B	£30	2 0	£24 19 6
GARRARD 3500 with GKS Cartridge	£25	15 0	£11 19 6
GOLDRING GL.69	£15	1 6	£21 5 0
GOLDRING 69P	£33	11 9	£28 19 6
GOLDRING GL.75	£36	8 2	£28 19 6
GOLDRING 75P	£46	18 8	£38 19 6
GOLDRING Covers for 69P and 75P	£4	4 3	£3 8 0
GOODMANS 3025	£37	14 9	£32 19 6
PHILIPS 228	£18	19 6	£16 19 6
PHILIPS GA146	£29	19 6	£24 19 6
PHILIPS 217	£32	9 0	£27 4 0
PHILIPS 202 Electronic	£64	0 0	£54 0 0
THORENS TD.125	£75	17 8	£59 19 6
THORENS 125AB	£120	3 11	£99 19 6
THORENS 150A Mk II	£43	12 7	£32 19 6
THORENS 150AB Mk II	£47	8 7	£40 19 6
THORENS TD.124/11	£46	15 10	£39 19 6

	Rec. Price	Retail Price	Comet Price
SPEAKERS			
ARENA HT 27	£18	18 0	£13 19 6
ARENA HT 28	£17	17 0	£12 19 6
ARENA HT 21	£10	10 0	£9 5 0
ARENA HT 7	£19	19 0	£17 0 0
ARENA HT 10	£22	1 0	£18 19 6
ARENA HT 20	£32	11 0	£26 19 6
ARENA HT 26	£78	15 0	£65 19 6
B & W DM3	£63	0 0	£53 6 0
B & W P2H	£94	10 0	£81 5 0
B & W DM1	£32	0 0	£25 19 6
CELESTION D11ton 10	£21	3 2	£17 5 0
CELESTION D11ton 15	£29	0 0	£22 10 0
DULCI AS 3	£8	8 0	£6 19 6
GOODMANS Majesta	£57	0 0	£48 19 6
GOODMANS Maxim	£20	7 9	£15 19 6
GOODMANS Mezzo II	£30	18 0	£24 19 6
GOODMANS Magnum-K	£40	2 0	£29 19 6
GOODMANS Marimba	£24	0 1	£19 19 6
GOODMANS Mambo	£22	5 6	£18 11 9
GOODMANS 3005 (pair)	£25	0 0	£21 0 0
KEF Celeste	£29	0 0	£22 10 0
KEF Concord	£43	10 0	£33 19 6
LEAK Sandwich	£45	10 0	£36 19 6
LEAK Mini-Sandwich	£29	15 0	£23 19 6
QUAD Electrostatic	£66	0 0	£52 19 6
PHILIPS RH 481	£11	0 0	£9 2 6
PHILIPS RH 482	£18	0 0	£14 18 6

	Rec. Price	Retail Price	Comet Price
WHARFEDALE Speakers			
Airedale	£69	10 0	£57 14 0
Denton	£19	0 0	£14 19 6
Super Linton	£22	10 0	£18 19 6
Melton	£29	10 0	£23 19 6
Dovedale 3	£39	10 0	£29 19 6
Rosedale	£59	10 0	£48 19 6
WHARFEDALE UNIT			
3 Speaker Kit	£11	19 6	£9 19 6
WHARFEDALE UNIT			
4 Speaker Kit	£16	0 0	£13 10 0
WHARFEDALE UNIT			
5 Speaker Kit	£23	10 0	£19 19 6

	Rec. Price	Retail Price	Comet Price
CHASSIS SPEAKERS			
GOODMANS Axletta 8	£7	2 1	£5 13 6
GOODMANS Twinaxletta 8	£8	0 7	£6 8 0
GOODMANS Axiom 10	£8	8 0	£6 14 0
GOODMANS Axiom 201	£12	10 0	£9 7 6
GOODMANS Axiom 301	£17	18 0	£13 8 6
GOODMANS Audiom 51	£11	6 0	£8 9 6
GOODMANS Audiom 61	£16	7 0	£12 5 6
GOODMANS Audiom 81	£27	12 0	£20 14 0
GOODMANS Audiom 91	£31	5 0	£26 8 6
GOODMANS Audiom 91/100	£34	17 0	£26 8 0
GOODMANS ARU 180	£37	17 8	£28 18 6
GOODMANS ARU 280	£37	18 8	£28 18 6
GOODMANS ARU 480	£5	8 5	£4 1 3
GOODMANS ARU 172	£37	18 8	£28 18 6
GOODMANS Trebax 100	£27	9 0	£21 18 6
GOODMANS Trebax 5K/20KL	£34	17 0	£26 8 0
GOODMANS Mixdax	£11	4 0	£8 8 0
GOODMANS Attenuator	£3	1 4	£2 6 0
GOODMANS Crossover			
Networks XO/950/5000	£8	8 7	£6 6 0
GOODMANS Crossover			
Networks XO/950	£6	7 9	£4 15 9
GOODMANS Crossover			
Networks XO/5000	£2	6 0	£1 14 6
WHARFEDALE 8 Inch			
Bronze/RS/DD	£4	8 0	£3 13 6
WHARFEDALE Super			
8/RS/DD	£7	12 0	£6 8 0
WHARFEDALE Super			
10/RS/DD	£12	14 0	£10 10 0
WHARFEDALE WMT 1			
Matching Transformer	16	9	13 6

	Rec. Price	Retail Price	Comet Price
HI-FI STEREO TAPE DECKS AND TAPE RECORDERS			
AKAI 150D	£130	2 4	£109 0 0
AKAI X-360	£339	0 0	£284 0 0
AKAI X-360D deck	£290	0 0	£243 0 0
AKAI 1710	£109	0 0	£89 19 6
AKAI 1800	£158	0 0	£133 0 0
AKAI 1800SD	£199	0 0	£167 0 0
AKAI 4000 D deck	£89	19 1	£71 19 6
ALBA R22 Battery/Mains	£50	5 0	£29 19 6
BUSH TP 60 Cassette Tape			
Recorder	£27	15 8	£24 19 6
FERGUSON 3224 Twin Track	£43	14 0	£24 19 6
FERGUSON 3246	£41	14 0	£32 19 6
FERGUSON 3247 4-track	£47	1 0	£37 19 6
FERGUSON 3244 Stereo 4-track	£97	18 0	£79 19 6
GRUNDIG C200 Cassette	£37	19 10	£29 19 6
GRUNDIG TK 120 Continental	£39	5 0	£29 19 6
GRUNDIG TK 124	£44	18 0	£34 19 6
GRUNDIG TK 144	£49	19 6	£39 19 6
GRUNDIG 149	£57	12 8	£47 19 6
MARCONI 4218 Stereo tape			
Recorder	£89	11 2	£69 19 6
PHILIPS 3302 Cassette			

do a 'which?' hunt on mini-meters



Which has a d.c. sensitivity of 20,000 ohms per volt?
 Which has an a.c. sensitivity of 2,000 ohms per volt?
 Which has a d.c. accuracy + 2½% F.S.D.?
 Which has an a.c. accuracy + 2¾% F.S.D.?
 Which maintains a.c. accuracy to 20/kcs?
 Which provides high voltage probes to extend the range to 25 or 30 kV d.c. for testing electronic equipment with high source impedance?
 Which provides probes that can be used with any other meter of similar sensitivity?
 Which type of case would you like? Leather or Vinyl. Both available.
 Which meter makes every user a devil's advocate for its performance and handiness?

The pocket size Minitest

Get the catalogue for a full briefing.

SALFORD ELECTRICAL INSTRUMENTS LIMITED
 Peel Works, Barton Lane, Eccles, Manchester M30 0HL
 Telephone 061-789 5081 Telex 66711
 A Member Company of GEC Electrical Components Ltd.



FABULOUS VALUE

TRANSISTORISED STEREO HI-FI RECORD PLAYER

Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.

Advanced solid state amplifier only 4½" deep. 14 transistors plus 4 diodes, separate Bass and Treble - 10 watts total power. Frequency response 50-15,000 c/s.

EASY TO INSTALL
 NO TECHNICAL KNOWLEDGE REQUIRED

Only **28** Gns. + P&P 17/6

Credit terms available, first monthly payment £3.6.2 followed by 9 monthly payments of £3.6.2. (Total "Credit Sale" Price £33.1.8). Send £4.3.8 today.

FANTASTIC BARGAIN OFFER!
 "TRANSCONTINENTAL"
 FULLY TRANSISTORISED STEREO PHONIC RADIOGRAM CHASSIS

Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price **ONLY**

10 Watts Total output **£36.10.0** P&P 17/6
 17 Transistors & 10 diodes

EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY
 Credit Terms available. First monthly payment £4.2.2 followed by 9 monthly payments of £4.2.2. (Total "Credit Sale" Price £41.1.8.) Send £4.10.8 today.

Callers Welcome

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name

Address

LEWIS radio 100 CHASE SIDE, SOUTHGATE, Dep. P670 LONDON, N.14. TELEPHONE 896 3733/8666.

TRANSISTOR TRANSFORMERS

Mounting lugs to suit printed circuit-boards. Fully vacuum varnish impregnated.

D/B1. Driver. OC71 into 2 x OC72 (2mW) 1:1 C.T. Sec. 10/6
 D/B2. Output. 2 x OC72 "Class B" into 3 ohm speech coil (200mW) 6-6:1 I.C.T. Prim. 14/9

D/B3. Driver. OC71 into 2 x OC72 Single ended p.p. (5mW) 3-6:1 +1 Split Sec. 14/6
 D/B4. Output. Single OC72 "Class A" into 3 ohm speech coil, (50mW) 9-2:1 12/3
 D/B5. Driver. OC81D into 2 x OC81 Single ended p.p. (2mW), 5-5:1 +1 Split Sec. 12/-
 D/B6. Driver. OC81D into 2 x OC81 (2mW) 2-8:1 C.T. Sec. 14/6
 D/B7. Output. 2 x OC81 "Class B" into 3 ohm speech coil, (500mW) 9-2:1 C.T. Prim. 14/8

Post & Packing 2/6 per Trans.

Transistor Clips (copper) for 6mm cases 6BA mounting slot 5/- dozen P. & P. 6d.

Mountings for Power Transistors 8/- Packet, 4 Mica Washers, 8 Insulating Bushes.
 Suit TO3 Transistors. P. & P. 1/-
 Heat Sinks—Extruded Section 11/3 P. & P. 2/6
 Extruded Aluminium finned sections with "Alcorom" anti-corrosive finish.
 Supplied undrilled in 4.00" lengths.
 Machined heat sinks to fit TP5 cases Thermal resistance 55° C./W. 3/6 each P. & P. 6d.

Transistor Mounting Pads, Moulded pads to suit TO5 or TO18 transistors. 2/- for 10, P. & P. 6d.

PRINTED CIRCUIT PANELS

The ready-punched wiring pattern enables many circuits to be built speedily with little additional wiring. Hot tinned for easy soldering. One end is formed so as to plug into a 8 way Edge connector which we can supply. Supplied with paper replica for circuit layout planning.

Valve Type Accommodates 3 B9A Bases, Size 6" x 2" X.062" 5/- each P. & P. 6d.

Transistor Type Accommodates 8 transistors. Base, collector and emitter terminals are marked. 6" x 2" x 0.62" 5/- each
 Edge Connectors General Purpose 8 way to suit panels above .150" pitch 10/- P. & P. 6d.

REPLACEMENT CONTROLS

Philips 5k, 8.P. Model Nos.: L1G 30T, 41T, 51T, 52T, L2G 37T, 47T, 50T, ST425A, 426, 431, 13RL161, 13RL265 8/6 P. & P. 6d.

We also supply Bakelite Sheet, Cables, Capacitors, Chokes smoothing, suppressor, Ferrite Beads, Ferrite Rods (Aerial), Grommets, Rubber, p.v.c. Integrated Circuits, Jack Plugs and Sockets, Meters, Pots, Rectifiers, germanium, meter, selenium, silicon, Relays, Relay cases, Resistors adjustable (trimmer) fixed carbon high stability mains dropping oxide meter (metal film) wirewound. Stepping, solder, Spindle Locks, Spring Kits, Stand Off Insulators, Storage Drawers, Studding, Suppressors, Auto. cr.t. cleaner, Switches, Decade, Micro, Reed, Toggle, Wafer, Transformers, Auto. cr.t. filament, intervalve, isolating, mains, matching, microphone, output, transistor, LINE-OUTPUT.

Regret no Lists. Please send S.A.E. for your requirements.

01-540 3955 01-540 3513

D. & B. TELEVISION (Wimbledon) LTD.
Transformer Manufacturers
 80 MERTON HIGH STREET, LONDON, S.W.19

COMPLETE STEREO SYSTEM

FOR ONLY

39 GNS


CARRIAGE 35/-



PREMIER STEREO SYSTEM "ONE" Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on off, stereo mono switch. Brushed aluminium front panel Black metal case with teakwood ends: Size 12 x 5½ x 3½in. high (Amplifier available separately if required £14.19.6. Carr. 7/6.)

PREMIER STEREO SYSTEM "TWO"
As system "ONE" above but with Garrard SP25.
PREMIER PRICE 45 Gns. Carr. 35/-

TELETON SAQ203E STEREO AMPLIFIER

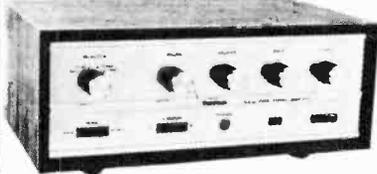

A small but powerful amplifier designed for stereo hi-fi reproduction. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble, Stereo/Mono slide switch. Stereo headphone socket. Attractive oiled walnut cabinet with brushed aluminium front panel. List Price £28.7.0

PREMIER PRICE 22 Gns. P. & P. 10/-

PREMIER STEREO SYSTEM "FOUR"

Teleton SAQ203E Amplifier (as above) .. £23.2.0
Garrard SP25 .. £11.19.6
Shure M3D .. £6.19.6
Teak base and cover .. £5.10.0
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers .. £26.5.0

Total cost if purchased separately .. £73.16.0

PREMIER PRICE 65 Gns. Carr. 35/-

VERITAS V-149 MIXER


Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2½in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phonoplugs output. Attractive teak wood grain finish case.



MONO MODEL 59/6 STEREO MODEL 69/6 P. & P. 2/6.

WIDE RANGE OF HI-FI STEREO EQUIPMENT ON DEMONSTRATION

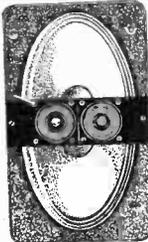All leading makes available including Rogers, Armstrong, Nikko, Wharfedale, Goodmans, Goldring, Shure, etc. etc.



E.M.I. 13x8ins. HI-FI SPEAKERS

Fitted two 2½in. tweeters and crossover network. Impedance 16 ohms. Handling capacity 10 watts. Brand new.

79/6

P. & P. 7/6



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 6ft lead and stereo jack plug.

49/6

P. & P. 8/-



WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. 67/6 P. & P. 2/-.

VERITAS V-313 TAPE HEAD DEFLUXER



A must for all tape users! Tape heads become permanently magnetized with constant use: this leads to background noise that prevents perfect recordings. Simply applied to recording head the V313 leaves head free of magnetism. Cleans any tape head in seconds. **34/6** P. & P. 1/6.

"NOVA" 505 STEREO AMPLIFIER



A superb stereo amplifier offering every facility for the hi-fi enthusiast. Output 5 watts per channel. Frequency response 40-20,000 Hz ± 3dB. Inputs for radio, P.U. Ceramic, P.U. Magnetic Tape. Separate bass and treble controls. Volume and Balance controls. Mono Stereo Switch. Also features headphone socket and tape output. Teak case with attractive illuminated front panel. Size 14½ x 9½ x 3½in. A.C. 200/250V.

PREMIER PRICE 18 Gns. Carr. 10/-

PREMIER STEREO SYSTEM "THREE"

Nova 505 Amplifier (as above) .. £18.18.0
Garrard SP25 .. £11.19.6
Sonotone 9TAHCD .. £2.15.0
Teak base and cover .. £5.10.0
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers .. £26.5.0

Total cost if purchased separately .. £65.7.6

PREMIER PRICE 55 Gns. Carr. 35/-

TWO STATION TRANSISTOR INTERCOMS.

Complete with battery and 50ft. connecting wire. Compact size, two way call system. Ideal for home office, factory, etc.



65/- P. & P. 4/-

TAPE CASSETTES



C60 (60 min.) 7/6

THREE FOR 21/-

C90 (90 min.) 12/6

THREE FOR 36/-

C120 (120 min.) 17/6

THREE FOR 51/- P. & P. 1/-.



CASSETTE HEAD CLEANER

Removes unwanted deposits from delicate tape heads. Fits all cassette recorders. **11/6** P. & P. 1/-.

All cassettes can be supplied with library cases at 6d extra each



"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped attractively boxed.

LP3 3' 250' P.V.C.	5/6	LP6 6½' 1200' P.V.C.	12/6
TT3 3' 450' POLYESTER	7/6	DT6 6½' 1800' POLYESTER	22/6
DT3 3½' 600' POLYESTER	11/6	TT8 8' 2400' POLYESTER	37/6
SP5 5' 600' P.V.C.	8/6	SP7 7' 1200' P.V.C.	12/6
LP5 5' 900' P.V.C.	10/-	LP7 7' 1800' P.V.C.	15/-
DT5 5' 1200' POLYESTER	15/-	DT7 7' 2400' POLYESTER	25/-
		TT7 7' 3600' POLYESTER	50/-

TAPE SPOOLS 3" 1/-, 5", 5½", 7" 1/9, Post and Packing 3" 1/-, 5", 5½", 1/6, 7" 2/- (3 reels and over Post Free).


PREMIER RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1

Tel: 01-636 3451



CAR LIGHT FLASHERS

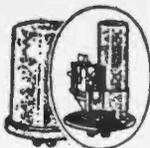

Heavy duty light flasher employs a condenser discharge principle operating on electro mechanical relay. (As inset). Housed in strong plastic case. Flashing rate between 60-120 per minute. 12V DC operation. Maximum load 6 amps. Size 2-11/16in. dia. x 4in. Supplied brand new at a fraction of original cost. 6/6 each. P. P. 2/6. (3 for 17/6. P. P. 4/6).

CLASS D WAVEMETERS



A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. £5.19.6. Carr. 7/6. Or brand new with accessories. £7.19.6. Carr. 7/6.

CLASS D WAVEMETERS No. 2
Crystal controlled. 1.2-19 Mc/s. Mains or 12V. D.C. operation. Complete with calibration charts. Excellent condition. £12.10.0. Carr. 30/-.

R209 MK II

COMMUNICATION RECEIVER

11 valve high grade communication receiver suitable for tropical use. 1.20 Mc/s on 4 bands. AM/CW/FM operation. Incorporates precision vernier driver, B.F.O., aerial trimmer, internal speaker and 12v. D.C. internal power supply. Supplied in excellent condition, fully tested and checked. £15.0.0. Carr. 20/-.

TYPE 13A DOUBLE BEAM OSCILLOSCOPES



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Mc/s. Bandwidth 5.5 Mc/s. Sensitivity 33mV/CM. Operating voltage 0/110/200/240V. A.C. Supplied in excellent working condition. £22.10.0. Or complete with all accessories, probe, leads, lid, etc. £25. Carriage 30/-.



MARCONI T/44/TF956 AF Absorption Wattmeter

1 μ/watt to 6 watts. £20. Carr. 10/-.

SOLARTRON CD 71152 Double Beam Oscilloscopes


D.C. to 9 Mc/s. Perfect order £65. Carr. 50/- (Few available less C.R.T.) £25 Carr. 50/-

TO-3 PORTABLE OSCILLOSCOPE



3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω 25pF X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5 cps-500KHz. Input Imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. £37.10.0. Carr. 10/-.

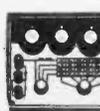TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE




A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11 meg Ω 6 Ranges ± 1% L.I. μ H - 11 HENRYS 6 Ranges -2% C. 10pF ± 110nF. 6 Ranges ± 2%. TURNS RATIO 1.1/1000-1.1/100. 6 Ranges ± 1%. Bridge voltage at 1,300 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/4 x 5 x 2 1/2in. £20. P. & P. 5/-.

UNR-30 4-BAND COMMUNICATION RECEIVER

Covering 550 Kcs-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6. **13 gns.**



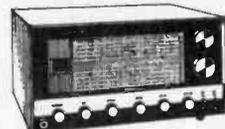TRIO JR-310 New Amateur Band 10-80 Metre Receiver in stock. £77.10.0.



LAFAYETTE SOLID STATE HA600 RECEIVER


5 BAND AM/CW/SSB AMATEUR AND SHORT WAVE 150 Kc/s-400 Kc/s and 550 Kc/s-30 Mc/s FET front end • 2 mechanical filters • Huge dial • Product detector • Variable BFO • Noise limiter • 8 meter • 24in Bandspread • 230V. A.C./12V. D.C. neg. earth operation • RF gain control. Size 10in. x 9 1/2in. x 8 1/2in. Weight 18 lbs. EXCEPTIONAL VALUE. £45. Carr. 10/- S.A.E. for full details.

LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER

Six bands 3-5.4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-54Mc/s. Dual conversion on all bands. 2 x 455 Kc/s mechanical filters. FET front end, product detector, variable BFO, 100Kc/s crystal calibrator. 'B' Meter. Huge slide rule dial. Operation 230V AC or 12V DC. Size 15 x 9 1/2 x 8 1/2in. Complete with instruction manual. £57.10.0 Carr. Paid. 100Kc/s crystal 39/6 extra.

UR-1A SOLID STATE COMMUNICATION RECEIVER

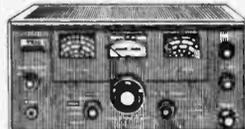4 bands covering 550 Kc/s-30 mc/s continuous. Special features are use of FET transistors. 8 meter, built in speaker and telescopic aerial, variable BFO for SSB reception, noise limiter, bandspread control, sensitivity control. Output for low impedance headphones. Operation 220/240 volt A.C. or 12 volt D.C. Size 12 1/2in. x 4 1/2in. x 7in. Excellent value. ONLY £24. Carr. 7/6.



TRIO COMMUNICATION RECEIVER MODEL 9R-59DE

4 band receiver covering 550 Kc/s to 30 Mc continuous and electrical bandspread on 10, 16, 20, 40 and 80 metres. 8 valve plus 7 diode circuit, 4/8 ohm output and phone jack. SSB-CW • ANL • Variable BFO • 8 meter • Sep. bandspread dial • IP 455 Kc/s • Audio output 1.5 W • Variable RF and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10in. With instruction manual and service data. £42. carriage paid. TRIO COMMUNICATION TYPE HEADPHONES. Normally £5.19.6. OUR PRICE £3.18.0 if purchased with above receiver.

TRIO JR. 500SE 10-80 Metre Receiver £69.10.0

TRIO TS 510 AMATEUR TRANS-CEIVER with speaker and mains P.S.U. £180 IN STOCK!




RCA COMMUNICATIONS RECEIVERS AR88D


Latest release by ministry BRAND NEW in original cases. 110-260V. A.C. operation. Frequency in 6 Bands. 535 Kc/s-32 Mc/s continuous. Output impedance 2.5-600 ohms. Incorporating crystal filter, noise limiter, variable BFO, variable selectivity, etc. Price £65.0.0. Carr. £2.

LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER

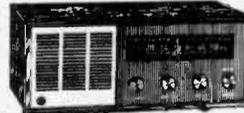A completely new transistorised receiver covering 152-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 75 Ω aerial input. Headphone jack. Operation 230V. A.C./12V. D.C. Neg. earth. £37.10.0. Carr. 10/-.



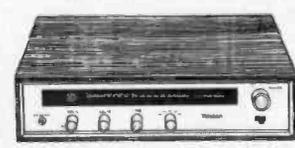TELETON CR-10T AM/FM STEREO TUNER AMPLIFIER



A new model from Teleton. 31 solid state devices. 4 + 4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600KHz FM 88-108MHz. Automatic FM Stereo reception. Stereo Indicator. Controls: Tuning, function selector, Tone and R & L volume controls. AFC switch. Stereo headphone socket. Size 13 1/2 x 3 1/2 x 9 1/2 approx. PRICE £34.0.0. Carr. 7/6.

CLEAR PLASTIC PANEL METERS



First grade quality Moving Coil panel meters. Type MR 381. 1 1/4in. square fronts.

500-0-500μA	£27/8	80mA	£27/8	150V. D.C.	£27/8
1mA	£27/8	100mA	£27/8	300V. D.C.	£27/8
1-0-1mA	£27/8	150mA	£27/8	500V. D.C.	£27/8
2mA	£27/8	200mA	£27/8	750V. D.C.	£27/8
5mA	£27/8	300mA	£27/8	15V. A.C.	£27/8
10mA	£27/8	600mA	£27/8	50V. A.C.	£27/8
750mA	£27/8	3V. D.C.	£27/8	150V. A.C.	£27/8
1 amp.	£27/8	10V. D.C.	£27/8	300V. A.C.	£27/8
2 amp.	£27/8	20V. D.C.	£27/8	500V. A.C.	£27/8
5 amp.	£27/8	20mA	£27/8	8 meter IMA	38/-
200μA	£27/8	100V. D.C.	£27/8	VU meter	42/-
500μA	£27/8				

FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET

Variable Voltage Transformers

Brand new, guaranteed and carriage paid. High quality construction. Input 230V. 60-60 cycles. Output full variable from 0-230 volts. Bulk quantities available. 1 amp.—£5.10.0; 2.5 amp.—£6.15.0; 5 amp.—£9.15.0; 8 amp.—£14.10.0; 10 amp.—£18.10.0; 12 amp.—£21.0.0; 20 amp.—£37.0.0.

CRYSTAL CALIBRATORS NO. 10



Small portable crystal controlled wavemeter. Size 7 x 7 1/4 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 200V. D.C. 15mA and 12V. D.C. 0.3A. £9/8. Carr. 7/6.

TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. Input 10 ranges: -01/003/1-3/11/10/30/100/300V. R.N.S. 4cps-1.2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.10.0 Carr. 5/-.



LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 6k Ω. Operation 200/250V. A.C. Supplied in perfect order. £12.10.0 Carr. 10/-.

TE-65 VALVE VOLTMETER

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. £17.10.0. P. & P. 6/- Additional probes available: R.F.35/- H.V.42/6.



COSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.C. coupled. Band width 1Kc/s. Perfect order. £25. Carr. 30/-.

AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airmec. Frequency coverage 50-50 Mc/s. AM CW/FM. Incorporates precision dial level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9in. Supplied in brand new condition complete with all connectors fully tested. £45. Carr. 20/-.



EDDYSTONE VHF RECEIVERS Model 770R. 10-165 Mc/s. Excellent condition. £150.

PLESSEY 8L403A 3 watt Integrated Amplifier Circuit 49/8. Post paid.

TE-16A Transistorised Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 6 1/2 x 5 1/2 x 3 1/2in. Complete with instructions and leads. £7.19.6. P. & P. 4/-.



HOSIDEN'DH-085 DE-LUXE STEREO HEADPHONES

Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead and stereo jack plug. £7.19.6. P. & P. 2/6.



AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded. 150 W. £2. 2/6. P. & P. 3/6. 300 W. £2.19.6. P. & P. 4/6. 500 W. £4.10.0. P. & P. 6/6. 1,000 W. £6.10.0. P. & P. 7/6. 1,500 W. £7.19.6. P. & P. 8/6. 7,500 W. £15.10.0. P. & P. 20/-.

G. W. SMITH & CO (RADIO) LTD. Also see oppos. page

ARF-100 COMBINED AF-RD SIGNAL GENERATOR



A.F. SINE WAVE
20 - 200,000 c/s.
Square wave 20 - 30,000 c/s. O.P.
HIGH IMP. 21V.
P/P800 Ω 3.8V. P/P
TF 100 Kc/s-300 Mc/s. Variable R.F. attenuation int/ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V. A.C. £22.10.0. Carr. 7/6.

TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 7/6. Size 140 x 215 x 170 mm.

PEAK-SOUND PRODUCTS. Full range of Amplifiers, Kits, Speakers, in stock.

TY75 AUDIO SIGNAL GENERATOR

Sine Wave 20c/s to 200 kc/s. Square Wave 20c/s to 30kc/s. High and low impedance output. Output variable up to 6 volts. 220/240 volts A.C. Size 210 x 150 x 120 mm. Brand new with instructions. £18. Carr. 7/6.



MARCONI TP142E DISTORTION FACTOR METERS. Excellent condition. Fully tested. £20. Carr. 15/-.


LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mFd 2 ohms 200 meg-ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New £17.10.0 Carr. 7/6.



TO-2 PORTABLE OSCILLOSCOPE

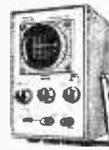A general purpose low cost economy oscilloscope for everyday use. Y and X. Bandwidth 2UPS-1 MHz. Input imp. 2 meg Ω 25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 v a.c. Supplied brand new with handbook. £22.10.0. Carr. 10/-.



ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons

J1B. AUDIO SIGNAL GENERATOR. 15 c/s to 50 Kc/s. Sine wave. Output 600 ohms or 5 ohms £30.0.0.

VM70. UHF MILIVOLT METER. 100 Kc/s to 1,000 Mc/s. A.C. 10mV to 3v. D.C. 10 mV to 3v. Current 0.01 uA to 0.3 mA. Resistance 1 ohm to 10 megohm. £125.0.0.


TT15. TRANSISTOR TESTER. Full range of facilities for testing PNP or NPN transistors in or out of circuit. £37.10.0. Carriage 10/- per item.

HOSIDEN DHO4S 2-WAY STEREO HEADSETS



Each headphone contains a 2in. woofer and a 1in. tweeter. Built in individual level controls. 8 Ω imp. 25-18,000 Ω with cable and stereo plug. £5.19.6. P. & P. 2/6.

AVOMETER MOVEMENTS

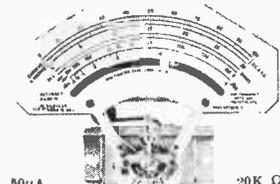

80μA 20K Ω/V Spare movements for Model 9 or 9. (Fitted with Model 9 scale) or basis for any multi-meter. Brand New & Boxed. 69/6. P. & P. 3/6.

The latest edition giving full details of a comprehensive range of the finest COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. Over 230 pages, fully illustrated and detailing thousands of items, many at bargain prices. FREE DISCOUNT COUPONS VALUE 10/-

Latest Catalogue

SEND NOW - ONLY 7/6 P&P!!

GARRARD

FULL CURRENT RANGE OFFERED BRAND NEW AT FANTASTIC SAVINGS

1025 stereo	£7.19.6	SL72B	£25.0.0
40 Mk II stereo	£8.8.0	APT75	£18.19.6
2025T/C stereo	£3.17.6	SL75	£25.19.6
3000 stereo	£9.19.6	SL75B	£28.0.0
SP25 Mk II	£11.9.6	SL95B	£35.0.0
SL55	£11.12.6	A70/11	£11.19.6
SL65B	£14.19.6	401	£25.0.0

Carriage 7/6 extra each item.
TEAK PLINTHS & PERSPEX COVERS.
1. For SP25, SL65, SL55, 3000, 2025 T/C 2025, 1000. £4.10.0
2. For AP75, SL75, SL95 £5.19.6.
3. For SP25 etc. to operate with lid in place £5.19.6.
Carriage 7/6 extra each type. Full range of Garrard accessories available.



SPECIAL OFFERS!

Garrard SP25 fitted Goldring (1800 cartridge and wooden plinth. Total list price £32.8.5.

OUR PRICE **£19.15.0** Carr. 10/-

GOLDRING GL69 fitted Goldring (1800 cartridge complete with deluxe base and cover.
Total list price £50.16.0.

OUR PRICE **£39** Carr. 10/-

RTCC49 4-TRACK TAPE DECK

British Made Speeds 1 1/2", 3 1/2", 7 1/2" P.S. Marriot Heads. 7" reel size. Push Button controls, fully interlocking. Size 13" x 10" x 1 1/2" above unit plate, 4 1/2" below. Full instructions. £18.19.6 Carr. 7/6



MULTIMETERS for EVERY purpose!

TE-51. NEW 20,000 Ω/VOLT MULTIMETER with overload protection and mirror scale. 0/5/60/120/1,200V. A.C. 0/3/30/60/300/600/3,000V. D.C. 0.60μA/1/2/3/30mA. 92.6. 0/80K/6 meg. ohm. 2/2. P. & P. 2/6.

TE-900 20,000 Ω/VOLT GIANT MULTIMETER mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 v. A.C. 0/25/12.5/10/50/250/1,000/5,000V. D.C. 0/50μA/110/100/500mA/10 amp. D.C. 0.2K/200K/20 MEG. OHM. £15. P. & P. 5/-.

MODEL AS-100D. 100K Ω/VOLT. 5in. mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1,200V D.C. 0/6/30/120/300/600V A.C. 0/10μA/6/60/300 mA/12 amp. 0/2K/200K/2M/200M Ω. -20 to +17dB. £12.10.0. P. & P. 3/6.

LAFAYETTE 57 Range Super 50k Ω/volt Multi-meter! D.C. volts 12 mV - 1000V. A.C. volts 1.5V - 1000V. D.C. current 25μA-10 amp. Ohms 0-10 meg Ω ΩB - 20 to +81 ΩB. Overload protection. £12.10.0. Carr. 3/6.

MODEL TE-90. 50,000 Ω/V mirror scale overload protection 0/3/12/60/300/600/1200V. D.C. 0/6/30/120/300/600/1200V. D.C. 0.3/6/60/600 mA. D.C. 16K/160K/1.6/16meg Ω. -20 to +63dB. £7.10.0. P. & P. 3/-.

MODEL TE-80. 20,000 O.P.V. 0/10/50/100/500/1,000V A.C. 0/5/25/50/250/500/1,000 v. D.C. 0-50μA. 5/50/500mA. 0/6K/60K/600K/6 meg. £4.17.6. P. & P. 3/-.

MODEL TE-70. 30,000 Ω/V. 0/3/15/60/300/600/1200V D.C. 0/6/30/120/600/1200V A.C. 0/50μA/3/30/300mA. 0/15K/150K/1.5M/16 Meg. Ω. £5.10.0. P. & P. 3/-.

MODEL TE-12 20,000 O.P.V. 0/0.6/6/30/120/600/1,200/3,000/6,000V. D.C. 0/6/30/120/600/1,200V. A.C. 0/60μA/6/60/600mA. 0/4K/60K/6Meg/60 Meg. Ω 50pF. 0.2mF. £5.19.6. P. & P. 3/6.

MODEL FT-34. 1,000 O.P.V. 0/10/50/250/500/1,000V A.C. and D.C. 0/1100/500mA D.C. 0/100K Ω. 39/6. P. & P. 1/6.

SAVE UP TO 33% OF HI-FI EQUIPMENT
Send for discount price list

AVO CT471A MULTIMETER

Battery operated, fully transistorised. Sensitivity 100mΩ/v. Measures AC/DC Voltages 12mV to 1,200V. AC/DC Current 12uA to 1.2 Amp. Resistance 12 ohm to 120 mΩ. HF, VHF, UHF Voltmeter with multiplier 4v to 400v up to 50 Mc/s, 40mV to 4v up to 1,000 Mc/s. Offered in perfect condition. £55 each. Carr. 10/-

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM



Operative over amazingly long distances. Separate call and press to talk buttons with 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.6. P. & P. 3/6.

SINCLAIR EQUIPMENT

Project 60 range of new models now in stock
Z30 Amplifier 59/6
STEREO 60 Control Unit £9.19.6
P25 Power Supply £4.19.6
P26 Power Supply £7.19.6
O16 Speakers £8.19.6
All Post Paid
SPECIAL PACKAGE OFFER!
2 x Z30 Amplifiers, Stereo 60 and P25 Power Supply £19. Carr. 7/6
or with 2 x Q16 Speakers £25 Carr. 7/6
Micromatic Radio Kit 49/6
Micromatic Radio Built 59/6
SINCLAIR 1C/10 IN STOCK 59/6
2000 Amplifier £23.10.0 Carr. 7/6
Neoteric Amplifier £46.0.0 Carr. 7/6

ECHO HS-606 STEREO HEADPHONES

Wonderfully comfortable. Lightweight adjustable vinyl headband. 6ft. cable and stereo jack plug. 25-17,000 cps. 8 ohm imp. 67/6 P. & P. 2/6.

TE111. DECADE RESISTANCE ATTENUATOR

Variable range 0-11dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz. (-3dB). Accuracy: 0.05dB. ±1 indication dB x 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new £27.10.0. P. & P. 5/-.

RECORDING HEADS

COSEMOOD 1-track heads. High imp. record/playback 65/-, Low imp. erase 20/-, MARRIOTT 1-track heads. High imp. record/playback 65/-, Low imp. erase 20/-, Post extra.

AMERICAN TAPE

First grade quality American tapes. Brand new. Discount on quantities.
3in. 225ft. L.P. acetate 3/6
3in. 600ft. T.P. mylar 10/0
5in. 600ft. std. plastic 8/6
5in. 900ft. L.P. acetate 10/0
5in. 1,200ft. D.P. mylar 15/6
5in. 1,200ft. L.P. acetate 12/6
5in. 1,200ft. L.P. mylar 16/6
5in. 1,400ft. D.P. mylar 22/6
5in. 2,400ft. T.P. mylar 12/6
7in. 1,200ft. std. acetate 10/0
7in. 1,800ft. L.P. acetate 15/6
7in. 1,800ft. L.P. mylar 20/6
7in. 2,400ft. D.P. mylar 25/6
7in. 3,800ft. T.P. mylar 45/6
Postage 2/-, Over £3 post paid.

TAPE CASSETTES

Top quality in plastic library boxes.
C60 60 min 8/6, 3 for 24/6
C90 90 min 12/6, 3 for 36/-
C120 120 min 15/-, 3 for 45/6
Cassette Head Cleaner 11/6. Post Extra.

G.W. SMITH & CO. (RADIO) LTD
3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

All Mail Orders to -
147, Church Street, London, W.2
Tel: 01-262 6852
(Trade supplied)

R.S.T. VALVE MAIL ORDER CO.

BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.
—5.30 p.m.
Closed Sat. 1.30—2.30 p.m.
Open Daily to Callers

Tel. 759-0199/1649

1A7	7/9	6BR8	12/8	6K7GT	4/6	10C1	20/-	25L6GT	7/-	150B2	11/8	DK32	7/9	ECH35	11/6	EY86	7/-	PCF80	6/9	FY801	9/8	UCL83	10/-
1D5	7/9	6B87	25/-	6K8	2/9	10C2	12/6	25Y3	6/-	150C4	9/6	DK91	6/-	ECH42	13/-	EZ35	6/8	PCF82	6/8	R2	7/8	UF41	10/8
1H5	7/-	6BW6	14/8	6K8M	11/8	10P1	14/9	25Z4	6/3	801	9/8	DK92	9/-	ECH81	5/9	EZ40	9/-	PCF84	8/-	R19	7/9	UF89	7/8
1LD6	6/-	6BW7	13/-	6K8G	3/8	10P2	18/-	25Z6	8/-	807	9/8	DK96	7/9	ECH83	8/9	EZ41	9/-	PCF86	9/-	RG5/500	8/0	UL14	12/-
1NGT	8/6	6C4	5/-	6K8CT	7/-	10P9	10/6	25Z6	8/6	813USA	120/-	DL62	25/-	ECL80	7/-	EZ80	5/8	PCF801	9/9	B130	4/0	UL84	7/6
1R5	6/-	6C5	5/-	6K8S	15/6	10P18	8/-	28D7	9/-	813	7/8	DL33	4/-	ECL82	7/-	EZ81	5/8	PCF802	9/9	BP4	8/-	UM80	5/6
1B4	5/6	6C6	3/9	6L1	12/-	10L1	8/-	30C1	6/9	954	15/-	DL84	6/9	ECL86	9/-	GZ30	10/-	PCF808	15/8	BP41	3/8	UT6	21/-
1B5	4/6	6C8G	6/-	6L6G	7/9	10LD11	10/8	30C15	15/-	866A	15/-	DL84	6/9	ECL86	9/-	GZ32	10/-	PCF808	15/8	BP61	8/8	UT7	21/-
1T4	4/-	6CD6G	24/-	6L18	6/-	10P13	13/6	30C17	16/-	954	6/3	DL95	7/9	ECL80030	9/-	GZ32	10/-	PCF808	15/8	BTY280/80	8/8	UT8	21/-
3A4	4/-	6CH6	7/6	6Q7G	6/-	11E3	7/0	30C18	15/-	1625	8/6	DL96	7/6	EF9	20/-	GZ34	11/-	PCL82	7/9	H33	9/5	UT9	8/3
3Q4	7/9	6CW4	13/6	6Q7GT	8/8	12AT6	4/9	30F5	17/-	4022AR	67/-	DM70	8/-	EF37A	7/-	HN309	20/-	PCL83	10/3	SU25	19/6	UY21	9/6
3Q5	7/-	6D6	8/9	6R47M	7/-	12AT7	6/-	30FL1	15/-	5763	12/-	DY86	8/-	EF39	8/-	KT36	18/-	PCL84	8/6	SU2150	12/8	UY41	8/6
3B4	6/9	6E3	7/6	6R47	7/-	12AU6	6/9	30FL12	19/-	7193	2/-	DY87	6/6	EF41	10/-	KT61	22/8	PCL85	9/3	T41	17/8	UY85	8/6
3V4	6/9	6F1	12/6	6R67	6/-	12AU7	5/9	30FL14	15/8	7475	14/-	EB8CC	12/-	EF80	5/-	KT66	20/-	PCL86	9/3	TDD4	8/8	VMP4G	17/-
6R4Y	10/8	6F5G	8/-	6R87	3/3	12AX7	6/3	30L16	17/-	A61	9/6	EAS0	3/6	EF80	4/6	KT81	35/-	PD500	29/-	U10	7/6	VP4B	26/-
6R4Y	5/6	6F6G	6/-	6R87	5/-	12BA6	6/-	30L17	17/-	ATP4	2/3	EABC80	6/8	EF85	7/-	KT81 (7C)	6/8	PEN4A	20/-	U14	7/8	VR105/30	6/8
5V4G	6/-	6F90	5/6	6R87GT	4/9	12BE6	6/3	30P4	22/6	ATP5	12/-	EAF42	10/-	EF86	6/8	KT88	24/-	PEN24	20/-	U19	35/-	VR105/30	6/8
5YGT	6/-	6F11	6/8	6R17GT	6/-	12C8GT	6/-	30P12	18/-	ATP7	8/6	EB41	10/-	EF89	5/8	KT88	24/-	PEN45	7/-	U25	15/6	VT25	16/-
6Z4G	7/-	6F13	6/8	6R37GT	5/8	12E1	20/-	30P19	15/-	AU2	8/0	EB91	3/-	EF91	8/8	KTW81	12/8	PEN46	4/-	U26	15/8	VT31	8/9
6/30L2	15/-	6F14	12/6	6R47	7/8	12J5GT	2/6	30PL1	16/-	AU5	8/9	EB33	8/8	EF92	2/6	KTZ41	6/-	PL36	10/9	U78	4/8	VT111	8/9
6A7	15/-	6F23	10/-	6U4GT	12/-	12J7GT	2/6	30PL13	18/6	AZ1	8/-	EB41	9/9	EF98	15/-	MLA	17/8	PL81	9/6	U91	13/9	VT120	12/6
6A80	12/8	6F24	14/-	6U6G	7/9	12K7GT	7/-	30PL14	15/-	AZ31	10/-	EB90	4/9	EF183	6/8	ML6	7/8	PL82	8/8	U251	10/8	VT508	55/-
6AC9	4/-	6F25	14/-	6V6G	4/8	12Q7GT	6/-	35A5	12/6	CBL31	16/-	EBF80	7/8	EF184	7/-	MSP4	10/8	PL83	7/8	U301	12/8	WB1M	13/6
6AK5	5/-	6F28	14/-	6V6G	4/8	12Q7GT	6/-	35L5	9/-	CCH35	15/-	EBF83	9/-	EL32	3/6	MU14	7/8	PL84	7/8	U403	6/8	XH1-5	5/-
6AM5	4/6	6F32	2/9	6V6GT	8/8	12R47	6/-	35W4	4/8	CL33	20/-	EBF89	6/8	EL33	12/6	MX40	12/6	PL500	14/6	U404	7/8	XPI-5	5/-
6AM6	3/6	6G6	3/8	6X4	4/8	12R67	6/-	35Z3	10/0	CV450	25/-	EBL1	14/-	EL34	10/8	N78	18/-	PL504	18/-	U801	23/6	XBG1-5	110/-
6AQ5	6/8	6H6	6/-	6X6G	4/8	12RH7	3/-	35Z4GT	8/8	CY30	12/6	EBL21	12/-	EL38	22/8	N108	25/-	PL508	29/-	U802	23/6	XBG1-5	110/-
6BR7G	10/8	6J5M	9/-	6X6GT	6/-	12R7	3/9	35Z5	9/-	CY31	8/6	EBL31	27/6	EL41	11/-	NGT1	8/8	PL509	29/-	UAF42	10/8	Tube	7/8
6A76	4/9	6J5G	4/-	7B6	11/8	12R87	4/8	37	6/6	DAC32	7/-	EC90	5/-	EL42	11/6	NGT7	55/-	PL802	16/6	UBC41	9/3	3EG1	65/-
6A76	5/-	6J6GT	5/8	7B7	7/8	12R87	5/-	42	6/-	DAF91	4/6	EC81	6/-	EL84	4/9	OA2	6/-	PX4	24/-	UBC81	9/3	3FP7	29/-
6B40	20/-	6J7C	22/8	14H7	9/6	12R87	5/8	50B5	6/8	DAF96	7/8	EC82	5/9	EL95	7/-	OC3	5/-	PX25	27/6	UBF80	7/6	6CP1	85/-
6BBG	2/-	6J7M	8/8	7C8	15/-	13AQ5	5/-	50C25	6/8	DC90	20/-	EC83	6/3	ELL80	20/-	OZ4	4/8	PY33	10/9	UBF89	7/6	CV1526	6/8
6BA5	5/-	6J7M	8/8	7D5	8/-	20D1	10/-	50CD6G	81/-	DF33	4/-	EC84	6/8	EM34	16/-	PC86	11/8	PY81	5/9	UC84	8/6	ACR131/100/-	7/8
6BE6	5/-	6J7GT	7/8	7H7	6/8	20P2	14/-	50L6GT	8/-	DF70	9/-	EC85	5/-	EM80	7/8	PC88	11/8	PY82	5/8	UC85	8/6	ACR131/100/-	7/8
6BH6	9/-	6K6GT	8/-	7R7	13/-	20L1	20/-	75	9/8	DF91	4/-	EC88	7/8	EM81	12/8	PC87	8/8	PY83	7/8	UCF80	8/6	VCR517B	46/-
6B76	9/-	6K7	1/8	787	45/-	20P4	20/-	78	5/-	DF92	7/8	EC89	6/8	EM84	7/8	PC88	8/6	PY500	18/6	UCH42	10/6	46/-	46/-
6BQ7A	7/-	6K7M	6/8	7Y4	3/8	20P5	20/-	80	7/8	DF96	3/8	ECF82	6/8	ESU150	20/-	PC89	10/6	PY500	29/-	UCH31	7/6	VCR517C	46/-
6BR7	17/-	6K7G	2/-	9BW6	7/-	25A6	5/9	86A2	7/8	DH77	4/9	ECR21	12/8	EY81	7/8	PC189	10/6	PY800	9/6	UCL82	7/6	46/-	46/-

Manufacturers and Export Inquiries Welcome
OBsolete TYPES A SPECIALTY
QUOTATIONS FOR ANY VALVE NOT LISTED
 Express postage 5d. per valve.
 Ordinary postage 6d. per valve. C.W.O. No C.O.D.
 Tube postage 10/- each
Special Express Mail Order Service

VALVES & TRANSISTORS

2G4V4	6/0	AC128	4/8	AF118	12/-	AO10	3/-	OC36	8/8	OC77	8/-	OC122	12/6
2N1305	5/-	AC176	6/2	BC108	3/6	AO200	2/-	OC58	12/6	OC81	4/-	OC141	12/3
2N2147	16/8	AC1Y8	4/-	BC109	3/8	AO202	2/-	OC59	17/6	OC81D	3/-	OC109	6/6
2N2398A	6/3	AC1Y27	6/-	BFV61	6/-	OA2242	4/8	OC70	3/6	OC81DM	3/-	OC170	5/6
2N2898	6/3	AC1Y28	4/-	BFV60	12/8	OA2246	4/8	OC71	3/6	OC81M	5/-	OC171	6/6
2N2926	3/6	AC1Y39	12/6	BY100	4/8	OC16	15/0	OC72	4/-	OC82	3/-	OC172	7/6
2N3705	4/-	AD149	12/-	GET114	4/-	OC19	8/6	OC73	7/3	OC82D	3/-	OC200	6/6
2N3819	8/-	AD161	7/8	GJ7M	6/8	OC20	20/-	OC74	4/6	OC83	4/6	OC201	8/6
AO107	5/6	AD162	7/-	NKT274	4/9	OC28	12/6	OC75	4/6	OC84	4/9	OC202	8/6
AC127	5/-	AF117	4/6	NKT113	7/8	OC35	6/3	OC76	3/6	OC114	7/6	OC203	6/6

SEND S.A.E. FOR LIST OF 3,000 TYPES

H.A.C. Electronic Kits

DID YOU KNOW?

That we have specialized in the supply of kits for the Amateur Constructor for over 35 years. (Established 1934.)

That we now have available a full range of Complete transistor kits with comprehensive instruction manual, for constructing—Radios—Resistance Bridge—Lightmeter—Electronic Counter—Voltmeter—80 metre Converter, etc. etc. (Details for 40 different electronic circuits are available.) Complete kits from 54/-. Fully guaranteed. Illustrated brochure upon application, send S.A.E. please.

H.A.C. Products, 29 Old Bond Street, London W.1.



SWOP your camera or hi fi for a TRIO

TRIO JR-500-SE
 Crystal controlled 1Kc Divisions—very stable £69.10.0. Carriage free. Full twelve month guarantee.

TRIO 9R-DE
 500 Kc/s to 30 Mc/s. Full ham band spread—free voltage stabilizer supplied

S.W. Receiver at **HOLDINGS PHOTO-AUDIO Mincing Lane/Darwen St. BLACKBURN**
 Tel: 59595 Closed Thurs.

SYLVANIA CIRCUIT BREAKERS gas filled providing a fast thermal response between 80° Will withstand pressures up to 2,000 lb. sq.in. rated 10 amp. at 240v. continuous. Fault current of 25 amps. at 120v. or 13 amp. at 240v. silver contacts. Supplied in any of the following opening temperatures (deg. cent.) 80, 85, 95, 100, 105, 110, 120, 125, 130, 135, 140, 145, 150, 155, 160, 170, 175, 10/- each or £4.10.0 per dozen.

MINIATURE "LATCHMASTER" RELAY 6, 12, or 24v. DC operation. One make one break, contacts rated 5 amps. at 30v. Once current is applied, relay remains latched until input polarity is reversed. Manufactured for high acceleration requirements by Sperry Gyroscope Co. Size: length 1/2 in. dia. 1/8 in (including mount). Please state vertical or horizontal mount and voltage, £2.5.0 each.

SYLVANIA MAGNETIC SWITCH—a magnetically activated switch operating in a vacuum. Switch speed—5ms. Temperature—54 to +200° C. Silver contacts normally closed rated 3 amps. at 120v. 1.5 amp. at 240v. 10/- each. £4.10.0 per dozen. Special quotations for 100 or over. Reference Magnets available 1/6 each.

"Knowles" (U.S.A.) Sub-Miniature Moving Coil Microphone Capsule. Type 1501: as used in miniature hearing-aids, bugging devices, etc. Size: 7/8" sq. x 1/4" thick. All tested, 20/- each. Also "Knowles" moving-coil sub.min. car transducers type 1630. Size: 7/8" x 1/2" x 1/4" thick, 15/- each.

"Welwyn" Resistors Type H12. One value only. 1 kilo-meg ± 20%. 5/- each. P. & P. 9d.

Tansitor (U.S.A.) Tantalum, Wet Sintered Anode Polarised Capacitors: 200 UF. 25v. D.C. size: 1/2 in. long x 1/4 in. dia. UF. 24v. D.C. size: 1/2 in. long x 1/4 in. dia. 150 UF. 30v. D.C. 1/2 in. long x 1/4 in. dia. 33UF. 75v. D.C. size: 1/2 in. long x 9/32 in. dia. One wire each end. All types 5/- each. Also few only Transistor "MICRO-MODULE" capacitors 0.2 Mfd. 15v. wire-ended, size: 3/32 in. dia (disc) 5/- each.

Ernest Turner 5in. x 4in. 0-1 Ma. Meters calibrated 0-10 in 50 divisions mirrored scale, handsome chrome escutcheon for flush mounting. A quality instrument. £6.10.0.

New 75-0-75 Micro-ammeter by Siltam. 750 ohm movement, clear reading, 50s divisions x 1/2 in.; plastic front, projection 1/2 in. (tapering forward). Size: 4 1/2 in. x 3 1/2 in. 5/8 each.

Welwyn high value Resistors Type GA 38501. Values between 9.4 and 10.9 kilo-meg ± 1%, glass encapsulated 15/-.

"Welwyn" Resistors Type H12. 1 value only. 1 kilo-meg ± 20%. 10/- per pair.

Isolation Transformers by Majestic Winding Company. 1 to 1 ratio, 240v. input 240v. centre tapped out, at 2 K.V.A., mounted in metal case measuring 8 1/2 in. x 8 1/2 in. x 1 1/2 in. high. Weight 65lbs. £16.10.0, carr. £1.10.0.

New "Magnetic Devices" Solenoid. 240V A.C. Type 42117. 1 to 3lb. pull, frame size: 1 1/2" x 1 1/2" x 1". 20/- each.

New "F.I.R.E." Plug-in Relay. 115V Coil 50/60 C.P.S. 3 heavy duty silver change-over contacts, perspex cover, very robust. 17/6 each.

New Diamond "H" 240V A.C. Relay. 3 heavy duty silver change-over contacts. 17/6 each.

New "Carter Electric" 12 r.p.m. Motor. Non-reversible 4" spindle. 240V A.C. open frame with cast aluminium cased gearbox. Stably constructed, approx. 20 lbs/in. overall size (approx.): 3" x 3" x 4" plus spindle. 45/- P. & P. 5/-.

ELECTRO-TECH. SALES 264 PENTONVILLE ROAD, LONDON, N.1

Where no carriage charge is indicated price is inclusive. Personal callers welcome. 9.30—6.0 p.m. 1 p.m. Sats. ONE MIN. FROM KINGS X STATION) Tel. 91-837 7441



LIND-AIR AUDIO

BATTERY ELIMINATOR



Enables transistor equipment to be operated from AC mains. 6/9/12v. output selector switch and complete with mains lead, connecting leads and instructions.

59/6 P. & P. 3/6.

on/off switch. Case size 4 1/2 x 2 1/2 x 2 1/2 in.

HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY

J1001 3"	L.P. PVC	225ft.	5/6	P & P 1/2
J1002 3"	T.P. Poly	600ft.	10/6	P & P 1/2
J1003 3"	L.P. PVC	900ft.	10/6	P & P 1/8
J1004 5"	D.P. Poly	1200ft.	15/-	P & P 1/8
J1005 5"	L.P. PVC	1200ft.	12/6	P & P 2/-
J1006 5"	D.P. Poly	1800ft.	22/6	P & P 2/-
J1007 7"	S.P. PVC	1200ft.	12/6	P & P 2/6
J1008 7"	L.P. PVC	1800ft.	17/6	P & P 2/6
J1009 7"	D.P. Poly	2400ft.	25/-	P & P 2/6
J1010 7"	T.P. Poly	3600ft.	50/-	P & P 2/6
C50 Cassette (Library cased)			8/6	P & P 1/8
C90 Cassette (Library cased)			13/-	P & P 1/8
C120 Cassette (Library cased)			18/-	P & P 1/8



DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug.

59/6 P. & P. 3/6.

VHF AIRCRAFT BAND CONVERTOR

When placed within line of a MW band radio full coverage of VHF Aircraft Band 108-135 Mc/s. can be obtained. All transistor. 9v battery operation. Fully tunable 18in x 7 section telescopic aerial. Size 4 x 2 1/2 x 1 1/2 in.



79/6 P. & P. 3/6.

C.1001 MULTI-TESTER




Overload protection. 20,000 opv. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-60K, 0-6 Meg ohm. Decibels -20 to +22dB. Size of meter 4 1/2 x 3 1/2 in. Complete with leather case.

85/- P. & P. 3/6.

LIND-AIR LA.20

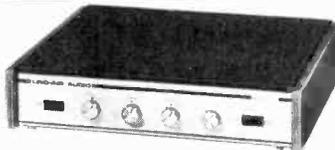A fantastic Stereo amplifier made exclusively for Lind-Air and represents considerable advance in solid state stereo amplifiers. Inputs for gram and radio tuner and provision for direct tape recording. Attractive and modern front panel with Bass, Treble, Balance and Volume Controls also on/off and stereo/mono switch. Output 5 watts per channel music power. Size 16 1/2 x 14 x 4 1/2 in.




LIND-AIR PRICE £24 10/- P & P

62 D. MULTI-TESTER

20,000 p.p.v. DC voltage 5-25-50-250-500-2.5 K (20,000 ohms per volt). AC voltage 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50 uA, 0-2.5 mA, 0-250 mA. Resistance: 0-6K, 0-6 Mg (300 ohm and 30K at centre scale). Capacitance: 10f to 0.01 mfd. 0.01 uF to 1 uF. Decibels -20 to +22dB. Size 4 1/2 x 3 1/2 in.

71/- P. & P. 3/6.

SINCLAIR PROJECT 60

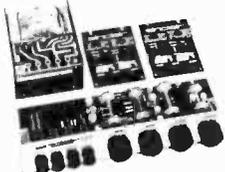

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. Z.30 24 watt Power Amplifier 89/6 (2 required). Stereo Sixty Control/Pre-amplifier £9.19.6. PZ.5 Power Supply Unit £4.19.6.

SINCLAIR PROJECT 60 Package deal price 19 Gns. P. & P. 12/6. Project 60 is supplied complete with instruction manual and templates for plinth mounting.

SINCLAIR IC-10 INTEGRATED CIRCUIT 10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years.

ONLY 59/6 P. & P. 1/6. SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250v. Output 13v. at 0.5 amp. 16/6 P. & P. 2/6.

WHARFEDALE SPEAKER KITS



Complete with all components for building into suitable cabinets.

Unit 3 Kit £11.99.8 each £21 per pair
Unit 4 Kit £16.0.0 each 28gns. per pair
Unit 5 Kit £23.10.0 each 38gns. per pair
P. & P. 10/- each 15/- pair

TELETON SAQ203 TRANSISTOR STEREO AMPLIFIER



Superb quality hi-fi. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal). Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble. Attractive oil/walnut cabinet and brushed aluminium front panel. List Price £28.7.0

LIND-AIR PRICE

22 Gns.

P. & P. 10/-.

SAVE ON AKAI!



AKAI 4000 Stereo Tape Recorder List Price £124.18.0 (as illus.)

OUR PRICE 99 Gns. Carr 30/-

AKAI 4000D STEREO TAPE DECK List Price £89.19.1

OUR PRICE 69 Gns. Carr 30/-

SPECIAL LIND-AIR OFFER!



ROTEL 100 AMP STEREO AMPLIFIER. Fully transistorised with all facilities for the home hi-fi system. List price £45

LIND-AIR PRICE

£37.10.0.

Carr. 10/-

TRANSISTOR MODULES

E.1311 PHONO PRE-AMPLIFIER. Size 2 x 3 1/2 in. Built-in R.I.A.A. characteristics enabling low output magnetic pickup cartridges to be amplified up to 1 volt. Input 100K ohm; Gain 28dB. Max. output 3v.

Max. input 50mV. Distortion 0.15% (at 1v level). Power supply 9-12v. 29/8. P. & P. 2/-.

E.1315 ELECTRONIC ORGAN TONE OSCILLATOR. Used in conjunction with an organ keyboard, variable resistances and a 9 volt power supply, this module acts as the oscillator unit for an electronic organ. Tone Frequency: 200-1,000Hz; Output 80mV; Current 15mA. 25/- P. & P. 2/-.

E.1316 MORSE CODE OSCILLATOR. A transistorised morse code oscillator (buzzer) to be used in conjunction with an operating key. Suitable for direct connection to a loudspeaker. Tone frequency 400Hz; Power output 80mV; Power supply 3-9v. Current 45mA. 25/- P. & P. 2/-.

GARRARD HI-FI TURNTABLES



2095 T/C with stereo cartridge... £8.19.6
3000 with Sonotone... £10.19.6
9TAHCD stereo cartridge... £10.19.6
SP25 Mk II... £15.19.6
SL55B... £15.19.6
Base and cover for above... £18.10.0
AP75... £18.10.0
SL72B... £24.19.6
SL75B... £28.7.0
SL95B... £39.8.0
£28.10.0
401... £39.19.6
Base and cover for above... £39.19.6
P. & P. Decks 12/6. Base & Cover 10/- Deck/Base/Cover 17/6.
SPECIAL OFFERS!
SP25 MkII with base £14.10.0. P. & P. 15/-
SP25 Mk II with Sonotone 9TAHCD cartridge and base £15.15.0. P. & P. 15/-
Sonotone 9TAHCD cartridge £2.15.0 P. & P. 1/6.

18/19,25 & 53 TOTTENHAM CT. ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679

Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

All Mail Orders and correspondence to Dept L5/7, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.

R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

★ Super 30 Amplifier (15 + 15 watt) in veneered housing
 ★ Goldring Transcription Turntable on Plinth
 ★ Shure or Goldring Magnetic Pick-up Cartridge
 ★ Pair of Stanway II Loudspeaker Units
 Special total price. Four fully wired units ready to "plug-in". Carr. 30/-.
86 Gns.
 TA12 Amplifier (6.5 + 6.5 watt) in veneered housing. Garrard 3000 4 sp. Autochanger unit on plinth. Sonotone RTA P.U. cartridge. Pair of Dorchester Loudspeaker units.
 Special Total Price **47½ Gns.** Carr. 25/-

Matching as recommended for optimum performance. Send for coloured brochure showing other money-saving offers.

Package prices apply provided all individual units are purchased from any branch within 3 months. See leaflet.



EXTREMELY ATTRACTIVE PLINTHS finished in Teak or Afrormosia veneer. Trans plastic cover.

★ Super 30 amplifier (15 + 15 watt) in veneered housing
 ★ Garrard SP25 Mk II Turntable on Plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus
 ★ Pair Stanway II Speaker Units
 Four fully wired units ready to "plug-in". Special total price **76 Gns.** Carr. 30/-

★ TA12 Amplifier (6.5 + 6.5 watt) in veneered housing
 ★ Garrard SP25 Mk II 4 sp. player unit on plinth
 ★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus
 ★ Pair of Dorchester Loudspeaker Units.
 Special total price Carr. 25/- (Total 59 gns.). Transparent plastic cover 3 gns. extra.

TERMS AVAILABLE ALL PACKAGE OFFERS

AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. "L" indicates Roll Rubber cone surround. Impedance 3 or 15 ohms. Please state choice. Exceptional performance at low cost.

HF510L 5"	10W	49/9	HF120 12"	15W	79/9
HF801D 8"	8W	54/3	HF120D 12"	15W	89/9
HF102D 10"	10W	67/11	HF126 12"	15W	£5.50
HF100D 10"	15W	£4.19.9	HF126D 12"	15W	£5.15.0
HF105DL 10"	10W	£4.9s.			

HIGH FIDELITY LOUSPEAKER UNITS
 Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. credit terms available.

DORCHESTER Size 16 x 11 x 9in. approx. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13x8in. Dual Cone spkr. Imp. 3 or 15 ohms. **£8.19.9**

STANWAY II Size 20x10x9in. approx. Rating 10 watts. Inc. Fane 13x8in. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet.

High flux tweeter. Handmade Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.**

R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -5dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-16 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case. 8x12x5in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **7 Gns.** Carr. 7/6

Or factory built with 12 months' guarantee. **£8.19.9**

RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amplifier or Tape recorder.

RP2C Garrard SP25 Mk II fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. Carr. 9/6 **23 Gns.**

RP5C Garrard 2025 Auto Unit fitted Garrard GCS 23 Stereo Cartridge with diamond tip. Plinth & Cover as RP2C Carr. 9/6 **15 Gns.**
 Other types available with Magnetic cartridges and with alternative design plinths.

Limited Number of CLEARANCE LINES in leading makes of Hi-Fi equipment at Branches only

R.S.C. PLINTHS

for Record playing units, cut for Garrard 1025, 2025, 3000, A.T60, SP25 etc. **3 gns.** Carr. free

Available with trans. plastic cover. Carr. free

INTEREST CHARGES REFUNDED

On Credit Sales settled in 3 months.

LINEAR L10 HIGH FIDELITY LOW AMPLIFIER 10 Gns.

with separate Pre-amp Magnetic P.U. matching. To clear

R.S.C. TA12 MKII 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL
 Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 30-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 300mV (2) 50mV (3) 100mV (4) 2mV. Output rating I.H.F.M. ★ Handsome brushed silver finish Facia and Knobs. Complete kit of parts with full wiring diagrams & instructions. Factory built with 12 mth gntee 17 Gns or Deposit £5.2.6 and 9 mthly pymnt 34/- (Total £20.8.8). Or in Teak or Afrormosia veneer housing 20½ Gns. Dep. £5.10.6 and 9 monthly payments £2.1.7 (Total £24.4.9).



AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure unsurprisingly realistic reproduction. **£5.15.0**
 Or Senior 15 Watt inc. HF126 15,000 line Speaker £6.15.0. Carr. 6/6 Carr. 5/9

HI-FI SPEAKER ENCLOSURES

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 5/- per enclosure
JES Size 16 x 11 x 8in. Pressurised. Gives **£4.14.6** pleasing results with any 8in. Hi-Fi speaker.
SEB For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 8in. Ported. **£5.15.0**
SE10 For outstanding results **SE12** For excel prnce with 12in. with 10in. Hi-Fi 'spkr Hi-Fi speaker and Tweeter. **£6.19.9**
 Size 24x15x10in. P'd. **£5.19.9** Size 25 x 16 x 10 1/2 in.

THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25x14x10in. COMPLETE KIT **20 Gns**
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms Carr. 12/6
 ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £5.10.6 and 9 monthly payments 30/- (Total £23.1.0).
 DEMONSTRATIONS AT ALL BRANCHES

R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

★ 200-250v. A.C. Mains operation. ★ High-sensitivity. ★ Sharp A.M. Rejection ★ Drift-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. Printed circuitry. A quality product at considerably less than the cost of comparable units. Factory built 16 Gns. Or in Teak finished cabinet as illustrated 21 gns. Terms: Deposit £6.1.0 and 9 monthly payments 2 gns. Total £24.19.0. Stereo version. 23 gns. Carr. 10/6 extra

R.S.C. SUPER 30 MKII HIGH FIDELITY STEREO AMPLIFIER

High Grade Components
 Specifications comparable with units costing considerably more.

TRANSISTORS 9 high quality types in each channel.
 OUTPUT 10 Watts R.M.S. continuous into 15 Ω (per channel). 15 Watts R.M.S. continuous into 3 Ω.

INPUT SENSITIVITIES Mag. P.U. 4 mV. Ceramic P.U. 36 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5 mV.
 FREQUENCY RESPONSE ± 2 dB. 10-20,000 c.p.s.

TREBLE CONTROL +17 dB to -14 dB at 10 Kc/s.
 BASS CONTROL +17 dB to -15 dB at 50 c/s.
 HUM LEVEL -80 dB.
 HARMONIC DISTORTION 0.1% at 10 watts 1,000 c.p.s.



Employing Twin Printed Circuits. 200/250v. A.C. mains operation. **CROSS TALK** 52 dB at 1,000 c.p.s.
CONTROLS 5 Position Input Selector. Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.
INPUT SOCKETS (1) P.U. (2) Tape Amp. (3) Radio, (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).
CHASSIS Strong Steel construction. Approx. 12 x 3 x 8in.

FACIA PLATE Attractive design in rigid plastic silver background black lettering. Silver finish matching control knobs as available.
 Eminently suitable for use with any make of pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first rate ancillary equipment.

COMPLETE KIT OF PARTS
 Point to point wiring diagrams **22 gns.** and detailed instructions. Carr. 15/-
UNIT FACTORY BUILT **29 gns.**
 With 12 months guarantee. Or Deposit £7.5.0 and 9 monthly payments 58/9 (Total £33.18.9) or in Teak or Afrormosia veneer housing 32 Gns. Carr. 15/- Terms: Deposit £7.3.8 and 9 monthly payments of 60/8 (Total £37.2.0). Send S.A.E. for leaflet.

R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BM1 An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx.
 Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s. is available. Complete kit with diagram 62/8 or assembled 3 Gns.

SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER

Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. **12½ gns.** Carr. 12/6
 OR FACTORY BUILT 15½ Gns. Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments 31/1 (Total £18.3.0). Available in Teak or Afrormosia veneered housing. 19gns.

PARTRIDGE "JOYSTICK" SHORT WAVE AERIALS AND TUNERS AT ALL BRANCHES (S.A.E. for full list)


- BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL** (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM** 30/31 Gs. Western Arcade 021-236-1279 (Half-day Wed.)
- DERBY** 26 Osaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: 102 Henconner Lane, Bramley, Leeds 13. NO C.O.D. under £1. Terms C.W. or C.O.D. Postage 4/6 extra under £2. 5/6 extra under £5. Trade supplied. S.A.E. with enquiries.
 Branches open all day Sats.
MAIL ORDERS MUST NOT BE SENT TO SHOPS

- 32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252 **LEEDS**
- 73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 **LIVERPOOL**
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. PAD 1629 **LONDON**
- 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 **MANCHESTER**
- 106 Newport Rd. (Half-day Wed.) Tel. 47096 **MIDDLESBROUGH**
- 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
- 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

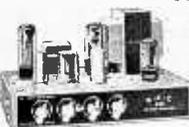R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive. Push-Pull high output, with Pre-amp. Tone Control Stages. Performance figures of factory built units: Hum level -70dB. Frequency response $\pm 3dB$ 30-20,000c/s. Sectionally wound output transformer. All high grade components. Valves 12X6, 6X8, 6X3, 607, 607, 6Z34. Separate Bass and Treble Controls. Sensitivity 36mV. Suitable for high impedance microphones. Crystal or Ceramic P.U.s. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitars, Strings Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mikes" can be mixed. 200-250v. 50c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. **15 Gns.** Carr. 12/6

Twin-handled perforated cover 35/-. Supplied factory built with EL34 output valves. 12 months' guarantee for 18 gns. **TERMS:** Deposit £8.3.0 and 9 monthly payments of 34/- (Total £21.9.0). Send S.A.E. for leaflet.


R.S.C. All High Fidelity 12-14 WATT AMPLIFIER



PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with mixing facilities High sensitivity, 5 valves. Independent Bass and Treble controls. Frequency response $\pm 3dB$ 30-20,000 c/s. Hum level -60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments etc. Std. A.C. mains. For 3 & 15 ohm spkrs. **9 1/2 Gns.** SAE for leaflet. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 11/6. Twin handled metal cover 35/-. Price Factory built 18 1/2 gns. or Deposit 99/6 and 9 monthly payments of 26/- (Total £18.13.6).

ESG ALL TRANSISTORISED VERSION of above complete kit 9 Gns. (Assembled 13 Gns.)

30 WATT HI-FI AMPLIFIER

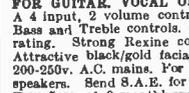

FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP A 4 input, 2 volume control Hi-Fi unit with Separate Bass and Treble controls. B.V.A. valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold facia panel. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm **19 Gns.** Carr. 12/6 speakers. Send S.A.E. for leaflet. Dep. 5 gns. & 9 monthly payments of 39/8 (Total 22 gns)

FANE ULTRA HIGH POWER LOUDSPEAKERS



All power ratings are R.M.S. continuous. 2 years' guarantee. High flux ceramic magnets. Heavy cast chassis. All prices carr. free

'POP' 100 18" 100 Watt 14,500 gauss 21 GNS. 8/15D	'POP' 60 15" 60 Watt 14,000 gauss 12 GNS. 8/15D	'POP' 50 12" 50 Watt 14,000 gauss 10 GNS. 15D
--	--	--

F.A.L. P.A. AMPLIFIERS PHASE 50 **29 GNS.** PHASE 100 **59 GNS.** S.A.E. for leaflets.

R.S.C. COLUMN SPEAKERS



Covered in Rexine and Vynair, ideal for vocalists and Public Address. 15 ohm matching.

TYPE C485 25/30 WATTS. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 48 x 10 x 5in.

16 Gns. Carr. 10/-
Or deposit 87/- and 9 monthly payments 24/9 (Total £18.19.9).

TYPE C4125 50 WATTS. Fitted four 12in. 11,000 line 15 watt speakers. Overall size 56 x 14 x 9in. approx.

26 Gns. Carr. 15/-
Or Deposit £5.17.6 and 9 monthly payments of 54/6 (Total £20.7.0)

HIGH QUALITY LOUDSPEAKERS

In Teak or Alrotrmosia veneered Cabinets

L13 13" x 8" 8-10 Watt
10,000 lines 3 or 15 ohms. **£4-19-9** Carr. 7/6

Type L12 12" 20 Watt
10,000 lines 15 ohms. **£8-19-9** Carr. 8/9

R.S.C. BASS-REGENT 50 WATT AMPLIFIER



A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating.

* Two extra heavy duty 12in. Loudspeakers. * Four Jack inputs and Two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls.

55 Gns. Carr. 30/- or dep. £13.4.9 and 9 monthly payments of 25.11.9. (Total 60 1/2 gns.). Send S.A.E. for leaflet.


G100 100 watt peak output with Fr. speaker columns and a Bass Unit (8ix 12" and Two 15" Speakers). 99 1/2 gns.

R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primarys 200-250v. 50c/s. Screened MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.

250v. 60mA, 6.3v. 2a.	17/11
250-0-250v. 60mA, 6.3v. 2a.	18/11
FULLY SHEROUDED UPRIGHT MOUNTING	
250-0-250v. 80mA, 6.3v. 2a. 0-5-6.3v. 2a.	24/9
250-0-250v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a.	39/9
300-0-300v. 100mA, 6.3v. 4a. 0-5-6.3v. 2a.	39/9
300-0-300v. 130mA, 6.3v. 4a. c.t. 6.3v. 1a.	47/11
For Mullard 510 Amplifier	47/11
350-0-350v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a.	39/9
350-0-350v. 150mA, 6.3v. 4a. 0-5-6.3v. 3a.	47/9
425-0-425v. 200mA, 6.3v. 4a. c.t. 5v. 3a.	89/9
425-0-425v. 200mA, 6.3v. 4a. 6.3v. 3a., 5v. 3a.	93/9
450-0-450v. 250mA, 6.3v. 4a. c.t. 6.3v. 3a.	99/9
TOP SHEROUDED DROP-THRO' TYPE	
250-0-250v. 70mA, 6.3v. 2a. 0-5-6.3v. 2a.	23/9
250-0-250v. 100mA, 6.3v. 3.5a.	27/9
250-0-250v. 100mA, 6.3v. 2a. 6.3v. 1a.	28/9
300-0-300v. 80mA, 6.3v. 2a. 0-5-6.3v. 2a.	39/9
300-0-300v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a.	39/9
300-0-300v. 130mA, 6.3v. 4a. 0-5-6.3v. 1a.	46/9
Suitable for Mullard 510 Amplifier	46/9
350-0-350v. 100mA, 6.3v. 4a. 0-5-6.3v. 3a.	39/9
350-0-350v. 150mA, 6.3v. 4a. 0-5-6.3v. 2a.	39/11
FILAMENT or TRANSISTOR POWER PACK	
Type 6.3v. 1.5a. 8/8; 6.3v. 2a. 9/8; 6.3v. 3a. 13/9;	13/9
6.3v. 6a. 22/9; 12v. 1a. 9/11; 12v. 3a. or 24v. 1.5a. 22/9; 0.9-18v. 1 1/2a. 19/11; 0-12-25-42v. 2a. 31/9	31/9
CHARGER TRANSFORMERS 0.9-18v. 1 1/2a. 18/9;	
2 1/2a. 19/11; 5a. 21/11; 6a. 25/11; 8a. 29/9; 9a. 36/9	36/9
AUTO (Step UP) DOWN TRANSFORMERS	
0-110/120v. 200-250-250v. 50-80 watts 19/9;	19/9
150 watts, 33/6 250 watts 49/9; 500 watts 105/-	105/-
OUTPUT TRANSFORMERS	
Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω	8/9
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω	14/9
Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8, 15 Ω	24/9
Push-Pull EL84 to 3 or 15 Ω 10-12 watts	23/9
Push-Pull Ultra Linear for Mullard 510, etc.	39/9
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω	35/9
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω 59/9	59/9
SMOOTHING CHOKES 150mA, 7-10H. 250 Ω 12/9; 100mA, 10H, 200 Ω 10/9; 80mA, 10H, 350 Ω 8/9; 60mA, 10H, 400 Ω 4/11.	
SELENIUM RECTIFIERS F. W. (Bridged)	
All 6/12v. D.C. output, Max. A.C. input 18v. 1a. 4/3. 2a. 6/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.	15/9

YOUR FREE 7 DAYS

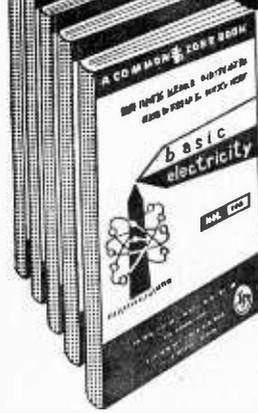

The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOL.) ELECTRONICS (6 VOL.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

WHAT READERS SAY

'Everything is clearly set out . . .'
 . . . I am well pleased with this pictorial system. Everything is clearly set out in diagrams, . . . L.P., Co. Armagh.

' . . . very pleased with the set . . .'
 . . . I was very pleased with the set of Basic Electronics. Please send Basic Electricity . . . D.W., Margate.

' . . . how understandable your books are . . .'
 . . . Pleased to say how understandable your books are, I now have a sound knowledge of the subject . . . A.A., Hull.

A TECH-PRESS PUBLICATION

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY 75/-** Cash Price, or Down Payment of 20/- followed by 3 fortnightly payments of 20/- each. **BASIC ELECTRONICS 90/-** Cash Price, or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY **BASIC ELECTRONICS**

Prices include Postage and Packing.

Signature _____
 (If under 21 signature required of parent or guardian)

NAME _____
 BLOCK LETTERS

FULL POSTAL ADDRESS _____

POST NOW FOR THIS OFFER!!

BRAND NEW AR88D COMMUNICATIONS RECEIVERS. AC mains input 110 volts or 250 volts. Frequency in 6 bands 535 kc/s up to 32 megs, output impedance 2.5-600 ohms. Complete with crystal filter noise limiter B.F.O. HF tone controls. Price £80 including spare set of valves, headphones and manual.

MARCONI CR 150/2 DOUBLE CONVERSION SHORT WAVE RECEIVERS, frequency 1.5-22 mc/s. Features are as follows: Fitted 's' meter, geared tuning with no backlash, 2 speed motion, slide rule dial, calibrated in M/Cs, logging scales for accuracy. 500 Kc/s Xtal Calibrator, mechanical bandspread. Technical description, 1st IF is 1.6 Mc/s, 2nd IF 465 with Xtal filter giving a passband from 100 c.p.s. to 10,000 c.p.s. BFO Variable 3-0-3 Kc/s. Rectified IFO/p, DF input, suit teleprinter o/p; output 600 ohms and 3 ohms for LS. Front end has 2 R.F stages of amplification giving a sensitivity of 2-4 μ v depending on band in use. Separate mixer/oscillator. 2nd oscillator is also variable 5-0-5 Kc/s bandspread. A separate power supply is needed to power the above set at 300v at 100 mA and 6.3v 4 amps Lt. AC/DC circuit connection supplied to purchasers of this very fine receiver. These RXs are not new but are in quite good condition and tested on despatch. Unrepeatable offer. Circuit supplied. Price £22.10.0 plus 30/- p.p.

R209 RECEIVER AM/CW/FM 1-20 Mc/s 6 bands, Vernier tuning, 12 volt DC input. Tested and working.

Price £13.10.0 plus £1 p.p.

COMPUTER BOARDS Min 30 transistors and diodes and res. etc. 10 boards at 10/- plus 2/6 p.p.; 25 boards at 22/6 plus 4/6 p.p.

AERIALS new condition, extending to 11 ft. fully open; whip type: 12/6 each plus 3/6 p.p. Whip aerials, 12ft. collapsible type; used condition: 10/- each plus 3/6 p.p. Bases for above 5/- each plus 2/6 p.p.

BARGAIN PARCELS 14lb at 29/- plus 6/6 p.p.; 28lb at 55/- plus 12/6 p.p.; 56lb at 90/- plus 25/- p.p. Contain pots, Res, Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save ££s. Lucky Dip Service.

FURZHILL BEAT FREQUENCY OSCILLATOR 0-10 kc/s, 110/250 volt. Good condition complete with spares.

£5.10.0 plus 25/- p.p.

VHF Receiver, Type 715, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested; complete with valves and speaker.

£3.0.0 plus £1 p.p.

VIBRATOR POWER SUPPLY TYPE 69 by BCC for 69T/R. Small compact 12V input gives 250V DC at 80mA and 12V output. Good condition.

25/- plus 7/6 p.p.

MOBILE POWER UNITS by PYE for the C12 T/R. Power output is 400V DC at 140mA and 300V DC at 100 mA. Good condition.

£3.10.0 plus £1 p.p.

INSULATION TESTERS. Bench and fieldwork; speed clutch, new condition, complete with leather case; 500V. 500 megohms.

£20.0.0 plus 12/6 p.p.

Also 1000V 1000 megohms with case. £23.0.0 plus 12/6 p.p.

CRYSTALS AS NEW: Hc 6u, 5,345; 5,055; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s and 10 x J465 Kc/s.

10/- each plus 1/6 p.p.

METERS MOVING COIL EX-EQUIPMENT. Good condition; all from 30mA, 50mA, 100mA, 500mA. All 2-in. round.

10/- each plus 5/- p.p.

From 15 amp D.C., 20 amp D.C., 40 amp D.C. All 2in. round.

10/- each plus 5/- p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS. 10% tolerance $\frac{1}{2}$ & $\frac{1}{4}$ watt. Preferred values in packets of 10. Our price 10/- per 100, 19/- per 200, 27/- per 300, 50/- at 42/6. Our selection. p.p. 1/6 per 100 and 6d. per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. airspaced trimmers on board with min. wire ended Xtal. Brand new. No details; Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice.

Trimmers without Xtal — 12/- per doz. plus 3/6 p.p.

Trimmers with Xtal — 15/- per doz. plus 3/6 p.p. Also 20 PF min. brand new air spaced.

10/- per doz. plus 3/6 p.p.

SIGNAL GENERATORS OSCILLATOR No. 2. Size 12in. x 8 1/2in. x 9in. Ideal for VHF work. 20-80 Mc/s. Functions are AM/CW. Deviation up to 40 Kc/s RF meter. Measuring levels: RF output 1 microvolt to 100 microvolts set. Mod-set carrier controls. Good condition with accessories; 230V AC 12V DC.

£20.0.0 plus 15/- p.p.

TF 144 G Signal Generators 85 Kc/s to 25 Mc/s. Good condition and complete with accessories.

£22.0.0 plus 30/- p.p.

RF Thermo Couple Meters. New and boxed. 0-1 amp, 2in. diameter.

17/6 plus 4/- p.p.

MAINS MOTOR, 250 volt AC; 1/40th H.P. at 1,500 R.P.M. Ex WD type; Size 6in x 4in. Tested and in good condition.

35/- plus 7/6 p.p.

TELESCOPIC MASTS. New condition, 20ft closes to 5ft 9in 90/-, carriage 15/-; 34ft closes to 5ft 9in 120/-, carr. 15/-. Used condition, 20ft 70/-, 34ft 80/-, carr. 15/-. Base for same 20/-, carr. 7/6.

A. H. THACKER,

Radio Dept.,
HIGH STREET, CHESLYN HAY,
Nr. Walsall, Staffs.

BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board—
obtainable from your local Retailer

Trade enquiries to
NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1
Technical enquiries to
VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants

A GUIDE TO AMATEUR RADIO

By Pat Hawker, G3VA

Fourteenth edition. 100 pages.

The new edition of this indispensable aid to all who want to know more about amateur radio. Designed to assist the newcomer to this unique hobby. Revised and expanded.

8s 10d post paid

RADIO COMMUNICATION HANDBOOK

over

20,000

copies sold

Now in its
second printing

Radio Communication Handbook

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. The standard work in its field.

69s post paid

THE VHF-UHF MANUAL

By George Jessop, G6JP

A complete manual for frequencies above 30 MHz. Covers aerials, receivers, transmitters and test equipment. The first book of its kind outside the USA.

23s post paid

Obtainable from:

RADIO SOCIETY of GREAT BRITAIN
35 DOUGHTY STREET, LONDON, WC1

FREE LIST!
SEND S.A.E.
FOR BUNGER FLOG
LIST

TECHNICAL TRADING

**BARGAIN SPRING
SALES AT ALL
BRANCHES**

★ LONDON (MUS 2639)
10 Tottenham Court Road
★ PORTSMOUTH (Tel. 22034)
368-362 Fratton Road
★ SOUTHAMPTON
72 East Street (Tel. 25851)
★ BRIGHTON (Tel. 23975)
8 Queen's Road

FANTASTICALLY POPULAR

★ JASON TAPE ★

We offer you fully tensiled polyester mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics at top grade prices. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports TRY ONE AND PROVE IT YOURSELF.

Standard Play		Long Play	
3in. 1,50ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 1/2in. 900ft.	10/6	5 1/2in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,800ft.	25/-
5in. 1,200ft.	15/-	5 1/2in. 2,400ft.	34/-
5 1/2in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,100ft.	27/-	Quadraple Play	
		3in. 600ft.	8/6

Postages U- reel.
Post Free less 5% on three reels.
Quantity and Trade enquiries invited.

All mail orders to DEVONIAN COURT, PK. CRES. PLACE, BRIGHTON (Tel 800722)

BI-PAK SEMICONDUCTORS

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and Quality
Satisfaction GUARANTEED in Every Pak, or money back.



I.C. AMPLIFIER
Identical encapsulation and pin configuration to the following: BL402-3, IC10 and IC403. Each circuit incorporates a pre-amp and class A-B Power amp stage capable of delivering up to 3 watts BMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 30/- each. 10 up 25/- each.

ADI61 PNP AD162 PNP
MATCHED COMPLEMENTARY PAIRS OF GERM-POWER TRANSISTORS. For mains driven output stages of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 12/6 PER PAIR.

UNIUNION
UT46. Eqty. 2N2646
Eqt. T1543. BEN3000
5/6 EACH
25-99 5/- 100 UP 4/-

PNP SILICON PLANAR
BC107/93, 2/- each 50-99, 1/10 100 up, 1/8 each, 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

PNP DIFFUSED SILICON PHOTO-DUODIODE
TYPE I5701 (2N2175) or Tape Readout, high switching and measurement indicators, 50V, 250mV. OUR PRICE 10/- EACH. 50 OR OVER 8/6. EACH. FULL DETAILS.

LET'S
2N 3819 8/-
1N 3920 25/-
MPP106 8/6

NEW LOW PRICED TESTED S.C.R.'s

1 A	3 A	7 A	16 A	30 A
(TO-5)	(TO-66)	(TO-48)	(TO-48)	(TO-48)
case	case	case	case	case
PIV	each	each	each	PIV
50	4/6	5/-	9/5	10/6
100	5/-	6/6	10/6	12/6
200	7/-	7/6	11/6	15/-
400	8/6	9/6	13/6	18/6
600	10/6	11/6	15/6	25/-
800	12/6	14/-	18/-	30/-
				400 80/-

SIL. REJECTS TESTED

PIV	750mA	3A	10A	30A
50	1/3	2/9	4/3	9/6
100	1/3	3/3	4/6	15/-
200	1/9	4/-	4/9	20/-
300	2/3	4/6	6/6	22/-
400	2/6	5/6	7/6	25/-
500	3/-	6/-	8/6	30/-
600	3/6	6/9	9/-	37/-
800	3/6	7/6	11/-	40/-
1000	5/-	9/3	12/6	50/-
1200	6/6	11/6	15/-	

PRINTED CIRCUITS EX-COMPUTER
Packed with semiconductors and components. 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/-, Plus 2/- p. & p.

TRIACS

VBOM	2A	6A	10A
(TO-1)	(TO-66)	(TO-88)	
100	14/-	15/-	22/6
200	17/6	20/-	28/-
400	20/-	25/-	35/-

VBOM = Blocking voltage in either direction.

TRANSISTOR EGYPT & SPECIFICATION BOOK (German publication). A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

2N3055 115 WATT SIL. POWER. NPN. OUR PRICE 12/6 EACH

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-18V. 400mV (DO-7 Case)

2/8 ea. 1-5W(T op-Hat)
3/8 ea. 10W. (SO-10 Stud) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

2N2060 NPN SIL. DUAL TRANS. CODED D1699 TEXAS. Our price 5/- ea.

120VCB NIXIE DRIVER TRANSISTOR. Sim. BSX21 & C407, 2N1893 FULLY TESTED AND CODED NPN. 1-24. 3/6 each. TO-5 NPN 25 up 8/- each.

BRAND NEW TEXAS GERM. TRANSISTORS Coded and Guaranteed.

Pak No.	EQVT
T1 8	2G371A OC71
T2 8	2G374 OC75
T3 8	2G374A OC81D
T4 8	2G381A OC81D
T5 8	2G382T OC82
T6 8	2G344A OC44
T7 8	2G345A OC45
T8 8	2G378 OC78
T9 8	2G399A 2N1302
T10 8	2G417 AF117

All 10/- each pack

MULLARD I.C. AMPLIFIERS

TAA243, Operational amplifier, 70/- each
TAA263, Linear AF amplifier, 18/6 each
TAA293, General purpose amplifier, 21/- each.

CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS
Audio Power Amplifier, 30/- each.

Pak No.

U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OAS. OA47	10/-
U4	40 Germanium Transistors like OC81, AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	30 Silicon Planar Transistors NPN sim. B8Y96A, 2N706	10/-
U7	16 NPN Rectifiers Top-Hat 750mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 260mA OA/200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1139	10/-
U13	30 PNP-NPN Sil. Transistors OC200 & 2B104	10/-
U14	150 Mixed Silicon and Germanium Diodes	10/-
U15	25 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U16	10 3-amp Silicon Rectifiers Stud Type up to 1,000 PIV	10/-
U17	30 Germanium PNP AF Transistors TO-5 like ACY17-22	10/-
U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U19	25 Silicon NPN Transistors like BC108	10/-
U20	12 1-6 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U21	30 AF Germanium alloy Transistors 2G300 Ser. & OC71	10/-
U23	30 Mad's like MAT Series PNP Transistors	10/-
U24	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U25	25 300Mc/s NPN Silicon Transistors 2N708, B8Y27	10/-
U26	30 Fast Switching Silicon Diodes like IN914 Micro-min.	10/-
U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces	20/-
U29	10 1-amp BCR's TO-5 can up to 600 PIV CR51/25-600	20/-
U31	20 Sil. Planar NPN trans. low noise Amp 2N3707	10/-
U32	25 Zener diodes 400mV D07 case mixed Volts, 3-18	10/-
U33	15 Plastic case 1 amp Silicon Rectifiers 1N4000 series	10/-
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4	10/-
U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U36	25 Sil. Planar NPN trans. TO-5 BFY 30/51/52	10/-
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2S322	10/-
U38	20 Fast Switching Sil. trans. NPN. 400 Mc/s 2N3011	10/-
U39	30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
U40	10 Dual trans. 6 lead TO-5 2N2906	10/-
U41	25 RF Germ. trans. TO-1 OC45 NKT72	10/-
U42	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these **EXCLUSIVE LOW PRICES**. TTL Digital SN74N Series fully coded, brand new to manufacturers' specifications. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.	Description	Price and qty. prices		
		1-24	25-99	100 up
BP00 = SN7400N	Quad 2-Input NAND GATE	6/6	5/8	4/6
BP01 = SN7401N	Quad 2-Input NAND Gate—OPEN COLLECTOR	6/6	5/8	4/6
BP04 = SN7404N	HEX INVERTER	6/6	5/6	4/6
BP10 = SN7410N	Triple 3-Input NAND GATE	6/6	5/8	4/6
BP20 = SN7420N	Dual 4-Input NAND GATE	6/6	5/8	4/6
BP30 = SN7430N	Single 8-Input NAND GATE	6/6	5/8	4/6
BP40 = SN7440N	Dual 4-Input BUFFER GATE	6/6	5/8	4/6
BP41 = SN7441AN	BCD to decimal decoder and NIT Driver	22/6	20/-	17/6
BP42 = SN7442N	BCD to decimal decoder (TTL 0/1)	22/6	20/-	17/6
BP60 = SN7450N	Dual 2-Input AND/OR/NOT GATE—expandable	9/6	5/6	4/6
BP53 = SN7453N	Single 8-Input AND/OR/NOT GATE—expandable	6/6	5/8	4/6
BP60 = SN7460N	Dual 4-Input—expandable	6/6	5/8	4/6
BP70 = SN7470N	Single JK Flip-flop—edge triggered	9/-	8/-	7/-
BP72 = SN7472N	Single Master Slave JK Flip-flop	9/-	8/-	7/-
BP73 = SN7473N	Dual Master Slave JK Flip-flop	10/-	9/-	8/6
BP74 = SN7474N	Dual D Flip-flop	10/-	9/-	8/6
BP75 = SN7475N	Quad Bistable Latch	11/-	10/-	9/6
BP76 = SN7476N	Dual Master Slave Flip-flop with preset and clear	11/-	10/-	9/6
BP83 = SN7483N	Four Bit Binary Adder	26/-	26/-	20/-
BP90 = SN7490N	BCD Decade Counter	22/6	20/-	17/6
BP92 = SN7492N	Divide by 12 4 Bit binary counter	22/6	20/-	17/6
BP93 = SN7493N	Divide by 16 4 Bit binary counter	22/6	20/-	17/6
BP94 = SN7494N	Dual Entry 4 Bit Shift Register	22/6	20/-	17/6
BP95 = SN7495N	4 Bit Up-Down Shift Register	22/6	20/-	17/6
BP96 = SN7496N	5 Bit shift register	24/-	21/-	18/6

Data is available for the SN74N Series of Integrated circuits in booklet form, price 2/6

INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and par. functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work, on testing some will be found perfect.

PAK No.	Price
UIC00 = 5 x 7400N	10/-
UIC01 = 5 x 7401N	10/-
UIC10 = 5 x 7410N	10/-
UIC20 = 5 x 7420N	10/-
UIC30 = 5 x 7430N	10/-
UIC40 = 5 x 7440N	10/-
UIC41 = 5 x 7441AN	10/-
UIC50 = 5 x 7450	10/-
UIC53 = 5 x 7453	10/-
UIC72 = 5 x 7472	10/-
UIC74 = 5 x 7474	10/-
UIC75 = 5 x 7475	10/-
UIC90 = 5 x 7490	10/-
UICX1 = 20 x asst'd. 74's	30/-

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

MOTOROLA DIGITAL I.C.'s

MDTL dual in-line package.	Price
Type MC844P expandable dual 4-input NAND Power Gate	10/- each
Type MC845P Clocked Flip-flop	15/- each

FULL DATA SUPPLIED WITH UNITS

BRAND NEW. FULL TO MANUFACTURERS' SPECIFICATION

BP709 Operational Amplifier, dual-in-line 14 pin package = SN72709 and similar to MIC709 and ZLD709C 10/6 9/- 8/-

This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits	Qty.	prices each
Epoxy case To-5 temp range 15°C to 55°C.	1-11	12-24 25-99 100 up
μL 900 Buffer	9/8	8/- 7/6 6/6
μL 914 Dual two-input GATE	9/8	8/- 7/6 6/6
μL 923 J-K Flip-flop	12/8	11/- 10/6 9/6
Full data and circuits for ICS in Booklet form price 1/6 each.		
μA703E Linear RF-IF AMPLIFIER	11/-	10/- 9/- 8/3
PLASTIC CASE TO-5 6 lead up to 100 mV/c.		

Please send all orders direct to our warehouse and despatch department.

Postal address:

BI-PAK SEMICONDUCTORS

P.O. BOX 6, WARE, HERTS.


Postage and packing add 1/-. Overseas add extra for Airmail. Minimum order 10/-. Cash with order please.

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

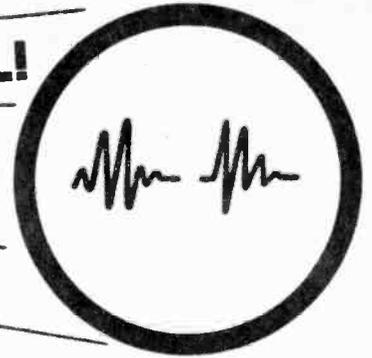


a new 4-way method of mastering

ELECTRONICS

by doing — and — seeing ...


1 OWN and HANDLE a

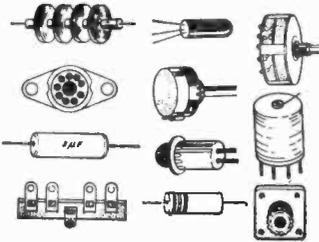complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




2 BUILD and USE

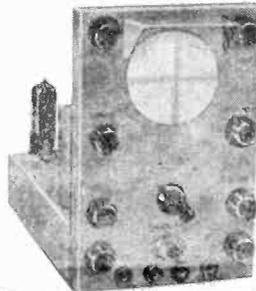a modern and professional **CATHODE RAY OSCILLOSCOPE**



3 READ and DRAW and

UNDERSTAND **CIRCUIT DIAGRAMS**

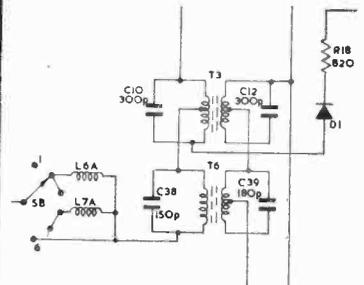

4 CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK ... INCLUDING ...

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW6

PRACTICAL WIRELESS

VOL 46 NO 3

Issue 761

JULY 1970

TOPIC OF THE MONTH

PROJECT AUTUMN

In order to produce a monthly magazine such as Practical Wireless, and to satisfy the requirements of its large readership, it is necessary to maintain a steady flow of material covering all the various facets of the hobby. Bearing in mind the differences in age, experience and preferences of our readers, the permutations involved in selecting a balanced set of contents for one volume of the magazine are rather daunting.

We draw our material from several sources. Some articles are written by members of the staff. Others are supplied by a well-established group of regular contributors, many of such articles being specially commissioned. But Practical Wireless is not a closed shop for prospective technical writers. We receive a constant flow of unsolicited material from almost every type of enthusiast, and quite a few of these ultimately appear in these pages.

One or two of our writers are full time professionals and quite a few more are employed in some technical capacity in the radio or electronics industries, putting in the occasional piece of writing in their spare time to add a little jam to the bread. But a large number of the by-lines which appear in Practical Wireless are of ordinary readers who have built a piece of equipment, or who have something they want to say.

Some of these spare-time writers produce very commendable efforts and our one regret is that many of them are heard from at too infrequent intervals. It has also occurred to us that, hidden among the anonymous ranks of the multitude, there must be quite a few promising potential authors. And it is with the aim of unearthing some of this latent talent that it has been decided to offer a new kind of incentive.

"Project Autumn" is the name of a special competition open to all readers of Practical Wireless. There will be a special trophy for the first prize, the winner being the author whom, in the opinion of a panel of judges, has submitted the best article within the period of the contest. Even losers may be lucky, since the best of the entries will be published at our normal rates. Full details will appear in the next issue. In the meantime, if you have a piece of equipment you think other readers may like to build, or if you want to build something specially for the competition, now is the time to start planning your article.

W. N. STEVENS—*Editor.*

**AUGUST ISSUE WILL BE PUBLISHED
ON JULY 10**

NEWS AND COMMENT

Leader	185
News . . . News . . . News . . .	186
On the Short Waves <i>by Malcolm Connah and David Gibson G3JDG</i>	214
Practically Wireless <i>by Henry</i>	216
CQ! CQ! CQ! CQ! CQ! CQ!	218
Letters to the Editor	225
MW Column <i>by Charles Molloy</i>	226

CONSTRUCTIONAL

Novel Signal Injector <i>by N. C. Bancil</i>	188
Mini Amp/Speaker <i>by F. G. Rayer</i>	190
Hybrid Modulator <i>by C. F. Fletcher, G3DXZ</i>	195
Transmitter/Receiver for the L.F. Bands Part 2 <i>by F. G. Rayer, G3OGR</i>	199
Take 20, Short Wave Receiver <i>by Julian Anderson</i>	203
Reverberation Unit <i>by Hal Moorshead</i>	208
Novel V.H.F. Aerial <i>by Arthur Dow</i>	217
Light Operated Switch <i>by R. Collins</i>	221
I.C. of the Month, TAA 310, <i>by L. A. J. Ireland</i>	233

OTHER FEATURES

Sums plus Circuits equals Understanding Part 4 <i>by Leslie Moore</i>	192
Voltage Stabilisation <i>by I. R. Sinclair</i>	204
Going Back . . . <i>by Colin Riches and Arthur Dow</i>	229

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

NEWS... NEWS... NEWS...

New from Philips



Philips have introduced two new radios, the RN214 and RN691. The RN214 is a m.w. l.w. manually tuned car radio, costing £17 0s. 0d. Power output is 5 Watts. The radio's modern styling is also safety styling; every forward edge is padded with rubber and the control knobs are designed to snap off at impact—yet are readily replaceable. Philips' research into microminiaturisation has been well used in the production of this receiver, so that there is room for the 5 Watt output transistors to fit inside the radio and not on the rear of the casing where they might have been damaged. The entire radio is screened against interference by a precision-made metal casing that virtually seals off the electronic circuitry. In addition, extra filtering circuits are built into a separate screened compartment.

Philips RN61 was first reviewed in prototype form at the 1969 Motor Show. It is a push-button radio covering long, medium, 50 metre s.w. and v.h.f./f.m. wavebands including all the BBC local stations. The RN691 has approximately 180 microminiaturised components on a printed panel no larger than a woman's hand. Extra circuits have been included to improve performance, such as a tuned r.f. stage and a.t.c. on the f.m. band to hold stations firmly in tune. The five push-buttons can be set to give an instant selection and give a high repeat accuracy; a continuous treble and bass tone control lets you match your car's acoustics; and the facilities are there to connect a car record player, Cassette player or recorder. Recommended retail price is £60.

Audio Transducer

A new device which reproduces music through a variety of ordinary household materials from an apparently invisible source is now available. Called the Sound Scan Capsule, the unit may be concealed in the ceiling, under floorboards, or behind doors, to envelop the whole room in an even volume of music no matter where the listener may be standing or sitting.

This effect is achieved by linking the unit to the output socket of any record player (mono or stereo), tape recorder, or amplifier. The capsule will work on almost any flat surface such as a table, picture or window, and will diffuse sound over large areas—



up to 2,000 square feet in ideal circumstances. It is weather-protected, will play under water and comes with a five-year warranty.

Measuring about 4 inches in diameter and less than 2 inches in depth, the Sound Scan Capsule is technically known as an audio-transducer. It was invented in the U.S.A. where it has been successfully marketed by Photo-Scan International of Los Angeles, manufacturers of electronic systems to combat shoplifting and pilferage.

Costing £10, the Capsule will be available throughout the country from radio and electrical shops.

Further details from: *Mr. Colin Stewart, Sound Scan Ltd., Oakwood House, 63 Pound Lane, Marlow, Bucks. Tel: Marlow 6655.*

U.S. Equipment

Four acoustic suspension loud-speaker systems; an ultra-low-rumble turntable; a 60+60W. amplifier and an f.m. receiver: this is the range of Acoustic Research high fidelity sound equipment now being introduced to the United Kingdom market by Bell & Howell Audio Products Division.

Heading the range of loud-speakers is the well-known AR-3a system. Like all AR speakers, it uses the acoustic suspension principle to achieve very low distortion at low frequencies and, as a result, has a uniform and extended bass response. Each system comprises a 12in. woofer in combination with 1½in. and ¾in. hemispherical domes for mid-range and high-frequency reproduction.

Guaranteed to meet the appropriate specifications for wow, flutter, rumble and speed accuracy laid down by the United States' National Association of Broadcasters, the AR turntable has a miniature synchronous motor.


Each AR turntable is ready-mounted on an oiled walnut base and comes complete with arm, plug-in cartridge shell and transparent plastic dust cover.

The AR amplifier uses silicon transistors and has an output of 60+60W. r.m.s. into 4 ohms and 50+50W. into 8 ohms. Frequency response with both channels at full output is 20-20,000Hz. ±1dB and IM distortion is less than 0.25% at any listening level.

The amplifier section of the f.m. receiver has basically the same specification. Receiver sensitivity extends to 2 microvolts and drift is limited to a maximum of 50kHz. Stereo separation exceeds 40dB at 400Hz.

The picture shows the AR amplifier.

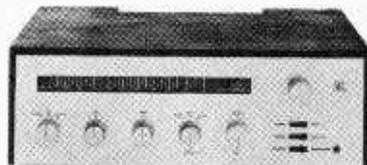
Bell & Howell Ltd., Alperton House, Bridgewater Road, Wembley, Middx., HA0 1EG.



NEWS... NEWS... NEWS...

Junior Electronic Experiment Kit

A new experimentation course in basic electronics for young people has just been introduced by Heathkit. Designated the Heathkit JK-18, it features 35 exciting experiments using the 'learn-by-doing' technique. The new JK-18 is both fun and educational. All the parts are mounted on a 'breadboard', and then various circuits are constructed according to instructions by connecting them with ordinary wire, as provided in the kit. For speed and easy circuit assembly and disassembly, solderless spring-clip connectors are used throughout the kit. The JK-18 builds any of these 35 different circuits; Code Flasher, Continuity Tester, Battery Tester, Diode Tester, Transistor Tester, Rain Alarm, Timing Relay, Listening Device, Public Address Amplifier, Intercom, Voice Relay, Earphone Code Oscillator, Loudspeaker Code Oscillator, Flasher, Experimental Multivibrator, Electronic Organ, Burglar Alarm, Metronome, Siren, Light Meter, Light Sensing Alarm, Target 'Hit' Alarm, Light Dependent Flasher, Light Dependent Oscillator, Sound Level Meter, three different Solid-State radios, Automatic (Light Dependent) Radio, Field Strength Indicator, Code Transmitter, Voice Transmitter, Capacity Relay,

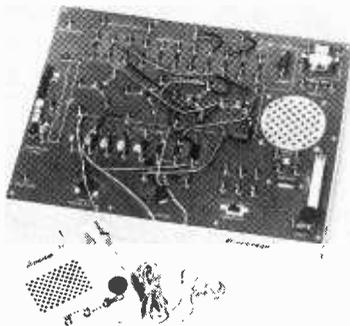

Wheatstone Bridge and Capacity Bridge. The illustrated manual that comes with the new Heathkit JK-18 includes a fold-out diagram for easy experiment which also describes the operation of the circuit in easy-to-understand language. All parts used in any given experiment are identified by both a pictorial diagram and the standard schematic representation so that the experimenter learns how to read circuit diagrams. The manual also includes a dictionary of common terms and the International Morse Code. Kit JK-18 costs £13 18s. incl. purchase tax; carriage is 5s extra. For further information about the Heathkit JK-18 write: *Daystrom Ltd., Heathkit Division, Gloucester. Tel. 29451.*

Mullard Data Book

Mullard Ltd. announce the publication of the 1970 edition of their Pocket Data Book. It follows the pattern of previous issues and embraces the complete Mullard ranges of valves, TV picture tubes, semiconductors and components for entertainment applications.

For easy reference different coloured paper is used for each of the main product sections. Equivalent and earlier types are listed in the valve section, replacement details are given in the tube section and information on comparables is shown in the semiconductor section.

The book is available through radio and TV dealers and bookshops, and the price is 4s. 0d. a copy.

Swansea Rally

On Sunday, June 21st, at 1 p.m., Swansea University Radio Society will be holding its mobile rally, the venue being the College Campus at Singleton Park (on the A4067 road).

There will be a talk-in on Topband and Two Metres for those unfamiliar with the area.

This will be the type of outing suitable for *all the family* as there are many local amenities. We are situated in spacious parklands *literally* a stone's throw from the beach (Swansea Bay), and we have adequate parking facilities.

Refreshments will, of course, be provided.

Further details may be obtained from *Philip Regan, Union House, University College, Swansea, SA2 8PP.*

Micro 70

An interesting conference sponsored by 'Microelectronics' and 'Electronic Equipment News' was held at the Royal Garden Hotel in London on 28/29th April with the title of "The Interface between the Integrated Circuit Manufacturers and their Customers".

What it turned out to be was a 'down-to-earth', 'face-to-face', very informative session of discussions between those that 'make-em' and those that 'use-em' with a view to better co-operation in the future and in particular to reduce the expenditure in the development field.

Speakers from the leading companies spoke on their own particular problems associated with the production of integrated circuits and delegates were able to quiz the speakers and to put forward their own views.


The conference was organised by *Business Conferences and Exhibitions Ltd.*

Mullard Educational Booklet

The most recent addition to the Mullard pamphlets in the series "Educational Projects in Electronics" describes how to build a simple inexpensive, f.e.t. voltmeter. The meter has eight ranges, the smallest being 0 to 250mV and the largest 0 to 500V. Because it has a high input impedance of at least 10M Ω on each range, the instrument is suitable for measuring d.c. levels in transistor and valve circuits.

The meter contains no close-tolerance resistors and the least expensive f.e.t. transistor (type BFW61) has been used. Nevertheless, the Educational prototype has been in constant use since it was built twelve months ago. However, design information is given for those who wish to make a more accurate instrument.

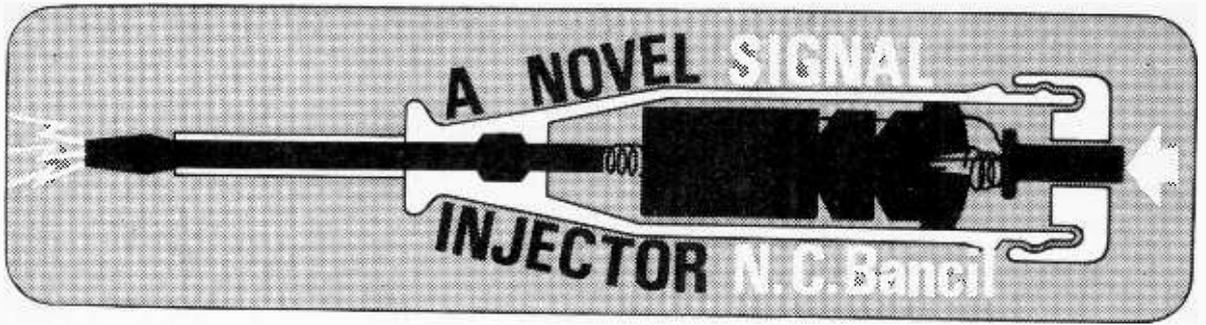Teachers, lecturers and others professionally concerned with science education can obtain a sample copy of the pamphlet from the *Mullard Educational Service, Mullard Limited, Mullard House, Torrington Place, London W.C.1.*



THE circuit employed is that of a simple multi-vibrator circuit, Fig. 1. There is no doubt that signal generators of this nature have been made before, but many serving the same function as this are cumbersome to use, and one hesitates to carry the instrument in one's pocket all the time.

The device can be used as a screwdriver, say for opening a receiver, and as a signal injector. The output is 2V peak to peak measured on Servoscope Type D31 and the frequency is 10kHz.

The tester is used mostly without an earth lead, so that even when checking a mains radio, one can, if required, inject a signal into a component carrying h.t. but this is not advisable.

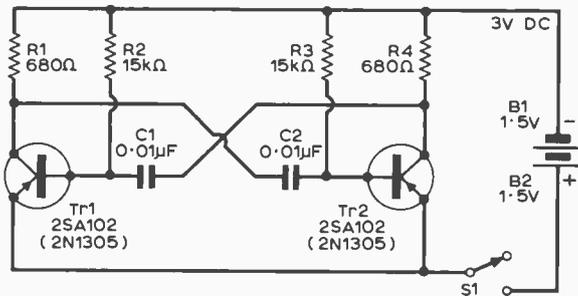


Fig. 1: Circuit diagram of signal injector. All resistors $\frac{1}{2}$ W 5%.

However, if the earth lead is required, a piece of wire pushed in the hole at the back of the press-button switch and the other end to earth may do the job. If the injector is used in the above condition, great care must be exercised not to put the injector across h.t. of higher than about 18 volts.

Any transistors of higher cut-off frequency and a reasonable gain may be used, as long as they are not too big. Transistors of case style TO.18 are preferred.

CONSTRUCTION

Step 1. Tin all the leads of the resistors and transistors right to the ends, using a heat sink on transistor leads.

Place resistor R1 nearest to the collector lead of the transistor Tr1. Bend the transistor lead and wrap it around the straight resistor wire. Keep the resistor very close to the transistor, taking great care while bending the transistor leads.

Place resistor R2 next to the base lead and do the same as above. Bend the resistor leads at the other end as shown in Fig. 2.

Step 2. Repeat this procedure with Tr2, R3 and R4 as in step 1. Place back to back, as close as possible, without leaving any space between the transistors, Fig. 3.

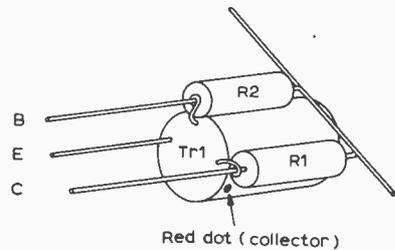


Fig. 2: Initial transistor assembly.

Cut three of the leads to a length so that they do not protrude. Solder all four leads as shown and bend one as close to transistor Tr2 as possible. Put a black sleeve over it, this is going to be the negative terminal. Leave this lead as long as possible.

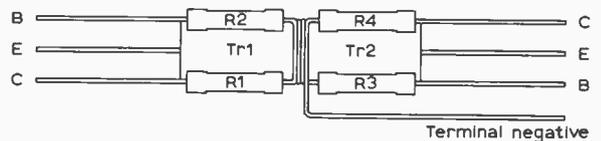


Fig. 3: Two assemblies soldered together.

Step 3. Bend the emitter leads backwards and solder in the middle position together with a 3in. piece of red wire, later to be connected to switch S1, Fig. 4.

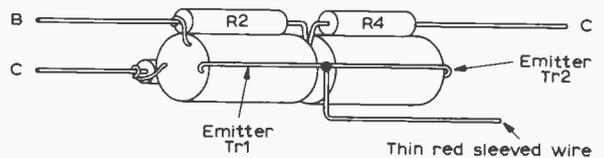


Fig. 4: Emitter connections.

Step 4. By placing capacitor C1 flat on its side, a lead is soldered to the collector. The capacitor must be very carefully placed so that it is roughly diametrically in position to Tr1 and its resistors. If it is out of 'the ring' it may be difficult to insert the whole assembly into the screwdriver, Fig. 5.

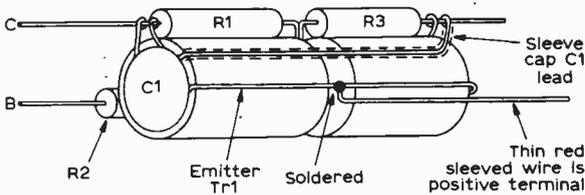


Fig. 5: Note careful placement of disc capacitor C1.

After soldering to the collector wire the rest of the wire of R1 is not cut. Similarly, capacitor C2 is soldered on to Tr2 and R3, R4. The other wire of capacitor C1 is soldered to R3 as shown. It must be sleeved, tightly (keeping the sleeve diameter as small as possible).

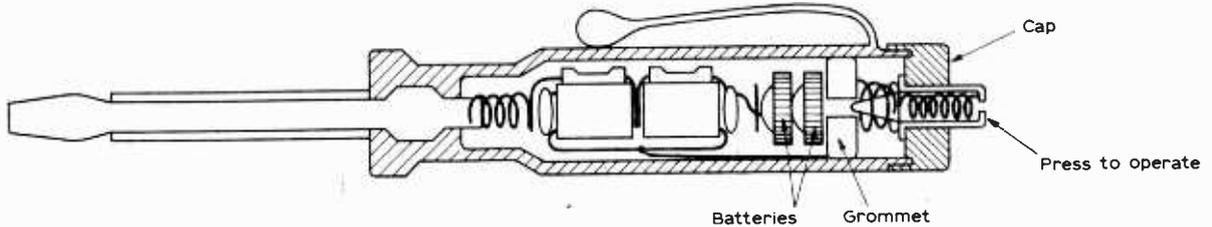


Fig. 9: Completed injector showing mercury cells to supply power.

The other wire of C2 is similarly brought out and wrapped around R2 and soldered. The excess wire of R2 is then cut. When buying the capacitors they must be so chosen that they have no unnecessary projecting material, as shown in Fig. 6. The excess ends of R2, R3 and R4 are now cut.

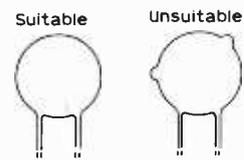


Fig. 6: Selecting suitable capacitor for C1

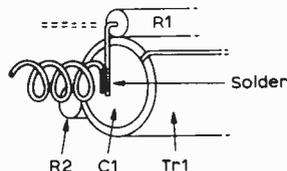


Fig. 7: Attaching spring to assembly.

Step 5. The long wire of R1 is now bent on top of C1 body and cut to a length slightly greater than the radius of C1 body. A piece of spring cut from the main spring found originally in a neon tester, or a ball point pen, is soldered as shown in Fig. 7.

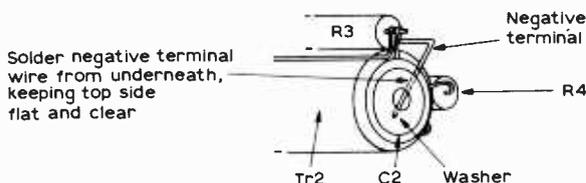


Fig. 8: Washer used as negative contact to battery.

Before soldering the spring, a piece of paper placed between the resistor wire and the capacitor will prevent capacitor wax from melting, and stop damage. The spring is soldered here in order to make firm contact with the metal shaft of the screwdriver.

Step 6. The black sleeved wire from the four resistors (Step 2) is bent over C2 body and cut to a length slightly greater than the radius of C2 and a thin copper washer is soldered to it. The washer should be one fitting easily inside the screwdriver.

Step 7. The assembly is now slid into the screwdriver body with the spring end first. The batteries are then put in and pressed lightly. If necessary, a packing of thick paper to insulate and prevent damage to the capacitor, should be placed between the transistor and capacitor, also between the capacitor and washer.

A rubber grommet of the same diameter as the hole of the screwdriver is cut in half and placed on the batteries.

The battery negative terminal should be placed so as to press against the washer. The red wire which is connected to the emitters is cut approximately by placing the whole assembly into the screwdriver and cutting the wire when just accessible from the top. Fig. 8.

The wire is then soldered to the middle of a spring found originally in a neon tester or ball pen. One end of the spring is crimped, so as to fit into the hole of the plastic plunger.

To the inside of the spring is soldered a piece of stiff wire shaped as a 'V', about 1/4 in. long.


The spring is put in the screwdriver and rests on the rubber grommet, thus insulating the positive lead, making contact when the plunger is pressed. The cap is then put on the screwdriver, together with the clip.

"PROJECT AUTUMN"

Practical Wireless is pleased to announce that it is sponsoring a new competition in which readers are invited to submit articles describing constructional projects for publication. The first prize, for the best article received, will be the P.W. Designers Trophy, which will be retained outright by the lucky winner. For general comments on this competition, refer to this month's leader.

FULL DETAILS OF THIS COMPETITION WILL BE PUBLISHED IN THE AUGUST ISSUE ON SALE FROM JULY 10th.

Don't miss this important announcement!

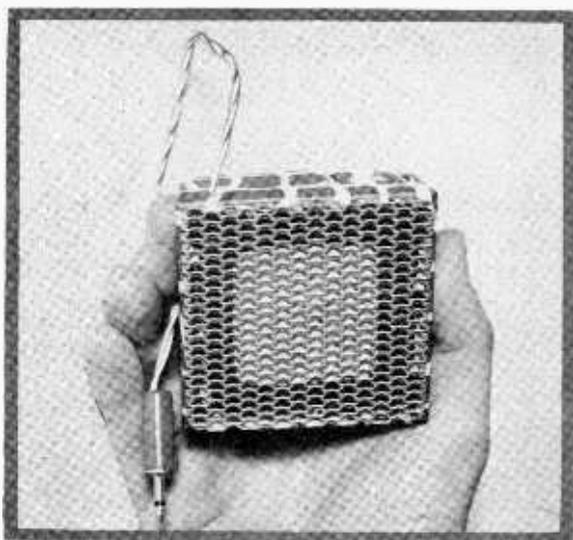

mini AMPLIFIER/SPEAKER

F. G. RAYER

THIS midget amplifier and speaker fit in a case approximately 3in. x 3in. x 1½in. deep inside dimensions, this including a PP4 9V battery. Though really intended to allow loudspeaker reception with the *Slimline Superhet* (P.W., June 1969) it can be used with other receivers which normally have only sufficient output for a personal phone or headphones.

Fig. 1 shows the circuit. T1 is the driver transformer, and the primary connections 5 and 6 are to a miniature jack plug which is inserted in the socket of the receiver, normally employed for phone output. The receiver can thus supply signals for the output stage, consisting of Tr1 and Tr2 in a single-ended push-pull circuit, the loudspeaker being coupled through C1.

The miniature amplifier/speaker has its own battery and on-off switch, so no other connections are required to the receiver. Volume is adjusted by the usual receiver audio gain control, so either phones, or the amplifier/speaker, may be plugged at once into the receiver.

The Mini Amplifier/Speaker has been used with other receivers of the type having a small single audio output transistor, and designed to operate headphones or a personal earpiece. In all cases satisfactory reception was possible.

The values used allow for economical running, with adequate volume. A similar type of circuit could be used with other driver transformers, transistors and speaker, but resistor values may then have to be modified to suit.

Circuit Board

The amplifier is constructed on a piece of ¼in. thick paxolin 2½in. x 2½in. (see Fig. 2). A 1½in. diameter hole is cut to clear the speaker magnet assembly. When all wiring is finished, the speaker

can be attached by bolts with extra nuts, passing through the holes S-S. If preferred, the speaker may be screwed inside the case, and have thin flexible leads to the amplifier.

The holes for resistor and other leads are ¼in. diameter. One wire of each resistor is bent over, so that these items fit as in Fig. 2.

The driver transformer T1 is held by its lugs, and by soldering wires to the projecting pins. For the transformer listed these come as in Fig. 2.

T1, C1 and the resistors are wired as in Fig. 2, with insulated sleeving where required. Prepare the transistors by placing about ¼in. of sleeving on each base lead. Pass the wires through the correct holes, solder as in Fig. 2, and snip off excess wire.

The battery positive lead is thin red flex, passed through a hole and fitted with a positive clip. The small slide switch is connected in the negative battery lead. This switch is later fixed to the side of the case with two small bolts, a small slot being cut to take the projection.

Input Connections

These go to 5 and 6 on T1 (Figs. 1 and 2). Thin twin flex was used, and the phase of connection seemed to have no effect on the results with any of the receivers employed. The flex terminates in a miniature jack plug of the same size as used for the receiver phones.

If a screened lead were used, the outer brading should be used as the jack sleeve connection, the inner lead going to the jack plug tip.

Testing

A meter in one battery lead should show about 4mA to 6mA with no signal, rising to 10mA to

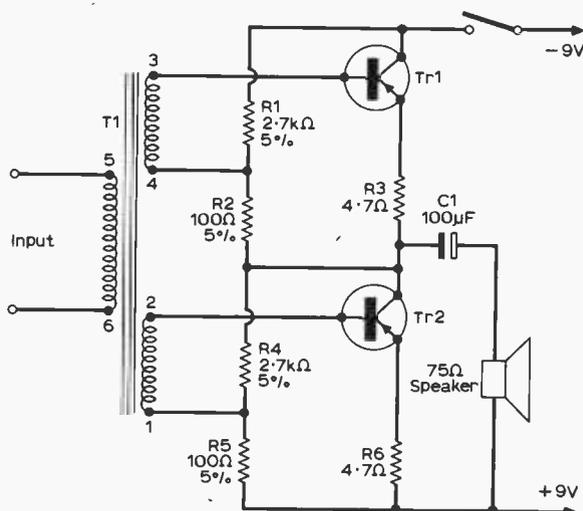


Fig. 1: The circuit of the amplifier


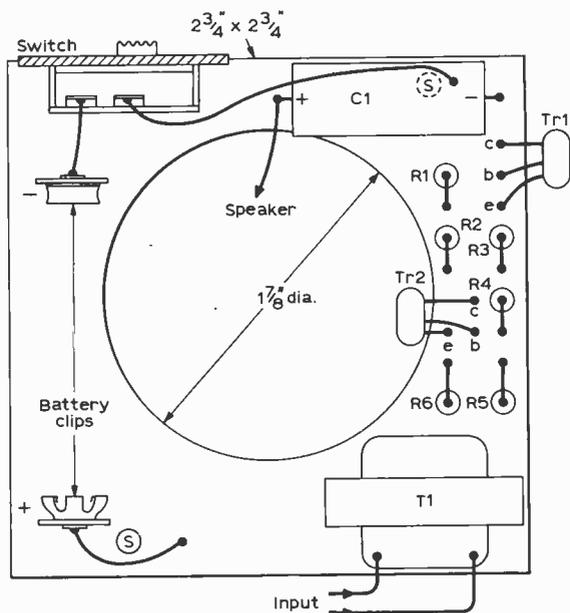


Fig. 2: The components are mounted on a drilled paxolin panel.

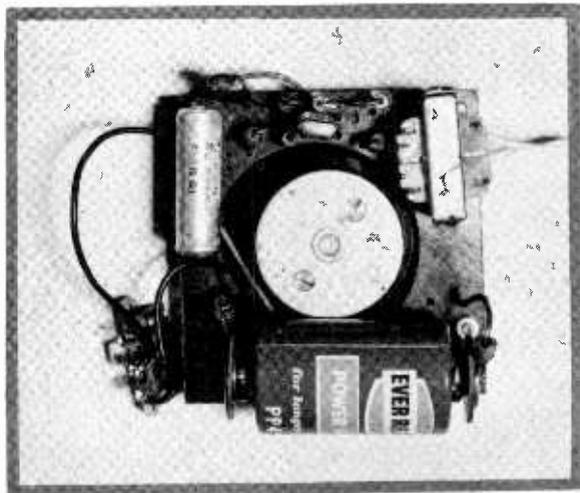

The completed unit.

15mA peaks, with normal volume. Should results sound distorted, then R1, R2, R4 and R5 may be incorrect. These resistors should be 5 per-cent tolerance. The 10 per-cent type should only be used if values can be tested with a meter, or if correct operation of Tr1 and Tr2 can be checked.

★ components list

R1	2.7kΩ 5%	R4	2.7kΩ 5%
R2	100Ω 5%	R5	100Ω 5%
R3	4.7Ω 10%	R6	4.7Ω 10%

All resistors 1/4 watt miniature types

C1 100μF 12V


Tr1/Tr2 Matched pair NKT251/OC72/AC128 etc.

T1 3.6:1 +1, Driver transformer, Home Radio Cat. No. TR61

Miniature slide switch.

W.B. 75 ohm 2 1/2 in. speaker or similar.

PP4 9V battery, clips, paxolin, etc.

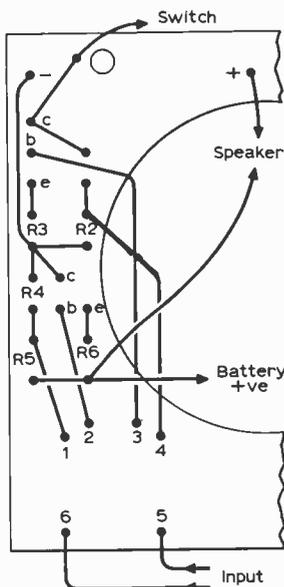

The case

A ready-made plastic box or similar case would be satisfactory. The one actually used was assembled from 1/8 in. thick insulated board, and covered to match the Slimline Superhet. An aperture 1 1/2 in. x 1 1/2 in. was provided in the front. The front surface, from this aperture to within 1/4 in. of the edge, all round, was painted black. Thin gold fabric was glued over the aperture inside. Outside, a piece of gold speaker fret metal slightly smaller than the case front was cemented on.

A piece of stout card is cut to fit inside the case and a hole which matches the speaker cone in size and position is cut in this card. When first testing the unit, remember that even this very small case makes an appreciable difference to the results from the loudspeaker. ■

PRACTICAL WIRELESS

QUERY SERVICE

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard textbooks. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

SUMS

plus

CIRCUITS

equals

UNDERSTANDING

PART 4

LESLIE MOORE

LOGARITHMS

AS numerous natural phenomena obey logarithmic relationships, electronic circuitry is often given specifications in logarithmic scales. Rather than give a logarithm a complicated definition, a simple example, given in Table 1 should provide a better illustration.

For numbers less than 1, the minus sign for the logarithm is drawn above the first figure in the log, therefore,

-1 becomes $\bar{1}$, called bar 1

-3 becomes $\bar{3}$, called bar 3..... etc.

TABLE 1

Number	Name	Symbol	Number written to the power of 10	Logarithm to the base of 10
1,000,000,000	GIGA	G	10 ⁹	9
1,000,000	MEGA	M	10 ⁶	6
1,000	KILO	k	10 ³	3
1	UNITY	—	10 ⁰	0
0.001	MILLI	m	10 ⁻³	-3
0.000001	MICRO	μ	10 ⁻⁶	-6
0.000000001	NANO	n	10 ⁻⁹	-9
0.000000000001	PICO	p	10 ⁻¹²	-12

This table illustrates how the values of resistors, capacitors, etc., in everyday use are related to each other, and the meaning of the various prefixes. It is important to note that the symbols have the same meaning regardless of the units to which they refer.

Any number can be given a logarithm, to any base, accepting the fact that the logarithms of infinity and zero are plus infinity and minus infinity respectively. Initially we shall discuss logarithms to the base of 10, often called *common logarithms*.

The uses of logarithms (logs) extend to multiplication and division problems; logs of numbers to be multiplied are added and those of numbers to be divided are subtracted; to demonstrate:

(i) 100 × 100 = 10,000
or 10² × 10² = 10⁴ i.e. add logs

(ii) 1000 ÷ 100 = 10
or 10³ - 10² = 10¹ i.e. subtract logs

Numbers which lie between 1 and 10, 10 and 100 etc. have logarithm values which contain a fraction of a whole number, and although there are methods for determining logarithms by tedious calculations, the logarithms of all numbers between 1 and 10 have been tabulated and are obtainable in book form from any book-shop (log table sets usually also contain the trigonometrical tables).

From log tables, the log of 2 = 0.3010
Should you wish to determine the log of 20, rewrite 20 as 2 × 10, and as shown before, add the logs of 2 and 10 giving,

0.3010 + 1.0 = 1.3010.

The logarithm of 0.2 is written as

$\bar{1} + 0.3010 = \bar{1}.3010$ (a)

and, equally true is also

$-1 + 0.3010 = \bar{0}.6990$ (b)

To demonstrate, using result (a).

$\bar{1}.3010 + 1 = 0.3010 = \log 2.$

using result (b)

$\bar{0}.6990 + 1 = 0.3010 = \log 2.$

Logarithms are obtained for the numbers which are to be multiplied or divided, then, when the appropriate additions or subtractions have been made the result must be converted back from the log form to true numerical. Firstly the figures should be broken down into two parts.

e.g. $4.3010 = 4 + 0.3010$

so that the final answer will appear as

$10^4 \times 2 = 20,000$

Anti-logarithm tables are used to determine the number relating to the fractional part of the term. Rules for using logarithm tables are usually given with sets of logs.

The Decibel

Electronic and radio engineers use the decibel as a unit for ratios, usually for amplifier gains or network losses. This is used because the human ear sensitivity has a logarithmic relationship with sound intensity.

The decibel, or dB, is defined mathematically as

$$\text{Power gain in dB} = 10 \log_{10} \frac{\text{power out}}{\text{power in}}$$

Suppose the gain is for an amplifier which has equal input and output resistances.

Then at the output:

$$V_{OUT} = I_{OUT} \times R_{OUT}$$

and at the input:

$$V_{IN} = I_{IN} \times R_{IN} = I_{IN} \times R_{OUT}$$

by Ohm's law: Dividing the two equations gives:

$$\frac{V_{OUT}}{V_{IN}} = \frac{I_{OUT}}{I_{IN}} \times \frac{R_{OUT}}{R_{OUT}} = \frac{I_{OUT}}{I_{IN}}$$

Now as Power out = $V_{OUT} \times I_{OUT}$
and Power in = $V_{IN} \times I_{IN}$

Therefore:

Gain in dB =

$$10 \log_{10} \frac{V_{OUT}}{V_{IN}} \times \frac{I_{OUT}}{I_{IN}} = 10 \log_{10} \left(\frac{V_{OUT}}{V_{IN}} \right)^2$$

By the rules of logarithms:

$$\log A^2 = \log (A \times A) = \log A + \log A = 2 \log A$$

Therefore:

$$10 \log_{10} \left(\frac{V_{OUT}}{V_{IN}} \right)^2 = 20 \log_{10} \frac{V_{OUT}}{V_{IN}} \\ = 20 \log_{10} (\text{voltage gain})$$

Usually in electronics, however, the assumption that input and output resistances must be the same is neglected, and for general use in electronics amplifier gain is given as above. Should the relationship $20 \log_{10}$ (voltage gain), ever be a negative value of dB, then the circuit whose gain it represents will attenuate.

Amplifier bandwidth is defined as the frequency which exists between the frequencies which causes the power gain to be reduced by a half.

However, in decibels,

$$\text{Power gain} = 10 \log_{10} \frac{P_{OUT}}{P_{IN}}$$

then at the half power points the new gains will be:

$$\text{Power gain} = 10 \log_{10} \frac{1}{2} \left(\frac{P_{OUT}}{P_{IN}} \right) \\ = 10 \log_{10} \frac{P_{OUT}}{P_{IN}} + 10 \log_{10} \frac{1}{2}$$

The term $10 \log_{10} \frac{1}{2}$ represents -3.010 decibels. (taken as -3.0 dB) therefore bandwidth can be redefined as the frequency band between the 3dB points of power gain. Fig. 4.1 demonstrates this.

An amplifier frequency response is usually plotted on log-linear graph paper, frequency along the log axis, gain along the linear axis. This means that the frequency range 1-10Hz will be displayed over a similar scale length to the 1,000-10,000 Hz range, and prevents information at the lower frequency end from being cramped.

The logarithmic characteristic of the ear has also given rise to the standard practice of using logarithmic potentiometers as radio/amplifier volume controls.

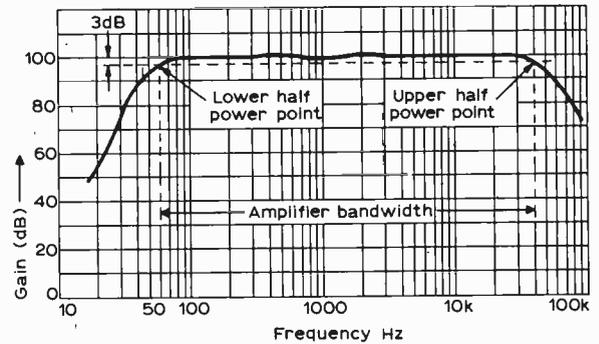


Fig. 4.1 : Amplifier bandwidth as defined by the half-power points.

This practice provides a linear increase in volume with rotation of the volume control whereas a linear potentiometer would provide a logarithmic increase in volume with volume control rotation.

Other Logarithms

Study of the table at the beginning of this article will lead to the conclusion that a logarithmic scale could be written for any base. However, with the exception of one number there are no other logarithmic scales which have much practical use.

The exception is the natural or Naperian logarithm, taken to the base of 'e' which has an approximate value of 2.71828.

Many physical and electrical systems obey formulae governed by natural logarithms, those with which we are concerned are limited to capacitor charge and discharge, however, the capacitance and inductance of concentric cables, parallel cables and numerous other combinations are dependent on natural log relationship.

The relationship with which we are mostly concerned is in the form:

$$y = A e^{-x} \dots\dots\dots(1)$$

$$y = A(1 - e^{-x}) \dots\dots\dots(2)$$

where A is constant, x and y are variable, and y is usually a function of time.

When $X = 0$, $e^0 = 1$ and for values of increasing X natural logarithm tables will give the necessary values.

Graphs given in Figures 4.2(a) and (b) result from equations. (1) and (2) respectively. The curves produced are "exponential" in shape.

Capacitors in d.c. circuits:

Place a capacitor directly across the terminals of a battery and it will "charge" almost instantaneously. Providing the dielectric is a good insulator then the charge will remain in the capacitor indefinitely. Place a resistor across the capacitor and current will flow in the resistor until the capacitor is discharged. Had the capacitor been connected to the battery, initially, through a resistor, then charging would have taken time.

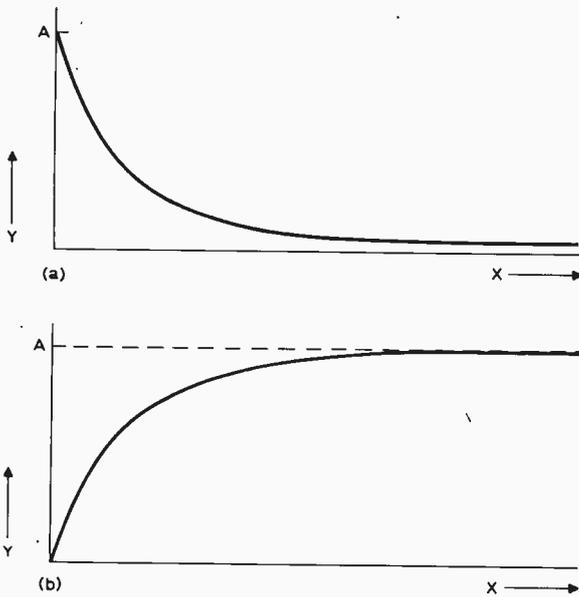


Fig. 4.2: Exponential curves derived from formulae. See text.

The speed at which capacitors charge and discharge in CR circuits depends on values of C and R which constitute the time constant $C \times R$.

For the series circuit shown in Fig 4.3, when the capacitor has no initial charge, the circuit relationships with time are determined by the equations:

$$i = I_{max} \cdot e^{-\frac{t}{CR}} \dots \dots \dots (3)$$

where I_{max} is obtained from Ohm's Law, i.e.

$$I_{max} = \frac{V}{R}$$

C is capacitance value in farads.

e.g. $5\mu F = 5 \times 10^{-6}$ Farads.

R is resistance in ohms.

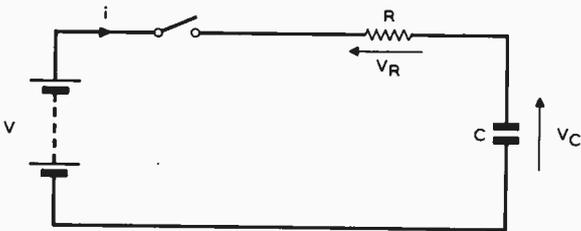


Fig.4.3: Basic circuit for investigating capacitor charging characteristics.

$$V_r = V - \frac{V}{e^{-\frac{t}{CR}}} \text{ which can be obtained from equation (3)}$$

by Ohm's law

$$\text{and } V_c = V (1 - e^{-\frac{t}{CR}})$$

The product $C \times R$ is known as the circuit time constant; t is the time after closing the switch. A characteristic of the C.R. circuit is that when the time after switching, $t=CR$ seconds, equation (3) will become:

$$i = I_{max} \cdot e^{-1}$$

and from Napierian logarithm tables this becomes.

$$i = I_{max} \times 0.3679.$$

Relating this to graph 4.2 (a) this means that in $C \times R$ seconds, the circuit time constant, the circuit current has fallen by $(1 - 0.3679) \times 100\%$
 $= 63.21\%$

By further investigation it will be seen that after a second time constant the current again will fall by approximately 63% of the current remaining after the first time constant. This would indicate that current would flow indefinitely. In practice however, it is usually assumed that three time constants are sufficient to charge or discharge a capacitor in a CR circuit.

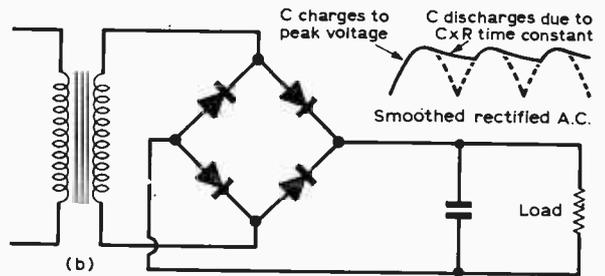
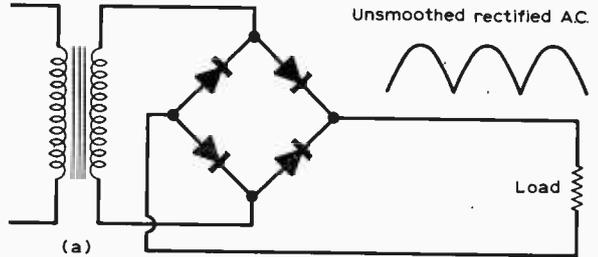


Fig. 4.4: (a) Unsmoothed output of a rectifier. (b) Action of a smoothing capacitor.

After three time constants the current has in fact changed by approx. 95% of its original value, if charging.

It should be noted that the time constant, $C \times R$ is made up in value of capacitance in farads and resistance in ohms. For $C = 1\mu F$, $R = 1M\Omega$ the time constant becomes:

$$1 \times 10^{-6} \times 1 \times 10^6 = 1 \text{ second.}$$

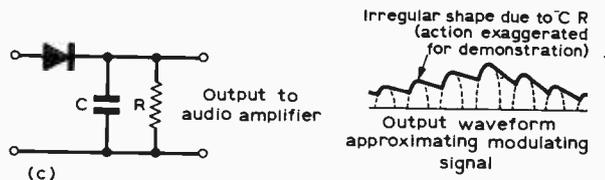


Fig. 4.5: Action of a smoothing capacitor applied to a detector circuit.

Charging and discharging of capacitors has numerous applications in power supplies, a.m. detectors and switching circuits (including multivibrators).


Power supply smoothing circuits are numerous in type. Fig 4.4 indicates capacitor operation and how the charge/discharge helps to smooth the output voltage.

An amplified amplitude modulated signal must be passed through a detector circuit to obtain the audio signal. Figure 4.5 demonstrates how the CR charge/discharge characteristic is utilised in this application.

Note that each of the CR circuits discussed assume that the capacitor charges almost instantaneously.

TO BE CONTINUED

A HYBRID MODULATOR

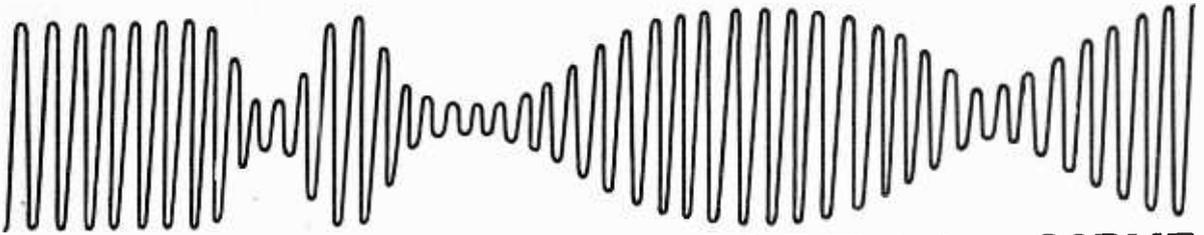

C.F. Fletcher G3DXZ

TO amplitude modulate an r.f. power amplifier one is faced with two basic choices. Firstly; produce a modulator capable of delivering just over half the power amplifier d.c. input-power and couple it into the final; or secondly, accept the maximum c.w. power available as the peak envelope power, reduce the mean carrier level to one quarter of this power and then modulate by a low power carrier control means.

When building a phone transmitter, high level anode/screen modulation, the first choice, has much to offer in terms of P.A. efficiency and ease of obtaining good results. Low power carrier control systems are generally favoured where space and cost considerations outweigh others or where the amplitude modulator is a second thought. It is not generally easy to obtain results from carrier control systems which are equal to those obtained from high level systems in terms of good quality modulation and ease of adjustment, but such results are possible and indeed easily obtainable with the system to be described.

SYSTEM THEORY

Series modulation is a very old system with very old drawbacks, the biggest one being the provision of a modulator valve capable of carrying the full P.A. current and a power supply capable of providing the modulators anode voltage and also handling the P.A. current. Now really all the modulator has to do is to vary the cathode potential in such a manner that the P.A. cathode current will vary linearly between zero and twice its unmodulated value. To overcome the nonlinearities of the control grid/cathode circuit, it is essential that the cathode current comes from a high source resistance and at the same time withstand the control grid volts necessary for P.A. current cut off.

Both of these functions can be provided by an n.p.n. transistor of the BFY51 variety. This transistor will stand 50V at the collector, more than enough to cut off most P.A. valves in the low and medium power range,

whilst its output resistance is very much larger than the input resistance of the P.A. cathode circuit.

MODULATOR CIRCUIT

Figure 1 shows the complete modulator circuit. It consists of a speech amplifier coupled via C3 to a current control section. The speech amplifier is formed by Tr1, Tr2 and Tr3 which make a simple 'ring of three' amplifier. The amplifier was designed for use with a crystal microphone and hence an input resistance of at least 100k Ω was needed. The input transistor Tr1 and its base bias circuit combine to produce an input resistance of about 20k Ω and R1 was introduced in series with the microphone to bring the input resistance up to the required minimum. Tr1 and Tr2 are directly coupled. At first glance this seems an unworkable arrangement as the collector voltage of Tr1 can only be equal to the emitter-base volts of Tr2. However, with silicon n.p.n. transistors, the switch-on base volts are 0.6V to 0.7V and the bottoming collector voltage is only 0.1V. For a small signal amplifier, 0.7V is adequate as a collector potential and direct coupling also results in economy of components and good frequency response; Tr2 and Tr3 are also coupled in this manner.

To obtain the maximum output voltage swing from Tr3, half the supply voltage needs to be dropped across R6 giving Tr3 a standing collector voltage of about 2.5V. The d.c. operating conditions of the 'ring of three' amplifier are stabilised by d.c.

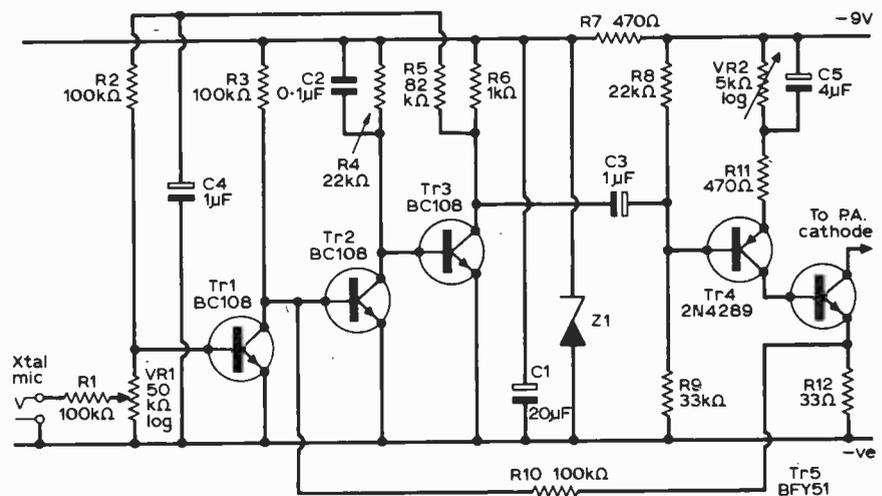


Fig. 1: The circuit of the modulator.

negative feedback via R2, R5 and VR1, giving good temperature stability. Capacitor C4 decouples the feedback loop at audio frequencies and allows a high audio gain to be achieved. Zener diode Z1, decouples the supply rail in conjunction with R7 and provides a stable d.c. voltage for the amplifier.

The P.A. current control system is formed by Tr4 and Tr5. Tr4 is a p.n.p. type whereas Tr5 is n.p.n. This choice of transistors again allows direct connection, collector to base, and no coupling components are required. Tr4 is a current source, the magnitude of the current being set by VR2. This current passes directly into the base of Tr5 which amplifies it and thus provides the P.A. cathode current.

The standing current produced by Tr4 is modulated by introducing the audio signal at its base, via C3. The maximum possible peak audio voltage is just less than half Tr3 supply volts, assuming best possible d.c. conditions, and this must be enough to swing Tr4 emitter current between zero and twice its standing value. To achieve this VR2 must be decoupled and R11 selected to provide the required current swing. The quoted value of 470Ω is sufficient to modulate a P.A. current of 50mA. If a greater standing PA current is to be controlled, R11 should be reduced until adequate control is achieved.

To linearise the audio amplifier and modulator, negative feedback is taken from the emitter of Tr5 via R10 and introduced at an early stage in the speech amplifier. As the emitter current of Tr5 is the cathode current of the P.A. stage, this feedback loop reduces distortion in the modulator by using the P.A. cathode current to produce the feedback voltage. This feature contributes directly to the good linearity of the modulator.

The power supply for the whole modulator is obtained from a 6.3V heater line, provided one side of the heater winding is earthed, using a silicon diode in a half-wave circuit. A positive supply of 7.5V to 8.0V is obtainable by this method, adequate smoothing being provided by C6.

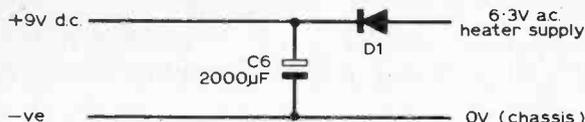


Fig. 2: The power supply circuit.

OPERATION AND ADJUSTMENT

The mechanism of setting up a carrier control modulator of this type is simplicity itself but the implications of such adjustments are not always so readily appreciated. So to begin with, the setting up procedure is as follows:


1. Set the P.A. current control (VR2) for maximum current. This will result in Tr5 bottoming and having no effect upon the P.A. current.

2. Tune up the P.A. to the maximum it will take. This statement assumes a medium-sized rig, 20 to 60 watt variety, and not on Top Band!

3. Note the maximum "loaded" P.A. current and reduce it using VR2 to half maximum.

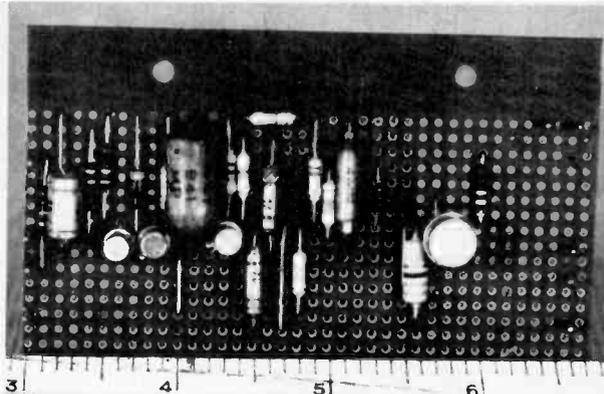4. Adjust the modulator gain, VR1, to produce a fully modulated carrier preferably using an oscilloscope.

The transmitter will now produce a fully modulated carrier with a mean carrier power one quarter



MADE IN ENGLAND
The completed modulator on Veroboard.

of the maximum reached in stage 2 of the setting up. Note carefully, that the P.A. loading should not be adjusted after the P.A. current has been reduced by VR2 to less than the maximum value. This is a temptation which must be resisted, for if tried, one will find that the output can be increased—in fact doubled! However, after such an adjustment, only downward modulation is possible and all that will be achieved is a poorly modulated carrier.

The reason for this apparent shortcoming becomes clear if the mechanism of the modulation system

★ components list

Resistors :

R1	100kΩ	R7	470Ω
R2	100kΩ	R8	22kΩ
R3	100kΩ	R9	33kΩ
R4	22kΩ	R10	100kΩ
R5	82kΩ	R11	470Ω
R6	1kΩ	R12	33Ω

All 5% tolerance, ½ watt except R12, ¼ watt

VR1 50kΩ log. pot.

VR2 5kΩ log. pot.

Capacitors :

C1	20µF 16V	C4	1µF 16V
C2	0.1µF 150V	C5	4µF 16V
C3	1µF 16V	C6	2,000µF 16V

Semiconductors

Tr1	BC108 or BC168	Tr5	BFY51
Tr2	BC108 or BC168	D1	Rectifier silicon diode,
Tr3	BC108 or BC168		100V p.i.v., 250mA
Tr4	2N4289 or 2N3702	Z1	4.7V zener diode,
			400mW, 20%

Miscellaneous :

Crystal microphone, input jack, Veroboard

is considered. Such consideration also highlights the necessity for the unusually high initial setting up powers.


An amplitude modulated carrier varies in amplitude, at 100% modulation, between zero and twice mean carrier. Now if the mean carrier is represented by a voltage E, then it will rise to 2E on peaks. The voltage E delivers a mean carrier power P into some

load resistance R, hence $P_{\text{mean}} = \frac{E^2}{R}$. Now when on

peaks E becomes 2E, then $P_{\text{max}} = \frac{(2E)^2}{R} = 4 P_{\text{mean}}$.

—continued on page 230

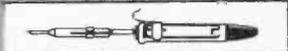take a good look at **ANTEX** miniature soldering irons



G 13 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 32/6.



E 20 watts. Fitted with 1/4" bit, interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From 35/-.




ES 25 watts. Fitted with 1/8" bit, interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From 36/-.



F 40 watts. Fitted 5/16" bit, interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From 42/6. Spare bits and elements for all models and voltages immediately available from stock.

Complete precision soldering kit

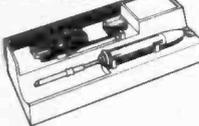

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 16 watts miniature iron, fitted 3/32" bit, interchangeable spare bits 3/32", 1/8"
- Real of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **49/6**



Model CN 240/2
15 watts - 240 volts
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **31/-**



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.
Telephone: Plymouth 67377/8.
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons

Quantity	Model	Bit Size	Volts	Price
.....
.....

I enclose cheque/P.O./cash value

NAME

ADDRESS

PW7

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
 THE VALVE SPECIALISTS Telephone 01-722 9090
 SAVE POSTAL COSTS! CASH AND CARRY BY CALLERS WELCOME

OA2 5/9	6BA6 4/6	6P26 12/-	12AV6 5/6	30P4 12/-	AC2PEN/	DLS10 9/6	ECC82 4/6	EL33 12/-	KT61 12/-	PCL85 9/-	R18 10/-	U19 84/6
OB2 6/0	6BE6 4/6	6P28 25/-	12AX7 4/6	30P4M 17/6	DD 19/6	DM70 7/6	ECC83 4/6	EL34 10/6	KT63 5/6	PCL86 9/6	R19 7/6	U22 7/0
OZ4 4/0	6BH6 7/6	6Q7 8/6	12AY7 9/9	30P4M 17/6	AC2PEN/7/6	DM71 7/6	ECC84 6/3	EL37 17/3	KT66 17/3	PCL88 16/-	R20 11/9	U25 12/0
LA3 4/0	6BR6 9/6	6Q7G 8/6	12BA6 6/0	30P12 12/9	AC/CPEN/6	DW4/3500/6	ECC85 5/6	EL41 11/-	KT74 12/6	PEN36C15/-	R52 7/6	U26 11/9
LA5 5/0	6BQ6 4/9	6R7 11/-	12BE6 5/9	30P19 13/9	AC/CPEN/7/6	DY87 5/9	ECC86 9/-	EL42 10/6	KT76 12/6	PEN45 7/-	RK34 7/6	U31 6/0
LA7GT 7/3	6BQ7A 7/6	6R7G 7/6	12BR7 6/0	30P19 13/9	AC/CPEN/7/6	DY87 5/9	ECC87 7/6	EL41 10/6	KT78 12/6	PEN45D1/-	RF42 12/6	U33 29/6
IC5 4/0	6BR7 15/9	6SA7GT 7/6	12E1 17/-	30P11 13/9	AC/TH110/10	E80F 24/-	ECC89 9/6	EL33 7/6	KT81 12/6	PEN46 15/-	RF41 12/6	U36 16/6
ID5 7/6	6BR8 12/6	6SA7GT 7/6	12J7 10/6	30P14 15/6	AC/TP 10/6	E80F 24/-	ECC89 9/6	EL33 7/6	KT82 12/6	PEN46 4/-	TH4B 10/0	U37 24/11
ID6 9/6	6BR8 25/-	6SCTGT 6/6	12K6 10/0	30P14 15/6	AC/VP10/6	E80F 24/-	ECC89 9/6	EL33 7/6	KT83 12/6	PEN46 4/-	TH4B 10/0	U45 15/6
IFD1 6/6	6BW6 14/3	6SCTGT 6/6	12K7GT 6/6	30P15 15/6	AC/VP10/6	E80F 24/-	ECC89 9/6	EL33 7/6	KT84 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
IFD8 4/3	6BW7 13/-	6SH7 3/-	12Q7GT 5/6	30A3 10/-	AL60 15/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT85 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
IG8 6/0	6BZ6 6/0	6S7 6/6	12SA7GT 6/6	30A5 10/-	ARF3 7/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT86 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
1H5GT 7/0	6C8 3/9	6SK7GT 4/6	8/0	30A5 10/-	ATP4 2/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT87 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
LL4 2/6	6C9 14/6	6SN7GT 4/6	128C7 5/6	30A5 10/-	AZ1 8/0	E180F 19/-	ECC89 9/6	EL33 7/6	KT88 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
LLD5 6/0	6CD6G 22/6	6SQGT 7/6	128G7 4/6	30A5 10/-	AZ31 4/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT89 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
LLN5 8/0	6C6H 7/0	6U4GT 12/6	128H7 3/6	30A5 10/-	AZ31 4/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT90 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
1N5GT 7/9	6CL8 9/6	6U7G 10/6	128J7 4/6	30A5 10/-	B36 6/0	E180F 19/-	ECC89 9/6	EL33 7/6	KT91 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
1R5 5/6	6CW4 12/6	6V8G 3/6	128K7 4/6	30A5 10/-	CL33 18/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT92 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
1R4 4/9	6D3 7/6	6V8GT 6/6	128QGT 6/6	30A5 10/-	CV6 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT93 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
1R5 4/3	6D6 3/0	6X4 4/3	14K7 9/6	30A5 10/-	CYC 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT94 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
1U4 5/9	6F1 12/6	6X5GT 6/6	1487 15/6	30A5 10/-	CY31 7/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT95 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
2D21 6/6	6F6 12/6	6Y7G 12/6	19A5 4/6	30A5 10/-	D63 5/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT96 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
3A5 10/0	6F6G 5/0	7B6 10/9	19E1 4/0	30A5 10/-	D77 2/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT97 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
3B7 5/6	6F12 3/6	7B7 7/0	20D1 13/6	30A5 10/-	DAC32 9/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT98 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
3D6 3/9	6F13 3/6	7C6 6/6	20D4 20/6	30A5 10/-	DAC32 9/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT99 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
3Q4 7/6	6F15 10/0	7F8 12/6	20F3 2/6	30A5 10/-	DAC32 9/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT100 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
3Q6GT 6/6	6F18 7/6	7H7 5/6	20L1 2/6	30A5 10/-	DAC32 9/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT101 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
3V4 5/6	6F23 14/3	7R7 13/0	20P1 17/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT102 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
3M4 6/3	6F24 13/6	7V7 5/0	20P3 17/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT103 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
5R4GY 10/6	6F25 13/6	8W6 7/0	20P4 18/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT104 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
5U4G 5/6	6F26 14/0	8D7 15/6	20P5 20/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT105 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
5V4G 7/6	6F32 3/0	10C1 28/6	25L6GT 5/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT106 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
5Y3GT 5/6	6H6GT 3/0	10C2 10/0	25Y5 6/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT107 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
5Z3 9/0	6J5G 3/9	10D1 8/0	25Y5G 6/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT108 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
5Z4G 7/0	6J6 3/0	10D2 14/6	25Z4G 6/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT109 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6R0L2 12/6	6J7G 4/9	10F1 18/0	25Z5 6/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT110 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AG 6/6	6J7GT 6/6	10F9 9/0	25Z6G 9/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT111 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AC7 3/0	6K7G 2/0	10F18 7/0	30C1 6/0	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT112 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6A05 4/0	6K7GT 4/6	10L1D11/0	30C15 13/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT113 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AK5 5/0	6K8G 4/0	10P13 13/6	30C17 16/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT114 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AK6 6/0	6L1 19/6	10P14 20/0	30C18 14/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT115 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AL5 2/6	6L6GT 7/9	12A6 12/6	30P5 16/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT116 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AM6 3/3	6L7GT 12/6	12AC6 7/6	30P11 13/9	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT117 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6A05 5/6	6L16 6/0	12AD6 7/6	30P12 15/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT118 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AR6 2/0	6L19 27/6	12AE6 12/6	30P12 15/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT119 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AT6 4/0	6LD20 9/6	12AB6 4/6	30P14 14/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT120 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6A06 5/6	6N7GT 6/6	12AT7 3/9	30L1 6/3	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT121 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6AV6 5/6	6P1 12/6	12AU6 4/9	30L15 13/9	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT122 12/6	PEN46 4/-	TH4B 10/0	U47 13/6
6B80 2/6	6P26 12/6	12AU7 4/6	30L17 15/6	30A5 10/-	DD4 10/6	E180F 19/-	ECC89 9/6	EL33 7/6	KT123 12/6	PEN46 4/-	TH4B 10/0	U47 13/6

All goods are new and subject to the maker's guarantee. We do not handle manufacturers' seconds, nor rejects, which are often described as "new and tested" but have a limited and unreliable life. Business hours Mon.-Fri. 9-5.30 p.m. Sats. 9-1 p.m. Terms of business. Cash with order only. Post/packing 6d. per item. Orders over 25 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 6d. extra. Complete catalogue of valves, transistors and components with conditions of sale, price 10d. post free. No enquiries answered unless S.A.E. enclosed for reply.

NEW BOOKS

(Editors & Engineers)
RADIO HAND BOOK
 18TH EDN.
 by William I. Orr (April) 105/-

HOW TO USE INTEGRATED
 CIRCUIT LOGIC ELEMENTS
 by J. W. Streater (March) 28/-

101 QUESTIONS & ANSWERS
 ABOUT HI-FI & STEREO
 by Leo G. Sands & Fred
 Shunaman (March) 24/-

SWL & ANTENNA
 CONSTRUCTION PROJECT
 by Edward M. Noll (June) 25/-

ABC'S VOLTAGE-DEPEN-
 DENTS & RESISTORS
 by Rufus P. Turner (June) 22/-

WORKSHOP IN SOLID STATE
 by Harold E. Ennes (July) 65/-

TAPE RECORDER SERVICING
 GUIDE
 by Robert G. Middleton (July) 35/-

ABC'S OF THERMISTORS
 by Rufus P. Turner (July) 22/-

FOULSHAM-SAMS TECHNICAL BOOKS

(W. FOULSHAM & CO. LTD.)
 YEovil RD., SLOUGH, BUCKS, ENGLAND

LOOK AT THESE PRICES

CARTRIDGES
 Acos GP67-2, GP91-38C 22/6; Acos GP93-1 26/8;
 Acos GP94-1 32/6; Sonotone 9TAHC 39/6; All
 above in makers cartons; Japanese Stereo 16/-.

1 WATT AMPLIFIER
 Complete with volume control, rectifier, smoothing
 cct, fully transistorised, OUR PRICE 27/6

PLUGS & SOCKETS
 Phono plugs, red, white, yellow, green, grey, blue,
 black 11d/9 per doz; Coaxial plugs, aluminium 1/6;
 Coaxial couplers 1/-; 2 pin DIN plugs 3/6; 3 pin
 DIN pins 3/6; 5 pin DIN pins 3/6; 2 pin, 3 pin
 DIN sockets 1/6; wandler Plugs 6d; sockets 8d;
 Banana plugs 1/1, sockets 1/-; 3.5mm J/Plugs 1/6
 & 8/8; Standard J/Plugs with solder terminals 3/-;
 Chrome 3/-; Side Entry J/Plugs black and chrome
 4/9; Insulated J/sockets, o/cct 3/3, c/cct 3/6.

ELECTROLYTIC CAPACITORS
 4uF, 150v 9d; 8uF 500v 3/-; 8uF 12v 10d; 8uF 4/
 8uF 450v 4/3; 10uF 150v 9d; 12uF 25v 9d; 16uF
 450v 2/8d; 16uF 16uF 450v 4/3; 30uF 10v 9d; 50uF
 10v 9d; 100uF 9v 9d; 100uF 12v 9d; 150uF 12v 9d;
 320uF 9v 1/-; 1500uF 30v 3/9; 2000uF 30v 4/2;
 5000uF 25v 10/-; 10,000uF 25v 15/-; 20,000uF
 30v 21/-.

MICROPHONES
 Acos Mic 45 22/6; Acos Mic 60 19/11; Planet CM70
 30/-; Hand Mike 15/-; Shure 201 5/5; Shure 444
 110.10.0.

VALVES
 FY81 7/2; PCL82 7/9; EF183 9/-; EF184 9/-.

GEORGE FRANCIS (Dept PW),
 93 Balderton Gate, Newark, Notts.
 Telephone: Newark 4733.

4-STATION INTERCOM

£7.5.0.

Solve your communication
 problems with this
 4-Station Transistor Intercom system (1 master and
 3 slave), in de-luxe plastic cabinets for desk or wall
 mounting. Call/talk/listen from Master to Slaves and
 Slaves to Master. Ideally suitable for Business, Sur-
 gery, Schools, Hospital, Office and Home. Operates
 on one 9V battery. On/off switch. Volume control.
 Complete with 3 connecting wires each 66ft. and
 other accessories. P. & F. 7/6.

MAINS INTERCOM
 No batteries—no wires. Just plug in the
 mains for instant two-way, loud and clear
 communication. On/off switch and volume
 control. Price £11.19.6. P. & F. 8/6 extra.


INTERCOM/BABY ALARM

Same as 4-Station Intercom for two-way instant
 communication. Ideal as Baby Alarm and Door
 Phone. Complete with 66ft. connecting wire.
 Battery 2/6. P. & F. 4/6.

Transistor TELEPHONE AMPLIFIER
 59/6

Why not boost
 business effi-
 ciency with this incredible De-luxe Telephone Ampli-
 fier. Take down long telephone messages or converse
 without holding the handset. A useful office aid. On/
 off switch. Volume Control. Battery 2/6 extra. P. & F.
 3/6. Full price refunded if not satisfied in 7 days.
SWEET LONDON DIRECT SUPPLIES (P/W4)
 169 KENSINGTON HIGH STREET, LONDON, W.8.

TRANSMITTER / RECEIVER

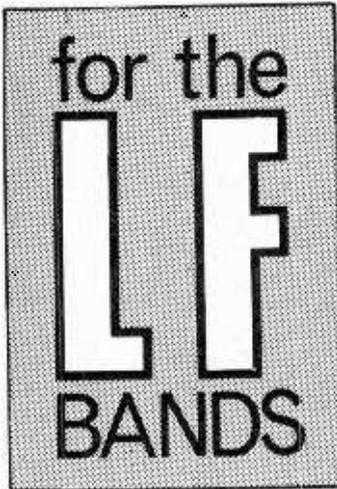

F.G. RAYER
G3OGR

Continued from
last month

RF Power Amplifier. Connect a 15 watt household lamp to a co-axial plug and insert in the aerial socket, or clip the lamp across VC3/4. To load the p.a. turn VC3/4 to maximum capacity, switch to transmit, and tune VC2 until the meter shows a dip in anode current. Input will be low and is raised by decreasing VC3/4, meanwhile readjusting VC2 for minimum current. At 9-15W input (30-50mA) the lamp should be quite bright.

Microphone Amplifier. The external lead must be screened in the usual way, and the connection from microphone socket to pin 7 of V4A runs against the chassis. Other leads should be clear of the heater connection X. Screened lead is used for connections to S5. Audio from the receiver was not taken to V4B because the extra stage of amplification was found unnecessary. The audio amplifier can be tested by temporarily shorting S5 and S7, the microphone and loadspeaker being well separated to avoid feedback.

Load up the transmitter into the lamp as described and tune in the signal with an independent receiver (r.f. gain of the latter should be at minimum, and the aerial removed). Speech into the microphone should sound clean and clear in the receiver speaker.

V5 operates at about maximum ratings on transmit, but screen grid and anode voltages fall to about 220V on receive, bias across R15 then dropping to about 10V.

Receiver RF Stage. It is only necessary to adjust the core of L4 so that VC5 is about half closed when resonant at 1.9MHz. VR1 is the r.f. gain control which is useful with very strong signals, and some kinds of noise.

Mixer and Oscillator. L4, L5 and L6 have small trimmers incorporated during manufacture. VC6/VC7 can have a maximum capacitance of about 20pF each section. The core and trimmer of L6 are adjusted to give coverage of about 1.8-2.0MHz, with a little to spare at the ends. The core of L5 is then adjusted near 1.8MHz, and the trimmer near 2.0MHz, for best reception.

With a given value for VC6/VC7, frequency coverage falls as L5/L6 trimmers are adjusted to

higher capacitance, the cores being unscrewed to restore band coverage. On the other hand, frequency coverage increases as inductance is increased by adjusting the cores, and the trimmers are re-set to a lower capacitance. In this way the receiver tuning can be closely matched to the v.f.o. tuning. It is also possible to use a 25pF+25pF or similar gang, with extra 30pF trimmers for both sections, L5 and L6 cores being unscrewed to compensate.

IF Circuits. A connection should pass across the holder for V8, as in Fig. 3, earthing the central spigot, or instability is likely. The four i.f.t. cores should be adjusted with a proper tool, either with a signal generator set to about 465kHz and fed to the input of V7 or with a stable signal. To avoid using shunts for a more sensitive meter the 50mA panel instrument reads the whole receiver current. This is about 30-35mA with no signal, falling to 25mA or so with average signals, or 15mA or so with the v.f.o. on and tuned to the receiver frequency. The procedure is thus to tune for minimum meter current and to peak VC5, cores and trimmers for lowest minimum.

It would be feasible to use a 1mA meter, with a shunt giving 0-50mA on transmit, and any standard S-meter circuit on receive but the metering as shown was found satisfactory.

Connections to VR2 were screened as shown in Fig. 3.

Power Circuit. With the transformer, rectifiers and choke listed, 300V was available at 100mA for transmission. With other transformers or chokes, it might be necessary to change R17 and R18. These may be increased if more than 300V is found at the anode of V3 or V5.

General Points

Tag strips help to secure various items, as shown in Fig. 3. Well insulated leads should be used where high voltages are present except for r.f. wiring. In many places 0.02 μ F 500 V disc ceramics, and 1800pF 1kV ceramics, are used as the cost of these is only a few pence but in most circuit positions other reasonable values can be fitted.

In case of any difficulty the equipment can be tested in sections—the receiver, alone and with V5, then V4A/B, and each stage of the transmitter r.f. circuit, and power pack.

Switching

Details of this have been mentioned and connections should be checked against Fig. 1. The switch must be a "break before make" type. A 3-way "make before break" switch can be used the central way being ignored. This was actually done the click mechanism modified accordingly.

As those switch tags which lie near the chassis cannot be reached very easily it is wise to solder on coloured leads beforehand, the colours used being marked on the circuit.

The section nearest to the co-axial lead and VC3/4

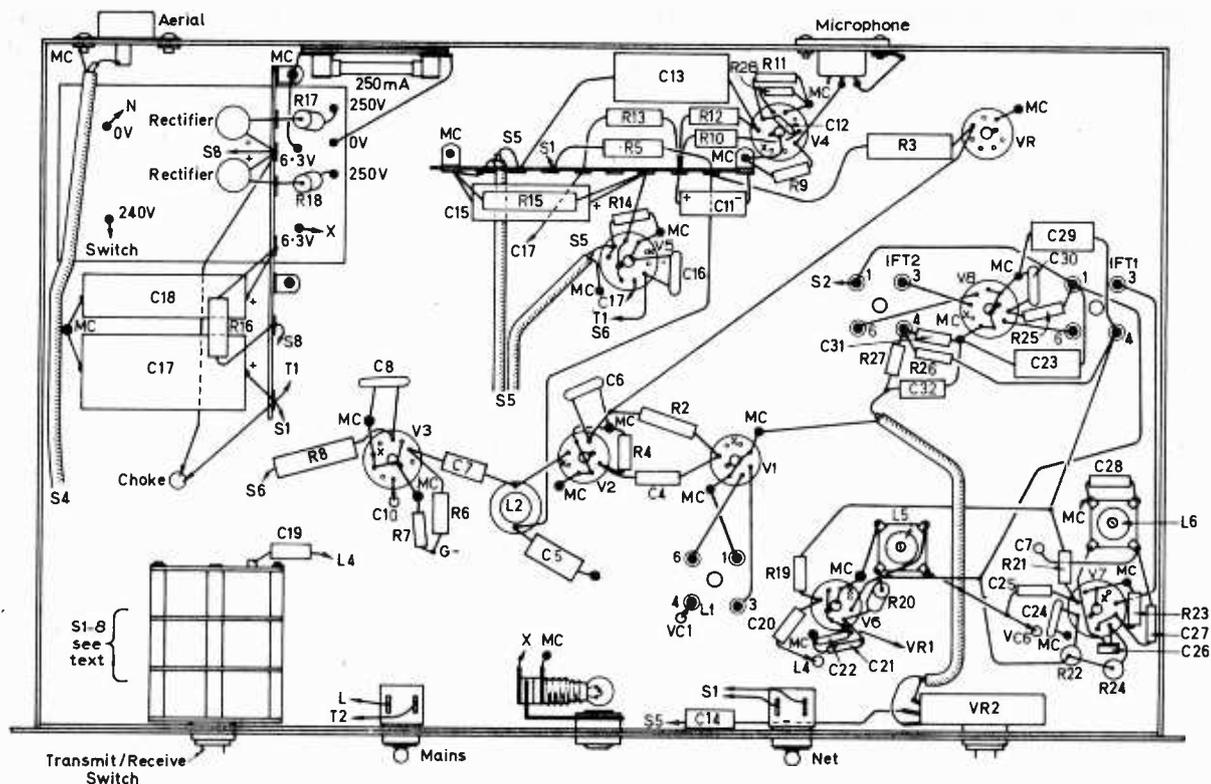


Fig. 3: Underneath of chassis with practical wiring details

is used for C4. S2, S3 and S6 can be adjacent on one wafer. S5 is on a separate wafer. If necessary, check with a meter after wiring, with the switch alternately in transmit and receive positions.

Notes on use

The v.f.o. is best calibrated with the aid of a 100kHz crystal marker, by tuning in the harmonics on 1.8, 1.9 and 2.0MHz, on a separate calibrated receiver and setting the v.f.o. to zero beat, and marking the frequency on the scale. Intermediate markings can be estimated, or found by using a receiver on the 3.6-4.0MHz range. The 2nd harmonic of 1.85MHz will be heard on 3.7MHz, and so on.

VC1 is a double-bearing metal frame type, with fixed plates well screened. A box 2 x 2½ x 4in. encloses VC1 and L1. This item is readily made from a "universal chassis" (Home Radio) 9 x 2in. flanged runner, cut to bend 2½in. from each end. The flanges can then be bolted to chassis and panel, and the top closed with a 4 x 2½in. plate fixed with self-tapping screws.

Input should not be over 10W on Top Band, and loading is carried out in a similar manner to that described using a lamp. The aerial can be a random length of wire, or a planned 160m system. Some aerial lengths fall outside the matching capability of the pi tank circuit. The simplest method of correcting this is to place a loading coil between the aerial socket and aerial, if a tuner is not available. The coil can be similar to that wound for L3, and should have eight or ten windings. The number of turns in circuit can then be adjusted

until normal tuning is possible. Such a method allows full power input with very short aeri- als, but a longer aerial will naturally give greater signal strength.

80m Working

An end-fed wire on 160m can also be used on 80m. At times this band is more active than 160m and is also capable of longer distance contacts.

The circuit in Fig. 1 has been found to give very good results on 80m, so it is quite in order to use it for this band, or for both 160m and 80m. For single band working on 80m a VFO4 unit is fitted instead of the VFO2, and calibrated for 3.5-3.8MHz. L2 is broadly resonant at about 3.65MHz. L3 is either an 80m tank circuit or one half the 160m tank circuit described. For VC2, about 500pF may be retained, but 250pF is adequate.

In the receiver section, L4, L5 and L6 are replaced by 3.5MHz type bandspread aerial, mixer and oscillator coils. C28 is 2000pF.

For switched 2-band working, which has also proved successful, the VFO2 unit can be adjusted to cover about 1.75-2.0MHz. The 1.8-2.0MHz sector is used for 160m, and the 1.75-1.9MHz section for 80m. For 80m, one-half of L3 is shorted by an on-off switch near L3, and connected from VC3/4 to a centre-tap on L3. V2 anode circuit is switched from L2 to an 80m coil, to double the v.f.o. frequencies.

In the receiver, a 2-way 6-pole switch is required, to transfer from 160m to 80m coils. An extra pole on this switch can change over the coils for V2. ■

MICRO SWITCH

5 amp. changover contacts, 1/8 each, 18/- doz. 15 amp Model 2/- each or 21/- doz.



TOGGLE SWITCH

3 amp 250v. with fixing ring, 1/6 each, 15/- doz.

CONSTRUCTORS PARCEL

1. Plessey miniature 2 gang tuning condenser with built in trimmers and wave gang switch. 2. Ferrite slab aerial with coils to suit the above tuning condenser. 3. Circuit diagram giving all component values for 6 transistor circuit covering full medium wave and the long wave band around Radio 2. The three items for only 7/6d which is half of the price of the tuning condenser alone.

10 AMP 24V BATTERY CHARGER

Ideal unit for garage, boat station etc. £22.10.0d. each plus carriage and cost.

BEHIND THE EAR DEAF-AID

Made by a very famous maker. Thoroughly overhauled, cleaned and re-conditioned. Guaranteed 6 months. Regular price around £50. Our price £10.

ISOLATION TRANSFORMERS 200-250 Mains

A must if you work on mains equipment. Prevents accidents and shocks even in damp conditions. Input and output separately screened by connection block. 100 watt £23.10.0. 250 watt £25.

SLOW MOTION DRIVES

For coupling to tuning condensers etc. One end in shaft, the other end fits to a 1/4 in. shaft with grub screws. Price 4/6 each 48/- dozen.

LARGE PANEL MOUNTING MOVING COIL METERS

Size 5in. x 4in. Centre zero 200-0-200 micro amp made by Sangamo Weston. Regular price probably £8. Our price 59/6. ditto but 100-0-100 79/6. A.C. Ammeter 0-5 amps. flush mounting—moving iron. Ex equipment but guaranteed perfect 99/6.

CIRCUIT BOARDS

Heavy copper on 3/32 paxolin sheet ideal for making power packs etc. as sheet is very strong and thick enough to allow copper to be cut away with hacksaw blade. 5in. x 5in. 1/6 each. 15in. x 5in. 4/6d. each.

6KVA Auto-transformer in ventilated sheet steel case—tapped 110v-140v-170v-200v-230v. Ex equipment but guaranteed perfect £19.10.0. carriage at cost.

PP3 BATTERY ELIMINATOR

Run your small transistor radio from the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 8/6 each.



REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature. 1in. long x approximately 1/4 in. diameter. Will make and break up to 1A up to 300 volts. Price 2/6 each. 24/- dozen.
Standard. 2in. long x 3/16 in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 2/- each. 18/- per dozen.
Flat. Flat type, 2in. long, just over 1/16 in. thick, approximately 1/4 in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each. 32/- per dozen.
Small ceramic magnets to operate these reed switches 1/9 each. 18/- dozen.

0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits 2/6 each, 24/- doz.

SUB-MINIATURE MOVING COIL MICROPHONE

as used in behind the ear deaf aid sets also as carbon type only 1/4 in. x 1/4 in. Regular price probably £3 or more. Our price 19/6. Note these are ex-equipment but if not in perfect working order they will be exchanged.

Chart Recorder Motor. Small 2" diameter (approx) instrument motor with fixing flange and spindle (1/2" long, 1/4" diameter) integral gear box gives 1 rev per 24 hours. 19/6.

Ignition (E.H.T.) Transformer made by Parmeko Ltd.. Primary 240V 50 cps. Secondary 5KV at 23 mA. Size approx. 4 1/2" x 3 1/2" x 2 1/2" thick. 99/6 plus 4/6 p. & p.

12V EXTRACTOR FAN BY DELCO

Ideal for ventilation in Caravan, Car or Boat. 6 Bladed 5" diameter fan inside heavy duty cylinder with 3 point fixing flange. 5 1/2" diameter fixing hole. Length approx. 4 1/2". Exceptional bargain 87/6 plus 5/6 post and insurance.

4 Push Switch. Ideal to control fan Heater, etc. 3 on switches and 1 off. Contacts rated at 15 amp on all switches. 4/6 each, 48/- doz.

INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. The ICs are all single silicon chip General Purpose Amplifiers. Regular price of which is well over £1 each. Full circuit details of the ICs are included and in addition you will receive a list of 50 different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only £1 post paid; or list and all data 10/- post free. Credited when you order IC's value of 30/- and upwards.



24 HOUR TIME SWITCH

Mains operated. Adjustable Contacts give 2 on/off periods per 24 hours. Contracts rated 15 amps, repeating mechanism so ideal for shop window control, or to switch hall lights (anti-burglar precaution) while you are on holiday. Made by the famous Smiths Company. This month only 29/6 with Perspex cover, plus 3/6 postage and insurance, a real snip which should not be missed.



DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets and on/off switch with neon warning light (in metal box). Takes standard 13 amp fused plugs. Supplied complete with 7 feet of heavy cable. £9/6 wired up, ready to work plus 4/6 post & insurance. 5 amp 3 pin model 85/-, 15 amp 3 pin model 45/-

BARGAIN OF THE YEAR

MICROSONIC

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/4 x 1 1/4 in.—complete with soft leather zippered bag. Specification—Circuit—7 transistor superheterodyne. Frequency range, 530 to 1600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency 465 Kc/s or 455 Kc/s. Power output 40mW. Antenna: ferrite rod. Loudspeaker Permanent magnet type. In transit from the East these sets suffered a slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only 24/6 plus 2/6 post and insurance rechargeable batteries 8/6 post. Plug in mains charger 12/6.

THE 5-5 WATT STEREO AMPLIFIER


Made by one of our most famous makers for a de-luxe player. This amplifier has a quality of reproduction much better than average. Using a total 16 transistors and a generously sized mains power pack. Controls include bass, treble, balance and volume. Suitable for 8-16 ohm impedance speakers with crossovers for tweeter mid-range and bass thus giving option of 1, 2 or 3 speakers per channel. Offered at about one third of its original price only £9.19.6d. plus 6/6d post and insurance.

THIS MONTH'S SNIP

Coloured Fluorescent tubes for special lighting effects. Wonderful for lighting the loggia or summer garden. All tubes perfect not seconds. Made by Atlas, Echo or similar companies. 2 ft. suitable for working at 20 or 40 watts depending upon choke used. Available in the following colours—Red, Yellow, Blue, Peach, Daylight, Natural, White. Special snip price on any quantity up to 12 when they would be post free. Note: Two tubes may be run off one choke. We can supply suitable choke, two starters and all other fittings required for 29/6 plus 4/6 post per kit.

1 HOUR MINUTE TIMER

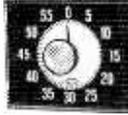Made by famous Smiths company, these have a large clear dial, size 4 1/2 x 3 1/2, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch 22/6.




A.C. CONDENSERS

These make good voltage droppers for working low voltage appliances from AC mains—the big advantage being there is no heat. Also useful in power factor correction, motor starting and in DC circuits where reverse voltage is encountered.

1.5 mfd 400v 3/6	5 mfd 570v 9/6	12 mfd 250v 11/6
2 mfd 440v 4/6	6.25 mfd 250v 8/6	15 mfd 250v 13/6
3.4 mfd 440v 6/6	8 mfd 250v 9/6	20 mfd 275v 16/6
3.5 mfd 250v 5/6	8 mfd 440v 11/6	

RE-CHARGEABLE TORCH

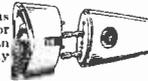Neat flat torch, fits unobtrusively in your pocket, contains 2 Nicad cells and built-in charger. Plugs into shaver adaptor and charges from our standard 200/240 volt mains. American made, sold originally at over 4 dollars. Our price only 19/6 each.



3kW TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running, is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 79/6. Postage and insurance 6/6. Don't miss this.



3 STAGE PERMEABILITY TUNER

This Tuner is a precision instrument made by the famous "Cydion" Company for the equally famous Radiomobile Car Radio. It is a medium wave tuner (but set of longwave coils available as an extra (if required) with a frequency coverage 1620 Kc/s-825 Kc/s and intended to operate with an I.F. value of 470 Kc/s. Extremely compact (size only 2 1/2 x 2 1/2 in. thick) with reduction gear for fine tuning. Snip price this month 12/6, with circuit of front end suitable for car radio or as a general purpose tuner for use with Amplifier. Post Free.



NEED A SPECIAL SWITCH

Double Leaf Contact. Very slight pressure closes both contacts, 1/8 each, 18/- doz. Plastic push-rod suitable for operating, 1/- each, 9/- doz.




50-Way Connector Block. Heavy duty block, size 2 1/4 in. x 3 1/4 in. x 1 1/4 in. approximately. Each of the 50 ways has a multi cable inlet and outlet designed for easy connection. Also, each way has 2 test sockets and a disconnecting plug. Ideal for inserting ammeter or other device without breaking circuit, offered at 69/6 each, which is only a fraction of the regular price, postage and insurance 5/6.

Under-floor Heating Cable. 200ft. lengths, suitable for dissipating 1,000 watts at 80 volts. Join three in series to make a 240 volt mains operated element of 3kW. Price 29/- per length, 4/6 post on any quantity.

3-Core Leads. Heavy duty 23/38, average length 5ft. 10/- per dozen lengths, plus 4/6 P. & I.

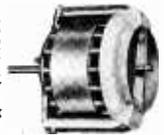Papet Motors. Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. 39/- each.



Instrument Knobs. 1/4 in. dia. head with 1/4 in. shank for flatted 1/4 in. spindle. 9d. each, 8/- dozen. Ditto but with metal disc, 1/- each, 11/- dozen.




Midget Output Transformer. Ratio 140:1. Size approx. 1 1/4 in. x 1 1/4 in. x 1 1/4 in. primary impedance 450 Ω. Connection by flying leads. 4/8 each 48/- doz.

Midget Output Transformer. Ratio 80:1. Size approx. 1 1/4 in. x 1 1/4 in. x 1 1/4 in. Primary impedance 132 Ω. Printed circuit board connection. 5/6 each. 23 doz.



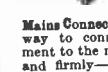4-Gang Air Spaced Tuning Condenser for AM/FM circuits. AM rf section 200 pf sec section 80 pf both with trimmers.—FM rf section 9.5 pf sec section 12 pf—integral slow-motion drive 9/6 each.



Mains Connector. A quick way to connect equipment to the mains safely and firmly—L, N, and E, coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one bar wire on up to four 7.029 cables. 12/6 each



CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electronically changes speed from approximately 1/2 to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions 19/6, plus 2/6 post and insurance. Made up model also available 37/6 plus 2/6 p. & p.

ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 89/6, less than the value of the clock alone—post and insurance 2/9.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP8, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 16/6, plus 3/6 postage.

Where postage is not stated then orders over £5 are post free. Below £5 add 2/- S.A.E. with enquiries please.

ELECTRONICS (CROYDON) LTD
Dept. PW, 266 London Rd., Croydon CP0-2TH
Also 102/3 Tamworth Road, Croydon

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



INTERNATIONAL
CORRESPONDENCE SCHOOLS

EST. 1891

Dept. 171, Intertext House, Stewart's Road, London, S.W.8.
Please send me the ICS prospectus—free and without obligation.
(state Subject or Exam).....

NAME.....

ADDRESS.....

7/70

INTERNATIONAL CORRESPONDENCE SCHOOLS

TRANSISTORS etc.

AC107	3/-	OA5	1/6	OC28	6/6	OC81D	2/8
AC126	2/6	OA9	1/6	OC44	3/6	OC82D	2/6
AF115	3/-	OA47	1/6	OC46	3/6	OC140	5/-
AF116	3/-	OA81	1/6	OC70	2/6	OC169	3/6
*AF117	4/-	OA85	1/6	OC71	2/6	*OC170	4/-
BFY18	4/6	OC23	6/6	OC72	2/6	OC171	3/6
BFY61	4/-	OC25	6/-	OC73	2/6	OC202	4/6
GE113	2/6	OC26	7/6	OC81	2/6	TK22C	1/6

* WITH 4 LEADS

(General purpose)

CRYSTAL DIODES—6 FOR 2/6 (1/-)
SILICON DIODE RECTIFIERS—BY 100—3/10 EACH
51& AMP. SERIES: BYZ13 300 PIV 4/-, BYZ12 600 PIV 5/-,
 BYZ11 900 PIV 6/-, BYZ10 1200 PIV 7/-
TRANSISTORS: 5 AMP SERIES 100 PIV 7/6, 200 PIV 9/-,
 300 PIV 10/6, 400 PIV 12/-, 800 PIV 25/-,
 10 AMP SERIES, 50 PIV 10/-, 100 PIV 12/-
 (POSTAGE PACKING & INS. ON ALL ABOVE, 1/- UP TO 11, 12 & OVER PAID
 MULLARD STACK P. W. BRIDGE 12A 100 PIV 39/6 (3/-))

ELECTROLYTIC CONDENSERS New list of 80 types from 2 to 40,000µF with sizes, make, type price free for a.s.e.
3 GANG VAR. CONDENSER: Mod., air-spaced, .0005 ea. sec. 5/- (2/-).
SUB-MIN TRANSFORMER: Output 3 Ω for OC72 etc) 2/6 driver, 3/- (up to 6 either 1/-).
MULTIMETER: 20,000 Ω/V D.C., 10,000 Ω/V A.C. 0-5/25/50/100/1K volts D.C.
 ● 10/50/100/500/1K volts A.C. ● 0-50µA 2.5mA/250mA D.C. ● 0-5K Ω/6 meg Ω.
 100Ω/100kΩ/1MΩ. ● 20 to ×22dB.
 ● Complete with test leads and instructions—
 ● Over-load protected 1970 model with every refinement. \$4.10.0 (2/6). JUNIOR MODEL at 47/8 (2/6). 1000 Ω/V described in free list. Spec. subject to slight variation.
SOLDERING IRON. 511m Mod. British High speed, 8 1/2in., all parts replaceable, fully guaranteed for professional, radio and general D.I.Y. use, 19/6 (1/6).

DIAMOND STYLII Replacements for BSE TC8LP, TC8/S and TC8LP/STEREO: CO LLARO "O"; RONETTE BF40LP; GARRARD GC2LP and GC8LP; ACOS GP65/67; all at 7/6 each (1/-). ACOS GP73 and GP91; BBR ST4 and ST9; SONOTONE ST4, 8 and 9TAHC; PHILIPS AGS306, 3060, (3063, 3066, 3301, 3302, 3304), all at 15/- (1/-).
DOUBLE DIAMOND Types: If you don't use the 78 side—this is the best buy—now available only in ST4 (ST3, ST5), ST9 (ST8), 9TA, 9TAHC, 3306, GP91 (for GP92, 93 and 94 Cartridges and GP918C for GP918C cartridges. 30/- each (1/-).
EARPIECE all the above 7/6 types only, also ACOS GP37 at 3/6 each (1/-). ACOS GP91 7/6 (1/-). No other types are pressed, and no 78 rpm available in any type.

PICK-UP CARTRIDGES 15/-.
 ● Stereo compatible—Mono which also plays Stereo records monaurally with min. wear. GP91/80, 21/-.
 ● Latest Stereo GP93, 24/6.
 ● Ceramic Stereo, top quality for expensive outfits, GP94, 28/6.
 ● Sonotone stereo 9TAHC diamond fitted cartridge 55/- (all at 1/-). More diamond types in list.
FLYBACKS (A.C.) 17/6 (1/6). **TWO STATION TRANS. INTER-COM.** Excellent baby alarm. Instant, easy fitting, with lead plugs and battery. All you require 52/6 (3/-).
TRANSFORMER AMPLIFIERS, 3 watt, 9V operation, 45/6 (1/6); 7 1/2 watt, 6 trans. 24V operation 67/6 (2/6).

RECORDING TAPE Finest quality British Mylar. **STANDARD:** 5in. 500ft. 7/6 (1/-). 5 1/2in. 1200ft. 11/8, 7in. 1800ft. 18/- (1/3 reel). Still the finest quality and value obtainable.
MICROPHONES—CRYSTAL MIC91, Desk, 18/6; MIC45, curved hand grip 17/6; Stick '60' 20/8; (1/6 each type). Cream plastic hand type with "Strut" stand, switch and 2 leads with 2.5 and 3.5 plugs 12/6 (1/8). Lapel (or hand) with clip 6/6 (1/-). Machined metal tapered stick type with neck cord and adaptor to fit standard floor stands, 25/- (1/6).
DIAPHRAGM: Cream hand held 15/6 (1/6). MELO 50K Ω, 34 + fin. with Base, Adaptor 27/6 (2/6). WELL, similar but fixed on flexible 15/6. Swan neck to switch-fitted base 42/6 (2/6).
CARDIOM DYNAMIC OMNI-DIRECTIONAL: Two highly successful types "SQUARE" 208, \$5.10.0. "BALL" type, 209, 21th 50K/600 ohms imp., \$5.17.6. Non-directional "ball", switch, cord adaptor—DM160—\$3.17.6 (all these types 5/-).
MICROPHONE INSERTS: Diameter 1.76in. or 0.9in., either size 5/6 (1/-).
SPEAKERS: 12in. round, fitted Tweeter, 6W, 3 or 15 Ω (state which), 27/6 (5/6); or for Stereo, 80/- per pair (charges paid), 21in. 3 Ω 7/6 (1/-); Limited quantity powerful 2 1/2in. PM transistor replacement speaker, high ohms, excellent tone, 12/6 (1/-). **HEADPHONES:** High Res. 2000 Ω ea. earpiece 18/6 (1/6); Stereo Dyn 8-16 Ω 23/- (3/-). **EARPIECES** with lead and min. jack plug, magnetic 1/6. Crystal 4/6 (up to 3 for 1/- on either). State if 2.5 mm. of 3.5mm. plug required. (Crystal 3.5mm. only).

AERIALS CAR TYPES—Telescopic vandal proof locks retracted, 2 keys and all fittings 27/6 (2/6) Superior type, telescopic steel, slightly longer, 30/- (2/6).
For Portables & F.M. Sets—4-section 61-25", 1" sliding threaded base, needs 1/2" hole 4/-
 6-section 51-25", screw hole in base 6/6
 7-section 51-32", screw hole in base 5/6
 10-section, 6/47", screw hole in base 12/6

DISAPPEARING, with swivel and sliding threaded socket, fixing nut on bottom section—
 10-section 51-25", 1" dia, 12/6
 10-section 51-25", 1" dia, 12/6
 10-section 51-25", 1" dia, 12/6
All are strongly plated (P. P. & I. on all above, up to three 1/-)
SWITCHES: Standard toggle, metal, 250V 2A. One hole fixing: SPST 2/6, SPDT 2/6, DPST 3/- DPDT 3/6. Slide type, Sub-min. DPDT 1/6 each. Small DPDT 3 way, centre "off" 1/6. Reed magnetic on/off 1/6 (up to three, 1/-; 1d each all additional). Rotary switches etc. in list.
VIBRATORS: Famous makes only, 12 volt 4 pin non-synch, 4/6. 12 volt 7 pin synch. 12/6 (1/- each either type). No other types available.
MAINS NEON TESTER: Fly leads 3/- . Pocket screwdriver type 3/6. **PLUGS:** 8td. Jack, plastic body 2/3. Screened 3/- . **VALVE HOLDERS:** B7G or B9A, Moulded 6d. (all above 1/- up to three). Many more British and Continental standard and miniature **PLUGS & SOCKETS** detailed in list. Also **STANDARD** and **BURPUSS VOLUME CONTROLS.**
CORRECTING WIRE: 5 coils ass'd. coils, each 5 yds. Solid Core 3/6. Flexible 3/6. Super thin Flex, Screened, Sheathed, 1 1/2 yd. (8td. up to 6 yds. over 6 yds. post free). **TWINE MIKE CABLE:** 1/8 yd. **SINGLE MIKE CABLE:** 8d. yd. Both flexible, screened and sheathed. (Up to 3 yds. 8d., each additional yard 1d. extra.)
R.F. FIELD INDICATOR, 6-band with antenna, monitoring crystal earpiece, visible indicator etc. 42/6 (1/6). Details in list.
RETRACTABLE FLEXIBLE LEADS, Space saving "Curly", many uses in car and home: with phono plug each end, 6ft., 4/6; 12ft., 7/6; With phono plug one end, phono socket at other, 6ft., 5/-, 12ft., 8/6 (1/- each all types).

CAR RADIO: Splendid new All-British dash-mounting radio using Mullard transistors and circuit. M. and L. wave. Separate speaker and baffle. Absolutely complete for + or - chassis, 42/6 (1/6). A. have success since introduction.
CURRENT LIST: With many more items sent with all orders free for S.A.E., Post Free Overseas. This advertisement cancels all previous ones and lists supplied prior to May 31st 1970.

FELSTEAD ELECTRONICS
 (PW32) LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot be accepted, and a minimum charge of 1/- is now made. Charges apply to G.B. and Eire only. Overseas orders welcomed. Air or surface mail at cost. Sent at buyer's risk, unregistered and uninsured unless specified and min. insurance/req. fee of 2/6 sent. S.A.E. please for all enquiries, otherwise regret cannot be replied to.

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build

Clearly remember the first project I ever tackled—a one valve short wave receiver; it took hours to build, especially the coil winding, but the final results were worth it. With the introduction of transistors things have become very much easier and the short wave receiver described here is the transistor equivalent of the frequently published “one-valve receiver” of a few years ago. The performance, though not comparable to a superhet, is quite good enough for the beginner and it will sort out the closely packed signals in the short wave bands with a 10ft. aerial. On the prototype 10 countries were logged in an hour and of course there were dozens of other signals that could have been identified with a little more patience.

In the published form the receiver should provide hours of fun but it is primarily designed as a starting point for experiments and at the end of the article I will give some clues on where to start.

THE CIRCUIT

The circuit may at first seem rather bewildering to the less experienced constructor. The transistor Tr1 is connected in the common base mode, an arrangement not often used outside v.h.f. tuners. The characteristics of this type of arrangement are low impedance input (about 50Ω), high output impedance (about 1MΩ), no current gain but high voltage gain. Additionally, the input and output are in the same phase and we make use of this in applying the regeneration.

The antenna is connected to the emitter via C1. The radio frequency choke (r.f.c.) connects the emitter to earth potential without losing any of the r.f. signal which cannot pass through it. The base of Tr1 is supplied with its bias by the potential divider R1 and R2, C2 smoothes the voltage. The tuned circuit comprises L1 and VC1. R3 and VR1 act as the audio load and the output is taken from across this to a crystal earpiece.

The unusual feature of this design is the method of feedback. Since the amount of feedback should be the same irrespective of frequency it must be

★ components list

R1	82kΩ 10%, ¼ watt	VC1, VC2	250pF + 250pF ganged
R2	470kΩ "	RFC	2.5mH choke, miniature
R3	1kΩ "	Tr1	2N2926G
VR1	25kΩ lin. pot with switch	L1	See text
C1	1000pF	J1	Earpiece output jack
C2	1000pF		
C3	500pF		

No. 15 SHORT WAVE RECEIVER

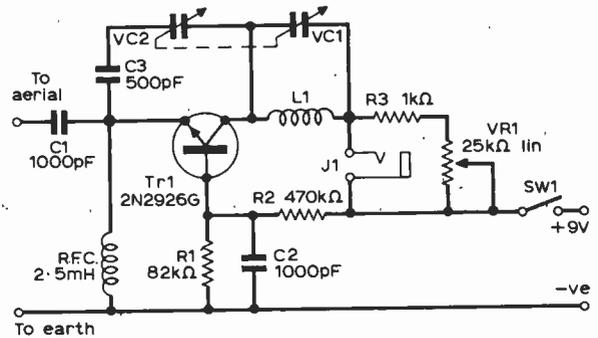


Fig. 1: The circuit of the one transistor short wave radio.

arranged that the value of the capacitor gets less with the increase in frequency. This is usually done by using a separate variable capacitor but here we are using a double-ganged capacitor and we obtain the correct value of feedback level by padding it with 500pF. This will mean that the level of regeneration will be roughly correct whatever the frequency. However, since the level of feedback has to be *exactly* correct for maximum performance in this type of receiver, a fine adjustment is obtained by varying the collector load resistor, VR1 achieves this.

CONSTRUCTION

We are limiting ourselves to 20s. in this series and

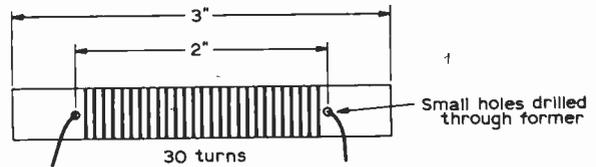


Fig. 2: The construction of L1.

VC1 and VC2 will take a handsome section of this, so if we don't want to go over the limit we shall have to wind our own coil. This is a very simple business and all we need is the plastic housing from an old “Bic” ball-point and a couple of feet of wire. Two holes should be drilled through opposite faces of the hexagonal (six-sided) body and thirty turns of wire wound around it using the holes as terminal anchoring points. The type and gauge of wire matters very little, anything between 20 and 36 s.w.g. will do—even plastic covered hook-up wire will do for those without a supply of enamelled copper wire. Figure 2 shows the construction of this. Coverage with this coil will be from 5 to 15MHz but this will depend on the actual capacitor chosen.

Note that the common connection of VC1/VC2 is not at earth potential, it is connected to the collector and therefore it will have to be isolated if a metal chassis is used.

Layout should not be too critical but do not try crowding the components—construction on tag-strips would probably be the easiest.

continued on page 222

VOLTAGE STABILISATION

I. R. SINCLAIR

THERE is hardly any piece of electronic circuitry which does not employ some form of voltage stabilisation, meaning that the voltage at some point is held steady despite variation in supply voltage or in current drain. The voltage from a power pack can vary in both ways; when the mains voltage varies, then the output voltage varies in the same ratio, and when the current supplied by the power pack increases the output voltage falls because of the drop across the internal impedance of the power pack.

The simplest and least effective form of voltage stabiliser is the decoupling capacitor (Fig. 1). When the supply voltage changes, the voltage across the capacitor changes much more slowly, so that the voltage is stable for a short time. In this way rapid changes of the input voltage (occurring in a time shorter than the time constant of the decoupling circuit) are stabilised.

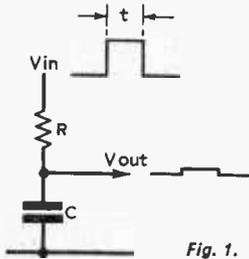


Fig. 1.

In addition, any extra demand for current by the device connected to the capacitor can be supplied from the capacitor (which stores an electric charge) for a short time so that the voltage is also stabilised against rapid changes of current.

These effects are illustrated by the use of decoupling circuits to prevent feedback of audio output to earlier stages of an amplifier as in Fig. 2(a) and by the use of a decoupling capacitor on the screen connection of a valve (to prevent negative feedback due to voltage variations as the current varies) as in Fig. 2(b).

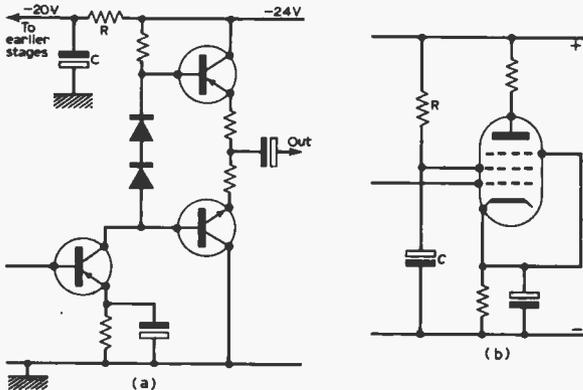


Fig. 2: Typical decoupling circuits utilising a capacitor C

The use of a decoupling capacitor, however, is not very effective when very low frequencies are concerned (hence the problem of stability in high-gain amplifiers having good low frequency response) and is quite ineffective when the steady voltage must be controlled, as for example, in an oscillator circuit where the frequency of the output is affected by the supply voltage.

In pulse circuitry also, voltage stabilisation is almost essential to avoid large pulses at one part of the circuit affecting stages which are easily triggered. Finally, when a power supply is used to test "breadboards", it is much more satisfactory to stabilise the power supply than to have to build in decoupling at every stage of the circuit under test.

Apart from the feature of stabilisation, many stabilised supplies can be varied in voltage, and this feature may in itself be extremely useful. A variable voltage can, of course, be obtained from a normal power supply if the mains feed is through a variable transformer or if a potentiometer is used to tap down the output.

The first method costs more than stabilisation, however, and the second considerably raises the impedance of the power supply, so causing large voltage variation when the current drain changes.

Stabilising Elements

All voltage stabilising circuits require some source of reference voltage to which the output voltage can be compared or from which the output can be taken. The three reference sources most often used are gas reference valves, zener diodes, and batteries.

Gas stabilising valves (Fig. 3) are diodes containing one or more of the rare gases found in very small quantities in the air (neon, argon, krypton) at a low pressure. At a low voltage between anode and cathode, no current flows, but at a certain voltage, the striking voltage, the gas is ionised and current passes, causing the gas to glow.


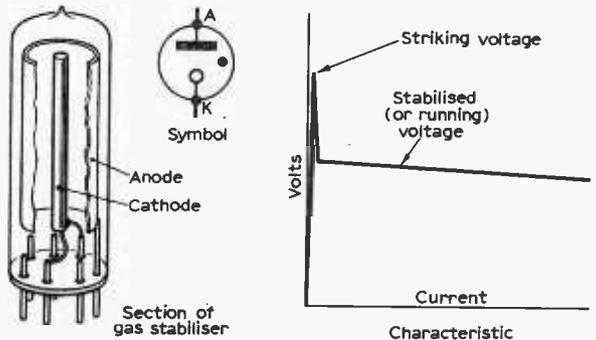


Fig. 3: Cut-away view of gas stabiliser and its characteristics (right)

At the same time the voltage between anode and cathode falls to a value called the *stabilised* voltage, and remains at this voltage almost unchanged for a wide range of currents. Gas stabilising valves, like any other gas-filled valve, must be fed from a resistance which can limit the current passing to a safe value, because the voltage across the valve falls as the current increases; compare this to a resistor, where the voltage across the resistor rises as current increases.

For this reason, gas stabilisers are said to have "negative resistance". The purity of the gas and the material used to form the cathode (usually a rod of molybdenum) and the anode (a cylinder of molybdenum or nickel) greatly affect the usefulness obtained with stable voltages of 45V, 75V, 80V, 90V, 105V, 150V and 180V (due to changes in the gas and other materials used), and the striking voltages which may be up to 50% greater.

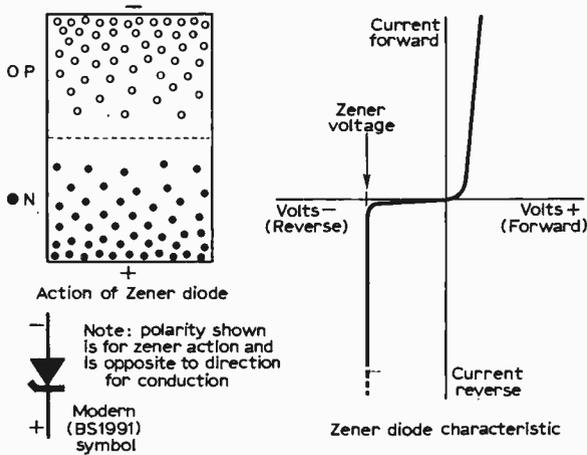

The zener diode (which should properly be called the avalanche diode) is the semiconductor equivalent of the gas stabiliser tube in its effects. When any junction diode has a reverse bias applied, a very small current flows due to the main current carrying charges in the semiconductor being attracted away from the junction (Fig. 4) leaving only the charges which are present in smaller amounts. As the reverse bias voltage is increased, however, the charges which are carrying the small current make more violent collisions with the atoms of the semiconductor, releasing more charges capable of carrying current. These in turn are accelerated and generate other charges by collision so that the current increases very greatly for only a small change in voltage. This process of creating new charges by collision is very similar to the process called avalanche multiplication which takes place in gas stabilisers, and has the same effect, that the voltage is almost steady for a very wide range of current when this effect is taking place.

Zener diodes can be made for a wide range of voltages from 1.5V to 180V and an equally wide range of dissipation from $\frac{1}{4}$ W to 50W or more, but the higher voltage and higher wattage versions are very expensive.

It is worth noting that a zener diode acts as a diode when biased forward and stabilises when

biased back so that zener stabilisers appear to be connected the wrong way round at first glance. By comparison, gas stabilisers act only as stabilisers and have no diode action where biased oppositely.

Batteries can also be used as sources of fairly stable voltages. Though dry cells have a high internal impedance making them unsuitable for maintaining a stable voltage when the current drawn varies, they can be used as a reference supply whose voltage is fixed providing that practically no current is drawn. Examples of circuits in which batteries can be used will be given later.

The simplest stabilising circuit consists of a resistor and a stabiliser gas valve or zener diode, as shown in Fig. 5. The resistor is chosen so that the current flowing through it is rather more than the maximum demand, and the voltage across it is the minimum power supply voltage less the stabilised voltage. When no current is being drawn from the stage, all the design current will flow through the stabiliser; when current is drawn, it is taken at the expense of the stabiliser.

If more than the designed current is drawn, the stabilisation will fail, and the voltage will drop sharply. As an example, consider the problem of supplying 10mA to an oscillator circuit at 9V, given a "12V" supply which actually delivers about 12.5V at zero current drain and 12V when 10mA are drawn, Fig. 6(a). A 9V zener will be used as the stabiliser, and the difference between stabilised voltage and supply voltage ($12-9=3$ V) must appear across the resistor when 10mA are being drawn.

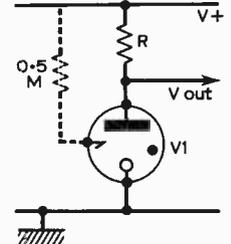


Fig. 5.

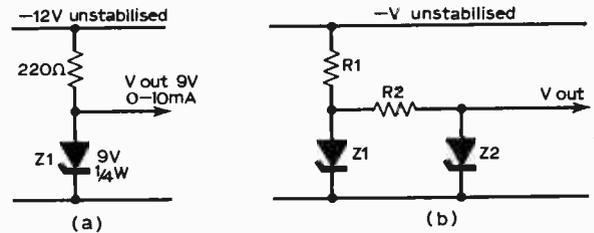


Fig. 6: (a) Simple zener diode circuit
(b) A second zener diode for additional stabilisation

Since most zener diodes require at least 1mA current through them to maintain the stable voltage, we shall design for a current of 12mA through the stabiliser, so requiring the voltage drop across the resistor to be about 3V at 12mA. Using Ohm's Law, $V=R \times I$, this gives a value for the resistor of $3/12\Omega=250\Omega$.

The nearest available values are 270 Ω and 220 Ω and to allow for a possible drop in the supply at 12mA, it is better to use the lower value, provided there is no likelihood of causing over-dissipation in the zener. When the load is not drawing current, the zener diode will be passing about 12mA; when the load is drawing 10mA the zener will be passing 2mA. The maximum dissipation in the zener diode will be when maximum current is passing at the stable

voltage, i.e. 12mA at 9V=108mW and the maximum dissipation in the resistor is 12mA at 3V=36mW.

A $\frac{1}{4}$ W zener and a $\frac{1}{8}$ W resistor would therefore give adequate safety margins in this design unless the load shorted, when the whole 12V would appear across the resistor, causing a dissipation

$$\left(I^2R \text{ or } \frac{V^2}{R}\right) \text{ of } \frac{12 \times 12}{250} \text{ watts or about } \frac{1}{8}\text{W.}$$

For the design to be "fireproof" therefore, the resistor should be rated at $\frac{1}{2}$ or $\frac{3}{4}$ W. This calculation has been done in detail because many users of zener diodes are rather hazy about the dissipation calculation.

The design of a gas-valve stabiliser of this type follows exactly similar lines, but there is one important difference. The gas stabiliser will not pass current until the voltage across it has reached the striking voltage, so that the voltage input must always be higher than the striking voltage. If excessive current is drawn, the valve will cease to conduct, and cannot conduct again until the striking voltage is reached.

Excessive current drawn from a gas stabiliser therefore means that the voltage will drop sharply (due to the excessive current) and will be unstabilised until the current has dropped sufficiently to allow the voltage across the stabiliser to reach the striking voltage—this may mean a long period of unstabilised operation with large changes in voltage. A zener diode, on the other hand, has no striking voltage. The current increases smoothly as voltage increases, so that stabilisation starts again whenever the stabilised voltage is reached.

Simple stabilised supplies of this kind are quite effective where low currents are drawn, as for example, in the stabilisation of one stage of a circuit (perhaps an oscillator) or when a transistor radio is run from a car battery or a mains power pack. When greater currents are needed, the dissipation in the stabiliser becomes excessive.

When greater stability is required from a simple stabiliser, two stabilisers can be used in tandem as shown in Fig. 6(b).

Indirect Stabilisers

Circuits in which the stabiliser (gas or zener) no longer supply the current taken by the load are indirect stabilisers; almost without exception they use the principle of the cathode or emitter follower.

In the circuit of Fig. 7(a), the gas stabiliser controls the voltage of the grid of triode V1, which is connected with the unstabilised voltage to its anode and the load to its cathode. If the load current varies, the valve acts to try to maintain a fixed voltage at the cathode.

For example: if the valve used has a Gm of 5mA/V and is passing 30mA at the bias setting used, then an increase of 5mA in load current requires an increase in bias of 1V which means that the cathode voltage will drop by 1V. This could be otherwise put by saying that the output impedance is 200Ω ($1\text{V}/5\text{mA}=0.2\text{K}=200\Omega$).

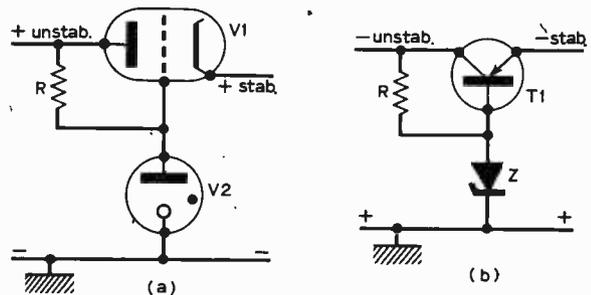


Fig. 7: (a) Gas stabiliser to control series valve stabiliser (b) Semi-conductor version of (a)

Obviously, for stabilising in this way, the higher the Gm used the better is the stabilisation, and transistors with their high Gm figures (about 40mA/V for each 1mA collector current) make excellent stabilising stages at the voltages at which they can be used.

More Complex Stabilisers

The simple stabiliser is useful for many circuits where the degree of stabilisation does not have to be very great. The voltage can even be altered by taking the grid supply from a potentiometer fed from the gas stabiliser (Fig. 8), though this does not work very well with transistor circuits due to the base current drawn from the potentiometer.

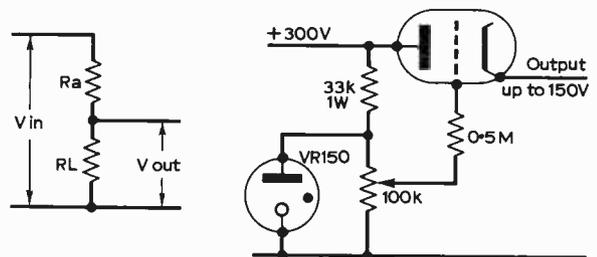


Fig. 8: Modification to permit variable stabilised output voltage

Fig. 9 shows a circuit which has been widely used. V1 is a pentode to which is applied both the gas valve voltage and a portion of the output voltage. The gas valve is used in the cathode of the pentode, and a bleed resistor ensures that some current flows through the gas valve even when the pentode cuts off.

The output voltage is divided by the resistor potentiometer chain and is applied to the grid, so that any change in output voltage is divided by the potentiometer ratio. This has the undesirable effect of reducing the stabilisation, and a capacitor is usually connected between the grid and the output line so that full stabilisation can be obtained against rapid voltage changes.

The bias on V1 is now the difference in voltage between the gas valves and the voltage at the potentiometer and this controls the current through the valve. Any change in this bias changes the current in the valve V1 which alters the voltage at the anode which in turn changes the bias on the series valve V2.

Note that the anode load of V1 is split between

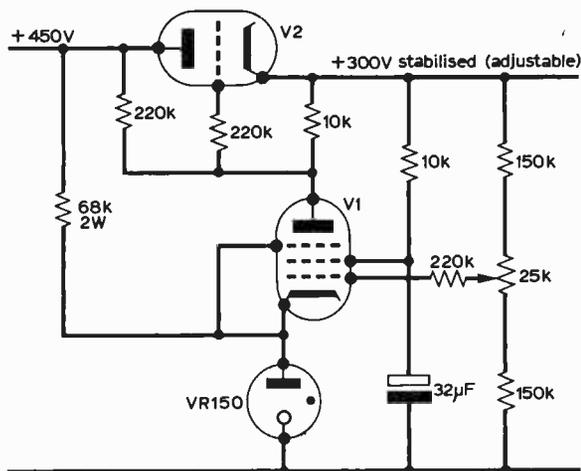


Fig. 9: Typical valve stabilising circuit with component values

output voltage and un-stabilised voltage (to keep a voltage at the anode in the event of failure of the other resistor) and that a grid stopper is used between the anode of V1 and the grid of V2 to avoid excessive grid current if the load should be shorted out.

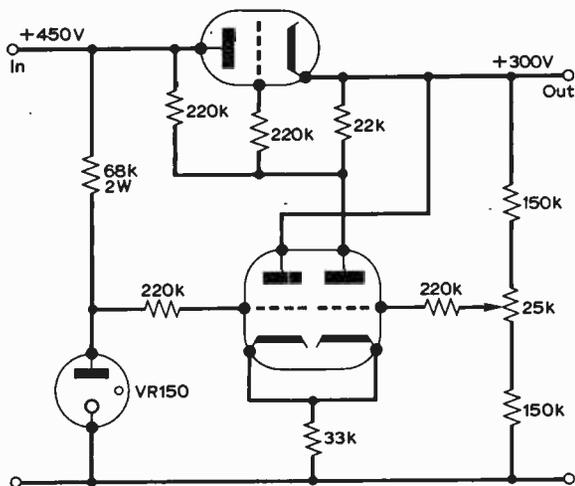


Fig. 10: Practical circuit using a double-triode instead of a pentode

A more elaborate stabiliser circuit is shown in Fig. 10. The stable voltage obtained from gas valve or zener diode is used to bias one half of a long-tailed pair, and the voltage obtained from a potential divider across the output is applied to the other half.

Notes On Design

Though the design and construction of a stabilised power supply is not particularly difficult, there is a sequence of steps which should be adhered to if trouble is to be avoided.

The choice of a series stabiliser is the first step. For low voltages, a power transistor will be the automatic choice, but for higher voltages both triode and tetrode (or pentode) valves are available. Generally, for the simple circuits where a gas valve

controls the series valve directly, a pentode gives better regulation, but requires a separate supply for the screen. This separate supply may have to be obtained from a separate rectifier.

For the more elaborate circuits, a triode with high Gm and very low Ra is better. A valve such as the type 6080 can handle very high currents and has a large anode dissipation, but tetrodes and pentodes can give good results when connected as triodes.

The type of valve or transistor chosen depends very much on the rating of the power supply—the maximum current to be drawn must be less than the current rating of the series valve or transistor, and the power dissipated in the series controller must be within the rated value.

The dissipation in the series controller is the maximum current (I_{max}) multiplied by the voltage across the stage (V_v), and this voltage is equal to the un-stabilised voltage (at maximum current) minus the stabilised voltage.

The rectifier stage must be able to supply sufficient voltage at maximum current to maintain a voltage across the series controller sufficient to pass maximum current through it. For this reason, transistors and triodes are preferred for elaborate series stabilisers, since they can pass large currents at low voltage differences. In general, for a 300V supply, a 350-0-350V mains transformer is the absolute minimum which can be used and many commercial designs use a 400-0-400V or 450-0-450V transformer.

Having selected the series controller, the maximum output voltage swing required from the amplifier stage is now known; it is equal to the grid base of the series controller. If, of course, a simple circuit is being used, design stops at the choice of the series controller!

The anode load for the amplifier valve is now chosen. It should be the resistor which will give an anode voltage equal to stabilised voltage minus half the grid base at a steady bias current of about 1mA; this is about the maximum load and minimum bias generally practicable, and some long-tailed, pair valves may need more bias.

Remember, especially in the case of the circuit of Fig. 9, that the cathode of the amplifier valve will not be at earth potential, but somewhere around the voltage of the gas stabiliser. Having fixed the load and current for the amplifier, the cathode circuit can be designed, either a stabiliser valve for the Fig. 9 circuit or a resistor for the Fig. 10 circuit.


Since the current and voltage are fixed for one half of the long-tailed pair, the value of the resistor depends on the current used in the other half. If this is now chosen as 1mA also the value of the resistor is approximately:— Voltage of gas valve/2 in kilohms.

The rest of the circuit almost designs itself. The potentiometer chain across the output must deliver voltage, at maximum setting, equal to the voltage of the gas valve, and the minimum voltage is less than this by the grid base of the amplifier, so that the amplifier can be almost cut off. The output voltage can then be controlled smoothly from minimum to maximum.

Design refinements can then be added, resistors to ensure that the gas stabiliser stays running under all conditions, capacitors to ensure sudden voltage changes cause a quick response, etc.

When transistor stabilisers are being designed,

—continued on page 226

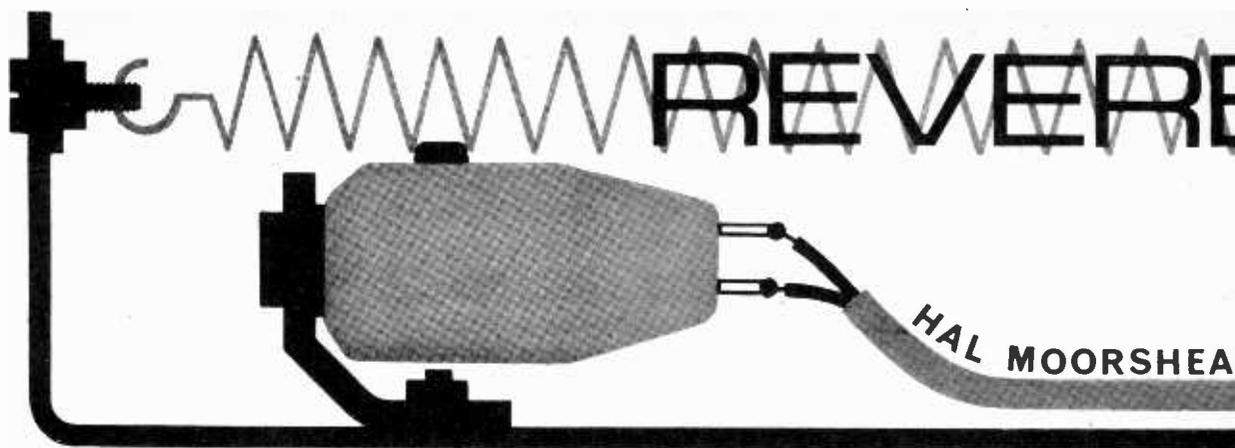

REVERBERATION is an effect which can greatly improve certain types of audio signal yet one which is underestimated and not greatly used outside professional recording studios. All of us have heard artificial reverberation frequently, even though we are rarely aware of it, because when used properly, it serves to make a sound *more* natural and not make it appear artificial.

A sound picked up on a microphone outside sounds very different to one inside because a tiny part of the signal picked up by a microphone will not be direct and will arrive after being reflected from walls etc. These reflected sound waves are almost impossible to identify by listening but although the percentage of these reflected signals is minute compared to the direct signal, their absence is very noticeable. In fact, to simulate 'out-of-doors' conditions in a studio involves special techniques and special rooms are used with high complicated sound absorbing walls.

Sounds with no vibration appear dead and the opposite applies—a sound containing reverberation takes on life.

The author has a fair interest in old gramophone records and has tried to improve the sound of these in several ways. It is a relatively simple matter to correct the frequency response of these and then to chop the bass rumble and the top scratch but anyone who has tried this knows that something is still lacking—in fact, reverberation is the missing link.

Although originally designed for use with old records, the unit can of course add "life" to any sound. Modern discs are normally superbly recorded and such a unit will add nothing, but recordings made at home can easily be improved.

Pop groups frequently make use of reverberation to increase the liveliness of their music but commercially available units are not inexpensive and usually need to be connected to additional amplifiers and mixer units.

The reverberation unit described here simply requires connection into the chain. It must be added that the unit has *not* been tested in surroundings of extreme high sound levels such as those produced by pop groups and use in this way could cause acoustic troubles since the spring used in the unit may be almost impossible to isolate from excessive sound. But for normal use—even with 12 watts operated in an average sized room—it has proved entirely satisfactory.

The 'delay' time in the prototype is extremely short but is more than enough to add life to a

sound. However, the principle holds good and it should be a simple matter to adapt the unit to give longer delays.

DESIGN CONSIDERATIONS

The reverberation unit makes use of a delay spring—this is the principle adopted in most types—and it is necessary to drive this spring at one end with an audio signal and to pick it up at the other. The spring keeps the sound going for a few fractions of a second after it has been triggered.

Originally the unit was designed using telephone pick-up coils to drive the spring and to pick it up at the other end but experiments were relatively unsuccessful due to the high power needed to drive the spring.

The unit described here uses normal crystal pick-ups—the type nearly always fitted to cheap record players. These are very sensitive and in practice proved ideal. These are widely available on the surplus market costing upwards of 7s. 6d.

High quality is not really necessary on the pick-up side because it comprises only a tiny fraction of the output but despite this, care was taken in the design of the amplifiers and other sections to keep the quality as high as possible throughout, bearing in mind that even minute distortion will add to the whole chain if introduced in the reverberation unit.


For versatility an early prototype incorporated a method of altering the spring tension, thus providing a method of easily adjusting the delay time. There were considerable problems in this, though later in the article an alternative method is shown by adjusting the length of delay path. For normal use however, the unit as it stands should prove perfectly adequate.

THE CIRCUIT

The block diagram in Fig. 1 should indicate the general operation of the unit, this is included since the circuit—shown fully in Fig. 2—appears bewildering at first sight.

The input is connected directly to VR1. It is assumed that most readers are using transistorised equipment and this unit presents an impedance of 10k Ω which should suit most equipment. There is gain in the unit and for use with high impedance equipment it is perfectly satisfactory to include a 330k Ω resistor at the input and increase the value of VR1 to 250k Ω as in Fig. 3a. This attenuates the signal but since low noise transistors are used no

REVERBERATION UNIT

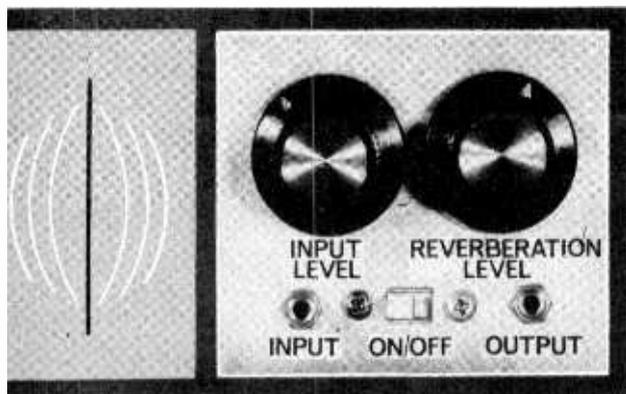

unacceptable factors are introduced when it is further amplified.

C1 couples the output of VR1 to the base of Tr1, a BC169C—a high gain, low noise transistor. With R1 acting as its collector load this first stage is directly coupled to Tr2, also a BC169C, which further amplifies the signal. R4 acts as the collector load and the output is taken via C3 to the drive crystal, X1. The emitter of Tr2 is raised to the necessary operating voltage by R3 decoupled by C2. R2 connects from here to provide the base bias for

Tr1. This mode of connecting the bias ensures d.c. stabilisation.

If it is found that VR1 is nearly always at a near minimum setting (indicating high input levels) C2 can be left out or removed later. This will lower the amplification of the amplifier by introducing negative feed back thus also improving the quality.

If C3 were only to drive the crystal its value need not exceed $0.1\mu\text{F}$ since it is feeding a high impedance but in fact the output of this amplifier is also taken to the final mixer unit. It is necessary to amplify the original signal because of the losses introduced at the mixer.

The pickup crystal, X2, has, like the drive crystal a high impedance and it is important this is connected to a high input impedance, in this case Tr3 arranged as an emitter follower stage (or common collector as it is also known).

The input impedance, being high, necessitates a capacitor of only $0.1\mu\text{F}$ (C5). The input impedance of this stage is approximately the emitter resistor times the gain of the transistor, in this case about 800, giving a figure of about $800\text{k}\Omega$ which provides a fairly decent match for the pickup.

The output from this matching stage is connected via C6 to Tr4, a 2N2926G, and this amplifies the signal which is finally coupled to VR2 via C7. The excellent properties of the BC169C are not really required for Tr4 but if desired one could be used here without any modifications to the circuit.

The output of the first amplifier, as we have already seen, couples to the drive crystal. It is also taken to the top of VR3 in the mixer.

VR2 and VR3 consists of a $25\text{k}\Omega + 25\text{k}\Omega$ ganged linear potentiometer and they are wired in

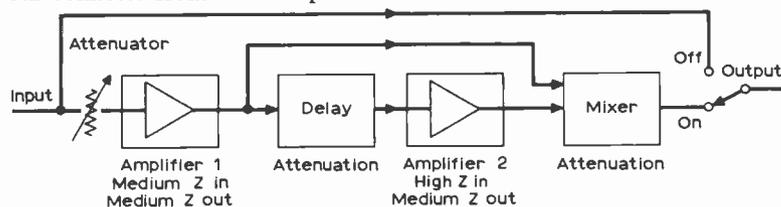


Fig. 1: Block diagram showing the basic operation.

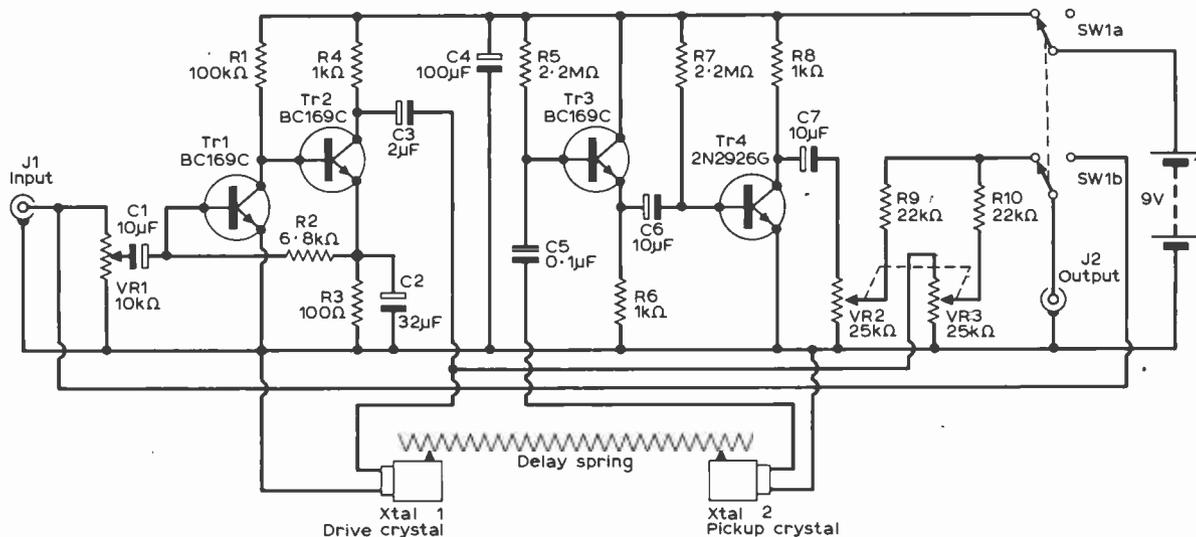


Fig. 2: The complete circuit of the reverberation unit.

such a way that when VR2 is at maximum, VR3 is at minimum and vice versa.

In this way one control provides a smooth transition from maximum reverberation to nil reverberation while always maintaining the same level.

To prevent interaction between the two sections of the control, R9 and R10 are connected to the sliders. The combination of these resistors and VR2 and VR3 give an output impedance of approximately 15kΩ which will be a close match to most transistor equipment.

If unity gain is required from the reverberation unit the output arrangement in Fig. 3b should be substituted.

To enable the unit to be connected at all times, SW1, a two-pole two-way slide switch, is connected in such a way that when the unit is off the input and output are connected directly together. C4, a 100μF capacitor, serves to decouple the two stages.

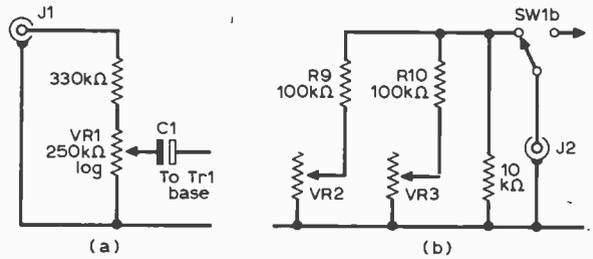


Fig. 3: (a) Modified input for use with high impedance source; (b) Modified output with attenuation.

THE DELAY UNIT CONSTRUCTION

Although the delay unit comprises a simple aluminium chassis to which the pickups are fitted and to which the spring is attached, care is needed in the construction. Figure 4 shows the metalwork details which should be prepared first. If when constructing the unit it is intended to build a longer delay unit it is recommended that initially the unit is built on a chassis with a 6in. bed as shown. This will greatly simplify testing and later it will only be necessary to cut the chassis in half and add a few more holes around the existing components.

The springs used can cause quite a tension between the two upright sections of chassis 1 and 16 s.w.g. aluminium is needed to avoid distortion of the vertical members.

Slight modification is necessary to the pickup cartridges. First, both needles must be removed. It will be seen on inspection that a small spring device provides the locking in either the L.P. or 78 position. This must be removed and be replaced by a screw, usually 6BA. This will firmly lock the crystal relative to the mounting. The turnover knob can be removed and the spindle cut off if required, though this only improves neatness.


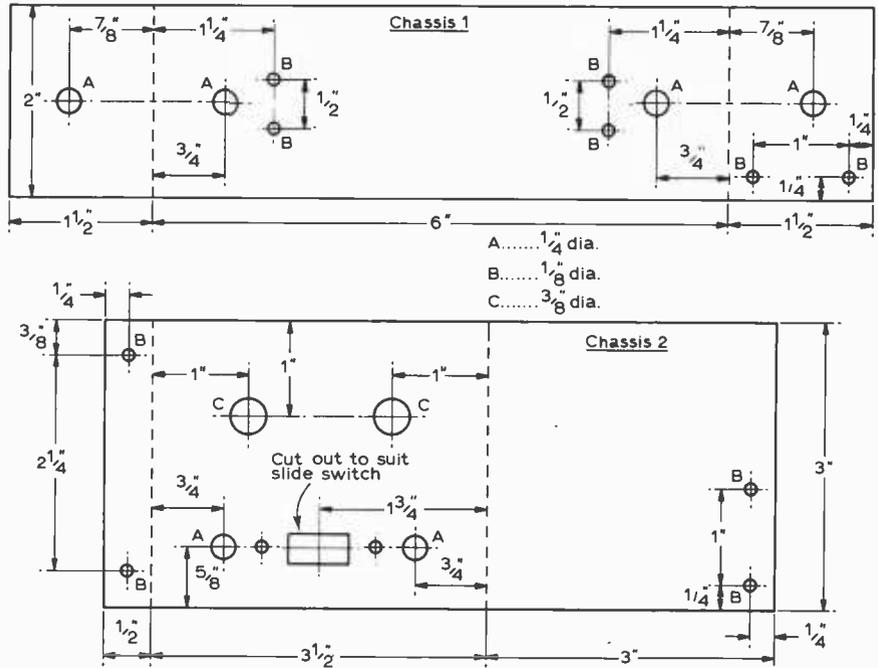


Fig. 4: The metalwork details for the two chassis.

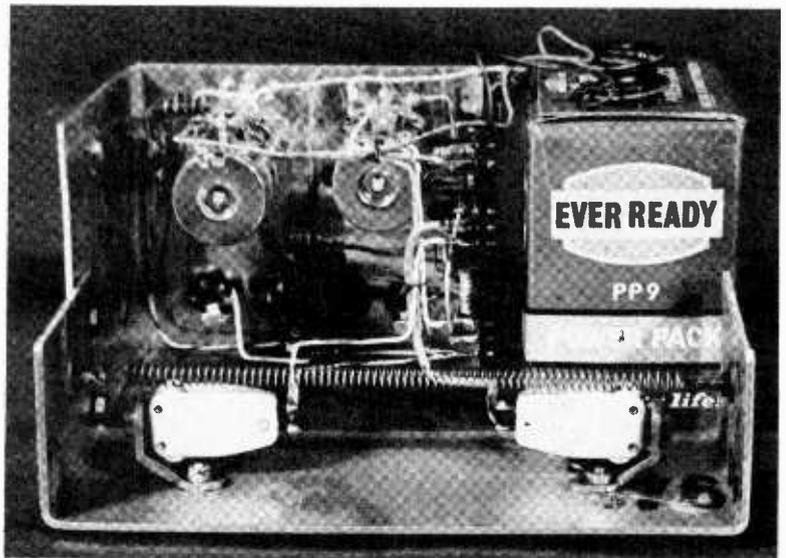

Rear view of the completed unit.

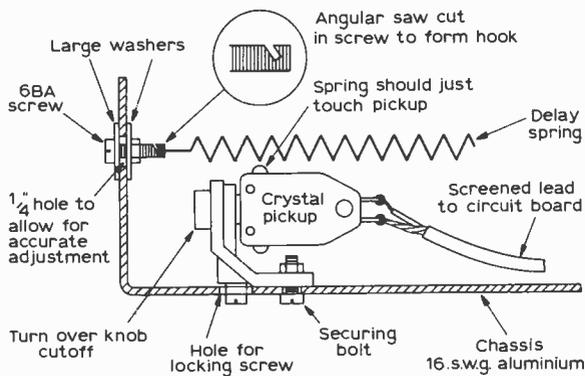


Fig. 5: The construction around the drive and pickup crystals.

The cartridges are mounted by means of 6BA screws passing through the base of the chassis and the oblong holes which are standard. These oblong holes make it possible to accurately align the cartridges if the holes are out.

A further hole has to be drilled in the chassis to take the head of the locking screw, its size is only important in that it should leave plenty of space for the head.

The spring itself is held by means of a 6BA screw with an angular sawcut as shown in Fig. 5. Before cutting, screw on a nut behind the area that will take the cut since when this nut is later unscrewed it will clear the odd burrs created by the cutting. Fit the head of the screw firmly in the vice and use a hacksaw at an angle for the actual cutting.

Two large washers should be fitted as shown as the screw passes through a $\frac{1}{4}$ in. hole.

It is very important that adequate adjustment is allowed for with the spring hooks as the spring itself must be carefully positioned so that one coil just touches on to the plastic needle holder which transfers the movement to the crystal itself.

The spring itself should have its final turn bent at right angles and shaped to lock onto the hook.

The choice of spring is not too important; it needs of course to be an expansion type of approximately $\frac{1}{4}$ in. diameter. The length should be between two-thirds and a quarter of the length of the bed. Obviously the spring should not be expanded beyond its return position.

On the prototype the spring used was about 2in. long unstretched and was from an old BSR TD2 deck. The springs may well be available as spares but as previously mentioned its actual origin is not too important.


Figure 5 shows in detail the construction around one end only but in fact both ends of the delay unit are identical.

The front panel should also be prepared at the same time as the other chassis; the size and drilling details are shown in Fig. 4.

The two $\frac{1}{4}$ in. holes on the right should line up with those on chassis 1 to enable the two to be bolted together.

VR1 and the ganged potentiometer VR2/VR3 fit through the two $\frac{1}{4}$ in. holes and the input jacks fit into the $\frac{1}{4}$ in. holes. SW1 is a two-pole two-way slide switch and as these vary in dimensions the cut-out and screw positions will have to be worked out by the constructor.

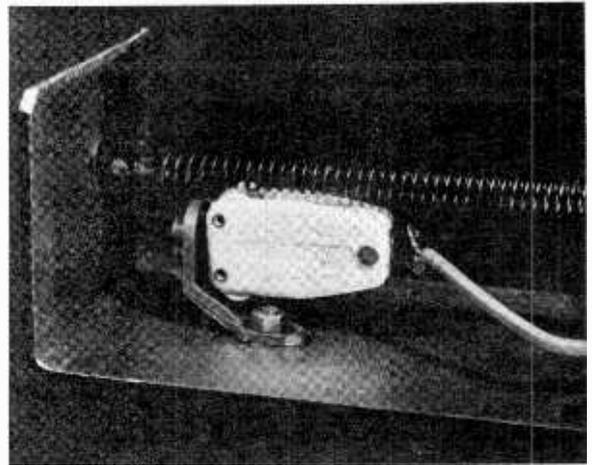The narrow flap on the left hand side of this



Close-up view of the pickup crystal.

chassis is designed to hold the circuit board and two holes $2\frac{1}{2}$ in. apart will line up with the holes made in this. The arrangement of the circuit board and control panel at right angles leads to a neat layout and one that can be worked on readily.

Once the control panel chassis has been prepared J1, J2, VR1, VR2/VR3 and SW1 should be mounted. A simple tag with one earth connection and one insulated connection should be mounted near VR2/VR3 to provide an anchoring point for R9 and R10.

Figure 7 details the wiring. Note that C4 is connected to the earthed tag mentioned above and to the slide switch as there is not sufficient room for it on the circuit board.

The input and output jacks are the 3.5mm type and it should only be necessary to connect one wire to these as the screw section is normally connected to the earthing tag.

Screened wires in this section are not really necessary since the impedances and the signal levels are fairly low.

THE CIRCUIT BOARD

The majority of the components are mounted on a piece of Veroboard, 0.15in. matrix, $2\frac{1}{2} \times 2$ in. (16 \times 12 holes) with the strips running across the shorter side. $2\frac{1}{2}$ in. is a standard width in Veroboard and the 12 hole length can be cut from a longer length.

It is necessary to drill out two corner holes as shown with an $\frac{1}{4}$ in. drill for the mounting screws and to break the strips around this to stop the bolts shorting them out.

The copper strips are broken at J2 and G6 and jumper wires are connected from K1 to K7 and from L5 to L13.

The arrangement shown in Fig. 6 brings all the connections to row L and pins are soldered to holes L2, L5, L6, L7, L12 and L14 for connections to be made later.

As Fig. 6 shows, some of the components are mounted vertically while others remain horizontal. All transistors are mounted in their 'natural' positions, that is none of their leads are crossed. All of the transistors have one flat edge and if Fig. 6 is followed there will be no possibility of wrong connection. Make sure that all electrolytic capacitors are mounted the correct way round, polarities are shown in Fig. 6.

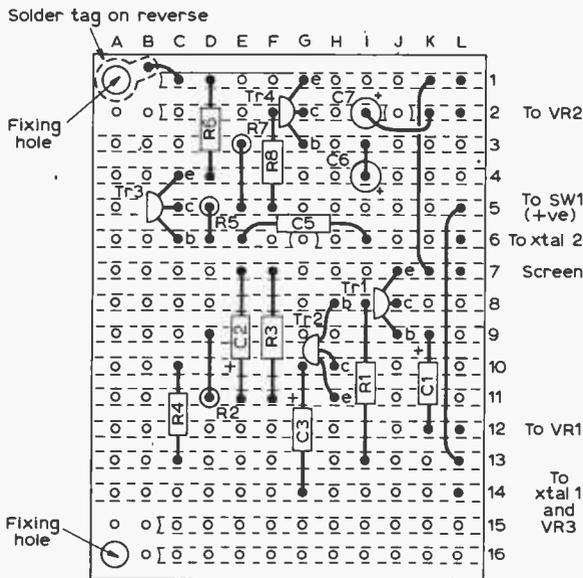


Fig. 6: The component layout on Veroboard.

When securing the circuit board to chassis 2 fit a solder tag under the top screw and run a wire to hole C1, this provides the negative connection; the battery negative lead also goes to this point.

Once the circuit board is fitted, the wires from the control panel can be connected to the pins as shown.

Wires must be run from L7 and L1 to X1, the drive crystal. These wires need not be screened as one side is at fairly low impedance. However the connection from X2, the pickup crystal runs from a high impedance to the high impedance presented by Tr3 and a screened lead must be used here. The inner should go to L6, the screen to L7.

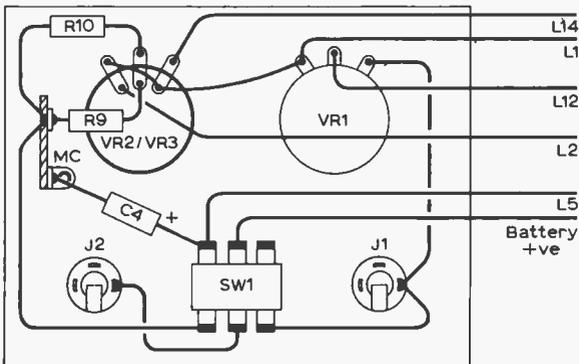


Fig. 7: Rear view wiring of the control panel.


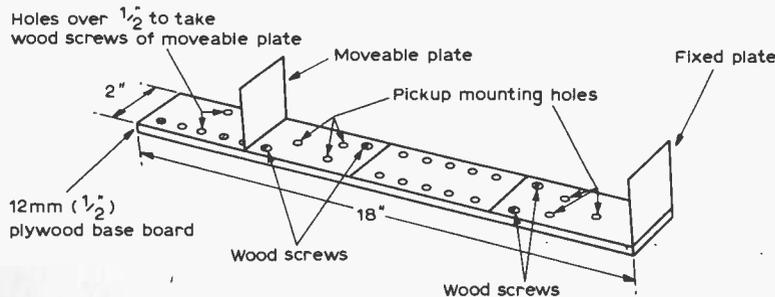


Fig. 8: Method of increasing delay period.

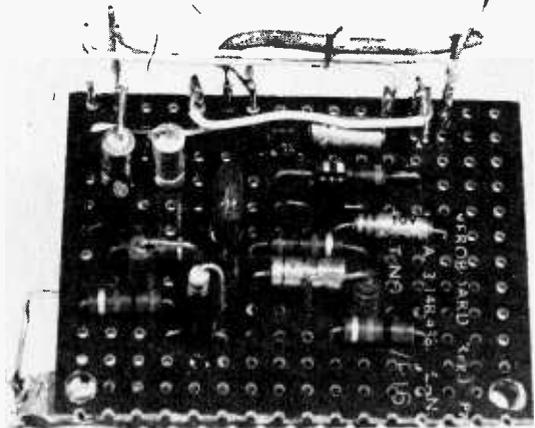

The Veroboard layout; compare this with Fig. 6.

OPERATIONAL NOTES

Once the connections have been made the unit is ready for testing. This is best done by connecting the input to the volume control on a transistor radio to J1 and using a crystal earphone with a 3.5mm plug in J2. The radio should provide a choice of different types of music and speech for testing. The reason for the crystal earphone is that it will not load the output and if there are any faults it is easy to connect a crocodile clip to the earth of the earphone and trace the signal through to establish the position of the fault.

When all is well, turning VR2/VR3 should now give a smooth transition between no reverberation and all reverberation. If a radio is used it will be noticed that the difference on music will be small but considerable on speech.

One problem that was envisaged by the author but which did not materialise was phasing. It could be that the outputs of amplifier 1 and amplifier 2 are out of phase and this will lead to no signal output—or a weird one—at the centre setting of VR2/VR3. Although not experienced by the author this may occur and the connections to one of the crystals might have to be reversed. If this does not cure it a different spring almost certainly will.

LONGER DELAY


Once the reverberation unit has been built and tested it is a simple matter to remove the delay spring and cut chassis 1 in half.

The right hand section (viewed from the front) should be screwed to a piece of 12mm (1/2 in.) plywood 18 in. x 2 in. The other pickup section can then be sited at an experimental length of say 12 in. from this and a longer spring fitted. A series of positions can well be drilled in the new plywood bed.

It is well worthwhile experimenting with various lengths and tensions of spring, bearing in mind the previously mentioned matter of phase relationship which may cause trouble.

Details of a cabinet are not given but this can be made easily from hardboard or plywood.

THE MW COLUMN

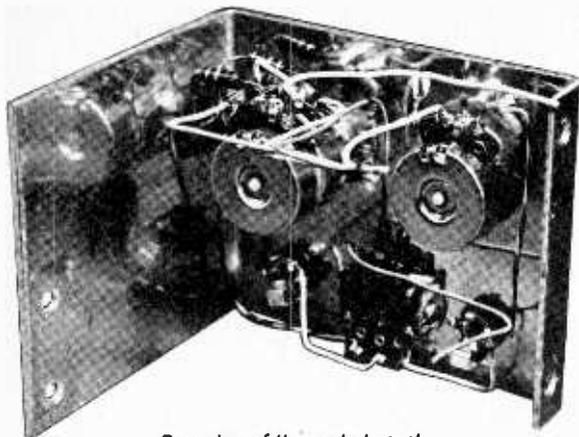

Rear view of the control panel.

★ components list

Resistors

R1 100k Ω	R6 1k Ω
R2 6.8k Ω	R7 2.2M Ω
R3 100 Ω	R8 1k Ω
R4 1k Ω	R9 22k Ω
R5 2.2M Ω	R10 22k Ω

All resistors $\frac{1}{2}$ watt 10% types
 VR1 10k Ω log.
 VR2 + VR3 25k Ω + 25k Ω ganged lin.

Capacitors

C1 10 μ F 16V	C5 0.1 μ F polyester
C2 32 μ F 16V	C6 10 μ F 16V
C3 2 μ F 16V	C7 10 μ F 16V
C4 100 μ F 16V	

Transistors

Tr1 BC169C	Tr3 BC169C
Tr2 BC169C	Tr4 2N2926G or BC169C

Miscellaneous

Two crystal pickups; two 3.5mm jack sockets; slide switch, two pole two way; Veroboard 2 $\frac{1}{2}$ in. \times 2in. (16 \times 12 holes) 0.15 in. matrix; PP9 9V battery; Insulated stand-off tag; metalwork and spring—see text.

However, make certain that the combined chassis are not fixed directly to the base but are mechanically insulated from it, using foam rubber, since the loudspeakers, which will presumably be operated in the same room, will otherwise cause acoustic troubles.

In operation the reverberation unit has proved entirely satisfactory, giving results better than hoped for, even using the extremely short delay of the 6in. bed.

P.W. BINDERS

Preserve your copies of Practical Wireless. Don't let them become torn and dirty—buy a hard-cover binder for 15s. 0d. from:

Binding Department,
 IPC Magazines Limited,
 Tower House,
 Southampton Street,
 London, W.C.2.

Price includes post and packing.

SOME of the more exotic DX on the medium waves is heard in mid-summer between the hours of 0200 and 0400 GMT. Last year Kitwe, Zambia 1070kHz was logged on July 1st at 0255hrs by Harold Emblem of Warrington, Lancashire, and Johannesburg 1286kHz by Glyn Morgan, Tredegar, South Wales on June 22nd at 0230hrs. Others heard in this country are Dar-es-Salaam, Tanzania 629; Bloemfontein 782; Lourenço Marques, Mozambique 917; Pretoria 1268. New stations that could be logged at this time are Abu Dhabi, Qatar in the Persian Gulf, on 809; *Radio Yaounde*, Cameroon on 998 with 10kW; *Radio Angola*, Portuguese West Africa, also on 998; *The Voice of the Coast*, Trucial Oman 737.

During the evenings in summer, stations from the Near East are often logged. From 2100hrs onwards look for Riyadh, Saudi Arabia on 588kHz approx. (it wanders); Jerusalem 677; Aleppo, Syria 746; Beirut, Lebanon 836; Omdurman, Sudan 960; Diyarbakir, Turkey 1061; Haifa, Israel 1097; Kuwait 1345; Shkodra, Albania 1394; BBC Relay Masirah Island 1410. The Greek Armed Forces operate a number of MV stations, two of which have been logged recently—Thessaloniki 1178 and an out-of-band and unlisted station on 1610kHz. Try the long waves for a change and some interesting DX in the late evening. The part of the LW band between 280 and 433kHz is clear of locals and contains a number of Asiatics plus a few distant Europeans. The regulars are Minsk, USSR on 281; Orenburg, USSR 300; Ashkhabad, Turkmenia 375; Kharkov, USSR 385; Minsk, 400; Oulu, Finland 433. A good outdoor aerial is an advantage on this band and a screened lead between the aerial and receiver should eliminate TV buzz.

It is now mid-winter in the Southern Hemisphere and we are at the height of the season for Latin American DX. Stations from the south of the continent appear at about 0130hrs GMT and gradually increase in strength until sunrise. Brazilian stations are usually very strong; look for PRA3, 860kHz, *Radio Mundial* in Rio de Janeiro; PRF4, 940, also in Rio; PRF8, 980, *Radio Nacional*, Rio; PRB9, 1000, *Radio Record*, Sao Paulo; PRG9, 1100, *Radio Nacional*, Sao Paulo; PRE3, 1180, *Radio Globo*, Rio; PRH6 1340 *Radio Guarani*, Belo Horizonte. The language used in Brazil is Portuguese. Spanish speaking Latin Americans include HJDK, 750kHz, *La Voz de Antioquia*, Medellin, Colombia; CX16, 850, *Radio Carve*, Montevideo in Uruguay; LR3, 950, *Radio Belgrano*, Buenos Aires; OAX4U, 1010, *Radio America*, Lima, Peru; YVRS, 1020, *R. Margarita*, Venezuela; CB106, 1060, *R. Mineria*, Santiago de Chile; LR1, 1070, *R. El Mundo*, Buenos Aires; CB118, 1180, *Radio Portales*, Santiago; CX140, 1400, Tacuarembó, Uruguay. The *Voice of America* operates a station on Marathon Key in Florida on 1180kHz which broadcasts in Spanish and could easily be mistaken for a Latin American. This frequency is shared with WHAM Rochester N.Y. and *Radio Globo* in Rio, any of which may be heard.

CHARLES MOLLOY

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

YET another month has gone by and still the number of reports to this page is on the increase; the first one this time comes from **C. R. S. Stacey** of Tunbridge Wells who has a Lafayette HA-700 and an indoor Joystick:—

- 4825 *Radio Ashkabad*, Home Sce. 1905-1945
- 4870 *Radio Ceylon*, Comm. Sce. 1707-1745
- 4965 *Zambia* in English at 1853-1928
- 4975 *Radio Dushanbe* at 1611-1637
- 21455 *VOA*, Tangier in English at 1435-1626
- 21480 *RSA*, S. Africa in English at 1800-1845
- 21485 *R. Australia* (Darwin) at 1417-1430

A new reporter this month is **V. P. Smith** of Banbury who does not say what equipment he uses but he managed to hear the following:—

- 9560 *R. Amman*, Jordon in English at 1706
- 9590 *R. Vilnius*, U.S.S.R. in English at 2230
- 11672 *R. Pakistan* in English at 1945-2030
- 11710 *RAE*, Argentina in English at 2300
- 11855 *Jeddah*, Saudi Arabia in French 2025
- 15160 *R. Ankara*, Turkey in English 2200-2230
- 15165 *R. Damascus*, Syria in English at 2030
- 15405 *R. Kuwait*, English news at 0800

Another new reporter is **R. Blakey** of Newcastle upon Tyne who used an R107 and a 50ft long-wire to hear some very interesting stations including:—

- 4810 *R. Popular*, Venezuela in Spanish at 0150
- 4980 *Ecos del Torbes*, Venezuela in Sp. at 0600
- 4990 *Barquisimento*, Venezuela in Spanish, 0600
- 5026 *Uganda* with news in English at 1800
- 9530 *R. Afghanistan* in English at 1800-1830
- 9545 *R. Ghana* in English at 2045-2215
- 15105 *R. Japan* in English at 2100-2130
- 15165 *VOA*, Philippines in English at 2200
- 15350 *R. Lebanon* in English at 1830
- 17895 *Free China* in English at 1800-1900

Roy Patrick of Derby sent in another interesting report. He starts by saying that he has logged *Radio Australia* on a new frequency of 21485 with sign-off at 1330, he believes that this is the Darwin relay station and he is correct in this assumption.

The full schedule from *Radio Iran* is as follows: Foreign Service on 17735 and 15135 with English at 2000. Roy has also heard these broadcasts on 7064. The Home Service operates on 11730, 7064 and 3998, and a number of regional stations operate as follows: *Radio Tabriz*, 6155, 7.5kW, 0220-2030; *Radio Rezaieh*, 6940, 500W; *Radio Sakandaj*, 6818, 400W; *Radio Gorgan*, 6520, 400W.

Roy has also received a press cutting from New Zealand which gives the news that the off-shore station *Radio Hauraki* has been granted a licence to operate a private commercial station in the Auckland area. *Radio International* which leases time from NZBC will also have a licence to operate a private commercial station in the same area. This is a

Times in GMT • Frequencies in kHz

THE BROADCAST BANDS

Malcolm Connah

reintroduction of private commercial radio in New Zealand.

S. J. Plant of Cwmbran, Monmouthshire, describes his equipment as "a domestic superhet complete with images, and the antenna used varies from a 30ft vertical (courtesy of T.V. rental company) to an 80ft long-wire end-fed." Some of the stations he heard were: *BBC*, Atlantic relay, Ascension Island on 15235 at 0730; *Radio Beirut*, Lebanon in English on 11785 at 0130 and on 11790 at 0230; *Radio Pakistan* in English on 11672 at 1950; and *Trans-World Radio*, Bonaire, Netherlands Antilles on 11820 at 0054.

Alan Crookes of Sheffield has a Unica UNR-30 receiver with a 120ft long aerial at 15ft and some of the stations he has heard are: *HCJB*, Ecuador in the 13 metre band; *Radio Sweden* in the 19 metre band; *The Voice of Vietnam* in the 19 metre band and the Windward Islands Broadcasting Service in the 13 metre band.

John Adams also of Sheffield has a Veritone CR-150 with a Joystick antenna and a Joymatch antenna and he received:—

- 15165 *R. Damascus*, Syria at 2050
- 15345 *Radio Kuwait* at 1655
- 17760 *Radio New York Worldwide* at 2100
- 21480 *RSA*, S. Africa at 1823
- 21595 *CBC*, Canada at 1638.

T. R. Gibbs of Swindon sent in the following list of stations that he has heard recently: *Radio Damascus* on 15165 from 2145-2215; *Radio Ankara* on 15160 at 2300-2330 and *Radio Ghana* on 9525 at 1445-1630.

Radio North Sea International

At the request of several people who have written to me I will include some details about this station. At the time of writing the short wave transmitter is still off the air. On the 10th of April the station re-opened on the new frequency of 1578kHz and they were very apologetic about the interference that they had caused to essential communications services. On the afternoon of the 15th April, however, a jamming signal was broadcast by the Ministry of Posts and Telecommunications and the station went off the air. I understand that they intend to start broadcasting again as soon as they have had a chance to change their frequency again.

Anyone who is interested in these broadcasts may be interested in joining the Free Radio Association whose address is 239 Eastwood Road, Rayleigh, Essex. *R.N.I.* announced that reception reports should be sent to this address.

All reports, preferably in frequency order, should arrive at 58 Kensington Gardens, Ilford, Essex by the 17th of each month.

THE AMATEUR BANDS

David Gibson, G3JDG

A SUGGESTION for something a bit different comes in this month from Alan Gordon, G3XOI. He suggests that hidden stations in D/F hunts may well appreciate a signal report. Alan is often a hidden signal generator himself, running 700mW to 1W, and says he will QSL 100 per cent for SWL cards giving useful information on his sigs from ten miles or more. He is in the Chelmsford area and lists the following D/F hunts for topband enthusiasts to listen out for: June 14 and 21; July 19 and 26; August 23 and September 13.

The bands have been kind to the patient this last month. John Young (Oxsted) logged half Europe on his Pye domestic receiver on 7 and 21MHz. J. Hind (Manchester) reckons that 2400 until the cock crows is the time to QRX on 7MHz if you want to bag the goodies. Fill in the time until midnight by digging a hole in the back garden. It'll be handy for a good earth and give the neighbours something to talk about, too.

David Robson (Co. Durham) admits that he is weakening and listening on the amateur bands when the BC bands are slack. (From killiwatts to milliwatts?) He says that the RA prefix is worn by v.h.f. types, but in the U.S.S.R. 28MHz is included.

High Logs

I have just joined the R.S.G.B. says J. Martin (Edinburgh). The receiver is a DFG 24/2 which duly reported signals on 14MHz from: AX3IAC, AX3MO, AX4ABJ, AX5MF, JA1JAN, JA1WOX, JA6PVR, PY1CAD, PY2BFO, PY7AOJ, PYØAWD, TF2WKP, TF5TP, W5IU, W6IZ, W7RS, ZM1BHO, ZM3DIJ, 4X4RW, 4X4WP, 4Z4BJH.

David Henbry (Rye), KW77, 7ft. vertical at 30ft. reports on some very nice 14MHz DX sigs from: AC3PT, AP5HQ, FB8WW, FK8BH, FO8AB, FR7ZG, KC6BY, KS6DH, KX6VF, TJ8AT, UA9VH/JT1, VKØHM, VQ9CD, VS5PH, YBØAAE, YBØAB, YK1AA, ZD5X, 9V1PM.

D. Brown (Kent), QP166, CR100/2, 45ft. end fed bagged these on twenty s.s.b. between 0600 and 0800: AX3AF, AX2PJ, AX2UDK, VE3AJK, VE2DDO, VK3LN, VK3OB, ZL3GE, ZL3UY.

M. Bayes (Surrey), 9R59DE, 100ft. long wire had a snuffle round 21MHz. Aromas à la r.f. from: CE3RR, CE6CA, CN8HL, CR6GA, CT2AT, EA6DJ, EA8AB, EL2BZ, EP2FB, ET3RU, HC1JC, HS5BD, JA1LCG, JA2LZN, JA3PDV, JA5FZR, JA6HSC, JA7GSN, JA8AHH, JAØCUV/P1, JH1FGS, JH1GNE, JR1VUH, JW7UH, K5QHS, KG6BZ, KP4OC, KR6HR, LU5DL, LX2LQ, MP4MBB, PJ9JR, PZ2AH, SU1CB, VE1ASJ, VE2AQS, VE3GCO, VE5NW, VE7ABB, VK5BB, VK5PB, VP9GE, VU2DK, W6OJO, W7IJX, WA5PDF/P/HC1, YA9VH, YV1SA, ZD9BM, ZE1GB, ZE2KL, ZM1AMK, ZM2MQ, ZM2NY, ZM3QM, ZS1AK, ZS2PD, ZS3TV, ZS6IW, ZX2DVH, 3Z8AJK, 3Z8JAC, 4U3OV, 4Z4HF, 5Z4LR, 7Q7BC, 9G1GD, 9H1BA, 9Q5FM, 9Y4MM. All these on s.s.b. with lowest report of 5 and 5.

A. Usher (Cheshire), B40, 80ft. long wire, deter-

mination, logged: AP5HQ, CR6GA, DU1FH, IRØCM, JA1WTI, JA6MBL, K6BW, K6ND, KR6UYC, TF2WKF, VU2OLK, VE5UI, VP7CG, VK2AN, W5BG, W6DQE, YD1CD, 9K2AV/A, on 21MHz s.s.b.

T. Maxwell (Lanarkshire) tells of hoards of a.m. Russian stations heard on 28MHz. Other stations heard on the CR70A and 18ft. end fed include: EP2DX, SVØWK, UH8BX, UT5OF, ZS6BDD, 3V8AL and 9J2EJ, all on s.s.b.

D. Clark (Bucks) has just completed a homebrew receiver using a GC166 front end, single conversion with a 1.6MHz i.f. Topband, yielded a signal from 9H1BL at 469; while at the other end, on ten metres, Desmond raised: CR6GA, CT3AW, CX2CN, FL8MB, FR7ZW, HK3VA, HR2HHP, HS1ABC, KG6AAY, KR6HS, KV4AD, PY2DVH, PZ1CU, RAØABV, TG1AU, VQ8CW, VU2KV, YA1EXZ, YS2CEN, ZE6JN, 5H3LV, 5N2ABG, 5Z4MD, 8P6BQ, 9J2EJ, 9K2BG, 9X5AA.

Low Logs

I. Simpson (Newcastle upon Tyne), Marconi Guardian receiver, 120ft. end fed had a session on 3.5MHz from 2105-0230. Results of the vigil include squeaks from: CR4BC, CT1MC, EA8HA, GC3UML, HM5KD, KZ5AE, OD5DA, PJØHTR, TW3AX, VO1NP, VS6DO, ZX2DO, 5Z4KW, 9H1DA, ZS8AJK.

P. Johnson (Durham), RX60, PR30, a.t.u. and "various aerials" reports weak r.f. on 3.5MHz from: CT1MC, CT2AK, K1OVO, K2RSR/VP9, PY7BFN, TF3BV, TF5TP, VE1AIH, VO1FG, VP2VI, YV5BTS, 6W8DY, 9H1BA.

S. Ireland (Kent), PW Clubman Mk. II, 19 set variometer, 67ft. end fed has been burning the candle at three ends. Surveillance times were 2230-2400 and 0430-0630. Resultant vibration to the eardrums from: CO2FA, CT1BH, CT2AT, CR4BC, EA8HA, HC4BS, HK3WD, HK3ACN, HKØBKW, HP1JC, HR2PEV, JW7UH, JX8IL, KG4AS, KZ5DA, OA8V, PJ7CC, PZ1AH, TF5TP, TG9CD, PY7AF, VEØMS, VP2EX, VP2SY, XE1J, XE1KS, YV5BTS, ZL2BDK, ZL2AJQ, ZL2BCG, LZ4NH, ZM3GQ, ZM3AAV, 4X4UF, 6W8DY, all 3.5MHz. Steve queries the callign O13QA.

J. Cross (Dorset), AR88D, 60ft. end fed braved 7MHz and surfaced with: AX3AOW, AX3HW, AX3ND, AX7KJ, CN8MN, OA4AB, PY2EWL, PY4AP, VK2AVA, XE2IH, YV1AGT, YV2OV, YV4TI, ZS6BDO, ZL2PG, all on s.s.b.

D. Quint reports a heavy concentration of G stations on 7MHz, which is often a good starting place to begin listening to the DX.

Happenings

Very busy month is June especially for rally enthusiasts. Contests include: June 6-7th, N.F.D.; 14th, microwave contest (above 1,296MHz); 14th, DF event at Salisbury; 21st, 4 metre portable; 28th, DF event at High Wycombe; July 4-5th, 1.8MHz contest; July 4-5th, 2 metre contest. Mobile rallies: June 14th, Anniversary rally at HMS Mercury, Portsmouth; 20-21st, Anglian rally at Ipswich; 21st, rally at Singleton Park, Swansea; 28th, Longleat rally.

practically wireless

commentary by **HENRY**

Mods to Follow

ONE knack I did learn at Oxford, said Alan Brien, was always to wait for the second edition of any work of scholarship. Only after all the author's friends and colleagues had courteously put the boot in could you be reasonably confident that major errors, omissions and misprints were corrected.

I must confess that I feel the same way about radio and audio equipment. My son, who is one of these mad rallyists, assures me that the same 'second-thought syndrome' is evident in the world of the automobile. He, and I, would not dream of purchasing a prototype, even if we could afford anything better than a 'one-owner, low mileage' second-hand model.

I can only hope that these remarks do not make too many readers glance nervously over their shoulders at that gleaming 'new' radio which has just been added to their insurable assets.

Those of us who are on the mailing lists of equipment makers are accustomed to receiving regularly the details of modifications to current equipment. The process begins even before we have unpacked the first of the new models—as if some Johnny in a white coat stood at the factory gates shouting: 'Bring that back, I haven't finished making it yet!'

Sometimes it seems pointless; half a sheet of foolscap wasted on the instruction, '... for watts read Watts' or a note that where a green wire is fitted the non-existent black will no longer be

used for an earth return. But at other times one studies the list of necessary alterations, mentally tots up the cost of the time needed to make them, deducts it from the profit on the sale and offers up curses.

Buttin: why can they not perfect the equipment before it is allowed to leave the factory?

Henry: well, I don't rightly know. Let's ask that Production Manager who just by chance happens to be passing through the office.

He, poor chap, has to waffle grandly about 'a continuing policy of improvement' to hide the fact that he blames it all on those lazy blighters in Design. They, with some justification, pass the ball back into production's court, and have a sideswipe at Inspection on the way.

'We are given a basic specification,' says an earnest-looking graduate. 'And we mock-up a working model. From there, someone else takes over and costs it—'

'—and what comes out is nothing like the ruddy original,' muttered his breadboard man. Fairly new to the game, he still resents his work being eschewed in the name of the great god Economy.

After that, the production line starts swinging along and several hundred sets have been made, tested and packed before somebody realises that changing the rectifier from ABC rating to XYZ means that the electrolytic capacitors are going to last about as long as it takes the first dealer to demonstrate the junk. Immediately the modification sheets are drawn up ... 'we leave no stone unturned ...' and better capacitors are forwarded to distributors. Then it strikes some boffin that the resultant surge is going to strain the emitter load of the output pair ... 'in our quest for perfection ...' and another emendation is made.




"Bring that back, I haven't finished"

But what about us? You and me, Joe. We may have bought a Superset Special, pristine fresh in its polystyrene packing. Shall we feel confident that we have got the ultimate in Superset design, or will there always remain that niggling doubt that there have been modifications that we shall never know about?


I think of all those owners of Mark I Buzz-Box amplifiers who have been uneasily accepting a hum level like the noise that the BBC are currently perpetrating on the West of England Home VHF (now that they have eradicated the whistle). Mark II models have the loudspeaker return lines earthed to a different point on the chassis than the outer end of a bus-bar where the input sockets are fixed.

Buttin: now you are inventing ...

Henry: don't kid yourself. Some of these half-baked essays in construction that reach the showrooms would shame PW readers with any pride in their workmanship. And most of the time the inadequacy is due to sheer greed and shortsightedness—a rush to get the thing onto the market before it has been thoroughly developed. Every new set ought to be given a six-month trial run in a houseful of growing kids. And just now again someone in authority might care to listen to the criticisms that feed back from the dealer and his service staff.

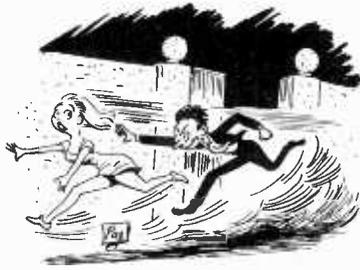

One knack I did learn at Oxford ...

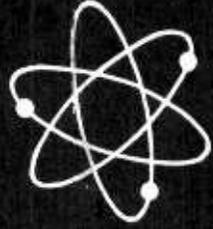

A NOVEL AERIAL FOR VHF

ARTHUR DOW

THE idea for this particular aerial came one day when the author found himself gazing absent-mindedly at one of those charming Chinese wall pictures that are to be seen occasionally in this country. These pictures are made of a frame of iron wire on which are mounted pieces of thin metal cut out to depict typical Chinese scenes such as pagodas, birds and farm animals, not forgetting the farmer.

However, the author, with his one-track mind, saw the wire frame as the basis of a u.h.f. slot aerial! Further thoughts developed along these lines and it became a ground plane and this led on to thinking about the DDDR aerial that to date seems to remain mainly a theoretical concept with little published information on successful practical applications, especially by amateurs.

The DDDR aerial, or to give it its rather clumsy full name of the Directional Discontinuity Ring Radiator, is vertically polarised normally and was first described by J. M. Boyer in 1963. Great things were expected of the design, which is basically a single loop aerial working against another loop on the ground or a ground plane which must be somewhat larger in area than the loop. (Fig. 1.)

The aerial is tuned to resonance by the variable capacitor and the feeder matched to the aerial by adjustment of the position of the feed point X. The various dimensions can be worked out for any particular frequency from the following formulæ:

$$\text{Height of loop } H = \frac{8.5}{F(\text{MHz})} \text{ ft}$$

$$\text{Circumference of loop } C = \frac{252}{F(\text{MHz})} \text{ ft.}$$

$$\text{Feeder tap } X = \frac{28}{F(\text{MHz})} \text{ ft.}$$

The formula for the feed point assumes the use of coaxial cable of about 52Ω impedance.

In starting to work out a practical design one is immediately struck by the compactness of the aerial, especially in view of the claims made for its performance. Typically, on the 20m amateur band the height would be only 6in. and the diameter of the loop 54in.!

However, the author's immediate problem was poor reception of the BBC v.h.f. programmes. The commercial receiver in use has a built-in aerial consisting of a loaded dipole which gives fair results when correctly aligned with respect to the local station. Unfortunately, the receiver is also a piece of furniture and its unalterable position in the drawing room puts the dipole end-on to the station!

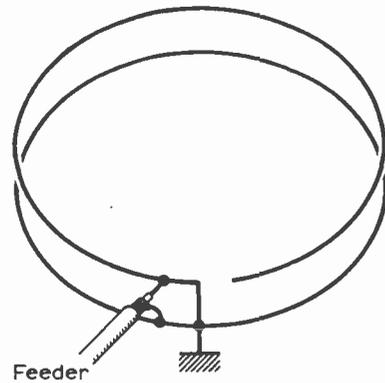


Fig. 1: Layout of the basic DDDR aerial.

It would, of course, be simplicity itself to put up an outside aerial but that project is a long way down the list of "things to be done". This is where the Chinese wall picture and the DDDR aerial came together and a design worked out for such an aerial which could be hung on a picture rail in the correct position for best reception, be near to the receiver and yet still be decorative.

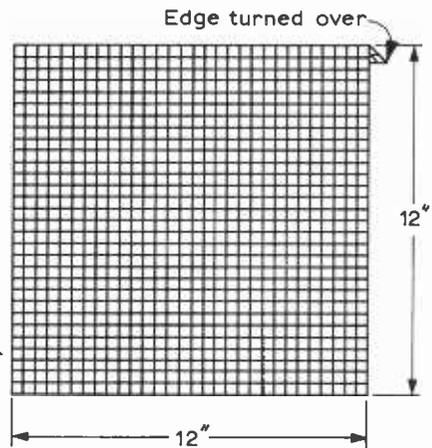


Fig. 2: Ground plane formed from wire netting.

Construction

The ground plane in this case is made from wire netting of about 1/4in. mesh with the top edge turned over to allow it to be hung on the picture rail. (Fig. 2.) The loop is formed from copper wire of 16 s.w.g.

bent to the shape shown, before fitting it to the ground plane. (Fig. 3.)

In the search for suitable stand-off insulators, some were found with soldering tags at each end and which were just the right height for the job. Three were used but more can be fitted for additional rigidity of the loop if thought necessary.

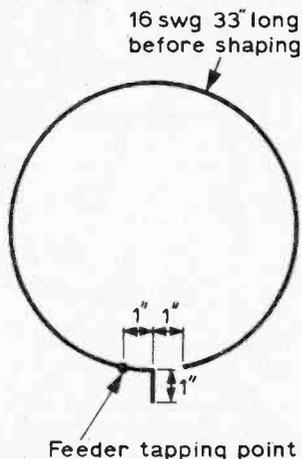


Fig. 3: Formation of aerial loop.

The loop is centralised on the ground plane and the end of the vertical portion of the loop soldered to the nearest convenient wire of the ground plane. The three insulators were then positioned and likewise soldered to the ground plane.

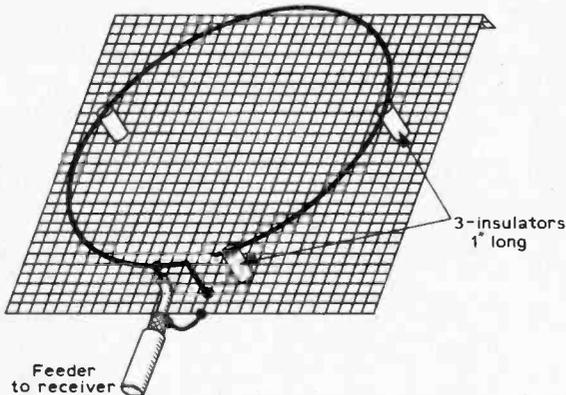


Fig. 4: Completed DRR aerial for VHF.

A suitable length of 72Ω coaxial cable about $\frac{1}{4}$ in. diameter was attached by soldering the outer braid to the ground plane and the inner conductor to the tapping point on the loop. A co-axial connector was fitted to the other end of the cable and plugged into the receiver after disconnecting the internal dipole.

The completed aerial (Fig. 4) was then sprayed with paint from an Aerosol can, the colour being chosen to match the decor of the room. Before painting, the insulators were temporarily covered with Sellotape to protect them.

When the aerial is hung up the ground plane is vertical and the polarisation horizontal as required for the v.h.f. transmissions. The aerial should be moved around until best reception is obtained. ■



ISSUES FOR DISPOSAL

- ... all 1968 issues of P.W.—G. Taylor, 57 Woodlawn Road, Fulham, London, S.W.8.
- ... P.W. from June 1965 to September 1967 except for September 1965 and May 1967. S.A.E. for details.—D. Pearey, Hiatt Baker Hall, Parry's Lane, Bristol, BS9 1AD.
- ... copies of P.W. and W.W. from 1931 to 1939. The P.W.'s are 1946-47 and odd issues up to 1968.—L. Keyte, 31 Greenfields, Redditch, Worcs.
- ... a number of P.W.'s from 1955 to 1966. S.A.E. for details.—L. V. Thomas, 69 Haverstock Court, St. Paul's Cray, Kent.
- ... over 40 copies of P.W. (1967 complete) (1968 January to July) with blueprints. Sell or swap for stamp collection.—Cyril Timmins, 16 High Street North, West Mersea, Colchester, Essex.
- ... May 1965-April 1966, May 1966-August 1967, January 1968-March 1968.—S. L. Stanbridge, 45 Roman Road, Worthing, Basingstoke, Hants.
- ... P.W. from December 1963 to February 1966. Will sell or exchange for transistor components.—A. Beveridge, The Schoolhouse, Tibbemor, Perth.
- ... issues of P.W. from 1951 to 1966.—L. Levell, Popes Hill, Newnham, Glos.
- ... 57 issues of P.W. from 1961-66 in excellent condition. 47 copies before 1961 in reasonable condition. S.A.E. please.—M. Pardoe, 3 Dunwell Avenue, Newby, Scarborough, Yorks.
- ... many issues of P.W. and P.T.V.—J. Foy, 101 Sandringham Road, Birmingham 22B.
- ... P.W. from January 1956-April 1968 inclusive. Will sell or swap for anything interesting electronic or otherwise.—I. R. W. Bram, 38 Muirfield, Perth, Scotland.
- ... 1968 issues January-November. Also Radio and Television Servicing 1966-67 models.—A. S. Holmwood, 8 Dock Street, Pembroke Dock, Pembro.
- ... copies of P.W. from 1959 to 1967 (42 copies).—E. D. May, 104 Northumberland Avenue, Hornchurch, Essex.
- ... P.W. July 1964 to April 1966, May 1966 to February 1969 and P.E. October 1965 to February 1969. S.A.E. for details.—I. P. Brockley, "Torbeth", New Road, Bignall End, Stoke-on-Trent, Staffs.
- ... 30 copies (1950-1953) of P.W., 60 copies (1963-1968) of P.W. and 48 copies (1948-1952) R.S.G.B. Bulletin.—W. H. Booker, 45 Annesley Road, Greenhill, Sheffield, S.
- ... most copies of P.W. from 1961. S.A.E. please.—P. Barrow-Maudsley, 1a Well Street, Buckingham.
- ... large numbers of P.W.'s and a full set of P.E. from start to May 1969. Offers.—S. Heap, 29 Broadway, Helmsshore, Rossendale, Lancs.
- ... all 1964, 1965 and 1966 issues. All 1967 except July and the full set of 1968. Can only dispose of in years.—J. Currie, 156 Hillhead Road, Kirkintilloch, Dunbartonshire, Scotland.
- ... copies of P.W., P.T.V. and P.E. and 400 service sheets. Large S.A.E.'s please.—D. W. Robson, 125 Atkinson Road, Newcastle-on-Tyne, NE4 8XX.
- ... numbers of P.W. in very good condition.—A. S. Davy, 123 Chapel Road, Brightlingsea, Essex.
- ... many issues of radio magazines going back to 1946.—A. G. W. Thompson, Thursley Cottage, Church Road, East Molesey, Surrey.
- ... May 1963, September and November 1964, November and December 1965 and January and February 1966.—D. P. Matthews, 18 Queen Anne's Gardens, Bush Hill Park, Enfield, Middx.
- ... P.W. issues January to December 1968, January to October 1969 and Radio & TV Servicing 1966 '67. S.A.E.—A. S. Holmwood, 8 Dock Street, Pembroke Dock, Pembro.
- ... many issues of P.W., P.T.V., W.W., P.E. and R.C. Will dispose of in years (12 issues).—E. T. Bradford, 160 West Drayton Road, Colham Green, Uxbridge, Middx.
- ... most issues of P.W. from 1943 to 1967. Sell or exchange WHY.—W. J. Anderson, 18 Stuart Road, Welwyn, Herts.
- ... an almost mint copy of No. 1, Volume 1 P.W. Offers ?—T. E. Phelps, 143 Barn Mead, Harlow, Essex.

BOOKS WANTED

- ... radio and Television Servicing volumes 61-62, 62-63 and 64-65. Details to P. Hoyle, 95A Pimlico Road, London S.W.1.

CORRESPONDENTS WANTED

- ... someone of my own age (13) who is studying for the RAE.—Kenneth May, 71 West Street, Erith, Kent.
- ... any reader who has modified and HRC. Also any reader who would be willing to sell me coil packs for this set and anyone who can give me information on the QP166.—Ian Burr, The Hollands, Lower Icknield Way, Chinnor, Oxon.
- ... a shortwave listener who is also interested in radio and electricity in England.—G. Evelyn, 28 Relgate Avenue, Sutton, Surrey.
- ... anyone of my own age (18) who is interested in amateur radio in general.—W. J. Cowell, 35 Bare Avenue, Bare, Morecambe, Lancashire.
- ... anyone of my own age (11) who is interested in semiconductors.—Paul Mallon, 522 Tay Street, Invercargill, New Zealand.
- ... anyone who knows how to wire up a crossover network in an audio system. The unit I am particularly interested in is a Harrow 3-way crossover network, model HN-3.—T. M. Blea, "Tilling", Fair Mile, Henley-on-Thames, Oxon.
- ... anyone of my own age (18) who is interested in short wave listening.—I. Simpson, 2 Taylor Cottages, Derryhale, Portadown, Co. Armagh, N. Ireland.
- ... someone who speaks English, is about 17 years old and who likes anything connected with electronics.—B. Cameron, 84 Pownall Street, Masterton, New Zealand.

TAPESONDENTS WANTED

- ... boy or girl of my own age (17). I have Phillips cassette recorder and a Grundig 4-track machine with speeds of $1\frac{1}{2}$, $3\frac{1}{2}$ and $7\frac{1}{2}$ i.p.s.—Louis Smit, 42 Lanston Road, Montclair, Durban, South Africa.
- ... girl with interest in Amateur radio or electronics. About 16 years old.—R. Collins, 17 Heathfield, Chippenham, Wilts.
- ... my own age (17) from Hong Kong, Kowloon area who are living in this country. I already have a pen friend in Caueway Bay, Hong Kong and know a little about the area. My tape speeds are: $1\frac{1}{2}$, $3\frac{1}{2}$ and $7\frac{1}{2}$ i.p.s. and my hobbies are short wave listening, tape recording and photography and electronics.—A. M. N. Hoare, 4 Fairfield Drive, Whitburn, Sunderland, Co. Durham.
- ... someone of my own age (16) who is interested in electronics and radio. I have a Ferguson 2-track machine with speeds of $1\frac{1}{2}$ and $3\frac{1}{2}$ i.p.s.—R. Richards, 33 Rogers Road, Canning Town, London, E.18.

INFORMATION WANTED

- ... service sheet for an Ultra T491 radio.—D. Gregory, 53 Wellinger Way, Leicester, LE3 1RG.
- ... the addresses of the agents for Japanese transistor receivers and in particular "Challenge" agent. Also details of connections to amplifier and switching connections of the Minister Transistor Royal 410 tape recorder.—G. Kingston, Kruse Cottage, Treveland, Liskeard, Cornwall.
- ... loan of theoretical circuit of Sound Sales amplifier type A-Z aerial A.50/75 and tone unit C51/2.—R. V. Flexman, Horseshoe Cottage, The Haven, Billinghamurst, Sussex.

BSR 4-SPEED SUPERSLIM MODEL UA25 RECORD CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. Size 11 1/2" x 11 1/2" x 11 1/2". Above motor board 3 1/2" below 2 1/2". AC 200/250V.



STEREO/MONO PRICE **£6.19.6** Post 5/6

BSR UA70 Stereo/Mono Transcription **£12.19.6**
Auto Changer. Calibrated Stylus Pressure.
BSR Minichanger UA60 Stereo/Mono. **£7.19.6**
Size 12 x 8 1/2 in. AC 200/250V. Post 5/6.

GARBAR PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond/Mono Sapphire. SP25 Mk II **£14.19.6**. AT90 Mk II **£14.19.6**. Model 3000 **£12.19.6**. Post 5/6.

RECORD PLAYER PORTABLE CABINET. Space for amplifier and autochanger. Post 5/6. **75/-**

80S DE-LUXE 3 WATT AMPLIFIER. Ready made and tested. A 2-stage unit using triode pentode valve, giving 3 watts output. Tone and volume controls. Isolated mains transformer. With knobs, loudspeakers and valves ECL82, EZ80. Frequency response 50-12,000 cps. Sensitivity 200mV. Post 5/6. **89/6**

R.C.S. TEAKWOOD BASE. Ready out for mounting (State player make and model) **77/6**
R.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted and attractive appearance. **77/6**

EMI PICK-UP ARM. Complete with mono cartridge 29/6.
EMI JUNIOR 4 SPEED RECORD PLAYER. Mains operated motor, turntable and pick up complete. Post 5/6. **59/6**

HI-FI PICK UP CARTRIDGES
GP94 55/-; GP93 45/-; GP91 30/-; GP67 19/6, AC08 LP. 50/- 10/6. All standard fixing complete with stylus.

CRYSTAL MIKE INSERTS
1 1/2" dia. 6/6. AC08 1 1/2" dia. 12/6. BM3, 1" dia. 9/6.

PORTABLE AMPLIFIER

Portable mini p.a. system. Many uses—ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player Amplifier, etc. Attractive resin covered cabinet, size 12 x 9 x 4 1/2 in., with powerful 7 x 4 in. speaker and four transistor one watt power amplifier. Uses PP9 battery Brand new in Maker's carton with full maker's guarantee. World famous make.



Only **75/-** Post 5/-

WEYRAD P50—TRANSISTOR COILS
RA5W Ferrite Aerial. 12/6
Osc. P50/1A0. 5/4
I.F. P50/200 470 kc/s. 5/7
3rd I.F. P50/300. 6/-
P51/1 or P51/3. 5/7
P51/3. 6/-
Ferrite Rod 3 x 1/4 in. 4/-, 6 x 1/4 in. 5/-.

VOLUME CONTROLS
Long spindles. Midset Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 8/-, D.P. 5/-
STEREO L/S 11/-. D.P. 15/-
Edze E.R. Transistor. 15/-
Ideal 925 lines.
WIRE-WOUND 3-WATT POTS. WIRE-WOUND 3-WATT Small type with small knob. Values 10 K to 30 K. Carbon 30 K to 2 meg. **5/-**
800ohm Coax 9d. vd. BRITISH AERIALITE AERAXIAL-AIR SPACED 40 yd. 28/-; 60 yd. 40/-
FRINGE LOSS LOSS 2/- yd. Ideal 925 lines.
LONG SPINDLE 8/-
10 OHMS to 100 K.

VEROBOARD 0.15 MATRIX
2 1/2 x 5 in. 3/8. 3 1/2 x 3 1/2. 3 1/2 x 3 1/2. 3 1/2 x 5 in. 5/2.
EDGE CONNECTORS 16 way 5/-; 24 way 7/6.
PINS 36 per packet 2/4. FACE CUTTERS 7/6.
S.R.E.P. Board 0.15 MATRIX 2 1/2 in. wide 6d. per lin. 3 1/2 in. wide 9d. per 1 in.; 5 in. side 1/- per lin. (np to 17 in.). S.R.E.P. undrilled 1/4 in. Board 10 x 5 in. 3/-.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides. 7 x 4 in., 9/-; 11 x 5 in., 7/6; 11 x 7 in., 9/6; 13 x 9 in., 10/6; 15 x 14 in., 15/-; 9 x 7 x 5 in., 8/6; 14 x 11 x 5 in., 14/6.
ALUMINIUM PANELS 18 s.w.g. 12 x 12 in. 6/6; 14 x 9 in. 5/6; 12 x 9 in. 4/6; 10 x 7 in. 3/6; 8 x 6 in. 2/6; 6 x 4 in. 1/6.
1-inch DIAMETER WAVE-CHANGE SWITCHES.
2 p. 4-way, or 2 p. 6-way, or 3 p. 4-way 4/6 each. 1 p. 12-way, or 2 p. 4-way, or 4 p. 3-way 4/6 each. 1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 12/-, 2 water 18/-, 3 water 24/-, 4 water 30/-, 5 water 36/-.
TOGGLE SWITCHES. sp. 2/8; sp. dt. 3/6; dp. 3/6; dp. dt. 4/6.

ALL PURPOSE HEADPHONES
H.E. HEADPHONES 2000 ohms Super Sensitive 35/-
LOW RESISTANCE HEADPHONES 2-5 ohms 39/6
DE LUXE PADDED HEADPHONE PHONES 3 ohms 79/6

"THE INSTANT"
BULK TAP
ERASER AND
RECORDING
HEAD
DEMAGNETIZER **42/6**
Post 2/6
200/250 v. A.C. Leaflet S.A.E.



★ ALL PURPOSE TRANSISTOR PRE AMPLIFIER BRITISH MADE ★
9-12v. and 200-300v. D.C. operation. Size 1 1/2" x 1 1/2" x 1". Response 2" c.p.s. to 25 Kc/s, 28 db gain. For use with valve or transistor equipment. Full instructions. **17/6 each**
Brand new. Guaranteed. Details S.A.E.

NEW TUBULAR ELECTROLYTICS CAN TYPES
2 350V .. 2/6 100/25V .. 2/- 16+16/500V 11/-
4 350V .. 2/6 250/25V .. 2/6 50+50/350V 7/-
5/450V .. 2/6 500/25V .. 4/- 80+100/350V 11/8
15/450V .. 4/- 3+3/450V .. 3/6 32+32/200V 3/6
32/450V .. 4/- 8+16/450V .. 3/6 32+32/450V 6/6
25/25V .. 2/- 16+16/450V 5/- 32+32+32/350V 6/9
50/50V .. 2/- 32+32/350V 5/- 100+50+50/350V 9/6

SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 2/-; 500, 1000mF 12V 3/6; 2000mF 25V 7/-.
CERAMIC 1pF to 0.01 mF. 9d. 0.1 mF. 3/6. 1mF 3/6. 2mF 150V 3/-.
PAPER 350V-0.1 9d. 0.5 2/6; 1mF 3/6; 2mF 150V 3/-.
500V-0.001 to 0.05 9d.; 0.1 1/-; 0.25 1/6; 0.47 5/-.
1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/6; 0.047, 0.1 2/6.
SILVER MICA. Close tolerance 1%; 2.5-2000pF 1/6; 560-2,200 pF 2/-; 2.700-5,600pF 4/-; 6,800pF-0.01, mtd 6/-; each.
TWIN GANG. "0-01" 206pF+176pF, 11/-; 810w motion drive 365+365 with 25+25pF, 11/-; 600pF 50w motion, standard 9/-; small 3-gang 500pF 22/-.
SHORT WAVE. Silicon 25pF, 11/-; Chrome Telescopic Aerial 22in. 5/-.

TUNING. Solid dielectric. 100pF, 800pF, 500pF, 7/- each. TRIMMERS. Compression 30, 50, 70pF, 1/-; 100pF, 150pF, 1/8; 250pF, 1/8; 600pF, 750pF, 2/-; 1000 pF, 2/6.
RECTIFIERS CONTACT COOLED 1/2 wave 60mA 7/6; 35mA 9/6. SILICON BY213 6/-; BY100 7/6.
Full wave Bridge 75mA, 150mA, 150mA, 9/6; 1/2 w. rect. 10/-.
NEON LAMP RECTIFIERS 200V A/C/D/DC Red. Amber 4/-.
RESISTORS. Preferred values, 10 ohms to 10 meg. 1/2 w. 1/2 w. 1 w. 20% 8d.; 1 1/2 w. 8d.; 2 w. 1/-; 1 w. 10% 6d. HIGH STABILITY. 1/2 w. 10 ohms to 10 meg., 2/-.
Ditto 5% Preferred values 10 ohms to 22 meg., 9d.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K. 2/- each; 2 1/2 watt, 1 ohm to 8.2 ohms 2/-.

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key
1 in. 16/-; 1 1/2 in. 17/6; 1 3/4 in. 19/6; 2 in. 24/-; 2 1/2 in. 44/8
1 in. 16/-; 1 1/2 in. 19/6; 2 in. 24/-; 2 1/2 in. 44/8
1 in. 18/9; 1 1/2 in. 19/6; 1 3/4 in. 21/6; 2 in. 28/-; 2 1/2 in. sq. 36/6

TRANSISTOR MAINS POWER PACKS. FULL WAVE
9 volt 500mA. Size 4 1/2 x 2 1/2 x 2 in. Metal case. **49/6**
Circuit finish. Output terminals. On/off switch.
Bracket Wave 9 volt 50mA. Size 2 1/2 x 1 1/2 in. Snap terminals 32/6

MAINS TRANSFORMERS

250-0-250 50 mA. 6.3 v. 2 amps. centre tapped ... 19/6
250-0-250 80 mA. 6.3 v. 4 amps. 28/-
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 38/-
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 38/-
300-0-300 v. 120 mA. 6.3 v. 2 a. C.T. 6.3 v. 2 a. 45/-
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 15/-
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 17/6
HEATER TRANS. 6.3 v. 1 1/2 a., 10/6; 6.3 v. 4 amp. 15/6
Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1 1/2 amp. 15/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 amp. 38/-
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60, 38/-
AUTO TRANSFORMERS 0-115-230 v. Input/Output, 60 v. 18/6; 180v. 28/-; 500v. 25/-; 1000v. 21/6.
CHARGER TRANSFORMERS. Inpnt 200/250V. 10c or 12v. 1 1/2 amp. 24/-; 4 amp. 38/-
FULL WAVE BRIDGE CHARGER RECTIFIERS:
6 or 12 v. outputs, 1 1/2 amp. 8/-; 2 amp. 11/-; 4 amp. 17/-.

COAXIAL PLUG 1/8, PANEL SOCKETS 1/8. LINE 3/6.
OUTLET BOXES, SURFACE OR FLUSH 5/-.
BALANCED TWIN FEEDERS 1/- yd. 80 ohms or 300 ohms.
JACK SOCKET 2id. 400 ohm 2/6; closed circuit 4/6;
Chrome Lead Socket 7/6. Phono Plug 1/-; Phono Socket 1/-.
JACK PLUGS 8id. Chrome 3/-; 3.5mm Chrome 2/6. DIN SOCKETS Chassis 3-pin 1/6; 5-pin 2/-; DIN SOCKETS Lead 3-pin 3/6; 5-pin 5/-; DIN PLUGS 3-pin 3/6; 5-pin 5/-.
VALVE HOLDERS, 9d.; CERAMIC 11/-; GANS 1/-.

E.M.I. 13 1/2 x 8 in. LOUSPEAKERS

With flared tweeter cone and ceramic magnet. 10 watts.
Bass res. 45-50 cps. Total response Flux 10,000 gauss.
Speech coil, 8 or 15 ohm. **45/-**
Also with twin tweeters. Complete with crossover, 3 or 8 or 15 ohms. 10 watt. **£4**
Recommended Teak Cabinet Size 16 x 10 x 8 in. **£5**

MINI-MODULE LOUSPEAKER KIT

10 WATT 65/- CARRIAGE 5/-
Triple speaker system combining on ready cut fl. fl. 1/2 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 8 ohm.
TEAK VENEREED BOOKSHELF ENCLOSURE. 16 x 10 x 9 in. Modern Scandinavian styled front design for Mini-Module. **£5** Post 5/-

ALL MODELS "BAKER SPEAKERS" IN STOCK
BAKER 12 in. MAJOR £8



30-14,500 c.p.s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell's. Bass resonance 45 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£10.19.6**

BAKER "GROUP SOUND" SPEAKERS—POST FREE
"Group 25" "Group 35" "Group 50"
12in. 6gns. 12in. 8 1/2 gns. 15in. 18gns.
25 watt 25 watt 25 watt 60 watt

TEAK HI-FI SPEAKER CABINETS. Fluted wood front. For 10 or 12 in. round Loudspeaker £9.0.0.
For 13 x 8 in. round Loudspeaker £4.0.0.
For 10 x 6 in. or 6 1/2 in. round Loudspeaker 24.0.0.
LOUDSPEAKER CABINET WADDING 12in. wide, 3/- 1/2

Horn Tweeters 2.1Kc/s, 1W 8 ohm 29/6.
De Luxe Horn Tweeters 2-15 Kc/s, 15W, 16 ohm 59/6.
EMI Plastic Cone 2 1/2 in 8 ohm 17/6.
CROSSOVERS 3 or 8 or 15 ohm 16/6.
SPECIAL OFFER: 80 ohm, 2 1/2 in. dia.: 35 ohm, 3 in. 25 ohm, 3 in. dia.; 6 x 4 in.; 8 x 3 in.; 8 x 6 in. **17/6 EACH**
8 ohm, 8 x 4 in.; 8 ohm, 2 1/2 in. 3 in. 5 in. 5 x 7 in. 7 x 4 in. LOUSPEAKERS P.M. 8 OHMS. 6 1/2 in. 29/6; 8 x 6 in. 21/-; 8 x 2 1/2 in. 21/-; 8 in. 35/-; 10 x 6 in. 30/-.
5 in. WOOFER 8 watts max. 20-10,000 cps. 8 or 15 ohm. 39/6
ELAC 8 in. De Luxe Ceramic 8 ohm or 15 ohm 50/-.
8 in LOUSPEAKER. TWIN CONE 15 ohm 35/-.
RICHARD ALLAN 10 or 12 in. Twin cone 8 or 15 ohm 39/6.
OUTPUT TRANS. EL84 etc. 5/- MIXE TRANS. 50-1 5/-
SPEAKER COVERING MATERIALS. Samples Large S.A.E.

SOUND ACTIVATED PSYCHEDELIC LIGHT

Fascinating light patterns of Green, Blue, Red and Amber. Works with any mono or stereo amplifier. Input required 0.8 watt. A.C. mains operated. Size 13 x 13 x 4 in. **£12.10.0**



ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES
ILLUSTRATED EAGLE CATALOGUE 5/- . Post Free
BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **79/6**
BARGAIN DE LUXE TAPE SPLICER. Cuts, trims, joins for editing and repairs. With 8 blades **22/6**
BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output 9 volt. **59/6**
BARGAIN FM TUNER 88-108 Mc/s 3in Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. **£9.10.0**
Walnut Cabinet. Size 7 x 5 x 4 in.
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. **69/6**

★ RADIO BOOKS ★ (Postage 9d.)
Practical Transistor Receivers 4/6
Practical Radio Inside Out 3/6
Practical Stereo Handbook 3/6
Supersensitive Transistor Pocket Radio Radio Valve Guide, Books 2, 3 or 4 ea. 5/- No. 5 ea. 6/-
T.V. Fault Finding 405/625 lines 8/6
Shortwave Transistor Receivers 5/-
Transistor Communication Sets 8/-
Sub-Minature Transistor Receivers 5/-
Wireless World Radio Valve Data 10/-
International Radio Stations Guide 2/8
Transistor Circuits for Radio Controlled Models 7/8
Valves, Transistors and Diodes equivalents Manual 10/8

3 inch MOVING COIL METERS BRITISH MADE
Various calibrations/movements. 500 Microamp. 1 Milliamp; 50-0-50 Microamp. etc. S.A.E. for list **37/6**

MAINS ELECTRIC MOTORS


(120v. or 240v. AC). Size 2 1/2 x 1 1/2 in. Clockwise 1,200 r.p.m. off load. Rev. duty 4 pole 50mA. Spindle 1 x 3/80 BARGAIN **17/6 EACH**
PRICE Post 2/6
8 for 50/-; 6 for 90/-



Minimum Post and Packing 2/6 RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME.
RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON
List 1/- . Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665
Open 9-5 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)

Never Built a Kit Before?

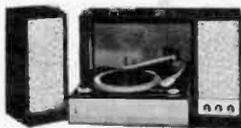Why not prove how easy it is the HEATHKIT way.
Build one of these beginner kits.



Stereo Record Player
Kit K/SRP-1 £27.6.0
Carr. 11/-



Economy SW Receiver
Kit K/GR-64 £24.16.0
Carr. 9/-



Deluxe Car Radio
Kit K/CR-1 (less Spk.)
£12.12.0
Carr. 5/-



Versatile Service VVM
Kit K/IM-18U £16.14.0
Carr. 5/-



Severn AM/FM Radio
Kit K/Severn £18.18.0
Carr. 5/-



Car Tune-up Meter
Kit K/ID-29 £17.8.0
Carr. 5/-



Model Builders Tacho
Kit K/GD-69
£11.0.0
Carr. Paid



D.I.Y. 2-Speaker System
Kit K/SCM-3 (less cab)
£12.6.0
Carr. 6/-

Many more kits in the FREE CATALOGUE

Please send me FREE Catalogue.

NAME

ADDRESS

..... Post Code

51/7



DAYSTROM LTD.
GLOUCESTER GL2-6EE

HOME RADIO (Components) Ltd.,
Dept. PW., 234 London Road, Mitcham CR4 3HD.
Phone 01-648 8422.



A Purchase a Home Radio Catalogue, using the Coupon below. Please enclose a cheque or postal order for 12/6 (8/6 plus 4/- packing & postage). Your catalogue will be sent by return of post.

B Choose your components. In the Home Radio Catalogue over 8,000 components are listed and more than 1,500 illustrated. A comprehensive index helps you to locate your requirements easily.

C Join our Credit Account Service. Full details are enclosed with every catalogue.

D Order your components. Having joined our Credit Account Service, you may order either by phone or post. If you phone out of office hours, a recording machine takes your message.

E Get started on that project! Whether it's constructing or servicing work, the fact that you can obtain the right components easily, without having to chase from shop to shop, will put you in the right frame of mind to make a better job of it.



Whether or not you want to use the Credit Account Service mentioned above, you certainly need the Home Radio Components Catalogue, if you construct or repair radio, television and electronic gadgets. By the way, the catalogue contains six vouchers, each worth a shilling when used as instructed, and with the catalogue we supply a 30-page Price Supplement and a Bookmark giving electronic abbreviations.

Post the Coupon today, with 12/6

The price of 12/6 applies only to catalogues purchased by customers residing in the U.K.

Please write your Name and Address in block capitals

Name

Address



HOME RADIO (Components) LTD.,
Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD

A LIGHT



Operated SWITCH

R. COLLINS

THIS unit will switch itself on automatically when light is dim and switch itself off again when light level increases. It is controlled by the varying amount of light falling upon an ORP12 light dependent resistor, (L.D.R.).

The ORP12 is a cadmium sulphide photoconductive cell and its resistance in bright light is between 75 and 300Ω and in complete darkness is greater than 10MΩ.

Care should be taken that the leads are not bent too close to the seal and heat conducted to the seal should be kept to the absolute minimum. The unit to be discussed contains a light-sensing element and an electronic switch using a "Schmitt Trigger" circuit.

THE SCHMITT TRIGGER

An example of the circuitry involved is shown in Fig. 1. Two transistors are employed with a common emitter load—resistor R4. Transistor Tr1 uses base bias network R1 and R3 which have their values selected to ensure that Tr1 is normally biased off. R5 and R6 comprise the base bias network for Tr2.

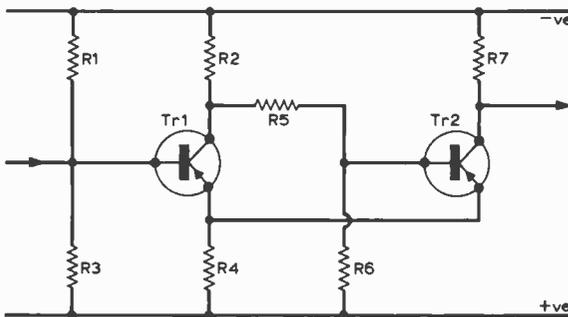


Fig. 1: Circuitry of a Schmitt Trigger.

Since Tr1 is normally off, its collector is near the full potential of the negative rail and Tr2 is biased on by a suitable choice of base bias resistor network.

Should a negative-going input signal be fed to the base of Tr1 and this signal be of sufficient magnitude to cause the transistor to begin to conduct, its collector will then become less negative, reducing the bias of Tr2 and so reducing its emitter current. This then results in positive feedback via the common emitter resistor R4 which increases the emitter current of Tr1 even further.

Cumulative action then takes place, switching Tr1 and Tr2 off. Should the input signal be removed, the circuit returns to its original state.

PRACTICAL APPLICATION

The circuit shown in Fig. 2 has an extra transistor added—Tr3—which carries the current to control the bulb used in the prototype. The voltage at the collector of Tr2 rises and this in turn raises the voltage on the base of Tr3 thus switching it on and causing current to flow through LP1.

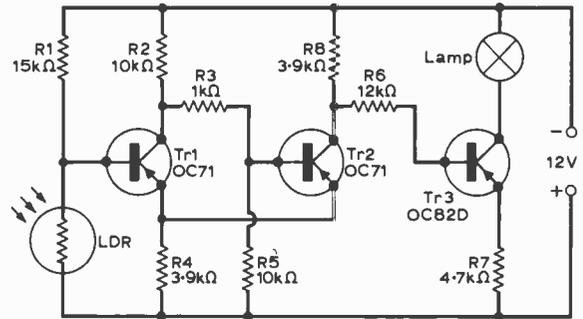


Fig. 2: The light-operated switch

Transistor Tr3 must be mounted on a heatsink so that it does not overheat and thus maintains its thermal stability. As it should not be made to pass a high current continuously thermal runaway is unlikely to occur.

ASSEMBLING THE UNIT

The circuit is assembled on a piece of Veroboard measuring 1½ × 1½ in. The layout and wiring of the components being shown in Fig. 3. The ORP12 cell is mounted so that it protrudes over an edge of the Veroboard and when the unit is mounted in a small

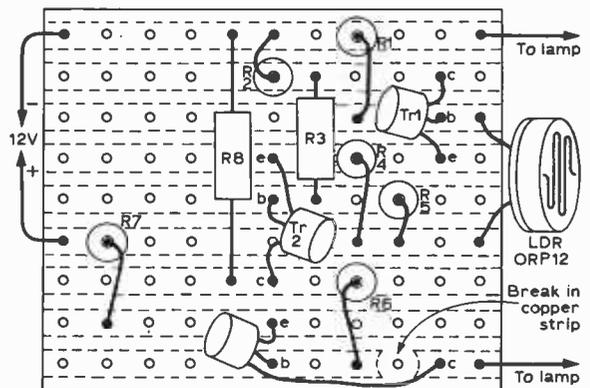


Fig. 3: Veroboard wiring and component layout.

plastic case, the cell can be mounted close to the plastic so that it can pick up the light easily (see photograph).

If it is decided to build the unit in a clear plastic case such as that illustrated, the case may be sealed with glue and so eliminate all possibility of dust and damp getting at the "works."

The mounting bolt for the Veroboard also acts as part of the heatsink for transistor Tr3 and is passed through the Veroboard and locked with a nut. A space of about $\frac{1}{2}$ in. is left, then another nut is fitted. The heatsink is then slipped over the shaft of the bolt and secured with another nut. A washer is then used, the bolt passed through the plastic case and finally secured with another washer and nut. If too much of the bolt is left protruding, it may be cut off.

★ components list

Resistors:

LDR	ORP12	
R1	15k Ω	
R2	10k Ω	
R3	1k Ω	
R4	3.9k Ω	All 20% $\frac{1}{2}$ W
R5	10k Ω	
R6	12k Ω	
R7	4.7k Ω	
R8	3.9k Ω	

Transistors:

Tr1	OC71
Tr2	OC71
Tr3	OC82D

Miscellaneous:

LP1, (6V 0.06A), heat sink for Tr3, 12V supply.

The reason the author did not insert this bolt from the outside of the case was that care must be taken to see that no nuts or washers short out the Veroboard strips and as a small-headed bolt was being used, it was thought advisable to mount it in the manner described.

The same care that one would exercise when soldering transistors (use of heat shunt, etc.) should be shown when soldering the ORP12 into the circuit.

USES


This versatile circuit may be employed in a number of applications. It may be used as an automobile parking light which will switch itself on automatically at dusk and switch itself off in the morning. As mentioned above, it should not pass a high current during the day time so that thermal runaway is unlikely to occur.

It is however very important that the completed unit when used in a vehicle should not be mounted near the engine which when warm may possibly affect the efficient working of the transistors.

Should the unit be built in a plastic box as described, a rubber sucker pad should be fixed so that the device may be mounted on either the inside of the windscreen of the car or on a flat metal surface inside. Some constructors may wish to glue a small bar magnet to the case in order that the unit may be attached to a metal part of the car.

The ORP12 should, when the unit is mounted in the vehicle, be placed in a shielded position, facing downwards and to the inside of the car. If this is not done, street lighting or the headlamps of other vehicles may make the device switch off the parking light!

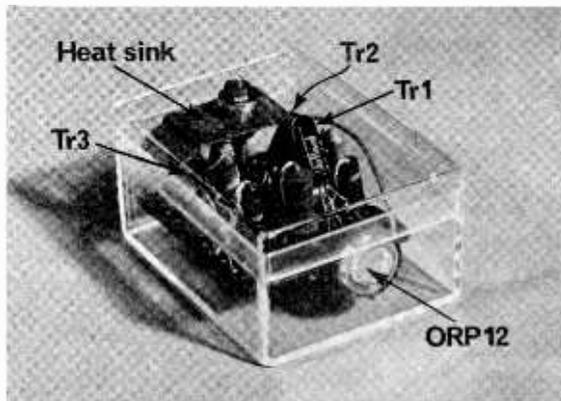It may be necessary to carry out a few experiments to find the best place to locate the automatic parking light to make sure that the light operates at the desired level of illumination.



Constructors should purchase one of the non-automatic parking lights that are available from garages and chain stores and which are designed to be clipped on to the side window of the car and which will, when illuminated, show a white light to the front and a red light to the rear.

It is possible that constructors building this unit may not be mobile and in this case other applications can be found. It may be used with a relay in the place of the bulb and used with a porch-light so that when it gets dark the unit will trigger the relay and switch on the light. ■

Take 20—continued from page 203

EXPERIMENTATION

The value of C3 should be chosen so that the tracking of VC2 gives the best possible results over the band. It will also be found to vary with aerial length and if an earth is used. VC2 and C3 can be replaced by a separate control and various types can be tried; where this is done R3 should be made 2.2k Ω and VR3 omitted.


Since the coil should cost virtually nothing to wind there is plenty of room for experiment in this direction.

Also try varying R2 by replacing it with a 500k Ω pot. with 47k Ω in series.


The value of C1 also bears experimenting with and the optimum value may well be less than 20pF depending on aerial characteristics. Other transistors can also be tried but some will be found to be unsatisfactory in that it will be hard to control the regeneration—this was found especially with the BC109. The f_t of the transistor should be at least 50MHz for satisfactory operation.

It is not an easy matter to add an amplifier to this set—though of course it can be done, since the amplifier could affect the operation of this very simple circuit. In the near future I will deal with this by describing a suitable amplifier in this series. ■

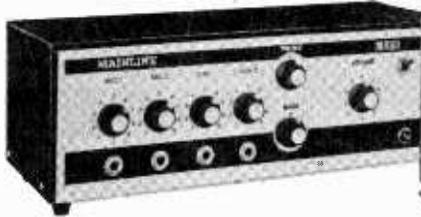Mainline set the NEW standard in amplifiers



Mainline 70ABD £64.0.0.

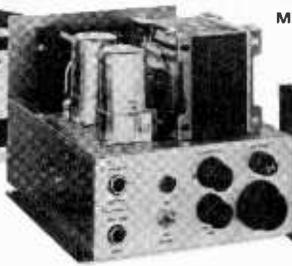

Mainline 70AB power amplifier £35.0.0.



Mainline Pre-4 mixer pre-amp control unit £24.0.0.

Mainline 70ABD

The 70ABD is a fully integrated Pre-amplifier and Power Amplifier to the specifications of the Pre-4 and 70AB. Size 6½" × 15½" × 4½".
Recommended Retail Price £64.0.0.

Mainline 70AB power amplifier

The MAINLINE 70AB is a high fidelity power amplifier, which is in every respect one of the finest units available on the market today, regardless of price. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit, and we can guarantee that it is virtually indestructible. Allied to this is the very high power output (70 watts RMS) a frequency range that is superb, and distortion well below 1% even at full output. The unit is suitable for use in discotheques, groups, P.A., etc., or anywhere that high quality, high output is required. Coupled to our Pre-4 Control Unit the results are quite remarkable. The Mainline 70AB main amplifier can be used with any other good quality control unit.

Specification

POWER OUTPUT 70 watts RMS ±1 db at 8 OHMS.
FREQUENCY RESPONSE 20-20,000 HZ ±1 db.
SIGNAL/NOISE RATIO—70 db at full output.
HARMONIC DISTORTION less than 5% at full output.

INPUT SENSITIVITY 700 mV at 20-30 K OHMS.
SIZE 7" × 9" × 6½".
A.C. FUSE 1.5 amps (British Standard).

Recommended Retail Price £35.0.0.

Mainline Pre-4 mixer pre-amp control unit

The MAINLINE Pre-4 is a high quality control unit, which has been designed specifically for use where mixing facilities are essential, and features many facilities not normally found on control units of this type.

The unit has four individual inputs each with its own gain control, plus separate bass, treble and master volume controls, for versatility in use. Inputs 3 and 4 are duplicated on the back panel so that if the unit is panel mounted the two auxiliary inputs (which are suitable for P.U. Tuners, Tape-recorders, etc.) may be connected from the rear. As the Pre-4 is self-powered it can be used with any other Power Amplifier, but has been designed basically as the control unit for our MAINLINE 70AB Amplifier Module.

Specification

INPUTS VOL. 1 8 mV at 50K OHMS (mic).
VOL. 2 8 mV at 50K OHMS (mic).
VOL. 3 50 mV at 500K OHMS (aux).
VOL. 4 50 mV at 500K OHMS (aux).
50 OHM and 600 OHM Mic inputs may be ordered at £2.0.0. extra per input.
1 or 2 meg OHM aux inputs may be ordered at no extra cost.
FREQUENCY RESPONSE 30-20,000 HZ ±3 db.

SIGNAL/NOISE RATIO Better than -65 db.
HARMONIC DISTORTION Less than 5% at 1 volt.
BASS Continuously variable 20 db at 100 HZ.
TREBLE Continuously variable 30 db at 10 KHZ.
SIZE 12½" × 6" × 4½".
CUT OUT REQUIRED 11½" × 5".
FUSE 60 ma internally mounted.

Recommended Retail Price £24.0.0.



5 stops you paying through the nose for your components

You could be paying too much for your semiconductors and electronic components. One sure way of saving money is to buy RCA, IR, SGS, Emihus, Semitron, Keyswitch, Plessey, Morganite, Litesold devices (together with manufacturers' application data) direct from us.

For example :-
PLESSEY SL403A

As described in *Practical Electronics*



Integrated Circuit (Dual in Line Package) Audio Amplifier incorporating its own Pre-Amplifier. A Class A-B Power Amplifier stage capable of delivering up to 3.5 Watts RMS. The SL403A can be used to form the basis of a simple Audio Amplifier using a minimum of external components. Complete with Data Sheet. 44/- each.

Build the NEW Mainline Audio Amplifier Kits - up to 70 watts



The results of the combined resources of SGS and RCA, these Universal Quasi Complementary Symmetry Amplifier kits use rugged NPN Hometaxial base output transistors and provide full power to beyond 20 KHz.

The all silicon circuit with nine transistors and eleven diodes provides outstanding performance for the most stringent requirements of Hi-fi equipment manufacturers.

Each kit is supplied complete with all semiconductors, resistors, capacitors, P.C. board and heat sink.

12A £7. 0. 0.

25A £8. 5. 0.

40A £9. 0. 0.

70A £10. 10. 0.

Any two will make an outstanding stereo equipment.

To: **MAINLINE ELECTRONICS LIMITED,**
THAMES AVENUE, WINDSOR, BERKSHIRE.

Please send me Mainline Pre-4 mixer pre-amps control unit(s)

Please send me Mainline 70AB power amplifier(s)

Please send me Mainline 70ABD integrated pre-amp and power amplifier(s)

I am interested in Amp Mainline Audio Amplifier kits.

Please send me kits Please send further data

Please send me your price-list guide. I enclose 5/-

Cash or cheques with orders please.

I would like further data on pre-amplifier and power supply kits before I order.

Name _____

Address _____


A member of the ECS Group of Companies

PW 7/70

MONO TRANSISTOR AMPLIFIER

HSL.700

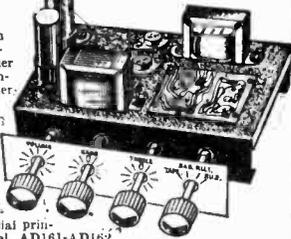A really high fidelity monaural amplifier with performance characteristics to suit the most discriminating listener.



6 transistor circuit with integrated pre-amplifier assembled on special printed sub panel. AD161-AD162 operating in symmetrical complementary pair. Output transformer coupled to 3 ohm and 15 ohm speaker sockets. Standard phone input sockets. Full wave bridge rectifier power supply for AC mains 200-240v. Controls: Bass, Treble, Volume/on/off. Function selector for P.U1, P.U2, Tape, Radio. The HSL.700 is strongly constructed on rigid steel chassis bronze hammer enamel finish. Size 9 1/2 x 5 1/4 in. high.

SENSITIVITY: P.U1-50mV, 50k input impedance. P.U2-110mV, 1 meg input impedance. Tap-110mV, 1 meg input impedance. Radio-110mV, 1 meg input impedance. Output power measured at 1Kc-6.2 watts RMS into 3 ohms. 5.8 watts RMS into 15 ohm. Overall frequency response 30 c/s-18 Kc/s: Continuously variable tone controls: Bass, +8dB, 10-12dB at 100c/s. Treble, +4-10dB to -10dB at 10Kc/s. The HSL.700 has been designed for true high fidelity reproduction from Radio Tuner, Gramophone deck and Tape Recorder preamp. Supplied ready built and tested, complete with knobs, attractive anodised aluminium front escutcheon panel, long spindles (can be cut to suit your housing requirements), full circuit diagram and operating instructions.

Our Special Price **£7.19.6** P & P 7/6

LOUDSPEAKER BARGAINS

5in. 3 ohm 14", P. & P. 3/-. 7 x 4in. 3 ohm 21", P. & P. 4/-. 10 x 6in. 3 ohm 27/8, P. & P. 6/-. E.M.I. 8 x 5in. 3 ohm with high flux magnet 26/-, P. & P. 4/-. E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet 42/- (15 ohm 45/-), P. & P. 6/-. E.M.I. 13 x 8in. 3 or 15 ohm with two built in tweeters and crossover network 4 5s. P. & P. 6/-.
BRAND NEW 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly **£5.10.0**. P. & P. 7/6. Guitars models: 25w. **£6.0.0**, 35w. **£8.0.0**.
 E.M.I. 3 1/2in. **HEAVY DUTY TWEETERS**. Powerful ceramic magnet. Available in 3 or 8 ohms 18/- each. 15 ohms 18/8 each. P. & P. 2/6.
 12in. "RA" **TWIN CONE LOUDSPEAKER**. 10 watts peak handling, 3 or 15 ohm 37/8, P. & P. 6/-.
35 OHM SPEAKERS
 3 1/2in. 14/-, P. & P. 2/6. 7 x 4in. 21/-, P. & P. 4/-.

VYNAR AND REZINE SPEAKER AND CABINET FABRICS. Approx. 1/4in. wide. Usually 35/- per yard. **OUR PRICE 15/-** per yard length. P. & P. 2/6 (min. one yd.). S.A.E. for samples.

BALANCED ARMATURE EARPHONE
 Approx 70 ohm impedance. Can be used as ultra sensitive mike or speaker. **ONLY 3/6**. P. & P. 1/6.
CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity, 18/8, P. & P. 1/6.
HIGH IMPEDANCE CRYSTAL STICK MIKES. **OUR PRICE 2/1-**, P. & P. 1/6.
HIGH IMPEDANCE DYNAMIC STICK MIKES. High sensitivity, 30/6, P. & P. 2/6.

HONEYWELL MICROSWITCHES. S/P. C/O. Push button action. Rating 250v. AC at 15 amps. Size approx. 1 1/2 x 7/8 x 3/8 in. P. & P. 1/- (or more post free).

SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG. 400pF + 148pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 k/c 1.F. Size approx. 2 x 1 x 1 1/2. **Only 8/6**. P. & P. 2/6.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 12 section Heavy Chrome. Extends from 7in. to approx. 56in. Maximum diameter 1in. 10/- each. P. & P. 1/6. 6 section Lacquered Brass. Extends from 6in. to 22 1/2in. approx. Maximum diameter 3/4 in. 5/- each. P. & P. 1/-.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Gives 13 alternatives. Primary: 0-21-240v. Secondary combinations 0-10-15-20-25-30-35-40-60v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price 32/6, P. & P. 6/-.
MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500mA. 11/-, P. & P. 2/6. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 14/6, P. & P. 2/6. Pri. 200/240v. Sec. 10-0-10 at 2 amp. 27/6, P. & P. 3/6. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 12/6, P. & P. 2/6.

BATTERY CHARGER TRANSFORMERS. 200/240v. input. Nominal output for 6 or 12v. batteries 3 amps. Size approx. 3" x 2 1/2" x 2 1/2". Brand New. Price 21/-, P. & P. 6/-.
HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4in. FIVE for 10/-, P. & P. 2/-.

SPECIAL OFFER ! !

Your opportunity to acquire a first class HI-FI LOUDSPEAKER SYSTEM at an extremely moderate price!
 Beautifully made teak finish enclosure with most attractive Tygan-Uynair front. Size 16 1/2" high x 10 1/2" wide x 8" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 15 ohm impedance.

OUR PRICE WHILE LIMITED STOCKS LAST **8 Gns.** Carriage 10/-

TRANSISTOR STEREO 8 + 8 MK II

Now using Silicon Transistors in first five stages on each channel resulting in even lower noise level with improved sensitivity. A really first-class HI-FI Stereo Amplifier Kit. Uses 14 transistors giving 8 watts push pull output per channel (16W. mono). Integrated pre-amp with Bass, Treble and Volume controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 3 to 15 ohms. Compact design, all parts supplied including drilled metal work, Cr-Kit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Pre. response $\pm 3dB$. 20-20,000 c/s. Bass boost approx. to $\pm 12dB$. Treble cut approx. to $-18dB$. Negative feedback 14dB over main amp. Power requirements 25V at 8 amp.
PRICES: AMPLIFIER KIT £10.10.0; POWER PACK KIT £3.0.0; CABINET £8.0.0. All Post Free.
 Also available STEREO 10 + 10. As above but 10 watts per channel. **PRICES: AMPLIFIER KIT £12; POWER PACK KIT £5.10.0.**
 Circuit diagram, construction details and parts list (free with kit) 1/6 (S.A.E.).

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. Can be operated from 9-18v. battery supply or direct from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 17/8, P. & P. 2/6.



SPECIAL PURCHASE!
E.M.I. 4-SPEED PLAYER
 Heavy 8 1/2in. metal turntable. Low flutter performance 200/250v. shaded motor (90v. tap). Complete with latest type lightweight pick-up arm and mono cartridge with t/o stylus for LP/78. **ONLY 63/-**. P. & P. 6/6.

QUALITY RECORD PLAYER AMPLIFIER MK II
 A top quality record player amplifier employing heavy duty double wound main transformer, EC83, EL84, E280 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 8in. high. Ready built and tested. **PRICE 75/-**. P. & P. 6/-.
ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. **PRICE 97/8**. P. & P. 7/6.

DELUXE QUALITY PORTABLE R/P CABINET MK II
 Uncut motor board size 14 1/2 x 12in. clearance 2in. below. 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE 79/8**. P. & P. 9/6.




3-VALVE AUDIO AMPLIFIER HA34 MK II
 Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis size 7 1/2" x 4 1/2" x 4 1/2". Incorporates EC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc. wired and tested for only **£4.15.0**. P. & P. 6/-.
HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/8, P. & P. 6/-.

HARVERSON'S SUPER MONO AMPLIFIER

A superb quality gram amplifier using a double wound mains transformer, E280 rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with valves and good quality output transformer. **FEW ONLY**.
OUR ROCK BOTTOM BARGAIN PRICE **55/-** P. & P. 6/-

DE LUXE STEREO AMPLIFIER

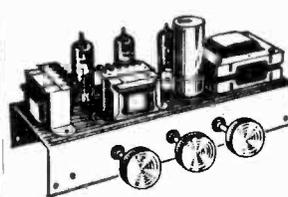


A.C. mains 200-240 v. U.S. 110 v. heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum.

Valve line up—2 x ECL86 Triode Pentodes, 1 x E280 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono) into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. **PRICE 8 gns. P. & P. 8/-**.


4-SPEED RECORD PLAYER BARGAINS
 Mains models. All brand new in maker's packing. **SPECIAL OFFER! Famous GARRARD 3500** offered Sonotone 9TAN Diamond Stereo Cartridge. List price over £16. Limited Number at **£10**. Carr. 8/6.
LATEST B.S.R. C109/21 4-SPEED AUTOCHANGER. With latest mono compatible cartridge **£6.19.8**. Carr. 6/6. With stereo cartridge **£7.19.8**. Carr. 6/6.
LATEST GARRARD MODELS. All types available 1925, 2025, SP25, 3000, AT60 etc. Send S.A.E. for latest PRICE LIST WITH CUTS out for Garrard Models, 1925, 2025, 2000, 3000, AT60, SP25. With transparent plastic cover. **OUR PRICE 5 gns.** complete. P. & P. 8/6.

LATEST ACOS GP91/180 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. 30/-, P. & P. 1/6.
SONOTONE 2539 High output Stereo Cartridge. T/O stylus for Stereo/LP/78. Complete with universal mounting bracket. List Price 48/7.
OUR PRICE 26/-. P. & P. 1/6.
SONOTONE STERIC compatible Stereo Cartridge with diamond stylus 50/-, P. & P. 2/-.
LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. 32/6, P. & P. 2/-.
LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. **Only 30/-**. P. & P. 2/-.

HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI
 ● Peak output in excess of 11 watts.
 ● All standard British components.
 ● Built on printed circuit board 5 x 3in.
 ● Generous size Driver and Output Transformers.
 ● Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (GET114 or 81 Mullard AC128D) and matched pair of AC128 o/p). ● 9 volt operation. ● Everything supplied, wire, battery clips, solder, etc. ● Comprehensive advice to follow instructions & circuit diagram 2/8 (Free with Kit). All parts sold separately. **SPECIAL PRICE 45/-**. P. & P. 3/-.
 Also ready built and tested, 52/8, P. & P. 3/-.

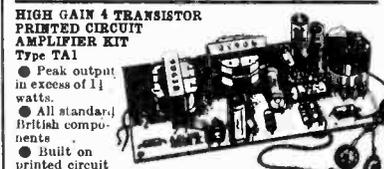

10 1/2 WATT HI-FI AMPLIFIER KIT
 A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EC83, E280 and E280 rectifier. Simple instruction booklet 2/8 (Free with parts). All parts sold separately. **ONLY 27.9.6**. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, **£9.5.0**. P. & P. 8/6.

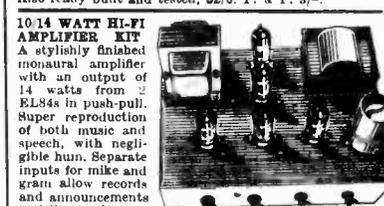

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 15/-, V15/Op 10/-; OC71 6/-; OC78 2/8 (Free with parts). All parts sold separately. **ONLY 27.9.6**. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, **£9.5.0**. P. & P. 8/6.

Open all day Saturday
 Early closing Wed. 1 p.m.
 A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.
 170 HIGH ST., MERTON, LONDON, S.W.19
 Tel.: 01-540 3985
 SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)
 PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Mains Colours

Mr. Baigent of High Wycombe is one of many people who condemn the new mains-lead colours, merely because they are used to the old colour code.

I welcome the new colours as I can now wire up apparatus without any danger of wrong connections. This has proved difficult in the past since I cannot distinguish red from green and some rubber insulation left both these colours looking very black.

Any change that eliminates the need to reorganise colour is, in my opinion, a change for the better.—**J. Gallacher** (*Motherwell*).

Discarded material boxes!

As a YL radio amateur, since 1936, may I point out that I have had radio junk boxes since 1924, and, although obviously no longer a *young* lady, still have several. Also I have the usual "clobber" that women acquire through the years—cotton reels—(some empty—they make good door stops) cotton reels with varying amounts of cotton, and sylko etc., pieces of material, wool (well I may want to repair that old pullover one day) needles, pins, scissors, tape measure and so on.

The only real difference is that women do not call it junk! My dictionary says that "junk" is "discarded material". It does not say that it is unusable—there is untold treasure in them there boxes, so please all of you, respect each other; I know which I prefer! Oh, by the way XYLs (wives), never attempt to dust "radio junk", it might shock you!—**Constance Hall, G8LY** (*Lee on the Solent, Hants*).

A reader comments

I was particularly interested in Mr. Jobe's comments on sound from transistors (Letters, Feb. 1970). I also have come across this effect.

I constructed a phase shift oscillator using computer transistors and I found that when the oscillator was set to around 6kHz, one of the transistors merrily squeaked at 6kHz. I believe this may be due to the Peizo Electric effect.—**P. Everett** (*Hull*).

A cheaper way

I would like to comment on H. C. Bennet-Clark's article on the repair of loudspeaker cones. For loudspeakers with minor cuts and holes etc. it is rather expensive to pay between 12s. 7d. and 14s. 9d. for such a small job, so I bought myself a packet of tissue handkerchiefs and a tube of thin glue.

The method I employed was: apply a thin coat of glue to the speaker cone and to the tissue. Place the tissue on the cone and apply a little pressure. Leave this to dry then if required, add another layer of tissue and glue.—**Jim Mahoney**, (*South Ockendon, Essex*).

The printed circuit

I feel I must point out that in my humble opinion, the term "printed circuit" is in many cases misused. A printed circuit board is one that has components actually etched out on its surface during manufacture, whereas a printed wiring board has components mounted on to a sheet and connected by copper strips.—**M. L. Clayton**, (*R.A.F. Gutersloh, B.F.P.O. 47*).

XYL's unite

I cannot agree with F. G. Sadler, G3UZ, in his article "Home and Dry", February issue of Practical Wireless. Not every XYL conforms to the nagging, dense, insensitive creature he portrays.

The radio shack in our house is in a recess in the kitchen. It measures 6ft. x 4ft. x 12ft. high, and is filled from top to bottom. From where I am sitting, I can see my husband bent over his workbench (an old dining-table). On his left is a 7ft. high shelving-unit crammed with various wireless sets in various stages of construction, or destruction, boxes of transistors, diodes, condensers, valves, etc., etc., etc. A small panel of sockets faces him, ready to connect any of the umpteen cables that festoon the shack. On his right are some small shelves holding tools and meters—at least that is what they are supposed to hold. At the moment, I can see a speaker, screwdrivers of various sizes and a tangled mass of spare cable. Above all this is a loft, used for storing larger spares, such as whole

wireless sets and cases which might come in useful for that thingummy he intends building when he can afford it.

If a howl of anguish or a heart-felt cuss-word issues from the shack, I know that my husband has reached for the soldering-bolt, while keeping his attention on a very delicate joint, and has found it sooner than he expected. But I don't let it worry me. If the bit breaks when he drops it, I'll allow him to buy another.

At the front of the shack, edging out into the kitchen, sits a hulking great B40 receiver. I was with my husband when he bought it, and have even learned what all the knobs, switches and dials are for. What's more, I enjoy it!

I must be one of the very few XYLs who are allowed to enter the Holy of Holies without protest. When I clean the bench I follow a very simple rule: Lift the article, dust under it, then replace it exactly as it was before. After all, there just might be an important reason for an expensive meter to be sitting right on the point of balance at the edge of the bench. When it comes to cleaning the floor I have another rule: Sweep round the larger objects, gather up the smaller ones which obviously have been dropped, then brush up everything else. Carefully sort through the dust, pieces of wire and cigarette ends, picking out the minute components, crocodile clips, screws, etc. Place all salvaged parts on a saucer and leave on a clear space (she must be joking) on the bench.

I do not, as Henry's wife seems to do, file magazines according to the colour of the cover. I bung them all in one ruddy great pile, sorted neither by name nor by date, and let him hunt happily, secure in the knowledge that it must be there, whatever it is.

As I write this, my spouse is almost strangling himself in a cable which loops from back to front of the shack, with a graceful but dangerous curl in the middle.

Perhaps I had better rescue him. Or would that be construed as interference?—**Morag Greer** (*Glasgow, W.4*).

NEXT MONTH IN

PRACTICAL WIRELESS

MODULAR 3 BAND S.W. RECEIVER

The beginner will appreciate this simple design for a short wave receiver covering 15 to 230 metres. The basic receiver will give good results using headphones but the extra audio amplifier on a separate module can be easily incorporated to provide loudspeaker reception.

ELECTRONIC METRONOME

A handful of components, quickly assembled, build up into this highly accurate Electronic Metronome. Giving sharp beats at a rate varying from 0.25 to 4 second intervals, this project has a wide variety of uses in hobbies ranging from music to photography.

VERSATILE 5/50 HAM-BAND TRANSMITTER

This transmitter will operate at 50 watts input on the five major amateur bands, from 10 to 80 metres. The main feature is instant bandswitching with a minimum of retuning between bands. A good solid design ensures success by any constructor.

PLUS THE REGULAR "TAKE 20" AND "I.C. OF THE MONTH" FEATURES AND OTHER CONSTRUCTIONAL ARTICLES AND FEATURES

Don't miss your copy of the August issue of Practical Wireless —on sale 10th July—price 3s. 6d.

Voltage Stabilisation—continued from page 207

several points of difference emerge. First, the series transistor is easily damaged if the output is shorted, and commercial stabilisers use elaborate protection circuits. Secondly, all the amplifying transistors require a current drive to the base, and the zener diode and voltage divider circuits must be able to supply this current.

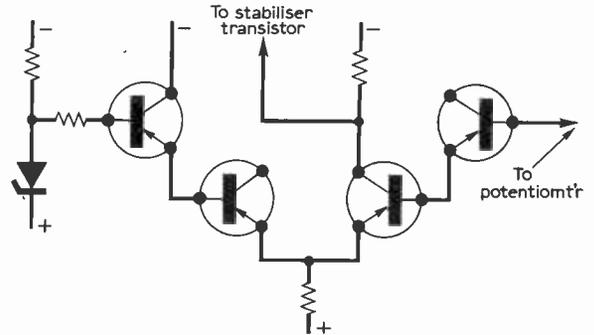


Fig. 11: Compounded circuit using semi-conductors

Thirdly, long-tailed pair circuits are usually compounded (Fig. 11) so that the final circuit can supply sufficient current drive to the power transistor used as the series stage.

More Advanced Methods

Many modern stabilised power supplies use a "prestabiliser" stage. This stage consists of a band of thyristors in place of the rectifiers of the conventional power pack and controlled from a source of stable voltage (gas or zener), so that the voltage output of the rectifiers is already stabilised against load variation and this can be done better when the conflicting requirements of main stabilisation are not required (as we have seen, good load current stability requires a low impedance output, good mains voltage stability requires a high impedance series valve).

The circuit of Fig. 10 is also found greatly elaborated with a valve or transistor used in place of the cathode resistor of the long-tailed pair, compounded long-tailed pairs, multiple series controllers, additional stages of amplification, etc. ■

BLUEPRINT SERVICE

We would like to draw readers' attention to the fact that the BLUEPRINT SERVICE has been discontinued and therefore no further BLUEPRINTS are available.


QUERY COUPON

This coupon is available until 10th July 1970 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, JULY 1970

DISCOSOUND

DJ DISCO-AMP

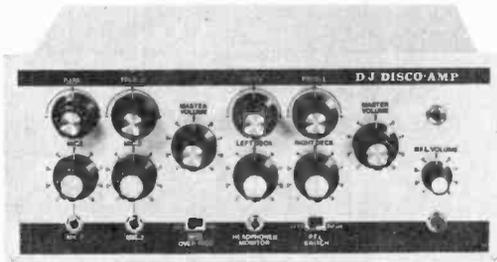

The DJ Disco-amp has been designed specifically for use with discotheques and has many exclusive features not normally found on P.A. amplifiers. The unit will be of use to the professional D.J. as well as in clubs and mobile discotheques.

The pre-amp section features independent inputs and volume controls for two mics with separate bass, treble and master volume, plus two independent inputs and volume controls for turntables, again with separate bass, treble and master volume controls.

A complete Pre-fade listen (P.F.L.) cueing monitor section is also featured with separate input for headphones (either stereo or mono) with an independent volume control for headphone monitoring, and a P.F.L. switch, so that either turntable can be monitored for accurate cueing up of records. A mic over-ride switch is also added which cuts the music volume by half so that mic announcements may be made over the music without altering the volume controls.

The power amplifier section has an output of 70 watts R.M.S. into 8 ohms and has elaborate protection against thermal, short or open circuit. The unit is designed for panel mounting.

SPECIFICATION


Output power	70 watts R.M.S. \pm 1db at 8 ohms.
Frequency response	30-20,000 Hz \pm 3 db.
Harmonic distortion	Less than 1% at full output.
Signal/noise ratio	Better than - 65db.
Speaker impedance	8-16 ohms.
Headphone impedance	8-16 ohms.
Bass control	Variable 20 db at 100 Hz.
Treble control	Variable 20db at 10 kHz.
Inputs:	Mic 1 & 2 5 mV at 50 K ohms.
turntable	1 & 2 100mV at 1 meg ohm.

50 ohm or 600 ohm mic inputs may be ordered at extra cost.
Size: Front Panel 16 $\frac{1}{2}$ " x 7". Cut out 15 $\frac{1}{2}$ " x 6". Fuses: A.C. 1.5 amp (B.S.) mounted on back panel.

PRICE £85.0.0 inc. P & P.

DISCOSOUND PRE-4


This is a four channel fully mixable pre-amp, with separate treble, bass and master volume controls, and is completely self powered. All four inputs are by standard jack socket on the front panel with the addition of inputs 3 and 4 being duplicated on the back panel, with two paralleled outputs also featured for versatility in use. Frequency response: 30-20,000 Hz \pm 3db. Signal/Noise Ratio: -65db. Size: front panel 12 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " cut out required 11 $\frac{1}{2}$ " x 4". Completely built and tested.

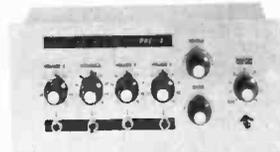

PRICE £18.0.0 inc. P & P.


DJ 30L PSYCHEDELIC LIGHT CONTROL UNIT

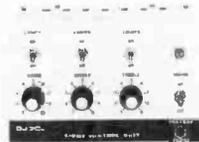3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation. Completely built and tested



PRICE £37.10.0 inc. P & P.

DJ 70S INTEGRATED MIXER-AMPLIFIER

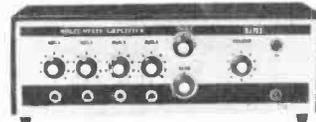

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70 watts R.M.S.) a frequency response (30-20,000 Hz \pm 3db) that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs etc., or anywhere that high quality high output is required. Size: 15 $\frac{1}{2}$ " x 5in x 6in.

PRICE £55.0.0 inc. P & P.

Also available DJ105S 30 watt P.A. Amplifier. Similar specification to above.

PRICE £35.0.0 inc. P & P.

DISCOSOUND 70 MAIN AMPLIFIER

A 70 watts RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response: 20-20,000 Hz \pm 2db. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound PRE-4, or can be used with any other high quality pre-amp control unit. Size: 7" x 9" x 6". Completely built and tested on steel Chassis.

PRICE £30.0.0 inc. P & P.

For full details of these and all Discosound Products write direct to:—

DISCOSOUND, 122 BALLS POND ROAD, LONDON, N.1. Tel: 01-254 5779

Full money back guarantee if returned within 10 days.
All Discosound Products are guaranteed for 12 months.
Demonstrations given at any time.

FULLY TESTED AND MARKED

AC1267	3/-	OC170	2/-
AC1268	2/6	OC171	4/-
AC127	3/6	OC200	3/6
AC128	2/6	OC201	2/6
AC176	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF114	4/-	2N1302-3	4/-
AF116	3/6	2N1304-5	4/-
AF116	3/6	2N1306-7	4/-
AF116	3/6	2N1308-9	4/-
AF259	12/6	2N3819 FET.	9/-
AF186	10/-	2N3844A	5/-
AF139	10/-	Power Transistors	
BFY60	4/-	OC20	18/-
BSY25	2/-	OC23	10/-
BSY28	3/-	OC25	5/-
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	7/6
BSY95A	3/-	OC35	5/-
OC4	2/6	OC36	7/6
OC44	2/6	AD149	10/-
OC45	2/6	AU7 10	10/-
OC7	2/6	2N3055	15/-
OC72	2/6	28034	10/-
OC73	3/6	Diodes	
OC8	2/6	AA542	2/-
OC81D	2/6	OA91	2/-
OC81	4/-	OA79	1/6
OC139	2/6	OA91	1/6
OC140	3/6	IN914	1/6

NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits. Date and Circuits of types, supplied with orders.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
B82	10	OC45, OC81D and OC81 Trans Mullard glass type.	10/-
B83	200	Trans. Makers rejects. NPN/PNP. Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
B86	150	High quality Germ Diodes. Min. glass type.	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types.	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN, PNP, equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B80	10	7 Watt Zener Diodes. Mixed voltages.	10/-
H5	16	1 Amp. Plastic Diodes, 50-1,000 Volts. 6 large, 10 small.	10/-
H6	40	250mW. Zener Diode DO-7 min. Glass Type. AV.40% Good.	10/-

NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries .3 to .5 volt, .5 to 2 ma.	10/-
H8	4	BY127 Silicon Recs. 1000 P.I.V. 1 amp. Plastic.	10/-
B79	4	1N4007 Sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Plastic.	10/-
B81	10	Reed Switches, mixed types, large and small.	10/-
B89	2	5SP5 Light Sensitive Cells. Light Rec. 400 Ω Dark 1M Ω	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45.	10/-
B92	4	NPN. Sil. Trans. A06 B8X20 2N2369 500 MHz, 360mW.	10/-
B93	5	GET113 Trans. equiv. to ACY17 to ACY21 PNP Germ.	10/-
B96	5	2N3136 PNP Sil Trans. TO-18, HFE 100-300 I.C. 600mA. 200MHz.	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NK271, etc.	10/-
B99	200	Capacitors, Electrolytics, paper, silver mica, etc. Post and packing, this Pak 2/6.	10/-
H4	250	Mixed Resistors, Post and packing 2/-.	10/-
H7	40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-

FREE! Packs of your own choice up to the value of 10/- with orders over £4.

RETURN OF THE UNBEATABLE P.I. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels, identification chart supplied to give some information on the transistors.

PI PLEASE ASK FOR PAK P.I. ONLY 10/-
2/- P. & P. on this Pak

Complimentary Set, NPN/PNP Germ. Trans., Pak F.3. **2/6 PAIR**

P.O. RELAYS 8 FOR
Various Contacts and Coil Resistances. Post & Packaging 5/- **20/-**

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CARD.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order OVERSEAS AND EXTRA FOR AIR MAIL.

Fully guaranteed Individually packed VALVES


CY31	7/-	EF36	3/6	OB2	6/-	OA5	2/6	OC29	15/-	OC172	7/6	3FR5	6/6	AF118	10/-	CRS3/20	10/6	6P25	11/-	19AQ5	7/9	5933	22/6
DAF96	7/6	EF37A	7/6	PAB080	7/6	OA10	6/-	OC35	8/6	OC200	6/6	3N128	17/6	AF139	10/-	CRS3/30	11/6	68A7	7/6	19G3	7/6	6057	10/6
DF96	7/6	EF39	6/-	PC97	9/6	OA70	2/-	OC38	8/6	OC201	7/6	3N139	35/-	AF178	12/6	CRS25/025	15/-	68ATGT	6/6	19G6	2/6	6060	7/6
DK96	7/6	EF40	10/6	PC900	9/6	OA71	2/-	OC44	4/6	OC206	10/6	3N140	19/6	AFY19	22/6	15/-	68C7	13/6	19H4	8/6	6064	7/6	
DL92	6/6	EF41	12/6	PC834	6/6	OA79	1/6	OC45	2/6	IN21	3/6	3N154	19/6	ABY26	5/6	CRS3/40	12/6	68CTGT	5/6	20P4	17/6	6065	13/6
DL94	6/6	EF80	5/6	PC889	9/6	OA81	1/6	OC70	3/6	IN21B	5/6	3N159	29/6	ABY28	5/6	GET103	4/6	68G7	6/6	25L6GT	7/3	6080	27/6
DM70	6/6	EF83	9/7	PC189	11/6	OA200	1/6	OC71	2/6	IN23	2/6	IN235	29/6	BAW19	5/6	GET115	5/6	68J7	6/6	30C15	15/6	6146	28/6
DM71	7/6	EF86	6/6	PC890	15/6	OA210	7/6	OC72	4/6	IN43	4/6	12FR60	14/6	BC107	3/6	GET118	8/6	68J7GT	6/6	30C17	16/6	8020	35/6
DY86	6/6	EF86	6/6	PC890	15/6	OA211	9/6	OC75	4/6	IN702-72573	23303	10/6	BCY10	9/6	BD928	6/6	68K7	7/6	30C18	15/6	9001	3/6	
DY87	6/6	EF89	5/6	PC892	9/6	OA220	11/6	OC76	5/6	IN746A	40694	27/6	BCY72	7/9	BD948	6/6	68L7GT	6/6	30F11	15/6	9003	10/6	
DY802	9/6	EF91	3/6	PCF84	9/6	OA220	11/6	OC81	4/6	series	5/3	40696	27/6	BFY61	4/6	BD968	7/3	68M7GT	6/6	30FL12	18/6	9004	2/6
E88CC/01	27/-	EF95	5/6	PCF200	15/6	OA220	10/6	OC82	3/6	IN821A	21/6	40636	20/6	BFY92	4/6	BD988	9/3	68Q7GT	7/9	30FL13	9/3	9006	2/6
EABC80	6/6	EF183	6/6	PCF201	15/6	OA220	10/6	OC82	3/6	IN824	28/6	40668	27/6	B805	7/6	V405A	7/6	68V6G	3/6	30FL14	15/6		
EAF42	10/6	EF184	7/6	PCF801	9/6	OA220	10/6	OC82DM	3/6	1ZMT10	6/9	AC126	4/6	B82	9/3	Zener Diodes		68V6GT	6/3	30L15	17/6	C.R. Tubes	
EB91	2/-	EF800	20/6	PCF802	9/6	OA221	10/6	OC83	4/6	1ZT5	13/6	AC128	4/6	BU100	36/6	3/6 ea.		63X4	4/6	30L17	17/6	VCR97	32/6
EB33	5/-	EF812	15/6	PCF805	14/6	OA223	10/6	OC83B	3/6	1ZT10	12/6	AC129	6/6	BY213	5/6	22A range		63X6	5/6	30P12	16/6	VCR517	50/6
EC041	10/6	EF1200	15/6	PCF806	13/6	OC16	15/6	OC16	15/6	OC12	10/6	2N1307	6/6	AC176	7/6	BY216	15/6	63X6GT	6/6	30P19	14/6	VCR517B55/-	
ECB01	6/6	EL34	10/6	PCF808	14/6	OC22	8/6	OC22	8/6	OC139	6/6	2N3053	6/6	AD149	11/6	CRS1/20	9/6	6760	11/6	30PL1	13/6	VCR517C45/-	
EBF80	7/6	EL41	11/6	PC1200	14/6	OC25	7/6	OC25	7/6	OC140	8/6	2N3064	12/6	AD161	7/6	CRS1/30	10/6	63012	14/6	30PL14	17/6	5CP77	28/6
EBF83	6/6	EL42	10/6	PC181	9/6	OC26	5/6	OC26	5/6	OC170	5/6	2N3055	15/6	AD162	7/6	CRS1/35	11/6	6761	7/6	35W4	5/6	88J	180/6
EBF89	6/6	EL84	4/6	PC182	7/6	OC28	8/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	705	14/6	35Z4T	9/6	88L	90/6
EC082	5/6	EL86	8/6	PC184	8/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	706	6/6	42	7/6		
EC083	5/6	EL90	6/6	PC185	9/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
EC084	6/6	EL95	7/6	PC186	9/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
EC085	7/6	EL90	17/6	PC1200	14/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
EC086	7/6	EL90	17/6	PC1200	14/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
EC189	6/9	EM31	6/6	PL81	8/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECF80	6/6	EM80	7/6	PL82	8/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECF82	6/6	EM84	7/6	PL83	7/3	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECF83	15/6	EM87	11/6	PL84	6/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECF801	12/6	EY61	8/6	PL500	14/9	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECF802	12/6	EY81	7/6	PL504	10/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECH35	11/6	EX106	8/6	PL509	9/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECHE42	13/6	EY88	8/6	PL514	14/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECHE18	5/9	EZ41	8/6	PX25	30/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECHE83	6/8	EZ80	5/6	PY33	12/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECHE84	7/6	EZ81	5/6	PY80	6/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECHE200	12/6	GZ34	10/6	PY81	5/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECLE80	9/6	KT86	27/6	PY82	6/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECLE82	6/6	KT88	33/6	PY83	8/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECLE83	10/6	N78	25/6	PY88	7/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	
ECLE86	8/6	OA2	6/6	PY80C	9/6	OC28	8/6	OC171	6/6	F100	12/6	AF117	4/9	CRS1/40	12/6	CRS3/05	6/6	717	5/6	60C5	7/6	Photo Tubes	

Open 9-12.30, 1.30-5.30 p.m. Thursday

GOING BACK...



COLIN RICHES
ARTHUR DOW

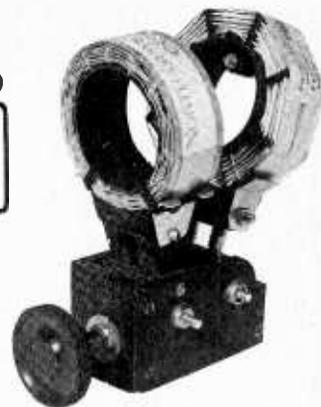

FOLLOWING his editorial, "The Vintage Years" in P.W. for May, another avalanche of letters descended on the Editor strengthening his conviction, if strengthening was needed, that P.W. should run a regular feature dealing with the early days of radio communication, or should we say "wireless"!

This is the first of that series and it is hoped that it will be possible to fill a much wanted need. We shall be including reviews of some of the equipment and of the experiments that were carried out in those early pioneering days. We shall not be forgetting contemporary stories and anecdotes some of which were incredibly prophetic!

How better to start this series than with a photograph of the 'father' of communication by wireless? But was Marconi really the first?



Marconi

1874-1937

Let's hear some comments on this point, circa 1923 . . . "Lord Riddell attributes it to Clerk-Maxwell but Marconi himself holds that James Bowman Lindsay, who sent a message across the river Tay without wires about 1840, was the inventor"!!

However, Clerk Maxwell's work was purely theoretical but it did point towards the possibility of communication by means of electromagnetic waves, his theory being published in 1864. It was Heinrich Hertz, in 1888, who proved the theory to be correct with his experiments with spark coils and resonators.

While early experimenters were able to detect radiation at short distances from spark discharges it is not so easy to decide who was responsible for putting the effect to good use as a means of communication.

It was Marconi, who, in 1901, demonstrated that electromagnetic waves could be detected well beyond the short visual ranges that had been obtained up to that time.

Utilising several tuned circuits in the transmitter at Poldhu, Cornwall, and in the receiver in Newfoundland, as outlined in the famous patent No. 7777 dated 1900, he was able to span the Atlantic by wireless for the first time.


Radiograms

"Will the aluminium chassis eventually entirely supersede the wooden baseboard which has held the field for so many years?? The aluminium chassis undoubtedly makes a neater and more workmanlike job but for sheer simplicity and quickness of assembly the baseboard scores every time" (October 1932)

. . . looking at the modern version of the base board we seem to have got back to the point from whence we started!

"The word selected by the *Daily News* as the prizewinner of their competition to suggest an alternative word to 'listener-in' was 'broadcatcher'. Other words suggested were radiolist, auditor, harker and Noah, the last being because they 'Ark!!! . . . no comment!' (February 1923).

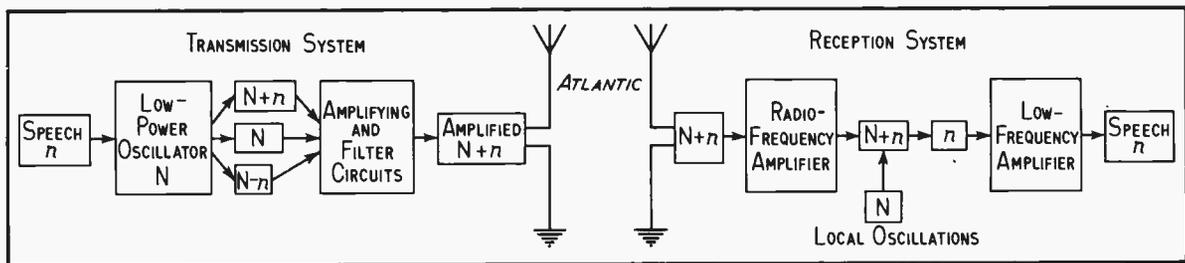"An improved amplifier is claimed to have been invented which will amplify the tone of the wireless voice, but not its imperfections" (March 1923) . . . we're still waiting!!



... SO WHAT'S NEW?

"The daily Press has recently reported on the successful transmission of speech from America to the British Isles. The achievement is the more remarkable in view of the fact that the transmission originated in a New York office which was connected to the wireless transmitting apparatus by an ordinary telephone line. At the time of writing no technical details have been published other than the fact that the transmission was accomplished on one 'side band', no carrier being used" (March 1923). *An excellent description of the system was given (see block diagram) . . . sooooo!! SSB is not so new-fangled after all!*

READERS COMMENT

...I still enjoy the "magic" of listening on a crystal set (*C. R. Gunn, Liverpool*).

... My first licence was obtained in 1921 (*Alfred Reeve, G & WN, Southampton*).

... It is almost fifty years since I acquired my first wireless magazine (*James Foye, Cornwall*).

... There is no doubt that the Twenties period was the heyday of radio experimentation (*E. J. Walker, Kent*).

... My—to me—priceless leftovers of that era are two books published in 1928 (*G. Valentin, Dundee*).

... The first radio broadcast I heard was in 1922

when I was allowed into a London pub for a few moments to listen to 2LO broadcasting from Savoy Hill (*P. W. Ellis, Hull*).

... In 1923 I acquired a double-barrelled crystal detector. The theory was that a crystal grabbed half a wave so that two crystals would get the lot with twice the volume (*R. A. Ball, Scotland*).

... One of my own favourite recollections is of a design published in the '30s of a 2-valve battery short-wave set (*J. W. Davidson, Co. Durham*).

... In the 1920-1930s radio was thrilling, exciting and wonderful (*C. Butler, Co. Durham*).

... I have a book of 1930 vintage. It is full of outdated methods and ideas but it is very interesting to be able to learn how radio was tackled in those days (*N. Taylor Suffolk*).

... I have been a reader for 40 years and have many fond memories of the early days (*J. W. Geoghegan, Wigan*).

... I am interested in the days when amateurs had to construct even the most basic of components (*P. J. Wardle, A6953, Co. Durham*).

... I would greatly appreciate reprints of early articles. They would bring back memories of the exciting past when radio was just really "growing up" (*G. J. Turnbull, C. Eng., M.I.E.E. Edinburgh*).

Vintage Radio Society

A final note . . . don't forget the Editor's offer to provide publicity for any efforts to form a Vintage Radio Society.

HYBRID MODULATOR

—continued from page 196

Now in carrier control systems, the peak carrier voltage is fixed by the h.t. supply and is approximately equal to it. So when the P.A. is loaded up, we in fact adjust the load resistance R such that the maximum P.A. anode current drops the whole of the h.t. across the tank circuit. When we subsequently reduce the P.A. anode current by half, then the voltage across the tank circuit will fall to half h.t. and the power produced to quarter peak power.

From the previous paragraph, two conclusions can be drawn. Firstly, as half P.A. current drops half h.t. across the tank circuit when correctly adjusted, it is obviously possible to re-adjust the effective load resistance to drop the whole h.t. and increase the output power as before mentioned. Secondly, the rating of the modulated carrier is only one-quarter of the maximum the P.A. can produce. For example, on top band, to produce a 10 watt modulated carrier, the P.A. must be capable of producing 40 watts of carrier on initial setting up! Anyone familiar with s.s.b. and linear amplifiers will realise that the same power considera-

tions pertain. Just one final point about power output. Knowing the P.A. h.t. volts, one is used to looking at the P.A. anode current and quoting the mean P.A. power as the product. In this case, once carrier control is in operation the mean power is half the product of the h.t. and the anode current.

CONSTRUCTION

Since little power is dissipated in Tr5, the whole modulator can be built on Veroboard. If the P.A. valve employed has a low mutual conductance or runs with a mean current above 50mA when adjusted for modulation, the BFY51 will need to be replaced by a transistor capable of greater collector dissipation. A BD123 type should cope with almost any conceivable P.A. stage if mounted on a suitable heat sink.

One worthwhile check on the speech amplifier after construction is Tr3 d.c. collector voltage, which should be between 2V and 3V positive with respect to the common rail.

As crystal microphones vary greatly in their output, should the amplifier be found to be short of gain, R11 may be reduced until adequate gain is available. ■

TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Total Building Costs

£6.19.6

Parts Price List and Easy Build Plans 5/- (FREE with parts).

P & P 7/6.



roamer seven mkIV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Five Section 22in. chrome plated telescopic aerial for Short Waves—can be angled and rotated for peak S.W. listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.




Total building costs
£5.19.6

P & P 7/6

NEW! trans eight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and cream knobs and dial with polished brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.

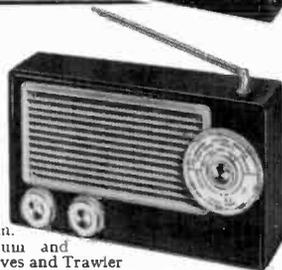


Total building costs **89'6**

P & P 5/6

pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

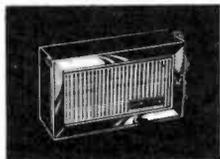Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
44'6

P. & P. 3/6

transona five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER AND EARPIECE

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stage—5 transistors and 3 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker also Personal Earpiece with switched socket for private listening. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs
47'6

P. & P. 3/9

roamer six

SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7½ x 5½ x 1½in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts).



Total building costs
79'6

P. & P. 4/6

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT ROAMER SEVEN
TRANSONA FIVE TRANS EIGHT
POCKET FIVE ROAMER SIX

Parts price list and plans for

Name

Address

PW49

* Callers side entrance Stylo Shoe Shop

* Open 10-1, 2.30-4.30 Mon-Fri. 9-12 Sat

Build working radio receivers and electronic circuits in an evening



Beginner or advanced student— you learn fast with Radionic kits

Circuits work first time with the Radionic 'no soldering' method. With the X30 kit, build 33 experiments: a printed circuit transistor radio, burglar alarm, morse code buzzer etc. The more advanced kits are suitable for G.C.E., City and Guilds, National Certificate and higher. Every set includes construction notes and all circuit diagrams. It's so easy for you to build *and* learn because you construct circuits that resemble the theoretical diagram. Re-use components easily, too — they're screw-in-mounted. *Send off this coupon today.*

TO: RADIONIC PRODUCTS LTD.,
St. Lawrence House, Broad Street, Bristol BS1 2HF

Please send me full details of all Radionic Kits please send me one Radionic Kit X30, for which I enclose £7 19s. 6d. (delete where inapplicable)

Name _____

Address _____



VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED

SETS 1R5, 1B5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 1R/8, DAF96, DF 96, DK96, DL96, 4 FOR 27/-.

0Z4	4/8	19BG6G17/8	DK92	8/8	EH90	6/3	PCL82	7/3	UBC41	9/-	
1A7GT	7/8	20P2	13/8	DK96	7/8	EL33	9/9	PCL83	12/-	UBF80	6/9
1HSGT	7/8	20P3	11/8	DL36	6/-	EL34	9/6	PCL84	7/8	UBF89	6/9
1NSGT	7/9	20P4	18/8	DL92	5/9	EL38	17/6	PCL85	9/-	UCB84	7/-
1R5	5/9	25LGT	5/-	DL94	6/3	EL41	11/-	PCL86	8/3	UCB85	7/3
1B5	4/3	25U4GT11/8	DL96	7/3	EL84	4/9	PENA4	12/8	UCF80	7/3	
1T4	2/9	30C1	6/6	DY86	5/9	EL90	4/6	PF120011/9	UCH42	12/6	
3B4	8/9	30C15	13/-	DY87	5/9	EL500	12/8	PL36	9/9	UCH81	6/6
3V4	6/3	30C17	16/-	EAB80	6/6	EM80	8/8	PL81	8/9	UCL82	7/-
5Y3GT	5/9	30C18	14/-	EAF42	10/-	EM81	8/6	PL8A	10/6	UCL83	11/9
5Z4G	7/6	30F5	16/-	EB91	2/3	EM84	6/9	PL82	6/6	UF41	10/6
6J30L2	12/-	30FL1	12/9	EBC33	8/-	EM87	7/8	PL83	6/6	UF85	6/9
6AL5	2/3	30FL12	14/6	EBC41	9/6	EY61	7/3	PL84	6/6	UF89	6/9
6AM6	2/9	30FL14	14/9	EBF80	6/9	EY86	6/6	PL500	13/-	UL41	12/-
6AQ6	4/6	30L1	6/6	EBF89	6/9	EZ40	8/-	PL504	13/8	UL44	20/-
6AT6	4/-	30L15	13/-	ECC81	3/9	EZ41	8/-	PL505	23/8	UL84	7/-
6AU6	4/6	30L17	15/6	ECC82	4/9	EZ80	4/6	PL584	7/8	UM84	6/6
6BA6	4/6	30P4	12/-	ECC83	7/-	EZ81	4/9	PX25	12/-	UY41	7/6
6BE6	4/9	30P12	13/9	ECC85	5/-	GZ39	8/9	PY32	10/-	UY85	5/9
6BJ6	8/6	30P19	12/8	ECC91	3/6	GZ34	9/9	PY33	10/-	VP48	10/-
6C6G	4/9	30PL1	14/9	ECC80	12/-	KT61	9/9	PY81	5/3	W77	3/6
6F13	3/6	30PL3	17/6	ECC80	6/6	KT66	16/9	PY82	5/3	W119	7/-
6F14	9/-	30PL4	16/6	ECC82	6/6	N78	17/6	PY93	5/9	Z77	2/9
6F23	14/3	35LGT	8/9	ECH35	6/-	PABC80	7/-	PY88	6/9	Transistors	
6F26	13/-	35W4	4/6	ECH42	13/6	PC86	10/3	PY800	7/6	AC107	3/6
6J5G	4/9	35Z4GT	5/-	ECH81	5/9	PC88	10/3	PY801	7/6	AC127	2/6
6J6	3/6	6083	12/6	ECH83	3/3	PC96	8/6	R19	6/6	AD140	7/6
6K7G	2/6	807	9/-	ECH84	7/6	PC97	8/6	R20	12/6	AF115	3/6
6K9G	2/9	AC/VP210/-		ECL90	7/-	PC900	7/8	TH21C	17/6	AF116	3/6
6L18	6/-	AZ31	9/6	ECL82	6/9	PC854	6/6	T26	13/-	AF117	4/6
6N7GT	4/3	B729	12/6	ECL83	3/6	PCC85	6/-	U26	12/-	AF125	3/6
6V6G	3/3	CCH36	13/6	ECL86	5/-	PCC88	9/-	U47	13/6	AF127	3/6
6V6GT	6/6	CL33	18/6	EF37A	6/6	PCC89	10/6	U49	13/6	OC26	5/-
6X4	4/3	CY31	6/9	EF39	4/9	PCX189	11/6	U78	4/3	OC44	2/6
6X5GT	5/9	DAC32	7/3	EF41	11/8	PCF80	6/6	U91	12/6	OC45	2/6
10F1	14/-	DAF91	4/3	EF80	4/6	PCF82	6/6	U93	8/6	OC71	2/6
10F18	7/-	DAF96	7/3	EF85	6/3	PCF86	10/6	U281	14/6	OC72	2/6
10P13	12/-	DF33	7/9	EF86	6/3	PCF80	18/6	U301	10/6	OC75	2/6
12AT7	3/9	DF91	2/9	EF89	5/3	PCF81	6/9	U329	14/6	OC81	2/6
12AU6	4/9	DF96	7/3	EF91	2/9	PCF802	9/-	U801	19/6	OC81D	3/6
12AV7	4/3	DF77	4/-	EP94	4/6	PCF805	14/-	UABC80	6/6	OC82	2/6
12AX7	4/9	DK32	7/6	EF183	5/9	PCF86	12/9	UAF42	10/3	OC82D	2/6
12K8GT	7/3	DK91	5/9	EF184	6/8	PCF808	14/6	UB41	6/6	OC170	4/6

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX.

Tel. 01-550 7441.

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

YOUR CAREER IN RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fulllest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.


Please send FREE BROCHURE to

NAME _____ Block

ADDRESS _____ Caps.

Please
1/70

BRITISH NATIONAL RADIO SCHOOL

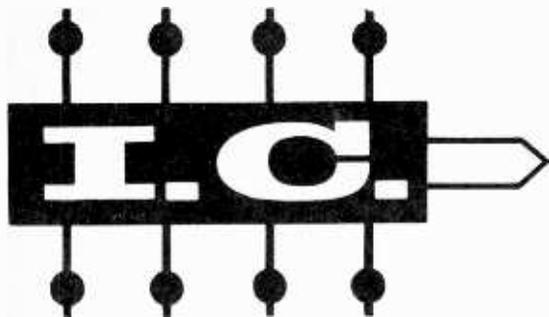

OF THE MONTH


L.A.J. IRELAND

Number 9

Mullard TAA310 Audio Preamplifier

IT is a prominent feature of the semiconductor scene at the present time that as areas of high demand are identified, integrated circuits specially designed to fill the need are quickly introduced. It is not that general purpose units will cease to find a market, as the discrete transistor is still commonly used, but as manufacturers build up experience, and i.c.s become accepted, response to demand becomes more rapid, and a smaller production run becomes economically feasible.

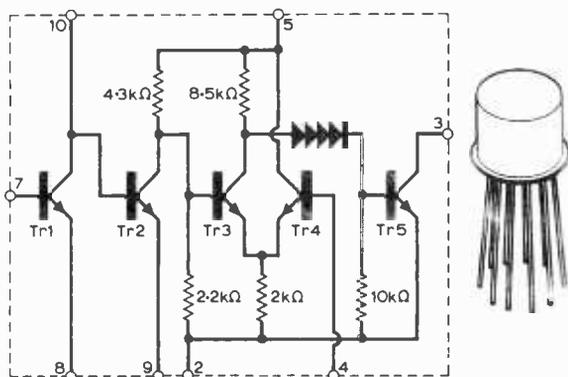One such device to be described this month is the Mullard type TAA310, a monolithic low noise audio preamplifier with specialised features for tape record-playback applications.




Circuit of TAA310 and package style.

Circuit

First, a brief look at the specification of the unit. In a TO-74 style ten pin package there is a five transistor, four stage, direct coupled amplifier, rated for the temperature range -20 to $+75^{\circ}\text{C}$., with a typical gain (open loop, i.e. without negative feedback) of 100 dB, and a noise figure of 4 dB on a 7 volt supply.

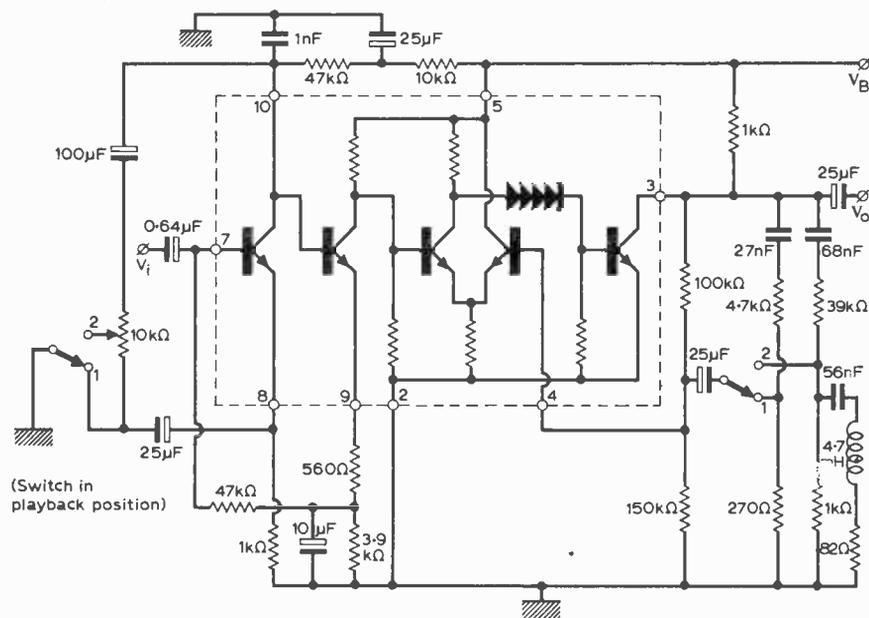In a practical circuit, the full open loop gain is not used; rather, use is made of the differential stage, comprising transistors Tr3 and Tr4, the third stage of the amplifier, to apply negative feedback. In a tape amplifier, the feedback loop is designed to have a frequency characteristic such that the ampli-




A practical circuit utilising the TAA310 integrated circuit package in a record playback configuration. A simple switch is all that is required to change the amplifier frequency response from that required for record to that for playback as shown on the separate graphs.

fier as a whole will have a performance in accordance with international tape standards without any additional tone or frequency selective networks.

As is evident from the diagram, only two poles of a two way switch are required to transfer from the characteristics for recording to those recommended for playback. (The switching between microphone or other signal source, and playback head, and between record head and power amplifier, are not included in the diagram as these are not strictly related to the application of the TAA310. They must, however, be remembered when designing the record/playback system as a whole).

A Practical Design

Now for a few points related to the operation of the unit. The input impedance of the circuit is typically 20 k Ω which should provide a satisfactory match for medium impedance microphones such as are commonly used for recording or p.a. work, and a signal level of 20mV is characteristic. It must be remembered that the circuit must also be a satisfactory match to the playback head of the tape deck with which it is used; there is a preset potentiometer (10 k Ω) in the input circuit in the record position only to compensate for any difference in the signal conditions.

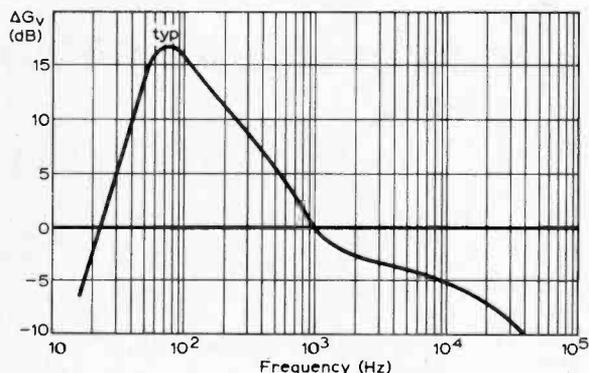


Frequency response curve of amplifier during playback.

The first two stages are conventional common emitter configurations, but note should be made of the method of biasing Tr1 from the emitter circuit of Tr2. Next is the differential stage, as already mentioned, with both a.c. and d.c. feedback from the output stage. Only the a.c. feedback requires special mention; it can be seen that the frequency response will be completely different depending on the setting of the record/playback switch.

In the record mode, high frequencies are emphasised, with low frequencies preferentially amplified in the playback configuration. The effective high-frequency cutoff of the tape preamp is 15 kHz. In the record mode the output from Tr5 is coupled through a capacitor to the recording head;

it may be noted that often the same head serves as record and playback head, with the erase function performed by a separate head or by a permanent magnet. (Somewhat different characteristics are required, e.g. a different "gap" in an erase head compared with those used for an audio signal).

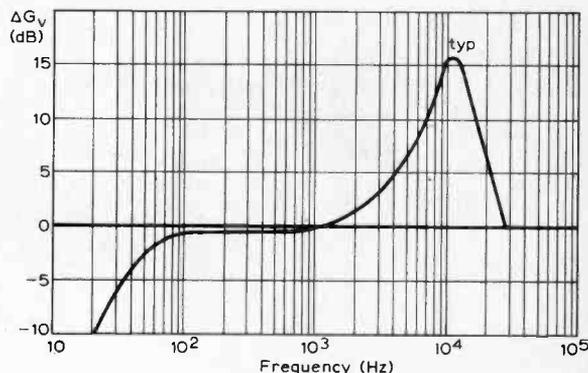It is also common practice to apply a small h.f. bias to the record head when transcribing material on to a tape. This is obtained from the erase oscillator, and of course will be inaudible during playback since it is at a frequency beyond those to which the ear responds, but it does result in a lower noise level on the tape by minimising permanent magnetisation of the poles.



Frequency response curve of amplifier during recording.


It can be applied through a small capacitor, say, 1000pF, from the erase oscillator coil. Should it be decided in the interests of simplicity to use permanent magnet erase, a d.c. bias in the recording head may be experimented with. Many small imported tape recorders use a bias current of 0.1 mA to achieve results only a little inferior to those from an h.f. system, and even without bias satisfactory reproduction may be expected.

The TAA310 should be available from any Mullard semiconductor supplier, or by post from Kinver Electronics Ltd., who advertise in this magazine.


One last item of news: Radiospares, who supply a wide range of electronic items to the retail market, are now distributing integrated circuits, notably an audio power amplifier with specifications identical to the SL402 described in these pages some time ago, and also a hybrid d.c. regulator operational up to 30 volts output. ■

NOTE TO RADIO CLUB SECRETARIES
If you would like to see your Club featured in PRACTICAL WIRELESS, drop a line to Colin R. Riches, IPC Magazines Ltd., Fleetway House, Farrington Street, London, E.C.4.

SINCLAIR IC-10

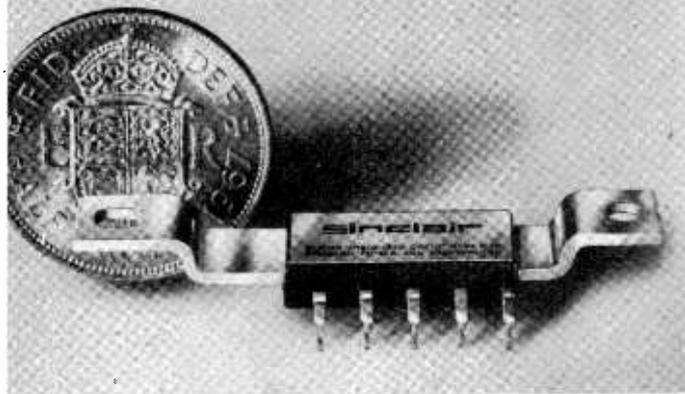

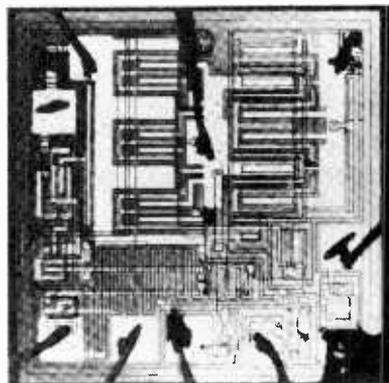MONOLITHIC INTEGRATED CIRCUIT HIGH FIDELITY AMPLIFIER AND PRE-AMP



the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output of 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 Zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required as part of the process of producing monolithic I.C.s are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. This enables us to cover every IC-10 with the Sinclair guarantee of reliability.

■ SPECIFICATIONS

Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz ± 1 dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5mV.
Input impedance	Adjustable externally up to 2.5 M ohms.

■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

SINCLAIR

IC.10 with *IC.10 manual* **59/6**

POST FREE

sinclair

SINCLAIR RADIONICS LIMITED
22 NEWMARKET ROAD · CAMBRIDGE
Telephone 0223 52731

Project 60

laboratory-standard high fidelity modules

Sinclair Project 60 comprises a range of modules which connect together simply to form a complete stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare in overall performance. Now with the addition of three new modules to the range, the constructor has choice of assemblies with either 20 or 40 watts output per channel, with or without filter facilities.

The modules are: 1. The Z-30 and Z-50 high gain power amplifiers, each of which is an immensely flexible unit in its own right. 2. The Stereo 60 pre-amplifier and control unit. 3. The Active Filter unit with both high and low audio frequency cut-offs. 4. The PZ-5 and PZ-6 power supplies. A complete system could comprise, for example, two Z-30's, one Stereo-60, and a PZ-5. The PZ-6 is stabilised and should be used where the highest possible continuous sine wave rating is required. An A.F.U. may be added as required. In a normal domestic application, there will be no significant difference between using a PZ-5 or PZ-6 unless loudspeakers of very low efficiency are being used, in which case the PZ-6 will be required. For assemblies using two Z-50's there is the

new PZ-8 stabilised supply unit to ensure maximum performance from these more powerful amplifiers.


All you need to assemble your Project 60 system is a screw-driver and soldering iron. No technical skill or knowledge whatsoever is required and, in the unlikely event of you hitting a problem, our customer service and advice department will put the matter right promptly and willingly. Project 60 modules have been carefully designed to fit into virtually all modern plinth or cabinets and only holes need be drilled into the wood of the plinth to mount the control unit and the A.F.U. Any slight slip here will be covered by the aluminium front panels of these two units.

The Project 60 manual gives all the building and operating instructions you can possibly want, clearly and concisely. Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future as the latest additions to the range show. A stereo F.M. tuner is next to come. These and all other modules we introduce will be compatible with those already available and may be added to your system at any time. And because Sinclair are the largest producers of constructor modules in Europe, Project 60 prices are remarkably low.

SINCLAIR RADIONICS LIMITED

22 NEWMARKET ROAD CAMBRIDGE

Telephone 0223 52731

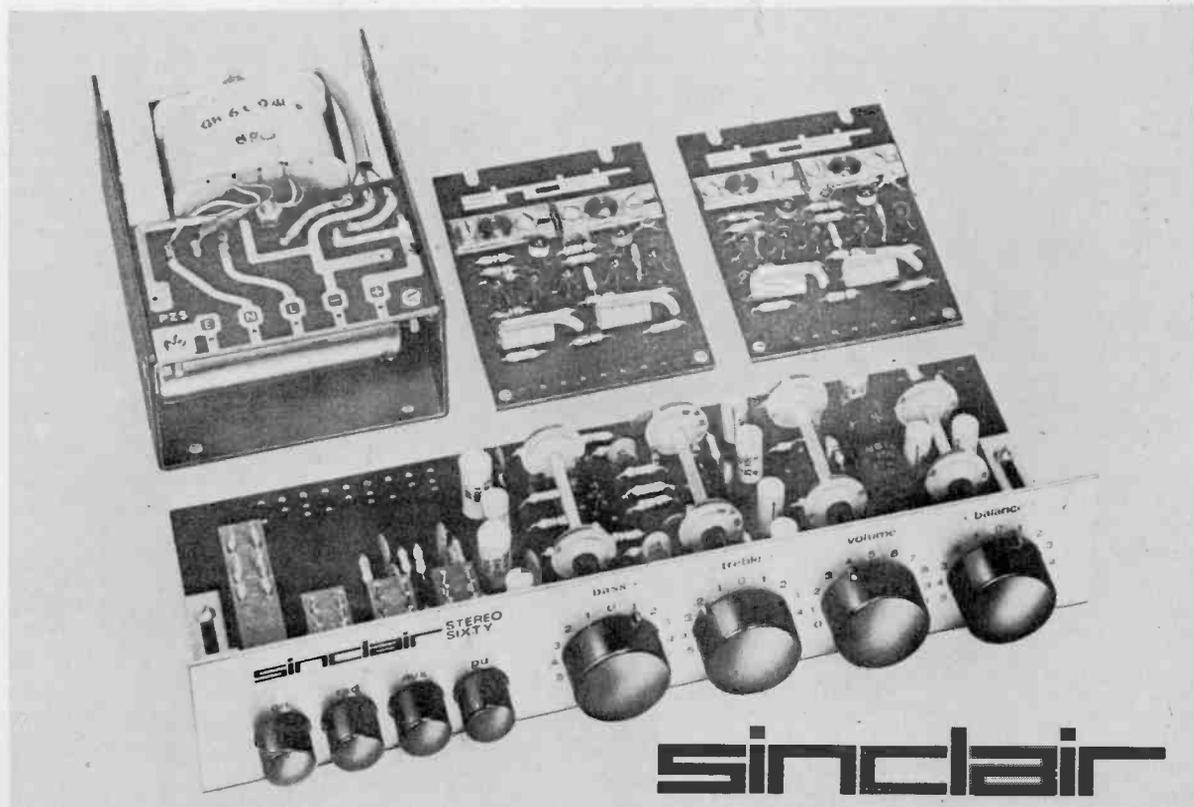

Z.30 20 WATT R.M.S. POWER AMPLIFIER (40 WATTS PEAK)

Z.50 40 WATT R.M.S. POWER AMPLIFIER (80 WATT PEAK)

The Z.30 together with the higher powered Z.50 are both of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use the Z.30 or Z.50 power amplifiers in your Project 60 system will depend on personal preference, but they are both the same physical size and may be used with other units in the Project 60 range equally well. The Z.30 is unique in that it may be used with any power source between 8 and 35 volts without need for adjustment and may thus be driven from a car battery for example. For operating from mains, for the Z.30 use PZ.5 power supply unit for most domestic requirements, or PZ.6 if you have very low efficiency loudspeakers. For Z.50, use the PZ.5, PZ.6 or the PZ.8 described below.

SPECIFICATIONS

The Z.50 is completely interchangeable with the Z.30 and can be used in all Z.30 applications

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms, using 35V; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms: 30 watts R.M.S. into 8 ohms, both continuous, using 50V.

Frequency response 30 to 300,000 Hz ± 1 dB

Distortion 0.02% into 8 ohms

Signal to noise ratio better than 70 dB unweighted


Input sensitivity 250mV into 100 Kohms

For speakers from 3 to 15 ohms impedance

Size 3½" x 2½" x ½"

APPLICATIONS

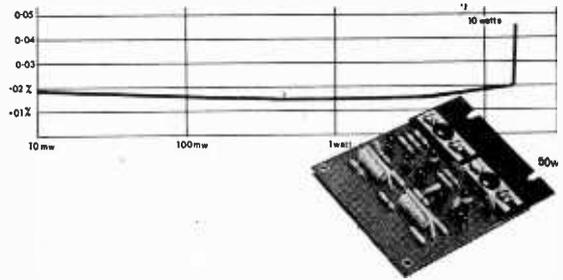Hi-fi amplifier; car radio amplifier; record player amplifier fed directly from pick-up; intercom; electronic music and instruments; P.A.; laboratory work etc. Full details for these and many other applications are given in the manual supplied with the Z.30.



Power versus distortion curve of Sinclair Z.30 and Z.50

Z.30 Built, tested and guaranteed with circuits and instructions **89/6**
Z.50 Built, tested and guaranteed with circuits and instructions **109/6**

STEREO 60 Pre-amp Control unit

The Stereo 60 is a stereo preamplifier and control unit designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout and great attention has been paid to achieving a really high signal-to-noise ratio and excellent tracking between the two channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs. The tone controls are also very carefully designed and tested.

- Input sensitivities—Radio—up to 3mV Mag. p.u.—3mV: correct to R.I.A.A. curve ± 1 dB: 20 to 25,000Hz. Ceramic p.u.—up to 3mV: Aux.—up to 3mV.
- Output—250mV
- Signal-to-noise ratio—better than 70 dB.

- Channel matching—within 1dB.
- Tone controls—TREBLE +15 to -15dB. at 10 kHz: BASS +15 to -15dB at 100Hz.
- Power consumption 5mA.
- Front panel—brushed aluminium with black knobs and controls.
- Size 8½ x 1½ x 4 ins.




Built, tested and guaranteed **£9.19.6**


ACTIVE FILTER UNIT High Pass and Low Pass

For use between Stereo 60 unit and to Z.30s or Z.50s, the Active Filter Unit matches the Stereo 60 in styling and is as easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible by reason of the careful design and generous negative feedback employed.

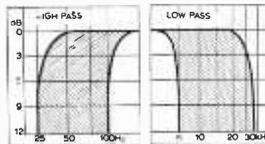Supply voltage—15 to 35V. Current—3mA
 H.F cut-off (-3dB) variable from 28kHz to 5kHz.
 L.F cut-off (-3dB) variable from 25Hz to 100Hz.
 Filter slope, both sections 12dB per octave
 Distortion at 1kHz (35V supply) 0.02% at rated output




SINCLAIR POWER SUPPLY UNITS

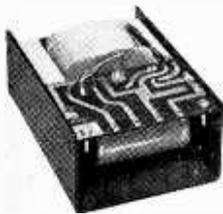

- PZ-5** 30 volts un stabilised **£4.19.6**
- PZ-6** 35 volts stabilised **£7.19.6**
- PZ-8** 45 volts stabilised **£5.19.6**
(less mains transformers)

GUARANTEE

If at any time within 3 months of purchasing Project 60 modules from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for services thereafter. No charge for postage by surface mail. Air-mail charged at cost.

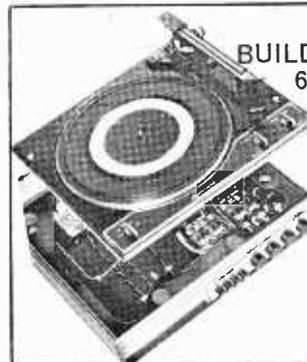

BUILDING A PROJECT 60 ASSEMBLY

The illustration here shows quite clearly how easily Project 60 can be contained in one of today's slim, modern plinths. Very little space is required to house these Sinclair units, and within the space of the motor plinth, you can install a stereo amplifier of the very highest quality. If, for example you have already put together an assembly as illustrated here, adding the Active Filter Unit would be very easy.

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE
 Please send

.....

NAME

ADDRESS

.....


For which I enclose cash/cheque/
 money order

PW 670

SINCLAIR Q.16

new elegance in an
outstanding loudspeaker

All the superb features which went to make the Sinclair Q.14 have been incorporated in the new Q.16 which gives an exciting new opportunity for you to match your Sinclair equipment with modern decor. Employing the same well proven acoustic system in which materials, processing and styling are used in such a radical and successful departure from conventional design, the new Q.16 presents an entirely new appearance with its attractive teak surround and all-over special cellular foam front chosen as much for its appearance as for its ability to pass all audio frequencies without loss. The Q.16 is compact and slim. Its new styling makes it eminently suitable for shelf mounting, but it is no less versatile than its famous predecessor. Listen to a pair of Q.16s in stereo and marvel at the standards of quality and clarity they give.

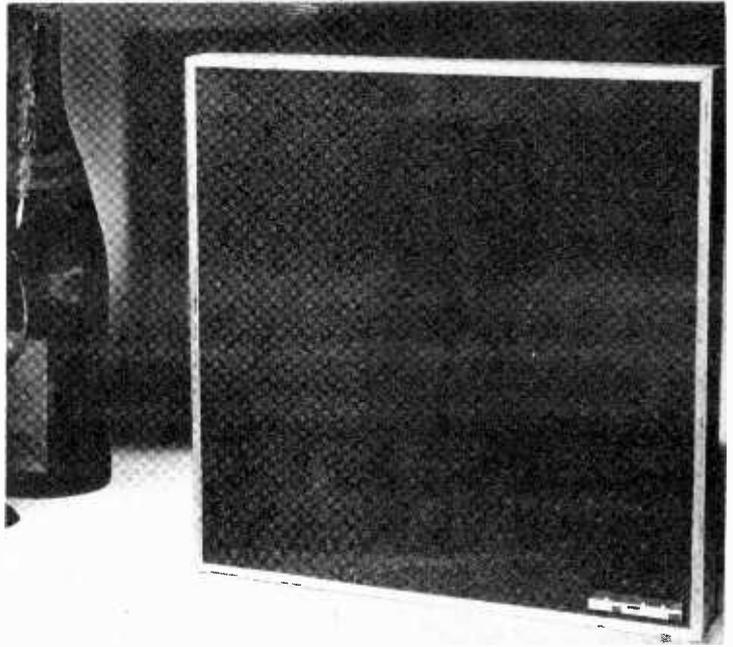

The Q.16 will handle loading up to 14 watts R.M.S. and presents an 8 ohm impedance to the amplifier output. Frequency response extends from 60 to 16,000Hz with exceptional smoothness. A specially designed driver system is used in a sealed and contoured pressure chamber to ensure good transient response at all frequencies. Size: 9½" square x 4½" deep from front to back.

£8.19.6

POST FREE

*The world's most
successful miniature
radio*

SINCLAIR MICROMATIC



SPECIFICATIONS—Size: 1 13/16" x 1 7/16" x 1/2" (46x33x13mm). Weight incl. batteries: 1 oz. (28.35gm) approx. Tuning: Medium wave band with bandspread at higher frequency end. Earpiece: Magnetic type. Case: Black plastic with anodized aluminium front panel, spun aluminium dial.

Complete kit incl. earpiece, case, solder and instructions in fitted pack. **49/6**

Ready built, tested and guaranteed, with earpiece. **59/6**

Mallory Mercury Cell RM675 (2 req.) 2/9 each

Considerably smaller than an ordinary box of matches, this is a multi-stage A.M. receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful A.G.C. is incorporated to counteract fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy at all times. Vernier type tuning plus the directional properties of the self-contained special ferrite rod aerial makes station separation much easier than with many larger sets. The plug-in magnetic earpiece which matches exactly with the output provides wonderful standards of reproduction. Everything including the batteries is contained within the attractively designed case. Whether you build your Micromatic or buy it ready built and tested, you will find it as easy to take with you as your wrist-watch, and dependable under the severest listening conditions.

SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

sinclair

SINCLAIR RADIONICS LIMITED

22 NEWMARKET ROAD, CAMBRIDGE

Tel: 0223 52731

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE
Please send

NAME

ADDRESS

.....

.....

.....

For which I enclose cash/cheque/
money order

PW 170

BAKER 12in. MAJOR £8



The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

Major Module 30-17,000 cps with tweeter, crossover, baffle £10.19.6
19" 12in. and instructions.

Baker Reproducers Ltd

Send 4d Stamp for Further Details

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

AMPLIFIER FOR MAGNAVOX TAPE DECKS — 4 TRACK CAN BE USED FOR 2-TRACK



Chassis 12½ x 5½ x 4½ in. high. Plastic front panel finished in Black and "Silver". 200-250 A.C. Record/Playback amp. switch; Off/On-Tone. Vol./Mic.; Vol./Gram; Mic. Input; Gram. Input; Valves 6BR7; 12AX7; EM84; EL84 and EZ20. Separate Output Transformer (Already wired to amp). PRICE £12 (10/- P. & P.). 3-ohm speaker 7" x 4" 16/- extra.

STEREO AMPLIFIER type HV—2 x 3 Watts

Fully built. On off sep. vol. and tone each channel 12 x 4½ x 6 in. high. EZ80. 2 x ECL82. For 3 ohm speakers, double wound main trans: fixing flanges and base plate, suitable for crystal cart, tuner etc. £8.10.0 (8/- p. & p., 200-250V. A.C. Superior version — separate base, treble & vol. each channel with mono/stereo switch 15/- extra.



STEREO AMPLIFIER type RC—2 x 3 Watts for 200-250V. A.C.

Fully built. 2 x UCL82, metal rect: ganged vol. and tone cont: on-off balance. 11 x 3½ x 4 in. high. Double wound mains trans. with supporting brackets. For 3-ohm speakers. £8 (8/- p. & p.)



MONO GRAM CHASSIS 3 WATT

3 Wave band long-meal-short, Gram., 200-250V A.C Ferrite aerial. Chassis 13 x 7 x 5 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH81, EF89, EBC81, EL84, EZ20. Price £10.12.6 (7/6 p. & p.) Output trans. for 3-ohm speaker



NEW TAPE AMPLIFIER for 4 track B.S.R. Deck TD2. Mains and output Trans. 10" x 6" x 4" overall. Rect.; ECC83, EL84. Mike and Gram Inputs. £7.5.0 (10/- p. & p.) For 3-ohm speaker. (For 200-250V. A.C.)

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.


(3 mins. from Station and Buses), FULL GUARANTEE. Aldershot 22240
CLOSED WEDNESDAY. S.A.E. for enquiries please.

multi-drawer storage units

NEW! HANDY! TIDY! I-N-T-E-R-L-O-C-K-I-N-G

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots—removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!
SINGLE UNITS (5ins x 2½ins x 2½ins) Usually 2/6 each. Our Price 24/- dozen
DOUBLE UNITS (5ins x 4½ins x 2½ins) Usually 4/6 each. Our Price: 40/- dozen
PLUS QUANTITY DISCOUNTS!
Orders £5 and over Deduct 1/- in the £
Orders £10 and over Deduct 1/6 in the £
Orders £20 and over Deduct 2/- in the £
Packing/Postage/Carrriage: Add 6/- to all orders under £3. Orders £3 and over, packing/postage/carrriage free
Quotations for Larger Quantities

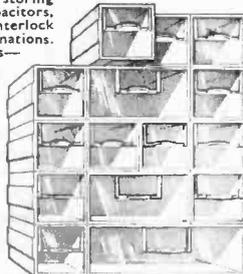

IVORYET LIMITED

(Dep. PW7) 31 ALBERT RD. HENDON - LONDON NW4

A place for everything
Everything in its place!

BRAND NEW FULLY GUARANTEED TRANSISTORS & DEVICES

1N4001	2/-	AAZ12	4/-	BPY10	19/8
1N4002	2/3	AAZ13	2/8	BX820	4/-
1N4003	2/6	AAZ17	2/-	BX821	5/-
1N4004	3/-	AC126	5/-	BX876	4/-
1N4005	3/6	AC127	5/8	BX827	4/-
1N4006	4/-	AC127Z	12/8	BX828	5/-
1N4007	5/-	AC128	5/-	BX829	5/-
1N4009	3/6	AC164	3/-	BX830	5/-
1N4148	1/6	AC169	5/-	BX833	6/-
2G210	12/6	AC163	4/-	BX866	5/-
2G240	49/6	AC176	5/-	BX867	5/-
2G301	4/-	AC187	5/-	BX95A	4/8
2G302	4/8	AC188	6/-	BX95	3/8
2G303	5/-	AC17	6/-	BX100	3/8
2G308	7/8	AC18	4/-	BX103	4/8
2G308	7/8	AC19	5/-	BX114	5/8
2G309	6/-	AC20	4/-	BX126	5/8
2G371	4/8	AC21	4/8	BX210	10/-
2G374	6/8	AC22	3/8	BX211	9/-
2G381	6/8	AC28	3/8	BX212	8/-
2G389	5/8	AC23	5/8	BX213	5/-
2G383	6/-	AC26	5/-	BX215	20/-
2N404	4/8	AC29	9/8	BX216	18/6
2N696	4/8	AC24	3/-	GET102	6/8
2N697	5/-	AD140	11/-	GET103	4/8
2N698	8/8	AD149	12/8	MFP102	8/8
2N699	1/8	AD161	7/8	MFP103	8/8
2N708A	2/8	AD162	7/8	MFP104	7/8
2N707	12/8	AF102	15/-	MFP105	8/8
2N708	3/-	AF114	6/8	OA5	3/-
2N914	4/8	AF115	6/8	OA7	4/-
2N916	4/8	AF116	6/8	OA9	3/-
2N918	7/8	AF117	5/-	OA10	4/-
2N919	4/-	AF118	10/8	OA11	2/-
2N920	5/-	AF124	6/8	OA70	2/-
2N922	8/8	AF125	5/-	OA71	2/-
2N930	7/8	AF126	4/-	OA73	2/-
2N1131	6/-	AF127	4/-	OA74	2/-
2N1132	8/-	AF139	6/-	OA79	2/-
2N1303	4/8	AF178	8/-	OA81	2/-
2N1304	5/-	AF181	8/8	OA85	2/6
2N1305	5/-	AF186	9/-	OA86	4/-
2N1306	5/-	AF239	8/-	OA90	2/-
2N1307	6/-	AFY19	22/8	OA91	1/8
2N1308	6/-	AFZ11	8/-	OA95	1/8
2N1309	6/-	AFZ12	10/-	OA200	1/8
2N1613	5/-	AS292	6/8	OA202	2/-
2N2147	17/8	AS27	7/8	OA210	6/8
2N2160	15/-	AS28	6/8	OA211	9/8
2N2287	25/-	AS29	6/8	OA225	7/8
2N2646	10/8	AS27	9/8	OA228	7/8
2N2904	8/8	AB221	8/8	OA229	9/8
2N2905	10/8	AY10	18/8	OA231	9/8
2N2925	4/-	B3M	19/8	OA234	7/8
2N2926	2/8	BA110	5/-	OA238	9/8
2N3011	7/8	BA231	2/-	OC16	10/-
2N3053	5/-	BC107	3/-	OC19	19/8
2N3054	12/6	BC108	2/8	OC20	10/8
2N3055	15/-	BC109	3/-	OC22	9/8
2N3702	3/8	BC113	6/8	OC23	12/8
2N3703	3/8	BC116	8/8	OC29	12/8
2N3704	4/-	BC118	7/8	OC26	7/8
2N3705	3/8	BC134	7/8	OC26	5/8
2N3707	4/-	BC135	6/8	OC28	12/8
2N3709	3/8	BC136	7/8	OC29	12/8
2N3710	3/8	BC137	8/8	OC35	10/-
2N3711	8/8	BC138	8/8	OC36	12/8
2N3730	10/-	BCY30	5/8	OC41	5/8
2N3731	12/6	BCY31	8/8	OC42	8/8
2N3794	2/8	BCY32	10/-	OC43	8/8
2N3819	8/-	BCY33	8/8	OC44	4/-
2N3830	19/8	BCY34	8/8	OC45	3/8
2N3832	17/8	BCY38	7/8	OC46	5/8
2N4058	5/8	BCY39	8/8	OC70	3/-
2N4061	4/-	BCY40	10/-	OC71	3/-
2N4286	3/-	BCY42	5/-	OC72	5/-
2N4288	3/-	BCY43	5/-	OC73	8/8
2N4289	8/8	BCY70	4/-	OC74	6/8
2N4290	3/-	BCZ11	7/8	OC76	5/-
2N4291	3/-	BC147	3/8	OC76	5/-
2N4292	3/-	BC148	2/8	OC77	8/8
40381	12/-	BC149	4/-	OC78	5/-
40382	13/8	BF182	6/8	OC81	5/-
28001	10/-	BF194	3/8	OC81D	4/-
28002	10/8	BF195	3/8	OC82	5/-
28003	9/8	BD124	12/8	OC83	5/-
28004	9/8	BEN3000	5/-	OC84	5/-
28005	14/-	BF115	5/-	OC122	10/-
28012	25/-	BF154	8/-	OC123	10/-
28013	20/-	BF158	8/-	OC139	5/-
28017	15/-	BF159	12/8	OC140	7/8
28034	12/6	BF163	8/8	OC141	15/8
28036	25/-	BF167	5/-	OC169	5/-
28290	9/-	BF173	8/8	OC170	5/-
28321	6/-	BF180	7/8	OC171	6/8
28322	7/8	BF181	7/8	OC200	5/-
28324	10/-	BFX30	6/8	OC201	9/8
28324	12/6	BFX88	5/-	OC202	12/8
28212	9/8	BFY20	12/8	OC203	7/8
28701	8/8	BFY60	5/-	OC204	8/8
28702	11/-	BFY61	4/8	OC205	12/8
28731	8/8	BFY62	5/-	OC206	15/-
28732	8/8	BFY63	8/8	OC207	16/-
28733	9/8	BFY64	8/8	OC271	19/8
AA178	8/8	BLV10	20/-	ORP12	12/8
AA179	5/-	BLV11	22/8	ORP60	8/8

INTEGRATED CIRCUITS

Type	1	12+	25+	100+	500+
UL914	9/9	9/-	8/-	7/3	6/6
UL923	12/6	11/9	11/-	10/-	9/3
SL403A	49/6	45/-	40/-	37/6	35/-
MC1303	52/6	48/-	45/-	40/8	35/-
MC1304	55/-	50/-	47/6	42/6	37/6
PA246	52/6	48/-	45/-	40/-	35/-

2N3055	15/-	2N3819	8/-
Mullard 115watt Silicon Power		Texas F.E.T.	
25 + 1/8		25 + 6/9	
100 + 1/1		100 + 5/9	
		500 + 5/-	

2N2926	2/-	2N2646	10/6
NPN Planar All Colours		Motorola Unijunction	
25 + 1/8		100 + 7/6	
100 + 1/6		500 + 6/9	

AF139	6/-	AF186	9/-
Siemens V.H.F.		Mullard V.H.F.	
25 + 5/3		25 + 8/-	
100 + 4/6		100 + 7/-	
500 + 3/9		500 + 6/-	

AD161/AD162	13/- pair	BY126	3/6
Mullard PNP		Mullard 800v 1 amp Plastic	
25 + 5/-		25 + 2/9	
100 + 4/3		100 + 2/6	

BY127	4/-	BY713	5/-
Mullard 800v 1 amp Plastic		Mullard 6a 200v	
25 + 3/3		25 + 4/9	
100 + 3/-		100 + 3/4	
		500 + 3/3	

BT102/500R	12/6	BC107/8/9	2/9 ea.
Mullard Thyristor		I.T.T. Planars	
500 p.i.v. 6.Sa		25 + 2/3	
25 + 11/-		100 + 2/5	
100 + 10/3		500 + 1/10	

OA200/OA202	1/9	OC71	19/6
SILICON Diodes		Mullard Photo	
25 + 1/6		25 + 17/3	
100 + 1/3		100 + 4/3	
500 + 1/1		500 + 13/6	

OC42	6/-	OC44	4/-
Mullard		Mullard	
25 + 5/3		25 + 3/3	
100 + 4/9		100 + 2/9	
500 + 4/3		500 + 2/4	

OC45	3/6	OC71	3/-
Mullard		Mullard	
25 + 3/-		25 + 2/3	
100 + 2/6		100 + 2/3	
500 + 2/-		500 + 1/9	

OC75	5/-	BCY34	6/-
Mullard		Mullard	
25 + 4/3		25 + 5/7	
100 + 3/6		100 + 4/3	
500 + 3/-		500 + 4/-	

OC20	19/6	IN4001/2/3 200	3/3
Mullard 10w		1 amp 1.3k	
25 + 15/9		25 + 1/10	
100 + 14/6		100 + 1/6	
500 + 13/3		500 + 1/4	

IN4004/5	3/-	ZENER DIODES	
400-600V 1 amp		400 MW 5%	
25 + 2/6		BZY88 Range	
100 + 2/-		All Voltages	
500 + 1/10		3.3v—33v 4/-	

IN4006/7	4/-	OC139	5/-
800-1000V 1 amp		Mullard	
25 + 3/4		25 + 4/-	
100 + 3/-		100 + 3/3	
500 + 2/6		500 + 3/3	

OC140	7/6	OC140</
-------	-----	---------

ELECTRONIC MULTIMETERS. AVO CT38 for 200/250v mains, ranges DC volts 250mV to 250V also 10kV with probe, DC amps 10 μ A to 25 amps, AC volts 100mV to 250v, AC amps 10 μ A to 25 amps, Ohms 0 to 1000 Meg, Power o/p 50 μ watts to 5 watts, R.F. probe to 250 Mc/s supplied tested with H.V. probe, circ. and leads **£18.10.**

CONTROL 595. Contains 2x 500 μ A meters, scales 0 to 2.5 & 50,000ft, 3x swts, small variac can used on 6v AC, Pots, Res etc new **£3**, RANGE CAL unit contains P.U. for 200/250 mains o/p 300v DC 120 mA 6.3 etc 2x chokes, 10 valves, swts, pots, conds and large number of other parts in case **£3-15.**

INDICATOR 152. Small special purpose Ind Unit with tube 3DP1S & valves 6AG5 x3, 2X2, tube 3" green screen in case size 7x7x12" **32/6** used **42/6** new.

SCOPE TROLLIES. Tektronix size 38x26x17" with stowage **£15.**

RADIO TELEMETERS. Low freq Rx unit with 6x valves, speaker, 2xmotors, tape head, coin box etc in neat case size 14x7x6" for 230v mains with circ & mods for Radio. 2. **£3-15.** RECT. 12v DC fw bridge at 4 amps **12/-.** CONDS. 8uf 1 kV wk size 4 $\frac{1}{2}$ x2 $\frac{1}{2}$ x3 $\frac{1}{2}$ 2 for **17/6.** TRANS. pria 230v, Sec 350-310-0-310-350 at 220 mA 5v 6a, 6.7 5a, 6.3 3a twice, 6.3 1a twice **42/6.**

TRANSISTOR INV. 12v DC I/P, O/P 250v at 100 mA & -25v in case size 9x3 $\frac{1}{2}$ x3" with smoothing + or - Ea **£3-5.** TRANSISTORS. OC35 or OC28 marked ex equip 4 for **15/-.** RELAYS. 6/12 DC coil as one N.O. 20 amp contact **7/6**, also 12v 280 ohm 2p c/o size 1 $\frac{1}{2}$ x1 $\frac{1}{2}$ " with cover & base **7/6.**

AMP PANEL with 3x OC71 & OC35 5x 0A81 2x pot cores etc mounted on vero panel long leads **12/6.** O/P & DRIVER TRANS. for use with amp panel reqs 2x OC35 3.5w 3 ohm o/p **15/-.** INV. TRANS. 12v I/P, O/P 300v at 150 MA reqs 2x OC28 or sim with circ **38/-.** TRANSIS. MOD. TRANS. used with 2x OC35 or sim to match QQVO3-10 also 15 ohm o/p supplied with driver trans. 10 watts **33/-.** CRYSTAL FILTER. 10.7 Mc/s 50Kc BW **27/6.** HELIPOTS. 10 turn 500 ohm, 2.5K & 50K all **16/6.** HELIPOT DIALS. 10 turn counter dials panel mounting **16/6.** VALVE UNIT with 12AX7 x2, 6BR7, 6BS7, 12BH7 relay close tol res etc **12/-.** METERS. 1 mA edgewise reading scale 0 to 2000yds in 10 div **20/-.** SMALL BOXES with lid size overhaul 3 $\frac{1}{2}$ x2 $\frac{1}{2}$ x1" plain All 10 for **10/-.** SWITCHES. 2p 22w 2b with knob **7/6.** RECT UNIT 200/250 I/P, 12v DC at 3 amps twice i.e. 24v 3a or 12v 6a **£3-15.**

CIRCUITS R1475 (88 set) and R1392 5/- ea.

The above prices include post or carr.


A. H. Supplies

57 MAIN ROAD SHEFFIELD S9 5HL

S.A.E. with enquiries

PHOTOELECTRIC KIT

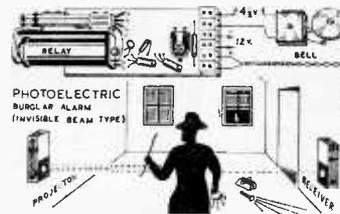CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT

39/6

Postage and Pack. 2/6 (UK)

Commonwealth:

SURFACE MAIL 3/6

AIR MAIL £1.0.0

Australia, New Zealand,

S. Africa, Canada and U.S.A.

Also Essential Data Circuits

and Plans for Building

10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price **19/6.** Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price **29/6.** Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.

CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs".

Price **19/6.** Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

JUNIOR OPTICAL KIT

Versatile Infra-Red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector, and photocell receiver for use with Junior Photoelectric Kit.

Price **10/6.** Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

YORK ELECTRICS

335 BATTERSEA PARK RD., LONDON S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDGE, YORKS.

Tel. Heckmondwike 4285

Amplifier Units Type A1413. Complete with Valves Type 5Z4 and 6V6GT. 230-250 Volt 50 cycles. Transformer Class, Clean Condition. Untested 25/-, Carriage B.R.S. 15/-.

Air Mileage Units complete with 24 volt Motor and Gears etc. Clean condition. Untested, less Relay 15/-, Carr. B.R.S. 12/-.

Special Sale of New C.V. Valves. Removed from units. 12 months Guarantee. P/P on any Valve 9d.

CV138 2/- CV140 2/- CV455 2/- CV136 2/-
CV287 1/- CV345 1/- CV284 1/-

Speakers P.M. All 3 ohm. Perfect condition, removed from TV sets. P/P on any Speaker 4/-, 6 inch Round 3/-, 5 inch Round 3/-, 8 x 5 Elliptical 6/-, 7 x 4 Elliptical 5/-, 6 x 4 Elliptical 3/-, Slot Speakers 8 x 2 Elliptical 3/-.

AW43/80 T.V. Tubes. Good Picture. No Guarantee £1. Plus carriage 15/-.

Reclaimed T.V. Tubes with 6 months Guarantee 17" Type AW43/80, AW43/88. £2 each. MW43/69 30/-. All Tubes 15/- carriage.

Silicon Rectifiers. 500 MA. 800 P.I.V. 2/6 or 24/- Per doz. Post Paid. Jap Earpieces, Magnetic. 8 ohms. Small or Large Plug. 1/11 Post Paid.

Top Grade Mylar Tapes 7 inch Long Play 14/-, 7 inch Standard 11/6, 5 inch Standard 7/9, 5 inch Long Play 10/-, Post on any Tape 1/9.

Panels of Resistors and Condensers. 9/- Post Paid Ex Units.

Complete Untested 17 inch T.V. Sets 12 Channel 50/- carriage £1.

VALVE LIST—Ex Equipment, 3 months' guarantee. Single Valves Post 7d., over 3 Valves p. & p. paid.

ARP12	1/6	EY86	5/-	PY33	5/-	6U4	5/-
EB91	9d	PCC84	2/-	PY82	1/6	10P13	2/6
EBF80	3/-	PCF80	2/-	PZ30	5/-	20D1	3/-
ECC81	3/-	PCL82	4/-	U191	5/-	20P1	5/-
ECC82	3/-	PL36	5/-	U251	5/-	20P3	2/6
EF50	1/-	PL81	4/-	6B8	1/6	30PL1	5/-
EF91	9d	PY81	1/6	6BW7	2/6	30F5	2/6

ELECTROVALUE

EVERYTHING BRAND NEW & TO SPECIFICATION • LARGE STOCKS

BARGAINS IN NEW SEMICONDUCTORS all power types supplied with free insulating sets

1N914	1/3	2N3706	3/3	40512	45/6	BC147	3/6	BFY51	4/3
1N3764	4/-	2N3707	4/-	40602	3/6	BC148	3/3	BBSX20	3/9
1N4148	1/9	2N3708	3/-	AC107	14/6	BC149	3/6	BY164	10/-
1N6054	4/-	2N3709	3/-	AC126	6/6	BC153	10/-	BY238	3/6
1S940	1/-	2N3710	3/6	AC127	6/-	BC154	11/-	CI06B1	14/6
2N698	0/6	2N3711	3/11	AC128	9/-	BC157	3/9	MC140	5/-
2N697	5/6	2N3731	24/-	AC176	11/-	BC158	3/3	MJ480	21/-
2N706	2/9	2N3794	3/3	ACY22	3/9	BC159	3/9	MJ481	27/-
2N1302	4/-	2N3819	8/6	ACY40	4/-	BC167	2/6	MJ491	80/-
2N1303	4/-	2N3820	25/6	AD140	19/-	BC168	2/6	MFF102	7/6
2N1304	4/6	2N3894	7/6	AD142	14/3	BC169	2/6	NKT403	15/6
2N1305	4/6	2N3906	7/6	AD149	17/6	BC177	6/3	NKT405	15/-
2N1306	6/9	2N4059	5/3	AD161/AD162	(matched) 19/- pr	BC178	5/6	OA47	1/9
2N1307	6/9	2N4060	4/3	AF114	7/-	BC179	6/-	OA90	1/3
2N1308	6/9	2N4061	4/3	AF115	7/-	BC182L	4/3	OA91	1/3
2N1309	8/9	2N4061	4/3	AF116	7/-	BC183L	2/3	OA95	1/3
2N1613	6/-	2N4062	4/3	AF116	6/6	BC184L	2/6	OA99	1/3
2N1711	7/-	2N4284	3/3	AF117	6/6	BC186	8/6	OA200	1/11
2N2147	18/9	2N4286	3/3	AF124	7/6	BC212L	5/-	OA202	6/-
2N2218	9/3	2N4289	3/3	AF127	7/-	BC213L	5/-	OC71	5/6
2N2270	12/9	2N4291	3/3	AF139	9/6	BC214L	5/3	TIP31A	17/6
2N2484	13/6	2N4292	3/3	AF190	18/6	BCY70	5/6	TIP32A	23/9
2N2646	10/9	2N4410	4/9	AF239	9/9	BD121	18/-	TIP43	10/6
2N2904	11/-	2N5062	12/3	AFY26	8/6	BD123	24/3	ZTX300	3/6
2N2924	4/-	2N5163	5/-	AFY27	8/3	BD124	15/3	ZTX301	3/6
2N2925	4/6	2N5192	25/-	AFY28	6/6	BF187	8/6	ZTX302	4/6
2N2926	2/3	2N5196	23/3	BF041	15/-	BF178	10/6	ZTX303	4/6
2N3039	5/6	2N5457	9/9	BA102	9/-	BF190	12/-	ZTX304	6/9
2N3054	14/3	2N5458	9/9	BA115	4/-	BF194	7/-	ZTX500	5/-
2N3055	16/-	2N5459	9/9	BA130	4/6	BF195	7/6	ZTX501	5/-
2N3325	10/9	40260	14/3	BA145	5/6	BFX29	10/9	ZTX502	6/-
2N3663	11/6	40361	12/6	BC107	2/9	BFX34	7/6	ZTX503	5/-
2N3702	3/6	40362	15/-	BC108	2/6	BFX35	8/3	ZTX504	12/-
2N3703	3/3	40408	16/3	BC109	2/9	BFX37	8/6	ZTX530	5/5
2N3704	3/9	40408	14/6	BC125	12/-	BFX88	6/9	ZTX531	6/9
2N3705	3/5	40430	37/-	BC126	12/-	BFY50	4/6		

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82Ω-220KΩ	E12	18	16	15
C	1/8W	5%	4.7Ω-330KΩ	E24	2-5	2	1-75
C	1/4W	10%	4.7Ω-10MΩ	E12	2-5	2	1-75
C	1/2W	5%	4.7Ω-10MΩ	E24	3	2-5	2-25
C	1W	10%	4.7Ω-10MΩ	E12	6	5	4-5
MO	1/2W	2%	10Ω-1MΩ	E24	9	8	7
WW	1W	10% ±1/20Ω	0.22Ω-3.92Ω	E12		15d all quantities	
WW	3W	5%	12Ω-10KΩ	E12		15d all quantities	
WW	7W	5%	12Ω-10KΩ	E12		15d all quantities	

Codes: C = carbon film high stability low noise
MO = metal oxide Electrocell TR5 ultra low noise
WW = wire wound Pleseyer.

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

INTEGRATED CIRCUIT AMPLIFIERS

SINGLAR IC10 complete with instruction book giving amplifier circuit details and range of applications. 50/6 nett.

Component pack for IC10 stereo amplifier, complete, inc. knobs, switch, neon ind. plugs, sockets, etc. £4 15 0 nett

WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W 4/9 each
SLIDER SWITCHES D.P.D.T. 3/- each

NEON INDICATOR LAMPS

all 200/250V. Square bezel, red only 3/9
Round chrome bezel red, amber, clear 4/9 each

Toggle switches, 250V a.c. 1.5A.
chrome dolly and chrome milled nut S.P.S.T. 3/9; S.P.D.T. 4/6; D.P.D.T. 5/9; S.P.D.T. centre off 5/-.

S-DeC's put an end to "birds nesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC only 30/- Compact T-DeC, increased capacity, may be temperature-cycled. T-DeC only 50/- post free. Full range stocked.

MULLARD polyester C280 series

250V 20%: 0-01; 0-022; 0-033; 0-047 8d ea. 0-068; 0-1 9d ea., 0-15 11d., 0-22 1/-, 10%: 0-33 1/5, 0-47 1/8, 0-68 2/3, 1μF 2/9, 1.5μF 4/2, 2-2μF 4/9.

MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 1/3 each
Values (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/64; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/64; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/64; 125/4; 125/10; 125/16; 160/2.5; 200/64; 200/10; 250/4; 320/2.5; 320/64; 400/4; 500/2.5.

LARGE CAPACITORS

High ripple current types: 1000/25 5/8; 1000/50 8/2; 1000/100 18/3; 2000/25 7/4; 2000/50 11/4; 2000/100 25/9; 2500/64 15/5; 2500/70 13/6; 5000/25 12/6; 5000/50 21/11; 5000/100 58/3; 10000/15 17/-; 10000/25 24/6; 10000/50 44/-; 10000/70 61/-.

MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 1/9; 100/25 1/9; 100/50 2/6; 250/25 2/6; 330/25 2/6; 250/50 3/9; 500/25 3/9; 500/50 4/8; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-.

SMALL ELECTROLYTICS

Axial leads: 4.7/10; 4.7/25; 5/50 1/- ea. 10/10; 10/25; 10/50; 33/10; 50/10 1/- ea. 25/25; 25/50; 47/25; 100/10; 220/10 1/3 ea.

PEAK SOUND PRODUCTS

ENGLEFIELD CABINET KITS

Build it 12 + 12 or 25 + 25



Stereo amplifier in modular kit form 12 watts per channel £38/9/-; 25 watts £58/15/- Cabinet kit only £6. These prices nett.
As recently reviewed in Hi Fi Sound.

BAXANDALL SPEAKER SYSTEM

Designed by Peter Baxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 15Ω 59RM109 speaker Unit Kit £13/12/- nett; built £18/8/6 nett.

STEREO AMPLIFIER S.A. 10-10.

Developed from the very successful SA.8-8 amplifier giving first class stereo amplification featuring separate volume controls for each channel, bass and treble controls, 10 watts per channel into 5 to 8Ω. Kit £19/7/6 nett; built £24/18/8 nett. Suitable 8Ω wide range speakers available £13/15/- each nett.

MAINLINE AMPLIFIER KITS

RCA/8GS designed main amplifier kits. Input sensitivity 600-700mV for full output into 8Ω.

Power	Kit price including components	Suitable unreg. power supply
12W	146/- nett	86/-
25W	185/- nett	N/A
40W	198/- nett	101/8
70W	216/- nett	131/-

30 WATT BAILEY AMPLIFIER KIT

Special summer reduction (to Sept. 30th 1970 only) Sensitivity 1.2V for full output into 8Ω. Transistors for one channel £7/5/8 list, £6 only nett. Transistors for two channels £14/11/- list £11 only nett. Capacitors and resistors (metal oxide) 30/- per channel nett. Complete unregulated power supply kit 87/6 nett

ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 4/6 each 1W: 6-8V to 82V 9/- each 1.5W: 4.7V to 75V 12/- each Clip to increase 1.5W rating to 3 watts (type 266F) 8d.

CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.
Single gang linear 220Ω to 2.2MΩ 2/6
Single gang log 4.7KΩ to 2.2MΩ 2/6
Dual gang linear 4.7KΩ to 2.2MΩ 8/6
Dual gang log 4.7KΩ to 2.2MΩ 8/6
Log/antilog 10K, 47K, 1MΩ only 8/6
Any type with 1/4 A.D.P. mains switch, extra 2/6

Please note: only decodes of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100Ω, 220Ω 470Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10MΩ Vertical or horizontal mounting 1/- each.

COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on net items).

POSTAGE AND PACKING

Free on orders over £2. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

ELECTROVALUE (Dept. PW.7) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY.
Hours: 9-5.30; Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3) Telex 264475

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 10s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

MISCELLANEOUS

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond, Surrey.

BUILD IT in a DEWBOX quality cabinet. 2in. x 2½in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

PARAPHYSICAL LABORATORY, Downton, Wilts. Telekinesis. Magazines. Send S.A.E. for list. Samples 20s.

SERVICE FOR THE AMATEUR electronic enthusiast. Are you building equipment requiring a transformer? If so, send for an immediate quotation, or s.a.e. for our comprehensive price list. Also available on request, enamelled copper wire price list.—Banner Transformers, 84 Old Lansdowne Rd, West Didsbury, Manchester, 20.

PHOTO ELECTRIC SWITCH KIT

Light cell, transistor, relay etc. Elegant case in hammer finish 5½" x 2½" x 4½" fitted with light hood. Ideal counter alarm, Dawn/Dusk switch, etc. **35/-** Post Paid.

6 OR 12 VOLT FLUORESCENT LIGHTS

12 Ins. 8 Watt tube ample light for caravan, tent etc. Fully transistorised, low battery drain. Unbeatable at **65/6** post paid.

or in kit form **57/6**

4 WATT GRAM AMPS.

Volume and tone controls, mains operation. 3Ω output, new and boxed **72/6** POST PAID

SALOP ELECTRONICS Callers welcome
23 Wyle Cgd, Shrewsbury,
Shropshire S.A.E. for lists

MUSICAL MIRACLES! Drum, Cymbals, Waa-Waa and Fuzz modules. New unique effects units, Percussion etc. Good waa-waa kits 49/-. Famous "Mister Bassman" bass pedal unit. Also bargain components list of reed switches etc. Send S.A.E. NOW!—D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops uses 41 valves. With 2s variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

FOR INFORMATION about the British Amateur Radio Teleprinter Group, write to The Secretary, G. Shirville, 2 Bradford Way, Toddington, Dunstable, Beds.

MISCELLANEOUS

(continued)

TOP TRANSISTORS

ACY22 1/9 OC45 1/9 ZTX300 1/9
BC108 1/9 OC71 1/9 2N706 1/9
BFY51 1/9 OC201 1/9 2N2926 1/9
BFY52 1/9 OC202 1/9 2N3708 1/9

All the above types are available at 16 for £1. Brand New. Individually Tested.

ANTEX SOLDER IRON

This is a lightweight iron fitted with a 15 watt nickel plated bit. It has been designed to enable you to weld reliable joints accurately. Special low price. Model CN240 volts.

ACT NOW 29/11

MONEY BACK GUARANTEE P. & P. 1/-

**J. M. KING (V), 17 Buckridge,
Portpool Lane, London, E.C.1.**

CHASSIS

ALUMINIUM with GUSSET PLATES
18 S.W.G. STANDARD 2½" WALLS

	s. d.		s. d.
4" x 3"	3 6	12" x 3"	6 6
6" x 3"	5 0	12" x 5"	7 3
6" x 4"	5 3	12" x 8"	10 6
6" x 6"	5 9	14" x 3"	7 0
8" x 3"	6 0	14" x 9"	14 0
8" x 6"	7 3	16" x 6"	11 0
10" x 7"	8 0	16" x 10"	16 6

P & P 2/- per order. Free on orders over £2

D. A. COGLAN

Electronic Chassis and Panel Makers,
6 GREEN WALKS, PRESTWICH,
MANCHESTER, LANCs.
Phone 061-773 5349

FOR SALE

MORSE MADE !! EASY

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. Ring, s.t.d. 01-680 2898 send 8d. stamp for explanatory booklet to:
G8CHS (BOX 11), 46 GREEN LANE, PURLEY, SURREY

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

TO CLEAR.—Sets of over 35 useful components from ex. adm. amplifier panels, sub chassis, rectifiers, condensers, diodes, resistors, James plugs, valve holders, etc. Only 5/- plus 1/6 P&P. Also valves CV2127, CV455, CV4055, CV4024, 2/6 each or 6 for 10/-.—Greene, Fieldings, Poulner, Ringwood, Hants.

FOR SALE

(continued)

YUKAN
SELF-SPRAY

Get these NOW! air drying **GREY HAMMER**
OR **BLACK WRINKLE**
(CRACKLE) Finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/6 at our counter or 16/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Plast finish (12 ozs. self-spray can only) 13/11 carriage paid.
SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/7) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:
Dept. M • **YUKAN**, 307A, EDGWARE ROAD, LONDON, W.2.
We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—we can supply you too.
Open all day Saturday. Closed Thursday afternoons.

ALL KINDS OF EVERYTHING for sale to Irish readers. Write for price list, plus Bargain page. Toner Electronics, Lismore Park, Waterford. Phone 3048.

FOR SALE. H.R.O. six coils, P.U. very good condition, £16. Chapman, 11 Moss-giel Ave., Troon, Ayrshire.

WANTED

CASH PAID for New Valves. Payment by return. WILLOW VALE, ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

WE BUY New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

WANTED NEW VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

WANTED NEW VALVES, televisions, radiograms, transistors, etc. STAN WILL-ETTS, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S WIRELESS STORES, 55 Worcester Street, Wolverhampton.

SERVICE SHEETS AND MANUALS PURCHASED. Highest prices paid. Sultan Radio, 29 Church Road, Tunbridge Wells, Kent. Phone T.W. 22093.

SERVICE SHEETS

SERVICE SHEETS (1925-1970) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 1/- Over 8,000 models available. Catalogue 2/6. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex.

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES LIMITED

30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1970 List now available at 2/- plus postage

If list is required indicate with X

From

Address

enclose remittance of

(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY (February PW)

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 2/-. S.A.E. enquiries. TEL-RAY, 11 Maudland Bank, Preston.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 5/- each, Manuals from 10/- plus large S.A.E.

(Uncrossed P.O. s please, original returned if service sheets not available.)

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

SERVICE SHEETS

(continued)

RADIO, TELEVISION over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London W.6. SHE 8441.

SERVICE SHEETS (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. THOMAS BOWER, 5 South Street, Oakenshaw, Bradford.

SITUATIONS VACANT

ENGINEERS, A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132 page guide: BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

TV and Radio, A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. Write for 132 page Handbook—FREE. Please state subject. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept 137K), Aldermaston Court, Aldermaston, Berks.

Radio Operators

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1971 and in subsequent years.

Specialist training courses lasting approximately nine months according to the trainee's progress are held at intervals. Applications are now invited for the course starting in January 1971.

During training a salary will be paid on the following scale:—

Age 21	£848 per annum
22	£906 " "
23	£943 " "
24	£981 " "
25 and over	£1,023 " "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade 1 scale:—

Age 21	£1,023 per annum
22	£1,087 " "
23	£1,150 " "
24	£1,214 " "
25 (highest age point)	£1,288 " "

then by six annual increases to a maximum of £1,749 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must normally be under 35 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or PMG qualifications.

Interviews will be arranged throughout 1970.

Application forms and further particulars from:—

RECRUITMENT OFFICER,
Government Communications
Headquarters,
Oakley, Priors Road,
CHELTENHAM, Glos. GL52 5AJ
Tel: No. Cheltenham 21491 Ext 2270

EDUCATIONAL

CITY & GUILDS (electrical, etc.) on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

EDUCATIONAL

(continued)

BECOME "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. CHAMBERS COLLEGE (Dept. 857K), 148 Holborn, London, E.C.1.

RADIO OFFICERS see the world! Seagoing and shore appointments. Trainee vacancies during 1970. Grants available. Day and Boarding students. Stamp for prospectus, Wireless College, Colwyn Bay, North Wales.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE,
STEWARTS ROAD, LONDON. SW8

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

BOOKS & PUBLICATIONS

TAPE RECORDING YEAR BOOK

COMPLETELY NEW NINTH EDITION WITH COMPREHENSIVE CATALOGUE SECTION AND ARTICLES BY EXPERTS

PRICE 10/6d. from
7 ALVERSTONE AVENUE,
EAST BARNET, HERTS.

SURPLUS HANDBOOKS

19 set Circuit and Notes ..	7/0 p/p 9d.
1155 set Circuit and Notes ..	7/0 p/p 9d.
H.R.O. Technical Instructions ..	6/0 p/p 9d.
38 set Technical Instructions ..	6/0 p/p 9d.
46 set Working Instructions ..	6/0 p/p 9d.
88 set Technical Instructions ..	7/6 p/p 9d.
BC.221 Circuit and Notes ..	6/0 p/p 9d.
Wavemeter Class D Tech. Instr. ..	6/0 p/p 9d.
18 set Circuit and Notes ..	6/0 p/p 9d.
BC.1000 (31 set) Circuit and Notes ..	6/0 p/p 9d.
CR.100/B.28 Circuit and Notes ..	10/6 p/p 1/-
R.107 Circuit and Notes ..	7/6 p/p 9d.
A.R.85D Instruction Manual ..	18/6 p/p 9d.
62 set Circuit and Notes ..	7/0 p/p 9d.
Circuit Diagram 5/6 each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.F.), BC.824, 22 set.	
Colour Code Indicator ..	2/6 p/p 6d.
52 set Sender and Receiver circuits 8/- post free	

S.A.E. with all enquiries please.
Postage rates apply to U.K. only.

Mail order only to:
INSTRUCTIONAL HANDBOOK SUPPLIES

DEPT. PW, TALBOT HOUSE,
28 TALBOT GARDENS, LEEDS 8

METAL WORK

METAL WORK: All types cabinets, chassis, racks etc., to your specifications. PHILPOTTS METAL WORKS LTD., Chapman Street, Loughborough.

LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 1/2 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.



CAXTON COLUMN. This is a column cabinet 23 1/2 x 5 1/2 x 5 1/2 in. deep finished in black or wood grain cloth with blue Vynair front. Key-hole slot for wall mounting. Fitted with three speaker units, 9 ohms impedance. Handles 8 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at 59/6d. P. & P. 10/6d. each.

SPEAKERS: Elac Heavy duty Ceramic Magnets 11,000 line, 10 x 6in, 3 ohm or 15 ohm, 49/6. P. & P. 5/6. 8in. round 15, 45/6. P. & P. 5/6. E.M.I. 134 x 8in. 3 ohm, 45/6, 15 ohm 48/6. P. & P. 3/6. E.M.I. 3in. tweeter 17/6. P. & P. 3/6. E.M.I. 134 x 8in. fitted two 2 1/2in. tweeters. 15 ohm 77/6. P. & P. 5/6. E.M.I. 134 x 8in. (15 ohm) Hi-Fi quality £5.19.6. P. & P. 5/6. E.M.I. Woofers, 6 1/2 x 6 1/2 in. square, 8 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 16/6. P. & P. 1/6. EAGLE Crossover units 3 or 16 ohms, 17/4. P. & P. 1/6. Bakers 12in., 25 watt 15 ohm £6.6.0. P. & P. 3/6.

VYNAIR Widths from 40 to 54in., 15/- yd. off roll. P. & P. 1/2. 1/2 yd, 8/-, P. & P. 1/9. Send 1/- stamps for samples.

SPEAKER MATCHING TRANSFORMERS. 3, 7, 15 ohms, 8 watt, 13/8. P. & P. 2/6.

BROADWAY ELECTRONICS

(Nr. Tooting Broadway Underground Stn) 92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 01-672 3884 (Closed all day Wed.)

CARTRIDGES. Stereo: Sonotone 8TA H/C Diamond, 47/6. Ronette S105 Medium Output, 28/6. S106 High Output 28/6. Acos GP93 1 Sapphire, 37/6. GP94 1 Sapphire, 39/6. GP91 Diamond, 42/6. GP91 Stereo Compatible (High, Medium or Low Output), 25/-. TA800 converts Philips AG3301, AG3306 to B.S.R. SX1H. Plug-in head complete with cartridge, 50/-. TA700 equivalent to B.S.R. SX1M, 35/-. Japanese equivalent to B.S.R. TC8s. 35/-. P. & P. 1/6.

Mono: Acos GP67/2 will replace Collaro and Garrard Mono cartridges. 18/6. T.T.C. Crystal High Gain, 15/-. B.S.R. TC8H Jap. equivalent, 26/-. Sonotone 2TSS, 15/-, P. & P. 1/6.

EARPIECES WITH CORD and 3.5mm. plug, 8 ohm magnetic, 3/-, 250 ohm, 4/-. 180 ohm with clip, 6/6. Xtal. P. & P. 6d.

PIANO KEY PUSH BUTTON SWITCHES. 7 button inc. mains on off. 6 banks of 6 P.C.O.. 8/6. P. & P. 1/6.

The **SHELLEY.** Size 21 x 11 x 6 1/2 in. An extremely elegant speaker system made of 12 m.m. chipboard covered with teak leathercloth with dark Vynair front (send S.A.E. for cloth samples). This unique system uses three ex T.V. speaker 6 1/2 in round for the Bass, 8 x 3 in for the Middle and 5 in round for Treble. Carefully matched and tested. Will handle 10-12 watts and will match 8 ohms impedance. If preferred the speakers can be wired in series parallel to match 3 ohms impedance. A real bargain at £4 19 6 plus 10/6 P. & P. MATCHING TRANSFORMER for 15 ohms 15/- post free.



Stella Nine Range Cases

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES which are made to fit Standard Alloy Chassis in grey blue or black with Aluminium Front Panels

Width	Depth	4" Height £ s. d.	6" Height £ s. d.	7 1/2" Height £ s. d.
6 1/2"	3 1/2"	18 0	18 0	1 1 6
6 1/2"	4 1/2"	18 3	1 5 0	1 5 0
8 1/2"	3 1/2"	18 0	1 5 0	1 5 0
8 1/2"	6 1/2"	1 5 0	1 11 9	1 17 0
10 1/2"	7 1/2"	1 14 6	2 2 6	2 6 0
12 1/2"	3 1/2"	1 5 0	1 11 9	1 17 6
12 1/2"	6 1/2"	1 14 0	2 2 0	2 5 6
12 1/2"	8 1/2"	2 3 0	2 11 8	2 16 6
14 1/2"	8 1/2"	1 10 0	1 17 6	2 2 0
14 1/2"	9 1/2"	2 11 6	3 7 0	3 10 0
16 1/2"	6 1/2"	2 6 0	2 15 6	3 1 9
16 1/2"	10 1/2"	3 0 0	3 18 0	4 6 0

Cases—Post 4s. 6d. per order. Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2 1/2" Walls

6" x 3"	6" x 4"	8" x 7"	10" x 7"	12" x 8"	14" x 9"	16" x 9"
6" x 3" 6 6	10" x 7" 10 3	14" x 3" 8 9	8" x 4" 8 9	12" x 3" 8 0	14" x 9" 17 3	8" x 7" 9 12
8" x 6" 9 3	12" x 8" 12 9	16" x 8" 12 9	10" x 7" 10 3	12" x 8" 12 9	16" x 10" 19 0	8" x 6" 9 3

Chassis—Post 3s. 0d. per order. Discounts available on quantities.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases
46 LOWFIELD ROAD
STOCKPORT - CHESHIRE
Tel: 061-480 2179

VALVE BARGAINS

Any 5, 9/-; 10, 14/-; 100, £5 10s from the following:
ECC82, ECL80, EF85, EF183, EBF89, EB91, EY86, PCC84, PCC89, PCF80, PCF86, PCL82, PCL83, PCL84, PL36, PL81, PY33, PY81, PY82, PY800.

AERIAL BOOSTERS 59/-

Three types of High Gain Transistorised pre-amplifiers all at the same price
UHF 625 Type L45, Tunable over the complete UHF Stations
VHF 405 Type L12 with Separate Tuning for Band 1 and Band 2. Please state channel numbers

FM UHF RADIO PRE-AMPLIFIER
SAE for Full Details. All complete with battery and leads, 7 day money back guarantee if not satisfied

VELCO ELECTRONICS, 62 BRIDGE ST. RAMSBOTTOM, BURY, LANCS.

SPEAKER CABINET BARGAIN



Beautifully finished in Straight Grained Teak Veneers with harmonising material front. Spare baffle, for any size of speaker up to 10 x 6ins. Size 16 x 8 x 6ins. Only 67/6d each or 2 at 62/6d each, carr. free. Send for free and illustrated lists. Albion Electronics Supplies, 16 Albion Road, Birchington, Kent.

NEW MODEL V.H.F. KIT MK2

Our latest Kit improved design and performance plus extra Amplifier Stage receives Alfrat, Amateurs, Mobile, Radio 2, 3, 4 etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

ONLY 88/- P. & P. FREE U.K. ONLY

"AUDIO 1" 8 WATT AMPLIFIER

Ready built, tested and guaranteed. Very attractive Cabinet in black leatherette with light grey front, size 10" x 4 1/2" x 4". Fitted large speaker, Jack Socket and Volume Control. Many uses e.g. Radio Kit Amplifier, Intercom, Record Player, Public Address or even Crystal Set Amplifier. OUR PRICE ONLY 97/- P. & P. 4/6d.



EXTENSION SPEAKER CABINET

The same Cabinet that houses our Amplifier with light grey front, size 10" x 4 1/2" x 4". Fitted large speaker, Jack Socket and Volume Control. Many uses e.g. Radio Kit Amplifier, Intercom, Record Player, Public Address or even Crystal Set Amplifier. OUR PRICE ONLY 97/- P. & P. 4/6d.

Cheques, Postal Orders to:
Dept. P.W.,
Galleon Trading Co., 288A Lodge Lane,
Romford, Essex

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hy-stab, Vitreous, 1-20 watt, 15/- Post Free. WHITSAM ELECTRICAL, 33 Drayton Green Road, West Ealing, W.13.

COMPLETE RANGE of Amateur Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

AMAZING VALUE ALL NEW FULL SPECIFICATION DEVICES

Integrated Circuits complete with data:
GE PA230 Audio Preampifier 18/6
GE PA234 1W Audio Amplifier 17/6
GE PA237 2W Audio Amplifier 32/6
Plessey SL402A Preamp and 2W Amp equivalent to I.C.10 42/-
MEL 11 Photo Darlington Amp 9/6
TTL Microcircuits for 5V Supply:
SN7400, SN7410, SN7420, SN7451 (each) 13/8
SN7473 31/5
Connectors for GE and TTL i.c.'s 7/-

High Quality low cost transistors:
GE 2N5172 NPN 200mW 1/9
ME 0412 PNP 200mW 3/9
TI 2N4059 PNP 250mW 3/6
MUL BFX86 NPN 800mW 6/-
MUL BD124 NPN 15W 12/-
S 2N3055 NPN 115W 14/6
Triacs for full wave power control:
RCA 40669 8A 400V 24/-
RCA 40583 Trigger Diode 5/3
Plastic rectifiers for power supplies:
1N 4820 1.5A 400V Si Rectifier 2/6
W005 1A 50V full wave bridge Si 7/6
PD40 2A 400V full wave bridge Si 15/-

JEF ELECTRONICS

York House, 12 York Drive, Grappenhall, Warrington, Lancs.
C.W.O. P. & P. 1/- per order. Mail Order only. Money back if not satisfied.

THYRISTORS. CRS 3/40 400V 3 amp, 8/6. BY100 3/-, post free. Quantity discount. 1 Old Shoreham Road, Southwick, Sussex.

TRANSFORMERS. Rewound, Prototypes supplied capacity for small quantity runs. S.A.E. please. Ratcliffe, 18 Beech Avenue, Thongsbridge, Huddersfield, Yorks.

RECEIVERS & COMPONENTS (continued)

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 10/- P. & P. 1/6. With a guaranteed minimum of 35 transistors. Transistor data included.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 3/6. With a guaranteed minimum of 85 transistors. Transistor data included.

PANELS with 2 power transistors sim. to OC28 on each board + components. 2 boards (4 x OC28) 10/- P. & P. 1/6d.

9 OAS, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13" x 4".
4 for 20/- P. & P. 5/-.

EX COMPUTER "MEMORY" CORE STORE PLANES

160 BITS £1 P. & P. 2/-
4,000 BITS £4 P. & P. 4/-

250 MIXED RESISTORS
½ & ¼ watt 12/6 P. & P. 1/6

DIODES EXCEPT SILICON

10 AMP 150 PIV 4 for 10/-
20 AMP 150 PIV 4 for £1
35 AMP 450 PIV 4 for 45/- P. & P. 1/-

EXTRACTOR / BLOWER FANS (Papst)

100 c.f.m. 4½" x 4½" x 2"
2800 r.p.m.
50/- ea. P. & P. 5/-



RELAY OFFER

Single pole changeover silver contacts
2" x 6" x 7" 2.5 KΩ coil operates on
25 to 50v 8 for 10/- P. & P. 1/6

PYE CAR RADIO

Push Button Tuning Heart

This PRESTOLOCK 5station Push-Button Tuner Heart with Manual Over-ride is an ideal basis for a quality AM car radio. Size 6½in. x 4in. x 2in. 25/- plus 3/- p. & p.



BUMPER BARGAIN PARCEL

We guarantee that this parcel contains at least 1,750 components. Short-leaded on panels, including a minimum of 350 transistors (mainly NPN & PNP germanium, audio and switching types—data supplied). The rest of the parcel is made up with: Resistors 5% or better (including some 1%) mainly metal oxide, carbon film, and composition types. Mainly ½ & ¼ watt diodes, miniature silicon types OA90, OA91, OA95, 1S130, etc. capacitors including tantalum, electrolytics, ceramics & polyester inductors, a selection of valves, also the odd transformer, trimpot, etc., etc. These are all miniature, up to date, professional, top quality components. Don't miss this, one of our best offers yet!! Price, 65/- Post and Packing 6/6d U.K. New Zealand 20/- post and packing. Limited stocks only.

150 HIGH STABS ½, ¼ and 1 Watt
5% and Better 12/6d. P. & P. 1/6

LARGE CAPACITY ELECTROLYTICS

1500 Mfd 150v
4000 Mfd 72v
16000 Mfd 12v

RIPPLE CURRENT

7/6 each
P. & P. 1/6d.

EXTENSION TELEPHONES

19/6 Ea. P. & P. 5/-
35/- for 2 P. & P. 10/-



These phones are extensions and do not contain bells.

MAILING ADDRESS

52 EARLS COURT ROAD, LONDON W8
WAREHOUSE & DISPATCH
01 478 8499

KEYTRONICS

AUDIOSCAN-HI-FI loudspeaker systems for the home constructor, cabinet kits, new range of Peerless speakers, speaker kit systems and cross-over networks, BAF wadding and all necessary components. Free speaker fabric samples on request. Send 9d in stamps to: AUDIOSCAN, Dept. P.W., 4 Princes Square, Harrogate, Yorks.

A CORNUCOPIA OF COMPONENTS! Scarce valve, selected T.V. components, Speakers, Cabinets, Computer panels—long leads NOT printed circuits. Transistors, resistors—new and recovered. State requirements. S.A.E. (F.S.) for details. MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.


MAINS POWER PACKS suitable for transistor amplifiers. 240 AC input. Nominal 24V DC, 350 MA out. 35/- plus 3/6 p.p. C.W.O., V.S. Audio, 44A High Road, Swaythling, Southampton.

BRAND NEW ELECTROLYTICS. 15/16V, 0.5, 1, 2, 5, 8, 10, 20, 30, 40, 50, 100 mfd, 8-5d. E12 series 5% resistors. Carbon Film ¼W 10Ω to 1MΩ, 1-5d. Wirewound 5W 15Ω to 15KΩ, 10d., postage 1/- The C. R. Supply Co., 127 Chesterfield Road, Sheffield 8.

EMSAC FOR ANTENNA SYSTEMS AND CONVERTERS. Please send s.a.e. for details of 2 metre converters, antennas and transmatchers for receiving and transmitting. ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD., Highfield House, West Kingsdown, Kent. Tel. W.K. 2344.

COMMUNICATIONS RECEIVERS: Ex-Govt. bargains in the £10 to £20 range, including: R209, PCR2, CR300, B40, B41, Murphy HF/MF, and others. Write or phone for details. P. R. GOLLEDGE, G3EDW, Glen Tor, Torrington, Devon. 08-052 2411.

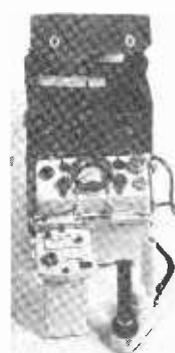GIEGER COUNTERS LATEST GOVERNMENT RELEASE OF THESE EXCEEDINGLY POPULAR AND WELL KNOWN CONTAMINATION METERS. Which were intended for use, should the need arise, by the Civil Defence etc.



These are new or virtually as new, being self stored only, and are complete with all parts including, Carrying Haversack, Cable and Probe, Instructions for use.

This Model incorporates a plug in Vibrator Power unit, instead of the normal Battery Holder, thereby using four standard Mallory R.M.12.R. Long Life Batteries. (Not supplied.)

The unit is completely portable, being made in Cast Aluminium, making it extremely light and strong. Every part is completely sealed and watertight. List Price £70.

SUPPLIED AS ABOVE IN MAKER'S CARTON COMPLETE AND TESTED 90/- POST 10/-, TWO CARRIAGE PAID.

J. H. TOWNEND

21 THE ROUNDWAY, MORLEY,
NR. LEEDS, YORKS.

dalyne Bargain Corner

Components you want—when you want them

Electrolytics		Electrolytics	
by General Instruments:		by G.C.L.:	
2µF 16V 8d	25µF 12V 10d	1500µF 25V 3/6	
10µF 12V 10d	40µF 12V 10d	470µF 63V 6/-	
20µF 6V 10d	150µF 15V 1/8	8µF 450V 2/6	
200µF 15V 10d	200µF 25V 2/-	32µF 250V 2/6	

TRANSISTORS

2N3702 3/- MJ481 55/6 BC125 9/- 2N3055 13/-
2N3703 3/- MJ491 28/9 BC126 9/- 2N706 2/9
2N3704 3/3 40361 12/- BC108 2/6 2N2926 4/-
BC169 2/8 40362 14/- BC109 2/8 BFY51 4/-
Rectifiers, wire ended (PIV stated) Zeners 5% 400mW
100V 0.75A 1/9 100V 1A 2/3 all preferred values
400V 1A 3/- 1000V 1.5A 4/6 3V to 30V 4/- each
200V 1A bridge 10/-
Volume controls lin or log: mono 2/6; stereo 8/- All preferred values in series 4.7, 10, 22, 47 etc.:-4.7KΩ to 2.2MΩ.

Terms: 10 or more of each item: *Induct* 20%
P. & P. on all orders 2/-; Postal services, U.K. only.
Prompt service and satisfaction guaranteed

dalyne components

Gayton Road,
Blisworth,
Northants.

AERIALS

BAKER AND BAINES

BBC dipole 30/- H 42/- 3 ele 89/- ITA 3 ele 26/- 5 ele 34/- 8 ele 47/5. 11 ele 57/6. ITA doubles 8 ele 112/- 11 ele 140/- 13 ele 159/- Combined BBC/ITA D+5 45/- D+8 52/- H+5 69/- X+5 75/- Combined Loft Special D+5 with loft pole and fixings 37/- UHF Aerials BBC-ITA 14 ele 37/- 18 ele 54/- 22 ele 63/- Doubles 22 ele 142/- CO-AX low loss at 1/3 and 2/3. Co-Ax plugs 1/4.
Diplexers—Triplexers—Matched UHF/UHF Diplexers—VHF/UHF Pre Amps 75/- Poles, Lashings, Clamps, Couplers, etc. Postage Paid inland on aerials. Extra on accessories. Please state channels when ordering.
11 Dale Cres., Tupton, Chesterfield.

HI-FI EQUIPMENT

SHURE Cartridges Post Free. M3D £4.19.6. M44/5/7 £7.10.0. M44E £8.17.6. M55E £9.17.6. M75E £2 £16.10.0. GOLDRING G 800 £7.17.6. Garrard SP 25 Mk. II £10.17.6. AP 75 £16.17.6. Teleton SAQ 203E £19.15.0. P.&P. 7/6. Ultimate Electronics, 38 Achilles Road, London, N.W.6. Mail Order Only.

ELECTRICAL

240 volt ELECTRICITY ANYWHERE



BEST EVER 200/240 VOLTS "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY

Exclusive World Scoop Purchase. The fabulous Mk. 12D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere.

Brand New and Fully Tested, only £59.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.

Dept. PW, SCIENTIFIC PRODUCTS
Mount Street, Fleetwood.


Est. 1943 **JOHNSONS** Tel: 24864

New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

JOHNSON'S (RADIO)

St. Martin's Gate, Worcester

DIMMASWITCH

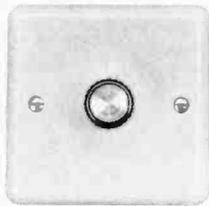

This is a dimmer of standard size in ivory and chrome to replace modern light switches without wiring change—controls 40-600 watts, 200/250 volts at 50HZ of all lights except fluorescents.

Two models are available with on/off switch to control from maximum to zero.

DS500/2 at £3 12s. 6d. with clockwise or reverse dimming, with the switch at full reverse rotation.

DS500/2/P at £3 18s. uses a patented switch giving on/off control at any position of dimming.

Both are available in D.I.Y. kit form at 10/- less. Fuse protection is available at 2/6 extra.

Please send C.W.O. to

DEXTER & COMPANY
ULVER HOUSE, 19 KING STREET
CHESTER CH1 2AH
Tel.: Chester 25883

As supplied to H.M. Government Departments, Hospitals, Local Authorities, etc.

AUDIO EFFECTS

5 SHAW LANE, HALIFAX YORKS

Buy with confidence and obtain the right results. Refunds without question if any of our Products fail to give 100% satisfaction.

AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT. No fuss, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front Panel. Push pull AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco plug in coils 2T. 0.5 to 1.54 Mhz 3T. 1.67 to 5.3 Mhz 4T. 5.0 to 15 Mhz 5T. 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 9 volt battery. Easy step by step instructions. Complete Kit. £8.19.6 plus 5/6 P. P. & Ins. Extra ranges 12/- per range.

POWER CONTROLLER. Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3kW triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions £6.9.6. Ready built £9.4.6 plus 5/6 P. P. & Ins. **REVERBERATION AMPLIFIER.** Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, effects, are created with a truly third dimension for added realism. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2 in x 3 in x 4 1/2 in. £10.4.0 plus 6/- P. P. & Ins.

VOX SWITCH. This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions £42/6. Ready built, tested and guaranteed. £2/6, plus 2/6 P. P. **METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive black and white polythene case, 37/6 post paid.

MORSE OSCILLATOR. PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 25/- post paid.

STRAIGHT FROM THE PRESS. Latest Mullard manual: Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi Tape, etc. etc. 32/6 post paid. **JUST ARRIVED IN STOCK.** Texas transistors. Complementary symmetry. Driver. NPN, PNP output. The set of three ONLY 6/6 post paid.

Free lists with every order. For lists only send 1/6 (deductible from first order).

NEW VALVES!

Guaranteed and Tested
24-HOUR SERVICE

1K5	5/8	DL92	5/8	EL84	4/9	PL500	12/9
1S5	4/3	DL94	5/9	EY61	7/-	PL504	13/3
1T4	2/9	DL96	7/-	EY86	6/3	PY32	10/-
2S4	5/8	DY86	5/3	EZ80	4/3	PY33	10/-
3A4	5/9	DY87	5/3	EZ81	4/6	PY81	5/-
6J0L2	11/6	EABC80	5/9	KT61	9/3	PY82	5/-
6AQ5	4/3	EB323	7/9	KT66	16/6	PY83	5/6
6V6G	3/-	EB341	9/3	N78	17/-	PY88	6/6
25L6GT	4/6	EB180	6/6	PC86	10/3	PY800	7/-
30C18	10/8	EBF89	5/9	PC88	10/3	PY801	6/9
30PL1	12/6	EC081	3/6	PC97	7/9	R19	6/3
30RL12	14/3	EC082	4/6	PC900	7/-	U23	12/9
30L15	12/9	EC083	4/9	PC084	6/3	U26	11/6
30P4	11/9	EC085	5/-	PC089	8/11	U191	12/-
30P19	11/9	EC135	5/6	PCF80	5/11	U193	8/6
30PL1	12/6	ECH81	5/9	PCF801	6/6	U251	14/-
6CH185	12/-	ECL80	6/6	PCF802	8/9	U329	14/-
CL33	17/6	ECL82	6/3	PCF805	10/9	UABC80	6/-
DAC32	6/9	ECL86	7/6	PCL82	6/9	UBC41	8/3
DAF91	4/3	EF37A	6/-	PCL83	11/9	UBF89	6/3
DAF96	6/8	EF39	4/6	PCL84	7/-	UC085	7/3
DF33	7/6	EF80	4/6	PCL85	8/6	UCH81	6/6
DF91	2/9	EF85	5/9	PCL96	8/-	UCL82	8/9
DF96	6/9	EF86	6/3	PCL901	11/6	UF41	10/6
DK32	6/9	EF89	4/9	PL36	9/3	UF89	6/-
DK91	5/6	EF183	5/6	PL81	8/6	UL41	11/9
DK92	8/3	EF184	6/-	PL82	5/9	UL84	6/3
DK96	7/3	EH90	8/-	PL83	6/3	UY41	7/-
DL35	4/9	EL33	9/3	PL84	6/-	UY85	5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any insured parcel against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials new fitted with tilting bracket and 4 element grid reflectors.
Loft Mounting Arrays, 7 element, 40/-, 11 element, 47/6. 14 element, 55/-, 18 element, 62/6. Wall Mounting with Cranked Arm, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. Mast Mounting with Zin. clamp, 7 element, 42/6. 11 element, 55/-, 14 element, 62/-, 18 element, 70/-, Chimney Mounting Arrays, Complete, 7 element, 72/6. 11 element, 80/-, 14 element, 87/6. 18 element, 95/-, Complete assembly instructions with every unit. Low Loss Cable, 1/6 yd. U.H.F. Preamps from 75/-, State clearly channel number required on all orders.

BBC - ITV AERIALS



BBC (Band 1). Loft, 25/-, External S/D, 30/-, "H" £215.0. ITV (Band 3). 3 element loft array, 30/-, 5 element, 40/-, 7 element, 50/-, Wall mounting, 3 element, 50/-, 5 element, 55/-, Combined BBC/ITV, Loft 1 + 3, 40/-; 1 + 5, 50/-; 1 + 7, 60/-; Wall mounting 1 + 3, 60/-; 1 + 5, 70/-; Chimney 1 + 3, 70/-; 1 + 5, 80/-, VHF transistor Pre-amps. 75/-


COMBINED BBC - ITV - BBC2 AERIALS 1 + 3 + 9, 70/-, 1 + 5 + 9, 80/-, 1 + 5 + 14, 90/-, 1 + 7 + 14, 100/-, Loft mounting only. F.M. (Band 2). Loft S/D, 17/6. "H", 35/-, 3 element, 57/6. External units available. Co-ax. cable 8d. yd. Co-ax. plugs, 1/6. Outlet boxes, 5/-, Diplexer Crossover Boxes, 17/6. C.W.O. or C.O.D. P. & P. 6/6. Send 6d. stamps for illustrated lists.

Callers welcomed — open all day Saturday

K.V.A. ELECTRONICS (Dept. P.W.)
40-41 MONARCH PARADE
LONDON ROAD, MITCHAM,
SURREY 01-648 8884

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

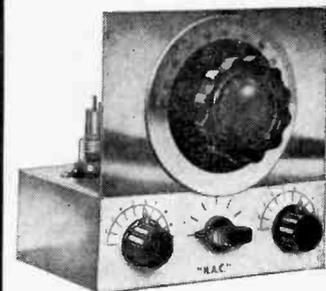

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1970 RANGE

One-valve model "DX", complete kit—price 58/6 (Postage and packing 3/6).

Customer writes:—"Definitely the best one-valve S.W. Kit available at any price. America and Australia received clearly at good volume." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only). Send now for a descriptive catalogue, order form.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117)	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	5/7
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117)	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	6/-
Rod Aerial	RA2W		12/6
Driver Transformer	LFDT4/1		9/6
Output Transformer	OPT1		10/6
Printed Circuit	PCA1		9/6

I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	7/6
T41/2E	2nd I.F. Transformer	7/6
T41/3T	3rd I.F. Transformer	10/6
T41/3T	B.F.O. Coil	10/6

Details of these and our other components are given in an illustrated folder which will be supplied on request with 4d. postage please.

WEYRAD (ELECTRONICS) LIMITED

SCHOOL STREET, WEYMOUTH, DORSET

M. & B. RADIO

38 BRIDGE END, LEEDS 1

Telephone: 0532-35649

VHF FM/MW/LW TRANSISTOR RADIO BRAND NEW 10 transistor plus 4 diode table model of well known British manufacture. The highly polished wood cabinet, speaker and pre-assembled chassis are supplied separate and only require fitting together and the 2 speaker connections making. CHASSIS & CABINET £9.10.0. SPEAKER 25/- carr. paid.



STC STEREO/MONO HEADPHONES. Brand new lightweight high quality comfortable padded headphones for stereo or mono use. Weight 10 oz. 20 c/s to 20 Kc/s 300 ohms per earpiece. Supplied with details of matching circuit for 15 ohms using only 3 resistors. 54/- plus 4/- pp.

12 VOLT TRANSISTOR INVERTERS. 12vdc input. 270vdc at 150mA approx output. Transformer 2in x 2in x 1 1/2in mounted on aluminium case 1 1/2in x 2 1/2in x 4in. Weight 15oz. 65/- plus 4/- pp.

TRANSISTOR MODULATOR PRE-AMP PANEL. BRAND NEW 4 transistors plus 1 diode. 4 1/2in x 2 1/2in. Fitted with pre-set microphone gain control and mod filter. Originally used to drive an NKT404 which drove a pair of NKT404s. Supplied brand new c/w circuit of complete modulator. 22/6d plus 1/6 pp.

TRANSISTOR AUDIO AND MUTING PANELS. Brand new set of 3 panels. Audio panel with transistor gate originally used to drive an NKT404 output transistor. 2 muting panels with Schmitt trigger circuit to operate the gate on the audio panel. 8 transistors in all. Supplied with full circuit 22/6d plus 2/6 pp.

455Kc/s FM I.F. PANEL. Brand new but faulty 6 transistor panel usually low in gain. 12/6 plus 1/6 pp.

HAND TELEPHONES. Brand new radiotelephone type press to talk handsets. 12/6 plus 1/6 pp.

VHF AERIAL C/O RELAYS. Used but OK. 6 or 12v. 4/- plus 1/6 pp.
60 UNTESTED MIXED TRANSISTORS 5/- plus 1/- pp.
60 UNTESTED MIXED DIODES 2/6 plus 1/- pp.

USED TESTED VALVES. 12AX7/ECC83 2/6. 6BJ6 1/6. 6AQ5/EL90 2/6. ECF80 2/- 6AT6 1/6.

ALSO VARIOUS VHF EQUIPMENT IN STOCK
S.A.E. AND 6d. STAMP FOR LISTS

EX-RENTAL TELEVISIONS

TWO-YEAR GUARANTEE

17" SLIMLINE 405 only

£11 10 0

19" SLIMLINE 405/625

39 Gns.


Carriage and Insurance 30/-

FREE ILLUSTRATED LIST OF TELEVISIONS

17"-19"-21"-23"

WIDE RANGE OF MODELS, SIZES AND PRICES

DEMONSTRATIONS DAILY

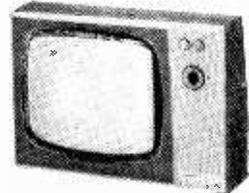

TWO-YEAR GUARANTEED TUBES 100% REGUNNED

Slim Line Tubes 110° 17" and 19" 109/6, 21" and 23" 129/6.

Normal Tubes 70° and 90° 17" 99/6, 21" 119/6, 14" and other sizes 79/6.

SPEAKERS 10/-, 2 1/2" 8Ω, 3 1/2" 25Ω, 4" 10Ω, 3" x 5" 8Ω, 7" x 4" 3Ω, 8" x 3" 3Ω. BRAND NEW. P. & P. 2/-.

RECORD PLAYER CABINET 49/6

Transistors: Mullard matched output kit 7/6, OC81D-2 OC81's. P. & P. FREE.

Transistor Radio Cases: 4 for £1. Size 9 1/2" x 6 1/2" x 3 1/2". P. & P. 9/6.

Ferrite Rods 3/6: 6" and 8" complete with LW/MW Coils. P. & P. FREE.

STRIP LIGHT TUBES 3/9 each. 11" (284mm). 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting, etc. 6 for £1. P. & P. free.



Cloth covered. Size 16 1/2" x 14 1/2" x 7 1/2". Takes any modern auto-changer. P. & P. 7/6.

(DUKE & CO. LONDON) LTD.

£21/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel. PARK 5841/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office
When sending cash with order, please include 2/6 in £ for postage and handling
MINIMUM CHARGE 2/6. No C.O.D. orders accepted
PLEASE NOTE THAT THE VALUES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel. LANGHAM 8403
Open all day Saturday

OA2 6/8		6AU6 5/		6F18 8/		10F9 10/		E812 10/		E813 10/		E814 10/		E1000 10/	
6A2	6/8	6A6	5/	6F18	8/	10F9	10/	E812	10/	E813	10/	E814	10/	E1000	10/

First Quality Fully Guaranteed



ELECTRONIC VALVES

30C15 15/-		811A 30/-		DY70 12/-		ECP86 12/8		E812 10/		E813 10/		E814 10/		E999 10/		E1000 10/	
30C15	15/-	811A	30/-	DY70	12/-	ECP86	12/8	E812	10/	E813	10/	E814	10/	E923	10/	E924	10/																																																																																																																																																								

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had *your* copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

**On 'SATISFACTION or
REFUND of FEE' terms**

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

**WHICH OF THESE IS
YOUR PET SUBJECT?**

RADIO ENGINEERING
Advanced Radio — Gen.
Radio — Radio & TV
Servicing — TV Eng. —
Telecommunications — Sound
Recording — Automation —
Practical Radio — Radio
Amateurs' Exam.

ELECTRICAL ENG.
Advanced Electrical Eng. —
Gen. Electrical Eng. —
Installations — Draughts-
manship — Illuminating Eng. —
Refrigeration — Elem.
Electrical Science — Electrical
Supply — Mining Elec.
Engineering.

CIVIL ENGINEERING
Advanced Civil Eng. — Gen.
Civil Eng. — Municipal
Eng. — Structural Eng. —
Sanitary Eng. — Road Eng. —
Hydraulics — Mining —
Water Supply — Petrol Tech.

ELECTRONIC ENG.
Advanced Electronic Eng. —
Gen. Electronic Eng. —
Applied Electronics — Prac.
Electronics — Radar Tech. —
Frequency Modulation —
Transistors.

MECHANICAL ENG.
Advanced Mechanical Eng. —
Gen. Mechanical Eng. —
Maintenance Eng. — Diesel
Eng. — Press Tool Design —
Sheet Metal Work — Welding
— Eng. Pattern Making —
Inspection — Draughtsman-
ship — Metallurgy — Pro-
duction Eng.

AUTOMOBILE ENG.
Advanced Automobile Eng. —
Gen. Automobile Eng. —
Automobile Maintenance —
Repair — Automobile Diesel
Maintenance — Automobile
Elec. Equipment — Garage
Management.

**"WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS IN-
CLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRU-
MENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.**

Which qualification would increase your earning power?
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B.,
A.M.I.P.E., A.M.I.M.I.L., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S.,
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT.
OF EDUCATION, ETC.

British Institute of Engineering Technology
453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT
CAREER - GUIDANCE

**PRACTICAL
EQUIPMENT**

Basic Practical and Theoretic Course for beginners in Radio, T.V., Electronics, Etc A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

**INCLUDING
TOOLS**

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy *now*—FREE and without obligation.



POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS


WRITE IF YOU PREFER NOT TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

HENRY'S RADIO LTD. ENGLAND'S LEADING COMPONENT AND EQUIPMENT CENTRES

COMPLETE STEREO SYSTEM FOR £39-10-0

HENELEC 5-5 STEREO AMPLIFIER. Inputs for ceramic cartridge. Aux/Tuner. Output for 8 to 15 ohms speakers. Silver with black and wood finish. British made. Size 12½ x 3½ x 6½. Fitted headphone socket. Complete system comprises 5-5 amplifier, Garrard 3000 or model 50 with 9TAHC diamond cartridge. Pair E.M.I. 10watt speakers, twin tweeters and crossover with polished wood cabinets 18" x 11" x 7". Also plinth and cover.

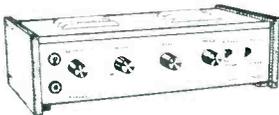

- COMPLETE STEREO SYSTEM (Rec. Price £50), £39-10-0 p.p. 20/-
- AMPLIFIER ONLY £13-19-6, p.p. 7/6
- DHO2S RECOMMENDED STEREO PHONES 45/-

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

PARTS TOTAL COST £6.19.6, p.p. 3/6
DECODER £5.19.6, (FOR STEREO) p.p. 3/-
ASK FOR BROCHURE No. 3.



New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.

BUILD YOURSELF A QUALITY RADIO



Total cost £6.19.6, p.p. 6/6

Ask for Leaflet No. 1.

SINCLAIR EQUIPMENT

Z30 75/- each, stereo 60 £8-10-0, PZ5 79/6,
PZ6 £6-19-6, Z50 £5-9-6, PZ8 £5-19-6.

SPECIAL OFFER

2 of Z30, stereo 60, PZ5 (usually £23-10) or with PZ6 in place of PZ5 £21

£19

Complete range of amplifiers and preamplifiers in stock. All detailed in catalogue above.

TEST EQUIPMENT FOR YOUR HOME




AF105 50k/v multimeter (illus.), price £8-10, p.p. 3/6, leather case 28/6
200M 20k/v multimeter price £3-17-6, p.p. 3/-, case 12/6
TE20D RF Generator (illus.), price £15, p.p. 7/6
TE22D Matching Audio Generator, price £17, p.p. 17/6
TE65 Valve Voltmeter, price £17-10-0, p.p. 7/6
Full details and complete range in catalogue



HENRY'S STOCK EVERY TYPE OF COMPONENT YOU NEED. A CATALOGUE IS A MUST!

Hi-Fi equipment to suit EVERY POCKET

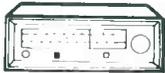

FREE

Stock List No. 16/17 on request

Choose from 100 complete stereo systems—Complete range of individual units also in stock. Demonstrations all day.

100 STEREO SYSTEMS

LOW CASH AND CREDIT/HP PRICES (Credit terms from £30 purchase-callers only).



HENRY'S LATEST CATALOGUE

New print. Now 350 pages. ★Components ★Equipment ★Special offers ★Testgear ★Modules
—Everything for the constructor
Complete with 10/- value discount voucher for use with purchase. Price 7/6, p.p. 2/-



WHY NOT SEND AWAY TODAY?


25watt and 50watt RMS SILICON AMPLIFIERS

LOOK AT THE SPECIFICATIONS!

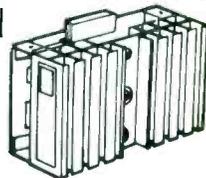- 0.3% Distortion at full power
- -1db 11c/s to 40kc/s at full power
- Response -1db 11c/s to 100kc/s

PA2510 Silicon Thristors Differential input, 25watts rms into Bohms, 700mV input. Size only 5" x 3" x 2". 4-hole fixing. Supplied with edge connector and harness.

PA50 12-Transistor Version, 50watt rms into 3 to 4ohms
MU442 Power supply for one or two PA25 or one PA50
● PA25 £7-10-0. ● PA50 £9-10-0. ● MU442 £6



NO SOLDERING—JUST PLUG CONNECTORS


YOU CAN SAVE 25% With brand new GARRARD units (Post ext. 7/6)

SP25mkII £11-9-6, AP75 £16-19-6, SL65B £14-19-6, SL72B £25 A70mkII £11-19-6

SPECIAL OFFER Above with Sonocone 9talc diam. Add £2, with magnetic add 70/-, with Goldring G800 add £8-10-0

Also fitted with 9talc diamond model 50 £8-10-0, 3000LM1 £9-15-0
Plinths/Covers: Standard 99/6, p.p. 4/6, De luxe £8-10-0, p.p. 6/-, SL72B type £8-10-0, p.p. 6/-, Not for A70

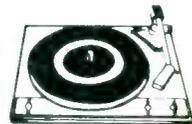
● Goldring GL69 with plinth and cover and G800 cartridge (usually £51) £39.10.0, p.p. 12/6.



SCOOP New ¼" TRACK TAPE DECKS


British made 3 speed mains operated tape machine. Fitted Marriot XRP517 and XES11 ¼ track heads. Piano key operation. Designed for the home constructor. Operates with up to 7" spools vertically or horizontally. Size 13" x 10" x 5½".

PRICE £13-19-6, p.p. 10/6

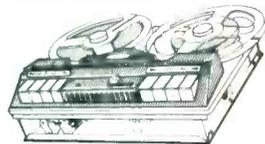

ELECTRONIC ORGANS

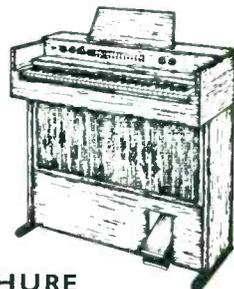- ★ MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT
- ★ TEAK VENEERED CABINETS FOR ALL MODELS
- ★ 49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE
- ★ KITS AVAILABLE IN SECTIONS AS REQUIRED
- ★ HP and CREDIT SALE FACILITIES
- ★ **FREE 16-PAGE BROCHURE**



Covering organs in kit form and ready built—write or phone to ORGAN DEPT. Ask for Peter Elvins.

HENRY'S RADIO LTD.

Mail Order Dept, Electronic Components and Equipment, and Electronic Organ Dept.
303 EDGWARE ROAD, LONDON W2.
Telephone: 01-723 1008/9
Open Mon-Sat. 9am-6pm, Thurs. 9am-1pm

High Fidelity and Audio Centre
309 EDGWARE ROAD, LONDON W2.
Telephone: 01-723 6963
Open all day Saturday.