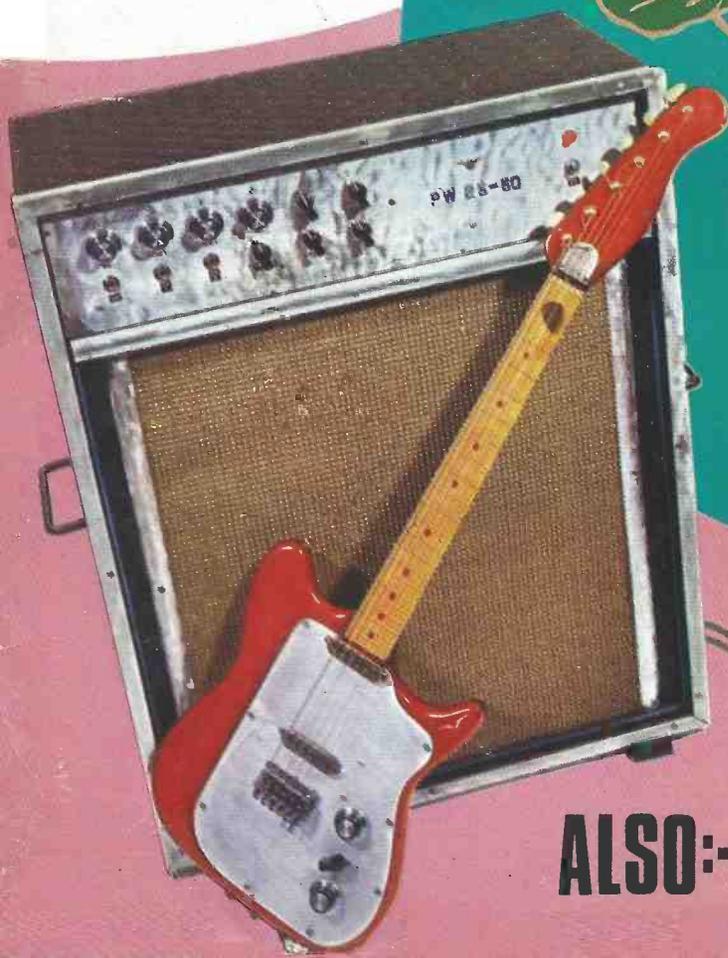


# PRACTICAL WIRELESS

SEPTEMBER  
1970

316

**PW**  
**VIBRASONIC**  
**25-50**  
**GUITAR**  
**AMPLIFIER**



**ALSO:-** ORGAN PEDAL BASS UNIT  
LOW BAND VHF CONVERTER

# ADCOLA Soldering Instruments add to your efficiency

## ADCOLA 64 for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

\*Additional Stock Bits (illustrated) available

### COPPER

- B 38**  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE
- B 14**  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE
- B 24**  $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE
- B 12**  $\frac{1}{8}$ " — 4.75 mm EVELET BIT
- B 58**  $\frac{1}{4}$ " — 6.34 mm CHISEL FACE

### LONG LIFE


- B 42 LL**  $\frac{1}{8}$ " — 4.75 mm CHISEL FACE
- B 38 LL**  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE
- B 14 LL**  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE
- B 44 LL**  $\frac{3}{16}$ " — 4.75 mm SCREWDRIVER FACE

Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



\* Write for price list and catalogue

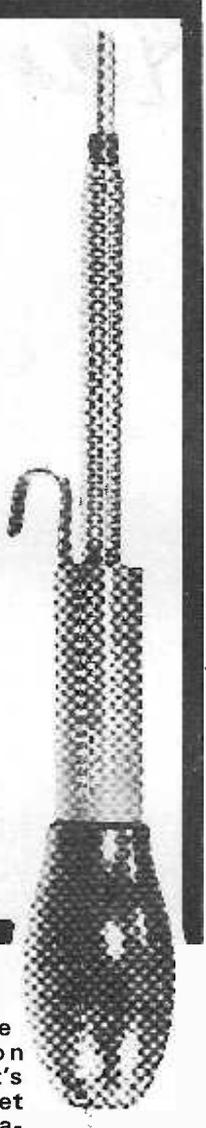**ADCOLA PRODUCTS LTD.,**  
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851



## SEMICONDUCTORS

BRAND NEW AND FULLY GUARANTEED

1N914 1/6	2N2923 3/6	AD162 7/6	BD182 19/6	MPP102 8/6
1N916 1/6	2N2924 3/6	AF114 5/-	BD142 19/6	MPP103 7/6
18021 4/-	2N2925 3/6	AF116 5/-	BF115 5/6	MPP104 7/6
18025 5/-	2N2926 3/6	AF117 5/-	BF117 5/6	MPP105 7/6
18113 3/6	" Green 3/6	AF118 12/6	BF195 5/6	NKT101 4/-
18120 2/6	" Yellow 2/6	AF124 4/6	BF173 6/6	NKT216 7/6
18121 2/6	" Orange 2/6	AF125 4/6	BF180 7/6	NKT217 8/6
18130 2/6	2N3011 6/-	AF126 4/6	BF181 6/6	NKT261 4/-
18131 2/6	2N3053 5/6	AF127 3/6	BF184 6/6	NKT262 4/6
18132 2/6	2N3054 11/-	AF139 7/6	BF194 4/6	NKT264 4/-
1844 2/-	2N3055 15/-	AF131 6/6	BF195 4/6	NKT271 4/-
18920 2/-	2N3702 3/6	AF186 9/6	BF197 3/6	NKT272 4/6
2G301 4/-	2N3703 4/6	AF239 8/6	BF244 9/6	NKT274 4/-
2G302 4/-	2N3704 4/6	ASY26 5/6	BFN61 13/6	NKT275 4/6
2G303 4/-	2N3705 4/6	ASY27 7/6	BFX13 4/6	NKT281 5/6
2G308 6/6	2N3706 4/6	ASY28 5/6	BFX29 8/6	NKT403 15/6
2G371 3/6	2N3707 4/6	ASY29 5/6	BFX30 9/6	NKT404 15/6
2N596 4/6	2N3708 3/6	ASY20 7/6	BFX35 19/6	NKT405 15/6
2N697 4/6	2N3709 3/6	ASZ21 8/6	BFX43 7/6	NKT613 6/6
2N698 5/6	2N3710 4/6	BA102 6/6	BFX44 7/6	NKT674 5/6
2N706 2/6	2N3711 4/6	BAX13 1/6	BFX84 6/6	NKT677 5/6
2N706A 2/6	2N3819 1/6	BAX16 1/6	BFX85 7/6	NKT713 5/6
2N708 3/6	2N3820 19/6	BAY31 1/6	BFX86 6/6	NKT773 5/6
2N709 5/6	2N3908 1/6	BCY38 6/6	BFY87 6/6	NKT801 8/6
2N1131 5/6	2N4058 5/6	BC107 3/6	BFX88 5/6	NKT20329 8/6
2N1132 6/6	2N4059 5/6	BC108 3/6	BFY43 12/6	NKT8011115 6/6
2N1302 3/6	2N4060 5/6	BC109 3/6	BFY50 4/6	NKT8011219 6/6
2N1303 3/6	2N4061 4/6	BC113 5/6	BFY51 4/6	NKT8011322 6/6
2N1304 4/6	2N4062 4/6	BC116 7/6	BFY52 4/6	OA5 3/6
2N1305 4/6	2N4284 3/6	BC118 6/6	BFY76 6/6	OA9 2/6
2N1306 5/6	2N4285 3/6	BC125 11/6	BFY90 18/6	OA70 1/6
2N1307 5/6	2N4286 3/6	BC126 11/6	BSX19 3/6	OA73 1/6
2N1308 6/6	2N4287 3/6	BC147 3/6	BSX20 3/6	OA79 1/6
2N1309 6/6	2N4288 3/6	BC148 3/6	BSX21 7/6	OA81 1/6
2N1507 5/6	2N4289 3/6	BC149 3/6	BSX26 9/6	OA85 1/6
2N1613 5/6	2N4291 3/6	BC157 3/6	BSX27 9/6	OA90 2/6
2N1711 5/6	2N4292 3/6	BC168B 3/6	BSX28 6/6	OA91 1/6
2N1889 6/6	40361 12/6	BC168C 3/6	BSY29 13/6	OA95 1/6
2N1893 8/6	40362 13/6	BC169B 2/6	BSY26 3/6	OA200 2/6
2N2102 14/6	3N128 18/6	BC169C 3/6	BSY27 3/6	OA202 2/6
2N2147 14/6	3N140 19/6	BC182L 4/6	BSY28 3/6	OC26 6/6
2N2148 12/6	3N142 19/6	BC121L 4/6	BSY29 3/6	OC28 6/6
2N2160 11/6	3N142 19/6	BCY30 5/6	BSY38 4/6	OC29 15/6
2N2193 9/6	AAZ13 2/6	BCY31 5/6	BSY39 4/6	OC35 8/6
2N2194A 4/6	AAZ15 2/6	BCY32 7/6	BSY40 6/6	OC36 12/6
2N2217 5/6	AAZ17 2/6	BCY33 4/6	BSY51 6/6	OC44 4/6
2N2218 6/6	AC107 6/6	BCY34 4/6	BSY52 6/6	OC45 2/6
2N2219 6/6	AC121 4/6	BCY38 4/6	BSY53 7/6	OC71 2/6
2N2220 5/6	AC127 5/6	BCY39 3/6	BSY54 8/6	OC72 2/6
2N2221 5/6	AC128 4/6	BCY40 7/6	BSY95A 2/6	OC75 4/6
2N2222 6/6	AC176 5/6	BCY42 3/6	BX100 4/6	OC81 4/6
2N2368 3/6	AC187 12/6	BCY43 3/6	BX110 5/6	OC83 5/6
2N2369 3/6	AC188 12/6	BCY54 6/6	BX120 9/6	OC84 4/6
2N2369A 4/6	AC17 4/6	BCY70 4/6	BX121 7/6	OC87 4/6
2N2395 4/6	ACY18 5/6	BCY71 3/6	BX122 6/6	OC139 6/6
2N2540 4/6	ACY19 5/6	BCY72 3/6	BX123 5/6	OC140 6/6
2N2646 11/6	ACY20 5/6	BDY20 22/6	MJ480 19/6	OC200 6/6
2N2904 7/6	ACY21 5/6	BD116 22/6	MJ481 25/6	OC201 9/6
2N2904A 8/6	ACY22 4/6	BD121 13/6	MJ490 20/6	OC202 12/6
2N2905 8/6	ACY23 4/6	BD123 13/6	MJ491 20/6	OC203 12/6
2N2905A 8/6	AD140 8/6	BD124 12/6	MJE520 17/6	ORP12 12/6
2N2906 6/6	AD149 11/6	BD181 19/6	MJE521 17/6	ORP61 10/6
2N2906A 6/6	AD161 7/6			

### PLESSEY INTEGRATED CIRCUITS

8L402A 42/6  
8L403A 42/6  
Data Sheets 2/-

### MULLARD LINEAR I.C.s.

TAA241 32/6  
TAA242 35/6  
TAA243 30/6  
TAA263 15/6  
TAA293 19/6  
TAA300 35/6  
TAA310 25/6  
TAA320 14/6  
TAA350 35/6  
TAA435 29/6  
TAA521 22/6  
TAA522 72/6  
TAA811 89/6  
TAB101 19/6  
TAD100 39/6  
TAD110 39/6  
Data Sheets 1/-  
(Free with I.C.s.)  
Also most Mullard Logics in stock.

**Heatsinks**  
TO-18, TO-5, TO-1, 1/-  
PINNED FOR ONE 8/6  
TO-3 6/6  
PINNED FOR TWO 9/6  
TO-3 9/6

### THERMISTORS

R53 (STC) 25/6  
K151 (IK) 2/6  
Various Mullard Thermistors in stock.  
Send 2/6 for new comprehensive catalogue. P.P. for Components 1/6 per order.

### THYRISTORS

1 AMP: 50V 5/-, 100V 5/6, 200V 7/-, 400V 9/6.  
3 AMP: 50V 6/-, 100V 7/6, 200V 8/-, 400V 10/6.  
ZENERS: 1W 2.7-33V 4/6, 10W 2.7-100V 7/6, 400m/w 3.0-33V 4/6, 1 Watt 2.4V-200V 7/6.

### INTEGRATED CIRCUITS—R.C.A.

CA3005 25/6, CA3011 16/6, CA3014 27/-, CA3018 19/-, CA3019 19/-, CA3020 27/-, CA3022 27/6, CA3023 27/6, CA3024 16/6, CA3025 27/6, CA3028 27/6, CA3031 16/6, CA3041 25/-, CA3042 25/-, CA3044 27/6, CA3046 19/6, CA3048 45/-, CA3050 39/6, CA3052 36/6.  
FAIRCHILD  
L900, 914 9/6, L923 12/6, L702C 36/6, L709C 21/-, L710C 21/-, L716C 50/-.

### G.E. INTEGRATED CIRCUITS

PA230 22/6, PA234 26/6, PA237 35/-, PA246 57/6.  
Data Sheet 1/-, PA424 55/-.

Presets std, horiz. or vert.  
Potentiometers, Log/Lin 4/6  
Twin-ganged Pots Log and Lin. 7/6

MFD	V	Price	MFD	V	Price	MFD	V	Price
1	40	1/6	25	25	1/6	200	16	2/-
2	15	1/6	25	50	1/6	250	25	2/6
2	350	2/-	32	15	1/6	250	50	3/6
2-5	16	1/6	32	450	1/6	320	10	3/6
4	15	1/6	40	6-4	1/6	400	16	2/6
4	40	1/6	40	16	1/6	500	25	3/6
4	350	2/3	50	12	1/6	500	50	4/6
5	15	1/6	50	25	1/6	640	16	3/6
6-4	25	1/6	50	50	2/6	1000	25	5/6
8	18	1/6	64	25	1/6	1000	50	7/6
8	40	1/6	80	16	1/6	2000	25	8/6
8	450	3/6	100	6-4	1/6	2000	50	12/6
10	15	1/6	100	12	1/6	2500	25	9/6
12-5	25	1/6	100	25	2/6	4000	64	45/6
16	18	1/6	100	50	2/6	4000	100	47/6
25	25	1/6	125	4	1/6	5000	25	12/6
25	10	1/6	200	6-4	1/6	5000	50	19/6

### VERBOARD

15 Matrix 3/6  
1 Matrix 4/6  
2 1/2in. x 3 1/2in. 3/6  
2 1/2in. x 5in. 4/6  
2 1/2in. x 3 1/2in. 4/6  
2 1/2in. x 5in. 5/6  
2 1/2in. x 17in. 12/6  
3 1/2in. x 17in. 16/-  
Cutter 9/-, Veropins (Bag 50) 5/-

### RESISTORS

1/2 watt 5%, 5d.  
1 watt 10%, 6d.  
2.5 watt 5%, 1/6  
5 watt 5%, 2/6  
10 watt 5%, 2/6  
1/2 watt 5%, 3d.  
1 watt M.O. 2%, 1/9

## A. MARSHALL & SON

28 CRICKLEWOOD BROADWAY, LONDON N.W.2  
TELEX 21492 01-452 0161/2/3 CALLERS WELCOME  
Post & Packing U.K. only 1/6. Europe 5/-. Commonwealth (Air) 13/-

# TMK METER KITS

These meter kits by TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinet is supplied with the meter scale and movement and the range selector in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full construction, circuit and operating instructions.

## MODEL 200

Features 24 measurement ranges with mirror scale. Large 3 2in meter. Full scale accuracy: DCV and current:  $\pm 2\%$ , ACV:  $\pm 3\%$ , resistance  $\pm 3\%$ . Special 0-6V DC range for transistor circuit measurements.

### SPECIFICATION


- DCV: 0-0.6-6-30-120-600-1,200V at 20K/OPV.
- ACV: 0-6-30-120-600-1,200V at 10K/OPV.
- DC Current: 0-6-0.6-600mA.
- Resistance: 0-10-K 100K-1M-10M/ohms (58-580-5.8K-58K at mid-scale).
- Capacitance: 0.002-0.2 $\mu$ F (AC 6V range).
- Decibels -20 to +83dB.
- Output: 0.05 $\mu$ F blocking capacitor.
- Uses two 1.5V (U7 type) batteries. Black bakelite cabinet. Size 5 1/2 x 3 1/2 x 1 1/2 in. Complete with test leads.



**KIT PRICE ONLY 92/-** Post 3/6

# WHARFEDALE

## UNIT 3 SPEAKER KIT

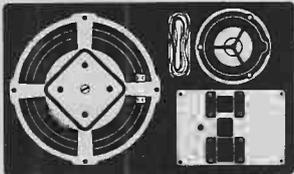

3in tweeter uses new Wharfedale "Acoustiprene" dome diaphragm. Crossover unit crossover freq. 1,750Hz. ALL accessories, acoustic wadding, mounting bolts, wire, etc., are supplied, you provide the cabinet to suit your needs. 8in. Bass/Mid. range speaker employing a powerful magnet assembly with diecast chassis and Flexiprene roll surround. The Wharfedale Unit 3 speaker kit can be constructed by anybody and with a suitable cabinet will provide a highly sophisticated system giving true Hi-Fi reproduction from 40-17,000Hz. Impedance 4/8 ohms. Max. power handling 15W.

**£11.19.6** each Post 5/- **£20** per pair Post 10/-

## UNIT 4 SPEAKER KIT

2 speakers (12in. Bass and 3in Treble) to give full range, balanced reproduction. Frequency response of 45-17,000Hz when housed in suitable cabinet. Superior 4-element crossover unit ensures optimum performance from each speaker.

**£16** each Post 5/- **£30** per pair Post 10/-

## UNIT 5 MONITOR SYSTEM KIT


3 speakers (12in Bass, 5in M.-R. unit, 1in Treble) give clean, smooth performance. Frequency response of 40-20,000Hz when housed in suitable cabinet. Unique mechanical/electrical 6 element crossover unit.

**£23.10** each Post 7/6 **£42** per pair Post 15/-

# TTC HEADPHONES
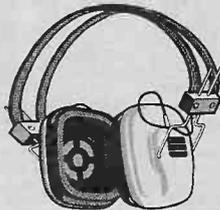
## MODEL G-III

Yet another outstanding TTC product which gives you exceptional value plus super quality. These stereo phones use two 3in low imp. high flux density dynamic reproducers. Freq. Res. 25-15,000Hz. Fitted with foam cushioned adjustable earpads for super listening comfort, imp. 8 ohms, matching 16 ohms. Max. Input 0.5W. Complete with 36in shielded grey cable. Pearl grey finish with double spring headband.



**ONLY 63/-** Post 3/6

# USA MADE CASSETTES

## AT LASKY'S BUDGET PRICES

C80 7/6 each post 1/-	35/- post 2/-	65/- post 3/-
C90 12/6 each post 1/-	57/6 post 2/-	115/- post 3/-
C120 17/6 each post 1/-	85/- post 2/-	165/- post 3/-

# Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271

33 TOTTENHAM CT. RD, LONDON, WIP 9RB. Tel: 01-636 2605

Open all day, 9 a.m.-6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812

152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

## HIGH FIDELITY AUDIO CENTRES

42-45 TOTTENHAM CT. RD, LONDON, WIP 9RD. Tel: 01-580 2573


Open all day, 9 a.m.-6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789

Open all day Saturday early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821

# EXCLUSIVE DIGITAL CLOCK SCOOP!

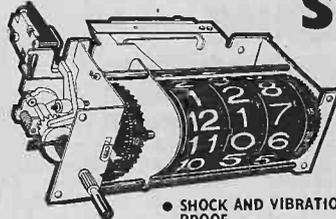

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance—radio, TV, light etc. at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning. The clock measures 4 1/2" x 1 1/2" x 3 1/2" (overall from front of drum to back of switch). SPEC: 210/240V A.C. 50Hz operation; switch rating 250V. 3A. Complete with instructions. HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS.

**LASKY'S PRICE £6.19.6** Post 3/6  
SPECIAL QUOTATIONS FOR QUANTITIES

# Audio Development



## AD-309K PRECISION PICK-UP ARM COMPLETE WITH AD-76K MAGNETIC CARTRIDGE

The new AUDIO DEVELOPMENT precision counter-balanced pick-up arm—ready fitted with the outstanding

AD-76K magnetic cartridge is constructed of brass throughout, heavily chrome plated; uses needle and miniature ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard pin, mounting centres and is finished in black enamel with chrome lifting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 7/16in dia. mounting hole.

**LASKY'S PRICE £9.19.6** POST 3/6

## AUDIO DEVELOPMENT AD-76K

Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. Tracking force: 2 gms 0.5 gm. **90/-** Post Free

## AUDIO DEVELOPMENT AD-96K

Stereo Magnetic Cartridge. Frequency response: 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. Tracking force: 2 gms. **£5.18.6** Post Free

# Audio Tronics 70

The 1970 edition of Lasky's Audio-Tronics catalogue is available FREE on request. Packed with 1000's of items for the Radio and Hi-Fi enthusiast, Electronics Hobbyist, Servicemen and Communications Ham. Covers every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals) Tape recording and Audio accessories plus Lasky's amazing money saving vouchers worth over £25. SEND TODAY. Send your name, address and 2/- for post and inclusion of your name on our regular mailing list.

**This month's voucher worth 30/-**



# Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the *fast*, modern way. You can give yourself the essential technical 'know-how' sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new **TECHNATRON** Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING.** The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You **LEARN**—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a 'non-technical' type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book—'ENGINEERING OPPORTUNITIES'—Free and without any obligation.



## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 372B, Aldermaston Court, Aldermaston, Berkshire.


To: B.I.E.T., Dept. 372B ALDERMASTON COURT, ALDERMASTON, BERKS.

I would like to know more about your Practical Radio & Electronics Course. Please send me full details and FREE 164-page book.

name.....  
address.....  
.....age.....

**POST THIS COUPON NOW!**

# Listen to the world with Eddystone

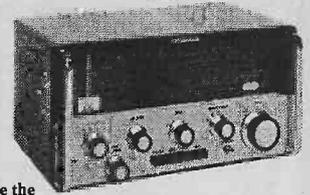

When you own an Eddystone communications receiver, you have the broadcasting world at your finger tips—wherever you happen to be—on land or at sea. The reputation these sets have attained is proof of their excellence and reliability and at Imhofs, there is a special Eddystone department, where you can see, hear and compare all models listed here. Same day despatch to any part of the world; free delivery in the U.K.; plus after sales service for which Imhofs and Eddystone are world famous. **EDDYSTONE EB35** Mark II broadcast receiver AM/FM transistorised. A high performance all-band receiver, can also be used as a 'Hi-Fi' tuner. Powered by 6 SP2 torch cells, or, with Type 924 power supply unit, from AC mains. £88.12.3d. Also stereo model. £97.10.9d. **EDDYSTONE 940** (13 valve) communications receiver. A connoisseur's instrument combining 'Professional' appearance with performance; has a world-wide reputation, two RF stages ensure high-sensitivity. £159.0.0d. **EDDYSTONE EC10** transistorised communications receiver. An enthusiast's receiver at a modest price. Embodies features usually only found in much more expensive designs. Powered by 6 SP2 torch cells or Type 924 power unit (AC). £62.10.0d. **EDDYSTONE EC10** Mark II transistorised communications receiver. A de-luxe version of this famous design now incorporating 'S' meter and limited fine tuner. £74.10.0d. **EDDYSTONE EA12** 'Ham Band' receiver. Built to professional standards but specifically for the amateur enthusiast. High sensitivity for all reception modes CW, MCW, AM and SSB. FSK adaptor available as ancillary £205.0.0d.

There is an Eddystone Communications receiver for any frequency between 10kHz and 870 MHz full details from Imhofs or your local Eddystone agent.

**IMHOF'S**

MAIN EDDYSTONE DISTRIBUTORS



Dept: PW7

112-116 New Oxford Street, London, WC1 Tel: 01-636 7878


R36D

## M. & B. RADIO

38 BRIDGE END, LEEDS 1

Telephone: 0532-35649

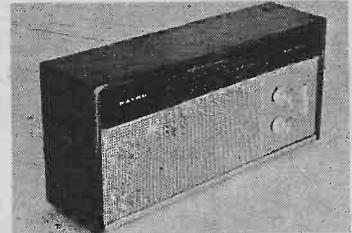VHF FM/MW/LW TRANSISTOR RADIO BRAND NEW 10 transistor plus 4 diode table model of well known British manufacture. The highly polished wood cabinet, speaker and pre-assembled chassis are supplied separate and only require fitting together and the 2 speaker connections making. CHASSIS & CABINET £9.10.0. SPEAKER 25/- carr. paid.



STC STEREO/MONO HEADPHONES. Brand new lightweight high quality comfortable padded headphones for stereo or mono use. Weight 10 oz. 20 c/s to 20 Kc/s 300 ohms per earpiece. Supplied with details of matching circuit for 15 ohms using only 3 resistors. 54/- plus 4/- pp.

12 VOLT TRANSISTOR INVERTERS. 12vdc input. 270vdc at 150mA approx output. Transformer 2in x 2in x 1 1/2in mounted on aluminium case 1 1/2in x 2 1/2in x 4in. Weight 15oz. 65/- plus 4/- pp.

TRANSISTOR MODULATOR PRE-AMP PANEL. BRAND NEW 4 transistors plus 1 diode. 4 1/2in x 2 1/2in. Fitted with pre-set microphone gain control and mod filter. Originally used to drive an NKT404 which drove a pair of NKT404s. Supplied brand new c/w circuit of complete modulator. 22/6d plus 1/6 pp.

TRANSISTOR AUDIO AND MUTING PANELS. Brand new set of 3 panels. Audio panel with transistor gate originally used to drive an NKT404 output transistor. 2 muting panels with Schmitt trigger circuit to operate the gate on the audio panel. 8 transistors in all. Supplied with full circuit 22/6d plus 2/6 pp.

455Kc/s FM LF PANEL. Brand new but faulty 6 transistor panel usually low in gain. 12/6 plus 1/6 pp.

HAND TELEPHONES. Brand new radiotelephone type press to talk handsets. 12/6 plus 1/6 pp.

VHF AERIAL C/O RELAYS. Used but OK. 6 or 12v. 4/- plus 1/6 pp

60 UNTESTED MIXED TRANSISTORS 5/- plus 1/- pp.

60 UNTESTED MIXED DIODES 2/6 plus 1/- pp.

USED TESTED VALVES. 12AX7/ECC83 2/6. 6BJ6 1/6. 6AQ5/EL90 2/6. ECF80 2/- . 6AT6 1/6.

ALSO VARIOUS VHF EQUIPMENT IN STOCK

S.A.E. AND 6d. STAMP FOR LISTS



**2kW KW HEATER**  
Three position switching to suit changes in the weather. Switch up for full heater (2kW), switch down for half heat (1kW), switch central blows cold for summer cooling. Fully adjustable thermostat acts as auto control and safety cut-out. Complete kit **£8.15.0** Post and ins. 7/6.

**FLUORESCENT CONTROL KITS**

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Crolux" tubes for neon fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. 19/6. Kit B—30-40 w. 19/6. Kit C—80 w. 25/6. Kit MFI is for 6in., 9in. and 12in. miniature tubes. 19/6. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit MFI 3/6 on first kit then 3/6 on each two kits ordered.

**3 DIGIT COUNTER**

For Tape Recorder or other application, re-settable by depressing button. Price 5/6.



**TRANSDUCER**

Made by Acos, reference No. I.D.1001. For measuring vibration, etc., to be used in conjunction with "G" Meter. Regular price £5. Our price 49/6. Brand new and unused.

**ISOLATION SWITCH**

20 Amp D.P. 250 volts. Ideal to control Water Heater or any other appliance. Neon indicator shows when current is on. 4/6. 48/- per dozen.



**LIGHT CELL**

Almost zero resistant in sunlight increases to 10 Ohms. Operates in dark or dull light, epoxy resin sealed. Size approx. 1in. dia. by 1/2in. thick. Rated at 500 MW, wire ended. 8/6 with circuit.

**FLEX BARGAINS**

**Screened 2 Core Flex.** Each core 14/0076 Copper PVC insulated and coloured. One 2 cores laid together and metal braided overall. Price £2.15.0 per 100 yds. coll. p. & 6/6.  
**18 Amp 8 Core Non-kink Flex.** 70/0076 insulated coloured cores, protected by tough rubber sheath, then black cotton braided with white tracer. A normal domestic flex as fitted to 3 Kw. fire. Regular price 3/6 per yd. 50 yd. coll. £4.10.0, p. & 6/6.  
**10 Amp 8 Core Non-kink Flex.** As above but cores are 28/0076 Copper. Normal price 2/6 per yd. 100 yd. coll. £7.10.0, p. & 6/6.  
**8 Amp 8 Core Flex.** As above, but 2 Cores each 28/0076 as used for Vacuum Cleaners, Electric Blankets, etc. 89/8 100 yd. coll. p. & 6/6.  
**28/0076 Triple Core P.V.C.** covered, circular, normally sold at 1/6 yd. Our price 100 yd. coll. £3.19.6. Post and Insurance 6/6.

**6, 12 or 24 VOLT SOLENOID**

For energising Reed Switches etc., 4/6 each, please state voltage.

**RADIO STETHOSCOPE**

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kits comprises two special transistors and all parts including probe tube and crystal earpiece, 28/6—twin stetho- instead of earpiece 11/- extra—post and ins. 2/6.

**TELESCOPIC AERIAL**

for portable, car radio or transmitter. Chrome plated—flex sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw, 7/6. **KNUCKLED MODEL FOR P.M. 9/6.**

**BATTERY OPERATED TAPE DECK**

With Capstan control. This unit is extremely well made and measures approx. 6x5x2 in. deep. Has three piano key type controls for Record, Playback and Rewind. Motor is a special heavy duty type intended for operation off 4/5 volts. Supplied complete with 2 spools ready to install. Record, Replayhead is the sensitive M4 type intended for use with transistor amplifier. Price 79/6. Post and insurance 4/6.

**INTEGRATED CIRCUIT BARGAIN**

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade devices, definitely not sub-standard or seconds. The ICs are all single silicon chip General Purpose Amplifiers. Regular price of which is well over £1 each. Full circuit details of the ICs are included and in addition you will receive a list of 50 different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only £1 post paid; or List and all data 10/- post free. Credited when you order IC's value of 30/- and upwards.

**DISTRIBUTION PANELS**

Just what you need for work bench or lab. 4 x 13 amp sockets and on/off switch with neon warning light (in metal box). Takes standard 13 amp fused plugs. Supplied complete with 7 feet of heavy cable. 39/6 wired up, ready to work plus 4/6 post & insurance. 5 amp 3 pin model 35/-, 13 amp 3 pin model 45/-

**STANDARD WAFER SWITCHES**

Standard Size 1 1/2 wafers—silver-plated 5 amp contact, standard 1/2" spindle 2", long—with locking washer and nut.

No. of Poles	1 way	3 way	4 way	6 way	6 way	8 way	9 way	10 way	12 way
1 pole	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
2 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
3 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
4 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
5 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
6 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
7 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
8 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
9 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
10 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
11 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
12 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6

**HI-FI SPEAKERS 15, 30, 40 & 100W**

**FULL FI 12 INCH LOUDSPEAKER.** This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwell—Power Handling 15 watts P.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—Specify 3 or 15 ohms—Mains resonance 60 c.p.s.—Chassis Diam. 12in.—13in. over mounting lugs—Baffle hole 11in. Diam.—Mounting holes 4, holes—1in. diam. or pitch circ. 11in. diam.—Overall height 5 1/2in. A 26 speaker offered for only £21.9.6 12in. 40watt £21.9.6. 15in. 25 watt £7.19.6 18in. 100 watt £12.10.0. plus 7/6 p. & p.



**THIS MONTH'S SNIP**

**FRIDGE UNIT (Sealed compressor type)**

Suitable for cabinets up to 7 cubic ft. We offer the sealed unit type as fitted to most of the letter fridges. Made originally to fit certain Philips and Stella models, the unit comprises a compressor, insulated and sealed in for silent operation, a cooling radiator, a freezer box and tubing, all gassed up ready for operation from our standard 230/240 volt mains. We offer these unused, in Makers' cartons, £6.19.6 each plus carriage at cost. We suggest you allow 30/- for this, any change will be returned to you.

**Horstmann "Time and Set" Switch**

(A 16 amp Switch). The best thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price 29/6, p. & ins. 4/6.

**OUT OF SEASON BARGAIN**

**3kW TANGENTIAL HEATER UNIT**

This heater unit is the very latest type, most efficient and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. 59/8, 2kW. Model as above except 2 kilowatts 89/8. Postage and insurance 6/6. Don't miss this.

**MOST AMAZING BARGAIN**

**PRINCESS AUTO CHANGER**

The most amazing bargain ever! A brand new Auto change record player for less than the price of a single player... due to a frustrated export order we are able to offer the Balfour Princess 4 speed Autochanger—a really fine machine at about one third of its regular price. The Balfour has two unique features (1) A patented brush system which automatically cleans stylus after each record playing and (2) at shut off the pick-up locks itself into its recess—other features include pick-up height and stylus pressure adjustments, and motor suitable for our 230/240 or for 115v. continental mains. Beautifully styled—this is a high class expensive instrument but you can purchase one this month for only 59/6 plus 8/6 post and packing. One point, these changers have been to France and back and the vibrations of the journey, etc., may have loosened screws or otherwise put them out of adjustment. However, with each we supply a 16 page service manual and fault finding chart which is so detailed that, if necessary you could completely re-build the changer. So this is truly a bargain that you will not want to miss so order today.



Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. Semiconductors add 1/- post. Over £1 post free. S.A.E. with enquiries please.

**NEED A SPECIAL SWITCH**

Double Leaf Contact. Very slight pressure closes both contacts, 1/3 each, 12/- doz. Plastic pushrod suitable for operating, 1/- each, 9/- doz.

**ELECTRIC CLOCK WITH 25 AMP SWITCH**


Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only 29/6, less than the value of the clock alone—post and insurance 2/6.



**CONTROL DRILL SPEEDS**

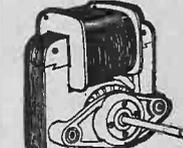**DRILL CONTROLLER**

Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. 19/6, plus 3/6 post and insurance. Made up model also available 37/6 plus 5/6 p. & p.



**MAINS MOTOR**

Precision made — as used in record decks and tape recorders—ideal also for extractor fan, blow heaters etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered, 12 and over post free.

**PP3 BATTERY ELIMINATOR**

Run your small transistor radio on the mains—full wave circuit—made up ready to wire into your set and adjustable high or low current. 8/6 each.



**AC FAN**

Small but very powerful mains motor with 8in. blades. Ideal for cooling equipment or as extractor. Silent but very efficient. 17/6, post 4/6. Mounts from back or front with 4BA screws.



**BALANCED ARMATURE UNIT**

300 ohm, operates speaker or microphone, so useful in Intercom or similar circuits, 6/6 ea., £3.10.0 doz. 60 ohm model 5/6.

**THERMOSTATS**

**Type "A"** 16 amp. for controlling room heaters, greenhouses, airing cupboard. Has spindle for pointer knob. Quickly adjustable from 30-90°F. 6/6 plus 1/6 post. Suitable box for wall mounting, 5/-, P. & P. 1/-.  
**Type "B"** 16 amp. This is a 17in. long rod type made by the famous Bunflo Co. Spindle adjusts this from 50-500°F. Internal screw allows the setting so this could be adjustable over 50° to 1000°F. Suitable for controlling furnace, oven, kiln, immersion heater or to make flame-stat or fire alarm, 8/6 plus 2/6 post and insurance.  
**Type "D"** We call this the Ice-stat as it cuts in and out at around freezing point. 2/3 amps. Has many uses one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (16 yd. 10/-) is wound round the pipes, 7/6, P. & P. 1/-.  
**Type "E"** This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 9/6, plus 1/- post.  
**Type "F"** Glass enclosed for controlling the temp. of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 50° to 150°F. Price 18/- plus 2/- post and insurance.

**THERMOSTAT**

Continuously variable 30°-90°C. Has sensor bulb connected by 33in. of flexible tubing. On operation 15 amp 250 volt switch is opened and in addition a plunger moves through approx. 1in. This could be used to open valve on ventilator etc. 29/6 plus 4/6 p. & ins.

**230 VOLT SOLENOID**

1/2in. stroke. Size 2 1/2in. x 2in. x 1 1/2in. 14/6, postage 2/9.

**ELECTRONICS (GROYDON) LTD**  
Dept. PW, 266 London Rd., Croydon CRO 2TH  
Also 102/3 Tamworth Road, Croydon

# Complete Stereo System £41

WITH  
**VISCOUNT**  
**F.E.T.**  
FIELD EFFECT TRANSISTORS  
**AMPLIFIER**



This superb stereo system is a real price break through. It comprises the VISCOUNT F.E.T. Mk I amplifier on which full details are given below, the famous Garrard SP 25 Mk II (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers. Measuring 17½ in x 10½ in x 6½ in, the Duo type 2 speakers are beautifully finished in teak veneer with matching vynair grills. They incorporate a 10½ in x 6½ in drive unit and high frequency speaker, both of which are of 3 ohms impedance. The Duo speaker system is also available separately at £6.6.0 each, plus 15/- p. & p.

Complete stereo system £41 plus £2.10. p. & p.

## The Viscount F.E.T. Mk I £14.5 plus 7/6 p. & p.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

**Specification**—Output per channel 10 watts r.m.s. Frequency bandwidth 20 Hz to 20 kHz + 1db at 1 watt. Total distortion at 1 kHz at 9 watts 0.5% Input sensitivities CER. P.U. 100mV into 3 meg ohms. Tuner 100mV into 100K ohms. Tape 100mV into 100K ohms. Overload Factor Better than 26db.

Signal to noise ratio—70db on all inputs (with vol. max). Controls—6 position selector switch (3 pos. stereo and 3 pos. mono). Separate volume controls for left and right channels. Bass ± 14db at 60 Hz. Treble (with D.P.S. on off) ± 12 db at 10 KHz. Tape recording output sockets on each channel. Size 12½ in. 6 in. 2½ in. in teak-

finished case. **BUILT & TESTED. MkII (MAG P.U.) £15.15 plus 10/- p. & p.** Specification same as Mk. 1, but with the following inputs. Mag. P.U. CER. P.U. Tuner. Spec. on Mag. P.U. 3mV at 1 kHz input impedance 47K. Fully equalised to within ±1db RIAA. Signal to noise ratio—65db (vol. max).

## The £29-10-0 Stereo system

The Duetto is a good quality stereo amplifier, attractively styled and finished. It gives superb reproduction previously associated with amplifiers costing far more.

**SPECIFICATION**—R.M.S. power output 3 watts per channel into 10 ohms speakers.

**INPUT SENSITIVITY.** Suitable for medium or high output crystal cartridges and tuners. Cross-talk better than 30dB at 1Kc/s.

**CONTROLS:** 4-position selector switch (2 pos. mono and 2 pos stereo) dual ganged volume control.



**TONE CONTROL** Treble lift and cut Separate on off switch. A preset balance control.

Duetto integrated transistor stereo Amp. Garrard Changer from Cover and teak finish plinth Duo Type 1 speakers (see opp. page) The above items purchased together

£9.10.0 + 7/6 p&p.  
£7.19.6 + 7/6 p&p.  
£4.15.0 + 7/6 p&p.  
ea. £4. 4.0 + 7/6 p&p.  
£29.10.0 + £1.10 p&p.

## CAR TRANSISTOR IGNITION SYSTEM

by famous manufacturer

For 6 volt or 12 volt positive earth systems, Comprising: special high voltage working hermetically sealed silicon transistor mounted in finned heat-sink, high output ignition coil, ballast resistor and hardware (screws, washers, etc.).

Price £4.19.6 plus 5/- P. & P.



## EXTRACTOR FAN


A.C. mains 230/250v. complete with pull switch. Size: 6 x 6 x 4in.

Price 27/6 plus 7/6 P. & P.
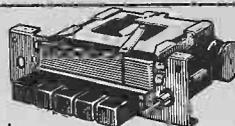
## PYE CAR RADIO

Push Button Tuning Heart

This PRESTOLOK 5 station Push-Button Tuner Heart with Manual Over-ride is an ideal basis for a quality AM car radio. Size 6½" x 4" x 2". As illustrated but without knobs.



25/- plus 3/- P. & P.


## THE DUO SPEAKER SYSTEM

Similar in design to those on the previous page the 2-way speaker system is beautifully finished in polished teak veneer, with matching vynalr grille. It is ideal for wall or shelf mounting either upright or horizontally.

Type 1 SPECIFICATION:—

Impedance 3, 8 or 10 ohms (please state requirement). It incorporates Goodmans high flux 6in x 4in speaker and 2½in speaker. Teak finish 12in x 6½in x 5½in. 4 guineas each. 7/6 p. & p.

## THE RELIANT

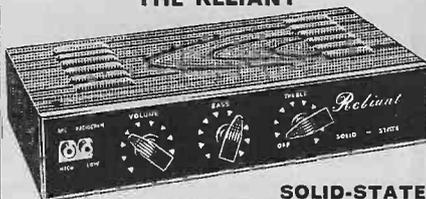

### SOLID-STATE GENERAL PURPOSE AMPLIFIER

#### SPECIFICATIONS

Output—10 watts. Output impedance—3 to 4 ohms. Input—1-xtal mic 10mV Tone Controls—Treble control range ±12dB at 10KHz. 2. -gram/radio 250mV. Bass control range ±13dB at 100Hz. Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than -60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10½in x 4½in x 2½in. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Separate bass and treble lift control. Two inputs with control from gram. and mike. Built and tested.


#### RELIANT Mk. I

As above less teak case  
£6.10 plus 7/6 P. & P.

#### RELIANT Mk. II

In teak finished case  
£7.5 plus 7/6 P. & P.

## 50 WATT AMPLIFIER

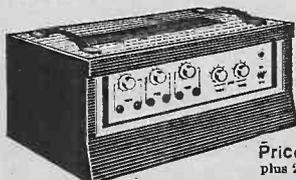

A.C. Mains 200-250V

Price £28.10 plus 20/- p. & p.

An extremely reliable general purpose valve amplifier. Its rugged construction yet space age styling and design makes it by far the best value for money.

#### TECHNICAL SPECIFICATIONS


3 electronically mixed channels, with 2 inputs per channel, enables the use of 6 separate instruments at the same time. The volume controls for each channel are located directly above the corresponding input sockets. SENSITIVITIES AND INPUT IMPEDANCES. Channels 1 and 2 4mV at 470K. These 2 channels (4 inputs) are suitable for microphone or guitars. Channels 3 and 4 300mV at 1m. Suitable for most high output instruments (gram, tuner, organ, etc). Input

sensitivity relative to 10w output. TONE CONTROLS ARE COMMON TO ALL INPUTS. Bass Boost +13dB at 60Hz. Bass Cut—13dB at 60Hz. Treble Boost +13dB at 15 KHz. Treble Cut—12dB at 15 KHz. With bass and treble controls central—3dB points at 20 Hz and 20 KHz. POWER OUTPUT: For speech and music 50 watts rms. 100 watts peak. For sustained music 45 watts rms. 90 watts peak. For sine wave 38.5 watts rms. Nearly 80 watts peak. Total distortion at rated output 3.2% at 1KHz. Total distortion at 20 watts 0.15% at 1KHz. Output to match into 8 or 15 ohm speaker system. NEGATIVE FEEDBACK 20dB at 1KHz. SIGNAL TO NOISE RATIO 60dB. MAINS VOLTAGES adjustable from 200-250V A.C. 50-60Hz. A protective fuse is located at the rear of the unit. Output-impedance 3, 8 and 15 ohms.


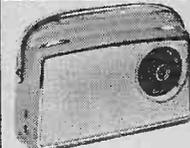
## The ELEGANT SEVEN Mk. III (350mW Output)

7 transistor fully-tunable M.W.—L.W. superb portable Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction. MAINS POWER PACK KIT: 9/6 extra. Price £5.5.0 plus 7/6 P. & P. Circuit 2/6 FREE WITH PARTS



## The DORSET (600mW Output) Price £5.5.0 plus 7/6 P. & P.

Circuit 2/6 FREE WITH PARTS


7-transistor fully tunable M.W.—L.W. superb portable—with baby alarm facility. Set of parts. The latest modularised and pre-alignment techniques makes this simple to build. Sizes: 12 x 8 x 3in. MAINS POWER PACK KIT: 9/6 extra

## QUALITY MAINS TRANSFORMER

Input 250 volts. OUTPUT (All RMS values) 4 windings of 11.5 volts connected in series total 46 volts at 4.5 amps (conservatively rated). The following combinations may be used. 1.23.0-23 volts 2.46 volts.

Both of these above voltages are commonly used in medium to high powered transistor amplifiers, power supplies, etc.

Price 35/- plus 7/6 P. & P.

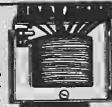

# LIQUIDATED STOCK DANSETTE TOURISTE MK3 CAR RADIO

## ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts.

Originally sold complete for £15.4.6.

## SET OF PARTS

**£6.6.0**

Circuit diagram 2/6. Free with parts

plus 7/6 P. & P.

Speaker, baffle and fixing kit 25/- extra plus 4/- P. & P. Postage free when ordered with parts.

See top of previous page for address



Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.


RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED

# COMPLETE STEREO SYSTEM

FOR ONLY

# 39 GNS

CARRIAGE 35/-

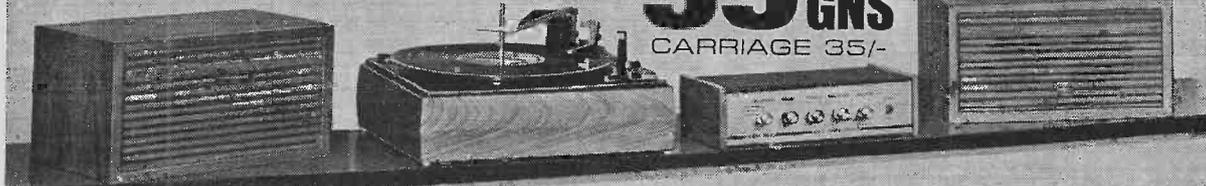

**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier, Garrard 2025 T,C auto manual record player unit fitted stereo mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on off, stereo mono switch. Brushed aluminium front panel Black metal case with teakwood ends: Size 12 x 5½ x 3¼in. high (Amplifier available separately if required £14.19.6. Carr. 7/6.)

**PREMIER STEREO SYSTEM "TWO"**  
As system "ONE" above but with Garrard SP25.  
**PREMIER PRICE 45 Gns.** Carr. 35/-

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250' P.V.C.	5/8	LP8 5 1/2" 1200' P.V.C.	12/8
TT3 3" 450' POLYESTER	7/8	DT8 5 1/2" 1800' POLYESTER	22/8
DT3 3 1/2" 600' POLYESTER	11/8	TT8 5 1/2" 2400' POLYESTER	37/8
SP5 5" 600' P.V.C.	8/8	SP7 7" 1200' P.V.C.	12/8
LP5 5" 900' P.V.C.	10/-	LP7 7" 1800' P.V.C.	15/-
DT5 5" 1200' POLYESTER	15/-	DT7 7" 2400' POLYESTER	25/-
TAPE SPOOLS 3" 1 1/2", 5", 5 1/2", 7", 7 1/2", 10", 10 1/2", 12", 12 1/2", 15", 15 1/2", 18", 18 1/2", 21", 297 1/2", 300", 300 1/2, 303, 303 1/2, 306, 306 1/2, 309, 2247 1/2, 2250, 225			

# BI-PAK SEMICONDUCTORS

**NEW LOW PRICED TESTED S.C.R.'s**

1A	3A	7A	16A	30A
(TO-5 case)	(TO-66 case)	(TO-48 case)	(TO-48 case)	
P1V each	each	each	P1V each	each
50 4/6	5/-	9/6	10/6	25 20/-
100 5/-	6/6	10/6	12/6	50 23/-
200 7/-	7/6	11/6	15/6	100 28/-
400 8/6	9/6	13/6	18/6	200 32/-
600 10/6	11/6	15/6	25/-	400 35/-
800 12/6	14/-	18/-	30/-	800 80/-

**PRINTED CIRCUITS EX-COMPUTER**  
Packed with semiconductors and components. 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/- Plus 2/- p. & p.

**TRANSISTOR EQVT. & SPECIFICATION BOOK** (German publication) A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 15/- each.

**9N2900 NPN SIL. DUAL TRANS.** CODE D1899  
TEXAS. Our price 5/- ea.

**120VCB NIXIE DRIVER TRANSISTOR.** Silm. B5X21 & C407, 2N1593  
FULLY TESTED AND CODED NDI20, 1-24, 3/6 each. TO-5 NPN 25 up 2/- each.

Sil. trans. suitable for P.E. Organ, Metal TO-18 Evt. ZTX300 1/- each. Any Qty.

**MULLARD I.C. AMPLIFIERS**  
TAA243, Operational amplifier, 70/- each.  
TAA263, Linear AF amplifier, 18/6 each.  
TAA293, General purpose amplifier, 21/- each.

**CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS**  
Audio Power Amplifier, 30/- each.

**SIL. RECTS TESTED**

P1V 750mA	3A	10A	30A
50 1/-	2/9	4/3	9/6
100 1/3	3/4	4/6	15/-
200 1/9	4/-	4/9	20/-
300 2/3	4/6	6/6	22/-
400 2/6	5/6	7/6	25/-
500 3/6	6/-	8/6	30/-
600 3/3	6/9	9/ 37/-	
800 3/6	7/6	11/-	40/-
1000 5/-	9/3	12/6	50/-
1200 6/6	11/6	15/-	

**TRIACS**

VBOM 2A	6A	10A
(TO-1) (TO-66)	(TO-88)	
100 14/-	15/-	22/6
200 17/6	20/-	28/-
400 20/-	25/-	35/-

VBOM = Blocking voltage in either direction.

**2N3055 115 WATT SIL. POWER. NPN.**  
OUR PRICE 12/6 EACH

**FULL RANGE OF ZENER DIODES**  
VOLTAGE RANGE 2-18V. 400mV (DO-7 Case) 2/8 ea. 1-5W(T op-Hat) 3/8 ea. 10W. (80-10 Stud) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

**BRAND NEW TEXAS GERM. TRANSISTORS**  
Coded and Guaranteed.

Pak No.	EQVT
T1 8 2G371A	OC71
T2 8 2G374	OC74
T3 8 2G374A	OC81D
T4 8 2G381A	OC81
T5 8 2G382T	OC82
T6 8 2G344A	OC44
T7 8 2G345A	OC45
T8 8 2G378	OC78
T9 8 2G389A	2N1302
T10 8 2G417	AF117

All 10/- each pack

## SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Unequaled Value and Quality  
Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.

U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
U2	60 Mixed Germanium Transistors AF/RF	10/-
U3	75 Germanium Gold Bonded Diodes sim. OA5. OA47	10/-
U4	40 Germanium Transistors like OC81. AC128	10/-
U5	60 200mA Sub-min. Sil. Diodes	10/-
U6	30 Silicon Planar Transistors NPN sim. BS796A. 2N706	10/-
U7	15 Silicon Rectifiers Top-Hat 760mA up to 1,000V	10/-
U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
U9	20 Mixed Volts 1 watt Zener Diodes	10/-
U10	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
U11	30 PNP-NPN Sil. Transistors OC200 & 2S104	10/-
U12	150 Mixed Silicon and Germanium Diodes	10/-
U13	25 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
U14	10 3-amp Silicon Rectifiers Stud Type up to 1,000 PIV	10/-
U15	30 Germanium PNP AF Transistors TO-5 like ACY17-22	10/-
U16	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
U17	25 Silicon NPN Transistors like BC108	10/-
U18	10 1-5 amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
U19	30 AF Germanium alloy Transistors 2G300 Ser. & OC71	10/-
U20	30 Mad's like MAT Series PNP Transistors	10/-
U21	20 Germanium 1-amp Rectifiers GJM up to 300 PIV	10/-
U22	25 300Mc/s NPN Silicon Transistors 2N708, BS727	10/-
U23	30 Fast Switching Silicon Diodes like IN914 Micro-min.	10/-
U24	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc. 8 Assorted Pieces	20/-
U25	10 1-amp SCR's TO-5 can up to 600 PIV CR81/25-800	20/-
U26	20 Sil. Planar NPN trans. low noise AMP 2N3707	10/-
U27	25 Zener diodes 400mV DO7 case mixed Volts. 3-18	10/-
U28	15 Plastic case 1 amp Silicon Rectifiers 1N4000 series	10/-
U29	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	10/-
U30	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
U31	25 Sil. Planar NPN trans. TO-5 BFY 50/51/52	10/-
U32	30 Sil. alloy trans. 80-2 PNP, OC200 2S322	10/-
U33	20 Fast Switching Sil. trans. NPN. 400 Mc/s 2N3011	10/-
U34	30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
U35	10 Dual trans. 6 lead TO-5 2N2960	10/-
U36	25 RF Germ. trans. TO-1 OC45 NKT72	10/-
U37	10 VHF Germ. PNP trans. TO-1 NKT667 AF117	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

## I.C. AMPLIFIER

Identical encapsulation and pin configuration to the following: 8L402-3, IC10 and IC403. Each circuit incorporates a pre-amp and class A.B. Power amp stage capable of driving up to 3 watts RMS. Fully tested and guaranteed. Supplied complete with circuit details and data. CODED BP1010. OUR LOWEST PRICE 80/- each. 10 up 25/- each.

**AD161 NPN AD162 PNP**  
MATCHED COMPLEMENTARY PAIRS OF GERM-POWER TRANSISTORS. For mains driven output stages of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 12/6 PER PAIR.

**UNIJUNCTION UT46.** Evt. 2N2464 Evt. T143. BEN3000 5/6 EACH 25-99 5/- 100 UP 4/-


**NPN SILICON PLANAR BC107/8/9.** 2/- each 50-99 1/10 100 up 1/8 each, 1,000 off, 1/6 each. Fully tested and coded TO-18 case.

**PNP/DIFFUSED SILICON PHOTO-DUODIODE TYPE 1S701 (2N2175) or Type Readout, high switching and measurement indicators. 50V. 250mV. OUR PRICE 10/- EACH 50 OR OVER 8/6 EACH. FULL DETAILS.**

**FE7's**  
2N 3819 ..... 8/-  
2N 3820 ..... 25/-  
MPF105 ..... 8/6
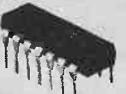
# BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.	SIM-TYPE	Description	Price and qty. prices		
			1-24	25-99	100 up
BP00 7400N	Quad 2-Input NAND GATE	...	6/8	5/8	4/6
BP01 7401N	Quad 2-Input NAND Gate—OPEN COLLECTOR	...	6/6	5/6	4/6
BP04 7404N	HEX INVERTER	...	6/6	5/6	4/6
BP10 7410N	Triple 3-Input NAND GATE	...	6/8	5/6	4/6
BP20 7420N	Dual 4-Input NAND GATE	...	6/6	5/6	4/6
BP30 7430N	Single 8-Input NAND GATE	...	6/6	5/6	4/6
BP40 7440N	Dual 4-Input BUFFER GATE	...	6/6	5/6	4/6
BP41 7441AN	BCD to decimal decoder and NIT Driver	...	22/8	20/-	17/6
BP42 7442N	BCD to decimal decode (TTL 0/1)	...	22/8	20/-	17/6
BP50 7450N	Dual 2-Input AND/OR/NOT GATE—expandable	...	6/6	5/6	4/6
BP53 7453N	Single 8-Input AND/OR/NOT GATE—expandable	...	6/6	5/6	4/6
BP60 7460N	Dual 4-Input—expandable	...	6/6	5/6	4/6
BP70 7470N	Single JK Flip-flop—edge triggered	...	9/-	8/-	7/-
BP72 7472N	Single Master Slave JK Flip-flop	...	9/-	8/-	7/-
BP73 7473N	Dual Master Slave JK Flip-flop	...	10/-	9/-	8/6
BP74 7474N	Dual D Flip-flop	...	10/-	9/-	8/6
BP75 7475N	Quad Bistable Latch	...	11/-	10/-	9/6
BP76 7476N	Dual Master Slave Flip-flop with preset and clear	...	11/-	10/-	9/6
BP83 7483N	Four Bit Binary Adder	...	28/-	22/8	20/-
BP90 7490N	BCD Decade Counter	...	22/8	20/-	17/6
BP92 7492N	Divide by 12 4 Bit binary counter	...	22/8	20/-	17/6
BP93 7493N	Divide by 16 4 Bit binary counter	...	22/8	20/-	17/6
BP94 7494N	Dual Entry 4 Bit Shift Register	...	22/8	20/-	17/6
BP95 7495N	4 Bit Up-Down Shift Register	...	22/8	20/-	17/6
BP96 7496N	5 Bit shift register	...	24/-	21/-	18/6

Data is available for the above Series of Integrated circuits in booklet form, price 2/8

**BRAND NEW, FULL TO MANUFACTURERS' SPECIFICATION** 1-24 Price each 25-99 100 up  
BP709 Operational amplifier, dual-in-line 14 pin package — BN7209 and similar to MIC709 and ZLD709C 10/6 9/- 8/-  
This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

## TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part ideal for learning about I.C.'s and experimental work, on testing some will be found perfect.

PAK No.	PAK No.	PAK No.
UIC00 = 5 x 7400N .10/-	UIC42 = 5 x 7442N .10/-	UIC80 = 5 x 7480N .10/-
UIC01 = 5 x 7401N .10/-	UIC46 = 6 x 7460N .10/-	UIC85 = 6 x 7485N .10/-
UIC02 = 5 x 7402N .10/-	UIC51 = 5 x 7451N .10/-	UIC93 = 5 x 7493N .10/-
UIC03 = 5 x 7403N .10/-	UIC80 = 5 x 7480N .10/-	UIC86 = 5 x 7486N .10/-
UIC04 = 5 x 7404N .10/-	UIC70 = 5 x 7470N .10/-	UIC90 = 5 x 7490N .10/-
UIC05 = 5 x 7405N .10/-	UIC72 = 5 x 7472N .10/-	UIC92 = 5 x 7492N .10/-
UIC10 = 5 x 7410N .10/-	UIC73 = 5 x 7473N .10/-	UIC93 = 5 x 7493N .10/-
UIC20 = 5 x 7420N .10/-	UIC74 = 5 x 7474N .10/-	UIC94 = 5 x 7494N .10/-
UIC40 = 5 x 7440N .10/-	UIC75 = 5 x 7475N .10/-	UIC95 = 5 x 7495N .10/-
UIC41 = 5 x 7441AN .10/-	UIC76 = 5 x 7476N .10/-	UIC96 = 5 x 7496N .10/-

UICX1 = 20 x asst'd 74's. 30/-

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

## DUAL-IN-LINE LOW PROFILE SOCKETS

14 AND 16 Lead Sockets for use with Dual-in-Line Intergrated Circuits.

Order No.	14 pin type	1-24	25-99	100 up
TS014	14 pin type	7/8	6/-	5/3
TS016	16 pin type	10/-	8/8	7/9

## RTL FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits	Qty. prices each
Epox. case To-5 temp range 15°C to 55°C.	1-11 12-24 25-99 100 +
μL 300 Buffer	8/- 7/- 6/6 5/6
μL 914 Dual two-input GATE	8/- 7/- 6/6 5/6
μL 923 J-K Flip-flop	10/8 10/- 9/8 9/-

Full data and circuits for ICS in Booklet form price 1/6 each.  
μA793E Linear RF-IF AMPLIFIER 11/- 10/- 9/- 8/3  
PLASTIC CASE To-5 6 lead up to 100 m/cs.

## DTL DIGITAL I.C.'s

DTL dual in-line package.

Type	Price
Type MC844P expandable dual 4-input NAND Power Gate	10/- each
Type MC845P Clocked Flip-flop	15/- each
Type 862 Triple 3-input NAND/NOR Gate	10/- each

FULL DATA SUPPLIED WITH UNITS

Please send all orders direct to our warehouse and despatch department.

## BI-PAK SEMICONDUCTORS P.O. BOX 6, WARE, HERTS.

Postage and packing add 1/- Overseas add extra for Airmail. Minimum order 10/- Cash with order please.

**BELCO AF-5A  
SOLID STATE SINE SQUARE  
WAVE C.R. OSCILLATOR**

Size 18—200,000 Hz. Square 18—50,000 Hz  
Output 100mA — 10 dB (10 K ohms)



Operation internal batteries  
Attractive 2-tone case 7 1/2" x 5" x 2".  
Price \$17.10.0.  
Carr. 3/6.

**CLASS D WAVEMETERS**



A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 6 volts D.C. Ideal for amateur use. Available in good used condition. \$5.19.6. Carr. 7/6. Or brand new with accessories. \$7.19.6. Carr. 7/6.

**CLASS D WAVEMETERS No. 2**  
Crystal controlled. 1.2-19 Mc/s. Mains or 12V. D.C. operation. Complete with calibration charts. Excellent condition. \$12.10.0. Carr. 30/-.

**R209 MK II  
COMMUNICATION RECEIVER**

11 valve high grade communication receiver suitable for tropical use. 1-20 Mc/s on 4 bands. AM/CW/FM driver. Incorporates precision vernier oscillator. B.F.O., aerial trimmer, internal speaker and 12V. D.C. internal power supply. Supplied in excellent condition, fully tested and checked. \$15.0.0. Carr. 20/-.



**TYPE 13A DOUBLE BEAM  
OSCILLOSCOPES**



An excellent general purpose D/B oscilloscope. T.B. 2 cps-750 Kc/s. Bandwidth 5.5 Mc/s. Sensitivity 33mV/CM. Operating voltage 0/110 200/250V. A.C. Supply. In excellent working condition. \$22.10.0. Carriage 30/-.



**MARCONI  
T/44/TF956**

AF Absorption  
Wattmeter  
1 μ/watt to 6 watts.  
\$20. Carr. 10/-.

**SOLARTRON CD 711S2**

Double Beam Oscilloscopes


D.C. to 9 Mc/s. Perfect order \$65. Carr. 60/-

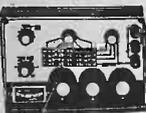**TO-3 PORTABLE OSCILLOSCOPE**



3in. tube. V amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 20pF X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5 cps-300KHz. Input imp. 2 meg Ω 20pF. Time base. 5 cps-300 KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 13 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. \$37.10.0. Carr. 10/-.

**TRANSISTORISED L.C.R. A.C.  
MEASURING BRIDGE**




Ranges ± 2%. TURNS RATIO 1:1/1000-1:11000. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100 μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2" x 5" x 2 1/2". \$20. P. & P. 5/-.

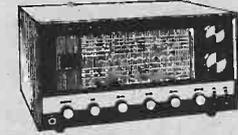**UNR-30 4-BAND COMMUNICATION RECEIVER**

Covering 550 Kcs-30 Mc/s. Incorporates BFO. Built in speaker and phone jack. Metal cabinet. Operation: 220/240V. A.C. Supplied brand new, guaranteed with instructions. Carr. 7/6. **13 gns.**



**TRIO JR.310 New Amateur Band 10-80  
Metre Receiver in stock. \$77.10.0.**



**LAFAYETTE HA-800 SOLID STATE  
AMATEUR COMMUNICATION RECEIVER**

Six bands 3-5.4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-54Mc/s. Dual conversion on all bands. 2 x 455 Kc/s mechanical filters. FET front end, product detector, variable BFO, 100Kc/s crystal calibrator. 'S' Meter. Huge slide rule dial. Operation 230V A.C. or 12V D.C. Size 15 x 9 1/2 x 8 1/2 in. Complete with instruction manual. \$57.10.0 Carr. Paid. 100Kc/s crystal 39/6 extra.


**VARIABLE TRANSFORMERS**

Input 230v. A.C. 50/60 cs.  
Output variable 0-280v.

BENCH MOUNTING		latest release	
1 amp	\$5.10.0	8 amp	\$14.10.0.
2 1/2 amp	\$6.15.0.	10 amp	\$18.10.0.
5 amp	\$9.15.0.	20 amp	\$27. 0.0.
PANEL MOUNTING		125 KHz-20 MHz	
1 amp	\$5.10.0.	2 1/2 amp	\$6.12.6.

**B.C. 221 FREQUENCY  
METERS**

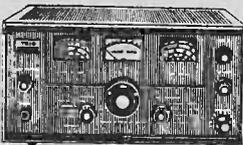125 KHz-20 MHz  
Excellent tuning  
Fully tested and checked and complete with calibrator charts.  
\$27.10.0 each. Carr. 10/-



4 band receiver covering 650 Kc/s to 30 Mc/s continuous, 15, electrical bandspread on 10, 15, 20 and 80 metres. 8 valve plus 7 diode circuit, 4/8 ohm output and phone jack. SSB-CW ● ANL ● Variable BFO ● 8 meter ● Sep. bandspread dial ● IF 455 Kc/s ● Audio output 1.5 W. ● Variable RF and AF gain controls. 115/250V. A.C. Mains. Beautifully designed. Size: 7 x 15 x 10 in. With instruction manual and service data. \$42. carriage paid. **TRIO COMMUNICATION TYPE HEADPHONES.** Normally \$5.19.6. **OUR PRICE \$3.15.0** if purchased with above receiver.

**TRIO JR. 500SE 10-80 Metre  
Receiver \$69.10.0**



**TRIO TS 510 AMATEUR TRANS-  
CIVER with speaker and mains P.S.U.  
\$212. IN STOCK!**

**LAFAYETTE PF-60 SOLID STATE VHF FM RECEIVER**

A completely new transistorised receiver covering 105-174 Mc/s. Fully tunable or crystal controlled (not supplied) for fixed frequency operation. Incorporates 4 INTEGRATED CIRCUITS. Built in speaker and illuminated dial. Squelch and volume controls. Tape recorder output. 76 Ω aerial input. Headphone jack. Operation 230V. A.C.; 12V. D.C. Neg. earth. \$37.10.0. Carr. 10/-.

**TELETON CR-10T AM/FM STEREO TUNER AMPLIFIER**

A new model from Teleton. 31 solid state devices. 4 + 4 watt output. Inputs for ceramic/crystal cartridge. Frequency range AM 540-1600KHz FM 88-108MHz. Automatic FM Stereo reception. Stereo Indicator. Controls: Tuning function selector, Tone and P & L volume controls. AFC switch. Stereo headphone socket. Size 13 1/2" x 3 1/2" x 9 1/2" approx. **PRICE \$34.0.0.** Carr. 7/6.

**CLEAR PLASTIC PANEL METERS**

First grade quality Moving Coil panel meters. Type MR 38P. 1 1/4 in. square fronts.

500-0-500μA	\$27/6	50mA	... 27/6	150V. D.C.	... 27/6
1mA	... 27/6	100mA	... 27/6	300V. D.C.	... 27/6
1-0-1mA	... 27/6	150mA	... 27/6	500V. D.C.	... 27/6
2mA	... 27/6	200mA	... 27/6	750V. D.C.	... 27/6
5mA	... 27/6	300mA	... 27/6	15V. A.C.	... 27/6
10mA	... 27/6	500mA	... 27/6	50V. A.C.	... 27/6
50-0-50μA	... 37/6	3V. D.C.	... 27/6	150V. A.C.	... 27/6
100μA	... 37/6	10V. D.C.	... 27/6	300V. A.C.	... 27/6
100-0-100μA	... 35/-	10V. D.C.	... 27/6	500V. A.C.	... 27/6
200μA	... 35/-	20V. D.C.	... 27/6	8 meter 1mA	... 32/-
500μA	... 40/-	100V. D.C.	... 27/6	VU meter	... 42/-


FULL RANGE OF OTHER SIZES IN STOCK. SEND S.A.E. FOR LEAFLET

**Variable Voltage Transformers**

Brand new, guaranteed and carriage paid.  
High quality construction. Input 230V. 50-60 cycles.  
Output full variable from 0-260 volts. Bulk quantities available.  
1 amp.—\$5.10.0; 2 amp.—\$6.15.0; 5 amp.—\$9.15.0;  
8 amp.—\$14.10.0; 10 amp.—\$18.10.0; 12 amp.—\$21.0.0;  
20 amp.—\$27.0.0.



**CRYSTAL CALIBRATORS NO. 10**

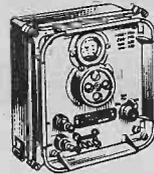

Small portable crystal controlled wavemeter. Size 7 x 7 1/4 x 4 in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V. D.C. 0.3A.

Excellent condition. \$9/6. Carr. 7/6.

**TE-40 HIGH SENSITIVITY  
A.C. VOLTMETER**

10 meg. input 10 ranges: 0.1/0.03/1/3/1.3/10/30/100 300V. R.N.S. 4 cps. 1-2 Mc/s. Decibels -40 to +20dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. \$17.10.0 Carr. 5/-.



**LELAND MODEL 27 BEAT  
FREQUENCY OSCILLATORS**

Frequency 0-20 Kc/s. on 2 ranges. Output 500 Ω or 5k Ω. Operation 200/250V. A.C. Supplied in perfect order. \$12.10.0 Carr. 10/-.


**TE-65 VALVE VOLTMETER**

High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. \$17.10.0. P. & P. 6/-.  
Additional probes available: R.F. 42/6. H.V. 50/-.



**COSOR 1049 DOUBLE  
BEAM OSCILLOSCOPES**

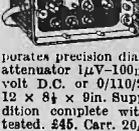D.C. coupled. Band width 1Kc/s. Perfect order. \$25. 30/-.



**AM/FM SIGNAL GENERATORS**

Oscillator Test No. 2. A high quality precision instrument made for the ministry by Airtec. Frequency coverage 20-80 Mc/s. AM CW/FM. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12 volt D.C. or 0/110/200/250 volt A.C. Size 12 x 8 1/2 x 9 in. Supplied in brand new condition complete with all connectors fully tested. \$45. Carr. 20/-.

**EDDYSTONE VHF RECEIVERS Model 770R.  
19-165 Mc/s. Excellent condition. \$160.**

**RUSSIAN C1-16 DOUBLE  
BEAM OSCILLOSCOPES**

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from .2 sec to 100 mill sec/cm. Supplied complete with all accessories and instructions \$87. Carr. paid.

**TE-16A Transistorised  
Signal Generator. 5 ranges  
400KHz-30mHz. An  
inexpensive instrument  
for the handman. Oper-  
ates on 9v battery. Wide  
easy to read scale.  
800KHz modulation.  
5 1/2 x 5 1/2 x 3 1/2 in.  
Complete with instructions  
and leads. \$7.19.6.  
P. & P. 4/-.**



**HOSIDEN DH-08S  
DE-LUXE STEREO  
HEADPHONES**

Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead & stereo jack pins \$7.19.6. P. & P. 2/6.



**AUTO TRANSFORMERS**

0/115/230V. Step up or step down. Fully shrouded.  
150 W. \$2. 2.6. P. & P. 3/6.  
300 W. \$3. 5.0. P. & P. 4/6.  
500 W. \$4. 10.0. P. & P. 5/6.  
1,000 W. \$8.10.0. P. & P. 7/6.  
1,500 W. \$7.19.6. P. & P. 8/6.  
7,500 W. \$15.10.0. P. & P. 20/-.

G. W. SMITH & CO (RADIO) LTD.  
Also see oppos. page

**ARF-100 COMBINED AF-RD SIGNAL GENERATOR**



**A.F. SINE WAVE**  
20 - 200,000 c/s.  
Square wave 20 - 30,000 c/s. O/P.  
**HIGH IMP. 21V.**  
P/2600  $\Omega$  3.5V. P/P  
T<sup>2</sup> 100 Kc/s-100 Mc/s. Variable R.F.  
attenuation int. ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V. A.C. £32.10.0. Carr. 7/6.

attenuation int. ext. modulation. Incorporates dual purpose meter to monitor AF output and % mod. on R.F. 220/240V. A.C. £32.10.0. Carr. 7/6.

**TE-20D RF SIGNAL GENERATOR**



Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 7/6. Size 140 x 215 x 170 mm.

**PEAK-SOUND PRODUCTS.** Full range of Amplifiers, Kits, Speakers, in stock.

**TY75 AUDIO SIGNAL GENERATOR**

Sine Wave 20c/s to 200 kc/s. Square Wave 20c/s to 30kc/s. High and low impedance output. Output variable up to 6 volts 220/240 volts A.C. Size 210 x 150 x 120 mm. Brand new with instructions. £16. Carr. 7/6.



**MARCONI TF142E DISTORTION FACTOR METERS.** Excellent condition. Fully tested. £20. Carr. 10/-.

**LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER**

2 pF-2000 nFd  
2 ohms 200 meg-ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New £17.10.0 Carr. 7/6.



**TO-2 PORTABLE OSCILLOSCOPE**

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPS-1 MHz. Input imp. 2 meg  $\Omega$  25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. £22.10.0. Carr. 10/-.



**ADVANCE TEST EQUIPMENT**

Brand new and boxed in original sealed cartons.

**J1B. AUDIO SIGNAL GENERATOR.**

VM79. UHF MILLIVOLT METER. 1000 Kc/s to 1,000 Mc/s. AC 10mV to 3v. DC 10 mV to 3v. Current 0.01  $\mu$ A to 0.3 mA. Resistance 1 ohm to 10 megohm. £125.0.0.

**T1S. TRANSISTOR TESTER.** Full range of facilities for testing PNP or NPN transistors in or out of circuit. £27.10.0. Carr. 10/- per item.

**HOSIDEN DHO4S 2-WAY STEREO HEADSETS**



Each headphone contains a 24in. woofer and a 1in. tweeter. Built in individual level controls. 8  $\Omega$  imp. 25-18,000 $\Omega$ s with cable and stereo plug. £5.19.6. P. & P. 2/6.

**BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR**



New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max +10 dB (10 K ohms). Operation 220/240V. A.C. Size 210mm x 150mm x 120mm. Price £27.10.0. Carr. 5/-

**Latest Catalogue**

The latest edition giving full details of a comprehensive range of HI FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. . . . Over 230 pages, fully illustrated and detailing thousands of items—many at bargain prices. FREE DISCOUNT COUPONS VALUE 10/-



SEND NOW—ONLY 7/6 P&P1/6

**GARRARD**

FULL CURRENT RANGE OFFERED BRAND NEW AT FANTASTIC SAVINGS

1025 stereo	£7.19.6	SL72B	£24.19.6
40 Mk II stereo	£8.8.0	AP75	£16.19.6
2025T/C stereo	£8.17.6	SL75	£25.19.6
3000 stereo	£9.19.6	SL75B	£27.19.6
SP25 Mk II	£10.19.6	SL95B	£37.10.0
SL55	£11.12.6	A70/11	£11.19.6
SL60B	£14.19.6	401	£25.0.0

Carrage 7/6 extra each item.  
**TEAK PLINTHS & PERSPEX COVERS**  
1. For SP25, SL65, SL55, 3000, 2025 T/C 2025, 1000. £4.10.0  
2. For AP75, SL75, SL95 £5.19.6.  
3. For SP25 etc. to operate with lid in place £5.19.6.  
Carrage 7/6 extra each type. Full range of Garrard accessories available.



**SPECIAL OFFERS!**

Garrard SP25 fitted Goldring G800 cartridge and wooden plinth. Total list price £32.8.5.

OUR PRICE £19.15.0 Carr. 10/-

Plastic cover 25/- extra  
GOLDRING GL69 fitted Goldring G800 cartridge complete with deluxe base and cover. Total list price £50.16.0.

OUR PRICE £39 Carr. 20/-


**RTC249 4-TRACK TAPE DECK**

British Made  
Speeds 1 1/2", 3 1/2", 7 1/2" P.S. Marriott Heads, 7 1/2" Test tape. Push Button control, fully interlocking. Size 13" x 10" x 1 1/2" above unit plate. 24" below. Full instructions. £13.19.6 Carr. 7/6



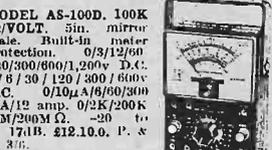**MULTIMETERS for EVERY purpose!**

**TE-51. NEW 20,000  $\Omega$  VOLT MULTIMETER**  
with overload protection and mirror scale. 0/6/60 120/1/200V. A.C. 0/3/30 60/300/600/3,000V. D.C. 0.40  $\mu$ A/12/300mA. D.C. 0/60K/6 meg. ohm. 0/2/6. P. & P. 2/6.



**TE-800 20,000  $\Omega$ /VOLT GIANT MULTIMETER**  
mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 v. A.C. 0/25/125/10/50/250/1,000/5,000v. D.C. 0/50  $\mu$ A/10/100/500mA/10 amp. D.C. 0/2K/200K/20 M $\Omega$ . O.H.M. £15. P. & P. 5/-.



**LAFAYETTE 57 Range Super 50K  $\Omega$  Volt Multimeter**  
D.C. volts 12 mV - 1000V. A.C. volts 1.5V - 1000V. D.C. current 25  $\mu$ A - 10 amp. Ohms 0 - 10 meg  $\Omega$ . 20 to +81 dB. Overload protection. £12.10.0. Carr. 3/6.

**MODEL AS-100D. 100K  $\Omega$ /VOLT. 5in. mirror scale. Built-in meter protection. 0/3/12/60 120/300/600/1,200V D.C. 0/3/30/120/300/600V A.C. 0/10  $\mu$ A/10/100/300 mA/12 amp. 0/2K/200K 1/2M/200M  $\Omega$ . -20 to +17.1dB. £12.10.0. P. & P. 3/6.**

**MODEL TE-200 20,000 O.P.V. Mirror scale, overload protection. 0/6/25/125/1,000 V.D.C. 0/10/50/250/1,000 V.A.C. 0/50  $\mu$ A/250 MA. 0/60K/6 meg. -20 to +4.2 db. 75/-.** P. & P. 2/6.

**MODEL TE-70. 30,000 O.P.V. Mirror scale, overload protection. 0/3/15/60/300/600/1,200V D.C. 0/6/30/120 600/1,200V A.C. 0/30  $\mu$ A/3/30/300mA. 0/16K/160 K/1.6M/7B Meg.  $\Omega$  £5.10.0. P. & P. 3/-.**

**MODEL PT-34. 1,000 O.P.V. 0/10/50/125/500/1,000V A.C. and D.C. 0/1/100/500mA D.C. 0/100K  $\Omega$ . 39/6. P. & P. 1/6.**

**MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection. 0/6/15/60/300/1,200V A.C. 0/6/30/130/600/1,200 V.A.C. 0/30  $\mu$ A/60mA/60mA 300mA/600mA. 0/8K/80K 800K/8 meg. -20 to +63 db. £5.19.6. P. & P. 3/-.**

**MODEL TE-10A. 20K  $\Omega$  Volt Mirror scale, overload protection. 0/3/15/100/500/1,500V. D.C. 0/10/50/100/500/1,000 v. A.C. 0/50  $\mu$ A/2.5mA/250mA D.C. 0/6K/6 meg. ohm. -20 to +22dB. 10.0, 100mFd. 0.100-0.1uFd. 69/6. P. & P. 2/6.**

**SAVE UP TO 33% OF HI-FI EQUIPMENT**  
Send for discount price list

**AVO CT471A MULTIMETER**

Battery operated, fully transistorised. Sensitivity 100m  $\Omega$ /v. Measures AC/DC Voltages 12mV to 1,200V. AC/DC Current 12mA to 1.2 Amp. Resistance 12 ohm to 120 M  $\Omega$ . HF, VHF, UHF Voltage with multiplier 4 to 400v up to 50 Mc/s, 40mV to 4v up to 1,000 Mc/s. Offered in perfect condition. £55 each. Carr. 10/-

**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**



Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.6. P. & P. 3/6.

**SINCLAIR EQUIPMENT**

Project 60. Package offers.  
2 x 250 amplifier, stereo 60 pre-amp. P25 power supply. £19.0.0.  
Carr. 7/6. Or with P26 power supply £21. Carr. 7/6.  
2 x 250 amplifier, stereo 60 pre-amp, P28 power supply. £21.10.0. Carr. 7/6.

Transformer for P28, 59/6 extra. Add to any of the above £4.17.6 for active filter unit and £16 for a pair of Q16 speakers. All other Sinclair products in stock. 2,000 amplifier £23. Carr. 7/6. Noteric amplifier £48. Carr. 7/6.

**SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS**

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 20v-230v. Model MR 2305 5 amp 68 x 48 x 43mm £8.7.6. Model MR 2310 10 amp 90 x 68 x 60mm £11.19.6. Postage 2/6

**TE111. DECADE RESISTANCE ATTENUATOR**

Variable range 0 - 111dB. Connections. Unbalanced T and Bridge T. Impedance 800  $\Omega$  range (0.1dB - 10) + (1dB X 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz (-3dB). Accuracy: 0.6dB. + Indication dB x 0.1. Maximum input less than 4W (50V). Built in 600  $\Omega$  load resistance with internal/external switch. Brand new £27.10.0. P. & P. 5/-.

**RECORDING HEADS**

COSMOGORD 4-track heads. High imp. record/playback 65/-, Low imp. erase 20/-  
MARRIOTT 4-track heads. High imp. record/playback 65/-, Low imp. erase 20/-, Post extra.

**AMERICAN TAPES**

First grade quality American tapes. Brand new. Discount on quantities.  
3in. 225ft. L.P. acetate ..... 3/6  
3in. 600ft. T.P. mylar ..... 10/-  
3in. 800ft. std. plastic ..... 8/6  
3in. 900ft. L.P. acetate ..... 10/-  
5in. 1,200ft. D.P. mylar ..... 15/-  
5in. 1,200ft. L.P. acetate ..... 12/6  
5in. 1,800ft. L.P. mylar ..... 18/-  
5in. 1,800ft. D.P. mylar ..... 22/6  
5in. 2,400ft. T.P. mylar ..... 39/6  
7in. 1,200ft. std. acetate ..... 12/6  
7in. 1,800ft. L.P. acetate ..... 15/-  
7in. 1,800ft. L.P. mylar ..... 20/-  
7in. 2,400ft. D.P. mylar ..... 25/-  
7in. 3,600ft. T.P. mylar ..... 45/-  
Postage 2/-, Over £3 post paid.

**TAPE CASSETTES**

Top quality in plastic library boxes.  
C90 90 min 8/6, 3 for 24/6  
C90 90 min 12/6, 3 for 38/-  
C120 120 min 15/-, 3 for 43/6  
Cassette Head Cleaner 11/3. Post Extra.

**G.W.SMITH & CO. (RADIO) LTD**

All Mail Orders to -  
147, Church Street, London, W.2  
Tel: 01-262 6562 (Trade supplied)

3, LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34, LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311, EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

### FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	3/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF114	4/-	2N1302-3	4/6
AF115	3/6	2N1304-5	5/-
AF116	3/6	2N1306-7	6/-
AF117	3/6	2N1308-9	6/-
AF239	12/6	2N3819 FET.	8/-
AF186	10/-	2N3844A	5/-
AF139	10/-	Power Transistors	
BFY50	4/-	OC20	10/-
BSY25	7/6	OC23	10/-
BSY26	3/-	OC25	8/-
BSY27	3/-	OC25	7/6
BSY28	3/-	OC26	5/-
BSY29	3/-	OC28	7/8
BSY95A	3/-	OC35	5/-
OC41	2/6	OC36	7/8
OC44	2/6	AD149	10/-
OC45	2/6	ADY 10	30/-
OC71	2/6	2N3055	15/-
OC72	2/6	28034	10/-
OC73	3/6	Diodes	
OC81	2/6	AAV42	2/-
OC81D	2/6	OA91	2/-
OC83	4/-	OA79	1/9
OC139	2/6	OA81	1/9
OC140	3/6	IN914	1/6

### NEW UNMARKED UNTESTED PAKS

H10 25	Mixed volts 1 1/2 watt Zeners Top Hat type.	10/-
B80 8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
H11 30	Mat series "Alloy" PNP Transistors.	10/-
B83 200	Trans. Makers rejects. NPN/PNP. Sil. and Germ.	10/-
B84 100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
H15 30	Top Hat Silicon Rectifiers 750 mA. Mixed volts.	10/-
B86 50	Sil. Diodes sub. min. IN914 and IN916 types.	10/-
H16 8	Experimenters' Pak of Integrated circuits. Data supplied.	10/-
B88 50	Sil. Trans. NPN, PNP, equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B60 10	7 Watt Zener Diodes. Mixed voltages.	10/-
H20 12	BY128/7 type Silicon Rectifiers 1 amp plastic. Up to 1,000 volts.	10/-
H6 40	250mW. Zener Diode DO-7 min. Class Type. AV.40% Good.	10/-

### NEW TESTED & GUARANTEED PAKS

B2 4	Photo Cells, Sun Batteries .3 to .5 volt, .5 to 2 ma.	10/-
H8 4	BY127 Silicon Recs. 1000 P.I.V. 1 amp. Plastic. Replaces the BY100	10/-
B79 4	1N4007 Sil. Rec. Diodes. 1,000 P.I.V. 1 amp. Plastic.	10/-
B81 10	Reed Switches, mixed types, large and small.	10/-
B89 2	5SP5 Light Sensitive Cells. Light Res. 400 Ω Dark 1M Ω	10/-
B91 8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45.	10/-
B92 4	NPN. Sil. Trans. A06 BSX20 2N2369 500 MHz, 360mW.	10/-
B93 5	GET113 Trans. equiv. to ACY17 to ACY21 PNP Germ.	10/-
B96 5	2N3138 PNP Sil Trans. TO-18, HFE 100-300 I.C. 600mA. 200MHz.	10/-
B98 10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NK271, etc.	10/-
H4 250	Mixed Resistors, Post and packing 2/-.	10/-
H7 40	Wirewound Resistors. Mixed Values. Postage 1/6.	10/-
H9 2	OCF71 Light Sensitive Photo Transistors.	10/-

**FREE!** Packs of your own choice up to the value of 10/- with orders over £4.

### RETURN OF THE UNBEATABLE P.I. PAK. NOW GREATER VALUE THAN EVER

Full of short lead semiconductor and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

**PI PLEASE ASK FOR PAK P.I. ONLY 10/-**  
2/- P. & P. on this Pak

Complimentary Set.  
NPN/PNP Germ.  
Trans., Pak F.3. **2/6**  
PAIR

**P.O. RELAYS 8 FOR**  
Various Contacts and Coil  
Resistances. **20/-**  
Post & Packaging 5/-

★ ALL OUR TESTED SEMICONDUCTORS HAVE A WRITTEN GUARANTEE ★

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENT WITH OUR FREE SUBSTITUTION CHART.

NO CONNECTION WITH ANY OTHER FIRM. MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order OVER SEAS AND EXTRA FOR AIR MAIL.

## LOOK AT THESE PRICES

### CARTRIDGES

Acos GP67-2, GP91-38C 22/6; Acos GP93-1 28/8; Acos GP94-1 22/6; Sonotone 9TAHC 39/6; All above in makers cartons; BSE X4H 80/-.

### 1 WATT AMPLIFIER

Complete with volume control, rectifier, smoothing ckt, fully transistorised, **OUR PRICE 27/3**

### PLUGS & SOCKETS

Phono plugs, red, white, yellow, green, grey, blue, black 11d 9/- per doz; Coaxial plugs, aluminium 1/6; Coaxial couplers 1/-; 2 pin DIN plugs 3/-; 3 pin DIN plugs 3/-; 5 pin DIN plugs 3/5; 2 pin, 3 pin DIN sockets 1/6; wander Plugs 6d; sockets 8d; Banana plugs 1/1, sockets 1/-; 3.5mm J/Plugs 1/6 & 2/6; Standard J/Plugs with solder terminals 2/-; Chrome 3/-; Side Entry J/Plugs black and chrome 4/9; Insulated j/sockets, o/ct 3/8, c/ct 3/6.

### ELECTROLYTIC CAPACITORS

4uF, 150v 9d; 8uF 500v 3/-; 8uF 12v 10d; 8uF + 8uF 450v 4/3; 10uF 150v 9d; 12uF 25v 9d; 10uF 450v 2/9d; 16uF + 16uF 450v 4/8; 30uF 150v 9d; 50uF 10v 9d; 100uF 9v 9d; 100uF 12v 9d; 150uF 12v 9d; 320uF 9v 1/-; 1500uF 30v 3/9; 2.5uF 16v 6d; 10uF 16v 1/6; 5000uF 25v 10/-; 10,000uF 25v 15/-; 20,000uF 30v 21/-.

### MICROPHONES

Acos Mic 45 22/6; Acos Mic 60 19/11; Planet CM70 30/-; Hand Mike 15/-; Shure 201 45; Shure 444 10.10.0.

### VALVES

PY81 7/2; PCL82 7/9; EF183 9/-; EF184 9/-.

## GEORGE FRANCIS (Dept PW),

83 Balderton Gate, Newark, Notts.  
Telephone: Newark 4783.

## BUY DIRECT FOR LOWEST PRICE!!

# SAVE £'s£'s!!

DESPITE RECENT  
PRICE INCREASES

LATEST NEW & IMPROVED "JULIETTE"  
NA5018A COMMUNICATIONS RECEIVER  
(with AFC)  
5 BAND MAINS/BATTERY SOLID STATE  
PORTABLE RECEIVER



**OUR PRICE 36 gns.**  
(cash only) + 9/- p/p  
**BFO-OPTIONAL**  
**EXTRA-ADD 35/-**

- AM Band: 540-1600 Kc's Full Medium wave cover.
- Marine Band: 1.6-4.6 Mc's Shipping, Hams, SW, etc.
- FM/VHF: 88-108 Mc's Radios 2, 3, 4; TV Sound, Public Services, etc.
- Aircraft 108-134 Mc's (improved sensitivity). Airlines and Ground Control
- PB (High VHF Band): 148-174 Mc's TV Sound, Fire, Ambulance, etc., Taxis, Shipping, Fuel Boards, Oil


Rigs, Gas and Electric Boards, Local Hams, Industrial and Commercial Mobiles, Military aircraft etc. (DEPENDENT ON LOCALITY).

**FEATURES**—4" Dynamic PM Speaker. Directional telescopic VHF aerial. Internal Ferrite rod aerial. Illuminated Dial, size 9 1/2" x 5 1/2" x 4". Weight 5 1/2 lbs. Impressive and sturdy design in Chrome and Black Leather. Ultra sensitive 15 transistor circuit. Earpiece and Socket. Leather carrying and shoulder straps. Batteries incl. (STANDARD EVER READY TYPE).

### RETAIL TRADERS SUPPLIED

Enquiries to wholesale dept.  
**STOCKTON PARTNERS (DEPT. PW)**  
**BRIGHOWGATE, GRIMSBY, LINCOS.**  
Tel: 0472 64196/58815  
Imports, Wholesale Electronic Equipment Distributors

## DIMMASWITCH

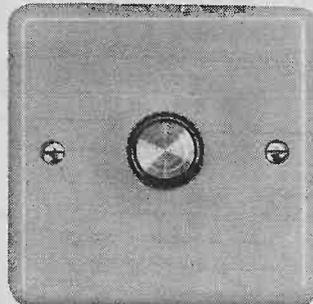

This is a dimmer of standard size in ivory and chrome to replace modern light switches without wiring change—controls 40-600W, 200/250V at 50Hz. of all lights except fluorescents.

Two models are available with on/off switch to control from maximum to zero.

DS500/2 at £3.12.6d. with clockwise or reverse dimming, with the switch at full reverse rotation.

DS500/2/P at £3.18s. uses a patented switch giving on/off control at any position of dimming.

Both are available in D.I.Y. kit form at 10/- less. Fuse protection is available at 2/6d. extra.

Please send C.W.O. to:


## DEXTER & COMPANY

ULVER HOUSE, 19 KING STREET  
CHESTER CH1 2AH  
Tel: Chester 25893

As supplied to H.M. Government Depts., Hospitals, Local Authorities, etc.

# DISCOSOUND

## DJ DISCO-AMP

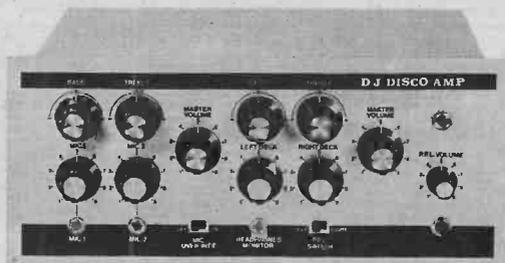

The DJ Disco-amp has been designed specifically for use with discotheques and has many exclusive features not normally found on P.A. amplifiers. The unit will be of use to the professional D.J. as well as in clubs and mobile discotheques.

The pre-amp section features independent inputs and volume controls for two mics with separate bass, treble and master volume, plus two independent inputs and volume controls for turntables, again with separate bass, treble and master volume controls.

A complete Pre-fade listen (P.F.L.) cueing monitor section is also featured with separate input for headphones (either stereo or mono) with an independent volume control for headphone monitoring, and a P.F.L. switch, so that either turntable can be monitored for accurate cueing up of records. A mic over-ride switch is also added which cuts the music volume by half so that mic announcements may be made over the music without altering the volume controls.

The power amplifier section has an output of 70 watts R.M.S. into 8 ohms and has elaborate protection against thermal, short or open circuit. The unit is designed for panel mounting.

### SPECIFICATION


Output power	70 watts R.M.S. $\pm$ 1db at 8 ohms.
Frequency response	30-20,000 Hz $\pm$ 3 db.
Harmonic distortion	Less than 1% at full output.
Signal/noise ratio	Better than - 65db.
Speaker impedance	8-16 ohms.
Headphone impedance	8-16 ohms.
Bass control	Variable 20 db at 100 Hz.
Treble control	Variable 20db at 10 kHz.
Inputs:	Mic 1 & 2 5 mV at 50 K ohms.
turntable	1 & 2 100mV at 1 meg ohm.

50 ohm or 600 ohm mic inputs may be ordered at extra cost.  
Size: Front Panel 16 $\frac{1}{2}$ " x 7". Cut out: 15 $\frac{1}{2}$ " x 6". Fuses: A.C. 1.5 amp (B.S.) mounted on back panel.

**PRICE £85.0.0 inc. P & P.**
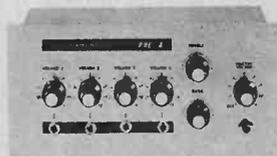
## DISCOSOUND PRE-4


This is a four channel fully mixable pre-amp, with separate treble, bass and master volume controls, and is completely self powered. All four inputs are by standard jack socket on the front panel with the addition of inputs 3 and 4 being duplicated on the back panel, with two paralleled outputs also featured for versatility in use. Frequency response: 30-20,000 Hz  $\pm$  3db. Signal/Noise Ratio: -65db. Size: front panel 12 $\frac{1}{2}$  x 5 $\frac{1}{2}$  cut out required 11 $\frac{1}{2}$  x 4 $\frac{1}{2}$ . Completely built and tested.



**PRICE £18.0.0 inc. P & P.**

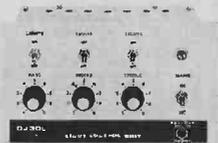
## DJ 30L PSYCHEDELIC LIGHT CONTROL UNIT

3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation. Completely built and tested.



**PRICE £37.10.0 inc. P & P.**

## DJ 70S INTEGRATED MIXER-AMPLIFIER

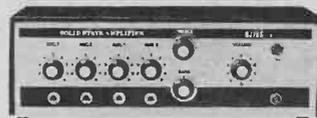

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70 watts R.M.S.) a frequency response (30-20,000 Hz  $\pm$  3db) that is superb, and distortion that is well below 1% even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs etc., or anywhere that high quality high output is required. Size: 15 $\frac{1}{2}$ in x 5in x 6in.

**PRICE £55.0.0 inc. P & P.**

Also available DJ105S 30 watt P.A. Amplifier. Similar specification to above.

**PRICE £35.0.0 inc. P & P.**

## DISCOSOUND 70 MAIN AMPLIFIER

A 70 watts RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response: 20-20,000 Hz  $\pm$  2db. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound PRE-4, or can be used with any other high quality pre-amp control unit. Size: 7" x 9" x 6". Completely built and tested on steel Chassis.

**PRICE £35.0.0 inc. P & P.**

For full details of these and all Discosound Products write direct to:—

**DISCOSOUND, 122 BALLS POND ROAD, LONDON, N.1. Tel: 01-254 5779**

Full money back guarantee if returned within 10 days.

All Discosound Products are guaranteed for 12 months.

Demonstrations given at any time.

# R.S.C. SENSATIONAL HIGH FIDELITY STEREO 'PACKAGE' OFFERS

★ Super 30 Amplifier (15+15 watt) in veneered housing  
 ★ Goldring Transcription Turntable on Plinth  
 ★ Shure or Goldring Magnetic Pick-up Cartridge  
 ★ Pair of Stanway II Loudspeaker Units  
 Special total price. Four fully wired units ready to "plug-in". Carr. 30%. **86 Gns.**

TA12 Amplifier (6.5+6.5 watt) in veneered housing. Garrard 3000 4 sp. Autochanger unit on plinth. Sonotone 9TA P.U. cartridge. Pair of Dorchester Loudspeaker units. Special Total Price **47 1/2 Gns.** Carr. 25%.

Matching as recommended for optimum performance. Send for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.



EXTREMELY ATTRACTIVE PLINTHS finished in Teak or Afrormosia veneer. Trans plastic cover.

★ Super 30 amplifier (15+15 watt) in veneered housing  
 ★ Garrard SP25 Mk II Turntable on Plinth  
 ★ Goldring CS90 Ceramic P.U. Cartridge with diamond stylus  
 ★ Pair Stanway II Speaker Units  
 Four fully wired units ready to "plug-in". Special total price **76 Gns.** Carr. 30%.

● TA12 Amplifier (6.5+6.5 watt) in veneered housing  
 ● Garrard SP25 Mk II 4 sp. player unit on plinth  
 ● Goldring CS90 Ceramic P.U. Cartridge **53 Gns.**  
 ● Pair of Dorchester Loudspeaker Units.  
 Special total price Carr. 25%.

Or Dep. £10.03 and 9 monthly payments **£5.15** (Total 59 gns.). Transparent plastic cover 3 gns. extra. **TERMS AVAILABLE ALL PACKAGE OFFERS**

## AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. "L" indicates Roll Rubber cone surround. Impedance 3 or 16 ohms. Please state choice. Exceptional performance at low cost.

HF801D 9" 8W 54/3 HF120 12" 15W 79/9  
 HF102D 10" 10W 67/11 HF120D 12" 15W 89/9  
 HF100D 10" 10W 67/11 HF126 12" 15W £5.15.0  
 HF106DL 10" 10W 69gns. HF126D 12" 15W £5.15.0

## HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak or Afrormosia veneer. Acoustically lined or flared acoustic damping. Ported where appropriate. credit terms available.



**DORCHESTER** Size 16 x 11 x 9 1/2 in. approx. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 1328lin. Dual Cone spkr. Imp. 3 or 16 ohms. **£8.19.9** Carr. 7/6

**STANWAY II** Size 20x18x9 1/2 in. approx. Rating 10 watts. Including 1328lin. speaker with highly flexible cone surround, long throw voice coil and 11,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. **16 Gns.**

## R.S.C. TA6 6 Watt HIGH FIDELITY SOLID STATE AMPLIFIER



200-250v. A.C. mains operated. Frequency Response 30-20,000 c.p.s. -20dB. Harmonic Distortion 0.8% at 1,000 c.p.s. Separate Bass and Treble

"lift" and "cut" controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 4-16 ohm spkrs. Max. sensitivity 6mV. Output rating 1.5 P.P.M. Fully enclosed enamelled case. 9 1/2 x 12 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **7 Gns.** Carr. 7/6  
**OR FACTORY BUILT with 12 months' guarantee. £8.19.9**

## RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amplifier or Tape recorder.

**RP2C** Garrard SP25 Mk II (with heavy turntable) fitted Goldring CS90 with compliance ceramic Stereo/Mono cartridge with diamond stylus. Carr. 9/6 **£24.12.6**

**RP5C** Garrard 2025 Auto Unit fitted Garrard GCS 23 Stereo Cartridge with diamond tip. Plinth & Cover as RP2C **15 Gns.**

Other types available with Magnetic cartridges and with alternative design plinths.

Limited Number of **CLEARANCE LINES** in leading makes of Hi-Fi equipment at Branches only

## R.S.C. PLINTHS



for Record Playing units, cut for Garrard 1025, 2025, 3000, AT80, SP25 etc. **3 gns.**  
**AVAILABLE WITH TRANSPARENT PLASTIC COVER 6 gns.**

## INTEREST CHARGES REFUNDED

On Credit Sales settled in 3 months.

## LINEAR L10 HIGH FIDELITY LOW AMPLIFIER 10 Gns.

with separate Pre-amp Magnetic P.U. matching. To clear

## R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram P.U. cartridge, Radio tuner, Tape recorder, 'Mike' etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. -20dB ★ Harmonic Distortion 0.3% at 1000 cps. Hum and Noise -70dB ★ Sensitivities (1) 50 mV. (2) 400 mV. (3) 100 mV. Output rating 1 H.F.M. ★ Handsome finish Facia plate and Knobs. Complete kit of parts with full wiring diagrams & instructions. **FACTORY BUILT with 12 mth gntee 17 Gns.** or Deposit **13 1/2 Gns.** £8 and 9 monthly payments **£8.10** (Total 19 1/2 Gns.). Or in Teak or Afrormosia veneer housing 20 1/2 Gns. Dep. 3 Gns. and 9 monthly payments 46/8 (Total 23 Gns.).



## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.15.0**

**OR SENIOR 15 WATT ICM. HF126 15,000 line 15ohm Speaker £6.15.0.** Carr. 6/6

## HI-FI SPEAKER ENCLOSURES

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 10% per enclosure.  
**JES** Size 16 x 11 x 9in. Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. **£4.14.6**  
**SES** For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported. **£5.15.0**  
**SE10** For outstanding results **SE12** For excellent performance with 12in. Hi-Fi speaker and Tweeter. **£6.19.9**  
 Size 24x15x10in. Ptd. **£5.19.9** Size 25 x 16 x 10 1/2 in.

## THE 'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size, only 25x14x10in. **COMPLETE KIT 20 Gns**  
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms Carr. 12/6  
 ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 8-way quarter section series cross-over system. (3) 8 x 8in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material (6) Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. 3 Gns. and 9 monthly payments 45/8 (Total £24 Gns.)



## R.S.C. TFM1 SOLID STATE VHF/FM RADIO TUNER

★ High-sensitivity. ★ 200-250v. A.C. Mains operation. ★ Sharp A.M. Rejection x ★ Drift-free reception. ★ Output ample for any amplifier (approx. 500 m.v.). ★ Output for feeding Stereo Multiplexer. ★ Tuner head using silicon Planar Transistors. ★ Designed for standard 80 ohm co-axial input. Visually matching our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. Printed circuitry. A quality product at considerably less than the cost of comparable units. **Factory built 18 gns.** Or in Teak finished cabinet as illustrated 21 gns. Terms: Deposit **£8.1.0** and 9 monthly payments. 2 gns. Total **£24.19.0**. Stereo version, 23 1/2 gns. Carr. 10/6 extra



# R.S.C. SUPER 30 MKII HIGH FIDELITY STEREO AMPLIFIER

High Grade Components Specifications comparable with units costing considerably more.

**TRANSISTORS** 9 high quality types in each channel.  
**OUTPUT** 10 Watts R.M.S. continuous into 15 Ω (per channel). 15 Watts R.M.S. continuous into 3 Ω.  
**INPUT SENSITIVITIES** Mag. P.U. 4 mV. Ceramic P.U. 35 mV. Tape Amp. 400 mV. Aux. 100 mV. Mic. 5 mV. Tape Head 2.5 mV.  
**FREQUENCY RESPONSE** ± 2 dB. 10-20,000 c.p.s.  
**TREBLE CONTROL** +17 dB to -14 dB at 10 Kc/s.  
**BASS CONTROL** +17 dB to -15 dB at 50 c/s.  
**HUM LEVEL** -80 dB.  
**HARMONIC DISTORTION** 0.1% at 10 watts 1,000 c.p.s.



Employing Twin Printed Circuits. 200/250v. A.C. mains operation. **CROSS TALK** 62 dB at 1,000 c.p.s.  
**CONTROLS** 5 Position Input Selector. Bass, Treble, Vol., Bal., Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.  
**INPUT SOCKETS** (1) P.U. (2) Tape Amp. (3) Radio, (4) Mic. or Tape Head. (Operation of Input Selector assures appropriate equalisation).  
**CHASSIS** Strong Steel construction. Approx. 12 x 3 x 8in.

**FACIA PLATE** Attractive design in rigid plastic silver background black lettering. Silver finish matching control knobs as available.  
 Eminently suitable for use with any make of pick-up or Mic. (Ceramic or Magnetic, Moving Coil, Ribbon or Crystal) currently available. Superb sound output quality can be obtained by use with first rate ancillary equipment.

**COMPLETE KIT OF PARTS 22 gns.** Point to point wiring diagrams and detailed instructions. Carr. 15/6  
**UNIT FACTORY BUILT 29 gns.** With 12 months guarantee. or Deposit **£4** and 9 monthly payments **69/8** (Total **£33.16.3**) or in Teak or Afrormosia veneer housing **82 Gns.** Carr. 15/6. Terms: Deposit **£4** and 9 monthly payments of **74/2** (Total **£37.7.8**). Send S.A.E. for leaflet.

## R.S.C. BATTERY/MAINS CONVERSION UNITS

Type BML An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram 59/9 or **ASSEMBLED 69/9.**  
**SUPER 15 HIGH FIDELITY SOLID STATE AMPLIFIER** Approx. as Super 30 but single channel. Complete kit with full constructional details and point to point wiring diagrams. **12 1/2 gns.** Carr. 12/6  
**OR FACTORY BUILT 15 1/2 Gns.** Carr. 12/6. Terms: Deposit 4 Gns. and 9 monthly payments **£11** (Total **£18.3.6**) Available in Teak or Afrormosia veneer housing **18gns.**

## PARTRIDGE "JOYSTICK" SHORT WAVE AERIALS AND TUNERS AT ALL BRANCHES (S.A.E. for full list)

- BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL** (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM** 30/31 Gt. Western Arcade (Half-day Wed.) 021-236-1279
- DERBY** 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. Waverley 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



HI-FI CENTRES LTD.

- 32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) **LEEDS** Tel. 28252
- 73 Dale St. (Half-day Wed.) Tel. CENTral 3573 **LIVERPOOL**
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. LONDON PAD 1629
- 60A Oldham Street (Half-day Wed.) Tel. CENTral 2778 **MANCHESTER**
- 106 Newport Rd. (Half-day Wed.) Tel. 47096 **MIDDLESBROUGH**
- 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLEUPON TYNE**
- 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

MAIL ORDERS TO: Audio House, Hancconer Lane, Leeds 13. No C.O.D. under £1. Terms C.W.O. or C.O.D. Postage 4/6 extra under £2. 5/9 extra under £5. Trade supplied. S.A.E. with enquiries. Branches open all day Sat. **MAIL ORDERS MUST NOT BE SENT TO SHOPS**

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



Highly sensitive. Push-Pull high output, with Pre-amp. Tone Control Stages. Performance figures of factory built units: Hum level -70dB. Frequency response  $\pm 3dB$  30-20,000/c/s. Sectionally wound output transformer. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 16mV. Suitable for high impedance microphones. Crystal or Ceramic P.U.s. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Radio or Tape. Reserve L.P. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250V. 500/c A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with point-to-point wiring diagrams and instructions. **15 Gns.** Carr. 12/6

Twin-handled perforated cover 35/- Supplied factory built with EL34 output valves. 12 months' guarantee for 18 gns. TERMS: Deposit £3.9.0 and 9 monthly payments of £2 (Total £21.9.0). Send S.A.E. for leaflet.

## R.S.C. A11 HIGH FIDELITY 12-14 WATT AMPLIFIER

PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP. Two input sockets with mixing facilities High sensitivity, 5 valves. Independent Bass and Treble controls. Frequency response  $\pm 3dB$  30-20,000 c/s. Hum level -60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments etc. Std. AC mains. For 3 & 15 ohm spkrs. SAE for leaflet. COMPLETE KIT. Full instructions **9 1/2 Gns.** and point-to-point wiring diagrams. Carr. 11/6. Twin handled metal cover 35/- PRICE FACTORY BUILT 131 gns. or Deposit £3 and 9 monthly payments of 30/5 (Total £16.13.9). RSC A11 TRANSISTORISED VERSION of above complete kit 9 Gns. (Assigned 13 Gns.)

## 30 WATT HI-FI AMPLIFIER

FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP A 4 input, 2 volume control Hi-Fi unit with separate Bass and Treble controls. B.V.A. valves. Peak output rating. Strong Resin covered cabinet with handles. Attractive black/gold facial panel. Neou indicator. For 200-250V. A.C. mains. For 3 or 15 ohm **19 Gns.** Carr. 12/6. Dep. 74/- & 9 mthly payments of 2 gns. (Total £22.12.0)

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 years' guarantee. High flux ceramic magnets. Heavy cast chassis.

'POP' 100	'POP' 60	'POP' 50	FANE LOUDSPEAKERS
18" 100Watt 14,500 gauss 8/150	15" 60 Watt 14,000 gauss 8/150	12" 50 Watt 14,000 gauss 10 GNS. 150	12" 25 Watt Dual cone 150 Unsuitable Bass Guitar or Elect. Organ.
21 GNS. Carr. free	12 GNS. Carr. free	10 GNS. 150 Carr. free	£5-19-9 Carr. free
Suit Bass or Rhythm Guitar or Elec. Organ		Gen. Purpose. Pr. req. for Base-Gtr.	

F.A.L. P.A. AMPLIFIERS PHASE 50 **29 GNS.** PHASE 100 **59 GNS.** S.A.E. for leaflets.

## R.S.C. COLUMN SPEAKERS

Covered in Resin and Vynair, ideal for vocalists and Public Address. 15 ohm matching.



TYPE C485 25/30 WATTS. Fitted four 8in. high flux 8 watt speakers. Overall size approx. 48 x 10 x 5in.

**16 Gns.** Carr. 10/-  
Or deposit £3 and 9 monthly payments 35/8 (Total £18.19.6)

TYPE C4125 50 WATTS. Fitted four 12in. 11,000 line 15 watt speakers. Overall size 58 x 14 x 9in. approx.

**26 Gns.** Carr. 15/-  
Or Deposit £4 and 9 monthly payments of 58/8 (Total £30.8.0)

## HIGH QUALITY LOUDSPEAKERS

In Teak or Alformosaa veneered Cabinets

L13 13" x 8" 8-10 Watt 10,000 lines 3 or 15 ohms **£4-19-9** Carr. 7/6

Type L12 12" 20 Watt 10,000 lines 15 ohms. **£8-19-9** Carr. 8/9

## R.S.C. BASS-REGENT 50 WATT AMPLIFIER



A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating.

★ Two extra heavy duty 12in. Loudspeakers.  
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls.

**55 Gns.** Carr. 30/- or dep. £13.4.9 and 9 monthly payments of £5.11.9. (Total 60 1/2 gns.) Send S.A.E. for leaflet.

G100 100 watt peak output with Pr. speaker columns and a Bass Unit (Six 12" and Two 15" Speakers). 98 1/2 gns.

## R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated. Primarys 200-250V. 500/c. Screened MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2in.

250V., 60mA, 6.3V. 2a. .... 17/11  
250-0-250V. 60mA 6.3V. 2a. .... 18/11

FULLY SHROUDED UPRIGHT MOUNTING  
250-0-250V. 60mA, 6.3V. 2a., 0-5-6.3V. 3a. 24/9  
250-0-250V. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. 33/9  
300-0-300V. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. 39/9  
300-0-300V. 130mA, 6.3V. 4a., c.t., 6.3V. 1a.

For Mullard 510 Amplifier **47/11**  
350-0-350V. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. 39/9  
350-0-350V. 130mA, 6.3V. 4a., 0-5-6.3V. 3a. 47/9  
425-0-425V. 200mA, 6.3V. 4a., c.t., sv. 3a. 59/9  
425-0-425V. 200mA, 6.3V. 4a., 6.3V. 3a., sv. 3a. 83/9  
450-0-450V. 250mA, 6.3V. 4a., c.t., sv. 3a. 99/9

TOP SHROUDED DROOP-THERO TYPE  
350-0-350V. 70mA, 6.3V. 2a., 0-5-6.3V. 2a. 23/9  
350-0-350V. 100mA, 6.3V. 3a., 0-5-6.3V. 2a. 27/9  
250-0-250V. 100mA, 6.3V. 2a., 6.3V. 1a. 28/9  
350-0-350V. 80mA, 6.3V. 2a., 0-5-6.3V. 2a. 29/11  
350-0-250V. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. 38/9  
300-0-300V. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. 39/9  
300-0-300V. 130mA, 6.3V. 4a., 0-5-6.3V. 1a. 46/9

Scalable for Mullard 510 Amplifier ... 46/9  
350-0-350V. 100mA, 6.3V. 3a., 0-5-6.3V. 3a. 39/9  
350-0-350V. 150mA, 6.3V. 4a., 0-5-6.3V. 3a. 46/11

## FILAMENT OR TRANSISTOR POWER PACK

Types 6.3V. 1.5a. 8/9; 6.3V. 2a. 9/9; 6.3V. 3a. 13/9; 6.3V. 6a. 22/9; 12V. 1a. 9/11; 12V. 3a. or 24V. 1.5a. 23/9; 0.9-18V. 11a. 19/11; 0.15-24V. 42a. 31/9

CHARGE TRANSFORMERS 0-0-15V. 1A. 18/9; 2A. 19/11; 3A. 21/11; 5A. 25/11; 6A. 29/9; 8A. 36/9.

AUTO (STEP UP/STEP DOWN) TRANSFORMERS  
0-110/120V. 200-230-250V., 50-80 watts 19/9;  
150 watts, 33/6 250 watts 49/9; 500 watts 105/-

OUTPUT TRANSFORMERS  
Standard Fentole 3,000  $\Omega$  or 7,000  $\Omega$  to 8  $\Omega$  8/9  
Push-Pull 8 watts EL84 to 3  $\Omega$  or 15  $\Omega$  11/9  
Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8 or 15  $\Omega$  24/9  
Push-Pull EL84 to 3 or 15  $\Omega$  10-12 watts 23/9  
Push-Pull Ultra Linear for Mullard 510, etc. 39/9  
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15  $\Omega$  35/9  
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15  $\Omega$  59/9


SMOOTHING CHOKES 150mA, 7-10H. 250  $\Omega$  12/9; 100mA, 10H, 200  $\Omega$  10/9; 80mA, 10H, 350  $\Omega$  8/9; 60mA, 10H, 400  $\Omega$  14/9.

SELENIUM RECTIFIERS F. W. (Bridged) All 6/12V. D.C. output. Max. A.C. input 18V. 1a. 4/3. 2a. 6/11. 3a. 9/9. 4a. 12/9. 6a. 15/9.
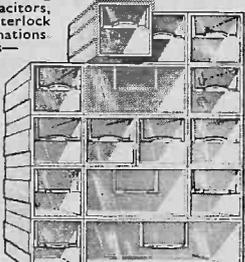
## multi-drawer storage units

NEW! HANDY! TIDY! I-N-T-E-R-L-O-C-K-I-N-G

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots—removable space dividers. Build up any size cabinet for wall, bench or table top.  
**BUY AT TRADE PRICES!**  
SINGLE UNITS (5ins x 2 1/2ins x 2 1/2ins) Usually 2/6 each. Our Price 24/- dozen  
DOUBLE UNITS (5ins x 4 1/2ins x 2 1/2ins) Usually 4/6 each. Our Price 40/- dozen  
**PLUS QUANTITY DISCOUNTS!** Orders £5 and over Deduct 1/- in the £  
Orders £10 and over Deduct 1/6 in the £  
Orders £20 and over Deduct 2/- in the £  
Packing/Postage/Carriage: Add 6/- to all orders under £3. Orders £3 and over, packing/postage/carriage free  
Quotations for Larger Quantities




**IVORYET LIMITED** (Dpt. PW9) 31 ALBERT RD. HENDON - LONDON NW4  
A place for everything Everything in its place!

## BUILD YOUR CIRCUITS on VEROBOARD

—the Universal Wiring Board—obtainable from your local Retailer  
Trade enquiries to: **NORMAN ROSE (ELECTRICAL) LTD.** 8 St. Chad's Place, Gray's Inn Road, London, W.C.1  
Technical enquiries to: **VERO ELECTRONICS LTD.** Industrial Estate, Chandler's Ford, Hants
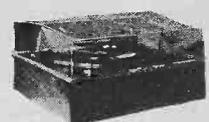
## GARRARD PRICES SLASHED!!! SP25 MkII £10-15-0 p.p. 10/-



**PLINTHS & COVERS**  
Teak finish, slenderly designed, ready for use. For Models SP25, 2025, 3000, SL65B. Spindle can be left in position whilst cover on. Cover tinted smokey.

## FANTASTIC VALUE 79/6 p.p. 7/6

**GARRARD TURNTABLES**

2025TC Son. 9talc dia.	£9 10 0
SP25 Mk. II less cart.	£10 15 0
3000 Son. 9talc dia.	£9 12 6
SL65B Son. 9talc dia.	£13 19 6
AP75 less cart.	£15 19 6
SL72B less cart.	£24 0 0
SL75B less cart.	£25 0 0

p.p. 10/- on each of the above

**MISC**  
L.L. Nova 565 Amp. Mag. & Cer. Cart. Input 5 watts per Chan. £15.10.0 p.p. 10/-.

**GARRARD SP25 AND OTHERS ON PLINTHS WITH COVERS**  
Complete, not wired. SP25. £14.12.6 p.p. 15/- Ready wired with 5 pin DIN or Phono 10/6 extra.  
For any other deck, 3000, 2025TC, SL65B, add price of deck to plinth and cover and 15/- p.p. and 10/6 for wiring.

"Master!" Magnetic Cart-ridge, Diamond Stylus. 65/- p.p. 5/-.

3 Way Speaker System. Teak cabinet size 14 1/2 x 8 x 6. 10 watts peak. £5.19.6 p.p. 7/6

Best Stereo Headphone 8 $\Omega$ , good quality. 52/6 p.p. 5/-.

**AUDIO SUPPLIES (QUOTE PW)**  
Callers—50A STAMFORD HILL, LONDON, N.16  
Mail orders—103A DALSTON LANE, LONDON, E.8 (Quote PW)  
TELEPHONE: 01-806-3611 or 01-254-4957  
Open Mon.-Sat. 9 a.m.-6 p.m. Thur. half day, Open Sunday 10 a.m.-2 p.m.

## This MONTH'S Best Buy ...



### AKG K50 Dynamic Stereo headphones

Complete with spare ear muffs.

Total (value £108/0d.) Our Price **£5.18.** + 4/6 p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

- \* High-fidelity reproduction due to broad frequency response (20-20,000Hz)
- \* Substantially increased stereo effect
- \* Headphones fit the head gently and do not shift
- \* Earpieces fit ears snugly (Cardanic suspension)
- \* Tone quality superior to conventional loudspeakers. Only expensive studio loudspeakers can match the reproduction quality of the K50
- \* Music can be reproduced at concert hall volume (1), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.



### GARRARD SP25

mk II **£10.19.6** Plus 10/- carriage


Normal price £15.11.4

Single record playing unit. Features include cue and pause and automatic pick-up return and switch off.

Wired with mains cable and 5ft. twin screened stereo cable, 5 pin plug, 10/6 extra.

AP75 Complete with base and cover **£25** plus 15/- carriage.
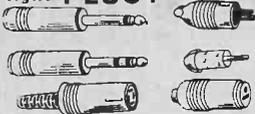
### Having trouble getting the right PLUG ?



Pack 107 5 Pin Din ... 4/-d.  
 Pack 108 3 Pin Din ... 3/6d.  
 Pack 135 3/4" Jack ... 5/-d.  
 Pack 130 3/4" Jack Stereo ... 9/6d.  
 Pack 103 Loudspeaker Plug ... 3/-d.  
 Pack 100 Phono Plug ... 1/3d.  
 Pack 230 3 pin Socket ... 4/6d.  
 Pack 236 5 pin Socket ... 6/-d.  
 Pack 234 Loudspeaker Socket ... 6/-d.  
 Special express delivery 6d. per unit postage. S.A.E. for list of plugs, sockets, drive belts, ready-made leads etc.

### PLINTH and COVER **£5.5.**

Unbeatable Value plus 10/- p. & p.

Suitable for AT60; SP25; 3000; 2500; 3500. Superb finish. Spindle can be left in position with cover on. Cover of neutral smoke tint perspex.

Also available for AP75; SL99; SL75 **£8.17.6** plus 10/- carr.



### Replacement Stereo DIAMOND STYLUS

8TA 9TA 9TAHC GP91 ST4 ST9 EV26 GC8 **15/-** each others on request p. & p. 1/6

### Countdown SPEAKER

Teak Cabinet

**£12** insurance & carr. 7/6

A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.



### EMI 20w MATCHED SPEAKER SET 350

rec. price £12.10.

**£6.19.6**

plus 7/6 p. & p.



13.5" x 8.125" elliptical woofer coupled to a coaxially mounted 3.125" high frequency choke and condenser dividing network. The high frequency unit has a critically curved cone and also uses a high flux ceramic magnet.

Also EMI 450 SPEAKER

our price **65/-** plus 7/6 carr.

### SINCLAIR Project 60

SAVE nearly £6 Normal price £24.18.0d.



Designed for building into plinths etc., complete with two Z30 Output stages **£19** plus 10/- carr.

(20 watt) and power supply unit. Send S.A.E. for full technical brochure. **SINCLAIR 2000 AMPLIFIER** SAVE 6gns. Our price 23gns.

### Magnetic cartridges

Diamond **95/-** styli

plus 2/6 p. & p.

Today's value **£6.**

Stylius replacement can be carried out without removing cartridge. Fully guaranteed.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) 25/- 2/6 p. & p.



### SONOTONE Cartridges ...

(Filled Diamond Styli) (Ceramic) list price 82/-

Sensitivity: 9TA 80mV **47/6**

9TAHC 55mV/cm/sec rms minimum at 45° plus

1,000Hz measured on 2/6

Decca SXL2057 p. & p.



# J. J. FRANCIS

(WOOD GREEN) LTD

123 ALEXANDRA ROAD, HORNSEY, LONDON, N.8. Tel: 01-888 1662

When in LUTON, BEDS, you must visit the ...

## SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.

Closed all day Wednesday.

## SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, BEDS

# RADIO COMMUNICATION HANDBOOK


over 22,000 copies sold

Now in its second printing

The standard work in its field

832 pages of everything in the science of radio communication. The handbook's UK origin ensures easy availability of components. **69s post paid**

RADIO COMMUNICATION HANDBOOK

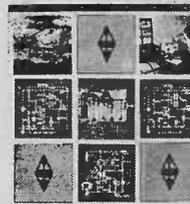

## Amateur radio circuits book

by George Jessop, G6JP

Second edition; reprinted 1970

Designed to meet the needs of the home constructor and experimenter. A comprehensive collection of up-to-date circuits covering a wide variety of applications. **13s 4d post paid**

## THE VHF-UHF MANUAL

By George Jessop, G6JP

A complete manual for frequencies above 30 MHz. Covers aerials, receivers, transmitters and test equipment. The first book of its kind outside the USA. **23s post paid**

Obtainable from:

**RADIO SOCIETY of GREAT BRITAIN**  
 35 DOUGHTY STREET, LONDON, WC1N 2AE

FREE LIST! SEND S.A.E. FOR BUMPER FLOG LIST

## TECHNICAL TRADING

FANTASTICALLY POPULAR

### ★ JASON TAPE ★

We offer you fully sensitized polyester mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. **TRY ONE AND PROVE IT YOURSELF!**

Standard Play		Long Play	
3in. 150ft.	2/3	3in. 225ft.	2/9
4in. 300ft.	4/6	4in. 450ft.	5/6
5in. 600ft.	7/6	5in. 900ft.	10/6
5 1/2 in. 900ft.	10/6	5 1/2 in. 1,200ft.	13/-
7in. 1,200ft.	12/6	7in. 1,800ft.	18/6
Double Play		Triple Play	
3in. 300ft.	4/-	4in. 900ft.	13/-
4in. 600ft.	8/-	5in. 1,800ft.	25/-
5in. 1,200ft.	15/-	5 1/2 in. 2,400ft.	34/-
5 1/2 in. 1,800ft.	19/6	7in. 3,600ft.	44/-
7in. 2,100ft.	27/-	Quaduple Play	
		3in. 600ft.	8/6

BARGAIN SPRING SALES AT ALL BRANCHES

- ★ LONDON (MUS 2639) 10 Tottenham Court Road
- ★ PORTSMOUTH (Tel. 22034) 350-352 Fratton Road
- ★ SOUTHAMPTON 72 East Street (Tel. 25851)
- ★ BRIGHTON (Tel. 23975) 8 Queen's Road

Postages 1/- reel. Post Free less 5% on three reels. Quantity and Trade enquiries invited.

All mail orders to DEVONIAN COURT, PK. CRES. PLACE, BRIGHTON (Tel. 880722)

# SMITHS FOR SERVICE & TOP DISCOUNT

## AMPLIFIERS

	Rec. Retail Price	Discount Price
ARENA F210 ...	£36 15 0	£29 10 0
ARMSTRONG 521 ...	£52 0 0	£44 0 0
CORAL 550 ...	£59 0 0	£48 0 0
DULCI 207 ...	£25 0 0	£17 0 0
ULCI 207M ...	£30 0 0	£21 10 0
GOODMANS Maxamp ...	£54 0 0	£42 10 0
GRUNDIG SV140 ...	£198 15 0	£157 10 0
GRUNDIG SV85 ...	£147 3 9	£125 0 0
LEAK Stereo 30 plus chassis ...	£53 0 0	£43 10 0
LEAK Stereo 30 plus teak ...	£59 10 0	£48 12 6
LEAK Stereo 70 chassis ...	£65 0 0	£53 10 0
LEAK Stereo 70 teak ...	£71 10 0	£57 10 0
LUX SQ 777 ...	£67 7 6	£59 5 0
LUX SQ 505 ...	£97 10 0	£79 10 0
LUX SQ 1220 ...	£124 10 0	£104 10 0
INEAR LT 66 ...	£18 18 0	£15 10 0
L.L. NOVA AMP ...	£30 9 0	£22 10 0
METRO SOUND ST20 ...	£32 0 0	£27 0 0
NIKKO TRM 30 ...	£36 0 0	£29 19 6
NIKKO TRM 40K ...	£46 10 0	£39 10 0
NIKKO TRM 50 ...	£95 10 0	£50 19 6
NIKKO TRM 120 ...	£95 0 0	£74 10 0
PHILIPS RH 580 ...	£26 0 0	£19 19 6
QUAD 33 and 303 ...	£98 0 0	£85 0 0
ROGERS Ravensbrook ...	£45 0 2	£37 10 0
ROGERS Ravensbrook Teak ...	£49 0 0	£39 10 0
ROGERS Ravensbourne Teak ...	£59 10 0	£48 10 0
ROTEL 100 ...	£64 0 0	£52 10 0
J.L. SUGDEN A51 Mk.2 ...	£44 0 0	£37 10 0
J. E. SUGDEN A51 C51 ...	£108 0 0	£49 10 0
SANSUI AU 222 ...	£62 17 7	£51 10 0
SANSUI AU 555 ...	£80 9 7	£65 0 0
SINCLAIR 2000 ...	£30 9 0	£23 15 0
SINCLAIR project 60 with PZ5 ...	£28 7 0	£20 10 0
TELETON SAQ 203E ...	£38 5 0	£29 0 0

## FM TUNERS

	Rec. Retail Price	Discount Price
ARENA F211 ...	£44 2 0	£36 15 0
ARMSTRONG 523 ...	£52 9 0	£44 17 6
ARMSTRONG 524 ...	£40 4 6	£34 17 6
ARMSTRONG M8 Dec. ...	£9 10 0	£7 15 0
DULCI FMT7 ...	£22 1 0	£17 19 6
DULCI FMT7S ...	£31 0 0	£25 5 0
GOODMANS Stereo-max ...	£82 10 0	£70 10 0
GRUNDIG R.T. 40M ...	£126 9 3	£104 10 0
GRUNDIG R.T. 100 ...	£181 11 9	£149 10 0
LEAK Stereofetic ...	£59 13 10	£50 19 6
LEAK teak ...	£67 3 6	£56 19 6
L.L. NOVA Tuner ...	£40 9 0	£32 10 0
NIKKO Fam 12F ...	£68 8 3	£59 10 0
PHILIPS RH690 ...	£39 0 0	£33 0 0
ROGERS Ravensbrook FET Teak ...	£51 10 0	£44 10 0
ROGERS Ravensbourne FET Teak ...	£61 17 9	£52 12 6
SINCLAIR 2000 ...	£26 14 6	£19 15 0
SANSUI TU555 ...	£69 20 0	£69 20 0
SANSUI TU777 ...	£82 10 0	£82 10 0
TELETON GT101 ...	£42 0 0	£42 0 0

## TUNER AMPLIFIERS

	Rec. Retail Price	Discount Price
ARENA T 1500F ...	£72 9 0	£62 15 0
ARENA T 2600 ...	£104 9 0	£89 10 0
ARENA T 2700 ...	£97 13 0	£82 10 0
ARENA T 9000 ...	£303 9 0	£255 0 0
ARMSTRONG 525 ...	£87 16 9	£74 15 0
ARMSTRONG 526 ...	£98 15 6	£85 10 0
GOODMANS 3000 ...	£77 14 9	£67 10 0
GRUNDIG RTV 400 ...	£172 6 5	£145 0 0
GRUNDIG RTV 600 ...	£212 0 0	£177 10 0
GRUNDIG RTV 650 ...	£243 17 10	£207 10 0
LUX SQ 555 ...	£187 10 0	£149 10 0
NIKKO STA 301 ...	£99 10 0	£84 10 0
NIKKO ST 501 ...	£121 17 11	£102 10 0
NIKKO ST 701 ...	£136 3 11	£112 10 0
SANSUI 200 ...	£89 10 0	£79 10 0
SANSUI 350 ...	£129 11 0	£105 0 0
SANSUI 800 ...	£148 0 0	£120 0 0
SANYO DC60E ...	£99 0 0	£84 10 0
ROTEL 130 ...	£79 10 0	£68 0 0

## SPEAKERS

	Rec. Retail Price	Discount Price
PHILIPS RH781 ...	£74 19 6	£63 10 0
PHILIPS RH91 ...	£83 10 0	£71 10 0
TELETON CR10T ...	£39 10 0	£35 0 0
TELETON F3000 ...	£51 19 0	£39 10 0
TELETON MX900 ...	£64 12 0	£49 10 0
TELETON R8000 ...	£69 10 0	£52 10 0
TELETON TFS50 ...	£100 10 0	£79 10 0
ARENA HT7 ...	£19 19 0	£16 15 0
ARENA HT10 ...	£22 1 0	£18 17 6
ARENA HT20 ...	£32 11 0	£27 15 0
ARENA HT21 ...	£10 10 9	£9 0 0
ARENA HT26 ...	£78 15 0	£65 10 0
ARENA HT27 ...	£18 18 0	£14 15 0
ARENA HT28 ...	£17 17 0	£13 17 6
B & W DM1 ...	£32 0 0	£26 10 0
B & W DM3 ...	£63 0 0	£54 10 0
B & W DM70 ...	£139 0 0	£117 10 0
CESTION Ditton 10 ...	£21 3 2	£17 5 0
CESTION Ditton 15 ...	£29 0 0	£23 0 0
CESTION Ditton 25 ...	£59 17 0	£45 0 0
DULCI AS3 ...	£9 9 0	£8 0 0
GOODMANS Maxim ...	£20 15 6	£16 15 0
GOODMANS Marimba ...	£24 0 5	£19 15 0
GOODMANS Mezzo II ...	£30 18 0	£24 0 0
GOODMANS Magister K ...	£40 2 0	£29 19 6
GOODMANS Magister ...	£57 0 0	£45 0 0
GRUNDIG System 300 ...	£66 4 10	£52 10 0
GRUNDIG System 412 ...	£86 7 10	£72 10 0
GRUNDIG System 740 ...	£176 9 10	£145 0 0
KEF Cresta ...	£22 3 7	£18 0 0
KEF Celeste Mk. 2 ...	£29 0 0	£22 10 0
KEF Concord ...	£43 10 0	£34 0 0
KEF Concord ...	£43 10 0	£34 0 0
KEF Concerto ...	£53 10 0	£42 10 0
LEAK Mini Sandwich ...	£29 15 0	£22 15 0
LEAK Sandwich ...	£43 10 0	£32 10 0
LOWTHER Acousta PM6 ...	£45 10 0	£37 10 0
MORDAUNT SHORT MS 100 ...	£40 19 0	£35 0 0
MORDAUNT SHORT MS 600 ...	£57 15 0	£45 0 0
PHILIPS RH481 per pair ...	£22 0 0	£17 10 0
PHILIPS RH481 per pair ...	£36 0 0	£29 0 0
SINCLAIR Q14 per pair ...	£8 2 5	£7 10 0
SANYO SX-X per pair ...	£37 16 0	£32 10 0
SANYO SX6 per pair ...	£79 16 0	£65 0 0
WHARFEDALE Denton ...	£37 16 0	£30 10 0
WHARFEDALE Super Linton ...	£45 0 0	£37 10 0
WHARFEDALE Melton ...	£29 10 0	£23 0 0
WHARFEDALE Dove-dale III ...	£39 10 0	£31 0 0
WHARFEDALE Aire-dale ...	£69 10 0	£56 10 0
WHARFEDALE Rose-dale ...	£57 0 0	£47 10 0
WHARFEDALE Unit 3 ...	£11 19 0	£9 15 0
WHARFEDALE Unit 4 ...	£16 0 0	£13 10 0
WHARFEDALE Unit 5 ...	£23 10 0	£19 0 0

## PLAYING DECKS

	Rec. Retail Price	Discount Price
GARRARD 401 ...	£31 14 2	£27 0 0
GARRARD SL95B ...	£45 9 1	£34 10 0
GARRARD SL75B ...	£35 12 2	£25 10 0
GARRARD SL65B ...	£19 6 5	£15 10 0
GARRARD SP25 ...	£15 15 11	£11 7 6
GARRARD AP75 ...	£23 16 0	£17 15 0
GARRARD 2025 T/C ...	£11 3 11	£9 10 0
GOLDRING GL69 ...	£25 1 6	£19 19 6
GOLDRING GL69D ...	£33 11 9	£27 10 0
GARRARD GL75 ...	£36 8 2	£28 10 0
GOLDRING GL75P ...	£46 18 6	£37 10 0
GOLDRING G99 ...	£24 14 1	£19 10 0
GOODMANS 3025 ...	£37 14 9	£31 10 0
THORENS TD150 A Mk. II ...	£43 12 7	£33 10 0
THORENS TD150 AB II ...	£47 8 7	£39 10 0
THORENS TD124 II ...	£46 15 10	£39 0 0
THORENS TD125 ...	£75 17 8	£59 10 0
THORENS TD125 AB ...	£120 3 11	£95 0 0

## STEREO CARTRIDGES

	Rec. Retail Price	Discount Price
AUDIO TECHNICA AT66 ...	£6 4 8	£5 10 0
AUDIO TECHNICA AT215 ...	£8 14 4	£7 10 0
AUDIO TECHNICA AT21X ...	£15 9 11	£13 0 0

	Rec. Retail Price	Discount Price
ADC 660 ...	£16 6 6	£13 10 0
ADC 10E Mk. II ...	£46 4 2	£36 10 0
GOLDRING C850 ...	£6 10 0	£5 10 0
GOLDRING G800 ...	£13 0 0	£10 0 0
GOLDRING G800E ...	£18 17 1	£15 10 0
GOLDRING G800 S/E ...	£26 0 0	£19 10 0
GOLDRING C590 ...	£5 4 0	£4 7 6
GOLDRING C591E ...	£7 16 1	£6 10 0
NEAT V70 ...	£5 4 8	£4 7 6
NEAT V70EZ ...	£7 15 3	£6 12 6
PICKERING V15/AMEZ ...	£19 5 10	£16 10 0
PICKERING V15 AM2 ...	£13 17 6	£11 10 0
PICKERING V15 AC2 ...	£10 14 8	£8 7 6
PICKERING V115 AC2 ...	£8 8 0	£6 17 6
SHURE M3D M ...	£7 8 3	£6 0 0
SHURE N3D ...	£5 11 2	£4 5 0
SHURE M31E ...	£12 19 5	£10 5 0
SHURE N31E ...	£9 5 3	£7 5 0
SHURE M32E ...	£12 0 11	£9 10 0
SHURE N32E ...	£8 6 9	£6 10 0
SHURE M44 7 ...	£10 3 10	£8 5 0
SHURE N44 7 ...	£6 9 8	£5 2 6
SHURE M44E ...	£14 16 6	£12 0 0
SHURE N44E ...	£10 3 10	£8 2 6
SHURE M55E ...	£16 13 6	£13 0 0
SHURE N55E ...	£11 12 4	£8 5 0
SHURE M75/6 ...	£16 13 6	£13 0 0
SHURE N75/6 ...	£8 6 9	£6 10 0
SHURE M75 EJ ...	£24 1 9	£19 0 0
SHURE N75 EJ ...	£11 2 4	£8 12 6
SHURE V15 II ...	£40 15 3	£31 10 0
SHURE VN15E ...	£16 13 6	£14 10 0

## STEREO TAPE DECKS AND RECORDERS

	Rec. Retail Price	Discount Price
AKAI 4000D ...	£87 10 0	£74 10 0
AKAI 1710W ...	£109 0 0	£89 10 0
AKAI 1710L ...	£109 0 0	£89 10 0
AKAI 150D ...	£130 2 4	£109 10 0
AKAI 1800 SD ...	£199 0 0	£165 0 0
REVOX 1104 ...	£204 15 0	£184 10 0
PHILIPS 4404 ...	£80 0 0	£67 10 0
PHILIPS 4407 ...	£103 15 4	£87 0 0
PHILIPS 4408 ...	£136 5 0	£110 0 0
SANYO MR 801 ...	£79 0 0	£67 10 0
SANYO MR 929 ...	£100 16 0	£86 0 0
SANYO MR 939 ...	£110 0 0	£91 10 0
SANYO MR 800 ...	£89 0 0	£75 0 0
TELETON FXB 570D ...	£52 10 0	£43 10 0
SHARP RD 712 ...	£75 0 0	£60 0 0
UHER 4200L ...	£162 14 10	£130 0 0
UHER 4400L ...	£162 14 10	£130 0 0

## TRANSCRIPTION ARMS

	Rec. Retail Price	Discount Price
SME 3009 with S2 shell ...	£31 6 3	£24 19 6
SME 3012 with S2 shell ...	£33 5 3	£26 19 6
GOLDRING L75 ...	£12 10 0	£9 19 6
GOLDRING L69 ...	£9 5 9	£8 5 0
NEAT G30 ...	£11 14 1	£9 10 0
NEAT G30 B ...	£13 18 5	£11 10 0

## STEREO HEADPHONES

	Rec. Retail Price	Discount Price
AKAI ASE9SE ...	£6 16 0	£5 10 0
SANSUI SS2 ...	£7 14 6	£6 10 0
SANSUI SS20 ...	£16 10 0	£13 15 0
TELETON SH301D ...	£4 10 0	£3 10 0
SHARP HP100 ...	£5 17 6	£4 10 0
GARRARD SP25 Mk. II complete with De Luxe plinth and perspex cover ready wired to 5 pin din plug ...	£21 15 0	£15 15 0
GARRARD AP 75 complete with De Luxe plinth and perspex cover ready wired to 5 pin din plug ...	£33 15 0	£23 19 6
GOLDRING GL75 with goldring plinth and hinged perspex cover ready fitted with Goldring 800E cartridge ready wired to 5 pin din or phono plug ...	£67 19 10	£54 0 0

All goods are in manufacturer's sealed cartons and are insured against loss or damage in transit. Guaranteed "by return" service. Carriage 10/- for speakers & stereo tape recorders, 7/6 for amplifiers, tuners, playing decks, tape decks, 5/- for cartridges, headphones and transcription arms. Send cash/cheque with order. Personal callers very welcome. 9.30 am—6 pm. Monday to Saturday. Thursday ½ day closing.

**Smith's Radio Service (Wolverhampton) Ltd.**


Mail Order Department, 26 Victoria Street, Wolverhampton, Staffs. Tel: Wolv. 29246

# LOOK!

**PRACTICAL!**

**VISUAL!**

**EXCITING!**

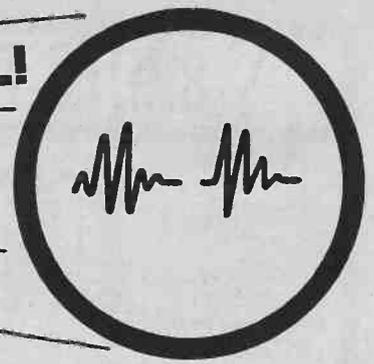


*a new 4-way method of mastering*

## **ELECTRONICS**

*by doing — and — seeing ...*

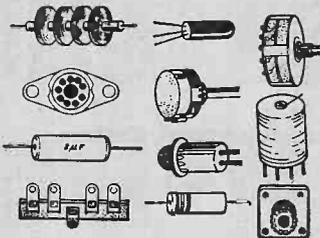
### **1 ▶ OWN and HANDLE a**

complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



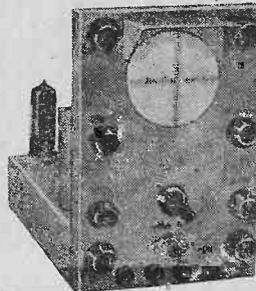
### **2 ▶ BUILD and USE**

a modern and professional **CATHODE RAY OSCILLOSCOPE**



### **3 ▶ READ and DRAW and**

**UNDERSTAND** **CIRCUIT DIAGRAMS**

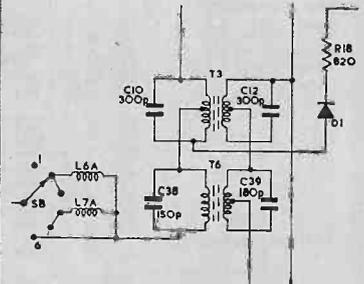

### **4 ▶ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK ... INCLUDING ...**

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME ..... **BLOCK CAPS**

ADDRESS ..... **PLEASE P.W.9**

# PRACTICAL WIRELESS

VOL 46 NO 5

Issue 763

SEPTEMBER 1970

## TOPIC OF THE MONTH

### Showtime

**T**EMPUS, as they say, certainly fugits. And here we are once again in that fag-end of the British summer which has become known traditionally as "show time". To add emphasis to this exhibition oriented season, the annual RSGB show has, this year, moved up from its usual October date to August, finishing at the time the round of annual radio trade shows begin. It is hoped that regular visitors to the RSGB show (known officially as the International Radio Engineering and Communications Exhibition—or Radiocom 70—) have taken note of this change of date; it is now August 19-22. For full details please refer to page 360. We hope many readers will be there; Practical Wireless will have the usual display of constructional projects on show.

After all this activity, the Audio Fair follows on in October. Once again Practical Wireless will be supporting the exhibition with displays and demonstrations of a range of audio projects, plus a special competition for the occasion. It is all a little feverish for those intimately connected with the trade and the technical press.

With the RSGB exhibition, so far as P.W. is concerned, our participation is very largely a matter of preaching to the converted, yet we think it well worthwhile to take part. Anything that encourages a greater interest in home construction meets with our approval and the RSGB exhibition has always stressed this side of the hobby. This year we are pleased to learn that small stands will be available to non-trade members of the Society to display and sell pieces of equipment.

Until fairly recent times, most radio amateurs built all their station gear. Nowadays the more general thing is to use commercially built transmitters and receivers. Whether this is due to that mysterious phenomena of having more leisure time than ever but less time to spare for building, or merely to being more affluent is hard to calculate.

But if amateurs cannot or will not build their own main equipment, then they can learn one lesson from the P.W. stand. That is, that there are very many auxiliary pieces of equipment that anyone can find the time to build, not only directly connected with the radio amateur station but in the various allied fields of radio, audio and electronics.

W. N. STEVENS—*Editor.*

**OCTOBER ISSUE WILL BE PUBLISHED  
ON SEPTEMBER 4**

## NEWS AND COMMENT

Leader	345
News . . . News . . . News . . .	346
On the Short Waves <i>by Malcolm Connah and David Gibson, G3JDG</i>	359
MW Column <i>by Charles Molloy</i>	365
Practically Wireless <i>by Henry</i>	389

## CONSTRUCTIONAL

Vibrasonic 25-50 Guitar Amplifier Part 1 <i>by F. C. Judd</i>	348
3-Band Preselector <i>by A. S. Carpenter, G3TYJ</i>	355
27MHz Field Strength Meter <i>by Richard Collins</i>	363
Car Aerial Signal Booster <i>by P. Hand</i>	364
Organ Pedal Bass Unit <i>by A. Lester-Rands</i>	368
Low Band V.H.F. Converter <i>by R. Bunney</i>	373
Take 20, Multimeter Extras <i>by Julian Anderson</i>	376
I.C. of the Month, Motorola MFC 4000P Audio Amplifier <i>by L. A. J. Ireland</i>	377
Transmitter/Receiver for the L.F. Bands, Further Notes, <i>by F. G. Rayer, G3OGR</i>	386
Two-Tone Tester <i>by A. S. Carpenter, G3TYJ</i>	393

## OTHER FEATURES

Project Autumn Entry Form	354
Checking Surplus Crystals <i>by Arthur Dow</i>	366
Going Back <i>by Colin Riches and Arthur Dow</i>	381

©IPC Magazines Limited 1969. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitation in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, E.C.4. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, E.C.4. Orders for back numbers should be addressed to IPC Magazines Ltd., Back Numbers Department, Carlton House, Gt. Queen Street, London W.C.2.

# NEWS... NEWS... NEWS...

## Dixons Stereo



When Dixons Photographic entered the Audio HiFi field in depth, their first units were updated versions of existing record reproducing systems, restyled for marketing through the Company's 100-plus Branches under the "PRINZ" label.

Now they are marketing their own Prinz Stereo System 6. Specific points in the system's specification are detailed. Amplifier: Solid state—12 transistors—a.c. Mains 220/250V. 50Hz. Frequency Range 50-18,000Hz. Noise level—55dB. Controls: On/Off and Volume, Bass, Treble and Stereo Balance. Output 5 watts Music Power per Channel. Turntable is a Garrard 4-speed Auto 2025TC, fitted with Acos GP93/1 stereo crystal cartridge with sapphire styli. Speakers are two sealed enclosures each containing one 8in. x 5in. loudspeaker, 10,000 lines, and complete with 8ft. of lead per enclosure, terminating in a 2-pin DIN plug. Cabinets are as in photograph, with teak veneer finish. Price is £55 complete.

## Two Metre Vertical

Two metre mobile enthusiasts will be pleased to hear of a new antenna manufactured by the American company Antenna Specialists Co., and available from KW Electronics Ltd., 1 Heath Street, Dartford, Kent.

This is a vertical whip, the ASP 629, which offers a gain of 2.5dB relative to a quarter wave antenna. It consists of a stainless steel whip and matching transformer assembly and may be tuned up anywhere in the range 130-174MHz.


The interference suppression ratio, relative to a quarter wave antenna, is better than 6dB. The mounting hole required is  $\frac{3}{4}$ in. in diameter and no access is needed from the inside of the vehicle.

The antenna could also prove suitable for a home station and would be extremely useful where space was at a premium. The cost of the ASP 629 is £3 10s. Antenna Specialists also manufacture vertical whip antennas suitable for 4 metres and 70cms.
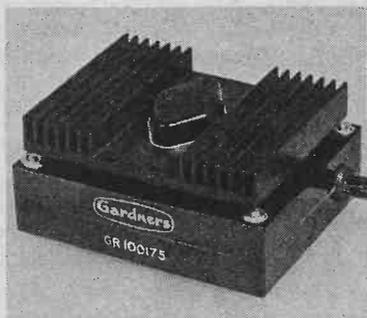
## New Inverter

A new range of Inverter Modules introduce a new service by Gardners Transformers Limited, of Christchurch, Hampshire, England.

The new range, known as the M48 E.H.S. Series, are the product of a development and manufacturing service which has been set up to cater for individual requirements and special applications.



They offer power ratings up to 30 watts stabilised or 50 watts un-stabilised in a standard mechanical assembly which will meet a wide variety of electrical parameters. The assembly incorporates a single power stabiliser which would be fitted in the d.c. output line for single output inverters or in the input to the inverter where multiple outputs are specified.

Finished dimensions for the power ratings quoted are 4in. x 3.3in. x 2in., and the weight is 24ozs. Fixing is by 4BA tapped bushes in the base of the unit.

Full details of the new range and the new service may be obtained from *Gardners Transformers Limited, Christchurch, Hampshire BH23 3PN.*

## Bi-Pak I.C.'s

A complete range of Digital T.T.L. Integrated Circuits is to be launched by Bi-Pak Semiconductor to cover the popular 74N series of logic units. These will be available in the dual-in-line plastic package at approximately half the normal distribution price. The range includes gates, flip-flops and complex units such as divide by 16 4-bit binary counters, shift registers and decimal decoders plus nixie tube drivers.

It is hoped that with the low price and guaranteed supply which Bi-Pak have arranged with the manufacturers the teaching and experimental use of Integrated Circuits which up to now have been almost non-existent for most amateur concerns will at last become a reality.

Bi-Pak hope to publish in the near future enough circuitry for building computers, calculators, etc., using the Integrated Circuits mentioned. Bi-Pak say their aim is to further reduce the cost for amateur electronics and at the same time make it the most interesting hobby of this day and age.

Full details and prices are available from: *Bi-Pak Semiconductors, P.O. Box 6, Ware, Herts.*

## Going Metric

A new leaflet 'Going Metric—Everyday Units' is now available free from the Metrication Board. The leaflet sets out the more common metric units and correct symbols for 14 everyday quantities including length, area, capacity, temperature and weight.

In the United Kingdom the basis for the metric system now coming into use is the International System of Units, known in all countries by the abbreviation SI. The units contained within this system are sufficient for all present needs of technology, science, industry, commerce and daily life.

Copies of the leaflet can be obtained without charge from *Information Division, Dept. 4, Metrication Board, 22 Kingsway, London, W.C.2.*

**Quick on the draw**

The  
Ersa  
Sprint

No, it's not a new kind of space gun—it's an Ersas Sprint soldering iron. Made in West Germany, the retailer in this country is Home Radio Ltd.

The interesting thing about this iron is that it weighs only 7ozs. and heats up in only 10 seconds. The technique used is different from usual quick heat irons because this switch is released once the operating temperature has been reached. Current consumption is 150W during heat-up period, dropping to 80W when operating temperature is reached. Working voltage is 200-250V a.c.

Home Radio stress that they supply a guarantee with these irons and they also stock a complete set of spare parts any of which can be changed in a matter of seconds.

The retail price of the Ersas Sprint is £3 19s. 6d. and the only retail supplier is: *Home Radio (Components) Limited, 234-240 London Road, Mitcham, Surrey, CR4.3HD.*

**Preston A.R.C.**

The P.A.R.S. are again holding a Mobile Rally. The venue, as in previous years is: Kimberley Barracks, Deepdale Road, Preston (next to Preston North End Football Ground).

The date is August 30th and a talk-in station will be active on 160m. Refreshments, both tea and the "hard stuff" will be available. Numerous trade stands will be in evidence. Further information may be obtained from (s.a.e. please): G. Wright, G3YOT, 56 Queensway, Bamber Bridge, Preston, PR5.6UD.

**R.A.I.B.C.**

The Radio Amateur Invalid and Bedfast Club will have a corner of their stand at the Radio Engineering and Communication Exhibition devoted to the collection of unwanted foreign stamps. So, if you have any stamps please take them along to the Exhibition and leave them at the R.A.I.B.C. stand. Also, on this stand, visitors will be able to see at first-hand the kind of good work the Club does.

Both the Hon. Sec. of the Club (Mrs. Woolley), G3LWY and Allan Herridge, G3IDG, will be present throughout the exhibition and look forward to meeting Practical Wireless and Practical Television readers.

**I.C. Amplifiers**

Motorola Semiconductors have announced a range of low-cost integrated circuits for the consumer-equipment field. Known as MFC units, these plastic-encapsulated devices use smaller chips and contain fewer circuit elements than the professional-equipment of i.c.'s. These new i.c.'s also have wider pin spacing to make them suitable for the printed-circuit boards used in consumer products.

The first two devices in the range to be introduced are a low-power audio amplifier and a wide-band amplifier. The former, Type MFC 4000, is a 250mW a.f. amplifier with a low total harmonic distortion (typically, 0.7% at 50mW output) and is designed for pocket radios. Contained in a four-lead package, it includes six transistors, three diodes and five resistors and requires no output transformer to match to a 16Ω load. The input sensitivity is 15mV r.m.s. for 50mW output. It requires a 9V d.c. supply and the quiescent current is 3.5mA.

The latter unit, Type MFC 4010, is a high gain (60dB) wide-band (100Hz to 4MHz, -6dB points) amplifier that could be used either as a general-purpose a.f. amplifier or as an i.f. amplifier at 465kHz. Typical output noise is 1mV r.m.s. Maximum power supply potential is 18V and typical current drain is 3mA.

**Hugh Greatorex**

The retirement was recently announced of Hugh Greatorex who for 37 years has been with the BBC Engineering Information Department. For the last 16 years he has been Assistant Head of that department. During this time his responsibilities included the organisation and management of the BBC technical enquiry stands at exhibitions and conferences. He made significant contributions to the promotion of new BBC services, in particular the v.h.f. radio service and latterly the u.h.f. and colour TV services.

Hugh has been a great friend of the Press for many years and we at *Practical Wireless* would like to wish him all good luck in his retirement.

**Do it yourself**

A new, inexpensive, educational aid to learning and teaching elements of logic, Boolean algebra and fundamentals of digital computers, COMPUKIT 1, has been announced by Limrose Electronics. It is supplied in kit form ready to be assembled on a specially designed printed circuit board. Logic circuits are constructed by making soldered, or solderless, connections to the terminal pins mounted on the p.c. board. Logic levels are indicated by miniature wire-ended bulbs on the board which is powered by a 4½ volt battery. The gates in the kit use transistors, diodes and resistors, and can be used not only for performing elementary logic functions, but also for wired-or, bi-stable and polyflop circuits and counters. The kit is complete and requires only a small soldering iron and a pair of cutting pliers to assemble. These can be purchased from the manufacturers as optional extras. The Instruction Book is written by a Fellow of the British Computer Society and avoids the use of jargon.

The basic kit costs only 7 Gns, and can be supplied in assembled form ready for use for an extra 27s. 6d. Further details from *Limrose Electronics, Lymm, Cheshire.*

**PW****F.C. JUDD****25-50**

# GUITAR AMPLIFIER

Part 1

**FOR TREBLE OR BASS GUITAR, ORGAN AND MICROPHONE WITH NEW "TONE TREMULANT" SYSTEM, BUILT-IN MIXING, VISUAL TREMULANT INDICATOR. MAX 50 WATTS R.M.S. POWER. COMPLETELY SELF CONTAINED. OPTIONAL FOOT CONTROLLED TREMULANT AND WAH-WAH.**

**S**ELF-CONTAINED high power guitar amplifiers with facilities similar to those of the PW 25-50, and which will be fully dealt with in this and following articles, do not come cheaply. A commercially made equivalent would cost in the region of £150 or more. All the components, including the power module, its power supply, the cabinet materials and the two special Goodmans power loudspeakers specified, can be obtained for approximately half this price.

The finished 50 watt amplifier is neither small nor light in weight because of the twin heavy duty loudspeakers and the very necessary rugged cabinet construction which is essential for power reproduction of guitar bass at the full 50 watts r.m.s. output. The cabinet is constructed from  $\frac{3}{4}$ in. thick Weyroc compressed chipboard.

There is, however, an alternative arrangement with regard to the loudspeakers and power output. For those who require the amplifier for treble guitar only with less power, a single type 12P 8 ohm Goodmans power speaker can be used and with this the PA50 power output module will deliver 25 watts r.m.s.

If the full 50 watts should be required at a later date, it will only be necessary to fit the additional loudspeaker. With a pair of type 12P Goodmans 12-inch 8 ohm loudspeakers used in parallel, the power module load becomes 4 ohms across which the module will deliver 50 watts (r.m.s.) power.

These Goodmans loudspeakers are a new range recently released by the manufacturers and have been specially designed for musical instrument amplifiers. Note that the use of loudspeakers, other than those specified, would in all probability spoil the performance of the amplifier. Under no circumstances must the power module output load be less than 3 ohms.

## Amplifier Facilities

One of the special features of this amplifier is the 'tone tremulant' system which produces a tremulant effect similar to that obtained from the rotating loudspeaker systems used in electronic organs (Leslie speakers). The tone tremulant can be varied to any degree but when turned off leaves normal amplitude tremulant as found on most guitar amplifiers. The

amplifier can, of course, be used without either of the tremulants.

Two inputs are provided for guitars, i.e., two instruments, bass or treble, can be plugged in and for which independent volume controls are provided. There is also an input for a microphone which may be high or low impedance, depending on whether a microphone transformer is used. The microphone channel has its own volume control and being quite separate from the guitar channels is not affected by the tremulant system. A master volume control is provided for all channels.



*The completed Vibrasonic amplifier which utilises two 12in. speakers to handle the output of 50 watts (r.m.s.)*

The function of the tremulant system is visually indicated by a front panel lamp which shows the tremulant speed and depth. However, when the tremulant is switched off the tone networks of the tremulant amplifier can still be used as a tone control. There is also a separate treble lift control in the guitar input pre-amplifier which together with the tremulant tone control can provide the very sharp tonal quality favoured by pop guitarists.

There are two optional facilities. One is a foot switch on-off control for the tremulant and the other a foot pedal-controlled wah-wah effect. Foot switch control of the tremulant simply requires an extra jack socket and a foot switch with a press 'on' and press again 'off' function. The wah-wah

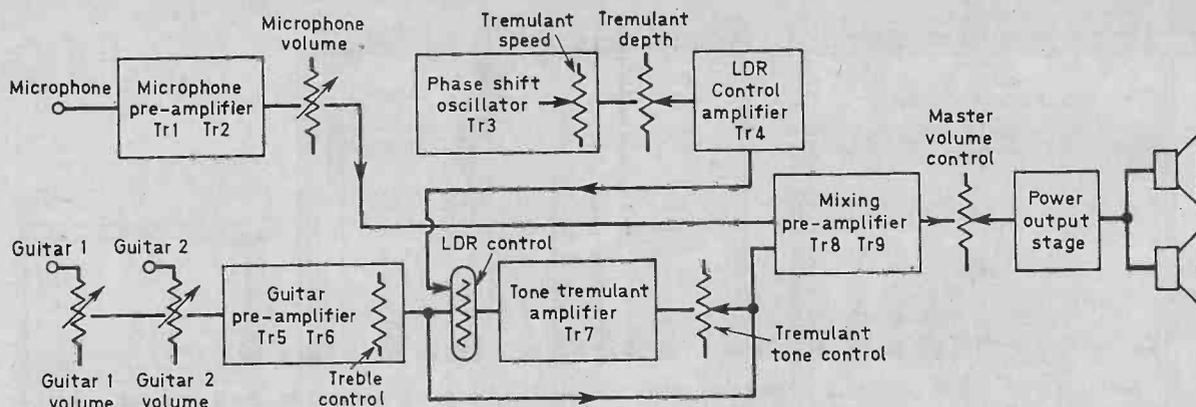


Fig. 1. Block diagram illustrating the function of each stage of the amplifier.

effect can be obtained with a pedal-operated potentiometer which can also be plug and socket connected to the guitar pre-amplifier.

## Power Amplifier Module and Power Supply

To facilitate construction for those with little experience in building and testing transistor power amplifiers, modules and regulated power supplies, the new Henelec 50 watt power amplifier module type PA50 and its matching power supply Henelec type MU442 have been chosen for the power output end of the PW25-50.

As previously mentioned the Henelec PA50 module will deliver 50 watts r.m.s. into a 4 ohm load or 25 watts to an 8 ohm load. Hence the reason for the designation PW25-50 and the use of either one or a pair of 8 ohm loudspeakers.

The Henelec PA50 module and its power supply are supplied complete with connecting cables, ready wired to the connectors, DIN loudspeaker plugs, a DIN signal input plug and a 3-pin mains input connector. To mount these units it is only necessary to drill the appropriate fixing holes on the PW25-50 chassis. The Henelec power module and power supply are tested before despatch so that no circuit adjustment whatever is necessary.

## Pre-amplifier and Control Circuit

The block diagram in Fig 1 may help to clarify the various functions of the pre-amplifier and tremulant control stages. The two guitar inputs can be mixed, i.e., each can be adjusted for volume independently of the other. The inputs are suitable for all medium to high impedance guitar pick-ups and the sensitivity of each input is 40mV for maximum rated power output.

Signal levels of 1 volt or more can be taken to these inputs and with the tremulant switched off they can be used for signals from other sources such as the output from a portable electronic organ, a tape recorder or high output gramophone pick-up, etc.

The guitar pre-amplifier also has a treble control which provides approximately 15dB lift at 10,000Hz. This has been included as many guitarists favour a tone with a strong upper harmonic content.

## New Tremulant System

The signal output from the guitar pre-amplifier is passed to a network which routes the signal via the tremulant l.d.r. (Light Dependent Resistor) to the tone tremulant amplifier and also directly to the input of the mixing pre-amplifier. The l.d.r. is controlled by means of a lamp, the brilliance of which is made to vary sinusoidally.

When the phase shift oscillator is running the amplitude of the guitar signals is varied at the requisite tremulant rate, between 5 and 10Hz as required. The signals that pass through the tone tremulant circuit are modified and the harmonic structure changed by means of the primary inductance of T3 and its RC network. The signals are phased reversed at the primary and therefore appear at the output of the tone tremulant amplifier 'in phase' with signals direct from the guitar pre-amplifier. The result is a complex variation (at tremulant rate) of the higher harmonics produced by the guitar, the aural effect being akin to that obtained with a rotating loudspeaker tremulant system (Leslie speaker).


The effect is much more pleasing than the usual straight amplitude variation tremulant used in commercially made amplifiers. The tonal quality of the tremulant is continuously variable and when turned off leaves a normal amplitude tremulant only, the tone of the guitar remaining unaffected.

This too can be switched off but the tone tremulant control can still be used as a tone control for the guitar providing even stronger upper harmonic sounds than those produced by the treble lift control.

The mixed outputs from the guitar pre-amplifier and the tone tremulant circuit are then taken to the mixing pre-amplifier together with the output from the microphone pre-amplifier. The mixing pre-amplifier output is then connected to the power amplifier module via the master volume control.

## Tremulant Control System

The tremulant control circuit consists of a phase shift oscillator with variable frequency control (approximately 5 to 10Hz), the signal from which is used to drive the l.d.r. control amplifier. There are two 6V 0.04A lamps in series with the collector of this transistor, one of which is used to control the

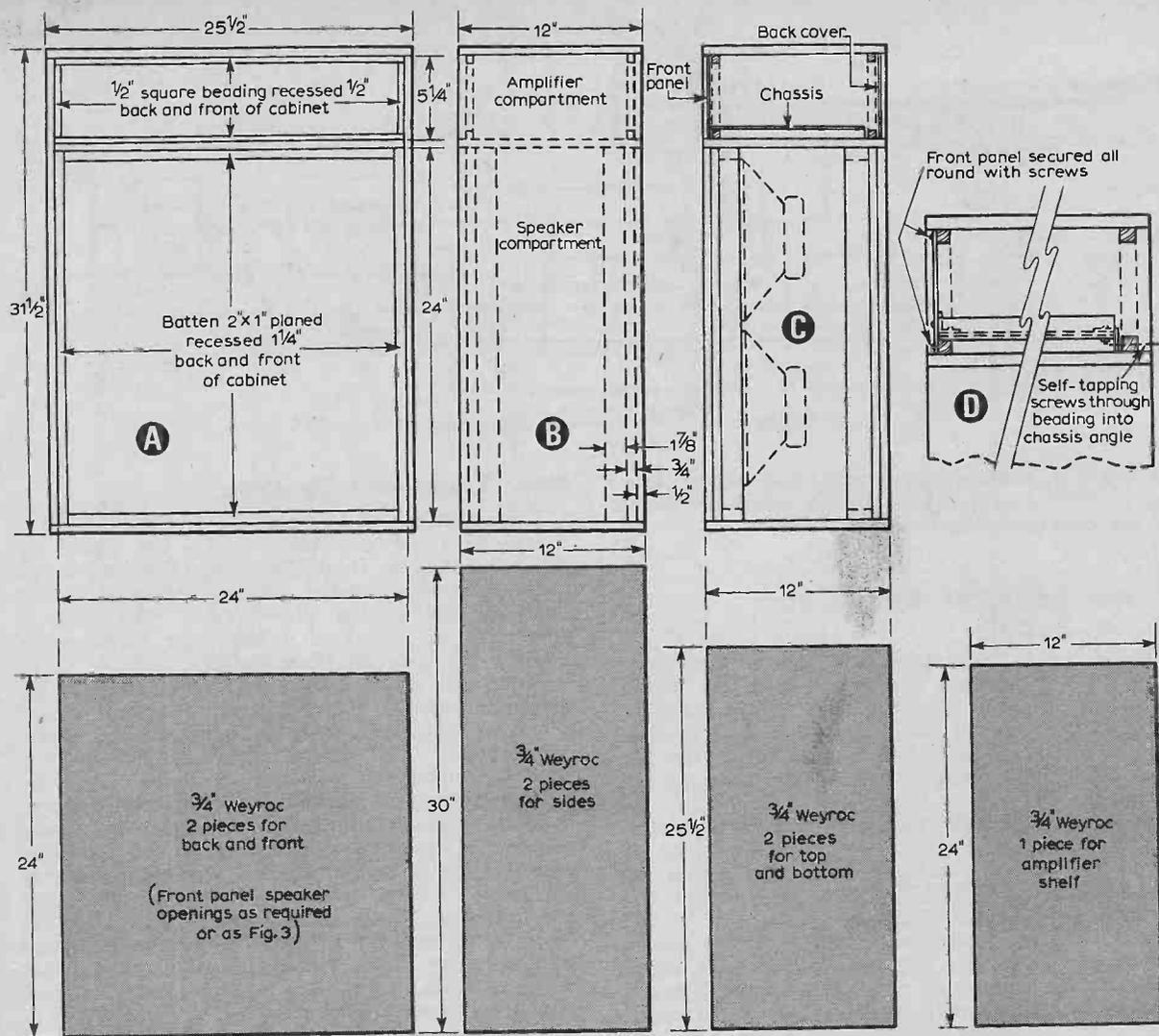

Figs. 2. (above) and 3 (right) give full details for the construction of the cabinet.

l.d.r. and the other as a visual tremulant indicator for the front panel.

The tremulant depth can be controlled so that a full or light tremulant can be obtained but the system is so arranged that the playing volume does not sharply increase when the tremulant is switched off. The l.d.r. control lamp remains alight when the tremulant is switched off, thus restoring the volume to a mean level. The rise and fall of the tremulant is rather like that of Class A modulation in a transmitter.

The l.d.r. system of control is completely free of the low frequency thump that is common with the usual combination of a phase shift oscillator and signal amplifier. The tremulant variation is perfectly sinusoidal.

### Construction (Cabinet)

The cabinet dimensions given in Fig 2 are in accordance with the enclosure space required by the loudspeakers for proper loading and for full

Cut this hole only for the single speaker 25 watt version


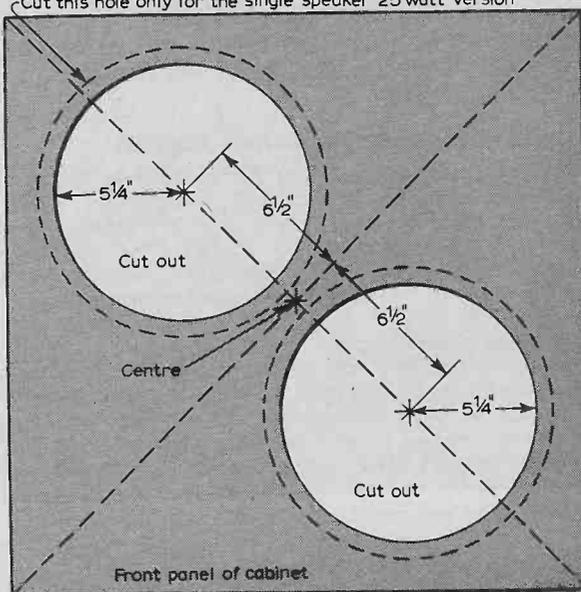


Fig. 4. Construction and drilling details for the amplifier chassis and panel. Note that the aluminium angle piece at the rear of the chassis is turned downwards while the side and front angle pieces are facing upwards. The sizes of the component mounting holes shown in the front panel may need to be altered to suit the components actually used. Check before drilling panel.

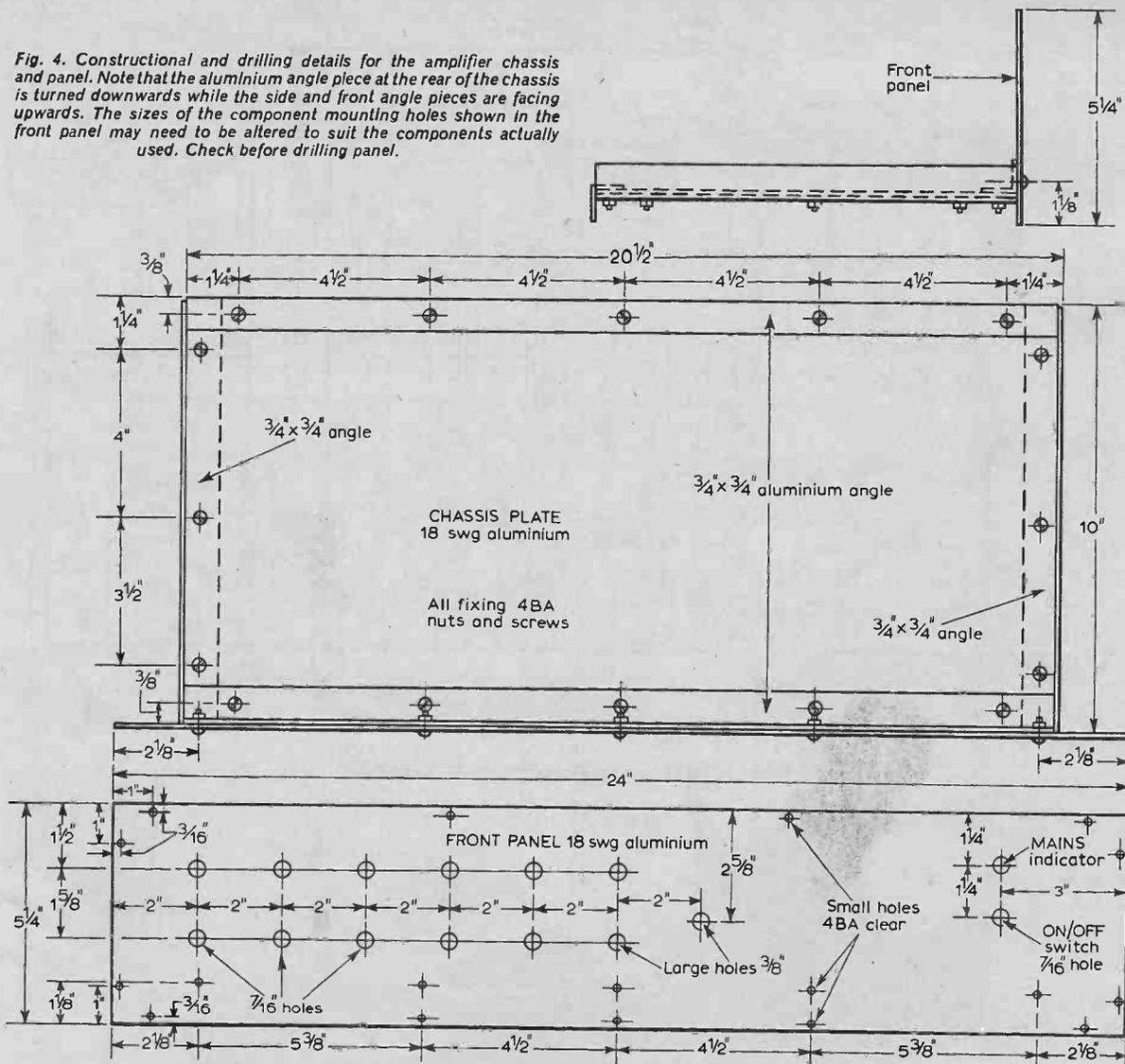

bass response down to about 40Hz. It is made from 3/4 in. thick Weyroc chipboard with joints strengthened by 2 x 1 in. planed battens.

All joints must be screwed as the cabinet is carrying a fair weight when the speakers and amplifiers are installed and because strong joints will prevent cabinet buzz at very low frequencies.

Weyroc is hard to cut but most local timber dealers with a power saw will cut the pieces exactly to size as in Fig. 2. One may then only have to cut the holes for the speaker(s). Fig 2A, B and C give all the cabinet assembly details.

Note the recessed beading around the front and back of the amplifier compartment and the recessed batten around the speaker compartment. It is not absolutely necessary to line the speaker compartment with felt but this may be worth doing to ensure no resonance effects whatsoever from the cabinet. Half-inch thick carpet felt glued around the inside and on the back panel would be sufficient.

The cabinet must have strong carrying handles, one each side, as these will be the only means of carrying it with ease. The base of the cabinet can

be fitted with rubber feet or two battens crosswise as can be seen in the photos or with roller castors. The actual finish of the cabinet can be left to the constructor's choice, but the prototype shown on the front cover was covered with plastic material as used for home decorating, the cabinet being finally edged at the front with 1/4 x 1/2 in. aluminium angle fixed with chromed instrument head screws.

The loudspeaker cut-outs are as shown in Fig 3. If the 25 watt version is to be constructed only one speaker will be used but if the second speaker and, therefore, higher output power is anticipated for a later date, then cut one hole for the single speaker in the top left-hand corner as in Fig 3. Otherwise a single speaker may be mounted centrally if desired.

### Construction (Amplifier Chassis)

The amplifier chassis occupies most of the area of the amplifier compartment and allows plenty of room for the three circuit boards, the pre-amplifier


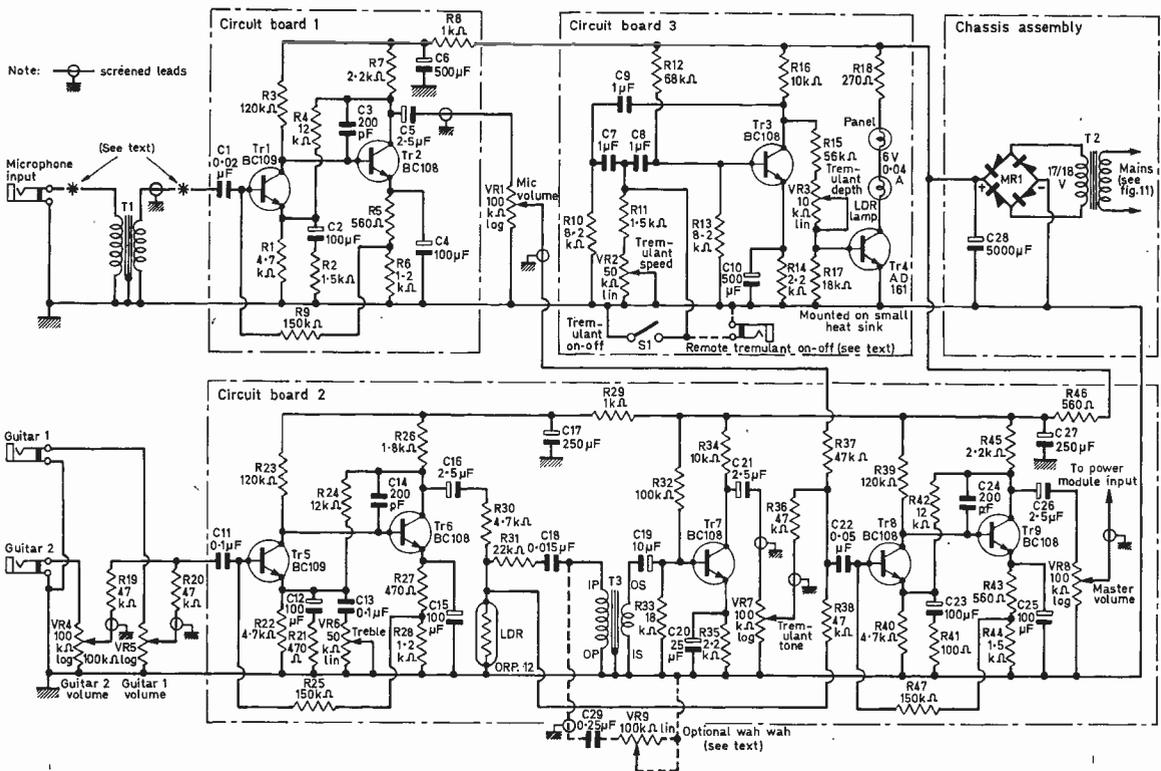


Fig. 5. Circuit of the complete pre-amplifier and its power supply.

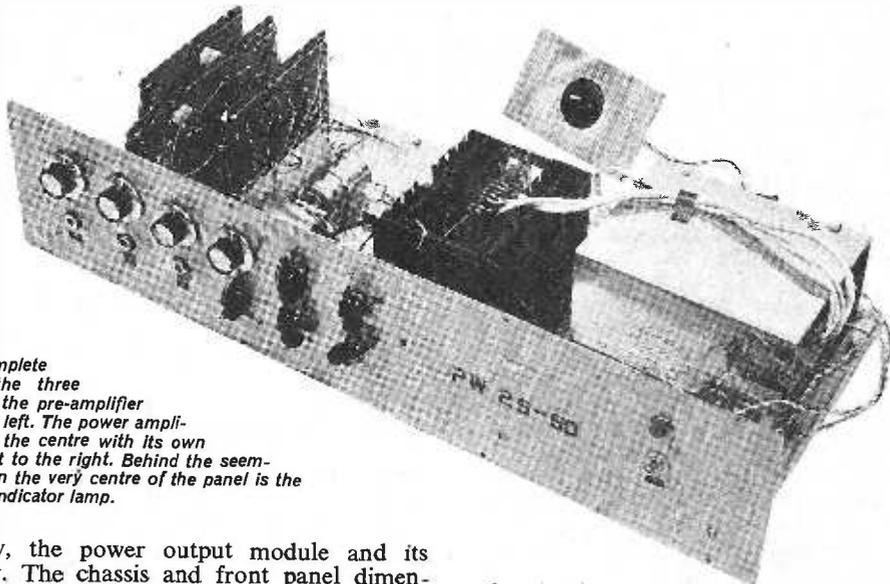

View of the complete amplifier with the three circuit boards of the pre-amplifier (see Fig. 5) at the left. The power amplifier module is in the centre with its own power supply unit to the right. Behind the seemingly blank hole in the very centre of the panel is the tremulant visual indicator lamp.

power supply, the power output module and its power supply. The chassis and front panel dimensions with drilling and assembly details are given in Fig. 4. Note how the finished chassis fits into and is secured in the amplifier compartment as shown in Fig. 2D.

### Pre-amplifier Circuit

The full pre-amplifier and tremulant control circuit is shown in Fig. 5. This is assembled on three s.r.b.p. circuit boards, the three sections being marked round by the dotted lines. The circuit function has

already been explained by means of the block diagram Fig. 1, but the following general circuit description may prove useful.

The microphone pre-amplifier Tr1 and Tr2 has a microphone transformer included in the input circuit which should be used if the microphone is low impedance (25 to 30 ohm type). Microphones of 200 ohms impedance can be used without a transformer as also can other microphones with a high impedance output i.e., with a built-in low to high impedance transformer.

—continued on page 354

## ★ components list

### Resistors:

R1 4.7kΩ	R13 8.2kΩ	R25 150kΩ	R37 47kΩ
R2 1.5kΩ	R14 2.2kΩ	R26 1.8kΩ	R38 47kΩ
R3 120kΩ	R15 56kΩ	R27 470Ω	R39 120kΩ
R4 12kΩ	R16 10kΩ	R28 1.2kΩ	R40 4.7kΩ
R5 560Ω	R17 18kΩ	R29 1kΩ	R41 100Ω
R6 1.2kΩ	R18 270Ω	R30 4.7kΩ	R42 12kΩ
R7 2.2kΩ	R19 47kΩ	R31 22kΩ	R43 560Ω
R8 1kΩ	R20 47kΩ	R32 100kΩ	R44 1.5kΩ
R9 150kΩ	R21 470Ω	R33 18kΩ	R45 2.2kΩ
R10 8.2kΩ	R22 4.7kΩ	R34 10kΩ	R46 560Ω
R11 1.5kΩ	R23 120kΩ	R35 2.2kΩ	
R12 68kΩ	R24 12kΩ	R36 47kΩ	

All resistors  $\frac{1}{4}$ W 10% miniature

VR1 (Microphone Volume)	100kΩ log.
VR2 (Tremulant Speed)	50kΩ linear
VR3 (Tremulant Depth)	10kΩ linear
VR4 (Guitar 1 Volume)	100kΩ log.
VR5 (Guitar 2 Volume)	100kΩ log.
VR6 (Treble Control)	50kΩ linear
VR7 (Tremulant Tone)	100kΩ log.
VR8 (Master Volume)	100kΩ log.
VR9 (Wah-wah Control)	100 kΩ linear

### Capacitors:

C1 0.02μF polyester	C11 0.1μF polyester	C21 2.5μF 25VW
C2 100μF 12VW	C12 100μF 12VW	C22 0.05μF polyester
C3 200pF	C13 0.1μF polyester	C23 100μF 12VW
C4 100μF 12VW	C14 200pF	C24 200pF
C5 2.5μF 25VW	C15 100μF 12VW	C25 100μF 12VW
C6 500μF 25VW	C16 2.5μF 25VW	C26 2.5μF 25VW
C7 1μF polyester	C17 250μF 25VW	C27 250μF 25VW
C8 1μF polyester	C18 0.015μF polyester	C28 5000μF 30VW
C9 1μF polyester	C19 10μF 12VW	C29 0.25μF polyester
C10 500μF 12VW	C20 25μF 12VW	

### Semi-conductors:

Tr1 BC109	Tr4 AD161	Tr7 BC108
Tr2 BC108	Tr5 BC109	Tr8 BC108
Tr3 BC108	Tr6 BC108	Tr9 BC108

All Mullard

### Loudspeakers:

50W Amplifier. 2 Goodmans Type 12P-50watt (12in. 8 ohm)  
25W Amplifier. 1 Goodmans Type 12P-50watt (12in. 8 ohm)

### Power Module and Supply:

Power amplifier module, Henelec Type PA50 (Henrys Radio Ltd)  
Mains power unit, Henelec Type MU422 (Henrys Radio Ltd)

### Miscellaneous:

Transformer T3 Type CP6713/2 (Henrys Radio Ltd)  
Transformer T2 240V/17V Type CT1 (Henrys Radio Ltd)  
Light Dependent Resistor LDR (Mullard ORP12). Lamps 6V, 0.04A, (2). Batten lampholder MES.  
Dial lampholder MES. Neon panel indicator 240V.  
Bridge rectifier MR1, 30V (Henrys Radio Ltd. Type LT 119 or 1H3). Jack sockets (3).  
Switch S1, 1 pole 2 way, (Henrys Radio Ltd. Wafer type A)  
Switch, 2 pole 2 way, mains toggle.  
Plug and socket, 3 pin, mains input (Henrys Radio Ltd. type 373).  
Knobs (4), (Henrys Radio Ltd. type NK2)  
Knobs (5), (Henrys Radio Ltd. type 7)  
Veroboards (3) 7 x 5in., 5 x 4in.; 5 x 4in. plain, 0.1in. matrix. Screened connecting cable.  
Mains lead, 3-core cable.

## ★ materials list

### Chassis and Panel:

Aluminium 18 s.w.g. Pieces as in Fig. 4.  
Aluminium angle,  $\frac{3}{4}$  x  $\frac{3}{4}$ in. Approx. 6 ft.  
Aluminium angle  $\frac{3}{8}$  x  $\frac{3}{4}$ in. Approx 2ft.  
Nuts and screws various, 4 BA.

### Cabinet:

Weyroc chipboard  $\frac{3}{4}$ in. Pieces as in Fig. 2.  
Planned batten, 2 x 1in. Approx 16ft.  
Square beading,  $\frac{1}{2}$  x  $\frac{3}{4}$ in. Approx 10ft  
Carrying handles (2). Sundry wood screws.  
Covering material. Felt,  $\frac{1}{4}$ in. thick if required.

If the microphone transformer is not required (it is not included in the pictorial diagrams to follow later) then simply connect the input jack to C1 as shown at the starred points. Note that the impedance of the microphone input without a transformer is approximately 100k $\Omega$  and is not suitable for crystal microphones.

The guitar pre-amplifier Tr4 and Tr5 is similar to the microphone pre-amplifier except that a treble lift control (VR6) has been incorporated which provides approximately 15dB lift at 10,000Hz. The output from the guitar pre-amplifier is divided across R31 and the l.d.r. and routed to the tone tremulant circuit input transformer T3 and on to the mixing pre-amplifier Tr8 and Tr9 via R38.

The transformer T3 must be the one specified in the components list and connected exactly as shown. The circuitry drawn in dotted line (C29-VR9) is for the optional wah-wah effect, further details of which will be given later.

The phase shift oscillator Tr3 is quite straightforward but note the optional dotted line circuitry for a foot control tremulant on-off switch which can be connected via a jack socket on the front panel. The tremulant control amplifier Tr4, which is an AD161, must be mounted on a small heat-sink as will be shown in Part 2.

The mixing pre-amplifier Tr8 and Tr9 completes the pre-amplifier section and the output from this is taken via VR8, the master volume control, to the power output module. The pre-amplifier power supply T2, the bridge rectifier MR1 and the smoothing capacitor C28 are mounted directly on the main chassis.

More detailed information concerning the pre-amplifier and tremulant circuitry, its function and performance, will be given in a later article. Next month will deal with the layout of the three circuit boards, the front panel controls and the power module and its supply.

TO BE CONTINUED

## "Project Autumn"

### ENTRY FORM

Full Name .....

Address .....

Title of Article .....

If my article does not win a prize I should like it

(a) to be considered for publication in the usual way,\*

(b) to be returned to me.\*

Signature..... Date.....

\*Delete as required.

Rules on page 390

PA-PW-9

## NEXT MONTH IN

# PRACTICAL WIRELESS

### TRANSISTOR AND DIODE TESTER

This unit is the first of a new range of test equipment, full constructional details of which will appear from time to time in PW. Simplicity of construction is the key-note of this tester which will measure the basic characteristics of most PNP or NPN transistors. All the components are mounted on the cover of a die-cast aluminium box which itself provides an elegant finish.

### SIMPLE MINI-ORGAN


This interesting project, which can be built in a few hours, will provide many more hours of entertainment for the constructor and family alike. The circuit uses four cheap transistors to produce a musical range of two octaves the notes being selected by a "magic wand".

### ELECTRONIC DIGITAL COMBINATION LOCK

A device which began life as a "gadget" to raise funds at a coffee party was developed into this sophisticated version which, although amusing, could have commercial possibilities. The two transistor circuit employing digital techniques need hold no fears for the average constructor.
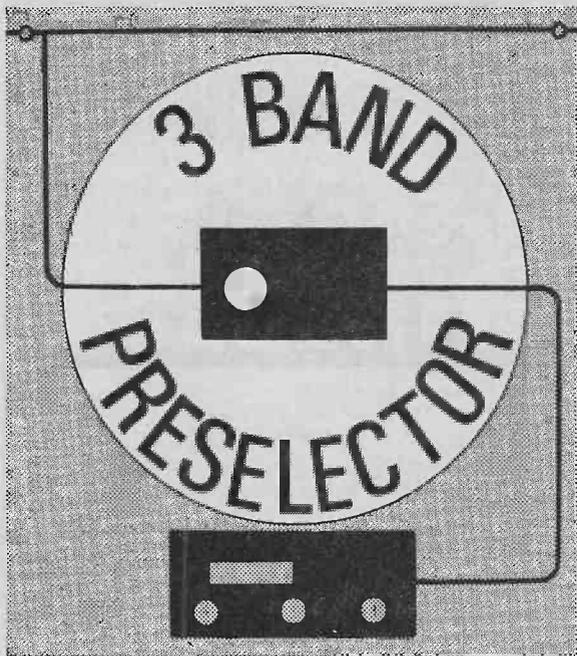
### PLUS THE REGULAR "TAKE 20" AND "I.C. OF THE MONTH" FEATURES AND OTHER CONSTRUCTIONAL ARTICLES AND FEATURES

Don't miss your copy of the October issue of Practical Wireless—on sale 4th September—price 3s. 6d.



**A.S. CARPENTER**

**G3TYJ**

**T**HE simple transistorised preselector to be described can be constructed and got working in a single evening. It costs approximately £2 to build and is a worth-while project for listeners who like to search out DX on the h.f. amateur bands.

Some of the communications-type receivers in use function well on the low frequency bands but do tend to become insensitive at higher frequencies of say 21MHz or so. Some operators aware of the problem have gone so far as to replace the older octal-based valves used in some such receivers with more modern types—but not always with complete success!

Some of the more up-to-date receivers too are by no means faultless in this respect; generally speaking the replacement of certain valves with more modern

types should be attempted only by experienced persons who have access to reliable test and alignment apparatus; without such test gear results obtained are likely to be problematical.

When first class results are required on the higher frequency bands attention should first be paid to the aerial and its aerial matching unit after which the use of a preselector can be considered, which can make the best possible use of such signals that are available from the aerial system.

## CIRCUIT

Reference to Fig.1 shows the final preselector circuit adopted. The components associated with Tr1 confer the required degree of r.f. amplification. Transistor Tr1 operating in common-emitter mode with the necessary tuned circuit L1/VC1 tied to the base element which allows continuous coverage over the frequency range of 13-30MHz. The three principal amateur bands used for DX, 10, 15 and 20 metres, are thus taken care of; in the prototype they appear on the dial pointer at approximately the 10, 1 and 2.30 o'clock positions.

Due to the damping effect of the aerial, preselector tuning tends to be broad and there is thus no need to fit a reduction drive to the peaking control VC1.

Amplified signals appear at the collector of Tr1 and go via capacitor C3 to transistor Tr2 operating as an emitter-follower stage; signals pass via C5 and the screened cable to the receiver aerial socket.

In order that the preselector can be switched off when the user wishes to listen on other bands—say 1.8, 3.5 or 7.0MHz—a combined In/Out/By-pass switch, S1a/b is provided. This disconnects the battery and at the same time allows the aerial to be fed through to the receiver.

The switch can also be used for checking the effectiveness of the unit by comparing receiver 'S' meter readings with the device alternatively 'In' and 'Out'. An increase of at least 2½ 'S' points has been noted on the meter of an Eddystone 888A on the 21MHz band with the signal peaked correctly by means of VC1. This means that the unit is of particular value when copying weak c.w. or a.m. signals.

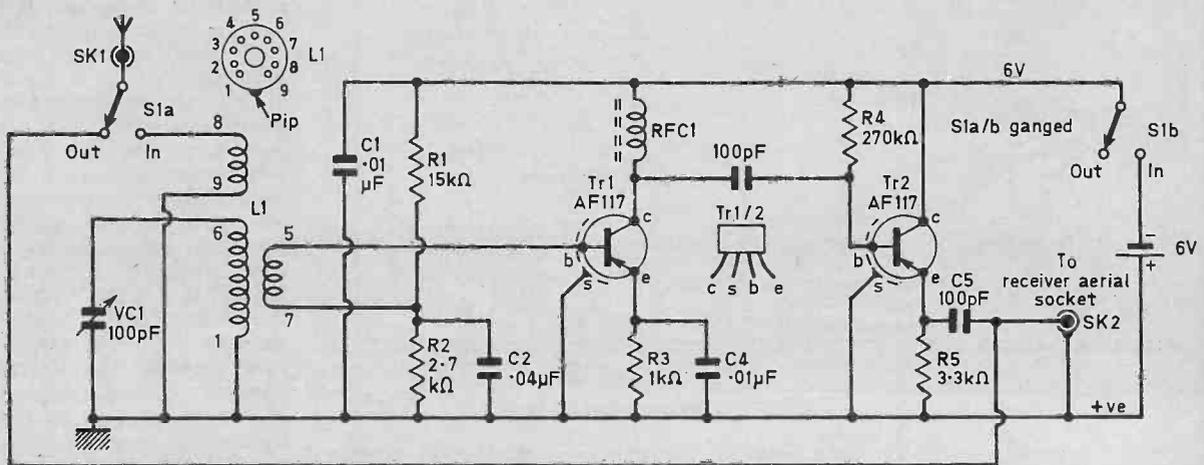


Fig. 1. Circuit of preselector. (Note:—the capacitor between Tr1 and Tr2 is C3, 100pF).

## CONSTRUCTION

A 6-in square of 18-s.w.g. aluminium sheet bent centrally into an 'L' shape is used as a combined panel and chassis. As may be seen from the wiring and layout plan of Fig.2 the battery can also be accommodated on the chassis. Two simple 'Lektro-kit' tag strips act as small component anchors; the transistors are soldered in last of all. The coil is fixed to the base-plate in the position shown, its brass-stemmed dust core being removed completely. In connection with the coil, care should be taken when soldering for excessive heat application will cause the polystyrene former to melt.

The length of screened cable to the receiver should be made no longer than required and it should be clamped firmly to the preselector base-plate. It is also necessary to fabricate a small metal bracket to carry the aerial socket SK1. Wiring associated with the slide switch S1a/b is shown inset in the interests of clarity.

## TESTING

Initially a test meter set to read 0-10mA may be inserted in series with the battery and S1. When the switch is moved to 'In' a current of approximately 2mA should be noted. Subsequently the test meter is removed and the preselector can be connected to the receiver and aerial with which it is to be used.

With the preselector switch at 'Out' a reasonably steady, but weak, signal should be sought on the receiver on the 14MHz amateur band and the 'S'

## ★ components list

### Resistors:

R1 15k $\Omega$   
R2 2.7k $\Omega$   
R3 1k $\Omega$   
R4 270k $\Omega$   
R5 3.3k $\Omega$

All  $\frac{1}{2}$ W 10%

### Capacitors:

C1 0.01 $\mu$ F ceramic  
C2 0.04 $\mu$ F tubular  
C3 100pF ceramic  
C4 0.01 $\mu$ F ceramic  
C5 100pF ceramic  
VC1 100pF variable

### Semi-conductors:

Tr 1 AF 117 or AF 115  
Tr 2 AF 117 or AF 115

### Inductors:

L1 Miniature transistor type Denco Range 4 (blue)  
RFC 1 Miniature ferrite cored choke 1.5mH.

### Miscellaneous:

Miniature switch, 2P 2W slide type K.  
6 x 6in aluminium sheet. 6V battery.  
Coaxial socket. Tag strips etc.

meter reading noted. If S1 is next moved to its 'In' position the amplifying effect of the preselector will be soon noted as VC1 is tuned to peak the transmission. The preselector can then be similarly tested on the 21 and 28MHz bands and thereafter finalized as required to suit the particular location.

Should it be found that the 21MHz band peaks when the vanes of VC1 are almost fully disengaged it will not be possible to achieve signal peaking on 28MHz; in such cases three turns may be removed from the tuned winding of coil L1. To do this, carefully snip the winding clear where it terminates at pin No. 6, unwind the necessary number of turns slowly, snip off the unwanted wire and re-make the connection to the vacated pin.

Advantages the simple preselector described has over a valved version are a physically small size plus the fact that it is completely independent of any mains connection and is thus safe. On the debit side noise generated by the transistorised preselector tends to be higher than that developed by a good valved specimen. Since to some extent noise-to-signal ratio changes with d.c. potentials supplied the lowest possible battery voltage should be applied to the transistorised unit compatible with adequate amplification. ■


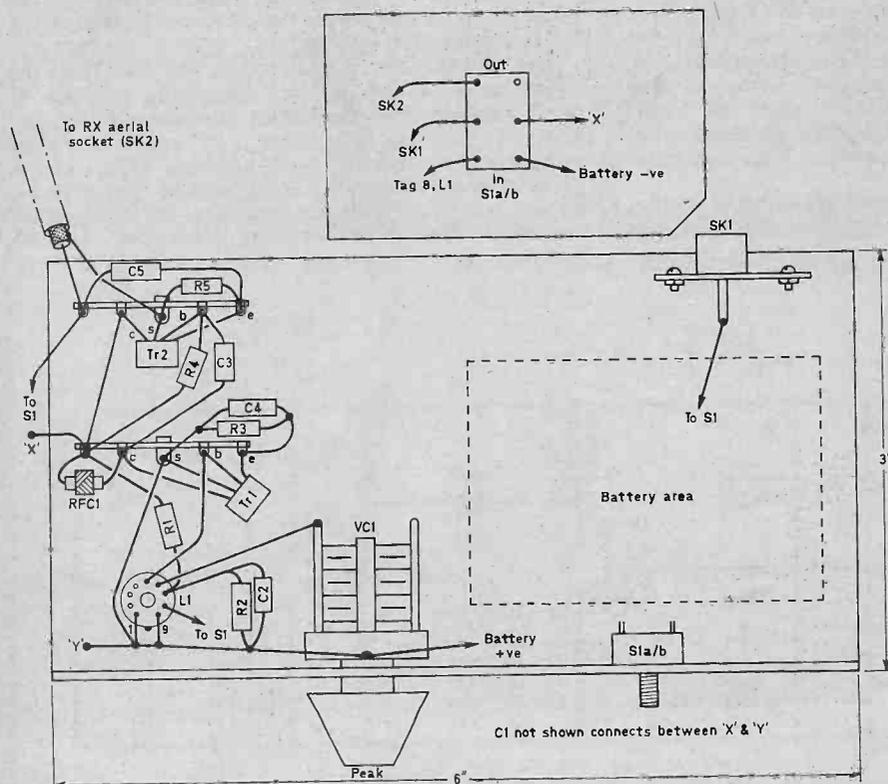


Fig. 2. Layout of the completed pre-selector.

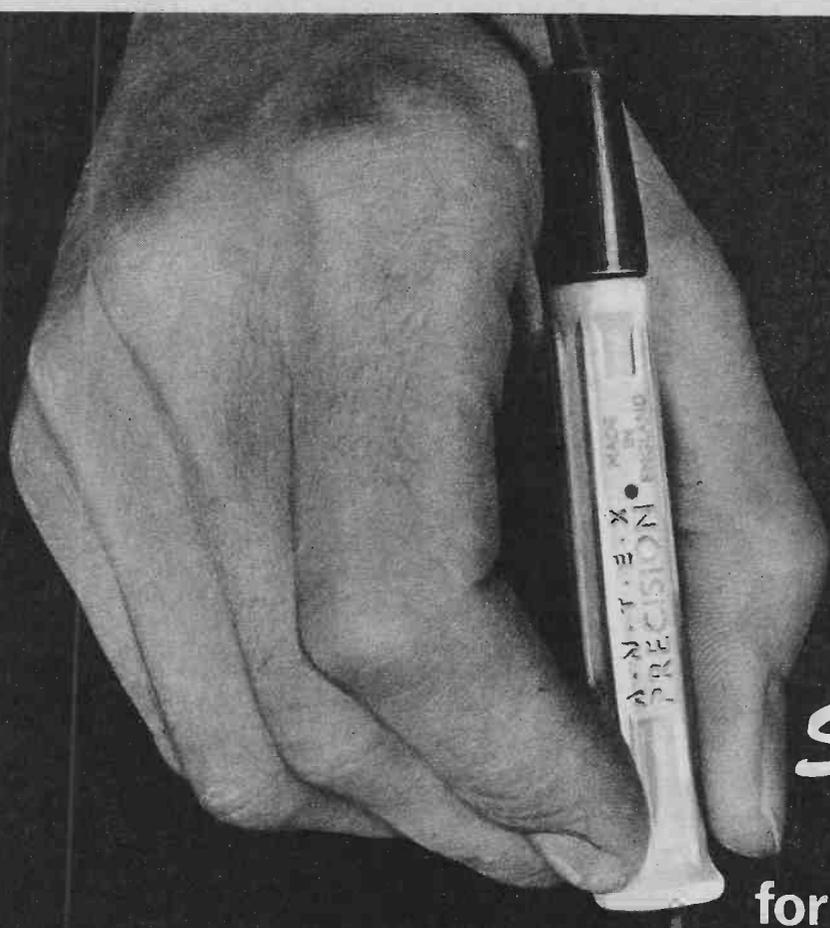

*Sign here!!*

for your  
miniature  
soldering  
iron.

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts. **from 34!-**



G18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. 36/-



E20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. 36/-




ES25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. 36/-



F40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. 47/0. Spare bits and elements for all models and voltages immediately available from stock.

**Complete precision soldering kit**

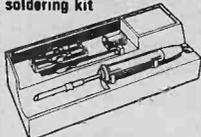

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

This kit—in a rigid plastic "tool-box" — contains

- Model CN 15 watts miniature iron, fitted 3/32" bit. Interchangeable spare bits: 1/8", 3/16", 1/4".
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. **55!-**



**Model CN 240/2**  
15 watts - 240 volts

Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex. **34!-**



**PRECISION MINIATURE SOLDERING IRONS**

Antex, Mayflower House, Plymouth, Devon.  
Telephone: Plymouth 67377/8.  
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |

I enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

PW9



# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

Times in GMT • Frequencies in kHz

### THE BROADCAST BANDS

Malcolm Connah

THIS month seems to have been a bumper one for Broadcast Bands listeners and I have been swamped with reports and letters.

**C. R. S. Stacey** of Tunbridge Wells who regularly uses his Lafayette HA-700 and Joystick to send in excellent reports like the following:

- 5047 *Radio Togo*, Eng. news at 1950
- 15165 *Syria*, Overseas Service, English, 1930
- 15300 *NHK*, Japan, Eng. 1800-1815
- 15435 *DW*, Kigali relay in Amharic 1415
- 15440 *FEBC*, Philippines in English at 1530.

**Glyn Morgan** of Tredegar has an impressive line-up of equipment including a Lafayette HA-230, an Eddystone-EC10 and a Hallicrafters SX130 and a 50ft. long-wire aerial. This equipment enabled him to send in a report which included:

- 3232 *R. Brazzaville*, Congo in French at 2205
- 3376 *CR6RP*, Angola, English music at 2205
- 4765 *R. TV Congolaise*, French at 2155
- 4815 *Upper Volta*, talk in French at 2220
- 4835 *R. Mali*, play in French at 2210
- 4850 *R. Mauritania* at 2050
- 4880 *Kinshasa*, Congo, African music at 2245
- 4885 *Nairobi*, Kenya, pop music at 1845
- 4905 *R. Relogio*, Brazil, Port. at 2145
- 4915 *Nairobi*, Kenya often heard at 1900
- 4926 *R. Ecuatorial*, Guinea, Spanish at 2140
- 4940 *R. Abidjan*, Ivory Coast, music at 2225
- 4976 *Kampala*, Uganda, music at 2025
- 4990 *R. Barquisimeto*, Ven., music at 0745
- 4995 *R. Brazil Central* with football at 2250
- 5026 *Kampala*, Uganda in vernacular at 1850
- 6045 *R. Clube Paranaense*, Brazil, 2300
- 6055 *R. Panamericana*, Brazil, at 2235
- 6250 *Santa Isabel*, Guinea, Spanish at 1930.

**John Trewick** of London Colney has a Perdio six transistor portable receiver with a telescopic antenna and a log which includes:

- 6145 *Deutsche Welle* to the USA a 0435-0555
- 7210 *Oslo*, Norway on Sundays at 1200 to 1235
- 11735 *Rabat*, Morocco with news at 1715
- 11740 *ABC*, Australia with news at 1700.

John also reports that a new station is *Trans-Europe*, Portugal at 0900-1000 on 9650 and 11720 and at 1345-1415 on 9625 and 11865. The first programme is in English from the Tourist Radio and the second is a relay of Deutsche Welle in English.

**Geoffrey Gilham** of London S.E.12. is a regular reporter to the column and his log includes:

- 4835 *R. Mali* with talk in French at 2045
- 4855 *R. C. Mozambique*, music at 2102
- 4923 *Radio Quito* with classical music at 0250
- 4967 *R. Kuwait* with pop music at 2052
- 6090 *R. Belgrano*, Argentina with talk at 0203
- 6160 *Emis. Nueva Grenada*, Col. at 0420.

Regular reporter **Roy Patrick** of Derby has sent in some more, very interesting, news items:

**FINLAND Radio Finland** has announced that it intends to drop its DX programme.

**IRAQ Radio Baghdad** has been logged on 9610 at 1930 with a programme in English.

**MONACO Radio Monte Carlo** is now broadcasting twelve hours a day in Italian on 1466 and the shortwave frequencies of 6035 and 7135. The latter frequency provides very good reception.

**Philip Batt** of Littleborough in Lancashire has a PCR3 receiver and a 60ft. long-wire antenna which enabled him to hear the following stations:

- 4920 *YVKR*, Caracas, Venezuela, 0600
- 15060 *Radio Peking* in English at 0930
- 15140 *Radio Vilnius*, Lithuania, sign-off at 2300
- 15160 *ABC*, Australia in English to Asia at 0700
- 15275 *R. Afghanistan* in English at 1800
- 15370 *R. Tamoio and Tupi*, Rio at 2200
- 17785 Tentative logging of *Radio New Zealand* with English news at 0700

17855 *Radio Japan* with English news at 0800

21505 *R. Accra*, Ghana in English at 1554.

**V. P. Hill** of Cwmbran owns a 5-valve domestic superhet. and an 80ft. long-wire and his log included:

- 9560 *ABC*, Australia in English at 0645
- 15160 *Voice of Turkey* at 2220
- 17445 *Radio Havana*, Cuba at 2042
- 17448 *WINB*, United States of America at 1956
- 17650 *Trans World Radio*, Bonaire at 2155.

**Stephen Wainwright** of St. Helens used his Sky-rover Mark II receiver and 100ft. long-wire to hear the following:

- 9465 *R. Pakistan* in English at 1945-2030
- 11815 *Bonaire*, Neth. Antilles in English at 0030-0130
- 15013 *Voice of Vietnam* in English at 2000-2030
- 17740 *VOA*, Monrovia, Liberia in English at 0800
- 21690 *Windward Islands Broadcasting Service*, Grenada in English from 1945-2200.

**Raymond Peart** of Worcestershire used his Spidola transistor receiver and 100ft. long-wire to log:

- 6145 *Deutsche Welle* in English at 0500-0555
- 9650 *ABC*, Australia in English at 0645-0915
- 9770 *Austrian Radio* in German at 0730
- 9833 *Radio Budapest* in German at 1330
- 21495 *Radio Portugal* in English at 1345-1430.

Due to the ever increasing number of reporters to this column I will, in the future, only be able to use those reports which contain accurate details of frequency and time and the name of the station.

All reports should arrive at 58 Kensington Gardens, Cranbrook, Ilford, Essex by the 17th of the month.

# THE AMATEUR BANDS

David Gibson, G3JDG

**L**OTS of interesting things happening this last month both on and off the Amateur Bands. For the c.w. versus a.m. versus s.s.b. addicts you've got a nasty shock coming from the professionals. At a recent conference in London a very strong case indeed was put up for double side band diminished carrier. On tests carried out in the field, a 6W d.s.b. transmitter consistently outdistanced a 25W a.m. transmission. The police force are seriously considering using d.s.b. and data transmissions at around 2.4 kilobits/second.

Yet another seminar discussed interference. One point which came out here was that of earthing. It was agreed that any interference problem (and earthing system) was very much an individual thing and that no one simple solution or set of rules existed. Makes you think about t.v.i. and that tiny splinter of copper you call an earth, doesn't it!

Lots of inquisitive ears have been flapping about this month and despite the warm weather many people sent in multiple logs. My thanks to all those owners of hot, swetty little lugs who persisted and perspired. You're doing a grand job slaves.

More mighty magnificence from the majestic **Master Moore**. John, who lives in Leicester bagged GM and GW on topband. On 14MHz, the CR100/2, a.t.u. and 130ft. long wire reported signals from—AX5LC, AXOLD (Macquarie Island), CE0AE, HK4AD, HR1KAS, HR2WTA, KH6BX, YN2EC, YV4YC, 8P6AH.

A quick pilfer round the pertinent portions of 21MHz raised—CN8AH, EL1B, EL2BZ, F0RT/FC/P, JA1EOD, JA2NPC, JA6YSS, TF3BV, VP9BY, VU2OLK, YA1EXZ, YA1GNT, 5H3KA, 5Z4DW, 9E3USA, 9H1BE, 9V1PA. Ten metres a.m. was heard from LU6DRB, and on s.s.b.—HK3AVA, KV4AD, VU2BEO, ZE2JA, ZS6AUD, 5Z4LS.

John is hoping to listen on 432MHz soon when he gets a homebrew converter perking and takes delivery of a 14-element skybeam. (Cor, think of the pleasure all those little prongs will give the birds.)

**Roger Boyd** is located in Victoria Park, Western Australia and has the distinction of sending the most DX log received this month. The rig is a Trio 9R-59DE and choice of 20 metre dipole or a 25ft. vertical. His log for 7MHz reads—DJ0JE, DK1CU, DL6WE, DL8MM, EA4KY, G3VYF/P, HB9ADQ, I1BAF, JA2VGQ, JA8TL, OZ5MV, PY7BPD, SP6DVB, UA1IG, UY5YS, YT1BCD. So, if the path from Europe to Australia is open, why don't more of us hear VK/AX stations on forty? Perhaps it's still the operator that counts and not so much the equipment.

**Malcolm Monro** (Cumberland) writes a sad tale of holding a G8 licence but the transistor transmitter won't work. Two metre fans will be pleased to hear of the latest Fairchild transistor, the MSA8506 which gives 25 watts at 175MHz from a 12V line. Twist in the tail is the price, which is around the £15 mark. However, the MSA8507 gives 8W for the same parameters and costs around £6. With luck the price should drop as production quantities build up. These devices will, however, withstand any non-oscillatory load from an open to a short circuit at full rated power.

Back to logland again. **Andy Crooks** (Leicester) RA1, PR30 and 45ft. end fed prowled 21MHz to find sigs from—CP5PD, CR6BF, CR6FP, EL2L, EP2BQ, HP1RC, JA1DJL, JA2QUQ, JA3QKU, JA4DGG, JA8BMK, JH1ECU, LJ2L (special prefix for Norwegian schools), LU2CF, LU4DM, OD5BZ, PY2CRN, PY5ATL, PY7GAH, TG9GF, VE7DG, VP2VI, VQ9RK (Seychelles), W5DL, W5GC, W7RI, ZP5GS, ZS3HX, 3V8AL, 5Z4CK, 9J2PV, 9Q5WV. All these using s.s.b.

**D. Browning** (Herts), CR7OA, PR3OX, 37ft. of bent wire in the loft shows what's been about on 3.5MHz. Heiroglyphics scribed in his log read—AX6HD, CT1BH, CT1GD, CT2AK, DL5YA/MM, F0RT/FC, PY1HA, 4U1ITU, 9H1K, 9H1CC, 9V1PP.

On 14MHz, Douglas bagged—AXOLD, CN8HL, CN8MJ, HV3SJ, HK4AD, KL7BJW, LU5NA, OJ0DX (Market Reef), OA4UY, TR8MC, XE1AE, XE1TX, YN2OM, YV5CQM, 3V8AV, 6W8BD, 7X2AL, 9X5AA. Listening on 21MHz, Douglas had the distinction of hearing King Hussein of Jordan, callsign JY1.

**N. Richardson** (Bucks.) sent in a 144MHz log obtained using earholes backed by a Garex converter into a PR30 and CR7OA tuning 28-30MHz. The antenna is an eight-element Yagi at 28ft. Signals received from—EI2AX/P, G3JQA/P, G8BCL, G8BEU, G8BMC, G8CAF, G8CIL, G8CSJ, G8CVK/P, GW3GIZ/P, GW3SRT/P, GW8ACG/P, GW8BIP, GD2HDZ (Isle of Man). Nicholas will have a rotator on the Yagi by the time you read this which will put the antenna clear of the chimney and roof.

**G3QG** is located at Luton Hoo and is active on 144-68MHz. Bill would appreciate any DX reports on his signals and will QSL for worthwhile details of his signals. How about it all you 2 metre sleuths?

A reminder to listen for **GB3WRA** operating 160-10 from the 24th. Annual Wycombe Show on Saturday, September 6th. If you can get along, visitors, s.w.l.s and licensed amateurs will be welcome. Perhaps a chance to go mobile?

Another one to listen for is **G2DRT** who will be operating as **EI2VCL** from September 5th. to 22nd. from Fenit County Kerry. Operation will be on 2 metres.

Happenings in August include: August 9th., D/F qualifying even at Chelmsford; 10th., 2 metre s.s.b. contest; 15th. and 16th., 4 metre c.w. contest; September 5th. and 6th., v.h.f. NFD.

Mobile Rallies: August 9th., Woburn Abbey; 9th., Stratford upon Avon Mobile Picnic; 16th., Torbay A.R.S. rally at Newton Abbot; 16th., Mobile Rally at Derby; 23rd., Wroughton Aerodrome near Swindon.

## RSGB EXHIBITION 1970

PRACTICAL WIRELESS  
PRACTICAL TELEVISION

Visit our Stand at the Show where we shall be glad to meet our readers and their friends.

WHEN?

Wednesday Aug. 19th to Saturday Aug. 22nd  
10 a.m. to 9 p.m. daily

WHERE?


The Royal Horticultural Society's New Hall,  
Greycoat Street, Westminster, London, S.W.1  
(Nearest Station—Victoria)
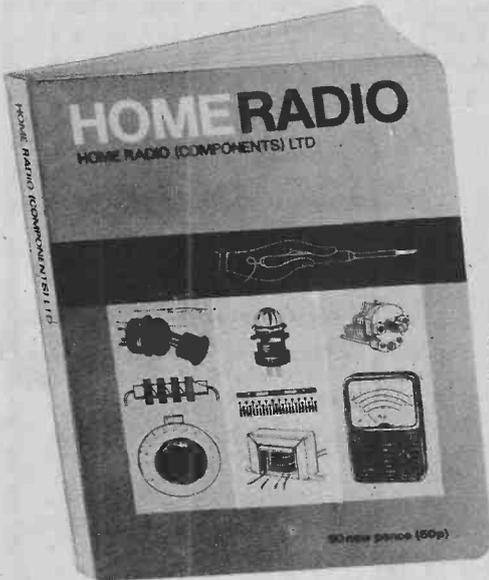
# Ever had karnt afindapartitis?



At some time or another most constructors of radio and electronic projects get hit by this complaint! The symptoms? Depression . . . exasperation . . . headaches . . . weariness . . . sore feet, etc. The causes? Frustrating hours spent in thumbing through inadequate out-of-date catalogues, making numerous fruitless phone calls, tramping or touring from shop to shop—all in a vain attempt to locate some vital components.

Here is the answer to the problem—the **Home Radio Components Catalogue** a world renowned medicine for preventing the complaint or for quickly clearing up the trouble if symptoms have already begun to appear! Just send the coupon with 8/6d plus 4/- postage & packing, and your copy will be despatched immediately. In its 350 pages over 8,000 components are clearly listed, over 1,500 of them illustrated. A cross-reference Index and a 30-page Price List enable you to locate your components without any trouble.



Once you have your Home Radio Catalogue you can, if you wish, make life even easier for yourself by joining our **Credit Account Service**. Then you can order by telephone any time of day or night, Sundays included! No need to bother with postal orders, cheques registering envelopes every time you order. We send prepaid envelopes and only one payment is required each month. So simple!  
Write for details or telephone : 01-648 8422.



**POST THIS COUPON NOW**  
with your cheque or P.O. for 12/6

Please write your Name and Address in block capitals

NAME .....

ADDRESS .....

HOME RADIO (Components) LTD., Dept. PW,  
234-240 London Road, Mitcham, Surrey, CR4 3HD

The price of 12/6 applies only to catalogues purchased by customers residing in the U.K.

**BRAND NEW AR88D COMMUNICATIONS RECEIVERS.** AC mains input 110 volts or 230 volts. Frequency in 6 bands 535 Kcs up to 39 megs, output impedance 2.5-600 ohms. Complete with crystal filter noise limiter B.F.O. HF tone controls. Price £80 including spare set of valves, headphones and manual.

**R200 RECEIVER AM/CW/FM** 1-20 Mc/s Four bands, Vernier tuning, 12 volt DC input. Tested and working. Price £13.10.0 plus £1 p.p.

**COMPUTER BOARDS** Min 30 transistors and diodes and res. etc. 10 boards at 10/- plus 2/6 p.p.; 25 boards at 22/6 plus 4/6 p.p.

**AERIALS** new condition, extending to 11 ft. fully open; whip type; 12/6 each plus 3/6 p.p. Whip aerials, 12ft. collapsible type; used condition. 10/- each plus 3/6 p.p. Bases for above 5/- each plus 2/6 p.p.

**BARGAIN PARCELS** 14lb at 29/- plus 6/6 p.p.; 28lb at 55/- plus 12/6 p.p.; 56lb at 90/- plus 25/- p.p. Contain pots, Res, Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £2s. Lucky Dip Service.

**FURZHILL BEAT FREQUENCY OSCILLATOR** 0-10 Kcs, 110/250 volt. Good condition complete with spares. £5.10.0 plus 25/- p.p.

**VHF Receiver, Type 715**, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested; complete with valves and speaker. £3.0.0 plus £1 p.p.

**VIBRATOR POWER SUPPLY TYPE 69** by BEC for 89T/R. Small compact 12V input gives 250V DC at 80mA and 12V output. Good condition. 25/- plus 7/6 p.p.

**MOBILE POWER UNITS** by PYE for the C12 T/R. Power output is 400V DC at 140mA and 300V DC at 100mA. Good condition. £3.10.0 plus £1 p.p.

**INSULATION TESTERS.** Bench and fieldwork; speed clutch, new condition, complete with leather case; 500V, 500 megohms. £20.0.0 plus 12/6 p.p. Also 1000V 1000 megohms with case. £23.0.0 plus 12/6 p.p.

**CRYSTALS AS NEW:** Hc 6u, 5,345; 5,055; 5,030; 5,005; 4,945; 4,875; 4,840; 4,796; 4,580; 4,660; 4,620; 4,610; 2,300; 2,295 Kcs/s and 10 x 3465 Kcs/s. 10/- each plus 1/6 p.p.

**SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS.** 10% tolerance  $\frac{1}{2}$  &  $\frac{1}{4}$  watt. Preferred values in packets of 10. Our price 10/- per 100, 19/- per 200, 27/- per 300, 50/- at 42/6. Our selection. p.p. 1/6 per 100 and 6d. per extra 100.

**TRIMMER BARGAINS.** These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details. Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice. Trimmers without Xtal — 12/- per doz. plus 3/6 p.p. Trimmers with Xtal — 15/- per doz. plus 3/6 p.p. Also 20 PF min. brand new air spaced. 10/- per doz. plus 3/6 p.p.

**SIGNAL GENERATORS OSCILLATOR No. 2.** Size 12in. x 8 1/2in. x 9in. Ideal for VHF work. 20-80 Mc/s. Functions are AM/CW. Deviation up to 40 Kc/s RF meter. Measuring levels: RF output 1 microvolt to 100 microvolts set. Mod-set carrier controls. Good condition with accessories: 230V AC 12V DC. £20.0.0 plus 15/- p.p.

**TF 144 G Signal Generators.** 85 Kcs to 25 Mc/s. Good condition and complete with accessories. £22.0.0 plus 30/- p.p.

**RF Thermo Couple Meters.** New and boxed. 0-1 amp, 2in. diameter. 17/6 plus 4/- p.p.

**MAINS MOTOR, 250 volt AC; 1/40th H.P. at 1,500 R.P.M.** Ex WD type; Size 6in x 4in. Tested and in good condition. 35/- plus 7/6 p.p.

**TELESCOPIC MASTS.** New condition, 20ft closes to 5ft 9in. 90/-, carriage 15/-; 34ft closes to 5ft 9in 120/-, carr. 15/-; Used condition, 20ft 70/-, 34ft 80/-, carr. 15/-; Base for same 20/-, carr. 7/6.

New toggle switches 12/6 dozen post and packing 2/6.

New lengths 50ft Coaxial cable 70 ohms, coax plug each end, price 20/- each post and packing 2/6.

Magnetic Transducers new, price 7/6 post and packing 2/-.

New small fuse boxes 250 volts 15 amps. 17/6 each post and packing 3/-.

Meters moving coil ex equipment good condition 100Ma, 500Ma, Also 15 amp DC, 20 amp DC, 40 amp DC. All at 10/- post and packing 5/-.

**A. H. THACKER,**  
Radio Dept.,  
HIGH STREET, CHESLYN HAY,  
Nr. Walsall, Staffs.

**AUDIO EFFECTS**

5 SHAW LANE, HALIFAX YORKS

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

**AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT.** No fuss, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco plug in coils 2T, 0.5 to 1.54 Mhz 3T, 1.67 to 5.3 Mhz 4T, 5.0 to 15 Mhz 5T, 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 9 volt battery. Easy step by step instructions. Complete Kit. £8.19.6 plus 5/6 P. P. & Ins. Extra ranges 12/- per range.

**POWER CONTROLLER.** Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3kW triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions £6.9.6. Ready built £9.4.6 plus 5/6 P. P. & Ins.

**REVERBERATION AMPLIFIER.** Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7 1/2in x 3in x 4 1/2in. £10.4.0 plus 6/- P. P. & Ins.

**VOX SWITCH.** The sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 42/6. Ready built, tested and guaranteed. 62/6, plus 2/6 P. P.

**METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini. earphone. In kit form 27/6, post paid. Ready built in an attractive black and white polythene case, 37/6 post paid.

**MORSE OSCILLATOR.** PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 25/- post paid.

**STRAIGHT FROM THE PRESS.** Latest Mullard manual; Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi Tape, etc. etc. 32/6 post paid.

**JUST ARRIVED IN STOCK.** Texas transistors. Complementary symmetry. Driver, NPN, PNP output. The set of three ONLY 6/6 post paid. Free lists with every order. For lists only send 1/6 (deductible from first order).

**NEW VALVES!**  
Guaranteed and Tested  
24-HOUR SERVICE

1R5 5/6	DK96 7/3	EL84 4/9	PL84 6/-
1R5 4/3	DL35 4/9	EY61 7/-	PL500 12/9
1T4 2/9	DL92 5/9	EY86 6/8	PL504 13/3
354 5/9	DL94 5/9	EZ80 4/8	PY32 10/-
FV4 5/9	EL96 7/3	EZ81 4/8	PY33 10/-
6/30L2 11/6	DY86 5/3	KT61 9/3	PY81 5/-
6AQ5 5/-	DY87 5/3	KT66 16/6	PY82 5/-
6SN7GT 4/-	EABC80 5/9	N78 17/-	PY83 5/8
26L6GT 4/6	EBC33 7/9	PC86 10/3	PY88 6/6
30C18 12/6	EB41 9/3	PC88 10/3	PY800 7/-
30FL1 12/6	EBF89 6/-	PC97 7/9	PY801 6/9
30FL12 14/3	ECC81 3/6	PC900 7/-	R19 8/3
30L15 12/9	ECC82 4/6	PC884 6/3	U25 12/9
30P4 11/6	ECC83 4/9	PC909 8/11	U26 11/6
30P19 11/9	ECC85 5/-	PC939 9/6	U91 13/-
30PFL 12/6	ECH35 5/6	PCF80 5/11	U251 14/-
30PFL13 14/6	ECH81 5/9	PCF801 6/6	U229 14/-
30PFL14 14/-	ECL80 6/6	PCF802 8/9	UABC80 6/-
CCH35 13/-	ECL82 6/3	PCF805 12/9	UBC41 8/3
CL33 17/6	ECL86 7/6	PCL82 6/9	UBF89 6/3
DAC32 6/9	EF89 4/6	PCL83 11/9	UC85 7/3
DAF91 4/3	EF90 4/6	PCL84 7/-	UCH81 6/6
DAF96 7/6	EF85 5/9	PCL85 8/6	UCL82 6/9
DF33 7/6	EF86 6/3	PCL96 8/-	UF41 10/6
DF91 2/9	EF89 4/6	PFL20011/6	UF89 6/-
DF96 7/6	EF183 5/6	PL36 9/3	UL41 11/9
DE32 6/9	EF184 6/-	FL81 9/3	UL84 6/3
DK91 5/6	EL90 6/-	PL82 5/9	UY41 7/-
DK92 8/3	EL33 9/3	FL83 6/3	UY85 5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any insured parcel against damage in transit 6d. extra. Office address, no callers.

**GERALD BERNARD**  
83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON, N.16

**BUY THIS  
BEST SELLER**

Sales exceed 100,000 copies

**T.V. FAULT FINDING  
405/625 LINES**



**4th REVISED EDITION**

Edited by J. R. Davies

124 pages only 8/6

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price 8/6 from your Bookseller

or post this Coupon together with remittance for 9/2 (to include postage) to

**DATA PUBLICATIONS LTD.**  
57 Maida Vale, London, W.6

Please send me the 4th revised edition of TV Fault Finding, Data Book No. 5.

I enclose cheque/crossed postal order for .....

NAME .....

ADDRESS .....

P.W. Block Letters Please

# 27MHz

# FIELD STRENGTH METER

RICHARD COLLINS

**I**N radio control work, it is often useful to use a field strength meter; it should not be regarded as a superfluous piece of equipment. It is a very simple circuit (see Fig. 1), easy to build and provides a very convenient way of checking that a transmitter is working correctly. Also, the field strength meter is handy for comparing the output power of different transmitters.

## THE CIRCUIT

Referring to Fig. 1, L1 and VC1 comprise the tuned circuit. The aerial, which should be a small telescopic type, connects to one side of the tuned circuit. The signal is tapped off from the tuned circuit, rectified by D1 and smoothed by C1. The voltage appearing across C1 will, for most applications, be enough to give a decent reading on a meter placed across it, but for further sensitivity this voltage is made to bias the base of Tr1; where this is done the meter is of course not required across C1.

VR1, R1, R2 and Tr1 form a bridge circuit and before taking any readings should be adjusted for zero current. The r.f. signal after being rectified will bias the transistor causing the bridge to unbalance and the meter will show a reading. It will quickly be seen that the higher the r.f. signal, the greater will be the unbalance of the circuit and so

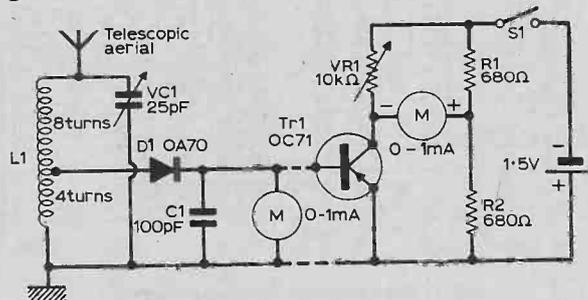


Fig. 1: The circuit of the field strength meter. Components to the right of the dotted line are only needed where the extra sensitivity version is required and here the meter is across the bridge circuit.

the reading on the meter will bear a direct relationship to the strength of the signal received at the tuned circuit.

The on/off switch is incorporated with VR1 but care should be taken to ensure that it is wired as shown. The battery used is a 1.5V pence.

## CONSTRUCTION

The only component to be constructed is L1, the coil. This is wound on  $\frac{1}{4}$ in. dowelling or anything of similar diameter, which may be later removed. Starting at one end of the former, using 16s.w.g. enamelled wire, (leaving about  $2\frac{1}{2}$ in. spare) wind on 8 turns, close wound. A small portion of the wire

should then be bared of enamel so that a tapping can be soldered on later. Another 4 turns are now wound making a 12 turn coil tapped at 8 turns. The coil can then be slipped off the former and stretched to a length of  $1\frac{1}{4}$ in.

Although the wiring is simple (Fig. 2.), it should be carried out with care. Every wire should be as straight as possible. Stiff wire is best as it is less likely to vibrate and cause slight variations in meter readings.

The unit may be housed in a small box measuring about  $2\frac{1}{2}$  x 3 x 6in. and the 25pF capacitor should preferably be of the ceramic base type with silver-plated plates.

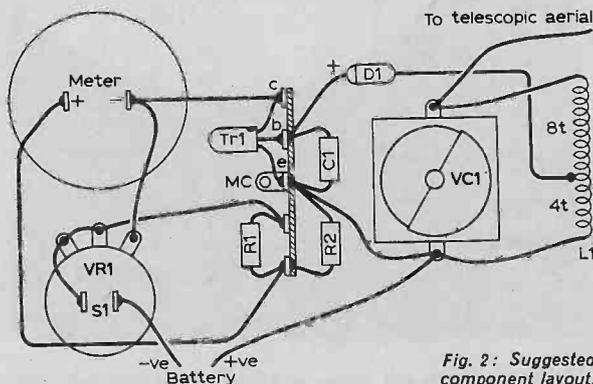


Fig. 2: Suggested component layout.

## ★ components list

VC1	25pF—see text
C1	100pF
D1	OA70
L1	see text
M1	0-1mA moving coil meter
Tr1	OC71
VR1	10kΩ pot with switch
R1	680Ω
R2	680Ω
B1	1.5V battery
Five way tag strip, case, telescopic aerial, 16 s.w.g. enamelled copper wire.	


## CALIBRATING AND TESTING

To test the unit, it should be held with its aerial about 18in. from the transmitter aerial. The field strength meter tuning control should then be turned slowly until a reading appears on the meter. It is advisable to get the field strength meter calibrated approximately and the easiest way of doing this is to use a signal generator, the earth of which should be connected to the positive rail. The output lead from

continued on page 365


# CAR AERIAL SIGNAL BOOSTER

P. HAND

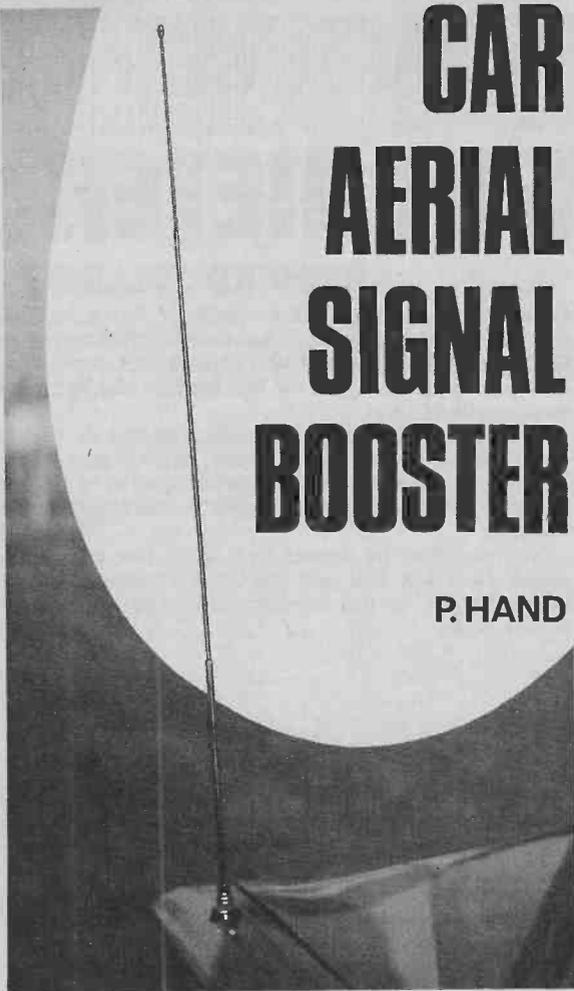

THE need for this amplifier became apparent because of the reduction in signal strength when operating a portable radio in a car. Listening was made practically impossible, particularly to B.B.C. Radio 2. Although the set has a socket for a car aerial which is connected to a loop winding on the ferrite rod and a proper wing mounted car aerial was used. A large amount of interference was picked up even though the sparking plug leads were suppressed, the car generator output terminal had a  $1\mu\text{F}$  capacitor to chassis and the coil

switch terminal a  $1\mu\text{F}$  capacitor to chassis. This was due to the small signal producing practically no a.g.c. voltage, therefore the sensitivity of the set was maximum, making the set acutely responsive to electrical interference. The addition of this small r.f. amplifier made a vast improvement. The increased signal input to the ferrite rod pushes the set hard into a.g.c., cutting out the interference and making listening a pleasure once more.

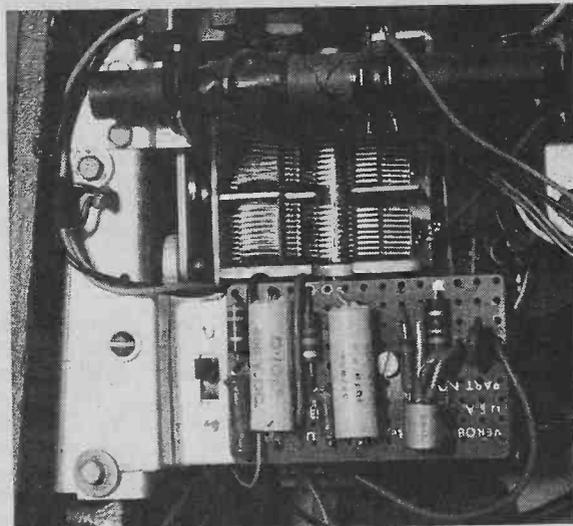

The signal booster may be mounted inside the existing cabinet as shown.

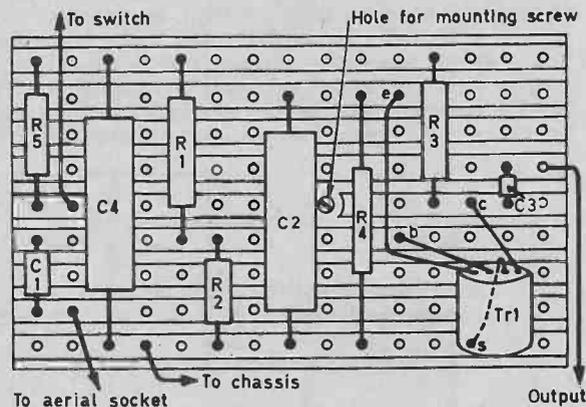


Fig. 2: The component layout on Veroboard.

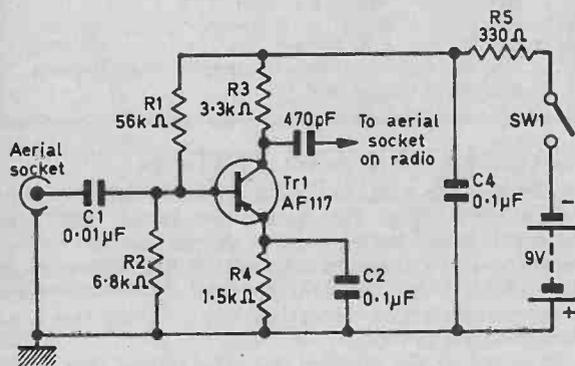



Fig. 1: The circuit of the signal booster.

## CIRCUIT DETAILS

The circuit uses an AF117 transistor in the common emitter mode. The base bias is set by the negative voltage at the junction of R1 and R2 and by the voltage across the emitter resistor R4. C2, the emitter by-pass capacitor is to prevent the emitter resistor affecting the signal. The signal is applied to the base via C1, R3 is the collector load and the output is taken from C3. The total current drain from the nine volt battery is under 1mA.

All the components except the switch are mounted on a piece of Veroboard  $2\frac{1}{8} \times 1\frac{1}{8}$  ins. Only one break in the Veroboard is required, the hole for mounting is also drilled at this point. Component layout is shown in Fig. 2.

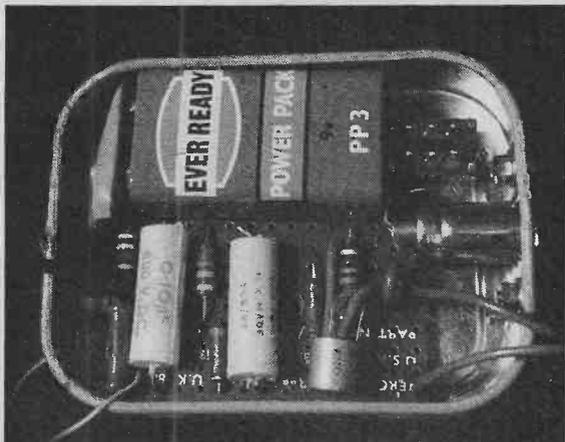Two methods of housing the amplifier are possible. The authors method was to mount the amplifier inside the case of the radio with which it is going to be used. A small bracket was made on which a double pole switch is mounted, together with the amplifier. A thin piece of insulating material is put behind the Veroboard to insulate it from the



Alternative method of using the signal booster is to build it into a tin as shown above.

bracket. This method of housing can be used when there is sufficient space.

The second method, should it prove impossible to find sufficient space, is to build the amplifier into a small case as shown in the photograph with its own battery. A short length of co-axial cable is used to connect the amplifier to the radio via the aerial socket.

## 27MHz FIELD STRENGTH METER

—continued from page 363

the generator should then be held near the field strength meter aerial. The signal generator should then be set to 27MHz and the field strength meter control VC1 tuned slowly for the maximum meter reading.

The dial reading on the field strength meter should then be noted and marked. This operation should then be repeated, with spot frequencies each side of 27MHz until the full coverage has been calibrated. It should be stressed that the coil should not be bent or touched at all after calibration as this will certainly alter the readings.

## USING THE INSTRUMENT

When used to check a transmitter, the field strength meter should be held about 18in. from the transmitter and adjusted for maximum meter reading. The dial setting can be compared with that obtained during calibration and this will indicate the transmitter's approximate frequency.

**See you at the  
R.S.G.B. Show  
August 19th—22nd**

# THE MW COLUMN

**A**UGUST marks the end of the summer season on the medium waves, the effect of the longer hours of darkness being apparent, even at the beginning of the month. North American stations are usually audible as early as 0030 hrs GMT. Canadians appearing first. Look for CBN 640kHz St. John's Newfoundland; CBH 860 Halifax Nova Scotia; CJON 930 St. John's; CHER 950 Sydney N.S.; CHNS 960 Halifax; CKBW 1000 Bridgewater N.S.; CBA 1070 Moncton New Brunswick; CKEC 1320 New Glasgow N.S. Stations from the East Coast of the United States appear a little later, the more prominent being WNBC 660kHz, WOR 710, WABC 770, WCBS 880, WINS 1010 all in New York City; WHDH 850 in Boston; WBAL 1090 Baltimore; WCAU 1210 Philadelphia; WKBW 1520 Buffalo N.Y. By 0230 hrs stations further inland may be heard:— WJR 760kHz 'The Great Voice of the Great Lakes' in Detroit; WBBM 780, WLS 890, WCFL 1000, in Chicago; WHO Des Moines Iowa on 1040; KMOX 1120 'The Voice of St. Louis'; WOAI 1200 San Antonio Texas. By the end of the month reception of the West Coast becomes possible from 0400 hrs GMT until sunrise. This is a favourable time of year for the West Coast since European QRM is light just before dawn while locals have not yet signed on. Last year the following stations were logged during the first week in September; KOMO 1000kHz and KING 1090kHz both in Seattle; KNX 1070 Los Angeles, KFBK 1530 Sacramento California. Others that might be heard are KSL 1160 in Salt Lake City Utah and KEX 1190 in Portland Oregon.

The recent interest in Vintage Radio brings to mind that early broadcast receivers operated mainly on the medium and long waves. Many of them could pull-in DX from North America, for in the mid-twenties it was not unusual to read of reception of stations such as 'WGY Schenectady N.Y. on 380 metres' by DXers using straight receivers and indoor aerials. The state of the MW band was more favourable for DX then, as there was little QRM while transmitters used flat-topped aerials which radiate lots of sky wave. Vintage receivers would hardly be successful on the medium waves today (though it would be intriguing to try one out), but many of the early stations are still broadcasting and are often logged by the DXer. WGY is currently on 810kHz; it was heard by the writer as recently as the 13th of June this year. Older DXers may care to look for CBO 910kHz in Ottawa; CBM 940 Montreal; KDKA 1020 Pittsburg; WBZ 1030 Boston; WBT 1110 Charlotte North Carolina; WHAM 1180 Rochester N.Y. A few old-timers have changed callsign. WFAF New York City is still on 660kHz (454m) but is now called WNBC. WLWL Cincinnati, which once had a power of 500kW is now WLW 700kHz with a modest 50 kW. It is interesting to note that a new 50kW transmitter installed at WOR New York City (710kHz) during 1968 replaced one which had been in service continuously since 1922.

CHARLES MOLLOY



# checking surplus crystals

ARTHUR DOW

**A**LTHOUGH surplus crystals are readily available, cheaply and in large quantities, many of them are not marked with their frequencies or at best are marked with a code or 'channel' number.

While it is possible to get information to decode these numbers it is far simpler in the long run to make a direct check on the crystal to determine its fundamental frequency.

In some cases the frequency indicated on the crystal holder is an operating harmonic frequency and not the fundamental. So once again the necessity arises to find the fundamental by direct means.

It is possible to build a simple transistorised oscillator using the Pierce circuit so that just about any crystal plugged into it will oscillate.

But to determine the fundamental frequency of this crystal with a receiver can lead to false answers because of the several spurious signals that can be generated due to the beating together of oscillators in the receiver and the fundamental and harmonics of the crystal under test.

Fortunately there is a simple way by which the fundamental frequency of any crystal can be found quite accurately before a final precise measurement is made.

## Conventional use of GDO

All that is required is a Grid-dip Oscillator or g.d.o. This will normally have plug-in coils and a roughly calibrated scale for each range. It should be stressed that this calibration is really quite rough since the coil is subject to outside influences that can seriously affect the frequency at which the g.d.o. will oscillate.

In normal use the g.d.o. is loosely coupled to the tuned circuit being investigated and then tuned until grid current shown on its meter suddenly dips. Fig. 1.

The g.d.o. is then moved away from the tuned circuit to reduce the coupling until a good clean sharp dip is obtained on the meter. The g.d.o. should, if possible, be placed with respect to the tuned circuit, so that it does not have to be held in the hand.

It is at this point that the signal from the g.d.o.

can be picked up by a nearby receiver and its frequency determined. This is only an approximate answer since the frequency of the g.d.o. is being measured and not that of the tuned circuit itself.

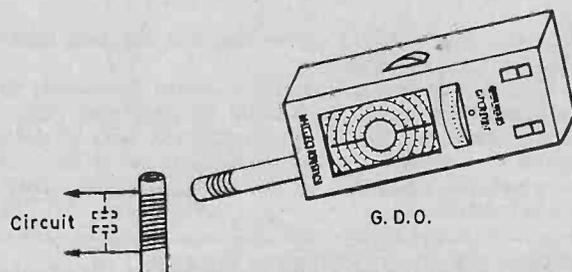


Fig. 1: Conventional use of a g.d.o. to investigate the resonant frequency of a tuned circuit.

It is no use getting a dip on a hand-held g.d.o. and then taking the g.d.o. across the room to a receiver and expecting the frequency to remain constant.

## Checking Crystals

When the g.d.o. is used to check the fundamental frequency of a crystal a slightly different technique is used. A few turns of wire are wound on a former which is slightly larger in internal diameter than the g.d.o. coils. The ends of the coil are connected to a suitable holder for the crystal, Fig. 2, but if it is

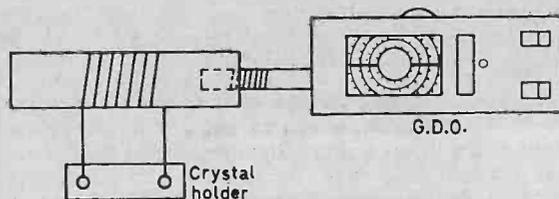


Fig. 2: Using a g.d.o. to "excite" a crystal at its fundamental frequency.

expected that a large number of crystals having different size pins and spacings are to be checked it is suggested that a permanent board be made up with a number of different holders, all connected in parallel.

The lowest frequency range of the g.d.o. is chosen to begin with and its coil inserted into the crystal coil. Tuning from the low end to the high end of the range very slowly a dip will occur as soon as the g.d.o. passes the frequency of the crystal. At this point the crystal is absorbing power from the g.d.o. and it should begin to oscillate at its own natural frequency provided that the coupling between the coils is sufficient.

When the g.d.o. is used to check a conventional tuned circuit the dip in grid current takes the form shown in Fig. 3(a) but when it is used to check a crystal the form changes to that of Fig. 3(b). This is because the g.d.o. frequency becomes locked to that of the crystal once the crystal is oscillating and the tuning of the g.d.o. is ineffective over a small range and its frequency is precisely that of the crystal.

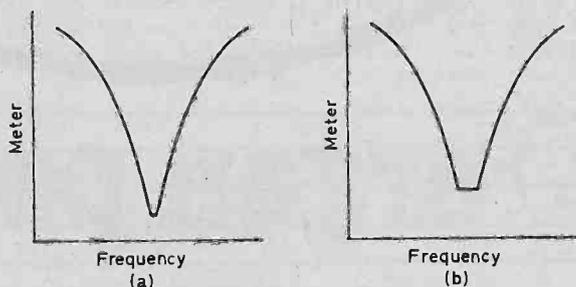


Fig. 3. (a) Grid current of g.d.o. when used conventionally as in Fig. 1. (b) grid current when used to "excite" crystal.

The g.d.o. frequency and hence that of the crystal can now be measured on a receiver in the conventional manner. Depending on the degree of accuracy of measurement required the calibration of the receiver should be cross checked against a standard crystal calibrator with 1MHz, 100kHz, 10kHz and possibly 1kHz check points.

It should be remembered that in practice the precise operating frequency of the crystal will depend upon the type of circuit in which it is used. If it is necessary to order a crystal for a specific frequency from a manufacturer the type of circuit to be employed should be stated.

## Notes

The 'locking' effect, mentioned above, between the g.d.o. and the crystal is very marked but if it is not obtained during the initial tests the coupling between the coils should be increased by sliding the g.d.o. coil further into the crystal coil.

It is important to begin with the g.d.o. on its lowest frequency range, probably about 1.5-4MHz, so that the crystal will oscillate initially on its fundamental frequency rather than on an overtone mode. If it should work on such a mode further confusion will arise if an attempt is made to measure the crystal frequency because of the fact that overtone frequencies are not integral multiples of the fundamental frequency. On, say, the fifth overtone

the measured frequency may be several kilohertz different from the fundamental frequency multiplied five times.

## Alternative method

If a g.d.o. is not available a signal generator or a frequency meter may be used using the set-up shown in Fig. 4. The voltmeter should have a high resistance of about 10,000Ω/volt or a general purpose meter may be used on a low voltage range. A valve voltmeter will be more sensitive and should be used in preference to a conventional test meter.

The procedure is to tune the signal generator from its lowest frequency, about 1MHz, upwards until a deflection is noted on the meter. In this case the peak indication is the point at which the crystal is resonant with the applied signal.

If the calibration of the signal generator is not to be relied upon then an external receiver can be used to measure the frequency as before. The author has found in practice that much too much faith is placed on the calibration of signal generators which do not have their own internal calibration facilities.

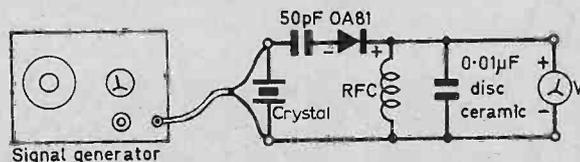


Fig. 4. Use of a signal generator instead of a g.d.o. to determine frequency of crystal.

If the output of the signal generator has a calibrated attenuator the 'goodness' of the various crystals can be estimated by keeping the input voltage to the crystals constant and noting the relative deflection on the meter when the signal generator is tuned to the frequency of the crystal under test.

Once the fundamental frequency of a crystal has been found its performance in the overtone mode can be judged by applying signal voltages from the g.d.o. or the signal generator at the third, fifth or higher harmonics. The dip shown on the g.d.o. will be less than that obtained on the fundamental of the crystal and in the same way the output indication using a signal generator will be less, as the order of the harmonic is increased.

Crystals designed especially for operation on the overtone mode will naturally perform better in this test than those that are not, but after testing a number of crystals, the good and the bad will be obvious.

**"Project Autumn"**

compete for the  
**Practical Wireless**

**"Designer's Trophy"**


see page 390

**T**HIS is a self contained 13 note (single octave) organ pedal bass unit that can be used with any portable or domestic electronic organ having no bass note pedals of its own. It can be tuned to pitch without having to alter the tuning of the individual notes i.e., the pitch of the whole octave can be raised or lowered by approximately one full note.

It features a drum brush accompaniment that sounds each time a pedal is pressed regardless of whether the pedal is pressed and released quickly for a bass note of short duration, or the pedal held down to sustain the bass note. The drum brush sound begins with an attack and decays of its own accord.

The output signal level is sufficient for any external amplifier requiring not more than 1 volt r.m.s. signal input.

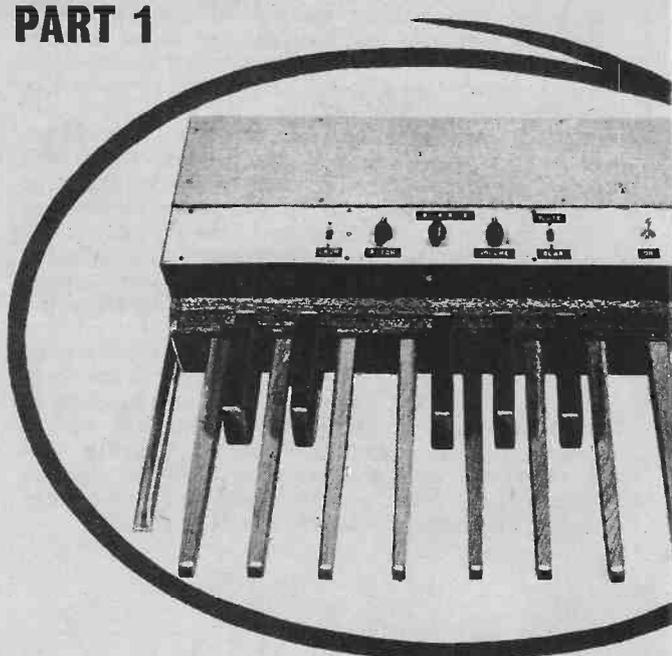The pitch available is 16ft. or 8ft., or 16 and 8ft. combined. The 16ft. octave is C to C (32 to 65Hz approx) and the 8ft C to C (65 to 130Hz approx). These two pitches are combined in equal proportions of amplitude when the 16+8ft. pitch is used. The voicing is flute or clarinet which is fairly conventional for domestic electronic organs.



## Circuit

The block diagram (Fig.1) shows the general circuit arrangement which employs a total of nine OC71 transistors. The consumption is quite low so that operation from a PP9 (9V) battery is economical. There is little point, therefore, in making the


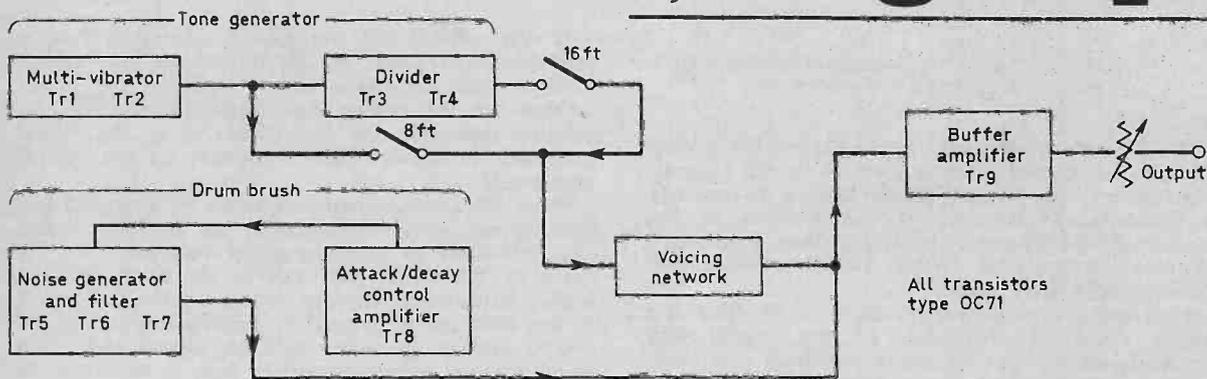


Fig. 1: Diagram showing the function of each stage of the Pedal Bass unit.

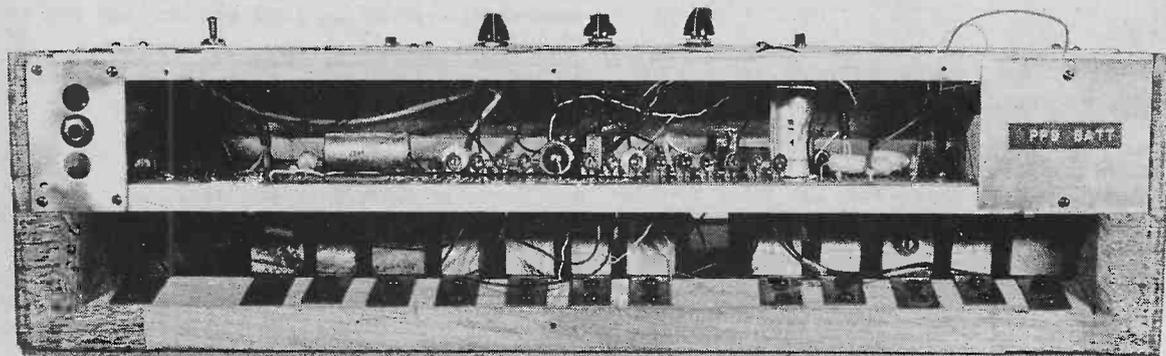

Rear view of unit shows, above, the circuit boards with the battery compartment to the right, and, below, the spring mounting of the pedals.



## A. LESTER-RANDS

# al bass unit

unit mains powered but there is no reason why this should not be done.

The main note generator is a multi-vibrator the output of which provides the 8ft. pitch notes. The pitch for 16ft. is obtained from a divider driven from the multi-vibrator. Then follows the voicing circuitry, the output of which is taken through a buffer amplifier and via a volume control to the output socket. The maximum signal level available at the

output is approximately 1V r.m.s.

The drum brush circuit consists of a three stage white noise generator and filter, the output being controlled by a special attack-decay circuit (control amplifier). The drum brush signal is then attenuated to balance with the pedal bass output and passed to the buffer amplifier.

## Pedal Frame and Case

The basic pedal frame complete with the thirteen pedals mounted and sprung can be obtained ready-made from Henrys Radio Limited (see materials list). The frame has a plywood top cover which is not required as a case to house the circuit boards and battery etc. has to be built up onto the frame itself. This top cover is  $\frac{3}{8}$ in. plywood and can be used for making the end pieces of the case.

Those who wish to make the pedal frame and pedals will find the dimensions etc., in the various diagrams. The main frame is shown in Fig.2 (A and B) and made from soft planed wood. Note that the rear member of the frame (the pedal support rail) is bevelled to the dimensions given in Fig.2B. The front main member of the pedal frame is fitted with guide posts for the pedals as shown in Fig.3. These posts are made from  $\frac{1}{8}$ in. diameter dowel and are glued in so that they just clear the upper pedal stop rail (see inset Fig.3).

Next, the pedals themselves should be made and checked for fitting within the frame but not secured until the case frame work has been completed. Details of the pedals (8 white and 5 black) are given in Fig.4. Note the soft leather or plastic binder around each pedal, a couple of turns of adhesive plastic insulating tape will do, and also the small hardboard pads which press on the keying contacts.

Each pedal is secured to the rear member of the main frame by means of a flat phosphor bronze spring, details of which are given in Fig.5. *Do not bend these strips*, they will bend themselves (Fig.6) when the pedals are finally fitted, and the springs secured to the rear pedal support rail.

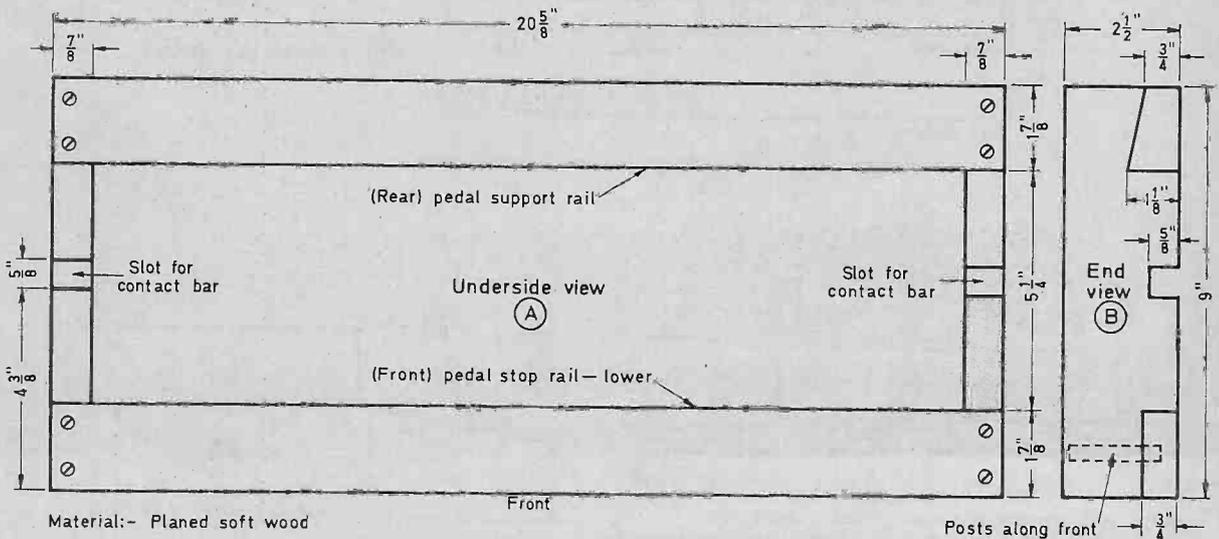


Fig. 2: Constructional details of the wooden pedal frame of the unit.

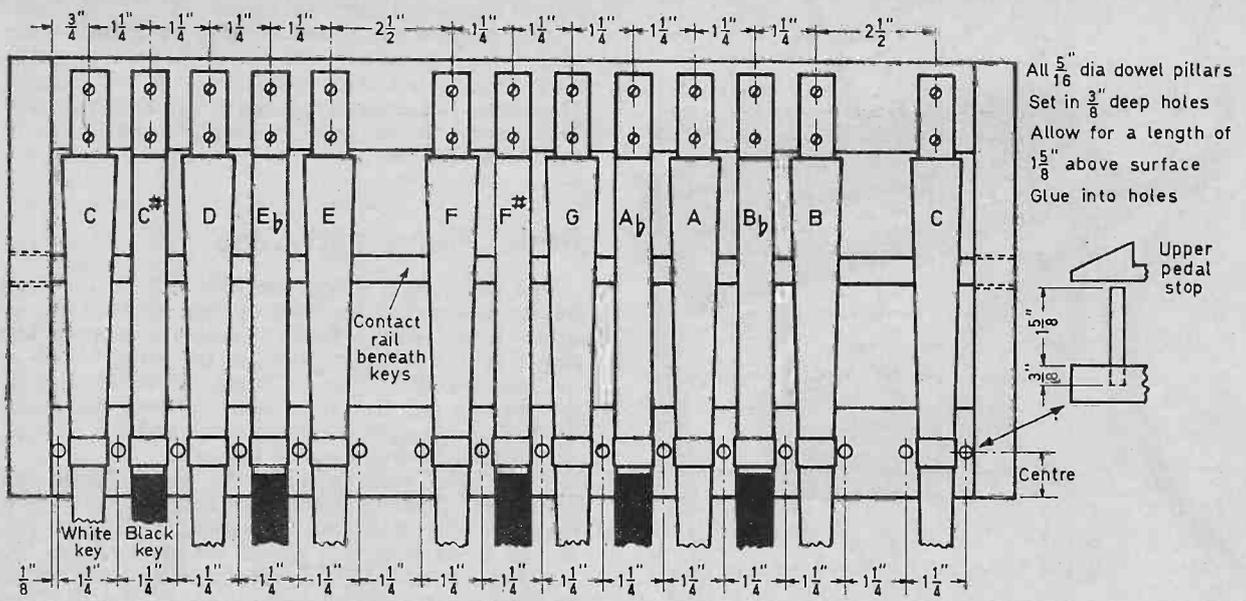


Fig. 3: Positioning of the pedals on the frame. Compare with the heading photograph of the completed unit.


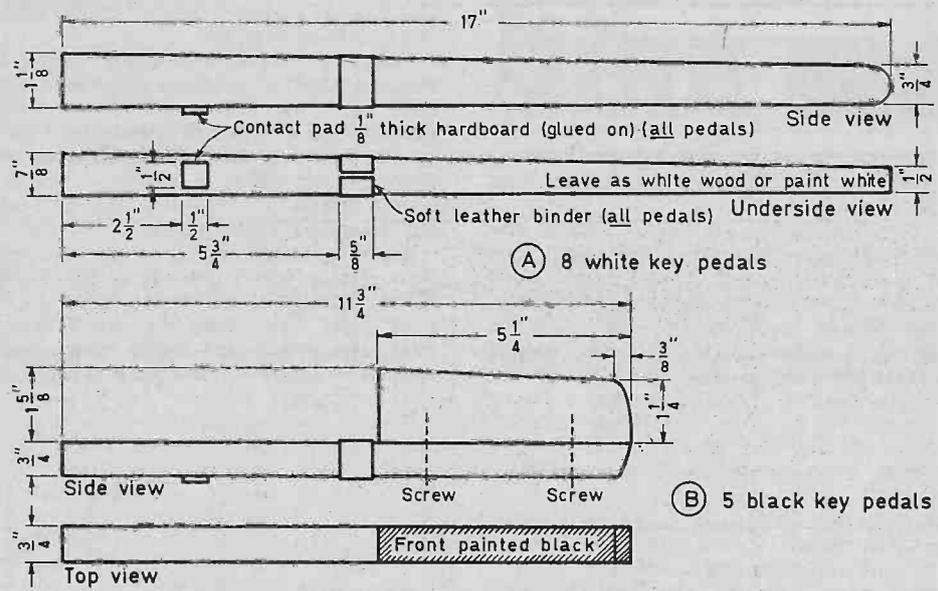


Fig. 4: Details for making the key pedals.

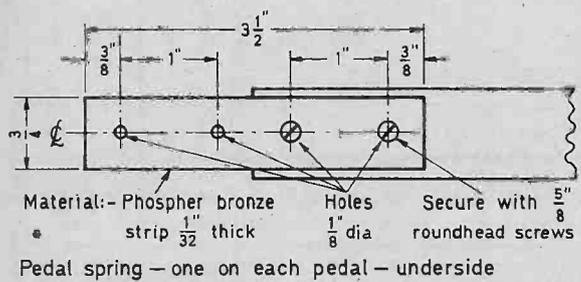

Material: - Phosphor bronze strip  $\frac{1}{32}$ " thick  
 Holes  $\frac{1}{8}$ " dia  
 Secure with  $\frac{5}{8}$ " roundhead screws  
 Pedal spring - one on each pedal - underside  
 Fig. 5: Details of the phosphor bronze springs and their fitment to the pedals.

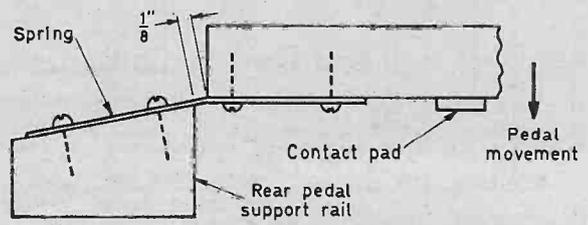


Fig. 6: Fitting of the springs to the pedal frame unit.

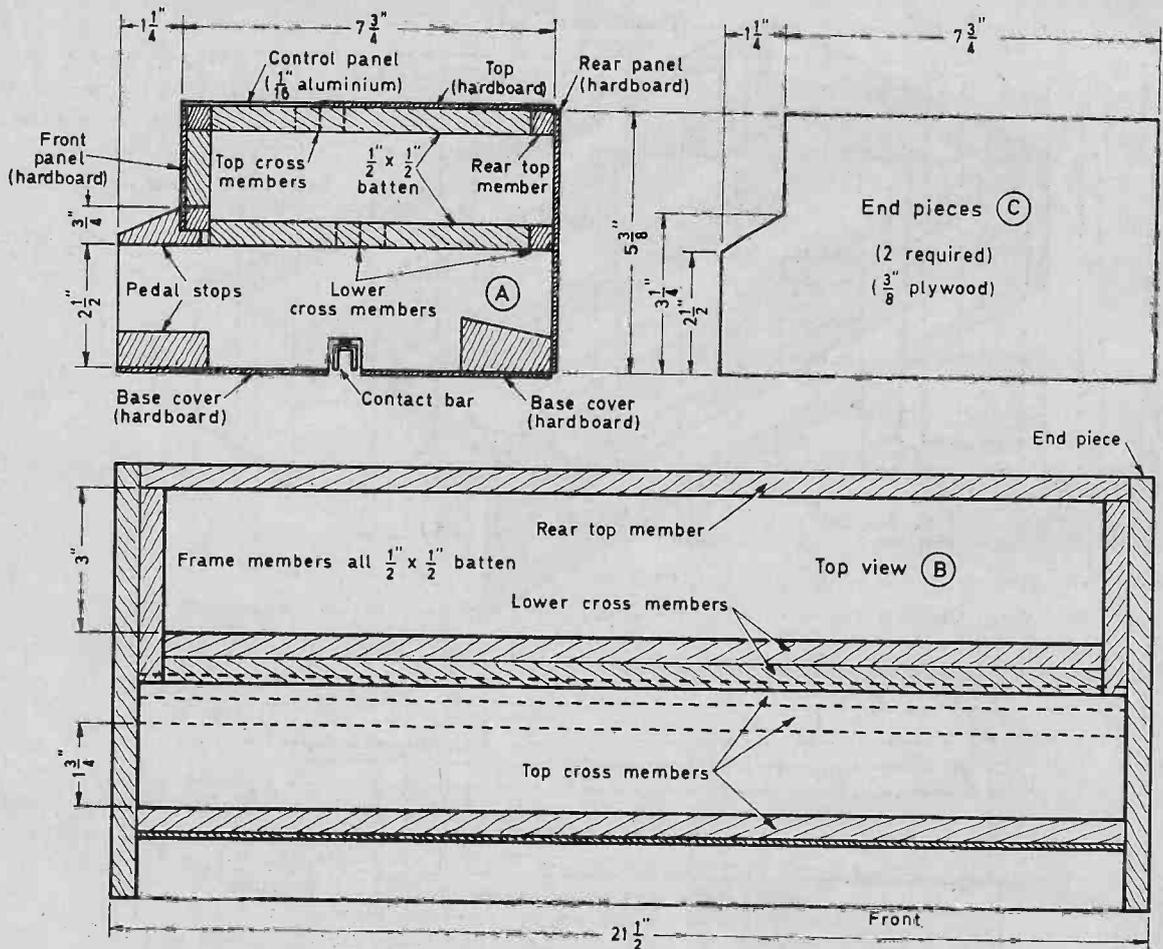


Fig. 7: Construction of the framework for the case.

Before fitting the pedals the case must be completed by first making and assembling the two end pieces (Fig.7C) and then by building up the framework. (Figs.7A and Fig.8). Note the shape of the upper pedal stop rail (Fig.7A). Wood of this shape can be obtained from most D.I.Y. decorating materials shops.

The alternative would be to use a rail  $1\frac{1}{4} \times \frac{3}{4}$  in. and drop the front panel accordingly. The frame members, (Fig.8) can be glued in place with Evostik. Leave the 'lower rear member' (Fig.8) until the pedals have been secured in place.

Pieces of hardboard cut to appropriate size can be glued to the frame members to form a box for the PP9 battery at the right hand end of the frame (looking from the rear) as shown in the photograph.

The contact assemblies have two pairs of contacts —one pair make as the other pair break and each pair is isolated. The press-to-make pair are used for keying the pedal bass notes and the press-to-break pair are used for actuating the drum bush sound.

The thirteen contact assemblies are mounted on the rail (Fig.10, inset) and the rail is then attached to the pedal frame so that the contact sets are uppermost beneath each pedal (Fig.9). Note the clearance for the downward movement of the pedal. To obtain the requisite spacing between the contact actuating buttons and the pads on the pedals small spacers can be fitted between the contact rail and the slots in the pedal frame.

## Contact Rail and Keying Contacts

The contact support rail is 'U' shaped aluminium channelling and fits underneath the pedal frame in the slots at the sides (Figs. 2A, 3, 7A and 9). Dimensions and drilling details for the rail are given (Fig.10). Note that the fixing holes for the contact assemblies must be  $\frac{3}{32}$  in. in diameter to take the self tapping screws supplied with them.

## ★ materials list

Planed wood for pedal frame and pedals. (The frame and pedals may be obtained, ready-made, from Henrys Radio Ltd. Type 13/2).  
 Pedal contact set (13 off), Leaf type, 1 pair make, 1 pair break. (Henrys Radio Ltd.) Aluminium U channelling,  $\frac{1}{2} \times \frac{1}{2} \times \frac{3}{4}$  in, 20 $\frac{3}{4}$  in. long.  
 Aluminium sheet, 18 s.w.g. for output socket panel.  
 Plywood, woodscrews, etc.

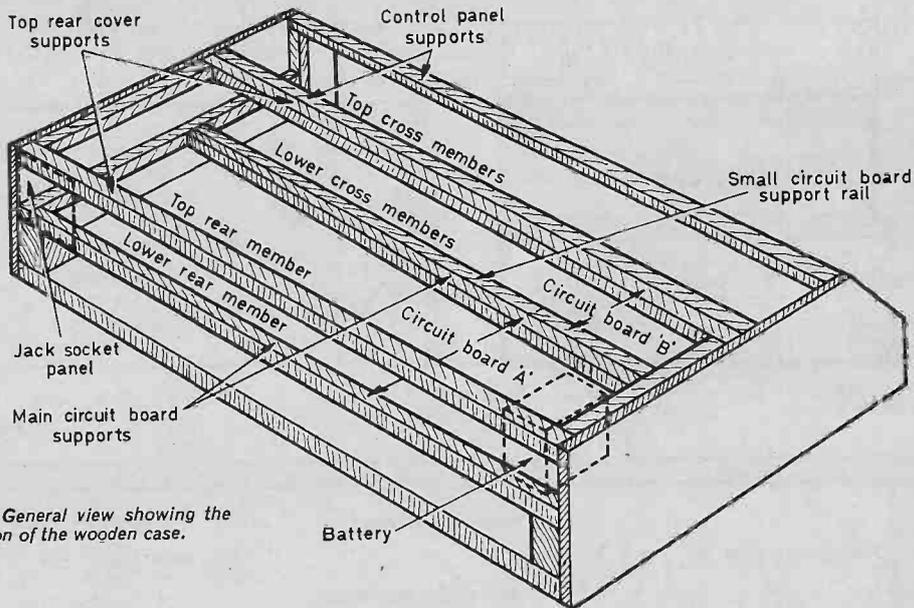


Fig. 8 (above): General view showing the construction of the wooden case.

Fig. 9 (below): Final assembly of the pedals and their positioning relative to the contact rail.


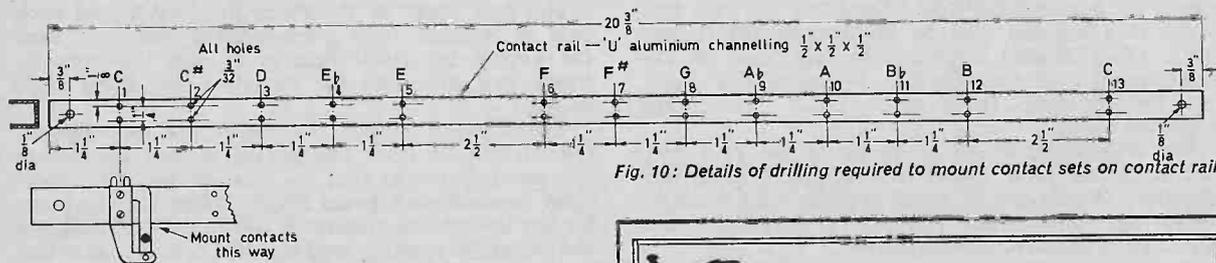


Fig. 10: Details of drilling required to mount contact sets on contact rail.

On completion of the pedals and contact rail assembly, fit felt strips along the front frame members beneath and above the pedals (Fig.9). Carefully check the movement of the pedals and that they do not rub against the guide pillars which, if necessary, can be filed down a little to obtain clearance. Check that all contacts operate on downward movement of the pedals i.e., check actual contact make and/or break with a continuity meter.


Part 2 will give the circuit diagram of the complete unit and describe its functions. There will also be details of the assembly of the circuit boards and a full components list.

**TO BE CONTINUED**

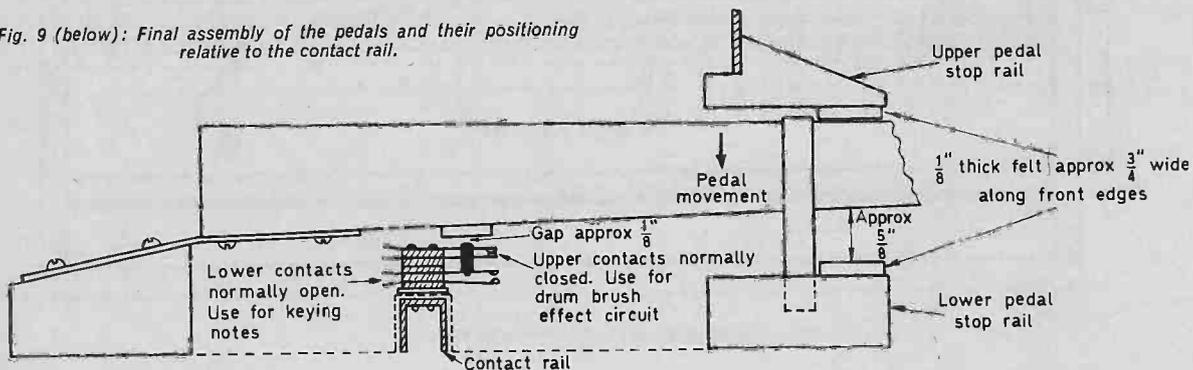

compete  
for the  
*Practical Wireless*  
"Designer's Trophy"

# R. BUNNEY

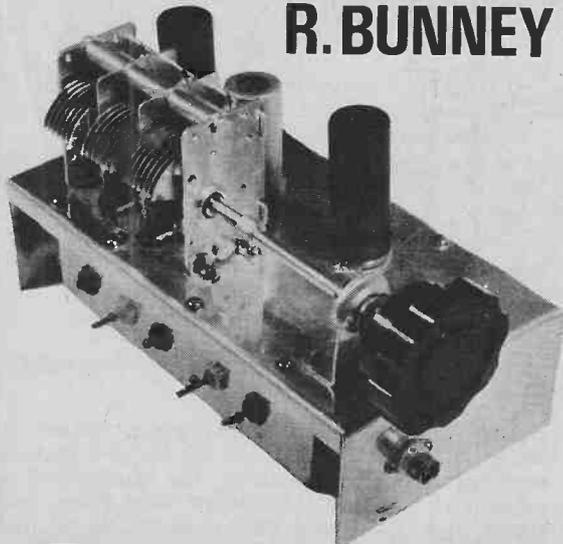

## LOW BAND VHF CONVERTER

CONSIDERABLE importance is attached by the author to the reception in this country of 'paging' stations operating in the United States on frequencies around 35MHz. Not from any 'eaves-dropping' aspect but as a check on the upward movement of the m.u.f. and the possibilities of reception of signals via the F2 layer.

The writer's interest lies with v.h.f. propagation, 30MHz and above, so with the increased activity in the low v.h.f. band over the past few years, due to maximum sunspot activity, need was felt to cover this part of the spectrum with something better than a modified RF25 unit. The RF25 unit, having switched positions, gave only limited coverage. It had been set to the main paging station frequencies, so coverage was inefficient at frequencies removed further than 500kHz from the preset position. Accordingly, a simple converter was made, using commercially available coils, giving fully tunable coverage from 26MHz to 53MHz.

### Circuit

Basically the unit (Fig. 1) contains an r.f. stage using an EF80 or EF184 pentode, feeding into an ECF80 frequency changer. Internal coupling between the triode oscillator and pentode mixer is sufficient for frequency conversion to the i.f. of 5MHz. The output from the frequency changer feeds into an i.f. amplifier, prior to feeding into the main receiver. By using an i.f. of 5MHz, the main receiver can be accurately set to 5MHz on a standard frequency station, before inserting the converter output. An alternative circuit is given (Fig. 2) for using an ECC84 cascode stage. No r.f. gain control is fitted, but those readers living adjacent to a channel B1 transmitter may find one necessary to prevent overload (Fig. 3).

### Construction

The layout of the various components can be seen from the photographs. The usual precautions of short, direct wiring and single earthing points for each stage should be observed.

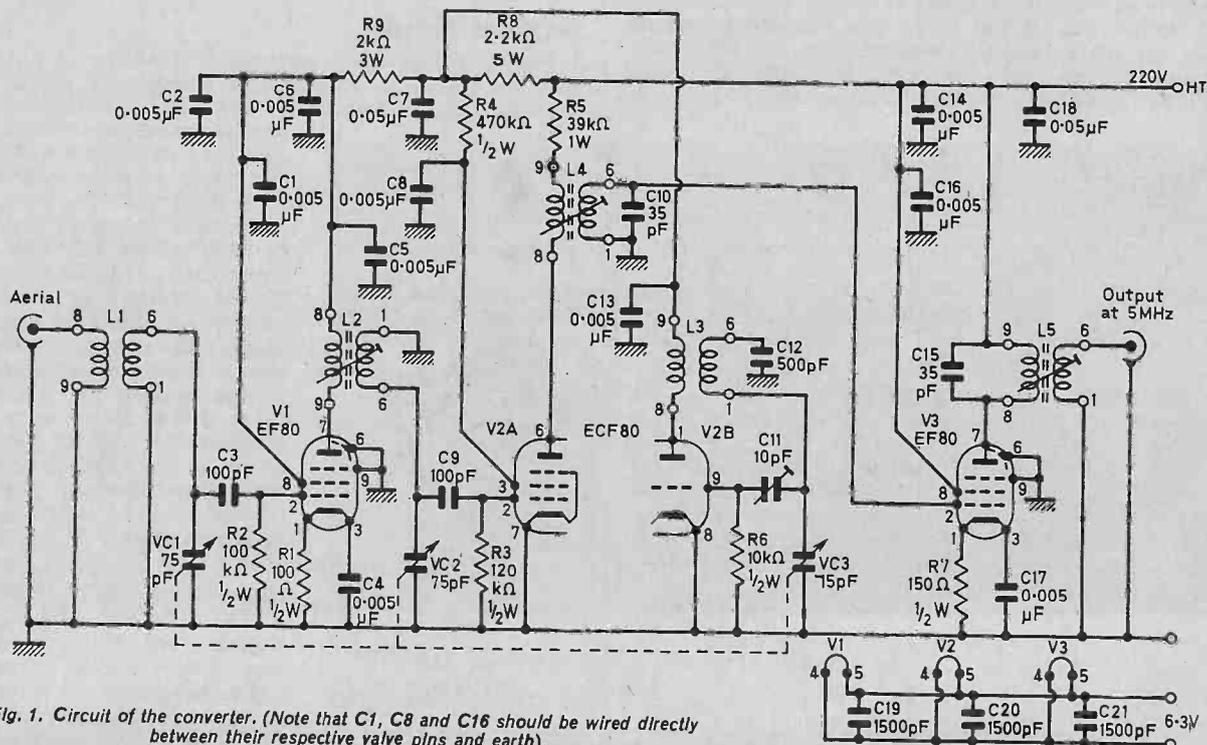


Fig. 1. Circuit of the converter. (Note that C1, C8 and C16 should be wired directly between their respective valve pins and earth).

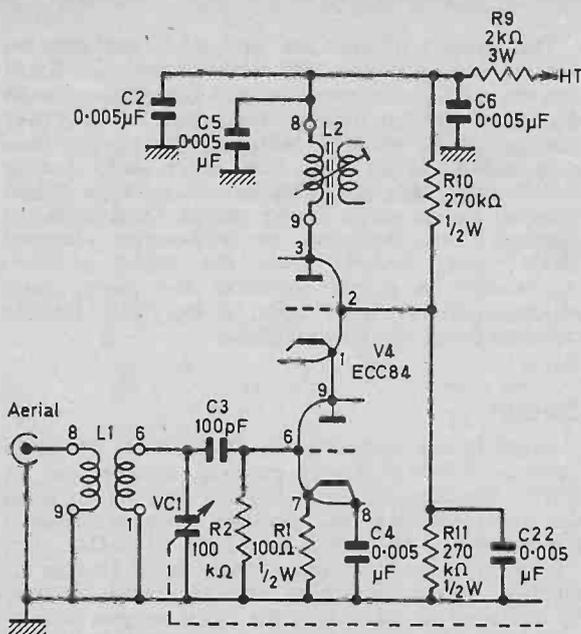


Fig. 2. Alternative r.f. stage using the cascode circuit.

The five coils are mounted on a sub-panel with shields between the coils. The power supply is fed into the unit via a four pin socket but constructors may wish to make their own arrangements in this respect. Likewise a suitable dial can be fitted and calibrated after the alignment of the unit has been finished.

### Alignment

The alignment of the converter is simple. Inject a low level modulated signal at 5MHz to pin 2 Valve 3. Adjust the core of L5 to give maximum reading on the main receiver 'S' meter, or for maximum sound output with the a.g.c. switched off. Now shortcircuit the oscillator section tuning gang to

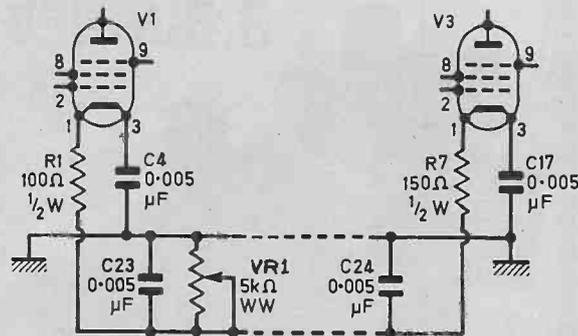


Fig. 3. Modified circuit incorporating an r.f. gain control.


chassis, and inject the 5MHz signal to pin 2 of Valve 2. Adjust the core of L4 to give maximum readings as before. Remove the shortcircuit and adjust C11 to approximately one third value. Find a signal such as Crystal Palace sound on 41.5MHz, and align L2 to give maximum signal. Alternatively inject low level signals from a signal generator at about 40MHz and adjust the core of L2. Check that the range 30-50MHz is covered, then seal C11 with wax to prevent movement.

Denco recommend that 50pF tuning capacitors are used, but at the time of construction a 3-gang unit of these values was not available, hence the use of a Jackson 3-gang 75pF unit was necessary, which tends to increase the l.f. coverage below 30MHz. It may be found that performance falls off below 26MHz, due to the low value of C11. Increasing its value to improve the l.f. coverage tends to deteriorate the h.f. performance at 50MHz. So C11 should be set for optimum v.h.f. reception.
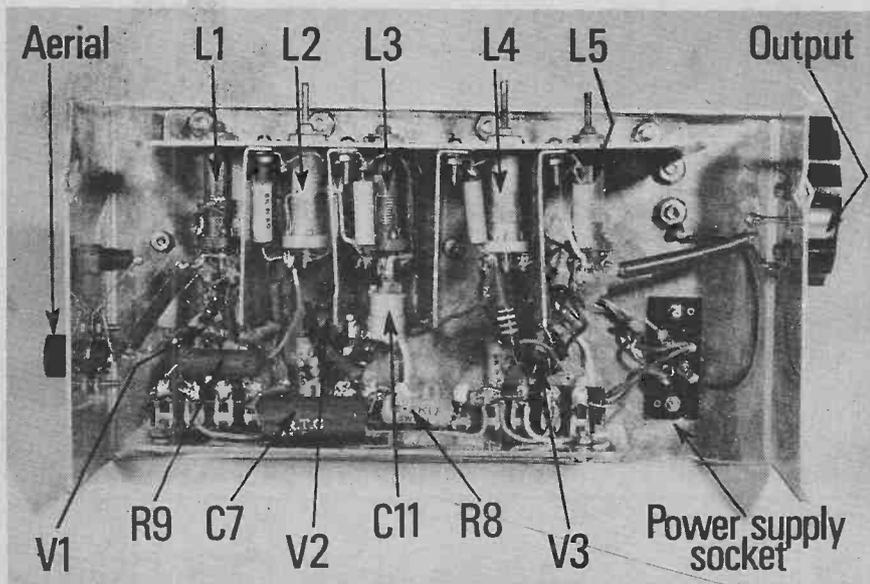
### General Notes

During the daytime, particularly in winter at sun-spot maximum, a considerable number of signals may be heard, often above the m.u.f. listings and predictions. From the east, forward-scatter networks and r.t.t.y. may be heard from the USSR. The most spectacular reception may be heard from the west, particularly from the United States. A large number of domestic services, such as waterworks undertakings, gas suppliers, private individuals and shops have 2-way communication circuits between 30 and 45MHz, and both base stations and mobiles can be heard in communication.

The most important frequencies are 35-22, 35-58, 43-22, 43-58MHz. Paging stations are situated in most towns, and in some cities there may be three or more. A subscriber carries a small radio receiver,



Bottom view of converter with identification of major components.

tuned to the paging station. If the subscriber leaves his office or home, and is wanted urgently, he is paged by the transmitter. Each transmitter will repeat the message on a tape loop, interspersed with its identification. Consequently it is extremely easy to identify and locate these transmitters by the call sign, and in most cases, the name of the town is given.

## ★ components list

### Resistors:

R1 100 $\Omega$ $\frac{1}{2}$ W	R6 10k $\Omega$ $\frac{1}{2}$ W
R2 100k $\Omega$ $\frac{1}{2}$ W	R7 150 $\Omega$ $\frac{1}{2}$ W
R3 120k $\Omega$ $\frac{1}{2}$ W	R8 2.2k $\Omega$ 5W
R4 470k $\Omega$ $\frac{1}{2}$ W	R9 2k $\Omega$ 3W
R5 39k $\Omega$ 1W	R10 270k $\Omega$ $\frac{1}{2}$ W
VR1 5K WW pot	R11 270k $\Omega$ $\frac{1}{2}$ W

All Resistors  $\pm 20\%$

### Capacitors:

C1 0.005 $\mu$ F 500V disc	C13 0.005 $\mu$ F 500V disc
C2 0.005 $\mu$ F 500V disc	C14 0.005 $\mu$ F 500V disc
C3 100pF 500V	C15 35pF 500V 1% S.M.
C4 0.005 $\mu$ F 500V disc	C16 0.005 $\mu$ F 500V disc
C5 0.005 $\mu$ F 500V disc	C17 0.005 $\mu$ F 500V disc
C6 0.005 $\mu$ F 500V disc	C18 0.05 $\mu$ F 500V
C7 0.05 $\mu$ F 500V	C19 1500pF 500V
C8 0.005 $\mu$ F 500V disc	C20 1500pF 500V
C9 100pF 500V	C21 1500pF 500V
C10 35pF 500V	C22 0.005 $\mu$ F 500V disc
C11 10pF trimmer	C23 0.005 $\mu$ F 500V disc
C12 500pF 500V 1% S.M.	C24 0.005 $\mu$ F 500V disc

VC1-2-3 3 gang 75pF per section (Jackson E3)

### Inductors:

L1 Blue —Range 6	} Denco, miniature dual purpose
L2 Yellow—Range 6	
L3 Red —Range 6	
L4 Yellow—Range 3	
L5 Yellow—Range 3	

### Valves:

V1, 3 EF80 (or EF184)
V2 ECF80
V4 ECC84

### Miscellaneous:

Chassis 9 x 5 x 2 $\frac{1}{2}$ in. Slow motion drive and knob.  
3 B9A Valve holders and screens. 2 co-axial sockets.  
Tag strips. 4 pin socket.

A number of paging stations is given, but this is only a few of the many presently transmitting, those listed having been received by the author.

KIF	651	Ft. Lauderdale	Fla.	35-58	MHz
KIY	508	Orlando	Fla.	35-22	
KEC	519	Rochester	NY	35-58	
KCC	482	Pembroke	N. Hamp.	35-22	
KQD	303	Detroit	Mich.	35-22	
KIQ	510	Jacksonville	Fla.	35-58	
KIM	905	Charlotte	N.C.	35-22	
KGC	400	Scranton	Penn.	35-58	
KGC	266	Allentown	Penn.		
KGC	223	Philadelphia	Penn.	35-22	
KKI	445	Houston	Tex.	35-58	
WWA	335	San Juan.	P. Rico	35-22	
KKM	248	Oklahoma City	Okl.	35-58	
KGC	397	Wilkes Barrie			
KIF	650	Birmingham	Ala.	35-58	
KIE	953	Atlanta	Ga.	35-58	

During good conditions in the winter of 1969, stations as far west as KKI 445 Houston and KKM 248 Oklahoma City, both on 35.58MHz were heard. Usually reception is easiest from the east coast, and especially down to KIY 508 Orlando, Fla. One rare pager, only heard twice here is WWA 335 San Juan, P. Rico on 35.22MHz. The aerial in use for these various signals in the lower v.h.f. band has been a vertical 12 foot whip. Activity in the west is usually from 1300-1800 b.s.t.

The Worldwide TV-FM DX Association often publishes articles and lists on activity within the 30-40MHz spectrum, in addition to their normal coverage of t.v. and f.m. DX proper. Information on this club may be obtained from W.TV.FM. DX Assoc., P.O. Box 5001, Harbor Sta., Milwaukee, Wis., 53204 U.S.A. For a sample bulletin enclose 2 IRC.

It should be pointed out that reception upon these high frequencies of ionospheric signals is dependent on sunspot activity (other than sporadic E). Consequently, there may be periods during which little or no activity is heard. However conditions can improve over the space of a few days. During January, 1970, the highest frequency noted was 39.8MHz, after which conditions deteriorated.

It must be stressed at this point, that **NO ATTEMPT MUST BE MADE TO VIEW THE SUN DIRECTLY**, to observe sunspot activity. One second is sufficient to damage the eye. A telescope on a tripod may be used to project the sun on to a card, and spots can then be observed upon the card, indicating sunspot activity.

Never look at the sun through a telescope, even though it may be supplied with a special filter to fit over the lens. These filters can fracture under concentrated heat. Even when the sun is setting, no attempt must be made to view the sun directly. ■

## "PROJECT AUTUMN"

Are you entering for the competition?

Are you stuck for ideas?

What about designing:—

A cassette tape recorder?

A general purpose oscilloscope?

A car radio/tape player?

An intercom system for the home?

A wavemeter to comply with the amateur transmitting service regulations?

See page 390 for details of

## "PROJECT AUTUMN"

VISIT US

RSGB SHOW

AUG 19-22

# TAKE 20

JULIAN ANDERSON

**A series of simple transistor projects, each using less than twenty components and costing less than twenty shillings to build.**

**T**HERE is one piece of equipment that all of us own (if we take the hobby at all seriously) and that is a multimeter. These cost anything from under £2 to over £30 though the majority fall in the £3 to £7 range. Although all of them will measure voltage, current and resistance the ranges are often inadequate, especially on the cheaper types. For a few bob several additional features can be added to the cheaper and simpler testmeters. We shall describe four circuits but with a little imagination and application of Ohms law it will be seen that still further ranges can be added.

## TRANSISTOR TESTER

Many readers will occasionally wish to test transistors but do not feel that the construction of a separate piece of equipment is justified. For these people a separate and simple circuit can be kept for the odd occasions on which it is needed—the cost should be no more than a few shillings as it uses only a three-pole four-way switch and a 100kΩ resistor.

Although this tester only measures the transistor using the internal battery (almost universally 1.5V in the cheaper range on multimeters) it will give an

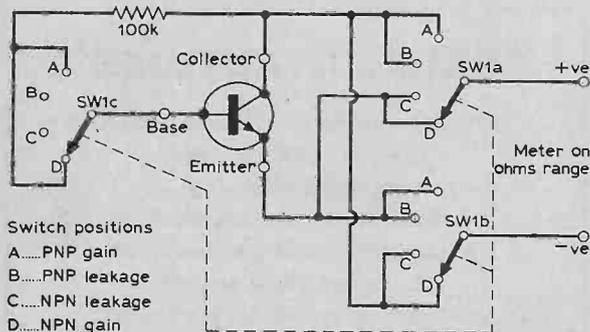


Fig. 1: The circuitry necessary for converting a multimeter to a transistor tester.

indication of leakage and gain. In position A the meter's battery negative is applied to the collector and the positive to the emitter, the resistor connected between the collector and the base applying a bias of about 10μA. A good device should show quite a deflection on the scale. In position B the bias is removed and the meter indicates the leakage. Positions C and D do the same for NPN transistors. Note that there is not a mistake in the circuit; the positive connection to the meter is in fact connected to the battery negative.

## LOW VOLTAGE RANGE

The base bias voltage on transistors is usually

## No. 17

## MULTIMETER EXTRAS

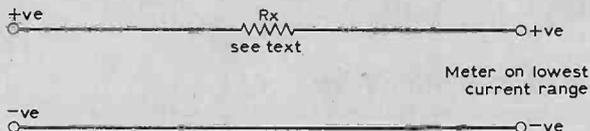


Fig. 2: Adding a 1V range is a simple matter but refer to the text for the value of Rx

between 0.3V and 0.8V but only a few meters have a 1V range. However this can be added simply by the addition of a resistor. With the meter on its lowest current range and a resistor equal to the meters sensitivity a 1V range is added. Thus a 1,000Ω/V meter would need a 1kΩ and a 20,000Ω/V meter a 20kΩ resistor. Unfortunately the internal resistance of the meter has to be subtracted from this. The simplest way to find the correct value is to fix a 100Ω pot across a 1.5V battery and adjust so that a 1V reading is obtained on your testmeter. This should be done with care as the accuracy of the scale will depend upon it. Then change over to the lowest current range and select a resistor that will give full scale deflection from the 1V supply. This will probably mean using two or even three resistors in series; once the exact value has been found the resistors can be soldered together.

## A.C. CURRENT RANGE

Only the most expensive multimeters include an a.c. current range and although this is rarely needed it is sometimes necessary to measure mains current. If a 1Ω resistor is inserted in the line a 1A current will drop 1V and a 10Ω resistor will drop 10V and of course we can measure a.c. volts. We won't attempt to describe this further but make sure that the resistor is a high wattage type and if used on the mains that careful insulation is used (we don't want to lose too many *Take 20* readers!).

## HIGH RESISTANCE RANGE

Many of the cheaper meters have very inadequate resistance ranges—the centre scale reading is usually only 3kΩ and it is practically impossible to get an accurate reading over 50kΩ. The additional com-


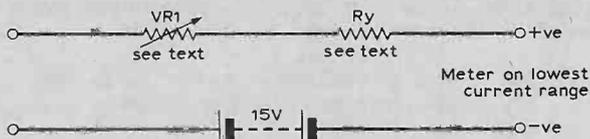


Fig. 3: A high resistance range can be added to nearly all test meters by using the above arrangement on the lowest current range.

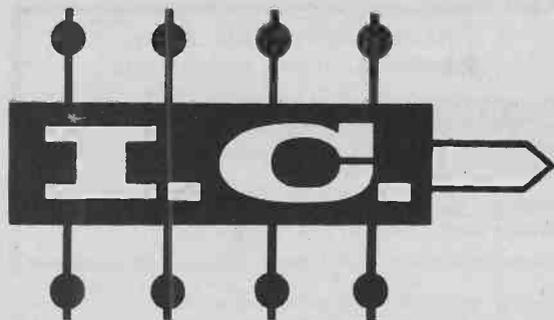ponents in Fig. 3 will improve the best resistance range by a factor of 10. Again we use the meter on its lowest current range and instead of the integral 1.5V battery we use an external 15V one (B154 or similar). The combined resistance of VR1 and Ry should be 15kΩ for a 1,000Ω/V type and 300kΩ for a 20,000Ω/V meter so for the former type a 12kΩ resistor and a 5kΩ pot should be used. ■



# OF THE MONTH

L.A.J. IRELAND

Number 11

Motorola MFC 4000P Audio Amplifier

**I**N presenting this month's integrated circuit there is the question of whether or not it would fit more appropriately in the "Take 20" slot, since the unit in question, the Motorola MFC4000P, costs little more than £1, and to date is probably the simplest unit to use. In a package occupying less than 1/100th of a cube inch it provides a  $\frac{1}{4}$  watt audio amplifier, matching a 16 ohm loudspeaker.

To add to the simplicity, only four leads connect the silicon monolithic chip to the outside world, d.c. power supply, signal input and output, and a common earth. The unit is the first of a series of "consumer" circuits, intended for the amateur constructor and for manufacturers of utility equipment such as portable radios and baby alarm or intercom units.

higher than the 9 volt battery which powers the standard pocket radio or domestic transistor device; the MFC 4000P on the other hand, will operate at full rating down to 6 volts d.c., though with the harmonic distortion raised to 4% due to crossover difficulties. At a nominal 9 volts a harmonic distortion figure of 0.7% is attained, a better performance than is common in the standard pocket radio preamplifier, driver and class B output lineup.


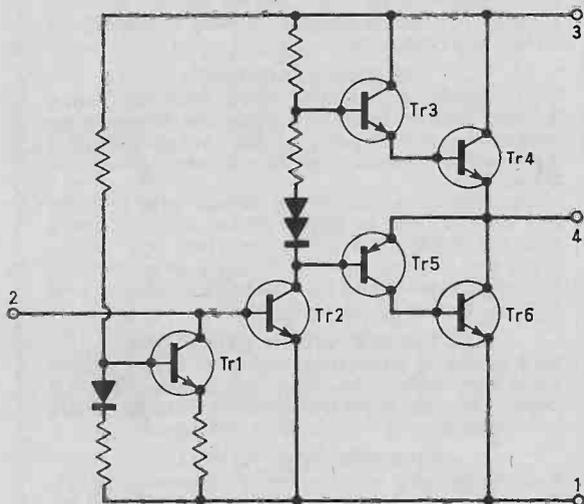


Fig. 1. Equivalent circuit of the MFC 4000P

As such, it does not match the G.E series of audio integrated circuits introduced to our readers in March 1970 "P.W.", or the increasingly familiar Plessey SL403, which are essentially hi-fi devices with internal noise levels 65dB. or more down, or with less than 0.5% total harmonic distortion.

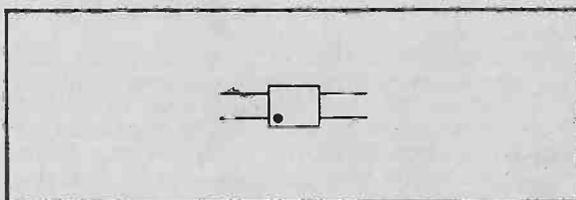On the other hand, those devices require feedback and decoupling connections to the chip, with multiple pins and an external metallic heat sink. Further, previous audio units required a d.c. supply



Actual size of the MFC 4000P. The dot identifies pin 1, the numbering going clockwise

Finally, the device is used in a completely transformerless circuit, enabling a degree of compactness to be achieved previously unobtainable in home built equipment. In use, the slightly higher noise and distortion figures are not significantly reflected in the output sound, since in the type of equipment for which this unit is intended, quality is inevitably loudspeaker limited, and there is no advantage to be attained by incorporating more expensive semiconductor complements.

## Circuit

Now for a brief consideration of the circuit itself, Fig. 1. It is a six transistor unit, with Tr1 acting as a stabilising element across the input, and therefore controlling all stages of the direct-coupled circuit. The preamplifier transistor, Tr2, is in an orthodox common emitter configuration and biased by d.c. feedback from the output stage of the circuit (shunted, as mentioned already, by the regulator Tr1, which however, does not affect the signal appearing at the base of Tr2 since the collector circuit of a transistor has a high impedance to applied signals).

It will be noted also that there is also a frequency-dependent element (the 0.003 $\mu$ F capacitor) in this negative feedback loop to determine the frequency response of the complete amplifier, Fig. 2.

The driver transistors, Tr3 and Tr5, are a complementary pair, as indicated by the direction

indications on the emitter symbols. Therefore, although the same signal is applied to each from the collector of Tr2, there is 180° phase difference between the signals passed on to the output pair, since Tr3 may be regarded as an emitter follower while Tr5 is common emitter and therefore signal inverting. Tr4 and Tr6, then, act as class B push-pull output transistors.

However, due to the presence of the diodes and small resistance between the bases of Tr3 and Tr5,

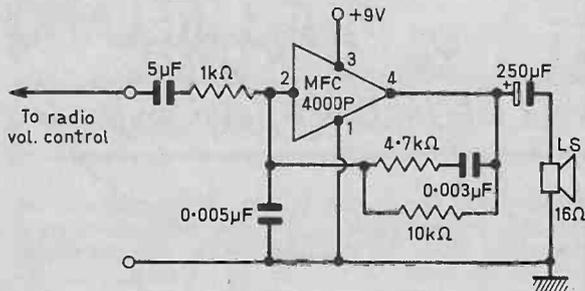


Fig. 2. Circuit of an audio stage suitable for a pocket radio

there is a small standing current in the output pair even in the no-signal or quiescent condition, to minimise the crossover distortion sometimes found in class B systems.

In practice, the current drain of the circuit rises from an average of 3.5mA in the quiescent condition to 60 mA on full load. The advantage of class B operation, with battery drain highly dependent on output, is evident. Sensitivity is high, with a power output of 50mW (average pocket radio listening level) available on an input signal of only 15 mV, but Fig. 3 indicates the use of an external preamplifier should one be desired for special low-signal applications, such as operation from a tape head. Otherwise the circuit shown in Fig. 2 should be fully satisfactory.

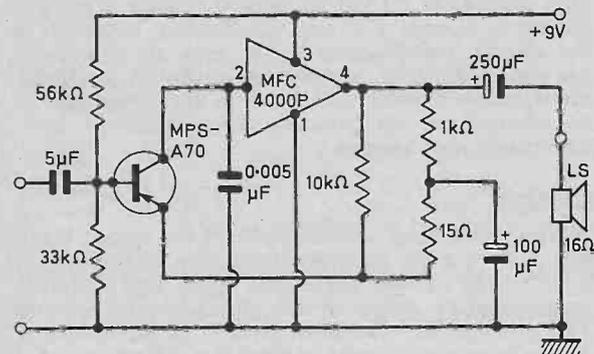


Fig. 3. Alternative circuit using a discrete pre-amplifier

It is hoped to introduce shortly the Motorola MFC4010P, as the next element in this series of sub-miniature 4-pin i.c.'s (it is a general purpose direct coupled amplifier, for a.f. or i.f. applications); until then, this attractive little unit should provide food for thought and work for the soldering iron! The unit is available from Jermyn Industries, Vestry Estate, Sevenoaks, Kent or Henrys Radio Ltd. who can also supply the transistor MPS A70. ■

## RADIO ENGINEERING AND COMMUNICATIONS EXHIBITION

If you're in Town Aug. 19-22, pop along to the above exhibition and see our latest designs. Venue is Royal Horticultural Society's New Hall, Greycoat Street, Westminster, London, S.W.1.

Exhibits include: Light Beam Phone; Vibrasonic Guitar Amp.; Organ Pedal Bass Unit.

## COME AND VISIT US AT THE 1970

### INTERNATIONAL AUDIO FESTIVAL & FAIR OLYMPIA, LONDON W.14

OCTOBER 20th-24th (10 a.m.-9 p.m. each day)

The PRACTICAL WIRELESS stand will feature many constructional features.

## PRACTICAL TELEVISION SEPTEMBER

### CONSTRUCTOR'S SINGLE-STANDARD I.F. STRIP

A vision and intercarrier sound i.f. strip is not an easy item for the constructor, with the high gain and wide bandwidth involved. This design has been very carefully devised by Keith Cummins with the problems of enthusiasts in mind to go with his 625-line receiver. Having two controlled stages, the strip is usable with almost any tuner unit.

### COLOUR TELEVISION

Two features next month on colour television. First a detailed look at burst and automatic chrominance control circuitry, including a pulse generator stage of a type which has not previously been used in domestic TV equipment.

Secondly an account of the various types of tubes that can be used to display colour pictures, beam masking, deflection and indexing types, their advantages and disadvantages. Includes a description of the Sony Trinitron and the "Essex" tube which could lead to big changes in TV receivers.

### ELECTRONIC VIDEO RECORDING

EVR is due to be with us soon and brings with it many new techniques. Next month we publish a detailed account of the system with a block schematic and description of a colour EVR teleplayer.

### LOG-PERIODIC AERIAL

The log-periodic aerial offers considerable advantages where narrow beam width and good front-to-back ratio are required. A practical design will be given together with an outline of the principles of this type of aerial.

ON SALE NOW

## QUERY COUPON

This coupon is available until 4th September 1970 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, SEPTEMBER 1970

# INCREASE YOUR KNOWLEDGE



Established 1891


**MANY COURSES TO CHOOSE FROM incl.**  
 RADIO & TV ENGINEERING & SERVICING,  
 TRANSISTOR & PRINTED CIRCUIT SERVICING,  
 COLOUR TV SERVICING, ELECTRONICS,  
 NUMERICAL CONTROL ELECTRONICS,  
 TELEMETRY TECHNIQUES, CONTROL SYSTEMS,  
 ELECTRONICS FOR AUTOMATION,  
 COMPUTERS, ETC.

**ALSO EXAMINATION COURSES FOR**

C. & G. Telecommunication Technicians' Certs  
 C. & G. Electronic Servicing  
 R.T.E.B. Radio/TV Servicing Certificate  
 P.M.G. Certificates in Radiotelegraphy  
 Radio Amateurs' Examination  
 General Certificate of Education, etc

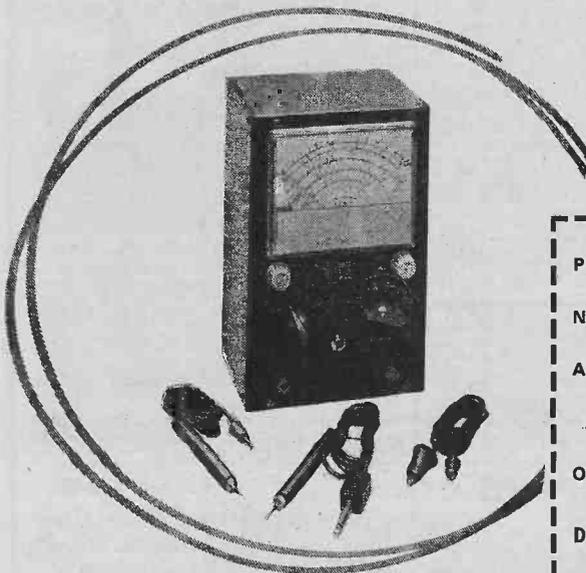**BUILD YOUR OWN RADIO AND INSTRUMENTS**

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments, incl. professional-type valve volt meter (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



## RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

### THERE IS AN **ICS** COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

**FILL IN AND POST THIS COUPON TODAY**

You will receive the **FREE ICS Prospectus** listing the examination and ICS technical courses in radio, television and electronics **PLUS** details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME .....

ADDRESS .....


OCCUPATION..... AGE.....

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
 Dept. 170, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8

9/70



# GOING BACK...

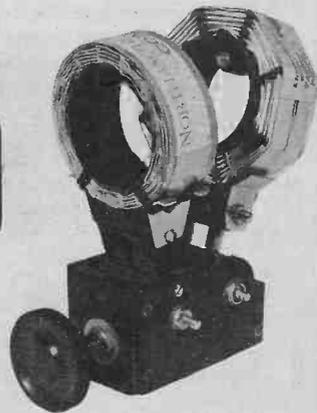

COLIN RICHES  
ARTHUR DOW

**N**OW that the name of Hertz has come into everyday use in the jargon of the electronic engineer it is perhaps opportune to look back at the work of that early pioneer in radio communication, Professor Heinrich Hertz, and to consider whether or not the perpetuation of his name as a technical term is really justified.

Heinrich Hertz, born in 1857, became a pupil of the famous physicist von Helmholtz and received a good grounding in electricity as far as the "state of the art" permitted at that time.

Although dying in 1894 at the early age of 36 Hertz was able to carry out many experiments that had the most far reaching effect on man's attempt to communicate at a distance.

In 1888 Hertz had progressed enough to be able to demonstrate the propagation of electromagnetic waves, or Hertzian waves as they were then known, thus confirming the earlier theoretical work of Maxwell.

Hertz showed that the waves conformed to the same laws as applied to the propagation of light namely that they could be bent and reflected.

Earlier experimenters had noticed spurious effects in the vicinity of large spark coils, when they were operating, such as secondary sparking between metal objects completely isolated from the coil.


Among those experimenters was Edison who coined the phrase "etheric force" to explain away the effect of secondary sparking at a distance.

Hertz's "receiver" consisted of nothing more than a length of wire formed into a circle leaving a minute gap at the ends across which a spark would jump when Hertzian waves were induced into the loop from the nearby spark coil "transmitter".

Hertz found that he could increase the effective range of his equipment by adding metal spheres and plates to the spark gap on the transmitter and to the ends of the receiver loop. He was in fact using what we now call "dipoles" and towards the end of his experiments Hertz was able to "resonate" his transmitter and receiver to approximately the same wavelength. The frequencies involved were in fact what we would now term v.h.f.!

As if these incredible experiments were not enough Hertz then demonstrated the phenomenon of "standing waves" using a long cage of wires strongly resembling the present-day Lecher wire system of measuring wavelength.

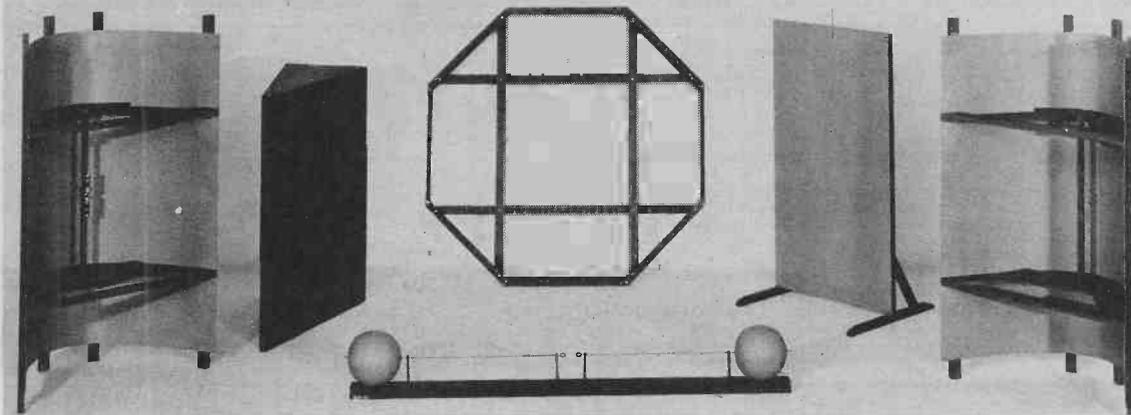Using sheet metal reflectors and reflectors made of wire stretched on wooden frames Hertz showed that his Hertzian waves could be treated as light waves and bent or reflected at will. Little did Hertz realise that he was really demonstrating the basic principle of radar!



"Crown Copyright, Science Museum, London"

Collection of reflectors and resonators used by Hertz in his experiments.

Since many modern v.h.f. and u.h.f. aerial systems strongly resemble the equipment used by Hertz in his famous experiments it would not be ungenerous if he were to be regarded as the "father" of v.h.f. communication. It is surely little enough reward for his name to be associated with the basic unit of frequency, the cycle per second, or Hertz (Hz), since he was the first to devise a method of measuring the frequency or perhaps the wavelength of electromagnetic waves.

## Mobile 1922

**I**N 1922 experiments were being made with radio receivers in cars and there follows a description of one of the first car radios: "The receiving apparatus used is a Marconiphone 6-valve set, five of the valves being high-frequency amplifiers and the other a rectifier. The valves are of the special low-current consumption type. The aerial is fitted on the roof of the car and is so constructed that it can be raised and lowered at will by means of a hand-wheel.

"The receiver is bedded in spongy rubber and mounted in a compartment under the floor boards immediately in front of the rear seats. Control is effected by means of three levers in the car interior

and on the control panel there is an indicating 'pilot' bulb which shows the intensity of the filament lighting of the valves. The valve filament lighting is effected from the starting and lighting battery of the car. High-tension batteries of the usual type are fitted in the same compartment as the receiver. In order to prevent interference from the ignition and lighting equipment of the car, the magneto and generator are screened.


Two pairs of double earpieces and two single earpieces may be employed, so that four persons can listen in at once.

The effective receiving range of the equipment is approximately fifty miles radial distance from a broadcasting centre when used with the frame aerial fitted to the car roof. When all the broadcasting stations are in operation a car fitted with this apparatus, will, therefore, practically be within range of broadcast."
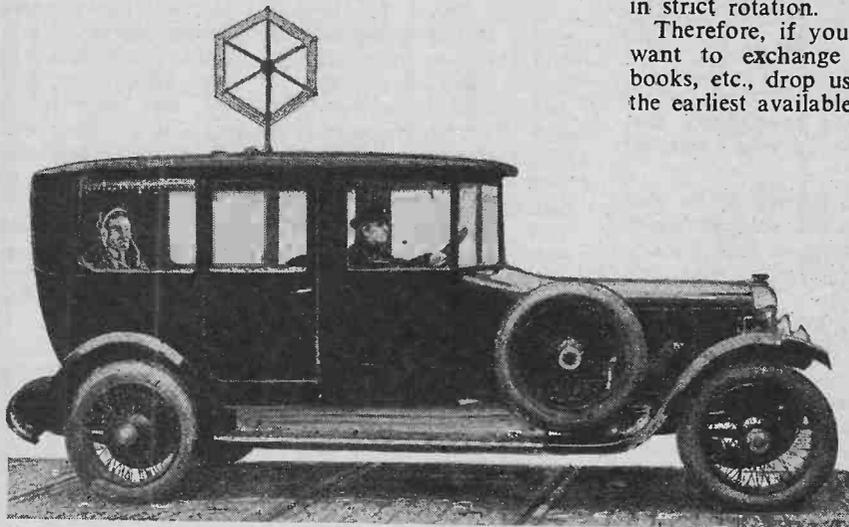
## Vintage CQ

Should readers wish to have a "Vintage CQ" published, we will be prepared to accept letters for inclusion. They will of course be inserted in the magazine when space permits and will be dealt with in strict rotation.

Therefore, if you have any queries on old gear, want to exchange or obtain vintage equipment, books, etc., drop us a line and we'll put a note in the earliest available issue.



*This photograph shows a Daimler car equipped with a Marconiphone receiver and frame aerial. A similar car was used in the Lord Mayor of London's procession 1922.*

## PRACTICAL WIRELESS QUERY SERVICE

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard textbooks. In order to prevent unnecessary disappointment, prospective users of the service should note that:

(a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.

(b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.

(c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.

## WELCOME ! TO OUR STAND

**International Radio Engineering  
and Communication Exhibition**

Royal Horticultural New Hall  
Greycoat Street, Westminster,  
London, S.W.1

August 19-22nd.

# COMET

## Hi-Fi DISCOUNT WAREHOUSES

- All items offered are brand new, latest models in manufacturers' sealed cartons. Fully guaranteed with after-sales service.
- Complete Free price list of over 800 items on request.



Customers Welcome  
Open Daily to the public from 9 a.m. Closed Tuesday 1 p.m.  
Mon. & Sat. 5-30 p.m. Open until 8 p.m. Wednesday, Thursday & Friday.

	Rec. Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>		
ARENA 210 Amplifier ..	£34 13 0	£28 0 0
ARMSTRONG 521 ..	£52 0 0	£42 10 0
DULCI 207 ..	£25 0 0	£17 0 0
DULCI 207M ..	£30 0 0	£20 10 0
GOODMANS Maxamp ..	£54 0 0	£44 10 0
LEAK Stereo 30 Plus ..	£53 0 0	£43 10 0
In teak case		
LEAK Stereo 70 ..	£59 10 0	£47 10 0
LEAK Stereo 70 In teak case ..	£65 0 0	£52 10 0
LINEAR LT.66 ..	£71 10 0	£56 10 0
METROSOUND ST 20 ..	£18 18 0	£15 10 0
PHILIPS RH 591 ..	£32 0 0	£25 10 0
PHILIPS RH 590 ..	£73 0 0	£55 10 0
PHILIPS RH 580 ..	£49 0 0	£37 12 6
PHILIPS RH 580 ..	£26 0 0	£19 10 0
PIONEER SA500 ..	£62 11 4	£45 0 0
PIONEER SA700 ..	£98 0 0	£74 10 0
PIONEER SA900 ..	£134 2 0	£99 10 0
PIONEER Reverbation ..	£45 9 11	£35 10 0
QUAD 35 Pre-amplifier ..	£43 0 0	£37 10 0
QUAD 303 Main Amplifier ..	£55 0 0	£43 10 0
ROGERS Ravensbourne ..	£59 10 0	£46 10 0
ROGERS Ravensbourne (cased) ..	£64 0 0	£49 10 0
ROGERS Ravensbrook ..	£44 0 0	£36 10 0
ROGERS Ravensbrook (cased) ..	£49 0 0	£39 10 0
SINCLAIR 2000 ..	£30 9 0	£24 10 0
TELETON 203E ..	£28 7 6	£19 10 0
TRUVOX TSA, 200 ..	£54 12 0	£34 10 0
VOLTEX 100 watt stereo discotechnique 8 electronically mixed inputs ..	£185 0 0	£139 0 0

	Rec. Retail Price	Comet Price
<b>TUNERS</b>		
ARENA F211 ..	£39 10 0	£33 10 0
ARMSTRONG 523 AM/FM ..	£52 9 0	£44 10 0
ARMSTRONG 524 FM ..	£40 4 6	£34 10 0
ARMSTRONG M8 decoder ..	£9 10 0	£7 10 0
DULCI FMT-7FM ..	£22 1 0	£17 10 0
DULCI FMT-7S Stereo ..	£31 0 0	£25 5 0
GOODMANS Stereomax ..	£62 5 0	£39 10 0
LEAK Stereofetic Chassis ..	£59 18 0	£45 10 0
LEAK Stereofetic In teak case ..	£67 3 6	£50 10 0
PHILIPS RH 690 ..	£39 0 0	£31 10 0
PIONEER TX500 AM/FM ..	£77 18 9	£63 10 0
PIONEER TX900 AM/FM ..	£153 13 10	£125 0 0
QUAD Stereo FM ..	£51 0 0	£39 10 0
ROGERS Ravensbourne ..	£61 17 9	£49 10 0
ROGERS Ravensbrook ..	£45 0 2	£39 10 0
ROGERS Ravensbrook (cased) ..	£51 5 3	£42 10 0
SINCLAIR 2000 ..	£26 14 6	£19 4 6
TRUVOX FM 200/1C ..	£60 11 10	£39 10 0
All above tuners are complete with MPX stereo decoder		

	Rec. Retail Price	Comet Price
<b>TUNER/AMPLIFIERS</b>		
ARENA 2400 ..	£90 6 0	£71 10 0
ARENA 2600 Stereo AM/FM ..	£111 6 0	£94 0 0
ARENA 2700 Stereo ..	£105 0 0	£85 0 0
ARENA T1500F ..	£72 9 0	£59 10 0
ARENA T9000 ..	£203 9 0	£239 0 0
ARMSTRONG 525 ..	£87 16 9	£68 10 0
ARMSTRONG 526 ..	£98 15 6	£79 10 0
ARMSTRONG M8 decoder ..	£9 10 0	£7 10 0
GOODMANS 3000 ..	£77 14 7	£66 10 0
PHILIPS RH781 ..	£74 19 6	£54 10 0
PHILIPS RH790 ..	£125 0 0	£101 10 0
PHILIPS RH691 ..	£83 0 0	£67 10 0
PIONEER KX330 AM/FM/SW ..	£78 12 4	£62 10 0
PIONEER SX770 AM/FM ..	£180 8 6	£129 10 0
PIONEER SX990 AM/FM ..	£194 14 8	£155 0 0
TELETON F.2000 ..	£51 0 0	£37 10 0
TELETON TAT1 ..	£133 0 0	£85 0 0
TELETON R4200 ..	£51 15 0	£39 10 0
TELETON CR10T ..	£39 0 0	£29 10 0
TELETON TFS50 ..	£74 0 0	£59 10 0
All above Tuner Amplifiers are complete with MPX decoder		

<b>CARTRIDGES ALL MAKES STOCKED AT DISCOUNT PRICES</b>		
<b>PICKUP ARMS</b>		
GOLDRING Lenco L75 ..	£12 6 6	£10 10 0
GOLDRING Lenco L69 ..	£9 5 9	£7 0 0
SME 3009 with S2 shell ..	£31 6 3	£25 10 0
SME 3012 with S2 shell ..	£33 7 3	£28 10 0



**SECURICOR**  
SPECIAL DELIVERY SERVICE

All in-stock items value over £50 delivered by **SECURICOR** WITHIN 72 HOURS (Add 12/- only for Securicor delivery)

ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

	Rec. Retail Price	Comet Price
<b>TURNABLES</b>		
ARENA SP25 with base, cover ..	£22 1 0	£17 10 0
B.S.R. McDONALD MP60 ..	£15 0 0	£10 10 0
B.S.R. McDONALD P10 ..	£18 19 6	£13 10 0
GARRARD SP25, fully wired with Goldring G800 magnetic cartridge, complete with base, plinth and cover ..	£22 1 0	£17 10 0
GARRARD SP-25 Mk II ..	£15 11 4	£10 10 0
GARRARD AP.75 ..	£23 16 0	£17 10 0
GARRARD SL.55 ..	£13 17 9	£11 12 6
GARRARD SL.65B ..	£19 6 5	£14 9 6
GARRARD SL.75B ..	£35 12 4	£28 10 0
GARRARD SL.95B ..	£45 9 1	£37 10 0
GARRARD 401 ..	£31 14 2	£26 10 0
GARRARD SL.72B ..	£30 2 0	£24 10 0
GARRARD 3500 with GKS Cartridge ..	£15 15 0	£11 10 0
GOLDRING GL.59 ..	£25 1 6	£21 5 0
GOLDRING 69P ..	£33 11 9	£28 10 0
GOLDRING GL.75 ..	£36 8 2	£29 10 0
GOLDRING 75P ..	£46 18 8	£38 10 0
GOLDRING Covers for 69P and 75P ..	£4 4 3	£3 8 0
GOODMANS 3025 ..	£37 14 9	£32 10 0
PHILIPS 228 ..	£19 19 6	£16 10 0
PHILIPS GA146 ..	£29 9 6	£24 10 0
PHILIPS 217 ..	£33 0 0	£27 4 0
PHILIPS 202 Electronic ..	£84 0 0	£54 0 0
THORENS TD.125 ..	£75 17 8	£59 10 0
THORENS 125AB ..	£120 3 11	£99 10 0
THORENS 150A Mk II ..	£43 12 7	£32 10 0
THORENS 150AB Mk II ..	£47 3 7	£40 10 0
THORENS TD.124/11 ..	£46 15 10	£39 10 0
Bases, plinths, and covers stocked.		

	Rec. Retail Price	Comet Price
<b>SPEAKERS</b>		
ARENA HT 27 ..	£18 18 0	£13 10 0
ARENA HT 28 ..	£17 17 0	£12 10 0
ARENA HT 21 ..	£10 10 0	£9 5 0
ARENA HT 7 ..	£19 19 0	£17 0 0
ARENA HT 10 ..	£22 1 0	£18 10 0
ARENA HT 20 ..	£32 11 0	£26 10 0
ARENA HT 26 ..	£78 15 0	£65 10 0
B & W DM3 ..	£63 0 0	£53 6 0
B & W P2H ..	£94 10 0	£79 0 0
B & W DM1 ..	£32 0 0	£25 10 0
CELESTION Ditton 10 ..	£21 2 4	£17 5 0
CELESTION Ditton 15 ..	£29 0 0	£22 10 0
CELESTION Ditton 25 ..	£59 17 0	£49 0 0
DULCI AS 3 ..	£8 8 0	£6 10 0
GOODMANS Malesia ..	£57 0 0	£48 10 0
GOODMANS Maxim ..	£20 7 9	£16 10 0
GOODMANS Mezzo II ..	£30 18 0	£23 10 0
GOODMANS Magnum-K ..	£40 2 0	£29 10 0
GOODMANS Marimba ..	£24 0 1	£19 10 0
GOODMANS Mambo ..	£22 5 6	£17 10 0
GOODMANS 3005 (pair) ..	£25 0 0	£21 0 0
KEF Celeste ..	£29 0 0	£21 10 0
KEF Concord ..	£43 10 0	£31 10 0
KEF Concerto ..	£53 10 0	£42 10 0
KEF Cresta ..	£22 3 4	£18 10 0
LEAK Sandwich ..	£45 10 0	£34 10 0
LEAK Mini-Sandwich ..	£29 15 0	£22 10 0
LOWTHER Acousta (with PM7) ..	£45 10 0	£38 7 6
LOWTHER Ideal Baffle ..	£35 10 0	£29 10 0

	Rec. Retail Price	Comet Price
<b>LOWTHER Acousta</b>		
(with PM7) ..	£53 0 0	£45 19 6
QUAD Electrostatic ..	£66 0 0	£52 19 6
PHILIPS RH 481 ..	£11 0 0	£9 2 6
PHILIPS RH 482 ..	£18 0 0	£14 19 6
<b>WHARFEDALE Speakers</b>		
Alredale ..	£69 10 0	£57 14 0
Denton ..	£19 0 0	£14 19 6
Super Linton ..	£22 10 0	£18 10 0
Melton ..	£29 10 0	£22 19 6
Dovedale 3 ..	£39 10 0	£29 19 6
Rosedale ..	£59 10 0	£48 19 6
<b>WHARFEDALE UNIT</b>		
3 Speaker Kit ..	£11 19 6	£9 19 6
4 Speaker Kit ..	£16 0 0	£13 10 0
5 Speaker Kit ..	£23 10 0	£19 19 6

	Rec. Retail Price	Comet Price
<b>CHASSIS SPEAKERS</b>		
GOODMANS Axlette 8 ..	£7 2 1	£5 13 6
GOODMANS Twinaxlette 8 ..	£8 0 7	£6 8 0
GOODMANS Axlim 10 ..	£8 8 0	£6 14 0
GOODMANS Axlim 201 ..	£12 10 0	£9 7 6
GOODMANS Axlim 301 ..	£17 18 0	£13 8 6
GOODMANS Audiom 51 ..	£11 6 0	£8 9 6
GOODMANS Audiom 61 ..	£16 7 0	£12 5 6
GOODMANS Audiom 81 ..	£27 12 0	£20 14 0
GOODMANS Audiom 91 ..	£31 5 0	£23 8 6
GOODMANS Audiom 91/100 ..	£34 17 0	£26 2 9
GOODMANS ARU 180 ..	£3 17 8	£2 18 6
GOODMANS ARU 280 ..	£3 17 8	£2 18 6
GOODMANS ARU 480 ..	£5 8 5	£4 1 3
GOODMANS ARU 172 ..	£3 17 8	£2 18 6
GOODMANS Trebax 100 ..	£7 9 0	£5 11 6
GOODMANS Trebax 5K/20K ..	£8 8 0	£6 6 0
GOODMANS Midax ..	£11 4 0	£8 8 0
GOODMANS Attenuator ..	£3 1 4	£2 6 0
GOODMANS Crossover Networks XO/950/5000 ..	£8 8 7	£6 6 0
GOODMANS Crossover Networks XO/950 ..	£6 7 9	£4 15 9
GOODMANS Crossover Networks XO/5000 ..	£2 6 0	£1 14 6
WHARFEDALE 8 Inch (RS/DD) ..	£4 8 0	£3 13 6
WHARFEDALE Super 8/RS/DD ..	£7 12 0	£6 6 0
WHARFEDALE Super 10/RS/DD ..	£12 14 0	£10 10 0
WHARFEDALE WMT 1 Matching Transformer ..	16 9	13 8

	Rec. Retail Price	Comet Price
<b>HI-FI STEREO TAPE DECKS AND TAPE RECORDERS</b>		
AKAI 150D ..	£130 2 4	£109 0 0
AKAI X-360 ..	£339 0 0	£284 0 0
AKAI X-360D deck ..	£290 0 0	£243 0 0
AKAI 1710 ..	£109 0 0	£85 19 6
AKAI 1800 ..	£158 0 0	£133 0 0
AKAI 1800SD ..	£199 0 0	£167 0 0
AKAI 4000 ..	£124 18 0	£99 19 6
AKAI 4000 D deck ..	£89 19 6	£72 19 6
ALBA P22 Battery/Main ..	£50 5 0	£29 19 6
BUSH TP 50 Cassette Tape Recorder ..	£27 15 8	£24 19 6
FERGUSON 3224 Twin Track 4-track ..	£33 14 0	£24 19 6
FERGUSON 3246 ..	£41 14 0	£32 19 6
FERGUSON 3247 4-track ..	£47 1 0	£37 19 6
FERGUSON 3244 Stereo 4-track ..	£97 18 0	£79 19 6
GRUNDIG C200 Cassette ..	£37 10 0	£29 19 6
GRUNDIG TK 120 Continental ..	£39 5 0	£29 10 0
GRUNDIG TK 124 ..	£44 18 0	£34 19 6
GRUNDIG TK 144 ..	£49 19 6	£39 19 6
GRUNDIG 149 ..	£57 12 8	£47 19 6
MARCONI 4218 Stereo tape Recorder ..	£89 11 2	£69 19 6
PHILIPS 3302 Cassette Tape Recorder ..	£28 7 0	£21 19 6
PHILIPS 4302 Twin Track Auto ..	£35 17 6	£25 19 6
PHILIPS 4307 4-track ..	£49 10 0	£38 19 6
PHILIPS N4404 (4 track stereo) ..	£83 0 0	£69 19 6
PHILIPS N4407 Stereo ..	£105 0 0	£89 19 6
PHILIPS N4308 ..	£60 10 0	£49 19 6
TELETON FXB 510D Stereo TRUVOX PD 102 Stereo Tape Recorder ..	£52 10 0	£43 19 6
	£114 15 3	£79 0 0

# COMET Hi-Fi DISCOUNT WAREHOUSES

Reservoir Road, Clough Road, Hull HU6 7QD. Tel 407906  
also at 68a Armley Rd (Artist St) Leeds LS12 2EF Tel 32055

Customers are welcome to call personally.  
Ample Car Parking facilities

Comet guarantee that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Hi-Fi Catalogue available 5/- Add 9/- for post and packing on all orders under £50 (cartridges 4/-). Orders over £50 add 12/- for Securicor delivery. Make cheques Money Orders payable to "COMET"

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-722 9090  
SAVE POSTAL COSTS! CASH AND CARRY BY CALLERS WELCOME

0A2	5/8	6B8G	2/8	807	8/8	12AX7	4/6	30L17	15/8	AC/CPEN/	DL150	9/8
0B2	6/	6BA6	4/6	6Q7G	6/	12AY7	9/9	30P1	12/	DD	DM70	7/6
0Z4	4/6	6BE6	4/6	6R7	11/	12BA6	6/	30P4M	8/	AC/CPEN/7/6	DM71	7/6
1A3	4/6	6BB6	7/6	6R7G	7/	12BE6	5/9		17/6	AC/CPEN (5)	DW4/3508/6	
1A5	5/	6BJ6	8/6	6SA7GT	7/	12BH7	6/	30P12	13/9	19/6	DW4/3508/6	
1A7GT	7/3	6BQ5	4/9	6SA7M	7/	12E1	17/	30P19	12/	AC/PEN (7)	DY867/ 5/9	
1C5	4/9	6BQ7A	7/	6SG7G	6/8	12F7GT	6/8	30P1L	13/9	19/6	DY802 9/6	
1D5	7/6	6BR7	15/9	6SG7GT	6/	12K5	10/	30P1L3	15/6	AC/T/HILLO	E80F 24/	
1D6	9/6	6BR8	12/6	6R7	3/	12K7GT	8/9	30P14	15/	AC/TF 19/6	E83F 24/	
1FD1	6/8	6BS7	25/	6R7	6/8	12K7GT	8/9	30P15	15/	AC/VP210/6	E8804 12/	
1FD9	4/3	6BW6	14/3	6SK7GT	4/6	12SA7GT		35A3	10/	AL60 15/6	E1801 15/	
1G8	6/	6BW7	13/	6SN7G	4/6		8/	35A5	15/	ARF3 7/	E1822 6/8	
1HG6T	7/	6BZ6	6/	6SQ7G	7/6	128C7	5/	35D5	12/6	ATP4 2/3	E1822 6/8	
1L4	2/6	6C8	3/9	6U4GT	12/	128G7	4/6	35L6GT	8/6	AZ1 8/	E1148 10/6	
1LD5	8/	6C9	14/6	6U7G	10/6	128H7	3/	35W4	4/6	AZ31 9/6	E1148 10/6	
1LN5	8/	6CD86	23/	6V8G	2/8	128J7	4/6	35Z3	10/	AZ41 10/6	E1148 10/6	
1NBGT	7/9	6CH6	7/	6V8GT	8/8	128K7	4/6	35Z4GT	4/9	H36 6/6	E1148 10/6	
1R5	5/6	6CL6	8/6	6X4	4/3	128QGT	7/8	35Z6GT	6/	CL33 18/6	E1148 10/6	
1R4	4/9	6CW4	12/	6X5GT	5/	1407	9/6	50B5	7/	CV6 10/6	E1148 10/6	
1R5	4/3	6D3	7/6	6Y6G	3/	1487	15/	50C5	6/3	CY1C 10/6	E1148 10/6	
1U4	5/9	6D6	8/	6Y7G	12/8	19AQ5	4/9	50C16	6/43	CE31 7/6	E1148 10/6	
2D21	6/6	6P1	12/6	7R6	10/8	19H1	4/	50L6GT	9/	D83 5/	E1148 10/6	
3A4	4/	6P8	12/6	7H7	7/	30D1	13/	72	8/6	D77 2/5	E1148 10/6	
3A5	10/	6P8G	5/	7C6	6/	20D4	20/5	85A2	8/6	DAC32 7/	E1148 10/6	
3B7	5/	6F12	3/3	7F8	12/6	20P2	14/	85A3	8/	DAF91 4/3	E1148 10/6	
3D6	3/9	6F13	3/6	7H7	5/6	20L1	20/	90AG	8/76	DAP96 6/8	E1148 10/6	
3Q4	7/6	6F16	10/	7R7	13/	20P1	17/6	90AV	6/76	DCC90 10/	E1148 10/6	
3Q6GT	6/	6F18	7/6	7V7	5/	20P3	18/	90CG	34/	DD4 10/6	E1148 10/6	
3R4	5/9	6P23	14/3	8R8W6		20P4	18/6	90CV	38/6	DE33 7/6	E1148 10/6	
3V4	8/3	6P24	13/6	8D7	15/8	20P5	20/	90C1	18/	DE91 2/8	E1148 10/6	
5R4GY	10/6	6P25	13/	10C1	25/5	25A6A	5/9	150B19	14/6	DE96 6/8	E1148 10/6	
5U4G	5/6	6P28	14/	10C2	10/	25L6	5/6	180C2	5/9	DF97 10/	E1148 10/6	
5V4G	7/6	6P32	3/	10D1	8/	25V5	8/	30L 20/	DH63 8/	EH76 5/	E1148 10/6	
5Y3GT	5/6	6H6GT	3/	10D2	14/	25Y5G	8/6	302 18/6	DH76 5/	EH77 4/	E1148 10/6	
5Z3	9/	6J8G	3/9	10F1	15/	25Z4G	8/	303 15/	DE77 4/	EH77 4/	E1148 10/6	
5Z4	7/	6J6	3/	10F9	7/	25Z5	8/	305 18/6	DE91 2/8	EH77 4/	E1148 10/6	
630L2	12/	6J7G	4/9	10F18	7/	25Z6G	8/6	306 13/	DH101 25/	EH77 4/	E1148 10/6	
6A8G	6/	6L7GT	6/8	10L11/10/	30L1 6/8	807	11/9	DH107			E1148 10/6	
6A7	3/	6K7G	2/	10P13	13/	30C13	13/	956	2/		E1148 10/6	
6A65	4/	6K7GT	4/6	10P14	20/	30C17	16/	1821	10/6	DK32 17/11	E1148 10/6	
6A65	5/	6K8G	4/	12A6	12/8	30C13	14/	5783	10/	DK40 10/6	E1148 10/6	
6A65	8/	6L1	19/6	12AC6	7/6	30F5	16/	6060	5/6	DK91 5/8	E1148 10/6	
6A15	2/3	6L6GT	7/9	12AD6	7/6	30FL1	13/9	7193	10/6	DK92 9/	E1148 10/6	
6A16	3/3	6L7GT	12/6	12AE6	12/8	30FL2	15/	7475	14/	DK96 7/	E1148 10/6	
6A25	5/6	6L18	6/	12AT6	4/6	30FL12	18/	A1834	20/	DL33 6/	E1148 10/6	
6A26	20/	6L19	27/6	12AT7	3/9	30FL14	18/	A2134	19/6	DL35 4/9	E1148 10/6	
6A76	4/	6LD20	9/6	12AU6	4/9	30L1	8/3	A3042	15/	DL92 5/8	E1148 10/6	
6A76	5/	6N7GT	2/8	12AU7	4/6	30L1	8/3	AC/CPEN	19/6	DL94 5/8	E1148 10/6	
6A76	5/6	6P28	25/	12AV6	5/6	30L16	13/9	DL96	7/		E1148 10/6	

All goods are new and subject to the maker's guarantee. We do not handle manufacturers' seconds, nor rejects, which are often described as "new and tested" but have a limited and unreliable life. Business hours Mon.-Fri. 9.5-30 p.m. Sat. 9-11 p.m. Terms of business: Cash with order only. Post/packing 6d. per item. Orders over £5 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 6d. extra. Complete catalogue of valves, transistors and components with conditions of sale, price 1/-, post free. No enquiries answered unless S.A.E. enclosed for reply.

# YOUR CAREER in RADIO & ELECTRONICS?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.


Please send FREE BROCHURE to

NAME ..... Block

ADDRESS ..... Caps.


Please 1/70

**BRITISH NATIONAL RADIO SCHOOL**

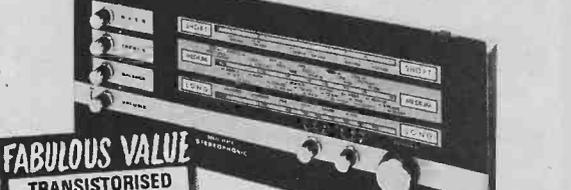

**FABULOUS VALUE**  
**TRANSISTORISED STEREO HI-FI RECORD PLAYER**  
 Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10" x 6" speakers and the latest BSR 4 Speed Stereo/Mono Record Changer.  
 Advanced solid state amplifier only 4 1/2" deep, 14 transistors plus 4 diodes, separate Bass and Treble—10 watts total power. Frequency response 50-15,000 c/s.  
 EASY TO INSTALL  
 NO TECHNICAL KNOWLEDGE REQUIRED  
 Only **28** Gns. + P&P 17/6  
 Credit terms available, first monthly payment £3.6.2 followed by 9 monthly payments of £3.6.2. (Total "Credit Sale" Price £33.1.8).  
 Send £4.3.8 today.

**FANTASTIC BARGAIN OFFER!**  
**"TRANSCONTINENTAL"**  
**FULLY TRANSISTORISED STEREO PHONIC RADIOGRAM CHASSIS**  
 Complete with 2-10" x 6" speakers and the latest BSR Mono/Stereo Record Changer—a complete radiogram at half normal price ONLY  
 10 Watts Total output **38 Gns.** P&P 17/6  
 17 Transistors & 10 diodes  
 EASILY FITTED NO TECHNICAL KNOWLEDGE NECESSARY  
 Credit Terms available. First monthly payment £4.9.10 followed by 9 monthly payments of £4.9.10. (Total "Credit Sale" Price £44.18.4.) Send £5.7.4 today.

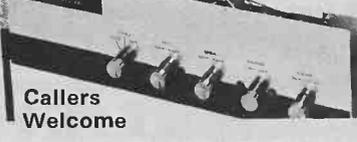

Callers Welcome

**POST THIS COUPON NOW!**  
 PLEASE SEND ME FREE DETAILS OF YOUR RANGE  
 Name .....  
 Address .....  
**LEWIS radio**  
 100 CHASE SIDE, SOUTHGATE, DEP. P10/70  
 LONDON, N.14. TELEPHONE 886 3733/9666



## for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price 15/-



### THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price 15/-



### A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	3/-*
Size 5 (Illustrated)	Savbit	18	3/-*
15	60/40	22	4/-*

\*Recommended Price



### INVALUABLE FOR STRIPPING FLEX. THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER.



easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 8/6



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

## EX-RENTAL TELEVISIONS

### TWO-YEAR GUARANTEE

17" SLIMLINE 405 only  
£11 10 0

19" SLIMLINE 405/625  
39 Gns.


Carriage and Insurance 30/-

FREE ILLUSTRATED LIST OF TELEVISIONS

17"-19"-21"-23"

WIDE RANGE OF MODELS, SIZES AND PRICES

DEMONSTRATIONS DAILY

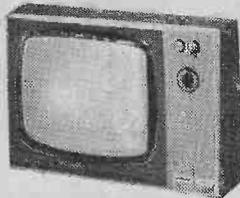

### TWO-YEAR GUARANTEED TUBES 100% REGUNDED

Slim Line Tubes 110° 17" and 19" 109/6, 21" and 23" 129/6.

Normal Tubes 70° and 90° 17" 99/6, 21" 119/6, 14" and other sizes 79/6.

**SPEAKERS** 10/-, 2½" 8Ω, 3½" 25Ω, 4" 10Ω, 3" x 5" 8Ω, 7" x 4" 3Ω, 8" x 3" 3Ω. BRAND NEW. P. & P. 2/-.

**Transistors:** Mullard matched output kit 7/6, OC81D—2 OC81's. P. & P. FREE.

**Transistor Radio Cases:** 4 for £1. Size 9½" x 6½" x 3½". P. & P. 9/6.

**Ferrite Rods** 3/6: 6" and 8" complete with LW/MW Coils. P. & P. FREE.

**STRIP LIGHT TUBES** 3/9 each. 11" (284mm), 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting, etc. 6 for £1. P. & P. free.

**RECORD PLAYER CABINET**  
49/6



Cloth covered. Size 16½" x 14½" x 7½". Takes any modern auto-changer. P. & P. 7/6.

(DUKE & CO. LONDON) LTD.

£21/3 Romford Road, London, E12

Tel. 01-478 6001/2/3

## RADIO SOCIETY GREAT BRITAIN



WIN £250

HQ 215 HAMMARLUND TRANSISTOR COMMUNICATION RECEIVER

AT THE

## INTERNATIONAL RADIO ENGINEERING COMMUNICATIONS EXHIBITION

ROYAL HORTICULTURAL NEW HALL  
GREYCOAT STREET, WESTMINSTER  
LONDON S.W.1

WEDNESDAY TO SATURDAY  
19th to 22nd AUGUST 1970

OPEN 10 a.m. to 9 p.m.

ADMISSION 4/-

DISPLAYS BY

- RADIO AND SPACE RESEARCH
- ROYAL SIGNALS GOLDEN JUBILEE
- ROYAL AIR FORCE
- ROYAL NAVY
- POST AND TELECOMMUNICATIONS
- HOME CONSTRUCTION AND DESIGN COMPETITION AND DISPLAY
- COMPLETE TRANSMITTING STATIONS WORKING THE WORLD
- EDUCATION AND TRAINING INFORMATION

HAND THIS ADVERTISEMENT IN AT THE DOOR FOR FREE ENTRY FOR THE ABOVE RECEIVER



# TRANSMITTER / RECEIVER

for the  
**LF**  
BANDS

F.G. RAYER  
G3OGR

FURTHER  
NOTES

Since the appearance of the LF bands transmitter/receiver in the June/July 1970 issues of "Practical Wireless" it is apparent that the v.f.o. coil unit is no longer available. There has also been interest in 2-band switching for the equipment. This has been employed for some time with excellent results, and results on 80m have been surprisingly good.

## The VFO

Fig. 1 is the circuit of a v.f.o. which can be built in the original v.f.o. box, using easily obtainable components, and giving correct coverage for both 160m and 80m, with the minimum of difficulty.

There are three 1% silver mica capacitors, and the coil is a Denco (Clacton) Ltd. "Yellow" Range 3. It is mounted inside the box, with the threaded rod protruding. The holder for the EF91 was mounted on the box, and thus encloses all the components in Fig.1. The r.f. choke is a miniature cored type (as used in transistor receivers).

It is only necessary to adjust the core of L1 until coverage is from 1.75MHz to 2.0MHz, with a little to spare at the extreme settings of the v.f.o. tuning capacitor.

For 160m, the dial is calibrated from 1.8-2.0MHz. For the 80m band, frequencies from 1.75-1.9MHz are doubled, giving coverage of 3.5MHz to 3.8MHz.

## Buffer and PA

Fig. 2 shows the switching of the buffer amplifier and p.a. circuits. S1 is a single pole 2-way rotary wafer switch, mounted under the chassis, below the v.f.o. tuning control. L2 is for 160m, and is a Denco "Blue" Range 2 coil, with the small coupling winding wholly removed. L3 is for 80m, and is a Denco "Red" Range 2 coil the small winding being removed, and 28 turns taken off the tuned winding.

These coils are under the chassis, with the threaded rods above. The switch S1 is set for 160m, the v.f.o. tuned to about 1.9MHz, and L2 core peaked for best p.a. grid current. With the v.f.o. tuned to about 3.7MHz, and S1 at 80m, L3 is similarly adjusted.


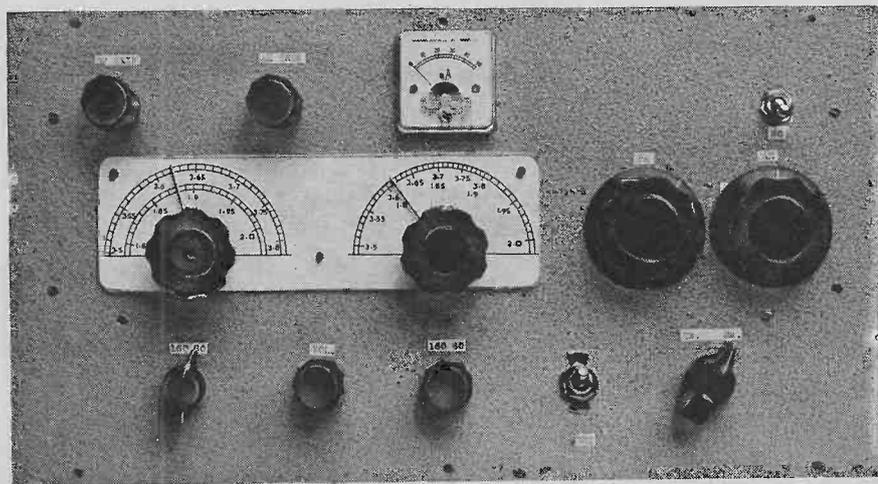


Fig. 1. (above) shows the circuit of the modified v.f.o. stage using readily available components.

The photograph (left) will assist in identifying the additional components required for 2-band operation. The receiver band-switch is below the receiver tuning dial at the left of the panel. The b.a. bandswitch S1 is below the v.f.o. dial, centre. The p.a. bandswitch is located in the top right hand corner of the panel.

—continued on page 390

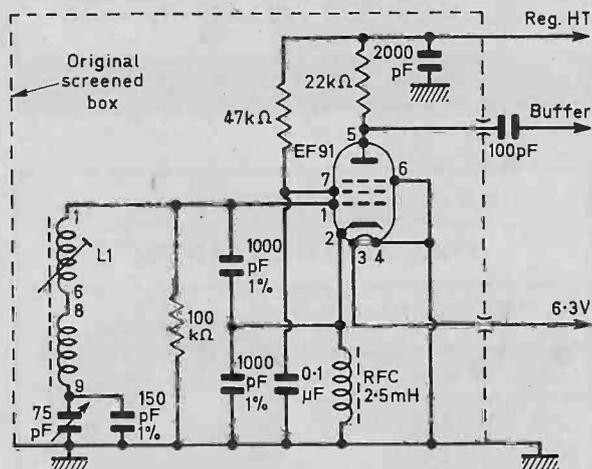

# CODAR CR.70A

## Communications Receiver 540-10 metres




The Codar CR.70A is an excellent general coverage communications receiver for the keen short wave listener. Very reasonably priced at just £22.10.0 the CR.70A is outstanding value for money. In four stable ranges, the receiver covers from 540 metres medium wave, right through the shipping and coastguard frequencies all the short wave and international amateur bands up to and including 10 metres.

The CR.70A has a high 'Q' aerial input stage using exclusive CODAR COIL air space inductor. Double tuned, iron cored I.F. transformers produce high selectivity. Ready to plug into 200-250 volt AC mains, the CR.70A needs only your aerial and a 2-3 ohm loudspeaker. The cabinet measures only 13" x 5½" x 7½" and the control panel is finished in black and white with chrome trim knobs. Fully guaranteed for 12 months!


New model has separate direct output socket for feeding tape recorder, Hi-Fi equipment, etc.
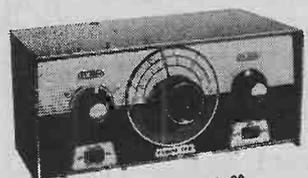
# £22-10-0


- Carriage 13/- extra
- \*Ideal for SWLs
  - \*5 valves (inc. two twin triodes) giving 7 valve line-up
  - \*Excellent on amateur and shipping frequencies
  - \*Calibrated signal strength meter (illuminated)
  - \*Automatic volume control
  - \*Separate B.F. oscillator for morse and S.S.B. signals
  - \*Two speed vernier tuning
  - \*Separate output for recording etc.



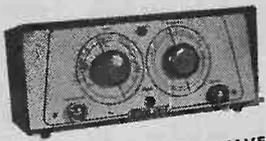**T28 RECEIVER FOR 160 & 80 METRES AMATEUR BANDS**  
 9 transistors, bandspread 1.8-2Mc/s and 3.5-4Mc/s 12 volts, only 8" x 4" x 3½". Ideal portable, mobile or home receiver. Efficient BFO, printed circuits. ONLY £16.10.0, Carr. 5/-.



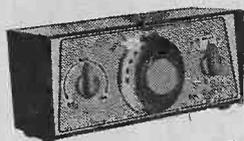**CR45 MAINS T.R.F. SHORT-WAVE RECEIVER**  
 World wide reception. \*Separate electrical output. \*3 slow motion drives. \*Output band-spread. \*3 ohm speaker. \*Valves EC81, 3 watts for 2/3 ohm speaker. \*CODAR-KIT FL34, EZ80. Size 12" x 5½" x 7". CR.45K with 3 coils (10-28, 25-75, 60-176 metres). £10.10.0, Carr. 10/- Extra coils 6/3 each.



**R.F. PRE-SELECTOR MODEL P.R.30**  
 Provides up to 20dB gain plus substantial 1.5-30Mc/s image rejection, improved signal/noise ratio and selectivity. Power requirements 180-250 volts 12mA H.T. 6.3 volts, .3 amp L.T. Size 8½" x 5" x 4". Ready built complete with cables, plugs and instructions. £6.10.0, Carr. 5/- Self-powered P.R.30x £8.10.0, Carr. 5/-.



**MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER**  
 \* Can be built in one evening. \* Complete with valve, one coil 25-75 metres and 4 page instruction manual. Price 55/-, Carr. 3/-. Extra coils 6/3.

**CRC** CODAR RADIO COMPANY  
 UNIT 1, MEADOW ROAD, INDUSTRIAL ESTATE, EAST WORTHING, SUSSEX. WORTHING 37315  
 World-wide Mail Order Service

Please supply (tick as required)

Enclose cheque/M.O./P.O. value of £.....

Ad stamp enclosed for leaflets

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

**POST ORDER FORM TODAY**

# practically wireless

## commentary by HENRY

### The Facer Faced

THE paths of progress are many and devious. Woe betide the inventive gambler who stakes his all on a technical dead-end. Pitying, progress watches the John Logie Bairds picking up the shards of mirror from a dusty floor, and sweeps on to electronic miracles that we unfeeling fellows take in our stride.

The rewards of progress come closer home. Henry is inspired this month by a recent visit to a Mullard Film Show, where Ian Nicholson was in fine form, chiding his audience because they dared to query the reliability of integrated circuits, and were so reactionary as to want plug-in devices.

Plugs and sockets are a technological cul-de-sac, we were given to understand. Despite the arguments of some industrial electronics boys who were slumming in Bristol that night, the signposts decidedly pointed to a 'solder-in, de-solder out' future, with aspirated soldering irons and a ruined 'chip'. 'What does it matter, if you have to break it to take it out?' said Mr. N., 'If you test intelligently, you will know it is faulty *before* you get to that stage. The emphasis must be upon logical diagnosis.'

But, of course, the implication was that things never went wrong


with Mullard chips, and when one chap persisted he was asked in what sphere these plug-in whatsits were to be found. It turned out that he was a ship-board electronics engineer. 'Oh, that explains it,' said Mr. Nicholson, 'I-Cs on the 'igh seas.'

Henry often wishes he had the gift of turning away the awkward question and dissolving his audience in friendly laughter. When things go wrong at one of his lectures, he can be a tongue-tied mug. Only last week there was the most appalling faux pas.

The occasion was a lecture on recording, and a number of musical illustrations had been taped. For the purposes of demonstration these were at different speeds and as is usual with one of Henry's lectures, time had us all by the forelock. A complicated chart had to be drawn on a rickety blackboard, demanding the utmost concentration, both to prevent the latter falling and the former degenerating into illegible graffiti. Henry craftily set the trusty 2000 in motion as he drew . . . and drew. . .

Minutes later, as a man dredges up his consciousness from dream-land, Henry became aware of something vaguely wrong. The horns of the New York Philharmonic had never sounded like that, no, not even in Mahler's day.

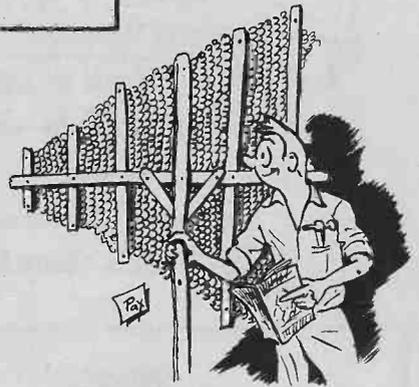I am ashamed to say that, without blinking an eyelid, our villain said: 'Let's go on to the third movement,' and while winding the tape forward, slyly switched the tape recorder to its higher, correct speed. And none of the class protested, although one did telephone the next day to say: 'What was that piece you played just after the interval?'



. . . chicken wire and wood batten.

Such a contretemps can happen to anybody. In the wireless world it happens even to the boffins. A little while ago, the British engineers at the Gloucester factory of Bang & Olufsen were instructed by their parent factory in Denmark to make one or two modifications to a stereo tuner-amplifier to cure 'viups'. Their radio wizard made the changes and noted an improvement in stability, especially at the top of the medium wave band.

A message went off to Denmark: 'Viups cured—what are they please?' And the answer returned from the Danes: 'Isn't it obvious? That's the sound the receiver makes when the fault is present!' And it was.

By the same token, Henry's new FET-IC tuner has a fault best described as Fizzz-crick-Hhhh!

But the trouble there is very simple; largely mechanical. Henry is patiently waiting for Gordon King or one of his colleagues to publish another of those revealing articles in *Practical Wireless* which show how an effective loft FM aerial for stereo multiplex FM reception 80 miles from the transmitter in the shadow of a hill can be constructed from a bale of chicken wire and a few lengths of wood batten.



He can be a tongue-tied mug.

# PROJECT Autumn

Readers of  
*Practical Wireless* are  
 invited to submit articles for  
 publication and to compete  
 for the  
*Practical Wireless*  
 "Designer's Trophy"

## RULES.

- Articles submitted for the competition should conform to the general style of material published in *Practical Wireless* and must describe the operation and construction of a piece of radio, audio or test equipment that has been designed and built by the author.
- Articles should, preferably, be typed using double spacing, leaving wide margins, and on one side only of each sheet. Circuit diagrams and any other drawings should be on separate sheets and numbered to agree with the text. Author's roughs must be clear enough to permit re-drawing. Component lists must also be separate and laid out to the standard PW format.
- Photographs of the equipment are desirable and should be in black and white, sharp and clear. Each photograph should be identified by sticking a piece of paper on the back rather than by writing on the photograph itself.
- Components used in the design must be readily available from retail sources.
- An entry form, properly completed, must accompany each article submitted. There is no limit to the number of articles submitted by any one author.
- Articles must reach the Editor, *Practical Wireless*, Old Fleetway House, Farringdon Street, London, E.C.4, by the first post on Monday, November 2nd 1970 with the envelope and title sheet clearly marked "Project Autumn". A stamped, self-addressed envelope must accompany each entry.
- All entries submitted will be considered by a panel of judges and the Editor's decision on all matters arising will be final. The Editor will require authors of winning entries to submit the equipment to him immediately on request for final assessment by the panel.
- Employees and staff of *Practical Wireless* are not eligible for entry to this competition.
- The winner of the competition will receive and retain outright the *Practical Wireless* "Designer's Trophy 1970". Other prizes will be awarded to the best runners-up. Any article published will be paid for at normal rates.

ENTRY FORM  
 PAGE 354

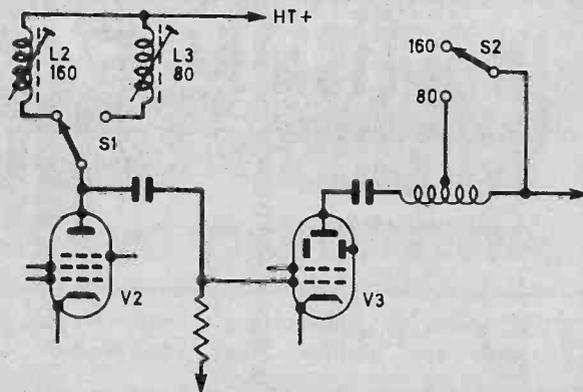


Fig. 2. Switching arrangements for 2-band operation of the b.a. and p.a. stages.

Lock v.f.o. and buffer/doubler cores with 6BA nuts. On 80m S2 shorts out one-half of the tank coil and is a toggle switch, fitted to the panel immediately behind the coil.

## Receiver Coils

Readily-available Denco coils are used for 160m and 80m, in the receiver section, Range 2 coils for 160m, and Range 3 coils for 80m. "Blue" coils are required for the aerial circuit, "Yellow" coils for the mixer grid, and "Red" coils for the oscillator.

The Range 2 "Blue" and "Yellow" coils each have 32 turns removed from the tuned winding.

Count these as they are unwound, and re-solder the wire to the pin. The "Red" coil for this band has 20 turns removed from the tuned winding.

A rotary wafer switch with three wafers, each having 2-pole 2-way sections, is fitted under the chassis below the ganged tuning capacitor. Connections for the coils are as follows:

**Blue.** 1 and 9 to chassis. 8 to aerial, via switch. 6 to r.f. grid, via switch.

**Yellow.** 8 to h.t. positive. 1 to chassis. 9 to r.f. anode via switch; 6 to mixer grid via switch.

**Red.** Range 2: 9 to chassis. 2 to 300pF padder, returned to chassis. 8 to oscillator anode capacitor via switch. 1 to oscillator grid capacitor via switch. Range 3: As Range 2, but no padder and pin 3 wired directly to chassis.

An individual 60pF trimmer is wired across the tuned section of "Yellow" and "Red" coils. Aerial coils are peaked with the panel trimmer. Coverage is of the 160m and 80m bands, with a little to spare, and the cores and trimmers are adjusted in the usual way. ■

## P.W. BINDERS

Preserve your copies of *Practical Wireless*. Don't let them become torn and dirty—buy a hard-cover binder for 15s. 0d. from:

Binding Department,  
 IPC Magazines Limited,  
 Tower House,  
 Southampton Street,  
 London, W.C.2.

Price includes post and packing.



# LIND-AIR AUDIO



## E.M.I. COMBINATION LOUDSPEAKERS

13 1/2" x 8" elliptical with twin tweeters 8 ohm impedance; power handling 10W. Brand new guaranteed. Lind Air

Price **89/6** P. & P. 7/8.

## HI-TONE RECORDING TAPE

BRITISH MADE TOP QUALITY

J1001	3"	L.P. PVC	225ft.	5/6	P & P 1/-
J1002	3"	T.P. Poly	600ft.	10/6	P & P 1/2
J1003	3"	L.P. PVC	900ft.	10/-	P & P 1/8
J1004	5"	D.P. Poly	1200ft.	15/-	P & P 1/8
J1005	5 1/2"	L.P. PVC	1200ft.	12/6	P & P 1/2
J1006	5 1/2"	D.P. Poly	1800ft.	22/6	P & P 2/6
J1007	7"	S.P. PVC	1200ft.	12/6	P & P 2/6
J1008	7"	L.P. PVC	1800ft.	17/6	P & P 2/6
J1009	7"	D.P. Poly	2400ft.	25/-	P & P 2/6
J1010	7"	T.P. Poly	3600ft.	50/-	P & P 2/6
C90	Cassette (Library cased)			8/6	P & P 1/-
C90	Cassette (Library cased)			13/-	P & P 1/-
C120	Cassette (Library cased)			18/-	P & P 1/-



## DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16 ohms. Frequency response 23-13,000 cps. With lead and stereo plug.

**59/6** P. & P. 3/6.

## VHF AIRCRAFT BAND CONVERTER

When placed within lin. of a MW band radio full coverage of VHF Aircraft Band 108-135 Mc/s. can be obtained. All transistor, 9v battery operation. Fully tunable 18 1/2" x 7" section telescopic aerial. Size 4 x 2 1/2 x 1 1/2 in.

**79/6** P. & P. 3/6.



## C1001 MULTI-TESTER



Overload protection. 30,000 opv. AC volts 10, 50, 250, 1,000v. DC volts 5-25, 125, 500, 2500v. D.C. Current 0-50 uA, 0-250 mA. Resistance 0-50K, 1-5 Meg ohm. Decibels -20 to +22dB. Size of meter 4 1/2 x 3 1/2 x 1 in. Complete with leather case 85/- P. & P. 3/6.

## 62D MULTI-TESTER

20,000 p.p.v. DC voltage 5-25-50-250-500-2.5 K (20,000 ohms per volt). AC voltage: 10-50-100-500-1000 volts (10,000 ohms per volt). DC Current: 0-50 uA, 0-2.5 mA, 0-250 mA. Resistance; 0-5K, 0-5 Mg (300 ohm and 30K at centre scale). Capacitance .10f. to .001 mid. .001 uf to 1 mf. Decibels: -20 to +22dB. Size 4 1/2 x 3 1/2 x 1 in. **71/-** P. & P. 3/6.



## LIND-AIR LA.20



A fantastic stereo amplifier made exclusively for Lind-Air and represents considerable advance in solid state stereo amplifiers. Inputs for gram and radio tuner and provision for direct tape recording. Attractive and modern panel with bass, treble balance and volume controls also on/off and stereo/mono switch. Output 5W per channel music power. Frequency response 40-20,000Hz 8-16 ohm speaker matching. Size 16 1/2" x 14" x 4".

LIND-AIR **£24** P. & P. PRICE 10/-.

## SINCLAIR IC-10 INTEGRATED CIRCUIT

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years.

ONLY **59/6** P. & P. 1/8. SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10 from A.C. mains 230/250v. Output 13v. at 0.5 amp. **16/6** P. & P. 2/6.

## NEW! STP.800 8-TRACK STEREO CARTRIDGE HOME PLAYER

TELETON STP. 800 8-TRACK STEREO CARTRIDGE HOME PLAYER A complete solid state unit ready to plug in and play. Hi Fi reproduction at 3 1/2 l.p.a. Player unit incorporates Volume, tone and balance controls and push button track selector. Size 14 1/2" x 10 1/2". Matched speakers size 11" x 5" x 5 1/2" each.



LIND-AIR PRICE **49 GNS.** Carr. 30/-

## WHARFEDALE SPEAKER KITS



Complete with all components for building into suitable cabinets.

Unit 3 Kit **£11.19.6** each  
**£21** per pair  
Unit 4 Kit **£16.0.0** each  
**£28.9s.** per pair  
Unit 5 Kit **£23.10.0** each  
**£39.9s.** per pair  
P. & P. 10/- each 15/- pair

## TELETON SAQ203 TRANSISTOR STEREO AMPLIFIER



Superb quality hi-fi. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble. Attractive oiled walnut cabinet and brushed aluminium front panel. List Price **£38.7.0**

LIND-AIR PRICE

**22 Gns.** P. & P. 10/-

## SAVE ON AKAI!



AKAI 4000 Stereo Tape Recorder List Price **£124.18.0** (as illus.)

OUR PRICE **99 Gns.** Carr 30/-

AKAI 4000D STEREO TAPE DECK List Price **£89.19.1**

OUR PRICE **69 Gns.** Carr 30/-

## SPECIAL LIND-AIR OFFER!




ROTEL 100 AMP STEREO AMPLIFIER. Fully transistorised with all facilities for the home hi-fi system. List price **£45**

LIND-AIR PRICE

**£37.10.0.** Carr. 10/-

## S-DEC BREADBOARD

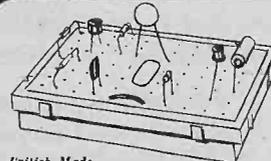

British Made Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DeC with Control Panel, Jigs and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits. 29/6. P. & P. 2/6.

4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories to the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. **£5.17.6.** P. & P. 3/6. T-DeC KIT **£5.17.6.** P. & P. 3/6.

## Carrard HI-FI TURNTABLES



2025 T/C with stereo cartridge ..	£8.19.6
3000 with Sonotone	
9TAHCD stereo cartridge .....	£10.19.6
SP25 Mk II .....	£10.19.6
SL65B .....	£15.19.6
Base and cover for above .....	£5.19.6
AP75 .....	£18.10.0
SL72B .....	£24.19.6
SL75B .....	£28.7.0
SL95B .....	£39.9.0
401 .....	£28.10.0
Base and cover for above .....	£8.19.6
P. & P. Decks 12/6. Base & Cover 10/- Deck/Base/Cover 17/6.	

SPECIAL OFFERS!  
SP25 MkII with base **£14.10.0.** P. & P. 15/-  
SP25 Mk II with Sonotone 9TAHCD cartridge, and base **£15.18.0.** P. & P. 15/-  
Sonotone 9TAHCD cartridge **£2.15.0.** P. & P. 1/6.

18/19,25 & 53 TOTTENHAM CT. ROAD, LONDON W.1.

Telephone: 01-580 2255/4532/7679

Open 9-6 pm. Monday to Saturday. Thursday until 7 pm.

All Mail Orders and correspondence to Dept L5/9, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.

# TECHNICAL TRAINING

*in radio television and electronics*

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

*Many diploma and examination courses available, including expert coaching for:*

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Colour T.V. Servicing
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, incl. professional-type valve volt meter—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



**INTERNATIONAL CORRESPONDENCE SCHOOLS**

Dept. 171, Intertext House, Stewart's Road, London, S.W.8.  
Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam).....

NAME .....  
ADDRESS.....

9/70

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

## BRAND NEW FULLY GUARANTEED TRANSISTORS & DEVICES

1N4001 2/-AAZ13 4/-BPY10 18/6	1N4002 2/3AAZ13 2/6B8X20 4/-	1N4003 2/6AAZ17 2/-B8X21 5/-	1N4004 3/-AC126 6/-B8X76 4/-	1N4005 3/6AC127 6/BBY27 4/-	1N4006 4/-AC127Z 12/BBY27 4/-	1N4007 5/-AC128 5/-BBY29 5/-	1N4009 1/6AC154 3/-BBY50 5/-	1N4148 1/9AC169 4/-BBY63 5/-	2G210 12/6AC163 4/-BBY66 5/-	2G240 49/6AC176 5/-BBY67 5/-	2G301 4/-AC187 5/-BBY68A 4/8	2G302 4/8AC188 6/-BBY68 3/-	2G303 5/-ACY17 6/-BY100 3/8	2G306 7/6ACY18 4/-BY103 4/8	2G308 7/6ACY19 5/-BY114 5/-	2G309 6/-ACY20 4/-BY126 5/-	2G371 4/6ACY21 4/8BYZ10 10/-	2G374 5/6ACY22 3/8BYZ11 9/-	2G382 6/-ACY34 4/-BYZ13 4/-	2G383 5/-ACY36 5/-BYZ15 20/-	2N404 4/6ACY39 9/8BYZ16 12/6	2N896 4/6AOY40 3/-GET102 6/-	2N897 5/-AD140 11/-GET103 4/8	2N898 8/6AD149 12/6MPP10 8/8	2N706 1/8AD161 7/8MPP103 7/-	2N706A 2/6AD162 7/8MPP104 7/8	2N707 12/6AF102 15/-MPP105 8/-	2N708 3/-AF114 6/6OA5 3/-	2N914 4/8AF115 6/-OA7 4/8	2N916 4/6AF116 6/6OA9 3/-	2N918 7/6AF117 5/-OA10 3/-	2N919 4/-AF118 12/6OA47 2/-	2N920 5/-AF124 6/-OA70 2/-	2N922 8/6AF125 5/-OA71 2/-	2N930 7/6AF126 4/-OA73 2/-	2N1131 6/-AF127 4/-OA74 2/-	2N1132 8/-AF129 6/-OA79 2/-	2N1303 4/6AF178 9/8OA81 2/-	2N1304 5/-AF181 8/6OA85 2/6	2N1305 5/-AF186 9/-OA86 4/-	2N1306 5/-AF239 8/-OA90 2/-	2N1307 5/-AFY19 22/6OA91 1/8	2N1308 6/-AFZ11 8/-OA95 1/8	2N1309 5/-AFZ12 10/-OA200 1/8	2N1613 5/-ASY26 6/8OA202 2/-	2N2147 17/8ASY27 7/8OA210 6/-	2N2160 15/-ASY28 6/8OA211 9/8	2N2287 25/-ASY29 6/-OA225 7/8	2N2846 10/6ASY67 9/8OA228 7/8	2N2804 8/6ASZ21 8/-OA229 9/8	2N2905 15/-ATY10 18/6OA230 9/8	2N2925 4/-B3M 19/8OA234 7/8	2N2926 2/6BA110 5/-OA238 9/8	2N3011 7/8BAY31 2/-OC16 10/-	2N3063 5/-BC107 3/-OC19 7/8	2N3064 12/6BC108 2/9OC20 18/8	2N3065 15/-BC109 5/-OC21 9/8	2N3702 3/8BC113 6/-OC23 12/8	2N3703 3/8BC116 8/-OC24 12/8	2N3704 4/-BC118 7/8OC25 7/8	2N3705 3/6BC134 7/8OC26 5/-	2N3707 4/-BC135 6/-OC28 12/8	2N3709 3/6BC136 7/-OC29 12/8	2N3710 3/-BC137 8/-OC30 10/-	2N3711 3/8BC138 8/-OC36 12/8	2N3730 10/-BCY30 5/6OC41 5/-	2N3731 12/6BCY31 8/8OC42 6/-	2N3794 2/6BCY32 10/-OC43 8/-	2N3819 8/-BCY33 5/-OC44 4/-	2N3820 19/8BCY34 6/-OC45 8/8	2N3823 17/6BCY38 7/-OC46 5/8	2N4058 5/6BCY39 8/8OC70 3/-	2N4061 4/-BCY40 10/-OC71 3/-	2N4286 3/-BCY42 5/-OC72 5/-	2N4288 3/-BCY43 5/-OC73 6/-	2N4291 3/-BCZ10 8/-OC74 5/-	2N4290 3/-BCZ11 7/8OC75 8/-	2N4291 3/-BC147 3/8OC76 5/-	2N4292 3/-BC148 2/8OC77 8/-	40361 12/-BC149 4/-OC78 5/-	40362 13/6BF162 6/-OC81 5/-	2S001 10/-BF194 3/8OC81D 4/-	2S002 10/6BF195 3/-OC82 5/-	2S003 9/6BD124 12/6OC83 5/-	2S004 9/6BEN3000 5/-OC84 5/-	2S005 14/-BF115 5/-OC122 10/-	2S012 25/-BF154 8/-OC123 10/-	2S013 20/-BF158 8/-OC139 5/-	2S017 15/-BF159 12/-OC140 7/8	2S034 12/6BF163 8/-OC141 15/-	2S036 25/-BF167 5/-OC169 5/-	2S320 9/-BF173 6/-OC170 5/-	2S321 6/-BF180 7/8OC171 6/-	2S322 7/6BF181 7/8OC200 10/-	2S323 10/-BFY30 6/-OC201 9/8	2S324 12/6BFY38 8/-OC202 12/8	2S512 9/6BFY20 12/8OC203 7/8	2S701 8/6BFY50 5/-OC204 8/-	2S702 11/-BFY61 4/8OC205 12/8	2S731 8/6BFY52 5/-OC206 15/-	2S732 8/6BFY53 4/-OC207 15/-	2S733 9/6BFY54 4/-OC208 15/8	AA178 8/6BLY10 20/-ORP12 12/8	AA172 5/-BLY11 22/6ORP60 8/-
<b>INTEGRATED CIRCUITS</b>		Type I 12+ 25+ 100+ 500+		UL914 9/9 9/- 8/- 7/3 6/6		UL923 12/6 11/9 40/- 10/- 9/3		SL402A 42/6 41/- 40/- 37/6 35/-		MC1303 52/6 48/- 45/- 40/- 35/-		MC1304 55/- 50/- 47/6 42/6 37/6		PA216 52/6 48/- 45/- 40/- 35/-																																																																																										
<b>2N3055 15/-</b>		Mullard 115Watt Silicon Power 25 + 13/- 100 + 11/-		<b>2N3819 7/-</b>		Texas F.E.T. 25 + 6/- 100 + 5/3 500 + 4/9		<b>2N2926 2/-</b>		NPN Planar All Colours 25 + 1/8 100 + 1/6		<b>2N2646 10/6</b>		Motorola Unijunction 25 + 8/9 100 + 7/6 500 + 6/9																																																																																										
<b>AF139 6/-</b>		Siemens V.H.F. 25 + 5/3 100 + 3/9 500 + 3/9		<b>AF186 9/-</b>		Mullard V.H.F. 25 + 8/- 100 + 7/- 500 + 6/-		<b>AD161/AD162 13/- pair</b>		Mullard NPN/PNP 25 + 10/- pr. 100 + 8/6 pr.		<b>BY126 3/6</b>		Mullard 800v 1 amp Plastic 25 + 2/9 100 + 2/6																																																																																										
<b>BY127 4/-</b>		Mullard 1000v 1 amp Plastic 25 + 3/3 100 + 3/-		<b>BYZ13 4/-</b>		Mullard 6a 200v 25 + 3/2 100 + 3/2 500 + 2/10		<b>BT102/500R 2/6</b>		Mullard Thyristor 500 p.i.v. 6.5a 25 + 11/- 100 + 10/3		<b>BC107/8/9 2/9 ea.</b>		I.T.T. Planars 25 + 2/5 100 + 2/- 500 + 1/10																																																																																										
<b>OA200/OA202 1/9</b>		SILICON Diodes 25 + 1/6 100 + 1/3 500 + 1/1		<b>OC42 6/-</b>		Mullard 25 + 5/3 100 + 4/9 500 + 4/3		<b>OC45 3/6</b>		Mullard 25 + 3/- 100 + 2/6 500 + 2/-		<b>OC71 3/-</b>		Mullard 25 + 2/3 100 + 2/- 500 + 1/9																																																																																										
<b>OC42 6/-</b>		Mullard 25 + 5/3 100 + 4/9 500 + 4/3		<b>OC75 5/-</b>		Mullard 25 + 4/3 100 + 3/6 500 + 3/-		<b>OC20 19/6</b>		Mullard 100v 25 + 15/9 100 + 14/6 500 + 13/3		<b>IN4004/5 3/-</b>		400-600v 1 amp 25 + 2/6 100 + 2/- 500 + 1/10																																																																																										
<b>IN4006/7 4/-</b>		800-1000v 1 amp 25 + 3/4 100 + 3/- 500 + 2/6		<b>OC139 5/-</b>		Mullard 25 + 4/- 100 + 3/3 500 + 3/-		<b>OC140 7/6</b>		Mullard 25 + 6/- 100 + 5/- 500 + 4/-		<b>ZENER DIODES</b>		400 MW 5% BZY88 Range All Voltages 3.3v-33v 4/- 25 + 1/6 100 + 2/- 500 + 1/9 1000 + 1/7 any one type																																																																																										

**PLEASE NOTE MINIMUM**  
Quantity Prices 100 + Phone (01) 723 0401 Ex. 4. All listed devices are from stock at time of going to press. Please add 1/6 post packing to your order.

**ORDER SHOULD BE 10/-**  
Send for your free copy of 1970 List No. 36 of over 1000 devices today!  
Discounts 10% on 12+ any one type 15% on 25+ any one type


**HENRY'S RADIO**

Mail Order Dept. Communications, Organ Etc.  
303 EDGWARE ROAD, LONDON W  
Telephone 01-723 1008 9
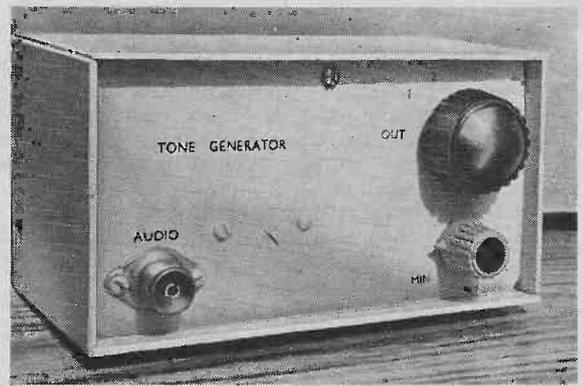
# A TWO-TONE TESTER

A.S. CARPENTER G3TYJ

**T**HERE is nothing unique in the circuitry presented here being rather a practical presentation of a transistorised device very useful in the modern amateur radio station. The device may also be used in other ways as will be mentioned later. It is easily copied and can be constructed in a few hours and will cost approximately 35s. even if every item has to be purchased. As the illustration shows the finalised unit is attractive in appearance and ruggedly built.



to dispense with the transformer and to use capacitors connected in series between input and output. Resistors associated with the feedback capacitors complete the RC network.

## Circuit

The complete circuit of the two-tone oscillator is given in Fig. 1 and will be seen to comprise two separate phase-shift audio oscillators. Resistor values used in each are identical but capacitors differ. The output is fed via a crude attenuator to outlet socket SK1, blocking capacitors C4 and C5 being chosen to offer similar reactance at the differing output frequencies.

Switch S1 offers four alternatives and when at position '1' the unit is 'Off'. At position '2' the output should approximate to 1000Hz whilst at position '3' 2000Hz signals are available. Both tones are available when position '4' is selected. The output amplitudes are equalised by preset potentiometer VR1. If necessary resistor R11 may also be a preset potentiometer but this has not been found necessary.

The purist might consider it an advantage however to make both VR1 and R11 2kΩ preset potentiometers with capacitors C5 and C10 connected to the respective sliders thereby introducing a degree of waveshaping. Dissimilar output amplitudes can also be equalized by making either R4 or R9 partially variable.


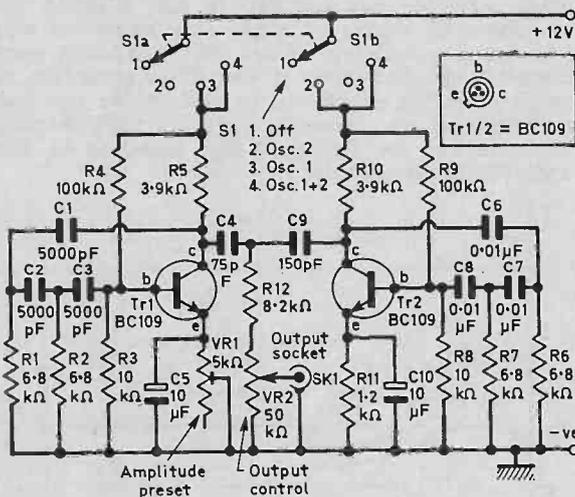


Fig. 1. Circuit of the Two-Tone Tester.

The use of a two-tone audio oscillator unit in conjunction with a suitable oscilloscope is the accepted way of adjusting a single-sideband transmitter and it is convenient if the tones used approximate to 1000 and 2000Hz.

The phase-shift type oscillator employing a ladder network is one of the simplest ways of producing a sine wave in conjunction with a single transistor. The required degree of phase-shift between input and output circuits necessary to ensure reliable oscillations at audio frequency can be obtained by using a transformer as the feedback element.

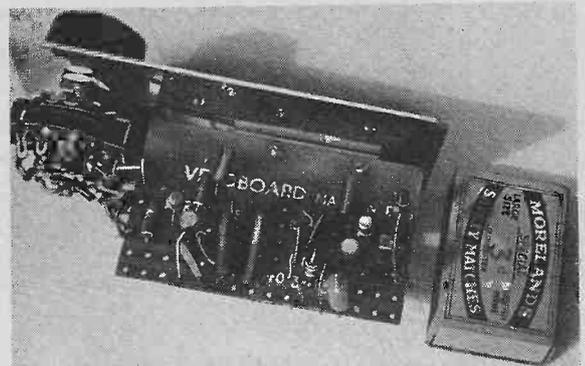Control of the operating frequency is not easily achieved in this way however and it is preferable



A very useful instrument in a very small space!

## Construction

The oscillators can be accommodated on a piece of Veroboard measuring approximately  $3\frac{1}{2} \times 1\frac{1}{8}$  in. with 0.1in. matrix and ten conductor strips are required. Considerable thought has been given to the layout and, due to this, little preparation of the Veroboard is required.

Looking at Fig. 2 it is seen that after cutting a piece of the board to suit it is only necessary to cut the strips in six places, indicated by 'X', along strips D, E, F, G, I and J.


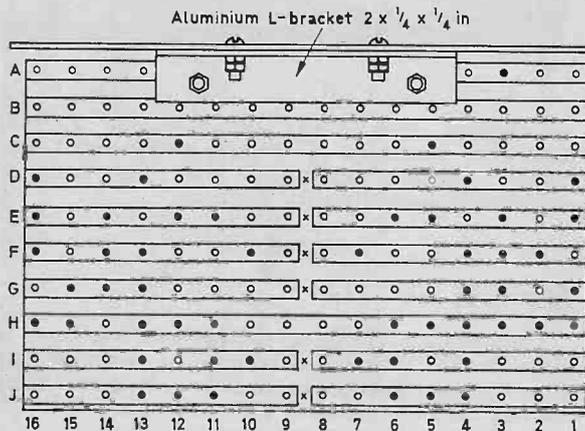


Fig. 2. Circuit board showing breaks required in conductor strips.

The Veroboard is then turned over and with the conductor strips on the underside the various small components are positioned as shown in Fig. 3. It is desirable to use modern high grade miniature resistors and capacitors and to test them prior to soldering them into position.

A piece of 18s.w.g. aluminium,  $5 \times 2\frac{1}{4}$  in., is required for the panel and the Veroboard is fixed to this using a small L-bracket with  $\frac{1}{4}$  in. sides and approximately 2in. in length. The panel is connected to earth by the link wire indicated in Fig. 3. The panel also carries the function switch, attenuator and outlet socket; these components together with essential dimensions and the remainder of the wiring can be seen in Fig. 4.

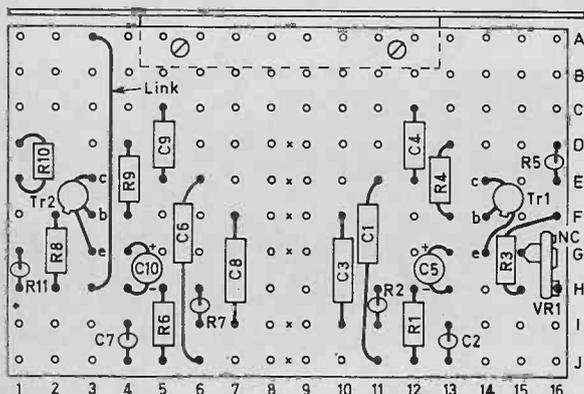

Veroboard  $3\frac{1}{4} \times 1\frac{1}{8}$  in approx.—0.1in matrix

Fig. 3. Component layout on top of circuit board.

## ★ components list

### Resistors:

R1	6.8k $\Omega$	R7	6.8k $\Omega$
R2	6.8k $\Omega$	R8	10k $\Omega$
R3	10k $\Omega$	R9	100k $\Omega$
R4	100k $\Omega$	R10	3.9k $\Omega$
R5	3.9k $\Omega$	R11	1.2k $\Omega$
R6	6.8k $\Omega$	R12	8.2k $\Omega$

All  $\frac{1}{2}$ W 10%

VR1	5k $\Omega$ skeleton pot.
VR2	50k $\Omega$ miniature pot.

### Capacitors:

C1	5000pF ceramic	C6	0.01 $\mu$ F ceramic
C2	5000pF ceramic	C7	0.01 $\mu$ F ceramic
C3	5000pF ceramic	C8	0.01 $\mu$ F ceramic
C4	75pF ceramic	C9	150pF ceramic
C5	10 $\mu$ F 12VW elec.	C10	10 $\mu$ F 12VW elec.

### Semiconductors:

Tr1/2 BC109

### Miscellaneous:

Switch, 2 pole 4 way wafer. Veroboard  $3\frac{1}{2} \times 1\frac{1}{8}$  in., 0.1in. matrix. Panel,  $5 \times 2\frac{1}{4}$  in., 18 s.w.g. aluminium. Output socket. Knobs. Case.

## Testing

The prototype was tested by connecting the output to an oscilloscope which showed a satisfactory waveform when the Tr2 circuit was functioning. The other oscillator was switched in and adjusted for amplitude by means of VR1. This waveform was also found satisfactory. When both oscillators were operating simultaneously it was found necessary to make a small re-adjustment to VR1, which also had an effect on the operating frequency. The outputs were checked for frequency and found to be 950 and 1900Hz respectively.


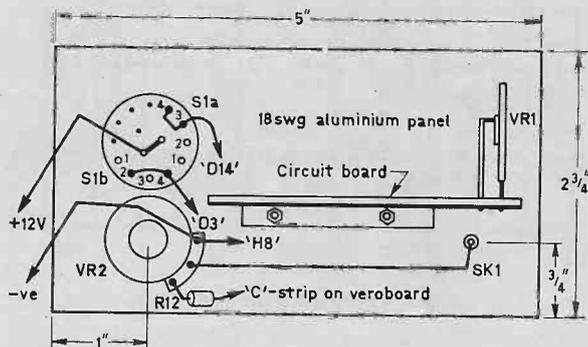


Fig. 4. Mounting of circuit board, function switch, attenuator and output socket on panel.


## Conclusion

Although intended mainly for use when adjusting s.s.b. transmitters other uses for the unit are possible and some will doubtless spring to mind! If preferred only one half of the unit, a single sine-wave oscillator, may be constructed. Recording enthusiasts may find the device useful as a 'Tape Tailer' and if its signal is introduced as the recording nears the end of the tape, on playback the warning note will save much re-threading on to an empty spool! ■

# SINCLAIR IC-10

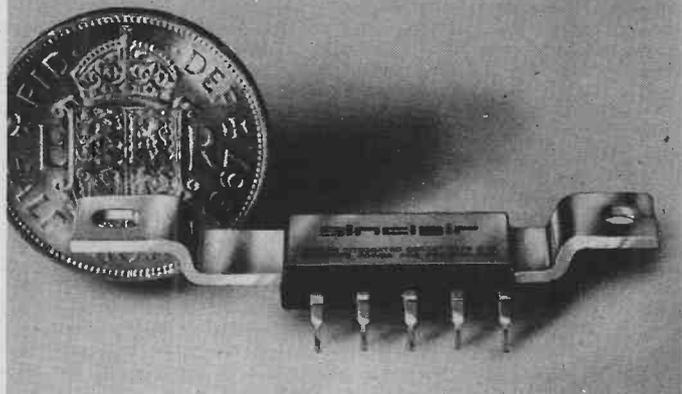
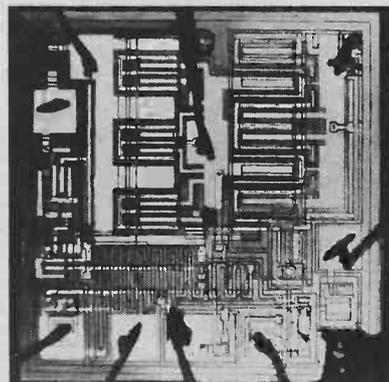
## MONOLITHIC INTEGRATED CIRCUIT HIGH FIDELITY AMPLIFIER AND PRE-AMP



## the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by a hundredth of an inch thick, has an output of 5 watts R.M.S. (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 Zener diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout) etc. The photographic masks required as part of the process of producing monolithic I.C.s are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. This enables us to cover every IC-10 with the Sinclair guarantee of reliability.

### ■ SPECIFICATIONS

Output	10 Watts peak, 5 Watts R.M.S. continuous.
Frequency response	5 Hz to 100 KHz $\pm$ 1dB.
Total harmonic distortion	Less than 1% at full output.
Load impedance	3 to 15 ohms.
Power gain	110dB (100,000,000,000 times) total.
Supply voltage	8 to 18 volts.
Size	1 x 0.4 x 0.2 inches.
Sensitivity	5mV.
Input impedance	Adjustable externally up to 2.5 M ohms.

### ■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

### ■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

SINCLAIR

**IC.10** with *IC.10 manual* **59/6**

POST FREE

# sinclair

**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET ROAD · CAMBRIDGE  
Telephone 0223 52731

# Project 60

## laboratory-standard high fidelity modules

**Sinclair Project 60** comprises a range of modules which connect together simply to form a compact stereo amplifier with really excellent performance. So good, in fact, that only 2 or 3 amplifiers in the world can compare in overall performance. Now with the addition of three new modules to the range, the constructor has choice of assemblies with either 20 or 40 watts output per channel, with or without filter facilities.

The modules are: 1. The Z-30 and Z-50 high gain power amplifiers, each of which is an immensely flexible unit in its own right. 2. The Stereo 60 pre-amplifier and control unit. 3. The Active Filter unit with both high and low audio frequency cut-offs. 4. The PZ-5 and PZ-6 power supplies. A complete system could comprise, for example, two Z-30's, one Stereo-60, and a PZ-5. The PZ-6 is stabilised and should be used where the highest possible continuous sine wave rating is required. An A.F.U. may be added as required. In a normal domestic application, there will be no significant difference between using a PZ-5 or PZ-6 unless loudspeakers of very low efficiency are being used, in which case the PZ-6 will be required. For assemblies using two Z-50's there is the

new PZ-8 stabilised supply unit to ensure maximum performance from these more powerful amplifiers.


All you need to assemble your Project 60 system is a screw-driver and soldering iron. No technical skill or knowledge whatsoever is required and, in the unlikely event of you hitting a problem, our customer service and advice department will put the matter right promptly and willingly. Project 60 modules have been carefully designed to fit into virtually all modern plinth or cabinets and only holes need be drilled into the wood of the plinth to mount the control unit and the A.F.U. Any slight slip here will be covered by the aluminium front panels of these two units.

The Project 60 manual gives all the building and operating instructions you can possibly want, clearly and concisely. Perhaps the greatest beauty of the system is that it is not only flexible now but will remain so in the future as the latest additions to the range show. A stereo F.M. tuner is next to come. These and all other modules we introduce will be compatible with those already available and may be added to your system at any time. And because Sinclair are the largest producers of constructor modules in Europe, Project 60 prices are remarkably low.

SINCLAIR RADIONICS LIMITED

22 NEWMARKET ROAD CAMBRIDGE

Telephone 0223 52731

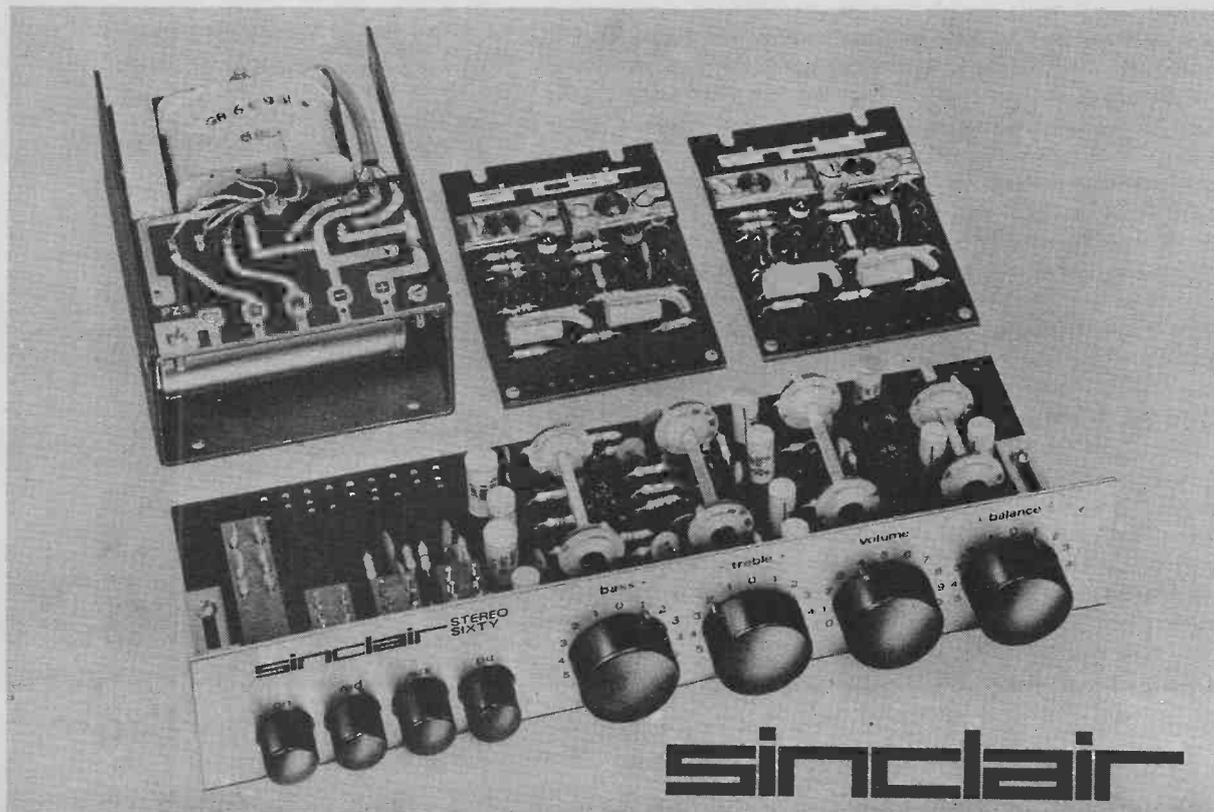

# Z.30

20 WATT R.M.S.  
POWER AMPLIFIER  
(40 WATTS PEAK)

The Z.30 together with the higher powered Z.50 are both of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use the Z.30 or Z.50 power amplifiers in your Project 60 system will depend on personal preference, but they are both the same physical size and may be used with other units in the Project 60 range equally well. The Z.30 is unique in that it may be used with any power source between 8 and 35 volts without need for adjustment and may thus be driven from a car battery for example. For operating from mains, for the Z.30 use PZ.5 power supply unit for most domestic requirements, or PZ.6 if you have very low efficiency loudspeakers. For Z.50, use the PZ.5, PZ.6 or the PZ.8 described below.

## SPECIFICATIONS

### Power Outputs

Z.30 15 watts R.M.S. into 8 ohms, using 35V; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms; 30 watts R.M.S. into 8 ohms, both continuous, using 50V.

Frequency response 30 to 300,000 Hz  $\pm$  1 dB

Distortion 0.02% into 8 ohms

Signal to noise ratio better than 70 dB unweighted

Input sensitivity 250mV into 100 Kohms

For speakers from 3 to 15 ohms impedance


Size 3 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x  $\frac{1}{2}$ "

# Z.50


40 WATT R.M.S.  
POWER AMPLIFIER  
(80 WATT PEAK)
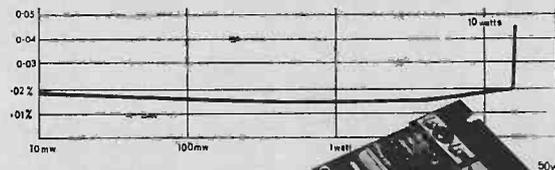
### APPLICATIONS

Hi-fi amplifier; car radio amplifier; record player amplifier fed directly from pick-up; Intercom; electronic music and Instruments; P.A.; laboratory work etc. Full details for these and many other applications are given in the manual supplied with the Z.30.



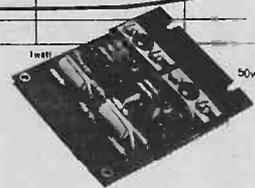Power versus distortion curve of Sinclair Z.30 and Z.50



The Z.50 is completely interchangeable with the Z.30 and can be used in all Z.30 applications

Z.30 Built, tested and guaranteed 89/6 with circuits and instructions Manual  
Z.50 Built, tested and guaranteed 109/6 with circuits and instructions manual

## STEREO 60 Pre-amplifier and tone control unit

The Stereo 60 is a stereo preamplifier and control unit designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout and great attention has been paid to achieving a really high signal-to-noise ratio and excellent tracking between the two channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs. The tone controls are also very carefully designed and tested.

- Input sensitivities—Radio—up to 3mV Mag. p.u.—3mV; correct to R.I.A.A. curve  $\pm$  1dB; 20 to 25,000Hz. Ceramic p.u.—up to 3mV; Aux.—up to 3mV
- Output—250mV
- Signal-to-noise ratio—better than 70 dB.



- Channel matching—within 1dB.
- Tone controls—TREBLE +15 to -15dB. at 10 kHz; BASS +15 to -15dB at 100Hz.
- Power consumption 5mA.
- Front panel—brushed aluminium with black knobs and controls.
- Size 8 $\frac{1}{2}$  x 1 $\frac{1}{2}$  x 4 ins.



Built, tested and guaranteed **£9.19.6**

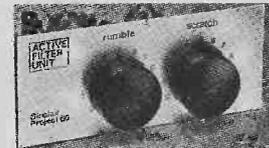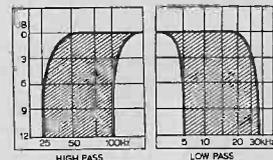
## ACTIVE FILTER UNIT High Pass and Low Pass

For use between Stereo 60 unit and to Z.30s or Z.50s, the Active Filter Unit matches the Stereo 60 in styling and is as easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible by reason of the careful design and generous negative feedback employed. Supply voltage—15 to 35V. Current—3mA. H.F cut-off (-3dB) variable from 28kHz to 5kHz. L.F cut-off (-3dB) variable from 25Hz to 100Hz. Filter slope, both sections 12dB per octave. Distortion at 1kHz (35V supply) 0.02% at rated output



Built, tested and guaranteed **£5.19.6**

## SINCLAIR POWER SUPPLY UNITS

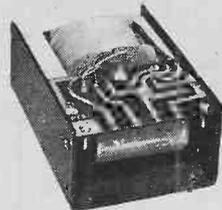

- PZ-5 30 volts un stabilised **£4.19.6**
- PZ-6 35 volts stabilised **£7.19.6**
- PZ-8 45 volts stabilised (less mains transformer) **£5.19.6**
- PZ-8 Mains transformer **£5.19.6**

## GUARANTEE

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for services thereafter. No charge for postage by surface mail. Air-mail charged at cost.

# sinclair

## BUILDING A PROJECT 60 ASSEMBLY



The illustration here shows quite clearly how easily Project 60 can be contained in one of today's slim, modern plinths. Very little space is required to house these Sinclair units, and within the space of the motor plinth, you can install a stereo amplifier of the very highest quality. If, for example you have already put together an assembly as illustrated here, adding the Active Filter Unit would be very easy.

The new Project 60 Manual—50 pages 2/6d.

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET RD., CAMBRIDGE  
Please send

.....  
.....  
.....  
.....  
For which I enclose cash/cheque/  
money order

NAME .....  
ADDRESS .....  
.....  
.....  
PW 970

# R.S.T. VALVE MAIL ORDER CO.

## BLACKWOOD HALL, 16a WELLFIELD ROAD, STREATHAM, S.W.16

Mon.—Sat. 9 a.m.—5.30 p.m.  
Closed Sat. 1.30—2.30 p.m.  
Open Daily to Callers

Tel. 759-0199/5649

1A7	7/9	6BR8	12/6	6K7GT	4/6	10C1	20/2	25L6GT	7/-	150B2	11/8	DK32	7/9	ECH85	11/8	EY86	7/-	PCF80	6/9	FY801	9/6	UCL82	7/6
1D5	7/6	6BS7	25/-	6K8	2/9	10C2	12/6	25Y5	6/-	150C4	9/6	DK91	6/9	ECH42	13/8	EZ35	6/-	PCF82	6/6	EZ82	7/6	UCL83	11/8
1E5	7/9	6BW6	14/8	6K8M	11/6	10F1	14/8	25Z4	6/3	801	9/6	DK92	9/9	ECH81	5/9	EZ40	9/-	PCF84	8/-	R19	7/9	UF94	10/6
1LD5	6/-	6BW7	13/-	6K8G	3/-	10F3	18/-	25Z5	8/-	807	9/6	DK96	7/9	ECH83	8/8	EZ41	9/6	PCF86	9/-	RG5/500	8/0	UF99	7/6
1N5GT	8/-	6C4	5/-	6K8GT	7/-	10F9	10/6	25Z6	8/6	813USA		DL66	25/-	ECL80	7/-	EZ20	5/6	PCF801	9/9	S130	40/-	UL41	12/-
1R5	6/-	6C5	5/-	6C5	15/-	10F18	8/-	30D7	9/3	813	120/-	DL92	6/9	ECL82	7/9	EZ21	5/6	PCF802	9/9	SP4	40/-	UL64	7/-
1S4	5/6	6C6	3/9	6L1	12/6	10L1	8/9	30C1	6/9	813	120/-	DL93	4/-	ECL83	10/8	EZ501	15/-	PCF803	15/-	SP41	6/8	UM80	5/6
1S5	4/6	6C8G	6/-	6L6G	7/9	10LD11	13/6	30C15	15/-	866A	15/-	DL94	6/9	ECL86	9/-	EZ30	10/-	PCF806	13/-	SP61	9/6	UT7	21/-
1T4	4/6	6CD6G	24/-	6L18	6/9	10D13	13/6	30C17	18/-	964	5/8	DL95	7/9	ECLL80030	-	EZ22	10/-	PCF808	15/6	STV280/80		UT7	21/-
2A4	4/6	6CH6	7/6	6Q7G	6/9	11E3	70/-	30C18	15/-	1625	6/6	DL96	7/9	EF9	20/-	EZ23	11/-	PCL82	7/9	U75	95/-	UT8	21/-
3Q4	7/9	6CW4	18/6	6Q7GT	8/6	12A76	4/9	30F5	17/-	4022AR	67/-	DM70	6/9	EF37A	7/-	HM309	20/-	PCL83	10/8	UT25	19/6	UT9	8/8
3Q5	7/9	6D6	3/9	6BA7M	7/-	12A77	6/9	30FL1	18/-	5768	12/-	DY86	6/9	EF39	8/-	KT36	18/-	PCL84	8/6	SU2150	12/6	UY21	9/6
3S4	6/3	6E5	7/8	6BC7	7/-	12A78	5/9	30FL12	19/-	7194	25/-	DL98	6/9	EF41	10/-	KT61	22/6	PCL85	9/3	T41	17/8	UY41	8/6
3V4	6/9	6F1	12/6	6BG7	6/-	12A79	5/9	30FL14	15/6	7475	14/-	EB8CC	12/-	EF50	6/-	KT66	30/-	PCL86	9/8	T104	8/6	UY65	6/6
5K4GY	10/6	6F5G	4/9	6BH7	3/3	12A7X	6/3	30L15	17/-	A81	9/6	EA50	3/8	EF80	4/6	KT81	35/-	PD500	20/-	U70	7/6	VMF4G	17/-
5U4G	5/6	6F6G	5/-	6B7	6/9	12BA6	6/9	30L17	17/-	ATP4	2/3	EABC80	6/6	EF85	7/-	KT81 (7C5)	20/-	PEA44	20/-	U74	7/6	VP4B	25/-
5V4G	8/-	6F8G	5/6	6BK7GT	4/9	12BE6	6/3	30P4	22/6	ATP5	12/-	EAF42	10/-	EF86	6/6	22/6	PEA24	20/-	U79	36/-	VR105/30	6/6	
5Y3GT	6/-	6F11	6/6	6BL7GT	6/9	12CGT	5/9	30P12	16/-	ATP7	8/6	EB41	10/-	EF89	5/8	KT88	33/6	PEA45	20/-	U75	15/6	VR105/30	6/6
6Z4G	7/9	6H13	6/6	6BN7GT	5/6	12E1	20/-	30P19	15/-	AU2	8/9	EB91	3/-	EF91	3/6	KTW61	12/6	PEA46	4/9	U26	15/6	VT25	15/-
630L2	15/-	6H14	12/6	6B7	7/8	12JGT	2/6	30PL1	18/-	AU5	9/9	EB33	8/6	EF92	2/6	KTZ41	6/-	PL36	10/8	U78	4/6	VT31	8/6
6A7	15/-	6F23	16/-	6D4GT	12/-	12J7GT	6/6	30PL13	18/6	AZ1	8/-	EB41	9/8	EF98	15/-	M14	17/8	PL81	8/6	U79	13/9	VU11	8/9
6A8G	12/6	6F24	14/-	6U5G	7/9	12K7GT	7/-	30PL14	15/-	AZ31	10/-	EB90	4/8	EF183	6/6	M16	7/6	PL82	8/6	U251	16/3	VU120	12/6
6AC7	4/9	6F25	15/-	6V6M	12/-	12K8GT	6/9	36A5	12/6	CBL31	18/-	EBF80	7/6	EF184	7/-	M8P4	10/-	PL83	7/6	U301	12/6	VU608	35/-
6AK6	5/6	6F28	14/-	6V6G	4/6	12Q7GT	6/9	35L6	9/-	CCL35	15/-	EBF83	9/-	EL32	3/6	MU14	7/6	PL84	7/6	U403	6/6	W81M	13/6
6AM6	4/6	6F32	2/9	6V9GT	6/6	12S47	8/-	35W4	4/6	CCH33	20/-	EBB89	6/6	EL33	12/6	MX40	12/6	PL500	14/6	U404	7/6	XH15	5/-
6AMS	3/6	6G6	3/6	6X4	4/6	12S7G	2/6	35Z3	10/-	CV450	8/9	EBL1	14/-	EL34	10/8	N78	19/-	PL504	16/-	U801	23/8	XP15	5/-
6A9S	6/3	6H6	3/-	6X5G	4/6	12S7H	3/-	35Z4GT	8/6	CY30	12/6	EBL11	12/6	EL38	8/6	N85	19/-	PL508	29/-	U802	23/8	YAC90	6/6
6A87G	15/-	6J5M	9/-	6X5GT	6/9	12S7J	3/9	35Z5	8/6	CY31	8/6	EBL12	27/6	EL41	11/-	NGT1	3/6	PL509	29/-	U803	23/8	YAC90	6/6
6AT6	4/9	6J6G	4/9	7B6	11/6	12S7K	4/9	37	6/6	DAC32	7/9	EC90	5/-	EL42	11/6	OA2	6/-	PL502	12/6	UBC41	9/6	3EG1	65/-
6AU6	5/6	6J6GT	5/6	7B7	7/6	12S7L	5/-	42	8/-	DAP91	4/6	EC881	6/6	EL44	4/9	OC3	5/-	PX4	24/-	UBC41	9/6	3FP7	29/-
6B4G	20/-	6J6	3/6	7C5	22/6	14H7	9/6	50B5	6/6	DAP96	7/6	EC882	5/9	EL95	7/-	OZ4	4/6	PX25	27/6	UBF80	7/6	5CP1	55/-
6B5G	2/-	6J7M	8/6	7C5	15/-	19A5	5/9	50C3	6/3	DAC90	20/-	EC883	6/6	ELL80	20/-	PC86	11/6	PY33	10/8	UBF89	7/6	CV1626	65/-
6BA6	5/6	6J7G	6/-	7D5	8/6	20D1	10/-	60CUD6	31/-	DAP93	8/6	EC884	6/6	EM34	16/-	PC86	11/6	PY81	5/9	UC84	8/6	ACR151100	8/6
6BE6	5/6	6J7GT	7/6	7H7	6/6	20F2	14/-	50L6GT	8/-	DF70	9/-	EC885	5/-	EM80	7/6	PC87	8/9	PY82	5/8	UC85	7/6	VC897	45/-
6BH6	9/-	6K6GT	8/-	7R7	13/-	20L1	20/-	75	9/6	DF91	4/9	EC887	7/6	EM81	12/6	PC84	6/6	PY83	7/6	UCF80	6/6	VCR1517B	46/-
6B7G	9/-	6K7	1/9	7H7	45/-	20P4	20/-	78	5/-	DF92	3/6	EC888	6/6	EM84	7/6	PC89	10/6	PY800	18/6	UC842	10/6		
6BQ7A	7/6	6K7M	6/6	7Y4	8/6	20P5	20/-	80	7/8	DF96	7/8	ECF80	6/6	ESU150	20/-	PCC189	10/6	PY800	9/6	UCH81	7/6	VCR1517C	46/-
6BR7	17/-	6K7G	2/-	6BW6	7/-	28A6	5/9	80A2	7/8	DH77	4/8	ECH21	12/6	EY51	7/6								

Manufacturers and Export Inquiries Welcome

OBsolete TYPES A SPECIALITY

QUOTATIONS FOR ANY VALVE NOT LISTED

Express postage 9d. per valve.

Ordinary postage 6d. per valve. C.W.O. No C.O.D.

Tube postage 10/- each


Special Express Mail Order Service

### TRANSISTORS

2G414	6/0	AC128	4/6	AF118	12/-	OC36	8/6	OC77	8/-	OC122	12/6
2N1305	5/-	AC176	6/2	BC108	3/6	OA200	2/-	OC88	3/-	OC128	4/4
2N2147	16/6	ACY18	4/-	BC109	3/6	OA202	2/-	OC99	3/6	OC139	7/6
2N2368A	5/-	ACY27	3/-	BFY51	6/-	OA242	4/6	OC70	3/6	OC141	12/3
2N2696	6/3	ACY38	4/-	BFY90	12/6	OAZ246	4/6	OC71	3/6	OC149	5/6
2N2926	3/-	ACY39	15/6	BY100	4/6	OC18	15/6	OC72	4/6	OC151	7/6
2N3705	4/-	AD149	12/-	EF114	4/-	OC19	8/6	OC73	4/6	OC152	7/6
2N3819	8/-	AD161	7/6	GJ7M	6/6	OC20	20/-	OC74	4/6	OC153	6/6
AC107	5/6	AD162	7/6	NKT274	4/9	OC28	12/6	OC75	4/6	OC154	8/6
AC127	5/6	AF117	4/6	NKT713	7/6	OC35	6/3	OC76	3/6	OC155	6/6

SEND S.A.E. FOR LIST OF 3,000 TYPES
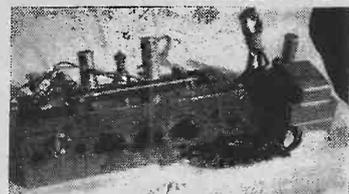
### AMPLIFIER FOR MAGNAVOX TAPE DECKS — 4 TRACK CAN BE USED FOR 2-TRACK



Chassis 12 1/2 x 5 1/2 x 4 1/2 in. high. Plastic front panel finished in Black and Silver. 200-250 A.C. Record/Playback amp. switch. Off/On-Tone. Vol./Me.; Vol./Gram; Mic. Input; Gram. Input; Valves 6BR7, 12AX7, 6EM84, EL84 and E290. Separate Output Transformer (Already wired to amp). PRICE £12 (10/- P. & P.). 3-ohm speaker 7" x 4" 16/- extra.

### STEREO AMPLIFIER type HV — 2 x 3 Watts

Fully built. On off sep. vol. and tone each channel 12 x 4 1/2 x 6 in. high. E280. 2 x ECL86; for 3 ohm speakers, double wound main trans: fixing flanges and base plate, suitable for crystal cart, tuner etc. £8.10 (8/- p. & p.). 200-250V. A.C. Superior version — separate base, treble & vol. each channel with mono/stereo switch 15/- extra.



### STEREO AMPLIFIER type RC — 2 x 3 Watts for 200-250V. A.C.

Fully built. 2 x UCL82, metal rect: ganged vol. and tone cont: on-off balance. 11 x 3 1/2 x 4 in. high. Double wound mains trans, with supporting brackets. For 3-ohm speakers. £8 (8/- p. & p.)



### MONO GRAM CHASSIS 3 WATT

3 Wave band long-med-short. Gram., 200-250V A.C. Ferrite aerial. Chassis 13 x 7 x 5 in. Dial 13 x 4 in. Double wound mains transformer 5 valve ECH81, EF89, ECH81, EL84, E280. Price £10.12.8. (7/6 p. & p.) Output trans. for 3-ohm speaker

NEW TAPE AMPLIFIER for 4 track B.S.R. Deck TD2. Mains and output Trans. 10" x 8" x 4" overall. Rect; ECC83, EL84. Mike and Gram Inputs. £7.5.0. (10/- p. & p.) For 3-ohm speaker. (For 200-250V. A.C.)


## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240 CLOSED WEDNESDAY. S.A.E. for enquiries please.
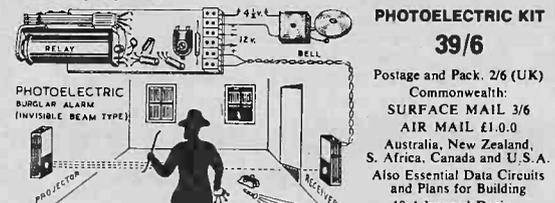
## PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



**INVISIBLE BEAM OPTICAL KIT**  
Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.  
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 8/-.

**LONG RANGE INVISIBLE BEAM OPTICAL KIT**  
CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price 29/6. Postage and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/6; Air Mail 10/-.

**JUNIOR PHOTOELECTRIC KIT**  
Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc. for the Experimenter.  
CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs".  
Price 19/6. Postage and Pack. 1/6 (U.K.). Commonwealth 2/-; Air Mail 4/-.

**JUNIOR OPTICAL KIT**  
CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.  
Price 10/6. Post and Pack. 1/6 (U.K.). Commonwealth: Surface Mail 2/-; Air Mail 4/-.

## YORK ELECTRICS

335 BATTERSEA PARK RD., LONDON S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

## NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. Five section 22in. chrome plated Telescopic aerial for Short Waves can be angled and rotated for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. Speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Total Building Costs £6.19.6 Parts Price List and Easy Build Plans 5/- (FREE with parts).


**£6.19.6**

P. & P. 7/6


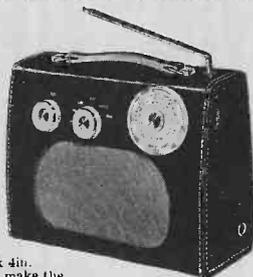
## roamer seven mk IV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts). Personal Earpiece with switched socket for private listening, 5/- extra.



Total building costs


**£5.19.6**

P. & P. 7/6
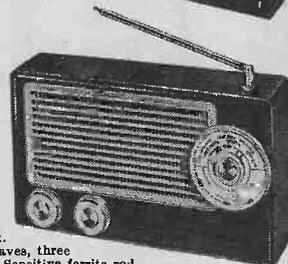
## NEW! trans eight

SIX WAVEBAND  
PORTABLE WITH  
3in. SPEAKER

Attractive case in black with red grilles and cream knobs and dial with polished brass inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts). Earpiece with switched socket for private listening 5/- extra.




Total building costs **89/6**

P. & P. 5/6
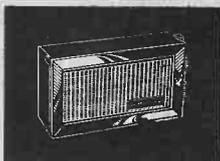
## pocket five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND PORTABLE  
WITH SPEAKER

Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

**44/6** P. & P. 3/6

## transona five

MEDIUM WAVE, LONG WAVE  
AND TRAWLER BAND  
PORTABLE  
WITH SPEAKER

Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs

**47/6** P. & P. 3/9

## roamer six

SIX WAVEBAND PORTABLE  
WITH 3in. SPEAKER

Attractive case with gilt fittings. Size 7 1/2 x 5 1/2 x 1 1/2in. Tunable on Medium and Long waves, two short waves, Trawler Band Plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short waves. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors etc. (Carrying strap 1/6 extra). Easy build plans and parts price list 2/- (FREE with parts). (Note: When present stocks of these cases are exhausted a new case similar to "Transeight" will be supplied).



Total building costs

**79/6** P. & P. 4/6

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for .....

Name .....

Address .....

PW.21

★ Callers side entrance Stylo Shoe Shop

★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

# ELECTROVALUE

EVERYTHING BRAND NEW & TO SPECIFICATION • LARGE STOCKS

## BARGAINS IN NEW SEMICONDUCTORS all power types supplied with free insulating sets

1N914	1/3	2N3706	3/3	40512	45/6	BC147	3/6	BFY51	4/3
1N3754	4/-	2N3707	4/-	40602	9/6	BC148	3/3	BSX20	3/9
1N4148	1/9	2N3708	3/-	AC107	14/6	BC149	3/6	BY164	10/-
1N5054	4/-	2N3709	3/-	AC126	6/6	BC153	10/-	BY238	3/6
18940	1/-	2N3710	3/6	AC127	6/6	BC154	11/-	C106B1	14/6
2N366	6/6	2N3711	3/11	AC128	6/-	BC157	3/9	MC140	5/-
2N687	6/6	2N3731	24/-	AC176	11/-	BC158	3/6	MJ480	21/-
2N706	2/9	2N3794	3/3	ACY23	3/9	BC159	3/9	MJ481	27/-
2N1302	4/-	2N3819	8/6	ACY40	4/-	BC187	2/6	MJ491	30/-
2N1303	4/-	2N3820	15/3	ACY41	5/-	BC168	2/3	MPP102	7/6
2N1304	4/6	2N3904	7/6	AD142	14/3	BC189	2/6	NKT403	16/6
2N1305	4/6	2N3906	7/6	AD149	17/6	BC177	6/3	NKT405	15/-
2N1306	6/9	2N4056	5/3	AD161/AD162	17/6	BC178	5/6	OA47	1/9
2N1307	6/9	2N4059	4/-	(matched) 16/-	pr	BC179	6/-	OA90	1/3
2N1308	8/9	2N4060	4/3	AF114	7/-	BC182L	4/3	OA91	1/3
2N1309	8/9	2N4061	4/3	AF115	7/-	BC183L	2/3	OA95	1/3
2N1613	6/6	2N4062	4/3	AF116	6/6	BC184L	2/6	OA99	3/-
2N1711	7/-	2N4284	3/3	AF117	6/6	BC186	8/6	OA920	1/11
2N2147	18/9	2N4286	3/3	AF124	7/6	BC212L	5/-	OA202	2/-
2N2218	9/3	2N4289	3/3	AF127	7/-	BC213L	5/-	OCT1	5/6
2N2270	12/9	2N4291	3/3	AF139	9/6	BC214L	5/3	TIP31A	17/6
2N2484	13/6	2N4292	3/3	AF180	18/6	BC270	5/6	TIP32A	23/9
2N2646	10/9	2N4410	4/9	AF239	9/9	BD121	18/-	TS43	10/6
2N2904	11/-	2N5062	12/3	ASV26	6/6	BD123	24/3	ZTX300	3/6
2N2924	4/-	2N5163	5/-	ASV27	8/3	BD124	18/-	ZTX301	3/6
2N2925	4/6	2N5192	25/-	ASV28	6/6	BF167	8/6	ZTX302	4/6
2N2926	2/3	2N5195	25/3	B5041	15/-	BF178	10/6	ZTX303	4/6
2N3053	5/6	2N5457	9/9	BA102	9/-	BF180	12/-	ZTX304	6/9
2N3054	14/3	2N5458	9/9	BA156	4/-	BF194	7/-	ZTX500	5/-
2N3055	16/-	2N5459	9/9	BA130	4/6	BF195	7/6	ZTX501	5/-
2N3325	10/9	40230	14/3	BA145	5/6	BFX29	10/9	ZTX502	6/-
2N3603	11/6	40361	12/6	BC107	2/9	BFX34	7/3	ZTX503	5/-
2N3702	3/6	40362	18/-	BC108	2/6	BFX45	8/3	ZTX504	12/-
2N3703	3/3	40496	16/3	BC109	2/6	BFX47	8/3	ZTX505	6/9
2N3704	3/9	40498	14/6	BC125	12/-	BFX88	6/9	ZTX531	6/9
2N3705	3/5	40430	37/-	BC126	12/-	BFY52	4/2		

## PEAK SOUND PRODUCTS

### ENGLEFIELD CABINET KITS

Build it 12 + 12 or 25 + 25



Stereo amplifier in modular kit form 12 watts per channel £38/9/-, 25 watts £58/15/- Cabinet kit only 28. These prices nett.  
As recently reviewed in Hi Fi Sound.

### BAXANDALL SPEAKER SYSTEM

Designed by Peter Baxandall. Superb reproduction for its size. Includes 10 watts with case. Uses ELAC 15 Ω 59RM109 speaker Unit. Kit £13/12/- nett; built £19/8/6 nett.



### STEREO AMPLIFIER S.A. 10-10.

Developed from the very successful S.A.8-S amplifier giving first class stereo amplification featuring separate volume controls for each channel, bass and treble controls. 10 watts per channel into 8 Ω. Kit £19/7/6 nett; built £24/16/8 nett. Suitable 8 Ω wide range sockets available £13/16/- each nett.



### MAINLINE AMPLIFIER KITS

RCA/SGS designed main amplifier kits. Input sensitivity 500-700mV for full output into 8 Ω. Power Kit price Suitable unreg. power supply including components kit

12W	188/- nett	92/-
15W	190/- nett	N/A
40W	210/- nett	115/1
70W	252/- nett	138/10

### 30 WATT BAILEY AMP. PARTS

Special summer reduction (to Sept. 30th 1970 only) Sensitivity 1.2V for full output into 8 Ω. Transistors for one channel 27/5/6 list, £6 only nett. Transistors for two channels £14/11/- list £11 only nett. Capacitors and resistors (metal oxide) 30/- per channel nett. Complete unregulated power supply kit 87/6 nett.

### ZENER DIODES

5% full range E24 values: 400mV; 2.7V to 30V 4/6 each 1W; 6.8V to 82V 9/- each 1.5W; 4.7V to 75V 12/- each Clip to increase 1.5W rating to 3 watts (type 266F) 8d.

### CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level. Single gang linear 220 Ω to 2.2M Ω 2/6  
Single gang log 4.7K Ω to 2.2M Ω 2/6  
Dual gang linear 4.7K Ω to 2.2M Ω 8/6  
Dual gang log 4.7K Ω to 2.2M Ω 8/6  
Log/antilog 10K, 47K, 1M Ω only 8/8  
Any type with ½ A.D.F. mains switch, extra 2/3  
Please note: only decades of 10, 22 and 47 are available within ranges quoted.

### CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω, 470 Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M Ω Vertical or horizontal mounting 1/- each.

### COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on net items).

### POSTAGE AND PACKING

Free on orders over £2. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω-220K Ω	E12	18	16	15
C	1/8W	5%	4.7 Ω-330K Ω	E24	2-5	2	1-75
C	1/4W	10%	4.7 Ω-10M Ω	E12	2-5	2	1-75
C	1/2W	5%	4.7 Ω-10M Ω	E24	3	5	2-25
C	1W	10%	4.7 Ω-10M Ω	E12	6	6	4-5
MO	1/2W	2%	10 Ω-1M Ω	E24	9	8	7
WW	1W	10% ± 1/20 Ω	0.22 Ω-3.9 Ω	E12		15d all quantities	
WW	3W	5%	12 Ω-10K Ω	E12		15d all quantities	
WW	7W	5%	12 Ω-10K Ω	E12		18d all quantities	

Codes: C = carbon film high stability low noise. MO = metal oxide Electroil TR5 ultra low noise WW = wire wound Plessey.

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

## INTEGRATED CIRCUIT AMPLIFIERS

SINCLAIR IC10 complete with instruction book giving amplifier circuit details and range of applications. 50/6 nett. PLESSEY SL408A Now only 42/6 nett 3W into 7.5 Ω for 18V supply. Application data sent with two more.

## WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W 4/9 each  
SLIDER SWITCHES D.P.D.T. 3/- each

## NEON INDICATOR LAMPS

all 200/250V. Square bezel, red only 3/9  
Round chrome bezel, amber, clear 4/9 each  
Toggle switches, 250V a.c. 1.5A.  
chrome dolly and chrome milled nut S.P.S.T. 3/9; S.P.D.T. 4/6; D.P.D.T. 5/9; S.F.D.T. centre off 5/-.

S-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC only 30/- Compact T-DeC, increased capacity, may be temperature-cycled. T-DeC only 50/- post free. Full range stocked.

## MULLARD polyester C280 series

250V 20%: 0-01; 0-022; 0-033, 0-047 8d ea. 0-068; 0-1 9d ea., 0-15 11d., 0-22 1/-, 10%: 0.33 1/5, 0-47 1/8, 0-68 2/3, 1 μF 2/9, 1.5 μF 4/2, 2.2 μF 4/9.

## MULLARD SUB-MIN ELECTROLYTIC

C428 range axial lead 1/3 each  
Values (μF/V): 0-64/64; 1/40; 1-6/25; 2-5/16; 2-5/64; 4/10; 4/40; 5/64; 6-4/80; 6-4/25; 8/4; 8/40; 10/2-5; 10/16; 10/64; 12-5/25; 16/40; 20/16; 20/64; 25/6-4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2-5; 50/8-4; 50/25; 50/40; 64/4; 64/10; 80/2-5; 80/16; 80/25; 100/5-4; 125/4; 125/10; 125/16; 150/2-5; 200/6-4; 200/10; 250/4; 320/2-5; 320/6-4; 400/4; 500/2-5.

## LARGE CAPACITORS

High ripple current types: 1000/25 5/6; 1000/50 8/2; 1000/100 16/3; 2000/25 7/4; 2000/50 11/4; 2000/50 11/4; 2000/100 28/8; 2500/64 15/8; 2500/70 19/6; 5000/25 12/6; 6000/50 21/11; 5000/100 58/3; 10000/15 17/-; 10000/25 24/8; 10000/50 44/-; 10000/70 61/-.

## MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 2/-; 100/25 2/-; 100/50 2/6; 250/25 2/6; 330/25 2/6; 250/50 3/9; 500/25 3/9; 500/50 4/6; 1000/25 4/-; 1000/50 6/-; 2000/25 6/-.

## SMALL ELECTROLYTICS

Axial leads: 4.7/10; 4.7/25; 5/50 1/- ea. 10/10; 10/25; 10/50; 33/10; 50/10 1/- ea. 22/25; 25/50; 47/25; 100/10; 220/10 1/3 ea.

# ELECTROVALUE

(Dept. PW.8) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY  
Hours: 9-5.30: Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3) Telex 264475

## TRANSISTORS etc.

AC107	3/-	OA5	1/8	OC26	7/6	OC81	2/6
AC126	2/3	OA9	1/8	OC28	8/6	OC81D	2/3
AF115	3/-	OA10	1/8	OC35	9/-	OC82D	2/6
AF116	4/-	OA47	1/8	OC44	2/9	OC140	5/-
*AF117	4/-	OA81	1/8	OC45	2/3	OC169	3/6
BFY18	4/6	OA85	1/6	OC70	2/3	*OC170	4/-
BFY51	4/-	OC23	6/6	OC71	2/3	OC171	2/3
GET13	2/6	OC25	6/-	OC72	2/3	OC202	4/6
				OC73	2/3	T K22C	1/8
				OC75	2/3	General purpose	1/6

\* WITH 4 LEADS

### SILICON DIODE RECTIFIERS -BY 100-2/10 EACH

**SIX AMP. SERIES:** BYZ13 300 PIV 4/- BYZ12 600 PIV 5/-  
BYZ11 900 PIV 6/- BYZ10 1200 PIV 7/-  
**THYRISTORS:** 5 AMP SERIES 100 PIV 7/6 300 PIV 9/6  
300 PIV 10/6 400 PIV 12/- 800 PIV 25/-  
10 AMP SERIES, 50 PIV 10/- 100 PIV 12/-

(POSTAGE PACKING & INS. ON ALL ABOVE, 1/- UP TO 11, 12 & OVER PAID)  
MULLARD STACK F. W. BRIDGE 12A 100 PIV 39/6 (3/-)

### ELECTROLYTIC CONDENSERS

Full details of many types from 6d each in our list (see below).  
**SUB-MIN TRANSFORMER:** Output (3 Ω for OC72) 2/9 (driver, 3/- (up to 6 either 1/-).  
**MULTIPLIER:** 20,000 Ω/V D.C., 10,000 Ω/V A.C. 0-5/25/50/100/1K coils D.C.  
10-150/100/50/25/10/5 A.C. 0-1/20/40/80/160/320/640/1280/2560/5120 A.C. 0-6K Ω/R meg Ω.  
● 10μF-0.01mf/1mf. ● 20 to x221R. ● Complete with test leads and instructions.  
● Over-load protected 1970 model with every refinement. £4.10.0 (2/6). **JUNIOR MODEL**  
at 47/6 (2/6). 1000 Ω/V described in free list. Spec. subject to slight variation.  
**SOLDERING IRON.** Slim Mod. British High speed. 4 1/2 in. all parts replaceable, fully  
guaranteed for professional, radio and general D.I.Y. use. 19/6 (1/6).

**DIAMOND STYLUS** Replacements for BSR T02LP, T03/8 and T08LP/STEREO;  
and GCSLP; ACOS GP45/57, all at 7/6 each (1/-). ACOS GP73 and GP91: BSR ST4 (ST3,  
ST5), ST8 (ST9); SONOTONE ST4, ST4A and ST4HC; PHILIPS A(3306, 3060, 3063,  
3066, 3301, 3302, 3304), all at 15/- (1/-). All are of the very highest quality.

**DOUBLE DIAMOND Types:** If you don't use the 78 side - this is the best buy - now  
available only in ST4 (ST3, ST3A), ST5 (ST9), ST4A, ST4HC. 3306, GP91 (for GP92,  
93 and 94 Cartridges and GP91SC for GP91SC cartridges, 30/- each (1/-).  
**SAPPHIRE** all types, 7/6 each (1/-). Also ACOS GP37 at 3/3 each (1/-). ACOS GP91  
at 7/6 (1/-). No other types at present, and no 78 rpm available in any type.

**PICK-UP CARTRIDGES** All fitted Styl and Standard fittings, Mono GP67/2,  
15/-, ● Stereo compatible - Mono which also plays  
Stereo records unaurally with min. wear, GP91/SC, 21/-, ● latest Stereo GP93, 25/6.  
● Ceramic Stereo, top quality for expensive outfits, GP94, 38/6. ● Monotone stereo, ST4HC  
diamond fitted cartridge 55/- (all at 1/-). More diamond types in list. Goldring cartridges  
in stock.

**EP3 EXTINGUISHER (A.C.)** 17/6 (1/6). **TWO STATION TRANS. INTER-COM.** Excellent baby  
alarm. Instant, easy fitting with leads, plugs and battery. All you require £2/6 (5/-).  
**TRANSISTORISED AMPLIFIER,** 3 watt, 9V operation, 45/6 (1/6).

Extra High Torque **MINI-MOTOR,** 4 1/2 to 12V, 1 1/2 x 1/2 in. 5/- (1/-), 9,000 r.p.m.  
**SUBSTITUTION BOXES.** Capacitance 25/6 (1/6). Resistance 32/6 (1/6). Both full range  
and complete. Full details in list.

**TEST PRODS:** Flexible, unbreakable 24in. Red and Black leads, thin 4 1/2 in. prods, 1 1/2 in.  
plugs 4/9 (1/-). **CROC. CLIPS:** Plated with screw, or with red/black handles, 6d. each,  
5/- doz. (1/-). Many other types in list.

**RECORDING TAPE** Finest quality British Mylar. **STANDARD:** 5in. 600ft. 7/3  
5 1/2 in. 900ft. 10/-, 7in. 1200ft. 11/3, **LONG PLAY** 5in. 900ft.  
10/-, 5 1/2 in. 1200ft. 11/3, 7in. 1800ft. 18/- (1/3 reel). Still the finest quality and value obtainable.

**MICROPHONES - CRYSTAL** MIC91, Desk, 16/3; MIC45, curved hand grip 17/6; Stick  
60/ 20/3 (1/3 each type). Cream plastic hand type with "Strut" stand, switch and 2 leads  
with 2.5 and 3.5 plugs 12/6 (1/3). Lapel (or hand) with clip 9/6 (1/-). CM70. Machined metal  
tapered stick type with neck cord and adaptor to fit standard floor stands. 29/6 (1/6).  
**DYNAMIC:** Cream hand/table 15/6 (1/6). MS10 50K Ω, 34 + rin. with Base. Adaptor 37/6  
(2/6). MS11, similar but fixed on flexible Swan neck to switch-fitted base 42/6 (2/6).

**CARDIOM DYNAMIC OMNI-DIRECTIONAL:** Highly successful "BALL" type, 209,  
50/800 ohms imp. £6.9. ● "Uni-directional ball type", switch cord adaptor - DM160 -  
£3.17/6 (both these types 5/-).

**MICROPHONE INSERTS:** Diameter 1.75in. or 0.9in., either size 6/6 (1/-).  
**SPEAKERS** 2in. round, fitted Tweeter, 6W, 3 or 15 Ω (state which), 37/6 (5/6); or for  
stereo, 80/- per pair (charges paid), 2 1/2 in. 3 Ω 7/6 (1/-); Limited quantity powerful 2 1/2 in.  
PM transistor replacement speaker, high ohms, excellent 5/9 (1/-). **HEADPHONES:**

Stereo Dyn 8-16 Ω 65/- (3/-). **EARRPHONES** with lead and min. jack plug, magnetic 1/9.  
Crystal 4/9 (up to 3 for 1/- on either). State if 2.5mm. of 3.5mm. plug required. (Crystal  
3.5mm. only).

**AERIALS CAR TYPES** - Telescopic vaudal proof locks retracted, 2 keys and all fittings  
27/6 (2/6) Superior type, slightly longer, 30/- (2/3).  
Extended Aerials for Portable F.M. Sets - 4-section 61-23", 3" sliding threaded base,  
needs 1" hole 4/-, 6-section 64-25", screw hole in base 4/-, 7-section 54-32", screw hole  
in base 6/6, 10-section, 6/47", screw hole in base 15/9. ● **DISAPPEARING**, with swivel  
and sliding threaded socket, fixing nut on bottom section - 8-section 54-29 1/2", 1 1/2" dia. 12/6. ●  
10-section 74-59 1/2", 1 1/2" dia. 15/9.

All are strongly plated (P. P. & L. on all above, up to three 1/-)  
**SWITCHES:** Standard toggle, metal, 250V 2A. On-hole fixing: SPST 2/3, SPST 2/9,  
DPST 3/-, DPST 3/9. Slide type, sub-min. DPDT 1/6 each. Small DPDT 3 way centre  
"off" 1/9. Reed magnetic on/off 1/9 (up to three, 1/-; 1d each all additional). Rotary  
Switches etc. in list.

**VIBRATORS:** Famous makes only. 12 volt 4 pin non-synch, 4/6. 12 volt 7 pin synch.  
12/6 (1/- each either type). No other types available.

**MAINS NEON TESTER:** Fly leads 2/-. Pocket screwdriver type 3/6. **PLUGS:** Std. Jack,  
plastic body 2/6. Screened 3/-. **VALVE HOLDERS:** B7C or B9A, 6d. (all above 1/-  
up to three). Many more British and Continental standard and miniature PLUGS &  
SOCKETS detailed in list. Also **STANDARD AND SURPLUS VOLUME CONTROLS.**

**CONNECTING WIRE:** 5 coils asstd. coils, each 5 yds. Solid Core 2/9. Flexible 3/3. Super  
thin for transistor wiring etc. 3/3 (1/- all types per 5 coils). **PICK-UP WIRE:** Twin Super  
thin Flex, Screened, Sheathed, 1/3 yd. (6d. up to 6 yds., over 6 yds. post free). **TWIN  
MIKE CABLE:** 1/3 yd. **SINGLE MIKE CABLE:** 8d. yd. Both flexible, screened and sheathed.  
(Up to 3 yds. 8d. each each 1d. extra).

**R.F. FIELD INDICATOR,** 5-band with antenna, monitoring crystal earpiece, visible  
indicator etc. 48/6 (1/6). Details in list.

**RETRACTABLE FLEXIBLE LEADS.** Space saving "Curly", many uses in car and home:  
with phono plug each end, 8ft., 4/6; 12ft., 7/9; With phono plug one end, phono socket  
at other, 6ft., 5/-, 12ft., 8/6 (1/- each all types).

**SPECIAL PURCHASE - COMPUTER PANELS** clean and unused.  
**TYPE 'A,'** 4 1/2" x 4" with eight Mullard OC43 transistors, 24 OA81 diodes, 32 resistors, etc.  
8/6 per panel.

**TYPE 'B'** 5" x 4" two Mullard OC43 transistors, six OA47 and four OA91 diodes, resistors  
and other items 5/6 per panel.

**POT CORES** type LA2, exactly as sold elsewhere at 15/- New and unused at 8/6 each  
(E.P. and 1 all three items 1/- up to 3 and pro rats).

**CURRENT LIST:** With many more items sent if requested with all orders or free for S.A.E.  
(Post free overseas). This advertisement cancels all previous ones and lists supplied prior to  
July 31st, 1970.

## FELSTEAD ELECTRONICS

(PW34) LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE, SK8 4EE

TERMS: Cash with order only. No C.O.D. or caller service. Post, packing and insurance  
charges are shown in brackets after all items. Regret orders under 5/- plus carriage cannot  
be accepted, and a minimum charge of 1/- is now made. Charges apply to G.B. and Eire  
only. Overseas orders welcomed. Air or surface mail at cost. Sent at buyer's risk, unregis-  
tered and uninsured unless specified and min. insurance/req. fee of 3/2 sent.  
S.A.E. Please or all enquiries otherwise regret cannot be replied to.

If you're a telecommunications man and match up to the qualifications below cut yourself into a slice of Britain's future

Become a

# Radio Technician

in the fast-growing world of Air Traffic Control

Please send me an application form and details of how I can join the fascinating world of Air Traffic Control Telecommunications

Name .....

Address .....

PWT/ET

Not applicable to residents outside the United Kingdom

To: A J Edwards, C Eng, MIEE,  
The Adelphi, Room 705, John Adam Street,  
London WC2  
marking your envelope 'Recruitment'

Sending this coupon could be your first step to a job that's growing in importance every year.

The National Air Traffic Control Service needs Radio Technicians to install and maintain the vital electronic aids that help control Britain's ever-increasing air traffic.

This is the kind of work that requires not only highly specialised technical skills but also a well developed sense of responsibility, and candidates must be prepared to undergo a rigorous selection process. Those who succeed are assured a steadily developing career of unusual interest and challenge. Starting salary varies from £1044 (at 19) to £1373 (at 25 or over); scale maximum £1590 (higher rates at Heathrow). There is a good annual leave allowance and a non-contributory pension for established staff.

You must be 19 or over, with at least one year's practical experience in telecommunications, ('ONC' or 'C' and 'G' qualifications preferred).

# NATCS

National Air Traffic Control Service

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/8d. per word (minimum order 20/-), box number 1/6d. extra. Semi-displayed setting £5 10s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4 for insertion in the next available issue.

## MISCELLANEOUS

### THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 4d. stamp.

**BUILD IT** in a DEWBOX quality cabinet. 2in. x 2 1/2in. x any length. D.E.W. Ltd., Ringwood Road, FERNDOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**PARAPHYSICAL LABORATORY.** Downton, Wilts. Telekinetic photographs/data. S.A.E. for list. Samples 20s.

**2 WATT TRANSISTOR AMPLIFIERS** (not a kit). Standard 3 ohm output. Frequency response  $\pm 2$ db from 12 to 12000 cps, on board measuring 2 1/2 x 3 1/2 in. Ideal record players etc., 22s 6d each, pp 1s 6d. A. Manley, 111 Mayow Road, Sydenham, S.E.26.

### TOP TRANSISTORS

ACV22 1/9	BFY51 1/9	OC201 1/9
BC108 1/9	BFY52 1/9	OC202 1/9
BC109 1/9	OC45 1/9	ZTX300 1/9
BC168 1/9	OC71 1/9	2N706 1/9
BC169 1/9	OC72 1/9	2N2926 1/9
BSY27 1/9	OC200 1/9	2N3708 1/9

All the above types are available at 16 for £1. Brand New. Individually Tested, unmarked but guaranteed to be within their correct specification, or money refunded.

### ANTEX SOLDER IRON

A lightweight iron with a 15 watt nickel plated bit. Designed to enable you to weld reliable joints accurately. Model CN240 volts. Special low price. Act Now Only 29/11

**MONEY BACK GUARANTEE P. & P. 1/-**  
**J. M. KING (R), 17 Buckridge,**  
**Portpool Lane, London, E.C.1**

**GOOD CONNECTIONS** take seconds with the revolutionary new Keynecter. Cuts out plugs, sockets and dangers from bare wires. Just the job for high speed testing of electronic equipment. A must for the do-it-yourself enthusiast. Send for leaflet to E.B. Instruments, Dept. P.W., 49/53 Pancras Road, London N.W.1 (837 7781). Only 46/6d plus postage.

**TV NOTES FOR UFO DETECTION**, and 2 Optical Detector circuits, 9/6. All-night Optical/Radiation circuit with electronic "memory", 9/6. Radar & Electronic Publications, "Highlands," Needham Market, Suffolk.

**ALL THOSE LITTLE ITEMS** which you can never find are available from our stock. Also speaker fabrics, BAF wadding, Peerless speakers, cabinet kits, cross-overs. For full details send 9d in stamps to Audioscan, Dept. P.W., 4 Princes Square, Harrogate, Yorks.

## MISCELLANEOUS

(continued)

### ENAMELLED COPPER WIRE

S.W.G.	Per 1/2lb reel	Per 1lb reel
18-22.	11/3d	16/6d
23-30.	11/9d	17/6d
31-35.	12/3d	18/6d
36-40.	15/-	24/-
41-44.	17/9d	29/6d

Orders despatched by return of post. Please add 1/- per item P. & P.

Supplied by: Banner Transformers, 84 Old Lansdowne Rd, West Didsbury, Manchester, 20.

### TRADE ENQUIRIES INVITED

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 5/- each. Television Manuals 7/6 each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond, Surrey.

### "SHURE" TAPE HEADS

Record/playback and erase in one unit. Mounted on bracket with tape guide etc. 10/- post paid "MARRIO" Single record/playback heads. 5/- post paid.

### PHOTO ELECTRIC SWITCH KIT

Light cell, transistor, relay etc. Elegant case in hammer finish 5 1/2" x 2 1/2" x 4 1/2" fitted with light hood, ideal counter alarm. Dawn/Dusk switch, etc. 35/- Post Paid.

### 6 OR 12 VOLT FLUORESCENT LIGHTS

12 In. 8 Watt tube ample light for caravan, tent etc. Fully transistorised, low battery drain. Unbeatable at 65/6 post paid.  
or in kit form 57/6

### 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed 72/6 POST PAID  
**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop, Shrewsbury, Shropshire S.A.E. for lists

**MUSICAL MIRACLES!** Drum, Cymbals, Waa-Waa and Fuzz modules. New unique effects units, Percussion etc. Good waa-waa kits 49/-. Famous "Mister Bassman" bass pedal unit. Also bargain components list of reed switches etc. Send S.A.E. NOW!—D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.

## AERIALS

### BAKER AND BAINES

BBC dipole 30/-, H 42/-, 3 ele 89/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/5, 11 ele 57/6, ITA doubles 8 ele 112/-, 11 ele 140/-, 13 ele 159/-, Combined BBC/ITA D+5 45/-, D+8 52/-, H+5 69/-, X+5 75/-, Combined Loft Special D+5 with loft pole and fixings 37/-, UHF Aerials BBC-ITA 14 ele 37/-, 18 ele 54/-, 22 ele 63/-, Double 22 ele 142/-, CO-AX low loss at 1/3 and 2/3, Co-Ax plugs 1/4.  
Diplexers—Triplexers—Matched UHF/VHF Diplexers. VHF/UHF Pre Amps 75/-  
Poles, Lashings, Clamps, Couplers, etc. Postage Paid inland on aeriels. Extra on accessories. Please state channels when ordering.  
11 Dale Cres., Tupton, Chesterfield.

## FOR SALE

### MORSE MADE EASY !!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring, s.t.d. 01-660 2896 send 8d. stamp for explanatory booklet to: G8CHS (BOX 11), 45 GREEN LANE, PURLEY, SURREY

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW. NEW MILLS, Stockport.

**YUKAN SELF-SPRAY** SO PROFESSIONAL THE YUKAN AEROSOL WAY

*Get these NOW!* **air drying GREY HAMMER OR BLACK WRINKLE (CRACKLE) finishes**

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 16/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.  
SPECIAL OFFER: 1 can plus optional transferable soap-on-rigger handle (value 5/3) for 18/11 carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to: Dept. M. YUKAN, LONDON, W.2. 307A, EDWARE ROAD.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—we can supply you too.  
Open all day Saturday, closed Thursday afternoons.

## ELECTRICAL

**240 VOLT ELECTRICITY ANYWHERE**



**BEST EVER 200/240 VOLTS "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY**

Exclusive World Scoop Purchase. The fabulous Mk. 12D American Heavy Duty Dynamo motor Unit with a Massive 220 watt output and giving the most brilliant 200/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal AC/DC mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested, only £59.6, plus 10/6 postage. C.O.D. with pleasure. Money back if not delighted. Please send s.a.e. for interesting illus. details.

**Dept. PW, SCIENTIFIC PRODUCTS**  
Rear Derby Road, North Promenade,  
Blackpool, Lancashire.

## METAL WORK

**METAL WORK:** All types cabinets, chassis, racks etc., to your specifications. PHILPOTTS METAL WORKS LTD., Chapman Street, Loughborough.

**RANK WHARFEDALE LIMITED**

require

**tester/  
troubleshooters**

The Company, who are leading producers of quality Hi-Fi equipment require suitably qualified staff for production line testing of transistorised electronic equipment.

Applicants should preferably possess either a formal qualification in radio servicing or testing, or have obtained equivalent experience in similar work.

Location — Bradford, Yorkshire.

The positions carry staff status, and good salaries will be paid to the successful candidates.

There is a contributory pension scheme and free life assurance benefit. Assistance with removal expenses will be paid if applicable.

Applications to:

The Personnel Manager,  
Rank Wharfedale Limited,  
Bradford Road,  
Idle, Bradford BD10 8SQ  
Yorkshire.  
Tel: Bradford 612552



**AUDIO  
VISUAL  
DIVISION**



**The Rank Organisation**

*The man with the gong — a man of many skills*



**ENGINEERS, A TECHNICAL CERTIFICATE** or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C.Eng., A.M.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts., Building, etc. For full details write for FREE 132 page guide: BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, (Dept. 169K), Aldermaston Court, Aldermaston, Berks.

**ELECTRONICS TECHNICIAN** and **JUNIOR TECHNICIAN** (16-20) required for Psychology Department to assist in development, construction and maintenance of electronic equipment for use in teaching and research laboratories. Little routine work; good opportunities to exercise initiative; excellent holidays. Salary scales: Technician: £1,060-£1,428 + supplementary allowance for approved higher qualifications. Junior Technician: £581-£869 (with paid day release for further study). Apply, stating age, qualifications, experience, and present salary, to Administrative Assistant (PI), Birkbeck College, Malet Street, London, WC1E 7HX.

TV and Radio. A.M.I.E.R.E., City & Guilds, R.T.E.B. Certs., etc on 'Satisfaction or Refund of Fee' terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment) in all branches of Radio, TV, Electronics, etc. Write for 132 page Handbook—FREE. Please state subject. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept 137K), Aldermaston Court, Aldermaston, Berks.

**EDUCATIONAL**

**BECOME** "Technically qualified" in your spare time, guaranteed diploma and exam. home-study courses in radio, TV servicing and maintenance. T.T.E.B., City and Guilds, etc.: highly informative 120-page Guide—free. CHAMBERS COLLEGE (Dept. 857K), 148 Holborn, London, E.C.1.

**CITY & GUILDS** (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page Handbook—FREE. B.I.E.T. (Dept. 168K), Aldermaston Court, Aldermaston, Berks.

# Radio Operators

There will be a number of vacancies in the Composite Signals Organisation for experienced Radio Operators in 1971 and in subsequent years.

Specialist training courses lasting approximately nine months according to the trainee's progress are held at intervals. Applications are now invited for the course starting in January 1971.

During training a salary will be paid on the following scale:—

Age 21	£848 per annum
22	£906 " "
23	£943 " "
24	£981 " "
25 and over	£1,023 " "

Free accommodation will be provided at the Training School.

After successful completion of the course, operators will be paid on the Grade I scale:—

Age 21	£1,023 per annum
22	£1,087 " "
23	£1,150 " "
24	£1,214 " "
25 (highest age point)	£1,288 " "

then by six annual increases to a maximum of £1,749 per annum.

Excellent conditions and good prospects of promotion. Opportunities for service abroad.

Applicants must normally be under 35 years of age at start of training course and must have at least two years' operating experience. Preference given to those who also have GCE or FMC qualifications.

Interviews will be arranged throughout 1970.

Application forms and further particulars from:—

**RECRUITMENT OFFICER,  
Government Communications  
Headquarters,  
Oakley, Priors Road,  
CHELTENHAM, Glos. GL52 5AJ  
Tel: No. Cheltenham 21491 Ext 2270**

**EDUCATIONAL  
(continued)****TRAIN FOR SUCCESS  
WITH ICS**

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE,  
STEWARTS ROAD, LONDON. SW8

**RADIO OFFICER** training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

**HI-FI EQUIPMENT**

**SHURE GOLDRING** Cartridges Post Free. G800, M44/5/7 £7.17.6. M3D £5.5.0. M44E £8.19.6. M55E £9.19.6. M75E/2 £16.10.0. GARRARD SP25/2 £10.17.6. AP 75 £16.17.6. p. & p. 7/6. Ultimate Electronics, 38 Achilles Road, London, N.W.6. Mail Order Only.

## WANTED

**CASH PAID** for New Valves. Payment by return. **WILLLOW VALE, ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

**WE BUY** New Valves and Transistors. State price: **A.D.A. MANUFACTURING CO.**, 116 Alfreton Road, Nottingham.

## WANTED NEW VALVES ONLY

Must be new and boxed  
Payment by return

**WILLIAM CARVIS LTD.**  
103 North Street, Leeds 7

**WANTED NEW VALVES**, televisions, radiograms, transistors, etc. **STAN WILLIAMS**, 37 High Street, West Bromwich, Staffs. Tel.: WES 0186.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

**WANTED EARLY WIRELESS ITEMS** 1900-1920. Outside Horn, Hand-operated, Springless, Gramophones. Please describe and price wanted. **T. Christen**, 12 Princess Terrace, Brighton 7, Sussex BN2-5JS.

**VALVES AND TRANSISTORS** required in new condition. Any quantity purchased. Quotation by return. **Langrex**, 16A Wellfield Road, Streatham, S.W.16. 01-769-0199.

**WANTED**. Six Truvox Rank Language Laboratory Pupil Decks in working order. **Headmaster**, Maes Garmon School, Mold, Flint.

## SERVICE SHEETS

**SERVICE SHEETS** (1925-1970) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 1/-. Over 8,000 models available. Catalogue 2/6. Please send S.A.E. with all orders/enquiries. **Hamilton Radio**, 54 London Road, Bexhill, Sussex.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 5/- each, Manuals from 10/- plus large S.A.E.

(Uncrossed P.O. s please, original returned if service sheets not available.)

**C. CARANNA**  
71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

## SERVICE SHEETS (continued)

**RADIO, TELEVISION** over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

**SERVICE SHEETS** (75,000) 5/- each: please add loose 4d. stamp: callers welcome; always open. **THOMAS BOWER**, 5 South Street, Oakenshaw, Bradford.

**SERVICE SHEETS**, Radio, TV etc. 8,000 models. List 2/-. S.A.E. enquiries. **TEL-RAY**, 11 Maudland Bank, Preston.

## TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

## OAKFIELD ENTERPRISES

LIMITED

30 CRAVEN STREET, STRAND  
LONDON WC2

Make	Model	Radio/TV

1970 List now available at 2/- plus postage

If list is required indicate with X

From .....

Address .....

enclose remittance of .....

(and a stamped addressed envelope)  
s.a.e. with enquiries please

**MAIL ORDER ONLY** (February PW)

## BOOKS & PUBLICATIONS

### SURPLUS HANDBOOKS

19 set Circuit and Notes ..	7/0 p/p 9d.
1155 set Circuit and Notes ..	7/0 p/p 9d.
H.R.O. Technical Instructions ..	6/0 p/p 9d.
38 set Technical Instructions ..	6/0 p/p 9d.
46 set Working Instructions ..	8/0 p/p 9d.
88 set Technical Instructions ..	7/6 p/p 9d.
BC.221 Circuit and Notes ..	6/0 p/p 9d.
Wavemeter Class D Tech. Instr. ..	6/0 p/p 9d.
18 set Circuit and Notes ..	6/0 p/p 9d.
BC.1000 (31 set) Circuit and Notes ..	6/0 p/p 9d.
CR.100/B.28 Circuit and Notes ..	10/6 p/p 1/-
R.107 Circuit and Notes ..	7/6 p/p 9d.
AR.88D Instruction Manual ..	18/6 p/p 9d.
62 set Circuit and Notes ..	7/0 p/p 9d.
<b>Circuit Diagram 5/6</b> each post free, R.1116/A, R.1224/A, R.1355, R.F. 24, 25 and 26, A.1134, T.1154, CR.300, BC.312, BC.342, BC.348J, BC.348 (E.M.P.), BC.624, 22, 1475 (88), 1392.	
Colour Code Indicator ..	2/6 p/p 6d.
52 set Sender and Receiver circuits 8/- post free	

S.A.E. with all enquiries please.

Postage rates apply to U.K. only.

Mail order only to:

**INSTRUCTIONAL HANDBOOK SUPPLIES**

DEPT. PW, TALBOT HOUSE,  
28 TALBOT GARDENS, LEEDS 8

## RECEIVERS & COMPONENTS

### NEW MODEL V.H.F. KIT MK2

Our latest Kit improved design and performance plus extra Amplifier Stage receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4 etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

ONLY 68/- P. & P. FREE U.K. ONLY

### "AUDIO 1" 3 WATT AMPLIFIER

Ready built, tested and guaranteed. Very attractive Cabinet in black leatherette with light grey front, size 10" x 4 1/2" x 4". Fitted large speaker, Jack Socket and Volume Control. Many uses e.g. Radio Kit Amplifier, Intercom, Record Player, Public Address or even Crystal Set Amplifier. **OUR PRICE ONLY 97/- P. & P. 4/6d.**



### EXTENSION SPEAKER CABINET

The same Cabinet that houses our Amplifier. **ONLY 26/- P. & P. 3/-**. Or with fitted Speaker 34/- P. & P. 3/6d.

Cheques, Postal orders to:

Dept. P.W.,  
**Galleon Trading Co.**, 288A Lodge Lane,  
Romford, Essex

## Stella Nine Range Cases

Manufactured in Black, Grey, or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g Alloy.

Now all Aluminium surfaces are coated with a strippable plastic for protection during manufacture and transit. All edges are polished.

### LIST OF PRICES AND SIZES

Width	Depth	4" Height	6" Height	7 1/2" Height
£ s. d.	£ s. d.	£ s. d.	£ s. d.	£ s. d.
6 1/2"	3 7/8"	15 0	18 0	1 1 6
6 1/2"	4 1/4"	16 3	1 1 6	1 5 0
8 1/2"	3 7/8"	18 0	1 5 0	1 5 0
8 1/2"	6 1/2"	1 5 0	1 11 9	1 17 0
10 1/2"	7 1/2"	1 14 6	2 2 6	2 6 0
12 1/2"	3 7/8"	1 5 0	1 11 9	1 17 6
12 1/2"	5 1/2"	1 14 0	2 2 0	2 5 6
12 1/2"	8 1/2"	2 3 0	2 11 6	2 15 6
14 1/2"	3 7/8"	1 10 0	1 17 6	2 2 0
14 1/2"	9 1/2"	2 11 6	3 7 0	3 10 0
16 1/2"	6 1/2"	2 6 0	2 15 6	3 1 9
16 1/2"	10 1/2"	3 0 0	3 18 0	4 6 0

Cases—Post 4s. 6d. per order.  
Discounts available on quantities.

### CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2 1/2" Walls

s. d.	s. d.	s. d.
6" x 3"	6 6	10" x 7" 10 3
6" x 4"	6 9	12" x 3" 8 0
8" x 3"	7 9	12" x 5" 9 0
8" x 6"	9 3	12" x 8" 12 9
		16" x 10" 19 0

Chassis—Post 3s. 0d. per order.  
Discounts available on quantities.

## E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE  
Tel: 061-480 2179

**BRAND NEW ELECTROLYTICS**, 15/16V, 0.5, 1, 2, 5, 10, 20, 30, 40, 50, 100 mfd, 8.5d. E12 series 5% resistors. Carbon Film 1/4W 10Ω to 1MΩ, 1.5d. Wirewound 5W 15Ω to 15KΩ, 10d., postage 1/-. **The C. R. Supply Co.**, 127 Chesterfield Rd., Sheffield 8.

**TRANSFORMERS**. Rewound, Prototypes supplied capacity for small quantity runs. S.A.E. please. **Ratcliffe**, 18 Beech Avenue, Thongsbridge, Huddersfield, Yorks.

## LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on 1/4 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested



**CAXTON COLUMN.** This is a column cabinet 23 1/2 x 5 1/2 x 5 1/2 in. deep finished in black or wood grain cloth with blue Vynair front. Key-hole slot for wall mounting. Fitted with three speaker units, 9 ohms impedance. Handles 8 watts. Makes all the difference in quality and volume of tape recorders and record players. Real bargain at 59/6d. P. & P. 11/- each.

**SPEAKERS:** E.M.I. 13 1/2 x 8 in. 3 ohm, 45/-, 15 ohm 48/6. P. & P. 5/6. E.M.I. 3 in. tweeter 17/6. P. & P. 2/6. E.M.I. 13 1/2 x 8 in. fitted two 2 1/2 in. tweeters. 15 ohm 77/6. P. & P. 5/6. E.M.I. 13 1/2 x 8 in. (15 ohm) Hi-Fi quality £5.19.6. P. & P. 5/6. E.M.I. Woofers, 6 1/2 x 4 1/2 in. square, 8 ohm, 59/6. P. & P. 4/6. E.M.I. Crossover, 16/6. P. & P. 1/-, EAGLE Crossover units 3 or 16 ohms, 17/4. P. & P. 1/6. Bakers 12 in., 25 watt 15 ohm £6.6.0. P. & P. 5/6.

**VYNAIR** Widths from 40 to 54 in., 15/- yd. off roll. P. & P. 1/9. 1/2 yd, 8/-, P. & P. 1/9. Send 11-stamps for samples.

**ELF.** An extension speaker of quality, 8 x 5 1/2 x 3 1/2 in. veneered in natural teak with smart gold and brown Vynair front trimmed with white. Fitted re-conned 5 in. 3 ohm speaker. The baffle is half inch thick. A real bargain at 37/6. P. & P. 4/9.



## BROADWAY ELECTRONICS

(Nr. Tooting Broadway Underground Stn)  
92 MITCHAM ROAD, TOOTING BROADWAY, LONDON, S.W.17 01-672 3984 (Closed all day Wed.)


**CARTRIDGES.** Stereo: Sonotone 9TA H/C Diamond, 47/6. Ronette S105 Medium Output, 28/6. S106 High Output 28/6. Acos GP93 1 Sapphire, 37/6. GP94 1 Sapphire, 39/6. GP91 Stereo Compatible (High, Medium or Low Output) 25/- TA800 converts Philips AG3301, AG3306 to B.S.R. SX1H. Plug-in head complete with cartridge, 50/-. TA700 equivalent to B.S.R. SX1M, 35/-, Japanese equivalent to B.S.R. TC8s, 35/-, P. & P. 1/6. Mono: Acos GP67/2 will replace Coilaro and Garrard Mono cartridges, 18/6. T.T.C. Crystal High Gain, 15/-. B.S.R. TC8H Jap. equivalent, 28/-, P. & P. 1/6.

**EARPIECES WITH CORD** and 3.5mm. plug, 6 ohm magnetic, 3/-, 250 ohm, 4/-, 180 ohm with clip, 6/6. Xtal. P. & P. 6d.

**PIANO KEY PUSH BUTTON SWITCHES.** 7 button inc. mains on off. 6 banks of 6 P.C.O., 8/6. P. & P. 1/6.

**The SHELLEY.** Size 21 x 11 x 6 1/2 in.

An extremely elegant speaker system made of 12 m.m. chipboard covered with teak leathercloth with dark Vynair front (send S.A.E. for cloth samples). This unique system uses three ex T.V. speaker 6 1/2 in round for the Bass, 8 x 3 in for the Middle and 5 in round for Treble. Carefully matched and tested. Will handle 10-12 watts and will match 8 ohms impedance. If preferred the speakers can be wired in series parallel to match 3 ohms impedance. A real bargain at £4 19 6 plus 12/9 P. & P. MATCHING TRANSFORMER for 15 ohms 16/- post free.

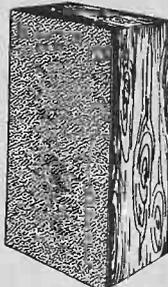

COMPLETE RANGE of Amateur Aircraft, Communications receivers. Chassis, panels, meters, cabinets, microphones, etc. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263-7829.

EMSA FOR ANTENNA SYSTEMS AND CONVERTERS. Please send s.a.c. for details of 2 metre converters, antennas and transmatchers for receiving and transmitting. ELECTRONIC & MECHANICAL SUB-ASSEMBLY CO. LTD., Highfield House, West Kingsdown, Kent. Tel. W.K. 2344.

Est. 1943 **JOHNSONS** Tel: 24864

New! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Integrated converter, receiver, and tuner-feeder. Fantastic single transistor performance! Comprehensive kit of high grade parts with three coils covering 80-178MHz, 9v battery, etc., together with simplified diagrams and instructions. Price complete, £4, post, packing and insurance paid, direct from makers. S.A.E. for literature.

**JOHNSONS (RADIO)**  
St. Martin's Gate, Worcester  
WR1 2DT

**PADGETTS RADIO STORES**  
OLD TOWN HALL, LIVERSEDE  
TEL. HECKMUNDWIK 4285

**Amplifier Unit Type A1413.** Complete with Valves Type 5Z4 and 6V6GT. 230-250 Volt, 50 Cycles Transformer. Clean Condition. Untested 25/-. Carriage B.R.S. 15/-.

**Airmileage Units.** Complete with 24 Volt Motor, and Gears, etc. less Relay. Clean Condition. Untested 15/-. Carriage B.R.S. 12/-.

Panel with two Miniature Relays and one Carpenter Relay with Base. Ex units 7/6. Post Paid.

Panels of Resistors and Condensers. Ex Equipment. 8/- per doz. Post Paid.

**AW43/80 TUBES.** Reclaimed. With 6 months Guarantee 25/-. Carriage 15/-.

**AW43/88 T.V. Tube.** Reclaimed with 6 months Guarantee £2. Plus 15/- Carriage. **MW43/69** 30/- Plus 15/- Carriage.

Speakers P.M. All 3 OHM. Perfect Condition. Ex T.V. Sets. P/P on any Speaker 4/-, 5" Round 3/-, 6 x 4 Elliptical 3/-, 7 x 4 Elliptical 5/-. Slot Speakers 8 x 2 1/2 3/-.

Silicon Rectifiers. 500 M.A. 800 P.I.V. 2/6 or 24/- per doz. Post Paid.

JAP. EARPIECES. Magnetic. 8 OHMS. Small or Large Plug 1/11 Post Paid.

**TOP GRADE MYLAR TAPES.** 7" Long Play 14/-, 7" Standard 11/6, 5" Long Play 10/-, 5" Standard 7/9. Post on any Tape 1/9.

Complete Untested 17" T.V. Sets. 12 Channel 50/-, Carr. £1.

**VALVE LIST EX EQUIPMENT.** 3 months' Guarantee. Single Valves.

ARP12	1/6	PCC84	2/-	PL36	5/-	6B8	1/6
EB91	9d.	PCF80	2/-	PL81	4/-	6BW7	2/6
EBF89	3/-	PCC89	3/-	PY81	1/6	6U4	4/-
ECC82	3/-	PCL85	5/-	PY800	3/6	20D1	3/-
ECL80	1/6	PCL84	4/-	PY82	1/6	20P1	5/-
EF183	3/-	PCL82	4/-	PY33	5/-	20P3	2/6
EF184	3/-	PCF86	4/-	U191	4/-	30PL1	5/-
EY86	4/-	PCL83	3/-	6F23	4/-	30P12	2/6
						30F5	4/9

GIEGER COUNTERS LATEST GOVERNMENT RELEASE, OF THESE EXCEEDINGLY POPULAR AND WELL KNOWN CONTAMINATION METERS. Which were intended for use, should the need arise, by the Civil Defence etc.



These are new or virtually as new, being shelf stored only, and are complete with all parts including, Carrying Haversack, Cable and Probe, Instructions for use.

This Model incorporates a plug in Vibrator Power unit, instead of the normal Battery Holder, thereby using four standard Mallory R.M.12.R. Long Life Batteries. (NOT supplied.)  
List Price £70.

SUPPLIED AS ABOVE IN MAKER'S CARTON COMPLETE AND TESTED 90/- POST 10/-, TWO CARRIAGE PAID.

FEW ONLY NOT BOXED SLIGHTLY SOILED CARRYING CASE ONLY 60/- Carr. 10/-

## J. H. TOWNEND

21 THE ROUNDWAY, MORLEY, NR. LEEDS, YORKS.

**A CORNUCOPIA OF COMPONENTS!** Scarce valve, selected T.V. components, Speakers, Cabinets, Computer panels—long leads NOT printed circuits. Transistors, resistors—new and recovered. State requirements. S.A.E. (F.S.) for details. MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

**NEW QUALITY COMPONENTS.** SAE list. M.L.H. Electronics, 114 Kingsway, Chandlers Ford, Hants.

## CONSTRUCTOR UNITS

**R.F. Generator.** Supplied with coils, tuning cap., switch and details for wiring and calibration. Covers 150KH/z to 30MH/z. 89/6 + 3/6 pp.

**A.F. Unit.** Osc. operates at 2 freq's. for A.F., R.F. checks, connects as amp. for continuity checks Dual freq. square wave o/p for audio/Hi-Fi tests. Provides modulation for R.F. unit. 39/6 + 3/6 pp.

S.A.E. for Details, Tweed Electronics (PW), 9 The Green, Hatfield Peverel, Chelmsford, Essex.

## AMAZING VALUE

### NEW BRANDED FULL SPEC. DEVICES

Plessey SL402A Preamp & 2W Amp.	40/-
GE PA234 1W Audio Amplifier	17/6
GE PA237 2W Audio Amplifier	31/6
RCA 40669 8A 400V Triac	24/-
RCA 40583 Trigger Diode	5/3
GE D40C1 4W Darlington Amp.	13/6

Notes supplied FREE with orders.

P. & P. 1/- per order. Overseas 7/6. Cash with order. Mail order only.

### JEF ELECTRONICS (P.W.9)

York House, 12 York Drive, Grappenhall, Warrington, Lancs.

Money back if not satisfied.

**COMMUNICATIONS RECEIVERS:** Ex-Govt. bargains in the £10 to £20 range. Example: B40, 640 kHz-30.5 MHz, cleaned, checked, aligned, with circuit information, £17. Carriage 40/- (England, Wales). Deposit on crate 30/-. Also Murphy CAS and Pye CAT first-class ex-navy receivers, B41, CR300, PCR2 and others. Money back guarantee. Calibrators, VTVMs, headphones, components, at competitive prices. SAE details. Phone any time. Callers welcome. P. R. GOLLEDGE, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

# WEYRAD

## COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117)	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	5/7
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117)	5/7
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	6/-
Rod Aerial	RA2W		12/6
Driver Transformer	LFDT4/1		9/6
Output Transformer	OPT1		10/6
Printed Circuit	PCA1		9/6

## I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	7/6
T41/2E	2nd I.F. Transformer	7/6
T41/3T	3rd I.F. Transformer	10/6
T41/3T	B.F.O. Coil	10/6

Details of these and our other components are given in an illustrated folder which will be supplied on request with 4d. postage please.

# WEYRAD (ELECTRONICS) LIMITED

SCHOOL STREET, WEYMOUTH, DORSET

## VALVES

**SAME DAY SERVICE**  
**NEW! TESTED! GUARANTEED**

**SETS** 1R5, 1R5, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for 18/6, DAF96, DF 96, DK96, DL96, 4 FOR 29/-.

OZ4	4/8	20P3	11/9	DK96	7/3	EL54	4/9	PCL84	7/8	UBF80	6/9
1A7GT	7/6	20P4	18/6	DL35	5/-	EL80	5/3	PCL85	9/-	UBF89	6/9
1B5GT	7/8	26L6GT	9/-	DL92	6/9	EL500	12/6	PCL86	8/8	UCC84	7/6
1B5GT	7/8	28T4GT11/6		DL84	7/3	EM50	8/3	PCL88	14/6	UCR85	7/6
1R5	5/9	30C1	16/6	DL96	7/3	EM31	8/3	PCL800	15/6	UCR90	7/3
1R5	4/3	30C15	13/-	DY86	5/9	EM54	6/9	PENA4	8/6	UCH2	12/6
1T4	2/9	30C17	18/-	DY87	5/9	EM87	7/6	PFL20011/9		UCH81	6/6
3B4	5/9	30C18	18/6	EABC80	6/6	EY81	7/8	PL36	9/9	UCL82	7/6
3V4	6/3	30P5	16/-	EAF42	10/-	EY86	6/6	PL81	9/3	UCL83	11/9
5Y3GT	5/9	30FL1	12/9	EB81	2/3	EZ40	8/-	PL82	6/6	UF41	10/6
5Z4G	7/6	30FL12	14/6	EBC83	6/-	EZ41	8/-	PL83	6/6	UF85	6/9
6/80L2	12/-	30FL14	14/6	EBC41	9/6	EZ80	4/6	PL84	6/6	UF89	6/9
6AL5	2/3	30L1	6/6	ERF80	6/9	EZ81	4/9	PL600	13/-	UL41	12/-
6AM6	2/9	30L15	13/-	ERF89	6/3	GZ33	8/9	PL604	13/6	UL44	20/-
6AQ6	5/3	30L17	15/6	ECC81	3/9	KT41	15/6	PL608	23/6	UL84	7/-
6AS6	9/-	30P4	12/-	ECC82	4/9	KT61	9/9	PM84	7/6	UM60	7/-
6AT6	4/-	30P12	13/9	ECC83	7/-	KT66	15/6	PX25	23/6	UM84	4/6
6AU6	4/6	30P19	12/-	ECC85	5/-	LN339	14/6	PY32	10/-	UY41	4/6
6BA6	4/6	30PL1	13/9	ECC804	12/-	N78	17/6	PY33	10/-	UY85	5/9
6BE6	4/9	30PL13	15/6	ECC80	6/6	P61	10/-	PY81	5/3	VP4B	15/6
6BJ6	6/6	30PL14	14/6	ECC82	6/6	PABC80	7/-	PY82	5/8	W77	3/6
6CS6	4/9	35L6GT	9/9	ECH35	6/-	PC85	10/3	PY83	5/9	W119	7/-
6FL4	9/-	35W4	4/6	ECH42	13/6	PC88	10/3	PY88	6/9	Z77	4/6
6F25	14/3	35Z4GT	5/6	ECH81	5/9	PC97	8/6	PY800	7/6	Transistors	
6F25	13/-	6063	12/6	ECH83	8/3	PC98	8/-	PY801	7/6	AC107	3/6
6J5G	4/9	807	7/6	ECH84	7/6	PC990	7/6	R19	8/6	AC127	2/6
6K7G	2/6	AC1/VP15/6		ECL80	7/-	PC824	6/6	R20	12/-	AD140	7/6
6K9G	2/9	AZ31	9/6	ECL82	6/9	PC85	6/-	SU2150A		AF115	3/-
6N7GT	4/3	B340	13/-	ECL86	8/-	PC88	9/-	U26	13/-	AF116	3/-
6SN6	3/8	B729	12/6	EF37A	6/6	PCC89	10/6	U26	12/-	AF125	3/6
6V6GT	6/6	CCH35	13/6	EF39	4/9	PCC189	9/9	U47	13/6	AF127	3/6
6X4	4/3	CL33	18/6	EF41	11/9	PCC805	13/-	U49	12/-	OC26	5/-
6X5GT	5/9	CY31	6/9	EF80	4/6	PCF80	6/6	U73	4/3	OC44	2/6
10F1	14/-	DA392	7/8	EF85	6/3	PCF82	6/6	U81	13/8	OC45	2/6
10F18	7/-	DAF91		EF86	6/3	PCF85	10/-	U91	13/8	OC45	2/6
10P13	12/-	DAF96	7/3	EF89	5/3	PCF800	13/6	U193	8/6	OC71	2/6
12AT7	3/9	DF33	7/9	EF91	2/9	PCF801	6/6	U251	14/8	OC72	2/6
12AU6	4/9	DF91	2/9	EF183	5/9	PCF802	9/-	U301	10/6	OC75	2/6
12AU7	4/9	DF96	7/3	EF184	6/6	PCF805	13/6	U329	14/6	OC81	2/6
12AX7	4/9	DE77	4/-	EL90	6/3	PCF806	12/9	U501	19/6	OC81D	2/6
12B5GT	7/3	DK32	7/6	EL95	6/3	PCF808	13/6	PABC80	6/6	OC82	2/6
19B6G17/8		DK91	5/9	EL34	5/6	PCL22	7/3	UAF42	10/3	OC82D	2/6
20F2	13/6	DK92	8/6	EL41	11/-	PCL83	12/-	UBC41	9/-	OC170	4/6

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra

## BAKER 12in. MAJOR £9



The remarkable quality and performance of the "Major" makes possible truly brilliant and rich sound from a single loudspeaker. It recreates the entire musical spectrum from 30 to 14,500 c.p.s. The unit consists of the latest double cone, woofer and tweeter cone together with a special Baker CERAMIC magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 45 c.p.s. For Hi-Fi or P.A. Rated 20 watts. Voice coils available 3 or 8 or 15 ohms.

Major Module 30-17,000 cps with tweeter, crossover, baffle 19 x 12 1/2 in. and instructions. £11.10.0


Send 4d Stamp for Further Details

**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

## MAKES 5 DIFFERENT TRANSISTOR RADIOS

Total Building Price **39/6**

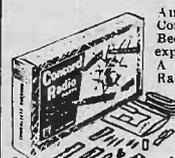

Amazing Radio Construction set! Become a radio expert for 39/6. A complete Home Radio Course. No experience needed. Parts including instructions for each design. Step-by-step plan. All Transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Box size 14" x 10" x 2"

## SHORTWAVE TRANSISTOR RADIO

Can be built in one evening only. **45/-**



At last! After trying countless circuits searching for easy build, work-first-time short wave, we chose this Sky Roma! Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. No soldering necessary. 76 stations logged on rod aerial in 30 minutes—Russia, Africa, U.S.A., etc. Experience thrilled of world wide news, sport, etc. Uses PF3 battery. Transistorised (no valves). Size only 3" x 4 1/2" x 1 1/2". 45/- + 3/6 p. & 9/- for all parts including cabinet, screws, instructions, etc. (Parts available separately.) Money back guarantee.

CONCORD ELECTRONICS LTD. (PW11), 8 Westbourne Grove, London. W.2. (nr. Bayswater Tube) Callers 9-6 inc. Sat.)

# LST

## ELECTRONIC COMPONENTS LTD

### = BETTER QUALITY, SERVICE, PRICES & LARGEST STOCKS

A1617/30	40/-	AM006	10/-	BD119	15/-	BSY95	3/2	NKT163	6/-	NKT351	10/-	OC70	2/6	40320	7/3	2N2148	12/6	3N140	15/3
AA390	1/7	AS226	4/5	BD121	18/-	BSY95A	2/12	NKT164	6/-	NKT352	17/6	OC71	3/3	40323	6/6	2N2150	14/9	3N141	14/6
AAZ13	3/2	AS272	6/-	BD123	21/6	BSW41	8/6	NKT165	6/-	NKT361	20/-	OC72	4/6	40324	9/3	2N2218	6/5	3N142	10/9
AC107	7/7	AS278	4/5	BD124	12/-	BSW70	5/6	NKT201	6/-	NKT362	20/-	OC74	8/-	40326	7/3	2N2368	3/4	3N143	13/3
AC126	5/-	AS279	6/-	BDY20	20/8	BY127	4/-	NKT202	6/-	NKT401	14/6	OC75	5/6	40329	4/9	2N2369	3/4	3N152	17/3
AC127	4/-	AS221	7/6	BF115	5/-	C106F	9/-	NKT204	6/-	NKT402	15/-	OC76	2/6	40344	5/3	2N2954	3/11	AA119	2/-
AC127Z	9/6	AU100	30/-	BF152	13/6	C111	18/-	NKT205	6/-	NKT403	14/9	OC77	5/6	40347	7/6	2N2614	4/-	AA213	2/6
AC129	4/-	B119	10/-	BF154	9/-	C111E	12/-	NKT206	6/-	NKT404	11/-	OC81	4/6	40348	10/3	2N2646	10/-	BA110	6/-
AC176	5/-	B2M	12/6	BF159	15/-	CR1-051C	8/-	NKT208	6/-	NKT405	11/-	OC81D	3/-	40360	8/6	2N2712	6/-	BA111	6/-
AC187	12/-	B3M	15/-	BF163	9/-	CR1-401C	10/-	NKT210	4/2	NKT406	9/11	OC82	5/-	40361	9/6	2N2713	5/6	BA112	1/6
AC188	12/-	B108	2/6	BF167	5/-	D13T1	10/-	NKT211	3/9	NKT420	28/11	OC82D	3/-	40362	11/6	2N2904	9/9	BA115	1/6
ACY17	5/9	BA111	6/-	BF173	6/-	FST3/8AF	5/-	NKT212	3/9	NKT451	9/11	OC83	4/6	40370	6/-	2N2905A	15/1	BA130	3/-
ACY18	4/-	BAK13	1/6	BF178	10/6	MJ480	20/6	NKT213	4/7	NKT452	9/6	OC84	5/-	40406	11/3	2N2924	4/-	BYX10	3/-
ACY19	4/-	BC107	2/9	BF179	12/6	MJ481	27/6	NKT214	3/5	NKT453	6/6	OC123	7/1	40408	13/3	2N2925	2/6	BYX36/150	2/6
ACY20	3/10	BC108	2/9	BF180	6/6	MJ490	22/6	NKT215	3/7	NKT603F	4/8	OC139	5/-	40462	11/3	Green	2/-	BYX36/300	2/10
ACY21	3/10	BC109	2/9	BF181	6/6	MJ491	29/6	NKT216	7/6	NKT613F	5/2	OC140	7/1	40467	16/6	2N2926	6/6	BYX36/600	3/9
ACY22	3/9	BC113	5/-	BF184	7/-	MPI102	8/6	NKT217	9/-	NKT654F	4/2	OC170	5/1	40468A	7/-	Yellow	2/-	BVZ10	3/-
ACY27	3/6	BC116	8/-	BF185	8/-	MPI103	7/6	NKT218	6/-	NKT675	6/8	OC171	6/-	40602	6/8	2N2926	6/8	BVZ12	6/-
ACY28	3/8	BC118	5/-	BF194	3/6	MPI104	7/6	NKT219	4/7	NKT676	5/-	OC200	6/3	2G302	3/9	Orange	2/-	BVZ13	5/-
ACY29	2/6	BC125	11/-	BF200	10/6	MPI105	8/-	NKT221	7/6	NKT677F	3/10	OC201	9/16	2G309A	5/-	2N2926	2/6	EA403	3/6
ACY30	7/6	BC126	11/-	BF274	8/-	NKT11	7/6	NKT222	6/-	NKT703	8/-	OC202	18/-	2G371	5/-	Brown	2/-	EA401	5/-
ACY31	4/7	BC134	5/-	BFX13	5/-	NKT12	5/5	NKT223	5/-	NKT713	3/10	OC203	7/6	2G371B	3/-	2N3053	4/5	EA402	4/8
ACY34	3/5	BC135	6/-	BFX29	6/2	NKT32	6/-	NKT224	3/7	NKT717	5/10	OC204	8/-	2G374	5/-	2N3054	12/6	EB383	3/6
ACY35	3/6	BC136	8/-	BFX34	6/-	NKT42	6/-	NKT225	3/6	NKT734	4/11	OC205	9/-	2G381	5/-	2N3055	15/-	OA5	3/6
ACY36	3/9	BC137	8/6	BFX44	8/-	NKT43	6/-	NKT226	11/6	NKT736	6/2	OC206	10/6	2N385A	1/2	2N3255	28/6	OA10	6/-
ACY39	12/-	BC138	12/-	BFX46	5/2	NKT72	3/9	NKT227	9/6	NKT773	3/7	OC207	7/6	2N388A	15/-	2N3395A	6/-	OA47	1/8
ACY40	3/1	BC140	13/3	BFX45	6/9	NKT73	3/7	NKT228	6/6	NKT774	6/-	OC271	19/6	2N404	4/6	2N3392	5/1	OA70	1/8
ACY41	3/-	BC147	2/9	BFX86	4/11	NKT101	6/-	NKT229	3/1	NKT0013	6/8	ORP12	9/6	2N696	3/7	2N3393	3/7	OA73	1/8
ACY44	8/-	BC148	3/3	BFX87	5/11	NKT102	6/-	NKT231	6/-	NKT10419	3/10	ORP60	8/-	2N697	3/10	2N3525	21/9	OA79	1/8
AD140	11/-	BC149	3/3	BFX88	5/3	NKT103	6/-	NKT232	6/-	NKT10519	4/5	ORP61	8/-	2N698	6/-	2N3702	2/6	OA81	1/8
AD149	11/6	BC154	12/-	BFY18	15/-	NKT104	6/-	NKT237	5/9	NKT10339	4/7	ORP63	9/-	2N705	2/4	2N3703	2/5	OA85	1/8
AD161	6/-	BC167	3/6	BFY50	4/6	NKT105	6/-	NKT238	4/-	NKT10439	5/5	P346A	3/9	2N706A	2/6	2N3704	3/2	OA90	1/8
AD162	6/-	BC168	3/9	BFY51	3/9	NKT106	6/-	NKT239	4/-	NKT12329	6/4	RA5310AF	6/-	2N708	3/3	2N3705	2/8	OA91	1/8
ADT140	12/6	BC169	3/9	BFY52	4/6	NKT107	6/-	NKT240	3/10	NKT12429	10/6	RA5308AF	10/6	2N709	8/6	2N3706	2/3	OA95	1/8
ADZ11	32/-	BC171	2/-	BFY53	3/2	NKT108	6/-	NKT241	3/9	NKT13329	3/11	RS220F	4/-	2N711	7/6	2N3707	1/10	OA200	2/-
AF102	12/6	BC182L	2/3	BFY90	24/6	NKT109	6/-	NKT242	2/11	NKT13429	3/11	S1M	19/-	2N711A	4/6	2N3708	1/10	OA202	2/-
AF106	7/6	BC183L	1/10	BFW57	6/-	NKT121	10/6	NKT243	12/-	NKT16229	2/5	S4M	33/6	2N743	7/6	2N3709	2/2	OA211	8/-
AF114	5/-	BC184L	3/3	BFW58	5/6	NKT122	10/-	NKT244	3/1	NKT20329	6/8	ST140	3/-	2N744	6/-	2N3710	2/3	OA224	10/-
AF115	5/-	BC212L	3/4	BFW59	5/-	NKT123	9/6	NKT245	3/1	NKT20339	6/4	ST141	5/-	2N911	10/-	2N3711	2/6	OA227	10/-
AF116	5/-	BCY10	10/-	BFW60	4/6	NKT124	6/5	NKT252	4/3	NKT23529	15/9	ST2	9/9	2N914	3/11	2N3819	7/1	SD19	7/6
AF117	5/-	BCY12	12/-	BLY47	31/3	NKT125	4/6	NKT263	4/3	OC20	1/9	T1407	9/8	2N918	8/5	2N3820	18/9	TD176	12/-
AF118	8/10	BCY30	5/-	BS05	10/6	NKT126	4/6	NKT264	4/3	OC29	19/6	T1544	1/9	2N929	5/3	2N3826	6/-	TD314A	4/-
AF121	6/-	BCY31	5/6	BSX19	3/3	NKT127	10/6	NKT265	5/6	OC22	8/-	TIP31A	12/4	2N930	6/-	2N3866	25/-	IN60	4/-
AF124	4/2	BCY32	10/-	BSX20	3/3	NKT128	10/-	NKT270	6/-	OC23	8/-	TIP32A	14/10	2N1131	6/11	2N4037	15/-	IN64	4/-
AF125	4/2	BCY33	4/-	BSX21	7/6	NKT129	8/6	NKT271	2/10	OC24	8/-	V205	20/-	2N1132	7/9	2N4038	3/1	IN82A	9/6
AF126	3/6	BCY34	5/6	BSX22	12/7	NKT130	6/1	NKT272	2/10	OC25	7/6	V405A	9/3	2N1302	3/7	2N4061	4/-	IN83A	4/6
AF127	3/6	BCY38	6/-	BSX61	7/1	NKT137	6/1	NKT273	3/8	OC26	6/6	40250	10/9	2N1303	3/7	2N4062	4/6	IN191	5/-
AF178	9/6	BCY40	10/-	BSX76	4/-	NKT141	10/6	NKT274	2/10	OC28	12/-	40309	6/6	2N1304	4/11	2N4287	3/-	IN194	1/9
AF179	11/6	BCY42	4/-	BSX77	6/-	NKT142	10/-	NKT275	3/4	OC29	15/-	40310	9/-	2N1305	4/11	2N4288	3/-	IN1448	1/9
AF180	12/6	BCY43	4/-	BSX78	6/6	NKT143	9/6	NKT276	3/6	OC35	9/-	40311	6/9	2N1306	6/-	2N4289	3/-	IS44	1/9
AF181	8/6	BCY54	7/6	BSY27	4/-	NKT144	8/-	NKT279A	2/6	OC36	12/6	40312	9/6	2N1307	6/-	2N4290	3/-	IS103	4/3
AF185W	9/-	BCY70	7/18	BSY29	5/-	NKT151	6/-	NKT281	5/-	OC41	4/6	40314	7/3	2N1308	6/-	2N4291	6/-	IS113	4/6
AF186G	9/-	BCY71	7/18	BSY32	5/-	NKT153	6/-	NKT301	18/-	OC42	4/6	40315	7/3	2N1309	6/3	2N4292	3/-	IS130	2/-
AF239	7/6	BCY72	3/12	BSY35	5/-	NKT154	6/-	NKT302	12/5	OC43	4/6	40316	9/3	2N1613	4/5	2N4871	6/9	IS131	2/-
AFY19	22/6	BCY87	86/9	BSY37	5/-	NKT161	6/-	NKT303	17/6	OC44	3/-	40317	7/3	2N1711	5/1	2S104	12/6	IS132	3/-
AFZ11	8/-	BCZ11	7/6	BSY38	4/-	NKT162	6/-	NKT304	9/10	OC45	3/-	40319	10/9	2N1747	16/3	3N128	13/9	IS420F	8/3

**BC107/8/9 2/9**  
NPN Planar transistors  
BC107  
25+ 25+2/5 100+2/2  
BC105 25+2/3 100+2/-

**2N3819 7/-**  
Texas FET  
25+ 6/- 100+ 5/3

**SILICON RECTIFIERS**  
1 Amp Miniature Moulded Junction Rectifiers.  
P.I.V. 1-24 25-99 100+  
1N4001 50 1/6 1/5 1/4  
1N4002 100 2/- 1/10 1/8  
1N4003 200 2/6 2/4 2/2  
1N4004 400 2/2 2/8 2/7  
1N4005 600 3/- 2/11 2/9  
1N4006 800 3/6 3/3 3/-  
1N4007 1000 3/9 3/4 3/-

**NEWS NEWS NEWS NEWS...**  
L.S.T. Electronic Components Limited are proud to announce their official appointment by Newmarket Transistors Ltd.—All Newmarket products now available at Industrial User prices. All R.C.A. Semiconductor and integrated circuits now also available from L.S.T. at industrial prices. Many Mullard, General Electric, Texas types also stock at LST at Industrial User Prices and better. And what's more our Retail catalogue is free to all. Iskra resistors, Mullard Capacitors, Veroboard, Repanco coils and other misc. components stocked in large quantities. Official International Rectifier Semiconductor Centre stockists.

**2N4871 6/9**  
Motorola unijunction  
25+ 5/9 100+ 4/9

**ADI61/2 10/-**  
Siemens/Telefunken  
NPN/PNP output pair  
25+ 9/- 100+ 8/-

**DISCOUNT:** Quantities of different 1N4000 series may be combined to qualify for the quantity discount prices quoted example: 10/1N4001 1/5, 10/1N4002 1/10, 5/1N4007 3/4 (25 total pieces).  
In the event of any 1N4000 series going temporarily out of stock we reserve the right to send higher voltage types at extra charges. 1000+ & over prices on application.

**INTEGRATED CIRCUITS**  
Some R.C.A. Linear types  
CA3005 23/6 CA3022 26/- CA3041 21/9  
CA3011 14/8 CA3023 25/3 CA3042 21/9  
CA3012 17/9 CA3026 20/- CA3043 27/6  
CA3013 21/- CA302

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel. PARK 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to the Head Office  
When sending cash with order, please include 2/6 in £ for postage and handling  
MINIMUM CHARGE 2/6. No C.O.D. orders accepted  
PLEASE NOTE THAT THE VALVES OFFERED BELOW ARE NOT NECESSARILY OF U.K. ORIGIN

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel. LANCqham 8463  
Open all day Saturday

0A2	6/8	8AU8	5/-	6F15	8/-	10F18	8/-
0A3	9/-	8AV8	6/-	6F22	8/6	10L11	8/-
0B2	6/6	6AW8A	11/-	6F23	15/6	10L11L	11/-
0B3	10/-	6B8A	4/6	6F24	13/6	10P13	11/-
0C3	7/-	6BE6	5/-	6F25	15/-	10P14	20/-
0D3	6/6	6BF6	16/-	6F26	7/-	12AB5	10/-
1B3GT	7/6	6BF8	9/-	6F28	14/-	12AC6	7/6
1L4	3/6	6BH6	12/-	6F29	8/6	12AD6	7/6
1R4	6/6	6B16	8/6	6F30	7/-	12A15	8/-
1R5	5/6	6BJ7A	9/6	6J4	9/6	12AQ5	8/-
1S4	5/6	6BK7A	10/-	6J5GT	6/-	12AT6	5/6
1S5	5/6	6BL8	7/-	6J7	8/6	12AT7	6/6
1T4	4/6	6BN5	8/6	6K6GT	10/-	12AU6	6/6
1U4	6/-	6BN6	9/-	6K7	8/6	12AU7	7/6
1U5	9/6	6BQ5	5/-	6K9L	8/-	12AV6	6/6
1V2	9/6	6BR8	13/-	6K28	10/-	12AV7	9/6
1X2H	7/6	6BR7	26/-	6K25	15/-	12AV7	7/6
2D1	6/6	6BW6	16/-	6L6GT	9/-	12AY7	13/6
3A4	4/-	6BW7	13/6	6L7	8/6	12B44	10/-
3B2R	42/6	6BX6	5/-	6L18	6/-	12B46	6/6
3B71	55/-	6BZ6	6/6	6L20	6/6	12B47	6/6
3C4	8/-	6C4	6/-	6N7GT	7/-	12B48	6/6
3S4	7/-	6CG5T	7/-	6P1	12/-	12B47	6/6
3V4	8/-	6CA4	5/6	6P28	12/6	12B47	10/-
8R40Y	11/-	6CA7	10/6	6Q7	7/6	12K5	10/-
6U4G	8/-	6C10	8/6	6H7G	7/-	12K7GT	7/-
6E4GB	7/6	6C10G	8/6	6H2	8/-	12Q7C	5/-
6V4G	8/-	6C10G	23/-	6H4	11/-	12K7C	5/-
6Y3GT	8/-	6C17	8/-	6H47	7/6	12K47	5/-
5Z3	9/-	6CH6	11/-	6H67	6/6	12H7	5/-
5Z4GT	8/-	6C16	10/-	6H7	7/6	12K7	5/-
6R0L2	15/-	6CW4	12/6	6K7	8/6	12K7	8/-
6A8A	6/6	6CY3	8/-	6H7GT	8/6	12L7GT	8/6
6A8A	9/6	6C77	12/-	6H7GT	8/6	12N7GT	8/6
6A87	7/6	6D3	8/6	6H97	8/-	12M7	8/6
6A8H	10/-	6DC6	13/6	6H7	7/6	12M7	6/6
6A8J	5/6	6DK6	8/6	6H8	6/6	12X1	8/6
6A8K	6/6	6DQ6B	12/-	6H4GT	12/6	1487	15/-
6A8K	11/6	6DQ6	15/-	6H8	7/-	201H	9/-
6A8L	8/6	6E48	11/-	6H7GT	6/6	20L1	20/-
6A8M	3/6	6E17	6/6	6H4	5/-	20P1	19/-
6A8M5	5/6	6E47	7/-	6H5GT	5/6	20P3	12/-
6A8M6	4/6	6E46	12/-	6X8	11/-	20P4	20/-
6A8Q	6/6	6F1	14/-	6Y6G	12/-	20P5	20/-
6A8Q	10/-	6F5	5/-	6Y4	12/-	23C6	9/-
6A8R	6/6	6F94	5/-	6H96	8/6	25L6GT	7/6
6A8R	6/6	6E12	4/6	10D1	8/-	25Z6G	8/-
6A8S	7/6	6F13	7/6	10D2	8/-	30A6	9/-
6A8T6	18/-	6F14	12/-	10F1	13/-	30A13	8/-
6A8T6	5/6	6F15	11/-	10F9	10/-	30C1	6/6

## First Quality Fully Guaranteed




## ELECTRONIC VALVES

30C15	15/-	811A	30/-	DM70	8/-	ECF80	7/-
30C17	18/-	812A	65/-	DY70	12/-	ECF82	7/-
30C18	15/-	813	15/-	DY84	6/6	ECF83	15/-
30F5	17/-	866A	14/-	DY87	7/-	ECF88	12/6
30FL1	15/-	5042	12/-	DY802	10/-	ECF804	30/-
30FL2	13/6	6146	30/-	E58L	55/-	ECH42	13/-
30FL13	10/-	6148	47/6	EB8CC	8/6	ECH81	5/6
30PL14	15/6	6267	6/6	E130L	100/-	ECH83	8/6
30L1	7/-	6269	12/-	E280	12/-	ECH84	9/6
30L15	17/-	6939	12/-	E280F	6/6	ECL86	9/6
30L17	17/-	7199	15/-	E810F	6/6	ECL81	8/6
30P12	16/-	7386	38/-	E810F	6/6	ECL82	6/6
30P18	7/-	7588	25/-	E84R2	10/-	ECL83	12/6
30P19	15/-	9005	6/6	EB8C3	9/6	ECL84	11/6
30PL14	15/6	9008	10/-	EB8C4	10/6	ECL85	10/6
30PL13	18/-	A21	10/6	ECL86	9/6	ECL86	9/6
30PL14	17/-	A231	10/6	EB8C9	5/6	ECL87	8/6
35A5	11/-	A241	8/6	EB8C1	6/-	EY87	8/6
35B5	13/-	A250	12/-	EB8F0	8/6	EY88	8/6
35L13	9/6	CB1L	10/-	EB8F3	8/6	EF39	8/-
35L17	9/6	CB1L1	17/-	EB8F8	8/6	EF40	10/-
35L21	9/6	CB1L2	17/-	EB8F9	8/6	EF41	12/6
35V4	5/-	DA41	7/-	EC86	12/-	E241	14/-
35Z3	11/-	DAF9	5/-	EC88	12/-	EF80	5/6
35Z4	5/-	DAF92	9/6	EC89	6/-	E281	5/6
35Z5GT	7/6	DAF96	7/6	EC92	6/6	E282	7/6
50A5	13/-	DP96	7/6	EC93	9/6	EF85	7/-
50L5	19/-	DK40	10/-	EC84	11/-	EF89	5/6
50C1	12/-	DK91	7/-	EC88	12/6	EF91	4/6
50C2	12/-	DK92	9/-	EC82	6/-	EF93	4/6
50L6GT	8/-	DK96	8/-	EC83	6/-	EF94	5/6
83A1	18/-	DL91	5/6	EC84	6/-	EF95	6/-
85A2	7/6	DL92	7/6	EC85	5/6	EF96	4/-
90A4	48/-	DL93	4/-	EC88	8/-	EF97	10/-
90C1	12/-	DL94	8/-	EC89	11/-	EF183	6/6
90C2	25/-	DL95	8/-	EC89	4/-	EF184	7/-
907	9/6	DL96	7/6	EC189	11/-	EF90	20/-

EF811	15/-	HL94	8/-	PL33	7/-	U404	7/6
EF812	15/6	KT85	27/6	PL36	11/-	U801	20/-
EF814	18/6	KT88	33/-	PL31	9/6	U808	6/6
EF820	5/-	N78	21/-	PL32	9/6	U840	10/-
EL34	10/6	P8C80	8/-	PL33	9/6	U841	10/-
EL36	9/6	P8C81	13/-	PL34	7/6	UB41	11/-
EL41	11/-	PC97	8/6	PL302	15/6	UB41	9/6
EL42	11/6	PC98	9/6	PL500	15/6	UBC81	8/6
EL81	10/-	PC94	7/-	PL504	18/-	UBF80	7/6
EL84	9/3	PC85	8/-	PL508	17/6	UBF89	7/6
EL85	8/6	PC89	10/6	PL509	30/-	UBL1	10/-
EL86	8/6	PC89	10/6	PL801	18/-	UBL2	12/-
EL90	6/6	PC89	10/6	PL802	14/-	UC92	6/6
EL91	5/6	PC89	10/6	PL803	14/-	UC93	6/6
EL95	7/6	PC89	10/6	PL804	9/6	UC98	10/6
EL96	7/6	PC89	10/6	PL805	17/6	UC99	10/6
EL97	7/6	PC89	10/6	PL806	17/6	UC99	10/6
EL98	7/6	PC89	10/6	PL807	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL808	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL809	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL810	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL811	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL812	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL813	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL814	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL815	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL816	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL817	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL818	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL819	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL820	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL821	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL822	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL823	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL824	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL825	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL826	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL827	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL828	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL829	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL830	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL831	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL832	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL833	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL834	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL835	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL836	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL837	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL838	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL839	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL840	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL841	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL842	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL843	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL844	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL845	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL846	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL847	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL848	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL849	17/6	UC99	10/6
EL99	7/6	PC89	10/6	PL850	17/6	UC99	10/6

## SYNCHROSCOPE TYPE C1-5

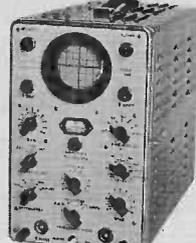

3-in tube fitted with telescopic viewing hood, giving bright display in full daylight.  
Bandwidth 10 c/s-10 mc/s. Triggered sweep pre-set at 1-2-5-10-30-100-300-1000-3000 µsec per stroke. Free-running time base 20 c/s to 2000c/s with built-in crystal calibrator providing timing marks at .05-2-10-5-20-100 µ sec ± 3%.  
Amplitude calibrator directly calibrated in volts. Input attenuator 1-10-100.  
Power supplies 127/230V AC.  
PRICE £39.0.0. Packing and carriage 30/-

## MINIATURE 1-IN CATHODE RAY TUBE TYPE

DH3-91-1CF1-1CF31  
63v heater. Anode voltage 300v. Sensitivity Y plates 45/cm; X plates 52/cm (typical) Y plates suitable for asymmetrical deflection. Green face, medium persistence.  
PRICE £8.0.0 p.p. 5/-

## DETECTOR DIODES

IN34A	4/-	GEX23	1/6	OAS5	1/6
IN38A	4/-	GEX44	1/6	OAS6	3/6
IN69	4/6	GEX54	2/-	OAS9	2/-
IN81	4/-	GEX94	4/-	OAS1	2/-
IN483	2/6	GEX901	4/3	OAS5	2/-
AAV11	2/3	OAS	3/6	OAS20	2/-
AAV30	2/-	OAS	4/-	OAS22	3/6
AAZ12	8/6	OAS	7/6	SK541	4/-
CG4E	6/-	OAS10	6/6	SK781	4/-
CG10E	1/6	OAS7	2/6	ZS10A	6/-
CG12E	2/-	OAS7	2/6	ZS10B	6/-
CG82H	1/6	OAS7	2/3	ZS20B	3/6
CV284	6/-	OAS1</			

# VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities" ?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

## On 'SATISFACTION or REFUND of FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

## WHICH OF THESE IS YOUR PET SUBJECT?

**RADIO ENGINEERING**  
Advanced Radio — Gen. Radio — Radio & TV Servicing — TV Eng. — Telecommunications— Sound Recording — Automation — Practical Radio — Radio Amateurs' Exam.

**ELECTRONIC ENG.**  
Advanced Electronic Eng. — Gen. Electronic Eng. — Applied Electronics — Prac. Electronics — Radar Tech. — Frequency Modulation — Transistors.

**ELECTRICAL ENG.**  
Advanced Electrical Eng. — Gen. Electrical Eng. — Installations — Draughtsmanship — Illuminating Eng. — Refrigeration — Elem. Electrical Science — Electrical Supply — Mining Elec. Engineering.

**MECHANICAL ENG.**  
Advanced Mechanical Eng. — Gen. Mechanical Eng. — Maintenance Eng. — Diesel Eng. — Press Tool Design — Sheet Metal Work—Welding — Eng. Pattern Making — Inspection — Draughtsmanship — Metallurgy — Production Eng.

**CIVIL ENGINEERING**  
Advanced Civil Eng. — Gen. Civil Eng. — Municipal Eng. — Structural Eng. — Sanitary Eng. — Road Eng. — Hydraulics — Mining — Water Supply — Petrol Tech.

**AUTOMOBILE ENG.**  
Advanced Automobile Eng. — Gen. Automobile Eng. — Automobile Maintenance — Repair — Automobile Diesel Maintenance — Automobile Elec. Equipment — Garage Management.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power? B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

**British Institute of Engineering Technology**

453A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

## THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT CAREER - GUIDANCE

PRACTICAL EQUIPMENT


INCLUDING TOOLS

Basic Practical and Theoretic Course for beginners in Radio, T.V., Electronics, Etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

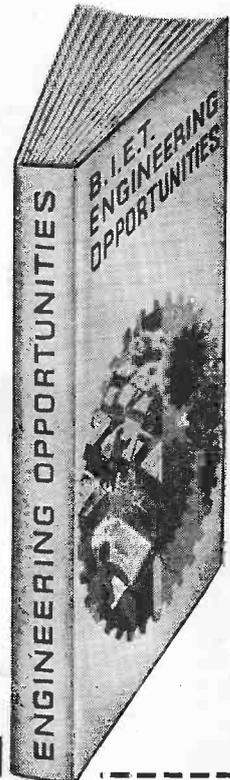**B.I.E.T.**

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy now—FREE and without obligation.



## POST NOW!

TO B.I.E.T., 453A, ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME .....

ADDRESS .....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-236 8080. Printed in England by Index Printers Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage); For one year to any part of the world £2 5s 0d. PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

# HENRY'S RADIO LTD • MAIL ORDER AND INDUSTRIAL SALES DEPT. 303, EDGWARE ROAD LONDON W.2 01 723 1008 9

● **ELECTRONIC COMPONENTS AND EQUIPMENT**  
AUDIO AND TEST GEAR  
356 EDGWARE ROAD LONDON W.2  
TEL. 01-402 4736

● **ELECTRONIC ORGANS, PUBLIC ADDRESS**  
DISCOTHEQUE EQUIPMENT  
309 EDGWARE ROAD LONDON W.2  
TEL. 01-723 6963


● **HIGH FIDELITY SALES**  
AND DEMONSTRATIONS  
354, EDGWARE ROAD LONDON W.2  
TEL. 01-402 5854

OPEN MONDAY TO SATURDAY 9AM TO 6PM. THURS 9AM TO 1PM. OPEN ALL DAY SATURDAY
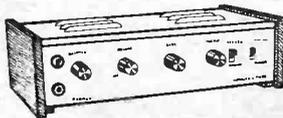
## COMPLETE STEREO SYSTEM FOR £39-10-0

**HENELEC 5-5 STEREO AMPLIFIER.** Inputs for ceramic cartridge. Aux./Tuner. Output for 8 to 15 ohms speakers. Silver with black and wood finish. British made. Size 12½ x 3½ x 6½. Fitted headphone socket.

Complete system comprises 5-5 amplifier, Garrard 3000 or model 50 with 9TAHC diamond cartridge. Pair E.M.I. 10watt speakers, twin tweeters and crossover with polished wood cabinets 18" x 11" x 7". Also plinth and cover. **CREDIT SALE FOR CALLERS**  
● **COMPLETE STEREO SYSTEM** (Rec. Price £50), **£39-10-0** p.p. 20/-



- **AMPLIFIER ONLY** £13-19-6, p.p. 7/6
- **TE1035 RECOMMENDED STEREO PHONES** 39/6

## BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.

**PARTS TOTAL COST** £6.19.6, p.p. 3/6  
**DECODER** £5.19.6, (FOR STEREO) p.p. 3/-  
ASK FOR BROCHURE No. 3.



New printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.

**BUILD YOURSELF A QUALITY RADIO**



Total cost £6.19.6, p.p. 6/6

Ask for Leaflet No. 1.

## SINCLAIR EQUIPMENT

Z30 75/-, each, stereo 60 £8-10-0, PZ5 79/6, PZ6 £6-19-6, Z50 £5-9-6, PZ8 £5-19-6.

**SPECIAL OFFER** 2 of Z30, stereo 60, PZ5 (usually £23-10) or with PZ6 in place of PZ5 **£19**

Complete range of amplifiers and preamplifiers in stock. All detailed in catalogue above.

## TEST EQUIPMENT FOR YOUR HOME



**AF105** 50k/v multimeter (illus.), price £8-10, p.p. 3/6, leather case 28/6  
**200H** 20k/v multimeter price £3-17-6, p.p. 3/-, case 12/6  
**TE20D** RF Generator (illus.), price £15, p.p. 7/6  
**TE22D** Matching Audio Generator, price £17, p.p. 7/6  
**TE65** Valve Voltmeter, price £17-10-0, p.p. 7/6  
Full details and complete range in catalogue



## SLIM POCKET TEST GEAR

- **SIGNAL INJECTOR** 35/- p.p. 1/6
- **SIGNAL TRACER** 29/6 p.p. 1/6

**NEW** WORLD'S LOWEST COST STEREO MAGNETIC CARTRIDGE O/P 7mV. 20 c/s-20 Kc/s. Diamond Stylus. Fits most decks. Recommended Price 79/6, p.p. 2/6.

## HI-FI equipment to suit EVERY POCKET



**FREE** Stock List No. 16/17 on request  
**BEST VALUE IN U.K.**

Choose from 100 complete stereo systems—Complete range of individual units also in stock. Demonstrations all day.

## 100 STEREO SYSTEMS

**LOW CASH AND CREDIT/HP**

**PRICES** (Credit terms from £30 purchase-callers only).



## HENRY'S LATEST CATALOGUE

New print. Now 350 pages.

- ★ **COMPONENTS, TEST GEAR**
- ★ **EQUIPMENT, MODULES**
- ★ **SPECIAL OFFERS ETC. ETC.**

Everything for the constructor  
Complete with 10/- value discount voucher for use with purchase. Price 7/6, p.p. 2/-

**WHY NOT SEND AWAY TODAY?**



## NEW 25watt and 50watt RMS SILICON AMPLIFIERS

**LOOK AT THE SPECIFICATIONS!**

- 0.3% Distortion at full power
- -1db 11c/s to 40kc/s at full power
- Response -1db 11c/s to 100kc/s


PA25 10 Silicon Thyristors Differential input, 25watts rms into 8ohms, 700mV input. Size only 5" x 3" x 2". 4-hole fixing.

Supplied with edge connector and harness.  
PA50 12-Transistor Version, 50watts rms into 3 to 4ohms MU442 Power supply for one or two PA25 or one PA50

● PA25 £7-10-0, ● PA50 £9-10-0, ● MU442 £6

**NEW! STEREO FET SELF POWERED PREAMPLIFIER**  
MODEL FET154

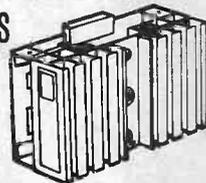Inputs for mag. Pickup, Tuner/Aux., Tape in and out. Response 20 c/s to 30kc/s. Output adjustable up to 1 volt. Mains operated stabilised supply. Slim design. Size 12" x 5½" x 1½". Price £16.10.0



## NO SOLDERING—JUST PLUG CONNECTORS

## YOU CAN SAVE 25% brand new GARRARD AND GOLDRING

(Post 7/6) COMPLETE LIST FREE ON REQUEST  
SP25mkII £11-9-6, AP75 £16-19-6, SL65B £14-19-6, SL72B £25 GL69 £22

**SPECIAL OFFER** Above with Sonotone 9tahc diam. Add £2, with magnetic add 70/-, with Goldring G800 add £7-10-0

Also Fitted with 9tahc diamond 2025TC £9-15-0, 3000LM £9-15-0

Plinths/Covers: Standard 99/6, p.p. 4/6. De Luxe £8-10-0, p.p. 6/-. SL72B type £8-10-0, p.p. 6/-. GL69 Type £9-15-0 p.p. 6/6.

● Goldring GL69 with plinth and cover and G800 cartridge (usually £51) £39.10.0, p.p. 12/6.



## SCOOP New ¼" TRACK TAPE DECKS

British made 3 speed mains operated tape machine. Fitted Marriott XRPS17 and XES11 ¼ track heads. Piano key operation. Designed for the home constructor. Operates with up to 7" spools vertically or horizontally. Size 13" x 10" x 5½".

**PRICE** £13-19-6, p.p. 10/6



## ELECTRONIC ORGANS

- ★ MODERN ALL BRITISH TRANSISTORISED DESIGNS AVAILABLE AS KITS OR READY BUILT
- ★ TEAK VENEERED CABINETS FOR ALL MODELS
- ★ 49 NOTE, 61 NOTE SINGLE MANUAL DESIGNS ALSO TWO MANUAL 49 NOTE
- ★ KITS AVAILABLE IN SECTIONS AS REQUIRED
- ★ HP and CREDIT SALE FACILITIES
- ★ **FREE 16-PAGE BROCHURE**

Covering organs in kit form and ready built—write or phone to ORGAN DEPT. Ask for Peter Elvins.



**HENRY'S RADIO LTD** **FOUR ELECTRONICS CENTRES** ALL WITHIN 100 YARDS  
303-309-354-356 EDGWARE ROAD LONDON W.2