

PRACTICAL WIRELESS

AUGUST
1971

20p

OTHER PROJECTS:-
DIRECT CONVERSION RECEIVER
L. F. BANDS TRANSMITTER

DW

T
TREASURE
T
TRACER

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

PRICE
£1.85



*Additional Stock Bits (illustrated) available

COPPER

B 38 — 3.2 mm CHISEL FACE

B 14 $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{3}{16}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{4}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{1}{8}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



ADCOLA PRODUCTS LTD.,
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 - Telegrams: Soljoint London Telex - Telex: Adcola London 21851

* Write for price list and catalogue

M. & B. COMPONENTS (LEEDS) LTD.

(INCORPORATING M. & B. RADIO)

PO Box 125, 38 BRIDGE END, LEEDS 1 Telephone 0532-35649

MB2/20A TWO METRE TRANSCEIVER Rx tuneable over 2 metre band. 20 watts RF output AM modulated. Ideal for mobile or fixed station, only requires connection to speaker, aerial and 12v DC supply to become fully operational (fuller details on list). **£50 inc. carr. U.K.**

AD 108D MARCONI COMMUNICATION RECEIVERS 9 miniature valves plus Xtal filter and tuneable BFO covering 20 to 510 Kc/s and 2 to 18.5 Mc/s in 4 switched bands. Slow motion dial with logging scale. Originally intended for 24 VDC operation but supplied with details for converting to mains operation in very clean tested condition. **£15.50 inc. carr. U.K.**

VHF FM/MW/LW TRANSISTOR RADIO PANELS Brand new panels. Baird model 298 (10 transistor) minus Vol and Tone controls, ferrite aerial and wavechange switch. **BARGAIN AT £2.15 inc. carr. U.K.**

6 to 12 VOLTS DC TRANSISTOR CONVERTOR Brand new 6 vdc input, 12 vdc output at 4 amps conservatively rated. Ideal VW owners. **£5.40 inc. carr. U.K.**

VHF AERIAL BASES. Brand new aerial base with provisions for tuning the Tx and Rx to the aerial independently. Contains 12v VHF aerial C/o relay. **£1.25 inc. carr. U.K.**

GEIGER COUNTERS Well known contamination meter comprised of main unit fitted with meter marked in Milli Rontgens/Hour probe lead and carrying case. Audio output available from socket on front panel. Supplied new or as-new condition. Model 1 fitted with vibrator P.S.U. using 4 pen cell batteries. **£4.85 inc. carr. U.K.**

12v INVERTER TRANSFORMERS complete with circuit to build inverter to give 350v output at 300 ma. **£2.20 inc. carr. U.K.**

ALL HEARSAY?

WE SAY:

THE STEREOPHONIC SOURCE SIMULATOR can effectively make the 'mono' facility redundant on a stereo amplifier. This solid-state device synthesises two distinctly different signals from a mono source to realistically simulate the stereo effect with music. For amplifiers with a tape-monitor facility, connection to the tape socket will allow operation from any selected mono source. Alternatively the unit may be connected in series with most programme sources. We provide a lead and 6 month guarantee. Send s.a.e. for further details stating amplifier.

A LEADING HI-FI JOURNAL SAYS:

"... the sample we have tried is beautifully made and carefully designed..." "Distortion is negligible and the noise-figure is excellent. Input impedance is very high, whilst the output impedance is sufficiently low to improve the noise-figure with some amplifiers." "... there is little doubt that on certain types of material the effect of this simulator is pleasing, never ludicrous and may well be judged worthwhile." *Hi-Fi News & Record Review (New Products section).*



A CUSTOMER SAYS: "I find that the simulator does all that is described in your advertisement. Mono transmissions have a new dimension. Reprocessed mono recordings are as good as some stereo recordings, and mono recordings played in simulated stereo offer more enjoyment in listening. I am thoroughly satisfied with the simulator." *Mr. W. J. C., Douglas, Isle of Man.*

ON DEMONSTRATION AT:


Audio T, Dryden Chambers, 119 Oxford Street, LONDON, W.1.
Norman H. Field Electronics, Vehicle & General House, Hurst Street, BIRMINGHAM.

Recommended retail price **£10** Stocked by good retailers, or obtainable direct. p. & p. 20p.

KAMPEL ELECTRONICS LTD.,

99 Old Christchurch Road, Bournemouth BH1 1EP.

NOW AVAILABLE SONY

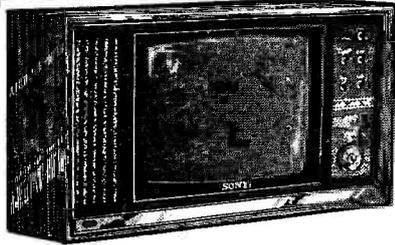

KV-132 13" COLOUR TELEVISION


This amazing value 13in. UHF colour TV is now available from Lasky's. Designed with the new TRINITRON tube to give you superb colour reproduction, sharper focusing with reliability and durability. Its light weight enables it to be moved from room to room with ease and like all Sony products it has solid state circuitry for trouble-free operation. Finished in a handsome teak cabinet 20in. x 13in. x 16in. Weight 39lbs. AC Mains. 240 volts.

COMPLETE with free Parabolic aerial valued at £6-00

**LASKY'S
PRICE ONLY
£199**

Post free U.K. only

DIGITAL CLOCK SCOOP!

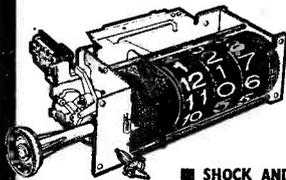

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR
- BUILT IN ALARM BUZZER

■ SHOCK AND VIBRATION PROOF

Exclusively from Lasky's in chassis form for you to mount in any housing you choose. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back of switch). SPEC.: 210/240V AC, 50Hz operation; switch rating 250V 3A. Complete with instructions.

HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS
LASKY'S PRICE £6-95 POST 18p SPECIAL QUOTATIONS FOR QUANTITIES

SENCOR CASSETTE RECORDER MODEL-S5002

This compact cassette recorder offers tremendous performance and value. Brief spec: 5 trans. circ., constant speed capstan drive, P.M. dyn. spk., economical operation on 4 x 1.5v batts. Features: Powerful volume. Built in auto. level control circ. assures perfect recording regardless of vol. control position. Handsome cabinet in stylish woodgrain with black plastic trim. Size: 8 1/2 x 5 1/2 x 2 1/2 in. Jack sockets for mic., earpiece. External 6v batt. pack or AC adaptor. Comp. with mic. earpiece, removable carrying strap and batts. and a free C-60 cassette.



LASKY'S PRICE £13-95 POST 25p

BSR McDONALD MP60

High precision low-mass counterbalanced pick up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.

LASKY'S PRICE £12-50 POST 35p

BSR McDONALD UNITS and PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

Model	A	B	C	D	E
610	£15-45	£18-75	£22-50	£24-50	£28-50
510	£13-45	£16-95	£20-75	£22-00	£26-00
310	£9-95	£13-45	£17-25	£21-00	£23-50
MP60	£12-50	£15-75	£19-50	£21-50	£25-50

GARRARD SL 55B Four-speed auto changer

LASKY'S PRICE £10-50 POST 35p

Garrard SP 25 Mk. III. £11-50

Garrard SP 25 Mk. III wired £12-00

Garrard SP 25 Mk. III with 9TA cart. £13-95

Garrard AP 76..... £20-95

Garrard 3000 with 9TA cart. £10-50

Garrard 2025TC with 9TA cart. £9-85

GARRARD PACKAGES

POST FOR ALL PACKAGES 50p.

Garrard AP 76 with AD 76K cart. and Lasky's plinth and cover..... £35-00

Garrard AP 76 with Shure M44E cart. and Lasky's plinth and cover £40-00

Garrard SP 25 Mk. III, AD 76K cart. and Lasky's plinth and cover..... £20-00

Garrard SP 25 Mk. III, Micro M 2100/e cart. and Lasky's plinth and cover £25-00

SONY TFM 8030L SCOOP!

High performance 11 transistor Battery/Mains portable

This top quality solid state receiver is now available from Lasky's at over 27% below the manufacturer's list price making it without doubt the SCOOP of 1971! Covers MW, LW and FM (VHF). 11 transistor circuit for high sensitivity and stability. Powerful output to sin. P.M. Dynamic speaker. AFC for drift free reception. Push button wavechange selectors and tone control. 3 power sources—9v batt. (PP9 or equiv.) household mains or car battery with adaptors. Dial light. External jacks for earphone, tape recording, external power input and car aerial. Padded leatherette cabinet, chrome trim, strong carrying handle. Tech. spec.: Freq. range: FM 87-108 MHz, LW 150-285KHz MW 530-1,605KHz. Circuit: 11 transistors, 7 diodes. Directional telescopic aerial for FM, internal ferrite bar for LW/MW 9 1/2(W) x 8(H) x 3 1/2(D). Comp. with earphone and batt.



LASKY'S PRICE £21-50 AC-90E AC adaptor £4-00; DCC-128 stabilised car battery cord £6-00. Post FREE if bought with radio.

INTERNATIONAL

MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in. Message tape, 150ft.	13p	5 1/2in. Long play, 1200ft. Mylar	75p
3in. Message tape, 225ft.	19p	5 1/2in. Triple play, 2400ft.	£1-75
3in. Message tape, 300ft.	38p	7in. Standard play, 1200ft.	63p
3 1/2in. Triple play, 600ft. Mylar	50p	7in. Acetate	63p
5in. Double play, 1200ft.	75p	7in. Standard play, 1200ft.	63p
5in. Long play, 900ft. Acetate	50p	7in. Mylar	98p
5in. Standard play 600ft.	40p	7in. Long play, 1800ft. Mylar	£1-25
5 1/2in. Double play, 1800ft. Mylar	£1-13	7in. Long play, 1800ft. Acetate	75p
5 1/2in. Long play 1200ft. Acetate	75p	7in. Standard play 900ft. PVC	63p
5 1/2in. Standard play 900ft. PVC	63p		

P. & P. 5p extra per reel. 4 reels and over Post Free. Special quotes for quantities


Lasky's COMPACT CASSETTES

C60 • C90 • C120

Exclusively made for us in USA Great Savings

	Each	Post	Five	Post	Ten	Post
C60	37p	5p	£1-65	20p	£5-95	25p
C90	57p	5p	£2-75	20p	£9-90	25p
C120	87p	5p	£3-75	20p	£12-10	25p

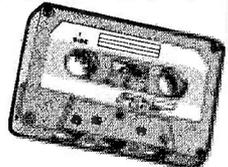U.S.A. Cassette head cleaner 53p. Post 5p



Lasky's Radio Ltd

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271
33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2655
Open all day 9.6m - 6p.m. Monday to Saturday
152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833
Open all day Thursday, early closing 1p.m. Saturday

The Home of High Fidelity
42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573
Open all day 9.6m - 6p.m. Monday to Saturday
NEW CITY BRANCH NOW OPEN
109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812
Open all day Thursday, early closing 1p.m. Saturday




ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN. Tel: 01-790 4821

FIND BURIED TREASURE WITH THIS
READY BUILT & TESTED

Treasure Locator Module

Only
£4.95
(99/-)

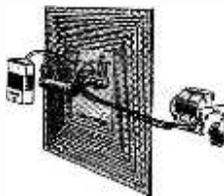

BRAND NEW FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and phones and it's working. But it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, wood, dirt, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC., ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! You could even pay for your holidays with two or three days electronic beachcombing—it's almost like having a licence to print money! Unclaimed treasure now exceeds the combined wealth of all nations. ORDER NOW WHILE PRESENT STOCKS LAST—TREMENDOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DESPATCHED IN STRICT ROTATION. SEND NOW £4.95 + 30p carr. (99/- + 6/-) etc. (High quality Danish Stethoscope headphones £2.75 (55/-) extra if required).


SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON



CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops!—a well known type of pink noise. A group of Dentists have experimented on patients with this pink noise—NO ANESTHETICS WERE USED! The noise ostensibly created a most definite reaction on these patients' nervous systems with the results that their pain systems were blocked. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—use this amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. TAKE IT ANYWHERE, pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost self-life) CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. NO soldering necessary. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc. etc. no soldering. Send only £2.25 + 25p (45/- + 5/-) p. & p. Parts available separately.)

GET A GOOD NIGHT'S SLEEP—EVERY NIGHT! INGENIOUS ELECTRONIC SLEEP INDUCER

only
£2.75
(55/-)

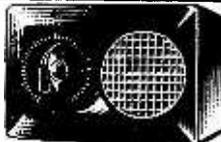

CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHE OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing and/or frequency sounds, continuously repeated—but as time goes on the sounds gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4 3/4" x 1 3/4"—take it anywhere. All parts including case, loudspeaker, components, nuts, wire, screws, etc. etc. THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2.75 + 25p (55/- + 5/-) p. & p. (parts available separately).

REAL WORKING ELECTRONIC ORGAN



ONLY
£2.75
(55/-)

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorized—no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13 1/2 x 10 x 2 1/2". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER. No soldering necessary. It really is as simple as a.b.c. to make, step-by-step, easily in one short evening following the fully illustrated, MENT at our low, low building price. ONLY £2.75 (55/-) + 30p (4/6) p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc. etc. Use standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.


SHORTWAVE TRANSISTOR RADIO Can be built in one evening



ONLY
£2.25
(45/-)

At last! After trying countless circuits searching for easy build, work first-time short waver. Giving advanced world-wide performance, we chose this "Sky Room". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorised (no valves). Size only 3" x 4 1/4" x 1 1/4". As tremendous demand anticipated price held to only £2.25 (40/-) + 17p (3/6) p. & p. for all parts incl. Cabinet, screws, instructions etc. (Part available separately).

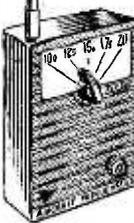EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT V.H.F. AIRCRAFT BAND CONVERTER



ONLY
£2.37
(47/6)

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross-talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve racking decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON RINGWAY, PRESTWICK ETC., ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. Our design team built four—everyone worked first time. NO knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio—(even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN, SEND NOW, ONLY £2.37 (47/6) + 23p (4/6) p. & p. for all parts, including case, nuts, screws, wire, etc., etc. (parts available separately).

BUILD 5 RADIO AND ELECTRONIC PROJECTS



TOTAL BUILDING PRICE
£1.97
(39/6)

Amazing Radio Construction set! Become a radio expert for £1.97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated Step-by-step plans, all Transistors, loudspeaker, phone, knobs, screws, etc., all you need. Presentation Box 37p (7/6) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only £1.97 (39/6) + 23p (4/6) p. & p.

FIND BURIED TREASURE! TREASURE LOCATOR TRANSISTORISED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses



ONLY
£2.37
(47/6)


any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAB SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC. Outdoors or indoors. Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is easy as A.B.C. transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 1/2" x 10" x 2 1/2". Great demand expected at this remarkably low price—ORDER WHILE PRESENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc. etc. ONLY £2.37 (47/6) + 27p (5/6) p. & p. (Sectional handle as illustrated 75p (15/-) extra). Parts available separately. Made up looks worth £15!

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

CONCORD ELECTRONICS LTD (Dept. PW22) 8 Westbourne Grove, London W.2.
(STAFF WANTED FOR ALL DEPARTMENTS) (Nr Bayswater & Queensway Tubes, 1 minute ABC Cinema) Callers Welcome 9 a.m.-6 p.m. inc. Saturday

28watts, r.m.s. 40Hz to 40kHz ± 3dB

There are two stereo amplifiers — the RT100 for ceramic Cartridges, the RT101 for magnetic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket for headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

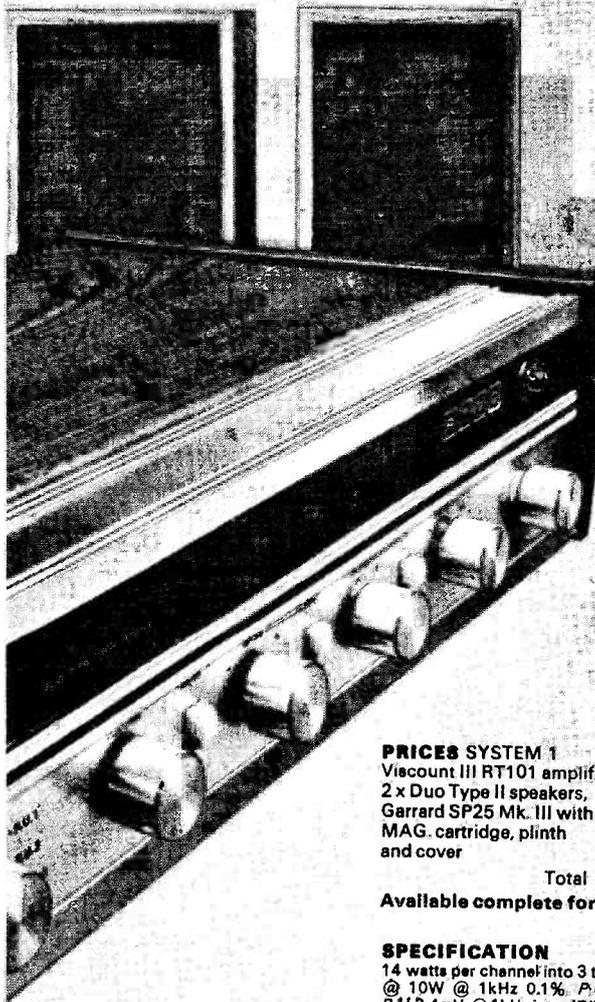

Viscount III Audio Suite complete £49

PRICES SYSTEM 1

Viscount III RT101 amplifier £22.00 + 90p p&p
 2 x Duo Type II speakers, £14.00 + £2 p&p
 Garrard SP25 Mk. III with
 MAG. cartridge, plinth
 and cover

£23.00 + £1 p&p
 Total £59.00

Available complete for only £62.00 + £2.50 p&p

SPECIFICATION

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 150mV into 3 Meg. P.U.2 4mV @ 1kHz into 47K. equalised within ±1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities: headphone socket, power out 250 mW per channel. Tone controls and filter characteristics. Bass: +12 dB to -17 dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12 dB to -12 dB @ 15 kHz. Treble filter: 12 dB per octave. Signal to noise ratio: (all controls at max) RT101 - P.U.1. & radio - 65dB, P.U.2 - 58 dB. RT100 same as RT101 but P.U.2. 450 mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics 26dB on all inputs. Size 13 1/2" x 9" x 3 1/2"

SYSTEM 2

As System 1, but with 2 x Duo Type III speakers at pair £32.00 + £3 p&p
 Available complete for £69 + £4 p&p

SYSTEM

Viscount III Amplifier RT100 £17.00 + 90p p&p
 2 x Duo Type II speakers, pair £14.00 + £2 p&p
 Garrard SP25 Mk. III with CER. diamond
 cartridge, plinth and cover £21.00 + £1 p&p
 Total £52.00

Available complete for only £49.00 + £2.50 p&p

SPEAKERS Duo Type II


Size 17" x 10 1/2" x 6 1/2". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 3 ohms. Teak veneer cabinet. £14 pair + £2 p&p.
 Duo Type III Size 23 1/2" x 11 1/2" x 9 1/2". Drive unit 13 1/2" x 8 1/2" with H.F. speaker. Max. power 20 watts at 3 ohms. Frequency range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

Radio and TV Components (Acton) Ltd. 21c High Street, Acton, London W3 6NG
 323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.

R+TV

SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

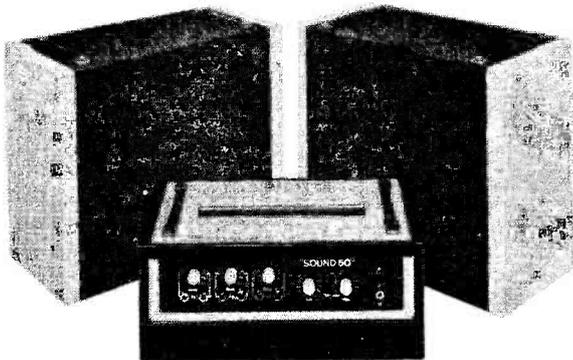

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power: 45 watts R.M.S. (Sine wave drive). **Frequency response:** —3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB.

Speaker Impedance: 3, 8 or 15 ohms. **Bass Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 KHz. **Inputs:** 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

SPEAKERS! Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

COMPLETE SYSTEM £50 Plus £4 P. & P.
Sound 50 amp and 2 speakers

or available separately.

Amplifier £28.50 plus £1.50 P. & P.
Speakers £12.50 each plus £1.75 P. & P.

TOURIST


MARK 3

CAR RADIO

ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

See previous page for address

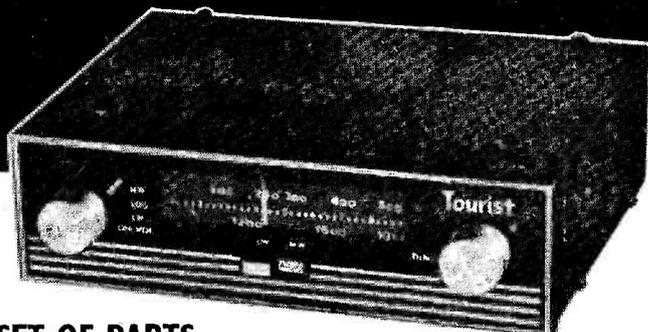

SET OF PARTS

£6.30

plus P. & P. 50p.

Circuit diagram 13p. Free with parts


Speaker, baffle and fixing kit

£1.25 extra plus 25p. p. & p.

Postage free when ordered with parts.

THE ELEGANT SEVEN Mk. III

(350m W Output)

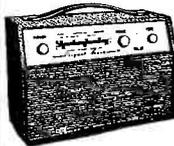


7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 75p extra.

Price **£5.25** plus 50p. P. & P.

Circuit 13p **FREE WITH PARTS.**


THE DORSET (600m W Output)

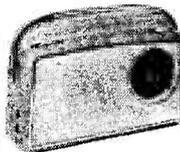

7-transistor fully tunable M.W.—L.W. superhet portable. Set of parts. The latest modulated and pre-alignment techniques make this simple to build. Sizes: 12 x 8 x 3in.

Price **£5.25** plus 50p P. & P.

Circuit 13p **FREE WITH PARTS**

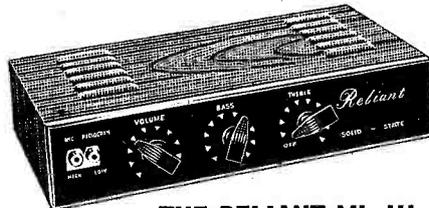

THE RELIANT Mk III SOLID-STATE GENERAL PURPOSE AMPLIFIER

in simulated teak case **£7.25** plus P. & P. 50p

SPECIFICATIONS

Output 10 watts.

Output impedance—3 to 4 ohms.
Input 1. -xtal mic 10mV Tone Controls—Treble control range ± 12dB at 10KHz. 2. -gram/radio 250mV. Bass control range ± 13dB at 100Hz.

Frequency Response—(with tone controls central) Minus 3dB points at 20Hz and 40KHz. Signal to Noise Ratio—better than —60dB. Transistors—4 silicon Planar type and 3 Germanium type. Mains input—220/250V. A.C. Size of chassis—10½in. x 4½in. x 2½in. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Built and tested.

RADIO & TV COMPONENTS
R+TV
(ACTON) LIMITED



COMMUNICATION RECEIVERS from the U.S.A. The leaders in specialist radios UNIQUE in VHF frequencies


UNSURPASSED in performance & styling
 They NOT ONLY receive Aircraft, Shipping (VHF and SW), Taxis, Ambulances, Fire Service, T.V. Sound, Hams, Gas, Electric and Water Boards, Public Services and many other Commercial and Industrial Radio. Telephone mobile transmissions . . .

BUT ALSO Classical Music, Pop and All That Jazz !!!
TURN ON TO INSTANT SOUND . . . These are Communications receivers and unique entertainment sources in one neat, transistorised portable package. They keep exciting Aircraft, Shipping, RT mobiles plus Medium Wave, FM National and Local broadcasts at your fingertips. Both are extremely reliable and feature large powerful PM dynamic wide range speakers, switchable AFC to prevent FM drift, tone control, dial lighting, sensitive swivel telescopic VHF and rod aerial, precise slide rule vernier tuning, external aerial and earphone sockets (cuts off speaker for private listening). Earpiece supplied. Operate from standard batteries or mains.

BUY DIRECT AT PRICES 15% BELOW RETAIL VALUES

MODEL MPR 3005 5 BAND

MODEL MPR 3016 6 BAND

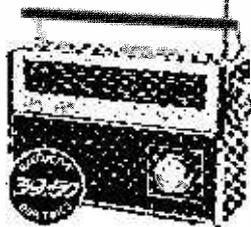

MEDIUM WAVE 530—1605Kcs
 MARINE 1.4—4.6Mc
 FM/VHF 87—108Mc
 AIRCRAFT VHF 108—136Mc
 HIGH VHF/PB 146—176Mc
 Batts. incl. Plus 6 2 1/2 P/P

Impressive finish in Walnut with deep Chrome die-cast side panels and grained inserts. Trimmed with brushed Aluminium and black speaker grille. Log scale for easy tuning. Size 9 3/4" x 12" x 4 1/2". Wt. 5 3/8 lbs. approx.



SAME BANDS & FREQUENCIES AS MODEL MPR 3005 PLUS ADDED FEATURE OF SW 5.0—12.0Mc (with Fine Tuner). Batts. incl. Plus 6 2 1/2 P/P

Styled in elegant black case with luxury Chrome trim, soft padded speaker grille, die-cast sides and walnut insert. Size 8 1/2" x 11" x 3 3/4". Wt. 5 lbs. approx.

EARPIECE SUPPLIED WITH BOTH MODELS

T.V.SOUND The latest in contemporary U.S.A. innovation
HEAR T.V. SOUND
 All channels 2-13. Also UHF (many areas) and RT mobiles

MODEL MPR 3073. THE FIRST IN T.V. SOUND PORTABLES.

Sensitive swivel telescopic aerial receives LOCAL AND DISTANT TV TRANSMISSIONS. PLUS FULL MEDIUM WAVE AND VHF/FM BANDS TO RECEIVE YOUR USUAL NATIONAL AND LOCAL RADIO STATIONS. This unique model has stylish leatherette trim, handsome walnut grain inserts and smart chrome trim. 22 transistor/diode superhet circuit. AFC, AGC, Tone Control, Slide rule tuning. Works from standard batteries or mains. Earpiece supplied for private listening. Log scale for easy tuning.



Plus 50p P/P. Batts. incl.
 BANDS:
 MW 535—1605Kcs
 FM/VHF 88—108Mc
 TV 1.58—88Mc
 TV 2.175—218Mc

STOCKTON PARTNERS

(Dept PW), Importers & Distributors, Brighowgate, Grimsby. Tel: 0472 64196/58815. Suppliers to Government Depts., Industry, Radio, TV, Press, etc.

VALVES

**SAME DAY SERVICE
 NEW! TESTED! GUARANTEED!**

SETS 1R5, 1R5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1.02, DAF96, DF96, DK96, DL96, 4 for £1.48.


1R5	-88	25U4GT	-57	DL96	-38	EL500	-62	PCL82	-86	UABC80	-83
1S6	-22	30C1	-30	DY86	-28	EM81	-41	PCL84	-37	UAC42	-51
1T4	-16	30C15	-63	DY87	-28	EM81	-41	PCL84	-37	UAC42	-51
3S4	-28	30C17	-80	DY802	-40	EM84	-33	PCL85	-45	UBF80	-34
3V4	-37	30C18	-67	EABC80	-32	EM87	-37	PCL86	-41	UBF89	-38
5V4G	-26	30F5	-76	EAF42	-50	EY51	-38	PCL88	-72	UCC84	-35
5V4G	-37	30FL1	-63	EB41	-40	EY86	-32	PCL800	-77	UCC85	-36
5Y9GT	-30	30FL12	-72	EB91	-11	EZ40	-43	PEN44	-42	UCF80	-36
EZ4G	-37	30FL14	-72	EB93	-40	EZ41	-43	PEN6C	-70	UCH42	-62
6/80L2	-58	30L1	-32	EBC41	-54	EZ80	-22	PFL200	-58	UCH81	-32
6AL5	-11	30L15	-62	EBC90	-22	EZ81	-24	PL36	-49	UCL82	-35
6AM6	-13	30L17	-73	EBF80	-33	GZ30	-37	PL81	-48	UCL83	-55
6A05	-26	30P4	-65	EBF89	-31	GZ32	-43	PL81A	-51	UF41	-56
6AT6	-22	30P12	-77	EOC81	-18	GZ34	-50	PL82	-35	UF89	-38
6AU6	-23	30P19	-65	ECC82	-23	KT41	-77	PL85	-35	UL41	-60
6BA6	-22	30P11	-83	ECC83	-35	KT61	-55	PL84	-33	UL44	£1.00
6BE6	-23	30P113	-85	ECC85	-28	KT66	-83	PL500	-65	UL84	-85
6BJ6	-42	30P114	-70	ECC804	-60	LN319	-63	PL504	-67	UM84	-22
6BW7	-60	30P115	-90	ECF80	-30	LN329	-72	PM84	-37	UY41	-41
6CD9G	£1.10	30L6GT	-45	ECF82	-30	LN389	-63	PX25	£1.17	UY85	-28
6E14	-45	3S4	-28	ECH35	-30	N78	-87	PY32	-55	VP4B	-77
6E28	-71	35Z4GT	-67	ECH42	-63	P61	-50	PY33	-55	Z77	-22
6E25	-62	807	-45	ECH81	-29	PABC80	-35	PY81	-27	Transistors	
6K7G	-12	6063	-62	ECH83	-41	PC86	-51	PY82	-27	ACI07	-17
6K8G	-17	AC/VP2	-77	ECH84	-37	PC88	-51	PY83	-28	ACI27	-18
6Q7G	-28	B349	-65	ECL80	-35	PC96	-42	PY88	-35	AD140	-37
6AT6	-22	30P12	-77	EOC81	-18	GZ34	-50	PL82	-35	UF89	-38
6AU6	-23	30P19	-65	ECC82	-23	KT41	-77	PL85	-35	UL41	-60
6BA6	-22	30P11	-83	ECC83	-35	KT61	-55	PL84	-33	UL44	£1.00
6BE6	-23	30P113	-85	ECC85	-28	KT66	-83	PL500	-65	UL84	-85
6BJ6	-42	30P114	-70	ECC804	-60	LN319	-63	PL504	-67	UM84	-22
6BW7	-60	30P115	-90	ECF80	-30	LN329	-72	PM84	-37	UY41	-41
6CD9G	£1.10	30L6GT	-45	ECF82	-30	LN389	-63	PX25	£1.17	UY85	-28
6E14	-45	3S4	-28	ECH35	-30	N78	-87	PY32	-55	VP4B	-77
6E28	-71	35Z4GT	-67	ECH42	-63	P61	-50	PY33	-55	Z77	-22
6E25	-62	807	-45	ECH81	-29	PABC80	-35	PY81	-27	Transistors	
6K7G	-12	6063	-62	ECH83	-41	PC86	-51	PY82	-27	ACI07	-17
6K8G	-17	AC/VP2	-77	ECH84	-37	PC88	-51	PY83	-28	ACI27	-18
6Q7G	-28	B349	-65	ECL80	-35	PC96	-42	PY88	-35	AD140	-37
6AT6	-22	30P12	-77	EOC81	-18	GZ34	-50	PL82	-35	UF89	-38
6AU6	-23	30P19	-65	ECC82	-23	KT41	-77	PL85	-35	UL41	-60
6BA6	-22	30P11	-83	ECC83	-35	KT61	-55	PL84	-33	UL44	£1.00
6BE6	-23	30P113	-85	ECC85	-28	KT66	-83	PL500	-65	UL84	-85
6BJ6	-42	30P114	-70	ECC804	-60	LN319	-63	PL504	-67	UM84	-22
6BW7	-60	30P115	-90	ECF80	-30	LN329	-72	PM84	-37	UY41	-41
6CD9G	£1.10	30L6GT	-45	ECF82	-30	LN389	-63	PX25	£1.17	UY85	-28
6E14	-45	3S4	-28	ECH35	-30	N78	-87	PY32	-55	VP4B	-77
6E28	-71	35Z4GT	-67	ECH42	-63	P61	-50	PY33	-55	Z77	-22
6E25	-62	807	-45	ECH81	-29	PABC80	-35	PY81	-27	Transistors	
6K7G	-12	6063	-62	ECH83	-41	PC86	-51	PY82	-27	ACI07	-17
6K8G	-17	AC/VP2	-77	ECH84	-37	PC88	-51	PY83	-28	ACI27	-18
6Q7G	-28	B349	-65	ECL80	-35	PC96	-42	PY88	-35	AD140	-37
6AT6	-22	30P12	-77	EOC81	-18	GZ34	-50	PL82	-35	UF89	-38
6AU6	-23	30P19	-65	ECC82	-23	KT41	-77	PL85	-35	UL41	-60
6BA6	-22	30P11	-83	ECC83	-35	KT61	-55	PL84	-33	UL44	£1.00
6BE6	-23	30P113	-85	ECC85	-28	KT66	-83	PL500	-65	UL84	-85
6BJ6	-42	30P114	-70	ECC804	-60	LN319	-63	PL504	-67	UM84	-22
6BW7	-60	30P115	-90	ECF80	-30	LN329	-72	PM84	-37	UY41	-41
6CD9G	£1.10	30L6GT	-45	ECF82	-30	LN389	-63	PX25	£1.17	UY85	-28
6E14	-45	3S4	-28	ECH35	-30	N78	-87	PY32	-55	VP4B	-77
6E28	-71	35Z4GT	-67	ECH42	-63	P61	-50	PY33	-55	Z77	-22
6E25	-62	807	-45	ECH81	-29	PABC80	-35	PY81	-27	Transistors	
6K7G	-12	6063	-62	ECH83	-41	PC86	-51	PY82	-27	ACI07	-17
6K8G	-17	AC/VP2	-77	ECH84	-37	PC88	-51	PY83	-28	ACI27	-18
6Q7G	-28	B349	-65	ECL80	-35	PC96	-42	PY88	-35	AD140	-37
6AT6	-22	30P12	-77	EOC81	-18	GZ34	-50	PL82	-35	UF89	-38
6AU6	-23	30P19	-65	ECC82	-23	KT41	-77	PL85	-35	UL41	-60
6BA6	-22	30P11	-83	ECC83	-35	KT61	-55	PL84	-33	UL44	£1.00
6BE6	-23	30P113	-85	ECC85	-28	KT66	-83	PL500	-65	UL84	-85
6BJ6	-42	30P114	-70	ECC804	-60	LN319	-63	PL504	-67	UM84	-22
6BW7	-60	30P115	-90	ECF80	-30	LN329	-72	PM84	-37	UY41	-41
6CD9G	£1.10	30L6GT	-45	ECF82	-30	LN389	-63	PX25	£1.17	UY85	-28
6E14	-45	3S4	-28	ECH35	-30	N78	-87	PY32	-55	VP4B	-77
6E28	-71	35Z4GT	-67	ECH42	-63	P61	-50	PY33	-55	Z77	-22
6E25	-62	807	-45	ECH81	-29	PABC80	-35	PY81	-27	Transistors	
6K7G	-12	6063	-62	ECH83	-41	PC86	-51	PY82	-27	ACI07	-17
6K8G	-17	AC/VP2	-77	ECH84	-37						

Discosound

P. A. AND DISCOTHEQUE EQUIPMENT

— A COMPREHENSIVE RANGE COVERING EVERY REQUIREMENT

AMPLIFIERS, MIXERS, LIGHT CONTROL UNITS.

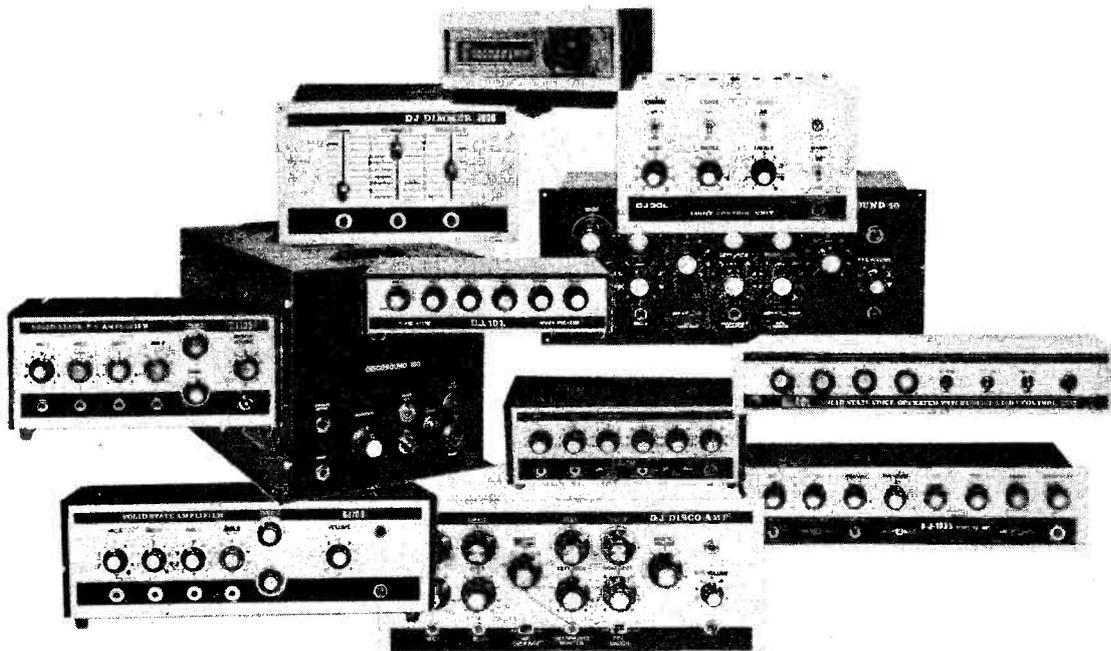

D.J. 102 Discotheque Mixer Pre-Amplifier

4 inputs each with its own volume control plus master volume control, PFL monitoring and mic override switches.

Size 10 $\frac{1}{2}$ " x 4".
Suggested Retail Price £25-00

D.J. 105S P.A. Amplifier

4 channel mixing facilities each with separate inputs and volume controls 30 watts r.m.s. power output A.C. Mains 200/250v A.C. Size 11 $\frac{1}{2}$ " x 5" x 6".

Suggested Retail Price £41-00

D.J. 70S Integrated Mixer Amplifier

Power output 70 watts r.m.s. 4 channel mixer with separate inputs and volume controls, plus master volume and separate bass and treble controls.

Size 15 $\frac{1}{2}$ " x 5" x 6".
Suggested Retail Price £83-00

D.J. Disco-Amp

Designed specifically for use with discotheques. Power output 100 watts r.m.s. Two mike inputs and two gram inputs, with independent volume controls plus bass and treble controls. Incorporates many exclusive features.

Front panel size 16 $\frac{1}{2}$ " x 7".
Suggested Retail Price £85-00

D.J. 101 Mixer Pre-Amplifier

Six inputs allow full mixing facilities for all types of equipment. 9v battery operation. Size 10 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ ".

Suggested Retail Price £14-00

Discosound 40 Discotheque Pre-Amplifier

Features independent inputs and volume controls for two microphones and two turntables plus separate bass, treble and master volume controls. Self powered and ideal for use with Discosound 100 Power Amplifier (is capable of running 10 of these power amplifiers—total 1000 watts)

Front panel size 16 $\frac{1}{2}$ " x 7".
Suggested Retail Price £40-00

Discosound 100 Power Amplifier

100 watts r.m.s. power amplifier (at 8 ohms) utilising all silicon transistors and features full automatic overload against short or open circuits. Frequency response 20-20,000 Hz \pm 3db. Distortion less than 1% at 70 watts r.m.s. \pm 1db.

Size 10 $\frac{1}{2}$ " x 8" x 7".
Suggested Retail Price £49-50

D.J. 103S Stereo Pre-Amplifier

A high quality stereo discotheque pre-amp unit. Incorporating two microphone and two turntable inputs each with independent volume control, plus bass, treble, balance and master volume control. Offers full mixing and monitoring facilities.

Front panel size 16 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ ".
Suggested Retail Price £49-50

D.J. 30L Psychedelic Light Control Unit

3 channel light unit enabling base, middle and treble frequencies from the amplifier to be operated individually. Handles 1000 watts per channel.

Front panel size 10" x 6".
Suggested Retail Price £37-50

D.J. 40L Sound Operated 3 Channel Light Unit

Features built-in microphone which eliminates the need for connections to any amplifier or sound source.

Handles 1000 watts per channel.
Suggested Retail Price £58-25

D.J. DIMMER 3000

3 channel light dimmer unit offered in two versions: Dimmer 3000—a straight three channel dimmer unit with mains input and three light outputs.

Dimmer 3000S—for use in conjunction with D.J. 30L Light Control unit only and has three mains inputs and three light outputs. Front Panel size 10" x 6".

Suggested Retail Price £32-50

Discosound Disco-Wheel

A projector designed to project a range of liquid wheels and colour change wheels for special lighting effects, adding colour and variety to any form of entertainment.

Size 7 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ ".
Suggested Retail Price £50-00

A range of complete Discotheques with matching Speakers also available.

DISCOSOUND PRODUCTS ARE GUARANTEED FOR 12 MONTHS

For full details of the Discosound range of products call at or write to your nearest Discotheque Centre — Demonstrations given at any time.

DISCOSOUND

122 Balls Pond Road, London N.1. Tel: 01-254 5779

HENRY'S RADIO LTD.,

309 Edgware Road, London W.2. Tel: 01-723 6963

AUDIO SUPPLIES

SLASH PRICES! UP TO 60%



SUPERB PLINTHS & COVERS £3:50

50p P.P. for Garrard and B.S.R. SP25, SL65B 3500, 3000, 2025TC, 2000, 1025, 5100, AT6, AT60, 40B, B.S.R. McDonald range. All decks are finished in teak polish and will blend in any modern home. The covers are of tinted Perspex (please state deck when ordering).

SUPERIOR PLINTHS AND COVERS FOR GARRARD AP75, AP76, SL72B, SL75B and SL95B, £4.99. P.P. 60p (R.R.P. £9.50)

FOR ALL YOUR NEEDS IN HI-FI EQUIPMENT SEND A LARGE S.A.E. or PAY A VISIT TO OUR 3-STORY WAREHOUSE

SPECIAL OFFER

GARRARD SP25 Mk. III GOLDRING G800H Superb Plinth and Cover. SINGLAIR Project 60—Stereo 60 Pre-Amplifier and Control Unit. 2. 23P's and P25. 2 WHARFEDALE Unit 3. List Price £82.31. OUR PRICE £55. P. & P. £1.75.

TURNTABLES P.P. 60p

Garrard SP25 Mk. III	£10.97
Garrard 2025TC with Sonotone 9TAHC Cartridge	£8.75
Garrard A70 Mk. II	£10.97
Garrard SL65B	£12.75
Garrard AP76	£18.75
Garrard SL72B	£25
Garrard SL75B	£27.75
Garrard 401	£27.50
Garrard SL95B	£34
Goldring GL75P	£35
Goldring GL75	£28.50

TURNTABLES (continued)

Goldring GL69	£21
Thorens TD125	£62
Thorens TD150AB/2	£38
Pioneer PL11AC complete	£39
Dual 1219	£49
Dual 1209	£34
Philips 202A	£54.00

CARTRIDGES P.P. 12p.

Goldring G850	£4.20
Goldring G800H	£6
Goldring G800	£7
Goldring G800/E	£11
Goldring G800/SE	£16
Sonotone 9TAHCD	£1.75
Shure M3D	£4.95
Shure M44E	£8.50
Shure M75E	£15
Shure M55E	£9.20
Shure M445/7	£7.20
SMC101	£3.25
MC15	£5
AT66 5/7 LC/HC	£4.70
ADC 10E Mk. 2	£27

TAPES

PHILIPS, BASF, SCOTCH, ETC. BIG DISCOUNTS. SEND FOR LIST.

Open 9.30 a.m. to 7 p.m. Monday to Wednesday; half day Thursday until 1 p.m.; late night Friday until 8 p.m.; Saturday 9.30 a.m. to 6 p.m.

2 Showrooms devoted to specially selected systems.


EASY TO FIND—50 YARDS FROM (B.R.) STOKE NEWINGTON STN. 67, 149, 247, 73, 76, 243 Buses Pass our door.

AUDIO SUPPLIES

PW8, 50 STAMFORD HILL, LONDON, N.16.

Telephone: 01-806 3611

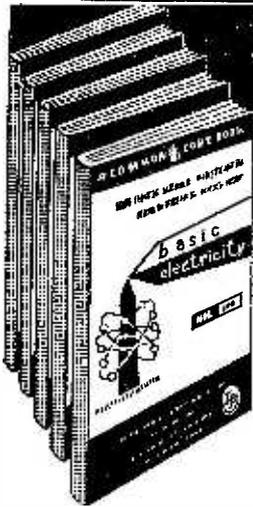PERSONAL CALLERS PLEASE NOTE—Cheques are only accepted when accompanied by a Bank Cheque Card (not Barclay Card).



YOURS FREE FOR 7 DAYS

The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

This carefully planned series of manuals has proved a valuable course in training technicians in Electricity, Electronics, Radio and Telecommunications.

WHAT READERS SAY

"READABLE AND INTERESTING"

The Manuals are so readable and interesting that I do not think this magazine does full justice to the wonderful contents.

S.T.P., Bangor.

"REAL HELP"

I find the Basic Manuals the best in their class and a real help in my work in phototype electronics.

C.L.P., Cardiff.

"FIRMEST RECOMMENDATION"

You have my firmest recommendation in favour of this method of Self Teaching.

B.W., Blackburn.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY** £4.50 Cash Price, or Down Payment of £1.00 followed by 4 fortnightly payments of £1.00 each. Total £5.00. **BASIC ELECTRONICS** £5.40 Cash Price, or Down Payment of £1.00 followed by 5 fortnightly payments £1.00 each. Total £6.00. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY **BASIC ELECTRONICS**

Prices include Postage and Packing.

Signature

(If under 21 signature required of parent or guardian)

NAME

BLOCK LETTERS

FULL POSTAL

ADDRESS

POST NOW FOR THIS OFFER!!

A TECH-PRESS PUBLICATION

TRANSISTORS

NEW LIST—NEW PRICES
SEND FOR FREE COPY TODAY
Brand New Fully Guaranteed

2N404 80p	BC107 12p	BYZ13 25p
2N695 15p	BC108 12p	BYZ16L1-00
2N697 15p	BC109 12p	GET980 87p
2N706 10p	BC113 12p	MA100 85p
2N708A 25p	BC114 12p	MAT101 25p
2N930 25p	BC115 20p	MAT120 25p
2N1131 25p	BC116 25p	MAT121 30p
2N1132 25p	BC116A 30p	MJ2801A1-37
2N1302 20p	BC118 25p	MJ2901A1-25
2N1303 20p	BC119 35p	MJE870 97p
2N1304 25p	BC124 25p	MJE820 87p
2N1305 25p	BC135 20p	MJE2845
2N1306 25p	BC136 22p	
2N1307 25p	BC137 25p	MJE805587p
2N1308 25p	BC138 25p	MFF102 42p
2N1309 25p	BC147 17p	MFF103 35p
2N1613 22p	BC148 12p	MFF104 37p
2N1247 70p	BC149 20p	MFF105 40p
2N210 60p	BC150 20p	NKT217 40p
2N2180 20p	BC157 20p	NKT277 20p
2N2210 20p	BC158 17p	NKT408 75p
2N2219 20p	BC159 20p	NKT40462p
2N2222 20p	BC160C 15p	OA5 20p
2N2222A25p	BC177 25p	OA9 10p
2N2369 20p	BC178 25p	OA10 10p
2N2374 35p	BC182 12p	OA17 10p
2N2646 50p	BC182L 12p	OA70 10p
2N2904 20p	BC183L 12p	OA73 10p
2N2904A25p	BC184L 15p	OA79 10p
2N2905 25p	BC212 12p	OA81 10p
2N2906 20p	BCY30 25p	OA85 12p
2N2906A25p	BCY2 30p	OA90 10p
2N2907 20p	BCY32 50p	OA91 7p
2N2926 10p	BCY33 25p	OA95 7p
2N3011 25p	BCY34 30p	OA200 7p
2N3065 20p	BCY38 40p	OA202 10p
2N3064 50p	BCY39 85p	OC16 50p
2N3065 75p	BCY40 50p	OC20 70p
2N355 21-10	BD125 50p	OC22 50p
2N3702 10p	BCY69 25p	OC23 80p
2N3703 10p	BCY70 15p	OC24 60p
2N3704 15p	BCY71 20p	OC25 37p
2N3705 15p	BCY72 15p	OC26 25p
2N3707 15p	BCY78 30p	OC28 60p
2N3709 10p	BCY79 30p	OC29 50p
2N3710 10p	BCZ10 35p	OC35 85p
2N3711 10p	BCZ11 45p	OC36 60p
2N3819 35p	BD112 60p	OC41 25p
2N3820 60p	BD121 65p	OC42 30p
2N4058 15p	BD123 80p	OC43 40p
2N4061 15p	BD124 75p	OC44 17p
2N4457 35p	BD125 50p	OC45 15p
2N6458 37p	BD131 75p	OC70 15p
2N6549 50p	BD132 85p	OC71 15p
2B301 50p	BD153 62p	OC72 25p
2B302 50p	RD156 57p	OC73 30p
2B303 60p	BDY1041-25	OC74 30p
2B304 75p	BDY1121-62	OC75 35p
40250 50p	BDY1141-50	OC76 25p
40361 50p	BDY1821-75	OC77 40p
40362 50p	BDY1941-97	OC81 25p
AA Y30 10p	BDY6121-25	OC82 25p
AA Y42 15p	BDY6221-00	OC83 25p
AA Z13 12p	BF115 25p	OC84 25p
AA Z17 10p	BF152 30p	OC89 25p
AC107 87p	BF153 30p	OC140 87p
AC126 25p	BF158 30p	OC141 62p
AC127 25p	BF159 60p	OC170 25p
AC128 25p	BF167 25p	OC171 30p
AC176 25p	BF170 35p	OC200 40p
AC187 30p	BF171 30p	OC301 70p
AC188 30p	BF177 40p	OC302 80p
ACY17 30p	BF178 25p	OC203 40p
ACY18 25p	BF179 40p	OC204 40p
ACY19 25p	BF180 35p	OC205 75p
ACY20 20p	BF181 35p	OC206 75p
ACY21 20p	BF182 30p	OC207 75p
ACY22 10p	BF184 30p	OC271 97p
ACY39 50p	BF185 20p	ORP12 50p
AD140 50p	BF194 17p	ORP60 40p
AD149 50p	BF195 15p	ORP61 42p
AD181 37p	BF196 15p	TIP23A 80p
AD182 37p	BF197 15p	TIP30 60p
AF114 25p	BF200 37p	TIP31A 75p
AF115 25p	BF204 37p	TIP32A 82p
AF116 25p	BFX13 25p	TIP33A
AF117 25p	BFX29 25p	TIP34A
AF118 62p	BFX37 25p	
AF124 25p	BFX84 25p	
AF125 20p	BFX85 25p	
AF126 17p	BFX86 25p	
AF127 17p	BFX87 25p	
AF139 30p	BFX88 20p	
AF178 47p	BFY18 80p	
AF179 85p	BFY50 82p	
AF180 52p	BFY51 20p	
AF181 42p	BFY52 20p	
AF186 40p	BFY53 17p	
AF230 40p	BFY90 65p	
AS Y26 25p	BX200 15p	
AS Y27 32p	BX221 60p	
AS Y28 25p	BX236 15p	
AS Y29 30p	BX237 15p	
AS Y67 47p	BY95A 15p	
AS Z21 42p	BY100 15p	
BA116 7p	BY126 15p	
BA164 10p	BY127 20p	
BA X13 6p	BY182 85p	
BA X16 7p	BY210 40p	
BA X31 7p	BY211 35p	
BA Y38 17p	BY212 30p	

HENRY'S LOW COST INTEGRATED CIRCUITS

WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW FULL SPECIFICATION LOW COST TTL 7400 RANGE OF INTEGRATED CIRCUITS

Part No.	Ceramic	Description	1-24	25-99	100	250+
7400		Quadruple 2-input NAND Gate	20p	15p	13p	13p
7401		Quadruple 2-input Positive NAND Gate (with open collector output)	23p	20p	15p	13p
7402		Quadruple 2-input Positive NOR Gates	23p	20p	15p	13p
7403		Quadruple 2-input Positive NAND Gates (with open collector output)	23p	20p	15p	13p
7404		Hex Inverters	23p	20p	15p	13p
7405		Hex Inverter with open collector	23p	20p	15p	13p
7410		Triple 3-input Positive NAND Gates	23p	20p	15p	13p
7413		Dual 4-input Schmitt Trigger	35p	32p	25p	25p
7420		Dual 4-input Positive NAND Gates	23p	20p	15p	13p
7420		8-input Positive NAND Gates	23p	20p	15p	13p
7440		Dual 4-input Positive NAND Buffers	23p	20p	15p	13p
7441		BCD to decimal decoder (4-10 lines, 1 of 10)	87p	77p	60p	60p
7442		BCD-Seven-Segment Decoder/Drivers (18-V Outputs)	87p	77p	60p	60p
7447		Expandable dual 2-input AND-OR-INVERT	£1.40	£1.30	£1.20	£1.05
7450		Dual 2-wide 2-input AND-OR-INVERT GATES	23p	20p	15p	13p
7453		Quad 2-input Expandable AND-OR-INVERT	23p	20p	15p	13p
7460		Dual 4-input AND-OR-INVERT GATES	23p	20p	15p	13p
7470		Single-phase J-K Flip-Flop	35p	32p	25p	25p
7472		Master-slave J-K Flip-Flop	35p	32p	25p	25p
7473		Dual Master slave J-K Flip-Flop	43p	40p	37p	33p
7474		Dual O type Flip-Flop	43p	40p	37p	33p
7475		Quad latch	47p	45p	43p	40p
7476		Dual J-K with pre-set and clear	47p	45p	43p	40p
7480		Gated Full Adders	77p	77p	67p	67p
7481		16-bit read/write memory	£1.80	£1.25	£1.15	£1.00
7482		2-bit Binary Full Adders	£1.30	£1.20	£1.00	85p
7483		Quad Full Adder	87p	77p	67p	60p
7486		Quad 2 input Exclusive OR Gates	80p	70p	60p	50p
7490		BCD decade counter	87p	77p	67p	60p
7491		8-bit Shift Registers	£1.20	£1.00	87p	60p
7492		Divide-by-Twelve Counters	87p	77p	67p	60p
7494		4-bit Binary Counters	87p	77p	67p	60p
7498		Dual entry 4-bit shift register	87p	77p	67p	60p
7495		4-bit up-down shift register	87p	77p	67p	60p
7496		5-bit Parallel in parallel out Shift Register	87p	77p	67p	60p
74108		8-bit Bistable Latches	£1.75	£1.65	£1.55	£1.35
74118		Hex Set-Reset Latches	£1.30	£1.20	£1.00	85p
74121		Monostable Multivibrators	87p	77p	67p	60p
74141		BCD-to-Decimal Decoder/Driver	87p	77p	67p	60p
74145		BCD-to-Decimal Decoder/Drivers	£1.80	£1.70	£1.60	£1.50
74151		8-bit Data Selectors (with Strobes)	£1.40	£1.30	£1.20	£1.05
74155		Dual 4-Line-to-1-Line Data Selectors/Multiplexers	£1.40	£1.30	£1.20	£1.05
74151		Binary Counter reversible	£3.00	£2.85	£2.60	£2.50

Devices may be mixed to qualify for quantity price.
Data available for above series in booklet form, price 10p. (Ref No. 30).
Larger quantity prices Ext'n. 4. Dual Inline 14 Pin Socket 30p each 16 Pin 35p each.

SILICON RECTIFIERS

1 AMP MINIATURE WIRE ENDED PLASTIC RECTIFIERS	
Type P.I.V. 1-49	50+ 100+ 500+ 1000+
IN4001	5p 8p 5p 4p
IN4002	10p 9p 8p 7p 5p 4p
IN4003	20p 10p 9p 7p 6p 5p
IN4004	40p 10p 9p 8p 7p 6p
IN4005	60p 12p 10p 9p 7p 7p
IN4006	100p 15p 11p 11p 8p
IN4007	1000p 20p 18p 13p 12p 10p

1.5 AMP MINIATURE WIRE ENDED PLASTIC RECTIFIERS	
Type P.I.V. 1-49	50+ 100+ 500+ 1000+
PL4001	5p 10p 8p 7p 6p
PL4002	10p 11p 10p 8p 7p
PL4003	20p 11p 11p 10p 9p 8p
PL4004	40p 12p 11p 10p 9p 8p
PL4005	60p 15p 13p 12p 10p
PL4006	100p 17p 15p 13p 11p
PL4007	1000p 20p 17p 15p 13p 11p

3 AMP PLASTIC WIRE ENDED RECTIFIERS	
Type P.I.V. 1-49	50+ 100+ 500+ 1000+
PL7001	5p 20p 15p 17p 14p
PL7002	10p 20p 18p 18p 17p 15p
PL7003	20p 20p 20p 18p 18p 16p
PL7004	40p 25p 23p 21p 20p 19p
PL7005	60p 26p 24p 23p 22p 20p
PL7006	80p 27p 25p 24p 23p 21p
PL7007	1000p 30p 28p 26p 24p 22p

POTTED BRIDGE RECTIFIERS (SILICON) SIZE 1 x 1 x 1/2 in.	
Cur.	
Type P.I.V. rent	1-49 50+ 100+ 500+
1002	100 2 amps 80p 85p 50p 45p
2002	200 2 amps 70p 65p 60p 55p
4002	400 2 amps 80p 75p 70p 65p
1004	100 4 amps 70p 65p 55p 50p
2004	200 4 amps 75p 70p 65p 60p
4004	400 4 amps 80p 75p 70p 65p
6002	600 4 amps 90p 80p 75p 70p
8004	600 4 amps 90p 80p 75p 70p
1006	100 6 amps 75p 70p 65p 60p
2006	200 6 amps 80p 75p 70p 65p
4006	400 6 amps £1.10 £1.00 90p 80p
5006	600 6 amps £1.25 £1.10 £1.00 90p

INTEGRATED CIRCUITS

MCFCA000P		LA709C 65p	
I.C. 12	£1.12	MC1304	£2.75
TA246	£2.45	MC724P	60p
TA246B	75p	741c (DIL)	35p
TAD100	£1.97	709c (DIL)	65p
TAD110	£1.97	709c (DIL)	65p
MC1303	£2.60	Toshiba 20 watt	
UL900	40p	Amp	£4.47
UL914	40p	Toshiba	
UL923	40p	PreAmp	£1.50

ZENER DIODES

400 MW 5% Miniature	
BEV 3 Range. All voltages 3-33	
Volt. 15p each.	
25+ 12p; 100+ 10p; 500+ 8p; 1000+ 6p. Any one type.	
1/2 Watt 5% Metal case. Wire Ends.	
6-8v. all voltages to 100v. 25p each.	
25+ 12p; 100+ 10p; 500+ 17p; 1000+ 15p. Any one type.	
3 Watt Plastic Wire Ends 5%	
All voltages 6-8-100v. 30p each.	
25+ 27p; 100+ 25p; 500+ 23p; 1000+ 21p. Any one type.	
10 Watt Stud Mounting 5%	
All voltages 5-1-100v. 40p each.	
25+ 37p; 100+ 35p. Any one type.	

TRIACS

Type P.I. Cur. (All stud mounting)		Type Volts rent	
SC35A	100 3amps 90p	75p	65p
SC35B	200 3amps 80p	80p	70p
SC35D	400 3amps £1.00	85p	75p
SC40A	100 6amps £1.00	85p	75p
SC40B	200 6amps £1.20	£1.00	

DISCOTHEQUE EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MKII AMPLIFIER PR. E.S.C. L12/25 35W L/S in cabinets Terms: Deposit £12.50 and 9 monthly payments of £5 (Total £55.50)	£38.50 £21.00	PACKAGE PRICE £49.50 carr. £1
F.A.L. PHASE 50 MKII AMPLIFIER PR. FANE POP 50 L/SPEAKERS Terms: Deposit £10.50 and 9 monthly payments of £5 (Total £55.50)	£38.50 £21	PACKAGE PRICE £49.50 carr. £1
F.A.L. PHASE 100 AMPLIFIER PR. L125 50W L/S in cabinets Terms: Deposit £22 and 9 monthly payments of £11 (Total £121)	£61.95 £59.80	PACKAGE PRICE £110 carr. £1.50
F.A.L. PHASE 100 AMPLIFIER 4 FANE POP 50 L/SPEAKERS Terms: Deposit £14 and 9 monthly payments of £10 (Total £104)	£61.95 £42	PACKAGE PRICE £94 carr. £1.50

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5.75**

OR SENIOR 15 WATT INC. **£6.75** Carr. 30p
HF126 15,000 LINE SPEAKER carr. 35p

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. Please state choice. Exceptional performance at low cost.

HF801D 8" 8W	£2.71	HF120D 12" 15W	£4.75
HF102D 10" 10W	£3.40	HF128 12" 15W	£5.50
HF120 12" 15W	£4.25	HF128 12" 15W	£5.90

FANE 807 HIGH FIDELITY LOUDSPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Impedance 3 or **£3.50** 8-15 Ω. Gauss 10,000. Remarkable value.

HI-FI SPEAKER ENCLOSURES

Modern design. Teak veneer finish. Acoustically lined. All sizes approx. Carr. 30p. per enclosure

JES Size 16 x 11 x 9in. Presurised. Gives pleasing results with any 8in. Hi-Fi speaker. SES For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported	£5.35 £6.47
SE10 For outstanding results SES For exelnt prinnce with 12in with 10in. Hi-Fi speaker and tweeter. Size 24x15x10in. P.t.d.	£6.74 Hi-Fi speaker and tweeter. Size 25 x 18 x 10in. £7.87

R.S.C. PLINTHS

for Record Superior Solid Natural Wood Construction Playing units, cut for Garrard 1025, 2025, 3000, AT60, SP25 etc. **£3.15** WITH TRANSPARENT PLASTIC COVER **£6.30**

LEADING MAKES HI-FI EQUIPMENT AT CLEARANCE PRICES AVAILABLE AT BRANCHES ONLY

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BEM1 An all-dry battery eliminator. Size 4 1/2 x 4 1/2 x 3 1/2 in. approx. Completely replaces batteries supplying 1.5v. and 90v. where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram £3 or assembled ready for use £5.50

R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift' and 'cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spks. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed unmetalised case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.50** Carr. 40p

OR FACTORY BUILT WITH 12 MONTHS GUARANTEE £9.75

R.S.C. A11 HI-FI 12-14 WATT AMPLIFIER

PUSH-OUT PUT. Two input sockets with sep. vol. controls for mixing. High sensitivity, 5 valves. Bass and treble controls. Response ± 3dB 30-20,000 c/s. Hum level -0.6dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.V.s. High Impedance "mikes". For Musical Instruments etc. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 60p SAE for leaflet. Twin handled metal cover **£10.50** Factory built **£14.75** or Dep. £3 and 9 mthly pymnts of **£1.60** (Total **£17.40**)

RECORD PLAYING UNITS

Money saving units. Mounted on Plinth. Supplied with transparent plastic cover. Ready to plug into Amp. or Tape recorder.

RPIC GARRARD 3000 4-speed Auto-change Unit with Sonotone 9TA/HC Ceramic Stereo Cartridge. **£19.45** Carr. 50p.

RP23C GARRARD SP25 Mk III fitted Goldring CS90 high compliance ceramic Stereo/Mono cartridge with diamond stylus. **£26.09** Carr. 50p.

RPC6 GARRARD 5200 Auto Unit fitted Stereo Cartridge, Plinth & Cover as RP23C. **£15** Carr. 50p

Other types available with Magnetic cartridges and with alternative design plinths.

R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine Vynair

TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C485 25-30 WATTS
Fitted four 8" high flux 8 watt speakers. Overall size approx 48 x 10 x 5 in. Carr 60p
Terms: Dep £3 and 9 monthly payments £3 (Total £21) **£17.75**

TYPE C4100 100 WATTS inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx 58 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £7.50 and 9 mthly. pyts. £5.45 (Total **£26.95**). Carr. £1

TYPE C4125 50 WATTS
Fitted four 12" 11,000 line 15 watt speakers. Overall size approx 56 x 14 x 9 in. Carr 75p
Terms: Dep. £4 and 9 monthly payments £3 (Total £31) **£27.50**

30 WATT HI-FI AMPLIFIER FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP.
A 2 or 4 input, 2 vol. control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £3.70 and 9 monthly payments of £2.10 (Total £22.60) **£19.95** Carr. 65p

HIGH QUALITY LOUDSPEAKER UNITS

IN TEAK VENEERED CABINETS

L18 18" x 8" 10 Watt 10,000 lines 3 or 15 ohms. State impedance required.	L12 12" 25 WATT 10,000 lines 15 ohms. covered	Also supplied Rexine covered
---	---	------------------------------

£5.25 carr. 40p **£10.50** carr. 45p

L125 50 WATT Two tone Rexine and Vynair finish. Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Or deposit £4 and 9 monthly payments of £3.85 Total **£24.15** Carr. 75p **£31**

R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit optional horizontal or vertical mounting. **£60** Carr. £1.50

* Two extra heavy duty 12in. Loudspeakers.
* Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes".
Bass and Treble controls. Send S.A.E. for leaflet.
Credit Terms Deposit £16 and 9 monthly payments of £5.75 (Total **£67.75**)

FAL PHASE 50 MkiI AMPLIFIER 50W FAL PHASE 100 AMPLIFIER 100W

Solid state 4 Separately controlled inputs. Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/s 3-30 ohms. Output 60 watts music rating. Or deposit £8 and 9 monthly payments £3.50. Total **£37.50** Carr. 65p

Solid State. 4 Separately controlled inputs. Plus master volume control. Ind. Bass and Treble Controls. Output for speaker/s 3-30 ohms. Protective circuit to guard against damage from accidental shorts. I.H.F.M. Output rating. Or deposit £12 and 9 monthly payments £8.25. Total **£68.25** Carr. 75p Send S.A.E. for leaflets.

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. Heavy cast chassis. All carr. free.

'POP' 100 18" 100 Watt 14,000 gauss 8/15Ω £22.05 Dep. £6 and 9 monthly payments £2.10 (Total £24.90) FOR BASS GUITAR, ELECT. ORGAN, ETC.	'POP' 60 15" 60 Watt 14,000 gauss 8/15Ω £12.90 Dep. £3.30 and 9 monthly payments. £1.30 (Total £15.15)	'POP' 50 12" 50 Watt 13,000 gauss 15Ω £10.50 Dep. £2 and 9 monthly payments £1.15 (Total £12.35) Fair suitable all purposes
---	---	--

F A N E LOUDSPEAKERS 'POP' 25/2 12in. 25 WATT

Dual Cone 15Ω (for use other than Bass Guitar or Electronic Organ). **£6.75** Carr. free or Dep. £1 and 9 mthly payments 75p (Total **£7.75**)

R.S.C A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER Highly sensitive. Push-Pull high output, Hum level -70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls Outdoor Functions, etc. For Electronic Organ, Guitar, Bass, etc. Gram, Radio, etc. (Step Up/Step Down) TRANSFORMERS 0-110/120v. 200-230-250v., 50-80 watts 89p; 150 watts, £1.70 250 watts £2.49; 500 watts 25.25.

OUTPUT TRANSFORMERS Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 45p Standard Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 75p Push-Pull 10 watts 6V6, ECL86 to 3 Ω, 5 Ω or 15 Ω 120p Push-Pull EL84 to 3 or 15 Ω 10-12 watts etc. £1.20 Push-Pull Ultra Linear for Mullard 510, etc. £1.99 Push-Pull 15-18 watts, sectionally wound 6T6, KT66, etc., for 3 or 15 Ω £1.80 Push-Pull 20 watt high quality sectionally wound EL34, 6L6, 6T66 etc. to 3 or 15 Ω £2.99 SMOOTHING CHOKES 100mA, 7-10H. 250 Ω 65p; 100mA, 10H, 200 Ω 55p; 80mA, 10H, 350 Ω 45p; 60mA, 10H, 400 Ω 25p.

RSC TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and interleaved where necessary

Primaries 200-250v. 50c/s. Screened

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in. 250v. 60mA, 6.3v. 2a 90p

250-0-250v., 60mA 6.3v. 2a 95p

FULLY SHEATHED UPRIGHT MOUNTING

250-0-250v., 60mA, 6.3v. 2a, 0.5-6.3v. 2a. **£1.25**

250-0-250v., 100mA, 6.3v. 4a., 0.5-6.3v. 3a. **£1.29**

300-0-300v., 100mA, 6.3v. 4a., 0.5-6.3v. 3a. **£1.89**

300-0-300v., 100mA, 6.3v. 4a., c.t., 6.3v. 1a. **£2.40**

For Mullard 610 Amplifier **£2.40**

350-0-350v., 100mA, 6.3v. 4a., 0.5-6.3v. 3a. **£1.99**

350-0-350v., 100mA, 6.3v. 4a., 0.5-6.3v. 3a. **£2.40**

425-0-425v., 200mA, 6.3v. 4a., c.t., 5v. 3a. **£2.49**

425-0-425v., 200mA, 6.3v. 4a., 6.3v. 3a., 5v. 3a. **£2.69**

450-0-450v., 250mA, 6.3v. 4a., c.t., 5v. 3a. **£2.49**

POP SHEATHED DROP-THRO' TYPE

250-0-250v., 70mA, 6.3v. 2a., 0.5-6.3v. 2a. **£1.99**

250-0-250v., 100mA, 6.3v. 4a., 0.5-6.3v. 2a. **£1.40**

250-0-250v., 100mA, 6.3v. 2a., 6.3v. 1a. **£1.45**

350-0-350v., 80mA, 6.3v. 2a., 0.5-6.3v. 2a. **£1.50**

250-0-250v., 100mA, 6.3v. 4a., 0.5-6.3v. 3a. **£1.99**

300-0-300v., 130mA, 6.3v. 4a., 0.5-6.3v. 1a. **£2.35**

Suitable for Mullard 610 Amplifier **£2.35**

350-0-350v., 150mA, 6.3v. 4a., 0.5-6.3v. 3a. **£1.99**


350-0-350v., 150mA, 6.3v. 4a., 0.5-6.3v. 3a. **£2.35**

SELENIUM RECTIFIERS F.W. (Bridged) All 1/2w. D.C. output. Max. A.C. input 18v. 1a. 25p. 2a. 35p. 3a. 50p. 4a. 65p. 6a. 80p.

Introducing R.S.C. MkIII SUPER 30 HI-FI STEREO AMPLIFIER

A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE. REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.

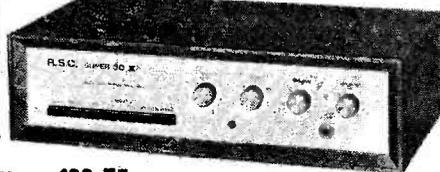Only high grade components by leading manufacturers. COMPLETE KIT OF PARTS **£25** Carr. 65p



- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE.
- ★ WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

Or FACTORY BUILT with 12 months guarantee Dep. £3.75 and 9 monthly payments £3.50 (Total £37.25) **£33.75**

Or FACTORY BUILT in cabinet as illustrated Dep. £6 and 9 monthly payments £3.86 (Total £40.74) **£36.75**

PRINTED CIRCUITRY, TWENTY SILICON TRANSISTORS. FOUR DIODES, FOUR RECTIFIERS.

TECHNICAL DETAILS (Applying to each channel where appropriate)

CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble, and Balance. Plus Ceramic/Mag P.U. Switch.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms.

HUM & NOISE -75dB Min. Vol. -85dB Full Vol. HARMONIC DISTORTION

FREQUENCY RESPONSE: -3dB 7Hz to 70KHz 0.1% at 1000 Hz 10 Watts

TREBLE CONTROL: +16dB to -12dB at 14KHz

BASS CONTROL: +17dB to -16dB at 40Hz

CROSS TALK -58dB

SENSITIVITIES: Disc Mag. 2.5mV. Ceramic 35mV. Radio 120mV. Tape 120mV.

REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

R.S.C. HIGH FIDELITY STEREO PACKAGE OFFERS

Four fully wire units ready to 'plug-in.' SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing

★ GARRARD SP25 MKIII Turntable on Plinth with cover

★ GOLDRING CS90 Ceramic Pick-up Cartridge with diamond stylus

★ PAIR OF STANWAY II Speaker Units

£79-80

Total Price Carr. £1-50

★ Super 30 Amplifier (15 + 15 watt) in veneered housing

★ Goldring GL69 II Transcription Turntable on Plinth as illustrated

★ Goldring Magnetic P.U. Cartridge.

★ Pair of Stanway II speaker units

Special Total Price **£96-75** Carr. £1.60

Matching as recommended for optimum performance. Send S.A.E for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.



Stanway II



ATTRACTIVE TEAK or AFROMOSIA VENEERED CABINETS and PLINTHS

★ TA12 AMPLIFIER 6.5+6.5 watt in veneered housing

★ GARRARD SP25 MK III Player unit on Plinth

★ GOLDRING CS90 Ceramic P.U. Cartridge with diamond stylus

★ PAIR OF DORCHESTER Loudspeaker Units

Special Total Price **£58**

Carr. £1.25

Or Deposit £7.15 and 9 monthly payments £6.35 (Total £64.30).

Trans. Plastic cover £3.15 extra.

Package as above but with Garrard 3000 Auto-changer and Sonotone 9TA Ceramic Cartridge in lieu of SP25 **£51.75** Carr. £1.25

Or Deposit £6 and 9 monthly payments £5.70 (Total £57.30)

Trans. Plastic cover £3.15 extra.

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25x14x10in. COMPLETE KIT **£22**

★ Response 30-20,000 c.p.s. Carr. 63p

★ Impedance 15 ohms

★ Performance comparable with units costing considerably more.

Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system

(3) 8 x 5in. High flux middle range speaker. (4) High efficiency tweeter.

(5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4.50 and 9 monthly payments £2.25 (Total £24.75).

DEMONSTRATIONS AT ALL BRANCHES

RSC G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Suitable for Crystal Pick-ups, etc., and for loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v A.C. mains operation. Attractive silver finished metal face plate & matching control knobs.

COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT

and comprehensive wiring diagram and instructions **£9-99** carr. 40p.

Or FACTORY BUILT IN TEAK **£12-99**

VENEERED CABINET as illustrated

or dep £2.50 and 9 mthly pymnts. £1.45 (Total £15.55)



HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.

DORCHESTER (Illustrated) Size 16x11x9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13x8in. **£9-45** Carr. 40p.

Dual Cone speaker. Imp. 3 or 15 ohms.

STANWAY II Size 20 x 10 1/2 x 9 1/2 in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives **£17-85** smooth realistic sound output. See 'package offers' for illustration

R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION

HIGH FIDELITY OUTPUT OF 6.6 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.8% at 1,000 c.p.s. Hum and Noise -70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & knobs. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS.

Factory built with 12 months guarantee **£19-50** or Deposit £3 and **£15-50** Carr. 40p.

9 mthly pymts £2-15 (Total £22-25). Or In Teak veneer housing **£23** Dep. £3 & 9 mthly payments £2-55 (Total £22-95). Send S.A.E. for leaflet



AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM

5 + 5 WATT OUTPUT

GARRARD 5200 CHANGER WITH LOW MASS PICK-UP ARM AND STEREO CARTRIDGE.

CONTROLS: TREBLE, BASS, VOLUME, STEREO, BALANCE.

Operation on 200-250v. A.C. mains.

Output rating. I.H.F.M



Luxurious Teak Veneer Finished Cabinets. Transparent plastic (tinted) cover included for main unit. Silver finished face plate and matching control knobs.

PAIR OF LOUDSPEAKER UNITS

incorporating high flux 8 x 5 ins. speaker.

Size approx. 13x7 1/4 x 8 1/2 ins.

Price complete **£42**

ONLY Carr. £1-25

Terms: Deposit £5.50 and 9 monthly payments £4.50 (Total £46.)

A REALLY SURPRISING STANDARD OF QUALITY IS OBTAINABLE FROM THIS COMPACT LOW PRICED SYSTEM

LOW DEPOSIT CREDIT TERMS

AVAILABLE ON PURCHASES OVER £8 (KITS OF PARTS EXCEPTED)

INTEREST CHARGES

REFUNDED

ON CREDIT SALES SETTLED IN 3 MONTHS

WIN A CASSETTE TAPE RECORDER THIS MONTH—FULL DETAILS AT ALL BRANCHES

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349

BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street

BIRMINGHAM 30/31 Gt. Western Arcade (Half-day Wed.) 021-236-1279

DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361

DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043

EDINBURGH 133 Leith St. (Half-day Wed.) Tel. 556 5766

GLASGOW 326 Argyle St. (Half-day Tues.) Tel. CITY 4158

HULL 91 Parazon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Henconner Lane, Leeds 13. Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 25p extra under £2. 30p extra over £2 or as quoted. Trade supplied. S.A.E. please with enquiries. Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS

32 High Street (Half-day Thurs.) Tel. 56420 LEICESTER

5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) LEEDS Tel. 28257

73 Dale St. (Half-day Wed.) Tel. CENTRAL 3573 LIVERPOOL

238 Edgware Road, W2 (Half-day Thurs.) Tel. LONDON PAD 1629

60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 MANCHESTER

106 Newport Rd. (Half-day Wed.) Tel. 47096 MIDDLESBROUGH

41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469 NEWCASTLE UPON TYNE

13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 SHEFFIELD

One year's electronics experience + ONC or C & G?

Then become a Radio Technician with the National Air Traffic Services. You would work on the installation and maintenance of a wide range of sophisticated electronic systems and specialised equipment throughout the U.K. You would be involved with RT, Radar, Data Transmission Links, Navigation Aids, Landing Systems, Closed Circuit T.V. and Computer Installations. You could also work on the development of new systems.

To qualify for entry to our training course you must be aged 19 or over, have at least one year's experience in electronics and preferably O.N.C. or C. & G. (Telecoms). Your starting salary would be £1,143 (at 19) to £1,503 (at 25 or over), scale max. £1,741 - shift duty allowances. Good career prospects.

Send NOW for full details of how you can become a Radio Technician. Complete the coupon and return to A. J. Edwards, C. Eng., M.I.E.E., Room 705, The Adelphi, John Adam Street, London WC2N 6BQ, marking your envelope 'Recruitment'.

I meet the requirements, please tell me more about the work of a Radio Technician.

NAME _____

ADDRESS _____

A/PW/17

Not applicable to residents outside the United Kingdom.

NATS
National Air Traffic Services

BC.221 MAINS POWER UNITS

200/250v I/P O/P plus 135v at 20 Ma from electronic voltage stabiliser also 6.3v A.C. for heaters. Uses 4 valves made to fit in battery compartment of unit with small control box with swt and fuses. Supplied new with circ and mains lead. Price **£5.00** plus 60p carr.

STATIC INVERTORS 115V 400 C/S 1 PHASE

These all-transistor units provide a sine wave O/P from a D.C. I/P of 23 to 28v D.C. at approx. 9 amps for an O/P of 180 VA. Use 14 transistors all silicon except O/P switching. Overall size 9 x 10 x 3". These units are fitted overload protection and have stabilised O/P. Made by A.C. Cossor to a very high specification. Supplied new unused with connecting data.

Price **£12.00** plus 50p carr.

RX/IND APN-9

This is a swt tuned Rx with CRT Ind unit, the Rx covers 1/8 to 2 Mc/s in 4 channels. The Ind section uses CRT type 3BP1 3" green screen and 34 octal type valves 6SN7, 6SL7, 6SK7, 6SJ7, 6H6, 6Y6, 5Z3, 2X2, VR105, 6N7, 6SA7, there is also a high grade 100Kc xtal, the CRT is fitted Mu Metal shield, all contained in case size 20 x 12 x 8" black crackle finish. These units are for 115v 400c/s supply, the tube is well suited to scope use or modification to 1.6 Mc/s Pan Adap. Supplied with circ. Available new with magnifier and visor at **£8** plus 75p carr.

HEAVY DUTY MAINS TRANS

Pria. 200/220/240v 50c/s Sec 500-0-500 at 400 Ma or can be connected to give 1 Kv at 200 Ma. Varnish finish tag connections, size overall 5½ x 5½ x 4½. Supplied in new cond.

Price **£2.25** plus 40p post.

OSCILLOSCOPES VARIOUS

Hartley type 13a with probe leads etc. Good condition. Price **£22.00**. Solatron CD513 used condition less graticule D.C. to 10 Mc/s blue phosphor tube **£18**. Solatron CD513.2 D.C. to 10 Mc/s green phosphor tube. Good condition. Price **£35**. USM-25 (OS-4) 115v 50c/s I/P high grade pulse and time measuring scope response to 11 Mc/s. Good condition. Can be used as general purpose scope with probes, etc. Price **£18** all scope plus **£1** carr. All units tested supplied with circuit diagrams.

MISC. ITEMS

Solatron Stabilised O/P P.U. 200/250v I/P, O/Ps H.T. 250 or 300v at 200 Ma, 6.3 at 4a twice, 6.3 at 1a. Price **£4.50**. Delay unit with 230v to 6.3 1.7a and 6.3 .3a trans, 6CH6, EF91, EB91, ECC82 valves, 2 x tog. swts, 2p 11w yax swt etc. Price **£1.50**. Trig Stab Unit with 2 x OC45 and 2 x OC41 transis. delay units, 6 x wander plugs, pots. etc. in case 11 x 6½ x 5". New **£1.50**. Variacs 115v 400 c/s can be used on 40v AC 50c/s to give 0 to 40v O/P at 5 amps **£1.75**. Meters 0 to 1 Ma 3½" scaled 0 to 1 **£1.50**. 1-0-1 Ma 3½" scaled 1-0-1 **£1.50**. 500 Ua scaled 0 to 5 2½" OSD **£1**. Transformers 230 Pria. Sec 235-0-235 at 80 Ma 6.3 3a 6.3 1a, 5v 2a. Price **£1.50**. Also Sec 250-0-250 at 60 Ma 5v 2a, 6.3 2a soiled. **£1.00**. Table Cabinets size 19" x 12" x 10" with front panel and some parts **£1.50**. American 73 Radio Mag, new back issues 8 for **£1.15**. Silicon Diodes IN1614 200 P.I.V. 5a ea. 4 for 50p. IN1206 600 P.I.V. 12a ea. 4 for **£1.25**. Choke L.V. .25H at 1 amp. Price **65p**.

All above prices include post or carr. All goods ex equipment unless stated otherwise. S.A.E. with enquiry

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9 5HL


PHILIPS STEREO AND MONO AUTOCHANGER
£9.75 Post 25p



Precision hi-fi quality at bargain price. Silver and grey deck enamelled finish. 10in. dia. turntable. 4 speeds, 16, 33 1/3, 45 and 78 rpm. Plays 7, 10, 12in. discs which can be mixed. Fitted removable Philips plug-in pick-up with stylus 1L Stereo/VE and 78. Sensitivity 100mV. Frequency response 30cps-10Kc/s. Lightweight stylus pressure 3-6 grammes. Board size required 14 x 12 1/2 in. Above 4in. Below 2 1/2 in.

PHILIPS PORTABLE PLAYER CABINET
 Size 18 x 15 1/2 x 7 1/2 in. Cut for above deck. Amplifier space 14 x 5 x 2 1/2 in. Satin aluminium front grille. Really smart appearance. Black/White or Green/Grey. **£4** Post 25p Chrome fittings.

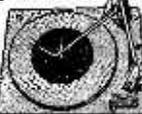BSR C.109 SUPERSLIM STEREO AND MONO CHANGER



Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 12 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL **£7.75** Post 25p.

GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond and Mono Sapphire. SP25 Mk II 215 Model 8600 Stereo and Mono Autochanger 214. Post 25p.

RECORD PLAYER PORTABLE CABINET £3.75
 Space for amplifier and microphone. Post 25p.

8PCS DE-LUXE 3 WATT AMPLIFIER. Ready made with 6-state triode pentode valve. 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL82, E2250. **£4**

RSC 2 WATT AMPLIFIER with loudspeaker and valves UCL82 and UY85 Post 25p **£3**

E.C.S. TEAKWOOD BASE. Ready cut out for mounting (State player make and model) **£2.75**

E.C.S. PLASTIC COVERS FOR ABOVE BASE. Durable tinted plastic, attractive appearance. **£2.75**

EMI PICK-UP ARM with mono xtal and stylus 21-25. **£3**

EMI JUNIOR 4 SPEED RECORD PLAYER with Mains operated motor, turntable and pick up **£3** Post 25p.

HI-FI PICK-UP CARTRIDGES: Diamond Stereo/Mono. JTA 22-90; GP24 22-75; GP23 22-35; Mono GP21 21-50; GC8 21-25; GP27 25p. ACOR L.P. only 50p. All standard fixing complete with stylus.

WEYRAD P50-TRANSISTOR COILS

RA2W Ferrite Aerial 65p	Spare Cores 3p
On. P50/1AG 30p	Driver Trans. LFD74 . . . 50p
LF. P50/2C0 470 k/ohs. 38p	Printed Circuit, PCA1 . . 50p
3rd L.F. P50/3CC 38p	J.B. Tuning Gang 65p
P51/1 or P51/2 38p	Weyrad Booklet 10p
P50/3V 38p	OPTI 55p

Mullard Ferrite Rod 8 x 1 in. 20p, 8 x 1 in. 25p.

VOLUME CONTROL
 Long spindles. Midget Size 5 K. Ohms to 2 Meg. LOG or L.N. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Ideal 5K S.P. Transistor 25p.

WIRE-WOUND 3-WATT POTS. Small type with small knob. Values 10 Ohm to 50 K. Carbon 30 K to 2 meg. **25p**

WIRE-WOUNDS 8-WATT STANDARD SIZE POTS. LONG SPINDLE. 10 OHMS to 100 K. **40p**

VEROBOARD 016 MATRIX
 EDGE CONNECTORS 16 way 25p; 24 way 38p.
 PINB 30 per packet 17p. FACE CUTTERS 38p.

S.R.E.P. Board 0-15 MATRIX 3in. wide 8p per lin. 3 1/2 in. wide 4p per 1 in.; 5in. side 5p per lin. (up to 17in.).
 S.R.E.P. undrilled 1/2 in. Board 10 x 8in. 15p.

BLANK ALUMINIUM CHASSIS 18 s.w.g. 2 1/2 in. sides. 6 x 4in. 45p; 8 x 6in. 50p; 10 x 7in. 70p; 14 x 8in. 90p; 16 x 6in. 90p; 12 x 8in. 60p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 8p; 8 x 6in. 15p; 10 x 7in. 17p; 12 x 8in. 23p; 14 x 9in. 27p; 12 x 12in. 32p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p.
 2 p. 2-way, or 2 p. 6-way or 3 p. 2-way 25p each. 1 p. 12-way or 4 p. 2-way, or 4 p. 3-way 25p.

1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, or 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 water 60p, 2 water 90p. Extra waters up to six 30p each.

TOGGLE SWITCHES, sp. 14p; dp. 18p; dp. dt. 23p.

ALL PURPOSE HEADPHONES

H.R. HEADPHONES 200 ohms Super Sensitive	41.75
16W RESISTANCE HEADPHONES 3-5 ohms	23.00
DE LUXE STEREO HEADPHONES 8 ohms	23.25

"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER



200/250 v. A.C. Leaflet S.A.E. **£2.35** Post 15p

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE
 for Mike, Tape, P.U., Guitar, etc.
 Battery 9-12v or H.T. line 200-800v D.C. operation. Size 1 1/2 x 1 1/2 x 1". Response 25 c.p.s. to 25 Kc/s. 26db gain. For use with valve or transistor equipment. Full instructions supplied. **90p** Post 10p
 Brand new. Guaranteed. Details S.A.E.

NEW TUBULAR ELECTROLYTICS

2/350V . . . 14p	100/25V . . . 10p	16+16/500V . . . 55p
4/450V . . . 14p	250/25V . . . 14p	60+50/350V . . . 35p
8/450V . . . 14p	500/25V . . . 20p	60+100/350V . . . 55p
12/450V . . . 14p	800/25V . . . 20p	32+32/350V . . . 15p
32/450V . . . 20p	1+16/450V . . . 20p	32+32/450V . . . 35p
25/25V . . . 10p	16+16/450V . . . 25p	32+32+32/350V . . . 45p
50/50V . . . 10p	32+32/350V . . . 25p	100+50+50/350V . . . 45p

SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p; 500, 1000mF 12V 18p; 2000mF 25V 35p. CERAMIC 1p to 0.01 mF, 5p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-01 4p, 0-5 13p; 1mF 15p; 2mF 150V 16p. 500V-0-001 to 0-05 4p, 0-1 5p; 0-25 8p, 0-47 25p. 1.00V-0-001, 0-002, 0-005, 0-01, 0-02, 0-05, 0-1, 0-47, 0-1 14p. SILVER MICA. Close tolerance 1% 2-2-500pF 8p; 500-2-200 pF 10p; 2-700-5-600pF 20p; 6-300pF 0-01 mfd 30p; each. TWIN GANG. "0-0" 20pF + 175pF, 65p; Slow motion drive 385+385 with 25+25pF, 50p 500pF slow motion, standard 45p; small 3-gang 500pF 41-10. SHORT WAVE. Single 25pF 65p. CUMING TELESCOPE Aerial, aerial base, 22in. 20p. CUMING Solid diodes, 100pF, 400pF, 35p each. TRIMMERS. Compression 30, 50, 70pF, 5p; 100pF, 150pF, 8p; 250pF, 18p; 600pF, 750pF, 10p; 1000 pF 10p. RECTIFIERS CONTACT COOLED 1 wave 50mA 38p; 85mA 48p. SILICON BY213 30p; BY100 30p; BY127 30p. EX-GOVERNMENT RECTIFIERS 250V, 500mA, 30p. NEON PANEL INDICATORS 250V A.C. Red or Amber 30p. RESISTORS. 1 w., 1/2 w., 20% 1p; 2 w. 5p. HIGH STABILITY. 1 w. 2% 10 ohms to 1 meg., 10p. Ditto 5% Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 ohms to 100K, 10p each; 2 watt, 1 ohm to 2 ohms 10p

Q MAX CHASSIS CUTTER
 Complete: a die, a punch, an Allen screw and key
 1in. 88p 1 1/2 in. 98p 1 1/4 in. 81-20 2 3/4 in. 22-21
 1in. 88p 1in. 88p 1 1/4 in. 81-25 2 1/2 in. 22-86
 1in. 84p 1 1/2 in. 88p 1 1/4 in. 21-08 2in. 21-99 1in. sq. 21-83

AM-FM/VHF TUNING GANG




Super quality small size 1 1/2 x 1 1/2 x 1 1/2 in., plus spindle 1 1/2 x 1 1/2 x 1 1/2 in. with 25 + 25 pF. British made. Geared slow motion drive 61. Plastic dust cover. SBA tapped front yring. Cast aluminium frame **50p** Post Free

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 50 mA. 6-3 v. 2 amps, centre tapped	£1.10
250-0-250 80 mA. 6-3 v. 2 amps	£1.40
250-0-250 80 mA. 6-3 v. 3-5 a. 6-3 v. 1 a. or 5 v. 2 a.	£2.00
350-0-350 80 mA. 6-3 v. 3-5 a. 6-3 v. 1 a. or 5 v. 2 a.	£2.00
300-0-300 v. 120 mA. 6-3 v. 4 a. C.T.; 6-3 v. 2 a.	£2.50
MINIATURE 200 v. 20mA. 6-3 v. 1 a. 2 1/2 x 2 1/2 in. 70p	
MIDGET 250 v. 45 mA. 6-3 v. 2 a. 2 1/2 x 2 1/2 in. 90p	
F.E. AVORON TRANS. 12 v. 12v. 500mA	£1.50
MINI-MAINS 20v. 100mA. 1 1/2 x 1 1/2 x 1 1/2 in.	60p
HEATER TRANS. 6-3v. 3 a.	60p
Ditto tapped sec. 1.4 v., 2, 3, 4, 5, 6-3 v. 1 1/2 amp.	30p

GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 2, 4, 6, 8, 10, 12, 15, 18, 24 and 30 v. 22-00 1 amp. 2, 4, 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60, 82-00 2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60. 23-00 AUTO TRANSFORMERS 115v. to 230v. or 280v. to 115v. Input/Output. 150w. 22-00; 500w. 25p; 1000w. 312. CHARGER TRANSFORMERS. Input 200/280V. For 6 or 12v., 11 amp. 31p; 2 amp. 21-40; 4 amp. 21-90. FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. outputs, 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p. All transformers Postage 25p extra.

E.M.I. 13 1/2 x 8in. LOUSPEAKERS

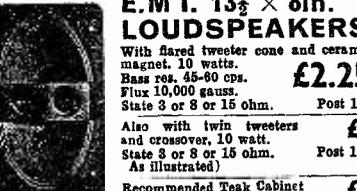

With flared tweeter cone and ceramic magnet. 10 watts. **£2.25**
 Bass res. 45-60 cps. Flat 10,000 gauss. Post 15p
 Size 3 or 8 or 15 ohm.

Also with twin tweeters and crossover, 10 watt. **£4**
 State 3 or 8 or 15 ohm. Post 15p
 (As illustrated)

Recommended Teak Cabinet **£5**
 Size 18 x 10 x 9in. Post 25p

10W MINI-MODULE £3.25 LOUSPEAKER KIT Post 25p

Triple speaker system combining on ready cut baffle. 1/2 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and a crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm.

TEAK VENEERED BOOKSHELF ENCLOSURE. 16 1/2 x 10 1/2 x 6in. Modern Design, dark grey Tygan covered baffle **£5** Post 25p

ALL MODELS "BAKER SPEAKERS" IN STOCK
BAKER 12in. MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£11.50**

BAKER "BIG-SOUND" SPEAKERS

'Group 25' 12 inch 25 watt 8 or 8 or 15 ohm	'Group 35' 12 inch 35 watt 8 or 8 or 15 ohm	'Group 50' 15 inch 50 watt 8 or 15 ohm
---	---	--

£7 **£9** **£19**

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. round Loudspeaker £9. Post 25p For 18 in. Loudspeaker £25. Post 25p For 10 x 6in. round Loudspeaker £4. Post 25p **LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft.**

THIS ELAC CONE TWEETER IS OF THE VERY LATEST DESIGN AND GIVES A HIGHER STANDARD OF PERFORMANCE THAN MORE EXPENSIVE UNITS.



The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 13,000 cps. Size 3 1/2 x 3 1/2 x 2in. deep. Rating 10 watts. 3 ohm or 15 ohm models. **£1.90** Post 10p

TWO-WAY COVER NETWORK 3000 c/s. With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5 1/2 in. x 4in. with control knob, tweeter and woofer leads and input terminals. Suitable for 2 to 8 ohm imp. **£1.90** Post 10p

GOODMANS HEAVY DUTY 10in. WOOFER. 10w. Large ceramic magnet. 30-12,000 cps. Ideal F.A.A. Columns, H.I.F.I. Enclosures, etc. **£4**

Horn Tweeters 2-16kc/s, 10w 8 ohm or 15 ohm £1.50. De Luxe Horn Tweeters 2-18 Kc/s 15W 8 ohm 25. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER! 80 ohm, 2 1/2 in. dia.; 35 ohm, 3in. 25 ohm, 3in. dia.; 6 x 4in.; 8 x 5in. 15 ohm 3 1/2 in. dia.; 7 x 4in.; 8 x 6in. 3 ohm, 2 1/2 in. dia.; 5 x 3in. 7 1/2 in. dia. £1.25; 8 x 2 1/2 in. 90p; 8in. 1 1/2 in. 10in. 3in. 90p. 1in. WOOFER 8 watts max. 20-10,000 cps. 8 or 15 ohm. 21-80. ELAC 8 in. De Luxe Ceramic 3 ohm or 15 ohm £2.50. RICHARD ALLAN TWIN CONE LOUSPEAKERS. 3in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 6 watt 8 or 8 or 15 ohm models £1.95 each. Post 15p. OVERTOP TRANS. EL34 40v. WIRE TRANS. 500 1.5S. SPEAKER COVERING MATERIALS. Samples Large 50c. GOODMANS'S OUTPUT TRANSFORMER 5 watt push-pull for valves EL84 etc., 3, 8 and 15 ohms 85p. Post 20p.

100 WATT ALL PURPOSE POWER AMPLIFIER
 4 input channels and more. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. **£36** Post Free
 Teak and Bass Controls Details. S.A.E.

ALL EAGLE PRODUCTS
 SUPPLIED AT LOWEST PRICES
 ILLUSTRATED EAGLE CATALOGUE 20p. Post Free.

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **£4**

BARGAIN 4 CHANNEL TRANSISTOR MIXER
 Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **£3**

BARGAIN FM TUNER 88-108 Mc/s Six Transistor. 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch **£10**

BARGAIN FM TUNER as above less cabinet **£7.50**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. **£3.50**

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p.

BALANCED TWIN FEEDERS 5p yd. 80 ohms or 300 ohms. JACK SOCKET Std. open-circuit 14p. closed circuit 23p; Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS Std. Chrome 15p; 8-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 6-pin 10p. DIN SOCKETS Lead 3-pin 18p; 6-pin 25p. DIN PLUGS 3-pin 15p; 6-pin 25p. VALVE HOLDERS, 6p; CERAMIC 8p; CANS 5p.

E.M.I. TAPE MOTORS

120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. Size 3 1/2 x 2 1/2 in. (Illustrated)	£1.25
---	-------

BALFOUR GRAM MOTORS
 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 50mA. Spindle 1/2 x 3/80. Size 2 1/2 x 2 1/2 x 1 1/2 in. Post 15p **85p**

Minimum Post and Packing 15p RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME
RADIO COMPONENT SPECIALISTS 337 WHITEHOUSE ROAD, CROYDON
 List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665
 Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)

IMPORTANT. THIS LATEST 1971 MODEL INCORPORATES ALL THE LATEST TECHNOLOGICAL IMPROVEMENTS AND SUPERSEDES ALL EARLIER MODELS! YES, THIS SENSATIONAL BRAND NEW VEF 204 RUSSIAN 8 WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION will probably make your present radio seem like a "crystal set"! It's far better than any other 8 wave radio that even they have produced before! If even incorporates a special MARINE WAVEBAND to receive spoken communications from ship-to-shore! Complete with optional battery eliminator for both battery and mains use! It represents the finest value we have ever offered! We're almost giving them away at only £13.97—a mere fraction of even today's Russian miracle price! In fact we challenge you to compare the performance and value with that of £42.00 radios! *You just can't lose, we'll refund your money instantly if you are not astounded! Furer and sweeter tone than ever! Much wider band spread than hitherto, for absolutely "pin-point" station selection! Yes, the Russians have really surpassed themselves this time, proving once again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spacebip and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO ITS TRUE VALUE! Yes, 8 separate wavebands, including Standard Long, Medium and Short Waves to cover the world. PLUS special "ship-to-shore" MARINE BAND! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions, and stations at your fingertips 24 hours a day, including ships at sea, etc. and messages from all over the world—truly nothing is secret! The radio enthusiast can have the world in the palm of his hand! You must hear it to believe it! Superb, sweet tone—controlled from a whisper to a roar that will fill a hall! Genuine push-pull output! Separate ON/OFF volume and Treble/Bass tone controls! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v. AC mains supply. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 31ins length. It's also a fabulous CAR RADIO—any speed, requires no additional aerial, UNIQUE! Elegant Black & Chrome finish case. SIZE 11ins. x 8ins. x 8ins. overall approx. Magnificently designed & superbly made to give years of perfect service. Complete with WRITTEN GUARANTEE, manual with simple operating instructions & circuit diagram. ONLY £13.97 (with mains/battery eliminator £1.38 extra). BOX, POST ETC. 50p. Standard batteries 88p extra. Can also be used through extension amplifier, tape recorder or public address system. Send today or call at either store, but HURRY! It's the chance of a lifetime. (Sorry—We cannot change these new radios for any earlier model already purchased). Send quickly or call. Refund guaranteed.

RUSSIAN WORLD BEATER!

JUST ARRIVED!

The Fabulous BRAND NEW 1971

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

VEF 204 8 WAVEBAND

10 TRANSISTOR PLUS 2 DIODES PORTABLE RADIO

AND NOW WITH SHIP-TO-SHORE MARINE BAND

BATTERY MODEL £13.97p

BOX POST ETC. 50p MAINS/BATTERY ELIMINATOR £1.38p extra

THIS OFFER ONLY FOR LIMITED!

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!



WE COULDN'T EVEN MAKE THEM FOR OUR FANTASTIC PRICE!

***COMPARE ITS PERFORMANCE WITH £42 RADIOS!**

Order by post to Uxbridge Road address. COMMERCIAL TRAVELERS PLEASE NOTE: Merchandising office at Holborn.

SHOPERTUNITIES LTD. SL

HOLBORN, LONDON, W.1 (opposite Chancery Lane). (Wednesday 1, Thursday 7). Both stores open MON.-SAT. 9-8.

Dept. WP/8 164 UXBRIDGE RD., LONDON, W.12 8AQ (facing Shepherd's Bush Green). (Thursday 1 pm. Friday 7 pm) ALSO 37/39 HIGH

LINEAR

RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors.




LT55 6 WATT AMPLIFIER
A HIGH FIDELITY UNIT PROVIDING EXCELLENT RESULTS AT MODEST OUTPUT LEVELS.

Recommended Retail price **£11**
Size 9 1/2 x 2 1/2 x 5 1/2 in. Approx.
Controls (5) Volume, Bass, Treble, Mains Switch, Input Selector Switch.

Sensitivity 5 mv (max).
Frequency Response 30-20,000 cps—2dB
Harmonic Distortion 0.5% at 1,000 cps
Output Rating I.H.F.M. 6 Watt
Input Sockets for "Mike," Gram and Radio Tuner/Tape Recorder.
Suitable for speakers 3-15 ohms.

LT66 12 WATT STEREO AMPLIFIER

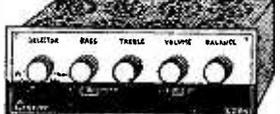A TWIN CHANNEL VERSION OF THE LT55 PROVIDING UP TO 6 WATTS I.H.F.M. HIGH FIDELITY OUTPUT ON EACH CHANNEL.
Switched Input Facilities
Socket (1) Tape or crystal PU
(2) Radio Tuner (3) Ceramic PU Microphone.



Recommended Retail price **£21**
Size 12 x 3 1/4 x 6 in. Approx.

Controls (6) Volume, Bass, Treble, Balance, Mains Switch, Input Selector Switch, Stereo/Mono Switch.
Facia Plate Rigid Perspex with black/silver background and matching black edged knobs with silver finish centres.

If required an attractive wood cabinet with veneer finish can be supplied for any model.
Prices From **£3.50**

PLEASE SEND A STAMPED ADDRESSED ENVELOPE FOR FULL DETAILS OF ABOVE UNITS


AVAILABLE FROM YOUR LOCAL HI-FI DEALER

Wholesale and Retail enquiries to:

LINEAR PRODUCTS LTD, Electron Works, Armley, Leeds

INTER-LOCKING PLASTIC STORAGE DRAWERS

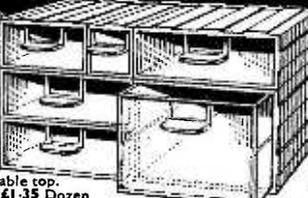Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top.




DISCOUNT PRICES
NEAT! HANDY! TIDY!
SINGLE UNITS (5" x 2 1/2" x 2 1/2") £1.35 Dozen
DOUBLE UNITS £2.25 Dozen
TREBLE (3D) £2.35 for 8
DOUBLE TREBLE 2 draws in one outer case (6D2) £3.65 for 8 extra large size (6D1) £3.30 for 8.

PLUS QUANTITY DISCOUNTS! Order £5 and over Deduct 5% in the £. Order £10 and over Deduct 7 1/2% in the £. Order £20 and over Deduct 10% in the £. Pack/Post/Carr.: Add 35p to all orders under £5. Orders over £5 P/P/C free.
IVORYET LIMITED (Dept. PW7) 124 CRICKLEWOOD BROADWAY, LONDON N.W.2

BAKER 12in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.
Maximum Power 15 watts
Bass Resonance 45 c.p.s.
Flux Density 12,000 gauss
Voice Coil impedance 3 or 8 or 15 ohm models
Useful response 45-13,000 c.p.s.
Nett weight 5 lbs. POST FREE
GUITAR MODEL "GROUP 25" £7
25 watt rating
Latest catalogue 5p with enclosure plans.

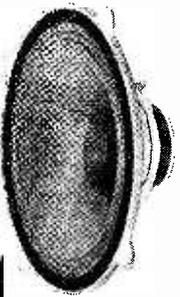

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

BRAND NEW GUARANTEED

SEMICONDUCTORS & COMPONENTS

RETURN OF POST SERVICE

SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

TRANSISTORS

2G901	20p	2N3403	22½p	40809	32½p	BC184	15p	BSX27	47½p	NKT275	20p
2G902	20p	2N3404	22½p	40810	35p	BC212L	18½p	BSX28	32½p	NKT281	27½p
2G903	20p	2N3405	45p	40811	35p	BCY30	27½p	BSX60	82½p	NKT401	87½p
2G906	42½p	2N3414	22½p	40812	47½p	BCY31	30p	BSX61	82½p	NKT402	90p
2G908	30p	2N3415	22½p	40814	37½p	BCY32	50p	BSX76	22½p	NKT403	75p
2G971	15p	2N3417	37½p	40820	47½p	BCY33	27½p	BSX77	27½p	NKT404	62½p
2G981	20p	2N3570	£1.05	40824	47½p	BCY34	30p	BSX78	27½p	NKT405	75p
2G982	20p	2N3572	97½p	40826	37½p	BCY38	40p	BSY10	27½p	NKT406	62½p
2N404	22½p	2N3605	27½p	40829	30p	BCY40	50p	BSY11	27½p	NKT451	62½p
2N696	20p	2N3606	27½p	40844	27½p	BCY42	15p	BSY26	15p	NKT452	62½p
2N697	20p	2N3607	22½p	40847	67½p	BCY43	15p	BSY27	17½p	NKT453	47½p
2N698	20p	2N3702	12½p	40848	32½p	BCY44	15p	BSY28	17½p	NKT613F	32½p
2N706	12½p	2N3703	12½p	40849	43½p	BCY58	22½p	BSY28	17½p	NKT674F	30p
2N708A	18½p	2N3704	17½p	40861	47½p	BCY69	22½p	BSY29	17½p	NKT677F	30p
2N708	18½p	2N3705	15p	40862	47½p	BCY80	97½p	BSY32	25p	NKT713	25p
2N709	62½p	2N3706	12½p	40870	32½p	BCY70	20p	BSY36	25p	NKT781	30p
2N718	25p	2N3707	15p	40446	67½p	BCY71	42½p	BSY37	35p	NKT10439	30p
2N726	30p	2N3708	09p	40407	40p	BCZ10	17½p	BSY39	22½p	NKT10519	37½p
2N727	30p	2N3709	10p	40410	62½p	BCZ11	42½p	BSY40	32½p	NKT10519	37½p
2N801	17½p	2N3710	11p	40411	62½p	BD116	£1.12	BSY51	32½p	NKT20329	32½p
2N816	17½p	2N3711	12p	40487A	87½p	BD121	85p	BSY52	32½p	NKT20330	47½p
2N818	30p	2N3715	£2.22	40468A	57½p	BD122	82½p	BSY53	37½p	NKT20331	47½p
2N929	22½p	2N3716	£2.90	40600	57½p	BD123	82½p	BSY54	40p	NKT80111	37½p
2N930	27½p	2N3721	£2.75	AC107	30p	BD124	82½p	BSY55	40p	NKT80112	37½p
2N1090	22½p	2N3819	35p	AC127	25p	BD131	70p	BSY66	30p	NKT80113	37½p
2N1091	22½p	2N3823	97½p	AC127	25p	BD132	85p	BSY78	47½p	NKT80114	37½p
2N1182	25p	2N3854A	27½p	AC128	30p	BDY10	£1.37	BSY79	45p	NKT80115	37½p
2N1302	17½p	2N3855	27½p	AC154	22½p	BDY11	£1.62	BSY82	52½p	NKT80116	37½p
2N1303	17½p	2N3855A	30p	AC176	25p	BDY12	£1.60	BSY86	58½p	NKT80117	37½p
2N1304	22½p	2N3856	30p	AC188	27½p	BDY13	£1.75	BSY95A	12½p	NKT80211	£1.12
2N1305	22½p	2N3856A	30p	AC197	27½p	BDY19	£1.97	BSW41	42½p	NKT80212	92½p
2N1306	22½p	2N3858	25p	ACY18	25p	BDY20	£1.12	BSW70	27½p	NKT80213	92½p
2N1307	25p	2N3858A	25p	ACY19	25p	BDY38	97½p	C111	75p	NKT80214	92½p
2N1308	30p	2N3859	27½p	ACY20	25p	BDY60	£1.25	C424	27½p	NKT80215	92½p
2N1309	30p	2N3859A	32½p	ACY21	25p	BDY61	£1.25	C425	55p	NKT80216	92½p
2N1607	17½p	2N3860	30p	ACY22	25p	BDY82	£1.00	C426	30p	NKT80217	92½p
2N1613	25p	2N3866	£1.60	ACY23	25p	BF195	25p	C428	37½p	NKT80218	92½p
2N1631	30p	2N3904	40p	ACY40	20p	BF163	37½p	C744	30p	NKT80219	92½p
2N1632	30p	2N3977A	40p	ACY41	20p	BF167	25p	D162F	40p	NKT80220	92½p
2N1638	27½p	2N3900	37½p	ACY44	40p	BF173	32½p	D162P	37½p	NKT80221	92½p
2N1639	27½p	2N3900A	40p	AD140	32½p	BF177	30p	D164	40p	NKT80222	92½p
2N1671B	£1.00	2N3901	97½p	AD149	37½p	BF178	30p	GET22	20p	OC20	75p
2N1711	25p	2N3903	35p	AD152	37½p	BF179	30p	GET113	20p	OC22	50p
2N1699	32½p	2N3904	35p	AD161	37½p	BF180	35p	GET114	20p	OC23	50p
2N1803	37½p	2N3905	37½p	AD162	37½p	BF181	32½p	GET118	20p	OC24	60p
2N2147	62½p	2N3906	37½p	AF106	42½p	BF184	25p	GET119	20p	OC26	60p
2N2148	57½p	2N4058	17½p	AF114	25p	BF185	42½p	GET120	52½p	OC27	60p
2N2160	57½p	2N4059	10p	AF115	25p	BF194	17½p	GET127	15p	OC28	27½p
2N2193	40p	2N4060	12½p	AF116	25p	BF195	20p	GET880	30p	OC28	62½p
2N2193A	42½p	2N4061	12½p	AF117	25p	BF196	42½p	GET887	30p	OC29	62½p
2N2194A	30p	2N4062	12½p	AF118	62½p	BF197	42½p	GET889	22½p	OC35	50p
2N2217	27½p	2N4244	47½p	AF119	20p	BF198	42½p	GET890	22½p	OC36	62½p
2N2218	32½p	2N4285	17½p	AF124	22½p	BF200	52½p	GET896	22½p	OC41	25p
2N2219	32½p	2N4286	17½p	AF125	22½p	BF224	20p	GET897	22½p	OC42	25p
2N2220	25p	2N4287	17½p	AF126	22½p	BF235	25p	GET898	22½p	OC44	20p
2N2221	25p	2N4288	17½p	AF127	17½p	BF237	22½p	MJ400	£1.17	OC45	12½p
2N2222	30p	2N4289	17½p	AF129	17½p	BF238	22½p	MJ420	£1.12	OC46	15p
2N2287	£1.07½p	2N4290	17½p	AF178	42½p	BF244	32½p	MJ421	£1.12	OC70	15p
2N2287	30p	2N4291	17½p	AF179	72½p	BFW61	47½p	MJ430	£1.02	OC71	15p
2N2287	30p	2N4292	12½p	AF180	32½p	BFX12	22½p	MJ440	35p	OC72	32½p
2N2368	17½p	2N4303	47½p	BF181	40p	BFX13	22½p	MJ450	97½p	OC74	32½p
2N2369	17½p	2N4304	47½p	BF182	40p	BFX29	30p	MJ481	£1.25	OC75	22½p
2N2369A	17½p	2N4305	47½p	BF183	40p	BFX30	30p	MJ490	£1.00	OC76	22½p
2N2410	42½p	2N5029	47½p	AF280	62½p	BFX42	37½p	MJ1890	£1.07	OC77	30p
2N2463	27½p	2N5030	42½p	AF211	32½p	BFX44	37½p	MJE340	62½p	OC81	30p
2N2484	32½p	2N5031	42½p	AF281	32½p	BFX65	67½p	MJE340	62½p	OC82	25p
2N2539	32½p	2N5032	42½p	AF282	32½p	BFX84	37½p	MJE341	62½p	OC83	25p
2N2540	32½p	2N5033	42½p	AF283	32½p	BFX85	32½p	MJE521	87½p	OC84	25p
2N2613	25p	2N5176	45p	AFY29	27½p	BFX86	25p	MPF102	42½p	OC39	32½p
2N2614	30p	2N5232A	30p	AFY36	25p	BFX87	27½p	MPF103	37½p	OC40	32½p
2N2646	52½p	2N5245	45p	AFY50	25p	BFX88	25p	MPF104	37½p	OC70	30p
2N2696	32½p	2N5246	42½p	AFY51	32½p	BFX89	62½p	MPF3838	32½p	OC200	40p
2N2711	25p	2N5249	37½p	AFY52	32½p	BFY10	32½p	NK7008	17½p	OC201	40p
2N2712	25p	2N5252	£2.25	AFY86	32½p	BFY11	10p	NK7013	47½p	OC202	75p
2N2713	27½p	2N5266	22½p	AU103	£1.25	BFY11	42½p	NK7124	42½p	OC203	42½p
2N2714	30p	2N5267	£2.62	ASZ21	42½p	BFY17	27½p	NK7125	27½p	OC204	42½p
2N2865	62½p	2N5305	37½p	BC107	12½p	BFY18	32½p	NK7126	27½p	OC205	90p
2N2904	30p	2N5306	40p	BC108	12½p	BFY19	30p	NK7127	27½p	OC206	90p
2N2904A	32½p	2N5307	37½p	BC109	12½p	BFY20	£1.80	NK7185	27½p	OC207	75p
2N2905	37½p	2N5308	37½p	BC113	20p	BFY21	42½p	NK7187	32½p	OC271	42½p
2N2905A	40p	2N5309	62½p	BC115	27½p	BFY24	45p	NK7210	30p	ORP12	62½p
2N2906	25p	2N5310	42½p	BC116A	47½p	BFY25	25p	NK7211	30p	ORP61	62½p
2N2906A	27½p	2N5354	27½p	BC118	32½p	BFY26	20p	NK7212	30p	P34A	22½p
2N2907	30p	2N5355	27½p	BC121	20p	BFY29	50p	NK7213	30p	T1834	40p
2N2923	15p	2N5356	47½p	BC125	35p	BFY41	50p	NK7214	22½p	T1844	12½p
2N2925	15p	2N5366	32½p	BC126	35p	BFY43	62½p	NK7215	22½p	T1845	12½p
2N2926	22½p	2N5367	37½p	BC140	37½p	BFY50	22½p	NK7217	42½p	T1846	12½p
Green	14p	2N5457	37½p	BC147	17½p	BFY61	22½p	NK7219	30p	T1847	12½p
Yellow	12p	2N8005	75p	BC148	12½p	BFY72	22½p	NK7220	22½p	T1848	12½p
Orange	12p	2N8020	£2.00	BC149	12½p	BFY73	22½p	NK7221	22½p	T1849	12½p
2N3011	30p	2N8102	50p	BC152	17½p	BFY86A	27½p	NK7222	22½p	T1850	12½p
2N3014	32½p	2N8103	25p	BC159	20p	BFY75	30p	NK7223	22½p	T1851	12½p
2N3053	25p	2N8104	25p	BC158	17½p	BFY76	42½p	NK7237	35p	T1852	12½p
2N3054	30p	2N8001	32½p	BC159	20p	BFY77	57½p	NK7238	35p	T1853	12½p
2N3055	75p	2N8002	35p	BC180	52½p	BFY79	67½p	NK7239	35p	T1854	12½p
2N3134	30p	2N8003	27½p	BC167	15p	BFW67	27½p	NK7240	27½p	T1855	12½p
2N3135	25p	2N8004	30p	BC168B	14p	BFW69	25p	NK7241	27½p	T1856	12½p
2N3136	25p	2N8128	70p	BC168C	15p	BFW60	25p	NK7242	20p	T1857	12½p
2N3136	25p	2N8140	77½p	BC169B	14p	BPX25	£1.85	NK7243	62½p	TIP29A	50p
2N3139	25p	2N8141	72½p	BC169C	15p	BPX29	£1.80	NK7245	30p	TIP30A	50p
2N3291	30p	2N8142	55p	BC170	12½p	BPY10	£1.45	NK7261	20p	TIP32A	62½p
2N3291A	30p	2N8143	57½p	BC171	15p	BRY39	47½p	NK7262	20p	TIP33A	75p
2N33											

CASH & CARRY GOODS

Sinclair 2000	£24
Sinclair 3000	£33
Metrosound ST20	£27
Teleton 203	
(Demonstration)	£17
Teleton F2000	
Tuner/Amp.	£31
Teleton SAQ 206	£19.75
Arena F212	£26

Please add 50p carr. per amplifier. Other Amplifiers — Tuners — Tape Recorders etc. Prices on application.

SINCLAIR Project 60
SAVE nearly £1 Normal price £23.90

Designed for building into plinths etc., complete with two 230 Output stages **£17** plus 50p carr.

(20 watt) and power supply unit.
Send S.A.E. for full technical brochure.

This MONTH'S Best Buy . . .

AKG K50 Dynamic Stereo headphones
Complete with spare ear muffs.

Total (value £10.40) Our Price **£5.90** + 23p p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

- * High-fidelity reproduction due to broad frequency response (20-20,000Hz)
- * Substantially increased stereo effect
- * Headphones fit the head gently and do not shift
- * Earpieces fit ears snugly (Cardanic suspension)
- * Tone quality superior to conventional loudspeakers.
- * Only expensive studio loudspeakers can match the reproduction quality of the K50.
- * Music can be reproduced at concert hall volume (1), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.

GARRARD SP25 mk III £12.50 Plus 50p carriage
Normal price £15.57

Wired with mains cable and 5ft. twin screened stereo cable, 5 pin din plug, 53p extra.
APT9 Complete with base and cover £25 plus 75p carriage.

PLINTH AND COVER SUITABLE FOR GARRARD RANGE £5.25 plus 50p p. & d.

PLUGS

Pack 107 5-Pin Din	20p
Pack 108 3-Pin Din	18p
Pack 135 1/2" Jack	25p
Pack 136 1/2" Jack Stereo	48p
Pack 103 Loudspeaker Plug	15p
Pack 100 Phono Plug	6p
Pack 230 3-Pin Socket	23p
Pack 236 5-Pin Socket	30p
Pack 234 Loudspeaker Socket	30p

Ready-made Leads

3-pin to 3-pin Din	63p
3-pin to open end	53p
5-pin to 5-pin Din	80p
5-pin to open end	65p
5-pin to 4 phono plugs	93p
Speaker lead Din to spade 12ft	38p
Extension lead Din plug to socket 12ft	63p

All leads approx. 6ft. in length. Post free, by return.

Replacement Stereo DIAMOND STYLII

9TA 9TA 9TAHC GP91 ST4 ST9 75p each
EY26 GC8 +13p p. & p.

others on request +13p p. & p.

Countdown SPEAKER
Teak Cabinet

£12 insurance & carr. 38p

A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.

EMI 20w matched loudspeaker set 3-50
Frequency range: 20 to 20,000Hz. **£7.50**
Normal price £13 plus 40p p. & p.

EMI 10w matched loudspeaker set 450
Our price **£3.75** plus 25p p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency units with associated crossover network. Frequency range 55 to 13,000Hz. The cone of the bass unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies. Also 150 KIT 10W **£2.50** plus 40p p. & p. 3, 8 or 15 ohms

Magnetic cartridges

Diamond stylus **£4.75**
plus 13p p. & p.
Today's value **£8.**

Stylus replacement can be carried out without removing cartridge. Fully guaranteed.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) £1.25 + 13p. p. & p.

SONOTONE Cartridge ...
(Fitted Diamond Stylus)
(Ceramic) list price £4.10

Sensitivity: 9TAHC 55mV/cm/sec **£2.50**
rms minimum at 45° at plus 1,000Hz measured on 13p Decca SXL2057 p. & p.

J. J. FRANCIS
(WOOD GREEN) LTD
123 ALEXANDRA ROAD, HORNSEY, LONDON, N.8. Tel: 01-888 1662

Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics
Your first day on Television: 7th September, 1971



This is your opportunity to train as a television and radio engineer on our full-time 2 year College Diploma Course. That is the way to get into a rapidly growing industry with a tremendous demand for skilled technicians. You will be given theoretical and practical instruction on colour television receivers, following a syllabus specially designed to cover the new City and Guilds Radio, Television and Electronic Technicians' Course.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Complete the coupon below and we will send you the details about training for an exciting, new career.

To: The Pembridge College of Electronics, (Dept. PW4), 34a Hereford Road, London, W2 5AJ.

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME

ADDRESS

HEARING AID AMPLIFIERS

(Ex behind ear deaf aids) 2 transistors on tiny P.C. board with volume control—whole thing only about half as big as Oxo cube. £1.75 or with sub-miniature microphone and L.S. attached £3.50.



MAINS OPERATED SOLENOIDS

Model 772—small but powerful 1/2" pull—approx size 1 1/2" x 1 1/2" x 1 1/2" 60p.
Model 400/1 1/2" pull Size 2 1/2" x 2" x 1 1/2" 75p.

Model TT10 1 1/2" pull Size 3" x 2 1/2" x 2 1/2"—£1.80 plus 20p post and insurance.

BEST QUALITY BRITISH MADE ELECTRICAL PLUGS AT APPROX. HALF PRICE


15 amp 3 pin 10p each or ten for 90p, 5 amp 3 pin 8p each or ten for 70p, 5 amp 2 pin 5p each or ten for 45p.

DRILL CONTROLLER NEW IKW MODEL

Electronically changes speed from approximately twelve to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 13p post and insurance. Made up model also available, £2.25 plus 13p post & p. 14p.

MAINS MOTOR

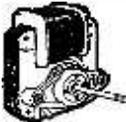Precision made as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.



NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 60p doz. Plastic pusher suitable for operating, 5p each, 45p doz.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 18p each, £1.80 dozen, your assortment



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

MICRO SWITCH

5 amp, changeover contacts, 9p each, £1 doz. 15 amp on/off 15p each, 15 amp changeover 15p each, 10 for £1.85.



MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Class 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2" x 2" x 2 1/2". £1 each.




PAPST MOTORS

Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. £1.50 each. Postage one 23p, two 33p.



EXTRACTOR FAN

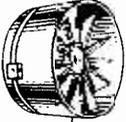Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bath rooms, factories, changing rooms, etc., it's quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets, £2 plus 36p post and ins.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (Class B working). Takes the place of any of the following batteries: PF1, PF3, PF4, PF6, PF7, PF9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 85p, plus 18p postage.


24V BUZZER.

Made by G.E.C. in brown heavy bakelite case, these work off AC mains through step down transformer. Price 40p each.

9 PIN PLUG AND SOCKET.

Suitable for connecting multicore flex to equipment. Socket size approx. 1 1/2" diameter. Plug size 9/10" diameter with flex entry. 25p pair.

OUT OF SEASON BARGAIN TANGENTIAL HEATERS

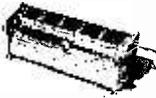

Once again we are able to make a special bargain offer of these very popular heating units. Tangential heaters although brought out a few years ago are still the latest and best type as nothing has yet been made which could be called an improvement on them. The tangential unit is still the only one used in good quality heaters made by Hoover, G.E.C. and all the famous names. The unit comprises quiet running AC induction motor with special bearings, the tangential impeller and a 2 section heater element which allows switching half and full heat in the case of the 2 k.w. and one third—two thirds and 1" heat in the case of the 3 k.w. These heaters are also fitted with a safety cutout to cut the heaters should the impeller stop or the air flow be impeded. They are free standing and need only the simplest of cases, even a wooden cabinet is suitable or the plinth of the kitchen cabinet. Lots of customers missed our special Summer offer of these heaters last year so order early. 200/240 2 k.w. model £2.50. 200/240 3 k.w. model £3.50. Control switch heaters only 25p or two-heat, cold-blow and off 35p. Postage and insurance 33p on heaters.

STANDARD WAFER SWITCHES

Standard size 1 1/2" wafer—silver-plated 5-amp contact, standard 3/4" spindle 2" long—with locking washer and nut.

No.	2	3	4	5	6	8	9	10	12
of Poles	way	way	way	way	way	way	way	way	way
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	70p	70p
3 poles	40p	40p	40p	40p	70p	70p	70p	85p	85p
4 poles	40p	40p	40p	70p	70p	70p	70p	£1.20	£1.20
5 poles	40p	40p	70p	70p	85p	85p	85p	£1.45	£1.45
6 poles	40p	70p	70p	85p	85p	85p	85p	£1.70	£1.70
7 poles	70p	70p	70p	85p	£1.20	£1.20	£1.20	£1.95	£1.95
8 poles	70p	70p	70p	85p	£1.20	£1.20	£1.20	£2.20	£2.20
9 poles	70p	70p	85p	85p	£1.45	£1.45	£1.45	£2.45	£2.45
10 poles	70p	70p	85p	£1.20	£1.45	£1.45	£1.45	£2.70	£2.70
11 poles	70p	85p	85p	£1.20	£1.70	£1.70	£1.70	£2.95	£2.95
12 poles	70p	85p	85p	£1.20	£1.70	£1.70	£1.70	£3.20	£3.20

AMPLIFIER MAINS TRANSFORMER

50v 1 1/2 amp. Upright mounting with fixing brackets and metal shrouds to contain magnetic field, 50 c/s primary, tapped 110v, 117v, 210v, 230v and 250v. 2 secondaries, one 50v 1 1/2 amp. other 6v 1 amp for pilot light, etc. £1.95, postage 30p.

THIS MONTH'S SNIP

BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £1.75 plus 20p postage.



COMPUTER TAPE

2,400 ft. of the best magnetic tape money can buy. Almost unbreakable and on a metal computer spool. Users have claimed successful results with video as well as sound recording 1" wide £1. 1 1/2" 85p. 1 3/4" 75p. P. & P. 33p extra. Spare spools 50p each. (Cassette to hold spool 50p each. No extra postage if ordered with tape, otherwise 30p extra.



CAPACITOR DISCHARGE IGNITION SYSTEM

Well proved that it helps starting and increases petrol economy. Also increases acceleration but saves contact wear. For details see Practical Wireless June. (Gives optional capacitor or standard ignition at the flick of a switch. Price £4.95

MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio is very pretty case, size 2 1/2" x 2 1/2" x 1 1/2"—complete with soft leather zippered bag. 7 transistor, ferrite rod. Loudspeaker.



In transit from the East these sets suffered corrosion as the batteries were left in them but when this corrosion is cleared away they should work—offered without guarantee except that they are new. Price only £1.25 less batteries plus 13p, post 6 for £7 post free. Pair of rechargeable batteries and charger 85p.

MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V. A.C. Good British Make. Unused. Size approx. 1 1/2" x 1".

Open construction	25p each	10 for £2.25
Single pole	32p each	10 for £2.80
Double pole	40p each	10 for £3.60
Treble pole	40p each	10 for £3.60

4 AMP VARIAC CONTROLLERS

With this you can vary the voltage applied to your circuit from zero to full mains without generating undue heat. One obvious application therefore is to dim lighting. Ex. equipment but little used—as good as new offered at approx. half price. 25 plus 75p. post and ins.



OVEN THERMOMETER WITH ALARM

Basically this is a thermometer which is calibrated between 500 and 900 deg. C using a sensor on a flexible lead. The second feature, however, is an alarm which can be set anywhere within the temperature range. When the temperature is reached a buzzer sounds. Presumably the buzzer could be replaced by a relay or contactor to work another device. Limited quantity only of these units, price £3.50, includes thermometer—scale—sensor and buzzer.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

ELECTRIC CLOCK SWITCH WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only £2, less than the value of the clock alone—post and insurance 14p.



P.W.

TREASURE TRACER

As described in this issue. Send today for price list of parts.

TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—5 sections—extends from 7 1/2 to 47in. Hole in bottom for 6BA screw, 38p. KNUCKLED MODEL FOR F.M. 50p.

QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12v. car model also available same price. Jug heater £1.50 plus p. & p. 14p.




THYRISTOR LIGHT DIMMERS

Will dim incandescent lighting up to 600 watts from full brilliance to out. Assembled and wired ready to install £3.



12 VOLT 1 1/2 AMP POWER PACK

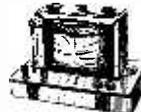This comprises a double-wound 230/240V mains transformer with full wave rectifier and 2000 m/10 smoothing. Price £1.50 + p. & p. 20p.



REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

Miniature. 1in. long x approximately 1/4in. diameter. Will make and break up to 1A up to 300 volts. Price 13p each, £1.30 dozen.
Standard. 2in long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 10p each, 90p per dozen.
Flat. Flat type, 2in. long, just over 1/16in. thick, approximately 1/4in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 30p each, 32p per dozen.
Small ceramic magnets to operate these reed switches 9p each, 90p per dozen.

PUSH BUTTON CHANGE OVER SWITCHES

This is a Honeywell micro switch mounted on a metal frame with spring loaded plunger to operate. Panel fixing by single 3/8" hole. Single Changeover switch 25p each or ten for £2.25, 2 changeover switch operated by single plunger 55p each or ten for £3.15, 3 changeover switches 45p each or ten for £4.05.



METER BOX

Designed to take 3 1/2" flush mounting meter. This has a 2 1/2" diameter hole with 3 meter fixing holes. Overall size of box 4" x 4" x 2 1/2" deep, hinged to a metal base 2 1/2" x 4 1/2" x 3 1/2" deep. Price 50p.

PILOT BULBS

6-8 Volts 15 amp tubular MES British made good quality. 1 dozen in a box. 25p per box.

5 AMP CONNECTOR STRIPS


This is the normal type of connector strip. 12 connectors with grub screws mounted in a line and mounted in polythene. 15p each £1.50 per dozen.

A New Service to Readers. A bulletin bringing news of new lines, special snips and "too few to advertise" lines will be posted to subscribers during first week of each month. The bulletin will be called "Advance Advert News" and the Subscription is 60p per year. Subscribers will also receive our completed 1971 catalogue when this is published.

J. BULL (ELECTRICAL) LTD.
Dept. P.W. 7, Park Street, Croydon CRO 1YD

COMET

HI-FI DISCOUNT WAREHOUSES

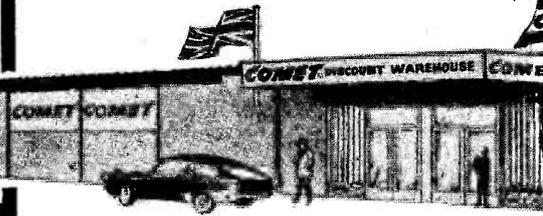

Rec. Retail Price Comet Price

STEREO AMPLIFIERS

ALBA UA 700	34.50	26.00
ARMSTRONG 521	56.00	42.50
*DULCI 207	26.00	17.50
DULCI 207M	32.00	21.95
FEROGRAPH F307	62.00	44.00
GOODMANS Mexamp	54.00	38.00
LEAK Stereo 30 Plus	56.50	43.00
LEAK Stereo 30 Plus, in teak case	62.50	47.95
LEAK Stereo 70	69.00	52.00
LEAK Stereo 70, in teak case	75.00	56.95
*LINEAR LT 66	21.00	17.00
METRO SOUND ST20	36.00	24.95
METRO SOUND ST20E	39.50	29.50
PHILIPS RH 591	79.00	61.50
PHILIPS RH 590	52.00	39.50
PHILIPS RH 580	29.00	23.00
PIONEER SA500	62.10	41.95
PIONEER SA700	98.00	68.95
PIONEER SA900	134.10	99.00
PIONEER Reverberation	45.50	31.95
ROGERS Ravensbourne	59.50	45.95
ROGERS Ravensbourne (cased)	64.00	49.50
ROGERS Ravensbrook Mk. II	47.50	36.50
ROGERS Ravensbrook (cased)		
Mk. II	52.50	41.50
SINCLAIR 2000	35.00	27.00
SINCLAIR PROJECT 60/2 X Z30/PZ5	23.90	16.50
SINCLAIR PROJECT 60/2 X Z50/PZ8/trans.	34.86	23.25
SINCLAIR AF7	5.95	4.95
SINCLAIR Neoteric	61.95	46.00
SINCLAIR 3000	45.00	34.95
TELETON SAQ 206 (new release)	29.00	18.50
VOLTEX 100w. Stereo Discotheque, 8 electronically mixed inputs	185.00	139.00

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.

TUNERS

*ARMSTRONG 523 AM/FM	53.76	42.00
*ARMSTRONG 524 FM	41.89	33.00
ARMSTRONG M8 Decoder	9.50	8.00
DULCI FMT. 7 FM	26.00	22.00
DULCI FMT. 7S Stereo	35.00	29.25
GOODMANS Stereomax	82.52	49.95
LEAK Stereofetic Chassis	66.50	52.00
LEAK Stereofetic in teak case	72.50	59.00
PHILIPS RH 890	47.00	38.00
PHILIPS RH 891	39.00	31.50
PIONEER TX500 AM/FM	77.94	63.50
PIONEER TX900 AM/FM	153.69	123.00
ROGERS Ravensbourne chassis	61.89	47.95
ROGERS Ravensbrook	45.01	38.00
ROGERS Ravensbrook (cased)	51.26	41.00
TELETON GT 101	45.50	31.95
TELETON 201X FM	36.00	27.50

All above Tuners are complete with MPX Stereo Decoder except where starred.

TUNER/AMPLIFIERS

AKAI AA 8500	229.00	181.00
AKAI 6800	142.53	112.60
ARENA R500	32.00	27.00
ARENA 2400	90.30	72.00
ARENA 2700	105.00	85.00
ARENA T9000	303.45	258.00
ARMSTRONG M8 Decoder	9.50	8.00
ARMSTRONG 521	81.89	74.50
ARMSTRONG 528	104.71	84.50
GOODMANS Module 80, 35w. R.M.S.	95.00	72.00
MIDLAND 19/542	49.56	37.50
PHILIPS RH 790	139.00	112.00
PIONEER SX770 AM/FM	160.43	128.00
PIONEER SX900 AM/FM	194.74	159.00
PIONEER 440	111.10	89.00
TANDBERG 1171 comp. with decoder	110.00	94.00
*TELETON F2000	51.50	39.50
TELETON T AT	105.00	77.95
TELETON 10 AT 1150w. RMS	160.00	143.00
TELETON TFS50	82.50	59.00
TELETON TFS 50LA MW/LW/VHF	87.50	63.50
*TELETON R.8000 with Speakers	63.25	37.50
TELETON CR55	120.00	87.00
TELETON GA101	37.50	28.50
WARRFEDALE 100.1	149.00	119.00

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges.

All the above Tuners and Tuner/Amplifiers include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.



COMET for after-sales service THROUGHOUT THE U.K.

Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goolle, Wakefield, Doncaster, and Bridlington

PICKUP ARMS

GOLDRING Lenco L75	12.33	10.50
GOLDRING Lenco L69	9.29	7.00
SME 3009 with S2 Shell	34.47	27.00
SME 3012 with S2 Shell	36.71	30.50

CARTRIDGES

GOLDRING 806	13.00	6.95
GOLDRING 800E	18.86	10.95
GOLDRING 800 Super E	26.01	19.50
*GOLDRING CS90 Stereo	5.20	4.25
*GOLDRING CS91E	7.81	6.25
GOLDRING G850	6.50	5.25
EMPIRE 1002E/X	63.00	32.50
EMPIRE 999VE/X	44.50	36.00
EMPIRE 998TE/X	27.60	22.50
EMPIRE 999SE/X	21.00	17.50
EMPIRE 999E/X	16.50	13.00
EMPIRE 999I/X	11.50	9.25
EMPIRE 909E/X	12.85	10.25
EMPIRE 909I/X	9.00	7.50
EMPIRE 90E/X	9.75	8.00
ORBIT Magnetic NM 22	Special Price	2.90
PICKERING V15 AC2	8.40	7.00
ORTOFON SL15E	29.65	23.75
ORTOFON 2X15K Transformer	7.00	5.25
SHURE M3DM	7.41	4.95
SHURE M31	12.05	8.95
SHURE M32E	11.10	8.25
SHURE M32-3	10.20	8.00
SHURE M44-5	11.10	7.95
SHURE M44-7	10.20	8.00
SHURE M-44C	10.20	8.00
SHURE M44E	12.05	8.25
SHURE M55E	12.95	9.50
SHURE M75G	17.60	14.00
SHURE M75-6	16.70	13.00
SHURE M75EJ	19.45	16.00
SHURE M75E-95G	23.15	18.00
SHURE M75E	21.30	14.50
SHURE V15-11	40.76	28.95
SHURE V15-11-7	38.90	29.00

Starred cartridges above are ceramic. All others are magnetic.

TURNTABLES

GARRARD AP76 turntable, fully wired complete with Goldring G.800 Cartridge base and cover. Special Price 30.95		
GARRARD SP25, Mk III fully wired with Goldring G800 Magnetic Cartridge. Complete with base, plinth and cover—Special Price 21.98		
GARRARD 2025 fully wired with Sonotone 9TAC Cartridge complete with base and cover. Special Price 15.50		
GOLDRING 705/P turntable, fully wired complete with Goldring G850 cartridge, base and cover 25.00 15.95		
DUAL 1219 transcription	60.40	50.00
DUAL 1209 transcription	42.62	35.00
GARRARD SP25 Mk III	16.45	11.90
GARRARD SL5 B	21.25	15.90
GARRARD SL75 B	39.20	28.90
GARRARD SL95 B	50.01	35.50
GARRARD 401	38.07	29.50
GARRARD SL72 B	33.11	27.90
GARRARD 3500, with GKS Cartridge	17.23	12.90
Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500. Special Price 4.00		
GARRARD 40B	13.84	10.97
GARRARD AP 76	28.88	21.50
GOLDRING GL69 Mk. II	26.63	21.25
GOLDRING GL69 P Mk. II	35.14	28.50
GOLDRING GL75	36.41	31.50


GOLDRING GL75 P	46.94	38.50
GOLDRING Covers for 69P and 75P	4.21	3.50
GOLDRING C99—plinth and cover for G99	11.45	9.90
GOLDRING G99	26.00	22.90
GOODMANS 3025	37.74	26.90
MCDONALD MP 60	35.70	11.50
MCDONALD 610	20.00	15.75
Base and Cover for MCDONALD MP 60 and 610 Special Price 4.50		
PHILIPS 228	20.00	17.00
PHILIPS GA 146	31.50	25.00
PHILIPS 202 Electronic	69.00	54.00
PIONEER PL 12A with base & cover	49.93	37.95
THORENS TX 25 cover	8.85	7.00
THORENS TD125	79.04	61.95
THORENS TD125AB	120.20	98.00
THORENS TD150A Mk. II	46.16	35.95
THORENS TD150AB Mk. II	49.96	42.95
THORENS TX11 Cover	4.43	3.95

SPEAKERS

B & W Model 70	159.50	121.95
B & W DM3	63.00	49.95
B & W DM1	32.00	25.50
CELESTION Ditton 120	24.00	18.00
CELESTION Ditton 15	32.00	25.50
CELESTION Ditton 25	65.00	50.95
GOODMANS Minister	35.70	11.50
GOODMANS Magister	62.50	47.95
GOODMANS Maxim	20.39	16.50
GOODMANS Mezzo 3	34.00	25.95
GOODMANS Magnum K2	44.00	33.00
KEF Cresta	22.17	18.00
KELETRON KN 500 4 speaker system (pair)	23.00	16.95
KELETRON KN 700 4 speaker system (pair)	27.50	19.95
KELETRON KN 1000 4 speaker system	19.25	13.95
KELETRON KN 1500 4 speaker system	24.75	18.95
KELETRON KN 2000 4 speaker system	28.75	20.95
LEAK 200	24.95	18.90
LEAK 300	32.50	23.95
LEAK 600	49.50	36.90
LOWTHER Acousta (with PM6)	45.50	35.50
LOWTHER Acousta (with PM7)	53.00	46.00
LOWTHER Ideal Baffle	35.50	30.00
METRO SOUND HFS 103 (pair)	25.00	17.95
METRO SOUND 202	21.50	15.95
METRO SOUND HFS 20 (pair)	39.00	25.95
METRO SOUND HFS 10 (pair)	27.44	22.95
PHILIPS RH481	11.00	8.95
PHILIPS RH482	11.00	14.95
SINCLAIR Q16	8.98	6.95
STE-MA 275 3 speaker system	23.10	15.95
WARRFEDALE Speakers		
Airedale	69.50	54.95
Denton	19.95	15.50
Super Linton	24.95	20.50
Melton	32.50	24.95
Dovedale 3	42.50	31.95
Rosedale	35.00	25.95
Triton (pair)	59.90	45.95
Unit 3 Speaker Kit	13.00	10.50
Unit 4 Speaker Kit	18.00	13.95
Unit 5 Speaker Kit	26.00	19.95

CHASSIS SPEAKERS

GOODMANS Axilette 8	8.10	6.50
GOODMANS Twinaxlette 8	9.17	7.50
GOODMANS Axiom 10	9.16	7.75
GOODMANS Axiom 80	28.31	23.75
GOODMANS Axiom 201	14.45	10.95
GOODMANS Axiom 301	20.70	15.75
GOODMANS Axiom 401	17.86	14.95
GOODMANS Audiom 8P	5.55	4.25

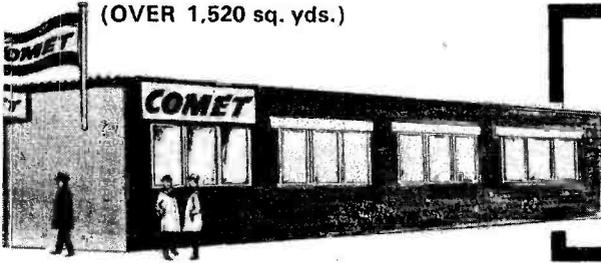

(OVER 1,520 sq. yds.)

OVER 1000 ITEMS ALWAYS IN STOCK

ALL FULLY GUARANTEED - WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

	Rec. Price	Retail Price	Comet Price
GOODMANS Audiom 10P	6-05	3-58	
GOODMANS Audiom 51	13-05	9-75	
GOODMANS Audiom 61	18-95	14-00	
GOODMANS 12P	12-37	10-00	
GOODMANS 18P	20-00	16-97	
GOODMANS Audiom 18P	34-00	26-97	
GOODMANS Twin Axium 10	10-23	8-25	
GOODMANS ARU 172	4-50	3-50	
GOODMANS Trebax 100	8-60	6-00	
GOODMANS Trebax 5K/20XL	9-70	7-50	
GOODMANS Midax	12-95	9-00	
GOODMANS Attenuator	3-55	2-50	
GOODMANS Crossover Networks XO1950/5000	9-75	7-25	
GOODMANS Crossover Networks XO1950	7-40	5-75	
GOODMANS Crossover Networks XO19000	2-65	2-00	
WHARFEDALE in Bronze/RS/DD	5-00	4-00	
WHARFEDALE Super 8/RS/DD	8-50	7-00	
WHARFEDALE Super 10/RS/DD	14-00	11-50	
WHARFEDALE WMT 1 Matching Transformer	0-84	0-75	

HI-FI STEREO SYSTEMS (complete)

ARENA MR15	145-00	115-95
ALBA UA552	47-50	35-95
ALBA UA662	62-97	47-95
DECCA Sound 603	72-50	58-95
DECCA Sound 604	72-50	60-95
DECCA Sound 1203	97-50	78-95
DECCALIAN 5, complete with stand.	65-50	52-95
EKCO SRG 609	88-50	69-95
EKCO ZU5	165-00	135-00
FERGUSON 3422	87-85	69-95
FERGUSON 3423	118-25	94-95
FERGUSON 3424	123-15	99-95
FERGUSON 3425	145-10	111-95
FIDELITY Music Master UA2	46-00	34-95
FIDELITY Music Master UA1	98-00	82-95
GOODMANS 3000 Suite	140-45	92-95
H.M.V. 2416	249-45	165-00
H.M.V. 204/5/6	202-85	165-00
K.B. KA1250, complete with two 653 speakers	72-00	59-95
K.B. KA1250, complete with two 651 speakers	83-00	65-95
LEAK 30/GOLDRING/WHARFEDALE	182-65	142-95
LEAK 70/THORENS/WHARFEDALE	226-87	175-00
MARCONI Unit 4	77-45	66-95
MARCONI Unit 3	86-00	69-95
METROSOUND Stereo 1010	82-30	65-95
PHILIPS 880/431/105	71-00	55-95
PHILIPS GF822	51-50	41-95
PHILIPS GF824	69-50	56-95
PHILIPS GF833	67-50	55-95
PHILIPS GF834	88-00	73-95
PHILIPS 882 (less L/S)	59-00	45-95
PHILIPS GF411	69-50	52-95
TELETON 2560F, with Stereo Radio	75-00	55-95
TOSHIBA SP8507	248-00	175-00
ULTRA 6405	79-95	66-95

TAPE RECORDERS AND TAPE DECKS

AKAI M10L	245-05	185-95
AKAI X200D	190-00	155-95
AKAI X5000 W/L	177-98	135-95
AKAI X330	342-57	285-95
AKAI X-330D	312-56	243-95
AKAI X-360	380-08	279-95
AKAI X-360 D-deck	318-92	243-00
AKAI 1800SD	199-42	185-95
AKAI 1710L	85-85	85-95
AKAI 1720L	97-21	77-50
AKAI CR80 8-track stereo recorder	115-03	99-95
AKAI CR80D 8-track stereo tape deck	95-00	79-95

	Rec. Price	Retail Price	Comet Price
AKAI 4000 4-track Stereo	124-90	97-95	
AKAI 4000 D 4-track Stereo deck	89-95	69-50	
BUSH TP 60 Cassette Tape Recorder	29-40	24-95	
BUSH TP 70 Cassette Battery/Mains Tape Recorder	29-95	23-95	
BUSH Discassette DC70	21-95	16-95	
FERGUSON 3252 4-track	104-30	83-95	
FERGUSON 3245 Twin track	38-00	29-95	
FERGUSON 3245 4-track	44-10	34-95	
FERGUSON 3247 4-track	49-85	39-95	
FERGUSON 3248 4-track	55-85	43-95	
FERROGRAPH 724	266-41	219-00	
FERROGRAPH 722	266-41	219-00	
FERROGRAPH 702 2 track tape deck	228-71	193-00	
FERROGRAPH 704/W 4 track tape deck	228-71	193-00	
GRUNDIG C200L deluxe Cassette	39-90	29-95	
GRUNDIG TK 141 (4-track)	61-85	49-95	
GRUNDIG TK 121 (Twin-track)	56-85	43-95	
GRUNDIG TK 146 (4-track Auto)	68-14	53-95	
GRUNDIG TK 149 4-track	57-63	47-95	
MIDLAND TC 144 cassette	18-10	13-95	
PHILIPS 2202 Cassette Tape Recorder	29-90	22-95	
PHILIPS 2204 cassette battery/mains	33-50	25-95	
PHILIPS 2205 Cassette Tape Rec.	43-15	34-95	
PHILIPS 3302 Cassette	23-90	18-95	
PHILIPS 4307	49-50	38-95	
PHILIPS 4404 2-track stereo recorder	95-00	73-95	
PHILIPS 4407 4-track stereo recorder	110-00	89-95	
PHILIPS 4303	43-00	34-95	
PHILIPS 4302 Twin Track Auto	39-00	32-00	
PHILIPS 4500 4-Track Stereo Tape Deck	126-00	98-95	
PHILIPS 4408 4-Track Stereo	139-00	109-00	
PHILIPS 4308 4-Track	60-50	45-50	
PHILIPS Cassette Stereo Tape Deck	54-00	45-95	
PYE Cassette Recorder/Radio (Batt./Mains)	45-50	36-95	
TANDBERG 1841 4-track Stereo Tape Deck	69-75	59-95	
TANDBERG 3021X twin track stereo	109-90	93-00	
TANDBERG 3041X 4-track stereo	109-90	93-00	
TANDBERG 4021X twin track stereo	180-00	150-00	
TANDBERG 4041X 4-track stereo	180-00	150-00	
TANDBERG 6021X twin track stereo	195-00	165-00	
TANDBERG 6041X track stereo	195-00	165-00	
TELETON 511 B /mains cassette	20-50	17-50	
TELETON FXB 510 D 4-track Stereo	67-50	52-00	
TELETON TRC 130 cassette, with VHF/AM radio, Battery/mains twin motors	41-75	31-90	
TELETON TC110 cassette, battery/mains	27-75	20-00	
TOSHIBA GT 840 S	110-00	67-95	
TOSHIBA GT 601v Twin Track	45-15	29-95	
TOSHIBA 850 SA	94-00	59-95	
WHARFEDALE Dolby DC9 Cassette Stereo Tape Deck	115-00	97-00	

BASES AND COVERS

GARRARD WBI Base	3-86	3-25
GARRARD W84 Base	5-99	4-75
GARRARD SPC 1 Cover	3-74	3-00
GARRARD SPC 4 Cover	4-44	3-75
Special offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500	Special Price	4-00
GOLDRING Plinth 75	8-52	7-00
GOLDRING Plinth 69	8-52	7-00
GOLDRING Covers for 69P and 75P	4-21	3-50
THORENS TX25 (for TD125AB)	8-22	6-50
THORENS TX11 Cover	4-11	3-75
Base and Cover for TD 125	15-18	12-50
SME Plinth System 2000	39-20	31-25
MOTORBOARDS only	4-95	3-00

COMPLETE HI-FI SYSTEMS

Completely wired, mounted and ready for use.

	Rec. Price	Retail Price	Comet Price
GOODMANS AUDIO SUITE, Goodmans Maxamp stereo amplifier, Goodmans stereomax AM/FM Tuner with decoder. Pair of Goodmans Magnum K2 speakers, Garrard AP76 turntable in base, complete with cover and Goldring G800 Cartridge. Beautifully finished in walnut	257-13	169-95	
GOLDRING 705P turntable complete with G850 Cartridge, Midland Tuner/Amp., pair of Metrosound 103 Speakers	99-56	69-95	
GOODMANS Module 80 Tuner/Amplifier, Goodmans 3025 Turntable with Goldring G800 Cartridge with 2 Goodmans Minister Speakers	182-74	139-00	
METROSOUND 448 8-track stereo play-back unit complete with 2 HFS 10 Speakers	83-56	70-95	
GOLDRING 705P turntable complete with G850 Cartridge, Teleton 203 Amplifier, pair of Keleton KN500 Speakers	77-00	49-95	
TELETON Stereo 8 track tape Audio system complete with speakers	54-75	48-00	
GARRARD SP 25, Mk. III mounted in base, plinth and cover with GOLDRING G800 Cartridge, Teleton 206 Stereo Amplifier 12 watts RMS, and 2 KELETON KN500 Speakers, each speaker is a 4 speaker system	88-33	58-95	
PIONEER PL 12 turntable, Goodmans Maxamp, Shure M55E Cartridge, 2 Keleton KN 700 speakers (each speaker cabinet contains 4 speakers)	144-38	105-00	
GARRARD AP76 turntable complete with Goldring G800 Cartridge, base and cover, Rogers Ravensbrook Amplifier in teak case and 2 Goodmans Minister Speakers	142-51	108-50	
LEAK 30/THORENS/WHARFEDALE	182-65	142-95	
GOLDRING GL 75P mounted in teak base with hinged perspex cover complete with GOLDRING G800E Cartridge, Leak Stereo 30 Plus Amplifier in Teak case, 2 GOODMANS Mezzo 3 Speakers	200-50	154-20	
THORENS TD 150AB Mk. III with TX11 dust cover, SHURE M55E Cartridge, LEAK Stereo 70 Amplifier in Teak case, 2 Wharfedale Dovedale 3 Speakers	226-87	175-00	
THORENS TD 125AB Electronic Turntable complete with cover, SHURE V15-11 Cartridge, GOODMANS Maxamp, GOODMANS Stereomax AM/FM Tuner, 2 GOODMANS Magister Speakers	422-48	309-00	

Complete Price List FREE on request!

COMET HIGH FIDELITY DISCOUNT WAREHOUSES

(Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407906 and 407877
 (Dept. P.W.) 68A Armley Rd. (Artist St.), Leeds LS12 2EE Tel. 32055 (5 lines)
 (Dept. P.W.) Teesway, Portrack Lane, North Teesside Tel. 66132/65215
 Industrial Estate, Teesside, TS18 2RH

(Service Dept., New Road Side, Horsforth, Leeds)

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) or, if Securicor delivery required, add £1.50 only. Make cheques, Money Orders payable to "COMET".



All in-stock items delivered by **SECURICOR** WITHIN 72 HOURS

(Add £1.50 only for Securicor delivery)

ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

Open daily to the public from 9-0 A.M. until—

5-30 P.M. MON.
 1-0 P.M. TUES.
 8-0 P.M. WED.
 8-0 P.M. THUR.
 8-0 P.M. FRI.
 5-30 P.M. SAT.

Customers are welcome to call - ample car parking facilities

SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 850 or AT66 MAGNETIC STEREO CARTRIDGE as available. COMPLETE IN TEAK PLINTH WITH RIGID FERREX COVER.

Total list price over £29.
PREMIER PRICE
£19-90
 P. & P. 50p.

TAPE CASSETTES



C60	(60 min.)	37p	3 for £1.05
C90	(90 min.)	62p	3 for £1.80
C120	(120 min.)	87p	3 for £2.55

P. & P. 5p.

All cassettes can be supplied with library cases at 3p. extra each

PREMIER QUALITY MICROPHONES



Precision made, beautifully designed and offering reliability at reasonable price.

FANON MKO-47 MINIATURE DYNAMIC
 Frequency response 60-13,000 Hz. Impedance 50K ohms (-59 db). Can be used with stand, hand held or around neck. Diecast body, satin chrome finish. Features removable windscreen. Complete with 8ft. cable, stand adaptor and Lavalier cord.
PREMIER PRICE £5-97. P. & P. 20p.

FANON MKO-45 3-WAY DYNAMIC
 Frequency response 60-12,000 Hz. High impedance. Complete with 8ft. cable, table stand and Lavalier cord.
PREMIER PRICE £2-87. P. & P. 20p.

FANON MKC-54 DYNAMIC
 Frequency response 80-12,000 Hz. Impedance 50K ohms (-80 db) and 150 ohms (-71 db). On/Off switch. Complete with 20ft. cable and stand adaptor.
PREMIER PRICE £8-97. P. & P. 20p.



E.M.I. 13x8in. HI-FI SPEAKERS
 Fitted two 2 1/2in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new.
£3-47 P. & P. 40p

METER BARGAINS



MODEL GT-800 MULTIMETER
 A precision made pocket sized test meter, ideally suited for testing electronic circuits or electronic appliances. Supplied complete with test lead and batteries. RANGES—DC Voltages: 10, 50, 250, 1,000V (1,000 opV). AC Voltage: 10, 50, 250, 1,000V (1,000 opV). DC Current: 1mA, 100mA. Resistance: 0-150K ohms. Decibel: -10 +22dB (at AC 10V range) £2-47. P. & P. 17p.



MULTIMETER 20,000 O.P.V.
 Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size: 4 1/2" x 3 1/2" x 1". RANGES D.C. Voltages 0-5-25-50-250-500-2500V. A.C. Voltages 0-10-50-100-500-1000V. D.C. Current: 0-50µA-2-5mA-250mA. Resistance: 0-6000 ohms 0-6 megohms (300 ohms and 30 Kohms, at centre scale). Capacity: 10 µF to +0.01µF, -0.01µF to -1µF. Decibels -20 to +25dB. £4-90. P. & P. 17p.



MODEL CT-62 MULTITESTER
 RANGES—DC Voltages: 0, 5, 25, 100, 500/1,000V (20,000 ohms/V). AC Voltages: 0, 5, 25, 100, 500, 1,000V (10,000 ohms/V). DC Current: 0, 50µA, 0, 5, 50, 500mA. Resistance: 0, 5K, 600K, 6M, 60M ohms. Decibels: -20 db to +92 db in 5 ranges. £5-82. P. & P. 17p.

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP5 3" 250'	P.V.C.	28p	DT6 5 1/2" 1800'	POLYESTER	£1-12
TT8 3 1/2" 450'	POLYESTER	37p	TT6 5 1/2" 2400'	POLYESTER	£1-87
SP5 3 1/2" 600'	POLYESTER	57p	SP7 7" 1200'	P.V.C.	62p
SP5 5" 800'	P.V.C.	42p	LP7 7" 1800'	ACETATE	76p
LP5 5" 900'	P.V.C.	50p	DT7 7" 2400'	POLYESTER	£1-25
DT5 5" 1200'	POLYESTER	76p	TT7 7" 3600'	POLYESTER	£2-50

TAPE SPOOLS 3" 10p, 5", 5 1/2", 7" 9p.
 Post and Packing 3" 5p, 5", 5 1/2", 7" 10p. (3 reels and over Post Free).



PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639
 HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



We'll give you the chance you didn't take at school.



'O' level standard in Maths, and Science or English, could get you a great career in today's Navy. We'll train you to be one of our top technicians, working on space-age equipment and earning £2,000 a year at 24. If you're 15 1/2-17 1/2 send for our free book.

APPRENTICESHIPS

Name _____

Address _____

Date of birth _____

(Enquiries from U.K. residents only)

Royal Naval Careers Service (830QM1),
 Old Admiralty Bldg., Whitehall,
 London S.W.1. Please send me,
 without obligation, your free booklet,
 "Royal Navy Technician Apprenticeships".



SPECIAL PURCHASE!

BRAND NEW FM MULTIPLEX STEREO DECODER UNITS.

Manufactured by PHILIPS. Size 2" x 3 1/2" x 1 1/2". All transistor 24v. at 6 mA. Supplied pre-aligned with full circuit diagram and connection details. **24 each Post Free**

FEW ONLY—LEAK MK 1 TRANSCRIPTION PICK-UP ARMS

Using the world famous gimbal pivot system. Complete but less pick up head. **22-50 P. & P. 20p**

INPUT MATCHING TRANSFORMER

Beautifully made in brass. Metal cylindrical case for minimum hum pickup. Size 1 1/2" high x 1 1/4" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick up from low to high impedance or vice versa. **75p each Post Free**

BLACK ANODISED 16s. ALUMINIUM HEAT SINKS

For TO3, complete with mica's & bushes. Size 2 1/2" x 3" approx. **25p pair P. & P. 5p.**

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speaker from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response: $\pm 3dB$ 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: $\pm 3dB$ 12-15,000 Hz. Bass boost approx. $\pm 12dB$. Treble cut approx. to -10dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES
AMPLIFIER KIT .. **£10-50 P. & P. 15p**
POWER PACK KIT .. **£3-00 P. & P. 30p**
CABINET .. **£3-00 P. & P. 30p**
(Post Free if all units purchased at same time)
Full after sales service

SPECIAL PURCHASE OF MANUFACTURERS' SURPLUS

All Transistor P.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. P.M. RF Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s output) which can be connected to standard built on printed circuit panel and fully screened. Extremely stable over range 88-108 Mc/s. Brand new and pre-aligned. Size 2 1/2" h x 1 1/4" w x 2 1/4" d. For 6v D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. **LIMITED NUMBER. Only £2.25 post free.** Connection details supplied.

HIGH GRADE COPPER LAMINATE BOARDS.

8 x 6 x 1/4 in. FIVE for 50p. P. & P. 13p.

TELESCOPIC AERIALS WITH SWIVEL JOINTS. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to 23 1/2 in. approx. Maximum diameter 3in. **25p each P. & P. 5p.**

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2 in. wide x 3in. deep. Price **£1.75 P. & P. 30p.**

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 0-40 at 500mA. **70p. P. & P. 13p.**

Pri. 200/240v. Sec. 12-0-12 at 1 amp. **85p. P. & P. 13p.**

Pri. 200/240v. Sec. 10-0-10 at 2 amp. **£1.38. P. & P. 30p.**

Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. **65p. P. & P. 13p.**

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Uynair front. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitter with E.M.I. Ceramic Magnet 13" x 8" base unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedances.

OUR PRICE £8.40 Carr. 65p

Cabinet Available Separately **£4-50 Carr 60p**
Also available in 8 ohms with EMI 13" x 8" base speaker with parasitic tweeter **£8-50 Carr. 65p**

LOUDSPEAKER BARGAINS

3" x 4 ohm 50p, P. & P. 8p. 5in. 3 ohm 80p, P. & P. 15p. 7 x 4in. 2 ohm £1-05, P. & P. 20p. 10 x 6in. 3 or 15 ohm £1-90, P. & P. 30p. E.M.I. 8 x 8in. 3 ohm with high flux magnet **£1-62. P. & P. 20p.** E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet **£2-10 (16 ohm £2-25), P. & P. 30p.** E.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network **£4-20, P. & P. 30p.** E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm **£2-25 P. & P. 30p.**

BRAND NEW 12in. 15w. H/D Speakers. 3 or 15 ohms. Current production by a well-known British maker. Now with Hifur ceramic ferrobar magnet assembly **25-50. Guitar models: 25v. £6-50, 35v. £8-50. P. & P. 38p.** E.M.I. 3 1/2in. HEAVY DUTY TWEETERS. Powerful ceramic magnet. Available in 3 or 8 or 15 ohms **93p each. P. & P. 13p.**

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm **£2-20, P. & P. 30p.**

35 ohm SPEAKERS 3in. only **68p P. & P. 13p.**

VYNAL & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1-75 yd., our price 75p yd. length. P. & P. 15p (min 1 yd.) S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexfoam ear-muffs. Wired and fitted with standard stereo 3 1/2 jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. **PRICE £2-95, P. & P. 15p.**

SINGLE HEADPHONE. With aluminium headband. Approx. 200 ohms. **25p. P. & P. 8p.**

CRYSTAL MIKES. High Imp. for desk or hand use. High sensitivity. **95p. P. & P. 25p.**

HIGH IMPEDANCE CRYSTAL STICK MIKES. **OUR PRICE £1-05, P. & P. 8p.**

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 20dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price **85p. P. & P. 13p.**

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST. Fitted mono 4 1/2 stylus and cartridge for LP/78. **ONLY £1, P. & P. 13p.**

QUALITY RECORD PLAYER AMPLIFIER MK II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. **PRICE £3-75 P. & P. 40p**

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. **PRICE £4-85 P. & P. 50p.**

DELUXE QUALITY PORTABLE R/P CABINET MK II. Durable motor board size 14 1/2 in. clearance 2in. below 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT80 and SP25). Size 18 x 15 x 8in. **PRICE £3-95. P. & P. 60p.**

10/14 WATT HI-FI AMPLIFIER KIT


A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good HF and cut. Valve line-up 2 EL84s, ECC83, ECR8 and ECR8 rectifier. Simple instruction booklet 15p (Free with parts). All parts sold separately. **ONLY £7-97 P. & P. 55p.** Also available ready built and tested complete with std. input sockets, **£9-97. P. & P. 55p.**

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p; V15/10 50p; OC71 25p; OC76 30p; AF17 15p; 2G339 (NPN) 15p.
Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 £1-25; ORP12 Cadmium Sulphide Cells 55p. All post free.

SPECIAL PURCHASE! SPEAKER CABINET FROM FAMOUS MAKER!

Beautifully made all wooden construction cabinet with medium walnut finish front. Roid anodised aluminium grille and dark sides. Approx. size overall 11 1/2" high x 8" deep x 13 1/2" wide at base. Easily removable baffle cut out for 8" speaker. Fibre board back. Could accommodate amplifier or radio together with speaker. An expensively made cabinet at a give away price. **LIMITED NUMBER ONLY £1-38 Post Free.**

DE LUXE STEREO AMPLIFIER

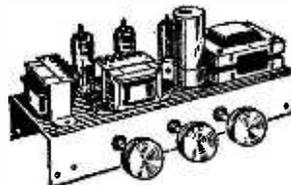

A.C. mains 200-240 v. Using very heavy duty fully isolated mains transformer with full wave rectification circuit and 15 valve smoothing with negligible hum.

Valve line up:—2 x ECL86 Triode Pentodes, 1 x E230 as rectifier. Two dual potentiometers provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Pull negative feedback in a carefully calculated circuit, allows high volume levels to be used without audible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. **PRICE £2-92 P. & P. 45p**

4-SPEED RECORD PLAYER BARGAINS
Main models. All brand new in maker's packing.
LATEST B.S.R. G109/AT1 4-SPEED AUTOCHANGER. With latest mono compatible cartridge **£8-97 Carr. 50p.** With stereo cartridge **£7-97 Carr. 50p.**
SUITABLE PLINTH UNIT FOR ABOVE with rigid plastic cover. **25-75 complete P. & P. 50p.**
LATEST GARRARD MODELS. All types available 1025, 2025, SP25, 3000, AT60 etc. S.A.E. for latest Prices!
PLINTH UNITS cut out for Garrard Models, 1025, 2025, 2000, 3000, 3500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. **OUR PRICE £5-75 complete. P. & P. 50p.**

LATEST AGOS GP91/180 mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. **£1-50 P. & P. 8p.**

SONOTONE STABCOMPATIBLE STEREO CARTRIDGE
T/O stylus Diamond Stereo LP and Sapphire 78. **ONLY £2-50 P. & P. 10p.** Also available fitted with twin Diamond T/O stylus for Stereo LP. **£3. P. & P. 10p.**
LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. **£1-63 P. & P. 10p.**
LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. **Only £1-50 P. & P. 10p.**

3-VALVE AUDIO AMPLIFIER HA34 MK II.
Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E230 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£4-75. P. & P. 35p.**

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **£8-98. P. & P. 40p.**

HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 8.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. **FEW ONLY. BARGAIN PRICE £2.75 P. & P. 85p**

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES
A must for servicemen and home constructors. 1971 edition including many 1000's of British, U.S.A., European and Japanese transistors. **ONLY 40p Post 5p.**

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)


PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

LOOK!

PRACTICAL!

VISUAL!

EXCITING!

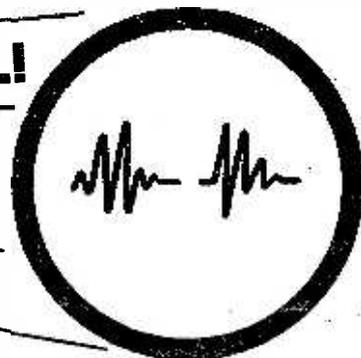

a new 4-way method of mastering


ELECTRONICS

by doing — and — seeing . . .

1

OWN and HANDLE a

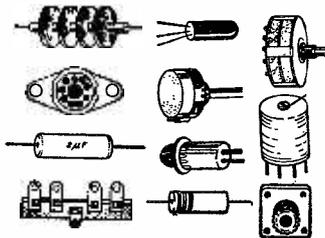
complete range of present-day **ELECTRONIC PARTS and COMPONENTS**



2

BUILD and USE

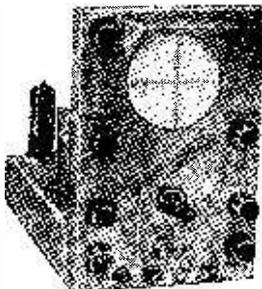
a modern and professional **CATHODE RAY OSCILLOSCOPE**



3

READ and DRAW and

UNDERSTAND CIRCUIT DIAGRAMS

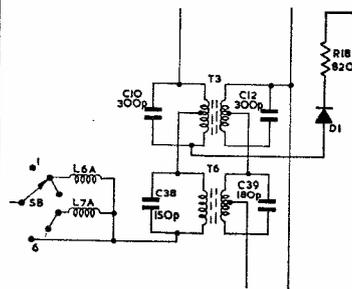

4

CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: *we do not employ representatives*

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PW8

PRACTICAL WIRELESS

VOL 47 NO 4

Issue 774

AUGUST 1971

Exhibitions R.I.P. ?

THERE are probably more exhibitions today than ever before, but those embracing areas of interest to readers of P.W. appear to have suffered the ravages of economics, indecision and wrong priorities.

The pre-war "Radiolympias" were intended for trade and public alike and even the last one in 1939 had lots of interest for the home constructor. Most hobbyists who could get to Olympia, went there. Post-war radio shows carried on the tradition, although with less and less for the amateur enthusiast—the trend was changing.

In the last decade, the unity of the radio industry began to deteriorate as first one, then another, major company broke away from the main exhibition (then at Earls Court) to hold their own private shows. In 1964 there were over ten "splinter" shows in London at exhibition-time and this mass exodus killed the public radio and TV show in this country. The costs of mounting stands in the exhibition halls available, plus the attitude of brushing off the public (the ultimate customers) were contributory factors.

Now, after some years of August trade-only exhibitions scattered all over London, manufacturers this year abandoned the traditional "showtime" period and held their shows during May. An attempt to get the industry together again under one roof failed. Next year, shows will again be held in the Spring. After that one needs a crystal ball. But still there seems to be no hope of anything for the public to see!

On another front, the various audio exhibitions overlap to some extent and are the subject of both praise and criticism. The Audio Fair gave up hotel rooms for the open spaces of Olympia and brought in photographic and then musical instrument interests. There has been talk of radio and TV exhibits. However, even if audio exhibitions do not please everyone, at least the public can get in!

Discounting the more specialised and professional orientated exhibitions, this leaves one more erstwhile important calendar date for the radio amateur—the RSGB Exhibition. We have seen this develop (or disintegrate?) from its unpretentious but delightfully social atmosphere of the Hotel Royal days, through various stages at Seymour Hall and Royal Horticultural Hall. It tried to change its angle, gave itself a pompous (and, we feel, misleading) name, lost its character and died. For this year there is to be no RSGB Exhibition.

A sad story for exhibition-minded radio enthusiasts. The problems will only be solved when we have more modern (and economic) exhibition halls for the larger shows and organisers, societies and manufacturers who are old-fashioned enough to think first of the public, then give them what they want.

W. N. STEVENS—*Editor.*

NEWS AND COMMENT

Leader	295
News . . . News . . . News . . .	296
On the Short Waves <i>by Malcolm Connah and David Gibson, G3JDG</i>	332
MW Column <i>by Charles Molloy</i>	334
Electronotes <i>by S. Ginsberg</i>	334
Practically Wireless <i>by Henry</i>	342

CONSTRUCTIONAL

Direct Conversion Receiver for 80m SSB/CW <i>by R. F. Graham</i>	298
QRP Transmitter for the LF Bands <i>by F. G. Rayer, G3OGR</i>	301
P.W. Treasure Tracer <i>by Halvor Moorshead</i>	316
X Take 20, No. 28, Touch Alarm <i>by Julian Anderson</i>	337

OTHER FEATURES


I.C. of the Month (G.E. PA264-265 Voltage Regulators) <i>by L. A. J. Ireland</i>	310
V.H.F. Interference Problems <i>by V. Capel</i>	311
SERVICING—Part 4 <i>by H. W. Hellyer</i>	323
The European Space Race <i>by John Chapman</i>	329
Going Back <i>by Colin Riches and Arthur Dow</i>	338

**SEPTEMBER ISSUE WILL BE
PUBLISHED ON AUGUST 6th**

©IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

NEWS... NEWS... NEWS...

12V Iron from Antex

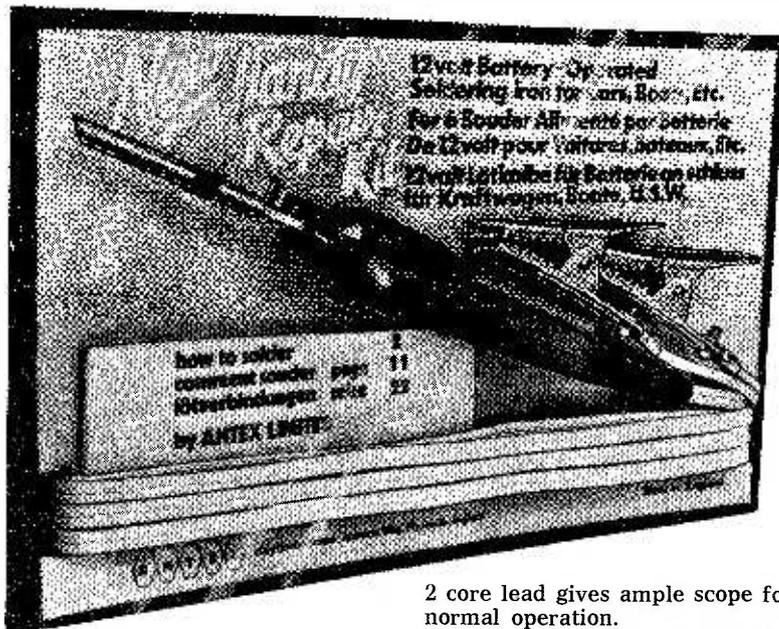

Antex have introduced the 'MES 12' soldering iron for operation from any 12 volt supply such as a car battery or accumulator.

Two large crocodile clips provide direct connection to the battery terminals and 15 feet of


2 core lead gives ample scope for normal operation.

This iron is absolutely ideal for use in conditions where a mains supply is not available. It is supplied in a durable plastic wallet which will 'house' the iron when not in use. Recommended U.K. price is £1.95. *Antex Limited, Mayflower House, Plymouth, Devon.*

Fudging irons

West Hyde Developments are asking: How often do you fudge a hole? They maintain that their taper reamers are the finest fudging irons available. These West Hyde reamers, due to their many flutes and cutting edges, will open a hole from $\frac{1}{8}$ in to $\frac{1}{4}$ in in a few seconds and the hole will be rounder than when drilled. On the many occasions when equipment cannot be put up on a drilling machine due to size and damaging the finish a West Hyde reamer in an ordinary hand brace will solve the problems without vibration and with little effort.

Two sizes are available, $\frac{1}{8}$ in. to $\frac{1}{2}$ in (3mm to 12mm) and $\frac{3}{8}$ in to 1in (9mm to 25mm). Prices are: small size £2.75+10p postage and packing. Large size £3.40+15p postage and packing.

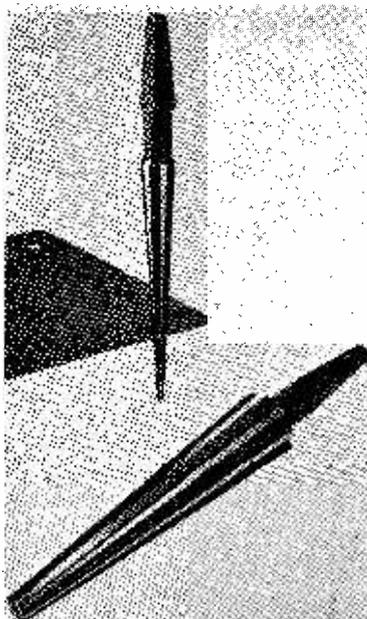

The I.B.C. 1972

One of the leading events in the world broadcasting calendar, the International Broadcasting Convention, will next be held in London from 4-8 September 1972. This will be the fourth IBC.

The Convention, which will be held at Grosvenor House, Park Lane, will comprise technical sessions and a comprehensive exhibition of the latest television and sound broadcasting equipment, both highlighting the future technological options available to broadcasting administrations.

IBC is sponsored by the Electronic Engineering Association, the Institution of Electrical Engineers, the Institute of Electrical and Electronics Engineers, the Institution of Electronic and Radio Engineers, the Royal Television Society and the Society of Motion Picture and Television Engineers.

All enquiries to *The Secretariat, International Broadcasting Convention, IEE, Savoy Place, London WC2R 0BL, England.*

Cut price stereo

Audio Supplies Limited have a supply of "The Great Musicians" stereo LPs and for £1.15p (p.p. free) they are offering three records. Each 10in. stereo LP is incorporated in an illustrated 12-page record book which gives an insight into the life of the composer and explains how his life influenced his work.


These LPs originally retailed for 13s. 11d. each and there are 55 titles from which to choose by 20 of the world's greatest composers. *Audio Supplies Limited, (Dept. P.W.) 50 Stamford Hill, London, N.16. Telex one 01-806 3611.*

Mobile rally diary

- July 11 Worcester, Upton on Severn.
- Aug 8 Woburn Abbey.
- Aug 15 Derby.
- Aug 22 Swindon, Wroughton Aerodrome.
- Aug 29 Stratford-on-Avon.

NEWS... NEWS... NEWS...

Zeiss Ikon P500 projector

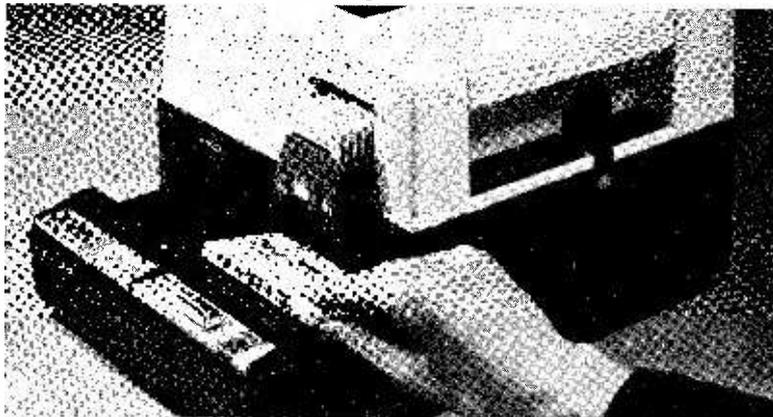

Basically, the P 500 consists of the Perkeo S 150 projector mounted on top of a Philips cassette tape recorder and loudspeaker to form a single unit. The projector can be used by itself in the normal manner and so can the tape recorder. Individual slides can be inserted in the gate without using the magazine—the importance of this feature will be appreciated by anyone who has done much slide-sorting. The forward and reverse movements of the magazine have also been retained and can be worked either manually (in which case you use a remote control cable instead of the push-buttons that are operated on the standard S 150) or else by means of the tape. To make the magazine move on to the next slide you put a short impulse on the tape; to make it move backwards to the slide shown previously you instead use a long impulse.

The Philips tape recorder is connected to the projector electrically. An extra record/playback head has been fitted to add the high-frequency impulse to the tape which changes the slides; the recorder itself is housed in a drawer which pulls out of the back of the unit. Space is provided to store spare cassettes, the microphone and various cables and accessories.

There are also, in addition to the mains inlet, four sockets. One allows you to connect an external speaker, useful when operating in a large hall. Another a combined input/outlet socket, lets you record from a source such as a microphone, radio, tape recorder, record player or mixer or alternatively to boost the output via an amplifier. A third allows the remote control for the projector to be fitted and the last one is for the cable that lets you put the slide change impulses on the tape.

The recommended price of the P 500 will vary according to the lens fitted, but with the Vario-Talon f3.5 70-120mm it is £222.18.6d (£222.92½), including £66.18.6d (£66.92½) P.T. The price includes the microphone and the impulse device.

IC's on the wall

Mr. J. Evans of the Mullard Press Dept., informs us that a large coloured chart produced by the Mullard Educational Service outlines the manufacturing process of integrated circuits. It measures nearly 30×22in. and has diagrams showing cut-away views of a silicon chip at different manufacturing stages as resistors, capacitors, diodes and transistors are formed

by various diffusion techniques. Captions alongside the diagrams detail what is done to the chip.

The chart is suitable for use in schools, colleges, universities and other training establishments where electronics is taught. Price 25p post free (send cash with order), it can be obtained from the Mullard Educational Service, Mullard Limited, Mullard House, Torrington Place, London WC1E 7HD.

Radio Brighton

From the start of programmes on Saturday, May 29, BBC Radio Brighton transmitted on 95.8MHz instead of 88.1MHz and the effective radiated power increased from 75 to 500W.

Lexor's board

Lexor Dis-Boards Limited now announce their brand new 'Mini-Board'. Having pioneered the multi-socket power board business more than ten years ago, Lexor are aware that 75% of users' needs can be met by only one model. This has now been specially designed and set up for quantity production and sells for only £3.95.

Four high-grade 13A ivory sockets are mounted in a slim blue leather-finish case and fed via 5ft. of cable from a ready-fitted 13A ivory fused plug. There is the characteristic red safety warning lamp, and the units can be used portable and free-standing or easily fixed permanently to walls, benches, etc. Simple cable extensions of 15ft. or 25ft. are available for the situations where the flex will not reach.


Illustrated brochures carrying full details, prices and sales terms are available from Lexor Dis-Boards Limited 25/31 Allesley Old Road, Coventry.



DIRECT CONVERSION RECEIVER

for 80 metre SSB/CW

R. F. GRAHAM

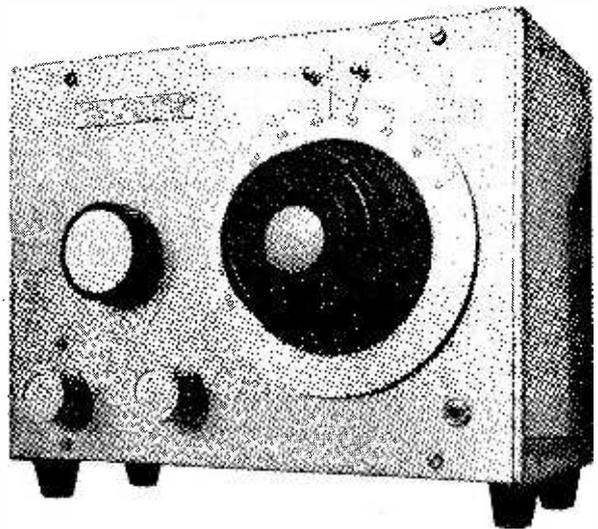

AS anyone who has become interested in the reception of single-sideband and c.w. (Morse) signals knows, the usual type of receiver for a.m. (amplitude modulation) reception is not able to resolve these transmission. When a beat frequency oscillator is present in the receiver, s.s.b. and c.w. can be received and modern communications receivers have a b.f.o. Older communications receivers having a b.f.o. allow reception of s.s.b. but with some difficulty unless the operator is experienced.

REQUIREMENTS

To clarify requirements for s.s.b./c.w. reception, Fig. 1A shows the stages of a typical superhet. (1) is the r.f. amplifier, which amplifies signals at the received frequency. (2) is the mixer, with oscillator (3), which may be separate, or combined in a single frequency-changer. Output from this section is at a fixed intermediate frequency, and passes through the i.f. amplifier (4) to the a.m. and product detector circuits (5). With domestic type receivers, this stage is an a.m. detector only where a.m. signals are demodulated, and passed through the audio amplifier (6) to the speaker (7).

Where the receiver is intended also for s.s.b./c.w. reception, (5) incorporates a product detector and a beat frequency oscillator (8) is also provided.

When s.s.b. signals are received, the b.f.o. supplies an unmodulated r.f. input, which replaces the "carrier", suppressed in s.s.b. transmission. This local carrier and the s.s.b. from the i.f. amplifier (4) are combined in such a way as to give an audio output, which passes to the audio amplifier and speaker.

For c.w. reception, the output of the b.f.o. (8) heterodynes with the c.w. coming through the i.f. amplifier (4) to give an audio tone, is amplified and fed to the speaker (7).

Fig. 1B is a direct conversion receiver and its much greater simplicity is obvious. (1) is the r.f. amplifier, tuned to the required signal in the usual way and fed to a product detector (2) which also receives input from the variable frequency oscillator (3) which covers the band upon which reception is wanted the circuit being so designed that an audio output is obtained directly from the product detector (2), which is amplified by stage (4) and routed to the speaker.

When receiving s.s.b. only those s.s.b. frequencies which combine with the v.f.o. frequency to give an audio output are heard. Thus the selectivity of the receiver does not depend upon the r.f. amplifier or product detector signal frequency circuits but upon the selectivity of the audio stages.

Thus apparent selectivity is achieved because unwanted signals are combined with the v.f.o. in stage (2) to give outputs which are not in the audio range of stage (4). To receive c.w. the v.f.o. is tuned to one side of the c.w. carrier to give an audio output from the product detector. This particular circuit is not really suitable for the reception of a.m. signals which require the local carrier to be phase-locked to the a.m. carrier.

The receiver described here will be found to give a very lively performance. As it is assumed that anyone just becoming interested in the reception of amateur s.s.b. and c.w. may not have much in the way of calibration or test equipment, the v.f.o. is designed to use three 1 per cent tolerance capacitors and a coil with adjustable core, so that it is only necessary to set the core to give 80m band coverage. The radio frequency circuits are peaked for best reception.


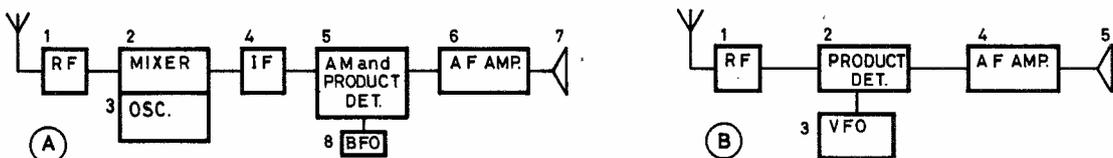


Fig. 1A shows the arrangement of the standard superhet while Fig. 1B illustrates the reduced number of stages required for a direct conversion receiver.

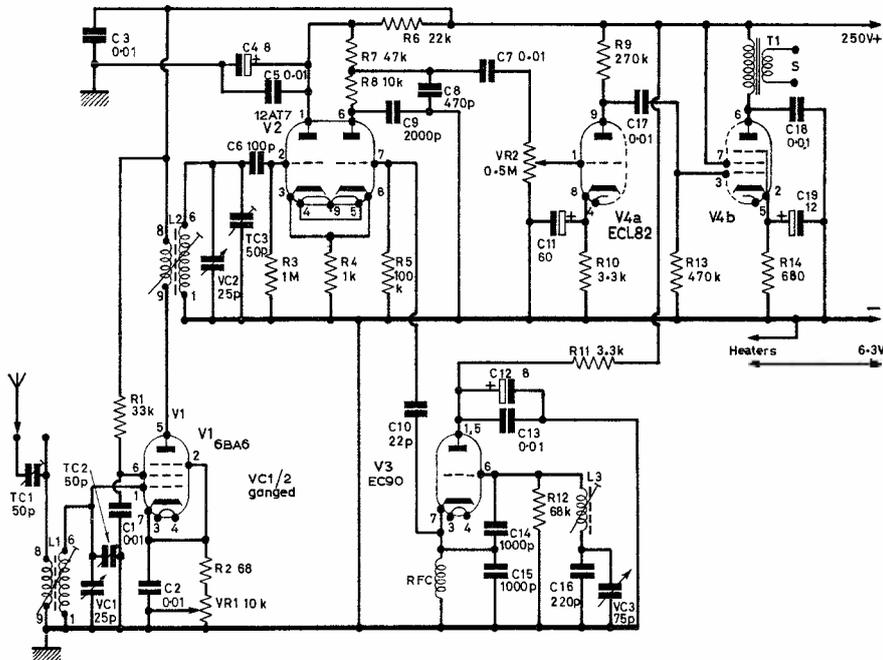

◀ Fig. 2. The complete circuit of the Direct Conversion Receiver. The main tuning dial (shown in the heading photograph) drives the v.f.o. tuning capacitor VC3.

▼ Fig. 3. Layout of the major components on top of the chassis with important dimensions shown.


CIRCUIT

Fig. 2 is the complete circuit. V1 (6BA6) is the r.f. amplifier, with gain control VR1. L1 and L2 are tuned by VC1/2, which is a small ganged capacitor for the r.f. tuning control.

V2 (12AT7) is the product detector, the wanted signal is present at one control grid and injection from the v.f.o. at the other grid. Audio output from the second anode passes to the 2-stage audio amplifier, VR2 being the volume control.

V3 (EC90) is the v.f.o. covering 3.5-3.8MHz, with a little to spare. VC3 is operated through a ball-drive and although tuning is quite critical it is eased by the narrow band covered by VC3. Coverage is determined by L3 and the three capacitors C14, C15 and C16, so it is only necessary to adjust the core of L3. Because of the large value of these capacitors changes in capacitance around V3 have little effect on its frequency.

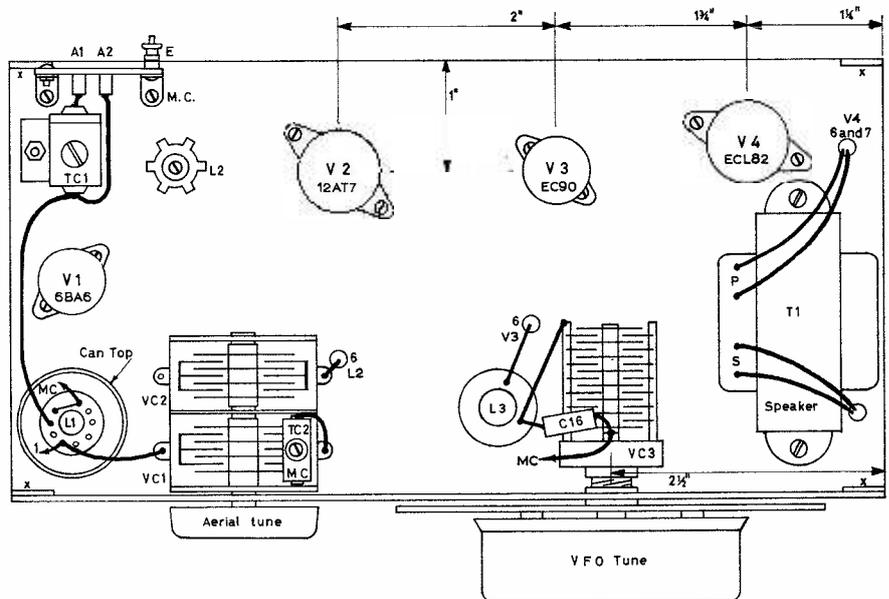C5 and C13 are r.f. by-pass capacitors with C4 and C12 in parallel with them to avoid hum from the h.t. supply and reduce audio feedback effects. The receiver is intended for use with a supply of about 220-250V at 40-50mA with the heaters drawing 1.53A at 6.3V.



CONSTRUCTION

The chassis, Fig. 3, is an 8×4in. "universal chassis" flanged member. This allows a complete case to be assembled by using two further 8×4in. members, top and bottom, with two 6×4in. members for the sides. The panel is 8×6in. and the surface of the chassis is 2in. above the bottom edge of the panel. Cut away the four corners "X" so that the 6×4in. sides fit round the chassis, allowing the box to be screwed together.

Flanges on the members listed are ready punched, and can be secured together with 4BA bolts and nuts while the receiver panel is secured to the top, bottom and side flanges with self-tapping screws. The case back should be of perforated metal, or have rows of ventilation holes.

VC1/2 is bolted to the panel, TC2 being soldered to a tag and VC1 as shown. The aerial coil L1 must be screened with the aluminium can supplied. The can lid is secured to the chassis by the fixing bush of L1. Leads for TC1 and VC1 pass out near the chassis. The lead from pin 6 passes through the chassis to tag 1 of V1. The normal adjusting screw of L1 cannot be reached because of VR1. So the core is removed, a shallow saw-cut is made across the end and it is replaced. Drill a hole in the screening can for this purpose and cut off about one-third of the screwed portion of the can, so that when it is tightly fitted it does not cut into the leads to TC1 and VC1.

TC1 is mounted on a strip of insulating material. A1 and A2 are optional aerial connections.

VC3 is fitted so that its spindle projects $\frac{9}{16}$ in. The ball drive is lined up so that it rotates freely and its lug is held with a long bolt with extra nuts. The lead MC from VC3 in Fig. 3 runs to a tag bolted to the chassis near L3.

The primary (P) connections of T1 run through to pins 6 and 7 of V4. Secondary leads (S) go to a small panel jack, for speaker or headphones.

Inductors. With the "Range 3" coils listed, Blue for L1 and Yellow for L2, adjustment of the cores and TC2 and TC3 gives easy coverage of 80m and VC1/2 need not be exactly 25pF.

L3 is 30 turns of 26 s.w.g. enamelled wire, close-wound on a $\frac{1}{2}$ in. diameter former with adjustable core. The winding is put near that end of the former furthest from the metal chassis and turns secured with Bostik 1.

Wiring. Wiring and components are shown in Fig. 4. The heater, grid and anode leads are run close to the chassis. Trimmer TC3 has one tag bolted to the chassis, so that it can be adjusted from the rear.

All connections should be reasonably short and direct, and run as shown. VFO wiring, especially to L3, C16 and VC3, is of stout wire, kept as short as possible.

Tag strips are used to support various small components. A 3-cored cable or coloured single flex

★ components list

Resistors :

R1 33k Ω 1W	R8 10k Ω
R2 68 Ω	R9 270k Ω
R3 1M Ω	R10 3.3k Ω
R4 1k Ω	R11 3.3k Ω 1W
R5 100k Ω	R12 68k Ω
R6 22k Ω	R13 470k Ω
R7 47k Ω	R14 680 Ω

All $\frac{1}{2}$ W 10% except as indicated.

VR1 10k Ω potentiometer, wire wound.

VR2 500k Ω potentiometer, log.

Capacitors :

C1 0.01 μ F 350V disc	C11 60 μ F 6V
C2 0.01 μ F 350V disc	C12 8 μ F 350V
C3 0.01 μ F 350V disc	C13 0.01 μ F 350V disc
C4 8 μ F 350V	C14 1000pF 1% SM
C5 0.01 μ F 350V disc	C15 1000pF 1% SM
C6 100pF SM	C16 220pF 1% SM
C7 0.01 μ F 350V	C17 0.01 μ F 350V
C8 470pF	C18 0.01 μ F 350V
C9 2000pF	C19 12 μ F 50V
C10 22pF SM	

VC1 2 x 25pF gang. (Jackson Type 02).

VC3 75pF variable. (Jackson Type C804).

TC1, 2, 3 50pF pre-set trimmers.

Valves :

V1 6BA6 (EF93)	V3 EC90
V2 12AT7	V4 ECL82

Chassis and Case :

- 2 off 6 x 4 in. sides, Type CU41B
- 2 off 8 x 4 in. sides, Type CU56A
- 1 off 8 x 6 in. plate, Type CU178
- 4 off Case feet, Type Z146
(all from Home Radio)

Miscellaneous :

- L1 Denco 'Blue' Range 3 (valve type).
- L2 Denco 'Yellow' Range 3 (valve type).
- L3, see text.
- Ball drive, (Jackson 4489/C) RFC, 2.5mH.
- 2 off B7G skirted valveholders and screens.
- 2 off B9A skirted valveholders and 1 screen.
- Knobs, tag-strips, output jack socket.
- T1, output transformer about 60:1 to carry 40mA.

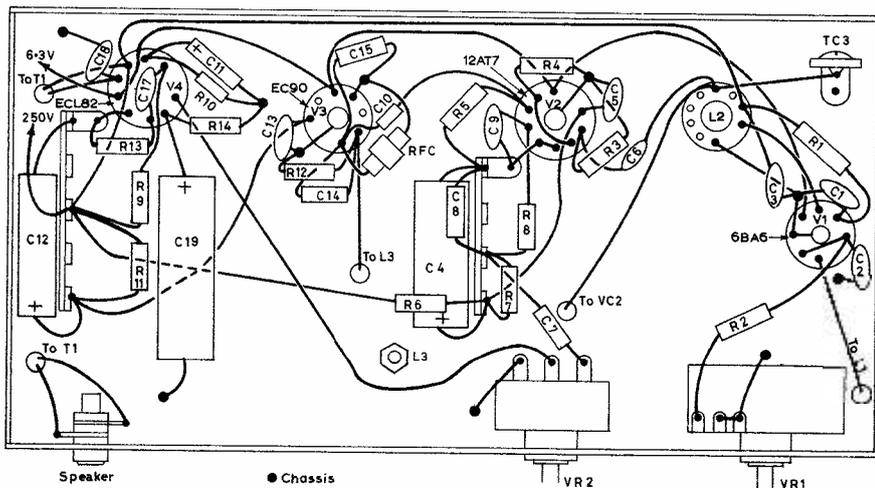


Fig. 4. Wiring guide for components underneath the chassis. Wiring around the v.f.o. valve V3 should be kept as short as possible to improve stability.

twisted together, is employed for h.t. positive, 6.3V, and common return connections—red may be used

IT is apparent that there is a good deal of interest in small transmitters for the low frequency bands. There are several reasons for this. Such equipment can be constructed at small cost, with easily obtained components, and only a modest power pack is needed to reach the maximum allowed power input of 10 watts in the case of the 160m band. Many newly licensed amateurs start with such equipment, and when using this power on the low frequency bands the chances of interference to TV are minimal.

The transmitter described here is primarily for 160m working, but will be found to be a very practical piece of equipment on 80m also, coverage of this second band being easily arranged. In addition, an end-fed aerial is often used for 160m, which will also generally perform well on 80m. The 80m band also offers greatly improved range over 160m and contacts during daylight, so it is well worth having.

to switch on the transmitter and to mute the receiver or speaker.

No external items of this kind are necessary with this transmitter, as the required switching is incorporated. This gives complete change-over from "Receive" to "Transmit" with single switch control.

The switch has four poles, section S1 switching the aerial to the tank coil L4 at T (Transmit), but transferring the aerial to the receiver at R (Receive). Section S2 short-circuits the aerial feed to the receiver during transmission, to minimise r.f. leaking through to the receiver. S3 is in series with one speaker lead, and so silences the speaker during transmission.


The transmitter power circuit is controlled by S4, which applies h.t. to all stages on transmit. S5 is a separate two-way switch, which allows h.t. to be put on V1 and V2 only. This allows the v.f.o. to be tuned to any wanted frequency, and be "netted"

QRP

TRANSMITTER

for the LF BANDS

F. G. RAYER G30GR

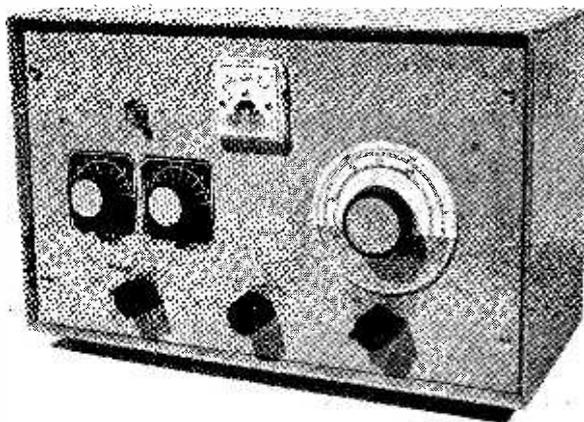

CIRCUIT

In Fig. 1, V1 (6C4) is the variable frequency oscillator, followed by V2 (6AM6) which is a buffer/doubler. V3 (6BW6) is the power amplifier, and runs at about 10 watts input, anode current being shown by the meter. This is a straightforward arrangement which gives good results with a minimum of difficulty.

VC1 tunes the v.f.o. from 1.75-2.0MHz and, for the 160m band, the 1.8-2.0MHz sector is used, transmitter output being on the same frequency as the v.f.o. For 80m, the v.f.o. is tuned over the range 1.75-1.9MHz, and V2 acts as doubler, so that the output frequency is from 3.5-3.8MHz. V6 provides a regulated supply for the v.f.o.

L2 and L3 are broadly resonant coils for 160m and 80m. When first testing the equipment, grid current in the p.a. stage can be checked by clipping a test-meter across R8. L4 is the pi-network tank coil, tapped for 80m.

The audio section has V4 (12AX7) as a high gain amplifier, followed by V5 (6BW6) which choke modulates V3. This arrangement has been found to give good modulation and quality when using a crystal microphone and it requires relatively few components.

With any set of transmitting/receiving equipment the problem arises of providing "Transmit" and "Receive" change-over facilities. A relay is often used to switch the aerial from receiver to transmitter,

with the receiver, either to answer a CQ, or to begin transmission on a selected channel.

The aerial, or matching device, if used, is plugged into the aerial co-axial socket. A co-axial lead of convenient length is made up, and plugged into the "Rx" outlet of the transmitter. This lead runs to the aerial and earth terminals of the receiver. Communications type receivers normally have a separate speaker, one lead of which is cut, and extended if necessary, so that plugs can be inserted into the "Mute" transmitter sockets.

The two switches on the transmitter then give complete control, for tuning the v.f.o. netting on a signal, and changing from reception to transmission.

CONSTRUCTION

VFO

By using a ready-made inductor and accurate capacitor values, experiments to obtain suitable band coverage are avoided. It is only necessary to adjust the core of L1, and trimmer TC1, to set the band so that VC1 tunes 1.75-2.0MHz, with a little to spare at each end of the dial.

The v.f.o. is assembled in a box 3×2×2in. which screens it completely and also helps isolate components from sources of heat. This box is readily

made from "universal chassis" strips. One strip is 7×2in., with flanges which are cut 2in. from each end, so that the strip can be bent into an open U-form 2in. high and 3in. wide, with flanges all round. An accurate bend is most easily obtained by holding the strip on a block of wood.

The second strip is 3×4in. and also has flanges. It is cut through centrally to obtain two pieces 3×2in. One of these is bolted to the front of the box as in Fig. 2 and carries VC1. After wiring is complete and the box is fixed to the chassis the second 3×2in. flanged piece is secured with self-tapping screws to close the back.

The v.f.o. is completely wired as in Fig. 2 before it is mounted. Trimmer TC1 is fixed just clear of the box top with a bracket or by bolts with spacers. A small hole is drilled in the box to permit adjustment of TC1. All connections are direct and rigid and points MC are joined with wire and also to tags bolted to the chassis.

The tag-strip in Fig. 2 is secured inside the box and supports the r.f. choke, C2, and C3. Coloured leads identify the wires which pass through the chassis—brown for h.t. (150V), blue for 6·3V, and yellow for the lead from C5.

The box is fixed to the chassis by bolts through the flanges which turn inwards (omitted in Fig. 2, for clarity) and through the front and back plates. It is placed so that the ball drive can be arranged as in Fig. 3.

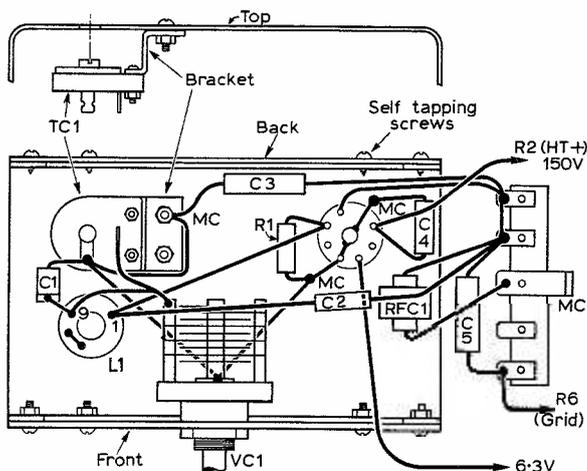


Fig. 2: Constructional details of the VFO assembly.

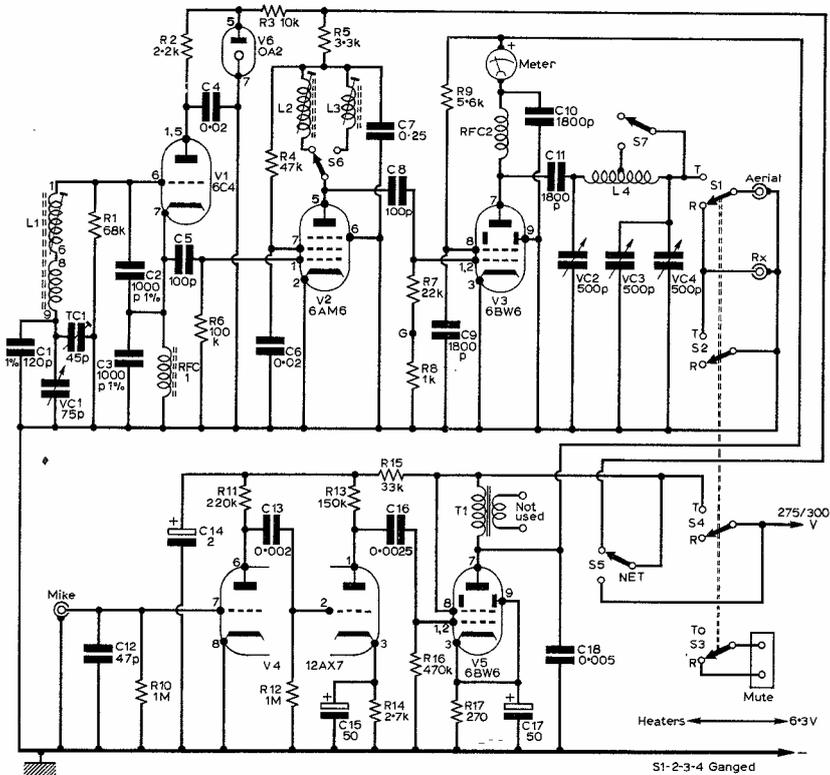


Fig. 1: Complete circuit of the QRP transmitter.

Top of Chassis

Fig. 3 shows the position of the major components. Capacitor VC2 is of a type fixed to the chassis with small feet. Capacitor VC3/4 has three holes in the front plate and is bolted to a small bracket to bring the spindle level with that of VC2. These spindles pass through 1/8in. clearance holes.

Panel and chassis are fixed together by the switches and panel brackets. The lower edge of the panel must project about 1/8in. beyond the chassis, to clear the mounting flange of the case.

Buffer Stage

Components are placed around V2 as in Fig. 4, with grid and anode circuits separated and heater leads close against the chassis. The MC connection to the central spigot of the valveholder passes across the holder, as shown.

The coupling winding provided on L2 and L3 is not required, and must be completely removed. The outer end of the larger winding of L3 is then unsoldered from its pin and 28 turns removed. The end of the wire is cleaned and re-soldered to the pin.

PA Stage

Grid circuit components are under the chassis, and are placed around V3 approximately as in Fig. 4. A hole is drilled in the chassis adjacent to the anode, pin 7, a lead passing directly through to the r.f.c. Anode circuit items are above the chassis.

C10 is anchored to a tag strip (Fig. 3) which also supports r.f.c.2, the top of the choke being held by C11. The 1800pF 1kV disc ceramic capacitors used in these positions are easily obtainable, but 2000pF

CN 15 Watts. Ideal for miniature and micro miniature soldering. 18 interchangeable spare bits available from .040" (1mm) up to 3/16" For 240, 220, 110, 50 or 24 volts.

from £1.70

Sign here..!

for your miniature soldering iron.


SK2 Soldering kit

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with 1/16" bit, 2 spare bits 3/32" and 3/32". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder"



£2.40

SK1 SOLDERING KIT

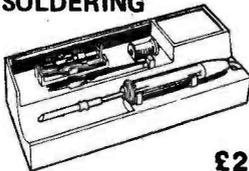

£2.75

In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted 1/16" bit. Spare bits 3/32" and 3/32". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder"

**Model CN 240/2
15 watts - 240 volts**



£1.70

Fitted with nickel plated 3/32" bit and packed in handy transparent box.



PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon. Telephone: Plymouth 67377/8. Telex: 45296. Giro No. 2681000.

Please send me the Antex colour catalogue

Please send me the following

Quantity Model Bit Size Volts Price

.....

.....

.....

.....

I enclose cheque/P.O./cash value


.....

NAME

ADDRESS

.....

..... PW8

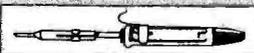

Model G - 18 watts. Fitted 3/32" bit. Spare bits 1/8", 3/16" and 1/4" available. For 240 or 220 volts. £1.83



Model F - 40 watts. Fitted 1/16" bit. Spare bits 3/32", 1/8", 3/16" and 1/4" available. For 240, 220, 110, 20 volts. From £2.38

Model E - 20 watts. Fitted 1/8" bit. Spare bits 3/32", 1/8" and 3/16" available. For 240, 220 or 110 volts. From £1.80

Model ES - 25 watts. Fitted 1/8" bit. Spare bits 3/32", 3/16" and 1/4" available. For 240, 220 or 110 volts. From £1.83

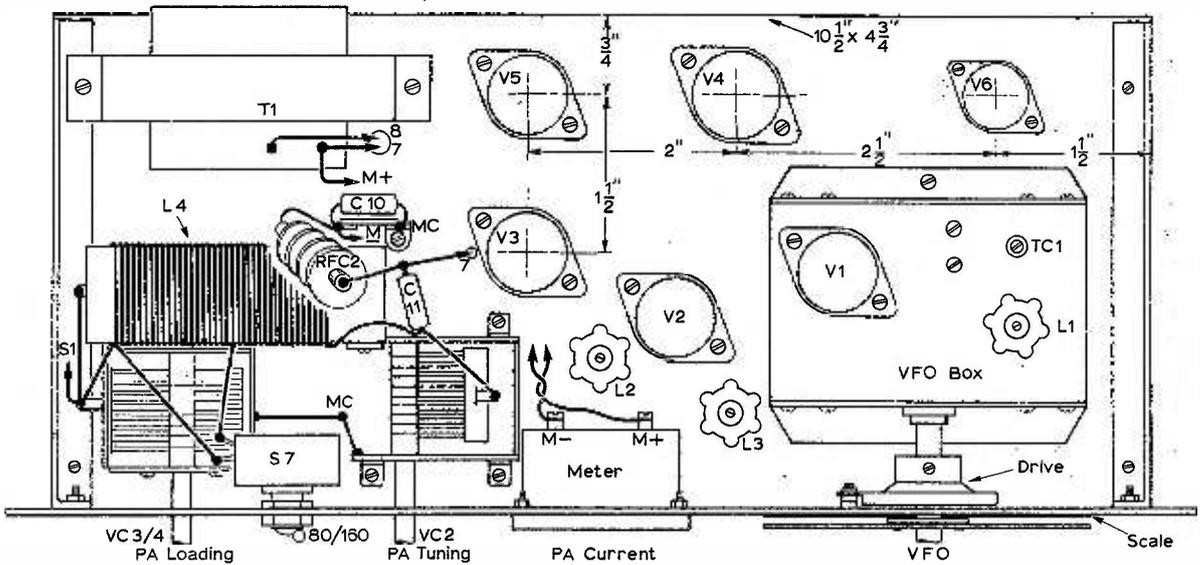


Fig. 3: Plan view of chassis showing disposition of major components.

mica capacitors of 750V rating could be used instead.

The p.a. coil has 63 turns of 22 s.w.g. enamelled wire, close-wound on a 1in. diameter paxolin tube about 2 3/4 in long. During winding, a loop is made at 33 turns for the switch S7 connection. This leaves 30 turns in circuit from VC2 to the switch.

The coil is mounted by bolting a 1in. long strip of paxolin to it and attaching this to the frame of VC2 with a second bolt. The coil is well clear of metal parts and the cabinet top.

Audio Section

Grid leads and components should be against the chassis especially connections to pin 7 of V4 otherwise there is some danger of instability or picking up of hum or r.f.

No gain control was included because it was found that speaking normally with a hand-held crystal

microphone gave just about the required audio level. Gain can be reduced by removing C15 or by substituting a 1 megohm potentiometer for R12 connecting the slider to pin 2 of V4. It should be mounted on the back runner near V4 or be connected with screened leads.

The modulation choke T1 is the primary of a mains pentode type speaker matching transformer and should be able to carry 70-80mA, and of low d.c. resistance, to avoid excessive voltage drop.

A test of the a.f. section can be made by connecting a speaker to the secondary of the transformer. The speaker must be well clear of the microphone, to avoid audio feedback. Speech should be reproduced at ample volume with good quality. Causes of distortion could be low emission valves, wrong resistor values, or slight leakage in C13 or C16 upsetting the bias of the following stage.

Fig. 4: The wiring underneath the chassis.


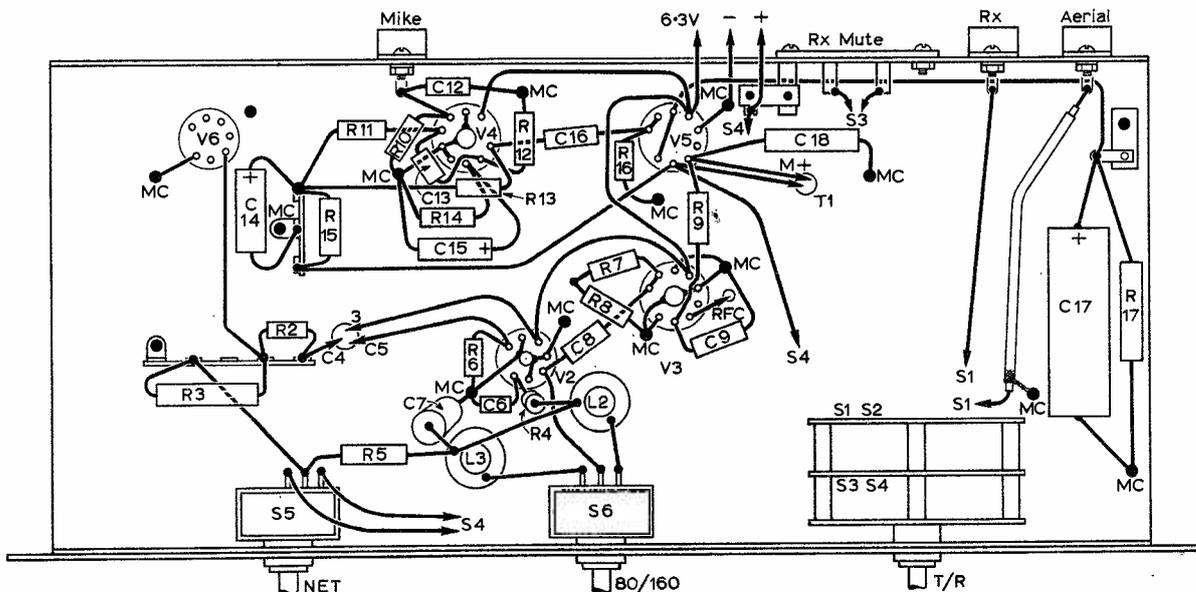


Fig. 5: An "exploded" view of the transmit-receive switch S1-4 and netting switch S5.

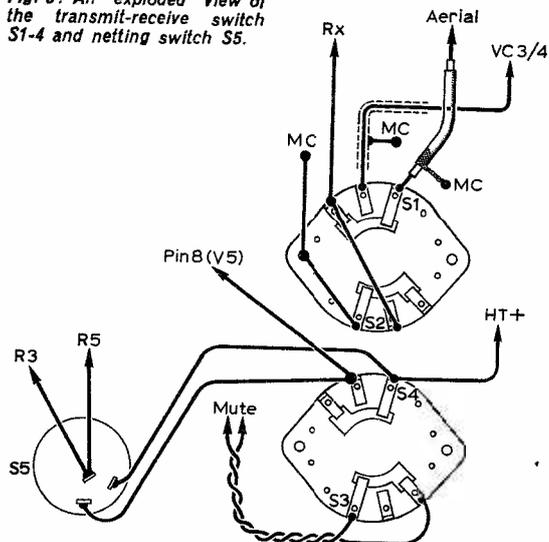

Switching


Fig. 5 shows switch connections. A co-axial lead is used for the aerial, taken to chassis at the socket, and at VC3/4. S5 is switched to the "Tune" position only when adjusting the v.f.o. frequency, and so S4 normally switches on all transmitter h.t. circuits.

VFO Dial

A pointer, cursor or disc of transparent material such as perspex can be mounted on the flange of the ball drive by two short 8BA screws. A disc with a line marked on it was used. A piece of thin card of larger diameter than needed was temporarily fixed to the panel, and calibration marks made around the edge of the disc. The card was removed, markings transferred to scales of suitable diameter, and the card cut down to size and cemented in place, finally checking that the calibration was still correct.

CW

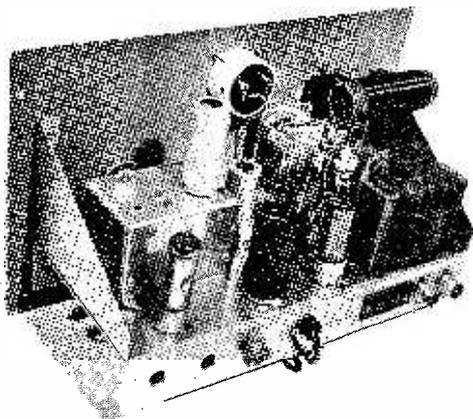V3 can be keyed by disconnecting pin 3 from the chassis, connecting a 5000pF capacitor directly from this tag to chassis and wiring a lead from pin 3 to a jack, normally closed to complete the circuit.



This places the key between cathode and chassis when the plug is in. It is also necessary to take T1 out of circuit, which can be done by fitting a two-way switch to the back runner, so that on c.w. h.t. reaches the r.f. section only. The lamp load mentioned later for a.m. tests is not suitable on c.w. Connect a 470 ohm resistor in series with a 5000pF capacitor across the key jack.

VFO CALIBRATION

Calibration is most easily done with a 100kHz crystal marker used in conjunction with a communications type receiver. First adjust the core of L1, and trimmer TC1, for suitable coverage. As TC1 is increased in value, the range of frequencies covered by VC1 will be reduced. TC1 and L1 also allow the band edges to be adjusted. It is best to arrange that almost the whole swing of VC1 is needed to tune from 1.75-2.0MHz, but to avoid the extreme positions.

★ components list

Resistors:

R1 68kΩ	R10 1MΩ
R2 2.2kΩ	R11 220kΩ
R3 10kΩ 3W	R12 1MΩ
R4 47kΩ	R13 150kΩ
R5 3.3kΩ 1W	R14 2.7kΩ
R6 100kΩ	R15 33kΩ 1W
R7 22kΩ	R16 470kΩ
R8 1kΩ	R17 270Ω 2W
R9 5.6kΩ 2W	

All ½W 10% unless indicated otherwise.

Capacitors:

C1 120pF SM 1%	C10 1800pF 1kV
C2 1000pF SM 1%	C11 1800pF 1kV
C3 1000pF SM 1%	C12 47pF SM
C4 0.02μF 350V	C13 0.002μF 350V
C5 100pF SM	C14 2μF 350V
C6 0.02μF 350V	C15 50μF 6V
C7 0.25μF 350V	C16 0.0025μF 350V
C8 100pF SM	C17 50μF 50V
C9 1800pF 1kV	C18 0.005μF 1kV

TC1 45pF trimmer, ceramic.

VC1 75pF miniature, air.

VC2 500pF variable, air.

VC3-4 500+500pF ganged variable, air.

Valves:

V1 6C4 (EC90)	V4 12AX7 (ECC83)
V2 6AM6 (EF91)	V5 6BW6
V3 6BW6	V6 OA2

Inductors:

L1 "Yellow", Range 3 (Denco)
L3 "Red", Range 2 (Denco)
L2 "Blue", Range 2 (Denco)
L4 See text
RFC1 2.5mH miniature iron-cored choke
RFC2 2.5mH 60mA sectionalised choke

Miscellaneous:

Valveholders, B7G with skirt (3) B9A with skirt (3). B7G screens (2) B9A screens (1). Co-axial sockets (3). Switches, 4 pole 2 way rotary (1) 1 pole 2 way rotary (1) on/off toggle (1). Miniature meter, 50mA f.s.d. T1, see text. Flanged ball drive. Knobs etc. Cabinet No. BX5 with chassis 10½ x 4½ x 1½ in. (Home Radio). VFO box made from flanged chassis strips CU136 and CU144 (Home Radio).

TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service

NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL


7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for Medium and Long Waves. 4 section 24' retractable chrome plated telescopic aerial for Short Waves for maximum performance. Push pull output using 600 mW transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. Eight transistors plus 3 diodes. Famous make 7in. x 4in. speaker. Air spaced ganged tuning condenser. On/Off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build.

Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building costs £6.98


Post, packing and insurance 41p.

Overseas P. & P. 90p

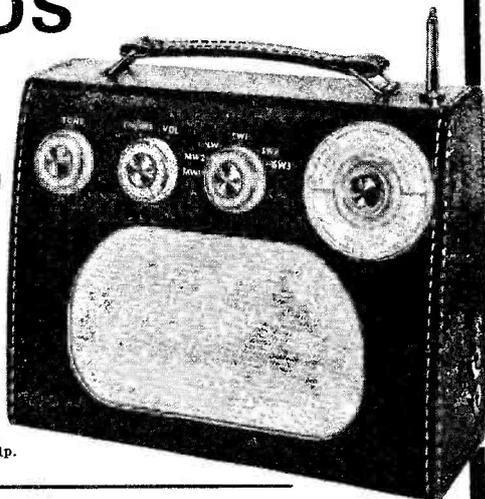

roamer seven mk IV

SEVEN FULLY TUNABLE WAVEBANDS—MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in. chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. Seven transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control.

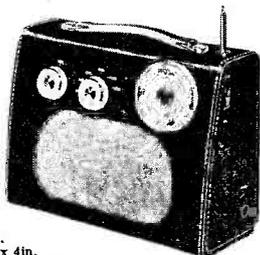

Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

Total building costs £5.98


Post, packing and insurance 41p.

Overseas P. & P. 90p

pocket five

MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

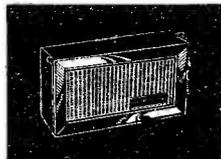Attractive black and gold case. Size 5½ x 1½ x 3½in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.



Total building costs

£2.23


Overseas P. & P. 55p

Post, packing and insurance 21p.

IMPROVED MODEL!

roamer six
SIX WAVEBAND PORTABLE
WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

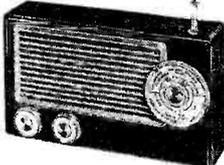

Total building costs

£3.98

Overseas P. & P. 70p

Post, packing and insurance 26p.


★ Callers side entrance Barratts Shoe Shop

★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

NEW! trans eight

SIX WAVEBAND
PORTABLE WITH
3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 x 5½ x 2½in. approx. Tunable on Medium and Long Waves, three Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. Eight improved type transistors plus 3 diodes. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

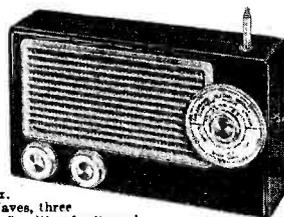

Total building costs £4.48

Post, packing and insurance 31p.

Overseas P. & P. 70p

transona five

MEDIUM WAVE, LONG WAVE
AND TRAWLER BAND
PORTABLE
WITH SPEAKER

Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (FREE with parts).

Earpiece with plug and switched socket for private listening 30p extra.



Total building costs

£2.38

Overseas P. & P. 55p

Post, packing and insurance 22p.

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>


Parts price list and plans for

Name

Address

PW.32

BETTER GET 'SET'

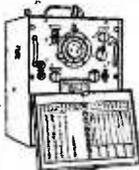

BEST OFFER YET!
FAMOUS BC.21
FREQUENCY METER
 125 KHz-20 MHz. Complete with valves, crystal and charts. **ONLY £18.50.** Carr. £1.50.
LIMITED NUMBER - ORDER NOW!

CRYSTAL CALIBRATOR

No. 10 Crystal controlled heterodyne wave-meter covering 500 KHz-10 MHz (Harmonics up to 80 MHz). Power required 300V, D.C. 15mA. 15v. 0.2A. D.C. Test equipment for 62TM/RC.



ONLY £4.25. P. & p. 50p.
FEW ONLY—No. 62 TM/RC
 1.5-10 MHz £17.50. Carr. £2.

MARCONI 801A SIGNAL GENERATOR
 1-310 MHz. In original transit case. £45. Carr. £2.50.

AERIAL MAST EQUIPMENT

30" TELESCOPIC MASTS
 £3.75. Carr. £1.
 5' 2" Extension Sections to fit bottom of above mast to increase height. £1.25 each (any number supplied).
95" MAST (7'-6" 2" interlocking sections) with base plate and 12 nylon guys with semi-auto tensioner.
 £22.50. Carr. £2.50.
70" MAST. Ditto. 16 guys, block and tackle. £45. Carr. £2.75.



R.F. ANTENNA TUNER (A.T.U.)

Cylinder design 10" x 4". Precision calibrated scale. Suitable for tuning most aerials for increased signal strength. A must for serious operators for BC or TM. Full instructions. **ONLY £1.75.** P. & p. 25p.



R.F. ANTENNA TUNER (A.T.U.) OPEN TYPE

Mounted on ceramic former and feet. "Roller Coaster" design 16 G silver or silver plated wheel traversing on wire on ceramic former. Will handle considerable R.F. In original packing. As used with No. 53 Transmitter. **ONLY £2.50.** P. & p. 50p.



VHF COMMUNICATION RECEIVER 1392

Frequency range 95-150 MHz. Normally crystal controlled. (Mode supplied for tuneable operation.) Power requirements 240v AC 80mA 6.5v-4A. **ONLY £8.50.** Carr. £1. Complete station with PSU and Control Unit **£12.50.** Carr. £2.50.



No. 19 TM/RC

Rebuilt. Complete station with PSU, Cables, Mic, Aerial etc. £22.50. Carr. £2.

No. 19 SET 500uA METERS

Scaled 0-800 and 0-15V. Brand new, boxed £1.25 Post Paid. (Quantity prices on request.)



ALL No. 19 SPARES IN STOCK
 Complete instruction book with circuits for No. 19 Equipment. 37p Post Paid.

R.F. AMPLIFIER. To increase output of No. 19 Set. **ONLY £3.75.** Carr. £1.25. Instruction Book for R.F. Amp. 37p Post Paid.



HEAVY DUTY BATTERIES

New in metal cases with carrying handles.

6v. 40 AH 10 1/2" x 9 1/2" x 5" £2.25. Carr. £1.25
 6v. 85 AH 18" x 9 1/2" x 7" £2.25. Carr. £1.25
 6v. 100/125AH 18" x 11" x 7" £2.25. Carr. £1.25
 6v. 170 AH 16 1/2" x 13" x 7" £4.25. Carr. £1.50
 (Special price for quantities.)

FAMOUS TELE 'F' FIELD TELEPHONES

Suitable for Farms, Building Sites etc. Communication up to 5 miles or more. Rugged construction, will last a lifetime. **ONLY £2.75 PAIR.** Carr. £1. (Twin telephone wire for above available—ask for price.) Many other Ex-Govt. Surplus Equipment items in stock. Receivers etc. in small quantities too numerous to mention. Enquiries invited. **LIST 25p Post Paid.** (Refundable against purchases over £3.)



Surplus Electronic Trading

DRIVERS END LANE, CODICOTE, HITCHIN, HERTS, SG4 5TF

NEW 2in. SPEAKERS 15 ohms 75p, p. & p. 10p.

BARGAIN PARCELS 14lb at £1.45 plus 32p p.p.; 28lb at £2.75 plus 62p p.p.; 56lb at £4.50 plus £1.25 p.p. Contain pots, Res, Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save 22s. Lucky Dip Service.

NEW 6 in. VHF AERIALS. Freq. 75-78 Mc/s, 70 ohms. £2.50p, p. & p. 50p.

VHF Receiver, Type 715, less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested; complete with valves and speaker. £3 plus £1 p.p.

VHF AERIAL TUNING UNITS consisting of the following: 1-1 1/2" 500 micro/ampmeter. 1 small 2-gang 75 PF capacitor. 1 various large wattage resistors for dummy load. Fair gears B.N.C. type sockets. Will tune 10 metres with 25/30 watts R.F. input. Size only 5 1/2" x 4 1/2" x 5" Sealed. Price £1.87 1/2 p.p. 25p

CRYSTALS AS NEW: Ho 6u, 5,345; 5,030; 5,005; 4,945; 4,875; 4,840; 4,795; 4,580; 4,560; 4,520; 4,510; 3,500; 2,295 Kc/s and 10 x J465 Kc/s. 50p each plus 5p. p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS. 10% tolerance 1/2 & 1 watt. Preferred values in packets of 10. Our price 50p per 100, 50p per 200, £1.25 per 300, 50p at £2.12 1/2. Our selection. p.p. 5p per 100 and 2p per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details: Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice. Trimmers without Xtal—50p per doz. plus 17p p.p. Trimmers with Xtal—75p per doz. plus 17p p.p. Also 20 PF min. brand new air spaced. 80p per doz. plus 17p p.p.

ANY HEIGHT AERIAL TUBULAR SECTIONS 1" dia x 3 ft. long. Brass screw in type, copper coated and painted. New 30p each, p.p. 5p. each. Minimum order 6.

BRAND NEW HARTLEY OSCILLOSCOPES CT316 in original packing. Band width up to 5 Mc/s. Mains supply. Price £40, p. & p. £1.00p.

AERIALS NEW CONDITION. Whip type 4ft 25p, 14ft. 77p. Used condition 4ft. 30p, 14ft. 62p. All collapsible type p. and p. 4ft. 10p, rest at 17p. Bases for above 35p, p.p. 12p. New matching unit coax connection for above 30p, p.p. 5p.

Huge release of valves for the 62 set TX/RX, in original rubber packing consisting of QV04/7 x 61M, ARF12 etc, 10 valves in all at the bargain price as seen 87p plus 17p p.p.

New Headphone and Mike rubber muff type. Low impedance. 37p, p. & p. 17p.

NEW AERIAL WIRE ON BOARDS 7/2S UNCOVERED. 75ft. 40p, 30ft. 47p, 100ft 55p, 150ft, 75p, 180ft, 95p. 250ft. £1.30p, p. & p 12p.

Headphones, ex Gov. DLR No. 5 high impedance. New 87p 17p p.p. Used condition 62p 17p p.p.

MURKHEAD DECADE A.F. SIGNAL GENERATOR.

This precision instrument can be used:
 1. To Measure Gain up to 60 dba.
 2. To Measure Loss up to 45 dba.
 3. To compare Power levels (A.F.).
 4. As an Audio Frequency Generator covering 100 Hz to 41 KHz. With a dial setting accuracy of ±0.5 Hz. Output —1 M/W into 600 ΩL. Complete with mains power unit. Tested. Good Condition. £15, p. & p. 75p.

Heavy New Coax Cable 750HM will handle at least 1KW 50ft lengths, Plug on end, £1.70p + 30p.p.

Also 1" 75 ohm Coax in 50ft coils with BNC plugs good condition. price £1 + 30p. p.p.

2 BNC plugs on short length coax cable large size low loss plugs 30p + 5p. p.p.

Block Type capacitor TOC 8UF + 15% 250 VDC WEG 60°C. 250 VDC WEG 70°C Type 62 C1M Price 40p + 13p p.p. New.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

A. H. THACKER,

Radio Dept., HIGH STREET, CHESLYN HAY, Nr. Walsall, Staffs.

RADIO CONSTRUCTOR

JULY issue
 features
I.C. STEREO AMPLIFIER



EASY TO BUILD, pierced and prepared printed circuit, 2.7 watts per channel. Fully continuous Bass and treble controls.

★
MANY OTHER PROJECTS
 ★
ON SALE NOW 20p

Copies may also be obtained direct from the Publishers 24p including postage.

Published by:
 Data Publications Ltd.
 57 Maida Vale, London, W.9

RADIO CONSTRUCTOR

SIMPLE SHORTWAVE RECEIVERS



by **F. A. Baldwin**
FOUR BASIC DESIGNS
 1, 2 and 3 VALVES

If you are interested in the hobby of receiver construction and short wave listening this is the book for you. It covers the whole field of s.w.l'ing from construction to operating.

140 pages

PRICE 80p

Copies may also be obtained direct from the Publishers 80p including postage.

Published by:
 Data Publications Ltd.
 57 Maida Vale, London, W.9

With S5 at the "Tune" position and a lead from the receiver lying near the transmitter, tune the receiver to 3.5MHz using the crystal marker, tune VC1 to zero beat, and mark the scale for 3.5MHz repeating for 3.6, 3.7 and 3.8MHz. Also mark 3.6 as 1.8, 3.7 as 1.85, and 3.8 as 1.9MHz. Continue with the 3.9 and 4.0MHz marker pips, but marking the v.f.o. for 1.95 and 2.0MHz only. If the extreme settings of VC1 have been avoided the 10kHz points can be filled in linearly between the 100kHz points.

A 10mA or multi-range meter is connected from "G" Fig. 1 to chassis, the latter being positive. The v.f.o. is set to 1.9MHz, S6 to 160m, and the core of L2 is adjusted for maximum grid current, which should be around 3mA. Then adjust the v.f.o. to about 3.7 MHz, switch to 80m adjusting L3 core for maximum grid current which will be around 2mA.

TESTING

It is simplest and best to test the whole equipment by feeding the transmitter output into an artificial aerial load. This can be a 15 watt or 25 watt 240V or similar household lamp. Clip it across VC3/4 and chassis, or fit a holder, lead and co-axial plug so that it may always be employed for tests.

P.A. tuning procedure is that generally employed with a pi-network. Check that S7 is closed for 80m, or open for 160m, to match the position of S6. Fully close VC3/4 and also VC2 (to prevent the possibility of doubling in the p.a.). Switch to "Transmit" and open VC2 to obtain a dip in anode current, as shown by the panel meter. Current will be low but loading is increased by opening VC3/4, meanwhile adjusting VC2 for minimum current. As this is done, the minimum current rises, and the 15 watt lamp should light with fair brilliance when the input reaches about 10W.

The d.c. input to V3 anode is anode volts \times anode current, thus 33mA at 300V will be 9.9 watts. A supply voltage of less than 275V is not recommended.

If the transmitter is loaded into the lamp, and a receiver is tuned to the signal, speech should sound clear and well modulated. The receiver should have its aerial disconnected and r.f. gain turned well back, or overloading may cause distortion.

POWER SUPPLY

Fig. 6 is the circuit of a suitable power supply. The mains transformer actually used was a Parmeko P.2931, 250/0/250V 150mA, with SE-05 rectifiers D1 and D2, and Parmeko P.3141 120mA choke. This provided 280V with a load of 120mA. BY100 rectifiers would also be suitable. The voltage obtained when using semi-conductor rectifiers is somewhat higher than with a valve rectifier. Many transformers have winding for valve rectifiers so a 5U4G is a suitable rectifier for a 5V 3A winding, or an EZ81 for a 6.3V 1A winding.

AERIALS

The simplest possible aerial is an end-fed wire. Some lengths will offer such a load impedance that the transmitter can be worked directly into the aerial, on one or both bands. Other lengths present load impedances which are outside those which can be matched by the transmitter, and then proper tuning or loading will be impossible. One of the

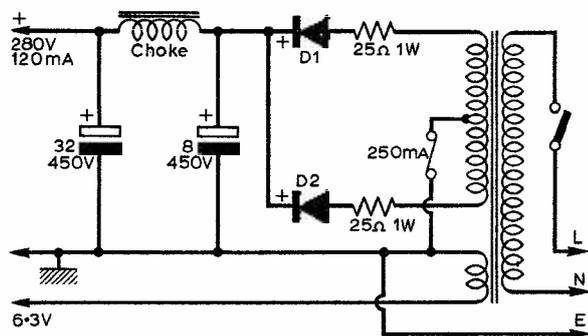


Fig. 6: Suggested power supply for the QRP transmitter.

matching circuits in Fig. 7 can then be used.

Fig. 7(a) is the simplest. L1 may be similar to the tank coil, or be a surplus tapped inductor, or may consist of a number of turns, found by trial and error, on a former lin. to 3in. in diameter.

Fig. 7(b) is similar but has a capacitor VC1 added, of about 250pF, which allows more accurate adjustment and has fewer tapings on L2.

Fig. 7(c) is series tuning often used for quarter-wave aerials on l.f. bands. VC2 can be 500pF and again L3 resembles the tank coil. The tapping makes L3 into an auto-transformer and may be set about 10 turns from earth for 160m, or 4 or 5 turns from earth for 80m. For the latter band only L3 may have fewer turns.

Fig. 7(d) is parallel tuning suitable for a half-wave aerial on 80m. L4 is about 30 turns on a lin. diameter former, with a 250pF capacitor for VC3 and L5 is about 4 turns of insulated wire over the earthed end of L4.


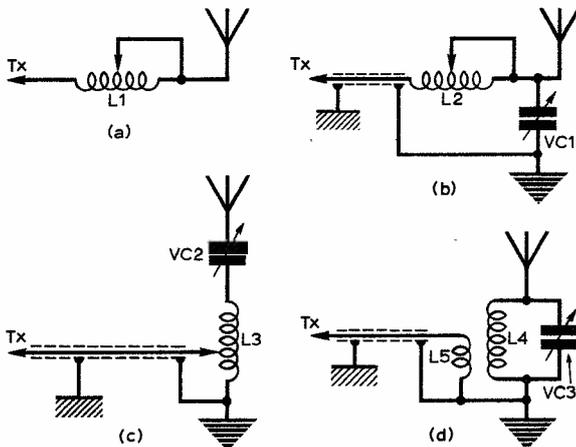


Fig. 7: Four circuits enabling almost any aerial to be matched to the transmitter.

A typical aerial of 126ft in length would be about a quarter-wave on 160m, and a half-wave on 80m, so Fig. 7(c) would be required for 160m, and Fig. 7(d) for 80m working. However, it is generally easier to make up a tuner with one of the circuits in Fig. 7 or a similar circuit and to experiment with tapings until the transmitter can be satisfactorily loaded by the aerial. Even very short wires (under 10ft.) may be used with these circuits but range is much reduced.

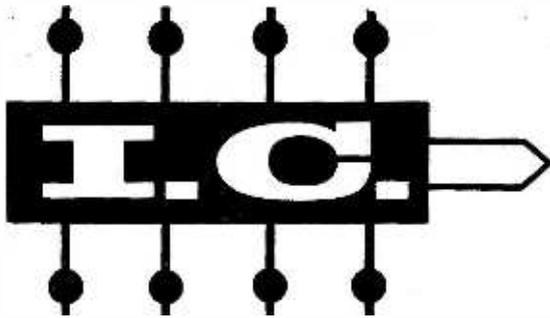

OF THE MONTH

L.A.J. IRELAND

Number 22

G.E. PA264-265 Voltage Regulators

MANY constructors will have come across the difficulty of having to operate 6 volt portable transistorised equipment from a 12 volt car battery. In such equipment current drain will usually be dependent upon the audio output so as to conserve the life of the battery and as a result the conventional voltage dropper resistor will not suffice. An alternative approach is to use some form of voltage regulator and lately the G.E. Company have released a monolithic i.c. capable of fulfilling just this function. With a 5 watt power dissipation capability, the i.c. eliminates the need of both a high power pass transistor and its associated drive components and with a half dozen or so discrete components needed to complete the unit, it makes an ideal compact in-line device.

However there are practical limitations to these methods in that the voltages set at pins 14 and 13 should be kept within the limits 1.5-3.5 volts for optimum performance. Values of components specified in Fig. 1 are for a 6 volt output but it should be remembered that any output above 3 volts may be obtained with suitable choice of components. The maximum voltage rating of the PA264 is 25V and of the PA265 37V and this in fact is the only difference in their electrical characteristics.

Packaging

The units are housed in a rather unusual epoxy package with eight staggered leads in addition to

Background

Readers familiar with the present series of articles will remember the precision voltage regulator type LM100 reviewed in the June 1970 issue of P.W. This was a rather sophisticated low-power i.c. in which a built-in reference voltage was compared to a fraction of the output voltage to achieve accurate stabilisation. One of its big draw-backs however was the need for an external power transistor if an output current in excess of 12mA were to be drawn and towards the end of the article attention was drawn to the G.E. unit, type PA264, which would overcome these difficulties but which at the time was only in the development stage of production.

Operation

Basically the PA264 functions as follows. By referring to Fig. 1 it can be seen that Tr1 and Tr2 form a differential comparator whose inputs are controlled by an external zener and a sample of the output voltage. Tr2 in turn directly controls the Darlington pair Tr4 and Tr5. Any tendency in the output voltage to decrease will be counteracted by a drop in voltage at the base of Tr2 which in turn will tend to increase the current through Tr4 and Tr5. The reverse situation occurs if the output voltage tends to increase and so the unit is self-compensating.

The output voltage may be varied in two ways, by potting down the reference voltage applied at pin 14 or by varying the feedback voltage at pin 13.

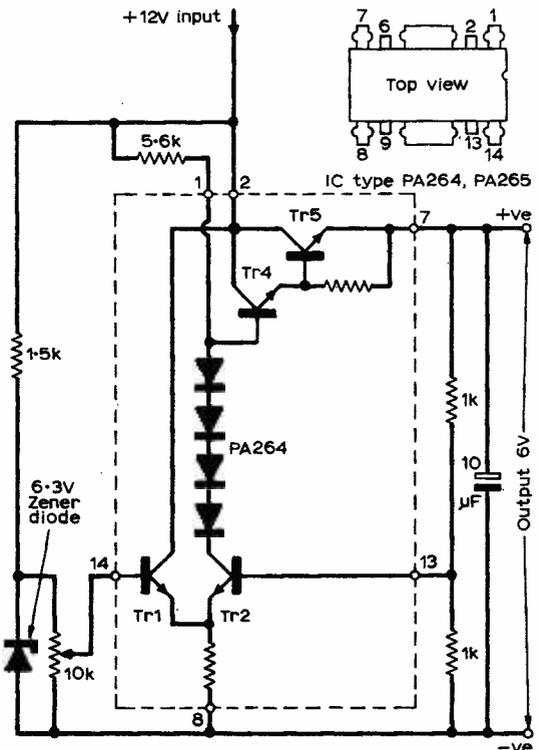


Fig. 1. Circuit of the PA264 with additional components required to provide 6v from 12v supply.

continued on page 322

VHF INTERFERENCE PROBLEMS

VIVIAN CAPEL

THE opening of local radio stations on the v.h.f. band and the continual plugging by the BBC of the better quality obtainable with frequency-modulation is increasing the public interest in this area of broadcast reception.

Unfortunately, the claims that reception is interference-free is far from true, and as a result users and engineers may face some tricky problems. While interference from foreign stations, the bane of medium-wave listening, is absent, there are other forms to take its place.

For those living on or near main roads, car ignition interference is probably the most troublesome. This is especially so if the road is on a hill, when not only is the interference generated by a car in low gear much worse, but it also takes longer to pass.


All new vehicles are now suppressed, and have been for the last few years, indeed it has been noticeable that ignition interference has been thinning out, as the older vehicles become fewer in comparison with the new ones. However, there are still sufficient passing on any main road in a given time to cause a number of serious interruptions to any particular programme.

While the irate listener may feel like taking drastic action against the offenders, the solution in this case cannot be applied to the source, and in any case would be illegal! Usually, part of the trouble lies with the aerial. The majority of chimney stacks are already so festooned with Band I and III television aerials plus probably u.h.f. as well, that there just isn't room for a Band II radio aerial. Often, in areas not too remote from the transmitter, quite good signal strength can be obtained with the internal aerial wire running around the back of the cabinet, or at least with one along the picture rail. So the idea of having anything more elaborate seems pointless and money-wasting.

However, although the signal may be strong enough to give reasonable fade-free reception, it is when a splash of interference comes along that the inadequacy becomes all too apparent. The signal-to-noise ratio is just not good enough.

If the chimney looks as though it just will not stand any more, the answer may be in the loft. A good loft aerial is much less expensive than an outdoor one as it does not have to be weather-proof, or need chimney lashings. It will give a much stronger signal, and being elevated well above the road will be out of the worse area of ignition interference.

The directional properties of the aerial will also help as any radiation from directions other than the transmitter will be reduced. If the transmitter direction is away from the road, mount the aerial on that side of the loft as this will put the bulk of the house between the aerial and the road, and so afford a degree of shielding. This really should reduce ignition interference to the level of background noise, if not entirely eliminate it.

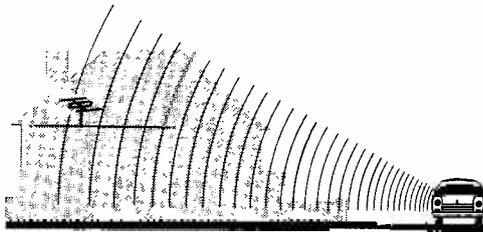

Loft aerial positioned on side of house furthest from the main road. House affords measure of screening from ignition interference.

The other form of interference can be more troublesome to deal with. There seems in most of our major cities a proliferation of private radio-telephone installations as used by police, ambulance, taxis and other services. These operate on a number of frequency bands, three of them in the v.h.f. range, 70-85MHz., 103-140MHz. and 168-175MHz. There is also one in the u.h.f. region. The broadcast v.h.f. frequencies of Radio 1, 2, 3, and the local stations lie within the range 88-96MHz. or right in between the two lowest radio-telephone bands, and so are vulnerable to interference from them.

Spurious Signals

To see how this interference can occur, we will review the ways by which spurious signals can be received with a superheterodyne receiver. First, there is breakthrough of signals at the *i.f.* frequency, which in the case of most f.m. receivers is 10.7MHz. The local oscillator has no effect on these, so they would be heard irrespective of the setting of the tuning dial, and in fact, this factor serves to identify them. There are no authorised transmissions at this

frequency, so this class of interference should not be encountered unless it was due to a short-wave transmitter operating illegally.

Another form of interference is the well-known *image* or *second-channel* type. There are two frequencies that will produce a response in a super-heterodyne receiver, one is the sum of the local oscillator frequency and the i.f., and the other is the difference between them. If, as is common practice, the oscillator is running higher than the programme signal, it is operating on the difference, and another signal which is the sum will produce interference.

We can use an example to illustrate: If the wanted signal is at 90MHz, the oscillator is running at $90+10\cdot7=100\cdot7$ MHz. An unwanted signal will produce the i.f. frequency at the output of the mixer if it is higher than the oscillator by the frequency of the i.f., or $100\cdot7+10\cdot7=111\cdot4$ MHz. As can be seen, this is within the middle band used by radio-telephone services. Second-channel interference then, arises from signals twice the frequency of the i.f. away from the wanted signal; higher if the oscillator is running high, and lower if it is low. For normal v.h.f. sets the interfering signal would be 21·4MHz higher than the broadcast frequency.

Similar, is the *i.f. harmonic interference*. This is the sum of the local oscillator and half the i.f., and also their difference. Such a signal will produce an output at the mixer anode of half the i.f. frequency, and it is the second harmonic of this which will be passed by the i.f. circuits.

Using our above example, the local oscillator frequency is again 100·7MHz, and the interfering frequencies will be $100\cdot7+5\cdot35=106\cdot05$ MHz and $100\cdot7-5\cdot35=95\cdot35$ MHz. In relation to our wanted signal of 90MHz, the frequencies are plus half and $1\frac{1}{2}$ times the i.f. Harmonics are not usually as strong as the fundamental, so interference from this cause is not so likely to give trouble unless the unwanted signal is very strong.

A further type is the *beat interference*. This occurs from a signal that is spaced from the wanted signal, either above or below, by the i.f. frequency, and is caused by the two signals beating together to form a resultant at the i.f. frequency. Actually, the interfering signal performs the same function as the local oscillator, only of course it carries its own modulation which is passed on through the i.f. stages and detector along with that of the wanted signal. If the interfering signal is strong enough, the set would continue to work with the local oscillator stopped, and this fact could be used to help identify this form of interference. Thus for a wanted signal of 90MHz, beat interference would be caused by signals at 79·3MHz and 100·7MHz.

Finally there is the interference caused by *oscillator harmonics*. All oscillators produce harmonics, and the second-harmonic of 100·7 which you remember is our local oscillator frequency for receiving a signal at 90MHz, is 201·4. Signals spaced above and below this by the i.f., i.e. $201\cdot4-10\cdot7=190\cdot7$, and $201\cdot4+10\cdot7=212\cdot1$ MHz, would therefore be passed into the i.f. circuits.

These frequencies are in the commercial television band and above the highest radio-telephone range. The third-harmonic of the oscillator would bring it even higher. Frequencies so remote from the wanted ones should be greatly attenuated by the tuning in the r.f. circuits and the tuned aerial, so should not present any problems. If though it is found that

commercial t.v. signals are breaking through, this is the probable cause.

Summing up then, interfering signals can be spaced from the wanted one by twice (second channel); $1\frac{1}{2}$ times (i.f. harmonic); once (beat interference); and half (i.f. harmonic) times the i.f. frequency, on the high side; and one (beat interference) times on the low side. So there are at least five possible frequencies that will interfere with each and every broadcast station. As there are four BBC programmes in most areas, this gives us some 20 possible interfering frequencies. The situation is aggravated by the fact that f.m. receivers are not sharply tuned as are a.m. sets. It is of course necessary to maintain a wide pass-band because of the nature of the f.m. signal. Broadcast deviations are up to 75kHz either side of the carrier frequency, so receiver circuits must extend well beyond these limits.

This means that interfering frequencies do not have to be spot on the values calculated, and if only near them, interference can result. With the previously noted increase in radio-telephone users, it can be seen that the possibility of interference with broadcast programmes is high, and is steadily increasing.

Radio-telephones

The question is, what can be done? Mobile units are not so much a nuisance, as they operate at low power, and usually cause interference only when they are fairly close to the receiver. The chance of a mobile operating at a frequency which could cause interference, coming sufficiently close to a working f.m. receiver tuned to a vulnerable frequency, is not very great, and the odd occasion when it may occur could hardly constitute a major nuisance.

It is the base stations that are the real menace. These are operating more or less continually, and are relatively high powered. Should one of these be within a few miles and operating on a critical frequency, then constant jamming will result.

The first step is to try to identify the offender. This is not too difficult as a number of his messages are being unwillingly intercepted. The class of business can be quickly deduced, and a local knowledge of the businesses of that type large enough to operate radio telephones, will help to narrow things down. One clue is whether the interference is present in the evenings or at week-ends. If it is, then a business that offers service outside normal hours will be the obvious culprit.

After eventually identifying the source, one can try swinging the aerial away from the direction of the transmitter while not losing too much of the broadcast signal. A local road map will help to obtain the precise directions involved. Do not swing too far away from the BBC station though, as the received signal may then be reflected and suffer phase-distortion, which is similar to ghosting on a television picture.

The next step is to find out the exact frequency of the transmitter. Once the owner has been identified, this should present no problem; if the reason for requiring the information is explained, he will no doubt be willing to co-operate. He may not know the frequency, perhaps being non-technical, but this should be shown on the transmitting licence or other paperwork connected with the system. The relation-

ship between the frequency and that of the broadcast signal with which it is interfering can then be seen and the type of interference identified.

If it has not proved possible to discover the source of the interfering transmission, it may be possible to deduce the type of interference from the clues given above, and so arrive at the possible frequency. For example, stopping the local oscillator (without shorting-out the input signal) will determine whether the interference is due to a beat-signal. If this is found to be the case, the frequency will be spaced either above or below the wanted signal by an amount equal to the i.f. So if receiving a station on 90MHz, the interference will be either 79.3 or 100.7MHz. As the latter does not fall within the band used for radio telephones, then it is fairly certain that 79.3MHz or thereabouts is the offending frequency.

Co-axial Stubs

Having discovered the interfering frequency, the next thing is to suppress it (electrically of course). One method of doing this which is often recommended is the parallel stub of co-axial cable. Co-ax exhibits the properties of inductance and capacitance and so will form a resonant tuned circuit. With a velocity factor of unity, the length of the stub should be a quarter of the wavelength of the signal it is desired to eliminate. It should then be connected in parallel with the aerial-feeder near to the aerial socket on the receiver, the free end being left open-circuited.

In theory then, it is a straightforward matter to calculate the length and connect up. Not so in practice. First of all, the velocity factor of the co-ax is not unity, but varies from one sample to another. Typical values are 0.67 for the solid dielectric type, and 0.85 for the semi-air spaced variety. This must be multiplied by the quarter-wavelength to arrive at the actual length, so an exact calculation with any sample of co-ax is not easy.

There is a further complication; much depends on the characteristics of the aerial input circuit, whether it is inductive or capacitive. At a frequency higher than resonance, a tuned circuit appears capacitive, whereas at a lower frequency it is inductive, the two balance out only at the resonant frequency. The receiver aerial circuits will be tuned to the wanted frequency, so at an interfering frequency, the circuit will appear either inductive or capacitive depending on whether the frequency is higher or lower than the wanted one, and the degree of inductance or capacitance will depend on the spacing of the frequencies and the Q of the circuit.

It can be seen then, that cutting a stub to the exact size is very much a matter of chance. The recommended method of tuning the stub is to cut it longer than the estimated length and cut off sections about $\frac{1}{2}$ inch at a time until the minimum level of interfering signal is attained. To do this as with most tuning procedures, it is necessary to go through the resonant point to ensure that the peak (or trough in this case) has been reached, and then tune back. Obviously it is not possible to stick back on the last few sections that have been chopped off, so the thing to do is carefully note how much has been removed since the signals started to increase, and then measure up a new stub made from the same type of co-ax.

Severe interference was being experienced on the author's own set-up which consisted of a separate f.m. tuner feeding the hi-fi system. The trouble was with the reception of Radio 3 from the Wenvoe transmitter which uses the frequency of 96.8MHz. Programmes were completely blotted out when the interference occurred, not only during the day but up to late at night and also at weekends. It was impossible to enjoy a concert, and tests with other f.m. receivers in the neighbourhood confirmed that they too likewise suffered. Their owners either put up with it, switched to a.m., or just didn't listen to Radio 3.

It was obvious from the messages received that the source was a television repair shop controlling its service vans. The fact that a number of vans were apparently in communication indicated a business of some size, and also the evening and weekend operation narrowed down the field among the local firms. A few phone calls to the short-list of suspects revealed that it was the local Rediffusion workshop. The chief engineer was co-operative and apologetic, offering to check the frequency of the transmitter and that it was duly suppressing its harmonics, but of course the frequency was assigned by the Post Office Telecommunications Department, and there was nothing he could do about that.

He was able to state the frequency which was 85.725MHz. It then became obvious that this was a case of beat interference, as the frequency is 10.7MHz away from 96.425MHz, which is just 0.375MHz off the Radio 3 centre frequency. It was an obvious boob by the Post Office in assigning so critical a frequency to a powerful base station. Admittedly, frequencies are scarce and the demand is great, but troublesome frequencies such as these could easily be assigned to mobiles.

An interference form was obtained from the Post Office, and all the details as to source of interference, frequency and type were included and duly sent off. However, nothing more was ever heard, and as the interference continued it appears that nothing was done by way of re-allocating the frequency.


Series Wavetrap

It was therefore decided to tackle the problem without G.P.O. assistance. First of all, stubs were tried, but the difficulties previously described foiled success with these. Unfortunately, the Rediffusion base was in exactly the same direction from the aerial as the Wenvoe transmitter, so no rejection could be obtained by swinging the aerial. Nonetheless it was tried, and although the f.m. signal dropped, the interference decreased more so, so some improvement in signal interference ratio was obtained.

Finally the possibility of a series resonant wavetrap in the aerial feeder was considered. A coil resonating with its self-capacity and tuned with a brass slug was needed to enable a quick and convenient adjustment frequency adjustment to be made. The problem was, how to make one with any degree of accuracy that would not need lengthy experiments with the intermittent signal source similar to a stub.

Looking around the workshop for some ready-made component which might fill the bill, attention turned to some old coil biscuits from scrapped television tuners. A channel 2 oscillator biscuit was

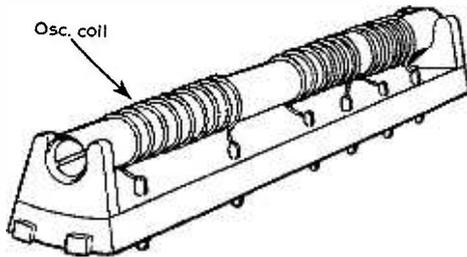found among them. The BBC station on channel 2 operates at 48·25MHz (sound). The sound i.f. for the set concerned, and which is now common for most modern t.v. receivers, is 38·15MHz. This means that the frequency of the oscillator coil was 86·4MHz. As the Rediffusion frequency was 85·725MHz., this was near enough to be within the tuning range of the coil.



Appearance of typical coil biscuit. Oscillator coil is usually the largest and contains a tuning slug.

Accordingly it was connected in series with the aerial feeder, and the interference was completely eliminated, without the need even to tune the coil.

Most t.v. workshops have old tuners knocking around, so a call at the local radio dealers could well produce a coil suitable for the purpose, should similar interference be experienced. The chart shows the frequencies of the main BBC band I television channels, and assuming a 38·15MHz sound i.f., the actual tuning range of an oscillator-coil biscuit. It will be noted that channels 3 and 4 coils will tune to frequencies within the v.h.f. radio band, so will be no use as wavetraps for radiotelephone frequencies as these are all outside this band. Channel 5 is just at the start of the medium radiotelephone band, and could easily tune to some of its lower frequencies.

TELEVISION CHANNEL	SOUND FREQUENCY	OSCILLATOR COIL FREQUENCY
1	41·5MHz	79·65MHz
2	48·25MHz	86·40MHz
3	53·25MHz	91·40MHz
4	58·25MHz	96·4MHz
5	63·25MHz	101·4MHz

Remember, too, that the range of the coil can be extended by the fitting of a different type of tuning slug. A brass slug will decrease the inductance, hence increase the frequency, while an iron slug will increase inductance and decrease the frequency. If the range is still outside the interfering frequency, a couple of turns taken off the coil will push it higher, or a small capacitor of a few pF. will bring it lower, if wired in parallel. The biscuit may have two or three coils on the same former, the oscillator is the one nearest the open end and which has the tuning slug. The other coils are coupling coils and should be ignored. ■

Direct Conversion Receiver continued from page 300


for h.t. positive, black for chassis and some other colour for the 6·3V heater supply.

ALIGNMENT

Set TC2 and TC3 about half closed and tune in any signal, with VC3 nearly open, and adjust TC2 and VC1/2 for best volume. Find a signal with VC3 nearly fully closed and peak VC1/2 for best results, then rotate the core of L1 for maximum volume.

If necessary, the core of L3 is rotated to obtain suitable band coverage with VC3. The coverage of VC3 can be checked by placing the aerial lead of a calibrated receiver near L3 and listening for the carrier produced by V3.

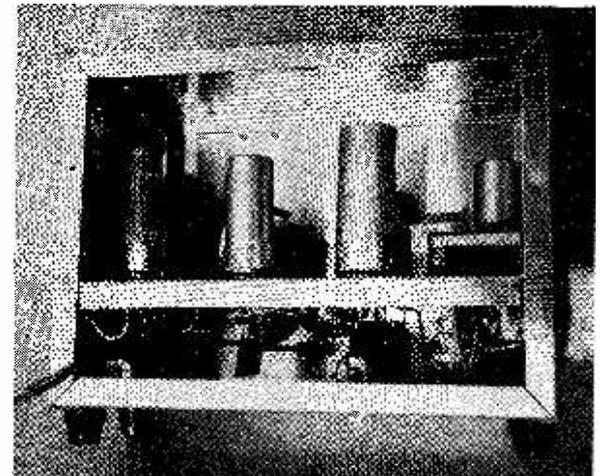At all times the r.f. gain control VC1/2 is adjusted as needed for best reception even though VR1 may have to be turned back with strong signals. The cores of L1 and L2 are adjusted around 3·5MHz and the trimmers TC2 and TC3 are set near 3·8MHz. TC2 may also need re-adjustment after changing the aerial. These circuits are merely peaked up for



Rear view of the finished receiver.


best volume and are not too critical. The extent of rotation of this control needed to tune from 3·8-3·5MHz can be increased by screwing down TC2 and TC3 and unscrewing the cores of L1 and L2 to compensate.

Power Supply. Any supply giving about the outputs mentioned should be satisfactory. If a power pack has to be made, one with full-wave rectification is most suitable. This may employ a 250/0/250V 60mA, 6·3V (1·5A or 2A) transformer, with smoothing by means of two 16µF 350V capacitors and a 60mA choke.

Speaker and Phones. A reasonably large 2/3 ohm speaker is most suitable with a cabinet or baffle.

When phones are plugged in, the mis-match can generally be disregarded. Inexpensive surplus 600 ohm phones will be found to work well. It would be possible to use an external matching transformer for high impedance phones or to feed them through reliable isolating capacitors from V4 anode.


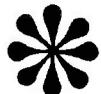
Aerials. Numerous transmissions were received with a short indoor aerial but changing to an outdoor wire tuned as for transmission purposes naturally gave a great increase in range and volume. In practice, any end-connected wire can be taken to A1 or A2 while the A2 connection is most suitable for short aerials. ■



IN NEXT MONTH'S

**PRACTICAL
WIRELESS**

DIGITAL FREQUENCY COUNTER/TIMER

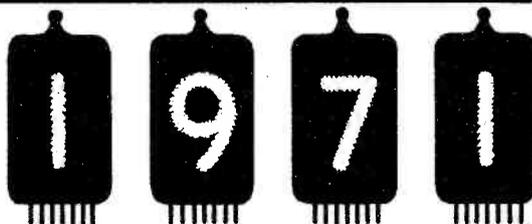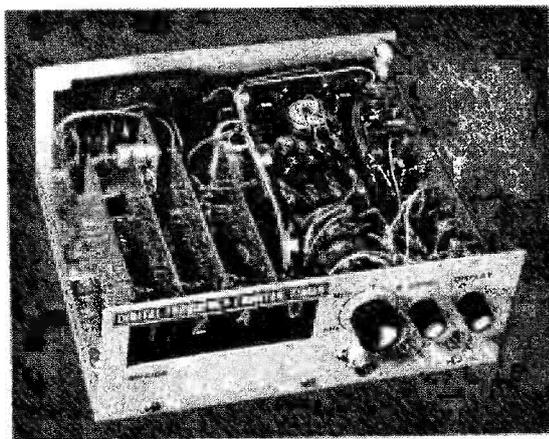


Yesterday's dreams have a habit of becoming today's realities in the field of electronics. Five years ago direct readout frequency meters cost so much that many companies flinched at the price but today inexpensive integrated circuits have brought these into the bracket for the home constructor.

Just imagine. Pop in any frequency (below 20MHz) and there you are—it's displayed before your eyes to the nearest cycle! The Digital Frequency Counter/Timer makes use of four digit neon numeral tube displays and uses the widely available "74" series of TTL i.c.'s.

Certainly this is a complex project—theoretically—but it's the i.c.'s that do the work, not you, and this project could be tackled by anyone who can wield a soldering iron.

ALSO:

**THE
'HARMONIC SIX'
RECEIVER**

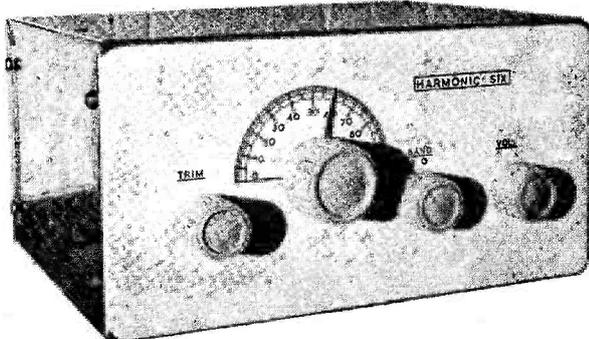

THE HARMONIC SIX RECEIVER

This is a six transistor superhet covering all the popular short wave bands and designed to power either a loudspeaker or headphones. The unusual feature is that there is no oscillator switching—instead the 2nd harmonic of the oscillator is used.

Standard parts are used throughout and this, together with the fact that it's designed by one of our top authors, makes this a first class project.

MINI-AMPLIFIER

Although measuring only 2" x 1" x 1", this amplifier using four silicon transistors has an output of 250mW into a 25Ω loudspeaker. A multitude of uses can be found for this project which can be built for a total cost of no more than £1.

**ALL IN THE SEPTEMBER
ISSUE ON SALE AUGUST 6th**



Fancy becoming a treasure hunter? Well, start here. We make no wild claims, just give you honest, proven results. Complete and detailed building instructions make this a suitable project for all levels.

HALVOR MOORSHEAD

WE thought very carefully before calling this article the PW Treasure Tracer. Certainly this sounds better than "metal locator" but could we justify the title? We think we can, especially after our test. We found nothing of great value but judging by the results we *could* have, that is, if there had been any there. Even if valuables are not found, certainly a whole lot of extremely interesting items will be and the history of an area of ground will yield up its secrets. However, your chances of finding coins are very good—about 150,000,000 coins are lost *every year* and a high proportion of these must be lost in areas where they can be found using a device of this type.

Not many months ago a hoard of Anglo-Saxon coins was found, using a metal locator, these were later auctioned for £9,000. It shows what can be done.

Metal locators work on a variety of principles and the author has experimented with a number of different circuits. Nearly all rely on the fact that metal objects distort magnetic fields. Complex designs have appeared from time to time making use of various effects—each claiming to be an improvement over others—but the author's experience has not borne out these claims. The principal used here—the Beat Frequency Type—is possibly the oldest and certainly the simplest. It needs only one wound coil, unlike many other circuits, and the sensitivity and results are excellent. We are deliberately not overstating our claims and the only figures for range etc. are those proved by our tests.

The Treasure Tracer comprises two low power r.f. oscillators working at about 130 kHz. One of the oscillators is screened inside the chassis and the frequency can be altered over a fairly wide range to match it close to the other. The second oscillator uses a frequency determined by the inductance of a winding which is used as the search coil.

In the absence of any material which will affect the inductance of this search coil, the oscillator is at one frequency. However when this coil is moved near some metal object, the inductance is altered slightly and the frequency of oscillation is changed. If the oscillators are set closely together an audio beat note is produced (equal to the difference in frequency) which may be amplified to feed a loudspeaker.

Finding a small copper clip (Item 16). The grass guard made from Perspex can be seen fitted under the coil framework.

Searching along were cart fitting; places should go



Let us assume that the search oscillator is working at 130·0kHz. The reference oscillator is adjusted to say 130·2kHz. The two signals are mixed together producing notes of $130·2 - 130·0 = 200\text{Hz}$. There is also another frequency produced, the sum of the two, 260·2kHz, but this can be ignored.

The presence of a metal object near the search coil will increase the inductance causing the frequency of the search coil oscillator to fall to say 129·8kHz. The beat note will now be $130·2 - 129·8 = 400\text{Hz}$ so the raising of frequency of the beat note will thus indicate the presence of a metal object near the coil.

From this theory the Treasure Tracer was built, using a frequency below 150kHz to conform to regulations. Initial tests in the lab showed that the prototype was working reasonably well and that a definite beat note was obtained—but how would it work in practice?

THE TESTS

The first test was arranged at the PW offices. A couple of dozen telephone directories were piled two high (making for a thickness of at least two inches) and coins ranging from 1/2p to 50p were hidden under certain piles. All coins were found immediately, but there was an extra reading—this turned out to be the wiring under the floor!

These tests in themselves were interesting and we were slightly encouraged but how would the metal locator (for we were still calling it that at this stage) fare in a field test? Only one way to find out—arrange one.

One Monday in late May Eric Dowdeswell (PW Editorial), Peter Metalli (Art Editor), Jack Wood (Photographer) and the author set out for Canvey Island in South Essex to put it to the test.

The weather was fantastic and the beach was far from empty and under the puzzled eyes of day trippers we began our search, panning up and down the beach, just above the water line.

Our hearts fell. For several minutes the whistle remained unaltered. Up and down we panned and gradually we began to think that the journey was wasted. Then suddenly the note changed frequency—a very definite, strong reading. As we dug Jack Wood

photographed us and the picture is that used on the cover. A quick dig produced a rusty hinge about three inches under the sand. We must have been unlucky to start with for after our first "find" we got readings every few yards. The items we found on this short stretch of beach and at other locations tried on the test are shown overleaf.

One thing cursed the search—silver paper. We found it everywhere and it accounted for over 75 per cent of all readings. We couldn't ignore these of course, for until we dug we didn't know what was causing the note to change frequency. The silver paper was from ice cream wrappings, cigarettes and sweets and even pieces so small that they were only found after extensive sifting, gave strong readings.

We altered our technique because of the sensitivity of the Treasure Tracer to small objects. As soon as we obtained a reading we carefully located the *exact* position before we began to dig—this could be done within an inch or two. As we dug we put the sand in two piles and checked at intervals with the Treasure Tracer that there was still a reading in the original position. If we had found nothing and the reading had disappeared we checked the two piles of sand. Invariably the metal was found in one of these. Even quite careful digging did not stop us missing several items the first time around.

Our deepest find was at 9in. The strength of the reading confused us at first—it was too strong and over a fairly wide area. The "treasure" turned out to be an aerosol can for retouching cars, a beer can of similar size was found at 4in with less trouble. The reading at 9in. was strong and it would be fair to assume that if the can had been deeper it would still have been found.

We were very successful near the sea wall where people were sunning themselves but due to the numbers already there we could only try a few yards of this but it was here that we found our only coin—which turned out to be a 1966 penny, badly corroded. We had expected to find more money and because of our failure to do so we arranged a test. One person buried coins of various sizes in a marked off area and we tried to locate them. These tests were successful and convinced us that we could unfailingly find all coins at depths up to four or five inches and larger coins at even more.

an old track. All we found here s (Items 1 and 26) but such nerally be more fruitful.



Money! Right against the sea wall we found our only coin—a 1966 penny, badly corroded.



The one that got away! The tide came in so fast that before we had time to dig out the "find" the water put an end to it.






what we found



- 1 Cart fitting (?). Found on the old farm road at 2" down.
- 2 Boiler clinker (?). Gave strong reading. 1" down.
- 3 Sheet metal handle, badly rusted. Found in author's garden at 2½".
- 4 Iron Hinge. Our first find, 3" under the sand.
- 5 Nail found under the beach, ½" down.
- 6 Copper gasket ring (?). Found under the beach at 6".
- 7 Shrapnel. Author's garden at 2".
- 8 Sharp metal spike. On the beach at 3".
- 9 Screw eye (from clothes line ?). Author's garden, 2" down.
- 10 Small piece of torn metal. Beach at 3".
- 11 Copper tube (squashed). Author's garden, 2" down.
- 12 Piece of unidentified iron. Beach at 1½".
- 13 File badly rusted. Garden at 2½".
- 14 Plant label (?). Zinc, garden at 4".
- 15 Shrapnel. Garden at 1".
- 16 Copper clip. Beach, found at 3".
- 17 Shrapnel, gun metal, beach at 4".
- 18 Screw-on bottle top, beach, 1" down.
- 19 Shrapnel. Author's garden at 3".
- 20 1966 penny. Beach at 3".
- 21 Encrusted iron fitting. Under the beach at 1½".
- 22 Thin copper tube (squashed). Beach at 2".
- 23 Copper tube (squashed). Author's garden at 2".
- 24 Piece of cast iron. Beach at 3".
- 25 Nail with small piece of wood attached. Beach at 1".
- 26 Cart fitting. Old farm road at 4".
- 27 Galvanised washer. Author's garden at 3½". Looked just like a coin until cleaned up.
- 28 and 29 (not shown) Aerosol can and beer can. At 9" and 4".

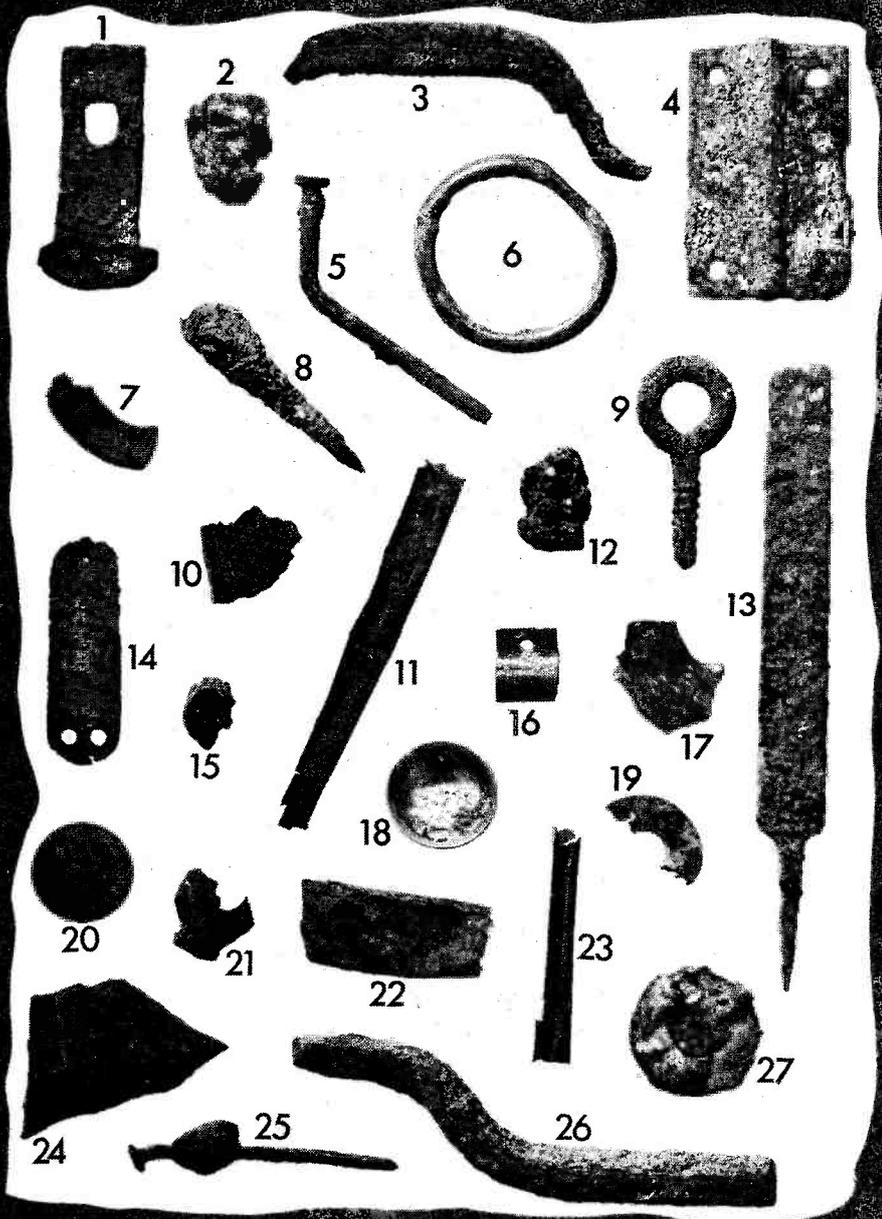

As we progressed experience enabled us to locate more accurately and our ears became more and more sensitive to changes in the note.

Just one word of caution. The beach will provide finds of all types but be careful near the water's edge. The spray landing on the search coil sent it haywire and searching became almost impossible. Later tests carried out in the light rain proved fruitless for the same reason. Not only does the impact of the spray or raindrop change the note but water trapped in the turns alters the inductance of the coil. As the water evaporates the pitch of the note changes—the effect lasts several minutes during which searching is impossible.

The second part of the test was made on the outskirts of a nearby castle. Not unreasonably the custodians would not let us search in the grounds but recommended trying outside, pointing the way to the original approach roads. A number of items were found, though none of any great age.

The final test was conducted in the author's garden in north-east London. Surprisingly most of the items were found at the same depth under the lawn. When a reading was obtained a circle of turf about 6in. in diameter was cut out, the item was found and the

earth replaced, laying the turf back in position; in this way no damage was done to lawn.

The house was built in 1913 and the lawn is probably original. The objects found were probably from the building process, spread out before turfing—though the file was probably lost by some workman long ago.

Some pieces of shrapnel were found. This is not really surprising for at the height of the London Blitz the fire from the anti-aircraft guns was so heavy that shrapnel apparently came down almost like "hail stones," according to a neighbour. Most of the shrapnel was cleared up but quite a lot would have buried itself in the ground.

A grass guard was developed from experience, this can be seen in the photographs. It is a piece of Perspex, 6×6in. fixed to the bottom of the search coil framework to stop blades of grass from touching the coil and so cause the beat note to change.

A total of four hours test searching was carried out to produce the finds shown. In that short period we became very much better at identifying signals and in the end knew exactly where to dig and even how deep we could expect to find the metal object.

HOW TO BUILD THE P.W. TREASURE TRACER

The circuit of Treasure Tracer comprises three distinct sections: the search coil oscillator, the reference oscillator and the audio amplifier.

The search coil oscillator is made around L1 which is wound on a wooden framework shown in Fig. 1. This is made up from two 6in. lengths of hardwood batten with a section of 1×³/₄in., though this section is not critical. These should be made into a cross by half-lapping as shown and small V shaped grooves cut into the ends. This framework must be rigid and if poor joints are made, these should be firmly glued.

The handle is made up from wood of the same cross section as the coil framework and about 4ft.

in length, though this will depend upon the height of the user. The base of this should be cut at 45° and screwed firmly to the coil former. A normal type screw can be used; it will alter the inductance of the coil but as it is a constant it does not affect operation.

A small three way stand off tag strip should be mounted a few inches from the bottom to provide a firm anchorage for the coil wires. A thin enamelled copper wire should be used; the gauge is not too critical and 32 to 38 s.w.g. will do. If the wire has to be specially bought, 36 s.w.g. (as used in the prototype) would be a good choice. The start of the wire should be soldered to one of the outside terminal tags and 48 turns should be wound in the upper grooves, ending by fixing to the centre terminal tag.

The second part of L1 is wound in the lower


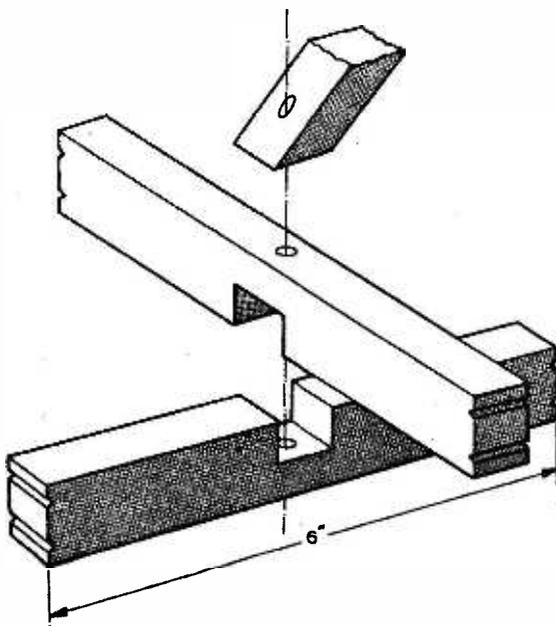


Fig. 1 : The construction of the search coil wooden framework.

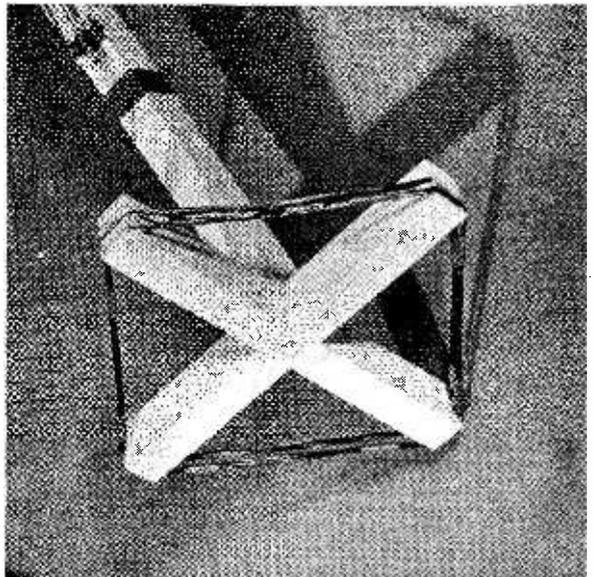

The search coil. Note the terminal tag at the top left and the taping of the wires.

grooves, again 48 turns, anchoring at the centre and other outer terminal. Both coils should be wound in the same direction and the centre terminal used only as a convenient centre tap which is needed for the circuit.

All windings should be tight, including the leadups to the terminal tag. Once completed the windings should be taped together at several points to hold them firmly.

It should be emphasised that the successful operation of the Treasure Tracer depends largely on the care taken in the construction of this search coil and loose windings will make operation very difficult and unreliable.

L1 is connected into the collector circuit of Tr1 as shown in the circuit diagram in Fig. 2. C2, shown as a 500pF capacitor, is connected across the coil and this combination will resonate at about 130kHz. The value of C2 and C4 (in the reference oscillator circuit) should be of the same type and reasonably close in value; miniature 5 per cent polystyrene types are very good here and inexpensive. It doesn't

matter too much what their values are as long as they are the same, but to stay within the regulation frequency band they should be over 390pF.

The components in the search coil oscillator are connected to form a Hartley oscillator, working at the frequency mentioned. R1 provides the base bias for Tr1 and C1 provides the feedback signal to maintain oscillation.

A low value resistor, R3, is connected in the emitter and this is shared by Tr2 which forms the reference oscillator.

L2 is a standard Denco LW aerial coil which is fitted with the three windings necessary. The main one (between points 1 and 6) is tuned by C4. Another of the windings is arranged to feed back to the base forming a blocking oscillator; this also carries the base bias to Tr2.

The shared emitter resistor R3 means that there is a mixing action in Tr2 and a degree of the search coil oscillator signal is mixed with that of the reference oscillator to make the beat note.

It is necessary to tune one of the oscillators to

bring it close to that of the other and here the reference oscillator can be tuned over a wide range by altering the position of the ferrite dust core. The coil should be mounted as shown in Fig. 3 with a small knob fixed to the brass thread attached to the dust core.

The take-off point of the coil comes from the third winding of L2 (between pins 8 and 9). This is d.c. blocked by C5, detected by D1, smoothed by C6 and applied to the base of Tr3.

The signal here will be the beat note or an audio

frequency represented by the difference in frequency of the two signals.

The base bias for Tr3 is provided by R5 with R6 acting as the collector load.

Tr4 further amplifies this audio signal and applies it to the 80Ω loudspeaker in the collector. R7 and C7 are included to raise the emitter voltage of Tr4 and to limit the quiescent current. The impedance of the

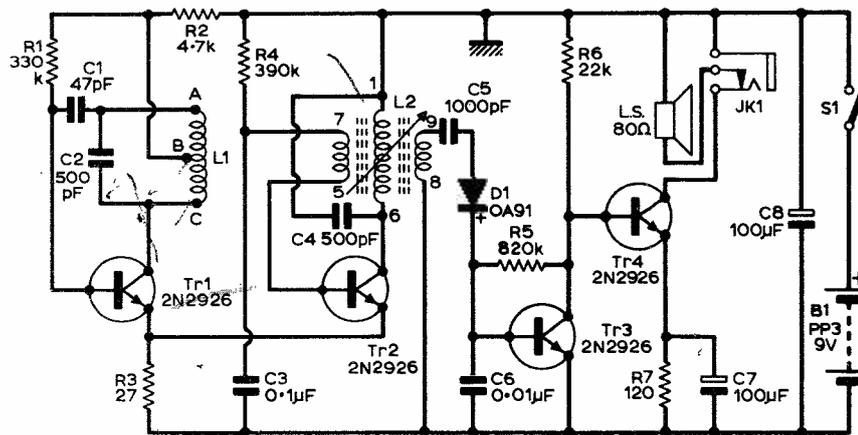


Fig. 2 : The complete circuit for the P.W. Treasure Tracer.

★ components list

Resistors

R1 330kΩ	R5 820kΩ
R2 4.7kΩ	R6 22kΩ
R3 27Ω	R7 120Ω
R4 390kΩ	All ½W, 5% types.

Capacitors

C1 47pF	C5 1000pF
C2 500pF†	C6 0.01μF
C3 0.1μF	C7 100μF 6V
C4 500pF†	C8 100μF 25V

† see text

Semiconductors

Tr1 2N2926	Tr3 2N2926
Tr2 2N2926	D1 OA91
Tr3 2N2926	

Miscellaneous

- L1—see text and drawings
- L2 Denco LW aerial coil, Type 1T
- LS 75-80Ω miniature loudspeaker
- JK1 3.5mm jack socket with cut-out switch
- SW1 On-Off slide switch
- B1 PP3, 9V battery
- Chassis 6½ x 2½ x 1½in., (H. L. Smith Ltd. 287/9 Edgware Road, London W.2.) 60p inc. postage.

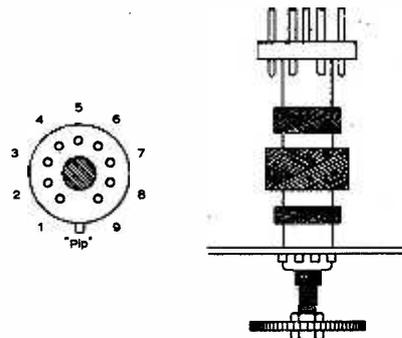


Fig. 3 : The pin numbering and mounting of L2.

loudspeaker can lie between 35Ω and 80Ω and various miniature types with impedances in this range are available. If difficulty is experienced in obtaining one of these, the loudspeaker can be replaced by a transistor output transformer (such as the Eagle LT 700) feeding a lower impedance loudspeaker.

There is a tendency for the two r.f. signals to lock together if they are within a few Hertz of each other. This is not too serious but the inclusion of R2, which drops the supply to Tr1, reduces this tendency. Theoretically the junction of R1 and R2 should be decoupled to the negative line using a $0.1\mu\text{F}$ capacitor; this however made no difference in the prototype but may be included if Tr1 fails to oscillate.

Note that the chassis is connected to the positive rail rather than the more conventional negative line. This enables simple fitting of the jack socket, JK1, one connection of which has to touch the chassis.


CONSTRUCTION

The majority of the components are mounted on a small piece of 0.15in. matrix Veroboard, 16 holes by 13 holes and this is shown in Fig. 4.

The chassis used in the prototype, and highly recommended, is available from H. L. Smith Ltd. (see components list) and the bottom of this is drilled as shown in Fig. 5. The three holes in a triangle are fitted with 1in. , 4BA screws and the component board is mounted on these, spaced off by nuts.

The loudspeaker can be glued in place and the wiring between the Veroboard and the other components is shown in Fig. 6.

The recommended chassis comes with a lipped lid which is screwed to the wooden handle as shown in Fig. 7. A hole $\frac{1}{4}\text{in.}$ in diameter is fitted with a rubber grommet to take the wires leading to the search coil L1. Stiff wire should be used to run between the chassis and the terminal tag and this should be firmly taped to the handle as shown in the photographs. A small loop is left before entering the chassis to enable it to be opened.

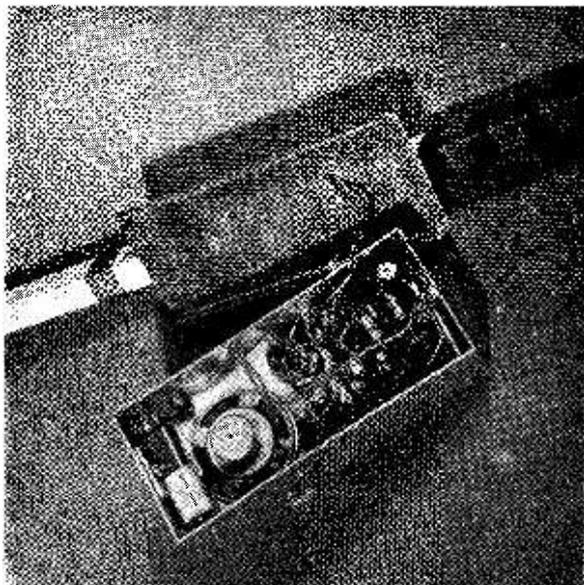

An internal view of the completed prototype.


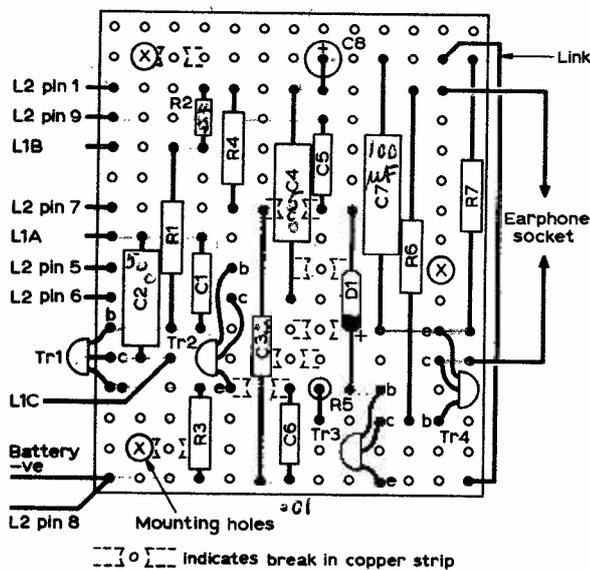


Fig. 4 The component layout on Veroboard.

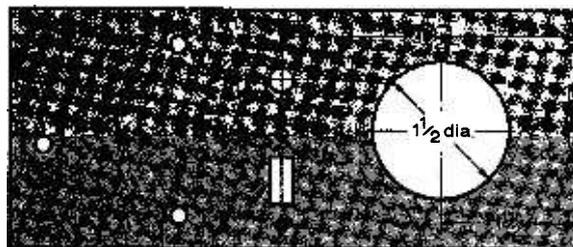

Cutout to suit switch

Fig. 5 : The drilling of the bottom of the chassis.

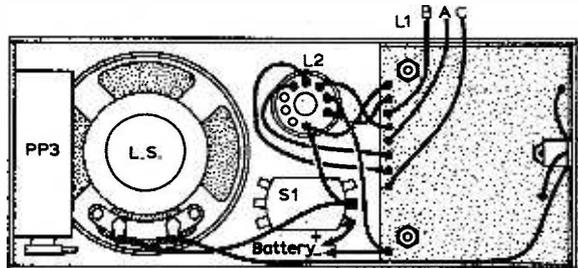


Fig. 6 : The wiring between the component board and the other components.

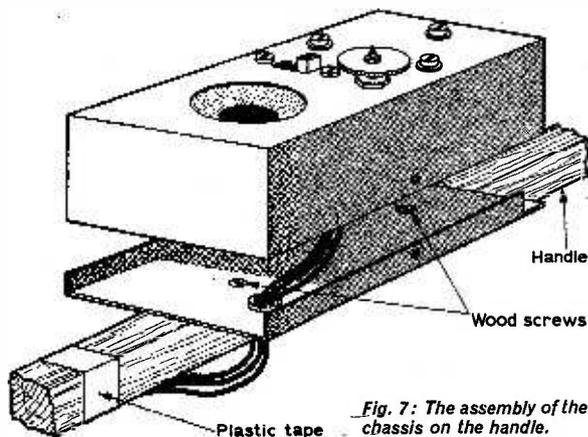


Fig. 7: The assembly of the chassis on the handle.

TESTING

Once all wiring is done a visual check should be made to ensure all is well and this being so, the Treasure Tracer can be switched on.

If all is correct the tuning of L2 will produce two positions where a strong beat note can be heard.

A number of weak signals may be heard at other settings. These are probably caused by radio signals on those frequencies but they are very low compared to the main signals.

The beat note should be set at the lowest stable audio note—probably between 50Hz and 200Hz. When a metal object is brought near L1 the note will either go up or down, depending on whether the search coil oscillator is working higher or lower than the reference oscillator.

By experience it was found that it was better to arrange for the note to go down in frequency when a metal object was approached but this is up to the user—a rising note may be preferred.

Certain objects—especially brass—go against the general trend and operate in reverse—causing the note to rise when iron and aluminium cause it to fall.

No volume control is fitted as the output from the loudspeaker is fairly low—about 75mW, though this proved sufficient and was not found too low even by the sea shore. Headphones or earpieces with impedances between 50Ω and 4000Ω all work when plugged into the socket—this automatically cuts the loudspeaker out if wired as shown.

The current consumption is not too high—it should certainly be under 20mA and several hours of searching are possible using the PP3 battery specified.

Before carrying out your first search, eliminate as much movement of the leadup wires as possible by taping them, as even a mild breeze will cause a change in note otherwise.

In testing it will be found that nearly all large objects cause some change in frequency—even laying the coil on the ground—but these changes will be minute compared to that caused by even a small piece of metal.

Do not expect to become an expert in a few minutes. The use of a device of this type needs a degree of skill and it took all of us several hours before we became reasonable at it. Now, after the test, we have used the detector to find a whole mass of new material, including more coins, but this was outside the testing period and the finds were not witnessed so we are not including later items in the list.

Well, where do you search? *Note that there are very heavy penalties for using such a device in areas scheduled as being of historical interest and there have been prosecutions for this.* However there is no need to search in such places and paths or

To conform with the Wireless Telegraphy Act (1949) a licence is required to use the Treasure Tracer described here.

Under Section 1(1) (Pipe Finder Licence) the band 16 to 150kHz can be used for equipment of this type.

A licence for five years costs 75p and can be applied for on a form obtainable from the Ministry of Posts and Telecommunications, Waterloo Bridge House, Waterloo Road, London S.E.1.

roads that have been in use for centuries are a good place to start; river banks will also prove fruitful.

An excellent small book "A Fortune Under Your Feet" by E. Fletcher elaborates on this and is recommended reading for those encouraged by early results.

If you find something of interest, let us know. We are offering £2 for the most interesting letter we receive dealing with objects found. It doesn't have to be valuable, just as long as it is interesting. ■

I.C. of the Month—continued from page 310

two heatsink tabs. If the i.c.'s are to be used to their full 5 watt rating some form of additional heatsinking is needed. This may take the form of directly soldering about two square inches of copper to each tab or alternatively to equivalent area of printed circuit board foil. At any rate, in most applications the full output ratings will not be approached so that the above precautions are necessary only for worst case operating conditions.



View of I.C. showing unusual heatsink tabs and staggered leads.

To find out the maximum output currents that the units can deliver all one has to do is to determine the product of the voltage drop across terminals 2 and 7 of the i.c. and the current drawn, making sure that the answer does not exceed 5 watts.

MAXWELL

by G8DSH



"He says never mind the beads—have you got any back numbers of Practical Wireless?"

parts of the i.f. circuitry are doing their job. But before we can do this, it is necessary to check the audio section and the detector.

Let me refresh your memory with Fig. 1. Here we have a skeleton circuit of an a.m. receiver, showing the tuned circuits with which we are concerned here, the detector and a hint of the audio section that will follow. It is obvious that a signal injected at a post-detector stage must be at audio frequencies. In the old days, it was easy enough. A finger tapped on the appropriate valve grid, or on the 'hot' end of the volume control would produce a healthy 'buzz'. Mains pickup and the high impedance of the input circuits made this possible. With a battery-operated piece of equipment or the low-impedance circuitry of semiconductor devices, the 'disturbance test' type of operation is not so effective. It can, in fact, be positively dangerous.

SIGNAL INJECTION

The answer is to inject a signal of known characteristic (even if unknown precise amplitude), simply to verify that the following stages are working. We are not interested so much, at this point, in their exact efficiency, their lack of distortion, their overall output. For the following tests we need some method of indicating variations of output, either at the final part of the receiver—the feed to the loudspeakers—or at some earlier audio stage, where the readings may be more convenient.

It must be stressed again that when signal injection methods are employed, we are not expected to measure the output accurately. As Gordon King has explained, the quality of one piece of test equipment is determined by (a) the standards to which one must test the circuit, (b) the quality of associated gear and (c) the standard of testing we wish to apply.

Signal injectors are the easiest of all test instruments to make and apply, and there have been numerous suggested circuits in PW. We shall skip lightly past the subject, pausing only to remark that if you are thinking of alignment, it can be argued that you will be using a signal generator. There are very few of these that do not incorporate an audio output facility. There is your post-detector tester, ready made.

The 400Hz or 1kHz note we hear from the loudspeaker is suitable for rough tests and basic alignment in an emergency. It is certainly no more than a guide for precise circuit adjustment of the modern set. Visual alignment checking is needed so a meter, or some other visual indicating device, will have to be used. So this is where the ordinary multimeter can be pressed into service.

With valved equipment, nothing is easier than a low a.c. voltage-reading meter (say from 0-5V a.c.) across the loudspeaker or a dummy load. The dummy load, it should be said, has not been outdated by transformerless output transistorised receivers. For test and measurement purposes, the output circuit should always be correctly loaded.

Figs. 2(a) and (b) show alternative ways of indicating audio output, for both valved and transistorised equipment. We include these notes on valved equipment simply because the accent here is on servicing and it is in the nature of things that servicing will be required more often on older equipment. Measurement of anode current in an output

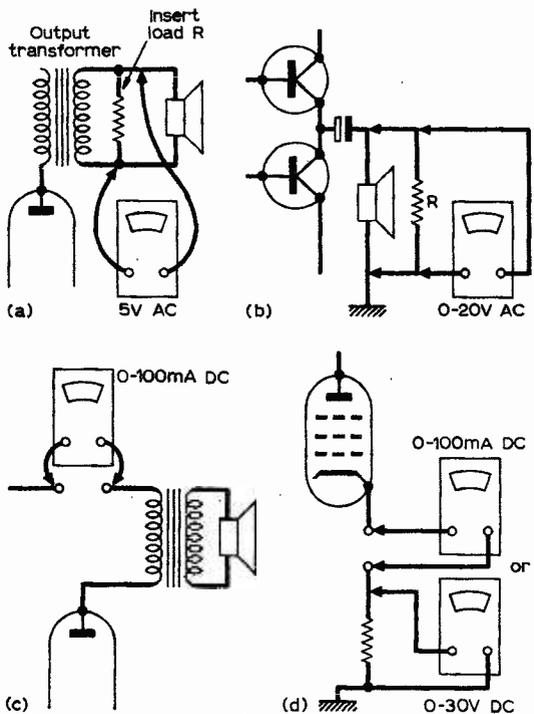


Fig. 2: Measuring output, (a) across dummy load or shunting speaker, (b) across speaker of transformerless stage, (c) current indication in series with anode load, (d) in series with cathode or voltage across bias resistor.

stage of valved equipment, either in the anode or cathode lead, is an alternative, where a low voltage d.c. meter, or a 0-100mA d.c. meter is available, Fig. 2(c) (d).

MEASURING OUTPUT

Breaking into the output stages of a transistorised amplifier for such alternative readings is neither easy nor desirable. Because of the low impedances of emitter circuits, voltage variations are too small to be of any great value, and should, in any case, be stabilised.

But let's do things properly. Let us consider the output power that we should get, and make arrangements to measure that. There are two things to consider here: audio power measurement and indication of standard audio output. They are not the same. As Gordon King will be showing later in greater detail, measurement of audio power is not a simple process, and interpretation of results must be made with great care.

Briefly, the expected outputs from general apparatus would be: (a) small transistorised radios, 500mW to 1 watt (b) larger radios, 1 watt to 3 watts (c) tape recorders and record players, 2-6 watts (d) small amplifiers, up to 10W (e) larger amplifiers, 10 watts upwards.

Standard outputs are related to the sensitivity of the apparatus. For example, a radio may be quoted as having a sensitivity of $25\mu\text{V}$ for m.w. reception, $40\mu\text{V}$ for l.w. reception and $1\mu\text{V}$ for both s.w. and v.h.f. reception. Alone, these figures mean nothing. They must be related to the standard audio output and to other factors such as signal-to-noise ratio. In the case of these quoted figures, the audio output

would be 50mW for a s/n ratio of 6dB, relative to the 0dB figure of $1\mu\text{V}$.

This gives us a clue to the statement 'decibels below 1 volt' which may sometimes be used. 'Decibels below 1 milliwatt' is another alternative and 'field strength' yet another. The last term is employed to assess sensitivity when loop or ferrite rod aërials are used.

For now, we do not need to worry too much about all this. Practical service work very often consists of bringing up to scratch the circuits that may be only a little out of alignment. If components in tuned circuits have been replaced or if maladjustment has occurred, then the procedure is to check the alignment throughout and to make the small alterations found to be needed.

VISUAL DISPLAY

The oscilloscope is invaluable here, saving hours of careful tabulation and giving both the facility of viewing the result of the input signal and of measuring it. A secondary facility, often overlooked, but quite important, is the ability we have, when viewing a trace, of determining how much output is signal and how much noise and distortion—common causes of faulty results when only a meter is used.

We shall later look more closely at this matter of noise and distortion assessment. For now, a brief note on the practical alignment of a typical receiver, using a standard signal generator and a measuring device, augmented by an oscilloscope. Response curves are the usual method of measurement and, very often, a manufacturer will give no more than the


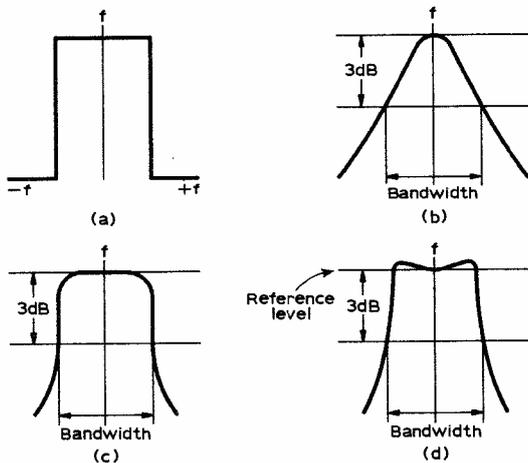


Fig. 3: (above) Response curves, carrier frequency f with $+f$ and $-f$ representing bandwidth limits. (a) Ideal curve, (b) peaked response, with bandwidth indicated at -3dB (c) flat tuning to give desired response, same peak level and bandwidth as (b) but quite different response. (d) double-hump tuning as approach to flat top response of (a)

Fig. 4. (right) Instrument set-up for measuring i.f. response. Note attenuator resistors R_a and R_b , and isolating capacitor C_1 .

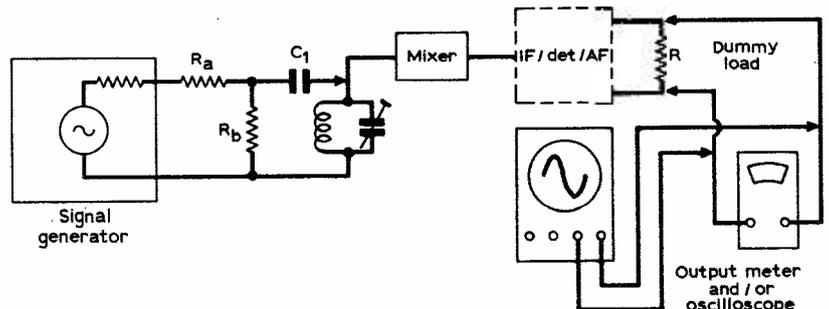

expected curves in his service manual, referenced to some level and bandwidth. It is as well to be clear at this point, therefore, what we mean by response curves, reference levels and bandwidth.

Fig. 3 shows a selection of the graphs one would produce by plotting the output from the receiver (vertical axis) against the frequency at which the signal was applied (horizontal axis). It is possible to produce these curves from careful and detailed measurements but it is much simpler to feed to the receiver a signal which varies regularly across the bandwidth, locking this to the timebase of the oscilloscope and displaying the output from the detector of the receiver. Such an input signal is obtained from a sweep generator, or 'wobbulator' (see page 1038 PW April 1971):

The response characteristic of a superhet receiver is mainly that of its i.f. circuits, for the r.f. circuits are not so sharply tuned. Quite often, response testing and alignment concentrates on the i.f. circuits, leaving the r.f. section of the receiver to be aligned on one or two spot frequencies and checking the padding and trimming of the oscillator.

The acceptance band of a receiver has to take in the sidebands of the transmission for full handling of the higher frequency components of the modulation, but if it extends too far beyond this, the signal-to-noise ratio will suffer. A perfect response characteristic—an impossible one—is shown in Fig. 3 (a). All the frequencies within the passband are received with the same sensitivity; those outside the passband having no effect. In practice, the response curve may be more as (b), where the 'usable' bandwidth is that between the -3dB points. This is where output power falls by 3dB or half its maximum value.

Note, however, that the response curve may be neither as flat as (a), nor as gently peaked as (b). In fact, it may be double-humped, as in (d). One important point here is that the reference point, relative to the -3dB level, is the centre frequency of the passband, and not the peak of the humps.

Merely to state the frequency limits at which a curve is 3dB down is not enough. This tells us what the gain of the receiver is, but not the extent of the rejection of unwanted frequencies. Always plot beyond the -3dB points, as shown in the accompanying curves.

Making response measurements of the a.m. receiver with a low audio frequency modulating signal (example: 30% modulation at 400Hz), we feed the signal generator to the mixer input, as shown in Fig. 4. It is essential that the impedance from which the signal is derived is as low as possible. In the mixer input, the tuned circuits will not be at the intermediate frequency, so the low impedance is needed. Hence the two resistors, R_a and R_b , where

a reduction of the generator output impedance from the usual 50 or 75 ohms to as little as 10 ohms can be effected. The values are easily worked out: for a generator of 50 ohms output, to present a 10 ohm (very nearly) load to the mixer input, we need to make R_a around 40 ohms (nearest preferred value 39 ohms) and R_b 10 ohms. The choice of values gives a 10:1 voltage ratio also, just in case you want to work out sensitivity figures.

The value of C_1 should be such as to make its reactance at the test frequencies no greater than 50 ohms. At an i.f. of 470kHz, C_1 would thus be around $0.01\mu F$. Its inclusion is to prevent the d.c. bias conditions being upset.


Disabling the a.g.c. is the next consideration although the method of disconnecting the a.g.c. line and putting a fixed bias in its place may not be so simple with modern sets. Sometimes the manufacturer will indicate a method of killing the a.g.c. action. The need to do so is evident from an understanding of a.g.c. action, which has already been described.

If we feed to a receiver aerial input a signal varying between say a microvolt and a volt, we may find that at around $5-10\mu V$ input, a 2:1 increase in input produces very nearly a 2:1 increase in output. But after about $100\mu V$ input, the curve relating output to input flattens drastically, and it needs a good deal more 'in' to produce just a little more 'out'. The a.g.c. curve, in other words has a definite 'threshold value' with two fairly linear slopes, above and below that threshold. In fact, a.g.c. "quality" is often defined in terms of the mean slope of the curve above the threshold.

Assuming first that the a.g.c. is prevented from working, our tests would comprise first setting the generator to the reference frequency, with its output adjusted so that at full receiver gain the rated full output is obtained. The generator output is then attenuated to produce the 'standard' output, 50mW. The receiver's gain control can be used to set the output indicator to a convenient value and then left strictly alone.

The generator is swung over the required frequency band and output plotted relative to the reference. The bandwidth is the frequency difference between the 3dB 'down' points.

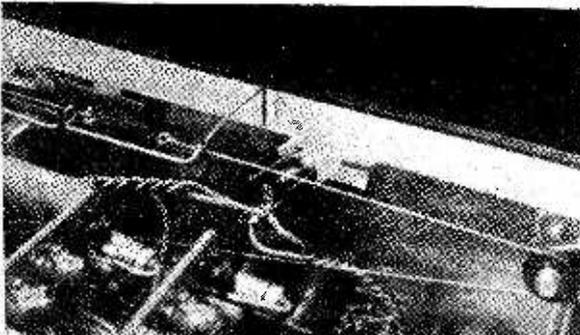If the a.g.c. cannot be 'killed', there are alternative ways of going about the checking. We can tackle the problem 'backwards', measuring for a constant output for a 3dB increase of input, with the attenuator of the signal generator set to increase the test input by 3dB, then the two limiting frequencies where the



Close-up of am.if.m. tuner showing part of a.m. ferrite rod aerial at left and drive cord and pointer.


monitor reading is returned to the reference level define the bandwidth.

Another way of testing bandwidth without having to 'kill' the a.g.c. is to keep the carrier frequency of the generator constant and to vary the bandwidth. This cannot be done with the normal signal generator, as modulation frequency and depth are often fixed. But where a c.w. only output is obtainable and a separate audio generator is available to apply a varying input, then the r.f. generator can be set up to the central frequency and the modulation varied in frequency, without any change in depth, and a note made of the points at which the output reading (across the detector load, for utmost accuracy) is 0.707 of the reference level. These limits are the bandwidth, i.e., bandwidth is twice modulation frequency.

CW TESTS

It is not so easy to align higher quality receivers. The sides of the response curve can appear deceptively steep, because of the relative phase shift of the sidebands. The way to overcome this possibility of error is to use a c.w. (unmodulated) input and to read off the d.c. voltage at the detector.

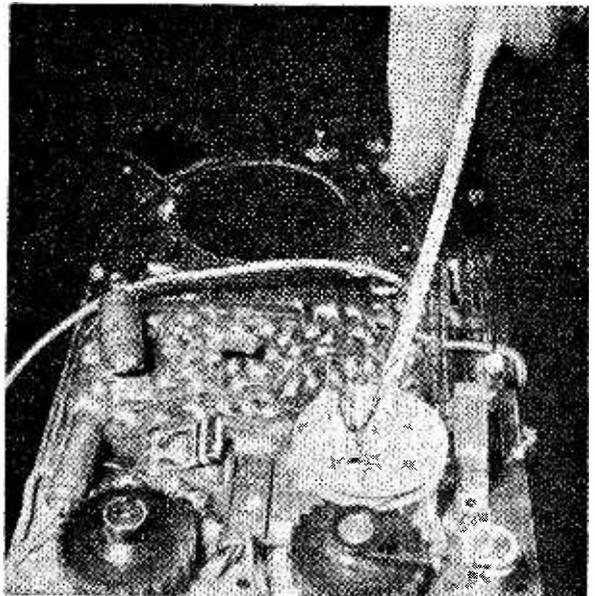One snag: there may be some standing d.c. voltage. It can be allowed for and carefully taken into



Before attempting alignment it is essential that drums, cords, springs and attachments are in order. Always check traverse of pointer before making adjustments.

account by subtracting it from final readings. The use of a d.c. valve voltmeter or similar instrument allows us to back off the settings to obtain a new zero.

Working on s.s.b. receivers can be a good deal easier. Better-class communications receivers work also in the single-sideband mode and these can be aligned by using the beat between the input signal and the internally generated carrier, with a.g.c. switched off—which is usually possible with these sets.

PRACTICAL POINTS

Procedures must differ between makes and models. Some general rules follow:—

(1) Allow sufficient warming up time before making tests. On valved equipment, fifteen minutes for both receiver and test gear should be regarded as the minimum. Despite all the advertising, transistorised equipment does not 'warm up' to operating conditions 'in the twinkling of an eye'. One very famous hi-fi amplifier I recently tested took seven-and-a-half minutes for the current in the output stages to settle to a steady reading, and that is not exceptional.

(2) Check mechanical points. Dials and cursors, pointers and drums should be run from end to end of their travel and limits noted. Where datum points are provided by makers, these should also be checked before alignment commences. In general, maximum frequency (minimum wavelength) should be indicated when the capacitor plates of the usual ganged capacitor are fully unmeshed.

(3) Make any necessary adjustments to counteract backlash, so that a setting of the cursor or pointer accurately reflects the setting of the tuned circuits.

(4) Check before operations that the required trimming tools that are available. It is simply asking for trouble to use worn grub-screw drivers where hexagon-holed slugs are used, or when core slots are only suitable for miniature plastic tools. Some time ago *PW* presented a set of plastic trimming tools to readers. Mine are still in use, augmented from time to time by filed plastic knitting needles and crochet hooks.

(5) Cores of inductors, despite all our efforts and care, may jam. The only recourse then is to drill or chip them out, taking great care not to damage the former wall or the inductor. Resetting of new cores may need either a rubber band inserted in the core or the use of a non-hardening adhesive. There are core-locking compounds that provide an adequate fixing but still allow some adjustment.

(6) Finally—before starting, make sure that test gear is isolated and that there are no false return loops. Connect the neutral side of a.c./d.c. equipment to chassis if you have no isolating transformer and provide capacitive isolation, as previously described.

GENERAL PROCEDURES

Consider a combination a.m./f.m. receiver, as shown in skeleton form in Fig. 5. Crystal filters are used widely and we can expect to find this trend growing. No alignment is normally required except

for the last stage, which will be peaked up to the intermediate frequency. A little care is needed here and some 'swing' about the nominal frequency may be necessary. A good idea is to peak the last i.f. to the input from a weak signal after the rest of the alignment has been done, bringing it into tune only temporarily at first.

Where tuned circuits are used throughout, inject a signal at the frequency changer that will produce a 50mW output across the appropriate load. As power in watts is the voltage squared divided by the resistance, we can work out the required reading. (For 3 ohms this will be 0.387V, for 8 ohms, 0.633 volts and so on.)

A meter that has a full-scale deflection of around 2.5V a.c. is required. Exact readings are not important at this stage as our aim is to maintain the output at the same level while bringing the circuits into tune, turning down the input as the gain increases. For this, the volume control will be turned to maximum, and if there are tone controls fitted, the treble control will be adjusted for the least top-cut.

Tuned circuits should be adjusted for peak output, starting at the rearmost and working toward the mixer. After initial peaking, go back over these adjustments. With some sets, there may be a tendency for one tuned circuit to 'pull' another, and readjustment should be made until no further improvement can be gained.

Where the response curve is humped, two peaks will be found as the signal generator is swung over the passband. In this case, the middle position should be used. Tune for the slight dip between the peaks.

IF REJECTION

Before readjusting the signal generator, remove it from the mixer input and apply the signal, still at intermediate frequency, to the aerial input, then tune any i.f. rejection circuit to give the **minimum** output. It is always wise to make this test early on, then rechecking after mixer alignment. For this test, increase the i.f. output from the generator and switch the receiver to the medium-wave band (where breakthrough could be bothersome), turning the tuning gang till the vanes are fully meshed, i.e. the low frequency end of the band.

Another rejection circuit that will be found nowadays is the 19kHz pilot tone filter. This is also tuned for minimum output with a strong 19kHz tone injected.

Alignment of the broadcast band is conveniently done at this point. Set the generator to around 600kHz (500m) and the pointer of the set to the same

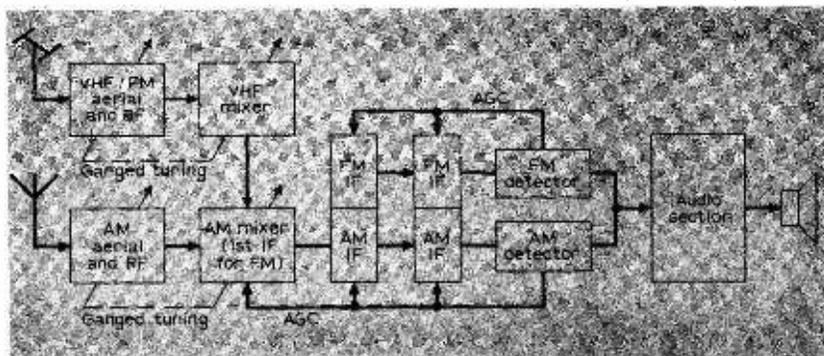


Fig. 5. Block diagram of combined a.m./f.m. receiver, with switching omitted, as a guide to following the alignment procedures described in the text.

frequency, after checking that it traverses the scale correctly, and reaches any datum points marked by the manufacturer with the correct scale indication.

Adjust the padder and/or the oscillator coil (if this is adjustable) and obtain maximum output. Then readjust to the other end of the band, setting the trimmer. Best procedure is to carry out these operations for the mixer first, then peak up the aerial circuits and return to the mixer for readjustment, then again to the aerial to make sure the circuits remain in tune. Adjustments of this nature take time and demand patience. Maybe this is why realignment of receivers can be a costly job! It is never good enough to make a perfunctory gesture of 'twiddling the cores'. The long wave adjustments can then be done.

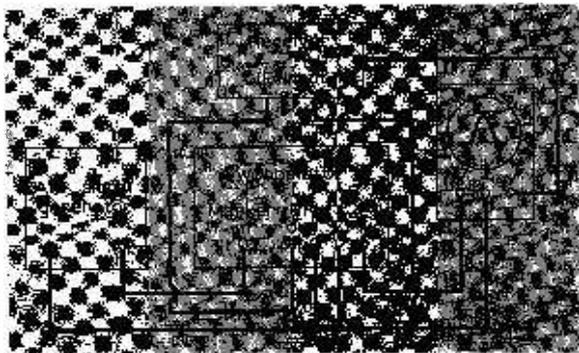


Fig. 6 Instrument set-up for checking i.f. response of f.m. receiver.

Do not attempt them in reverse order, as settings of the medium wave tuning can affect the long wave band. Similarly, where there are several short wave bands, first adjust the highest frequency band.

Long wave adjustment often consists of adjustment of one trimmer in the mixer circuits and one in the aerial circuits. There is rarely any need to check tracking over the band as carefully as one would with medium wave tuning, there being few stations available.

Short wave adjustment often requires slight movement of coil turns and care has to be taken with the dressing of leads. Tuning is considerably simplified by the omission of padders in the short-wave section of most receivers. Instead, we find coil adjustments, or core settings being made at the low frequency end of each band and trimming used at the high frequency end.

FM ALIGNMENT

Most adjustments to f.m. tuned circuits are carried out nowadays with the aid of a wobulator and oscilloscope. Here, we find the output displayed, the signal swept over the response band and variable capacitors and coil cores adjusted to obtain the correct response curve. Addition of an a.m. marker generator aids the set-up, and the inter-connection of these instruments is shown in Fig. 6.

Because the average serviceman is unlikely to possess a wobulator, we shall concentrate here on the adjustment of f.m. circuits using only an ordinary signal generator and a high-resistance meter. A more tedious job, but practically as efficient.

First requirement is a d.c. voltmeter, capable of reading around 10 volts, with a 20,000 ohms/volt sensitivity at least. This is connected across the d.c. load of the ratio detector, the aim here being to keep the reading to a set level, determined by circuit characteristics, by turning down the generator input as the circuits are brought into line.

With the generator tuned to the f.m. intermediate frequency (10.7MHz), and with the modulation switched off, the signal is injected at the mixer and



◀ Oscilloscope trace of response curve using wobulator, with marker pip at top of curve (centre frequency f).

A similar response curve but this time the marker pip is placed at the -3dB level on one side of the curve. ▶



the i.f. circuits aligned for maximum output. The correct procedure, again, is to start at the rearmost and work forward, but even more care is needed and constant rechecking is necessary.

If a ratio detector is used, the next step is to note the output reading from this 'peaked-up' process, transfer the meter to the a.f. output capacitor and note that the reading is now exactly one-half of what it was before. The ratio detector winding is adjusted to achieve this.

After this, repeat the steps until no further improvement can be gained. It is important to ensure that later steps do not impair earlier results; hence this need for repeated operations.

The ratio detector is finally balanced. The coil that gave its 'half-volts' reading earlier is now readjusted for a minimum reading. The mean of these two is calculated: i.e., halfway between the maximum and minimum voltages that can be obtained by adjusting the coil of the ratio detector. This is the setting for correct alignment.

END OF PART FOUR

NEXT MONTH 'MAC' HELLYER WILL DISCUSS HOW FM STEREO SIGNALS ARE GENERATED AND TRANSMITTED. THEN FOLLOWS DETAILS OF TYPICAL STEREO DECODERS AND THEIR ALIGNMENT.

the EUROPEAN SPACE RACE

Marconi sets the running with a multi-million pound contract for Skynet II.

by JOHN CHAPMAN

THE first communications satellite system to be designed and built in Europe will be a British venture. Marconi Space and Defence Systems, a member of the GEC-Marconi Electronics group, has won a multi-million pound Ministry of Defence contract to design and build two satellites to gradually take over the expanding military communications traffic currently being carried by "Skynet I," a satellite built by the Americans for exclusive use by the British Armed Forces.

Skynet II will be more powerful than the existing satellite and will be one of the most advanced satellites in orbit in the world.


The first of the new satellites will be launched into a near synchronous orbit over the Indian Ocean in the first half of 1973. By this time the American built Skynet I will be approaching the end of its design life: the second of the new satellites will be used as a standby and launched later in 1973.

The GEC-Marconi group has already played a major role in the provision of ground stations for the Skynet system. Four 21-foot diameter dish transportable stations have been supplied by Marconi Space and Defence Systems at Stanmore and this part of the company is at an advanced stage in the development of a 3½-foot diameter aerial terminal (called SCOT) which can be mounted on a ship to provide the Royal Navy with further links into the Skynet system. Marconi Communications Systems, based at Chelmsford, built the first three earth terminals back in 1966. Two of these 40-foot diameter ground stations which were used with the satellite system built for the U.S. Government and used successfully by the American Armed Forces have now been modified to form part of the Skynet system.

Outlining the activities of Marconi Space and Defence Systems at Portsmouth, the company's manager Mr. M. Lovell said that their experience in spacecraft electronics has been developed over a period of about seven years in which time they have provided the satellite electronics for every British spacecraft programme to date.

The first of these was Aerial 3 (later called UK3), a satellite launched in May 1967 as part of a scientific programme. Although this satellite had a design life of a year, it was not switched off until 1968 and furthermore, the system was reactivated last September in order to check on the long-term reliability of the electronics equipment in a space environment.

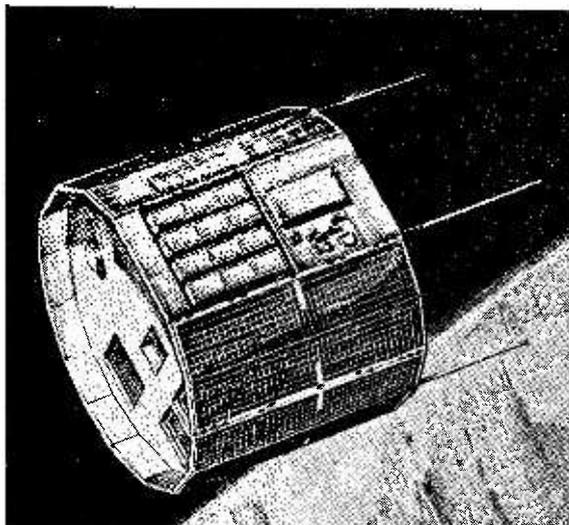The next important project was the X3 satellite which will be the first technological satellite to be launched in a Black Arrow launch vehicle. In this project Marconi engineers are responsible not only for the onboard electronics but also for satellite assembly, system test and the preparation of the



spacecraft for launch. By contrast with the earlier satellite, X3 features modular electronics systems built to conform with ESRO standards which are suitable for use in a wider range of satellites.

Marconi has also been heavily involved in the UK4 and UK5 satellites. The later satellite is packed with electronic equipment and offers two important advances to the experimenters taking part in the joint NASA/Science Research Council project. Firstly it will be possible to adjust the direction of the spin axis of the spacecraft using a propane attitude control system so that experimenters can scan space for objects of potential interest and then point a second set of experiments along the spin axis at selected sources. Secondly, through the use of the spacecraft's magnetic core stores, it will be possible to collect data around an orbit and to replay this upon command in a format most convenient for the experimenters.

CONSTRUCTION

The Skynet II satellite is to be built in the form of a cylindrical drum, with solar cells covering the entire curved surface to provide the power for all of the electronics. It will measure approximately 78 inches long with a diameter of 75 inches. Launch weight will be about 960 pounds.

An apogee motor contained in the satellite itself, and mounted along the major axis of the cylinder, will be used to transfer Skynet II into its synchronous orbit. It will be spin-stabilised at about 90 revolutions per minute from the time the second stage burning ceases and once placed in synchronous orbit by the solid fuel apogee motor, the communications antenna will be de-spun and controlled to point continuously at the earth.

Attitude control will be achieved by means of hydrazine jets which will be used to adjust the attitude of the satellite, both before the apogee

motor burn, and subsequently for the life of the satellite after it has achieved the required synchronous orbit. Control movements will be provided by a single pair of jets located at the edge of the satellite and thrusting parallel to the axis of the satellite, with another pair of jets mounted in the curved surface of the satellite, and pointing radially out from the centre. These jets when fired will be pulsed to synchronise with the rotation of the satellite so as not to upset the high rate of spin which will eliminate any tendency of the satellite to rock, or even tumble and so interrupt communications traffic.

During the initial manoeuvres and the final positioning, control communications will be carried out through an omnidirectional aerial system consisting of an array of cavity-back dipoles operating at S-band. This array is mounted in a single band round the complete circumference of the satellite. Once synchronous orbit has been attained and the satellite has been turned into the correct position with respect to earth, a single horn aerial mounted on the major axis of the satellite—at the opposite end to the rocket motor—will be brought into use to provide the main communications function of the satellite. This aerial whose beam-width is just sufficient to cover the entire visible portion of the earth's surface will be mechanically de-spun and aimed directly towards the centre of the earth.

Much of the technical detail of the electronic packages onboard Skynet II is, of course, classified. Presumably the transmitter/receiver operates in the GHz band using sophisticated multiplexing techniques to cope with the wide variety of traffic it will be called to handle. Also it will have to cope with a variety of powers, since the ground stations with which it will have to work range from tiny ship and shore-based portables with 3.5-foot diameter dish shaped aerials to the large 40-foot units having outputs measured in kW.

TECHNOLOGY SATELLITE

Much more information is available on the technology satellite X3 which is in the final stages of preparation for launching shortly. The satellite has been checked in the solar chamber at RAE Farnborough and at the time of writing it is being checked for magnetic inter-reaction at the ESRO European Space Technology Centre in Holland prior to installation on to a Black Arrow launcher.

The Black Arrow 'X' series of technology satellites is aimed at improving British technology in spacecraft and launch vehicles. All of the satellite systems are designed with future requirements in mind and some of the operational data equipment is duplicated in new experimental form to be proved in space.

Marconi has designed and built the power conditioning system, the telemetry transmitters, telecommand receivers and decoders and the data conditioning systems for the satellite to the relevant NASA and ESRO standards.

Although the power requirements of X3 is only 10 watts, the power conditioning system has been designed for future spacecraft in the series and is rated to supply up to 30 watts continuously, both in sunlight and eclipse conditions. A 6 ampere-hour nickel-cadmium battery charged by the solar cell array supports the equipment during eclipse periods.

Owing to the limitations of the pulse frequency modulation data system used on previous satellites, channel capacity has been increased through the



This picture shows the assembly of a welded circuit for an r.f. module. (Skynet II).

adoption of a modular pulse code modulation data system. Besides meeting the immediate requirements of the X3 satellite, the system could be expanded easily to cope with more complex data systems of future spacecraft.

The new data handling system uses a small number of standardised logic elements, such as shift registers and multipliers, packaged in all-welded "modules" assembled to form a complete telemetry system. Essential modules are duplicated to enhance system reliability.

The telemetry, tracking and command system makes use of an r.f. package comprising 6 sub-units based on common piece parts. Again the telemetry transmitter is duplicated to increase reliability. Two receivers are used and connected in polarization diversity configuration to minimise the effects of spin modulation of the r.f. signal—induced by the rotation of the satellite.

A completely new command decoder has been developed for X3. This operates on the NASA Tone-Digital Command Standards and provides a capacity of up to 70 commands per decoder address. Two of these are fitted to the satellite. For a transmitted command to have any effect on the satellite, the r.f. carrier frequency, the tone frequency, the relative timing and lengths of the tone bursts, and the number of bits per word must all be correct and the decoder must also recognise its allocated address followed by a valid execute code within a defined time period. Reasonably secure!

TOTAL CAPABILITY

Now that a British company has won its spurs in the space race, Marconi is in an ideal position to open up satellite communications for commercial applications. Already there are suggestions that countries like Canada and several in Africa where the population is spread over wide areas could make use of communications satellites feeding small ground stations such as the SCOT terminal being built for the British Armed Forces.

By the end of the decade radio and television direct from 'stationary' satellites could become a reality. The technology is here already—it seems to be more a matter of getting the economics right.

ELECTROVALUE

EVERYTHING BRAND NEW & TO SPEC • LARGE STOCKS • NO SURPLUS

BARGAINS IN NEW SEMICONDUCTORS all power types supplied with free insulating sets MANY ITEMS AT NEW REDUCED PRICES

1N914	5p	2N2905A	47p	40361	55p	BC148	9p	BFX87	39p
1N4148	5p	2N2924	20p	40362	55p	BC149	10p	BFX88	26p
2N696	20p	2N2925	22p	AC107	46p	BC153	19p	BFY50	23p
2N697	22p	2N2926	11p	AC126	20p	BC154	20p	BFY51	20p
2N706	12p	2N3063	27p	AC127	20p	BC157	12p	BFY52	23p
2N930	29p	2N3065	65p	AC128	20p	BC158	11p	B8X20	16p
2N1131	36p	2N3702	13p	AC153K	22p	BC159	12p	CA07	17p
2N1132	40p	2N3703	13p	AC176	16p	BC167	11p	MC140	25p
2N1302	19p	2N3704	13p	ACY20	20p	BC168	10p	MPS6531	35p
2N1303	19p	2N3705	13p	ACY22	16p	BC169	11p	MPS6534	30p
2N1304	23p	2N3706	13p	AD140	56p	BC177	14p	NKT211	25p
2N1305	33p	2N3707	13p	AD142	50p	BC178	13p	NKT212	25p
2N1306	33p	2N3708	13p	AD149	60p	BC179	14p	NKT214	23p
2N1307	36p	2N3709	13p	AD161	23p	BC182L	16p	NKT274	19p
2N1308	36p	2N3710	13p	AD162	36p	BC183L	10p	NKT403	65p
2N1309	36p	2N3711	13p	AF114	30p	BC184L	11p	NKT405	79p
2N1313	23p	2N3714	15p	AF115	30p	BC212L	16p	OC71	28p
2N1711	26p	2N3819	35p	AF117	28p	BC213L	16p	OC81	25p
2N1893	54p	2N3906	35p	AF124	30p	BC214L	16p	OC83	20p
2N2147	95p	2N4058	13p	AF127	28p	BCY70	19p	ZTX300	17p
2N2218	34p	2N4059	10p	AF139	33p	BCY71	33p	ZTX301	17p
2N2218A	43p	2N4060	11p	AF236	38p	BCY72	15p	ZTX302	22p
2N2219	38p	2N4061	11p	AS Y26	27p	BF115	23p	ZTX303	22p
2N2219A	53p	2N4062	12p	AS Y28	27p	BF167	18p	ZTX304	27p
2N2270	62p	2N4124	18p	BC107	12p	BF173	19p	ZTX500	18p
2N2369A	19p	2N4126	87p	BC108	11p	BF194	14p	ZTX501	21p
2N2483	35p	2N4294	15p	BC109	12p	BF195	15p	ZTX502	25p
2N2484	42p	2N4286	15p	BC125	15p	BFX29	31p	ZTX503	22p
2N2646	64p	2N4289	15p	BC126	25p	BFX84	25p	ZTX504	22p
2N2904A	42p	2N4291	15p	BC147	10p	BFX85	34p	ZTX530	27p
2N2905	44p	2N4292	15p						

Appointed distributors for
SIEMENS (U.K.) LTD.

Appointed stockists for
NEWMARKET TRANSISTORS
RADIOHM POTENTIOMETERS

NEW! NEW! NEW! SIEMENS TTL INTEGRATED CIRCUITS

Full range of these important devices in stock for the experimenter and worker on Transistor-Transistor Logic ICs. Send S.A.E. for Electrovalue List

SIEMENS POLYCARBONATE CAPACITORS

250V up to 0.1mF: 100V 0.1 mF and above	
0-01, 0-012, 0-015, 0-018, 0-022, 0-027	5p
0-033, 0-029, 0-047, 0-056, 0-068, 0-082, 0-1, 0-12, 0-15, 0-18, 0-22	6p
0-27	7p
0-33	8p

30 WATT BAILEY AMP. PARTS RESISTORS

Transistors and PCB for one channel 30-46
Capacitors and resistors 28-41 per channel

INTEGRATED CIRCUITS

PLESSEY SL408A Now only 42-10 nett 3W into 7-5 Ω for 18V supply. Application data sent 10p.

S-DeCs puts an end to birds nesting

Components still plug in—saves time—allows re-use of components. S-Dec (70 points), £1.00
Complete T-Dec, may be temperature-cycled (208 points) £2.50 Also µ-Decs and IC carriers.

NEON INDICATOR LAMPS

Chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C, 24p. Neon, square red type LS5C/R, 18p; amber type LS5C/A, 18p; clear type LS5C/C, 18p. All above are for 240v. mains operation. Filament types: 6v, 0.04A square red type LS5C/R-6v, 30p; 6v, 0.04A amber type LS5C/A-6v, 30p; 6v, 0.04A clear type, LS5C/C-6v, 30p; 6v, 0.04A green type LS5C/G-6v, 30p; 12v, 0.04A LS5C/R-12v, 34p; 28v, 0.04A LS5C/R-28v, 45p.

DIN CONNECTORS

Loudspeaker	2-pole	12p	10p
Audio	3-pole	13p	10p
Audio	4-pole	14p	12p
Audio	5-pole 180deg.	15p	12p
Audio	5-pole 240deg.	15p	12p
Audio	6-pole	15p	13p

CORED SOLDER—60/40 alloy, 20 s.w.g. 8oz. reel, 65p. 1lb. reel £1.20.

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

SAVE £6.25 ON THE NEWEST PEAK SOUND AMPLIFIER

Englefield 840 with 20+20 watts RMS output into 8 Ω speaker, plus unique add-in facility for stereo tuner unit and superbly styled cabinet (black, green, red or blue simulated soft leather covering to choice) as advertised at £45 available from Electrovalue brand new & guaranteed 338.75.

£38.75

RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω-320K Ω	E12	9	8	7
C	1/8W	5%	4.7 Ω-470K Ω	E24	1	0-8	0-7
C	1/4W	10%	4.7 Ω-10M Ω	E24	1-2	1	0-7
C	1/2W	5%	4.7 Ω-10M Ω	E12	2-5	2	1-8
C	1W	10%	10 Ω-1M Ω	E24	4	3-5	3
MO	1/2W	2%	10 Ω-1M Ω	E12	7	7	6
WW	1W	10% ± 1/20 Ω	0-22 Ω-39 Ω	E12	7	7	6
WW	3W	5%	12 Ω-10K Ω	E12	7	7	6
WW	7W	5%	12 Ω-10K Ω	E12	9	9	8

Codes: C = carbon film high stability low noise
MO = metal oxide Electroval TR5 ultra low noise
WW = wire wound Plessey.

Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 81 and their decades.

ZENER DIODES

5% full range E24 values; 400mW: 2-7V to 30V 15p each
1W: 6-5V to 82V 27p each 1.5W: 4-7V to 75V 60p each
Clip to increase 1-5W rating to 3 watts (type 266F) 4p.

CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.
Single gang linear 220 Ω to 2.2M Ω 12p
Single gang log 4.7K Ω to 2.2M Ω 42p
Dual gang linear 4.7K Ω to 2.2M Ω 42p
Dual gang log 4.7K Ω to 2.2M Ω 42p
Log/antilog 10K, 47K, 1M Ω only 42p
Any type with 1A D.P. mains switch, extra 12p
Please note: only decades of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω, 470 Ω, 1K, 2K, 4K, 7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10M Ω Vertical or horizontal mounting 5p each.

ENAMELLED COPPER WIRE even No S.W.G. only.
20z reels 16.23 S.W.G. 25p; 24-30 S.W.G. 30p; 32-34 S.W.G. 33p; 36-40 S.W.G. 35p; 40z reels 16-22 S.W.G. only 41p.

MULLARD polyester C280 series

250V 20% 0-01: 0-022: 0-033, 0-047 3p ea. 0-068: 0-1, 0-15 4p, 0-22 5p, 10%: 0-33 7p, 0-47 8p, 0-68 11p, 1μF 14p, 1.5μF 21p, 2.2μF 24p.

MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 6p each
Values (μF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/64; 8/40; 8/25; 8/40; 10/25; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/64; 25/25; 32/40; 32/10; 32/40; 32/64; 40/16; 40/25; 50/64; 50/25; 50/40; 64/4; 64/10; 80/25; 80/16; 80/25; 100/64; 125/4; 125/10; 125/16; 160/25; 200/64; 200/10; 250/4; 320/25; 320/64; 400/4; 500/25.

LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 41p; 1000/100 52p; 2000/25 37p; 2000/50 57p; 2000/100 11.44; 2500/64 77p; 2500/70 82p; 5000/25 62p; 5000/50 11.10; 5000/100 22.21; 10000/50 22.40.

COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2. Overseas orders welcome: carriage and insurance charged at cost. Send S.A.E. for latest list. Prices subject to alteration without notice.

ELECTROVALUE

(Dept. PW.871) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) T. ex 264475

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

THE onset of fine, summery weather has caused the usual drop in the number of reports as DXer's leave their shacks for the great outdoors. Among the stalwarts who remained in their shacks was **John Trewick** of London Colney who used his Lafayette HE-40 and vertical whip to hear the following:—

- 9525 *RSA, South Africa* in English at 2020.
- 11820 *BBC, Ascension*, 'The Music Scene' at 2015.
- 15018 *Hanoi, Vietnam* with 'Letterbox' at 2000.
- 15170 *ELWA, Liberia* in French at 2030.
- 15185 *Helsinki, Finland* in English at 1800.
- 15195 *Ankara, Turkey* in German at 2100.
- 15265 *Kabul, Afghanistan* in English at 1800.
- 17730 *Havana, Cuba* with news in English at 2010.
- 21535 *NHK, Japan* with 'DX Corner' at 0800.
- 21535 *RSA, South Africa* with Folk Songs at 1120.

Howard Stephenson of Newcastle-upon-Tyne has used his Eddystone EC10, Mk. II receiver and Joystick antenna to hear some interesting stations including:—

- 3260 *R. Niamey, Niger*, African music at 2015.
- 3905 *All India Radio* in English at 2245.
- 3915 *BBC, Tebrau, Malaysia* relay at 2215.
- 4680 *HCWE1, R. Nac. Espejo, Ecuador* with Latin-American music at 0545.
- 4680 *HCWE1, R. Nac. Espejo, Ecuador* with Latin-
- 15395 *VOA, Tinang, Philippines* at 2200.

Ray Warren of Bury St. Edmunds has used his Astrad Auriga receiver and a Koyo 1661 receiver to hear the following:—

- 6195 *Tunis, Tunisia* in French at 0840.
- 6540 *Pyongyang, N. Korea* in English, 1900.
- 9489 *Radio Tirana, Albania*, English, 1830.
- 9570 *R. Nacional, Spain* in Spanish at 1540.
- 15180 *Radio Australia*, pop music at 0800.
- 15460 *Radio Kuwait*, news in English at 1830.

R. J. Downes of Bournemouth does not mention what equipment he uses but he heard:—

- 6010 *R.T. Belgium* in Dutch at 1430.
- 11710 *RAE, Argentina* in English from 2300 to 2400.
- 11965 *Trans Europe Radio* in English, 1345.
- 15160 *Ankara, Turkey* in English from 2200.
- 15185 *Nigeria B.C.* noted in English at 0715.

Derek J. Hart of Lancaster sent in the following list of stations which he has heard recently:—

- 6080 *Radio Berlin International* at 2037.
- 9505 *Radio Tirana, Albania* news at 2035.
- 9625 *Israel B.C.*, news at 2056.
- 9915 *All India Radio*, news at 2056.
- 11672 *Radio Pakistan*, news at 2045.
- 15125 *Radio Australia* to Pacific at 0830.

Nigel Williams of Caewern, Neath, Glamorgan, has a Lafayette receiver and a Joystick antenna with which he heard:—

- 4990 *Radio Kiev, Ukraine*, DX programme at 1945.
- 5015 *Windward Islands B.S.* to Europe at 2345.

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

- 6130 *Radio Tirana, Albania* in English at 2130.
- 7306 *Polish Pathfinders* in English at 1700.
- 15230 *BBC, Ascension* relay at 1710.
- 15250 *RSA, South Africa* at 1750.
- 21460 *HCJB, Quito, Ecuador*, DX programme at 1945.
- 21595 *Radio Canada International* at 1850.

C. Gibbs gives no indication of the equipment used but he managed to hear the following at his shack in Camberley:—

- 6020 *Radio Nederland* in English at 1515.
- 6025 *Radio Portugal* at 2125.
- 6025 *Radio Budapest, Hungary* in English at 2130.
- 7145 *Radio Warsaw, Poland* in English at 1600.
- 9535 *SBC, Berne, Switzerland* at 1115.
- 9730 *Radio Berlin International* from 1515.
- 9735 *NHK, Japan* in Japanese at 2012.
- 15325 *Radio Canada* in French at 2045.

A new reporter from Hesse in East Yorkshire is **Ian Jarvis** who owns a Lafayette HA-700 receiver and a 50 foot long aerial which enabled him to hear:—

- 7210 *The International Radio Service of the Red Cross* from Switzerland at 1200.
- 7290 *Trans World Radio, Monaco* at 1645.
- 9770 *Austrian Radio*, English for Europe at 2045.
- 11672 *Radio Pakistan* in English at 2015.
- 15130 *Radio Australia* in English at 0815.
- 15240 *Radio Sweden* in English at 2245.

The article in the May issue has prompted a number of queries as to which is the best receiver for the Broadcast Bands DXer. This is a very difficult question to answer but my general advice is to pick one of the following ex-military sets: CR100, AR88, R1155 or an HRO. If you prefer a new receiver the following two sets are good value for money: Lafayette HA-600 or Trio 9R59DE. Both these receivers retail at about £45, much better sets can be purchased if the money is available of course.

KJ Catalogue

KJ Enterprises announce their latest Leisure-sound Mail Order catalogue. There are 128 pages, containing stereo systems, record players of every variety, tape and cassette recorders, amplifiers, speakers, turntables, microphones, p.a. equipment, all types of recording tape, cassettes, books 8-track cartridge players, car radios, countless hundreds of accessories of every kind, radios, specialist furniture lines etc. As usual the majority of items are available at substantial discounts and where possible recommended retail prices are listed for direct comparison with KJ. Although this catalogue is automatically distributed to existing KJ customers it is available *FREE* on request, to anyone interested. *KJ Enterprises, 33 Bridle Path, Watford, Herts.*

YOUR chance this month to get a special QSL card. The Irish Radio Transmitters Society are off on a DX-pedition to Dalkey Island which is, according to the map, a small island off the coast of the Republic of Ireland (see if you can find it). Operating dates are 1200 on July 31 to 1200 on August 2. Operation will be A1 and A3a on all bands from 3.5 to 30MHz. **Sean Nolan**, EI7CD, says that the call sign to listen for is EI0DI and the station will QSL all contacts. Station will be operating from petrol generators, according to Sean, so if you intend to have a QSO—don't smoke.

D. Palmer (Glasgow), tells that ZS1MH has been heard operating a DX net several evenings on forty and is rumoured to be in on a similar net on eighty. Another one on forty is LU7ACC who, with the ZS, has been logged around 2145hrs. Aerial at the Glasgow location is described as a V-beam with arms approximately 170° which almost merits a dipole rating. Feeding the output to a balanced a.t.u. gives a significant improvement in signal to noise ratio. Receiver is a modified 19 set with a crystal filter which bagged: CP6EL, CT2AK, CX1AA, CX1BBR, JW7UH, LU8AJG, PY2ELZ, PY4BSZ, PY5OF, PY6JM, PY7BBD, VP2MM, ZS1JA all on 7MHz s.s.b.

S. Chuck (Harrogate), comments that stations have been dying out rather earlier on 14MHz and says that 80 has been very good of late. Surprisingly though, his log is for 7MHY from which his best were HI3PY and JA6SM.

"The a.t.u. has been made from a cannibalised crystal set", says **Stefan Kaye** (Witney). Further admissions include a confession to using an AR88 to log these on 80; EA6BN, F6ABP/M, JY9WB, KV4FS, PY7BFN, PY0AD, VO1BT, ZC4IK, ZD7SD, ZS1MH, 4X4NJ, 6W8DY, 9G1DY.

S. Elsdon (Halesowen) warns, "You can be sure of hearing from me again soon", and promptly describes the gear as a CR-70A. Samuel also has a 240ft. long wire bent in the middle (nasty) and managed VK3IQ and VK3LR on 3.5MHz.

John Moore (Leicester) says he's come to the conclusion that people who don't tune the low ends of bands are missing about one-third of the DX. Non-c.w. types please note. John also reminds that Italian prefixes are allocated according to area and range from I1 to I0. This might not be a bad idea for G stations and would make life on two metres and up a whole lot easier.

John's log shows GM3SVK/A back on from the Shetlands on topband together with OK1FJS. Twenty metres s.s.b. showed: EA8GZ, ET3DS, JA3IXL, JW5NM, LU8DB, PY1CCC, PY2ZAD, PZ1DF, TA3HC, UK9AAQ, VE8RX, VK3ATN, VK6KK, VO1CM, YB3AAAY, YB0AAG, 9HI1CD, 9Q5BV. Ten metres raised: JA1ZTC, LU9FAN, PY2EWF, UK9HAD, VE2ASZ, VE3BKA, VE3FIQ, W3DQD/YVI.

G. Kent (St. Leonards-on-Sea) uses a B40 receiver and the aerial is "a strand of Woolworth's wire", (sounds a bit of a thin story to me). Although only

some 15ft. long (the aerial not G. Kent) the following were heard on 14MHz: CT1SG, JA4HM, JH1OTO, JM2HCA, K2OUS, VE3GMT, VE6MC, VK2WC, VK4DY, VK5ED, VK5NB, ZL4BX, ZP2KN, 4X4VB.

Someone's got a favourite band. Don't worry, your address at Satinforth Road, Ilford, Essex, is safe with me. I know you didn't sign the letter and just for that I won't tell anyone that you heard: CR4AJ, CR6EM, CR7FM, CT2AK, DU6MG, EA6AS, EA9AA, EL7TL, EP2BQ, ET3USA, FC8APT, G3DJK/P/W1, HC1HV, HR3VFJ, IS1PZR, JA1QJE, JA7JLB, JH1JLR, K7ZTM, KC4USP, KG4CS, KP4DCR, LU1CBR, LX1HD, MP4BEU, MP4BJE, OX3DL, PY2BDY, PY8ZZA, SV1AE, SV0WDD, SZ0SU/P, TI3E, TJ1DA, VQ9RK, VU2HLU, VU2REG, VS9MB, VS9MT, W3UBM/MM/1, WA4MOC/P/8R1, WA6DBP/P/4X4, W6DLE/4X4, W6VLH, W9LGV, YU2REE/MM (off coast of Cameroons), ZC4CB, ZD9BN, ZL1HA, ZS6ES, ZS6ON, 3B8CZ, 4U1ITU, 4X4IX, 4Z4GV, 4Z4HF, 5H3JR, 5N2AAF, 5N2ABG, 5Z4DV, 6W8BD, 7X2OM, 7X2SX, 8P6AJ, 9E3USA, 9H1R, 9H1V, 9M2BQ, 9N1MM, 9V1PX, 9X5WJ, all on 21MHz and probably s.s.b. too.

J. Iredale (Llandudno) expresses great delights at his newly-installed JR-500SE receiver (JDG's going all green again). A preliminary peep on 14MHz revealed: HK3CFM, LU2DEK, LX1BA, MP4BFO (resolves his own sideband?), SV0WW, WA6AUE, 4X4DK, 4Z4HF, 5X5NA.

A Hallicrafters S120 and a 66ft. end-fed located at Ilford allowed **Mark Marsden** to bag these on 20 s.s.b.: JA20XF, JA7GY, HP9AVQ/MM, KX6DQ, TA6JB, TR8MC, VE6ARC, VK3CR, VK2AB, W3GLY/V56, ZS5DJ, 4Z4HF.

Come into my antenna says **C. Henderson** whose aerial does bear a remarkable resemblance to a spider's web. Receiver is a B40 and the other antenna is a 120ft. long wire. Goodies on fifteen include: CR4BC, CR71C, HB9TE, HI8FED, KV4AD, OD5AO, PY2AAA, PY5EG, SUIBN, VE3BMB, VS9MT, XW8BP, YA2GNT, YV4YC, YV5BNR, ZC4MU, 4U1ITU, 4X4CW, 5N2AAJ, 9Q5RH, 9Y4RB. Crispin says that 20 metres has been excellent at round 0100hrs.

S. Wainwright (St. Helen's), 9R-59DE, PR30, 70ft. inverted L at 28ft., all s.s.b. on 14MHz: FG7TD, FM7AA, FM7WW, HZ1TA, JR6JU, KS6CY, PJ8DZ, VR6TC, WA8FPN/P/KS6, ZF1GC.

Happenings for July include: 3-4, topband contest; 3-4, two metre contest; 3-4, two metre listeners contest; 10-11, Field Day; 11, Worcester Mobile Rally, Upton-on-Severn; 18, 70cms open contest; 18, 70cms listeners contest; 10-25 listen for G3EKW/A at the Nottingham Festival '71. August 7-8, WAE c.w. contest.

Logs, in alphabetical order please, to arrive by the 15th of the month to:

12 Gross Way, Harpenden, Herts.

THE MW COLUMN

OVERCROWDING on the medium waves has encouraged DXers to develop the MW loop aerial. This type of indoor antenna is both tunable and directional. Maximum pick-up is along the plane of the windings and there are two nulls—directions of little or no pick-up—opposite each other at right angles to the windings. These nulls enable DXers to reduce or eliminate interference simply by rotating the loop on its vertical axis so that stations such as Malaga 1007kHz can be heard with the null on Hilversum or Buenos Aires on 1070kHz with the null on CBA Moncton N.B. in Canada. Since a loop is an indoor aerial it can be used in locations where it would be impossible to erect an outdoor one. The writer invariably uses a loop in preference to a 90ft longwire as the overall performance is nearly always better.

R. Garwood of Bournemouth has asked for constructional details. The standard MW loop consists of 7 turns of plastic covered hookup wire wound in the shape of a square of 40in. side together with a one-turn coupling winding wound parallel and central to the main winding. The windings are supported on a frame made out of two pieces of 1 inch square wood joined at right angles at the centre to form an X. The turns are kept apart by means of four paxolin spacers which have saw cuts $\frac{1}{4}$ in. apart along one edge to retain the windings. The spacers are fixed to the ends of the arms. The main winding terminates on a 500pF variable capacitor mounted at the centre of the loop. This is the tuning control. The single coupling winding ends at a small terminal block from which a 5ft. length of twin feeder (plastic covered lighting flex will do) connects to the receiver dipole input or to the aerial and earth terminals. The loop is fixed to a stand so that it can be rotated on its vertical axis.

To use the loop, tune in a station on the receiver, peak-up the signal with the loop tuning control and rotate the loop for optimum reception. As well as reducing co-channel interference, a loop will usually have a better signal-to-noise ratio than a longwire and it will often reduce cross-modulation, splash and occasionally static. **Ray Eaton**, a retired reader who lives in Brighton has been experimenting with loop aerials on frequencies up to 4MHz and reports some success.

South Americans are at their best in summer so now is the time to look for the rarer countries. Between 0100hrs GMT and sunrise listen for Radio Cruz del Sur on 1380 and Radio Minería 1060kHz; both are 7,000 miles away in Chile. OAX4U 1010kHz Radio America is in Lima, Peru. It is normally a strong signal and has been logged already this year by a DXer in Norfolk. ZP4 1330kHz Radio Chaco in Paraguay and CP57 Radio Progreso 1090kHz in La Paz, Bolivia were heard last year while CP4 1020kHz also in La Paz is another recent catch from this difficult DX country. Conditions are at their best during the hour before dawn and the band is often alive with Latin Americans at this time.

CHARLES MOLLOY



IT'S those integrated circuits again. Different types appear on the professional market almost daily. A fairly recent one is of great interest since it could well affect a whole industry. This 16-pin dual in-line beast is called the TBA 631 and hidden within the confines of its diminutive carcass is a limiting amplifier, an f.m. coincidence detector, low frequency separator, low frequency preamplifier and self-balancing circuit, driver and audio amplifier. It's immediate application is in television receivers and the trend is that the average black and white receiver will be reduced to five integrated circuits (which should make the do-it-yourself t.v. builder jump for joy). Colour sets will need another two i.c.s.

There is more to it than merely simplifying construction, although from the manufacturing point of view this is extremely important. Servicing becomes an important aspect of many things, especially television receivers. If this trend of reducing a black and white set to five i.c.s continues, then the servicing aspect becomes a comparatively simple matter, since the would-be service man has, at worst, only to work his way round the set simply substituting "good" i.c.s. for each one in the set until the fault is cleared. This in turn implies that initial servicing in the home could be performed by an unskilled person.

It is not possible to fault the idea in terms of initial cost either, since the TAB 631 markets for around £2.80 for quantities of 1 to 24. Again, the chip in question will supply 3 watts into a 16Ω speaker for 10 per cent distortion with a 24V line. Limiting sensitivity of the unit is less than 100μV at 6MHz for the quoted output. The output stage is class B and is capacitively-coupled to the speaker. The r.f. amplification, demodulation and output separator section has its own power supply terminations and will work at voltages from 4.5V to 15V. The quiescent current at 12V is typically 18mA and the frequency range of the r.f. stage is between 5kHz and 60MHz. Over 60dB of gain is available from the limiting amplifier alone, while a.m. rejection is given as better than 45dB. A few resistors and capacitors plus tuned circuits are all that are needed to get this chip perking happily.

While the cathode ray tube and power supply are still required and have not, as yet, been reduced to a chip, experiments in solid state readout devices look promising although many companies have these behind locked doors. With advances like this, the wristwatch television doesn't seem quite such a ludicrous idea after all.

STEPHENS

ELECTRONICS,
P.O. BOX 26,
AYLESBURY, BUCKS.

SEND S.A.E. FOR LISTS
GUARANTEE
Satisfaction or money
refunded.

GUARANTEED VALVES BY THE LEADING MANUFACTURERS BY RETURN SERVICE 1 YEAR'S GUARANTEE ON OWN BRAND, 3 MONTHS' ON OTHERS

AZ31 50p	ECF80/2 47p	EL803 85p	PC085 42p	PY83 50p	UL141 57p	6AR5 38p	6EJ7 35p	6SE7 32p	12BE6 32p	30PL1 77p
AZ50 60p	ECF86 55p	EL821 55p	PC088 70p	PY88 50p	UL184 55p	6AR6 32p	6EJ6 50p	6SL7GT 32p	12BH7 32p	30PL13 90p
CB131 85p	ECH42 65p	EM34 80p	PC089 61p	PY90 41p	UM80/4 45p	6AR7 35p	6F1 70p	6SN7GT 30p	12BY7 50p	30PL14 80p
CY31 85p	ECH81 61p	EM71 62p	PCF80 51p	QU02-6 42p	UY41 40p	6AS7G 30p	6F8 40p	6HQ7 40p	12K5 50p	35A3 50p
DAF91 41p	ECH84 47p	EM80 40p	PCF82 52p	QU03-10 11p	UY85 34p	6AT6 45p	6F9 40p	6K7 37p	12K7GT 35p	35A5 50p
DAF96 41p	ECH84 47p	EM81 42p	PCF84 47p	UV35 11p	UY85 34p	6AT6 45p	6F11 32p	6K7 37p	12L7GT 25p	35B5 35p
DF91 45p	ECL80 40p	EM84 37p	PCF86 61p	QV03-12 65p	UY91 72p	6AU6 30p	6F12 22p	6U4GT 62p	12SG7 25p	35C5 35p
DF96 40p	ECL82 49p	EM87 55p	PCF200/1 81p	R18 65p	UY93 41p	6BE6 60p	6F14 60p	6V6GT 32p	12SH7 25p	35L6GT 47p
DK91 57p	ECL85 57p	EN91 36p	PCF89 61p	R20 75p	UY91 41p	6BE6 60p	6F15 55p	6X4 25p	12SH7 25p	35W4 25p
DK96 57p	ECL86 45p	EN91 36p	PCF89 61p	SU2150A 75p	W99 55p	6BE6 60p	6F16 55p	6X4 25p	12SL7GT 40p	35Z3 25p
DL92 37p	ECLL800 45p	EY80 45p	PCF805 85p	T21 22p	Z759 11p	6B7A 50p	6F18 40p	6X8 35p	12SL7GT 40p	35Z4G 25p
DL94 37p	EY81 45p	EY81 45p	PCF806 61p	TT22 22p	Z759 11p	6B7A 50p	6F18 40p	6Y8G 60p	12SN7GT 40p	35Z5GT 37p
DL96 37p	EY82 45p	EY82 45p	PCF807 61p	U18/20 67p	U20 67p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50A5 65p
DM70 32p	EF80 40p	EY86 40p	PCH200 70p	U20 67p	U20 67p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50B5 35p
DY86/7 40p	EF83 50p	EY87 42p	PCL92 51p	U26 75p	U26 75p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50C5 35p
DY80/2 42p	EF84 50p	EY88 42p	PCL93 61p	U26 75p	U26 75p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50D5 35p
ES51 22p	EF86 41p	EZ55 45p	PCL94 51p	U31 45p	U31 45p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50E5 35p
ES8CC 40p	EF89 40p	EZ40 45p	PCL95 52p	U37 11p	U37 11p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50F5 35p
EL30L 24.50p	EF91 42p	EZ41 45p	PCL96 51p	U50 30p	U50 30p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50G5 35p
EL30F 95p	EF92 50p	EZ20 27p	PCD50 11.52p	U52 30p	U52 30p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50H5 35p
EA0C80 52p	EF93 47p	EZ31 27p	PFL200 74p	U76 25p	U76 25p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50I5 35p
EA0F42 50p	EF94 77p	EZ30 25p	P36 64p	U78 25p	U78 25p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50J5 35p
EA0C83 52p	EF95 62p	EY90 25p	PCF89 61p	U91 25p	U91 25p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50K5 35p
EA0C84 47p	EF183 55p	GY501 80p	PL81 40p	U201 32p	U201 32p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50L5 35p
EA0C85 32p	EF184 35p	GZ30 37p	PL81A 62p	U281 40p	U281 40p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50M5 35p
EA0C86 47p	EF280F 22.10p	GZ31 30p	PL82 36p	U282 40p	U282 40p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50N5 35p
EA0C87 40p	EF800 21.00p	GZ32 37p	PL83 51p	U301 57p	U301 57p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50O5 35p
EA0C88 40p	EF804 21.00p	GZ33 40p	PL84 41p	U493 50p	U493 50p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50P5 35p
EA0C89 40p	EF811 70p	GZ34 35p	PL85 60p	U404 37p	U404 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50Q5 35p
EA0C90 22p	EF84 52p	PA0C80 25.40p	PL86 32p	U405 37p	U405 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50R5 35p
EA0C91 40p	EL86 42p	PC86/80 40p	PL87 41p	U406 37p	U406 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50S5 35p
EA0C92 40p	EL89 32p	PC95 38p	PL88 41p	U407 37p	U407 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50T5 35p
EA0C93 40p	EL90 32p	PC95 38p	PL89 41p	U408 37p	U408 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50U5 35p
EA0C94 40p	EL91 25p	PC97 41p	PL90 41p	U409 37p	U409 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50V5 35p
EA0C95 40p	EL95 35p	PC97 41p	PL91 41p	U410 37p	U410 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50W5 35p
EA0C96 40p	EL96 35p	PC97 41p	PL92 41p	U411 37p	U411 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50X5 35p
EA0C97 40p	EL97 35p	PC97 41p	PL93 41p	U412 37p	U412 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50Y5 35p
EA0C98 40p	EL98 35p	PC97 41p	PL94 41p	U413 37p	U413 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50Z5 35p
EA0C99 40p	EL99 35p	PC97 41p	PL95 41p	U414 37p	U414 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50A5 35p
EA0C100 40p	EL100 35p	PC97 41p	PL96 41p	U415 37p	U415 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50B5 35p
EA0C101 40p	EL101 35p	PC97 41p	PL97 41p	U416 37p	U416 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50C5 35p
EA0C102 40p	EL102 35p	PC97 41p	PL98 41p	U417 37p	U417 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50D5 35p
EA0C103 40p	EL103 35p	PC97 41p	PL99 41p	U418 37p	U418 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50E5 35p
EA0C104 40p	EL104 35p	PC97 41p	PL100 41p	U419 37p	U419 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50F5 35p
EA0C105 40p	EL105 35p	PC97 41p	PL101 41p	U420 37p	U420 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50G5 35p
EA0C106 40p	EL106 35p	PC97 41p	PL102 41p	U421 37p	U421 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50H5 35p
EA0C107 40p	EL107 35p	PC97 41p	PL103 41p	U422 37p	U422 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50I5 35p
EA0C108 40p	EL108 35p	PC97 41p	PL104 41p	U423 37p	U423 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50J5 35p
EA0C109 40p	EL109 35p	PC97 41p	PL105 41p	U424 37p	U424 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50K5 35p
EA0C110 40p	EL110 35p	PC97 41p	PL106 41p	U425 37p	U425 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50L5 35p
EA0C111 40p	EL111 35p	PC97 41p	PL107 41p	U426 37p	U426 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50M5 35p
EA0C112 40p	EL112 35p	PC97 41p	PL108 41p	U427 37p	U427 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50N5 35p
EA0C113 40p	EL113 35p	PC97 41p	PL109 41p	U428 37p	U428 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50O5 35p
EA0C114 40p	EL114 35p	PC97 41p	PL110 41p	U429 37p	U429 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50P5 35p
EA0C115 40p	EL115 35p	PC97 41p	PL111 41p	U430 37p	U430 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50Q5 35p
EA0C116 40p	EL116 35p	PC97 41p	PL112 41p	U431 37p	U431 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50R5 35p
EA0C117 40p	EL117 35p	PC97 41p	PL113 41p	U432 37p	U432 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50S5 35p
EA0C118 40p	EL118 35p	PC97 41p	PL114 41p	U433 37p	U433 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50T5 35p
EA0C119 40p	EL119 35p	PC97 41p	PL115 41p	U434 37p	U434 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50U5 35p
EA0C120 40p	EL120 35p	PC97 41p	PL116 41p	U435 37p	U435 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50V5 35p
EA0C121 40p	EL121 35p	PC97 41p	PL117 41p	U436 37p	U436 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50W5 35p
EA0C122 40p	EL122 35p	PC97 41p	PL118 41p	U437 37p	U437 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50X5 35p
EA0C123 40p	EL123 35p	PC97 41p	PL119 41p	U438 37p	U438 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50Y5 35p
EA0C124 40p	EL124 35p	PC97 41p	PL120 41p	U439 37p	U439 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50Z5 35p
EA0C125 40p	EL125 35p	PC97 41p	PL121 41p	U440 37p	U440 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50A5 35p
EA0C126 40p	EL126 35p	PC97 41p	PL122 41p	U441 37p	U441 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50B5 35p
EA0C127 40p	EL127 35p	PC97 41p	PL123 41p	U442 37p	U442 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50C5 35p
EA0C128 40p	EL128 35p	PC97 41p	PL124 41p	U443 37p	U443 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50D5 35p
EA0C129 40p	EL129 35p	PC97 41p	PL125 41p	U444 37p	U444 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50E5 35p
EA0C130 40p	EL130 35p	PC97 41p	PL126 41p	U445 37p	U445 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50F5 35p
EA0C131 40p	EL131 35p	PC97 41p	PL127 41p	U446 37p	U446 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50G5 35p
EA0C132 40p	EL132 35p	PC97 41p	PL128 41p	U447 37p	U447 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50H5 35p
EA0C133 40p	EL133 35p	PC97 41p	PL129 41p	U448 37p	U448 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50I5 35p
EA0C134 40p	EL134 35p	PC97 41p	PL130 41p	U449 37p	U449 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50J5 35p
EA0C135 40p	EL135 35p	PC97 41p	PL131 41p	U450 37p	U450 37p	6B7A 50p	6F18 40p	6Y8G 60p	12SR7 32p	50K5 35p
EA0C136 40p	EL136 35p	PC97 41p	PL132 41p	U451 37p	U451 37p					

WICKS FOR BARGAINS

E.A. STEREO AMPLIFIER:
5 watts per channel; In attractive afrommosia veneered sleeve. Controls: On-off volume: Bass: Treble: Balance: Selector: Headphone Jack. Ceramic or Magnetic PU. Radio and Tape Inputs: Tape output and speaker output. Fully guaranteed 12 months parts. 6 months free service. Size 14½"W x 9½"D x 45"H approx. £16.50 inc. post.

3 WAY SPEAKER SYSTEM:
8" twin cone Bass speaker and 3" tweeter, fitted in extremely elegant teak veneered cabinet. Size: 18½"H x 11½"W x 10"D. 8 ohms handle 10 watts. £7.50 inc. Carr.

GARRARD OFFERS
Garrard SP25 Mk III (Rec. Price (£16.44) **Our Price £11.25.** Carr. & Ins. 50p.
Garrard SP25 Mk III ready wired in beautiful teak plinth with tinted perspex cover. (Fitted with 5-pin DIN plug or phono plugs—state choice) (Rec. Price £23.79) **Our Price £16.** Carr. & Ins. 75p.
Or with choice of fitted cartridges.
SP25 Mk III/Sonotone 9TAHC (Rec. Price £27.89) **Our Price £18.** Carr. & Ins. 75p.
SP25 Mk III/Shure M3DM (Rec. Price £31.62) **Our Price £20.** Carr. & Ins. 75p.
SP25 Mk III/Goldring G800 (Rec. Price £36.79) **Our Price £21.** Carr. & Ins. 75p.
SP25 Mk III/Shure M55E (Rec. Price £36.76) **Our Price £21.** Carr. & Ins. 75p.
Note! Garrard **SL65B** (Automatic Changer version of **SP25 Mk III**) alternatively supplied—please add £3 to above prices.
Garrard AP76 (Rec. Price £28.88) **Our Price £20.85.** Carr. & Ins. 50p.
Garrard AP76 ready wired in beautiful teak plinth with perspex cover (fitted with 5 pin DIN or Phono plugs). Please state choice. (Rec. Price £40.88) **Our Price £27.** Carr. & Ins. 75p.

OR WITH CHOICE OF FITTED CARTRIDGES.
Garrard AP76/Shure M3D (Rec. Price £48.29) **Our Price £30.55.** Carr. & Ins. 75p.
Garrard AP76/Shure M55E (Rec. Price £53.85) **Our Price £33.35.** Carr. & Ins. 75p.
Garrard AP76/Goldring G800 (Rec. Price £53.85) **Our Price £33.35.** Carr. & Ins. 75p.
Garrard 2025TC fitted with stereo/mono cartridge. £8.99. Carr. Paid.

TEAK PLINTH & PERSPEX COVER
Ready cut to take 2025TC, SP25 III, SL65B available at £4.99. Carr. & Ins. 35p.

CARTRIDGES
Sonotone 9TAHC dia. Rec. Price £4.10. **Our Price £1.99**
Shure M3DM (Rec. Price £7.41) **Our Price £4.87.**
Shure M55E (Rec. Price £12.97) **Our Price £9.50.**
Goldring 800 (Rec. Price £13.00) **Our Price £7.50.**
Goldring 800 H (Rec. Price £10.69) **Our Price £6.99.**
P & P 18p any type

D. T. WICKS & CO. 49 North Station Rd, Colchester, Essex.

- Guaranteed all brand new best quality goods. No rubbish.
- Mail order only.
- By return Post service.
- All enquiries SAE please.

Special Offer!
Grundig GDM312 Dynamic Microphones. List £7.35 **OUR PRICE £3.** P & P 30p

Service Sheets
1,000's on all makes T.V.'s, Radios, Tape Recorders, Record Players. 13p incl. post. Please state model. Cheques & open P.O.'s returned if sheets not available.

Hi-Fi Stereo Headphones
(Value £5.00) Only £2.25 inc. post.

Speaker Cloth
Best quality. Width 36". Under half price at 55p per yd. Black with gold fleck, will blend with any room setting. End of stock line, yds and yds must go.

Plugs, Sockets and Leads.

Phono plugs: 3p each 30p per dozen.
2 pin Din spkr. plugs 10p each.
3 pin Din plugs. 15p each
5 pin Din plugs. 13p each.
5 pin Din sockets (chassis) 7p each.
Stereo Jack Sockets c/cct. 13p each.
Phono sockets (chassis) 2 way 3p; 3 way 4p; 4 way 5p.
6ft. stereo lead 5 pin Din to open end. 45p
6ft. stereo lead 2 phono to open end. 37p
12ft. spkr. lead 2 pin Din to open end. 40p.
Please add P & P 5p.

100 Mixed Resistors
½ watt 10% all best quality (no ex government) 40p.

Pots
100K x 100K lins & Logs. stereo. 35p inc. post.
100K DP switch stereo. log. 45p inc. post.
50K single Balance. 15p inc. post.

4 B.A. brass nuts
50 for 25p inc. post.

Speaker cabinets
Attractively veneered in afrommosia, black front. Size approx. 7½"W x 9½"D x 4½"H. Ready cut to take 8" x 5" speaker. £1.99. P. & P. 12p.

RSGB BOOKS FOR YOU

VHF-UHF MANUAL

By G. R. Jessop, C Eng, MIERE, G6JP

2nd edition. Considerably enlarged and revised. Transmitters, receivers and test equipment for use at vhf and uhf are all fully covered on a practical basis in this new edition. **£1.80 post paid**

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. Complete coverage of the technical and constructional fields. A superb hard-bound volume. **£3.50 post paid**

AMATEUR RADIO TECHNIQUES

By Pat Hawker, G3VA

Third edition. A source of many useful circuits and aials incorporating the latest amateur techniques. Contains 208 pages and nearly 500 diagrams. **£1.13 post paid**


These are three of a complete range of technical publications, log books and maps, all obtainable from:

RADIO SOCIETY of GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE

PHOTOELECTRIC KIT

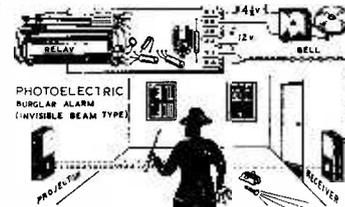CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



PHOTOELECTRIC KIT
£1.95

Postage and Pack. 15p (UK)
Commonwealth:
SURFACE MAIL 20p
AIR MAIL £1.00
Australia, New Zealand, S. Africa, Canada and U.S.A.
Also Essential Data Circuits and Plans for Building 10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT
Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price £1.00 Postage and Pack. 5p (U.K.). Commonwealth: Surface Mail 10p, Air Mail 30p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT
CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £1.50. Postage and Pack 5p (U.K.). Commonwealth: Surface Mail 15p, Air Mail 50p.

JUNIOR PHOTOELECTRIC KIT
Versatile invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.
CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price £1.00. Postage and Pack. 5p (U.K.). Commonwealth 10p; Airmail 20p.

JUNIOR OPTICAL KIT
CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.
Price 50p. Post. and Pack. 5p (U.K.). Commonwealth: Surface Mail 10p; Air Mail 20p.

YORK ELECTRICS Mail Order Dept.

335 BATTERSEA PARK RD., LONDON S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

WELL, we've only just made it this month as far as price limit is concerned but it is worth it, I hope. It is rather an unusual circuit and has not appeared before, as far as I am aware, in any form. The circuit is that of a "Touch Alarm" which does exactly what the title suggests; an alarm sounds off as soon as a metal plate is touched and stays on until the supply voltage is taken away. The metal plate can be all sorts of things, a safe, french windows, door handle, etc., etc.,. The applications and construction are left up to you but the circuit is not exactly complex and should take no more than a couple of hours to build once the components are assembled.

THE CIRCUIT

The first transistor, Tr1, is coupled in the common-collector mode (also known as the emitter-follower mode) with the base wired to the touch plate. The characteristics of this configuration are very high input impedance and low output impedance and this is the key to the operation.

The input impedance is roughly equal to the gain of the transistor times the emitter load resistor (here 6.8k Ω). The BC169C has very high gain figures, up to 900, but a more common figure would be 400. Therefore on this basis the input impedance is 400 \times 6,800 which equals nearly 3M Ω . As soon as anything touches this base it biases the transistor on and the same voltage which has been applied to the base at very high input impedance, appears at the emitter at the same voltage level but at a usable impedance.

Most of you have dabbled a damp figure at the input of an amplifier and heard the resulting sounds, made up from radio signals and hum. Here we are making the best use of these signals and putting them to use. All sorts of "muck" is picked up when the plate is touched and this appears at the emitter as an a.c. voltage. The detector diode rectifies the signals and applies them across the capacitor C1. This charges up so that a positive supply appears at the junction of D1, C1 and R2. This voltage applies a bias via the resistor to the base of Tr2 which conducts and in turn applies bias to Tr3 and a pulse passes through the primary of the output transformer. However C2 is connected in a manner which causes the second two transistors to oscillate.

The beauty about the values and configuration used here is that once the alarm oscillator has started it is self-holding. That is, the pulses through C2 themselves bias Tr2 to maintain the cycle necessary for a continually sounding alarm. So it will be seen that R2 is only necessary to start the alarm which can only be switched off by disconnecting the battery supply. C3, which decouples the supply, is not essential but with a low battery it does help the operation.

No. 28 TOUCH ALARM

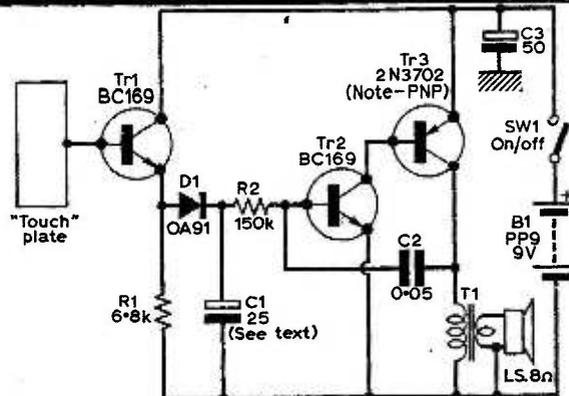


Fig. 1: The circuit of the touch alarm

★ components list

Tr1	BC169	11p†
Tr2	BC169	11p†
Tr3	2N3702	13p†
D1	OA91	5p†
R1	6.8k Ω , 10%, $\frac{1}{4}$ W	1p†
R2	150k Ω , 10%, $\frac{1}{4}$ W	1p†
C1	25 μ F, 25V Mullard	6p†
C2	0.1 μ F Mullard	4p†
C3	50 μ F, 25V Mullard	6p†
SW1	D.P.S.T. Toggle switch	5p*
T1	Transistor output transformer, Eagle LT700	20p‡
LS	6 x 4in, 3 Ω loudspeaker	15p*
		98p

† Electrovalue Ltd.

* Padgetts Radio Stores

‡ Henrys Radio Ltd.


Prices are those advertised in June 1971 and may have changed. No allowance is made for minimum order costs or for postage and packing; this should be checked before ordering.

Current drain is important in all alarm circuits because if it is high, batteries, which are continually left on would rapidly run down. In the quiescent condition current consumption was measured as 1 μ A in the prototype as silicon transistors are used throughout, though when in operation this rises to over 20mA and a PP9 type battery has to be used.

C1 can be left out. If this is done the alarm is triggered by the slightest pulse—even by the switching on of fluorescent lights and this is a disadvantage. The inclusion of C2 has a slight delaying action as it takes time to charge up.

In certain locations the level of "muck" may be so high as to trigger the alarm *without* it being touched. In this case the value of R1 should be reduced to a suitable level which only triggers on touch; this also applies if a large touch plate is used.

GOING BACK...

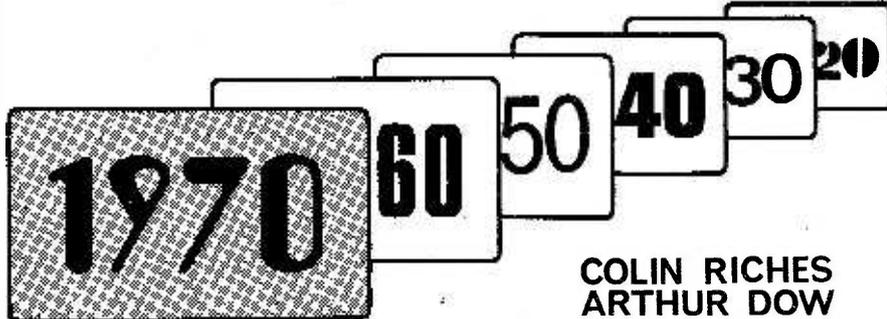

COLIN RICHES
ARTHUR DOW



TITANIC DISASTER

We are at present compiling a Going Back article about the Titanic Disaster and the radio messages that were transmitted and received on that tragic day. If any readers have any information or photographs that they think may help us, we would be very glad to hear from them.

MR. WILLIAM COBBETT tells us that he has a Harmsworth's Wireless Encyclopedia which was published in 1923. He says that it contains many interesting features and drawings, etc., the preface being written by Oliver Lodge himself. Mr. Cobbett says that 50 years after the books were first published it is amusing to read a line that states, "It is with great hesitation that we predict the time when each individual will possess his own pocket wireless set."

Perhaps any readers of *Practical Wireless* requiring information on wireless in the 1920's would like to contact Mr. Cobbett at 15 Copford Road, Billericay, Essex.

By the way, he tells us that anyone wishing to purchase the books will have to wait another 50 years!

Mr. C. R. Gunn of 48 Aldwark Road, Liverpool, L14.0N6 asks if anyone could tell him whether Paris (Eiffel Tower) still transmits the 300 dot second Time Signal that it used to years ago on long wave. Mr. Gunn cannot recall the wavelength of the transmissions but says that it used to be very interesting as with a microphone in the case of the Grandfather clock and a phone earpiece on one ear together with the radio phone on the other ear, the times when the two signals coincided were noted and checked by the time given after the transmission.

Mr. Gunn also asks if there is a publication giving a list of long wave stations transmitting Morse and what are the longest wavelength stations today? So if there are any readers who have any information that may interest Mr. Gunn, please write to him at the above mentioned address.

Basil D. Van Der Syde, F.S.E.R.T., 30 Langdon Road, Parkstone, Poole, Dorset, BH14 9EH asks if anyone can date a pair of headphones he has containing a built-in crystal receiver. There is no makers name and the "cans" are about twice the

normal depth. In the back of one there is a tapped inductance with a 20-position selector switch for tuning. This earpiece has two terminals marked A and E. The other earpiece has a centrally fitted crystal detector, part of which is missing but the cap end contains a piece of "galena" crystal. Also contained within this earpiece is a wind-up aerial of some 20 feet of wire-woven tape about 1/2 in. wide, and two small terminals marked "phones" (extension phones!). There is a Postmaster General approved stamp and the number 4145 printed on it. The crystal detector is integral with the small handle that winds the aerial in and the words "detector" prov. pat. printed below this—Mr. Van Der Syde mentions that when fitted with an 0A70 or similar diode, this set still provides fair MW signals (*Charles Molloy please note!*)

Many readers, we are sure, will remember our great colleague John Scott-Taggart. He used to bring out one "star" receiver for the home constructor every year in the magazine *Popular Wireless*. Mr. Van Der Syde says that checking over his collection of these magazines some years back, he was suddenly struck with the fact that the series was broken—that is that it began with ST100 then went to ST300, 400, 500 and so on up to about ST900—in other words no ST200! At first he thought his collection was not complete but this did not appear to be so. This made him wonder if there had ever been a ST200 design and if not, why not?—or if so, had it been withdrawn? He made many enquiries and at last managed to contact JST himself in about 1963. He wrote to him but in his reply, JST was unable positively to give any information about an ST200. He thought that there may have been one and that details may be found in one of his early radio books *Practical Wireless Valve Circuits* or its sequel *More Practical Valve Circuits* published by the Radio Press about 1924/25.

Can any readers help to clear up the mystery of the missing ST200? If so, please write to us (because this one has us puzzled) and we will pass your letters on to Mr. Van Der Syde.

Vintage enthusiast S. Ellis, 30 Pynne Close, Stockwood, Bristol 4 writes to ask if we have any information on the receiver used for the "Committee Superfet" article. Unfortunately we don't as this receiver was kindly donated to us by a reader who said that a relative of his had constructed it from a kit in the 20's (we would like to say here that Arthur Dow did not rip the set open and implant an inte-

BI-PAK SEMICONDUCTORS

SILICON RECTIFIERS—TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	4p	5p	5p	7p	14p	21p	47p
100	4p	5p	5p	15p	16p	23p	75p
200	5p	9p	9p	15p	20p	24p	21
400	6p	18p	17p	20p	27p	37p	21.25
800	7p	16p	10p	23p	34p	45p	21.88
1000	11p	25p	15p	30p	45p	65p	22-50
1200	—	35p	—	38p	57p	75p	—

NEW LOW PRICED TESTED S.C.R.'s

PIV	1A	3A	7A	10A	16A	30A
	TO6	TO66	TO66	TO48	TO48	TO48
50	23p	26p	47p	50p	58p	41-15
100	25p	38p	58p	58p	68p	41-40
200	35p	37p	57p	61p	75p	41-80
400	43p	47p	67p	75p	95p	41-75
600	55p	57p	77p	87p	11.25	—
800	68p	70p	90p	11.20	11-50	24

2A POTTED BRIDGE RECTIFIERS. 200V. 50p

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalent book for European, American and Japanese Transistors. Exclusive to BI-PAK. 75p each.

UNIJUNCTIONS
UT46. Eqt. 2N2646 Eqt. T1843. BEN3000 27p each. 26-99 25p, 100 UP 20p

NPN SILICON PLANAR
BC107/8/9 10p each. 50-99 9p, 100 up 8p each. 1,000 off, 7p each. Fully tested and coded TO-18 case.

ADI161 NPN ADI162 PNP
MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS
OUR LOWEST PRICE OF 65p PER PAIR

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqt. ZTX300 5p each. Any Qty.

TRIACS.

TO	6A	10A
V80M	2G TO66 TO48	200 50p 82p 21
200	70p 90p 41-25	
400	90p 21 81-60	

V80M—Blocking voltage in either direction.

SILICON DIAC
For use with Triacs
BR100 87p each

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed

Pak No.	EQVT.
T1 8 2G371A	OC71
T2 8 2G374	OC72
T3 8 2G374A	OC81D
T4 8 2G381A	OC81
T5 8 2G382T	OC82
T6 8 2G344A	OC44
T7 8 2G345A	OC45
T8 8 2G378	OC78
T9 8 2G368A	SN1802
T10 8 2G417	AF117

All 50p each pack.

CADMIUM CELLS
ORP12 45p
ORP60, ORP61 40p each

PHOTO TRANS.
OCF71 Type 43p

FREE
One 50p Pack of your own choice free with orders valued \$4 or over.


SIL. G.P. DIODES
300mW 30 50p
40PIV (Min.) 100 21.50
Sub-Min. 200 45
Full Tested 1000 29
Ideal for Organ Builders

ANOTHER BI-PAK FIRST!

THE NEW SGS EA 1000 AUDIO AMPLIFIER MODULE

* GUARANTEED NOT LESS THAN 3 WATTS RMS

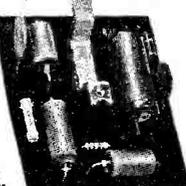Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TAA621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. OTHER USES—portable applications where supply rails as low as 9V are of prime importance.



- Sensitivity 40 mV for 1 watt VOLTAGE GAIN 40 dB can be varied up to 73 dB for some applications.
- Signal to Noise Ratio 86 dB.
- Frequency response better than 50 Hz to 25 KHz for —3 dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 OHM Loads.
- Overall Size 2" x 3" x 1".
- Typical Total Harmonic distortion at 1 watt less than 1%.
- Supply Voltage (Vs)—24V 15 ohm load.

MODUL TESTED AND GUARANTEED.
Qty. 1-9 10-25 Larger quantities
Price each £2-63 £2-28 quoted on request

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

"Q" PAKS QUALITY TESTED SEMICONDUCTORS

Pak Qty.	Description	Price
Q 1 20	Red spot trans. P.N.P.	50p
Q 2 16	White spot R.F. trans. P.N.P.	50p
Q 3 4	OC 77 type trans.	50p
Q 4 6	Matched trans. OC44/46/81/81D	50p
Q 5 4	OC 75 transistors	50p
Q 6 4	OC 75 transistors	50p
Q 7 4	AC 128 trans. P.N.P. high gain	50p
Q 8 4	AC 128 trans. P.N.P.	50p
Q 9 7	OC 81 type trans.	50p
Q 10 7	OC 71 type trans.	50p
Q 11 2	OC 127/128 Comp. pairs PNP/	50p
Q 12 3	AF 116 type trans.	50p
Q 13 3	AF 117 type trans.	50p
Q 14 3	OC 171 H.F. type trans.	50p
Q 15 2	2N2926 81L Epoxy trans.	50p
Q 16 2	GET880 low noise Germ. trans.	50p
Q 17 3	PNP 1 9T141 & 2 9T140	50p
Q 18 4	Mat'd 2 MAT 100 & 2 MAT 150	50p
Q 19 3	Mat'd 2 MAT 101 & 1 MAT 121	50p
Q 20 4	OC 44 Germ. trans. A.F.	50p
Q 21 3	AC 127 NPN Germ. trans.	50p
Q 22 20	NKT trans. A.F. R.F. coded	50p
Q 23 10	OA209 Sil. diodes sub-min.	50p
Q 24 8	UA 81 diodes	50p
Q 25 6	IN914 Sil. diodes 75PIV 75mA	50p
Q 26 8	OA95 Germ. diodes sub-min. IN 69	50p
Q 27 2	10A 600PIV Sil. Rects. 18425R	50p
Q 28 2	Sil. power rect. BYZ 13	50p
Q 29 4	Sil. trans. 2x2N696, 1x2N697, 1x2N698	50p
Q 30 7	Sil. switch trans. 2N708 NPN	50p
Q 31 6	Sil. switch trans. 2N709 NPN	50p
Q 32 3	PNP Sil. trans. 2x2N1131, 1x2N1132	50p
Q 33 3	Sil. NPN trans. 2N1711	50p
Q 34 7	Sil. NPN trans. 2N2369, 500MHZ	50p
Q 35 3	Sil. NPN TO-18 2x2N2904 & 1x2N295	50p
Q 36 7	2N3646 TO-18 plastic 300MHZ NPN	50p
Q 37 3	2N3953 NPN Sil. trans.	50p
Q 38 7	PNP trans. 4x2N3703, 3x 2N3702	50p
Q 39 7	NPN trans. 4x2N3704, 3x 2N3705	50p
Q 40 7	NPN amp. 4x2N3707, 3x 2N3708	50p
Q 41 3	Plastic NPN TO-18 2N3904	50p
Q 42 6	NPN trans. 2N5172	50p
Q 43 7	BC 107 NPN trans.	50p
Q 44 7	NPN trans. 4xBC105, 3x BC109	50p

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. T.T.L. Digital SN74N Series full packaged, brand new to Manufacturers' Specifications. Dual In-Line plastic 14 & 16 pin packages.

BI-PAL Order No.	Description	Price and Qty.	Prices 1-24	25-99	100 up
BP 00=7400	Quadrate 2-input NAND Gate	23p	20p	15p	
BP 01=7401	Quadrate 2-input Positive NAND Gate (with open collector output)	23p	20p	15p	
BP 02=7402	Quadrate 2-input Positive NOR Gates	23p	20p	15p	
BP 03=7403	Quadrate 2-input Positive NAND Gates (with Open-Collector Output)	23p	20p	15p	
BP 04=7404	Hex Inverters	23p	20p	15p	
BP 10=7410	Triple 3-input Positive NAND Gates	23p	20p	15p	
BP 18=7413	Dual 4-input Schmitt Trigger	34p	29p	29p	
BP 20=7420	Dual 4-input Positive NAND Gates	23p	20p	15p	
BP 30=7430	8-input Positive NAND Gates	23p	20p	15p	
BP 40=7440	Dual 4-input Positive NAND Buffers	23p	20p	15p	
BP 41=7441	BCD to decimal nixie driver	87p	77p	67p	
BP 42=7442	BCD to decimal decoder (4-10 lines, 1 of 10)	87p	77p	67p	
BP 47=7447	BCD-Sven-Segment Decoder/Drivers (15-V Outputs)	1.40	1.30	1.20	
BP 50=7450	Expandable dual 2-input AND-OR-INVERT	23p	20p	15p	
BP 51=7451	Dual 2-wide 2-input AND-OR-INVERT GATES	23p	20p	15p	
BP 53=7453	Quad 2-input Expandable AND-OR-INVERT	23p	20p	15p	
BP 54=7454	4-wide 2-input AND-OR-INVERT Gates	23p	20p	15p	
BP 60=7460	Dual 4-input Expander	23p	20p	15p	
BP 70=7470	Single-phase J-K Flip-Flop	35p	29p	29p	
BP 72=7472	Master-slave J-K Flip-Flop	35p	29p	29p	
BP 73=7473	Dual Master slave J-K Flip-Flop	49p	40p	37p	
BP 74=7474	Dual 0 type Flip-Flop	49p	40p	37p	
BP 75=7475	Quad latch	47p	45p	48p	
BP 76=7476	Dual J-K with pre-set and clear	47p	45p	45p	
BP 80=7480	Gated Full Adders	87p	77p	67p	
BP 81=7481	16-bit read/write memory	21.85	21.85	21.15	
BP 82=7482	2-bit Binary Full Adders	1.30	1.20	1.10	
BP 83=7483	Quad Full Adder	87p	77p	67p	
BP 86=7486	Quad 3 input Exclusive OR Gates	80	70p	60p	
BP 90=7490	BCD decade counter	87p	77p	67p	
BP 91=7491	8-bit Shift Registers	21.21	21.00	87p	
BP 92=7492	Divide-by-Twelve Counters	87p	77p	67p	
BP 93=7493	4-bit Binary Counters	87p	77p	67p	
BP 94=7494	Dual entry 4-bit shift register	87p	77p	67p	
BP 95=7495	8-bit up-down shift register	87p	77p	67p	
BP 96=7496	5-bit Parallel in parallel out Shift-Register	21.10	21.00	90p	
BP100=74100	8-bit Bistable Latches	21.75	21.65	21.15	
BP118=74118	Hex Set-Reset Latches	21.80	21.20	21.00	
BP121=74121	Monostable Multivibrators	87p	77p	67p	
BP141=74141	BCD-to-Decimal Decoder/Driver	87p	77p	67p	
BP145=74145	BCD-to-Decimal Decoder/Drivers	21.80	21.70	21.80	
BP151=74151	8-bit Data Selectors (with Strobes)	21.40	21.30	21.10	
BP153=74153	Dual 4-Line-to-Line Data Selectors/Multiplexers	21.40	21.30	21.20	
BP191=74191	Binary Counter reversible	23.60	23.25	23.00	

Devices may be mixed to qualify for quantity price. Larger quantities—prices on application. (TTL 74 series only).

Data is available for the above series of I.C.'s in booklet form. PRICE 13p.

LINEAR I.C.'s

Type No.	Case	Leads	Description	Price 1-24	25-99	100
BP201C—SL201C	TO-5	8	G.P. Amp	63p	58p	48p
BP701C—SL701C	TO-5	8	OP Amp	63p	50p	45p
BP702C—SL702C	TO-5	8	OP Amp Direct O/P	63p	50p	45p
BP703C—72702	D.L.L.	11	G.P. O.P. Amp (Wide Band)	53p	45p	40p
BP709P—VA709C	TO-5	8	High Gain OP Amp.	53p	45p	40p
BP741—72741	D.L.L.	14	High Gain OP Amp (Protected)	75p	60p	50p
MA703C—MA703C	TP-5	6	F.R.—IF Amp	43p	35p	27p
TAA293	TO-72	4	A.F. Amp	60p	60p	55p
TAA293	TO-74	10	G.P. Amp	90p	75p	70p

TTL INTEGRATED CIRCUITS

Manufacturers' "Full out"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00=12x7400N 50p	UIC42=5x7450N 50p	UIC80=5x7480N 50p
UIC01=12x7401N 50p	UIC50=12x7450N 50p	UIC82=5x7482N 50p
UIC02=12x7402N 50p	UIC51=12x7451N 50p	UIC83=5x7483N 50p
UIC03=12x7403N 50p	UIC60=12x7460N 50p	UIC86=5x7486N 50p
UIC04=12x7404N 50p	UIC70=8x7470N 50p	UIC90=5x7490N 50p
UIC05=12x7405N 50p	UIC72=8x7472N 50p	UIC92=5x7492N 50p
UIC10=12x7410N 50p	UIC73=8x7473N 50p	UIC83=5x7483N 50p
UIC20=12x7420N 50p	UIC74=8x7474N 50p	UIC84=5x7484N 50p
UIC40=12x7440N 50p	UIC75=8x7475N 50p	UIC85=5x7485N 50p
UIC41=5x7441AN 50p	UIC76=8x7476N 50p	UIC95=5x7495N 50p
	UICX1=25xAsst'd 74's 21-50	

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

DTL (Diode Transistor Logic) INTEGRATED CIRCUITS manufacturers "Fall out"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

Pak No.	Pak No.
UIC930=12xμA930 50p	UIC948=8xμA 948 50p
UIC932=12xμA 932 50p	UIC951=5xμA 951 50p
UIC933=12xμA 933 50p	UIC961=12xμA 961 50p
UIC935=12xμA 935 50p	UIC983=5xμA 983 50p
UIC936=12xμA 936 50p	UIC984=5xμA 984 50p
UIC944=12xμA 944 50p	UIC987=5xμA 987 50p
UIC945=8xμA 945 50p	UIC989=5xμA 989 50p
UIC946=12xμA 946 50p	UIC 925 Assorted 930 Series 21-50

Packs cannot be split but 25 Assorted Pieces (our mix) is available as PAK UICX9. Every PAK carries our BI-PAK Satisfaction or money back guarantee. Data Booklet available for the BP980 Series, PRICE 13p

ALL PRICES IN NEW PENCE.
Please send all orders direct to our warehouse and despatch department.
BI-PAK SEMICONDUCTORS
P.O. BOX 6, WARE, HERTS.
Postage and packing add 7p. Overseas add extra for Airmail. Minimum order 50p. Cash with order please. *GRO No. 388-7006

ALL OUR UNTESTED SUPER PAKS ARE STILL AVAILABLE. See nearest issue for details or send S.A.E. for LISTS

PROGRESSIVE POWER SUPPLY MODULES

Based on many years experience in industrial electronics we have designed a carefully graded range of power supply modules. Intended for the serious constructor they are also suitable for Technical Colleges and other educational purposes. Our design and manufacturing experience and component bulk buying capacity make it possible to offer modules built

and tested at very modest prices. All modules are sold with a "Money Back" guarantee of satisfaction. Built with the professional touch on specially designed printed circuit boards, all modules are fitted with edge connectors to permit easy insertion and removal. They may also be wired in where desired.

71Z RANGE. Basic zener stabilised P.U. with floating output. For general use including switching & op. amp. circuits. Size 4" x 4".

71Z9	± 9v at 30mA	} Price £3.95 each + £0.25 P & P
71Z12	± 12v at 15mA	
71Z15	± 15v at 10mA	


71ZR RANGE. A more complex circuit than the 71Z Range giving greater stability with changing loads and with reduced ripple content. Output current limiting is included for general protection. An ideal P.U. for electronic instruments and control circuits. Size 4" x 3".

71ZR9	+ 9v at 40mA nom.	} Price £4.50 each +£0.25 P & P.
71ZR12	+ 12v at 40mA nom.	
71ZR15	+ 15v at 40mA nom.	

71ZA. An extension of the 71ZR embodying an error amplifier with current limiting and adjustable output voltage regulated to better than 1.5% for load and mains variations. Ripple better than 3mV. Size 4" x 4.4".

71ZA. 15v ± 3v at 100mA. Price £5.50 each + £0.25 P & P.

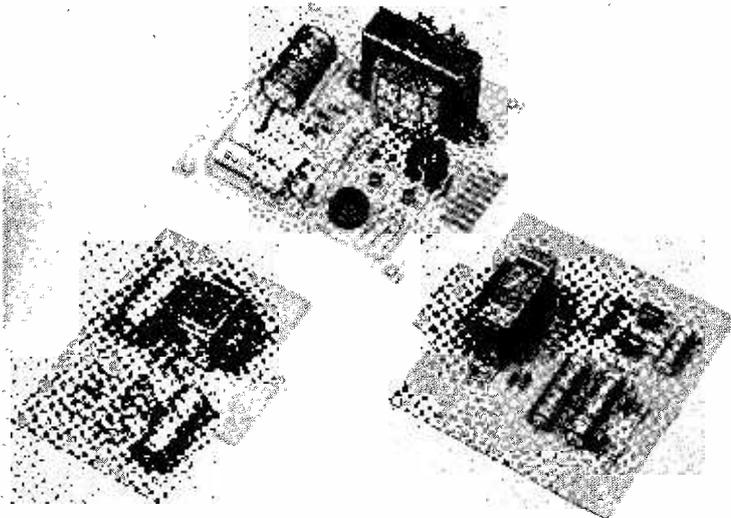714. Special power unit suitable for the Audio Signal Generator described in the May issue. Price £4.20 each + £0.25 P & P. Trade enquiries invited.



We are also distributors of the full range of Newmarket Transistors Limited's P.C. Modules
HARVEY HALL (Dept. P.W.), BRECKLAND WORKS, EARLS ST., THETFORD, NORFOLK.

LOOK AT THESE PRICES

CARTRIDGES

Acos GP67-2, GP91-35C £1.12½; Acos GP93-1 £1.33½; Acos GP94-1 £1.62½; Sonotone 9TACB £1.97½. All above in makers' cartons. BSR X4H £1.50.

THIS MONTH'S SPECIAL OFFER

Garrard SP25 Mk. III with KS40A cartridge. In good quality teak plinth with perspex dust cover. Complete with all leads ready to use £20. SP25 Mk. III deck only less cartridge £11.87.

PLUGS & SOCKETS

Phono plugs, assorted colours 4½p; 45p per doz.; Coaxial plugs, aluminium 7½p; Coaxial couplers 7½p; 2 pin DIN plugs 15p; 3 pin DIN plugs 15p; 5 pin DIN plugs 17p; 2 pin, 3 pin & 5 pin DIN sockets 7½p; Wander plugs 3½p; sockets 8½p; Banana plugs 5½p; Sockets 5p; 3.5mm J/Plugs 7½p and 12½p; Standard J/Plugs with solder terminals 10p; Chrome 15p; Side Entry J/Plugs black and chrome 24p; Insulated j/sockets—o/cct 20p, c/ect 17p.

ELECTROLYTIC CAPACITORS

4uF 150v 4p; 8uF 500v 15p; 10uF 150v 4p; 12uF 25v 4p; 16uF 450v 14p; 16uF + 16uF 450v 23½p; 30uF 10v 4p; 50uF 10v 4p; 100uF 9v 4p; 100uF 12v 4p; 150uF 12v 4p; 320uF 9v 5p; 1500uF 30v 19p; 10uF 16v 7½p; 5000uF 25v 50p; 10,000uF 25v 75p; 20,000uF 30v £1.05.

MICROPHONES

Acos Mic 45 £1.12½; Acos Mic 60 99½p; Planet CM70 £1.50; Hand Mike 75p.

VALVES

FY81 36p; PCL82 39p; EF183 45p; EF184 45p


Postage extra.

GEORGE FRANCIS (Dept PW),

12-14, MIDDLE GATE, NEWARK, NOTTS.
 Telephone: Newark 4733.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

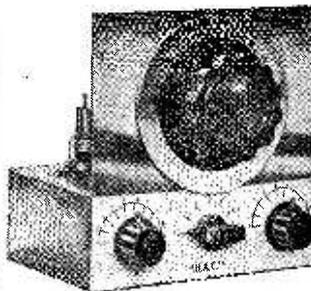

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER


Improved one-valve model "DX" mark 2. Complete kit—price £9.50 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS
 29 Old Bond Street, London W.1

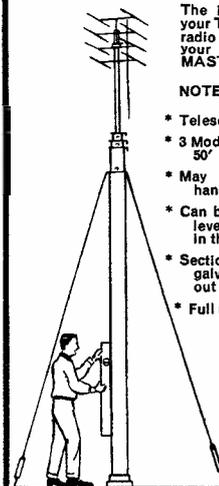PUT YOUR AERIAL WHERE IT CAN REALLY WORK!



The ideal way to boost your TV, amateur or 2-way radio signal is to mount your aerial on a TEO-MAST

NOTE THESE FEATURES

- * Telescopes down to 10'
- * 3 Models giving 30', 40' or 50'
- * May be erected single handed
- * Can be rotated at ground level to point the aerial in the required direction
- * Sections slide smoothly; galvanised inside and out
- * Full range of accessories for ground wall or roof mounting
- * Rigging kits include guys, hinged base, thimbles, etc.

Prices (carr. paid)	Mast only	Mast and Rigging Kit
U.K. Mainline	30' £14.40	£19.95
	40' £16.50	£25.50
	50' £19.50	£31.50


WESTERN ELECTRONICS (U.K.) LTD.
 ROOM I.P.W. OSBORNE ROAD,
 TOTTEN, SOUTHAMPTON SO4 4DN
 Tel: Totton 4930 Cables: Aerial Southampton.

grated circuit—it was a clever bit of camera trickery!). Anyway, Mr. Ellis says that in his set there are more wires with nothing at the end of them than there are connecting components. The components appear to be in good condition. There valves are included (PM1A, D210, PM1LF—possibly), the valve-holders are square and the four pins marked F, A, F, G. Stamped on the holders is the word “Benjamin” and “Genuine Bakelite.”

There are two variable capacitors made by Ormond Engineering Co. each fitted with a dial similar to the “Committee Superfet”. The coil is 7in. long and 4in. in diameter and is stamped “Trade ISOLO Mark” there are three windings of cotton or silk covered wire. Resistors are Dubilier Dumetohm which have the appearance of cartridge fuses, each one clipping into a holder. The capacitors have thumbscrew terminals as does a fully-shrouded transformer inscribed “Hollingwood” with markings for secondary, primary, grid, plate, h.t.+ and +D. Also, one point to note is that there is a bracket attached to the base-board reading “Etherplus.”

Once again, the staff of P.W. would like to hear more about this, so please drop us a line, and we’ll pass the letters on.

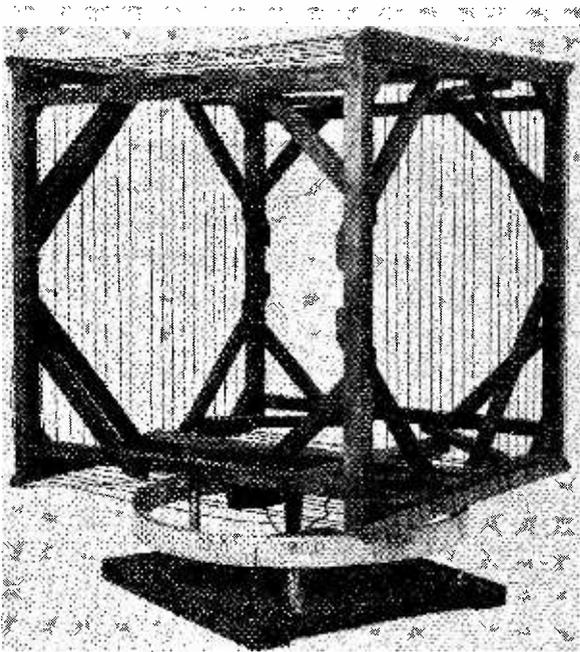Our aerial photograph is enough to make Dave Gibson’s hair curl (“what hair?” shouts someone from the back row). What about strapping this one on the top of your wagon, Gibby and working a bit of mobile DX?



Actually it's an early frame aerial used for direction-finding in aircraft. The date is about 1916 and the photograph was lent to the Science Museum by the National Physical Laboratory.

In “Going Back” May 1971, we published a photograph which we captioned “Magnetic Detector”. This should have read “Multiple Tuner” and we would like to thank all those readers who were kind enough to point this out.

PROJECT Autumn

Practical Wireless “Designer’s Trophy”

1971

This year we are sponsoring another Project Autumn competition. The rules have been amended so that the PW “Designer’s Trophy” 1971 will be awarded to the author of the best constructional article published in PW issues dated July 71 to March 72 inc.

NO DELAYS!

PAYMENT ON PUBLICATION

NO FORMS!

RULES

1. The winning entry will be chosen by a panel of judges from among articles published in issues of PW dated July 1971 to March 1972 inclusive. The Editor’s decision on all matters arising will be final.
2. The winner of the competition will receive and retain outright the PW “Designer’s Trophy 1971”. Other prizes will be awarded to the best runners-up. Articles will be paid for as soon as possible after publication.
3. Articles submitted for the competition should conform to the general style of material published in PW and must describe the operation and construction of a piece of radio, audio or test equipment that has been designed and built by the author.
4. Articles should, preferably, be typed using double spacing, leaving wide margins, on one side only of each sheet. Circuit diagrams and any other drawings must be separate and numbered to agree with the text. Author’s roughs must be clear enough to permit re-drawing. Components lists must also be separate and laid out to the standard PW format.
5. Photographs of the equipment are desirable and should be in black and white, sharp and clear. Photographs may be identified by sticking a label on the reverse instead of writing on the back of the photograph itself.
6. Components used in the design must be readily available from retail sources.
7. Articles should be sent to the Editor, Practical Wireless, Old Fleetway House, Farringdon Street, London, E.C.4. Authors will be advised as soon as possible of the acceptance or rejection of their articles. Equipment, the subject of an article must not be sent to the Editor until advised to do so.
8. Employees and staff of PW are not eligible for entry to this competition.

SUBMIT YOUR ARTICLES NOW

practically wireless commentary by HENRY

MOTORING correspondents are fond of telling us the tales of woe they experience with their new cars. Doors jam, windscreen wipers fail, handles fall off, and other, more technical failings begin to show after a short spell of use. "The suspension suffered badly



... experience with their new cars.

from hugging on anything more than a twenty-degree bend . . ."

They don't know the half of it. The benefits of mass production hit the radio industry long ago, and with all the paraphernalia of printed circuits and peripheral hardware, modern radio and audio equipment has reached its nadir of vulnerability.

Only last week we had a very expensive, very elaborate hi-fi amplifier on the bench, sighing dolefully. It couldn't sing; its protection circuits, which comprised more than half the twisted jungle through which we tried to hack our way, did their work too thoroughly. Every time a signal pushed past the preamps, Tr1 switched hard on, putting Tr2 "off" and interrupting the bias control of Tr3 which promptly bottomed. This overcame the zener regulation of Tr4 which is in the feedback line of . . .

Henry tuned in last week, hoping to brush up his faltering maths, and was greeted with the pontifical statement: "Mathematics is not so much about numbers as about sets."

Sets? Sets of what? Or did the Professor mean wireless sets? It might have been appropriate to our subject if he did, for the ensuing discussion was more

philosophical than enlightening.

Some of the equipment that comes in for service within weeks of being sold must have been assembled under similar conditions. Perhaps, in the Buzzbox factory in Arnold's Wick, SW 19, the wires have got crossed and those overtime earners on Saturday mornings are listening to the cut and thrust of O-U discussion.

Well, not so much cut and thrust as snip and shove. Which may account for some of the un-tightened bearing clamps, twisted drive cords, unsealed iron-dust cores and knobs that fall off. The operator is away in a dream, lapped by the lulling voices. There used to be a saying in a radio factory where Henry once worked: "Lil's in love again."

It was invoked whenever we slaves of the troubleshooting department discovered a "run" of faults.

The inspectors would reject one set in five for "no-go" faults, normally. Then would come a spate of rejections, and we—the only true engineers in the factory, we averred, *not* excepting the designer—ran our delicate diagnostic probiscuses over them.

Hovering at our shoulder, the Production manager waited for the dread words: "R21 wrong value, should be 33k, not 33 ohms." We laid bets on the number of sets that Lil had allowed through as she dreamed over the new boy. The variables for handicapping were the rate of the conveyor, the alacrity of the Production manager and, top weight for the course, the slowness of the troubleshooter.

In that sort of job, every day was Saturday. Down in Arnold's Wick, SW 19, the Monday set, the rogue receiver, is the speciality of their range. After a week of use it hesitates and splutters.

We bang it. A knob falls off. We shake, and two programmes arrive together. The volume con-

trol adds its crackling obligatto and then the tiny loudspeaker squawks in protest. So we take it in for service.

The knowledgeable salesman shakes his head sadly. "Perhaps the worst model they made," he pronounces. "You didn't buy it here of course?" His question is more a statement; that isn't the sort of trash they would sell. But they do, eventually, repair it, after weeks of waiting for irreplaceable parts that have to be ferried from Japan in a leaking sampan.

And within another week it splutters and coughs into silence. A little tense, we face the salesman again. Could we see the manager? Not, it seems, without an appointment, but they guarantee their work and condescend to look at it again.

This time, again with a bill to pay, we are told that another vital component has failed. "Quite unforeseeable. The quality of the components used in these—er—less expensive receivers . . ." The




'Lil's in love again.'

work done on their last job, the guaranteed work, could not cover the eventuality of that component's failure.

It would have been better, less expensive, if we had faced up to the truth. Ours was a Saturday set, or a Monday set, or whatever day our Lil habitually assembles errors down in Arnold's Wick, SW 19. Better thrown away.

new

Super IC-12

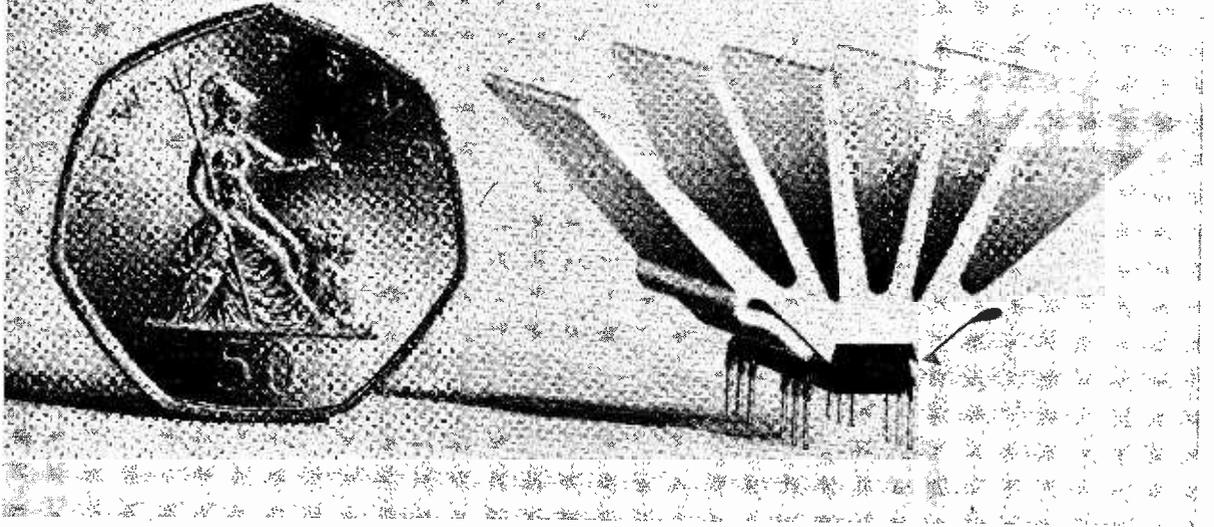

High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

Output power 6 watts RMS continuous (12 watts peak).

Frequency Response 5 Hz to 100KHz \pm 1dB.

Total Harmonic Distortion Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

Load Impedance 3 to 15 ohms.

Power Gain 90dB (1,000,000,000 times) after feedback.

Supply Voltage 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

Size 22 x 45 x 28 mm including pins and heat sink.

Input Impedance 250 Kohms nominal.

Quiescent current 8mA at 28 volts.

Price: including FREE printed circuit board for mounting, **£2.98** Post free

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project 60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.

Sinclair Radionics Ltd., London Rd, St. Ives
Huntingdonshire PE17 4HJ
Telephone St Ives (048 06) 4311

sinclair

Sinclair Project 60



the world's most advanced high fidelity modules

Sinclair Project 60 presents high fidelity in such a way that it meets every requirement of performance, design, quality and value and now that the remarkable phase lock loop stereo FM tuner is available, it becomes the most versatile of high fidelity systems. With Project 60, it is possible to start with a

modest mono record reproducer and expand it to a sophisticated stereophonic radio and record reproducing system of fantastically good quality to hold its own with any other equipment, no matter how expensive. Project 60 is a unique high fidelity module system where compactness and ease of assembly are combined with

circuitry that is far in advance of any other manufacturer in the world. Thus it is extraordinarily easy to assemble any combination of modules using nothing more complicated than the simplest of tools, and you certainly do not have to be experienced to build with complete confidence. The 48 page manual free with Project 60 equipment makes everything easy and you can house your assembly in an existing cabinet, motor plinth, free standing cabinet or virtually any arrangement you wish. Once you have completed your assembly you will have superlatively good equipment to give you years of service and enjoyment. You will have obtained superb value for money because Project 60 is the best selling modular system in Europe and can therefore be produced at extremely competitive prices and with excellent quality control.


Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE17 4HJ.
Tel: St. Ives (048 06) 4311

sinclair

System	The Units to use	together with	Cost of Units
A Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£4.48
B Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
C 20+20 W. R.M.S. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., most dynamic speakers, F.M. tuner etc.	£23.90
D 20+20 W. R.M.S. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
E 40+40W. R.M.S. de-luxe stereo amplifier	2 x Z.50s, Stereo 60 PZ.8, mains trsfrmr	As for D	£34.88
F Outdoor P.A. system	Z.50	Mic., up to 4 P.A. speakers controls, etc.	£5.48
G Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43
H High pass and low pass filters	A.F.U.	C, D or E	£5.98
J Radio	Stereo F.M. Tuner	C, D or E	£25.00

Sinclair Project 60

Z.30 & Z.50 power amplifiers

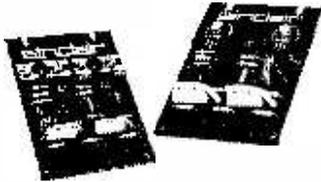

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms, using 50 volts.

Frequency response: 30 to 300 000 Hz \pm 1dB.

Distortion: 0.02% into 8 ohms.

Signal to noise ratio: better than 70dB un-weighted.

Input sensitivity: 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size $3\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$ in.

Z.30

Built, tested and guaranteed with circuits and instructions manual


£4.48

Z.50

Built, tested and guaranteed with circuits and instructions manual.

£5.48

Power Supply Units

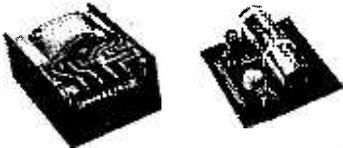

Designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

PZ-5 30 volts un-stabilised £4.98

PZ-6 35 volts stabilised £7.98

PZ-8 45 volts stabilised

(less mains transformer) £7.98

PZ-8 mains transformer £5.98

Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

Stereo 60 pre-amp/control unit



Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS

Input sensitivities: Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve \pm 1dB; 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; Aux—up to 3mV.

Output: 250mV

Signal-to-noise ratio: better than 70dB.

Channel matching: within 1dB.

Tone controls: TREBLE + 15 to -15dB at 10KHz; BASS + 15 to -15dB at 100Hz.


Front panel: brushed aluminium with black knobs and controls.

Size: $8\frac{1}{4} \times 1\frac{1}{2} \times 4$ ins.

Built, tested and guaranteed.

£9.98

Active Filter Unit

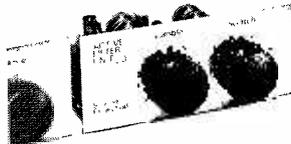


For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass). Supply voltage—15 to 35V. Current—3mA. H.F. cut-off (-3dB) variable from 28KHz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1kHz (35V. supply) 0.02% at rated output.

Built, tested and guaranteed

£5.98

Stereo FM Tuner

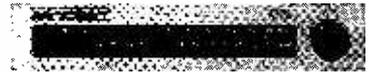

first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time, the principle has been applied to an FM tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Sensitivity is such that good reception becomes possible in difficult areas. Foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

SPECIFICATIONS:

Number of transistors: 16 plus 20 in I.C.

Tuning range: 87.5 to 108 MHz

Capture ratio: 1.5dB

Sensitivity: 2 μ V for 30dB quieting; 7 μ V for full limiting.

Squelch level: 20 μ V.

A. F. C. range: \pm 200 KHz

Signal to noise ratio: >65dB

Audio frequency response: 10Hz—15KHz (\pm 1dB)

Total harmonic distortion: 0.15% for 30% modulation

Stereo decoder operating level: 2 μ V

Pilot tone suppression: 30dB

Cross talk: 40dB

I. F. frequency: 10.7 MHz


Output voltage: 2 x 150mV R.M.S.

Aerial Impedance: 75 Ohms

Indicators: Mains on; Stereo on; tuning indicator

Operating voltage: 25-30 VDC

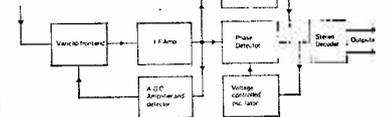Size: 3.6 x 1.6 x 8.15 inches; 91.5 x 40 x 207 mm



Price: **£25** built and tested. Post free

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send _____


Name _____

Address _____

for which I enclose cash/cheque/money order.

PW772


BARGAIN COMPUTER BUMPER BOARDS

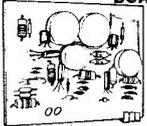

Many Resistors, Condensers, Diodes and Transistors (minimum of 4 transistors on each board).
5 BOARDS FOR 120p. Post Free.

LIGHT DIMMER

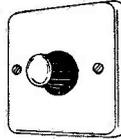The unit comes complete with MK Ivory Front Plate and Control Knob, when used in place of Light Switch it will control your room lighting from, off to full brightness. Power—up to 300 watts interference suppressed



£2.75 + P. & P. 8p.

EMI LOUDSPEAKER 450

10W 13in x 8in ± two 2-24in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-16 ohm imp
£3.50 plus 38p P. & P. each.



Our new branch is now open:

13 SOUTH MALL, EDMONTON GREEN, EDMONTON, N. 9

Phone 01-803-1685
Carrying an ever-increasing stock of components. Electrical, surplus and H.F.I.

CHROMOSONIC SOUND OPERATED LIGHT DISPLAY



This compact unit (size 8½" x 5½" x 3" high) is connected directly across the speaker output of an amplifier, it will then convert audio signals into a spectacular three colour light display (600 watts light output each colour) Send S.A.E. for further details.
£18.50 P. & P. 39p
Please call in No. 11 for demonstrations.

CRESCENT

RADIO LTD
11 & 40 MAYES RD
LONDON N22 6TL

888-3206


MAIL ORDER DEPT.
No. 11
MAYES RD.
LONDON
N22 6TL

TRANSFORMER SCOOP



Primary 220, 250 v. fused. Secondary, 220 v. at 50mA. 6.3v at 1 amp. Overall size 2¼" x 2" x 2¾" high.
63p each. P. & P. 15p.

D.P.D.T. SLIDE SWITCH

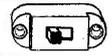

SIZE 1½ ins long & wide each
19p each. Post 3p

100 WATT

HIGH POWER AMPLIFIER



- In excess of 100 watt peak output
- Open and short circuit proof
- Sensitivity 10mV for full output
- Frequency Response 10-25,000Hz
- Safe with all loudspeaker systems.
- 4 to 16 ohms
- Silicon transistors used throughout
- F.E.T. Front end

▲ **£42.00** If purchased with light unit above **£40.00**
Post and Insurance £1.00.

Battery Eliminator Plug your transistor radio, amplifier, cassette, etc., into AC mains through this compact eliminator. 2½" x 2½" x 3½" approx. 6v £1.50; 9v £1.50; 7½v complete with cable & plug for Philips cassette £2.00, p & p 8p each

G.E.C. RATCHET RELAY

No RELIA/008/07 Coil—375 Ω 3-make break contacts. 1-changeover. All New and Boxed.
30p. each. Post 5p.

SOLID STATE BLOCK MODULES




Phono pre-amp E1311 input 100k; gain 28dB max out 3 volt; max input 50mV. Tape pre-amp as above E1313. Power amp E1314 input 1,000 ohms gain 20dB 300mW. Organ tone osc E1315 tone freq. 200-1k Hz output 80mW. All above modules 9 volt. Dual flasher E1318 flash time 1-4 secs power 6 volt. Lamp 6v 150mA. All at **£1.25 P. & P. 10p**

COMPONENT CENTRE

- 8 x 8 Printed circuit board 10p each
 - By100 Type rectifier 800 Piv 750 mA 18p "
 - 4 Pin transistor holders 21p "
 - 2½ Ohm speaker 32p "
 - U2 Battery holders 5p "
 - 100HM W/W Pots 12p "
 - OC81 Heat clips (double) 23p "
 - Tape rev counters 40p "
 - 1,500mF 150v DC 4" x 2" dia approx 25p "
 - Flex connector 2amp approx Non-reversible 8p "
- Ideal for loudspeaker connections.
Please include Post & Packing
Send S.A.E. for return of post quote of your electronic project.

DWELL TIME UNIT

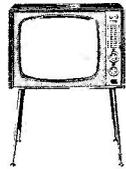These small units contain the following components: 700 ohm D.P.T. relay with base, 1µF 250v. paper, 0.01µF 400v. paper, 50µF 35v. electrolytic, 3 diodes OC200 transistor, a 2N2926 type transistor unmarked, a skeleton pre-set pot, 4 pin din plug & socket, 4 foot of 4 core screen. All housed in a small neat metal box. Can be made into many timing devices.
43p p & p 8p



EX RENTAL TV's

19" — £29.95
23" — £39.95

All Channels 405/625
2 Years Guarantee.
Free List by return.


17" Slim line TV's £11.95, 19" Slim line TV's £15.95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1.95. Daily demonstrations to personal shoppers.

TEAK HI-FI STEREO CABINETS £14.95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1.00.
TRANSISTOR GANG CONDENSERS 30p. Miniature AM precision Tape Motors £1.95 famous German manufacturer. 200/250V. Post 20p.

Transistor Radio Cases: 25p each. Size 9½" x 6½" x 3½". P. & P. 15p.
SPEAKERS 50p 2½" 8Ω BRAND NEW. P. & P. 5p.

TV TUBES REBUILT GUARANTEED 2 YEARS

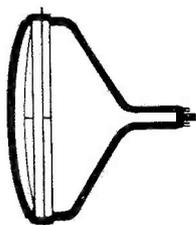

14"—£3.95, 17" & 19"—£5.95,
21" & 23"—£6.45.
Exchanged Bowls. Carr. 53p.

TRANSISTORS Post Free
AC 125 AF 179 OC 81
AC 128 OC 44 OC 81D
AF 114 OC 45
AF 117 OC 71 15p each

POTENTIOMETERS 23p each
Double & Switched 500 KΩ/500 KΩ 3½" shaft
Double & Switched 500 KΩ/100 KΩ 2" shaft
Double & Switched 1 MEG/100 KΩ 1½" shaft
Post. & Pack. 5p.—4 for 10p

KNOBS 100,000 to clear (Brand New)
100 assorted Radio & T.V. knobs 50p. Postage 10p. (If you require sets 2 to 6 just ask)

DUKE & CO. (LONDON) LTD.
621/3 Romford Road, Manor Park, E12
Phone 01-478 6001-2-3 Stamp for Free List

FREE FLOG LIST No. 6

Scores Special Bargains

SEND S.A.E. OR CALL AT ANY BRANCH FOR YOURS

HUGE RANGE OF SPECIAL SNIP—STEREOS, DECKS, TAPE RECORDERS, AMPLIFIERS, SPEAKERS, TRANSISTORS, VALVES, COMPONENTS—AT ALL BRANCHES.

ENORMOUS PURCHASE. GUARANTEED. APPROX. HALF PRICE.

WORLD FAMOUS TAPE

Standard Play		Double Play	
3in. 150ft. 12p	3in. 300ft. 20p	4in. 600ft. 40p	5in. 1,200ft. 75p
4in. 300ft. 23p	4in. 600ft. 45p	5½in. 1,800ft. 95p	7in. 2,400ft. £1.35
5½in. 900ft. 53p	5½in. 1,800ft. 95p	Triple Play	
7in. 1,200ft. 63p	7in. 2,400ft. £1.35	3in. 225ft. 14p	4in. 900ft. 65p
Long Play		4in. 450ft. 28p	5in. 1,800ft. £1.25
3in. 225ft. 14p	4in. 900ft. 65p	5½in. 2,400ft. £1.70	7in. 3,600ft. £2.20
4in. 450ft. 28p	5in. 1,800ft. £1.25	7in. 1,800ft. 83p	Quadruple Play
5in. 900ft. 53p	5½in. 2,400ft. £1.70	7in. 1,800ft. 83p	3in. 600ft. 43p

Postage 5p reel. 3in. 600ft. 43p
Post Free less 5% on three reels. Quantity and Trade enquiries invited



★ Portsmouth—350 Fratton Rd. Tel. 22034
★ Southampton—72 East St. Tel:25851
★ Southampton—77 East St. Tel:31276
★ Brighton—6 Queens Rd. Tel:23975
★ All Mail Order Tel: 0993 882299 15-17 QUEEN ST. ARUNDEL

When in LUTON, BEDS, you must visit the SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.
Closed all day Wednesday.

SURPLECTRONICS
216 LEAGRAVE ROAD, LUTON, BEDS

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
AC177	0-15	2G303	0-13
AF139	0-37	2N1302-3	0-20
AF186	0-50	2N1304-5	0-25
AF139	0-37	2N1306-7	0-30
BC154	0-25	2N1308-9	0-35
BC171 = BC107	0-13	2N3819FET	0-45
BC172 = BC108	0-13		
BF194	0-15	Power	
BF274	0-15	Transistors	
BSY25	0-57	OC20	0-50
BSY26	0-13	OC23	0-30
BSY27	0-13	OC25	0-25
BSY28	0-13	OC26	0-25
BSY29	0-13	OC28	0-30
BSY95A	0-13	OC35	0-25
OC41	0-13	OC36	0-37
OC44	0-13	AD149	0-30
OC45	0-13	AU110	1-25
OC71	0-13	2S034	0-25
OC72	0-13	2N3055	0-63
OC73	0-17	Diodes	
OC81	0-13	AY42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN9114	0-07

FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

CLEARANCE LINES

TO MAKE ROOM FOR NEW STOCK
 OC71, OC72 transistors unmarked fully tested 5p.
 TIC45 thyristors 6 amp 60V fully marked and tested Texas plastic-type 15p.
 CR525/025 Thyristors 25 amp 25V 25p.
 I.C.'s fully marked and tested by AEI. Gates 25p.
 Flip flops 50p.
 709C linear amp TO-5 can 50p.
 1 watt zener diodes 7-5V, 6-8V, 24V, 27V, 30V and 43V 5p each.
 OA47 gold bonded diodes 3p.

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each
 post and packing 23p.

SPECIAL LINE

1 AMP Bridge rectifiers 3in Square
 100 PIV.=25p. 400 PIV.=17p. 800 PIV.=50p.

PAK F.3..... 13p
 Complementary Set. PAIR
 NPN/PNP Germ. Trans.

BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1

Post and packing 25p.

NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V, 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Postage 13p Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	20	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoded black glass type PNP Germ.	50p
H19	10	OC81/81D uncoded white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoded TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

F.E.T. PRICE BREAKTHROUGH!!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

1-10 30p each, 10-50 25p each, 50+ 20p each.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car.

£1 each

FREE CATALOGUE AND LISTS for:—

ZENER DIODES TRANSISTORS, RECTIFIERS FULL PRE-PAK LISTS & SUBSTITUTION CHART

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

P.O. RELAYS 8 FOR

Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

£1

OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

TYPE "A" PNP Silicon alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range.

TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.

TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.

TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors TO-18 mixed untested similar to 2N706-6A-8, BSY26-7A9-95A and BC170 etc. £4-25 per 500. £8 per 1000.

NPN Silicon Planar transistors plastic encapsulation untested similar to 2N3707 to 3711. £4-25 per 500. £8 per 1000.

Silicon planar diodes do-7 glass similar to OA200-202, BAY31-36. £4-50 per 1000.

NPN/PNP Silicon planar transistors plastic TO-18 similar to BC113-4, BC153-4, BF153-160, etc. £4-25 per 500. £8 per 1000.

NPN Silicon planar transistors TO-5 can similar to BC142/3, BFY50-2-3. £5-25 per 500, £10 per 1000.

OC44, OC45 transistors fully marked and tested 500 to 999, 8p each, 1000+ 6p each.

OC71 transistors fully marked and tested, 500 to 999, 6 each, 1000+ 5p each.

A amp miniature plastic diodes IN4001 at 500 to 999, 4p each, 1000+ 3p each.
 IN4004 at 500 to 999, 5p each, 1000+ 4p each.
 IN4006 at 500 to 999, 6p each, 1000+ 5p each.
 IN4007 at 500 to 999, 8p each, 1000+ 7p each.

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1½ watt Zeners. Top hat type	50p
H11	30	MAT Series "alloy" pnp Transistors	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.	50p

FREE! A WRITTEN GUARANTEE WITH ALL OUR SEMICONDUCTORS

BI-PRE-PAK LTD

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
 TELEPHONE: SOUTHEND (0702) 46344

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

You LEARN—but it’s as fascinating as a hobby

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of “OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B8, ALDERMASTON COURT, READING RG7 4PF

POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B8 Aldermaston Court, Reading RG7 4PF
Please send books and full information — FREE and without obligation.



NAME..... AGE.....

ADDRESS.....

OCCUPATION.....

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

LIND-AIR AUDIO

GARRARD HI-FI TURNTABLES



- SP25 Mk III..... £11-97
 - Base and cover for above..... £4-95
 - AP76..... £20-85
 - SL72 B..... £24-97½
 - SL75 B..... £28-35
 - SL95 B..... £39-45
 - Base and cover for above..... £5-97½
 - 401..... £31-50
- P. & P. Decks 62½p. Base & Cover 50p.
Deck/Base/Cover 87½p.

THIS MONTH'S SPECIAL OFFERS!

- SP25 Mk III with base £18-98. P. & P. 75p
- SP25 Mk III with Sonotone 9TAHCD cartridge and base £18-75½. P. & P. 75p.


VHF AIRCRAFT BAND CONVERTER Model VHF.105

When placed within 1in. of a MW band Radio full coverage of VHF Aircraft Band 110-135 Mc/s. can be obtained. All transistor, 9v battery operation. Fully tunable 18½ in. x 7 section telescopic aerial. Size 4 x 2½ x 1½in.



OUR PRICE £3-60 P. & P. 20p

SINCLAIR PROJECT 90

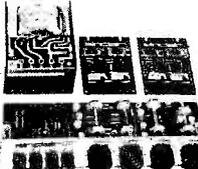

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. Z30 24 watt Power Amplifier £4-47½ (2 required).

Stereo Sixty Control/Pre-amplifier £9-97½

PZ.5 Power Supply Unit £4-97½

SINCLAIR PROJECT 60 Package deal price £19-95 P. & P. 62½p

Project 60 is supplied complete with instruction manual and templates for plinth mounting.

SINCLAIR IC-10 INTEGRATED CIRCUITS

10 watt Amplifier. Size only 1 x 0.4 x 0.2in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years.

£2-97 P. & P. 8p

SINCLAIR IC.10 with special transformer to operate from AC Mains 230/250v. Output 13v at 0.5 amp £8-98 P. & P. 15p.

All Mail Orders to:—Dept. PW8
53 TOTTENHAM CT. RD., LONDON W1. 01-637 1801

Callers welcome also at

18-19 TOTTENHAM CT. RD., LONDON W1. 01-580 2255

85 TOTTENHAM CT. RD. LONDON W1. 01-580 7679

149 FLEET STREET, LONDON EC4. 01-553 1419

94-98 UPPER PARLIAMENT ST. NOTTINGHAM. Tel: 40408

SAVE AT LEAST £13 BRAND NEW EXCLUSIVE OFFER



CASSETTE TAPE RECORDER and MUSIC CASSETTE PLAYER
FANTASTIC BARGAIN PRICE
£13.95 P. & P. 30p

No fiddly tape threading, just snap in a compact cassette. Amazing performance from all transistorised circuit. Auto level control. Luxurious wood grain and black finish. Runs on 4 x 1.5 batteries. Complete with remote control mike, stand and strap. 90 min play cassette 65p extra (*Rec. price of indent. mod. with case £29.40).


E.M.I. LOUSPEAKERS

- MODEL 450**
18½" x 8" elliptical with twin tweeters. 8 ohm impedance. 10 watts. Brand New, guaranteed. Lind-Air Price
£3-97½
P. & P. 22½p
- MODEL 150**
18½" x 8" elliptical, 3 and 15 ohm impedance 10 watts. Lind-Air Price
£2-97½
P. & P. 22½p

UNILEX AUDIO MODULES

Build a stereo amplifier for as little as
£15.00. Send 25p for Mullard "Do It Yourself Stereo" booklet. All items in stock.

S-DeC BREADBOARD

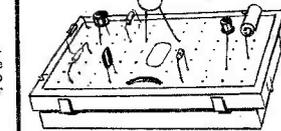

Solderless breadboard panels, for fast reliable component connections. Single DeCs. One S-DeC with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-DeC" giving construction details for a variety of circuits.

£1-00 P. & P. 17½p

4-DeC KIT. Four S-DeCs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user.

£3-95 P. & P. 22½p

T-DeC KIT **£2-50** P. & P. 17½p

S-DeC STOR **£2-50** P. & P. 22½p

HI-FI CATALOGUE

100 pages fully illustrated with 8 Page F.A. section. All leading makes and accessories plus details of Budget Stereo systems.

25p P. & P. 5p

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS
TYPE SW.100
 100 x 80 mm.

50μA	\$3.47	20V. D.C. ...	\$2.97
50-0-50μA	\$3.37	50V. D.C. ...	\$2.97
100μA	\$3.37	300V. D.C. ...	\$2.97
100-0-100μA	\$3.25	1 amp. D.C. ...	\$2.97
500μA	\$3.19	5 amp. D.C. ...	\$2.97
1mA	\$2.97	300V. A.C. ...	\$2.97
		VU Meter. ...	\$3.75

BAKELITE PANEL METERS
TYPE S-80
 80 mm. square fronts

50μA	\$3.19	50V. D.C. ...	\$2.47
50-0-50μA	\$2.87	300V. D.C. ...	\$2.47
100μA	\$2.87	1 amp. D.C. ...	\$2.47
100-0-100μA	\$2.75	5 amp. D.C. ...	\$2.47
500μA	\$2.69	300V. A.C. ...	\$2.47
1mA	\$2.47	VU Meter. ...	\$3.75

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts.

50μA	\$3.60	50μA	\$2.80
50-0-50μA	\$3.10	100μA	\$2.80
100μA	\$3.10	500μA	\$2.80
100-0-100μA	\$3.10	1 amp. ...	\$2.80
500μA	\$2.87	5 amp. ...	\$2.80
500-0-500μA	\$2.80	15 amp. ...	\$2.80
1mA	\$2.60	30 amp. ...	\$2.80
1-0-1mA	\$2.60	50V. D.C. ...	\$2.80
5mA	\$2.60	100V. D.C. ...	\$2.80
10mA	\$2.60	15V. A.C. ...	\$2.80
50mA	\$2.60	300V. A.C. ...	\$2.80
1 amp. ...	\$2.60	5 Meter 1mA ...	\$2.80
5 amp. ...	\$2.60	VU Meter ...	\$3.75
		30 amp. A.C. ...	\$2.80

Type MR.52P. 2 1/2 in. square fronts.

50μA	\$3.10	10V. D.C. ...	\$2.80
50-0-50μA	\$2.80	20V. D.C. ...	\$2.80
100μA	\$2.80	50V. D.C. ...	\$2.80
100-0-100μA	\$2.87	300V. D.C. ...	\$2.80
500μA	\$2.25	15V. A.C. ...	\$2.80
1mA	\$2.00	300V. A.C. ...	\$2.80
5mA	\$2.00	5 Meter 1mA ...	\$2.10
10mA	\$2.00	VU Meter ...	\$3.10
50mA	\$2.00	5 amp. A.C. ...	\$2.00
100mA	\$2.00	10 amp. A.C. ...	\$2.00
500mA	\$2.00	20 amp. A.C. ...	\$2.00
1 amp. ...	\$2.00	30 amp. A.C. ...	\$2.00
5 amp. ...	\$2.00		

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts.

50μA	\$3.75	10V. D.C. ...	\$2.10
50-0-50μA	\$2.75	20V. D.C. ...	\$2.10
100μA	\$2.75	50V. D.C. ...	\$2.10
100-0-100μA	\$2.60	300V. D.C. ...	\$2.10
500μA	\$2.37	15V. A.C. ...	\$2.10
500-0-500μA	\$2.10	50V. A.C. ...	\$2.10
1mA	\$2.10	100V. A.C. ...	\$2.10
5mA	\$2.10	300V. A.C. ...	\$2.10
10mA	\$2.10	5 Meter 1mA ...	\$2.37
50mA	\$2.10	VU Meter. ...	\$3.37
1 amp. ...	\$2.10	50mA A.C. ...	\$2.10
5 amp. ...	\$2.10	100mA A.C. ...	\$2.10
10 amp. ...	\$2.10	200mA A.C. ...	\$2.10
20 amp. ...	\$2.10	500mA A.C. ...	\$2.10
30 amp. ...	\$2.10	1 amp. A.C. ...	\$2.10
50 amp. ...	\$2.10	20 amp. A.C. ...	\$2.10
5V. D.C. ...	\$2.10	30 amp. A.C. ...	\$2.10

***MOVING IRON— ALL OTHERS MOVING COIL**
 Please add postage

SEW EDUCATIONAL METERS



Type ED.107. Size overall 100mm x 90mm x 108mm.
 A new range of high quality moving coil instruments ideal in school experiments and other bench applications. 3" mirror scale. The easily accessible to demonstrate internal working. Available in the following ranges:

50μA	\$4.50	20V d.c. ...	\$3.97
100μA	\$4.25	50V d.c. ...	\$3.97
1mA	\$3.97	300V d.c. ...	\$3.97
50-0-50μA	\$4.25		
1-0-1mA	\$3.97	Dual range	
1A d.c. ...	\$3.97	500mA/5A d.c.	\$4.25
10V d.c. ...	\$3.97	5V/50V d.c.	\$4.25

Type MR.85P. 1 1/2 in. square fronts.

200mA	\$1.37	50μA	\$2.00
300mA	\$1.37	50-0-50μA	\$1.87
500mA	\$1.37	100μA	\$1.87
750mA	\$1.37	100-0-100μA	\$1.75
1 amp. ...	\$1.37	200μA	\$1.50
2 amp. ...	\$1.37	500μA	\$1.50
5 amp. ...	\$1.37	500-0-500μA	\$1.37
10 amp. ...	\$1.37	1mA	\$1.37
3V. D.C. ...	\$1.37	1-0-1mA	\$1.37
10V. D.C. ...	\$1.37	5mA	\$1.37
15V. D.C. ...	\$1.37	10mA	\$1.37
20V. D.C. ...	\$1.37	20mA	\$1.37
100V. D.C. ...	\$1.37	50mA	\$1.37
150V. D.C. ...	\$1.37	100mA	\$1.37
300V. D.C. ...	\$1.37	150mA	\$1.37
500V. D.C. ...	\$1.37	150μA	\$1.37
750V. D.C. ...	\$1.37		
15V. A.C. ...	\$1.37		
30V. A.C. ...	\$1.37		
150V. A.C. ...	\$1.37		
300V. A.C. ...	\$1.37		
500V. A.C. ...	\$1.37		
8 Meter 1mA ...	\$1.40		
VU Meter. ...	\$2.10		

Type MR.45P. 2 in. square fronts.

50μA	\$2.25	5 amp. ...	\$1.50
50-0-50μA	\$2.10	10V. D.C. ...	\$1.50
100μA	\$2.10	20V. D.C. ...	\$1.50
100-0-100μA	\$1.87	50V. D.C. ...	\$1.50
200μA	\$1.87	300V. D.C. ...	\$1.50
500μA	\$1.60	15V. A.C. ...	\$1.50
500-0-500μA	\$1.50	300V. A.C. ...	\$1.50
1mA	\$1.50	5 Meter 1mA ...	\$1.87
5mA	\$1.50	VU Meter. ...	\$2.25
10mA	\$1.50	1 amp. A.C. ...	\$1.50
50mA	\$1.50	5 amp. A.C. ...	\$1.50
100mA	\$1.50	10 amp. A.C. ...	\$1.50
500mA	\$1.50	20 amp. A.C. ...	\$1.50
1 amp. ...	\$1.50	30 amp. A.C. ...	\$1.50

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts.

500mA	\$1.75	25μA	\$3.50
1 amp. ...	\$1.75	50μA	\$3.25
5 amp. ...	\$1.75	50-0-50μA	\$2.25
15 amp. ...	\$1.75	100μA	\$2.25
30 amp. ...	\$1.75	100-0-100μA	\$2.25
50 amp. ...	\$1.75	500μA	\$2.10
5V. D.C. ...	\$1.75	1mA	\$1.75
10V. D.C. ...	\$1.75	1-0-1mA	\$1.75
20V. D.C. ...	\$1.75	5mA	\$1.75
50V. D.C. ...	\$1.75	10mA	\$1.75
150V. D.C. ...	\$1.75	50mA	\$1.75
300V. D.C. ...	\$1.75	100mA	\$1.75
30V. A.C. ...	\$1.75		
50V. A.C. ...	\$1.75		
150V. A.C. ...	\$1.75		
300V. A.C. ...	\$1.75		
500mA A.C. ...	\$1.75		
1 amp. A.C. ...	\$1.75		
5 amp. A.C. ...	\$1.75		
10 amp. A.C. ...	\$1.75		
20 amp. A.C. ...	\$1.75		
30 amp. A.C. ...	\$1.75		
50 amp. A.C. ...	\$1.75		
VU Meter. ...	\$2.10		

EDGWISE METERS

Type PE.70. 8 1/2 in. x 1 1/2 in. x 1 1/2 in. deep.

50μA	\$3.00	500μA	\$2.60
50-0-50μA	\$2.87	1mA	\$2.37
100μA	\$2.87	10mA	\$2.37
100-0-100μA	\$2.75	50mA	\$2.37
200μA	\$2.75	100mA	\$2.37
		VU Meter. ...	\$3.25

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

MULTIMETERS for EVERY purpose!



TECH PT-24. 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/100/500mA. D.C. 0/100K. \$1.97.
 P. & P. 124p

HONOR TE.10A. 20K Ω/Volt 5/25/50/250/500/2,500 V. D.C. 10/50/100/500/1,000 V. A.C. 0/50mA/2.5mA/250mA. D.C. 0/8K/6 meg. ohm. -20 to +22 db. 10-0. 100 mfd. 0.100-0.1 mid. \$3.47.
 P. & P. 15p.



MODEL TE-200. 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000 V.D.C. 0/10/50/250/1,000 V.A.C. 0/50 uA/250 mA. 0/60K/6 meg Ω. -20 to +62 db. \$3.75.
 P. & P. 10p.

MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection. 0/5/15/60/300/600/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/80uA/8mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm -20 to +63 db. \$5.97. P. & P. 15p.



MODEL TE-70. 30,000 O.P.V. 0/3/15/60/300/600/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/50mA/3/50mA. 0/15K/150K/1.5M/16 Meg Ω. \$5.50. P. & P. 15p.

TMK MODEL MD.120 Mirror scale. 20K/Volt D.C. 10K Ω/Volt A.C. 30/60/300/600/3,000 V. D.C. 6/120/1,200 V. A.C. Current 0-60mA/0-1 1/4 300mA. 0-60K/0-8 Mohms -20 to +63 db. \$4.62. P & P 15p



MODEL TE-12 30,000 O.P.V. 0/0.6/30/150/600/1,200/3,000/6,000V. D.C. 0/6/30/120/600/1,200V. A.C. 0/60uA/6/60/600mA. 0/8K/800K/6Meg/60 Meg Ω 50pF. 0.2Mfd. \$5.97. P. & P. 174p.

MODEL TE-90 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200 V. D.C. 0/6/30/120/300/1,200 V. D.C. 0.3/6/60/600mA. D.C. 10K/100K/1/616 MEG Ω. -20 to +63 db. \$7.50. P. & P. 15p.



MODEL FL438 20K Ω/Volt D.C. 3k Ω/Volt A.C. Mirror scale. 0-6/3/120/120/600V D.C. 3/30/120/600V A.C. 50/600mA/60/600mA/60/600mA/10/100uA/500mA. 12 amp. D.C. 0.2Mfd. \$6.75. P. & P. 124p

SKYWOOD SW-500 50K Ω/Volt. Mirror scale. DC Volts 0.6/3/12/30/600/600. DC Current 20mA/8/600mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +67 db. \$7.50. P. & P. 15p.



MODEL 500 30,000 O.P.V. with overload protection. mirror scale 0/5/25/10/25/100/250/500/1,000V. D.C. 1/2-5/10/25/100/250/500/1,000V. A.C. 0/50uA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg/60 Meg Ω. \$8.74. Post paid.

MODEL AS-100D. 100K Ω/Volt. 6in. mirror scale. Built-in meter protection 0/3/15/60/120/300/600/1,200 V. D.C. 0/6/30/120/300/600 V. A.C. 0/10uA/6/60/300mA/12 Amp. 0/2K/200K/2M/200M Ω. -20 to +17 db. \$12.50. P. & P. 174p.



TMK MODEL TW-200C FEATURES RESETTABLE OVERLOAD BUTTON. Sensitivity: 20K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-4K, 50K, 0-500K, 5 MEG Ω. Decibels: -20 to +52 db. \$11.50. P. & P. 174p.

TE-900 20,000 Ω/VOLT GIANT MULTIMETER. Mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 V. A.C. 0/25/12.5/10/50/250/1,000/5,000 V. D.C. 0/90uA/110/100/500mA/10 amp. D.C. 0.2K/200K/30 MEG. OHM. \$15. P. & P. 25p.



TMK LAB TESTER. 100,000 O.P.V. 6in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω/Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000 V. A.C. Volts: 3, 1.5, 50, 50, 250, 500, 1,000V. D.C. Current: 10, 100mA, 10, 100, 500mA, 2.5, 10 100 MEG Ω. Decibels: -10 to 49 db. Plastic Case with Carrying Handle. Size 7 1/2 in. x 6 1/2 in. x 3 1/2 in. \$13.90. P. & P. 25p.

FC-401 TRANSISTOR TESTER
 Full capabilities for measuring A, B and 100. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. \$8.97. P. & P. 15p.



270° WIDE ANGLE 1mA METERS
 MW1-6 60mm square \$3.97
 MW1-8 80mm square \$4.97
 P. & P. extra

HONEYWELL DIGITAL VOLTMETER VT.100
 Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2 ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999) Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2 in. x 2 1/2 in. x 3 1/2 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE \$49.97 1/2 Carr. 50p.



TE-40 HIGH SENSITIVITY A.C. VOLTMETER
 10 meg. input 10 ranges: 0/1/008/1/3/13/10/30/100/300V. R.M.S. 4cps.-12 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. \$17.50. Carr. 25p.



TE-65 VALVE VOLTMETER
 High quality instrument with 28 ranges. D.C. volts 1-5-1,500V. A.C. volts 1-5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe

SEMI-CONDUCTORS/VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors		2N3415		2N5458		2N5459		2N5460		2N6273		2N	
-------------	--	--------	--	--------	--	--------	--	--------	--	----	--

HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE
SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!

RECORD DECKS

- B.S.E.**
 Mini Mono† \$4.97
 CI29* \$6.97
 MP60 \$11.95
 610 \$15.90
 510 \$13.95
 810 \$10.95
 MP60 T.P.D.I. \$19.50
 MP60 T.P.D.2 \$18.25
 10 T.P.D.1 \$22.97
 510 T.P.D.I. \$20.97
 210 Package* \$11.75
 H.T.70 \$17.25
 H.T.70 Package \$24.97
- THORENS**
 TD125 \$64.95
 TD125AB \$99.97
 TX25 \$6.95
 TD150AH \$39.50
 TD150AB† \$42.95
 TX11 \$3.92



- GARRARD**
 A40 II* \$8.40
 2025 T/C* \$9.87
 3000* \$10.50
 SP25 III \$11.75
 A70 II \$11.97
 SL65B \$14.97
 AP76 \$20.97
 SL72B \$26.00
 SL75B \$28.50
 SL95B \$38.50
 401 \$29.50
- GOLDRING**
 GL69/2 \$29.20
 GL69P/2 \$29.50
 GL75 \$29.97
 GL75P \$39.97
 LD69/75 \$3.40
 G99 \$21.97
- PIONEER**
 PL12AC \$37.92

† Mono * Stereo Cartridge
 All other models less Cartridge
 Carriage 50p extra any model.

RECORD DECK PACKAGES

- Decks supplied ready wired in plinth and cover fitted with cartridge.
 Garrard 2025 T/C with Sonotone \$15.00
 Garrard SP25III Goldring G800... \$20.95
 Garrard AP76 Goldring G800... \$30.95
 BSR MP60 Audio Technica AT.55... \$21.00
 Goldring GL69/2 Goldring G800... \$39.00
 Goldring GL75 Goldring G800... \$47.50
 Goldring GL75 Goldring G800E... \$52.50
 Carriage 50p extra any model.



SINCLAIR EQUIPMENT

Project 60. Package offers.

2 x Z30 amplifier, stereo 60 pre-amp, P25 power supply. \$16.75 Carr. 37p. Or with P26 power supply \$18.85 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, P28 power supply. \$20.25 Carr. 37p.
 Transformer for P25. \$2.97 extra.
 Add to any of the above \$4.75 for active filter unit and £16 for a pair of Q16 speakers.
 Project 60 FM Tuner \$20.97. Carr. 37p.
 All other Sinclair products in stock.
 2000 Amp \$25.00 Carr. 37p. 3000 Amp \$35. Carr. 37p. Nectric Amp \$45.97 Carr. 37p.
 IC10/IC22 \$2.50



LATEST CATALOGUE



SEND NOW!
STILL ONLY 37 1/2 p
P & P 10p

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

NOTE! ALL SHOPS AND OFFICES CLOSED FOR ANNUAL HOLIDAYS AUGUST 2nd to AUGUST 14th. No goods will be despatched during this period—please order early.



TELETON SAQ-206 STEREO AMPLIFIER

Latest exciting release. Brand new model. 6 - 6 watts rms. Inputs for mag, atal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List \$22.50 OUR PRICE \$19.97 Carr. 37p.



TELETON SPECIAL OFFER!

CRIOI AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR SA1008 SPEAKER SYSTEMS. Output 4 watts per channel. Excellent reception, AFC, built-in MEX. Cer/XTAL Input. Total List \$55.25. OUR PRICE \$29.95. Carr. 62p.
 Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired \$48. Carr. £1.00.

★ TRANSISTORISED FM TUNER

TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6 x 4 x 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9 V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. \$6.37. P. & P. 12p. Stereo multiplex adaptors \$4.97.

MARCONI CT44/TF956 AF ABSORPTION WATTMETER

1watts to 6 watts \$20 Carr. £1.

BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Size 1 1/2 Hz to 100 KHz. Square 90 Hz to 20 KHz. Output max + 10 dB (10 K ohms). Operation 220/240V. A.C. Size 215mm x 150mm x 45mm. Price \$27.50. Carr. 25p.

MARCONI TF142E DISTORTION FACTOR METER

Excellent condition. Fully tested. \$20. Carr. 75p.

TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V A.C. Brand new with instruction. \$15. P. & P. 37p. S.A.E. for details.


TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20cs to 200 kc/s on 4 bands. Square: 20cs to 200 kc/s. Output impedance 5,000 ohms, 200/250V. A.C. Supplied brand new and guaranteed with instruction manual and leads. \$15.50. Carr. 37p.



TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

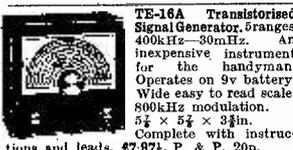A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 15Ω to 1 megΩ. G Ranges ± 1%. L 1 μH - 111 μH. C. 10pF to 1110nF. D. 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA Meter indication. Attractive 2 tone metal case. Size 7 1/4 x 5 x 2 in. \$20. P. & P. 25p




LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mF and 2 ohms 20 meg-ohms. Also checks impedance, turns ratio, insulation, 200/250V. A.C. Brand New \$17.50. Carr. 37p.

TO-3 PORTABLE OSCILLOSCOPE

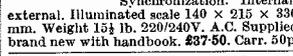3in. tube. Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 megΩ 25pF. X amp. sensitivity 0.9v p-p/CM. Bandwidth 1.5 cps-800KHz. Input imp. 2 megΩ 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronisation 10 MHz. external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. \$37.50. Carr. 50p.



RUSSIAN OC1-16 DOUBLE BEAM OSCILLOSCOPES

6 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from *2 sec to 100 mill sec/cm. Supplied complete with all accessories and instructions \$57. Carr. paid.

TE11, DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency a.c. to 200KHz (-3dB). Accuracy: ± 0.05dB. ± Indication dB ± 0.01. Maximum input less than 4W (50V). Built in 600Ω load resistance with internal/external switch. Brand new. \$27.50. P. & P. 25p.

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-600 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. \$15. Carr. 37p. Size 140 x 215 x 170 mm.

POWER RHEOSTATS


High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush. Continuous rating. Wide range extra stock. Single hole fixing, 1/4 in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 72p. P. & P. 7 1/2p. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, £1.05 P. & P. 7 1/2p. 100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms, £1.37 P. & P. 7 1/2p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery

S-260 General Purpose Bench Mounting		S-260B Panel Mounting	
1 Amp	\$5.50	1 Amp	\$5.50
2.5 Amp	\$6.75	2.5 Amp	\$6.62
5 Amp	\$9.75		
8 Amp	\$14.50		
10 Amp	\$18.50		
12 Amp	\$21.00		
20 Amp	\$37.00		

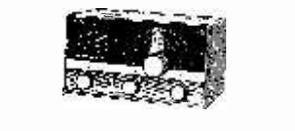Please add postage ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES. OUTPUT VARIABLE 0-260 VOLTS. Special discounts for quantity



UNR-30 RECEIVER
 4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 220/240V. A.C. Brand new with instructions. \$15.75. Carr. 37p.

WS62 TRANCEIVERS

Large quantity available for EXPORT! Excellent condition. Enquiries invited.

LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s, 550 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, S. Meter, Bandspread. RF Gain 15 x 97 x 84, 13 lbs. 220/240V. A.C. or 12V. D.C. Brand new with instructions. \$35. Carr. 50p.

FULL RANGE TRIO EQUIPMENT

CRYSTAL CALIBRATORS NO. 10

Small portable crystal controlled wavemeter. Size 7 x 7 x 4 in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300V, D.C. 15mA and 12V D.C. 0.3A. Excellent condition. \$4.47. Carr. 37p.

B.C. 221 FREQUENCY METERS

latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. \$27.50. Carr. 50p.

SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 20V-230V. Model MR 2305 5 amp 68 x 46 x 43mm \$8.37. \$11.97. Postage 12p.

AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

150 W.	\$2.37	P. & P. 17p
300 W.	\$2.25	P. & P. 23p
500 W.	\$4.97	P. & P. 29p
1000 W.	\$7.25	P. & P. 37p
1500 W.	\$9.97	P. & P. 42p
5000 W.	\$36.00	P. & P. £1

VOLTAGE STABILISER TRANSFORMERS

180-260V. input. Output 230V. Available 150w or 225w. \$12.50. Carr. 25p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots 240). Quantities available.

LARGE STOCKS OF TEST EQUIPMENT AND RECEIVERS—MARCONI ETC FOR CALLERS



G.W. SMITH & CO (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
 3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
 34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
 311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-6 MONDAY TO SATURDAY

All Mail Orders to—
 13-12, Paddington Goods, London W.2
 Tel. 01-262 6562 (Trade supplied)

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- C. & G. Electronic Servicing
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- Radio Operator Certificates
- General Certificate of Education, etc.

Now available Colour T.V. Servicing Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



**INTERNATIONAL
CORRESPONDENCE SCHOOLS**

EST. 1891

Dept. 171, Intertext House, Stewarts Road, London, S.W.8 4UJ
Please send me the ICS prospectus—free and without obligation.
(state Subject or Exam).....

NAME
(BLOCK CAPITALS PLEASE)

ADDRESS

.....

AGE..... OCCUPATION..... /71

INTERNATIONAL CORRESPONDENCE SCHOOLS

Selections from FELSTEAD ELECTRONICS' List

(Sent free for stamped addressed envelope to address below)
Transistors etc. AC126 12tp. AF116 20p. AF116 15p. AF117 20p. OA5 7tp. OA10 7tp. OA81 7tp. OA85 7tp. OC23 82tp. OC25 30p. OC26 37tp. OC28 42tp. OC35 42tp. OC44 14p. OC45 12tp. OC71 12tp. OC72 12tp. OC75 12tp. OC81 12tp. OC81D 12tp. OC82D 12tp. OC170 20p. OC171 12tp. Many more in list. S.D.R. BY100 800piv 14p. 6 amp series: BYZ13 800piv 20p. BYZ12 600piv 25p. BYZ11 900piv 30p. BYZ10 1200piv 35p. (Charges 6tp up to 11, paid for 12 and over). **Sub-Min Transistors:** OUTPUT 3Ω for OC73 etc.) 14p (up to 6, 6tp). **MULTIMETER.** Our famous 20000 Ω per V 54-62½ (15p). Details and other in list. **SOLDERING IRON.** Slim, modern, British highspeed 81", all parts replaceable, highest quality, full guarantee: £1-07½ (10p). **DIAMOND SYLLI** Replacements for BSR TCS/LP, TCS/S, TCS/LP/STEREO: COLLARO 'O' : RONTTE BF 40LP: Garrard GC2/LP and GC8/LP: ACOS GP65/67, all at 40p (6p). ACOS GP73, GP91: BSR ST4 (ST), ST5 (ST), ST6 (ST), SONOTONE STA, STA, STAHC: PHILIPS AG3306, 3067, 3068, 3069, 3301, 3302, 3304; Garrard GK25, GCM2, GC25, and many more 'Garrard' etc. types. All at 75p. (6p). All are of the very highest quality. **DOUBLE DIAMOND:** ST4 (ST), ST5; ST10 (ST), ST8; 9TA, 9TAHC, 3306, GP91 (For GP92, GP93, GP94 cartridges); GP91-SC for all GP91-SC Cartridges. All at £1-50 each (6p). **PICK-UP CARTRIDGES.** All Standard fittings and stylus. Mono GP67/2 80p. STEREO-COMPATIBLE (MONO) GP91/SC £1-10 STEREO GP93 £1-30 STEREO CERAMIC GP94 £1-25 SONOTONE STEREO 9TAHC (DIA.) £2-40. GOLDRING (G850 £4-87½, G800 £3-50, G800E £13-50, G800 SUPER B £19-50 (6p) all types or Res. Post. 22tp). **STYLII FOR ALL ABOVE TYPES,** including GOLDRING available. **RECORDING TAPE.** Still the finest quality British Mylar available: Standard 5" 600ft. 36p. 5½" 900ft. 50p. 7" 1200ft. 56p. LONG PLAY 5" 900ft. 50p. 5½" 1200ft. 56p. 7" 1800ft. 90p. (7tp on 5" and 5½", 9p on 7"). **MICROPHONES** Crystal Mic 91, hand/desk 81p. MIC45. Curved metal hand-grip £1-00. CM21 Grey hand desk 62tp. Slock 600 £1-02½. CM70 "Planet" machined metal tapered stick type with neck cord, adaptor to fit floor stands £1-47½ (all 9p). LABEL (or hand) with clip 82tp (6p). All are fitted with leads. **DYNAMIC MS10 50K Ω** for desk, tapered with base and slide-out adaptor £1-97½. MS11. Similar, but fixed on swivel swan neck to switch-fitted base, £2-22½ (Either 15p). **Type 208 Cardioid** ball, 50K/600 Ω, omni-dir., built-in vol. control, on/off switch, special lead, handle (as good as money can buy) £6-80. UD130 Uni-Dir. Ball, mesh, 50K/600 Ω, Adap. cable, jack plug £4-20. (20p). DM160. omni-dir., Ball, 50K Cable adaptor £3-87½ (call us 87tp). **MICROPHONE INSERTS.** Dia. 1½" OR 0-0" either size 87tp (6p). **SPEAKERS** with 2in. and min. jack plug (2-5 or 3-5 mm., state which). **Magnetic 9p Crystal (3.5 only) 24p** (Up to 3 for 6p on any). **HEADPHONES** De-luxe STEREO 8-16 Ohms £2-47½. Same, fitted vol. control each earpiece £4-20. Both have lead and stereo jack plug (17tp.) High Res. 2000 ohm. Adjustable 82tp (7tp). **SPEAKERS** 12" ROUND fitted tweeter, 3 or 15 Ω (state which) £1-87½ (27tp) or for Stereo £4-25 pair, carr. paid 2½" 3 OR 3 Ω (state which) 87tp (6p). **EMI 12V X 3"** 3, 4 or 1.5 Ω (state which) £2-12½ (25p) LW with two tweeters and crossover network 15 Ω £3-75 (25p). **VIBRATORS.** 12V 4-pin non-synch. 121HD4, 24" ex. priv. 27tp. 12V 7-pin Synch. (12SR7) 62tp. (Both types 6tp per vibrator). **CONNECTING WIRE.** Packs of 5 coils asstd. cols. ea. coil 5yds. Solid core 14p (6p). Flexible 16p (7tp). Super thin for transistor wiring 16p (6p). **PICK-UP WIRE.** Super thin twin flex, screened and sheathed 6p yd. (6p up to 6yds.—over free). **RETRACTABLE Flex. Leads.** (Curries) Phonoplug each end 12ft. 30p. 6ft. phone plug/phone socket other end 25p. 12ft. 42tp (6p per lead all types). SEND S.A.E. for full free lists.—Small 3W and 7W trans. amplifiers, Electrolytics, Vol. Controls, all types of Radio switches, car and portable expanding aerials, Meters, Test prods. all types of Brit. and Cont. standard and min. plugs and sockets SDR's, Thyristors, cros. clips (various) terminals, etc. etc. and "Special Offer" lines at lowest possible prices.

FELSTEAD ELECTRONICS (PW 47)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE
 Cash with order only. No COD or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p excluding postage, unacceptable. SAE please for enquiries or cannot be replied to. Charges apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).

FANTASTIC BARGAIN OFFER! TRANSEUROPEAN

Transistorised Stereophonic High Fidelity
AM/FM Tuner Amplifier System.



This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM, Medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in. matching elliptical speakers. A complete Hi-Fi Stereo Radiogram at less than half normal price.

SPECIAL OFFER

Easily fitted no technical knowledge necessary.

£44

Credit Terms available. First monthly payment of £5-83 followed by 9 monthly payments of £4-95. Total Credit Sale Price £49-50. Send £5-83 today.



P. & P. 88p

FABULOUS VALUE

Transistorised Stereo Hi-Fi Record Player
 Build your own Hi-Fi Record Player with the Serenade fully transistorised amplifier which comes complete with 2-10in. x 6in. speakers and the latest 4 Speed BSR Speed Stereo/Mono Record Changer.

£30 P. & P. 88p
 Credit terms 1st monthly payment £2-46 followed by 9 monthly payments of £3-38 (Total c/s price £33-80). Send £2-46 today.

EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.

Post coupon NOW for **FREE** leaflets

PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name P8/71
 Address

LEWIS radio 100, Chase Side London N.14
 Tel: 01-886 3733/9666

Your
STARTER QUESTION is


"What is today's
most useful electronics
catalogue?"



... and your
BONUS QUESTION is

"What goes up
and at the same
time comes down?"

The answer to the Starter question is obvious—the ubiquitous HOME RADIO COMPONENTS CATALOGUE. You all got that right! And the answer to the Bonus question is—the same! May we explain "this most ingenious paradox?" The price is now 50 pence, but with each catalogue we now include 10 vouchers each worth 5 pence, when used as directed. This means that if you spend a quite modest sum in ordering components from us over a period the catalogue will have cost you *nothing*—bar 20 pence for post and packing. So then—for today's most useful electronics catalogue, 50p if you call and collect, or 70p if you send the coupon with a cheque or Postal Order. Join the winning team—*act now!*

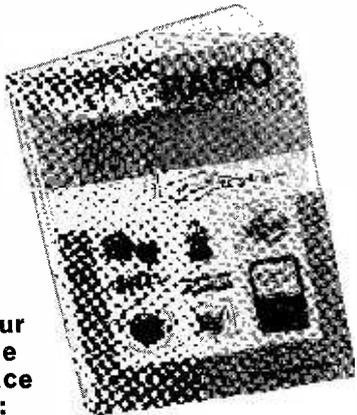

24-hour
Phone
Service
Ring:
01-648 8422

POST THIS
COUPON
with your
cheque or
postal
order for
70 pence



Please write Name and Address in block capitals.

Name

Address



HOME RADIO (Components) LTD.
Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
THE VALVE SPECIALISTS Telephone 01-722-9090

0A2	30	6P13	.38	10F9	.45	30C15	.62	DF39	.37	ECC85	.27	EM87	.32	PC885	.49	PL505	1.44	UF85	.34	AC156	.20	BF159	.25	0A200	.09	
0B2	30	6P14	.44	10F18	.36	30C17	.79	DF91	.14	ECC88	.40	EM87	.32	PC885	.49	PL508	1.16	UF86	.63	AC157	.25	BF163	.30	0A202	.10	
1A7GT	33	6F18	.45	10LD11	.33	30C18	.63	DF96	.35	ECC88	.35	EM87	.32	PC885	.49	PL509	1.44	UF89	.30	AC166	.25	BF173	.38	OC22	.38	
1H5GT	33	6F23	.60	10P13	.69	30F5	.72	DF97	.63	ECC189	.48	EM87	.32	PC885	.49	PL802	.75	UL41	.59	AC188	.35	BF180	.30	OC23	.38	
1L4	.13	6F24	.68	10P14	1.10	30FL1	.62	DE63	.30	ECC804	.67	EM87	.32	PC885	.49	PM84	.38	UL84	.32	AC178	.55	BF181	.40	OC24	.38	
1N5GT	.37	6F25	.60	10P18	.82	30FL2	.75	DE76	.28	ECC8071.35		EM87	.32	PC885	.49	PC900	.35	UL84	.32	AC178	.55	BF181	.40	OC24	.38	
1R5	.27	6F28	.70	12A6	.68	30FL12	.71	DE77	.20	ECC808	.28	EM87	.32	PC885	.49	PC900	.35	UL84	.32	AC178	.55	BF181	.40	OC24	.38	
1S4	.24	6F60GT	.15	12AC6	.40	30FL14	.70	DK40	.58	ECC87	.62	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC177	.25	BF185	.41	OC25	.38	
1S5	.20	6F60	.19	12AD6	.40	30L1	.31	DK92	.41	ECC86	.65	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
1U4	.29	6J5GT	.29	12AE6	.48	30L15	.60	DK96	.36	ECC8042.10		EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
1U5	.48	6J6	.18	12AT6	.23	30L17	.71	DL96	.36	ECH21	.63	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
2D21	.35	6J7G	.24	12AT7	.17	30P4MR	.98	DM70	.38	ECH42	.62	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
3D6	.19	6J7GT	.38	12AU6	.22	30P12	.69	DM71	.38	ECH81	.28	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
3Q4	.33	6K7G	.10	12AU7	.20	30P19	.60	DM71	.38	ECH81	.28	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
3Q5GT	.35	6K7GT	.23	12AV6	.23	30P19	.60	DM71	.38	ECH81	.28	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
3S4	.27	6K8	.18	12AX7	.33	30P11	.61	DM74	.38	ECH82	.31	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
3V4	.32	6L6GT	.89	12BA6	.30	30P112	.33	500	.33	ECL82	.31	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
5V4G	.36	6L7GT	.63	12BE6	.30	30P113	.78	DY86/7	.26	ECL83	.62	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
5Y3GT	.28	6L18	.45	12BH7	.40	30P114	.67	DY802	.48	ECL84	.58	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
5Z4G	.35	6L19	1.38	12EL1	.85	30P115	.89	E80F	1.20	ECL85	.55	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6R0L2	.57	6D120	.45	12G7GT	.33	35L6GT	.42	E80F	1.20	ECL86	.27	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6ASG	.33	6N7GT	.40	12K5	.50	35W4	.23	E88CC	.60	EF22	.63	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6AC7	.15	6Q7	.43	12K7GT	.34	35Z4GT	.24	E180F	.95	EF36	.38	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6AG5	.25	6Q7G	.30	12Q7GT	.28	35Z5GT	.30	E182CC1.13		EF37A	.35	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6AR5	.25	6R7	.55	12SA7GT	.50	50L6GT	.45	E1148	.53	EF39	.40	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6AL5	.11	6R7G	.35			70	.22	EA50	.18	EF40	.50	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6AQ5	.25	6RA7GT	.35	12SC7	.35	85A2	.48	EAT6	.38	EF41	.50	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6AT8	.20	6SA7M	.35	12SG7	.28	807	.59	EABC80	.31	EF42	.33	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6AV6	.81	6SC7GT	.33	12SH7	.15	8753	.50	EAC91	.38	EF54	.98	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6B8G	.30	6SG7GT	.33	12SJ7	.22	AC2/PEN		EAF42	.49	EF80	.23	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6B9G	.18	6SH7	.53	12SK7	.24		.98	EB34	.20	EF83	.48	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6BA6	.21	6SJ7	.35	12SQ7GT		AC2/PEN		EB91	.11	EF85	.23	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6BB6	.22	6SK7GT	.28	12SC7	.35	85A2	.48	EB41	.48	EF86	.31	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6BT6	.20	6SA7M	.35	12SG7	.28	1.15	AC2/PEN	.38	EB8C81	.33	EF89	.24	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38
6BV6	.41	6V6G	.17	19A0G5	.24	AC/PEN(7)		EB9C1	.30	EF91	.17	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6BQ7A	.38	6V6GT	.31	20F2	.68		.98	EBF80	.32	EF92	.13	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6BR7	.79	6X4	.22	20L1	.98	AC/TH1	.98	EBF83	.40	EF97	.55	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6BR8	.63	6X5GT	.25	20P1	.88	AC/TP	.98	EBF89	.30	EF98	.60	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6BW6	.72	7A7	.58	20P3	.84	AL60	.78	EBL21	.60	EF182	.27	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6BW7	.57	7B6	.53	20P4	.91	ATP4	.19	ECS6	.63	EF184	.30	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6CB6	.73	7C5	.30	20E1	1.00	AZ1	.40	ECS8	.80	EH90	.38	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6CD6	.25	6Z6GT	.40	20E6G	.29	AZ31	.46	EC92	.35	EL32	.18	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6C8G	1.09	7H7	.28	25L6G	.22	AZ41	.63	ECC92	1.58	EL34	.46	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6CH6	.38	7R7	.65	25Y5	.33	B36	.38	ECC33	1.58	EL35	1.00	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6CL6	.63	7Z4	.50	25Y5G	.43	CY1C	.58	ECC40	.60	EL37	.64	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6CW4	.63	9D7	.78	25Z4G	.30	CY31	.32	ECC81	.23	EL41	.54	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
9F1	.68	10C1	1.25	25Z6	.40	DAC52	.38	ECC82	.20	EL42	.58	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6F6	.68	10C2	.50	25Z6G	.43	DAF91	.20	ECC83	.23	EL51	.50	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	
6F6G	.25	10F1	.76	30C1	.28	DAF96	.35	ECC84	.30	EL53	.38	EM87	.32	PC885	.49	PK25	1.16	UY1N	.50	AC178	.25	BF185	.41	OC25	.38	

All valves are unused, boxed, and subject to the standard 90 day guarantee. Terms of business—Cash or cheque with order only. Post/packing 0.02 per item, subject to a minimum of 0.09. Orders over 5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit or only 0.03 extra per order. Complete catalogue with conditions of sale price 0.07 post paid. Business hours Mon-Fri, 9-5.30 p.m. Sat, 9-1 p.m. We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 8½p per word (minimum 12 words), box number 7½p extra. Semi-displayed setting £6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

Miscellaneous

BUILD IT in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond Surrey.

TOP TRANSISTORS

Unmarked but brand new and individually tested. We will refund your money and postage in full if any of our transistors are found to be faulty. All at 9p each or

Any 12 transistors for only £1

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee. P. & P. 10p.

J. M. KING (I)

17 Buckridge, Portpool Lane, London, E.C.1

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.20 NOW

TO: 'BOFFIN PROJECTS'
DEPT. KW2010
4 CUNCLIFFE ROAD
STONELEIGH, EWELL, SURREY

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 2½p stamp.

RECORD TV SOUND using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p + 10p P&P. CROWBOROUGH ELECTRONICS (P.W.), Eridge Road, Crowborough, Sussex.

Miscellaneous

ETCH YOUR OWN P.C.B.

High quality printed circuit boards can be produced using a procedure employed in development laboratories for prototype construction. A kit of boards, etchant, adhesive resist pads and tape with full instructions is obtainable for £1.90 post free from:

INTEK ELECTRONICS LTD.,
4 Lowfield Lane, Hoddesdon, Herts.

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, Ideal for Caravan, Tent, Emergency Lighting etc. Fully Transistorised, Low Battery Drain, With ON/OFF Switch and 12v Socket to Run other Lights or 12V Equipment.

Unbeatable at **£3.30** post paid
or in kit form **£2.90**

4 WATT GRAM AMPS.

Volume and tone controls, mains operation. 3Ω output, new and boxed **£3.63** POST PAID

SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire S.A.E. for lists

BARGAINS. P.S.U.s, test gear, lists, S.A.E. Don Smith, 12 Channel Heights, Weston super Mare, Somerset.

IRISH READERS. Eagle products available, send 10p in stamps for latest illustrated catalogue to Toner Electronics, Lismore Park, Waterford.

AE 396

PICK-UP CONVERSION KIT

To replace E.M.I. Double 'C' cartridge, comprising pick up head shell, turn-over holder and dual sapphire cartridge. Mono only. Full D.I.Y. instructions supplied.

£3.72

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

R. D. I. LTD.,
Chilton Works, Garden Road,
Richmond, Surrey.

ENGINEERING SERVICE for constructors. Lathe work, milling, sheet metal, castings, etc. S.A.E. for details. Chelmsford Machine Tool Company, P.O. Box 55, Chelmsford CM1 2AU.

Miscellaneous

JOHN SAYS...

RING MODULATOR by Dewtron is professional, transformerless, 5-transistor, has adjustable F/I/F2 rejection. Module £7. Unit £8.90. WAA-WAA Pedal kit of all parts, incl. all mechanics & instr. Only £2.45. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, foxtrot etc. costs £16.55 in modules. **ORGAN PERCUSSION** and other fascinating effects. Send 15p for illust. list. D.E.W. Ltd., 254 Ringwood Road, Farndown, Dorset.

We stock all those components and materials required by the home HI-FI constructor, including speaker grille fabrics, BAF wadding, speaker kits, cabinets, cross-over networks, inductors, etc. AT TOP DISCOUNTS. Price list free of charge. Send 2 x 3p stamps for pattern card of speaker grille fabrics. Mail order ONLY. No callers please.

AUDIOSCAN Dept. PW8
4, PRINCES SQUARE,
HARRGATE, YORKS.

17 BBC/ITV TELEVISIONS £5

Working Perfectly
plus P&P £1 CWO.

SUITABLE FOR ANY AREA

3 Channel 19in D/S TVs. ITV, BBC 1, BBC 2, £25 inc. carriage. 17in 13 Channel, complete but untested £1.50 each, plus £1 P&P. CWO.

SPEAKERS

6in x 4in, 7in x 4in 3OHM
20p plus 8p P&P each. CWO.

Regular deliveries throughout England and N. Ireland.

TRADE TV's

407 Thornton Road, Gillingham, Bradford 8, Yorks.

DAILY UFO Flight Patterns, 37½p. UFO Map, S. England, 37½p. TV Notes UFO Detection, 2 Optical Circuits, 50p. UFO Wave pattern and prediction, 45p. Radar & Electronic Publications, "Highlands," Needham Market, Suffolk.

Wanted

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S WIRELESS STORES, 55 Worcester Street, Wolverhampton.

WE BUY New Valves and Transistors. State price: A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

HIGHEST POSSIBLE CASH PRICES for Revox, Ferragraph, Brenell, Vortexion, Tandberg. 9.30-5.00. 01-472 2185.

Queen's Award to Industry

A PROUD DAY FOR REDIFON

THE Queen's Award to Industry for 1970 was formally presented to Redifon Limited and Redifon Air Trainers Limited on June 8 by Field Marshal Sir Gerald Templer, Her Majesty's Lieutenant for Greater London.

New marine radio telephone

MARINE Division has introduced a new SSB radio-telephone for operation in the marine 2 MHz band. It is designed to satisfy all current and future international regulations covering the phasing out of DSB transmissions, and to meet type approval

TEST ENGINEERS

£1248-£1749+

Continuing expansion means we need more test engineers with the practical experience and real technical knowledge to work on the alignment and testing of HF and VHF equipment.

Theoretical and practical experience of semi conductors, SSB and frequency synthesis will be a great advantage.

Age is not important, since initial earnings will be directly related to experience.

You could start at £1248, but for more senior personnel this could be in excess of £1749

Benefits include Pension, Life Assurance, 3 weeks holiday. Ring or write with brief details to: Norman Manion, REDIFON LIMITED, Broomhill Road, Wandsworth, London SW18. 01-874 7281

REDIFON 

A Member Company of the Redifusion Organisation



Redifon

REDIFON LTD. has won an order from Cable and Wireless to supply radio transmitting and receiving equipment for a new ground-to-air service in the Seychelles, where an airport is under construction for the first regular air service to the islands by land-based aircraft. Valued at over £25,000, contract also includes the provision of transmitters for a radio beacon which, while operating in the aeronautical

A NEW MILITARY RADIO STATION

A NEW 100 watt SSB (single sideband) military radio station, developed by the Communications Division is now in quantity production and delivery of an order valued at £156,000 for the Royal Air Force has already been completed.

Wanted

TOP PRICES PAID for NEW VALVES
popular T.V. and Radio types.
KENSINGTON SUPPLIES (C).
367 Kensington Street, Bradford 8,
Yorkshire.

CASH PAID for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

NEWNES R. & T. Servicing, 1963-64, 1964-65. Also Valve Tester. Cash, 4 Cavendish Place, Bath.

For Sale

MORSE MADE !! EASY !!

FACT NOT FICTION If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 15 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to:

G3850 (Box 19), 45 GREEN LANE, FURLEY, SURREY

YUKAN SELF-SPRAY 250ml (8.8 FL. OZ.)

Get those **GREY HAMMERS** OR **BLACK WRINKLE** (CRACKLE) finishes

Yukan Aerosol spraykit contains 455g. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue Modern Eggshell Black Wrinkle (Crackle) all at 65p at our counter or 90p. carriage paid. per push-button self-spray can. Also Durable, heat and water resistant Black Heat finish (309g. self-spray can only) 75p carriage paid.

SPECIAL OFFERS: 1 can plus optional transferable snap-on trigger handle Valve 250ml or 450p. carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

Dept. 27 YUKAN, 307A, EDGWARE ROAD, LONDON, W2 1BN

We supply many Government, Department, Municipal Authorities, Inns, Tires and Leading Industrial Organisations—We can supply you too. Open all day Saturday. Closed Thursday afternoons.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

AUSTRALIAN READERS! SEND S.A.E. FOR ELECTRONICS CATALOGUE. HOBIFAK, P.O. Box 224, Carlton South, 3053, Victoria, Australia.

PYE Mobile Radio Equipment. 3302 Base Station. 2 mobile type 2102. 1 Dash mounted mobile. Aerial. Mast. Best offer secures. Bormford, Allesborough, Pershore, Worcs.

Metal Work

METAL WORK: All types cabinets, chassis, racks, etc., to your specifications. **PHILPOTTS METAL WORKS LTD.**, Chapman Street, Loughborough.

Service Sheets

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

RADIO, TELEVISION over 3,000 models. **JOHN GILBERT TELEVISION**, 1b Shepherds Bush Rd., London W.6. SHE 8441.

Service Sheets (continued)

Service Sheets & Manuals

LARGE RANGE OF MODELS AVAILABLE FOR RADIO, TELEVISION, TAPE RECORDERS, R/PLAYERS, ETC. FROM 25p EACH — S.A.E. WITH ENQUIRIES PLEASE — 1971 LISTS ARE AVAILABLE 13p.

MULLARD TRANSISTOR AUDIO AND RADIO CIRCUITS	PRICE £1-63p	} Post free
T.V. FAULT FINDING BOOK by DATA PUBLICATIONS LTD.	55p	
MULLARD VALVE & SEMI CONDUCTOR DATA BOOK	23p	
MAZDA VALVE & PICTURE TUBE DATA BOOKLET	23p	
BRIMAR VALVES & TELE TUBE DATA LIST	20p	
RESISTOR COLOUR CODE INDICATOR DISC	13p	

Sets of Brand New Valves supplied for most makes of Radio / T.V. etc. Prices on request.

BELL'S TELEVISION SERVICES
Albert Place Harrogate Yorkshire Tel 0453-86844

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each, Manuals from 50p.
"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS" Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

TRADER SERVICE SHEETS

30p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES

LIMITED

29 CHURCH ROAD,
TUNBRIDGE WELLS, KENT

Make	Model	Radio/TV

1971 List now available at 10p, plus postage

If list is required indicate with X

From

Address

enclose remittance of

(and a stamped addressed envelope) s.a.e. with enquiries please

MAIL ORDER ONLY (February PW)

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex.

SERVICE SHEETS. TV, Radio, etc., 25p. Large stocks. S.A.E. with enquiries please, callers welcome. K. L. Bower, 55 Briarwood Drive, Wibsey, Bradford.

Ladders

VARNISHED TIMBER LADDERS from manufacturer. Lowest prices anywhere. 15½ ft. extd. £6-20, 17ft. ext. £6-50, 20ft. ext. £7, 21½ ft. ext. £7-75, 24½ ft. ext. £8-90, 29ft. ext. £10-25, 31½ ft. triple ext. £12-25, 36ft. triple ext. £16. Carr. 80p. Free lists. Also Aluminium Ext. & Loft Ladders. Callers welcome.—(Dept. W.L.S.) Home Sales, Baldwin Road, Stourport, Worcs. Phone 02-993 2574/5222. Placing order on C.O.D.

Educational

YOUNG MEN (AND WOMEN) trained as Radio Officers on liners and other ships. Salaries rising to £2,500 per year (all found), immediate vacancies. Grants available for Day full-time course. For details of training write to:

THE RADIO COLLEGE,

91 Lancaster Road, Preston, Lancs. stating if interested in Day or Postal Course.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON. SW8

R.T.E.B. Certs., City & Guilds. Colour TV, Radio, Computers, Radio Amateurs' Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—**FREE. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**, Dept. 137K, Aldermaston Court, Reading RG7 4PF.

RADIO OFFICER training courses. Write: Principal, Newport and Monmouthshire College of Technology, Newport, Mon.

Educational

LEC

TELEVISION AND RADIO TRAINING (DAY ATTENDANCE COURSES)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of one year's duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Radar and Radio Transmission are also available following the TV course. Write for prospectus to: London Electronics College, Dept. B/4, 20 Penywern Road, Earls Court, London, S.W.5. Tel. 01-373 8721.

A.M.S.E. (Elec.), City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on 'Satisfaction or Refund' terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio & TV., etc. Send for full details and illustrated book—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept 168K, Aldermaston Court, Reading RG7 4PF.

MEN! You can earn £50 p.w. Learn Computer Operating. Send for FREE brochure—London Computer Operators Training Centre, C94 Oxford House, 9-15 Oxford Street, London, W.1.

Situations Vacant

EAGLE INTERNATIONAL require Audio Engineers; excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact Mr. Morrow 01-636 0961.

RADIO OPERATORS

DO YOU HOLD PMG II OR PMG I OR NEW GENERAL CERTIFICATE OR HAD TWO YEARS' RADIO OPERATING EXPERIENCE?

Looking for a secure job with good pay and conditions

Then apply for a post with the Composite Signals Organisation—these are Civil Service posts, with opportunities for service abroad, and of becoming established i.e. non-contributory pension scheme.

Specialist training courses (free accommodation) starting January, April and September 1972.

If you are British born and resident in the United Kingdom write NOW for full details and application form from:

**RECRUITMENT OFFICER
GOVERNMENT COMMUNICATIONS
HEADQUARTERS
OAKLEY, PRIOR ROAD, CHELTENHAM,
GLOS. GL52 5AJ**

Telephone: Cheltenham 21491 Ext. 2270

Receivers and Components

EX-GOVT. COMMUNICATIONS RECEIVERS, calibrators, signal generators, components, etc., with money back guarantee. SAE list. Callers welcome, please phone first.—P. R. Gollidge, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

Receivers and Components (continued)

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards **50np** + 7np P. & P. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for **£1**, P. & P. 18np. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board + components. 2 boards (4 x OC28) **50np** + 6np P. & P.

9 OAS, 3 OAI0, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for **£1** + 25np P. & P.

LARGE CAPACITY ELECTROLYTICS
10000MFD 30V } 40np + 6np P. & P.
16000MFD 12V }
or **£3.50** per doz. Carr. 50np

250 MIXED RESISTORS **62np**
± & ± watt.

150 MIXED HI STABS **62np**
± & ± watt 5% and better.

QUARTZ HALOGEN BULBS
With long leads. 12V 55W for car spot lights, projectors etc. **50p** each p & p.

DIODES ex EQPT; SILICON
1 Amp 1000 PIV, 4 for **50np**.
20 Amp 150 PIV, 4 for **£1**. + 5np P. & P.

BARGAIN RELAY OFFER
Single pole change over silver contacts. 25V to 50V, 2.5kΩ coil. 8 for **50np**. + 5np P. & P.

KEYTRONICS mail order only
**44 EARLS COURT ROAD,
LONDON W.8 01-478 8499**

NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only **£3-40**, P. & P. Free U.K. only

Illustrated Catalogue of Selected Kits and Components 12pp. P. & P. Free.

Cheques, Postal Orders to:

Dept. P.W.,
Galleon Trading Co., 25 Avelon Road,
Romford, Essex

COMMUNICATIONS RECEIVERS

Checked, tested, HRO CR100 B40/41 R1392 etc. Many other types available, also power supplies and amateur test-gear. SAE your requirements. R1155N Receivers 200KHz to 18-5MHz including Trawler Band. Good condition. Tested with details, **£10-25**, carriage **£1**.

Richard Sellers, Eastington, Goole, Yorks. Callers please phone 04305 254/01-428 8076.

Stelia Nine Range Cases

LIST OF PRICES AND SIZES

Width	Depth	4" Height	6" Height	7½" Height
6½"	3½"	90p	£1-05	£1-23
6½"	4½"	96p	£1-23	£1-40
8½"	3½"	£1-05	£1-40	£1-40
8½"	6½"	£1-40	£1-74	£2-00
10½"	7½"	£1-88	£2-28	£2-45
12½"	3½"	£1-40	£1-74	£2-03
12½"	5½"	£1-85	£2-25	£2-43
12½"	8½"	£2-30	£2-74	£2-93
14½"	3½"	£1-65	£2-03	£2-25
14½"	9½"	£2-73	£3-50	£3-65
16½"	6½"	£2-45	£2-93	£3-24
16½"	10½"	£3-15	£4-05	£4-45

Cases—Post 25p. per order.

Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2½" Walls

6" x 3"	33p	10" x 7"	51p	14" x 3"	44p
6" x 4"	34p	12" x 3"	40p	14" x 9"	84p
8" x 3"	39p	12" x 5"	45p	16" x 6"	64p
8" x 6"	46p	12" x 8"	64p	16" x 10"	95p

Chassis—Post 15p. per order.

Discounts available on quantities.

Electro magnetic counters. New Boxed. 500 ohm 4 digit 30p post free.
Copper Laminate board ½" single sided. 12" x 12" 30p. post free.
P.O. relays (600 Type) 500 ohm + 500 ohm. 1 make 1 break 2 change over New boxed 30p post free.
Heavy duty sliding reostat. 1 ohm 12 amp New boxed £1-25p. post free.

E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases
**46 LOWFIELD ROAD
STOCKPORT - CHESHIRE**
Tel: 061-480 2179

BRAND NEW Texas T.T.L. I.Cs. 20p each. SN7400N, 7402, 7420. C.W.O. Postage 6p. M. Rees, 5 Hillcrest Ave., London, N.W.11.

PRINTED CIRCUITS

PW 10 Watt Amplifier (May 1971) Price 55p inc. p/p.

PW HI-FI Signal Generator (May 1971) with separate Stabilised Power Supply. Total price £1.15 inc. p/p.

All boards are drilled and tin plated with the reverse side screen printed for easy component and connection identification.

SERVITRON ELECTRONICS
18 Beckdean Ave, Poulton-le-Flyde,
Blackpool, Lancs. FY6 8BG.

CIRCUITS CIRCUITS CIRCUITS

Ten exciting circuits per month with instructions to build. Every month a completely new set. This month's circuits cover

TRANSMITTERS OF ALL KINDS
Only 50p per set of ten p & p free
Free Data and Technical A-Z cards (build up the complete set month by month).
Cheques and PO to Dept PWC, Photonics, 3 Whitehall Gardens, London, E4.
Sae for details.

Kits for P.W. CONSTRUCTIONAL ARTICLES

Amateur Bands Communications Receiver £23.85, p. & p. 75p (or in 3 parts). RF Detector £9.64 p & p 25p. Signal Injector Tracer £3.95 p. & p. 20p. Workshop Oscilloscope £28.35 p. & p. 60.0p Crystal Companion £1.95 p. & p. 20p. Hi-Z Voltmeter £4.52 p. & p. 20p. 10W Audio Amplifier £8.75 p. & p. 35p. Hi-Fi Signal Generator £11.30 p. & p. 35p. Simple Signal Generator £6.95 p. & p. 30p. For prices of recent kits please send S.A.E.

F. & B. ELECTRONICS 5, Staples Inn, Holborn Bars, London WC1V 7QH
C.W.O. mail order only—please enquire for overseas p. & p.

EX RENTAL TV's

17" Semi Slim (90 degree tube) 22
17"/21" Slimline (110 degree tube) 45
19" Slimline 48
19" 3 channel sets 415
All TV's sold complete but unserviced, 12 channel tuners, good cabinets, plus carriage £1.

PERFECT SPEAKERS EX TV

PM 3 ohm (minimum order two) 5" round, 8" by 2" rectangular—12/p each. Add 7/p per speaker postage and packaging.

VALVES EX EQUIPMENT

EB91 5p	30L15 12/p	PCL82 17/p	6F23 17/p
EBF89 12/p	30P4 12/p	PL36 22/p	30P12 20/p
EC082 12/p	PC07 17/p	PL81 17/p	30F5 10/p
EF80 12/p	PCF86 17/p	PY81 15/p	30L17 17/p
EF85 12/p	PC84 7/p	PY80 15/p	30E11 12/p
EF13 12/p	PCF80 7/p	PY82 7/p	30P19 20/p
EF184 12/p	PC089 12/p	PY33 22/p	
EY86 17/p	PCL85 22/p	U191 17/p	

ADD 2/p PER VALVE P. & P. ORDERS OVER £1 P. & P. FREE

UHF TUNERS

To suit Ferguson 850 900 Chassis £2.50p P. & P. 50p

SLOT METERS

Smiths 6d/2p switchmaster Mk II £1 including P. & P. £8 for 10 delivered.

Dept. T.S.

THORNBURY TRADE DISPOSALS

Thornbury Roundabout, Leeds Rd., Bradford
Telephone 665870

MULLARD CR25 Resistors. 0.4W 5% HS 47Ω-1MΩ 1p each. P&P 5p. Spring Electronics Ltd., 25 Cranley Gardens, Muswell Hill, N.10.

CHROMASONIC ELECTRONICS

supply only 1st Grade branded goods subject to makers guarantees.

SN7400N, 1, 2, 4, 5, 10, 20, 36, 30, 40, 50, 51, 54
SN7460N all 25p ea.
SN7411AN, 42, 75, 81, 82, 90, 92, 93, 94, 95 all £1 ea.

PA230 82p	PA246 21-60	TAA310 21-25
PA234 87p	TAA283 70p	TAA320 65p
PA237 21-57	TAA293 90p	TAD100 21-95
PA239 22-50	TAA300 21-50	TAD110 21-95

LOW NOISE HI-STABS

1/2 watt 5% all E24 values 3 for 2p plus p. & p 6p up to 50 resistors plus 1p for each additional 50

FREE CATALOGUE p. & p. 3p.
p. & p. on all orders other than resistors 6p.
56, Fortis Green Road, London, N10 3HN.

MICROCIRCUITS:

709 40p	SL402A £1.75	7420 21p
741 73p	MEL 11 35p	7430 21p
PA230 97p	D40C1 55p	7473 43p
PA234 97p	7400 21p	7474 43p
PA237 £1.63	7410 21p	DIL Conn. 25p

TRANSISTORS:

MEF104 50p	ME1002 12p	MP8111 35p
ME0402 21p	ME4101 11p	2N5172 7p
ME0412 20p	ME4102 12p	2N3055 60p
ME0413 15p	ME6101 15p	BFX 86 21p

1W ZENER DIODES:

4.7V 12p	6.2V 12p	9.1V 12p
----------	----------	----------

Etch resist filled Marker Pen for making printed circuits 80p

JEF ELECTRONICS (P.W.8)

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. C.W.O. P.&P. 5p per order. Overseas 40p. Money back if not satisfied. List free on application.

BRAND NEW COMPONENTS by return.

Electrolytics 15 or 25 volts, 1, 2, 5, 10 mfd. 5.5p 25, 50 4p, 100 5p. Mylar film 100V .001, .002, .005, .01, .02 2p, .04, .05, .1 2.5p. Mullard miniature Carbon Film Resistors 1/2W 10-10MΩ for 5p. Postage 5p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

TRANSFORMERS, Chokes, Solenoids rewound.

Modern, obsolete or unusual—types, any size or voltages. Guaranteed as new. SAE enquiries. Ratcliffe, 18 Beech Avenue, Thongsbridge, Huddersfield.

COMPLETE RANGE of receivers by Trio, Lafayette, Hallicrafters, etc.

Chassis, panels, cabinets. S.A.E. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263 7829.



AIRCRAFT BAND RADIOS

Flight 2 MW/Air... £10.50	Mirage FM/MW/Air £15.00
Flight 3 MW/FM/Air £14.00	Koyo 5 MW/SW/FM/Air/PSB £34.00
Interceptor MW/Air £14.50	Juliette MW/MB/FM/Air/PSB £38.00
	Imperial SW1/2/MB/LW/MW/FM/Air/PSB £55.00

Special Offers Flight 4 MW/FM/(88-108) Air(108-140) Public(140-175) £16.95 (listed @ £18.50)

Waltham LW/SW/MW/FM/Air/PSB (88-175) £33.00 (listed @ £36.85)

Koyo 8 SW1/2/MB/LW/MW/FM/Air/PSB £45.00 (listed @ £55.00)

Koyo 8 Deluxe, with BFO £48.00

Money-Back Guarantee
Mail Order

LANGTON'S RADIO

58 HIGH STREET, ROCHESTER, STAFFS., ST14 5JU. Tel. 388

Full Lists Free
Counter Service

NEW VALVES!

Guaranteed and Tested 24-HOUR SERVICE

IR5 -27	30P4 -60	EABC80 -31	EF183 -29	PCF85 -45	PY800 -35
IS5 -21	30P19 -30	EB91 -11	EF184 -30	PCF801 -32	PY801 -35
IT4 -18	30P11 -61	EB038 -38	EL33 -54	PCF802 -44	R19 -81
384 -28	30P113 -77	EBF89 -30	EL84 -24	PCF805 -68	U26 -65
2V4 -37	30P114 -87	EC081 -17	EY51 -36	PCL82 -33	U28 -59
5Y3GT -27	CCH35 -65	EC082 -30	EY86 -31	PCL84 -35	UY91 -60
6J30L2 -57	DAF91 -21	EC083 -23	EZ80 -22	PCL85 -42	UY91 -70
6AQ5 -25	DAF96 -35	EC080 -28	EZ81 -23	PCL86 -40	UZ29 -70
6BW7 -57	DCC90 -80	ECF82 -28	GZ37 -70	PFL200 -54	UBF89 -31
6P1 -60	DF91 -18	KCH85 -27	KT61 -54	PL36 -49	UC086 -26
6P23 -70	DF96 -25	KCH81 -28	KT66 -22	PL81 -45	UC081 -32
6P25 -60	DK91 -27	ECF80 -33	N75 -36	PL82 -31	UC182 -34
25L6GT -22	DK92 -41	ECL82 -31	PC86 -49	PL83 -34	UC183 -30
30C15 -62	DK96 -37	ECL86 -37	PC88 -49	PL84 -31	UF89 -30
30C18 -63	DL92 -28	EF89 -22	PC97 -39	PL500 -64	UL84 -32
30F5 -72	DL94 -37	EF90 -24	PC900 -35	PL504 -65	UY85 -97
30FL1 -62	DL96 -37	EF95 -23	PCC84 -31	PY32 -54	Z77 -18
30FL14 -70	DF96 -28	EF96 -24	PCC89 -46	PY81 -26	
30LL5 -60	DY97 -26	EF99 -24	PCCL89 -50	PY81 -26	
30L17 -71	DY802 -38	EF91 -12	PCF80 -29	PY82 -26	

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra. Office address, no calls.

GERALD BERNARD
83, OSBALDESTON RD., STOKE NEWINGTON, LONDON, N.16

12 WATT HI-FI AMPLIFIERS

6 TRANSISTOR PRINTED CIRCUIT DESIGN BUILT, TESTED & GUARANTEED WITH INSTRUCTION MANUAL

£3.75

+ 0.25 p. & p.

TECHNICAL SPECIFICATIONS

- 12 watts R.M.S. into 8Ω load
- 15cs—19kcs ± 1 db at all powers
- Signal to noise ratio — 65 dB
- Input Sensitivity 600mv for full output
- Power requirements—30v unswitched



H ELECTRONICS
105 GRANGE ROAD SOUTH NORWOOD S.E.25

Receivers and Components (continued)

SINCLAIR PROJECT 60 OFFERS

Stereo 60/2 Z30/PZ5	£16.40
Stereo 60/2 Z30/PZ6	£18.25
Stereo 60/2 Z50/PZ8	£19.75
Transformer for PZ8	£2.25
Project 60 FM tuner	£29.50
Active Filter Unit	£4.75
Q16 Loudspeaker	£7.70
Kit of extra capacitors, plugs, cables, fuse to complete Project 60	£2.20

POWER SUPPLY BARGAIN

Sinclair PZ5 power supply units 30 V at 1.5 A. Ideal, compact, general purpose supply. List price £4.98. Our price **£3.80**.

SINCLAIR 1C10

10 W integrated circuit combined amplifier and pre-amp complete with instruction book. **£2.43**.

S-DECs AND T-DECs

Buy at our new low prices. Solderless, plugin, breadboard panels allowing rapid construction of lashups and unending re-use of components. S-DeC (70 points)

T-DeC (208 points)

THE 0.7P TRANSISTOR

Surplus PNP silicon transistors supplied complete with data. From 2S300 series. Typical Vcb = 25 V, hfe = 35, ft = 1 Mcs, Pmax = 300 mW. Untested and unmarked, but we guarantee at least 80% are good. 50 for 40p, 100 for 70p.

SWANLEY ELECTRONICS

32 GOLDSSEL RD., SWANLEY, KENT

Mail order only. Postage 37p on Project 60 orders, 10p on others. All goods are brand new. Money back if not satisfied.

JOHNSONS (RADIO)

ST. MARTINS GATE, WORCESTER
Est. 1943 Tel. 24884

NEW! CV2—a unique triple-purpose VHF kit for the Amateur enthusiast. Converter, Receiver and tuner-feeder. Fantastic single transistor performance! Complete kit of high grade parts with coils covering 80-170MHz, 9v battery, etc., plus easy/build diagrams and instructions, £4.13p direct from makers. S.A.E. for free literature

poly-planar

20-Watt Full Range Speaker

Completely replaces the
conventional cone speaker



Super-thin construction
permits new installation ideas.

Power capability: 20 watts peak
Frequency range: 40 Hz—20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input
Input impedance: 8 ohms
Operating temperature range: -20°F to +175°F
Size (WxDxL): 1-7/16" x 1-1/4" x 1-11/16"
Weight: 19 ounces

£ 5.75 (p&p20p) each

Stereo pair £11.40 post free

web europa

P.O. Box 162 'Bushey
Watford WD2 1LF

THE SHORT CUT TO SMOOTHER MOTORING PRACTICAL MOTORIST

Britain's widest-read motoring monthly

Place a regular order today! 15p

SAVE MONEY build your own speakers

And save even more with Cave's
Big Discounts

	List	Cash
TANNOY 111LZ	£21.00	£27.15
TANNOY 12" GOLD	£39.90	£31.95
TANNOY 15" GOLD	£43.35	£37.85
WHARFEDALE UNIT 3	£13.00	£11.90
WHARFEDALE UNIT 5	£26.30	£21.10
WHARFEDALE 10" RSDD	£12.20	£11.10
WHARFEDALE 8" RSDD	£4.40	£4.00
KEF KIT 3	£36.00	£30.80
KEF B138	£19.40	£16.60
KEF DN12	£4.50	£3.85
EMI 450 KIT	£3.15	£2.50
GOODMANS TREBAX 100	£2.80	£2.10
GOODMANS MIDDAX 650	£12.95	£11.30
GOODMANS AUDIOM 61	£18.95	£16.80
GOODMANS AXIOM 10	£9.60	£8.65
RICHARD ALLAN TWIN	£10.97	£9.75
RICHARD ALLAN TRIPLE	£20.35	£17.50
RICHARD ALLAN SUPER	£24.00	£20.95
SINCLAIR STEREO 60 FILTER UNIT	£5.97	£5.10
SINCLAIR STEREO 60 PRE AMP CONTROL	£9.97	£8.50
SINCLAIR PZ8 POWER UNIT	£7.99	£6.60
SINCLAIR PZ8 POWER UNIT	£7.97	£6.60
SINCLAIR PZ5 UNSTABILIZED	£4.97	£4.10
SINCLAIR Z50 POWER AMP	£5.47	£4.50
SINCLAIR Z30 POWER AMP	£4.47	£3.75
MULLARD EP9000 AMP	£2.90	£2.50
MULLARD EP9001 PRE AMP	£3.10	£2.65
MULLARD EP9002 POWER UNIT	£4.60	£3.95
MULLARD CONTROL UNIT	£3.25	£2.95

SEND 5p STAMP FOR TREMENDOUS
MONEY SAVING CATALOGUE—
COMPARE OUR PRICES AND START
SAVING MONEY RIGHT AWAY

F. CAVE TOP DISCOUNTS

Dep. PW, 5 BRIDGE ST., RICHMOND, SY.

Tel. 01-948 1441.

Dep. PW, 27 EDEN ST., KINGSTON, SY.

Tel. 01-546 7845.

MAIL ORDERS TO RICHMOND

Please mention

PRACTICAL WIRELESS

when replying to
advertisements

FAMOUS TELETON-AM/FM

Stereo Tuner Amplifier R8000


Supplied complete with 2 speakers. Total 12 watts RMS. Specification MPX Beacon, AFC Connections for Tape Recorder, Stereo Headphone Socket, etc. Mfgs. Rec. Price £63.50

P.S.P. FANTASTIC OFFER **only £39.95**



Plus GARRARD DECK 2025 Complete with plinth and perspex cover. Fitted with superb Sonotone 9TAHCO cartridge. P.S.P. offer **ONLY IF YOU**

BUY THE ABOVE only £15.40

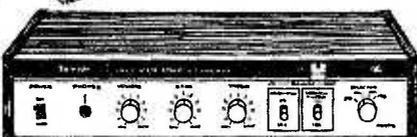

STOP PRESS!
FREE FREE! Pair
Teleton Stereo Head-
phones, value £5,
if you order the above
before August 31

TELETON SAQ 206 STEREO AMPLIFIER

Latest release, beautifully styled in walnut case, 6+6 watts r.m.s. Switched inputs for magnetic X tal, aux, Tape. Incorporates volume, bass, treble and, slide balance control, scratch filter and loudness control. Rec. £32.50.

Our price **£19.95**.

Suggested System.

SAQ 206 Amplifier, SP25 III Plinth and Cover, G800 cartridge, pair large 3-way speaker system incorporating large EMI 12" in network. Would normally cost £85 complete. Our price **£59.9**

PERSONAL SHOPPERS PLAN LTD.

The Centre

36-38 West Green Road, Tottenham, N.15

Tel. No. 01-800 5533

SAVE £££

ANOTHER PSP
SUPER
SCOOP



Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 12½p in £ for postage and handling
MINIMUM CHARGE 12½p. No C.O.D. orders accepted
Please note that the values offered below are not necessarily of U.K. origin

RETAIL SHOP
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

0A2	0.88	6A06	0.55	6F1	0.70	9BW6	0.50
0A3	0.45	6AR5	0.35	6F5	0.50	10C2	0.50
0B2	0.35	6AR6	0.40	6F6G	0.60	10D1	0.50
0B3	0.60	6AR11	1.25	6F11	0.38	10D2	0.40
0C3	0.38	6AS5	0.35	6F13	0.38	10F1	0.90
0D3	0.35	6AR7G	0.60	6F14	0.85	10F9	0.50
1B3GT	0.58	6AT6	0.30	6F15	0.30	10F18	0.45
1C3B1	0.58	6AU6	0.25	6F18	0.45	10L1	0.45
1L4	0.20	6AV6	0.30	6F23	0.30	10LD11.0	0.60
1R4	0.35	6AW8A	0.55	6F24	0.75	10L13	0.55
1R5	0.35	6BA6	0.25	6F25	0.75	10P14	1.10
1S4	0.27	6BE6	0.80	6F26	0.35	12AB3	0.60
1S5	0.25	6BF5	0.30	6F28	0.60	12AC6	0.40
1T4	0.35	6B7G	0.50	6F4	0.50	12A15	0.45
1U4	0.27	6BH6	0.45	6J5GT	0.80	12A20	0.43
1U5	0.50	6B7E	0.45	6J7	0.45	12A27	0.30
1V2	0.50	6BK7A	0.55	6K6GT	0.55	12B17	0.38
1X2B	0.40	6BN6	0.43	6K7	0.35	12A2U	0.30
2D21	0.35	6BN6	0.40	6K8G	0.35	12A27	0.80
3A4	0.35	6BQ5	0.25	6K25	0.75	12A75	0.35
3B28	2.15	6BR5	0.85	6L6GT	0.45	12A77	0.50
3BP1	2.75	6B87	1.30	6L7	0.40	12A27	0.30
3Q4	0.40	6BW6	0.75	6L18	0.45	12A27	0.75
3S4	0.35	6B7W	0.70	6LD20	0.40	12B44	A0.55
3V4	0.45	6BK6	0.25	6N7GT	0.40	12BA8	0.35
5B4GY	0.40	6BZ6	0.35	6P1	0.50	12B47	0.35
5F4G	0.33	6C4	0.33	6P25	1.25	12B2E5	0.35
5U4GB	0.42	6C5GT	0.40	6P28	0.65	12BHT	0.40
5V4G	0.42	6CB6	0.30	6Q7	0.40	12B77	0.55
5Y3GT	0.32	6CD6GAL1.5		6SA7	0.40	12K5	0.55
5Z3	0.50	6CG7	0.50	6S67	0.35	12K7GT0.35	
5Z4G	0.40	6CB6	0.55	6SK7	0.35	12Q7	0.30
6B3E	0.75	6BZ6	0.35	6S8GT0.50		12S15	0.35
6AB4	0.35	6C4W	0.83	6SN7GT0.35		1487	0.80
6AF4A	0.50	6CY5	0.43	6S87	0.40	20D1	1.45
6AG7	0.40	6C77	0.85	6R7	0.40	20L1	1.10
6A16E	0.50	6D3	0.45	6T8	0.35	20P1	0.50
6A18	0.30	6D8	0.75	6T4GT	0.60	20P4	1.10
6A15	0.30	6K6	0.45	6T8A	0.40	3B23	0.60
6A16	0.57	6DQB	0.83	6V6GT	0.35	25C5	0.50
6A13	0.43	6D84	0.75	6X4	0.30	35L6GT0.40	
6A15	0.20	6EA8	0.58	6X5GT	0.35	50A5	0.70
6AM5	0.32	6E7H	0.30	6X8	0.55	52BGT0.65	
6AM6	0.33	6E7J	0.85	6Y6G	0.65	30A5	0.45
6AQ5	0.35	6EW6	0.95	7Y4	0.80	30A3E5	0.40

First Quality Fully Guaranteed



BRAND


ELECTRONIC VALVES

30C1	0.80	50L6GT0.50	DK96	0.42	ECC85	0.40	
30C15	0.25	58A2	0.40	DL96	0.42	ECC88	0.40
30C17	0.85	90A4	2.40	DM160	0.65	ECC99	0.50
30C18	0.75	90AV	2.50	EY86	0.33	ECC91	0.30
30F5	0.35	90C1	0.80	DY87	0.35	ECC189	0.60
30FL1	0.70	90CV	1.25	DY802	0.50	ECCF80	0.35
30FL12	0.93	807	0.50	E88CC	0.65	ECCF82	0.35
30FL14	0.75	813	3.75	E180F	0.95	ECCF86	0.65
30L1	0.40	866A	0.75	E810F	2.90	ECCF8041.50	
30L15	0.55	8642	0.85	EABCC80.85		ECH42	0.70
30L17	0.30	6090	1.50	EA42	0.55	ECH81	0.30
30P12	0.50	6146	1.50	EB33	0.50	ECH83	0.40
30P19	0.50	6360	1.25	EBC41	0.55	ECH84	0.45
30PL1	0.70	6870	2.50	EBC81	0.30	ECL80	0.40
30PL13	0.93	6939	2.15	EBF80	0.40	ECL81	0.45
30P14	0.90	7199	0.75	EBF83	0.40	ECL82	0.35
30A3	0.55	7300	1.90	EBF89	0.30	ECL83	0.65
30A5	0.75	7586	1.25	EC93	0.50	ECL84	0.55
30B5	0.85	7895	1.25	EC86	0.80	ECL85	0.55
30C2	0.40	9002	0.35	EC88	0.60	ECL86	0.40
30D5	0.70	9003	0.50	EC90	0.33	ECL800	
35L6GT0.50		AZ1	0.48	EC91	0.50	EN31	1.50
3B23	0.60	AZ21	0.55	EC92	0.35	EV51	0.40
3BL1	0.80	CB1	0.80	EC93	0.50	EV50	0.45
3BL31	0.90	CB1.90	0.25	EF40	0.50	EV51	0.40
CV31	0.35	CC40	0.60	EF41	0.65	EV83	0.55
DAF96	0.42	CC81	0.33	EF42	0.70	EV86	0.40
DF96	0.42	CC82	0.30	EF80	0.25	EV87	0.43
DK40	0.55	CC83	0.30	EF83	0.55	EV88	0.43
50C5	0.40	DK92	0.50	EF85	0.35	EZ40	0.45

TRANSISTORS

2N404	0.17	2S102	0.40	BC175	0.85
2N444A	0.25	2S104	0.50	BCY30	0.35
2N696	0.20	2S701	0.50	BCY33	0.35
2N697	0.25	2S702	0.50	BCY34	0.30
2N698	0.40	2S746	0.30	BCY72	0.20
2N705	0.70	AC113	0.15	BCZ11	0.40
2N706	0.15	AC125	0.30	BD121	0.80
2N708	0.20	AC126	0.30	BD133	0.30
2N753	0.25	AC127	0.50	BF115	0.20
2N929	0.30	AC128	0.30	BF167	0.35
2N930	0.35	AC132	0.25	BF173	0.25
2N997	0.35	AC153	0.25	BF181	0.25
2N1131	0.40	AC154	0.15	BF184	0.25
2N1132	0.45	AC156	0.25	BF190	0.25
2N1184	1.25	AC158	0.50	BF194	0.20
2N1201	0.40	AC169	0.10	BF195	0.15
2N1202	0.25	AC176	0.25	BF196	0.20
2N1304	0.25	AC187	0.30	BF197	0.20
2N1305	0.25	AC193	0.40	BF197B	0.20
2N1306	0.25	AC197	0.30	BFW88	0.25
2N1307	0.30	ACY18	0.20	BFW89	0.25
2N1308	0.40	ACY19	0.25	BFW91	0.20
2N1309	0.35	ACY20	0.20	BFX88	0.25
2N1613	0.25	ADY21	0.90	BFY17	0.40
2N1711	0.30	ADY16	0.30	BFY18	0.30
2N1756	0.75	ADY19	0.80	BFY50	0.25
2N2147	0.75	AD149	0.50	BFY51	0.20
2N2160	1.25	AD161	0.35	BFY52	0.25
2N2217	0.30	AD162	0.35	BSY26	0.25
2N2218	0.40	AF114	0.25	BSY27	0.30
2N2219	0.45	AF115	0.30	BSY28	0.30
2N2869A	0.25	AF116	0.25	BSY65	0.30
2N2477	0.65	AF117	0.20	BSY95A	0.20
2N2646	0.60	AF118	0.45	OC16	0.75
2N2905	0.50	AF125	0.25	OC22	0.25
2N2923	0.15	AF127	0.25	OC23	0.60
2N2924	0.15	AF178	0.40	OC24	0.60
2N2926	0.15	AF180	0.35	OC25	0.60
2N3063	0.30	AF181	0.35	OC26	0.30
2N3065	0.75	AF186	0.50	OC28	0.60
2N3133	0.35	AF239	0.40	OC29	0.65
2N3134	0.80	AF211	0.45	OC30	0.75
2N3391	0.20	ASV26	0.25	OC32	0.50
2N3392	0.15	ASV27	0.30	OC36	0.60
2N3393	0.15	ASV28	0.30	OC38	0.60
2N3394	0.15	ASV29	0.30	OC44	0.30
2N3395	0.20	ASV54	0.25	OC45	0.20
2N3402	0.15	ASV74	0.50	OC70	0.20
2N3403	0.15	ASV77	0.35	OC71	0.15
2N3404	0.35	ASV82	0.20	OC72	0.25
2N3414	0.20	ASV86	0.50	OC73	0.40
2N3415	0.15	ASZ16	0.70	OC75	0.25
2N3416	0.25	ASZ17	0.75	OC76	0.25
2N3417	0.25	ASZ18	0.75	OC78	0.25
2N3702	0.15	ASZ21	0.50	OC78D	0.20
2N3703	0.15	BC107	0.15	OC81	0.25
2N3704	0.20	BC108	0.15	OC81D	0.15
2N3707	0.20	BC109	0.20	OC82	0.30
2N3709	0.15	BC118	0.40	OC139	0.35
2N3710	0.15	BC118	0.30	OC140	0.40
2N3819	0.35	BC134	0.30	OC141	0.60
2N3906	0.30	BC147	0.20	OC170	0.25
2S002	1.00	BC149	0.15	OC171	0.25
2S004	1.00	BC149	0.15	OC200	0.50
2S034	1.00	BC152	0.15	OC202	0.65

SYNCHROSCOPE TYPE CF-5

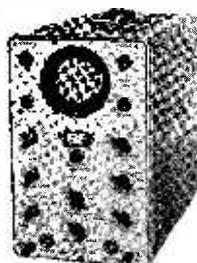

3-in tube fitted with telescopic viewing hood, giving bright display in full daylight.
Bandwidth 10 c/s—10 mc/s. Triggered sweep pre-set at 1-2.5-10-30-100-300-1000-3000 μsec per stroke. Free-running time base 20 c/s to 2000k/s with built-in crystal calibrator providing timing marks at 0.5-2.1-5-20-100 μsec ± 5%.
Amplitude calibrator directly calibrated in volts. Input attenuator 1-10-100.
Power supplies 127/230V AC.
PRICE £39.00. Packing and carriage 1.50

100-AMP THYRISTORS

CR100-151A	150 p.i.v.	£1.75
CR100-901A	300 p.i.v.	£2.50
CR100-351A	350 p.i.v.	£3.00
CR100-401A	400 p.i.v.	£3.50

Minimum Gate Firing Voltage is 3V at 150ms.

SOLID STATE LIGHT EMITTING DIODES MV10B

T018 outline. Brightness 500 FT-L at 50mA. Forward voltage 1.65 to 2V. Diode gives bright red pinpoint of light when supplied from a 2V source. Lens diameter 0.170in. PRICE £1.05

OUR NEW 1970/1971 CATALOGUE IS NOW READY AND AVAILABLE FREE OF CHARGE. PLEASE SEND QUARTO STAMPED AND ADDRESSED ENVELOPE FOR THIS VALUABLE SOURCE OF REFERENCE LISTING MANY THOUSAND TYPES OF VALVES, SEMICONDUCTORS, TUBES ETC.

TWO NEW MULTIMETERS FROM RUSSIA



Type U4312 U4313

with AC current ranges
Type U4312—Low sensitivity instrument (667 o.p.v.) 1% accuracy on DC (300μA to 6A) and 8 current ranges on AC (1.6mA to 5A), 9 voltage ranges 0-3 to 900V AC/DC. Resistance 0-2 to 30k Ω. Mirror scale.
PRICE, complete with leads and steel carrying case £9.75
Type U4313—20,000 o.p.v. DC and 2,000 o.p.v. on AC. 8 DC current ranges 60μA to 1.5A. 6 AC current ranges 0-6 to 1.6A. 9 DC and AC voltage ranges 1.5-500V. Resistance ranges 0-5-500k Ω. Accuracy 1.5% DC and 2.5% AC. Mirror scale.
PRICE, complete with test leads and steel carrying case £10.50

MINIATURE CERAMIC CAPACITORS 25V WORKING

5% tolerance 22-27-33-39-47-56-68-82-100-120-150-180-220-270-330-390-470-560-680-820-1000PF
All at 20mp per twenty.
+50%—20% tolerance 1500-2200-3300-4700-6800-10,000
15,000PF—All at 25mp per twenty.
+80%—20% tolerance 0.022-0.033-0.047 μF.
All at 25mp per twenty.
Minimum orders 20 of one size.

HALF WAVE SILICON WIRE ENDED RECTIFIERS

BY101	50 p.i.v.	1 Amp	10mp
IN4002	100 p.i.v.	1 Amp	10mp
BY125	200 p.i.v.	425mA	13mp
IN4004	400 p.i.v.	1 Amp	15mp
BY150	450 p.i.v.	800 mA	10mp
BY127	600 p.i.v.	1 Amp	15mp
IN4006	800 p.i.v.	1 Amp	15mp
BY105	800 p.i.v.	1-1 Amp	20mp

INTEGRATED MONOLITHIC DUAL OPERATIONAL AMPLIFIER MC1455P

Two identical amplifiers in 14-pin dual-in-line epoxy package. 400mW dissipation. Typical open loop voltage gain 7000. Max. differential input ± 5V. Power supplies 6 to 9V. Max. frequency 1

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home – equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast – makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION – OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT— SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." – Case History G/321.

"In addition to having my salary doubled, my future is assured." – Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." – Case History B/461.

FIND OUT FOR YOURSELF

These letters – and there are many more on file at Aldermaston Court – speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept D258, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



POST THIS COUPON TODAY

To: B.I.E.T., Dept D258, Aldermaston Court, Reading RG7 4PF.
Please send me book and details of your Courses in

Name..... Age.....

Address.....

Occupation.....

B.I.E.T. – IN ASSOCIATION WITH THE SCHOOL OF CAREERS – ALDERMASTON COURT, BERKSHIRE


HENRY'S RADIO LIMITED

HENRY'S RADIO

ENGLAND'S LEADING ELECTRONIC CENTRES

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

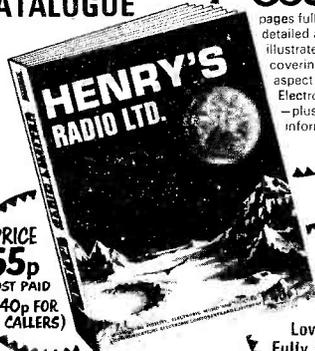**COMPLETELY NEW
10th EDITION
CATALOGUE**



350

pages fully detailed and illustrated covering every aspect of Electronics — plus data and information

PRICE 55p

POST PAID (40p FOR CALLERS)

10,000

Stock lines at Special Low Prices and Fully Guaranteed

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

FREE to Industry, Educational or any Organisation, including Schools and Colleges etc. Apply on Official heading to our "303" address.

A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!

To Henry's Radio Ltd. (Dept. P.W.)
3, Albemarle Way, London, E.C.1.

Please send copies at 55p each Post Paid

I enclose Cheque/PO for

(Use BLOCK CAPITALS—cut out and send with Cheque or Postal Order (No cash please) Use only for ordering catalogue)

Name

Address

P.W.

Allow 7-10 days from date of posting.

MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

*Components from stock for almost all published designs.

TRANSISTOR AMPLIFIERS

NEW RANGES NOW IN STOCK (Leaflets Ref. No. 6 and 8) Post etc. 20p

- 4-300 4 TR 9V 300mW £1-75
- 104 4 TR 9V 1W £2-12
- 304 4 TR 9V 3W £2-47
- 555 6 TR 12V 3W £2-75
- PA7 6 TR 16V 7W £3-62
- 608 6 TR 24V 10W £4-12
- 410 4 TR 28V 10W £4-97
- MPA12/3 6 TR 18V 12W £4-50
- MPA12/15 6 TR 36V 12W £5-25
- Z30 9 TR 30V 20W £3-75
- PA25 10 TR (Spl) 25W £7-50
- Z50 30V 40W £5-47
- PA50 12TR (Spl) 50W £9-50
- 100 100W with Power Supply £45-00 Post 45p

OPTIONAL POWER SUPPLIES


- Post etc. 20p.
- PS00 (One or Two) for 104, 304 £2-62
 - PS20 (One or Two) for PA7 £3-47
 - MU24/40 (One or Two) for MPA12/3 or MPA12/15 £4-55
 - PZ5 for Z30 £3-97
 - PZ8 for Z50 £5-97
 - P11 for 608 £2-87
 - MU442 for 1 or 2 PA25 or 1 only PA50 £6-50
 - Transformer for PZ6 for Z30 £6-97
 - Transformer for P15 for 410 £2-25
 - P15 for 410 £2-62
 - P15 for 410 £6-50

NEW MINIATURE LOW COST AMPLIFIER

MODEL 4-300

9 volt operated or mains unit optional transformer (MT98 70p). 1-10mV adjustable sensitivity. P/P output for 3-8 ohms. Fixed volume control and leads. Size 5 1/4" x 1 1/2" x 1". Thousands of uses—takes magnetic, dynamic and crystal inputs direct. Output 300mW—very high gain—built in rectifier circuit. Complete with FREE leaflet No. 8.

PRICE £1-75 p.p. 15p

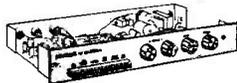

HENELEC EQUIPMENT (as previously advertised)

SELF-POWERED SILICON PRE-AMPLIFIERS

- FET.154 Stereo £16-50 Post 25p
- FET.9/4 Mono with mike mixer £12-50 Post 20p

SILICON POWER AMPLIFIERS FOR USE WITH ABOVE

- PA25 25 watts into 8 ohms £7-50 Post 20p
- PA50 50 watts into 4 ohms £9-50 Post 20p



- MU442 Power Supply for 1 or 2 PA25's or 1 only PA50 £6-00 Post 20p

PACKAGE DEALS

- FET.9/4 plus MU442 £27 Post 40p
- FET.9/4 plus PA50 plus MU442 £36 Post 40p
- FET.154 plus 2xPA25 plus MU442 £36 Post 50p
- FET.154 plus 2xPA50 plus 2xMU442 £40 Post 50p

NO SOLDERING—JUST EDGE CONNECTORS AND DIN PLUGS/SOCKETS

FREE BROCHURE No. 25

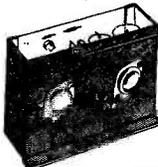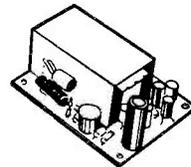

HI-FI TO SUIT EVERY POCKET



CHOOSE 100 STEREO SYSTEMS FROM

and a complete range of individual units in stock—Demonstrations All day—visit our new Hi-Fi Store, LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only).

FREE—Stock list No. 16, 17 on request—BEST VALUE IN U.K.

GARRARD TAPE DECK



9 volt operated 2-speed tape deck fitted Record/Replay 1/2 track and Erase/Bias Osc. Head. Complete with Oscillator/Record head circuit. Unit size 9" x 6 1/2" x 1 1/2" and 2 1/4" below motor board. Takes up to 4" spools. Supplied Brand New. Price £9-97 P. & P. 33p 3 1/2" Tape 300' and spool 40p

BUILD YOURSELF A QUALITY RADIO

Excellent printed circuit design with full power output. Fully tuneable on both M/LW bands. 7 Mullard transistors. Fitted 5in. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silvered front. All local and continental stations. Complete detailed instructions. Total cost £6-98 p.p. 35p. All parts sold separately. Ask for leaflet No. 1.



SINCLAIR PROJECT 60 PACKAGE DEALS

- 2xZ30 amplifier, stereo 60 pre-amp, PZ5 power supply, £16-75. Carr. 40p. Or with PZ6 power supply £18-25. Carr. 40. 2xZ50 amplifier, stereo 60 pre-amp, PZ8 power supply, £20-25 Carr. 40p. Transformer for PZ8 £2-25 extra. Any of the above with Active Filter unit add £4-75 or with pair Q16 speakers add £15. Also new FM Tuner £21.

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BAND-WIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. TOTAL £6-97 p.p. 20p. Cabinet 100p, Decoder Kit £5-97 Tuning meter £1-75 (Mains unit (optional) Model PS900 £2-47 Mains unit for Tuner and Decoder PS1200 £2-62



Electronic Components, Audio and Test Gear Centre
356 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
354 EDGWARE ROAD, LONDON, W.2.
Tel: 01-402 5854

Electronic Organs, P.A. & Discotheque Centre
309 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 6963

Mail Orders, Special Bargain Shop, Industrial Sales
303 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY