

# PRACTICAL WIRELESS

OCTOBER  
1971

20p

**EXTRA INSIDE**


**8 PAGE SUPPLEMENT**

**SMALL  
WORKSHOP  
TOOLS**

*plus*

Wall Chart

**CIRCUIT  
BUILDING  
BRICKS**

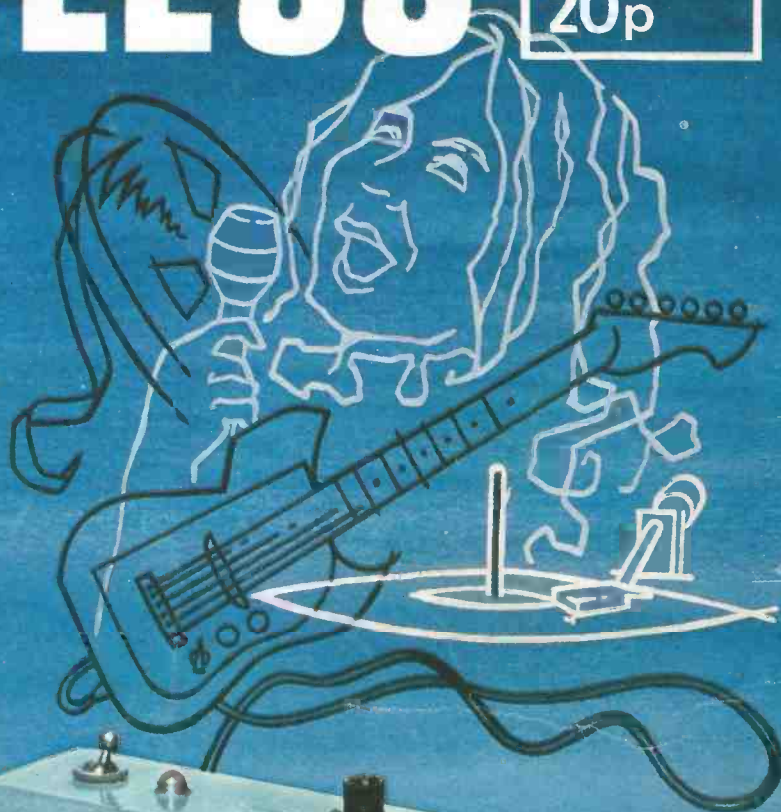

**MODULAR AUDIO MIXING SYSTEM**

# ADCOLA Soldering Instruments add to your efficiency

## THE NEW 'INVADER'

### ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*.  
Standard temp. 360 c at 23 watts.  
Special temps. from 250°c—410 c.

**PRICE**  
**£1.85**



#### \*Additional Stock Bits (illustrated) available

##### COPPER

B 38  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

B 24  $\frac{1}{8}$ " — 4.75 mm SCREWDRIVER FACE

B 12  $\frac{3}{16}$ " — 4.75 mm EYELET BIT

B 58  $\frac{1}{4}$ " — 6.34 mm CHISEL FACE

##### LONG LIFE

B 42 LL  $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL  $\frac{1}{4}$ " — 3.2 mm CHISEL FACE

B 14 LL  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

B 44 LL  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

\* Write for price list and catalogue



**ADCOLA PRODUCTS LTD.,**  
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 - Telegrams: Soljoint London Telex • Telex: Adcola London 21851



## for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price **75p**  
Size 12



### THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price **75p**  
Size 10



### A RANGE OF SOLDERS IN HANDY DISPENSERS.

#### REF. ALLOY SWG

19A 60/40 18 18p\*

Size 5 (illustrated) Savbit 18 18p\*

15 60/40 22 22p\*

\*Recommended Price



### INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIF WIRE STRIPPER AND CUTTER, easily

adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price **50p**



From Electrical and Hardware shops. If unobtainable, write to: **Multicore Solders Ltd., Hemel Hempstead, Herts.**




## RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors.
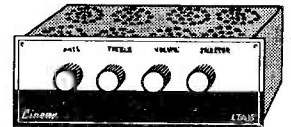
### LTA 15 WATT AMPLIFIER

HIGH FIDELITY OUTPUT SWITCHED INPUTS FOR GRAM, 'MIKE', TAPE, AND RADIO

Frequency Response 10-40,000 cps—3dB. Bass Control+17dB to—16dB at 40cps. Treble Control—17dB to—14dB at 14Kcs. Hum and Noise—80dB. Harmonic Distortion 0.2% at rated output. Output for 3-8-15 ohm Loudspeakers.




Recommended **£19**  
Retail Price  
Size 9½ x 3½ x 5½ in. approx.

### PTA30 HI-FI PUBLIC ADDRESS AMPLIFIER

A SUCCESSOR TO OUR POPULAR CONCHORD 30 WATT UNIT

Input Sensitivity 2 mv (max.)  
Output 30 watts.

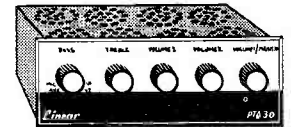Output Sockets for Loudspeaker or combination of Speakers with total impedance between 3 ohms and 30 ohms. Three individually controlled Inputs for mixing purposes. Housed in fully enclosed stove enamelled steel case. Controls Vol. (1) Vol. (2) Vol. (3) with mains switch, Treble 'lift', and 'cut'. Bass 'lift' and 'cut'.



Recommended **£24**  
Retail Price  
Size 12 x 3½ x 6 in. approx.

AN IDEAL UNIT FOR VOCAL AND INSTRUMENTAL GROUPS, SUITABLE FOR ANY KIND OF 'MIKE' AND INSTRUMENT PICK-UP, ALSO FOR RADIO, TAPE OR GRAM.

Please send a stamped addressed envelope for full descriptive details of above units.


If required an attractive wood cabinet with veneer finish can be supplied for any model. **£3.50**  
Prices from

AVAILABLE FROM YOUR LOCAL HI-FI DEALER  
Wholesale and Retail enquiries to:

**LINEAR PRODUCTS LTD,**  
Electron Works, Armley, Leeds

## SUPER SPEAKER BARGAINS WHARFEDALE DENTONS

A compact system sold in matched pairs for a perfectly balanced stereo system. Each Denton contains an 8in. bass unit with 3in. pressure unit, coupled by a Wharfedale crossover network. Rated input: 15 watts maximum. Frequency response: 65-17,000Hz. Impedance: 4/8 ohms. Cabinet 9 1/2in. x 14in. x 8 1/2in. These most attractive units are available in oiled teak, white or walnut and are small enough to blend in with most surroundings.

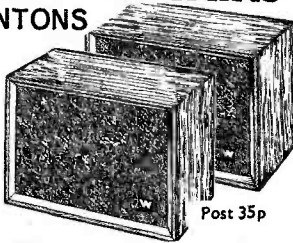


Post 35p

LIST PRICE £39.00 **£28.00** Walnut White

**£27.00** Teak

## WHARFEDALE TRITONS

A new and exciting addition to the Wharfedale range, this three speaker system will satisfy the most ardent Hi-Fi enthusiast. Shelf or floor standing—hand finished in oiled teak or polished walnut. Frequency response 55-22,000Hz. C.A.B. Dome pressure unit. Bass unit 8in. Mid-range unit 5in. Treble unit 2in. Impedance 8 ohms. Size 2 1/2in. x 9 1/2in. x 9in.

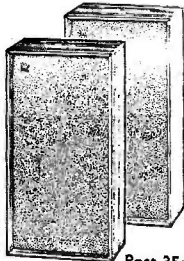

Post 35p.

LIST PRICE £59.90

**LASKY'S £36.00** Teak

**PRICE £38.00** Walnut White

## BSR McDONALD MP60

High precision low-mass counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.

**LASKY'S PRICE £12.50** Post 35p



### BSR McDONALD UNITS & PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

MODEL	A	B	C	D	E
610	£15.45	£18.75	£22.50	£24.50	£28.50
510	£13.45	£16.95	£20.75	£22.00	£26.00
310	£9.95	£13.45	£17.25	£21.00	£23.50
MP60	£12.50	£15.75	£19.50	£21.50	£25.50

## GARRARD UNITS AND PACKAGES

### GARRARD SL 55B

Four speed autochanger

**LASKY'S PRICE £10.50** Post 35p



Garrard SP25 Mk. III	£11.50	Garrard SL40B	£9.95
Garrard SP25, Mk. III wired	£12.00	Garrard AP76 without cart.	£20.95
Garrard SP25 Mk. III with 9TA cart.	£13.95	Garrard 3000 with 9TA cart.	£10.50
		Garrard 2025TC with 9TA cart.	£9.85

### GARRARD PACKAGES

Post on packages 50p

Garrard AP76 with AD76K cart. and Lasky's plinth and cover	£35
Garrard AP76 with Shure M44E cart. and Lasky's plinth and cover	£40
Garrard SP25 Mk. III, AD76K cart. and Lasky's plinth and cover	£20
Garrard SP25 Mk. III, Micro M2100e cart. and Lasky's plinth and cover	£25

## LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

Type	Singles	5	10	20
C-60	41p	£1.82	£3.41	£6.55
C-90	63p	£3.04	£5.78	£10.89
C-120	96p	£4.13	£7.43	£13.41

Post Each 5p. 5-20p. 10-25. 20-50p.

## SONY 8FC 59W SCOOP

### DIGITAL AM/FM CLOCK RADIO



Digital Alarm Clock Radio. The digital clock shows you the time minute by minute with matchless accuracy and once set the Digimatic will wake you up at the same time every morning without having to be re-set. The radio section features Sony's unique sleep button, you fall gently to sleep lulled by the sweet tone of the radio, which switches itself off at a predetermined time. Available in either black, white or red (8FC-59W). Frequency range 530-1,605KHz (AM); 87-108MHz (FM). Uses 8 transistors and 8 semi-conductors, built-in ferrite aerial and 3 1/2in loudspeaker. Power requirements: 230V AC 50Hz. Dimensions: 12 1/2in x 3 1/2in. x 5 1/2in.

LIST PRICE £30.00

**LASKY'S PRICE £22.50** Post free in U.K.

## KATONE AM/AIRCRAFT PORTABLE RADIO


### BATTERY/MAINS

A combined battery and mains portable of exceptionally attractive design. Housed in a leatherette covered case, size 8 1/2in. x 5 1/2in. x 3 1/2in., fitted with an 8-section external telescopic aerial for FM and internal ferrite rod for MW wave bands, and clear easy-to-read dial with logging scale. Wave band coverage is FM 88-108MHz, AM 535-1,600KHz. A highly selective circuit using 9 transistors and 9 semi-conductors operating from either 4 x 1.5 volt torch batteries or direct from 230 volts 50Hz AC house mains, from a built-in mains unit. A socket is fitted for a personal earphone. Easy-to-use silver colour knobs, with "woodgrain" panel enhances the appearance of this fine radio.



**LASKY'S PRICE £9.95** Post 15p

## DIGITAL CLOCK SCOOP

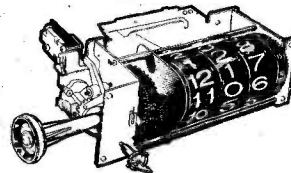

EXCLUSIVELY FROM LASKY'S


for you to mount into any housing. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back of switch). SPEC.: 210/240V a.c., 50Hz operation; switch rating 250V 5A. Complete with instructions. HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS.

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
  - MAINS OPERATION
  - 12-HOUR ALARM
  - AUTO "SLEEP" SWITCH
  - HOURS, MINUTES AND SECONDS READ-OFF
  - FORWARD AND BACKWARD TIME ADJUSTMENT
  - SILENT OPERATION SYNCHRONOUS MOTOR
  - SHOCK AND VIBRATION PROOF
  - BUILT IN ALARM BUZZER
- SPECIAL QUOTES FOR QUANTITIES

**LASKY'S PRICE £6.95** Post 18p
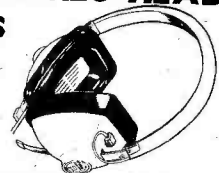
## TRIO HS.1 & HS.2 STEREO HEADPHONE BARGAINS

Models HS-1 and HS-2. Both these sets by TRIO offer really superb stereo reproduction in a lightweight, fully adjustable headset designed for optimum comfort. Listening fatigue is unknown with TRIO headphones. Brief spec. both models: Imp. 80 nominal (matching 4 to 80); max. input 0.5W; frequency response 20-19 kHz; output sensitivity at 1mW input; HS-1 118 dB, HS-2 111 dB; weight 0.66lbs. Identical in appearance—both models are finished in ivory with contrasting foam filled ear pads and head band.



LIST PRICE £8.40 **LASKY'S PRICE £6.75**

**HS.1 £5.20p HS.2 £4.15p** Post 18p

## Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271  
33 TOTTENHAM C. RD., LONDON, W.1 Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

**NEW CITY BRANCH NOW OPEN**

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel: 01-790 4821



# RADIO CONSTRUCTOR



Special  
IN THIS ISSUE

# THE RADIO CONSTRUCTOR

## September Issue

Constructional Articles include

### SEMI-CONDUCTOR GATE-DIP OSCILLATOR

Bringing the grid-dip oscillator up to date with the aid of a modern low-cost field-effect transistor. The unit described is capable of operation from 4 to 145MHz.

### BRAKE LIGHT FAILURE INDICATOR

### AUTOMATIC MORSE PRACTICE KEYS

### HIGH IMPEDANCE TRANSISTOR PRE-AMPLIFIER

PLUS

- MORE CONSTRUCTIONAL PROJECTS
- NEWS COVERAGE
- SHORT WAVE SCENE
- SUPPORTING FEATURES
- DATA SHEET 54

Copies may also be obtained direct from the Publishers 24p including postage. Published by:  
Data Publications Ltd., 57 Maida Vale, London W.9

## ON SALE NOW 20p

### 4-STATION INTERCOM



£6.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. £0.40.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way loud and clear communication. On off switch and volume control. Price £13.95 P. & P. £0.25.

### INTERCOM/BABY ALARM



OUR PRICE ONLY £3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 13p. P. & P. £0.25.

### Transistor TELEPHONE AMPLIFIER



£2.98

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 13p. extra. P. & P. 20p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.S)  
189 KENSINGTON HIGH STREET, LONDON, W.8.

### The Unique MULTI-MINI TWIN-VICE



An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5.90 (24p P & P)

ALSO AVAILABLE

SINGLE VICE: £3.37½ (20p P & P)

COVENTRY MOVEMENT CO LTD.

Dept. P.W.3

BURNSALL ROAD, COVENTRY CV5 6BU

STD O203-74363

### MAINS UNITS for all types of TRANSISTOR EQUIPMENT



### RUN YOUR TAPE RECORDER OFF A.C. MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.)

£2.50 P. & P. 15p

### 12 VOLT CAR BATTERY UNIT

Enables you to run your cassette recorder off 12V. car battery. (State 6v or 7½v output, model and plug required.)

£2.00 P. & P. 15p

### PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v, 7½v and 9v. D.C. attractive case with indicator light, mains lead output socket, plug and lead. Size 4½ x 3½ x 2½ in.

£3.00 P. & P. 15p.



Extra lead with plug to fit your cassette recorder 50p. (State model and plug required.)

MAINS UNIT FOR ALL TRANSISTOR RADIOS, ETC., USING PP3 TYPE BATTERY. (ALSO AVAILABLE FOR 6V.)

£1.15 P. & P. 10p.

### MAIN UNITS

For single outputs, 6v, 9v, 12v, 18v, £2.00. For two separate outputs, 4½v + 4½v, 6v + 6v, 9v + 9v, £2.50. P. & P. 15p. per unit. (Please state outputs reqd.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.G.S. PRODUCTS (RADIO) LTD.  
(Dept. P.W.), 31 Oliver Road, London, E17

# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171 = BC107	0-13	2N1308-9	0-35
BC172 = BC108	0-13	2N3819FET	0-45
BF194	0-15		
BF274	0-15	<b>Power Transistors</b>	
BFY50	0-20	OC20	0-50
BSY25	0-57	OC23	0-30
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-13	OC35	0-25
BSY95A	0-15	OC36	0-37
OC41	0-13	AD149	1-30
OC44	0-13	AUY10	0-20
OC45	0-13	2S034	0-25
OC71	0-13	2N3055	0-63
OC72	0-13		
OC73	0-17	<b>Diodes</b>	
OC81	0-13	AA42	0-10
OC81D	0-13	OA95	0-19
OC83	0-20	OA79	0-99
OC49	0-13	OA81	0-99
OC140	0-17	IN9114	0-07

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

## OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

- TYPE "A" PNP Silicon alloy, metal TO-5 can. 25300 type, direct replacement for the OC200/203 range.
- TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.
- TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.
- TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

## BULK BUYING CORNER

- NPN/PNP Silicon Planar Transistors TO-18 mixed untested similar to 2N706-6A-8, BSY26-7A9-95A and BCY70 etc. £4-25 per 500. £8 per 1000.
- NPN Silicon Planar transistors plastic encapsulation untested similar to 2N3707 to 3711. £4-25 per 500. £8 per 1000.
- Silicon planar diodes do-7 glass similar to OA200-202, BAY31-36. £4-50 per 1000.
- NPN/PNP Silicon planar transistors plastic TO-18 similar to BC113-4, BC153-4, BF153-160, etc. £4-25 per 500. £8 per 1000.
- NPN Silicon planar transistors TO-5 can similar to BC142/3, BFY50-2-3. £5-25 per 500. £10 per 1000.
- OC44, OC45 transistors fully marked and tested 500 to 999, 8p each, 1000+ 6p each.
- OC71 transistors fully marked and tested, 500 to 999, 6 each, 1000+ 5p each.
- A amp miniature plastic diodes IN4001 at 500 to 999, 4p each, 1000+ 3p each. IN4004 at 500 to 999, 5p each, 1000+ 4p each. IN4006 at 500 to 999, 6p each, 1000+ 5p each. IN4007 at 500 to 999, 8p each, 1000+ 7p each.

## CLEARANCE LINES

SL403D Audio Amp.	1.10	10.50	50+
IC 709C Linear Opp. Amp.	2-00	1-95	1-80
A.E.I. Fully marked & tested Gates	50p	40p	35p
A.E.I. Fully marked & tested Flipflops	25p	22p	20p
OC71/72 Fully tested, unmarked	50p	40p	30p
Matched Sets 1-OC44, 2-OC45 Per set	5p	5p	4p
Matched Sets, OC45, 1st & 2nd I.F. Per set	25p	20p	15p
TIC45 Thyristors, 6A, 60V Texas	15p	12p	10p
OA47 Gold bonded Diodes, marked & tested	15p	15p	12p
1W Zener Diodes 6.8V, 7.5V, 24V, 27V, 30V & 43V	3p	3p	3p
10W Zener Diodes: 7.5V, 11V, 13V, 20V & 100V	5p	4p	3p
Micro Switches, S/P, C/O Popular size	20p	17p	15p
1 Amp Bridge Rectifiers 25V, RMS	25p	20p	15p

1 Amp Plastic Rectifiers. These are voltage, reverse Polarity and other rejects from the BY 127 range. Ideal for low voltage Power Units etc. Price £1 per 100.

## COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each Post and packing 23p.

## BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1 Post and packing 25p.

## NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Postage 13p Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	20	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

## F.E.T. PRICE BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

1-10 30p each, 10-50 25p each, 50+ 20p each.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

## FREE CATALOGUE AND LISTS FOR:-

ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

P.O. RELAYS **8 FOR £1**  
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

FREE! A WRITTEN GUARANTEE WITH ALL OUR SEMICONDUCTORS

# BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344


# JUST BEGINNING?

Then try out **8-Watt, 10-Transistor Stereo Amplifier R.137**

**ROC price**  
**£10.50**

Separate tone and volume controls for each channel, inputs for turntable (ceramic cartridge), tuner and tape. Attractive black crackle finish with brushed aluminium front. Frequency response: 70-20,000 Hz  $\pm$  3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 80mV; tuner/aux 80mV.

Normal retail price: **£14.70**

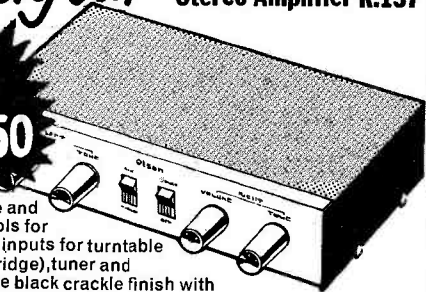


# FIRST STEP TO STEREO!

**5-Watt Transistor Stereo Amplifier Chassis R.123**

Completely self-contained, fully transistorised, mains-powered (240v AC) amplifier, needing only cabinet and knobs. Ideal for adapting mono players to stereo. Frequency response: 40-17,000 Hz  $\pm$  3dB. Output: 2.5 watts per channel @ 8 ohms. Input: Phono 600mV.

Normal retail price: **£7.30**

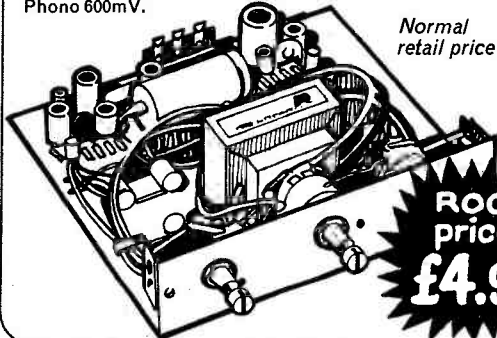

**ROC price**  
**£4.95**

# SOUNDS SENSATIONAL

**AM/FM/MPX Stereo Tuner Amplifier R.124**

A top quality amplifier with facility for receiving stereo broadcasts. Separate bass and treble controls, automatic frequency response, stereo headphone socket, output power: 8 watts. FM frequency range 88-108 MHz; AM frequency range 535-1605 K Hz. Inputs for turntable (ceramic cartridge) and tape. Frequency response: 50-10,000 Hz  $\pm$  3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 200mV, tape 100mV. FM: Sensitivity 20 $\mu$ V, stereo separation 26dB, image rejection 55dB. AM: Sensitivity 300 $\mu$ V.

Normal retail price: **£42.00**

**ROC price: £29.95**




# World wide reception

**Professional Solid-state, Four-band Communications Receiver R.135**

Fully transistorised with continuous coverage from 555K Hz to 30 M Hz in four bands (with illuminated bandspread for 160-10 metres). Incorporates internal speaker, automatic noise limiter, SSB/AM/CW switch, AVC switch, S Meter, Receive and Standby switch, external socket for headphone or speaker, bandspread control, BFO control, on/off/AF gain, band selector, antenna trimmer and RF gain. Runs off 240 v AC, batteries or any 12 v DC negative ground source. Frequency ranges (in MHz): Band A, 535-1.6; B, 1.55-4.5; C, 4.5-13; D, 13-30. Sensitivity: 0.5 $\mu$ V @ 30mHz. Bandspread: 10-160 metres.

Normal retail price: **£65.00**

**ROC price: £45.00**

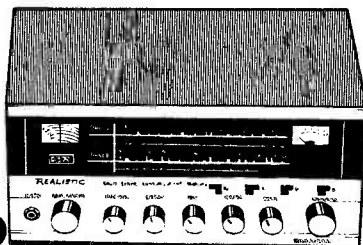


# AMAZING OFFER!

**Stereo Cassette Tape Unit R.142**

Complete stereo record and playback unit with line and microphone inputs. Fitted with tape counter, separate pause control, recording level metres for each channel, pop-up cassette ejection. Supplied complete with two pencil microphones. Wow & flutter better than 0.3%, frequency response 100-10,000 Hz. Tape speed: 1 1/2 IPS, 4.75 CMS. Rewind time: Better than 60 sec (C.60 cassette).  
Normal retail price: **£65.00**

**ROC price**  
**£49.50**

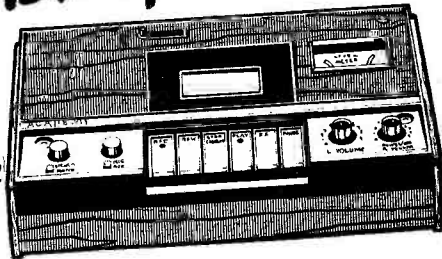


# We don't want you to

Every piece of electronic or audio-equipment we sell is built to our specifications. It comes complete with a Guarantee. And it's tested before it leaves us.

We bend over backwards in our advertising to make sure everything we say is factually accurate. But, buying mail-order, even though you're buying from us, we accept you could still end up with a piece of equipment that's not exactly what you wanted. And we think that's unfair.

# FANTASTIC BARGAIN

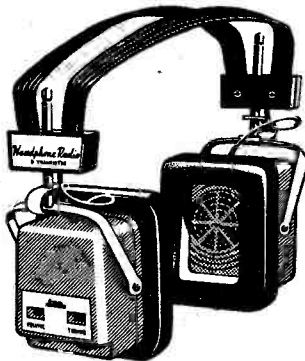


**Headphone Radio R.143**  
For completely private listening without the distortion of the ordinary earphone adaptor. Battery operated; PP3. Fully transistorised. Frequency range: 535-1600 K Hz, Medium Wave Band. Maximum output: 300mW.

**ROC price**  
**£6.90**

Normal retail price: £9.40

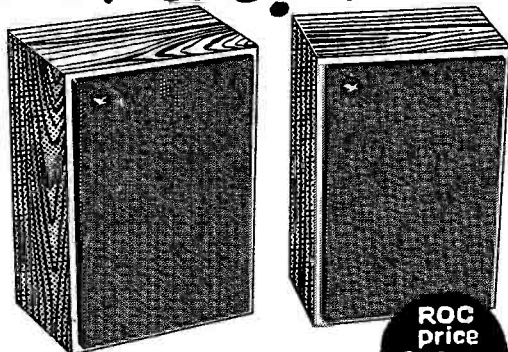**2 for the price of one!** **Matched Stereo Speakers R.446**



Heavily lagged teak finish cabinets each with large dual cone base unit and separate tweeter. Power handling: 10 watts peak; frequency range: 40-18,000 Hz, impedance: 8 ohms. Size: 14 x 8½ x 6½.

**ROC price**  
**£16.40**

Normal retail price: £19.60

## pay for your mistakes

So we've got a proposition for you. If you buy a piece of Roc equipment, and it's not quite what you expected, send it back within seven days, and as long as it's as good as new we'll give you your money back. O.K.?

Return of post mail-order service; orders over £10 post free, (U.K. only) add 25p for p & p to orders under £10. HP terms available.

**ROC ELECTRONICS LIMITED**

B. Jory Esq 193 Edgware Rd., London W2 1ET. 01-723 6211. Callers at Shop welcome 9-6 Mon to Sat (Thurs 1pm)

# STEREO headphones


*only*  
**£2.40**



Light and comfortable, with a frequency response of 30-15,000 Hz for real listening pleasure. Complete with jack plug, impedance 8-16 ohms.  
Normal retail price: £2.95
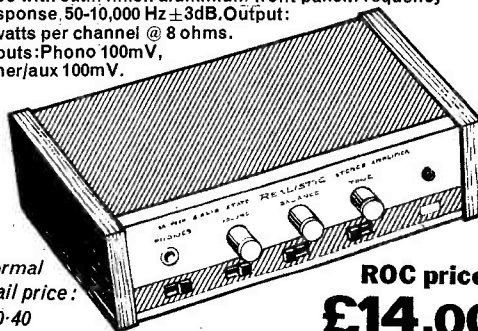
## Don't read this!

**10-watt Transistor Stereo Amplifier R.136**  
Ganged volume, balance and tone controls. Inputs for turntable (ceramic cartridge), tuner (see R.134) or tape. Oiled walnut case with satin finish aluminium front panel. Frequency response: 50-10,000 Hz ± 3dB. Output: 5 watts per channel @ 8 ohms. Inputs: Phono 100mV, tuner/aux 100mV.



Normal retail price: £20.40

**ROC price:**  
**£14.00**

## The Perfect match!



Matching unit to the R.136 amplifier. Covers AM and FM tuning bands with automatic stereo signal light. FM frequency range: 88-108MHz; AM frequency range: 535-1605kHz. FM: Sensitivity 5µV, stereo separation 25dB @ 1kHz, image rejection 50dB. AM: Sensitivity 250µV.

Normal retail price: £28.60

**ROC price**  
**£22**




## High Salary A Dream House A New Car And A Secure Future

Get into the Computer Industry the fast and easy way.

Now for the first time, anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a **computer operator in only 4 weeks** — and can earn £2,000 ++ p.a.

How? We are the only commercial training organisation in the U.K. permitted to use the famous 'Eduputer'.

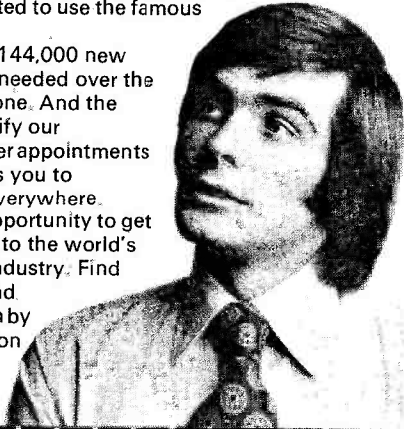**JOBS GALORE!** 144,000 new operators will be needed over the next five years alone. And the moment you qualify our exclusive computer appointments bureau introduces you to computer users everywhere. This is your big opportunity to get out of a rut and into the world's fastest growing industry. Find out more **FREE** and without obligation by posting this coupon **TO-DAY.**



### London Computer Operators Training Centre

**C19, Oxford House, 9/15, Oxford Street, London, W1.**  
Telephone: 01-734 2874  
**127/131 The Piazza, Dept. C19, Piccadilly Plaza, Manchester 1.** Telephone: 061-236 2935.

Please send me your **FREE** illustrated brochure on exclusive Eduputer 'hands on' training for computer operating.

Name

Address

Tel

### BATTERY/MAINS

SUPERHETERODYNE

## PORTABLE RECEIVER

**8 WAVEBANDS.** The most exciting radio ever! Picks up ALL THE USUAL BBC Programmes. All the new local radio stations. \*Continental. \*World-wide transmissions. \*Pop Pirate. \*Radio Mags. \*Aircraft. \*Shipping. \*Police. \*Taxi. \*R.A.C. \*A.A. \*Fire Brigades. \*T.V. Sound. \*Ambulances and 1,000s more. **THE BEST PORTABLE RADIO EVER MADE!** We think so. What radio priced at under £120 gives you such a varied choice of transmissions? As well as the standard long and medium wavebands it has three shortwave bands (including the Marine and Trawler Band) AND NO LESS THAN THREE V.H.F. BANDS — truly a complete **WORLD-WIDE** communications Receiver. Hours and hours of enjoyable listening **JUST THINK!** One minute you can be listening to your favourite B.S.C. programme and then — at the flick of a switch — you can tune into the control tower and hear a crippled airliner being talked down to safety. Or listen to the trawlers and Ocean-going liners! Eavesdrop on the taxi-cabs, fire brigades, ambulances, A.A., R.A.C. and 100s of other R.T. mobiles — even your local police! Extensive shortwave coverage can give you Australia, Pakistan, Luxembourg, North America, Far East, etc., etc. you name it — it gets it! Manufactured by one of the world's leading specialists in communications and T.V. equipment each set carries a **FULL 3-YEAR WRITTEN GUARANTEE.** Beautifully finished in teak wood and stainless steel — will add distinction to any living room. Completely portable 12in. x 9in. x 4in. using standard batteries — or can be plugged directly into mains. 14 transformers, 7 diodes, 1 thermister, r.f. output, 1,200 mW output, internal ferrite rod aerial PLUS two external telescopic antennae — with sockets for additional aerials or car aerials. Automatic Frequency Control — locks onto a station and ensures Drift Free reception. Very latest sliding tone and volume controls. Fine squelch control. Hi-Frequency earphones which automatically cut out the main speaker when in use, local DX switch. **FREQUENCIES:** Long W 150-350 Kcs. Medium W 340-1605 Kcs. Marine 16-4 Mcs. Short W 1-37 Mcs. Short W 2-722 Mcs. F.M. (V.H.F.) 88-108 Mcs. Aircraft (V.H.F.) 108-136 Mcs. Public Service (V.H.F.) 148-174 Mcs.

**NOT JUST A RADIO — BUT A COMPLETE COMMUNICATIONS RECEIVER**

**THE ULTIMATE in communications Receivers** — used by professionals and Amateur Enthusiasts all over the world. **INSTANT CASH REFUND** if not overwhelmed by the superb tone, clarity and performance range


CASH PRICE

**£47.50**

Plus 50p post & packing or sent for £12.50 deposit and 6 monthly payments of £7. (Total Credit Price £54.50 plus 50p p. & p.). Refund guarantee.

### SCIENTIFIC AND TECHNICAL SERVICES (P.W.2).

507-511 London Road, Westcliff, Essex.

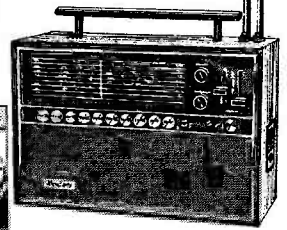

## FANTASTIC BARGAIN OFFER! TRANSEUROPEAN

Transistorised Stereophonic High Fidelity AM FM Tuner Amplifier System.




This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM, medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in matching elliptical speakers. A complete Hi-Fi Stereo Radiogram at less than half normal price.

Easily fitted no technical knowledge necessary.

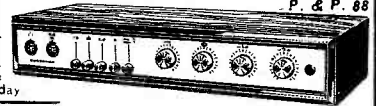**SPECIAL OFFER £44**

P. & P. 88

Credit Terms available. First monthly payment of £5.83 followed by 9 monthly payments of £4.95. Total Credit Sale Price £49.50. Send £5.83 today



### FABULOUS VALUE

Hi-Fi stereo at a new low. System Ten-Ten; 4 speed BSR autochanger with cue and pause control plus solid state amplifier, 20 watt total output. Frequency response 20-20,000 Hz. Two elliptical speakers in book shelf enclosures — 100% complete.

**ONLY £4.93 DOWN**

CREDIT SALE TERMS: Send £4.93 (being the first of TEN monthly payments of £4.05 plus 88p Carriage and Packing). To be followed by NINE monthly payments of £4.05 (Total Credit Sale Price £40.50)

**EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.**

**CALLERS WELCOME** PLEASE SEND ME FREE DETAILS OF YOUR RANGE


Name  Address  P10/71

Post coupon NOW for... **FREE** leaflets

**LEWIS radio** 100, Chase Side London N14  
Tel: 01-886 3733/9666


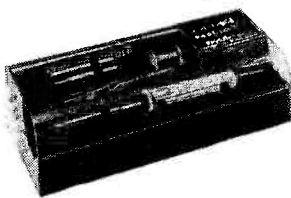
# cut out this coupon and answer your soldering problems



### SK1 SOLDERING KIT

In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted with  $\frac{3}{16}$ " bit. Spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder".

£2.75



### SK2 SOLDERING KIT

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with  $\frac{3}{16}$ " bit, 2 spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".

£2.40



Model CN 240/2  
- 15 watts  
- 240 volts

Fitted with nickel plated  $\frac{3}{32}$ " bit and packed in handy transparent box.


£1.70



ES240 D 25 watt  
soldering iron

In transparent display pack, fitted with long life iron-coated bit  $\frac{1}{8}$ " diam. Interchangeable spare bits  $\frac{3}{32}$ ",  $\frac{1}{16}$ ",  $\frac{1}{4}$ " (extra) available. Improved design to ensure strong and reliable high speed iron. Heats up in 2 minutes.

£1.83

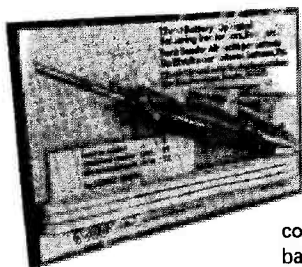

### M.E.S. Battery-operated 12 volt soldering iron

Complete with 15 ft (4.50m) lead, 2 heavy gauge clips for instant

connection to car battery and a guide 'How to Solder'. Packed in strong plastic wallet.

£1.95



from electrical and radio shops or by Free Post (No stamp required) from ANTEX Ltd. FREE POST. PLYMOUTH, PL1 1BR Tel: (0782) 67377/8

- Please send the ANTEX colour catalogue.
- Please send the following: .....

I enclose cheque / P.O. / Cash (Giro No. 2581001)

..... NAME .....

..... ADDRESS .....

.....

PW10

# LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on tin. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.

We still do the well known Shelley and Caxton column speaker systems.




## STEREO HEADPHONE JUNCTION BOX

Simple unit connects direct to amplifier and speakers to give attenuated headphone output, has 2 position switch to give headphones only—speakers only. Only £1.37 each P & P 12½.
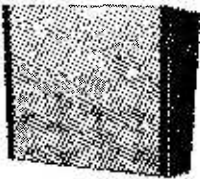
## CARTRIDGES-Stereo

Sonotone 9TA H/C Diamond £2.40, Ronette S105 Medium Output, £1.40, S106 High Output £1.40, Acos GP93/1 Sapphire, £1.90, GP94 1 Sapphire, £2. TA700 equivalent to B.S.R. SX1M, £1.75. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7np on each.



## DUDLEY


11" x 9½" x 5" deep, tapering to 3½" deep covered in Black Reseal and Mottled fawn Vynair £2.10 P & P 25p.

## SPEAKERS

E.M.I. 13½ x 8in, 3 ohm £2.50, 15 ohm. P. & P. 30np. E.M.I. 13½ x 8in, fitted two 2½in. tweeters, 15 ohm £4.50. P. & P. 30np. E.M.I. 13½ x 8in. (15 ohm) Hi-Fi quality £6.25. P. & P. 30np. Bakers 12in. 25 watt 8 and 15 ohms £7. P. & P. 30np. Eagle Crossover 86np. P. & P. 5np.
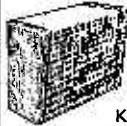
## VYNAIR

Widths from 50 to 54 in., 75np yd. off roll. P. & P. 10np, ½ yard 40np. P. & P. 10np. Send 5np stamps for samples.



## IMP

Wedge shaped extension speaker 7½ x 6½ x 4in. (max.). Covered in walnut wood grain cloth with mottled Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only £1.25. P. & P. 36np each

## CARTRIDGES-Mono


GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. T.T.C. Crystal High Gain, 75np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.

## SPEAKER MATCHING

TRANSFORMERS 3, 7, 15 ohms, 8 watt, 70np. P. & P. 17np.
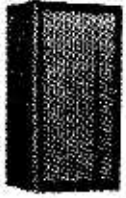
## FARRADAY

5½" x 11" x 4½" covered in White, Green or Black rexine or Teak cloth with Silver coloured metal front £2.90 P & P 25p.




## CLARENCE



11" wide x 8½" x 4½" deep with volume control covered in Black rexine and Mottled Vynair. £2.25 P & P 25p.

## NOCTURNE 73 STEREO SYSTEM

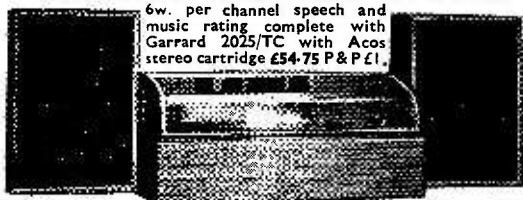

6w. per channel speech and music rating complete with Garrard 2025/TC with Acos stereo cartridge £54.75 P & P £1.

# BROADWAY ELECTRONICS

82 MITCHAM ROAD, TOTTENHAM BROADWAY, LONDON S.W.17 01-672 9884 (Closed all Wednesday)

# M. & B. COMPONENTS (LEEDS) LTD.

(INCORPORATING M. & B. RADIO)

PO Box 125, 38 BRIDGE END, LEEDS 1 Telephone 0532-35649

**MB2/20A TWO METRE TRANSCEIVER.** Rx Tuneable over 2 metre band, 20 watts RF output AM modulated. Ideal for mobile or fixed station. Only requires connection to speaker, aerial and 12v DC supply to become fully operational. (Full details on list.) £50 inc. carr. U.K.

**AD 108D MARCONI COMMUNICATION RECEIVERS.** 9 miniature valves plus Xtal filter and tuneable BFO covering 260 to 510 Kc/s and 2 to 18.5 Mc/s in 4 switched bands. Slow motion dial with logging scale. Originally intended for 24v DC operation but supplied with details for converting to mains operation. In very clean, tested condition. £15.50 inc. carr. U.K.

**EX-ARMY 88 WALKIE TALKIES.** 3 channel, less handset. Untested but complete and in clean condition. With circuit. ONLY £4.75 or £8 for 2 inc. carr. U.K.

**6 TO 12 VOLTS DC TRANSISTOR CONVERTOR.** Brand new 6v DC input, 12v DC output at 4 amps conservatively rated. Ideal VW owners. £5.40 inc. carr. U.K.

**9 TRANSISTOR 455 KC/S IF STRIPS.** Ideal basis for receiver. BARGAIN. Only £1.20 inc. carr. U.K.

**GEIGER COUNTERS.** Well known contamination meter comprised of main unit fitted with meter marked in Milli Rontgens/hour, probe lead and carrying case. Audio output available from socket on front panel. Supplied new or as-new condition. Model I fitted with vibrator PSU using 5 pen cell batteries. £4.85 inc. carr. U.K.

**12v INVERTER TRANSFORMERS.** Complete with circuit to build inverter to give 350v output at 300 m/a. £2.20 inc. carr. U.K.

Send S.A.E. for complete list of items in stock.

# VALVES

SAME DAY SERVICE  
NEW! TESTED! GUARANTEED!

SETS 1R5, 1B5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL82, DL94. Set of 4 for £1.02, DAF96, DF96, DK96, DL96, 4 for £1.48.

1R5	28	25U4GT	57	DY86	26	EL600	62	PCL82	83	UABC80	88
1B5	28	30C1	29	DY87	26	EM80	41	PCL83	69	UAF42	51
3T4	18	30C15	63	DY802	40	EM81	41	PCL84	85	UBC41	52
384	28	30C17	30	EAB030	82	EM84	32	PCL85	42	UBF80	34
3V4	37	30C18	63	EAF42	50	EM87	38	PCL86	40	UBF89	33
5U4G	26	30F5	70	EB41	40	EY51	38	PCL88	72	UCC84	38
5V4G	26	30FL1	68	EB91	41	EY86	81	PCL800	77	UCC85	38
5Y3GT	28	30FL12	70	EBC33	40	EZ40	43	PEN44	77	UCF80	34
5Z40	26	30FL14	70	EBC41	44	EZ41	43	PEN36C	70	UCH42	62
6J90L2	58	30L1	30	EB300	22	EZ90	22	PFL200	63	UCB1	32
6AL5	11	30L15	59	EBF80	85	EZ81	23	PL56	49	UCL82	34
6AM6	18	30L17	71	EBF89	81	GZ30	35	PL81	48	UCL83	35
6AQ5	26	30P4	65	ECC81	17	GZ32	42	PL81A	49	UF41	66
6AT6	22	30P12	77	ECC82	20	GZ34	60	PL82	81	UF89	31
6AU6	21	30P19	66	PCC83	35	KT41	77	PL83	83	UL41	60
6BA6	21	30P11	68	ECC85	26	KT61	65	PL84	30	UL44	£1.00
6BE6	28	30PL13	78	ECC804	67	KT66	81	PL60	60	UL84	33
6BJ6	41	30PL14	87	ECP80	30	LN319	62	PL604	64	UM84	32
6BW7	55	30PL16	90	ECP82	28	LN829	72	PM84	85	UY41	40
6CD6G	£1.07	35L6GT	45	ECH55	30	LN389	68	PX25	£1.00	UY85	28
6F14	42	35W4	25	ECH42	61	N78	87	PY32	65	VP4B	77
6F23	70	35Z4GT	25	ECH81	29	P61	46	PY33	65	Z77	22
6F25	60	807	45	ECH83	40	PAB030	84	PY81	27	Transistors	
6K7G	12	6063	62	ECH84	38	PC86	82	EY82	85	AC107	17
6K8G	17	AC/VP2	77	ECL80	32	PC88	48	EY83	28	AC127	18
6Q7G	28	B349	65	ECL82	31	PC96	42	EY88	38	AD140	87
6N7GT	30	B729	62	ECL86	38	PC97	40	PY800	84	AF115	20
6V6G	31	CCH35	67	EF39	38	PC900	33	PY801	84	AF116	20
6X4	25	CY31	32	EF41	60	PC84	30	R19	30	AF117	20
6X4GT	28	DAF91	22	EF80	23	PC85	27	R20	69	AF118	48
7B7	38	DAF96	36	EF85	28	PCC88	42	U25	65	AF125	17
10P13	58	DF33	38	EF86	31	PCC89	46	U26	69	AF127	17
12A7	17	DF91	18	EF89	29	PCC189	48	U47	66	OC26	25
12AH8	22-26	DF96	38	EF91	13	PCC805	69	U49	59	OC44	12
12AT7	17	DH77	22	EF183	23	PCF80	23	U50	65	OC45	12
12AU6	29	DK32	37	EF184	31	PCF82	31	U52	31	OC71	18
12AU7	20	DK91	28	EH90	37	PCF86	45	U78	24	OC72	12
12AX7	23	DK92	42	EL33	55	PCF800	67	U91	80	OC75	13
19BG6G	87	DK96	38	EL34	45	PCF801	81	U93	42	OC81	12
20F2	67	DL35	40	EL41	54	PCF802	44	U21	66	OC81D	12
20P2	30	DL92	26	EL54	23	PCF809	63	U301	45	OC82	12
20P4	92	DL94	27	EL90	28	PCF806	68	U329	66	OC82D	12
25L6GT	20	DL96	38	EL95	33	PCF808	70	U801	98	OC170	22

# READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.

# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

**10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER, BAND, VHF AND AIRCRAFT BAND**


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 7in x 4in Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

**£8-50**

P. P. & Ins. 50p

(Overseas P. & P. £1)

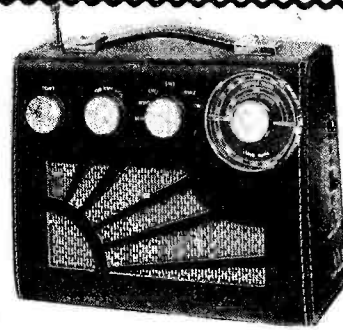

### ROAMER EIGHT Mk I



**NOW WITH SWITCHED TONE CONTROL**

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 7in x 4in. Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p. (Overseas P. & P. £1)


### ROAMER SEVEN MK IV



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy R.F. Transistors. 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

Total building costs **£5-98** P. P. & Ins. 41p. (Overseas P. & P. £1)


### ROAMER SIX

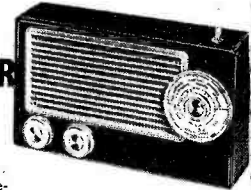

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£3-98** P. P. & Ins. 26p. (Overseas P. & P. £1)


### POCKET FIVE

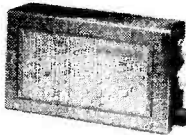

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & Ins. 21p. (Overseas P. & P. 65p)

### TRANSONA FIVE

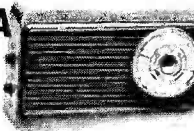


**NOW WITH 3in SPEAKER**

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—3 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone 3in. moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P. P. & Ins. 22p. (Overseas P. & P. 63p)

### TRANS EIGHT

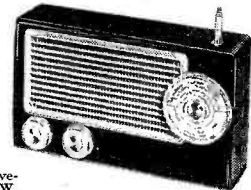

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P. P. & Ins. 31p. (Overseas P. & P. £1)

## NEW! "EDU-KIT"

**BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.**

**COMPONENTS INCLUDE:**

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4"x2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 1 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including Case and Plans **£5-50** P. P. & Ins. 31p. (Overseas P. & P. £1)



**FULL AFTER SALES SERVICE**

\* Callers side entrance Barratts Shoe Shop  
\* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN  ROAMER SEVEN   
ROAMER EIGHT  TRANS EIGHT   
TRANSONA FIVE  ROAMER SIX   
POCKET FIVE  EDU-KIT

Parts price list and plans for .....

Name .....

Address .....

PW.34

## DISCOTHEQUE EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MKII AMPLIFIER PR. FANE POP 25/2 SPEAKERS Terms: Deposit \$5.50 and 9 monthly payments of \$4.72 (Total \$47.98)	\$33.50 \$13.50 \$47.00	PACKAGE PRICE \$44 carr. \$1
F.A.L. PHASE 50 MKII AMPLIFIER PR. FANE POP 50 L/SPEAKERS Terms: Deposit \$10.50 and 9 monthly payments of \$5 (Total \$55.50)	\$33.50 \$21 \$54.50	PACKAGE PRICE \$49.50 carr. \$1
F.A.L. PHASE 100 AMPLIFIER PR. L125 50W L/S in cabinets Terms: Deposit \$22 and 9 monthly payments of \$11 (Total \$111)	\$61.95 \$59.90 \$121.75	PACKAGE PRICE \$110 carr. \$1.50
F.A.L. PHASE 100 AMPLIFIER 4 FANE POP 50 L/SPEAKERS Terms: Deposit \$14 and 9 monthly payments of \$10 (Total \$104)	\$31.95 \$22 \$103.95	PACKAGE PRICE \$94 carr. \$1.50

## F.A.L. DISCOTHEQUE CONSOLE



Incorporating twin Garrard SP25 Mk.III turntables and Goldring CS90 Ceramic Cartridges with diamond styli. Separate Vol. Bass and Treble controls for each turntable plus MONITORING FACILITIES. Black Rexine covered Cabinet with lid.

**£65** Carr. \$1.25 (Total \$71.80)

Terms: Deposit \$11 and 9 monthly payments of \$6.70 (Total \$71.80)

## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction.

**£5.75** Carr. 30p

OR SENIOR 15 WATT INC. £6.75 Carr. 30p  
HF126 15,000 LINE SPEAKER carr. 35p

## AUDIOTRINE HIGH FIDELITY LOUSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. Please state choice. Exceptional performance at low cost.

HF801D 8" SW £2.71 HF180D 12" 15W £4.75  
HF102D 10" 18W £3.40 HF128 12" 15W £5.60  
HF120 12" 15W £4.25 HF128D 12" 15W £5.90

## FANE 807 HIGH FIDELITY LOUSPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.T.C. cone surround and low throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Impedance 3 or 8-15 Ω. Gauss 10,000. Remarkable value.

**£3.50**

## HI-FI SPEAKER ENCLOSURES

Modern design. Teak veneer finish. Acoustically lined. All sizes approx. Carr. 30p. per enclosure  
JES Size 16 x 11 x 9in. Pressurised. Gives pleasing results with 8in. Hi-Fi speaker. **£5.35**  
SES For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported. **£6.47**  
SE10 For outstanding results SE12 For excnt prfmanc with 12in. with 10in. Hi-Fi 'spkr' HI-FI speaker and Tweeter. **£7.87**  
Size 24x16x10in. P.t'd. Size 25 x 15 x 10in.

## R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v and 90v, where A.C. mains 200/250v. 50c/s is available. Complete kit with diagram **£3** Assembled ready for use **£3.50**

## R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 6 1/2in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.50** Carr. 40p.

OR FACTORY BUILT WITH 12 MONTHS GUARANTEE **£9.75**

## R.S.C. A11 HI-FI 12-14 WATT AMPLIFIER

PUSH-PULL OUTPUT. Two input sockets with sep. vol. controls for mixing. High sensitivity, 5 valves. Bass and treble controls. Response ± 3dB 30-20,000 c/s. Hum level -60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments etc.

SAE A.C. mains. For 3 & 15 ohm spkrs. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 60p SAE for leadst. Twin handled metal cover **£1.75** Factory built **£14.75** or Dep. \$3 and 9 mthly pymts of **£1.60** (Total **£17.40**)

## R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine Vynair  
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

**TYPE C485 25-30 WATTS**  
Fitted four 8" high flux 8 watt speakers.  
Overall size approx 48 x 10 x 5 in. Carr. 60p  
Terms: Dep £3 and 9 monthly payments £17.75

**TYPE C4125 50 WATTS**  
Fitted four 12" 11,000 line 15 watt speakers: Overall size approx 56 x 14 x 9 in. Carr. 75p  
payments £2 (Total \$81) **£27.50**

**TYPE C4100 100 WATTS** inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx 68 x 16 x 10" Acoustically filled and pressurized. Terms: Dep. £7.50 and 9 mthly. pymts. £6.45 (Total \$56.55). Carr. £1 **£50.50**

## 30 WATT HI-FI AMPLIFIER FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP.

A 2 or 4 input, 2 vol. control HI-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet.

Terms: Deposit £3.70 and 9 monthly payments of £2.10 (Total £22.60) **£19.95** Carr. 65p

## HIGH QUALITY LOUSPEAKER UNITS

IN TEAK VENEERED CABINETS

L13 13" x 8" 10 Watt L12 12" Also  
10,000 lines 3 or 15 25 WATT supplied  
ohms. State impedance 10,000 lines Rexine  
required. 15 ohms. covered

**£5.25** carr. 40p **£10.50** carr. 45p

L125 50 WATT  
Two tone Rexine and Vynair finish. Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Or deposit £4 and 9 monthly payments of £3.35. Total £34.15 Carr. 75p **£31** Carr. 75p

## R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalist, gram, radio, tape. Peak Output rating. Loudspeaker unit optional horizontal or vertical mounting. **£60**

★ Two extra heavy duty 12in. Loudspeakers. Carr. £1.50  
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms Deposit £16 and 9 monthly payments of £5.75 (Total £67.75)

## FAL PHASE 50 MKII AMPLIFIER 50W FAL PHASE 100 AMPLIFIER 100W

Solid state. 4 Separately controlled inputs. Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/s 3-30 ohms. Size 17" x 7" x 7" 200-250v. A.C. mains. Output 60 watts music rating. Or deposit £6 & 9 monthly payments £33.50 Carr. 65p

Solid State. 4 Separately controlled inputs Plus master volume control. Ind. Bass and Treble Controls. Output for speaker/s 3-30 ohms. Protective circuit to guard against damage from accidental shorts. I.H.F.M. Output rating. Or deposit £12 & 9 monthly payments £61.95 Carr. 75p Send S.A.E. for leaflets.

## FANE ULTRA HIGH POWER LOUSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE  
High flux ceramic magnets. Heavy cast chassis. All carr. free.

<b>'POP' 100</b> 18" 100 Watt 14,000 gauss 8/15Ω <b>£22.05</b> Dep. £6 and 9 monthly payments £2-10 (Total £115)	<b>'POP' 60</b> 15" 60 Watt 14,000 gauss 8/15Ω <b>£12.90</b> Dep. £3.80 and 9 monthly payments. £1.80 (Total £115)	<b>'POP' 50</b> 12" 50 Watt 13,000 gauss 15Ω <b>£10.50</b> Dep. £2 and 9 monthly payments £1.16 (Total £12.85) Pair suitable all purposes
---	---	---

FOR BASS GUITAR, ELECT. ORGAN, ETC.

## F A N E LOUSPEAKERS 'POP' 25/2

12in. 25 WATT  
Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). **£6.75** Carr. free or Dep. £1 and 9 mthly payments 75p (Total £7.75)

## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Hum level -70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves 6F86, 6F66, EC638, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 35 millivolts. For High Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. to be used for mixing purposes, 200-250 v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete kit of parts with wiring diagram and instructions. Twin-handled perforated cover **£15.75** Carr. 65p  
TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22.80). Send S.A.E. for leaflet.

## RSC TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary

Primaries 200-250v. 50c/s. Screened  
MIDGET GAMBUR TYPE 2 1/2 x 2 1/2 in. 99p  
250v. 60mA, 6.3V. 2a. £1.05  
250-0-250v. 60mA, 6.3V. 2a. £1.05  
FIXED SHROUDED UPRIGHT MOUNTING  
250-0-250v. 60mA, 6.3V. 2a., 0-5-6.3V. 2a. £1.40  
250-0-250v. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.20  
300-0-300v. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.20  
300-0-300v. 180mA, 6.3V. 4a., c.t., 6.3V. 1a. £2.45  
For Mullard 610 Amplifier £2.45  
250-0-250v. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.20  
350-0-350v. 150mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.65  
425-0-425v. 200mA, 6.3V. 4a., c.t., 5v. 3a. £2.45  
425-0-425v. 200mA, 6.3V. 4a., 6.3v. 3a., 5v. 3a. £5.10  
450-0-450v. 250mA, 6.3V. 4a., c.t., 5v. 3a. £5.50  
TOP SHROUDED DROP-TYPE TYPE  
250-0-250v. 70mA, 6.3V. 2a., 0-5-6.3V. 2a. £1.35  
250-0-250v. 100mA, 6.3V. 3.5a. £1.55  
250-0-250v. 100mA, 6.3V. 2a., 6.3v. 1a. £1.60  
350-0-350v. 80mA, 6.3V. 2a., 0-5-6.3V. 2a. £1.65  
250-0-250v. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.20  
300-0-300v. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.20  
300-0-300v. 150mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.20  
Suitable for Mullard 610 Amplifier £2.60  
350-0-350v. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.20  
450-0-450v. 100mA, 6.3V. 4a., 0-5-6.3V. 3a. £2.60

FILAMENT OR TRANSISTOR POWER PACK  
Types 6.3v. 1.5a. 49p; 6.3v. 2a. 54p; 6.3v. 3a. 76p;  
6.3v. 6a. £1.30; 12v. 1a. 55p; 12v. 2a. 62p;  
1.5a. £1.35; 0.9-1.8v. 1.5a. £1.10; 0.12-25-43v. 2a. £1.76  
CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. 89p;  
2a. £1.10; 3a. £1.25; 6a. £1.45; 6a. £1.65; 8a. £2.00  
AUTO (Step UP/Step DOWN) TRANSFORMERS  
0-110/120v. 200-250-250v., 60-80 watts £1-10;  
160 watts, £1.90 250 watts £2.75; 600 watts £6.75.  
OUTPUT TRANSFORMERS  
Standard Pentode 6.000 Ω or 7,000 Ω to 3 Ω 50p  
Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 85p  
Push-Pull 10 watts 6V6, ECL86 to 3 or 3.5, 8 or 15 Ω £1.37  
Push-Pull EL84 to 3 or 15 Ω 10-12 watts £1.85  
Push-Pull Ultra Linear for Mullard 610, etc. £2.20  
Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω £1.99  
Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £3.30  
SMOOTHING CHOKES 150mA, 7-10H, 250 Ω 70p; 100mA, 10H, 200 Ω 60p; 80mA, 10H, 350 Ω 60p; 60mA, 10H, 400 Ω 75p.  
SELENIUM RECTIFIERS F. W. (Bridged)  
All 6/12v. D.C. output. Max. A.C. input 18v.  
1a. 25p. 2a. 35p. 3a. 50p. 4a. 65p. 6a. 80p.

# Introducing R.S.G. MkIII SUPER 30 HI-FI STEREO AMPLIFIER

A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE. REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.

Only high grade components by leading manufacturers. COMPLETE KIT OF PARTS **£25** Carr. 65p

Or FACTORY BUILT with 12 months guarantee Dep. **£3-75** and 9 monthly payments **£3-50** (Total **£37-25**)  
Or FACTORY BUILT in cabinet as illustrated Dep. **£8** and 9 monthly payments **£3-88** (Total **£40-74**)

PRINTED CIRCUITRY, TWENTY SILICON TRANSISTORS. FOUR DIODES, FOUR RECTIFIERS. TECHNICAL DETAILS (Applying to each channel where appropriate) CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble, and Balance. Plus Ceramic/Mag P.U. Switch.



- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETED MODEL VENEERED IN SATIN TEAK, SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE.
- ★ WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms.  
HUM & NOISE - 75dB Min. Vol. - 65dB Full Vol. HARMONIC DISTORTION  
FREQUENCY RESPONSE: -3dB 7Hz to 70KHz 0.1% at 1000 Hz 10 Watts  
TREBLE CONTROL: +16dB to -12dB at 14KHz  
BASS CONTROL: +17dB to -16dB at 40Hz  
SENSITIVITIES: Disc Mag. 2.5mV. Ceramic 35mV. Radio 120mV. Tape 120mV.  
REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

## R.S.G. HIGH FIDELITY STEREO PACKAGE OFFERS

- ★ Four fully wired units ready to 'plug in.'
  - ★ SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
  - ★ GARRARD SP25 MKIII Turntable on Plinth with cover
  - ★ GOLDRING CS90 Ceramic Pick up Cartridge with diamond stylus
  - ★ PAIR OF STANWAY II Speaker Units
- £79-80**  
Total Price Carr. £1-50

Matching as recommended for optimum performance. Send S.A.E for coloured brochure showing other money-saving offers.



Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.

ATTRACTIVE TEAK or AFROBROSIA VENEERED CABINETS and PLINTHS

- ★ TA12 AMPLIFIER 6.5 + 6.5 watt in veneered housing
  - ★ GARRARD SP25 MK III Player unit on Plinth
  - ★ GOLDRING CS90 Ceramic P.U. Cartridge with diamond stylus
  - ★ PAIR OF DORCHESTER Loudspeaker Units
- £58**  
Special Total Price Carr. £1-25

Or Deposit **£7-15** and 9 monthly payments **£6-35** (Total **£64-30**). Trans. Plastic Cover **£3-15** extra.

Package as above but with Garrard 8000 Auto-changer and Sonotone 9FA Ceramic Cartridge in lieu of SP25 and CS90 **£51-75** Carr. £1-25

Or Deposit **£6** and 9 monthly payments **£5-70** (Total **£57-30**) Trans. Plastic cover **£3-15** extra.

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
  - ★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
  - ★ Goldring Magnetic P.U. Cartridge.
  - ★ Pair of Stanway II speaker units
- £96-75**  
Special Total Price Carr. £1-50

### TERMS AVAILABLE ON ALL PACKAGE OFFERS


### 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in. COMPLETE KIT **£22** Carr. 63p
- ★ Response 30-20,000 c.p.s. Impedance 15 ohms
- ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. **£4-50** and 9 monthly payments **£2-25** (Total **£24-75**).

#### DEMONSTRATIONS AT ALL BRANCHES
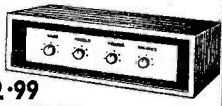
### R.S.G. G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Suitable for Crystal Pick-ups, etc., and for loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v A.C. mains operation. Attractive silver finished metal face plate & matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£9-99** carr. 40p.  
Or FACTORY BUILT IN TEAK **£12-99**  
VENEERED CABINET as illustrated **£12-99**  
or dep **£2-50** and 9 mthly pymnts. **£1-45** (Total **£15-55**).



### HIGH FIDELITY LOUSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.  
DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 3in. Dual Cone speaker. Imp. 3 or 15 ohms. **£9-45** Carr. 40p.  
STANWAY II Size 20 x 10 1/2 x 9 1/2in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives **£17-85** smooth realistic sound output. See 'package offers' for illustration

### R.S.G. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER FULLY TRANSISTORISED. SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge. Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & Knobs. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS. Factory built with 18 months guarantee **£19-50** or Deposit **£8** and 9 mthly pymts **£8-18** (Total **£82-85**). Or in Teak veneer housing **£15-50** Carr. 40p. **£23** Dep. **£8** and 9 mthly payments **£2-55** (Total **£25-95**). Send S.A.E. for leaflet



### R.S.G. PLINTHS

Superior Solid Natural Wood Construction for Record Playing units, cut for Garrard 1025, 2025, 3000, AT80, SP25 etc. **£3-15**  
WITH TRANSPARENT PLASTIC COVER **£6-30**



### SPECIAL HI-FI OFFERS

WHARFEDALE/F.A.L. 1 pr Wharfedale Super Linton Speakers, 1 F.A.L. Phase 32 15 + 15 watt Stereo Amplifier Total Rec. Retail Price **£67-70**  
**PACKAGE PRICE £66-50**  
Above brand new goods. Following have been unpacked for display purposes only:-  
**LEAK MINI-SANDWICH** (Teak finish) **£18**

ROGERS RAVENSBROOK STEREO AMPLIFIER **£39**  
TANDBERG 62X TAPE RECORDER (Stereo) **£88**  
GOLDRING GL68 Transcription Turntable and Pick-up **£14-50**  
GOODMANS AUDIOM 91 **£19-95**

### LOW DEPOSIT CREDIT TERMS

AVAILABLE ON PURCHASES OVER **£8** (KITS OF PARTS EXCEPTED)  
**INTEREST CHARGES REFUNDED**  
ON CREDIT SALES SETTLED IN 3 MONTHS

- BRADFORD** 10 North Parade. (Half-day Wed.) Tel. 25349
- BLACKPOOL** (Agent) O. & C. Electronics, 227 Church Street
- BIRMINGHAM** 30/31 Gt. Western Arcade (Half-day Wed.) Tel. 021-36-1279
- DERBY** 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON** 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH** 133 Leith St. (Half-day Wed.) Tel. 556 5766
- GLASGOW** 326 Argyle St. (Half-day Tues.) Tel. CITY 4158
- HULL** 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Hencorner Lane, Leeds 15. Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 25p extra under £2. 30p extra over £2 or as quoted. Trade supplied. S.A.E. please with enquiries. Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS

- 32 High Street (Half-day Thurs.) Tel. 56420 **LEICESTER**
- 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) **LEEDS** Tel. 28252
- 73 Dale St. (Half-day Wed.) Tel. CENTRAL **LIVERPOOL**
- 238 Edgware Road, W2 (Half-day Thurs.) Tel. 3573 **LONDON** PAD 1629
- 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 **MANCHESTER**
- 106 Newport Rd. (Half-day Wed.) Tel. 47096 **MIDDLESBROUGH**
- 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469 **NEWCASTLE UPON TYNE**
- 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 **SHEFFIELD**

### BC221 MAINS POWER UNITS

200/250v I/P, O/Ps 135v at 20 mA from electronic stabiliser also 6.3v AC for heaters. Uses 4 valves made to fit in battery compartment of unit with small control box with swt and fuses. Supplied new with circ and mains lead.

Price £6.00 plus 60p carr.  
Spares for above, set of 4 new valves £1.00  
New mains trans £1.50 both post paid.

### R.F. 26 TUNING UNITS

These tune 50 to 65 Mc/s use 3 valves I.F. O/P 7 Mc/s will mod up to 100 Mc/s fitted slow motion dial etc. Supplied in good cond. with circ. Price £2.10 plus 40p post.  
Rx unit 3645 for use with above £2.25 carr. paid

### METER UNITS

Radio altimeter units 6.5 mA F.S.D. 270° scale size front 3 3/4" sq. fitted on/off and range swt ideal for use as rev. counters; good condition.

Price 80p plus 15p post

### AMPLIFIER UNIT 115v 50c/s I/P

These are a small self contained unit, uses 3 valves 6X4 Rect, 6AK6 O/P and 12AX7 Amp; these are low impedance I/P & 500 ohm O/P, fully enclosed size 10 x 3 1/2 x 3 1/2". Supplied with circ. & mods. for 3 ohm O/P, ideal unit for beginner, Ex USAF surplus good cond. Price £2.50 plus 25p post. Small 230/110 trans for above 75p post paid.

### HEAVY DUTY MAINS TRANS.

Pria 200/220/240v 50c/s Sec 500-0-500 at 400 mA or can be connected to give 1 kV at 200 mA; varnish finish tag connections; size overall 5 1/2 x 5 1/2 x 4 1/2; supplied in new condition ex service.

Price £2.25 plus 40p post.

### POWER UNITS

These are a transistorised power unit high cycle I/P and contain 8 type 2S012A Silicon NPN pow trans (Texas); these are Vc 70v 1c 2a good to 2 Mc/s also 18 Silicon diodes 200 P.I.V. 5a to 8a large Ledex swt, large board with transistors, etc. misc potted trans supplied new crated, modern Guided Missile equip.

Price £4.50 plus 75p carr.

### MISC. ITEMS

Scope tube 3BP1 3" green screen with base and Mu Met shield and base connections £2.50. Crystal units 100 Kc high grade with base £1.40. Relays coil 14K 1p c/o sealed new ex equip also 24v 700 ohm 2p c/o sealed both 2 for 30p. Block conds 8uf 1Kv 2 for 90p. 8uf 750v 2 for 60p. Valves 6SN7 or 6SL7 5 for 50p. Relay panel with 4x min 2p c/o relays coil 1K new ex equip 55p. Diodes type GJ5M 300 P.I.V. 1 amp mounted on small h/s 8 for 40p. Miniature plug and sk 18 way with clamp and cover good quality 15p pair. L.V. Smoothing Conds 4000µf 50v 5 x 2" 50p. 2500µf 75v 4 x 2" 50p. 800µf 50v 5 x 1 1/2 30p all with fully insulated cases and fix brackets, good quality. I.F. strips 30 Mc/s wide band 10 valves miniatures, size 18 x 4 x 4". USAF surplus £1.80. Pre Amp for I.F. strip 90p. Relays coil 6/12v D.C. 1p N.O. rated 20a 40p. Control knobs to fit 1/2 shafts assorted 12 for 50p. Pot Cores LA66 4 for 50p. LA2503 Vinkors 4 for 50p. American 73 Radio Mag new back issues 8 for £1.15. Speaker units portable 8" unit in case 18 x 18 x 8" 3 ohm with 600 to 3 ohm trans new £2.90. Test unit with 2x LA2503 Vinkors 4 Sil Transis 4 min relays min valves etc. new boxed 85p. T.S.210 (test osc) covers 20 to 85 Mc/s in 4 bands with xtal check noise gen etc. reqs 250v ht and 6.3v with charts good cond. £3.90. Swt unit yax type 4p 4w 4b with 12 7/45pf trimmers 35p Tuning Cond air spaced 60pf with small drive 35p. EHT Cond. 1 x 5µf 2kV wk size 4 x 2 x 2" inc term 50p. Group board with 7x 400 P.I.V. 500 mA diodes, min relay II tant conds etc. new ex equip. 50p. OC16 med pwr transis P.N.P. type 2 for 25p. Transformers Pria 115/120v sc 850-0-850v at 600 mA or 1700v 300 mA potted type new Amer supplied in pairs £4.60. Circuit diagrams, 1392 Rx, 1155Rx, 1475 (88) Rx all 30p. Schemes CD513.2 £1.50. 13A, CD518 (CT316), Os-8, 50p ea. CT38 later series 50p.

All above prices include post or carr. All goods ex equipment unless stated otherwise. S.A.E. with enquiry

# A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9 5HL



### EX RENTAL TV'S

19" — £29.95

23" — £39.95

All Channels 405/625  
2 Years Guarantee.  
Free List by return.

17" Slim line TV's £11-95, 19" Slim line TV's £15-95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1-95. Daily demonstrations to personal shoppers.


### TEAK HI-FI STEREO CABINETS £14.95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1.00.

TRANSISTOR GANG CONDENSERS 30p. Miniature AM precision Tape Motors £1-95 famous German manufacturer. 200/250V. Post 20p.

Transistor Radio Cases: 25p each. Size 8 1/2" x 6 1/2" x 3 1/2". P. & P. 15p. SPEAKERS 50p 2 1/2" 8Ω BRAND NEW. P. & P. 5p.

### TV TUBES REBUILT. GUARANTEED 2 YEARS

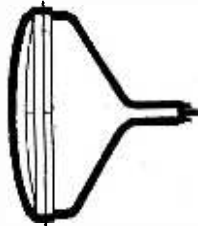

### TRANSISTORS Post Free

AC 128	AF 179	OC 81
AC 128	OC 44	OC 81D
AF 114	OC 45	
AF 117	OC 71	15p each

### POTENTIOMETERS 23p each

Double & Switched	500 KΩ/500 KΩ	3 1/2" shaft
Double & Switched	500 KΩ/100 KΩ	2" shaft
Double & Switched	1 MEG/100 KΩ	1 1/2" shaft

Post. & Pack. 5p.—4 for 10p

### KNOBS 100,000 to clear (Brand New)

100 assorted-Radio & T.V. knobs 50p. Postage 10p. (If you require sets 2 to 6 just ask)

14"—£3.95, 17" & 19"—£5.95,

21" & 23"—£8.45.

Exchanged Bowls. Carr. 53p.

## DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Phone 01-478 6001-2-3 Stamp for Free List

### Selections from FELSTEAD ELECTRONICS' List

(Sent free for stamped addressed envelope to address below)


Transistors etc. AC126 124p. AF115 20p. AF116 15p. AF117 20p. OA5 71p. OA10 71p. OA81 71p. OA85 71p. OC23 82p. OC25 80p. OC26 37p. OC28 42p. OC35 42p. OC44 14p. OC45 124p. OC71 124p. OC72 124p. OC75 124p. OC81 124p. OC81D 124p. OC82D 124p. OC170 20p. OC171 124p. Many more in list. S.D.R. BY110 800piv 14p. 6 amp series: BY213 300piv 20p. BY212 600piv 25p. BY211 900piv 30p. BY210 1200piv 35p. (Charges 5p up to 11, paid for 12 and over). Sub-Min Transistors: OUTPUT 3 Ω for OCT2 etc. 14p (up to 5.54p). SOLDERING IRON, Slim, modern, British highspeed 8 1/2", all parts replaceable, highest quality, full guarantee: £1-07 1/2 (10p). DIAMOND STYLLI Replacements for BSR TC8/LP, TC8/S, TC8/LP/STEREO: COLLARO 'O' : RONETTE BF 401P; Garrard GC2/LP and GC8/LP: ACOS GP65/67, all at 40p (6p). ACOS GP73, GP91, GP91SC, GP104: BSR ST4 (ST3, ST5), ST6 (ST7); SONOTONE STA, STAH, STAHIC; PHILLIPS AC3806, 3060 (3059, 3069, 3301, 3302, 3304); Garrard GK825, GCM21, GC823 and many more 'Garrard' etc. types. All at 75p. (6p). All are of the very highest quality and many more 'Garrard' etc. types. All at 75p. (6p). All are of the very highest quality. DOUBLE DIAMOND: ST4 (ST3, ST5); ST10 (ST9, ST8); STA, STAH, STAHIC, GP91 (for GP92, GP93, GP94 cartridges); GP91-SC for all GP91-SC Cartridges. All at £1.50 each (6p). SAPPHIRE STYLLI. All those types shown above under 'Diamond Stylli at 40p' also £6.97 at 17 1/2p each (6p) and GP91 and GP91SC at 40p (6p). No others. PICK-UP CARTRIDGES. All standard fittings and styli. Mono GP67/2 80p. STEREO CERAMIC GP94 £1.95 SONOTONE STEREO STAH (DIA) £2.40. RECORDING TAPE. Still the finest quality British Mylar available: Standard 5" 600ft. 36p. 5 1/2" 900ft. 50p. 7" 1200ft 56p. LONG PLAY 5" 900ft. 50p. 5 1/2" 1200ft. 56p. 7" 1200ft. 80p. (71p on 5" and 5 1/2", 9p on 7"). Other sizes of Tapes, also Cassettes in list. MICROPHONES. Crystal Mic 91, hand/desk 81p. MIC45. Curved metal hand-grip £1.00. CM21 Grey hand desk 62p. Stick '60' £1.02. CM70 'Planet' machined metal tapered stick type with neck cord, adaptor to fit floor stands £1.47 (all 9p). LAPEL (or hand) with clip 82p (6p). All are fitted with leads. Dynamic MS10 50K Ω for desk, tapered with base and slide-out adaptor £1-97 1/2. MS11. Similar, but fixed on swivel swan-neck to switch-fitted base, £2-22 1/2 (Either 16p). Type 209 Cardioid ball, 50K/600 Ω, omnidirectional, built-in vol. control, on/off switch, special lead, handle (as good as money can buy) £2-30. UD180 Uni-Dir. Ball, mesh, 50K/600 Ω, Adap., cable jack plug £2-20. (20p). DM100, omn-dir., Ball, 50K Cable adaptor £2-87 1/2 (all at 27p). MICROPHONE INSERTS. Dia. 1.75" OR 0.9" either size 27p (6p). EARPIECES with lead and min. jack plug (2.5 or 3.5 mm., state which). Magnetic 9p Crystal (3.5 only) 24p (Up to 3 for 6p on any). HEADPHONES De-luxe STEREO 8-16 Ohms £2-47 1/2. Same, fitted vol. control each earpiece £4-20. Both have lead and stereo jack plug (17 1/2p). High Res. 2000 ohm. Adjustable 92p (77p). SPEAKERS 12" ROUND fitted tweeter, 3 or 16 Ω (state which) £1-87 1/2 (27p) or for Stereo £4-25 pair, carr. paid. 21", 3 OR 8 Ω (state which) 87p (6p). EME 13" x 8" 3, 5 or 16 Ω (state which) £2-12 1/2 (25p). with two tweeters and (6p). EME 12" x 8" 3, 5 or 16 Ω (state which) £2-12 1/2 (25p). with two tweeters and (6p) per set all types). SEND S.A.E. for full free list of mains eliminators, amplifiers, extension aerials (car and portable), electrolytics, vol. controls, move microphones, transistors, thyristors and SDRs and other devices, switches of many types, rotary, toggle min. and sub-min. slide types, multitest meters, panel meters, all types of British and continental plugs and sockets, croc. clips, terminals, valve holders also Goldring 6800 series cartridges etc. etc. Special Offer lines at very low prices.

### FELSTEAD ELECTRONICS (PW 49)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Cash with order only. No COD or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p excluding postage, unacceptable. S.A.E. please for enquiries or cannot be replied to. Charges apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).
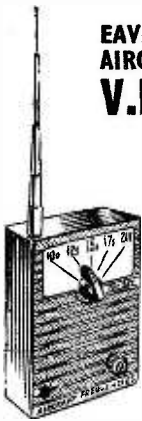
## EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT V.H.F. AIRCRAFT BAND CONVERTER



**ONLY £2-37**  
(47/6)

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross-talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve ripling decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN. SEND NOW, ONLY £2-37 (47/6) + 23p (4/6) p. & p. for all parts, including case nuts, screws, wire, etc., etc. (Parts available separately).

## FIND BURIED TREASURE! TREASURE LOCATOR TRANSISTORISED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—It signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits into—no connections needed. FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC. Outdoors or indoors. Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderful clear, easy to follow, step-by-step, fully illustrated instructions—it really is easy as A.B.C. transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 1/2" x 10" x 2 1/2". Great demand expected at this remarkably low price—ORDER WHILE PRESENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc. etc. ONLY £2-37 (47/6) + 27p (5/6) p. & p. (Sectional handle as illustrated 75p (15/-) extra). Parts available separately. Made up looks worth £15!



**ONLY £2-37**  
(47/6)

**ONLY £2-37**  
(47/6)


## BUILD 5 RADIO AND ELECTRONIC PROJECTS



**TOTAL BUILDING PRICE £1-97**  
(39/6)

Amazing Radio Construction set! Become a radio expert for £1-97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated Step-by-step plans, all Transistors, loud speaker, a personal

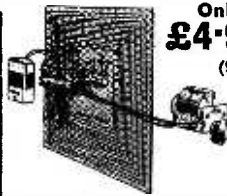phone, knobs, screws, etc., all you need. Presentation Box 37p (7/6) extra as illus. (if required) (extra parts available separately no soldering necessary. Send only £1-97 (39/6) + 23p (4/6) p. & p.



Only **£4-95** (99/-) FIND BURIED TREASURE WITH THIS READY BUILT & TESTED

## Treasure Locator Module

BRAND NEW FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EARLY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, wood, dirt, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! You could even pay for your holidays with two or three days electronic beachcombing—it's almost like having a licence to print money! Unclaimed treasure now exceeds the combined wealth of all nations. ORDER NOW WHILE PRESENT STOCKS LAST—TREMENDOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DESPATCHED IN STRICT ROTATION. SEND NOW £4-95 + 30p carr. (99/- + 8/-) etc. (High quality Danish Stethoscope headphones £2-75 (55/-) extra if required).

## SHORTWAVE TRANSISTOR RADIO

**£2-25**  
(45/-)

Can be built in one evening

At last! After trying countless circuits searching for easy build, work first-time short wave. Giving advanced world-wide performance, we chose this 'Sky Roma'. Anyone from 3 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and everyone worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorised (no valves). Size only 3" x 4 1/2" x 1 1/4". As tremendous demand anticipated price held to only £2-25 (45/-) + 17p (3/6) p. & p. for all parts incl. Cabinet, screws, instructions etc. (Parts available separately).



## SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

**CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES!** Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops!—a well known type of pink noise. A group of Dentists have experimented on patients with this pink noise—NO ANESTHETICS WERE USED! The noise ostensibly created a most definite reaction on these patients' nervous systems with the result that their pain systems were blocked. IF YOU WORK IN NOISE OR DISTRACTING SOUNDS, IF YOU FEEL TENSED, UNABLE TO RELAX—SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, use this amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. TAKE IT ANYWHERE, pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life) CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc. etc. no soldering. Send only £2-25 + 25p (45/- + 5/-) p. & p. Parts available separately.

only **£2-25**  
(45/-)



## GET A GOOD NIGHT'S SLEEP—EVERY NIGHT! INGENIOUS ELECTRONIC SLEEP INDUCER

only **£2-75**  
(55/-)

CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. If even sleep by itself to you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sounds gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or works needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4 1/2" x 1 1/4"—take it anywhere. All parts including case, loudspeaker, components, nuts, wire, screws, etc. etc. THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2-75 + 25p (55/- + 5/-) p. & p. (parts available separately).



## REAL WORKING ELECTRONIC ORGAN



**ONLY £2-75**  
(55/-)

Anyone from nine years upwards can build it easily in one short evening following the fully illustrated step-by-step, simply worded instructions. BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT AT our low, low building price. ONLY £2-75 (55/-) + 23p (4/6) p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc. etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, with an exciting gift for someone.

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised—no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13 1/2" x 10" x 2 1/2". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere, NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER. No soldering necessary, it really is as simple as a.b.c. to make.

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

**CONCORD ELECTRONICS LTD (Dept. PW24)** 8 Westbourne Grove, London W.2.  
(STAFF WANTED FOR ALL DEPARTMENTS) (Nr Bayswater & Queensway Tubes. 1 minute ABC Cinema) Callers Welcome 9 a.m.-6 p.m. inc. Saturday



**AMPEX 7.5v. D.C. MOTOR.** This is an ultra-precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60 ma on run, 600rpm +5% speed adjustment. Internal AF/RF suppression  $\frac{1}{2}$ " dia.  $\frac{1}{8}$ " spindle, motor 3" dia.  $\frac{1}{2}$ ". Original cost £16.50. Our price £4.25. P. & P. 25p. Mu-metal enclosure available 75p each.

**SYNCHRONOUS MOTORS.** 220/380 v. 50/60 Hz. 250-300 rpm. 75p each.  
**MYCALEX MAINS.** Shaded pole, 1425 rpm,  $\frac{1}{8}$ " spindle. 2 for £1.25. Carriage Paid.

**MAINS INDUCTION MOTOR.** Open frame,  $\frac{3}{8}$ " spindle, weight  $\frac{1}{2}$  lb. Powerful. 88p each. P. & P. 12p.

**GEARED MOTORS** Shaded pole 240v. 50 Hz. 200 rpm. 10lb. in. £2.50. P. & P. 25p.  
**MYCALEX.** Open frame, shaded pole motors, 240v. 50 Hz. 7 rpm. 28 lb. in. 80 rpm. 12 lb. in. £2.25 each. P. & P. 25p.

**"CROUZET" TYPE 965.** 115/240v. 50 Hz. 47/68 watts. 50 rpm. Stoutly constructed. Size:  $2\frac{1}{4}$ " dia.  $\times$   $3\frac{1}{2}$ " long plus spindle  $1\frac{1}{2}$ "  $\times$   $\frac{1}{4}$ " dia. Anti-clock. £2.75. P. & P. 25p.

**TYPE 955.** Same as above, but 3 rpm. £3.00. P. & P. 25p.

**"M A L L O R Y" LONG LIFE BATTERIES.** Type A. RM12 cell 1.35v. 3,600 ma/h. CAP. 250/300 ma cont. current. Size:  $2\frac{1}{2}$ "  $\times$   $2\frac{1}{2}$ "  $\times$  1" for £1.00 or £2.00 per doz. Carr. Paid. Type B. Comprises 8  $\times$  RM 625 cells. Nom. volts. 1.35 each 10.5v. Overall, 350ma/H CAP. 20/25 ma cont. current. Size:  $2\frac{1}{2}$ "  $\times$   $1\frac{1}{2}$ "  $\times$  3" for £1.00 or £3.00 per doz. Carr. Paid.

**A.C./D.C. M/IRON AMMETERS.** 0-5 amps or 0-8 amps (suitable battery chargers etc.). Perspex front. Size:  $1\frac{1}{2}$ "  $\times$   $1\frac{1}{2}$ ". Any 2 for £1.10. Carr. Paid.

**ERNEST TURNER 800 $\mu$ A METER.** 160 $\Omega$  movement, 2" case elipic, plastic front. Green-Red-Green uncalibrated scale £1.50 each. Carriage paid.

**PAINTON BOURNS TRIMPOTS.** 1k, 2k, 2.5k, 5k, 10k, 20k, 50k, 500k. Other Trimmer pots in stock. RIL 10k. MORGANITE 1k. MEC 200  $\Omega$  (tubular) 50 $\Omega$ . Any 3 for £1.10 carr. paid.

**PROGRAMME TIMER BY HONEYWELL.** A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Originally cost £15.00 plus. Many applications, such as lighting effects etc. New in original makers cartons. First class value at £5.75 plus 25p. P. & P.



**PRECISION FAN CO. (SMITHS INDUSTRIES) DOUBLE ENTRY CENTRIFUGAL FAN/BLOWER.** This is a beautifully balanced, particularly quiet running unit giving approx. 90 cubic ft./min. The motor is a 2 pole shaded pole Mycalox, drawing only 240ma on run. Weight 2 $\frac{1}{2}$  lbs. Sizes: case dia. 3.1 ins. width (case only) 3.125 ins. Width overall (inc. 5.25 ins. Aperture 3.125 ins  $\times$  1.85 ins. Offered well below makers price at £2.95. P. & P. 25p.

**Brand New "DISCUS" Centrifugal Blower** by Watkins & Watson. 240v. 50 Hz. Powered by A.E.I. continuous rating 2850 rpm motor. Cowl diameter 10". Outlet flange 2" I.D. Coupling flange supplied. These superb precision units are ideally suited for Organ construction. Offered at approx. half makers price £12.50. Carriage £1.50.

**PLUNGER SWITCHES.** Spring return 3 P.D.T. 1 amp. Single action. Size:  $1\frac{1}{2}$ "  $\times$   $1\frac{1}{2}$ " plus plunger. £1.50 per doz. Carr. Paid

**"HONEYWELL" TYPE 23AC-NE.**—15 amp. change-over micro switch is fitted on angled metal mount with spring-loaded plastic rod operating cam. 50p. each.

**VINKOR POT CORE ASS. TYPE LA. 2103** (core LA. 2100). Normal price £1.48. Our price 75p each. Special quote for quantity.

**UNISELECTORS.** 8 Bank 25-way, 24 volt Double sweep. Brand new in maker's boxes £5.25 P. & P. 25p.

**Special offer of AMPEX professional tape heads.** Mu-metal shrouded. (Designed for model AG20). Full track record, or playback, £3.00. Erase head £2.00. Set of 3 with mounting bracket and cover £7.50. Half track record only. £3.00 each. Carriage paid.



**"BENSON BROS." 12v. D.C. HEAVY DUTY SOLENOID.** Size: 3" overall  $\times$   $1\frac{1}{2}$ "  $\times$  1". Very powerful, with secondary low current hold coil. Cont. rated £1.00 each. P. & P. 15p.

**"DECCO" MAINS SOLENOID.** Compact and very powerful. 16 lb. pull.  $\frac{1}{2}$ " travel which can be increased to  $\frac{1}{2}$ " by removing captive-end-plate. Overall size 2"  $\times$  2 $\frac{1}{2}$ "  $\times$  2 $\frac{1}{2}$ " high. £4.50. P. & P. 25p.

**"MAGNETIC DEVICES" Mains Solenoid.**—2"  $\times$  1 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{2}$ " approx. 2lb. pull. Plunger Travel  $\frac{1}{2}$ ". New in makers boxes; offered at half original cost. 75p. P. & P. 25p.

**"FIBRE GLASS" COPPER CLAD.** Top grade. One size only. 7 $\frac{1}{2}$ "  $\times$  4 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{2}$ ". 3 panels £1.00. 12 panels £3.50. P. & P. 15p.

**"SRBP" COPPER CLAD.** Sizes: 7 $\frac{1}{2}$ "  $\times$  4 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{2}$ ", 16 for £1.00. 14 $\frac{1}{2}$ "  $\times$  5 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{2}$ ", 8 for £1.00. 19 $\frac{1}{2}$ "  $\times$  7 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{2}$ ", 4 for £1.00.

**SLIDER SWITCHES.** 3 amp. type P.D.P.T. 1"  $\times$   $1\frac{1}{2}$ "  $\times$   $1\frac{1}{2}$ " deep. 1 amp. type P.D.T. 1"  $\times$   $1\frac{1}{2}$ "  $\times$   $1\frac{1}{2}$ " deep. £1.25 per doz. Either type or mixed as required. Carr. Paid.

**L.T. TRANSFORMERS.** Prim. 0-110-240v. Sec. 4-5-0-45v. at 1 amp. Size: 1 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{2}$ ". 60p. P. & P. 15p  
 Prim. 0-20-240 v. Sec. 0-5-10-15-20 v. at 2 amps. £1.25. P. & P. 15p

Prim 200/240v Sec 0-1-55-58-60 at 3-5 amps plus 0-90 at 100 ma. wax impregnated with screw term blocks. Weight 10 lbs £3.60 plus 40p P. & P.

**CURRENT FLOW INDICATOR.** Ideal for all types of battery operated equipment (portable machines, tape recorders etc.). Four white segments appear when current flows. Coil is 600 $\Omega$  6/12v. Drawing only 8 ma on function. Neat in appearance. Size: dia. 1 $\frac{1}{2}$ "  $\times$  1 $\frac{1}{2}$ " deep. Fixing centres  $\frac{1}{4}$ ". £1.25 each. Carr. Paid.

**ELECTRO-TECH SALES**

**BUSINESS HOURS:** 9.30-6 (1 p.m. Sat.)

**264 PENTONVILLE ROAD, LONDON, N.1**  
 P.W.10 (ONE MIN. FROM KINGS X STATION) Tel. 01-837 74012

**YOUR CAREER in RADIO & ELECTRONICS ?**

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to


NAME ..... Block

ADDRESS ..... Caps.

10/71

**BRITISH NATIONAL RADIO SCHOOL**

**UNBEATABLE RUSSIAN VALUE**

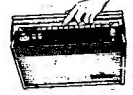

**TECHNICAL DATA :**  
 Waveband (frequency)  
 LW 2000—735.5m.  
 SW 571.4—185.9m  
 SW3 53.1—40.54m  
 SW2 31.91—24.79m  
 SW1 19.87—16.76m  
 VHF 3-43—288m  
 (5—104 mc/s)  
 17 transistors, 8 diodes

**PERFORMANCE CAN BE COMPARED WITH 865 RADIOS!**  
 Sockets for tape recorder, record player, extension speaker, earphone, external power supply (12V DC), external line and dipole aerials. Battery life approx. 800 hours.  
 At last, the Astrad Solar Radio combining quality with value and a specification not before available from Russia. Designed for the man who appreciates the extras necessary for quality performance. This 6 waveband Radio has twin speakers for quality. Fully independent Treble and Bass tone controls for ultimate performance and twin separate tuning controls for AM & FM broadcasts. 12 push buttons for waveband selection including automatic frequency control on V.H.F. This is the big set from Russia, overall dimensions—14"  $\times$  9 $\frac{1}{2}$ "  $\times$  4 $\frac{1}{2}$ ". Included in this incredible specification is an inbuilt tuning meter to ensure that you are spot-on the station you select. Telescopic aerial on universal joint and a push-button dial light. All presented in a luxurious padded case with carrying handle. This fabulous Radio is fully warranted for 1 year. Only limited supplies available at a never to be repeated price.

**NEW BUDGET PRICES**  
**£22-97**

Earphones 25p. P. & P. 75p  
 SEBA ELECTRONICS, Dept. M/O, 104 Unbridge Road, Hanwell, London, W7. Phone: 01-579 5644

**A CASE FOR "IMPEX"**

**PROBLEM :** I have a tuner, timer, mixer and digital clock for which I require suitable cases.  
**ANSWER :** "IMPEX" Instrument Cases.

**PROBLEM :** All the instruments are different sizes.  
**ANSWER :** "IMPEX" have a standard range of 36 sizes.

**PROBLEM :** I want them to be robust and stylish.  
**ANSWER :** "IMPEX" cases are both functional and attractive.

**PROBLEM :** My budget is strictly limited.  
**FINAL ANSWER :** "IMPEX" cases are very competitively priced.

Find out how they answer many problems. Details from:

**"IMPEX"**

P.O. Box 2BB, Newcastle-upon-Tyne, NE99 2BB.  
 (Makers of the M.S.7 Magnetic Pickup Pre-amplifier)





# 28watts, r.m.s. 40Hz to 40kHz ±3dB



## Viscount III Audio Suite complete £49

There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket for headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

### PRICES SYSTEM 1

Viscount III R101 amplifier	£22.00+90p p&p
2 x Duo Type II speakers,	£14.00+£2 p&p
Garrard SP25 Mk. III with MAG. cart ridge plinth and cover	£23.00+£1.50 p&p
<b>Total</b>	<b>£59.00</b>

Available complete for only £52.00+£3.50 p&p

### SYSTEM 2

Viscount R101 amplifier	£22.00+90p p&p
2 x Duo Type III speakers	£32.00+£3 p&p
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover	£23.00+£1.50 p&p
<b>Total</b>	<b>£77.00</b>

Available complete for £69+£4 p&p

### SYSTEM 3

Viscount III Amplifier R100	£17.00+90p p&p
2 x Duo Type II speakers, pair	£14.00+£2 p&p
Garrard SP25 Mk. III with CER. diamond cartridge, plinth and cover	£21.00+£1.50 p&p
<b>Total</b>	<b>£52.00</b>

Available complete for only £49.00+£3.50 p&p

### SPEAKERS Duo Type II

Size 17" x 10½" x 6½". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 3 ohms. Simulated Teak cabinet. £14 pair+£2 p&p.

Duo Type III Size 23½" x 11½" x 9½". Drive unit 13½" x 8½" with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair+£3 p&p.

### SPECIFICATION R100/101


14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within ± 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities; headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max) R101—P.U.1 and radio—65dB. P.U.2. -58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size 13½" x 9" x 3½".

# R+TV

Radio and TV Components (Acton) Ltd, 21c High Street, Acton, London W3 6NG  
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.  
Goods not despatched outside U.K.

# SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

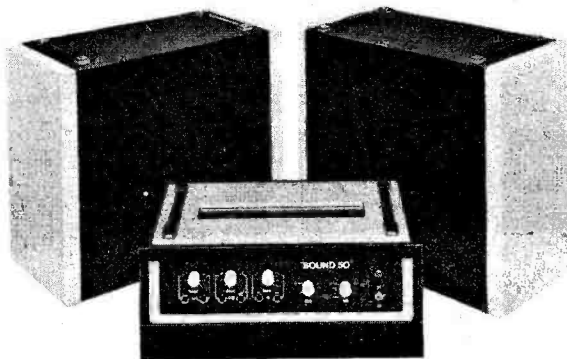

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power: 45 watts R.M.S. (Sine wave drive). Frequency response: —3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB.

Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range: ±13dB at 60Hz. Treble Control Range: ±12dB at 10 KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

**SPEAKERS!** Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM £50** Plus £6 P. & P.  
Sound 50 amp and 2 speakers

or available separately. Amplifier £28.50 plus £1.50 P. & P.  
Speakers £12.50 each plus £2.25 P. & P.

## THE ELEGANT SEVEN Mk. III

(350m W Output)




7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 75p extra.

Price £5.25 plus 50p. P. & P.

Circuit 13p FREE WITH PARTS.

## THE DORSET (600m W Output)

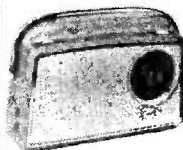


7-transistor fully tunable M.W.—L.W. superhet portable. Set of parts. The latest modified and pre-alignment techniques make this simple to build. Sizes: 12 x 8 x 3in.

Price £5.25 plus 50p P. & P.

Circuit 13p FREE WITH PARTS
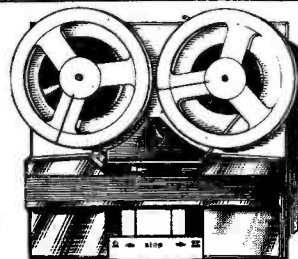
## CONTINENTAL 4 TRACK, 3 SPEED TAPE DECK



with high impedance heads

R.C. 74 tape deck. Three speeds—7½, 3½ and 1½ ips.

4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7". The R.C. 74 is driven by a powerful 200/250V 50-cycle A.C. motor. A heavy, accurately balanced, flywheel brings wow and flutter levels down to approx. 0.3% total at 3½ and 7½ ips. Fast rewind in both directions.

Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12½ x 11½ x 6 inches. Every single deck fully tested before dispatch. Spools not supplied.

Price complete £15-00. Plus 75p P. & P.

## RELIANT mk. IV



The Reliant Mk. IV provides a high standard of sound reproduction, with full mixing facilities. It's versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- \* Five Electronically Mixed Inputs
- \* Three Individual Mixing Controls
- \* Separate bass and treble controls common to all five inputs
- \* Mixer employing P.E.T. (Field Effect Transistor)
- \* Solid State Circuitry
- \* Attractive Styling

**£9.50** PRICE plus P. & P. 60p.

### SPECIFICATIONS

**INPUTS:**—1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.) All 250mV sensitivity.

**CONTROLS:**—3 Volume controls. Bass control range ±13db @ 60 Hz. Treble control range ±12db @ 15KHz. Separate ON/OFF Switch, Neon Indicator.

**POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohms speaker.

**SIGNAL/NOISE:**—Better than —60db on inputs 3, 4 and 5 & —50db on 1 & 2.

**SUPPLY:**—220 — 250 AC. Mains.

**SIZE:**—12½" x 6" x 3½".

## TOURIST MARK 3 CAR RADIO



### ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

### SET OF PARTS

**£6.30**

plus P. & P. 50p.

See previous page for address

Circuit diagram 13p. Free with parts  
Speaker, baffle and fixing kit £1-25  
extra plus 25p. p. & p. Postage free  
when ordered with parts.

RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED

**ONLY FROM US! LATEST SHIPMENT JUST ARRIVED!**

**BRAND NEW 1971 Model!**

**RUSSIAN WORLD BEATER!**

**6 WAVEBAND 10 TRANSISTOR PORTABLE RADIO**

**WORLD WIDE RECEPTION**

**£9.97**

THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

BOX POST ETC. 43p

**NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!**

**WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!**

THE LATEST 1971 MODEL, SUPERSEDING ALL PREVIOUS MODELS—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO. DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! Finest value we've ever offered! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios! ★ Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection. Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE! Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover world! Unique six control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over world—nothing is secret! The radio enthusiast has the world in his hand! Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble Bass tone controls! Take it anywhere—tune economically on standard batteries. Internal ferrite aerial plus built-in telescopic aerial extending to full 33 1/2 in. length. It's also a fabulous CAR RADIO—any speed, requires no additional aerial. UNIQUE! Elegant Black, White and Chrome finish case. SIZE 10 1/2" x 8" x 3 1/2" overall approx. Magnificently designed, made to give years of perfect service. With WRITTEN GUARANTEE, manual with simple operating instructions and circuit diagram. ONLY £9.97, POST ETC. 43p. Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

**SAVE £13.98 NOW!**

FIRST CLASS MAKERS

**BRAND NEW Cassette TAPE RECORDER and PLAYER**

**fabulous 1971 Model!**

**DE LUXE MODEL!**

RECOMMENDED LIST PRICE £26.96

**OUR PRICE £12.99**

POST ETC 30p

WITH REMOTE CONTROL MICROPHONE

MAKE NO MISTAKE—this is the EXPENSIVE model with "PIANO KEYBOARD" CONTROL PANEL and "MAGIC FEED" AUTOMATIC REWINDING LEVEL.

SAVE £13.98! Due to price we cannot mention famous maker's name—but rest assured you're getting one of the BEST! 1971 cassette model—no fiddling with awkward tape and reels. Just "slap-in a cassette and off you go! (takes 30, 60 or 90 minute standard Philips cassette tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Separate volume control! Rapid rewind! Beautiful tone from a whisper to a roar! Completely self-contained—record anywhere. Separate jacks for remote control microphone, etc. Size 9" x 4 1/2" x 2 1/2" overall approx. With carry strap. WRITTEN GUARANTEE and instructions. Only £12.99, post 30p. Refund 6% fee. BONUS one per customer: Cassette tape, set of standard batteries AND microphone stand all for 51p extra if required.

**\*WHY PAY £40 OR MORE?**

ADVANCED 1972 MODEL! COMPLETE HIGH FIDELITY COMMUNICATIONS & RADIO RECEIVER

V.H.F. WITH SPECIAL AIRCRAFT WAVEBAND

AND AC/DC MAINS and BATTERY

BUILT-IN MAINS BATTERY BOOSTER!

MIRACLE PRICE — REDUCED TO

**£9.99**

POST ETC 38p

Yes—advance 1972 model—NOW! Our introductory price is miraculous! Control to AIRCRAFT, SHIPS, POP PIRATES, TAXIS, AMBULANCES, LOCAL STATIONS, CONTINENTAL STATIONS, ALL B.B.C., V.H.F. AND MANY MORE, including public service transmissions we are not allowed to mention! Far more than an ordinary radio! Frequency range: MW 540-1600KHz. FM 88-108MHz. Air 108-145MHz. Intermediate Frequency: AM 455KHz, FM 10-7MHz. Air 10-7MHz. 18 SEMI CONDUCTORS!—Transistors 11, Diodes 6+Thermister! Automatic frequency control 'locks-in' eliminating drift. Pinpoint station selection! Built-in 8-section 36" Telescopic aerial. Leather-grained finish case with carry handle. 10 1/2" x 6 1/2" x 4" overall approx. Written guarantee. Only £9.99, post etc., 38p. Runs off mains—AC 230-250 volts, or off standard batteries. But that's not all! It's got a built-in Battery Booster too! Just plug in to mains whenever you wish! ★ Compare it with sets costing £40 or more. Refund 6% fee. BONUS TO EVERY PURCHASER! Shoulder Strap, earphone for personal listening and dry batteries, all for 31p extra, if required.

Send to Uxbridge Road or call at either store. (COMMERCIAL TRAVELLERS' NOTE: Merchandising Office at Holborn)

**SHOPERTUNITIES LTD. SL** Dept. WF10, 184 UXBRIDGE RD (Facing Shepherd's Bush Green London, W12 8AQ. (Thurs. 1, Fri. 7). Also 37, High Holborn, London. WC1 (Thursday 7 p.m.) Both Stores open from Monday to Saturday from 9 a.m. to 6 p.m.



## Train for tomorrow's world in Radio and Television at The Pembridge College of Electronics

### Your first day on Television: 5th January, 1972

This is your opportunity to train as a television and radio engineer on our full-time 2 year College Diploma Course. That is the way to get into a rapidly growing industry with a tremendous demand for skilled technicians. You will be given theoretical and practical instruction on colour television receivers, following a syllabus specially designed to cover the new City and Guilds Radio, Television and Electronic Technicians' Course.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

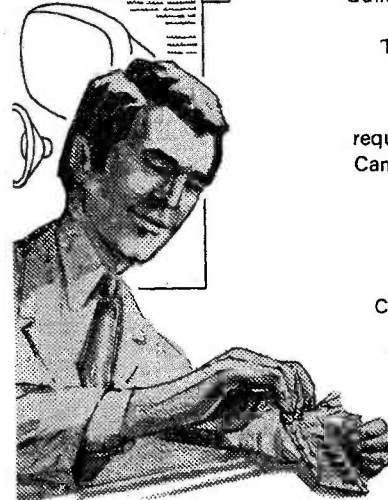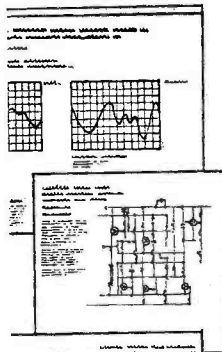Complete the coupon below and we will send you the details about training for an exciting, new career.



To: The Pembridge College of Electronics, (Dept. PW6), 34a Hereford Road, London, W2 5AJ.

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME .....

ADDRESS .....

# AUDIO SUPPLIES

## SLASH PRICES! UP TO 60%

### SUPERB Plinths & Covers



ONLY

**£3.25** P. & P. 30p

for GARRARD and B.S.R. SP25, SL65B, 3500, 3000 2025TC, 2000, 1025, 5100, AT6, AT60, 40B, B.S.R. McDonald range. All decks are finished in teak polish and will blend in any modern home. The covers are of tinted Perspex (please state deck when ordering).

**SUPERIOR PLINTHS AND COVERS FOR GARRARD AP75, AP76, SL72B, SL75B and SL95B.**  
£4.99. P.P. 60p (R.R.P. £9.50)

#### STEREO AMPLIFIERS p.p. 50p

ARMSTRONG 521 .....	£40.00
AMSTRAD 8000 .....	£15.00
H.L. SA707 .....	£18.00
TELETON SAQ206 .....	£42.00
VICEROY VAS70 .....	£42.00
VICEROY 55 .....	£16.00
SANSUI full range in stock P.O.A.	
METRO SOUND ST20 .....	£24.00
SINCLAIR 2000 MkII .....	£22.00
SINCLAIR 3000 .....	£32.00
SINCLAIR NEOTERIC .....	£46.00
SINCLAIR A.F.U. .....	£4.50
SINCLAIR S60 + 2 Z30/PZ5 .....	£15.00
SINCLAIR S60 + 2 Z30/PZ6 .....	£17.50
SINCLAIR S60 + 2 Z50 + PZ8 and Mains trans. .....	£23.00

Sonab special offer for personal callers only

#### TUNER AMPLIFIERS p.p. 50p

ARMSTRONG 526 .....	£80.00
ARMSTRONG 525 .....	£70.00
RODGERS RAVENSBROOK .....	P.O.A.
TELETON CR107 with speakers .....	£25.50
TELETON F2100 .....	£30.00
PHILIPS RH781 .....	£163.00
WHARFEDALE 100-1 .....	£53.00
GOODMANS MODULE 80 .....	£72.00
TELETON R8000 with speakers .....	£35.00
TOSHIBA range P.O.A.	

Sonab special offer for personal callers only

#### TUNERS p.p. 50p

ARMSTRONG M8 .....	£7.75
ARMSTRONG 523 .....	£40.00
ARMSTRONG 524 .....	£31.00
TELETON GT101 .....	£32.00
SINCLAIR Pro. 60 .....	£19.50
RODGERS RAVENSBORNE FET2 Chassis .....	£45.00
LEEK STEREO STETIC Chassis .....	£48.00

Easy to find—50 yards from (B.R.)  
Stoke Newington Stn.  
67, 149, 247, 73, 76, 243 Buses Pass our  
door.

STEREO LPs  
of the great  
musicians

3 for £1.15 free p. & p.

Send S.A.E. for lists

**WHY  
PAY MORE ?**

**Post Budget  
Purchase Tax  
Reductions.**

Send S.A.E. for quote on  
equipment you require.

Most good  
manufacturers products  
available.

**GOODMANS MAGISTERS**  
£80.00 per pair, p. & p. £2.50

#### PICK-UP ARMS p.p. 45p

SME 3009/S2 .....	£25.00
SME 3012/S2 .....	£26.50
GOLDRING L75 .....	£10.00
GOLDRING L69 .....	£8.00
AUDIO TECHNICA AT1005 .....	£16.25

**VISIT OUR 3-STORY WARE-  
HOUSE PACKED WITH HI-FI &  
STEREO EQUIPMENT. 1000's OF  
ITEMS ALWAYS AVAILABLE  
TO SELECT FROM.**

**FOR ALL YOUR NEEDS IN HI-FI  
EQUIPMENT SEND A LARGE S.A.E.  
or PAY A VISIT**

**2 SHOWROOMS DEVOTED TO  
DEMONSTRATING SPECIALLY  
SELECTED SYSTEMS**

### SPECIAL OFFERS

GARRARD SP25 Mk. III  
GOLDRING G800 Superb Plinth  
and Cover.

SINCLAIR Project 60—Stereo 60  
Pre-Amplifier and Control Unit,  
2 Z30's and PZ5. 2 WHARFEDALE  
Unit 3. List Price £84.00. OUR PRICE  
£55. P. & P. £1.75.

GARRARD SP25 Mk III  
GOLDRING G800 H

Plinth and Cover complete  
OUR PRICE £18.00. P. & P. 75p.

ARMSTRONG 526  
GARRARD AP76  
SHURE M55E

Plinth & Cover complete  
STE-MA 400 speakers  
OUR PRICE £148.00. P. & P. £1.25

#### CARTRIDGES p.p. 3p

GOLDRING G850 .....	£3.50
GOLDRING G800H .....	£5.00
GOLDRING G800 .....	£7.00
GOLDRING G800/E .....	£10.75
GOLDRING G800/SE .....	£16.00
SHURE M50 .....	£4.75
SHURE M44/S77C .....	£7.00
SHURE M55E .....	£9.00
SHURE M75E type 2 .....	£15.00
SHURE V15 type 2 .....	£30.00
SHURE 44E .....	£8.50
SHURE 31E .....	£8.00
SHURE 32E .....	£8.25
SONATONE 9TAHCD .....	£1.50
AUDIO TECHNICA AT66 .....	£4.00
ADC 10/E MkII .....	£25.00

#### GARRARD 0/100 IN STOCK SPECIAL PRICE ON APPLICATION

#### TURNTABLES p.p. 60p

GARRARD SP25/Mk. III .....	£10.00
GARRARD 2025TC with Sonotone 9TAHCD Diamond Cartridge .....	£8.00
GARRARD A70 Mk. II .....	£19.97
GARRARD SL65B .....	£12.75
GARRARD A76 .....	£18.00
GARRARD SL72B .....	£25
GARRARD SL75B .....	£27.00
GARRARD 401 .....	£27.40
GARRARD SL95B .....	£34
GOLDRING GL75P .....	£35
GOLDRING GL75 .....	£28.50
GOLDRING GL69 .....	£21
THORENS TD125 .....	£42
THORENS TD150AB/2 .....	£38
PIONEER PL11AC complete .....	£39
Dual 1219 .....	£49
DUAL 1209 .....	£34
PHILIPS 202A .....	£54

#### OPEN

Monday - Wednesday 9.30 a.m.-6 p.m.  
Half day Thursday until 1 p.m.  
Late night Friday until 8 p.m.  
SATURDAY 9.30 a.m.-6 p.m.

SEND CHEQUES, P.O., MONEY ORDER, etc. to—

# AUDIO SUPPLIES

PW10, 50 STAMFORD HILL, LONDON, N.16.  
Telephone: 01-806 3611/7311

PERSONAL CALLERS PLEASE NOTE—Cheques are only accepted when accompanied by a Bank Cheque Card (not Barclay Card).

All prices subject to change without notice



# -the lowest prices!

## 74 series T.T.L. I.C's

### DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C's. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed.



BI-PAK Order No.	Similar Types to:—Description	Price and qty. prices		
		1-24 \$p	25-99 \$p	100 up \$p
BP00 = 7400	Quad 2-input NAND gate	0-15	0-14	0-12
BP01 = 7401	Quad 2-input pos. NAND gate (with open collector output)	0-15	0-14	0-12
BP02 = 7402	Quad 2-input pos. NOR gates	0-15	0-14	0-12
BP03 = 7403	Quad 2-input pos. NAND gates (with open collector output)	0-15	0-14	0-12
BP04 = 7404	Hex Inverters	0-15	0-14	0-12
BP05 = 7405	Hex Inverter (with open collector output)	0-15	0-14	0-12
BP10 = 7410	Triple 3-input pos. NAND gates	0-15	0-14	0-12
BP13 = 7413	Dual 4-input Schmitt trigger	0-29	0-28	0-24
BP20 = 7420	Dual 4-input pos. NAND gates	0-15	0-14	0-12
BP30 = 7430	8-input pos. NAND gates	0-15	0-14	0-12
BP40 = 7440	Dual 4-input pos. NAND buffers	0-15	0-14	0-12
BP41 = 7441	BCD to decimal mixer driver	0-87	0-84	0-58
BP42 = 7442	BCD to decimal decoder (4-10 lines)	0-87	0-84	0-58
BP46 = 7446	BCD-to-seven-segment decoder/driver	2-00	1-75	1-50
BP47 = 7447	BCD-to-seven-segment decoder/drivers (15V outputs)	0-97	0-94	0-88
BP48 = 7448	BCD-to-seven-segment decoder/driver	0-97	0-94	0-88
BP50 = 7450	Expandable dual 2-input and-or-invert	0-15	0-14	0-12
BP51 = 7451	Dual 2-wide 2-input and-or-invert gates	0-15	0-14	0-12
BP53 = 7453	Quad 2-input expandable and-or-invert	0-15	0-14	0-12
BP54 = 7454	4-wide 2-input and-or-invert gates	0-15	0-14	0-12
BP60 = 7460	Dual 4-input NAND	0-15	0-14	0-12
BP70 = 7470	Single-phase J-K flip-flop	0-29	0-28	0-24
BP72 = 7472	Master slave J-K flip-flop	0-29	0-28	0-24
BP73 = 7473	Dual Master slave J-K flip-flop	0-37	0-35	0-32
BP74 = 7474	Dual D type flip-flop	0-37	0-35	0-32
BP76 = 7476	Quad latch	0-47	0-45	0-42
BP78 = 7478	Dual J-K with pre-set and clear	0-43	0-40	0-38
BP80 = 7480	Expand full adders	0-67	0-64	0-58
BP81 = 7481	16-bit read/write memory	0-97	0-94	0-88
BP82 = 7482	2-bit binary full adders	0-97	0-94	0-88
BP83 = 7483	Quad full adder	1-10	1-05	0-95
BP86 = 7486	Quad 2-input exclusive NOR gates	0-32	0-30	0-28
BP90 = 7490	BCD decade counter	0-67	0-64	0-58
BP91 = 7491	8-bit shift registers	0-87	0-84	0-78
BP92 = 7492	Divide-by-twelve counters	0-67	0-64	0-58
BP93 = 7493	4-bit binary counters	0-67	0-64	0-58
BP94 = 7494	Dual entry 4-bit shift register	0-77	0-74	0-68
BP95 = 7495	4-bit up-down shift register	0-77	0-74	0-68
BP96 = 7496	5-bit parallel in parallel out shift register	0-77	0-74	0-68
BP100 = 74100	8-bit bistable latches	0-77	0-74	0-68
BP104 = 74104	Single J-K flip-flop equivalent 9000 series	1-75	1-65	1-55
BP105 = 74105	Single J-K flip flop equivalent 9001 series	0-97	0-94	0-88
BP107 = 74107	Dual Master slave flip-flops	0-40	0-38	0-36
BP110 = 74110	Gates master-slave flip-flops	0-55	0-53	0-50
BP111 = 74111	Dual data lock-out flip-flop	1-25	1-15	1-00
BP118 = 74118	Hex set-reset latches	1-00	0-95	0-90
BP119 = 74119	Hex set-reset latches, 24-pin	1-35	1-25	1-10
BP121 = 74121	Monostable multivibrators	0-67	0-64	0-58
BP141 = 74141	BCD-to-decimal decoder/driver	0-67	0-64	0-58
BP145 = 74145	BCD-to-decimal decoder/driver O/C	1-50	1-40	1-30
BP150 = 74150	16-bit data selector	1-80	1-70	1-60
BP151 = 74151	8-bit data selectors (with strobe)	1-00	0-95	0-90
BP153 = 74153	Dual 4-line-to-1-line data	1-20	1-10	0-95
BP154 = 74154	4- to 16-line decoder	1-80	1-70	1-60
BP155 = 74155	Dual 2- to 4-line decoder	1-40	1-30	1-20
BP156 = 74156	Dual 2- to 4-line decoder O/C	1-40	1-30	1-20
BP160 = 74160	Sync. decade counter	1-80	1-70	1-60
BP161 = 74161	Sync. 4-bit binary counter	1-80	1-70	1-60
BP190 = 74190	Sync. up-down BCD counter	3-50	3-25	3-00
BP191 = 74191	Sync. binary up-down counter (single clock line)	3-50	3-25	3-00
BP192 = 74192	Sync. up-down decade counter	2-10	1-95	1-75
BP193 = 74193	Sync. binary up-down counter (two clock lines)	2-10	1-95	1-75
BP196 = 74196	Pre-settable 50MHz decade counter	1-80	1-70	1-60
BP197 = 74197	Pre-settable 50MHz binary counter	1-80	1-70	1-60
BP198 = 74198	8-bit parallel L-R shift register	5-50	5-00	4-00
BP199 = 74199	8-bit parallel access shift register	5-50	5-00	4-00

D devices may be mixed to qualify for quantity price. Larger quantities—prices on application (DTL 74 Series only).

Data is available for the above series of I.C's in booklet form. Price 13p.


### TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C's and experimental work.

PAK No.	PAK No.	PAK No.
UIC00 = 12 x 7400N	UIC42 = 5 x 7450N	UIC80 = 5 x 7480N
UIC01 = 12 x 7401N	UIC50 = 12 x 7450N	UIC82 = 5 x 7482N
UIC02 = 12 x 7402N	UIC51 = 12 x 7451N	UIC83 = 5 x 7483N
UIC03 = 12 x 7403N	UIC60 = 12 x 7460N	UIC86 = 5 x 7486N
UIC04 = 12 x 7404N	UIC70 = 8 x 7470N	UIC90 = 5 x 7490N
UIC05 = 12 x 7405N	UIC72 = 8 x 7472N	UIC92 = 5 x 7492N
UIC10 = 12 x 7410N	UIC73 = 8 x 7473N	UIC93 = 5 x 7493N
UIC20 = 12 x 7420N	UIC74 = 8 x 7474N	UIC94 = 5 x 7494N
UIC40 = 12 x 7440N	UIC75 = 8 x 7475N	UIC95 = 5 x 7495N
UIC41 = 5 x 7441AN	UIC76 = 8 x 7476N	UIC96 = 5 x 7496N

PAK cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries out BI-PAK Satisfaction or money back GUARANTEE.

## ANOTHER BI-PAK FIRST!

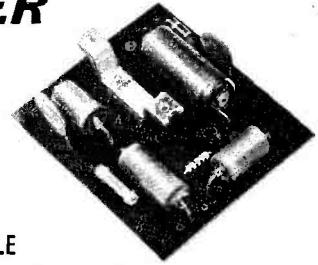

THE NEW S.G.S. EA 1000 AUDIO AMPLIFIER MODULE

### \*GUARANTEED NOT LESS THAN 3 WATTS RMS

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA/621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. OTHER USES: portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt VOLTAGE GAIN 40dB but can be varied up to 73dB for some applications.
- Signal to Noise Ratio 86dB.
- Frequency response better than 50 Hz to 25 KHz for -3dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 OHM Loads.
- Overall Size 2" x 3" x 1/2".
- Typical Total Harmonic distortion at 1 watt less than 1%.

\*Supply voltage (Vs) = 24V 15ohm load.

Module Tested and Guaranteed

Quantity 1-9 10-25  
Price each £2.63 £2.28  
Larger quantities quoted on request

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

### ROCK BOTTOM PRICES—CAN'T BE BEATEN!

LOGIC Type No.	Function	DTL 930 SERIES	IC's
BP930	Expandable dual 4-input NAND	1-24	25-99 100 up
BP932	Expandable dual 4-input NAND buffer	12p	11p 10p
BP933	Dual 4-input expander	13p	12p 11p
BP935	Expandable Hex Inverter	13p	12p 11p
BP936	Hex Inverter	13p	12p 11p
BP944	Dual 4-input NAND expandable buffer without pull-up	13p	12p 11p
BP945	Master-slave JK or RS	25p	24p 22p
BP946	Quad, 2-input NAND	12p	11p 10p
BP948	Master-slave JK or RS	25p	24p 22p
BP951	Monostable	65p	60p 55p
BP962	Triple 3-input NAND	12p	11p 10p
BP9098	Dual Master-slave JK with separate clock	40p	38p 35p
BP9094	Dual Master-slave JK with separate clock	40p	38p 35p
BP9097	Dual Master-slave JK with Common Clock	40p	38p 35p
BP9099	Dual Master-slave JK Common Clock	40p	38p 35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

### BRAND NEW LINEAR I.C's—FULL SPEC.

Type No.	Case	Leads	Description	Price
BP 201C—SL201C	TO-5	8	G.P. Amp	1-24 25-99 100 up
BP 701C—SL701C	TO-5	8	G.P. Amp	63p 53p 45p
BP 702C—SL702C	TO-5	8	OP Amp Direct OP	63p 50p 45p
BP 702—72702	D.I.L.	14	G.P. OP Amp (Wide Band)	53p 45p 40p
BP 709—72709	D.I.L.	14	High OP Amp	53p 45p 40p
BP 709F—7A709C	TO-5	8	High Gain OP Amp	58p 45p 40p
BP 711—7A711	TO-5	10	Dual comparator	58p 50p 45p
BP 741—72741	D.I.L.	14	High Gain OP Amp (Protected)	75p 60p 50p
7A 703C—7A703C	TO-5	6	R.L.F. Amp	45p 35p 27p
TAA 262—	TO-72	4	A.E. Amp	70p 60p 55p
TAA 293—	TO-74	10	G.P. Amp	90p 75p 70p

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

## P.O. BOX 6, WARE · HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

# 3 WAYS

HOME RADIO (Components) LTD.  
Dept. PW, 234-240 London Rd.,  
Mitcham, CR4 3HD. 01-648 8422

## of obtaining components *quickly & easily*

# 1

**CALL AT No. 240  
London Rd., Mitcham**

If you live within easy reach of Mitcham or are in the area at any time do call on us. We are almost opposite Mitcham Baths. We open 9 a.m. every weekday. On Wednesdays we close 1 p.m. and all other days, including Saturdays, 5.30 p.m. On Saturdays we have extra staff to deal with queries. We carry a vast stock of components, and 999 times out of a 1,000 we can immediately lay our hands on the particular item required.

# 2

**JOIN OUR CREDIT  
ACCOUNT SERVICE**

We began our Credit Account Service about 18 months ago and it has proved extremely popular. Little wonder! Our customers find it a very simple and convenient way of purchasing all their radio and electronic needs. We supply pre-paid envelopes and order forms and no matter how many orders you send us you make only one payment per month. There are several other advantages with our Credit Account Service. Please write or phone for details.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

# 3

**and  
ORDER BY MAIL  
OR TELEPHONE**

Although we are kept busy selling "over the counter" we supply even more by Mail Order. You can telephone any time of day or night, Sundays included. If you ring out of office hours a recording machine takes your message for us to deal with as soon as we open shop again. Our number is 01-648 8422. If you wish to order by post our address is in the panel at the top of the page. We deal with all orders promptly.



**WHICHEVER WAY YOU  
CHOOSE** you need the  
Home Radio Catalogue

In its 315 pages are listed over 8,000 components, over 1,500 of them illustrated. Each copy contains 10 Vouchers, each worth 5p when used as instructed. Free Supplements are supplied regularly to keep you up-to-date. The Catalogue costs 50p over the counter, or 70p including postage and packing.

*Post this Coupon with  
Cheque or PO for 70p*

*Please write Name and Address in block capitals.*

Name .....

Address .....

.....

**HOME RADIO (Components) LTD.**  
Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD



# PRACTICAL WIRELESS

VOL 47 NO 6

Issue 776

OCTOBER 1971

## Who makes what?

**W**ELL, of course, that's easy! When you buy a radio set, hi-fi amplifier or piece of electrical equipment, the trade mark tells you that. Or if the mark is an unfamiliar one you can find the piece moulded on the cabinet or printed on the carton which says 'Made in Outer Mongolia' or whatever.

People are interested in where products are made for a variety of reasons. The possible standard of workmanship, value-for-money, reputation, reliability, the position of after-sales service, availability of spare parts—or even personal political motives—are all valid reasons why a purchaser would want to know who makes what, and where.

From November 30th, however, the Merchandise Marks Act comes to an end and from that date it will no longer be obligatory for imported goods to bear a 'country-of-origin' mark. The casual customer will therefore not be sure if he is buying a radio set made in Birmingham or Baluchistan, or an amplifier which is a Chinese-copy of an American design made in Hong Kong or Japan.

Of course, there will still be trade marks which proclaim that the goods are true-blue British or come from well-respected foreign companies. Sadly, though, things are not always what they seem for many tape recorders, radio and TV receivers, bearing the names of old-established British manufacturers have for some time been made overseas and imported for the home market.

From November 30th, protection of the consumer has been thrown at the retailer who, when asked, will be expected to disclose where a particular product is made. Unfortunately in many cases he will have no way of giving the required information. For instance, 'household-name' UK companies are none too keen to admit that some of their goods are being made in low-cost labour countries. Moreover, if a retailer does not know the country of origin, or (even inadvertently) gives the wrong answer, he will be at risk under the Trade Descriptions Act!

Apart from the factors mentioned earlier, which allow a customer to assess the advisability or otherwise of making a purchase, a particularly disturbing aspect of electrical goods (notably electric blankets and appliances) is that safety specifications may fall far short of those imposed on British-made goods and expose the user to potential hazards.

So, together with the British Radio Equipment Manufacturers' Association, the Radio and Television Retailers' Association and the Association of Manufacturers of Domestic Appliances, we beg the Secretary for Trade and Industry to think again. And to would-be purchasers after November 30th we can only say, most emphatically *caveat emptor!*

W. N. STEVENS—*Editor.*

## NEWS AND COMMENT

Leader	471
News . . . News . . . News . . .	472
MW Column by <i>Charles Molloy</i>	478
Practically Wireless by <i>Henry</i>	518
On the Short Waves	
by <i>Malcolm Connah</i> and	
<i>David Gibson, G3JDG</i>	521
Electronotes by <i>S. Ginsberg</i>	534

## CONSTRUCTIONAL

Modular Audio Mixing System	
by <i>F. C. Judd</i>	474
Digital Frequency Counter/Timer,	
Part 2 by <i>John Thornton Lawrence,</i>	
<i>GW3JGA</i>	480
General Purpose Power Supply	
by <i>M. Wallis</i>	492
Wavemeter Monitor by <i>R. F. Graham</i>	529
Take 20, No. 30, Automatic Light,	
by <i>Julian Anderson</i>	533

## OTHER FEATURES

Testing Surplus Transistors	
by <i>R. A. Butterworth</i>	489
Transistor Circuitry for Beginners,	
Part 1, by <i>H. W. Hellyer</i>	507
I.C. of the Month,	
LM373 Multiple-mode Detector	
by <i>L. A. J. Ireland</i>	510
SERVICING—Part 6, by <i>G. J. King</i>	513
Going Back by <i>Colin Riches</i> and	
<i>Arthur Dow</i>	525

## SPECIAL FEATURES

Choosing Small Workshop Tools	
by <i>S. Yeatman</i>	497
FREE WALL CHART:	
Circuit Building Blocks	

**NOVEMBER ISSUE WILL BE  
PUBLISHED ON OCTOBER 8th**

©IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

# NEWS... NEWS... NEWS...

## Viscount value



The Viscount III Audio System is the first of a range of audio equipment marketed in the UK by R+TV Components (Acton) Ltd. under the Viscount brand name.

The complete system includes a choice of two amplifiers, a Garrard SP25 Mk III turntable and two Duo type II or type III speakers.

Amplifier RT100 is for ceramic cartridges and model RT101 which has an additional input stage accepts magnetic types. Both amplifiers incorporate f.e.t.'s giving excellent signal to noise ratios.

Prices are: RT100, £17; RT101, £22; Garrard SP25 with ceramic cartridge, £21 or with magnetic cartridge, £23. Duo type II speakers cost £14 the pair and Duo type III, £32.

Savings can be made by buying complete systems.

## Impex cases

In last month's issue we stated the following about Impex instrument cases:

"At no additional cost, Impex cases can be supplied with all or some of these specifications: alternative colours of blue or bronze; no hood; no ventilating slots or back/front anodised front/rear panels".

What we should have mentioned is that these additions can only be supplied free of charge for quantities over 24.

## NHK's anniversary

June 1 saw the anniversary of the Radio Japan Service. Thirty-six years ago NHK commenced this service in commemoration of the 10th anniversary of radio broadcasting in Japan and the attainment of 2 million licensed subscribers.

From June 1934 to 1945, NHK broadcast its domestic programmes to Korea, Taiwan and Manchuria, then Japan's outlying territories, utilising telephone channels of the International Telephone Company. Shortwave broadcasts were received in various parts other than the areas directed, and reception reports

began to come to NHK from Japanese residing abroad and from large numbers of overseas people. In those days, Japanese living in various parts of the world totalled nearly two million. These people raised their voices requesting the establishment of an overseas broadcasting service. In Japan, too, commencement of an overseas broadcasting service was also strongly desired, since this country had been isolated after her withdrawal from the League of Nations and was in need of reinforcing its public relations abroad. At first the service was known as Radio Tokyo (Radio Japan was first used in 1952).

## Avo wall chart


Avo Limited (Thorn Group) announce a new wall chart featuring the latest Mark 4 version of the Avometer Model 8. The design and layout is such that it will prove of great interest not only to Avometer users but also to technical schools and general education establishments as a teaching aid.

Information is presented in a clear, logical manner and the theoretical and practical information is both concise and easy to understand. Magnetic theory is developed pictorially to outline the operation of the moving coil movement whilst a mathematical treatment is used to derive the various ranges of a multimeter.

Illustrations of the interior of the instrument include an exploded view of the movement to simplify the constructional detail and a circuit diagram provides an introduction to standard symbols and references.

The Avometer chart (size 20×30in., 508×762mm.) is ideal for black-board or wall presentation and is available from *Spares Dept., Avo Limited, Avocet House, Dover*, at 75p per copy, including post and packing.

## AVOMETERS

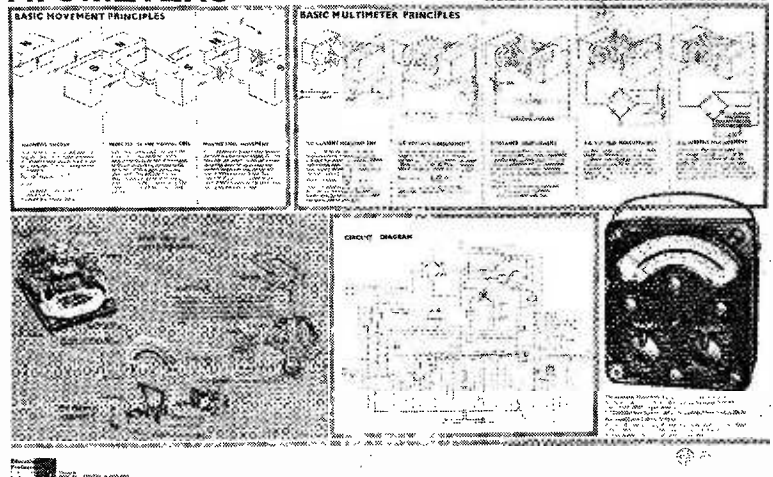

# NEWS... NEWS... NEWS...

## Windermere VHF

The v.h.f. radio services from the Windermere relay station started on August 7. Radio 2 is on 88.6MHz, Radio 3 on 90.8MHz and Radio 4 on 93.0MHz, all with horizontal polarization.

The v.h.f. radio transmissions from this new relay station, which is situated on Claife Heights, above the western shore of Lake Windermere, will serve Ambleside, Windermere town, Bowness-on-Windermere, and an area around the northern shores of the lake.

## Stereo from Rowbridge

The necessary equipment has now been installed at Rowbridge to enable the Radio 3 transmitter (90.7MHz) to broadcast stereo-phony. This is being brought into use immediately, so that listeners can hear the Promenade Concerts in stereo—all except four of the concerts will be broadcast stereophonically in Radio 3. The stereo transmissions from Rowbridge will initially be on an engineering test basis; every effort will be made to maintain them, but there may be occasions when it will be necessary to revert to monophonic transmissions. The date for the start of the full stereophonic service will be announced later.

## Miniature Electric Tools

A range of battery-operated miniature tools has been introduced by Expo (Drills) Ltd., 62 Neal Street, London, W.C.2.

Two basic models are available. The 'Reliant' is designed for lighter work such as model making, and has a full load current of 1.5A. Its rated torque is 1.38oz. in. (100 gm.cm.). For jobs requiring a more powerful tool and for professional applications the 'Titan Super' is rated at 3.5A on full load. It has a rated torque of 350cmp operating at 4000-9000rpm. An extremely large range of accessories is also available for both models. Various collets and accessories are supplied with the different models, which range in price from £3 to £5.50.

## Lectures


THE Polytechnic of North London Department of Electronic and Communications Engineering is running a course on Audio and Acoustic Measurements on Thursdays 6.30-8.30 p.m. 1971/2. 1971: Oct., 28, Parameters and Standards of Measurement R. N. Baldock, B.Sc., F.B.K.S.T.S. Nov. 4, Measurement of Microphone Performance, H. D. Harwood, B.Sc., B.B.C. Research; 11, Electrical and Mechanical Measurements in Tape Recording, R. L. West, B.Sc., C.Eng., F.I.E.R.E.; 18, Measurements in Professional Recording, Angus McKensie; 25, Electrical and Mechanical Measurements on Disc, Pickups and Accelerometers, S. Kelly, C.Eng., F.I.E.R.E. Dec. 2, Measurement of Loudspeaker Performance I, R. L. West; 9, Measurement of Loudspeaker Performance II, R. C. Driscoll, M.Sc.; 16, Measurement of Studio Characteristics, R. C. Driscoll, M.Sc. 1972: Jan. 13, Measurement of Noise Transmission, J. Moir C.Eng., F.I.E.E.; 20, Assessment of Noise Nuisance, J. Moir, C.Eng., F.I.E.E.; 27, Visit to A.I.R.O. Laboratories, Hemel Hempstead, G. Berry, B.Sc., C.Eng., M.I.Mech.E. and Assocs.

## Grand Junk Sale

The Star Short Wave Club, G3ZWA, is holding a "Grand Junk Sale" in aid of Radio Amateur Invalid Bedfast Club funds. It is to be held at the New Inn Hotel, Bramley Town Street, Bramley, Leeds 13. The date is Wednesday September 15th and time 7.30.

If any readers have any junk, the Star Club will collect within a radius of 25 miles from Leeds. Please contact Mr. T. Leeman, G8BUU, 115 Asket Drive, Seacroft, Leeds, LS14 1HX.


## Chip "C's"

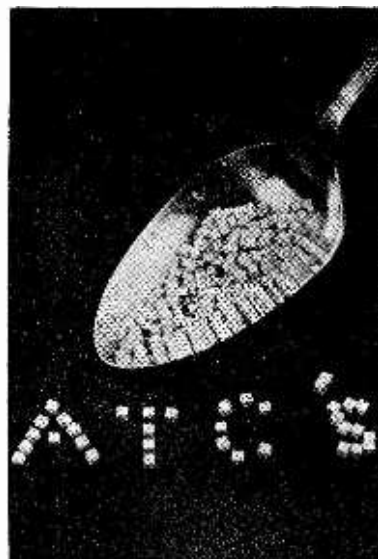


Featuring a very low insertion loss, a very high Q and high capacitance-to-volume ratios, a new range of ceramic and porcelain chip capacitors from Guest International Limited is ideal for u.h.f. and microwave applications. Apart from the basic pellet and chip, there is a wide choice of lead variations: stripline, axial and radial wire, axial and radial ribbon.

ATC 100 series are porcelain chips with an insertion loss of 0.03dB, a Q of over 10,000 and a capacitance range of 0.1 to 1000pF. In a case size of only 0.110in.square, the working voltage is up to 500V d.c.

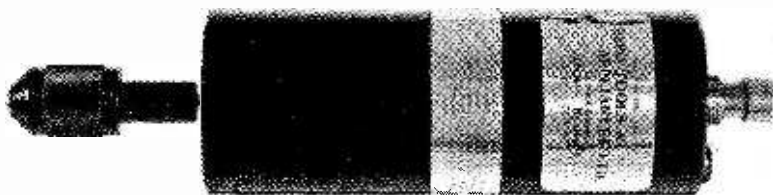ATC 200 series are ceramic chips with an insertion loss of 0.05dB. The capacitance range is 10pF to 1.2µF and chips are available in case sizes 0.050, 0.110 and 0.250in.square, depending on the value and the working voltage.



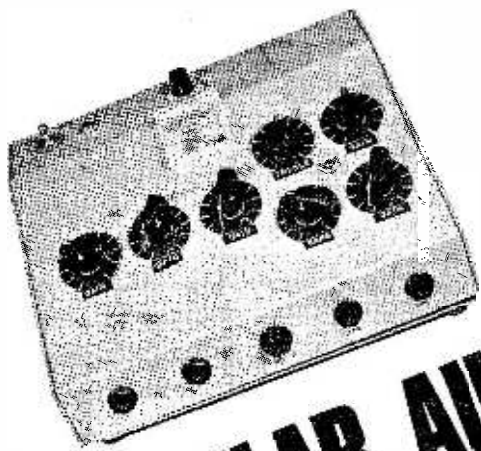

# MODULAR AUDIO MIXING SYSTEM

F.C. JUDD



So many audio sources are now in common use that an article describing a specific design would meet the needs of only a few. This problem is overcome here by giving circuits for virtually all sources and care in design has made possible a large number of permutations so that a custom built audio mixer is possible even for those readers unable to design their own. The clever constructional method employed also allows for rapid modification to meet any mixing need.

**A** STUDY of the four block diagrams in Fig. 1 will show how the various signal preamplifiers, the tone control unit and line amplifier etc. can be used to build audio signal mixing systems to cater for tape recording, public address, discotheque and even Hi-Fi applications. The combinations given are but a few of the permutations which can be extended for stereo use simply by duplication.

Each signal preamp has the same output level, 100mV, and will match directly into either the tone control unit or the line amplifier, both of which are designed to accept a signal level of 100mV. The tone control has unity gain so this provides 100mV output to match into the line amplifier. Any group of signal preamplifiers can therefore be coupled directly to the line amplifier or via the tone control unit and then to the line amplifier. This allows any of the signal preamplifiers to be used with or without the tone control unit.

The line amplifier has a nominal output of 1V r.m.s. at a fairly low impedance and can be used to drive a power amplifier module requiring between 500mV. to 1V input, or it can be coupled to a tape recorder or radio input, or to a public address or music amplifier with inputs rated for 500mV to 1V. Groups of the preamplifiers and line amplifier can be run from batteries or from an 18V mains power supply.

## COMBINATIONS


A fairly simple arrangement is shown in Fig. 1a and is intended for use as a general purpose signal mixer as shown on the front cover. This would be suitable for tape recording, as it has two microphone inputs, one input for low impedance pick-up (with R.I.A.A. correction), and two line level (200mV to over 1V) inputs. The tone control operates for the mic. and pickup inputs, whilst the line inputs go directly to the line amplifier. The system also includes a VU meter with variable control so that the meter can be set to read with the level meter on a tape recorder.

The combination shown in Fig. 1b has the same input channels but no tone control unit. The arrangement in Fig. 1c might be suitable for a small discotheque with one mic. input, two pickup inputs both via a tone control unit and one line input, suitable for the output from a tape recorder. For music application, Fig. 1d provides two mic. and two guitar inputs with separate tone control units for each guitar input. In each case the VU meter is optional but can be used as an overload indicator as will be shown later.


## PERFORMANCE SPECIFICATIONS

Seven preamplifiers will be described, each catering for specific signal sources as follows:—

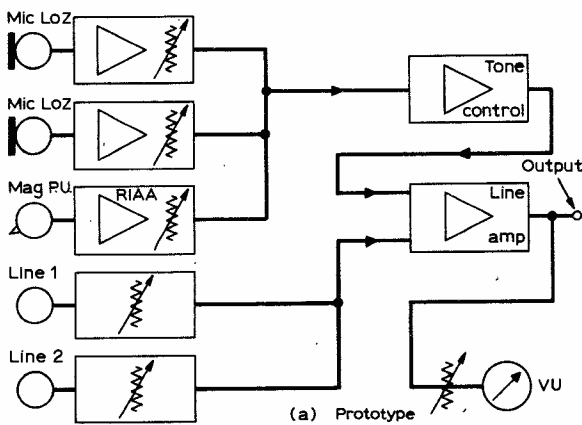
1. **LOW IMPEDANCE MICS.** (25 to 600 $\Omega$ ). Direct input, no transformer required. Input sensitivity 50 $\mu$ V. Output 100mV. Frequency response  $\pm$ 1dB. 30 to 30,000Hz. Signal-to-noise -50dB. (Code: **Mic. Lo-Z**).
2. **FOR MICROPHONES WITH BUILT-IN TRANSFORMERS.** Medium to high impedance. Input sensitivity 1mV. Output 100mV. Frequency response  $\pm$ 1dB 20 to 30,000Hz. Signal-to-noise -60dB. (Code: **Mic. Hi-ZT**).
3. **FOR CRYSTAL MICS.** High impedance. Input sensitivity 2mV. Output 100mV. Frequency response  $\pm$ 1dB 30 to 12,000Hz. Signal-to-noise -50dB. (Code: **Mic. Hi-ZX**).
4. **MAGNETIC PICKUP.** Impedance 56k $\Omega$ . Input sensitivity 5mV. Output 100mV. Frequency response to R.I.A.A. as shown in Fig. 2. Signal-to-noise -60dB. (Code: **PU Mag.**)




(a) Prototype

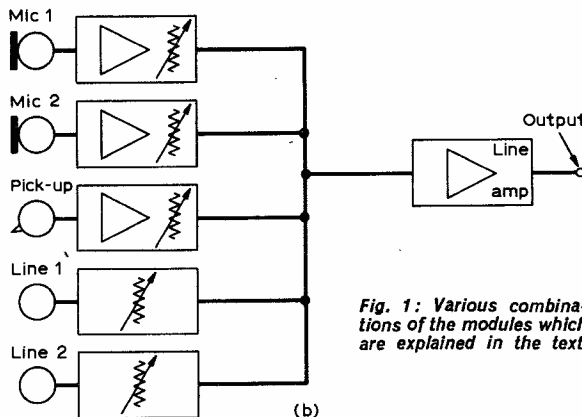

(b)

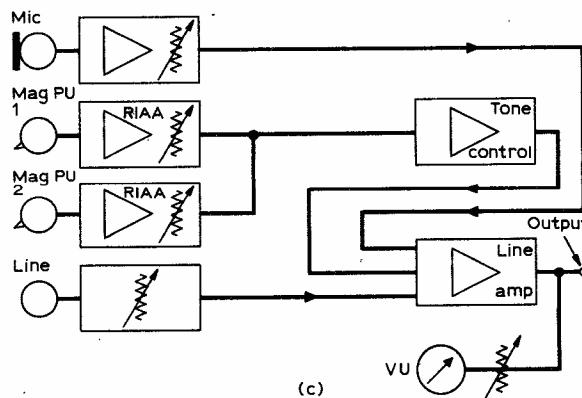

(c)

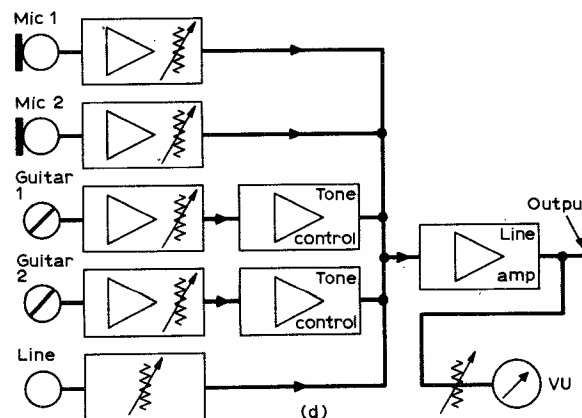

(d)

Fig. 1: Various combinations of the modules which are explained in the text.

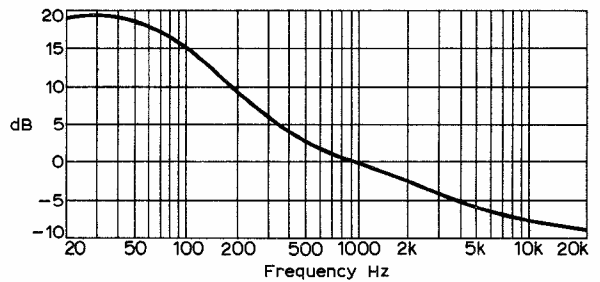


Fig. 2: The RIAA response curve incorporated in the magnetic pickup module.

5. CERAMIC PICKUP. Input impedance 2MΩ. Input sensitivity 60mV. Output 100mV. Frequency response approximately 20 to 20,000Hz ±1dB. Equalisation automatic due to high input impedance. Signal-to-noise -50dB. (Code: PU Cer.)
6. CRYSTAL PICKUP. Input impedance about 1MΩ. Input sensitivity 850mV. Output 100mV. Frequency response approximately 20 to 20,000Hz ±1dB. Equalisation automatic due to high input impedance. Signal-to-noise -60dB. (Code: PU Xtal.)
7. GUITAR PREAMP. Input impedance medium, 10 to 100kΩ. Input sensitivity variable. 50 to 100mV. Output 100mV. Frequency response ±1dB 20 to 30,000Hz. Signal-to-noise -50 to -60dB. (Code: G.)

The tone control unit will take the output from any of the preamps and provides 100mV output so that it can be coupled directly to the line amplifier. Its performance is as follows:— With tone controls neutral the flat response is 10 to 80,000Hz ±1dB. The response of the bass and treble controls is shown in Fig. 3 providing 15dB lift and 12dB cut at 40Hz and 15dB lift to 12dB cut at 20,000Hz The signal to noise performance is better than -90dB. (Code: TC.)

The line amplifier unit will accept the output from any of the preamps or the tone control unit and therefore has an input sensitivity of 100mV. The output signal level available is 1V r.m.s at an impedance of approximately 600Ω. The frequency response is flat from 10 to nearly 100,000Hz and the signal-to-noise performance -80dB. The output can be fed simultaneously to one or more tape recorders and/or amplifiers via series output resistors as will be shown. The overall gain of the line amplifier is adjustable i.e., the input sensitivity can be increased. (Code: LA.)

The line inputs do not require separate pre-amplifiers as these are arranged in passive network coupling directly to the line amplifier. The input sensitivity will be 200mV to over 1V r.m.s. at approximately 10kΩ impedance. (Code: L input.)

## CONSTRUCTION

The construction of each of the preamplifier modules is such that the circuit board is mounted on a small screen this, in turn, being secured to the fixing bush of the gain control (VR1 in each circuit). The complete preamp can therefore be secured to a front panel by the lock nut of the gain control. The tone control unit is similar except that there are two potentiometers and both are mounted on the small screen and then secured to the panel. The line amplifier can be simply mounted on a piece of aluminium angle (3/8 x 3/8 in) or on stand-off pillars as convenient. It need not be fixed to a panel but must

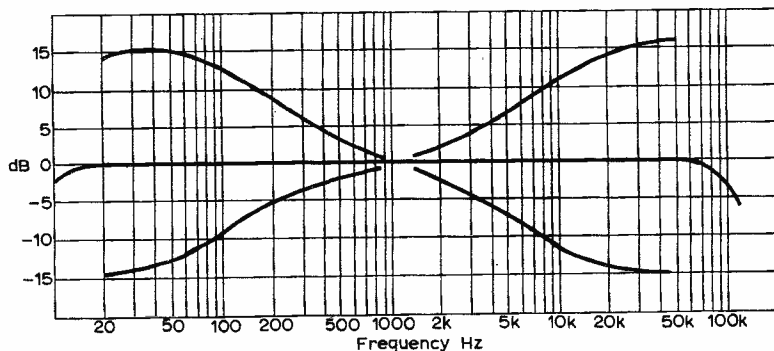


Fig. 3: Response curves of the tone control module.

be fairly well clear of mains power supply components. The input sockets for all inputs must be insulated from the front panel and earthed only at the common earthing point on the preamplifier board. If the mixing unit is to be mains powered, the components for the power supply must be kept as far away from the amplifier boards as possible and preferably with a screen around them.

The seven preamplifier boards are exactly the same and details for construction are given in Fig. 4. In each case the gain control (VR1) is fitted as shown


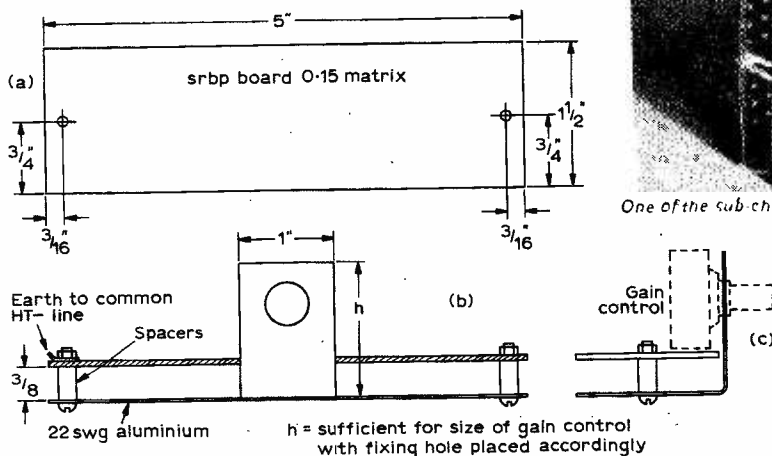


Fig. 4: Details of the sub-chassis used for each module.

in Fig. 4c. The construction of the tone control board is similar except that two controls have to be fitted so the screen has two flaps as shown in Fig. 5. The height of each flap and the position of the fixing hole will depend on the physical size of the potentiometers used.
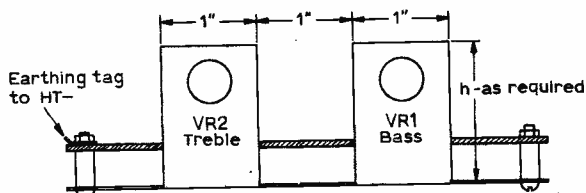
## CIRCUITS AND ASSEMBLY OF THE MODULES

Each of the amplifier modules and the tone control




Controls mounted as in Fig. 4 (c)

Fig. 5: Modified sub-chassis for the tone control module.

can be tested separately by operating them from an 18V battery (two 9V units) and by checking each one with an audio signal generator and audio voltmeter or by connecting an appropriate input signal source and feeding the output to an amplifier.
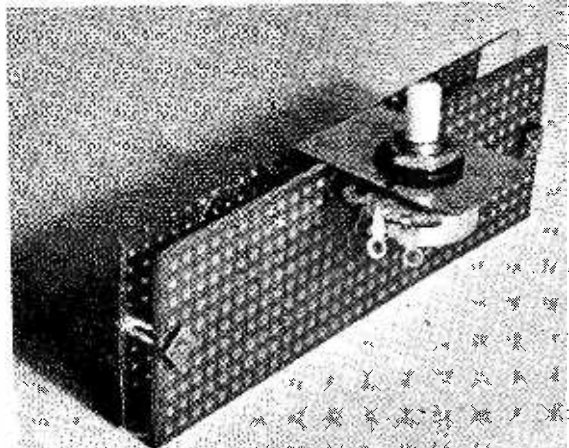
## LINE AMPLIFIER


The best order of construction is to build the line amplifier (code: LA) first so that the preamps can be tested with it as each is completed. The circuit is given in Fig. 6 and the board layout in Fig. 7. As



One of the sub-chassis before the components are fitted; dimensions are given in Fig. 4.

with all the circuits except the tone control unit only one type of transistor is used—the BC109 silicon NPN—which is readily available and inexpensive. The line amplifier employs three of these beginning with Tr1 as an emitter follower input stage with Tr2 as the amplifier.

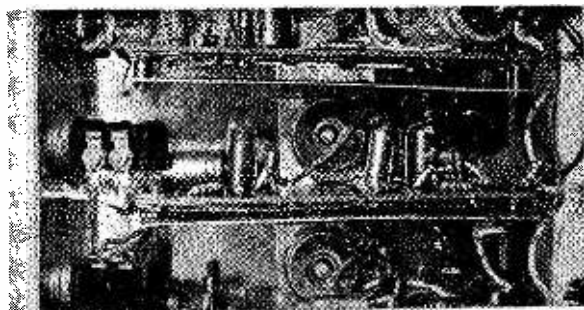Negative feedback between Tr2 and Tr1 via the pre-set PR1 ensures a linear response and some adjustment over total gain. The pre-set should be adjusted so that with a 100mV input signal the output at C6 is exactly IV. If a signal generator and audio voltmeter are unavailable, set PR1 to mid-way position. The output transistor Tr3 operates as an emitter follower and provides a low impedance



An internal view of the prototype showing one of the modules. The input jack is on the left with the common wiring on the right.

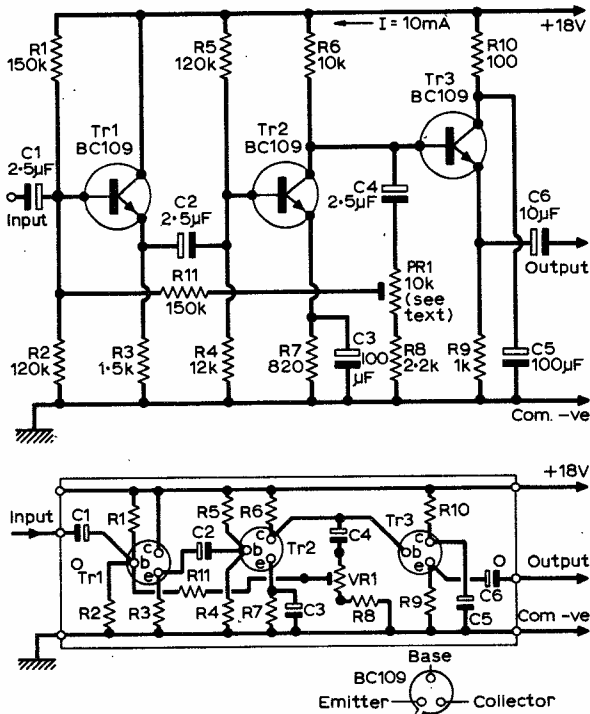


Fig. 6: (above) and Fig. 7 (below): The circuit and layout of the line amplifier module.

output. Details for feeding more than one power amplifier and/or tape recorder from the line amplifier output will be given later.

### MICROPHONE PREAMP (Mic Lo-Z)

The circuit is given in Fig. 8 and the board layout

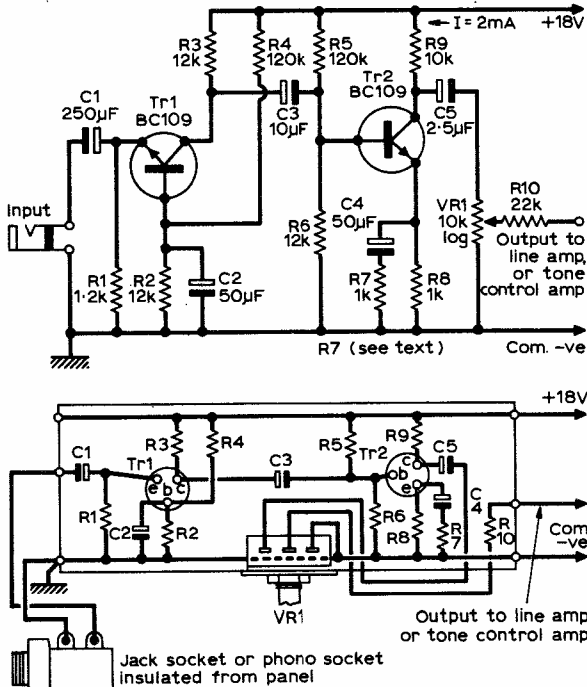


Fig. 8 (above) and Fig. 9 (below): The circuit and layout of the low impedance microphone preamplifier module.

## ★ components list

### Amplifier Modules Circuit Boards

1/16" MATRIX s.r.b.p. board to sizes given. 22 g. w.g. aluminum for module screens to sizes given.

#### Line Amplifier (LA)

Tr1, Tr2, Tr3 BC109  
PR1 10kΩ Miniature carbon pre-set

#### Resistors

R1	150kΩ	R6	10kΩ
R2	120kΩ	R7	820Ω
R3	1.5kΩ	R8	2.2kΩ
R4	12kΩ	R9	1kΩ
R5	100kΩ	R10	100Ω

All 1/4W, 10% types

#### Capacitors

C1	2.5μF	25V	C4	2.5μF	25V
C2	2.5μF	25V	C5	100μF	25V
C3	100μF	25V	C6	10μF	25V

#### Microphone Pre-amplifier (Mic. Lo-Z)

Tr1, Tr2 BC109  
VR1 10kΩ Log. Potentiometer

#### Resistors

R1	1.2kΩ	R6	10kΩ
R2	15kΩ	R7	1kΩ
R3	12kΩ	R8	1kΩ
R4	12kΩ	R9	10kΩ
R5	120kΩ	R10	22kΩ

All 1/4W, 10% types

#### Capacitors

C1	250μF	25V	C4	50μF	25V
C2	50μF	25V	C5	2.5μF	25V
C3	10μF	25V			

#### Power Supply

Transformer T1 18V Secondary Henry's Radio Type MT95  
Bridge Rectifier MR1 Henry's Radio Type LT118

C1	250μF	25-30V
C2	5000μF	25-30V
R	1W	see text

On/Off main toggle switch.  
Panel neon indicator.  
All electrolytics used in the amplifier circuits should be rated for at least 25V working.  
Each pre-amplifier will require an input jack socket or phono socket of the type that can be insulated from the panel on which they are mounted.


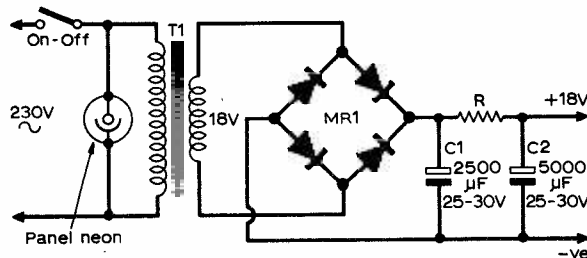


Fig. 10: Suggested circuit for a mains power supply to power the mixer.


in Fig. 9. The input transistor Tr1 operates as a grounded base amplifier and provides a very low impedance input. Tr2 is a signal amplifier with negative feedback introduced by R7 in series with the emitter by-pass capacitor C4. This resistor can be reduced a little in value to obtain more gain for very low output microphones, although it should not be less than 680Ω otherwise the noise level will rise excessively. As with all the preamplifiers the output is taken to the gain control VR1 and thence via the series resistor (R10) which becomes part of the passive mixing network common to all the preamps.
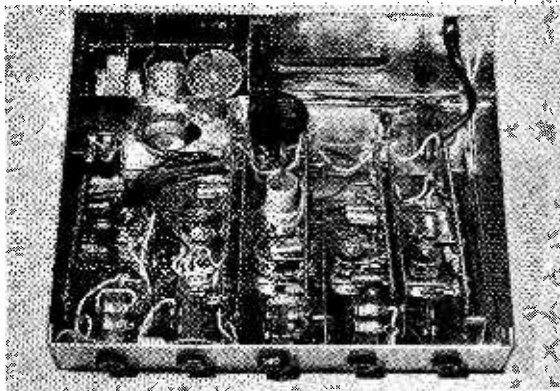
## MAINS POWER SUPPLY

The current consumption of the preamplifiers at



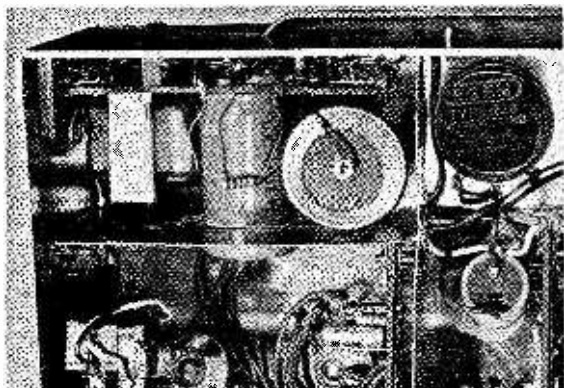*Internal view of the completed prototype.*



*The power supply should be properly screened as shown.*

18V varies between about 2 and 5mA. The line amplifier takes 10mA and the tone control unit 5mA. Four preamplifiers, a line amplifier and say one tone control unit, would require about 25mA which could be drawn from an 18V battery with reasonable economy. Two PP9 batteries would be ideal. Larger mixing units, particularly if built for stereo use and requiring duplication of preamps etc. are best operated from a mains power supply. One that will provide well over 100mA is given in Fig. 10 (see components list for transformer and rectifier details). The resistor R will be around 1kΩ for low current drain and of lower value for higher current drain. With the mixing circuits running, adjust R to obtain 18V across C2.

Part 2 next month, will deal with the rest of the preamplifier modules.

**TO BE CONTINUED**

CHARLES MOLLOY

# THE Medium Wave Column

**A** NEW 1000kW station on 1457kHz located near Tirana in Albania is being heard in this country as a background to BBC Radio 4, (South and West). It relays Radio Peking and has been heard at 2100hrs GMT with the identification 'Govarit Peking' followed by programmes in Russian. An increasing number of superpower broadcasters are appearing on the medium waves. Urumchi in Western China (2000kW) is audible all evening on 1525kHz; listen between Prague 1520kHz and Vatican Radio 1529kHz for Russian speech plus jamming. Libya has two megawatters—El Beida on 1124kHz and Tripoli on 1250kHz. El Beida is the stronger of the two; it is heard with EAJ15 Barcelona on the same frequency throughout the evening. Tripoli suffers from interference from Dublin/Cork until 2245hrs when the latter close down, leaving the channel clear. Further east, Riyadh (1200kW) in Saudi Arabia is on 587kHz and has been logged before midnight with Arabic programming.

Calcutta 1130kHz (1000kW) was heard frequently last winter before sign-off at 1700hrs. It is now on extended schedule and has been several times during the summer at 2230hrs GMT, as it changes from Chinese to Indian programming. There are three Voice of America stations in the Far East, each with 1000kW, all of which have been heard in the U.K. Bangkok, Thailand 1580kHz was logged at the end of September last year at 2200hrs GMT while Poro 1140kHz in the Phillipines and Okinawa 1178kHz in the Ryuku Islands are both heard in winter before sign-off at 1700hrs.

'Book of the World 1971' is the title of an unusual paperback now on sale in the bookshops. Sections deal with 181 different countries, each with a map plus details of the type of government, languages spoken, religions and currency. As well as providing the DXer with a valuable aid to station identification, this book gives background information on countries logged and adds interest to the hobby.

Broadcasts in English on the medium waves can be heard from a number of unexpected places during the late evening. Timisoara, Rumania on 755kHz has a programme in English, French and German at 2250hrs GMT, which should not be confused with the Voice of the West, in Portugal, also on 755, which starts its English programmes at 2245hrs. The Voice of America in Rhodes is 1259kHz is heard regularly in English between 2100hrs and midnight, with some interference from Wroclaw in Poland. Rhodes is one of the Dodecanese Islands situated near the coast of Turkey, which are usually counted as a separate country by DXers. The VOA is also heard in English from Thessalonika, Greece 791kHz between 2100hrs and 2130hrs. Enugu, Nigeria 1320kHz, although only 10kW, is a weak but consistent signal at 2300hrs GMT when it carries it's final news in English before closing down. ELBC Monrovia, Liberia on 629kHz has English programming and is usually logged between 2330hrs and sign-off at 0045hrs.






# IN NEXT MONTH'S

# PRACTICAL WIRELESS


## 2-Octave Miniature Organ

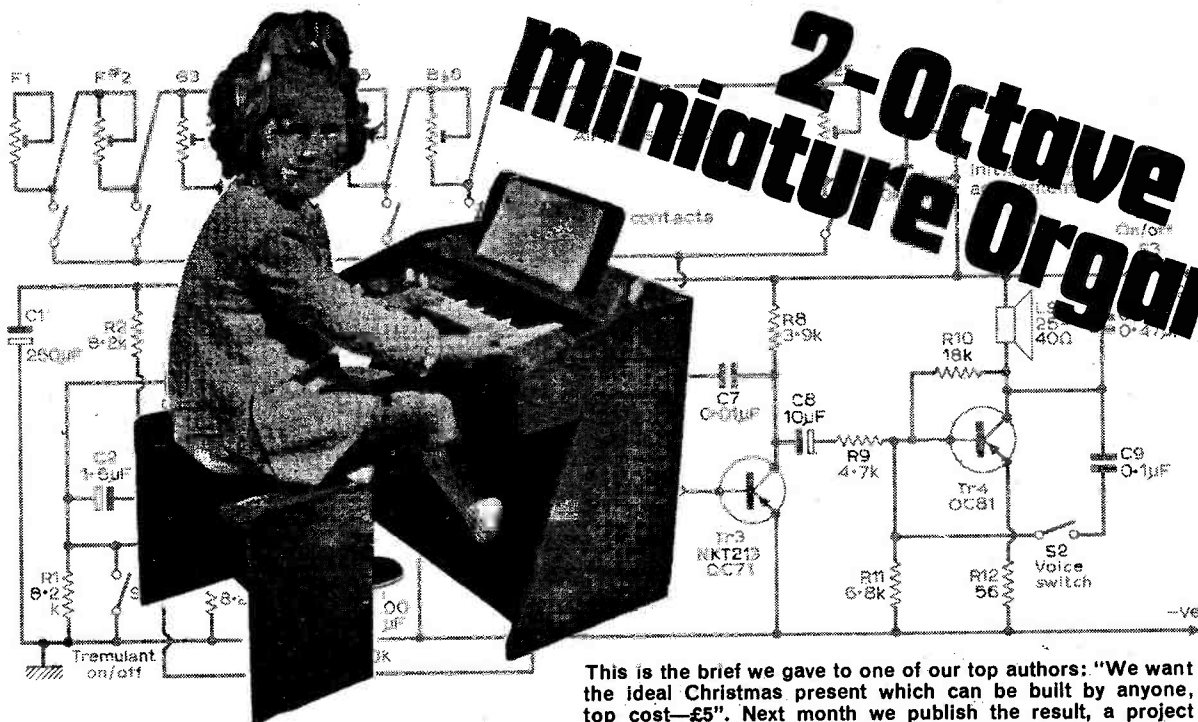
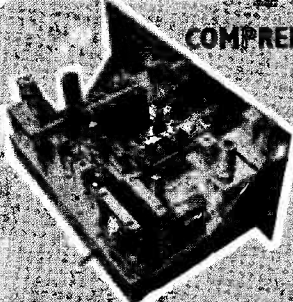
### Special Feature


This is the brief we gave to one of our top authors: "We want the ideal Christmas present which can be built by anyone, top cost—£5". Next month we publish the result, a project which will go down as one of the all-time 'greats', a **2-Octave Miniature Organ**—complete with voicing and tremulant. The electronics is dead simple (just look at the circuit sketch above!) and the cabinet woodwork can be built by anyone who can use a saw. The £5 cost includes everything—just as you see it.

\*  
 What  
 to look  
 for at the  
**AUDIO  
 FAIR**  
 \*



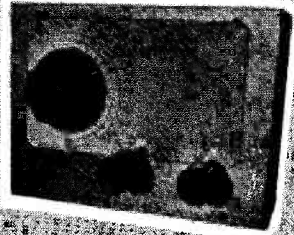**COMPREHENSIVE MULTI-BAND RECEIVER**

Do you want to build a communications receiver in easy stages? This design initially provides a basic 3 valve receiver, complete in itself, covering 550kHz to 30MHz with full bandwidth. At your leisure add an RF stage, a simple crystal filter, a carrier oscillator/product detector for receiving SSB/CW and finally a crystal marker. Full constructional details.





**BASIC SIGNAL GENERATOR**

A signal generator is essential for the testing, alignment and calibration of receivers and for quick tests of audio circuits. For the beginner or occasional dabbler, this basic design should prove ideal, with modulated or unmodulated outputs from 150kHz to 1.6MHz, plus a direct audio source; all outputs are fed via a variable attenuator.

**ALL IN THE NOVEMBER ISSUE  
 ON SALE OCTOBER 8th**

Plus many other constructional articles and all the regular features. Be certain not to miss the next issue, price 20p.

# DIGITAL FREQUENCY COUNTER/TIMER

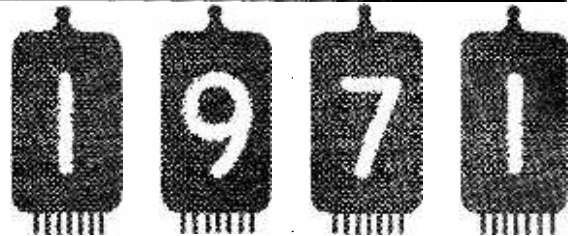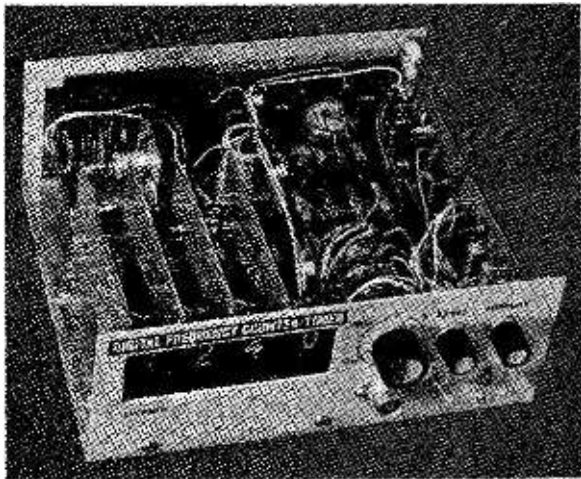

J. THORNTON-LAWRENCE GW3JGA

## PART 2 (continued from the September issue)

This negative going step is passed by C5 to Tr7 base which moves by  $-5$  volts thus cutting off Tr7 and allowing the collector of Tr7 to rise to  $+5$ V.

The current through VR2 and R14 discharges C5 so that the negative voltage on Tr7 base rises exponentially until Tr7 conducts. The rate is determined by the setting of VR2, the DISPLAY control.

When Tr7 conducts, its collector voltage starts to fall, turning off Tr6 and thus increasing the base current to Tr7 and producing a fast negative going voltage at Tr7 collector. This voltage step is differen-

tiated by C7, R16 and R17 and inverted by IC2d to give a positive pulse of  $200\mu\text{s}$  duration.

The positive going edge of this pulse resets the counter to zero and the negative going edge sets the JK flip-flop IC1a and causes the cycle of operation to be repeated. The time for which the reading is displayed is controlled by the DISPLAY control and this is adjustable from about 0.5 second to 2 seconds.

### NOTE

Several wiring connections were omitted from figure 6 in the September issue. Pin 10, on IC's 3, 4, 5, 6 and 7, should be shown connected to the OV rail. Pins 1 and 12 on IC's 9, 11, 13 and 15, should be shown joined.

On IC1, pin 4 is the  $+5$ V supply rail and pin 11 is OV supply rail. On IC2, pin 14 is  $+5$ V supply rail and pin 7 OV supply rail. These latter connections were omitted from figure 6 for clarity.

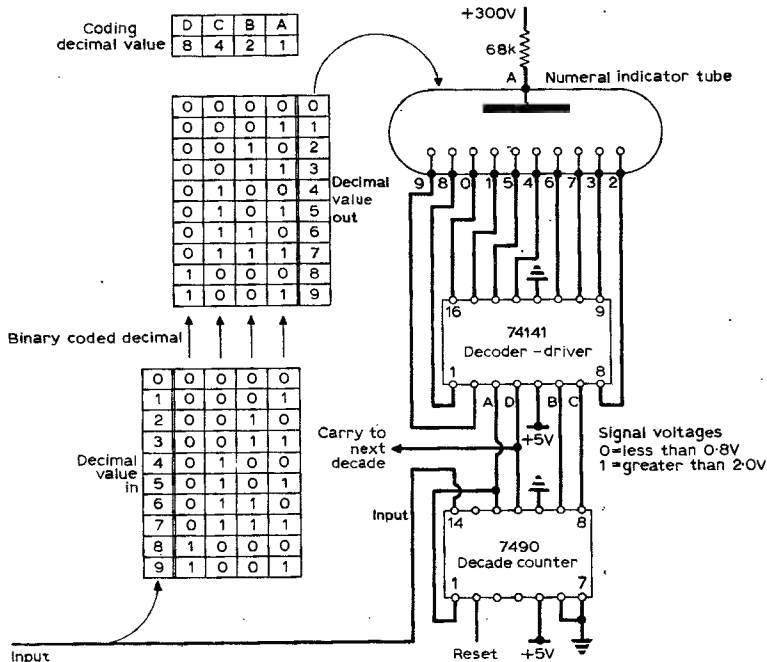


Fig. 9: Table showing the operation of the decade counter and decoder-driver.

## Counter and Display

The counter and display has four decades, each decade operates in the same way. The output of one decade is linked to the input of the next higher decade to perform the 'carry' operation and a reset connection is common to all decades.

The input to the counter is a series of pulses. The counting has to be carried out in binary form and then decoded into decimal form for display.

This is done using a decade counter I.C. type SN7490N, which consists of 4 master-slave flip-flops forming a  $\pm 2$  counter and a  $\pm 5$  counter.

The input signal goes to the input of the  $\pm 2$  counter (pin 14) and the output of this (pin 12) is linked externally to the input of the  $\pm 5$  counter (pin 1).

The outputs of the four flip-flops are called A, B, C, D and have a decimal value of 1, 2, 4, 8 respectively. The table showing the operation of the decade counter is included in Fig. 9.

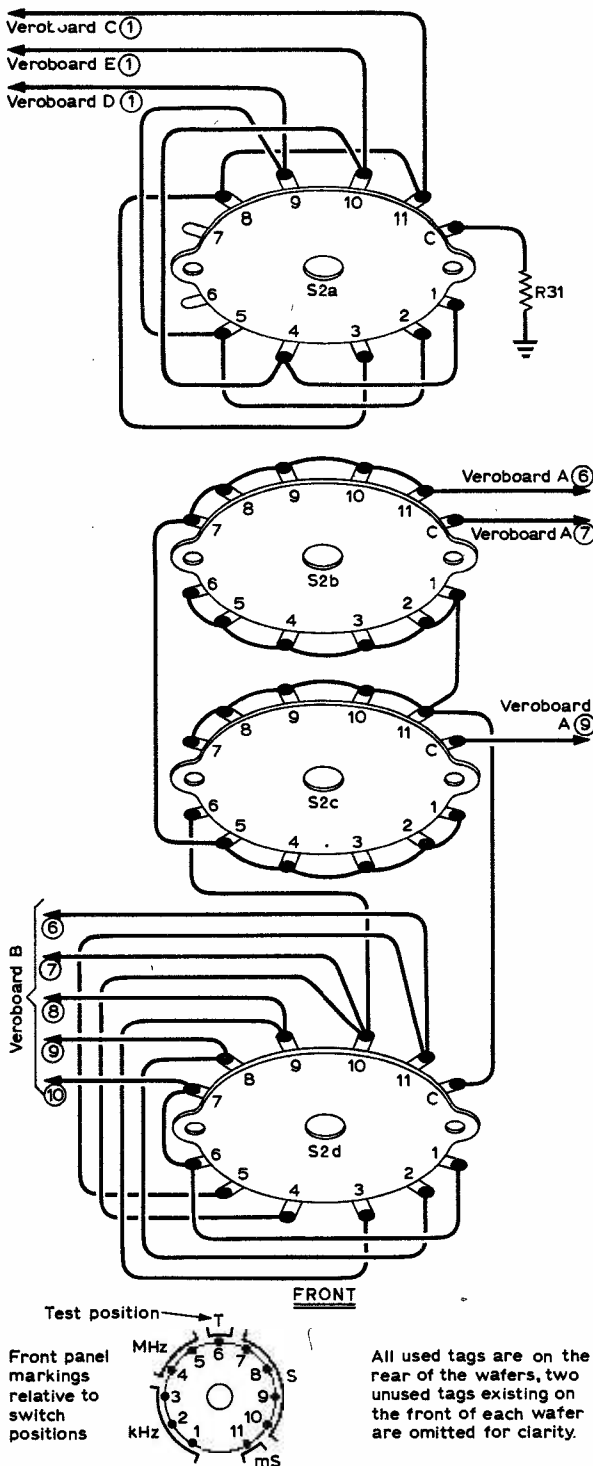


Fig. 10: Exploded view of the function switch S2, viewed from the front.

The counter can be reset to zero at any time by the application of a positive pulse to pin 2.

The binary coded decimal output from the counter, A, B, C, D is connected directly to the inputs of the decoder/numeral tube driver I.C. type SN74141N. Here the inputs are decoded back into decimal form

for driving the numeral tube (Hivac Type XN13).

The numeral tube contains neon gas at low pressure and has an anode and 10 wire cathodes in the form of numerals, 0-9.

With the anode connected to HT+ through a current limiting resistor, any cathode which is connected to 0V will be surrounded by a glow showing up the shape of the number.

The outputs of the decoder-driver are collector circuits of high voltage transistors which, when made to conduct, effectively connect the appropriate cathode to 0V. For example, suppose the input to the decade counter receives 5 pulses or cycles of input signal. The output will be D low, C high, B low, A high, representing a binary number of 0101. This number is decoded in the decoder/driver to figure 5 and the figure 5 output (pin 14) becomes switched to 0V causing the figure 5 to be displayed in the numeral tube.

Each counter, decoder/driver and tube is built on a Veroboard panel and the inter connection of these panels is shown in the main diagram Fig. 6.

The decimal indication is provided by miniature wire ended neon indicator lamps mounted between two numeral tubes and these are switched by the function switch S2a.

## Function Switch

The function switch S2 is made up from Radiospares Miniature 'Maka Switch' parts and consists of a shafting unit and 4 break-before-make 1 pole 12 way wafers. The wafers are spaced by 2 spacers on each side. Only 11 positions are used and the stop on the indexing mechanism is adjusted accordingly.

The wafers are lettered a, b, c and d, starting at the rear and working towards the indexing mechanism. Wafer 'a' controls the decimal point neon lamps, wafer 'b' the clock period input to the gate, wafer 'c' the signal input to the gate and wafer 'd' the output from the clock divider.

In the frequency positions 1 to 5, the output from the input stage is fed to the 'Signal Input' of the gate and the appropriate clock signal is fed to the 'Clock Period Input' of the gate. In the time positions, 7 to 11 of the switch, the output from the input stage is fed to the 'Clock Period Input' of the gate and the appropriate clock signal is fed to the 'Signal Input' of the gate.

A test position is provided in position 6 where the 1kHz clock output is counted for a period of 1 second to give a reading of 1,000. The test position only serves to check that the gate, counter and display are functioning, it does not provide a check of the crystal oscillator frequency.

The wiring and connections to the switch are shown in Fig. 10. The method of assembly is as follows:

1. On the shafting unit, check that the lengths of studding are screwed fully into the indexing mechanism plate and remove the end nuts and washers.
2. Rotate the switch spindle to the fully anti-clockwise position (as viewed from the front). The flats on the wafer end of the spindle should be in line with the studding. This is position "1".
3. The switch should now be held so that the lengths

of studding are at each side and the control knob end of the spindle is towards you, as shown in Fig. 10.

4. Take a 1 pole 12-way wafer and hold this with the side having the majority of tags, away from you and with the two tags that are facing you positioned in the top right hand segment. Rotate the rotor section until the common or rotor contact is making contact with tag 1. The slot in the rotor should now be horizontal.

5. Assemble the wafer on to the shafting assembly, keeping the side with the majority of tags facing away from the indexing mechanism. This wafer is now wafer "d" in Fig. 10.

6. Fit 2 spacers on each piece of studding.

7. Fit another wafer as described in operation 4 and 5 (wafer "c").

8. Repeat operations 6 and 7 until four wafers have been fitted (wafers "b" and "a").

9. Fit washers and fixing nuts to the studding.

10. The rotation of the switch should now be checked to see that all parts operate smoothly.

11. The rotatable stop plate, which is located on the face of the indexing mechanism, should now be set to give 11 positions, working clockwise and commencing from the maximum anti-clockwise position. This is the position at which all the wafers have been set. The stop plate may be held in place temporarily by the mounting nut, ready for assembly to the front panel.

12. The wiring of the switch may now be carried out as shown in Fig. 10. 22 s.w.g. tinned copper wire is used for wiring from tag to tag, sleeving being necessary only when crossing between wafers.

13. The correctness of the wiring can be checked by using an ohm or continuity meter and measuring between the appropriate tags whilst the switch is rotated, e.g. S2b/C is connected to S2d/C in positions 1, 2, 3, 4, 5 and 6.

## Power Supply

The power supply consists of a Radiospares Midget Mains transformer which with its associated rectifiers smoothing and regulators provides

+300V at 10mA	Unregulated
+5V at 350mA	Regulated
-5V at 5mA	Regulated

The output from the 250 volt secondary winding is rectified by D7 and smoothed by C12 to give about +300V output. The negative return is through R24 and D9 to 0V. The negative supply derived in this way is smoothed by C13 and regulated by the zener diode D9 to give -5V. The I.C. logic requires about 350mA at +5V and this is provided by the 6.3 volt filament winding on the transformer.

The 6.3 volt output is full wave bridge rectified to give about +7.5 volt across the reservoir capacitor C14. This feeds the zener diode D6 and the power emitter follower Tr11 to give the required 5V output.

## Veroboard Panels

The layout drawings of the 0.1x0.1in matrix Veroboard show the copper strip side of the panel the components on the reverse side being "seen through" the copper strips.

Each copper strip is given a letter code and each

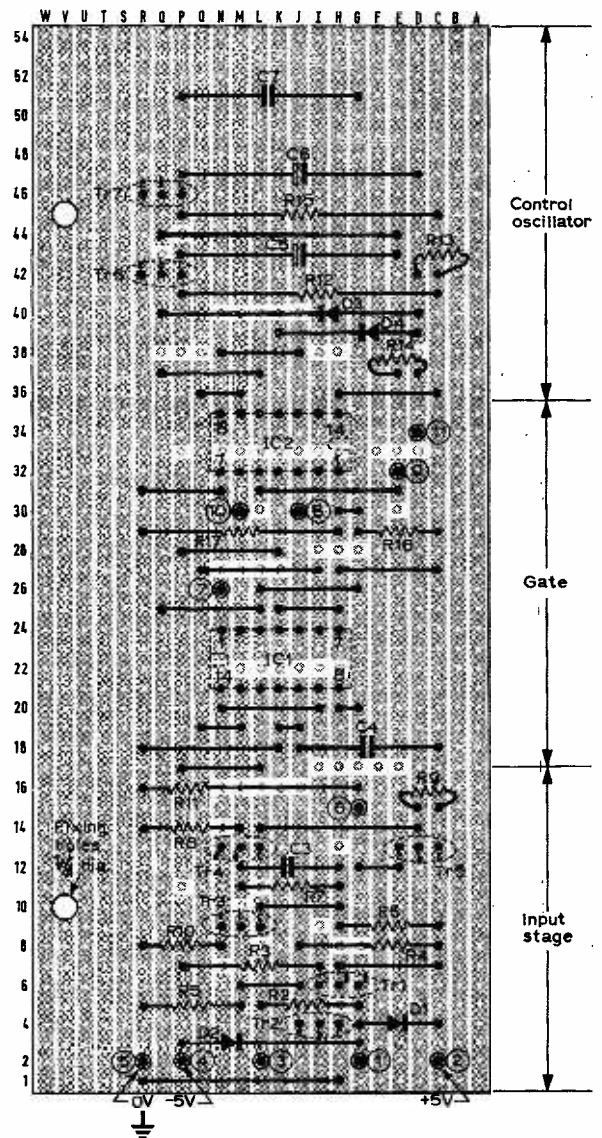


Fig. 11. Veroboard panel A. Input stage, gate and control oscillator. Viewed from copper side. Note correct orientation of integrated circuits when fitting. The integrated circuits and their holders are indented at one end to assist orientation.

horizontal row of holes, a number.

All solid horizontal lines represent wire links which connect one strip to another.

The orientation of integrated circuits and transistors should be noted carefully, some transistors may have unusual lead positions and these may have to be crossed over for the connections to be correct. Assembly of the components, etc., must be carried out in a systematic manner or errors will result. A suggested method is as follows:

1. Cut the Veroboard to the correct dimensions using a fine toothed saw and working from the copper side. Apart from checking the physical dimensions, also check that the correct number of holes appear in each direction.

2. Fix strips of masking tape on all four edges of the Veroboard panels. Also fix masking tape to the same edges on the reverse (copper) side of the board.

# DISCOUNTS UP TO 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

SONY · LEAK · SINCLAIR · TELETON · ARMSTRONG · THORENS · PHILIPS · K.E.F. · TEAC · ROGERS · PIONEER

## SPECIAL OFFER

Garrard SP25 Mk.III.

Goldring G800H

Teak plinth and tinted cover. Ready wired for immediate use.

£18-50

Please add £1.15 for post & packing

## TURNTABLES

Please add 50p for post and packing

*Garrard SP25 Mk.III	£10-75
*Garrard 2025TC with stereo cart.	£8-00
*Garrard 2025TC with Sonotone 9TAHC	£8-95
*Garrard 3000 with Sonotone 9TAHC	£10-25
*Garrard SL65B	£18-25
*Garrard AP76	£18-75
*Garrard SL72B	£24-00
*Garrard SL76B	£28-00
*Garrard SL95B	£35-50
Garrard 401	£27-00
*B.S.R. MP60	£11-00
Pioneer PL12AC	£39-00
Thorens TD 126	£32-50
Thorens TD 126 AB	£38-50
Thorens 150 AB11	£42-50
Goldring GL69/2	£21-50
Goldring GL69 P2	£29-50

\* Items marked can be mounted in plinth and cover, ready wired for £4-50 extra plus 25p for post & packing.

## AMPLIFIERS

Please add 50p for post and packing

Armstrong 521 (cased)	£41-95
Armstrad 8000	£17-70
Dulci 207	£15-95
Dulci 207M	£21-00
Euromon 10+10	£14-50
H.L. Audio 707	£17-75
Metrosond ST20E	£29-00
Philips R580	£20-50
Pioneer SA500	£41-50
Pioneer SA700	£38-00
Pioneer SA900	£34-50
Rogers Ravensbrook Chassis	£35-00
Rogers Ravensbrook Cased	£41-00
Rogers Ravensbourne Chassis	£45-00
Rogers Ravensbourne Cased	£48-50
Sinclair 2000-Mk1	£21-00
Sinclair 2000 Mk1I	£22-25
Sinclair 3000	£22-50
Sinclair PRO 60/2 x Z30/P25	£15-75
Sinclair PRO 60/2 x Z30/P26	£18-00
Sinclair PRO 60/2 x Z50/P28/Trans	£22-95
Teleton SAQ208	£18-00

## TUNERS

Please add 50p for post and packing

Armstrong 523 AM/FM	£40-00
Armstrong 524 FM	£31-00
Dulci FMT7	£19-50
Dulci FMT7 Stereo	£26-00
Teleton GT101 MP1X	£30-50
Rogers Ravensbourne FET 2 Chassis	£45-50
Rogers Ravensbourne FET 3 Cased	£49-00
Rogers Ravensbrook FET 4 Chassis	£37-50
Rogers Ravensbrook FET 4 cased	£33-00

## PICK-UP ARMS

Please add 35p for post and packing

SME 3009/S2	£33-95
SME 3012/S2	£25-75
Goldring L75	£9-80
Goldring L69	£7-50
Audio-Technica AT1005	£14-95

## TUNER AMPLIFIERS

Please add 75p for post and packing

Armstrong 525FM	£38-75
Armstrong 528 AM/FM	£78-75
Teleton CR10T with speakers	£26-25
Teleton F2300 (new product)	£38-50
Teleton CR55	£27-00
Teleton TRF50	£31-75
Teleton P2000	£31-00
Wharfedale 100-1	£103-00
Teleton TRF50LA	£80-00
Teleton 2100	£34-00

## SPEAKERS

Please add £1.25 for post and packing

(PRICE PER PAIR)

Wharfedale Denton	£29-75
Wharfedale Melton	£49-90
Wharfedale Triton	£45-75
Wharfedale S/Linton	£40-75
Keleton KN500	£15-00
Keleton KN700	£18-00
Keleton KN123/3	£11-50
Keleton KN1000	£27-50
Keleton KN1500	£27-00
Keleton KN2000	£41-60
K.E.F.	by letter
Celestion Ditton 120	£25-50
Celestion Ditton 15	£49-50
Celestion Ditton 25	£101-00
Celestion Ditton 10	£27-50
Ste-Ma 400	£34-00
Ste-Ma 300	£48-50
Ste-Ma Hi-Fi 4	£78-00
Ste-Ma Hi-Fi 115	£17-50
Ste-Ma Hi-Fi 3	£39-50

## GLOBAL CONTRACT SERIES

Contract 8 3-way 7 watts R.M.S.	£16-00
Contract 6 3-way 5 watts R.M.S.	£10-75

## SPEAKER KITS

Wharfedale Unit 3	£20-50
Wharfedale Unit 4	£27-00
Wharfedale Unit 5	£39-00

## CARTRIDGES

Please add 10p for post and packing

Goldring G850	£3-75
Goldring G800H	£5-50
Goldring G800	£2-75
Goldring G800E	£10-50
Goldring G800SE	£15-25
Sonotone 9TAHC Diamond	£1-75
Shure M3DM	£4-75
Shure M445/7/C	£7-00
Shure M55	£9-00
Shure M75E	£14-00
Shure V15 Type 2	£28-00
Shure M44E	£3-00
Shure M31E	£2-50
Shure M32E	£3-00
Audio-Technica AT66	£4-95
Audio-Technica AT35	£14-25
SMC 101	£2-75
MC15	£4-50

## TAPE DECKS & RECORDERS

Please add 75p for post and packing

Teleton FXB 510D	£44-75
Teleton TCR150	£23-90

## PERSONAL CALLERS VERY WELCOME!

Come and browse through our multi 1,000 foot warehouse/showroom. NO PARKING PROBLEM

## PURCHASE TAX CUT!!

—we pass these reductions to you

The following branded names are not allowed to be advertised at Discount Rates—SONY, SANYO, BANG & OLUFSEN, TRIO, RADFORD, SONAB, NIKKO, CHILTON, FERROGRAPH, LUXOR, CELESTION, AKAI, TANNAY, TANDBERG, TEAC, CAMBRIDGE, ARENA, ROTEL. Send a stamped addressed envelope for a GUARANTEED DISCOUNT PRICE.

## PLINTHS & COVERS

(as illustrated)

£3-20



plus 35p post and packing

Finished in real teak veneer with tinted dustcover. Ready to use (fully assembled). Suitable for Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B.

ALSO FOR B.S.R. McDONALD MP60 AND OTHERS Plinths and Covers for AP76; AP75; SL72B; SL75B; SL95B. £4-20 plus 35p post and packing.

Also finished in walnut to match Japanese equipment—no extra charge.

## GLOBAL TRANSEUROPEAN COMBO

Made by world famous European manufacturer

## COMPLETE HI-FI STEREO SYSTEM

### VHF/MEDIUM/LONG WAVE Tuner Amplifier

4 watt per channel, separate tone and balance controls. Two neat speakers with wooden slatted front. Single play deck in plinth and cover. Finished in teak. Fully guaranteed 12 months. On constant demonstration.

£37-50

plus £1-25 carriage



# GLOBAL AUDIO DISCOUNT WAREHOUSES


Dept. (p.w.z.) 174 Pentonville Road, London, N1. Telephone 01-278 1769

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).


# BETTER GET 'SET'

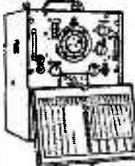

**BEST OFFER YET!**  
**FAMOUS BC.211**  
**FREQUENCY METER**  
 125 KHz-20 MHz. Complete  
 with valves, crystal and charts.  
 ONLY £18.50. Carr. £1.50.  
**LIMITED NUMBER - ORDER**  
**NOW!**
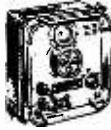
## CRYSTAL CALIBRATOR

**No. 10** Crystal controlled hetero-  
 dyne wave-meter covering 500 KHz-  
 10 MHz (Harmonics up to 30 MHz).  
 Power required 300V. D.C. 15mA.  
 12v. 0.8A. D.C. Test equipment for  
 627M/BC.  
 ONLY £4.25. P. & p. 50p.  
**FEW ONLY - No. 63 TM/BC**  
 1.5-10 MHz at £17.50. Carr. £2.



**MARCONI 801A SIGNAL GENERATOR**  
 10-310 MHz. In original transit case. £45. Carr. £2.50.

## AERIAL MAST

### EQUIPMENT

#### 20' TELESCOPE MASTS


£3.75. Carr. £1.

5' 2" Extension Sections to fit bottom of above mast to increase height. £1.25 each (any number supplied).

30' MAST 7-5' 2" interlocking sections with base plate and 12 nylon guys with semi-auto tensioner.

£23.50. Carr. £2.50.

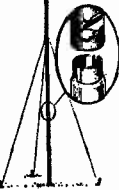70' MAST. Ditto. 16 guys, block and tackle. £45. Carr. £2.75.



## AERIAL RODS 3ft.

Screw-in 1/4" dia. sections. Brand New, green finish. Suitable for many other uses. 10 for £2. Carr. 50p. 25 for £5. Carr. Paid.



## R.F. ANTENNA TUNER (A.T.U.)

Cylinder design 10" x 4". Precision calibrated scale. Suitable for tuning most aerials for increased signal strength. A must for serious operators for BC or TM. Full instructions. ONLY £1.75. P. & p. 25p.

## R.F. ANTENNA TUNER (A.T.U.)

### OPEN TYPE

Mounted on ceramic former and feet. "Roller Coaster" design 16 G silver or silver plated wheel traversing on wire on ceramic former. Will handle considerable R.F. In original packing. As used with No. 63 Transmitter. ONLY £2.50. P. & p. 50p.



## No. 19 SET TRANSMITTER RECEIVER

Rebuilt. Complete station with PSU, Cables, Mic, Aerial, etc. £23.50. Carr. £3.

## No. 19 SET 500uA METERS

Scaled 0-600 and 0-15V. Brand new, boxed £1.25 Post Paid. (Quantity prices on request.)



**R.F. AMPLIFIER.** To increase output of No. 19 Set. ONLY £3.75. Carr. £1.25. Instruction Book for R.F. Amp. 37pp Post Paid.

## ALL No. 19 SPARES IN STOCK

Complete instruction book with circuits for No. 19 Equipment. 37pp Post Paid.

## HEAVY DUTY BATTERIES

New in metal cases with carrying handles.

6v. 85 AH 18" x 9 1/4" x 7" £3.25. Carr. £1.25



## FAMOUS TELE 'F' FIELD TELEPHONES

Suitable for Farms, Building Sites etc. Communication up to 5 miles or more. Rugged construction, will last a lifetime. ONLY £5.75 PAIR. Carr. £1. (Twin telephone wire for above available - ask for price.) Many other Ex-Govt. Surplus Equipment items in stock. Receivers etc. in small quantities too numerous to mention. Enquiries invited. LIST 25p Post Paid. (Refundable against purchases over £3.) C.W.O. Carriage charges apply to Mainland only.



**NEW 3in. SPEAKERS** 16 ohms 75p. p. & p. 10p.

**BARGAIN PARCELS** 14lb at £1.45 plus 24pp p.p.; 28lb at £2.75 plus 52pp p.p.; 56lb at £4.50 plus £1.25 p.p. Contain pots, Res. Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £22s. Lucky Dip Service.

**NEW 6 ft. VHF AERIALS.** Freq. 75-78 Mc/s. 70 ohms. £2.50p. p. & p. 50p.

**VHF Receiver, Type 715,** less crystal 60-100 Mc/s can be operated on 2 or 4 meters or made tunable 12 volt input, not tested: complete with valves and 42pp. £3 plus £1 p.p.

**VHF AERIAL TUNING UNITS** consisting of the following: 1-1/4" 500 micro/ampmeter. 1 small 2-gang 75 PF capacitor. 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs with 25/30 watts R.F. input. Size only 1 1/2" x 4 1/2" x 3" Sealed. Price £1.37 1/2 p.p. 25p

**CRYSTALS AS NEW:** Hc 6u, 5.345; 5.030; 5.005; 4.945; 4.875; 4.840; 4.795; 4.680; 4.660; 4.520; 4.510; 2,300; 2,395 Kc/s. 50p each plus 5p. p.p.

**SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS.** 10% tolerance 1/4 & 1/2 watt. Preferred values in packets of 10. Our price 50p per 100. 50p per 200, £1.35 per 300, 60p at £2.13. Our selection. p.p. 5p per 100 and 25p per extra 100.

**TRIMMER BARGAINS.** These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details: Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice. Trimmers without Xtal - 60p per doz. plus 17 1/2p p.p. Trimmers with Xtal - 75p per doz. plus 17 1/2p p.p. Also 20 PF min. brand new air spaced. 50p per doz. plus 17 1/2p p.p.

**ANY HEIGHT AERIAL TUBULAR SECTIONS** 1/4" dia x 3 ft. long. Brass screw in type, copper coated and painted. New 20p each. p.p. 5p. each. Minimum order 6.

**BRAND NEW HARTLEY OSCILLOSCOPES CT318** in original packing. Band width up to 5 Mc/s. Mains supply. Price £40. p. & p. £1.50p.

**AERIALS NEW CONDITION.** Whip type 4ft 25p, 14ft. 77 1/2p. Used condition 4ft. 20p, 14ft. 62 1/2p. All collapsible type p. and p. 4ft. 10p, rest at 17 1/2p. Bases for above 25p. p.p. 12 1/2p. New matching unit coax connection for above 30p. p.p. 5p.

Huge release of valves for the 62 set TX/BX. In original rubber packing consisting of QV04/7 x 61M, ARP12 etc. 10 valves in all at the bargain price as seen 87pp plus 17 1/2p p.p.

R209. Set of valves 62pp. p.p. 25p.

New Headphone and Mike rubber muff type. Low impedance. 97 1/2p. p. & p. 17 1/2p.

**NEW AERIAL WIRE ON BOARDS 7/82 UNCOVERED.** 75ft, 40p, 90ft, 47 1/2p, 100ft 55p, 150ft, 75p, 180ft, 95p, 250ft, £1.30p. p. & p. 13 1/2p.

Headphones, ex Gov. DLR No. 5 high impedance. New 87pp 17 1/2p p.p. Used condition 82pp 17 1/2p p.p.

## MURHEAD DECADE A.F. SIGNAL GENERATOR.

This precision instrument can be used:

1. To Measure Gain up to 50 db.
2. To Measure Loss up to 45 db.
3. To compare Power levels (A.F.).
4. As an Audio Frequency Generator covering 100 Hz to 41 kHz. With a dial setting accuracy of ±0.5 Hz. Output: -1 M/W into 600 ΩL. Complete with mains power unit. Tested. Good Condition. £12. p. & p. 70p.

Heavy New Coax Cable 750HM will handle at least 1KW 50ft lengths, Plug on end, £1.70 + 30p.p.

Also 1/2" 75 ohm Coax in 50ft coils with BNC plugs good condition. price £1 + 30p. p.p.

2 BNC plugs on short length coax cable large size low loss plugs 30p + 5p. p.p.

Block Type capacitor TCC 8UF + 15% 350 VDC WK4 60°C. 250 VDC WK9 70°C Type 62 CIM Price 40p + 13p p.p. New.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

# STROBE! - STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/240V a.c. operation. **EXPERIMENTERS' ECONOMY KIT** Speed adjustable 1 to 36 flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6.30 plus 25p P. & P.

## NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10.50. P. & P. 50p.

## HY-LIGHT STROBE MK III

This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £12.00 P. & P. 50p. Suitable metal case £3.50 extra.

## AND NOW!

## THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well known Hy-Light strobe.

Incorporating:

- Heavy duty power supply.
- Variable speed from 1-23 flash per sec.
- Fantastic Octal based tube with massive electrodes.
- Reactor control circuit producing an intense white light.

The brilliant light output of the 'SUPER' HY-LIGHT gives fabulous effects with colour filters.

Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus. 75p P. & P. Suitable metal case £5.50 extra.

## 7-inch POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

## LIGHT SENSITIVE SWITCHES

All parts incl. ORP.12, relay, transistor and circuit. 6 or 12v. operation Price £1.25 plus 12p P. & P.

## 120/240 AC MAINS MODEL

Transformer, rectifier, special relay 1 make, 1 break. £2.38. P. & P. 20p inc. circuit.

**INSULATED TERMINALS** in black, red, white, yellow, blue and green. New, 10p each post paid.

## VENNER ELECTRIC

### TIME SWITCH

200/250V Ex. GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.

## 200-250V A.C. NEON INDICATOR

Available in red or amber at 20p each. Or in green at 32p each. Minimum order 3 units. P. & P. 5p.

## ELECTRONIC ORGAN KIT

Easy to build, Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2V batteries. Complete set of parts including speaker etc., together with full instructions and 10 tunes. Price £3.00. P. & P. 22p.

## 50 IN 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

## CRYSTAL RADIO KIT

Complete set of parts, including Crystal Diode, Ferrite Aerial, Drilled Chassis and Personal Ear Piece. No soldering, easy to build, full step by step instructions. £1.75 inc. post.

## 12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3750 RPM complete with external gear train (removable) giving final speed of 125 RPM. Size: 4 1/2" x 2 1/2" dia. Price 95p inc. p

# SERVICE TRADING CO

All Mail Orders, Also Callers, Parking Space. Dept. PW10, 57 BRIDGMAN ROAD, LONDON, W4 5BB. Phone 01-995 1360. Showrooms now open, Mon.-Fri.

Personal Callers only. Open SAT. 9 LITTLE NEWPORT ST. LONDON. WC2H 7JJ 01-437 0576.

## Surplus Electronic Trading

DRIVERS END LANE, CODICOTE, HITCHIN, HERTS, SG4 8TP

Hours of business: 8-5 Mon.-Fri., 8-12 Sat. Telephone: Codicote 242 for appointment




or solder to bridge the 0.025in gap between the copper strips.

8. Connections to the Veroboard panel are made to pins inserted in the appropriate places and soldered to the copper strip. These pins are Vero type TP 11032 or similar.

An insertion tool for this pin is Vero part No. IT 2151.

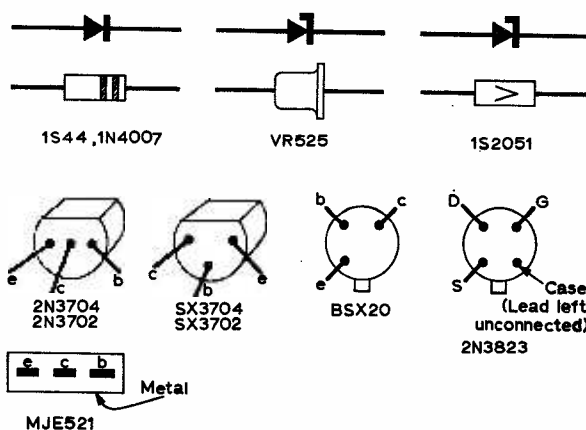9. Tick off each break, link, component and pin on the drawings as they are fitted, this will identify any items which otherwise might be missed.




## Semiconductors

The 3702 and 3704 transistors are specified in the components list as being the '2N' types, these are the most popular version and are readily available.

The 3702 and 3704 transistors are also available

Fig. 14 (left) Cabinet and chassis construction.

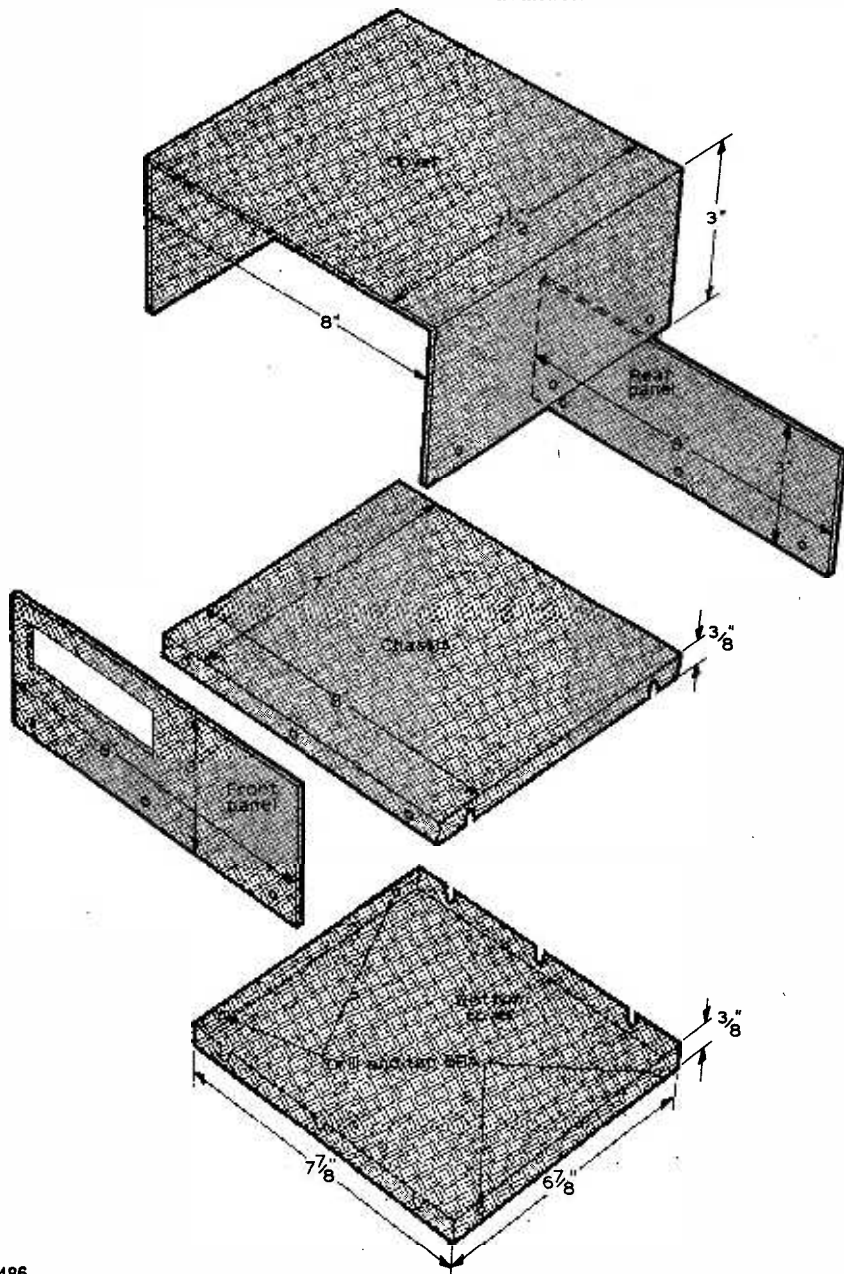

in an 'SX' version. The lead connections for these types are all different from each other and are shown in the diagram above.

It should be noted that on the Veroboard panels, the connections run e.b.c. and when the '2N' version is used, the collector and base leads will have to be crossed over to line up with the appropriate holes in the Veroboard panel.

## Sockets for Integrated Circuits

Sockets are used for all the integrated circuits and although this increases the overall cost and is not essential for the operation of the instrument, it does provide the facility for disconnecting or changing an I.C. should a fault condition exist, also it does allow various parts of the instrument to be tested without incurring the expense of buying all the I.C.'s at once, 16-way sockets are required for I.C.8, 10, 12 and 14 and 14-way sockets for all the others.

The instrument is built using a simple aluminium chassis, panel and cover type of construction, as shown in Fig. 14. The finished chassis size is 8x7x3/8in deep and has a front and rear panel, each size 8x3in, fastened to the front and rear edges with 6BA screws and nuts.

(To be continued)



# ATTRACTIVE DISCOUNTS at all times

# ELECTROVALU Electronic Component Specialists

EVERYTHING BRAND NEW & TO SPEC • LARGE STOCKS • NO SURPLUS

## BARGAINS IN NEW SEMI-CONDUCTORS

MANY AT NEW REDUCED PRICES • ALL POWER TYPES WITH FREE INSULATING SETS

40361	55p	2N2905	44p	2N4291	15p	BC148	9p	BFX87	28p
40362	68p	2N2906A	47p	2N4292	15p	BC149	10p	BFX88	26p
2N696	17p	2N2974	20p	AC107	48p	BC153	19p	BFY50	28p
2N706	18p	2N2926	22p	AC126	20p	BC154	20p	BFY51	28p
2N790	12p	2N2926	11p	AC127	20p	BC157	12p	BFY52	28p
2N1131	29p	2N3053	27p	AC128	20p	BC158	11p	B8X20	16p
2N132	29p	2N3055	60p	AC153K	22p	BC159	12p	C407	17p
2N1302	19p	2N3702	18p	AC176	16p	BC167	11p	MO140	25p
2N1303	19p	2N3703	13p	ACY20	20p	BC168	10p	MP85531	35p
2N1304	28p	2N3704	13p	ACY22	16p	BC169	11p	MP85534	30p
2N1305	28p	2N3705	13p	AD140	63p	BC177	14p	NKT211	25p
2N1306	33p	2N3706	13p	AD142	50p	BC178	13p	NKT212	25p
2N1307	33p	2N3707	13p	AD149	55p	BC179	14p	NKT214	25p
2N1308	36p	2N3708	10p	AD161	33p	BC182L	11p	NKT274	45p
2N1309	36p	2N3709	11p	AD162	39p	BC183L	10p	NKT409	55p
2N1313	28p	2N3710	13p	AF114	24p	BC184L	11p	NKT405	75p
2N1711	36p	2N3711	13p	AF115	24p	BC212L	16p	OC71	38p
2N1893	54p	2N3819	23p	AF117	22p	BC213L	16p	OC81	25p
2N2147	95p	2N3904	35p	AF124	24p	BC214L	16p	OC81D	25p
2N2218	34p	2N3906	35p	AF127	22p	BCY70	18p	ZTX300	14p
2N2218A	44p	2N4058	13p	AF139	33p	BCY79	38p	ZTX301	16p
2N2219	38p	2N4059	10p	AF339	36p	BCY72	15p	ZTX302	22p
2N2219A	53p	11 ASY26	27p	BF115	23p	BF115	23p	ZTX303	22p
2N2270	62p	2N4061	11p	ASY28	27p	BF172	19p	ZTX304	27p
2N2369A	19p	2N4062	12p	BC107	12p	BF173	19p	ZTX500	18p
2N2483	35p	2N4124	18p	BC108	11p	BF194	14p	ZTX501	21p
2N2484	35p	2N4126	27p	BC109	12p	BF195	15p	ZTX502	25p
2N2484A	42p	2N4284	15p	BC125	15p	BFX85	25p	ZTX503	22p
2N2646	47p	2N4286	15p	BC128	22p	BFX86	25p	ZTX504	52p
2N2904A	42p	2N4289	15p	BC147	10p	BFX85	32p		

Appointed distributors for SIEMENS (U.K.) LTD.

Appointed stockists for

NEWMARKET TRANSISTORS RADIOHM POTENTIOMETERS

## SAVE £6.25 ON THE NEW ENGLEFIELD 840 AMPLIFIER

This latest Peak Sound high fidelity amplifier incorporates many strikingly original features including facilities for adding in stereo FM tuner. Superb performance characteristics and luxurious styling. Electrovalue choice of simulated soft leather covering in black, blue, red or dark green. As now advertised at £49.50. Our price **£38.75** nett

## MAINLINE AMPLIFIER KITS

70W. £12.60 nett. (main amplifier module).

## 30 WATT BAILEY AMPLIFIER PARTS

Transistors and PCB for one channel £6.46 Capacitors, resistors (metal oxide), and transistors, one channel. £8.41. Complete unregulated power supply pack, £4.75. Suitable heatsink 10DN 400C. 55p.

## SIEMENS' TTL INTEGRATED

We stock a large range of all types for very wide range of applications. For full details, see our latest catalogue.

## S-DeC RANGE

S-DeC £1.44; DeCSTOR £2.98; S-DeC 4 Pack £5.10; T-DeC £2.88; µDeC 'A' £2.18; µDeC 'B' £5.91. All prices include postage. Prices increased approx. 20% since publication of our 1971 catalogue (pages E1-53). Guide prices unchanged.

## INDICATOR LAMPS

NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C, 24p. Neon, square red type LS5C/P, 18p; amber type LS5C/A, 18p; clear type LS5C/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0.04A square red type LS5C/R-6V, 30p, 6V 0.04A amber type LS5C/A-6V, 30p; 6V 0.04A clear type LS5C/C-6V, 30p; 6V 0.04A green type LS5C/G-6V, 30p; 12V 0.04A LS5C/R-12V, 34p; 34V 0.04A LS5C/R-28V, 45p.

## SIEMENS' POLYCARBONATE CAPACITORS

5% tolerance 250V up to 0.1mF, 100V 0.1mF and above. 0.01, 0.012, 0.015, 0.018, 0.022, 0.027, 5p, 0.033, 0.039, 0.047, 0.056, 0.068, 0.082, 0.1, 0.12, 0.15, 0.18, 0.22, 6p, 0.27, 7p, 0.33, 9p, 0.39, 9p, 0.47, 10p, 0.56, 13p, 0.68, 15p

## DIN CONNECTORS

	plug	socket
Loudspeaker	2-pole	12p
Audio	3-pole	12p
Audio	4-pole	12p
Audio	5-pole 180 deg.	15p
Audio	5-pole 240 deg.	15p
Audio	6-pole	15p

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

ELECTROVALUE 1971 CATALOGUE. 64 pages and covers. Packed with items and information. Post free 10p

## RESISTORS 10% - 5% - 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82Ω-220KΩ	E12	9	8	7
C	1/8W	5%	47Ω-470KΩ	E24	1	0-8	0-7
C	1/4W	10%	47Ω-10MΩ	E12	1	0-8	0-7
C	1/2W	5%	47Ω-10MΩ	E24	1-2	1	0-9
C	1W	10%	47Ω-10MΩ	E12	2	1	0-9
MO	1/2W	2%	10Ω-1MΩ	E24	4	3-5	3
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12	7	7	6
WW	3W	5%	12Ω-10KΩ	E12	7	7	6
WW	7W	5%	12Ω-10KΩ	E12	9	9	8

Codes: C = carbon film high stability low noise MO = metal oxide Electrostrict TR5 ultra low noise WW = wire wound Pleseeey.

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 15, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

## ZENER DIODES

5% full range E24 values; 400mW: 2-7V to 30V 15p each 1W: 6-8V to 82V 27p each 1.5W: 4-7V to 73V 60p each Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

## CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level. Single gang linear 220Ω to 2.2MΩ 12p Single gang log 4.7KΩ to 2.2MΩ 12p Dual gang linear 4.7KΩ to 2.2MΩ 42p Dual gang log 4.7KΩ to 2.2MΩ 42p Log/anti-log 10K, 47K, 1MΩ only 42p Any type with 1/4 D.P. mains switch, extra 12p

Please note: only decades of 10, 22 and 47 are available within ranges quoted.

## CARBON SKELETON PRE-SETS

Small high quality, type P.R. linear only 100Ω, 220Ω 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10MΩ Vertical or horizontal mounting 5p each.

ENAMELLED COPPER WIRE even No. S.W.G. only. 2oz reels 18/22 S.W.G. 25p; 24/30 S.W.G. 30p; 32-34 S.W.G. 33p; 36-40 S.W.G. 35p. 4oz reels 16-22 S.W.G. only 41p.

## MULLARD polyester C280 series

250V 20%; 0.01; 0.022; 0.033; 0.047 3p ea. 0.068; 0.1, 0.15 4p, 0.22 5p, 10%; 0.33 7p, 0.47 8p, 0.68 11p, 1µF 14p, 1.5µF 21p, 2.2µF 24p.

## MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 6p each Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/54; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/18; 10/64; 12.5/25; 16/40; 20/18; 20/64; 25/6.4; 25/25; 32/4; 32/40; 32/64; 40/18; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

## LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 41p; 1000/100 82p; 2000/25 37p; 2000/50 57p; 2000/100 £1.44; 2500/64 77p; 2500/70 98p; 5000/25 62p; 5000/50 £1.10; 5000/100 £2.91; 10000/50 £2.40.

## COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

## POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2. Overseas orders welcome: carriage and insurance charged at cost. Prices subject to alteration without notice. U.S.A. CUSTOMERS: U.S.A. orders charged at prices as advertised by ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.

# ELECTROVALUE

(Dept. PW.1071) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY

Hours: 9-5.30; Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) Telex 264475

**CASH & CARRY GOODS**

Sinclair 2000 £24  
 Sinclair 3000 £33  
 Metrosound ST20 £27  
 Teleton 203 (Demonstration) £17  
 Teleton F2000 Tuner/Amp. £31  
 Teleton SAQ 206 £19.75  
 Alpha F212 £26

**SINCLAIR Project 60**  
 SAVE nearly £7 Normal price £23-90

Designed for building into plinths etc., complete with two Z30 Output stages (20 watt) and power supply unit. Send S.A.E. for full technical brochure.

plus 50p carr. £17

Please add 50p carr. per amplifier. Other Amplifiers — Tuners — Tape Recorders etc. Prices on application.

**This MONTH'S Best Buy . . .**

**AKG K50 Dynamic Stereo headphones**  
 Complete with spare ear muffs.

Total (value £10.40) Our Price **£5.90** p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last.

\* High-fidelity reproduction due to broad frequency response (20-20,000Hz)  
 \* Substantially increased stereo effect \* Headphones fit the head gently and do not shift \* Earpieces fit ears snugly (Cardanic suspension) \* Tone quality superior to conventional loudspeakers. \* Only expensive studio loudspeakers can match the reproduction quality of the K50. \* Music can be reproduced at concert hall volume (!), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.

**GARRARD SP25 mk III £12.50** Plus 50p carriage

Normal price £15.50

Wired with mains cable and 5ft. twin screened stereo cable, 5 pin din plug, 53p extra.  
 AP75 Complete with base and cover £25 plus 75p carriage.

**PLINTH AND COVER SUITABLE FOR GARRARD RANGE** £5.25 plus 50p p. & p.

**PLUGS**

Pack 107 5-Pin Din . . . . . 20p  
 Pack 108 3-Pin Din . . . . . 18p  
 Pack 109 1/2" Jack . . . . . 25p  
 Pack 130 1/2" Jack Stereo . . . . . 45p  
 Pack 103 Loudspeaker Plug . . . . . 15p  
 Pack 100 Phono Plug . . . . . 6p  
 Pack 230 3-Pin Socket . . . . . 23p  
 Pack 235 5-Pin Socket . . . . . 30p  
 Pack 234 Loudspeaker Socket . . . . . 30p

Ready-made Leads

3-pin to 3-pin Din . . . . . 63p  
 3-pin to open end . . . . . 53p  
 5-pin to 5-pin Din . . . . . 80p  
 5-pin to open end . . . . . 65p  
 5-pin to 4 phono plugs . . . . . 93p  
 5 speaker lead Din to spade 12ft 38p  
 Extension lead Din plug to socket 12ft 85p

All leads approx. 6ft. in length. Post free, by return.

**Replacement Stereo DIAMOND STYLII**

9TA 9TA 9TAHC  
 G91 S74 ST9  
 EV28 GC9 **75p** each  
 others on request +13p p. & p.

**Countdown SPEAKER**  
 Teak Cabinet

**£12** insurance & carr. 38p

A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.

**EMI 20w matched loudspeaker set 350**  
 Frequency range: 20 to 20,000Hz. **£7.50**  
 Normal price £13 plus 40p p & p

**EMI 10w matched loudspeaker set 450**  
 Our price **£3.75** plus 25p p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency unit with associated crossover network. Frequency range 55 to 13000Hz. The cone of the bass unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies. Also 150 KIT 10W **£2.50** plus 3, 8 or 15 ohms 40p p & p

**Magnetic cartridges**

**Diamond £4.75**  
 stylus plus 13p p. & p.

Today's value £6.  
 Stylus replacement can be carried out without removing cartridge. Fully guaranteed.

**Ronette 105 Stereo cartridge** (Sapphire 78 Diamond LP) **£1.25** + 13p. p. & p.

**SONOTONE Cartridge . . .**  
 (Fitted Diamond Stylus)  
 (Ceramic) list price **£4.10**

Sensitivity: 55mV/cm/sec  
 91AH minimum at 45° plus 1,000Hz measured on Decca SX12057 **£2.50** p. & p.

**J. J. FRANCIS (WOOD GREEN) LTD**  
 123 ALEXANDRA ROAD, HORNSEY, LONDON, N.8. Tel: 01-888 1662

**YOUR OWN PROFESSIONAL SOLID STATE CLOSED CIRCUIT TELEVISION CAMERA**

**ONLY £70 INCLUDING LENS & VIDICON TUBE**

**INCLUDING LENS & VIDICON TUBE**  
 Designed by the Mullard Educational Service, and shown on the BBC's 'Tomorrow's World' programme, the Linstead camera provides a composite output comprising sync. pulse and picture information.

**Free 78-page manual**  
 We give you a superb, fully illustrated 78-page construction and service manual with this kit. Apart from full assembly instructions, a complete description of basic camera principles, vidicon tube operation and circuit diagram, this manual shows all waveforms within the circuitry. We also supply a copy of the BBC Test Card F.

The basic kit, excluding lens and tube costs only **£45**

**A COMPLETE FULLY CONSTRUCTED AND TESTED CAMERA COST ONLY £99.85**

Components are also available separately (for instance mains transformer £2.50 each)

For full details, send S.A.E. today.

**RoslynWorks, Roslyn Rd. LONDON, N.15**  
 Telephone: 01-802 5144

**INTER-LOCKING PLASTIC STORAGE DRAWERS**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top.

**DISCOUNT PRICES**

**SINGLE UNITS** (5" x 2 1/2" x 2 1/2") **£1.35** Dozen  
**DOUBLE UNITS** £2.25 Dozen  
**TREBLE (3D)** £2.35 for 9  
**DOUBLE TREBLE 2** draws in one outer case (6D2) **£3.65** for 8 extra large size (6D1) **£3.30** for 8.

**PLUS QUANTITY DISCOUNTS!** Order £5 and over Deduct 5% in the £. Order £10 and over Deduct 7 1/2% in the £. Order £20 and over Deduct 10% in the £. Pack./Post./Carr.: Add 35p to all orders under £5. Orders over £5 P/P/C free. (Dept PW10) 124 CRICKLEWOOD BROADWAY, LONDON N.W.2

**NEW VALVES!** Guaranteed and Tested 24-HOUR SERVICE

1R5	26	30L17	68	EABC80	30	EF91	12	PCF80	28	PY801	33
1B5	21	30P4	60	EB91	10	EF183	28	PCF86	44	R19	30
1Z4	14	30P19	60	EBC83	38	EF184	29	PCF801	30	U25	64
3Z4	20	30PL1	60	EBF59	29	EL33	54	PCF802	43	U26	58
3V4	37	30PL13	60	ECC81	18	EL37	75	PCF805	62	UL91	59
5Y3GT	27	30PL14	65	ECC82	19	EL84	22	PCL82	32	U291	95
6A0L2	56	DAF91	21	ECC83	22	EY51	34	PCL84	34	U329	65
6AQ5	24	DAF96	35	ECC85	25	EY86	30	PLC85	40	UBF89	31
6BW7	55	DC90	80	ECC80	27	EZ80	21	PLC86	38	UCC85	34
6E1	60	DF91	14	ECC82	26	EZ81	22	PFL200	52	UCH81	30
6F28	89	DF96	35	ECC85	27	EL37	34	PL81	45	UCL82	56
6P25	55	DK91	28	ECH81	27	KT66	80	PL81	45	UCL83	48
6N7GT	28	DK92	40	ECL80	31	N78	85	PL82	30	UFB89	29
25L6GT	20	DK96	36	ECL82	30	PC86	47	PL83	32	UL84	31
30C15	60	DL92	26	ECL86	36	PC88	47	PL84	30	UY85	26
30C18	62	DL94	37	EF99	36	PC97	38	PL500	62	Z77	18
30E7	97	DL96	36	EF80	23	PC900	32	PL504	63		
30FL1	60	DY86	24	EF85	23	PC984	30	PY81	24		
30FL14	69	DY87	24	EF86	30	PC989	45	PY82	22		
30L15	58	DY802	38	EF89	24	PCC189	48	PY800	33		

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra. Office address, no callers.

**GERALD BERNARD**  
 83, OSBALDESTON RD., STOKE NEWINGTON, LONDON, N.16

# TESTING

R A BUTTERWORTH



# surplus transistors


THE technical press offer so many transistor projects that many of us have bought and acquired a fair stock of transistors gathered from bargain packs or labouriously removed them from surplus computer boards. We then go through them only to find that many are un-marked, indecipherable, or have some queer markings not contained in any lists. The manufacturers are reluctant to supply data because they have been made to "customer requirements". A few hours spent in sorting these into NPN or PNP and grading them into four categories will save a lot of time, patience and money on the next project development. The methods of grading are only approximate and there are only four grades:—

1. RF types.
2. Low gain types.
3. High gain types.
4. All others which do not pass the tests described.

## PRELIMINARY TESTING

First do a thorough visual examination and sort the transistors into *known* and *unknown*. The *knowns*, however, should be put through the tests since they may be blown or below spec. If your collection contains transistors removed from computer boards, the leads will be short. Fortunately when these boards are assembled, small plastic

Fig. 1: Some transistor lead connections. These are only the most common arrangements and variations do exist.

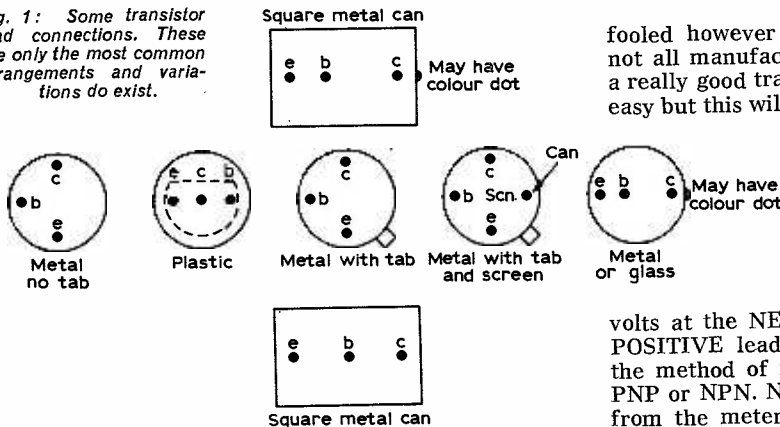

spacers are fitted, in most cases to comply with manufacturer's recommendations as to bending and heat dissipation. The makers also usually bend over about  $\frac{1}{8}$  in on the solder side with the result that the lead lengths are in a safe condition. Any that are too short should be thrown away. Figure 1 shows the bases of seven categories into which these recovered units fall. Some may have a coloured dot, usually red or white, indicating the collector lead, also some are internally connected collector-to-can. Do not be

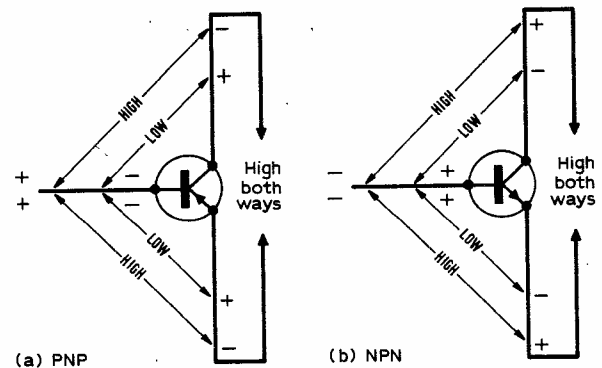


Fig. 2: Resistance readings found on a good transistor—see text for details.

fooled however by coloured sleeving on the leads; not all manufacturers use the same code. Of course a really good transistor checker can make things very easy but this will cost a good deal of money.

## IDENTIFYING THE LEADS

The first checks, sorting the PNP and NPN types and the leads are done with a multimeter on its low ohms range. A word of warning first about that multimeter. Most meters on the ohms range give positive volts at the NEGATIVE LEAD and negative at the POSITIVE lead, so check first. Figure 2 illustrates the method of finding out whether the transistor is PNP or NPN. Never be scared of reversing the leads from the meter; with about 1.5V, which is usually

available from the meter on low ohms ranges, you won't do any harm. Should you get a low resistance reading both ways between base and either of the other connections you can be fairly certain that there is an internal short. If you get a low reading between the base and one lead and a high at the other it is either bad or you are not on the base. It is probable that you will meet with marginal readings at times, so make tests as follows with reference to Fig. 3.

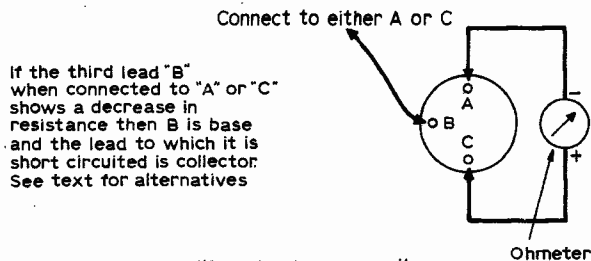


Fig. 3: Tests for identifying the base connections.

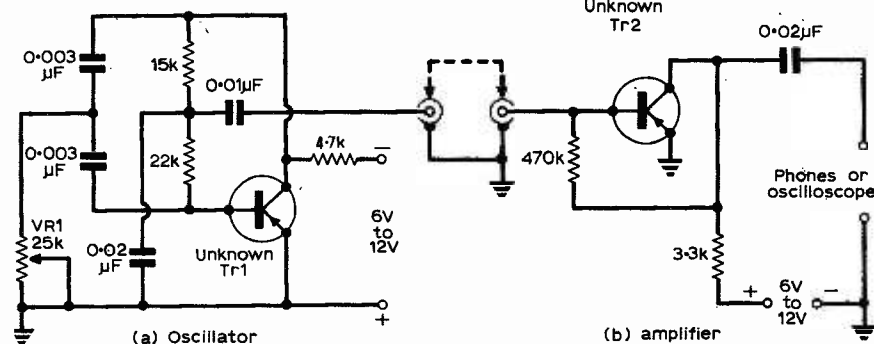


Fig. 4: The circuit used for the gain and amplification tests. Note that for NPN devices the battery polarity must be reversed.

Draw a base diagram of the base of the transistor and mark them 'A', 'B', 'C'; you are now faced with three permutations, of pairs 'AB', 'AC' 'BC'. Now take any pair and connect to the ohmmeter on low ohms range, then connect the other lead to each lead in turn: if the resistance falls the unpaired lead is the base lead and the lead to which the base was shorted is the collector. Check to see if this lead is connected to the metal can, this could confirm that it is the collector. If you do not get these results then check each of the three pairs using the same procedure. If the base cannot be identified for certain and there is high resistance both ways it is most probable that the third lead is base. To check, assume this is base and check with the meter whether it is a PNP or NPN in Fig. 1. You should then have established the base connection; the emitter and collector connections will be identified by reversing the leads in the grading test.

#### TESTING FOR GAIN

To test for gain two simple circuits are required as shown in Fig. 4. Good quality transistor sockets are essential since we are most likely dealing with short leaved transistors and soldering in and out will become tedious. The assembly of the the circuits is an individual choice, though the author used 'S-Dec' and found it ideal. When the test rig is assembled, put in two good known transistors, say an OC44 or OC45 for Tr1 and an OC70 or OC72 for Tr2, connect up the battery and headphones. If you can use a

'scope, all the better. Now adjust VR1 until a tone (or trace) is observed, then start to substitute the unknowns for Tr1. If a tone is present the gain will be more than 30, if no oscillation occurs then it is less than 30. At this point those transistors which have connections which are difficult to identify can be checked and identified by insertion, keeping the assumed base connection and reversing the other two unknown leads in the socket. If no oscillation occurs, keep it for the two further tests. Do not be afraid to reverse leads even at this higher voltage; if it blows then it was probably useless anyway.

#### AMPLIFICATION TEST

Now replace the original test transistor i.e. the OC44/45 (or one of the good ones known to oscillate) and then one by one test all those which failed the high gain test by substitution in the Tr2 position. The note heard in the headphones will tell you if it will amplify at all. If it is possible to use an oscilloscope, a little more information will be gained on this last test which is for low gain. By means of the trace shown on the 'scope, you can classify some transistors in the large signal class because the waveform will be distorted or clipped. The assumption in the tests up to now has been that the surplus transistors are in the small signal group.

#### R.F. TESTS

All the transistors available should be put through the r.f. test, irrespective of whether they have passed the previous tests. The r.f. test circuit is shown in Fig. 5. Here the reader will have to arrange for the crystal, Tr1, L1 and C1, according to what he has available, to check frequency. As a guide, with a 20MHz overtone crystal, an OC170, L1 being eight turns of 18s.w.g. on a 1/2in former, tuned with a 50pF capacitor. the circuit will cover the range up to

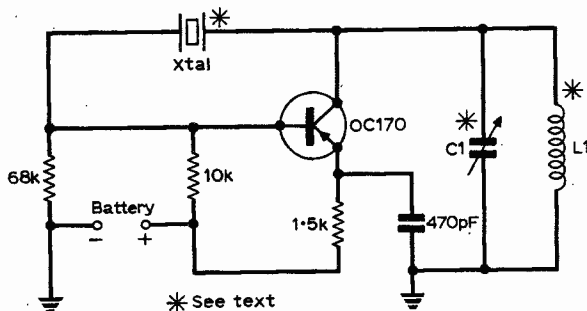


Fig. 5: The r.f. test circuit. For NPN devices the battery polarity must be reversed.

30MHz. Here a receiver or G.D.O. is necessary to detect the oscillation. Once oscillation is established it is merely a matter of substituting as before.

With your collection graded, as outlined, it is simply a matter of substitution of various types within that grade for optimum results in a particular project. The methods described are by no means comprehensive but at least you will have got a little order out of chaos and the building of many projects will be made much easier.

**HEARING AID AMPLIFIERS**  
(Ex behind ear deaf aids) 3 transistors on tiny P.C. board with volume control—whole thing only about half as big as Oxio cube. \$1.75 or with sub-miniature microphone and I.S. attached \$2-50.



**MAINS OPERATED SOLENOIDS**

Model 772—small but powerful 1" pull—approx size 1 1/4" x 1 1/2" 60p.  
Model 400/1 1/2" pull. Size 2 1/4" x 3" x 1 1/2" 75p.  
Model TT10 1 1/2" pull Size 2 1/4" x 2 1/4"—\$1.80 plus 20p post and insurance.

**BEST QUALITY BRITISH MADE ELECTRICAL PLUGS AT APPROX. HALF PRICE**

15 amp 3 pin 10p each or ten for 90p, 5 amp 3 pin 8p each or ten for 70p, 5 amp 2 pin 5p each or ten for 45p.

**DRILL CONTROLLER NEW IKW MODEL**

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. \$1.50 plus 18p post and insurance. Made up model also available, \$2.25 plus 18p post and insurance.

**CONTROL DRILL SPEEDS**



**PRECISION MADE — as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.**

**NEED A SPECIAL SWITCH?**

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 60p doz. Plastic push rod suitable for operating, 5p each, 45p doz.


**MINIATURE WAFER SWITCHES**

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 18p each, \$1.80 dozen, your assortment.

**SEE LAST MONTH for prices of STANDARD WAFER SWITCHES**

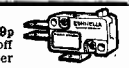**MICRO SWITCH**

5 amp, changeover contacts, 8p each, \$1 doz. 15 amp, on/off 10p each, 15 amp changeover 15p each, 10 for \$1.35.



**MAINS OPERATED CONTACTOR**

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2" x 2" x 2in. \$1 each.

**PAPST MOTORS**

Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. \$1.50 each. Postage one 23p, two 35p.



**EXTRACTOR FAN**

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets, \$2 plus 36p post and ins.

**MAINS TRANSISTOR POWER PACK**


Designed to operate transistor sets and amplifiers. Adjustable output 8v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: P1, P3, P4, P6, P7, P9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 89p, plus 18p postage.

**COMPONENT BARGAINS**

100 Ercle 1 watt resistors, 50 different values up to 1 meg. 50p.  
50 assorted capacitors, 25 different values up to 5,000 p.f. 60p.  
Both parcels \$1 post paid.

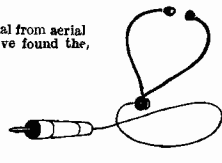**RADIO STETHOSCOPE**

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. \$2—twin stethoscope instead of earpiece 75p extra—post and ins. 20p.



**BATTERY CONDITION TESTER**

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—lead—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 2 1/2" x 2" with leads and prods. Price \$1.75 plus 20p postage.


**1 HOUR MINUTE TIMER**

Made by famous Smiths company, these have a large clear dial, size 4 1/2 x 3 1/2, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch \$1.15.



**THIS MONTH'S SNIP**

**CENTRIFUGAL FAN**

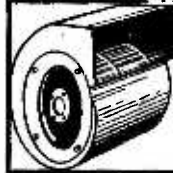

Mains operated, turbo-blower type. Pressed steel Housing contains motor and aluminium impeller. Motor is 1/10th hp giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2" wide by 12" dia. Outlet into trunking 10 1/2" x 4 1/2". \$2.95 + \$1.

**MICROSONIC KEYCHAIN RADIO**

7 transistor Keychain Radio in very pretty case, size 2 1/2 x 2 1/4 x 1 1/2—complete with soft leather zipped bag, 7 transistor, ferrite rod. Loudspeaker. In transit from the East these sets suffered corrosion as the batteries were left in them but when this corrosion is cleared away they should work—offered without guarantee except that they are new. Price only \$1.25 less batteries plus 18p. post 6 for \$7 post free. Pair of rechargeable batteries and charger \$5p.



**24-HOUR TIME SWITCH**

Made by Smiths, these are AC mains operated, NOT GLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours. 5 amp changeover contacts will switch circuit on or off during these periods. \$2.50 post and ins. 23p. Additional time contacts \$0p pair

**DIGITAL FREQUENCY COUNTER TIMER**

as described in this and last months issues. Kit of parts including case \$39.50 post paid.

**THE FULL-FI STEREO SIX**

The amplifier sensation of the year You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled in simulated teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners. It has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. UNREPEATABLE PRICE is \$29 plus 33p post and insurance.




**DISTRIBUTION PANELS**

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, \$2 less plus \$2.25 with fitted 13 amp plug; \$2.40 with fitted 15 amp plug, plus 23p P. & I.



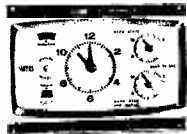**ELECTRIC CLOCK WITH 20 AMP SWITCH**

Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another time or alarm—this may be set in minutes up to 1 hour. At the end of the period a bell will sound. Offered at only a fraction of the regular price—\$2.50, less than the value of the clock alone—post and ins. 15p.



**CAPACITOR DISCHARGE CAR IGNITION**

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for improved and even more efficient version (P.W. June), price \$4-95. When ordering please state whether for positive or negative systems. Plus 30p post.

**FLUORESCENT CONTROL KITS**

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—16-20 w. \$1 Kit B—30-40 w. \$1 Kit C—50-80 w. \$1.80. Kit E—60 w. \$1.20. Kit F for 8ft. 125 w. tube \$1.75. Kit MF1 is for 6in., 9in. and 12in. miniature tubes \$1. Kit MF2 for 21in. 13 w. miniature tube \$1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and B 23p on first kit then 18p for each kit ordered. Kit F 33p then 23p for each kit ordered. Kit MF1 15p on first kit then 15p on each two kits ordered.

**THYRISTOR LIGHT DIMMER**

For any lamp up to 300 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price \$1-99 Plus 20p post and insurance.



**TREASURE TRACER**

Complete Kit (except wooden battery) to make the metal detector as described editorially in Practical Wireless August issue. \$2-50 plus 20p post and insurance.



**TELESCOPIC AERIAL**

For portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2" to 47in. Hole in bottom for 8BA screw. \$8p. KNUCKLED MODEL FOR P.M.S. 50p.


**QUICK CUPPA**

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Uses any socket or lamp holder. Have at bedside for tea, baby's food, etc. \$2.25, post and insurance 14p. 13v. car motor model also available same price. Jug heater \$1.50 plus p. & p. 14p.



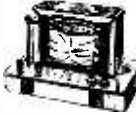**SLAVE FLASH UNIT**

As described in last months P.W. Kit with case \$1.10 plus p. & p. 20p.



**12 VOLT 1 1/2 AMP POWER PACK**

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd/50 smoothing. Price \$1.50 plus p. & p. 20p.

**REED SWITCHES**

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types: Miniature. 1in. long x approximately 1/4in. diameter. Will make and break up to 1A up to 300 volts. Price 15p each. \$1.20 dozen. Standard. 2in long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 10p each, 80p per dozen. Flat. Flat type, 2in. long, just over 1/16in. thick, approximately 1/2in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 30p each. \$3 per dozen. Small ceramic magnets to operate these reed switches 5p each. 80p per dozen.

**METER BOX**

Designed to take 3 1/2" flush mounting meter. This has a 2 1/2" diameter hole with 3 meter fixing holes. Overall size of box 4" x 4" x 2 1/2" deep, hinged to a metal base 2 1/2" x 4 1/2" x 1/2" deep. Price 50p.

**PILOT BULBS**

6-9 Volts 15 amp tubular MES British made good quality. 1 dozen in a box. 25p per box. A New Service to Readers. A bulletin bringing news of new lines, special snips and "too few to advertise" lines will be posted to subscribers during first week of each month. The bulletin will be called "Advance Advert News" and the Subscription is 60p per year. Subscribers will also receive our completed 1971 catalogue when this is published.

Where postage is not stated then orders over 45 are post free. Below 45 add 20p.

Semi-conductors add 5p post. Over 21 post free. S.A.E. with enquiries please.

**J. BULL (ELECTRICAL) LTD.**  
Dept. P.W. 7, Park Street, Croydon CRO 1YD



# GENERAL PURPOSE

# power supply

M. WALLIS

**I**N the "good old days" of valves, power supplies were simple. Some 90 per cent of equipment operated with an h.t. supply of about 300V and the heaters were nearly all 6.3V. A single power supply would operate the vast majority of equipment that one was experimenting with. Today the semiconductor rules the day and power supplies are very much less standardised. Checking through a recent copy of *Practical Wireless* showed that there were six circuits given—and five different supply voltages were specified, ranging from 6V to 30V. Batteries can cope with a number of these, especially the most common 9V supply, but even the most half-hearted experimenter needs quite a range of batteries to pursue his hobby—even for quick lash-ups.

One can of course build a sophisticated, stabilised power supply with variable output covering quite a large range but such circuits are expensive, are by no means simple in their construction and most of the time the sophistication is not required.

By incorporating a simple two-pole, six-way rotary switch into the circuit of a standard power supply, it is possible to build a power unit with six different outputs—all with low internal impedance—and which will simulate exactly the supply that you finally build into the equipment.

A few refinements can be incorporated into such a power supply such as an indicator neon and fuse protected output which are not always necessary on the final supply which is fitted permanently but which make life simpler (and cheaper!) while experimenting.

## the circuit

The wide proliferation of supply voltages needed for semiconductor designs has brought about the introduction of mains transformers with a wide range of secondary windings and it is simply by selecting the appropriate ones of these that various output voltages can be obtained.

The transformer specified in the components list is a good one to use but other types with multiple secondaries can be adopted.

This one is fitted with 12, 15, 20, 24 and 30V windings (these of course refer to a.c. r.m.s. volts)

TABLE 1

VOLTS (d.c.)	VOLTS (a.c.)	Connections from which derived
4.5	3	12-15
6	4	20-24
7.5	5	15-20
9	6	24-30
12	8	12-20
13.5	9	15-24
15	10	20-30
18	12	0-12 or 12-24
22.5	15	0-15 or 15-30
27	18	12-30
30	20	0-20
37.5	24	0-24
45	30	0-30

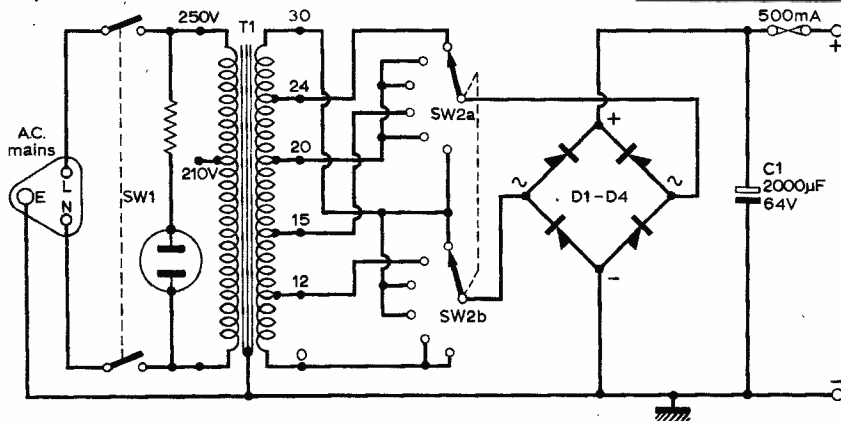


Fig. 1: The circuit of the general purpose power supply.

and a total of 13 different voltages can be selected from this as shown in the table. Those shown in the drawings, and for which the wiring is done, tend to be the higher voltages as batteries are still the best bet up to about 9V but it is a matter of personal choice which are selected.

Note that the d.c. voltages are those which should be read with no loading and are only approximate. In any case it has been found by

## ★ components list

T1	Mains transformer, 250V primary, 500V multiple secondary, or 250V/500V Douglas Type MT12AT or similar.
D1-D4	Silicon Bridge Rectifier, BY164 or similar.
C1	2000µF 64V
SW1	Double pole on-off switch.
SW2	2-pole, 6-way rotary switch.
	Panel neon with built-in resistor.
	Robert Electronics Fuse.
	Plastic encapsulated terminals.
	Tap wire for switch.
	Capacitor clamp.
	Aluminium chassis, 6" x 4" x 1/2", K. L. Smith, Ltd., 287 Edgware Rd., London W2.

experience that the secondary taps are by no means always accurate and quite large differences have been measured from the theoretical voltage but as exact voltages are rarely needed, variations are allowable.

The output voltage from the prototype, which can be seen marked on the chassis, are those measured, not those calculated, and these discrepancies can only be due to winding inaccuracies as it is wired up exactly as in Fig. 1.

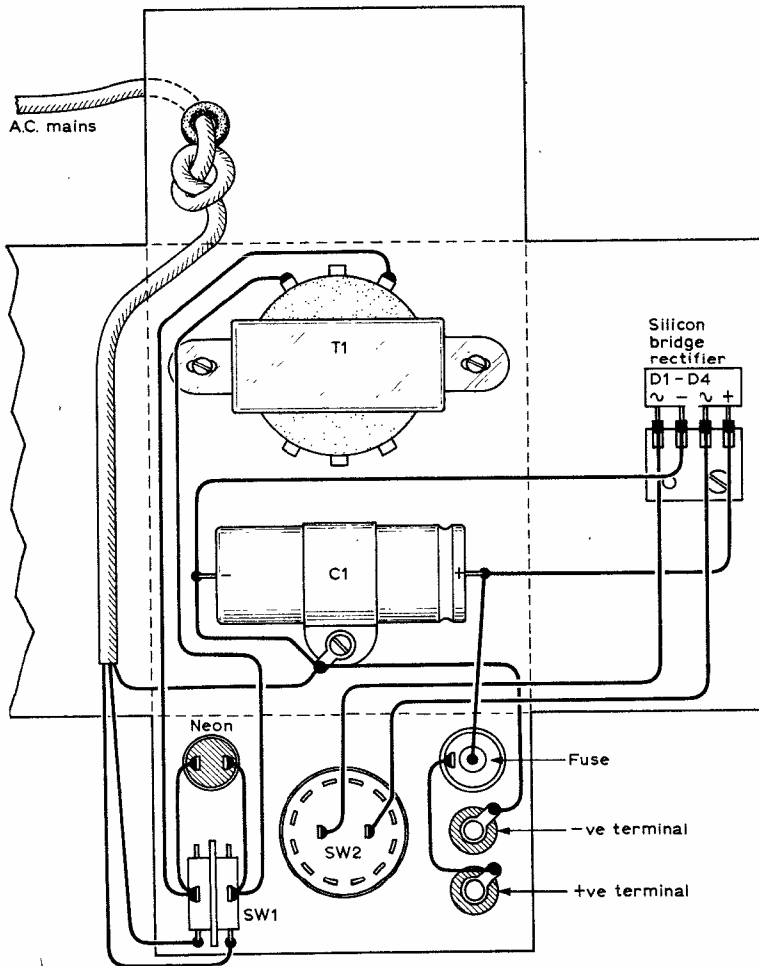


Fig. 2: The component layout and wiring details.

The current rating required from a general purpose power supply will depend on the uses to which it is put. Only power amplifiers at peaks take more than about 500mA and that was the rating chosen; it is sufficient for nearly all experimental work.

More than one company makes transformers with the voltage taps used here, but the most widely available is possibly the Douglas MT12AT. The same transformer with a 2A rating is coded MT3AT and although it will just fit into the chassis shown, it is a tight fit and a larger one is recommended.

The mains supply is connected to the correct primary (either 210V or 250V) of the transformer via a double-pole switch. A panel neon, connected

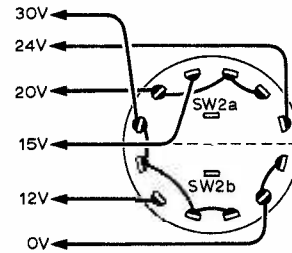


Fig. 3: The switch wiring used on the prototype.

across the primary is very useful. Today most neons are supplied with a built-in resistor but if one is not fitted, a 220kΩ should be wired in series as shown in the circuit.

The earth line is shown connected to the negative line but may equally well go the positive if used in conjunction with PNP type equipment which is earthed by some other means. Whatever happens the aluminium chassis should be earthed for safety reasons.

The various connections to the voltage selector switch are taken from the appropriate tapings and the switch wipers are connected directly to the bridge rectifier a.c. contacts. Plastic encapsulated silicon bridge rectifiers are widely available at reasonable prices and come under a variety of codings. The ratings must be 50V peak, 1A. The Mullard BY164 is suitable here.

Adequate smoothing for all purposes is provided by the 2000µF capacitor; the voltage rating of this should be well above the 45V or so applied and a 64V type was used in the prototype.

To provide a measure of protection, a 500mA fuse should be connected in the supply as shown.

## construction

The prototype was built in a

small aluminium chassis size  $5 \times 4 \times 2\frac{1}{2}$  inches, fitted with a drop-in lid. These chassis are available from H. L. Smith Ltd., the address is given in the components list.

The layout of the components is shown in Fig. 2 and can be seen in the photograph.

The bridge rectifier can be mounted on a small lag strip on one long side. the transformer and the


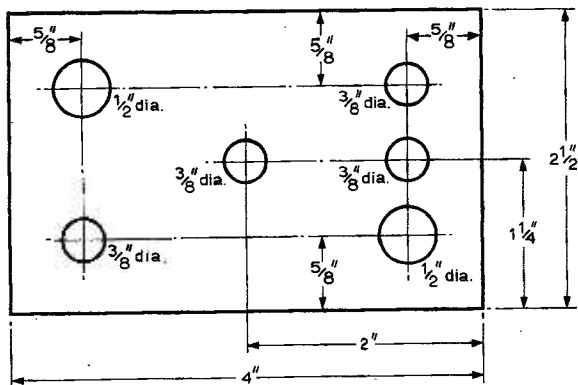


Fig. 4: The front panel drilling details.

capacitor on the base, with the remaining components on the front panel.

The switch wiring needs quite a lot of planning unless that used in the prototype is copied exactly, this is shown in Fig. 3. If other voltages, selected from the table, are required, the wiring should be planned carefully first of all. It is far easier to do the wiring on the switch leaving a few inches of wire which will finally be wired to the transformer.

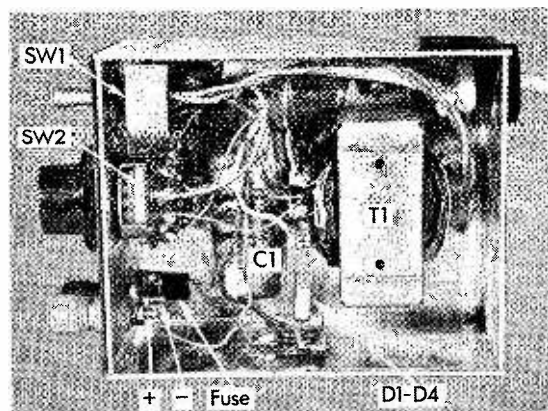When all wiring is completed a thorough check should be made to see that there is no possibility of



Internal view of the prototype showing component siting. Compare this with Fig. 2.

mains being applied to the case and that no bare wires can touch each other.

Connect a voltmeter to the terminal sockets and switch on, ensuring that a voltage reading is obtained in each switch position. Wrong wiring on a switch of this sort can lead to a direct short of the secondary and—unless noted very quickly—unpleasant things can happen to both the transformer and the switch.

There may be a very small amount of sparking while switching but this does no harm. The prototype has been in use continuously for several months with no ill effects.

There is just one point that must be made. The charge stored in a smoothing capacitor of this size lasts for a long while and if the power supply has been on a high range the capacitor should be shorted out (with the mains switch off) before being applied to a circuit where a high voltage could cause damage. This should be done through a resistor, not directly, as the fuse may blow otherwise.

If, due to the nature of the experimenting, a considerable amount of switching is envisaged, a resistor can be wired permanently between the output terminals so that a small current is drawn at all times and the capacitor will then settle down very quickly to the applied voltage. A  $4.7k\Omega$  resistor with a  $\frac{1}{2}W$  rating will serve this purpose.

## CROSSWORD No.2 WINNERS and SOLUTION

The Practical Wireless Crossword Competition No. 2, published in the June 1971 issue, has now closed and the prizes of £10 vouchers, exchangeable with any advertiser in Practical Wireless have been awarded to:

Mr. J. Rutter  
Newcastle-upon-Tyne


Mr. D. Bell  
Silvertown, London E.16

Mr. R. W. Clarke  
Bedfont, Middx.

Mr. W. Easton  
Whitby, Yorks

Mr. M. R. Edmunds  
Southampton, Hants

## SOLUTION TO COMPETITION NO. 2

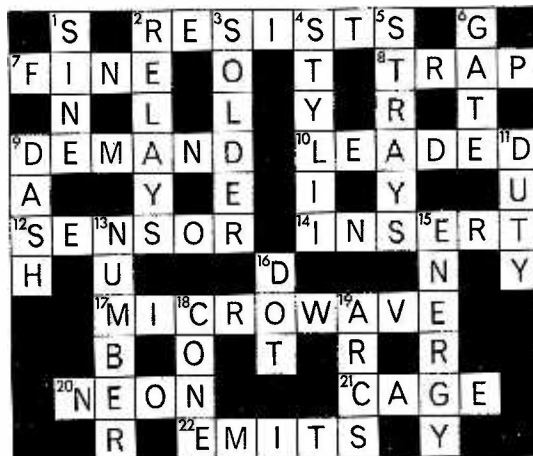



# INCREASE YOUR KNOWLEDGE



Established 1891



**MANY COURSES TO CHOOSE FROM incl.**  
 RADIO & TV ENGINEERING & SERVICING,  
 TRANSISTOR & PRINTED CIRCUIT SERVICING,  
 COLOUR TV SERVICING, ELECTRONICS,  
 NUMERICAL CONTROL ELECTRONICS,  
 TELEMTRY TECHNIQUES, CONTROL SYSTEMS,  
 ELECTRONICS FOR AUTOMATION,  
 COMPUTERS, ETC.

**ALSO EXAMINATION COURSES FOR**

C. & G. Telecommunication Technicians' Certificates  
 Radio Operator Certificates  
 Radio Amateurs' Examination  
 General Certificate of Education, etc.

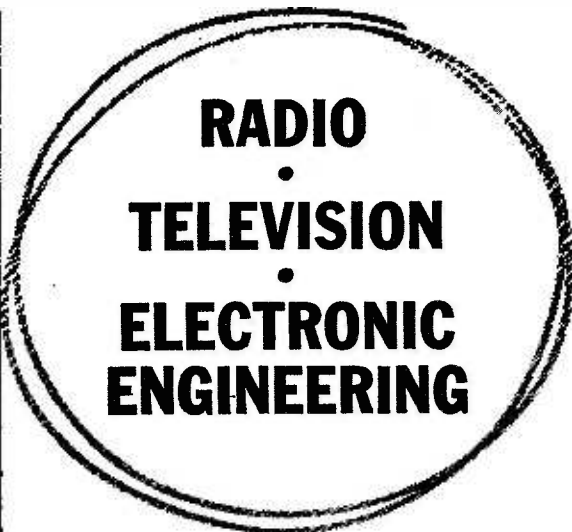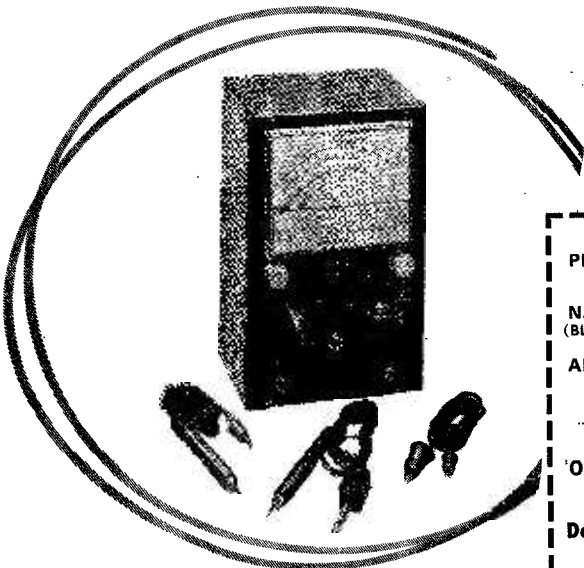**BUILD YOUR OWN RADIO AND INSTRUMENTS**

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



**RADIO  
TELEVISION  
ELECTRONIC  
ENGINEERING**

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

## THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid-men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

**FILL IN AND POST THIS COUPON TODAY**

*You will receive the FREE ICS Prospectus listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.*

PLEASE SEND FREE BOOK ON.....

NAME .....  
 (BLOCK CAPITALS PLEASE)

ADDRESS .....

.....

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS  
 Dept. 170, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8 4UJ.  
 10/71

# AT HOME SOLDERING ?

Our miniature irons are used all over the world in that most exacting market—the modern electronics industry, the rapidly developing technology of which has made possible the enormous growth of activities available to the technical hobbyist.

He now also requires equipment to the highest commercial standards. Like our soldering irons, for example.

Look at the ADAMIN Model 15. If there is a smaller iron for mains use, we haven't seen it. It weighs a mere  $\frac{1}{2}$  oz (less flex) and is about 7 inches long.

But it has a big performance. Used with interchangeable bits from  $\frac{3}{32}$ " to  $\frac{3}{16}$ " it is suitable for all work, from Hearing Aids to Colour Television.

Use the mains version at home or clip the 12 volt model to the car battery or 12 volt power unit (consumption only 1.25A).

Send for HOBBY PACK 10 consisting of Model 15 iron with four bits,  $\frac{3}{32}$ ",  $\frac{3}{16}$ ",  $\frac{3}{8}$ " and tube of Bit Lubricant. State voltage required—12v or 220/240v.

**PRICE: HOBBY PACK £2.30**  
p & p FREE

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL  
Telephone 01-688 8589 and 4559



## JERMYN 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk-buyer's prices! Cash with order only.

### THIS MONTH:

<b>1N4148</b>	Signal Diode (= 1N914)	18 for 50p
<b>1N5060</b>	1 Amp Rectifier 400V avalanche protected (= A14D)	7 for 50p
<b>2N2926</b>	NPN Silicon Transistor (Red) hfe 55-110	8 for 50p
<b>2N2923</b>	NPN Silicon Transistor hfe 90-180	7 for 50p
<b>2N2646</b>	Versatile Unijunction	3 for 100p

Post and packing 10p for 1 or 2 packs;  
3 packs or more post free.

Order any quantity, till sold (but we regret packs cannot be subdivided).



P.O. or Cheque payable Jermyn Industries,  
Vestry Estate, Sevenoaks, Kent.

## BAKER 12in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.

Maximum Power 15 watts  
Bass Resonance 45 c.p.s.  
Flux Density 12,000 gauss  
Voice Coil impedance  
3 or 8 or 15 ohm models


Useful response 45-13,000 c.p.s.

Nett weight 5 lbs.

GUITAR MODEL "GROUP 25" 25 watt rating

Latest catalogue 5p with enclosure plans.

£7

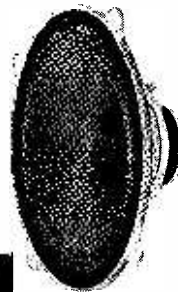

Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

When in LUTON, BEDS, you must visit the . . .

### SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.

Closed all day Wednesday.

**SURPLECTRONICS**

216 LEAGRAVE ROAD, LUTON, BEDS



PRACTICAL WIRELESS  
SUPPLEMENT  
OCTOBER 1971



Choosing

## SMALL WORKSHOP TOOLS S. YEATMAN

**S**INCE YOU ARE reading Practical Wireless the chances are that you have already tried your hand at constructing one of our projects. If you are already well fitted out with tools or have access to workshop facilities the bending up of a piece of aluminium to make a chassis or the punching and drilling of various holes would not have presented you with much of a problem. But if you are a newcomer to home electronics you have probably employed 'knife and fork' techniques, utilising kitchen knives and similar tools!

This really is doing things the hard way and the effort involved can put a considerable damper on anyone's enthusiasm for home construction, apart from any ensuing domestic problems when the lady of the kitchen discovers that her best kitchen knife now looks like a hacksaw blade!

If you are really taken with the idea of constructing electronic gear then be prepared to start off properly by buying a few good essential tools designed for the job in hand. Forget Dad's woodworking screwdriver with its  $\frac{1}{2}$ " wide blade filed so thin that it seems to fit any screw head from 8BA upwards! Very convenient, of course, but what a mess it makes of screw heads! Dad's pliers, too, are very handy—they 'fit' any size of nut you like to mention but by the time they have slipped a couple of times that nut looks pretty sorry for itself.

When you find out what fun these electronic projects can be you will begin to take pride in the finished job and Mum's knives and Dad's tools just won't be good enough. So, start off on the right foot by getting the proper tools and remember that, like most 'bargains', cheap tools can turn out to be expensive in the long run. Spend a little more on tools from manufacturers of repute and scorn imported tools made of inferior materials.

The following review lists small workshop tools more or less in the order of necessity bearing in mind the requirements of the home constructor. The soldering iron takes precedence since even the simplest bought kit of parts needs the odd soldered joint or two.

In a review of this kind only general reference can be made to the great variety and range of tools that are available today. Specific recommendations are impossible without some knowledge of the amount of money it is intended to spend and the precise nature of the work to be undertaken in the workshop.

Workshops tend to 'just grow' from a few simple tools. As the limitations of these tools become apparent so more tools are bought to fill the gaps, thus it can be seen that a large initial outlay is not necessary.

Spreading the cost over a period allows emphasis to be made here on the requirement to buy quality, a policy which, if followed, will not be regretted.




**SOLDERING IRONS.** There is a wide variety of electric soldering irons available today, the main problem being the selection of one of a suitable wattage for the home constructor of radio gear. For the average Practical Wireless project a 25 watt iron should prove satisfactory but if a lot of work is likely to be done on printed circuit boards a 15 watt iron would be more appropriate. These circuit boards often contain many small components fitted quite close together and thus vulnerable to the heat of a soldering iron. Excessive heat can also damage the copper strips of the board itself.

With these irons goes a wide range of copper bits of differing diameters, some straight and some angled. Initially a straight bit  $\frac{1}{8}$ " or  $\frac{3}{16}$ " in diameter can be chosen for general purpose work with an angled bit for the awkward spots. At a little extra cost special bits are available which contain additives to the copper designed to prolong the life of the bit.


For home use a soldering iron operating directly from the 230 volt mains supply is usual but, for anyone who might feel a little happier with a lower working voltage, irons are available to work from as low as 6 volts via a mains isolating transformer.

When wiring an electric iron to its mains plug ensure that the instructions supplied with the iron are strictly adhered to so that the iron is properly earthed. This is a very important point for the builder of electronic equipment when wiring in transistors and other solid-state devices. Irreparable damage can be caused to these devices by stray earth currents if the soldering iron is not properly earthed.

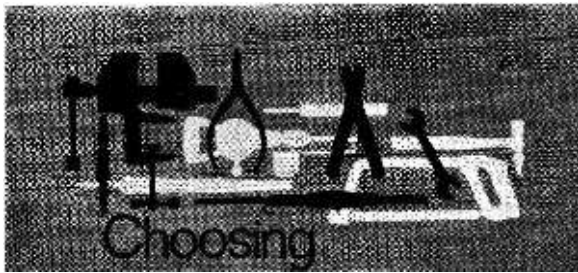Advancing rapidly in popularity are the soldering guns or 'heat guns', as they are sometimes known. The copper bit is, in fact, part of a low voltage secondary winding of the built-in transformer. Exaggerated claims are sometimes made concerning the short heat-up time for these guns,



## Choosing SMALL WORKSHOP TOOLS

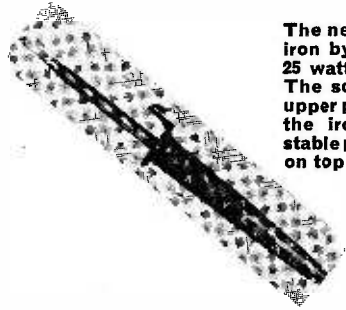


The new Invader soldering iron by Adcola is rated at 25 watts and has a  $\frac{1}{16}$ " bit. The square styling of the upper part of handle causes the iron to remain in a stable position when placed on top of the workbench.

One of the Litesold range of irons available in ratings from 10 to 60 watts, covering all requirements in



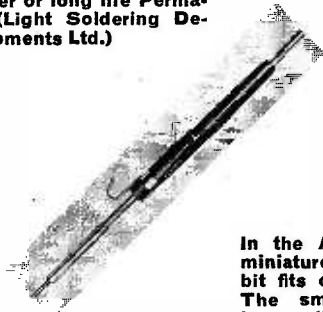electronic soldering. Various tips are obtainable in copper or long life Perma-tip. (Light Soldering Developments Ltd.)



In the Adamin series of miniature irons the copper bit fits over the element. The smallest, Model 6, has a rating of only 6 watts at 6 volts. (L.S.D. Ltd.)



This soldering iron bench stand guards against accidental burns or even fires. The iron maintains its normal operating temperature while in the stand. A bit cleaning pad is fixed to the front of the stand. (L.S.D. Ltd.)

typically 10 seconds, but the better known makes can be relied upon in this respect.

The trigger style on-off switch on these guns often has two positions, for fast heat-up and for running heat, thus giving a dual-heat facility. Sometimes other types of bit are available which can be used to cut sheet plastics or to weld plastic sheet and so on.

Solder today, as used on electronic work, invariably has several cores of flux to ensure better distribution of the flux around the joint and consequently a better joint. The solder contains tin and lead in varying proportions which affect the temperature at which the solder will melt. The usual ratio of tin to lead is 60/40 for radio work and the diameter of the solder can be between 18 and 22 s.w.g. depending upon the fineness of the work being done.

While short lengths of solder can be bought for a few pence the  $\frac{1}{2}$  or 1lb. reel will be found to be more economical for the home constructor. If however he wishes to experiment with various solders he will find many easy-to-use dispensers and handy-packs available with different types of solder such as 40/60 or 60/40 tin-lead alloys as well as solders containing a small amount of copper which is calculated to reduce the amount of wear on the copper soldering bit.

Although soldering irons are usually fitted with a hook of some kind so that they can be hooked onto a convenient point it is a good policy to provide some kind of metal stand for use on top of the bench. Such a stand can be easily made out of an odd piece of aluminium or tinplate.

Soldering iron manufacturers naturally produce their own stands or 'protective shields' for their irons and these are designed to ensure that the iron does not overheat when the iron is not being used but is still switched on. For convenience a cleaning pad for the bit may be incorporated and possibly a holder for a reel of solder.

A 'must' in soldering is a sharp pick or long needle for clearing out holes in soldering tags and removing surplus solder. Commercial versions are usually made of aluminium, to prevent the solder sticking to the needle, and with a plastic handle or covering. One end may be pointed and the other end split to enable wires to be unravelled from tags etc., while the solder is molten.

Another de-soldering aid available is in the form of copper wire braid. When the end of the braid is touched on a hot soldered joint surplus solder travels up the braid by capillary action. The end of the braid is snipped off ready for the next joint.



**PLIERS AND CUTTERS.** Again a very large field of choice and again the rejoinder to pay a bit extra to get quality. Two pairs of pliers will suffice for most constructional work, a long-nosed pair with tapered jaws coming to a reasonable fine point and a heavier pair with stocky jaws, maybe  $\frac{1}{2}$ " wide, and probably incorporating a pair of sidecutters.

The long-nosed pliers will always be in the hand of the electronics constructor, for twisting wires round tags and forming the wire ends of components before soldering them into position. Don't forget that a wiring joint should always be mechanically sound before it is finally soldered, although the true experimenter will not go along with this principle because he will want to use the same components time and again!

Variations on the pliers theme include those with angled

jaws of various lengths, round jaws and flat narrow jaws rather than pointed ones. When buying pliers see that the opening and closing action is not too loose or the jaw tips will not close together properly and it will be difficult to get hold of fine wires when wiring up.

Wirecutters will be used as often as the pliers so, again, only the best must be chosen. They should be about the same size as the long-nosed pliers with the cutting edges at an angle to the body. Other types have the cutting edges across the top or parallel with the body.

When buying sidecutters hold them up to the light and see that the cutting edges come together cleanly and evenly throughout their length. Try this test with a cheap imported pair of cutters and see the difference! The previous remarks concerning the action of pliers applies just as much to sidecutters. A loose action and the cutting action will be greatly impaired. On the other hand, there is nothing more annoying than a pair of cutters or pliers that need two hands to open them!

**WIRESTRIPPERS.** Different people have different ways of stripping the insulation from wire, varying from the use of the front teeth to an old kitchen knife! If the wire is nicked, and it often is, it will eventually break if it is subject to vibration or flexing. The ordinary sidecutters are frequently pressed into service as wirestrippers mainly because they will have just been used to cut off a piece of wire and are still in the hand! However there are plenty of wirestrippers on the market designed for the job so there is no excuse for improvisation.

Wirestrippers usually have some means of adjustment to cater for different size wires. It is important not to try to strip wires of a larger gauge than that for which the wirestripper has been set, or the wire will be nicked. One of the latest style wirestrippers on the market has a four position cam that can be adjusted immediately to another gauge of wire, while still held in the hand. Incidentally, this model also has wire cutters which have ground edges, a great improvement.

A feature on some types of wirestrippers, which the author considers of great importance, is the provision of a spring that keeps the cutters normally open, the cutting action taking place against the spring.

**SCREWDRIVERS.** Strictly speaking, every different sized screw needs its own screwdriver, if the blade is to fit the screw slot properly, but not many of us are likely to go to that extreme. The width of the blade should be about the diameter of the screw head or wider, rather than narrower. For electronic construction work it is best to buy a set of screwdrivers with blade widths from about  $\frac{1}{8}$ " up to  $\frac{1}{4}$ " or  $\frac{5}{16}$ ". Three screwdrivers should be sufficient. A useful addition is one for the Philips style screws, that is the screws with crossed slots.

Screwdriver sets are available consisting of several blades that can be fitted to a common handle. Although these may be cheaper than individual screwdrivers they are less convenient in practice.

The screwdriver blade itself should be about 6" or so long depending upon the blade width. One very useful size of blade is one about  $\frac{3}{8}$ " wide for use with knob setscrews. The blade should be as long as possible so as to reach a knob in spite of the clutter of other knobs, dials etc. on a panel.


Don't take any notice of the markings on some screwdrivers that seem to indicate that one can use them with safety on 10000 volt circuits! Anyone having that sort of voltage around should know the precautions he should take. They would not include the use of a screwdriver on 10000 volts!

Variations on the basic screwdriver include the ratchet


A most useful de-soldering aid is a reel of specially treated copper braid which will completely remove unwanted solder from a joint by capillary action.



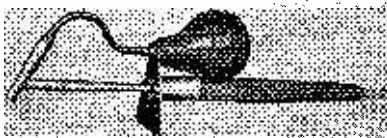
The Adcola protective shield is intended for wall or bench mounting and has slots for a spindle carrying a reel of solder.



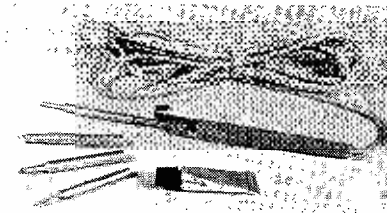This de-soldering tool (L.S.D. Ltd.) could be invaluable when stripping components from surplus equipment. It is self-contained and simple to operate and may be used as a conventional soldering iron.




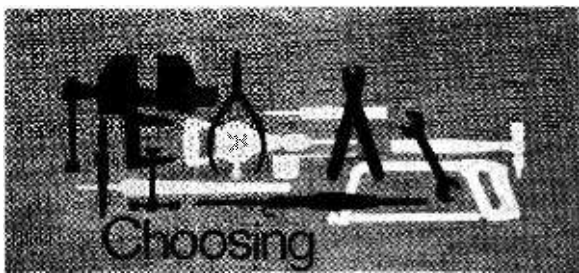The Adamin miniature iron, Model 15, can be obtained complete with a set of four bits of differing size. The tube of special lubricant is used to prevent the bits from sticking to the heating element.




Choosing


## SMALL WORKSHOP TOOLS

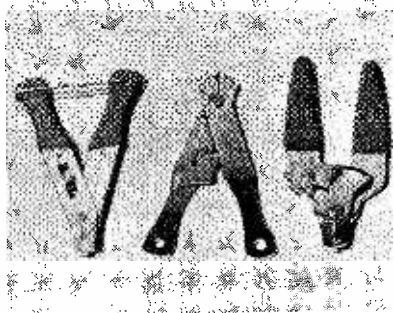

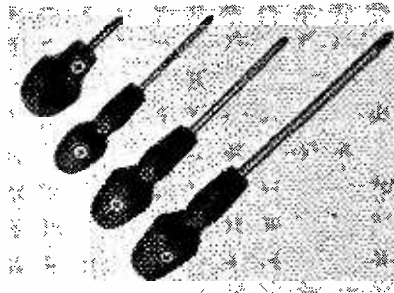Three of the Bib range of wirecutter, strippers by Multicore Solders Ltd. The latest, centre, is the Model 3A with an instantly adjustable cam enabling the strippers to deal with most wire sizes. The cutters have ground cutting edges. The ends of the arms are, in fact, flat spanners for 4 and 6BA nuts, a most unusual feature.



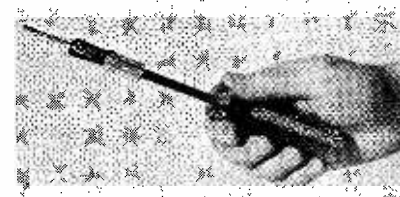A set of Stanley 'Pozi-drive' screwdrivers enabling Philips type screws to be reached in the most awkward corners.



The Stanley range of 'Spee-D-Grip' screwdrivers incorporating a spring clip which holds screws in position for starting in inaccessible places.

types which remove the necessity of continually lifting the screwdriver from a screwhead thus, incidentally, reducing the risk of the blade slipping and doing damage. Of course, if one used a screwdriver properly, the blade should never leave the slot, but this seldom happens!

A most valuable addition to a set of screwdrivers is one having a spring attachment at the tip of the blade to firmly hold a screw while it is being inserted into place. Its value in awkward spots is inestimable. Such an attachment can sometimes be bought separately for use on almost any screwdriver.

**SPANNERS.** There is always a temptation to use a pair of pliers on any nut that needs tightening, usually because the pliers are ready to hand. It should be remembered that the opposite faces of a nut are parallel to each other where-as the jaws of a pair of pliers are only parallel when they are closed. That's why the pliers always slip off the nut and cause damage.

First of all, get a set of box spanners covering 0 to 8BA either single or double ended. The single ended ones with a wooden or plastic handle are recommended. Just two, for 4 and 6BA, are worth their weight in gold in a workshop. Having long stems they are invaluable for placing nuts into odd corners where fingers or pliers cannot reach.

It is always good practice, wherever possible, to tighten a nut on to a screw rather than use a screwdriver on the screwhead. This is particularly important where the screwhead is visible such as on the front panel of a piece of equipment where a damaged slot on a screw would be an eyesore.

Another requirement in the spanner line is a set of flat spanners, again covering the BA sizes, possibly 0 to 8BA. These can very well be double ended ones since the length of the spanners is not of much importance.

Some sets are single ended but bolted together at one end so that one can be selected and the others swung out of the way, rather like a set of feeler gauges.



**DRILLS.** In the past a hand drill would have been a first acquisition in a workshop, followed by an electric drill when the money was available. Today the cost of electric drills is such as to justify buying one from the outset.

The simple electric drill will have a single speed and accommodate drills up to  $\frac{1}{4}$ " in diameter, ('twist drill' is really the proper name for the bit that does the cutting). This model will perform just about all the routine drilling jobs in a workshop where electronic projects predominate. A chuck adaptor to take drills up to  $\frac{3}{8}$ " in diameter is highly desirable, enabling the usual holes for mounting potentiometers etc. to be drilled without having to resort to files or reamers.

If the drill is likely to be used for other duties around the house then the two speed drill with a chuck taking drills up to  $\frac{1}{2}$ " in diameter can be considered. A popular accessory for the electric drill is the speed controller which is an electronic device enabling the speed to be varied continuously from a few r.p.m. to maximum speed. Such controllers are available in kit form or ready assembled.

If a lot of drilling is anticipated, particularly on chassis work, a drill stand will prove a boon. Most electric drill manufacturers have such stands but their design is such that they will accommodate most makes of drill. Such

stands ensure that holes are drilled vertically, which may not be very important on sheet metal work but could be critical with a deep hole. Holes will be more accurate both in size and positioning when drilled on a stand rather than with a hand held electric drill.

When using drill adaptors enabling, say, a  $\frac{3}{8}$ " drill to be used in a chuck of nominal  $\frac{1}{4}$ " capacity, remember not to overload the motor by exerting excessive pressure on the drill especially in hard materials.

Hand operated drills suitable for the small workshop range from the simplest single speed ones with a  $\frac{1}{4}$ " capacity to those taking drills up to  $\frac{1}{2}$ " and having an integral gearbox providing either a low speed or a high speed at the chuck. A little extra spent on a good hand drill will be a worthwhile investment. In particular the gears will run more smoothly and require less energy and the chuck will be of a better quality.

Now, what about the twist drills themselves? These are bought singly, as required, or, if starting more or less from scratch, then in a set complete with a stand for use on top of the bench. They may be had in sizes from about  $\frac{1}{32}$ " to  $\frac{1}{4}$ " in diameter or in a numbered range from No. 80 (0-0135") to No. 1 (0-228"). Letter drills carry the range on upwards from 'A' (0-234") to 'Z' (0-413").

For many years the author has had just four drills always to hand, No's 12, 24, 32 and 43. These will cover the drilling of holes for tapping or clearing for 2, 4 and 6BA screws.

As far as the quality of twist drills is concerned, it is necessary to take a little more care over their selection than with other tools since there are a lot of drills on the market that seem to be made of little more than soft iron! So once again beware of cheap imitations and if the pocket will stand it, buy a small set of genuine high speed drills. These will last for ever and seldom need sharpening if not abused.

**PUNCHES.** Whenever it is required to drill a hole in a chassis, or anywhere else for that matter, it is essential to use a centre punch to mark the spot where the hole is required. Otherwise it is almost certain that the drill will wander off the spot, scratching or damaging the surface being drilled. This particularly applies to hard surfaces and when using a hand held electric drill especially if care is not taken to keep the drill vertical.

There's not much to say about centre punches. A good one will be of tempered steel with a sharp round point, usually machine ground. Spring loaded punches are available which obviate the need for a hammer, so these punches are very convenient and the extra cost well justified.

Chassis punches are a necessity although the number bought for a small workshop will probably depend upon the funds available. These punches will cut holes ranging from  $\frac{3}{8}$ " to 3" in diameter but it is recommended that at least two be obtained,  $\frac{3}{8}$ " diameter for B7G valveholders and  $\frac{1}{2}$ " diameter for B9A valveholders. These punches require a suitable Allen key to operate them and their cutting limit is about 16 s.w.g. mild steel. They will cut through the usual 16 s.w.g. aluminium sheet like the proverbial knife through butter, thus saving a great deal of time and energy.


A useful tip . . . the resulting hole will have a burr on one side so place the cutting part of the punch on the side of the panel or chassis that might be of some importance from the point of view of appearance.

Other chassis cutters are available that will cut square or rectangular shaped holes but the infrequent need for such cutters does not justify their purchase.


The predecessor of the chassis cutter was the tank cutter. This had an adjustable cutting bar for different diameters of hole, but unless used in a lathe or drill press,



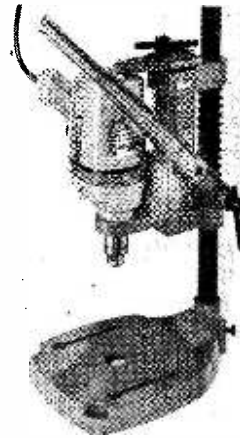
This bench clamp enables a portable electric drill to be used with grinding, polishing or other attachments (Wolf). The drill is a Wolf Sapphire 73.



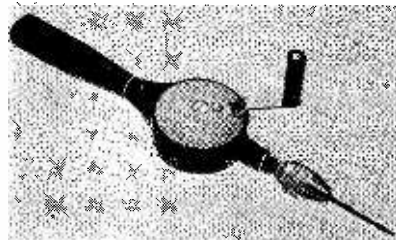
For precision drilling a bench drill stand is essential. The spring loaded press magnifies the hand pressure some ten times. (Wolf)



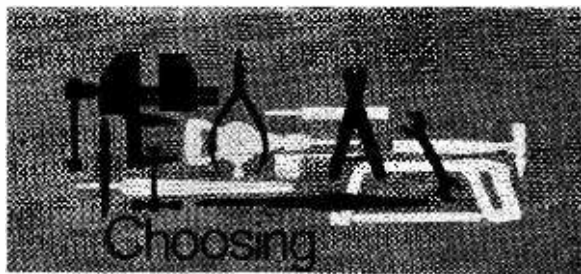The old-fashioned hand drill now has a streamlined appearance. In this Stanley drill the gears are completely enclosed protecting them from dirt, swarf etc. and obviating nipped fingers!




## Choosing SMALL WORKSHOP TOOLS

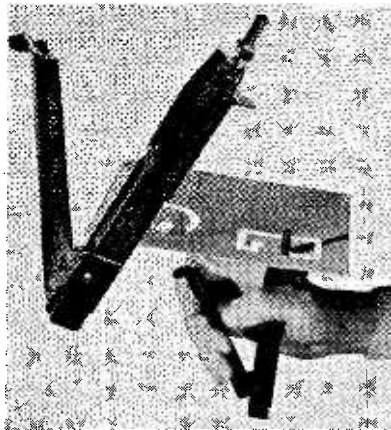

Requiring only a  $\frac{1}{8}$ " hole to begin operations this Adel nibbling tool will cut a hole of any shape or size in sheet steel up to 18 gauge steel or aluminium up to 16 gauge. (West Hyde Developments Ltd.) The punch and die action cuts without distorting the metal.



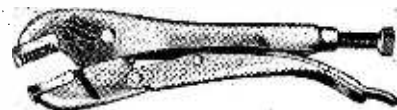This precision made Mole 'Supercut' tool has a powerful action capable of cutting long straight lengths, curves or angles in sheet materials such as steel, aluminium, plastic laminates etc. A replacement blade can be fitted very easily.



The standard Mole wrench has many uses in the small workshop. In spite of its immense gripping power it can be opened at a touch on the release lever.

the resulting hole could be a little rough in appearance. A slow cutting speed was essential and for this a carpenter's brace was ideal.

Other hand tools for cutting holes in sheet metal include the family of 'nibblers'. A small hole is first drilled in the sheet metal, the nibbler inserted and the action of the tool nibbles the material away to form a hole of almost any shape desired. The hole can be finished off with the usual files.

Shears, or tinsnips, will be needed for cutting sheet metal and a 10" pair with straight jaws should suffice for general work. The will make a straight cut in sheet metal for a limited distance although the 'goosebill' type will usually prove better for this work.

**TAPS.** Now and again the necessity will arise to tap a thread in a hole and for this two taps for each size thread are required, together with a tap wrench. The first tap is tapered, to start the thread, and the second tap is full size. Sometimes a third tap of intermediate taper is used but this is not really required for small threads.

The tap sizes most likely to be required are the usual 2, 4 and 6BA. Taps can be broken off relatively easily and for this reason a proper tap wrench is strongly recommended.

The simplest and probably the best tap wrench is the bar type with a screw grip on to the tap. The chuck model is more expensive but it does enable the tap to reach positions that would be inaccessible with the bar type wrench.



**FILES.** For finishing off the edges of metalwork and suchlike a 10" flat file will be quite adequate. That known as 'second cut' will prove best being neither too coarse nor too fine for work on soft metals. A similar sized half round file is very useful for finishing off large holes such as those required for meters. While smaller holes, for valveholders etc., can be cut with chassis punches the cost of similar punches for large meter holes tends to be prohibitive, especially as they are used relatively infrequently. Such large holes can be made by drilling a circle of small holes, then knocking out the disc of metal and finishing the work with a half round file.

A  $\frac{1}{4}$ " round file completes the essential complement of files. This will find most use in enlarging small holes in the absence of a reamer or for 'drifting' holes that are not quite where they ought to be! Perhaps the spot was not properly spotted with a centre punch before drilling!

With the advent into common use of slide switches on electronic equipment the need has arisen for a couple of small needle files, one round and the other square, for finishing off the rectangular holes required in panels for these switches. If a set of needle files can be managed then so much the better as these sets contain files of circular, triangular and flat sections as well as those already recommended.

When buying files get suitable wooden handles for them at the same time. Don't try to use a file without a handle or there will be a grave risk of the tang of the file entering the wrist if the file should jam or stick in the work.

**HAMMERS.** As far as hammers are concerned the small workshop should have one with a plastic or rubber head for bending sheet metal, without causing undue marking of the metal. A second hammer should be a light



one of the 'ball-pein' variety for general work around the place. A good make is advisable to ensure that the hammer-head is properly attached to the shaft as a hammerhead in orbit around the workshop is not funny!

**REAMERS.** During the construction of a piece of electronic equipment one always seems to need to drill a hole that is between the sizes of the drills available. In such a case a tapered reamer can be invaluable, as an alternative to filing out the hole with a round file, a process that does not endear one to one's family, if they are within earshot!

A pair of reamers can deal with holes between  $\frac{1}{8}$ " and 1" in diameter producing a clean circular hole with little or no burr. They are usually intended for use in a hand brace but can on occasion be held in the hand.

**VICES.** If a bench or table is permanently available for constructional work then a vice of some sort will prove to be a great boon especially when fabricating metal work. While smaller sizes are obtainable, an engineer's vice with 4" wide jaws should be the smallest size to be considered. Such a vice is extremely rugged and will take a lot of punishment, including using it as an anvil!

Since the vice jaws are made of hardened steel, and serrated at that, it is essential to make up a pair of soft jaws to protect work held in the vice. These jaws can be made from pieces of aluminium or other soft metal. Other vices have clip-on jaws which are plain, serrated or slotted to hold tubing or round material more securely. Another model of vice has a separate mounting plate that can be attached to almost any flat surface by means of a suction pad.

A carpenter's vice with 6" or 8" jaws is even better for sheet metal work since the jaws can be opened to a far greater extent than those of an engineer's vice. However the space needed to permanently mount a carpenter's vice, especially below and behind the vice, is considerably more than that needed for an engineer's vice. However, there are some portable vices on the market that seem to combine the best points of both types.


Although one may possess a bench vice there is always a need for a portable clamping or holding device and this is where the wrench comes in very handy.

The modern version of the wrench has an easily operated lever that allows the wrench to be locked on to the work and just as easily released. A clamp to hold the wrench is also available, which can be fitted to a table or bench top with a single clamping screw, thus providing a fixed vice if necessary. The jaw opening of the wrench can be adjusted over a wide range by a single screw fitting.


**RULES.** For marking out on sheet metal a rule and a square (trysquare) will be required, if an accurate job is to be done. A 12" rule is good enough and although it would seem that choosing such a simple tool would be no problem, the choice is, in fact, very wide indeed, ranging from rather inaccurate wooden rules, with printed graduations, to engraved steel ones.

Although a 6" square can be bought separately it really pays to buy a combination square since this incorporates a rule and square, usually of reasonable quality.

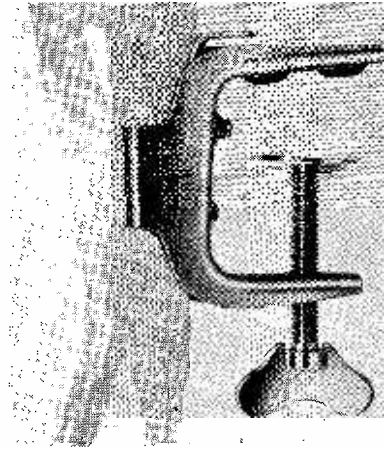**HACKSAWS.** The hacksaw will come in for quite a bit of use in the small workshop, mainly for cutting sheet metal to size before forming into a chassis. Some of the cheaper hacksaw frames will be found to twist when the blade is tightened up, so a good quality frame will be a sound buy. The adjusting nuts, too, can be difficult to turn owing to poorly formed threads.



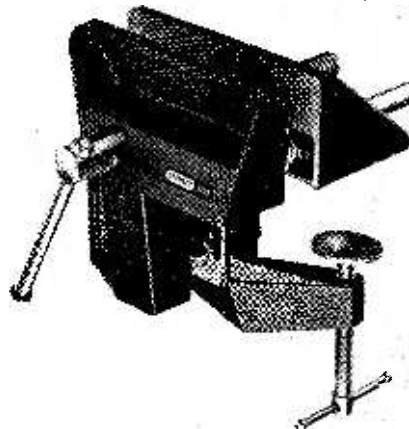
The versatility of the Mole wrench can be greatly increased by the use of this table or bench clamp, converting the wrench into a portable vice.



This Stanley aluminium portable vice has 5" jaws and can be clamped to any convenient surface. It is eminently suitable for bending sheet metal into chassis etc.



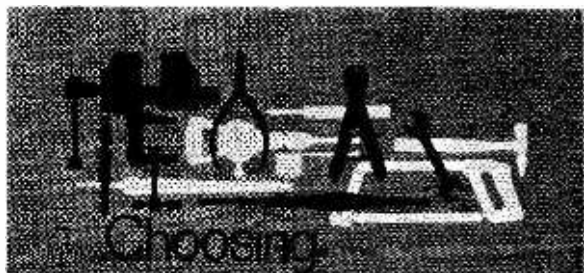
The Mini-Mole is just 5" long and very useful for getting into those tight corners, inaccessible to its 'big brother'. The curved jaws provide maximum contact with round or irregular shapes.


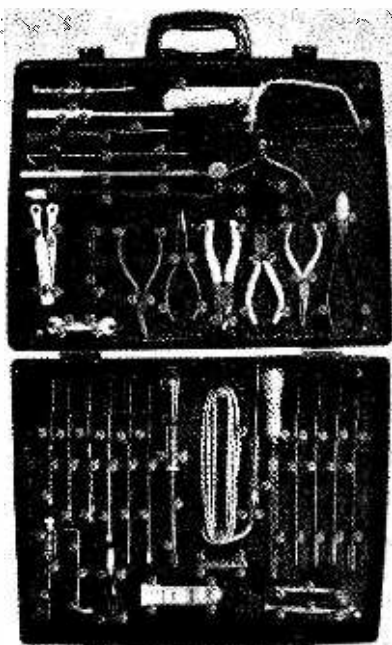
## SMALL WORKSHOP TOOLS



This set of Philips trimming tools and adaptors will cover every conceivable requirement when aligning electronic equipment. The compact packaging makes the set particularly useful to the service engineer. (Combined Electronic Services Ltd.)



If you don't feel like tramping around the tool shops to gather together your collection of small workshop tools then this very comprehensive tool kit may be the answer. It has a wide variety of spanners, screwdrivers, pliers, cutters, a soldering iron and solder, and even an angled mirror for viewing components tucked away in tight corners. (C.E.S Ltd.)

A frame to take 10" or 12" blades is big enough and the blades themselves can be of the low tungsten flexible type. These will deal with general cutting of mild steel, brass and aluminium etc. and absorb a lot of misuse without breaking. For maximum performance high speed flexible blades are to be preferred although they are a little more expensive.

For maximum efficiency the size of the teeth on the blade must be related to the material being cut. For soft metals, such as aluminium, a coarse blade is desirable to prevent the teeth from clogging, but on harder metals such as brass or on thin sheet metal a finer toothed blade is required. The number of teeth per inch of blade normally runs from 14 to 32 for hand held saws.

A very useful addition to the standard hacksaw is the 'junior' or bow-frame saw in which the blade is held under tension by the bow. The standard blade is 6" long with fine teeth. This saw is very handy for the smaller, finer jobs where the standard hacksaw would prove clumsy. In the electronic workshop the bow saw will be used a great deal for shortening the spindles of potentiometers, capacitors etc. Remember to hold the unwanted end of the spindle in the vice while cutting, rather than the component itself.


**TRIMMING TOOLS.** Although perhaps it is wandering into the realms of servicing it is not inappropriate in this review to mention trimming tools for electronic equipment. After all, having built a lovely radio set in our nice new workshop, it won't be of much use unless the tools to align it are to hand.

These trimming tools can be bought individually, as needed, but preferably they ought to be obtained as a kit. This will prevent the use of ordinary screwdrivers for adjusting iron cores which can only cause damage in the long run.

A kit may consist of one basic tool holder with several types of trimming tool that can be fitted into the holder or, in the more expensive kits, a complete trimmer for each purpose, such as adjusting iron cores, capacitors and special types of capacitors, such as the Philips pre-set beehive capacitors, which are met with quite frequently.

In conclusion it should be pointed out that for every basic tool mentioned in this review there are a dozen or more variations on the market. Like women, there are short ones, tall ones, thin ones and fat ones! Each one to his own fancy! The average D.I.Y. or tool shop is sated with gadgets that promise to relieve us of the tedium and work required to do a particular job. Few succeed, and those that do probably take twice as long to set up to do the job as one would take using basic tools alone.

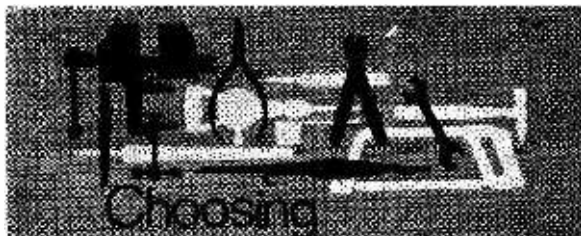It's surprising how often one resorts to basic methods and tools in the workshop. If funds are limited then put them to good use by buying only the best in tools from reliable manufacturers. If their names happen to be a household words they would not have reached those dizzy heights by selling rubbish.



## SMALL WORKSHOP TOOLS



# Out now! The 1971/2 Mullard data book.

An easy reference guide to the Mullard consumer electronics range of semiconductors, valves, television picture tubes and passive components.

Pocket size and colour coded for handy reference.

All components concisely listed in alpha-numeric sequence with Mullard equivalents, comparables and replacements.

Concise data on component types.

All this for just

**30p**



## How to get your copy:

available from your local bookseller or cash with order plus 5p for p & p from Selrøy Book Co., 60 Hayes Hill, Bromley, Kent.

The new Mullard book

## 'Applications of Infrared Detectors'

also now available.

CED 137

# CASCENT

**MAIL ORDER DEPARTMENT**  
No. 11 Mayes Rd., London, N22 6TL

## RADIO LTD

**BARGAIN COMPUTER BUMPER BOARDS**

Many Resistors, Condensers, Diodes and Transistors (minimum of 4 transistors on each board).  
**5 BOARDS FOR 120p.**  
Post Free.

**BLACK TERMINALS**

Length as indicated 1 inch  
10p per pair P. & P. 3p.

**BATTERY ELIMINATOR**

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2 1/2 in x 2 in x 3 in approx. 4 1/2 V £1.50, 6V £1.50, 9V £1.50, 7 1/2 V complete with cable and plug for Philips Cassette. **£2** plus 8p P. & P. each.

**SEND S.A.E. FOR GREAT BARGAINS IN MICROPHONES, AMPS, DECKS, COMPLETE DISCOTHEQUE CONSOLS, SPEAKERS AND MANY OTHER ITEMS**

**BRANCHES** 11e 40 MAYES RD LONDON N22 888 3206  
13 SOUTH MALL EDMONTON GREEN LONDON NS 803 1685

### LIGHT DIMMER

The unit comes complete with MK Ivory Front Plate and Control Knob, when used in place of Light Switch it will control your room lighting from off to full brightness. Power—up to 300 watts interference suppressed.  
**£2.75 P. & P. 8p**

### SOLID STATE BLOCK MODULES

Phono pre-amp E1311 input 100k, gain 28dB max out 3 volts; max input 50mV. Tape pre-amp as above E1313. Power amp E1314 input 1,000 ohms gain 20dB 300mW. Organ tone osc E1315 tone freq. 200-1k, Hz output 80mW. All above modules 9 volt. Dual flasher E1318 flash time 1-4 secs power 6 volt. Lamp 6v 150mA. All at **£1.25 P. & P. 10p**

### D.P.D.T. SLIDE SWITCH

**13p** each  
3p Postage

**Transformer Scoop**

Primary 220, 250 v. fused. Secondary 220 v. at 50mA, 6-8v. at 1 amp. Overall size 2 1/2" x 2" x 2 1/2" high. **63p** each. P. & P. 15p.

### COMPONENT CENTRE

8 x 6 Printed circuit board	10p	each
By100 Type rectifier 800 Piv 750 mA	18p	"
4 Pin transistor holders	3p	"
2 1/2 8-ohm speaker	33p	"
U2 Battery holders	5p	"
100OHM W/W Pots	13p	"
OC31 Heat clips (double)	3p	"
Tape rev counters	25p	"
1,500mF 150v DC 4" x 2" dia approx	40p	"
Flex connector 2amp approx non-reversible	13p	"
Ideal for loudspeaker connections	8p	"
2 1/2 8 ohm Speaker	33p	"

Please include Post & Packing  
Send S.A.E. for return of post quote of your electronic project.

### CHROMOSONIC SOUND OPERATED LIGHT DISPLAY

This compact unit (size 8 1/2" x 5 1/2" x 3" high) is connected directly across the speaker output of an amplifier, it will then convert audio signals into a spectacular three colour light display (600 watts light output each colour). Send S.A.E. for further details or call in at any branch for demonstration. **£18.50** P. & P. 33p

## 100 WATT

### HIGH POWER AMPLIFIER


- In excess of 100 watt peak output
- Open and short circuit proof
- Sensitivity 10mV for full output
- Frequency Response 10-25,000Hz
- Safe with all loudspeaker systems 4 to 16 ohms
- Silicon transistors used throughout
- F.E.T. Front end

Send S.A.E. for further details.  
▲ **£42.00** if purchased with light unit above **£40.00**  
Post and Insurance £1.00.

**GUARANTEED 12 MONTHS**
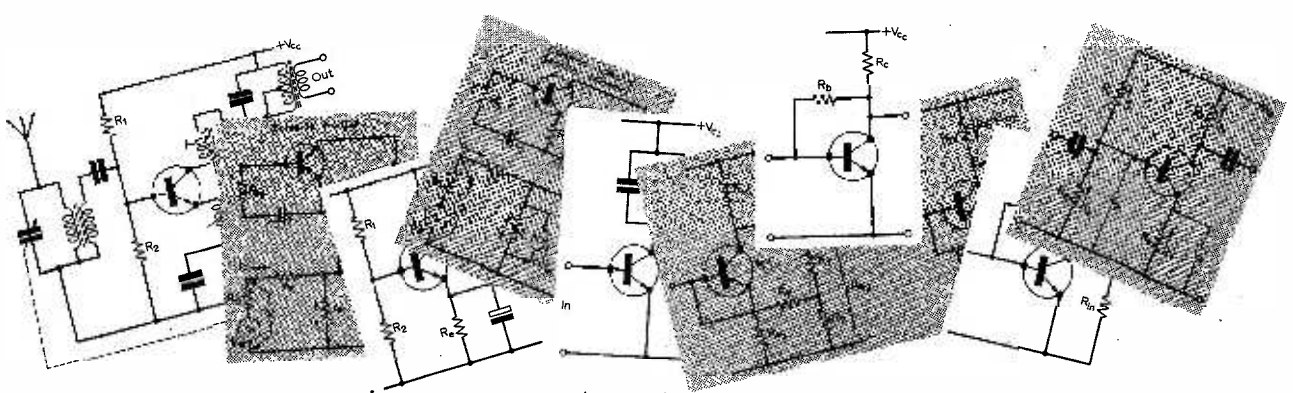
### DWELL TIME UNIT

These small units contain the following components: 700 ohm D.P.D.T. relay with base, 1µF 250v paper, 0.01µF 400v. paper, 50µF 35v. electrolytic, 3 diodes OC200 transistor, a 2N2926 type transistor unmarked, a skeleton pre-set pot, 4 pin din plug & skt., 4 foot of 4 core screen. All housed in a small neat metal box. Can be made into many timing devices. **43p** P. & P. 8p



# TRANSISTOR CIRCUITRY for beginners'

PART 1 H.W.HELLYER

**SPECIAL SERIES-READ IN CONJUNCTION WITH OUR FREE WALL CHART!**

WHEN the idea for this series was first broached, everything seemed straightforward and simple. We would entitle the wallchart 'Building Bricks,' said the Editor, in an inspired moment, and the articles would take up each 'brick' and develop it so that newcomers to transistor circuitry could understand what was happening inside those inscrutable black boxes.

Which was all very fine—but it completely overlooked the fact that any beginner worth his salt is going to say 'But Why???'

No good my declaring '... an input signal to the base of Tr1 turns it on, which causes Tr2 to turn off and Tr3 and Tr4 to return to the stable mode, releasing Tr5, which now bottoms and allows ... etc.' It would sound like a paragraph from Henry!

To understand transistor action, it is imperative that we begin by understanding what makes the darned things tick. That means going back to pure physics, not too deeply, preferably without mathematics, and then progressing to the methods of construction and the reasons why there are essential parameters—rules of operation, if you like—and this is what we shall begin with.

## Semiconduction

As the name implies, the semiconductor is neither pure insulator nor electrical conductor, but something in between. Its resistivity lies roughly midway between that of conductors and insulators. This resistivity, moreover, decreases with increase of temperature (the resistance of a conductor increases slightly as the temperature is raised). This is one important difference between semiconductors and conductors.

Next, perhaps more important, is the way in which current flows in a semiconductor. There can be two processes; either a flow of negative electrons, as in the case of a conductor, or a flow in the opposite direction of positive 'holes'. The concept of hole flow is so vital to the understanding of transistor operation that we must begin with a simple discussion of atomic structure in order to get a grasp of it.

## Atomic Structure

An atom consists of a central nucleus containing positively charged protons with a number of negatively charged electrons orbiting around it. The negative charge carried by an electron is equal to, and exactly opposite to, the positive charge of a proton. In a neutral atom, the numbers of each are equal.

Different elements have atoms containing different numbers of electrons, orbiting at different distances from the nucleus. The electrons close to the nucleus are tightly bound to the nucleus, but those circling in the outer orbits are more loosely bound, and are easier to dislodge from the parent atom. The outer ring is called the **valence ring**, and the valence electrons are those with which we are mainly concerned in this work. The looser they are bound to the atom—in any material—the better a conductor a piece of that material will make. This is because loosely bound valence electrons are free to be attracted by a positive charge, such as a voltage applied across a conductor by means of a battery.

Electrons flow out of the conductor into the battery at the positive connection, but an equal number pass from the negative connection of the battery into the conductor at the negative terminal, keeping the overall total of electrons the same.

Conversely, an insulator is a material in which all electrons are tightly bound to the nucleus, so that a large amount of energy is needed to break any loose to make a current flow.

## Crystal Structure

The structure of a crystal of germanium or silicon is depicted in Fig. 1. It can be seen that there are four valence electrons in the outer ring and these are balanced in the nucleus by four positively charged protons, as indicated. In the three-dimensional structure that exists in reality, every atom is equi-distant from four other atoms and each valence electron forms a pair with one from an adjacent atom.

In two-dimensional form this can be shown as in Fig. 1, with pairs of electrons forming co-valent

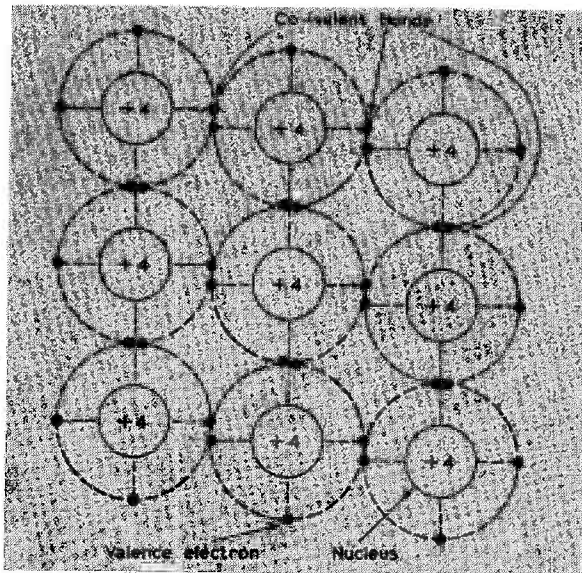


Fig. 1: Illustrating the structure of a germanium or silicon crystal.

bonds. This is a perfect crystal, with no impurities; and no electrons are dislodged from their atoms. This is, in fact, the basic structure of a perfect insulator, at absolute zero temperature, but as temperature increases, the energy of each atom is increased and some electrons can break away. If a voltage is applied, these free electrons are attracted to the positive pole and a current flow results. The space left in the crystal structure by a dislodged electron is termed a 'hole' and this represents a net positive charge.

We can therefore think of a movement of negative electrons toward the positive voltage terminal and a virtual movement of positive 'holes' (as successive electrons move to fill the vacant spaces) toward the negative pole.

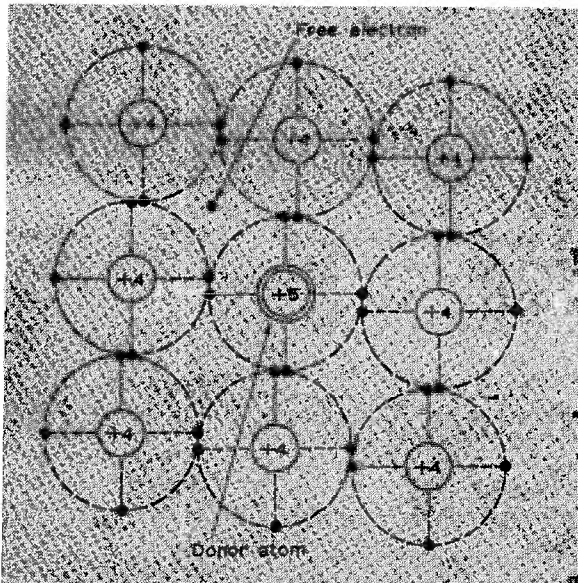


Fig. 2: Adding a 'donor' atom producing an excess free electron. N-type crystal.

## N- and P-Type Semiconductor

This is a simplified explanation, but suffices to show the principle of hole movement. In a pure semiconductor there must be one hole for each free electron. Such a pure semiconductor is termed an **intrinsic material**. However, if an element of impurity is added to the intrinsic material an imbalance is obtained. If, for example, a "donor atom" having five valence electrons is added to the crystal, as in Fig. 2, there is an excess free electron. Four of the donor atom's valence electrons form co-valent bonds, in the manner previously described, but the free atom cannot do so and orbits loosely.

Some materials with a valency of five are antimony, arsenic and phosphorus. These can be added to the germanium or silicon crystal in proportions of as little as one part in a hundred million and reduce the resistivity of the germanium from 70 ohms/cm to 1 ohm/cm. Because the donor atoms in such a material contribute free electrons, which carry a negative electric charge, a material "doped" in this

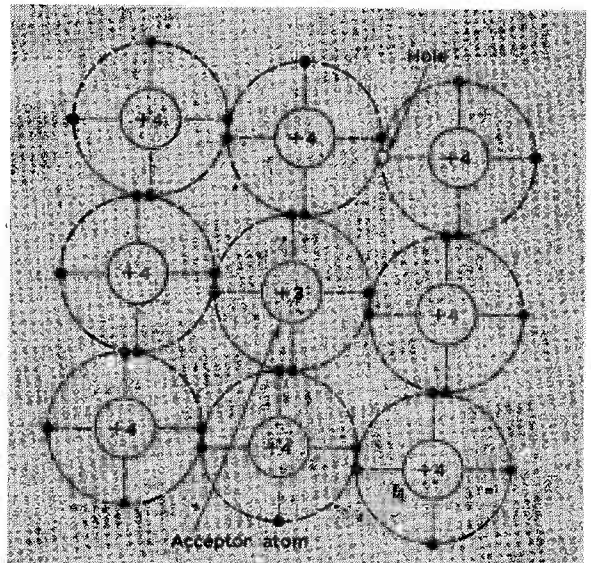


Fig. 3: In this case, an 'acceptor' atom creates a 'hole'. P-type crystal.

way is called an **n-type** semiconductor (i.e. it possesses an excess of negative current carriers).

The opposite process takes place if indium, borium or aluminium atoms are added to the basic semiconductor material, germanium or silicon. These materials have three valence electrons, and the addition of them creates holes in the semiconductor material, as shown in Fig. 3. The resultant semiconductor material has an excess of positively charged holes and is termed **p-type**.

## Minority Carriers

Minority carriers are another important factor of semiconductor physics. If a few electrons are injected into p-type material they are called minority carriers (the majority of current carriers in p-type material being, as we have seen, holes). Recombination takes place as the electrons move to fill the holes.

Similarly, holes injected into an n-type material

form minority carriers in this type of material, and small currents arise as recombination takes place. The time this takes to happen, termed the minority carrier lifetime, is an important property of a semiconductor material and the operation of most transistors depends on the movement of minority carriers.

## PN Junction

A single piece of p-type or n-type semiconductor material is purely resistive: reversing the applied voltage does not alter the current flow. But if p-type and n-type regions are formed in a piece of semiconductor material, with the regions adjoining each other, a rectifying device is formed: when voltage is applied in one direction, current flows, but in the other direction little or no current flows. Such an arrangement is termed a pn junction.

In Fig. 4, the region to the right of the centre line is n-type, possessing a certain density of free electrons. To the left of the line is a region of p-type material possessing a number of positively charged holes. When the junction is first formed, it becomes an area of activity for a short period as free electrons tend to cross into the p-type region and holes move over to the n-type region.

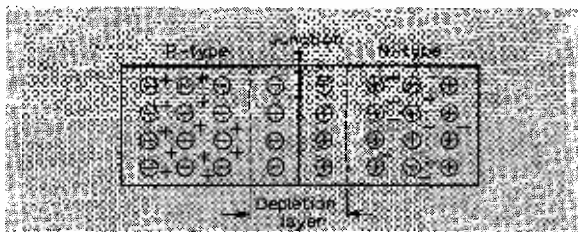


Fig. 4: Showing the charges existing in an unbiased PN junction.

This process of diffusion results in a potential building up across the junction, as the p-region gains a net negative charge with respect to the n region in the vicinity of the junction, and vice-versa, and this potential prevents further diffusion. This potential is termed the barrier potential and the region in the immediate vicinity of the junction, where there are very few free current carriers remaining after the initial diffusion, is termed the depletion layer or region, as shown in Fig. 4.

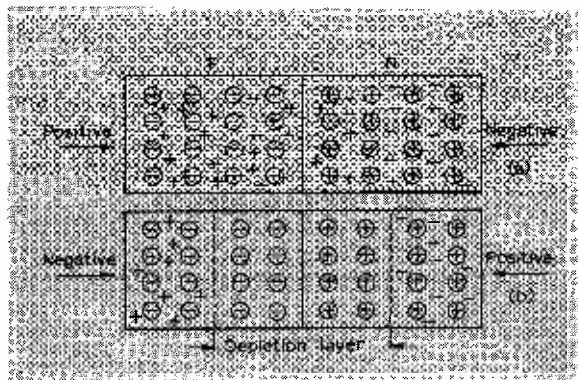


Fig. 5(a): Position of the charges with forward biasing and Fig. 5(b): with reverse biasing.

## Forward and Reverse Biasing

We now have a piece of material with pronounced non-linear characteristics: when an external voltage is applied, current will flow in one direction only. If the p-type side is made positive with respect to the n-type (see Fig. 5(a), forward biasing), the effect is that the barrier potential is reduced. Majority carrier holes will diffuse across to the n-type (where they become minority carriers), and majority carrier electrons will move in to the p-type region. A relatively large current can flow across the junction in this way.

Reversing the bias, i.e. applying it as shown in Fig. 5(b), increases the barrier potential (since the external voltage adds to that across the depletion layer already) so that current flow is made very low—in fact virtually nil. However, due to the effect of temperature a number of holes and free electrons will be generated on either side of the junction—this happens even at room temperatures—and this will give the effect of a small reverse current flowing across the junction. The forward current may be quoted in milliamps but the reverse current only in microamps.

## Characteristics of PN Junction

Fig. 6 shows the characteristics of a pn junction. As the forward voltage is increased from zero, the forward current increases slowly at first until the junction barrier is overcome, then rises rapidly. (In alternative terms, it can be said that the resistance of the forward biased junction is low.) In the reverse direction, the current remains low and practically


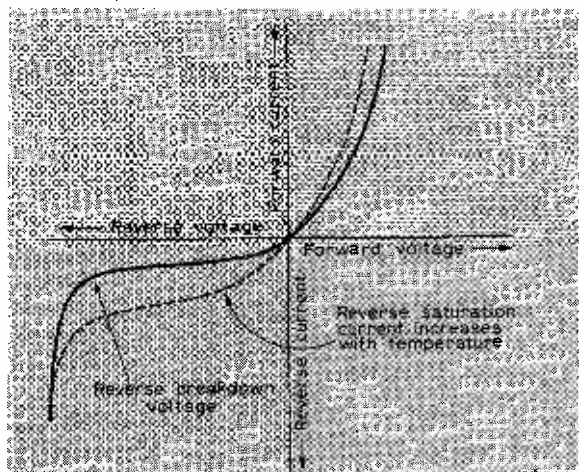


Fig. 6: The electrical characteristics of a PN junction.

constant as voltage is increased, i.e. reverse resistance is very high. Eventually, however, a point is reached where the reverse voltage accelerates the reverse current carriers to such a speed that they break down covalent bonds in the crystal structure, thereby releasing more carriers and producing an avalanche breakdown (when the junction may be destroyed). The value of voltage at which this occurs depends on the resistivity of the material.

As the reverse saturation current is due to the effect of heat, it increases with temperature, giving

—continued on page 512

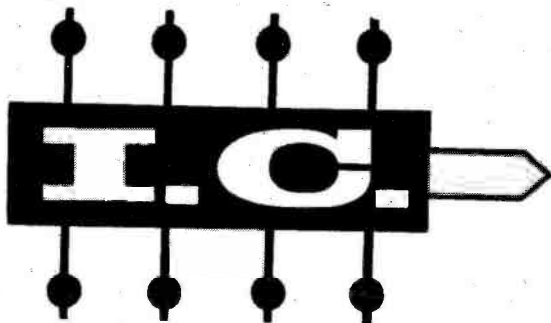

# OF THE MONTH

L.A.J. IRELAND

## Number 24 LM373 Multiple-mode Detector

SOME months ago these notes described the Motorola MC1596 balanced mixer integrated circuit and outlined its operation as a multiple-mode detector in receiver circuits. The unit discussed now goes further; full i.f. amplification facilities, at any chosen frequency up to 12MHz., are incorporated, as well as multiple-mode detection. It is the National Semiconductors (U.S.A.) type LM373, available in the U.K. from: Athena Semiconductor Marketing Co. Ltd., 140 High Street, Egham, Surrey: or Rastra Electronics Ltd., 275 King Street, Hammersmith, London W.6.

### Uses

The unit is intended, not just to operate in each mode, but to make it possible to design a receiver in which intermode switching would be simple without reduction of performance. As well as the standard a.m. and f.m. modes, as used for broadcast entertainment in the m.f. and v.h.f. bands, the LM373


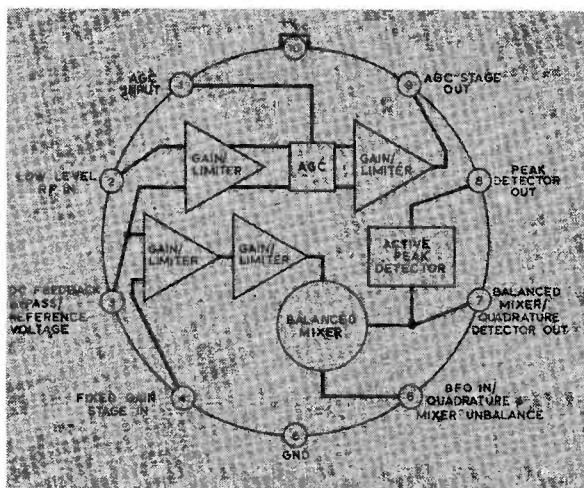


Fig. 1: The equivalent circuit of the LM373 (below) with (above) the top view of the pin connections to the various 'blocks'.

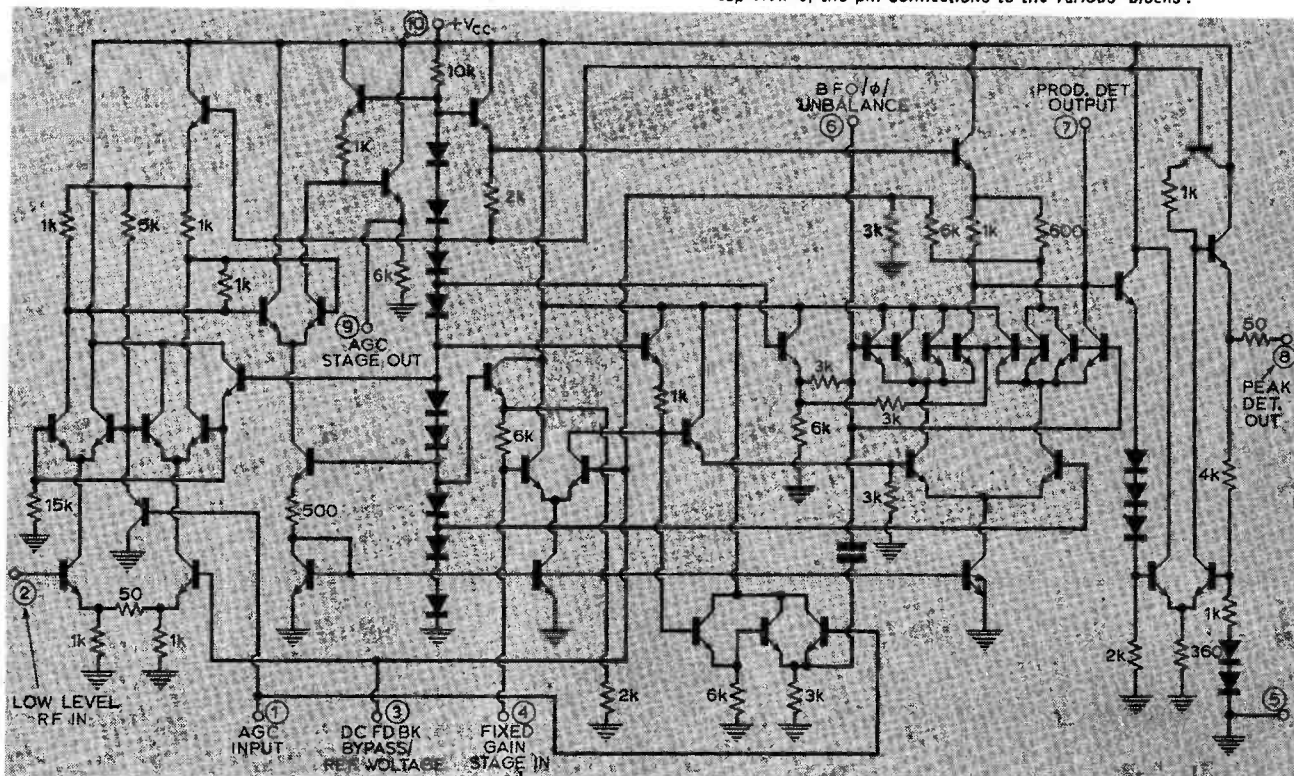



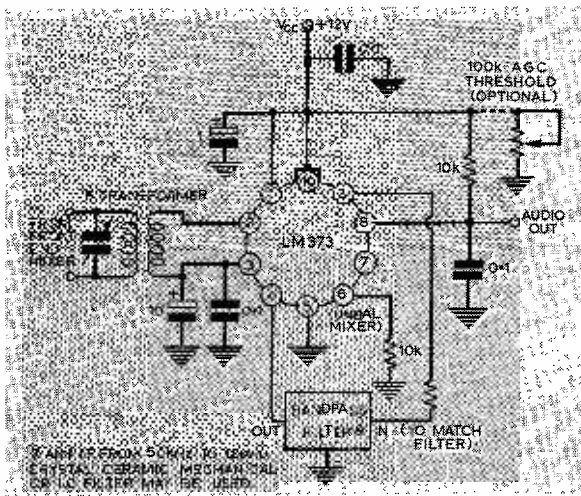


Fig. 2: External circuitry required for the LM373 when used as an AM IF strip.

can handle n.b.f.m. (narrow-band frequency modulation) increasingly used in mobile radiotelephone systems, and s.s.b. (single sideband suppressed carrier) transmissions of commercial or amateur origin.

### Design

Considerable ingenuity is exercised in the design of the i.c. to reconcile the conflicting demands of each transmission system with the minimum of intermode switching in the receiver. A.M. and s.s.b. receivers must have a linear amplitude response, maintained, despite the wide range of signal strength received off the air, by an automatic gain control subcircuit. An f.m. i.f. amplifier strip, on the other hand, is essentially nonlinear, in that any input signal is amplified to a limiting level before application to the detector stage. It follows that automatic gain control has no place in such a system.

To provide the facilities indicated, the LM373 incorporates four gain blocks, which can be operated in a limiting mode, as well as an automatic gain

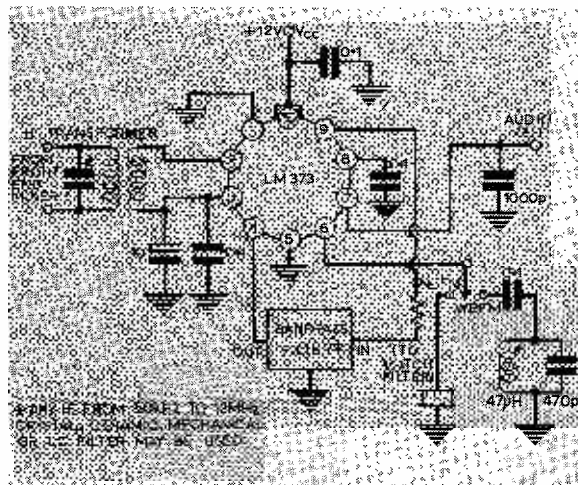


Fig. 3: The LM373 in its role of an FM IF strip suitable for narrow or wideband reception.

control system and two detectors, one a balanced mixer similar to that in the Motorola circuit already mentioned, and the other a peak detector for a.m. operation. The equivalent circuit and pin diagram given in Fig. 1 allows these sections to be identified.

### Operation

Some discussion of the circuit would appear necessary. Each gain block is essentially the familiar differential amplifier, which can be operated in its linear region when the circuit is used for a.m. or s.s.b. reception, or driven to full gain as a limiter for f.m.

The automatic gain control characteristic is secured through a pair of transistors shunting the differential interstage coupling components. When no a.g.c. voltage is applied, these transistors are cut off, but as the control voltage is increased, they draw off an increasing fraction of the signal current; finally the point is reached where the signal from

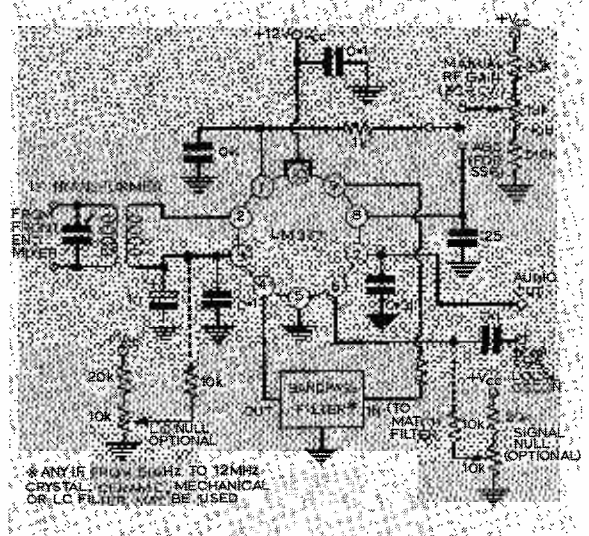


Fig. 4: The SSB/CW IF strip shown here further demonstrates the versatility of the LM373.

the first gain block is shorted out, and coupling to the second is merely through stray capacitance.

This approach secures the unusual a.g.c. range of over 70dB., enabling linear a.m. detection to be attained with input signals from 40 microvolts up to 200 millivolts. The string of reference diodes and emitter follower transistors from the d.c. +ve. line provide power supplies with decoupling to each stage of the amplifier strip, together with appropriate bias voltages to set the operating point of each element. As well as simplifying the external decoupling requirements of the circuit, these imply that each stage essentially has its own regulated supply, so minimizing the effects of power line variations.

The balanced mixer stage is easily identified by the cross-coupling of its component transistors. For f.m. it operates as a quadrature detector, a system outlined when describing the MC1496, as was the product detector system used for s.s.b. In a.m. operation, this section is deliberately unbalanced by an externally applied bias, leaving only one side of

the differential system connected to its load effectively.

N.b.f.m. demodulation requires a quadrature element of a higher Q factor, i.e. more rapid change of phase with frequency, and therefore a quartz crystal is substituted for the more familiar l.c. circuit. The final section is the peak detector, acting as a.m. detector and a.g.c. voltage source for linear a.m. and s.s.b. operation.

A few precautions are necessary for successful operation. The a.g.c. stage output at pin 9 has a very low impedance, being taken from an emitter follower. A value of 70 ohms is quoted, so that if a high Q crystal filter is employed here a series resistor is advocated, so that the resonance peak of the component will not be damped. The manufacturer of the crystal in question will quote a recommended source impedance, allowing selection of an appropriate resistor.

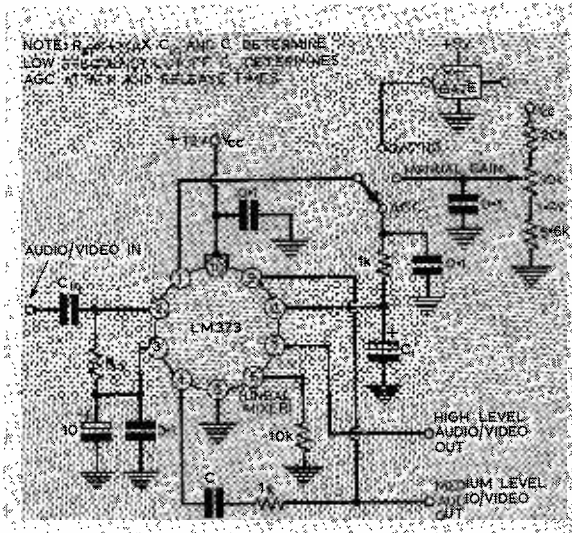


Fig. 5: In TV circuitry the LM373 can be used as an audio/video amplifier with a.g.c., manual gain control or gating.

The d.c. feedback loop at pin 3 must be carefully bypassed, since the decoupling must be effective throughout the passband of the LM373; an electrolytic or tantalum capacitor, as used for a.f. decoupling, has too high a reactance at high frequencies to be effective alone, so a small disc ceramic or silver mica is added.

For s.s.b., bypassing of r.f. at pin 7 is particularly important, as any local oscillator component reaching the peak detector would increase the a.g.c. voltage generated, and lead to an unnecessary reduction of system gain. The optional nulling circuits may be used to maximise gain should that prove necessary (an unlikely event).

Figs. 2-5 indicate the circuitry in which the LM373 may be employed, and it should be noted that the communications receiver applications for which it was designed do not exhaust the potential of this versatile unit, as is indicated by the circuit for a wideband amplifier indicated in Fig.5. Other reported applications have included use as an amplitude-modulated r.f. oscillator, an s.s.b. generator, or indeed any of the applications open to the balanced mixer circuit in which extra wideband gain is useful. So presumably more will be heard of the LM373!

## TRANSISTOR CIRCUITRY FOR BEGINNERS

—continued from page 509

the effect shown by the dotted line in Fig. 6.

Junction devices of this type are known as diodes, and widely used in radio, television and other electronic applications. The diode is essentially a one-way valve, as we have seen from the forward and reverse bias characteristics.

Germanium diodes were the first types developed for commercial use, but the current-handling capacity of these devices was limited, and it was not until research provided a means of treating silicon that power rectifier semiconductors became a practical proposition. Silicon is more difficult to melt and purify than germanium, but can be doped with donor and acceptor impurities in the same way as germanium, is less sensitive to temperature, and will handle higher powers more efficiently. Common types pass currents of half-an-ampere and more with a practically negligible forward resistance. Silicon diodes have a high reverse voltage rating. (On the other hand, a germanium has greater efficiency at low voltages and at higher frequencies, and is thus retained for signal circuits.)

The pn junction forms the basis of most forms of semiconductor diode and transistor. One other form of construction is important in connection with diodes—the point contact type. In this the rectifying property is possessed by a contact between a thin metal wire and a piece of semi-conductor material. Though junction devices predominate today, point contact diodes are still much used as detectors in radio equipment. Their characteristic is similar to that of the pn junction, shown in Fig. 6, except that as the reverse current increases beyond the reverse breakdown point, reverse voltage tends to fall.

TO BE CONTINUED

# TELEVISION

SEPTEMBER

## TV INTEGRATED CIRCUITS

Integrated circuits are beginning to appear in the new TV chassis in increasing numbers, particularly in colour receivers. The types used have been specifically developed to fulfil the signal processing requirements of TV sets but nevertheless bring with them numerous new techniques. In a new series starting this month we shall be examining these new i.c.s. to familiarise readers with the various changes in TV set design they involve.

## SERVICING TV RECEIVERS

Recent articles have concentrated on fairly up-to-date chassis. This month however we are going back to a widely distributed "625-line convertible" chassis, the Sobell ST195/ST282 series. This will give us an opportunity to examine the faults common in older sets.

PLUS ALL THE REGULAR FEATURES

ON SALE NOW

# SERVICING

## AN INTRODUCTION TO FAULT-FINDING

### PART 6

G. J. KING

**THIS MONTH G. J. KING RETURNS TO THE SERIES TO ELABORATE ON AUDIO MATTERS, DEALING WITH CONVENTIONAL VALVE AMPLIFIERS AS WELL AS TRANSISTORISED HI-FI EQUIPMENT.**

**N**OW that colleague Hellyer has cleared the decks on alignment, superhet theory and f.m. stereo, it is my turn to have a go on audio equipment.

#### GRAM AUDIO STAGES

An ordinary radiogram differs little at the pre-audio stages from a radio receiver, so much of the information presented earlier will also be applicable here. However, most contemporary radiograms are equipped for f.m. reception, possibly with a decoder to abstract the stereo information and to direct the left and right channel signals separately to the corresponding audio channels. Thus, many radiograms and record reproducers feature a pair of audio channels and speaker systems. These are very much twin partners, the design of one following very closely the design of the other.

A mono radiogram has just the single audio channel and speaker system (though some designs employ more than one speaker unit, the mono signal being applied to them all in suitable frequency division). Whether mono or stereo, the f.m. front-end is a fairly common factor, the demodulator these days usually being the ratio detector in unbalanced or (in better quality equipment) balanced mode.

However, while the f.m. detector in a mono receiver feeds the audio channel direct (via the  $50\mu\text{S}$  de-emphasis), the f.m. detector in a stereo receiver delivers the multiplex signal to the stereo decoder, the function of which is to process the sidebands of the stereo information (the difference signal) in conjunction with the mono information and the 38kHz reference signal (derived by frequency multiplication from the 19kHz pilot tone) to retrieve the left and right transmitted audio signals in the best isolation (e.g., with the least crosstalk).

De-emphasis and sometimes subchannel suppression (deleting the residual 19kHz and 38kHz multiplex components which can interfere with the audio section and add whistles to tape recordings) are engineered into the left and right audio channels, prior to the power amplifiers.

I shall be having something to say about f.m. front-ends, i.f. channels and stereo decoders later, but for now let us concentrate on the audio channels.

The simplest audio channel is designed round the triode-pentode valve, the triode receiving the detector's signal, amplifying it and then passing it to the control grid of the pentode for power amplification, Fig.1. Quite a lot of valve radiograms are equipped with this kind of audio section, as also are the inexpensive species of record reproducers. These were in fashion when stereo started, so early stereo models boast two such audio sections.

The advent of stereo was concurrent with the development of transistor equipment, which was fortunate for the receiver designers, so the audio channels we now find in stereo equipment are mostly transistorised.

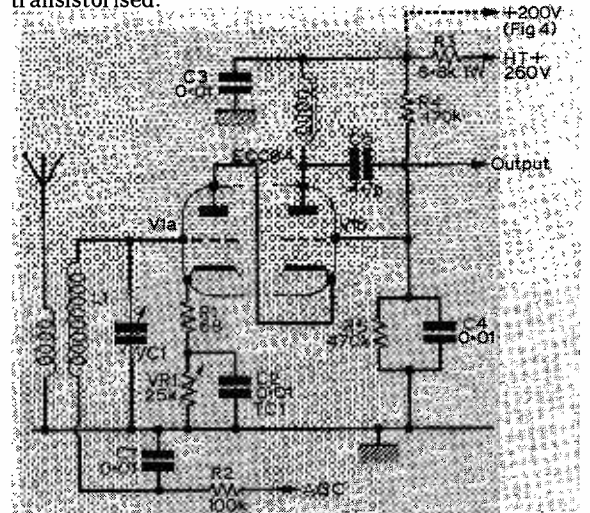


Fig. 1: A typical mono audio amplifier using a single triode-pentode valve.

Some designers favoured the use of a triode voltage amplifier (often one section of a double-triode valve) followed by a separate power pentode. This allows for greater audio power than generally possible from the pentode section of a triode-pentode valve, particularly so far as the early triode-pentode valves are concerned. Such a circuit is shown in Fig. 2, which will be seen to have much in common with that in Fig. 1.

Better quality receivers have been made with a pair of triode-pentodes in each channel to provide push-pull working. In this type of circuit the two pentodes are the push-pull output valves, while the two triodes are arranged as phase splitters supplying the anti-phase drives to the pentodes. However, since few receivers like this are in the field, there is not much point in detailing the circuit, but it is worth bearing in mind.

Let us return to Fig. 1. The audio signal from pickup or radio detector is coupled by C1 to the top of the volume control VR1, the selected level of signal then being applied via C2 to the triode grid. Note that the grid is returned to chassis through R1 (10M $\Omega$ ) and that the cathode of the triode is returned direct to chassis. This is a common trick to secure grid bias for the triode. Contact potential in the valve causes a minute current to flow through R1, and because of the high value of this resistor a small

potential developed across it, and since it is negative at the grid it serves as grid bias. It requires an electronic testmeter to measure this bias (since a normal meter would swamp the 10M $\Omega$  with its own resistance).

A common cause of distortion in this kind of circuit stems from a faulty triode, the fault resulting in excessive grid current and hence a potential across R1 in opposite polarity to that of the bias. The triode anode current rises, and often the valve tends to overheat.

R2 is the triode anode load, with R3 and C3 the decoupling components. The signal across R2 is coupled by C4 to g1 of the pentode, which is biased by the voltage drop across the cathode resistor R4, the grid being returned to chassis through R5. C5 is the cathode bypass capacitor (always an electrolytic in audio output stages).

The anode of the pentode is loaded by the low impedance speaker via the output transformer T1. C6 across the primary attenuates high-order harmonic distortion and makes the reproduction more palatable, as there is no negative feedback and no cancellation of second-harmonic distortion by any push-pull action.

## FAULTS

Owing to the simplicity of this circuit, (Fig. 1) faults are not generally very difficult to define or locate. A cause of bad distortion is poor insulation of the coupling capacitor C4. This would permit a positive potential to exist at the control grid of the pentode with a consequent counteracting of the negative bias. It would be accompanied by excessive positive voltage at the cathode of the pentode, which could result in the failure of C5. The valve would also

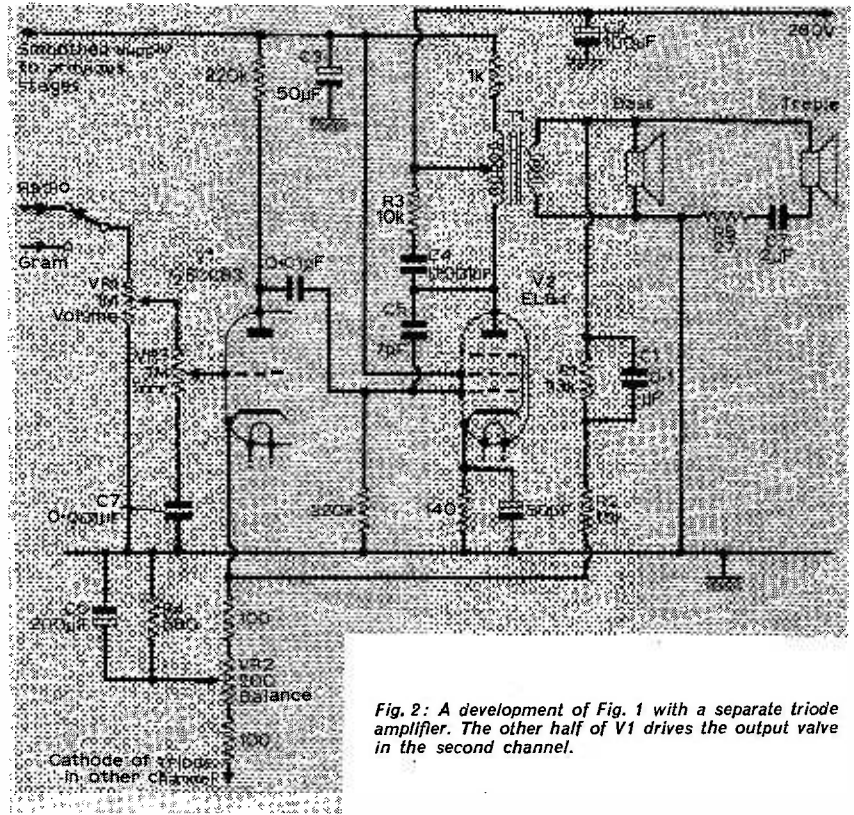


Fig. 2: A development of Fig. 1 with a separate triode amplifier. The other half of V1 drives the output valve in the second channel.

run very hot, possibly with the pentode anode glowing red.

Complete failure (e.g., audio drive at the top of the volume control VR1, but no speaker output) should first lead to a valve test, followed, if necessary, by voltage checks on the appropriate electrodes. C6 is subjected to audio voltage peaks which sometimes result in it shorting. This would cut the output completely, of course, but without affecting the pentode anode voltage much, so look out for this if the valve and electrode voltages seem to be normal.

Open-circuit of T1 primary deletes the pentode anode voltage, a fault condition which is often revealed by the screen grid (g2) of the pentode glowing red hot.

Low gain or volume at maximum volume control setting, assuming normal audio drive from the detector or gram pickup, is not uncommonly caused by C5 going open-circuit or low in value. This results in negative current feedback from the audio then developed across R4. The quickest way of checking this is by shunting an electrolytic across C5.

The symptom can also be caused (possibly accompanied by distortion) by the triode anode load R2 going high. If R3 goes high or C3 becomes electrically 'leaky,' the voltage at the top of R2, and hence the triode anode voltage, will drop, which again will cause low gain and possible distortion.

Before going on to more modern transistor circuits, let us have a look at some possible fault conditions in the valve circuit in Fig. 2. The faults described for Fig. 1 circuit would also be applicable here, with one or two qualifications. First, there are two separate valves involved, the triode voltage amplifier in this case being one section of a double-triode, the other triode serving as the voltage amplifier of the partnering stereo channel (not shown).

If one channel only is in trouble one can easily compare the voltages, etc. with those at the same points in the active channel, which is a quick way of bringing the fault to light. It is also possible to substitute the same type of valves (V2, for example) between the two channels, which would tell conclusively whether the valve is responsible.

There are refinements in Fig. 2, not found in Fig. 1 circuit. For example, voltage negative feedback is applied from the secondary of the output transformer T1 to the cathode of the voltage amplifier V1, and for this to happen one side of the secondary has to be connected to chassis. The amount of feedback is determined by R1 and R2, while C1 in parallel with R1 corrects the phase of the feedback signal, ensuring that it remains substantially negative over the audio spectrum. Thus, if there is a significant rise in gain (e.g., full output at a low setting of the volume control VR1) and abnormally high distortion, then R1 and R2 should be checked for value.

C1 open-circuit could encourage instability at certain frequencies, and this is sometimes 'triggered' by transients of the music. The oscillation could be at a frequency above audio, and the only way to prove this is by connecting an oscilloscope across the secondary of the output transformer T1, preferably when the amplifier is driven by a sinewave signal from an audio generator. The oscillogram in Fig. 3 gives some idea of what the spurious signal could look like on the sinewave. The audio generator would be coupled to the grid of the triode, of course.

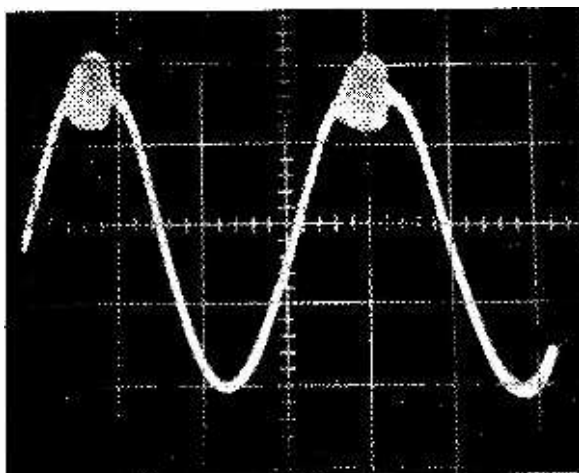


Fig. 3: This oscillogram shows spurious oscillation triggered off by transients in the signal

If the earth and feedback connections are reversed on the transformer the feedback would be positive and the amplifier would turn into a violent oscillator! Take care, therefore, when fitting a replacement transformer! Moreover, designs like this are geared to an output transformer of specific characteristics, so if it becomes necessary to replace the transformer, and the exact type is not available, then it might be necessary to alter the feedback resistors and the phase-correcting capacitor so that the values provide the correct conditions of feedback.

An interesting feature of the circuit is the tap on T1 primary. An output transformer of this kind serves both for speaker coupling and for 'smoothing' the h.t. supply fed to the earlier stages. In fact, it acts in part rather like a smoothing choke. In the

circuit, C2 is the reservoir capacitor across the power supply output and C3 is the main smoothing electrolytic.

R3 and C4 series combination across the signal part of T1 primary attenuates the higher-frequency distortion components while, with C5, providing a degree of corrective phase shift.

The triode V1 in this circuit is cathode-biased, the main cathode resistor being R4, decoupled by C6. VR2 is the stereo balance control, which feeds either side the 100-ohm resistors (one to the cathode circuit of the partnering channel). The 100-ohm resistors provide a small degree of negative current feedback since they are out of the decoupling influence of C6. The voltage developed either side of VR2 relative to the slider also contributes to the feedback. Thus it will be appreciated that by adjusting VR2 from its centre setting, the feedback on one channel will decrease, while increasing on the other channel. This, therefore, allows the gains of the two channels to be adjusted relatively for the most desirable stereo effect.

VR3 is a simple 'tone' control which works as a reactive potential-divider in conjunction with C7. With increasing frequency the reactance of C7 falls, which means that as the slider of VR3 is turned towards this end of the track the bass is lifted and the treble diminished.

It will also be seen that two speaker units are employed. That for bass is connected directly across the secondary of T1, while the treble unit receives drive via R5 and C7. R5 reduces the power, while C7 passes only the higher frequency signals. This is a very simple frequency-divider, which cannot be regarded as 'hi-fi.'

## HI-FI CIRCUIT

One channel of a slightly different circuit which, possibly differing in detail, is found in some hi-fi equipment. This is the power amplifier department only, Fig. 4, where Tr1 is the input transistor, coupling to the d.c.-coupled pair Tr2/Tr3 via C1. The coupling is from Tr1 emitter (the collector 'earthed' to signal through C2). The stage is thus an emitter-follower, which has a relatively high base input impedance, giving the correct match from the control section.

Tr4/Tr5 constitute a complementary driver pair (complementary because one is n.p.n and the other p.n.p.). These drive the push-pull output transistors Tr6/Tr7 alternatively into conduction and cut-off on each half-cycle of signal. It will be noted that the base of Tr4 is fed from the same source (e.g., Tr3 collector) as the base of Tr5. Thus on a positive half-cycle Tr4 conducts and pushes a positive half-cycle into Tr6 base. At the same time Tr5 is driven downwards and since Tr7 base is connected this time to Tr5 collector a negative half-cycle appears at Tr7 base, pushing this transistor into cut-off. On a negative half-cycle of drive the conditions reverse, so that Tr6 is driven into cut-off and Tr7 into conduction.

The two half-cycles are reconstituted as a complete waveform in the load comprising the speaker, coupled through C3.

C4 is a bootstrapping capacitor which applies feedback in such a way as to increase the driver input impedance. A.C. negative voltage feedback is applied to Tr2 emitter circuit from the push-pull pair, via C5

Fig. 4: Circuit of one channel of a transistorised hi-fi stereo amplifier.

and R1. Feedback of 60dB is a common hi-fi value, which reduces the output impedance to a fraction of one ohm.

D.C. coupling exists right through to the output transistors from Tr2, so by adjusting the d.c. conditions, both the drive 'balancing' and the quiescent current of the output transistors are affected. Some circuits have no means of adjusting these parameters, so if the value of a critical component alters, so might the quiescent current and balancing.

However, in Fig. 4 VR1 adjusts the balancing and VR2 the quiescent current, which leads us neatly to hi-fi equipment fault-finding and tests. But before going on to this it is noteworthy that temperature stabilisation is often provided in or around VR2 circuit to hold the quiescent current steady with increase in temperature of the transistors. The 'thermal element,' TH1 in Fig. 4 provides this function.


### AMPLIFIER TESTS AND FAULT FINDING

For detailed testing in audio circuits, especially high quality circuits in which transistors are employed, we require an audio signal generator, audio millivoltmeter and an oscilloscope, at least. For distortion tests, we require in addition a distortion factor meter or similar instrument.

If it is assumed that the radio or pickup source signal is reaching the input of the amplifier and there is no output from the speaker, then we should check as far as possible into the amplifier with a signal tracer (e.g., pair of headphones, etc.—see Part 3, PW July 1971). In Fig. 4, for example, we could get to the base of Tr2, but possibly not any further owing to the d.c. couplings of the subsequent stages. Indeed, it is often necessary to consider the power amplifier proper as a complete circuit from the testing point of view. This is because a faulty transistor or component in one stage could reflect fault conditions into the other stages as a result of the d.c. couplings. This possibility is often overlooked when testing in circuits of this kind.

When we reach the point where the signal disappears, therefore, we may have to continue the exercise in terms of voltage measurements at the electrodes of the various transistors, comparing them with the correct values given in the service manual or on the circuit. Complete failure commonly implies significant change in the d.c. conditions, so the fault area should soon be revealed by voltage testing. If a coupling capacitor has failed, then signal tracing should reveal this without much trouble.

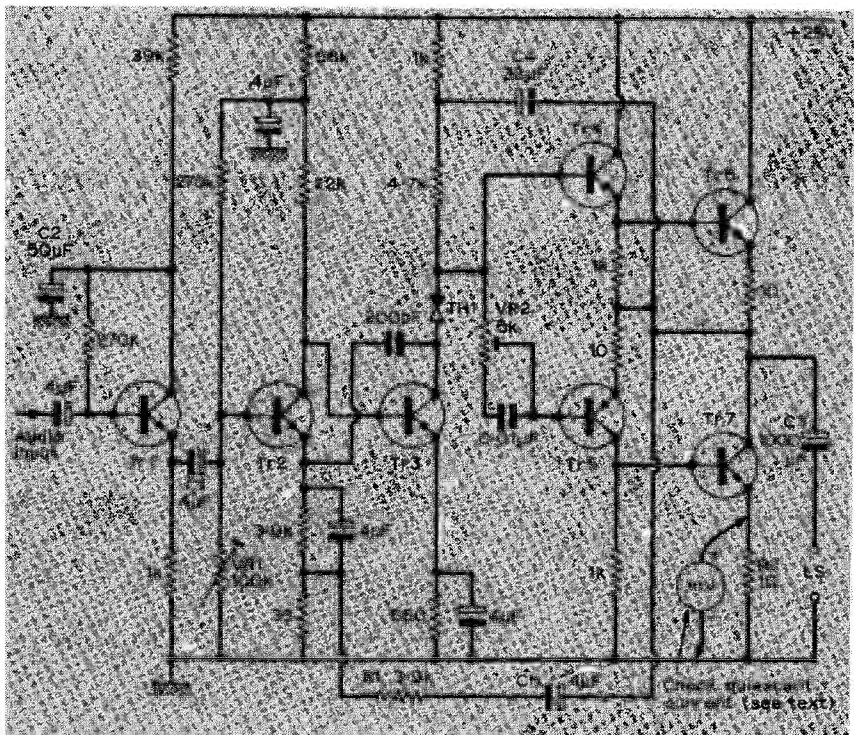More difficult faults to locate are those resulting in low gain, intermittent crackling and distortion at all powers or only at high power. Starting first with distortion, a preliminary test should be that of



quiescent current (assuming the amplifier to be 'Class B,' which it usually is in these days of transistors).

If possible, one should avoid connecting a milliammeter in series with the output pair for this test, owing to the resistance of the meter movement. In a circuit like that in Fig 4, the voltage across the emitter resistor (R2) of Tr7 should be measured on a d.c. millivoltmeter. The voltage will be very low because R2 is only 1 ohm! Anyway, suppose we measure 25mV, then by Ohm's law we can calculate that the current is 25mA (1 ohm resistor, since  $I=V/R$ , where I is in mA when V is in mV). A current of 25mA is, in fact, a common quiescent current value, and it can be adjusted accurately by a preset such as VR2.

If there is no preset and the current is way out, the values of the resistors associated with this part of the circuit should be measured (also the thermistor, etc., if used). Excessive quiescent current will cause the output transistors to run hot and limit the output

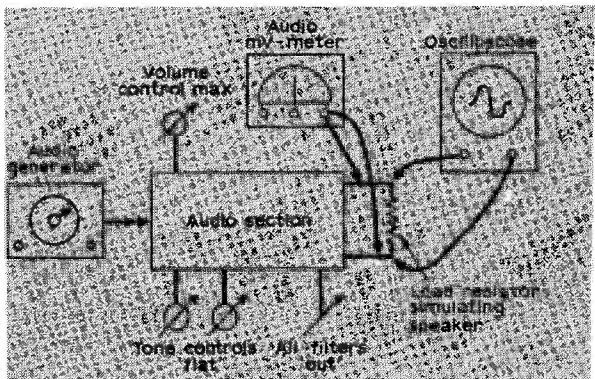


Fig. 5: Equipment set-up required to check the balance of output transistors.

power, while too low a value will precipitate high distortion (crossover distortion) at low volume.

Balancing requires an oscilloscope to monitor the output sine wave fed from an audio generator. The setup is shown in Fig. 5 where it will be seen that the speaker is replaced by a load resistor of suitable power rating (to match the steady-state power of the amplifier). The volume control should be fully advanced, and the generator signal increased until the tips of the displayed waveform commence to clip. When the balancing is correct both tips will clip together. If one clips before the other then the balancing preset (such as VR1 in Fig. 4) should be adjusted for symmetrical clipping. The waveforms are shown in Fig. 6.

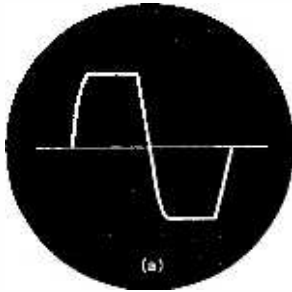


Fig. 6(a) Symmetrical clipping of the waveform when the gain is advanced indicates correct balance.

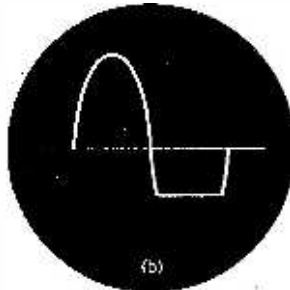


Fig. 6(b) Output waveform with an unbalanced stage.

We can use the setup in Fig. 5 to measure the steady-state power of the amplifier. For this test the oscilloscope should either be accurately calibrated in peak-to-peak voltage (so that the r.m.s. voltage of the waveform can be determined by multiplying the peak voltage—i.e., half p-p voltage—by 0.7) or an r.m.s.-reading audio millivoltmeter should also be connected across the load, as shown in Fig. 5.

The load voltage just prior to the clipping point should be noted, and the steady-state power in watts is equal to the load voltage squared divided by the load value in ohms (i.e.,  $W = V^2/R$ ). The power is usually taken at 1kHz, but the power bandwidth can be appraised by noting the reduction in power at the low and high frequency ends of the spectrum.


Low power, but good waveshape often signifies low supply rail voltage, and this can result from low mains voltage or incorrect mains voltage tapping.

## DISTORTION TEST

Finally, total harmonic distortion testing. For this we require either a complete distortion factor meter or the set-up in Fig. 5 with a distortion measuring unit which, as was noted in the Test Instrument supplement, April 1971, is a 'notch filter' which

tunes out the fundamental frequency of the output signal, leaving only the harmonic components, the voltage sum of which is compared in ratio with the voltage of the fundamental frequency across the load, to give the dB or percentage total harmonic distortion.

The complete set-up is shown in Fig. 7. The voltage across the load is first measured at the required power (use the oscilloscope for maximum power test to indicate the clipping level) with the switch in position A, then switching to position B, allowing the audio millivoltmeter to read the voltage of the summed harmonics. For this to happen, however, the distortion measuring unit needs to be very accurately tuned and balanced for the least indication on the audio millivoltmeter, which requires the range of the millivoltmeter progressively to be stepped down. The total harmonic distortion is the voltage ratio between the readings at switch positions A and B.

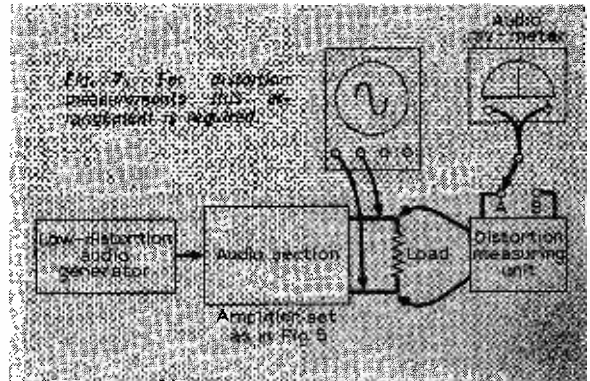

For example, if voltage A is 9V (which across 8 ohms would correspond to about 10W) and voltage B is 90mV, the ratio would be 100:1 or 40dB, corresponding to 1% t.h.d. With 9mV at B it would represent a ratio of 1000:1 or 60dB, corresponding to 0.1% t.h.d.

Remember, though, that a simple distortion measuring set 'notches out' only the fundamental, leaving wideband noise as well as t.h.d. components, so the distortion readout will include noise. Residual hum is generally removed by a high-pass filter in the test set-up, but such filtering, of course, cannot be used for distortion measurements at low-frequency for obvious reasons.

## END OF PART SIX

### Back Numbers Important Announcement

We regret to inform readers that owing to the closure by the Company of the department concerned it will no longer be possible to supply back numbers of **Practical Wireless** and **Television**.

To ensure obtaining regular copies of these magazines readers are strongly urged to place a regular order with their local newsagent, or to take out an annual postal subscription.

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CQ" column which appears in most issues.

# practically wireless

## commentary by HENRY

Ted  
and  
Lid

NO, not *that* Ted. Henry is not taking the lid off political chicanery—leave that to out-of-office politicians. TED, or, more properly, T.E.D., is a beautiful phrase I heard during a broadcast interview recently. That ubiquitous character, A. Spokesman, was defending the Post Office in the face of polite but relentless attacks from the BBC, who were following up listeners' complaints about crossed lines.

'How does it happen,' came the suave question, *'that we pick up our telephone and find our conversation interrupted by a pair of drooling lovers or an irate customer who has lost his laundry?'*

Ah, well, our indefatigable spokesman countered, that is probably caused by a Transient Equipment Defect. Isn't that lovely? Imagine, Joe, when wifey grumbles about the birdies that chirp unwantably during her 'Housewives' Choice', being able to say airily: *"Can't do much about that, I'm afraid. That's TED."*

The point is that the faults are not just short-lived, ephemeral, unidentified phenomena—giving them a name has fixed them, preserved them for posterity, entered them on the list of recognisable bugbears.

Wireless work is full of such



We cheer when we get a half-scale reading . . .

instances; for example, the intermittently blowing fuse. We pursue diligent tests before replacing the offending glass tube. We measure resistance, cheer when we get a half-scale reading, then remember that we intended to change the battery of the meter last time we used it.

Baffled by the lack of short-circuits we decide to beat the brute by checking the current. Meter in series—ah, which way round? Switch on. No, the other way around: *is that pointer bent?* But the reading is no greater than expected, and certainly less than the rating of the fuse, which we refit. Perhaps it is the result of overheating. We cover the now smug-looking set with our jacket and wait.

It is a bad habit of some manufacturers to let dirty great heat-sinks jut out at the back, and the fallacy about cool-running transistors is shattered as we smell singeing Harris Tweed and realise we have a Class A output to contend with.

Touching the fins to confirm our nose, we snatch fingers back with a howl and, sucking them, muse that the problem could not have been temperature at all. And the fuse still holds.

Obviously, TED has been at work. He is only waiting for us to settle comfortably with a book and a glass at our elbow before blowing the fuse again. Or, more likely, lulling us into a false sense of security, will allow us the whole evening's listening, then, while we sleep through the small CQ hours, will sneakily contract that vulnerable thread of wire again so that rising betimes, we gaily throw the switch and get: silence!

TED is no fool. That Post Office bloke urged 'sweet reasonableness' upon subscribers when their lines were crossed. The inference was that if we pretended not to notice the fault it would go away. Any PW reader could have told him that is the wrong approach.



. . . and we snatch our fingers back with a howl.

How many times have you had a piece of equipment propped up on the bench, festooned with test leads, bedizened with warning lights, burbling away in the corner of your mind, and leaped into the breach as the expected fault occurs, only to be greeted with a return to normality the moment you touch the chassis?

Tracking down TED is the work of an expert. One tests piecemeal. One uses not sweet reasonableness, but bitter reason. Diagnosis, as our soon-to-finish series on Servicing has emphasised, is the secret of success. And for *diagnosis*, where TED is concerned, read *inspired guesswork*. This is where LID comes in. LID is one of those contractions I am no longer likely to forget, since talking to Bob Stockwell, publicity manager of Bang & Olufsen, the day after an exhausting exhibition.


'How do you manage to organise it?'

'It's not easy,' he said, *'but we begin by catering for the Largest Imaginable Disaster and take it from there. . . .'*

That is the secret of dealing with TED. Put the LID on him: when the fuse blows, imagine the worst that could happen and assume that it has! But don't try to telephone the repairman—you will probably get the laundry company again.



# electronics mastered!\*

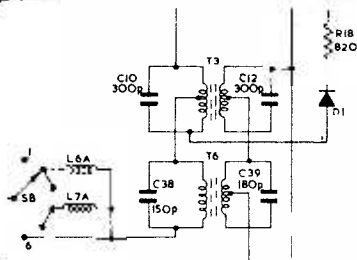

by our highly practical  
**BUILD, SEE & LEARN** system

Step by step we take you through the apparent intricacies of electronics and show you how easily you can master the subject. Write for the brochure which shows, in full detail, how you can do it.

**1**

We provide a full range of components and sub-assemblies, with details of what they do, so that you learn to recognise all the 'bits and pieces'. Using some of these you are instructed in how to build this oscilloscope, simply and quickly.



**2**

You are shown how to read and understand circuit diagrams so that you can later build more advanced equipment or draw your own diagrams.

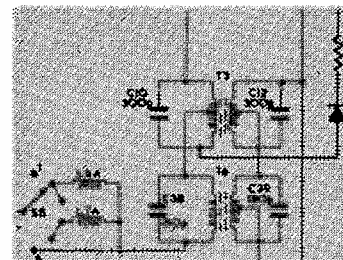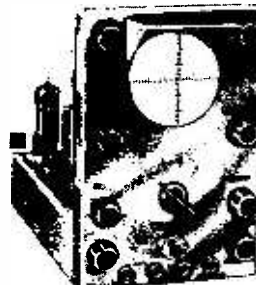**3**

You can construct over 40 kits, including:—

- Valve experiments
- Transistor experiments
- Amplifiers
- Oscillators
- Signal tracer
- Photo electric circuit
- Computer circuit
- Basic radio receiver
- Electronic switch
- Simple transmitter
- a.c. experiments
- d.c. experiments
- Simple counter
- Time delay circuit
- Servicing procedures



This course has been designed to help even those who are complete newcomers to electronics. **No Maths needed!**

**POST NOW  
FOR  
FREE BROCHURE**

BLOCK CAPITALS PLEASE

To: **British National Radio School, Reading, Berks.**

Please send your free Brochure, without obligation, to:

NAME

ADDRESS

P10/71

**FREE**

**SPECIAL ELECTRONIC GIFT  
to all our Students POST COUPON NOW!**

# ELECTRONIC VALVES

0A2	0-88	6L7GT	0-85	DY87	0-85	PC88	0-55
0A3	0-45	6F9GT	0-85	EF82	0-60	PC89	0-60
0B2	0-35	88Q7	0-40	EB8C3	0-65	PC89	0-55
0B3	0-60	68R7	0-40	EL80F	0-95	PC8065	0-85
0C3	0-58	6T8	0-35	EB10F	0-90	PC8066	0-80
0D3	0-35	6U4GT	0-60	EAB2C8	0-35	PCF80	0-30
138GT	0-38	6V8A	0-40	EAF42	0-55	PCF82	0-35
1CP31	0-60	6X6T	0-38	EB8C33	0-50	PCF84	0-60
1R4	0-20	6BC41	0-65	EB841	0-55	PCF87	0-80
1R4	0-85	6K5GT	0-85	EB8C81	0-50	PCF87	0-85
1R5	0-35	6K5	0-55	EBF80	0-40	PCF801	0-50
1S4	0-27	6Y6G	0-65	EBF83	0-40	PCF802	0-50
1S5	0-26	7Y4	0-60	EBF89	0-30	PCF805	0-75
1T4	0-25	9BW6	0-60	EC53	0-50	PCF806	0-70
1U4	0-27	10C1	0-50	EC86	0-60	PCF806	0-75
1U5	0-60	10D1	0-50	EC60	0-60	PCF806	0-70
1V2	0-45	10D2	0-40	EC90	0-38	PCL81	0-50
1X2B	0-40	10F1	0-60	EC91	0-50	PCL82	0-55
2D21	0-35	10F9	0-50	EC92	0-35	PCL83	0-65
3A4	0-35	10F18	0-45	EC93	0-50	PCL84	0-45
3Z8	2-15	10L1	0-45	EC8010	2-25	PCL85	0-40
3ZF1	2-75	10LD11	0-60	EC8011	2-40	PCL86	0-45
3Q4	0-40	10P13	0-55	EC831	0-38	PCL88	0-90
384	0-55	10P14	1-10	EC82	0-30	PCFL80	0-98
3V4	0-45	12AB5	0-60	EC83	0-30	PCFL801	0-70
5B4GY	0-60	12AC8	0-40	EC84	0-30	PD500	1-50
5Y4G	0-35	12AL5	0-45	EC85	0-40	PR86	0-60
5U4G	0-35	12AQ3	0-45	EC86	0-40	PR88	0-85
5V4G	0-40	12AT8	0-45	EC89	0-60	PFL200	0-70
5Y3GT	0-32	12AT7	0-38	EC91	0-90	PL3	0-85
5Z3	0-50	12AU6	0-30	ECC189	0-60	PL36	0-65
5Z4G	0-40	12AU7	0-30	ECC80	0-35	PL81	0-50
6/30L2	0-75	12AV6	0-38	ECCF82	0-35	PL82	0-45
6AD4	0-25	12AV7	0-50	ECCF86	0-65	PL83	0-45
6AD4A	0-25	12AX7	0-80	ECCF84	1-50	PL84	0-40
6AG7	0-40	12AX7	0-70	ECH42	0-70	PL302	0-80
6AH6	0-50	12BA4A	0-65	ECH81	0-30	PL504	0-80
6AJ2	0-30	12BA6A	0-35	ECH83	0-40	PL508	0-90
6AK5	0-30	12BA7	0-35	ECH84	0-45	PL509	1-30
6AK6	0-57	12BE6	0-35	ECH90	0-40	PL801	0-80
6ALS	0-43	12BH7	0-40	ECL1	0-45	PM84	0-50
6AL5	0-35	12BX7	0-35	ECL2	0-45	PM84	0-50
6AM5	0-32	12K5	0-55	ECL83	0-45	PY83	0-38
6AM6	0-38	12K7GT	0-38	ECL84	0-55	PY80	0-35
6AQ5	0-35	12Q7G	0-30	ECL85	0-55	PY81	0-30
6AQ6	0-55	12R7	0-35	ECL86	0-40	PY82	0-30
6AR5	0-35	1487	0-80	ECL89	0-60	PY83	0-38
6AR6	0-40	14D1	0-60	ECL89	1-50	QY81	0-40
6AR11	1-25	20L1	1-10	EF73A	0-60	PY800	1-50
6AS5	0-35	20P1	0-50	EF87A	0-40	PY801	0-50
6AS7G	0-30	20P4	1-10	EF40	0-50	PY801	0-50
6AT6	0-30	20P5	1-20	EF41	0-65	PZ80	0-35
6AU5	0-25	25C5	0-30	EF42	0-70	QQV2-6	2-15
6AV6	0-30	25L6GT	0-45	EF80	0-25	QQV8-10	2-25
6AW8A	0-55	25Z4G	0-60	EF83	0-35	QQV8-10	2-15
6BA4	0-25	25Z6GT	0-65	EF85	0-35	QQV3-20A	3-55
6BE6	0-30	30A5	0-45	EF86	0-30	QQV3-20A	3-55
6BF5	0-30	30AE3	0-40	EF89	0-28	QQV6-4A	5-50
6BF6	0-50	30C1	0-30	EF91	0-33	TT21	2-65
6BH5	0-45	30C15	0-80	EF92	0-40	TT22	2-85
6B7B	0-45	30C17	0-45	EF95	0-30	U18/20	2-75
6BK7A	0-55	30C18	0-75	EF97	0-65	U25	0-75
6BN6	0-43	30F5	0-85	EF98	0-65	U26	0-75
6BQ6	0-25	30FL1	0-70	EF183	0-30	U31	0-45
6BQ5	0-25	30FL12	0-98	EF184	0-35	U37	1-50
6BR8	0-65	30FL14	0-75	EF800	1-00	UT2	0-85
6BS7	1-30	30L7	0-45	EF804	1-25	UT2	0-85
6BW6	0-55	30L15	0-85	EK90	0-30	U76	0-30
6BX6	0-25	30L17	0-80	EL33	1-25	U78	0-30
6BX6	0-25	30P12	0-80	EL34	0-50	U191	0-75
6BX6	0-25	30P19	0-80	EL36	0-50	U201	0-85
6C4	0-38	30FL11	0-70	EL37	1-25	U281	0-40
6C5GT	0-45	30FL13	0-85	EL38	1-50	U32	0-40
6CB6	0-30	30FL14	0-90	EL42	0-68	U801	0-40
6CD6A	1-15	35A3	0-55	EL81	0-55	U403	0-50
6CQ7	0-50	35A5	0-75	EL82	0-42	U404	0-40
6C86	0-55	35B5	0-65	EL84	0-25	U801	1-30
6CLO	0-50	35C5	0-40	EL85	0-48	UACB80	0-85
6CW4	0-80	35D5	0-60	EZ86	0-50	UAF1	0-50
6CXY5	0-45	35L6GT	0-50	EL90	0-35	UAF42	0-55
6C7	0-68	35W4	0-30	EL96	0-85	UBC41	0-50
6D3	0-45	35Z3	0-30	EL803	1-00	UBC81	0-40
6D6G	0-75	35Z4G	0-60	EL821	0-55	UBF80	0-40
6D8	0-45	35Z6GT	0-40	EL822	0-90	UBF89	0-35
6DQ6B	0-65	35A5	0-50	EZ86	0-75	UBLA	0-50
6DS4	0-75	50R5	0-45	EM34	0-90	UBL21	0-60
6EA8	0-58	50C5	0-40	EM71	0-75	UC92	0-35
6ER7	0-60	50CD6G	1-65	EM80	0-40	UC85	0-40
6EJ7	0-35	50L6GT	0-50	EM81	0-80	UCF80	0-55
6FV6	0-55	85A2	0-40	EM84	0-35	UCM21	0-60
6F1	0-70	90A6	2-40	EM85	1-00	UCF42	0-70
6F5	0-50	90AV	2-50	EM87	0-55	UCH43	0-75
6FG6	0-30	90C1	0-60	EN91	0-85	UCH81	0-35
6F11	0-38	90CV	1-25	EY61	0-40	UCL81	0-60
6F13	0-38	807	0-50	EY80	0-45	UCL82	0-35
6F14	0-65	813	3-75	EY81	0-40	UCL83	0-80
6F15	0-85	809B	0-50	EY83	0-55	UFA1	0-60
6F18	0-45	5642	0-65	EY86	0-40	UFA2	0-60
6F23	0-80	6080	1-50	EY87	0-43	UFA3	0-65
6F24	0-75	6146	1-50	EY88	0-43	UFS8	0-80
6F25	0-75	6386	1-25	EZ40	0-45	UF85	0-40
6F26	0-35	6870	2-50	EZ41	0-45	UF89	0-35
6F28	0-60	7199	1-15	EZ50	0-85	UL41	0-60
6J4	0-30	7199	0-75	EZ51	0-28	UM84	0-30
6J5GT	0-80	7360	1-80	GY501	0-80	UM84	0-20
6K7	0-45	7586	1-25	GZ30	0-40	UY1N	0-50
6K6GT	0-55	7885	1-25	GZ31	0-33	UY11	0-65
6K7	0-35	9002	0-35	GZ32	0-48	UY41	0-45
6K6G	0-55	9003	0-50	GZ33	0-70	UF83	0-60
6K25	0-75	AZ1	0-48	GZ34	0-60	UY86	0-30
6L6GT	0-45	AZ31	0-55	HABC80	0-40	WT29	0-60
6L7	0-40	CB11	0-80	HK90	0-35	ZT59	1-85
6L18	0-45	CB13	0-90	KT66	2-05	Z803U	0-90
6LD20	0-40	CY31	0-35	KT88	2-00		
6N7GT	0-40	DAF96	0-42	N78	1-45		
6P4	0-60	DF96	0-42	PACB60	0-40		
6P25	1-25	DK40	0-55	PC86	0-60		
6P28	0-65	DK92	0-50	PC88	0-60		
6Q7	0-40	DK96	0-42	PC97	0-50		
68A7	0-40	DL96	0-42	PC90	0-48		
68G7	0-35	DM160	0-65	PC84	0-40		
68K7	0-35	DY86	0-38	PC85	0-40		

# STEPHENS

ELECTRONICS  
P.O. BOX 26  
AYLESBURY, BUCKS.

SEND S.A.E. FOR LISTS GUARANTEE:- Satisfaction or money refunded.  
TERMS CASH WITH ORDER ONLY. ALL ITEMS ADVERTISED IN LAST POST AND PACKING PAYABLE MONTH'S ISSUE ALWAYS IN STOCK FOR SAME DAY DISPATCH  
ON ORDERS UP TO £6, AFTER THAT FREE, EXCEPT C.R.T.'s

### SEMICONDUCTORS BRAND NEW MANUFACTURERS MARKINGS NO REMARKED DEVICES

2N388A	62p	2N3702	17p	ACY18	25p	AF127	17p	BC184	22p	BFY52	22p
2N614	30p	2N3704	22p	ACY19	25p	AF139	37p	BC187	22p	B8X21	37p
2N697	20p	2N3705	20p	ACY20	25p	AF178	45p	BC23L	22p	OC25	25p
2N698	20p	2N3711	20p	ACY21	25p	AF179	45p	BCY32	37p	OC26	32p
2N706	12p	2N3819	35	ACY22	20p	AF180	52p	BCY58	22p	OC28	62p
2N706A	12p	2N3826	30p	ACY28	20p	AF181	42p	BCY70	20p	OC29	75p
2N706B	12p	2N3895	37p	ACY40	20p	AF186	66p	BD115	78p	OC35	40p
2N739	32p	2N3914	P.A.	ACY41	25p	AF239	42p	BD129	82p	OC42	25p
2N1132	27p	R.C.A.	47p	ACY74	40p	AS728	25p	BD132	82p	OC44	30p
2N1303	17p	R.C.A.	47p	ACY74	40p	BC107	15p	BD132	82p	OC45	32p
2N1305	25p	40253	P.A.	AD140	40p	BC109	15p	BD132	82p	OC46	15p
2N1306	25p	40298	P.A.	AD142	58p	BC108	15p	BD131	87p	OC45	15p
2N1307	25p	40454	P.A.	AD149	57p	BC109	15p	BD132	82p	OC46	15p
2N1711	25p	2N4061	22p	AD150	62p	BC113	27p	BF115	25p	OC70	15p
2N1747	78p	2N4082	22p	AD161	37p	BC114	37p	BF117	47p	OC71	12p
2N2160	57p	2N4286	17p	AD162	37p	BC115	32p	BF180	P.A.	OC72	12p
2N2614	30p	2N4281	17p	AF102	85p	BC116	62p	BF181	P.A.	OC74	32p
2N2646	57p	AC107	30p	AF106	42p	BC116A	37p	BF188	P.A.	OC75	22p
2N2905	40p	AC117	80p	AF114	25p	BC117	39p	BF187	25p	OC76	22p
2N2926	40p	AC126	20p	AF115	30p	BC118	32p	BF173	32p	OC77	27p
Green	12p	AC127	25p	AF116	25p	BC134	57p	BF178	35p	OC78	25p
Yellow	12p	AC128	20p	AF117	25p	BC135	P.A.	BF179	72p	OC81	20p
Orange	12p	AC154	25p	AF118	60p	BC136	P.A.	BF180	85p	OC81D	20p
2N3053	27p										

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

**T**HE first report this month comes from a new reporter D. A. Hairon from Jersey in the Channel Islands. The equipment used was a Codar CR70A receiver, a 50ft long wire and a 19 metre band dipole. This combination enabled him to hear the following stations:—

- 9480 Radio Peking in English at 0130.
- 9625 CBC, Canada in English at 0200.
- 11710 R. Nacional de Espana in Spanish at 0130.
- 11720 CBC, Canada in English at 0200.
- 11730 R. Nederland, Bonaire, English at 0200.
- 11745 HCJB, Quito, Ecuador, English at 0000.
- 11775 TWR, Bonaire in Spanish at 0215.
- 11810 RAI, Rome in English at 0100.
- 15195 R. Ankara, Turkey, Turkish at 1600.
- 15250 RSA, South Africa in French at 1856.
- 15300 HCJB, Quito, Ecuador in Spanish at 2145, and in Portuguese at 0000.
- 15305 SBC, Switzerland in English at 1315.
- 15345 Radio Kuwait in English at 1630.
- 15355 ABC, Australia in English at 0530.
- 17655 R. Cairo, U.A.R. in English at 1730.
- 17715 ABC, Australia in French at 2315.
- 17810 R. Nederland, Bonaire in Spanish at 2130.
- 17830 R. Lebanon in English at 1830.
- 17825 NHK, Japan in English at 0800.
- 21525 WNYW, U.S.A. in English at 1800.
- 21640 R. Nederland, Bonaire, English at 1830.
- 25730 R. Norway in English at 1200.

Ray Warren of Bury St. Edmunds has used his Koyo 1661 receiver to good effect and heard the following:—

- 3980 Voice of America in English at 1720.
- 5970 R. Free Europe, Germany at 1450.
- 6075 WNBC, New York, news at 1630.
- 6085 R. Nederland in English at 0930.
- 9030 R. Peking in English at 2050.
- 9390 R. Tirana, Albania in English at 1530.
- 9750 SBC, Switzerland, news in English, 1540.
- 15300 HCJB, Quito, Ecuador, English news, 1410.

Peter Hall of Pocklington, Yorkshire, has a Meridian 10 transistor superhet and a 50 foot aerial which enabled him to hear:—

- 6070 R. Sofia, Bulgaria in English at 1930.
- 6130 HCJB, Quito, Ecuador in English at 0800.
- 7275 RAI, Rome in English at 1940.
- 9550 Radio Finland in English at 1815.
- 9580 BBC, Ascension Island relay at 2115.
- 9620 R. Belgrade, Yugoslavia at 1800.
- 9625 Israel B.C. in English at 2045.
- 9630 R. Trans Europe, Portugal at 2100.
- 9700 R. Sofia, Bulgaria in English at 2140.
- 11620 AIR, Delhi in English at 2010.
- 11672 R. Pakistan in English at 2030.

## THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

- 11755 R. Finland in English at 0930.
- 11915 BBC, Cyprus relay at 1645.
- 11965 TWR, Monaco in English at 1700.

Ross Pullen of Crawley used his Murphy A72 communications receiver and a 100 foot long-wire to hear some interesting stations:—

- 6015 VOA, Rhodes, music and talk at 2200.
- 6145 R. Nacional, Brazil in Spanish at 2245.
- 9510 R. Noumea, New Caledonia, French at 0910.
- 9605 HCJB, Quito, Ecuador, English at 0730.
- 9745 R. Baghdad, Iraq in English at 2015.
- 9775 R. Diffusion-Television Nationale Congolaise, African music at 2200.
- 11672 R. Pakistan, English at 2002.
- 11965 Rwanda relay of Deutsche Welle at 2037.
- 17705 R. Havana, Cuba, Spanish news at 2015.

F. Wall of Walthamstow, London, E.17, has a homebrew 5-valve superhet and a 20 foot wire aerial, this equipment enabling him to hear:—

- 6035 R. Warsaw with Polish news at 1620.
- 6070 R. Sofia, Bulgaria in English at 1930.
- 9912 AIR, Delhi English news at 2000.
- 9630 R. Sweden 'Calling DXers' at 1230.
- 9660 R. Trans Europe in English at 1250.
- 9833 R. Budapest, Hungary, requests at 1945.
- 11735 R. Belgrade, Yugoslavia, English at 1530.
- 11740 ABC, Australia at 1530.
- 11755 R. Finland in English at 1500.
- 11765 ABC, Australia, sports programme at 0830.
- 11955 BBC, Malaysian relay at 1815.
- 15325 CBC, Canada, sports news at 1200.
- 21460 HCJB, Quito, Ecuador sign-on in French at 2015.
- 21535 RSA, South Africa, English news at 0930.
- 21595 CBC, Canada with news at 1910.
- 25790 RSA, South Africa, English news at 1500.

Stephen Mathews of Hull with his Bush 4-valve domestic receiver and 90 foot loft aerial heard the following:—

- 9660 YVLM Radio Rumbos, Venezuela at 0320.
- 9833 R. Espana Independiente, clandestine at 2230.
- 11765 ZYB8, R. Diffusion, Brazil at 0220.
- 11795 WINB, Red Lion, U.S.A. English at 2100.
- 11815 ZYW24, R. Brazil Central at 0045.
- 15260 FEBA, Seychelles testing at 1700.
- 17890 BED-40, Taiwan, weak at 0330.
- 21690 WIBS, Grenada in English at 1945.
- 21720 R. Ghana in English at 1445.

Reports should arrive by the 15th of the month and be addressed to the author at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

# SHORT WAVES

## THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

**H**IGH noise levels have been the main complaint this past month with many people confessing to giving up and going off to watch television (sacrilege!). Despite these conditions there was still a large number of listeners who persisted, despite the noise, and managed to log some worthwhile DX as reward for their labours. Just goes to show, while you are busy moaning about the QRM and QRN, someone else is just getting on with it and working half the world.

News that G5ZT has received slow-scan television pictures from FG7XT in Guadeloupe makes you think. Many people would be only too pleased to hear an FG7 on c.w. **John Rimmer** (Deal) warns that VS9MF is on from Gan—a small island in the Maldive group of islands. Listen on 14 and 21MHz; sorry, no specific freqs given.

No activity reported on ten metres this month and it rather looks as though everyone has migrated to 14MHz. This latter band is an early morning/late night affair nowadays with everything dying out from mid-morning to late afternoon. On fifteen metres the same remarks apply, although occasionally South American stations appear during the daytime. For those who would like to persist on 28MHz, suggested time for a listen is from 1400 to 1600hrs.

Incidentally, this is one of the best bands on which to play with aerials since these normally work out to a very reasonable size. A quarter wave vertical is only around the 8ft. 6in. mark, exact size depending upon frequency since ten metres is one of the widest bands we have among those l.f. of 144MHz. If sunspot counts are any indication, then September would be a very good time for ten metres.

A few contests this month just to get your ears in trim for the long winter evenings. September 11 and 12, WAE phone contest; 12, 3.5MHz Field Day; October 2 and 3, u.h.f./s.h.f. Field Day; 2 and 3, Oceania contest—a chance to bag a nice list of VK/ZL callsigns; 2 and 3, IARU Region 1 u.h.f./s.h.f. contest. Don't forget the Cumulative Activity on 70MHz from October 9 to December 30. This is our "use or lose" band and all support is very welcome, if not essential. You might try listening for some of the RAEN activity on four metres. The Radio Amateur Emergency Network has numerous "local" groups and the favourite band is 70MHz. How about listening out for your local group, or perhaps even joining them? Name and address of the Secretary of RAEN is; E. Bassett, 57 Upper St Helen's Road, Hedge End, Southampton, SO3 4LG.

## Logs

A solitary log for two metres arrived this month from **David Sheekay** (Ashford). Gear is a super-regen using three transistors and an i.c. audio amplifier, homebrew, and antenna is described as "telescopic". Stations logged include; G2JF, G2VB, G3EFX/P, G3JXN, G3LTF, G3TDP/M, G3UNT,

G4AAR, G4AAZ/M, G5OX, G8BYC, G8CCO, G8EBV, G8ELW and F0UJ. What about it all you converter and superhet types—you can't let a super-regen show you up, or can you?

**Richard Mortimore** (Cardiff), is now up to 20 w.p.m. at c.w. and says that he recommends all s.w.l.s to learn morse. Small sample from his list of c.w. pickings on 21MHz includes; CR6ID, JA3IL, KZ5BB, PY2EYE, PY4UK, W4NZK, WB4QVQ.

**Mark Marsden** (Ilford) uses a cassette tape recorder which has its input wired in parallel with the headphones. He claims this is very useful for checking calls heard against calls logged afterwards. Seems a very good idea. Calls heard, checked, recorded and logged on 14MHz include signals from; CE5ID, JA3JH, KV4HE, KZ5JF, PY2ZAC, PY4AEB, SV0WZ, VK3ART, VK4PJ, VP2AA, WA1DYR/MM, WB6YIY/MM, YV5CPA, YN2SC, ZL5ISJ, 4X4JU, 4X4OC, 9Q5IA.

"My uncle has given me all the PWs he can spare", writes **Kevin Davies**. Receiver is an R107 and the antenna 120ft. l.w. The following were in evidence on 14MHz s.s.b.; CT1ZE, EA3KO, EA4LM, EL2C, EL4A, HR3VSJ, JA1VK, K1WPS/CT1, LU4DMG, W1CMG/P1, W1MYA/MM, WA5KHM, WB6YIY, 4U1ITU, 4X4HT.

**Paul Newman** is at a new QTH which is some 680ft. a.s.l. Antenna at present is an 80ft. end fed and the receiver a modified BC348R ex G3HXS. With this gear, and from his lofty perch at Aylesbury, Paul bagged these on 14MHz; OD5BV, PY6AT, PY8LM, (Sao Luis Island), WA5STY/P/YV5 (Caracas) 4X4BL, 4X4GV, 5Z4KL, 9K2AL.

**Jim Martin** says that as it's the start of his holidays he thought he'd send in a report. (May the sun shine on your antenna, Sir.) His recently-purchased HA500 is nourished with an inverted V and rewards on 14MHz were; CR6EF, CR7IK, EL2CY, FP8CS, HC6CB, JA3IXL, JA4EDY, JA6FUV, JY9XL, KG4AN, KH6FP, KH6BB (Kure Island), KL7DIV, KR6US, KV4AD, KZ5AO, LG5LG, MP4MBC, PY1FN, PJ2MI, PZ1AD, PZ1AW, TG9GF, VK3JS, VP2MO, VQ9R, VS5CB, VS9MT, VU2BEZ, YV5EC, ZE1DO, ZP5GU.

On 3.5MHz c.w. it was UA1YUZ. Up on 7MHz, signals came from CX6CG, LX1BJ, PYCVX, PZ1AX, UW3NG, ZB2A, and ZP5AR. Gear is a JR500SE with 132ft. end fed. Operator's ears belong to **Julian Iredale** (Llandudno), and up on 14MHz s.s.b. Julian heard CR6GA, HV3SJ, OG5A, (Finnish Field Day prefix), PY2ZAC, PY4ATL, PZ1DL, TI2J, 5A4DL.

**P. McKay** advises that he never notices any logs for 7MHz in the Amateur Bands, and sends in a list of G-stations heard on this band. Well, the G's must have been working someone, so how about a listen this month?

*Logs, in alphabetical order please, to arrive by the 15th of the month to:*

**12, Cross Way, Harpenden, Herts.**

# BUDGET HIGH-FIDELITY STEREO SYSTEMS



**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 2000 amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off. Solid teak cabinet with aluminium front panel. Size 12 1/2" x 4 1/2" x 3 1/2" high (Amplifier available separately if required £14.95 Carr. 40p).  
**PREMIER STEREO SYSTEM "TWO"**, as above but with Garrard SP25 MK III—ONLY 247. Carr. £1.75

**ONLY £40-95**  
carr. £1.75

**ONLY £57-75**  
carr. £1.75

**PREMIER STEREO SYSTEM "THREE"** This consists of KLINGER KC908 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pickup, tuner, tape in and out. Stereo earphone socket. Garrard SP20 Mk III in teak finish plinth with cover and fitted Sonotone 9TAHC diamond stereo cartridge. A pair of HMF Speakers size 16 1/2" x 10 1/2" x 9" fitted EMI units complete the matching system.  
**ONLY £67-75 Carr. £1.75**

ALL SYSTEMS SUPPLIED WITH FREE LEADS AND PLUGS

## PREMIER HI-FI OFFERS!

- Rogers Ravensbrook II Stereo Amplifier in teak case (List £52.50) **£39.50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49.00**
- Metrosound ST20 Stereo Amplifier in teak case (List £36) **£24.50**
- Garrard SP25 III less cartridge **£11.90**
- Garrard AP76 **£19.50**
- Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£8.97**

### SPECIAL BARGAINS!

- Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£14**
- Carriage and Insurance 50p extra any item.

## SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED AT66 MAGNETIC STEREO CARTRIDGE as available. COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER.  
 Total list price over £29.

PREMIER PRICE **£19.90**  
P. & P. 50p.



### HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 8ft lead and stereo jack plug.

**£2.47 P. & P.**

STEREO STETHOSCOPE SET Low Imp. £1.25 P. & P. 10p  
 MONO STETHOSCOPE SET Low Imp. 52p. P. & P. 10p.



### E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2 1/2in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new.

**£3.47 P. & P. 40p**

## PREMIER QUALITY MICROPHONES



Precision made, beautifully designed and offering reliability at reasonable price.

**FANON MKO-47 MINIATURE DYNAMIC**  
 Frequency response 60-13,000 Hz. Impedance 50K ohms (-89 db). Can be used with stand, hand held or around neck. Diecast body satin chrome finish. Features removable windscreen. Complete with 8ft. cable, stand adaptor and Lavalier cord.  
**PREMIER PRICE £5.97. P. & P. 20p.**

**FANON MKO-46 3-WAY DYNAMIC**  
 Frequency response 100-10,000 Hz. High impedance. Complete with 8ft. cable, and table stand.  
**PREMIER PRICE £2.97. P. & P. 20p.**

**FANON MKC-54 DYNAMIC**  
 Frequency response 60-12,000 Hz. Impedance 50K ohms (-60 db) and 150 ohms (-71 db). On/Off switch. Complete with 20ft. cable and stand adaptor.  
**PREMIER PRICE £8.97. P. & P. 20p**



### TAPE CASSETTES

C60	(60 min.)	37p	3 for £1.05
C90	(90 min.)	62p	3 for £1.80
C120	(120 min.)	87p	3 for £2.55

P. & P. 5p.

**FREE CASSETTE HEAD CLEANER** with every 10 cassettes purchased.

All cassettes can be supplied with library cases at 3p. extra each

### VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2in. suitable for crystal microphone, low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono-plugs output. Attractive teak wood grain finish case.



MONO MODEL **£3** STEREO MODEL **£3.47** P. & P. 12p



**MULTIMETER 20,000 O.P.V.**  
 Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size: 4 1/2" x 3 1/2" x 1". RANGES D.C. Voltages 0-5-25-50-250-500-2500v. A.C. Voltages 0-10-50-100-500-1000v. D.C. Current: 0-50uA-2.5mA-250mA. Resistance: 0-5000 ohms 0-6 megohms (300 ohms and 20 Kohms, at centre scale). Capacity: 10 µf to .001µf, .001µf to .1µf. Labels -20 to +22dB. **£4.90. P. & P. 17p.**

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LPS 3'	250'	P.V.C.	25p	51'	1200' POLYESTER	75p
TT3 3'	450'	POLYESTER	37p	DT6 6'	1800' POLYESTER	£1.12
DT3 3 1/2'	600'	POLYESTER	57p	TT5 5'	2400' POLYESTER	£1.87
SP5 5'	600'	P.V.C.	42p	SP7 7'	1200' P.V.C.	62p
LP5 5'	900'	P.V.C.	50p	LP7 7'	1800' ACETATE	75p
DT5 5'	1200' POLYESTER	75p	DT7 7'	2400' POLYESTER	£1.25	
TAPE SPOOLS 3" 5p, 5" 5 1/2" 7" 9p,	TT7 7'	3800' POLYESTER	£2.50			

Post and Packing 3" 5p, 5" 5 1/2" 7" 9p, 7" 10p. (3 reels and over Post Free).



# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639  
 HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



# TECHNICAL TRAINING

## in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
  - Radio Amateurs' Examination
  - Radio Operator Certificates
  - General Certificate of Education, etc.
- Now available Colour T.V. Servicing


Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
EST. 1891

Dept. 171, Intertext House, Stewarts Road, London, S.W.8 4UJ  
Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam).....

NAME .....  
(BLOCK CAPITALS PLEASE)


ADDRESS .....

AGE..... OCCUPATION..... 10/71

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

<b>OSCILLOSCOPES</b>	
E.M.I. WM18. Complete with Dual Trace Plug-in Amp/Differential Plug-in Amp.	£175
SOLARTRON CD.1220. With Wide Band Unit	£190
SOLARTRON CD.1220. With Dual Trace Unit	£220
SOLARTRON CD.1220. With Differential Amp Unit	£240
SOLARTRON CD.711S.2. Double Beam.	£80
CAWKELL REMSCOPE S.O.L. Storage Oscilloscope	£200
E.M.I. W.M.8. Complete with Amplifier Type 8	£55
<b>TEST GEAR</b>	
WAYNE KERR. Universal Bridge Type B.221	£65
MARCONI. Q Meter Type TF 329G	£45
MARCONI. Video Oscillator Type TF 885A 25HZ-5MHZ	£45
MARCONI. Vacuum Tube Voltmeter TF 1041A.	£80
MARCONI. FM/AM Signal Generator TF995A/4	£175
POWER UNIT. 240V. a.c. 1/F.D.C. Output 400V 170mA/6-3V 3A.	£10
R.F. GENERATOR. 200 Mc/s. 275 Watts	£25
R.F. GENERATOR. 25 Watts	£15
SERVOMEX CONTROLS LTD. Motor Controller Type MC47 Complete with Motor	£65
<b>T.V. CAMERA LENSES</b>	
RANK TAYLOR HOBSON VIDITAL LENSES. Standard -C" Mounts. Focal lengths 2cm, 5cm, 8cm	£25 each
R.C.A. AR88. Receiver	£40
<b>MINIATURE GEARED MOTORS</b>	
1 R.P.M. HAYDEN. 240V a.c. Clockwise Rotation	} .. 80p each
1/5 R.P.M. CROUZET. 240V a.c. Anticlockwise Rotation	
2 R.P.M. CROUZET. 20V a.c./12V d.c. Anticlockwise Rotation	
<b>RELAYS</b>	
SIEMENS/VARLEY PLUG-IN. Complete with Transparent Dust Cover	
2 Pole C/O 35p each. 4 Pole C/O 50p each	
S.T.C. Miniature Sealed Relays. 6V, 12V, 24V, 48V. 2 Pole C/O	50p each
G.P.O. Relays, 2000Ω. 2p C/O 50p. 4p C/O 60p each	
HEAVY DUTY. Relays 5A and 10A Contacts 12V, 24V, d.c. 110V, 240V a.c.	
2p. C/O	90p each
LATCHING RELAYS. B. & R. Type HO2/T498 2p. C/O	95p each
<b>SOLENOIDS</b>	
12V. d.c. 2 1/2" x 1 1/4" Dia.	50p each
<b>WIRE WOUND POTENTIOMETERS</b>	
COLVERN. RELIANCE. All Values from 1Ω-100K Ω. Brand New	19p each
360° WIRE WOUND POTS. COLVERN CLR/6605/418 10K Ω	} £1.50 each
CLR/6605/ 18 100K Ω	
BOURNS. 10 Turn Pots. 10K Ω ± 5% LIN 0-25%	£1.98 each
<b>ILLUMINATED PUSH BUTTON SWITCHES</b>	
Non-Locking Only. 2p C/O	35p each
<b>PUSH BUTTON SWITCHES</b>	
Multibank Push Button Switch assemblies now in Stock. Any combination, latching, non-latching, push-push, push to change over, push to hold etc.	
2p. C/O	20p per button.
4p. C/O	30p per button.
6p. C/O	40p per button.
<b>MULTIPIN PLUGS AND SOCKETS</b>	
PAINTON/JONES 2/4/6/8/12/18/24/33 Way.	
P.E.T., B.N.C., AMPHENOL, CANNON, D.I.N., Plus Complete Audio Range.	
<b>TRANSFORMERS</b>	
D. C. TIBBLES & CO. PRI. 0-100-110-220-240V. SEC. 12V. 20A	£6-50 each
MINIATURE TRANSFORMERS. PRI. 240V SEC 12V 100mA	} All Types 65p each
2" x 1 1/4" x 1 1/4"	
PRI. 240V SEC 0, 20V, 30V 100mA	
PRI. 240V SEC 0, 18, 36, 0, 18, 36 100mA	
SHROUDED TRANSFORMERS. PRI. 0-120-240V SEC. 24V 1A	£1-25 each
PRI. 0-240V SEC 20V 1A	£1-60 each
C-CORE TRANSFORMERS. PRI. 240V SEC 0, 7.5, 15V 1A	£1-20 each
HEATER TRANSFORMERS. PR. 0-110-200-220-240 SEC 6-3V 3A	£1-00 each
<b>ALARM BELLS</b>	
Suitable for Burglar Alarms. AGRO Type 4145 200/250V a.c.	£3-50 each
<b>PANEL METERS</b>	
SIFAM MOVING COIL 1mA Size 4 1/2" x 4"	£3-25 each
SIFAM MOVING COIL 100μA Size 3 1/2" x 3"	£3-00 each
TAYLOR MOVING COIL 50-0-50μA Edgewise 2 1/2" scale	£4-25 each
ERNEST TURNER 270° Movement/Centre zero Circular 0-5-0-0-5 mA	} £3-00 each
2 1/2" Dia.	
ERNEST TURNER 270° Movement/Centre zero Circular 1-0-1mA	} £4-25 each
3 1/2" Dia.	
SANGAMO-WESTON ILLUMINATED METER 500μA F.S.D. 4 1/2" x 3 1/2"	£3-90 each
SANGAMO WESTON. 50μA F.S.D. 4 1/2" x 3 1/2"	£4-75 each
We also have a large number of assorted meters of different shapes/sizes/movements in stock.	
<p style="text-align: center;"><b>SOUND-TO-LIGHT MODULES SUITABLE FOR DISCO THEQUES ETC.</b></p> <p>SINGLE CHANNEL 750 Watt Model .. .. . £8-00 each</p> <p>THREE CHANNEL MODEL .. .. . £18-00 each</p> <p>150W. LIQUID OIL WHEEL PROJECTORS COM- PLETE WITH WHEEL .. .. . £35-00 each</p> <p>EXTRA WHEELS 6" Dia .. .. . £6-00 each</p>	
<b>COMPONENTS</b>	
METAL OXIDE RESISTORS. 2%. T.R.5 Complete Range always in Stock. 1 off 5p each. 100 off 8 1/2p each.	
MULLARD ELECTROLYTIC CAPACITORS. Complete Range always in stock.	
MULLARD POLYESTER CAPACITORS. Complete Range always in Stock.	
LEMCO SILVER MICA CAPACITORS. Complete Range always in Stock.	
POLYSTYRENE CAPACITORS. Complete Range always in Stock.	
WIREWOUND RESISTORS. 1W, 3W, 6W, 12W, 15W, 30W. Complete Range always in Stock.	
SEMICONDUCTORS. Transistors, Diodes, Rectifier Blocks, Thyristors, U.J.T.'s Diacs, Triacs, F.E.T.'s, Zeners, Photocells etc.	
10% DISCOUNT On any Cash Sale for Customers Presenting this Advertisement. 10% DISCOUNT	
<h2>C. T. ELECTRONICS</h2>	
267, ACTON LANE, LONDON, W.4 <span style="float: right;">01-994-6275</span>	
Nearest Underground—Chiswick Park (District Line), Acton Town (Piccadilly Line)-Bus Routes E3, 88, 207, 15, 7, 260.	
(Please note: As yet we do not have a catalogue available. Any queries please phone or call at the above address).	
BUSINESS HOURS: MON.-SAT. 9.30 a.m.-6 p.m. WED. 9.30 a.m.-1 p.m.	
WANTED. SURPLUS OR REDUNDANT COMPONENTS AND TEST EQUIPMENT	

# GOING BACK...

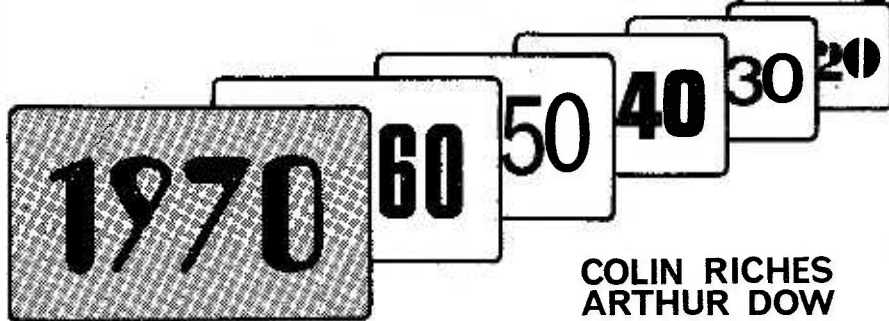

COLIN RICHES  
ARTHUR DOW



**M**ANY readers have written to ask us if we can suggest any gramophone records that may help them to bring alive even more vividly the days of vintage radio. After a certain amount of research we have discovered that Fountain Press, the book publishers, have now announced a new "Fountain" record label of Vintage Jazz music. The first 12in. LP releases feature historic jazz and blues recordings but future plans include Music Hall, Opera and other music of the "Good Old Days".

The records are housed in attractive double sleeves which open, displaying an authentically documented note section with accurate historical background information and photographs.

The first two releases are: "Original Dixieland Jazz Band and the Louisiana Five"—from the extremely rare Aeolian sessions of 1917 (catalogue number FJ-101). "Ladds Black Aces—Vol. 1"—the first 16 sides recorded by another pioneer white jazz band during 1921-1922 (Cat. No. FJ-102). Following soon are "Naylor's Seven Aces" (c 1923-4). "Jelly Roll Morton" 1923-4 piano solos. "Lovie Austin's Blues Serenaders" (1924-6), and "Annette Hanshawe. Vol. 1"—Miss Hanshawe enjoyed public acclaim as a singer of popular songs in the 1920's and 1930's and her records are great collectors' items today.

These records are available from record shops at £2.10 or direct at £2.25 which includes post and packing, from *Fountain Records, 46 Chancery Lane, London WC2A 1JU.*

If you have any questions or queries on these records or any other Vintage records or performers please write to us at *Practical Wireless* and we'll do our best to help you.

## The Mystery of the ST.200

We would, at this point, like to thank the many enthusiasts who have been kind enough to write and help us try to clear up the mystery of the missing John Scott Taggart design "ST.200" mentioned in "Going Back", August 1971.

One theory put forward by **Mr. F. W. Snow**, Belper, Derby, is that there never was a design called the ST.200 but one called "The ST Twin"—a 2-valve reflex. It was published in *The Wireless Constructor* and not the *Popular Wireless* magazine during the late 1924's and early 1925's.

**Mr. J. Crossley** hailing from Failsworth, Manchester, also maintains that the ST.200 never existed. He

says that J.S.T. visited the United States just after the advent of the ST.100. On his return, he was full of enthusiasm about a gentleman by the name of Armstrong, and *Popular Wireless* published a circuit by this man which J.S.T. had brought back with him. It was the "Armstrong Regenerative Circuit". J.S.T. then went on to publish the ST.300 design, so it appears that Armstrong's receiver may have taken the place of the missing ST.200.

**Mr. A. H. Jenkins**, Dringhouses, York, writes to say that as far as he recollects, the ST.200 may well have been just a mains-operated version of the ST.100 and therefore did not differ operationally from that design. It did however, need an extra valve. Mr. Jenkins also informs us that the S.T. series did not start at ST.100, although this was the most famous. He says that he used to have a limp covered book of J.S.T. circuits which started at crystal sets and worked up through one valvers. He seems to remember an ST.37 which was quite well-known at the time.


## Vintage Sets

**Mr. William Pozniak**, from 37 Manley Road, Oldham, Lancashire, has loaned us some photographs. He says that for three years he has been routing through old cellars and derelict radio shops throughout the North (we hope you came out for food now and again, Mr. Pozniak) and has produced the collection of Vintage gear shown in the first picture. He says that it takes him most of his time to strip down and restore these sets to as near as possible their original condition. The sets he has are as follows: The Burndept Screened Four, The Burndept Portable Five, the Burndept Ethophone Five and the Burndept Ethophone Two.


Mr. Pozniak believes there were about 20 Burndept receivers. This figure is agreed by Mr. Keith Lancaster who we mentioned some time ago as wanting to start a Vintage Radio Club. Incidentally, response has not been too good and if readers are interested in such a Club, would they please contact *Keith Lancaster, 40 Great Gardens Road, Hornchurch, Essex.*

The rest of Mr. Pozniak's collection contains a Marconiphone Type 32 three valver, a domestic Cossor two valver, a small set in a metal case named a GECOPHONE Victor 3 and a few home-constructed receivers.

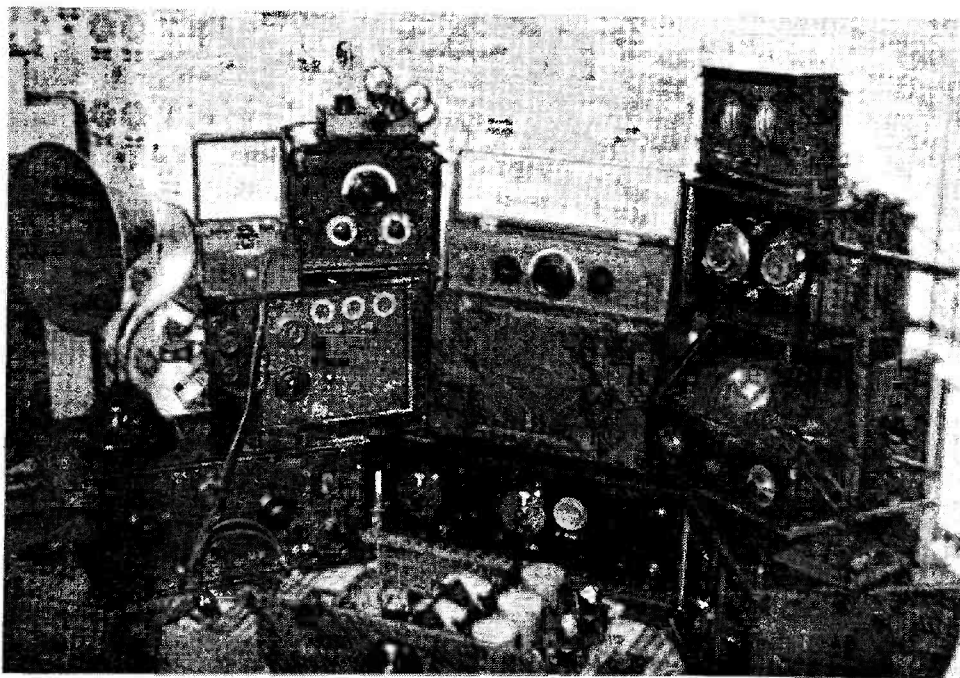The receiver shown in the second picture is a



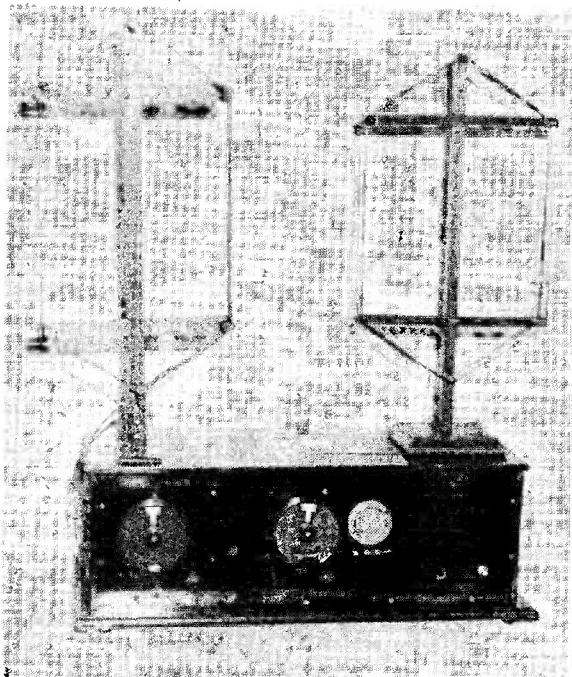
An overall view of Mr. Pozniak's collection of Burndept receivers. The small receiver shown at the top centre of the picture and the set in the centre of the picture together with frame aerials are shown enlarged below.



The James Super Six All Waver (c 1927).

1927 James Super Six All Waver (medium, long and short). The reader says that he purchased this set from an old radio shop which was a booming concern in the 1920's, together with a BTH horn speaker, and the person who sold it to him, told him, as he removed the set from the dusty shelf, that he was the first person to touch the set in 40 years.

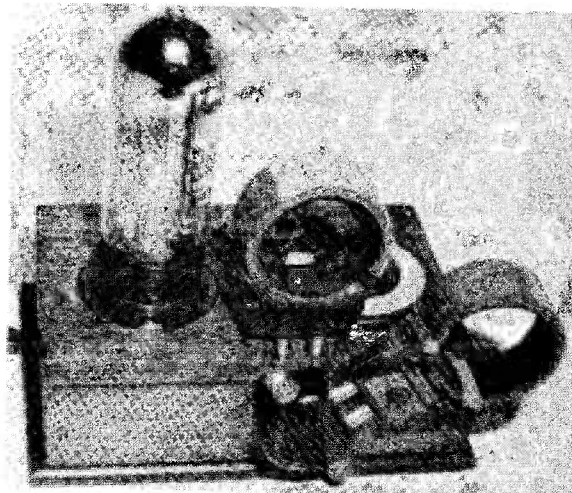The neat little receiver shown in the third photograph seems to Mr. Pozniak to be an unusual type, for he says that there appear to be two resistors and



Louwe receiver with encapsulated components.

two capacitors encapsulated in glass tubes which have then been assembled inside the glass envelope of the valve. The make on the case reads "Louwe Radio Berlin" and on the valve it states "Louwe Radio British Made". This set is in working order on headphones although it was originally made to drive some sort of speaker. The reader would like to know the date and origin of this set if anyone can help him and he would also be interested if anyone could supply him with original Burndept valves for any of their makes of receivers.

#### TITANIC DISASTER

We would like to thank the many readers who have written to us about the Titanic Disaster. We are gradually answering all the letters and we hope you will bear with us.



## SPECIAL PURCHASE!

### BRAND NEW FM MULTIPLEX STEREO DECODER UNITS.

Manufactured by PHILIPS. Size 2" x 3 1/4" x 1". All transistor 24v. at 6 mA. Supplied pre-aligned with full circuit diagram and connection details. £4 each Post Free.

### FEW ONLY—LEAK MK I TRANSCRIPTION PICK-UP ARMS

Using the world famous gimbal pivot system. Complete but less pick up head. £2-50 P. & P. 20p

### INPUT MATCHING TRANSFORMER

Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/2" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick up from low to high impedance or vice versa. 75p each Post Free

### BLACK ANODISED 16g. ALUMINIUM HEAT SINKS

For TOS, complete with mica's & bushes. Size 2 1/2" x 3" approx. 25p pair P. & P. 5p.

## HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



### NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm 3\text{dB}$  15-20,000 Hz. Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm 3\text{dB}$  12-15,000 Hz. Bass boost approx. to  $\pm 12\text{dB}$ . Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES	
AMPLIFIER KIT	£1-50 P. & P. 15p
POWER PACK KIT	£3-00 P. & P. 30p
CABINET	£3-00 P. & P. 30p
	(Post Free if all units purchased at same time)

Full after sales service  
Also available ready built and tested £20-40. Post Free.  
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque use, etc.

### SPECIAL PURCHASE OF MANUFACTURERS SURPLUS!

All Transistor F.M. tuner head with twin A.M. Gang Incorporated. Beautifully engineered with precision geared reduction drive. FM RF transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s output) with optional AFC connection. Built on printed circuit panel and fully screened. Extremely stable over range 88-108Mc/s. Brand new and pre-aligned. Size 2 1/4" x 1 1/2" x 2 1/4" d. For 6v D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. LIMITED NUMBER. Only £2.25 post free. Connection details supplied.

### HIGH GRADE COPPER LAMINATE BOARDS.

8 x 6 x 1/4 in. FIVE for 50p. P. & P. 13p.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to 22 1/2 in. approx. Maximum diameter 1/4 in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. Half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2 in. wide x 3in. deep. Price £1-75 P. & P. 30p.

MAINS TRANSFORMER. For resistor power supplies. P1. 200/240v. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. P2. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. P3. 200/240v. Sec. 10-0-10 at 2 amp. £1-95. P. & P. 30p. Tapped Primary. 200-220-240v. Sec. 21.5v. at 500mA. 65p. P. & P. 13p.

Open 9-5.30 Monday to Saturday  
Early closing Wed. 1 p.m.  
A few minutes from South Wimbeldon Tube Station.

## SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Uynair front. Size 16 1/2" high x 10 1/2" wide x 11 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £8.40 Carr. 65p  
Cabinet Available Separately £4-50 Carr. 60p  
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8-50 Carr. 65p

### LOUDSPEAKER BARGAINS

3" 4 ohm 50p. P. & P. 8p. 6in. 3 ohm 80p. P. & P. 15p. 7 x 4in. 3 ohm £1-05. P. & P. 20p. 10 x 6in. 3 or 15 ohm £1-90. P. & P. 30p. E.M.I. 8 x 6in. 3 ohm with high flux magnet £1-82. P. & P. 20p. E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet £2-10 (15 ohm £2-25). P. & P. 30p. E.M.I. 13 x 8in. 3 or 15 ohm with two inbuilt tweeters and crossover network £4-80. P. & P. 30p. E.M.I. 13" x 8" twin cone (parastatic tweeter) 8 ohm £2-25 P. & P. 30p.

BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly £5-50. Guitar models: 25w. £8-50, 35w. £8-50. P. & P. 35p. E.M.I. 3in. HEAVY DUTY TWEETERS. Powerful ceramic magnets. Available in 3 or 8 or 15 ohms 88p each. P. & P. 13p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm £2-20. P. & P. 30p.

35 ohm SPEAKERS 3in. only 65p. P. & P. 13p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1-75 yd., our price 75p yd. length. P. & P. 15p (mainly 1 yd.). S.A.E. for samples.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexiform ear-muffs. Wired and fitted with 2mm diameter 3in. jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE £2-95. P. & P. 15p.

SINGLE HEADPHONE. With aluminium headband. Approx. 200 ohm, 25p. P. & P. 8p

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity, 93p. P. & P. 8p

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1-05. P. & P. 8p

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P. U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 89p. P. & P. 13p.

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST. Fitted mono t/o stylus and cartridge for LP/78. ONLY £1.0 P. & P. 13p.

QUALITY RECORD PLAYER AMPLIFIER MK II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. £2-75 P. & P. 40p

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4-88 P. & P. 50p.

DELUXE QUALITY PORTABLE R/P CABINET MK II. Above motor board size 14 1/2 x 12in. clearance 2in. below, 5 1/2 in. height. Will take above amplifier and any B.S.R. or GARRARD changer or Single Playars (except AT60 and SP25). Size 18 x 15 x 3in. PRICE £3-98. P. & P. 50p.

## 10/14 WATT HI-FI AMPLIFIER KIT


A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7-97 P. & P. 65p. Also available ready built and tested complete with std. input sockets, £9-97. P. & P. 55p.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p; V15/100 50p; OC71 25p; OC76 30p; A11 15p; 2N39 (NPN) 15p. Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 £1-25; ORP12 Cadmium Sulphide Cells 53p. All post free.

## SPECIAL PURCHASE! SPEAKER CABINET FROM FAMOUS MAKER!

Beautifully made all wooden construction cabinet with medium walnut finish front, gold anodised expanded aluminium grille and dark sides. Approx. size overall 11 1/2" high x 5" deep x 13 1/2" wide at base. Easily removable baffle cut out for 8" speaker. Fibre board back. Could accommodate amplifier or radio together with speaker. An expensively made cabinet at a give away price. LIMITED NUMBER ONLY £1-98 Post Free.

## DE LUXE STEREO AMPLIFIER

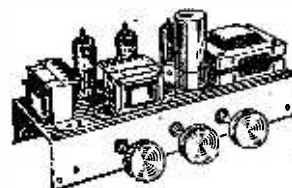

Valve line up:- 2 x ECL86 Triode Pentodes, x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "Balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 6". Ready built & tested to a high standard. PRICE £8-92 P. & P. 45p

### 4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £6-97 Carr. 50p. With stereo cartridge £7-97 Carr. 60p.

SUITABLE PLYNTH UNIT FOR ABOVE with rigid plastic cover. £5-75 complete P. & P. 50p.

LATEST GARRARD MODELS. All types available 1925-2025, SP25, 3000, AT60. S.A.E. for latest PRICE! PLYNTH UNITS cut out for Garrard Models, 1925, 2025-2000, 3000, 3500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £6.75 complete. P. & P. 50p.

LATEST ACOS GPR1/150 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

SONOTONE STACH COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78.

ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP Stereo 78. £1-43 P. & P. 10p. LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

### 8-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis size 7 1/2" w x 4" d x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4-75. P. & P. 35p.

### ESL "FOUR" AMPLIFIER KIT. Similar in appearance to HA4 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3-98. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER A super quality gram amplifier using a fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. FEW ONLY. BARGAIN PRICE £2.75 P. & P. 35p

### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. 1971 edition including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p Post 5p.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



# WAVE METER

# MONITOR

R. F. GRAHAM

**T**HIS unit has four switch-selected bands, covering from 1600kHz to 100MHz and it can be used as a wavemeter, field strength meter or phone transmission monitor. It is fully enclosed, self-contained, and requires no battery.

Figure 1 shows the circuit. One pole of the switch, S1, selects the inductors L1, L2, L3 or L4, which are tuned by VC1. Pole S2 switches the diode D1 to the appropriate small coupling winding. When the circuit is tuned to resonance by VC1, rectified current is indicated by the meter.

To monitor phone signals, high impedance headphones or earpiece can be plugged into the phone jack and the phones are then in series with the meter. C1 is for r.f. and a.f. by-pass purposes, while C2 is an r.f. by-pass capacitor.

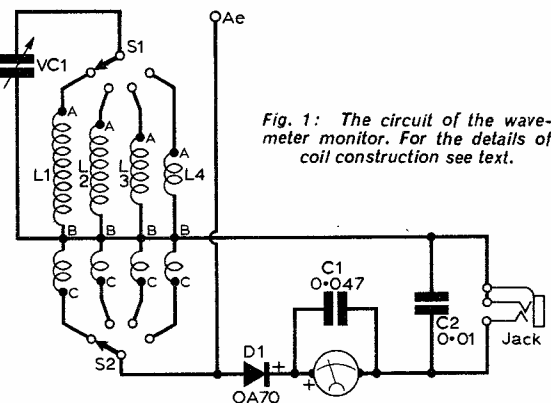
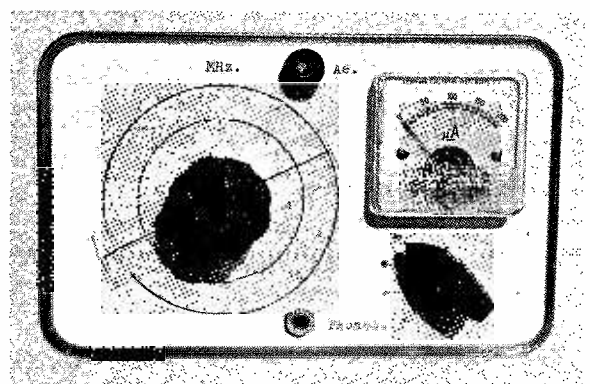


Fig. 1: The circuit of the wave-meter monitor. For the details of coil construction see text.

## INDUCTORS

L1, L2 and L3 are wound on  $\frac{1}{2}$ in. diameter paxolin formers. These can be prepared by cutting  $1\frac{1}{2}$ in. lengths of  $\frac{1}{2}$ in. diameter tube, and drilling small holes to secure the ends of the windings. The tubes can later be fixed with adhesive, with small brackets or by having them a push fit on small discs of insulating material screwed in place. Surplus or junk box formers could probably be utilised, but if these are of different diameter it may be necessary to modify the number of turns to suit.

L1 is wound with 34 s.w.g. enamelled copper wire. The tuned portion A to B is 65 turns, in a compact pile about  $\frac{3}{16}$ in. long. A space of about  $\frac{3}{16}$ in. is left and section B to C is wound on in the same direction, and has 8 turns side by side.

L2 also uses 34 s.w.g. enamelled copper wire. A to B is 50 turns wound side by side. A space is left as before, and a 4 turn coupling winding ends at C.

L3 uses 24 s.w.g. enamelled wire and has  $12\frac{1}{2}$  turns from A to B, and 2 turns from B to C. Figure 2 shows the general construction of L1, L2 and L3.

The windings are doped, smeared with clear *Bostik 1* or with some other suitable coil cement.

L4 is self-supporting, of 16 s.w.g. bare wire, and is shown in Fig. 3. It is wound and shaped to have 8 turns in all and is  $\frac{1}{2}$ in. outside diameter, and 1in. long. B is a tapping 2 turns from end C. This coil is soldered directly to tags A and C of the 4-way switch as shown in Fig. 3. A lead runs from tapping B

## ★ components list

- VC1 200pF Wavemaster variable capacitor.
- C1 0.047F or similar.
- C2 0.01F or similar.
- D1 OA70 or OA71 diode.
- S1 50 3-pole 4-way miniature rotary switch.
- Small closed circuit jack.
- 200uA miniature meter.
- Inductors as text.
- Paxolin or other box about 6 x 3½ x 2½in., aerial socket, knobs etc.

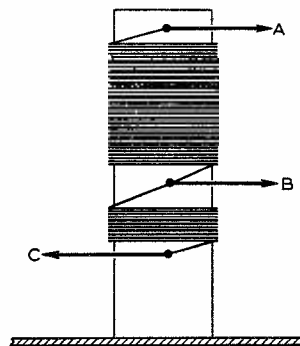


Fig. 2: The general construction of coils L1, L2 and L3 wound on  $\frac{1}{2}$ in. diameter paxolin formers. Details of L4 are given in the text and in Fig. 3.

directly to the moving plates tag of the variable capacitor.

## CONSTRUCTION

The wavemeter was built to occupy a rigid plastic 'snack box' approximately 6in.  $\times$  3 $\frac{1}{2}$ in.  $\times$  2 $\frac{1}{2}$ in. deep. A piece of paxolin sheet, a little under 6in.  $\times$  3 $\frac{1}{2}$ in., was cut to fit inside the box lid. The wavemeter is built wholly on this paxolin panel.

Screws holding L1, L2 and L3 are countersunk. A piece of stout paper to bear dial markings is cut the same size as the paxolin, and cemented to it. The wavemeter is then assembled and calibrated and the scales are marked. The meter and fixing nuts of the switch, jack, and VC1 are then removed and the paxolin panel is fitted inside the box lid. This places the scales under the transparent material of the lid. Paxolin and lid are held together by the meter and the nuts mentioned.

Holes for the jack, switch and VC1 are first drilled in the paxolin and the meter hole cut with an adjustable washer or tank cutter. The paxolin is then placed in the lid, and the positions of holes marked on the lid itself, so that they can be made to match up correctly with those in the paxolin.

The box should be of material which is reasonably strong. It should be drilled and cut with tools which are really sharp, and without forcing, to avoid cracking.

A suitable case could be assembled from  $\frac{1}{4}$ in. thick wood, glued and pinned at the joints. The paxolin panel would then be large enough to be fixed with small wood screws.


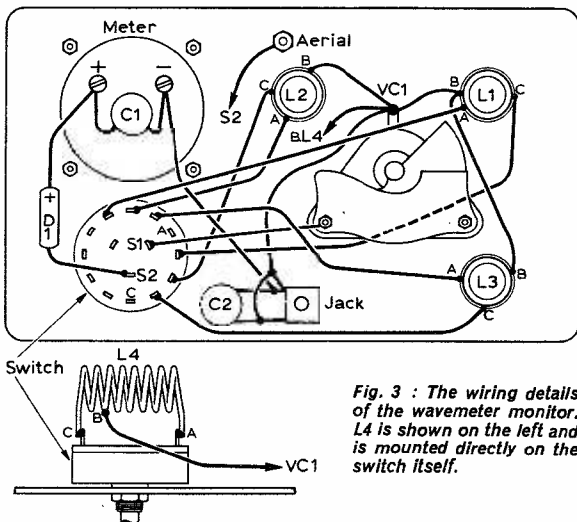


Fig. 3: The wiring details of the wavemeter monitor. L4 is shown on the left and is mounted directly on the switch itself.

All wiring is shown in Fig. 3. Connections should be of stout wire and run clear of each other, and should be reasonably short and direct, especially for L3 and L4.

VC1 is 200pF, but this exact value is not essential, provided that the ranges overlap a little. If an alternative diode is fitted, be sure it is suitable for frequencies up to 100MHz.

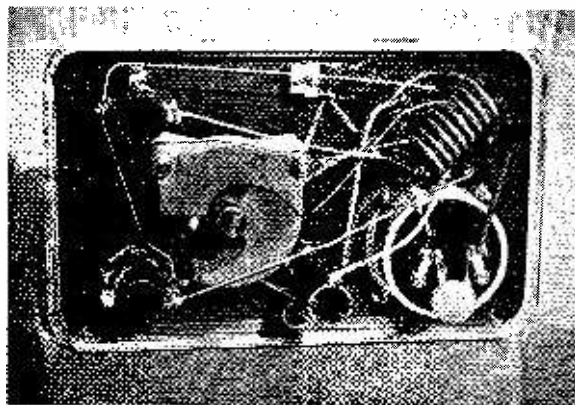A 100 $\mu$ A meter would be a little more sensitive than the one specified, but would also cost a little more. Should a 500 $\mu$ A meter be to hand, it is suitable, though less sensitive. The sensitivity with a 1mA meter becomes rather low so an instrument in the neighbourhood of 200 $\mu$ A is probably most suitable.



An internal view of the completed prototype.

The dial cursor is a 2 $\frac{3}{4}$ in. piece of perspex about  $\frac{5}{8}$ in. wide, marked with a hair line. Readings will be confused if VC1 can rotate through 360°, so the extreme corner of the back moving plate was turned up with pliers to limit rotation to about 180°.

Values used for C1 and C2 are not particularly important. A medium or high impedance pair of headphones will give best general results.

## CALIBRATION

Actual band coverage with the inductors described is as follows

- Range 1 1.6-4MHz
- Range 2 2.8-10MHz
- Range 3 8-32MHz
- Range 4 21-100MHz

This gives 160 and 80m bands in Range 1, 80 and 40m bands in Range 2, all h.f. bands 20-10m in Range 3, and 15-10m bands and harmonics in Range 4, without having to use the extreme h.f. end of the ranges, where readings become close together.

The simplest means of calibration is to use a grid dip oscillator, placing its coil 2in. or so from the appropriate inductor in the wavemeter. This allows complete calibration of all ranges with a minimum of difficulty.

A transmitter can be used for calibration in the amateur bands, and these will probably be of most importance. Place the wavemeter some distance from the transmitter, its dummy load or the aerial lead or tuner, as required to obtain a deflection on the meter.

Some signal generators have an r.f. level meter. If the output of the generator is coupled to the wavemeter by a small loop, a dip may be observed on the level meter when the wavemeter is tuned to resonance. This offers another possible way to secure calibration.

If the wavemeter is coupled to a receiver having a sensitive S-meter, a slight dip in the S-meter reading can be observed when the wavemeter is tuned to the receiver frequency. Input to the receiver can be from a signal generator, or transmission.

All calibration is made with no external connection to the wavemeter and minimum coupling to avoid unnecessary inaccuracy.

## USES

A wavemeter is normally used to indicate frequency bands and harmonics, not exact frequencies within a narrow band. It is placed or held to pick up sufficient r.f. energy from the circuit being investiga-

—continued on page 534

**BRAND NEW  
GUARANTEED**

**SEMICONDUCTORS & COMPONENTS**

**RETURN OF POST  
SERVICE**

SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

**TRANSISTORS**

2G301	20p	2N3404	32p	40310	45p	BC212L	13p	BX238	32p	NKT281	27p
2G302	20p	2N3405	45p	40311	35p	BCY30	27p	BX260	82p	NKT401	87p
2G303	20p	2N3414	45p	40312	47p	BCY31	30p	BX261	62p	NKT402	80p
2G304	42p	2N3415	25p	40313	47p	BCY32	30p	BX262	82p	NKT403	75p
2G308	30p	2N3416	37p	40320	47p	BCY33	25p	BX277	25p	NKT405	75p
2G309	30p	2N3417	37p	40323	32p	BCY34	30p	BX278	27p	NKT406	75p
2G371	15p	2N3570	11-25	40324	47p	BCY38	40p	BX280	27p	NKT406	62p
2G374	20p	2N3572	87p	40326	37p	BCY39	60p	BX281	27p	NKT451	62p
2G381	22p	2N3605	27p	40329	37p	BCY40	50p	BX294	15p	NKT452	62p
2G401	20p	2N3622	27p	40342	47p	BCY42	15p	BX295	15p	NKT453	47p
2N696	20p	2N3607	22p	40437	57p	BCY43	15p	BX296	15p	NKT453	47p
2N697	17p	2N3702	11p	40348	52p	BCY64	32p	BX297	17p	NKT700P	32p
2N698	25p	2N3703	10p	40360	42p	BCY68	25p	BX298	17p	NKT767F	30p
2N706	12p	2N3704	11p	40361	47p	BCY69	22p	BX299	17p	NKT767F	30p
2N705A	12p	2N3705	10p	40362	47p	BCY60	97p	BX322	25p	NKT7713	25p
2N708	15p	2N3706	09p	40370	32p	BCY70	20p	BX326	25p	NKT781	30p
2N709	62p	2N3707	11p	40406	37p	BCY72	25p	BX327	25p	NKT10419	30p
2N718	25p	2N3708	07p	40407	40p	BCY79	17p	BX328	25p	NKT10433	37p
2N726	30p	2N3709	09p	40408	52p	BCZ10	27p	BX329	25p		
2N727	30p	2N3710	09p	40410	62p	BCZ11	42p	BX340	32p	NKT10519	
2N914	17p	2N3711	12p	40467A	57p	BD116	11-12p	BSY51	32p		
2N916	17p	2N3715	11-23	40468A	57p	BD121	65p	BSY52	32p	NKT20329	
2N918	30p	2N3716	11-30	40600	57p	BD123	32p	BSY53	37p		
2N921	22p	2N3717	20p	40601	67p	BD107	32p	BSY54	40p	NKT20333	37p
2N930	27p	2N3819	35p	AC126	20p	BD131	75p	BSY56	90p		
2N1090	22p	2N3823	97p	AC127	20p	BD132	85p	BSY78	47p	NKT80111	
2N1091	22p	2N3854	27p	AC128	20p	BDY10	11-37p	BSY79	45p		
2N1131	22p	2N3864A	27p	AC184	22p	BDY11	11-62p	BSY82	62p	NKT80112	
2N1132	22p	2N3856	27p	AC176	25p	BDY17	11-50	BSY90	57p		
2N1302	22p	2N3858A	30p	AC187	62p	BDY18	11-75	BSY95A	12p	NKT80113	
2N1303	17p	2N3856	30p	AC188	37p	BDY19	11-97p	BSY92	42p		
2N1304	22p	2N3856A	35p	ACY17	27p	BDY20	11-121	BW670	27p	NKT80211	
2N1305	22p	2N3858	25p	ACY18	25p	BDY38	97p	C111	75p		
2N1306	25p	2N3858A	30p	ACY19	25p	BDY90	11-25	C424	27p	NKT80212	
2N1307	25p	2N3859	27p	ACY20	25p	BDY61	11-25	C425	55p		
2N1308A	30p	2N3858A	32p	ACY21	25p	BFY82	11-00	C426	40p	NKT80213	
2N1309	30p	2N3860	30p	ACY22	20p	BF115	25p	C428	37p		
2N1507	17p	2N3866	11-50	ACY28	20p	BF117	47p	C744	42p	NKT80214	
2N1613	20p	2N3877	40p	ACY40	20p	BF163	37p	D16P1	37p		
2N1621	35p	2N3877A	40p	ACY41	25p	BF167	18p	D16P2	42p	NKT80215	
2N1632	30p	2N3900	37p	ACY44	40p	BF173	18p	D16P3	37p		
2N1638	27p	2N3901	47p	AD140	53p	BF177	30p	D16T1	47p	NKT80216	
2N1639	27p	2N3901	47p	AD140	53p	BF178	30p	GET102	62p		
2N1671B	11-00	2N3903	35p	AD150	62p	BF179	30p	GET113	20p	OC20	75p
2N1721	25p	2N3904	35p	AD161	37p	BF180	35p	GET114	20p	OC22	50p
2N1889	32p	2N3905	37p	AD162	37p	BF181	32p	GET118	20p	OC23	60p
2N1893	37p	2N3906	37p	AD166	42p	BF184	25p	GET119	20p	OC24	60p
2N1917	22p	2N3905	17p	AF114	45p	BF185	42p	GET120	62p	OC25	50p
2N2148	27p	2N4059	17p	AF115	25p	BF186	42p	GET121	12p	OC26	25p
2N2160	57p	2N4060	17p	AF116	25p	BF195	15p	GET880	30p	OC28	62p
2N2193	40p	2N4061	12p	AF117	25p	BF196	42p	GET887	20p	OC29	62p
2N2193A	42p	2N4062	12p	AF118	62p	BF197	42p	GET889	22p	OC35	50p
2N2194A	30p	2N4244	47p	AF119	20p	BF198	42p	GET890	22p	OC36	62p
2N2217	27p	2N4285	17p	AF124	22p	BF200	32p	GET896	22p	OC41	62p
2N2219	25p	2N4286	12p	AF126	25p	BF202	14p	GET892	22p	OC42	25p
2N2219	25p	2N4287	17p	AF126	20p	BF225	20p	GET898	22p	OC43	22p
2N2220	25p	2N4288	17p	AF127	17p	BF237	28p	MJ400	11-07p	OC45	12p
2N2221	25p	2N4289	17p	AF139	37p	BF238	28p	MJ420	11-12p	OC46	15p
2N2222	30p	2N4290	17p	AF178	42p	BF244	28p	MJ421	11-12p	OC70	15p
2N2270	47p	2N4291	17p	AF179	72p	BFW61	47p	MJ430	11-02p	OC71	12p
2N2297	27p	2N4302	17p	AF180	57p	BFX1	32p	MJ440	35p	OC72	12p
2N2368	17p	2N4303	47p	AF181	42p	BFX13	22p	MJ448	37p	OC73	12p
2N2369	17p	2N4307	52p	AF239	42p	BFX29	30p	MJ481	11-25	OC75	22p
2N2369A	17p	2N5028	57p	AF279	47p	BFX30	30p	MJ490	11-00	OC76	22p
2N2410	42p	2N5029	47p	AF280	62p	BFX42	37p	MJ491	11-37p	OC77	30p
2N2483	27p	2N5030	48p	AF291	32p	BFX44	47p	MJ1800	22-17p	OC81	30p
2N2484	32p	2N5172	12p	ASV26	65p	BFX68	67p	MJE340	62p	OC81D	22p
2N2589	22p	2N5174	52p	ASV27	37p	BFX84	27p	MJE521	27p	OC82	25p
2N2540	42p	2N5175	52p	ASV28	27p	BFX85	32p	MJE521	27p	OC84	25p
2N2613	35p	2N6176	45p	ASV29	27p	BFX86	25p	MPF102	42p	OC139	32p
2N2914	30p	2N6292A	30p	ASV38	25p	BFX87	27p	MPF103	37p	OC140	32p
2N2946	52p	2N6293	45p	ASV39	25p	BFX88	25p	MPF104	37p	OC170	30p
2N2956	32p	2N5246	42p	ASV41	32p	BFY89	62p	MPT105	37p	OC20	30p
2N2711	25p	2N5249	67p	ASV44	25p	MPS5638	32p	OC200	40p		
2N2712	25p	2N5265	11-25	ASV86	32p	BFY10	32p	NKT0013	47p	OC201	60p
2N2713	27p	2N5266	22-75	AU103	11-25	BFY11	42p	NKT1214	47p	OC202	75p
2N2714	30p	2N5267	22-82	ASV21	42p	BFY17	22p	NKT1225	27p	OC203	42p
2N2965	62p	2N5305	37p	BD107	10p	BFY18	22p	NKT1226	27p	OC204	42p
2N2990	30p	2N5306	40p	BC130	19p	BFY19	22p	NKT1227	27p	OC205	60p
2N2904A	32p	2N5307	37p	BC109	10p	BFY20	11-60	NKT135	27p	OC207	75p
2N2905	37p	2N5308	37p	BC113	15p	BFY21	42p	NKT137	32p	OC271	42p
2N2905A	40p	2N5309	62p	BC115	15p	BFY24	45p	NKT210	30p	ORP12	62p
2N2906	25p	2N5310	42p	BC116A	15p	BFY25	25p	NKT211	30p	ORP61	50p
2N2906A	27p	2N5354	27p	BC118	10p	BFY26	20p	NKT212	30p	P346A	22p
2N2907	30p	2N5355	27p	BC121	20p	BFY29	50p	NKT213	30p	TIS84	37p
2N2923	25p	2N5356	32p	BC122	20p	BFY30	50p	NKT214	22p	TIS843	27p
2N2924	25p	2N5365	47p	BC125	20p	BFY41	50p	NKT215	22p	TIS844	10p
2N2925	15p	2N5366	32p	BC126	20p	BFY43	62p	NKT216	37p	TIS845	10p
2N2926	15p	2N5367	37p	BC140	37p	BFV50	28p	NKT217	42p	TIS846	11p
Green	14p	2N5457	37p	BC147	10p	BFV51	30p	NKT219	30p	TIS847	11p
Yellow	12p	2S005	75p	BC148	10p	BFV52	25p	NKT220	27p	TIS848	13p
Orange	12p	2S020	11-00	BC149	12p	BFV53	12p	NKT224	27p	TIS849	13p
2N3011	30p	2S102	60p	BC152	17p	BFV56A	57p	NKT225	22p	TIS850	17p
2N3014	32p	2S103	35p	BC157	30p	BFV75	30p	NKT229	30p	TIS851	12p
2N3053	18p	2S104	25p	BC158	11p	BFV76	42p	NKT237	35p	TIS852	12p
2N3064	40p	2S501	32p	BC169	12p	BFV77	57p	NKT238	25p	TIS853	22p
2N3065	62p	2S502	35p	BC160	62p	BFV78	57p	NKT240	27p	TIS854	22p
2N3133	30p	2S503	37p	BC167	11p	BFW68	27p	NKT2			

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way*.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Built Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

### You LEARN—but it’s as fascinating as a hobby

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, Practical Projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

### New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of “OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



## FREE

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B8, ALDERMASTON COURT, READING RG7 4PF

### POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B8 Aldermaston Court, Reading RG7 4PF  
Please send books and full information — FREE and without obligation.



NAME ..... AGE .....

ADDRESS .....

OCCUPATION .....

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# WICKS FOR BARGAINS

### E.A. STEREO AMPLIFIER:

5 watts per channel; In attractive afrormosia veneered sleeve. Controls: On-off volume: Bass: Treble: Balance: Selector: Headphone Jack. Ceramic or Magnetic PU. Radio and Tape Inputs: Tape output and speaker output. Fully guaranteed 12 months parts. 6 months free service. Size 14½”W x 9½”D x 45”H approx. £16·50 inc. post.

- Guaranteed all brand new best quality goods. No rubbish.
- Mail order only.
- All enquiries SAE please.

### 3 WAY SPEAKER SYSTEM:

8” twin cone Bass speaker and 3” tweeter, fitted in extremely elegant teak veneered cabinet. Size : 18½”H x 11½”W x 10”D. 8 ohms handle 10 watts. £7·50 inc. Carr.

### GARRARD OFFERS

Garrard SP25 Mk III (Rec. Price (£15·85) Our Price £11·25. Carr. & Ins. 50p.

Garrard SP25 Mk III ready wired in beautiful teak plinth with tinted perspex cover. (Fitted with 5-pin DIN plug or phono plugs—state choice) (Rec. Price £23·19). Our Price £16. Carr. & Ins. 75p.

Or with choice of fitted cartridges.

SP25 Mk III/Sonotone 9TAHC (Rec. Price £27·29) Our Price £18. Carr. & Ins. 75p.

SP25 Mk III/Shure M3DM (Rec. Price £31·02) Our Price £20. Carr. & Ins. 75p.

SP25 Mk III/Goldring G800 (Rec. Price £36·19) Our Price £21. Carr. & Ins. 75p.

SP25 Mk III/Shure M55E (Rec. Price £36·16) Our Price £21. Carr. & Ins. 75p.

Note! Garrard SL65B (Automatic Changer version of SP25 Mk III) alternatively supplied—please add £3 to above prices.

Garrard AP76 (Rec. Price £27·85) Our Price £18·85. Carr. & Ins. 50p.

Garrard AP76 ready wired in beautiful teak plinth with perspex cover (fitted with 5 pin DIN or Phono plugs). Please state choice. (Rec. Price £39·85). Our Price £24·94 Carr. & Ins. 75p.

### OR WITH CHOICE OF FITTED CARTRIDGES.

Garrard AP76/Shure M3D (Rec. Price £47·26) Our Price £28·94. Carr. & Ins. 75p. Garrard AP76/Shure M55E (Rec. Price £52·82). Our Price £31·35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52·82) Our Price £31·35. Carr. & Ins. 75p.

Garrard 2025TC fitted with stereo/mono cartridge. £8·99. Carr. Paid.

TEAK PLINTH & PERSPEX COVER Ready cut to take 2025TC, SP25 III, SL65B available at £4·99. Carr. & Ins. 35p.

CARTRIDGES (All with diamond stylus) Sonotone 9TAHC dia. Rec. Price £4·10. Our Price £1·99

Shure M3DM (Rec. Price £7·41) Our Price £4·87.

Shure M55E (Rec. Price £12·97) Our Price £9·00.

Goldring 800 (Rec. Price £13·00) Our Price £7·50.

Goldring 800 H (Rec. Price £10·69) Our Price £6·99.

P & P 18p any type

**Special Offer!**  
Grundig GDM312 Dynamic Microphones. List £7.35 OUR PRICE £3. P & P 30p

**Hi-Fi Stereo Headphones**  
(Value £5·00)  
Only £2·25 inc. post.

**Speaker Cloth**  
Best quality. Width 36”. Under half price at 55p per yd. Black with gold fleck, will blend with any room setting. End of stock line, yds and yds must go.

### Plugs, Sockets and Leads.

Phono plugs; 3p each 30p per dozen.  
2 pin Din spkr. plugs 10p each.  
3 pin Din plugs. 15p each.  
5 pin Din plugs. 15p each.  
5 pin Din sockets (chassis) 7p each.  
Stereo Jack Sockets 1/2cct. 15p each.  
Phono sockets (chassis) 2 way 3p; 3 way 4p; 4 way 5p.  
6ft. stereo lead 5 pin Din to open end. 45p  
6ft. stereo lead 2 phono to open end. 37p  
12ft. spkr. lead 2 pin Din to open end. 40p.  
Please add P & P 5p.

### 100 Mixed Resistors

½ watt 10% all best quality (no ex government) 40p.

### Pots

100K x 100K lns & Logs. stereo. 35p inc. post.  
100K DP switch stereo, log. 45p inc. post.  
50K single Balance. 15p inc. post.

4 B.A. brass nuts 50 for 25p inc. post.

### Speaker cabinets

Attractively veneered in afrormosia, black front. Size approx. 7½”W x 9½”D x 4½”H. Ready cut to take 8” x 5” speaker. £1·99. P. & P. 12p.

**D. T. WICKS & CO.** 49 North Station Rd, Colchester, Essex.  
Tel: (0206) 78807

# TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

“WHAT’s an automatic light?” you may well ask. Well, lights are only needed when it’s dark, and a very simple electronic switch circuit can be made to turn a small light on as soon as the general light level drops below a certain level; this has its most obvious application in motor cars. Many parts of the country have local regulations requiring cars to display lights shortly after sunset, even when parked. In other areas car parking lights are needed only when the local street lighting is turned off, which in some areas is as late as 2 a.m. There cannot be many people who relish the thought of going out to their cars at that hour to turn on the side or parking lights.

Porch lights which automatically turn themselves on after dusk are another application and although the circuit as shown is not really meant for this, many readers will realise the potential and modify the circuit to operate a thyristor or relay to apply the mains supply to the porch light.

## THE CIRCUIT

Like last month we are making use of a light dependent resistor, that is a resistor whose value in ohms falls with an increase in light falling on it. Also like last month this component is coupled into the base bias potential divider circuit, thus controlling the bias on the transistor, Tr1. R1 may have to be altered in value in order to make the “switch” operate at the correct light level.

As darkness falls, the potential at the base of Tr1 falls as the value of the LDR rises and after a certain point Tr1 begins to turn off, less current is passed and the potential between the emitter and the collector rises. This in turn starts to turn Tr2 on. This transistor, when light was falling on the LDR, thus holding Tr1 on, was off since the potential between base and emitter was held at a very low level due to the small potential across Tr1. As soon as Tr2 begins to conduct this increases the current through R4, thus causing Tr1 to cut off even more and in turn switching Tr2 more on. This action takes place very quickly and Tr2 is switched fully on, applying the supply voltage across the bulb causing it to light up.

This switching circuit is known as the *Schmitt Trigger* and a very useful circuit, it is too, with applications in many fields of electronics. As can be seen, only a few components are required and the switching action, using modern transistors, is very rapid and very positive. As soon as the potential at the base of Tr1 either reaches or falls to a preset level, Tr2 will switch.

The supply necessary to operate the circuit is taken directly from the car battery, though it is good practice to take this via the car’s fuse as any

—continued overleaf

## No. 30 AUTOMATIC LIGHT

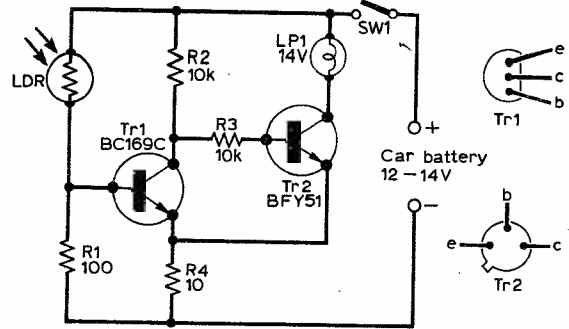


Fig. 1: The circuit of the automatic light with the lead connections of the transistors shown on the right.

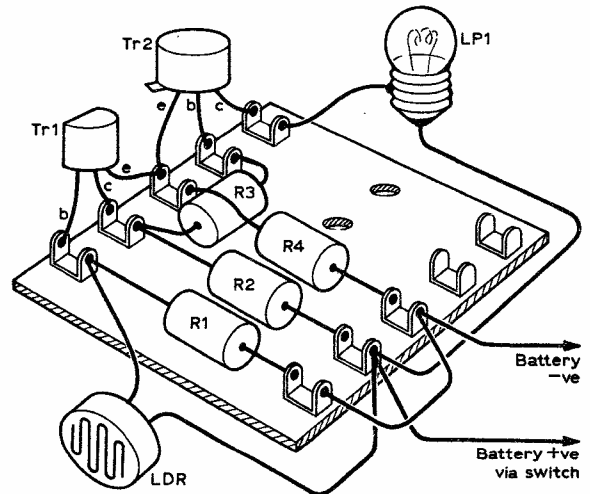


Fig. 2: A suggested component layout on a small piece of tag board.

## ★ components list

Tr1	BC169C	10p
Tr2	BFY51	20p
LDR	Light Dependent Resistor	40p
R1	100Ω 1/2W	10
R2	10kΩ 1/2W	10
R3	10kΩ 1/2W	10
R4	10Ω 1/2W	10
LP1	14V LED Lamp Radiolux type	10
SW1	DPDT toggle switch	10
		25p

† Electronic Ltd.  
 ‡ J. G. (Electronics) Ltd.  
 ††† Radio Shack

The above sources listed are available from most main  
 component stockists. Prices are those currently available  
 and may have changed. No alternative is made for  
 alternative order codes or part numbers and packing  
 charges should be checked before ordering.

mistakes or serious component failure could create a fire risk.

Car batteries are capable of giving very high currents and therefore the quiescent current is of no great importance but it is in fact low, in the order of 2mA. The recommended bulb draws 40mA and it can be seen that these currents can be supplied by a number of dry batteries, though operation in this manner will not be cheap.

The bulb should last a considerable time as it is being slightly under-run; there is of course a small volts drop across R4 and Tr2.

## CONSTRUCTION

A suggested layout is shown in Fig. 2 but this is not critical. One point must be watched however; if the light from the bulb is allowed to fall onto the LDR it will switch the circuit in the same way that sunlight will. This will cause the circuit to oscillate; this can easily be seen as the bulb will flicker or flash. To avoid this the LDR must be pointed away from the bulb. ■

## WAVEMETER MONITOR—by R. F. GRAHAM

continued from page 530

ted. Tuning resonance is shown by maximum meter reading. In driver and similar circuits with small power, the wavemeter needs to be reasonably close to the circuit inductor. For P.A. and high power circuits, it can be at some small distance.

To check the frequency of low level multipliers and similar circuits, or those which are inaccessible, a link line may be used. This is twin flex or co-axial cable about 2ft. long with a loop of two or three turns each end. One loop is held near the equipment inductor, and the other near the wavemeter inductor. Clipping a lead to jack and aerial socket also allows the coil primaries to be used for coupling. Resonance will be shown by a dip in grid current in a subsequent stage.


To monitor the audio of an outgoing transmission, plug in phones, tune to resonance and situate the unit where pick-up gives adequate volume.

To tune an aerial, transmitter, tuner or coupling device for maximum radiation from the aerial, a vertical rod or wire is plugged into the aerial socket of the unit, which should be at some distance. Adjustments are then for maximum meter reading, which corresponds to maximum field strength. It is also possible to link couple a dipole or aerial-earth system to the wavemeter for this purpose, or take a short aerial to VC1, ignoring calibration.

The wavemeter produces no signal. It can be used to find bands on a t.r.f. receiver by adjusting the latter until oscillation just arises, and holding the wavemeter coil in line with the receiver coil. Resonance when tuning the wavemeter is then shown by the receiver going out of oscillation. ■
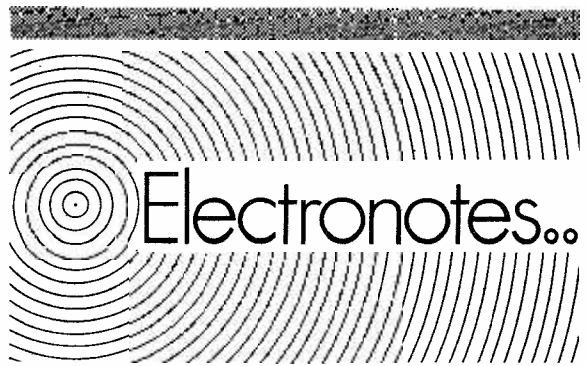
### BLUEPRINT SERVICE

We would like to draw readers' attention to the fact that the BLUEPRINT SERVICE has been discontinued and therefore no further BLUEPRINTS are available.



## S. GINSBERG

**I**N the beginning there were photocells enclosed in glass envelopes. Variations of these were more sensitive and multi-electrode secondary emission cells appeared like the 931A photomultiplier tube.

In more recent years, many experimenters, and indeed, most of the electronics industry too, has opted for solid state when thinking in terms of a light sensing device. An example here is the ORP12 light-dependent resistor, not to mention the earlier plastic-encapsulated transistors with some of their paint removed!

In America, work is currently proceeding on a technique known as charge coupling for imaging devices. One oxidised surface of a tiny silicon chip is covered with some 288 minute electrodes. These are arranged into groups of three, the last electrode in each group being a common conductor for the whole array.

The area immediately beneath each group of three elements forms a tiny light sensitive device in its own right. Minority carriers are generated in the silicon beneath the electrodes whenever light is focussed onto them. The greater the intensity of the light, the greater the charge, thus forming a direct relationship between light intensity and electrical charge.

The centre electrode of each group is purposely made more positive than the other two elements and thus the charges on minority carriers are attracted to, and congregate at, these centre electrodes.

Individual charges are next moved along the array from one electrode group to the next by putting a successively greater positive voltage on the electrode next to the one which is holding the charge. Eventually all the charges will have been passed along to the end of the device where they are collected by an output electrode.

Because the size of the charge will be dependent upon the amount of original light applied, the final electrode has, in effect, an analogue electrical signal which has a linear relationship to original light patterns of intensity.

How big is a 100,000 $\mu$ F capacitor—think of the size of some electrolytics. Now imagine how big a one Farad capacitor would be. Just to stretch the imagination even further, think of a 50 Farad capacitor. Fantastic—but they exist and are for sale. Twist in the tale is that the 50F is contained within one-third of a cubic inch. The devices will also retain their storage (if charged with a voltage) and leakage is so low that even after 16 months they will have retained over 97 per cent of the original charge. Think; they could be charged up and used as a form of battery. When discharged, they could simply be recharged again ad infinitum.



# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

### NEW "SEW" DESIGNS!

#### CLEAR PLASTIC METERS



**TYPESW.100**  
100 x 80 mm.

#### BAKELITE PANEL METERS




**TYPE S-80**  
80 mm.  
square fronts

50μA ..... \$3.47	20V. D.C. .... \$2.97	50μA ..... \$2.19	50V. D.C. .... \$2.47
500-500μA ..... \$3.37	50V. D.C. .... \$3.97	100-500μA ..... \$2.97	300V. D.C. .... \$2.47
100μA ..... \$3.37	300V. D.C. .... \$2.97	500-1000μA ..... \$3.71	1 amp. D.C. .... \$2.47
100-100μA ..... \$2.25	1 amp. D.C. .... \$2.97	500μA ..... \$2.97	300V. A.C. .... \$2.25
500μA ..... \$2.12	5 amp. A.C. .... \$2.97	1mA ..... \$1.87	20V. D.C. .... \$2.47
1mA ..... \$2.97	VU Meter ..... \$3.75		


### "SEW" CLEAR PLASTIC METERS

#### Type MR.55P. 4 1/2 in. x 4 1/2 in. fronts.



50mA ..... \$2.60	100mA ..... \$2.60	500mA ..... \$2.60	1 amp. .... \$2.60	5 amp. .... \$2.60	15 amp. .... \$2.60	30 amp. .... \$2.60	20V. D.C. .... \$2.60	50V. D.C. .... \$2.60	150V. D.C. .... \$2.60	300V. D.C. .... \$2.60	15V. A.C. .... \$2.60	300V. A.C. .... \$2.60	8 Meter 1mA ..... \$2.60	5 Meter 1mA ..... \$2.60	1 amp. A.C. .... \$2.60	5 amp. A.C. .... \$2.60	10 amp. A.C. .... \$2.60	20 amp. A.C. .... \$2.60	30 amp. A.C. .... \$2.60
-------------------	--------------------	--------------------	--------------------	--------------------	---------------------	---------------------	-----------------------	-----------------------	------------------------	------------------------	-----------------------	------------------------	--------------------------	--------------------------	-------------------------	-------------------------	--------------------------	--------------------------	--------------------------

#### Type MR.55P. 1 21/32 in. square fronts.



50μA ..... \$2.60	100-500μA ..... \$1.87	500μA ..... \$1.87	100-100μA ..... \$1.75	200μA ..... \$1.75	500μA ..... \$1.60	500-500μA ..... \$1.87	1mA ..... \$1.87	1-0-1mA ..... \$1.87	2mA ..... \$1.87	5mA ..... \$1.87	10mA ..... \$1.87	20mA ..... \$1.87	50mA ..... \$1.87	100mA ..... \$1.87	150mA ..... \$1.87	5 amp. .... \$1.50	10V. D.C. .... \$1.50	50V. D.C. .... \$1.50	100-100μA ..... \$1.87	200μA ..... \$1.60	500μA ..... \$1.60	500-500μA ..... \$1.87	1mA ..... \$1.50	10mA ..... \$1.50	100mA ..... \$1.50	500mA ..... \$1.50	1 amp. .... \$1.50
-------------------	------------------------	--------------------	------------------------	--------------------	--------------------	------------------------	------------------	----------------------	------------------	------------------	-------------------	-------------------	-------------------	--------------------	--------------------	--------------------	-----------------------	-----------------------	------------------------	--------------------	--------------------	------------------------	------------------	-------------------	--------------------	--------------------	--------------------

### "SEW" BAKELITE PANEL METERS

#### Type MR.55P. 3 1/2 in. x 3 1/2 in. fronts.



50μA ..... \$3.37	50-50μA ..... \$2.75	100μA ..... \$2.60	100-100μA ..... \$2.37	200μA ..... \$2.60	500μA ..... \$2.97	500-500μA ..... \$2.10	1mA ..... \$2.10	5mA ..... \$2.10	10mA ..... \$2.10	50mA ..... \$2.10	100mA ..... \$2.10	500mA ..... \$2.10	1 amp. .... \$2.10	10V. D.C. .... \$2.10	20V. D.C. .... \$2.10	50V. D.C. .... \$2.10	150V. D.C. .... \$2.10	300V. D.C. .... \$2.10	15V. A.C. .... \$2.10	300V. A.C. .... \$2.10	8 Meter 1mA ..... \$2.10	5 Meter 1mA ..... \$2.10	1 amp. A.C. .... \$2.10	5 amp. A.C. .... \$2.10	10 amp. A.C. .... \$2.10	20 amp. A.C. .... \$2.10	30 amp. A.C. .... \$2.10	5V. D.C. .... \$2.10
-------------------	----------------------	--------------------	------------------------	--------------------	--------------------	------------------------	------------------	------------------	-------------------	-------------------	--------------------	--------------------	--------------------	-----------------------	-----------------------	-----------------------	------------------------	------------------------	-----------------------	------------------------	--------------------------	--------------------------	-------------------------	-------------------------	--------------------------	--------------------------	--------------------------	----------------------

#### Type MR.55P. 2 1/2 in. square fronts.



50μA ..... \$2.25	50-50μA ..... \$2.10	100μA ..... \$2.10	100-100μA ..... \$1.87	200μA ..... \$1.60	500μA ..... \$1.60	500-500μA ..... \$1.50	1mA ..... \$1.50	10mA ..... \$1.50	50mA ..... \$1.50	100mA ..... \$1.50	500mA ..... \$1.50	1 amp. .... \$1.50	5 amp. .... \$1.50	10V. D.C. .... \$1.50	50V. D.C. .... \$1.50	100-100μA ..... \$1.87	200μA ..... \$1.60	500μA ..... \$1.60	500-500μA ..... \$1.50	1mA ..... \$1.50	10mA ..... \$1.50	50mA ..... \$1.50	100mA ..... \$1.50	500mA ..... \$1.50	1 amp. .... \$1.50
-------------------	----------------------	--------------------	------------------------	--------------------	--------------------	------------------------	------------------	-------------------	-------------------	--------------------	--------------------	--------------------	--------------------	-----------------------	-----------------------	------------------------	--------------------	--------------------	------------------------	------------------	-------------------	-------------------	--------------------	--------------------	--------------------

**\*MOVING IRON— ALL OTHERS MOVING COIL**  
Please add postage

### SEW EDUCATIONAL METERS



Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible to demonstrate internal working. Available in the following ranges:

50μA ..... \$4.50	20V. d.c. .... \$3.97
100μA ..... \$4.25	50V. d.c. .... \$3.97
1mA ..... \$3.97	300V. d.c. .... \$3.97
50-0-50μA ..... \$4.25	
1-0-1mA ..... \$3.97	
1A d.c. .... \$3.97	500mA/5A d.c. \$4.25
5A d.c. .... \$3.97	5V/50V d.c. .... \$4.25
10V d.c. .... \$3.97	

### EDGWISSE METERS

Type PE.70. 3 17/32 in. x 1 15/32 in. x 2 1/2 in. deep.

50μA ..... \$3.00	500μA ..... \$3.60
50-0-50μA ..... \$3.87	1mA ..... \$3.87
100μA ..... \$3.87	300V. A.C. .... \$3.87
100-0-100μA ..... \$2.75	50 amp. D.C. .... \$2.75
200μA ..... \$2.75	VU Meter ..... \$3.25

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

# MULTIMETERS for EVERY purpose!

**TECH FT-34. 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/10/100/500mA. D.C. 0/100K. \$1.97. P. & P. 12tp.**



**HONOR TE.10A 20K Ω/Volt 6/25/50/250/500/2,500 V. D.C. 10/50/100/500/1,000 V. A.C. 0/800mA/2.5mA/250mA. D.C. 0/6K/6 meg. ohm. -20 to +22 db. 10-0, 100 mid. 0.100-0.1 mid. \$3.47. P. & P. 15tp.**



**MODEL TE-200 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000 V.D.C. 0/10/50/250/1,000 V. A.C. 0/80 uA/250 mA. 0/600 Meg Ω. -20 to +62 db. \$3.75. P. & P. 15tp.**



**MODEL TE-70 30,000 O.P.V. 0/3/15/75/300/600/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/300A/3/30/300mA. 0/16K/160K/1.6M/1.6 Meg Ω. \$5.50. P. & P. 15tp.**



**MODEL TE-12 20,000 O.P.V. 0/0.5/6/30/120/600/1,200/3,000/6,000V. D.C. 0/6/30/120/600/1,200V. A.C. 0/600A/6/60/600K/6Meg. 60 Meg Ω. 5 P. 17tp.**



**MODEL TE-90 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200 V. D.C. 0/6/30/120/300/1,200 V. A.C. 0/300A/300mA. D.C. 16K/160K/1.6M MEG Ω. -20 to +63 db. \$7.50. P. & P. 15tp.**



**MODEL PL436 20K Ω/Volt D.C. 8k Ω/Volt A.C. Mirror scale. 0/3/12/30/120/600V. D.C. 3/30/120/600V. A.C. 50/600mA/60/600 mA. 10/100K/1 Meg/1 Meg/10 Meg Ω. -20 to +46db. \$6.97. P & P 12tp**



**MODEL 500 80,000 O.P.V. with overload protection. Mirror scale 0/5/25/50/100/250/500/1,000V. D.C. 1/2-5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg. 180 Meg Ω. \$3.87. Post paid.**



**SKYWOOD SW-500 50K Ω/Volt. Mirror scale DC Volts 0.3/12/30/300/600. DC Current 200A/60/600mA. AC 0/30/120/600mA. D.C. 16K/160K/1.6M MEG Ω. Meg. Decibels -20 to +57 db. \$7.50. P. & P. 15tp.**



**MODEL AS-100D. 100K Ω/Volt. 5in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200 V. D.C. 0/6/30/120/300/600 V. A.C. 0/100A/100/300mA/12 Amp. 0/2K/200K/2M/200K Ω. -20 to +17 db. \$12.50. P. & P. 17tp.**



**TE-900 20,000 Ω/VOLT GIANT MULTIMETER. Mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/25/100/500/250 V. A.C. 0/25/12.5/10/50/250/1,000/5,000 V. D.C. 0/500μA/110/100/500mA/10 amp. D.C. 0/2K/200K/20 MEG. OHM. \$15. P. & P. 25tp.**



**TEK LAB TESTER. 100,000 O.P.V. 6pin. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω/Volt A.C. D.C. Volts: 5, 2.5, 1.0, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K. 5 MEG Ω. Decibels: -20 to +52 db. \$11.50. P. & P. 17tp.**



**TEK MODEL TW-200B FEATURABLE OVERLOAD RESISTANCE. 20K Ω/Volt D.C. 5K Ω/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K. 5 MEG Ω. Decibels: -20 to +52 db. \$11.50. P. & P. 17tp.**



**TEK LAB TESTER. 100,000 O.P.V. 6pin. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K Ω/Volt A.C. D.C. Volts: 5, 2.5, 1.0, 50, 250, 1,000V. A.C. Volts: 3, 10, 50, 60, 250, 500, 1,000V. D.C. Current: 10, 100mA, 10, 100, 500mA, 2.5, 10. 100 MEG Ω. Decibels: -10 to 49 db. Plastic Case with Carrying Handle. Size 7 1/2 in. x 3 1/2 in. \$18.90. P. & P. 25tp.**



**70° WIDE ANGLE 1mA METERS**  
MW1-6 60mm square \$3.97  
MW1-8 80mm square \$4.97  
P. & P. extra



**TE-40 HIGH SENSITIVITY A.C. VOLTMETER**  
10 meg. input 10 ranges: 0/1/008/1/3/1/3/10/30/100/300V. R.M.S. 4cps.-1-2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 280V. A.C. \$17.50. Carr. 25p.



**TE-45 VALVE VOLTMETER**  
High quality instrument with 28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. \$17.50. P. & P. 30p. Additional probes available: R.P. \$2.12; H.V. \$2.50.



**FTC-401 TRANSISTOR TESTER**  
Full capabilities for measuring A, B and ICO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. \$6.97. P. & P. 15tp.



**HONEYWELL DIGITAL VOLTMETER VT.100**  
Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.3 ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999) Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60-cycles. Overall size: 5 1/2 in. x 2 1/2 in. x 3 1/2 in.



**£49-97 1/2 Carr. 50p.**

**G. W. SMITH & CO (RADIO) LTD.**  
Also see next two pages

www.americanradiohistory.com

535

# SEMI-CONDUCTOR VALVES

## ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3415	2N3417	2N3418	2N3419	2N3549	2N3550
2N3415	2N3417	2N3418	2N3419	2N3550	

Integrated Circuits	FJH101	FJH111	FJH121	FJH991	FJH1001
FJH101	FJH111	FJH121	FJH1001	

### VALVES

Valves	6X4	6X5	6X6	6X7	6X8	6X9	6X10	6X11	6X12	6X13	6X14	6X15	6X16	6X17	6X18	6X19	6X20	6X21	6X22	6X23	6X24	6X25	6X26	6X27	6X28	6X29	6X30	6X31	6X32	6X33	6X34	6X35	6X36	6X37	6X38	6X39	6X40	6X41	6X42	6X43	6X44	6X45	6X46	6X47	6X48	6X49	6X50	6X51	6X52	6X53	6X54	6X55	6X56	6X57	6X58	6X59	6X60	6X61	6X62	6X63	6X64	6X65	6X66	6X67	6X68	6X69	6X70	6X71	6X72	6X73	6X74	6X75	6X76	6X77	6X78	6X79	6X80	6X81	6X82	6X83	6X84	6X85	6X86	6X87	6X88	6X89	6X90	6X91	6X92	6X93	6X94	6X95	6X96	6X97	6X98	6X99	6X100
6X4	6X5	6X6	6X7	6X8	6X9	6X10	6X11	6X12	6X13	6X14	6X15	6X16	6X17	6X18	6X19	6X20	6X21	6X22	6X23	6X24	6X25	6X26	6X27	6X28	6X29	6X30	6X31	6X32	6X33	6X34	6X35	6X36	6X37	6X38	6X39	6X40	6X41	6X42	6X43	6X44	6X45	6X46	6X47	6X48	6X49	6X50	6X51	6X52	6X53	6X54	6X55	6X56	6X57	6X58	6X59	6X60	6X61	6X62	6X63	6X64	6X65	6X66	6X67	6X68	6X69	6X70	6X71	6X72	6X73	6X74	6X75	6X76	6X77	6X78	6X79	6X80	6X81	6X82	6X83	6X84	6X85	6X86	6X87	6X88	6X89	6X90	6X91	6X92	6X93	6X94	6X95	6X96	6X97	6X98	6X99	6X100	

See previous page • G. W. SMITH & Co. (RADIO) LTD. • See opposite page

# HI-FI EQUIPMENT

SAVE UP TO  
**33 1/3% OR MORE**  
SEND S.A.E. FOR  
DISCOUNT PRICE LISTS  
AND PACKAGE OFFERS!



## RECORD DECKS

<b>B.S.R.</b>		
MI20* Mono†	£4-97	
CI20*	£8-70	
MP60	£11-30	
610	£15-15	
510	£12-47	
310	£10-55	
MP60 T.P.D.I.	£18-75	
MP60 T.P.D.2	£17-55	
610 T.P.D.1	£22-12	
510 T.P.D.1	£20-19	
210 Package*	£11-30	
H.T.70	£16-80	
H.T.70 Package	£24-00	
<b>THORENS</b>		
TD125	£59-65	
TD125AB	£94-25	
TX25	£6-70	
TD150AI	£34-60	
TD150AIII	£41-35	
TX11	£3-77	

† Mono \* Stereo Cartridge  
All other models less Cartridge  
Carriage 50p extra any model.

## RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cartridge.

Garrard 2025 T/C with Sonotone	£18-95
Garrard 320II Goldring G800	£20-65
Garrard AP78 Goldring G800	£21-00
BSR MP60 Audio Technica AT.55	£27-50
Golding GL69/2 Goldring G800	£45-50
Golding GL75 Goldring G800E	£50-00

Carriage 50p extra any model.

## SINCLAIR EQUIPMENT

Project 60. Package offers.

2 x Z80 amplifier, stereo 60 pre-amp, PZ5 power supply, £18-75 Carr. 37p. Or with PZ8 power supply £19-95 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply, £20-25 Carr. 37p. Transformer for PZ3, £2-97; extra. Add to any of the above £4-87; for active filter unit and £16 for a pair of Q16 speakers. Project 60 FM Tuner £20-97; Carr. 37p. All other Sinclair products in stock. 2000 Amp £24-50 Carr. 37p.; 3000 Amp £31-50 Carr. 37p.; Neoteric Amp £45-97; Carr. 37p. IC10/IC12 £2-50

## LATEST CATALOGUE



SEND NOW!  
•  
STILL ONLY  
**37 1/2 p**  
P & P  
10p

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

## TELETON SAQ-206 STEREO AMPLIFIER



Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List £32.50 OUR PRICE £18-50 Carr. 37p.

## TELETON SPECIAL OFFER!



CR10T AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR SA1008 SPEAKER SYSTEMS. Output 4 watts per channel. Excellent reception. AFC, built-in MPX. Car/XTAL Input. Total List £50-25. OUR PRICE £29-95. Carr. 62p. Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired £42-50. Carr. £1-00.

## ★ TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2in. 3 I.F. stages. Double tuned discriminator. Amplify output to feed most 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6-87; P. & P. 12p. Stereo multiplex adapters £4-97;.



TE-1085 STEREO HEADPHONES  
Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedance. 25-18,000 Hz. With lead and stereo jack plug. ONLY £1-97; P. & P. 12p

## BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Size 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max +10 dB complete with calibrator K ohms. Operation 220/240V. A.C. Size 216mm x 150mm x 120mm. Price £27-50. Carr. 25p.


## TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-300 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instructions. £15. P. & P. 37p. S.A.E. for details.

## B.C. 221 FREQUENCY METERS

latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27-50 each. Carr. 50p.
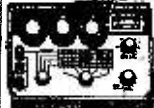
## TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 Ω-11 meg Ω. 6 Ranges ± 1%. L. 1 μH-1111 HENRYs. C. Ranges 2-2% C. 10pF-1110mFd. 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/4 x 5 x 2 1/2in. £20. P. & P. 25p



TE-16A Transistorised Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800kHz modulation. 5 1/2 x 5 1/2 x 3 1/2in. Complete with instructions and leads. £7-97; P. & P. 20p.

## LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mFd. 20 ohms 200 megohms. Also checks impedance, turns ratio, insulation. 200/250V. A.C. Brand New £17-50. Carr. 37p.

## RUSSIAN 22 RANGE MULTIMETER

Model U437 20,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100 μA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £5-97 P. & P. 25p.

## RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band, Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 2 sec to 100 milli sec/cm. Supplied complete with all accessories and instructions £27. Carr. paid.

## TEIII. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections, Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200/300/1000/2500 cps. Accuracy: 0.05dB. + Indication dB 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new. £27-50. P. & P. 25p.

## ROUND SCALE TYPE PENCIL TESTER MODEL TS.68

Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V A.C. and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY £1-97 P. & P. 13p.

## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush type. Continuous rating. Wide range ex-stock. Single hole fixing, 1/4in. dia. shafts. Bulk quantities available. 50 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 72p; P. & P. 7p. 100 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, £1-05 P. & P. 7p. 500 WATT. 15/50/250/1000/2500/5000 or 25000 ohms, £1-37; P. & P. 7p.

## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality . Low price . Immediate delivery	
<b>S-860 General Purpose Bench</b>	<b>S-280B Panel Mounting</b>
1 Amp £5-50	1 Amp £5-50
2.5 Amp £6-75	2.5 Amp £6-62;
5 Amp £9-75	Please add postage
8 Amp £14-50	ALL MODELS
10 Amp £18-50	INPUT 230 VOLTS,
12 Amp £21-00	50/60 CYCLES,
20 Amp £27-00	OUTPUT VARIABLE
	0-260 VOLTS.

Special discounts for quantity

**UR-1A SOLID STATE COMMUNICATION RECEIVER**  
4 Bands covering 550kc/s-30mc/s. FET, S. Meter, Variable BFO for SSB, Built-in Speaker, Bandsread, Sensitivity Control. 220/240V. A.C. or 12V D.C. 10" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37p.

**UNR-30 RECEIVER**  
4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 320/240V. A.C. Brand new with instructions. £15-75. Carr. 37p.

**LAFAYETTE HA-600 SOLID STATE RECEIVER**  
General coverage 150-400kc/s, 560 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, S. Meter, Bandsread. RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12V. D.C. Brand new with instructions. £45. Carr. 50p.

**CRYSTAL CALIBRATORS NO. 10**  
Small portable crystal controlled wavemeter. Size 7 x 7 x 4in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on optional). (B. Monocycle). Calibrated dial. Power requirements 300V. D.C. 15mA and 12V D.C. 0.3A. Excellent condition. £4-47; Carr. 37p.

**SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS**  
Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 20V-230V. Model MR 3205 5 amp 68 x 45 x 45mm £3-71; £11-97; Postage 12p.

**AUTO TRANSFORMERS**  
0/115/230V. Step up or step down. Fully shrouded.  
150 W. £2-37; P. & P. 17p  
300 W. £2-25 P. & P. 22p  
500 W. £4-97; P. & P. 32p  
1000 W. £7-25 P. & P. 37p  
1500 W. £9-97; P. & P. 42p  
5000 W. £28-00 P. & P. £1

**VOLTAGE STABILISER TRANSFORMERS**  
180-280V. input. Output 230V. Available 150w or 225w. £19-50. Carr. 25p.

**230 VOLT A.C. 50 CYCLES RELAYS**  
Brand new 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40). Quantities available.

**G.W. SMITH & CO. (RADIO) LTD**

27 TOTTENHAM CT. RD. LONDON, W1 Tel: 01-636 3715  
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 3204  
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-5 MONDAY TO SATURDAY

All Mail Orders to:-  
11-12, Paddington Green,  
London, W.2  
Tel: 01-262 6562  
1 pds supplied

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-722-9090

OA2	.30	6CL6	.48	6X5GT	.25	20P1	.88	AC/TP	.98	ECC81	.16	EM80	.38	N339	.44	PL504/500	.48	UCL83	.48	AC107	.15	BCZ11	.38	OA73	.15
OB2	.30	6CU5	.50	7A7	.88	20P2	.88	AL60	.78	ECC82	.19	EM81	.39	P1	.43	PL505	1.30	UP41	.50	AC113	.25	BF158	.29	OA78	.08
IA7GT	.33	6CW4	.63	7B7	.38	20P4	.89	ATP4	.12	ECC83	.22	EM83	.75	PC86	.48	PL508	.90	UP80	.35	AC128	.20	BF163	.20	OA85	.08
IB3GT	.37	6DE7	.50	7BT	.35	20P6	1.00	AZ1	.40	ECC84	.28	EM84	.81	PC88	.48	PL509	1.30	UP85	.34	AC156	.20	BF173	.38	OA90	.13
IF5GT	.36	6DT6	.60	7C6	.60	25A6G	.29	AZ21	.40	ECC85	.25	EM87	.35	PC89	.45	PL512	.75	UP86	.63	AC157	.25	BF180	.30	OA91	.09
II4	.15	6EW6	.65	7HT	.23	25L8G	.22	AZ41	.58	ECC86	.40	EY61	.38	PCF20	.28	PL515	1.16	UP87	.54	AC166	.25	BF181	.40	OA95	.09
IN3GT	.37	6F1	.59	7RT	.45	25Y5	.35	CL33	.90	ECC88	.45	EY81	.35	PCF22	.30	PL518	.50	UM80	.33	AC177	.28	BFY50	.38	OC22	.38
IR5	.27	6F6	.63	7Z4	.50	25Y5G	.43	CY1C	.63	ECC189	.48	EY83	.55	PCF24	.40	PL520	.75	UY21	.55	ACY18	.20	BFY52	.20	OC24	.88
184	.22	6F6G	.65	9D7	.78	25Z4G	.30	CY31	.81	ECC804	.55	EY84	.50	PCF28	.44	PL522	.75	UY41	.38	ACY19	.19	BY100	.18	OC25	.38
1U4	.29	6F13	.33	10C1	1.25	25Z5	.40	DAF91	.20	ECC807L	.70	EY87/6	.30	PCF30	.28	PL523	.75	UY51	.25	ACY20	.18	BY105	.18	OC26	.24
1U5	.48	6F14	.43	10C2	.50	25Z6G	.43	DAF96	.33	ECC808	.27	EY88	.43	PCF32	.30	PL524	.75	UY61	.45	ACY21	.19	BY114	.18	OC28	.60
2D21	.35	6F18	.45	10D17	.50	30C1	.28	DF91	.14	ECC828	.27	EY91	.53	PCF34	.40	PL525	.75	UY71	.45	ACY22	.19	BY126	.15	OC29	.63
3D6	.19	6F22	.68	10F9	.45	30C15	.60	DF95	.33	ECC866	.65	EZ40	.40	PCF36	.44	PL526	.75	UY81	.45	ACY23	.19	BY137	.18	OC35	.32
3Q4	.38	6F24	.68	10F18	.35	30C17	.77	DF97	.63	ECC8042	.10	EZ41	.43	PCF38	.68	PL527	.75	UY91	.68	ACY24	.20	CG12E	.20	OC36	.43
3Q5GT	.35	6F25	.68	10LD11	.53	30C18	.60	DI76	.68	EZ20	.21	EZ21	.22	PCF40	.67	PL528	.75	UY92	.68	ACY25	.20	CG12E	.20	OC37	.27
384	.27	6F28	.70	10P13	.54	30F5	.70	DK40	.55	ECH42	.61	EZ21	.22	PCF42	.44	PL529	.75	UY93	.68	ACY26	.20	CG12E	.20	OC38	.43
3V4	.32	6F28	.70	10P13	.54	30F5	.70	DK40	.55	ECH42	.61	EZ21	.22	PCF42	.44	PL529	.75	UY93	.68	ACY26	.20	CG12E	.20	OC38	.43
5V4G	.35	6GH8A	.15	10P14	1.10	30F1L	.60	DK92	.38	ECH81	.27	EZ20	.20	PCF44	.33	PL530	1.98	UY94	.68	ACY27	.20	CG12E	.20	OC39	.63
5V4G	.35	6GH8A	.15	10P14	1.10	30F1L	.60	DK92	.38	ECH81	.27	EZ20	.20	PCF44	.33	PL530	1.98	UY94	.68	ACY27	.20	CG12E	.20	OC39	.63
5V4G	.35	6GH8A	.15	10P14	1.10	30F1L	.60	DK92	.38	ECH81	.27	EZ20	.20	PCF44	.33	PL530	1.98	UY94	.68	ACY27	.20	CG12E	.20	OC39	.63
5V4G	.35	6GH8A	.15	10P14	1.10	30F1L	.60	DK92	.38	ECH81	.27	EZ20	.20	PCF44	.33	PL530	1.98	UY94	.68	ACY27	.20	CG12E	.20	OC39	.63
5V4G	.35	6GH8A	.15	10P14	1.10	30F1L	.60	DK92	.38	ECH81	.27	EZ20	.20	PCF44	.33	PL530	1.98	UY94	.68	ACY27	.20				

# new

## Super IC-12



### High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

#### SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

**Output power** 6 watts RMS continuous (12 watts peak).

**Frequency Response** 5 Hz to 100KHz  $\pm$  1 dB.

**Total Harmonic Distortion** Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

**Load Impedance** 3 to 15 ohms.

**Power Gain** 90dB (1,000,000,000 times) after feedback.

**Supply Voltage** 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

**Size** 22 x 45 x 28 mm including pins and heat sink.

**Input Impedance** 250 Kohms nominal.

**Quiescent current** 8mA at 28 volts.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.



Price, inc. FREE printed circuit board for mounting.





**£2.98** Post free

Sinclair Radionics Ltd, London Rd, St. Ives Huntingdonshire PE17 4HJ  
Telephone St Ives (048 06) 4311

## sinclair
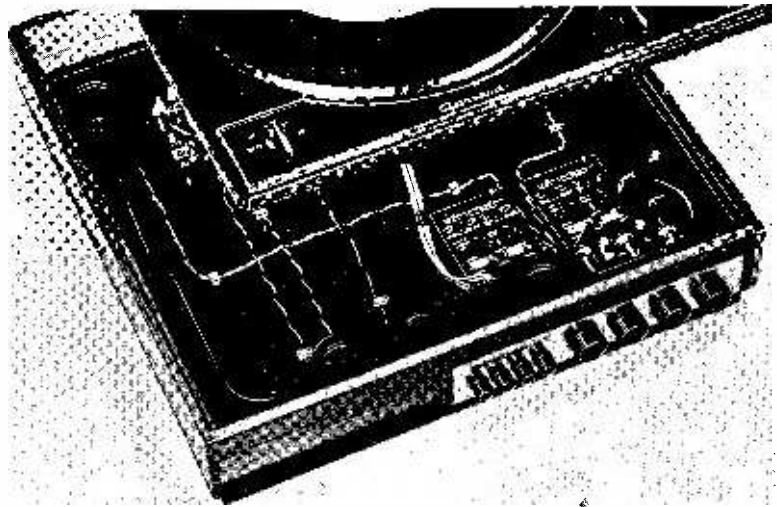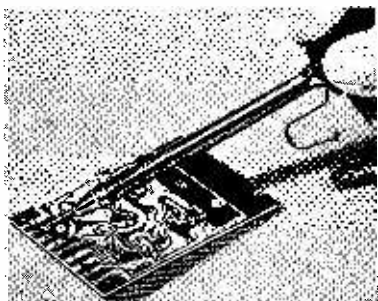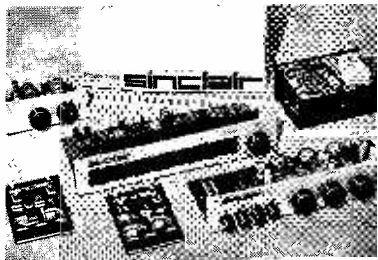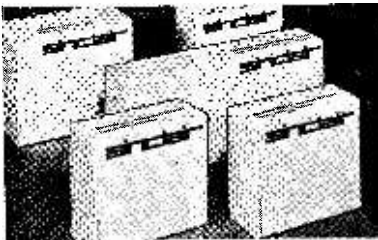
# Sinclair Project 60

The World's leading range of high fidelity modules



Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.

#### Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control	<b>£4.48</b>
Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U. volume control etc.	<b>£9.45</b>
20 + 20 W. stereo amplifier for most needs	<b>2 x Z.30s, Stereo 60, PZ.5</b>	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	<b>£23.90</b>
20 + 20 W. stereo amplifier with high performance spkrs.	<b>2 x Z.30s, Stereo 60, PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
40 + 40 W. R.M.S. de-luxe stereo amplifier	<b>2 x Z.50s, Stereo 60 PZ.8, mains trsfmr</b>	As above	<b>£34.88</b>
Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>


F.M. Stereo Tuner (**£25**) & A.F.U. Filter Unit (**£5.98**) may be added as required.

Sinclair Radionics Limited, London Road,  
St. Ives, Huntingdonshire PE17 4HJ.  
Tel : St. Ives (048 06) 4311

**sinclair**

# from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

## Z.30 & Z.50 power amplifiers

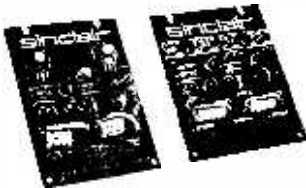

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).**

### Power Outputs

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

**Frequency response:** 30 to 300,000Hz  $\pm 1$  dB.

**Distortion:** 0.02% into 8 ohms.

**Signal to noise ratio:** better than 70dB unweighted.

**Input sensitivity:** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

**Size:** 14 x 80 x 57 mm.

### Z.30

Built, tested and guaranteed with circuits and instructions manual. **£4.48**

### Z.50

Built, tested and guaranteed with circuits and instructions manual. **£5.48**

## Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.


**PZ.5** 30 volts un stabilised **£4.98**

**PZ.6** 35 volts stabilised **£7.98**

**PZ.8** 45 volts stabilised

(less mains transformer) **£7.98**

**PZ.8** mains transformer **£5.98**

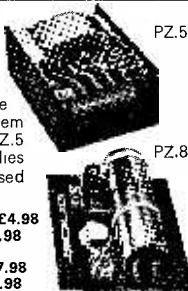

## Project 60 Stereo F.M. Tuner



*First in the world to use the phase lock loop principle*

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 2 $\mu$ V for 30dB quieting; 7 $\mu$ V for full limiting. **Squelch level:** 20 $\mu$ V. **A.F.C. range:**  $\pm 200$  KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz ( $\pm 1$ dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 $\mu$ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Mains on; Stereo on; tuning. **Size:** 93 x 40 x 207 mm.

Built and tested. Post free.

**£25**

## Stereo 60 Pre-amp/control unit



Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.


**SPECIFICATIONS—Input sensitivities:** Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve  $\pm 1$ dB; 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; A.U.—up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +15 to -15dB at 10 KHz; BASS +15 to -15dB at 100Hz.

**Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed.

**£9.98**

## A.F.U. High & Low Pass Filter Unit

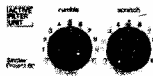

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages—rumble (high pass) and scratch (low pass). Supply voltage—15 to 35V. Current—3mA. H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) (0.02% at rated output. **Size:** 66 x 40 x 90 mm.

Built tested and guaranteed.

**£5.98**

## The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

I enclose cash/cheque/money order.

PW 10

**VALVES**

All prices in pounds and new prices																						
6BA6	25	6J6	20	7C5	£1-13	12SR7	35	37	40	DAF91	25	E8L31	£1-38	EL41	55	N78	£1-00	PL504	80	U404	40	
6BE6	30	6J7M	45	7C6	75	14H7	50	42	50	DAF96	42	EC90	33	EL42	58	N108	£1-50	PL508	90	U801	£1-18	
6BH6	45	6J7G	30	7D5	55	19AQ5	40	50B5	45	DC900	£1-00	ECC81	33	EL84	35	OA2	38	PL509	£1-45	UABC80	35	
1A7GT	40	6J3GT	45	7H7	55	20D11	50	50C5	40	DF38	48	ECC82	30	EL95	35	OC2	38	PL502	£1-45	UAF42	55	
1CP31	£6-00	6RQ7A	40	8K6GT	55	7Z7	70	20F2	70	50C0D6G	£1-55	DF70	45	ECC83	30	OL20	£1-00	OZ4	40	EX4	£2-00	
LD5	40	6KR7	65	8K7M	25	7S7	£2-25	20L1	£1-10	50L6GT	50	DF81	25	EC834	30	EM84	30	PC86	60	EX25	£2-00	
LE3	45	6K7C	30	7Y4	50	20P2	£1-10	75	50	DF92	20	ECC85	25	EM80	40	PC88	60	PC88	60	UBP80	45	
IN5GT	48	6BS7	£1-50	6K7GT	35	9BW6	50	20P5	£1-20	78	45	DF96	48	ECC88	40	EM81	63	PC97	50	Y81	30	
IR5	35	6BW6	85	6K8M	60	10C2	35	25A6	35	80	DH3-91	£6-00	ECH21	63	EM84	38	PC884	40	Y82	30		
IS4	27	6BW7	70	6K8G	35	10F1	90	25L6GT	45	85A2	40	DH77	30	ECH35	60	EY51	40	PC899	53	Y83	38	
IS5	25	6C4	33	6K8GT	50	10F3	90	25Y5	60	160B2	60	DK32	40	ECH42	70	EY86	40	PC189	55	Y800	£1-00	
IT4	25	6C5G	30	6K25	75	10F9	50	25Z4	45	10C4	60	DK91	50	DF1	25	EC834	30	PC89	38	Y800	£1-00	
IA4	35	6C5	50	6L6C	45	10F18	50	25Z6GT	55	801	50	DK92	50	ECC83	43	EZ40	45	PCF82	35	Y801	50	
3Q4	40	6CD6G	£1-20	6L18	45	10LD11	60	25Z6	65	807	50	DK96	42	ECL80	40	EZ41	48	PCF84	50	R2	60	
8Q5	45	6CH6	55	6Q7G	30	10P13	68	30C1	33	813USA	£3-75	DL66	£1-25	ECL82	65	EZ80	28	PCF86	60	R19	40	
3S4	35	6CW4	63	6Q7GT	43	11E3	£4-00	30C15	80	866A	75	DL92	35	ECL83	65	EZ81	28	PCF81	50	S130	£1-75	
3V4	45	6D6	25	68A7M	40	12A7E	30	30C17	35	954	60	DL93	35	ECL86	45	GY501	80	PCF802	50	SP4	50	
5R4GY	60	6E2	38	68CTM	70	12A77	30	30C18	78	1025	40	DL94	45	ECL800	40	EZ82	£1-50	PCF806	70	SP41	45	
5V4G	42	6F5G	50	68HTM	35	12A7U	30	30F1L	75	5763	70	DL96	48	EF9	£1-00	GZ34	60	PCF808	78	STV280/50	UM80	
5Y3GT	38	6F6G	30	68J7GT	30	12A7X	30	30F1L2	95	7193	20	DM70	40	EF37A	60	HN309	£1-50	PCF82	38	U10	£10-00	
5Z4G	40	6F8G	35	68K7GT	30	12BA6	35	30F1L4	75	7475	40	DY86	33	EF39	40	K736	£1-00	PCF83	58	SU25	£1-00	
6/30L2	75	6F11	38	68L7GT	35	12BE6	35	30L15	85	A61	48	DY87	35	EF41	65	K761	£1-25	PCF84	48	UT2160	75	
6A7	75	6F13	38	68N7GT	35	12C9GT	35	30L17	85	ATP4	35	EB8CC	65	EF50	25	K766	£1-70	PCF85	40	T41	£1-00	
6A8G	63	6F14	65	68Q7GT	40	12E1	£1-35	30P4	£1-12	ATP5	60	EAS0	28	EF80	25	K781	£1-75	PCF86	45	TD4	50	
6AK5	30	6F23	80	6T4GT	60	12J5GT	30	ATP7	80	EABCS0	50	EAF85	35	EF88	35	K781(7C5)	PD500	£1-50	TH41	£1-75	UY41	45
6AM5	32	6F25	75	6V6M	60	12J7GT	35	30P19	80	AU2	£4-00	BAF42	55	EF86	33	£1-13	PEN4A	£1-00	U10	60	UY85	33
6AM6	33	6F28	70	6V6G	30	12K8GT	50	30P1L3	93	AZ1	48	EBB33	50	EF91	33	KTW61	£1-00	PEN45	40	U19	£2-50	
6AQ5	35	6F32	25	6V6GT	30	12Q7GT	35	30P1L4	90	AZ31	55	EBB41	55	EF92	40	KTZ41	45	PEN46	40	U26	78	
6AS7G	80	6G6	25	6X4	30	12SA7GT	40	38A5	75	CB13L	90	EBB90	30	EF98	75	M14	88	PL36	55	U36	78	
6AT6	30	6H6	23	6X5G	35	12S7G	35	35L5	50	CB13S	75	EBF80	40	EF183	35	ML6	40	PL81	60	U76	80	
6AU6	25	6J5M	50	6X6GT	35	12S7E	30	38Z3	60	CY30	63	EBF89	33	EL32	30	MSP4	50	PL83	45	U91	80	
6B4G	£1-00	6J5G	30	7B6	70	12S77	30	35Z4GT	50	CY31	43	E8L1	70	EL33	63	MU14	60	PL84	40	U92	68	
6B8G	20	6J5GT	30	7B7	45	12S7K7	45	35Z5	40	DAC32	42	E8L21	60	EL34	53	MX40	63	PL500	80	U403	50	

**Transistors**

1N914	08	2N697	18	2N2218	30	2N4989	18	AD149	60	BC169C	13	GE782	25	NKT228	33	OA2200	55	OC81D	20	ZS170	10		
18115	25	2N706	10	2N2219	33	AAZ12	30	AD161	38	BF898	28	GJ7M	38	NKT211	24	OA2201	50	OC82	25	Z8271	18		
18092	28	2N1192	30	2N269A	20	AC126	25	AF115	30	BF750	28	KS100A	20	NKT765	25	OA2207	48	OC82D	15	U93	15		
2G302	23	2N1305	25	2N3026	13	AC137	25	AF117	25	BF751	20	MJ520	10	OA2210	48	OC84	25	OC84	25	Z1108	15		
2G371	23	2N2147	15	2N3702	18	ACY20	23	BC107	13	BY100	18	MJ2955	10	OA2222	40	OC58	60	OC170	30	Z1X300	13		
2N404	23	2N2160	63	2N3819	35	5C108	13	CR81-40	18	BY88	18	£1-75	OA81	10	OA2224	38	OC59	65	OC171	30	Z1X304	28	
						5C109	13	DD003	15	CR81-40	18	MJ3065	93	OA85	13	OA2241	23	OC71	15	OC200	40	Z1X500	20
						5C113	18	DD005	16	NKT212	27	OA91	08	OA2242	23	OC72	25	OC72	25	OC72	25	Z1X503	20
						5C119	13	GET102	30	NKT214	15	OA211	38	OA2246	23	OC81	25	ORF12	50	Z1X531	30		30

**TRANSISTOR POSTAGE 1p EACH, OVER 10 POST FREE**

Express Postage & Insurance 5p one valve plus 1p each additional valve. ORDERS over £5 Post free. 6,000 types in stock send for lists, 5p.

# R.S.T.


**“Renowned for Service”**

**BLACKWOOD HALL, WELLFIELD RD., STREATHAM, SW16 2BF**

■ Tel. 01-769-0199/1649. Open to callers Mon-Sat 9 a.m.—5 p.m. Closed Saturday 1.00—2.30 p.m.

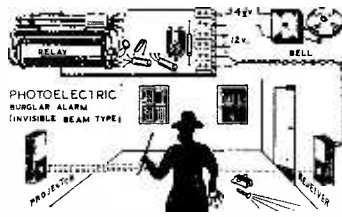**PHOTOELECTRIC KIT**

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



**PHOTOELECTRIC KIT**  
**£1.95**  
 Postage and Pack. 15p (UK)  
 Commonwealth:  
 SURFACE MAIL 20p  
 AIR MAIL £1.00  
 Australia, New Zealand,  
 S. Africa, Canada and U.S.A.  
 Also Essential Data Circuits  
 and Plans for Building  
 10 Advanced Designs

**INVISIBLE BEAM OPTICAL KIT**  
 Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.  
 CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price £1.00 Postage and Pack. 5p (U.K.). Commonwealth: Surface Mail 10p, Air Mail 30p.

**LONG RANGE INVISIBLE BEAM OPTICAL KIT**  
 CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £1.50. Postage and Pack 5p (U.K.). Commonwealth: Surface Mail 15p, Air Mail 50p.

**JUNIOR PHOTOELECTRIC KIT**  
 Versatile invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.  
 CONTENTS: Infra-Red Sensitive Photo-transistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet “10 Advanced Photoelectric Designs”.  
 Price £1.00. Postage and Pack. 5p (U.K.). Commonwealth 10p; Airmail 20p.

**JUNIOR OPTICAL KIT**  
 CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit.  
 Price 50p. Post. and Pack. 5p (U.K.). Commonwealth: Surface Mail 10p; Air Mail 20p.

**YORK ELECTRICS Mail Order Dept.**  
**335 BATTERSEA PARK RD., LONDON S.W.11**  
 Send S.A.E. for full details, a brief description of all Kits and Projects

**ELEKON STAR BARGAIN OFFERS**

ELECTROLYTIC AND PAPER CAPACITORS BY PLESSEY, C.O.L.L. HUNTS AND AMERICAN. Manufactured in 1968-69-70.

Capacitance in µF	Volt-inches	Size in inches	Terminals	Price in £ p	Postage	Capacitance in µF	Volt-inches	Size in inches	Terminals	Price in £ p	Postage
4	370V	2 1/2 x 2 1/2	T/E	0-40	0-08	4,000	50V	4 1/2 x 1 1/2	S/T	0-40	0-12
7	370V	2 1/2 x 3 x 2	T/E	0-40	0-09	5,000	55V	4 1/2 x 1 1/2	S/T	0-60	0-12
10	600V	4 x 3 x 2	T/E	0-60	0-10	6,600	50V	4 1/2 x 2 1/2	S/T	0-65	0-12
32	450V	1 1/2 x 1	T/E	0-20	0-05	7,000	50V	4 1/2 x 2 1/2	S/T	0-75	0-12
32	500V	2 x 1 1/2	C	0-20	0-05	8,000	50V	4 1/2 x 2 1/2	S/T	0-75	0-12
50	450V	3 x 1	W/E	0-20	0-05	9,200	35V	4 1/2 x 2 1/2	S/T	0-50	0-12
60	300V	3 x 1	C	0-30	0-05	10,000	70V	4 1/2 x 2 1/2	C	0-80	0-12
80	300V	2 1/2 x 1	W/E	0-30	0-05	13,000	38V	4 1/2 x 2 1/2	S/T	0-60	0-12
100	450V	3 x 1 1/2	C	0-35	0-05	14,000	35V	4 1/2 x 3	S/T	0-60	0-15
1,000	70V	3 x 1 1/2	C	0-35	0-05	20,000	50V	6 x 3	S/T	1-25	0-18
1,200	350V	4 1/2 x 2 1/2	C	0-20	0-15	33,000	25V	4 1/2 x 2 1/2	C	0-70	0-12
1,500	50V	4 1/2 x 1 1/2	C	0-35	0-08	34,800	40V	6 x 3	S/T	2-00	0-18
2,000	35V	4 x 1	C	0-40	0-07	100-4-200	300V	4 1/2 x 1 1/2	C	0-50	0-08
2,500	60V	4 1/2 x 1	C	0-40	0-07	100-4-200	275V	4 1/2 x 1 1/2	P.C.	0-50	0-08
3,000	100V	4 1/2 x 2 1/2	C	0-60	0-15	200-4-200	350V	4 1/2 x 1 1/2	C	0-50	0-12
3,600	20V	4 1/2 x 1 1/2	S/T	0-50	0-12						


T/E=Tag ends. C=Can. W/E=Wire end. S/T=Screw terminals. P.C.=Printed Circuit. The above references only a mere fraction of our huge stocks.  
**OSCILLOSCOPE TUBES CV2184** 4 volt heaters, £1.50, p.p. 25p.  
**MULLARD POWER DIODES** 0.2Z 224 6.3V 10 watts, 25p post free.  
**PLESSEY MOLDED TRACK POTENTIOMETERS** less Switch Linear. 470 ohms, 4.7K, 6.8K, 22K, 15p post free. 250+250 ohms ganged lin. pre-set, 25p post free.  
**OVER LOAD CUT-OUTS** BY SUNVIC CONTROLS. All types encased. Type F102-5M control volts 220/230, load watts 2,000, 50p, p.p. 15p. Type F103/3M control volts 220/230, load rating 15 amp, 75p, p.p. 25p. Type F106/3M control volts 220/230, Load watt 5,000, £1.25, p.p. 30p.  
**UNMASKED N.P.N. P.N.P. SILICON TRANSISTORS.** 75% guaranteed OK. 100 for only 50p. p.p. 10p.  
**PYE PUSH-BUTTON COIL PACK** for MW, LW, SW & FM wave-bands, 60p, p.p. 10p.  
**MULLARD BY127 DIODES,** 15p post free. Discount on quantities.  
**CASSETTE TAPES IN LIBRARY BOXES.** C90 62p or 3 for £1-80. C120, 75p or 3 for £2-15. All post free.  
**DOUBLE-SIDED COPPER LAMINATED BOARD** 12 x 12 x 1/8 ins. 25p, p.p. 8p.  
**G.P.O. TYPE 3000 RELAYS** from 1 ohm up to 40,000 ohms. Various contacts or made up to your requirements.  
 If you have difficulty in obtaining any electronic parts try our service next time. Our location nr. Goodge St. Station, opposite Heals of Tottenham Court Road.

**ELEKON ENTERPRISES**  
 12A TOTTENHAM STREET, LONDON W1P 9PQ Telephone 01-680-7891


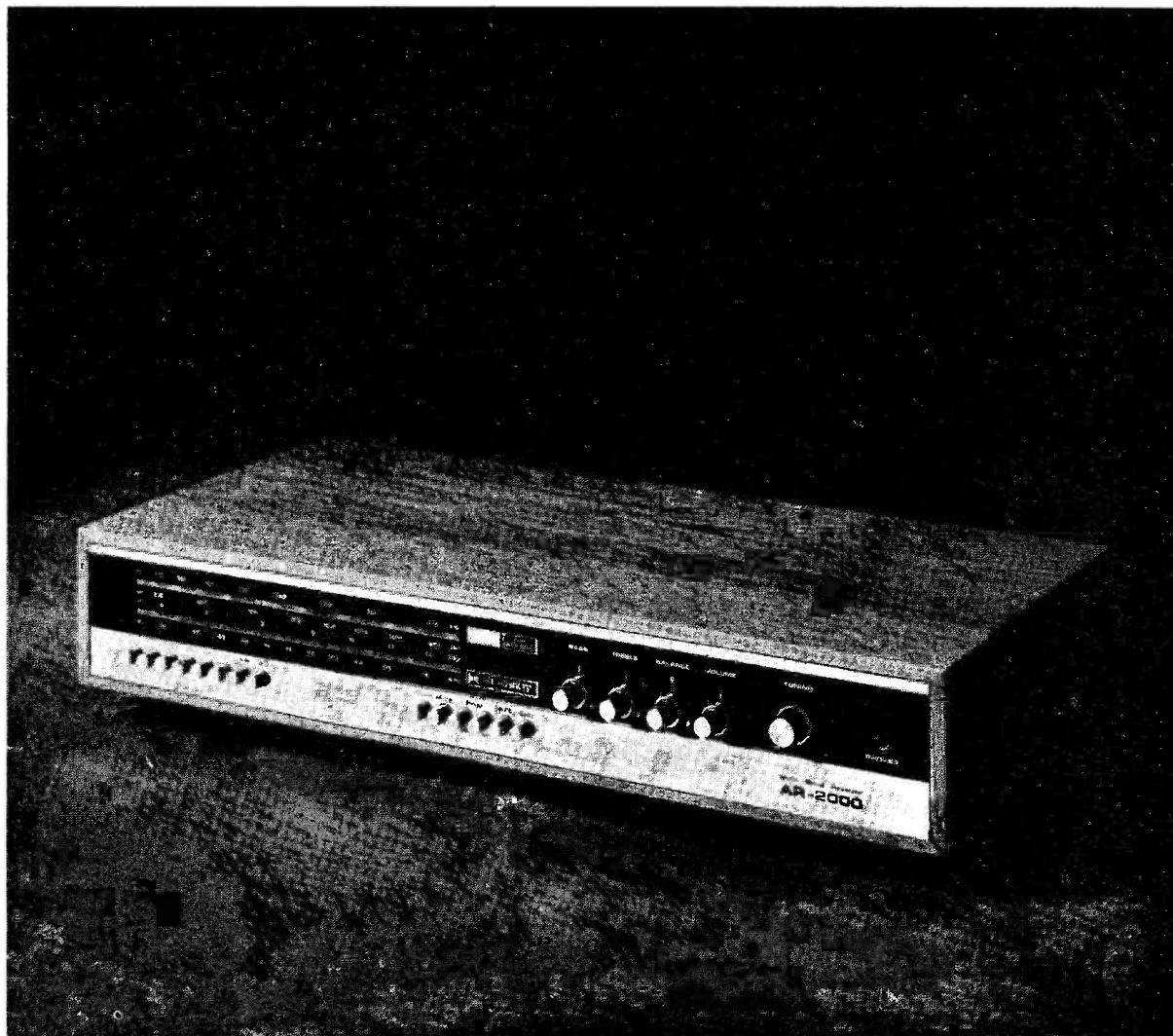
# Send for Heathkit – and send for the best

The best in hi-fi; the best in short-wave;  
the best in domestic, marine and auto equipment;  
the best in everything electronic.




The new AR 2000

Heathkit comes direct from the world's leading suppliers of top-quality electronic equipment. You assemble your components using the unique Heathkit 'step-and-check' method and there's a team of experts ready to help and advise you on any problem. But you won't need them. Hardly anyone does!

Send for your FREE catalogue – NOW.

-----  
Please send me details of your complete  
range of kits.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
Heath (Gloucester) Limited,  
Gloucester, GL2 6EE.  
  
A SCHMIDTKE COMPANY  
PW 10

# COMET

## HI-FI DISCOUNT WAREHOUSES

	Rec. Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>		
ALBA UA 700	34-50	26-00
ANSTRAD 8000	25-95	16-95
ARMSTRONG 521	56-00	42-50
DULCI 207M	62-00	21-95
FERROGRAPH F307	62-00	21-95
GOODMANS Maxamp	54-00	36-00
LEAK Stereo 30 Plus	56-50	43-00
LEAK Stereo 30 Plus, in teak case	62-50	47-95
LEAK Stereo 70 Chassis	69-00	52-00
LEAK Stereo 70 Casod	75-00	58-95
METROSOUND ST20E	35-50	21-50
PHILIPS RH 591	79-00	61-50
PHILIPS RH 590	52-00	39-50
PHILIPS RH 580	29-00	23-00
PIONEER SA500	62-10	41-95
PIONEER SA700	98-00	69-95
PIONEER SA900	134-10	99-95
PIONEER Reverberation	45-00	32-95
RANK Rotel 310	69-00	49-95
RANK Rotel 610	69-00	49-95
ROGERS Ravensbourne	59-50	45-95
ROGERS Ravensbourne (cased)	64-00	49-50
ROGERS Ravensbrook Mk. II	47-50	36-50
ROGERS Ravensbrook (cased)		
Mr. I	52-50	41-50
SINCLAIR 2000	35-00	23-95
SINCLAIR Project 60/2 x Z30/PZ5	23-90	16-50
SINCLAIR PROJECT 60/2 x Z50/PZ3/trans.	34-96	23-25
SINCLAIR AFU	9-95	4-95
SINCLAIR Neoteric	61-95	46-00
SINCLAIR 3000	45-00	32-50
TELETON SAQ 206	29-00	18-50
TELETON GA101	37-50	28-50
VOLTEX 100w. Stereo Diacothèque, 8 electronically mixed inputs	185-00	139-00

All the above take both ceramic and magnetic cartridges.

	Rec. Retail Price	Comet Price
<b>TUNERS</b>		
*ARMSTRONG 523 AM/FM	53-76	42-00
*ARMSTRONG 524 FM	41-99	33-00
ARMSTRONG M8 Decoder	9-50	8-00
*DULCI FMT. 7 FM	26-00	22-00
DULCI FMT. 7S Stereo	35-00	28-25
GOODMANS Stereomax	82-52	49-95
LEAK Stereofetic Chassis	66-50	52-00
LEAK Stereofetic in teak case	72-50	58-90
PHILIPS RH 690	47-00	36-00
PHILIPS RH 680	89-00	75-50
PIONEER TX500-AM/FM	77-94	63-50
PIONEER TX900 AM/FM	153-69	123-00
RANK Rotel 320	54-57	42-95
ROGERS Ravensbourne chassis	61-99	47-95
ROGERS Ravensbrook	45-01	31-95
ROGERS Ravensbrook (cased)	51-26	41-00
TELETON GT 101	45-50	31-95

All above Tuners are complete with MPX Stereo Decoder except where starred.

	Rec. Retail Price	Comet Price
<b>TUNER/AMPLIFIERS</b>		
AKAI AA 8500	229-00	181-00
AKAI 8600	142-53	112-00
AKAI 8300	128-85	99-95
ARENA R500	82-00	67-00
ARENA 2400	90-30	72-00
ARENA 2700	105-00	85-00
ARENA T9000	303-45	258-00
ARMSTRONG M8 Decoder	9-50	8-00
ARMSTRONG 525	91-89	74-50
ARMSTRONG 526	104-71	84-50
GOODMANS Mod. 90, 35w. R.M.S.	95-00	72-00
MIDLAND 19542	49-56	37-50
PHILIPS RH 790	139-00	112-00
PIONEER SX770 AM/FM	180-43	126-00
PIONEER SX980 AM/FM	194-74	150-00
PIONEER 440	111-10	89-00
TANDBERG 1171 comp. with decoder	110-00	94-00
*TELETON F2000	51-50	39-50
TELETON 7AT20	105-00	77-95
TELETON 10AT1 150w. RMS	160-00	103-00
TELETON TFS50	82-50	59-00
TELETON TFS 80LA MW/LW/VHF	87-50	63-50
TELETON R 3000 with Speakers	63-25	37-50
TELETON CR55	120-00	87-00
WHARFEALE 100-1	149-00	119-00

Starred items above take ceramic cartridges only. All others take both ceramic and magnetic cartridges. All the above Tuners and Tuner/Amplifiers include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.



**COMET for after-sales service**  
THROUGHOUT THE U.K.  
Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goole, Wakefield, Doncaster, Bridlington and Birmingham

	Rec. Retail Price	Comet Price
GOLDRING G850	6-50	5-25
EMPIRE 1000ZE/X	63-00	52-50
EMPIRE 999VE/X	44-50	36-00
EMPIRE 999TE/X	27-80	22-50
EMPIRE 999SE/X	21-00	17-50
EMPIRE 999E/X	16-50	13-00
EMPIRE 999/X	11-50	9-25
EMPIRE 909E/X	12-85	10-25
EMPIRE 909/X	9-00	7-50
EMPIRE 90EE/X	9-75	8-00
ORBIT Magnetic NM 22	Special Price 2-80	
PICKERING V18 AC2	8-40	7-00
ORTOFON SL15E	29-65	23-75
ORTOFON 2X15K Transformer	7-00	5-25
SHURE M3DM	7-41	5-50
SHURE M31E	12-05	8-95
SHURE M32E	11-10	8-25
SHURE M32-3	10-20	8-90
SHURE M44-7	11-10	7-95
SHURE M44-5	10-20	8-00
SHURE M44C	10-20	8-00
SHURE M44E	12-05	8-25
SHURE M55E	12-95	9-50
SHURE M75G	17-00	14-00
SHURE M75EJ	16-70	13-00
SHURE M75-6	19-45	18-00
SHURE M75E-85G	23-15	18-00
SHURE M75E	21-30	14-50
SHURE V15-11	40-78	28-85
SHURE V15-11-7	38-90	29-00

Starred cartridges above are ceramic. All others are magnetic.

	Rec. Retail Price	Comet Price
<b>PICKUP ARMS</b>		
GOLDRING Lenco L75	12-33	10-50
GOLDRING Lenco L69	9-29	7-00
SME 3009 with S2 Shell	34-47	27-00
SME 3012 with S2 Shell	36-71	30-50

	Rec. Retail Price	Comet Price
<b>TURNTABLES</b>		
The following Turntables are complete with base, plinth, perspex cover and cartridge. Fully wired and ready for use. All at special prices.		
GARRARD SP25 Mk 111 with Goldring G.800	Special Price £21-98	
GARRARD SP25 Mk 111 with Shure M.44-7	Special Price £22-95	
GARRARD SP25 Mk 111 with Shure M.155E	Special Price £23-95	
GARRARD AP76 with Goldring 6800	Special Price £30-95	
GARRARD AP76 with Shure M55E	Special Price £32-85	
GARRARD AP76 with Shure M75E	Special Price £36-95	
GARRARD 2025 with Sonotone STAHK	Special Price £15-50	
GOLDRING 705/P with G850	Special Price £15-95	
GOODMANS 3025 with G300	Special Price £28-90	

DUAL 1219 transcription	60-40	50-00
OVAL 1209 transcription	42-62	35-00
GARRARD SP25 Mk III	16-45	11-90
GARRARD SL65 B	21-25	15-50
GARRARD SL75 B	39-20	28-50
GARRARD SL95 B	50-01	35-50
GARRARD 401	39-67	32-50
GARRARD SL72 B	33-11	25-90
GARRARD 3500, with GKS Carf. Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500	Special Price 4-00	
GARRARD 4078	13-84	10-97
GARRARD AP76	28-88	21-50
GOLDRING GL69 Mk. II	25-63	21-25
GOLDRING GL89P Mk. II	35-14	28-50
GOLDRING GL75	36-41	31-50

	Rec. Retail Price	Comet Price
GOLDRING GL75P	46-94	38-50
GOLDRING Covers for 69P and 75P	4-21	3-50
GOLDRING C99—plinth and cover for G99	11-45	9-90
GOLDRING G99	26-00	22-90
GOODMANS 3025	37-74	28-90
MCDONALD MP 50	15-75	11-75
MCDONALD 610	20-00	15-75
Base and Cover for MCDONALD MP 60 and 810	Special Price 4-50	
PHILIPS 220	31-50	25-00
PHILIPS GA146	69-00	54-00
PHILIPS 202 Electronic	39-00	32-95
PHILIPS 306 transcription unit complete with base and cover	49-93	37-95
PIONEER PL12A with base & cover	8-85	7-00
THORENS TX25 cover	70-04	61-95
THORENS TD125	180-20	88-00
THORENS TD125AB	46-16	35-95
THORENS TD150A Mk. II	49-96	42-95
THORENS TX11 Cover	4-43	3-95

	Rec. Retail Price	Comet Price
<b>SPEAKERS</b>		
B & W Model 70	159-50	121-95
B & W DM3	63-00	49-95
B & W DM1	32-00	23-50
CELESTION Ditton 16	34-00	18-90
CELESTION Ditton 25	32-00	23-50
CELESTION Ditton 25	65-00	50-95
GOODMANS Minister	25-00	20-50
GOODMANS Magister	62-80	47-95
GOODMANS Maxim	20-49	16-50
GOODMANS M320 3	34-00	27-90
GOODMANS Magnum KG	44-00	33-00
J & S Model SXMT (pair)	26-95	14-95
KEF Cresta	22-17	18-00
KELETRON Speakers		
KN500 4 speaker system (pair)	23-00	15-50
KN700 4 speaker system	27-50	18-25
KN1000 4 speaker system	19-25	13-95
KN1500 4 speaker system	24-75	18-95
KN2000 4 speaker system	28-75	20-95
LEAK 200	24-95	18-90
LEAK 300	32-50	23-95
LEAK 600	49-50	36-95
LOWTHER Acousta (with PM6)	45-50	38-50
LOWTHER Acousta (with PM7)	53-00	46-00
LWTHER Ideal Baffle	35-50	30-00
METROSOUND HFS103 (pair)	25-00	17-95
METROSOUND 202	21-50	15-95
METROSOUND HFS20 (pair)	39-00	27-95
METROSOUND HFS10 (pair)	27-44	22-95
PHILIPS RH481	11-00	8-95
PHILIPS RH482	18-00	14-95
SINCLAIR O16	8-98	6-95
STE-MA 278 3 speaker system	23-10	15-95
TANDBERG TAN 7	22-30	18-50
TANDBERG TAN 11	19-30	16-50
TANDBERG TAN 15	45-00	35-95
<b>WHARFEALE Speakers</b>		
Airedale.....Speakers	69-50	54-95
Denton	19-95	16-75
Super Linton	24-90	20-50
Melton	32-50	24-95
Rosedale	42-50	31-95
Trifon (pair)	65-00	50-95
Unit 3 Speaker Kit	59-90	45-95
Unit 4 Speaker Kit	13-00	10-95
Unit 5 Speaker Kit	18-00	13-95
Unit 6 Speaker Kit	26-00	19-95
<b>CHASSIS SPEAKERS</b>		
GOODMANS Axlette 8	8-10	6-50
GOODMANS Twinaxlette 8	9-17	7-95
GOODMANS Axium 10	9-16	7-75
GOODMANS Axium 80	28-31	23-75
GOODMANS Axium 201	14-45	10-95
GOODMANS Axium 401	17-86	14-95
GOODMANS Axium 8P	5-55	4-25
GOODMANS Axium 10P	6-05	3-95

(OVER 1,520 sq. yds.)

# OVER 1000 ITEMS ALWAYS IN STOCK

## ALL FULLY GUARANTEED - WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

### COMPLETE HI-FI SYSTEMS

Completely wired, mounted and ready for use.

	Rec. Price	Retail Price	Comet Price
GOODMANS Audiom 51	13-05	18-95	9-75
GOODMANS Audiom 61	18-95	24-00	14-00
GOODMANS 2P	12-37	20-00	10-00
GOODMANS 15P	34-00	26-97	26-97
GOODMANS Audiom 18P	20-00	16-97	16-97
GOODMANS Twin Axlom 10	10-23	8-25	8-25
GOODMANS ARU172	4-50	3-50	3-50
GOODMANS Trebax 100	8-60	6-00	6-00
GOODMANS Trebax 5K/20XL	9-70	7-50	7-50
GOODMANS Midax	12-95	9-00	9-00
GOODMANS Attenuator	3-55	2-50	2-50
GOODMANS Crossover Networks			
XO/850/5000	9-75	7-25	7-25
GOODMANS Crossover Networks			
XO/850	7-40	5-75	5-75
GOODMANS Crossover Networks			
XO/5000	2-85	2-00	2-00
WHARFEDALE 8In. Bronze/RS/DD	5-00	4-00	4-00
WHARFEDALE Super 8/RS/DD	8-50	7-00	7-00
WHARFEDALE Super 10/RS/DD	14-00	11-50	11-50
WHARFEDALE WMT1 Matching Transformer	0-84	0-75	0-75

#### HI-FI STEREO SYSTEMS COMPLETE

ARENA MR15	145-00	109-95	109-95
ALBA UA552	45-88	35-50	35-50
ALBA UA682	60-32	46-95	46-95
DECCA Sound 6013	69-89	57-95	57-95
DECCA Sound 6014	70-86	68-95	68-95
DECCA Sound 1204	95-30	75-95	75-95
DECCA Compact 3	100-14	109-95	109-95
DECCALIA 5 complete with stand	65-50	51-95	51-95
EKCO SRG 609	85-44	66-95	66-95
EKCO ZUS	159-29	129-00	129-00
FERGUSON 3422	84-80	67-95	67-95
FERGUSON 3423	114-15	89-95	89-95
FERGUSON 3424	119-00	94-95	94-95
FERGUSON 3425	120-10	109-95	109-95
FERGUSON 3450 with radio	74-40	59-95	59-95
FIDELITY UA2 Music Master	44-41	31-95	31-95
FIDELITY UA1 Music Master	103-30	82-95	82-95
HMV 2416	129-70	99-95	99-95
HMV 2045/6	199-00	159-95	159-95
HMV 2482	65-65	53-95	53-95
HMV 2450 with stereo radio	134-20	109-00	109-00
KB KA1250 complete with two 653 speakers	71-55	58-50	58-50
KB KA1250 complete with two 651 speakers	80-25	64-95	64-95
KB 2010 with radio	73-40	60-95	60-95
LEAK 30/Goldring/Wharfedale	182-65	142-95	142-95
LEAK 70/Thorens/Wharfedale	226-87	175-00	175-00
MARCONI Unit 4	74-77	63-95	63-95
MARCONI Unit 3	84-79	67-95	67-95
METROSOUND Stereo 1010	92-30	69-95	69-95
PHILIPS 580/481/105	71-00	55-95	55-95
PHILIPS GF 823	47-79	38-95	38-95
PHILIPS GF 824	67-09	54-95	54-95
PHILIPS GF 833	65-16	54-95	54-95
PHILIPS GF 834	84-85	69-95	69-95
PHILIPS GF 417	96-06	73-95	73-95
PHILIPS 882	96-50	76-95	76-95
TELETON 2S80F with radio	72-40	53-95	53-95
TELETON 8TK Stereo System	54-75	48-00	48-00
TOSHIBA SP8507	248-00	175-00	175-00
ULTRA 6405	77-00	64-95	64-95

#### TAPE RECORDERS AND TAPE DECKS

AKAI 1720L	93-67	65-95	65-95
AKAI 4000 D 8-track stereo deck	86-68	67-50	67-50
AKAI CR 80D 8-track stereo tape deck	91-56	78-95	78-95
AKAI CR80 8-track stereo recorder	110-83	96-95	96-95
AKAI X200D	183-07	129-95	129-95
AKAI 1800SD	192-16	129-00	129-00
AKAI 2000SD	300-00	239-00	239-00
BUSH Diacand Stereo 2000	21-19	16-50	16-50
BUSH TP60 Cassette tape recorder	28-38	23-95	23-95

	Rec. Price	Retail Price	Comet Price
BUSH TP70 Cassette battery/mains tape recorder	28-91	23-50	23-50
FERGUSON 3245 Twin track	38-70	28-95	28-95
FERGUSON 3246 4-track	42-55	33-95	33-95
FERGUSON 3247 4-track	47-93	38-95	38-95
FERGUSON 3248 4-track	52-76	42-95	42-95
FERGUSON 3252 4-track	100-70	81-95	81-95
FERROGRAPH 702 2-track tape deck	220-22	189-00	189-00
FERROGRAPH 704/W 4-track tape deck			
FERROGRAPH 722	220-22	189-00	189-00
FERROGRAPH 724	257-52	215-00	215-00
GRUNDIG C200 De Luxe Cassette	38-46	28-95	28-95
GRUNDIG TK 121 twin track	55-30	42-95	42-95
GRUNDIG TK 149 4-track	57-63	47-95	47-95
GRUNDIG TK 141 4-track	61-82	49-50	49-50
GRUNDIG TK 146 4-track Auto	67-30	52-95	52-95
GRUNDIG 222 stereo cassette	57-70	47-95	47-95
GRUNDIG TK 147 4-track Auto	93-96	77-95	77-95
MIDLAND TC 144 cassettes	18-00	11-95	11-95
PHILIPS 2202 cassette	26-89	19-95	19-95
PHILIPS 2204 cassette battery/mains	32-30	25-50	25-50
PHILIPS 2205 cassette tape recorder	41-59	33-95	33-95
PHILIPS 3302 cassette tape recorder	23-04	17-95	17-95
PHILIPS 4303 new release	40-55	33-95	33-95
PHILIPS 4307 4-track	47-78	37-95	37-95
PHILIPS 4308 De luxe 4-track	58-40	43-95	43-95
PHILIPS 4402 4-track stereo recorder	91-71	71-95	71-95
PHILIPS 4407 4-track stereo recorder	106-19	87-95	87-95
PHILIPS 4500 4-track stereo tape deck			
PHILIPS 4408 4-track stereo	121-64	96-95	96-95
PHILIPS Cassette Stereo N2503 tape deck	134-18	106-00	106-00
PYC Cassette Recorder/Radio 9000 battery/mains	52-05	44-95	44-95
PHILIPS 2400 stereo cassette less L/S	43-86	35-95	35-95
TANDBERG 1841 4-track stereo tape deck	65-55	57-95	57-95
TANDBERG 3021 4-track stereo	69-75	50-95	50-95
TANDBERG 3041X 4-track stereo	109-90	83-00	83-00
TANDBERG 4021X twin track stereo	109-90	83-00	83-00
TANDBERG 4041X 4-track stereo	180-00	150-00	150-00
TANDBERG 6041X 4-track stereo	188-00	158-00	158-00
TANDBERG 6021X twin track stereo	188-00	158-00	158-00
TELETON 610 cassette	22-00	14-95	14-95
TELETON TC110 cassette battery/mains	26-79	19-50	19-50
TELETON TRC130 cassette with VHF/AM Radio Batt./Mains twin motors	40-31	31-50	31-50
TELETON 611 battery/mains cassette			
TELETON FXB 510 D 4-track stereo	29-50	17-50	17-50
TOSHIBA GT 601V twin track	65-16	47-50	47-50
TOSHIBA 850 SA 4-track stereo tape deck	43-95	25-95	25-95
TOSHIBA GT 840S 4-track stereo tape deck	91-50	49-95	49-95
WHARFEDALE Dolby DC9 cassette stereo tape deck	105-20	55-95	55-95

#### BASES AND COVERS

GARRARD WBI Base	3-86	3-25	3-25
GARRARD WB4 Base	5-69	4-75	4-75
GARRARD SPC 1 Cover	3-74	3-00	3-00
GARRARD SPC 4 Cover	4-44	3-75	3-75
Special offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500			
GOLDRING Plinth 69	Special Price	4-00	4-00
GOLDRING Covers for 69P and 75P	8-52	7-00	7-00
GOLDRING Covers for 69P and 75P (for TD125AB)	4-21	3-50	3-50
THORENS TX25 (for TD125AB)	8-22	6-50	6-50
THORENS TX11 Cover	4-11	3-75	3-75
Base and Cover for TD125	15-18	12-90	12-90
PHILIPS Stereo 2000	39-20	31-25	31-25
MOTORBOARDS only	4-95	3-00	3-00

	Rec. Price	Retail Price	Comet Price
GOODMANS AUDIO SUITE, Goodmans Maxamp stereo amplifier, Goodmans stereomax AM/FM Tuner with decoder, Pair of Goodmans Magnum K2 speakers, Garrard AP78 turntable in base, complete with cover and Goldring G800 Cartridge. Beautifully finished in walnut	257-13	169-95	169-95
GOLDRING 705P turntable complete with G800 Cartridge, Midland Tuner/Amp., pair of Melrosound 103 Speakers	99-56	69-95	69-95
GOODMANS Module 80 Tuner/Amplifier, Garrard AP78 Turntable with Goldring G800 Cartridge and 2 Goodmans Minister Speakers	199-00	139-00	139-00
METROSOUND 448 8-track stereo play-back unit complete with 2 HFS 10 Speakers	83-56	70-95	70-95
GOLDRING 705P turntable complete with G800 Cartridge, Teleton 206 Amplifier, pair of Keletron KN500 Speakers	77-00	49-95	49-95
TELETON STP 801 Stereo 8 track tape Audio system complete with speakers	54-75	48-00	48-00
GARRARD SP 25, Mk. III mounted in base, plinth and cover with GOLDRING G800 Cartridge, Teleton 206 Stereo Amplifier 12 watts RMS, and 2 KELETRON KN500 Speakers, each speaker is a 4 speaker system	88-33	58-95	58-95
PIONEER PL 12 turntable, Goodmans Maxamp, Shure M55E Cartridge, 2 Keletron KN 700 speakers (each speaker cabinet contains 4 speakers)	144-38	105-00	105-00
GARRARD AP78 turntable complete with Goldring G800 Cartridge, base and cover, Rogers Ravensbrook Amplifier in teak case and 2 Goodmans Minister Speakers	142-51	108-50	108-50
LEAK 30/THORENS/WHARFEDALE	182-65	142-95	142-95
GOLDRING GL 75P mounted in teak base with hinged perspex cover complete with GOLDRING G800E Cartridge, Leak Stereo 30 Plus Amplifier in Teak case, 2 GOODMANS Mezzo 3 Speakers	200-50	154-20	154-20
THORENS TD 150A Mk. II with TX11 dust cover, SHURE M55E Cartridge, LEAK Stereo 70 Amplifier in Teak case, 2 Wharfedale Dovedale 3 Speakers	226-87	175-00	175-00
THORENS TD 125AB Electronic Turntable complete with cover, SHURE V15-1 Cartridge, GOODMANS Maxamp, GOODMANS Stereomax AM/FM Tuner, 2 GOODMANS Magister Speakers	422-48	309-00	309-00
TELETON STP 801, Stereo 8 track Tape Audio Systems comp. with speakers	54-75	48-00	48-00



All in-stock items delivered by **SECURICOR** WITHIN 72 HOURS  
(Add £1.75 only for Securicor delivery)  
ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

Open daily to the public from 9-0 A.M. until—

5-30 P.M. MON.  
1-0 P.M. TUES.  
8-0 P.M. WED.  
8-0 P.M. THUR.  
8-0 P.M. FRI.  
5-30 P.M. SAT.

Customers are welcome to call -  
Ample car parking facilities

Complete Price List FREE on request!

## COMET HIGH FIDELITY DISCOUNT WAREHOUSES

(Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407906 and 407877

(Dept. P.W.) 68A Armley Rd. (Artist St.), Leeds LS12 2EE Tel. 32055 (5 lines)

(Dept. P.W.) Teesway, Portrack Lane, North Teesside Tel. 66132/65215

Industrial Estate, Teesside, TS18 2RH  
(Dept. P.W.) Heeley Road, Selly Oak, Birmingham  
Tel. 021-472 6181

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press.  
Add 75p for postage, packing and Insurance on all orders (Cartridges 20p) or, if Securicor delivery required, add £1.75 only.  
Make cheques, Money Orders payable to "COMET".

Free Technical Advisory Service. If in doubt, ask us!

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 8½p per word (minimum 12 words), box number 7½p extra. Semi-displayed setting £6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

## Educational

### TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: London Electronics College, Dept. A/10, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.

**LEC**

RTEB CERTS., City & Guilds, Colour TV, Radio, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—FREE: BIET, (Dept. H.7), Aldermaston Court, Reading, RG7 4PF.

#### Situations Vacant

EAGLE INTERNATIONAL require Audio Engineers; excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact Mr. Morrow 01-636 0961.

GO TO SEA as a Radio Officer. Write: Principal, National College, Broadwater, Fleetwood FY7 8JZ.

#### TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs) R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON, SW8 4UJ

CIE, AMSE, City & Guilds, etc., on 'Satisfaction or Refund' terms. Thousands of exam. successes. Postal Courses for all branches of Engineering. Illustrated prospectus FREE. Please state subject of interest: BIET, (Dept. H.8), Aldermaston Court, Reading, RG7 4PF.

#### Receivers and Components

##### MICROCIRCUITS:

709	36p	SL402A	£1.75	7430	19p
741	73p	MEL 11	35p	7473	42p
PA230	87p	D40C1	55p	7474	44p
PA234	86p	7400	19p	7486	33p
PA237	£1.55	7410	19p	D1Lconn.	25p

##### TRANSISTORS:

2N3055	54p	ME0402	21p	ME4102	12p
2N5172	7p	ME0412	20p	ME6001	13p
BOY70	16p	ME0413	15p	ME6101	15p
BD124	73p	ME1002	12p	MEF104	45p
BFX86	15p	ME4101	11p	MP8111	35p

##### 1 AMP RECTIFIERS

57V	3p	400V	6p	600V	9p	1000V	14p
Bridges	—	50V	25p	100V	26p	200V	27p

Printed Circuit Resist Pen .. 80p

##### JEF ELECTRONICS (P.W.9)

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. C.W.O.

P.&P. 5p per order. Overseas 40p.

Money back if not satisfied.

List free on application.

#### NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc. This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only £3.40. P. & P. Free U.K. only

Illustrated Catalogue of Selected Kits and Components 12½p. P. & P. Free.

Cheques, Postal orders to:

Dept. F.W.

Gallion Trading Co., 25 Avelon Road, Romford, Essex

EX COMPUTER PRINTED CIRCUIT PANELS 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards 50np + 7np P. & P. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 18np. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board + components. 2 boards (4 x OC28) 50np + 6np P. & P.

9 OAS, 3 OAI0, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for £1 + 25np P. & P.

##### LARGE CAPACITY ELECTROLYTICS

10000MFD 30V } 40np + 6np P. & P.  
16000MFD 12V }  
or £3.50 per doz. Carr. 50np

250 MIXED RESISTORS 62np

± & ± watt.

150 MIXED HI STABS 62np

± & ± 1 watt 5% and better.

##### QUARTZ HALOGEN BULBS

With long leads, 12V 55W for car spot lights, projectors etc. 50p each p & p 5p.

##### DIODES SILICON

1 Amp 1000 PIV. 4 for 50np. + 5np P. & P.

##### BARGAIN RELAY OFFER

Single pole change over silver contacts. 25V to 50V. 2.5kΩ coil. 8 for 50np. + 5np P. & P.

##### KEYTRONICS mail order only

44 EARLS COURT ROAD,

LONDON W.8

01-478 8499

## RADIO OPERATORS

DO YOU HOLD PMG II OR PMG I OR NEW GENERAL CERTIFICATE OR HAD TWO YEARS' RADIO OPERATING EXPERIENCE?

Looking for a secure job with good pay and conditions?

Then apply for a post with the Composite Signals Organisation.

These are Civil Service posts, with opportunities for service abroad, and of becoming established, i.e., non-contributory pension scheme. Specialist Training Courses (free accommodation) starting January, April and September, 1972.

If you are British born and resident in the United Kingdom, under 35 years of age (40 for exceptionally well qualified candidates), write NOW for full details and an application form from:—

#### GOVERNMENT COMMUNICATIONS HEADQUARTERS,

Recruitment Officer, Oakley, Priors Road, Cheltenham, Glos. GL52 5AJ.

(Telephone: Cheltenham 21491, Ext. 2270.)

# Kits for P.W. CONSTRUCTIONAL ARTICLES

**Amateur Bands Communications Receiver £23-85**, p. & p. 75p (or in 3 parts). RF Detector £9-64 p. & p. 25p. Signal Injector Tracer £3-95 p. & p. 20. **Workshop Oscilloscope £28-35** p. & p. 60p. Crystal Companion £1-95 p. & p. 20p. Hi-Z Voltmeter £4-52 p. & p. 20p. 10W Audio Amplifier £8-75 p. & p. 35p. Hi-Fi Signal Generator £11-30 p. & p. 35p. Simple Signal Generator £6-95 p. & p. 30p. Electronic Ignition System £6-30 p. & p. 30p. Solid State Enlarger Timer £6-30 p. & p. 35p. For prices of recent kits please send S.A.E.

**F. & B. ELECTRONICS** 5, Staples Inn, Holborn Bars, London WC1V 7QH  
C.W.O. mail order only—please enquire for overseas p. & p.

COMPLETE RANGE of receivers by Trio, Lafayette, Hallicrafters, etc. Chassis, panels, cabinets, S.A.E. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263 7829.

<b>PROJECT 60 OFFERS</b>	Post 37p
Stereo 60/2 Z30/PZ5	£16-40
Stereo 60/2 Z30/PZ6	£19-00
Stereo 60/2 Z50/PZ3	£21-25
Transformer for PZ3	£2-20
Project 60 FM tuner	£20-50
Active Filter Unit	£4-75
Q16 Loudspeaker	£7-70
Kit of extra capacitors, plugs, cables, fuse to complete Project 60	£2-40
Antex 15W soldering iron CN240/2	£1-70
All items available separately.	

**SINCLAIR SUPER IC-12**  
Ideal for use with PZ5 power unit. Supplied with instructions and free PC board .. £2-45

**SINCLAIR BARGAINS**  
Power units: PZ5 £3-80, PZ6 £6-40, PZ8 £8-40  
Amplifiers: Z30 £3-60, Z50 £4-35, Stereo 60 £8-35.  
Receivers: Micromatic kits £2-25, Assembled £2-75. Batteries 27p extra.

**SINCLAIR SYSTEM 3000**  
£32-90, Post 37p

**S-DECS**  
S-DeCs £0-95, T-DeCs £2-25, µ-DeC A £3-10  
Carriers with sockets to mount 14 and 16 pin in line ICs on T-DeCs and µ-DeC A £1-25.

**MULLARD UNILEX**  
EP9000 Amp £2-40, EP9001 Pre-amp £2-60, EP9002 Power unit £3-90, Control unit £2-80, Unilex booklet £0-22.

**THE 0.7P TRANSISTOR**  
PNP silicon transistors from 2S300 series with data. Typical V<sub>cb</sub>=25 V, h<sub>fe</sub>=35, ft=1 Mca, P<sub>max</sub>=300 mW. Untested and unmarked, but at least 80% are perfect to maker's spec. 50 for 40p, 100 for 70p.

**SWANLEY ELECTRONICS**  
32 GOLDSIEL RD., SWANLEY, KENT  
Mail order only.  
Minimum postage 10p per order.

**CIRCUITS CIRCUITS CIRCUITS**  
Ten exciting circuits per month with instructions to build. Every month a completely new set. This month's circuits cover

**MISCELLANEOUS PROJECTS**  
Only 50p per set of ten p & p free  
Free Data and Technical A-Z cards (build up the complete set month by month).  
Cheques and PO to Dept. PWC Electronics, 3 Whitehall Gardens, London, E4.

**COMMUNICATION RECEIVERS**  
Checked, tested HRO, AR88, B40 and many others, also Power Supplies, Testgear etc. SAE please, stating requirements.

**STC AIRCRAFT RECEIVERS**  
Small compact 18 valve double conversion RX of modern design, covering 2-8-18.5 MHz in 3 bands. Features include: Unit Construction, Variable Selectivity, Xtal Controlled BFO, Manual or Remote Tuning, Illuminated Dial.  
The RX is designed to operate from 24 volts DC on 24 channels but can easily be modified for continuous tuning and mains operation. Circuit and modification details supplied with each unit. Excellent condition. £6-95. Carr. £1.

**RICHARD SELLERS,**  
EASTINGTON, GOOLE, YORKSHIRE.  
04-305 254

## TV's TV's TV's

**SPECIAL OFFER LIMITED PERIOD ONLY**

19" slim Thorn 800 TV's. 13 channel Good working order. Polished cabinets. Only £9-60 PLUS £1-60 Carr.

## EX-RENTAL TV's (Untested)

Complete with 13 channel tuners. Good cabinets. Carriage £1-50 extra.  
17" Semi Slim (90° Tube) .. £8-50  
17"/21" Slim (110° Tube) .. £4-60  
19" Slimline .. £8-50  
23" Slimline .. £8-50  
19" BBC2 Sets .. £14-50

## PERFECT SPEAKERS EX T.V.

Pm 8 ohm (minimum order two) 5 in. round, 8 in by 2 in rectangular—12½p each. Add 7½p per speaker p. & p.

## VALVES EX EQUIPMENT

EB91	5p	30F4	13½p	FY81	15p
EBF89	12½p	PC97	17½p	FY800	15p
ECC82	12½p	PCF86	17½p	FY82	7½p
EC180	7½p	PC84	7½p	FY33	22½p
EF85	12½p	PCF80	7½p	U191	17½p
EF86	12½p	PC89	12½p	6P28	17½p
EF183	12½p	PCL86	22½p	30PL1	22½p
EF184	12½p	PCL82	17½p	30F12	30p
EV86	17½p	PCL86	17½p	30F8	10p
30PL13	20p	PCL83	12½p		
630LZ	12½p	PL36	22½p		
30L15	12½p	PL81	17½p		

Add 2½p per valve p. & p., orders over £1 p. & p. free

## UHF TUNERS

For Ferguson 850 900 chassis adaptable for KB, Ekco T415, 1084 Chassis £2-50, p. & p. 30p.

## SLOT METERS SPECIAL OFFER

Smiths Mk. II 6d. Convertible to 5p. (Smiths Kit costs 35p each) £1 each inc. p. & pkg. or 10 for £5 inc. p. & pkg.  
Please write with SAE for quotations on any spares.

## TRADE DISPOSALS (Dept. T.S.)

Thornbury Roundabout, Leeds Road, Bradford.  
(Telephone 665670)

## AERIAL BOOSTERS (£2-95)

We make four types of R.F. high gain transistorized pre-amplifiers L45 U.H.F. TV, L12 V.H.F. TV, L11 V.H.F. radio, L10 medium and short wave. For full details send S.A.E.

## PRINTED CIRCUIT BOARDS

2—9in by 4in boards with etching powder and instructions. 50p

## MAINS DROPPER

Three section 33 ohms by 33 ohms by 33 ohms. 9p each

## TV VALVES (Ex Eq)

Any 5—45p, 10—70p, ECC82, ECL80, EF80, EF85, EF183, EB91, EY86, PCC84, PCC89, PCF80, PCF86, PCL82, PCL83, PCL84, PL36, PY33, PY81, PY82, Y800, 30L15

P&P ALL ORDERS 10p, SAE for details  
**VELCO ELECTRONICS**, 62a Bridge St, Ramsbottom, Bury, Lancs.

## 3 MILLION RESISTOR SCOOP

Fantastic savings by huge purchase from manufacturer. High stability, close tolerance (1% to 5%) Carbon Film and a few Electrofilm, watt to 2 watt, 20 to 40 Meg Ω packed in 10's except 2 watt in 5's. Big choice values and wattages with plenty small types. Our selection: 85p per 500 car, 25p

£1-50 per 1,000 car. 28p  
£15 per 10,000 car. free  
DON'T MISS THIS BARGAIN OFFER CANNOT BE REPEATED

**ELEY ELECTRONICS**  
112 Groby Road, Glenfield, Leicester LE3 8GL

## Stella Nine Range Cases LIST OF PRICES AND SIZES

Width	Depth	4" Height	6" Height	7 1/2" Height
64"	37"	90p	£1-05	£1-23
64"	47"	96p	£1-23	£1-40
84"	37"	£1-05	£1-40	£1-40
84"	67"	£1-40	£1-74	£2-00
102"	77"	£1-88	£2-28	£2-45
124"	37"	£1-40	£1-74	£2-03
124"	57"	£1-85	£2-25	£2-43
124"	87"	£2-30	£2-74	£2-93
142"	37"	£1-65	£2-03	£2-25
142"	97"	£2-73	£3-50	£3-65
162"	67"	£2-45	£2-93	£3-24
162"	107"	£3-15	£4-05	£4-45

Cases—Post 25p. per order.  
Discounts available on quantities.

## CHASSIS IN Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases. All 2 1/2" Walls

6" x 3"	33p	10" x 7"	51p	14" x 3"	44p
6" x 4"	34p	12" x 3"	40p	14" x 9"	84p
8" x 3"	39p	12" x 5"	45p	16" x 6"	64p
8" x 6"	46p	12" x 8"	64p	16" x 9"	95p

Chassis—Post 15p. per order.  
Discounts available on quantities.  
Electro magnetic counters. New Boxed. 500 ohm 4 digit 30p post free.  
Copper Laminate Board "1/8" single sided. 12" x 12" 30p. post free.  
P.O. relays (600 Type) 500 ohm + 500 ohm. 1 make 1 break 2 change over New boxed 30p post free.  
Heavy duty sliding reostat. 1 ohm 12 amp New boxed £1-25p. post free.

**E. R. NICHOLLS**  
Manufacturer of Electronic Instrument Cases  
46 LOWFIELD ROAD STOCKPORT - CHESHIRE  
Tel: 061-480 2179

## CHROMASONIC electronics

supply only brand new guaranteed goods

### LOW NOISE HI-STABS

1 watt 5% all E24 values 3 for 5p plus p. & p. 6p up to 50 resistors + 1p for each additional 50.

**CAPACITORS**

Mullard C280 -01 µf, -015 µf, -022 µf, -033 µf, -047 µf, 3p each. -068 µf 8½p, -1 µf, -15 µf 4p. -22 µf 6p. -33 µf 8½p. -47 µf 8p. -68 µf 11p. 1 µf 13p. 15 µf 30p. 2-2 µf 24p.

C280 series now all 5p. Also in stock C388, C431 and C437 series, plus polystyrene and S. mica.

**INTEGRATED CIRCUITS**

SN7400N, 1, 2, 4, 5, 10, 20, 26, 30, 40, 50, 51, 54  
SN7460N .. all 23p ea.  
SN7441AN, 42, 75, 81, 82, 90, 92, 93, 94, 95 all 87p ea.  
MC1303L £1-55 PA234 87p TAA320 86p  
MC1304P £2-60 PA237 81p TAD100 £1-95  
MC1805P £2-50 PA246 £1-60 µA709e 85p  
MFC4000P 70p TAA263 70p µA710 85p  
MFC4010P 75p TAA981B £1-90 µA741C 75p

**TRANSISTORS**

BC107 13p AC128 17p BF167 25p  
BC108 11p AD161/162 88p BF173 25p  
BC109 13p 2N348 15p BC109 15p  
BC168 15p 2N2928 O/Y 15p BB105G 87p  
BC261 30p 2N3707 15p BZY88 series  
BFY51 21p 2N4058 17p 7eners 15p  
2N3063 25p 2N5458 48p 2N3819 35p  
2N3054 50p OA81/90/91 7p TIF48 38p  
2N3055 70p 1N914 7p 1N4004 10p

**FREE CATALOGUE p. & p. 3p.**  
P. & p. on all orders other than resistors 6p  
56 FORTIS GREEN ROAD, LONDON, N10 3HN

## Receivers and Components

**EX-GOVT. COMMUNICATIONS RECEIVERS.** calibrators, signal generators, components, etc., with money back guarantee. SAE list. Callers welcome, please phone first.—P. R. Gollidge, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

**BRAND NEW COMPONENTS** by return. Electrolytics 15 or 25 volts, 1, 2, 5, 10 mfd. 3.5p 25, 50 4p, 100 5p. Mylar film 100V .001, .002, .005, .01, .02 2p, .04, .05, .1 2.5p. Mullard miniature Carbon Film Resistors 1/2 W E.12 series 10-10M08 for 5p. Postage 5p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

## Service Sheets

# SERVICE SHEETS & MANUALS

LARGE RANGE OF MODELS AVAILABLE FOR RADIO, TELEVISION, TAPE RECORDERS, ETC. FROM 40p EACH - S.A.E. WITH ENQUIRIES PLEASE - 1971 INDEX LIST AVAILABLE 20p

MULLARD TRANSISTOR AUDIO AND RADIO CIRCUITS	PRICE £1,70p )
T.V. FAULT FINDING BOOK by DATA PUBLICATIONS LTD.	" 57p )
MULLARD VALVE & SEMI CONDUCTOR DATA BOOK	" 25p ) POST
MAZDA VALVE & PICTURE TUBE DATA BOOKLET	" 25p ) FREE
BRIMAR VALVES & TELE-TUBE DATA LIST	" 20p )
RESISTOR COLOUR CODE INDICATOR DISC	" 13p )

Large selection of Television Colour Manuals available - Prices on request.

## BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorkshire. Tel. 0423 - 86844

**SERVICE SHEETS.** Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS (1925-1971)** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc.; by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone Bexhill 7097.

**SERVICE SHEETS.** TV, Radio, etc., 40p. Large stocks. S.A.E. with enquiries please, callers welcome. K. L. Bower, 35 Briarwood Drive, Wibsey, Bradford.

## TRADER SERVICE SHEETS

40p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

## OAKFIELD ENTERPRISES LIMITED

29 CHURCH ROAD, TUNBRIDGE WELLS, KENT

Make	Model	Radio/TV

1971 List now available at 10p. plus postage

If list is required indicate with X

From .....

Address .....

enclose remittance of .....

(and a stamped addressed envelope) s.a.e. with enquiries please

**MAIL ORDER ONLY**

**RADIO, TELEVISION** and Tape Recorders, 50 mixed odd sheets 50p. Also large stock of Obsolete/Current Valves. John Gilbert TV, 1B Shepherds Bush Road, London W6. 01-745 8441. SAE enquiries.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each, Manuals from 50p. **"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"** Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

**C. CARANNA**  
71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.  
Mail order only.

## QUICK, EFFICIENT, UNIQUE SERVICE SHEET SERVICE

Very Large Stock  
TVs, Radio, Amps, Test Gear.  
Special Telephone Service available to Trade Customers.  
Colour TV and Test Gear Circuits.  
Exchange Service.

Full details with First Order.  
List price 10p post free.

State Make and Model Number  
Large S.A.E. and 25p unfiled P.O.

Mail Order Only.

**A.S.L., 21c Drydon Chambers,**  
119 Oxford Street,  
London, W1R 1PB

## Courses

# BOURNEMOUTH COLLEGE OF TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

## B.Sc. (Eng.) HONOURS DEGREE

in Electrical and Electronic Engineering

Entrance Requirements G.C.E. O or A Levels, O.N.D., O.N.C. or H.N.C.

## DIPLOMA IN COMPUTER TECHNOLOGY

Two year full-time course of O.N.D. standard. Entrance requirements G.C.E., O or C.S.E.

For details and application forms write to T. A. Goodchild, Head of Department of Electrical and Electronic Engineering, Room E3, College of Technology, Lansdowne, Bournemouth, BH1 3JJ.

## For Sale

# MORSE MADE EASY !!

**FACT NOT FICTION** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course G.O.D. ring 8.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to:

**G8SHO (Box 19), 45 GREEN LANE, PURLEY, SURREY**

**YUKAN SELF-SPRAY** OF PROFESSIONAL GRADE FOR EVERY OCCASION

Get these **air-drying GREY HAMMER** **OR BLACK WRINKLE** **(CRACKLE) Finishes** **NOW!**

Yukan Aerosol sprays contain 45% fine quality durable easy instant spray. No stove baking required. Finishes available in grey, blue, Modern Eggshell Black Wrinkle (Crackle) all as 85p in our 400ml or 900ml carriage paid per push-button self-spray can. Also Durable, heat and water resistant Black Mat Finish (399p self-spray cart only) 75p carriage paid.

**SPECIAL OFFER:** 1 can plus optional transferable 250000 tagger handle (value 250000 99p, carriage paid). Choice of 13 self-spray plain colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

**Dept: M9 YUKAN, LONDON, W2 1BN**  
We supply many Government, Department, Municipal Authorities, Institutes and Leading Industrial Organizations. We can supply you too.  
Open all day Saturday, Closed Thursday afternoon.

**SEEN MY CAT? 5,000 items.** Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**BUSH TP60** Cassette Recorder, Mains supply, microphone, extra output socket, good condition, maker's carton, £12 o.n.o.—Box No. 98.

## Wanted

**WE BUY New Valves and Transistors.**  
State price: A.D.A. MANUFACTURING  
CO., 116 Alfreton Road, Nottingham.

### TOP PRICES PAID FOR NEW VALVES

popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C),**

367 Kensington Street, Bradford 8,  
Yorkshire.

**WE BUY New Valves, Transistors and  
clean new components, large or small  
quantities, all details, quotation by  
return. WALTON'S WIRELESS  
STORES, 55 Worcester Street, Wolver-  
hampton.**

**CASH PAID for New Valves. Payment  
by return. WILLOW VALE, ELEC-  
TRONICS, 4 The Broadway, Hanwell,  
London, W.7. 01-567/5400-2971.**

**WANTED. Ex-RAF HF Transmitter  
Type T1119 or T1138. Circuit. Condition  
not important. Box No. 97.**

**HIGHEST POSSIBLE cash prices for  
Akai, B. & O., Brenell, Ferrograph,  
Revox, Sanyo, Sony, Tandberg, Uher,  
Vortexion, etc. 9.30-5.00. 01-242 7401.**

## Ladders

**VARNISHED TIMBER LADDERS** from  
manufacturer. Lowest prices anywhere.  
15½ ft. extd. £6-20, 17ft. ext. £6-50, 20ft.  
ext. £7, 21½ ft. ext. £7-75, 24½ ft. ext.  
£8-90, 29ft. ext. £10-25, 31½ ft. triple  
ext. £12-25, 36ft. triple ext. £16. Carr.  
80p. Free lists. Also Aluminium Ext. &  
Loft Ladders. Callers welcome.—(Dept.  
W.L.S.) Home Sales, Baldwin Road,  
Stourport, Worcs. Phone 02-993 2574/  
5222. Placing order on C.O.D.

## Metal Work

**METAL WORK:** All types cabinets,  
chassis, racks, etc., to your specifica-  
tions. **PHILPOTTS METAL WORKS  
LTD.,** Chapman Street, Loughborough.

## Miscellaneous

## TOP TRANSISTORS

Brand New and Individually Tested Tran-  
sistors supplied unmarked, but packed  
separately for identification and guaranteed  
to be within their correct specification or  
money refunded. All at 9p. each or

Any 25 transistors for only £1.90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

**J. M. KING (M)**

17 Buckridge, Portpool Lane, London, E.C.1

## LIGHTWEIGHT TREASURE-PROBE

Look for **BURIED COINS**, silver, gold  
and metal relics **PROFESSIONALLY**  
with the **BOFFIN** solid-state **TREASURE-  
PROBE**. An extremely **EASY-TO-BUILD**  
kit that **REALLY DOES WORK**! **SIMPLE-  
TO-FOLLOW INSTRUCTIONS**. It comes  
to your doorstep with maximum-copper  
**PRINTED-CIRCUIT BOARD** plus **ALL**  
**ELECTRONIC COMPONENTS** including  
search-coil and earphone. Think of the  
fun you'll have **BEACHCOMBING** with  
the sensitive **TREASURE-PROBE** and  
the expectancy of hearing its **LOUD**  
**'BEEP'** to tell you **"YOU'RE ON TO  
SOMETHING"** **GET YOUR TREASURE-  
PROBE SEND £6-95 NOW!**

### BOFFIN PROJECTS

4, CUNLIFFE RD.  
STONELEIGH EWELL  
SURREY

Designed by **GERRY BROWN & JOHN  
SALMON** and presented on TV

## THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an elec-  
tric organ? Constructional data available  
—full circuits, drawings and notes! It has  
5 octaves, 2 manuals and pedals with 24  
stops—uses 41 valves. With its variable  
attack you can play Classics and Swing.  
Write **NOW** for free leaflet and further  
details to **C. & S., 20 Maude Street,  
Darlington, Durham.** Send 2½p stamp.

## 12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, Ideal  
for Caravan, Tent, Emergency Lighting etc,  
Fully Transistorised, Low Battery Drain,  
With ON/OFF Switch and 12v Socket to  
Run other Lights or 12V Equipment.

Unbeatable at **£3-30** post paid  
or in kit form **£2-90**

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire S.A.E. for lists

## INCOMPARABLE V.H.F. KIT

CV2—unique triple-purpose (Converter,  
Receiver, Tuner-Feeder) kit for the Amateur  
enthusiast. Fantastic transistorized per-  
formance, World Wide Sales. Complete  
kit of top grade parts with coils covering  
80-180 MHz, plus easy/built diagrams and  
instructions. £4 direct from makers or  
S.A.E. for free literature.

### JOHNSONS (RADIO)

**ST. MARTINS GATE WORCESTER**  
Est. 1943 Tel. 24864

(A division of the G-BAN Organisation)

## TAPE HEADS PICK-UP CARTRIDGES

**SERVICE MANUALS** for Pre 1958  
H.M.V. and E.M.I. MODELS.  
Radio and Record Player Manuals  
25p each. Television Manuals  
37½p each. Send C.W.O. stating  
model required.

Send stamp for comprehensive  
lists of transformers, condensers,  
resistors, cartridges and tape  
heads.

**R. D. I. LTD.,**  
Chilton Works, Garden Road,  
Richmond, Surrey.

## 17" BBC/ITV TELEVISIONS £5

Working Perfectly  
plus P&P £1 CWO.

### SUITABLE FOR ANY AREA

3 Channel 19in D/S TVs. ITV, BBC 1, BBC 2,  
£25 inc. carriage. 17in 13 Channel, complete  
but untested £1-50 each, plus £1 P&P. CWO.

### SPEAKERS

6in x 4in, 7in x 4in 3OHM  
20p plus 8p P&P each. CWO.

Regular deliveries throughout England and  
N. Ireland.

### TRADE TV'S

407 Thornton Road, Gillington, Bradford 8,  
Yorks.

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver  
kit does not use R.F. and you can get one easily.  
Your transmissions will be virtually **SECRET** since  
they won't be heard by conventional means.  
Actually it's **TWO KITS IN ONE** because you get all  
the printed-circuit boards and components for both  
the transmitter **AND** receiver. You're going to find  
this project **REALLY FUN-TO-BUILD** with the  
**EASY-TO-FOLLOW** instructions. An extremely  
flexible design with quite an **AMAZING RANGE**—  
has obvious applications for **HOUSE-TO-HOUSE**  
**USE**, **SCHOOL PROJECTS**, **LANGUAGE**,  
**LABORATORIES**, **SCOUT CAMPS**, etc.

GET YOURS! SEND **£5-20 NOW**

**TO: 'BOFFIN PROJECTS'**  
DEPT. KW2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

## JOHN SAYS...

**RING MODULATOR** by Dewtron is  
professional, transformerless, 5-transistor,  
has adjustable FI/F2 rejection. Module £7.  
Unit £8-90. **WAA-WAA** Pedal kit of all  
parts, incl. all mechanics & instr. Only  
£2-45. **AUTO RHYTHM** from Dewtron  
modules. Simple unit for waltz, foxtrot  
etc. costs £16-55 in modules. **SYNTHES-  
ISER MODULES** and other miracles.  
Send 15p for illust. list.  
**D.E.W. Ltd., 254 Ringwood Road,  
Ferndown, Dorset.**

We stock all those components and  
materials required by the home Hi-Fi  
constructor, including speaker grille  
fabrics, BAF wadding, speaker kits,  
cabinets, cross-over networks, inductors,  
etc. **AT TOP DISCOUNTS.** Price list free  
of charge. Send 2 x 3p stamps for pattern  
card of speaker grille fabrics. Mail order  
**ONLY.** No callers please.

**AUDIOSCAN** Dept. PW9  
4 PRINCES SQUARE  
HARRISBURG, YORKS.

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond Surrey.

**DAILY UFO** Flight Patterns, 37½p. UFO Map, S. England, 37½p. TV Notes on UFO Detection, two Optical Circuits, 50p. UFO Wave Pattern and Prediction, 45p. R & P Publications, "Highlands," Needham Market, Suffolk.

**PETERBOROUGH MOBILE RALLY** will be held on Sunday, 26th September. From 11 a.m. to 5 p.m., at Walton School, Walton, 3 miles north of Peterborough.

**HEADPHONES** (Stereo) Diplomat Model by S. G. Brown, 10 pairs. Bargain £4.95 each. R.J.W. 27 Huxley Road, London, E.10. Tel. 01-556 8362.

**BUILD IT** in a DEWBOX quality cabinet. 2in x 2½ in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**RECORD TV SOUND** using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p +10p P&P. CROWBOROUGH ELECTRONICS (P.W.), Eridge Road, Crowborough, Sussex.

## SYNTHESISER MODULES

Send SAE for details of voltage-controlled modules for synthesiser construction to D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.

# FAMOUS TELETON—AM/FM Stereo Tuner Amplifier R8000

Supplied complete with 2 speakers. Total 12 watts RMS. Specification MPX Beacon, AFC Connections for Tape Recorder, Stereo Headphone Socket, etc. Mfgs. Rec. Price £63.50

P.S.P. FANTASTIC OFFER **only £39.95**



Plus GARRARD DECK 2025 Complete with plinth and perspex cover. Fitted with superb Sonotone 9TAHCO cartridge. P.S.P. offer **ONLY IF YOU BUY THE ABOVE only £15.40**



**PERSONAL SHOPPERS PLAN LTD.**

The Centre  
36-38 West Green Road, Tottenham, N.15  
Tel. No. 01-800 5533



All orders C.W.O. Special Securicor fast delivery £3.

### TELETON SAQ 206 STEREO AMPLIFIER

Latest release, beautifully styled in walnut case, 6+6 watts r.m.s. Switched inputs for magnetic X tal, aux. Tape. Incorporates volume, bass, treble and, slide balance control, scratch filter and loudness control. Rec. £32.50. Our price £19.95.

#### Suggested System.

SAQ 206 Amplifier, SP25 III Plinth and Cover, G800 cartridge, pair large 3-way speaker system size 18" x 10" x 7" Would normally cost £85 complete. Our price £59.95

# The BATTERIES That Won't Let You Down! RECHARGEABLE

Cells in U2, U11 and Penlite U7 sizes  
Kestrel Battery Charging Unit



Uses:  
Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you must have utterly dependable battery power—then these new Alkaline-Manganese rechargeable cells will provide it. The cells can be recharged many times, a simple job with the Kestrel Charging Unit which has been specially designed for these new type batteries.

**PRICES**  
Batteries U2 equiv. £1-25

Penlite U7 equiv. 50p

U11 equiv. £1-03

Charging unit £3-99 with one battery holder

## LOOK AT THESE PRICES

### CARTRIDGES

Acos GP67-2, GP91-35C £1-12½; Acos GP93-1 £1-33½; Acos GP94-1 £1-62½; Sonotone 9TAHC £1-97. All above in makers' cartons. BSR X4H £1-50.

### THIS MONTH'S SPECIAL OFFER

Garrard SP25 Mk. III with KS40A cartridge. In good quality teak plinth with perspex dust cover. Complete with all leads ready to use £20. SP25 Mk. III deck only less cartridge £11-87.

### PLUGS & SOCKETS

Phono plugs, assorted colours 4½p; 45p per doz.; Coaxial plugs, aluminium 7½p; Coaxial couplers 7½p; 2 pin DIN plugs 15p; 3 pin DIN plugs 15p; 5 pin DIN plugs 17p; 2 pin, 3 pin & 5 pin DIN sockets 7½p; Wander plugs 2½p; sockets 3½p; Banana plugs 5½p; Sockets 5p; 3-5mm J/Plugs 7½p and 12½p; Standard J/Plugs with solder terminals 10p; Chrome 15p; Side Entry J/Plugs black and chrome 24p; Insulated J/sockets—o/cot 20p, e/cet 17p.

### ELECTROLYTIC CAPACITORS

4uF 160v 4p; 8uF 500v 15p; 10uF 160v 4p; 12uF 25v 4p; 16uF 450v 14p; 16uF + 16uF 450v 23½p; 30uF 10v 4p; 50uF 10v 4p; 100uF 9v 4p; 100uF 12v 4p; 150uF 12v 4p; 320uF 9v 5p; 1500uF 30v 19p; 10uF 16v 7½p; 5000uF 25v 50p; 10,000uF 25v 75p; 20,000uF 30v £1.05.

### MICROPHONES

Acos Mic 45 £1-12½; Acos Mic 60 99½p; Planet CM70 £1-50; Hand Mike 75p.

### VALVES

PY81 36p; PCL82 39p; EF183 45p; EF184 45p

Postage extra.

**GEORGE FRANCIS (Dept PW),**

12-14, MIDDLE GATE, NEWARK, NOTTS.  
Telephone: Newark 4733.

## U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

**LOFT MOUNTING ARRAYS**  
7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75.  
**WALL MOUNTING c/w WALL ARM & BRACKET**  
7 element 3-25. 11 element 3-75. 14 element 4-25. 18 element 4-75. **CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT.** 7 element 4-00. 11 element 4-50. 14 element 4-75. 18 element 5-25. **MAST MOUNTING arrays only.** 7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75. Complete assembly instructions with every aerial. **LOW LOSS** coaxial cable 99p yd. **KING TELEBOOSTERS** from 3-75. **LABGEAR** all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7-50. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np. C.W.O. Min. C.O.D. charge 25np.

**BBC-ITV-FM AERIALS**  
**BBC** (band 1) Wall S/D 2-00. **LOFT** inverted 'T' 1-25. **EXTERNAL 'H'** array only 3-00. **ITV** (band 3) 5 element loft array 2-50. 7 element 3-00. **COMBINED BBC-ITV-FM** 1+5 2-75. 1+7 3-50. **WALL & CHIMNEY UNITS** ALSO AVAILABLE. Pre-amps from 3-75. **COMBINED U.H.F.—V.H.F.** aerials 1+5+9 4-00. 1+5+14 4-50. 1+7+14 5-00. **F.M. RADIO** loft S/D 1-00 3 element 3-25. 4 element 3-50. Standard coaxial plugs 9np. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

**CALLERS WELCOMED**  
**OPEN ALL DAY SATURDAY**  
**K.V.A. ELECTRONICS**  
40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY  
Telephone 01-648 4884




Send to:  
275 WEST END LANE  
LONDON, N.W.8  
01-794 9611


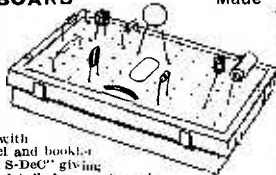
### S-DeC BREADBOARD

Solderless bread-boards panels, for fast, reliable component connections.



British Made

Single DeCs. One S-DeC with Control Panel and booklet "Projects on S-DeC" giving construction details for a variety of circuits. £1. P. & P. 17½p.

4-DeC KIT. Four S-DeCs with two Control Panels, and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £3.95. P. & P. 17½p.

T-DeC KIT £2.50. P. & P. 17½p.

S-DeC STOR £2.50. P. & P. 17½p.

### VHF AIRCRAFT BAND CONVERTER

When placed within 1in. of a MW band radio full coverage of VHF Aircraft Band 110-135 Mc/s can be obtained. All transistor, 9V battery operation. Fully tunable 18½in. x 7 section telescopic aerial. Size 4in. x 2½in. x 1½in.



OUR PRICE £3.60. P. & P. 20p

### GARRARD TURNTABLES

SP25 Mk.III £11.75  
2025 T/C... £9.87  
Base and cover for above... £5.98  
AP76... £19.50  
SL72B... £24.97  
SL75B... £28.35  
SL95B... £39.45 Base and cover for above £8.97+  
401... £31.50 P. & P. Decks, 62½p. Base & Cover, 50p. Deck/Base/Cover, 87p.



#### This Months Special Offers:

SP25 Mk.III with base £18.98. P. & P. 75p  
SP25 Mk.III with Sonotone 9TAHCD cartridge and base £18.75. P. & P. 75p

#### LIND-AIR AUDIO

(DEPT. PW10), 58 TOTTENHAM COURT ROAD LONDON. W.1. Tel.: 01-637 1601

**PIEZO DYNAMIC MICROPHONE**  
50k Ω £1.00 pp 8p

**MULLARD SCREW TERMINAL CAP**  
4,300uf 64v 50p pp 13p.

**BELLING LEE** 1.5 amp in-line rubber covered interference suppressor 25p pp 8p.

**SOLENOIDS 12 VOLT PULL ACTION**  
2" x 1" x ¼" 40p pp 8p.

**STO SEALED RELAYS DOUBLE POLE CHANGEOVER**  
48v 2500 Ex-equip. 15p pp 5p. Miniature 12v 280 New 2 changeover 40p pp 8p new.

**SIEMENS MINIATURE RELAY.** Double pole changeover dust cover/base 48v 2500 50p pp 5p new.

**TELESCOPIC AERIALS**  
Chromed 7" closed 28" extended 6 section ball jointed base 23p pp 8p new.

**MULLARD 4 DM 160 INDICATORS** in plastic holder/cover ex-equip. size approx. 1¼" x 1¼" x ½" 30p pp 8p.

**PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200**  
Diodes: 1 reed relay: 10 AZ 229 zener ass. capacitor/resistors. Power supply 22v 250 m/A DC. Output 240v. AC £1 pp 20p ex-equip.

**TOGGLE SWITCHES.** Single pole Double Throw ex-equip. new condition, 50p doz. pp 13p.

**FIBRE GLASS TAPE.** 100 yd. roll: 3" 3¼" wide £1 per roll pp 20p.

**PAINTON PLUG SOCKETS** Type 139 series working voltage 350v AC/DC current max. 3 amp AC/DC 7 pin plug & socket 50p pp 10p. 15 pin plug & socket £1 pp 10p.


CASH WITH ORDER PLEASE

# FIELD ELECTRIC LIMITED

3 SHENLEY ROAD, BOREHAMWOOD, HERTS.  
Adjacent Elstree Mainline Station  
Tel: 01-953 6009.

## H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

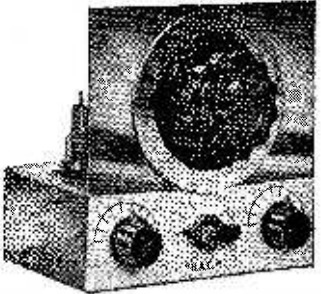

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

#### NEW "DX" RECEIVER

Improved one-valve model "DX" mark 2. Complete kit—price £3.30 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1

# INDEX TO ADVERTISERS

ASL .. .. .	548	Field Electric Ltd. .. .. .	551	Padgetts Radio .. .. .	536
Adcola Products Ltd. .. .	Cov. II	Francis, George .. .. .	550	Pembridge College of Electronics, The .. .. .	466
A. H. Supplies .. .. .	460	Francis, J. J. (Wood Green) Ltd. .. .	488	Personal Shoppers Plan Ltd. .. .	550
Antex .. .. .	455	Galleon Trading Co. .. .. .	546	Phonitronics .. .. .	547
Audio Supplies .. .. .	467	Global Audio Discount Warehouse	483	Premier Radio .. .. .	523
Audioscan .. .. .	549	Government Communications Headquarters .. .. .	546	R.D.I. Ltd. .. .. .	549
Baker Reproducers Ltd. .. .	496	'HAC' Shortwave Products .. .. .	551	Radio Components Specialist .. .	505
Bell's Television .. .. .	548	Harverson Supplies Co. Ltd. .. .. .	527	Radio Exchange Co. .. .. .	457
Bentley Acoustic Corporation Ltd.	536	Heath (Gloucester) Ltd. .. .. .	543	Radio Society of Great Britain .. .	536
Bernard, Gerald .. .. .	488	Henry's Radio Ltd. .. .. .	Cov. IV	Radio & T.V. Components (Acton) Ltd. .. .. .	464, 465
B.I.E.T. .. .. .	456, 532. Cov. III	Home Radio (Components) Ltd. .. .	470	Readers Radio .. .. .	456
Bi-Pak Semiconductors .. .	468, 469	International Correspondence Schools .. .. .	546, 495, 524	ROC Electronics Ltd. .. .. .	452, 453
Bi-Pre-Pak Ltd. .. .. .	451	Ivoryet .. .. .	488	RCS Products Ltd. .. .. .	450
Boffin Projects .. .. .	549	Jef Electronics .. .. .	546	RSC Hi Fi Centres Ltd. .. .. .	458, 459
Bournemouth College of Technology .. .	548	Jermyn Industries .. .. .	496	RST .. .. .	542
British National Radio School .. .	462, 519	Johnsons (Radio) Ltd. .. .. .	549	Scientific & Technical Services .. .	454
Broadway Electronics .. .. .	456	KVA Electronics .. .. .	550	SEBA Electronic Photography .. .	462
Bull, J., Electrical Ltd. .. .. .	491	Kensington Supplies .. .. .	549	Service Trading Co. .. .. .	484
Bush & Meissner Ltd. .. .. .	550	Keytronics .. .. .	546	Salop Electronics .. .. .	549
C. and S. .. .. .	549	King, J. M. .. .. .	549	Sellers, Richard .. .. .	547
Caranna, C. .. .. .	548	Lasky's Radio Ltd. .. .. .	449	Selray Book Co., The .. .. .	500, 528
Chromasonic Electronics .. .. .	547	Light Soldering Developments Ltd.	496	Sinclair Radionics Ltd. .. .. .	539, 540, 541
Colomar (Electronics) Ltd. .. .	528	Lindair (Optronics) Ltd. .. .. .	551	Shopertunities Ltd. .. .. .	466
Comet High Fidelity Discount Warehouse .. .	544, 545	Linear Products .. .. .	Cov. II	Smith G. W. & Co. (Radio) Ltd. .. .. .	535, 536, 537
Concord Electronics Ltd. .. .. .	464	Lewis Radio .. .. .	454	Stephens Electronics .. .. .	520
Coventry Movement .. .. .	450	Linstead .. .. .	488	Surpluetronics .. .. .	496
Crescent Radio .. .. .	506	London Computer Operators Training Centre .. .. .	454	Surplus Electronics Trading .. .	484
C. T. Electronics .. .. .	524	London Electronics College .. .. .	546	Swanley Electronics .. .. .	547
Data Publications Ltd. .. .. .	450	M & B Components (Leeds) Ltd. .. .	456	Thacker, A. H. .. .. .	484
D.E.W. Ltd. .. .. .	549, 550	Marshall, A., Son. .. .. .	531	Trade TV's .. .. .	549
Duke & Co. (London) Ltd. .. .	460	McArdle & Brainsby (Import & Export) Ltd. .. .. .	462	Velco Electronics .. .. .	547
Electro Value .. .. .	487	Multicore Solders Ltd. .. .. .	Cov. II	West London Direct Supplies .. .	450
Electrotec .. .. .	462	Nicholls, E. R. .. .. .	547	Wicks, D. T. & Co. .. .. .	532
Elekon Enterprises .. .. .	542	Oakfield Enterprises .. .. .	548	York Electronics .. .. .	542
Eley Electronics .. .. .	547			Yukan .. .. .	548
F. and B. Electronics .. .. .	547			Z & I Aero Services Ltd. .. .. .	552
Felstead Electronics .. .. .	560				

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 12½np in £ for postage and handling  
MINIMUM CHARGE 15np. No C.O.D. orders accepted  
Please note that the valves offered below are not necessarily of U.K. origin

85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

First Quality Fully Guaranteed



BRAND

ELECTRONIC VALVES

0A2	0.88	6AR11	1.25	6F11	0.40	10D2	0.50
0A3	0.45	6AS5	0.45	6F13	0.45	10F1	0.75
0B2	0.75	6AS7G	0.85	6F14	0.70	10F9	0.80
0B3	0.30	6AT6	0.35	6F15	0.85	10F18	0.50
0C3	0.85	6AU6	0.25	6F18	0.50	10L1	0.50
0D3	0.85	6AV6	0.80	6F23	0.85	10LD11	0.85
1B3GT	4.00	6AW8A	0.80	6F24	0.75	10P13	0.80
1C3P1	7.00	6BA6	0.25	6F25	0.30	10P14	1.10
1L4	0.40	6BE8	0.80	6F26	0.35	12AB5	0.70
1R4	0.45	6BF5	1.00	6F28	0.85	12AC6	0.50
1R5	0.40	6BF6	0.55	6J4	0.50	12AD6	0.55
1S4	0.30	6BH6	0.75	6J5GT	0.80	12AE6	0.55
1S6	0.80	6BJ6	0.50	6K7	0.30	12AL6	0.50
1T4	0.50	6BTA	0.60	6L7	0.45	12AQ6	0.50
1U4	0.30	6BN6	0.45	6K6GT	0.60	12AR6	0.80
1U5	0.60	6BN6	0.45	6K7	0.35	12AT7	0.35
1V2	0.50	6BQ5	0.25	6K8G	0.40	12AU6	0.85
1X2B	0.50	6BR8	0.70	6K25	0.75	12AU7	0.80
2D21	0.30	6BS7	1.80	6L6GT	0.45	12AV6	0.40
3A4	0.40	6BW6	0.85	6L7	0.40	12AV7	0.65
3B1P	3.00	6BW7	0.80	6L8	0.45	12AX7	0.30
3B4	0.35	6BX6	0.25	6LD20	0.50	12AY7	0.70
3V4	0.48	6BZ6	0.40	6N7GT	0.45	12B44	0.60
5R4GY	0.75	6C4	0.88	6P1	0.60	12BA6	0.40
5U4G	0.35	6CGT	0.40	6P28	0.65	12B47	0.40
5V4G	0.45	6CB6	0.85	6Q7	0.40	12BE6	0.40
5Y3GT	0.40	6CGA	0.25	6R7	0.40	12B7T	0.45
5Z4G	0.40	6CH6	0.80	6S7	0.40	12B7T	0.45
6B3OL2	0.80	6CL6	0.55	6S7GT0.35	0.85	12K7GT0.40	0.45
6BA3	0.35	6CW4	0.45	6S7GT0.35	0.85	12Q7GT0.40	0.45
6AF4A	0.55	6CY5	0.85	6S7GT0.40	0.98	12R87	0.40
6A7	0.40	6C7	0.70	6SR7	0.40	20D1	0.50
6A16	0.60	6DC6	0.50	6T5	0.35	20L1	1.15
6A78	0.30	6D8	0.80	6U4GT	0.65	20P1	0.50
6AK5	0.35	6DK6	0.50	6U8A	0.40	20P4	1.10
6AK6	0.60	6DQ6B	0.70	6V6GT	0.40	20P5	1.20
6AL3	0.43	6DS4	0.75	6X4	0.35	25C5	0.50
6AL5	0.20	6EAS	0.80	6X5GT	0.40	25L6GT0.50	0.50
6AM5	0.35	6E7	0.85	6Y2	0.15	30A5	0.75
6AM6	0.38	6E7	0.35	6Y6G	0.70	25Z6GT0.85	0.80
6AQ5	0.38	6EW6	0.70	7Y4	0.65	50A5	0.50
6AQ6	0.65	6F1	0.75	9DW6	0.40	50C6GL2.00	DL96
6AR5	0.45	6F5	0.75	10C2	0.50	30C1	0.30
6AR6	0.55	6F6G	0.85	10D1	0.55	30C15	0.80

30C17	0.90	90A4G	2.40	DY87	0.33	ECC189	0.65
30C18	0.80	90A5	2.50	DY802	0.35	ECCF80	0.35
30C15	0.85	90C1	0.65	EB8CC	0.65	ECF82	0.35
30FL1	0.75	90CV	2.40	EB180F	2.00	ECF86	0.65
30FL12	1.20	807	0.50	ECF804.1.65	EL822	1.30	
30FL14	0.85	813	3.75	EABC800.25	ECH42	0.75	
30L1	0.40	866A	0.75	EAF42	0.55	ECH81	0.30
30L15	0.85	5642	0.70	EBC33	0.50	ECH83	0.45
30L17	0.80	6080	1.60	EBC41	0.55	EM80	0.45
30P12	0.80	6146	1.60	EBC81	0.30	ECL80	0.50
30P19	0.85	6360	1.25	EBF80	0.40	ECL81	0.50
30P11	0.75	6989	2.25	EBF83	0.40	ECL82	0.35
30PL13	0.60	7199	0.80	EBF89	0.20	ECL83	0.70
30PL14	0.90	7380	2.00	EC83	0.50	ECL84	0.55
35A3	0.55	7586	1.25	EC86	0.80	ECL85	0.55
35A5	0.75	7895	1.25	EC88	0.60	ECL86	0.40
35B5	0.65	9002	0.40	EC90	0.32	ECL800	0.80
35C5	0.50	9003	0.50	EC91	0.80	EY38	0.55
35D5	0.75	AZ1	0.55	EC92	0.65	EY86	0.40
35L6GT0.50	0.50	AZ21	0.55	EC93	0.55	EY87	0.43
35Z4G	0.35	CY31	0.85	ECC10	2.25	EY88	0.43
35Z6GT0.80	0.80	DAF96	0.45	ECC40	0.65	EY89	0.43
50A5	0.75	DF96	0.45	ECC82	0.30	EZ40	0.50
50B5	0.50	DK40	0.60	ECC83	0.80	EZ45	0.50
50C5	0.50	DK92	0.55	ECC84	0.30	EZ46	0.50
50C6GL2.00	DL96	DL96	0.45	ECC85	0.40	EZ47	0.50
50L6GT0.55	DM160	DM160	0.65	ECC88	0.60	EZ48	0.50
85A2	0.50	DY86	0.32	ECC89	0.50	EZ49	0.50
				ECC91	0.20	EZ50	0.50

EP98	0.65	GZ34	0.60	PL82	0.45	U301	0.40
EF183	0.30	HABC800.45		PL83	0.45	U403	0.60
EF184	0.30	HE90	0.40	PL84	0.40	U404	0.60
EF800	1.00	KT66	2.05	PL92	0.35	U801	0.80
EK90	0.30	KT68	2.00	PL50A	0.80	UABC80	
EL33	1.25	N78	1.50	PL508	0.90		0.40
EL34	0.50	PABC800.40		PL509	1.10	UAF41	0.50
EL36	0.50	PC86	0.60	PL801	0.80	UAF42	0.55
EL37	1.80	PC88	0.60	PL802	0.85	UBC41	0.50
EL41	0.60	PC87	0.50	PM84	0.80	UBC81	0.40
EL42	0.65	PC900	0.48	PY31	0.30	UB80	0.40
EL81	0.55	PC94	0.40	PY33	0.63	UBF89	0.35
EL83	0.42	PC85	0.40	PY80	0.40	UBL1	0.60
EL84	0.25	PC88	0.55	PY81	0.30	UBL21	0.65
EL85	0.43	PC89	0.55	PY82	0.35	UC92	0.40
EL86	0.40	PC189	0.55	PY83	0.38	UC86	0.40
EL90	0.38	PC806	0.85	PY88	0.40	UC90	0.55
EL95	0.35	PC806	0.80	PY500	1.00	UC91	0.60
EL82	0.60	PCF80	0.80	PY800	0.40	UCH42	0.70
EL822	1.30	*CF82	0.35	PY801	0.50	UCH81	0.40
ELL80	0.75	ELL80	0.75	PCF84	0.60	UC18	0.60
ECH81	0.30	EM34	1.00	PCF86	0.60	UC182	0.35
EM71	0.80	PCF87	0.60	PCF88	0.85	UC183	0.60
ECH84	0.45	EM80	0.45	PCF801	0.50	QQV09-6	
ECL80	0.50	EM81	0.60	PCF802	0.50	1.25	UF42
EM84	0.35	PCF805	0.80	PCF806	0.70	QQV09-20A	
EM85	1.00	PCF806	0.70	PCF808	0.85	UF43	0.60
EM87	0.70	PCF808	0.85	PCF809	0.70	UF48	0.35
EN81	0.38	PCL800.70		PCF810	0.50	UF80	0.80
ECL81	0.50	EY81	0.40	PCF812	0.85	UF85	0.40
ECL82	0.35	EY80	0.55	PCF813	0.65	UF89	0.40
ECL83	0.70	EY81	0.40	PCF815	0.85	UY41	0.48
ECL84	0.55	EY80	0.55	PCF816	0.35	UY42	0.40
ECL85	0.55	EY81	0.40	PCF817	0.85	UY43	0.40
ECL86	0.40	EY80	0.55	PCF818	0.65	UY44	0.40
ECL800	0.80	EY83	0.55	PCF819	0.35	UY45	0.40
EY38	0.55	EY86	0.40	PCF820	0.70	UY46	0.40
EY86	0.40	PCL85	0.40	PCF821	0.70	UY47	0.40
EY87	0.43	PCL86	0.45	PCF822	0.70	UY48	0.40
EY88	0.43	PCL87	0.45	PCF823	0.70	UY49	0.40
EY89	0.43	PCL88	0.45	PCF824	0.70	UY50	0.40
EZ40	0.50	PCL89	0.45	PCF825	0.70	UY51	0.40
EZ45	0.50	PCL90	0.45	PCF826	0.70	UY52	0.40
EZ46	0.50	PCL91	0.45	PCF827	0.70	UY53	0.40
EZ47	0.50	PCL92	0.45	PCF828	0.70	UY54	0.40
EZ48	0.50	PCL93	0.45	PCF829	0.70	UY55	0.40
EZ49	0.50	PCL94	0.45	PCF830	0.70	UY56	0.40
EZ50	0.50	PCL95	0.45	PCF831	0.70	UY57	0.40
EZ51	0.50	PCL96	0.45	PCF832	0.70	UY58	0.40
EZ52	0.50	PCL97	0.45	PCF833	0.70	UY59	0.40
EZ53	0.50	PCL98	0.45	PCF834	0.70	UY60	0.40
EZ54	0.50	PCL99	0.45	PCF835	0.70	UY61	0.40
EZ55	0.50	PCL100	0.45	PCF836	0.70	UY62	0.40
EZ56	0.50	PCL101	0.45	PCF837	0.70	UY63	0.40
EZ57	0.50	PCL102	0.45	PCF838	0.70	UY64	0.40
EZ58	0.50	PCL103	0.45	PCF839	0.70	UY65	0.40
EZ59	0.50	PCL104	0.45	PCF840	0.70	UY66	0.40
EZ60	0.50	PCL105	0.45	PCF841	0.70	UY67	0.40
EZ61	0.50	PCL106	0.45	PCF842	0.70	UY68	0.40
EZ62	0.50	PCL107	0.45	PCF843	0.70	UY69	0.40
EZ63	0.50	PCL108	0.45	PCF844	0.70	UY70	0.40
EZ64	0.50	PCL109	0.45	PCF845	0.70	UY71	0.40
EZ65	0.50	PCL110	0.45	PCF846	0.70	UY72	0.40
EZ66	0.50	PCL111	0.45	PCF847	0.70	UY73	0.40
EZ67	0.50	PCL112	0.45	PCF848	0.70	UY74	0.40
EZ68	0.50	PCL113	0.45	PCF849	0.70	UY75	0.40
EZ69	0.50	PCL114	0.45	PCF850	0.70	UY76	0.40
EZ70	0.50	PCL115	0.45	PCF851	0.70	UY77	0.40
EZ71	0.50	PCL116	0.45	PCF852	0.70	UY78	0.40
EZ72	0.50	PCL117	0.45	PCF853	0.70	UY79	0.40
EZ73	0.50	PCL118	0.45	PCF854	0.70	UY80	0.40
EZ74	0.50	PCL119	0.45	PCF855	0.70	UY81	0.40
EZ75	0.50	PCL120	0.45	PCF856	0.70	UY82	0.40
EZ76	0.50	PCL121	0.45	PCF857	0.70	UY83	0.40
EZ77	0.50	PCL122	0.45	PCF858	0.70	UY84	0.40
EZ78	0.50	PCL123	0.45	PCF859	0.70	UY85	0.40
EZ79	0.50	PCL124	0.45	PCF860	0.70	UY86	0.40
EZ80	0.50	PCL125	0.45	PCF861	0.70	UY87	0.40
EZ81	0.50	PCL126	0.45	PCF862	0.70	UY88	0.40
EZ82	0.50	PCL127	0.45	PCF863	0.70	UY89	0.40
EZ83	0.50	PCL128	0.45	PCF864	0.70	UY90	0.40
EZ84	0.50	PCL129	0.45	PCF865	0.70	UY91	0.40
EZ85	0.50	PCL130	0.45	PCF866	0.70	UY92	0.40
EZ86	0.50	PCL131	0.45	PCF867</			

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

**Draughtsmanship**  
A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

**Electrical & Electronic**  
A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

**Radio & Telecomms.**  
C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

**Auto & Aero**  
A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

**Management & Production**  
Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing

**Numerical Control**  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

**Constructional**  
A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

**General**  
C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

**General Certificate of Education**  
Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT— SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B2, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



## POST THIS COUPON TODAY

To: B.I.E.T., Dept B2, Aldermaston Court, Reading RG7 4PF.  
Please send me book and details of your Courses in

Name..... Age.....

Address.....

Occupation.....

**B.I.E.T.—IN ASSOCIATION WITH THE SCHOOL OF CAREERS—ALDERMASTON COURT, BERKSHIRE**

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/Sia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage); For one year to any part of the world £2.65.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.


# HENRY'S RADIO LIMITED
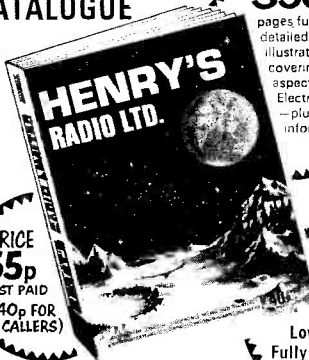
## ENGLAND'S LEADING ELECTRONIC CENTRES



HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

**COMPLETELY NEW  
10th EDITION  
CATALOGUE**



**350**

pages fully detailed and illustrated covering every aspect of Electronics — plus data and information

**PRICE 55p**  
POST PAID  
(40p FOR CALLERS)

**10,000** Stock lines at Special Low Prices and Fully Guaranteed

**PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES**

Send to this address—Henry's Radio Ltd., (Dept. PW), 3 Albemarle Way, London, E.C.1.—for catalogue only.

**A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!**

### TEST EQUIPMENT FOR EVERY PURPOSE



AF105 50k/V multimeter (illus.). Price £8-50, p.p. 20p. Leather case £1-42.  
200H 20k/V. Price £3-87, p.p. 20p. Case 62p.  
500 30k/V multimeter. Price £8-87, p.p. 20p. Leather case £1-50.  
THL33 2k/V. Price £4-12, p.p. 15p. Leather case £1-15.  
TE65 Valve voltmeter (illus.). Price £17-50, p.p. 40p.  
SE250B Pocket pencil signal injector. Price £1-75, p.p. 15p.

SE500 Pocket pencil signal tracer. Price £1-50, p.p. 15p.  
TE20D RF generator. Price £15, p.p. 40p.  
TE22D Matching audio generator. Price £17, p.p. 40p.  
TE15 Grid dip meter. Price £12-50, p.p. 40p.  
TO3 Scope 3 in. tube. Price £37-50, p.p. 50p.  
TE22 Audio Generator. Price £17, p.p. 40p.



### PANEL METERS

Complete range in stock. 38, 65 and 85 types plus large range Edge types also 240°-250° types. (Get a copy of our latest catalogue for full specifications and further ranges.)


**MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S**

**★ COMPONENTS IN STOCK FOR ALMOST ALL PUBLISHED DESIGNS. YOUR ENQUIRIES INVITED. SEND LARGE S.A.E. FOR QUOTATION.**

See our advertisement inside this magazine for the largest range of transistors etc. available in U.K.—Free list No. 36 on request.

**HENRY'S SUPPLY ALL YOUR AUDIO-ELECTRONIC NEEDS!**

### TRANSISTOR AMPLIFIERS

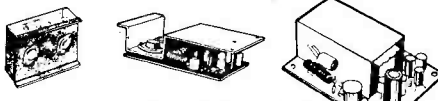

(Leaflets Ref. No. 6 and 8)

Post, etc. 20p.

4-300 4TR 9V 300mW £1-75 PA7 6TR 16V 7W £3-62  
104 4TR 9V 1W £2-12 608 6TR 24V 10W £4-12  
304 4TR 9V 3W £2-47 410 4TR 28V 10W £4-97  
555 6TR 12V 3W £2-75 MPA12/3 6TR 18V 12W £4-50

**OPTIONAL POWER SUPPLIES** Post, etc. 20p  
P500 (1 or 2) for 104, 304 £2-62  
P520 (1 or 2) for PA7 £3-47  
MU24/40 (1 or 2) for MPA12/3 or MPA12/15 £4-50  
P11 for 608 £2-87 P15 for 410 £2-62

### SINCLAIR PROJECT 60 PACKAGE DEALS—SAVE POUNDS!



2xZ30 amplifier, stereo 60 pre-amp, PZ5 power supply, £16-75, Carr. 40p. Or with PZ6 power supply £18-25. Carr. 40p.  
2xZ50 amplifier, stereo 60 pre-amp, PZ8 power supply £20-25 Carr. 40p. Transformer for PZ8 £2-45 extra. Any of the above with Active Filter unit add £4-75 or with pair Q15 speakers add £16. Also new FM Tuner £21. 2000 Amplifier £24-50, p.p. 50p. 3000 Amplifier £31-50, p.p. 50p. Also IC12 £2-50.

### LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2" x 8 1/2"

TYPE 150 6 watt, 3, 8 or 15 ohms £2-12. Post 22p.

TYPE 150TC Twin cone version £2-75. Post 22p.

TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3-50. Post 25p.

TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7-50. Post 28p.


**POLISHED CABINETS**

For 150, 150TC and 450 £4-50. Post 30p.

**TERRIFIC RANGE OF SPEAKERS, KITS AND CABINETS IN STOCK—SEE CATALOGUE OR YOUR ENQUIRIES INVITED.**



### HI-FI TO SUIT EVERY POCKET

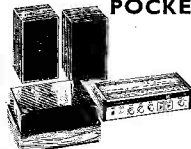

**TELETON '206'**, Garrard SP75, 10 Goldring G800 Series Carr., Plinth/Cover, 10 watt 3 way bookshelf Speaker Systems. All leads etc. (Rec. Price £81).

SAVE **£59-45** Carr. £2  
PLUS FREE STEREO HEADPHONES.

**TELETON F2000**, Med. Wave, Stereo FM Tuner Amplifier, Garrard 2025TC, 9TAHC Diam., Plinth/Cover, 10 watt Speaker Systems as above, all leads etc. (Rec. Price £91).

SAVE **£64-50** Carr. £2  
PLUS FREE STEREO HEADPHONES.

THE TWO MOST POPULAR SYSTEMS EVER—PLUS FULL 12 MONTHS' GUARANTEE AS WITH ALL "HENRY'S" OFFERS!

**FREE** 12 page Audio-Hi Fi Stock and Stereo Systems Discounts Lists. Save up to 40%! Demonstrations and Credit Terms (to callers) plus 12 months' guarantee.

### MONO, STEREO AND MIXING EQUIPMENT. HIGH QUALITY WITH LOW PRICES.



### SELF POWERED SILICON-FET CONTROL UNITS / PRE-AMPLIFIERS

FET 9/4 Mono or single channel. Adjustable levels. All facilities plus microphone. Mixing. Price £12-50  
FET 154 Stereo with all facilities, magnetic cart. input etc. Price £16-50

### SILICON POWER AMPLIFIERS FOR USE WITH ABOVE

PA 25 25 watts into 8 ohms £7-50  
PA 50 50 watts into 4 ohms £9-50  
MU442. Power Supply for 1 or 2 PA25's or 1 only PA50 £6-00. Post 20p.  
FREE BROCHURE NO. 25 ON REQUEST.  
NO SOLDERING—ALL UNITS INTERCONNECTING ON DEMONSTRATION AT "356"

### BUILD THIS VHF FM TUNER


5 MULLARD TRANSISTORS 300 kc/s BAND-WIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.



**TOTAL £6-97** p.p. 20p. Cabinet 100p. Decoder Kit £5-97  
Tuning meter £1-75  
Mains unit (optional) Model PS900 £2-47  
Mains unit for Tuner and Decoder PS1200 £2-62
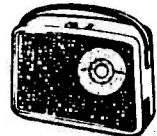
### BUILD YOURSELF A QUALITY RADIO

Excellent printed circuit design with full power output. Fully tuneable on both MW/LW bands. 7 Mullard transistors. Fitted Sin. speaker. Room filling power. Easy to build with terrific results. Two colour leather-cloth cabinet with silvered front. All local and continental stations. Complete detailed instructions.



Total cost £6-98 p.p. 35p. All parts sold separately. Ask for leaflet No. 1.

### PUBLIC ADDRESS AND DISCOTHEQUE EQUIPMENT

The largest and most versatile range available—all your requirements for outdoor, indoor, mobile and permanent installations. Sound and lighting supplied. Brochure No. 18 on request or call into "309" and see for yourself. Also Electronic Organs in Kit form—ask for Brochure No. 9.

**Electronic Components, Audio and Test Gear Centre**  
356 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-402 4736

**High Fidelity Sales & Demonstrations Centre**  
354 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-402 5854

**Electronic Organs, P.A. & Discotheque Centre**  
309 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-723 6963

**Mail Orders, Special Bargain Shop, Industrial Sales**  
303 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY