

PRACTICAL WIRELESS

FEBRUARY
1972

20p

Quality
HI-FI SYSTEM



ALSO:
CAR REV-COUNTER
TRANSISTORISED 'SCOPE

THE SOUND OF QUALITY



A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE.

REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.

SUPER 30 MkIII HI-FI STEREO AMPLIFIER

Only high grade components by leading manufacturers.

COMPLETE KIT OF PARTS Carr. 65p

Or FACTORY BUILT £33-75

with 12 months guarantee

Dep. £5-75 and 9 monthly payments £3-50 (Total £37-25)

Or FACTORY BUILT in Teak finished case as illus. Dep. £6 and 9 monthly payments £3-86

(Total £40-74)

PRINTED CIRCUITRY, TWENTY SILICON TRANSISTORS, FOUR DIODES, FOUR RECTIFIERS.

TECHNICAL DETAILS (Applying to each channel where appropriate)

CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono (5) Mono R (6) SPEAKER DIS. (7) Mains on/off.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms.

£25



£37-75

- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE.
- ★ WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

HUM & NOISE - 75dB Min. Vol. - 65dB Full Vol. HARMONIC DISTORTION
 FREQUENCY RESPONSE - 3dB 7Hz to 70KHz 0-1% at 1000 Hz 10 Watts
 TREBLE CONTROL: +16dB to -12dB at 14KHz
 BASS CONTROL: +17dB to -16dB at 40Hz
 CROSS TALK - 58dB
 SENSITIVITIES: Disc Mag. 2-5mV. Ceramic 35mV. Radio 120mV. Tape 120mV.
 REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio, (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

RSC G66 MkII 6+6 Watt HIGH QUALITY STEREO AMPLIFIER



Individual Ganged Controls. Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output

rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12dB. Treble Control ± 13dB. Selector switch for P.U. or Tape/ Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250V A.C. mains operation. Attractive Black and Silver finished metal facia plate and matching knobs.

COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT Carr. 40p


Comprehensive wiring diagrams and instructions

Or FACTORY BUILT IN TEAK VENEERED CABINET

Dep. £3-20 and 9 monthly payments £1-70 (Total £18-50)

£12-50

£15-99

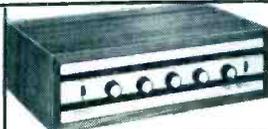

R.S.C. TA12 MKIII 6-5 + 6-5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED

SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6-5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram-P.U. cartridge. Radio tuner, Tape Recorder, etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls

★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250V. A.C. mains ★ Frequency Response 20-20,000 c.p.s. - 2dB

★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB

★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. Carr. 40p.

★ Handsome Brush Facia plate & Knobs. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS. £15-50

Factory built with £19-50 or Dep. £3 & 9 mthly pymts £2-15 (Total £22-85)

12 mths guarantee

Or in Teak veneer housing £23 Dep. £3 & 9 mthly payments £2-55 (Total £25-95)

Send S.A.E. for leaflet

FANE 807 HIGH FIDELITY LOUDSPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω

Please state impedance when ordering



£3-50

HI-FI SPEAKER ENCLOSURES

Modern design. Teak veneer finish. Acoustically lined. All sizes approx. Carr. 30p. per enclosure. JE8 Size 16 x 11 x 9in. Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. SE8 For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported

SE10 For outstanding results with 10in. Hi-Fi speaker Size 24 x 15 x 10in. P.t'd. £6-74

SE12 For excellent performance with 12in. Hi-Fi speaker and Tweeter. Size 25x16x10 1/2 £7-87



£5-35

£6-47

£7-87

R.S.C. A11 HI-FI 12-14 WATT AMPLIFIER

PUSH-PULL OUTPUT. Two input sockets with sep. vol. controls for mixing S.A.E. for leaflet.



FACTORY BUILT £14-75

or Dep. £3 and 9 monthly payments of £1-60 (Total £17-40)

High sensitivity, 5 valves. Bass and treble controls. Response ± 3dB 30-20,000 c.s. Hum level - 60dB Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "links". For Musical Instruments etc. Std. AC mains. For 3 & 15 ohm spkrs. Complete kit. Full instructions and point-to-point wiring diagrams. £10-50 Carr. 60p

Twin handled metal cover £1-75

FANE PRESSURE TWEETER

Model 303 Gauss 10,000. Impedance 3 ohms or 8-15 ohms. Excellent value

£2-50

Post Free

SPECIAL HI-FI OFFER

WHARFEDALE UNIT '3' SPEAKER KITS

Normally £12-53 Carr. 25p.

£10-50

★ DEMONSTRATION FACILITIES AT ALL BRANCHES

ALL RSC UNITS MANUFACTURED TO EXACTING SPECIFICATIONS



R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER

200-250V. AC mains operated. Frequency Response 30-20,000 c.p.s. - 2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift' and 'cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 50mV. Output rating I.H.F.M. Fully enclosed enamelled case. 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. £7-50 Carr. 40p

Or FACTORY BUILT WITH 12 MONTHS' GUARANTEE £9-75

R.S.C. PLINTHS

Superior Solid Natural Wood Construction for Record Playing Units, cut for Garrard 1025, 2025, 3000, AT60, SP25 etc. £3-15 WITH TRANSPARENT PLASTIC COVER £6-30





HIGH-FIDELITY STEREO

PACKAGE OFFERS

Four fully wired units ready to 'plug in'.
 ★ SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
 ★ GARRARD SP25 MK III Turntable on Plinth with cover
 ★ GOLDRING CS90 Ceramic Pick-up Cartridge with diamond stylus
 ★ PAIR OF STANWAY II Speaker Units
 Special Total Price **£79-80**
 Carr. £1-50

Terms: Deposit £12 and 9 monthly payments £8-55 (Total £88-95).

★ Super 30 Amplifier (15 + 15 watt) in veneered housing
 ★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
 ★ Goldring Magnetic P.U. Cartridge.
 ★ Pair of Stanway II speaker units.
 Special Total Price **£97-75** Carr. £1-50

Terms: Deposit £15 and 9 monthly payments £10-53 (Total £114-55).



ATTRACTIVE TEAK OR AFROMOSIA VENEERED CABINETS AND PLINTHS
 Send S.A.E. for coloured brochure showing other money saving offers.


★ TA12 AMPLIFIER 6.5 + 6.5 watt in veneered housing
 ★ GARRARD SP25 MK III Player unit on Plinth
 ★ GOLDRING CS90 Ceramic P.U. Cartridge with diamond stylus
 ★ PAIR OF DORCHESTER Loudspeaker Units
 Special Total Price **£58**
 Or Deposit £7-15 and 9 monthly payments £6-35 (Total £64-30). Carr. £1-25
 Trans. Plastic Cover £3-15 extra.

PACKAGE AS ABOVE but with Garrard 3000 Autochanger and Sonotone 9TA Ceramic Cartridge in lieu of SP25 and CS90 Carr. **£51-75**
 Or Deposit £6 and 9 monthly payments £5-70 (Total £57-30)
 Trans. Plastic cover £3-15 extra.

Matching as recommended for optimum performance. Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.

HIGH FIDELITY SPEAKER UNITS

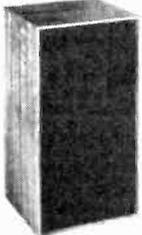Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.




DORCHESTER (Illustrated) Size 16x11x9in. apprx. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13x8in. Dual Cone speaker. Imp. 3 or 15 ohms. **£9-45** Carr. 40p.

STANWAY II Size 20x10 1/2 x 9 1/2 in. approx. Rating 10 watts. Inc. 13x8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives **£17-85** smooth realistic sound output. See 'package offers' for above illustration.

'YORK' HIGH FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25x14x10in.
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms
 ★ Performance comparable with units costing considerably more.

Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 8x5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-60 and 9 monthly payments £2-47 (Total £26-83).

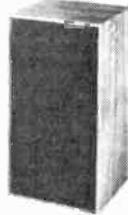

COMPLETE KIT **£23** Carr. 65p


DEMONSTRATIONS AT ALL BRANCHES

AUDIOTRINE A55 HIGH QUALITY STEREO SYSTEM

5 + 5 WATT OUTPUT

Garrard 5200 Changer with low mass pick-up arm and Stereo Cartridge. Controls: TREBLE, BASS, VOLUME, STEREO, BALANCE. Operation on 200-250v. A.C. mains. Output rating I.H.F.M.

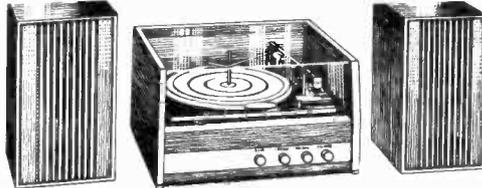Luxurious Teak Veneer Finished Cabinets. Silver finished fascia plate and matching control knobs.



Transparent plastic (tinted) cover included for main unit.
 PAIR OF LOUDSPEAKERS incorporating high flux 8in. 5in. speaker. Size approx. 13 x 7 1/2 x 8 1/2 in.

PRICE COMPLETE ONLY **£42**

Carr. £1-25

Terms: Deposit £5-50 and 9 monthly payments £4-50 (Total £46).

A REALLY SURPRISING STANDARD OF QUALITY IS OBTAINED FROM THIS COMPACT LOW PRICED SYSTEM

RSC TRANSFORMERS, L.F. CHOKES and RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary

Primaries 200-250v, 50c/s. Screened
MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.
 250v, 60mA, 6.3v. 2a. 99p
 250-0-250v, 60mA, 6.3v. 2a. £1-05
FULLY SHROUDED UPRIGHT MOUNTING
 250-0-250v, 60mA, 6.3v. 2a., 0-5-6.3v. 2a. £1-40
 250-0-250v, 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
 300-0-300v, 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
 300-0-300v, 130mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-45
 For Mullard 610 Amplifier. £2-45
 350-0-350v, 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
 350-0-350v, 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-65
 425-0-425v, 200mA, 6.3v. 4a., c.t., 6.3v. 3a. £4-95
 425-0-425v, 200mA, 6.3v. 4a., 6.3v. 3a., 5v. 2a. £5-10
 450-0-450v, 250mA, 6.3v. 4a., c.t., 5v. 3a. £5-50
TOP SHROUDED DROP-THO' TYPE
 250-0-250v, 70mA, 6.3v. 2a., 0-5-6.3v. 2a. £1-35
 250-0-250v, 100mA, 6.3v. 3.5a. £1-55
 250-0-250v, 100mA, 6.3v. 2a., 6.3v. 1a. £1-60
 350-0-350v, 80mA, 6.3v. 2a., 0-5-6.3v. 2a. £1-65
 250-0-250v, 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
 300-0-300v, 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
 300-0-300v, 6.3v. 130mA 4a. c.t. 6.3v. 1a. c.t. £2-80
 350-0-350v, 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
 350-0-350v, 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-60

FILAMENT or TRANSISTOR POWER PACK
 Types 6.3v. 1.5a. 48p; 6.3v. 2a. 54p; 6.3v. 3a. 76p;
 6.3v. 6a. £1-30; 12v. 1a. 55p; 12v. 3a. or 24v. 1.5a. £1-35; 0.9-18v. 1 1/2a. £1-10; 0-12-25-42v. 2a. £1-76
CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. 99p;
 2 1/2a. £1-10; 3a. £1-25; 5a. £1-45; 6a. £1-65; 8a. £2-20
AUTO (Step UP/step DOWN) TRANSFORMERS
 0-110/120v. 200-230-250v., 50-80 watts £1-10;
 150 watts, £1-90 250 watts £2-75; 500 watts £5-75.

OUTPUT TRANSFORMERS
 Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 50p
 Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 83p
 Push-Pull 10 watts 6V6, 6CL6 to 3, 5, 8 or 15 Ω £1-27
 Push-Pull EL84 to 3 or 15 Ω 10-12 watts £1-35
 Push-Pull Ultra Linear for Mullard 610, etc. £2-20
 Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15 Ω £1-99
 Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £3-30

You're never very far from an RSC HI-FI CENTRE

R.S.C. BATTERY/MAINS CONVERSION UNITS



TYPE BMI. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 in approx. Completely replaces batteries supplying 1.5v. and 90v. to battery radio where A.C. mains 200/250v. 50c/s is available.

Complete kit with diagram. **£3-25** Assembled ready for use **£3-75**

SMOOTHING CHOKES

150mA, 7-10H, 250 Ω 70p;
 100mA, 10H, 200 Ω 80p;
 80mA, 10H, 350 Ω 50p;
 60mA, 10H, 400 Ω 25p.

SELENIUM RECTIFIERS F.W. (Bridged)

All 6/12v. D.C. Output. Max. A.C. Input 18v 1a. 25p, 2a 35p, 3a. 50p, 4a. 65p, 6a. 80p.

RSC BULK BUYING ENSURES YOU GET BETTER VALUE

BRADFORD BLACKPOOL (AGENT) BIRMINGHAM DARLINGTON DERBY EDINBURGH GLASGOW HULL LEICESTER LEEDS LIVERPOOL LONDON MANCHESTER MIDDLESBROUGH NEWCASTLE-ON-TYNE NOTTINGHAM SHEFFIELD

SEE NEXT PAGE FOR TERMS OF BUSINESS, ADDRESSES etc.

THE SOUND

RSC

OF QUALITY

50 WATT SPEAKER



HEADPHONES
MICROPHONE
SEND S.A.E.
FOR LEAFLET



100 WATT AMPLIFIER

HI-FI CENTRES
LTD.

50 WATT SPEAKER



TWIN TURNTABLE
WITH PRE-AMP

**DISCOTHEQUE
EQUIPMENT**

—SAVINGS ON
PACKAGE OFFER

- (1) FAL FG1/2 Console
- (2) 100W Power Amplifier
- (3) Pair High Quality Headphones
- (4) Matching Microphone fitted to Headphones
- (5) Pair 50W Speakers black rexine covered Size approx. 18" x 18" x 8"

TOTAL COST OF ALL
ILLUSTRATED UNITS **£132**

Carr. £2.50
Terms: Deposit £20 and 9 monthly
payments of £14.34 (Total £149.06).

**RSC BASS REGENT
50 WATT AMPLIFIER**



A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram., radio, tape. Peak Output rating. Loudspeaker unit optional horizontal or vertical mounting.
★ Two extra heavy duty 12in. 50 watt Loudspeakers.
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes".
★ Bass and Treble controls.
Send S.A.E. for leaflet.

ONLY £60

Credit Terms Deposit
£16 & 9 mthly pymts Carr.£1.50
of £5.75 (Total £67.75)

SEND S.A.E. FOR LEAFLET

**FAL DISCOTHEQUE CONSOLE
FG1/2**



SEND S.A.E. FOR LEAFLET

Separate Volume Controls plus Treble & Bass Controls
Microphone Socket with associated Switch & Vol. Control
Incorporating twin Garrard SP25 Mk. III turntables and
Golding CS90 Ceramic Cartridges with diamond styli.
Size approx. 36" x 61" x 15".
Black Rexine covered Cabinet with lid. Fitted carrying handle.

TWIN
TURNTABLE
UNIT WITH
MONITORING
FACILITIES

£65 Carr.
£1.25

Terms: Deposit
£11 and 9 monthly
payments of £6.70
(Total £71.80).

DISCO/GROUP EQUIPMENT PACKAGE OFFERS

F.A.L. PACKAGE	PACKAGE PRICE	TERMS
F.A.L. PHASE 50 Mk. II AMPLIFIER PAIR FANE POP 25/2 25W L/SPEAKERS.	£44 carr. £1	Deposit £5.50 and 9 monthly payments of £4.72 (Total £47.98).
F.A.L. PHASE 50 Mk. II AMPLIFIER PAIR FANE POP 50 L/SPEAKERS OR PAIR L12/25 Cabineted Speakers.	£49.50 carr. £1	Deposit £10.50 and 9 monthly payments of £5 (Total £55.50)
F.A.L. PHASE 100 AMPLIFIER PAIR L125 50W L/Speakers in cabinets.	£118 carr. £2.50	Deposit £25 and 9 monthly payments of £11.82. (Total £129.58).
F.A.L. PHASE 100 AMPLIFIER 4 FANE POP 50 LOUDSPEAKERS.	£99 carr. £2	Deposit £15 and 9 monthly payments of £10.52 (Total £109.50).

**30 WATT HI-FI
AMPLIFIER**

FOR GUITAR, VOCAL OR
INSTRUMENTAL GROUP

A 4 input, 2 volume control Hi-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.C. facia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers.



ONLY £19.95 Carr.
65p

Terms: Deposit £3.70
and 9 monthly payments
of £2.10 (Total
£22.60).



**R.S.C. A10 30 WATT ULTRA LINEAR
HI-FI AMPLIFIER**

Highly sensitive, Push-Pull high output, 11um level, 70dB. Response ±3dB 30-20,000 c/s. All high grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 36 millivolts. For 11gh Impedance microphones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Functions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram., Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and Pick-up etc. to be used for mixing purposes, 200-250 v. 50 c/s A.C. mains. For 3 and 15 ohm speakers. Complete Kit of parts with wiring diagram and instructions. Twin-handled perforated cover £15.75
£1.90 Or factory built with EL34 output valves and 12 months' guarantee for £19.75 Carr. 65p
TERMS: Deposit £4 and 9 monthly payments of £2.10 (Total £22.90). Send S.A.E. for leaflet.

MINIMUM 12 MONTHS GUARANTEE, LABOUR & MATERIALS (Excl. Valves) ON ADVERTISED GOODS

**RE-FUND
OF INTEREST
CHARGES
ON CREDIT SALES
SETTLED IN
3 MONTHS**

**PHASE 50 Mk II
50W AMPLIFIER**

OUTPUT
50 Watts (Music)
40 .. R.M.S.
(Cont.)
100 .. (Peak)

£33.50 Carr.
65p

Terms: Deposit £6 and
9 monthly payments £3.50
(Total £37.50).

SOLID STATE, ALL SILICON TRANSISTORS. ★ Protective circuitry in case of overload or short circuiting of output. ★ Frequency Range 30-20,000 c.p.s. ★ 4 Separately controlled inputs for mixing; plus master volume control. ★ Individual Bass and Treble Controls. ★ Suitable for any loudspeaker combination between 3 & 30 ohms. ★ Cabinet covered in black rexine. Brushed silver finish metal facia, with black lettering. Matching control knobs. For Clubs, Discotheques, Hotels, Restaurants, Schools, Theatres, etc. For Vocal & Instrumental Groups, Gram., Radio or Tape. Send S.A.E. for leaflets.



**PHASE 100
100W AMPLIFIER**

OUTPUT
100 Watts (Music)
70 .. R.M.S.
(Cont.)

I.H.F.M. Output rating
£61.95 Carr.
75p


Terms: Deposit £12 and
9 monthly payments £6.25
(Total £68.25).

RSC

GABINET LOUDSPEAKERS

L13 8-10 WATTS

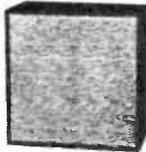Incorporating high flux 13" x 8" 8-10 watt loudspeaker. Available with 3 or 15 ohm impedance. (State when ordering.) Cabinet finished in Teak or Afrormosia Veneer. **£5-25** (Carr. 37p)



L12/25 25 WATTS



12" 25 watt heavy duty loudspeaker. Impedance 15 ohms. 18" x 18" x 8" approx. Veneered or Rexine/Vynair finish. Suitable small Discotheques, Clubs, Schools etc., etc. (Carr. 45p) **£10-50**

Terms: Deposit £3 and 9 monthly payments £1 (Total £12)

B4/100 100 WATTS

Fitted four extra heavy duty 12" 14,000 Gauss 50 watt speakers for conservative rating of 100 watts. Impedance 15 ohms. Cabinet in 1/2" chipboard with centre reinforcement back to front. Rexine/Vynair covered. Acoustically filled and pressurised. 27" x 27" x 14" approx. Ideal for bass guitar or electronic organ. **£55** Carr. £1-50

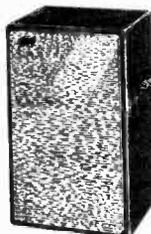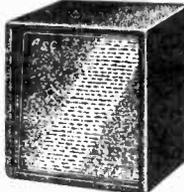
Or Deposit £8 and 9 monthly payments £5-90 (Total £61-10).



L125 50 WATTS

Incorporating two 12" 50 watt 14,000 Gauss extra heavy duty loudspeakers for conservative rating of 50 watts. Impedance 8-15 ohms. Sturdy pressurised cabinet in 1/2" chipboard. Rexine/Vynair Covered 31" x 20" x 16" approx. Suitable Vocal or Instrumental Groups. Bass Guitar or Electronic Organ, etc. For use in Discotheques, Clubs, etc. **£31** (Carr. £1-50)

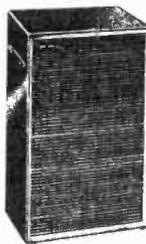Or Deposit £4 and 9 monthly payments £3-35 (Total £34-15).



FAL DUO/100

Employing two FANE 'CRESCENDO 12" 100 watt, super efficient, high flux, high power, full range speakers. Gauss 20,000. ULTRA HIGH SENSITIVITY. Ideal for Vocalists and Instrumental Groups. Frequency Range 30-16,000 c.p.s. Impedance 8 ohms. Cabinet constructed in heavy 1" Chipboard and covered in black Rexine and pleasing shade of Vynair with aluminium trim. Attractive design. Size 30" x 19" x 15 1/2" approx. Conservatively rated at 100 watts. (Carriage £1-50) **£63**

Terms: Deposit £9 and 9 monthly payments of £8-70 (Total Credit Price £89-80)

RSC

COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

C48S 25-30 WATTS

Fitted four 8" high flux 8 watt speakers. Overall size approx 48" x 10" x 5".

Terms: Dep £3 and 9 monthly payments £2 (Total £21)

£17-75

Carr 50p

C412S 50 WATTS

Fitted four 12" 11,000 line 15 watt speakers: Overall size approx 56" x 14" x 9".

Terms: Dep. £4 and 9 monthly payments £3 (Total £31)

£27-50

Carr 75p

C4/100 100WATTS

inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx 58" x 16" x 10" Acoustically filled and pressurised.

RECOMMENDED FOR DISCOTHEQUES, OR INSTRUMENTAL GROUPS

ONLY £50-50

Carr. £1



Terms: Dep. £7-50 and 9 monthly payments £5-45 (Total £56-55).

ALL FANE LOUDSPEAKERS GUARANTEED 2 YEARS

FANE 'POP' 25/2 LOUDSPEAKERS ONLY £6-75

12in. 25 Watt Dual Cone 15Ω. (for uses other than Bass Guitar or Electronic Organ),

or Dep. £1 and 9 mthly payments 75p (Total £7-75).

FANE ULTRA HIGH POWER LOUDSPEAKERS

ALL POWER RATINGS ARE R.M.S. CONTINUOUS. 2 YEARS' GUARANTEE. HIGH FLUX CERAMIC MAGNETS. ALL CARRIAGE FREE.



18" 'POP' 100

RATING 100 WATTS R.M.S. 14,000 gauss 8/15Ω

£22-50 Dep. £6 and 9 monthly payments £2-15. Total £25-35

15" 'POP' 60

RATING 60 WATTS R.M.S. 14,000 gauss 8/15Ω

£12-90 Dep. £3-30 and 9 monthly payments £1-30 (Total £15).

12" 'POP' 50

RATING 50 WATTS R.M.S. 13,000 gauss 15Ω

£10-50 Dep. £2 and 9 monthly payments £1-15. Total £12-35

PAIR SUITABLE ALL PURPOSES

FOR BASS GUITAR, ELECTRONIC ORGAN, ETC.

R.S.C. Branches listed below
Branches open all day Sat.

BRADFORD 10 North Parade (Half-day Wed.). Tel. 25349
BLACKPOOL (Agent) O & C Electronics 227 Church Street
BIRMINGHAM 30/31 Great Western Arcade, Tel. 021-236 1279 (Half-day Wed)
DERBY 26 Osmoston Rd. The Spot (Half-day Wed.). Tel. 41361
DARLINGTON 18 Priestgate (Half-day Wed.). Tel. 68043
EDINBURGH 133 Leith St. (Half-day Wed.). Tel. 556 5766
GLASGOW 326 Argyle St. (Half-day Tues.). Tel. 248 4158
HULL 91 Paragon Street (Half-day Thurs.). Tel. 20505
LEICESTER 32 High Street (Half-day Thurs.). Tel. 56420
LEEDS 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.). Tel. 28252
LIVERPOOL 73 Dale Street (Half-day Wed.). Tel. 236 3573
LONDON 238 Edgware Road, W.2 (Half-day Thurs.). Tel. 723 1629
MANCHESTER 60A Oldham Street (Half-day Wed.). Tel. 236 2778
MIDDLESBROUGH 106 Newport Rd. (Half-day Wed.). Tel. 47096
NEWCASTLE UPON TYNE 41 Blakett Street (opp. Fenwick's Store) (Half-day Wed.). Tel. 21469
NOTTINGHAM 19/19A Market Street (Half-day Thurs.)
SHEFFIELD 13 Exchange Street (Castle Market Bldg.) (Half-day Thurs.). Tel. 20716

Another New Branch!

NOW OPEN AT—
19/19A MARKET STREET

NOTTINGHAM

(Half Day Thursday)

Tel: 48068

RSC
HI-FI CENTRES LTD.

MAIL ORDERS & EXPORT ENQUIRIES TO:—
AUDIO HOUSE, HENCONNER LANE, LEEDS, 13.
Tel: Pudsey (08735) 77831.
TERMS C.W.O. or C.O.D. No C.O.D. under £1.
Postage 25p extra under £2. 30p extra over £2 or as quoted.
Trade supplied, S.A.E. please with enquiries.
Suppliers to Govt. Depts. Education Authorities, Schools
Hospitals H.M. Forces etc.
MAIL ORDERS MUST NOT BE SENT TO SHOPS

ADVERTISED UNITS are subject to the most stringent tests in our Quality Control Depot

ILLUSTRATED LEAFLETS on most advertised products available on request. Kindly ensure stamped addressed envelope enclosed.

95%
U.K. MAIL ORDERS
DESPATCHED
SAME DAY

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
THE VALVE SPECIALISTS Telephone 01-722-9090

OA2	.30	6BW6	.72	6R7G	.35	12SH7	.15	50FH5	.55	EAF42	.48	EL32	.18	KTW62	.63	PL81	.44	UCH81	.30	AC107	.15	HCY33	.20	OA200	.09
OB2	.20	6BW7	.54	6BA7GT	.35	12SJ7	.23	50L8GT	.45	E834	.20	EL34	.14	KTW63	.50	PL81A	.44	UCH82	.33	AC113	.25	HCY38	.23	OA202	.10
OZ4	.25	6BZ6	.31	6BA7M	.35	12SH7	.24	83A2	.43	EB31	.10	EL33	1.00	MHLDE	.75	PL82	.30	UCH83	.48	AC127	.17	HCY11	.38	OC23	.38
1A7GT	.35	6CB6A	.28	68C7GT	.33	12BQ7GT		90C1	.59	EB41	.48	EL37	.74	N78	2.05	PL83	.32	UF41	.50	AC128	.20	BF158	.29	OC23	.38
1B9GT	.35	6C4	.28	68C7GT	.33			150B2	.58	EB41	.29	EL41	.53	N308	.95	PL84	.30	UF42	.60	AC154	.25	BF159	.25	OC24	.38
1H5GT	.33	6C9	.73	68H7	.53	13D3	.45	807	.59	EB90	.28	EL42	.53	N339	.44	PL504/500	UF80	.35	AC156	.20	BF163	.20	OC25	.38	
1L4	.13	6CD6G	1.06	68J7	.35	1487	.75	5709	.80	EBF80	.30	EL81	.50	P61	.44	UF85	.34	AC157	.25	BF173	.38	OC26	.38		
1N5GT	.37	6CQ8A	.50	68K7GT	.23	19A45	.24	5763	.50	EBF83	.38	EL83	.38	PABC80	.33	PL505	1.30	UF86	.68	AC165	.25	BF180	.30	OC28	.60
1R5	.28	6C16	.38	68Q7GT	.35	20B6G	.85	AC3/PEN		EBF89	.27	EL84	.22	PC88	.47	PL509	1.80	UF89	.27	AC166	.25	BF181	.40	OC29	.63
184	.22	6CL6	.43	6V6G	.17	19G6	.50			EBL21	.60	EL85		PC89	.53	PL802	.75	UL84	.31	AC176	.55	BF194	.15	OC36	.43
1U4	.29	6CM7	.50	6V6GT	.80	20D4	1.05	AC3/PEN		EC86	.59	EL86	.38	PC95	.53	PM84	.34	UM80	.33	AC177	.28	BFY50	.23	OC42	.63
1U5	.48	6CU5	.30	6X4	.20	20P2	.65	DD	.98	EC88	.59	EL91	.23	PC97	.36	PC90	.32	PX4	1.16	UY1N	.50	ACY17	.25	BFY52	.20
2D21	.35	6CW4	.83	6X5GT	.25	20L1	.98	AC/PEN	.38	EC92	.34	EL95	.32	PC90	.32	PCX25	.88	UY41	.38	ACY18	.20	BFY52	.20	OC45	.11
2GK5	.50	6DE7	.50	7A7	.78	20P1	.50	AC/PEN(7)		EC92	1.50	EL360	.49	PCX84	.29	PY33/2	.60	UY85	.25	ACY19	.18	BY100	.18	OC46	.15
2A4	.25	6DT6A	.50	7B6	.55	20P3	.79		.98	EC93	1.50	EM80	.38	PCX85	.28	UY86	.25	ACY20	.18	BY105	.18	OC70	.15		
3D6	.19	6E2	.35	7B7	.32	20P4	.89	AC/TH1	.50	EC94	.60	EM81	.39	PCX88	.41	PY80	.33	U10	.45	ACY21	.19	BY114	.18	OC71	.11
3Q4	.38	6E6W6	.55	7C6	.80	20P5	1.00	AC/TP	.98	EC98	.18	EM84	.31	PCX89	.45	PY81	.28	U18/20	.75	ACY22	.15	BY126	.15	OC72	.11
3Q5GT	.35	6F1	.59	7H7	.28	25A6G	.29	AL60	.78	EC93	.18	EM84	.31	PCX89	.48	PY82	.24	U18/20	.75	ACY22	.15	BY126	.15	OC72	.11
384	.25	6F6	.63	7H7	.65	25L6G	.20	ATP4	.12	EC93	.22	EM85	1.00	PCF80	.28	PY83	.28	U19	1.73	ACY28	.18	BY127	.18	OC74	.23
3V4	.32	6F6G	.25	7Z4	.50	25Y5	.38	AZ1	.40	EC94	.28	EM87	.35	PCF82	.30	PY88	.32	U22	.39	AD140	.36	BYZ10	.25	OC75	.11
4C8B	.50	6F13	.33	9D7	.78	25Y5G	.43	AZ31	.48	EC95	.24	EY51	.35	PCF84	.40	PY500	.95	U26	.64	AD149	.50	BYZ11	.25	OC76	.15
5C8B	.50	6F14	.42	10C2	.49	25Z4A	.28	AZ41	.53	EC96	.40	EY81	.42	PCF86	.38	PY800	.38	U28	.58	AD161	.45	BYZ12	.25	OC77	.27
5V4G	.34	6F18	.45	10D8T	.50	25Z5	.40	CL33	.90	EC98	.35	EY83	.54	PCF200	.68	PY801	.38	U45	.78	AD162	.45	BYZ13	.25	OC78	.15
5Y3GT	.28	6F23	.68	10F9	.45	25Z6G	.43	CV43	.53	EC9189	.48	EY84	.50	PCF801	.29	PZ30	.48	U47	.64	ADT140	.63	CG12E	.20	OC78D	.15
5Z40	.34	6F24	.68	10F18	.35	30A5	.44	CY1C	.53	EC904	.55	EY87/6	.30	PCF802	.40	QQV03/10	U191	.58	AF102	.90	F8Y11A	.23	OC81	.11	
6/30L2	.55	6P25	.54	10LD11	.53	30C1	.28	CY1C	.28	EC907	1.70	EY88	.40	PCF805	.60	Q95/10	.49	U281	.55	AF106	.50	F8Y41A	.23	OC81D	.11
6A8G	.33	6F28	.60	10P13	.54	30C15	.60	DAP91	.20	ECF80	.27	EY91	.53	PCF806	.57	QV04/7	.68	U281	.40	AF114	.25	GD9	.20	OC82	.11
6A8T	.15	6F32	.15	10P14	1.08	30C17	.77	DAF96	.33	ECF82	.28	EZ40	.40	PCF808	.68	U282	.40	AF115	.15	GET113	.20	OC82D	.11		
6A8S	.25	6G18A	.50	12A6	.63	30C18	.60	DF91	.14	ECF86	.64	EZ41	.42	PCF890	.82	R10	.75	U301	.40	AF117	.19	GET116	.40	OC83	.20
6A8J	.43	6K6	.50	12A6G	.40	30F5	.65	DF96	.34	ECF8042	.10	EZ80	.21	PCL82	.32	R11	.98	U403	.33	AF121	.30	GET118	.20	OC84	.24
6A8K	.25	6G07	.50	12A08	.40	30FL1	.60	DY86	.28	ECH21	.68	EZ81	.22	PCL83	.68	R16	1.75	U404	.38	AF124	.25	GET119	.20	OC123	.23
6A8L	.30	6H6GT	.15	12A26	.48	30FL2	.60	DK40	.55	ECH42	.60	EZ80	.20	PCL84	.34	R17	.88	U801	.98	AF126	.18	GET573	.38	OC139	.23
6A8M	.50	6J5G	.29	12A76	.28	30FL12	.69	DK92	.35	ECH81	.27	PW4/500.75	.39	PCL85/85	.84	R19	.30	U4020	.38	AF139	.65	GET587	.43	OC140	.95
6A8N	.49	6J5GT	.19	12A77	.18	30FL14	.68	DK96	.35	ECH83	.39	PW4/900.75	.40	SP42	.75	VP23	.40	AF178	.68	GET873	.23	OC169	.23		
6A8Q	.22	6J6	.18	12A06	.21	30L1	.28	DL96	.35	ECH84	.34	GZ30	.34	PCL86	.38	SP61	.28	VP41	.38	AF180	.48	GET887	.23	OC172	.35
6A8R	.30	6J7G	.24	12A07	.18	30L15	.58	DM70	.30	ECL80	.30	GZ32	.41	PCL88	.65	TH4B	.50	VP61A	.35	AF186	.55	GET897	.23	OC200	.22
6A8T6	.18	6J7GT	.38	12A06	.28	30L17	.67	DM71	.38	ECL82	.30	GZ33	.70	PD500	1.44	TH233	.98	VU111	.44	AF239	.38	GET898	.23	OC201	.38
6A8U	.20	6J8A	.50	12A07	.29	30P4MR	.95	DY86/7	.24	ECL83	.52	GZ34	.48	PEN4DD		TP2820	.98	VU120	.60	BA102	.45	M1	.15	OC202	.43
6A8V	.28	6K7G	.10	12BA6	.30	30P12	.69	DY802	.35	ECL84	.54	GZ37	.67	UABC80	.30	VU120A	.60	BA115	.14	M3	.15	OC203	.30		
6A8W	.54	6K7GT	.23	12B6G	.30	30P19	.87	E80F	1.20	ECL85	.54	HABC80	.44	UAF42	.49	VU133	.35	BA116	.25	OA5	.28	OC204	.30		
6A8X	.39	6K8G	.16	12B17	.27	30P4	.58	E83F	1.20	ECL86	.40	HD10		PEN36C	.75	UBC41	.45	W107	.54	BA125	.13	OA5	.13	OC205	.43
6B8A	.13	6L1	.98	12E1	.85	30PL1	.59	E88CC	.60	EF22	.63	HL41DD	.98	PEN45	.40	UBC81	.40	W107	.50	BA130	.10	OA10	.43	ORP13	.53
6B8B	.20	6L7GT	.38	12J5GT	.30	30PL13	.75	E92CC	.40	EF40	.49														
6B8C	.50	6L18	.44	12J7GT	.33	30PL14	.65	E180F	.90	EF41	.53														
6B8E	.21	6L19	1.38	12K5	.50	30PL15	.87	E182CC1	.00	EF42	.33														
6B8F	.43	6L20	.48	12K7GT	.34	35A3	.48	E1148	.53	EF54	.98														
6B8G	.39	6N7G	.16	12S4GT	.27	35L6GT	.42	E450	.18	EF72	.75														
6B8Q	.38	6Q7	.43			35W4	.23	E476	.88	EF80	.22														
6B8R	.79	6Q7G	.27	128C7	.35	35Z4T	.24	E48C80	.30	EF83	.48														
6B8S	.63	6R7	.55	128G7	.23	35Z5GT	.30	E4C91	.38	EF85	.28														

All valves are unused, boxed, and subject to the standard 90 day guarantee. Terms of business - Cash or cheque with order only. Post/packing 3p. per item, subject to a minimum of 9p per order. Orders over £5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p. extra per order. Complete catalogue with conditions of sale 22p. price P. post paid. Business hours Mon.-Fri. 9-5.30 p.m. Sat. 9-1 p.m.

We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.

TOP QUALITY - LOW COST


AMATEUR RADIO EQUIPMENT



NEW!

MULTIBAND-6 TRF SHORT WAVE RECEIVER KIT

This new all transistor T.R.F. Receiver tunes 550 Khz-30 Mhz (540-10 metres) complete coverage, no gaps. Trawlers, Ship to Shore telephone, Six Amateur Bands, 160-10 metres, International Broadcast, Australia, Far East, Russia, USA, etc. etc., using miniature plug in coils. Hi-Gain FET Regen. Dec./Pre-Amp A.F./A.F. Module giving full loud speaker output to any external 2/3 ohm speaker. Two separate Tuning Dials, Calibrated Mhz and Degrees. Electrical Bands spread on all bands. Regen. det. receives CW/SSB signals also. Handsome styling with Black Perspex Panel, Steel Cabinet in Charcoal finish with Chrome Trim. This is a quality CODAR-KIT with full 12 months guarantee. No technical knowledge required, printed circuit construction. Instruction Manual with pictorial drawings backed by friendly Help-U After Sales Service if you have any queries. Complete Kit (even to the resin-cored solder) with 3 Coils. £11.50 Carriage 50p. Available NOW! NEW AT5 MK 2, 12 WATT. Transmitter 160-80 metres. Also NEW PR40 FET Pre-Selector. Stamp brings illustrated leaflets.

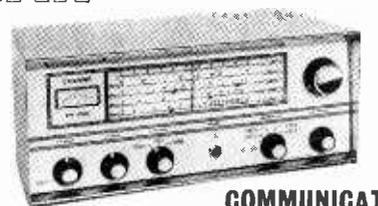

CR 70A COMMUNICATION RECEIVER

The CODAR CR 70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, Illuminated "S" Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals, 5 valves inc. two twin triodes giving 7 valve line-up, separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee. Complete ready built £24.50. Carriage 50p. Ask the chap who's got one, there's lots of them!


ON THE DESIGN STAFF - G3SZM G3IRE G8BBI

CODAR RADIO COMPANY

Unit 1, Meadow Road Industrial Estate, East Worthing, Sussex.

NEW from Lasky's

Criterion Mk X

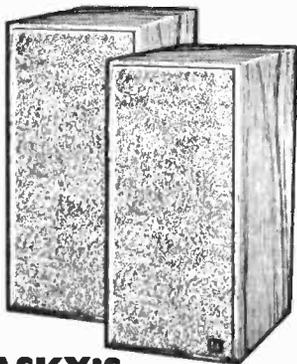

Because of the increasing demand for inexpensive, high quality bookshelf speakers, we have seen fit to introduce the Criterion Mk. X bookshelf system. The speaker is a sealed infinite baffle type enclosure using 8in. woofer, a 5in. mid. range and 2 1/2in. tweeter. The compact cabinet is in oiled walnut and black woven speaker grille cloth. Frequency response 40Hz—20KHz. Power handling capacity: Max. 20 watts. Impedance: 8 ohms. The Criterion is fitted with two types of speaker lead connections—screw terminal or phono. Size: 18 1/2in. (H.) x 9 1/2in. (W.) x 9 1/2in. (D). Operational horizontally or vertically.

LASKY'S AMAZING PRICE

£25

C & P £1.00
£13.50 each

INTERNATIONAL

MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in. RT.20 Message Tape 225ft.	19p	5 1/2in. RT.25 Triple play, 2,400ft.	£1.31
3 1/2in. RT.21 Triple play, 600ft. Mylar	50p	7in. RT.22 Standard play, 1,200ft. Acetate	63p
5in. RT.23 Double play, 1,200ft.	75p	7in. RT.10 Standard play, 1,200ft. Mylar	63p
5in. RT.18 Long play, 900ft. Acetate	50p	7in. RT.12 Long play, 1,800ft. Mylar	95p
5in. RT.17 Standard play 600ft.	43p	7in. RT.13 Double play, 2,400ft. Mylar	£1.25
5 1/2in. RT.15 Double play, 1,800ft. Mylar	£1.13	7in. RT.11 Long play, 1,800ft. Acetate	75p
5 1/2in. RT.16 Long play 1,200ft. Acetate	75p	7in. RT.19 Triple play, 3,600ft. Mylar	£2.50
5 1/2in. RT.24 Standard play 900ft. P.V.C.	68p	3 1/2in. RT.22 Quad play, 1,100ft.	£1.02
5 1/2in. RT.14 Long play 1,200ft. Mylar	75p		

P. & P. 5p extra per reel, 4 reels & over Post Free. Special quotes for quantities

OUT NOW! 1972 AUDIO TRONICS

The great new 1972 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 44 newspaper size pages—many in full colour—are packed with 1,000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories and don't miss LASKY'S AUDIO TRONICS CREDIT CARD SCHEME offering holders one months interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

ALSO the fantastic £1,000 plus SONY COLOUR TV Audio Tronics '72 Competition

BSR McDONALD MP60


High precision low-mass counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.

LASKY'S PRICE £10.95 C & P 50p

BSR McDONALD UNITS & PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

MODEL	A	B	C	D	E
MP.60	10.95	15.50	18.50	18.73	22.00
HT.70	15.90	19.90	23.50	23.73	27.00
610	14.50	18.75	23.00	22.25	25.50
510	12.10	16.50	18.85	20.09	22.85
310	9.75	14.00	16.50	17.25	20.28
210					9.95
MP.60 TPD2 Styrene base				17.50	21.00

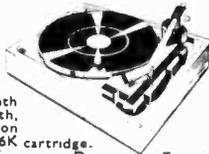

GARRARD UNITS AND PACKAGES

GARRARD SL 55B

Four speed autochanger

LASKY'S PRICE £10.25 C & P 50p

Now available ZERO 100S

£43.50, C & P £1.50

Garrard SP25 Mk. III £11.50



Garrard SL40B £9.95
Garrard AP76 without cart. £20.95
Garrard 3000 with 9TA cart. £10.50
Garrard 2025TC with K540A cart. £8.50

GARRARD PACKAGES

Post on packages 75p

Garrard AP76 with Micro M2100e cart. and Lasky's plinth and cover £31.50
Garrard AP76 with Shure M44E cart. and Lasky's plinth and cover £33.75
Garrard SP25 Mk. III, AD76K cart. and Lasky's plinth and cover... £18.50
Garrard SP25 Mk. III with Shure M3 cart. and Lasky's plinth and cover £23.95

LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

Type	Singles	5	10	20
C-60	32p	£1.52	£2.96	£5.60
C-90	50p	£2.37	£4.62	£8.75
C-120	69p	£3.28	£6.38	£10.85

Carriage and packing: each-7p, 5-25p, 10-40p, 20-68p.

Lasky's Radio Limited

Branches

207 EGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605

Open all day, 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day, 9 a.m. - 6 p.m. Monday to Saturday


NEW CITY BRANCH NOW OPEN

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel.: 01-790 4821

DIGITAL CLOCK SCOOP

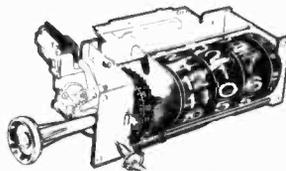

EXCLUSIVELY FROM LASKY'S

for you to mount into any housing. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back o. switch). SPEC.: 210/240V a.c., 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS.

LASKY'S PRICE £6.50

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12-HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR
- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER
- SPECIAL QUOTES FOR QUANTITIES
- C & P 52p

TRIO HS.1 & HS.2 STEREO HEADPHONE BARGAINS

Models HS-1 and HS-2. Both these sets by TRIO offer really superb stereo reproduction in a lightweight, fully adjustable headset designed for optimum comfort. Listening fatigue is unknown with TRIO headphones. Brief spec. both models: Input imp. 80 nominal (matching 4 to 8Ω); max. input: 0.5W; frequency response 20-19 kHz; output sensitivity at 1mW input; HS-1 118 dB, HS-2 111 dB; weight 0.66lbs. Identical in appearance—both models are finished in ivory with contrasting foam filled ear pads and head band.



LIST PRICE £8.40 LIST PRICE £6.75

HS.1 £5 HS.2 £4 Post 18p



RUSSIAN WORLD BEATER!

JUST ARRIVED! The Fabulous BRAND NEW

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

VEF 204
8 WAVEBAND
10 TRANSISTOR PLUS 3 DIODES PORTABLE RADIO

THIS OFFER ONLY FROM US!

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!



AND NOW WITH SHIP-TO-SHORE MARINE BAND

BATTERY MODEL £13.97p
BOX POST ETC. 50p
MAINS/BATTERY ELIMINATOR £13p extra

WE COULDN'T EVEN MAKE THEM FOR OUR FANTASTIC PRICE!
*COMPARE ITS PERFORMANCE with £42 RADIOS!

Important! This very latest model incorporates all the latest technological improvements and supersedes all earlier models! Yes DESIGNED FOR WORLD WIDE RECEPTION—it'll probably make your present radio seem like a "crystal set"! It even incorporates a special MARINE WAVEBAND to receive spoken communications from ship-to-shore! We're almost giving them away at only £13.97p—a mere fraction of even today's Russian miracle price! Compare performance with £42 radios! *Refund if not astounded! Purer and sweeter tone than ever! Wider band spread for "pin-point" station selection! The Russians have really surpassed themselves this time proving again their ability in the field of space communications. Yes, 8 separate wavebands, including Standard Long, Medium and Short waves to cover the world, PLUS special "ship-to-shore" MARINE BAND! Thousands of different transmissions and stations at your fingertips 24 hours a day, including ships at sea, etc., and messages from all over world—truly nothing is secret! You must hear it to believe it! Superb, sweet tone—controlled from a whisper to a roar! Push-pull output! Separate ON/OFF volume & Treble/Bass tone controls! Press-button dial illumination! Take it anywhere—runs economically on standard batteries or through battery eliminator from 220/240v. AC mains. Internal ferrite rod plus telescopic aerial. It's also a fabulous CAR RADIO! Black & Chrome case 11ins x 8ins x 3ins. overall approx. Made to give years of perfect service. Complete with WRITTEN GUARANTEE, manual with simple operating instructions & circuit diagram. ONLY £13.97p (with mains/battery eliminator £13.97p extra). POST 50p. Standard batteries 38p extra. Can also be used through extension amplifier, tape recorder or public address system. Send today or call. (SORRY—we cannot change these new radios for any earlier model already purchased!)

fabulous BRAND NEW MODEL **SAVE £13.98 NOW!** FIRST CLASS MAKER'S DE LUXE MODEL

Cassette TAPE RECORDER and PLAYER

WITH REMOTE CONTROL MICROPHONE

RECOMMENDED LIST PRICE £26.97p
OUR PRICE £12.99
POST ETC. 30p

MAKE NO MISTAKE—this is the EXPENSIVE model with "PIANO KEYBOARD" CONTROL PANEL and SPECIAL RECORDING LEVEL! SAVE £13.98! Due to price we cannot mention famous maker's name—but rest assured you're getting one of the BEST! Our latest cassette model—no fiddling with awkward tape and reels, just "slap in" a cassette and off you go! (takes 30-, 60-, and 90-minute standard Philips Cassette tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction. Remote control microphone. Separate volume control! Rapid rewind! Beautiful tone from a whisper to a roar! Completely self-contained—record anywhere. Separate jacks for remote control microphone, etc. Size 9" x 4 1/2" x 2 1/2" overall approx. Case design can vary slightly. With carry handle. With WRITTEN G'TEE and instructions. Only £12.99, post 30p. ALSO AVAILABLE: SPECIAL BATTERY/MAINS AC/DC MODEL, ready to plug in, £2.50 extra if required. Refund g'tee. BONUS one per customer: Cassette tape, set of Standard batteries and microphone stand all for 51p extra if required. Send quickly or call.

Send quickly to Uxbridge Road or call at either. (COMMERCIAL TRAVELLERS! PLEASE NOTE: Merchandising Office at Holborn store.)

SHOPERTUNITIES LTD. SL

Dept. WF/13, 184 UXBRIDGE RD. (facing Shepherds Bush Green), LONDON, W12 8AQ. (Thurs. 1, Fri. 7). Also 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C1. (Thursday 7 p.m.). BOTH STORES OPEN MON-SAT FROM 9 a.m.-6 p.m.

THIS FANTASTIC OFFER ONLY FROM US! fabulous BRAND NEW **SAVE £20.25 NOW!** This equipment got EVERYTHING!

SOLID STATE

BATTERY/MAINS AC/DC

Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

WITH REMOTE CONTROL MICROPHONE

OUR PRICE **£23.75** CARR. ETC. 35p

RECOMMENDED RETAIL PRICE £44

FANTASTIC (even by our standards!) Brand new—the latest sensation in the world of sound! First class makers! Not only a fabulous VHF AM/FM Radio AND Cassette Tape Recorder and Player combined, but it also runs off standard batteries or mains (simply plug in the built-in 220/240v. AC line cord) Now you can record and play back anything, anywhere! You can even tape direct from the Radio as you listen! RECOMMENDED RETAIL PRICE GENUINELY £44. YET WE OFFER AT ALMOST HALF PRICE! Just look at these wonderful features:—*Press button Keyboard Control panel! *New 'pop-up' Cassette, ejection system! *"MAGIC EYE" Visual Battery check/recording level indicator! *Separate ON/OFF, and HI-LO volume controls! *Heavy duty built-in speaker! *Earphone (for personal listening or "monitoring") and extension speaker sockets! *Remote control microphone! *Built-in swivel telescopic extension aerial (24 inches approx)! Magnificently made case, size 11ins. x 9ins. x 3ins. overall approx., with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120 minute Philips Cassette Tapes obtainable everywhere. But wait, the amazing built-in full circuit VHF AM/FM Radio gives you superb clarity of tone and incredible station selection—Unique rotating Station Selector Dial—get all local city & regional stations in every part of the country plus B.B.C. National VHF. Picks up dozens of foreign stations and short mobile transmissions. Fabulous in car! You could pay ££££ more for a Car Radio or Car Cassette Tape Player ALONE! OUR PRICE, ONLY £23.75 CARR. ETC. 35p. Complete with simple instructions, personal listening earphone, remote control microphone with on/off switch and microphone stand, with WRITTEN GUARANTEE. BONUS OFFER—Standard Batteries and Cassette Tape 25p extra. Refund g'tee. it's an offer you cannot afford to miss!

ONLY FROM US! **FIRST SHIPMENT JUST ARRIVED!**

BRAND NEW MODEL

RUSSIAN WORLD BEATER! WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!

6 WAVEBAND 10 TRANSISTOR PLUS 3 DIODES PORTABLE RADIO

WORLD WIDE RECEPTION THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

£9.97p BOX POST ETC. 43p

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

*COMPARE ITS PERFORMANCE with £34 RADIOS!

THE VERY LATEST MODEL, SUPERSEDING ALL PREVIOUS MODELS—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! Finest value we've ever offered! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare the performance and value with that of £34 radios!

*Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection. Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over world—nothing is secret! The radio enthusiast has the world in his hand! Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume Treble/Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2in. length. It's also a fabulous CAR RADIO—any speed, requires no additional aerial. UNIQUE! Elegant Black, White and Chrome finish case. SIZE 10 1/2" x 8" x 3 1/2" overall approx. Magnificently designed, made to give years of perfect service. With WRITTEN GUARANTEE, manual with simple operating instructions and circuit diagram. ONLY £9.97, POST ETC. 43p. Standard batteries 25p extra if required. Can also be used through extension amplifier, tape recorder or public address.

SEND OR CALL A VISIT TO SHOPERTUNITIES COULD SAVE YOU £££!


JUST BEGINNING?

Then try our **8-Watt, 10-Transistor Stereo Amplifier R.137**

ROC price
£10.50

Separate tone and volume controls for each channel, inputs for turntable (ceramic cartridge), tuner and tape. Attractive black crackle finish with brushed aluminium front. Frequency response: 70-20,000 Hz \pm 3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 80mV; tuner/aux 80mV.

Normal retail price: £14.70

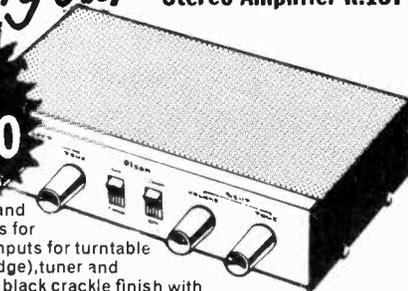


FIRST STEP TO STEREO!

5-Watt Transistor Stereo Amplifier Chassis R.123

Completely self-contained, fully transistorised, mains-powered (240v AC) amplifier, needing only cabinet and knobs. Ideal for adapting mono players to stereo. Frequency response: 40-17,000 Hz \pm 3dB. Output: 2.5 watts per channel @ 8 ohms. Input: Phono 600mV.

Normal retail price: £7.30

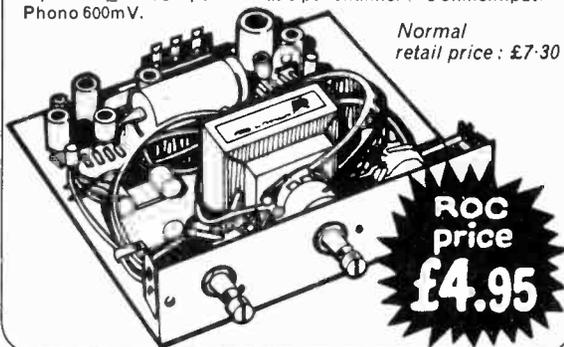

ROC price
£4.95


SOUNDS SENSATIONAL

AM/FM/MPX Stereo Tuner Amplifier R.124

A top quality amplifier with facility for receiving stereo broadcasts. Separate bass and treble controls, automatic frequency response, stereo headphone socket, output power: 8 watts. FM frequency range 88-108 MHz; AM frequency range 535-1605 KHz. Inputs for turntable (ceramic cartridge) and tape. Frequency response: 50-10,000 Hz \pm 3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 200mV, tape 100mV. FM: Sensitivity 20 μ V, stereo separation 26dB, image rejection 55dB. AM: Sensitivity 300 μ V.

Normal retail price: £42.00

ROC price: £29.95

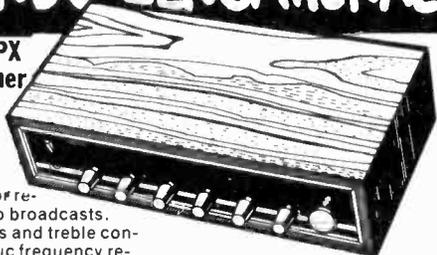

SAVE
£14

AM/FM/MPX Stereo Tuner R.132

Matching unit to the R.131 amplifier. Covers full AM and FM bands. Separate signal meter. FM frequency range: 87-108 MHz; AM frequency range 525-1605kHz. AM: Sensitivity 3 μ V, stereo separation 30dB @ 1kHz, image rejection 60dB. AM: Sensitivity 250 μ V.


Normal retail price: £50.00

ROC PRICE
£36



AMAZING OFFER!

Stereo Cassette Tape Unit R.142

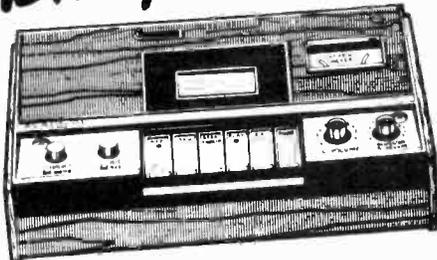

Complete stereo record and playback unit with line and microphone inputs. Fitted with tape counter, separate pause control, recording level metres for each channel, pop-up cassette ejection. Supplied complete with two pencil microphones. Wow & flutter better than 0.3%, frequency response 100-10,000 Hz. Tape speed: 1 $\frac{1}{2}$ IPS, 4.75 CMS. Rewind time: Better than 60 sec (C.60 cassette).
Normal retail price: £65.00

ROC price
£49.50

We don't want you to

Every piece of electronic or audio equipment we sell is built to our specifications. It comes complete with a Guarantee. And it's tested before it leaves us.

We bend over backwards in our advertising to make sure everything we say is factually accurate. But, buying mail-order, even though you're buying from us, we accept you could still end up with a piece of equipment that's not exactly what you wanted. And we think that's unfair.

TOP VALUE




40-WATT TRANSISTOR STEREO AMPLIFIER R.131

Separate bass and treble controls, separate left and right volume controls. Separate loudness control. Switches main and remote speaker outputs. Inputs for turntable (switched for magnetic or ceramic), tuner (see R.132) and tape. Outputs for tape and headphones. Frequency response 20-20,000 Hz \pm 3dB. Output: 20 watts per channel @ 8 ohms. Inputs: Phono magnetic 3.0mV RIAA, crystal 100mV, tape 160mV, tuner 160mV.

Normal retail price: £39.60

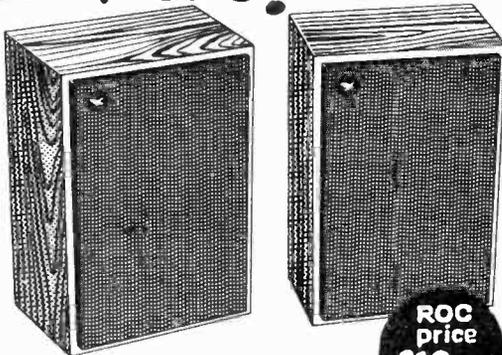2 for the price of one! Matched Stereo Speakers R.446



Heavily lagged teak finish cabinets each with large dual cone base unit and separate tweeter. Power handling: 16 watts peak; frequency range: 40-18,000 Hz; impedance: 8 ohms. Size: 14 x 8 1/2 x 6 1/2.

Normal retail price: £19.60


pay for your mistakes

So we've got a proposition for you. If you buy a piece of Roc equipment, and it's not quite what you expected, send it back within seven days, and as long as it's as good as new we'll give you your money back. O.K.?

Return of post mail-order service; orders over £10 post free, (U.K. only) add 25p for p & p to orders under £10. HP terms available.

ROC ELECTRONICS LIMITED
B. Jory Esq 193 Edgware Rd., London W2 1ET. 01-723 6211.
Callers at Shop welcome 9-6 Mon to Sat (Thurs 1pm)

FANTASTIC BARGAIN

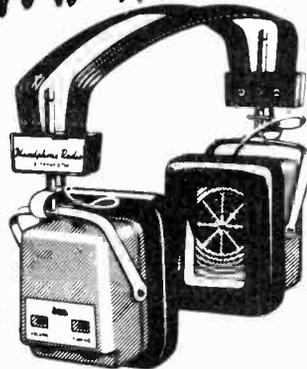

Headphone Radio R.143


For completely private listening without the distortion of the ordinary earphone adaptor. Battery operated; PP3. Fully transistorised. Frequency range: 535-1600 K Hz, Medium Wave Band. Maximum output: 300mW.

Normal retail price: £9.40

Don't read this!

10-watt Transistor Stereo Amplifier R.136

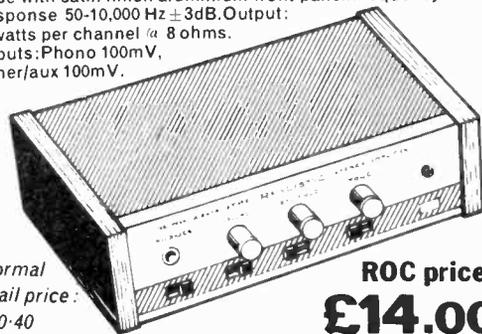Ganged volume, balance and tone controls. Inputs for turntable (ceramic cartridge), tuner (see R.134) or tape. Oiled walnut case with satin finish aluminium front panel. Frequency response 50-10,000 Hz \pm 3dB. Output: 5 watts per channel @ 8 ohms. Inputs: Phono 100mV, tuner/aux 100mV.



Normal retail price: £20.40

ROC price: £14.00

The Perfect match!

AM/FM/MPX Stereo Tuner R.134



Matching unit to the R.136 amplifier. Covers AM and FM tuning bands with automatic stereo signal light. FM frequency range: 88-108mHz; AM frequency range: 535-1605kHz. FM: Sensitivity 5uV, stereo separation 25dB @ 1kHz, image rejection 50dB. AM: Sensitivity 250uV.

Normal retail price: £28.60

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
 - Radio Amateurs' Examination
 - Radio Operator Certificates
 - General Certificate of Education, etc.
- Now available Colour T.V. Servicing

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

Accredited by the CACC.



**INTERNATIONAL
CORRESPONDENCE SCHOOLS**

EST. 1891

Dept. 171, Intertext House, Stewarts Road, London, S.W.8 4UJ
Please send me the ICS prospectus—free and without obligation.
(state Subject or Exam).....

NAME (BLOCK CAPITALS PLEASE).....
ADDRESS

AGE.....OCCUPATION..... 2/72

INTERNATIONAL CORRESPONDENCE SCHOOLS

This MONTH'S Best Buy...



AKG K50 Dynamic Stereo headphones

Complete with spare ear muffs.

Total (value £10.40) Our Price **£5.90** + 23p p. & p.

Available only from us at this price. Due to entire purchase of manufacturer's remaining stock this fantastic offer is open only while stocks last. Send a a. e. for full Technical Leaflet.

BARGAINS FOR PERSONNEL SHOPPERS ONLY

Plinth covers various sizes 75p. Garrard AP75 units £15. Garrard SL75 units £20. Garrard SL95 units £25. SP25 units (damaged) £6. Teleton 203 Amps. £14. EMI 450 kits 150 only £2.50.

CASH & CARRY GOODS



Sinclair 2000	£22
Sinclair 3000	£30
Metrosound ST20	£24
Teleton 203B	£18
Alpha F212	£26

SINCLAIR Project 60

SAVE nearly £8 Normal price £23.90

Designed for building into plinths etc., complete with two Z30 Output stages **£16** plus 50p carr. (20 watt) and power supply unit. Send S.A.E. for full technical brochure.



GARRARD SP25 mk III

£10.50 Plus 50p carriage Normal price £15.57

Wired with mains cable and 5ft. twin screened stereo cable, 5 pin din plug. 53p extra.

Plinth and Cover for above £4 plus 50p p. & p.

AP75 P & C (slightly soiled) £3.50 plus 50p p. & p.

PLUGS



Pack 107 5-Pin Din	20p
Pack 108 3-Pin Din	18p
Pack 135 1/2" Jack	25p
Pack 130 1/2" Jack Stereo	48p
Pack 103 Loudspeaker Plug	15p
Pack 100 Phono Plug	6p
Pack 230 3-Pin Socket	23p
Pack 236 5-Pin Socket	30p
Pack 234 Loudspeaker Socket	30p
Ready-made Leads	
3-pin to 3-pin Din	63p
3-pin to open end	53p
5-pin to 5-pin Din	80p
5-pin to open end	85p
5-pin to 4 phono plugs	93p
Speaker lead Din to spade 12ft	38p
Extension lead Din plug to socket 12ft	85p
All leads approx. 6ft. in length. Post free, by return.	

Replacement Stereo

DIAMOND STYLI

8TA 9TA 9TAHC GP91 ST4 ST9 EV26 GC8 **75p** each others on request +13p p. & p. Double Diamond add 50p.

Countdown SPEAKER

Teak Cabinet

£12 plus 38p carr. & ins.

A speaker of outstanding specifications and technical merit. Solid teak cabinet size: 14" x 10" x 6". Originally designed for use with our Countdown stereo budget system but now available separately.



EMI 20w matched loudspeaker set 350

Frequency range: 20 to 20,000Hz. **£7** plus 50p p. & p.

EMI 10w matched loudspeaker set 450

Our price **£3.35** plus 25p. p. & p.

13 1/2" x 8 1/2" elliptical loudspeaker and independent high frequency units with associated crossover network. Frequency range 55 to 13,000Hz. The cone of the bass unit has a surround designed for high travel giving freedom from distortion when operated at low frequencies. EMI 14A/770C **£14.50** plus 50p p. & p. Bass Speaker



Magnetic cartridges

Diamond **£4.00** stylus

plus 13p p. & p.

Today's value **£6**. Stylus replacement can be carried out without removing cartridge. Styli £2.13 + 13p p. & p.



SONOTONE Cartridge ...

(Fitted Diamond Styli) (Ceramic) list price **£4.10**

Sensitivity: 9TAHC 55mV/cm/sec rms minimum at 45° at 1,000Hz measured on Decca SXL2057 **£2.50** plus 13p p. & p.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) **£1.25** + 13p. p. & p.

J. J. FRANCIS (WOOD GREEN) LTD

123 ALEXANDRA ROAD, HORNSEY, LONDON, N.8. Tel: 01-888 1662



E.240 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price **£1.80**.

ES.240 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit and packed in a transparent display box. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price **£1.83**



CN.240/2 Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price **£1.70**

CN.240 Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price **£1.70**

G.240 Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price **£1.83**.



your soldering appliance specialists.



CCN.240 New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety; fitted with 3/32" iron coated bit. Spare bits 1/8" 3/16" and 1/4" available. Can also be supplied for 220 volts. Price **£1.80**

CCN.240/7 The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price **£1.95**



SK. 2 SOLDERING KIT


This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price **£2.40**.



MES. 12

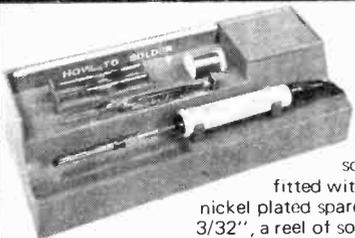A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price **£1.95**.




SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.

Price **£2.75**

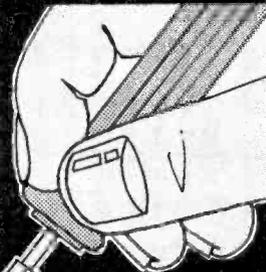sign here to answer all your soldering problems.



from electrical, radio or car accessory shops or from **Antex Ltd., Freeport** (no stamp required) **Plymouth**

PL1 1BR Telephone 0752 67377/8

Please send the Antex colour catalogue.

Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

Name _____

Address _____

P.W.2

MAIL ORDER DEPARTMENT
 No. 11 Mayes Rd., London, N22 6TL
 01-888-3206

RADIO LTD

MULTIMETERS T.T.C. RANGE

C1000 £2-60
 Resistance Range x 1K ohms
 AC/DC Volts 1000V, 250V,
 50V & 10V
 DC Current 1mA 100mA
 AC/DC Range 1000 ohms/Volt
C1050 £4-92 Res. Range x1K, x10
 DC Volts 1-2V, 600V, 150V, 15V & 3V
 AC Volts 1-2KV, 300V, 30V & 6V
 DC Current 120 micro A 300mA
 AC 5,000 ohms/V DC 10,000 ohms/V
C1052 £6-50 Res. Range x1, x10, x100 & x1K
 AC Volts 1-2KV, 600V, 300V, 30V & 6V
 DC Volts 3KV, 1-2KV, 600V, 300V, 30V & 6V
 DC Current 600mA, 30mA, 3mA, 30 micro A
 AC 15,000 ohms/V DC 30,000 ohms/V
C1084 £11-00
 Res. Range x1, x100, x1K, x10K
 DC/AC Volts 1-2KV, 600V, 300V, 60V, 12V,
 3V & 0-6V
 DC Current 12A, 300mA, 30mA, 3mA & 60
 micro A
 Switch—Divide by 2 on Volts and Amps. Ranges
 DC 50 & 25K ohms/V 5 & 2.5 Kohms/V
C1085 (Illustrated) £16-25
 Res. Range x1, x10, x1K, x10K
 AC Volts 1-2KV, 600V, 300V, 60V, 12V, 3V
 DC Volts 1-2KV, 600V, 120V, 60V, 12V, 3V,
 1-2V, 0-6V
 DC Current 12A, 300mA, 60mA, 6mA, 30 micro A
 Switch—Divide by 2 on Volts and Amps. Ranges
 DC 100,000 ohms/V AC 10,000 ohms/V
 Postage and Insurance 40p per Meter.
 Each meter comes complete with test leads
 and battery/batteries.



BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator, 2 1/2 in x 2 in x 3 in approx. 4 1/2 V £1-50, 6V £1-50, 9V £1-50, 7 1/2 V complete with cable and plug for Philips Cassette. **£2** plus 8p P. & P. each.



BARGAIN S.C.R.
 Tested Thyristor.
 400V, 3Amp.
 45p each.
 5 for £2-00.
 5p P. & P.



2N3055 POWER TRANSISTOR
 New low price
 80p each.
 5p P. & P.

LIGHT DIMMER

The unit comes complete with MK Ivory Front Plate and Control Knob, when used in place of Light Switch it will control your room lighting from off to full brightness. Power—up to 300 watts interference suppressed.
£2-75 plus 8p



D.P.D.T. SLIDE SWITCH



SIZE
 1 1/2 ins long 1/2 wide
 each
13p
 3p Postage

MINI LOUD-SPEAKERS

2 1/2 inch 40 ohm 38p
 2 1/2 inch 75 ohm 38p
 2 1/2 inch 8 ohm 33p
 2 1/2 inch 25 ohm 33p
 3 inch 8 ohm 40p
 Plus 3p post & packing each



ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL
 Spec.: 5 Section

Extended Length 100cm
 Length under Fender 40cm
 Cable Length 150cm

Supplied complete with Fixing Bracket and Control **£5-50** plus P. & P. 25p. Switch.




CHROMOSONIC SOUND OPERATED LIGHT DISPLAY

This compact unit (size 8 1/2" x 5 1/2" x 3" high) is connected directly across the speaker output of an amplifier, it will then convert audio signals into a spectacular three colour light display (500 watts light output each colour). Send S.A.E. for further details or call in at any branch for demonstration. **£18-50** P. & P. 38p



100 WATT

HIGH POWER AMPLIFIER

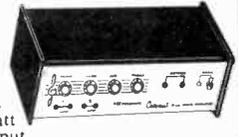

- In excess of 100 watt peak output
 - Open and short circuit proof
 - Sensitivity 10mV for full output
 - Frequency Response 10-25,000Hz
 - Safe with all loudspeaker systems 4 to 16 ohms
 - Silicon transistors used throughout
 - F.E.T. Front end
 - Send S.A.E. for further details.
- ▲ **£42-00** if purchased with light unit above **£40-00**
 Post and Insurance £1-00.

GUARANTEED 12 MONTHS

MINI STROBE


Another Bargain from Crescent. 1/4 Joule output, speed variable from 2-10 flashes per sec. and powered from AC mains 220V-250V. Housed in its small attractive fibreglass case (size approx. 6ins x 4ins x 4ins high). Makes an ideal Strobe Unit for Discos, Experimental Work, Photography and many other uses. **£18-50** plus P. & P. 38p.



BRANCHES

11e 40 MAYES RD LONDON N22-888-3206
 13 SOUTH MALL EDMONTON GREEN LONDON N9 803-1685

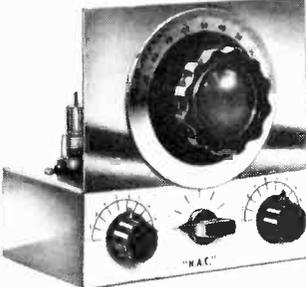H.A.C. SHORT-WAVE KITS
WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER

Improved one-valve model "DX" mark 2. Complete kit—price £3.80 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS
 29 Old Bond Street, London W.1

QUALITY HI-FI SYSTEM

COMPONENTS FOR THE SAND FILLED ENCLOSURES DESCRIBED IN THIS ISSUE.

- BAKER MAJOR 12" 8Ω £9**
- EAGLE—M.H10 TWEETER £3-15p**
- EAGLE CN 216 ACROSSOVER 95p**
- 2P 6W Brilliant Switch + Knob**
 + Resistors 58p

TWO COMPLETE KITS ONLY £27
POST FREE. OTHERWISE 15p p. & p.

R. - B. TELEVISION

82 NORTH LANE, EAST PRESTON, SUSSEX.
 MAIL ORDER

The Unique MULTI-MINI TWIN-VICE



An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5.90 (24p P & P)
 ALSO AVAILABLE
SINGLE VICE: £3.37½ (20p P & P)
COVENTRY MOVEMENT CO LTD.
 Dept. P.W.5.
 BURNSALL ROAD, COVENTRY CV5 6BU
 STD O203-74363

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATION & AUTHORITIES, ETC.
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS

CLEAR PLASTIC METERS TYPESW.100 100 x 80 mm.		BAKELITE PANEL METERS TYPE S-80 80 mm. square fronts	
50μA \$3.60	20V. D.C. ... \$2.10	50μA \$2.20	200mA \$1.80
50-0-50μA \$3.30	50V. D.C. ... \$2.10	50-0-50μA \$2.10	300mA \$1.80
50-0-100μA \$3.45	300V. D.C. \$2.10	100μA \$2.75	50V. D.C. ... \$2.60
100μA \$3.20	1 amp. D.C. \$2.10	100-0-100μA \$2.10	300V. D.C. \$2.60
100-0-100μA \$3.45	5 amp. D.C. \$2.10	500μA \$2.00	5 amp. A.C. \$2.60
500μA \$3.35	300V. A.C. \$2.10	1mA \$2.60	300V. A.C. \$2.60
1mA \$2.10	VU Meter... \$2.75	20V. D.C. ... \$2.60	VU Meter... \$2.87

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/4in. x 4 1/4in. fronts.		Type MR.38P. 1 21/32in. square fronts.	
50μA \$3.60	10V. D.C. ... \$2.00	50μA \$2.10	5 amp. \$1.70
50-0-50μA \$3.30	20V. D.C. ... \$2.00	50-0-50μA \$2.10	10V. D.C. ... \$1.50
100μA \$2.80	50V. D.C. ... \$2.00	100μA \$2.10	20V. D.C. ... \$1.50
100-0-100μA \$2.50	300V. D.C. \$2.00	100-0-100μA \$1.75	50V. D.C. ... \$1.50
1mA \$2.80	15V. A.C. ... \$2.00	200μA \$1.75	150V. A.C. \$1.70
100-0-100μA \$2.50	300V. A.C. \$2.00	500μA \$1.75	300V. D.C. \$1.50
5mA \$2.00	S Meter 1mA \$2.10	1mA \$1.70	15V. A.C. ... \$1.70
50μA \$2.00	VU Meter... \$2.20	5mA \$1.70	50V. A.C. ... \$1.70
100μA \$2.00	5 amp. A.C.* \$2.00	10mA \$1.70	300V. A.C. \$1.70
500μA \$2.00	10 amp. A.C.* \$2.00	50mA \$1.70	500V. A.C. \$1.70
1 amp. \$2.00	30 amp. A.C.* \$2.00	100mA \$1.60	S Meter 1mA \$2.10
5 amp. \$2.00		150mA \$1.60	VU Meter... \$1.70

Type MR.52P. 2 1/2in. square fronts.		Type MR.45P. 2in. square fronts.	
50μA \$3.10	10V. D.C. ... \$2.00	50μA \$2.25	5 amp. \$1.70
50-0-50μA \$2.80	20V. D.C. ... \$2.00	50-0-50μA \$2.10	10V. D.C. ... \$1.50
100μA \$2.60	50V. D.C. ... \$2.00	100μA \$2.10	20V. D.C. ... \$1.50
100-0-100μA \$2.50	300V. D.C. \$2.00	100-0-100μA \$1.75	50V. D.C. ... \$1.50
1mA \$2.60	15V. A.C. ... \$2.10	200μA \$1.87	150V. A.C. \$1.70
100-0-100μA \$2.50	300V. A.C. \$2.10	500μA \$1.75	300V. D.C. \$1.50
5mA \$2.00	S Meter 1mA \$2.10	1mA \$1.70	15V. A.C. ... \$1.80
50μA \$2.00	VU Meter... \$2.20	5mA \$1.70	300V. A.C. \$1.80
100μA \$2.00	5 amp. A.C.* \$2.00	10mA \$1.70	S Meter 1mA \$1.85
500μA \$2.00	10 amp. A.C.* \$2.00	50mA \$1.70	5 amp. A.C.* \$2.25
1 amp. \$2.00	30 amp. A.C.* \$2.00	100mA \$1.70	10 amp. A.C.* \$2.10
5 amp. \$2.00		500mA \$1.70	50 amp. A.C.* \$2.10
		1 amp. \$1.70	30 amp. A.C.* \$2.10

***MOVING IRON—ALLOTHERS MOVING COIL**
 Please add postage

SEW EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA \$5.00	20V d.c. \$4.40
100μA \$4.25	50V d.c. \$4.40
1mA \$4.40	300V d.c. \$4.40
50-0-50μA \$4.45	
1-0-10μA \$4.40	Dual range
1A d.c. \$4.40	500mA/5A d.c. \$4.65
5A d.c. \$4.40	5V/50V d.c. \$4.65
10V d.c. \$4.40	

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/4in. square fronts.

500mA \$1.90	1 amp. \$1.90
5 amp. \$1.90	15 amp. \$1.90
30 amp. \$1.90	50 amp. \$1.90
5V. D.C. ... \$1.90	10V. D.C. ... \$1.90
20V. D.C. ... \$1.90	50V. D.C. ... \$1.90
150V. D.C. \$1.90	300V. D.C. \$1.90
50V. D.C. ... \$1.90	30V. A.C. ... \$1.95
150V. D.C. \$1.90	50V. A.C. ... \$1.95
300V. D.C. \$1.90	300V. A.C. \$1.95
30V. A.C. ... \$1.95	5 amp. A.C.* \$1.95
50V. A.C. ... \$1.95	10 amp. A.C.* \$1.95
300V. A.C. \$1.95	20 amp. A.C.* \$1.95
50 amp. A.C.* \$1.95	30 amp. A.C.* \$1.95
50 amp. A.C.* \$1.95	50 amp. A.C.* \$1.95
VU Meter... \$2.10	



EDGWISE METERS


Type PE.70. 3 17/32in. x 1 15/32in. x 2 1/2 in. deep.

50μA \$3.10	500μA \$2.75
50-0-50μA \$3.00	100μA \$2.45
100μA \$3.00	300V. A.C. \$2.45
100-0-100μA \$2.90	VU Meter... \$2.40
200μA \$2.90	

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

MULTIMETERS for EVERY purpose!

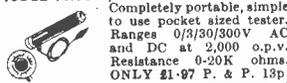ROUND SCALE TYPE PENCIL TESTER MODEL TS.68



Completely portable, simple to use pocket sized tester. Ranges 0/5/30/300V AC and DC at 2,000 ohms. Resistance 0-20K ohms. ONLY \$1.97 P. & P. 13p

MODEL TE-90 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200 V. D.C. 0/3/30/120/300/1,200 V. A.C. 0/3/6/60/600mA. D.C. 16K/160K/1.6/16 MEGΩ. -20 to +63 db. \$7.50. P. & P. 15p.



SKYWOOD SW-500 50K Ω/Volt. Mirror scale DC Volts 0.6/3/12/30/300/600. DC Current 200μA/60/600mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +67 db. \$7.50. P. & P. 15p.



370 WTR MULTI-METER Features A.C. current ranges. 20,000 o.p.v. 0/5/2-5/10/50/250/500 1000 V DC. 0/2-5/10/50/250/500/1000 V AC. 0/50mA/1/10/100mA/1/10 Amp DC. 0/100mA/1/10 Amp AC 0/5K/50K/500K/5MEG/50MEG. -20 + 62 db. \$15. P. & P. 25p.




FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and IGO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. \$8.97. P. & P. 15p.



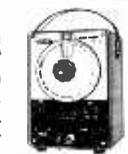AG78 AUDIO GENERATOR Portable, mains operated. Sine wave 20 to 200,000 Hz. Square wave 20 to 30,000 Hz. Output voltage 5ine 17V P/P. Square 21V P/P. Distortion less than 1%. \$17.50. P. & P. 37p.



TE-200 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. \$15. Carr. \$7.1p. Size 140 x 215 x 170 mm.



BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max +10 dB (10 K ohms). Operation 220/240V. A.C. Size 215mm x 150mm x 120mm. Price \$27.50. Carr. \$25p.




240° Wide Angle 1mA Meters MW1-6 60mm square \$3.97 MW1-8 80mm square \$4.97 P. & P. extra



TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

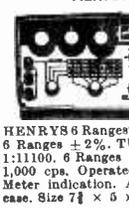A new portable bridge offering excellent range and accuracy at low cost. Ranges: R 1Ω-11.1 meg Ω 6 Ranges ± 1% L 1 μ H to 11 HENRY 6 Ranges ± 2% TURNS RATIO 1:1/1000-1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100μA Meter indication. Attractive 2 tone metal case. Size 7 1/4 x 5 x 2in. \$20. P. & P. 25p



UM.049 MULTIMETER 20,000 O.P.V. overload protection. 0/3/30/60/300/600/3000 V DC. 0/6/60/120/600/1200 V AC. 0/60mA/12/300 MA. DC. 0/60K/6M EG. -20 + 63 db \$4.60. P. & P. 15p.

Models 100TR MULTIMETER/TRANSISTOR TESTER. 100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 VDC. 0/6/30/120/600 VAC. 0/12/600μA/12/300MA/12 AMP DC. 0/10 K/1 MEG/100 MEG. -20 to +50 db. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries. Instructions and leads. \$13.50. P/P 25p.

TMK MODEL TW-50K 46 ranges, mirror scale, 50K/Volt. D.C. 5K/Volt A.C. D.C.: Volts 125, 25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 15, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50μA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +81.5 db. \$25.50. P. & P. 17 1/2p

HT100BA MULTI-METER Features A.C. current ranges. 100,000 o.p.v. Mirror Scale, Overload protection. 0/5/2-5/10/50/250/500/1000 V DC. 0/2-5/10/50/250/1000 V AC. 0/10/250mA/2-5/25/250 mA/10 Amp DC. 0/100mA/10 Amp AC 0/20K/200K/2MEG/20 MEG. -20 + 62 db. \$12.50. P. & P. 25p.


RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/100V AC. DC Current 10 μA/1/10/100 mA. Resistance 300 ohms/3/30/300K/3M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$5.97 P. & P. 20p.

TO-3 PORTABLE OSCILLOSCOPE 3in. tube. V. amp. Sensitivity 0.1V p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input Imp. 2 meg Ω 25pF X amp. sensitivity 0.9V p-p/CM. Bandwidth 1.5 cps-800K Hz. Input Imp. 2 meg Ω 20pF. Time base. 1 per second. 10 cps-300 KHz. Synchronization. Internal. external. Illuminated scale 140 x 215 x 330 mm. Weight 154 lb. 220/240V. A.C. Supplied brand new with handbook. \$27.50. Carr. 50p

HONEYWELL DIGITAL VOLTMETER VT.100 Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input Impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2in. x 2 1/2in. x 8 3/16in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE. \$49.97. Carr. 50p.

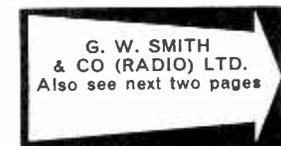G. W. SMITH & CO (RADIO) LTD. Also see next two pages



SEMI-CONDUCTOR JOINTS VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3415	2N3416	2N3417	2N3540	2N3541
2N3415	2N3416	2N3417	2N3541	

Integrated Circuits	FJH101	FJH111	FJH121	FJH991	FJH1001
FJH101	FJH111	FJH121	FJH1001	

VALVES	6X4	6X5	6X6	6X7	6X8	6X9	6X10	6X11	6X12	6X13	6X14	6X15	6X16	6X17	6X18	6X19	6X20	6X21	6X22	6X23	6X24	6X25	6X26	6X27	6X28	6X29	6X30	6X31	6X32	6X33	6X34	6X35	6X36	6X37	6X38	6X39	6X40	6X41	6X42	6X43	6X44	6X45	6X46	6X47	6X48	6X49	6X50	6X51	6X52	6X53	6X54	6X55	6X56	6X57	6X58	6X59	6X60	6X61	6X62	6X63	6X64	6X65	6X66	6X67	6X68	6X69	6X70	6X71	6X72	6X73	6X74	6X75	6X76	6X77	6X78	6X79	6X80	6X81	6X82	6X83	6X84	6X85	6X86	6X87	6X88	6X89	6X90	6X91	6X92	6X93	6X94	6X95	6X96	6X97	6X98	6X99	6X100
6X4	6X5	6X6	6X7	6X8	6X9	6X10	6X11	6X12	6X13	6X14	6X15	6X16	6X17	6X18	6X19	6X20	6X21	6X22	6X23	6X24	6X25	6X26	6X27	6X28	6X29	6X30	6X31	6X32	6X33	6X34	6X35	6X36	6X37	6X38	6X39	6X40	6X41	6X42	6X43	6X44	6X45	6X46	6X47	6X48	6X49	6X50	6X51	6X52	6X53	6X54	6X55	6X56	6X57	6X58	6X59	6X60	6X61	6X62	6X63	6X64	6X65	6X66	6X67	6X68	6X69	6X70	6X71	6X72	6X73	6X74	6X75	6X76	6X77	6X78	6X79	6X80	6X81	6X82	6X83	6X84	6X85	6X86	6X87	6X88	6X89	6X90	6X91	6X92	6X93	6X94	6X95	6X96	6X97	6X98	6X99	6X100	

See previous page

G. W. SMITH & Co. (RADIO) LTD.

See opposite page

HI-FI EQUIPMENT

SAVE UP TO
33 1/3% OR MORE
SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!

RECORD DECKS

B.S.R. Mini Mono†	£4.97	
C125†	£6.70	
MP60	£10.75	
610	£14.65	
510	£11.85	
310	£9.65	
810	£24.47	
MP60 TPD1	£17.65	
MP60 TPD2	£15.85	
610 T.P.D.1	£20.97	
510 T.P.D.1	£18.75	
210 Package*		
	£9.85	
H.T.70	£15.55	
H.T.70 Package		£22.50
THORENS		
TD125	£59.65	
TD125AB	£94.25	
TX25	£6.70	
TD150AII	£34.50	
TD150ABII	£40.25	
TX11	£3.77	

† Mono * Stereo Cartridge
All other models less Cartridge
Carriage 50p extra any model.

RECORD DECK PACKAGES

Decks supplied ready wired in plinth and cover fitted with cartridge. GARRARD

2025 T/C with Sonotone 9TAHCD	£19.95
2025 T/C with Sonotone 9TAHCD	£19.95
Garrard SP25III Goldring G800	£18.95
Garrard SP25III/Shure M75-6	£19.95
Garrard AP76/Shure M75-6	£30.95
Garrard AP76 Goldring G800	£29.95
BBS MP60 Audio Technica AT.55	£21.00
Goldring GL72 Goldring G800	£27.50
Goldring GL75 Goldring G800	£28.50
Goldring GL75 Goldring G800E	£48.65

Carriage 50p extra any model.

★ TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER, 8 1/2" ONLY 6" x 4" x 2 1/2" 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £8.87. P. & P. 12 1/2p. Stereo multiplex adaptors £4.97.

SINCLAIR EQUIPMENT

Project 60. Package offers.

2 x Z30 amplifier, stereo 60 pre-amp, PZ5 power supply. £16.75 Carr. 37 1/2p. Or with PZ6 power supply £18.85 Carr. 37 1/2p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply. £20.25 Carr. 37 1/2p.

Transformer for PZ8. £2.97 extra.

Add to any of the above £4.87 for active filter unit and £13.90 for pair of Q16 speakers. Project 60 FM Tuner £20.25 Carr. 37 1/2p. All other Sinclair products in stock.

2000 Amp £23.75 Carr. 37 1/2p. 3000 Amp £31.50 Carr. 37 1/2p. Neotec Amp £43.95 Carr. 37 1/2p. IC10/IC12 £2.50

NEW PROJECT 605 — £20.97 Carr. 37 1/2p.

LATEST CATALOGUE


Our new 8th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

SEND NOW

ONLY
37 1/2 p
P & P
10p



TELETON SAQ-206 STEREO AMPLIFIER

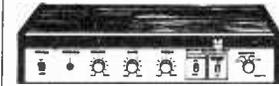

Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal, aux. tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List £29.50 OUR PRICE £18.50 Carr. 37p.

TELETON SPECIAL OFFER!



CRIST AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR OF SPEAKER SYSTEMS. Output 4 watts per channel. Excellent reception. A.C. built-in MPX. Cer/XTAL Input. Total List £50.25. OUR PRICE £23.75 Carr. 62 1/2p. Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired £36.50. Carr. £1.00.

LAFAYETTE LA. 324 STEREO AMPLIFIER

12.5 + 12.5 watt B.M.S. Mag/Cer/Tuner/Tape Inputs. Excellent performance. Compares with amplifiers up to £40.

OUR PRICE £24, Carr. 37 1/2p.

TAPE CASSETTES

Top quality in plastic library boxes.

C90 60 min 87 1/2p, 3 for £1.05

C60 90 min 80p, 3 for £1.85

C120 120 min 87 1/2p, 3 for £1.80

Cassette Head Cleaner 56p. Post Extra

TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 01/003/1/2/1/3/10/30/100/300V. R.M.S. decs. 1-2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.50. Carr. 25p.

TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.3 - 1200V. AC VOLTS 3 - 300V R.M.S. 8-0 - 900V P-P. DC CURRENT -12 - 12MA. Resistance up to 2000M ohm. Decibels -20 to +51 db Complete with leads/instructions. £17.50, P. & P. 20p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots 240). Quantities available.

HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station £2.97. P. & P. 15p.
3 Station £5.25. P. & P. 15p.
4 Station £8.62. P. & P. 17p.



EMI LOUDSPEAKERS Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7.50 each. P. & P. 37p.

Model 450. 13" x 8" with twin tweeters/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £8.50 each. P. & P. 25p.

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £1.97. P. & P. 15p.

MP7 MIXER PREAMPLIFIER 5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mics: 3 x 3mV 50K, 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. £8.97. P. & P. 20p.

HOSIDEN DH-025 STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and stereo jack plug. ONLY £2.87. P. & P. 12 1/2p.

1081 STEREO LISTENING STATION

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2.25, P. & P. 16p.

TE-16A Transistorised Signal Generator, 5 ranges 400KHz - 30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2" x 5 1/2" x 3 1/2". Complete with instructions and leads. £7.97. P. & P. 20p.

RUSSIAN C11-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 3 sec to 100 mill sec/cm. Supplied complete with all accessories and instructions £27. Carr. paid.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery

8-260 General Purpose Bench Mounting		8-260B Panel Mounting	
1 Amp	£7.00	1 Amp	£7.00
2.5 Amp	£8.05	2.5 Amp	£8.05
5 Amp	£11.75		
8 Amp	£15.90		
10 Amp	£22.50		
12 Amp	£23.60		
20 Amp	£49.00		

Please add postage AT 300V AC INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS. Special discounts for quantity

PRS-2 PHOTO ELECTRIC RELAY SYSTEM

Inexpensive warning or counting system consisting of an enciter and relay unit. Relay unit has variable sensitivity control and switch for intermittent alarm operation. Enciter unit has removable infra red filter and A.C. outlet socket to operate bells, counters, etc. 240V AC. Complete with cables and instructions. £9.97 P. & P. 25p.

RP214 REGULATED POWER SUPPLY

Solid state. Variable output 0-24V DC up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V AC. Size 185 x 85 x 105mm. £8.97. P. & P. 25p.

PS1000B REGULATED POWER SUPPLY

Solid state. Output 6.9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V AC. Size 4" x 3 1/2" x 6 1/2". £11.97. P. & P. 25p.



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kc/s-30mc/s. FET, 8 Meter, Variable BFO for 88B, Built-in Speaker, Bandspread, Sensitivity Control. 220/240V. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37 1/2p.

LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s, 550 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter. 8. Meter, Bandspread, RF Gain 15' x 9 1/2" x 8 1/2". 220/240V. A.C. or 12v. D.C. Brand new with instructions. £45. Carr. 50p.

TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2CF8-1MEHZ. Input imp. 2 meg Ω 25 P.P. Illuminated scale. zin. tube. 115 x 180 x 230mm. Weight 8lb. 220/240 V. a.c. Supplied brand new with hand-book. £22.50. Carr. 50p.

SH628 STEREO HEADSET

Outstanding value. Soft earpads, adjustable headband. 8 - 16 ohms. 20-20,000Hz. Complete with cable and stereo jack plug. £1.87. P. & P. 15p.

MCA 220 AUTOMATIC VOLTAGE STABILISER

Input 84-125 VAC. Output 120 VAC or 176-250V input output 240 VAC. 200 VA rating. £11.97. Carr. 50p.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, 1/4 in. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 72 1/2p. P. & P. 7 1/2p.

50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, 81-05 P. & P. 7 1/2p.

100 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms, 21-87 P. & P. 7 1/2p.

G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-5 MONDAY TO SATURDAY


WE ARE WELL WORTH A VISIT!

PSP

DEMONSTRATIONS ALL DAY LONG
NO PARKING PROBLEMS

The Country's Cheapest

ONLY
£39.95
Famous
Teleton

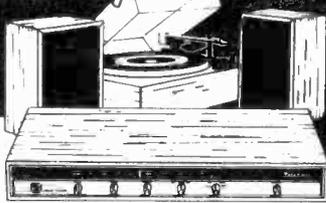

R8000 AM-FM STEREO TUNER AMPLIFIER

Supplied complete with 2 speakers. Total 12 watts RMS. Specification: MPX Beacon, AFC, Connections for Tape Recorder, Stereo Headphone Socket, etc. Mfgs. Rec. Price £63.50. **P.S.P. FANTASTIC OFFER. ONLY £39.95**

Plus GARRARD DECK 2025. Fitted in Famous 'Thorpe Grenville' Plinth & Cover with patented moulded motor board. Fitted with superb Sonotone 9TANCO cartridge. P.S.P. offer **ONLY IF YOU BUY THE ABOVE. ONLY £15.40**

SAVE
£25.00
on Fabulous

Complete Stereo System


Teleton SAQ206

STEREO AMPLIFIER

Latest release, beautifully styled in walnut case, 6+6 watts r.m.s. Switched inputs for magnetic Xtal, aux. Tape. Incorporates volume, bass, treble and slide balance control, scratch filter and loudness control. Rec. £32.50.

Suggested System.

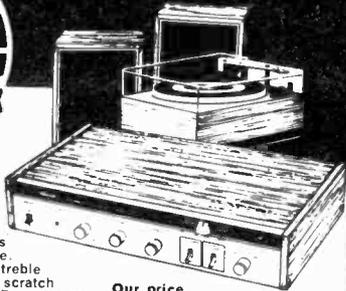SAQ 206 Amplifier, SP25 III Plinth and Cover, G800 cartridge, pair large 3-way speaker system. Also available with EMI 13 x 8 speaker system £63.95. Would normally cost £85 complete.



Our price
£19.95

Our price
£59.95

Tape Recorders	List Price	P.S.P. Price
Ferguson 3245	£36.00	£31.95
" 3247	£47.95	£41.50
" 3248	£53.75	£45.95
" 3258	£72.00	£63.25
Philips 4303	£42.00	£37.50
" 4307	£49.50	£43.50
" 4308	£60.50	£53.50

Available at special prices. Linton's, Denton's, Warfedale speakers. Goldring GL69P & 6775P decks; Leak, Delta 30 & 70 Rogers Ravensbrook, Ravensborne amplifiers, Sinclair 3,000 amp & The Fidelity U1A/UA2

Plus a wide range of stereo units.

	List price	P.S.P. Price
HMV 2452 Stereo System	£125.00	£110.00
RH92 Philips (Choice of speakers available, prices on application).		

KB Audio Stereo 2010 £103.40 **£92.50**
Ultra 6028 Group 3 stereo £59.75 **£52.50**

Also available full range of Grundig Tape Recorders at attractive discounts.

Magnetic Cartridges	List price	P.S.P. price
Goldring G800	£12.55	£6.55
Goldring G 800 H	£12.55	£6.55
Shure M55E	£12.52	£9.40
Shure M 44-7	£9.84	£7.45

Ferguson unit audio	£84.50	£74.24
Ultra 6405	£77.00	£67.25
Ferguson 3450 Stereo	£72.00	£63.50




PERSONAL SHOPPERS PLAN LTD.

The Centre
36-38 West Green Road, Tottenham,
N.15 Tel. No. 01-800 5533

All orders C.W.O. Special Securicor fast delivery £3.

PHOTOELECTRIC KIT

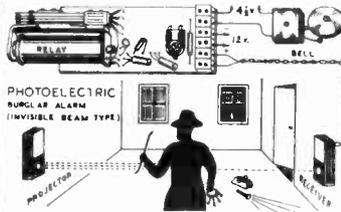CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Phototransistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Protect No. 1) which can be modified for modulated-light operation



PHOTOELECTRIC KIT £2.60

Postage and Pack. 15p (UK)

Commonwealth:
SURFACE MAIL 25p
AIR MAIL £1.40

Australia, New Zealand, S. Africa, Canada and U.S.A. Also Essential Data Circuits and Plans for Building 10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price £1.25 Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £1.85. Postage and Pack 15p (U.K.) Commonwealth: Surface Mail 20p, Air Mail £1.15.

JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter. CONTENTS: Infra-Red Sensitive Phototransistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price £1.25. Postage and Pack. 10p (U.K.). Commonwealth 20p; Airmail 50p.

JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plats, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photocell receiver for use with Junior Photoelectric Kit. Price 75p. Post. and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p; Air Mail 50p.

YORK ELECTRICS Mail Order Dept.


335 BATTERSEA PARK RD., LONDON S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects



S.D.C. FESTIVE

BONANZA

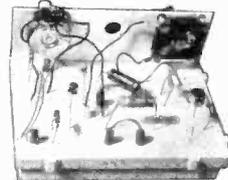

S-DeC
SPECIAL OFFER

25
OFF P

(1) YES! The ideal present for any electronics enthusiast, so do not miss this great opportunity.

(2) JUST TAKE THIS COUPON TO YOUR LOCAL STOCKIST WHO WILL SUPPLY ONE S-DeC for only **£1.19**

(3) OR in case of difficulty send coupon and cash to:—

S.D.C. ELECTRONICS (SALES) LTD., 34 ARKWRIGHT ROAD ASTMOOR INDUSTRIAL ESTATE, RUNCORN, CHESHIRE WA7 1NU

Name

Address

(4) Offer closes January 31, 1972.

Build yourself a TRANSISTOR RADIO

NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS AND AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 5" heavy duty Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

£8-50

P. P. & Ins. 30p

(Overseas P. & P. £1)



ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 5" heavy duty Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P.P. & Ins. 41p. (Overseas P. & P. £1)

ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler

Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy R.F. Transistors. 5" heavy duty speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening. 30p extra.


Total building costs **£5-98** P.P. & Ins. 41p. (Overseas P. & P. £1)



ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—8 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

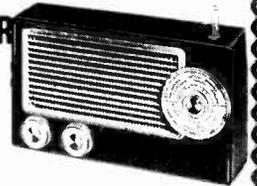
Total building costs **£3-98** P.P. & Ins. 28p. (Overseas P. & P. £1)



POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 6 1/2 x 1 1/2 x 2 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

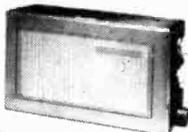Total building costs **£2-23** P.P. & Ins. 23p. (Overseas P. & P. 63p)




TRANSONA FIVE

NOW WITH 3in SPEAKER

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone 3in. moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

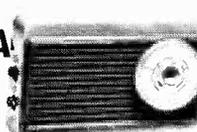Total building costs **£2-50** P.P. & Ins. 22p. (Overseas P. & P. 63p)




TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ampie power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

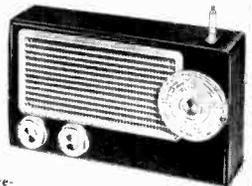Total building costs **£4-48** P.P. & Ins. 31p. (Overseas P. & P. £1)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY TO GO DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.

COMPONENTS INCLUDE:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4"x2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Test Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 4" Knobs.

Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including **£5-50** P.P. & Ins. 31p. (Overseas P. & P. £1)

FULL AFTER SALES SERVICE

• Callers side entrance Barratts Shoe Shop
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for

Name

Address

PW.38

28watts, r.m.s. 40Hz to 40kHz ±3dB



Viscount III Audio Suite complete **£49**

There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic and ceramic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

PRICES SYSTEM 1

Viscount III R101 amplifier	£22.00+90p p&p
2 x Duo Type II speakers,	£14.00+£2 p&p
Garrard SP25 Mk. III with MAG.	
cart ridge plinth and cover	£23.00+£1.50
	p&p

Total £59.00

Available complete for only **£52.00+£3.50 p&p**

SYSTEM 2

Viscount R101 amplifier	£22.00+90p p&p
2 x Duo Type III speakers	£32.00+£3 p&p
Garrard SP25 Mk. III with MAG.	
cartridge, plinth and cover	£23.00+£1.50
	p&p

Total £77.00

Available complete for **£69+£4 p&p**

SYSTEM 3

Viscount III Amplifier R100	£17.00+90p p&p
2 x Duo Type II speakers, pair	£14.00+£2 p&p
Garrard SP25 Mk. III with CER. diamond	
cartridge, plinth and cover	£21.00+£1.50
	p&p

Total £52.00

Available complete for only **£49.00+£3.50 p&p**

SPEAKERS Duo Type II

Size approx 17" x 10½" x 6½". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts. 3 ohms. Simulated Teak cabinet. **£14 pair+£2 p&p.**

Duo Type III Size approx 23½" x 11½" x 9½". Drive unit 13½" x 8½" with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. **£32 pair+£3 p&p.**

SPECIFICATION R101

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within ± 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities; headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max) R101—P.U.1 and radio—65dB. P.U.2. —58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. *Cross talk* better than -35dB on all inputs. *Overload characteristics* better than 26dB on all inputs. Size approx 13½" x 9" x 3½".

R+TV

Radio and TV Components (Acton) Ltd. 21C High Street, Acton, London W3 6NG
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.
Goods not despatched outside U.K.

SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM



The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power: 45 watts R.M.S. (Sine wave drive). **Frequency response:** -3dB points 30Hz at 18KHz. **Total distortion:** less than 2% at rated output. **Signal to noise ratio:** better than 60dB. **Speaker Impedance:** 3, 8 or 15 ohms. **Bass Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 KHz. **Inputs:** 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

SPEAKERS! Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

COMPLETE SYSTEM £50 Plus £6 P. & P.

Sound 50 amp and 2 speakers

or available separately.

Amplifier £28.50 plus £1.50 P. & P.
Speakers £12.50 each plus £2.25 P. & P.

RELIANT mk. IV



Provides a high standard of sound reproduction, with full mixing facilities. It's versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- ★ Five Electronically Mixed Inputs
- ★ Three Individual Mixing Controls
- ★ Separate base and treble controls common to all five inputs
- ★ Mixer employing F.E.T. (Field Effect Transistor)
- ★ Solid State Circuitry ★ Attractive Styling

£9.50 plus P. & P. 60p.

INPUTS:—1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.). All 250mV sensitivity.

CONTROLS:—3 Volume controls. Bass control range: 13db @ 60 Hz. Treble control range ±12db @ 15KHz. Separate ON/OFF Switch. Neon Indicator.


POWER OUTPUT:—12 Watts R.M.S. into 3 to 4 ohms speaker

SIGNAL/NOISE:—Better than -60db on inputs 3, 4 and 5 & -50db on 1 & 2

SUPPLY:—220 - 250 AC Mains. **SIZE:**—12 1/2" x 6" x 3 1/2"

THE ELEGANT SEVEN Mk. III

(350m W Output)

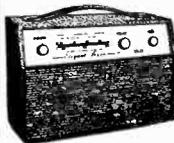


7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

MAINS POWER PACK KIT: 75p extra.

Price **£5.25** plus 50p. P. & P.

Circuit 13p **FREE WITH PARTS.**

THE DORSET (600m W Output)

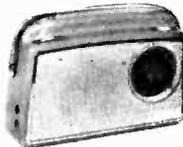


7-transistor fully tunable M.W.—L.W. superhet portable. Set of parts. The latest modulated and pre-alignment techniques make this simple to build. Sizes: 12 x 8 x 3in.

Price **£5.25** plus 50p P. & P.

Circuit 13p **FREE WITH PARTS**

CONTINENTAL 4 TRACK, 3 SPEED TAPE DECK

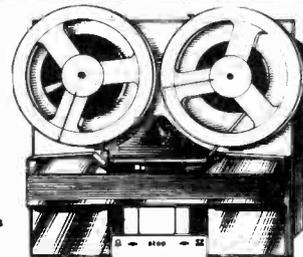

with high impedance heads

R.C. 74 tape deck. Three speeds—7 1/2, 3 1/2 and 1 1/2 ips.

4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7". The R.C. 74 is driven by a powerful 200/250V 50-cycle A.C. motor. A heavy, accurately balanced, flywheel brings wow and flutter levels down to approx. 0.3% total at 3 1/2 and 7 1/2 ips. Fast rewind in both directions.


Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12 1/2" x 11 1/2" x 6 inches. Every single deck fully tested before dispatch. Spools not supplied.

Price complete **£15.00.** Plus 75p P. & P.

TOURIST CAR RADIO

MARK 3

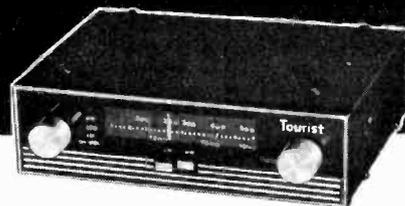

ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4 1/2in deep.

SET OF PARTS

£6.30

plus P. & P. 50p.

Circuit diagram 13p. Free with parts Speaker, baffle and fixing kit £1.25 extra plus 25p. p. & p. Postage free when ordered with parts.

See previous page for address



NEW - TO U.K. MARKET PARTRIDGE EXPORT EQUIPMENT

Size: 6" x 2 1/4" x 4 3/4"
Weight: 2lb



Finish: Gold stove enamel with fascia off-white on maroon.

AND
SPECIAL BARGAIN OFFERS!

Protected by World Patents
and Trade Marks

7' 6" (2.28m) long. Wt. 1 1/2 lb. The new improved "JOYSTICK" V.F.A.

In matching gold stove enamel, black and red finish.

The "JOYMATCH" 111 A.T.U. for RECEIVING ONLY tunes the "JOYSTICK" V.F.A. and many other antennae from 500 kHz through 30 MHz plus.

The new "JOYSTICK" V.F.A. is extremely lightweight, exceptionally strong, rigid, tough and weather proofed when assembled by screwing three sections together in seconds.

The new "JOYSTICK" V.F.A. OUTPERFORMS many beam antennae in practice BECAUSE of its low reflected power factor and absence of harmonics.

On RECEPTION—High Selectivity & Sensitivity on both Amateur & Broadcast Bands.

GENUINE BARGAINS — MAIL ORDER ONLY — WHILE STOCKS LAST!

1. Superb A.T.U. in kit form with step by step assembly and operating instructions £4-50; or £5-50 assembled. Tunes Receiver (communications or solid state) 1.2 mHz to 32 mHz. On Transmit Handles 300w PEP (PA input) 160 thru 10m—with "JOYSTICK" V.F.A.
2. Lo-z "JOYMATCH" A.T.U. (the world famous one!) £9-50.
3. New "JOYSTICK" V.F.A. in white stove enamel plus FREE external mounting insulators £8-00. Add 40p p/p or 45p if two items ordered together.

Details 3p stamp (not S.A.E.)

Phone: (Thanet) 0843 62535



VALVES		25 6JB		20 7C5		11-13 12SR7		40 37		40 DAF91		30 EBL31		21-50 EL41		60 N78		21-50 PL504		80 U404		60	
1A7GT	45	6B6	30	6J7M	45	7C6	75	14H7	60	42	50 DAF96	45	EC90	33	EL42	65	N108	21-50	PL508	90	U801	21-18	
1CP31	20-00	6B7A	45	6K6GT	60	7D5	30	19A5	50	50B5	50	DC90	21-35	ECC81	35	EL84	25	OA2	38	PL509	21-10	UABC80	40
1D5	50	6BR7	90	6K7M	60	7R7	75	20F2	70	50C5	50	DF33	55	ECC82	30	EL95	35	OC3	38	PL802	85	UAF42	55
1H5	50	6BR8	70	6K7G	35	7X4	22-25	20P1	11-10	50D6GT	55	DF91	30	ECC84	30	EM34	21-00	PC86	60	PX4	22-50	UBC41	50
1NSGT	55	6BR8	21-30	6K7GT	35	9BW6	60	20P5	21-20	7L	45	DF92	20	ECC83	40	EM80	45	PC88	80	PY33	85	UBF90	40
1R5	40	6BW6	85	6K8M	60	10C2	85	25A6	35	80	55	DH3-91	20-00	ECH21	63	EM84	35	PC84	40	PY82	35	UCC84	43
1R4	30	6BW7	80	6K8G	40	10F1	75	25L6GT	50	85A2	50	DH77	35	ECH35	21-00	EY51	40	PC89	50	PY88	38	UCC85	40
1R5	30	6C4	33	6K8GT	50	10F3	90	25Y5	65	150B2	80	DK32	45	ECH42	75	EY86	40	PCU89	55	PY500	21-00	UCP80	55
1T4	30	6C5G	35	6K25	75	10F8	60	25Z4	30	150C4	60	DK31	40	ECH81	30	EZ35	40	PCF80	30	PY800	40	UCH42	70
3A4	40	6C6	25	6L6G	50	10F18	50	25Z8GT	55	801	80	DK92	55	ECH83	45	EZ40	50	PCF82	35	PY801	50	UCB81	40
3Q4	50	6CD4G	21-25	6L18	45	10LD11	85	25Z6	65	807	50	DK96	50	ECL80	45	EZ41	50	PCF84	60	R2	75	UCL82	35
3Q5	50	6CH6	60	6Q7G	40	10P13	60	30C1	35	8131'NA	23-75	DL66	21-25	ECL82	35	EZ80	20	PCF86	60	R19	50	ULC83	60
3B4	35	6C'W4	65	6Q7GT	43	11E3	24-00	30C15	80	886A	75	DL92	35	ECL83	70	EZ81	29	PCF801	50	S130	21-75	UF41	60
3V4	48	6D6	35	68A7M	40	12A76	30	30C17	90	954	80	DL93	40	ECL86	40	G'Y501	30	PCF802	50	SP4	50	UF89	40
5R4GY	75	6E5	60	68C7M	75	12A77	35	30C14	80	1925	55	DL84	48	ECL800	40	GZ30	40	PCF805	60	SP41	60	UL41	65
5U4G	35	6F1	70	68G7M	40	12A76	35	30F5	65	402'AR	25-50	DL85	50	GZ32	48	PCF86	45	PCF806	70	SP81	75	UL84	40
5V4G	45	6F5G	90	68H7M	40	12A77	30	30FL1	75	5763	70	DL96	45	EF9	75	GZ34	60	PCF808	85	STV280/80	UM80	30	
5Y3GT	40	6F6G	35	68J7M	30	12A77	30	30FL2	21-20	7193	30	DM70	45	EF37A	21-20	HN309	21-60	PCL82	35	SU25	21-00	UU6	21-05
5Z4G	40	6F8G	50	68K7GT	40	12B46	40	30FL14	35	7475	50	DY86	33	EF39	50	KT36	21-00	PCL83	65	SU25	21-00	UU7	21-05
6J30L2	80	6F11	40	68L7GT	35	12C86	40	30L15	85	A61	48	DY87	33	EF41	65	KT61	21-25	PCL84	45	SU2150	75	UU8	21-05
6A7	75	6F15	45	68N7GT	35	12C8GT	35	30L17	50	ATP4	45	EY88C	65	EF50	25	KT66	22-05	PCL85	40	T41	21-00	UU9	21-05
6A8G	40	6F14	70	68Q7GT	40	12E11	21-30	30P4	41-12	ATP5	60	EAS0	20	EF80	60	KT81	21-75	PCL86	45	TDD4	60	UU21	50
6AK5	35	6F23	65	6U4GT	65	12J5GT	30	30P12	80	ATP7	60	EABC80	35	EF85	35	KT81(7C5)	PD500	21-30	TH41	21-75	UY41	48	
6AM6	35	6F25	21-00	6V5M	30	12K7GT	40	30P19	85	AU2	24-00	EAF42	55	EF86	30	21-13	HN304	21-00	U10	75	UY85	40	
6AM6	35	6F28	65	6V8G	30	12K8GT	50	30PL13	93	AZ1	55	EBC33	50	EF91	33	KTW61	21-00	PEN45	75	U19	23-00	VP4B	21-85
6AQ5	38	6F32	25	6V8GT	40	12Q7GT	40	30PL14	90	AZ31	55	EBC34	55	EF92	35	KTZ41	50	PEN46	40	U35	80	VR105/30	38
6A87G	55	6H6	25	6X4	35	12S4GT	50	38A5	75	CB'L31	21-00	EBC30	30	EF98	75	ML4	88	PL36	55	U26	80	VR160/30	35
6A76	35	6H6	23	6X5G	40	12S17	35	38L6	50	OCH33	75	EBF80	40	EF183	30	ML4	88	PL81	50	U78	35	VU111	75
6A76	35	6H6	23	6X5G	40	12S17	35	38W4	35	CL33	21-30	EBF83	40	EF184	35	ML6	40	PL82	45	U191	75	VU120	21-00
6A76	35	6H6	23	6X5GT	40	12S17	35	35Z3	70	CY30	68	EBF89	30	EL32	50	MP4	50	PL83	45	U261	80	VU508	23-00
6B4G	21-00	6J5G	20	7B6	70	12S7	40	35Z4GT	60	CY31	43	EBL1	21-00	EL33	21-25	MT'14	75	PL84	40	U301	63	W81M	63
6B8G	25	6J5GT	30	7B7	70	12S87	50	35Z5	50	DAC32	50	EBL21	60	EL34	50	MX40	63	PL500	80	U403	60	T63	50

Transistors		2N2218		2N2444		AD149		50 BC169C		15 BFT82		25 NKT223		33 OAZ201		50 OC35		50 OC81D		20 Z8170		10	
1N914	07-2N697	15	2N2646	45	AC126	25	AF127	25	BFY50	25	BFY50	25	BFY50	25	BFY50	25	BFY50	25	BFY50	25	BFY50	25	BFY50
1N118	25 2N706	10	2N2904	20	AC127	25	AF116	25	BFY100	15	MJE2955	10	OA71	10	OAZ224	45	OC58	60	OC170	25	ZTX300	12	
18202	23 2N1132	25	2N2928	10	AC128	20	BC107	10	ZY88	15		11-37	OA81	08	OAZ241	22	OC69	65	OC171	30	ZTX304	25	
2G302	22 2N1305	22	2N3055	75	AC129	20	BC108	10	CRN1-40	47	MJE3055	87	OA85	12	OAZ242	23	OC71	12	OC200	40	ZTX500	16	
2G371	22 2N1347	75	2N3702	10	AD139	60	BC109	10	DDT03	15	NKT212	27	OA91	07	OAZ245	23	OC72	20	OCP71	97	ZTX503	17	
2N404	20 2N2160	60	2N3819	35	AD149	50																	

TRANSISTOR POSTAGE 1p EACH, OVER 10 POST FREE

Express Postage & Insurance 5p one valve plus 1p each additional valve. ORDERS over £5 Post free.

6,000 types in stock send for lists, 5p.

R.S.T.

"Renowned for Service"



BLACKWOOD HALL, WELLFIELD RD., STREATHAM, SW16 2BS

Tel. 01-769-0199/1649. Open to callers Mon-Sat 9 a.m.—5 p.m. Closed Saturday 1.00—2.30 p.m.

look! electronics really mastered

... practical
... visual
... exciting!

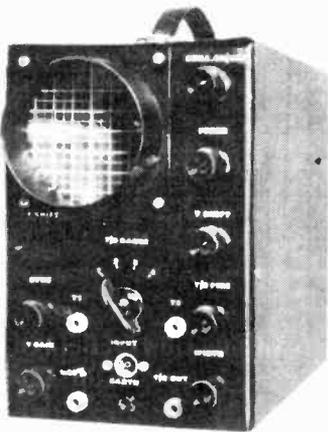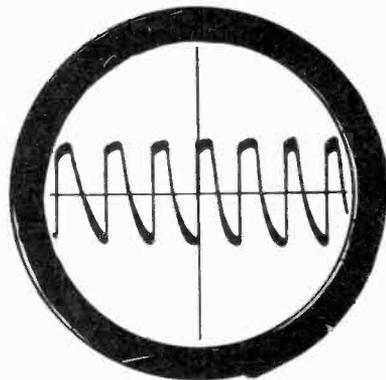no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

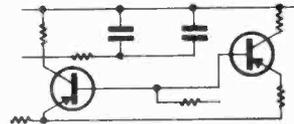2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME

BLOCK CAPS

ADDRESS

PLEASE P.W.6

special free gift also to all our students

ADCOLA Soldering Instruments add to your efficiency

THE NEW 'INVADER'

ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit*. Standard temp. 360°C at 23 watts. Special temps. from 250°C—410°C.

*Additional Stock Bits (illustrated) available

COPPER

B 38 $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 24 $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

B 12 $\frac{3}{16}$ " — 4.75 mm EYELET BIT

B 58 $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

LONG LIFE

B 42 LL $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

PRICE
£1.85



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.



* Write for price list and catalogue

ADCOLA PRODUCTS LTD.,
(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

WICKS FOR BARGAINS

E.A. STEREO AMPLIFIER:

5 watts per channel; In attractive afrormosia veneered sleeve. Controls: On-off volume: Bass: Treble: Balance: Selector: Headphone Jack. Ceramic or Magnetic PU. Radio and Tape Inputs: Tape output and speaker output. Fully guaranteed 12 months parts. 6 months free service. Size 14½"W x 9½"D x 45"H approx. £16-50 inc. post.

• Guaranteed all brand new best quality goods. No rubbish.

• Mail order only.

• All enquiries SAE please.

3 WAY SPEAKER SYSTEM:

8" twin cone Bass speaker and 3" tweeter, fitted in extremely elegant teak veneered cabinet. Size: 18½"H x 11½"W x 10"D. 8 ohms handle 10 watts. £7-50 inc. Carr.

GARRARD OFFERS

Garrard SP25 Mk III (Rec. Price (£15-85) Our Price £11-25. Carr. & Ins. 50p.

Garrard SP25 Mk III ready wired in beautiful teak plinth with tinted perspex cover. (Fitted with 5-pin DIN plug or phono plugs—state choice) (Rec. Price £23-19). Our Price £16. Carr. & Ins. 75p.

Or with choice of fitted cartridges.

SP25 Mk III/Sonotone 9TAHC (Rec. Price £27-29) Our Price £18. Carr. & Ins. 75p.

SP25 Mk III/Shure M3DM (Rec. Price £31-02) Our Price £20. Carr. & Ins. 75p.

SP25 Mk III/Goldring G800 (Rec. Price £36-19) Our Price £21. Carr. & Ins. 75p.

SP25 Mk III/Shure M55E (Rec. Price £36-16) Our Price £21. Carr. & Ins. 75p.

Note! Garrard SL65B (Automatic Changer version of SP25 Mk III) alternatively supplied—please add £3 to above prices.

Garrard AP76 (Rec. Price £27-85)

Our Price £18-85. Carr. & Ins. 50p.

Garrard AP76 ready wired in beautiful teak plinth with perspex cover (fitted with 5 pin DIN or Phono plugs).

Please state choice. (Rec. Price £39-85).

Our Price £24-94 Carr. & Ins. 75p.

OR WITH CHOICE OF FITTED CARTRIDGES.

Garrard AP76/Shure M3D (Rec. Price £47-26) Our Price £28-94.

Carr. & Ins. 75p. Garrard AP76/Shure

M55E (Rec. Price £52-82). Our Price

£31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52-82) Our Price £31-35. Carr. & Ins. 75p.

Special Offer!
Grundig GDM312 Dynamic Microphones. List £7.35 OUR PRICE £3. P & P 30p

Hi-Fi Stereo Headphones
(Value £5-00)
Only £2-25 inc. post.

Speaker Cloth
Best quality. Width 36". Under half price at 55p per yd. Black with gold fleck, will blend with any room setting. End of stock line, yds and yds must go.

Plugs, Sockets and Leads.
Phono plugs: 3p each 3p per dozen.
2 pin Din sprk. plugs 10p each.
3 pin Din plugs. 15p each
5 pin Din plugs. 13p each.
5 pin Din sockets (chassis) 7p each.
Stereo Jack Sockets c/cct. 13p each.
Phono sockets (chassis) 2 way 3p; 3 way 4p; 4 way 5p.
6ft. stereo lead 5 pin Din to open end. 45p
6ft. stereo lead 2 phono to open end. 37p
12ft. sprk. lead 2 pin Din to open end. 49p.
Please add P & P 5p.

100 Mixed Resistors
½ watt 10% all best quality (no ex government) 40p.

Pots
100K x 100K lns & Logs. stereo. 35p inc. post.
100K DP switch stereo. log. 45p inc. post.
50K single Balance. 15p inc. post.

4 B.A. brass nuts
50 for 25p inc. post.

Speaker cabinets
Attractively veneered in afrormosia, black front. Size approx. 7½"W x 9½"D x 4½"H. Ready cut to take 8" x 5" speaker. £1-99. P. & P. 12p.

D. T. WICKS & CO. 49 North Station Rd, Colchester, Essex.

Tel: (0206) 78807

**BROAD NEW
GUARANTEED**

SEMICONDUCTORS & COMPONENTS
SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA), IN U.K.

**RETURN OF POST
SERVICE**

TRANSISTORS

2G301 20p	2N3404 32p	40310 45p	BC212L 13p	B8X28 32p	NKT281 27p
2G302 20p	2N3405 45p	40311 35p	BCY30 27p	B8X60 32p	NKT401 27p
2G303 20p	2N3414 32p	40312 47p	BCY31 30p	B8X72 32p	NKT402 27p
2G306 42p	2N3415 27p	40314 37p	BCY32 50p	B8X76 27p	NKT403 75p
2G308 30p	2N3416 37p	40320 47p	BCY33 25p	B8X77 27p	NKT404 62p
2G309 30p	2N3417 37p	40323 32p	BCY34 30p	B8X78 27p	NKT405 75p
2G371 15p	2N3570 1.25	40324 47p	BCY38 40p	B8Y10 27p	NKT406 62p
2G374 20p	2N3572 97p	40326 37p	BCY39 60p	B8Y11 27p	NKT451 62p
2G381 20p	2N3605 40p	40329 30p	BCY40 50p	B8Y24 15p	NKT452 47p
2N401 22p	2N3606 27p	40334 27p	BCY42 15p	B8Y25 15p	NKT603 32p
2N096 20p	2N3607 22p	40347 57p	BCY43 15p	B8Y26 17p	NKT613 32p
2N697 17p	2N3702 11p	40348 52p	BCY44 32p	B8Y27 17p	NKT674 F 30p
2N698 25p	2N3703 10p	40360 42p	BCY58 22p	B8Y28 17p	NKT677 F 20p
2N705 12p	2N3704 11p	40361 47p	BCY59 22p	B8Y29 17p	NKT713 20p
2N706 12p	2N3705 10p	40362 57p	BCY60 27p	B8Y32 25p	NKT715 20p
2N708 15p	2N3706 10p	40370 32p	BCY70 20p	B8Y36 25p	NKT781 30p
2N709 62p	2N3707 11p	40406 57p	BCY71 25p	B8Y37 25p	NKT1049 30p
2N718 25p	2N3708 07p	40407 40p	BCY72 17p	B8Y38 22p	NKT10439
2N726 30p	2N3709 09p	40408 52p	BCZ10 27p	B8Y39 22p	
2N727 30p	2N3710 09p	40410 52p	BCZ11 42p	B8Y40 22p	NKT10519
2N914 17p	2N3711 12p	40467A 57p	BD116 1.12	B8Y51 32p	
2N915 17p	2N3715 1.25	40474 57p	BD121 65p	B8Y52 32p	NKT20329
2N918 30p	2N3716 1.30	40600 57p	BD123 22p	B8Y53 27p	
2N929 22p	2N3791 22.06	AC 107 30p	BD124 60p	B8Y54 40p	NKT20339
2N930 27p	2N3819 35p	AC126 20p	BD131 75p	B8Y56 90p	
2N1090 22p	2N3823 97p	AC127 25p	BD132 85p	B8Y78 47p	NKT80111
2N1091 22p	2N3854 27p	AC128 20p	BDY10 11.37	B8Y79 45p	
2N1131 25p	2N3854A 27p	AC154 22p	BDY11 11.02	B8Y82 52p	NKT80112
2N1132 25p	2N3859 27p	ACY20 25p	BDY51 1.25	C425 25p	
2N1302 17p	2N3855A 27p	AC167 62p	BDY18 11.75	BSY90 15p	NKT80113
2N1303 17p	2N3856 50p	AC188 27p	BDY19 11.97	BSY95A 18p	
2N1304 22p	2N3866A 35p	ACY17 27p	BDY20 11.12	BSW70 27p	NKT80211
2N1305 22p	2N3858 25p	ACY18 25p	BDY38 97p	C111 75p	
2N1306 25p	2N3858A 30p	ACY19 25p	BDY60 1.25	C424 27p	NKT80212
2N1307 25p	2N3859 27p	ACY20 25p	BF051 21.25	C425 25p	
2N1308 30p	2N3859A 32p	ACY21 25p	BDY62 11.00	C426 40p	NKT80213
2N1309 30p	2N3860 30p	ACY22 20p	BF115 25p	C428 37p	
2N1507 17p	2N3866 1.50	ACY28 20p	BF117 47p	C744 30p	NKT80214
2N1613 25p	2N3877 40p	ACY40 20p	BF163 37p	D16P1 37p	
2N1631 35p	2N3877A 40p	ACY41 40p	BF167 18p	D16P2 40p	NKT80215
2N1632 30p	2N3900 37p	AD140 40p	BF173 15p	D16P3 37p	
2N1638 27p	2N3900A 37p	AD140 52p	BF183 42p	D16P 30p	NKT80216
2N1639 27p	2N3901 37p	AD149 57p	BF178 30p	GET102 30p	
2N1671B 11.00	2N3903 85p	AD150 62p	BF179 30p	GET113 20p	OC20 75p
2N1711 25p	2N3904 35p	AD161 37p	BF180 85p	GET114 20p	OC22 60p
2N1889 32p	2N3905 37p	AD162 37p	BF181 35p	GET118 20p	OC23 60p
2N1893 37p	2N3906 37p	AF105 42p	BF184 25p	GET119 20p	OC24 60p
2N1917 32p	2N3908 17p	AF124 25p	BF185 42p	GET120 52p	OC25 25p
2N1948 37p	2N4059 10p	AF115 25p	BF194 17p	GET173 18p	OC26 27p
2N2160 57p	2N4060 12p	AF116 25p	BF195 15p	GET180 30p	OC28 62p
2N2193 40p	2N4061 18p	AF117 25p	BF196 15p	GET187 20p	OC29 62p
2N2193A 42p	2N4062 12p	AF118 62p	BF197 42p	GET189 22p	OC35 50p
2N2194 30p	2N4244 47p	AF119 20p	BF198 42p	GET189 22p	OC36 62p
2N2217 27p	2N4286 17p	AF125 20p	BF206 52p	GET196 22p	OC41 20p
2N2218 25p	2N4286 17p	AF125 20p	BF224 25p	GET197 22p	OC42 25p
2N2219 25p	2N4287 17p	AF126 20p	BF225 10p	GET198 22p	OC44 20p
2N2220 25p	2N4288 17p	AF127 17p	BF237 22p	MJ400 11.07	OC45 12p
2N2221 25p	2N4289 17p	AF129 37p	BF238 22p	MJ420 11.12	OC46 15p
2N2222 30p	2N4290 17p	AF178 42p	BF244 22p	MJ421 11.12	OC70 15p
2N2279 47p	2N4291 17p	AF179 32p	BF245 47p	MJ430 11.25	OC71 15p
2N2280 25p	2N4292 12p	AF180 52p	BF246 47p	MJ440 98p	OC72 12p
2N2368 17p	2N4303 47p	AF181 42p	BFX13 22p	MJ480 97p	OC74 32p
2N2369 17p	2N6027 52p	AF239 42p	BFX29 30p	MJ481 11.25	OC75 22p
2N2369A 17p	2N6028 57p	AF279 42p	BFX30 30p	MJ490 11.00	OC76 22p
2N2410 42p	2N6029 47p	AF280 62p	BFX42 37p	MJ491 11.37	OC77 30p
2N2482 27p	2N6030 47p	AF214 25p	BFX43 37p	MJ492 11.37	OC78 30p
2N2484 32p	2N6172 12p	ASV26 25p	BFX68 67p	MJE340 22p	OC81D 22p
2N2539 22p	2N6174 52p	ASV27 37p	BFX84 25p	MJE520 60p	OC83 25p
2N2540 22p	2N6175 52p	ASV28 27p	BFX85 32p	MJE521 73p	OC84 25p
2N2613 35p	2N6176 45p	ASV29 27p	BFX86 25p	MPP102 42p	OC139 32p
2N2614 35p	2N6232A 30p	ASV36 25p	BFX87 27p	MPP103 37p	OC140 32p
2N2616 52p	2N6246 42p	ASV38 25p	BFX88 25p	MPP104 37p	OC71 30p
2N2686 32p	2N6246 42p	ASV51 32p	BFX89 62p	MPP105 37p	OC171 30p
2N2711 25p	2N6249 37p	ASV54 25p	BFY93A 70p	MPS3638 32p	OC200 40p
2N2712 25p	2N6265 22.75	ASV86 32p	BFY10 32p	MKT0013 47p	OC201 60p
2N2713 27p	2N6266 22.75	AU103 11.25	BFY11 42p	NKT124 42p	OC202 75p
2N2714 30p	2N6267 22.02	AS221 42p	BFY17 22p	NKT125 27p	OC203 42p
2N2865 62p	2N6346 37p	BC147 10p	BFY18 32p	NKT126 27p	OC204 42p
2N2904 30p	2N6306 40p	BC108 10p	BFY19 32p	NKT128 27p	OC205 80p
2N2904A 32p	2N6307 37p	BC109 10p	BFY20 1.60	NKT135 27p	OC207 75p
2N2905 37p	2N6308 37p	BC113 15p	BFY21 42p	NKT137 32p	OCPT1 42p
2N2905A 40p	2N6309 62p	BC115 15p	BFY24 45p	NKT210 30p	ORP12 50p
2N2906 25p	2N6310 42p	BC116A 15p	BFY25 25p	NKT211 30p	ORP61 62p
2N2906A 27p	2N6314 27p	BC118 10p	BFY26 20p	NKT212 30p	ORP64 22p
2N2907 30p	2N6355 27p	BC121 20p	BFY29 50p	NKT213 30p	T183A 22p
2N2923 15p	2N6356 32p	BC122 30p	BFY30 50p	NKT214 22p	T1843 27p
2N2924 15p	2N6365 47p	BC125 20p	BFY41 50p	NKT215 22p	T1844 10p
2N2925 15p	2N6366 32p	BC126 20p	BFY43 62p	NKT216 27p	T1845 10p
2N2926 15p	2N6367 37p	BC140 37p	BFY50 22p	NKT217 42p	T1846 11p
Green 14p	2N6377 27p	BC147 20p	BFY51 20p	NKT219 25p	T1847 11p
Yellow 12p	2R005 75p	BC148 10p	BFY52 23p	NKT223 27p	T1848 12p
Orange 12p	2R020 25.00	BC149 12p	BFY53 17p	NKT224 25p	T1849 12p
2N3011 30p	2R102 50p	BC152 17p	BFY56A 57p	NKT225 22p	T1850 17p
2N3014 32p	2R103 25p	BC157 20p	BFY75 80p	NKT229 80p	T1851 12p
2N3053 18p	2R104 25p	BC158 11p	BFY76 42p	NKT237 35p	T1852 12p
2N3054 18p	2R105 32p	BC159 12p	BFY77 12p	NKT238 35p	T1853 22p
2N3055 62p	2R202 35p	BC160 62p	BFY90 67p	NKT240 27p	T1860 22p
2N3133 30p	2R203 27p	BC167 11p	BFW68 27p	NKT241 27p	T1861 25p
2N3134 30p	3N83 40p	BC168B 10p	BFW59 25p	NKT242 20p	T1862 27p
2N3135 25p	3N128 70p	BC169C 11p	BFW60 25p	NKT243 62p	T1P29A 60p
2N3136 25p	3N140 77p	BC198B 11p	BFX25 1.85	NKT244 17p	T1P30A 60p
2N3391 25p	4022 72p	BC199 12p	BFX29 1.80	NKT245 20p	T1P31A 60p
2N3391A 20p	3N142 55p	BC170 12p	BPY10 11.45	NKT261 20p	T1P32A 75p
2N3391A 30p	3N143 67p	BC171 15p	BPY39 37p	NKT262 30p	TIP33A
2N3392 17p	3N152 87p	BC172 15p	B8X19 17p	NKT264 20p	11.02p
2N3393 15p	R.C.A. 52p	BC176 22p	B8X20 17p	NKT271 30p	TIP34A 22.05
2N3394 15p	40680 55p	BC182 10p	B8X21 37p	NKT272 30p	TIP35A 22.90
2N3402 32p	4022 72p	BC198 10p	NKT273 45p	NKT274 30p	TIP36A 22.90
2N3403 22p	40309 32p	BC184 11p	B8X27 47p	NKT275 30p	

TTL LOGIC I.C. NEW PRICES

1-11 12-24		1-11 12-24		1-11 12-24		
SN7400	\$p	\$p	SN7433	\$p	\$p	
SN7401	0.60 18	0.58 18	SN7437	0.80 75	SN7472	0.82 80
SN7402	0.20 18	0.18 18	SN7438	0.64 80	SN7473	0.48 0.41
SN7403	0.20 18	0.18 18	SN7440	0.23 0.21	SN7474	0.48 0.41
SN7405	0.20 18	0.18 18	SN7441A	0.87 0.83	SN7475	0.45 0.44
SN7406	0.80 75	0.78 75	SN7442	0.86 0.81	SN7480	0.70 0.65
SN7407	0.80 75	0.78 75	SN7443	2.86 2.70	SN7481	1.40 1.38
SN7408	0.20 18	0.18 18	SN7444	2.88 2.70	SN7482	0.87 0.82
SN7409	0.20 18	0.18 18	SN7445	3.60 3.40	SN7483	0.87 0.82
SN7410	0.20 18	0.18 18	SN7446	1.00 0.95	SN7484	2.00 1.85
SN7411	0.22 0.21	0.21 0.20	SN7447	1.00 0.95	SN7485	8.00 3.40
SN7412	0.48 0.46	0.46 0.44	SN7448	1.00 0.95	SN7486	0.88 0.80
SN7413	0.40 0.38	0.38 0.36	SN7449	1.00 0.95	SN7487	0.87 0.84
SN7420	0.20 0.18	0.18 0.17	SN7450	0.20 0.18	SN7491A	1.21 1.10
SN7423	0.48 0.45	0.45 0.43	SN7451	0.20 0.18	SN7492	0.87 0.84
SN7427	0.48 0.45	0.45 0.43	SN7453	0.20 0.18	SN7493	0.87 0.84
SN7428	0.80 0.75	0.75 0.74	SN7454	0.20 0.18	SN7494	0.87 0.84
SN7430	0.22 0.15	0.15 0.14	SN7460	0.20 0.18	SN7495	0.87 0.84
SN7432	0.48 0.42	0.42 0.40	SN			


BUDGET HIGH-FIDELITY STEREO SYSTEMS



ONLY
£40-95
carr. £1-75

PREMIER STEREO SYSTEM "ONE" Consists of the new Premier 800 p.p.t. transistor stereo amplifier, Garrard 4025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loud-speaker systems. Absolutely complete and supplied ready to plug in and play. 800 amplifier has an output of 5 watts per channel with inputs for ceramic and magnetic pick-up, tape and tuner also tape output socket and headphone socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off, Mono/Stereo switch, Stereo Headphone socket, Black leatherette cabinet with aluminium front panel. Size: 12 1/2" x 6 1/2" x 2 1/2". (Amplifier available separately if required £18-25. Carr. 40p).

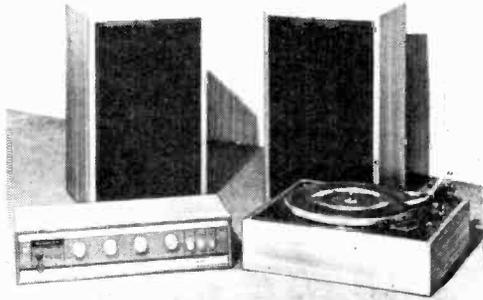PREMIER STEREO SYSTEM "TWO", as above but with Garrard SP25 MK III and magnetic cartridge. **ONLY** £48. Carr. £1-75.



ONLY
£57-75
carr. £1-75

PREMIER STEREO SYSTEM "THREE" This consists of KLINGER KC903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pick-up, tuner, tape in and out, Stereo earphone socket, Garrard SP25 Mk. III in teak finish plinth with cover and fitted Sonotone 9TAHCD diamond stereo cartridge. A pair of HMF Speakers size 16 1/2" x 10 1/2" x 9" fitted EMI units complete the matching system. **ONLY** £57-75. Carr. £1-75.

FREE

STEREO HEADPHONES

and all leads and plugs supplied with all systems.

PREMIER HI-FI OFFERS

- Philips 580 Stereo Amplifier (List £29-00) **£21-00**
- Rogers Ravensbrook II Stereo Amplifier in teak case (List £52-50) **£39-50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49-00**
- Metrosound ST20E Stereo Amplifier in teak case (List £39-50) **£28-50**
- Goldring GL75 less cartridge (List £41-61) **£29-00**
- Garrard SP25 III with Goldring G800 cartridge (List £28-35) **£15-50**
- Garrard AP76 less cartridge **£19-50**

Garrard 3500 with Sonotone 9TA stereo cartridge (List £15-50) **£9-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£9-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£14-00**

Carriage and Insurance 50p extra any item.

SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED GOLDRING 800 MAGNETIC STEREO CARTRIDGE as available. COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER. Total list price over £34.

PREMIER PRICE
£18-90

P. & P. 50p.



HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with fit lead and stereo jack plug. **£2-47** P. & P.


STEREO STETHOSCOPE SET Low imp. £1-25 P. & P. 10p
MONO STETHOSCOPE SET Low imp. 52p P. & P. 10p



E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2 1/2in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new. **£3-47** P. & P. 40p

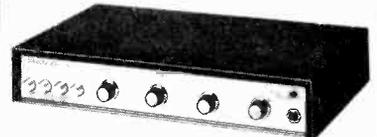NEW LOW COST PREMIER 800 STEREO AMPLIFIER



A truly high quality stereo amplifier—compare the specification, compare the price. Output: 5 watts per channel. Frequency response: 30-20,000 Hz = 2 db. Distortion: 1% Output Impedance 8 ohms nom. Inputs equalised to R.I.A.A. Magnetic 4mV. Ceramic 100mV. Tuner 100mV. Tape 100mV. Tape out 150mV. Din sockets for inputs and outputs. Stereo headphone socket. Attractive slim line design black leatherette cabinet with aluminium front panel. Size 12 1/2" x 6 1/2" x 2 1/2".

ONLY £16-25 Carr. 40p.



WELLER "EXPERT" SOLDER GUN. Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat. 100/140 watt. 240 volt A.C. **£4-25** P & P 30p

"Marksman" Soldering Iron. Lightweight 1/2" pencil bit. Ideal for regular bench use and around the home. 25 watt. 240 volt A.C. £1-50 P & P 15p



TAPE CASSETTES

- C60 (60 min.) 37p 3 for £1.05
- C90 (90 min.) 62p 3 for £1.80
- C120 (120 min.) 87p 3 for £2.55

P. & P. 5p.

FREE CASSETTE HEAD CLEANER with every 10 cassettes purchased.

All cassettes can be supplied with library cases at 3p. extra each

"VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED. TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

- | | | | |
|---------------------------|-----|----------------------------|-------|
| LP3 3" 250' P.V.C. | 28p | LP6 5 1/2" 1200' P.V.C. | 75p |
| TT3 3" 450' POLYESTER | 37p | DT6 6 1/2" 1800' POLYESTER | £1-12 |
| DT3 3 1/2" 600' POLYESTER | 57p | TT6 5 1/2" 2400' POLYESTER | £1-87 |
| SP5 5" 800' P.V.C. | 42p | BP7 7" 1200' P.V.C. | 62p |
| LP5 5" 900' P.V.C. | 50p | LP7 7" 1800' P.V.C. | 75p |
| DT5 5" 1200' POLYESTER | 75p | DT7 7" 2400' POLYESTER | £1-25 |
| | | TT7 7" 3600' POLYESTER | £2-50 |

TAPE SPOOLS 3" 5p, 5", 5 1/2", 7" 9p.
Post and packing 3" 5p, 5", 5 1/2", 6p, 7" 10p. (3 reels and over Post Free).



PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



PRACTICAL WIRELESS

VOL 47 NO 10

Issue 780

FEBRUARY 1972

Preview '72

THIS is the first issue of P.W. to hit the bookstalls, or land on your doormat, in this brand new year of 1972. As you read these lines, the Christmas and New Year festivities will be receding into the past with, we hope, a rosy nostalgic haze. On the other hand, these notes are being written in the rather hectic period just before, as they say, the holiday breaks out. The mood at the moment of writing is perhaps more of looking back over the year that has gone, whereas a more appropriate theme for the moment of reading is 'never mind all that—we are more interested in what is to come.' Therefore, bowing to popular demand, here is a brief preview of some of the items we have in store for the coming year.

Observant readers will note that we have kicked off with a meaty start. The quality hi-fi stereo system, transistor oscilloscope (which was shown at last year's Audio Fair), a car rev-counter, a gate dip oscillator, notes on SSB reception, Take 20, IC of the Month and all the other regulars is a fair mixture. Next month is something of a special issue and will feature a novel cube radio you will all want to build, a car radio signal booster to give that extra something to your mobile radio reception and a special DX Data wall chart which incorporates information not hitherto published in this country.

The line-up of interesting constructional projects jostling for publication include the digital clock which aroused such interest at the Audio Fair, a shortwave receiver covering from 1.7–30MHz, a simple wobblulator for the MW band, a THD distortion meter, a 2-metre FET converter, a transistor tester, a 160m converter, and many more, including some surprise items. Articles on installing car radios, on how to use the oscilloscope (with many waveforms) and thermionic devices in modern electronics will number among the supporting features.

The May issue will include a special extra 8-page supplement and will be of great importance as it will introduce full constructional details of a hi-fi amplifier of radical design, specially developed for P.W. Using ICs, and constructed for low-profile presentation, this new design should cause quite a stir in the world of audio.

These, then, are some of the things we have in store for the coming year and there will, of course, be others introduced into the schedule as convenient. Since we are now unfortunately unable to supply back numbers make sure you get your copy every month by placing a regular order with your newsagent or taking out a subscription. We'd hate you to be disappointed!

W. N. STEVENS—*Editor*

NEWS AND COMMENT

Leader	881
News . . . News . . . News . . .	882
Electronotes by <i>S. Ginsberg</i>	917
Letters	918
On the Short Waves by <i>Malcolm Connah</i> and <i>David Gibson, G3JDG</i>	921
Practically Wireless by <i>Henry</i>	925
New Books	926
MW Column by <i>Charles Molloy</i>	934

CONSTRUCTIONAL

Transistorised Oscilloscope-Part 1 by <i>J. Ransome</i>	884
Gate Dip Oscillator by <i>B. Wood</i>	889
Car Rev-Counter by <i>A. Lester-Rands</i>	894
Adapting for SSB Reception by <i>R. F. Graham</i>	900
Quality Hi-Fi System-Part 1 by <i>C. R. Bradley</i>	904
Take 20, No. 33, Two Transistor Radio, by <i>Julian Anderson</i>	930


OTHER FEATURES

Transistor Circuitry for Beginners, Part 5 by <i>H. W. Hellyer</i> and <i>Michael Hollier</i>	912
IC of the Month, S.G.S. TBA 631 Audio Detector/Amplifier, by <i>L. A. J. Ireland</i>	929
Going Back by <i>Colin Riches</i> and <i>Arthur Dow</i>	933

**MARCH ISSUE WILL BE
PUBLISHED ON FEBRUARY 4th**

©IPC Magazines Limited 1972. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

Wiring Board

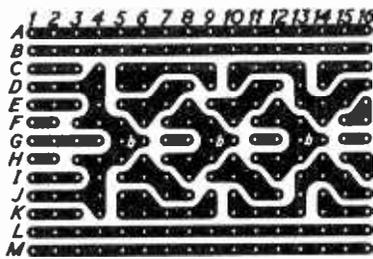

© Copyright design NIP Electronics 1971 NIPPBOARD 'A'

Nippiboard is a simple to use multi-purpose printed wiring board. It has a specially designed layout that can be used as a basis on which to assemble several kinds of circuit, including amplifiers, oscillators, tone circuits, switching circuits, timers, etc.

The list is formidable, but it can be done on one basic Nippi-

board pattern with up to four or five small transistors. And the amazing thing is that one Nippiboard Type 1a or 1b is little larger than a matchbox.


There are two ranges at present available: Range 'A' has an s.r.b.p. base and Range 'B' has a fibreglass base. The s.r.b.p. base is cheaper and easy to work with, but the fibreglass base overcomes some of the problems of "movement" in extreme atmospheric conditions. All Nippiboards are flux varnished to keep the copper clean and make soldering easier.

If larger circuits are multiple circuit systems or building blocks are required, Nippiboard can be obtained in nine different arrangements covering between one and ten basic patterns. Type 1a single basic pattern as shown costs 15p. NIP Electronics, P.O. Box 11, St. Albans, Herts.

Mini Scope

The Tektronix Type 211 is an all solid state miniature oscilloscope with double insulation, and is designed for use in severe environments. Bandwidth is 500kHz. Weighing only 3 pounds and measuring 3 x 5 $\frac{1}{4}$ x 9in., the Type 211 operates from a.c. line or up to 5 hours on internal batteries. Deflection factors are 1mV/div to 50V/div. Sweep rates extend to 1 μ s/div.

In many industrial applications it is frequently necessary to "float" an oscilloscope. The Type 211 may be elevated to 700 Volts above ground when operated from batteries, and to 250 Volts r.m.s. above ground from a.c. Trigger controls are simplified to one rotary control. A bright baseline is provided at all sweep rates, even with no signal in. When a signal is received, the oscilloscope triggers on the signal. Internal and external trigger circuits provide stable displays from about seven hertz to at least 500kHz. Price delivered in the UK is:— Type 211 Oscilloscope £262 including batteries. Duty £29.60. Further information available from: Tektronix U.K. Ltd., P.O. Box 69, Harpenden, Herts.

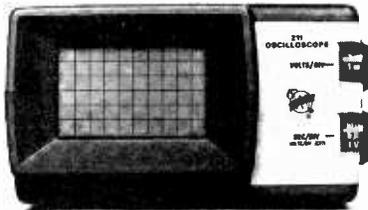


"Verobox"

Vero Electronics announce the introduction of the "E" Series range of cases. The basic shell is identical to the "D" Series but since no front trim is fitted, a slightly larger front panel is required. $\frac{1}{4}$ UNF Front Panel fixing screws are included and the case is finished in R.A.F. blue grey hammertone. Vero Electronics Ltd., Industrial Estate, Chandlers Ford, Hampshire, SO5 3ZR.



Duplex 25

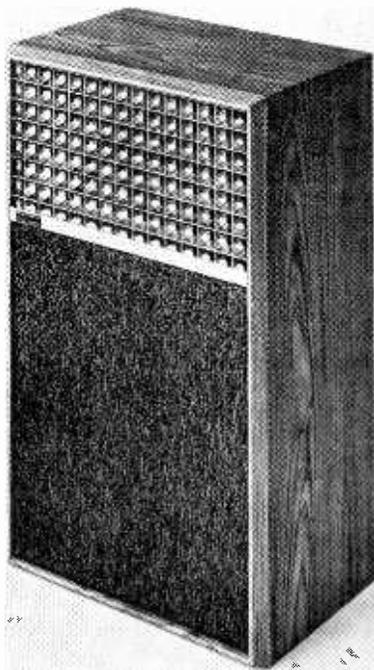

The new Duplex 25 speaker from Metrosound handles a full 25 Watts of power. It has two speaker units—one long throw cone type and the other a radically different electrostatic unit based upon an entirely new patent. The electrostatic unit is mounted behind a lenticular grille. The other is fronted by a specially woven acoustically transparent vinyl cloth. Impedance is 8 ohms. Response 40-18,000Hz. Dimensions: width 16 $\frac{1}{2}$ in., height 27 $\frac{1}{2}$ in., depth 12in.

The smaller version is also available. Called the Duplex 15 it handles 15 Watts and like its big brother it uses both cone and electrostatic units. Impedance 8 ohms. Response of the Duplex 15 is 45-17,000Hz. Dimensions: width 18 $\frac{1}{4}$ in., height 18 $\frac{1}{4}$ in., depth 8 $\frac{1}{2}$ in. For both models the electrostatic unit is energised by a supply voltage of 190-250V, 50-60Hz. Prices: Duplex 15—£32. Duplex 25—£52. Metrosound Audio Products Ltd., Audio Works, Cartersfield Road, Waltham Abbey, Essex.

Moon Laser

A group of scientists of the Moscow Physics Institute and the Crimean Astrophysical Observatory of the U.S.S.R. Academy of Sciences have carried out sessions for laser locating the angular light reflector put on the moon by the *Apollo-15* crew. Clear return signals were recorded.

The angular reflector was placed in the south-east part of the Sea of Rains in the foothills of the lunar apennines, on the dark side of the lunar surface. In order to sight the telescope on it as accurately as possible a small crater was selected on the illuminated part of the moon. Knowing the bearings of this crater and the reflector, one can calculate the angular distance between them. The calculations necessary for sighting the telescope on the light reflector were done at the Academy's Institute of Theoretical Astronomy.

One of the most important tasks of the experiment—the accurate sighting of the laser device on the target—has been solved.

The current experiment is a continuation of the work to investigate the “earth-moon” system by the laser location method. The first Soviet laser locating experiment, for spotting the French reflector mounted on *Lunokhod-1*, was carried out in December 1970 when the measuring accuracy of the distance to the reflectors was of the order of a few metres.

A distinctive feature of the present experiment is that it was possible for the first time to measure the distance to the American angular reflector.

American scientists failed to locate the French reflector mounted on *Lunokhod-1*. This was apparently due to the different methods of calculating the assumed bearings of the reflector.


Detailed processing of the results obtained during the location sessions will make it possible to adjust thoroughly many important characteristics of the “earth-moon” system.

Decade Boxes

Two relatively miniature resistance and capacitance decade units are now available from Londex.

Features of Logade units include single-knob operation over the entire range of four decades, and push-fit terminal sockets accepting standard 4mm plugs.

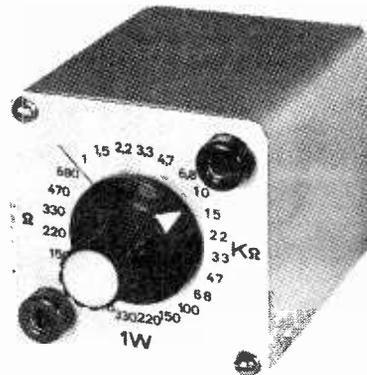Resistance Decade Type R1 has an overall range of 100 ohm up



to 680kΩ, with a tolerance of ± 2 per cent. Maximum operating voltage is 500V r.m.s., and the rating is 1W continuous.

Capacitance Decade Type C1 has an overall range of 100pF up to 0.68µF, with a tolerance of ± 10 per cent. Maximum voltage ratings are 1,000V d.c. or 400V a.c. Descriptive leaflet (List 253) is available from: *Londex Limited*, 207 Anerley Road, London, SE20 8EW. Telephone: 01-778-3111.


Logic Probes from C.I.

Circuit Integration have announced the introduction of a new product line—a series of Logic Probes.

These pocket-sized probes are designed for the testing of all types of equipment incorporating Integrated Circuits. The units are powered by the equipment under test, and colour-coded readout lights at the probe tip give a clear, accurate indication of “true”, “zero” or “pulse” conditions.

The units can be used with virtually any DTL/TTL IC system, including calculators, business machines, numerical control equipment, computers etc., as an invaluable aid to field service engineers, and as a testing device during laboratory development and manufacture.

There are five models in the series, covering the testing and advanced testing of logic systems

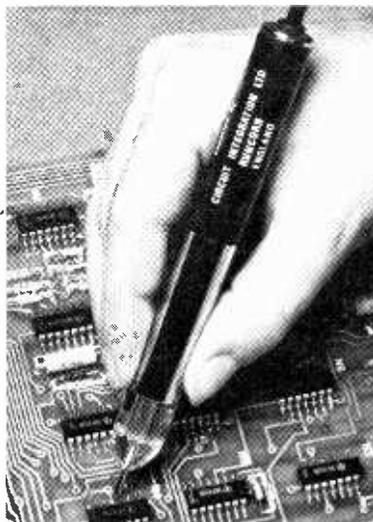

from 4.7V d.c. to 15V d.c. All models incorporate overload protection to protect the circuit under test.

Full details available from:—*Circuit Integration Ltd.*, Davey Rd., Astmoor Industrial Estate, Runcorn, Cheshire. Tel.: Runcorn, 75973/6.

THIS oscilloscope was specifically designed for the first Project Autumn Competition. The most important rule (in the writer's opinion) of that competition was that all components should be readily available; to this the designer has added his own requirement that all circuitry should be completely proved and easily set up using simple test-gear. To the writer there is nothing more frustrating than building up a circuit exactly to the published plans only to find that it does not work because certain component values have been determined empirically and are highly specific to the valves or transistors used in the original equipment. Also, any design that calls for elaborate setting-up or requires specialised test gear for accurate calibration is bound to have an appeal limited to those having either well lined pockets or industrial contacts.

In this design, none of the components is stretched to its limits and this offers the constructor the ability to substitute a wide variety of transistor types for those shown—where transistor selection is somewhat critical this is indicated in the text. If the unit is assembled in the order described then the only test-instrument required is a milliammeter capable of reading currents in the ranges 0-10mA and 0-500mA.

It was thought desirable to make the unit as portable as possible so that it could be used for field work. This, of course, requires that the unit should be capable of working from batteries. A quick calculation revealed that the power consumption



TRANSISTORISED

PART 1

OSCILLOSCOPE

would be such that the use of dry batteries would be out of the question so it was decided that secondary cells would be used as the power source. The obvious choice of supply voltage is 12V as this is readily available from car batteries.

In order to reduce the weight of the unit, no provision for working from the mains has been incorporated, though a 12V power supply can easily be built.

The use of a 12V supply means that the use of valves in the circuit is undesirable from the point of view of efficiency and for this reason it was decided to use transistors throughout. The employment of solid state circuitry enables both weight and power demand to be minimised.

The circuitry and construction of the oscilloscope will be described in sections starting with the power supply. A block diagram showing the relationship of these sections to the finished project is shown in Fig. 1. By tackling each section as it were in reverse, each section can be checked and will be fully functional on completion.

The complete unit is housed in a metal case, the construction of which is shown in Fig. 2. No precise drilling details are given as these will vary according to the components used.

As the layout is completely uncritical the chassis can, in fact, take any conversion form. Indeed there is no need to have a special chassis made as there are many manufacturers of standard ranges of cases and chassis who regularly advertise through the columns of this journal—any of their products will be satisfactory if made from aluminium or other

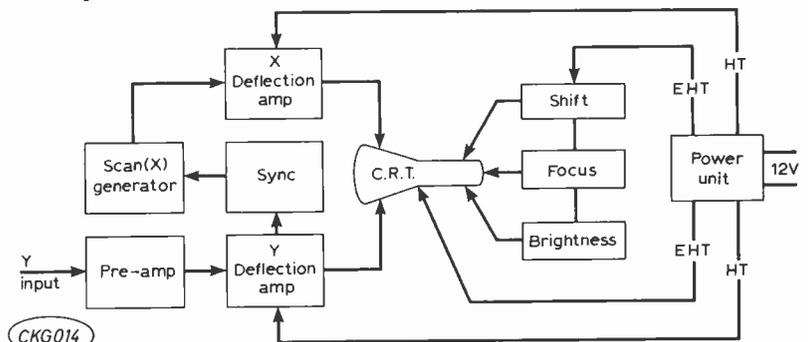


Fig. 1: Block diagram showing the relationship between the various units which will be described separately.

non-magnetic material.

Each component unit will now be described in the suggested building sequence together with the appropriate testing procedures.

POWER SUPPLY UNIT

This was the only part of the whole unit which presented problems from the design point of view. The total h.t. power demand is 3.4 watts and the e.h.t. demand is a little over 1W so that allowing for a conversion efficiency of, say, 60 per cent, the power input to the primary must be in the order of 8W. Using saturated switching circuits it is possible to obtain this sort of power from a single-ended stage but, unfortunately, all the attempts by the writer to attain this theoretical goal ended in failure or disaster!

The next type of circuit to be tried was the push-pull oscillator. Whilst this circuit worked reasonably well, the construction of a suitable transformer appeared to be beyond the scope of this constructor as either one used an inordinate number of turns to get a primary inductance that was satisfactory on the standard range of pot-cores available, or one used a pot-core which is not readily available. After much experimentation the circuit shown in Fig. 3 was developed.

The use of a multivibrator circuit does not seem to offer theoretical advantages over its competitors. Its principle disadvantages being the lower efficiency and the use of more passive components. To the practical constructor, however, it has three major advantages:

- a) it does not stall under heavy load
- b) it is a first-time starter
- c) the construction of the transformer is not critical

Of these (c) is most important in that the transformer windings do not have to be neat, tidy and accurate so long as an adequate turns ratio is maintained. The writer constructed three of these units with differing transistor types and succeeded in getting all three to work first time.

The circuit operation is quite straightforward. Tr1 and Tr2 form a simple common emitter multivibrator. The collector load for each transistor is provided by the primary of the transformer T1. The resonant frequency of the circuit is made as high as possible so that the primary inductance can be minimised, for by reducing the primary inductance we lower the number of turns required on the primary of the transformer. This has the effect of reducing the turns-per-volt characteristic of the transformer and eases

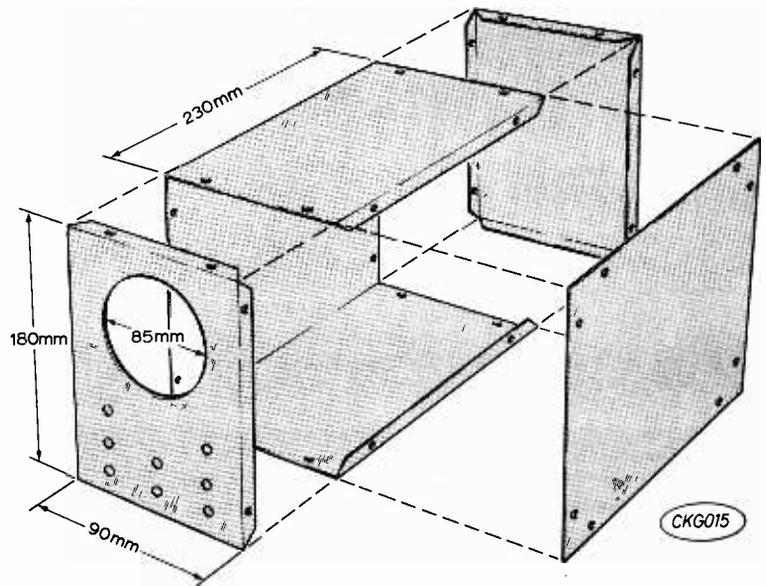


Fig. 2: The basic dimensions of the case used for the prototype and its construction.

construction of the high voltage secondary.

For the circuit shown the total primary inductance is in the order of 1mH and the turns/volt relationship is 1.5 turns-per-volt.

The secondary of the transformer is wound to give an equivalent r.m.s. output voltage in the region of 220V. As the voltage waveform from the transformer is a peaky triangular shape rather than the more conventional sine wave, measurement of the output voltage by means of the normal a.c. voltmeter is misleading and the only valid way of checking the circuit is to measure the d.c. output from the rectifier. Thus we refer to an equivalent r.m.s. output rather than the true peak-to-peak output.

The secondary of the transformer provides power for the h.t. rail via the bridge rectifier D1-D4 and the smoothing and stabilising circuit of C3, R3, ZD1 and C4, and for the e.h.t. line via the voltage doubling circuits of C5, D5 and D6 and the associated smoothing capacitor C19. This circuitry is completely

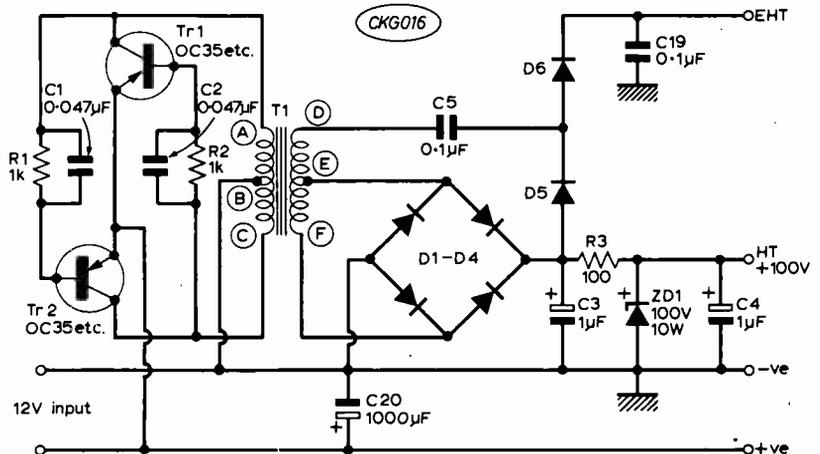


Fig. 3: The power supply circuit which provides the three different voltages necessary.

conventional and does not warrant further discussion here.

The complete power supply is built on to the back of the chassis; the siting of the main components is shown in Fig. 4.

CONSTRUCTION OF T1

T1 is wound on a Mullard LA4 pot-core which is readily available from advertisers in this magazine.

Dismantle the pot core and locate the winding bobbin. This item is fairly fragile and should be handled with care. Wind on to the bobbin 18 turns of 28 s.w.g. double cotton covered enamelled wire. This should occupy one complete layer on the bobbin. Leave several inches of wire at each end of the winding to serve as lead-out wires. Wind on a further 18 turns over the first layer and in the same direction as the previous winding and twist together the end of this winding with the end of the first winding. This is the primary centre tap. Now wrap 1½ turns of p.v.c. self-adhesive tape around the windings. Next wind on 120 turns of 32 s.w.g. enamelled wire (try to be as neat as possible but don't worry about the occasional overlap). Pull off sufficient wire from the coil to form the centre tap and wind on sufficient turns to fill the bobbin (the number of turns will depend on how evenly the previous layers were wound—anything between 100-150 turns will be satisfactory). The lead-out wires forming the start, the tap and the finish of this winding should then be sleeved and the winding taped in place.

The whole unit can now be reassembled by first placing the coil inside the ferrite ring and bringing the lead-out wires through the slots cut in the ring. Now drop this assembly over the core and put on the top-plate. Bolt up the complete assembly tightly.

The transistors Tr1 and Tr2 should next be bolted on to the chassis back-plate which acts as a heat sink and T1 fixed in position together with the battery supply terminals. Note that Tr1 and Tr2 should be insulated from the chassis using mica washers. Once the primary circuit has been built up the unit may be tested. Connect the 12V supply via a milliammeter. The meter should indicate a standing current of 200-300mA. If the current is higher than this, disconnect, and check the wiring particularly on the secondary side.

If all is well connect a 250V neon across the rectifier output (- and +); the neon will light up and the current drawn from the 12V source will increase by about 80mA. If a neon lamp is not available disconnect the milliammeter from the primary circuit and connect in series with a 10kΩ resistor when, if the unit is running correctly, a current of 5-8mA will be indicated. This will rise to 15mA if a 1μF 250V electrolytic capacitor is also connected across the rectifier. The second phase of the power unit construction can now be undertaken. The tag-strips holding the components are anchored at various convenient points as shown in the photograph. The zener diode must be mounted on a heat dissipating plate about 2in. square. This plate should not be anchored to the oscilloscope chassis (unless insulated electrically). Note that some zener diodes of this power rating have their mounting stud at the cathode end of the diode while on others the stud is the anode.

As the e.h.t. voltage is fairly low (about 500V) no special precautions need be taken other than to


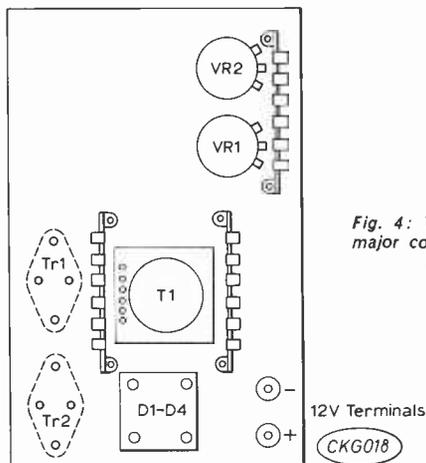


Fig. 4: The siting of the major components on the back panel.

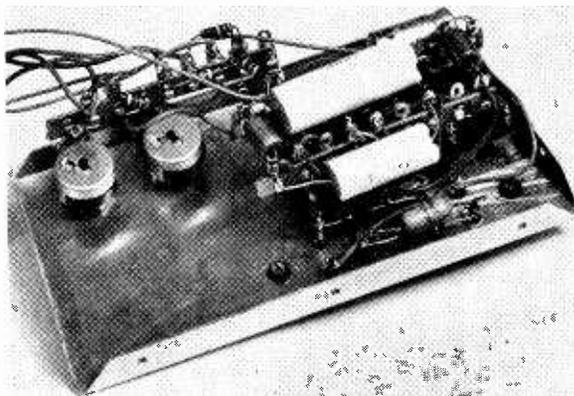

Compare this view of the back panel with Fig. 4.

ensure that there is a reasonable spacing between the components of the e.h.t. circuitry and the other low voltage items.

TESTING

Check all wiring—particularly the e.h.t. side for faults and potential short circuits. As the oscillator is capable of generating sufficient power to burn out the transformer or the transistors under short circuit conditions, this visual check is a wise precaution.

Connect the milliammeter in series with the battery supply lead and switch on. The current consumption should be about 400-500mA. If the current drain is significantly higher than this, switch off immediately and check the wiring. If all is well remove the ammeter from the battery leads and using a 10kΩ resistor in series with one lead, apply this across C4. A current flow of about 10mA is correct. Remove the meter from the circuit and replace the 10kΩ resistor with one of 470kΩ. Apply the meter and series resistance across C19 (remembering that C19 will have across it a voltage of anything up to 600V). Approximately 1mA should be taken by the meter.

The power supply is now complete and ready to connect to the next phase of construction—the Display Unit.

THE DISPLAY UNIT

The theoretical circuit of the Display Unit is shown in Fig. 5. Again the circuitry is absolutely standard and well tried. The potential divider chain of R11, VR4, VR3, R10 and R6 and R7 with VR2 and VR1 in parallel has a total resistance of $1.5M\Omega$ and draws approximately $300\mu A$ from the e.h.t. supply. This gives a control range of 3V to 33V for VR4 and 33V to 185V for VR3. The shift controls have 100V across them and give, therefore, 50V shift either side of the mid-point voltage determined by R6 and R7.

The resistors R4, R5 and R8 and R9 serve to isolate the X and Y plates from "cross-talk" and give a measure of protection to the transistor output stage described later.

CONSTRUCTION

The shift components and X and Y bias and isolating resistors are mounted on the back plate of the chassis next to the power supplies. As the shift controls are only 500V above earth potential they can be mounted directly onto the aluminium plate without further insulation.


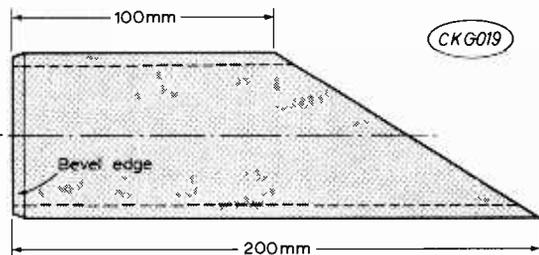


Fig. 6: The dimensions of the CRT cradle.

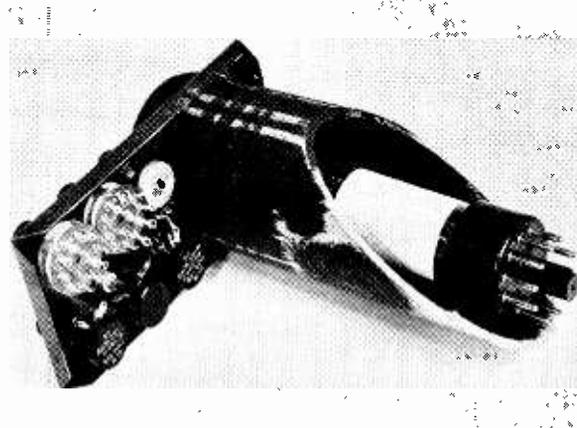

The front panel, showing the CRT cradle, before wiring.

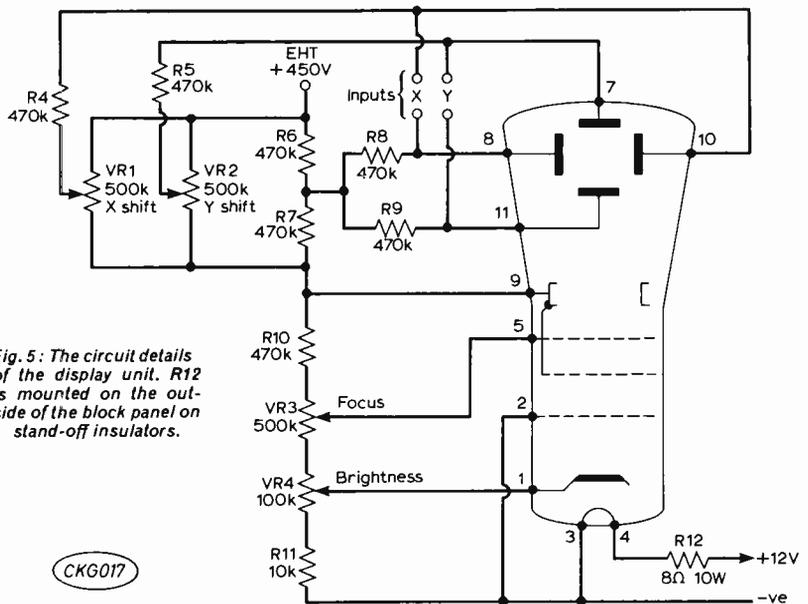


Fig. 5: The circuit details of the display unit. R12 is mounted on the outside of the block panel on stand-off insulators.

The tube itself is mounted inside a cradle which also serves as a light shield. The cradle is made from 75mm dia. ABS or PVC drain-pipe (the actual pipe used by the writer was an Osman soil-pipe). About 200mm is required and this is cut and bevelled as shown in Fig. 6. After cleaning up the cut surfaces the pipe is painted matt black (alternatively use a gloss black pipe which is available from some builders rather than the more usual grey).

The cathode ray tube face rim is next padded to prevent mechanical damage if the unit is dropped. The writer used a self-adhesive foam draught excluder winding two complete turns around the tube rim. The foam should be dyed or painted black.

When the paint is dry the cradle can be pushed through the CRT hole in the front panel (push in from the front) leaving about 10mm of the bevelled edge protruding. The CRT is then pushed into the cradle from the rear and should be a snug fit inside the pipe.

TESTING

Having checked the wiring to the tube base and the e.h.t. connections, set VR4 slider to the R11 end of its travel and set VR3 to its mid-point. Switch on the power unit. Allow a minute for the tube to warm-up and adjust VR1 and VR2 until the spot is at the centre of the screen. Adjust VR4 and VR3 for minimum brightness and spot size.

If no spot can be resolved, insert the meter between R11 and VR4 and check for a current flow of about $300\mu A$. If this current is absent, or very low, follow the e.h.t. down the chain using the meter and the 250kΩ resistor until the break is found. If no break can be discovered, check to see that R11 is taken to the negative line. Inability to centre the spot and/or elliptical movement of the spot is caused by incorrect connections to the X and Y plates.

If all is well, the deflection test unit of Fig. 7 may be built up to test the circuit so far. In building the test unit, make certain that the live leg of the mains is connected to the top of the $1M\Omega$ resistor. For added safety the two neon lamps may be incorporated into the circuit. Only use the test unit when N100 is illuminated.

The high level output from the deflection test unit is first applied to the X input when a straight line about 40mm long will be produced. Turn the tube physically until this line is horizontal. When all is well apply the test unit to the Y input when a vertical line will be produced of roughly equal length

★ components list (complete unit)

Resistors

R1 1kΩ ½W	R19 4.7kΩ ½W	R37 470Ω ½W
R2 1kΩ ½W	R20 4.7kΩ ½W	R38 2.7MΩ ½W 5%
R3 100Ω ½W	R21 10kΩ ½W	R39 1MΩ ½W 5%
R4 470kΩ ½W	R22 10kΩ ½W	R40 470kΩ ½W 5%
R5 470kΩ ½W	R23 1kΩ ½W	R41 33kΩ ½W 5%
R6 470kΩ ½W	R24 1kΩ ½W	R42 27kΩ ½W
R7 470kΩ ½W	R25 10kΩ ½W	R43 47kΩ ½W
R8 470kΩ ½W	R26 47kΩ ½W	R44 1kΩ ½W
R9 470kΩ ½W	R27 1kΩ ½W	R45 18kΩ ½W
R10 470kΩ ½W	R28 47Ω ½W	R46 33kΩ ½W
R11 10kΩ ½W	R29 100Ω ½W	R47 33kΩ ½W
R12 8Ω 10W	R30 47kΩ ½W	R48 18kΩ ½W
R13 33kΩ ½W	R31 47kΩ ½W	R49 1kΩ ½W
R14 10kΩ ½W	R32 1MΩ ½W	R50 220Ω ½W
R15 2.2kΩ ½W	R33 82kΩ ½W	R51 8.2kΩ ½W
R16 2.2kΩ ½W	R34 10kΩ ½W	R52 220kΩ ½W
R17 See text, ½W	R35 470Ω ½W	R53 2.2kΩ ½W
R18 See text, ½W	R36 4.7kΩ ½W	

NOTE: Two off each required R13 to R24 inclusive. All 10% types except where shown.

VR1 500kΩ lin. pot VR4 100kΩ lin. pot VR7 5kΩ
 VR2 500kΩ lin. pot VR5 10kΩ lin. pot log. pot.
 VR3 500kΩ lin. pot VR6 5kΩ preset

Capacitors

C1 0.047μF 150V	C8 0.1μF 1000V	C15 5μF 15V
C2 0.047μF 150V	C9 0.1μF 1000V	C16 1000pF
C3 1μF 250V	C10 5μF 15V	C17 0.1μF 150V
C4 1μF 250V	C11 0.1μF 150V	C18 0.01μF 150V
C5 0.1μF 1000V	C12 6.4μF 25V	C19 0.1μF 1000V
C6 5μF 15V	C13 5μF 15V	C20 1000μF 25V
C7 5μF 15V	C14 64μF 15V	

NOTE: Two off each required C6 to C9 inclusive.

Time base capacitors

CTa 1μF	CTc 0.01μF
CTb 0.1μF	CTd 1,000pF

Semiconductors

Tr1 OC35, 2G222 etc.	Tr7 BSX21	Tr13 2N3906
Tr2 OC35, 2G222 etc.	Tr8 2N3702	Tr14 2N3906
Tr3 2N3906	Tr9 2N2160	Tr15 2N3906
Tr4 2N3906	Tr10 2N3906	Tr16 2N3906
Tr5 BSX21	Tr11 2N3906	Tr17 2N3702
Tr6 2N3906	Tr12 2N3906	

NOTE: Two off each required Tr3 to Tr7 inclusive.

D1-D4 OA202 or combined bridge

D5 1000V 0.6A silicon

D6 1000V 0.6A silicon

D7 OA81.

ZD1 100V, 10W zener

Cathode Ray Tube

ECR30 or VCR139A

Switches

SW1 Timebase 1-pole, 4-way
SW2 Input atten., 1-pole, 3-way
SW3 Sync in/out, on-off toggle.
SW4 Int/Ext Sync, 1-pole, 2-way toggle

Miscellaneous

B12B tube base; 3in diam. pipe for CRT cradle;
 T1, see text, LA4 pot core, 28 s.w.g. D.C.C. enam.
 wire, 32 s.w.g. enam. wire; Tag strips; Veroboard;
 Switches, etc.

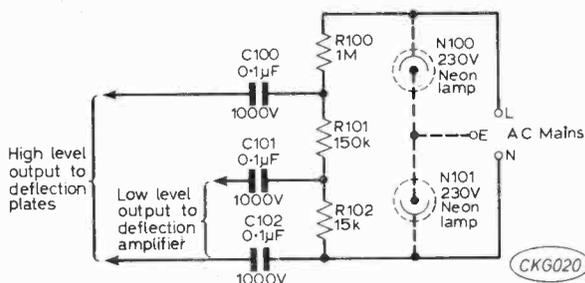


Fig. 7: The deflection test unit.

of that of the horizontal line. Next, connect the X1 and Y1 inputs together and the X2 and Y2 plates together. Apply the test voltage across the combined plates when a circle (or ellipse, depending on the relative deflection sensitivity of the plates) should be produced.

The unit as it now stands can be used as a simple a.m. transmitter modulation monitor.

For this purpose a small demodulation unit will be required—this is shown in Fig. 8. Power from the transmitter is fed directly into the tuned circuit. Modulated r.f. is fed directly to the Y plates of the display unit while the X plates receive the a.f. signal from the demodulation network. The resultant trace is shown in Fig. 9. The area occupied by the

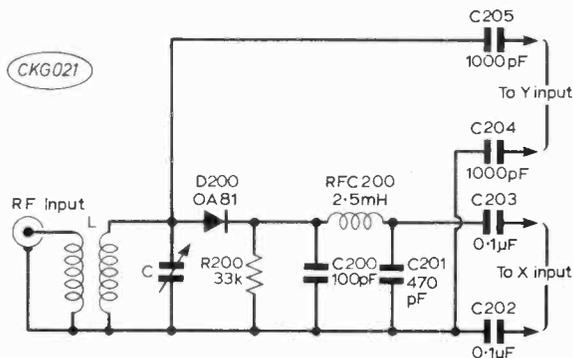


Fig. 8 (above): The circuit of the demodulator unit. L and C are chosen to resonate at the transmitter frequency.

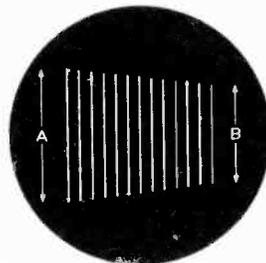


Fig. 9 (left): The display from the demodulator unit. The modulation depth is

$$\frac{A - B}{A + B} \times 100 \text{ per cent.}$$

A and B are measured in any convenient units (mm etc.)

trace is controlled by the power output of the transmitter—by making the r.f. input coil of L loose over the coil former, the coupling and thereby the power input to the demodulator may be varied.

TO BE CONTINUED

GATE DIP OSCILLATOR

B. WOOD

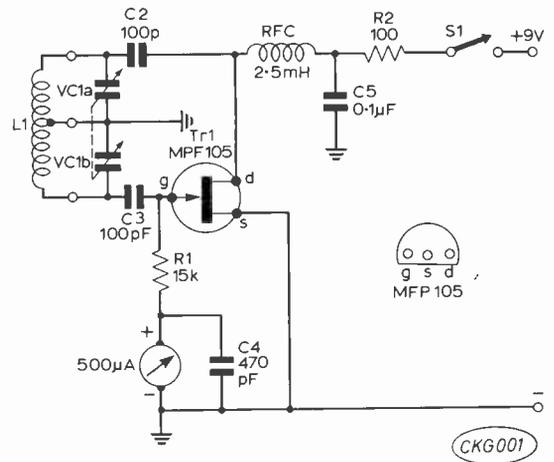


Fig. 1: Circuit of a simple gate dip oscillator.

amended circuit and it will be seen that few extra components are needed. VR1 was included to enable the meter pointer to be adjusted and kept on scale when using different coils.

Fig. 3 shows the addition of a simple modulator. T1 was removed from a small pocket-type transistor set. Modulation was obtainable using several combinations of the windings, but those noted on the circuit diagram proved the best. Failure to oscillate may require the reversal of the leads to either the primary or secondary of the transformer.

The function switch provides the following modes:—

Position 1. Instrument off.

Position 2. S2 closed. Meter amplifier operative. Measurement of the frequency of coil/capacitor combinations in "hot" circuits.

Position 3. S1 and S2 closed. Operates as an unmodulated r.f. oscillator enabling:—

- (a) The adjustment of "cold" coil/capacitor combinations.
- (b) Frequency measurement. Beating the g.d.o. with a station tuned in on the receiver.
- (c) As a beat frequency oscillator. Useful also for resolving s.s.b. signals.

ONE of the most useful and versatile of instruments, usually noticeable by its absence, is the grid or gate dip oscillator. The drawback in the pre-transistor age was that such instruments were valved and hence needed a mains power pack or bulky batteries which restricted operation. To be so restricted when measuring the resonant frequency of a whip aerial, or adjusting the traps on a dipole, is to say the least, inconvenient. The purpose of this article is to show how the author was able to construct a fairly versatile and readily portable g.d.o. almost entirely from bits and pieces found in his junk-box.

DEVELOPMENT

The original circuit is shown in Fig. 1. The f.e.t. costs under 40p, whilst the meter was taken from a No. 19 set. Acceptable results were obtained from this set up, but it was felt that the addition of a diode and an OC71 meter amplifier would increase the usefulness of the instrument. Fig. 2 shows the

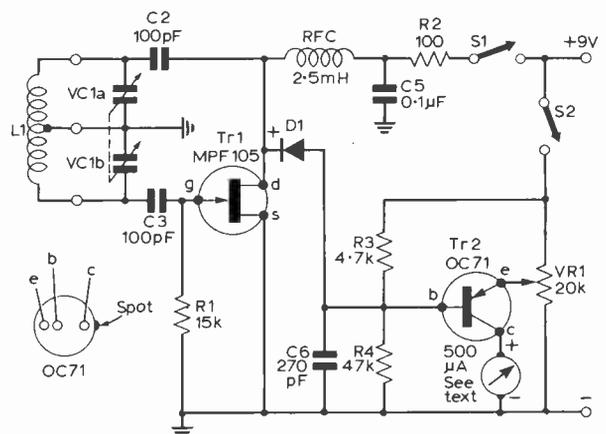



Fig. 2: G.d.o. with d.c. amplifier to permit use of less sensitive meter.

BSR C.109 SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in.

Above motor board 3 1/2 in. wide motor board 2 1/2 in. with STEREO and MONO XTAL

£7.75 Post 25p.

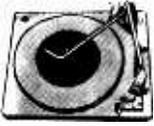

RCS DE-LUXE 3 WATT AMPLIFIER.

Ready made with 2-stage triode pentode valve, 3 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL82, EZ80/81.

Response 50-12,000 cps. Sensitivity 200mV. Post 25p.

£4

R.C.S. PORTABLE PLAYER CABINET



Really smart appearance with space for R.C.S. Amplifiers and most modern autochangers. Size 18 1/2 x 15 x 9 1/2 in. Metal fitting. Carrying handle. Two-tone resin coated. Popular colours.

£4 25p.

GARRARD SINGLE PLAY TA MK II Ideal

Discotheque or Hi-Fi. Stereo/Mono

£10

GARRARD PLAYERS with Sonotone 9TA Cartridges

Stereo Diamond and Mono Sapphire. SP25 MK III £16. Model 3500 Stereo and Mono Autochanger £4. Post 25p.

R.C.S. TEAKWOOD BASE.

Ready cut out for mounting (State player make and model)

£2.75

R.C.S. PLASTIC COVERS FOR ABOVE BASE.

Durable tinted plastic, attractive appearance.

£2.25

EMI PICK-UP ARM with mono xtal and stylus £1.25.

HI-FI PICK-UP CARTRIDGES. Diamond Stereo/Mono. 9TA £2.50; GP04 £2.50; GP03 £2.00; Mono GP01 £1.50; GP6 £1.25; ACPS L.P. only 50p.

E.M.I. WOOFER AND TWEETER KIT

£5.75 Post 25p

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 44oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines.

Impedance Standard 8 ohms
Maximum Power 12 watts
Useful Response 35 to 18,000 cps
Base Resonance 45 cps



WEYRARD P50-TRANSISTOR COILS

RA2W Ferrite Aerial..... 65p	Spate Cores 3p
One. P50/1AC..... 30p	Driver Trans. LPD74..... 50p
1.F. P50/2C/470 kc/s..... 33p	Printed Circuit. PCAL..... 50p
3rd I.F. P50/3C..... 33p	J.B. Tuning Gank..... 65p
P51/1 or P51/2..... 33p	Weyrard Booklet..... 10p
P50/3..... 33p	OPTI..... 50p

Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 25p.

VOLUME CONTROLS

Long spindle, Midget Size 5 K ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. EDGE 5K. S.P. Transistor 25p

800ohm Coax 4p. yd. BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1.40; 60 yd. £2. FRINGE LOSS 10p yd. Ideal 625 and colour.

WIRE-WOUND 3-WATT POTS.

Small type with small knob. Values 10Ω to 30 K. CARBON 30 K to 2 meg. **25p**

WIRE-WOUND 3-WATT STANDARD SIZE POTS. 10 OHMS to 100 K. **40p**

VEROBOARD 0.15 MATRIX

2 1/2 x 5in. 25p. 2 1/2 x 3 1/2 in. 17p. 3 1/2 x 3 1/2 in. 25p. 3 1/2 x 5in. 30p. EDGE CONNECTORS 16 way 25p; 24 way 38p. PINS 36 per packet 21p. FACE CUTTERS 35p.

S.R.B.P. Board 0.15 MATRIX 2 1/2 in. wide 3p per lin., 4 1/2 in. wide 4p per 1 in.; 5in. wide 5p per lin. (up to 17in.). S.R.B.P. undrilled 4 in. Board 10 x 8 in. 15p.

BLANK ALUMINIUM CHASSIS

18 s.w.g. 2in. sides. 7 x 4in. 45p; 9 x 7in. 50p; 11 x 7in. 70p; 13 x 9in. 90p; 14 x 11in. 95p; 15 x 14in. 90p; 11 x 3in. 50p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 9p; 8 x 6in. 15p; 14 x 8in. 18p; 10 x 7in. 19p; 12 x 5in. 20p; 12 x 8in. 28p; 16 x 8in. 28p; 14 x 9in. 34p; 12 x 12in. 40p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES

25p. 2 p. 2-way, or 2 p. 6-way or 3 p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p.

1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 6 p. 2-way, 1 p. water 60p, 2 water 90p. Extra wafers up to 50p each.

TOGGLE SWITCHES. sp. 14p; dp. 18p; dp. dt. 23p.

"THE INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER

200/250v. A.C. **£2.35** Post Leaflet S.A.E. 15p



HI-FI STOCKISTS. RETURN OF POST DESPATCH.

RADIO COMPONENT SPECIALISTS

List 5p. Written guarantee with every purchase.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V. AC. Output voltages available 6 or 9 or 12 or 15 or 18 or 20v. DC at 100mA or less.

PLEASE STATE VOLTAGE REQUIRED. **£2** POST FREE
Details S.A.E.

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12v or H.T. line 200-300V D.C. operation. Size 1 1/2 x 1 1/2 x 1". Response 25 c.p.s. to 25 Kcs. 26db gain. For use with valve or transistor equipment. Full instructions supplied.

Brand new. Guaranteed. Details S.A.E. **90p** Post 10p

NEW TUBULAR ELECTROLYTICS CAN TYPES

2/350V .. 14p	250/25V .. 14p	18-18/500V .. 55p
4/350V .. 14p	500/25V .. 20p	50-50/350V .. 55p
8/450V .. 14p	1000/25V .. 35p	60-100/350V .. 55p
15/450V .. 14p	1000/50V .. 47p	32-32/250V .. 18p
32/450V 20d	8+8/450V 18p	32-32/450V .. 33p
25/25V 10p	8+16/450V 20p	350+50/325V .. 50p
50/50V .. 10p	16-16/450V 25p	32-32-32/350V 43p
100/25V 10p	32-32/350V 25p	100+50-50/350V 48p

SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p; 500, 1000mF 12V 18p; 2000mF 25V 42p.

CERAMIC 12F to 0.01 mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%; 2-2500pF 8p; 500-2-200 pF 10p; 2-700-5-600pF 20p; 6-800pF-0.01, mfd 30p; each. TWIN GANG. "0-0" 208pF; 170pF, 65p; Slow motion drive 365-385 with 25-25pF 50p 500pF slow motion, standard 4p; small 3-gang 500pF £1.60.

SHORT WAVE. SINGLE. 10pF 30p; 25pF 55p; 50pF 55p. CHROME TELESCOPIC AERIAL. swivel base, 23in. 20p. TUNING. Solid dielectric. 100pF. 500pF. 35p each. TRIMMERS. Compression 30, 50, 70pF, 5p; 100pF, 150pF, 8p; 250pF, 10p; 600pF, 1p; 75pF 10p; 150pF 10p. SILICON REC. CAP. 2DS500 Bridge 70V 5 amp £1. RECTIFIERS CONTACT COOLED + wave 60mA 38p; 85mA 48p. SILICON BYZ13 30p; BY100 30p; BY127 30p. EX-GOVERNMENT RECTIFIERS 250V, 200mA, 30p. NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p. RESISTORS. 1 w. 1/2 w. 20, 1p; 3 w. 5p. 10 ohms to 10 meg. HIGH STABILITY. 1 w. 20, 10 ohms to 1 meg. 10p. Ditto 5%. Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K. 10p each; 2 1/2 watt, 1 ohm to 8.2 ohms 10p

SCOOP! METAL PLINTH AND PLASTIC COVER

Cut out ready for Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Antimagnetic. 12 1/2 x 14 1/2 x 7 1/2 in. high including cover.

£5.50 Post 25p

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp.	£1.40
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£2.00
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£2.00
300-0-300 v. 120 mA. 6.3 v. 2 a. A.C.T. 8.3 v. 2 a.	£2.50
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in.	75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in.	90p
P.E. AUBORA TRANS. 12 v. 127. 500mA	£1.50
MINI-MAINS 20v. 100mA. 1 1/2 x 1 1/2 x 1 1/2 in.	50p
HEATER TRANS. 6.3v. 3 a.	60p
Diode tapped sec. 1.4 v. 2, 3.4, 5.6, 3 v. 1 1/2 amp.	80p

GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 8, 9, 10, 12, 15, 12, 24 and 30 v. £2.00

1 amp. 6, 8, 10, 12, 15, 12, 24, 30, 36, 40, 48, 60. £2.00

2 amp. 8, 8, 10, 12, 18, 20, 24, 30, 36, 40, 48, 60. £3.00

AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. Input/Output. 150w. £2.00; 500w. £5; 1000w. £12.

CHARGER TRANSFORMERS. Input 200/250v. for 6 or 12v. 1 amp. £1.20; 2 amp. £1.40; 4 amp. £2.00.

FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. outputs, 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p. All transformers Postage 25p extra.

E.M.I. 1 1/2 x 8in. LOUDSPEAKERS

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) **£4** Post 15p

With flared tweeter cone and ceramic magnet, 10 watts. Bass res. 45-60 cps. Input 10,000 gauss. State 3 or 8 or 15 ohm. **£2.25** Post 15p

Recommended Teak Cabinet Size 16 x 10 x 9in. Post 25p **£5**

10W MINI-MODULE £3.25 LOUDSPEAKER KIT

Post 25p

Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. x 8 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 16 x 10 x 9in. Modern design with **£5** Post 25p fluted wood front. Highly recommended.

ALL MODELS "BAKER SPEAKERS" IN STOCK

BAKER 12in. MAJOR £9

30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. **£11.50**

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch £7	12 inch £9	15 inch £19
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. dia. speaker 20 x 13 x 9in. .. £9. Post 25p For 13 x 8in. speaker 16 x 10 x 9in. .. £5. Post 25p For 10 x 6in. speaker 16 x 8 x 6in. .. £4. Post 25p

LOUDSPEAKER CABINET WADDING 18in. wide, 15pft.

GOODMANS HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. Hi-Fi Enclosures Systems, etc. **£4**



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watts. 3 ohm or 15 ohm models. **£1.90** Post 10p



Horn Tweeters 2-16Kcs, 10W 8 ohm or 15 ohm £1.50. De Luxe Horn Tweeters 2-16 Kcs, 15W, 8 ohm 25p. TWO-WAY CROSSOVERS 3 or 8 or 15 ohm 95p. SPECIAL OFFER: 80 ohm, 2 1/2 in. dia.: 35 ohm, 2 1/2 in. dia.: 25 ohm, 2 1/2 in. dia.: 3in. dia.: 8 x 5in.; 8 x 5in. £1 EACH 15 ohm, 3 1/2 in. dia.: 7 x 4in.; 8 x 5in. £1. TYPE 8 ohm, 8 x 4in. 3 ohm, 2 1/2 in. 3in. 5in. 5 x 3in. 7 x 4in. LOUDSPEAKERS P.M. 3 OHMS. 6in. 11.10.8 x 5in. £1.25: 8 x 2 1/2 in. 80p; Sin. £1.75: 10 x 2 1/2 in. 80p. HI-FI WOOFER 8 watt max. 20-10,000 cps. 8 or 15 ohm. £1.80. ELAC 10in. 10W. De Luxe Ceramic, 8 ohm. £4. RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. dia. 4 watt; 10in. dia. 5 watt; 12in. dia. 8 watt 3 or 8 or 15 ohm models £1.85 each. Post 15p. OUTPUT TRANS. EL34 etc. 25p. MIKE TRANS. 50:1 25p. SPEAKER COVERING EL34 etc. 30p. Amplifier, garage S.A.E. GOODMANS OUTPUT TRANSFORMER 5 watt push-pull for valves EL84 etc., 3, 8 and 15 ohms 85p. Post 20p.

BAKER 10W TATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. 200/250v. Separate Treble and Bass controls. Guaranteed Details S.A.E. **£39** POST FREE



ALL EAGLE PRODUCTS

BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. **£4**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4.25.

BARGAIN FM TUNER 88-108 Mc/s. Six Transistor. 9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch **£10**

BARGAIN FM TUNER as above less cabinet **£7.50**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. **£3.50**

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS 5p yd. 80 ohms or 300 ohms. JACK SOCKET Std. open-circuit 14p, closed circuit 23p; Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 15p; 5-pin 25p. DIN PLUGS 3-pin 15p; 5-pin 25p. VALVE HOLDERS. 5p. CERAMIC 5p. CANS 5p.

E.M.I. TAPE MOTORS Post 15p.

120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75in. **£1.25** Size 8 1/2 x 2 1/2 in. (Illustrated).

BALFOUR GRAM MOTORS

120v. or 240v. A.C. 1,200 r.p.m. 4 pole 50mA. Spindle 2 x 3/20. Size **85p** 2 1/2 x 2 1/2 in. Post 15p



CUSTOMERS FREE CAR PARK. CALLERS WELCOME

337 WHITEHORSE ROAD, CROYDON

Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.) Buses 50, 68, 159 pass door. Rail Selhurst Tel. 01-684-1665

NEW FROM LINEAR

Representing really exceptional value

TWO STEREO AMPLIFIERS

IN ELEGANT TEAK FINISH CASES!



LINEAR 606
6+6 WATTS
Recommended Retail Price
£22.50

0-200-230-250v. 50 Hz
A.C. mains operation.
Inputs for magnetic or
Ceramic Pickup, Tape or
Radio Tuner.

TECHNICAL DETAILS

Bass Control ± 12 dB at 40 Hz.
Treble Control ± 12 dB at 14 KHz.
Sensitivities Mag. P.U. 3.5 m.v.
into 47K ohm R.I.A.A. Ceramic
P.U. 35 m.v. into 100K ohm. Tape
Amp. 100 m.v. into 100K. Radio
Tuner 400 m.v. into 400K ohm.
Crosstalk 53 dB.
Hum and Noise -75 dB min.
vol. -85 dB max. vol.
**Total Harmonic
Distortion** 0.1% at 1watt
into 15 ohms.
Output (per channel)
6.5 watts I.H.F.M.

- ★ Individual Bass and Treble Controls.
- ★ Frequency Response $\pm 1\frac{1}{2}$ dB
20 Hz to 65 KHz.
- ★ Outputs for Speaker impedances
between 3 and 15 ohms.
- ★ Stereo/Mono Switch.
- ★ Input Selector Switch.
- ★ Solid State Circuitry.
- ★ Attractive silver finished metal facia
and matching control knobs.

- ★ A modestly priced solid state unit.
- ★ The Silver Facia with black lettering enhanced by
matching control knobs, provides a high standard of
appearance.
- ★ Suitable for crystal or ceramic Gram. Pick-up
cartridges, and Radio input.
- ★ A wide range of tone variation is provided by the
separate Bass and Treble 'lift' and 'cut' controls.
- ★ A selector switch permits instantaneous selection of
Gram. or Radio.
- ★ Speaker impedances between 3 and 15 ohms are
suitable.

TECHNICAL DETAILS

Frequency Range 20 Hz to
20 KHz
Output (per channel) 5 watts
I.H.F.M.
Bass Control ± 12 dB at 60 Hz.
Treble Control ± 14 dB. at
14 KHz.

PRINTED CIRCUIT CONSTRUCTION
EMPLOYING 10 TRANSISTORS



LINEAR 505 5+5 WATTS
Recommended Retail Price
£17.50 0-200-250v. 50 Hz A.C.
mains operation

Wholesale and Retail enquiries to the Manufacturers

ALL LINEAR AMPLIFIERS GUARANTEED FOR 12 MONTHS

LINEAR PRODUCTS LTD.; Electron Works, Armley, Leeds. LS12 3SA Tel.630126



become a RADIO-AMATEUR!

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO SCHOOL
READING, BERKS

NAME : _____
ADDRESS : _____

—BLOCK CAPS please

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDGE,
YORKS

TEL. HECKMONDWIKE 4285

Amplifier Unit Type A413. Complete with 524 & 6V6GT valves. 250/230 Volt Transformer. Clean condition untested. £1.25. Carriage 75p.

Air Position Indicator. Contains Gears. Ball Races. Dimmer Unit. Lamps. Four numbered Counters. 24 Volt Motor etc. Great interest to the model makers. Good condition 75p. Carriage 50p.

Ground Position Indicator. Contains 24 Volt Lamp. Prisms Mirror and Gears. Could interest schools and model makers. 75p. Carriage 75p.

Latest Air Ministry Release Radio Receiver. Type R4187. 2.8 to 18 MHz in Three Bands. Complete with 17 miniature valves. 26 Volt Motor. Power supply motor and manually tuned. Very clean, but not tested. £5. Carriage and Insurance 75p.

Control Unit. Type 4190. Complete with three miniature valves. 1 $\frac{1}{2}$ " 500 μ A Meter. Six Relays. Model makers Motor with Gears. 24 Press Buttons. Lots of spares. Clean condition. £1.50. Carriage and Insurance 75p.

Autostabiliser Amplifier Unit. Complete with Carpenter Relay and Base. Many spares. 50p. P/P 33p.

Special Offer. Aircraft Sighting Head. Comprising flexible drive, lens prism unit, Giro. Useful for model constructors, schools, etc. Condition fair. 75p. Carr. 75p.

Reclaimed T.V. Tubes. All with 12 months guarantee.
AW43/88. £2. AW43/80. £1.50. MW43/89 £1. Special offer Brand New Brimar Tubes C17P.M. £1. Many older types in stock. Carriage and insurance on any tube £1-10.

Breaking-up. Ferguson Model 506T. Tested L.O.P.T. £1.45. Post paid. Fireball Tuner Unit with Valves less Knobs. 75p. Post paid. S.A.E. for Price List of other spares for this set and other types.

Valve List Ex Equipment All Valves Tested on a Mullard Valve Tester before despatched. 3 Months Guarantee on all Valves Single Valves P/P 3p. Over three Valves P/P Paid.

ARP12	5p	PCC84	5p	U191	20p
EB91	4p	PCF80	5p	U251	12½p
EF85	12½p	PCL82	12½p	6BW7	10p
EBF80	12½p	PCL83	12½p	6U4	10p
EBF89	12½p	PCF82	12½p	6F23	20p
ECC81	10p	PL36	20p	20P1	20p
ECC82	12½p	PL81	17½p	20P3	10p
ECC83	12½p	PY81	7½p	20D1	10p
ECL80	7½p	PY33	17½p	30P4	20p
EF80	7½p	PY82	7½p	30P12	20p
EF91	4p	PL82	7½p	30FL1	20p
EY86	20p	PL83	7½p	6/30L2	20p
		PCL84	12½p	30F5	10p

loosely coupled to the aerial socket of the station receiver via a short length of wire. With the g.d.o. variable capacitor vanes fully in mesh, a search is made on the receiver for the modulated signal. The search must begin at a frequency much lower than that expected, in order to ensure that one is not working on harmonics of the signal. Throughout calibration, the small variable capacitor should be kept at half mesh.

Having found the lowest frequency to which the

coil will tune, it is only necessary to open up the vanes of the g.d.o. and gradually follow the signal on the receiver up to a higher frequency, in fact to its limit. Should the desired coverage not be obtained on any range it may be necessary to add or take off a few turns of wire.

During calibration use can be made of standard frequency transmissions for checking the receiver as well as the g.d.o. Oscillation on the l.f. ranges could only be obtained if the coils were centre tapped, as indicated.

Should a crystal calibrator be available use can be made of it in the calibration procedure. Loosely couple the calibrator to the station receiver, switch the g.d.o. to c.w. and zero beat the two signals, taking care that the beat is taking place with fundamentals of the g.d.o. In the case of the Class D Wavemeter, it is switched to 1MHz, and coupled to the g.d.o. coil by a 3 turn-coil, when it is possible with the phones connected to the wavemeter, and the g.d.o. switched to c.w., to hear the 1MHz harmonics when tuning the g.d.o. Having marked these in on the dial, it is then possible to fill in the gaps with the 100kHz crystal. It is then only necessary to identify any one of these points by using the g.d.o. in conjunction with the station receiver, to complete the rest of the calibration for that coil. Calibration of the remaining coils was carried out in the same way, working down from the h.f. to the l.f. coils.

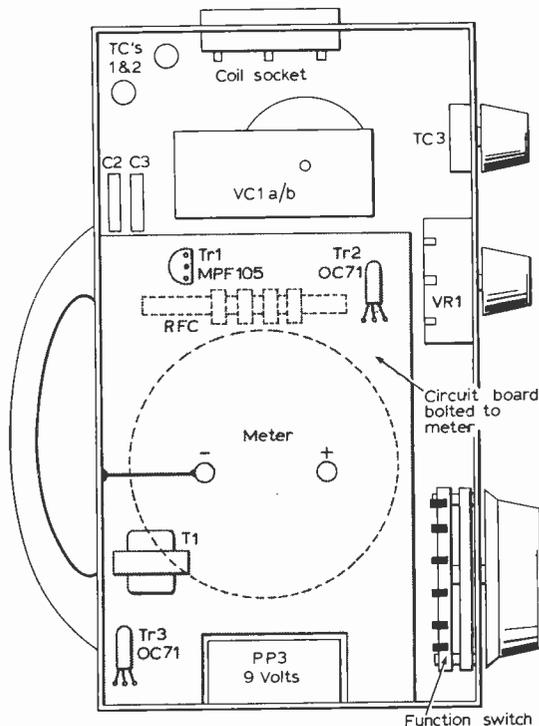


Fig. 4: Layout of main components in the g.d.o. constructed by the author.

★ components list (Fig. 3)

Resistors

R1 15k Ω	R5 1k Ω
R2 100 Ω	R6 1k Ω
R3 4.7k Ω	R7 15k Ω
R4 47k Ω	All $\frac{1}{4}$ W 10%
	VR1 20k Ω linear potentiometer

Capacitors

VC1a-b 250 + 250pF approx. See text	
C2 100pF SM	C6 270pF SM
C3 100pF SM	C7 0.1 μ F
C4 470pF (Fig. 1)	C8 0.33 μ F
C5 0.1 μ F	C9 0.01 μ F
TC1/2 3-30pF trimmer. See text	
TC3 5pF trimmer. See text	

Miscellaneous

Transistor MPF105(1) OC71(2). Miniature audio transformer (T1). RFC 2.5mH.
Meter, see text. Wafer switch 1 pole, 4 way, shorting consecutively.

TELEVISION

FEBRUARY ISSUE

THE DO-BE OSCILLATOR

A timebase oscillator circuit for the constructor—the double-beam oscillator, so called because it employs two valves in a blocking oscillator/discharge valve arrangement. Whilst using a double-triode and transformer the circuit is nevertheless economical in other components and has the advantage of very good locking. Field and line generator circuits are given.

SIMPLE WALL-MOUNTING UHF AERIAL

Another design for the constructor. The main advantage of this dipole-plus-sheet-reflector assembly is that it is very short and can be mounted quite unobtrusively just inside or outside a window. Dimensions are given for group A, B and C/D versions.


THE SANYO 10-T120U

A further instalment in our series on the interesting circuitry to be found in imported TV receivers. This 10in. mains/battery portable for example features a keyed a.g.c. circuit, noise-cancelled sync separator circuit, emitter-follower line output stage and other arrangements which are illustrated and described.


PLUS ALL THE REGULAR FEATURES

ON SALE JANUARY 17

A. LESTER-RANDS'

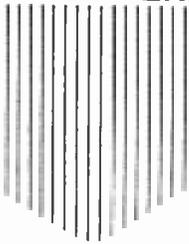

CAR Rev-Counter

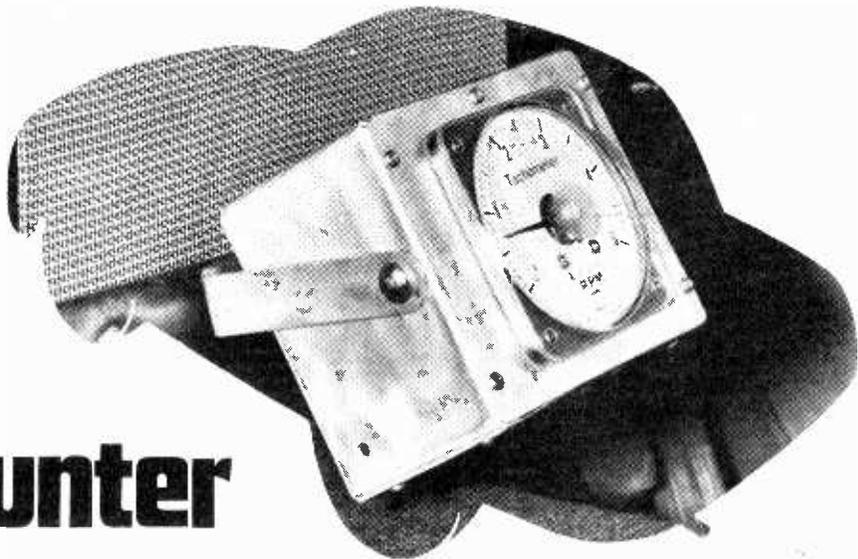

MANY car owners, particularly those who have cars with high revving engines, consider an engine tachometer an essential dashboard instrument and manufacturers of some modern cars now fit a rev counter as a standard. A tachometer gives a direct reading of engine revolutions per minute which can be related to brake horsepower and torque to enable the car owner to get the best performance from the engine with the least wear and tear and at the most economical fuel consumption.

The tachometer described in this article employs a fairly simple circuit which can be adjusted for use with 4, 6 or 8 cylinder engines and calibrated for revolutions per minute of 0-5,000, 0-8,000 or 0-10,000. To give an example of this, the writer's car has a 4 cylinder engine and develops maximum brake horse power at 4,600 r.p.m.; in this case calibration was adjusted for 0-5,000 r.p.m.

The instrument will operate from the car battery regardless of which polarity of the battery is earthed to the car body and no direct electrical connection is necessary to pick up the ignition pulses. The pulse pick-up is capacitive by means of a few turns of insulated wire wrapped around the main ignition lead.

The actual r.p.m. indicator may be any 1mA f.s.d. meter but for a longer calibration scale and a more pleasing appearance, a meter with a 240° scale is worth the extra cost; most of those available have a 3in. diameter scale. The meter can of course be a conventional 90° scale type or an edge scale meter which might lend itself better for dashboard mounting. If there is no room on the dashboard, the complete tachometer could be mounted in a small box of its own and secured where it can be seen at a glance.

THE CIRCUIT

The tachometer circuit is shown in Fig. 1 and is a fairly conventional arrangement using a flip-flop (Tr1 and Tr2) from which to derive a constant amplitude narrow square-wave. The time constant in the flip-flop produces an output pulse of approximately 0.5mS. The supply voltage is held stable by the Zener Diode to 8.2V so that variations in the battery voltage do not effect the readings. The output from Tr3 is, as far as the meter is concerned, a recurrent positive-going pulse of constant amplitude and duration. The meter will read the mean positive voltage developed by the pulses so the slower the pulses the lower will be the meter reading and vice versa. However, the meter reading can be altered by increasing or decreasing the amplitude of the pulse current passing through it by inserting series resistance (PR1 and Rx). This makes it possible to adjust full scale deflection for different maximum readings. Equally the pulse amplitude to the meter can be adjusted relative to the pulse rate so that the meter can be calibrated for 4, 6 or 8 cylinder engines as

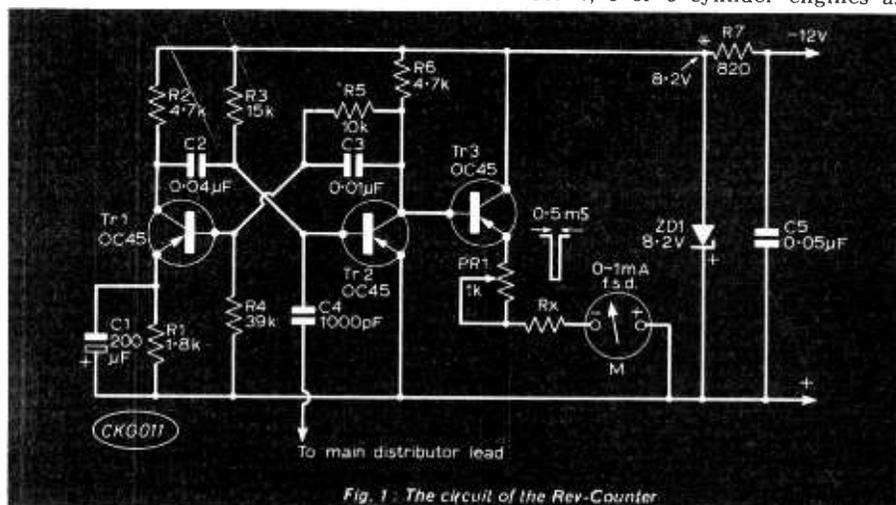


Fig. 1. The circuit of the Rev-Counter

CONTROL DRILL SPEEDS

DRILL CONTROLLER NEW 1KW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. \$1.50 plus 13p. post and insurance. Make up model also available, \$2.25 plus 13p. post & p.

MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 3 circuits each rated at 10amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2 1/2. \$1 each.



NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 80p doz. Plastic pusher suitable for operating. 5p each, 45p doz.



AUTO-ELECTRIC CAR AERIAL

with dashboard control switch fully extendable to 40in or fully retractable. Suitable for 12v positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. \$6 plus 23p post and ins.



TOGGLE SWITCH

3 amp. 250v. with fixing ring 7 1/2 each. 75p doz



MICRO SWITCH

5 amp. changeover contacts. 9p each. \$1 doz. 15 amp. Model 10p each or \$1.05 doz.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—4 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 18p each, \$1.80 dozen, your assortment.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.



BLANKET SWITCH

Double pole with neon led into side so luminous in dark. Ideal for dark room light or for use with waterproof element, new plastic case 30p each. 3 heat model 40p.



CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 38p each or 10 for \$3.42.




TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. \$2.95 plus 20p post and insurance.



QUICK CUPPA

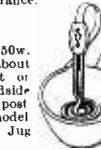Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use as socket or lamp holder. Have at bedside for tea, baby's food, etc. \$1.25, post and insurance 14p. 12v. car model also available same price. Jug heater \$1.50 plus p. & p. 14p.



SNAP ACTION SLIDE SWITCH

Rated 5a. 240v. Made by Arrow. Type fitted in the handles of electric drills, vacuumms, etc. 5p each, 10 for 45p.



NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XN. 3. Price \$1.45 each, 10 for \$13.



12 WAY SUB-MINIATURE MULTI-CORE CABLE

7-0076 copper cores each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 20p per yard.



LIGHT CELL

Almost zero resistant in sunlight increases to 10 K Ohms in dark or null light, epoxy resin sealed. Size approx. 1in. dia. by 1/4in. thick. Rated at 500 MW, wire ended. 43p with circuit.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines. Display lighting in meters and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £5.75 plus 25p post and insurance. Don't miss this terrific bargain.



THE FULL-FI STEREO SIX

The amplifier sensation of the year

You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled in simulated teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.M. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and gated volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. UNREPEATABLE PRICE is £9 plus 38p post and insurance

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £3 plus 25p post and insurance. £2.50 with fitted 13 amp plug; £2.40 with fitted 15 amp plug, plus 23p P. & I.



THIS MONTH'S SNIP

Smiths 24 hour 2 on/2 off Time Switch This is the popular model, as used in the Autosec and Morphy Richards time switches. Only needs a case and an output socket. 250v. 50 cycle. Contacts switch up to 13 amps. Price £2.75p



TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal fire case or cabinet. Only need control switch. £3.50. 2kW. Model as above except 2 kilowatts £2.50. Don't miss this Control Switch 35p P & P. 40p



POCKET CIRCUIT TESTER

Test continuity for any low resistance circuit, house wiring, car electrics. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied). 30p or £ for 60p. Post paid



COMPUTER TAPE

2,400ft. of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1in wide £1.00 plus 38p post and insurance, with cassette. 1/2in. wide £1.00 plus 30p post and insurance with cassette. 1/2in. wide 75p plus 26p post and insurance with cassette. Spare spools and tapes 1in. 75p, 1in. 75p each plus 20p post and insurance.

1 HOUR MINUTE TIMER

Made by famous Smiths company, these have a large clear dial, size 4 1/2 x 3 1/2, which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch £1.15.

RADIO STETHOSCOPE

Easiest way to find and—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal capsule. £2—in stethoscope instead of earpiece 75p extra—post and ins. 20p.



SOLDER GUN

A must for every busy man, gives almost instant heat also illuminates job. Dual heat 100/140 watt £3.75 plus post & ins. 40p. 20p. BIG JOB 260 watt model. £4.75 plus post & ins. 40p.

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply a kit of parts for an improved and even more efficient version (Practical Wireless June). Price £4.95 plus 30p post. When ordering mention version for positive or negative systems. Also available, ready made ignition systems for 6v. vehicles, £5.25 plus 20p.

ELECTRONIC IGNITION

TYPE 25 RELAYS

These are miniature relays. Size approx. 1 3/16in. high x 3/16in. wide x 1/4in. deep. Change over silver/gold contacts. Contact rating lamp 100V. D.C. Fitted with a plastic cover. Coil operates approx. 260Mv. D.C. Available with the following coils: 280ohms for 4-7.5v. 450hm for 1-2.5v 520hm for 4-9-6v 960hm for 5-5-11.5v 1300hm for 10-15v 5300hm for 17-36v 12500hm for 27-44v 25000hm for 31-65v 58000hm for 27-44v. 75p each, 10 for £6.75. Also one with 16,500hm coil but this has only 2 heavy duty change over gold contacts. Price £1.45.



Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

Veroboard. We are now stocking this in various sizes. Prices as follows:

3 1/2 x 3 1/2	0 1	0 15
2 1/2 x 3 1/2	22p	16p
3 1/2 x 5 1/2	24p	24p
3 1/2 x 6 1/2	24p	24p
3 1/2 x 8 1/2	27p	27p
17 x 2 1/2	75p	57 1/2p
17 x 3 1/2	100p	75p
17 x 6 (plain)		75p
17 x 3 1/2 (plain)		82 1/2p
17 x 2 1/2 (plain)		87 1/2p
2 1/2 x 6 (plain)		17 1/2p
2 1/2 x 3 1/2 (plain)		15p
Pin intersection tool	47 1/2p	47 1/2p
Spot face cutter	37 1/2p	37 1/2p
Pkt. 50 pins	20p	20p

FLUORESCENT CONTROL KITS

Each kit comprises seven items—'choke', 2 tube ends, starter, holder and 2 tub clips, with wiring instructions. Suitable for normal fluorescent tubes or the new 'Grolux' tubes for fish tanks and indoor plants. Choices are super-sized, mostly resin filled. Kit A—15-20 w. £1. Kit B—30-40 w. £1. Kit C—40-60 w. £1.20. Kit E—65 w. £1.20. Kit F for 8ft. 125 w. tube £1.75. Kit MF1 is for 6in., 9 in. and 12in. miniature tubes £1. Kit MF2 for 2 1/2in. 13 w. miniature tube £1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and E 23p on first kit then 18p for each kit ordered. Kit F 33p on first kit then 23p for each kit ordered. Kit MF1 15p on first kit then 15p on each two kits ordered.

0-8 AMMETER

2 in. square full vision for flush mounting. Moving iron instrument. Suitable for charger. Price 43p each 10 for £3.90.



Box Sign for Window Display, at home, office or shop, 2 ft. wide x 14 in. high x 5 in. deep. This is an illuminated box sign made from sheet metal hammer finish enamel with a clear plastic window. You simply have your message printed or written on poster board or thick card. (Or use stick down letters available at most stationers.) You will then have a box sign normally costing anything between £10-£15. Illumination is by a 2 ft. fluorescent tube with control gear enclosed. Message card can be changed quite easily from hinged top back. Price £3 each, plus 65p post, etc.

Motivated Illuminated Box Sign. A previous item but with geared motor moving the message making it change eight times a minute. Very attention arresting. To use this for your own messages you would have to have each sign on card and the one supplied with the box sign. Price £4.50, plus 65p post and service.

Geared Motor with take off socket. The gear train is driven by normal type induction motor and gives a final speed of 8 r.p.m. The motor is mounted behind a chrome plate through which the take off drive protrudes and was originally intended to drive a spit for cooking, is also ideal for driving models or for driving a colour changing disc for the local dance hall, discotheque, etc. Really well made assembly. Price £1.75 plus 26p post etc.

Dry Film Lubricant. In aerosol can for easy application and for putting lubricant into places where the normal oil can cannot reach. Home and every-day uses. We have purchased a large quantity of these from the Liquidator and are able to offer them to you at about half of the original list price. 30p per (8 oz.) can or 12 cans for £3 post paid. The lubricant is I.C.I. Bucon L169.

REED SWITCHES

Class enclosed, switches operated by external magnet—gold welded contacts. We can now offer 3 types. Miniature. 1" long x approximately 1/4" diameter. Will make and break up to 1/4 A up to 300V. Price 18p each, £1.20 dozen. Standard. 2" long x 1/4" diameter. This will break currents of up to 1A, voltage up to 250V. Price 10p each, 90p per dozen. Flat. Flat type, 2" long, just over 1/4" thick, flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1A 200V. Price 30p each £3 per dozen. Small ceramic magnets to operate these reed switches 9p each, 90p dozen. Dry Reed Relays. Solenoids on moulded bobbins with magnetic shields—printout circuit or panel mounting.

Ref.	Coil Resistance	Reed Switches	Price
71005	2 K	1 normally open	25p
81916	1 K	1 normally open	25p
		1 normally closed	75p
		1 normally open	25p
05003	4 K	1 normally open	35p
62040	1500 & 500 ohms	1 normally open	25p
Multiple Reed Relay. Ref. 53001. Contains 13 normally open reeds within a solenoid. Operates on 60mW. Coil resistance 9K ohms. Price £1.95 each.			
Multiple Reed Relay. Ref. 081. 2 normally open 1 normally closed coil resistance 30 ohms. Price 75p.			
Thermostat. This is a thermostat with Sensor on the end of a long capillary tube. The temperature range is 50-120° C. approx. The setting is by range is for pointer knob (knob not supplied). The sensor can be immersed in the liquid or can be fixed to the container or as when used on an electric cooker, this can be fitted in the centre of a heating element. Price 65p each. £5.85 for ten. Many other thermostats available please request list.			

J. BULL (ELECTRICAL) LTD.
(Dept. P.W.), 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, Croydon.

**Fully guaranteed
Individually packed
VALVES**

B12H	£1.75p	ECH200	82p	OA2	35p
CY31	35p	ECL90	45p	OB2	35p
DAF96	35p	ECL82	32p	PA BCB30	37p
DF96	37p	ECL83	40p	PC97	40p
DL96	41p	ECL86	42p	PC900	47p
DK92	32p	EF36	45p	PCF84	37p
DL94	40p	EF37A	45p	PCF89	45p
DL96	41p	EF39	40p	PCF189	55p
DM70	30p	EF40	50p	PCF800	75p
DY86	45p	EF41	32p	PCF80	30p
DY87	55p	EF80	25p	PCF82	32p
DY802	48p	EF83	55p	PCF84	46p
E88C0/01	£1.80p	EF85	32p	PCF86	57p
E180C	90p	EF86	81p	PCF200	77p
E182C	90p	EF89	21p	PCF201	77p
EF95	37p	EF91	32p	PCF802	48p
EF95	37p	PCF805	72p	PCF805	72p
EA0C80	32p	EF183	32p	PCF806	65p
EA0F42	60p	EF184	35p	PCF808	72p
EB91	15p	EPL200	75p	PCH200	70p
EB93	50p	EPL21	52p	PCL81	47p
EB04	52p	EL41	57p	PCL82	37p
ECC81	30p	EL42	53p	PCL83	65p
EF80	42p	EL84	23p	PCL84	42p
EF83	42p	EL85	40p	PCL85	42p
EF89	30p	EL90	35p	PFL200	57p
ECC82	28p	EL95	35p	PL36	53p
ECC83	30p	EL500	85p	PL81	50p
ECC84	20p	EM31	25p	PL82	40p
ECC85	40p	EM80	40p	PL83	42p
ECC86	50p	EM84	35p	PL84	35p
ECC87	52p	EM87	35p	PL500	75p
RC189	32p	EY51	40p	PL604	75p
ECF80	35p	EY86	35p	PY33	60p
ECF82	35p	EY81	35p	PY80	35p
ECF83	75p	EY88	40p	PY81	27p
ECF801	62p	EZ41	42p	PY82	27p
ECF802	62p	EZ80	25p	PY83	35p
ECH85	65p	EZ81	37p	PY88	37p
ECH42	65p	GZ34	52p	PY800	52p
ECH81	28p	KT95	£1.00p	PY801	52p
ECH83	42p	KT88	£2.15p	QV003-10	
ECH84	45p	N78	£1.25p		

29/41H. AERIALS each consisting of ten 3ft. jin. dia. tubular screw-in sections. 11ft. (6-section) with aerial with adaptor to fit the jin. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect. In canvas bag £4. P. & P. 50p.

METERS

Full List of our very large stock of meters on request.

TRANSISTORS, ZENER DIODES etc.

SPECIAL OFFER	OC25	37p	OC200	40p	2N3055	75p	AD149	50p	BYZ13	25p		
OBJ tube	OC26	25p	OC201	60p	2N3730	50p	AD161	37p	BYZ16	85p		
	OC28	62p	OC206	90p	2N3731	£2.75p	AD162	37p	CR81/10	28p		
	OC29	62p	IN21	17p	2N5109	£2.05p	AF118	62p	CR81/20	38p		
	OA5	25p	OC35	50p	IN21B	25p	AF127	17p	CR81/30	40p		
	OA10	25p	OC38	42p	IN215	60p	AF139	30p	CR81/35	48p		
	OA70	10p	OC44	17p	IN43	10p	AF178	45p	CR81/40	45p		
	OA71	10p	OC45	15p	IN70	7p	PRF5	32p	AF186	40p		
	OA73	10p	OC70	12p	IN702-72536P	3N128	87p	AFY19	£1.13p	CR83/20	38p	
	OA74	10p	OC71	15p	IN823A	£1.30	3N139	£1.75p	ABY26	25p	CR83/30	43p
	OA79	10p	OC72	25p	IZM75	35p	3N140	95p	ABY28	25p	CR825/025	
	OA81	10p	OC73	30p	IZM710	35p	3N154	90p	ABY67	48p		
	OA91	7p	OC75	25p	IZT15	67p	3N159	£1.45p	BAW19	25p		
	OA200	7p	OC76	25p	IZT10	68p	6PR5	45p	BC107	12p	CR83/40	50p
	OA202	10p	OC81	25p	24385	51p	12FR60	73p	BC108	12p	GET103	23p
	OA210	25p	OC81D	20p	2G403	15p	10D1	18p	BC113	25p	GET115	45p
	OA211	37p	OC81DM	20p	IN4785	50p	40594	£1.37p	BC118	38p	GET116	50p
	OA221	32p	OC82	25p	2N277	52p	40595	£1.37p	BCY72	15p	GEX66	£1.10p
	OA220	10p	OC83	25p	2N2918	37p	40686	£1.45p	BF115	25p	NKT222	20p
	OA2206	42p	OC83B	15p	2N1304	25p	40689	£1.45p	BFY51	20p	NKT304	50p
	OA2207	47p	OC84	25p	2N1306	25p	40626	23p	BFY52	23p	BD918	28p
	OA2208	16p	OC122	50p	2N1307	25p	AC127	25p	BS03	38p	BD928	31p
	OA2213	32p	OC139	25p	2N2147	74p	AC128	25p	BS	45p	BD938	32p
	OA2223	10p	OC140	37p	2N2904A	32p	AC176	25p	BS2	47p	BD94	21p
	OA2225	50p	OC170	25p	2N2904A	32p	AC176	25p	BS2	47p	BD94	21p
	OC16	50p	OC171	30p	2N3054	55p	ACY17	30p	BSY29	25p	SD988	46p
	OC22	50p	OC172	37p	2N3054	60p	ACY28	17p	BU100	£1.80p	UA05A	40p
	OC29	62p	OC29	62p	IN21	17p	2N5109	£2.05p	AF118	62p	CR81/20	38p
	OC35	50p	OC35	50p	IN21B	25p	40382	60p	AF127	17p	CR81/30	40p
	OC38	42p	OC38	42p	IN215	60p	40383	60p	AF139	30p	CR81/35	48p
	OC44	17p	OC44	17p	IN43	10p	3F100	87p	AF178	45p	CR81/40	45p
	OC45	15p	OC45	15p	IN70	7p	3PR5	32p	AF186	40p	CR83/05	30p
	OC70	12p	OC70	12p	IN702-72536P	3N128	87p	AFY19	£1.13p	CR83/20	38p	
	OC71	15p	OC71	15p	IN823A	£1.30	3N139	£1.75p	ABY26	25p	CR83/30	43p
	OC72	25p	OC72	25p	IZM75	35p	3N140	95p	ABY28	25p	CR825/025	
	OC73	30p	OC73	30p	IZM710	35p	3N154	90p	ABY67	48p		
	OC75	25p	OC75	25p	IZT15	67p	3N159	£1.45p	BAW19	25p		
	OC76	25p	OC76	25p	IZT10	68p	6PR5	45p	BC107	12p	CR83/40	50p
	OC81	25p	OC81	25p	24385	51p	12FR60	73p	BC108	12p	GET103	23p
	OC81D	20p	OC81D	20p	2G403	15p	10D1	18p	BC113	25p	GET115	45p
	OC81DM	20p	OC81DM	20p	IN4785	50p	40594	£1.37p	BC118	38p	GET116	50p
	OC82	25p	OC82	25p	2N277	52p	40595	£1.37p	BCY72	15p	GEX66	£1.10p
	OC83	25p	OC83	25p	2N2918	37p	40686	£1.45p	BF115	25p	NKT222	20p
	OC83B	15p	OC83B	15p	2N1304	25p	40689	£1.45p	BFY51	20p	NKT304	50p
	OC84	25p	OC84	25p	2N1306	25p	40626	23p	BFY52	23p	BD918	28p
	OC122	50p	OC122	50p	2N1307	25p	AC127	25p	BS03	38p	BD928	31p
	OC139	25p	OC139	25p	2N2147	74p	AC128	25p	BS	45p	BD938	32p
	OC140	37p	OC140	37p	2N2904A	32p	AC176	25p	BS2	47p	BD94	21p
	OC170	25p	OC170	25p	2N2904A	32p	AC176	25p	BS2	47p	BD94	21p
	OC171	30p	OC171	30p	2N3054	55p	ACY17	30p	BSY29	25p	SD988	46p
	OC172	37p	OC172	37p	2N3054	60p	ACY28	17p	BU100	£1.80p	UA05A	40p
	OC29	62p	OC29	62p	IN21	17p	2N5109	£2.05p	AF118	62p	CR81/20	38p
	OC35	50p	OC35	50p	IN21B	25p	40382	60p	AF127	17p	CR81/30	40p
	OC38	42p	OC38	42p	IN215	60p	40383	60p	AF139	30p	CR81/35	48p
	OC44	17p	OC44	17p	IN43	10p	3F100	87p	AF178	45p	CR81/40	45p
	OC45	15p	OC45	15p	IN70	7p	3PR5	32p	AF186	40p	CR83/05	30p
	OC70	12p	OC70	12p	IN702-72536P	3N128	87p	AFY19	£1.13p	CR83/20	38p	
	OC71	15p	OC71	15p	IN823A	£1.30	3N139	£1.75p	ABY26	25p	CR83/30	43p
	OC72	25p	OC72	25p	IZM75	35p	3N140	95p	ABY28	25p	CR825/025	
	OC73	30p	OC73	30p	IZM710	35p	3N154	90p	ABY67	48p		
	OC75	25p	OC75	25p	IZT15	67p	3N159	£1.45p	BAW19	25p		
	OC76	25p	OC76	25p	IZT10	68p	6PR5	45p	BC107	12p	CR83/40	50p
	OC81	25p	OC81	25p	24385	51p	12FR60	73p	BC108	12p	GET103	23p
	OC81D	20p	OC81D	20p	2G403	15p	10D1	18p	BC113	25p	GET115	45p
	OC81DM	20p	OC81DM	20p	IN4785	50p	40594	£1.37p	BC118	38p	GET116	50p
	OC82	25p	OC82	25p	2N277	52p	40595	£1.37p	BCY72	15p	GEX66	£1.10p
	OC83	25p	OC83	25p	2N2918	37p	40686	£1.45p	BF115	25p	NKT222	20p
	OC83B	15p	OC83B	15p	2N1304	25p	40689	£1.45p	BFY51	20p	NKT304	50p
	OC84	25p	OC84	25p	2N1306	25p	40626	23p	BFY52	23p	BD918	28p
	OC122	50p	OC122	50p	2N1307	25p	AC127	25p	BS03	38p	BD928	31p
	OC139	25p	OC139	25p	2N2147	74p	AC128	25p	BS	45p	BD938	32p
	OC140	37p	OC140	37p	2N2904A	32p	AC176	25p	BS2	47p	BD94	21p
	OC170	25p	OC170	25p	2N2904A	32p	AC176	25p	BS2	47p	BD94	21p
	OC171	30p	OC171	30p	2N3054	55p	ACY17	30p	BSY29	25p	SD988	46p
	OC172	37p	OC172	37p	2N3054	60p	ACY28	17p	BU100	£1.80p	UA05A	40p
	OC29	62p	OC29	62p	IN21	17p	2N5109	£2.05p	AF118	62p	CR81/20	38p
	OC35	50p	OC35	50p	IN21B	25p	40382	60p	AF127	17p	CR81/30	40p
	OC38	42p	OC38	42p	IN215	60p	40383	60p	AF139	30p	CR81/35	48p
	OC44	17p	OC44	17p	IN43	10p	3F100	87p	AF178	45p	CR81/40	45p
	OC45	15p	OC45	15p	IN70	7p	3PR5	32p	AF186	40p	CR83/05	30p
	OC70	12p	OC70	12p	IN702-72536P	3N128	87p	AFY19	£1.13p	CR83/20	38p	
	OC71	15p	OC71	15p	IN823A	£1.30	3N139	£1.75p	ABY26	25p	CR83/30	43p
	OC72	25p	OC72	25p	IZM75	35p	3N140	95p	ABY28	25p	CR825/025	
	OC73	30p	OC73	30p	IZM710	35p	3N154	90p	ABY67	48p		
	OC75	25p	OC75	25p	IZT15	67p	3N159	£1.45p	BAW19	25p		
	OC76	25p	OC76	25p	IZT10	68p	6PR5	45p	BC107	12p	CR83/40	50p
	OC81	25p	OC81	25p	24385	51p	12FR60	73p	BC108	12p	GET103	23p
	OC81D	20p	OC81D</									

well as for maximum r.p.m. indications mentioned previously for the different number of cylinders.

CONSTRUCTION

The circuit board and component layout is shown in Fig. 2. The board can be quite small and could be either mounted on the back of the meter as shown or installed behind the dashboard by itself but it must be clear of the direct airflow from the car heater


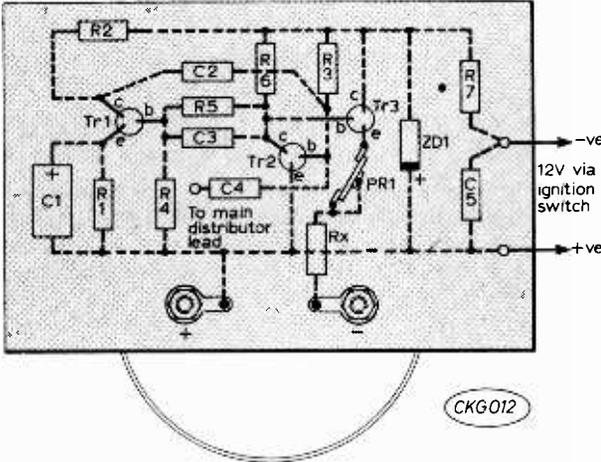


Fig. 2: A suggested component layout. The board is mounted directly on the terminal screws of the meter.

system. In the prototype the board was attached to the back of the meter by the terminal screws. The component layout is not critical and can be altered a little from that shown in Fig. 2. It is most important however, not to connect the common positive supply rail of the circuit directly to either the car body or meter case. The circuit will be effectively 'earthed' via whichever lead, positive or negative, is connected eventually to the car body i.e., via whichever side of the car battery is bonded to the car body. The 12V supply should be taken after the ignition switch.

The only other connection is a length of thin plastic covered wire from the tachometer input C4 which is taken through to the centre ignition lead on the distributor. The end of this wire is wrapped around the centre ignition lead and taped into place as shown in Fig. 3. Between 5 and 10 turns should be sufficient for ignition pulse pick up.

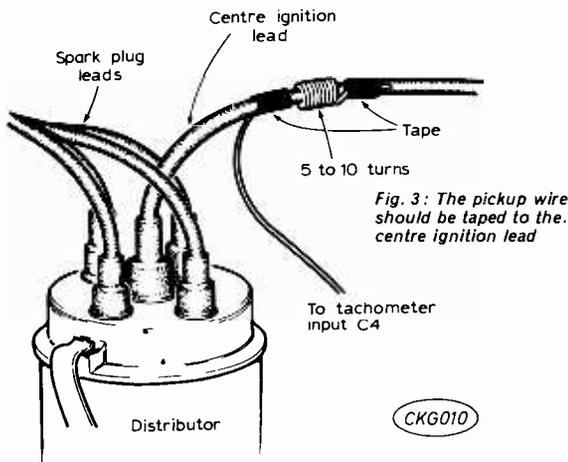

CKG010

CALIBRATION

The ideal method of calibrating the meter is to drive the tachometer from a square-wave audio signal generator. The square-wave should have a peak amplitude of at least 2V and must be differentiated by a simple RC network as in Fig. 4. The output will

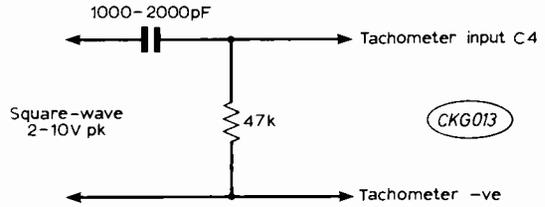


Fig. 4: The differentiating circuit for calibration.

be a series of positive and negative going pulses. The tachometer will respond to the positive going pulses only. It is essential to understand that when the tachometer is driven from a car ignition system (from the centre distributor lead) it will receive either four, six or eight pulses for *each* revolution of the engine, depending on the number of cylinders. The engine r.p.m. will therefore be the number of pulses per minute divided by the number of cylinders. For example, if the pulse frequency per minute is 10,000, the r.p.m. for a 4 cylinder engine would be 2,500. For calibration with a signal generator it is easier to work with pulses per second, so in order to set the tachometer scale for say 2,500 r.p.m. the generator frequency is set to

$$\frac{10,000}{60} = 166.6\text{Hz.}$$

It would be easier of course to set the generator to an even frequency so, for example, 200Hz would be equal to 12,000 pulses per minute (200×60) or $12,000/4$ which equals 3,000 r.p.m. for a 4 cylinder engine.

★ components list

Resistors	
R1 1.8k Ω	R6 4.7k Ω
R2 4.7k Ω	R7 820 Ω
R3 15k Ω	Rx see text
R4 39k Ω	PR1 1k Ω skeleton preset
R5 10k Ω	
All resistors 10%, 1/4W types	
Capacitors	
C1 200 μ F	C4 1000pF
C2 0.04 μ F	C5 0.05 μ F
C3 0.01 μ F	
Semiconductors	
Tr1 OC45	ZD1 NKT/C8V2 or BZY88/C8V2 (Electrovalue)
Tr2 OC45	
Tr3 OC45	
Miscellaneous	
0.1mA f.s.d. meter—see text, prototype type LS65, 240° (Henry's Radio); circuit board; case to suit.	

Most meters, including the 240° type, will have calibration marks of 0 to 10 which is convenient for either 0-5,000 or 0-10,000 r.p.m. The meter scale can of course be taken out and new figures inscribed.

A scale of 0-8,000 would mean providing new calibration marks of 0.8 i.e., the scale must be divided into 8 equal parts. The maximum r.p.m. range must therefore be decided and the meter scale marked accordingly.

Having done this the instrument can be calibrated and to assist in this the following tables relate r.p.m. to frequency and number of cylinders.

Four Cylinder Engines

Engine R.P.M.	Pulses per minute from ignition	Generator Frequency (Hz)
500	2,000	33.3
1,000	4,000	66.6
1,500	6,000	100
2,000	8,000	133.3
2,500	10,000	166.6
3,000	12,000	200
3,500	14,000	233.3
4,000	16,000	266.6
5,000	20,000	333.3
6,000	24,000	400
7,000	28,000	466.6
8,000	32,000	533.3
9,000	36,000	600
10,000	40,000	666.6

The suggested calibration checks for 0-5,000 r.p.m. are as follows:— Set the generator to 200Hz and adjust PR1 to obtain meter reading of 3,000 r.p.m. Set generator at 100Hz and check that meter is reading 1,500 r.p.m. If not, slightly re-adjust PR1 and check again for reading at 3,000 r.p.m. Much the same procedure is adopted for higher maximum r.p.m. readings i.e., for 8,000 r.p.m. full scale use a 400Hz test signal and set PR1 for a reading of 6,000 r.p.m. and check with 200Hz for a reading of 3,000 r.p.m. For a 10,000 r.p.m. maximum set generator to 600Hz and PR1 to obtain meter reading of 9,000 r.p.m. Recheck at 3,000 r.p.m. with 200Hz.

Six Cylinder Engines

Engine R.P.M.	Pulses per minute from ignition	Generator frequency (Hz)
500	3,000	50
1,000	6,000	100
2,000	12,000	200
3,000	18,000	300
4,000	24,000	400
5,000	30,000	500
6,000	36,000	600
7,000	42,000	700
8,000	48,000	800
10,000	60,000	1,000

As the generator test frequencies all come out at even figures the calibration for six cylinder engines for any maximum r.p.m. reading of up to 10,000 is quite easy but a similar procedure i.e., the initial setting of PR1 for a high calibration reading and then check at a lower one, can be adopted.

No table is included for 8 cylinder engines as the 4 cylinder engine table can be used by simply doubling the test frequencies.

CALIBRATION WITHOUT A GENERATOR

With a square-wave generator a calibration accuracy of better than 1 per cent can be obtained, especially if the generator is first checked for

accuracy against the 50Hz mains frequency with an oscilloscope and Lissajou's patterns.

Reasonable accuracy, however, can be obtained by setting the value of PR1 with an ohmmeter. The table shows the values at which PR1 should be set to obtain 0-5,000, or 0-8,000 or 0-10,000 r.p.m. for a 4 or 6 cylinder engine. For 8 cylinder engines the value of PR1 will be double those of the 4 cylinder ones.

Value of PR1 plus Rx for simple calibration

Max. Revs.	Four Cylinders	Six Cylinders
5,000	180Ω	500Ω
8,000	520Ω	1,200Ω
10,000	800Ω	1,500Ω

In operation the meter needle will waver slightly about the engine r.p.m. reading. Violent fluctuation or erratic indication could be due to ignition pulse pick up being too great, in which case reduce the number of turns of the pick up coil. From tick-over the needle should rise quickly as the accelerator is pressed down. **Don't** rev the engine just to see the tachometer read maximum r.p.m., it won't do the engine any good. For test purposes about half the engine maximum r.p.m. will be sufficient to see that the tachometer reading rises accordingly. ■

CO! CO! CO! CO! CO! CO! CO!

INFORMATION WANTED

- ...any information or circuit literature etc. on the Practical Wireless "Strand" amplifier.—G. A. Hocknell, School House, King's School, Canterbury, Kent.
- ...circuit designs for a car anti-theft device of the tuned circuit or capacitance type.—R. E. Hannah, 16 Winton Way, Rainford, Nr. St. Helens, Lancashire.
- ...Heathkit manual for kit EW-1. To be borrowed or bought for £1.—W. Amman, 1 Montague Avenue, London, S.E. 6.
- ...any gen on where I may obtain 5 dust cores for the i.f. transformers for my E.V.R. Radio-Packa Gram.—K. Gibbs, 10 Hayston Ple., North Road West, Plymouth, Devon, PL1 5DU.
- ...information or circuit details and power requirements for the BC-433G and BC-434A radio and direction-finding equipment.—D. Eaton, "Glenfield", Le Foulton, St. Andrew's, Guernsey, C.I.
- ...valve line-up and any relevant data, circuit diagram etc. on the Marconi 219 serial number 942995 receiver which is 20-25 years old. This is needed to help some boys in their school project.—B. C. Matthews (Senior Physics Master) Roan Grammar School for Boys, Maze Hill, Blackheath, London, S.E. 3.
- ...information on converting to stereo the Dansette RG 31 radiogram. It has a stereo-wired autochanger.—R. C. Emery, Kelsall, Saxmundham, Suffolk, IP17 2PA.
- ...instruction book for my Geloaso communications receiver also the address of Geloaso in Italy; the model No. is G207 DR and the serial No. 838 H.—A. G. Tewes, 17 Queens Road, Luton, Chatham, Kent.
- ...circuit diagram and component list for F. J. Camm's Superhet Coronet 4 (a.c.)—G. L. Perkins, "Pensith", High Street, Porlock, Nr. Minehead, Somerset.
- ...information, handbook, etc., of the Kuba German radiogram. Imperial chassis 612.—F. C. Dillien, 20 Hamden Crescent, Fritland Lane, Dagenham, Essex.
- ...any gen at all on the receiver type R3003 Ref. 10db/2.—John Hutcheon, c/o Walter Hannah, High Altercannoch, Barrhill, Giruan, Ayrshire.
- ...service sheet for a Bush TV135R valved version TV.—J. D. Mendham, 12 Henton Road, Edwinstowe, Notts.
- ...any gen on scope tube DG7-5.—C. R. Follenfant, 4 Ash Road, Shirley, Croydon, Surrey.
- ...circuit diagram, alignment information and operating instructions for the Lafayette KT 320 communications receiver.—A. D. Temple, 56 Wood Road, Chorlton, Manchester.
- ...instruction books and spares for the Invicta 500 and 300 a.c.—Ralph Hamilton, Ballyhelmore, Tandragee, NI.
- ...any technical information regarding the photomultiplier tube type 931A.—A. J. Dickinson, 22 Kensington Place, Brighton, Sussex, BN1 4RJ.
- ...any information, diagrams, etc., on Pamphonic type 601F amplifier with 2 x EL34, one U56 and six other valves. Also any of the following issues of P.W.: June 1966, July 1964, June and January 1963, December 1962, September 1962 or earlier.—M. McLean, Stamford Villa, Station Avenue, Haddington, East Lothian.
- ...any details of the power transformer of the Coscor scope model 1039 Mk. 2.—David Snodley, 9 Alexandra Park Avenue, Belfast BT 15ER, N. Ireland.
- ...the book entitled "Oscilloscope Equipment Circuits" by Easterling (Norman Price—out of print). Will buy or borrow.—F. D. Cosgrove, Rowan Chalet, Lower Road, Postcombe, Oxford, OX9 7DU.

ISSUES FOR DISPOSAL

- ...P.W. for May 1969 to December 1970. Offers please to N. J. Moore, 33 Highcliff Drive, Leigh-on-Sea, Essex.

Items in this section are carried free of charge as a service to readers. We only ask that those making use of the service answer all correspondence resulting and reimburse postage and all reasonable expenses. We cannot guarantee inclusion and requests for inclusion will not be acknowledged. Material for inclusion should be sent to Practical Wireless Editorial, Fleetway House, Farringdon Street, London, E.C.4.

BI-PRE-PAK



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 50p

8 RELAYS FOR £1
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

NEW TESTED AND GUARANTEED PACKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V. 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncoated black glass type PNP Germ.	50p
H19	10	OC81/81D uncoated white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncoated TO-5 can	50p
H29	20	OA47 gold bonded diodes coded PCS2	50p

NEW UNMARKED UNTESTED PACKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1/2/3/706A, BS195A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1½ watt Zeners Top hat type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers. 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

4p		6p	
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
AC177	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC107	0-13	2N1308-9	0-35
BC108	0-13	2N3819FET	0-45
BC109	0-14		
BF194	0-15	Power Transistors	
BF274	0-15	OC20	0-50
BFY50	0-20	OC23	0-30
BSY25	0-57	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-15	AD149	0-30
OC41	0-13	AU110	1-25
OC44	0-13	2S034	0-25
OC45	0-13	2N3055	0-63
OC71	0-13	Diodes	
OC72	0-13	AA42	0-10
OC81	0-13	OA95	0-19
OC81D	0-13	OA79	0-09
OC83	0-20	OA81	0-09
OC139	0-13	IN914	0-07
OC140	0-17		

F.E.T. PRICE BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each.



BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BS126-29, BS195A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 6p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested. 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

1 amp Miniature Plastic Diodes:

IN4001, 500+ at 4p each; 1,000+ at 3p each.
IN4004, 500+ at 5p each; 1,000+ at 3p each.
IN4006, 500+ at 6p each; 1,000+ at 5p each.
IN4007, 500+ at 8p each; 1,000+ at 7p each.

FREE CATALOGUE AND LISTS FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS & SUBSTITUTION CHARTS



CLEARANCE LINES

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each
post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
Matched Sets of OC45's 1st and 2nd IF	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7.5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5.1, 8.2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	2-00	1-95	1-80
709C Linear Opp. Amp.	50p	40p	35p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
PA234 1-watt Audio Amp.	1-00	90p	80p
UL914 Dual 2 1/P Gate	40p	35p	30p

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines: B.F.I. Transistor Equivalents and Substitutes 40p

This includes many thousands of British U.S.A., European and C.V. equivalents. The Iliffe Radio Valve & Transistor Data Book 9th Edition; 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

Adapting for SSB Reception

R. F. GRAHAM

FOR amateur band reception a receiver able to resolve s.s.b. (single sideband) signals is essential. This mode of telephony transmission is used almost exclusively on many amateur frequencies.

Home-constructed or commercial receivers which have no b.f.o. (beat frequency oscillator) cannot be used at all for s.s.b. reception. Other receivers, of communications type but not of recent manufacture, will have a b.f.o., but unsuitable injection, or no product detector and as a result, s.s.b. reception may be poor, unsatisfactory, or tricky.

Fortunately it is easy to overcome these difficulties, by constructing a separate b.f.o. or product detector, and inserting it into the circuit. The older type of communications receiver is then generally able to give excellent s.s.b. reception.

TRANSMISSION MODES

Three main modes of transmission are commonly employed on the short wave bands. A receiver can only produce intelligible signals from those modes for which it is equipped to deal.

AM. Amplitude modulated signals are the usual speech and music obtainable with any domestic receiver. The presence of a carrier allows detection with a diode or other detector.

SSB. With single sideband signals the carrier and one sideband are suppressed, only the other sideband being transmitted. This allows the whole transmitter power to give useful signals, instead of power being wasted on the carrier, as in a.m. To resolve s.s.b. the receiver must provide a carrier which can be

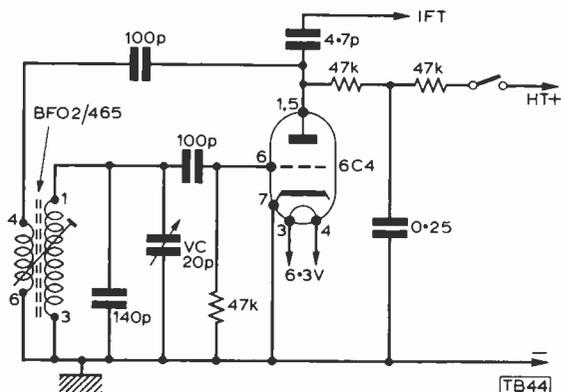


Fig. 1: Simple valve b.f.o. mainly intended to allow reception of c.w. signals.

adjusted in frequency to replace that suppressed before transmission.

CW. CW, or Morse, is a carrier only, interrupted by keying, and the presence of a beat frequency oscillator in the receiver will result in an audio tone. If the receiver has no b.f.o. the same conversion which allows s.s.b. reception will also permit c.w. reception.

BFO

Fig. 1 is a typical b.f.o. circuit for valve receivers, using readily available components. The Denco BFO2/465 b.f.o. coil is suitable for receivers having an intermediate frequency of 455-470kHz. If the circuit is constructed as an addition to a receiver having no b.f.o., the small 6C4 triode is ideal requiring only 0.15A at 6.3V for the heater. When more convenient, one section of a twin triode may be used instead.

The few components are readily assembled on a small chassis or plate. Variable capacitor VC has an extension spindle, or is so placed that it can be controlled by a knob on the receiver panel. The b.f.o.

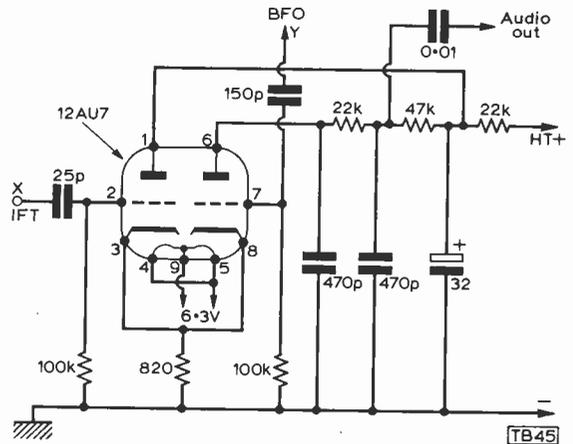


Fig. 2: Twin triode product detector. Used with the b.f.o. it permits satisfactory resolution of s.s.b. signals.

unit is bolted to the main receiver chassis close to the last i.f. transformer.

A 180-250V h.t. supply is suitable. A refinement is to use a stabilised 150V supply, but this is not essential. A switch, anywhere convenient on the panel, interrupts the h.t. supply for a.m. reception.

The circuit is adjusted by placing VC half closed, tuning in a signal, and rotating the b.f.o. coil core until the audible beat falls to zero. Turning VC slightly either way will then cause an audio note which rises in frequency.

For c.w. reception, VC is adjusted to that position which gives best results with the wanted Morse signals.

INJECTION ON SSB


With such a b.f.o., or an older receiver having a similar b.f.o., satisfactory s.s.b. reception is only possible when the s.s.b. signal is weak at the detector. This means that the receiver r.f. gain (and possibly i.f. gain) control must be turned towards minimum

gain, the a.f. gain near maximum. The s.s.b. signal can then be resolved if the b.f.o. frequency is tuned so that it replaces the carrier removed before transmission.

One way to improve matters with the minimum of circuit change is to increase the b.f.o. injection at the final i.f.t. With some receivers, the coupling capacitor (4.7pF in Fig. 1) is of extremely low value, less than 1pF. Changing this to a 3-30pF or similar trimmer will allow increased injection. It is then possible to deal with s.s.b. signals of somewhat greater strength at the detector. The improvement is only relatively slight and insufficient carrier will be available from the b.f.o. to allow the a.m. type detector to deal satisfactorily with strong s.s.b. signals. These, if resolved, will sound like distorted, much over-modulated a.m.


PRODUCT DETECTOR

Fig. 2 is a straightforward standard product detector using a twin triode, cathode coupled, which was found to give very good results with the minimum of difficulty.

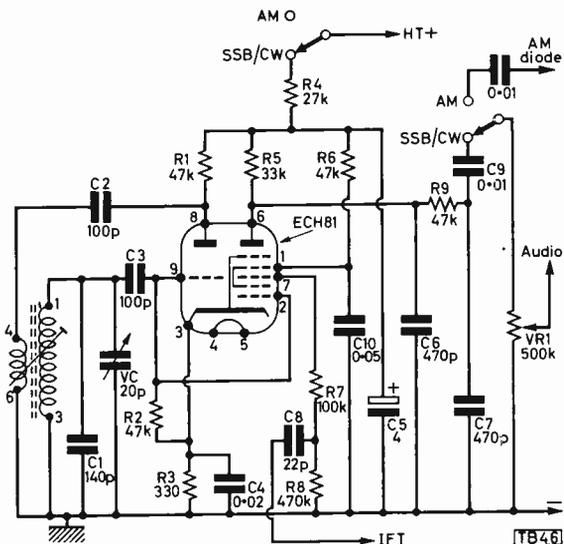

Point X is taken directly to the secondary of the last i.f.t. This tag will have previously been wired to the a.m. detector diode. Point Y is connected to the b.f.o. stage anode. (A few commercial circuits use a tap on the b.f.o. coil for the cathode, with the anode grounded for r.f. In this case, take Y to the b.f.o. cathode.)


Component values were not found to be particularly critical. The 32μF capacitor is to ensure a decoupled and well smoothed h.t. supply. The audio output runs to the volume control on the first a.f. amplifier. This circuit was found to work very well indeed over a wide range of s.s.b. signal strengths, from extremely weak signals barely audible, to those giving much more loudspeaker volume than could be tolerated without reducing receiver gain.

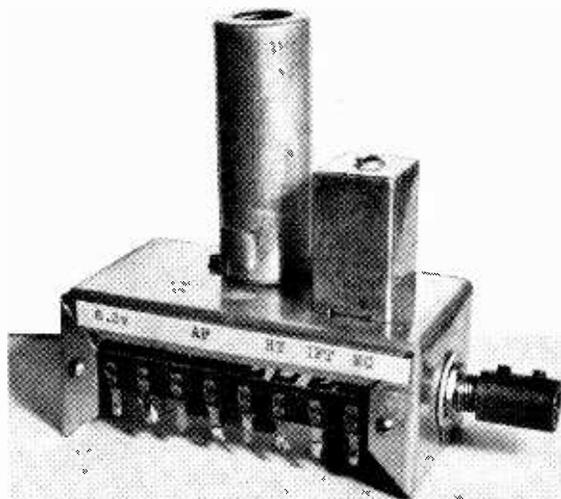

▲ Completed product detector/b.f.o. unit using the single valve circuit of Fig. 3.

◀ Fig. 3: Circuit using an ECH81 as combined product detector/b.f.o.

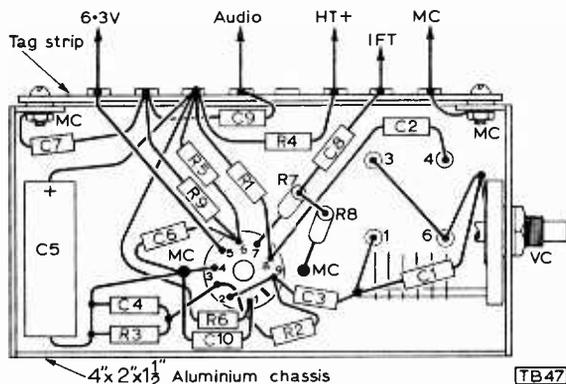▼ Fig. 4: Suggested component layout of circuit shown in Fig. 3.



PRODUCT DETECTOR WITH B.F.O.

The circuit in Fig. 3 has only one valve, an ECH81. B.f.o. injection is to grid 1 of the heptode section, with signals from the final i.f.t. to grid 3. The triode of the ECH81 acts as the b.f.o. oscillator for carrier insertion.

The main advantage of this circuit is that it needs only one valve, and a 2-pole 2-way switch provides for a.m., s.s.b. or c.w. reception. One pole applies h.t. to the ECH81 while the other pole transfers the receiver audio gain control from the usual a.m. detector to the product detector.

All the components may be assembled on a small chassis, Fig. 4 shows suggested construction and wiring. A similar method of building can be adopted with the circuits in Figs. 1 and 2.

The unit is completely wired and tested, then bolted to the receiver chassis, with VC extended

through the panel. The b.f.o. section should be adjusted in the way described for Fig. 1.

TRANSISTOR RECEIVERS

These can be adapted with equal success, and the changes are particularly useful for those receivers which cover several amateur bands.

Fig. 5 is a b.f.o. circuit using a Denco IFT14 coil, for receivers with 465kHz or similar intermediate frequency. A simple method of assembly is to fit the b.f.o. coil, transistor, Z1, resistors and capacitors on a small circuit board, which can be mounted near the 20pF variable capacitor VC, which is attached to the receiver panel. The switch in the negative line cuts the oscillator for a.m. reception and can be located anywhere convenient. The layout should provide a short, direct connection from X to the last i.f. transformer.

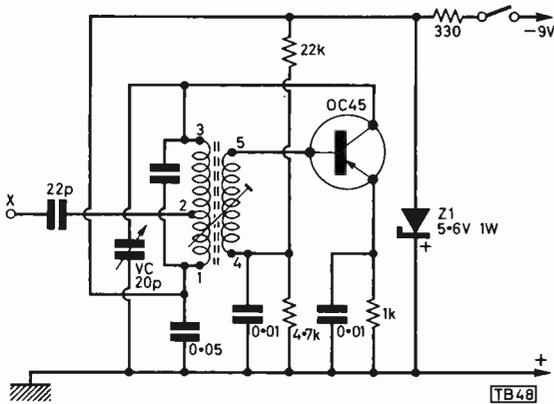


Fig. 5: Circuit of b.f.o. for use with transistorized receiver.

A zener stabilised supply is essential for the oscillator. Most receivers have an audio output stage in which the current drawn fluctuates with the audio signal level and this may cause troublesome frequency modulation effects in the oscillator. The circuit draws about 10mA.

Fig. 5 alone is satisfactory for c.w. reception. It will also provide reception of s.s.b. when the strength of the s.s.b. signal is limited in the way described for Fig. 1. An a.m. signal should first be tuned in and VC set half closed. The coil core is then adjusted as for

Fig. 1 Varying VC then allows best reception of c.w. or s.s.b. signals.

Fig. 6 is a product detector which can be used in conjunction with Fig. 5. It has the advantage of providing a.m. detection when the b.f.o. is switched off, so that no switching of audio circuits is required.

Carrier injection is at Y, from point X in Fig. 5. Signals reach the second transistor via the 100pF isolating capacitor. This connection may be to the primary or secondary of the last i.f.t. in the receiver, according to which gives the better results.

Audio output is taken to the usual audio gain control. Other transistors of similar type may be used, and the supply to this part of the circuit need not be stabilised. With transistor receivers, a diode generally provides a.g.c. and a.m. detection, and this diode can be retained for a.g.c. purposes. In many circuits a 5kΩ potentiometer serving as a.f. gain control is also the diode load resistor. As this is now not available for this purpose, a 5.6kΩ resistor should be substituted.

Most transistor receivers have no manual gain control for the i.f. stages (or r.f. stage, if present) and since such a control is useful for s.s.b., it can be inserted by disconnecting the i.f. stage emitter resistors and adding a 2kΩ potentiometer between this point and the positive line.

NOTES

Some receivers have a 1.6MHz i.f. in which case the appropriate b.f.o. coil must be used (Denco BFO2/1.6).

When adjusting the variable capacitor VC, the b.f.o. must be put on the correct side of the s.s.b. transmission. Speech can then be resolved and VC carefully adjusted for the best results. If VC is altered to put the b.f.o. on the wrong side of the s.s.b. signal no possible adjustment will resolve the signals. The manner of adjusting VC, for upper or lower sideband signals as the case may be, will soon become clear in use. The standard practice is upper sideband (USB) above 10MHz and lower sideband (LSB) below 10MHz.

When making or altering connections to the last i.f.t., alignment may be slightly upset. So a final check should be made of this, and the i.f.t. cores re-adjusted for best results.

In some circuits, the same diode is employed to obtain a.g.c. voltage and a.m. detection. Then when a b.f.o. is added as in Fig. 1, its carrier will produce an a.g.c. voltage, reducing sensitivity. This still arises when a.g.c. is derived from a separate diode, usually with a small capacitor to the last i.f. anode. With a circuit like Fig. 2, the a.g.c. can be left in use. Otherwise a switch may be added, to short the a.g.c. line to earth for s.s.b. or c.w. reception. Communications type receivers generally have a manual control for r.f. gain, i.f. gain, or both. If this is not present in a receiver, it should be fitted. A cathode bias potentiometer is generally employed.

Bandspread tuning, or an excellent slow motion drive, will be found helpful for s.s.b. reception.

Normal circuit precautions should be taken when wiring. The i.f. leads should be short, and clear of earlier i.f. circuits. H.T. and heater leads can run against the chassis. Where a.f. circuits are extended, as for Fig. 3, the leads should be screened, or carefully placed to avoid picking up hum from heater circuits.


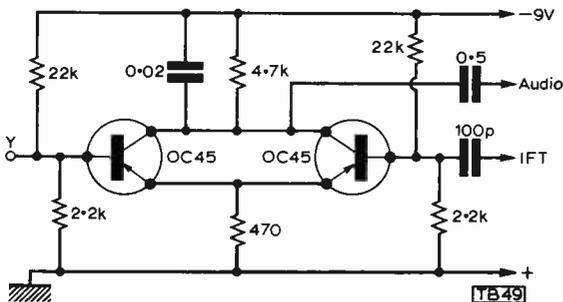


Fig. 6: Two transistor product detector used in conjunction with the b.f.o. of Fig. 5.

FREE INSIDE NEXT MONTH'S...

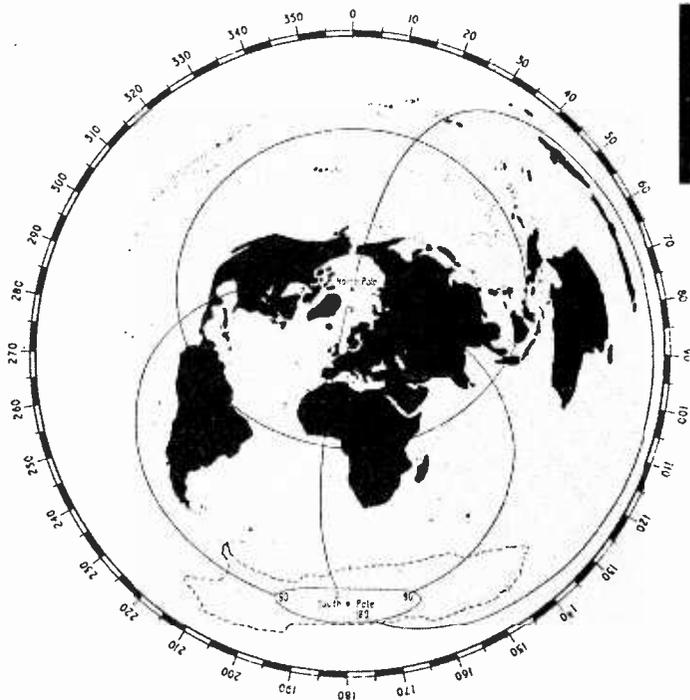

PRACTICAL WIRELESS

DX DATA WALL CHART

Next month your QSL cards will have a companion—our **DX DATA WALL CHART**—and it's one that you'll keep for years. Features include a P.W. Exclusive: a specially designed frequency allocation chart giving all broadcasting and amateur bands, shipping and aeronautical frequencies and a lot, lot more—much of this information has never before been published in this country. **PLUS** a large great circle map based on London to give true distances and bearings together with a World Time table and International Call Sign allocations.

ARTICLES INCLUDE:

the P.W. **CUBE RADIO** 7 Transistor Superhet


With "Novelty Radios" the emphasis is more often on the 'novelty' rather than the 'radio'; the electronics is sacrificed to the appearance. But not in ours. Built into a perspex cabinet, the **P.W. CUBE RADIO** is a full seven transistor superhet receiver giving exceptional performance for its size. Be sure not to miss this one; full details are given to build this ingenious project.

DARKROOM THERMOMETER


We don't want to deride conventional thermometers but from the photographers point of view they leave a lot to be desired in the darkroom. This circuit uses a thermistor and has rapid response, is very easy to read in the worst light and is accurate to within 0.25°C—and all this with a mere handful of components.

CAR RADIO SIGNAL BOOSTER

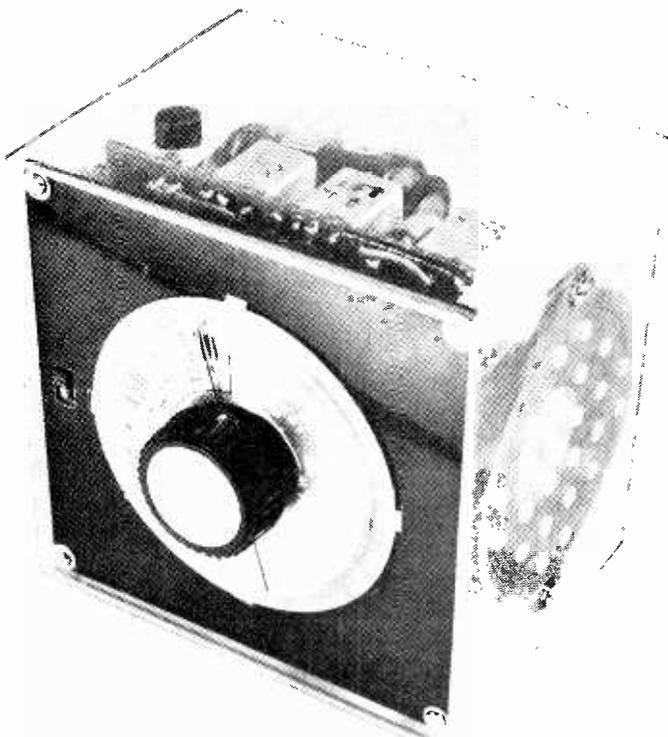This simple amplifier gives a useful improvement in MW and LW reception on any car radio. It has the feature that it is designed for mounting at the base of the aerial to overcome interference pickup. The total cost for this project is something under 50p!



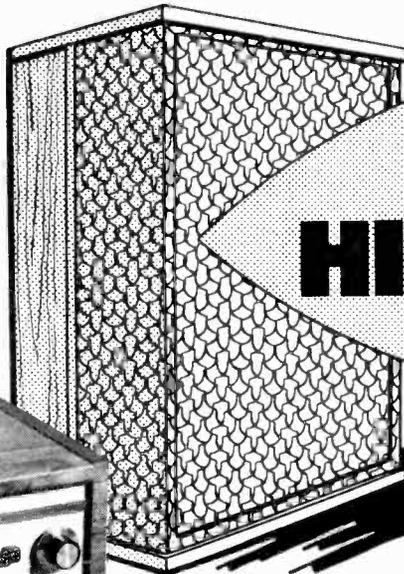**ALL IN THE MARCH
ISSUE ON SALE FEB. 4th.**



Qua
HI-FI S



PART 1



SELECTING the units of a hi-fi system these days is mainly an exercise in economics. The more expensive equipment from any of the many reputable makers will invariably give a good performance as the specification is the prime selling feature in this market. There is a danger not so much of getting poor value for money in the separate units (of the chain turntable-cartridge-amplifiers-loudspeakers) but of budgeting unevenly so that the performance of some links in the chain exceeds that of others. When this happens, the system's performance is somewhat *below* that of its worst component and the unexploited potential of the better units can be regarded as so much wasted money.

There are three basic units in the design to be described. They are:

The plinth which contains the turntable, amplifiers and controls, and *two* identical floor-standing *loudspeaker enclosures*.

Either design may be of interest for use with other equipment, but together they form a well matched system in which no performance is wasted. The three units are finished with teak veneer to match in appearance.

The Plinth

The plinth carries the turntable and separate pickup arm. These are covered by a hinged transparent tinted lid. This props in an open position for changing records and can be closed while playing. Inside the plinth is the power supply for the system, the preamplifiers which are in the form of two plug-in boards, and the power amplifiers. These are a

fairly new type of hybrid Class AB module with a rating of no less than 25 watts r.m.s. each into the correct loudspeaker loads. On the front of the plinth are all the controls for the system, with space provided for future expansion. This might be the addition of an in-built f.m. multiplex tuner, or audio filters.

The Loudspeaker Enclosures

The loudspeaker enclosures are intentionally massive. The author regards their internal volumes of 8 cubic feet as essential to reproducing the full bass content of modern records. A separate woofer and tweeter, fed separately by a crossover network and brilliance control, are used in each enclosure. The enclosures are the infinite baffle type, i.e. are completely sealed. This type is only effective if it is completely airtight, and there is no flexing of the enclosure walls under low frequency sound pressure. To achieve the densest possible structure, the vertical walls are a sandwich of two sheets of hardboard with a $\frac{1}{2}$ in. gap between, packed with fine sand. The top, bottom and speaker mounting boards are solid $\frac{1}{2}$ in. thick chipboard. To minimise internal reflections the interior is heavily damped with carpet felt. The felt is not attached directly to the inner surfaces, but is spaced about $1\frac{1}{2}$ inches away from them by a layer of fibre egg-crate material for better reduction of standing waves. The internal height, width and depth are in the ratios 3:2, again to reduce standing waves. The front and the forward parts of the sides are covered with Tygan fret, other visible parts are veneered in teak.

When the walls are filled with sand, each speaker can hardly be lifted by four men! But the payoff is

lity SYSTEM



C.R. BRADLEY

The system to be described in this series embodies the author's ideas on the best way to spend about £130 on stereo record playing equipment. A fair amount of carpentry is required but no special skill. Constructors may well introduce modifications to the design but if the system is built as described, one will obtain a very high standard of reproduction at a cost so far below that of equivalent commercial equipment (there is nothing sufficiently similar for a direct comparison anyway) that the saving is hard to calculate. The best assessment the author can offer of the pleasure the system provides is that he has not yet heard any commercial equipment for which he would care to swap his system.

that with a good stereo record, the complete orchestral volume can be reproduced with a bass realism that is truly free of resonance, boxy-ness or boomy-ness. Midrange and treble performances are also very satisfactory, with no harshness. The speakers have a crisp presence which can be modified by a 6-position Brilliance control for best stereo directionality in a particular room.

Construction of the Loudspeaker Enclosures

Each identical enclosure is based on a skeleton frame made up from nominally 1in. square pine, which when bought usually turns out to be nearer $\frac{7}{8}$ in. square—see Fig. 2. Saw the lengths listed as accurately as possible with the ends square. No difficult joints are required, the pieces being simply butted together and fixed with countersunk $1\frac{1}{2}$ in. woodscrews at the ends.

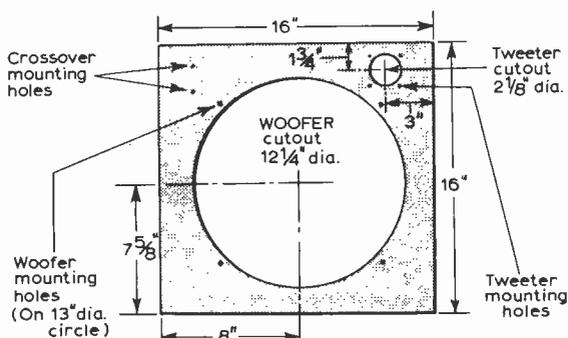


Fig. 1: Speaker mounting board, rear view.

The speaker mounting board is cut from 1in. chipboard to suit the units specified—see Fig. 1. The large cutout for the woofer is easiest made with a jigsaw, or more laboriously by drilling holes around the circumference and knocking out the middle. Use wood that is perfectly flat or the woofer chassis may be irreparably distorted when it is screwed down. The board should fit snugly in the centre of its aperture in the frame. The join at the top must be airtight, which is ensured by gluing a strip of wood ('S' in Fig. 1) along the outside of the join; this piece also keeps the top edge of the fret straight.

The inner hardboard sheets can now be fitted. These must be cut accurately or there will be problems of inward sand leakage. They are screwed from the inside to the frame by screws every 6 inches approx. Their vertical edges simply butt together and these joints must be made sand-tight by a wide strip of adhesive tape (e.g. 2in. Tuftape) stuck along the *outside* i.e. just behind the four corner verticals. Drill the small hole for the speaker leads at the centre of the inner rear sheet.

Cut out the outer hardboard sheets, again accurately. Make an appropriate cutout in the rear sheet at bottom centre for a small aluminium panel to carry the terminals and the brilliance control; this is made up along the lines indicated in Fig. 3. Mount the panels in place, without sand, and fix with countersunk screws every 6 inches approx. Paint the entire front of the enclosure and the forward 10in. of the sides matt black so the speaker cutouts will not be visible after the fret is fitted.

Next cut out and fit the top and bottom pieces (both 1in. chipboard). Screw down firmly and check that the fit is reasonably airtight, planing the surfaces if necessary.

Sand Panels

The sand filling can now begin. The sand used is fine beach sand, usually available from seed merchants. The author used 'real' beach sand but this had first to be dried thoroughly (in the kitchen oven!) and sifted free of pebbles. The filling must be done as follows to minimise the strain on the enclosure structure.

QUALITY HI-FI SYSTEM—SPECIFICATION

PLINTH SPECIFICATION

PREAMPLIFIERS (two)

General: Each preamplifier consists of a circuit using four silicon planar transistors and is wired on a piece of Veroboard which plugs into a 24-way edge connector.

Frequency response: 10Hz to 30kHz (—3dB points)

Disc equalisation: RIAA microgroove standard

Signal-to-noise ratio: Better than 80dB

Input impedances and sensitivities: (for 400mV output)

TUNER: 150mV into 500k Ω

DISC: 4mV into 47k Ω

AUXILIARY: 300mV into 500k Ω (Alternative sensitivities possible e.g. to suit crystal or ceramic devices)

Tape output: 3.5mV into 10k Ω , 350mV into 2M Ω

Distortion: Below 0.15% (on 400mV output); at least 20dB overload possible (i.e.: 4V output) without serious distortion.

Tone controls: Baxandall type giving approx. 20dB max. boost and cut at 20Hz and 20kHz

AMPLIFIERS (two)

General: Each amplifier is a Sanken SI-1020A hybrid module containing a complete single-ended push-pull Class AB amplifier on an isolated heat sink. (6 transistors).

Frequency response: 20Hz to 100kHz

Output power into 8 ohm load: 25 watts r.m.s. continuous, approx. 40 watts peak.

Distortion: Below 0.1% at usual listening levels (see graph)

Short circuit protection: Can be adequately protected by a 1 amp power fuse.

FRONT PANEL LAYOUT

RADIO - DISC - AUXILIARY, VOLUME, TREBLE, BASS, BALANCE, Stereo headphone outlet, Pilot lamp, OFF - HEADPHONE - SPEAKERS.

REAR PANEL

Stereo radio, auxiliary and spare inputs, and stereo tape recorder output (all phono sockets).

Left, right and common loudspeaker connections (screw terminals)

POWER SUPPLY

General: Unstabilised, silicon bridge rectifier.

Outputs: Separately fused 45V, 1A supplies to amplifiers; 30V (low ripple) to preamplifiers.

ENCLOSURE SPECIFICATION

TYPE: Two-way floor-standing infinite baffle, sand loaded walls.

SIZE: 38in. high x 27 $\frac{3}{4}$ in. wide x 18 $\frac{3}{4}$ in. deep overall approx.

WOOFER:

Type: Baker Major 12in.

Quoted response: 30Hz to 14.5kHz

Flux density: 14,000 gauss

Voice coil: 1 $\frac{1}{2}$ in. diameter, 8 ohm impedance

Main cone: paper with roll surround, fitted with concentric parasitic cone for higher frequencies

Mounting requirements: 11in. diameter aperture, four fixing holes on 13in. diameter circle.

TWEETER:

Type: Eagle MHT10, metal diaphragm with exponential horn type

Quoted response: 2kHz to 18kHz

Flux density: 13,000 gauss

Impedance: 8 ohm

CROSSOVER:

Eagle type CN28, 8 ohm series LC type


Crossover frequency: 3kHz

BRILLIANCE CONTROL:

Six-position resistive attenuator, unmatched.

Lay the enclosure on one side. Remove the uppermost panel and use rubber solution or putty to seal any possible leakage points in the two sand compartments revealed. Ensure that all the other panels are screwed on firmly to give strength to the structure. Fill the compartments with fine sand and level off. Replace and screw down the outer panel checking that no sand is trapped between it and the frame to spoil the seal. Also be sure no sand enters the screw holes or the screws may break; steel screws are preferable to brass for this reason. Tip the enclosure on

its back, supporting it as necessary to avoid crushing the rear terminals and brilliance control. Remove the outer front panel and fill the compartments with sand as before. Next fill the remaining side, and lastly the back. At this stage the connecting wires can be laid through the sand from the aluminium panel to the hole in the inner rear panel, which must be sealed with rubber solution to prevent inward sand leakage. Before fitting the back, be sure that the brilliance control switch is well sealed against sand ingress by means of a polythene bag or something similar.

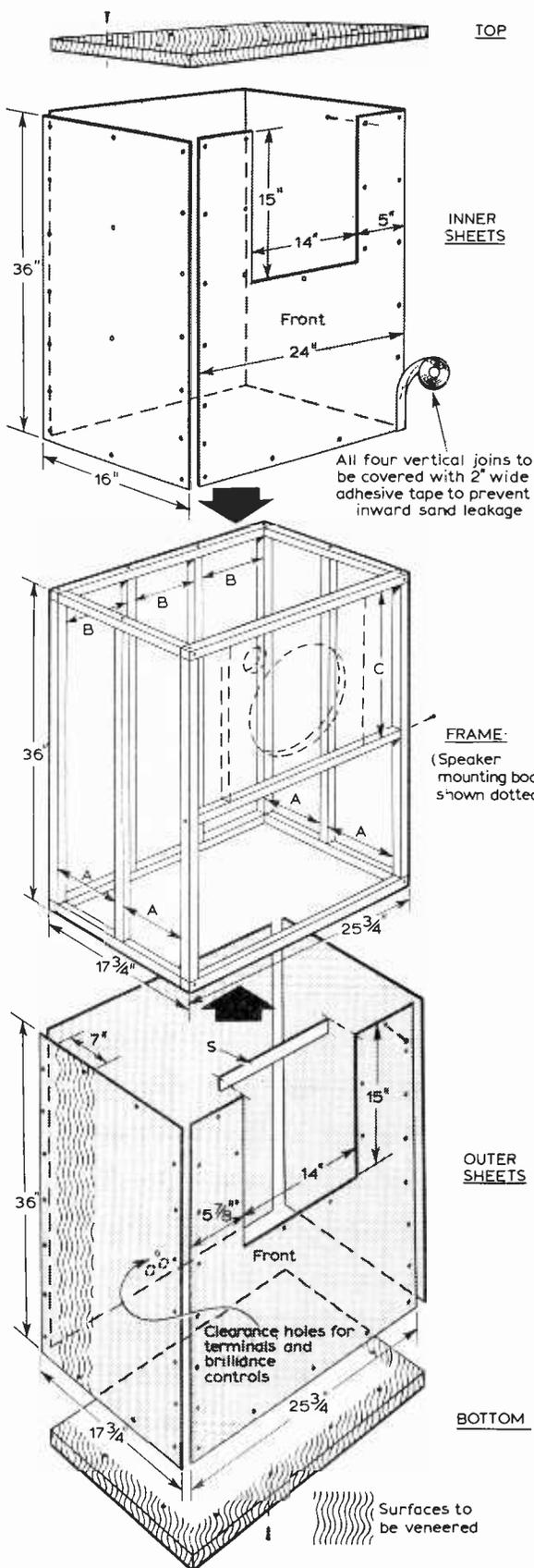

Material:
 27 $\frac{1}{4}$ in. \times 18 $\frac{1}{4}$ in. \times 1in. chipboard
 Fix to frame with 1 $\frac{1}{2}$ in. countersunk woodscrews.
 Front and side edges protrude 1in. approx. Fit must be airtight (see text).

Material:
 2 off 36in. \times 24in. \times $\frac{1}{4}$ in. hardboard
 2 off 36in. \times 16in. \times $\frac{1}{4}$ in. hardboard
 Fix sheets to frame with 1in. countersunk woodscrews, screwed from inside. Drill small hole at centre of rear sheet for speaker wires.

Material:
 8 off 34 $\frac{1}{2}$ in. \times $\frac{7}{8}$ in. \times $\frac{7}{8}$ in. pine (verticals)
 4 off 25 $\frac{3}{4}$ in. \times $\frac{7}{8}$ in. \times $\frac{7}{8}$ in. pine
 1 off 24in. \times $\frac{7}{8}$ in. \times $\frac{7}{8}$ in. pine
 ($\frac{7}{8}$ in. \times $\frac{7}{8}$ in. bought as nominal 1in. \times 1in. pine)
 A = 7 $\frac{9}{16}$ in., B = 7 $\frac{1}{2}$ in., C = 16in.
 Fix joints with 1 $\frac{1}{2}$ in. countersunk woodscrews.

Material:
 2 off 36in. \times 25 $\frac{3}{4}$ in. \times $\frac{1}{4}$ in. hardboard
 2 off 36in. \times 17 $\frac{3}{4}$ in. \times $\frac{1}{4}$ in. hardboard
 1 off 14in. \times 1 $\frac{1}{2}$ in. \times $\frac{1}{4}$ in. wood or hardboard (S)
 Fix sheets to frame with 1in. countersunk woodscrews (steel preferred—see text), screwed from outside. Glue strip S over joint at top of speaker mounting board to make airtight.

Material: as Top section

Fig. 2: Construction details of loudspeaker enclosures.

Mount the woofer, tweeter and crossover, and connect them as shown in Fig. 4. This is a convenient stage at which to start running the speaker since the sound vibration will help shake down the sand. For the woofer the manufacturer recommends a 'running in' period at less than full power. The sound quality will not be good until the damping material is fitted as follows.

Obtain some large corrugated fibre (not plastic) egg-crates such as most grocers throw away. Glue these over the whole inside area of the enclosure including the top and bottom pieces, but not the speaker mounting board. Allow plenty of ventilation as the glue vapour might possibly be harmful to the woofer. The egg-crate alone provides some acoustic damping but it serves mainly to space the carpet felt away from the inner walls. This felt should be the


heaviest grade obtainable and most carpet dealers will have suitable offcuts. A single piece can be used for the whole enclosure apart from the top piece. Fix the felt in place by tacking down the edges all round so the egg-crate volume is sealed off.

Again check the fit of the top and bottom pieces for airtightness. The danger here is that the weight of the sand may have warped the frame. If necessary a thin strip of expanded polystyrene or draught excluder can be used to pack any gaps. Once airtightness is ensured the enclosure is functionally complete.

The author decided to cover as much as possible of the enclosure with Tygan loudspeaker fret (maroon/gold pattern). A 36in×54in. piece of this is enough to cover the whole of the front and part of the sides. This is cut into three pieces and glued to the panels

continued on p 911

Fig. 3: Theoretical diagram showing loudspeaker enclosure circuitry.

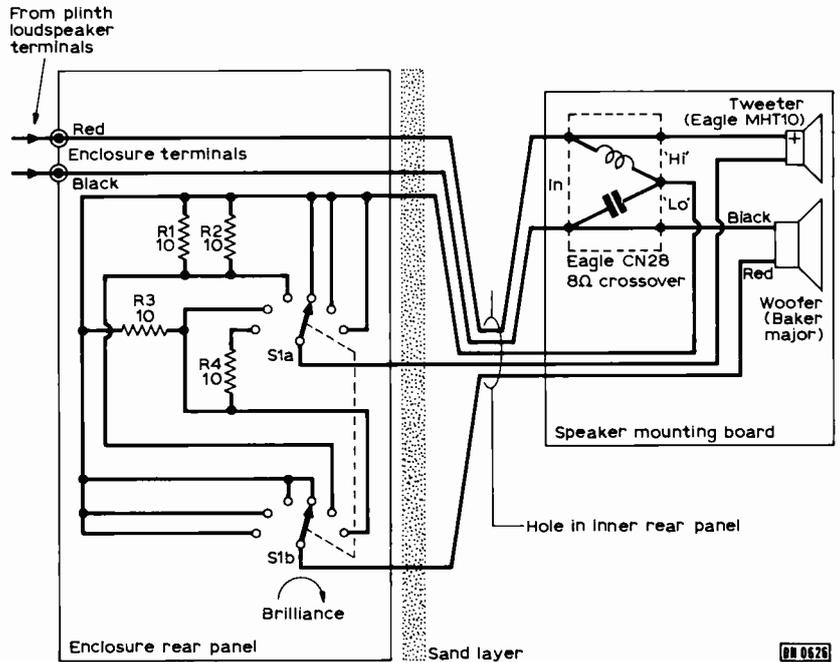

DN 0626

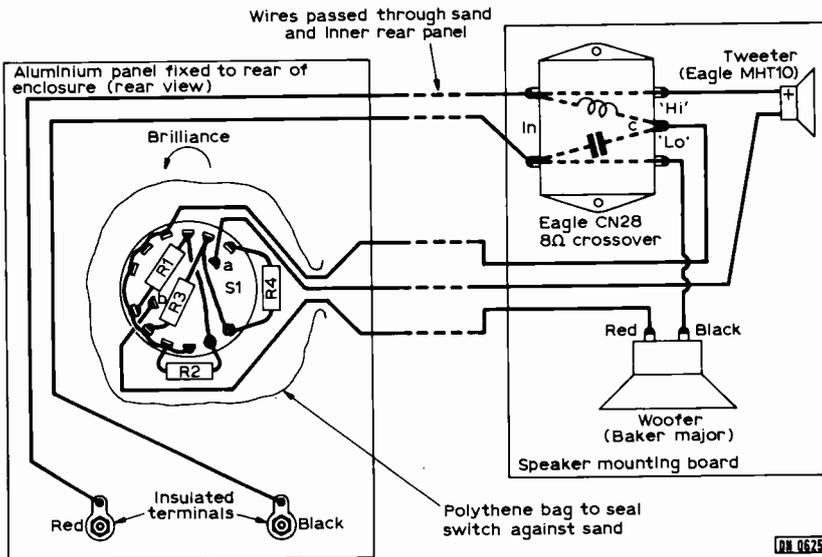


Fig. 4: Wiring details of each loudspeaker enclosure. Observe polarity of woofer and tweeter connections for correct phasing.

DN 0625


SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, ecutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE \pounds 10-50. P. & P. 25p.

r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, ecutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE \pounds 10-50. P. & P. 25p.

DE LUXE STEREO AMPLIFIER

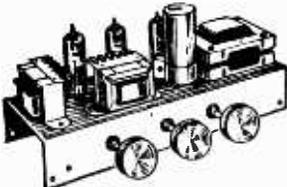

A.C. mains 200-240 V. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4". Overall height including valves 5". Ready built & tested to a high standard. PRICE \pounds 28-92 P. & P. 45p.

Valve line up:—2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4". Overall height including valves 5". Ready built & tested to a high standard. PRICE \pounds 28-92 P. & P. 45p.

SPECIAL PURCHASE OF MANUFACTURERS SURPLUS! All Transistor P.M. tuner head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive, P.M.R.F. Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s output) with optional AFC connection. Built on printed circuit panel and fully screened. Extremely stable over range 88-108Mc/s. Brand new and pre-aligned. Size 2 1/2" x 1 1/2" x 2 1/4". For 6V D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits.



UNITED NUMBER. Only \pounds 2.25 post free. Connection details supplied.

SPECIAL PURCHASE!

BRAND NEW FM MULTIPLEX STEREO DECODERS. Manufactured by PHILIPS. Size 2" x 3 1/2" x 1". All transistor 24v. at 6mA. Supplied pre-aligned with full circuit diagram and connection details. \pounds 4 each. Post Free. **INPUT MATCHING TRANSFORMER.** Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/2" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick up from low to high impedance or vice versa. 75p each. Post Free.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4 in. FIVE for 50p. P. & P. 13p.

TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to 22 1/2 in. approx. Maximum diameter 3in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. Half watt at 1 amp. or 10-0-10, 20-0-20, 30-0-30r. at 2 amps full wave. Size 3in. long x 3 1/2 in. wide x 3in. deep. Price \pounds 1-75 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri 200/240v. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. \pounds 1-38. P. & P. 30p. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 85p. P. & P. 13p.

4 AMP BATTERY CHARGER TRANSFORMER. Brand new. For 6 or 12v. 240V. Primary. Secondary volts rms of load 10v and 16.5v. Overall size approx. 2 1/2" x 2 1/2" x 3". Weight 3lbs. Limited number at \pounds 1-85. P. & P. 35p.

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbledon Tube Station.

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing.
LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER.
With latest mono compatible cartridge \pounds 6-97 Carr. 50p.
With stereo cartridge \pounds 7-97 Carr. 50p.

LATEST GARRARD MODELS. S.A.E. for latest Prices!

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, EL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Choice of Black leatherette or Teak grain finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). PRICE \pounds 5-50. P. & P. 60p.

LATEST ACOS GP81/15C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. \pounds 1-50 P. & P. 8p.

SOMOTONE 9TACH COMPATIBLE STEREO CARTRIDGE
T/O stylus Diamond Stereo LP and Sapphire 78. ONLY \pounds 2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. \pounds 3. P. & P. 10p.

LATEST BOWETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. \pounds 1-68 P. & P. 10p.
LATEST BOWETTE T/O MONO COMPATIBLE CARTRIDGE for mono EP/LP/78 mono or stereo records on mono equipment. Only \pounds 1-50 P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top quality record player amplifier employing heavy duty double wound mains transformer, EC835, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE \pounds 3-75 P. & P. 40p.
ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE \pounds 4-68 P. & P. 50p.

DELUXE QUALITY PORTABLE R/P CABINET MK II.
Circuit motor board size 14 1/2 x 12in. clearance 2in. below, 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE \pounds 4-75. P. & P. 60p.

SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tyran-Clynal front. Size 14 1/2" high x 10 1/2" wide x 3 1/2" deep. Fitter with E.M.I. Ceramic Magnet 13" x 8" bass unit, 2 x 1 1/2" tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE \pounds 8.40 Carr. 65p
Cabinet Available Separately \pounds 4-50 Carr 60p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter \pounds 6-60 Carr. 60p

LOUDSPEAKER BARGAINS
5in. 3 ohm 80p. P. & P. 15p. 7 x 4in. 3 ohm \pounds 1-05. P. & P. 20p. 10 x 6in. 3 or 15 ohm \pounds 1-90. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet \pounds 1-62. P. & P. 20p. E.M.I. 13 1/2 x 8in. 3 ohm with high flux ceramic magnet \pounds 2-10 (15 ohm \pounds 2-25). P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network \pounds 4-20. P. & P. 30p. E.M.I. 13 x 8in. twin cone (parasitic tweeter) 8 ohm \pounds 2-25. P. & P. 30p.

BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly \pounds 5-50. Other models: 20w. \pounds 6-50. 25w. \pounds 8-50. P. & P. 35p. E.M.I. 8in. **HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3 or 8 or 15 ohms 99p each. P. & P. 13p.

12in. "EA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3, 8 or 15 ohm \pounds 2-20. P. & P. 30p. 35 ohm SPEAKERS 3in. only 65p. P. & P. 13p.

"POLY PLANNER" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER. Size 11" x 14" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only \pounds 5-75 each. P. & P. 25p.

PYNAIR & BEXINS SPEAKERS & CABINET FABRICS
ap. 54 in. wide. Usually \pounds 1-75 yd., our price 75p yd. length. P. & P. 15p (min 1 yd.) S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE \pounds 2-95. P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES.
OUR PRICE \pounds 1-05. P. & P. 8p

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.1. Tape, Mike, Guitar, etc. and suitable for push pull valve or transistor equipment. 9.15v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 88p. P. & P. 13p.

CENTRE ZERO MINIATURE MOVING COIL METRE. 100uA. For balance or typing. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.

HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 15p plus large S.A.E.

PRICES:
AMPLIFIER KIT \pounds 10-50 P. & P. 15p
POWER PACK KIT \pounds 2-00 P. & P. 30p
CABINET \pounds 3-00 P. & P. 30p
(Post Free if all units purchased at same time)

Full after sales service.
Also available ready built and tested \pounds 20-50. Post Free.
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Diarhoque use, etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II


Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates EC835, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only \pounds 4-75. P. & P. 35p.

HBL '400UR' AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. \pounds 3-98. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.
FEW ONLY. \pounds 7.75 P. & P.
BARGAIN PRICE 35p

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, EC835, EF86 and E280 rectifier. Simple instruction booklet 15p (Free with parts). All parts sold separately. ONLY \pounds 7-97 P. & P. 55p.

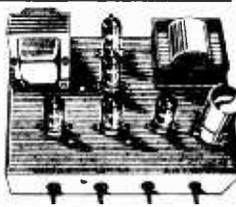

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES
A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985


SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

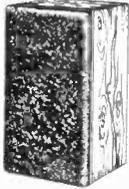All cabinets are new and carefully designed acoustically with speakers mounted on 3/4 in. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.



ELF

An extension speaker of quality; 9 x 5 1/2 x 3 1/2 in. veneered in natural teak with smart gold and mottled Vynair front 3 ohm speaker. The baffle is half inch thick. A real bargain at £1-85 P. & P. 37 1/2p.

THE SHELLEY


Size 21 x 11 x 6 1/2 in.

An extremely elegant speaker system made of 12mm. chipboard covered with teak leathercloth with mottled Vynair front. This unique system uses three ex TV speakers. Carefully matched and tested. Will handle 10 watts and will match 8 ohms impedance, if preferred the speakers can be wired in series parallel to match 3 ohms impedance. A real bargain at £4-95 plus 70p P. & P. MATCHING TRANSFORMER for 15 ohms 85p post free.



VYNAIR

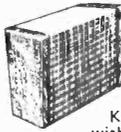Widths from 50 to 54 in., 75p yd. off roll. P. & P. 10p, 1/2 yard 40p. P. & P. 10p. Send 5p stamps for samples.



IMP

Wedge shaped extension speaker 7 1/2 x 6 1/2 x 4 in. (max.). Covered in walnut wood grain cloth with mottled Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only £1.25. P. & P. 36p each

CARTRIDGES-Mono

GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95p. T.T.C. Crystal High Gain, 75p. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7p.

HI-FI STEREO HEADPHONES

Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms. frequency range 30-15,000 Hz 6ft. cord and standard stereo plug. Only £2-57 1/2. P. & P. 27p.

Stereo Headphone Junction Box

Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 2 position switch to give headphones only, speakers only. Only £1-50. P. & P. 12 1/2p.



BOOST THE SOUND

TAPE RECORDERS, RECORD PLAYERS
£2-95 CAXTON EXTENSION SPEAKERS
P. & P. 57p
Makes all the difference to volume and quality. Contains 3 speakers in series—ex-TV with hi-flux magnet recon., tested for Mono or Stereo. Output 8 watts. Impedance 9 ohms. Available in black leathercloth. Size 23 1/2" x 5 1/2" x 5 1/2". Keyhole slot for wall mounting. Twin connecting cable 12yds., 35p min. Matching transformers if required for other output impedance 85p post free.

CLARENCE

11" wide x 8 1/2" x 4 1/2" deep with volume control covered in Black rexine and Mottled Vynair. £2-25 P & P 25p.



CARTRIDGES-Stereo

Sonotone 9TA H/C Diamond £2.40. Ronette S105 Medium Output, £1.40. S106 High Output £1.40. Acos GP93/1 Sapphire, £1.90. GP94 1 Sapphire, £2. TA700 equivalent to B.S.R. SX1M, £1.75. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7p on each.

SPEAKERS

E.M.I. 13 1/2 x 8 in, 3 ohm £2.50, 15 ohm. P. & P. 30p. E.M.I. 13 1/2 x 8 in. fitted two 2 1/2 in. tweeters, 15 ohm £4.50. P. & P. 30p. E.M.I. 13 1/2 x 8 in. (15 ohm) Hi-Fi quality £6.25. P. & P. 35p. Bakers 12 in. 25 watt 8 and 15 ohms £7. P. & P. 30p. Eagle Crossover 86p. P. & P. 5p.

BROADWAY ELECTRONICS


92 MITCHAM ROAD, TOOTING BROADWAY, LONDON S.W.17 01-672 3984
(Nr. Tooting Broadway Underground Station)

(Closed all Wednesday)



S.D.C. FESTIVE

BONANZA

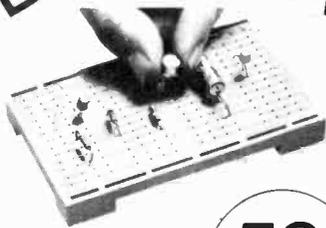

T-DeC
SPECIAL OFFER

50p
OFF

(1) YES! The ideal present for any electronics enthusiast, so do not miss this great opportunity.

(2) JUST TAKE THIS COUPON TO YOUR LOCAL STOCKIST WHO WILL SUPPLY ONE T-DeC for only £2-38

(3) OR in case of difficulty send coupon and cash to:—

S.D.C. ELECTRONICS (SALES) LTD., 34 ARKWRIGHT ROAD
ASTMOOR INDUSTRIAL ESTATE, RUNCORN, CHESHIRE WA7 1NU

Name _____

Address _____

(4) Offer closes January 31, 1972.

GIANT PACK OF HIGH GRADE SILICON DIODES

50 P.I.V. 500mA rating. Glass encapsulated, wire-ended. Not rejects, but unmarked brand new, currently produced devices by a famous manufacturer. Suitable for Bridge circuits; Diode Logic; Electronic Organ applications; Rectifying, Switching, Detecting and Protection circuits; inexpensive Zener applications; and many other uses. Not mixed, all devices are of the same type. At less than one-tenth wholesale price.

PROOPS BROTHERS LIMITED,
The Hyde Industrial Estate, Edgware Road,
London NW9 6JS. Tel. 01-205 8006. Personal
shoppers: 52 Tottenham Court Road, London
W1P 0BA

Pack of
more than
200
only
£1 Post Free

When in LUTON, BEDS, you must visit the
SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes
of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.
Closed all day Wednesday.

SURPLECTRONICS
216 LEAGRAVE ROAD, LUTON, BEDS

separately in such a way that the screws are just accessible, so that the panels can be removed occasionally to top up the sand. All other visible parts of the enclosure are covered with teak veneer. Fig. 5 shows how teak strips and standard corner moulding (itself covered with matching fret) are used to hide the screws at the sides and the join between front and sides respectively. These additions are held lightly in place by dabs of glue so they can be removed easily when required.

During the first month or so of use the sand will shake down and require topping up. This can be done without removing any vertical panels if $\frac{1}{4}$ in. diameter holes are drilled through the frame at the top of each sand compartment.


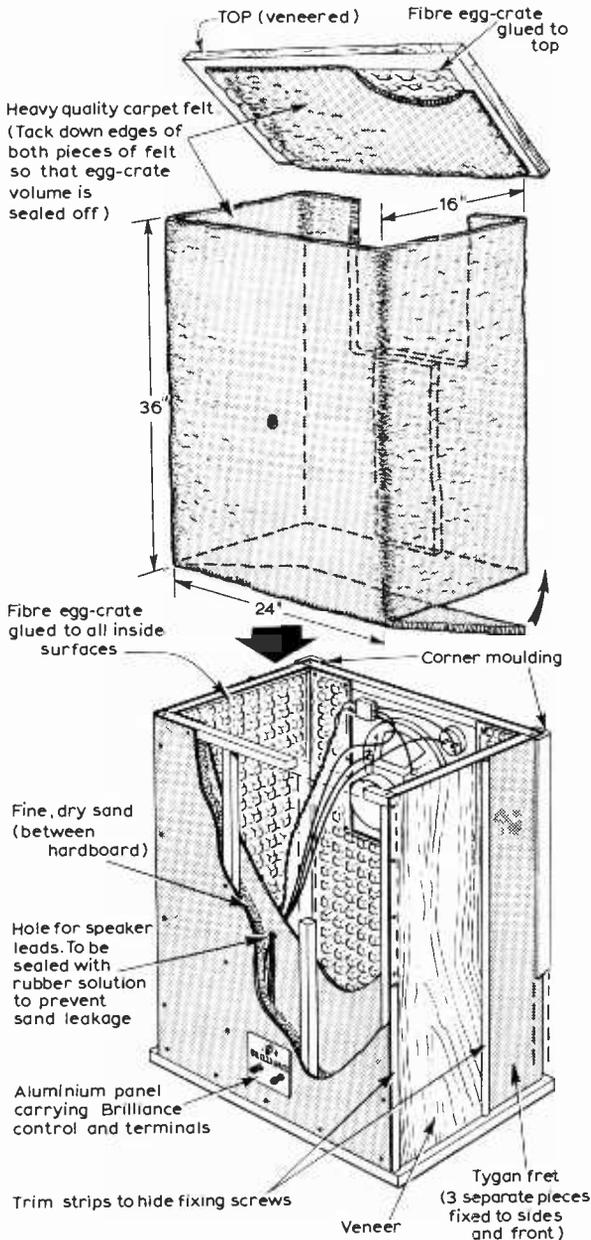


Fig. 5: Cutaway rear view of loudspeaker enclosure showing damping and external finish arrangements.

Crossover

The enclosure circuit is shown in Fig. 3. With the brilliance switch S1 in the position drawn the coil and capacitor in the ready-made crossover unit divide the incoming signal so that high frequencies pass to the tweeter and low frequencies to the woofer. The separation is not abrupt but occurs progressively above and below about 3kHz. The two frequency ranges combine again in the listener's ear so that nothing unusual should be heard. The advantage of a two-way speaker system such as this is that there is less of the intermodulation distortion which arises when a single speaker is asked to reproduce high and low frequencies simultaneously.

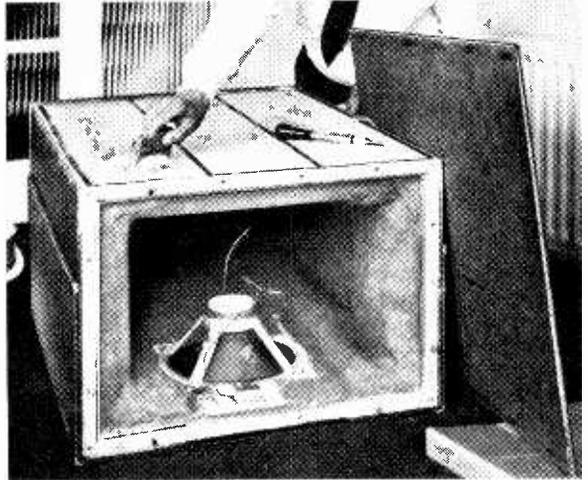


Photograph shows sand filling of a loudspeaker enclosure in progress.

Brilliance Control

The sound heard by the listener will only be satisfactory if the sound levels from the woofer and tweeter are correctly related. Several things can upset this, such as the two units having different efficiencies, the fact that the tweeter is more directional than the woofer so that the listener's position is important, and the acoustics of the room. The enclosures are therefore fitted with brilliance controls which vary the relative sound volumes from the woofer and tweeter. The subjective effect of these controls and their optimum setting for a particular room is usually quickly found. If retarded too much the sound is mellow and poorly located, if advanced too far the sound has excessive 'presence' and may seem harsh. Independent adjustment of these controls may improve the stereo 'spread' obtainable with speaker positioning which is not ideally symmetrical but dictated by the shape of the room.

It may be argued that the brilliance control must upset the action of the crossover whose component values are calculated for 8 ohm speaker loads, since it works by inserting resistance in series with the speakers. However listening tests indicated there was nothing to be gained by using a more theoretically correct version which would maintain correct matching but need many more components.

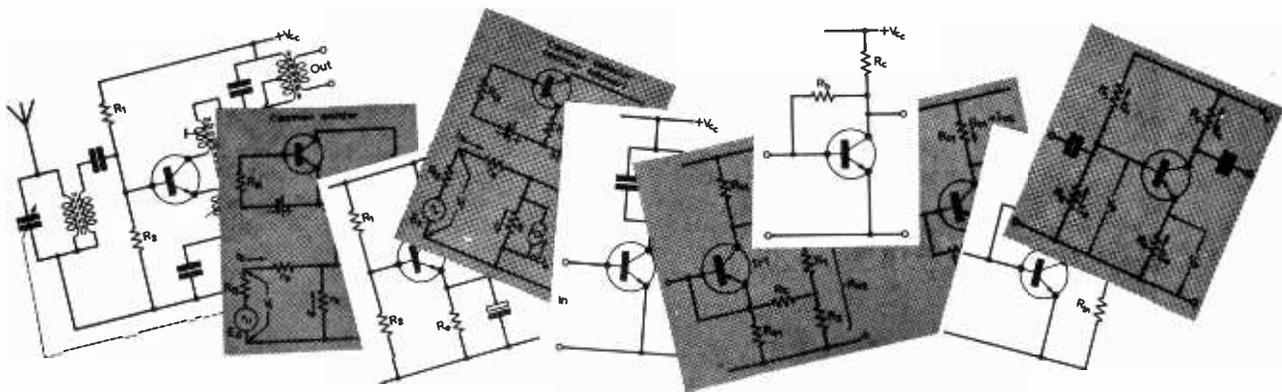Constructional details follow for the plinth next month.



TRANSISTOR CIRCUITRY for beginners

PART 5

H.W. HELLYER & MICHAEL HOLLIER

Circuit Building

Meet Mike. This month, a practical exercise in circuit building, from scratch. My friend and colleague, M. E. Hollier, is an ardent home constructor, and a gifted designer—the sort of chap who pursues a problem to the roots, even to the extent of making his own printed circuits by the photo-resist method. He has compromised to some extent this month, for our benefit, by designing and building the buffer to be described on easily obtainable Veroboard. The device is a high-to-low impedance converter. It can be used to overcome many of those difficult matching problems.

Our brief was to make transistor circuitry clear for the beginner and to be helpful to the more advanced reader. You may be surprised: I have among my correspondents an aircraft fitter who has built an electronic organ in his front room, currently valued at over seven hundred pounds, and a Ph.D. who cannot usefully wield a soldering iron. We must, as our Editor commented in his personal piece a couple of months ago, cast our nets as widely as possible.

To comply with this brief, Mike has torn a few basic circuits to bits, showing what makes them tick. This means that we shall, to some extent, be repeating some of the data I have already expounded: but repetition of salient points helps to fix them in the mind, so I'll make no excuses for that.

After digging a little into the theory, we shall construct the practical circuit, and make this the basis for future designs. The article concludes with some measurements of the constructed device, as much to illustrate the sort of deviations from pure theory that the constructor must learn to expect as to prove that the darn thing really works!

Silicon Planar Epitaxial Transistors

The most modern development in audio bipolar transistors is the silicon planar epitaxial device. We

touched briefly on these in Part 2, underlined their use in Part 3, and now come to the practical problem of using them.

Some possible troubles have been anticipated by the makers. Silicon planar epitaxial transistors such as the BC108 and BC109 that we shall be using this month, have their surfaces protected by a layer of silicon oxide which prevents contamination—which would alter the characteristics.

From the design viewpoint, working with such transistors is made easier because their collector leakage current is almost negligible. Moreover, they are easily obtainable—everybody seems to make a BC109! More about minor differences later.

Parameters

In previous articles, and in the wallchart, a choice of several parameters was given. No, let's be precise—a choice between ways of expressing transistor parameters. Our choice is determined by convenience as much as by an academic ache for accuracy. So we use, this month, the 'h' or hybrid parameter.

Hybrid, in this context, means that the symbols

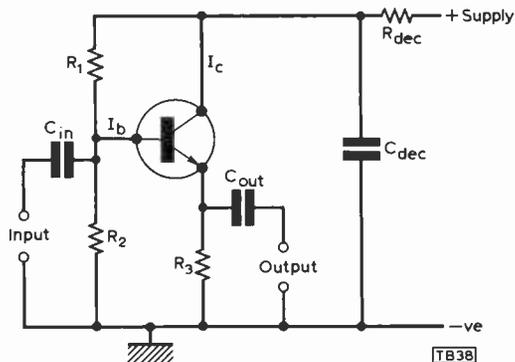


Fig. 20 : Basic single stage circuit. Emitter-follower configuration.

represent a mixture of ratios, impedances and admittance values. (Admittance is impedance upside-down; its reciprocal.)

We use the lower case 'h' as our parameter indicator, and the two subscripts after it indicate either d.c. or large-signal measurements. For example: h_{FE} , or, small-signal, h_{fe} . These will be explained as we need to use them.

In Fig. 20, we see an emitter follower circuit that we have met before. The emitter follower is so called because the input to the stage that comes after it FOLLOWS the emitter of the stage. Alternatively, we could call this a common collector circuit; the collector is common to both input and output signals.

The output signal is taken from C_{out} , the live side with reference to the signal. The input is between the C_{in} live side and the collector. Hence, common collector. But while the earthy side of the input terminals is quite obviously connected to the negative line, we have to remember that the decoupling capacitor, C_{dec} , presents almost a short-circuit to the frequencies we are working with. The collector line is therefore virtually connected to the earth line so far as alternating currents are concerned. Our signal is a.c.: ergo, the collector is common.

Input Impedance

One of the constant bothers is the calculation of input impedance. It seems at first alarming, even when, as in Fig. 20, we know the component values. So we begin, as in Fig. 21, by breaking it down to fundamentals, taking the transistor with its internal resistances, r_b and r_e .

The input resistance of the transistor, looking into the base, in this grounded emitter configuration, is h_{ie} . H parameters again, but h_{ie} simply means input resistance, common emitter mode. Sometimes, we can get this easily from maker's data and there may be a graph so that h_{ie} can be plotted against collector current, I_c . Then the input resistance of the transistor can quickly be found.

If this graphical information is not immediately available, we must have recourse to a bit of simple arithmetic. The internal resistance, r_e , and h_{fe} , the small signal current gain, are what we need at first.

Whereas h_{fe} will almost invariably be specified, r_e and r_b may not. We can take r_e as around 25 ohms in a planar transistor where the collector current is about 1mA. From the known facts we obtain the formula,

$$h_{ie} = \frac{25 \text{ ohms}}{I_c \text{ (mA)}} \times h_{fe}$$

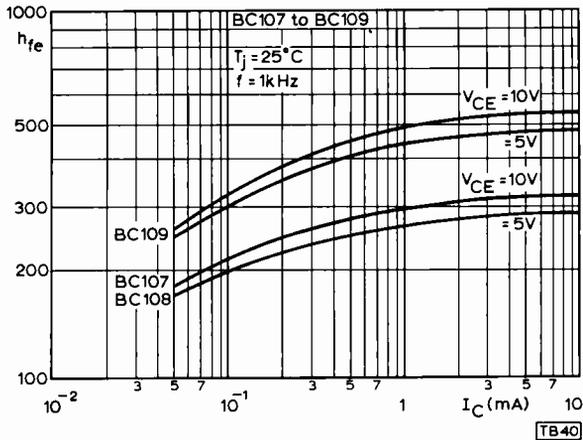
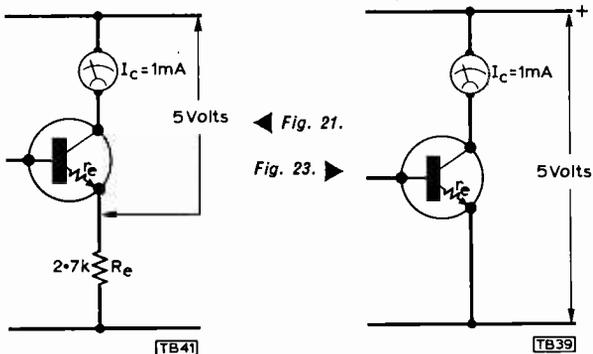


Fig. 22: Typical variation of input impedance and small signal forward current transfer ratio with collector current.

r_b is so small in relation to the result of this formula that it can be ignored for all practical purposes.

If we take a practical example (see Fig. 21), for a BC109 operating at a collector current of 1mA, the voltage between collector and emitter (V_{CE}) being 5 volts. From the data sheet (see Fig. 22) we find that the h_{fe} is 440. Putting this into the above formula, we now have:

$$\begin{aligned} h_{ie} &= \frac{25}{1} \times 440 \\ &= 11,000 \text{ (11k } \Omega \text{ input resistance).} \end{aligned}$$

External R_e

The presence of an emitter resistor in the circuit of Fig. 21 alters the calculations. If we now look at Fig. 23 we see that the voltage reading is still across collector/emitter, but as R_e is not bypassed, the input impedance will increase by an amount equal to the resistive value of R_e , multiplied by h_{fe} . From this, we can construct a formula for input impedance, R_{in} . Since we now have a component external to the transistor, h_{ie} can no longer be applied to this value of input impedance.

Let us take R_e to be 2.7kΩ. Now we get:—

$$\begin{aligned} R_{in} &= (R_e \times h_{fe}) + h_{ie} \\ &= (2,700 \times 440) + 11,000 \\ &= 1188k\Omega + 11k\Omega \\ &= 1.2M\Omega \end{aligned}$$

The input impedance can be increased by the addition of an unbypassed emitter resistor.

Base Bias

Now we develop the circuit by adding base bias resistors R_1 and R_2 in Fig. 24, and a few more voltages have to be considered. Take a collector current of 1mA. Since the base current is very small, we can say the emitter current—for practical purposes—is the same.

So 1mA through the emitter resistor, R_e , which is 2.7kΩ, gives us a volts drop of 2.7V. This is the emitter voltage. To work out the required supply voltage, we take the voltage across the transistor.

V_{CE} and add to it the 2.7 volts across R_E . Answer: 7.7V.

There is an irreducible voltage between base and emitter of a transistor and in the case of silicon transistors, this is generally 0.6V. Simple addition gives us a base voltage of $0.6 + 2.7 = 3.3$ volts. The base to collector voltage must therefore be $7.7 - 3.3 = 4.4$ volts.

In this form of potential divider biasing, to maintain stabilisation of the circuit, it is normal to have five times as much current flowing through the biasing resistors as the base current of the transistor.

The base current, I_B , is found from the formula

$$I_B = \frac{I_C}{H_{FE}}$$

where H_{FE} is the d.c. current gain of the transistor.

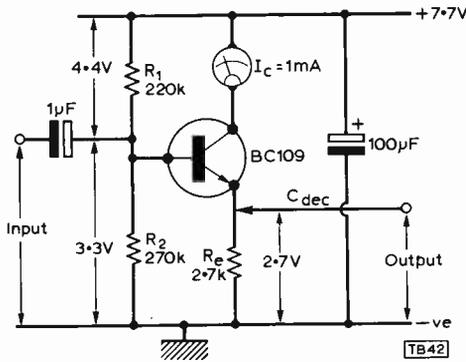


Fig. 24 : The final circuit. Component values are worked out and explained in the text.

For the BC109, with an I_C of 1mA, this is typically 380.

$$\text{So } I_B = \frac{1\text{mA}}{380} = 2.6 \text{ microamps.}$$

Taking a value of five times this we get 13 microamps. So the voltage drop across R_2 is 3.3V, the current 13 microamps and the ohmic value of R_2 must be:—

$$\frac{3.3}{0.000013} \text{ or } \frac{3.3 \times 10^6}{13} = 254\text{k}\Omega.$$

The nearest preferred value resistor would be 270k Ω . A 5% component will do.

A different condition obtains with R_1 , which has the base current of the transistor flowing through it as well as the $5 \times I_B$ which flows through R_2 . So we have a total current of six times I_B . The formula for R_1 is:—

$$R_1 = \frac{4.4}{0.0000156} = \frac{44 \times 10^6}{156} = 211\text{k}\Omega$$

The nearest preferred value is 220k Ω , at 5%.

Stage Resistance

Now that we have the component values, we can calculate stage resistance. Input resistance is what we are interested in here. Remember that as far as

alternating currents are concerned, the top end of R_1 is joined to the lower end of R_2 by the very low impedance of C_{dec} . So the input resistance is effectively R_1 , R_2 and R_{in} , all in parallel. Again applying Ohm's Law:—

$$\begin{aligned} \frac{1}{R_{IN}} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{in}} \\ &= \frac{1}{220\text{k}\Omega} + \frac{1}{270\text{k}\Omega} + \frac{1}{1.2\text{M}\Omega} \\ &= 110\text{k}\Omega \end{aligned}$$

Output resistance is calculated from a combination of R_E , the total input resistance of the transistor and r_e .

Total input resistance presented to the base of the transistor is the parallel combination of R_1 , R_2 and the output impedance of the device which is feeding the input of our considered circuit. The effect of this lumped resistance (R_s) on the emitter circuit is reduced by the h_{fe} of the transistor, i.e. the lumped resistance is divided by h_{fe} .

If the source resistance is one-fifth of R_{IN} , say 20k Ω , then R_s is R_1 , R_2 and the external source resistance, all in parallel, or

$$\begin{aligned} \frac{1}{R_s} &= \frac{1}{220\text{k}\Omega} + \frac{1}{270\text{k}\Omega} + \frac{1}{20\text{k}\Omega} \\ &= 17.2\text{k}\Omega. \end{aligned}$$

This resistance when looked at by the emitter seems smaller, due to h_{fe} :—

$$\frac{R_s}{h_{fe}} = \frac{17.2\text{k}}{440} = 39 \text{ ohms.}$$

This is in parallel with R_E and any external load. If we consider an external load of a minimum value of 20k Ω (and these 'taken' values, throughout, are not just dreamed up; they are 'from life'), then the minimum output resistance would be:—

$$\begin{aligned} \frac{1}{R_{out}(\text{min})} &= \frac{1}{39} + \frac{1}{2.7\text{k}\Omega} + \frac{1}{20\text{k}\Omega} \\ &= 38.2 \text{ ohms.} \end{aligned}$$

In other words, for an input of 100k Ω , our stage has given us an impedance reduction of around 2,500:1.

Coupling Capacitors

A stumbling block to many would-be circuit designers. . . . the value of the capacitor which joins two stages is very important and must be calculated in the following way for optimum performance.

This input capacitor, C_{in} , must have a reactance that is small in relation to the input resistance of the stage, at the lowest frequency we want the stage to handle.

Taking a practical example, if C_{in} was made 0.02 μf , its reactance at little under a 100Hz would be 100k Ω . Since this is the same as the input resistance of the stage, which we have already worked out, a 2:1 attenuator would be formed at the critical frequency, actually 90Hz. In fact, the voltage drop would be 6dB, around half this would fall with decreasing frequency at the rate of 6dB per octave.

If we made C_{out} as low as 0.02 μf and then fed our



3 WAYS

HOME RADIO (Components) LTD.
 Dept. PW, 234-240 London Rd.,
 Mitcham, CR4 3HD. 01-648 8422

of obtaining components *quickly & easily*

1 **CALL AT No. 240
 London Rd., Mitcham**

If you live within easy reach of Mitcham or are in the area at any time do call on us. We are almost opposite Mitcham Baths. We open 9 a.m. every weekday. On Wednesdays we close 1 p.m. and all other days, including Saturdays, 5.30 p.m. On Saturdays we have extra staff to deal with queries. We carry a vast stock of components, and 999 times out of a 1,000 we can immediately lay our hands on the particular item required.

2 **JOIN OUR CREDIT
 ACCOUNT SERVICE**

We began our Credit Account Service about 18 months ago and it has proved extremely popular. Little wonder! Our customers find it a very simple and convenient way of purchasing all their radio and electronic needs. We supply pre-paid envelopes and order forms and no matter how many orders you send us you make only one payment per month. There are several other advantages with our Credit Account Service. Please write or phone for details.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

3 **and
 ORDER BY MAIL
 OR TELEPHONE**

Although we are kept busy selling "over the counter" we supply even more by Mail Order. You can telephone any time of day or night, Sundays included. If you ring out of office hours a recording machine takes your message for us to deal with as soon as we open shop again. Our number is 01-648 8422. If you wish to order by post our address is in the panel at the top of the page. We deal with all orders promptly.



**WHICHEVER WAY YOU
 CHOOSE** you need the
Home Radio Catalogue

In its 315 pages are listed over 8,000 components, over 1,500 of them illustrated. Each copy contains 10 Vouchers, each worth 5p when used as instructed. Free Supplements are supplied regularly to keep you up-to-date. The Catalogue costs 50p over the counter, or 70p including postage and packing.

*Post this Coupon with
 Cheque or PO for 70p*

Please write Name and Address in block capitals.

Name

Address

.....

.....

HOME RADIO (Components) LTD.
 Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD

emitter follower into a 100kΩ input, we would have a 12dB drop at the critical frequency with a falling off equal to 12dB per octave.

Normally, with a circuit of this type, acting simply as a buffer, the low-frequency roll-off will have been determined by associated circuitry.

A value of $C_{in}=1\mu\text{f}$ and $C_{out} 10\mu\text{f}$ are adequate down to a few hertz, even if the load into which the circuit is feeding is as low as 20kΩ.

The load on the circuit should be at least 5 times greater than the output impedance: preferably, ten times.

Decoupling Components

We must consider the practical matter of the available supply voltage and what we have calculated as being desirable. For convenience, a 9-volt battery will do. This could be a PP6, for the current being drawn by this device does not demand a battery of large capacity.

Our circuit calls for a supply voltage of 7.7 volts, so the difference will have to be dropped by a resistor, R_{dec} . The current flowing through this resistor will be the collector current, I_c , which is 1mA, plus the $6 \times I_B$ current in the base bias network. This gives us a total current of 1.0156mA, not significantly far from 1mA to matter.

So, again having recourse to Ohm's Law, we say that:—

$$R_{dec} = \frac{1.3}{1 \times 10^{-3}} = 1,300 \text{ or } 1.3\text{k}\Omega.$$

For our purpose, 1.2kΩ at 5% is enough, but it so happens that 1.3kΩ is a standard value in the E24 resistor series, so if you have one of these available, so much the better.

The decoupling capacitor has to have a low reactance for us to maintain good low frequency response. Another function C_{dec} performs is to bypass any signal currents which may have crept into the supply line from other sections of circuitry. A value ten times greater than C_{out} is desirable.

From this, without further calculation, we make $C_{dec} 100\mu\text{f}$. This gives us a reactance at 20Hz of around 80ohms, which will be quite small in comparison with the minimum a.c. load on the circuit of 20kΩ.

Construction

Fig. 25 should be self-explanatory. Mike chose Veroboard, cutting a portion of a group board to make a 13-way section. This type of board has three copper strips at each outer line, leaving the centre clear. Holes can be cleared with a No. 33 drill (6BA clearance), and relating to the grid of our Fig. 25 holes are first drilled at 2F and 12F for mounting. Next stage is to fit the links, 3B to 4B and 4B to 6B, going around 5B. Link 7B to 8B, and 7B to 6I, using sleeved wire, and the same for 5B to 10B. Link 4I to 5I and 5I to 8I and 9I.

Battery connections are red, positive, to 7J and black, negative, to 5J. Input lead, 'live', 3J with the earthy braid to 4J; output live to 10J, earthy braid to 9J. Finally the BC109 transistor, which should be fitted as shown, to 5A (emitter), 6A (base), and 7A (collector). Components are mounted as shown.

Results

Measurements on the prototype built from this circuit gave an output of 1.85 volts r.m.s. at the onset of clipping. This is equivalent to 2.6 volts peak, the measured emitter voltage on the prototype. A glance at the circuit shows that the emitter voltage, when driven by a sine wave, can swing down to the negative line. This represents a peak negative swing of 2.7 volts.

The positive swing, however, can push the emitter voltage up near collector voltage of 7.7 volts, a peak swing of 5 volts. Since this circuit would only be called upon to handle a few hundred millivolts, this unbalance is only academic—but the point is worth making.

Input impedance measured 105kΩ, output impedance 78.5 ohms with 20kΩ source. Deviations from the calculated value can easily occur due to the spreads in h_{fe} . For example: the h_{fe} spread for a BC109 operating at a collector current of 1mA is from 240 to 960, a ratio of very nearly four to one. Frequency response was within 0.1dB of reference (1kHz) from 10Hz to 100kHz.

The upper limit frequency will be determined by the source resistance of the device being fed into our circuit, and the capacity of the interconnecting cables.

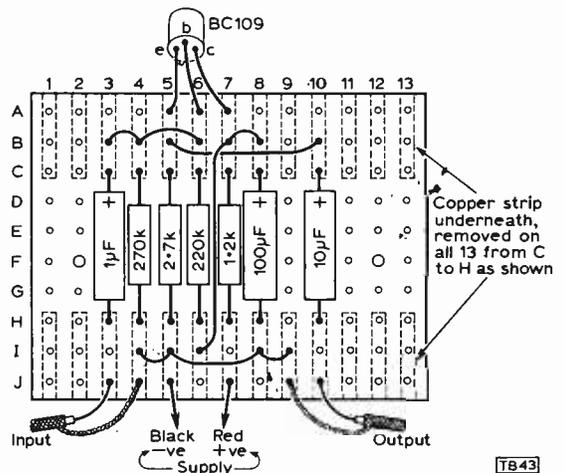



Fig. 25 : Practical layout using 0.15in. matrix Veroboard. Approximately to scale.

Gain, between input and output, is less than unity, a measured 0.98. The object of the exercise is not to get gain but to convert impedances—very often, when doing this, one is also concerned to attenuate, but this is done externally.

Total harmonic distortion is almost too low for measurement with normal workshop instruments. In fact, the figures were as follows:—

Output level	20Hz	1kHz	20kHz
300mV	0.008 %	0.007 %	0.005 %
500mV		0.01 %	
750mV		0.06 %	
1V		0.08 %	

TO BE CONTINUED

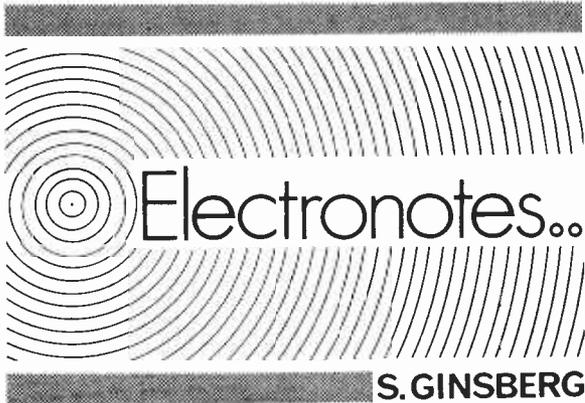

Electronotes..

S. GINSBERG

It seems that there are very few areas where electronics has not penetrated in one way or another. The automobile industry is a natural market for electronics but it seems to be slow in getting off the ground. The home constructor and "amateur" has not been slow to appreciate the benefits, however, and items like windscreen wiper speed controls have appeared in the popular construction journals. For the do-it-yourself man there is a good opportunity to get electronics into his car and to increase the comfort and efficiency. Transistorised ignition is one example and one company, Transmetrix (Research & Development) Ltd., have just launched a tiny transistorised ignition unit which sells for just over £10. It was tested, along with those from other manufacturers, by a leading motor magazine and came out number one. At this sort of price, one wonders how long it will be before the motor car manufacturer fits transistorised ignition as a standard or at least an available option on all models.


Another thing which has a great deal to offer is thick film technology but again it is a thing which has been slow to catch on. Thick film circuitry is achieved by taking an insulating substrate and printing the wiring pattern on it with a special conducting ink using silk screen printing techniques. The circuit is then put on a belt which passes through a special oven which fuses the ink and bakes it.

The inks are composed mainly of glass together with a conductive element. By reducing the amount of conductive material in the ink, the pattern will have a greater and greater resistance dependent upon the amount of conductive material remaining. Thus resistors can be "printed" down in the same way as the wiring. Usually, these resistors have a tolerance of around 15%—good enough for some circuits.


For closer tolerance, down below 1 per cent for example, the circuit is put in a jig and probes measure the actual value of resistance. This is fed to a circuit which compares this actual resistance against the value required. A jet of air plus an abrasive is then fired at the resistor through a tiny nozzle. This erodes away tiny parts of the resistor pattern, gradually reducing the resistance value. When the actual value reaches the required value set up on the resistance bridge, the air/abrasive is automatically switched off.

Capacitors, transistors and integrated circuits may be bonded onto the thick film substrate once the initial pattern has been laid down. By laying down an insulating layer, another pattern may be printed over the top of the first and thus a multilayer circuit can be built up.

Toshiba HI-FI STEREO AMPLIFIERS

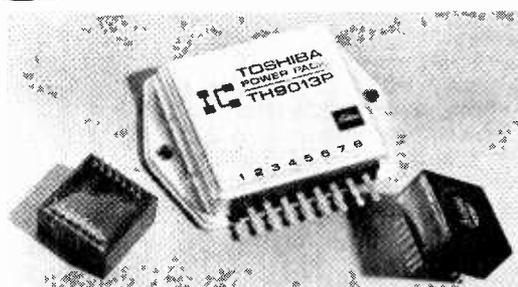

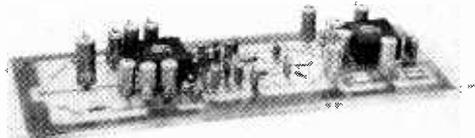We are now supplying a printed circuit board (for the pre-amplifier circuit) to achieve instant success with this fabulous amplifier kit.



A made-up pre-amplifier using 2 x TH9014P & 1 component kit.

Typical distortion level at 1,000 Hz for 20 watts mean power is approximately 0.3% of third harmonic.

Tone controls: 15 dB (typical) cut and lift in bass and treble regions.

Input sensitivity; suitable for 4 mV magnetic pickup.

Output: 20 watts (RMS).

Toshiba —TH9013P 20 watt Hi-Fi Power Amplifier £4.57 each

Toshiba —TH9014P. Pre-Amplifier. Voltage gain 75 dB (typical). Output noise voltage 0.1 mV (typical) £1.50 each.

Printed Circuit Board £1.50 each

Complete Kits of all Capacitors & Resistors, & Ganged Potentiometers £6.95 each

Transformer Kit (Including Rectifier) £5.00 each

Comprehensive instructions, circuit diagrams & suggested layout etc., supplied with each kit.

SEND LARGE S.A.E. FOR DATA

Hawnt

Officially appointed distributors for ERIE, MULLARD, Etc.

HAWNT & CO. LTD., DEPT. PW1
112-114 Pritchett Street,
Birmingham B6 4EN Telephone 021 359 4301

LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents

Buy British

I recently asked at a local radio shop for an OC44 transistor and was offered one marked "Mullard, Foreign Made" and when I asked the price I was told it would be 70p. When I protested at the price I was informed that others I said I could obtain cheaper could only be "seconds".

I tried another radio shop a few miles away and obtained an OC44 marked "Mullard, British Made" for 41p, which the dealer assured me was the correct price according to his list.

Since then, I have had occasion to purchase a volume control, tone control/switch for a well-known continental radio and the price in this case was £1.90 plus 10p purchase tax. A comparable British-made component would certainly not have been more than 50p and apart from this, the printed circuit was in my opinion inferior in workmanship to many Hong Kong made sets costing a fraction of the price this one did.

—R. J. Hall (Penzance, Cornwall).

purpose and I do know they were tried on me with this intention.

Whether they worked or not is obscured by other issues—but none of the people using them had any radio knowledge at all and I am wondering how many of their claims belong to the realm of legends.

I am aware that some years ago, there were reports of odd individuals who claimed that they could receive BBC transmissions without receiving apparatus, but whether such claims have been substantiated, I do not know.

If however, telemetering is a reality, would anyone be kind enough to give me in brief, the principles on which it is accomplished?

I am highly suspicious about claims that I have heard made: particularly since the accepted sense of the word "telemetering" is in connection with recording instruments being read at a distance.—V. D. Butler (Kirkstall Hill, Leeds).

has been unmarked or otherwise of surplus origin, and in several cases your name has been mentioned as the supplier. In addition the diagram I saw shows D5 connected in reverse.

It is imperative that any modification to a car ignition system be as reliable as possible since sudden failure could, in certain circumstances, cause an accident situation. For this reason I must condemn the use of unmarked or otherwise low grade components.

Unfortunately many constructors have become disillusioned with the results and have laid the blame at my door saying that it is a design fault. This has caused me a lot of unnecessary work and expense in replying to this type of complaint, and has delayed the writing of a follow up article since I feel I must in future recommend specific types and sources of all components.

Yours faithfully,
S. Soar."

Ignition!

This is a copy of a letter sent to one of our advertisers by Mr. S. Soar, author of the Electronic Ignition article published in P.W. June 1971. We do not feel that any further comment by us is needed.—Editor.

"Dear Sirs,

With reference to the electronic ignition article, I have one or two comments which I would like to raise.

As the author of the original article I have received several hundreds of letters from constructors, in the main these have been very encouraging and I estimate that the unit has now covered an aggregate distance in excess of one million miles.

However, several constructors writing to me have been disappointed with the results, and in general they fall into two categories, circuit construction faults and component failure, the latter accounting for something like 90 per cent of all problems encountered. In almost every case of component failure or malfunction the component in question

WHO MAKES WHAT?

In the October 1971 issue, the Editor expressed his concern at the winding up of the Merchandise Marks Act as from November 30th last, after which it was no longer obligatory for imported goods to bear a "country of origin" mark. One aspect of concern was the fact that some goods bearing well-established UK trade names are, in fact, made in low-cost labour countries and that after the ending of the Act there would be no way of telling where, the goods were actually manufactured.

While it appears that there is little hope of reversing the decision to end the Act, one ray of hope is that the Government is likely to support a Private Member's Bill which will provide that if a UK company's name or trade mark or any UK place name appears on imported goods it will have to be accompanied by a statement of where the goods were actually made.

All in the mind

I would be grateful if anyone could assist me in a little private research. What I need is an authoritative assertion or denial as to whether it is possible by the use of radio equipment to transmit any messages that can be received by people without any receiving equipment at all. In other words, can messages be transmitted directly to a person's mind?

I have heard this claimed on several occasions—the first time being from a Gendarmee Commissionier in France in 1946 and although he was a learned man, he was not familiar with radio technology. From that time, I had heard nothing more about it until three years ago.

In a district I left two years ago, a great deal of talk centred around this subject under the name of "telemetering" and I do know that a number of people had radio transmitters which they claimed they were using for this

HENRY'S FOR **FIRST GRADE BRAND NEW BRANDED** GERMANIUM AND SILICON TRANSISTORS, DIODES, RECTIFIERS, TRIACS, FETS, ZENERS, BRIDGES and INTEGRATED CIRCUITS
 BY ATES · EMIHUS · FAIRCHILD · FERRANTI · I.T.T. · MULLARD · NEWMARKET · PHILIPS · R.C.A. · TEXAS

TRANSISTORS

A SELECTION FROM OUR LIST

AA30	10p	BD115	75p	OC16	50p	2N1303	18p
AA32	15p	BD123	85p	OC20	85p	2N1304	22p
AAZ13	10p	BD122	80p	OC22	80p	2N1305	22p
AAZ15	10p	BD131	75p	OC23	60p	2N1306	25p
AAZ17	10p	BD132	80p	OC24	60p	2N1307	25p
AC107	35p	BDY11		OC25	40p	2N1308	25p
AC126	30p		£1.50	OC26	25p	2N1309	25p
AC127	25p	BDY17		OC28	60p	2N1613	20p
AC127Z	25p		£1.50	OC29	60p	2N2147	75p
AC129	20p	BDY38	65p	OC30	50p	2N2160	60p
AC176	20p	BDY60		OC36	60p	2N2160	60p
AC187	25p		£1.00	OC42	40p	2N2217	25p
AC188	25p			OC43	50p	2N2218	20p
ACY17	30p	BF115	25p	OC44	15p	2N2218A	
ACY18	25p	BF154	20p	OC45	12p	2N2219	20p
ACY19	25p	BF158	15p	OC70	12p	2N2221	20p
ACY20	20p	BF159	35p	OC71	15p	2N2221A	
ACY21	20p	BF180	35p	OC72	25p	2N2222	20p
ACY22	10p	BF194	15p	OC75	25p	2N2222	25p
ACY39	55p	BF195	15p	OC76	25p	2N2221	20p
ACY40	20p	BF196	15p	OC77	40p	2N2221A	
ACY41	15p	BF197	15p	OC81	20p	2N2222	20p
ACY44	25p	BFX13	25p	OC81D	20p	2N2222	20p
AD140	50p	BFX12	25p	OC82	20p	2N2222	20p
AD145	50p	BFX30	25p	OC83	25p	2N2222	20p
AD161	35p	BFX84	25p	OC84	25p	2N2369	15p
AD162	35p	BFX85	30p	OC139	25p	2N2369A	
AF114	25p	BFX86	25p	OC140	40p	2N2646	40p
AF115	25p	BFX87	25p	OC170	25p	2N2904	20p
AF116	25p	BFX88	20p	OC171	30p	2N2904	20p
AF117	20p	BFY18	25p	OC172	40p	2N2905	25p
AF118	60p	BFY51	20p	OC201	70p	2N2905A	
AF124	25p	BFY52	20p	OC202	80p	2N2906	20p
AF125	20p	BFY53	15p	OC206	95p	2N2906A	
AF126	20p	BFY90	65p	OC207	97p	2N2906A	
AF127	30p	BFY90	65p	OC207	97p	2N2906A	
AF139	30p	BFY90	65p	OC207	97p	2N2906A	
AF180	50p	BSK21	20p	ORP60	40p	2N2907	25p
AF181	45p	BSK21	20p	ORP60	40p	2N2907	25p
AF185	50p	BST95A	15p	ST11	15p	2N2907A	
AF186	40p	BST95A	15p	ST11	15p	2N2907A	
AF239	40p	BU105	22.25p	TIP30A	60p	2N2925	15p
AS726	25p	BY100	15p	TIP31A	60p	2N2926	15p
AS727	30p	BY126	12p	TIP32A	70p	2N3011	20p
AS728	25p	BY124	15p	TIP33A	20p	2N3053	50p
AS729	20p	BY125	15p	TIP33A	20p	2N3053	50p
AS721	55p	BY210	85p	TIP34	£1.00	2N3055	70p
BA100	15p	BY211	30p	TIP34	£1.00	2N3525	
BA102	30p	BY212	30p	TI843	40p	£1.00	
BA110	25p	BY213	25p	TI850	12p	2N3614	55p
BA115	7p	BZV78L1	0p	TI851	10p	2N3702	10p
BA131	5p	GET102	35p	TI852	10p	2N3703	10p
BA136	7p	GET103	25p	TI860	18p	2N3704	12p
BA137	7p	GET111	45p	TI861	20p	2N3705	10p
BA138	15p	GET113	25p	TI862	25p	2N3707	12p
BC107	10p	GET114	20p	V405A	25p	2N3708	10p
BC108	10p	GET116	55p	VR255	35p	2N3714	
BC109	10p	GET116	55p	W01	30p	£2.00	
BC109C	12p	GET880	45p	W06	45p	2N3715	
BC113	10p	GET982	30p	ZTX107	15p	£2.20	
BC114	20p	GEX6	30p	ZTX108	12p	2N3716	
BC115	20p		£1.50	ZTX109	15p	£2.85	
BC116	20p	GM378A	55p	ZTX300	12p	2N3771	
BC116A	25p	MAT101	25p	ZTX301	15p	£2.00	
BC117	20p	MAT121	25p	ZTX302	20p	2N3772	
BC118	20p	MCT24P	60p	ZTX303	20p	£2.05	
BC119	30p	MJ420	80p	ZTX304	25p	2N3772	£2.05
BC134	20p	MJ421	80p	ZTX500	15p	£2.35	
BC135	15p	MJ2801		ZTX501	15p	2N3791	
BC136	20p		£1.10	ZTX502	20p	£2.75	
BC137	20p	MJ2901		ZTX503	17p	2N3819	35p
BC138	20p		£1.50	ZTX504	40p	2N3820	55p
BC147	12p	MJE340	50p	ZTX505	25p	2N3821	55p
BC148	10p	MJE370	20p	IN914	7p	2N3824	95p
BC149	12p	MJE371	80p	IN916	10p	2N3903	20p
BC153	20p	MJE520	75p	IN4148	7p	2N3906	25p
BC154	20p	MJE521	70p	IN844	7p	2N4058	12p
BC167	15p	MJE2855		IR821	7p	2N4061	12p
BC169	12p		£1.10	IR822	8p	2N4062	12p
BC169C	12p	MJE3051		2G301	25p	2N4289	15p
BC177	20p		75p	2G302	30p	2N4290	12p
BC178	20p	MPC806	25p	2G303	35p	2N4871	35p
BC179	20p	MPC806	25p	2N404	20p	2N5457	30p
BC182L	10p	MPC870	15p	2N696	15p	2N5458	30p
BC183L	10p	MPC806	25p	2N697	15p	2N5459	40p
BC184L	12p	MPC806	25p	2N698	30p	40250	50p
BC212L	12p	NKT214	20p	2N706	10p	40380	40p
BC213L	12p	NKT216	35p	2N706A	12p	40381	40p
BC214L	15p	NKT403	75p	2N708	15p	40382	50p
BCY30	35p	NKT404	65p	2N930	20p	40430	£1.00
BCY31	40p	OA5	25p	2N987	40p	40543	85p
BCY32	60p	OA10	25p	2N1131	25p	40594	£1.05
BCY33	30p	OA17	10p	2N1132	25p	40595	£1.05
BCY34	35p	OA70	10p	2N1302	18p	40638	£1.10
BCY38	45p	OA79	10p				
BCY39		OA81	8p				
	£1.00	OA90	8p				
BCY40	50p	OA91	7p				
BCY41	15p	OA92	7p				
BCY71	20p	OA200	7p				
BCY72	15p	OA202	10p				

Full transistor list available - send for your free copy today!

HENRY'S LOW COST INTEGRATED CIRCUITS

BRAND NEW FULL SPECIFICATION TTL74 SERIES
BRANDED FAIRCHILD, I.T.T. AND TEXAS
 DEVICES MAY BE MIXED TO QUALIFY FOR QUANTITY PRICES

No.	Description	1-11	12-24	25-99	100+	250+
7400	Quad 2-input NAND gates	20p	18p	16p	14p	12p
7401	Quad 2-input open collector NAND gates	20p	18p	16p	14p	12p
7402	Quad 2-input NOR gates	20p	18p	16p	14p	12p
7403	Quad 2-input open collector NAND gates	20p	18p	16p	14p	12p
7404	Hexuple inverters	20p	18p	16p	14p	12p
7405	Hex inverters with open collector outputs	20p	18p	16p	14p	12p
7410	Triple 3-input NAND gates	20p	18p	16p	14p	12p
7413	Dual 4-input Schmitt triggers	30p	27p	25p	22p	20p
7420	Dual 4-input NAND gates	20p	18p	16p	14p	12p
7430	Dual 8-input NAND gates	20p	18p	16p	14p	12p
7440	Dual 4-input NAND buffer gates	20p	18p	16p	14p	12p
7441	BCD-Decimal decoder/Nixie driver	75p	72p	70p	60p	55p
7442	BCD-Decimal decoder (4-10-line) TTL O/P	75p	72p	70p	60p	55p
7443	Excess 3-Decimal decoder TTL outputs	£1.00	95p	90p	80p	70p
7447	BCD-Decimal 7 seg. decoder/indicator driver	£1.75	£1.60	£1.45	£1.30	£1.15
7448	BCD-Decimal 7 seg. decoder/indicator TTL O/P	£1.75	£1.60	£1.45	£1.30	£1.15
7450	Expand dual 2-input AND-OR-INVERT gates	20p	18p	16p	14p	12p
7451	Dual 2-wide 2-input AND-OR-INVERT gates	20p	18p	16p	14p	12p
7453	Quad 2-input expand AND-OR-INVERT gates	20p	18p	16p	14p	12p
7454	4-wide 2-input AND-OR-INVERT gates	20p	18p	16p	14p	12p
7460	Dual 4-input expanders	20p	18p	16p	14p	12p
7470	Single J-K flip-flop (gated inputs)	30p	27p	25p	22p	20p
7472	Single J-K flip-flop (gated inputs)	30p	27p	25p	22p	20p
7473	Dual J-K flip-flop	40p	37p	35p	33p	30p
7474	Dual D flip-flop	40p	37p	35p	33p	30p
7475	Quad 2-input bistable latch	45p	42p	40p	38p	35p
7476	Dual J-K flip-flops with Preset and Clear	40p	37p	34p	31p	28p
7480	Gated Full Adder	80p	72p	67p	59p	55p
7481	16-bit read/write memory	£1.25	£1.15	£1.10	£1.00	90p
7482	2-bit binary Full Adder	87p	80p	70p	65p	60p
7483	4-bit binary Full Adder	£1.00	90p	85p	80p	75p
7484	16-bit RAM with gated write inputs	£1.00	90p	85p	80p	75p
7486	Quad 2-input 2-input Exclusive OR gates	45p	41p	38p	35p	33p
7490	BCD decade counter	75p	70p	65p	60p	55p
7491	8-bit shift register	£1.00	95p	90p	80p	70p
7492	Divide twelve counter	75p	70p	65p	60p	55p
7493	4-bit binary counter	75p	70p	65p	60p	55p
7494	Dual entry 4-bit shift register	80p	75p	70p	65p	60p
7498	5-bit parallel/serial in/out shift register	£1.00	95p	90p	80p	70p
74100	8-bit bistable latch	£2.50	£2.30	£2.00	£1.75	£1.50
74118	Hexuple Set-Reset latches	£1.00	95p	90p	80p	70p
74121	Monostable multivibrators	60p	55p	50p	46p	41p
74141	BCD-Decimal decoder/Nixie driver	£1.00	95p	90p	80p	70p
74145	BCD-Decimal decoder (1-4 line) TTL O/P	£1.50	£1.40	£1.30	£1.10	£1.00
74151	16-bit data selector/multiplexer	£2.00	£1.75	£1.55	£1.30	£1.05
74153	Dual 4-line to 1-line data selector/multiplexer	£1.35	£1.27	£1.20	£1.15	£1.10
74154	16-bit decoder/demultiplexer	£2.00	£1.75	£1.55	£1.30	£1.05
74155	Dual 2-line to 4-line decoder/demultiplexer	£1.55	£1.47	£1.35	£1.10	£1.05
74156	Dual 2-line to 4-line decoder/demultiplexer	£1.55	£1.47	£1.35	£1.10	£1.05
74180	Sync decade up-down counter, 1-line mode	£1.95	£1.85	£1.75	£1.60	£1.50
74181	Sync 4-bit up-down counter, 1-line mode	£1.95	£1.85	£1.75	£1.60	£1.50
74182	Sync decade up-down counter, 2-line mode	£2.00	£1.90	£1.80	£1.65	£1.55
74183	Sync 4-bit up-down counter, 2-line mode	£2.00	£1.90	£1.80	£1.60	£1.40
74196	Asynchronous presettable decade counter	£1.50	£1.40	£1.30	£1.10	£1.00
74197	Asynchronous presettable 4-bit binary counter	£1.50	£1.40	£1.30	£1.10	£1.00

Complete data on the above in booklet 20 pages. Ref. 29, issue 2 at 15p post paid.
 Texas I.C. Handbook. Complete information on 100 types, 40p. Post 10p.
 Integrated circuit sockets 14 pin D.I.L. 25p; 16 pin D.I.L. 30p.

QUANTITY OFFERS!
FROM STOCK

AF117	Mullard	20p	25 + 17p	100 + 15p	500 + 12p	1000 + 10p
2N2646	Motorola	40p	25 + 35p	100 + 32p	500 + 28p	1000 + 23p
OC170	Mullard	25p	25 + 20p	100 + 18p	500 + 13p	1000 + 10p
BY127	Mullard	15p	25 + 12p	100 + 10p	500 + 9p	1000 + 8p
OC35	Mullard	50p	25 + 45p	100 + 40p	500 + 35p	1000 + 30p
2N2926	Green	10p	25 + 9p	1		

RX UNIT TYPE R1155

These well known communications receivers cover the following ranges 75 to 200 Kc, 200 to 500 Kc, 600 to 1500Kc, 3 to 7.5 Mc/s & 7.5 to 18 Mc/s. These have R.F. and 2 I.F. stages, B.F.O. Tuning Ind. C.W. filter, A.V.C. or Manual control, and are fitted with the N type super slow motion drive. These require an ext P.U. to supply 250v H.T. at 60 Ma and 6.3v A.C. 4 amps, O/P is for H/Phones, if speaker is to be used O/P stage is required. These are supplied with all valves inc. D.F. section, circuit diagram, tested, in good used condition. Price £17 plus £1 carr.

U.H.F. TEST SET

These are a mains operated T.S. that cover the range 600 to 1200 Mc/s and are directly calibrated, the O/P is radiated from a small Parabolic Reflector that is part of the unit. Supplied with mains lead (230v 50c/s) in used cond in transit case. Ideal for U.H.F. T.V. Band. Price £6 plus £1 carr.

POWER UNIT 78AY

I/P 230v 50c/s provides a stabilised O/P of 250v at 400 Ma this can be adjusted over the range 235 to 285v this can be modified to give 200 to 300v, will also provide 400v at 400 Ma or both 250 and 400v up to 400 Ma, these units have large monitor meter that can be switched to read Volts or Ma, use 13 valves, 19" rack mounting, fitted mains and H.T. on Ind. Supplied in new condition, with connections, quality unit. Price £8 plus £1 carr.

METER UNITS

These are a 270 deg. meter with a F.S.D. of 1 Ma, scale marked 0, 2, 4, 6 & 8 x 100 Deg. cent white letters on black, size 2" O.S.D. 3 1/4" long, high grade Aircraft meter. Supplied new unused, boxed. Price £1.25 plus 15p post.

RX/IND APN-9

Contain Tube 3BP1 3" green screen ideal scope use, has 34 valves, 100Kc crystal unit etc. fitted tube magnifier, supplied new boxed with circ. and inst. book. Price £8 plus 75p carr.

MISC. ITEMS

Ind Unit 266 contains 6" tube VCR97, 18 valves, 40-1 slow motion dial, tuning conds etc. in case with cover £3.50. O/P & T.U. contains 2 x LA2503 Vinkors, 4 Transis, 4 min relays etc., new 85p. Heli pots 10 turn 500 ohm, 2.5K, 50K all 85p ea. 2K pre set 55p. Relays 12v 180 ohm sealed 4p. c/o contacts M.B.B. ex new equip. 50p. W.F. Gen unit contains 24 B7g valves, 24v blower etc. in case £2. American 73 Radio Mags new back issues, 8 for £1.15. Small panel with 7 x 400 P.I.V. diodes, min relay, 11 tant conds etc., new 50p. Valves 6SN7 5 for 50p. Small Amp units 115v 50c/s I/P uses 6X4, 12AX7 & 6AK6 valves 500 ohm o/p with circ & mods. £1.80. Diodes 800 P.I.V. 1a 12 for £1. Transistors type OC42 P.N.P. suitable swt flip flop etc. 1/4" leads 12 for 50p. Chokes 25 H 1 amp C core 70p. Miniature plug & Sk 18 way with clamp & cover 15p. Relays sealed coil 14K 1p c/o & coil 700 ohm 27v 2p c/o both ex new equip 2 for 30p. Tuning cond 60pf with small drive air spaced 35p. Swt unit with 4p 4w 4b swt & 12 7/45pf trimmers 35p. Fan Unit 8" dia 120v 50c/s 3,300 RPM with grill very powerful £3. H.F. Aircraft Rx xtal controlled 2-8 to 18 Mc/s in 3 bands 24v I/P, 3 ohm O/P £7. Circuit Diagrams R1155, BFLM 1392 Rx, 1475(88) Rx, ARR-2, APN-9 all 30p. Scopes 13A, CD518(CT316) 50p. Cossor 1035 Mk1, Mk2, Mk3, all 50p. 1049 Mk3a 50p. T.S. C138 late circ. 50p. T.S.2 1930p. American scopes OS-8, 208, 50p.

All above prices include post or carr; all goods ex equipment unless otherwise stated. S.A.E. with enquiry.

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9 5HL

RSGB BOOKS FOR YOU

RSGB AMATEUR RADIO CALL BOOK

1972 edition now available

Includes details of new calls notified by the M.P.T. up to August 1971, and contains over 2,600 amendments to entries in the 1971 edition. 128 pages. 57p post paid

VHF-UHF MANUAL

By G. R. Jessop, C Eng, MIERE, G6JP

2nd edition. Considerably enlarged and revised. Transmitters, receivers and test equipment for use at vhf and uhf are all fully covered on a practical basis in this new edition. £1.80 post paid

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. Complete coverage of the technical and constructional fields. A superb hard-bound volume. £3.50 post paid

These are three of a complete range of technical publications, log books and maps, all obtainable from:

RADIO SOCIETY of GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE


BAKER 12in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.

Maximum Power 15 watts
Bass Resonance 45 c.p.s.
Flux Density 12,000 gauss
Voice Coil impedance 3 or 8 or 15 ohm models
Useful response 45-13,000 c.p.s.

£7

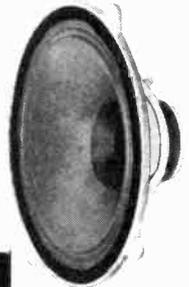Nett weight 5 lbs. POST FREE
GUITAR MODEL "GROUP 25" £7
25 watt rating
Latest catalogue 5p with enclosure plans.



Baker Reproducers Ltd

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

G. T. ELECTRONICS

FOR REAL SERVICE WITH THE LARGEST SELECTION OF ELECTRONIC COMPONENTS AND TEST EQUIPMENT YOU MUST VISIT:—

G. T. ELECTRONICS

267 ACTON LANE, CHISWICK, LONDON W.4

9.30 a.m.—6.00 p.m. Mon.—Sat.

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

NEW ZEALAND is one of the countries that can only be heard for a few months in each year.

The transmitter power is only 7.5kW and the aerials are beamed to Australia and the Pacific Islands. Propagation conditions only allow reception in this country in the last few months of the year and possibly in January as well.

Our first reporter this month is **David Watters** of Edinburgh. The equipment consists of an old Philips domestic superhet and a six foot whip antenna fixed on the roof. David's reports of Radio New Zealand should prove useful to all those trying to catch this rare country.

- 6010 *R.T. Belge*, Belgium in Dutch at 1430.
- 7105 *CBC, Canada* in Russian at 0330.
- 9520 *New Zealand* in English at 0900.
- 9525 *RSA, South Africa* in English at 0500.
- 9540 *New Zealand* in English at 0600.
- 9550 *Finland* in English at 1800.
- 9560 *ABC, Australia* in English at 0645.
- 9625 *CBC, Canada* in English at 0715.
- 9755 *New Zealand* in English at 1700.

Jean A. Meghriche of Elstree has again concentrated on the 60 metre band and produced the following results:—

- 4920 *R. Caracas, Venezuela* at 0620.
- 4945 *R. Colosal, Colombia* at 0610.
- 4955 *R. Nacional, Colombia, s/off* at 0505.
- 4965 *R. Santa Fe, Colombia* at 0605.
- 4970 *R. Rumbos, Venezuela* at 0450.
- 4980 *Radio Accra, Ghana* at 1815.
- 4980 *Ecos del Torbes, Venezuela* at 2320.
- 4990 *R. Barquisimeto, Venezuela* at 0305.
- 5010 *R. Cristal, Dominican Republic* at 0525.
- 5025 *R. Clube de Huila, Angola* at 2010.
- 5035 *R. Bangui, Cent. African Rep.* at 2000.
- 5047 *R. Lome, Togo* at 0630.
- 9535 *ETLF, Ethiopia* at 1830.
- 11920 *R. Abidjan, Ivory Coast* at 1750.
- 11925 *R. Bandeirantes, Brazil* at 2050.
- 11865 *R. Clube de Pernambuco, Brazil* at 2015.

Alexander Morton of Framlington, Suffolk has a VEF-204 receiver and a 20 foot long-wire in the loft. This combination produced a very long log of which the following is an extract:—

- 5875 *HCJB, Quito, Ecuador* in English at 0810.
- 6025 *Radio Sweden* in English at 1600.
- 9770 *R. Sofia, Bulgaria* in English at 1930.
- 11860 *R. Portugal* in English at 1900.
- 15225 *RSA, South Africa, news* at 1600.
- 15380 *CBC, Canada* at 1120.
- 17787 *WINB, Red Lion, U.S.A.* at 1820.
- 17840 *HCJB, Quito Ecuador* at 2030.
- 17885 *R. Lebanon* in English at 1840.
- 17970 *R. Pakistan, news* in English at 1350.

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

- 21560 *RSA, South Africa* at 1400.
- 21582 *Radio Accra, Ghana* at 1445.
- 21800 *Radio Norway, in English* at 1800.

Steve Mathews of Hull has used his Trio 9R-59DS and 90 foot long-wire to hear the following:—

- 3265 *R. Clube Mozambique* in English at 2100.
- 4833 *Bamako, Mali* in French at 2130.
- 5010 *R. Cristal, Dominican Republic* at 0245.
- 6040 *Voice of the Coast, Dubai* at 0410.
- 6055 *ABC, Australia (Darwin relay)* at 1715.
- 6120 *R. El Mundo, Argentina* at 0200.
- 15430 *KBS, Korea* in Spanish at 0205.
- 15440 *FEBC, Philippines* at 1545.
- 21500 *R. Brazzaville, Congo, French* at 0845.

D. A. Hairon of St. Clement, Jersey is now using a Codar CR70A, a PR30 preselector, a 19 metre band dipole and a 100 foot long-wire. His log for this month included:—

- 9560 *RSA, South Africa* in English at 0230.
- 9710 *HCJB, Quito, Ecuador* in English at 0245.
- 11710 *AIR, Delhi* in English at 2330.
- 11765 *R. Dif. Sao Paulo, football* at 0100.
- 11775 *VOA, Philippines, s/off* at 1700.
- 11785 *TWR, Bonaire* in English at 0115.
- 11885 *R. Maua, Brazil* in Portuguese at 0000.
- 11925 *R. Bandeirantes, Brazil* at 2030.
- 15185 *R. Havana, Cuba* in English at 2010.
- 21570 *NHK, Japan* in English at 0800.

Craig Tyson of Wembley, Western Australia has concentrated on 19 metres and his log includes:—

- 15105 *R.T. Belge, Belgium* at 1600.
- 15120 *Radio Ceylon* in English at 0320.
- 15155 *RSA, South Africa* in English at 1810.
- 15165 *R. Damascus, Syria* in French at 1950.
- 15175 *R. Norway* in English at 0800.
- 15190 *R. Brazzaville, Congo, French* at 1810.
- 15235 *NHK, Japan* in English at 0930.
- 15285 *R. Accra, Ghana* in English at 1820.
- 15345 *VOA, Philippines* in English at 1100.
- 15355 *R. Lebanon* at 2300.

Stephen Hillman of Warley has a Teleton 136F4 receiver connected to a 50 foot long-wire enabling him to hear:—

- 4970 *R. Rumbos* in Spanish at 0200.
- 5960 *HCJB, Quito, Ecuador* in English at 0800.
- 11795 *WINB, Red Lion, USA* in English at 2000.
- 11805 *R. Globo, Brazil* in Portuguese at 2030.

Reports should arrive by the 15th of the month and be addressed to me at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

SHORT WAVES

THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz ● Times in GMT

HANDS up all those who got a new receiver from Santa. Just think of all those exotic callsigns you'll be hearing—or perhaps you've heard them already in which case how about sending in a log?

What antennas are you going to try this year? Now is the time to start planning and doing all the paperwork. If '3JDG's experience is anything to go by then this definitely is the time. After you've changed your mind half a dozen times and bought lengths of wire you find you don't need after all it works out a bit expensive in both time and money. Much better to work out everything while you're sitting by the fire in the cold months. You'd be surprised how much time you can save by planning well in advance. How about an all-band automatically-switched vertical for the loft?

"The most exciting band for me this month was two metres," says **Stefan Kaye** (Witney). Gear is a 4-over-4 in the loft, Space Mark converter and an AR88D tuning 12-14MHz. Ears are the Kaye, MK1 types and were stimulated to the tunes of the following on 144MHz; DC2JN, DC6EQ, DJ4AX, DJ4EU/P, DK4TP, DL0ER, DL0WU, DL1XG, F1KCG, G8ABP, G8EJH, ON5NY, PA0QX, PA0WCH.

Some people have written in asking how a receiver tunes in 144MHz signals since the frequency given for the receiver tuning is never anywhere near 144MHz. Idea is that you use a converter between the main station receiver and the aerial. The converter "converts" (surprise, surprise) the 144MHz incoming signals and lowers the frequency down to a range which can be covered by the main receiver. Popular converter output frequencies are 12-14MHz and 28-30MHz. The converter doesn't need tuning, you just plug the antenna in one end and the receiver into the other.

But I digress! **R. Gillon** uses a Wein Flight 4 on 144MHz. Signals received from: DM0ER, DL0PT, EI2BY, F6AP, GW8ASA, GM3NYY/P, OL60L, ON5NY, PA0LM. QTH is Richmond.

Brian Lucas (Gillingham) has an RBX-2 Halli-crafter and describes the antenna as "chopped down v.h.f. dipole loitering on the end of a 3ft beam under the eaves." (Bet he only listens in the evenings! Squeaks of r.f. on 144MHz from: DL0ER, F0YT/M, F1PD, F1AXI, F1BMF, F1BCD, F5ID, F6HWH plus 12 G3s, a G4 and 18 Gs.

A 46 (forty-six) element Multibeam, converter and 9R59DE tuning 28-30MHz is **N. Richardson's** visiting card on 70cm. Goodies arriving at Aylesbury at this rarified frequency include: DC8AMA, DC8UA, PA0DGH, PA0JNH, PA0EZ, PA0QX.

Down on 144MHz, **Nicholas** and 8-element yagi, converter plus 9R59DE, did a bit of eavesdropping on: DC0QA, DJ8SW, DJ8VRA, DJ9UXA, DK2T/P, DK4TP, DL0ER, DL1XG, F1AEX, F2XO, F5DA, F6BBA, F6BOM, F9QW, GC8AWE, GC8BMO, ON4OR, ON5QW, ON5VU, PA0APE, PA0HWB, PA0CML, PA0ELL, PA0HAG.

All this v.h.f. is a bit too rich for the old '3JDG blood, let's flick the bandswitch to 28MHz and see who heard what. Ten metre addict **M. Shields** (Abergavenny), JR500-SE, 70ft long wire end fed running NS, sends in a mouth-watering log of callsigns. Pages from an immaculate log read: CE3EZ, CE7TJ, CR4BS, CR6IK, CR6TP, CR7LE, CR7IA, CP6FG, CT3AS, CX7BF, CX8BE, CN8HD, DJ4OI, EL8I, FY7AD, F9XF, G3MUL/CE3, HK4AFT, HR1JA, KV4FD, KP4CQB, K4AVD, LU6ECE, PY3BNJ, RA3AFL, VP8MM, VP9DC, W6JIF/4, W3FXG, XX6FL, YN2OM, ZP5AQ, ZC4AVU, ZE1BP, ZE1GDS, ZS2AG, ZS4UCC, ZS5KS, ZS6ATA, 4Z4HF, 5N5ABG, 8R1G, 9G1DY, 9H1AQ, 9J2DT, 9Q5ELA.

Letter from **Karl Muller** (Swaziland) informs that ZD5 stations are now all 3D6A stations. Karl says that forty metres has been disappointing in the evenings mainly because of QRM from BC stations. How about all transmitting amateurs having a 1972 40-metre activity year, I'm sure we could make some of these pests QSY out of our band? It would make forty a greater attraction for the s.w.l. and would dissuade greedy eyes from pilfering our last (in the UK) 100kHz. How about it, r.f. makers?

Robert Ferguson (near Birmingham), has an HRO plus a "... one element rotatable beam." (Good gracious, Holmes!). Ten metres yielded: CX8BE, CR6TP, CX8BE, LU5DTA, VK9XK, ZS1JA, 7Q7BC, 9G1DY, 9J2DT, 9Y4VU plus hoards of JAs.

Best from **Martin Evans** (Colwyn Bay) on 3.5MHz using a three-transistor t.r.f. with 150ft end fed plus a.t.u. were: CT1BH/P, OX3RA, OY400, TF5TP, TI2GI, VE1AM/VP9, VP7NH, ZS6DW, 4U1ITU, 4X4YM, 4Z4HF.

Keith Monham (Feltham) bagged these on phone on 160 metres; DJ4SS, DK2JX DL0WU, EI9ONE, GM3NVU, GM3YCB, GM4NR/P, GW3AAC, GW4AJ/A, OH1VR, OH5GM, OH5SM, PA0PN. Cor, think what was about on c.w. Gear is a 60ft. end fed with a.t.u. plus a B40 receiver which draws sparks between earth wire and chassis. (Shocking state of affairs!).

Nicholas Minns (Letchworth), CR300, 110ft. end fed, sends in this list of topband hearings; DK0WA, DK2WA, HB9CM, OH1VR, OH5SM, PA0PN, EI9ONE.

On 3.5MHz, the same set up raised: FM7WN, HR1WSG, OY2X, PJ2CW, PZ1CU, TI2CAP, WA6EGL/P/TF, VP2VAG, ZB2AV. While the dreaded forty metres surrendered signals from: CN8CS, EP2BQ, FL7ZX, JA6BSM, 4X4LNI, 6W8DY.

Logs, in alphabetical order please, to arrive by the 15th of the month to:

12 Cross Way, Harpenden, Herts.

INCREASE YOUR KNOWLEDGE



Established 1891

MANY COURSES TO CHOOSE FROM incl.


RADIO & TV ENGINEERING & SERVICING,
TRANSISTOR & PRINTED CIRCUIT SERVICING,
COLOUR TV SERVICING, ELECTRONICS,
NUMERICAL CONTROL ELECTRONICS,
TELEMETRY TECHNIQUES, CONTROL SYSTEMS,
ELECTRONICS FOR AUTOMATION,
COMPUTERS, ETC.

ALSO EXAMINATION COURSES FOR

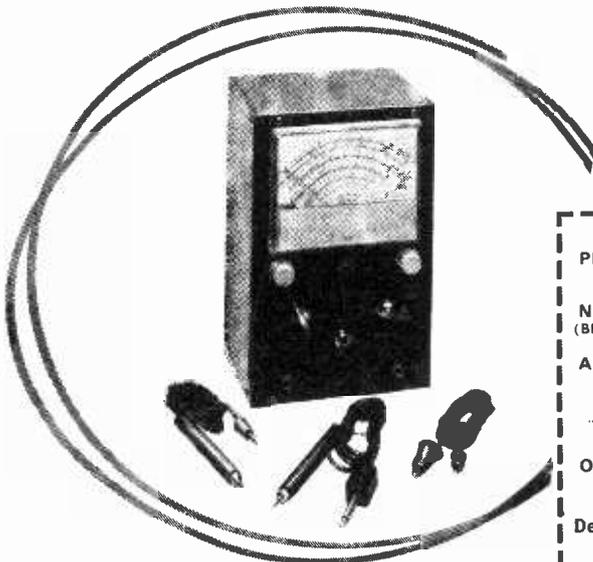C. & G. Telecommunication Technicians' Certificates
Radio Operator Certificates
Radio Amateurs' Examination
General Certificate of Education, etc.

BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION
OF BRITISH CORRESPONDENCE COLLEGES

THERE IS AN ICS COURSE FOR YOU.

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

FILL IN AND POST THIS COUPON TODAY

You will receive the FREE ICS Prospectus listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.

Accredited by the CACC.

PLEASE SEND FREE BOOK ON

NAME
(BLOCK CAPITALS PLEASE)

ADDRESS

.....

OCCUPATION AGE

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. CB28, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8 4UJ.

DISCOUNTS UP TO

60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

AKAI · LEAK · SINCLAIR · TELETON · ARMSTRONG · ROTEL
THORENS · PHILIPS · GOLDRING · ROGERS · PIONEER

SPECIAL OFFER £18

Garrard SP25 Mk. III
Goldring G800H
Teak plinth and tinted cover.
Ready wired for immediate use.
Please add £1.25 for post and packing.

TURNTABLES

- Please add 75p for P. & P.
- Garrard SP25 Mk. III £10.25
 - Garrard 2025TC with Sonotone 9TAHC £8.95
 - Garrard Zero 100-Auto (New Product) £40.95
 - Garrard Zero 100-Single Play (New Product) £37.95
 - Garrard SL65B £13.50
 - Garrard AP76 £11.95
 - Garrard 401 £27.00
 - BSR MP60 £10.00
 - Pioneer PL12AC £36.00
 - Thorens TD125 £62.50
 - Thorens 150ABII £42.50
 - Goldring GL69/2 £20.00
 - Goldring GL69 P2 £26.95
 - Goldring GL75 £27.95
 - Goldring GL75 P £35.95

AMPLIFIERS


- Please add 50p for P. & P.
- Alpha Highgate FA212 £27.50
 - Alpha Highgate FA300 £29.00
 - Alpha Highgate FA400 £23.00
 - Armstrong S21 (cased) £44.95
 - Armstrad 8000 Mk. II £16.95
 - Amstrad IC2000 £34.00
 - Dulci 207 £15.95
 - Dulci 207m £21.00
 - Leak 30 Delta Range (New Prod.) £51.00
 - Leak 70 Delta Range (New Prod.) £61.00
 - Metrosound ST20E £26.50
 - Philips R580 £18.00
 - Pioneer SA500 £36.00
 - Pioneer SA700 £68.00
 - Pioneer SA900 £92.00
 - Rogers R/brook Chassis £35.50
 - Rogers R/brook Cased £39.50
 - Rogers R/bourne Chassis £44.00
 - Rogers R/bourne Cased £48.00
 - Sansui AU101 £31.00
 - Sansui 555A £59.95
 - Sansui AU666 £75.00

- Rotel RA 301 £32.75
- Rotel RA 601 £49.80
- Sinclair 2000 Mk. II £42.50
- Sinclair 3000 £32.50
- Sinclair PRO 60/2 + Z30 PZ5 £15.00
- Sinclair PRO 60/2 + Z30 PZ6 £17.75
- Sinclair PRO 60/2 + Z50 £17.75
- PZ8/Trans £22.95
- Sinclair AFU £4.70
- Sinclair 605 (New Product) £20.50
- Goodmans Max Amp £37.95
- Teleton SAQ206B (New Prod.) £17.95
- Wharfedale £49.75
- Sinclair IC12 integrated circuit amplifier £1.85
- Eagle TSA 149 7w RMS £34.95
- Eagle TSA 151 15w RMS £24.50

CARTRIDGES

- Please add 10p for P. & P.
- Goldring G850 £3.75
 - Goldring G800 £6.50
 - Goldring G800 £6.50
 - Goldring G800E £10.50
 - Goldring G800SE £15.50
 - Sonotone 9TAHC Diamond £1.75
 - Shure M3DM £4.50
 - Shure M445/7/C £7.00
 - Shure M55E £8.75
 - Shure M75E £12.75
 - Shure V15 Type 2 £27.75
 - Shure M44E £7.00
 - Shure M31E £8.50
 - Shure M32E £8.00
 - Audio Technica AT35 £12.95

PLINTHS & COVERS

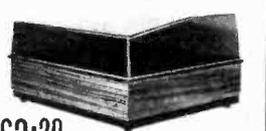

£3.20 (As illustrated)
Plus 35p post and packing.
Finished in real teak veneer with tinted dust cover. Ready to use (fully assembled). Suitable for Garrard SP25; 2025TC; 300; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for McDonald MP60 and others.

For AP76; AP75; SL72B; SL75; SL95B: £4 plus 35p P. & P. Also finished in walnut to match Japanese equipment—at no extra charge.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PW6) 174 Pentonville Road, London, N1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).
2 minutes from KING'S CROSS EUSTON & ST PANCRAS on main road leading to the East and West Country



for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price 75p
Size 12



THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price 75p
Size 10



A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF.	ALLOY	SWG
19A	60/40	18 18p*
Size 5 (ill-ultra-ted)		
19	60/40	18 18p*
15	60/40	22 22p*

* Recommended Price



INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 50p



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

FELSTEAD ELECTRONICS (PW 53)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas). Cash with Order only—No C.O.D. or Caller service. Charges (Min. 6p) in brackets after all items apply to G.B. & Eire only. Regret Orders under 25p plus charges unacceptable. R.A.K. please, for enquiries or cannot be replied to. Overseas Orders welcomed.

RECORDING TAPE: Finest quality/value British Mylar available. STANDARD 5" 600ft 38p; 6" 900ft. 50p; 7" 1200ft. 56p; LONG PLAY 5" 900ft. 50p; 5 1/2" 1200ft. 56p; 7" 1800ft. 90p. (7p on 5" and 5 1/2", 9p on 7"). Other sizes, Cassettes and accessories in List.

CARTRIDGES. All with standard fittings and styli. Mono GP87 85p; Stereo-compatible Mono GP91/8C £1.10; STEREO GP93 £1.40; Stereo Ceramic GP94 £1.85. (6p) Comparatives shown in List, with more types incl. Sonotone 9TAHC, Goldring etc. at below prices.

DIAMOND STYLUS: Single tip types: Acos GP7, GP8, GP9, GP17, BSR TCR/EPST, COLLEO O. P. etc. DC284; GARRARD GC2, GC8, GC12, GC810; RONETTE BF40. O. P. and T: PHILIPS 3301 (3080, 3066, 3302, 3304), 3010 (12, 13, 16); SONOTONE 19T/20T ALL AT 40p each (6p). Double-tip turn-over types (78 sap. on other side). For ACOS GP73, GP91 (for cartridges GP93, GP94 etc). GP918C (for stereo-compat. types) GP104, BSR ST4 (ST3, ST5), ST9 (ST8), ST12/14/15, SONOTONE 8TA, 9TA, 9TAHC, PHILIPS 3308 (3310, 3224, 3228/32, GP280), GARRARD GC21, 22, GC83, GC85, 28 and 28, CM917 and 22T, GK24T, GC8231, GK823T & 26T GC831, GC836, GC835, GC838, K840A, K841B ETC. ALL AT 75p (6p). **DOUBLE DIAMOND STYLUS:** (Same dia. tip each side: no 78) All types £1.50 (6p). **PICK-UP WIRE:** Super thin twin flex screened, sheathed, 6p per yard (Up to 6 yds. 6p over charges paid). All sapphires in list.

MICROPHONES: CRYSTAL: LAPTEL 1 1/2", clip/hand, lead 3.5mm jack plug 32p (6p). CM20 Cream Plastic hand 58p; CM21 Grey Plastic Hand/Desk 62p; both have 3.5mm jack plug and lead (8p either). "BTOK" 6p £1.02; CM70 "PLANET" Metal, tapered, with neck cord, adaptor for stand £1.474; "MIC 91" hand/clip 81p; "MIC 45" Curved metal hand/grip £1.00. ALL with leads (all 8p). **MICROPHONE INSERTS:** Dia. 1.75" or 0.9" either size 27p (Up to 6 for 8p). DYNAMIC: 209 Car-Hold Ball, 50K/800 Ω built-in volume control, on/off switch, special 20ft. lead, the best value anywhere at £8.30; U0130, uni-dir. mesh ball 50K/800 Ω jack plug, cable, adaptor, £4.80; D3150, omni-dir. Ball mesh, 50K, jack plug and lead (8p either). "BTOK" 6p £1.02; CM70 "PLANET" Metal, tapered, fitted tweeter, 3 or 15 ohms (state which) £1.871 (27p) — or pair for stereo £4.25, charge-paid. **HEAD 2 1/2"** 3 Ω or 8 Ω, (state which) 87p (6p). More speakers in List. **HEADPHONES:** High resistance 2000 Ω adjustable: 82p (7p). **EARPIECES:** With lead and min. 2.5mm or 3.5mm (state which) jack plug, MAGNETIC 8p. CRYSTAL (3.5mm plug only) 24p (Up to 3 for 6p any type). **SOLDERING IRON:** 81mm, modern, British high speed, 91", all parts replaceable, highest quality fully guaranteed £1.71 (10p). **TRANSFORMERS:** Sub-min 11 x 11 x 12mm. OUTPUT 1 (3 Ω for OC72, etc.) 14p or DRIVER 15p (Up to 12 for 6p). **CONNECTING WIRE.** Packs of 5 coils, each coil 5 yds. asstd. coils. **SOLID CORE:** 14p. FLEXIBLE or SUPER THIN for transistor wiring, etc. either 18p (Any pack 6p). **RETRACTABLE FLEXIBLE LEADS.** (CURLIES): With phono plug, each end, 6ft 83p, 12ft 30p. With phono plug/phone socket other end 6ft, 25p, 12ft, 42p (6p lead any type). **WIRE TORS:** 12 1/4 pin non-crimp, highest quality £1.71 (10p). **TRANSFORMERS:** USA, 20p, 12v/7 pin, synch. (12BR7) 2 1/2" ex. plug 82p (6p any type). **TRANSISTORS,** etc. AC/128 12p, AF115 20p, AF116 15p, AF117 20p, OA5 10p, OA10 10p, OA81 10p, OC44 14p, OC45, OC71, OC72, OC75, OC81D, OC82D, all at 12p each. OC81 15p, OC170 20p, OC171 12p, BY100/800 p/v 14p. Many more incl. power tubes, thyristors, etc. in List.

MAINS NEONS, 6v leads 10p. **NEON SCREWDRIVER** (pocket tester) 17p (6p either). **BATTERY ELIMINATOR:** Input 240v-AC. Output 3, 6, 7.1 and 9v-DC by switch selector. On/off switch, pilot lamp, leads, plug, adaptor to suit most transistor sets and cassette recorders. Suitable for model use: £3.15 (24p).

OUR CURRENT LIST (see heading) includes more details of all above plus cartridge replacement table, many unrepeatable Special Offers, and cable, cord, clips, Volume control-Din plugs, G-Ax, standard, miniature, phono plugs, sockets and adaptors, Tape Recorder and Record Player assemblies, panel and test meters and equipment, Multimeters, multi-motors, test probes, cabinets, rotary, toggle, slide, cam, etc. electrolytics, terminals, Veroboard, valve holders, extending aerials for cars and portable sets, incl. lamps and bulbs, diodes, mikes, telephone amplifiers and pick-ups, drive cord, Inter-com, sub (testing) boxes, Stereo Headphones etc. etc.

practically wireless

commentary by **HENRY**

No. 87

Milk
Teeth

IT IS ALL TOO EASY to blame lack of foresight on teething troubles. That, after all, is what happens when car doors fall off, when vacuum cleaners shed belts, when 'fridges go up in smoke—or when radio gear develops a case of the twitches only weeks after delivery.

"Teething troubles," if I may quote John Pudney, "is an indulgent phrase which has become a blanket term for incompetence."

Ralph Nader may have a lot to say about the automobile industry and its tendency to blanket its failings with next year's model draped with nudes, or not. Henry cannot cap his quotes, perhaps because he has had to manage with a succession of second-hand cars—and you know what the public thinks of *their* advertisements. . . . But on the subject of newly-sold radios and associated gear, your correspondent speaks with some authority.

And bitterness! I often wish some fully-equipped Nader would rise and berate the manufacturers of our domestic electronic equipment. And not only our homegrown makers, for at least we must give them a Beta-minus for trying, but also the importers.

However elegant the drawn circuit, reality will always have rough edges. Any constructor will verify that. Even with the

mollycoddling given to us by such redoubtables as Heathkit, it is possible to make mistakes. Human error enters into Fate's formula and *reductio ad absurdum* is the result.

Absurd as the contretemps Henry observed when working as a "tester" in a radio factory—instructions were given to those doing routine alignment: "twiddle until the needle on the meter reaches maximum, then seal the screw." Nobody considered that there were two alternative peaks when the mixer circuit was tuned in—so, of a batch of well over a thousand sets, boxed and despatched, a goodly proportion were completely misaligned—and nobody noticed till the complaints came rolling in!

Teething troubles were blamed for many of the television set assinities that kept field engineers buzzing about like bluebottles when ITV first opened, when dual-standard receivers became the vogue, and harass them now, when colour is the order of the day.

Teething troubles are given as the reason why quite famous hi-fi makers foist amplifiers on the public with an inherent rumble and noisome hiss and then announce a Mark II model with alternative front-end transistors.

There will always be teething troubles while makers, greedy for profit without the responsibility that once pervaded our industry, market gear that is not in any way backed with a spares service or even the vital information the retailer's engineer will need.

Ask half the agents that are pushing their newest models, and you'll get the answer: "Our service manual's being prepared." And by that time, the poor old dealer has had to rip half a dozen of the units to bits to find why sundry minor ailments were apparently missed on final test.

A reviewer, not a hundred miles from where I sit, refuses pointblank to accept equipment



My largest pair of pliers.

for appraisal unless it is accompanied by the service information that was available to the factory engineers. He has bitter memories of putting a mediocre system through its paces, according to British Standards, only to be hauled over the coals because he had not tested it the way originally laid down. The fact that *their* way was a palpable con trick (resetting tone controls to fiddle a flat response curve) made but little difference—he should have waited for the gen. So now he does, and the panting manufacturer can whistle for his review.

But I don't know whether that is preferable to those who launch a new radio in a blaze of publicity, then proceed to Mark II, III and IV during a twelvemonth without a word to anyone. Which becomes embarrassing, when a customer toddles into one's shop with a request for a "volume control for the Superstar, please." How does one explain that there have been a veritable constellation of models bearing that name, and the clue is in the suffix to the number on the back?

I'd like to solve some of those makers' teething troubles with my largest pair of pliers.



Buzzing around like bluebottles.



New Books

Books reviewed on this page are normally obtainable through any retail bookshop. In this instance, the information printed in **heavy type** should be quoted.

FOUNDATIONS OF WIRELESS AND ELECTRONICS

By M. G. Scroggie

Published by Iliffe Books,

521 pages, 9 × 6in. £3.00 (hard cover)

HOW do you start to review a book that will without doubt become a classic? Do you try to pick holes in it to fill out the copy? That would be unfair and very difficult so all there is left to do is to praise it as strongly as you can and thoroughly recommend it to all and sundry.

I don't know how old Mr. Scroggie is; we are told on the flyleaf that he graduated in 1922 and has been writing ever since. Here he has produced a book that radiates freshness and originality and is far more up-to-date than any book I have seen for several years.

The author appears to recognise that the semiconductor is here to stay and now forms the basis of electronics and he has started from scratch with this new edition to take this into account—what a contrast to authors half his age who still regard semiconductors as upstarts!

In future, whenever I am asked to recommend a book for beginners, I shall quote this one; it doesn't give circuits or constructional details of course—it isn't that sort of book—but the explanations are clear, complete and logical.

Congratulations Mr. Scroggie and Iliffe—a fine book!—*H.W.M.*

SIMPLE SHORT WAVE RECEIVERS

By F. A. Baldwin

Published by Data Publications.

140 pages, 8½ × 5½in. Price 80p.

FRANK Baldwin is an author who certainly knows what he's talking about when it comes to short-wave listening and it is a name that crops up frequently as the author of articles in *Radio Constructor* and amongst the short wave listening fraternity. This book is a collection of simple short wave circuits—four in all—and they are all good stuff and I have no doubts that they all work—and work well. Drawings, circuits and descriptions are all very clear and well presented and these in themselves should give the reader a certain amount of confidence.

Having said that, some less kind comments must follow. All circuits use valves—and some are very old types indeed. The date is 1971—transistors rule the day, yet there is not one mention of them in the whole book. A title such as "Simple Short-Wave Receivers" must surely be aimed at beginners and wouldn't circuits using semiconductors have been far, far better? Still this is a criticism that can be levelled at nearly all books of this type and it is a reflection on *all* authors and publishers rather than on this book.

For what the book sets out to do, it is excellent. Without actually building the circuits it is difficult to judge the performance but they are all well tried and tested circuits and are described in great detail. It is tempting to find fault with the length—it is very long for only four circuits—but that would be unfair for the price is very reasonable at 80p and for that you do not feel cheated and the extra space has at least been used to detail the construction thoroughly.

J.A.

ABC'S OF THERMISTORS

By Rufus P. Turner

Published by Foulsham-Sams

96 pages, 8½ × 5½in. Price £1.10.

ONE'S first reaction to this book is to wonder how nearly one hundred pages can have been written on such a simple device as the thermistor. Knowing that "thermistor" derives from "thermally sensitive resistor" and that its temperature coefficient can be positive but is usually negative, what else is there to say?

After the "specially written chapter for the guidance of the English reader" the rest of the book, printed in the United States, does give an adequate description of the characteristics of the thermistor and its many applications, in a non-mathematical way.

It was pleasant to see a reference to the fact that our own Michael Faraday observed the negative temperature coefficient of silver sulphide as long ago as 1833.

Circuits show the thermistor in its basic role as a temperature measuring device as well as its derived use as an anemometer, flowmeter, vacuum gauge etc. and as an altimeter. This last application is based on the fact that the boiling point of a liquid decreases with altitude but it is hoped that expeditions to the Himalayas have something more sophisticated to determine their altitude than a thermistor in a pot of boiling liquid as shown in this book!

A most useful application of the thermistor in the electronics field is the measurement of r.f. power levels well into the microwave region by means of a small bead type thermistor mounted within a waveguide; others include audio compressors/expanders, c.r.t. deflection circuitry, a.g.c. systems and oscillators where the thermistor is used to control negative feedback.

Unfortunately all the circuits shown are purely theoretical, no thermistor type numbers are indicated or values given for other components. The introductory chapter "for the English reader" does admit that the circuits are basic and not for the d.i.y. types and that values of small components etc. are not stated. In fact no values are given anywhere in the book for any component, large or small.

A pity, because the book *could* have been so good.—*AED.*

ELECTRONIC VALVES

1A2	0-25	51L7GT	0-25	DY87	0-50	PC888	0-50
OA3	0-45	68N7GT	0-35	DY802	0-50	PC089	0-50
OB2	0-35	68Q7	0-40	E88CC	0-50	PC189	0-50
OB3	0-60	68R7	0-40	E180F	0-50	PC285	0-50
OC3	0-38	67R	0-35	E810F	2-90	PC806	0-85
OD3	0-35	6U4GT	0-60	EABC80	0-35	PCF80	0-30
1B3GT	0-88	6U8A	0-40	EAF42	0-55	PCF82	0-35
1CP31	6-00	6V6GT	0-38	EBC33	0-50	PCF84	0-50
1L4	2-00	6X4	0-30	EBC41	0-55	PCF85	0-50
1B4	0-35	6X6GT	0-35	EBC57	0-30	PCF87	0-50
1R5	0-35	6X8	0-55	EBF80	0-40	PCF801	0-50
184	0-27	6Y6G	0-65	EBF83	0-40	PCF802	0-50
185	0-25	7Y4	0-60	EBF89	0-30	PCF805	0-75
1T4	0-25	9BW6	0-50	EC53	0-50	PCF806	0-70
1U4	0-27	10C2	0-50	EC86	0-60	PCF809	0-75
1U5	0-60	10D1	0-50	EC88	0-60	PCL200	0-70
1V2	0-45	10D2	0-40	EC96	0-33	PCL81	0-50
1X2B	0-40	10F1	0-90	EC91	0-50	PCL82	0-35
2D21	0-35	10F9	0-50	EC92	0-35	PCL83	0-65
3A4	0-35	10F18	0-45	EC93	0-50	PCL84	0-45
3B28	2-15	10L1	0-45	EC8010	2-25	PCL85	0-40
3BF1	2-75	10LD11	0-60	ECU40	0-60	PCL86	0-45
3Q4	0-40	10P13	0-55	EC881	0-33	PCL88	0-50
5V3	0-45	10P14	1-10	EC882	0-30	PCL800	0-83
3V4	0-45	12A5	0-90	EC883	0-30	PCL801	0-70
5Y4GY	0-60	12AC6	0-40	EC884	0-30	PD600	1-50
5Y4G	0-38	12A15	0-45	EC885	0-40	PF86	0-60
5U4GB	0-42	12A25	0-43	EC888	0-40	PF818	0-85
5V3	0-42	12A7E	0-30	EC889	0-50	PLF200	0-70
5Y3GT	0-32	12B7	0-30	EC890	0-30	PL82	0-35
5Z4	0-40	13U16	0-30	EC8189	0-60	PL36	0-85
5Z4G	0-40	12AU7	0-30	ECF80	0-35	PL81	0-50
6J90L2	0-75	12AV6	0-33	ECF82	0-35	PL82	0-45
6A8A	0-35	12AV7	0-50	ECF86	0-65	PL83	0-45
6AF4A	0-50	12AX7	0-30	ECF804	1-50	PL84	0-40
6AG7	0-40	12AX7	0-70	EG142	0-30	PL89	0-30
6AH6	0-30	12BA6	0-35	EG44A	0-30	PL504	0-80
6AJ8	0-30	12BA6	0-85	EC1H83	0-40	PL508	0-90
6AK5	0-30	12BA7	0-35	EC1H84	0-45	PL509	1-30
6AK6	0-57	12BE6	0-35	ECL80	0-40	PL801	0-80
6AL3	0-43	12BH7	0-40	ECL81	0-45	PM84	0-50
6AL5	0-20	12BY7	0-55	ECL82	0-35	PY31	0-80
6AM5	0-32	12C43	0-35	ECL83	0-45	PY33	0-85
6AM6	0-33	12K7GT	0-85	ECL84	0-55	PY80	0-35
6AQ5	0-35	12Q7G	0-30	ECL85	0-55	PY81	0-30
6AQ6	0-55	12R7	0-35	ECL86	0-40	PY82	0-30
6AR5	0-35	14S7	0-80	ECLL800		PY83	0-38
6AR6	0-40	20D1	0-45		1-50	PY88	0-40
6AR11	1-25	20F1	1-10	EF37A	0-40	PY900	0-50
6AS7	0-35	20P1	0-50	EF39	0-40	PY900	0-50
6AS7G	0-80	20P4	1-10	EF40	0-50	PY901	0-50
6AT6	0-30	20P5	1-20	EF41	0-65	PZ30	0-35
6AU6	0-25	25C5	0-50	EF42	0-70	QQV2-6	2-15
6AV6	0-30	25L6GT	0-45	EF80	0-25	QQV3-10	
6AW8A	0-55	25Z4C	0-30	EF83	0-35	QQV3-20A	
6BA6	0-25	25Z6GT	0-65	EF85	0-35	QQV6-4A	5-25
6BE6	0-30	30A5	0-45	EF86	0-30		
6BF5	0-60	30AE3	0-40	EF89	0-28		
6BF6	0-50	30C1	0-30	EF91	0-33		
6BH5	0-45	30C15	0-50	EF92	0-40	TT21	2-85
6BJ8	0-45	30C17	0-35	EF93	0-45	TT22	2-80
6BZ7A	0-55	30F18	0-75	EF97	0-65	18H/20	0-75
6BN6	0-43	30F5	0-85	EP98	0-65	U25	0-75
6BN6G	0-40	30FL1	0-70	EP183	0-30	U26	0-75
6BQ6	0-25	30FL12	0-93	EP184	0-35	U31	0-45
6BR8	0-65	30FL14	0-78	EP800	1-00	U37	1-60
6BR7	1-30	30L1	0-40	EP804	0-35	U38	0-40
6BW8	0-35	30L15	0-85	EK90	0-30	U78	0-80
6BW7	0-70	30L17	0-80	EL33	1-25	U78	0-80
6BX6	0-25	30P12	0-80	EL34	0-50	U191	0-75
6BZ6	0-35	30P19	0-80	EL36	0-50	U201	0-35
6C4	0-33	30P11	0-70	EL37	1-25	U281	0-40
6C6GT	0-40	30PL13	0-68	EL38	0-75	U282	0-40
6CB8	0-30	30PL14	0-60	EL42	0-85	U301	0-40
6CD6GA	1-15	35A3	0-55	EL81	0-55	U403	0-50
6CG7	0-50	35A5	0-75	EL83	0-42	U404	0-50
6CH6	0-55	35B5	0-65	EL84	0-25	U801	1-00
6CL6	0-50	35C5	0-40	EL85	0-45	UABC80	0-35
6CW4	0-63	35D5	0-70	EL86	0-50	UAF41	0-50
6CY5	0-43	35F6GT	0-80	EL90	0-35	UAF42	0-55
6C7	0-45	35W4	0-30	EL95	0-35	UBC41	0-50
6D3	0-45	35Z3	0-60	EL803	1-00	UBC81	0-40
6DC6	0-75	35Z4G	0-30	EL821	0-55	UBF80	0-40
6DK6	0-48	35Z5GT	0-40	EL822	0-80	UBF89	0-35
6DQ6B	0-62	50A5	0-70	ELL50	0-78	UBL1	0-50
6D84	0-75	50B5	0-45	EM34	0-90	UBL21	0-60
6EA8	0-58	50C5	0-40	EM71	0-75	UC92	0-35
6EH7	0-30	50CD6G	1-65	EM80	0-40	UCC85	0-40
6EJ7	0-35	50L6GT	0-50	EM81	0-60	UCF80	0-55
6EW6	0-65	85A2	0-40	EM84	0-35	UCH21	0-80
6F1	0-70	90AG	2-40	EM85	1-00	UCH42	0-70
6F3	0-50	90AV	2-50	EM87	0-55	UCH43	0-75
6F6G	0-30	90C1	0-60	EN91	0-35	UCHR1	0-35
6F11	0-38	90CV	1-25	EY51	0-40	UCL81	0-80
6F13	0-33	807	0-50	EY80	0-45	UCL82	0-35
6F14	0-65	813	3-75	EY81	0-40	UCL83	0-80
6F15	0-65	806A	0-75	EY83	0-38	UF41	0-60
6F18	0-45	EY82	0-60	EY86	0-90	UF42	0-60
6F23	0-80	6080	1-50	EY87	0-43	UF43	0-80
6F24	0-75	6146	1-60	EY88	0-43	UF80	0-35
6F25	0-75	6360	1-25	EZ40	0-45	UF85	0-40
6F26	0-35	6670	2-50	EZ41	0-45	UF89	0-35
6F28	0-80	6939	2-15	EZ80	0-35	UL41	0-65
6F4	0-50	7197	0-75	EZ81	0-28	UM84	0-30
6J5GT	0-30	7360	1-80	GY601	0-80	UM84	0-30
6J7	0-45	7586	1-25	GZ30	0-40	UY1N	0-50
6K6GT	0-55	7895	1-25	GZ31	0-33	UY11	0-60
6K7	0-35	9002	0-35	GZ32	0-48	UY41	0-45
6K8G	0-35	9003	0-50	GZ33	0-30	UY92	0-50
6K35	0-60	AZ1	0-45	EZ34	0-48	UY85	0-80
6LAGT	0-45	AZ31	0-55	HABC80	0-40	WZ29	0-60
6L7	0-40	CBL1	0-80	HK90	0-35	Z789	1-85
6L18	0-45	CBL31	0-90	KT66	0-20	Z803U	0-90
6LD20	0-40	CY31	0-35	KT88	2-05		
6N7GT	0-40	DAF96	0-42	N78	1-45		
6P1	0-60	DF96	0-45	PAABC80	0-40		
6P25	1-25	DK40	0-55	PC86	0-60		
6P28	0-65	DK92	0-50	PC88	0-60		
6Q7	0-40	DK96	0-42	PC97	0-50		
6SA7	0-40	DL96	0-42	PC90	0-48		
6SG7	0-35	DM160	0-65	PC84	0-30		
6SK7	0-35	DY86	0-33	PC83	0-40		

STEPHENS

ELECTRONICS
P.O. BOX 26
AYLESBURY, BUCKS.

SEND S.A.E. FOR LISTS
GUARANTEE—
TERMS CASH WITH ORDER ONLY.
POST AND PACKING PAYABLE
ON ORDERS UP TO £6, AFTER
THAT FREE, EXCEPT C.R.T.'s

Satisfaction or money refunded.

ALL ITEMS ADVERTISED IN LAST
MONTH'S ISSUE ALWAYS IN
STOCK FOR SAME DAY
DISPATCH

SEMICONDUCTORS BRAND NEW MANUFACTURERS MARKINGS NO REMARKED DEVICES

2N388A 621p	2N3702 171p	ACY18 25p	AF127 171p	BC184 221p	BFY62 221p
2N614 30p	2N3704 221p	ACY19 25p	AF139 371p	BC187 281p	BBX21 371p
2N697 20p	2N3705 20p	ACY20 25p	AF178 45p	BC213L 261p	OC25 50p
2N698 25p	2N3711 20p	ACY21 25p	AF179 45p	BCY32 371p	OC26 321p
2N706 121p	2N3819 35p	ACY22 20p	AF180 521p	BCY58 221p	OC28 621p
2N706A 131p	2N3826 30p	ACY28 20p	AF181 421p	BCY70 20p	OC29 75p
2N830 271p	2N3905 37p	ACY40 20p	AF186 861p	BD115 75p	OC35 40p
2N1132 321p	2N3914 P.A.	ACY41 25p	AF239 421p	BD121 521p	OC36 621p
2N1303 171p	R.C.A.	ACY44 40p	AF282 28p	BD123 851p	OC42 25p
2N1305 251p	40253 P.A.	AD140 40p	BC107 15p	BD124 621p	OC44 20p
2N1306 25p	40398 P.A.	AD142 58p	BC108 15p	BD131 971p	OC45 121p
2N1307 25p	40458 P.A.	AD149 571p	BC109 15p	BD132 971p	OC46 16p
2N1711 35p	2N4021 30p	AD150 621p	BC113 271p	BF115 25p	OC70 15p
2N5147 75p	2N4062 221p	AD161 371p	BC114 371p	BF117 471p	OC71 121p
2N2160 571p	2N4286 171p	AD162 371p	BC115 321p	BF160 P.A.	OC72 181p
2N2614 30p	2N4291 171p	AF102 58p	BC116 621p	BF162 P.A.	OC74 321p
2N2646 571p	AC107 30p	AF106 421p	BC116A 371p	BF163 35p	OC75 221p
2N2905 40p	AC117 80p	AF114 25p	BC117 30p	BF167 20p	OC76 221p
2N2926	AC126 20p	AF115 30p	BC118 321p	BF173 321p	OC77 271p
Green 14p	AC127 25p	AF116 25p	BC134 P.A.	BF178 35p	OC78 25p
Yellow 12p	AC128 20p	AF117 25p	BC135 P.A.	BF179 721p	OC81 20p
Orange 121p	AC164 221p	AF118 60p	BC136 P.A.	BF180 36p	OC81D 20p
2N3053 271p	AC176 25p	AF119 20p	BC137 P.A.	BF181 321p	OC83 25p
2N3055 75p	AC187 621p	AF124 221p	BC138 P.A.	BF184 221p	OC84 25p
2N3391 20p	AC198 371p	AF125 20p	BC142 30p	BF194 221p	OC139 321p
2N3392 20p	ACY17 271p	AF126 20p	BC143 P.A.	BF195 271p	OC140 321p
				BC147 171p	OC170 30p
				BC148 15p	OC171 20p
				BC149 171p	OC200 321p

THE BIG DISCOUNT HOUSE

TURNABLES P.P. 80p

Garrard	£9 95
SP 25 MK III	£8 50
2025 cc with Sonotone 9TAHCD cart.	£9 95
A70 MK II (Transcription Deck)	£13 25
SL 65b	£18 50
AP 76	£26 00
401	£24 00
SL 72b	£25 00
SL 75b	£34 00
SL 95b	£35 00
ZERO 100	
B.S.R. McDonald Range in stock.	
Sonab 75s and 85s in stock.	
Transcriptors Range in stock.	
Goldring-Lenco	
GL 85	£47 50
GL 85/P	£57 00
LID 85	£5 25
GL 75	£28 50
GL 75/P	£36 50
Plinth 75	£7 00
LID 75	£3 75
GL 72	£23 00
GL 72/P	£31 00
Plinth 72	£7 00
Lid 72	£3 75
G.99	£22 00
C.99	£9 00
G.101/P	£22 00
Philips GA 202	£53 00
Philips GA 160	£27 00
Philips GA 105	£15 50
Philips GA 308	£30 00
Thorens TD 150 AB	£40 00
Thorens TD 150 A	£36 00
Thorens TXII	£3 90
Thorens TD 150	£31 50
Thorens TD 125	£61 00
Thorens TD 125 AB	£92 00
Thorens TX 25	£7 50
Connoisseur	P.O.A.

SPECIAL OFFER

A Free 10" L.P. for personal callers buying a complete system Monday to Wednesday.

CARTRIDGES P.P. 15p

Goldring G.850	£4 10
Goldring G.800	£7 00
Goldring G.800/E	£11 75
Goldring G.800/SE	£17 00
Sonotone 9TAHCD	£1 65
Shure M3D	£4 95
Shure M44 5/7	£6 75
Shure M44/E	£7 95
Shure M55/E	£8 75
Shure M75E type II	£14 00
Shure M75E/II	£13 50
Shure M75E	£10 50
Shure V15 II	£26 50
Ortofon MF15E	£18 75
Audio Technica AT66	£4 10
Audio Technica AT55	£3 75
ADC 10E II in stock	
ADC 26	£47 00
ADC 27	£39 00
ADC 550XE	£14 00
Empire 100ZE	£50 00
Empire 999 VE/X	£34 75
Empire 999 TE/X	£20 75
Empire 999 SE/X	£16 75
Empire 999 E/X	£12 50
Empire 999/X	£10 00
Empire 909 E/X	£9 75
Empire 909/X	£7 60
Empire 90EE/X	£7 70

SPEAKER KITS priced per pair

Wharfedale Unit 3	£19 00p
Wharfedale Unit 4	£25 00p
Wharfedale Unit 5	£35 00p
Richard Allan Twin Assembly	£18 00p
Richard Allan Triple Assembly	£27 50p
Richard Allan Super Triple Assembly	£35 00p
KEF	P.O.A.
Goodmans DIN 20 Kit	£19 95p
Peerless 20-2 Cont. D.	£22 00p
Peerless 20-3	£31 00p
Peerless 43-12	£38 00p

A FULL RANGE OF
SINCLAIR
PRODUCTS IN STOCK

SEND A LARGE S.A.E. FOR
OUR COMPLETE LIST OF ALL
HI-FI EQUIPMENT.

NEW AMSTRAD IC 2000
AMPLIFIER OUR PRICE
£31, p.p. FREE

PERSONAL SHOPPERS
WELCOME

OPEN
Mon. to Wed. 9.30 am - 6 pm Fri open until 8.00 pm
CLOSED THURSDAY. SAT. 9.30 am - 5 pm

Personal callers please note that Cheques are only accepted if backed by a relevant bank cheque card. Payment by Barclaycard accepted by arrangement.

All prices subject to change without notice as and when necessary.

AUDI SUPPLIES

Dept No. PW2 50 STAMFORD HILL, LONDON N16 Telephone: 01-806 3611

We are easy to find, 50 yds from Stoke Newington (BR) Station. 106, 67, 149, 76, 73, 249, 243, 247 Buses pass our door.

NEW B.V.A. VALVES

Full list. Return Post Service. Cash with order. Stamped addressed envelope. Post Free over £3.00 order.

DY86/7	40p	U25	75p	OC41	13p
EB91	25p	U26	75p	OC44	13p
ECC82	42p	U37	75p	45	13p
ECC80	40p	U191	72p	71	13p
EF80	40p	U193	41p	72	13p
EF85	41p	U251	87p	73	17p
EF183/4	56p	6/30L2	77p	81	13p
EH90	51p	6AT6	49p	OC81D	13p
EY51	37p	6BW7	69p	OC83	20p
PC86	51p	6CD6	140p	OC170	23p
PC97	41p	6F23	77p	OC171	23p
PC900	51p	20L1	97p	OC200	25p
PCC84	46p	20P4	100p	OC201	25p
PCC89	61p	30C15	69p	2N3819FET	45p
PCF80	51p	30C17	79p		
PCF86	61p	30F5	82p	POWER TRANSISTORS	
PCF801/2	61p	30FL1	64p	OC26	25p
PCF805	65p	33FL2	64p	28	30p
PCF808	67p	30L15	76p	35	25p
PCL82	52p	30L17	72p	AD149	30p
PCL83	61p			2N3055	63p
PCL84	51p	TRANSISTORS		R2008B	100p
PCL805	57p	AC107	15p		
PCL86	51p	126	13p	DIODES	
PL36	75p	127	17p	BY127	20p
PL81	57p	128	13p	BY133	20p
PL83	51p	176	25p	30P12	77p
PL84	60p	ACY17	15p	30PL1	64p
PL500	85p	AF239	37p	30P4MR	100p
PL504	85p	AF186	50p	30P19	75p
PY81	45p	AF139	37p	30PL13	92p
PY82	35p	BC108	13p	30PL14	92p
PY800/1	45p	107	13p	30PL15	92p
R19	65p	BF194	15p		

R. J. BENNISON

WHOLESALE SUPPLIES

1 WHARFEDAILE PLACE, HARROGATE

JERMYN 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk-buyer's prices! Cash with order only.

THIS MONTH:


2N3391	Si NPN Hi Gain (250-500) low noise transistor.	3 for 50p
2N5355	Si PNP Hi Gain, low noise, near complement to above.	3 for 50p
2N2923	25V version of 2N2926. (orange)	7 for 50p
1N4148 (=1N914)	Signal Diode.	18 for 50p
2N3721	Gen. Purpose Transistor	8 for 50p

Post and packing 10p for 1 or 2 packs; 3 packs or more post free.

Order any quantity, till sold (but we regret packs cannot be subdivided).

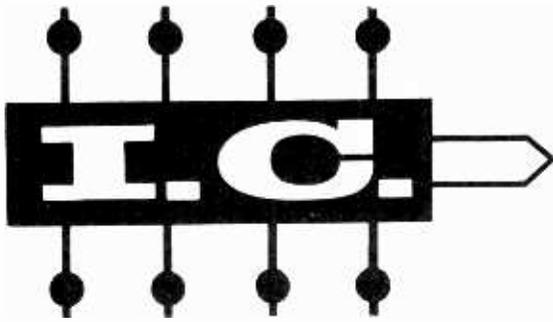P.O. or Cheque payable Jermyn Industries, Vestry Estate, Sevenoaks, Kent.





OF THE MONTH

L.A.J. IRELAND

Number 26

S.G.S. TBA631 TV Audio Detector/Amplifier

IN modern times, after-sales service in the electronics industry is proving to be far too costly so any advance which limits this service to simply plugging in replacement units will be enthusiastically welcomed by both manufacturer and consumer alike. Lately the way has been paved for the introduction of a complete modular TV consisting of plug-in type i.c. sub-systems thereby providing enormous savings in production costs and after-sales service.

In addition to the obvious advantages of lower cost and greater reliability, inexperienced or semi-skilled technicians can perform repairs on a trial and error basis by simply plugging in replacement i.c.'s until the set functions.

Over the past few years great strides have been made particularly in the TV industry in this regard and today practically every i.c. manufacturer has on offer an integrated form of the i.f. sound amplifier and detector. In fact some firms included an audio preamp on the same chip as the i.f. strip and so it was only a logical step from here that eventually the complete audio power amplifier and i.f. sound section should appear in integrated form.

S.G.S. have recently released a new i.c. device capable of performing just these functions (TBA631), with the very attractive feature of having a price tag less than £3 and an audio power output in excess of 2.5 watts.

As far back as Dec. 1967 PW published a design for an i.c. f.m. tuner using an RCA type CA3014. Other manufacturers quickly followed with remarkably similar versions of this i.c. and in fact the wide band limiting section of the TBA631 is almost identical with it. However, the similarity ends there as a coincidence type detector, low frequency separator and low frequency preamp follows before the recovered audio signal enters the more or less separate power amplifier, on the silicon chip.

Specification

The electrical specifications of the TBA631 are quite good. It gives an almost flat frequency response from 50Hz to 10MHz with an input threshold limiting voltage of 100 microvolts at 5MHz rising to 230 microvolts at 10MHz. Total harmonic distortion at an output power of 2 watts is less than 1% and this provides adequate volume for most domestic purposes.

A separate power supply is used for the r.f. and demodulation part of the circuit and this is designed

to operate at any voltage between 4.5 and 15V. Up to 24 volts can be applied to the power amplifier and with a quiescent current of a mere 18mA with a 12 volt supply, the i.c. should prove particularly useful for inclusion in portable tv systems.

The i.c. consists of an i.f. limiting amplifier section following the well established differential amplifier patterns. A phase shift network applied between pins 10 and 11 allows for the demodulation of the inter-carrier signal and, electrically isolated from the i.f. stages, follows a typical i.c. power output stage.

Applications

Fig. 1 shows a practical application of the TBA631 in the sound section of a TV receiver. Overall savings in components and simplification of alignment is fairly obvious and of course a similar circuit with a rearrangement of coil values can be made to function admirably as the i.f. and output stages of an f.m. tuner. The drop in gain of 4dB in the i.f. stage as compared to its operation at 5.5MHz will hardly be noticed.

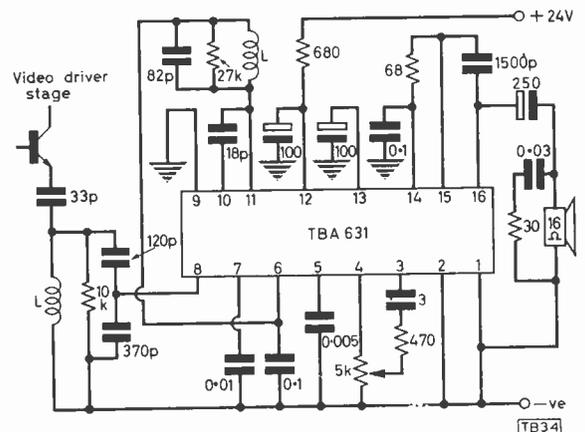


Fig. 1: In this practical application, inductors L may consist of 55 turn of 36g. enamel wire on a $\frac{1}{4}$ in former, for 5.5MHz.

At its price and specification the TBA631 is a good buy and no doubt its appearance will shortly be felt in the consumer TV market. It is available from any S.G.S. distributor or from Neltronics, 14 Wellington Park, Belfast, BT9 6DJ.

TAKE 20

JULIAN ANDERSON

A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.

I CONFESS that I don't know very much about Mr. Darlington but his name has been given to a transistor circuit configuration which has many uses in many fields of electronics. Some months ago we featured an ultra simple audio amplifier using two transistors, a resistor, a loudspeaker, a capacitor and a volume control and from the reaction of readers, it was a highly popular little circuit.

This month we are using basically the same circuit configuration but this time it is for a simple medium wave radio. It is the aim of this column to get the best possible use out of the minimum number of components and this circuit certainly achieves that. No external aerial or earth are required and reception may be expected of all local and some more powerful distant stations. The circuit operates from a PP3 battery and the small size of this and the other components means that the circuit lends itself to miniaturisation.

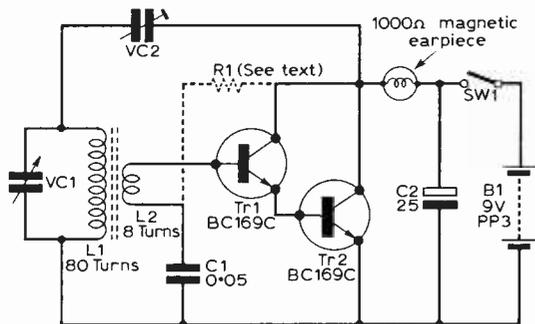


Fig. 1: The Circuit.

TB18

The magic of the Darlington Pair lies in the massive amplification available; the gain of the combined pair is equal to the product of the individual transistor gains. So, taking the best case, where both transistors have a gain of 900 (the maximum quoted for a BC169C), the circuit gain will be a massive 810,000. We are unlikely, however, to have two such high gain transistors but even with the minimum gain versions we shall have plenty of amplification in what is effectively a single stage.

The r.f. signals are induced into the tuned circuit comprising VC1 and L1 and are transformed by L2 and fed to the base of Tr1. This feeds directly to Tr2 where the signal is further amplified and applied to the magnetic earpiece. Astute readers will note that there is no obvious way in which the r.f. signals are detected and smoothed. Detection takes place in two ways: a circuit of this simplicity is hardly likely to amplify completely linearly and this means that there is a degree of detection. Alternatively there is a small degree of regeneration applied to the tuned circuit via VC2 and this aids detection. The self-capacity of the earpiece has been found sufficient to smooth the r.f. to allow it to be heard.

No. 33

TWO TRANSISTOR RADIO

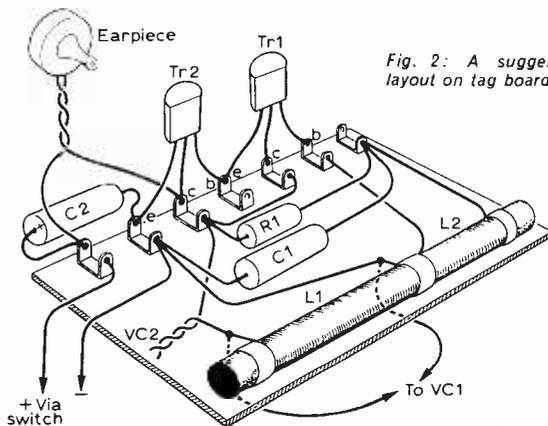


Fig. 2: A suggested layout on tag board.

TB19

★ components list

R1	See text	1p
C1	0.05µF	4p
C2	25µF 25V	6p
Tr1	BC169C	11p
Tr2	BC169C	11p
VC1	500pF	30p
VC2	See text	
L1, L2	See text	10p
Magnetic earpiece	See text	25p
		98p

Prices are those recently advertised and may have changed. No allowance is made for minimum order costs or for postage and packing and these should be checked carefully before ordering.

R1 is shown dotted in the circuit. The value of this resistor will depend entirely on the individual transistors used and it is not possible to give an absolute value for all types—indeed with several combinations of transistors used in the prototype it was not even found necessary; the gain is so high that the tiny leakage currents were sufficient to apply the bias. However a resistor will normally be required and the value may lie anywhere between 470kΩ and 10MΩ.

The aerial comprises 80 turns of enamelled copper wire (about 30 s.w.g. but this is not critical) wound on a 3in. length of 3/8in. diameter ferrite rod. L2 comprises a further 8 turns. VC2, as shown is made up from two short lengths of insulated wire, twisted together for optimum performance over the complete band.

The magnetic earpiece is shown in the circuit as 1000Ω impedance; this is the ideal but any type between 250Ω and 2,000Ω will suffice. Low impedance types (usually 8Ω) and crystal types will not work in this circuit.

A suggested layout is shown in Fig. 2 on a short piece of tagboard with the tags along one side removed. If, by twisting VC2 together, there is no improvement or tendency to oscillation, then the connections to L2 should be reversed.

EVERYTHING BRAND NEW AND TO SPECIFICATION

No surplus, clearance lines or manufacturers' seconds.

ELECTROVALUE

Electronic Component Specialists

SEMI-CONDUCTORS

All power types with free insulating sets

1N914	5p	AC142H	25p	BD131	79p
1N916	10p	AC142HK	29p	BD132	86p
1N1763A	24p	AC153K	22p	BD136	38p
1N3754	20p	AC176	16p	BD136	44p
1N5389	21p	AC176K	17p	BD136	92p
1N5407	28p	AC187K	17p	BF15	23p
1844	9p	ACY11	31p	BF167	18p
18940	5p	ACY18	19p	BF173	25p
2N696	17p	ACY19	23p	BF177	19p
2N697	18p	ACY20	20p	BF194	14p
2N706	12p	ACY21	21p	BF195	15p
2N930	29p	ACY22	21p	BF254	14p
2N1132	26p	ACT39	63p	BF255	15p
2N1302	21p	ACY40	17p	BFX29	31p
2N1303	19p	ACY41	18p	BFX84	25p
2N1304	26p	ACY44	31p	BFX85	32p
2N1305	26p	AD142	50p	BFX87	29p
2N1306	33p	AD149	58p	BFX88	26p
2N1307	33p	AD150	50p	BFY50	23p
2N1309	36p	AD161	33p	BFY51	20p
2N1613	23p	AD162	36p	BFY52	23p
2N1711	26p	AF114	24p	BFX20	16p
2N1893	54p	AF115	24p	BY164	45p
2N2147	95p	AF116	22p	RY238	18p
2N2218	34p	AF117	23p	RYX38-300	82p
2N2218A	26p	AF118	23p	RYX38-300R	38p
2N2219	38p	AF124	24p	C407	17p
2N2270	62p	AF125	24p	C762	19p
2N2369A	19p	AF126	22p	EA403	10p
2N2483	35p	AF127	22p	EB383	10p
2N2484	42p	AF139	33p	EC401	18p
2N2646	47p	AF239	36p	EC402	17p
2N2904	38p	ASY26	27p	NKT211	25p
2N2905	44p	ASY27	36p	NKT212	25p
2N2905A	47p	ASY28	27p	NKT213	25p
2N2924	20p	ASY29	36p	NKT214	23p
2N2925	22p	AU111	97p	NKT217	50p
2N2926	11p	B30C250	24p	NKT261	21p
2N3053	27p	B1912	66p	NKT271	18p
2N3054	60p	B5041	72p	NKT274	18p
2N3702	13p	BA102	22p	NKT403	65p
2N3703	13p	BA130	22p	NKT405	79p
2N3704	13p	BA145	27p	NKT613F	34p
2N3705	13p	BA156	13p	NKT674F	20p
2N3706	13p	BI103B	16p	OA47	8p
2N3708	10p	BI103G	16p	OA90	5p
2N3709	11p	BC108	11p	OA91	5p
2N3710	13p	BC109	12p	OA95	6p
2N3711	13p	BC122	21p	OA200	9p
2N3794	15p	BC125	15p	OA202	10p
2N3819	23p	BC126	22p	OC19	50p
2N3820	53p	BC140	30p	OC25	42p
2N3904	35p	BC147	10p	OC29	76p
2N3906	35p	BC148	9p	OC35	60p
2N4036	55p	BC149	10p	OC36	65p
2N4058	13p	BC153	19p	OC41	42p
2N4059	10p	BC159	11p	OC44	42p
2N4060	11p	BC177	14p	OC70	21p
2N4061	11p	BC178	13p	OC71	38p
2N4124	18p	BC179	14p	OC75	40p
2N4126	27p	BC182L	11p	OC81	25p
2N4284	15p	BC183L	10p	OC81D	25p
2N4286	15p	BC184L	11p	OC83	25p
2N4289	15p	BC186	42p	OC84	25p
2N4291	15p	BC212L	16p	P346A	26p
2N4410	24p	BC213L	16p	S2CN1	10p
2N4991	62p	BC214L	16p	SD1	10p
2N5062	61p	BC257	9p	8D4	12p
2N5457	49p	BC259	9p	V763	25p
2N5459	49p	BC267	17p	W106B1	45p
40250	71p	BC268	15p	W02	40p
40251	89p	BC269	17p	WP02	95p
40381	55p	BC300	49p	ZTX300	14p
40382	68p	BC301	37p	ZTX301	16p
40602	52p	BC303	60p	ZTX302	22p
AC107	48p	BCY30	60p	ZTX303	22p
AC126	20p	BCY31	75p	ZTX304	27p
AC127	20p	BCY70	18p	ZTX300	23p
AC128	20p	BCY71	33p	ZTX331	27p
AC141H	34p	BCY72	15p	ZTX500	18p
AC141HK	37p	BD130	50p		

Add good appearance to your building

SIEMENS CAPACITORS



These electrolytic capacitors are all in the same style and colour and greatly enhance the appearance of the finished article when built. With axial leads and clearly marked polarity.

0.47µF/100V., 2.2/100V., 4.7/100V., 7p: 10/100V., 8p: 22/100V., 9p: 470µF/100V., 47µF/100V., 220/35V., 100/63V., 470/25V., 12p: 220/50V., 1000/16V., 470/35V., 220/33V., 100/100V., 15p: 1000/25V., 470/50V., 22p: 2200/16V., 1000/35V., 220/100V., 27p: 4700/16V., 39p. (Page 34 of catalogue for full list of more than 60 values.)

SIEMENS TTL I.C.s—wide range in stock at all time low prices.

Advertisement No. PW63A

DISCOUNTS

10% discount is allowed on orders for £5 to £15 in value.
15% discount allowed on orders over £15. No discount on items marked *Nett*. Prices subject to alteration without notice.

CATALOGUE

The latest (1971) Electrovalue catalogue contains 64 pages packed with hundreds of items and valuable illustrated information. Post free 10p.

RESISTORS 10%—5%—2%

Code	Power	Tolerance	Range	Values	1 to 9	10 to 99	100 up
C	1/20W	5%	82-220K	E12	9	8	7
C	1/8W	5%	4.7-470K	E24	1	0.8	0.7
C	1/4W	10%	4.7-10M	E12	1	0.6	0.7
C	1/2W	5%	4.7-10M	E24	1.2	1	0.9
C	1W	5%	4.7-10M	E12	2.5	2	1.9
MO	1/2W	2%	10-1M	E24	4	3.5	3
WW	1W	10% ± 1/20Ω	0.22-3.9	E12	7	7	6
WW	3W	5%	12-10K	E12	7	7	6
WW	7W	5%	12-10K	E12	9	9	8

Codes: C—carbon film high stability low noise
MO—metal oxide Electrofil TR5 ultra low noise
WW—wire wound Plesey

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 72, 91 and their decades. Prices are in pence each for same ohmic value and power rating, NOT mixed values. (Ignore fractions of 1p on total value of resistor order.)

VEROBOARD. All popular sizes: INDICATOR LIGHTS; DIN CONNECTORS, etc.

MULLARD polyester C280 series

0.1W 20%, 0.01; 0.022; 0.033, 0.047 3p ea. 0.068; 0.1, 0.15 4p, 0.22 5p, 10%; 0.33 7p, 0.47 8p, 0.68 11p, 1µF 14p, 1.5µF 21p, 2.2µF 24p.

MULLARD SUB-MIN ELECTROLYTIC

C420 range axial lead 6p each
Value (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5.6/4; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 100/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 41p; 1000/100 82p; 2000/25 37p; 2000/50 57p; 2000/100 £1.43; 2500/64 77p; 2500/70 95p; 5000/25 62p; 5000/50 £1.10; 5000/100 £2.91; 10000/50 £2.40.

SIEMENS' 5% TOLERANCE POLYCARBONATE CAPACITORS

250V up to 0.1mF, 100V 0.1mF and above.
0.01, 0.12, 0.015, 0.018, 0.022, 0.027 5p
0.033, 0.047, 0.056, 0.068, 0.081, 0.01, 0.1 to 0.22 6p.
0.33, 0.39, 9p, 0.47, 10p, 0.56, 13p, 0.68, 15p.

S-DeCS

Manufacturer's prices increase roughly by 20% on these on pages 51, 52 and 53 since printing our catalogue. S-DeC £1.44, Four pack £5.10, DeCSTOR pack £2.88, T-Dec, may be temperature-cycled (208 points), £2.88, µDecA, £3.18, µDecB, £5.94. Also I.C. carriers.

AMPLIFIERS

30 WATT BAILEY PARTS

Transistors and PCB for one channel £6.46

Capacitors, resistors (metal Oxide), and transistors, one channel. £8.41
Complete unregulated power supply pack. £4.75

Suitable heatsink 10DN400C. 55p

MAINLINE

70W. main amplifier module £12.60 nett.

Power supply kit £6.00 nett
Suitable pre-amp kit £6.25 nett (less chassis & panel)

Above for mono only.

STEREO PACK OF UNITS for building into your own cabinet—2 power amps, pre-amp control unit, power supply unit and matched controls, nett £38.40.

ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 15p each
1W: 6.8V to 82V 27p each 1.5W: 4.7V to 75V 60p each
Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

CARBON TRACK POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.
Single gang linear 100 Ω to 2.2M Ω 12p
Single gang log 4.7K Ω to 2.2M Ω 12p
Dual gang linear 4.7K Ω to 2.2M Ω 42p
Dual gang log 4.7K Ω to 2.2M Ω 42p
Log/antilog 10K, 47K, 1M Ω only 42p
Any type with ½ A D.P. mains switch, extra 12p

Please note: only decades of 10, 22 and 47 are available within ranges quoted.

CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100 Ω, 220 Ω, 470 Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10M Ω vertical or horizontal mounting 5p each.

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone.)

POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2. Overseas orders welcome: carriage and insurance charged at cost.

U.S.A. CUSTOMERS are invited to contact ELECTRO-VALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081 for special prices

NEW LOW PRICE OFFER!!

PEAK SOUND ENGLEFIELD 840A AMPLIFIER
20-20 watt R.M.S. into 8 Ω speakers. Unique add-in facility for FM stereo tuner, and other original features. A de-luxe job in every way. Maker's R.R.P. £49.50. From Electrovalue, nett £33.75 (Carr. & Packing to anywhere in U.K. add 75p)

ELECTROVALUE

(Dept. PW.172) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY

Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) Telex 264475

FIND BURIED TREASURE!



ONLY £2-37

This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC. ETC.** Extremely sensitive. **NO SIGNIFICANT PRESENCE OF CERTAIN OBJECTS BURIED SEVERAL FEET BELOW GROUND** No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards with the clear, easy to follow, step-by-step, fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. **ONLY £2-37 + 27p p. & p.** (Sectional handle as illustrated 75p extra). Parts available separately. Made up looks worth £15!

Eavesdrop on the exciting world of Aircraft Communications

V.H.F. AIRCRAFT BAND CONVERTER ONLY £2-37

Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, KINGWAY, PRESTWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place close to any ordinary medium wave radio (even tiny portables). **NO CONNECTIONS WHAT-EVER NEEDED!** ONLY £2-37 + 23p p. & p. for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

SHORTWAVE TRANSISTOR RADIO



only £2-25

Anyone from 9 years up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 75 stations logged on rod aerial in 80 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2" Only £2-25 + 17p p. & p. Kit includes cabinet, screws, instructions, etc. (Parts available separately).

INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY £2-75

CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. **No soldering necessary.** Works off standard batteries, extremely economical. Size only 3" x 4 1/2" x 1 1/2"—take it anywhere. Kit includes case, nuts, wire, screws, etc. **SEND £2-75 + 25p p. & p.** (parts available separately).

ELECTRONIC ORGAN



ONLY £2-75

Don't confuse with ordinary electronic organs that simply blow air over mouth organ type reeds etc. Fully transistorised. **SELF TUNING LOUDSPEAKER.** Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne" etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real live portable electronic organ. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED.** No soldering necessary, Simple as ABC to make. **Anyone over nine years can build it easily in one short evening following the fully illustrated step-by-step, simple instructions.** ONLY £2-75 + 23p p. & p. for kit including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Find buried treasure with this READY BUILT & TESTED TREASURE LOCATOR MODULE

ONLY £4-95

FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. **penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC.** Signals exact location by "beep" pitch increasing as you near buried metallic objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! £4-95 + 30p carr. etc. (High quality Danish Stethoscope headphones £2-75 extra if required). **EXCHANGE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.**

BUILD 5 RADIO AND ELECTRONIC CIRCUITS

only £1-97



Amazing Radio Construction set! Become a radio expert for £1-97. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 37p extra as illus. (if required) (parts available separately) no soldering necessary. **SEND £1-97 + 23p p. & p.**

SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHE YOUR NERVES! Don't underestimate the use of this fantastic new design—the RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rather mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. IF YOU WORK IN NOISY OR DISTRACTING surroundings, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). **CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE** using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, components, nuts, screws, wire, etc. no soldering. **£2-25 + 25p p. & p.** Parts available separately

Only £2-25

CONCORD ELECTRONICS LTD. (PW3) 8 Westbourne Grove, London, W.2. Callers welcome 9 a.m.-6 p.m. inc. Saturday

FANTASTIC BARGAIN OFFER!

TRANSEUROPEAN

Transistorised Stereophonic High Fidelity AM/FM Tuner Amplifier System.

This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM, Short, medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in. matching elliptical speakers. A complete Hi-Fi Stereo Radiogram at less than half normal price. **SPECIAL OFFER £44**

Credit Terms available First monthly payment of £5-83 followed by 9 monthly payments of £4-95. Total Credit Sale Price £49-50. Send £5-83 today.

FABULOUS VALUE

Hi-Fi stereo at a new low. System Ten-Ten; 4 speed BSR autochanger with cue and pause control plus solid state amplifier, 2 speed BSR total output. Frequency response 20-20,000 Hz.

ONLY £4-93 DOWN

CREDIT SALE TERMS: Send £4-93 (being the first of TEN monthly payments of £4-05 plus 88p. Carriage and Packing). To be followed by NINE monthly payments of £4-05 (Total Credit Sale Price £40-50).

EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.

CALLERS WELCOME PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name _____ Address _____ PW2 7Z

LEWIS radio 100, Chase Side London N.14 Tel: 01-886 3733/9666

Post coupon NOW for FREE leaflets

VALVES

SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 185, 1T4, 354, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1-02. DAF96, DF96, DK96, DL96, 4 for £1-48.


1R5	-28	30C17	-76	EABC80	-32	EM81	-41	PCL84	-34	UBC41	-52
1R4	-22	30C18	-81	EP42	-50	EM84	-32	PCL85	-38	UBF80	-34
1T4	-18	30F5	-64	EB41	-40	EM87	-34	PCL86	-38	UBF89	-32
354	-21	30FL1	-61	EB71	-41	EF81	-33	PCL88	-65	UCB84	-32
3V4	-37	30FL12	-69	EB33	-40	EF82	-29	PCL89	-32	UCB85	-36
5U4G	-31	30FL14	-68	EB41	-54	EZ40	-43	PEN44	-77	UCF80	-32
5V4G	-36	30L1	-29	EB90	-22	EZ41	-43	PEN36C	-70	UCH42	-58
5Y3GT	-26	30L15	-57	EBF80	-32	EZ80	-22	PFL200	-52	UCH81	-32
6Z4G	-35	30L17	-67	EBF89	-29	EZ81	-22	PL36	-49	UCB82	-32
930L2	-54	30PL1	-57	EC81	-27	GZ30	-34	PL81	-44	UCF83	-55
6AL5	-21	30P12	-72	EC82	-22	GZ32	-40	PL84	-47	UF41	-56
6AM6	-18	30P19	-57	EC83	-25	GZ34	-48	PL89	-31	UF89	-30
6AQ5	-22	30PL1	-60	EC85	-34	KT41	-77	PL83	-33	UL41	-57
6AT6	-20	30PL13	-75	EC90A	-54	KT61	-55	PL84	-30	UL44	£1-00
6AU6	-20	30PL14	-65	ECF80	-27	KT66	-78	PL800	-63	UL84	-30
6BA6	-20	30PL15	-90	ECF82	-28	LN319	-63	PL504	-63	UM84	-22
6BE6	-21	35L6GT	-45	ECB35	-30	LN329	-72	PM84	-33	UY41	-42
6BJ6	-41	35W4	-25	ECB42	-61	LN339	-63	PT25	-95	UY85	-25
6BW7	-52	35Z4GT	-25	ECH81	-29	N78	-87	PT32	-55	VF4B	-77
6F14	-40	807	-45	ECH83	-40	P61	-40	PY33	-55	X78	£2-75
6F23	-68	6063	-62	ECH84	-36	PABC90	-34	PY81	-25	X79	£2-75
6F22	-53	AC/VF2	-77	ECL80	-30	PC86	-47	PY82	-25	Z77	-22
6F71	-19	B45	-61	ECL82	-31	PC88	-47	PY83	-23	Transistors	-19
6K8G	-17	B29	-62	ECL86	-37	PC96	-43	PY89	-32	AC10	-17
6Q7G	-35	CC35	-67	EP39	-38	PC97	-39	PY800	-24	AC127	-18
68N70T	-30	CY31	-30	EP41	-60	PC900	-31	PY801	-34	AD140	-37
6V6G	-23	DAF91	-22	EP80	-23	PC884	-20	R19	-30	AF115	-20
6V6GT	-23	DAF96	-38	EP85	-28	PC86	-26	R20	-58	AF116	-20
8T4	-23	DF92	-38	EP86	-30	PC88	-40	U25	-64	AF117	-20
6X6GT	-28	DF91	-18	EP89	-26	PC89	-45	U36	-56	AF118	-45
10P13	-58	DF96	-36	EP91	-13	PC189	-48	U47	-64	AF123	-17
12AT7	-17	DH77	-20	EP98	-66	PC805	-58	U49	-56	AF127	-17
12AU6	-20	DK32	-33	EP183	-28	PCF80	-28	U30	-26	OC26	-25
12AU7	-20	DK91	-28	EP184	-31	PCF82	-31	U52	-31	OC44	-12
12AX7	-22	DK92	-38	EP190	-35	PCF86	-46	U78	-59	OC45	-12
198BG4	-87	DK96	-38	EL33	-62	PCF90	-58	U161	-59	OC71	-12
20F2	-67	DL36	-40	EL34	-45	PCF801	-28	U193	-42	OC72	-12
20P3	-77	DL92	-26	EL41	-54	PCF802	-40	L251	-64	OC75	-12
20P4	-98	DL94	-37	EL42	-23	PCF805	-61	U301	-38	OC81	-12
26L6GT	-20	DL96	-38	EL90	-28	PCF806	-56	U329	-68	OC81D	-12
28U4GT	-57	DY86	-24	EL95	-33	PCF808	-88	U801	-80	OC82	-12
30C1	-62	DY87	-24	EL90	-62	PL42	-32	TA BC90	-32	OC82D	-12
30C15	-58	DY802	-33	EM80	-41	PCL83	-57	UAF42	-51	OC170	-33

READERS RADIO


85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Post/Packing on 1 valve 6p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.

GOING BACK...

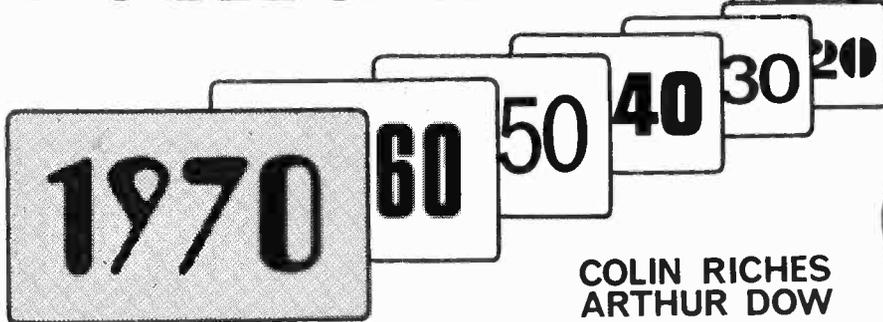

COLIN RICHES
ARTHUR DOW

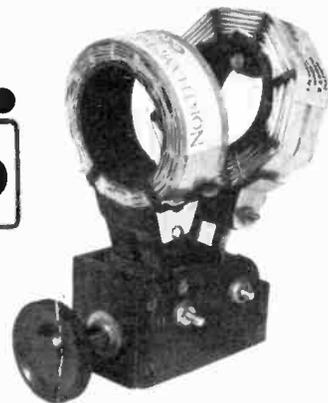


QUITE a few of our readers, interested in the history of wireless, will have paid a visit to the Science Museum in South Kensington, London, and seen the collection of the old and not so old equipment on view there. The old gallery has now been moved to the third floor and on October 26th last a new and resplendent Telecommunications Gallery was formally declared open by the Minister for Posts and Telecommunications, the Rt. Hon. Christopher Chataway, M.P. Later the Minister, accompanied by Sir Harold Bishop, Chairman of the Museum's Advisory Council, toured the gallery with other distinguished visitors.

The North side of the gallery is devoted to the development of telegraph and telephone systems and many pieces of equipment from the early 1800's are displayed. The South side of the gallery is perhaps of more interest to our readers since it covers



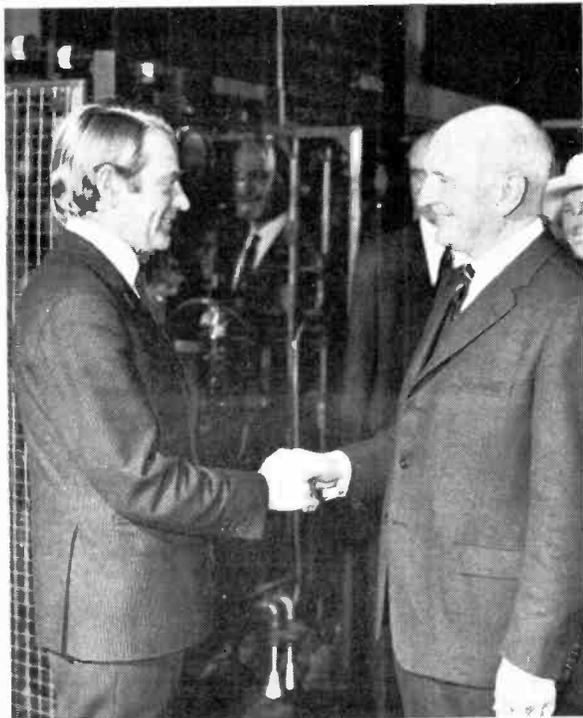The spacious nature of the new gallery is illustrated in this view of part of the collection of Army equipment.



The Minister for Posts and Telecommunications (left) is greeted by Sir David Follett, Director of the Science Museum.

radar and radio communications as well as broadcasting. Many examples of equipment, both civil and military, are exhibited in well-lit spacious showcases with detailed descriptive explanations.

Many were the oo's and ah's among us older visitors as we spied transmitters and receivers from the early days of the last war! Memories were stirred as thoughts went back to the problems of getting that last watt from a transmitter in a bouncing aircraft or bumping tank!


The equipment on view traces the history of wireless from the late 1800's and the discovery of the existence of electromagnetic waves by Hertz, who, although proving that the waves could pass through solid objects, took the matter no further. This aspect was left to Marconi who developed a practical wireless telegraphy system despite the very crude equipment of the time and the scorn of the "line-of-sight only" scientists of the day.

Great progress was made when shipping companies accepted the idea of ship-borne wireless realising its value from the commercial point of view and its potential as a means of getting assistance for their ships when they ran into trouble.

The next great push forward came with the 1914-18 war when rapid developments provided radio telegraphy and telephony facilities for the forces on land, sea and in the air. The crude spark and arc

days were over and valves came into their own. Following the early experimental work of the radio amateurs long distance commercial circuits were established on short waves.

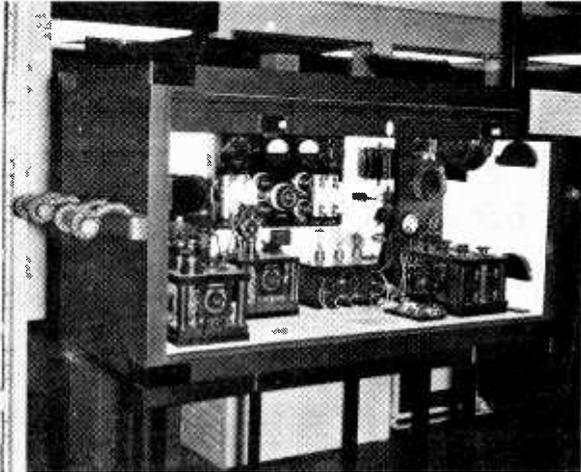Subsequent discoveries are hardly "vintage" having taken place in the lifetime of many of us but even so the early radar equipment and certainly the Army's communication gear of that time looks crude beyond belief.



A complete 120watt field wireless station of 1918.

Broadcasting and TV have not been forgotten in the new gallery which, inevitably, includes Baird's 30-line television receiver. A visit to the exhibition is a must and after spending a while in the gallery one can return to the present day by visiting the amateur radio station GB2SM now re-sited adjacent to the new gallery.

MAXWELL

by G8DSH



"You're biased!"

CHARLES MOLLOY

THE Medium Wave Column

"IMPOSSIBLE," I thought, writes **Ian Rennison** of Horsham, Sussex, when he read reports in *Practical Wireless* of American and Canadian stations being heard in UK on the medium waves. Ian now has a Trio 9R59D and he sends an impressive list of stations heard using a medium wave loop antenna in his bedroom.

CBNA 600kHz St. Anthony Nfld; CKCM 620 Grand Falls Nfld; CBN 640 St. John's Nfld; WNBC 660 New York; WOR 710 New York; CJOX 710 Grand Bank Nfld; WSB 750 Atlanta Georgia; WJR 760 Detroit Michigan (The Great Voice of the Great Lakes); WABC 770 New York; WCBS 880 New York; CJON 930 St. John's; CBM 940 Montreal; CHER 950 Sydney N.S.; CHNS 960 Halifax N.S.; WINS 1010 New York (All-news all the time); CFRB 1010 Toronto; WHN 1050 New York; CBA 1070 Moncton N.B.; WBAL 1090 Baltimore; WNEW 1130 New York; WHAM 1180 Rochester N.Y.; WOWO 1190 Ft. Wayne, Indiana; WCAU 1210 Philadelphia; WLOB 1310 Portland, Maine (5kW); WKLX 1350 Portsmouth, Virginia (5kW); WMYR 1410 Fort Myers, Florida (1kW at night); WTOP 1500 Washington D.C.; WMBX 1510 Boston; CJRS 1510 Sherbrook, Quebec; WKBW 1520 Buffalo, N.Y.; WCKY 1530 Cincinnati, Ohio.

Hugh Martin (G3XCD) of Wallasey, Cheshire, abandoned the Amateur Bands temporarily and connected his 20m dipole with 30ft downlead, to a BC946 medium wave 'Command' receiver. The time was 2340 hrs and he heard WINS 1010kHz New York and CBA 1070kHz Moncton N.B. This one-band receiver covers 520kHz to 1530kHz and only requires to be modified to convert from 28V to mains working. The MW Command receiver is not often available from commercial sources these days, but one can often be obtained, suitably modified, from private hands, for quite a modest sum.


George Harpur of Brentwood, Essex, logged 4 North American medium wave stations between 2300hrs and 2330hrs, the first time he tried out his new Eddystone 680X. George raises some interesting questions on operating techniques. Always turn OFF the a.v.c. when DXing on the medium waves. Set the l.f. (audio) gain control to a comfortable level and control the incoming signal with the r.f. gain. If the a.v.c. is left ON and an attempt is made to listen to a weak station only a kHz or two from a strong one, then the strong signal will operate the a.v.c., reduce the receiver gain and the weak station will be missed.

Conditions on the medium waves are better now than for several years and will continue to improve as we approach the minimum of the current sunspot cycle. Many North Americans can be heard before midnight, WINS 1010 New York being particularly prominent.

Send logs and information about the Medium Waves to:
132 SEGERS LANE, SOUTHPORT
PR8 3JG

new

Super IC-12

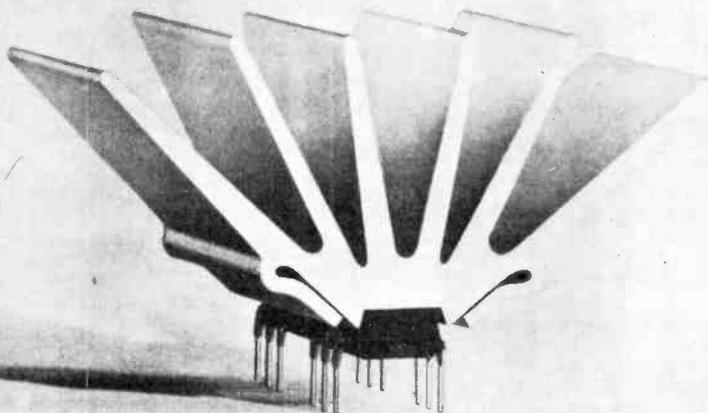

High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

Output power 6 watts RMS continuous (12 watts peak).

Frequency Response 5 Hz to 100KHz \pm 1 dB.

Total Harmonic Distortion Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

Load Impedance 3 to 15 ohms.

Power Gain 90dB (1,000,000,000 times) after feedback.

Supply Voltage 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

Size 22 x 45 x 28 mm including pins and heat sink.

Input Impedance 250 Kohms nominal.

Quiescent current 8mA at 28 volts.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.



Price, inc. FREE printed circuit board for mounting.



£2.98 Post free

Sinclair Radionics Ltd, London Rd. St. Ives Huntingdonshire PE17 4HJ
Telephone St Ives (048 06) 4311

sinclair

Sinclair Project 60

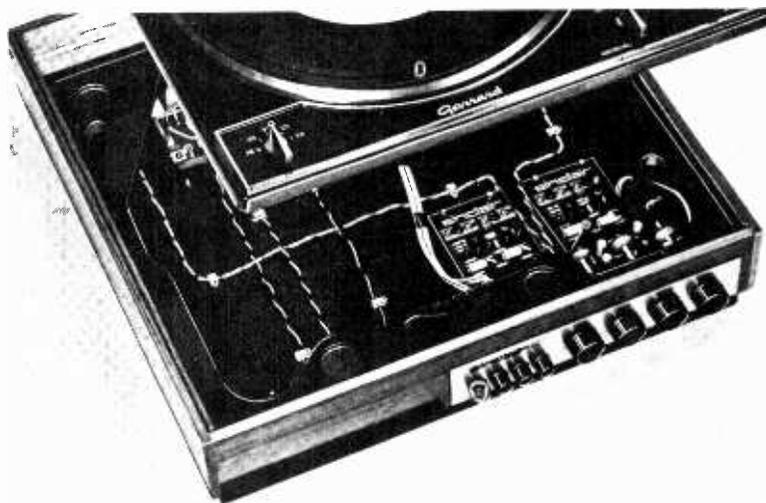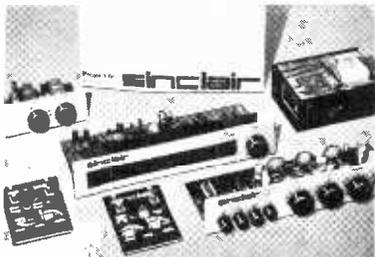The World's leading range of high fidelity modules



New!

Project 605

The easy way to buy and build Project 60



Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

All you need for a superb 30 watt high fidelity stereo amplifier.

Sinclair Radionics Limited, London Road,
St. Ives, Huntingdonshire PE17 4HJ.
Tel: St. Ives (048 06) 4311

sinclair

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.


Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
20 + 20 W. stereo amplifier for most needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
20 + 20 W. stereo amplifier with high performance spkrs.	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc	£26.90
40 + 40 W. R.M.S. de-luxe stereo amplifier	2 x Z.50s, Stereo 60, PZ.8, mains trsfmr	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. Filter Unit (£5.98) may be added as required.

from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

Z.30 & Z.50 power amplifiers

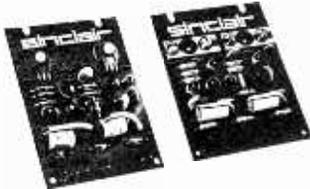

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

Frequency response: 30 to 300,000Hz \pm 1dB.

Distortion: 0.02% into 8 ohms.

Signal to noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance

Size: 14 x 80 x 57 mm.

Z.30

Built, tested and guaranteed with circuits and instructions manual. **£4.48**

Z.50

Built, tested and guaranteed with circuits and instructions manual. **£5.48**

Project 60 Stereo F.M. Tuner



First in the world to use the phase lock loop principle


The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB **Sensitivity:** 2 μ V for 30dB quieting; 7 μ V for lock-in over full deviation. **Squelch level:** 20 μ V. **A.F.C. range:** \pm 200 KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz - 15 KHz (\pm 1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Power on/tuning/stereo. **Size:** 93 x 40 x 207 mm.

£25

Built and tested. Post free.

Stereo 60 Pre-amp/control unit

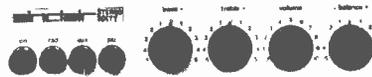

Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS—Input sensitivities: Radio - up to 3mV. Mag. p.u. 3mV. correct to R.I.A.A curve \pm 1dB; 20 to 25,000 Hz. Ceramic p.u. - up to 3mV; A.L.X. - up to 3mV. **Output:** 250mV.

Signal to noise ratio: better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE \pm 15 to \pm 15dB at 10 KHz; BASS \pm 15 to \pm 15dB at 100Hz.

Front panel: brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

£9.98

Built, tested and guaranteed.

Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

PZ.5 30 volts un stabilised **£4.98**

PZ.6 35 volts stabilised **£7.98**

PZ.8 45 volts stabilised (less mains transformer) **£7.98**

PZ.8 mains transformer **£5.98**



A.F.U. High & Low Pass Filter Unit



For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less

loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages - rumble (high pass) and scratch (low pass). Supply voltage - 15 to 35V. Current - 3mA. H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V supply) (0.02% at rated output. **Size:** 66 x 40 x 90 mm.

Built tested and guaranteed. **£5.98**

The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send _____

Name _____

Address _____

I enclose cash/cheque/money order.

PW272

Sinclair Q16/Micromatic

Q16 High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies without loss.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

Specifications:

Construction: Special sealed seamless sound or pressure chamber with internal baffle.

Loading: up to 14 watts RMS.


Input Impedance: 8 ohms.

Frequency response: From 60 to 16,000 Hz. confirmed by independently plotted B and K curve.

Driver unit: Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension for excellent transient response.

Size and styling: 9½ in. square on face x 4½ in. deep with neat pedestal base. Black all over cellular foam front with natural solid teak surround.

Price £8.98.

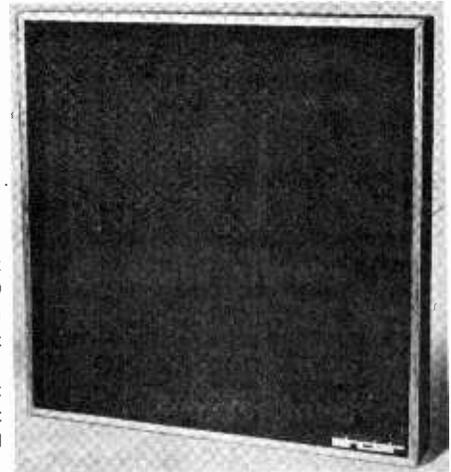

Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided, matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

Specifications:

Size: 36 x 33 x 13 mm (1.8 x 1.3 x 0.5 in.)

Weight: including batteries, 28.4 gm (1 oz.)

Case: Black plastic with anodised aluminium front panel and spun aluminium dial.

Tuning: medium wave band with bandspread at higher frequencies (550 to 1,600 KHz).

Earpiece: Magnetic type.

On/off switching: By inserting and withdrawing earpiece plug.

Kit in pack with earpiece, case, instructions and solder **£2.48.**

Ready built, tested and guaranteed, with earpiece **£2.98.**

Two Mallory Mercury batteries type RM675 required from radio shops, chemists, etc.



To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send _____

Name _____

Address _____

for which I enclose cash/cheque/money order

PW272

Sinclair Radionics Ltd., London Rd, St. Ives
Huntingdonshire PE17 4HJ.
Telephone St. Ives (048 06) 4311

sinclair


MW/LW TRANSISTOR RADIO



Complete set of parts for this MW/LW Transistor Radio. Originally sold by world-famous company as a set for more than £17. Coverage 192-550m+1070. 1870m. 9 volt 6 transistor superhet using 3 AF117 in RF and IF stages powered by a two stage AF amplifier using 3 x AC128. Output approx. 500MW. Also works off car-aerial. Full instruction book 121p free with parts. Reel only, ply case, resin covered. Requires PP7 battery, price 221p extra. 3 1/2 in high-quality speaker. Price £6 plus 40p P. & P. Size 8 1/2" x 6" x 3".

STEREO AMPLIFIER Type SHV—2 x 3 watts

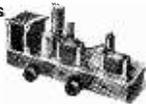Fully built. Separate vol., base and treble controls each channel; 12 x 4 1/2 x 6 in high. EZ80, ECC83. 2 x ECL86 valves. O.P. trans. for 3-ohm speakers. Double wound mains trans. Suitable for crystal, magn. cartridge, tuner, etc. Fitted mono-stereo switch. 200-250V a.c. mains. £7 25, 30p P. & P.



MONO GRAM CHASSIS 3 WATT

3 Wave band long-med-short. Gram., 200-250V A.C. Ferrite aerial. Chassis 13 x 7 x 1 1/2 in. Dial 13 x 4 in. Double wound mains transformer 5 valves ECH81, EF99, EIM81, EL84, EZ80. Price £10 821. (371p p. & p.) Output trans. for 3-ohm speaker



MAINS TRANSFORMERS (240-250V input)

Postage in bracket
6.3V at 21A, 40p (15p)
250V at 50mA and 6.3V at 11A, 50p (20p).
22V at 1A, 6.3V at 2A and 250V at 50mA, 75p (25p).
90V at 20mA and 1.4V at 250mA, 50p (15p).
Deduct 10 per cent from total bill for more than one transformer.

Miniature A.M. transistor tuning gang, 250 + 250pf ± 2 x ohm. fixings, size 1 1/2 x 1 1/2 x 1 in; gearing 3:1 to 3/4 in dia. moulded bush. Plastic dust cover; Plessey. 25p post. pd., less 10% for 6.



GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT. Hants

(2 mins. from Station and Buses). FULL GUARANTEE. Aldershot 22240
CLOSED WEDNESDAY. S.A.E. for enquiries please.

6 Watt QUALITY STEREO

At a competitive price you can afford




This is a genuine high quality low distortion (0.2%) stereo amplifier incorporating two of the latest Plessey integrated circuit amplifiers each with its own separate 3 transistor pre-amp plus 11 transistor main-amp and built in thyristor protector circuit in case of wiring accidents. With a total maximum power of up to 6 watts r.m.s. (8Ω load 3w/channel), this amplifier has more than enough power to rock the average living room. The circuit features Volume, Balance and tone controls, has a separate on/off switch, and requires only a source of 14v a.c. to be fully operational. Input is designed to suit most crystal pick-ups and frequency response is 50-15KHz. Price £6-25

Also Dual Tone Control Model Price £7-48
Mains transformer for either of the above amplifiers 99p.
and Mini Discotheque three colour lamp driver attachment, has three bright 6w lamps, fun for any party! at £8-20

Cheques, P.O.s to
THE AUTOTRON COMPANY, HIXON, STAFFS
SPECIAL TERMS FOR QUANTITY ORDERS (100+)

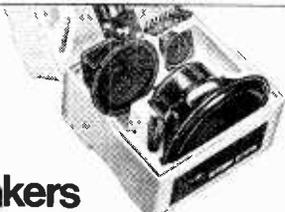Build your own Peerless stereo loudspeakers



It's very easy. And you have to pay for the materials only. The result is a world-famous Peerless hi-fi loudspeaker system of superior quality. For particulars about the various loudspeaker kits, please apply to

Peerless

P.F. & A.R. Helme Ltd.
Summerbridge
Harrogate HG3 4DR
Yorkshire

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

You LEARN—but it's as fascinating as a hobby

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of "OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO". This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.

FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B8, ALDERMASTON COURT, READING RG7 4PF



POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B8 Aldermaston Court, Reading RG7 4PF
Please send book and full information — FREE and without obligation.



NAME..... AGE.....
BLOCK CAPITALS PLEASE
ADDRESS.....

OCCUPATION.....

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
Accredited by the Council for the Accreditation of Correspondence Colleges.

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV	1A	3A	7A	10A	18A	30A
TO-5	TO-66	TO-66	TO-48	TO-48	TO-48	TO-48
\$p	\$p	\$p	\$p	\$p	\$p	\$p
50	0.23	0.25	0.47	0.50	0.53	1.15
100	0.25	0.33	0.53	0.58	0.63	1.40
200	0.35	0.37	0.57	0.61	0.75	1.60
400	0.43	0.47	0.67	0.75	0.93	1.75
600	0.53	0.57	0.77	0.97	1.25	
800	0.63	0.70	0.90	1.20	1.50	4.00

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
\$p	\$p	\$p	\$p	\$p	\$p	\$p	\$p
50	0.40	0.05	0.05	0.07	0.14	0.21	0.47
100	0.04	0.08	0.05	0.13	0.16	0.23	0.75
200	0.05	0.09	0.06	0.14	0.20	0.24	1.00
400	0.06	0.13	0.07	0.20	0.27	0.37	1.25
600	0.07	0.18	0.10	0.23	0.34	0.46	1.35
800	0.10	0.17	0.13	0.25	0.37	0.55	2.00
1000	0.11	0.25	0.15	0.30	0.46	0.63	2.50
1200	—	0.33	—	0.33	0.57	0.75	—

TRIACS

VBOM	2A	6A	10A
TO-1	TO-66	TO-88	
\$p	\$p	\$p	
100	30	50	76
200	50	60	90
400	70	75	1-10

LUCAS SILICON RECTIFIERS

35 amp. 400 p.i.v. stud type. \$1.10p each.

DIACS FOR USE WITH TRIACS BR100 (D32) 37p each

2A POTTED BRIDGE RECTIFIERS 200V 50p

UNIUNION

UT48. Eqv. 2N2646, Eqv. T1843, BEN3000
27p each, 25-99 25p
100 UP 20p.

PNP SILICON PLANAR

BC107/8/6, 10p each.
50-99 8p; 100 un.
8p each, 1,000 off.
7p each. Fully-tested and coded TO-18 case.

FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

AFV39 PNP GERM. SIEMENS VHF TRANSISTORS. RF MIXER & OSC. UP TO 900 MHz. USE AS REPLACEMENT FOR AF139-AF198 & 100% OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE:—1-24 87p each, 25-99 34p each, 100+ 30p each.

SPECIAL OFFER

2N2928 (Y) (O)
10 for 80p, 25 for \$1
20,000 TO CLEAR

CADMIUM CELLS

ORP12 43p
ORP60, ORP61 40p each

PHOTO TRANS.

OCPT1 Type. 43p

SIL. G.P. DIODES 5p

300mV 30. .050
40P(V)(Min.) 100. .150
Sub-Min. 500. .500
Full Tested 1,000. .900
Ideal for Organ Builders.

DI3D1 Silicon Unilateral switch 50p each.

A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

JUMBO COMPONENT PAKS

MIXED ELECTRONIC COMPONENTS Exceptionally good value

Resistors, capacitors, pot., electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price incl. P. & F. \$1.50 only

Plus our satisfaction or money back guarantee.

FULL RANGE OF ZENER DIODES

2-55V. 400mW TO-7 Case) 13p ea. 14W (Top Hat) 18p ea. 10W (SQ-10 Stud) 25p ea. All fully tested 8% tol. and marked. State voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed Pak No. EQVT
T1 8 2G3713 OC71
T2 8 D1374 OC75
T3 8 D1316 OC81D
T4 8 2G381T OC81
T5 8 2G382T OC82
T6 8 2G344B OC44
T7 8 2G345B OC45
T8 8 2G378 OC78
T9 8 2G399A 2N1302
T10 8 2G417 AF117
All 50p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699

TEXAS. Our price 25p each

120 VCB MIXIE DRIVER TRANSISTOR 8m.

BSX21 & C407, 2N1893 FULLY TESTED AND CODED ND 120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqv. ZTX300 5p each. Any Qty.

EX-EQUIPMENT MULLARD

AF117 transistors. Large can 4 leads type. Leads cut short but still usable, real value at 15 for 50p.

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	5p
U1	120 Glass sub-min. general purpose germanium diodes	0.50
U2	60 Mixed germanium transistors AF/RF	0.50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0.50
U4	40 Germanium transistors like OC81, AC128	0.50
U5	60 200mA sub-min. Sil. diodes	0.50
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N708	0.50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0.50
U8	50 Sil. planar diodes 250mA, OA/200/202	0.50
U9	20 Mixed volta 1 watt Zener diodes.	0.50
U11	30 PNP silicon planar transistors TO-5 sim. 2N1132	0.50
U13	30 PNP-NPN all. transistors OC290 & 28104	0.50
U14	150 Mixed silicon and germanium diodes	0.50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0.50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0.50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0.50
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV	0.50
U19	25 Silicon NPN transistors like BC108	0.50
U20	12 1.5 Amp silicon rectifiers Top-Hat up to 1,000 PIV	0.50
U21	39 A.F. germanium alloy transistors 2G300 series & OC71	0.50
U23	30 Mull's like MAT series PNP transistors	0.50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0.50
U25	25 300 Mc/s NPN silicon transistors 2N708, BBY27	0.50
U26	30 Fast switching silicon diodes like IN914 micro-fin	0.50
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600	1.00
U31	20 Sil. Planar NPN trans. low noise amp 8N3707	0.50
U32	25 Zener diodes 400mW D07 case mixed volta, 3-18.	0.50
U33	51 Plastic case 1 amp silicon rectifiers IN4000 series	0.50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	0.50
U35	25 Sil. planar trans. PNP TO-18 2N2906	0.50
U36	25 Sil. planar PNP trans. TO-5 BFY50/51/52	0.50
U37	30 Sil. alloy trans. SO-2 PNP. OC200 28322	0.50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	0.50
U39	30 RF gerin. PNP trans. 2N1303 5 TO-5	0.50
U40	10 Dual trans. 6 lead TO-5 2N2060.	0.50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0.50
U42	10 VHF germ. PNP trans. TO-1 NKT987, AF117	0.50
U43	25 Sil. trans. plastic TO-18 A.F. BC131/114	0.50
U44	20 Sil. trans. plastic TO-5 BC115/116	0.50
U45	7 3A SCR's TO-66 up to 600 Piv.	1.00

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

NEW QUALITY TESTED PAKS

Pak Description	Price 5p
Q1 20 Red spot trans. PNP AF	0.50
Q2 16 White spot R.F. trans. PNP	0.50
Q3 4 OC77 type trans.	0.50
Q4 6 Matched trans. OC44/45/81/81D	0.50
Q5 4 OC75 transistors	0.50
Q6 4 OC72 transistors	0.50
Q7 4 AC128 trans. PNP high gain	0.50
Q8 4 AC126 trans. PNP	0.50
Q9 7 OC81 type trans.	0.50
Q10 7 OC71 type trans.	0.50
Q11 2 AC127/128 comp. pairs PNP/NPN	0.50
Q12 3 AF114 type trans.	0.50
Q13 3 AF117 type trans.	0.50
Q14 3 OC171 H.F. type trans.	0.50
Q15 5 2N2926 all. epoxy trans.	0.50
Q16 2 (ET880 low noise germ. trans.	0.50
Q17 3 NPN 1 8T141 & 2 8T140	0.50
Q18 4 Madic's 2 MAT 100 & 2 MAT 190	0.50
Q19 3 Madic's 2 MAT 101 & 1 MAT 121	0.50
Q20 4 OC45 trans. A.F.	0.50
Q21 3 AC127 NPN germ. trans.	0.50
Q22 20 NKT trans. A.F. R.F. code	0.50
Q23 10 OA202 sil. diodes sub-min.	0.50
Q24 8 OA81 diodes.	0.50
Q25 6 IN914 sil. diodes 75PIV 75mA	0.50
Q26 8 OA85 germ. diodes sub-min. IN69.	0.50
Q27 2 16A 800Piv all. rect. 1845R	0.50
Q28 2 8il. power rect. BYZ13	0.50
Q29 4 8il. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	0.50
Q30 7 8il. switch trans. 2N706 PNP	0.50
Q31 6 8il. switch trans. 2N708 NPN	0.50
Q32 3 PNP all. trans. 2 x 2N1131, 1 x 2N1132	0.50
Q33 3 8il. NPN trans. 2N1711	0.50
Q34 7 8il. NPN trans. 2N2369, 500MHZ	0.50
Q35 3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	0.50
Q36 7 2N3548 TO-18 plastic 300MHZ	0.50
Q37 5 2N3055 NPN sil. trans.	0.50
Q38 7 PNP trans. 4 x 2N3703, 3 x 2N3702	0.50
Q39 7 NPN trans. 4 x 2N3704, 3 x 2N3705	0.50
Q40 7 NPN trans. 4 x 2N3707, 3 x 2N3708	0.50
Q41 3 Planar NPN TO-18 2N3904	0.50
Q42 6 NPN trans. 2N5172	0.50
Q43 7 BC107 NPN trans.	0.50
Q44 7 NPN trans. 4 x BC108, 3 x BC109	0.50
Q45 3 BC113 NPN TO-18 trans.	0.50
Q46 3 BC115 NPN TO-5 trans.	0.50
Q47 6 NPN high gain 3 x BC167, 3 x BC168	0.50
Q48 4 BCV70 NPN trans. TO-18	0.50
Q49 4 NPN trans. 2 x BFY51, 2 x BFY52	0.50
Q50 7 BSY28 NPN switch TO-18	0.50
Q51 7 BSY95A NPN trans. 300MHZ	0.50
Q52 8 BY100 type sil. rect.	1.00
Q53 25 Sil. & germ. trans. mixed all. marked new	1.50

PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components. 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p Plus 10p P. & P. 100 Boards \$3. P. & P. 30p.

NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

F.E.T.'S

2N3819	35p
2N3820	50p
2N3821	35p
2N3823	30p
2N5458	50p
2N5459	50p
BFW 10	40p
MFF105	40p

PHOTO TRANS.

OCPT1 Type. 43p

SILICON PHOTO TRANSISTOR.

TO-18 Lens end NPN 8im. to BP x 25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Priced each 45p 40p 35p

POWER TRANSISTOR BONANZA!

GENERAL PURPOSE GERM. PNP
Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE.—OC25-28-29-30-35-36. NKT 401-403-404-405-406-430-451-452-453. T13027-3028, 2N250A, 2N458A-457A-458A, 2N511 A & B. 2G220-222. ETC. VCEO 80V VCEO 60V IC 10A PT. 30 WATTS Hie 30-170.
PRICE 1-24 25-99 100 up
43p each 40p each 36p each

AD161 PNP
AD162 PNP
M/P COMP GERM TRANS.
OUR LOWEST PRICE OF 63p PER PAIR

2N3055
115 WATT SIL POWER NPN 83p EACH

SILICON 50 WATTS MATCHED NPN/PNP BIP 19 NPN TO-3
Priced as follows:
BIP 20 PNP. Brand new.
VCEO 100V VCEO 50p IC 10A. HFE type 100/ft 3mHz.
OUR PRICE PER PAIR 1-24 25-99 100
prs. prs. prs.
60p 55p 50p

SILICON HIGH VOLTAGE 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded E 2400 VCEO 250V VCEO 100V IC 6A/30 Watts. HFE type 20/IT 5MHZ.
OUR PRICE EACH: 1-24 25-99 100 up
50p 45p 40p

EX-STOCK TYPE EACH AS PRICED
OC20 50p OC28 40p AD149 43p BD131 70p BD139 75p
OC22 30p OC29 40p AL102 85p BD132 80p BD140 85p
OC23 83p OC35 33p AL103 85p BD133 70p BD155 75p
OC24 45p OC36 40p BD121 80p BD138 80p BU105 43p
OC25 25p AD140 40p BD123 75p RD137 70p 2N3005 44p
OC26 25p AD142 40p BD124 70p BD138 80p

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, BSY27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP 8im. to 2N2906, BCY70. When ordering please state preference NPN or PNP.
PRICE 20 For 0.50 100 For 1.75 500 For 7.50 60 For 1.00 1000 For 13.00

OUR STOCKS of individual devices are now too numerous to mention in this advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available EX-Stock at very competitive prices.

RTL MICROLOGIC CIRCUITS

Epoxy TO-5 case 1-24 25-99 100 up
uL900 Buffer 35p 35p 27p
uL914 Dual 21/p 85p 85p 57p
uL923 J-K flip-flop 50p 47p 45p
Date and Circuits Booklet for IC's Price 7p.

Dual-In-Line Low Profile Sockets

14 and 16 Lead Sockets for use with Dual-In-Line Integrated Circuits

Price each
Order No. 1-24 25-99 100 up
TSO 14 pin type 30p 27p 25p
TSO 16 pin type 35p 32p 30p

-the lowest prices!

74 series T.T.L. I.C.'s DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any LC's. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed.

BI-PAK Order No.	Similar Types to:—Description	Price and qty. prices		
		1-24	25-99	100 up
BP00 = 7400	Quad 2-input NAND gate	0.16	0.14	0.12
BP01 = 7401	Quad 2-input pos. NAND gate (with open collector output)	0.15	0.14	0.12
BP02 = 7402	Quad 2-input pos. NOR gates	0.15	0.14	0.12
BP03 = 7403	Quad 2-input pos. NAND gates (with open collector output)	0.15	0.14	0.12
BP04 = 7404	Hex Inverters	0.15	0.14	0.12
BP05 = 7405	Hex Inverter (with open-collector output)	0.15	0.14	0.12
BP10 = 7410	Triple 3-input pos. NAND gates	0.15	0.14	0.12
BP13 = 7413	Dual 4-input Schmitt trigger	0.29	0.26	0.24
BP20 = 7420	Dual 4-input pos. NAND gates	0.15	0.14	0.12
BP30 = 7430	8-input pos. NAND gates	0.15	0.14	0.12
BP40 = 7440	Dual 4-input pos. NAND buffers	0.15	0.14	0.12
BP41 = 7441	BCD to decimal trix driver	0.67	0.64	0.58
BP42 = 7442	BCD to decimal decoder (4-10 lines, BCD to 10)	0.67	0.64	0.58
BP46 = 7446	BCD-to-seven-segment decoder/driver (15V outputs)	2.00	1.75	1.50
BP47 = 7447	BCD-to-seven-segment decoder/drivers (15V outputs)	0.97	0.94	0.88
BP49 = 7449	BCD-to-seven-segment decoder driver	0.97	0.94	0.88
BP50 = 7450	Expandable dual 2-input and-or-invert	0.15	0.14	0.12
BP51 = 7451	Dual 2-wide 2-input and-or-invert gates	0.15	0.14	0.12
BP63 = 7453	Quad 2-input expandable and-or-invert	0.15	0.14	0.12
BP64 = 7454	4-wide 2-input and-or-invert gates	0.15	0.14	0.12
BP60 = 7460	Dual 4-input expander	0.15	0.14	0.12
BP79 = 7479	Single-base J-K flip-flop	0.29	0.26	0.24
BP72 = 7472	Master slave J-K flip-flop	0.29	0.26	0.24
BP73 = 7473	Dual Master slave J-K flip-flop	0.37	0.35	0.32
BP74 = 7474	Dual D type flip-flop	0.37	0.35	0.32
BP75 = 7475	Quad latch	0.47	0.45	0.42
BP76 = 7476	Dual J-K with pre-set and clear	0.43	0.40	0.38
BP90 = 7490	Gateful full adders	0.67	0.64	0.58
BP81 = 7481	16-bit read/write memory	0.97	0.94	0.88
BP82 = 7482	2-bit binary full adders	0.97	0.94	0.88
BP83 = 7483	Quad full adder	1.10	1.05	0.95
BP86 = 7486	Quad 2-input exclusive NOR gates	0.32	0.30	0.28
BP90 = 7490	BCD decade counter	0.87	0.84	0.78
BP91 = 7491	8-bit shift registers	0.87	0.84	0.78
BP92 = 7492	Divide-by-two counters	0.67	0.64	0.58
BP93 = 7493	4-bit binary counters	0.67	0.64	0.58
BP94 = 7494	Dual entry 4-bit shift register	0.77	0.74	0.68
BP95 = 7495	4-bit up-down shift register	0.77	0.74	0.68
BP96 = 9496	5-bit parallel in parallel out shift-register	0.77	0.77	0.68
BP100 = 74100	8-bit bistable latches	1.75	1.65	1.55
BP104 = 74104	Single J-K flip-flop equivalent 9000 series	0.97	0.94	0.88
BP105 = 74105	Single J-K flip flop equivalent 9001 series	0.97	0.94	0.88
BP107 = 74107	Dual Master slave flip-flops	0.40	0.38	0.36
BP110 = 74110	Gate master-slave flip-flop	0.55	0.53	0.50
BP111 = 74111	Dual data lock-out flip-flop	1.25	1.15	1.00
BP118 = 74118	Hex set-reset latches	1.00	0.95	0.90
BP119 = 74119	Hex set-reset latches. 24-pin	1.35	1.25	1.10
BP121 = 74121	Monostable multivibrators	0.87	0.84	0.88
BP141 = 74141	BCD-to-decimal decoder/driver	0.87	0.84	0.88
BP145 = 74145	BCD-to-decimal decoder/driver O/C	1.50	1.40	1.30
BP150 = 74150	16-bit data selector	1.80	1.70	1.60
BP151 = 74151	8-bit data selectors (with strobe)	1.00	0.95	0.90
BP152 = 74152	Dual 4-line-to-1-line data	1.20	1.10	0.95
BP154 = 74154	4- to 16-line decoder	1.80	1.70	1.60
BP155 = 74155	Dual 2- to 4 line decoder	1.40	1.30	1.20
BP156 = 74156	Dual 2- to 4-line decoder O/C	1.40	1.30	1.20
BP180 = 74180	Sync. decade counter	1.80	1.70	1.60
BP161 = 74161	Sync. 4-bit binary counter	1.80	1.70	1.60
BP190 = 74190	Sync. up-down BCD counter	3.50	3.25	3.00
BP191 = 74191	Sync. binary up-down counter (single clock line)	3.50	3.25	3.00
BP192 = 74192	Sync. up-down decade counter	2.10	1.95	1.75
BP193 = 74193	Sync. binary up-down counter (two clock lines)	2.10	1.95	1.55
BP196 = 74196	Pre-settable 80MHz decade counter	1.80	1.70	1.60
BP197 = 74197	Pre-settable 80MHz binary counter	1.80	1.70	1.60
BP198 = 74198	8-bit parallel L-R shift register	5.50	5.00	4.00
BP199 = 74199	8-bit parallel access shift register	5.50	5.00	4.00


Devices may be mixed to qualify for quantity price. Larger quantities—prices on application (TTL 74 Series only).
Data is available for the above series of I.C.'s in booklet form. Price 18p.
Owing to the ever increasing range of TTL 74 Series; please check with us for supplies of any devices not listed above, as it is probably now in stock.

BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	1-24	25-99	100 up
BP 201C—8L201C	TO-9	8	G.P. Amp	83p	53p	45p
BP 701C—8L701C	TO-5	8	OP Amp	88p	50p	45p
BP 702C—8L702C	TO-5	8	OP Amp Direct OP	83p	50p	45p
BP 702—72702	D.I.L.	14	G.P. OP Amp Wide Band	53p	45p	40p
BP 709—72709	D.I.L.	14	High OP Amp	53p	45p	40p
BP 709P— μ A709C	TO-5	8	High Gain OP Amp	53p	45p	40p
BP 710—72710	D.I.L.	14	Differential comparator	53p	45p	40p
BP 711— μ A711	TO-5	10	Dual comparator	53p	50p	45p
BP 741—72741	D.I.L.	14	High Gain OP Amp (Protected)	75p	60p	50p
μ A 703C— μ A703C	TO-5	6	R.F.—I.F. Amp	47p	35p	27p
TAA 263—	TO-72	4	A.F. Amp	70p	60p	55p
TAA 293—	TO-74	10	G.P. Amp	90p	75p	70p
TAA 350	TO5	8	Wide band limiting amplifier	170p	158p	150p

ANOTHER BI-PAK FIRST!

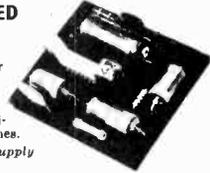THE NEW S.G.S. EA 1000 AUDIO AMPLIFIER MODULE *GUARANTEED NOT LESS THAN 3 WATTS RMS



Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA/821 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines.

OTHER USES: portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt.
- Voltage Gain 40dB but can be varied up to 73dB for some applications.
- Signal to Noise Ratio 86dB.
- Frequency response better than 50 Hz to 25 KHz for -3dB.
- Overall Size 2" x 3" x 1".
- Typical Total Harmonic Distortion at 1 watt less than 1%.
- Supply voltage (V_s) = 24V 15ohm load. Module Tested and Guaranteed.

Quantity Price each 1-9 10-25 26-99 100 up
\$2.63 \$2.28
Larger quantities quoted on request.

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

NOTE THESE PRICES!

Type No.	Function	Price		
		1-24	25-99	100 up
BP930	Expandable dual 4-input NAND	23p	20p	15p
BP932	Expandable dual 4-input NAND buffer	25p	23p	20p
BP933	Dual 4-input expander	25p	23p	20p
BP935	Expandable Hex inverter	25p	23p	20p
BP936	Hex Inverter	25p	23p	20p
BP944	Dual 4-input NAND expandable buffer without pull-up	25p	23p	20p
BP945	Master-slave JK or RS	35p	32p	29p
BP946	Quad, 2 input NAND	23p	20p	15p
BP948	Master-slave JK or RS	35p	32p	29p
BP951	Monostable	90p	85p	80p
BP962	Triple 3 input NAND	23p	20p	15p
BP9098	Dual Master-slave JK with separate clock	80p	75p	70p
BP9094	Dual Master-slave JK with separate clock	80p	75p	70p
BP9097	Dual Master-slave JK with Common Clock	80p	75p	70p
BP9099	Dual Master-slave JK Common Clock	80p	75p	70p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

DTL & TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

Pak No.	Pak No.	Pak No.	Pak No.
UIC930 = 12 x μ A 930	50p	UIC946 = 8 x μ A 946	50p
UIC932 = 12 x μ A 932	50p	UIC961 = 8 x μ A 961	50p
UIC933 = 12 x μ A 933	50p	UIC961 = 8 x μ A 961	50p
UIC935 = 12 x μ A 935	50p	UIC9093 = 5 x μ A 9093	50p
UIC936 = 12 x μ A 936	50p	UIC9094 = 5 x μ A 9094	50p
UIC944 = 12 x μ A 944	50p	UIC9097 = 5 x μ A 9097	50p
UIC945 = 8 x μ A 945	50p	UIC9099 = 5 x μ A 9099	50p
UIC946 = 12 x μ A 946	50p	UIC x 925 Assorted 930 Series	£15-50

Packs cannot be split but 25 Assorted Pieces (our mix) is available as Pack UICX9 Data Booklet available for the BP930 Series, PRICE 13p

UIC00 = 12 x 7400N	50p	UIC46 = 5 x 7446N	50p	UIC81 = 5 x 7481N	50p
UIC01 = 12 x 7401N	50p	UIC47 = 5 x 7447N	50p	UIC82 = 5 x 7482N	50p
UIC02 = 12 x 7402N	50p	UIC48 = 5 x 7448N	50p	UIC83 = 5 x 7483N	50p
UIC03 = 12 x 7303N	50p	UIC50 = 12 x 7450N	50p	UIC84 = 5 x 7484N	50p
UIC04 = 12 x 7404N	50p	UIC51 = 12 x 7451N	50p	UIC85 = 5 x 7485N	50p
UIC05 = 12 x 7405N	50p	UIC53 = 12 x 7453N	50p	UIC86 = 5 x 7486N	50p
UIC10 = 12 x 7410N	50p	UIC54 = 12 x 7454N	50p	UIC87 = 5 x 7487N	50p
UIC13 = 8 x 7413N	50p	UIC70 = 12 x 7460N	50p	UIC89 = 5 x 7489N	50p
UIC20 = 12 x 7420N	50p	UIC72 = 8 x 7472N	50p	UIC94 = 5 x 7494N	50p
UIC40 = 12 x 7440N	50p	UIC73 = 8 x 7473N	50p	UIC95 = 5 x 7495N	50p
UIC41 = 5 x 7441N	50p	UIC74 = 8 x 7474N	50p	UIC96 = 5 x 7496N	50p
UIC42 = 5 x 7442N	50p	UIC75 = 8 x 7475N	50p	UIC121 = 5 x 74121N	50p
UIC43 = 5 x 7443N	50p	UIC76 = 8 x 7476N	50p	UICX1 = 26 x Ass'd	74's \$1.50
UIC44 = 6 x 7444N	50p	UIC77 = 8 x 7477N	50p		
UIC45 = 6 x 7445N	50p	UIC80 = 5 x 7480N	50p		

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE - HERTS

Postage and packing add 7p. Overseas add extra for airmail.
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

SUB MIN CROC CLIPS. Red or Black, insulated 4p. Min. quantity, 6 pp. 3p.

GARRARD MAG TAPE DECKS: 1 1/2ips, 50v solenoid operated brakes, etc. Mains voltage motors £7-50 each, pp £1-23.

4 1/2" PLANNAIR FANS. Complete, capacitor, ex-equip. 2,800 r.p.m. £3-50, pp 40p.

ELECTRIC MOTORS, HOOVER OR CROMPTON PARKINSON.

1 h.p. 1,440 r.p.m. £3-75 pp £1-00
 1 h.p. 1,425 r.p.m. £6-75 pp £1-25
 1 h.p. 1,440 r.p.m. £2-25 pp 75p

AUDIO CONNECTORS

3 pin Din Plug .. 13p each
 5 pin Din Plug A type, B type .. 15p ..
 2 pin Din Speaker Plug .. 10p ..
 3 pin Din Line Socket .. 13p ..
 3.5mm Jack Plug Screened .. 10p ..
 Standard Jack Plug .. 10p ..
 Screened Standard Jack Plugs .. 15p ..
 Stereo Jack Plug .. 13p ..
 Screened Stereo Jack Plug .. 15p ..
 pp on above items 3p.

B.S.R. MINI AUTO-CHANGER.
 Mono Cartridge £4-75 pp 30p.

PHONO PLUGS: Red or Black 3p each.

MAINS NEONS.
 Red or Green. Size: 1" x 1" 15p, pp 3p.

LEVER ACTION P.O.1000 TYPE SWITCHES.
 Lock 4-pole changeover 15p, pp 3p. (ex-equip.)

SCREENED PHONO LEADS 46" long, 15p, pp 3p.

PIEZO DYNAMIC MICROPHONE
 50k Ω £1-00 pp 8p.

MULLARD SCREW TERMINAL CAP
 4.500uf 64v 50p pp 13p.

BELLING LEE 1.5 amp in-line rubber covered interference suppressor 25p pp 8p.

SOLENOIDS 12 VOLT PULL ACTION
 2" x 1" x 1/2" 40p pp 8p.

STC SEALED RELAYS DOUBLE POLE CHANGEOVER
 48v 2500 Ex-equip. 15p pp 5p.

SIEMENS MINIATURE RELAY. Double pole changeover (dust cover)/base 48v 2500 50p pp 5p new.

STC MINIATURE RELAY 280 Ω Perspex Cover 6-15v new, 35p pp 5p.

GARDNER'S POTTED TRANSFORMER 0-250v Input: 18v 500mA/50v 150 mA, 6v 250 mA Output. Size 3" x 2 1/2" x 2 1/2". £1.00, pp 20p. Ex equip tested.

TELESCOPIC AERIALS
 Chromed 7" closed 28" extended 6 section ball jointed base 23p pp 8p new.

MULLARD 4 DM 180 INDICATORS in plastic holder/cover ex-equip. size approx. 1 1/2" x 1 1/2" x 1 1/2" 36p pp 8p.

PRINTED CIRCUIT BOARD/19 ACY 19" x 10" OA300
 Diodes: 1 recd relay: 10 AZ 229 zenner ass. capacitor/ resistors. Power supply 22v 250 mA/A DC. Output 240v. AC £1 pp 20p ex-equip.

TOGGLE SWITCHES. Single pole Double Throw ex-equip. new condition. 50p doz. pp 13p.

FIBRE GLASS TAPE. 100 yd. roll: 3" 3 1/2" wide £1 per roll pp 20p.

PAINTON PLUG SOCKETS Type 150 series working voltage 350v AC/DC current max. 3 amp AC/DC 7 pin plug & socket 50p pp 10p. 15 pin plug & socket £1 pp 10p.

CASH WITH ORDER PLEASE

FIELD ELECTRIC LIMITED

3 Shenley Road,
 Borehamwood, Herts.
 Ajacent Elstree Mainline Station
 Tel: 01-953 6009.

The BATTERIES That Won't Let You Down! RECHARGEABLE

Cells in U2, U11 and Penlite U7 sizes
Kestral Battery Charging Unit



Uses:
 Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you must have utterly dependable battery power—then these new Alkaline-Manganese rechargeable cells will provide it. The cells can be recharged many times, a simple job with the Kestral Charging Unit which has been specially designed for these new type batteries.


PRICES
 Batteries U2 equiv. £1-25
 Penlite U7 equiv. 50p
 U11 equiv. £1-03
 Charging unit £3-99 with one battery holder



Send to:
**275 WEST END LANE
 LONDON, N.W.6
 01-764 9611**

U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME

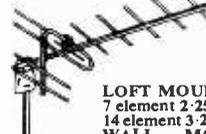

RECEPTION
 All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS
 7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75.

WALL MOUNTING c/w WALL ARM & BRACKET
 7 element 3-25. 11 element 3-75. 14 element 4-25. 18 element 4-75. CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT. 7 element 4-00. 11 element 4-50. 14 element 4-75. 18 element 5-25. MAST MOUNTING arrays only. 7 element 2-25. 11 element 2-75. 14 element 3-25. 18 element 3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9np yd. KING TELEBOOSTERS from 3-75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7-50. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np C.W.O. Min. C.O.D. charge 25np.

BBC—ITV—FM AERIALS
 BBC (band 1) Wall S/D 2-00. LOFT inverted 'T' 1-25. EXTERNAL 'H' array only 3-00. ITV (band 3) 5 element loft array 2-50. 7 element 3-00. COMBINED BBC—ITV, loft 1+5 2-75. 1+7 3-50. WALL & CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from 3-75. COMBINED U.H.F.—V.H.F. aerials 1+5+9 4-00. 1+5+14 4-50. 1+7+14 5-00. F.M. RADIO loft S/D 1-00 3 element 3-25. 4 element 3-50. Standard coaxial plugs 9np. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists. CALLERS WELCOMED OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS
 40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY
 Telephone 01-648 4884

NEW 5in. SPEAKERS 15 ohms 75p, p. & p. 10p.

BARGAIN PARCELS 14lb at £1-45 plus 32p p.p.: 28lb at £2-75 plus 52p p.p.: 56lb at £4-50 plus £1-25 p.p. Contain pots, Res, Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH, Medium Persistence, green. Ideal scope tube. List price £5. Our price £1-40 carriage paid.

500 μ AMP METERS. Approx. 1 1/2" on panel with plug and switch ex new equip. 75p p. & p. paid.

NEW HEAVY COAX CABLE dia. 1/2" 70 ohms approx. 50ft. lengths £1-40, p. & p. 30p. 100 ft. lengths £2-70, p. & p. 50p.

VHF AERIAL TUNING UNITS consisting of the following: 1-14" 500 micro/ampmeter. 1 small 2-gang 75 PF capacitor. 1 various large wattage resistors for dummy load. Pair gears B.N.C. type sockets. Will tune 10 mtrs with 25/30 watts R.F. input. Size only 5 1/2" x 4 1/2" x 5" Sealed. Price £1-37 1/2 p.p. 25p

CRYSTALS AS NEW: He 6u, 5.345; 5.030; 5.005; 4.945; 4.875; 4.840; 4.795; 4.580; 4.660; 4.520; 4.510; 2.300; 2.295 Kc/s. 50p each plus 8p. p.p.

SCOOP PURCHASE OF BRAND NEW CARBON RESISTORS. 10% tolerance 1/2 & 1/4 watt. Preferred values in packets of 10. Our price 50p per 100, 95p per 200, £1-35 per 300, 500 at £2-12 1/2. Our selection. p. 8p per 100 and 21p per extra 100.

TRIMMER BARGAINS. These are 10PF sub-min. air-spaced trimmers on board with min. wire ended Xtal. Brand new. No details: Contents 12 trimmers, some ceramic caps. Xtal frequency 3RD overtone 249 mc/s-250 Mc/s, 255 Mc/s. No choice.

Trimmers without Xtal—80p per doz. plus 17 1/2p p.p. Trimmers with Xtal—75p per doz. plus 17 1/2p p.p. Also 20 PF min. brand new air spaced. 50p per doz. plus 17 1/2p p.p.

ANY HEIGHT AERIAL TUBULAR SECTIONS 1" dia x 3 ft. long. Brass screw in ends, copper coated and painted. Good condition. 20p, p. & p. 5p each. Minimum order 10.

BRAND NEW HARTLEY OSCILLOSCOPES CT316 in original packing. Band width up to 5 Mc/s. Mains supply. Price £40, p. & p. £1-50p.

AERIALS NEW CONDITION. Whip type 4ft. 25p, 11ft. 75p, 14ft. 87p. Used condition 4ft 20p, 14ft. 75p. All collapsible type. P. & p. 4ft. 10p, rest at 17 1/2p p.p. Bands on adjustable clamp for above. 24p p. & p. 25p. New matching unit coax connection for above 30p p. 5p.

Huge release of valves for the 62 set TX/RX. In original rubber packing consisting of QV04/7 x 61M, ARP12 etc. 10 valves in all at the bargain price as seen 87p plus 17 1/2p p.p.

R209. Set of valves 62p. p.p. 25p.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 75ft. 40p, 90ft. 47p, 100ft. 55p, 180ft. 85p, 250ft. £1-30p, p. & p. 20p.

MURHEAD DECADE A.F. SIGNAL GENERATOR.
 This precision instrument can be used:
 1. To Measure Gain up to 50 db.
 2. To Measure Loss up to 45 db.
 3. To compare Power levels (A.F.).
 4. As an Audio Frequency Generator covering 100 Hz to 41 kHz. With a dial setting accuracy of ± 0.5 Hz. Output: -1 M/W into 600 Ω L. Complete with mains power unit. Tested. Good Condition. £12, p. & p. 75p.

ENCLOSED AERIAL RELAY COIL. Res. 700 ohms approx. 25 watts RF BNC outlet, working voltage 12v. 75p, p. & p. 10p. £1 with BNC plugs.

Also 1/2 75 ohm Coax in 50ft coils with BNC plugs good condition. price £1 + 30p. p.p.

NEW BOXED AMP METERS 1 1/2" 20-0-20 dc. 65p, p. & p. 5p.

AS NEW UNUSED REJECTOR UNITS for rejecting unwanted signals. Four ranges 1-2-10 Mc/s. £1-50 p. & p. 20p each.

AS NEW UNUSED AERIAL VARIOMETER. Cylinder design 10" x 4 1/2", suitable for tuning most aerials for signal strength. £1-50 p. & p. 25p.

NEW HEADPHONES AND MIKE RUBBER muff type low impedance 87 1/2p p. & p. 17 1/2p. Also DLR number 5. low impedance used condition 62p p. & p. 17 1/2p.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER,
 Radio Dept.,
 HIGH STREET, CHESLYN HAY,
 Nr. Walsall, Staffs.

4-STATION INTERCOM



£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. £0.40.

MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £12.40 P. & P. £0.55

INTERCOM/BABY ALARM



OUR PRICE ONLY **£3.35**

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 14p. P. & P. £0.25.

Transistor TELEPHONE AMPLIFIER



£2.99

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 14p. extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.8)
189 KENSINGTON HIGH STREET, LONDON, W.8.

PRACTICAL WIRELESS ELECTRONIC IGNITION SYSTEM



This Capacitor-discharge Electronic ignition system was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the Standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the De-luxe version containing a ready-drilled roller-trimmed printed circuit board and fully machined die-cast case with electrical connection block. Each kit is supplied with a custom wound transformer, first-grade components and full construction details. Suitable for 12V. systems only, pos. or neg. earth. All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, refundable on purchase of kit.

Price : Standard kit ... £7.25 post free
De-luxe ... £8.75 post free
Trade enquiries invited. ... Mail order only.

DABAR ELECTRONIC PRODUCTS

98a, LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34365



LOUDSPEAKER BARGAINS

Fane Pop 100 watt 18" 8/15 ohm	£19.50
Fane Pop 60 watt 15" 8/15 ohm	£11.15
Fane Pop 50 watt 12" 8/15 ohm	£9.25
Top 20 12" 25 watt 8 or 15 ohm	£6.75
Top 10 10" 10 watt 8 or 15 ohm	£3.25
Baker Group 25 12" 25 watt 3, 8 or 15 ohm	£6.55
EMI 13 x 8, 3, 8 or 15 ohm	£2.25
EMI 13 x 8 with tweeter 3, 8 or 15 ohm	£2.95
EMI 13 x 8 twin tweeter 3, 8 or 15 ohm	£3.90
Handsome teak finish cabinet 17" x 10" x 6" for above 13 x 8 units (p. & p. 35p)	£5.00
Celestion PS8 Round 15 ohm	£2.05
Celestion PS8 for Unilex	£2.55
Richard Allan 8" Round 8 ohm	£2.75
Fane 8" dual cone 8 ohm	£2.85
Handsome teak finish cabinet 17" x 10" x 6" to suit all above 8" units (p. & p. 35p)	£5.00
Elac or Goodmans 8" x 5" 3, 8 or 15 ohm	£2.15
Handsome teak finish cabinet 12" x 8" x 6" for above 8 x 5 units (p. & p. 25p)	£3.45
Goodmans 6 1/2" twin cone 8 ohm	£2.45
E.M.I. 10 x 6 1/2, 8 or 15 ohm	£2.15
Fane 7 x 4, 3 or 8 ohm	£1.50
Richard Allan 12" round 3 or 15 ohm	£2.50
EMI 2 1/2" tweeter 3 ohm	65
Plessey 3" 80 ohm	65
Eagle CT10 tweeter	£1.50

All units guaranteed new and perfect. Prompt despatch p. & p. 25p per speaker.

Send 9p stamps for our fabulous discount catalogue of radios, tape recorders, HiFi, etc. (illustrated).

WILMSLOW AUDIO, M. O. Dept.

10 Swan St., Wilmslow, Cheshire

MAINS UNITS for all types of TRANSISTOR EQUIPMENT



RUN YOUR TAPE RECORDER OFF A.C. MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.)

£2.50 P. & P. 15p

12 VOLT CAR BATTERY UNIT

Enables you to run your cassette recorder off 12V. car battery. (State 6v or 7 1/2v output, model and plug required.)

£2.00 P. & P. 15p

PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v., 7 1/2v. and 9v. DC. attractive case with indicator light, mains lead output socket, plug and lead. Size 4 1/2 x 3 1/2 x 2 1/2 in.

£3.00 P. & P. 15p.



Extra lead with plug to fit your cassette recorder 50p. (State model and plug required.)

MAINS UNIT FOR ALL TRANSISTOR RADIOS, ETC., USING PPT TYPE BATTERY. ALSO AVAILABLE FOR 6V.)

£1.15 P. & P. 10p.

MAIN UNITS

For single outputs, 6v, 9v, 12v, 18v, £2.00. For two separate outputs, 4 1/2v + 4 1/2v, 6v + 6v., 9v + 9v, £2.50. P. & P. 15p. per unit. (Please state outputs reqd.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.), 31 Ollver Road, London, E.17

CLEAR TONE HI-FI LTD

166, BLACKBURN ROAD, BOLTON, LANCs.
Tel. 22636

4, IRLAM SHOPPING CENTRE, IRLAM, MANCHESTER

*ITEMS STARRED ON COMPARATOR DEMONSTRATION BOLTON **BOTH

	Rec. Retail	Our Price
STEREO AMPLIFIERS (Cased)		
*Leak Delta 30	£65.00	£49.00
*Leak Delta 70	£79.50	£61.00
**Alba UA700	£34.50	£24.00
**Metrosound ST20E	£39.50	£27.50
**Rotel 310	£45.00	£32.00
*Rogers Ravensbrook 2	£52.50	£40.00
**Armstrong 521	£56.00	£45.00
*Leak 30+	£62.50	£44.00
*Rogers Ravensbourne	£64.00	£49.00
*Leak 70	£75.00	£54.00
CARRIAGE £1.00		

	Rec. Retail	Our Price
SPEAKERS		
**Wharfedale Denton 2/pr.	£39.90	£32.00
**Wharfedale Linton 2/pr.	£49.90	£40.00
*New Leak 150/pr.	£49.90	£40.00
*R. Allen Flamenco/pr.	£59.26	£46.00
*New Leak 250/pr.	£65.00	£48.00
*R. Allen Pavane/pr.	£70.50	£49.00
*Wharfedale Melton 2/pr.	£70.00	£50.00
**Celestion Ditton 15/pr.	£76.94	£60.00
*Wharfedale Dovedale 3/pr.	£90.00	£65.00
CARRIAGE £1.00		

	Rec. Retail	Our Price
CARRIAGES		
*Sonotone 9TA/HC Dia	£3.75	£2.00
*Goldring G850 Dia.	£6.27	£4.00
*Goldring G800 Dia.	£12.55	£6.50
*Shure M44.7 Dia.	£9.84	£7.50
*Goldring G800E Dia.	£18.16	£11.00
*Shure M55E Dia.	£12.52	£9.50
*Shure M75E/2 Dia.	£20.57	£14.00
CARRIAGE FREE		

	Rec. Retail	Our Price
TURNABLES		
**Garrard SP25 Mk. 3	£15.85	£10.50
**McDonald MP60	£15.20	£10.50
*Goldring GL69/2	£27.60	£19.50
**Goldring GL69/2/P	£36.21	£26.00

	Rec. Retail	Our Price
*Connoisseur BD2/SAU2	£31.00	£25.00
*Connoisseur BD2/SAU2/P/C	£38.00	£33.00
*Goldring GL75	£40.15	£30.00
**Goldring GL75P	£48.76	£36.00
*Garrard 401/3009/2 arm	£71.26	£53.00
PI Spacer and Mtg. Board	£6.00	£4.00
Plinths and Covers Stocked CARRIAGE £1.00		

SPECIAL OFFERS

Garrard SP25 Mk 3 fitted in Teak Veneer Plinth with Cover wired Din or Phono to order ... **£13.00**
with 9TA/HC Cartridge ... **£15.00**
with G850 Cartridge ... **£17.00**
with G800 Cartridge ... **£19.50**
SME 3009 Mk 2 Arm & Shell ... **£33.80**
Connoisseur BDI Kits ... **£71.00**
CARRIAGE AND INSURANCE ON ABOVE ITEMS £1.00

ALL ITEMS GUARANTEED. AFTER SALES SERVICE. PRICE LIST ON REQUEST.

STEREO TUNER AMPS

*Leak Stereofectic/30	£131.03	£94.00
*Leak Stereofectic/70	£143.53	£103.00
CARRIAGE £1.00		

BOLTON

OPEN 9.00-5.30 Monday-Tuesday
9.00-8.00 Thursday-Friday
9.00-4.00 Saturday
CLOSED ALL DAY WEDNESDAY
CLOSED 1.30-2.30 Except Saturday

COMET

HI-FI DISCOUNT WAREHOUSES



	Rec. Price	Retail Price	Comet Price
STEREO AMPLIFIERS			
ALBA UA 700	34.50	24.95	
ALPHA 212 By Highgate	36.75	26.95	
AMSTRAD Stereo 8000 Mk 2	27.95	17.95	
AMSTRAD J.C. 2000	42.95	27.95	
ARMSTRONG 521	59.00	44.95	
DULCI 207	26.00	16.95	
DULCI 207M	32.00	19.95	
FERROGRAPH F307 Mk. II (cased)	64.00	46.95	
FERROGRAPH F307 MII (Metalcase)	60.00	43.95	
GOODMANS Maxamp	54.00	37.95	
LEAK Delta 30 (cased)	85.00	51.95	
LEAK Delta 70 (cased)	79.50	63.95	
METRO SOUND ST20E	39.50	27.95	
METRO SOUND ST60	70.00	49.95	
PHILIPS RH 591	79.00	54.95	
PHILIPS RH 590	52.00	36.95	
PHILIPS RH 580	29.00	19.95	
PIONEER SA500	53.62	38.95	
PIONEER SA600	83.75	59.95	
PIONEER SA700	97.97	66.95	
PIONEER SA800	109.21	75.95	
PIONEER SA900	133.83	93.95	
PIONEER SA1000	137.56	95.95	
PIONEER Reverberation 202	46.35	33.95	
RANK Rotel 310	47.50	35.95	
RANK Rotel 610	74.50	53.95	
RANK ROTEL 210	34.90	24.95	
ROGERS Ravensbourne	59.50	42.95	
ROGERS Ravensbourne (cased)	64.00	47.95	
ROGERS Ravensbrook Mk. II	47.50	36.95	
ROGERS Ravensbrook (cased) Mk. II	52.50	39.95	
SINCLAIR 2000	35.00	23.75	
SINCLAIR Project 60/2 x Z30/PZ5	23.90	15.95	
SINCLAIR PROJECT 60/2 x Z50/			
PZ8/trans	34.86	23.25	
SINCLAIR PROJECT 605	29.95	21.95	
SINCLAIR AFU	5.95	4.45	
SINCLAIR Neoteric	61.95	43.95	
SINCLAIR 3000	45.00	31.50	
TELETON SAQ 206	32.50	18.25	
VOLTEX 100w. Stereo Discotheque,	185.00	139.00	
8 electronically mixed inputs			
WHARFEDALE Linton Amplifier	60.00	47.95	
All take both ceramic and magnetic cartridges.			
TUNERS			
*ARMSTRONG 523 AM/FM	54.22	42.95	
*ARMSTRONG 524 FM	42.17	33.95	
ARMSTRONG M8 Decoder	9.50	7.70	
*DULCI FMT. 7 FM	25.10	17.95	
DULCI FMT. 7S Stereo	33.79	27.25	
GOODMANS Stereomax	80.07	47.95	
LEAK Delta FM	75.00	58.95	
LEAK Delta AM/FM	89.50	69.50	
PHILIPS RH 690	45.30	36.50	
PHILIPS RH 691	85.80	69.95	
PIONEER TX500 AM/FM	66.09	57.95	
PIONEER TX900 AM/FM	147.15	118.00	
RANK ROTEL 320	54.94	43.95	
ROGERS Ravensbourne chassis	59.63	46.95	
ROGERS Ravensbourne in teak case	64.45	48.95	
ROGERS Ravensbrook chassis	43.37	34.95	
ROGERS Ravensbrook (cased)	49.39	38.95	
SINCLAIR 2000	45.90	33.95	
SINCLAIR Project 60 Tuner (stereo)	25.00	19.95	
TELETON GT 101	43.93	30.95	
All above Tuners are complete with MPX Stereo Decoder except where starred.			
TUNER/AMPLIFIERS			
AKAI AA 8500	221.85	175.00	
AKAI 6600	137.34	108.00	
AKAI 6300	128.85	99.95	
AKAI 6200	91.56	79.95	
ARENA 2600	111.30	69.95	
ARENA 2700	88.63	73.95	
ARENA T9000	303.45	285.00	
ARMSTRONG M8 Decoder	9.50	7.70	
ARMSTRONG 525	92.77	71.95	
ARMSTRONG 526	105.75	84.95	
GOODMANS Module 80, 35w. RMS	91.59	71.95	
GOODMANS Module 80 Compact	165.00	129.00	
GOODMANS Model 110 FM/MV/LW/SW 100W RMS	135.00	108.00	
LEAK Delta 75	165.00	139.95	
MIDLAND 18/542	49.43	37.50	
PHILIPS 882 with stereo cas./rec.	95.50	76.95	
PHILIPS RH 790	134.00	79.95	
PIONEER SX770 AM/FM	139.23	109.95	
PIONEER SX990 AM/FM	167.83	129.95	
PIONEER 440	104.18	82.95	
ROGERS Ravensbrook Chassis	99.39	81.95	
ROGERS Ravensbrook (cased)	108.43	89.95	
ROTEL RX150	69.90	54.95	
TANDBERG 1171	110.00	91.95	
TANDBERG TR200	99.00	82.95	
TELETON F2000	51.50	28.95	
TELETON T7A T20	119.75	69.95	
TELETON 10/T1 150w. RMS	160.00	94.00	
TELETON TFS50	79.65	52.95	
TELETON TFS50 LA MW/LW/FM	86.64	60.95	
TELETON CR55	125.26	67.95	
WHARFEDALE 100-1	139.00	89.95	
All the above Tuners and Tuner/Amplifiers take both ceramic and magnetic cartridges except Teleton			



COMET for after-sales service
THROUGHOUT THE U.K.
Pictured, Service Dept. at Clough Rd., Hull also at Leeds, Stockton, Goole, Wakefield, Doncaster, Bridlington, Birmingham, Edinburgh, Leicester and Rochdale

F2000 which takes ceramic only. All include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.

	Rec. Price	Retail Price	Comet Price
CARTRIDGES			
AUDIO TECHNICA AT66	6.47	4.50	
GOLDRING 800	12.35	8.75	
GOLDRING 800E	18.16	10.50	
GOLDRING 800 Super E	25.10	15.95	
*GOLDRING CS90 Stereo	5.02	4.10	
*GOLDRING CS91E	7.53	6.00	
GOLDRING G850	6.27	3.95	
EMPIRE 1000ZE/X	60.34	51.25	
EMPIRE 999E/X	43.00	34.95	
EMPIRE 999TE/X	28.69	21.00	
EMPIRE 999SE/X	20.31	16.95	
EMPIRE 999E/X	15.89	12.50	
EMPIRE 999I/X	12.55	10.25	
EMPIRE 909E/X	12.37	9.95	
EMPIRE 909I/X	9.26	7.75	
EMPIRE 909E/X	9.56	7.95	
ORBIT Magnetic NM 22	Special Price	2.95	
ORTOFON SL15E	28.62	22.95	
ORTOFON 2 x 15K Transformer	7.00	4.95	
ORTOFON M15E	29.08	23.50	
SHURE M3DM	7.16	4.75	
SHURE M31E	11.63	8.70	
SHURE M32E	10.73	8.05	
SHURE M32-3	9.84	7.80	
SHURE M44-5	10.73	7.19	
SHURE M44-7	9.84	7.15	
SHURE M44E	9.84	7.15	
SHURE M55E	12.52	8.95	
SHURE M75G	16.99	13.75	
SHURE M75-6	16.10	12.45	
SHURE M75EJ	18.78	14.95	
SHURE M75E	20.57	13.50	
SHURE V15-11	39.35	27.95	
Starred cartridges above are ceramic. All others are magnetic.			
PICKUP ARMS			
GOLDRING Lenco 75	13.98	9.50	
GOLDRING Lenco L69	10.04	6.50	
SME 3009 with S2 Shell	33.26	24.95	
SME 3012 with S2 Shell	35.42	26.45	
TURNABLES			
The following Turntables are complete with base, plinth, perspex cover and cartridge. Fully wired and ready for use. All at special prices.			
GARRARD SP25 Mk III with Goldring G.800	Special Price	£19.95	
GARRARD SP25 Mk III with Shure M.44.7	Special Price	£22.95	
GARRARD SP25 Mk III with Shure M.55E	Special Price	£23.95	
GARRARD AP76 with Goldring G800	Special Price	£32.95	
GARRARD AP76 with Shure M55E	Special Price	£35.95	
GARRARD AP76 with Shure M75EJ	Special Price	£39.95	
GARRARD 2025 with Sonotone 9T4HC	Special Price	£14.50	
GOLDRING 705/P with G850 26-00	£16.95		
GOLDRING GL75 with G800	Special Price	£39.95	
GARRARD SP25 Mk III	15.85	9.95	
GARRARD SL65 B	20.48	13.45	
GARRARD SL95 B	49.23	32.95	
GARRARD 401	39.26	27.45	
GARRARD SL72 B	31.83	23.95	
GARRARD Zero 100A	56.25	42.95	
GARRARD Zero 100S	51.75	41.95	
Base and Cover to fit GARRARD SP25, SL55, SL65B	Special Price	3.95	
GARRARD 40B	13.34	10.49	
GARRARD AP76	27.85	18.90	
GOLDRING GL69 Mk. II	27.60	19.50	
GOLDRING GL69P Mk. II	36.21	28.95	
GOLDRING GL75	40.15	28.95	

	Rec. Price	Retail Price	Comet Price
GOLDRING GL75P	48.76	35.95	
GOLDRING Covers for 69P and 75P	4.48	3.75	
GOLDRING C99—plinth and cover for G99	11.05	9.75	
GOLDRING G99	26.89	19.95	
GOLDRING G101P	28.68	22.95	
GOLDRING GL72 Chassis	28.68	22.95	
GOLDRING GL72P	37.29	29.95	
GOLDRING GL85	62.74	47.95	
GOLDRING GL85P	72.78	55.95	
GOODMANS 3025	37.74	21.95	
MCDONALD MP 60	15.20	10.95	
MCDONALD 610	19.28	14.50	
MCDONALD HT 70	21.22	17.50	
MCDONALD HT70 Inc. plinth & cov. Base and Cover for MCDONALD MP 60 and 610	Special Price	4.25	
PHILIPS GA146	30.35	23.95	
PHILIPS 202 Electronic	66.50	49.95	
PHILIPS 308 transcription unit complete with base and cover	37.60	29.95	
PIONEER PL12A with base & cover	48.34	36.95	
THORENS TX25 cover	8.52	6.85	
THORENS TD125	76.03	58.95	
THORENS TD125AB	115.57	94.50	
THORENS TD150 Mk. II	34.67	28.95	
THORENS TD150A Mk. II	44.40	34.50	
THORENS TD150AB Mk. II	48.05	40.25	
THORENS TX11 Cover	4.26	3.75	
WHARFEDALE Linton with base and cover and Shure M447 cartridge	35.00	28.95	
SPEAKERS			
ARENA HD 227 (pair)	42.00	26.95	
AKAI SW 155	58.48	39.95	
B & W Model 70	159.50	114.95	
B & W DM3	63.00	48.40	
B. and W DMI (per pair)	76.94	62.95	
CELESTION Ditton 120 (per pair)	57.70	45.95	
CELESTION Ditton 15	38.47	29.95	
CELESTION Ditton 25	65.00	48.95	
CELESTION DITTON 44	54.00	42.95	
GOODMANS Minister (per pair)	48.20	37.95	
GOODMANS Havant (per pair)	56.00	43.95	
GOODMANS Magister	62.50	41.95	
GOODMANS Double Maxim	33.00	25.95	
GOODMANS Mazza 3	34.00	24.95	
GOODMANS Magnum K2	44.00	30.95	
GOODMANS Dimension 8	69.00	49.95	
GOODMANS DIN 20NT kit	12.54	9.95	
KELETRON KN400 2-speaker System (pair)	16.10	12.95	
KN600 3-speaker System (pair)	26.86	18.95	
KN800 3-speaker System	15.90	10.95	
KN100 4-speaker System	20.40	14.20	
KN1600 3-speaker System	25.20	16.95	
KN2100 3-speaker System	30.60	20.95	
LEAK 150 (per pair)	49.90	37.95	
LEAK 250 (per pair)	38.00	29.95	
LEAK 600	49.50	35.95	
LOWTHER Acousta (with PM6)	52.50	45.50	
LOWTHER Acousta (with PM7)	65.00	54.00	
LOWTHER Ideal Baffle	37.50	32.00	
METRO SOUND HFS 103 (pair)	30.05	23.95	
METRO SOUND 202	21.50	16.95	
PHILIPS RH 411 (pair)	21.20	16.95	
PHILIPS RH 481 (pair)	21.20	16.95	
PHILIPS RH 482 (per pair)	34.70	28.95	
SINCLAIR Q16	8.95	6.95	
STE-M40	24.00	18.95	
TANDBERG TAN 7	25.00	23.95	
TANDBERG TAN 11 (per pair)	38.00	31.95	
TANDBERG TAN 15	45.00	35.95	
VOLTEX (Teak) pair	20.50	14.95	
WHARFEDALE Speakers			
Denton Mark II (per pair)	39.90	31.85	
Linton Mark II (per pair)	45.00	39.95	
Melton Mark II	35.00	27.95	
Dovedale 3	45.00	26.95	
Rosedale	65.00	48.50	
Triton (pair)	72.16	37.95	
Unit 3 Speaker Kit	12.53	9.70	
Unit 4 Speaker Kit	18.00	12.50	
Unit 5 Speaker Kit	26.00	16.50	

(OVER 1,520 sq. yds.)

COMET

OVER 1000 ITEMS ALWAYS IN STOCK ALL FULLY GUARANTEED - WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

COMPLETE HI-FI SYSTEMS

Completely wired mounted
and ready for use

	Rec. Price	Retail Price	Comet Price
GOODMANS AXIETTE 8	7.81	8.25	6.25
GOODMANS AXIOM 201	14.45	10.45	10.45
GOODMANS AXIOM 401	17.86	13.95	13.95
GOODMANS AXIOM 10	9.86	7.50	7.50
GOODMANS AUDIUM 8P	5.35	4.05	4.05
GOODMANS AUDIUM 10P	5.83	4.50	4.50
GOODMANS AUDIUM 12P	12.37	9.50	9.50
GOODMANS AUDIUM 15P	20.00	16.50	16.50
GOODMANS AUDIUM 18P	34.00	25.95	25.95
GOODMANS ARU172	4.50	3.25	3.25
GOODMANS TREBAX 100	8.60	5.50	5.50
GOODMANS AXENT 100	6.90	4.95	4.95
GOODMANS MIDAX 650	12.95	8.50	8.50
GOODMANS ATTENUATOR	3.55	2.25	2.25
GOODMANS CROSSOVER NETWORKS XO/950/5000	9.75	7.15	7.15
GOODMANS CROSSOVER NETWORKS XO/950	7.40	5.50	5.50
GOODMANS CROSSOVER NETWORKS XO/5000	2.65	1.85	1.85
WHARFEDALE 8in. Bronze RS/DD	4.82	3.50	3.50
WHARFEDALE Super 8/RS/DD	8.19	6.75	6.75
WHARFEDALE Super 10/RS/DD	11.20	9.50	9.50
WHARFEDALE WMT1 Matching Transformer	0.84	0.70	0.70
HI-FI STEREO SYSTEMS COMPLETE			
ALBA UA552	45.86	35.50	35.50
ALBA UA662	60.32	48.95	48.95
AMSTRAD Stereo 1000	48.00	36.95	36.95
DECCA Sound 613	70.14	57.95	57.95
DECCA Sound 614	66.55	54.95	54.95
DECCA Sound 1204	89.44	72.95	72.95
DECCA Compact 3	119.56	103.95	103.95
FERGUSON 3423	114.15	89.95	89.95
FERGUSON 3425 with radio	140.10	109.00	109.00
FERGUSON 3450 with radio	72.40	61.95	61.95
FERGUSON 3451	99.50	79.95	79.95
FIDELITY UA2 Music Master	44.41	34.95	34.95
FIDELITY UA1 Music Master with radio	103.29	79.97	79.97
GOODMANS Module 80 Compact System FM/35W. R.M.S. (less L/S)	165.00	129.00	129.00
SPECIAL OFFER			
GOODMANS Max-amp Stereo Amplifier, Goodmans Stereo-max AM/FM Tuner with Decoder, Pair of Goodmans Magnum K2 Spea- kers, Garrard A.P.76 Turntable in base, complete with cover and Goldring G.800 Cartridge. Beauti- fully finished in Walnut	257.13	155.00	155.00
H.M.V. 2404/5/6 with radio	198.00	153.00	153.00
HMV 2452	65.65	54.95	54.95
HMV 2450 with stereo radio	134.20	109.00	109.00
MARCONI 4450 with radio	72.40	56.95	56.95
MARCONI 4452	76.00	57.95	57.95
METROSOUND Stereo 1010 com- plete with speakers	79.34	55.95	55.95
MURPHY Studio One with Stereo Radio	86.84	66.95	66.95
PHILCO Ford M1500	99.93	68.50	68.50
PHILIPS 580/481/105	71.00	55.95	55.95
PHILIPS GF 823	47.80	37.95	37.95
PHILIPS GF 824	67.10	53.95	53.95
PHILIPS GF 831	67.10	52.95	52.95
PHILIPS GF 834	86.40	66.95	66.95
PHILIPS GF 417	96.06	69.95	69.95
PYE Black Box Unit Stereo 1022	93.45	69.95	69.95
STEEPLETONE Stereo system	41.75	33.95	33.95
TELETON STP 8-track Stereo System	54.75	47.00	47.00
ULTRA 6405	77.00	64.95	64.95
TAPE RECORDERS AND TAPE DECKS			
AKAI 1200L 4-track Stereo	83.73	81.95	81.95
AKAI 4000D 4-track stereo deck	89.95	65.95	65.95
AKAI CR80D 8-track stereo tape deck	79.95	58.95	58.95
AKAI CR80 8-track stereo recorder	99.95	75.95	75.95
AKAI X200D	145.95	111.00	111.00
AKAI 1600SD	153.00	117.00	117.00
AKAI 2000SD	289.00	216.00	216.00
BUSH Discassette DC70	21.19	16.95	16.95
BUSH TP60 Cassette tape recorder	28.38	23.95	23.95
BUSH TP70 Cassette, battery/mains tape recorder	28.91	23.50	23.50
FERGUSON 3245 4-track stereo	36.70	27.95	27.95
FERGUSON 3246 4-track	42.55	32.95	32.95
FERGUSON 3247 4-track	47.95	37.95	37.95
FERGUSON 3248 4-track	53.75	41.95	41.95
FERGUSON 3252 4-track	100.52	80.95	80.95
FERGUSON 3258 4-track	72.40	55.95	55.95
FERROGRAPH 702 2-track tape deck	220.22	185.00	185.00
FERROGRAPH 704/W 4-track tape deck	220.22	185.00	185.00
FERROGRAPH 722	256.52	209.00	209.00
FERROGRAPH 702 Dolby	272.25	229.00	229.00
FERROGRAPH 724	256.52	209.00	209.00
FERROGRAPH 722 Dolby	308.55	262.00	262.00
GRUNDIG C200 De Luxe Cassette	38.45	28.95	28.95
GRUNDIG TK 121 twin track	57.90	42.95	42.95
GRUNDIG TK 141 4-track	63.90	47.95	47.95
GRUNDIG TK 146 4-track Auto	68.90	53.95	53.95
GRUNDIG 222 stereo cassette	59.85	47.95	47.95
GRUNDIG TK 147 4-track Auto	95.75	79.95	79.95
MIDLAND TC 144 cassette	18.00	14.95	14.95
PHILIPS 2202 cassette	26.90	21.95	21.95
PHILIPS 2204 cassette, battery/mains	32.30	25.95	25.95
PHILIPS 3302 cassette	23.05	17.50	17.50
PHILIPS 4303 new release	40.55	32.50	32.50
PHILIPS 4307 4-track	47.80	36.95	36.95
PHILIPS 4308 De Luxe 4-track	58.40	44.95	44.95
PHILIPS 4404 2-track stereo recorder	91.70	69.95	69.95
PHILIPS 4407 4-track stereo recorder	106.20	86.95	86.95
PHILIPS 4500 4-track stereo tape deck	121.65	95.95	95.95
PHILIPS 4408 4-track stereo	134.20	105.95	105.95
PHILIPS 2503 Cassette Stereo tape deck	52.05	45.95	45.95
PHILIPS 2400 stereo cassette less L/S	65.55	58.45	58.45
PYE Cassette Recorder/Radio 9000 battery/mains	43.86	35.95	35.95
PYE 9109 cassette	23.04	18.95	18.95
PYE 9116 Stereo cassette	65.55	51.95	51.95
TANDBERG 1841 4-track stereo tape deck	68.00	57.50	57.50
TANDBERG 3021X twin track stereo	107.00	91.00	91.00
TANDBERG 3041X 4-track stereo	107.00	89.95	89.95
TANDBERG 4021X twin track stereo	174.00	145.00	145.00
TANDBERG 4041X 4-track stereo	174.00	145.00	145.00
TANDBERG 6011X 4-track stereo	188.00	156.95	156.95
TANDBERG 6021X twin track stereo	188.00	158.00	158.00
TELETON 8100 cassette	26.75	14.95	14.95
TELETON TC110 cassette battery/ mains	26.79	18.95	18.95
TELETON TRC130 cassette with VHF/AM Radio, batt./mains, twin motors	40.31	27.95	27.95
TELETON 511 battery/mains cassette	29.50	16.00	16.00
WHARFEDALE Dolby DC9 cas- sette stereo tape deck	110.00	94.50	94.50
BASES AND COVERS			
GARRARD WB4 Base	3.71	3.25	3.25
GARRARD WB4 Base	5.49	4.75	4.75
GARRARD SPC1 Cover	3.60	2.95	2.95
GARRARD SPC4 Cover	4.27	2.75	2.75
Special offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500			
GOLDRING Plinth 75	Special Price 3.95	8.60	7.00
GOLDRING Plinth 69	8.60	7.00	7.00
GOLDRING Covers for 69P and 75P	4.48	3.75	3.75
THORENS TX25 (for TD125AB)	8.52	6.95	6.95
THORENS TX11 Cover	4.26	3.75	3.75
Base and Cover for TD 125	15.04	12.45	12.45
SME Plinth System 2000	41.36	33.50	33.50
MOTORBOARDS only	5.22	3.25	3.25



All in-stock items delivered by
SECURICOR
WITHIN 72 HOURS
(Add £1.75 only for Securicor delivery)
ALL GOODS FULLY INSURED AGAINST
LOSS OR DAMAGE WHILST IN TRANSIT

	Rec. Price	Retail Price	Comet Price
CHASSIS SPEAKERS			
GOODMANS Axiette 8	7.81	8.25	6.25
GOODMANS Twin-axiette 8	8.84	6.95	6.95
GOODMANS Axlom 201	14.45	10.45	10.45
GOODMANS Axlom 401	17.86	13.95	13.95
GOODMANS Twin Axlom 10	9.86	7.50	7.50
GOODMANS Audium 8P	5.35	4.05	4.05
GOODMANS Audium 10P	5.83	4.50	4.50
GOODMANS Audium 12P	12.37	9.50	9.50
GOODMANS Audium 15P	20.00	16.50	16.50
GOODMANS Audium 18P	34.00	25.95	25.95
GOODMANS ARU172	4.50	3.25	3.25
GOODMANS Trebax 100	8.60	5.50	5.50
GOODMANS Axent 100	6.90	4.95	4.95
GOODMANS Midax 650	12.95	8.50	8.50
GOODMANS Attenuator	3.55	2.25	2.25
GOODMANS Crossover Networks XO/950/5000	9.75	7.15	7.15
GOODMANS Crossover Networks XO/950	7.40	5.50	5.50
GOODMANS Crossover Networks XO/5000	2.65	1.85	1.85
WHARFEDALE 8in. Bronze RS/DD	4.82	3.50	3.50
WHARFEDALE Super 8/RS/DD	8.19	6.75	6.75
WHARFEDALE Super 10/RS/DD	11.20	9.50	9.50
WHARFEDALE WMT1 Matching Transformer	0.84	0.70	0.70
HI-FI STEREO SYSTEMS COMPLETE			
ALBA UA552	45.86	35.50	35.50
ALBA UA662	60.32	48.95	48.95
AMSTRAD Stereo 1000	48.00	36.95	36.95
DECCA Sound 613	70.14	57.95	57.95
DECCA Sound 614	66.55	54.95	54.95
DECCA Sound 1204	89.44	72.95	72.95
DECCA Compact 3	119.56	103.95	103.95
FERGUSON 3423	114.15	89.95	89.95
FERGUSON 3425 with radio	140.10	109.00	109.00
FERGUSON 3450 with radio	72.40	61.95	61.95
FERGUSON 3451	99.50	79.95	79.95
FIDELITY UA2 Music Master	44.41	34.95	34.95
FIDELITY UA1 Music Master with radio	103.29	79.97	79.97
GOODMANS Module 80 Compact System FM/35W. R.M.S. (less L/S)	165.00	129.00	129.00
SPECIAL OFFER			
GOODMANS Max-amp Stereo Amplifier, Goodmans Stereo-max AM/FM Tuner with Decoder, Pair of Goodmans Magnum K2 Spea- kers, Garrard A.P.76 Turntable in base, complete with cover and Goldring G.800 Cartridge. Beauti- fully finished in Walnut	257.13	155.00	155.00
H.M.V. 2404/5/6 with radio	198.00	153.00	153.00
HMV 2452	65.65	54.95	54.95
HMV 2450 with stereo radio	134.20	109.00	109.00
MARCONI 4450 with radio	72.40	56.95	56.95
MARCONI 4452	76.00	57.95	57.95
METROSOUND Stereo 1010 com- plete with speakers	79.34	55.95	55.95
MURPHY Studio One with Stereo Radio	86.84	66.95	66.95
PHILCO Ford M1500	99.93	68.50	68.50
PHILIPS 580/481/105	71.00	55.95	55.95
PHILIPS GF 823	47.80	37.95	37.95
PHILIPS GF 824	67.10	53.95	53.95
PHILIPS GF 831	67.10	52.95	52.95
PHILIPS GF 834	86.40	66.95	66.95
PHILIPS GF 417	96.06	69.95	69.95
PYE Black Box Unit Stereo 1022	93.45	69.95	69.95
STEEPLETONE Stereo system	41.75	33.95	33.95
TELETON STP 8-track Stereo System	54.75	47.00	47.00
ULTRA 6405	77.00	64.95	64.95
TAPE RECORDERS AND TAPE DECKS			
AKAI 1200L 4-track Stereo	83.73	81.95	81.95
AKAI 4000D 4-track stereo deck	89.95	65.95	65.95
AKAI CR80D 8-track stereo tape deck	79.95	58.95	58.95

Complete Price List FREE on request! **COMET HIGH FIDELITY DISCOUNT WAREHOUSES**

- (Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407906 and 407877
- (Dept. P.W.) 68A Armlay Rd., (Artist St.), Leeds LS12 2EF Tel. 32055 (5 lines)
- (Dept. P.W.) Teesway, Portrack Lane, North Teesside Industrial Estate, Teesside, TS18 2RH Tel. 66132 and 65215
- (Dept. P.W.) Heeley Road, Selly Oak, Birmingham Tel. 021-472 6181
- (Dept. P.W.) 7, Newhaven Road, Edinburgh EH6 5QX Tel. 554 8501
- (Dept. P.W.) Syston Street, Leicester Tel. 52236
- (Dept. P.W.) Well i' th' Lane and Corner of Queensway, Rochdale Tel. 50606

Open daily to the public from 9-0 A.M. until—
5-30 P.M. MON.
1-0 P.M. TUES.
8-0 P.M. WED.
8-0 P.M. THUR.
8-0 P.M. FRI.
5-30 P.M. SAT.
Customers are welcome to call. Ample car parking facilities

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) or if Securicor delivery required add £1.75 only. Make cheques, Money Orders payable to "COMET"

Free Technical Advisory Service. If in doubt, ask us!

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 9p per word (minimum 12 words), box number 10p extra. Semi-displayed setting £6.50 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

Miscellaneous

... LOTS OF

suppliers forget to tell you that their metal locators won't function until you've first got a transistor radio with which to beat the locators signal. The **BOFFIN TREASURE PROBE**, however, comes to your doorstep with **PRINTED CIRCUIT BOARD**, all **ELECTRONIC COMPONENTS**, a ready-drilled box to put it in plus search-coil and earphone. Think of the fun you'll have **BEACH-COMBING** with the sensitive **TREASURE-PROBE**, and the expectancy of hearing its **LOUD "BEEP"** tell you **"YOU'RE ON TO SOMETHING"**. **GET YOUR TREASURE-PROBE, SEND £4.95 NOW!**

BOFFIN PROJECTS
4, CUNLIFFE RD.
STONELEIGH EWELL
SURREY

Designed by **GERRY BROWN & JOHN SALMON** and presented on TV

DO-IT-YOURSELF ... we stock a large range of audio and electronic components at very competitive prices, e.g.: chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale & Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for **FREE** list (2 x 3p stamps for fabric samples). Mail order **ONLY**. No callers please.

AUDIOSCAN Dept. PW2.72
4, PRINCES SQUARE
HARROGATE, YORKS.

SYNTHESISER MODULES

Send SAE for details of voltage-controlled modules for synthesiser construction to **D.E.W. Ltd.**, 254 Ringwood Road, Fern-down, Dorset.

CHROMASONIC electronics

1972 CATALOGUE

10p post free

56 FORTIS GREEN ROAD, LONDON N10 3HN

THE NEW ELECTRONIC MUSIC FOR YOU

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing. Write **NOW** for free leaflet and further details to **C. & S.**, 20 Maude Street, Darlington, Durham. Send 21p stamp.

TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1.90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

J. M. KING (U)

17 Buckridge, Portpool Lane, London, E.C.1

12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins Ø watt Tube, Ideal for Caravan, Tent, Emergency Lighting etc, Fully Transistorised, Low Battery Drain, With ON/OFF Switch and 12v Socket to Run other Lights or 12V Equipment.

Unbeatable at **£3.30** post paid
or in kit form **£2.90**

SALOP ELECTRONICS Callers welcome
23 Wyle Cop
Shrewsbury, Shropshire S.A.E. for lists

TAPE HEADS PICK-UP CARTRIDGES

SERVICE MANUALS for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required.

Send stamp for comprehensive lists of transformers, condensers, resistors, cartridges and tape heads.

R. D. I. LTD.

Chilton Works, Garden Road,
Richmond, Surrey.

JOHN SAYS...

RING MODULATOR by Dewtron is professional, transformerless, 5-transistor, has adjustable FI/F2 rejection. Module £7. Unit £8.90, **WAA-WAA** Pedal kit of all parts, incl. all mechanics & instr. Only £2.95, **AUTO RHYTHM** from Dewtron modules. Simple units for waltz, fox-trot etc. costs under £20 in modules. **SYNTHESISER MODULES** and other miracles. Send 15p for illust. list.
D.E.W. Ltd., 254 Ringwood Road,
Fern-down, Dorset.

RECORD TV SOUND using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p +10p P&P. **CROWBOROUGH ELECTRONICS** (P.W.), Eridge Road, Crowborough, Sussex.

GENUINE FULL SIZE 18 element TV aerial

as used by leading rental companies

FOR ONLY

£1.99

+ 34p p&p



A fantastic buy, save money and do-it-yourself. Receives BBC1, BBC2 and ITV on UHF 625 channels, colour and black/white. 18 element aerial with grid reflector for better reception. A proper aerial, usually supplied only by riggers. Buy now and cut out the middle man. An ideal aerial for the person who likes to do it himself. Complete with fixing clamp and instructions. Money back guarantee. Use inside or out.

IMPERIAL TRADING

Dept. PW10, 45 AREWRIGHT ST., NOTTINGHAM

BUILD IT in a **DEWBOX** quality cabinet. 2in x 2½in x any length. **D.E.W. Ltd.**, Ringwood Road, **FERN-DOWN**, Dorset. S.A.E. for leaflet. Write now—Right now.

TRANSISTOR OPTICAL Burglar/Fire/UFO Circuit, 60p. TV Notes **UFO** Detection, Two Optical Circuits, 50p. Portfolio **UFO** Patterns, Map £1. R & E Publications, "Highlands" Needham Market, Suffolk.

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this **GPO** approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually **SECRET** since they won't be heard by conventional means. Actually it's **TWO KITS IN ONE** because you get all the printed-circuit boards and components for both the transmitter **AND** receiver. You're going to find this project **REALLY FUN-TO-BUILD** with the **EASY-TO-FOLLOW** instructions. An extremely flexible design with quite an **AMAZING RANGE**—has obvious applications for **SCHOOL PROJECTS**, **LANGUAGE LABORATORIES**, **SCOUT CAMPS**, etc.

GET YOURS! SEND £5.20 NOW

TO: **'BOFFIN PROJECTS'**

DEPT. KW2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

WORLD RADIO TV Handbook 1972, post free £2.25. World Radio Bulletin, fortnightly from Denmark, £2.55 surface mail, £3.17 airmail. S.A.E. for sample. Ordered together 35p off. **McGarva**, Chambers Street Union, Edinburgh 1.

Aerials

Direct from the Manufacturers
U.H.F. AERIALS
EASY ASSEMBLY KITS
10 Element **SAVE**
£125.40 on normal retail price
14 Element 18 Element
£150 £175
Ready assembled and ZUP.
Allow 22" for carriage and packing.
Please state which channels of group.
APEX AERIALS (P.W.)
ALBAN WORKS, MARLY ST. JOHNSTONE, RENFREWSHIRE

BAINES for HIGH FREQUENCY AERIALS AND FITTINGS
POSTAGE PAID ON ALL AERIALS INLAND UHF MULTIBEAMS: These aerials are high gain, broad banded and supplied complete with a clamp for most fitting. MBM 10, £1-90; MBM 18, £2-65; MBM 30, £3-60; MBM 38, £5-10; MBM 46, £5-50. BBC 405 AERIALS: Dipole, £1-75; H, £2-50; X, £2-40. ITA 405 AERIALS: 5 element, £2; 8 element, £2-70. FM for MONO or STEREO: Dipole, £1-40; 2 element, £2. COMBINED BBC/ITA 405: Dipole and 5, £2-70; H and 5, £4-10. ACCESSORIES—Postage by Weight, 6" Chimney lashing, £1; 12", £1-15. 6" wall bracket, 45p; 12", £1-85. 5" x 1" poles, 55p. Clamps 1" x 1", 25p; 2" x 1", 45p. Co-ax 5p and UHF 9p. Co-ax plugs, 7p. Outlet box, 50p. PRE-AMPS: Masthead, £12, postage paid. Set mounted, £3-88, postage paid. Please state channels on all aerial orders.
R. BAINES, 11 DALE CRES., TUPTON, CHESTERFIELD

Service Sheets

TRADER SERVICE SHEETS

40p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES LIMITED

29 CHURCH ROAD,
TUNBRIDGE WELLS, KENT

Make	Model	Radio/TV

1971 List now available at 10p plus postage

If list is required indicate with X

From

Address

enclose remittance of

(and a stamped addressed envelope)
s.a.e. with enquiries please

MAIL ORDER ONLY

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

Service Sheets

★ Service Sheets and Manuals ★ COVERING RADIOS, TELEVISIONS, TAPE RECORDERS, RECORD PLAYERS, ETC. FROM 1933 UP-TO-DATE FROM 40p. EACH - 1971 SERVICE SHEET INDEX LIST 20p. - S.A.E. WITH ENQUIRIES PLEASE

	Price	Post
◀ NEW BOOKS & PUBLICATIONS ▶		
BEGINNER'S GUIDE TO RADIO by Gordon J. King, 7th Edition. 204 pages	£1.00	10p
BEGINNER'S GUIDE TO TELEVISION by Gordon J. King, 208 pages	£1.00	10p
RADIO VALVE AND TRANSISTOR DATA by A.M. Ball, 9th Edition. 232 pages	£0.75	15p
UNDERSTANDING THE SEMICONDUCTOR by C.N.G. Matthews. 128 pages	£1.00	10p
UNDERSTANDING TELEVISION by J.R. Davies. 512 pages	£1.88	20p
THE PRACTICAL AERIAL HANDBOOK by Gordon J. King. 232 pages	£2.70	15p
COLOUR TELEVISION PICTURE FAULTS by K.J. Bohlman, AM.Inst.E. Illustrated in Colour.	£2.50	15p
T.V. FAULT FINDING BOOK by Data Publications Ltd. 405/625 Edition. 124 pages	£0.50	7p
1971-1972 MULLARD DATA BOOK. Data on Valves & Semiconductors	£0.30	5p
1970-1971 MULLARD DATA BOOK. Data on Valves & Semiconductors	£0.20	5p
TRANSISTOR EQUIVALENTS & SUBSTITUTES HANDBOOK by B.B. Babani	£0.40	5p
RESISTOR COLOUR CODE INDICATOR DISC	£0.10	3p

Send S.A.E. for 'FREE' List of Practical and Technical Books on Radio & Television now available to:-

BELL'S TELEVISION SERVICES
Albert Place, Harrogate, Yorkshire. Telephone 0423-86844

SERVICE SHEETS (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 15p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone Bexhill 7097.

RADIO, TELEVISION and Tape Recorders, 50 mixed odd sheets 50p. Also large stock of Obsolete/Current Valves. John Gilbert TV, 1B Shepherds Bush Road, London W6. 01-743 8441. SAE enquiries.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
Only 25p each.

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"
Otherwise cannot be attended to (Uncrossed P.O.s please, original returned if service sheets not available.)

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order only.

Wanted

WE BUY New Valves and Transistors. State price: A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S WIRELESS STORES**, 55 Worcester Street, Wolverhampton.

CASH PAID for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

TOP PRICES PAID for NEW VALVES
popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

HIGHEST POSSIBLE cash prices for Akai, B. & O., Brenell, Ferragroph, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

For Sale

YUKAN SELF-SPRAY
Get these air-drying GREY HAMMER or BLACK WRINKLE (CRACKLE) Finishes NOW!
Yukan Aerosol spraykit contains 493g fine quality durable easy instant spray. No stove baking required. Hammers available in grey/blue. Modern Eggshell Black Wrinkle (Crackle) all at 89p in our counter or 90p carriage paid per push button set-up as can. Also Durable, heat and water resistant Black Matt finish (395g self-spray cans only). 75p carriage paid.
SPECIAL OFFER: I can plus optional transferable finish on 1-gger handle valve 75p for 90p carriage paid. Choice of 13 self-spray paint colours and primer (Motor car quality) also available. Please enclose cheque or crossed P.O. for total amount.
Dept. YUKAN, 307A, EDGWARE ROAD, PW2
We supply many Government Departments, Municipal Authorities, Industries and Leading Industrial Organisations. We can supply you too. Open all day Saturday. Closed Thursday afternoons.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

MORSE MADE !! EASY !!

FACT NOT FICTION if you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed. Complete Course £4.50 (Overseas £1.00 Extra) Details only 4p stamp. 01-660 2898 or 01-668-3255.

G&HC (Box 19), 45 GREEN LANE, PURLEY, SURREY

Educational

CIE, AMSE, City & Guilds, etc., on 'Satisfaction or Refund' terms. Thousands of exam. successes. Postal Courses for all branches of Engineering. Illustrated prospectus **FREE**. Please state subject of interest: BIET, (Dept. H.8), Aldermaston Court, Reading, RG7 4PF.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.



TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: London Electronics College, Dept. A/2, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs') RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS RD., LONDON, SW8 4UJ
"ACCREDITED BY THE CACC"

RTEB CERTS., City & Guilds, Colour TV, Radio, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—FREE: BIET, (Dept. H.7), Aldermaston Court, Reading, RG7 4PF.

Situations Vacant

RADIO OPERATORS

DO YOU HAVE PMG I, PMG II, MPT 2 YEARS OPERATING EXPERIENCE?

Possession of one of these qualifies you for consideration for a Radio Operator post with the Composite Signals Organisation.

On satisfactory completion of a 7-month specialist training course, successful applicants are paid on scale rising to £2200 pa; commencing salary according to age—25 years and over £1548 pa. During training salary also by age, 25 and over £1152 pa with free accommodation.

The future holds good opportunities for established (i.e. pensionable) status, service overseas and promotion. Training courses commence every January, April and September. Earliest possible application advised.

Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered. Full details from:

RECRUITMENT OFFICER,
GOVERNMENT COMMUNICATIONS HEADQUARTERS,
Room A/1105 Oakley, Priors Road,
CHELTENHAM, Glos. GL52 5AJ
(Telephone: Cheltenham 21491, Ext. 2270)

Situations Vacant

EAGLE INTERNATIONAL require Audio Engineers; excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact Mr. Morrow 01-903 0144.

Receivers and Components

nippiboard

PRINTED WIRING BOARD for transistor circuits
BUILD THESE **PW** DESIGNS

- Take Twenty-TYPE 1A Nippiboard
- Mini-Amplifier-TYPE 1A Nippiboard
- Modular Audio Mixer—TYPE 1A per circuit or 4xTYPE 2A
- Two-octave Miniature Organ—TYPE 2A Nippiboard
- Transistor Tape Recorder (Mono)—TYPE 2A
- Stereo Decoder Unit—TYPE 6BS Nippiboard
- Experimenters' Circuits Supplement—Various Types
- AF/RF Mini-probe—TYPE 1B Nippiboard
- Sound Generated Flash—TYPE 1B Nippiboard

srtp		Nippiboards		fibreglass	
Type 1A	15p	Type 1B	18p		
2A	28p	2B	34p		
2AS	28p	6BS	72p	2BS	34p
4AS	44p	4BS	52p		

NIP ELECTRONICS Dept. NBW
P.O. BOX 11 ST ALBANS, HERTS

EX-RENTAL TV's (UNTESTED)

Complete with 13 channel tuners. Good cabinets. Carriage £1.50 extra.

17" Beml Slim (90° Tube)	£2-50
17"/21" Slim (110° Tube)	£4-50
19" Slimline	£6-80
23" Slimline	£8-80
19" BBC2 Beta	£14-60

TUBES EX EQUIPMENT (Tested)

SINGLE PANEL

17" any type	£2-00
19"/21" any type	£3-00
23" any type	£4-00

TWIN PANEL (BONDED)

19" bonded	£5-00
23" bonded	£6-00

PANORAMA TUBES (METAL RIM)

19" Panorama	£5-00
23" Panorama	£6-00

All tubes add £1 carriage.

PERFECT SPEAKERS EX T.V.

Pm 3 ohm (minimum order two) 5 in. round, 8 in. by 2 in. rectangular—12 1/2p each. Add 7 1/2p per speaker p. & p.

Special offer:—100 Speakers delivered for £15.00.

VALVES EX EQUIPMENT

EB91	5p	30L15	12 1/2p	PL36	22 1/2p
EBF89	12 1/2p	30P4	12 1/2p	PL81	17 1/2p
ECC82	12 1/2p	PC97	17 1/2p	FY81	15p
EC180	7 1/2p	PC96	17 1/2p	FY80	15p
EF80	12 1/2p	PC84	7 1/2p	PY82	7 1/2p
EF85	12 1/2p	PCF80	7 1/2p	PY83	22 1/2p
EF183	12 1/2p	PCC89	12 1/2p	UI91	17 1/2p
EF184	12 1/2p	PCL85	22 1/2p	6P23	17 1/2p
EY86	17 1/2p	PCL82	17 1/2p	30PL1	22 1/2p
30PL13	20p	PCL86	17 1/2p	30P12	20p
830LZ	12 1/2p	PCL83	12 1/2p	30F5	10p

Add 2 1/2p per valve p. & p., orders over £1 p. & p. free

UHF TUNERS

For Ferguson 850 900 chassis. Adaptable for most UHF Chassis £2-50, p. & p. 50p.

TRADE DISPOSALS (Dept. PW/TS)

Thornbury Roundabout, Leeds Rd., Bradford.
Telephone 0274/865670

SINCLAIR IC-12 £2-45

Integrated circuit amplifier and pre-amp with 8W rms output. Frequency response 5Hz-100kHz. Harmonic distortion less than 1%, and typically 0.1%. Supplied complete with instructions and free printed circuit. Also available kits of parts including simple volume and tone controls to complete mono version £1-00. Similar for stereo version £2-45. Loudspeakers 5" (3 ohm) 90p, 8" x 5" (6 ohm) £1-35. Ideal power supply for the IC-12 is the Sinclair PZ5 £3-80.

WORLD'S SMALLEST RADIO

Sinclair Micromatic receivers complete with earphone and instructions. Kit £2-20. Built £2-60. Batteries 27p extra.

SINCLAIR PROJECT 60S

The easy new way to buy and build project 60. Comes in one handy pack containing PZ5, two Z30 amplifiers, Stereo 60 and the new master-link module, which has all the input sockets and output components needed. Special cut to length leads make all soldering unnecessary. ONLY £20-95 Post 30p.

TRANSISTOR SENSATION

Thanks to bulk buying we have been able to smash the price of our well known surplus PNP Silicon transistors from the 23300 series. These are untested and unmarked but we guarantee that at least 80% are good useable transistors. 100 for 35p, 200 for £1-00, 1000 for £3-60.

S-DECS AND T-DECS

S-DeCs £1-25. T-DeCs £2-50. µ-DeC A £2-80. Carriers with sockets to mount 14 and 18 pin in line ICs on T-DeC and µ-DeC A £1-10.

PROJECT 60 MODULES

All at incredible, low prices	
Completion Kit (See below)	£2-40
Project 60 FM tuner	£18-50
Active filter unit	£4-50
PZ5 Power unit, 30V un stabilized	£3-80
PZ6 Power unit, 35V stabilized	£6-40
PZ8 Power unit, 45V stabilized	£6-40
Transformer for PZ3	£2-45
Z30 Amplifier, 15W rms into 8 Ohms	£3-60
Z50 Amplifier, 30W rms into 8 Ohms	£4-15
Stereo 60 Preamp/Control unit	£7-80
Q16 Loudspeaker	£7-40

PROJECT 60 KIT

Our extremely popular completion kit contains the extra capacitors, DIN plugs and sockets, cables and fuse holder needed to complete Project 60 at the attractive price of £2-40.

MULLARD UNILEX

EP9000 Amp £2-40. EP9001 Pre-amp £2-80. EP9002 Power unit £3-90. Control unit £2-80. Unilex booklet £0-22.

SINCLAIR 3000 £30-60 Post 50p.

SWANLEY ELECTRONICS

32 Goldsel Road, Swanley, Kent

Mail order only. Postage 37p on Project 60 orders, 10p on others.

COMMUNICATION RECEIVERS

Checked, tested B40, R209, etc., SAE requirements.

R1155 RX

Latest release, with super S/M drive in fine condition. 75kHz-1.5 MHz 3-18.5 MHz in 5 bands. BFO, tuning ind. etc. Tested with CCT £10, carriage £1.

VHF RX 67907

Compact double conversion RX with 20 min valves. AM/FM 10 ch. XTAL controlled. 250MHz approx. 500µA check/tuning meter etc., suitable for conversion to 2M £4-50, carriage £1. Some for callers at £4.

RICHARD SELLERS
EASTRINGTON (254),
GOOLE, YORKSHIRE

Receivers and Components

D. J. COMPONENTS 14B, Sussex Road, Harrow, Middlesex

All devices brand new, fully tested and guaranteed
Prices in New Pence each unless otherwise stated

INTEGRATED CIRCUITS 74 series D.I.L. 7400, 01, 02, 03, 04, 05, 10, 20, 30, 40, 50, 51, 53, 54, 60, 15p. 41, 42, 80, 83, 90, 92, 93, 94, 95, 67p. 75, 76, 45p. 70, 72, 30p. 81, 82, 91, 118, 145, 151, 95p. 73, 74, 40p. 86, 121, 50p. 7447, 90p.

CARBON FILM RESISTORS
1/2W 5% 10 to 1.5M ohms 1-9 1p.
10-99 0.9p.

LINEAR IC's TOS/DIL 709 40p
MC1303 (stereo) £1.45.

SILICON RECTIFIERS

PIV	50	100	200	400	600	800	1Kv
3A	4	4 1/2	5	5	8	10	13
1A	4 1/2	4 1/2	5	6	9	12	14
3A	13	15	19	21	23	25	28

ELECTROLYTIC CAPACITORS

25V	1.0, 2.2, 3.3, 4.7, 10, 22mf.
16V	33, 100, 220mf. All 5p each.
16V	22mf 4p, 330mf 10p, 16V 470mf 18p, 1000mf 20p.

SMALL SIGNAL TRANSISTORS

BC107, 108, 109, ZTX108 10p.
ZTX107, 109, 13p. ME0412, 15p.
ME0411, 0413, 14p. 0414, 11p.
ME6001, 15p. ME8003, 20p.

BRIDGE RECTIFIERS

	100V	200V	400V
1A	40	45	50
3A	60	65	70
6A	70	75	80

ZENER DIODES

0.4W, 5% tol 3.3-43V
12p. 1W, 5% tol 6.8-200V. 17p.

Discount 10% on orders over £2. P. & P. 5p. Mail order only.

LOW PRICED

SEMI CONDUCTORS

ALL OUR STOCKS ARE BRAND NEW, NO REJECTS, NO SECONDS. ALL GUARANTEED. P. & P. 5p.

TRANSISTORS

AC 188K	2N 3055	49p
AC 187K	AD 142	50p
Matched Pair	BC 107	8p
AC 141K	BC 108	8p
AC 142K	BC 109	8p
AL 102	BC 142	35p
AU 103	BC 142	35p
ME 0412	BFY 51	10p
ME 4101	BFY 52	10p
ME 4102		10p
ME 6002	W 005	30p
MP 8111	W 02	30p

DIODES & RECTIFIERS

IN 4001 8p
400mW ZENER DIODE IN 4904 9p
3.3v to 30v 12p
SEND S.A.E. FOR FREE PRICE LIST. Includes hundreds of TRANSISTORS, CAP'S, TTL'S ETC. FREE EQUIVALENT CHART.

C. HADLEY (P.W.)
24 WOODHILL, HARLOW, ESSEX

NEW GUARANTEED DEVICES ORDER WITH CONFIDENCE

MICROCIRCUITS:

SN76013 (like IC12) £1.50; 709 33p; 741 3p; PA230 90p; PA234 84p; PA237 £1.50; SL402A £1.75; SL702C 40p.
TTL GATES 15p; FLIPFLOPS 37p.

TRANSISTORS:

2N2926 Grn 8p; 2N3055 50p; BC107B 9p; BC108C 9p; BC109C 9p; BFX 86 15p; ME0402 21p; ME0411 19p; ME0412 20p; ME0413 15p; ME1002 11p; ME101 11p; ME4102 12p; ME6101 15p; ME6102 17p; ME8001 15p; MP8111 35p; MP8112 45p.

1 AMP RECTIFIERS:

50V 3p; 100V 4p; 200V 5p; 400V 6p.
BRIDGES: 50V 30p; 100V 31p; 400V 33p.
3 AMP RECTIFIERS: 400V 12p; 200V 10p.

PRINTED CIRCUIT RESIST PEN: 80p.

Discounts begin at 10 off.

JEF ELECTRONICS (P.W.2)

York House, 12 York Drive, Grappenhall, Warrington, WA4 2EJ Mail Order Only.
C.W.O. P & P 7p per order. Overseas 65p.
Money back if not satisfied.
List free on application.

ELECTRONIC MUSIC

Build your own units or even a complete sound machine from our circuit assemblies. These include I-C Ring Modulator, Phasing amps, White Sound effects, auto Waa-Waa, an amazing V-C oscillator, and many others. Send 10p for catalogue; mail-order only.
Taylor Electronic Music Devices
Tegid House, Bala, Merioneth

EX COMPUTER PRINTED CIRCUIT PANELS
2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p. P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 30 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875, All long leaded on panels 13in x 4in. 4 for £1, P. & P. 25p.

708C OPERATIONAL AMPLIFIER
705 8 lead I.C. 1 off 50p; 50 off 35p; 100 off 20p.

250 MIXED RESISTORS 62p
1 & 1/2 watt

150 MIXED HI STABS 62p
1, 1/2 & 1 watt 5% & better

QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

GPO EXTENSION TELEPHONES

With dial but without bell.
95p each, P. & P. 30p.
£1.75 for 2, P. & P. 30p.

BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V, 2.5kΩ coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
44 EARLS COURT ROAD,
LONDON W.8 01-478 8499

BRAND NEW COMPONENTS by return. Electrolytics 15 or 25V 1, 2, 5, 10 mfd.-3.5p; 25, 50-4p; 100-5p. Mylar Film 100V .001, .002, .005 .01, .02-2p; .04, .05-2.5p; .068, .1-3p. Mullard miniature Carbon Film resistors E.12 series 1/3W 10-10MΩ 8 for 5p. Insured postage 8p. The C.R. Supply Co., 127, Chesterfield Rd., Sheffield S8.

EX-GOVT. COMMUNICATIONS RECEIVERS, calibrators, signal generators, components, etc., with money back guarantee. S.A.E. list. Callers welcome, please phone first. P. R. Gollidge, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

NOW DIRECT TO YOU!
THE SINCLAIR PROJECT 605 AMPLIFIER
AT A HUGE SAVING

Sinclair Project 605 Amplifier



NO SOLDERING NEEDED
Now you can assemble your own high fidelity system to world beating standards with the SINCLAIR PROJECT 605.
In one neat package you obtain everything you need to build a complete 30 watt stereo amp. (I remember no soldering is needed, you simply follow the clear and well illustrated instruction book. Your SINCLAIR amplifier will match the finest in the world and you can add to it and increase the power at anytime. Send now, your money will be refunded (within 7 days) if you are not delighted.

£24.95

PLUS 25p P&P

BRITAIN'S SMALLEST RADIO
GREAT FOR THE KIDS



This must be the gift idea of the year. The SINCLAIR MICRO-MATIC is smaller than a box of matches yet it gives reception as good as a radio so you have the fun of building it yourself. Comes complete with earphone and instructions.

£2.25


PLUS 20p P&P

INCLUDES POSTAL INSURANCE

SENDS SUPPLY CO
10 COUNTY ROAD,
LIVERPOOL 4

(NO PERSONAL CALLERS PLEASE)

BUILD YOUR CIRCUITS on VEROBOARD

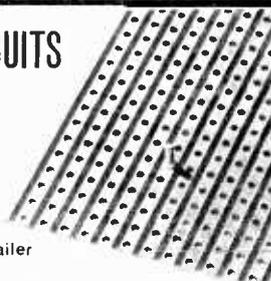

—the Universal Wiring Board—
obtainable from your local Retailer

Trade enquiries to:
NORMAN ROSE (ELECTRICAL) LTD.
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to
VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford, Hants

Receivers and Components

IDEAL GIFT

))) TONE TESTER

Is a neatly designed solid state continuity tester in a small black aluminium case. Its bleep can be heard from at least 50ft. Ideal for tracing cable faults etc. It will work into 80,000Ω loop.

USED BY

- HI-FI ENTHUSIASTS
- DO-IT-YOURSELF MEN
- TELEPHONE ENGINEERS
- ELECTRICIANS
- TESTERS
- MOTORISTS

How many times have you found yourself in a situation unable to check a simple thing like a fuse for example.

PRICE £2.75 including postage and battery. Send P.O. or // cheque.

HIGHAMS ELECTRONIC COMMUNICATIONS LTD., Dept. PW1, 58-60 Redchurch Street, London E.2.

WITWORTH TRANSFORMERS

TV LINE OUT-PUT TRANSFORMERS

Manufacturers of the largest range in the country. All makes supplied.

Free catalogue

Modern **BAIRD, BUSH, GEC, PHILIPS** Replacement types ex-stock.

For "By-return" service, contact:

London: 01-948 3702

Tidman Mail Order Ltd., Dept. PW, 236 Sandycroft Rd., Richmond, Surrey

Valves, Tubes, Condensers, Resistors, Rectifiers and Frame out-put Transformers also stocked. (182)

CALLERS WELCOME

Assorted Miniature and Subminiature Electrolytic Capacitors. Good selection, no rubbish. 50 for 60p. P.P. 10p.

Assorted Wire-Wound Resistors 1-10 Watts (2 x 25 different values). 50 for 60p. P.P. 10p.

Japanese Tape Recorder Motors. Operates from 9 volt battery. 25p. Post 5p.

Slide Switches D.P.D.T. Exceptionally good quality. 10p. Post 3p.

B.S.R. 1" Tape Heads for Record/Replay. Limited quantity only. 60p. P.P. 5p.

Plessey 50K + 50K Ganged Linear Potentiometers. 25p. P.P. 5p.

Plessey Vibrators Type 1214 12 Volt 4 Pin. 75p. Post Paid.

Mail Order Only

XEROZA RADIO

1 EAST STREET,
BISHOP'S TAWTON, DEVON

B.T.H. PHOTOCCELL AMPLIFIER UNITS

A lens system focusing on to small lens-end photo cell. 3 transistor amplifier, 2 relays with H/D contacts—size 3½ in. x 6½ in. x 5½ in. high, ex-new equipment with circuit. 50p+25p carr.

B & R transistor operated relay—2S702 transistor mounted in relay base, with H/D contacts—20V d.c.—up to 100KΩ between 2 pins will operate relay—ideal rain alarm/liquid level alarm. With circuit 35p+15p carr.

H/D Condensers—135,000MF 5 volt—50p+20p carr.
12,800MF 75 volt—50p+20p carr.
12,800MF 75 volt—50p+20p carr.
500MF 100 volt—10p+15p carr.
15MF 275 volt a.c.—50p+25p carr.

ELEY ELECTRONICS
112 Groby Road, Glenfield, Leicester LE3 8GL

Receivers and Components

VHF AIRCRAFT, Public Service band radios. FLIGHT 4: Medium Wave, FM 88-108, Aircraft 108-140, Public Service 140-175. AFC. 9in. x 7in. x 4in., £16. WALTHAM. MW/LW/SW/FM/VHF 108-175. Battery/mains. AFC 11in x 9in x 4in., £33. Full lists s.a.e. Money-back guarantee. Langtons Radio, High Street, ROCESTER, Staffordshire. Tel. 388.

Ladders

LADDERS, timber, 20ft. £7, 29ft. £10.25. Carr. 80p. Brochure. Order C.O.D. Phone 02-993 5222 (Dept WLS) Home Sales, Baldwin Road, Stourport, Worcs. Callers welcome.

NEW VALVES!

Guaranteed and Tested
24-HOUR SERVICE

1R5	25	DCC90	80	EF86	28	PCL85	37
185	21	DF91	14	EF89	24	PCL86	37
1T4	14	DF96	35	EF91	12	PFL200	51
384	24	DK91	25	EF183	26	PL36	47
3V4	37	DK92	35	EF184	28	PL81	43
5Y3GT	25	DK96	35	EL33	54	PL82	39
6J30L2	58	DL92	24	EL37	72	PL83	31
6AQ5	21	DL94	37	EL84	22	PL84	29
6BW7	50	DL96	36	EY51	30	PL600	61
6FL	57	DY86	23	EY86	28	PL604	61
6F23	67	DY87	23	EZ80	20	PY81	23
6F25	51	DY802	30	EZ81	21	PY82	24
6SN7GT	25	EBC80	30	KT81	84	PY800	32
25L6GT	18	EB91	9	KT66	75	PY801	32
30C15	56	EBC33	38	N78	85	R19	29
30C17	76	EBF89	27	PC86	45	U25	63
30C18	59	ECC81	15	PC88	45	U26	55
30F5	63	ECC82	18	PC900	30	U191	57
30FL1	59	ECC83	21	PC284	22	U261	63
30FL14	67	ECP80	26	PC289	43	U329	65
30L15	56	ECP82	26	PCC189	47	U801	78
30L17	66	ECH35	27	PCF80	27	UBF89	29
30P4	56	ECH81	26	PCF86	43	UCC85	34
30P19	56	ECL80	29	PCF801	27	UCH81	30
30PL1	59	ECL82	29	PCF802	38	UCL82	31
30PL13	73	ECL86	34	PCF805	59	UF89	28
30PL14	63	EF39	36	PCL82	30	UL84	29
DAF91	21	EF80	22	PCL83	55	UY85	24
DAF96	35	EF85	26	PCL84	38	Z77	18

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD,
STOKE NEWINGTON, LONDON, N.16

INCOMPARABLE V.H.F. KIT


Johnsons CV2—unique triple-purpose (Converter, Receiver, Tuner-Feeder) kit for the Amateur enthusiast. Fantastic transistorized performance, World Wide Sales. Complete kit of top grade parts with coils covering 80-180 MHz, plus easy/build diagrams and instructions. £4 direct from makers or S.A.E. for free literature.

JOHNSONS (RADIO)


ST. MARTINS GATE
WORCESTER WRI 2DT
Est. 1943 Tel. 24864
(A division of the G-BAN Organization)

Please mention
PRACTICAL WIRELESS
when replying to advertisements

BETTER GET 'SET'

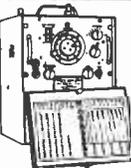

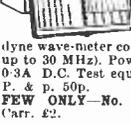BEST OFFER YET!
FAMOUS BC.221 FREQUENCY METER
125 KHz—20 MHz. Complete with valves, crystal and charts. ONLY £18.50. Carr. £1.50
Less charts & carriage £11.5. Less charts & crystal £5, carriage £1.50.



CRYSTAL CALIBRATOR
No. 10 Crystal controlled heterodyne wave-meter covering 500KHz—10 MHz (Harmonics up to 30 MHz). Power required 300V. D.C. 15mA. 12V. 0-3A D.C. Test equipment for 62TM/RC. ONLY £4.25. P. & p. 50p.
FEW ONLY—No. 62 TM/RC 1.5—10 MHz £17.50. Carr. £2.



R.209 MK II COMMUNICATION RECEIVERS 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW. BFO. 12V DC. Internal Power Supply. As New. Tested. £18.50. Carr. £1.50.

MARCONI 801A SIGNAL GENERATOR
10—310 MHz. In original transit case. £45. Carr. £2.50.

AERIAL MAST EQUIPMENT

20' TELESCOPIC MASTS £3.75. Carr. £1.
3' 2" Extension Sections to fit bottom of above mast to increase height. £1.25 each (any number supplied).
3A' MAST (7-5' 2" interlocking sections) with base plate and 12 nylon guys with semi-automatic tensioner. £22.50 Carr. £2.50.
70' MAST. Ditto. 16 guys, block and tackle. £45. Carr. £2.75.

AERIAL RACKS 3ft. Screw-in 1" dia. sections. Brand New, green finish. Suitable for many other uses. 10 for £2. Carr. 50p. 25 for £5. Carr. Paid.

R.F. ANTENNA TUNER (A.T.U.)
Cylinder design 10" x 4". Precision calibrated scale. Suitable for tuning most aerials for increased signal strength. A must for serious operators for RC or TM. Full instructions. ONLY £1.75. P. & p. 25p.

R.F. ANTENNA TUNER (A.T.U.) OPEN TYPE Mounted on ceramic former and feet. "Roller Coaster" design 16 G silver or silver plated wheel travelling on wire on ceramic former. Will handle considerable R.F. In original packing. As used with No. 53 Transmitter. ONLY £2.50. P. & p. 30p.

No. 19 SET TRANSMITTER RECEIVER Rebuilt. Complete station with PSU, Cables, Mic, Aerial, etc. £22.50. Carr. £3.

No. 19 SET 500uA METERS Scaled 0-800 and 0-15V. Brand new, boxed £1.25 Post Paid. (Quantity prices on request.)

R.F. AMPLIFIER. To increase output of No. 19 Set. ONLY £3.75. Carr. £1.25. Instruction Book for RF Amp. 871p Post Paid.

ALL No. 19 SPARES IN STOCK
Complete instruction book with circuits for No. 19 Equipment. 871p Post Paid.

HEAVY DUTY BATTERIES
New in metal cases with carrying handles.
6V. 100/125AH. 15" x 11" x 7" £5.25. Carr. £1.25.
6V. 170AH. 15½" x 13" x 7" £6.25. Carr. £1.25.

LIQUID PRISMATIC COMPASSES
2" diameter £7.60, p. & p. 25p

FAMOUS TELE 'F' FIELD TELEPHONES
Suitable for Farms, Building Sites etc. Communication up to 5 miles or more. Rugged construction, will last a lifetime. ONLY £6.25. P.A.R. Carr. £1.25 (Twin telephone wire for above available—ask for price.) Many other Ex-Govt. Surplus Equipment items in stock. Receivers etc. in small quantities too numerous to mention. Enquiries invited. LIST 25p Post Paid. (Refundable against purchases over £3.)

C.W.O. Carriage charges apply to Mainland only. Minimum Export Order £50.

Surplus Electronic Trading

DRIVERS END LANE, CODICOTE, HITCHIN, HERTS, SG4 8TP
Hours of business: 8-5 Mon.-Fri., 8-12 Sat.
Telephone: Codicote 242 for appointment

Discosound

Manufacturers of a comprehensive range of High Quality Equipment

**DISCOTHEQUES · PA AMPLIFIERS
MIXERS · LIGHT CONTROL UNITS
SPEAKERS ETC.**

Send for full details of the Discosound range

Discosound 122 Balls Pond Rd, London N.1 Tel: 01-254 5779



AERIAL BOOSTERS

We make four types of Aerial Boosters. L45 V.H.F., L12 V.H.F., TV, L11 V.H.F. Radio, L10 M/W & S/W. Price L45, L12 & L11 £2 95, L10 £2 45.

VALVE BARGAINS

Any 5 45p, 10 70p:
EC782, ECL80, EF80, EF85, EF183, EF184, EBF89, EB91, EY86, PCC84, PC789, PC97, PCF80, PCF86, PCL83, PCL83, PCL84, PCL85, PL38, PY83, PY82, PY80, PY801, 30L15, 30C15, 6-3012.

TRANSISTOR BARGAINS

We offer the following brand new, marked transistors for sale. Any 5 - 40p, 10 - 75p: BC113, BC115, BC117, BC171, BC135, BC153.

All the following at 15p each: BF115, BP173, BF184, AF116, BF200, BA102, BA129.

PRINTED CIRCUIT BOARD

2-8 ins by 4 ins boards complete with etching compound and instructions - 40p.

MAINS DROPPERS

Three section 33-33-33 Ohms 9p.

POST & PACKING under £1-5p Over £1-10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

VELCO ELECTRONICS

62A Bridge Street, Ramsbottom, Bury, Lancs.

SCOOP OFFER

Twin Power Supply Panels contains 2 x Texas 1810J10 silicon bridge rectifiers 100 p.i.v. at 1 amp, 1 x Mullard OAZ 225 Zener Diode, 1 x I.T.T Zener, 5 x Texas silicon diodes, 2 x Plessey 1000µF 25V, 2 x Plessey 50µF 50V, 2 x Mullard 250µF 25V, 2 x Mullard 640µF 25V electrolytic capacitors includes circuit. A very definite bargain £1 00 post 10p.
Metal Panels with 2 x McMurdo nylon 11 pin relay or nixie tube bases, 1 x 8 way edge plug & socket, 1 x 10 way edge plug & socket 2 panels for 50p post 15p.
10 Wire-wound Potentiometers 50p, post 10p
Component Parcels includes plugs, sockets, electrolytic capacitors, etc etc. Each parcel 4lb nett weight £1 00, post 30p
Transformers: Primary 10-0-100-125-200-220-240 volts. Secondary 10-0-10 volts @ 15 mA also 1 25V @ 1 amp 50p, post 15p.
S.T.C. Miniature Metal Sealed Relays 6-24-48 volts, 10 for £1-50, post 25p
Slow Rev Motors, 1 rev per 6 hrs/12 hrs etc. Write for details
Convex Lenses 2 x Plano focal length 2ins. 50p, post 6p.

ELEKON ENTERPRISES

12A TOTTENHAM STREET, LONDON, W1P 9PQ
Telephone 01-580 7391

INDEX TO ADVERTISERS

A. H. Supplies	920	Felstead Electronics	924	Padgetts Radio Store	892
Adcola Products Ltd.	878	Field Electric Ltd.	942	Partridge Electronics Ltd.	876
Antex Ltd.	867	Francis, J. J. (Wood Green) Ltd.	866	Personal Shoppers Plan Ltd.	872
Apex Aerials	947	Gladstone Radio	939	Premier Radio	880
Audio Supplies	928	Global Audio Discount Warehouse	924	Proops Bros Ltd.	910
Audioscan	946	Government Communications Headquarters	948	R-B Television	868
Autotron Co.	939	'HAC' Shortwave Products	868	Radio Components Specialists	891
Baker Reproducers Ltd.	920	Hadley, C.	949	Radio Exchange Co.	873
Baines, R.	947	Haunt & Co.	917	Radio Society of Great Britain	920
Bells' Television	947	Haverson Supplies Co. Ltd.	909	Radio & T.V. Components (Acton) Ltd.	874, 875
Bennison, R. J.	928	Helme, PH & AR, Ltd. (Peerless)	939	Readers Radio	932
Bentley Acoustics Corporation Ltd.	860	Henry's Radio Ltd.	919 cov. iv	RCS Electronics Ltd.	864, 865
Bernard, Gerald	950	Highams Electronics	960	RCS Products (Radio) Ltd.	943
B.I.E.T.	939 cov. iii	Home Radio (Components) Ltd.	915	RSC Hi-Fi Centres Ltd. cov. ii	857, 858, 859
Bi-Pak Semiconductors	940, 941	Imperial Trading	946	R.S.T.	876
Bi-Pre-Pak Ltd.	899	I.C.S.	866, 923, 948	S.D.C. (Electronics) Sales Ltd.	872, 910
Boffin Projects	946	Jackson Bros. (London) Ltd.	862	Salop Electronics	946
British National Radio School	877, 892	Jef Electronics	949	Sands Supply Ltd.	949
Broadway Electronics	910	Jermyn Industries	928	Sellers, J. R.	948
Bull, J. Electrical Ltd.	895	Johnsons (Radio) Ltd.	950	Sinclair Radionics Ltd.	935, 936, 937, 938
Bush & Meissner Ltd.	942	KVA Electronics	942	Shoptunities Ltd.	863
Carrana, C.	947	Kensington Supplies	947	Smith, G. W. & Co. (Radio) Ltd.	869, 870, 871
Circuit & Supplies	946	Keytronics	949	Stephens Electronics	927
Chromasonic Electronics	946	King, J. M.	946	Surpnetronics	910
Clear-Tone-Hi-Fi Ltd.	943	Lasky's Radio Ltd.	861	Surplus Electronic Trading	950
Codar Radio Co.	860	Lewis Radio	932	Swanley Electronics	948
College, L. E.	948	Linear Products Ltd.	892	Thacker, A. H.	942
Colomor (Electronics) Ltd.	896	London Computer Operators Training Centre	862	Thornbury Trade Disposals	948
Comet High Fidelity Discount Warehouse	944, 945	M & B Components (Leeds) Ltd.	896	Tidman Mail Order	950
Concord Electronics Ltd.	932	Marshall, A. Son	879	Velco Electronics	951
Coventry Movement Co. Ltd.	868	Morse Made Easy	947	Vero Electronics Ltd.	949
Crescent Radio Ltd.	868	Multicore Solders Ltd.	924	West London Direct Surplus	943
Coventry Movement Co. Ltd.	868	NIP Electronics	948	Wicks, D. T. & Co.	878
C.T. Electronics	920	Oakfield Enterprises	947	Wilmslow Audio	943
Dabar Electronics Products	943			York Electronics	872
Dewtron	946			Z. & I. Aero Services Ltd.	952
DEW Wokingham	946				
Discosound	951				
Duke & Co. (London) Ltd.	896				
Electrovalue	931				
Elekon Enterprises	951				

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 12½p in £ for postage and handling
MINIMUM CHARGE 15p. No C.O.D. orders accepted
Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

0A2	0.38	6A05	0.38	6EA8	0.60	6X4	0.35
0A3	0.45	6A06	0.65	6E17	0.30	6X5GT	0.40
0B2	0.35	6AR5	0.45	6E37	0.35	6X8	0.60
0B3	0.70	6AR6	0.55	6E38	0.70	6Y9	0.75
0C3	0.38	6AR11	1.25	6F1	0.60	7Y4	0.40
0D3	0.85	6AR5	0.45	6F5	0.75	9B36	0.60
1B30T	0.40	6A87G	0.85	6F6G	0.35	10C2	0.50
1L4	0.20	6AT6	0.35	6F11	0.40	10D1	0.55
1R4	0.45	6AU6	0.25	6F13	0.45	10D2	0.50
1R5	0.40	6AV9	0.80	6F14	0.70	10P1	0.75
1R4	0.30	6AW8A	0.60	6F15	0.55	10P9	0.60
1R5	0.30	6AX4GTB	0.60	6F18	0.50	10P18	0.60
1T4	0.30		0.60	6F23	0.85	10L1	0.50
1U4	0.30	6AW8A	0.60	6F24	0.75	10L1D11	0.65
1V5	0.60	6BA6	0.25	6F25	1.00	10P13	0.60
1V2	0.60	6BE9	0.30	6F26	0.35	10P14	1.10
1X2B	0.50	6B5	1.00	6F28	0.65	12AB5	0.70
2A3	0.50	6BF6	0.55	6GK6	0.60	12AC6	0.50
2C4	0.70	6BH6	0.75	6J4	0.50	12AD6	0.55
2D21	0.38	6BJ6	0.50	6J6GT	0.30	12AE6	0.55
3A4	0.40	6BK7A	0.60	6J6	0.20	12AL5	0.50
3BP1	3.00	6BN5	0.43	6J7	0.45	12AQ5	0.50
3B28	2.50	6BN6	0.45	6K6GT	0.60	12AT6	0.80
3B4	0.35	6BQ6	0.25	6K7	0.35	12AT7	0.35
3V4	0.45	6BR8	0.70	6K8G	0.40	12AU6	0.35
3H44Y	0.75	6BS7	1.30	6K25	0.75	12AU7	0.30
6U4G	0.35	6BW6	0.85	6L6GT	0.45	12AV6	0.40
6V4G	0.45	6BW7	0.80	6L7	0.40	12AV7	0.85
6Y3GT	0.40	6BZ6	0.25	6L18	0.45	12AX7	0.80
6Z3	0.60	6BZ6	0.60	6L20	0.60	12AY7	0.75
6Z4G	0.40	6C4	0.33	6NTGT	0.45	12BA4	0.60
6J30L2	0.80	6C5GT	0.40	6P1	0.60	12BA6	0.40
6AB4	0.35	6CB6	0.35	6P28	0.65	12BA7	0.40
6AF4A	0.55	6CD6GAL	2.25	6Q7	0.40	12BE6	0.40
6AG5	0.25	6CG7	0.55	6R4	0.40	12BH7	0.45
6AG7	0.40	6CH6	0.80	6R7	0.45	12BY7	0.60
6AH6	0.50	6CL6	0.55	6RK4	0.50	12K75	0.70
6AJ8	0.30	6CW4	0.65	6RL7GT	0.35	12K7GT	0.40
6AK6	0.35	6CY5	0.45	6RN7GT	0.35	12Q7GT	0.40
6AK6	0.60	6CY7	0.70	6RQ7	0.40	19AR7	0.40
6AL3	0.43	6D3	0.50	6SR7	0.40	20D1	0.60
6AL5	0.20	6DC5	0.25	6T5	0.35	20L1	1.10
6AM5	0.35	6D6B	0.70	6T8A	0.40	20P4	1.10
6AM6	0.38	6D84	0.75	6V6GT	0.40	20P5	1.20

First Quality Fully Guaranteed



ELECTRONIC VALVES

25C5	0.50	50A5	0.75	DK40	0.60	ECC85	0.40
25L6GT	0.50	50B5	0.50	DK92	0.55	ECC89	0.40
25Z4G	0.30	50C5	0.50	DL96	0.45	ECC99	0.50
25Z6GT	0.65	50C6DG	1.20	DM180	0.65	ECC91	0.20
30A5	0.50	50L6GT	0.55	DT86	0.32	ECC189	0.65
30AE3	0.40	85A2	0.50	DT97	0.33	ECC90	0.35
30C1	0.30	90A	2.40	DY802	0.35	ECCF2	0.35
30C15	0.80	90AG	2.50	E88C	0.65	EEL22	1.30
30C17	0.90	90C1	0.45	E180F	1.00	ECF80A1	0.55
30C18	0.80	90CV	2.40	E101F	2.90	ECH42	0.75
30F5	0.65	90T	3.75	EAF42	0.55	ECH83	0.45
30FL1	0.75	813	3.75	EBC33	0.60	ECH84	0.45
30FL12	1.20	866A	0.75	EBC33	0.60	ECL80	0.45
30FL14	0.85	942	1.70	EBC41	0.55	ECL81	0.50
30FL15	0.50	0680	1.60	EBC81	0.30	ECL81	0.50
30FL15	0.85	6146	1.60	EBF80	0.40	ECL82	0.35
30FL17	0.80	6360	1.25	EBF83	0.40	ECL83	0.45
30P12	0.80	9039	2.25	EBF89	0.30	ECL84	0.55
30P19	0.85	7199	0.80	EC53	0.60	ECL85	0.55
30PL1	0.75	7360	2.00	EC68	0.60	ECL86	0.40
30PL13	0.93	7586	1.25	EC88	0.60	EF40	0.50
30PL14	0.80	7895	1.25	EC90	0.33	EF41	0.55
35A3	0.55	9022	0.40	EC91	0.60	EF42	0.70
35A5	0.75	9003	0.40	EC92	0.35	EF80	0.25
35B5	0.65	AZ1	0.55	EC93	0.55	EF83	0.55
35C5	0.50	AZ31	0.55	EC8010	2.25	EF85	0.35
35D5	0.75	CB11	0.90	EC35	1.00	EF86	0.30
35L6GT	0.50	CB13L	0.50	EC40	0.65	EF89	0.38
35W4	0.35	CY31	0.35	EC81	0.35	EP91	0.33
35Z4	0.35	DF96	0.45	EC92	0.30	EP92	0.35
35Z4G	0.35	DF96	0.45	EC93	0.30	EP92	0.35
35Z6GT	0.60	DK96	0.60	EC84	0.30	EP95	0.35

EP97	0.65	GZ33	0.70	PL36	0.55	U281	0.40
EP98	0.65	GZ34	0.60	PL81	0.50	U282	0.40
EP183	0.30	HAB8C00.45		PL82	0.45	U301	0.40
EP184	0.35	HK90	0.40	PL83	0.45	U403	0.60
EP800	1.00	KT66	2.05	PL84	0.40	U404	0.60
EK30	0.80	KT98	2.00	PL302	0.85	U601	0.80
EL33	1.25	N78	1.50	PL50	0.30	UABC89	
EL34	0.50	PABC80.40		PL608	0.90		
EL36	0.50	PC86	0.60	PL509	1.10	UAF41	0.50
EL37	1.60	PC88	0.90	PL801	0.80	UAF42	0.55
EL41	0.60	PC97	0.50	PL802	0.95	UB41	0.60
EL42	0.65	PC90	0.48	PM84	0.80	UBC41	0.50
EL51	0.55	PABC80.40		PY31	0.20	UBC81	0.40
EL83	0.42	PC84	0.40	PY33	0.85	UBF80	0.40
EL84	0.25	PC85	0.40	PY80	0.40	UBF89	0.35
EL85	0.43	PC88	0.55	PY81	0.30	UBL1	0.60
EL86	0.40	PC89	0.55	PY82	0.35	UBL21	0.65
EL90	0.38	PC189	0.65	PY83	0.38	UC92	0.40
EL95	0.35	PC305	0.85	PY88	0.40	UC95	0.40
EL821	0.60	PC806	0.80	PY89	1.00	UC98	0.55
EL822	1.30	PCF80	0.40	PY800	0.40	UCH21	0.60
EL823	0.35	*CF82	0.35	PY801	0.50	UCH42	0.70
EL824	0.75	*CF84	0.60	PZ30	0.35	UCH81	0.40
EM34	1.00	PCF84	0.60	QQV02-6		UCL1	0.60
EM71	0.80	PCF86	0.60	QQV03-10	2.25	UCL82	0.35
EM80	0.45	PCF87	0.90	QQV03-15	3.00	UC138	0.50
EM81	0.50	PCF801	0.50	QQV03-15	1.25	UF9	0.60
EM84	0.35	PCF802	0.50	QQV03-20A	1.25	UF11	0.60
EM85	1.00	PCF805	0.70	QQV06-40A	5.25	UF41	0.60
EM87	0.70	PCF806	0.75	UF42	0.60	UF43	0.60
EN91	0.38	PCF808	0.85	UF43	0.60	UF80	0.40
EY51	0.40	PCL2000.70		TT21	2.50	UF82	0.40
EY80	0.55	PCL81	0.50	TT22	3.60	UF85	0.40
EY81	0.40	PCL82	0.85	TT2-125		UF89	0.40
EY83	0.55	PCL83	0.65	UL41	0.65		
EY86	0.40	PCL84	0.45	U18-20	7.75	UL84	0.40
EY87	0.43	PCL85	0.40	U25	0.80	UM84	0.25
EY88	0.43	PCL86	0.45	U26	0.80	UY18	0.50
EY89	0.55	EZ40	0.60	PCL801	0.93	UY11	1.00
EZ41	0.50	PCL801	0.75	U37	2.10	UY41	0.48
EZ80	0.27	PD500	1.30	U52	0.35	UY82	0.50
EZ81	0.29	PF86	0.65	U76	0.35	UY85	0.40
GY501	0.80	PF86	0.65	U78	0.35	W729	0.75
GZ30	0.40	PF818	0.55	U79	0.35	Z739	0.00
GZ31	0.35	PF200	0.65	U91	0.75	Z803U	1.20
GZ32	0.48	PL33	0.35	U201	0.35		

TRANSISTORS

2N696	0.17	AC127	0.20	BD123	0.80
2N697	0.17	AC128	0.15	BD131	0.85
2N698	0.30	AC132	0.35	BD132	0.85
2N705	0.70	AC130	0.20	BF116	0.20
2N706	0.15	AC154	0.15	BF119	0.18
2N708	0.15	AC157	0.20	BF173	0.20
2N753	0.25	AC169	0.10	BF179	0.30
2N929	0.22	AC176	0.25	BF180	0.35
2N930	0.25	AC187	0.30	BF181	0.25
2N947	0.30	AC188	0.30	BF184	0.25
2N1131	0.25	ACV17	0.275	BF185	0.25
2N1132	0.25	ACV18	0.20	BF184	0.15
2N1184	1.25	ACV19	0.25	BF195	0.15
2N1301	0.40	ACV20	0.20	BF196	0.20
2N1802	0.75	ACV21	0.20	BF197	0.20
2N1804	0.25	ACV22	0.15	BF200	0.35
2N1905	0.25	AD140	0.20	BFW87	0.20
2N1906	0.25	AD149	0.50	BFW88	0.25
2N1907	0.30	AD161	0.35	BFW89	0.20
2N1908	0.25	AD162	0.35	BFW91	0.20
2N1909	0.30	ADZ11	1.25	BFX88	0.25
2N1913	0.22	ADZ12	1.25	BFY17	0.40
2N1911	0.25	BF119	0.20	BFY19	0.50
2N1916	0.75	BF115	0.20	BFY50	0.25
2N2147	0.75	BF116	0.20	BFY51	0.20
2N2160	0.65	AF117	0.20	BFY52	0.25
2N2217	0.30	AF118	0.45	BSY26	0.20
2N2218	0.30	AF119	0.25	BSY27	0.20
2N2219	0.35	AF120	0.20	BSY28	0.20
2N2369A	0.20	AF180	0.35	BSY65	0.20
2N2477	0.65	AF181	0.35	BSY95A	0.15
2N2646	0.65	AF186	0.40	OC16	0.50
2N2905	0.35	AF239	0.40	OC22	0.50
2N2923	0.15	AFZ11	0.45	OC23	0.60
2N2924	0.15	AFZ26	0.25	OC24	0.60
2N2926	0.125	ASY27	0.30	OC25	0.35
2N3053	0.25	ASY28	0.25	OC26	0.25
2N3054	0.60	ASY29	0.30	OC28	0.80
2N3055	0.75	ASY84	0.25	OC29	0.60
2N3133	0.30	ASZ15	0.70	OC30	0.75
2N3134	0.30	ASZ16	0.65	OC35	0.60
2N3391	0.20	ASZ17	0.75	OC36	0.60
2N3392	0.15	ASZ18	0.75	OC42	0.20
2N3393	0.15				

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn.

If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. - Civ.
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating
Architecture
Builders' Quantities

General

C.E.L.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:

English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT— SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B2, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



POST THIS COUPON TODAY

To: B.I.E.T., Dept B2, Aldermaston Court, Reading RG7 4PF.
Please send me book and details of your Courses in

Name.....
BLOCK CAPITALS PLEASE
Address.....

OCCUPATION..... AGE.....

Accredited by the Council for the Accreditation of Correspondence Colleges.

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE


HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES



HI-FI · ELECTRONIC COMPONENTS · TEST PA · DISCOTHEQUE · LIGHTING · MAIL ORDER

10th EDITION CATALOGUE

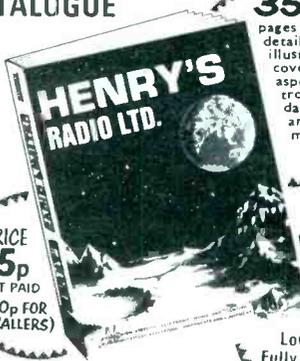

350 pages fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information

PRICE **55p** POST PAID (40p FOR CALLERS)

10,000 Stock lines at Special Low Prices and Fully Guaranteed

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES

Send to this address—Henry's Radio Ltd., (Dept. PW), 3 Albemarle Way, London, E.C.1.—for catalogue by post only.

All other mail and callers to "303"; see below
A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!

HOME EQUIPMENT

- AF105 50k/v multimeter (illus.). Price £8.50, p.p. 20p. Leather case £1.42.
- 200H 20k/v. Price £3.87, p.p. 20p. Case 62p.
- 500 30k/v multimeter. Price £8.87, p.p. 20p. Leather case £1.50.
- THL33 2k/v. Price £4.12, p.p. 15p. Leather case £1.15.
- TE65 Valve voltmeter. Price £17.50, p.p. 40p.
- SE250B Pocket pencil signal injector. Price £1.75, p.p. 15p.
- SE500 Pocket pencil signal tracer. Price £1.50, p.p. 15p.
- TE20D RF generator. Price £15, p.p. 40p.
- TE22D Matching audio generator. Price £17, p.p. 40p.
- TE15 Grid dip meter. Price £12.50, p.p. 40p.
- TO3 Scope 3 in. tube. Price £37.50, p.p. 50p.
- TE22 Audio Generator. Price £17, p.p. 40p.
- CI-5 Pulse Scope. £39.00, p.p. 50p.
- U4341 AC/DC Multitester and transistor tester. AC & DC Current. In steel case. Price £10.50, p.p. 15p.
- TMK 500 30k/v Multitester. Price £8.87, p.p. 13p. Leather case £1.98.
- LARGEST RANGE of Panel Meters, Edge Meters and Test Equipment of every sort. Full details in latest catalogue—see above.

LOW COST HI-FI SPEAKERS

- E.M.I. Size 13 3/4" x 8 1/4". Large Ceramic Magnet. TYPE 150 6 watt, 3, 8 or 15 ohms £2.12. Post 22p.
- TYPE 150TC Twin cone version £2.75. Post 22p.
- TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3.50. Post 25p.
- TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7.50. Post 28p.

POLISHED CABINETS For 150, 150TC and 450 £4.50. Post 30p.

SPEAKER KITS

- WHARFEDALE 4-8 ohms. PEERLESS 8 ohm Systems.
- Unit 3. 8" 15W £10.50. 20-2 8" 30W £11.25.
- Unit 4. 12" 25W £14.25. 20-3 8" 40W £16.75.
- Unit 5. 12" 35W. £20.25. 4-30/12 12" 40W £22.75.
- GOODMANS DIN 20 KIT 20W 4ohm £11.75
- Carriage etc. 50p each or 75p per pair for Kits.

- ### STEREO HEADPHONES
- With stereo jack. Post 15p
 - Dulic SH650D £2.25
 - Rotel RH600 £4.67
 - Akai ASE9S £5.50
 - Eagle SE30 £5.97
 - Koss K711 £7.97
 - Pioneer SE30 £9.45
 - Koss PRO4A £15.50

HI-FI TO SUIT EVERY POCKET



SAVE UP TO 40% ON LIST UP TO 40% ON LIST PLUS FREE "BIB" Groove-Clean Record Cleaner Value £1.99

- ROTA 1500. 5 + 5 watts. Garrard 2025TC with 9TAHC diamond ceramic. Plinth/Cover. SDLI Compact Speakers. Size 15 x 10 1/2 x 7"
- SAVE £47.75 Carr. £2

TELETON '206'. Garrard SP25 Mk. 111, Goldring G800 Series Cart., Plinth/Cover. New 15 watt Quality SDLI Bookshelf Speaker Systems, all leads etc.

- SAVE £54.95 Carr. £2
- £30.00

TELETON F2000, Med. Wave, Stereo FM Tuner Amplifier, Garrard 2025TC, 9TAHC Diam., Plinth/Cover. New 15 watt Speaker Systems as above, all leads, etc.

- SAVE £59.95 Carr. £2
- £36

or with 2 x SA125 Speakers £48.95 Carr. £2

ROTA 2200 10 + 10 Watt. Garrard SP25 III/G800H. Plinth/Cover. New 15 watt SDLI Twin Speaker Systems, all leads, etc.

- SAVE £62.50 Carr. £2
- £32

LOW PRICES PLUS 12 MONTHS GUARANTEE & DEMONSTRATIONS FREE

LATEST SPECIAL PRICE STOCK LIST & STEREO SYSTEMS Ref. 16/17

FREE BROCHURES

- * P.A. DISCO and LIGHTING No. 18
- * TRANSISTORS, I.C.'s No. 36

20 WATT I.C. AMPLIFIER

Toshiba 20 watt Power Amplifier. £4.57

Toshiba Pre-Amplifier I.C., £1.50.

Data and suggested circuits No. 42, 10p.

SL403D 3 watt I.C. with 8 page data and circuits. £1.50

IC12 6 watt I.C. £2.50.

TEXAS PRE-AMPLIFIERS & I-100W AMPLIFIERS

Circuits, layouts and data £1.25 post paid.

NIXIE TUBES (post 15p per order)

XN3 or XN13 0-9 side view with data sheet. 85p each.

GN4 end view 0-9 with socket and data. £1.75. All I.C.'s for Digital Clocks in stock. HENRY'S CLOCK CIRCUIT No. 29/2 15p.

BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300 kc/s BAND-WIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION, MONO AND STEREO.

A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.

TOTAL £6.97, p.p. 20p. Cabinet 100p. Decoder Kit £5.97.

Tuning meter £1.75

Mains unit (optional) Model PS900 £2.47.

Mains unit for Tuner and Decoder PS1200 £2.62.



HIGH QUALITY SILICON AMPLIFIERS AND PRE-AMPLIFIERS

Self powered Silicon—FET Pre Amplifiers. Push button selectors, tape record/play, adjustable levels, drive up to 4 x PA25 or 2 x PA50 per channel.

FET 9/4 Mono or single channel. All facilities plus microphone. Missing Price £12.50

FET 5/4 Stereo with all facilities, magnetic cart. input etc Price £16.50.

SILICON POWER AMPLIFIERS RMS OUTPUT

- PA 25 25 watts into 8 ohms £7.50.
- PA 50 50 watts into 4 ohms £9.50.
- MU442 Power Supply for 1 or 2 PA25's or 1 only PA50, £6.00. Post 20p.

FREE BROCHURE No. 25 ON REQUEST. NO SOLDERING—ALL UNITS INTERCONNECTING. ON DEMONSTRATION AT "356".

TERRIFIC SAVINGS!

GARRARD - BSR - THORENS GOLDRING PIONEER CONNOISSEUR

CHASSIS (P)	ASSEMBLED (P)	ASSEMBLED (with cart. P & C)
*SP25 Mk III £11.30	MP60(TDIP) £17.75	2025TC/9TAHCD £13.95
†AP76 £19.97	HT70 PC £24.00	£13.95
●MP60 £11.30	PL12AC £36.50	SP25/3-G800H £18.95
●MP610 £15.15	GL72 PC £36.95	AP76-G800 £29.95
●HT70 £16.60	GL75 PC £43.75	
GL72 £22.95	TD150AB £45.50	
GL75 £28.97	TXII £32.25	
Dual 1215 £39.00	BD2 £32.25	

CHASSIS WITH CARTRIDGE

- *2025TC/9TAHCD £9.50
- *3000/9TAHCD £9.98
- TEAK *PI/TI Std. £3.00
- PLINTH *BN1 Deluxe £8.00
- WITH †P4/T4 Std. £4.25
- COVER †BN4 Deluxe £8.00
- (State *P6/T6 Std. £3.00)
- deck ●BSR Deluxe £6.25

Post etc.—Chassis 50p, with plinth/cover 70p, Plinth/Cover 30p Carts. 15p.

(P) SPECIAL PRICE WITH CARTRIDGE—ADD

- All magnetic—Recommended Y940 (=AD-76K) £3.25; AT66 £4.95; G850 £4.25; AT21 £9.60; G800 or G800H £6.55; M44.7 or C £7.45; 909X £7.32

300mW TRANSISTOR AMPLIFIER MODEL 4-300

Fully assembled ATR Amplifier. Size 5 1/2 x 1 1/2 x 1 in. 1-10mV adjustable sensitivity. Output 3-8 ohms. Fitted Vol. control. 9 volt operated. Thousands of uses plus low cost.

Price £1.75, p.p. 15p (or 2 for £3.25, p.p. 15p).

SINCLAIR PROJECT 60 PACKAGE DEALS—SAVE POUNDS!

2 x Z30 amplifier, stereo 60 pre-amp. PZ5 power supply, £16.75, Carr. 40p. Or with PZ6 power supply £18.25. Carr. 40p.

2 x Z50 amplifier, stereo 60 pre-amp. PZ8 power supply £20.25, Carr. 40p.

Transformer for PZ8 £2.45 extra. NEW1 Project '60S' stereo system £20.97. Any of the above with Active Filter unit add £4.75 or with pair Q16 speakers add £16. Also new FM Tuner £20.25, 2000 Amplifier £23.75, p.p. 50p. 3000 Amplifier £31.50. Also IC12 £2.50.

"BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance.

TOTAL COST TO BUILD £7.98, p.p. 32p (Battery 22p). All parts sold separately—Leaflet No. 2.

7T PORTABLE (as previously advertised) £6.98, p.p. 35p from stock—Leaflet No. 1.

MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

Electronic Components, Audio and Test Gear Centre
 356 EDGWARE ROAD, LONDON, W.2
 Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre
 354 EDGWARE ROAD, LONDON, W.2.
 Tel: 01-402 5854

P.A., Disco & Lighting Centre
 309 EDGWARE ROAD, LONDON, W.2.
 Tel: 01-723 6963

Mail Orders, Special Bargain Shop, Industrial Sales
 303 EDGWARE ROAD, LONDON, W.2.
 Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY