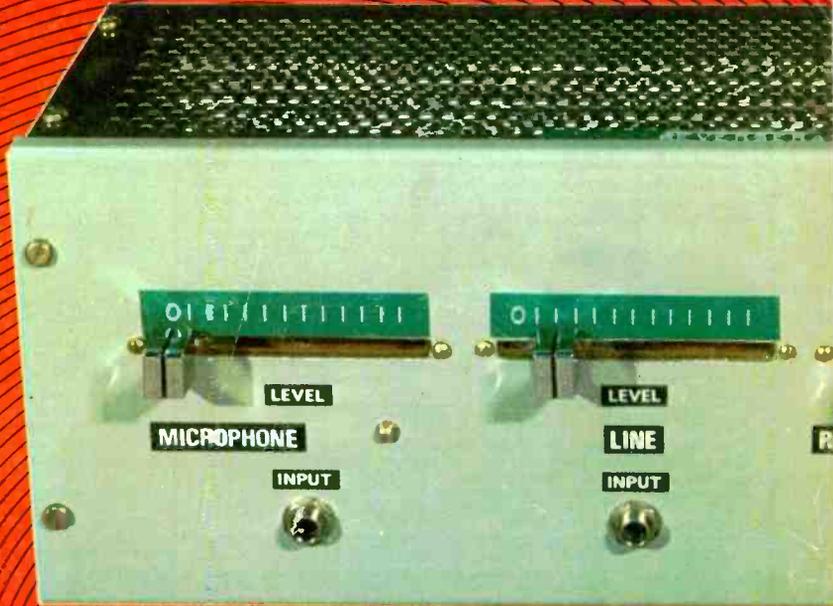


# PRACTICAL WIRELESS


NOVEMBER  
1972

20p

**EXTRA**  
**THE abc**  
**OF hi-fi**  
**SUPPLEMENT**



## PW Reverberation unit

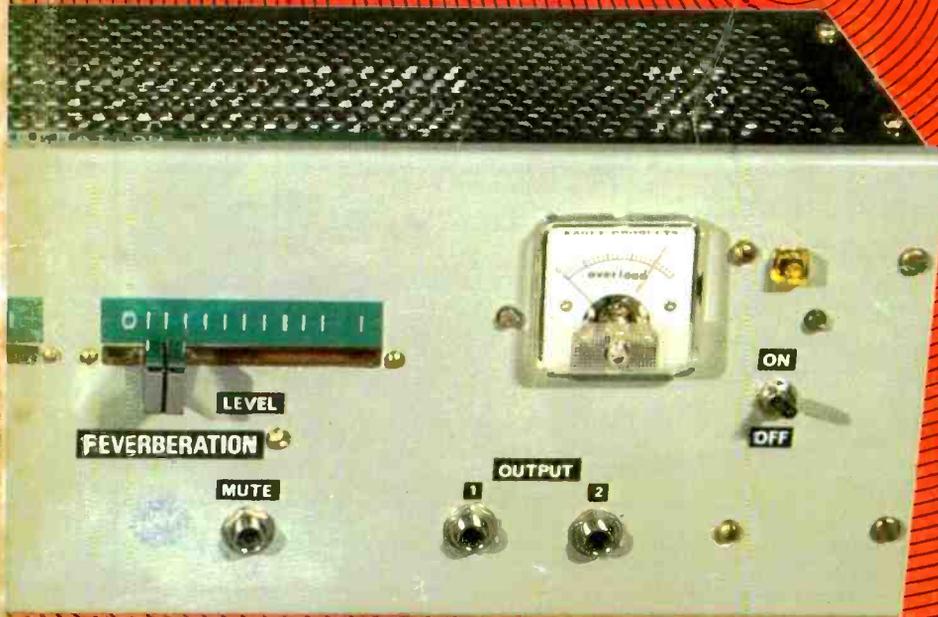

**Also:**  
8 WATT SILICON  
AUDIO AMPLIFIER  
SIMPLE RF  
SIGNAL GENERATOR

## RSC HIGH-FIDELITY STEREO PACKAGE OFFERS

- ★ SUPER 30 AMPLIFIER (15+15 watt) in veneered housing
- ★ GARRARD SP25 MK III Turntable on Plinth with cover
- ★ GOLDRING G850 Magnetic cartridge with diamond stylus
- ★ PAIR OF STANWAY II Speaker Units Special Total Price

**£87.95**

Terms: Deposit £12.77 and 9 monthly payments £9.39 (Total £97.28).

- ★ Super 30 Amplifier (15+15 watt) in veneered housing
- ★ Goldring GL69 II Transcription Turntable on Plinth
- ★ Goldring Magnetic P.U. Cartridge
- ★ Pair of Stanway II speaker units

**£98.63**

Terms: Deposit £13.63 and 9 monthly payments £10.82 (Total £109.21).



ATTRACTIVE TEAK OR AFRORMOLIA VENEERED CABINETS AND PLINTHS

Four fully wired units ready to 'plug in'.

- ★ TA12 AMPLIFIER 6.5+6.5 watt in veneered housing
- ★ GARRARD SP25 MK III Player unit on Plinth
- ★ SONOTONE 9TAHC Ceramic Cartridge (diamond stylus)
- ★ PAIR OF DORCHESTER Loudspeaker Units

**£59**

Or Deposit £8.40 and 9 mthly. payments of £2.32 (Total £85.28).

Trans. Plastic Cover £3.15 extra. Carr. £1.25.

PACKAGE AS ABOVE but with Garrard 8000 Antochanger and Sonotone 9TA Ceramic Cartridge in lieu of SP25. Carr. £1.25. **£51.75**

Or Deposit £7.50 and 9 monthly payments £5.64 (Total £58.26). Trans. Plastic Cover £3.15 extra.

★ Send S.A.E. for coloured brochure showing other money-saving offers.

## 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in. approx.
- ★ Response 30-20,000 c.p.s. Impedance 15 ohms
- ★ Performance comparable with units costing considerably more.

**COMPLETE KIT £23**

Carr. 65p

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 3 x 1/2 high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4.60 and 9 monthly payments £2.47 (Total £26.88).

DEMONSTRATIONS AT ALL BRANCHES

## HIGH FIDELITY LOUDSPEAKER UNITS

Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.

DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. **£9.45**

Carr. 40p.

DUAL CONE speaker. Imp. 3 or 15 ohms. MONARCH Size 19 x 10 x 9in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible P.V.C. cone surround, long throw voice coil and 10,000 line magnet. High flux pressure tweeter. Handsome cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. See 'package offers' for illustration Carr. 50p **£19.35**

## RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal facia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions **£11.50** Carr. 40p

OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £14.99 or dep. £2.20 and 9 monthly payments £1.70 (Total £17.50).

## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER **£6.95** Carr. 30p



## AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.

Exceptional performance at low cost.					
HF808T	8" 10W	£2.88	HF120D	12" 15W	£4.99
HF102D	10" 10W	£3.40	HF126	12" 15W	£5.75
HF120	12" 15W	£4.50	HF126D	12" 15W	£8.25

## FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ohms. **£3.85**



## R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2 1/2 in.		TOP SHROUDED DROP-THRO' TYPE	
250v., 60mA, 6.3v. 2a.	99p	250-0-250v. 70mA, 6.3v. 2a.	0-5-6.3v. 2a. £1.35
250-0-250v., 60mA 6.3v. 2a.	£1.05	250-0-250v. 100mA, 6.3v. 3.5a.	£1.55
FULLY SHROUDED UPRIGHT MOUNTING		250-0-250v. 100mA, 6.3v. 2a., 0-5-6.3v. 1a.	£1.80
250-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a.	£1.40	350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a.	£1.65
250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.20	250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.20
300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.20	300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.20
300-0-300v. 130mA, 6.3v. 4a. c.t., 6.3v. 1a.	£2.65	300-0-300v. 150mA, 6.3v. 4a., c.t. 6.3v. 1a.	£2.65
For Mullard 510 Amplifier.		Suitable for Mullard 510 Amplifier.	£2.60
350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.20	350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.20
350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.65	350-0-350v. 160mA, 6.3v. 4a., 0-5-6.3v. 3a.	£2.60
425-0-425v. 200mA, 6.3v. 4a., c.t., 5v. 3a.	£4.95	FILAMENT or TRANSFORMER POWER PACK	
425-0-425v. 200mA, 6.3v. 4a., 6.3v. 3a., 5v.	£5.10	Types B-3v. 1.5a. 49p; B-6v. 2a. 54p; B-6v. 3v. 3a. 79p;	
450-0-450v. 200mA, 6.3v. 4a., c.t., 5v. 3a.	£5.50	B-3v. 3a. 28p; B-6v. 1.5v. 1a. 55p; 12v. 3a. or 24v.	
		1.5a. 21.35p; 0-15v. 1 1/2a. £1.10; 0.12-25-42v. 2a. £1.78.	

## R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'Hi' and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.75** Carr. 40p.

## R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'Hi' and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.75** Carr. 40p.

## R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'Hi' and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish facia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.75** Carr. 40p.

## R.S.C. Mk III SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

A completely new design further improved in both appearance and performance. Representing value far higher than the prices suggest.

Only high grade components by leading manufacturers.

COMPLETE KIT OF PARTS

OR FACTORY BUILT with 12 months guarantee. Dep. £5.75 and 9 monthly payments £3.50 (Total £37.25).

OR FACTORY BUILT in cabinet as illustrated. Dep. £7 and 9 monthly payments £3.99 (Total £42.91)

TECHNICAL DETAILS (Applying to each channel where appropriate) CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape

(4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble and Balance. Plus Ceramic Mag P.U. Switch.

**£25** Carr. 65p

**£33.75**

**£38.75**


Printed Circuitry  
Twenty Silicon Transistors, Four Diodes,  
Four Rectifiers




FREQ. RESPONSE: -3dB 7Hz to 70kHz. TREBLE CONTROL: +16dB to -12dB at 14kHz. SENSITIVITIES: Disc Mag. 2.5 mV. Ceramic 35mV. Radio 120mV. REAR PANEL SELECTOR FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections. Visually matches Super 30 MkII Only **£44.95**

# RSC GROUP/DISCO UNITS


50 WATT  
SPEAKER

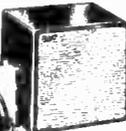

100 WATT  
AMPLIFIER

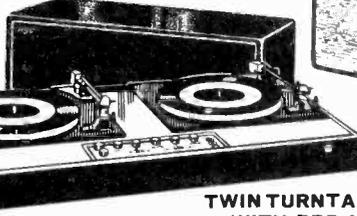

50 WATT  
SPEAKER

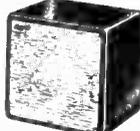

HEADPHONES  
MICROPHONE

TWIN TURNTABLE  
WITH PRE-AMP.

## PACKAGE OFFER

- Units listed below
- (a) 100w POWER AMPLIFIER
  - (b) PAIR OF HI-FI HEAD-  
PHONES
  - (c) MATCHING DYNAMIC  
'MIKE' (attached to  
headphones)
  - (d) PAIR 50 WATT SPEAKERS  
Black Rexine covered  
Cabinets
- Size approx.  
18" x 18" x 8" **£72-85**  
(a)(b)(c)&(d)

Terms on Amps. Speakers and Head-  
phone/Mike. Deposit £15 and 18  
monthly payments of £4-00 (Total  
£87-00).



TDI DISCO  
CONSOLE

Incorporating twin Garrard SP25  
Mk.III turntables and Sonotone or  
Acos Cartridges with diamond styl.  
Separate Vol. controls for each  
turntable. Also MONITORING  
FACILITIES, plus Treble and Bass  
Controls. Separate input for 'mike'  
with vol. control switch. Black  
Rexine covered Cabinet with lid.  
see illus. on left  
Car. £1-25  
Or Dep. £18-25 and  
9 mthly pymts £8-88  
(Total £75-17) or Dep. £15 and 18  
mthly payments £3-82 (Total £80-82).

**£67-10**

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE  
High flux ceramic magnets. ALL CARRIAGE FREE.



'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
<b>£22-95</b>	<b>£12-90</b>	<b>£10-90</b>
Dep. £8 and 9 mthly payments £2-20 (Total £25-80)	Dep. £3-30 and 9 monthly payments. £1-30 (Total £15-00)	Dep. £2 and 9 monthly pay- ments £1-20 (Total £18-00)

FOR BASS GUITAR, ELECT. ORGAN, ETC.

PAIR SUITABLE  
ALL PURPOSES

## R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair

TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

**TYPE C485 25-30 WATTS**  
Fitted four 8" high flux 8 watt speakers  
Overall size approx. 48 x 10 x 5in.  
Terms: Dep. £2 and 9 monthly  
payments £2 (Total £21) Carr. 50p. **£31**

**TYPE C4125 50 WATTS**  
Fitted four 12" 11,000 line 15 watt  
speakers. Overall size approx. 55 x 14 x 9in.  
Terms: Dep. £4 and 9 monthly pay-  
ments £3-37 (Total £34-33) Carr. 75p. **£65**

**TYPE C4100 100 WATTS** inc. four 12" 50 watt speakers for conserva-  
tive rating. Extra heavy construction. Size approx. 58 x 16 x 10" Acoustically  
filled and pressurised. Terms: Dep. £12 and 12 mthly. pyts. £5-18 (Total £73-18). Carr. £1




## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high  
output. Hum level -70dB. Response  
±3dB 30-20,000 c/s. All high grade components. Valves E186  
EF86, ECC83, EL34, EL34, C234. Separate Bass and Treble  
Controls. Sensitivity 36 millivolts. For High Impedance micro-  
phones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Func-  
tions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram.

Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and  
Pick-up etc. for mixing purposes. 200-250v. 50 c/s A.C. mains. For 3 and 15 ohm  
speakers. Twin-handled perforated cover £1-90. 12 MONTHS' GUARANTEE. Carr. 65p  
TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22-00). Send S.A.E. for leaflet. **£19-75**
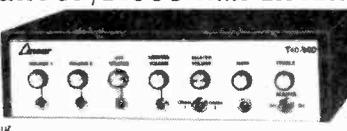
## LINEAR T40/60D 50W GROUP/DISCO AMPLIFIER

- ★ FULL MONITORING FACILITIES
- ★ Individual Bass and Treble controls
- ★ Twin Jack output sockets for speakers
- ★ Input sockets for medium or high impedance  
Microphones or Guitar P.U.s and Crystal  
Ceramic Gram. P.U.s
- ★ Frequency response 30-20,000 Hz.
- ★ Output overload protection plus double fusing



FRONT PANEL (Jack Inputs)  
Gram, Gram, Microphone/Guitar P.U.; plus monitoring  
socket.

CONTROLS Vol. (1) (2) (3) and (4). Bass, Treble,  
Master Vol., Monitor Selection Switch Gram (1) or (2).  
Mains Switch

TERMS: Deposit £7-50  
and 9 monthly  
payments £5-37  
(Total £55-83) Carr.  
free  
Simulated black  
rexine, plastic bonded  
metal case **£40-50**




## FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled inputs Plus master vol.  
control. Ind. Bass and Treble Controls. Protective circuit to  
guard against damage from accidental shorts. Output for  
Speakers/s 3 to 30 ohms. Size 17" x 7" x 7 1/2" 200-250v. A.C.  
mains. Output 50 watts music rating.  
Or deposit £7-25 & 9 monthly pay-  
ments £3-55. Total £39-20. **£34-95** Carr.  
75p.
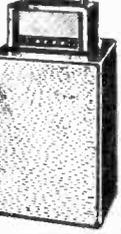
## RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose  
unit for lead, rhythm, bass guitar,  
vocalists, gram, radio, tape. Peak  
Output rating. Loudspeaker unit  
optional horizontal or vertical  
mounting.

- ★ Two extra heavy duty 12in. 50w L'spkrs.
  - ★ Four Jack inputs and two Volume  
Controls for instant use of up to four pick-ups  
or "mikes". Bass and Treble controls.
- Credit Terms: Deposit  
£15 & 9 monthly  
pyts of £6-25 Carr. **£65**  
(Total £71-25) £2 S.E.  
leaflet. for



## RSC GP30 HI-FI AMPLIFIER



For Guitar, Vocal or  
Instrumental Group

A 4 input, 2 vol. control HI-FI  
30 watt unit with Separate  
Bass and Treble controls.  
Current valves. Peak output  
rating. Strong Rexine covered  
cabinet with handles. Attractive  
black/gold P.V.C. fascia.

Neon indicator. For 200-250v. A.C. mains.  
For 3 and 15 ohm speakers. Send S.A.E. for  
leaflet. Terms: Deposit £4-40 and 9 monthly  
payments of £2-45 (Total £26-45). **£23-50** Carr.  
65p

## \* CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

NOW THREE NEW BRANCHES  
19/19A MARKET STREET  
**NOTTINGHAM**  
ALSO 5 MARKET SQUARE  
**SUNDERLAND**  
8 LITTLE UNDERBANK  
**STOCKPORT**  
AND NEW MUCH LARGER PREMISES  
24 NEWGATE CENTRE, NEWCASTLE



MAIL ORDERS & EXPORT ENQUIRIES TO:—  
AUDIO HOUSE, HEMCONNER LANE, LEEDS, 13.  
Tel. Pudsey 0975 7783.  
TERMS C.W.O. or C.O.D. No C.O.D. under £1.  
POSTAGE 25p EXTRA UNDER £2. 30p EXTRA  
OVER £2 OR AS QUOTED. TRADE SUPPLIED.  
S.A.E. PLEASE WITH ENQUIRIES.  
SUPPLIERS TO GOVERNMENT DEPARTMENTS.  
EDUCATION AUTHORITIES, SCHOOLS,  
HOSPITALS, H.M. FORCES ETC.  
MAIL ORDERS MUST BE SENT TO SHOPS

## R.S.C. Branches listed below open

- all day Saturdays and operate a 5-day week
- BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
  - BLACKPOOL (Agent) O & C Electronics 227 Church Street
  - BIRMINGHAM 30/31 Great Western Arcade, Tel. 021-236 1279 (Closed Wed.)
  - DERBY 26 Osmaston Rd., The Spot (Closed Wed.) Tel. 41354
  - DARLINGTON 18 Priestgate (Closed Wed) Tel 68043
  - EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
  - GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158
  - HULL 91 Paragon Street (Closed Thurs.). Tel. 20505.
  - LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
  - LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252
  - LIVERPOOL 73 Dale Street (Closed Wed.). Tel. 236 3573
  - LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629
  - MANCHESTER 60A Oldham Street, (Closed Wed.). Tel. 236 2778
  - MIDDLESBROUGH 106 Newport Rd. (Closed Wed.). Tel. 47096
  - NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469
  - NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel: 48068
  - SHEFFIELD 13 Exchange Street (Castle Market Bldgs.) (Closed Thurs.). Tel. 20716
  - SUNDERLAND 5 Market Sq. (Closed Wed.) Tel. 70573

# Come and listen at the year's most exciting exhibition

Join thousands of Hi-Fi enthusiasts in an atmosphere that will set your ears tingling with excitement. Whatever your taste – classics, jazz or pop – there will be something for you. The international giants of the Hi-Fi industry will be there – showing the latest specialist equipment: unit audio; tape recorders, cassette, cartridge and reel-to-reel; loudspeakers; AM/FM tuners, receivers; amplifiers, radios; tapes and discs. There will be continuous demonstrations in over 65 special Audio Studios – plus daily presentations, lectures and discussions in the Hi-Fi Theatre. And the Sunday Mirror is offering concession rates of admission to its readers, plus exciting competitions. Don't miss this great event.

## THE 1972 INTERNATIONAL AUDIO FESTIVAL AND FAIR

Sponsored by the Sunday Mirror



**OLYMPIA** London

Tuesday 24 October to

Saturday 28 October

Daily 10 a.m. to 9 p.m.

Admission 40p

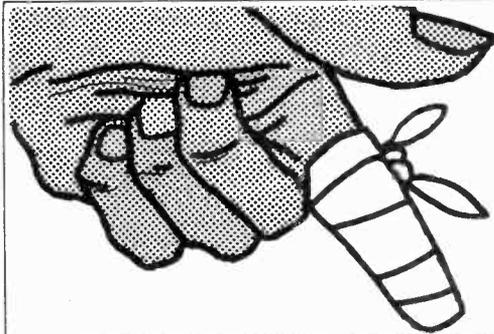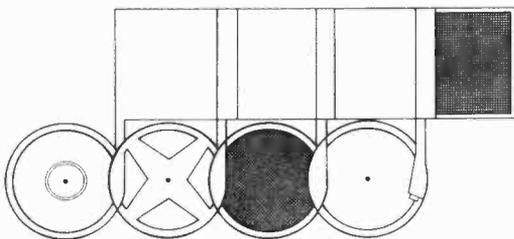


Burns and scalds can rob your fingers of the dexterity essential to your hobby. So keep Burneze close to hand for minor burns. This unique scientific aerosol cools the heat out in just 8 seconds, anaesthetizes pain, reduces swelling. Be well-equipped—buy Burneze, from chemists.



Potter & Clarke Ltd Croydon CR9 3LP

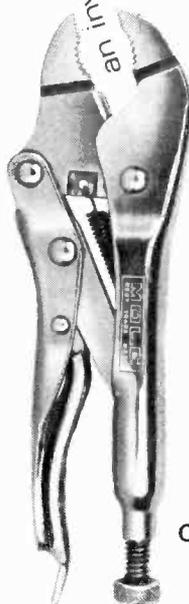an invaluable aid to practical wireless enthusiasts



The pocket size dimensions and versatility, of the MINI MOLE Wrench, makes it 'just the job' for intricate difficult-to-get-at components situated in awkward corners.

The steel jaws lock-on with a positive grip, and a flick of the lever releases their grip instantly.

Available from Hardware and Motor Accessory Shops.

**MINI  
MOLE**  
SELF GRIP WRENCH

only 80p



M. MOLE & SON LIMITED, NEWPORT, MON. NPT 5XZ.

# Why take the risk?

of damage to expensive transistors and integrated circuits, when soldering?

**Use Antex low-leakage soldering irons**



220-240 Volts or 100-120 Volts

## Model X25

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with it's truly remarkable neat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8".  
2 other bits available 3/32" and 3/16".

Totally enclosed element in ceramic and steel shaft Bits do not "freeze" and can easily be removed

PRICE: £1.75 (rec. retail)  
Suitable for production work and as a general purpose iron

## Model CCN 220 volts or 240 volts

The 15 watt miniature model CCN, also has negligible leakage.

Test voltage 4000v. A.C.

Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"

4 other bits available 1/8", 3/16" 1/4" and 1/16"

PRICE: £1.80 (rec. retail)

OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8"

PRICE: £1.95 (rec. retail)

## A SELECTION OF OTHER SOLDERING EQUIPMENT.



### MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24  
PRICE: £1.70 (rec. retail)

### MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.  
PRICE: £1.70 (rec. retail)



### MODEL G

18 Watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110.  
PRICE: £1.83 (rec. retail)

### MODEL SK.1 KIT



contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE £2.75 (Rec. retail)

### MODEL SK.2 KIT

contains 15 Watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32"

heat sink, solder and

booklet "How to Solder"



PRICE £2.40 (Rec. retail)

### MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder."

PRICE £1.95 (Rec. retail)



From radio or electrical dealers, car accessory shops or, in case of difficulty direct from: —  
**ANTEX LTD. FREEPOST**  
(no stamp required) **Plymouth**  
**PL1 1BR Tel: 0752 67377**


- Please send the ANTEX colour catalogue.
- Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PW/11

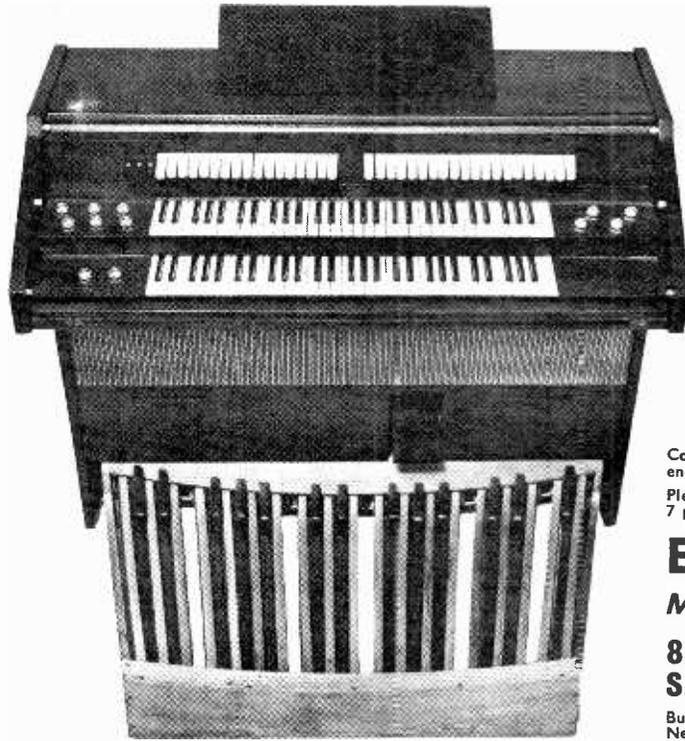

## ORGAN KITS

Build your own Electronic Organ, if you want the best value for your money. Yes you really save over 50% and get the best and up-to-date designs. There are four models to choose from.

- ★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, at £114.41, P/P £2.00.
- ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato built in amplifier and 50 watt 12" Goodmans speaker at £199.75, P/P £8.00.
- ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Percussion, Wah Wah, etc. at £406.00. Carr. paid on complete kit U.K. only.
- ★ Console—2 x 5 octave keyboards and 32 note pedal boards, 32 voices. Vibrato, Delay Vibrato, Sustain Reverberation, Percussion, 3 Couplers, etc., at £572.55 carr. paid on complete kit U.K. only.

Components can be bought separately. Trade and overseas enquiries welcomed. Send 25p for latest catalogue.

Please call in for demonstration. Business hours: 10 a.m. to 7 p.m. Monday to Saturday. Thursday closed.

## ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE RD., LONDON  
S.W.18 TEL: 01-870 4949

Bus numbers 37, 220, 225, 168 pass the door.  
Nearest Stations, Wandsworth Town, East Putney, Putney & Putney Bridge.

## The BATTERIES That Won't Let You Down! RECHARGEABLE

Mallory Cells  
in U2, U11 and  
Penlite U7 sizes,  
Kestrel Battery  
Charging Unit



Uses:  
Tape recorders, Portable  
radio and TV, Radio controlled model  
aircraft and boats, Cine cameras, Flashguns,  
Cordless shavers and other battery appliances.

Whenever you must have  
utterly dependable battery  
power—then these new  
Alkaline-Manganese re-  
chargeable cells will pro-  
vide it. The cells can be  
recharged many times, a  
simple job with the Kestrel  
Charging Unit which has  
been specially designed for  
these new type batteries.

**PRICES**  
Batteries U2  
equiv. £1.38  
Penlite U7  
equiv. 50p  
U11 equiv.  
£1.03  
Charging  
unit £3.99  
with one  
battery  
holder

**KESTREL**

Send to:  
275 WEST END LANE  
LONDON, N.W.8  
01-704 9811

*Bush & Meissner*

### 4-STATION INTERCOM



£7.25

Solve your communica-  
tion problems with this  
4-Station Transistor Intercom system (1 master and  
3 Subs), in de-luxe plastic cabinets for desk or wall  
mounting. Call/talk/listen from Master to Subs and  
Subs to Master. Ideally suitable for Business, Surgery,  
Schools, Hospital, Office and Home. Operates  
on one 9V battery. On/off switch. Volume control.  
Complete with 3 connecting wires each 66ft. and  
other accessories. P. & P. £0.40.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains  
for instant two-way, loud and clear communication.  
On off switch and volume control. Price £12.40  
P. & P. £0.55

### INTERCOM/BABY ALARM



OUR  
PRICE  
ONLY  
£3.35

Same as 4-Station Intercom for two-way instant  
communication. Ideal as Baby Alarm and Door  
Phone. Complete with 66ft. connecting wire.  
Battery 14p. P. & P. £0.55



£2.99

Why not boost  
business effi-  
ciency with this Incredible De-luxe Telephone Ampli-  
fier. Take down long telephone messages or converse  
without holding the handset. A useful office aid. On/  
off switch. Volume Control. Battery 14p. extra.  
P. & P. 22p. Full price refunded if not satisfied in  
7 days.

WEST LONDON DIRECT SUPPLIES (P.W.S.)  
169 KENNINGTON HIGH STREET, LONDON, W.8.



## LOUDSPEAKER BARGAINS

Fane Pop 100 Watt 18" 8/15 ohm	£19.50
Fane Pop 60 Watt 15" 8/15 ohm	£17.75
Fane Pop 50 Watt 12" 8/15 ohm	£9.25
Fane Pop 25/2 12" 25 watts	£7.40
Fane Pop 15 12" 10 watts	£4.00
Baker Group 25 12" 3, 8 or 15 ohm	£6.60
Celestion P58 for Unilux	£2.35
EMI 13 x 8, 3, 8 or 15 ohms	£2.25
EMI 13 x 8 d/cone 3, 8 or 15 ohms	£2.60
EMI 13 x 8 twin tweeter 3, 8 or 15 ohms	£3.60
Richard Allen 8" 3, 8 or 15 ohm	£2.35
Fane 8" dual cone 800T	£2.85
Fane 8" d/cone roll surround 807T	£3.50
Elac 59RM109 9" x 5" 15 ohm	£2.70
Elac 59RM114 9" x 5" 8 ohm	£2.70
Elac 8 1/2 d/cone 8 ohm	£2.25
Elac 4" tweeter 8 ohm	£1.50
Crossover for above (post free)	£1.50
Richard Allen 12" 3 or 15 ohm	£2.50
Goodmans 8 P, 8 or 15 ohm	£4.75
Goodmans 10 P, 8 or 15 ohm	£5.25
Goodmans 12 P, 8 or 15 ohm	£10.50
Goodmans 15 P, 8 or 15 ohm	£17.00
Goodmans 18 P, 8 or 15 ohms	£27.50
7" x 2 1/2" or 3" 80 ohm or 2 1/2" 64 ohm	£5.65
8" x 5" 3 or 8 ohm	£1.50
8" x 5" 3 or 8 ohm	£1.50
10" x 6" 3, 8 or 15 ohm	£2.00
Phillips 5" 8 ohm	£1.95

FREE with orders over £6—"Hi-Fi Loudspeaker  
Enclosures" book.

All units guaranteed new and perfect.  
Prompt despatch p. & p. 25p per speaker.

**WILMSLOW  
AUDIO, Dept. PW**  
10 Swan St., Wilmslow,  
Cheshire, SK9 1HF

## Garrard Record Players

SP25 Mk. III  
Deck Only  
4 speed



Automatic Single Player

Lasky's price **£11-50**

Garrard SL95B Deck	£32-50
Garrard SL95B on base with 9TA cart.	£44-00
Garrard AP76 deck only	£18-75
Garrard 40B deck only	£9-50
complete with stereo cartridge	£11-50
Garrard SL55B deck only	£9-00
Garrard 2025TC deck only	£7-95
complete with KS40A stereo ceramic cartridge	£39-95
Garrard ZERO 100 Automatic	£37-50
	C & P £1-50
Garrard ZERO 100S Single Player	£37-50
	C & P £1-50

## Garrard Plinths & Covers

WB4 Mk. II Plinth	£5-45
SPC4 Mk. II cover	£4-25
Price together	£8-70
WB1 Plinth	£3-70
SPC1 cover	£3-60
Price together	£6-50

## Garrard Module Series

Modules are complete wired units with cartridge, plinth and cover.

### SP25 Mk. III Module

SP25 Mk. III with SHURE M75/6 cart. **£23-95**

### AP76 Module

AP76 with SHURE M75/6 cartridge **£33-95**

### AP96 Module

Single play version of SL95B with SHURE M75/6 cartridge **£38-75**

### Zero 100S Module

ZERO 100S with SHURE M93/E cartridge **£52-75**

## CARRIAGE—all units

DECK ONLY 50p. PLINTH & COVER ONLY 25p. DECK WITH PLINTH AND COVER 75p.

## BSR McDONALD MP60

High precision low-mass counter-balanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.



LASKY'S PRICE **£10-95** C & P 50p

BSR McDONALD UNITS & PACKAGES  
A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

MODEL	A	B	C	D	E
MP.60	10-95	15-50	18-50	18-75	22-00
HT.70	15-90	19-90	23-50	23-75	27-00
610	14-50	18-75	23-00	22-25	25-50
210 Complete with plinth, cover & BSR cartridge					
MP.60 TPD2 Styrene base			17-50		21-00
810 transcription model					£33-50
810 with BSR plinth and cover					£45-00

## BSR TD8S

### 8 TRACK STEREO CARTRIDGE PLAYER

The TD8S is suitable for use with most modern stereo amplifiers and delivers a pre-amp output of 125mW. Power requirements: 210/250V AC, 50Hz. Frequency response: 50Hz-10KHz. 4 pole dynamically balanced synchronous motor. Black and woodgrain plastic cabinet. Size: 8½(H) X 3½(H) X 10½(D) in. List Price **£24-20** LASKY'S PRICE **£17-95**



# AUDIO-TRONICS

'73 JUST PUBLISHED

The 1973 edition of Lasky's famous "Audio-Tronics Pictorial" is now available. Bigger, brighter and better than ever. Lasky's brand new catalogue now contains 48 pages packed with all the latest Hi-Fi and electronics equipment—everything for the layman and enthusiast alike. All the goods shown in the "Audio-Tronics Catalogue" are available from any of our branches or by Mail Order to any address in the U.K. or overseas. Free on request. Just send your name, address and 15p for post and inclusion on our regular mailing list.

# FREE

SEND TODAY—and bring the benefit of shopping at Lasky's to you in the comfort of your home.

## INTERNATIONAL MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in. RT.20 Message Tape 225ft.	19p
3½in. RT.21 Triple play, 600ft. Mylar	50p
5in. RT.23 Double play, 1,200ft.	75p
5in. RT.18 Long play, 900ft. Acetate	50p
5in. RT.17 Standard play 600ft.	43p
5½in. RT.15 Double play, 1,800ft. Mylar	£1-13
5½in. RT.16 Long play, 1,200ft. Acetate	75p
5½in. RT.24 Standard play 900ft. P.V.C.	68p
5½in. RT.14 Long play, 1,200ft. Mylar	£1-31
5½in. RT.25 Triple play, 2,400ft.	63p
7in. RT.22 Standard play, 1,200ft. Acetate	63p
7in. RT.10 Standard play, 1,200ft. Mylar	95p
7in. RT.12 Long play, 1,800ft. Mylar	£1-25
7in. RT.13 Double play, 2,400ft. Mylar	75p
7in. RT.11 Long play, 1,800ft. Acetate	£2-50
7in. RT.19 Triple play, 3,600ft. Mylar	£1-02
3½in. RT.22 Quad play, 1,100ft.	£1-02

P & P 5p extra per reel, 4 reels and over Post Free. Special quotes for quantities.

## LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

Type	Singles	5	10	15
C64	28p	£1-37	£2-70	£3-99
C98	38p	£1-86	£3-67	£5-42
C120	48p	£2-35	£4-63	£6-84

Each cassette individually boxed in Philips, type plastic library.  
C & P: each 7p, 5—25p, 10—40p, 20—68p.



AKAI 4000D illustrated List Price £93-65 Lasky's Price **£61-50**

AKAI I720L List Price £87-36 Lasky's Price **£58-95**

AKAI X1800SD List Price £162-79 Lasky's Price **£111-50**

AKAI X200D List Price £157-93 Lasky's Price **£106-50**


2 CSS-8 Speakers List Price £25-00 Lasky's Price **£15-95** C & P 50p

2 ADM 11/8 mics. Suitable for use on all Akai tape recorders. List Price £11-90. Lasky's Price **£7-50**. C & P 15p.

## AKAI TAPE RECORDER SCOOP!

(C & P 75p on all Tape Decks.)

## BSR TAPE DECK SCOOP

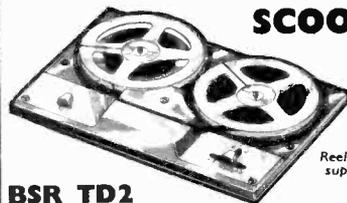

Reels not supplied

### BSR TD2

FANTASTIC VALUE, ONLY Lasky's can offer you a tape deck at such an amazing price. The BSR TD2 tape deck operates by a simple reliable mechanism. Available with ¼ track or ½ track mono or stereo heads. Incorporates fast wind and fast rewind, takes up to 5½in. spools. Size 13in. x 8½in. front to rear, 2½in. below plate, 1½in. above plate.

ALSO SUITABLE FOR USE AS A TAPE TRANSPORTER  
LASKY'S PRICE **£8-95** C & P 35p

## SINCLAIR PHASE LOCK LOOP STEREO FM TUNER



Incorporates varicap diodes, printed circuit, coils, squelch circuit I.C. Decoder, etc., supplied completely built and tested and ready to use with any High Fidelity Amplifier. Power requirements 25/30V DC. Size 8½" x 1½" x 3½".

LIST PRICE LASKY'S PRICE **£15-75** C & P 25p  
PZ5 power supply £4-15 extra.

## NEW DIGITAL CLOCK NOW WITH ILLUMINATED DIAL EXCLUSIVELY FROM LASKY'S

The clock measures 5½" W x 2½" H x 3½" D (overall from front of drum to back of switch). SPEC.: 210/240V a.c. 50Hz operation; switch rating 250V, 3A. Complete with instructions. COMPLETE WITH KNOBS. FEATURES: ● MAINS WITH AUTOMATIC 12-HOUR ALARM ● AUTO "SLEEP" SWITCH ● HOURS, MINUTES AND SECONDS READ-OFF ● FORWARD AND BACKWARD TIME ADJUSTMENT ● SILENT OPERATION ● SHOCK AND VIBRATION PROOF ● BUILT IN ALARM BUZZER  
SPECIAL QUOTES LASKY'S PRICE **£6-75** C & P 25p FOR QUANTITIES



## NEW WELLER MINI-SHOP KIT-600K

Powered by a 25,000rpm, 115 volts, 75 amp Universal motor. This small versatile, easy to handle, power tool is ideal for handymen, and professionals. The wide selection of bits helps you grind, sharpen, drill, rout, cut etc. Perfect for delicate work. The complete kit is housed in a strong plastic case. MODEL 600K 37 piece Kit contains: ● Model 600 Power Unit ● Accessory Caddy ● 8 Grinding/Sharpening Bits ● 3 Polishing Wheels ● 4 Cleaning Bits ● 8 Abrasive Discs ● 3 Abrasive Bands ● Expanding Drum ● Drill Bit ● Mandrel ● Chuck Wrench ● Dressing Stone ● Plastic Polish ● Jewellers Rouge ● Complete with owners manual ● Size of power unit only 7½".

LASKY'S PRICE **£17-95** C & P 35p



# Lasky's Radio Limited

Branches

33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605  
Open all day, 9 a.m.—6 p.m. Monday to Saturday

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271  
Open all day, 9 a.m.—6 p.m. Monday to Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 0845  
Open all day, 9 a.m.—6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812  
Open all day Thursday, early closing 1 p.m. Saturday

MAIL ORDERS TO: 3-15 CAVELL ST. LONDON E1 2BN 01-790 4821



# S.C.S. COMPONENTS

P.O. BOX No. 26, WEMBLEY, MIDDLESEX, HA0 1YY  
the 'PROFESSIONAL' amateur supplier

**NEW**  
SIGNETICS DATA BOOK £1.00 each postage and packing 10p. Book one digital bipolar circuits—contains full Data Sheets and Application notes on complete Signetics range of Digital devices. 596 pages.  
Book two covers full range signetics linear devices including Audio Amplifiers and preamplifiers. 240 pages.

## SPECIAL OFFERS

MEL12	50p	LM301A	90p
EP401	8p	2N5459	49p
TT3643	30p	BC108	10p
MA741	34p	2N3643	25p
2N3648	£1.10	BC178	22p
IN914	6p	2N2646	37p
BC107	10p	EM404	8p
CI0611	50p	CI0601	55p
UA709	31p	UA748	34p
1 M Ω Trimpots	...	...	11p

Texan 20+20 watt Stereo. Complete kit of Semiconductors £5.30

\*\*2N3055 Si NPN power TX 115 watt. 35p\*\*\*

send SAE for priced list of all parts for any E.T.I. constructional project.

## SIGNETICS NE555V Timer

first time offered to constructors.

### Features

- Timing from microseconds through 1 Hr.
- Can either free run or hatch.
- Adjustable duty cycle.
- Time delays can be reset.
- Temperature stability 0.0005% per °C.
- Operates from 4 to 15 volts. for 1% change in timing.
- Timing can be changed 10-1 with control voltage.
- Output can source or sink 100 M.A.
- 8 pin plastic D.I.L. package plus Data and Application Notes 90p

## SEMICONDUCTORS

AA119	9p	BC136	20p	BF161	45p	OA81	10p
AA111	10p	BC137	20p	BF178	25p	OA85	12p
AA130	10p	BC139	25p	BF179	30p	OA90	8p
AA213	10p	BC142	21p	BF180	35p	OA91	7p
AC107	34p	BC143	23p	BF184	20p	OA95	7p
AC126	25p	BC147	12p	BF185	20p	OA200	7p
AC127	30p	BC148	15p	BF194	15p	OA202	10p
AC128	25p	BC149	12p	BF195	15p	OA2223	45p
AC141K	25p	BC152	20p	BF196	15p	OA2230	45p
AC142K	18p	BC153	20p	BF197	15p	OC28	55p
AC153	25p	BC157	15p	BF200	35p	OC35	60p
AC153K	22p	BC158	12p	BF222	30p	OC36	65p
AC175K	30p	BC159	15p	BF241	30p	OC44	15p
AC176	25p	BC170	15p	BF256L	30p	OC45	15p
AC176K	20p	BC171	15p	BF256LC	34p	OC70	15p
AC187	25p	BC171A	17p	BF536A	37p	OC71	11p
AC187K	25p	BC177	20p	BFW17A	£1.22	OC74	25p
AC188K	25p	BC177B	23p	BFX37	23p	OC75	23p
AC193K	25p	BC178B	10p	BFX94	15p	OC170	23p
AC194K	27p	BC179	20p	BFX85	25p	R2008	£3.5
AC194K	20p	BC182L	10p	BFY50	20p	R2009	£2.5
AC194K	20p	BC182LB	10p	BFY51	20p	R2010	£2.5
AC194K	20p	BC183	10p	BFY52	20p	SP8385	£1.0
AD143	45p	BC183L	10p	BFY50	59p	TJ700	£2.4
AD161	35p	BC183LB	10p	BSX20	15p	TAD100	£1.3
AD162	35p	BC184LC	12p	BSX60	50p	TBA500	£2.0
AF115	25p	BC186	25p	BSX61	35p	TBA510	£2.0
AF117	20p	BC187	25p	BT106	85p	TBA520	£2.5
AF121	30p	BC208A	14p	BU105/02	£2	TBA520Q	£2.5
AF124	25p	BC212	10p	BY126	15p	TBA530	£1.8
AF126	20p	BC212A	10p	BY127	15p	TBA530Q	£1.8
AF127	20p	BC212LA	13p	BY147	£1.04	TBA540	£2.0
AF139	30p	BC213L	12p	BY164	35p	TBA550	£3.0
AF179	25p	BC214	15p	BZY88 ser 9-5p	5p	TBA550Q	£3.0
AF178	55p	BC214L	15p	BZY94 ser 9-5p	5p	TBA570Q	£1.2
AF170	60p	BC250B	14p	BR100	26p	TBA750	£1.4
AF239	40p	BC261	16p	BRC4443	90p	TBA750Q	£1.4
ASZ17	50p	BC268	11p	BRY39	30p	TIC46	40p
BA102	30p	BC308A	17p	E1222	40p	TIP29A	50p
BA145	15p	BC317	20p	E5024	40p	TIS60M/61M33P	37p
BA148	15p	BCY21	96p	GET102	39p	TIS61	20p
BA154	9p	BCY31	40p	GET103	25p	TIS91	17p
BA155	10p	BCY42	30p	IS921	8p	2N404	15p
BA163	90p	BCY70	15p	IS923	12p	2N697	15p
BAX12	12p	BCY71	20p	ME0404	11p	2N706	9p
BAW63	36p	BCY72	15p	ME0412	15p	2N708	12p
BAW65	36p	BCY89	97p	ME0413	12p	2N753	10p
BAW67	35p	BD115	75p	ME0462	19p	2N919	45p
BB105	37p	BD124	80p	ME2002	8p	2N920	42p
BBY20	37p	BD131	75p	ME4003	12p	2N1302	17p
BC107	10p	BD132	80p	ME4102	10p	2N1304	21p
BC107B	12p	BD135	75p	ME4104	8p	2N1306	24p
BC108	10p	BD175	44p	ME6002	12p	2N1307	24p
BC108A	10p	BD181	90p	ME6101	12p	2N1308	24p
BC108C	15p	BD184	£1.3	ME6102	13p	2N1309	24p
BC109	15p	BF121	25p	ME8001	12p	2N3053	20p
BC113	10p	BF123	30p	ME8003	13p	2N3054	50p
BC116	20p	BF125	25p	MEF104	34p	2N3055	55p
BC117	20p	BF127	30p	MEL11	30p	IN914	6p
BC119	30p	BF153	20p	MP8112	34p	IN916	10p
BC121	25p	BF154	20p	MP8113	30p	IN4148	6p
BC125B	25p	BF160	25p	OA47	10p		

TERMS. Retail mail order subject to £1.00 minimum order. Cash with order only. Trade and educational establishments M/A/C on application (minimum £5). Postage 10p inland, 25p Europe. GUARANTEE. All goods carry full manufacturer's warranty. Special Enquiries etc. Please enclose stamped addressed envelope.



## for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required

## IDEAL FOR HOME CONSTRUCTORS



Size 1 cartons all at 25p each in 40/60, 60/40, or Savbit alloys in 7 gauges.

## EASY-TO-USE DISPENSERS



Size 5 (Savbit) 18swg, 18p (illustrated)

Size 19A (60/40 alloy) 18swg, 18p

Size 15 (60/40 alloy) 22swg, 22p

## BIB WIRE STRIPPER AND CUTTER



Model 3A. Strips insulation from cable or flex without nicking wire. 4 different settings, 4&6 BA spanner ends, ground cutting edges. Price 32p. Also available, de luxe Model 8. Price 58p.

From Electrical and Hardware Shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.



## AMAZING MINI-DRILL

### FOR PRECISION MODEL WORK



ONLY £2 P.A.P. 10p

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £4.95 p.p. 13p. De Luxe Professional Kit with 17 tools. £7.65 p.p. 23p. Money ref. g'tee.

MERLIN SUPPLY CO.

Dept. PW 11/72 Nailsea, Bristol BS19 2LP

## INTER-LOCKING PLASTIC STORAGE DRAWERS

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots / removable space dividers. Build up any size cabinet for wall, bench or table top.

**DISCOUNT PRICES**

SINGLE UNITS (5" x 2 1/2" x 2 1/4") £1.35 Dozen  
DOUBLE UNITS £2.35 Dozen  
DOUBLE TREBLE (3D) £2.35 for 8  
DOUBLE TREBLE 2 draws in one outer case (6D2) £3.65 for 8 extra large size (6D1) £3.30 for 8.

**PLUS QUANTITY DISCOUNTS!** Order £5 and over Deduct 5% in the £. Order £10 and over Deduct 7½% in the £. Order £20 and over Deduct 10% in the £. Pack./Post./Carr.: Add 35p to all orders under £5. Orders over £5 P/P/C free.

(Dept PW11) 124 CRICKLEWOOD BROADWAY, LONDON N.W.2



**ALMOST UNBELIEVABLE!** Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible Russians have done it all **NOW!** It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £80 radios! \*You can't lose, we'll refund instantly if you are not astounded! Elegant black and chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer and sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space and satellite communications. **Yes, EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth 24 hours a day, including all normal transmissions, VHF, AM, FM, MW, LW, USW, plus local and new stations not yet operational and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240v AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE** 14ins x 10ins x 4ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities and spares available for years and years to come, if ever necessary!). With **WRITTEN GUARANTEE** manual with simple operating instructions and circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra). **BOX, POST, ETC. 50p.** \***BUT WAIT**, for only 55p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (it enables you to time, pinpoint and get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) PLUS Standard 'longlife' batteries **PLUS** ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) **HURRY!** Send today or call at either store. It's a chance of a lifetime that nobody can afford to miss.

**JUST ARRIVED!** **THIS YEAR'S NEW \* COMPUTERISED!**  
**RUSSIAN MIRACLE!**

**BRAND NEW SPACE AGE model SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING MANY LOOK OUT OF DATE IN 1984!**

**THE FABULOUS ASTRAD 17**

**PORTABLE RADIO & COMMUNICATIONS RECEIVER**

**WORLD WIDE RECEPTION**  
 THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!

"MAGIC EYE" tuning level indicator

**\*COMPARE ITS PERFORMANCE with £80 RADIOS!**

**28 TRANSISTORS AND DIODES!**

**WAVEBANDS:**  
 STANDARD LONG and MEDIUM  
 Plus 5 SHORT WAVEBANDS  
 Plus ULTRA SHORT WAVES  
 (V.H.F. AM, FM, MW, LW, USW.)

**BATTERY MODEL £20.75** **BOX POST ETC. 50p**  
**MAINS/BATTERY ELIMINATOR £1.48 extra**

**FIRST TIME EVER!**  
 \*NOW AVAILABLE WITH fabulous "COMPUTERISED" **WORLD TUNING GUIDE!**  
**NO MORE GUESSWORK!**  
**INSTANT DATA** at your fingertips—enables you to **TUNE IN A FLASH** to transmissions the world over!

**SHOPPERTUNITIES FOR BARGAINS!**

**ANOTHER EAST EUROPEAN MIRACLE!**

**FANTASTIC 2-in-1 PERSONAL PORTABLE and CAR RADIO**

**NOW WORLD WIDE RECEPTION**

**IN YOUR CAR TOO! (RUNS OFF 12V. CAR BATTERY)**

**4 WAVEBAND VHF AM FM / LONG & SHORT WAVEBANDS**

**FANTASTIC PRICE £9.95**

**BOX, POST ETC. 45p.**

Position it for **CAR RADIO**, results will justify! OR detach & use carry handle for **PORTABLE** with its own batteries!

**TRY AND MATCH IT FOR UNDER £35!**

**FANTASTIC!** Brand spanking new. Another East European Miracle! This incredible 2-in-1 Radio! First class makers—because of our crazy price, contact suppliers, we must NOT mention name! Beautifully made, 9 x 5 x 2 1/2 inches overall approx. Every up-to-date technological improvement. 15 SEMI-CONDUCTORS: 9 Transistors, 2 Diodes, and 4 stabilisers! **FOUR WAVEBANDS!** Yes, VHF model with AM/FM Long and Short wavebands! Will get stations around the world, including Standard Long, Medium and Short Wave, also local and new stations not yet operational! Built-in

**THIS FANTASTIC OFFER ONLY FROM US!** **SAVE £20.25 NOW!**

**Fabulous BRAND NEW SOLID STATE**

**BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**

**WITH REMOTE CONTROL MICROPHONE**

**OUR PRICE £23.75** **CARR. ETC. 35p**

**RECOMMENDED RETAIL PRICE £44**

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!) We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers' Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined and it also runs off standard batteries or mains. (Simply plug in the 220/240v. AC line cord. Record and play back anything, anywhere! Even tape direct from the Radio as you listen! **RECOMMENDED RETAIL PRICE GENUINELY £44!** **WE OFFER AT ALMOST HALF PRICE!** Wonderful features: \* Press-button Keyboard Control Panel or latest **MAGIC SWITCH CONTROL!** \* "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! \* Separate ON/OFF and HI-LO volume controls! \* Heavy duty built-in speaker! \* Earphone (for personal listening or "monitoring") and extension speaker sockets! \* Remote control microphone! \* Built-in swivel telescopic extension aerial (24in. approx.) Magnificently made case with carry handle. (**DESIGNS VARY SLIGHTLY**) Takes standard 90, 60, 30, 15 minute Cassette Tapes that are obtainable everywhere. **TRY AND MATCH IT FOR UNDER £35!** Unique rotating Station Selector Dial—er! local and regional stations in every part of the country plus B.B.C. National, Millions of dozens of foreign stations. Fabulous in your car! You could pay £20 more for a Car Radio or Car Cassette player plus remote control microphone, an on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send today or call at either store. **BONUS OFFER:** Batteries and Cassette Tape 25p extra if required.

Internal ferrite aerial plus 5 section 28in. swivel telescopic aerial. On/Off/volume and tone controls. Clear Station Selector Dial. Waveband selector. Equally wonderful in CAR or HOME! **TWO Tuning Dials** for flat or upright use as illustrated. **RUNS OFF 12 VOLT BATTERY!** (AS A PORTABLE it runs on standard batteries, using car battery only. **TOR JACK PROVIDED** and automatically cut out internal batteries, using car battery only. Don't you think it's marvellous? Spare the 0v. one and pull in hundreds of transmissions day and night including short wave—even in car! **BUT WAIT**—simply remove Radio from case, snap on optional carry handle. **AND YOU HAVE A DE-LUXE PORTABLE.** with additional upright for use and **WRITTEN GUARANTEE.** Only £8.95 box, post 45p. \*Sprung all metal matching detachable carry handle (as illus.) AND set of batteries only 25p extra if required. Match with sets costing £35 or more. See for yourself! Test 7 days—refund if not delighted.

Send quickly to our **Uxbridge Road** address or call at either store. (COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising Office at Holborn stores.)

**SHOPPERTUNITIES LTD.**

3rd, WP/23, 164 UXBURIDGE RD., LONDON, W12 8AQ  
 (Thurs. 1, Fri. 7) (Facing Shepherd's Bush Green). Also 37 High Holborn, London, W.C.1 (Thursday 7 p.m.) Both Mon. to Sat. 9 a.m.—6 p.m.

# RTVC THE

## THE FABULOUSLY SUCCESSFUL VISCOUNT III AUDIO £52 complete

14 + 14 watts r.m.s. 40Hz to 40kHz  $\pm 3$ dB. Total distortion at 10 watts at 1kHz -0.1%

This is real value for money! We have designed 2 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect transistors) are incorporated on the Input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For both systems we have chosen the famous Garrard SP25 Mk. III deck which comes with fitted magnetic cartridge, simulated teak plinth and tinted acrylic dust cover. The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

### SPEAKERS

**Duo Type II** Size approx. 17in. x 10 $\frac{1}{2}$ in. x 6 $\frac{1}{2}$ in. Drive unit 13in. x 8in. with parasitic tweeter. Max. power 10 watts, 8 ohms. Simulated Teak cabinet. £14 pair + £2 p&p.

**Duo Type III** Size approx. 23 $\frac{1}{2}$ in. x 11 $\frac{1}{2}$ in. x 9 $\frac{1}{2}$ in. Drive unit 13 $\frac{1}{2}$ in. x 8 $\frac{1}{2}$ in. with H.F. speaker. Max power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

### SPECIFICATION R 101

14 watts per channel into 3 to 4 ohms. (suitable 3-15 ohms). Total distortion @ 10W @ 1kHz 0.1%. P.U.1. (for ceramic cartridges) 150mV into 3 Meg. P.U.2. (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within  $\pm 1$ dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal-to-noise ratio: (all controls at max) -P.U.1. and radio -65dB, P.U.2 -58dB. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$  x 9in. x 3 $\frac{1}{2}$ in.

### BRITISH MADE—12 MONTHS WRITTEN GUARANTEE

Send S.A.E. for fully illustrated brochure


—ONLY FROM US

<b>PRICES: SYSTEM 1</b>	
Viscount III R101 amplifier	£22.00+90p p&p
2 x Duo Type II speakers	£14.00+£2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00+£1.50 p&p
<b>Total</b>	<b>£59.00</b>

Available complete for only £52 + £3.50 p&p

<b>PRICES: SYSTEM 2</b>	
Viscount R101 amplifier	£22.00+90p p&p
2 x Duo Type III speakers	£32.00+£3 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00+£1.50 p&p
<b>Total</b>	<b>£77.00</b>

Available complete for £69 + £4 p&p

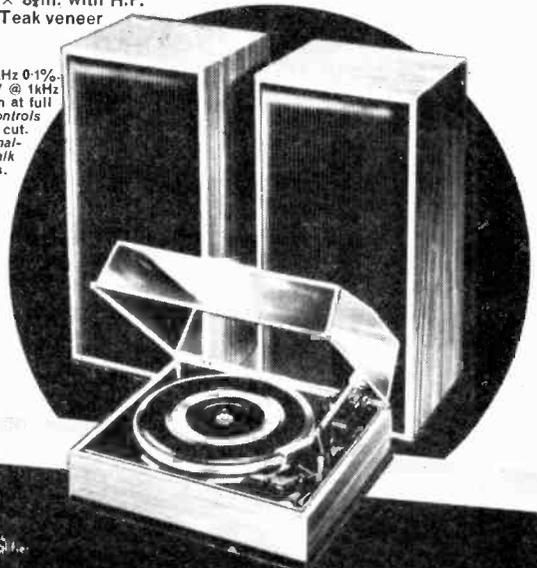

# MUSIC MAKERS

## UNISOUND FOR THE NEW SOUND

AT £25

The whole system is complete including superb cabinets in simulated teak—just simply screw together the components and you save pounds!

Amplifier is based on the famous Mullard Unilex system. Garrard 2025TC turntable complete with stereo ceramic cartridge, teak simulated plinth and tinted acrylic cover. Plus the big 13" x 8" EMI Twin-cone speakers ready for mounting in their elegant cabinets, which simply need screwing and glueing together. All glue and screws supplied.

Easy to follow step-by-step instructions guide you quickly and effortlessly to taking the wraps off truly realistic stereo sound.

£25 complete plus £2.80 p. & p.

Diamond Stylus £1.25 extra.

Power output: 4 watts per channel into 8 ohms.


Inputs: 120 mV (for ceramic cartridges).

Stereo headphones with adaptor £4.00
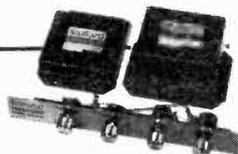
### UNISOUND MODULES ONLY £6.95

If you prefer, you can buy the three modules—pre-amplifier, power supply/dual power amplifier, and control panel—by themselves for only £6.95. P. & P. 50p extra.

No soldering, just simply screw together with screwdriver supplied. Their overall specification is the same as shown for the complete Unisound console, using the high efficient I.C. monolithic power chips to ensure very low distortion at all power levels, correct operation in all ambient temperatures. Full power over the audio spectrum.



AN **R T V C** EXCLUSIVE DESIGN

## A 'NATURAL' ONLY FROM THE TOURIST PB CAR RADIO KIT

**R T V C**

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components, this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. Four push-buttons for medium wave, one for long wave. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohm speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms. Power consumption is less than 1 amp.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale for easy reading at night. Chassis size is: 7in. wide, 2in. high and 4 1/2 in. deep (excluding front panel, etc.).

★ Circuit diagram and comprehensive instructions 50p, free with parts.

★ Fully retractable, lockable, Car aerial £1.25 post paid.

Price only £7.00 + 50p p&p. 8 ohm speaker with baffle and fixing strips £1.50 post free if bought with kit + 25p p&p.

If you can solder on printed circuit board you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.



## RELIANT MK.IV

- ★ 5 Electronically Mixed Inputs. ★ 3 Individual Mixing Controls. ★ Separate bass and treble controls common to all 5 inputs. ★ Mixer employing F.E.T. (Field Effect Transistor). ★ Solid State Circuitry. ★ Attractive Styling.
- ★ Sides Finished in solid teak

**INPUTS:**—1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram., Tuner, Monitor, Organ, etc.). All 250mV sensitivity. **CONTROLS:**—3 Volume controls. Bass control range: -13dB @ 60Hz. Treble control range ±12dB @ 15KHz. Separate ON/OFF Switch. Neon Indicator. **POWER OUTPUT:**—12 Watts R.M.S. Into 3 to 4 ohms speaker. **SIGNAL/NOISE:**—Better than -60dB on Inputs 3, 4 and 5 & -50dB on 1 & 2. **SUPPLY:**—220-250 AC Mains. **SIZE:**—12 1/2" x 6" x 3 1/2".

**£10.50**  
plus p. & p. 80p

VISIT OUR SHOWROOMS

**R T V C**

S.A.E. for fully illustrated leaflet.

Radio and TV Components (Acton) Ltd.  
21C High Street, Acton, London W3 6NG  
323 Edgware Road, London, W2.

Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.  
Goods not dispatched outside UK.




# AMPLIFIERS

FOR GUITAR PICK-UPS  
GRAM PICK-UPS RADIO or TAPE

OVERLOAD PROTECTION INCORPORATED. SOLID STATE CIRCUITRY

Suitable for application of Loudspeakers impedances between 3 and 30 ohms. Combinations not to measure less than 6 ohms across both speaker output jacks simultaneously.

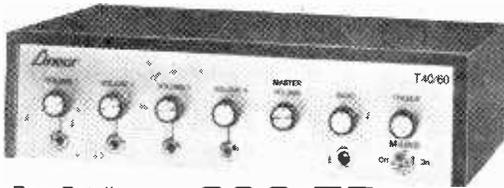The Amplifier cover is made of rigid plastic, bonded metal on the top and two sides. Finished in Black to suitably contrast with anodised metal control panel. Size approx. 14" x 4 1/2" x 9 1/2".



## GENERAL PURPOSE AMPLIFIER

Model 40/60 40 - 50 Watts Output Power

Four individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'.

Compact size, robust construction. Ideal for clubs, hotels, restaurants, schools etc. Inputs for almost any type of microphone


Rec. Retail Price **£39.75**

## GENERAL PURPOSE GROUP/DISCO AMPLIFIER Model T40/60D

40 - 50 Watts Output Power

Three individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'. Compact size. Robust construction. Ideal for discotheques, clubs, hotels, schools, etc. Inputs for most types of microphones. Facilities for head-phone monitoring with changeover switch from input (1) to input (2).

Rec. Retail Price **£49.50**

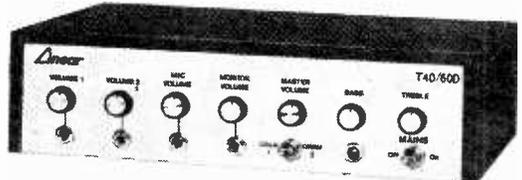

Wholesale and Retail enquiries to the Manufacturers Send S.A.E. for leaflet/s All Linear Amplifiers Guaranteed for 12 Months

**LINEAR PRODUCTS LTD.,** Electron Works, Armley, Leeds. LS12 3SA Tel. 630126

### PADGETT'S RADIO STORE

OLD TOWN HALL, LIVERSEDEGE,  
YORKS WF15, 6PQ  
TEL. HECKMONDWIKE 4285

**SPEAKERS EX TV SETS.** Sound tested 7" x 4", 6" x 4", 8" x 2 1/2", all 3ohm pm 25p each. Post on any speaker 10p.

**Valve Voltmeter. Type CT54.** Ohms Range 1K To 10 Meg In 5 Ranges. Volts Range 2.5 To 480 V AC DC. Untested Clean Condition. Less Batteries. £5. Carriage & Ins. £1.

**Tapes 7" LP 75p. 7" ST. 60p. 5" ST 40p. 5" LP 50p** Post on any tape 10p.

**JAP Earpieces.** Small plug 10p. Crystal diodes 20p doz. Post paid.

**Latest Air Ministry Release Radio Receiver. Type R4187.** 2.8 To 18 MHZ In Three Bands, Complete with 17 Miniature Valves, 26 Volt Motor. Power supply Motor and Manually Tuned. Very Clean. But not tested. £5. Carriage and Ins. 75p.

Everyone loves a bargain. And these T.V. sets we offer are the best you will find at the price.

Complete untested T.V. sets with all valves back and knobs BBC1 and ITV. 17" 90" tube £2. 17" 110" tube £3. 19" slim £5. Carriage and Ins. £1.50.

We are now breaking up many Slimline Sets. Send S.A.E. and please quote model and serial number and part you require.

For example tested L.O.P.T. £1.45. Fireball Tuners with Valves 75p. Droppers all types 50p.

**Breaking up Ferguson Type 506T.** Tested L.O.P.T. £1.45. Post paid. Fireball Tuner Unit with Valves less knobs 75p post paid. S.A.E. for other spares for this set.

**Reclaimed T.V. Tubes. All with 12 months guarantee.** AW43/88, £1.50. AW43/80 £1.50. MW43/69 £1. Special Offer, Brand New Brimar Tubes C17PM £1. Many older types in stock. Carriage and ins. on any tube £1.50.

**Valve Hat ex equipment. All valves tested on a Mullard valve tester before despatched. 3 months guarantee on all valves. Single valves P/P 3p. Over post paid.**

ARP12	5p	PCC84	5p	U191	20p
EB91	4p	PCF80	5p	U251	12p
EF80	8p	PCL82	12p	6BW7	10p
EF85	12p	PCL83	12p	6U4	10p
EF80	12p	PCL84	12p	20P1	20p
EBF69	12p	PL36	20p	20P3	10p
ECC81	10p	PL81	17p	20D1	10p
ECC82	12p	PY81	8p	30P4	20p
ECC83	12p	PY33	17p	30F5	20p
ECL80	8p	PY82	8p	30P12	20p
EF91	4p	PL82	8p	30FL1	20p
EY85	20p	PL83	8p	6/30L2	20p
EP50	60p per doz.				

#### REED COILS

3, 6, 9, 12, 24V Miniature 27p  
Small 27p  
Standard 34p

P & P. 7p on all orders.

#### REED PUSH BUTTON SWITCHES

Momentary Action  
1 contact £1-00  
2 contacts £1-25  
Illuminated 1 contact £1-30  
Illuminated 2 contacts £1-55

#### REED SWITCHES

Large range of many sizes, types and manufacture  
Popular types:  
E Small n/o 10 for 50p  
A Miniature n/o 24p each  
B Standard c/o 40p each

#### REED RELAYS

Many versions available, popular types: 3, 6, 9, 12, 24V  
Miniature 1/A normally open 56p  
Small 2/E 1 contact 36p  
2/EE 2 contacts 44p  
2/EEE 3 contacts 52p  
STD 3/B change over 87p

#### REELS OF ENAMELLED COPPER WIRE

20 s.w.g. to 47 s.w.g. 50, 100 & 200 grams. Send for prices

#### C.B.M. ELECTRONIC COMPONENTS LTD.

26 Avon Trading Estate, Avonmore Road, London, W.14

**'SOKSOL' DESOLDERING KIT:** Here is a kit that has really been worth waiting for. You make it up to your own exacting requirements, it desolders transistors, I.C.'s, wrap-round solder joints on switches, potentiometers, etc., etc. It is simple to use, just drop special braid in the supplied chemical solution, pull out and allow to dry. When ready to use just simply place braid on device to be desoldered. Put soldering iron on braid and the rest is sheer magic, as all solder is soaked up in seconds. Save yourself time in getting at those normally inaccessible solder joints. Highly recommended for service engineers in all walks of industry.

The kit includes 20 feet of special braid, chemical solution and full instructions £1-00, post 15p. Money back refund if dissatisfied.

Delco-Remy 12 Volt Car Horn Relays. Brand New 40p, post free.

Bargain Component Panels, contains I.C.'s, Thyristors, Transistors, Diodes, Trim-Pots etc. Don't miss this bargain. 5 assorted Panels £1-00, post 20p.

Bargain Component Panels, includes Resistors, Silver Mica, Polystyrene and Electrolytic Capacitors, Valve Holders, Rotary Switches, Transistor Panels. Plus a generous selection of other components. Fantastic value. 4lb nett weight £1-00, post 40p.

If after you purchase one of above parcels and you feel dissatisfied you may return goods and have your money back.

Flexible Connecting Wire Assorted Colours. 50 yards for only 50p.


## ELEKON ENTERPRISES

224a St Paul's Road, Highbury Corner, London N.1



# I.L.P. (Electronics) Ltd

## THE HY41

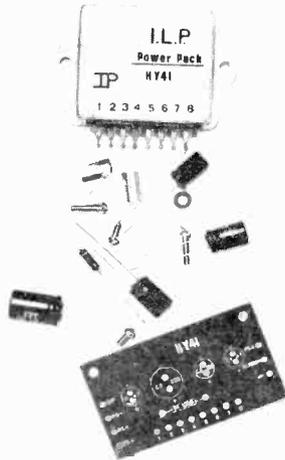

The HY41 supersedes the popular HY40 introduced by ILP last year. This highly improved module achieves true High Fidelity with a dramatic reduction in distortion (typically 0.05% at 1KHz into 8 ohms!) and is electronically and mechanically compatible with the HY40.

With this important improvement the HY41 retains all of the quality characteristics found in the earlier version and P.C. board, Resistor, Capacitors, Hardware Mountings and comprehensive manual are included in the basic kit. No further components are required to construct a complete power amplifier of extremely high performance sufficiently versatile to provide power not merely for Hi-Fi but also for public address systems and industry.

The free manual gives a full circuit diagram of the HY41 and its various applications including a complete stereo amplifier.

Like its predecessor the HY41 is based on conventional and proven circuit techniques developed over recent years.

**OUTPUT POWER:** British Rating 40 WATTS PEAK, 20 watts R.M.S. continuous.

**LOAD IMPEDANCE:** 4-16 ohms.

**INPUT IMPEDANCE:** 30K ohms at 1KHz.

**VOLTAGE GAIN:** 30db at 1KHz

**TOTAL HARMONIC DISTORTION:** less than 0.15% (typical 0.05%) at 1KHz.

**FREQUENCY RESPONSE:** 5Hz-50KHz  $\pm$  1db.

**SUPPLY VOLTAGE:** + 22.5volts D.C.

**SUPPLY CURRENT:** 0.8 amps maximum.

PRICE: inc. comprehensive manual, P.C. board, five extra components and P. & P.:-  
**MONO: £4.90**                      **STEREO: £9.80**

## UNIQUE HYBRID PRE-AMPLIFIER

The HY5 has rapidly established a position in the WORLD as the sole hybrid pre-amplifier to contain all feedback and equalization networks within an integrated pre-amplifier circuit.

Supplied with the HY5 are two stabilizing capacitors and by the addition of volume, treble and bass potentiometers it is ready for use.

Internally the HY5 provides equalization for almost every conceivable input, the desired function is achieved by use of a multi-way switch or by direct interconnection.

Two distinctive features of the HY5 are its inbuilt stabilization circuit, allowing it to be run off any unregulated power supply from 16-25 Volts and a balance circuit which, when linked by a balance control to a second HY5, forms a complete stereo pre-amplifier.

Specifically and critically designed to meet exacting Hi-Fi standards, the HY5 combines extremely low noise with a high overload capability. When used in conjunction with the HY41 and PSU45 forms a completely integrated system.

### INPUTS

Magnetic Pick-up (within  $\pm$ 1db RIAA curve)

2mV. 47K  $\Omega$

Tape Replay (external components to suit head).

4mV. 47K  $\Omega$

Microphone (flat) 10mV. 47K  $\Omega$

Ceramic Pick-up (equalized and compensatable) 20-2000mV. variable.

Tuner (flat) 250mV. 100K  $\Omega$

Auxiliary 1 250mV. 47K  $\Omega$

Auxiliary 2 2-20mV. 100K  $\Omega$

### OUTPUTS

Main Pre-amp output 500mV.

Direct tape output 120mV.

### ACTIVE TONE CONTROLS (Bexendall)

Treble  $\pm$  12db.

Bass  $\pm$  12db.

### INTERNAL STABILIZATION

Enables the HY5 to share an unregulated supply with the Power Amplifier.

### SUPPLY VOLTAGE

16-25 volts

PRICE: **MONO: £3.60**

**STEREO: £7.20**


### SUPPLY CURRENT

6mA approx.

### OVERLOAD CAPABILITY

better than 26db on most sensitive input infinite on tuner and aux1.

**OUTPUT NOISE VOLTAGE: 0.5mV.**

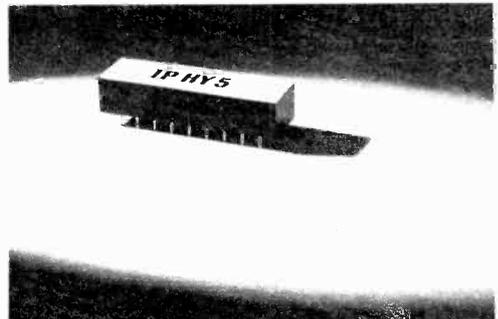

## POWER SUPPLY PSU45

The versatile P.S.U.45 is designed to supply your HY41's +HY5's in stereo or mono format.

### Specification

Input: 200-240 Volts.

Output:  $\pm$  22.5 Volts at 2 amps.

Overall Dimensions: L. 7"; D. 3.8"; H. 3.1"

PRICE: **£4.50 inc. P. & P.**



CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

# DISCOUNTS UP TO

# 60%

**Global's GOLDEN Guarantee**

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

**SPECIAL OFFER £17.95**

Garrard SP25 Mk. III  
Golding G800  
Teak plinth and tinted cover. All leads supplied.  
Please add £1.25 for P. & P.

## TURNTABLES

Please add 75p for P. & P.

Garrard SP25 Mk. III	£10.25
Garrard AP76	£17.75
Garrard SL65B	£12.65
Garrard 401	£26.00
Garrard Zero 100 (Auto)	£38.75
Garrard Zero 100 (Single)	£36.55
Garrard SL72B	£23.50
Garrard SL75B	£25.50
Garrard SL95B	£34.25
BSR MP60	£9.45
Golding GL72	£22.00
Golding GL72/P	£28.75
Golding GL75	£29.50
Golding GL75/P	£35.75
Golding 101/PC	£22.00
Wharfedale Linton & cart.	£27.95
Thorns TD125	£57.50
Thorns TD125AB	£92.00
Thorns TD150 Mk. II	£27.50
Thorns TD150A Mk. II	£33.50

## TUNERS

Please add 75p P. & P.

Amstrad Multiplex 3000	£28.75
Armstrong 523	£39.50
Armstrong 524	£30.95
Rogers Ravensbrook FET4 (Chassis)	£31.00
Rogers Ravensbrook FET4 (Cased)	£35.00
Rogers Ravensbourne FET4 (Chassis)	£43.00
Rogers Ravensbourne FET4 (Cased)	£48.00
Sinclair PRO60 (Module)	£16.50
Sinclair 2000/3000 Tuner	£31.95
Leak Delta FM (Cased)	£54.75
Leak Delta AM/FM (Cased)	£64.50
Alpha Highgate FT 150	£34.95

## TUNER/AMPLIFIERS

Please add 75p for P. & P.

Alpha Highgate 150	£44.25
Armstrong 525 (Teak cased)	£67.95
Armstrong 526 AM/FM (Teak cased)	£77.75
Leak Delta 75	£124.75
Philips RH761	£50.00
Philips RH702	£82.50
Teleton 2100	£29.95
Goodmans One Ten	£99.50
Rogers R/brook (Teak)	£78.50
Rogers R/brook (Chassis)	£72.75
Alpha FR 3000	£66.00

## AMPLIFIERS

Please add 75p P. & P.

Amstrad 8000 Mk. II	£16.25
Amstrad IC2000	£27.50
Amstrad Integra 4000	£21.95
Armstrong 521 (teak cased)	£43.95
Alpha Highgate 212	£24.95
Alpha Highgate FA300	£30.95
Alpha Highgate FA400	£31.95
Leak Delta 30	£48.75
Leak Delta 70	£57.95
Metrosound ST20E	£24.45
Metrosound ST60	£45.95
Pioneer SA1000	£94.00
Rogers R/brook (Chassis)	£35.00
Rogers R/brook (Cased)	£37.00
Rogers R/bourne (Chassis)	£41.95
Rogers R/bourne (Cased)	£47.50
Sinclair PRO60 2 x Z30/PZ5	£14.95
Sinclair PRO60 2 x Z30/PZ6	£17.00
Sinclair PRO60 2 x Z50/PZ8/Trans	£21.50
Sinclair AFU (Filter Unit)	£4.40
Sinclair 605	£18.50
Sinclair 2000 Mk. II	£21.50
Sinclair 3000 Mk. II	£29.50
Wharfedale Linton	£37.50
Goodmans Max Amp	£37.95
Teleton SAQ307	£22.50
Rotel RA 210	£24.50
Rotel RA 310	£31.00
Rotel RA 610	£48.50

## SPEAKERS

Please add £1.25 P. & P. per pair

Amstrad 138	£15.95
Wharfedale Denton 2	£28.30
Wharfedale Linton 2	£35.90
Wharfedale Melton 2	£47.25
Wharfedale Dovedale 3	£59.50
Celestion Ditton 120	£37.45
Celestion Ditton 15	£52.00
Celestion Ditton 25	£87.00
Wharfedale Linton	£37.95
Celestion County (new prod.)	£55.95
Goodmans Double Maxim	£48.25
Goodmans Mezzo 3	£44.95
Goodmans Magister	£74.00
Sinclair Q16	£12.50

£3.20



Plus 35p p. & p.  
Finished in teak veneer with tinted dust cover fully assembled. For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for BSR McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B; £4.20 plus 55p P. & P.  
Also finished in walnut to match Japanese equipment—at no extra.

## CARTRIDGES

Please add 10p for P. & P.

Golding G850	£3.25
Golding G800	£5.75
Golding G800E	£8.50
Golding G800 Super E	£14.35
Shure M3D	£3.95
Shure M44E	£5.65
Shure M55E	£5.85
Shure M75E Type 2	£10.35
Sonotone 9TAHC	£1.75

# SOUND BARGAINS



**BEST OF ALL WORLDS**  
VHF, FM, AM, AFC, AIR BAND, PUBLIC SERVICE AND WEATHER BANDS

**GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER**

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM  
MAINS/BATTERY plus BUILT-IN BATTERY BOSTER

**£10.50 40p. P. & P.**

BATTERY CHECK INDICATOR

OUR PRICE **£28.95** + 50p P. & P.



**8 WAVE BANDS AND WORLD MAP & TIME ZONE DIAL**

Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240 volt domestic mains supply.  
14 Transistors; 9 diodes; 1 thermister. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVE BANDS. Complete with Hi-Fi earphone for personal listening.  
Frequency ranges: Long wave 150-350Kcs. Medium 353-1605Kcs. Marine 1.6-4.5Mc. Short Wave 12-24Mc. FM/VHF 88-108Mc. Aircraft 108-135Mc. PUBLIC SERVICE BANDS 135-174Mc. Fully guaranteed.

N.B. The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

**MARKTYME**

(DEPT. 46 372 EDOWARE ROAD, LONDON, W2 Tel. 01-723 0094. Callers welcome Monday to Saturday 9 a.m. to 6 p.m.)

# Train for television

Course commences 3rd January, 1973

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name \_\_\_\_\_

Address \_\_\_\_\_

**THE PEMBRIDGE COLLEGE OF ELECTRONICS**

(Dept. PW13 34a Hereford Rd., London W2 5AJ)



All prices correct at time of press E. & O.E.

**GLOBAL AUDIO DISCOUNT WAREHOUSES**

Dept. PW13 174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. **LATE NIGHT FRIDAY 7 p.m.**

**MAIL ORDERS:** Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

# SAXON ENTERTAINMENTS.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT  
NEW & SECONDHAND MUSICAL INSTRUMENTS. MAIN  
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

## SA25-SA35-SA100

LOW-PRICED AUDIO MODULES  
FOR DOMESTIC & COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

**SA25 £2.95** carr. free

25 WATTS RMS. 7 transistors 7 diodes

**SA35 £4.45** carr. free

35 WATTS RMS. 7 transistors 7 diodes

**SA100 £10.90** carr. free

100 WATTS RMS. 11 transistors 6 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE.

### BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000 Hz $\pm$ 1dB
Distortion	0.2% at 1 kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	25-45 volts SA25/35 40-70 volts SA100
Size	4 1/2" x 4" x 1" (SA100) 4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

### POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

Stab PS45	Stabilized module for 2 SA25's or two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3.50 carr. 20p
PU70	Unstabilized supply for one or two SA100	£8.75 carr. 40p
PS70	Stabilized supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON  
GLASS FIBRE P.C. BOARD

## OTHER SAXON PRODUCTS...

**120 WATT HEAVY DUTY MODULE** £13.90 + 20p carr. or with supply  
£18.95 + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

### SPECIFICATION


Power output 120 watts into 8 ohms  
Freq. response 30-30,000 HZ  $\pm$  2dB  
Input sensitivity 200 mV into 10K  
Construction Fibreglass board  
Size 8" x 4" x 4" (5" with supply)  
Low distortion parallel push-pull output stage.


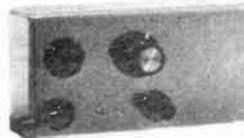
### SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mis-range notes by the addition of components costing less than 5p.



**£8.90** carr. free

### THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000 watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough white steel case with a blue stielvette hooded cover. Fully guaranteed.

**£19.75** carr. 30p

### SAXON STEREO CONTROL UNIT




**£15.80** carr. 30p  
MONO VERSION  
£8.50 carr. 20p

(As illustrated left S.A.E. details 9 volt operation)  
Outputs up to 1 volt RMS

Two decks, and full headphones monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.

### COMPLETE AMPLIFIERS

**The CSE 100. £34.90 carr. free**

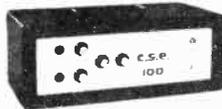

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous sine wave outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.S., etc.

**The SAXON 100 £48.50 carr. free**



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

### LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £4.95 carr. 30p. 15" 50W.8/15 ohm £14.50 carr. 50p.  
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p.  
A.K.G. microphones suitable for disco, group or general P.A. use.  
D11DHL rrp £11.00 our price £9.45 post free  
D1900C High Z rrp £21.50 our price £17.45 post free  
D1000C 24 ct gold plate rrp £37.00 our price £32.00 post free

SEND SAE FOR  
OUR AKG PRICE  
LIST. DISCOUNTS  
ON ALL MICS.

### CALLERS & MAIL ORDER:

327-331 Whitehorse Rd.,  
West Croydon, Surrey.  
CRO 2HS 01-684 8385

### CALLERS ONLY:

6a Deice Rd., Rochester,  
Kent. Medway 404199

### BUSINESS HOURS:

9.30 a.m.  
to 5.30 p.m.

### TERMS OF BUSINESS:

C.W.O. or C.O.D. (35p extra)  
All cash in regd. envelopes please!  
Telephone orders to our CROYDON BRANCH.  
TRADE & EXPORT enquiries invited.

# COMET HI-FI discount warehouses



## NEW LOW PRICES

	Rec. Retail Price	Comet Price
<b>STEREO AMPLIFIERS</b>		
ALBA UA 700	37-93	24-95
ALPHA 212 by Highgate	37-75	25-95
AMSTRAD Stereo 8000 Mk 2	27-95	14-50
AMSTRAD I.C. 2000	42-85	27-95
DULCI 207M	59-00	44-95
FERROGRAPH 5307 Mk. II (cased)	64-00	45-95
GOODMANS Maxamp	54-00	34-95
H.L. Audio Phoenix 707	29-00	15-95
JVC Nivico MCA 104Z	85-00	70-95
MCA 105E	130-50	109-95
MCA VSE Quadraphonic	89-00	74-95
MCA VSE Quadraphonic	148-00	124-95
LEAK Delta 30 (cased)	69-90	46-95
LEAK Delta 70 (cased)	85-90	57-95
METROSOUND ST20E	39-50	28-95
METROSOUND ST60	70-00	46-95
PHILIPS RH501	79-00	54-95
PHILIPS RH500	52-00	36-50
PHILIPS RH580	29-00	20-50
PIONEER SA500A	47-10	32-95
PIONEER SA600	95-48	61-95
PIONEER SA800	126-55	79-95
PIONEER SA900	133-83	86-95
PIONEER SA1000	155-82	99-95
PIONEER QL600 Quadraphonic converter	76-50	49-50
QD 210 Quadraphonic decoder	42-85	29-50
QA 800 Quadraphonic	188-60	122-95
QC 800 Quadraphonic pre-amp.	129-98	84-95
QM 800 Quadraphonic pow. amp.	160-84	104-95
Reverberation 202W	54-95	35-95
RANK Rotel 210	34-90	23-95
RANK Rotel 310	47-50	31-95
RANK Rotel 610	74-50	48-95
ROGERS Ravensbourne	64-50	49-95
ROGERS Ravensbourne (cased)	69-50	53-95
ROGERS Ravensbrook Mk. II	59-50	38-95
ROGERS Ravensbrook (cased) Mk. II	55-50	42-95
SINCLAIR 2000	35-00	23-50
3000	45-00	29-50
Project 80/2 x Z30/PZ5	23-90	15-95
Project 80/2 x Z50/PZ8/trans	34-86	21-95
Project 805	29-85	18-90
AFU	5-98	4-50
SOLARVOX AM108 2 x 8 watts.		
RMS plus MATRIX 4 channel	28-45	19-95
SOLARVOX AM318 2 x 18 watts.		
plus MATRIX 4 channel	41-38	28-95
TANDBERG TA300	69-90	54-95
TELETON SAQ 206B	33-00	19-50
307	33-00	20-50
GA202 15 watt RMS Per Chan.	45-75	28-95
WHARFEDALE Linton Amplifier	65-00	41-95
All take both ceramic and magnetic cartridges.		
<b>TUNERS</b>		
AMSTRAD Multiplex 3000 FM	36-50	27-95
*ARMSTRONG 523 AM/FM	52-68	40-95
*ARMSTRONG 524 FM	40-97	31-95
ARMSTRONG M8 Decoder	9-50	6-95
*DULCI FMT 7	24-43	17-50
*DULCI FMT S Stereo	32-99	24-50
GOODMANS Stereomax	75-74	46-95
JVC Nivico		
MCT VSE AM/FM Quadraphonic	86-89	69-95
MCT V7E AM/FM Quadraphonic	122-42	99-95
LEAK Delta 30 AM/FM	79-50	57-95
LEAK Delta 70 AM/FM	89-50	69-95
PHILIPS RH 690	44-15	29-95
PIONEER TX500A AM/FM	75-52	52-95
PIONEER TX600 AM/FM	104-57	73-95
RANK ROTEL 320	53-38	38-50
RANK ROTEL 620	86-33	63-95
ROGERS Ravensbourne chassis	57-95	43-95
ROGERS Ravensbourne in teak case	62-63	47-95
ROGERS Ravensbrook chassis	42-14	31-95
ROGERS Ravensbrook (cased)	48-00	36-95
SINCLAIR 2000	45-00	29-95
SINCLAIR 3000	45-00	29-95
SINCLAIR Project 60 tuner (stereo)	25-00	17-50
TELETON GT202	46-75	30-95
All above Tuners are complete with MPX Stereo Decoder except where starred.		
<b>TUNER AMPLIFIERS</b>		
AKAI CR80T AM/FM Tuner Amplifier with built in Eight Track Tape Recorder	149-84	89-95
AKAI AA 8500	228-34	175-00
AKAI 6800	145-26	109-00
AKAI 6300	128-83	94-95
AKAI 6200	97-09	74-95
ARENA 2600	111-30	59-95
ARMSTRONG M8 Decoder	9-50	6-95
ARMSTRONG 525	90-14	69-95
ARMSTRONG 526	102-72	77-95
CARLTON M4000 AM/FM with 8 track player and speakers	69-95	39-95
GOODMANS Module 80, 35w. RMS	89-02	67-95
GOODMANS Module 80 Compact	160-38	122-95
GOODMANS Module 110 FM/MW/LW/SW 100w RMS	131-22	99-95
JVC Nivico VR 5501 AM/FM	96-96	61-95
JVC Nivico M4000 AM/FM	175-15	146-95
VR 5521L AM/FM and SW	212-00	179-95
4VR 5414 Quadraphonic	175-00	129-95
LEAK Delta 75	49-56	36-75

	Rec. Retail Price	Comet Price
<b>TUNER/AMPLIFIERS—continued</b>		
PHILIPS RH 700	134-00	74-95
PIONEER SX525	140-53	98-95
SX626	192-49	134-35
SX727	231-74	162-95
SX828	297-20	208-95
OX3000 Quadraphonic	286-24	199-95
ROGERS Ravensbrook Chassis	98-57	73-95
ROGERS Ravensbrook (cased)	105-35	79-95
ROTEL RX200	89-02	64-95
ROTEL RX150	67-93	48-95
SOLARVOX TAM1105 2 x 8 watts RMS AM/FM Multiplex comp. with 2 speakers and featuring Matrix 4 channel	38-50	28-95
TANDBERG 1171 MPX	103-03	64-95
TANDBERG TR200 MPX	106-00	87-95
TANDBERG TR1000 FM MPX (teak)	156-00	129-60
TELETON F2000	51-50	27-25
TELETON CR55	125-26	88-50
TELETON R3000 AM/FM	42-16	21-95
All the above take magnetic cartridges except Teleton F2000 and 8000 which take ceramic only. All include MPX Stereo Decoder with the exception of Armstrong where M8 decoder is extra.		
<b>TURNTABLES</b>		
GARRARD SP25 Mk III	16-17	10-50
GARRARD SL65B	20-93	13-95
GARRARD SL95B	49-21	32-95
GARRARD 401	39-04	27-95
GARRARD 720P	32-60	21-95
GARRARD Zero 100A	57-42	40-95
GARRARD Zero 100S	52-83	38-50
GARRARD W84 base Mk II/2 to fit Zero 100 & Zero 100S.	6-55	4-95
The following Turntables are complete with base, plinth, perspex cover and cartridge. Fully wired and ready for use. All at special prices.		
GARRARD SP25 Mk III with Goldring G800	Special Price £18-50	
MCDONALD MP60 with Goldring G800	Special Price £18-50	
MCDONALD MP60 with SHURE M 44/7	Special Price £19-50	
MCDONALD MP60 with SHURE M 44/E	Special Price £20-25	
GARRARD AP76 with Goldring G800	Special Price £28-25	
GARRARD AP76 with Shure M5E	Special Price £30-95	
GARRARD AP76 with Shure M7EJ	Special Price £32-95	
GARRARD 2025 with Sonotone STAHC	Special Price £12-95	
GOLDRING GL75 with G800	Special Price £38-95	
THORENS 150 AB with TX11 cover	£60-35 £49-95	
Shure M55E cartridge		
<b>Base and Cover to fit GARRARD</b>		
SP25, SL55, SL65B	Spec. Price £3-60	
GARRARD 40B	13-63	10-95
GARRARD AP76	28-44	17-95
GOLDRING GL69 MKII	26-86	18-50
GL69P Mk. II	35-23	25-95
GL75	41-86	28-50
GL75P	51-62	35-50
Covers for 72P	4-71	3-25
Cover for 75P Deluxe	5-23	3-60
Cover for 85P	6-98	4-95
C99—plinth and cover for G99	15-35	11-95
GOLDRING G99	29-64	19-95
GOLDRING G101P/C	29-64	20-50
GOLDRING GL72 Chassis	31-39	21-75
GOLDRING GL72P	40-81	27-95
GOLDRING GL85P	61-03	41-95
GOLDRING GL85P	70-80	48-95
GOLDRING GL85P/Cover	87-19	59-95
LEAK Delta	69-50	52-50
JVC Nivico SRP 473 Quadraphonic, including plinth and cover	69-50	58-95
MCDONALD MP60	14-78	9-95
610	18-75	12-95
HT70	20-63	14-50
HT70 Inc. plinth and cover	29-84	20-95
Base and Cover for MP60 and 610	Spec. Price £3-95	
PHILIPS 202 Electronic	64-65	49-50
PHILIPS 308 transcription unit complete with base and cover	36-55	28-50
PHILIPS GA 105 with base, cover and cartridge	20-00	13-95
PIONEER PL12AC with base & cover	47-86	33-95
THORENS TX25 cover	8-85	6-95
THORENS TD125	76-73	59-95
THORENS TD125 Mk. II	82-63	66-95
THORENS TD125AB	115-69	89-95
THORENS TD 125AB Mk. II with TP 16 arm	124-54	99-95
THORENS TD150 Mk. II	36-30	28-95
THORENS TD150A Mk. II	46-33	36-95
THORENS TD150AB Mk. II	50-17	39-95
THORENS TX11 Cover	4-49	3-60
WHARFEDALE Linton with base and cover and Shure M44-7 cartridge	37-50	26-95

	Rec. Retail Price	Comet Price
<b>SPEAKERS</b>		
AMSTRAD 138 (pair) 13" x 8" twin cone teak	28-00	13-95
AKAI SW 155	59-50	41-50
B & W Model 70	159-50	111-95
B & W DM2	80-76	46-95
B & W DM3	63-00	45-50
B & W DM1 (pair)	75-20	57-25
CELESTION County	23-97	18-50
CELESTION Dilton 120 (pair)	56-40	41-80
CELESTION Dilton 25	37-40	27-95
CELESTION Dilton 45	69-00	46-50
CELESTION Dilton 44	54-00	38-95
CELESTION Dilton 66	99-00	70-95
FERROGRAPH S1 Inc. stand	95-00	69-95
GOODMANS Havant (pair)	54-42	38-95
GOODMANS Minitar (pair)	50-62	35-95
GOODMANS Magister	65-63	44-95
GOODMANS Double Maxim	32-07	24-50
GOODMANS Mezzo 3	35-70	23-95
GOODMANS Magnum K2	46-20	28-95
GOODMANS Dimension 8	72-44	48-95
GOODMANS DIN 20NT kit	12-19	8-50
KELETRON KN400 2-speaker System (pair)	15-86	11-95
KN600 3-speaker System (pair)	26-46	17-50
KN800 3-speaker System	15-90	9-95
KN1100 4-speaker System	20-40	12-95
KN1600 3-speaker System	25-20	15-95
KN2100 3-speaker System	30-60	19-95
LEAK 150 (pair)	50-00	36-95
LEAK 250 (pair)	63-00	46-95
LEAK 800	49-50	33-95
LINEAR 10 watt teak (pair)	Sp. Price	13-50
METROSOUND HFS 103 (pair)	29-21	20-95
METROSOUND 202	21-08	17-75
METROSOUND Duplex 15	32-00	21-95
METROSOUND Duplex 25	56-00	37-95
PIONEER CS33	46-72	29-95
SINCLAIR G18	6-98	6-50
STE-M 450	25-00	16-95
TANDBERG TAN 7	29-50	24-50
TANDBERG Tan 11 (pair)	40-00	33-25
TANDBERG Tan 12 teak (pair)	44-00	36-75
TANDBERG Tan 25 teak (pair)	71-50	59-50
TANDBERG Tan 50 teak	68-00	52-95
TELETON 8000 (pair)	21-08	17-75
THORPE Grenville TG 100 (pair)	28-95	11-95
Grenville TG 200 (pair)	41-95	25-95
Grenville TG 300 (pair)	55-95	31-95
<b>WHARFEDALE</b>		
Denton Mark II (pair)	42-00	27-95
Denton Mark II (pair)	52-00	36-95
Melton Mark II	35-00	23-95
Dovedale 3 Mark II	47-50	31-95
Rosedale	69-00	46-95
Trilton III (pair)	65-00	46-95
Unit 3 Speaker Kit	12-50	8-95
Unit 4 Speaker Kit	19-00	12-95
Unit 5 Speaker Kit	27-50	18-75
<b>CHASSIS SPEAKERS</b>		
GOODMANS Twin-Axion 8	8-85	6-95
Axion 10	9-58	7-50
Axion 401	17-68	11-95
Audiom 8P	5-20	4-15
Audiom 10P	5-67	4-50
Audiom 12P	13-00	9-25
Audiom 15P	21-00	14-95
Audiom 18P	26-70	24-95
Audiom 100 40 watts DIN	48-50	34-50
ARU 172	4-50	3-20
Axiem 100	6-90	4-90
Midxax 650	13-59	9-50
Attenuator	3-73	2-70
Crossover Network XO/950	7-77	5-45
WHARFEDALE 8L Bronze/RS/DD	4-75	3-40
Super 8/RS/DD	8-50	6-25
Super 10/RS/DD	14-00	9-95
<b>CARTRIDGES</b>		
AMSTRAD 900C	4-95	3-50
AMSTRAD 900D	7-50	5-50
AMSTRAD 900 EX	11-00	8-75
AUDIO TECHNICA AT66	6-47	3-60
GOLDRING G850	6-10	3-30
GOLDRING G800	12-00	8-95
GOLDRING G300E	12-21	4-75
GOLDRING G800 Super E	24-41	15-95
*GOLDRING CS90 Stereo	4-88	3-95
*GOLDRING CS91/E	7-33	5-50
EMPIRE 10002E/X	59-12	44-95
EMPIRE 999VE/X	42-14	32-50
EMPIRE 999TE/X	24-18	15-95
EMPIRE 999SE/X	19-90	15-25
EMPIRE 999E/X	15-57	11-70
EMPIRE 909E/X	12-12	9-25
EMPIRE 909E/X	9-37	7-15
ORTOPON M15E	27-60	22-75
SHURE M33M	6-10	4-50
SHURE M31E	11-63	6-95
SHURE M32E	10-73	6-50
SHURE M44-G	6-50	4-95
SHURE M44-7	7-90	4-90
SHURE M44C	7-90	4-90
SHURE M44E	8-60	5-25
SHURE M55E	8-70	5-95

# OVER 1000 ITEMS ALWAYS IN STOCK

All items brand new and fully Guaranteed and backed by after-sales service

— latest models in manufacturers' sealed cartons



## COMET for after-Sales Service THROUGHOUT THE U.K.

Pictured: Service Dept at Cleugh Rd., Hull, also at Birmingham, Bridlington, Doncaster, Edinburgh, Galashiels, Leeds, Luton, Newcastle, Rochdale, Sheffield, Stockton, Wakefield and York.

CARTRIDGES—continued	Rec. Price	Comet Price
SHURE M75-6	13.60	7.90
SHURE M75EJ	15.40	9.25
SHURE M75E	19.00	11.50
SHURE M75 ED	19.00	11.50
SHURE M75E/95G	20.80	12.95
SHURE V15-11	39.40	27.95
*SONOTONE 8TACH Diam/Saph.	3.75	1.45

### BASES AND COVERS

GARRARD WB1 Base	3.78	2.95
WB4 Base	5.60	4.25
SPC1 Cover	3.68	2.75
SPC4 Cover	4.38	3.25

Special offer of Base and Cover to fit SP25, SL55, SL65B and 3500	Special Price	3.60
WB4 base Mk II/2 to fit Zero 100 and Zero 100S	6.55	4.80
GOLDRING Plinth 75	4.77	6.75
GOLDRING Plinth 72	9.42	6.50
GOLDRING Covers for 72P	4.71	3.25
Cover for 75P De Luxe	5.23	3.60
Cover for 85P	6.98	4.95
THORENS TX25 (for TD125AB)	9.85	6.95
THORENS TX11 Cover	4.49	3.60
SME Plinth System 2000 with motor-board	46.20	34.50
MOTORBOARDS only	5.85	4.45
SME P1 Spacer	0.98	0.75

### BLANK TAPES

SCOTCH DYNARANGE CASSETTES		
C60	0.71	0.40
C90	0.99	0.50
C120	1.49	0.75

SCOTCH HIGH ENERGY COBALT CASSETTES		
C60	0.85	0.65
C90	1.45	0.85

SCOTCH Low Noise 8-TRACK BLANK CARTRIDGES		
40 mins	1.50	0.90
80 mins	1.80	1.10

SCOTCH LONG LIFE SPOOLED TAPES		
5" L.P. 900	7.11	0.85
57" L.P. 1200	1.76	1.10
7" L.P. 1800	2.52	1.50

SCOTCH HI-FI DYNARANGE SPOOLED TAPES		
57" L.P. 1200	2.20	1.30
7" L.P. 1800	2.95	1.80

Postage—Tapes, cassettes and 8T cartridges 1-9 items 5p per order. Packs of ten post free.

### MANUFACTURERS' HI-FI STEREO SYSTEMS COMPLETE

ALBA UA552	47.75	29.95
BUSH A1005	69.89	53.25
DANSETTE Consort Stereo	34.43	24.95
DANSETTE 4005	71.45	53.25
DECCA Sound 613	Special Price	47.95
DECCA Sound 614	Special Price	52.95
DECCA Sound 1204	Special Price	70.95
DECCA Compact 2	Special Price	76.95
DECCA Compact 3	Special Price	99.95
DECCA 403	Special Price	44.95
ELIZABETHAN LZ101	58.33	41.85
FERGUSON 3425	136.35	102.75
FERGUSON 3430 with Radio	74.20	55.95
FERGUSON 3451 with Radio	101.70	79.95
FIDELITY UA2 Music Master	43.50	30.95
UA1 Music Master with Radio	100.00	69.95
Stereo Nine	38.50	22.50
GOODMANS Module 80 compact system FM/35 watts. RMS (Less L/S)	165.00	125.75
HMV 2450 with Stereo Radio	138.00	106.95
HMV 2451	122.00	95.95
HMV 2452	66.00	49.95
KB1025 with 657 speakers	48.25	37.95
KB 2250 with 658 speakers	124.00	95.95
KB 2010 with 658 speakers	101.50	77.95
MARCONI 4452	77.00	56.95
MCDONALD MP60 complete with base, cover and Goldring G800 cartridge, Amstrad IC 2000 amplifier, 2 Wharfedale Denton speakers	114.96	74.40
MURPHY 902 Studio 1, AM/VHF Radio	84.50	64.95
MURPHY 903	84.42	64.95
PHILCO FORD M1500	97.96	66.75
PHILIPS 808	105.00	71.95
PHILIPS GF824	65.30	49.65
PHILIPS 825	49.50	38.95
PHILIPS 826	65.00	52.95
PHILIPS 835	79.50	49.55

HI-FI STEREO SYSTEMS—Rec. Retail Comet continued	Price	Price
PHILIPS 836	95.00	69.95
PYE Black Box unit stereo 1022	90.93	68.95
RIGONDA Parly Time	27.50	19.95
STEEPLETONE stereo system	41.75	25.95
TELETON STP 8 track stereo system	57.50	38.95
TELETON R 8000 Tuner/Amplifier with stereo decoder, Garrard 2025 TC turntable and one pair of Teleton 8000 speakers	87.95	47.80
ULTRA 6028	59.95	45.95
ULTRA 6450	74.20	57.95
ULTRA 6454	38.85	28.95
ULTRA 6455	41.35	31.95

Full range of Headphones, Pick Up Arms & Heads available at discounted prices.

TAPE RECORDERS AND TAPE DECKS	Rec. Price	Comet Price
AKAI 1720L 4-track Stereo	87.36	59.95
AKAI 4000D 4-track stereo deck	93.65	64.95
AKAI CR80D 8-track stereo tape deck	85.02	58.45
AKAI CR80 8-track stereo recorder	106.39	74.00
AKAI CR80T 8-track stereo recorder and tuner/amplifier	149.84	89.95
AKAI X800D	157.93	100.45
AKAI GX220D	223.00	164.95
AKAI 1800SD	162.79	102.30
AKAI 2000SD	289.07	223.30
BSR TD8S 8-track deck	23.58	18.95
FERGUSON 3247 4-track	47.95	34.95
FERGUSON 3248 4-track	53.75	38.95
FERGUSON 3252 4-track	98.00	74.95
FERGUSON 3258 4-track	70.45	51.95
FERROGRAPH 702/4 Dolby	264.38	224.50
FERROGRAPH 702H Dolby	274.95	233.50
FERROGRAPH 722/4 Dolby	301.98	255.95
FERROGRAPH 722H Dolby	312.55	264.95
FERROGRAPH 702/2 track tape deck	224.43	170.85
FERROGRAPH 704/MW 4-track deck	224.43	170.85
FERROGRAPH TK 148 (4-track auto 2 speed)	262.03	190.15
FERROGRAPH 724	262.03	190.15
FIDELITY BRAEMAR 4-track	34.75	19.95
GRUNDIG TK 121 twin track	56.25	38.95
GRUNDIG TK 141 4-track	62.10	44.95
GRUNDIG TK 146 4-track Auto	66.95	48.95
GRUNDIG TK 147 4-track Auto	98.65	74.95
GRUNDIG TK 148 (4-track auto 2 speed)	74.10	56.95
PHILIPS 4303 Twin-track	39.46	24.95
4307 4-track	50.00	35.95
4308 De Luxe 4-track	59.00	42.95
4404 4-track stereo recorder	89.25	65.95
4407 4-track stereo recorder	108.50	73.95

TAPE RECORDERS—continued	Rec. Price	Comet Price
4418 4-track stereo	189.75	129.00
4450 4-track stereo	295.00	229.00
4500 4-track stereo tape deck	124.30	91.65
TANDBERG 2041 4-track (Stereo)	130.00	108.50
TANDBERG 1841 4-track stereo deck	66.00	49.95
TANDBERG 3021X twin track stereo	113.00	89.95
TANDBERG 3041X 4-track stereo	113.00	89.95
TANDBERG 4021X twin track stereo	179.00	145.95
TANDBERG 4041X 4-track stereo	179.00	145.95
TANDBERG 6041X 4-track stereo	199.30	159.95
TANDBERG 6021X twin track stereo	199.30	159.95

### TAPE RECORDERS (CASSETTE)

AKAI CS 50 recorder	125.83	92.95
AKAI CS 50D Deck	104.46	77.95
AKAI GX 40D Tape Deck	295.00	229.00
AKAI GX 40 Recorder	111.75	83.85
APCO Batt./Mains with AM/FM Radio	35.00	22.95
BUSH Discassette DC70	20.62	15.95
BUSH TP60	27.62	15.95
BUSH TP 66 Batt./Mains	28.18	21.50
BUSH TP 70 battery/mains	34.26	19.95
CANTONE LCR500	Sp. Price	11.95
DANSETTE DC105	20.62	14.50
DECCA 2000 (batt./mains)	Sp. Price	22.95
DECCA CR1000 with VHF Radio	Sp. Price	32.95
EKCO 350 Bt./Mns. VHF/MW Radio	37.42	28.75
EKCO 351 Battery/Mains	23.23	18.45
FERGUSON 3240 with case	24.90	15.95
FERGUSON 3253	43.55	31.95
FERGUSON 3262 Battery/Mains	30.15	22.95
GRUNDIG C200 De Luxe	37.55	26.95
GRUNDIG C210 batt./mains	48.75	36.95
GRUNDIG C410	41.55	29.95
HARVARD Elite with AM/FM radio batt./mains	42.00	23.95
JVC NIVICO 9420 L/S with AM/FM radio batt./mains	61.45	42.95
PHILIPS R.R. 392 with MW/VHF Radio Cassette	49.95	36.55
2202	22.85	17.95
2204 battery/mains	29.10	23.95
3302	21.50	15.95
2400 stereo less L/S	66.10	51.95
PYE 9109	20.37	14.95
PYE 9116 Stereo	66.10	49.95
PYE 9118	29.11	22.95
TELETON TRC 130 with VHF/AM radio battery/mains	42.50	28.00
TC110 battery/mains	27.50	18.50
STC 105 Stereo Deck	46.45	30.95

## COMPLETE HI-FI SYSTEMS

AMSTRAD 8000 Mk II amplifier 7 watts. RMS per channel, McDonald MP60 turntable with plinth, cover and Goldring G800 magnetic cartridge, fully wired, and 2 Amstrad 138 twin cone teak speakers. 86.96 48.95

SOLARVOX TAM 1105 2 x 5 watts. RMS output. AM/FM Multiplex Tuner/Amplifier plus Matrix 4 channel, McDonald MP60 deck with plinth, cover and Shure M44/7 cartridge, plus two Solarvox speakers. 67.20 49.45

H.L. Audio Phoenix 707 amp. McDonald MP60 turntable with plinth, cover and Shure M44/7 cartridge. Fully wired plus 2 Thorpe Grenville 100 loudspeakers. 86.65 53.40

CARLTON M4000 AM/FM tuner amp. with 8 track stereo player, 2 speakers, Garrard 2025/TC turntable, base, cover and Sonotone 9TACH cartridge. Sp. Price 52.90

SINCLAIR 2000 amp. with McDonald M960 turntable, plinth, cover and Shure M44/7 plus 2 Sinclair Q16 loudspeakers. 81.66 58.00

ROTEL RA210 amplifier with McDonald MP60, base cover and Goldring G800 magnetic cartridge. Plus two Linear 10 watts. Speakers (Teak). 88.91 56.40

METRO SOUND ST20E. amp. 10 watts RMS per channel, with McDonald MP60, plinth cover and Goldring G800 cartridge, plus 2 Metro sound HFS103 Speakers. 101.72 68.40

Completely wired mounted and ready for use

TELETON 206B amp. with McDonald MP60 turntable, plinth, cover and Shure M44-7 cartridge. Plus two Wharfedale Denton Mk II speakers. 103.70 66.95

SOLARVOX AM108 2 x 8 watts RMS output plus Matrix 4 channel amplifier, McDonald MP60 deck plinth and cover with Shure 44/7 Cartridge and four Amstrad 138 Speakers. 109.15 67.35

AMSTRAD IC2000 integrated circuit amp. 20 watts per channel, with McDonald MP60 turntable, plinth, cover and Goldring G800 cartridge. Plus two Wharfedale Denton Mk II speakers. 117.96 74.40

TELETON F307 amp. with McDonald MP60 turntable, plinth, cover and Shure M44-7 cartridge. Plus 2 x Goodmans Minister speakers. 112.32 75.95

SINCLAIR 3000 amplifier, with McDonald MP60 turntable, plinth, cover and Shure M44-E cartridge. Plus two Thorpe-Grenville 200 speakers. 116.35 75.70

PIONEER SA500A amp. with McDonald MP60 turntable, plinth, cover and Shure M44-E cartridge. Plus two Wharfedale Denton speakers. 118.50 81.15

TELETON GA202 amplifier, 15 watts. per channel, RMS with McDonald MP60 turntable, plinth, cover and Shure M44-E cartridge, plus two Wharfedale Linton Mk II speakers. 124.15 86.15

FREE Technical Advisory Service. If in doubt ask us! Price list on request. Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue is closed for press. Add 5p for postage, packing and insurance on all orders (Cartridges 20p) OR, IF SECURICOR DELIVERY REQUIRED ADD £1.75 ONLY. Make cheques, Money Orders payable to 'COMET'.

# COMET HIGH FIDELITY DISTANCE WAREHOUSES

OPEN DAILY TO THE PUBLIC FROM:  
9am-5pm Monday  
9am-10pm Tuesday  
9am-8pm Wednesday  
9am-8pm Thursday  
9am-9pm Friday  
9am-5.30pm Saturday

Dept. PW BIRMINGHAM: Heeley Road, Selly Oak B29 6EY. Tel.: 021-472 6181.  
Dept. PW BIRMINGHAM: Tivoli Shopping Centre, 1570-1572 Coventry Road, Yardley, B26 1BJ Tel.: 021-706 0684.  
Dept. PW EDINBURGH: 1 Newhaven Road EH6 5QX. Tel.: 554 8501 (5 lines).  
Dept. PW HULL: Reservoir Road, Clough Road HU6 7QD. Tel.: 46441 (6 lines).  
Dept. PW LEEDS: 78 Armlay Road LS12 2EF. Tel.: Leeds 40551 (10 lines).  
Dept. PW STOCKTON: Teesway, Portrack Lane, Teesside TS18 2RH. Tel.: 66132/65215.  
Dept. PW ROCHESTER: Corner of Well 1/1th Lane and Queensway. Tel.: 50606.  
Dept. PW LEICESTER: Syston Street. Tel.: 0533 52236.  
Dept. PW SHEFFIELD: The Mill, 1 Loxley Rd., Malin Bridge, S6 4TN. Tel.: 0742 341721/6.  
Dept. PW WIGAN: Warfe Mill, Princess St., WM3 4EZ


**SECURICOR**  
SPECIAL DELIVERY SERVICE  
All in-stock items delivered by SECURICOR within 72 hours. (Add £1.75 only for service delivery). ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILST IN TRANSIT

# The *Litesold* CONQUEROR

An outstandingly simple and efficient new soldering tool, featuring a fully enclosed element and slip-on bits which can't seize. Five tip sizes available,  $\frac{1}{16}$  in to  $\frac{1}{4}$  in, covering most work with one iron only. Lighter and slimmer than comparable irons, and with better performance. A pleasure to use and excellent value. Mains or low voltages. Conqueror spring stand gives complete safety and convenience, and holds spare bits.

Note that we are now supplying a range of small pliers, cutters, soldering aids and other small tools for use in Electronics.

Please ask for leaflet.

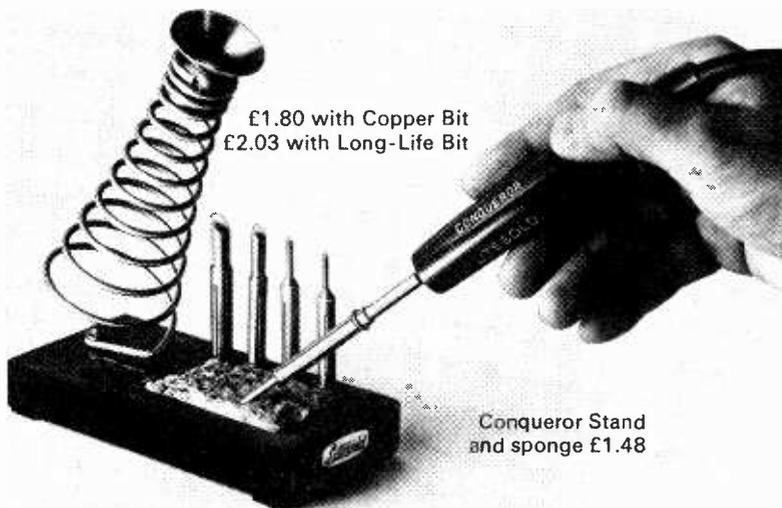

£1.80 with Copper Bit  
£2.03 with Long-Life Bit

Conqueror Stand  
and sponge £1.48

Please ask for leaflet 10/1016.

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road . Croydon CR9 2LL

01-688 8589/4559

NOT JUST A RADIO BUT A COMPLETE COMMUNICATIONS RECEIVER  
**BATTERY/MAINS PORTABLE RECEIVER**

WHAT RADIO PRICED AT UNDER £120 GIVES YOU SUCH A VARIED CHOICE OF TRANSMISSIONS?

**WHAT A SENSATIONAL RADIO!**

No less than 8 wavebands

Picks up ALL THE USUAL BBC Programmes \* All the new local radio stations \* Continental \* World-wide transmissions \* Pop Pirates \* Radio Hams \* Aircraft \* Shipping \* Police \* Taxis \* R.A.C. \* A.A. \* Fire Brigade \* T.V. Sound \* Ambulances and 1,000s more.

**THE BEST PORTABLE RADIO EVER MADE!** We think so. What radio priced at under £120 gives you such a varied choice of transmissions? As well as the standard long and medium wavebands it has three short wave bands (including the Marine and Trawler Band) AND NO LESS THAN THREE V.H.F. BANDS truly a complete WORLD-WIDE communications Receiver. JUST THINK! one minute you can be listening to your favourite B.B.C. programme and then—at the flick of a switch—you can tune into the control tower and hear a "crippled airliner" being talked down to safety. Or listen to the trawlers and ocean-going liners—Eavesdrop on the taxi-cabs, fire brigades, ambulances, A.A., R.A.C. and 100s of other R.T. mobiles! Extensive shortwave coverage can give you Australia, Pakistan, Luxembourg, North America, Far East, etc., etc., you name it—it gets it! Manufactured by one of the world's leading specialists in communications and TV equipment, each set carries a **FULL 3-YEAR WRITTEN GUARANTEE**. Beautifully finished in Teak Wood and Stainless Steel—will add distinction to any living-room. Completely portable 12in x 9in x 4in, using standard batteries—or can be plugged directly into mains. 14 transistors, 6 diodes, 1 thermistor, internal ferrite rod aerial PLUS two external telescopic antennas—with sockets for additional aerials. Complete with beat frequency oscillator for the real enthusiast, or car aerials. Automatic Drift-Free Reception. Tone control. Fine squelch control. Hi-Fidelity earphone for private listening, local DX switch

**FREQUENCIES:** Long W 150-350Kcs. Medium W 540-1605 Kcs. Marine 1.6-4 Mcs Short W 13.7-9 Mcs. Short W 2.9-22 Mcs. F.M. (VHF) 88-108 Mcs. Aircraft (VHF) 108-136 Mcs. Public Service (VHF) 148-174 Mcs. THE ULTIMATE in communications receivers—used by professionals and amateur enthusiasts all over the world. INSTANT CASH REFUND if not overwhelmed by the superb tone clarity and performance range

**NOTE.**—The Ministry of Posts & Telecommunications state a Licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft Shipping, etc.

**SCIENTIFIC AND TECHNICAL**

(PW11) 507-511 LONDON ROAD, WESTCLIFF, ESSEX

## NEW VALVES!

GUARANTEED AND TESTED

### 24-HOUR SERVICE

1R5	25	30FL14	67	EBF89	27	EF92	28	PCC189	46	PY82	23
1R5	21	30L17	66	ECC81	15	EF183	25	PCF80	20	PY800	30
1T4	14	30FL1	55	ECC82	18	EF184	27	PCF86	44	PY801	30
354	24	DAF91	21	ECC83	21	EH90	33	PCF801	27	R19	27
3V4	46	DAF86	35	ECC85	31	EL33	54	PCF802	28	U251	60
6/30L2	52	DF91	14	ECP82	28	EL41	52	PCF805	58	U329	65
6AQ5	21	DF96	35	ECH35	53	EL84	21	PCL82	28	U801	78
6BW7	48	DK91	25	ECH42	56	EY86	27	PCL83	53	UBF89	28
6F1	57	DK96	43	ECH61	28	EZ80	19	PCL84	31	UC086	28
6F23	64	DL91	24	ECL80	35	KZ81	21	PCL86	36	UCH42	56
6F25	49	DL94	40	ECL82	27	KT61	54	PCL86	25	UCH81	28
6SN7GT	28	DL96	36	ECL86	32	KT66	75	PFL200	49	UCL82	30
12AU7	18	DY88	21	EF39	35	N78	85	PL86	45	UF41	49
25L6GT	18	DY87	21	EF41	56	PC86	44	PL81	41	UF89	28
30C15	56	DY802	28	EF80	22	PC88	44	PL82	29	UL41	52
30C17	75	EABC80	28	EF85	26	PC97	35	PL83	31	UL84	27
30C18	56	EB91	09	EF86	27	PC900	28	PL84	28	UY41	37
30F6	80	EBC33	88	EF89	24	PCC84	27	PL500	59	UY85	28
30FL1	59	EBC41	47	EF91	12	PCC89	21	PL504	59	W77	48
								PY81	23	Z77	18

Post/Packing on 1 valve 7p. plus 3p. per valve on each extra valve. Any parcel insured against damage in transit 3p. extra. Office address, no callers.

**GERALD BERNARD** 83 Osbaldeston Road, Stoke Newington, London N.16

## poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker  
Super-thin construction permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 11-3/4" x 14-11/16". Weight: 19 ounces.

£6.50 each Stereo pair £12.50 post free

**web europa**

P.O. Box 162, Watford WD1 1AA




# From a recent copy of "Everyday Electronics" . . .

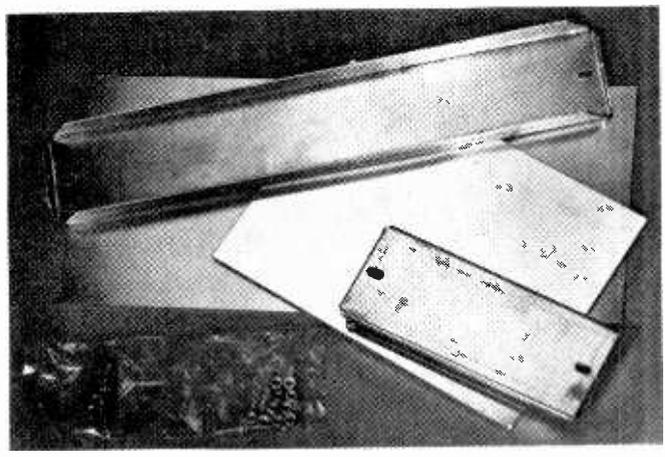**Problems**  
 Now to try and deal with some of the problems. We have had a number of reader's asking where the universal chassis parts that we have specified for some projects are available, the answer is Home Radio Components Ltd., who advertise their catalogue in our pages regularly.

*Editorial extract reproduced by kind permission of the Editor of "Everyday Electronics"*


Our famous Universal Chassis, which for many years has formed the basis of thousands of radio and electronic projects, consists of a top and four separate sides. The five parts, which are made of 18 S.W.G. aluminium, can be quickly assembled with the screws provided to form a chassis even more rigid than the standard type.



The advantages of this unique chassis are:

1. From stock, we can offer you a choice of 188 sizes, ranging from 3 x 3 x 1 ins. to 14 x 14 x 4 ins.
2. All parts are sold separately, so that a spoiled plate can be quickly and cheaply replaced. This is invaluable to the experimenter, who can use the same sides over and over again.
3. By fitting a plate to the bottom a whole range of small metal cabinets, complete with handles if required, can be assembled.

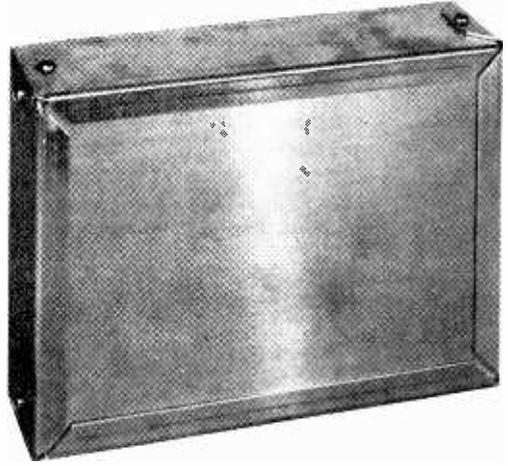**This unique UNIVERSAL CHASSIS is obtainable ONLY from Home Radio (Components) Ltd.**



A full list of plate sizes, together with reference numbers for ordering, is given in our Components Catalogue. This famous "Constructor's Bible" lists over 8,000 components, over 1,500 of them illustrated. It provides the quick, simple means of ordering all your components needs. Every catalogue contains 10 vouchers, each worth 5p when used as instructed. The catalogue costs 70p, including postage and packing: Drop us a line or use the coupon.

**POST THIS COUPON with your cheque or postal order for 70p.**



It would help us considerably if we knew whether this was your first Home Radio Components Catalogue. If it is please place a tick in the box.

Ring 01-648 8422

Ask for details of our Credit Account Service

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.



Please write your Name and Address in block capitals  
 This is my first H.R. Components Catalogue

Name .....

Address .....

.....

**HOME RADIO (Components) LTD.**  
 Dept. PW, 234-240 London Road, Mitcham CR4 3HD




# BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY,  
LONDON S.W.17 01-672 3984  
(Nr. Tooting Broadway Underground Station)  
(Closed all Wednesday)
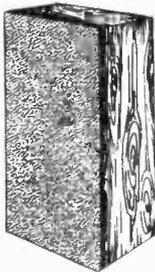
## THE SHELLEY

Size 21 x 11 x 6 1/2 in.

An extremely elegant speaker system made of 12mm. chipboard covered with black leathercloth with mottled Vynair front. This unique system uses three ex-TV speakers. Will handle 10 watts and will match 8 ohms impedance. A real bargain at £5.15 plus 70p. British Isles.



## CARTRIDGES—Stereo

Sonotone 9TA H/C Diamond £2.40. Ronette S105 Medium Output, £1.40. S106 High Output £1.40. Acos GP93/1 Sapphire, £1.90. GP94 1 Sapphire, £2. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7np on each.

## CARTRIDGES—Mono

GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.

## FARRA-DAY

5 1/2" x 11" x 4 1/2" covered in White, Green or Black rexine or Teak cloth with Silver coloured metal front 3ohm ex. tv speaker. £2.90 P & P 25p



## ELF

An extension speaker of quality; 9 x 5 1/2 x 3 1/2 in. veneered in natural teak with smart gold and mottled Vynair front 3 ohm ex-TV speaker. The baffle is half inch thick. A real bargain at £1.92 1/2. Post and packing. 37 1/2p.

## SPEAKER MATCHING TRANSFORMERS 3, 7, 15 ohms.

8 watt, 70np. P. & P. 17np.

## HI-FI STEREO HEADPHONES

Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms. frequency range 30-15,000 Hz 6ft. cord and standard stereo plug. Only £2.57 1/2. P. & P. 27 1/2p.



## STEREO HEADPHONE JUNCTION BOX

Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones. Only £1.50. P. & P. 13p.



## VYNAIR

Widths from 50 to 54in., 75np yd. off roll. P. & P. 10np, 1/2 yard 40np. P. & P. 10np. Send 5np stamps for samples.

**BOOST THE SOUND**  
£3.15  
CAXTON EXTENSION SPEAKERS  
P. & P. 61p

Makes all the difference to volume and quality. Contains 3 speakers in series—ex-TV Output 8 watts. Impedance 9 ohms. Available in black leathercloth. Size 23 1/2" x 5 1/2" x 5 1/2". Keyhole slot for wall mounting. Twin connecting cable 12yds., 35p min.

**TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88—108Mcs, with circuit diagram. £2.10p.**

**B.F.W. 10 Fet. New (unmarked) 5 for £1 00p.**

**SPECIAL OFFERS of Unmarked Tested Power Transistors.**  
2N3055 Silicon NPN 30p each 4 for £1.  
2N3054 Silicon 20p each 3 for 50p.  
Plastic 40 Watt NPN 25 Volt 20p each 3 for 50p.

**P-C BOARDS (not computer panels).**

1 off 6 transistors single wave band  
1 off 4 transistor audio  
1 off 3 transistor £1.50 the three.

Encapsulated bridge rectifier (itt usd 3 3mdh) 100 PIV 2 amps. 50p each.

Transistor F.M. Stereo Multiplex Decoder. Size: 5 1/2 x 2 1/2 x 1 1/2. As used in well known British stereo units with circuit. £3.75.

**GARRARD SP25 MK. II less Cartridge £10.50.**

**10 VOLUME CONTROLS** consisting of 2 off each.

100K log. ganged L/S—20K log. ganged L/S  
470K log. D.P Switch—10K lin. L/S—50K lin. L/S. £1.25.

**4 PHONO SOCKETS ON PANEL.** 10 panels for £1.25.

**12 PLASTIC KNOBS.** Chrome and Gold, 3 types—4 off each—spring clip £1.25.

**10 COMPUTER PANELS** packed with components including one panel with 2 Power Transistors. £1.00.

All items post paid in


GREAT BRITAIN

# SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

*Why pay more - look at our Fantastic Bargain Offer!*


## THE AVON AUDIO SYSTEM

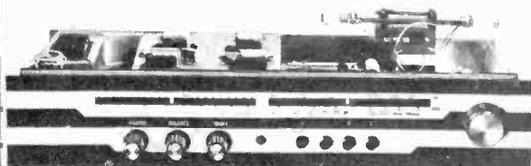

This uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection. 10 watts total output. Frequency response 25-18000 Hz.

BSR 4 SPEED STEREO/MONO RECORD CHANGER plays all types of 7in., 10in. and 12in. Mono or Stereo records. Manual or automatic play.

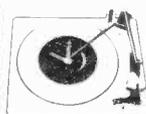TWIN ELLIPTICAL SPEAKER. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.



EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £46.20, OUR PRICE £37.00. Credit Terms £4.17 deposit plus 88p Post & Packing followed by 9 payments of £4.17 (Total Credit Terms £41.70) Don't miss this bargain. SEND £5.05 TODAY.

ALL EQUIPMENT COVERED BY 12 MONTHS FULL GUARANTEE.

CALLERS WELCOME

Please send me free details of your range

Name .....

Address .....

PW 11 72

Post coupon NOW for...  
**FREE**  
leaflets

**LEWIS radio** 100, Chase Side London N.14  
Tel: 01-886 3733/9666

Now that you've got

# Audio

You've never heard it so good!



It had to happen . . . and it has. **Audio** is the new-style magazine that brings excitement and vitality to the interests of music and hi-fi.

Written and designed by an expert editorial team, **Audio** is about the latest advances in equipment, its installation, its operation. Radio and television in the home . . . tape or disc . . . film or video . . . car stereo, slot or cassette. **Audio** takes it all in; reports on all important developments.

**Audio** is about the music made . . . the places where the making is done . . . the reason it's done the way it is . . . the artists and composers you most enjoy.

Performance test on the latest Nivico Tape Recorder

**David Burnett James** writes on the new Wharfedale Isodynamic Headphones.

**Christopher Headington** writes about a notable anniversary in Solti is Sixty . . .

Other contributors include: **Katie Boyle** **Colin Wilson** . . . **Richard Williams** . . .

**Top-name contributors . . . outstanding features and illustrations special technical and record reviews.**

**FREE!** unique 7" flexible record  
**Audio past present and future**

with commentary spoken by **RICHARD BAKER** 33 $\frac{1}{3}$  rpm Stereo Mono

# Audio


*for your greater enjoyment of leisure listening — Monthly 20p*

**ISSUE ONE (NOVEMBER) OUT OCT 19**

# Have fun with electronics...



## Radionic Construction Kits

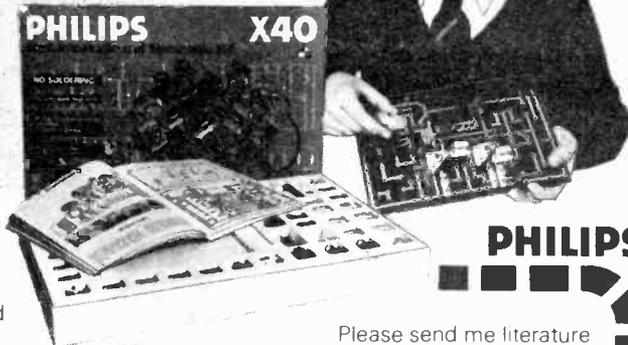

### NO SOLDERING BATTERY OPERATED

Build your own radio receiver and many exciting experiments with the unique printed circuit board and mounted components. Easy to build, no soldering, battery operated, plus a fully illustrated instruction manual giving precise directions for each experiment. Ideally suitable for both the experimenter and beginner.

### Radionic Products Limited

St. Lawrence House, Broad Street, Bristol BS1 2HF  
Tel: 0272 25351

Member of the ESL BRISTOL Group of Companies

**PHILIPS**

Please send me literature on Radionic radio and electronics construction kits.

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

PW2

## MAINS UNITS for all types of TRANSISTOR EQUIPMENT
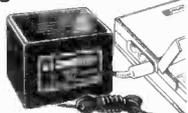
### RUN YOUR TAPE RECORDER OFF AC MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, make and type of plug required, if in doubt send diagram of recorder socket.)



ONLY £2.50, P & P 15p

### PLUS-3 MAINS UNIT



Provides three separate switched output voltages 6v., 7½v. and 9v. DC. Attractive case with indicator light, mains lead output socket, plug and lead. Size 4½ x 3½ x 2½in. ONLY £3.00, P & P 15p.

Extra lead with plug to fit your cassette recorder 50p. (State model and plug required.)

### SINGLE OUTPUT MAINS UNITS

For radios, recorders etc. 6v. or 9v. or 12v. ONLY £2.00, P & P 15p. (Please state output required.) All units are completely isolated from mains by double wound transformer ensuring 100% safety.



**R.C.S. PRODUCTS (RADIO) LTD.**  
(DEPT. P.W.), 31 OLIVER ROAD, LONDON, E.17

## U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

**LOFT MOUNTING ARRAYS**  
7 element 2.25. 11 element 2.75. 14 element 3.25. 18 element 3.75.

**WALL MOUNTING c/w WALL ARM & BRACKET**  
7 element 3.25. 11 element 3.75. 14 element 4.25. 18 element 4.75.

**CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT.** 7 element 4.00. 11 element 4.50. 14 element 4.75. 18 element 5.25.

**MAST MOUNTING arrays only.** 7 element 2.25. 11 element 2.75. 14 element 3.25. 18 element 3.75.

Complete assembly instructions with every aerial. **LOW LOSS** coaxial cable 9np yd. **KING TELEBOOSTERS** from 3.75. **LAGGEAR** all band V.H.F.—U.H.F.—F.M.

radio mains operated pre-amps 7.50. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np C.W.O. Min. C.O.D. charge 25np.

**BBC—ITV—FM AERIALS**

**BBC** (band 1) Wall S/D 2.00. **LOFT** inverted 'T' 1.25. **EXTERNAL 'H'** array only 3.00.

**ITV** (band 3) 5 element loft array 2.50. 7 element 3.00. **COMBINED BBC—ITV.** loft 1+5 2.75. 1+7 3.50. **WALL & CHIMNEY UNITS ALSO AVAILABLE.** Pre-amps from 3.75. **COMBINED U.H.F.—V.H.F. aerials** 1+5+9 4.00. 1+5+14 4.50. 1+7+14 5.00. **F.M. RADIO** loft S/D 1.00

3 element 3.25. 4 element 3.50. Standard coaxial plugs 9np. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

**CALLERS WELCOMED OPEN ALL DAY SATURDAY**


**K.V.A. ELECTRONICS**

40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY

Telephone 01-648 4884

## H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

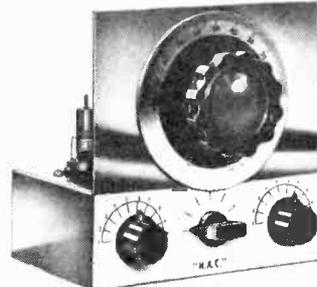

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

### NEW "DX" RECEIVER

Complete kit—price £3.90 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. **EXCITING COMPETITION** for Short-Wave listeners. Send stamped envelope for details.

**"H.A.C." SHORT-WAVE PRODUCTS**  
29 Old Bond Street, London W.1

# Disco

# SOUND & LIGHTING EQUIPMENT


from 4 SPECIALISED DISCO STUDIOS

## HIGH POWER SPEAKER SYSTEMS

Strong leather cloth finish 1" board, fully lagged. Fitted high efficiency 8 or 16 ohm speakers.

**PRINCE.** 50 watt rms. 12". Size 24" x 16" x 12".  
**CONSORT.** 100 watt rms. 2-12" speakers. Size 36" x 18" x 12".  
**MAJESTIC.** 100 watt rms. 15" Crescendo. Size 38" x 24" x 15".  
**SOVEREIGN.** 100 watt rms. 18" Bass. 12" Full range. Size 50" x 26" x 14".

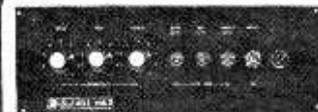**FULL RANGE OF MICROPHONES, STANDS, ETC. ALWAYS IN STOCK**



## SOUND CONTROLLED AND SOUND TO LIGHT UNITS

Mid, Treble and Bass Channels, up to 1kw of lamps per channel plus override switching.  
**DJ30L.** Sound to light. Takes output from most amplifiers. Adjustable levels.  
**DJ40L.** Sound controlled version. Built in microphone. No connections required.


## ASSEMBLED DISCOTHEQUES

**DISCO-PLINTH.** Consists of 2 turntables fitted with high quality ceramic cartridges. The unit has a built in cross-fade rotary control for transferring the sound from left to right decks. The unit has no amplification built in and must be used with amplifiers such as the D.J. 1058 or D.J. 708. Size 32" x 14 1/2" x 7" (incl. lid). **£65-00**  
**DISCO-IMP.** The latest addition to the Disco-sound Range of discotheques. Even smaller and more compact than the Disco-Mini, it contains all the necessary features for the smooth running of a mobile unit. Size 29" x 18 1/2" x 7". **£79-00**  
**DISCO-MINI.** Complete portable Disco with built-in full function pre-amplifier/mixer. For use with any power amplifier such as "Disc-master". Size 30" x 20" x 8". **£98-50**  
**DISCO-STANDARD.** Has all the facilities of the Disco-Mini with the addition of a built-in 100 watt power amplifier making it a completely self contained disco unit. A V.U. meter gives visual indication of output levels. Size 32" x 27" x 7 1/2". **£180-00**  
**DISCO-SUPER.** A slightly larger version of the Disco-Standard. Fitted individual controls for both mic. and deck inputs plus a cross-fade for deck to deck transfer. A built in P.F.L. cueing system, mic. override, also a V.U. meter gives visual indication of output levels. DJ. 30L (3000V) 3-channel psychedelic light unit is a standard fitting. Deck cut out switches are also featured for ease of cueing. Size 38" x 27" x 10". **£224-00**  
**DISCO-SUPREME.** All facilities of the Disco-Super plus a third turntable which can be used for Jingles or other effects without using the main deck system. Flexi lights are also fitted. Size 50" x 27" x 10". **£281-00.**
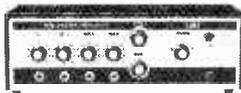
## PA-DISCO AMPLIFIERS



**DISCO-AMP.** 100 watt rms. output for 8-16 ohms, 4 channel inputs, 2-mic, 2 decks. Separate volume control plus masters. Response 30Hz -30KHz, distortion less than 1%. Treble/Bass/PFL/Mic over-ride etc. Panel size 16 1/2" x 7".



**DJ.70S MIXER/AMPLIFIER.** 70 watt rms. output for 8-16 ohms. 2-mic, 2-aux/decks. Master volume/Bass/Treble. Size 15 1/2" x 5" x 6".


**DJ.105S.** 30 watt rms. version. Size 11 1/2" x 5" x 6".

**DISCMaster SLAVE AMPLIFIER.** 100 watt rms. for 8-16 ohms. **£59-50**
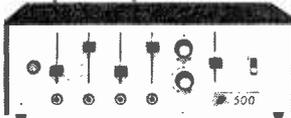
## NEW D.J. 500 SERIES P.A. AMPLIFIERS 50 WATT, 70 WATT & 100 WATT MODELS

This new range incorporates many features that make them ideal for the professional user, clubs, discotheques, factories etc. Fibre glass P.C. Boards are used throughout with low noise silicon transistors, high stability resistors, generously rated components and hand-wired assembly to ensure reliability and quality.

- ★ Exclusive "Fall Safe" Electronic Protection circuit.
- ★ Fault Condition warning lamp.
- ★ Built in bass boost below 30 Hz.
- ★ 4 channel mixer with slider controls.



All three amplifiers have a built in emitter follower output socket for connecting a slave amplifier to enable the power output to be increased up to 1000 watts or more if required. A matching range of slave power amplifiers and a separate matching 100V line transformer is available

### SPECIFICATION

Frequency Response 50-20,000 Hz  $\pm$  3db (10dB Bass Boost at 10 Hz)  
 Signal/Noise Ratio better than -60db.  
 Harmonic Distortion less than 1%  
 Speaker Impedance 8-16 ohms.  
 Inputs: Mic 1 & 2 5mV at 50K ohms (50 or 600 ohm to order)  
 Aux 3 & 4 100mV at 1 meg ohm.  
 Size (all models) 15 1/2" x 5" x 6".  
 Power Output: Model D.J.500 — 50 watts R.M.S. **£58-25**  
 (at 8 ohms) Model D.J.700 — 70 watts R.M.S. **£87-50**  
 Model D.J.1000 — 100 watts R.M.S. **£79-00**

## DISCO MINI

Hardly larger than a suitcase yet contains all the necessary features for a high quality mobile unit. The pre-amp has separate tone controls for both mic. and decks and each input has its own individual volume controls and inputs, plus the addition of a cross fade for deck to deck sound transfer. A built in P.F.L. system for cueing, together with mic-over-ride facility are standard on all units. Response 20-20,000 Hz. Mic. input 5mV. 50K. Output 1 volt.  
 McDonald M.P.60 Turntables are used with high quality ceramic cartridges, and each deck has its own individual cut out switch fitted. This unit is suitable for Discos or Clubs having a power amplifier, or for use with the 'Discmaster' 100 watt power amplifier as above. Size 32" x 20" x 8". **£98-50.**



## EFFECTS PROJECTORS



A small selection from our vast stock

**DISCO COLT.** 150 watt.  
**LIQUIMATIC MINI.** 50 watt Q1 with 6" wheel  
**DISCOWHEEL.** 50 watt Q1 with quick change Cassette.  
**GNOME 150.** 150 watt Q1 with Cassette.  
**LIQUIMATIC.** 150 watt Q1 with 6" wheel.  
**PLUTO TUTOR-2.** 250 watt Q1 with Cassette and 6" wheel.  
**TUTOR-2.** with Liquisplode Tank.  
**KALEIDOSCOPE LENS** (for Tutor-2) 6" Liquid Wheel and Crystal Wheel Liquid Cassette and Moire (24 different types to choose from). Portable Hi-Power Strobes.  
**YOU WILL BE SURPRISED BY THE LOW PRICES & PERFORMANCE**

## SDL POWER SPEAKERS

High efficiency 12" speakers. Ferrite magnets. Heavy duty voice coils and cones for Disco and Group use.  
 12" 50 watt rms. 8 ohm Full range.  
 12" 25 watt rms. 15 ohm Mid-Treble.  
 15" 50 watt rms. 15 ohm. Full range.  
 15" 100 watt rms. 15 ohm. Bass.  
 18" 100 watt rms. 15 ohm. Bass.

## DISCO SPOT BANK



Designed to take three E/8 Type spot or colour bulbs up to 150 watts each. The unit is of all metal construction and has one 3-pin mains input socket plus one 3-pin mains output socket for connecting more than one bank together if required. The unit can be left free-standing or wall mounted if needed. Black crackle finish gives the unit a very professional appearance.

Size 18" x 6" x 7" (excluding bulbs)  
 Also in stock: Ultra Violet Spot Lamps and Fluorescent Lamps, Standard and Colour Spot Lamps and Fittings, Rotating Colour Displays, Flexilights, Fibre Optics, Dimmers, Flashers Effects Foils, etc. Your enquiries invited.

## MIXER UNITS

**DJ.101.** Battery powered, 6-channel, variable levels, 3 x 50k mic., 1 x 100mV. aux., 2 x 100mV p.u. Output 250mV.  
**DJ.102.** Mains operated, 4-channel, variable levels, 2 x 50k mic., 2 x 100mV p.u. PFL control, master volume, mic. over-ride, output variable 0-500mV.  
**DISCO 40.** Pre amp part of Disco amp (see above). All facilities. Output will drive up to ten 100 watt amplifiers.

**Discoscene**  
 536, Sutton Road,  
 Southend, Essex.  
 (0702) 611577

**Discosound**  
 122, Balls Pond Road,  
 London, N.1  
 (01) 254 5779

**Discosound**  
 (Birmingham) Ltd.  
 494, Bristol Road,  
 Selly Oak, B'ham 29.  
 (021) 472 1141


**Henry's Disco**  
 309, Edgware Road,  
 London, W.2  
 (01) 723 6963

CHECK WITH YOUR NEAREST STUDIO FOR LATEST PRICES AND DETAILS (TRADE AND RETAIL SUPPLIED)

**VEROBOARD INSIDE**  
**RADIO & ELECTRONICS**  
**CONSTRUCTOR** 20p

Vol. 26 No. 3

OCTOBER 1972

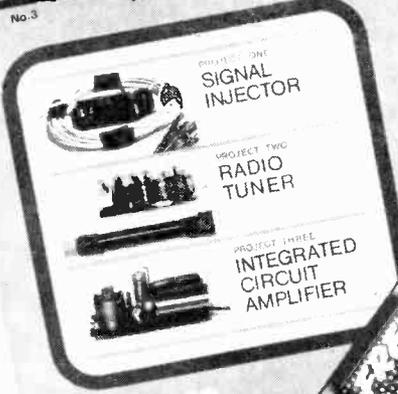

**PROJECT ISSUE**

**FREE VEROBOARD**  
**IN OCTOBER ISSUE**  
**LOOK FOR THIS COVER**  
**ON SALE NOW**

PROJECT 1 SIGNAL INJECTOR	Very suitable for beginners - consists of a wide-band signal injector which is capable of injecting an amplitude modulated signal into any medium and long wave receiver having a ferrite rod aerial - a useful and inexpensive item of test equipment.
PROJECT 2 RADIO 2 TUNER	A fairly complex assembly making full use of the connection points on the Veroboard. A pre-tuned Radio 2 Tuner incorporating two transistors. Current consumption from the 9 volt battery is of the order of 2mA only.
PROJECT 3 INTEGRATED CIRCUIT AMPLIFIER	Designed around the readily available R.C.A. CA3020 i.c., this a.f. amplifier offers a high level of performance and relatively few components are needed - output in excess of 300mW, input impedance 50kΩ.

Copies may also be obtained direct from the Publishers, 26p including postage. Published by Data Publications Ltd. 57 Maida Vale, London W.9.

*Buy NOW and be sure of your copy - PRICE 20p*

**TOP QUALITY — LOW COST**



**AMATEUR RADIO EQUIPMENT**

**CODAR**




**P.R.40**  
**SOLID STATE**  
**R.F. PRESELECTOR**

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supercedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30 dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee. ... £8.90 Carriage 30p.



**MULTIBAND-6**  
**SOLID STATE**  
**SHORT WAVE RECEIVER KIT**

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery). £13.20 Carriage 35p. Stamp brings illustrated leaflets.

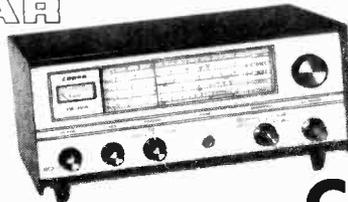

**CR70A**  
**COMMUNICATION RECEIVER**

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.

It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder.

Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

Complete ready built £27.50, Carriage 70p. Ask the chap who's got one, there's lots of them!

**NOTE:** These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers and are FREE of Purchase Tax. Some portable receivers being advertised as Communication Receivers do not meet these requirements.



ON THE DESIGN STAFF—  
**G3SZM G3IRE G8BBI**

**CODAR**

TELECOMMUNICATIONS AND ELECTRONIC EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS GOVERNMENTS

**VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX**

Tel. 090-63-61901

# THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

## BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-20	AD162	0-33	BC148	0-10	BD137	0-45	BF188	0-40	OC19	0-35	2G371	0-16	2N2219	0-20	2N3054	0-46	2N4059	0-10
AC113	0-20	AD161 & AD162 (MP)		BC149	0-12	BD138	0-50	BF194	0-12	OC20	0-63	2G371B	0-12	2N2220	0-22	2N3055	0-50	2N4060	0-12
AC115	0-23	AD162 (MP)		BC150	0-18	BD139	0-55	BF195	0-12	OC22	0-28	2G373	0-17	2N2221	0-20	2N3056	0-14	2N4061	0-12
AC117K	0-20		0-55	BC151	0-20	BD140	0-60	BF196	0-14	OC23	0-42	2G374	0-17	2N2222	0-20	2N3057	0-14	2N4062	0-12
AC122	0-12	ADT140	0-50	BC152	0-17	BD141	0-60	BF197	0-14	OC24	0-56	2G375	0-30	2N2223	0-17	2N3058	0-14	2N4063	0-12
AC125	0-17	AF114	0-24	BC153	0-28	BD142	0-65	BF198	0-14	OC25	0-28	2G376	0-16	2N2224	0-17	2N3059	0-14	2N4064	0-12
AC126	0-17	AF115	0-24	BC154	0-30	BD143	0-60	BF199	0-14	OC26	0-25	2G381	0-16	2N2225	0-14	2N3060	0-14	2N4065	0-12
AC127	0-17	AF116	0-24	BC157	0-18	BD144	0-65	BF200	0-14	OC28	0-50	2G382	0-16	2N2226	0-14	2N3061	0-14	2N4066	0-12
AC128	0-17	AF117	0-24	BC158	0-12	BD145	0-65	BF201	0-14	OC29	0-50	2G401	0-30	2N2227	0-14	2N3062	0-14	2N4067	0-12
AC132	0-14	AF118	0-35	BC159	0-12	BD146	0-60	BF202	0-14	OC30	0-42	2G414	0-30	2N2228	0-14	2N3063	0-14	2N4068	0-12
AC134	0-14	AF124	0-30	BC160	0-45	BD147	0-70	BF203	0-14	OC35	0-50	2G417	0-25	2N2229	0-14	2N3064	0-14	2N4069	0-12
AC137	0-14	AF125	0-25	BC161	0-50	BD148	0-65	BF204	0-14	OC36	0-50	2G417	0-25	2N2230	0-14	2N3065	0-14	2N4070	0-12
AC141	0-14	AF126	0-28	BC167	0-12	BD149	0-60	BF205	0-14	OC41	0-20	2N385	0-35	2N2231	0-14	2N3066	0-14	2N4071	0-12
AC141K	0-17	AF127	0-28	BC168	0-12	BD150	0-70	BF206	0-14	OC42	0-24	2N388A	0-55	2N2232	0-14	2N3067	0-14	2N4072	0-12
AC142	0-14	AF139	0-30	BC169	0-12	BD151	0-70	BF207	0-14	OC44	0-15	2N404	0-20	2N2233	0-14	2N3068	0-14	2N4073	0-12
AC142K	0-17	AF139	0-30	BC169	0-12	BD152	0-70	BF208	0-14	OC45	0-12	2N404A	0-20	2N2234	0-14	2N3069	0-14	2N4074	0-12
AC143	0-17	AF178	0-50	BC170	0-12	BD153	0-75	BF209	0-14	OC46	0-10	2N404	0-20	2N2235	0-14	2N3070	0-14	2N4075	0-12
AC144	0-15	AF179	0-50	BC171	0-14	BD154	0-75	BF210	0-14	OC71	0-10	N527	0-42	2N2236	0-14	2N3071	0-14	2N4076	0-12
AC154	0-20	AF180	0-50	BC172	0-14	BD155	0-85	BF211	0-14	OC72	0-10	N528	0-42	2N2237	0-14	2N3072	0-14	2N4077	0-12
AC155	0-20	AF181	0-45	BC173	0-14	BD156	0-85	BF212	0-14	OC74	0-14	2N599	0-45	2N2238	0-14	2N3073	0-14	2N4078	0-12
AC156	0-20	AF186	0-45	BC174	0-14	BD157	0-90	BF213	0-14	OC75	0-15	2N696	0-12	2N2239	0-14	2N3074	0-14	2N4079	0-12
AC157	0-24	AF239	0-37	BC175	0-22	BD158	0-90	BF214	0-14	OC76	0-15	2N697	0-13	2N2240	0-14	2N3075	0-14	2N4080	0-12
AC165	0-20	AL102	0-65	BC177	0-19	BD159	0-95	BF215	0-14	OC77	0-25	2N698	0-24	2N2241	0-14	2N3076	0-14	2N4081	0-12
AC166	0-20	AL103	0-65	BC178	0-19	BD160	0-95	BF216	0-14	OC81	0-15	2N699	0-35	2N2242	0-14	2N3077	0-14	2N4082	0-12
AC167	0-20	ALY26	0-25	BC179	0-19	BD205	0-80	BF283	0-22	OC81D	0-15	2N706	0-08	2N2243	0-14	2N3078	0-14	2N4083	0-12
AC168	0-24	ASV27	0-30	BC180	0-24	BD206	0-80	BF284	0-22	OC82	0-15	2N706A	0-09	2N2244	0-14	2N3079	0-14	2N4084	0-12
AC169	0-14	ASV28	0-25	BC181	0-24	BD207	0-95	BF285	0-22	OC82D	0-15	2N708	0-12	2N2245	0-14	2N3080	0-14	2N4085	0-12
AC176	0-20	ASV29	0-25	BC182	0-10	BD208	0-95	BF286	0-22	OC83	0-20	2N711	0-30	2N2246	0-14	2N3081	0-14	2N4086	0-12
AC177	0-24	ASV50	0-25	BC182L	0-10	BDY20	1-00	BFY53	0-17	OC84	0-20	2N717	0-35	2N2247	0-14	2N3082	0-14	2N4087	0-12
AC178	0-28	ASV51	0-25	BC183	0-10	BF115	2-24	BPX25	0-85	OC89	0-20	2N718	0-24	2N2248	0-14	2N3083	0-14	2N4088	0-12
AC179	0-28	ASV52	0-25	EC183L	0-10	BF117	0-45	BRX19	0-15	OC140	0-20	2N718A	0-50	2N2249	0-14	2N3084	0-14	2N4089	0-12
AC180	0-17	ASV54	0-25	BC184	0-12	BF118	0-70	BRX20	0-15	OC141	0-25	2N726	0-28	2N2250	0-14	2N3085	0-14	2N4090	0-12
AC180K	0-20	ASV55	0-25	BC184L	0-12	BF119	0-70	BRX21	0-15	OC170	0-25	2N727	0-28	2N2251	0-14	2N3086	0-14	2N4091	0-12
AC181	0-17	ASV56	0-25	BC186	0-28	BF121	0-45	BSY26	0-15	OC171	0-25	2N743	0-20	2N2252	0-14	2N3087	0-14	2N4092	0-12
AC181K	0-20	ASV57	0-25	BC187	0-28	BF123	0-50	BSY27	0-15	OC201	0-25	2N744	0-20	2N2253	0-14	2N3088	0-14	2N4093	0-12
AC187	0-22	ASV58	0-25	BC207	0-11	BF125	0-45	BSY28	0-15	OC202	0-28	2N914	0-14	2N2254	0-14	2N3089	0-14	2N4094	0-12
AC187K	0-20	ASZ21	0-40	HC208	0-11	BF127	0-50	BSY29	0-15	OC202	0-28	2N918	0-30	2N2255	0-14	2N3090	0-14	2N4095	0-12
AC188	0-22	BC107	0-09	BC209	0-12	BF152	0-55	BSY38	0-18	OC203	0-25	2N929	0-21	2N2256	0-14	2N3091	0-14	2N4096	0-12
AC188K	0-20	ASV56	0-25	BC212L	0-11	BF153	0-45	BSY39	0-18	OC204	0-25	2N930	0-21	2N2257	0-14	2N3092	0-14	2N4097	0-12
AC197	0-25	BC109	0-10	BC214L	0-11	BF154	0-45	BSY40	0-28	OC205	0-35	2N131	0-20	2N2258	0-14	2N3093	0-14	2N4098	0-12
AC198	0-20	BC113	0-10	BC214L	0-14	BF155	0-70	BSY41	0-28	OC309	0-40	2N132	0-22	2N2259	0-14	2N3094	0-14	2N4099	0-12
AC199	0-20	BC114	0-15	BC225	0-25	BF156	0-48	BSY95	0-12	P346A	0-20	2N1302	0-14	2N2260	0-14	2N3095	0-14	2N4100	0-12
AC200	0-20	BC115	0-15	BC226	0-35	BF157	0-55	BSY95A	0-12	P397	0-42	2N1303	0-14	2N2261	0-14	2N3096	0-14	2N4101	0-12
AC201	0-20	BC116	0-15	BCY30	0-24	BF158	0-55	BU105	2-00	CP71	0-43	2N1304	0-17	2N2262	0-14	2N3097	0-14	2N4102	0-12
AC202	0-18	BC117	0-15	BCY31	0-28	BF159	0-60	CL11E	0-50	RP12	0-43	2N1305	0-17	2N2263	0-14	2N3098	0-14	2N4103	0-12
AC203	0-18	BC118	0-10	BCY32	0-30	BF160	0-40	C400	0-30	ORP60	0-40	2N1306	0-21	2N2264	0-14	2N3099	0-14	2N4104	0-12
AC204	0-18	BC119	0-10	BCY33	0-22	BF162	0-40	C407	0-25	ORP61	0-40	2N1307	0-21	2N2265	0-14	2N3100	0-14	2N4105	0-12
AC205	0-35	BC120	0-80	RCY34	0-25	BF163	0-40	C424	0-20	ST140	0-12	2N1308	0-23	2N2266	0-14	2N3101	0-14	2N4106	0-12
AC206	0-28	BC125	0-12	BCY70	0-14	BF164	0-40	C425	0-50	ST141	0-17	2N1309	0-23	2N2267	0-14	2N3102	0-14	2N4107	0-12
AC207	0-28	BC126	0-18	BCY71	0-18	BF165	0-40	C426	0-35	TS43	0-30	2N1613	0-20	2N2268	0-14	2N3103	0-14	2N4108	0-12
AC208	0-21	BC132	0-12	BCY72	0-14	BF167	0-22	C428	0-20	UT46	0-27	2N1711	0-20	2N2269	0-14	2N3104	0-14	2N4109	0-12
AC209	0-28	BC135	0-12	BCZ11	0-25	BF176	0-35	C442	0-30	2C301	0-09	2N1889	0-32	2N2270	0-14	2N3105	0-14	2N4110	0-12
AC210	0-17	BC136	0-15	BCZ12	0-25	BF177	0-35	C444	0-35	2C303	0-19	2N1890	0-45	2N2271	0-14	2N3106	0-14	2N4111	0-12
AC211	0-18	BC137	0-15	BD121	0-60	BF178	0-30	C460	0-22	2C304	0-24	2N2147	0-57	2N2272	0-14	2N3107	0-14	2N4112	0-12
AC212	0-15	BC139	0-40	BD123	0-65	BF179	0-30	MAT100	0-18	2C306	0-40	2N2148	0-57	2N2273	0-14	2N3108	0-14	2N4113	0-12
AD130	0-38	BC140	0-30	BD124	0-60	BF180	0-30	MAT101	0-20	2C308	0-35	2N2160	0-60	2N2274	0-14	2N3109	0-14	2N4114	0-12
AD142	0-48	BC141	0-30	BD125	0-60	BF181	0-30	MAT120	0-18	2C309	0-35	2N2192	0-35	2N2275	0-14	2N3110	0-14	2N4115	0-12
AD143	0-38	BC142	0-30	BD126	0-60	BF182	0-40	MAT121	0-20	2C339	0-20	2N2193	0-35	2N2276	0-14	2N3111	0-14	2N4116	0-12
AD143	0-38	BC143	0-30	BD127	0-65	BF183	0-40	MFF102	0-42	2C339A	0-16	2N2194	0-35	2N2277	0-14	2N3112	0-14	2N4117	0-12
AD149	0-50	BC145	0-45	BD135	0-40	BF184	0-25	MFF104	0-37	2G344	0-18	2N2217	0-22	2N2278	0-14	2N3113	0-14	2N4118	0-12
AD161	0-33	BC147	0-10	BD136	0-40	BF185	0-30	MFF105	0-37	2G345	0-18	2N2218	0-20	2N2279	0-14	2N3114	0-14	2N4119	0-12

DIODES AND RECTIFIERS					
AA119	0-08	BY133	0-21	OA10	0-35
AA120	0-08	BY164	0-50	OA47	0-07
AA129	0-08	BYX38/30		OA70	0-07
AA130	0-09		0-42	OA79	0-07
AAZ13	0-10	BYZ10	0-35		

# The largest selection

## NEW LOW PRICE TESTED S.C.R.'s

P1V 1A	3A	5A	7A	10A	16A	30A
TO-18	TO-66	TO-66	TO-47	TO-47	TO-47	TO-47
50-0-23	0-25	0-35	0-35	0-47	0-50	0-83
100-0-25	0-33	0-47	0-47	0-50	0-58	0-63
200-0-35	0-37	0-49	0-49	0-57	0-61	0-75
400-0-53	0-47	0-66	0-66	0-77	0-75	0-93
600-0-57	0-57	0-88	0-88	0-87	0-87	1-25
800-0-63	0-70	0-80	0-80	0-90	1-20	1-50
						4-00

## SIL. RECTS. TESTED

P1V 300mA	750mA	1A	1.5A	6A	10A	30A
50-0-04	0-05	0-05	0-05	0-14	0-21	0-60
100-0-04	0-06	0-06	0-13	0-16	0-23	0-75
200-0-05	0-09	0-09	0-07	0-20	0-24	1-00
400-0-05	0-13	0-07	0-10	0-27	0-37	1-25
600-0-07	0-16	0-11	0-25	0-34	0-46	1-86
800-0-10	0-17	0-11	0-25	0-37	0-55	2-00
1000-0-11	0-25	0-14	0-30	0-46	0-63	2-50
1200	0-33	0-38	0-57	0-75		

## TRIACS

V BOM 2A	6A	10A
TO-1 TO-66	TO-88	
\$p	\$p	\$p
100	20	50
200	60	60
400	70	75

## FULL RANGE OF ZENER DIODES

VOLTAGE	RANGE
2-33V	400mV (DO-7)
Caspi 13p	ea. 14W (Top Hat) 18p ea. 10W (SO-10)
Standard 25p ea.	All fully tested 25p, 50p, and marked. State voltage required.

**10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 90p each**

## NEW LINE Plastic Encapsulated 2 Amp. BRIDGE RECTS.

50 v RMS	32p each
100 v RMS	37p ..
400 v RMS	46p ..
Size 15 mm x 6 mm.	

## UNIJUNCTION

UT46	Eqvt. 2N2646
Eqvt. T1843	2N3000
T2	2p each, 25-99 25p
100 UP 20p.	

## CADMIUM CELLS

ORP12 43p
ORP60, ORP61 40p each

## GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N706/8, BY-27/28/95A.	All usable devices no open or short circuits. ALSO AVAILABLE in PNP SIM. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

	\$p	
20	For	0.50
50	For	1.00
100	For	1.75
500	For	7.50
1000	For	15.00

## SIL. G.P. DIODES 3p

300mW	30	0.50
40PIV (Min.)	100	1.50
Sub-Min.	500	5.00
Full Tested 1,000	9.00	
Ideal for Organ Builders.		

## GENERAL PURPOSE GERM. PNP

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE. — OC25-28-29-30-35-36. NKT 401-403-404-405-406-407-408-409-410-411-412-413. T1907-3028, 2N260A, 2N456A-457A-458A, 2N511 A & B. 2G220-222, ETC. VBO 40V VCEO 50V IC 10A PT. 30 WATTS HFE 30-170.

PRICE	1-24	25-99	100 up
	43p each	40p each	39p each

**2N3055**  
115 WATT SIL PNP POWER EACH  
50p EACH

## KING OF THE PAKS Unequalled Value and Quality

# SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.50
U 2	60 Mixed Germanium Transistors AF/RF	0.50
U 3	75 Germanium Gold Bonded Sub-Min. like OA6, OA47	0.50
U 4	40 Germanium Transistors like OC81, AC128	0.50
U 5	60 200m A Sub-Min. Silicon Diodes	0.50
U 6	30 Sil. Planar Trans. NPN like BS795A, 2N706	0.50
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V	0.50
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.50
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.50
U 10	20 BA750 charge storage Diodes DO-7 Glass	0.50
U 11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.50
U 12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0.50
U 13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0.50
U 14	150 Mixed Silicon and Germanium Diodes	0.50
U 15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0.50
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.50
U 17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.50
U 18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.50
U 19	25 Silicon NPN Transistors like BC108	0.50
U 20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.50
U 21	30 AF. Germanium Alloy Transistors 2G300 Series & OCT 1	0.50
U 22	30 MATT's like MHz Series PNP Transistors	0.50
U 23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.50
U 24	25 300 MHz NPN Silicon Transistors 2N706, BY27	0.50
U 25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.50
U 26	12 NPN Germanium AF Transistors TO-1 like AC127	0.50
U 27	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	0.50
U 28	15 Plastic Silicon Planar Trans. NPN 2N2926	0.50
U 29	20 Silicon Planar Plastic PNP Trans. Low Noise Amp 2N3707	0.50
U 30	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	0.50
U 31	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.50
U 32	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0.50
U 33	25 Silicon Planar Transistors PNP TO-18 2N2906	0.50
U 34	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.50
U 35	30 Silicon Alloy Transistors 80-2 PNP OC200, 28322	0.50
U 36	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.50
U 37	30 RF. GERM. PNP Transistors 2N1303/5 TO-5	0.50
U 38	10 Dual Transistors 6 lead TO-5 2N2060	0.50
U 39	25 RF Germanium Transistors TO-5, OC45, NKT72	0.50
U 40	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0.50
U 41	25 Rtl. Trans. Plastic TO-18 A.F. BC113/114	0.50
U 42	40 Btl. Trans. Plastic TO-5 BC115/NPN	0.50
U 43	7 3A SCR. TO66 up to 600PIV	1.00

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

### SILICON PHOTO TRANSISTOR, TO-18 Lens and NPN Sim. to BP X25 and P21

BRAND NEW! Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 35p

### F.E.T.'S

2N3819	35p	2N5458	50p
2N3820	50p	2N5459	40p
2N3821	35p	BPW10	40p
2N3823	35p	MPP105	40p

## NEW EDITION 1971

**TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

**A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.**

## QUALITY TESTED SEMICONDUCTORS

Pak No.	Contents	Price
Q1	20 Red spot transistors PNP	0.50
Q2	16 White spot R.F. transistors PNP	0.50
Q3	4 OC 77 type transistors	0.50
Q4	6 Matched transistors OC44/45/81/81D	0.50
Q5	4 OC 75 transistors	0.50
Q6	5 OC 72 transistors	0.50
Q7	4 AC 128 transistors PNP high gain	0.50
Q8	4 AC 126 transistors PNP	0.50
Q9	7 OC 81 type transistors	0.50
Q10	7 OC 71 type transistors	0.50
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0.50
Q12	3 AF 116 type transistors	0.50
Q13	3 AF 117 type transistors	0.50
Q14	3 OC 171 H.F. type transistors	0.50
Q15	7 2N2926 811. Epoxy transistors mixed colours	0.50
Q16	2 GET880 low noise Germanium transistors	0.50
Q17	5 NPN 2 x ST.141 & 3 x ST.140.	0.50
Q18	4 MADDT'S 2 x MAT 100 & 2 x MAT 120	0.50
Q19	3 MADDT'S 2 x MAT 101 & 1 x MAT 121	0.50
Q20	4 OC 44 Germanium transistors A.F.	0.50
Q21	4 AC 127 NPN Germanium transistors	0.50
Q22	20 NKT transistors A.F. H.F. cooled	0.50
Q23	10 OA 202 Silicon diodes sub-min.	0.50
Q24	8 OA 81 diodes	0.50
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0.50
Q26	8 OA95 Germanium diodes sub-min. IN669	0.50
Q27	2 10A PIV Silicon rectifiers 1842B	0.50
Q28	2 Silicon power rectifiers BYZ 13	0.50
Q29	4 Silicon transistors 2 x 2N696. 1 x 2N697. 1 x 2N698	0.50
Q30	7 Silicon switch transistors 2N706 NPN	0.50
Q31	6 Silicon switch transistors 2N705 NPN	0.50
Q32	3 PNP Silicon transistors 2 x 2N1131. 1 x 2N1132	0.50
Q33	3 Silicon NPN transistors 2N1711	0.50
Q34	7 Silicon NPN transistors 2N2369. 5000Hz (code P37)	0.50
Q35	3 Silicon PNP TO-5. 2 x 2N2904 & 1 x 2N2905	0.50
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0.50
Q37	3 2N3053 NPN Silicon transistors	0.50
Q38	7 NPN transistors 4 x 2N3703. 3 x 2N3702	0.50

## ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales—Conversion of Frequency and Wavelength. Calculation of L, C and f of Tuned Circuits. Resistance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and e Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2 cm x 4cm. Complete with case and instructions. Price each: £3.35

## INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	12 x 7400	0.50	UIC46	5 x 7448	0.50	UIC86	5 x 7486	0.50
UIC01	12 x 7401	0.50	UIC47	5 x 7447	0.50	UIC87	5 x 7480	0.50
UIC02	12 x 7402	0.50	UIC48	5 x 7448	0.50	UIC91	5 x 7491	0.50
UIC03	12 x 7403	0.50	UIC49	5 x 7450	0.50	UIC92	5 x 7492	0.50
UIC04	12 x 7404	0.50	UIC51	12 x 7451	0.50	UIC93	5 x 7493	0.50
UIC05	12 x 7405	0.50	UIC53	12 x 7453	0.50	UIC94	5 x 7494	0.50
UIC06	8 x 7406	0.50	UIC54	12 x 7454	0.50	UIC95	5 x 7495	0.50
UIC07	8 x 7407	0.50	UIC60	12 x 7460	0.50	UIC96	5 x 7496	0.50
UIC10	12 x 7410	0.50	UIC70	8 x 7470	0.50	UIC100	5 x 74100	0.50
UIC13	8 x 7413	0.50	UIC72	8 x 7472	0.50	UIC121	5 x 74121	0.50
UIC20	12 x 7420	0.50	UIC73	8 x 7473	0.50	UIC141	5 x 74141	0.50
UIC30	12 x 7430	0.50	UIC74	8 x 7474	0.50	UIC151	5 x 74151	0.50
UIC40	12 x 7440	0.50	UIC75	8 x 7475	0.50	UIC154	5 x 74154	0.50
UIC41	5 x 7441	0.50	UIC76	8 x 7476	0.50	UIC193	5 x 74193	0.50
UIC42	5 x 7442	0.50	UIC80	5 x 7480	0.50	UIC199	5 x 74199	0.50
UIC43	5 x 7443	0.50	UIC81	5 x 7481	0.50			
UIC44	5 x 7444	0.50	UIC82	5 x 7482	0.50			
UIC45	5 x 7445	0.50	UIC83	5 x 7483	0.50			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

**BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES—18 BALDOCK STREET (A10), WARE, HERTS. TEL. (STD 0920) 61593. OPEN MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY UNTIL 8 p.m.**

All mail orders please add 10p post and packing. Send all orders to BI-PAK P.O. Box 6, WARE, HERTS.

All mail orders please add 10p post and packing. Send all orders to BI-PAK P.O. BOX 6, WARE, HERTS.

# -the lowest prices!

## 74 Series T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS



	1	25	100+
SN7400	0.15	0.14	0.12
SN7401	0.15	0.14	0.12
SN7402	0.15	0.14	0.12
SN7403	0.15	0.14	0.12
SN7404	0.15	0.14	0.12
SN7405	0.15	0.14	0.12
SN7406	0.35	0.31	0.28
SN7407	0.35	0.31	0.28
SN7408	0.18	0.17	0.16
SN7409	0.18	0.17	0.16
SN7410	0.15	0.14	0.12
SN7411	0.25	0.24	0.23
SN7412	0.35	0.31	0.28
SN7413	0.29	0.26	0.24
SN7414	0.43	0.40	0.38
SN7417	0.43	0.40	0.38
SN7420	0.15	0.14	0.12
SN7422	0.50	0.48	0.45
SN7423	0.50	0.48	0.45
SN7425	0.50	0.48	0.45
SN7427	0.45	0.42	0.40
SN7428	0.70	0.65	0.60
SN7430	0.15	0.14	0.12
SN7432	0.45	0.42	0.40
SN7433	0.80	0.75	0.70
SN7437	0.64	0.62	0.60
SN7438	0.64	0.62	0.60
SN7440	0.15	0.14	0.12
SN7441	0.67	0.64	0.58
SN7442	0.67	0.64	0.58
SN7443	£1.30	£1.25	£1.20
SN7444	£1.30	£1.25	£1.20
SN7445	£1.80	£1.77	£1.75
SN7446	0.97	0.94	0.95
SN7447	£1.00	0.97	0.95
SN7448	£1.00	0.97	0.95
SN7450	0.15	0.14	0.12
SN7451	0.15	0.14	0.12
SN7453	0.15	0.14	0.12
SN7454	0.15	0.14	0.12
SN7460	0.15	0.14	0.12
SN7470	0.29	0.26	0.24

	1	25	100+
SN7472	0.29	0.26	0.24
SN7473	0.37	0.35	0.32
SN7474	0.37	0.35	0.32
SN7475	0.45	0.43	0.42
SN7476	0.40	0.39	0.38
SN7480	0.87	0.84	0.85
SN7481	£1.20	£1.15	£1.10
SN7482	0.87	0.86	0.85
SN7483	£1.10	£1.05	£1.05
SN7484	£1.00	0.95	0.90
SN7485	£3.60	£3.50	£3.40
SN7486	0.32	0.31	0.30
SN7489	£5.50	£5.25	£5.00
SN7490	0.87	0.84	0.80
SN7491	£1.00	0.95	0.90
SN7492	0.87	0.84	0.85
SN7493	0.87	0.84	0.85
SN7494	0.77	0.74	0.78
SN7495	0.77	0.74	0.68
SN7496	0.87	0.84	0.78
SN74100	£1.65	£1.60	£1.55
SN74104	0.97	0.94	0.88
SN74105	0.87	0.84	0.85
SN74107	0.40	0.39	0.38
SN74110	0.55	0.53	0.50
SN74111	£1.25	£1.15	£1.10
SN74118	£1.00	0.95	0.90
SN74119	£1.35	£1.25	£1.10
SN74121	0.40	0.37	0.34
SN74122	£1.40	£1.30	£1.20
SN74123	£2.80	£2.70	£2.60
SN74141	0.87	0.84	0.85
SN74145	£1.50	£1.40	£1.30
SN74150	£3.00	£2.70	£2.50
SN74151	£1.00	0.95	0.90
SN74153	£1.20	£1.10	0.95
SN74154	£1.80	£1.70	£1.60
SN74155	£1.40	£1.30	£1.20
SN74156	£1.40	£1.30	£1.20
SN74157	£1.90	£1.80	£1.70

## LINEAR I.C.'s—FULL SPEC.

Type No.	1-24	25-99	100 up
BP 201C—SL201C	63p	53p	45p
BP701C—SL701C	63p	50p	45p
BP 702C—SL702C	63p	50p	45p
BP 702—72702	53p	45p	40p
BP709—72709	35p	34p	30p
BP 709P—LA709C	36p	34p	30p
BP 710—72710	44p	42p	40p
BP 711—LA711	45p	43p	40p
BP 741—72741	75p	60p	50p
LA703C—LA703C	25p	26p	24p
TAA 283	70p	69p	65p
TAA 293—	90p	75p	70p
TAA 350	170p	158p	150p

E.G.S. EA1000 2-63

## ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type No.	1-24	25-99	100 up
BP930	12p	11p	10p
BP932	13p	12p	11p
BP933	13p	12p	11p
BP935	13p	12p	11p
BP936	13p	12p	11p
BP944	13p	12p	11p
BP945	22p	24p	22p
BP946	12p	11p	10p
BP948	25p	24p	22p
BP951	65p	60p	55p
BP962	12p	11p	10p
BP9093	46p	38p	35p
BP9094	46p	38p	35p
BP9097	46p	38p	35p
BP9099	46p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

## NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015F Minitron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2-3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0.9 + Decimal point. All side viewing. Full data for all types available on request.

## RTL MICROLOGIC CIRCUITS

	Price each
Epoxy TO-5 case	1-24 25-99 100 up
uL900 Buffer	35p 33p 27p
uL914 Dual 2/p gate	35p 33p 27p
uL923 J-K flip-flop	50p 47p 45p

Date and Circuits Booklet for IC's Price 7p.

## DUAL IN LINE SOCKETS.

14 & 15 Lead Sockets for use with DUAL-IN-LINE I.C.'s. TWO Ranges PROFESSIONAL & NEW LOW COST. PROF. TYPE No. 1-24 25-99 100up. TSO 14 pin type 20p 27p 25p. TSO 16 " " 25p 32p 30p.

LOW COST No.	15p	18p	11p
BPS 14	15p	18p	11p
BPS 16	16p	14p	12p


## BI-PAK DO IT AGAIN!

# 50W pk 25w (RMS)

0.1% DISTORTION!  
HI-FI AUDIO AMPLIFIER
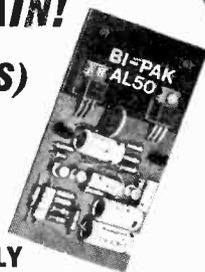
## THE AL50

- ★ Frequency Response 15Hz to 100,000—1dB. **ONLY £3.25p each**
- ★ Load—3, 4, 8 or 16 ohms.
- ★ Distortion—better than 1% at 1KHz.
- ★ Signal to noise ratio 80dB.
- ★ Supply voltage 10-35 Volts.
- ★ Overall size 63mm x 105mm x 13mm.



Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT—TESTED—GUARANTEED.

## STABILISED POWER MODULE SPM80



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disc Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £2.95**

TRANSFORMER BMT80 £1.95 p. & p. 25p.

## STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



### SPECIFICATION

Frequency Response	20Hz — 20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs : 1. Tape Head	1-25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1-5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters : Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than — 65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm

**ONLY £11.95**

**SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23.00 FREE p. & p.**

All prices quoted in new pence Giro No. 388-7006  
Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 7p. Overseas add extra for airmail.  
Minimum order, 50p. Cash with order please.

**Guaranteed Satisfaction or Money Back**

# NEW! FROM ADCOLA

## THE BEST IN SOLDERING KITS

Styrene packed with see-through top  
Makes the perfect gift!





**Contents**  
**BOX OF SOLDER**  
**TWO SPARE BITS**  
**HINTS ON SOLDERING**  
**686 SOLDERING STAND**  
**646 INVADER SOLDERING TOOL**

### Built to world safety standards

The Adcola Invader Soldering Kit comes to you in a presentation pack!  
 The 'READY TO USE KIT' offers maximum versatility of a 23 watt soldering instrument.

**only £3.99**

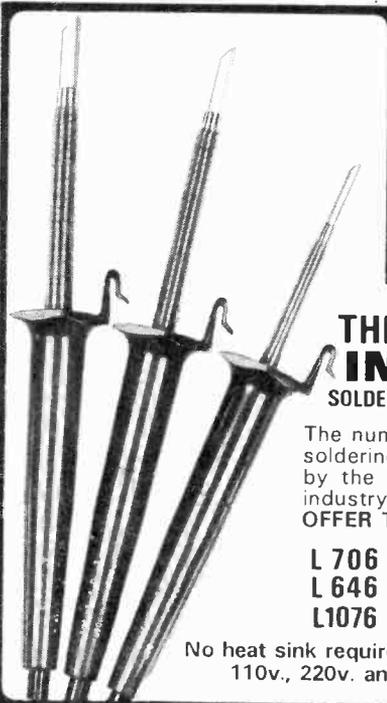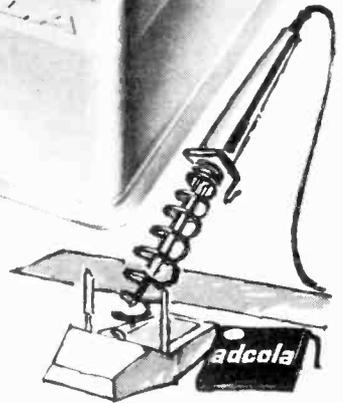

### THE FABULOUS INVADERS

SOLDERING INSTRUMENTS

The number one accepted soldering instrument used by the professional in industry. IS NOW ON OFFER TO YOU.

- L 706 19 watts £1.96
- L 646 23 watts £2.12
- L1076 27 watts £2.18

No heat sink required. Stock voltages 110v., 220v. and 230/250v.

### L686 SOLDERING INSTRUMENT STAND



The perfect instrument stand for your 'Invader'.

**£1.71**

### MULTI-CHANNELLED SOLDER



Pre fluxed solder 'READY TO USE' produced to B.S.I. 441 IN HANDY SIZES. **£0.41 and £1.16**

PLEASE SEND ME THE FOLLOWING ITEMS

NAME & ADDRESS \_\_\_\_\_

INVADER SOLDERING KIT

1076 'INVADER' \_\_\_\_\_

646 'INVADER' \_\_\_\_\_

706 'INVADER' \_\_\_\_\_

686 SOLDERING STATION \_\_\_\_\_

1/2 kg SOLDER REEL \_\_\_\_\_

SMALL SOLDER REEL \_\_\_\_\_

Postage & packing add 10p. free over £2

Enclosing P/O and cheque



ADCOLA PRODUCTS LTD. ADCOLA HOUSE  
 GAUDEN ROAD LONDON, SW4 6LH  
 TELEPHONE: 01-622-0291/3

PW

# PRACTICAL WIRELESS

VOL 48 NO 7

Issue 789

NOVEMBER 1972

## Is Ignorance Bliss?

MORE than £100,000,000's-worth of audio equipment, half of which is hi-fi, is being sold in the UK every year. But according to the findings of the commercial research department of Philips Electrical, who published details of a survey earlier this year, this buoyant industry thrives in a sea of appalling ignorance.

The report doesn't mince words. It says that "*the level of ignorance encountered in a number of shops was startling*". Many of them had inadequate audio facilities and expertise. When questioned, most dealers considered that the most important factor was the price, this being considered far ahead of design and performance.

This will come as no surprise to knowledgeable types who have had to buy goods from such shops. But the report goes on to say that the customers' largest single source of information is not from friends, magazines, sales literature or advertisements, but from dealers. It goes without saying, then, that in this classic example of the blind leading the blind, the average customer comes out of the ordeal in a state of mental fog.

To quote from the results of random samples: 44% did not know whether their cartridge was magnetic or ceramic; 75% did not know the frequency response of their amplifier; 60% could not give the audio output, and of those who could, 33% did not know if the figure was r.m.s. or music rating. Of more pertinent interest is that many people do not know whether or not they are listening to stereo. Many thought they were hearing stereo on Radios 1 and 2 and 75% of intending buyers interviewed thought they heard stereo on Radio 1!

It does not need a research team to expose the sad lack of competence (and, often, interest) in many shops, and it follows logically that many customers must be similarly ill-informed. However, we feel that there is a dividing line between the depth of knowledge a customer needs to use his equipment properly and the knowledge which is simply a technical luxury. In view of this, we were delighted to read that, despite the epidemic of ignorance, 64% of customers were "very satisfied" with their equipment.

One trade journal has suggested that we want a "*big effort to create more unsatisfied customers*". However, although we want people to appreciate good sound reproduction, is it ethical to unsettle people who are perfectly content with their equipment in order to gain a few more kHz and a little less distortion which they probably could not distinguish? In general we are against ignorance but sometimes, especially in audio, it can be bliss!

W. N. STEVENS—*Editor*.

## NEWS AND COMMENT

Leader	587
News . . . News . . . News	588
MW Column by <i>Charles Molloy</i>	610
Letters	618
Electronotes by <i>S. Ginsberg</i>	625
CQ! CQ! CQ!	625, 642
Practically Wireless by <i>Henry</i>	626
On the Short Waves by <i>Malcolm Connah and David Gibson, G3JDG</i>	629

## CONSTRUCTIONAL

Reverberation Unit Part 1, by <i>F. C. Judd</i>	590
The Progressive Six by <i>F. G. Rayer</i>	597
8W Silicon Amplifier by <i>F. C. Judd</i>	606
Take 20, No. 42, "Hunt the Bleeper" by <i>Julian Anderson</i>	612
IC Stabilised Power Supplies by <i>D. J. Silvester</i>	613
Simple R.F. Signal Generator by <i>Halvor Moorshead</i>	621

## OTHER FEATURES

Transistor Circuitry for Beginners, Part 12 by <i>H. W. Hellyer and Michael Hollier</i>	633
Going Back by <i>Colin Riches and Arthur Dow</i>	641

## SUPPLEMENT

The ABC of Hi-Fi by *Gordon J. King*

**THE DECEMBER ISSUE WILL BE  
PUBLISHED ON NOVEMBER 3rd**

©IPC Magazines Limited 1972. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

### Mini calculator

Sinclair Radionics Ltd., announce the world's smallest electronic calculator, just over 1/4 in. thick,

The Sinclair "Executive" performs all the functions of large desk machines although it is only 2 inches wide by 5 1/2 inches long. The total weight, including batteries, is 2 1/2 ounces. The illuminated display has a capacity of 8 digits and the machine will add, subtract, divide and multiply virtually instantaneously. Other features include automatic squaring, reciprocals, fixed or floating decimal point operation, and a memory for locking in instructions to repeatedly multiply or divide by a pre-determined factor.

This calculator uses a single MOS chip containing 7,000 transistors. Normally this type of I.C. consumes in the region of 350mW which alone would rule out a really slim pocket calculator because of the large batteries that would be required. The Sinclair calculator, however, includes a special circuit (patents applied for) which reduces the consumption to an average of only about 20mW. This is achieved in two ways; firstly by switching off the I.C. completely in between clock pulses, relying on the capacitance associated with the active elements to store the information, and secondly by reducing the clock rate considerably (and hence the "on" period) when the calculator is not actually performing a calculation.

Another factor contributing to the low overall power of the calculator is the way in which the display is driven. The battery voltage is chosen so that it is just sufficient to drive the monolithic gallium arsenide phosphide display directly so that no power is wasted in large dropper resistors. Indeed no such resistors are used at all as the display is driven directly from the chip. The batteries themselves are three tiny mercury cells of the type commonly used in hearing aids. These provide 20 hours of life.

The keyboard, another item which contributes to the thick-



ness of competitive machines, was specially developed for this calculator and is extremely thin, being only 4mm in depth. Price is £79 and every unit is guaranteed five years. Sinclair Radionics Limited, London Road, St. Ives, Huntingdonshire PE 17 4HJ. St. Ives (04806) 4311.

### Texan Reprints

Reprints of the "Texan" 20+20W Stereo Amplifier are now available.

They may be obtained by sending 35p (30p + 5p postage/packing) to Practical Wireless Editorial, Fleetway House, Farringdon Street, London, EC4A 4AD. — Hurry the demand will be great!

### Sheffield exhibition

Sheffield Education Committee will be holding an exhibition next month with the theme "Communications Today" at the Yewlands Comprehensive School, Creswick Lane, Grenoside, Sheffield, S30 3NN.

The dates of the exhibition are Friday and Saturday 3rd and 4th November and further information may be obtained from J. M. Nicholson, M.A., at the Yewlands School, telephone Ecclesfield 3778 (from London the code is 074 15 3778).

### Record care

New from Bib is the Record Care Kit Ref. 43. Contained in a presentation 3-colour printed see-through box will be a new all-chrome finish Groov-Kleen Automatic Record Cleaner incorporating counterweight, arm-rest and all the features of the other two Bib Groov-Kleen's Models 42 and 50, turntable spirit level, plastic record dust-off, stylus & turntable cleaning liquid, right angle cleaning brush suitable for stylus and Groov-Kleen pad, and a turntable cleaning cloth. Recommended retail price for the Record Care Kit Ref. 43 is £2.49, including P.T.



# NEWS...

# NEWS...

# NEWS...

## Siemens equipment

The first Siemens record player to become available in the UK is announced by Interconti Electronics, who also announce the introduction of the RS303 tuner amplifier.

The RW346 stereo record player, comes complete with plinth and a protective dust cover. The arm is fitted with Shure magnetic pickup system and diamond stylus. The cabinet is available either in white or a light satinwood finish.

The recommended retail price of the unit is £100.66p.

The RS303 tuner amplifier to which the RW346 can be linked, is a stereo drive unit providing quadrosound reproduction. The receiver is equipped with built-in antennae covering all wave ranges. Station selection in the f.m. range is accomplished easily by using the five pre-set tuners each of which is tuned by a given control button. Price is £180. *Interconti Electronics Ltd., Albany House, Petty France, London, S.W.1.*



## R.F. signal generator

Taylor Electrical Instruments have introduced the re-styled 68A/M Mk 11 signal generator which covers 100kHz to 240MHz in eight switched ranges with 30% internal amplitude modulation between 50Hz and 5kHz. All controls and sockets are panel mounted and include Set r.f. Level (with meter indication), Set a.f. Level, r.f. Output (switched 1-10), Attenuator (0 to -80dB.).

## Stubec Radio

The above company have published a new catalogue which contains details and prices of radio components and special details of do-it-yourself loudspeaker components and grill fabrics.

For your copy of this catalogue, send a stamped addressed foolscap envelope to: *Stubec Audio, 2 St. Faith's Street, Maidstone, Kent.*

## Strobe unit

Dave Instruments Limited announce stroboscope, Type



1209D. In addition to the many features of the well established Transistor Strobflash, the new design provides a high sensitivity input (minimum external trigger: 200mV r.m.s.) which enables the Strobflash to be triggered directly from such sources as vibration meters, vibration analysers or from an electromagnetic pickup.

The Strobflash produces a high intensity white light and is capable of directly measuring the speed of any shaft or rotating part within the range 300 rev/min to 18,000 rev/min. The very short duration of the light flashes makes it possible to measure speeds up to 180,000 rev/min! *Dave Instruments Ltd., Western Avenue, London, W3 OSD.*

## "RP75"



The Super Sovereign RP75 covers medium, long, two short and f.m. bands and it's the latest in the Hacker range of portable radios, taking over from the well-known Hacker "Sovereign." Retail price is £69.


## COME AND SEE US AT THE "AUDIO FAIR" . . .

Practical Wireless will be on Stand 18 (ground floor) at the International Audio Festival and Fair, Olympia from October 23rd-28th.

One of the highlights of our stand will be a display devoted to the "TEXAN" 20+20W Stereo Amplifier. You will also be able to get a reprint of the "TEXAN" for 30p.

Amongst other items featured, there will be a Reverberation Unit, Loud-Hailer, Buzz-Bar, Car Radio, Miniature Organ, Radio Transmitter, Receiver, Power Supply and Audio Test Instruments.

# Reverberation Unit

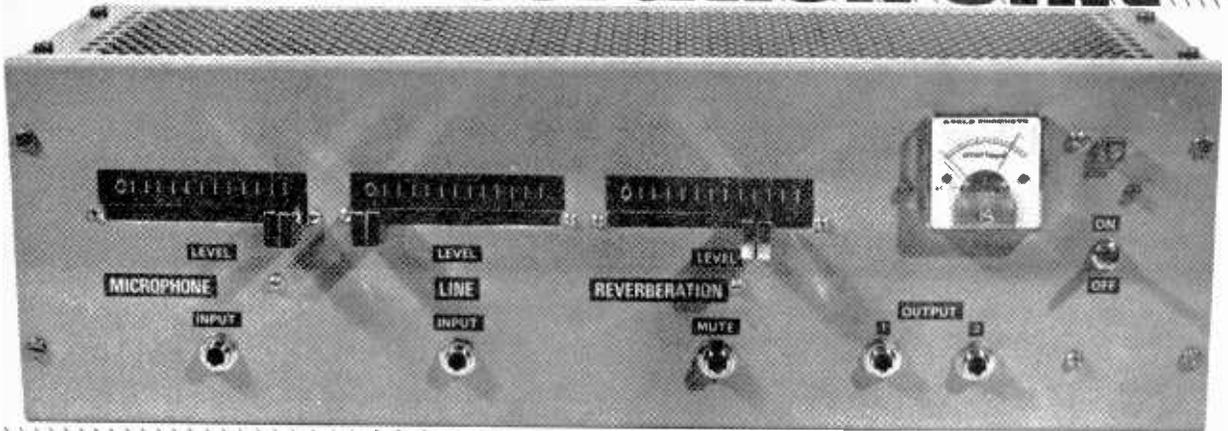

F.C. JUDD

## PART ONE

**R**EVERBERATION is an acoustical effect caused by the reflection of sound from hard surfaces within an enclosed space such as a large room or hall containing little sound absorbing material such as carpeting and padded furniture etc. The reflections become multiplied as the sound bounces from surface to surface and reaches the ears as a series of echoes of very short duration. The overall effect however, is a sustained sound because the reflections may take a considerable time to die away completely, depending on the volume of the enclosed space. In a very large hall the dying away, or decay time, may be as much as several seconds. Reverberation is quite unlike the more distinct single echoes caused by sound reflection in the open air from a single surface, such as a large building, or the echo effect produced by feeding a recorded signal from tape back into the recording amplifier.

### Spring Line Reverberation

Reverberation is quite easy to produce artificially. All that is required is a) a means of obtaining a series of echoes of short duration, of a few milliseconds in fact, and b) a means of sustaining repetition of the echoes for at least two seconds. A length of coiled springy wire will do this if it is mechanically excited at one end; this can be done by using a simple electromagnetic sound transducer. The speed of sound vibration up and down the spring line is very slow when compared with the speed of elec-

## Specification

Microphone Sensitivity	0.5mV for 800mV output (without reverb)
Line Input Sensitivity	200mV for 800mV output (without reverb)
Microphone Input Impedance	Nominal 100kΩ
Line Input Impedance	Nominal 10kΩ
Output Impedance	Nominal 5kΩ
Frequency Response (without reverb)	20Hz to 20kHz, either input
Signal to Noise (without reverb)	Microphone: -60dB
Distortion Factor (without reverb)	Line: -80dB
Reverb Delay Time	Less than 0.5 per cent
	Approx 2 seconds maximum

trical sound through wires. The spring line offers little resistance to vibration travelling along it and because of this the vibrations will continue to travel up and down the line for some time. The strength of the vibrations do, however, decrease slowly and eventually cease altogether.


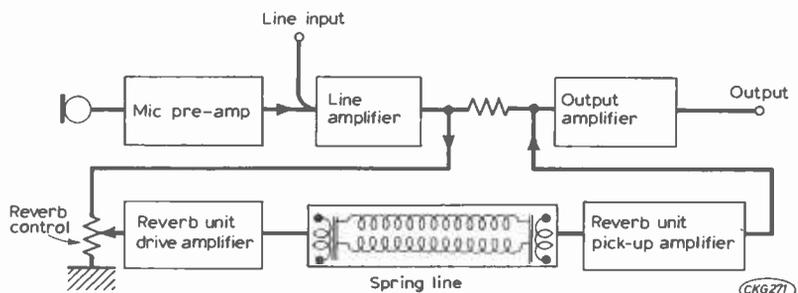


Fig. 1: Block diagram of the spring line reverberation unit.

CKG271

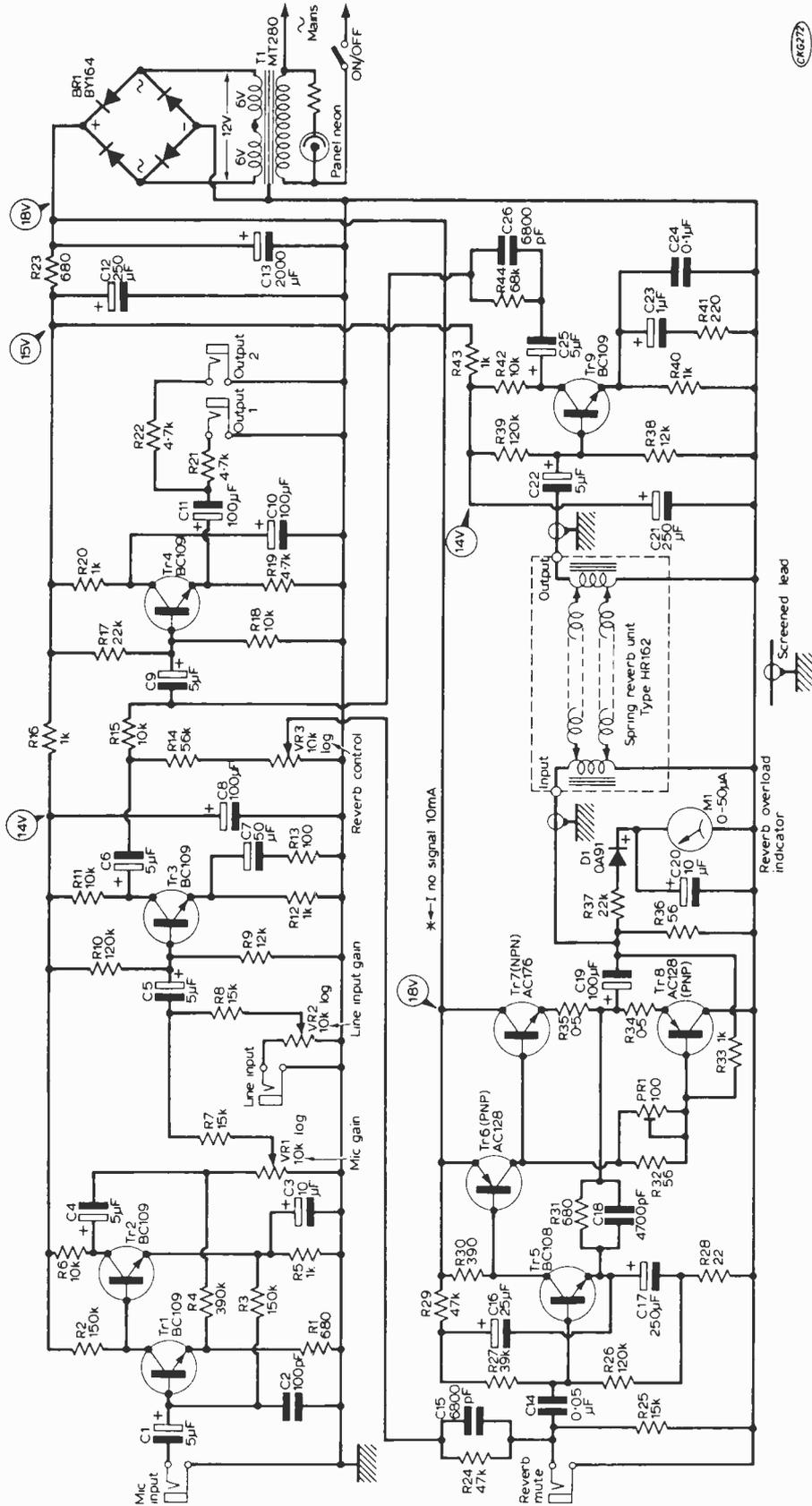

86272

Fig. 2: Circuit diagram of the complete reverbation unit.

## The complete reverberation unit

The block diagram in Fig. 1 will help to clarify the principle of a spring line reverb system. First the direct signals from a microphone or other external signal source are taken into the appropriate input. These are amplified and taken both to the output amplifier and to the spring line driving amplifier. The output from the latter drives the spring line and the reverberated signals are taken from the other end of the line, amplified and mixed with the direct signal. The output signal is therefore a mixture of both direct and delay signals. A control is inserted so that the level of signal from the reverberation circuit can be adjusted to provide different reverberation levels or it can be cut off altogether. One can simulate the short reverberation of a small room or the long sustained reverberation of a large hall.

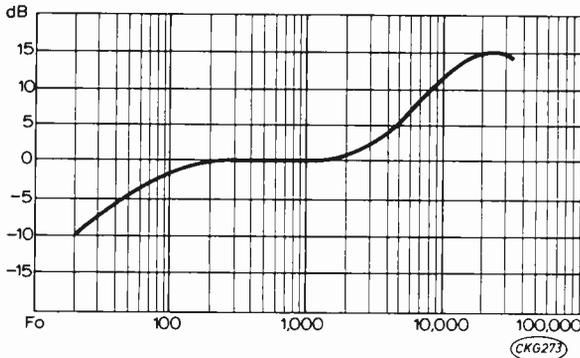


Fig. 3: Frequency response of the spring line driver amplifier.

## The Circuit

The complete circuit is given in Fig. 2. The microphone preamplifier Tr1 and Tr2 is suitable for microphones of 200-600Ω, or low impedance microphones with a matching transformer, or with a crystal microphone. The output from this is taken to a passive mixing network via the microphone gain control VR1. The line level signal input, suitable for any linear signals from about 200mV upward, is taken via the line input gain control VR2 and thence to the passive mixing network R7 and R8.

The mixing network losses are recovered by the amplifier Tr3 and the output from this is taken via a passive network to a) the output emitter follower stage Tr4 and b) to the reverb unit driving amplifier Tr5, Tr6, Tr7 and Tr8. This amplifier delivers around 1W at full reverb i.e., with the reverb control VR3 at maximum. The amplifier also has a special frequency response as shown in Fig. 3 to suit the response require-

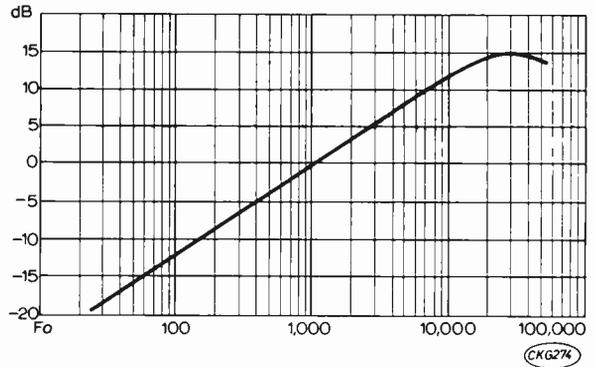


Fig. 4: Frequency response curve of the reverb output amplifier.


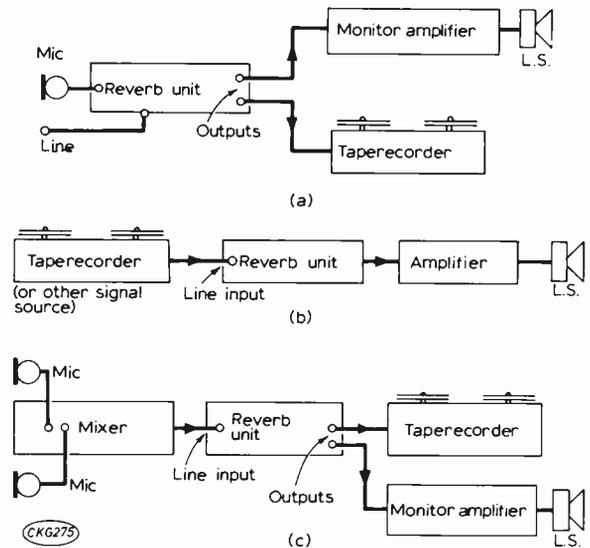


Fig. 5: Ways of using the spring line reverb unit.

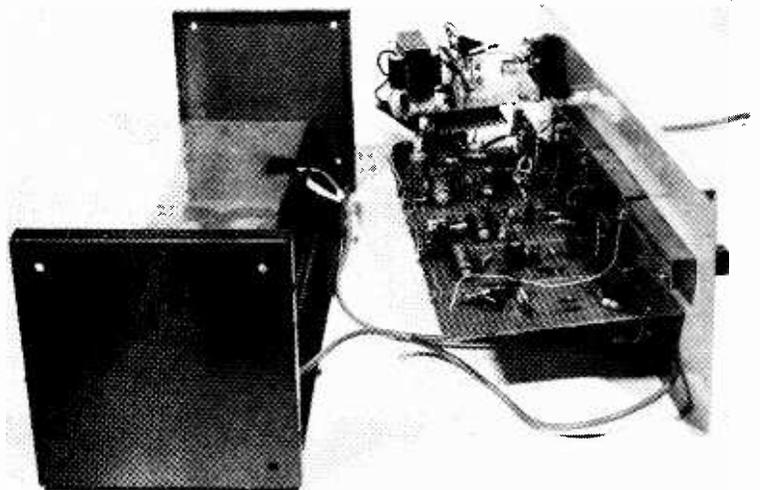

A view of the prototype showing the delay line at the bottom of the case with the electronic components mounted on the back of the front panel.

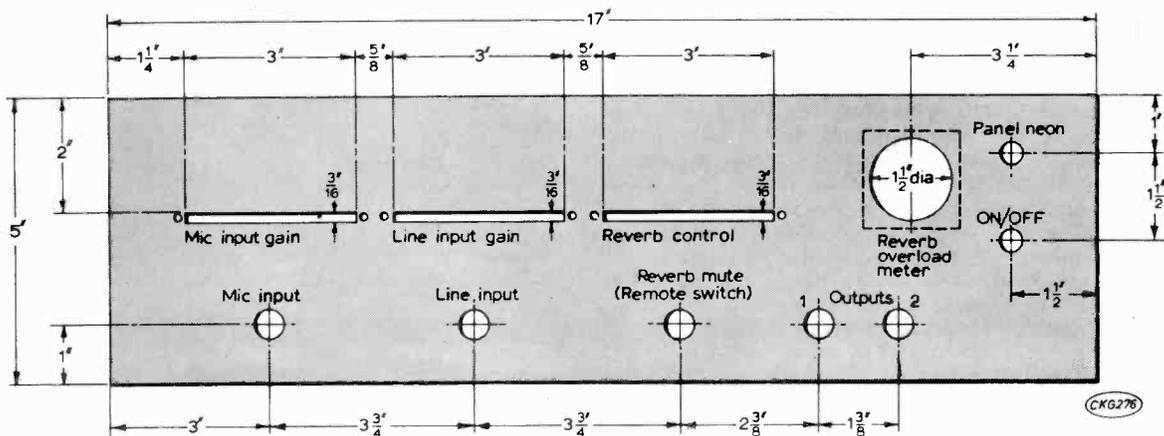


Fig. 6: Details of the front panel component positions and the drilling dimensions

ments of the spring line driving transducer.

The output from the driving amplifier is taken to the spring line unit socket marked 'Input' and also to the reverb overload meter circuit R37, D1, C20 and the 50 $\mu$ A meter. The use of the meter will be explained later.

The output from the spring line unit, from the socket marked 'Output', is taken to the amplifier Tr9 which also has a special frequency response as shown in Fig. 4. The signal from this amplifier is then taken to the emitter follower output stage Tr4.

The output from Tr4 is split to two output sockets, both of which can be used to feed a tape recorder and/or amplifier, or two tape recorders, or amplifiers as required and as shown in Fig. 5.

The reverb unit is mains operated by the trans-

former T1, bridge rectifier BR1 and smoothing network C13, R23, and C12. The supply rail at C13 is 18V positive and this goes direct to the spring line driving amplifier. Further smoothing is needed for the signal amplifier stages, hence the addition of R23 and C12 from which the supply rail is 15V positive. Note that the transformer MT280 has two 6V secondary windings which are connected in series to provide 12V to the bridge rectifier BR1.

## Construction

The spring line reverb unit is a type HR162 (Henry's Radio Limited) and is 167 $\frac{7}{8}$ in long. This will just fit into a Lektrokit case (17in long) in which the prototype unit as shown in the photos was built

## ★ components list

### Resistors

R1 680 $\Omega$	R16 1k $\Omega$	R31 680 $\Omega$
R2 150k $\Omega$	R17 22k $\Omega$	R32 56 $\Omega$
R3 150k $\Omega$	R18 10k $\Omega$	R33 1k $\Omega$
R4 390k $\Omega$	R19 4.7k $\Omega$	R34 0.5 $\Omega$
R5 1k $\Omega$	R20 1k $\Omega$	R35 0.5 $\Omega$
R6 10k $\Omega$	R21 4.7k $\Omega$	R36 56 $\Omega$
R7 15k $\Omega$	R22 4.7k $\Omega$	R37 22k $\Omega$
R8 15k $\Omega$	R23 680 $\Omega$	R38 12k $\Omega$
R9 12k $\Omega$	R24 47k $\Omega$	R39 120k $\Omega$
R10 120k $\Omega$	R25 15k $\Omega$	R40 1k $\Omega$
R11 10k $\Omega$	R26 120k $\Omega$	R41 220 $\Omega$
R12 1k $\Omega$	R27 39k $\Omega$	R42 10k $\Omega$
R13 100 $\Omega$	R28 22 $\Omega$	R43 1k $\Omega$
R14 56k $\Omega$	R29 47k $\Omega$	R44 68k $\Omega$
R15 10k $\Omega$	R30 390 $\Omega$	

All resistors  $\frac{1}{4}$ W, 5 per cent tolerance except R34 and R35 which are 1W.

### Capacitors

C1 5 $\mu$ F	C10 100 $\mu$ F	C19 100 $\mu$ F
C2 100pF	C11 100 $\mu$ F	C20 10 $\mu$ F
C3 10 $\mu$ F	C12 250 $\mu$ F	C21 250 $\mu$ F
C4 5 $\mu$ F	C13 2000 $\mu$ F	C22 5 $\mu$ F
C5 5 $\mu$ F	C14 0.05 $\mu$ F	C23 1 $\mu$ F
C6 5 $\mu$ F	C15 6800pF	C24 0.1 $\mu$ F
C7 50 $\mu$ F	C16 25 $\mu$ F	C25 5 $\mu$ F
C8 100 $\mu$ F	C17 250 $\mu$ F	C26 6800pF
C9 5 $\mu$ F	C18 4700pF	

All values above 1 $\mu$ F are electrolytic types and should have a working voltage of at least 25V, except C13 which should be at least 35V. Values below 1 $\mu$ F can be any type, Mylar, ceramic etc.

### Semiconductors

Tr1 BC109	Tr5 BC108	Tr9 BC109
Tr2 BC109	Tr6 AC128	BR1 BY164 or similar silicon bridge rectifier (40V, 1.5A)
Tr3 BC109	Tr7 AC176	
Tr4 BC109	Tr8 AC128	

### Miscellaneous

VR1, VR2 and VR3	Each 10k $\Omega$ log. Slider types Eagle RR11
PR1	100 $\Omega$ preset carbon type
Spring Line Unit	Type HR162 (Henry's Radio Ltd.)
Transformer T1	240V primary, 6V + 6V secondary, 280mA (Eagle Type MT280)
Neon	Panel type (prototype is Eagle RR30)
On-off switch SW1	Toggle type
Overload Meter M1	50 $\mu$ A, Eagle type MR2P
Jack Sockets	5-off required
Phono Plugs	2-off required

**Case** Lektrokit, 17 x 5 x 5in. Made up from Front panel (1) LK401, Side Plates (2) LK311, Top, Back and Bottom Plates (3) LK501.

**Circuit Board** Available from Home Radio Plain Veroboard, 0.15in. matrix, see text

**Aluminium** 16s.w.g. (for heatsink and power supply chassis);  $\frac{3}{8}$  x  $\frac{3}{8}$ in. angle.

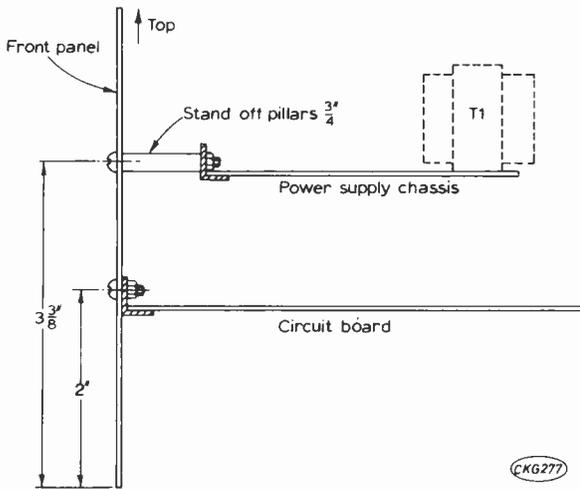


Fig. 7 (left): Location of the main circuit board and the power supply chassis behind the front panel.

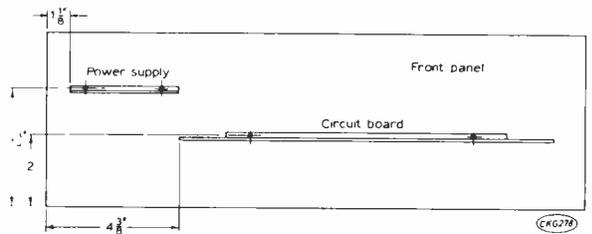


Fig. 8 (above): Rear view of the front panel showing the siting of the circuit boards.


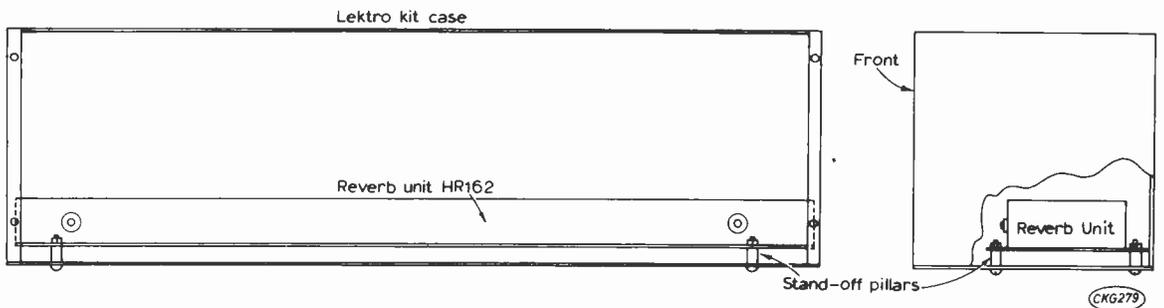


Fig. 9 (above): Siting of the spring line unit within the case.

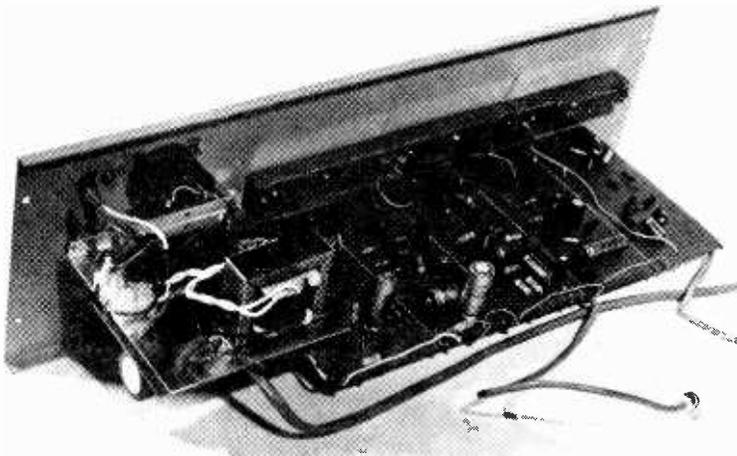

On the left is shown a view of the prototype illustrating the siting of the component boards.

(see components list for details of the Lektrokit case which is 17×5×5in). A similar metal case of the same dimensions could of course be used.

Details for drilling the front panel to accommodate the slider type controls and signal sockets etc. are given in Fig. 6. The size of the hole for the overload meter will depend on the meter used but it must be a 50 $\mu$ A type.

The circuit board containing all the amplifier stages is mounted behind the front panel as shown in Figs. 7 and 8. The power supply is assembled as a separate chassis and this is mounted as shown. The spring line unit is mounted at the bottom and rear of the case and raised slightly on stand-off pillars as shown in Fig. 9 and with the output and input sockets facing towards the front.

The next stage is the circuit board which is 10 $\frac{7}{8}$ ×5in. and is mounted on the front panel by means of  $\frac{3}{8}$ × $\frac{3}{8}$ in. aluminium angle and the stand-off pillars as in Fig. 7. Note that Tr7 and Tr8 must be mounted on a heatsink as in Fig. 10 which is made of 16 s.w.g. aluminium to the dimensions given.


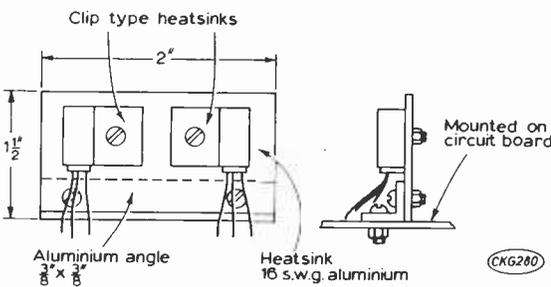


Fig. 10: Details of the heatsink for Tr7 and Tr8.

TO BE CONTINUED

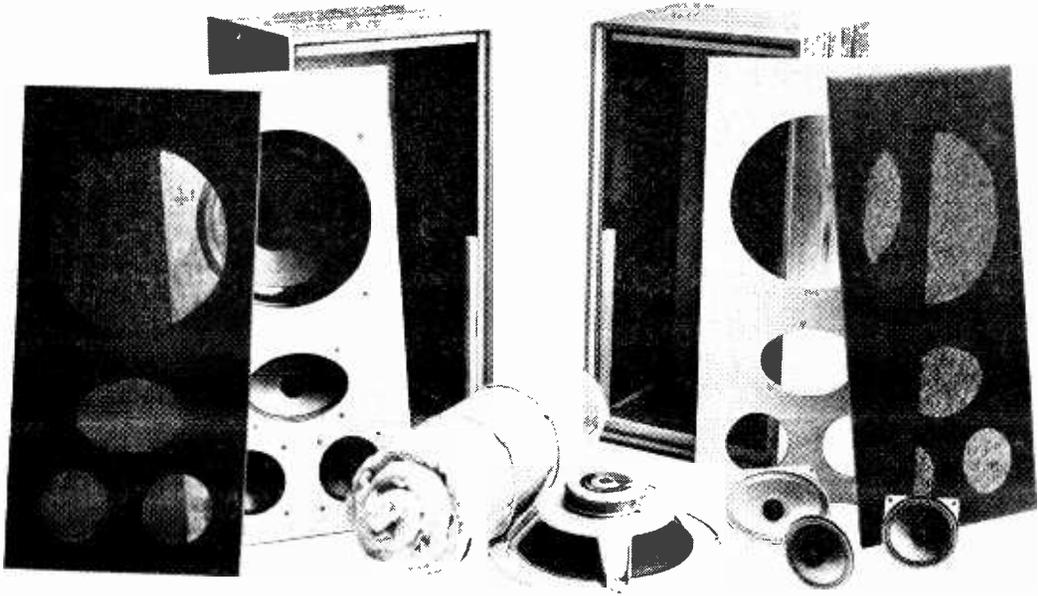

# If you want a job done properly, do it yourself.

Incredibly, almost half the money you spend on a speaker system simply goes to pay for the package it comes in: the cabinet.

As a result, if you're on a tight budget, the quality of the speaker drive unit suffers.

At Eagle, we've a simple solution to the problem, do-it-yourself.

Stereo speaker systems are easy to build and cost very little.

Yet you'll end up with the same quality as a lot of the higher priced systems you'll find in the shops. (You can even match them to your furniture.)

Have a look at the chart below and you can see how many good quality Eagle speaker drive units there are to choose from.

You'll find all full range speaker drive units come with full cabinet working drawings\*.

And all accessories come with complete installation instructions.

Once the job's done, you'll find you can go on adding to your system too.

Since all Eagle drive units are compatible, adding in a mid range speaker or tweeter is no problem.

After that, of course, you'll have nothing more to do but sit back and enjoy the music.

With the extra satisfaction of knowing there are still a few people around who can do a job properly.

## Eagle International<sup>®</sup>

Eagle International Precision Centre Heather Park Drive  
Wembley HA0 1SU Telephone 01 903 0144

MODEL	TYPE	PRICE	MODEL	TYPE	PRICE
<b>Base/Full Range Units</b>			<b>Mid Range Units</b>		
FR4	Cone	4 90	AA12	Cone	4 23
FR65	Dual Cone	6 80	<b>High Frequency Units</b>		
FR8	Dual Cone	8 90	CT5	Cone	1 20
<b>Crossover Networks</b>			CT10/8	Horn	2 40
CN23	2 way	1 10	CT10/16	Horn	2 40
CN28	2 way	1 10	HT15	Horn	3 50
CN216	2 way	1 10	MHT10	Horn	3 60
SN75	2 way	2 20	HT21	Horn	4 20
FF5	3 way	2 60	DT33	Dome	5 20

\*Please send me your free advance copy of full cabinet details.

Name

Address

PW2

THE MIDLAND  
**NATIONAL**  
 AMATEUR  
 RADIO  
 &  
**ELECTRONICS**  
**EXHIBITION**

AT THE  
**GRANBY HALLS**  
**LEICESTER**

**OCTOBER**  
**26th to 28th 1972**

SPONSORED BY THE AMATEUR  
 RADIO RETAILERS ASSOCIATION

COME AND SEE THE LATEST  
 DEVELOPMENTS IN RADIO  
 COMMUNICATIONS AND  
 ELECTRONICS. WORLD-WIDE  
 CONTACTS FROM THE  
 EXHIBITION.

LARGE CAR PARKS  
 EASY ACCESS FROM M1  
 MOTORWAY.

ADMISSION 20p.  
 THIS INCLUDES A CHANCE TO  
 WIN A PIECE OF THE BEST IN  
 RADIO EQUIPMENT.

OPENING TIMES THUR.-FRI. 26th.-27th.  
 12 NOON to 9pm.

SATURDAY 28th. 10am. to 7pm.

OVERSEA VISITORS FROM PARIS-FRANKFURT  
 -AMSTERDAM & BRUSSELS. PLEASE CONTACT:  
 "MIDAWAY LTD." 40A HILLSIDE, CASTLE  
 DONNINGTON, Nr. DERBY. FOR INFORMATION  
 REGARDING INCLUSIVE AIR CHARTER FLIGHTS  
 TO AND FROM THE SHOW.

**YOU MUST HEAR**

**miniWISE audiLECT**  
**YOUR**  
**PERSONAL TUTOR**

**THE**  
**No. 1**  
**HIT**

Bring PLEASURE to your CAREER or  
 HOBBY through Integrated LEARNING.  
 ORGANISED TUITION in your own HOME  
 at your own SPEED—with the TUTOR OF  
 YOUR CHOICE will give you rapid UNDER-  
 STANDING—the key to SUCCESS.  
 ASSURE YOUR FUTURE IN RADIO, T.V.  
 or ELECTRONICS

Write now—right now to—

**MINIWISE PRODUCTS**  
 Freepost, Bletchley, Bucks.  
 (No stamp required)

For FREE details of  
 UNIQUE sensible method just send us your name and address  
 quoting PW11. No one will call. Or include only 90p  
 to own a trial lesson\* on either a C90 cassette in lib.  
 case, or L.P. Tape (state which).

\* Your money INSTANTLY REFUNDABLE if not 100%  
 convinced that this can be the turning point in your  
 hobby or career.

**THE NATURAL WAY TO LEARN**

BRITISH MADE AMATEUR RADIO EQUIPMENT

**K. W. ELECTRONICS LTD**

DEPT. 'A', 1 HEATH STREET, DARTFORD, KENT DA1 2LH

Why not improve your reception or transmission of Amateur signals  
 by using British designed and built equipment from K.W. ELEC-  
 TRONICS. Listed below are some of the many items either built or  
 stocked by us:—

**ANTENNAS**

K.W. Trap Dipole, for improved reception and transmission, covering  
 10 to 80 metres Prices £14 to £20  
 (Above can be supplied in D.I.Y. Kits) Prices from £15-00  
 18AVT/WB Vertical Antenna 10 to 80m Price £35-50  
 ASP 629 2 metre Mobile Whip £6-00  
 TRI-BANDER G-WHIP Mobile (with 30" telescopic section) £10-45  
 Insulators 3" Black Poly Per pair 20p  
 Co-Axial Cable 52 or 75 OHM Per metre 23p  
 Enamelled Copper Wire 14swg Per metre 4p  
 Polypropylene Cord ML2 200 lbs B/S per 100 metres £1-33  
 ML6 600 lbs B/S per 100 metres £3-65  
 Balun. K.W. Type £1-95  
 H.Z.P. Type I-A £4-80  
 Belling-Lee TV Antenna Balun 75p  
 1 pair K.W. Traps plus 1 ceramic Tee peice £4-50


K.W. E-ZEE Match. Antenna matching unit 10-80m £15-00  
 K.W. Antenna Switching Unit (switches 1 to 3 antennas) £3-75  
 K.W. 101 Standing Wave Ratio Meter £9-25  
 K.W. 103 S.W.R. and Power meter combined £12-50  
 K.W. Dummy Load (52 or 75 OHM) £7-00  
 K.W. 107 comprising:—S.W.R. meter, watt meter, Dummy  
 Load (52 or 75 OHM) E-ZEE Match,  
 and an Antenna switching system  
 (to switch up to 5 separate anten-  
 nas). Built into the K.W. 'G' Line  
 Cabinet £40-00

**OTHER EQUIPMENT FROM K.W.:**—

Complete Amateur Stations,  
 Transceivers. Receivers. Transmitters.  
 All in matching 'G' line Cabinets.

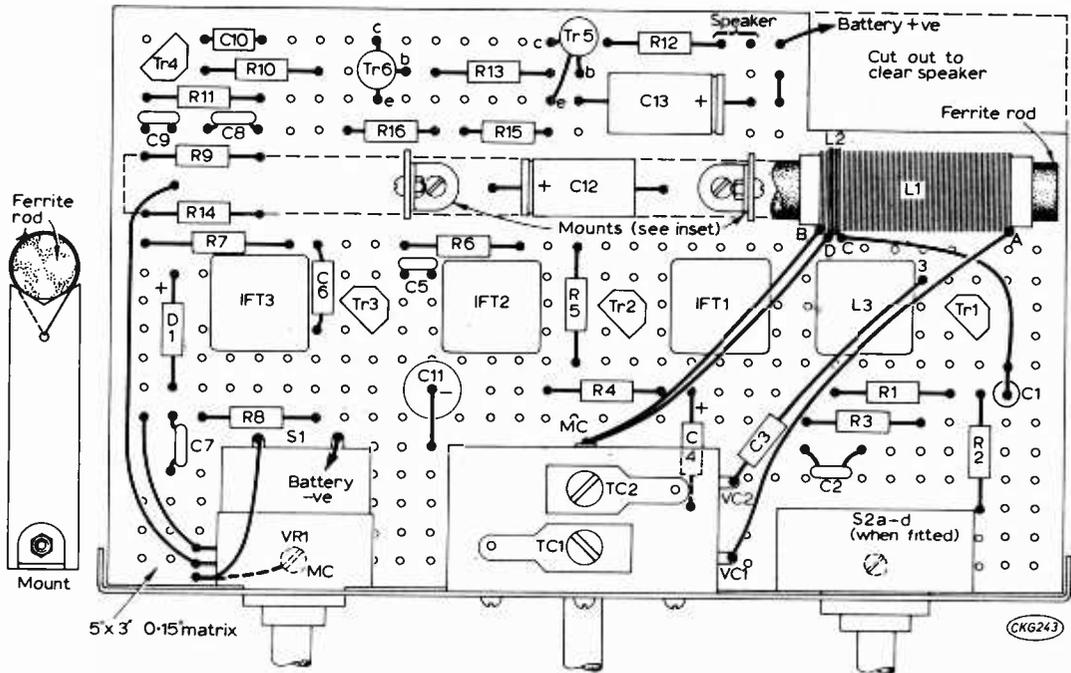
SEND A LARGE S.A.E. FOR FURTHER DETAILS OF EQUIP-  
 MENT LISTED ABOVE, AND MANY OTHER ITEMS TOO  
 NUMEROUS TO DETAIL HERE





▲ Fig. 2: Plan view of components mounted on top of circuit board with details of the mounting for the ferrite rod aerial. NOTE: Speaker should be shown connected to centre and RIGHT-HAND pin.

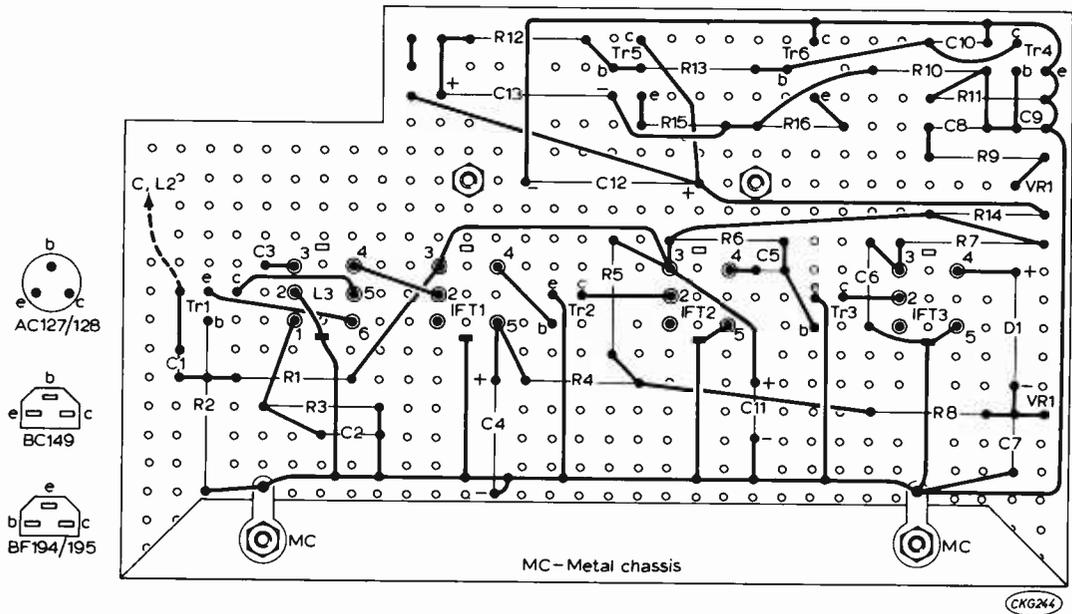▼ Fig. 3: Wiring on reverse side of circuit board together with transistor lead-out connections.



a ganged capacitor with the trimmers TC1 and TC2 incorporated.

L2 is the m.w. base coupling winding for the oscillator/mixer Tr1. Tr2 and Tr3 are the IF amplifiers using BF195's. Diode D1 is the detector or demodulator which also provides a.g.c. bias for Tr2. The collector circuit of Tr3 is decoupled by C6 and R7. Because of the very high gain of these transistors, it may be necessary to take certain steps to avoid squegging or instability, as described later. This depends to some extent on individual transistor characteristics.

VR1 is the volume control feeding Tr4. Tr5 and Tr6 are used in a directly coupled driver-output arrangement which will be found to give good results and plenty of volume with a 15Ω or 18Ω speaker.

## CONSTRUCTION

The controls are mounted on a 5×2in. "universal chassis" flanged member, Fig. 2. The top flange is cut off, to clear TC1 and the variable capacitor. When mounting this item, with its spindle through a clearance hole, it is necessary to use very short bolts, or

# FREE

\*Information on our sophisticated but low-cost kits . . .

\*New 1214 Audio Range. Build your system in a few evenings.

\*New loudspeaker range.

\*Unbeatable quality and specifications.

\*Incredibly good value for your money.

\*New continuous credit and no-deposit terms. Even includes instruments.

\*Over 30 new models.

\*Over 130 models in range.

\*Packed full of invaluable information about the world's finest electronics . . .

It's New. It's the biggest Audio/Instrument kit catalogue in the U.K. And it's absolutely FREE.

Our new jumbo size Heathkit catalogue is full of good things: low-cost Testers and Instruments, Metal Detectors, Electronic Calculator, Intercoms., Amplifiers, Tuner/Amplifiers, Tuners and Loudspeakers - there's even a Battery Charger.

You name it, Heathkit can supply. What's more, you can build everything yourself. Heathkit help you each step of the way. Simply follow the Heathkit step-by-step construction manual. It's like painting by numbers but with something unique at the end of it. Fantastically satisfying, and less expensive than buying readymade. Our products are advanced in specification and performance. And they're regularly reviewed by leading journals. You have to be good to merit that sort of treatment.


We guarantee that by using the Heathkit step-by-step construction method you can build a piece of electronic equipment without needing to know the first thing about electronics.

Mail the coupon today for your copy of the free Heathkit catalogue. The kits shown take just one or two evenings, and we promise that whichever kit you choose it'll be more rewarding than washing the car or watching television.



Want to know more?

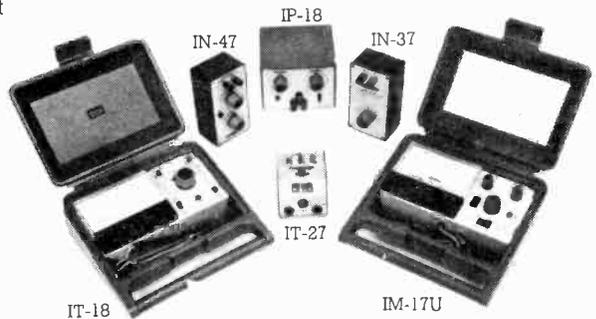Mail the coupon for a FREE CATALOGUE. Don't forget . . . This includes Instruments and low-cost Testers.



Why not visit your Heathkit Electronics Centres . . . and see our Instruments and Testers.

**London** 233 Tottenham Court Road. Telephone: 01 636 7349  
Open hours: Monday - Saturday 9-6.00 p.m.

**Birmingham** 17-18 St. Martin's House, Bull Ring.  
Telephone 021 643 4386 Open hours: Friday - Saturday 10-5.30 p.m.

**Gloucester** Cole Avenue Roundabout, Bristol Road.  
Telephone 0452 29451 Open hours: Monday - Friday 9-5.00 p.m.  
Saturday 9-12.30 p.m.

Please send me the FREE New 1972 Heathkit catalogue

Name .....

Address.....

.....

HEATHKIT  
Schlumberger

HEATH (Gloucester) Ltd.,  
Dept. PW 11/72  
Gloucester GL2 6EE



### MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 65p. Postage 20p for first one then 10p for each one ordered.



### MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 20p each #1-80 for ten, your assortment.

### SPARTAN Portable RADIO


#1-99 Only. Six transistor medium wave pocket loud-speaker radio. Loud and with good tone will make wonderful Christmas present. Buy while stocks last. Pull money back guarantee.



### RENITONE clock, wave 7 transistors £1-95
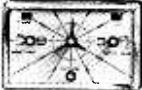
### ELECTRIC CLOCK WITH 20AMP. SWITCH

These units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another time or alarm—this may be set in minutes up to 1 hour. At the end of the set in minutes up to 1 hour. At the end of the period a bell will sound. Offered at only a fraction of the regular price—£2-50, less than the value of the clock alone—post and ins. 15p.



### WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

### RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only 21 each or £11 per dozen, exactly 5, 10 or 15 amp—simply fit in place of switch.

### FLUORESCENT CONTROL KIT

Each kit comprises seven items—Choke, 2 tube ends, starter, holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Crolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled. Kit A—15-20 w. £1. Kit B—30-40 w. #1. Kit C—40 w. #1.20. Kit E—65 w. #1.20. Kit F for 8ft. 125 w. tube #1.75. Kit MF1 is for 6in., 9in. and 12in. miniature tubes #1. Kit MF2 for 21in. 13 w. miniature tube #1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and E 23p on first kit then 18p for each kit ordered. Kit F 33p then 23p for each kit ordered. Kit MF1 18p on first kit then 15p on each two kits ordered.

### DOOR INTERCOM

Know who is calling and speak to them without leaving bed, or chair. Outfit comprises microphone with call push button, connectors and master intercom. Simply plugs together. Originally sold at £10. Special snip price £3-50 plus 20p postage.

### SOLDER GUN

A must for every busy man, gives almost instant heat also illuminated job. 100 watt £2-25 plus post and ins. #1-2 £2-25 watt model £4-75 plus post and ins. 40p.

### MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 85p, plus 20p postage.

### MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 600m watt power output 75p. Model 1172 750m watt power output 85p. Model EP9000 4 watt power output #1-45. 10% discount if 10 or more ordered.

### MULLARD 4 + 4 STEREO AMPLIFIER



We demonstrate these daily and almost always a sale result; it really is a cracking amplifier. Only Mullard with their know how could have made it possible at this low price. SPEC. Mains operated. 4 watts music or speech per channel. Double wired power supply eliminates cross talk. Harmonic distortion less than 2%. Frequency response 50Hz-16KHz. Input suitable for pick up tuner or microphone. 6 month guarantee. Only £9-95 + 30p postage and insurance.

### COMPUTER TAPE

2,400ft of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1in. wide £1-00 plus 33p post and insurance, with cassette. 1/2 in wide £1-00 plus 30p post and insurance with cassette. 1in. wide 85p plus 25p post and insurance with cassette. Spare spools and cassettes—1in 75p, 1/2 in 75p each plus 20p post and insurance.



### TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only need control switch. £3-50, 3kW Model as above except 2 kilowatts £2-50. Don't miss this. Control Switch 35p. P. & P. 40p.



### HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £2-75 plus 25p post and insurance. Don't miss this terrific bargain.



### THIS MONTH'S SNIP

**TIMAC 24 hour 15 amp Clock Switch.** Self-contained unit for flex connection to the mains. Clock switches 2 on/off per 24 hours. Operates a 15 amp switch. All neatly made up in an ivory moulded case with outlet socket. The only snag is that the outlet socket is the continental type. Plugs for these can be bought in this country alternatively you could fit a connector strip in place of the outlet socket. Overall size of this unit is approx. 4" x 2 1/2" x 3" and the clock has a clear perspex cover which is easily removable for reprogramming. Ideal for blanket controller etc. Price £2-75 each.



### THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2-95, plus 20p post and insurance.



### DIGITAL COUNTER TIMER

Very stable and reliable crystal controlled circuit. Capable of work in excess of 15 MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case £39-50 or construction data and price list 60p.



### MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 700mW into 8 ohms speakers. Input suitable for crystal mic. or pick-up 9V battery operated. Size 2in long x 1 1/2 in wide x 1in high. SPECIAL SNIP PRICE 80p each. 10 for £5-40, 100 for £50.



### 3 STAGE PERMEABILITY TUNER


Made originally for Radiomobile car radios. This is a medium wave tuner with a frequency coverage 16kc—525kc. Aerial, RF and oscillator sections (long wave coil available) small size, only 2 1/2" x 2" x 1 1/2". Can be used with our IF module and AF modules and a few inter connection components to make a complete compact receiver. Circuit supplied. Price 65p. less 10% for 10.



Slide Switches. SP Change over spring return 250v 1 amp. 10p.
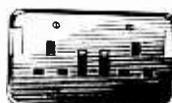
### IMMERSION HEATERS BY REMPLY

Standard fitting for domestic water tanks, made by the famous Remply Company. Complete with sealing washers suitable for 200-240 volts A.C. Depth into tank 11". 2 1/2 kw or 3 kw. £2 plus 40p each post and insurance.



### 13 AMP TWIN GANG SOCKETS

Offered at less than wholesale price your opportunity to replace those dangerous adaptors—brown bakelite flush mounting—standard fitting. Unswitched 80p each, separately switched 30p each. Separately switched and with neon on/off indicators 45p each. Less 10% ten or more + 20p postage if order under £5-00.

### POCKET CIRCUIT TESTER

Test continuity of any low resistance circuit, house wiring, car electric. Tests polarity of diodes and rectifiers. Also ideal size for conversion to special detector (circuit supplied). 80p or 2 for 150p post paid.



### AMPLIFIER IN CASE WITH SPEAKER

Marketed by British Relay under the name Luxitor. This is in a very neat looking cabinet and is ideal around the home or in the workshop for trouble shooting or for testing out a quick lash up. Size approx. 2 1/2" x 6 1/2" x 3 1/2" deep. Input is via a matching transformer and volume control and amplifier may be powered by an internal battery or an external 110v source. Speaker is R-A elliptical 6" x 3 1/2" x 10,000 gauss. The amplifier proper is a Newmarket model ref. P.C.4. Price £3-50 each, 10 for £31-80. Post and insurance 10p.



### BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2 1/2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price 45p each.

### TELEPHONES

Complete as illustrated. Save your legs, time and temper, simply by putting in some telephones. Ex. G.P.O. not new—but guaranteed in good condition and serviceable. Includes with diagram and instructions showing how to connect. Price 75p each + 50p post or 2 for £2 post paid. Also available separately, dials and handsets 50p each + 20p post.



### ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1" x 1 1/2" 6p each, 10 for 54p.



### SLIDE SWITCHES

Slide Switch, 2-pole changeover panel mounting by two 6B.A. screws. Size approx. 1in x 1in rated 250V amp. 6p each. 10 for 54p, 100 for £3-10, 500 for £24. Ditto as above but for printed circuit 5p each 10 for 45p, 100 for £4-25. Sub Miniature Slide Switch, DPDT 19mm (1in approx.) between fixing centres. 18p. each or 10 for £1-08. SP Change over spring return 250v 1 amp. 10p.

### EDUCATIONAL KITS—all with pictorial instructions



### THIS BALANCE KIT FREE

Eagle educational kits. Japanese made these are excellent value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 40p each post paid. Special price for all 8 kits £3-00 with free balance kit.

**KA2 Lens Kit.** Eleven parts, including candle, one concave lens, one convex lens, stage and slit frame, etc. Watch light rays bend as they pass through different lenses.

**KA3 Water Pump Kit.** Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily while working. Three types of pump may be made: Lift pump, Force Pump and Force Pump with reservoir and nozzle.

**KA4 Buzzer Kit.** Eleven parts. Transparent covers allow the operation of buzzer to be seen. Illustrates and teaches how electromagnetism with an automatic switch results in an operating buzzer.

**KA5 2-Pole Motor Kit.** Twenty-four parts, including enamel wire, armature and pole piece, etc. Motor operates from 1 1/2 volt battery. Illustrates and teaches how electro-magnetism operates a motor.

**KA7 Electro-Magnet Kit.** Fifteen parts, includes compass. Makes two electro-magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works.

**KA8 Current and Resistance Kit.** Twenty-nine parts, including bench and light bulb, Conduct interesting and educational projects to learn the application of "OHMS LAW" and see the differences in current and resistance with different types and lengths of wire.

**KA9 Bell Kit.** Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring.

**KA10 Morse Key buzzer and bell kit.** 25 part kit easy to construct, simple to operate.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

## J. BULL (ELECTRICAL) LTD.

(Dept. P.W.) 7 Park Street, Croydon CRO 1YD  
Callers to: 102/3 Tamworth Road, CROYDON

## ★ components list

### Resistors

R1 18kΩ	R7 390Ω	R13 47Ω
R2 15kΩ	R8 27kΩ	R14 1.5kΩ
R3 2.7kΩ	R9 2.2kΩ	R15 2.2Ω
R4 47kΩ	R10 270kΩ	R16 2.2Ω
R5 120kΩ	R11 220kΩ	
R6 330kΩ	R12 680Ω	All ½W 5%

VR1 10kΩ log. pot. with switch (S1)

### Capacitors

C1 0.01μF	C9 0.01μF
C2 0.02μF	C10 0.1μF
C3 200pF 5%	C11 200μF 12V
C4 2μF 6V	C12 200μF 12V
C5 0.01μF	C13 320μF 6V
C6 0.1μF	C14 150pF 5%
C7 0.047μF	C15 30pF SM
C8 0.1μF	

VC1-2 208+176pF gang with slow motion and trimmers (TC1-2) (Jackson OO)

TC3-4-5 60pF compression trimmers.

### Semiconductors

Tr1 BF194	Tr4 BC149	D1 AA119
Tr2 BF195	Tr5 AC127	
Tr3 BF195	Tr6 AC128	

### Inductors

Ferrite rod aerial with m.w. and l.w. windings (Denco MW/LW/5FR)

L3 Oscillator (TOC1 Denco)


IFT1-2 (IFT13 Denco) IFT3 (IFT14 Denco)

### Miscellaneous

Speaker 2½in. dia. 15 to 30Ω. S2, 4 pole 3 way wafer switch. Veroboard 5 x 3in. 0.15in. matrix. Universal chassis members 6 x 3in. (2 off), 5 x 2in. (1) (Home Radio). Knobs, materials for case.

extra washers, to avoid shorting or damaging the front section. Two bolts through the circuit board and remaining flange hold these together, soldering tags being fitted for chassis connections, as in Figs. 2 and 3.

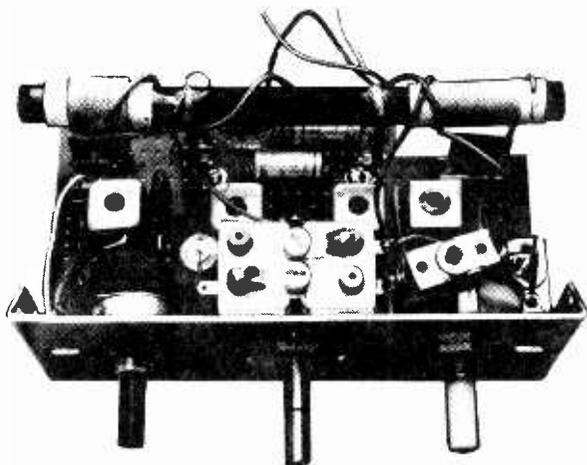If the 0.15in. matrix board has 19 rows of holes one way and 32 rows the other, this will allow parts to be placed exactly as shown. The board is 5×3in.



View of completed chassis incorporating band switching.

Prepare it in advance by drilling holes for the bolts and for the pins and screening can tags of L3 and the i.f.t.'s. A very small round file can be very useful here if any holes are not quite correctly placed. Note that L3 has closer spacing between pins 1-2 and 5-6, and must be fitted as in Fig. 3.

A bare wire, such as 22 s.w.g. tinned copper, is soldered between the tags, as in Fig. 3, for earth returns. One screening can tag of L3 and each i.f.t. is connected to this.

Resistors and capacitors are inserted into the board as in Fig. 2, with their wire ends projecting. The wires are then bent over and connected as in Fig. 3, excess being snipped off. Insulated sleeving should be put on all leads which may touch each other or any metal part. In some places connecting leads have to be soldered on to reach to other components.

It is quite helpful to use black sleeving for the negative leads, red for positive wires and some other colour for other connections, as this makes it easier to check, if necessary.

Leads for the speaker and battery positive can be soldered to pins in these holes, or the wires may project a little and be used as soldering points.

## TRANSISTORS

If Tr1, Tr2, Tr3 and Tr4 are placed as in Fig. 2, the pins will come as in Fig. 3. Leads to these pins should be soldered carefully so as to obtain proper joints, yet avoiding lengthy heating. Note that the BC149 pin connections differ from the BF194/195 types.

Place Tr5 and Tr6 so that their lead-out wires emerge as in Fig. 3. These transistors can be left with ½in. or so of lead above the circuit board. Fit diode D1 with the polarity correct as shown.

## FERRITE AERIAL


Two strips of paxolin or other insulating material are cut as in Fig. 2 to raise the rod about 1½in. from the circuit board. These strips are fixed with brackets, and the rod is held with string, thread or elastic through holes and round the rod.

For m.w., the m.w. section only is required, and is placed with the coupling winding L2 away from the rod end, Fig. 2. A and B are the ends of the long winding L1, and C and D are the ends of the smaller winding L2. Thin sleeving is put on the wires and enough slack left to allow the windings to be slid along the rod.
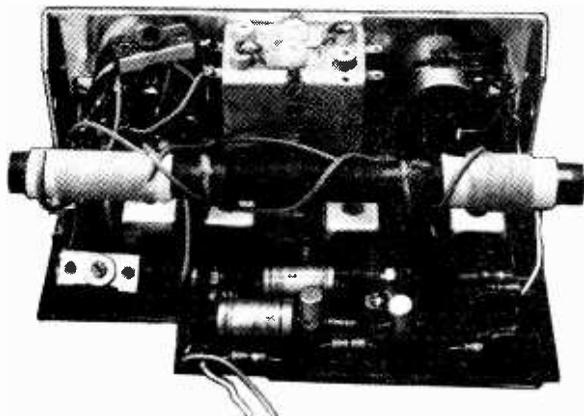
## IF ALIGNMENT

The speaker should be connected to the points as shown. Core settings of the i.f.t.'s as supplied should be found to be approximately correct, but small adjustments are made for the best results, using a Denco TT5 tool or similar means of rotating the cores.

If a signal generator is available, tune it to 470kHz and couple it to the base of Tr1 through a small isolating capacitor, or place an insulated lead near C1. The i.f.t. cores are then adjusted for best volume. If this is done by ear, set VR1 at about maximum volume, and keep the generator signal input down so that the actual volume is quite low.



Rear view of receiver. Cut-out in veroboard to clear particular speaker used.

When no signal generator is available, tune in properly any stable transmission and adjust the cores for best results. Repeat with a weak signal.

Once the i.f.t. cores are adjusted for best results, they do not need any further attention and should be left.

## MW ALIGNMENT

If a signal generator is used, band coverage can be set by adjusting TC2 at the h.f. end of the band and the core of L3 at the l.f. end of the band. A small adjustment of L3 core has considerable influence on band coverage.

A signal is then tuned in with VC1/2 nearly open and TC1 adjusted for best reception. VC1/2 is then adjusted to tune in a signal near the l.f. end of the band and the m.w. winding on the rod moved along to give best results. As these adjustments influence each other they are repeated until no further improvement can be obtained. If alignment is correct adjustment of TC1 or the winding on the rod should not give any important increase in sensitivity anywhere throughout the tuning range.

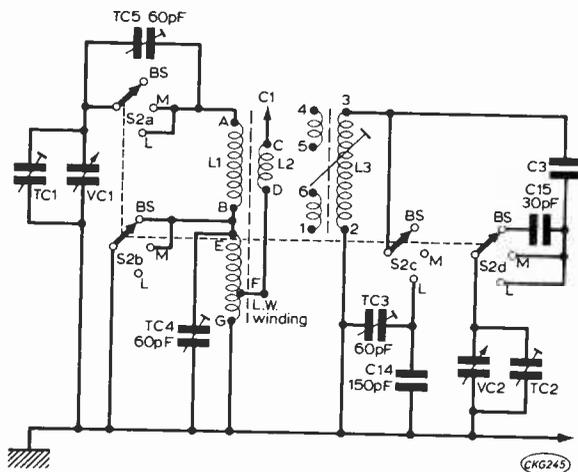


Fig. 4: Modification of Fig. 1 to permit reception on long waves plus bandspreading of h.f. end of medium wave band.

## LW AND BANDSPREAD

Long waves and bandspreading are added by changing the aerial and oscillator circuit to that shown in Fig. 4. The 4-pole 3-way switch S2 has three positions BS, MW and LW.

In the BS position, S2d places C15 in series with C3, reducing the coverage obtained with the full swing of VC2. S2a leaves TC5 in circuit, to obtain a suitably reduced tuning coverage in the aerial circuit.

For m.w. reception, C15 and TC5 are out of circuit and S2b shorts the l.w. section of the aerial, giving m.w. tuning as for the circuit in Fig. 1.

When l.w. reception is wanted, S2c places the m.w. and l.w. aerial windings in series, while S2c brings in the additional capacitor C14, with parallel trimmer TC3, to shift the oscillator coil coverage.

The tuning ranges obtained were as follows:

BS—1800-1425kHz.

MW—1525-560kHz.

LW—280-170kHz.

Any departure from this is not important, however, provided the circuits are adjusted for best results, as described.

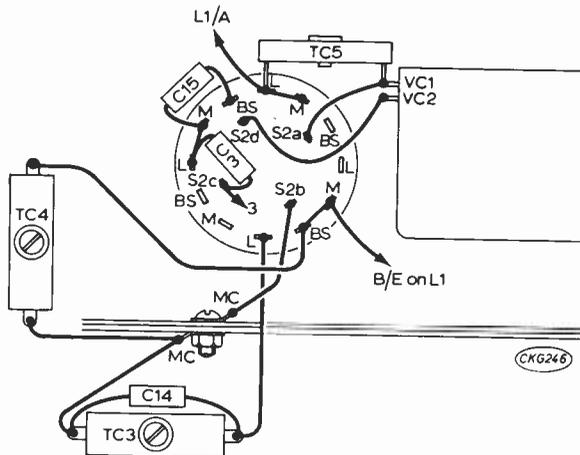


Fig. 5: Wiring of the components around the bandswitch shown in Fig. 4.

Fig. 5 shows the wiring of the bandswitch. TC5 is soldered directly from VC1 to the switch tag, while TC3 and TC4 occupy the space left on the circuit board.

Place the l.w. section of the aerial winding so that the end having two leads is towards the end of the rod. The twisted connection, consisting of two wires, is tapping F and D of the m.w. section is soldered to this. The single wire at the rod end, point G, is soldered to tag MC on VC1/2, Fig. 2. Ends B and E are soldered together and to the tags of S2b.

Note that the tapping F is electrically near point G. There are many more turns from E to F, than from F to G. The direction in which the turns are wound from A, through to B, to E and through to G, is the same. This will be so if the windings are connected as described. If one winding is reversed, l.w. alignment is impossible. Turns C to D and F to G should also be in the same direction throughout. If necessary leads C and D are reversed to secure this.

# BI-PRE-PAK

## COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE

**ONLY 95p**

POST & PACKING 35p EACH



## TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

**ONLY 50p**

POST & PACKING 15p

## OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.

### FULLY TESTED AND MARKED SEMICONDUCTORS

4p		6p	
AC107	0-15	OC139	0-13
AC126	0-15	OC140	0-15
AC127	0-17	OC170	0-23
AC128	0-15	OC171	0-23
AC176	0-20	OC200	0-23
ACY17	0-20	OC201	0-25
AF239	0-30	2N1302-3	0-13
AF186	0-20	2N1304-5	0-17
AF139	0-30	2N1306-7	0-20
BC154	0-20	2N1308-9	0-22
EC107	0-10	2N3819FET	0-40
EC108	0-10	2N416FET	0-35
EC109	0-10	Power Transistors	
EC148	0-10	OC20	0-40
EC169	0-12	OC20	0-25
BF194	0-15	OC23	0-25
BF274	0-20	OC25	0-25
BFY50	0-15	OC26	0-25
BSY25	0-13	OC28	0-30
BSY26	0-13	OC35	0-25
BSY27	0-13	AD149	0-35
BSY28	0-13	AU101	0-75
BSY29	0-13	20534	0-25
BSY95A	0-15	2N3055	0-40
OC41	0-10	Diodes	
OC44	0-13	AA42	0-10
OC45	0-10	OA95	0-07
OC71	0-10	OA79	0-07
OC72	0-10	OA81	0-07
OC81	0-13	OA95	0-07
OC81D	0-13	IN914	0-06
OC83	0-18		

## FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

### TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0-5V, 0-5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H28	20	OC200/1/2/3 PNP Silicon unceded TO-5 can	50p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6.8 - 43V.	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon Planar types.	50p

### UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1/2/3, 2N706A, BS195A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p

## MAKE A REV COUNTER FOR YOUR CAR

The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



## F.E.T. PRICE BREAKTHROUGH !!

This field effect transistor is the 2N3323 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+20p each.



## A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printer Circuit Board. A four position switch give X-hatch, Dot, Vertical or Horizontal lines Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

**This complete kit of parts cost: £3.50, post paid.**

A MUST for Colour T.V. Alignment.

## Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. Only 50p. 10p P & P on this Pak.

## 8 RELAYS FOR VARIOUS TYPES P & P 25p £1

### COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

**NOW ONLY 50p each** post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's. Per Set.	25p	20p	15p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7-5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1 8-2, 11, 13, 16, 24, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

### INTEGRATED CIRCUITS

SL403D Audio Amp. 3-Watts	1-50	1-37	1-32
709C Linear Opp. Amp.	25p	20p	15p
Gates, Factory Marked and Tested by A.E.I.	10p	9p	8p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	20p	18p	15p
SN7490 Decade Counter	45p	60p	55p
UL914 Dual 2 1/2 Gate	40p	35p	30p

### LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each  
16 pin type at 16p each.

### BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:  
**B.P.I. Transistor Equivalents and Substitutes:** 40p  
This includes many thousands of British U.S.A., European and C.V. equivalents.  
Postage and Packing 21p.  
**The Iliffe Radio Valve & Transistor Data Book 9th Edition;** 75p  
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.  
Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME: .....

ADDRESS: .....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE


**BI-PRE-PAK LTD** DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF  
TELEPHONE: SOUTHEND (0702) 46344

# SAVE £4.65 on TOSHIBA AMPLIFIER KITS!

We are now offering this fabulous stereo amplifier kit comprising the following:

- 2 - TH9014P Preamp I.C.'s
- 2 - TH9013P Power Amp I.C.'s
- 1 - P.C.B. for Preamp circuit
- 1 - Capacitor resistor kit
- 1 - Power Kit

In fact everything for only £20.95

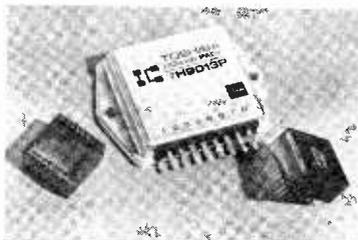

A made-up pre-amplifier using 2 x TH9014P & 1 component kit.

Typical distortion level at 1,000 Hz for 20 watts mean power is approximately 0.3% of third harmonic.

Tone controls: 15 dB (typical) cut and lift in bass and treble regions.

Input sensitivity; suitable for 4 mV magnetic pickup.

Output: 20 watts (RMS).

SEND LARGE S.A.E. FOR DATA

## Hawnt

Officially appointed distributors for  
ERIE, MULLARD, Etc.

**HAWNT & CO., LTD.**  
Dept. PW3  
112-114 Pritchett  
Street,  
Birmingham B6 4EN

Telephone 021 359 4301

## SAVE TIME AND MONEY

LIST PRICE £6.25 | OUR PRICE £4.84



As supplied by us to SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY. Silver grey stove enameled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21 1/2" x 11 1/2" x 6 1/2". Size of drawers 6 1/2" x 2 1/2" x 1 1/2". Other sizes available. Callers welcome Mon.-Sat. 9 a.m.-1 p.m. 2 p.m.-6 p.m. NEW as illustrated OUR PRICE ONLY £4.84 plus 50p carriage on orders less than £10. Money back guarantee. SEND FOR FREE COLOUR BROCHURE.


## TRADE AIDS

(DEPT. PW4), 111 CHILTERN DRIVE,  
BERRYLANDS, SURBITON, SURREY

01-399 4383

100 yds. Berrylands Railway Station.

## CAPACITOR DISCHARGE IGNITION KIT

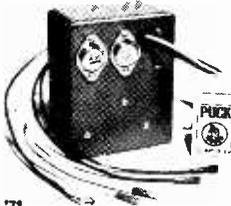

PW JUNE '71

A comprehensive kit of parts with detailed constructional details, ready drilled diecast case, screws, leads, terminals etc.

Available in both 6 and 12v versions. State whether positive or negative earth. £8.75 incl. p. & p. U.K. only

De-coupling kit for impulse tachometer and interference suppression. £1.00 incl. p. & p. U.K. only  
All our kits use guaranteed quality components and have been approved by the Author.

## MAGTOR LTD.

68 DALE ST., MANCHESTER  
M1 2HS 06-1236 3031

## HOME HI-FI CATALOGUE

The latest edition of our full colour catalogue is now available, packed with an exciting range of audio, radio and component bargains. Price 16p post free.

### 6 TRANSISTOR RADIO £2.45

Covers the medium wave band giving excellent tone from its internal speaker. Attractively housed in a plastic case with carrying strap.

### SINCLAIR PROJECT 60

Z30 £3.50

Z30 £4.25

PZ5 \*£3.70

PZ8 \*£5.00

PZ8 with

trans \*£7.32

Q16 \*£8.85

AFU £4.40



Stereo 60 Preamp/Control Unit ..	£7.00
Project 60 kit (see below) ..	£2.50
Stereo 60/2 Z30/PZ5 ..	*£15.00
Stereo 60/2 Z30/PZ8 ..	*£17.00
Stereo 60/2 Z50/PZ8/Trans ..	*£21.00
Project 605 ..	*£18.00
Project 60 FM tuner ..	*£16.00

### PROJECT 60 KIT

Our extremely popular kit contains the extra capacitors, DIN plugs and sockets, cables and fuse holder needed to complete Project 60 at the attractive price of £2.50.

### S-DECS AND T-DECS

The breadboards for the transistor age

S-DECS


£1.40

T-DECS

£2.00

µ-DEC A


£3.00

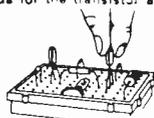

Carriers with sockets to mount 14 and 16 pin in line ICs on T-DeC and µ-DeC A £1.25.

### SINCLAIR SUPER IC12

ONLY  
£1.80

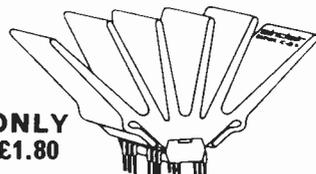

Complete with free printed circuit board and 44 page instruction book.

### IC12 KITS

**POWER UNIT** Components for a 28V 0.5 Amp power unit ideal for all versions \*£2.00. Also suitable Sinclair PZ5 \*£3.70.

**LOUD SPEAKER** Specially chosen for the IC12. 5" x 8" 8 ohm £1.45. 10" x 6" 15 ohm \*£2.00.

**BASIC KIT** Contains components for the P.C. board and volume and simple tone controls. Mono version £1.10. Stereo model with balance control £2.60

**DELUXE KIT** Contains components for P.C. board and volume and full treble and bass controls. Should be used with one of preamps below. Mono unit £1.30. Stereo model with balance control £3.00.

**PREAMP KIT** Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1.20. Stereo £2.20. Type 2 for ceramic or crystal pickups. Mono 48p. Stereo 96p.

## SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent.


Mail order only. Postage 37p per order on orders containing one or more items with prices marked with an \*. Postage on other orders 10p.

### 3-BAND ALIGNMENT

With the switch at MW align as previously described. A check can be made that coverage is about 560-1525kHz. If very much out, adjust L3 core and TC2 to correct this. Adjust TC1 at about 1450kHz and L1 on the rod, at about 625kHz for best results.

With the switch at BS, C15 is fixed, so no change of coverage can be arranged, except by altering coverage on m.w. Adjust TC5 at about 1500kHz for best reception. This adjustment should be found to remain substantially correct through this range but TC5 may be peaked on Luxembourg if wished.

With the switch at LW, adjust TC3 so that the BBC on 200kHz is about the middle of the band. TC4 may then be peaked at about 250kHz and the long wave aerial winding slid along the rod, at about 180kHz, for best results. The position of the core of L3 greatly influences l.w. coverage, so it is necessary either to set this for a m.w. coverage about as mentioned, or to adjust L3 until l.w. reception is suitable, afterwards moving L1 slightly to compensate so that m.w. reception is also satisfactory. All the adjustments can be repeated, in the order given, until no further improvement is possible.

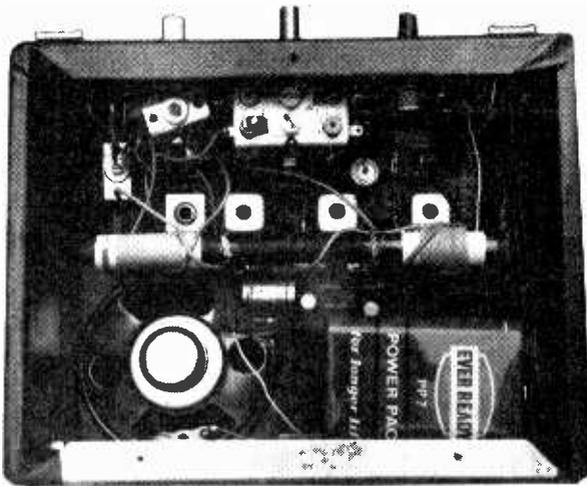

Rear view of the completed receiver showing placement of the battery and speaker.

### INSTABILITY

Commercially made receivers may employ individually selected sets of transistors or make provision for changes to some values, to suit individual transistors, in order to avoid instability.

In this circuit, where oscillation may arise due to particularly "good" transistors, a cure can be effected by adding a  $\frac{1}{4}$ W resistor between pin 4 of L3, and pin 2 of i.f.t.1. The lowest value which prevents oscillation is used, but it is not critical. A few spare resistors, such as 220 $\Omega$ , 470 $\Omega$ , 680 $\Omega$  or 1k $\Omega$  can easily be tried. Should the trouble seem difficult to cure, a resistor of some 47 or 100 $\Omega$  or so may be placed between point C of L2 and C1. Alternatively, a turn or so may be removed from L2, but this is less easy and difficult to replace.

### COMPLETION

The completed receiver, with speaker and battery, can be fitted in any suitable wooden or plastic case. The case illustrated is quite easily made and is approximately 5in. high, 6 $\frac{3}{8}$ in. wide, and 3 $\frac{3}{8}$ in. deep.

Top and bottom consist of "universal chassis" flanged members 6 $\times$ 3in. The top is drilled so that the bushes of the bandswitch, VR1 and VC1/2 spindle, can pass through. Washers or spare nuts are put on the bushes of the switch and VR1 and the receiver is then secured in place by further nuts on these bushes, when the case is finished.

The case sides are  $\frac{3}{8}$ in. 3-ply, each 5 $\times$ 3in. They are fixed to the top and bottom by 6BA countersunk bolts through the end flanges. Front and back are similar 3-ply and are 6 $\frac{3}{8}$  $\times$ 5in.

An aperture is cut in the front panel to match the position and diameter of the speaker cone. Adhesive is spread on the case edges and the front fixed by countersunk bolts through the flanges with a few small panel pins driven through into the wooden sides. The back is held with self-tapping screws into the back flanges.

A piece of speaker material about 5 $\frac{1}{2}$  $\times$ 3 $\frac{1}{2}$ in. is glued across the front. The front was then covered with self-adhesive material, which can be obtained in many colours and styles. Top and sides are covered in the same way. Strips are cemented on to cover the junction between the speaker gauze and the case covering material. ■

# TELEVISION

## NOVEMBER ISSUE

### LARGE-SCREEN TV

For large-screen public TV displays it is necessary to adopt some system other than the simple direct viewing of a c.r.t. screen. Many systems have been tried and used and some are suitable for colour TV displays. Development work is still in progress on some techniques. A particularly interesting large-screen colour TV system was used at EXPO 70: this employed mechanical scanning and, as the light source, gas lasers. We shall be looking at this and other systems—such as Eidophor techniques—this month.

### RENOVATING THE RENTALS

Caleb Bradley tackles another colour chassis widely used for first-generation rental purposes, the Bush-Murphy CTV25/CV2510 series.


### COLOUR RECEIVER CIRCUITS

Gordon King resumes his series, investigating vertical shift techniques and line oscillator circuits, both valve and transistor.

ON SALE OCTOBER 16

# 8W silicon amplifier

F. C. JUDD

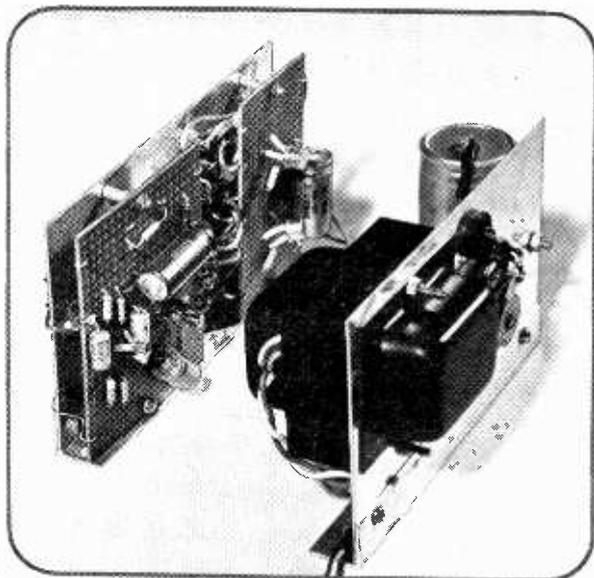


**A**LTHOUGH desirable for reliability in operation, silicon power transistors were, until recently, rather costly devices. They can now be obtained at prices comparable with germanium types and for this particular project the Newmarket type NKT 0033 have been chosen for the output stage, together with other small signal silicon types for the driver and input stages and for a recommended signal preamplifier.

The power amplifier, the circuit shown in Fig. 1, will deliver 8W r.m.s. into an 8Ω load for a THD factor of not greater than 0.2 per cent. The input sensitivity can be varied between 250mV and 1V depending on the value of R<sub>b</sub> which sets the amount of negative feedback. The output pair are controlled against temperature rise by diodes D1 and D2 although it is most unlikely that any problem in this direction would occur, providing the heatsink for the output pair is of sufficient area.

The signal input is taken via Tr1 to the initial driver Tr2 which is in series with the bias pre-set PR1 for setting the d.c. condition of the driver and output stages. The drivers (Tr3 and Tr4) are a complementary NPN-PNP pair. Overall feedback is controlled

**Table 1. Main Amp Specification**

Frequency Response	30Hz to 30kHz ± 1dB
Max. Power Output	8W into 8Ω load
Signal-to-Noise	Better than -90dB
Distortion at 1kHz	8W less than 0.2 per cent 1W less than 0.3 per cent 500mW less than 0.4 per cent

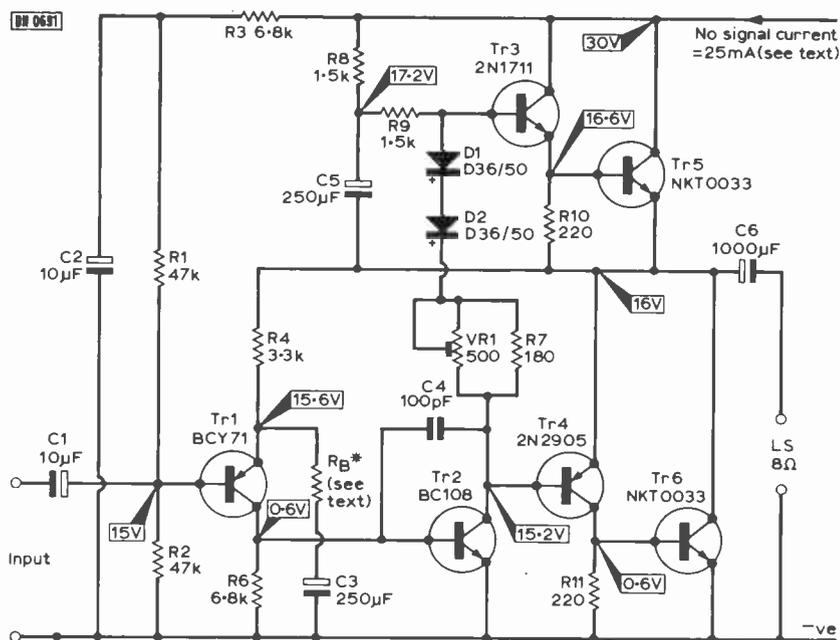

\*R<sub>b</sub> for:-  
 Input sensitivity  
 250mV = 100Ω  
 400mV = 180Ω (for pre-amp Fig. 8)  
 500mV = 220Ω  
 1V = 390Ω

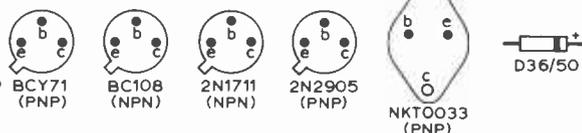


Fig. 1: The circuit of the main amplifier which uses all silicon transistors and gives an output of 8W r.m.s.

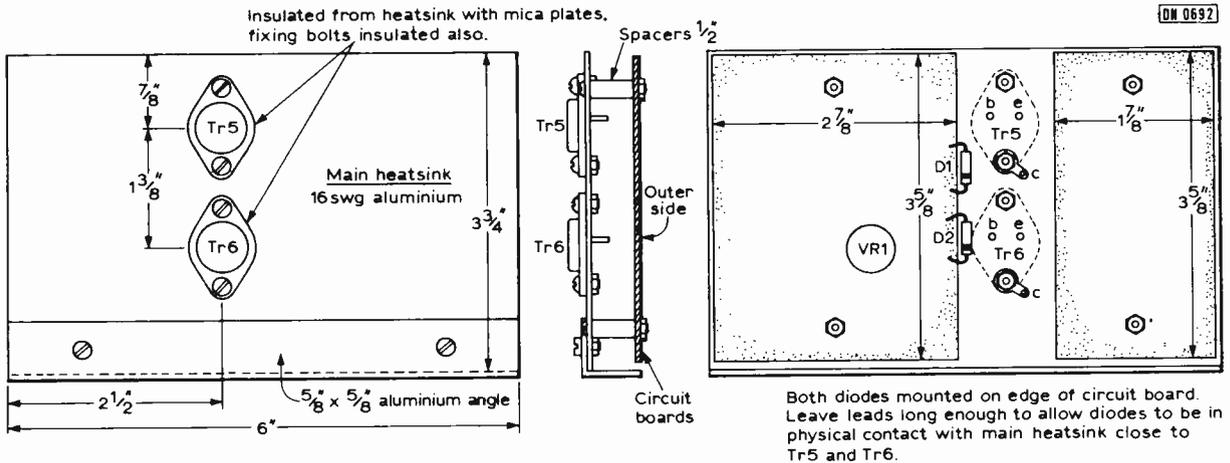


Fig. 2: (a) The heatsink for the output transistors. (b) An edge view showing the mounting of the circuit board. (c) The siting of the two circuit boards.

by the value of Rb and this also determines the required input sensitivity. The table shows the overall performance obtained with the prototype.

The amplifier is stable on loads down to 4Ω and will operate at reduced power output (approx 6W) into a 15Ω load. The quiescent (no signal) current is approximately 25mA for a supply rail of 30V. Total current at maximum power output (8Ω load) is about 400mA at which the supply voltage falls to about 26V to 27V.

### CONSTRUCTION

The construction and assembly of the prototype

### ★ components list - Main Amplifier

R1 47kΩ	R7 180Ω
R2 47kΩ	R8 1.5kΩ
R3 6.8kΩ	R9 1.5kΩ
R4 3.3kΩ	R10 220Ω
R5 Rb—see text	R11 220Ω
R6 6.8kΩ	

All resistors 1/2W, 5 per cent types.  
 VR1 500Ω (or 470Ω) carbon pre-set type

**Capacitors**

C1 10μF 20V min.	C4 100pF
C2 10μF 35V min.	C5 250μF 10V min.
C3 250μF 20V min.	C6 1000μF 35V min.


**Semiconductors**

Tr1 BCY71	Tr5 NKT0033
Tr2 BC108	Tr6 NKT0033
Tr3 2N1711	D1 D36/50 or 1N4001
Tr4 2N2905	D2 D36/30 or 1N4001

The semiconductors are available from either Electrovalue Ltd., 28 St. Judes Road, Englefield Green, Egham, Surrey or Arrow Electronics, 7 Coptfold Road, Brentwood, Essex.

**Power Supply**

Transformer T1	240V/17W Type TS 18/2 (Henry's Radio)
Bridge Rectifier MR1	Type LT119, 30V, 1A (Henry's Radio)
Capacitor C1	5000μF 50V

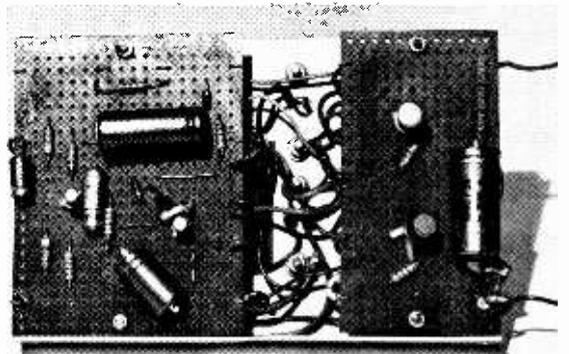

A view of the prototype illustrating the arrangement shown in Fig. 2c.

is shown in Fig. 2. The heatsink must not be less than the area specified, even if an alternative layout and construction is adopted. The assembly shown makes a quite compact unit with the two circuit boards backed onto the main heatsink.

The layout and wiring are shown in Fig. 3a but note that the components are as seen from the outer side of the boards and the wiring from the inner side. The power transistors Tr5 and Tr6 must of course be completely insulated from the heatsink with mica spacers and fixing bolt insulators as shown in Fig. 3b. Note also that the two diodes D1 and D2 must be wired so that they can be pushed down to make physical contact with the heatsink. The complementary pair drivers Tr3 and Tr4 do not require heatsinks.

### POWER SUPPLY

The circuit and layout are given in Figs. 4 and 5 respectively. The construction of the prototype is on the same lines as the power module with the transformer and rectifier etc. mounted on a piece of aluminium 6in x 3 3/4in. The transformer and rectifier specified will only supply sufficient current for one power amplifier module and a signal amplifier. If two power modules are to be used for stereo operation then the power supply must be able to deliver at least 1A with a maintained voltage (under maximum

Components as seen from outer side of circuit boards. Wiring as seen from opposite side.

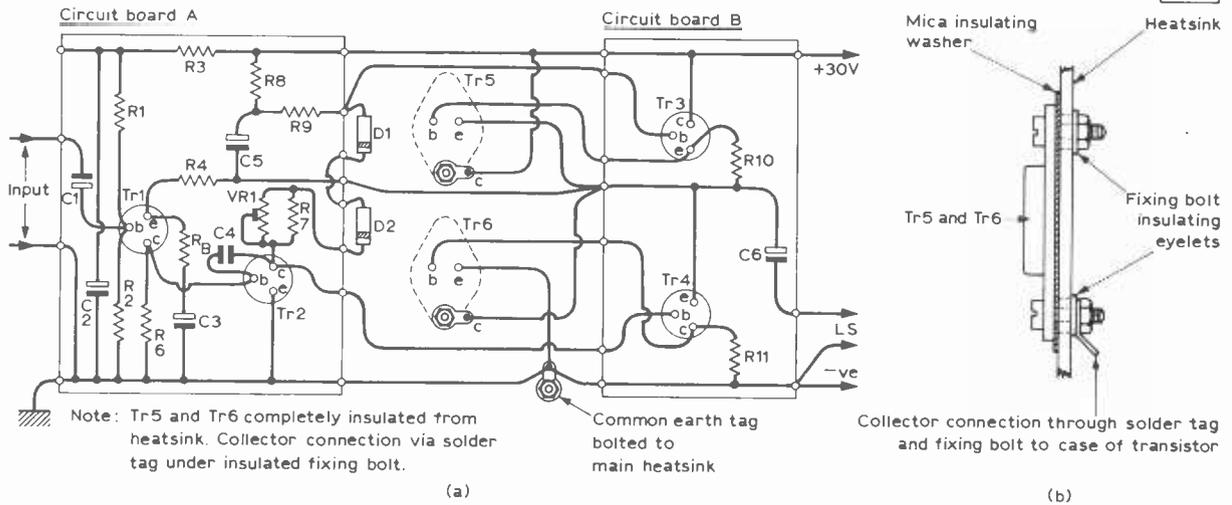


Fig. 3: (a) The component wiring of the main amplifier. (b) The mounting of the output transistors.

Fig. 4 (below): The circuit of the power supply.

Fig. 5 (right): The wiring of the power supply.

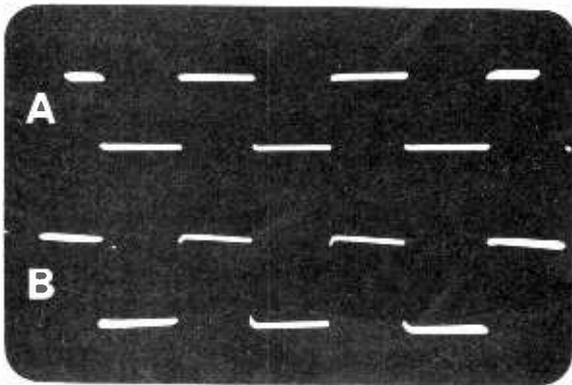
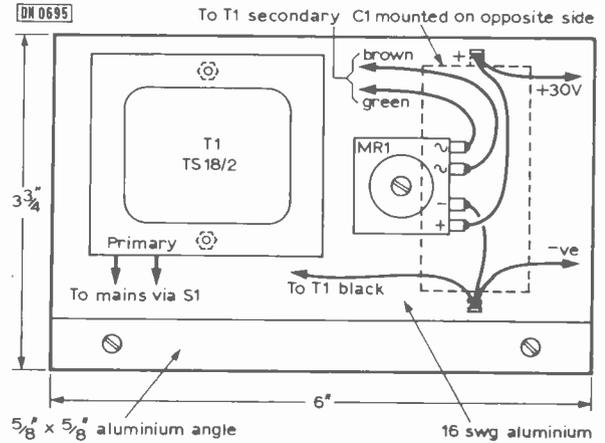
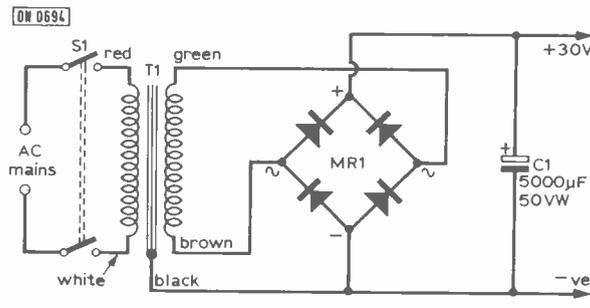


Fig. 6: Square wave results on the main amplifier.

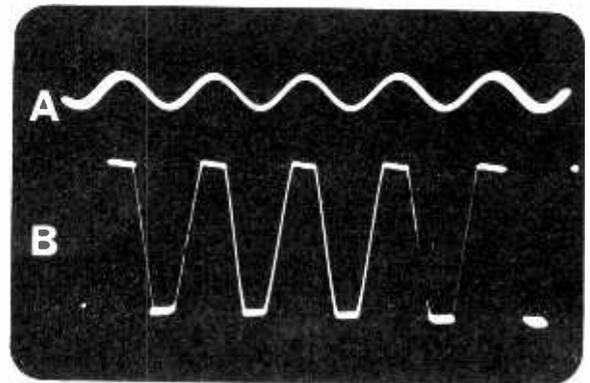



Fig. 7: Oscilloscope showing symmetrical clipping.

power load) of 26-27V. The same rectifier may be used, as this is rated for 1A at 30V but a transformer capable of supplying the higher current will be required.
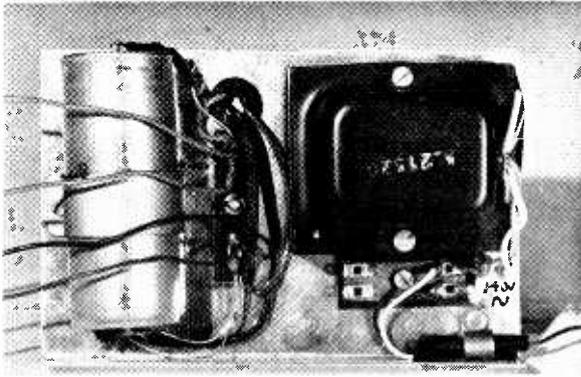
## POWER AMPLIFIER PERFORMANCE

Before connecting the supply voltage, set PR1 to midway travel. Connect a milliamp meter in series with the positive line and reset VR1 to obtain a reading of 25mA. At maximum power, (just before


clipping) the total current should not exceed 400mA. The input sensitivity can be adjusted by the value of Rb and typical settings for this are given in Fig. 1. The overall performance should be as given earlier but square-wave tests will further prove the performance. The result of the usual 1kHz square-wave test on the prototype is shown in Fig. 6 in which the input is the oscilloscope A and the output from the amplifier is oscilloscope B. Symmetrical clipping should be obtained at just over maximum (sine-



The prototype power supply.

## Table 2. Preamplifier Specification

<b>Frequency Response</b>	Linear: $\pm 1$ dB, 10Hz to 100kHz Tape Head: CCIR plus treble lift Mag.P.U.: RIAA
<b>Tone Controls</b>	Bass $\pm 14$ dB at 50Hz Treble $\pm 12$ dB at 10kHz
<b>Distortion Factor</b>	Less than 0.2 per cent
<b>Signal-to-Noise</b>	-60dB ref. 400mV output
<b>Inputs (for 400mV out)</b>	Tape Head: 68k $\Omega$ , 5-10mV Mag. P.U.: 56k $\Omega$ , 5mV Cer. P.U.: 820k $\Omega$ , 80mV Radio: 200k $\Omega$ , 80mV

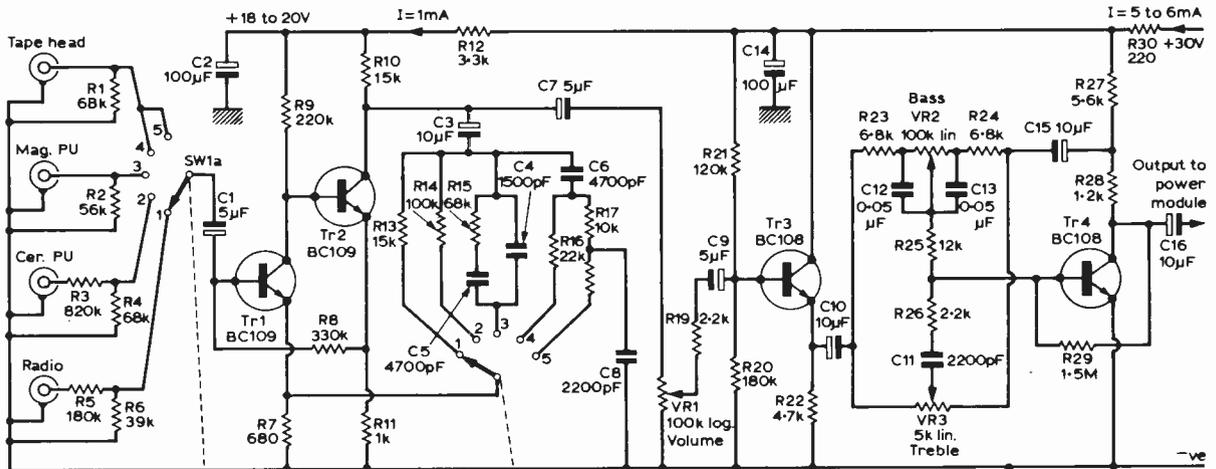

- SW1a and SW1b positions:**
- 1.....Radio or auxilliary
  - 2.....Cer. PU
  - 3.....Mag. PU
  - 4.....Tape head 15 or 7 1/2 ips
  - 5.....Tape head 3 3/4 or 1 7/8 ips

Fig. 8: The circuit of a suitable preamplifier; no constructional details are given.

wave) power output as shown in Fig. 7 in which A is a 1kHz sine-wave input and B the clipped output.

The average d.c. potentials that should be obtained with a 20,000 ohms per volt meter at various points in the amplifier are marked on the circuit; all with respect to common negative.

## PREAMPLIFIER

A circuit for a suitable preamplifier is given in Fig. 8 and this caters for magnetic or ceramic pick-up cartridges, tape head and audio. The radio input can be used for tape replay from a unit with built-in preamp. The performance of the preamplifier is shown in Table 2.

The overall gain has been adjusted to provide 400mV output to match the input requirements of the power amplifier with Rb (as in Fig. 1) a value of 180 $\Omega$ . The input circuit Tr1/Tr2 is quite conventional with selective feedback to provide equalisation for tape head and/or magnetic pick-up. The tape head response has been adjusted to comply with the recording characteristic most frequently used on domestic tape recorders; one which has less treble

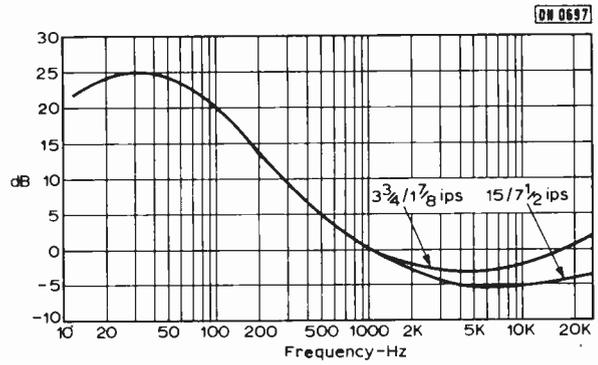


Fig. 9: Preamplifier response when switched to Tape Head.

lift than the original C.C.I.R. characteristic. The replay response obtained with the preamplifier is shown in Fig. 9 and provides what is effectively treble lift towards 20kHz but which is adjusted accordingly for tape speeds of 15 and 7 1/2 or 3 3/4 and

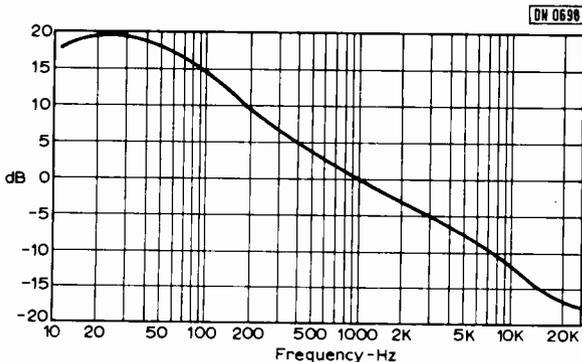


Fig. 10: The preamp response on Mag. P.U. showing R.I.A.A. curve.

## ★ components list - Preamplifier

### RESISTORS

R1	68kΩ	R16	22kΩ
R2	56kΩ	R17	10kΩ
R3	820kΩ	R18	12kΩ
R4	68kΩ	R19	2.2kΩ
R5	180kΩ	R20	180kΩ
R6	39kΩ	R21	120kΩ
R7	680Ω	R22	4.7kΩ
R8	330kΩ	R23	6.8kΩ
R9	220kΩ	R24	6.8kΩ
R10	15kΩ	R25	12kΩ
R11	1kΩ	R26	2.2kΩ
R12	3.3kΩ	R27	5.6kΩ
R13	15kΩ	R28	1.2kΩ
R14	100kΩ	R29	1.5MΩ
R15	68kΩ		

All resistors 1/4W, 5 per cent types

VR1 100kΩ log. pot. (volume)

VR2 100kΩ lin. pot. (bass)

VR3 5kΩ lin. pot. (treble)

### Capacitors

C1	5μF 25V min.	C9	5μF 25V min.
C2	100μF 25V min.	C10	10μF 25V min.
C3	10μF 25V min.	C11	2200pF
C4	1500pF	C12	0.05μF
C5	4700pF	C13	0.05μF
C6	4700pF	C14	100μF 35V min.
C7	5μF 25V min.	C15	10μF 25V min.
C8	2200pF	C16	10μF 25V min.

### Semiconductors

Tr1	BC109	Tr3	BC108
Tr2	BC109	Tr4	BC108
SW1	Double pole, five way rotary switch		

17<sub>8</sub> i.p.s. The response for magnetic pick-up is to R.I.A.A. characteristic as shown in Fig. 10.

The output from the first stage (Tr1/Tr2) is taken via the volume control to an emitter follower Tr3 and then via the active (feedback) tone control network to Tr4.

Care should be taken to prevent hum pick-up in the first stages, particularly in view of the high gain when the tape head or magnetic p.u. inputs are in use. The preamplifier can of course be duplicated for stereo use, in which case a balance control could be included between the output and the power amplifier. The insertion of a balance control will of course reduce the overall output signal in which case the feedback resistor R<sub>b</sub> in the power amplifier should be about 100Ω. ■

CHARLES MOLLOY

# THE Medium Wave Column

**D**• MAYHEW who lives in Littlehampton asks for information about English broadcasts beamed from abroad. As the medium waves are mainly used for local broadcasting there are not many special broadcasts in English to be heard, but the few known to the writer include Radio Sweden on 1178kHz, Radio Portugal on 755kHz and 1161kHz, Deutschlandfunk (West Germany) on 1268kHz, Radio Pyrgos (Greece) on 1349kHz, Radio Montecarlo 1466kHz.

Radio Sweden is on the air nightly at 2245hr GMT in English and it features a special programme "Sweden Calling DXers" every Tuesday. Radio Portugal transmits the English version of the "Voice of the West" at 2245hrs, its programme for DXers appearing on a Monday. Deutschlandfunk can be heard every evening at 1745hrs and there is a fortnightly DX broadcast on a Wednesday. In spite of rumours of a closedown, Radio Pyrgos is still on 1349kHz. It can be heard in English at 0100hrs on Mondays and its DX broadcast is on the last Friday of the month at midnight. The Vatican Radio's 250kW outlet on 1529kHz is received well in this country and there is a short broadcast in English every evening at 2100hrs. Trans World Radio uses the Radio Montecarlo transmitter on 1466kHz for religious broadcasts which can be heard at 2100hrs.

Harold Emblem of Mirfield in Yorkshire reports reception of the new Voice of America transmitter at Kavalla in Greece which is on 791kHz. The time of reception was 0300hrs GMT. At the moment this station is only using 150kW but it will soon be on full power of 2500kW when it will become the most powerful medium wave broadcaster in Europe. Harold also mentions the Voice of America at Rhodes on 1259kHz; Omdurman, Sudan on 960kHz with the call "Huna Omdurman"; the BBC Central Mediterranean Relay at Point Delimara, Malta on 1511kHz at 0345hrs with Big Ben and "Huna London" at the start of the Arabic service.

An interesting letter comes from Norman Burton who lives in Revesby N.S.W. in Australia. He is a keen MW DXer and he says "This place is good for MW DX. I've copied KFSO (560kHz, 1kW) in San Francisco at midnight, 8500 miles away. At this hour it is 6 a.m. in Frisco as it is across the international dateline." Norman is constructing the PW MW loop antenna which was described in the November 1966 edition of Practical Wireless. Although this issue is now out of print, copies are available in public reference libraries.



Please send logs and information about the medium waves to the author at 132 Segars Lane, Southport PR8 3JG.

**PRACTICAL WIRELESS**  
will be at  
**THE AUDIO FAIR, OLYMPIA**

# 4 OF THE GREAT FEATURES IN NEXT MONTH'S PW!

★ 1

10  
'scopes  
to be  
won!

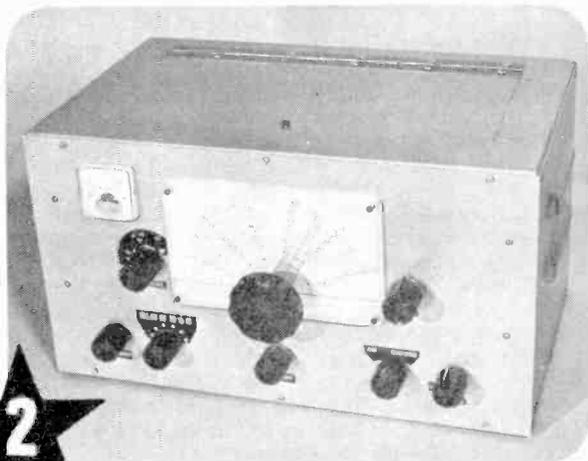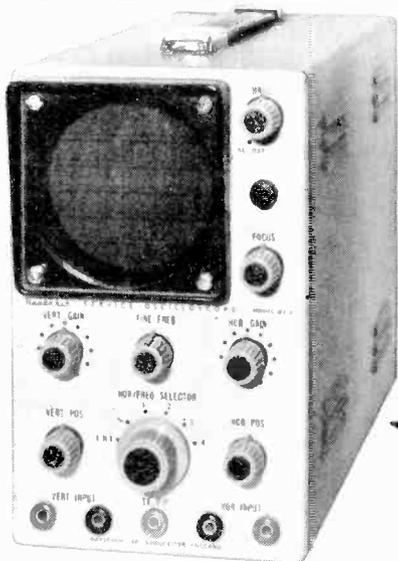

★ 2



★ 3

★ 1 FREE COMPETITION!

A great, free competition, open to all readers of P.W. Ten (yes, TEN!) Heathkit Oscilloscope Kits Type OS-2 MUST be won. All you have to do is list eight of the excellent features in their order of importance and you could be the winner of a fabulous 'scope. Watch out for the entry forms which will appear in both the December and January issues.

★ 3 THE 'MUSIC-MAKER'

The Music Maker will be one of the most popular features of the year; a portable, keyless, electronic organ which can be built for a song! The prototype has given the P.W. staff endless hours of fun . . . and it couldn't be easier: we have arranged for the supply of a special printed circuit board, the case and all unusual components at favourable prices.



★ 4

★ 2 AMATEUR-BANDS RADIO

By employing a double conversion circuit, this 6-band receiver provides good adjacent channel selectivity, utilising a crystal filter at 455kHz, while the tuneable first i.f. stage, covering 3.5 to 4MHz, virtually eliminates image interference. The project can be built in easy stages, initially as a receiver for the 80m band, later adding a product detector, BFO and crystal controlled front end converter.

★ 4 LOUDHAILER & SIREN

You'll certainly be able to stir up the atmosphere with our combined loudhailer and siren . . . it has all the facilities of commercial models with a lot of extras. Operated from dry batteries inside the main case and using a ready built power module, this is not a complex project. No difficult metalwork is an added attraction to this unusual feature.

PLUS MANY OTHER FEATURES ALL IN THE DECEMBER ISSUE ON SALE 3rd. NOV.

# TAKE 20

JULIAN ANDERSON

THOSE readers of this column who are blessed with offspring will not need reminding that children love noise. Most of the time they will be discouraged but at parties there is no harm in allowing them to let off a little steam. Our project this month makes an excellent, if noisy, children's party game; it is a variation on the time-tested "Hunt the Thimble" game. Instead of a thimble, we use a small "bleeper" which gives off a high-pitched whistle but at very low level so that it can only be heard in quiet surroundings. The idea is to divide the children into two teams; the organiser chooses the hiding place and when this is done the two teams are set loose. They can either concentrate on finding the bleeper or on making so much noise that the other team will not be able to hear it. Teams can of course divide their forces and have "searchers" and "noise-makers"; it doesn't take much imagination to predict which most children will opt for!

The bleeper, if built up as shown, is very robust and should stand up to the rough handling to which it is bound to be subjected. As with all our projects the cost is low, in this case even new components will set you back only about 50p plus the battery cost, well worth it for a popular party game.

The circuit is shown in Fig. 1. It is a simple multivibrator working at about 2kHz although the exact frequency will depend on the particular transistors used.

The sound output is taken to a very cheap crystal earpiece which is wired in parallel with R4. The circuit works perfectly well with a 1.5V single cell battery but space is a bit limited and a mercury cell Type RM401H may be better. The current drain of the circuit using the specified components is only about 600µA—less than a milliamp—and mercury cells will easily give this.

The operation of the multivibrator is not as simple as many people believe but we have described the operation before and no doubt will do so in the future; for this reason we shall not go into the actual theory. All that you need to know is that it is very easy to build and very reliable.

The prototype was built into a 35mm film can. A hole can be made in the lid and the crystal earpiece fitted through it. All the crystal earpieces that I have seen are of the same type, though there may be others. In the commonest (if not only available) type the plastic part which fits into the ear screws off and if the hole is made just large enough to take this thread, the lid of the can may be trapped when the earpiece is reassembled. This is illustrated in Fig. 2.

There is no room for a circuit board but there are very few components and these can be wired to each other as shown in Fig. 3. When this has been completed and tested the components can be wrapped in insulating tape to prevent shorting to the can. A switch is shown in the circuit but once again room precludes the use of a conventional type and a wander plug and socket can be used or even wires twisted together and untwisted after use.

## No. 42

### "HUNT THE BLEEPER"

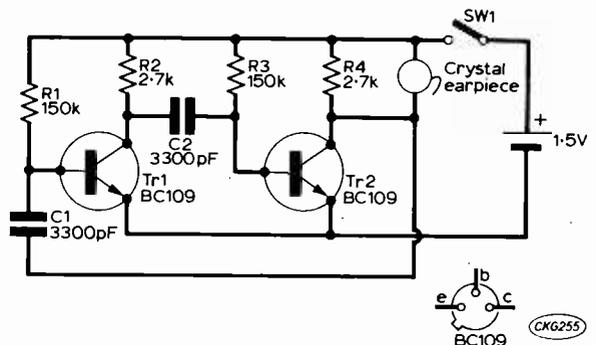


Fig. 1: The circuit is a simple a.f. multivibrator feeding a crystal earpiece.

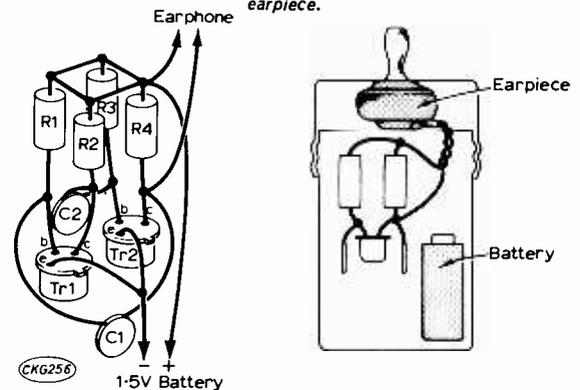


Fig. 2 (left): The components should be wired to each other as shown. Fig. 3 (right): Shows how the components fit into the can.

### ★ components list

R1	150kΩ 5% ¼W	1p
R2	2.7kΩ 5% ¼W	1p
R3	150kΩ 5% ¼W	1p
R4	2.7kΩ 5% ¼W	1p
C1	3300pF ceramic or polystyrene	3p
C2	3300pF ceramic or polystyrene	3p
Tr1	BC109	10p
Tr2	BC109	10p
Crystal earpiece		20p
35mm film can		—
		<hr/> 50p

Prices are those recently advertised and may have changed. No allowance is made for minimum order costs or for postage and packing and these points should be carefully checked before ordering.

Contacts to the mercury cell will have to be made by soldering wires directly to it and this operation should be performed with care. I don't know too much about the chemistry of mercury cells but if the soldering operation is not done quickly the cell appears to discharge almost instantly making the case extremely hot and destroying it, so do take care not to heat the cell up too much.



With Hi-Fi now a booming industry the potential purchaser of audio equipment for home entertainment is faced with a mountain of shiny brochures often describing the merits and specifications of equipment in a jargon he finds difficult to understand. This supplement, compiled by Gordon King, the well-known writer on all types of electronic equipment, is aimed at clarifying the more commonly used terms in the field of Hi-Fi.

**N**EW terminology is being introduced by the progressing art of hi-fi and it is the purpose of this supplement to explain the more important terms used by manufacturers in their specifications as well as some of the established ones found in abundance in the hi-fi literature.

The terms and their definitions, along with sometimes revealing comment, are classified under three headings to which they most appropriately relate. These are **Amplifiers**, **Tuners** and **Ancillary**, the third dealing chiefly with those terms applicable to equipment other than amplifiers and tuners. Sometimes, of course, a term, such as distortion, will be equally applicable under the three headings.

## AMPLIFIERS

### **AMPLITUDE DISTORTION**

This distortion is present when the amplitude of the output signal fails to follow exactly any increase or decrease in the amplitude of the input signal. It results from non-linearity of the transfer function and gives rise to harmonic and intermodulation distortion. No amplifier is completely free from the effect because its transfer function is slightly curved.

The nature of the curvature determines the order of the distortion produced, but negative feedback and other artifices used in hi-fi amplifiers minimise the curvature within the dynamic range and hence keep the distortion at a very low level.

### **ATTACK**

This term describes the 'responsiveness' of the amplifier to signals with a fast rise-time, such as produced by percussive sounds of a transient nature. See under Rise-Time.

### **CHANNEL SEPARATION**

This refers to the 'leakage' of signal from one channel of a stereo amplifier into the other channel. The separation is greatest when the signal leakage is the smallest. The leakage signal is commonly expressed as a decibel ratio referred to the full output of the amplifier when the channel in which the leakage signal is measured is correctly terminated both at the input and output. Thus a separation of 40dB means that the voltage of the leakage signal at the output of the channel tested is 100 times below that of the voltage of the signal at the output of the talking channel.


Owing to capacitive effects, the channel separation sometimes falls with increasing frequency, while impairment at the i.f. end can indicate a common impedance coupling between the two channels. One cause of poor separation is the common impedance presented by the wiper of the balance control on the track of the potentiometer.

### **CLASS A**

This implies biasing the valves or transistors to the middle parts of their transfer characteristics so that the device is driven upwards on one half cycle and downwards on the other half cycle. In a push-pull power amplifier, one of the device pair is driven upwards on negative half cycles while its partner is driven downwards, the mode reversing on the positive half cycles. The stage thus draws a constant current at all drive levels within the dynamic range of the amplifier. A class A power amplifier has an efficiency of almost 50 per cent.
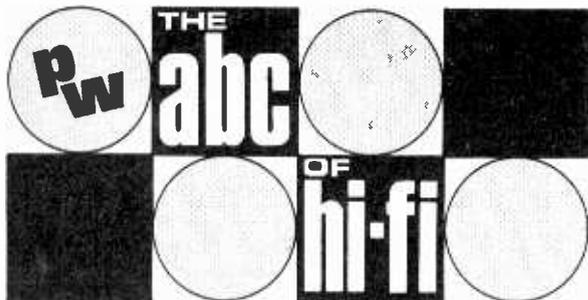
### **CLASS AB**

One type of power amplifier of this class is engineered so that at low drive level the stage operates class A, while at increasing drive level the mode changes to class B.




The Mullard Pi-Mode class AB power amplifier design is arranged so that the actual biasing changes from class A to class B with increasing drive.

### CLASS B

The majority of transistor amplifiers adopt this class of power amplifier. The biasing is adjusted such that the push-pull transistors (could be valves) operate at a low no-drive current (called quiescent current). When drive is applied the current in one of the pair rises while the partner is pushed into cut-off on one half cycle, the mode reversing on the other half cycle. Maximum efficiency of a class B power amplifier is 78.5 per cent. Current increases with drive.
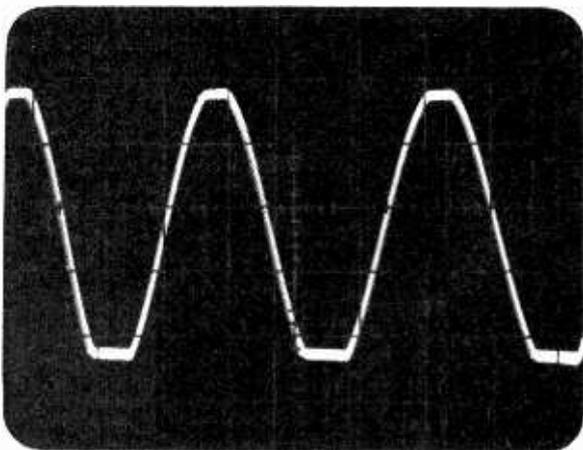
### CLIPPING

This is the term used to express the clipping of the peaks of a waveform when an amplifier is driven beyond its power capacity.



Clipping. The flattening of the tips of a sine wave due to clipping.

### COMPLEMENTARY PUSH-PULL

A power amplifier where the output transistors are of complementary polarities (i.e., p-n-p and n-p-n). In some amplifiers of this kind the driver transistors also constitute a complementary pair.

### CROSSOVER DISTORTION

The type of distortion resulting from class B push-pull power amplifiers owing to the lack of coincidence of the two transfer characteristics at the crossover point. The effect is reduced by applying a critical value of biasing to optimise the quiescent current (see under Class B and Quiescent Current) and hence 'linearise' the middle portion of the transfer characteristic. The situation is further

improved by heavy negative feedback and by circuit design, such that the crossover distortion from hi-fi amplifiers is very small.

### DAMPING FACTOR

This is the ratio of load or speaker impedance to the amplifier's output impedance. Thus the smaller the output impedance the greater the damping factor. The damping factor increases with increase of voltage negative feedback, and with the large amounts of feedback applied to transistor hi-fi amplifiers the source or output impedance can be as low as 0.1 ohm, giving a damping factor of 80 referred to an 8-ohm load.

Such a small value of output impedance is 'seen' by the speaker as a virtual short-circuit, excluding the resistance of the speaker connecting cable, and this has the effect of damping the cone movement electromagnetically, thereby minimising the speaker output at the resonance frequencies. The bass resonance is important from this respect, so the damping factor should remain desirably high down to 40Hz or less.

### DERIVED CENTRE CHANNEL

Some amplifiers are now appearing with a centre channel output derived from the addition of the left and right signals by a matrix. This output can be fed to a single-channel power amplifier operating a speaker for location between the left and right stereo speakers.

### DIRECT COUPLING

This refers to interstage couplings or the speaker coupling being direct with no intervening transformer or capacitor. To the speaker it ensures that the damping factor remains high at l.f. (but increasing power supply impedance at l.f. can influence this), while direct coupling generally minimises l.f. phase shift and encourages enhanced bass performance.

### DYNAMIC RANGE


This is the range of reproduction limited on the one hand by the intrinsic noise of the amplifier (see under Noise) and the ambient background noise level of the listening environment and on the other by the power capacity of the amplifier and speaker system. In many cases the dynamic range is limited by the programme signal, but well recorded gramophone records are capable of a dynamic range approaching 60dB, which is 10<sup>6</sup>:1 power ratio (one million).

### EQUALISATION

When emphasis is given to a range of frequencies during processing or recording (or transmitting), the correction required to normalise the signals during reproduction is called equalisation. Typical is the RIAA recording characteristic which, apart from ensuring that the recording amplitude is reduced from about 800Hz downwards, boosts the recording level with increasing frequency so that the required de-emphasis (equalisation) during reproduction not only 'flattens' the overall response but also reduces the record noise at the same time.
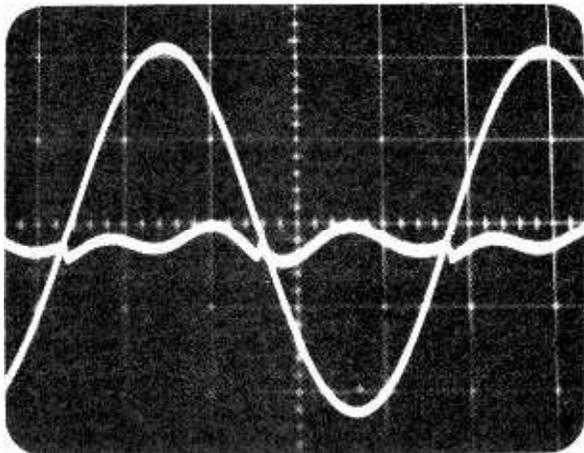
### FEEDBACK

This refers to the feedback of the output signal (or a portion of it) to the input. When the feedback signal is negative it subtracts from the input signal and thus reduces the effective output and when it is positive it adds to the input and increases the effective output. Positive feedback produces sustained oscillation or howl. One example is acoustic feedback where sound from the speaker causes



**Crossover Distortion.** Artifacts on the distortion residual produced by very mild crossover distortion.

response at a gramophone pickup or microphone, a feedback loop then being completed through the amplifier. Howl or oscillation develops at the frequency corresponding to a major resonance in the loop.

### FREQUENCY DISTORTION

This is the unequal amplification of all frequencies over the passband of the amplifier (also see under Frequency Response).

### FREQUENCY RESPONSE

The range of frequencies over which an amplifier responds within defined limits of amplification (or signal output). A parameter expressed as 20Hz to 20kHz is the frequency range and is of limited value, while the parameter expressed as 20Hz to 20kHz  $\pm$  1dB is the frequency response which means that the deviation of amplification from 20Hz to 20kHz is a mere +1dB or -1dB, which is much more meaningful.

### HARMONIC DISTORTION

The voltages of harmonics resulting from amplitude distortion expressed as a percentage of the voltage of the fundamental. A common measurement is total harmonic distortion (THD) where the fundamental of a very low distortion sinewave test signal is removed by a steep notch filter, the summed harmonics remaining then being measured as a voltage and expressed as a percentage (or dB value) of the voltage of the fundamental at the required test power of the amplifier.

When measured in this manner the term THD is not really correct since the distortion also has the amplifier noise added to it within the test passband. The correct term is **distortion factor**.

### HEAT SINK

A metal 'radiator' used in transistor amplifiers to conduct the heat away from the power transistors, thereby allowing them to be used for the delivery of greater power.

### HIGH-PASS FILTER

A filter which, above a critical frequency, allows the unrestricted passage of high-frequency signals. Reciprocally, a bass-cut filter.

### HUM

Spurious signal at the mains frequency (50Hz in the UK) and its harmonics. It is sometimes expressed with noise (see under Noise), so that the total effect is hum and noise.

### HUM-LOOP

A condition arising from the connection of two or more 'earths' to an amplifier system whereby circulating currents of low value at mains frequency and harmonics are added to the programme signals, causing hum to appear in the background.

### INPUT IMPEDANCE

The effective impedance at the input circuits of an amplifier across which the signal source is connected. In this respect the source is loaded by the input impedance. A load sensitive source is a magnetic pickup, most of which are designed for optimum treble response connected to a load of about 47k $\Omega$ . A higher resistance will cause a rise in treble, and a lower one a fall in treble.

### INTEGRATED AMPLIFIER

An amplifier which embodies in a common housing the preamplifier and control section and the power amplifier. Some early amplifiers of large power were in two separate units, one the control unit with preamplifiers and the other the power amplifier.

### INTERMODULATION DISTORTION

Resulting from amplitude distortion (i.e., non-linearity) two or more signals passing through an amplifier intermodulate and hence produce spurious signals, known as intermodulation distortion. Since the distortion components are inharmonic they are subjectively disturbing, more so than low order, even harmonic distortion. Discontinuity in the crossover function of class B amplifiers is responsible for intermodulation distortion and, sometimes, the listening fatigue resulting therefrom. Measurement in based on the voltage of the intermodulation components expressed as a percentage of the voltage of one of the test signals, when two signals are applied to the amplifier in a 4:1 amplitude relationship at a low (100Hz) and high (5kHz) frequency.

### LINE INPUT

Input channel of an amplifier designed to accept signal at a given level from a line at a specific impedance, usually 600 $\Omega$ .

### LINE OUTPUT

Output channel of an amplifier designed to deliver signal at a given level to a line at a specific impedance, usually 600 $\Omega$ .

### LOAD


The circuit or transducer (e.g., speaker) connected to the output of an amplifier. The source (e.g., pickup) is loaded by the amplifier's input impedance (see under Input Impedance).

### LOUDNESS CONTROL

A control, often the volume control suitably switched, which boosts the bass and to a lesser degree the treble as it is retarded as a means artificially of compensating for the ear's loss of sensitivity at bass and treble frequencies at reducing loudness. A volume control which is permanently arranged to operate in this manner (i.e., loudness effect not switchable) is deprecated by some people and hi-fi enthusiasts.
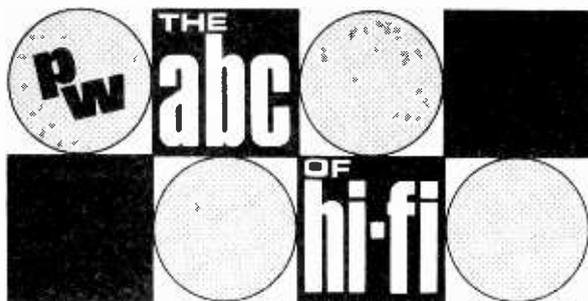
### LOW-PASS FILTER

A filter which, below a critical frequency, allows unrestricted passage of low-frequency signals. Reciprocally, a treble-cut filter.



## MATCHING

This commonly refers to the selection of the correct impedance to match the source or load and of the correct sensitivity of the input to match the source signal. If the source yields a signal substantially greater than the input sensitivity of the amplifier the volume control will have to be operated at a low setting and overloading of the input preamplifier may result.

## MISMATCH

A condition whereby the coupled impedances inhibit optimum power transference or the source or output signal fails to match the amplifier sensitivity or the load's (i.e., speaker) power capacity.

## MUSIC POWER

Sometimes called **dynamic power**, and refers to the power that the amplifier (with both channels working, when stereo) is capable of delivering on music type signal. Output is rated in watts into a specified load value and the test signal is sometimes interrupted sinewave signal (i.e., tone bursts). This method of power expression fails to take account of the power supply impedance and regulation and the efficiency of the power transistor heat sinks. The power obtained is always greater than that measured when the test signal is continuous wave (i.e., steady-state sinewave signal) and with both channels driven together (see under Output Power).

## NOISE

Spurious signal resulting from the random electrical charges existing in conductors, components, valves and transistors. It is heard from the loudspeaker as a 'hiss'. Hum (see under Hum) is also sometimes included as general noise, but since the hum is sometimes filtered in certain measurements, hum and noise may be expressed separately.

## OUTPUT IMPEDANCE

Effective impedance across the output terminals of an amplifier as reflected across the load (i.e., speaker). This impedance is generally much lower than that of the speaker (see under Damping Factor).

## OUTPUT POWER

The maximum amount of power, limited by clipping or a specified value of distortion, the amplifier is capable of delivering to a load of given value (also see under Music Power).

Many transistor amplifiers yield increasing power with reducing load value, and the power is generally given at 4 and 8Ω (sometimes also at 16Ω). The power of stereo amplifiers is given per-channel with one channel only driven and/or with both channels driven together. The almost double demands on the power supply when both channels are driven together reduces the per-channel

power significantly unless the supply is regulated or of a very low impedance when the power amplifiers are class B (see under Class B). However, this does not follow with class A amplifiers (see under Class A) because the power input remains constant within the dynamic range (see under Dynamic Range) of the amplifier.

The most meaningful power rating is that based on continuous wave (i.e., uninterrupted sinewave) signal with both channels driven to capacity together, referred to a specified level of distortion (0.5 per cent or 1 per cent), the power then being calculated by squaring the r.m.s. voltage across the load and dividing by the load value on ohms. This gives the **average power** per-channel, both running, **not** the r.m.s. power as often thought and, indeed, specified by many manufacturers!

The peak power on a continuous wave signal is equal to the square of the peak value of the sinewave divided by the load in ohms. Thus when the sinewave passes through zero the power is zero. Hence the average power is equal to half the peak power. The peak power is also equal to the square of the r.m.s. voltage across the load times the square of root-two divided by the load in ohms. Hence half of this, which is then equal to the square of the r.m.s. voltage divided by the load in ohms, is the **average power**. The power in r.m.s. watts can be obtained by calculation, and it works out to **1.225 times** the average power! This is almost 23 per cent higher than the average power. We often wonder whether the spec. writers are aware of this.

## OVERLOAD

When an amplifier is driven beyond its capacity the waveform is clipped and overloading and hence heavy distortion results.

## OVERLOAD MARGIN

It is desirable to have a margin prior to the onset of overload to avoid clipping on transients. This also enhances the reproduction, giving it a 'smoother' quality in many cases.

## POWER BANDWIDTH

The bandwidth over which the full power does not drop below a specified value. The l.f. and h.f. points where the power is half that at 1kHz (i.e., full power) are often given. This is the **half-power bandwidth**. Expression is commonly such as '20Hz to 35kHz — 3dB', the —3dB indicating a power drop to half the full value.

Sometimes the bandwidth is referred to the low and high terminal frequencies where the distortion fails to rise above a specified value, the DIN value being 1 per cent.

## QUIESCENT CURRENT

The static current drawn by the valves or transistors of a push-pull class B output stage as determined by the biasing in the absence of drive signal. See also under Class B.

## RADIO BREAKTHROUGH

The breakthrough of modulated radio signals into the channels of an audio amplifier owing to the presence of high-level radio signal fields. The effect is that the base/emitter junction of the low-level input transistor rectifies the signals picked up by the wiring or circuit components and the resulting audio is then handled by the amplifier in the ordinary way so that the radio programmes appear as a disconcerting background on the wanted source signal.

Since the pickup preamplifier has the lowest level input, this source is most troublesome, particularly when the volume control is well advanced. In many cases the trouble can be cured without affecting the amplifier's

response or unduly changing the input impedance (when the preamplifier is in an equalising feedback loop) by connecting a 2000pF capacitor between the base and emitter of the pickup input transistor, using the shortest possible connecting wires. Both channels of a stereo amplifier must be processed.

#### **RIAA**

Standing for Record Industry Association of America and refers to the recording characteristic of gramophone records. The pickup equalising is a reciprocal of this characteristic.

#### **RISE-TIME**

Time taken by an amplifier for its output to rise from 10 per cent to 90 per cent of its final value when a perfect step (i.e., one with zero rise-time) is applied to the input. The rise-time is a function of the bandwidth.

The upper frequency response of most hi-fi amplifiers, with the treble filter off, is generally sufficient to give a rise-time well in advance of that of most programme material. (see also under Attack and Transient Distortion).

#### **ROLL-OFF**

The rate of attenuation of a filter at the bass end (high-pass) or treble end (low-pass). The crossover frequency is that frequency where the response is -3dB of the mid-frequency response. The roll-off of an amplifier is similarly defined but in terms of decrease in amplification.

#### **RUMBLE**

Infrasonic disturbance due to the electro-mechanical action of a record player.

#### **SENSITIVITY**

Input signal voltage (r.m.s.) at 1kHz required to produce maximum amplifier output when the volume control is at maximum and the tone controls and filters set for a 'flat' response and, in the case of stereo amplifiers, with the balance control at neutral.

#### **SIGNAL/NOISE RATIO**

Voltage or power output due to unwanted noise referred to the full power of an amplifier or to some other datum. A S/N ratio of 60dB implies that the unwanted noise is  $10^6$  below the full power or  $10^3$  below the full voltage of the amplifier. The noise may or may not include hum. This is sometimes made clear by the parameter being expressed such as 'hum and noise 60dB below full output'.

#### **TRANSIENT**

Signal component of fast rising leading side and usually of short duration.

#### **TRANSIENT DISTORTION**

Distortion of a transient signal component such as produced by resonance and lack of damping, the effect being overshoot or ringing following the fast rising leading side of the signal component.

#### **WATTS RMS**

A commonly incorrectly used term for continuous wave power (see under Output Power).

#### **WEIGHTED**

Often applies to the filtering of a disturbance signal (such as noise) to take account of its annoyance value rather than its absolute value. A weighted S/N ratio is

always better than that obtained from the same amplifier (etc.) when unweighted.

# **TUNERS**

#### **AMPLITUDE MODULATION (AM)**

Where the audio (or other) information applied to a radio wave causes changes in amplitude. Used generally in the long, medium and short wavebands but is not a hi-fi system as currently employed.

#### **ATTENUATOR**

Network for reducing signal level. Sometimes necessary in the aerial circuit of a tuner to avoid overloading by strong, local signals.

#### **AUTOMATIC FREQUENCY CORRECTION (AFC)**

Often termed automatic frequency control and is a circuit arrangement used in f.m. tuners to correct automatically for any initial, long or medium term tuning error. Currently based on a capacitor diode in the oscillator tuning whose reverse bias is adjusted by a potential delivered by the f.m. detector when the tuning is in error. In some applications it is desirable for the correction to be switchable to avoid the tuning pulling on to a strong station when it is required to receive an adjacent weaker one.

#### **AUTOMATIC GAIN CONTROL (AGC)**


Circuit arrangement which yields a gain reducing bias with increase in signal strength as a method of keeping the output of the tuner constant irrespective of the strength of the received signal.

#### **BALUN**


Usually a transformer designed to accept 75Ω unbalanced input (coaxial cable) and deliver the signal at 300Ω balanced (twin feeder). Usable in the converse sense, and sometimes necessary for matching a tuner with 300Ω balanced aerial terminals to 75Ω coaxial feeder.
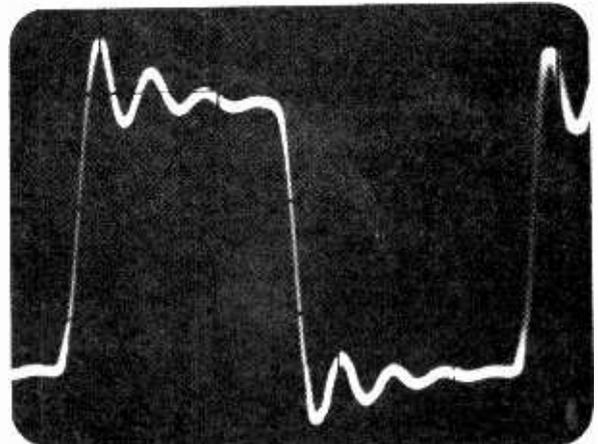
#### **CAPTURE EFFECT**

Effect characteristic of the f.m. system whereby the stronger of two signals, even when in the same channel, 'captures' the tuner so that it responds mostly to this one, pushing the weaker unwanted one well into the background.



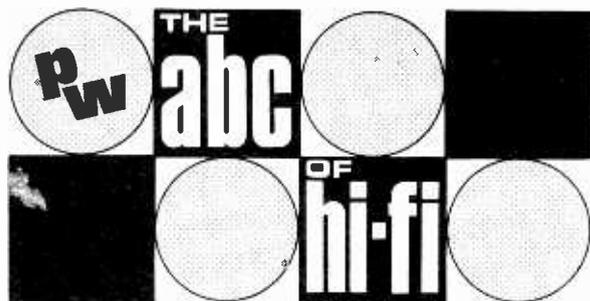**Transient Distortion.** Example of transient distortion where the fast leading edge of a squarewave initiates ringing.



### CAPTURE RATIO

IHF term which refers to the power ratio of two signals in the same channel required to keep the signal/interference ratio to a value of 30dB referred to 100 per cent modulation and 1mV input signal level. The ratio of the powers of the two input signals is expressed in decibels, the smaller the dB number the better the capture ratio. Top-flight tuners have a value as low as 1dB.

### DECODER

Device used in stereo tuners for yielding the left and right channel signals from the multiplex signal fed in from the f.m. detector.

### DISTORTION

Harmonic distortion produced by tuners is generally given at 100 per cent or 30 per cent modulation and 1kHz. F.M. detector non-linearity may cause the distortion to rise with increasing modulation percentage. Owing to the attenuation of the higher-order harmonics, the THD may be less from tuners with the American 75 $\mu$ S de-emphasis than from those based on the British (and European) 50 $\mu$ S de-emphasis. Distortion on stereo is also usually higher than on mono.

### FIELD EFFECT TRANSISTOR (FET)

Transistor whereby the current is controlled by electrostatic means. These devices have greater overload immunity than bipolar transistors and a square-law characteristic (minimising third harmonic components) and for these reasons are favoured by many designers for use in the r.f. amplifier and mixer stages.

### FREQUENCY MODULATION (FM)

Where the audio (or other) information applied to a radio wave (i.e., carrier wave) causes changes in the instantaneous frequency of the wave at a rate determined by the modulation frequency and by an amount determined by its magnitude. 100 per cent f.m. corresponds to  $\pm 75$ kHz deviation on the broadcasting system. F.M. is a hi-fi system of broadcasting also allowing the addition (in a subchannel) of stereo information. See under Decoder.

### IMAGE REJECTION

This refers to the rejection by the tuner of a signal at the image (second channel) frequency, corresponding to the tuned (real) frequency plus twice the intermediate-frequency when the local oscillator is working above the signal frequency or minus twice the intermediate-frequency when the local oscillator is working below the signal frequency.

The IHF image rejection ratio refers to the ratio (in decibels) of the signal required for a 30dB S/N ratio to that required for the same ratio but at the image frequency. Front-end selectivity increases the ratio.

### INTERMEDIATE FREQUENCY (IF)

The fixed frequency resulting from heterodyning (i.e., 'beating' or modulating to develop the sum or difference frequency signal) the incoming signal with a signal from the local oscillator. The i.f. used in f.m. tuners is commonly 10.7MHz and in a.m. tuners 470kHz. The i.f. signal is amplified in the i.f. channel and it is here where most of the selectivity is introduced by tuned bandpass couplings and/or crystal or ceramic filters.

### INTERMODULATION

This can result in the tuner front-end owing to the application of two or more powerful signals. In the group of the three f.m. stations (Radios 2, 3 and 4), third-order intermodulation can put interference on Radio 3. The solution lies in reducing the strength of the signals by attenuation.

### MULTIPATH DISTORTION/RECEPTION

Owing to reflection of the v.h.f. f.m. signal by large buildings, hills, etc., the tuner sometimes receives not only the direct signal but also a reflected signal slightly later due to the greater path distance travelled. This results in high-order harmonic distortion and impairment to the stereo separation and quality.

### MULTIPLEX (MPX)

The name sometimes given to the stereo system of broadcasting and the complex signal delivered by the f.m. detector for application to the stereo decoder.

### PILOT TONE

The signal included with the stereo information, and applied in a subchannel on the f.m. signal, which is used to reform the suppressed subcarrier and synchronise the switching of the detectors in the stereo decoder. Pilot tone frequency is 19kHz, and doubling this (38kHz) gives the subcarrier frequency. The pilot tone also activates the stereo indicator light switching.

### QUIETENING (MUTING)

A muting circuit which 'quietens' the audio channel when tuning between f.m. stations and which is 'cancelled' when the incoming signal is of a pre-determined (preset) level.

### QUIETING

The amount (expressed in decibels) by which the noise output of an f.m. tuner is reduced when the input signal is at a given level (see also under S/N Ratio and Sensitivity).

### SELECTIVITY

The ability of a tuner to select the wanted frequency without interference from signals at adjacent frequencies. Front-end selectivity enhances the image (and i.f.) rejection ratio, while good i.f. channel selectivity prevents interference from unwanted stations at frequencies near to the tuned frequency.


Good i.f. selectivity is required by f.m. tuners to minimise 'birdies' interference on stereo reception, coupled with low-pass filtering (critical frequency about 53kHz) between the f.m. detector and stereo decoder.

The IHF selectivity, given in many tuner specs., refers to the ratio of the level of a signal in the alternate channel (400kHz away from the required station) to the level of the wanted signal for a signal/interference ratio of 30dB when the wanted signal is applied at a level of 100 $\mu$ V. The signal ratio is given in decibels, and the larger the number the

better the selectivity. Top-flight tuners with ceramic or crystal i.f. filters can have an IHF selectivity better than 50dB.
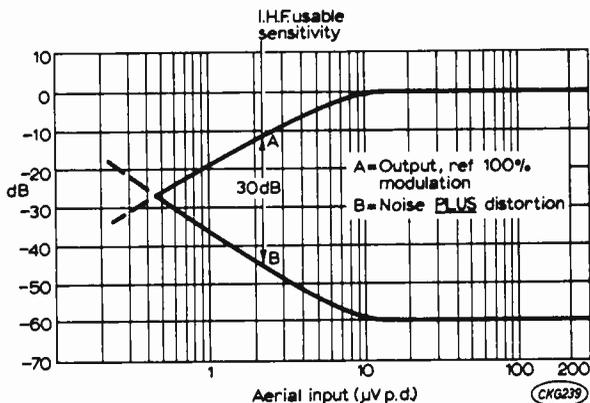
### SENSITIVITY


In general refers to the aerial input signal required for a given S/N ratio or quieting ratio (see S/N Ratio). The IHF usable sensitivity, frequently given in tuner specs., is the least aerial signal required across the tuner aerial terminals (p.d.) for a signal/noise plus distortion ratio of 30dB. Instead of the modulation being switched off it is notched out by a steep filter so that only the distortion and noise remains. The test is made with 100 per cent modulation.



**Sensitivity.** Graphical representation of IHF usable sensitivity.
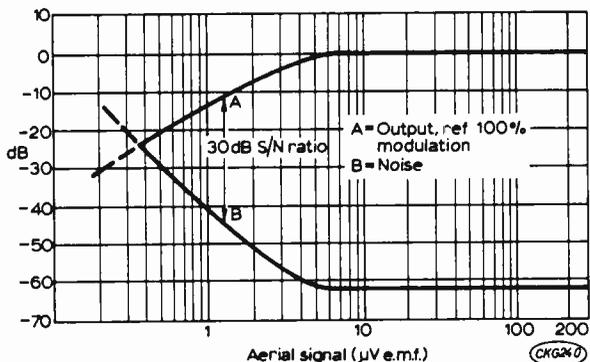
### SIGNAL/NOISE (S/N) RATIO

The ratio of the output signal to the noise at any given level of aerial signal. Signal modulation is either 30 per cent or 100, the latter giving an improvement over the former of about 9dB. A 0dB datum is established on the modulation, which is then switched off and the remaining noise measured. See also under Quieting and Sensitivity.



**Signal/Noise Ratio.** Curve A is tuner output referred to 0dB and 100% modulation. Curve B is noise output without modulation. Max. S/N ratio about 63dB while input of 1.4µV results in S/N ratio of 30dB.

### SPURIOUS RESPONSE REJECTION

The ability of an f.m. tuner to reject spurious signals falling outside the tuned frequency or the immunity of the tuner itself to the production of spurious signals as the result of intermodulation, etc. (see under Intermodulation).

### SUBCARRIER

The carrier used in stereo broadcasting to accommodate the subchannel stereo components. Frequency is 38kHz and is suppressed at the transmitter, leaving only the

sidebands, but is reformed at the receiver for detection of the stereo components by doubling the synchronised 19kHz pilot tone (see under Pilot Tone).

### TUNING INDICATOR

Often a meter which gives both an impression of the signal strength and the correct tuning point at maximum deflection. As maximum S/N ratio and least distortion occurs from an f.m. tuner only when the station is accurately tuned, a centre-zero meter might also be incorporated, and the tuning is carefully adjusted until this shows the correct condition of balance.

## ANCILLARY

### AMBIENCE

The term sometimes given to the 'colouration' of the signals due to the concert hall, etc. A kind of 'ambience' from stereo signals can sometimes be obtained by feeding the difference signals (appearing across the two 'live' terminals of the left and right channels) to a speaker sited behind the listener. More advanced matrices are necessary for full effect.

### ANTI-SKATING BIAS

A bias force applied to a pivoted pickup arm to counteract the inward force (towards the centre of the record) resulting from the drag of the stylus in the groove and the offset angle of the head.

### AUXILIARY BASS RADIATOR

A parasitic (non-electrically-driven) unit resembling a bass speaker unit located in a loudspeaker enclosure, as if it were an ordinary unit, to increase the movement of air and hence enhance the bass performance at a given enclosure volume.

### AZIMUTH

Referring to the vertical setting (alignment) of the head in a tape recorder.

### CCIR

Short for International Radio Consultative Committee, responsible for certain audio standards and tape play characteristics, among other matters.

### CERAMIC PICKUP

A pickup whose generator system is based on piezo electricity produced by the stressing of natural and man-polarised crystals.

### COMPLIANCE


Opposite to stiffness. A mechanical unit whose electrical analog is capacitance. In gramophone pickups one 'compliance unit' is taken as  $10^{-6}$  cm/dyne.

### CONE BREAKUP

The inability of a speaker cone to work as a piston at high frequencies, the effect being that the cone is not under the complete control of the speech coil, certain parts of it moving in opposition to other parts like a 'rippled rope'. Responsible for uneven frequency response.
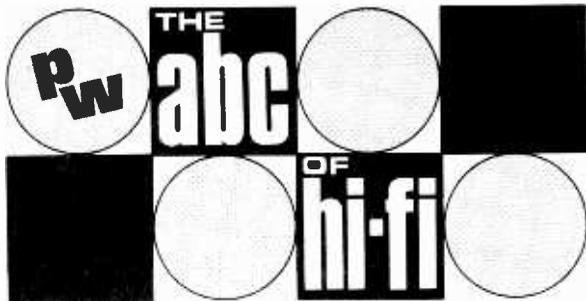
### DE-EMPHASIS

A method of signal equalisation where pre-emphasis is used during recording or transmission. Such as the pre-emphasis of the treble modulation on f.m. and the equalising de-emphasis at the tuner. Used essentially as a noise reducing artifice.



#### **DOLBY SYSTEM**

A noise reducing system whereby the recorded signal is 'compressed' and the replay signal 'expanded'. Originally used professionally, but a simplified version for domestic applications (for tape recorders, especially those based on cassettes) has recently been developed.

#### **DROP-OUT**

Short pause in tape replay due to bad tape coating.

#### **DUAL CONE**

Speaker unit containing a main cone for bass and middle frequencies and a smaller, stiffer inner cone for treble frequencies, sometimes called a 'full range' speaker unit.

#### **DYNE**

Unit of force equal to 1/980 gram at latitude 45° at sea level. Used in pickup mechanics especially.

#### **ELECTROMOTIVE FORCE (EMF)**

Electrical pressure at source. Not to be confused with potential difference (p.d.) which is the voltage developed across a resistance or impedance due to current flowing through it. Both are measured in volts.

#### **FLUTTER**

Cyclic speed variation of tape recorder (e.g. above about 10Hz) producing spurious signal related to the frequency.

#### **HEADSHELL**

The end of a pickup arm where the cartridge fits. Sometimes bonded to the arm, though often detachable.

#### **INERTIA**

Resulting from mass and inhibiting change in velocity. Important in pickup mechanics.

#### **INFINITE Baffle SPEAKER SYSTEM**

A speaker system where the bass driver is located in an almost airtight enclosure.

#### **LABYRINTH**

A type of speaker enclosure where a maze-like construction extends the air column. Resonances are tamed by heavy damping material.

#### **MASS**

The bulk of matter though not necessarily equal to its weight. A mechanical unit whose electrical analog is inductance.

#### **OMNIDIRECTIONAL**

Having no particular direction of maximum emission or sensitivity. Omnidirectional speaker is one which radiates theoretically equally in all directions.

#### **PARALLEL TRACKING ARM**

Pickup system which allows the cartridge to track on the true radius of the record, as the recording was made, thereby minimising lateral tracking error.

#### **PINCH EFFECT**

Slight variation in the width of the groove resulting from the mechanics of recording which cause the pickup stylus to vibrate vertically at twice the recorded frequency, giving second harmonic distortion.

#### **PLAYING WEIGHT**

The downward force required on the pickup stylus to keep it in the groove and to counter the mechanical reactions of replay.

#### **PRE-DISTORTION**

A scheme sometimes adopted during recording to nullify the effect of tracing distortion on replay. The distortion deliberately introduced is the reciprocal of that produced on replay.

#### **PRE-EMPHASIS**

Deliberate boosting of high frequency to allow attenuation on replay (or reception in the case of f.m.) as a noise reducing artifice. See also under De-Emphasis.

#### **QUADRAPHONY**

A scheme of extended 'stereo' whereby ambient and dimensional information is fed directly or via a matrix to a set of four speaker systems suitably orientated in the listening room. Two main systems are currently under development. One based on four discrete channels and the other on two channels into which are matrixed the information of the other two channels. In the latter system a reciprocal matrix at the reproducing end delivers a version of the original four channels for application to separate amplifiers and speaker systems.

#### **REFLEX SPEAKER**

This differs from an infinite baffle enclosure in that an air vent is incorporated which is tuned by its dimensions for the best bass performance in conjunction with the bass driver and the volume of the enclosure. The auxiliary bass radiator is a development of this technique.

#### **TIP MASS**

The effective mass at the tip of the stylus of a pickup cartridge. Modern techniques have reduced this mass towards 1 milligram or below.

#### **TRACKABILITY**

How well the pickup system will track high amplitude and velocity modulation at a given tracking weight.

#### **UNIPIVOT PICKUP ARM**

An arm which secures both the lateral and vertical movements from a single highly engineered pivot. Difficult to engineer, but characteristics (i.e., very low bearing friction) desirable when well engineered.

#### **VELOCITY PICKUP**

Magnetic pickup whose output increases with increase of recorded velocity. This differs from the ceramic pickup whose output is a function of amplitude or deflection of the stylus.

#### **WOW**

The complement of flutter, but at frequencies below about 10Hz.

# IC STABILISED POWER SUPPLIES

D. J. SILVESTER

THE design and construction of a compact high stability power supply results in a number of difficulties when the use of a 4½in. x 3½in. x 2in diecast aluminium box is contemplated. This particular supply unit has obvious uses as a 9V battery replacement, and since output current limiting can easily be added, the supply unit can be used in radio repair work where a current overload would otherwise cause irreparable damage. There is a limitation to the size of the mains transformer due to the smallness of the box, resulting in large variations of unregulated d.c. voltage, a difficulty which can be overcome.

The simple transistor-assisted zener circuit proved to be unstable because of these large voltage variations and the usual multi-transistor feedback circuits needed to give a stable output required more space than was available. The next step was to examine the possibility of using an integrated circuit as the feedback amplifier, and after this was done successfully a second and more powerful supply was built.

## PRINCIPLE OF OPERATION

The block diagram of Fig. 1 shows the basic circuit of the two power supplies. The principle of negative feedback requires that part of the output voltage be compared with a reference voltage, and the output regulator drive adjusted so that the two voltages become equal. The amount of correction applied to the output regulator is controlled by the gain of the

amplifier. It can be shown that the stability of the regulated output depends upon:—

1. The gain of the amplifier.
2. The variations of the amplifier output with changes in the unregulated d.c. supply.
3. The stability of the reference voltage.

The integrated circuit has a very high gain (100,000 times) and has been designed so that a change of 1V in the unregulated supply will cause only a 30µV change in the output. The first two


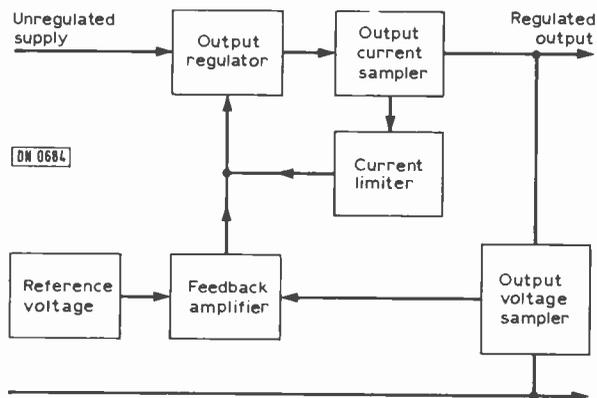


Fig. 1: Block diagram showing the various feedback paths of the stabilised supply.

sources of design difficulty are eliminated in practice if an i.c. is used as the feedback amplifier. The third source of instability due to the internal resistance of the zener diode can be overcome by providing a stable bias current from the regulated output, and by choosing a diode with a low internal resistance.
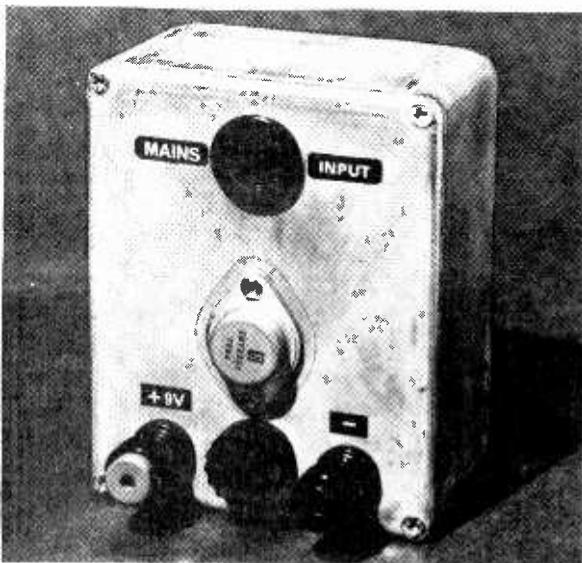
## FIXED 9 volts supply

The final circuit used for the smaller supply is shown in Fig. 2, the few changes required to give a higher output power will be discussed later. It is possible to use either a µA709C or µA741C integrated circuit as the feedback amplifier, and as five possible package alternatives exist, this component has been represented by the box with connections A to E. These alternatives, as well as the three extra frequency stabilising components required with the µA709C are shown in Fig. 3. It is preferable to use the µA741C integrated circuit since this device will be undamaged should the inputs or



Front view of the completed 9V supply.

DN 0685


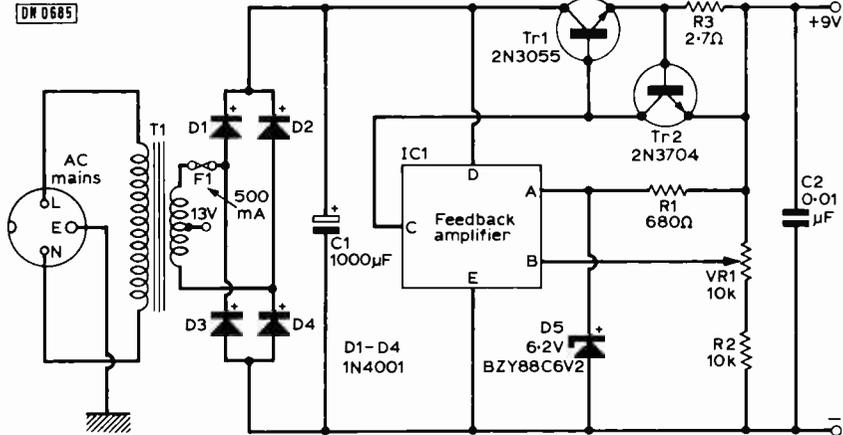


Fig. 2: Above, complete circuit of the fixed 9V supply. Fig. 3: left, connections of the various forms of the integrated circuit that can be used. Fig. 4: below, shows the veroboard layout for the smaller components. The 5000pF capacitors and 1.5kΩ resistor (see text) were fitted on the prototype.

DN 0686

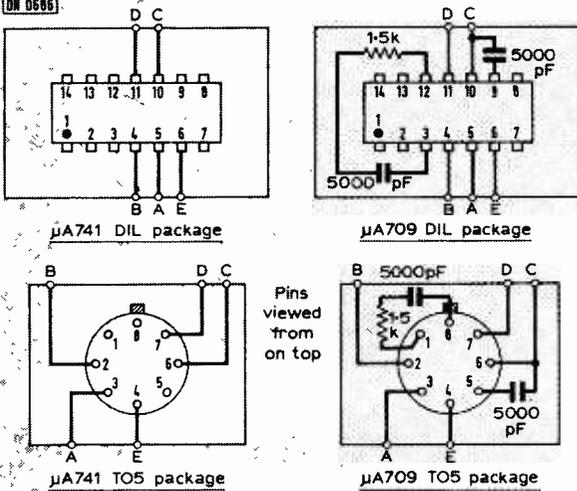


### ★ components list

R1 680Ω 1/4W 5%      R2 10kΩ 1/4W 5%  
 R3 2.7Ω 3W wirewound      C1 1000μF 25VW  
 C2 0.01μF      VR1 10kΩ skeleton preset

Tr1 2N3055      Tr2 2N3704  
 D1-4 1N4001 or 1A bridge rectifier  
 D5 BZY88C6V2 (6.2V 400mW)  
 IC1 μA741C (μA709C may be used, see text)  
 T1 230V/12-13V 500mA

Red and black insulated terminals. Die cast box, 4 1/4 x 3 1/2 x 2 1/2 in. Mains input plug and socket. Fuse 500mA and holder. Veroboard 3 x 1 1/2 in. 0.1 in. matrix. insulating kit for 2N3055.


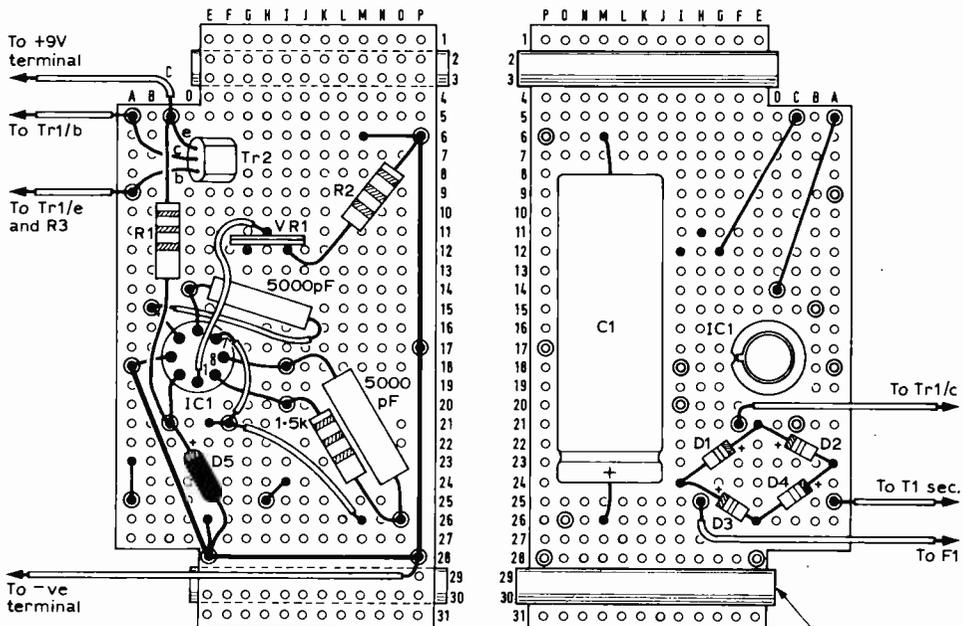


DN 0687
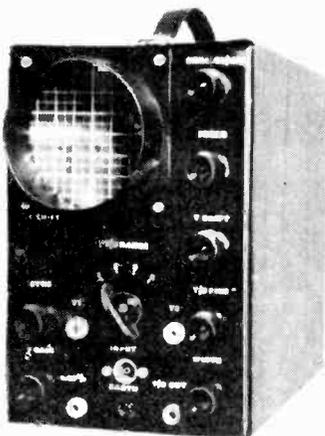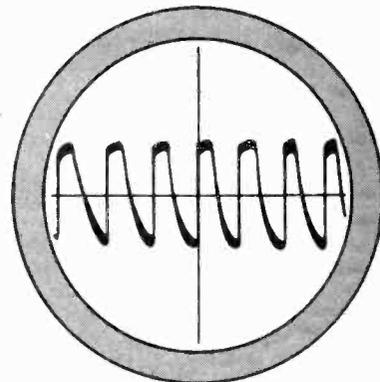
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
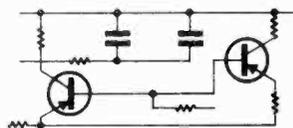
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
*we do not employ representatives*

NAME

**BLOCK CAPS**

ADDRESS

PLEASE WL112

**special free gift also to all our students**

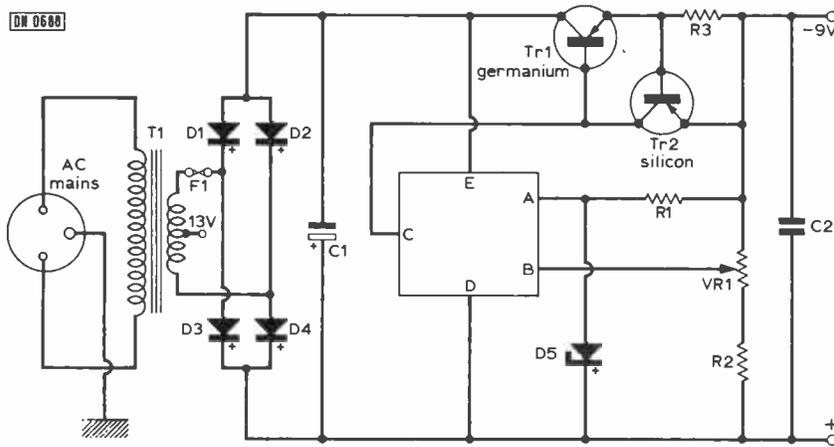


Fig. 5: Variation of circuit shown in Fig. 2 to permit the use of p.n.p. transistors such as may be found in an existing unregulated supply.

output be shorted to either chassis or the unregulated d.c. supply.

The current limiting device consisting of R3 and Tr2 can be omitted if this facility is not required. The short circuit current with the components chosen is 250mA. The potentiometer VR1 is used in place of a single resistor in the output sampler, so that the output voltage may be set accurately to 9V when construction has been completed. It was not necessary to reduce the sensitivity of this control by using a three resistor potential divider.

### CONSTRUCTION

Very little information is required on the layout of the circuit components, which, with the exception of Tr1, R3 and the transformer, can be assembled on a very small piece of veroboard (Fig. 4). One idea which greatly helps the final wiring is that all the components and board are mounted on the lid of the box. A neater appearance results if the larger components and the circuit board are stuck to the lid with epoxy resin adhesive.

The power transistor uses the box as a heat sink but it must be electrically isolated with washers. The wiring should be thoroughly checked before switching on, after which the output can be set to 9V by adjusting VR1. A 47Ω resistor connected across the output should not cause any change in the output voltage.

### VARIATIONS


It is possible to alter an existing power supply having germanium p.n.p. transistors, by using a variation of the original circuit, shown in Fig. 5. The unregulated d.c. supply must not exceed 36V or the i.c. will be damaged. If a different value of output voltage is required the values of R1, and VR1 and R3 must be recalculated.

If only a small current is required from the regulated output the power transistor can be replaced by a BFY51 or removed completely if an output of less than 10mA is required.
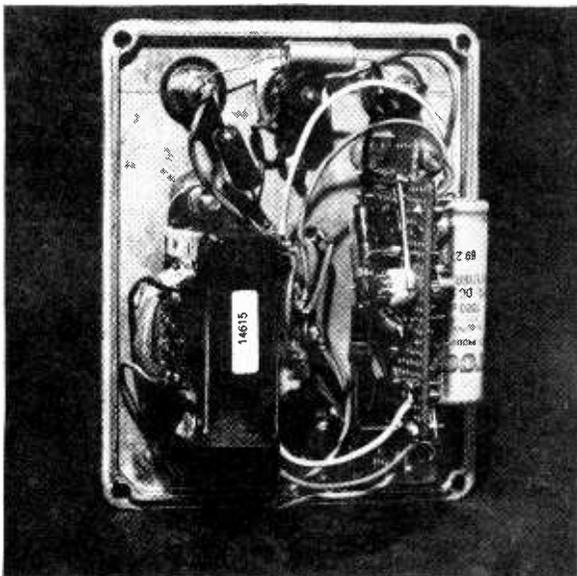
## VARIABLE voltage supply

After the successful construction of the 9V fixed supply it was decided that a much more versatile supply could be constructed using the same basic circuitry. This new supply would be capable of powering small hi-fi amplifiers, and it was decided that in order to increase its usefulness the supply should be able to deliver a constant voltage in the range 10 to 25V at a maximum current of 1A. A few small design changes must be made to the circuit of the fixed supply, but one difficulty, the large variations in the unregulated d.c. supply, is to some extent overcome. The final circuit of the second supply is shown in Fig. 6.

The transformer used gave between 20 and 23V a.c. to the bridge rectifier consisting of four 3A 50V diodes, D1 to D4. These diodes produce a d.c. voltage of between 30 and 36V across the capacitor C1, the value of this component being increased to 5000μF by using two separate 2500μF electrolytics in parallel.



Inside the fixed voltage supply unit. The transformer is fixed to the lid with epoxy resin as are short lengths of studding to locate the circuit board.

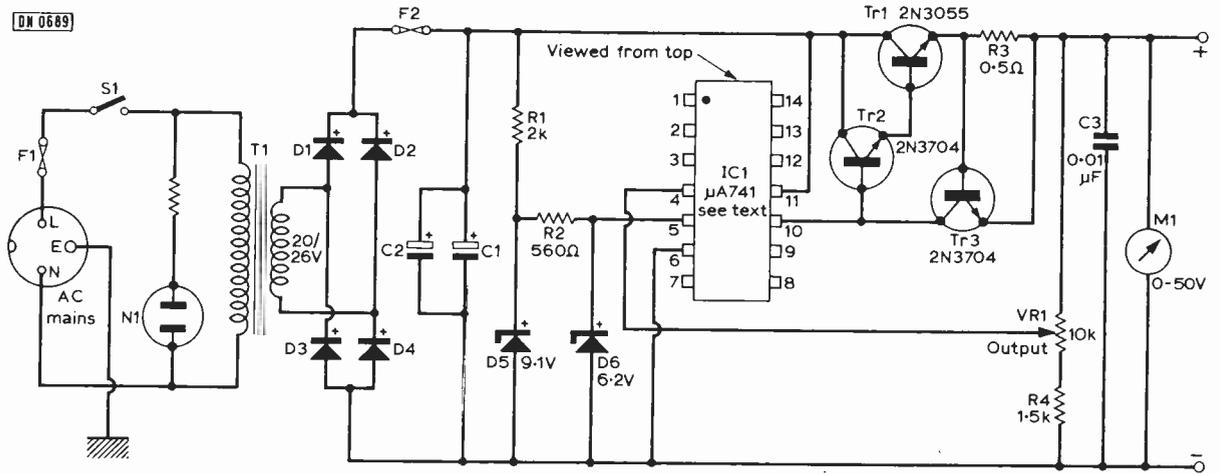


Fig. 6: Circuit of the variable voltage power supply which includes a meter to monitor the actual output voltage.

It should be noted that on no account, or under any load conditions, must the voltage across C1 exceed 36V or the i.c. will be destroyed.

### OUTPUT CURRENT REGULATOR

The first transistor used for the current output stage is again a 2N3055 being the cheapest of a number of alternatives. The current gain of this transistor is about 20, which means that at maximum output current this transistor will require a base current of 50mA which is greater than the i.c. can supply. The final output current stage consists of a darlington pair Tr1, Tr2 using the 2N3055 and 2N3704/BFY51 transistors. It is calculated that the maximum current demand on the i.c. is now reduced to below 1mA. The value of the limited output current is 1.2A, obtained by reducing the value of R3 to half an ohm.

### REFERENCE VOLTAGE


The reference voltage is derived from a zener diode D6, and as the stability of this component directly affects the stability of the output voltage

some method of supplying D6 with a constant current must be found. The zener cannot be supplied directly from the regulated output so the most obvious alternative is to provide a stable d.c. voltage from a second zener diode, D5, biased from the unregulated supply. The amplifier chosen is the  $\mu$ A741C type used in the fixed supply but any of the alternatives given in Fig. 3 may be used if required.


### OUTPUT VOLTAGE SAMPLER

This part of the circuit consists of a resistor chain across the regulated output. The minimum output voltage occurs when the inverting input (lettered A in Fig. 3) is connected to the output rail, the output voltage being equal to the zener voltage of D6. The maximum output voltage is determined by the values of VR1 and R4. The value of R4 is calculated to be 1.3k $\Omega$  for an output of 30V. The preferred value nearest to this, 1.5k $\Omega$ , produced a drop in the maximum output voltage. There is a rapid increase in voltage with rotation of the potentiometer at the high voltage end, and although this causes some slight inconvenience it was not considered necessary to use separate resistor chains.

—continued on page 642

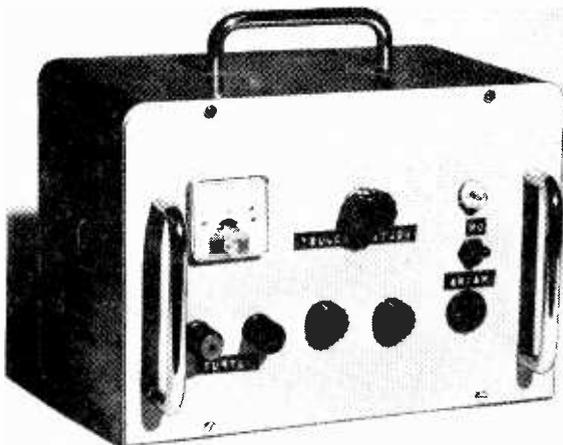

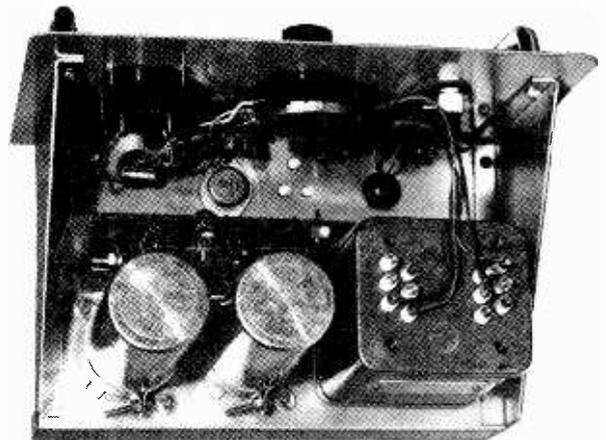Front view of the larger unit contained in a standard instrument case.



The smaller components are mounted on a vertical board shown above the large capacitors C1 and C2.

# LETTERS...

The Editor does not necessarily endorse the views expressed by correspondents

## Only knocks

I would like to comment on the correspondence regarding v.h.f. radio in your October issue.

Mr. James W. Robson's technical explanation for v.h.f. not having caught on is ingenious, but I fear, nonsensical. When f.m. was introduced in this country, and for several years after, only mains driven equipment was available for its reception. In those years, given suitable incentives, a large proportion of listeners could have been persuaded to buy f.m. radios. As it was, shackled by a monopoly broadcasting service, v.h.f. never stood a chance.

In the preface to "Radio & Television Servicing, 1955-56", a purely technical publication, the editors wrote: "... The outstanding feature of this period has undoubtedly been the inclusion, in the ranges of most manufacturers, of combined a.m./f.m. receivers for the reception of the BBC very-high-frequency (Band 2) transmissions..." In a subsequent edition it was stated that sales resistance to v.h.f. only sets was strong, and that the absence of Luxembourg on this band was partly to blame. And that is the situation in a nutshell. If only the opportunity had been taken at the time of the new channels becoming available to introduce independent radio stations, listeners would have clamoured for sets to receive them. Few saw the point of spending money to obtain carbon copies of existing programmes. A parallel may be drawn with the introduction of independent television on Band 3. In the two years following the opening of the Lichfield transmitter I supplied and installed upwards of 1,000 Band 3 converters. In the first two years of the BBC-2 625-line service I had orders for just two conversion kits. Even to this day I find customers with facilities for v.h.f. radio and 625 line television who have no intention of using them. What a monument to wasted opportunity!

One might have thought that the instant and overwhelming success of the so-called "Pirate" radio stations in 1965 would be construed as a clear indication that something was seriously

wrong with broadcasting in this country. Attempts to legalise the pirates were frustrated by the BBC, who solemnly announced that it was quite impossible to find space for any more stations on the medium wave band. No one appears to have thought of offering the largely unused v.h.f. band. Now the BBC has done a complete about turn by foisting its local radio stations onto medium waves. Nothing could be a greater admission of failure on the part of monopoly broadcasting to attract listeners to v.h.f.

The promised commercial stations may inject some life into v.h.f. reception, if only because all will be capable of transmitting in stereo, but by and large I am compelled to admit that I am far from sanguine. Even Lord Hill, contemplating the prospect of medium-wave reception in the future, is quoted as saying, "... and may the Lord have mercy on you after dark!" Unfortunately, f.m. broadcasting missed the boat 17 years ago, and opportunity, as they say, only knocks once. — **Charles Miller** (*Uttoxeter*).

## Local radio

No doubt many readers will have noticed the additional interference caused in the m.w. band by the opening of local radio station m.w. transmitters recently, by the BBC. These transmissions, at night, can scarcely be described as local, with a range of over 200 miles. In my location, Radio London is very powerful, and has been received at night in Holland, France and Northern England. This rather defeats the BBC's good original object of a local radio service. Could not the BBC shut down the 206 metres Radio London m.w. outlet, and other outlets, at night, when local radio simply relays programmes carried by Radios One and Two. The v.h.f. outlets could of course remain, as they have done previously. This step would reduce the amount of interference with foreign services, and would bring BBC local radio in line with the proposed restrictions to be imposed upon local commercial radio stations.—**John Manners** (*Middlesex*).

## Quadraphonics

I am interested in building myself a Quadraphonic Hi Fi system.

The design of the preamplifiers and power amplifiers is relatively straightforward, but as yet I have been unable to find any details on how to design the four channel matrix decoder.

An article in your magazine on either the principle of operation or a practical circuit would be of considerable value to myself and I am sure to other people.—**P. M. Cunnington** (*Essex*).

Your letter has been forwarded to me by the Editor and I must comment, with a copy to the Editor, in the hope he may publish, for your letter raises one or two interesting points.

First, before we could contemplate publishing the circuit for a decoder, we must know something of the encoding. Quadraphonics is very much in a state of flux.

In April, there was a show at Osaka, and about half of the 38 exhibitors had some sort of four-channel exhibition. Few were convincing. Most annoying was the fact that few were mutually compatible—nor even tried to be!

There are, basically, three systems of stereo recording: the CD-4 of Matsushita and JVC-Nivico, with American backing from RCA; the SQ, with CBS and Sony throwing in their weight, to which EMI have now added their backing in this country. And last is what might be called a 'Regular Matrix' system, like the Sansui QS, and several related alternatives.

There is no 'universal' decoder, and until the vast commercial battle is won and there is a 'standard' method of encoding, we should play it very close to the chest. I would advise you, Mr. Cunnington, to forgo the pleasure of anything but purely discreet quadraphonics until your way ahead is sufficiently clear. In any case, you can go ahead with preamps and power amps—and, I hope, separated power supplies—with the knowledge that whatever decoder is appropriate to the software available to us (mostly SQ at present, will soon be made available to the constructor.—**H. W. Hellyer** (*Bristol*).

# The BIG discount house!

## AMPLIFIERS

Amstrad Integra 4000	£22-70
Amstrad 8000	£13-95
Amstrad 8000 MK II	£15-95
Amstrad IC 2000	£27-00
Amphonic 1000	£14-95
Cambridge P50	£68-00
Cambridge P100	£115-00
Dulci & Eagle—Full range available	
Ferrograph F307	
MKII Wood Case	£45-95
Leak Delta 30	£48-00
Leak Delta 70	£58-75
Linear 606	£17-25
Linear LT66	£16-75
Linear 505	£13-75
Metrosound ST 20E	£24-25
Metrosound ST.60	£45-75
Phillips RH 580	£39-00
Phillips RH 590	£39-00
Phillips RH 591	£59-00
Pioneer—Full range available	
Rogers R/Brook CH	£36-00
Rogers R/Brook Cased	£40-00
Rogers R/Bourn CH	£41-95
Rogers R/Bourn Cased	£48-50
Rotel RA 210	£23-00
Rotel RA 310	£30-50
Rotel RA 610	£48-00
Revox A 78	£104-00
Sansui Full Range In Stock.	
Sinclair, Wharfedale Linton & Quad—Full range available	

## (Carriage and packing 50p.)

## TUNER AMPLIFIERS

AKAI AA 5501	£167-95
AKAI AA 6600	£104-00
AKAI AA 6300	£92-00
AKAI AA 6200	£71-95
Wharfedale 100.1	£89-00
SONAB R4000	£130-00
Sansui full range in stock	
Phillips RH 702	£69-00
Phillips RH 901 with SPKS	£74-00
Goodmans Module 80	£68-95
Goodmans One Ten	£99-00
Leak Delta 75	£124-00
Rogers R/Brk Cased	£78-50
Rotel Fax 311A	£64-95
Rotel Fax 550A	£76-95
Rotel Fax 660A	£83-75
Rotel RX 150	£52-95
Rotel RX 200	£67-00
Rotel RX 400	£76-95
Sharp STA 32L	£89-95

## Carriage and packing 50p.

## TUNERS

Amstrad MLX 3000	£28-70
Leak Delta FM	£55-95
Leak Delta AM FM	£66-00
Korting T 600	£39-75
Pioneer TX 1000	£130-00
Pioneer TX 900	£109-00
Pioneer TX 800	£92-00
Pioneer TX 700	£82-00
Pioneer TX 600	£75-95
Pioneer TX 500A	£51-00
Sinclair PRO 60	£16-75
Sinclair 2000/3000	£32-50
Rogers R/Brk Cased	£35-00
Rogers R/Brk CH	£31-00
Rogers R/Brk Cased	£31-95
Rogers R/Born CH	£43-00
Rotel RT 320	£38-50
Rotel RT 620	£69-00
Sansui full range in stock	
Revox A 76 FM	£150-00

## TUNERS carriage and packing 50p.

## SPEAKERS Priced per pair

Bowers & Wilkins D.M.1	£54-00 A
Bowers & Wilkins D.M.2	£87-00 B
Bowers & Wilkins D.M.3	£84-00 C
Bowers & Wilkins D.M.4	£220-00 CC
Cambridge R.40	£102-00 D
Cambridge R.50	£158-00 CD
Celestion Ditton 15	£53-00 B
Celestion Ditton 44	£75-00 C
Celestion Ditton County	£36-00 B
Celestion Ditton 25	£86-00 D
Celestion Ditton 66	£137-00 CD
Celestion Ditton 10	£36-00 A

Decca Deram	£34-00 A
Goodmans Magister	£77-50 D
Goodmans Magnum K 11	£58-50 C
Goodmans Mezzo 3	£44-75 B
Goodmans Dimens.on 8	£87-00 C
Goodmans Double Maxim	£48-00 B
Goodmans Havant	£39-50 B
K.E.F. Concerto	£90-00 2
K.E.F. Cadenza	£65-00 C
K.E.F. Chorale	£55-00 B
K.E.F. Celeste	£46-00 B
K.E.F. Crestor	£39-00 A
K.E.F. Canta	£41-00 A
K.E.F. Coda	£35-00 A
Keletron KN400	£13-00 A
Keletron KN600	£21-00 A
Keletron KN800	£26-00 A
Keletron KN1100	£32-00 B
Keletron KN1600	£40-00 C
Keletron KN2100	£50-00 C
Metrosound Duplex 15	£43-00 B
Metrosound Duplex 25	£75-00 B
Leak 600	£66-00 D
Leak 250	£47-00 D
Leak 150	£36-95 A
Phillips RH 407	£80-00 C
Phillips RH 406	£59-00 B
Phillips RH 402	£33-00 A
Phillips RH 412	£28-00 A
Phillips RH 411	£18-00 A
Ste-Ma HI-F15	£85-95 D
Ste-Ma 350	£54-00 C
Ste-Ma 450	£42-00 B
SONAB A VI	£91-00 A
SONAB OA 4	£86-00 C
SONAB OA 5	£110-00 C
SONAB OA 5K	£65-00 C
SONAB OA 5K	£65-00 C
SONAB S55	£17-50 A
SONAB OA6	£248-00 D
Tannoy Chatsworth	£57-00 D
Tannoy 12 Lancaster	£104-00 D
Tannoy 15 Lancaster	£114-00 D
Tannoy 3 LZ	£67-00 B
Wharfedale Denton 2	£29-00 A
Wharfedale Linton 2	£36-00 A
Wharfedale Triton 3	£52-00 B
Wharfedale Melton 2	£48-00 B
Wharfedale Dovedale 3	£59-00 B
Sinclair Q16	£12-00 A
Eagle DL67	£30-00 A
Viceroy VSE 10	£25-00 A
Viceroy VSE 8	£20-00 A
Viceroy VSM 15	£32-00 B
Viceroy VSM 5	£12-00 A
Viceroy VSM 20	£25-00 A
Viceroy Major	£50-00 B
Ferrograph SI Monitor (Stand Inc.)	£140-00 CC
Quad Electrostatic	£112-00 CC

## Carriage & Packing A-75p. B-£1-25p. C-£2. D-£2-50p.

## SPEAKER KITS AND CHASSIS

### Full selection in stock including

Priced Per Pair	
K.E.F.K. 2	£38-00 B
K.E.F.K. 3	£57-00 C
K.E.F.T.15 MKII	£9-75 A
K.E.F.T.27	£8-00 A
K.E.F.B.200	£15-00 A
K.E.F.B.110	£14-00 A
K.E.F.N.19 MKII	£47-95 B
Wharfedale Unit 3	£18-00 A
Wharfedale Unit 4	£24-00 B
Wharfedale Unit 5	£35-50 D
Peerless 2-8 Kit	£10-50 A
Peerless 3-25 Kit	£16-00 A
Peerless 20-2 Kit	£30-00 C
Peerless 20-3 Kit	£31-00 B
Peerless 3-15 Kit	£21-00 B
Peerless 430/12 Kit	£44-00 D
Carriage & Packing A-50p B-75p C-£1 D-£1-50p.	

## CASSETTE & 8 TRACK DECKS/RECORDERS

AKAI CR80	£80-00 B
AKAI CR80D	£65-50 B
AKAI CS50	£93-00 B

AKAI CS500	£78-00 B
AKAI GXC 40	£82-25 B
AKAI GX40D	£67-75 B
Phillips EL 3302	£15-00 A
Phillips N 2202	£117-75 A
Phillips N 2204	£22-75 A
Phillips N 2205	£32-50 A
Phillips N 2209	£39-50 A
Phillips N 2400	£51-75 A
Phillips N 2401	£62-50 A
Phillips N 2405	£54-00 A
Phillips N 2506	£47-00 A
Phillips N 2000	£10-50
Wharfedale DC9	£87-25 B
Metrosound 448	£41-00 A
Metrosound SS30	£64-75 A
Carriage & Packing A-50p, B-£1.00	

## CARRIDGES

Audio Technica AT 66	£3-75
Audio Technica AT 55	£5-00
Amstrad 9000	£3-45
Amstrad 900EX	£8-70
A.D.C. 10/E Mark 4	£20-50
A.D.C. 26	£44-00
A.D.C. 25	£63-00
Empire & Ortofon—Full range available	
Sonatore 8TAHCD	£1-45
Goldring G850	£3-25
Goldring G800	£5-00
Goldring G800/E	£7-00
Goldring G800 SE	£14-25
Shure V.15 Type 2 Impr	£24-50
Shure M75ED	£10-25
Shure M75EJ Type 2	£8-95
Shure M75 E	£7-25
Shure M55/E	£3-25
Shure M55/E	£5-65
Shure M44/E	£4-90
Shure M44C.5.7.	£4-55
Shure M3D	£3-94

## COMBINATION UNITS/COMPACT SYSTEMS

Phillips GF 836 Inc Spks	£63-00
Phillips GF 808 Inc Spks	£77-00
Phillips GF 805 Inc Spks	£59-00
Phillips GF 980 Inc Spks	£117-00
Phillips RH 811 Inc Spks	£95-00
Phillips RH 814 Inc Spks	£109-00
Phillips RF 835 Inc Spks	£54-00
Phillips RF 836 Inc Spks	£72-00
Phillips RH 802	£119-00
Phillips RH 891	£191-00
Fidelity UAI	£72-00
Decca Sound 613	£54-75
Decca Sound 614	£48-00
Decca Sound 1204	£75-00
Decca Sound 1203	£71-00
Decca Compact 3	£103-00
Goodmans Compact 80 White	£138-00
Goodmans Compact 80 Teak	£124-50

## PRECISION PICK-UP ARMS.

S.M.E. 3009/S2	£21-45
S.M.E. 3012/S2	£25-00
S.M.E. 3009/S2 (HE)	£28-00
S.M.E. 3012/S2 (HE)	£27-00
S.M.E. 3012/S2	£27-00
S.M.R. PI Spacer	£1-00
Audio Technica AT1005 MK II	£14-95
Audio Technica Lint L2	£3-00
Decca International	£19-65
Goldring L 69	£5-50
Goldring L 75	£9-50
Ortofon AS 212	£24-25
Neat G30	£11-95
Neat G30B	£13-95
Neat Life	£3-10
Transcriptor Fluid (Carriage and Packing 15p)	£24-00

## PLINTHS & COVERS

S.M.E. 2000 System in Teak, Walnut or Rosewood.	£37-50 B
Viceroy De Luxe for Garrard—AP76	
SL958 Zero 100 Base Teak—Top Perspex	
Size Approx: D. 38½ W. 38cm. H. 19cm	
Standard Version	£4-75 A
£4-50 A	

Viceroy De Luxe for Garrard 2025TC	
SP25, SL658 Base Teak—Top Perspex	
Size D. 32cm W. 37cm H. 18cm.	£4-50 A
Standard Version	£2-95 A

## HOWLAND AND WEST

Full range in stock Plinths & Covers (Carriage and Packing A-50p B-£1).

## TURNTABLES

Carriage & Packing 50p	
Garrard SP25 MK III	£10-00
Garrard AP76	£18-00
Garrard 401	£25-95
Garrard SL95B	£31-50
Garrard SL72B	£22-00
Garrard SL65B	£12-95
Garrard 2025 TC with	£9-00
Sonaton 9TAHCD	
Garrard Zero 100S	£36-00
Garrard Zero 100/A	£37-00
B.S.R. MP60	£9-50
B.S.R. MP60 TPD 1	£19-00
B.S.R. MP60 TPD 2	£17-00
B.S.R. HT70	£19-00
B.S.R. HT70 P-C	£28-00
Transcriptors Saturn	£54-00
Transcriptors	£75-00
Hydraulic REF.	
Transcriptors	£87-50
Hydraulic REF with 9" or 10" Arm	
Goldring GL/85/P with lid	£61-00
Goldring GL 75	£27-00
Goldring GL 75/P	£34-00
Goldring GL 69/P	£22-50
Goldring GL 72	£22-00
Goldring GL 72/P	£28-50
Goldring GL Lid	£5-00
Goldring GL Plynth	£7-00
Goldring G101/P-c	£28-00
Goldring G99	£24-00
Thorens TD 150AB	£37-00
Thorens TD 150A	£33-00
Thorens TX 11	£4-00
Thorens TD 150	£27-00
Thorens TD 150	£56-75
Thorens TD 125 mk II	£92-00

## MK II

Thorens TX 25	£6-50
Pioneer PL 12AC	£34-95
Pioneer PLA 25	£62-50
Phillips GA 202A with Cart.	£49-00
Phillips G. A. 212	POA
Phillips GA 308 Less Cart.	£31-00
Phillips GA 160 with Cart	£30-00
Sansui Full range in stock	
Sonab 75S	£53-00

## HEADPHONES

Koss PRO 600 4 AA	£23-00
Koss PRO 4 AA	£20-25
Koss KO 727B	£12-00
Koss K6	£9-00
Koss K6/LC	£10-00
Koss K7/11	£7-00
Koss ES P6	£33-99
Koss ESP9	£48-00
Koss KO 747	£15-00
Amstrad PHS5A	£3-90
Amstrad PHS6A	£6-70
Amstrad HPS 7A	£9-90
AKAI ASE 9	£4-25
AKAI ASE 22	£7-25
AKAI ASE 20	£6-00
Rogers R/Brook	£13-00
Pioneer best prices on application	
Pioneer SE30A	£8-00
Rotel 600	£4-50
Rotel 700	£7-25
Sennheiser HD414	£8-25
Wharfedale DJ	£8-35
Sansui full range in stock	
Stax SR. 3	£38-75
Tripletone TSH 1500	£11-00
Clark 103	£18-00
Grosvenor	£10-00
Phillips LBB 9901	£4-50
Carriage and Packing 15p.	

# AUDIO SUPPLIES

## THE BIG DISCOUNT HOUSE

We specialise in mail order/personal callers welcome. Send cheques, Money Orders P/O, Giro, Bank Draft or Cash (Registered) Barclaycard facilities by mail order.  
By quoting your Barclaycard number, name and address and expiry date, any item can be yours without delay by telephone or letter.  
Credit facilities available for Personal callers spending £50 or more. All goods are brand new, and carry manufacturers guarantees.  
For an extra charge: 36 hour securitor delivery (from when cheque is cleared). Personal callers Note: We are easy to get to by public transport (Open Mon., Tues., Weds., Thurs., 9.30 to 6 pm Sat 9.00 to 5pm).

Late Night: Friday 9.30 to 7.30pm.  
Send large stamped addressed envelope with all correspondence (except orders).  
All prices are subject to change as and when necessary.  
All mail order to Stamford Hill Address  
50 Stamford Hill, London N.6. Tel: 01-806-3611.  
120 Nottinghill Gate, London W11.  
Tel: 01-229 1437.  
Tivoli Shopping Centre,  
1536 Coventry Road, Yardley, Birmingham.  
12 London Road, North End,  
Portsmouth, Hants.

Please rush me the following items. P. & P. extra.  
I enclose cheque/money order to the value of.....  
Payable to Audio Supplies Ltd.  
Barclaycard No.....

NAME .....


ADDRESS .....

(Block Capitals Please) PW.11.



# SIMPLE R.F. SIGNAL GENERATOR

HALVOR MOORSHEAD

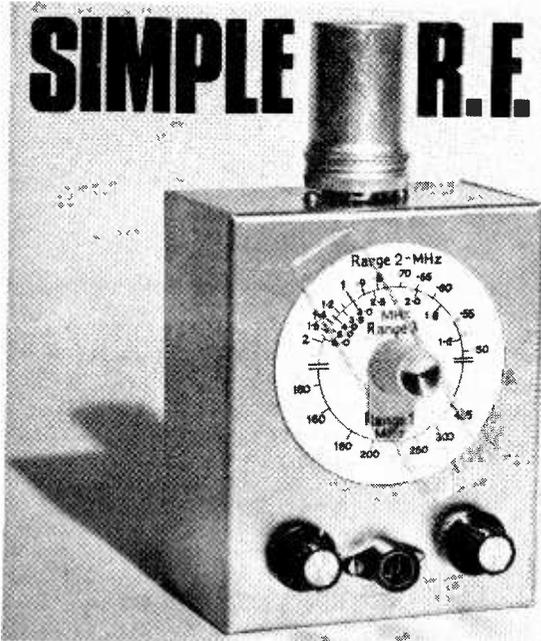

be considered in two distinct parts, the r.f. oscillator and the a.f. modulator. The r.f. side is very simple and comprises a tuned circuit (VC1 and La) with base coupling (Lb) with a feedback winding (Lc). Base bias for the transistor is provided through R1 while C1 decouples the supply line with the take off point being C2 from the collector of Tr1. A BC169C is used, mainly because of the lead configuration; this is a plastic encapsulated version of the BC109. The supply for this stage is provided through a dropping resistor R2.

The a.f. section comprises Tr2 and associated components. This is a Hartley configuration using a transistor output transformer type LT700. This is a completely conventional arrangement, the primary of the transformer is tuned by C4 with C5 providing the feedback coupling and R3 the base bias to start the operation (this resistor may not be necessary as the feedback should be of sufficient level to maintain oscillation but it is as well to include it to make sure).

The output from the a.f. oscillator is at a fixed frequency—in the case of the prototype it is about 800Hz but the exact frequency will depend on the particular transformer and on component tolerances etc. The frequency can be increased by lowering the value of C4 or omitting it altogether, relying on the self-capacity of the windings to tune it. The frequency can be lowered by increasing the value of C4.

The waveform from the audio oscillator is far from a pure sine-wave but this is of no consequence and serves the desired purpose admirably.

## FUNCTION SWITCH

Switch SW1 is the main function switch providing the on-off facility, r.f., modulated r.f. or a.f. at the output socket. In position A the battery is unconnected and so the circuit is off. In position B the

**T**HE r.f. signal generator forming the subject of this article was designed for the alignment of superhet receivers as well as for general purpose usage. The cost should be low as the coils are of the Denco plug-in type and do not form a permanent part of the circuit. This has additional advantages in that range switching is not necessary and all r.f. leads and connections can be kept very short; construction is also simplified greatly by using this method. The coverage of the generator depends entirely on the reader. Two coils will cover the medium waves, long waves and the i.f. of 465kHz but the prototype also worked on the short waves up to at least 10MHz; this however is not so vital as the harmonics of the lower ranges will get up to this frequency and way beyond. The circuit used has proved very reliable and gives a good output.

## THE CIRCUIT

The complete circuit is given in Fig. 1 and may

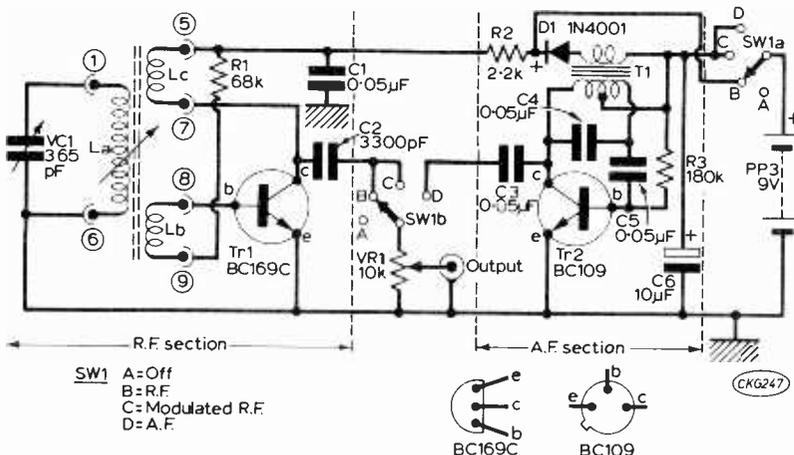


Fig. 1: The complete circuit of the R.F. Signal Generator. The required range is selected by plugging in the appropriate coil. SW1a and SW1b are ganged to give the required output.

positive supply is connected between D1 and R2. In this mode the diode will block any current to the a.f. oscillator and this will be inoperative. Current, however, is allowed to reach the r.f. stage and SW1b connects the output level control to the output of Tr1 via the d.c. blocking capacitors.

In position C, VR1 remains connected to the output of the r.f. section but SW1a applies current directly to the a.f. oscillator stage. In this mode D1 allows current to reach Tr1 but the positive supply is now connected via the secondary of the a.f. oscillator transformer. This creates a small, rapid change in the supply voltage in sympathy with the frequency of operation (800Hz in the case of the prototype) and so the output from Tr1 will also vary, modulating the signal. Normally it is not good practice to modulate an oscillator as this can cause both amplitude and frequency modulation but in practice some slight f.m. can be ignored. This arrangement gives a modulation depth of about 20 per cent.

In position D the positive supply is as for C but SW1b connects to the collector of Tr2 via the d.c. blocking capacitor C3 giving an audio output. If it is important that only pure a.f. is provided, the r.f. section can be made inoperative simply by unplugging the coil.

Capacitor C6 decouples the supply of the a.f. stage, the relatively low value is quite sufficient because of the audio frequency used.

The output of the r.f. section is about 500mV and that of the a.f. section about 400mV; in both cases this is more than adequate for normal usage and both outputs connect via the level control VR1 before connecting to the coax output socket.

## CONSTRUCTION

The coils used are the Denco plug-in types, these fit into a B9A valve-holder. The leads can be kept very short by building the r.f. section directly onto

## ★ components list

### Resistors

R1 68k $\Omega$  R3 180k $\Omega$   
 R2 2.2k $\Omega$  VR1 10k $\Omega$  lin. pot.  
 All fixed resistors  $\frac{1}{2}$ W, 5 per cent tolerance

### Capacitors

C1 0.05 $\mu$ F ceramic disc  
 C2 3300pF ceramic, polystyrene or silver mica  
 C3 0.05 $\mu$ F ceramic disc  
 C4 0.05 $\mu$ F ceramic disc  
 C5 0.05 $\mu$ F ceramic disc  
 C6 10 $\mu$ F 12V electrolytic  
 (All 0.05 $\mu$ F can be 0.047 $\mu$ F)  
 VC1 365pF tuning capacitor, Jackson Type 00

### Semiconductors

Tr1 BC169C D1 1N4001 or similar  
 Tr2 BC109

### Miscellaneous

Coils: Denco transistor range, Blue, 1T, 2T, 3T of to suit; T1: Eagle transistor output transformer type LT700; SW1: 4-way, 2-pole rotary type; B9A valve holder; Coax output socket; Veroboard 0.15in. matrix 16 x 13 holes; PP3 battery and battery clip; Terry clip for holding battery; Aluminium angle; Plastic sheet for pointer; Knobs to suit; Metal chassis 5 x 4 x 2 $\frac{1}{2}$ in.

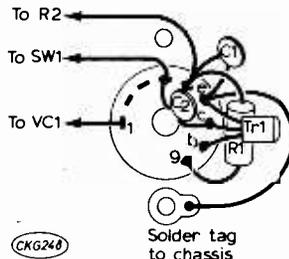


Fig. 2: The wiring of the r.f. section on the B9A valve base into which the coil is plugged.

the pins of the valveholder as shown in Fig. 2. To neaten the layout some changes have been made to the recommended Denco connections but the electrical result is the same. To bring the negative chassis connection to this part of the circuit a short wire runs to a solder tag fitted underneath one of the valveholder mounting screws.

Pin 4 of the valveholder does not connect to the coil and is only used as a convenient anchoring point for C2.

The layout and construction of the a.f. section is much less critical than that of the r.f. oscillator and can be built in any convenient form. In the prototype these components are mounted on a piece of Veroboard of standard 2 $\frac{1}{2}$ in. width, 13 holes long. The layout of this section is shown in Fig. 3.

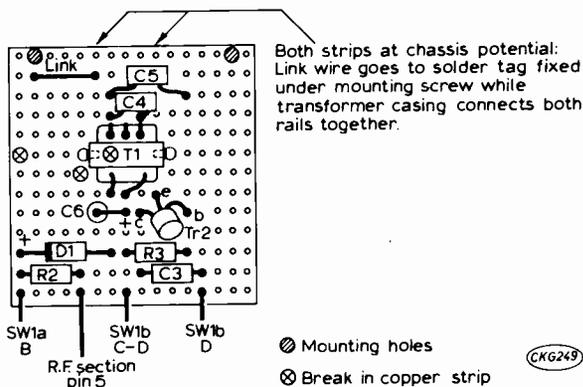


Fig. 3: The component layout of the a.f. section on Veroboard.

Holes should be drilled out to take the mounting screws and the lugs of the transformer. There are two strips on this board which are connected to chassis potential, these are linked together through the transformer casing, the lugs being bent inwards and soldered to the adjacent strip. One of these strips also connects to a link wire which runs to a solder tag fitted under one of the component board mounting screws.

There is no crowding of the components and construction should present no problems.

A few breaks are necessary in the conductor strip; one underneath the transformer is absolutely necessary, the other two will only be needed if the solder tag or the transformer lugs touch an adjacent strip.

Four take-off points are required; these are shown in Fig. 3 and Fig. 4, the latter shows the wiring not dealt with in the other drawings. A stiff wire should

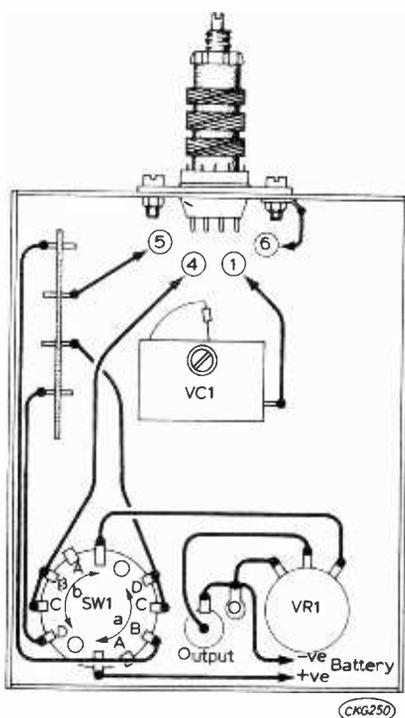


Fig. 4: The wiring between the controls and the two main operative sections.

be used from the fixed vanes of VC1 to pin 1 of the valveholder.

The rotary switch used is unlikely to look like that in Fig. 4, it is only shown in this way for clarity. The coax output socket used was of the insulated type and so a chassis connection has to be made to it; more conventional types will not need this.

It is very important that a good quality valveholder is used. Initially the author used rather a poor one and this later had to be replaced. The frequent plugging and unplugging of the coils demands a first rate quality component here.

The pointer can be made from any thin rigid clear plastic; the dimensions for this are given in Fig. 5a. A score mark should be made centrally on the underside, this can be inked in to make it clearer.

The component board is fixed to the chassis by


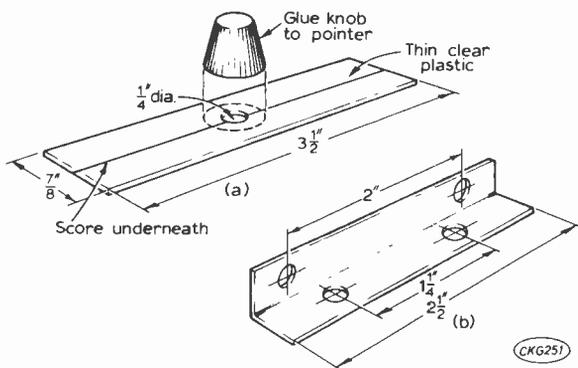


Fig. 5: (a) The construction of the frequency pointer. (b) The mounting bracket for the a.f. section component board.

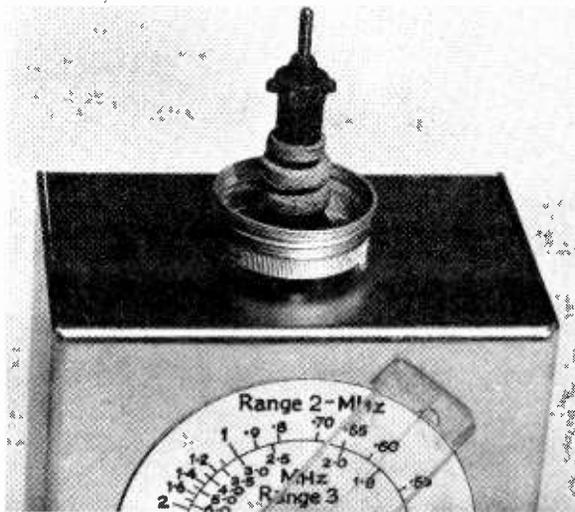means of an aluminium angle bracket as shown in Fig. 5b.



The screening can lid should be fixed on top of the valve base, ensuring that there is an electrical connection.

The main case is a  $5 \times 4 \times 2\frac{1}{2}$  in. chassis—this is a fairly common size and the drilling of the face is shown in Fig. 6. The only part of this which may cause problems is the mounting of VC1; the dimensions of these holes and their siting are rather critical. It is best to first drill a  $\frac{1}{2}$  in. diameter hole, this will then accommodate the raised section around the ball race. The capacitor itself can then be used as a template for finding the exact locations of the two mounting screw holes. Very short screws must be used to mount this component, if they are too long they will foul the moving vanes of the capacitor.

The valveholder is mounted centrally on the top


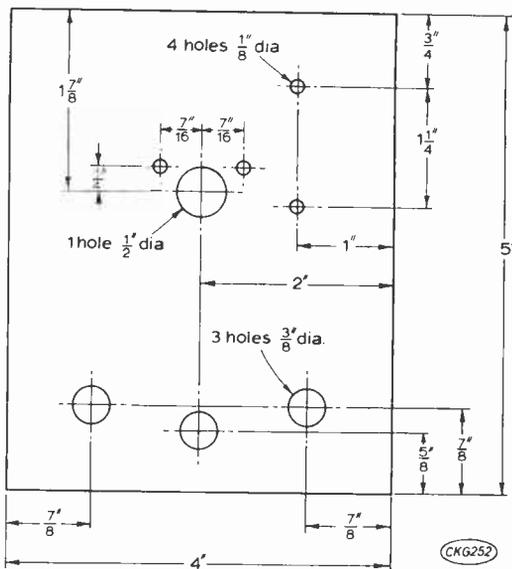


Fig. 6: The drilling details of the chassis face.

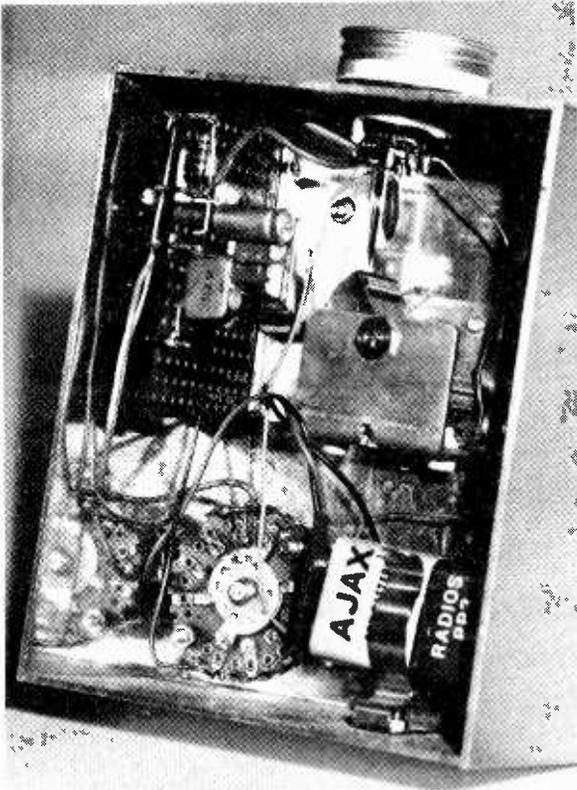

Rear view of the completed prototype.

Easily received MW/LW Radio Stations that can be used for calibration. Extra points can be found by interpolation

Range 1		Range 2	
Frequency	Station	Frequency	Station
151	Deutschlandfunk	529	Algeria
180	Europe No. 1	602	France
200	BBC Radio 2	647	BBC Radio 3
233	Luxembourg	701	Andorra
245	Denmark	746	Hilversum 1
		800	W. Germany
		908	BBC Radio 4
		1007	Hilversum 2
		1106	AFN Munich
		1196	VOA Munich
		1295	BBC European Service
		1403	France
		1502	Warsaw (Often English in late evenings)
		1594	BBC Radio Leicester

should be turned down as low as possible to prevent pulling in the receiver.

The receiver should be tuned to the German *Deutschlandfunk* programme on 151kHz—this is usually well received throughout Europe. With the vanes of VC1 fully closed and the pointer lined up with the end of the scale the core of the coil should be adjusted till the a.f. note, combined with a beat note, is heard. When this is done, tune VC1 to a point where the vanes are almost completely open. If the receiver is a superhet with an i.f. of 465kHz (or 455kHz for many imported sets) another note will be heard. Unlike the 151kHz point this note will be heard from the receiver irrespective of the band or frequency (though not on v.h.f.) the receiver is tuned to. When this point is found it should be

of the case; no problems are likely to be associated with this and so dimensions are not given.

Battery mounting is often a problem; it has been solved in this case by using a Terry clip which grips the PP3 battery; this is fitted behind the level control.

To have control over the output level, the coil should be screened; if it is not it will radiate considerable power. The screening can be supplied with the coils may be used for this. A  $\frac{3}{4}$ in. diameter hole should be cut in the lid and this glued over the valve base at the same time ensuring that there is an electrical connection to chassis. A hole should also be drilled in the top of the can to provide access to the coil core adjusting screw.

## CALIBRATION

Articles on r.f. signal generators frequently make a lot of calibration, this however need present no problems if you have available an all-band radio. Radio stations maintain very accurate frequency control and by beating the r.f. of our signal generator with their carriers, we can obtain very accurate calibration.

A blank calibration panel is given in Fig. 7. This can be cut out and stuck onto the face of the case or copied.

It is best to calibrate the long wave band (range 1) first as this will also give us our i.f. frequency. Assuming that all is well with the circuit and wiring, when the range 1 coil is plugged in and the function switch is set to MOD, the output should be tuneable over the long wave band and this will be heard on a radio. A wire should be connected to the inner of the coax socket and placed near the radio, the level

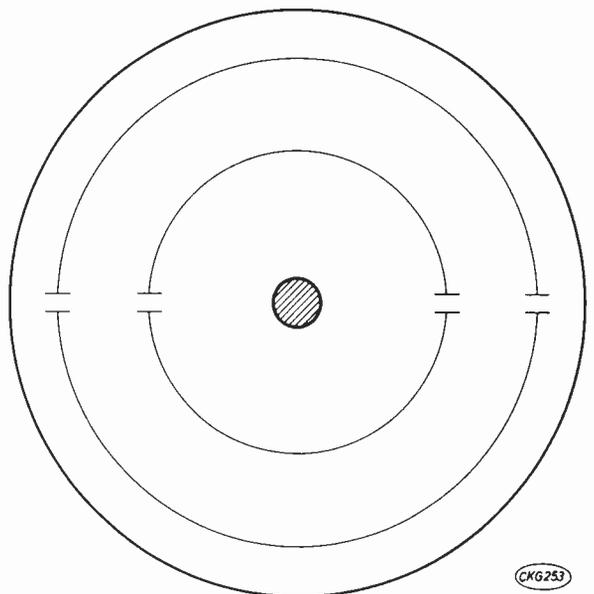


Fig. 7: This basic scale may be cut out and calibrated as described in the text.

carefully marked as this is the i.f. If possible, two positions should be marked, one for 455kHz and another for 465kHz.

Range 2 should be adjusted in a slightly different way. If we adjusted the core of the coil to operate on, say, 529kHz (*Algeria*), the high frequency end of the medium wave band would be badly cramped as this point would be reached before the vanes of VC1 reached their "extra spread" setting. For best results the core should be adjusted so that at a frequency of about 700kHz coincides with the vanes half open (pointer vertical). *Andorra* on 701kHz can be used for this. The range should then extend from 500kHz to over 2MHz, encompassing the complete medium wave band and the 1.6MHz i.f.

Range 3 should be adjusted so 1.6MHz coincides with the vanes fully closed. This range should then go up to about 6MHz.

The harmonics of range 3 can be used to give coverage of up to 30MHz though these are of less use and will be of lower level.


Various low level whistles may be heard on the wrong frequencies—these can be due to harmonics or receiver action but they should always be at a low level and there should never be any real doubt about determining the fundamental, it will be by far the strongest.

A table of useful stations for helping in the calibration are given; for a more complete list, reference books such as the "Guide to Broadcasting Station" or "World Radio TV Handbook" should be consulted.


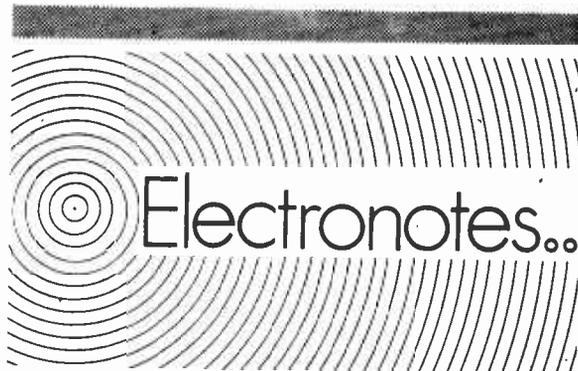
#### ISSUES WANTED

- ...P.W. January 1971, Feb. to Dec. 1971 (inclusive) and Jan. 1972.—G. A. Hunt, 38 Garrick Close, Ings Road, Hull, Yorkshire.
- ...P.W. Oct., Nov., Dec. 1971.—Alan Ward, 3 Cressbrook Avenue, North Wingfield, Nr. Chesterfield, Derbyshire, S42 5NL.
- ...P.W. March 1968 and June 1968 with items on "Clubman" receiver. Also required information on Lafayette HE 40 radio, including circuit diagram. Willing to loan or buy.—B. S. Smith, "Barnston", 58 Blackburn Road, Rishton, Blackburn, Lancs.
- ...Beginner requires any back numbers of P.W. and P.T. particularly P.T. June/July 1970, June/July 1966.—L. Cooke, 21 St. Anthony's Road, Bournemouth, Hants.
- ...P.E. April 1970, for any information as to power supply for the 50+50 watt amplifier featured in that issue. Urgent.—P. Elliott, 4 Rowlands Avenue, Upton, Pontefract, Yorks.
- ...P.W. for Jan. and Feb. 1971 containing details of Stereo tape recorder construction.—M. Scott, 13 Upper Montagu St., London, W1H 1RR.
- ...P.E. Feb. 1968 containing I.C. tape recorder.—D. Hollis, 15 Merlin Close, Collier Row, Romford, Essex.
- ...Wanted P.W. October 1971 and April 1972. Postage and cost refunded.—K. Foster, 148 Malmesbury Road, Shirley, Southampton, SO1 5EY.
- ...Feb. and March issues of 1971 containing the P.W. Stereo Tape Recorder.—D. J. Thomas, 16 Western Road, Urnston, Lancs. M31 3LF.
- ...April and May 1960 copies of P.W. and any information on 19 set Mk. III.—T. Izard, 41 Clumber Drive, Radcliff-on-Trent, Notts.
- ...P.T. Feb. 1966.—J. S. Fairrie, 5 Douglaston Crescent, Milingavie, Glasgow, Scotland.
- ...P.W. Jan. 1972 and Feb. 1972 issues.—C. W. Lo, 183 Lodge Avenue, Dagenham, Essex.
- ...P.W. Feb. to June 1967 and Aug. to Dec. 1970. P.E. Volumes 4, 5, 6 and Feb. 1971, All in very clean condition for binding.—E. Somerville, 2 Hillcrest Place, Killwinning, Ayrshire.
- ...Popular Hi-fi April, June and October 1971.—R. S. Wood, Preston Secondary School, Monks Dale, Yeovil, Somerset.
- ...wanted P.W. Feb. 1972.—P. Ducker, 50 Cheshire Road, Leicester.
- ...P.W. Oct. 1971 to Feb. 1972 Transistor Circuitry for beginners required by.—David John Cullen, 7 O'Neill St., Clonmel, County Tipperary, Ireland.
- ...April 1968 issue of P.W.—C. Saylis, 60 Hardens Mead, Chippenham, Wilts.
- ...P.W. May and June 1971.—A. Duffy, 52 Glenbervie Drive, Whitehurst Park, Killwinning, Ayrshire, KA13 6QH.
- ...Jan. 1972 issue of P.W.—S. Bouma, Wild Hoeflaan 31, The Hague, Netherlands.
- ...April 1970, May 1970 and June 1970 P.W.—J. Slim, 1 Whitehall Road, Smethwick, Warley, Worcestershire.
- ...P.W. Feb. 1972.—G. Burns, 31 Beechwood Drive, Eaton, Congleton, Cheshire, CW12 2NQ.
- ...P.W. Jan. 1972 and Feb. 1972.—B. A. Colton, 15A, Thomas King House, Wellington St., Coventry.
- ...P.W. Aug. 1969 to September 1971 inclusive. Price please to.—P.O. Rox 341, Hastings, New Zealand (Airmail).
- ...P.W. Feb. 1972.—P. Parker, 31 Fair View, Handsacre, Rugeley, Staffs, WS15 4DJ.
- ...April 1966 P.W. including '19' Set Mods. Article.—A. C. Arthur, Pinkworthy Farm, Pyworthy, Holsworthy, Devon, EX22 6AQ.



S. GINSBERG

THE art of sonar is not quite as simple as it sounds. In radar, an electromagnetic wave is transmitted in bursts and the energy from these which is reflected by surrounding objects is viewed on a cathode ray tube. Different objects cause different amounts of reflection and thus cause a pattern to be set up.

Sonar does the same sort of thing but with two major differences. First, it uses sound waves instead of radio waves. Secondly, it functions under water, the classic application being in ships.

Basically, sonar sounds simple until one considers it in greater depth—so to speak! A moving target generates acoustic energy, a form of noise, which can be detected. Thus no generated pulses would be needed in this passive mode. Perhaps, already I have stimulated anglers into thoughts of being able to actually "see" the big ones or shoals? Incidentally, professional systems do exist which can detect a single cod at 600ft!

In the case of sonar, the speed of data collection is limited mainly by the velocity of the propagation of acoustic energy through the water. In sea water, this is about 1,500 metres/second. Although this may sound (sorry!) fast, compare it with electromagnetic energy which has a velocity of propagation of some  $3 \times 10^8$  metres/second. Thus radar would take only 1/1,000th. of a second to receive a reflection from a target nearly 100 miles away. For sonar, it would take something in the order of four seconds for a target about 3,200 yards away—barely two miles.

Like its r.f. counterpart, sonar has problems with noise. The surface of the sea is in a continual state of variation due to the weather. Marine organisms cause noise, so does seabed turbulence.

At u.h.f., microwave energy in the earth's atmosphere travels in a straight line tending to follow the curvature of the terrain. Unhappily, sonar's acoustic energy is very reluctant to follow any straight line in sea water.

To complicate matters further, water temperature has an affect. In the sea, there is a temperature gradient. One "layer" of water is a little warmer than the next one down which in turn is a different temperature to the one immediately below it. It is not until nearly a mile down that an almost constant temperature is reached.

It is interesting that the velocity of acoustic energy varies dependant upon the temperature, pressure, salinity etc. Thus the acoustic waves are bent or diffracted (like light waves in water and glass) the amount of diffraction depending upon

—continued on page 641

# practically wireless commentary by HENRY

No. 93  
Do you  
read me?

SOME while ago, Henry had the uncomfortable pleasure working beside a pedantic colleague who corrected every casual remark as if invested with the guardianship of the English language.

A favourite dampener was: in answer to a query, "What does the meter say?" "The meter doesn't. You have to read it!"

Recent forays into the world of instrumentation have convinced this traveller that we shall soon render Old Niggly out of date. We have lately been promised computer type voltmeters that will store a measurement and notify a comparison. A sort of digital poor cousin of the storage 'scope. It is but a small step to the meter that will shout: "Hey! Give over" when overloaded, or a prim: "Three-point-seven millivolts" at the appropriate moment. With, of course, a built-in recorder (opto-magnetic; I mean to invent it) so that Old Niggly cannot dispute the matter, though he is sure to contest the manner of its delivery.

Avid and persistent collectors of Henribilia will by now have gathered that the subject of digital read-out devices for the ordinary radio workshop occupies the upper layer of the author's



The meter that will shout "Hey! Give over!"

(for want of a better word) mind.

It is true. I have recently come into proud possession of a digital multimeter.

Quite apart from a phenomenal accuracy, better than the thickness of a conventional pointer on the lowest voltage or highest resistance scale, the Digivom has the advantage of push-button range selection, and a read-out large enough to satisfy the most myopic niggler.

Mind you, it is not all plain sailing. There are one or two disadvantages the brochure omitted to mention. One is the tendency the Digivom has of sending out its own identifying signal—a series of chopped pulses that render its use as a measuring instrument for delicate audio (and some radio) purposes, about as valid as a Bobby Fischer unpaid checkmate.

The darned thing radiates all through the workshop. And if you enclose it in a tin box, leaving only the display tubes glowing through their visor like the Red Knight's menace, it still manages to jigger the f.m. band on the next-door engineer's rush job.

At the moment, I have a Solartron rival which uses diode display devices and these radiate only a mild hash, presumably there is hope for we humble servicemen yet. Except that this one has a read-out much smaller and of a style which, like the numbers my friendly, neighbourhood bank manager scrawls along the bottom of my cheques, defies analysis except by logical devices.

It is fascinating to watch the digivoms trundling down through the voltages when one reads off the h.t. line. Almost like a Cape Kennedy transmission!

Henry was happy with his push-buttons till Old Niggly sowed the seed of doubt in his mind. "Why not", he said, "do away with the push-button range selection?" After all, if you can read-off an overload indication and produce



Throw one or two in the makers' faces.

a flashing light, and do a similar service for the wrong d.c. polarity, why not build in a trigger circuit fed from a sensing device so that the meter must always switch itself to a range appropriate to the voltage applied to its terminals?

Well, why not? I asked an electronics designer whose name you will have seen if you read the glossier audio journals or works on instrumentation. He said calmly: "It has been done," and quoted me one of his own patents.


Now Henry doesn't pretend to be a designer or an inventor, and his only claim to-innovatory fame is a range of hook-up switch-boxes. But, fired by the ambition engendered by necessity—and not a little niggled by chagrin at spending over a hundred quid on a digivom before discovering its drawbacks—he has sworn to throw one or two modifications in the makers' faces before the year is out. Watch this space for details. . . .

The modifications will not, true, confound Old Niggly by making the machine shout its readings to all and sundry. I cannot hope to incorporate storage facilities. But the least that can be done for an instrument that boasts only one current scale, and that the "basic one", is a switched range of external shunts. That should not be beyond Henry's abilities—when he gets five minutes to spare.



"Where can I get exclusive units at lowest prices?..."

# ROC ELECTRONICS!

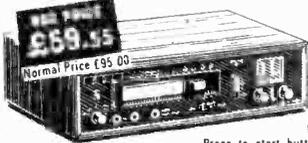

### 8-TRACK STEREO CARTRIDGE TAPE DECK MODEL RP-1000ST

The popular Lear-Jet type recording unit is the heart of the fantastic RP-1000ST, which has full record and playback facilities. Automatic track change with manual over-ride.

Press to start button. Stereo headphone and Left and Right Mic sockets on front panel. Dual recording level meter, and Left and Right volume controls. Built-in pre-amp. Tape speed 3 1/2 ips (9.5 cms). Frequency response: playback 30-10,000 Hz, recording/playback 30-8,000 Hz. Line output: fully variable 0-500mV. The RP-1000ST incorporates all the features you'd expect on a top quality Cartridge Tape Deck. Size 16" wide, 4" high, 9" deep. Cabinet in walnut. Including connecting leads.



### A-3000 36-WATT SOLID STATE STEREO AMPLIFIER

The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front—all the controls you're ever likely to need plus a headphone socket. On the rear—signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (± 2db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux, Tape Play. Size: 345mm x 300mm x 130mm.



**ROC PRICE £10.50**  
Normal Price £15.70

**DLSON AM-357 4-WATT STEREO AMPLIFIER**  
Here's a marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz ± 3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV; tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.

### REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted—for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push button input controls—magnetic phono (high/low) tuner, aux, mono, monitor Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz ± 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono—50db, tuner/aux—65db. How's that for a specification! Size 14 1/2" wide, 3 1/2" high, 10 1/2" deep.



As reviewed in "POPULAR HI-FI" February 1972

**ROC PRICE £35.20**  
Normal Price £55.50



### DLSON RA-310 AM/FM/MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as its good looking design! But of course it's also ideal for use with any other amplifier. The RA-310 costs £10.00 less than the normal retail value and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM 87-108 MHz, AM: 525-1605 kHz. FM Sensitivities: FM 3µV, AM, 250µV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size: 11 1/2" wide, 4" high, 7 1/2" deep.

**ROC PRICE £31.20**  
Normal Price £50.00



### REALISTIC SA-100B 6-WATT STEREO AMPLIFIER

Here's a fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide x 3" high x 5 1/2" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/tuner and power on/off slide switches. The ends are oiled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz ± 3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.

**ROC PRICE £12.45**  
Normal Price £21.00

**EAGLE LC.05 STEREO MAGNETIC CARTRIDGE**  
For fabulous reproduction at a very low price you'll find it hard to beat. 0.7 mil diamond stylus. Output: 6mV per channel. Frequency range: 30-18,000 Hz. Channel balance: +1-5dB. Channel separation: 20dB. Recommended stylus pressure: 2.4 grams. Compliance: 9 x 10-6 cm/dyne. **ROC PRICE £4.75**

**EAGLE LC.07 STEREO MDVING-MAGNET CARTRIDGE**  
Here's your opportunity to own a transcription cartridge for the price of a ceramic! It is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: -1dB. Channel separation: 28dB. Compliance: 12 x 10-6 cm/dyne. **ROC PRICE £6.37**



### OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3.0mV RIAA, crystal phono 100mV, tape 160mV; tuner 160mV. Size 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well—sounds even better!

**ROC PRICE £24.10**  
Normal Price £39.50

## CONSTRUCTORS KITS

**CRYSTAL RADIO KIT**  
Complete with earpiece **£1.50**

**TWO TRANSISTOR RADIO KIT**  
Complete with solar cell **£2.50**

**10 PROJECT INTEGRATED CIRCUIT KIT**  
Build a radio, Morse key etc. **£3.50**

**SOLAR ELECTRONIC KIT**  
20 ways of harnessing the sun's energy **£4.50**

**TWO OCTAVE ELECTRONIC ORGAN KIT**  
Make your own music. Complete with speaker. **£4.50**


**LIMITED STOCKS BUY NOW FOR XMAS!**


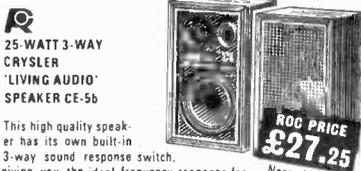
### R.4463 3-WAY MATCHED SPEAKERS

These will do justice to your amplifier—and to your pocket. At only £16.40 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a large dual cone base unit, plus a separate tweeter. Frequency range: 40 to 19,000 Hz. Size 14" high, 9" wide, 6 1/2" deep.

**ROC PRICE £17.80**  
Normal Price £25.00 per pair.




### 25-WATT 3-WAY CRYSLER 'LIVING AUDIO' SPEAKER CE-5b

This high quality speaker has its own built-in 3-way sound response switch. Giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units an 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s. into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2" x 7 1/2" x 8 1/2". Exactly right for matching the most modern decor.


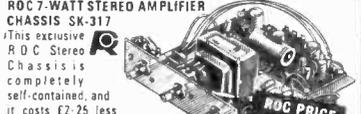
### PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16


This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received—that's the time to switch to 'Stereo'! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much—separate volume, bass, treble, balance and tuning controls. Selector switch for stereo, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz, AM 535-1605 kHz. Frequency response: 50-10,000 Hz ± 3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.



### ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317

This exclusive R O C Stereo Chassis is completely self-contained, and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 1 1/2" high and 6 1/2" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz ± 3dB; output 3.5 watts music power per channel into 8 ohms; input, phono, 600mV; signal-to-noise ratio better than 45dB.

**ROC PRICE £5.50**  
Normal Price £7.75

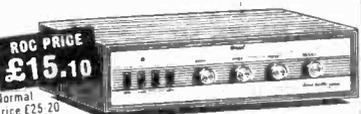

### OLSON AM-372 16-WATT STEREO AMPLIFIER


Here's a really good amplifier at a really down-to-earth price—nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you—reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3dB. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

**ROC PRICE £15.10**  
Normal Price £25.20
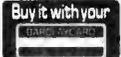
## ROC ELECTRONICS LTD

M. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211  
CALLERS WELCOME 9-6 MON. TO SAT.

ALSO AT 87 TOTTENHAM COURT RD. LONDON W1  
TEL: 01-580 3739 OPEN 9-6 MON.—FRI. SAT. 9-1



Return-of-post mail order service. Orders over £10 post free (UK only). Add 25p for p & p to orders under £10. HP terms available for callers

# ATTRACTIVE DISCOUNTS ON MANY ITEMS

# ELECTROVALUE Electronic Component Specialists

## TRANSISTORS

Brand new—no seconds or surplus. Highest quality and reliability. Insulating sets FREE with power types.

MANY HUNDREDS OF DIFFERENT TYPES IN STOCK—THEY'RE ALL IN OUR NEWEST CATALOGUE

1N4148	4p	AF139	33p
1N5399	24p	AF239	36p
2N2646	37p	BC107	13p
2N3055	85p	BC109	14p
2N3702	10p	BC148	9p
2N3703	10p	BC177	15p
2N3704	10p	BC184L	11p
2N3819	25p	BC212L	14p
2N4286	15p	BD130	65p
2N4289	15p	BD131	77p
2N4443	85p	BD132	81p
2N5082	42p	BD136	25p
2N5088	48p	BD136	27p
2N5192	77p	BDY20	97p
2N6195	90p	BFY51	20p
2N5457	30p	BFY39	80p
40361	45p	BY164	45p
40362	45p	MJ481	120p
40432	178p	MJ49	135p
40612	180p	MJ30	68p
40669	180p	OA91	6p
AC128	21p	OC35	63p
AD142	50p	OC35	12p
AD149	68p	82CN	12p
AD16	42p	82CN	9p
AD182	40p	82CN	9p

TO3 Transistor Covers, ea. 7p

## RESISTORS 10% — 5% — 2%

Code	Power	Tolerance	Range in ohms	Values 1 to 9	10 to 99	100 up
C	1/8W	5%	4.7-470K	E24	1	0-8
C	1/4W	10%	4.7-10M	E12	1	0-8
C	1/2W	5%	4.7-10M	E24	1-2	0-9
C	1W	5%	4.7-10M	E12	2-5	1-9
MO	1/2W	2%	10-1M	E24	4	3
WW	1W	10%	0.22-3.9	E12	7	7
WW	3W	5%	1Ω-10K	E12	7	7
WW	7W	5%	1Ω-10K	E12	7	8

Codes: C—carbon film high stability low noise  
MO—metal oxide Electroslit TR5 ultra low noise  
WW—wire wound Pleasay

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 72, 91 and their decades. Prices are in pence each for some ohmic value and power rating, NOT mixed values. (Ignores fractions of 1p on total value of resistor order).

## BAXANDALL SPEAKER

As designed by P. J. Baxandall and originally described in "Wireless World". Complete kit inc. speaker, equaliser and special cabinet kit (18" x 12" x 10") cut to size. 10 watt RMS/16Ω loading. Part cost of £13.81 carr. and ins. in U.K. 60p

Speaker unit and equaliser kit post free nett £4.81. Pack flat cabinet assembly (all cut to shape) natural teak finish £9.00 nett. Part cost of carr. in U.K. 60p.

**CARBON SKELETON PRE-SETS**  
Small high quality, type PB linear only: 100Ω, 220Ω, 470Ω, 1K, 2K, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10MΩ. Vertical or horizontal mounting, 5p each.


**ZENER DIODES** 5% full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 76V, 48p each.  
CUp to increase 1.5W rating to 3 watts (type 266P) 4p.

**MINIATURE TOGGLE SWITCHES**  
2A/250V. DP/DT, 48p.

**MAINLINE AMPLIFIER KITS**  
70 watt power amp. module kit, £12.60 nett. Power supply kit, £6.50 nett.

**SIEMENS THYRISTORS**  
0.8A—400V 56p; 600V 80p. 3A—400V 70p; 600V 85p.

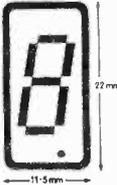**Q.E.D.** High quality amplifier systems. Built to your personal specifications. Enquiries invited. Please quote P.W.8.



## MINITRON DIGITAL INDICATOR

TYPE 3015F Seven segment indicator compatible with standard logic modules and power supplies. Figs. 0-9 from well illuminated filament segments to give character of 9mm height plus decimal point. Power requirement 8mA from 5V D.C. per segment. A limited number of alphabetical symbols also available. In 16 lead DIL case


£2.00  
£1.36

Suitable BCD driver type FLL121T nett.  
DIL Socket: 16 lead 30p.  
No. 3015G showing + or - and fig. 1 and decimal point £2.00.

## PRECISION COMPONENTS

Resistors by Rivlin 0.1% to 0.01%, £1-42.  
Capacitors by MFD 0.01μF-22μF 1% 70p to £1.

## SLIDE POTENTIOMETERS

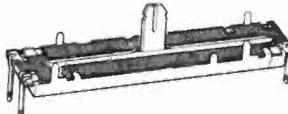

Robust construction, smooth silent action. In values from 4K7 to 1 megohm, linear or log, each 26p. Light grey escutcheon, 10p. Knobs flat, grip type in black/Red/Green/Yellow/Blue/Light Grey/Dark Grey or White each 5p.

## We are appointed stockists for SOLDERSTAT SOLDER IRONS

As appointed distributors for well-known Eremco-Wolf "Soldostat" irons we offer this light weight model HMS in 16 or 24 watt, ratings 220/240V a.c. £1.87 nett.

## INFINITELY VARIABLE TEMPERATURE CONTROLLED SOLDER IRON

complete with temperature setting control, nett £9.20

## DE-SOLDER BRAID 50p

## NIPPIBOARD multipurpose component

mounting boards in various working area combinations. 1A one pattern on one board 15p. 2A 2 patterns side by side 28p. 2AS dual channel 28p. 3A 3 patterns alongside 38p. 4AS dual channel 2 above, 2 below 44p. In full range up to 10A.

TYGAN 36" x 27" £1.68, 18" x 27" 85p.  
VYNAIR 36" x 25" 98p. 15" x 25" 56p.  
(Pattern Book 3p & S.A.E.)

## SIEMENS TTL I.Cs

Prices quoted here are nett.

FLH101 (7400)	80p	FLJ121 (7473)	45p
FLH101 (7401)	20p	FLJ141 (7474)	45p
FLH201 (7402)	20p	FLJ151 (7475)	45p
FLH301 (7403)	20p	FLJ131 (7476)	45p
FLH211 (7404)	25p	FLH211 (7480)	68p
FLH271 (7405)	25p	FLH231 (7482)	87p
FLH381 (7406)	25p	FLH241 (7483)	132p
FLH391 (7408)	25p	FLH311 (7485)	33p
FLH101 (7410)	20p	FLJ161 (7490)	80p
FLH351 (7413)	35p	FLJ221 (7491)	AN
FLH121 (7420)	20p	AN	1.28
FLH131 (7430)	20p	FLJ171 (7492)	85p
FLH141 (7440)	24p	FLJ181 (7493)	80p
FLH101 (7414)	1.22	FLJ231 (7494)	1.13
FLH281 (7442)	1.18	FLJ191 (7495)	87p
FLH361 (7443)	1.45	FLJ261 (7496)	1.48
FLH371 (7444)	1.45	FLJ301 (74100)	1.64
FLH161 (7450)	20p	FLJ281 (74104)	48p
FLH161 (7451)	20p	FLJ271 (74107)	52p
FLH171 (7453)	20p	PLK101 (74121)	48p
FLH181 (7454)	20p	PLJ201 (74130)	1.80
FLH191 (7456)	20p	PLJ211 (74131)	1.80
FLJ101 (7470)	45p	PLJ241 (74191)	1.80
FLJ101 (7471)	45p	PLJ241 (74192)	1.74
FLJ111 (7472)	32p	FLJ251 (74193)	1.74

## NEWMARKET LINEAR I.Cs

LIC 7060/14 Dual in line—34p 709C/5, TO6 39p  
LIC 741C/14 Dual in line—40p 741C/5, TO3 42p

## CARBON TRACK POTENTIOMETERS

long spindles. Double wipers for low noise. SINGLE GANG P.20 lin. 100Ω to 2.2MΩ, 12p; Single gang log, 4.7kΩ to 2.2MΩ, 12p; Dual gang linear 4.7kΩ to 2.2MΩ, 42p; Dual gang log, 4.7kΩ to 2.2MΩ, 42p; Log/antilog, 10K, 22K, 47K, 1MΩ only 42p. Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra. Only decades of 10, 22 & 47 available in ranges quoted. DUAL CONCENTRIC in any combination of P.20 values as above, 60p, with switch, 72p. Knobs, pair 24p

## DISCOUNTS

10% on orders £5 to £15.  
15% on orders over £15. No discount on items marked Nett. Prices subject to alteration without notice.

## POSTAGE AND PACKING

FREE unless otherwise stated. Handling surcharge 10p on mail orders under £2.  
Overseas orders: carr. & Insurance charged at cost. U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.

ENQUIRIES FROM TRADE AND OTHER LARGE QUANTITY USERS INVITED.

## SIEMENS CAPACITORS

### POLYCARBONATE—5% TOLERANCE

250V. up to 0.1μF; 100V/0.1μF and above  
0-01; 0-012; 0-015; 0-018; 0-022; 0-027; 0-033; 0-047; 0-056 each 4p  
0-063; 0-082; 0-1; 0-12; 0-15 each 4p.  
0-18; 0-22; each 5p.  
0-27; 0-33; 6p; 0-397p; 0-478p; 0-5610p; 0-6311p; 1μF 13p.

### ELECTROLYTIC (values in μF/V)

0-47/100; 1/100; 2/63; 4/33; 4/7/35; 10/25; 22/16; 47/10; 47/25; 100/10; 22/3—each 7p.  
10/63; 22/35; 47/35; 100/16; 100/25; 220/5; 220/10; 220/16; 470/3 each 7p.  
47/50; 47/63; 100/35; 220/16 each 8p.  
100/50; 220/35; each 10p; 100/63; 470/25; 1000/10 each 12p  
220/63; 470/35; 1000/16; each 17p.  
1000/25—20p; 470/63; 1000/35 each 23p. 2200/25—36p.  
1000/63; 2,200/35; 4,700/16—each 40p.  
Tantalum and other capacitors etc.—see latest 1972 Catalogue—Issue No. 6.

## 1972 ELECTROVALUE CATALOGUE (NO.6)

3rd printing 96 pages plus cover. More items, more information, more diagrams than ever. Latest price and information details. Post free in U.K.—10p.

(Dept. P.W. 11) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB  
Hours: 9—5.30: Sat. 1p.m. Tel.: Egham 3603 (STD 0784-3) Telex 264475  
ELECTROVALUE LTD—AN INDEPENDENT COMPANY SINCE ITS ESTABLISHMENT ORIGINALLY IN 1965

# ELECTROVALUE

# ON THE SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

IT IS a generally accepted axiom that good short-wave reception is 50 per cent dependent on the aerial, the other 50 per cent accounts for the receiver and skill of the operator etc. I know many people who have bought expensive receivers and been disappointed with the results simply because they did not have an effective aerial system.

The simplest form of aerial is the long wire, and the longer the wire is the better the reception will be. The strength of the signal is measured in microvolts per metre; the longer the aerial is, the stronger the signal will be because the voltage induced in the aerial will be higher. All receivers have a certain sensitivity which is a measure of the voltage required at the aerial input to give a useful audio output.

A long-wire aerial of 50 feet will usually give adequate reception whilst one of 100 feet is very good. Other factors affect the performance of such an aerial, consequently the higher above ground it is the better it will perform. Care should also be taken to keep the aerial as far away as possible from buildings, trees and any other obstructions which may reduce the signal induced. It is also essential to keep the aerial as remote as possible from any sources of man-made interference.

A better type of aerial is the dipole. This type of aerial is restricted in use because it can only be tuned to a single band. The advantage of a dipole, however, is that being tuned its performance on the band of interest is superior to that of a long-wire.

The dipole aerial consists of a single length of wire which is cut in half, the two halves are connected via a coaxial cable to the two terminals at the rear of the receiver. The overall lengths for the various Broadcast Bands are as follows:

Frequency Band	Length of aerial
25 MHz.	5.60 metres
21 MHz.	6.65 metres
17 MHz.	8.00 metres
15 MHz.	9.30 metres
11 MHz.	12.10 metres
9 MHz.	14.80 metres
7 MHz.	20.00 metres
6 MHz.	23.40 metres

For the benefit of those who have not been converted to the metric system one metre is approximately equal to 3.28 feet (e.g. 20.00 metres = 65.6 feet).

An interesting feature of the dipole is that it is a directional aerial. If the wire is aligned North-South the best reception will be from due East and due West.

It is possible to use a dipole on all bands but without the same sensitivity as the band to which it

## THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

is tuned. For example a 7MHz. dipole will be a sensitive, directional aerial on the band of interest. but on all other bands it will perform as a non-directional, 66 foot long-wire.

Most listeners have one band in which they are particularly interested, the ideal solution in this case would be to erect a dipole for this band and a long-wire for general listening on the other bands.

The first report this month comes from **Michael Berry** in Dewsbury, Yorkshire. Michael is still using his Eddystone EB35 receiver but has replaced his vertical aerial with a 20 foot long-wire in the loft. The stations logged included:

- 3960 *Baghdad, Iraq* in Arabic at 2310.
- 4800 *R. Lara, Venezuela* in Spanish at 0240.
- 4820 *Voz Evangelica, Honduras*, English at 0340.
- 4880 *R. Universo, Venezuela*, Spanish at 0330.
- 4990 *R. Barquisimeto, Venezuela* at 0230.
- 4995 *R. Brazil Central* in Portuguese at 0110.
- 5075 *R. Sutatenza, Columbia* at 0100.

**Richard Keen** of Hayes in Middlesex has just erected a long-wire of 120 feet which enabled him to hear:

- 4790 *R. Ondas Portenas, Venezuela* at 2055.
- 9510 *R. Barquisimeto, Venezuela* at 2015.
- 9595 *R. Cultura de Bahia, Brazil* at 2025.
- 9965 *R. Lisbon, Portugal* in English at 2050.
- 11875 *R. Nacional de Nicaragua*, Spanish at 2010.
- 12550 *R. Nacional, Tanganyika* at 2100.

**John Adams** of Sheffield returns to the column after a long absence. John has an Eddystone EC10 receiver, a Codar PR30X preselector and a 72 foot long-wire. His log included:

- 9570 *Radio Australia* with music at 0710.
- 9625 *Kol Israel, English news* at 2035.
- 11620 *AIR, Delhi* with news in English at 2008.
- 11650 *R. Bangladesh* in English at 1715.
- 13220 *R. Euzkadi* in Basque at 2135.
- 15018 *Voice of Vietnam, Hanoi* at 2005.
- 21495 *R. Portugal* with DX News at 0800.

**Nigel Knowlman** of Cullompton in Devon has sent in another good log which includes:

- 9570 *Radio Australia* in English at 0830.
- 9912 *All India Radio* in English at 2000.
- 15105 *Radio Japan*, English news at 0945.
- 15165 *R. Denmark* in English and Danish at 1200.
- 17655 *Radio Cairo, 'Arabic by Radio'* at 1800.
- 21535 *RSA, South Africa*, English news at 1400.
- 21545 *Radio Ghana* in English at 1440.

Reports should arrive by the 15th of the month and be addressed to me at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

# SHORT WAVES

**F**IRST letter out of the postbag this month comes from **GW3ZSV**. He tells enthusiastically of an 80 metre contest to be run by the Sully & District Short Wave Club on October 22. First section from 0900-1100 and the second from 1700 to 1900. Great news—the contest is open to both licenced Amateurs and s.w.l.s so there's no excuse for not having a go. Rules are just about the simplest and easiest to follow that I've ever seen. Why not send GW3ZSV a s.a.e. and get all the gen? Address is 3 Thorley Close, Cyncoed, Cardiff, South Wales. For local s.w.l.s with no club at present, the Sully gang meet every Tuesday at 1930 at the Sully Bowls Social Club. Sully is about 6 miles from Cardiff on the coast road to Barry. They cater specially for the s.w.l., too.

Elated squeaks from **Bill Waldron** (Cwmbran) whose 144MHz score since April 1 this year has now topped 40 counties and six countries. Bill mentions the infuriating situation during a recent 2 metre opening when London and Midland stations could be heard calling LA, SM, ON, OZ, etc., but only the faintest of whispers and bits of EU callsigns detectable down in Wales. He also remarks on hearing many QSO's of, say, Dudley talking to Wolverhampton and other local natters. He again asks why these locals don't turn their beams round towards GW. Almost every night, GW3ZTH, GW3LEW and GW3TMM are active on the s.s.b. channel. How about it you northern types—or are those beams rusted in position from the habit of local gossips?

On 80 metres, Bill complains of high static levels but still managed to log some s.s.b. from: EL0H/MM, FP0BG, OA4AS, PY2RT, PY3CGP, VE3GCS, VO1GQ/M, VP7ND, VP9BK, WA2FCA, W4NJF, W8BT, 5Z4MO, 8P6SJ (Scout Jamboree station).

Pretty stamp and long epistle from **Victor Springer** (St. Lucy, Barbados) relates hair-raising tales of s.s.b. received on a receiver using battery valves and a 90V h.t. line. Modifications include items like half of a 12AU7 as an outboard tuneable b.f.o. whose signal is injected by winding a few turns of wire around the first DF96. (Transistor types will doubtless find all this way above their heads!). (No, a 12AU7 hasn't got a collector). Heard on 14MHz with the aid of 150ft of aluminium wire in an unspecified shape; CE3AJE, DJ1HP, DJ2WF, DJ8EG, F3OX, G3KTJ, G3XJN, G4OO, G6GA, GB3MKT, HB9KM, HC2JX, HK5ACP, I5MLI, JA1BRK, JA4YAR, OA4AEH, PY1AGO, VXVK2SG, VK3JW, VK9JW, XE1LAG, YK1AA, ZD3A, ZK2DX, 4Z4JX, 5V2AT, 5V4GE, 5V8AR, 7X7Y.

Chance to get yourself a nice QSL from the land of **GC. Ken, GC3GPL** (ex G3GPL) is now active on c.w. between 14·000MHz and 14·050MHz most evenings between 1900 and 2230 plus Sunday mornings. He has put up a special antenna which, he hopes, will give reliable short skip signals into the UK. He will QSL any s.w.l. who sends him a useful report on

## THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz ● Times in GMT

his signals. Address for those useful (note that word, not just a "Heard you 579 pse QSL) reports is Haut du Pre, Fern Valley, St. Helier, Jersey, Channel Isles.

**Patrick Funnell** (Nottingham) has an 8-element Yagi on two metres. This feeds a dual-gate m.o.s.f.e.t. converter which in turn feeds a PW Clubman receiver used as a tuneable i.f. covering from 2-4MHz. He comments that the Clubman is a very good receiver and includes a 2 metre log which mentions stations like; OZ1EP OZ4HW, PA0KOK, PA0LSG (using n.b.f.m.), PA0PMQ, PA0TLX (n.b.f.m.) plus numerous G stations. It is interesting to note the number of stations using narrow band frequency modulation (n.b.f.m.).

Log from the quill of **Alan Smith** (Lancs.) using a JR310, 60ft. long wire plus a E-ZEE Match a.t.u. He complains of "... a combination of night starvation and v.f.o. tuners cramp". (Wait till you get knob nippers gout, that's when we really separate the men from the boys). Alan's log for 14MHz reads; CE3AQW, CE3OE, CO8GL, CP1JV, EA8EN, EP2TW, FC9VN, FM7WN, FY7AE, HC4BS, HK6CBS, HP1XIS, MP4TDM, OA4LV, OA4WJ, OD5AU, OX3HV, OX3JW, PJ2CC, PJ9AD, PZ5CW, T12AS, VE1TB, VE7BNJ, VE8RCS, VK2QM, VK3DO, VK4CZ, VK5ID, VK6FD, VK7AK, VK0RC, VP2VAM, VP7MG, VS6DO, VU2ALU, VU2BX, XE1DO, XE1EH, XE3RE, ZL1VY, ZL2CB, ZL3JD, ZL4BC, ZM2ASJ, ZM4CR, 9K2AR, 8P6BC.


DX on ten metres is a GW, claims **Martin "Squiggle"** whose second name I can't decipher. (It's when your own g.d.o. is d.x. you start worrying!). Treasured possessions include a 640 receiver, a 20 metre dipole and a "flimsy bit of co-ax". Mr. Squiggle comments on the d.x. stations claimed by users of simple t.r.f. receivers, headphones made of draught excluders and coat-hanger aerials. He wonders if they use an SB303 receiver as a pre-amp and just forget to mention it. (Play fair lads, if you use a 30 transistor pre-amp, you gotta say).

A 9R59DE, 7MHz dipole and **B. Mainwaring** (Walsall) raised this lot on 21MHz; CE3OE, CP1HG, CR6CA, EA3VC, EA6BJ, EP2TC, JA1MTP, JA2MJ, JH1TMR, JH3ONP, OD5HF, OE6PN, PA0WF, PY1MT, SM4APD, 4Z4MO, 7X7Y. Interesting to note the European stations here (many haven't been included). Many s.w.l.s commented on the short skip conditions which prevailed this past month. Effects like G stations on 20 metres being 5 and 9 were common. Wonder what things will be like next month, and how do you think the bands will fare this coming Winter? How about a line airing your views?

Logs, in alphabetical order please to arrive by the 15th of the month to 12 Cross Way, Harpenden, Herts.

**SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT, PRESENT  
AN OUTSTANDING RANGE OF KITS FOR THE ELECTRONICS & AUDIO  
ENTHUSIAST ALIKE**

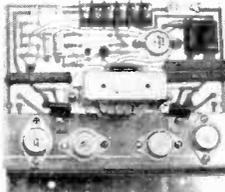**ALL OUTPUT POWER RATINGS ARE R.M.S. CONTINUOUS  
SINE WAVE:  $\pm 0.5$ dB USING SPECIFIED SUPPLY**



SIZE 6" x 6 1/2"

**POWER AMPLIFIER MODULES**

**TP 100W** 170W RMS sq. wave (illus-  
trated) 300W instantaneous peak into 8 $\Omega$   
**£14.28** Carr. 45p (60W into 16 $\Omega$ )

**TP 50W** 85W RMS sq. wave  
135W instantaneous peak into 8 $\Omega$   
**£9.31** Carr. 40p (45W into 16 $\Omega$ )

**TP 25W** 40W RMS sq. wave into 8 $\Omega$   
**£7.25** Carr. 40p (15W into 16 $\Omega$ )

Output matching transformer to match power modules to  
4-8-16-60-100 $\Omega$ . 110W. **£7.50** Carr. 45p.

**Brief Tech. Spec. for all 3  
modules.**

Full Power Response 10Hz-22kHz  
 $\pm 2$ dB. Input Sensitivity 30mV  
R.M.S. Output Impedance 8 and  
16 $\Omega$ . Hum and Noise better than  
-70dB. Supply Voltages and  
currents on full load.

TP 100W 46-0-46 V.D.C. 2.0A  
TP 50W 38-0-38 V.D.C. 1.5A  
TP 25W 40 V.D.C. 1.0A


All TUAC power modules are  
constructed on glass fibre P.C.  
board and each circuit incorpora-  
tes a robust driver transformer  
stage with full thermal overload  
protection on the output stage.  
Each unit is individually tested  
using the latest computer con-  
trolled techniques. External  
chassis type heat sink required.

**PRE AMP MODULES**

- 4 Control preamp (illus.) vol,  
treble, middle and bass controls.  
**£3.96** Carr. 25p
- 3 Control preamp vol, treble and  
bass controls. **£3.09** Carr. 25p
- 5 Control stereo pre-amp, as 4  
control + bal. **£7.75** Carr. 25p.

Brief Tech. Spec. for both preamps.  
Gain 10 times at 1kHz. 30dB varia-  
tion on each tone control. Frequency  
Response 10Hz-30kHz. Supply Vol-  
tage 40 V.D.C.  
Maximum output 2V R.M.S. at 1kHz.

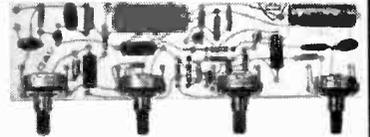These low priced high quality  
preamp modules are designed  
and built to suit most re-  
quirements using F.E.T. first  
stage and may be used to  
drive any amplifier.



**POWER SUPPLIES SUITABLE WITH ABOVE INCLUDING TRANSFORMERS**

PS 100 <b>£9.66p</b> Carr. 50p	PS 100/100 <b>£16.00</b> Carr. 65p	For use with 2 power modules, i.e. stereo.
PS 50 <b>£6.12p</b> Carr. 50p	PS 50/50 <b>£9.68</b> Carr. 65p	
PS 25 <b>£3.95p</b> Carr. 40p	PS 25/25 <b>£7.35</b> Carr. 55p	


Superb general purpose preamp suitable for tape  
p.u., guitar, etc. 9 V.D.C. supply upwards. Response  
10Hz-30kHz. Gain approx. 50 times. Application.  
Transistor or valve equipment. Size 2" x 2" x 1"  
only **£1** post 10p.

**SPECIAL REDUCTION**

**IF ANY 2 OR MORE UNITS ON THIS  
PAGE ARE PURCHASED TOGETHER,  
A REDUCTION OF 10% WILL BE GIVEN  
+ FREE CARR.**

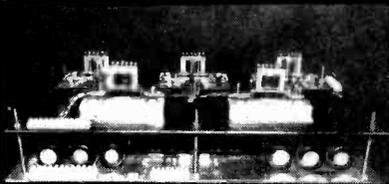**SPRING LINE REVERBERATION UNITS**

THIS HIGH QUALITY UNIT INCORPORATES THE 18" GIBBS 4C SPRING  
READY TO FIT ON TO ANY CHASSIS. 2 SEPARATE HIGH IMPEDANCE  
INPUT CHANNELS, WILL MATCH ANY SIGNAL: USEFUL FRE-  
QUENCY RESPONSE OF SPRING 80Hz-6kHz: DECAY TIME 2 SECS AT  
360Hz. STANDARD 240V MAINS OPERATION, BUILT IN POWER SUPPLY.  
**£17.50p** Carr. 40p.



SIZE 26" x 18" x 14"

CUSTOM 500W PREAMP



**READY ASSEMBLED POWER AMPLIFIER CHASSIS (MIXER/PREAMP AS  
ILLUS. PRICES ON REQUEST).**

These high power units are available in a variety of powers from  
100 to 1,000 watts, complete with power supply and ready wired for  
immediate use. Each complete amplifier is constructed in 100W  
"blocks" therefore allowing separate control over the input and  
output stages if necessary.

TC 100W	Chassis <b>£32.50</b> Carr. 70p
TC 200W	" <b>£45.00</b> Carr. 85p
TC 300W	" <b>£95.00</b> Carr. £1.00
TC 400W	" <b>£125.00</b> Carr. £1.15
TC 500W	" <b>£155.00</b> Carr. £1.25 (ILLUS.)

Prices above 500W given on application.

**TUAC AMPLIFICATION**

3 OF THE UNITS AVAILABLE FROM THE COMPREHENSIVE RANGE OF TUAC EQUIPMENT ARE ILLUSTRATED BELOW DESIGNED AS GENERAL  
PURPOSE AMPLIFIERS, SUITABLE FOR GUITAR, DISCO, PA, ORGAN, ETC, FOR USE WITH MOST SPEAKER SYSTEMS



**£55.00 CARR. £1.00**



**£37.50 CARR 50p**



**£45.00 CARR £1.00**

**EACH PIECE OF EQUIPMENT MANUFACTURED BY TUAC IS FULLY GUARANTEED FOR 12 MONTHS**

ALL TUAC KITS SUPPLIED WITH FULL  
EASY TO FOLLOW WIRING INSTRUCTIONS  
INCLUDING CIRCUIT DIAGRAM AND COM-  
PLETE COMPONENT COMPLEMENT

**TUAC**

TRADE ENQUIRIES WELCOME


S.A.E. WITH ALL ENQUIRIES. PLEASE  
CALL, WRITE OR PHONE FOR FULL  
DETAILS OF ABOVE AND OTHER PRO-  
DUCTS NOT LISTED

# POWERTRAN ELECTRONICS


Specialists in high quality kits for high quality audio equipment. Previously concentrating on advanced Wireless World designs (pre-amps, power amplifiers from 10 to 100 watts, power supplies, tape recorder) we now proudly add the Practical Wireless TEXAN to our range.
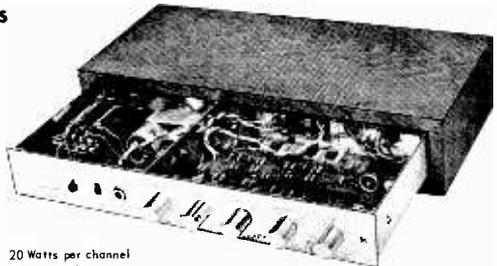
## APPOINTED DISTRIBUTORS FOR THE 'TEXAN'

TEXAS INSTRUMENTS DESIGNED  
& APPROVED FULL KIT



### SLIDER POTENTIOMETERS

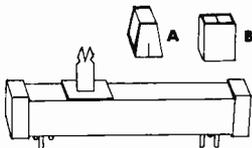

- Single: log or lin 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M **35p**
- Dual: log or lin 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M **55p**
- Balance: special dual track 10K Black/Chrome knob: type A or B **60p**
- 23mm CARBON POTENTIOMETERS**
- Single: lin 1K to 2M2 **12p**  
log 4K7 to 2M2 **12p**
- Dual: 10K or log 4K7 to 2M2 **35p**
- Balance: log or A log **40p**
- Balance: Purpose designed; better than Log./A Log. No attenuation at mid point. 22K only **45p**

2N4699	0.30	40361	0.40	MPS466	0.40
2N4813	0.20	40362	0.45	MPSH05	0.20
2N1711	0.25	BC107	0.08	MPSU05	0.60
2N2926G	0.10	BC108	0.08	MPSU55	0.70
2N3053	0.20	BC109	0.08	SN72741P	0.95
2N3055	0.45	BC125	0.15	SN72748P	0.95
2N344	1.20	BC126	0.15	THB11	1.10
2N3702	0.11	BC182K	0.10	TIP29A	0.50
2N3703	0.10	BC212K	0.12	TIP30A	0.60
2N3704	0.10	BC182L	0.10	TIP31A	0.60
2N3705	0.10	BC184L	0.11	TIP32A	0.70
2N3706	0.09	BC212L	0.12	TIP33A	1.00
2N3708	0.07	BC214L	0.14	TIP34A	1.50
2N3709	0.09	BF257	0.55	TIP41A	0.74
2N3710	0.09	BF259	0.60	TIP42A	0.90
2N3711	0.09	BFY29	0.30	TIP3055	0.60
2N3819	0.23	BFY50	0.20	1808 T20	0.50
2N3904	0.17	MJ481	1.20	1840K20	1.40
2N3906	0.20	MJ491	1.30	1N914	0.07
2N4058	0.12	MJ521	0.70	1N916	0.07
2N4062	0.11	MPSA05	0.30	1544	0.05
2N4302	0.60	MPSA12	0.55	15920	0.10
2N5457	0.30	MPSA14	0.35	153062	0.25
2N5830	0.30	MPSA55	0.35	5805	1.20
		MPSA65	0.35		

**£28.50** post (UK) 45p  
INCLUDES TEAK CASE

### SEMICONDUCTORS

20 Watts per channel  
6 integrated circuits  
10 Transistors  
HARMONIC DISTORTION  
0.05% at 15W 1KHz into 15 ohm  
0.09% at 20W 1KHz into 8 ohm  
FREQUENCY RESPONSE  
5Hz to 35KHz (-3dB)  
SIGNAL TO NOISE RATIO  
60dB magnetic pick-up  
72dB radio

Components available in separate packs  
Eg.  
Resistors and capacitors £ 3 70  
Switches and controls £ 2 35  
Fibre Glass PCB £ 1 50  
Semiconductors £ 8 35  
For other parts and full specification please see our free list.

### THYRISTORS

### RECTIFIERS

PIV	1A	3A	7A	16A	1A	1.5A	3A
50	25p	27p	45p	60p	7p	8p	19p
100	27p	30p	50p	65p	7p	9p	20p
200	35p	37p	55p	75p	8p	10p	22p
300	40p	45p	60p	85p	9p	11p	25p
400	45p	50p	65p	90p	10p	12p	26p

FOR FREE ILLUSTRATED LIST PLEASE WRITE TO

DEPT. D

22 THE PANTILES BEXLEYHEATH KENT

UK POST FREE EXCEPT WHERE STATED OVERSEAS AT COST  
MAIL ORDER ONLY

## VALVES

SAME DAY SERVICE  
NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3B4, 3V4, 6AF91, DP91, DK91, DL92, DL94.  
Set of 4 for £1-12. DAF96, DP96, DK96, DL96, 4 for £1-55.

1R5	-28	30C15	-58	EABCR0	-32	EL500	-62	PCF808	-68	U801	-75
1S5	-22	30C17	-76	EAF42	-50	EM80	-38	PC182	-30	UABC80	-32
1T4	-16	30C18	-68	EB91	-10	EM81	-38	PC183	-67	UAF42	-60
3B4	-26	30P3	-64	EB33	-40	EM84	-32	PC184	-84	UBC41	-65
3V4	-47	30FL1	-65	EB34	-49	EM87	-50	PC185	-88	UBF89	-84
6U4G	-31	30FL12	-68	EB38	-20	EY61	-38	PC186	-88	UBF89	-82
6V4G	-35	30FL14	-68	EB390	-22	EY66	-59	PC188	-68	UCB84	-82
6Y3GT	-34	30L1	-29	EBF80	-32	EY87	-29	PC1800	-80	UCB86	-85
6Z4G	-35	30L15	-70	EBF83	-39	EZ40	-39	PCL805	-88	UCF80	-82
6Z6L2	-54	30L17	-67	EBF89	-29	EZ41	-39	PEN44	-77	UCH42	-88
6AL5	-11	30P4	-65	EBC81	-17	EZ80	-21	PEN360	-70	UCH81	-80
6AM6	-13	30P12	-69	EBC82	-20	EZ81	-22	PFL200	-62	UCH82	-82
6AQ5	-22	30P19	-65	EBC83	-35	EZ90	-25	PL36	-49	UCL83	-55
6AT6	-20	30P11	-60	ECC85	-34	GZ30	-34	PL81	-44	UF41	-52
6AU6	-20	30P113	-89	ECC804	-54	GZ32	-40	PL81A	-47	UF89	-80
6BA6	-20	30P114	-85	ECCF80	-31	KT41	-77	PL82	-31	UL41	-83
6BE6	-21	35L6GT	-45	ECCF82	-26	KT61	-55	PL83	-83	UL84	-80
6BJ6	-41	35W4	-25	ECH35	-55	KT66	-78	PL84	-80	UM84	-82
6BW7	-50	35Z4GT	-25	ECH42	-59	LN319	-63	PL500	-63	UY41	-89
6F14	-40	50CD6G	-68	ECH81	-29	LN329	-72	PL504	-63	UY85	-25
6P23	-68	807	-49	ECH83	-38	LN339	-63	PM84	-83	VP4B	-77
6P25	-53	AC/VP2	-77	ECH84	-35	N78	-87	PX25	-85	W77	-43
6J7G	-24	B349	-65	ECL80	-35	P61	-40	PT32	-52	Z77	-22
6E7G5	-12	B729	-62	ECL82	-29	PABC80	-34	PY33	-52	Transistors	
6K8G	-17	COH35	-67	ECL86	-35	PC86	-47	PY81	-25	AC107	-17
6Q7G	-35	CY31	-30	EF39	-38	PC88	-47	PY82	-25	AC127	-18
6SL7GT	-30	DAF91	-22	EF41	-57	PC96	-42	PY83	-28	AD140	-87
6SN7GT	-30	DAF96	-36	EF80	-33	PC97	-36	PY88	-34	AF115	-80
6V6G	-28	DF91	-18	EF85	-28	PC990	-29	PY800	-34	AF116	-80
6V6GT	-28	DF96	-36	EF86	-30	PC984	-29	PY801	-34	AF117	-80
6X4	-23	DH77	-20	EF89	-26	PC986	-23	R19	-30	AF125	-17
6X5GT	-28	DK32	-33	EP91	-13	PC888	-38	R20	-70	AF127	-17
10P13	-53	DK91	-28	EP92	-27	PC889	-43	U25	-73	OC26	-25
12A7	-17	DK92	-50	EP98	-85	PC8189	-48	U26	-70	OC44	-12
12AU7	-20	DK96	-45	EP183	-28	PC808	-70	U47	-75	OC72	-18
12AX7	-22	DL35	-40	EP184	-31	PCF80	-29	U49	-70	OC71	-18
19B6G	-75	DL92	-26	EH90	-34	PCF82	-33	U52	-81	OC72	-12
20P2	-67	DL94	-47	EL33	-55	PCF86	-46	U78	-24	OC75	-12
20P3	-75	DL96	-38	EL34	-55	PCF800	-58	U91	-68	OC81	-12
25L6GT	-19	DY86	-24	EL41	-44	PCF801	-28	U93	-42	OC81D	-12
25U4GT	-57	DY87	-24	EL84	-23	PCF802	-40	U951	-64	OC82	-12
30C1	-28	DY802	-33	EL95	-33	PCF806	-58	U929	-68	OC82D	-12

## READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Minimum post/packing on 1 valve 7p., on each additional valve, (3p. per. valve extra)  
Any parcel insured against damage in transit 3p extra.

## GEIGER COUNTERS

(FOR MAINS OR PORTABLE BATTERY USE)

Latest Home Office release and probably the last, of this well known Contamination Meter No. 1, this very useful instrument is used for the measurement of Radio-Activity. Indicated on an Internal Meter scaled 0-1 to 10 milli Rontgens/Hour, a socket is also provided for additional sound Monitoring on Headphones. This instrument is housed in a Strong light Alloy Case, placed in a carrying Haversack with shoulder strap. Contains 4 AA Hand held Probe, Instruction sheet, plus the latest type 6V1 vibrator Power Unit, which uses current small Transistor Batteries (4 Mallory Long Life RM12 or 4 EverReady H.P.7 or equivalent makes).



For Mobile use anywhere. (Cost Gov. approx. £70 each). Supplied Brand New in Carton only £55.00 carr. 50p. An additional plug-in socket for transistor use operates from 100-120 volts or 200-250 volts A.C. Mains is available. Supplied Brand New in Carton only £2-50 post 25p. Headphones (not necessary) if required £1-50 at only £4-50.

A few Geiger Counters as above but not boxed in cardboard cartons, available at only £4-50.

## JOHNS RADIO

Dept. D, 424 Bradford Road, Bately, Yorks. Phone Bally 7732

## 6 Watt STEREO AMPLIFIER BARGAIN!


FOR REAL QUALITY RESULTS!

Base your own stereo system on one of these super quality stereo amplifiers. With low distortion levels (averaging 0.2%) and total power of 6 Watts r.m.s. (8Ω load 3w/channel) they will give you a rousing dynamic performance with good speakers. Each has two of the well proven Plessey integrated circuit amplifiers with built in preamplifier sections providing 100mV sensitivity and, with a bandwidth of 50 to 15kHz, are ideal for tuners and crystal pick-ups. The circuit features controls for Bass, Treble, Volume and Mains on/off. All leads and Din speaker plugs and sockets can be supplied. All units are fully guaranteed.

602 Amplifier as above (10" w x 2 1/2" D) £7.48  
601 Amplifier as above but single tone control (8 1/2" w x 2 1/2" D) £5.95.  
Mains Transistor 600 series amplifiers £1.20.  
Lead, plug and socket set 38p

Cheques & P.O.s plus 20p post and packing to:

The AUTOTRON Company, HIXON, STAFFORD

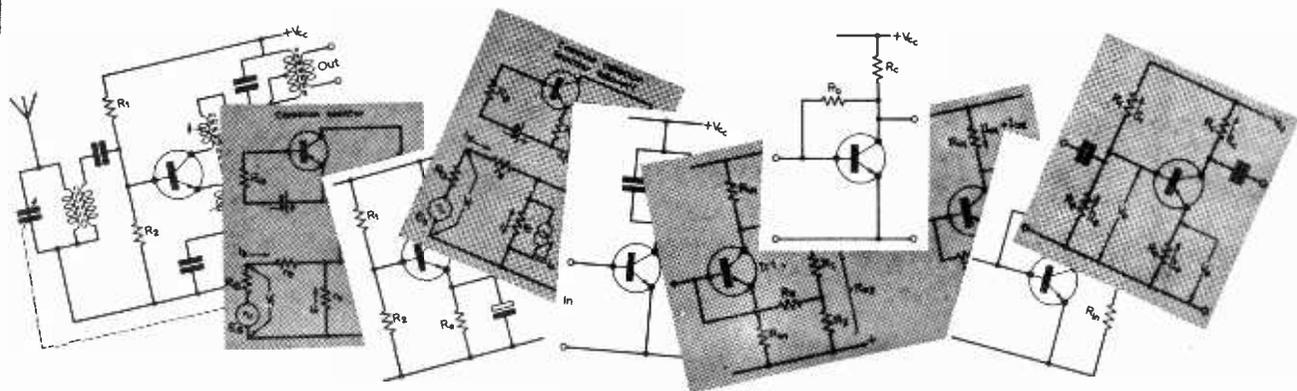

# TRANSISTOR CIRCUITRY for beginners

H.W. HELLYER & MICHAEL HOLLIER

## PART 12

### Virtual Earth in practice

Theory is all very well; an interesting intellectual exercise. Sooner or later, we must put our theories to the test, our principles into practice, and it is then—as any constructor will tell you—that the moment of truth comes. When you switch on, hold your breath, tentatively measure, go back meticulously over every step you have made and find the snags. That feeling of utter elation when a self-designed, self-made circuit bursts into life has no parallel in the world of module-massing. Humble though our circuitry may be, we are tempted to say: 'A poor thing, but mine own . . .'

So this month, following a discussion of virtual earth principles that may have left some of you

wondering what all the fuss is about, we put our theories into practice. Again, we shall proceed step by step, explaining *why* each component has to be its particular value, and what it does. Only this way is it possible to adapt ideas to your particular situation, i.e., to make your own design.

Part 10 in September *PW*, left us with a directly coupled pair of transistors, the first device acting as a collector-follower and with a potential divider for the derivation of its base bias. The second transistor operated in the common collector mode—that is, it was an emitter follower—and its base bias was derived from the collector of the first transistor, to which it is, (see Fig. 53, page 429, September *PW*) directly connected.

In the subsequent issue, under the guise of giving us all a breather, we talked about virtual earth circuitry, but you will have noted, in Fig. 60, that we again used a pair of transistors, intimately connected, directly coupled, so that their combined operation can be regarded, with some provisos, as that of a single unit.

Now let's take a look at a redrawn circuit of our earlier arrangement. Fig. 61 (a) is the redrawn circuit of our previous direct-coupled pair, this time with some components removed for simplicity. These are the base bias resistors, the input and the output coupling capacitors.

We still need base bias current, and this time we get it from the emitter of the second transistor. The important component is  $R_b$ . Take a look at another way of presenting such a circuit, Fig. 61 (b), which is really a redrawn Fig. 51 (*PW* Aug. 1972): now compare this with (c), which is, of course, a redrawn version of (a). The essential modification is that the base-emitter junction of the second transistor is included now in series with  $R_b$ . The similarity of the circuits is significant: similar spreads can be expected.

### Gain

With this circuit, just as with the circuit of Part 10, gain is determined by the ratio of collector and emitter resistors of Tr1, which is to say,  $R_{c1}/R_{e1}$ .

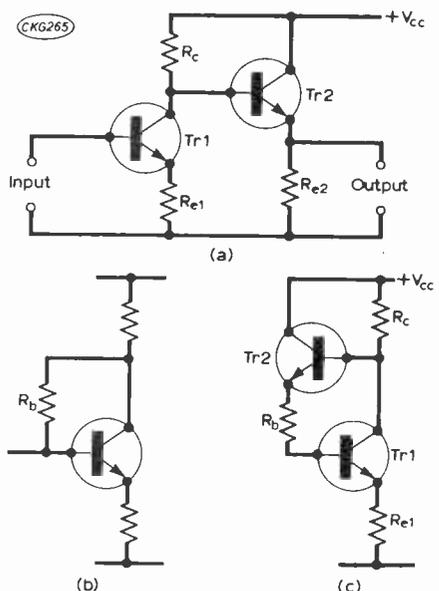


Fig. 61 (a): Redrawn circuit of Fig. 53 with some components omitted for simplicity. (b) base bias can be derived this way, included in (c) we have redrawn version of (a).


But this gain is before any feedback is applied. It is called the OPEN LOOP GAIN, and is denoted by the term  $G_o$ . As we shall see later, though it can be calculated fairly enough, it is not quite so easy to verify by practical measurement.

When we put a bit of negative feedback in circuit, conditions alter. We are now taking a portion of the output and applying it to the input of our amplifier in such a way as to reduce the gain in proportion to the growth of the signal. If we apply the same feedback another way, of course, we can cause the amplifier to increase its gain in accordance with the signal, and thus go haywire. We are concerned here with *negative feedback*, reducing the gain selectively. So we get CLOSED LOOP GAIN.

The determination now is from the value of that feedback and the source input. In plain symbols the ratio of feedback resistor to source resistance, or

$$\frac{R_b}{R_1 + \text{source resistance}}$$

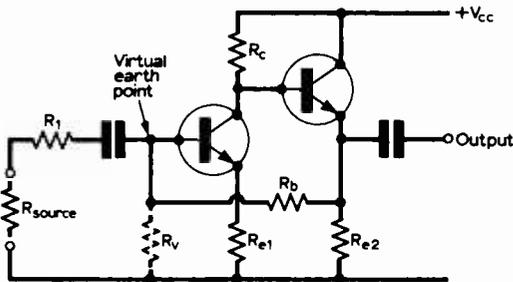That magical term (if you read the right brochures!) the 'Virtual Earth' occupied us last month and we shall now return to it, as in Fig. 62.



Open loop gain  $G_o = \frac{R_c}{R_{e1}}$   
 Closed loop gain  $G_c = \frac{R_b}{R_1 + R_{\text{source}}}$   
 Effective virtual earth resistance  $R_v = \frac{R_b}{G_o}$

CKG268

Fig. 62: Virtual earth amplifier with feedback emitter Tr2 to base of Tr1.

Here, the virtual earth point is indicated and we must remember that the *effective* resistance at this point is determined by the ratio of that feedback resistor  $R_b$  and the open loop gain of the stage. This is  $R_b/G_o$ . Take a close look at this circuit, study it so that it can be recognised immediately, for this virtual earth circuitry will not show  $R_v$ , even dotted, as we have, and it is very easy to miss the implication. So let's now start to calculate the component values, for a practical circuit that can be part of a mixer, a microphone pre-amplifier, a variable gain pre-amplifier for an oscilloscope, and several other things.


## Calculations

In Fig. 63(a) we have the same circuit, again shorn of unnecessary frills, and now we have a 'rail voltage', or h.t. positive, of  $V_{cc}$ , whichever term your age group has committed you to using, of 20 volts. The point is that we want a reasonable voltage 'swing' and if a collector is going to go up and down like a yo-yo, there will be a need for a high enough  $V_{cc}$  to accommodate this change in collector voltage. Thus far, we have been managing with 9-volt


batteries, convenient, easily obtainable, a constructor's aid. Now we must face the need for adding several in series or building a power supply operated from the a.c. mains. We shall look at the latter in a moment. For now, remember that the  $V_{cc}$  is 20 volts and for an emitter current of 2mA in the Tr2 circuitry, and a voltage at the emitter of about half the supply, we get  $R_{e2} = 10/0.002 = 5,000$  ohms.

Remembering that the base-emitter voltage will normally be 0.6V for the BC109, we say the base voltage will be 10.6V, and this is also the voltage at the Tr1 collector. We have already noted that for good stability it is desirable that the voltage drop across  $R_b$  is small. Under these proposed conditions, Tr1 would be operating with a collector to emitter voltage of a mere 600mV.

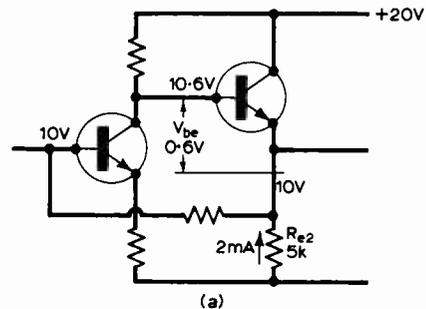Now it is perfectly possible to use a transistor under these conditions, but the signal swing will be somewhat limited, so we look for an alternative way of doing things. One method is to split the feedback point, as in Fig. 63(b).  $R_{e1}$  is maintained at the same ohmic value, but the feedback is tapped off



(a)

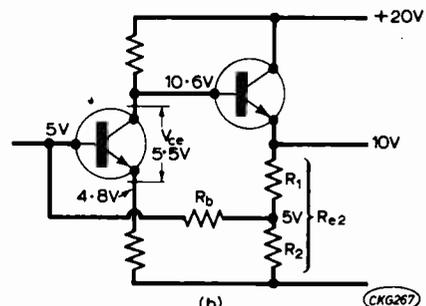

(b)

CKG267

Fig. 63 (a): V.E. circuit redrawn. (b) tapping off of feedback point.

from the junction of the divided  $R_{e2}$ , so that 5 volts is available at the base of Tr1 as bias. The voltages at Tr2 base and collector have not altered, so we have the condition now where Tr1 operates at a collector-to-emitter voltage of something like 5.5 volts.

Again allowing a 0.6 volts difference between base and emitter, we can now calculate Tr1 emitter resistor. The current flowing through  $R_{e1}$  can be large, using a small value of resistor, but this will not help us guard against noise. On the other hand, if we aim at a very low current, and hence a large resistor, our open-loop gain goes for a chop! Take an example: if the emitter current of the first transistor were to be 100 microamps, then  $R_{e1}$  would be 48k $\Omega$  and  $R_{c1}$  would have to be something like

$$94k\Omega. \text{ From our earlier formula, } G_o = \frac{R_c}{R_e} = \frac{94k\Omega}{48k\Omega}$$

i.e., an open loop gain of something like two!

# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

**10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND**


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated Telescopic Aerial, for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Air Spaced ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 80p (FREE with parts).

Total building cost

**£8-50**


P. P. & Ins. 50p

(Overseas P. & P. £1)

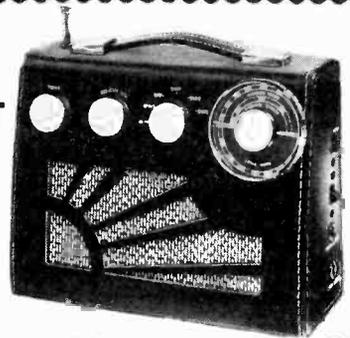

## ROAMER EIGHT Mk I

**NOW WITH VARIABLE TONE CONTROL**

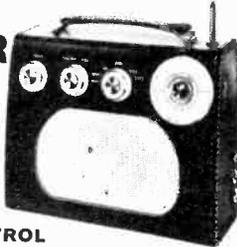

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P.P. & Overseas P. & P. £1) Ins. 41p.

## ROAMER SEVEN MK IV




7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

Total building costs **£5-98** P.P. & Overseas P. & P. £1) Ins. 41p.
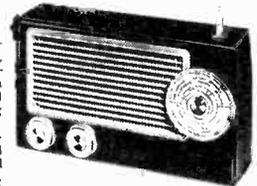
## ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra M.W. band for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6½ x 2½in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.




Total building costs **£3-98** P.P. & Overseas P. & P. £1) Ins. 30p
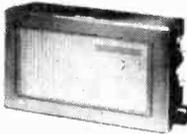
## POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5½ x 1½ x 3½in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-29** P.P. & Overseas P. & P. £1) Ins. 21p




## TRANSONA FIVE

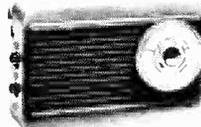**5 TRANSISTORS AND 2 DIODES**

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6½ x 4½ x 1½in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-50** P.P. & Overseas P. & P. £1) Ins. 22p




## TRANS EIGHT

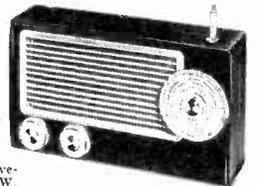**8 TRANSISTORS and 3 DIODES**

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P.P. & Overseas P. & P. £1) Ins. 31p



## NEW! "EDU-KIT"

**BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY-TO-FOLLOW STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.**

**COMPONENTS INCLUDE:**  
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 3 inch Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs.

Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction

All parts including **£5-50** P.P. & Case and Plans Ins. 31p (Overseas P. & P. £1)



**FULL AFTER SALES SERVICE**

• Callers: side entrance Barratts Shoe Shop  
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>


Parts price list and plans for .....

Name .....

Address .....

PW47

# LINDAIR (ELECTRO-TECH) LTD

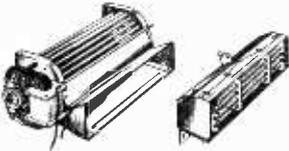

## TANGENTIAL HEATER

Silently driven by a shaded pole Mylex motor. Compact, powerful and quiet running with aluminium Impeller (outlet  $\frac{3}{4}$  x  $\frac{1}{4}$ ). Mains voltage. PLUS matching heater unit with spiral element. May be switched for 500 or 1,000 watts. PRICE ONLY **£1.60** P. & P. 40p

## SYNCHRONOUS AUTO-RESET PROCESS TIMER



**BY LONDEX LIMITED**  
Type IMP Mk. 2. Brand New and Boxed. These well known timers are already in world-wide use and are perfect for Industrial Electronic Timing. Research and for all machine control timing problems. Repetitive accuracy better than 0.5% of full scale setting. Two or more can be interconnected to give control of a series of processes, 230/250v. 50Hz, also available 60Hz. 15 minutes full scale, 15 secs. per division. Driven by self-starting sync. motor. Contact rating 5 amp at 250v. a.c. Incorporates solenoid operated clutch Also, lever actuated micro switches. Normal price probably in excess of £18. Complete with multi-pin connector as illustrated.

OUR PRICE ONLY **£6.50**

## SEEN THIS ?

This is the only way we could illustrate this fabulous item.

**NORPLEX** the famous American fibre-glass copper-clad laminate. Finest quality with Woven Glass base of Epoxy-resin. Excellent mech. and elec. conductive properties. Heat Resistant. Ideal for P.C.s. etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST. Sizes: 12" x 12"; 24" x 12"; 24" x 24"; FULL SHEET 48" x 37" (11 sq. ft.). Single sided copper with thicknesses of  $\frac{1}{32}$ ",  $\frac{1}{16}$ ",  $\frac{1}{8}$ ",  $\frac{1}{4}$ ",  $\frac{1}{2}$ ", also Double sided  $\frac{1}{32}$ ",  $\frac{1}{16}$ ",  $\frac{1}{8}$ ".

PRICE ONLY **£1** per sq. ft. **£3** per full sheet. P. & P. 25p up to 4 sq. ft. Over 4 sq. ft. (cut sizes only) Post FREE. Full sheets post by rail G.B. only **£1** one or more sheets.

## MICRO-LITES

Wonderful engineering—micro miniature incandescent lamp small enough to pass through the eye of a needle! 1,000's of uses. Will operate from the output of a transistor. Rating: 1.5v, 10-15ma. Size 4.4 x 1.4mm. dia. Leads 22mm. These fantastic lamps have a life expectancy of 1,000 hrs.

OUR PRICE **£3.25** per doz. Free p. & p.


## NEW AND UNUSED

Postal or carriage charges are for Great Britain only. We welcome orders from established companies, educational depts., etc. All orders under **£2.50**, cash with order please.

## FURTHER BULK PURCHASE SILVANIA MAGNETIC SWITCH

**£2.10**  
NOW COMPLETE WITH REFERENCE MAGNET! A magnetically activated switch. Vacuum sealed in a glass envelope. Silver contacts normally closed, rated 3 amp at 120v, 1 1/2 amp at 240v. Size (approx.) 1 7/16" long x 1/2" dia. Ideal for Burglar Alarms, Security systems, etc., and wherever non-mechanical switching is required. New Lower Price. Only **£2.10** for 12, **£3** for 50 or **£15** for 100 complete with magnet.

## PROGRAMMER TIMER BY HONEYWELL

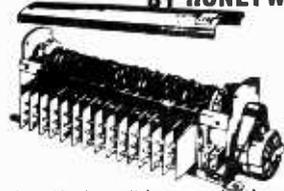

A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Designed originally for vending machines at a cost of **£15.00** plus. Many applications where continuous sequence programmes are required, such as lighting effects etc. New in original makers cartons. First class value at **£5.75** plus 25p P. & P.

**£5.75**

315 EDGWARE ROAD, LONDON W2. Tel: 01-262 2251. Open 9 a.m.-6 p.m. MON to SAT

## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt **£3.20**. Kit Form **£2.70**  
300 Watt — **£2.70**. Kit Form **£2.20**

All plus 10p post and packing. Please send C.W.O. to:

**DEXTER & COMPANY**  
2 ULVER HOUSE, 19 KING STREET,  
CHESTER CH1 2AH Tel: 0244-25883

As supplied to H.M. Government Departments.

## TRANSFORMERS

### DOUGLAS GUARANTEED 12 or 24 volts

Output V. & Amps.	Ref. No.	Price P. & P.
12V x 2 250 mA x 2	MT111 CS*†	£0.81 9p
12V x 2 500 mA x 2	MT113 CT*†	£0.97 16p
12V x 2 1A x 2	MT 71 AT†	£1.48 24p
12V x 2 2A x 2	MT 18 AT	£2.06 30p
12V x 2 3A x 2	MT 70 AT	£2.59 36p
12V x 2 4A x 2	MT 108 AT	£2.82 34p
12V x 2 5A x 2	MT 72 AT	£2.96 42p

30 volts. All tapped at 0-12-15-20-24-30V

put Amps.	Ref. No.	Price P. & P.
500 mA MT 112 CT†	16p	3A MT 20 AT 2-84 32p
1A MT 79 AT†	1-55 30p	4A MT 21 AT 3-10 40p
2A MT 3 AT	1-50 50p	5A MT 51 AT 4-31 42p

50 volts. All tapped at 0-19-25-33-40-50V.

put Amps.	Ref. No.	Price P. & P.
500 mA MT 102 AT†	1-41 20p	3A MT 105 AT 8-91 41p
1A MT 103 AT	1-57 20p	4A MT 106 AT 5-08 41p
2A MT 104 AT	3-10 32p	5A MT 107 AT 7-47 50p

60 Volts. All tapped at 0-24-30-40-45-60V.

put Amps.	Ref. No.	Price P. & P.
500 mA MT 124 AT†	1-46 30p	2A MT 127 AT 8-18 41p
1A MT 126 AT	2-24 32p	3A MT 125 AT 4-59 41p

### AUTO-WOUND RANGE

Power output	Winding tapped at	Ref. No.	Price P. & P.
20 VA	0-115-210-240	MT 113 CT	£0.89 16p
75 VA	"	MT 64 AT	£1.72 30p
150 VA	0-115-200-220-240	MT 4 AT	£2.15 32p
200 VA	"	MT 65 AT	£2.00 32p

400 V. Output at 50 Hz. Ref. IT3 AT Price P. & P. C-D Ignition system by R. M. Marston **£2.30 29p**

### EQUIPMENT RANGE

Sec. Output (r.m.s.)	Ref. No.	Price P. & P.
3-0.3 V.	200 mA MT 238 CS*†	£0.89 8p
9-0.9 V.	100 mA MT 13 CS*†	£0.91 8p
12-0.12	50 mA MT 239 CS*†	£0.91 8p
20-0.20	30 mA MT 241 CS*†	£0.91 8p
0-20 x 2	300 x 2 MT 214 CT*†	£1.51 16p
0-8-9 x 2	500 mA x 2 MT 207 CT*†	£1.51 19p
0-15-20 x 2	500 mA x 2 MT 205 AT*†	£2.12 29p
0-15-27 x 2	500 mA x 2 MT 203 AT*	£2.45 29p
0-15-27 x 2	1A x 2 MT 204 AT*	£3.42 30p
10-12-0-12-20 700 mA (d.c.)	MT 221 AT*	£1.12 26p

AT Indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; \* with interwinding screen; † untapped 240V Primary; ‡ Primary tapped at 210-240V. other Primaries tapped at 200-220-240V. Over 200 types in stock through agents or direct. Send for list.

DOUGLAS ELECTRONICS INDUSTRIES LTD. (Dept. M06FW), Thames St., LOUTH, Lincs. LN11 7AD

**N-E-W** Fully electronic voice operated Auto-fade unit.

**N-O-W** With built in Mic. pre-amp for Auto music fade system.

**£6.00** per kit. **£8.75** ready to use.

**N-E-W** Quality stereo pickup Pre-amps with tone controls.

**N-O-W** On 90mm. square fibre glass board (for MAG, CER, or CRY.)

**£9.00** per kit. **£12.00** ready to use.

**N-E-W** Expandable audio mixer cabinets.

**N-O-W** Offer economical low cost system.

Please add 25p for postage & packing.

S.A.E. for details

**PARTRIDGE ELECTRONICS**  
23-25 HART ROAD, BENFLEET  
ESSEX SS7 3PB

We can, true, bypass the first emitter resistor with a whacking great capacitor, but let's not complicate matters at this stage. I hope the point is gradually being made that in this type of deceptively simple transistor circuit design one has to consider both a.c. and d.c. conditions; one can affect the other. What may be fine from the bias point of view may not be the best for signal conditions. We must press on . . .

### In practice

The practical answer to the problem is to use the potential divider again, but this time as shown in Fig. 64. This circuit is more like the real thing, as our airy-fairy calculated values of components now give way to preferred values, such as 4.7kΩ for Re2.

Calculating the rest of the values requires recourse to the graphs for the particular transistor. If you have been following this series—and our mail-bag shows, bless you, that quite a few have—you will be able to turn up the June issue and refer to Fig. 42, which was the  $h_{FE}$  against  $I_c$  curve for a BC109. We ignore the illustrative co-ordinates this time, and find that for an  $I_c$  of 2mA, the  $h_{FE}$  is 440,

so our base current of Tr2 is  $\frac{2mA}{440}$  or around 4.5 microamps.

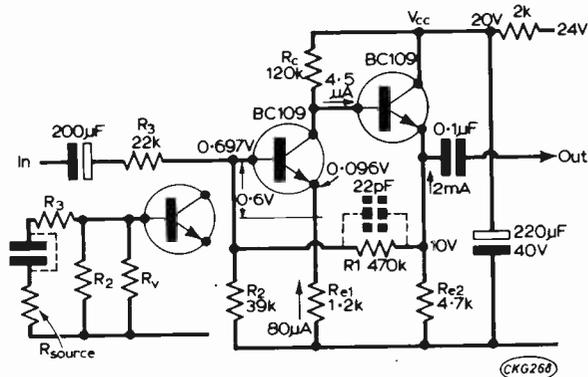


Fig. 64: Working circuit with component values.

As this current is flowing through the collector load of the first transistor, and is very small in comparison with the collector current of Tr1, we can safely disregard it in our next calculation. The emitter voltage of Tr2, we have said, is 10V, and the base will be 0.6V greater, so this 10.6 volts will be the collector voltage of Tr1. Therefore, the voltage across Rc1 will be the difference between the supply of 20 volts and this 10.6V, i.e., 9.4V.

From what we have already said about the choice between noise figures and signal swing at Tr1, we realise that there are limitations, upper and lower, for the emitter current, and for the balance between the feedback resistor and R2, now part of the bias circuit. Practically, our limits are from a minimum of 3 microamps and an upper of 200 microamps, which gives us R1+R2 of between 47kΩ and 3.4MΩ.

Plenty of choice? Maybe, but for a compromise value of emitter current that gives us preferred values of resistors and practical conditions, we have plumped for a figure of 80 microamps, as shown in

Fig. 64. So  $R_c$  becomes  $\frac{9.4}{80 \times 10^{-6}}$  or approx. 120kΩ.

An open loop gain  $G_o$  of 100 is a healthy figure and as this is  $\frac{R_c}{R_e}$  so  $R_e$  becomes  $\frac{120k\Omega}{100}$  or 1.2kΩ.

If we again ignore the very small base current of the transistor, we can take it that the emitter current of Tr1 will be very near 80 microamps, and the voltage drop across Re1 will be 0.096V, which gives us a base voltage of nearly 0.7V. Referring again to the graph, we find for an  $I_c$  of 80 microamps we get an  $h_{FE}$  of around 280. So the base current will

be  $\frac{I_c I}{h_{FE} I} = \frac{80 \text{ microamps}}{280}$  or 0.2857 microamps.

If the base current is to be provided by the potential divider R1 and R2, to provide the current through these resistors is much greater than this, then Ib1 can be left out of subsequent calculations. But too low a combination of these resistors will affect the bias conditions of Tr2 (since we shall be shunting Re2 with the R1+R2 network). If we aim at a sum of the two at least 10 times that of Re2, we shall be safe. This summed resistance would be 47kΩ, and the current through them would be 200 microamps approximately—nearly a thousand times Ib1.

As to those limits: the minimum current we can allow through R1+R2 will be ten times Ib1, around 3 microamps, and the sum resistance would be 3.4MΩ. We have a very wide choice of values, but experience tells us that we cannot dip indiscriminately into the spares box.

TO BE CONTINUED

# NATIONAL AMATEUR RADIO AND ELECTRONICS EXHIBITION

at the

## GRANBY HALLS, LEICESTER OCTOBER 26th to 28th 1972

Opening times:

Thursday, Friday 26th, 27th, 12 noon to 9 p.m.  
Saturday 28th, 10 a.m. to 7 p.m.

Sponsored by the  
Amateur Radio Retailers Association



Come and see the latest developments in radio communications and electronics. World-wide contacts from the Exhibition.

Large car parks

Easy access from M1 Motorway Junction

Admission 20p

# GOING BACK...

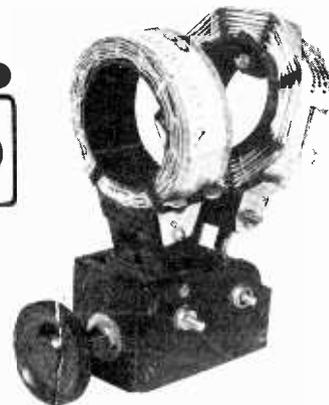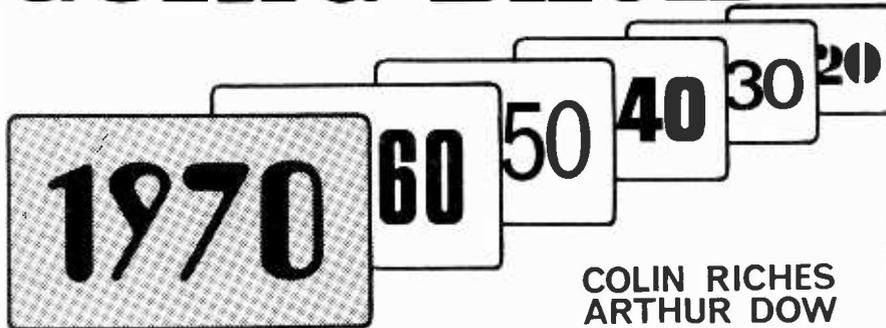

COLIN RICHES  
ARTHUR DOW

**F**IRST, we would like to apologise if anyone has written to us and not received a reply but from correspondence we are now receiving, it appears as though a few letters have gone astray. If, therefore, you have not heard from us and would like to repeat your letters, we will be pleased to reply as soon as possible.

We have received quite a large number of "points from the post" that we feel merit publishing almost as they have been written, so, without any more ado, let's begin . . .

**R. L. Graper**, 16 St. John's Avenue, Chelmsford, Essex tells us . . .

"In June 1922 I bought the first issue of *Popular Wireless* . . . No. 1, Vol. 1, and later, also the first issue of *Television*, No. 1, Vol. 1 in March 1928. I kept them and still have them (a little soiled) in the hope that they might later become valuable as "collectors items". As the address of *Popular Wireless* is the same as that of your present premises, I am wondering whether you took over the above journal.

There is much of interest in this first issue, and I quote you a few items as follows.

"Have you a wireless? First take out a licence. In a week or so this may be obtained direct from any post office. At present you must apply to the Secretary of the G.P.O. Cost of licence . . . 10/-.

Article. "Mr. Selfridge expresses his views. The business man and radio, by G. Selfridge."

I do not think the radiophone will ever supercede the telephone. Many wild predictions have been made on this point, and it has even been said that before long the man in the street will have his pocket transmitter with which to call up his friends or business colleagues. That prediction is very far fetched indeed. The pocket radiophone will never replace the telephone, because it will always be limited by the number of messages that can travel through the ether at the same time. At the moment, American amateurs are realising the bad effects of unlimited radio transmission . . . The ether is crammed with their messages, which consequently get so mixed up that it is impossible to hear a coherent sentence when listening in".

Short NEWS FLASH . . . Mr. Marconi's voyage . . . Mr. Marconi proposes to carry out experiments on the Atlantic with direction finders on the Short-wave, and the Long-wave transmission. Besides his other experiments, Mr. Marconi will carry out tests for the Meteorological Office. The "Electra", Mr. Mar-

coni's steam yacht of 700 tons, is the finest equipped floating wireless laboratory in the world."

Interesting prices . . . Instrument wires. Aerial Wire 7/23, which was of course seven strands of 23 swg. copper wire. Price: 6/6 per 100 feet. Double silk covered wire 12 swg: 4/- per lb, Single valve Detector panel: 32/-, single valve h.f. panel: 35/-. These two panels together gave, it was claimed by the advertiser, a complete two valve receiving set. This was capable of receiving all music, speech etc. from all British stations.

In my copy of *Television* No. 1, March 1928, there are many interesting items, such as the early experiments by Baird, with a short paragraph giving details of his first demonstration before the Royal Institution.

There are pages of advertisements for (guess what) Radio sets and parts for the radio constructor. As no *Television* receiver is shown or advertised, I presume this came a few months later. The first experimental transmissions on the 30 line system could be received on home made apparatus, and there are articles (most detailed) on Disc Receivers, Light sensitive cells, a cartoon drawn specially by Heath Robinson, and several articles on the future miracles of this new science . . . which indeed have in some cases become fact today.

In this year there were quite a number of Valve Portables, then priced in the £30 region, but one would rather call them "transportables" I think.

## Vintage Equipment


Mr. G. H. Wallace was recently presented with a pair of old headphones and he would like to know what impedance they are and what vintage they are likely to be.



continued on page 641
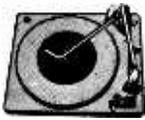
## BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL MONO-COMPATIBLE Plays all records



£8.75 Post 25p.  
£7.75 Post 25p.

RC5 DE-LUXE 8 WATT AMPLIFIER. Ready made tested. Printed circuit. 3 watts output. Tone and volume controls. Complete with two knobs, output valve and rectifier and high performance loudspeaker. Double wound fully insulated mains transformer. A.C. Mains 200/250V. Response 50-12,000 cps. Sensitivity 300mV. £4 Post 25p.

## GARRARD DISCO DECK

£10 Post Free

4 speeds. Plays all sizes of records. 4 pole heavy duty motor. 8 in. belt turntable. Plug in head complete with stereo/mono cartridge. Adjustable stylus pressure. Autostop. Brown and Cream finish. AC mains 110/240V. Base plate size 12 1/2 x 8 in. Operating area 14 1/2 x 12 1/2 in. Above motor board 8 in., below motor board 2 1/2 in. Ideal for Home Hi-Fi or Discotheque.



GARRARD AUTOCHANGERS with Sonotone Cartridges Stereo Diamond and Mono Sapphire. Model 1025 £10. Model 8500 Stereo and Mono Autochanger £14. Post 25p.

BSR JUNIOR SINGLE PLAYER £4.50 Turntable, 4-speed motor and separate pick-up

HI-FI PICK-UP CARTRIDGES. Diamond LP/Stereo Stereo/Mono DTA £2.50; GP94 £2.50; GP93 £2.00; Sapphire Mono GP91 £1.50; Power-point LP/78. 80p.

## E.M.I. WOOFER AND TWEETER KIT

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 44oz, Gauss 18,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser supplied. Impedance Standard 8 ohms Maximum Power 12 watts Useful Response 35 to 18,000 cps Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in, £9 POST 25p MODERN TEAK DESIGN



WEYRAD P50—TRANSISTOR COILS

RAEW Ferrite Aerial 7sp Spare Cores 3p  
Osc. P50/LAC 33p Driver Trans. LEFDTs 58p  
I.F. P50/200 470 kc/s. 88p Printed Circuit, PCAL 1.58p  
3rd I.F. P50/300 38p J.B. Tuning Gang 60p  
P51/1 or P61/2 38p Weyrad Booklet 15p  
P50/37 68p OPT 68p

Mylard Ferrite Rod 8 x 1 1/2 in. 20p, 8 x 1 1/2 in. 20p.

## VOLUME CONTROLS

800hm Coax 4p. yd. BRITISH AERIALTE  
ing spindles. Midget Size AERAXIAL-AIR SPACED  
P.K. ohms to 2 Meg. LOG or 40p. £1.40; 80p. yd. £2.  
STEREO L/S 55p. D.P. 75p. FRINGE LOSS 10p yd.  
Edge 6K. S.P. Transistor 25p. Ideal 625 and colour.

## 8in & 10in ELAC HI-FI SPEAKERS

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm coil. 8in. 10 watt, 10in. 12 watt music power.



£3.75

## E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 25p

With flared tweeter cone and ceramic magnet, 10 watts. Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p

BLANK ALUMINIUM CHASSIS 18 s.w.g. 2in. sides. 7 x 4in. 45p; 9 x 7in. 60p; 11 x 7in. 70p; 13 x 9in. 90p; 14 x 11in. 95p; 15 x 14in. 99p; 11 x 8in. 50p; 18 x 10in. £1

ALUMINIUM PANELS 18 s.w.g. 2 x 4in. 9p; 8 x 8in. 15p; 14 x 8in. 19p; 10 x 7in. 19p; 12 x 8in. 20p; 12 x 8in. 25p; 16 x 8in. 29p; 14 x 8in. 34p; 12 x 12in. 40p; 18 x 10in. 50p.

HI-FI STOCKISTS RETURN OF POST DESPATCH MINIMUM POST AND PACKING 15p

## RADIO COMPONENT SPECIALISTS

Radio Books & Component Lists 5p. Written guarantee. (Export: Remit cash and extra postage.)

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer Input 200/240V. AC. Output voltages available 8 or 9 or 12 or 15 or 18 or 20v. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST DETAILS S.A.E. Size 8 1/2 x 1 1/2 x 1 1/2 in. POST FREE

## GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12v or H.T. line 200-300v D.C. operation. Size 1 1/2 x 1 1/2 x 1 1/2 in. Response 25 c.p.s. to 25 Kc/s. 26db gain. For use with valve or transistor equipment. 90p Post Full instructions supplied. Details S.A.E. 10p

NEW TUBULAR ELECTROLYTICS

2/350V .. 14p	250/25V .. 14p	50+50/350V .. 35p
4/350V .. 14p	500/25V .. 20p	60+100/350V .. 58p
9/450V .. 14p	1000/25V .. 35p	32+32/250V .. 18p
16/450V 15p	1000/50V .. 47p	32+32/450V .. 33p
32/450V 20p	8+8/450V 18p	350+50/325V 80p
25/25V 10p	8+16/450V 20p	32+32/350V 43p
60/50V .. 10p	18+16/450V 25p	100+50+50/350V 48p
100/25V 10p	32+32/350V 25p	

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.  
500mF. 12V. 15p; 25V. 20p; 50V. 30p.  
1000mF. 12V. 17p; 25V. 25p; 50V. 47p; 100V. 70p.  
3000mF. 6V. 25p; 25V. 42p; 50V. 47p.  
2500mF. 50V. 82p; 3000mF. 25V. 47p; 50 65p.  
5000mF. 6V. 25p; 1200mF. 25V. 75p; 50V. 85p.

CERAMIC 1pF to 0.01 mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 380V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1% 2.2-500pF 8p; 500-2.200 pF 10p; 2,700-5,800pF 20p; 8,800pF-0.01, mid 30p; each. TWIN GANG. "9-0" 208pF 1.75pF, 65p; Slow motion drive 385+385 with 250pF, 50p 500pF slow motion, standard 45p; small 8-gang 500pF £1.00.

SHORT WAVE STICKS 100F 250V; 25pF 55p; 50pF 55p. NEON PANEL INDICATORS 250V AC/DV Amber 20p. RESISTORS, 1/4 w., 1/8 w., 20%; 1/2 w., 2 w. 5p 10 ohms to 10 meg HIGH STABILITY, 1 w., 2% 10 ohms to 1 meg., 10p. DITTO 5% Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 ohms to 100K, 10p each; 2 1/2 watt, 1 ohm to 8 ohms 10p

## GARRARD DECADEC SP25 MK II RECORD PLAYER

With Stereo/Mono Detam Cartridge transcription head and arm Four speeds 10 1/2 in. turntable. Anti-rumble filter Bias compensation. Laboratory motor.



SPECIAL PRICE £18.50 Post 25p

## METAL PLINTH & PLASTIC COVER

Cut out for most Garrard or B.S.R. Will play with cover in position. Latest design. Covered in black leatherette. Post 25p

Antimagnetic, 12 1/2 x 14 1/2 x 3 1/2 in. ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH AT SAME PRICE

£5.50

## MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp. £1.50  
250-0-250 80 mA. 6.3 v. 3.5 amp. 1.1 a. or 5 v. 2 a. £2.50  
350-0-350 80 mA. 6.3 v. 3.5 amp. 0.3 v. 1 a. or 5 v. 2 a. £3.00  
400-0-400 v. 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. £2.25  
MINIATURE 200 v. 20mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p  
MINI-MAINS 200, 100mA. 1 1/2 x 1 1/2 x 1 1/2 in. 50p  
HEATER TRANS. 6.3 v. 2 x 4.5 6.3 v. 1 1/2 amp. 85p  
Ditto tapped sec. 1.5 v., 2 x 4.5 6.3 v. 1 1/2 amp. 85p  
GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2-25  
1 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £2-25  
2 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £2-25  
5 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £2-25  
AUTO TRANSFORMERS 115v. 0.25 amp. or 230v. to 115v. 150w. £2.25; 500w. £2.25; 750w. £1.00; 1000w. £1.4

CHARGER TRANSFORMERS. Input 200/250v. for 6 or 12v. 1 1/2 amp. £1.50; 2 amp. £1.80; 4 amp. £2.50. FULL WAVE BRIDGE CIRCUIT RECTIFIERS 6 or 12v. outputs, 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p LUCAS 2DS500 Bridge 70V 5 amp £1.

MAINS ISOLATING TRANSFORMER. Primary 0-110 240v. Secondary 0 240v. 3 amps. Fully watted. Insulated terminals. Various impedances. Fully enclosed in steel case with fixing feet. Famous make. BARGAIN £10 Carriage 50p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 85p. 2 p. 2-way, or 2 p. 6-way or 2 p. 8-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p

TOGGLE SWITCHES. 8p. 14p; dp. 18p; dp. dt. 23p.

## "THE INSTANT" BULK TEAK ERASER & HEAD DEMAGNETISER

200/250v. A.C. £2.35 Post Leaflet S.A.E. 15p



TEAK CABINET 16 x 10 x 9in. Fluted Front £5 Post 25p.

ALL MODELS "BAKER SPEAKERS" IN STOCK Hi Fi Enclosure Manual containing 20 plans, crossover data and cubic tables. 42p. Post Free

## BAKER 12in. MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50

## BAKER "BIG-SOUND" SPEAKERS

'Group 25' £8 12 inch 25 watt 3 or 8 or 15 ohm  
'Group 35' £9 12 inch 35 watt 3 or 8 or 15 ohm  
'Group 50' £20 15 inch 50 watt 8 or 15 ohm

TEAK HI-FI SPEAKER CABINETS. Fluted wood front For 12in. or 10in. dia. speaker 20 x 12 x 9in. 28. Post 25p For 13 x 8in. or 8in. speaker 18 x 10 x 9in. 25. Post 25p For 10 x 8in. or 8in. speaker 18 x 8 x 8in. 24. Post 25p LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft.

## GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm. 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns, Hi-Fi Enclosures Systems, etc. £4



## ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 x 2in. deep. Rating 10 watts. 3 ohm or 15 ohm models. £1.90 Post 10p

## SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-10kc/s, 10W 8 ohm or 15 ohm £1.50. De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm £3. TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 85p. SPECIAL OFFER: 50 ohm 2 1/2 in., 2 1/2 in., 3 1/2 in., 3 in 25 ohm, 2 1/2 in., 3 in dia.; 8 x 4 in.; 8 x 5 in. £1 EACH 15 ohm, 3 1/2 in. dia.; 8 x 4 in.; 7 x 4 in.; 3 ohm, 2 1/2 in. 3 in. 5 in. dia. LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1.25; 6 1/2 in. £1.50; 8 x 5 in. £1.60; 8 x 2 1/2 in. £1.50 8 in. £1.75; 10 x 6 in. £1.90. RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in. dia. 4 watt; 10 in. dia. 5 watt; 12 in. dia. 8 watt 3 or 8 or 15 ohm models £2-20 each. Post 15p. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 6 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p.

## BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £49 Post Free



## BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4.50

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £4.50

BARGAIN FM TUNER 88-108 Mc/s Six Transistor, 9 volt Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 inch £12.50

BARGAIN FM TUNER as above less cabinet £8.85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.50

COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 8p.

BALANCED TWIN RIBBON FEEDER 900 ohms 5p yd.

JACK SOCKET Std. open-circuit 14p. closed circuit 23p;

Chrome Lead Socket 45p; Phono Plugs 5p. Phono Socket 5p.

JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC SP; CANS 5p.

E.M.I. TAPE MOTORS Post 15p. 120v. or 240v. A.C. 1,200 r.p.m. pole 135mA. Spindle 0.187 x 0.76in. £1.25

E.M.I. GRAM MOTORS 120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Spindle 1/4 x 1/4 in. 75p

Size 2 1/2 x 2 1/2 x 3 1/2 in. Post 15p.

CUSTOMERS FREE CAR PARK CALLERS WELCOME

337 WHITEHORSE ROAD, CROYDON

Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)

Buses 50, 68, 159. Rail Selhurst. Tel. 01-684-1665

**BARGAIN PRICE**  
**BRAND NEW HARTLEY OSCILLO-**  
**SCOPES CT316** in original packing. Band  
width up to 5 Mc/s. Mains supply. Price £40.  
p. & p. £1.50p.

**BARGAIN PARCELS** 14lb at £1.45 plus  
32½p p.p.; 28lb at £2.75 plus 52½p p.p.; 56lb at  
£4.50 plus £1.25 p.p. Contain pots, Res.  
Valves, Diodes, Tagboards, Chassis, Valve-  
holders, etc. Good value save effts. Lucky Dip  
Service.

**FANTASTIC BARGAIN.** New 6 inch tubes.  
E450 4.B/16 4VH. medium Persistence. green.  
Ideal scope tube.  
Also 09J 4½in. dia. 1 length 15in. Also 7BP7 and  
5EP7. All unused as new. Price £1.40 post paid.

**NEW HEAVY COAX CABLE** dia. ½" 70 ohms  
approx. 50ft. lengths £1.40. p. & p. 30p. 100 ft.  
lengths £2.70. p. & p. 50p.

**AERIALS.** New Condition Whip Type. 4ft. 20p;  
11ft. 75p. all collapsible type. P. & p. 4ft. 10p.  
11ft. 15p. New bases on adjustable clamp for  
the above. 62½p. p. & p. 25p.

**CRYSTALS AS NEW:** Hc 6u. 5.345; 5.030;  
4.945; 4.875; 4.840; 4.795; 4.580; 4.660; 4.520;  
4.510; 2.300; 2.295 Kcs. 50p each plus 8p p.p.

**TRIMMER BARGAINS.** These are 10PF sub-  
min. air-spaced trimmers on board with min.  
wire ended Xtal. Brand new. No details: Con-  
tents 12 trimmers, some ceramic caps. Xtal  
frequency 3RD overtone 249 mc/s-250 Mc/s,  
255 Mc/s. No choice.

Trimmers without Xtal—60p per doz. plus  
17½p p.p.  
Trimmers with Xtal—75p per doz. plus 17½p  
p.p.

**ANY HEIGHT AERIAL TUBULAR SEC-**  
**TIONS** ½" dia. x 3 ft. long. Brass screw in ends.  
copper coated and painted. Good condition.  
20p. p. & p. 5p each. Minimum order 6.

**AS NEW AERIAL TUNER UNIT No. 6 RF.**  
consisting of 1½ inch 500 micro/ampmeter 3 gang  
tuner 75 PF geared BNC type socket size 5½" x  
4½" x 5". Price £1 50. p. & p. 25p.

**HEADPHONES DI.** High impedance. Good  
condition 75p. p. & p. 15p.

R209. Set of valves 62½p. p.p. 25p.

**NEW AERIAL WIRE ON BOARDS 7/22**  
**UNCOVERED** 75ft. 40p. 90ft. 47½p. 100ft. 55p.  
p. & p. 20p.

**MURKHEAD DECADE A.F. SIGNAL GEN-**  
**ERATOR.** This precision instrument can be used:  
1. To Measure Gain up to 40 db.  
2. To Measure Loss up to 45 db.  
3. To compare Power levels (A.F.).  
4. As an Audio Frequency Generator covering  
100 Hz. to 41 KHz. With a dial setting  
accuracy of ±0.5 Hz. Output—1 M/W into  
600 SL. Complete with mains power unit.  
Tested. Good Condition. £12. p. & p. 75p.

**AERIAL MAST POLES** approx. 5ft high 2" dia.  
Interlocking ends. Minimum order three. New  
condition. £1 each section. Carriage 35p each  
section.

½" 75 ohms Coax in 50ft coils with BNC plugs  
good condition. Price £1 + 30p p.p.

**2in. METERS.** 0-40 amps. 0-20 amps. All  
moving coil. 62½p. p.p. 12½p.

**SLIDING RESISTORS.** 12 amp. 1ohm. Approx.  
9in. long. 1-4 amp., 14 ohms. Approx. 7in. long.  
As new Ex Eap. 75p. p.p. 15p.

QUOTATIONS FOR QUANTITY.

**AS NEW UNUSED REJECTOR UNITS** for  
rejecting unwanted signals. Four ranges 1-2-10  
Mc/s. £1.50 p. & p. 20p each.

**C.W.O. CARRIAGE CHARGES MAINLAND**  
**ONLY**

**WOULD CUSTOMERS PLEASE ENSURE**  
**THAT ALL ORDERS ARE PRINTED IN**  
**BLOCK CAPITALS AND INCLUDE YOUR**  
**ADDRESS.**

**A. H. THACKER,**  
Radio Dept.,  
**HIGH STREET, CHESLYN HAY.**  
Nr. Walsall, Staffs.

**EX COMPUTER PRINTED CIRCUIT PANELS**  
2in x 4in packed with semi-conductors and top  
quality resistors, capacitors, diodes, etc. Our  
price 10 boards 50p. P. & P. 7p. With a guaran-  
teed minimum of 35 transistors. Data on  
transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1-  
P. & P. 18p. With a guaranteed minimum of 85  
transistors. Data on transistors included.

**250 MIXED CAPACITORS** 62p  
Plus 9p P. & P.

**709C OPERATIONAL AMPLIFIER T05**  
8 lead I.C. 1 off 50p. 50 off 35p.  
100 off 20p.

**250 MIXED RESISTORS** 62p  
½ & ¼ watt.

**150 MIXED HI STABS** 62p  
½ & 1 watt 5% & better.

**QUARTZ HALOGEN BULBS**  
12V 55W for car spot lights, projectors, etc.  
50p each. P. & P. 5p.

**GPO EXTENSION TELEPHONES**  
with dial but without bell. 95p each. P. & P. 30p.  
£1.75 for 2. P. & P. 50p.

**BARGAIN RELAY OFFER**  
Single pole change over silver contacts 25V to  
50V. 2.5k coil. 8 for 50p. P. & P. 5p.

**KEYTRONICS mail order only**  
**44 EARLS COURT ROAD**  
**LONDON, W.8 01-478 8499**

**EX-RENTAL TV's (UNTESTED)**  
Complete with 13 channel tuners. Good cabinets.  
Carriage £1.50 extra.  
19"/21" slimline (110° tube) .. £5-00  
23" slimline .. .. £7-50  
19" BBC 2 sets .. .. £14-50

**TUBES EX EQUIPMENT (Tested)**  
**SINGLE PANEL**  
19"/21" any type .. .. £3-00  
23" any type .. .. £4-00  
**TWIN PANEL (BONDED)**  
19" bonded .. .. £5-00  
All tubes add £1 carriage.

**VALVES EX EQUIPMENT**

*EF91	5p	30L15	12½p	PL36	22½p
EBF89	12½p	30P4	12½p	PL51	17½p
ECC82	12½p	PC97	17½p	PY81	16p
EC180	7½p	PCF86	17½p	PY800	16p
EF80	12½p	PC84	7½p	PY82	7½p
EF85	12½p	PCF80	7½p	PY33	22½p
EF183	12½p	PCF89	12½p	U191	17½p
EF184	12½p	PCF85	22½p	6P23	17½p
EY86	17½p	PCF82	17½p	30PL1	22½p
30PL13	20p	PCF86	17½p	30P12	20p
630LZ	12½p	PCL83	12½p	30F5	8p

Add 2½p per valve p. & p., orders over £1 p. & p. free

**UHF TUNERS**

For Ferguson 850 900 chassis. Adaptable for most UHF  
Chassis £2.50. p. & p. 50p.

**SLOT METERS**

Smiths reconditioned switchmaster MK III. Decimalized.  
Perfect working order. 12 for £25 delivered. For sample  
send £2.80 c.w.o.

**TRADE DISPOSALS**  
**(Dept. PW/TS)**

Thornbury Roundabout, Leeds Rd., Bradford.  
Telephone 0274/686870

**BELLING LEE INSULATED TERMINALS.** Red or  
Black, 5 amp. max. 10p pair, pp 3½p

**BERCOSTAT WIREWOUND RHEOSTAT.** 50 volt,  
800 Ω 25 watts, 2" dia. 25p. pp 7½p.

**FINED ALUMINIUM HEATSINK** 9" x 1½", Ready  
Drilled. 20p. pp 6½p

**SMITHS CIRCULAR TAPE POSITION INDICATORS**  
Resettable, 60p. pp 5p.

**G.E.C. 5 AMP 240 VOLT A.C. CIRCUIT BREAKER.**  
75p. pp 10½p.

**SUB MIN CROC CLIPS.** Red or Black, insulated 4p.  
Min. quantity, 6 pp 3½p.

**GARRARD MAG TAPE DECKS:** 1½ips, 50v solenoid  
operated brakes etc. Mains voltage motors £7-50  
each, pp £1-23.

**4½" PLANNAIR FANS.** Complete, capacitor, ex-  
equip. 2,800 r.p.m. £3-50, pp 40p.

**ELECTRIC MOTORS, HOOPER OR CROMPTON**  
**PARKINSON.** 250v. Single Phase A.C.  
½ h.p. 1,440 r.p.m. £3-75 pp £1-00  
¼ h.p. 1,425 r.p.m. or 2,800 r.p.m. £6-75  
pp £1-25  
½ h.p. 1,440 r.p.m. £2-25 pp 75p

**AUDIO CONNECTORS**  
3 pin Din Plug .. .. 18p each  
5 pin Din Plug A type, B type .. 18p ..  
2 pin Din Speaker Plug/socket .. 10p ..  
3 pin Din Line Socket .. .. 18p ..  
3.5mm Jack Plug Screened .. .. 10p ..  
Standard Jack Plug .. .. 10p ..  
Screened Standard Jack Plugs .. 16p ..  
Stereo Jack Plug .. .. 18p ..  
Screened Stereo Jack Plug .. .. 18p ..

**Phono Plugs:** Red or Black 3p each.  
pp on above items 3½p.

**B.S.R. MINI AUTO-CHANGER**  
Mono Cartridge £4-75 pp 30p.

**MAINS NEONS.**  
Red or Green. Size: ½" x 1½" 15p, pp 3½p.  
**LEVER ACTION P.O.1000 TYPE SWITCHES.**  
Lock 4-pole changeover 16p, pp 3½p. (ex-equip.)  
Lock 2 Pole Changeover 10p pp 3½p. (ex-equip.)

**AUDIO LEADS**  
Screened Phono Leads 46" long, 15p  
3-5 mm JACK/3-5mm JACK 7' 6" long 40p  
5-Pin Din A Type, 5-PIN A TYPE. Approx 6½' long  
70p. pp above items 5½p.

**PIEZO DYNAMIC MICROPHONE**  
60kΩ £1-00 pp 8p.

**MULTI-PIN SCREW TERMINAL CAPACITORS.**  
4,500 uf 63V 7100 uf 40v. 50p each pp 10p.

**BELLING LEE 15 amp. in-line rubber covered**  
interference suppressor 25p pp 8p.

**RUBBER 3 PIN 5 AMP NON REVERSIBLE CABLE**  
**CONNECTORS** 20p pp 5½p.

**SOLENOIDS 12 VOLT PULL ACTION**  
2" x 1" x 1" 40p pp 8p.

**SIEMENS MINIATURE RELAY.** Double pole  
changeover dust cover/base 48v 2500 50p pp 8p new.

**OMRON MK2 MIDGET POWER RELAY.** 12v DC  
Double pole Changeover. New. 70p pp 8p.

**SETC MINIATURE RELAY** 280 Ω Perspex Cover  
6-15v new, 35p pp 5p.

**GARDNER'S POTTED TRANSFORMER** 0-250v  
Input: 18v 500mA/50 150 mVA, 6v 250 mVA Output.  
Size 3" x 2½" x 2½", £1-00, pp 20p. Ex equip tested.

**TELESCOPIC AERIALS**  
Chromed 7" closed 28" extended 6 section ball  
jointed base 23p pp 8p new.

**MULLARD 4 DM 180 INDICATORS** in plastic  
holder/cover ex-equip. size approx. 1½" x 1½" x 1½"  
36p pp 8p.

**PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200**  
Diodes: 1 reed relay: 1 AZ 229 zenner ass. capacitor/  
resistors. Power supply 22v 250 mVA DC. Output  
240v. AC £1 pp 20p ex-equip.

**TOGGLE SWITCHES.** Single pole Double Throw  
ex-equip. new condition. 50p doz. pp 13p.

**PAINTON PLUG SOCKETS** Type 159 series working  
voltage 350v AC/DC current max. 3 amp AC/DC  
7 pin plug & socket 50p pp 6p. 15 pin plug & socket  
£1 pp 6p. 31 WAY PLUG & SOCKET. £1-50.  
pp 6p.

CASH WITH ORDER PLEASE

**FIELD**  
**ELECTRIC**  
**LIMITED**  
**3 Shenley Road,**  
**Borehamwood, Herts.**  
**Adjacent Elstree Mainline Station**  
**Tel: 01-953 6009.**

**GOING BACK** —continued from page 638

They are about 2½ in. diameter and constructed from aluminium. We have persuaded the great "PAX" of "Practically Wireless" fame to switch off his vintage Hawaiian 78's for a moment and do a sketch to show how Mr. Wallace's headphones look.

If you have any information on these, please send it to Mr. Wallace at 3 Woodside Avenue, Kilmarnock, Ayrshire, Scotland.

Miss C. Crabb writing from Bournemouth, Hampshire, tells us that she recently unearthed the receiver and speaker shown in the photographs.


The receiver was licensed under the Marconi patent and has reactance tuning. The grid bias battery is fitted inside the cabinet.



Miss C. Crabb's horn loudspeaker

Miss Crabb asks if this equipment is of any value as a curio or as a collectors' item.

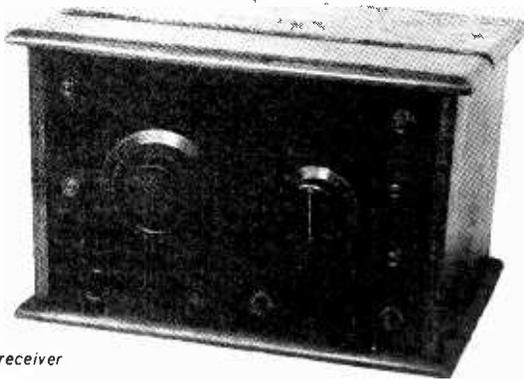In answer, we can only stress once more that equipment of this vintage (and indeed any equipment pre-1930) is certainly worth hanging on to. Collectors would put a value on it and even the person wanting such an item as just a "curio to put on the shelving in the lounge" would possibly be prepared to offer a reasonable sum.



The receiver

If any other readers have any information on this receiver and would care to write to us, we will be pleased to pass on the information to Miss Crabb.

## Vintage Record Bazaar

We would like to thank readers who have written in letting us know of their old gramophone records and equipment. We hope to run an article in a future issue on early gramophones, and will find the information you have provided will help us greatly in our project.

Readers may also be interested to know that the 5th annual Vintage Record Bazaar will be held on Saturday, Oct. 14th, at St. Silas Hall, 74 Penton Street, Islington, London, N.1.

The first two of these record sales, five years ago were held in conjunction with vintage car rallies, there being 15 record stalls.

This year, there will be 50 stalls with over 30,000 vintage records on sale. Vintage post cards will also be in evidence if you are interested in collecting them. In addition, there is a strong possibility that there will be some vintage radio equipment there!

The Bazaar is open from 10 a.m. to 5 p.m. and admission is 25p.

If anyone would like any further information on the Vintage Record Bazaar, phone John Carter (Shurlock Row) 539, or if you are phoning from London, 0735-81-539.

**ELECTRONOTES**—continued from page 625

the physical properties of the medium at various depths.

These points are important since the acoustic signal pulsed out by the transmitter in an "active" system could be diffracted in a curved path and thus there would be certain completely blind areas.

The thermal profile of the water at various depths can be quite a complex thing. This profile will alter daily being dependant upon the day to day variation of the solar activity of the sun. Again, winds and rain cause a mixing action which is yet another variable.

We have barely scratched the surface of this fascinating subject. However, it appears that we have a long time to wait before some boffin comes up with a useful sonar device for the accurate location of the soap in murky bath water. Or does some reader just happen to have a practical circuit handy?

### CHASSIS and CASES by



**H. L. SMITH & CO LTD**  
287/9 Edgware Road  
London W2 1BE  
Telephone: 01-723 5891

### BLANK CHASSIS

FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6x4x2"	34p	17p	10x8x2½"	66p	30p
7x4x1½"	33p	18p	12x7x2½"	66p	33p
7x5x2"	40p	19p	12x9x2½"	76p	38p
8x4x2"	38p	19p	13x8x2½"	76p	38p
8½x5½x2"	44p	21p	14x7x3"	80p	36p
9x7x2"	50p	26p	14x10x2½"	88p	47p
10x4x2½"	50p	21p	15x10x2½"	92p	50p
12x4x2½"	55p	22p	17x10x3"	£1.10	55p
12x5x3"	66p	26p			

Plus post and packing


### CASES

ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
N	8x6x2"	£1.00	W	12x7x7"	£2.50
N	6x6x3"	£1.05	W	15x9x8"	£3.15
N	4x4x2"	80p	Y	8x6x6"	£2.25
U	4x4x4"	95p	Y	12x7x7"	£2.80
U	5½x4½x4½"	£1.15	Y	13x7x9"	£3.15
U	8x6x6"	£1.45	Y	15x9x7"	£3.35
U	9½x7½x3½"	£1.55	Z	17x10x9"	£4.15
U	15x9x9"	£3.00	Z	19x10x8½"	£4.35
W	8x6x6"	£1.90			

\*Height

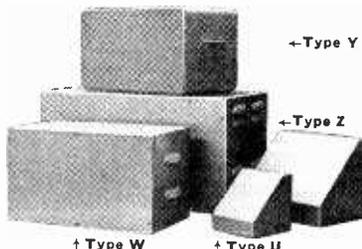Type N has removable bottom. Type U removable bottom or back. Type W removable front. Type Y all screwed construction. Type Z removable back and front. Plus p.& p.



### TO FIT OUR CASES

7x5½x1½"	38p	21p	12x6½x2"	60p	33p
7x5½x2"	43p	21p	14x8½x2"	74p	44p
11x6½x1½"	48p	30p	15½x9½x2½"	94p	52p
11x6½x2"	55p	30p	17½x9½x2½"	£1.05	59p

Plus post & packing

PANELS: Any size up to 3ft. at 36p sq. ft. 16 s.w.g. (18 s.w.g. 32p) Plus postage and packing

**NOTES**

Although component layout is unimportant two details *must* be observed. The voltage across C1 must be less than 36V before the i.c. is inserted into the circuit. If the voltage across C1 exceeds 36V this voltage can be reduced by altering the tapping of the transformer. Secondly it should be noted that the output power transistor will, under current limiting conditions, have to dissipate about 40W. An adequate heat sink for this component must be provided, the chassis of the supply being used for this

★ **components list**

R1 2kΩ ½W 5%	R2 560Ω ½W 5%	
R3 0.5Ω 3W wirewound	R4 1.5kΩ ½W 5%	
VR1 10kΩ skeleton preset potentiometer		
C1, C2 2500µF 40VW minimum. C3 0.01µF		
Tr1 2N3055	Tr2 2N3704	Tr3 2N3704
D1-4 3A silicon rectifiers or bridge		
D5 BZY88C9V1 (9-1V 400mW)		
D6 BZY88C6V2 (6-2V 400mW)		
ICI µA741C T1 230V/24V 1.5-2A		

Red and black insulated terminals. Neon lamp and holder 230V. Fuses 2.5A and 1A with holders. Meter 50VDC. Mains input plug and socket. On-off switch. Case and chassis. Veroboard 4½ x 4in.

The components list above applies only to the variable voltage supply. The veroboard used in the prototype has pins fitted which plug into a chassis mounted socket.

purpose. The transistor is however electrically isolated from the chassis by using a greased mica washer and bushes. Although no other difficulties should arise it is recommended that the semiconductors, and especially the i.c. should be guaranteed to be to the full specification. Providing all these precautions are taken the supply should prove to be completely reliable. ■

**MAXWELL**

by G8DSH



"I should like to introduce you to the wife of our Stereo expert!"

**CO! CO! CO! CO! CO!**

**BOOKS WANTED**

...buy or borrow any books on crystal radios, and extremely simple translator amplifiers or radios; also any useful circuits.—B. Ewing, 25 Water Lane, Seven Kings, Ilford, Essex.

**ISSUES FOR DISPOSAL**

...most copies of P.W. 1960-1970 inclusive for sale.—E. Dale, 2 Fordham Square Sunderland SR5 0BB.  
 ...the following volumes of P.W. Vol 42 (May 1966—April 1967), vol 43 (May 1967—April 1968), Vol 44 (April 1968—May 1969), Vol 45 (May 1969—April 1970) at 75p per vol postage included.—C. Butler, 81 Rutland Avenue, Southend-on-Sea, Essex.  
 ...Practical Wireless 1948-1965 and Practical Television 1950-1964. Offers to J. Skelly, 8 Sylvia Avenue, Hutton, Brentwood, Essex.  
 ...full issues for 1967-1968-1969-1970 and 1971 in mint condition, for which I will accept the best offers, plus postage.—L. J. Bellingham, Woodside, Red Lane, Limpfield, Surrey.  
 ...P.W. 1962-1964 (inc) Feb 1962, May 1963, Sept. 1964 missing. P.E. Nov 1964-Apr. 1966 with Vol. 1 binder. Offers to C.J. Barrett, 13B Millers Road, Brighton, BN1 5NP.  
 ...issues of P. W. June 1969—March 1972 all in good condition. Offers please to.—M. Wolock, October Cottage, Station Road, Eynsford, Kent.  
 ...P.E. from Oct 1959—Dec. 1971, sell at cover price & P & P, any reasonable offers accepted.—S. Smith, Ardaros, Main Street, Polmont, Falkirk.  
 ...many P.W. and P.E. from 1964 on.—A.G. Hodgett, 3 Ely Way, Fellgate, Co Durham.  
 ...approx 85 P.W. 1962-1969 also most blueprints. Few P.W., 1949-1950, 1958, 1960, 1961, 17 in all, approx 100 PT 1952-1963. Most Short Wave Mag, 1963-1967 Offers.—M. Blackburn, 107 St. Paul's Road, Jarrow, Co. Durham.  
 ...P.W. Feb. 1970—May 1972, also Jul. 1969—Jan. 1970.—P. Dunn, 3 Tassie Place, East Kilbride, G74 3EB.  
 ...various dates: P.Ts. 1959-1965, P.Ws. 1968-1971 P.Es 1965-1968, P.W. 21st ANN; Oct. 1953, (1) "Wireless Constructor" 1931.—S.W. Owen Bryngwynedd, Rhiw, Blaenau, Ffestiniog, Merionethshire.  
 ...complete Vol. P.W.—1969-1970 & 1971 complete Vol. R. Communication 1969 & 1970. Also P.W. April—Dec. 1968.—V. Simpson, 107 Derryhale Road, Portadown, Co. Armagh, NI.  
 ...I have the following issues for disposal Feb, Apr—Jun, Aug, Oct, Nov, 1967, Mar—Jun, Aug, Sep, Nov, Dec. 1968, Jan., Feb., May 1969, Feb.—May, Oct, 1970 Aug. 1971 and 2 each Jul. 1967, 1968 of P.W. Jun. 1966, Jun. 1967, Dec., 1967, Jan., Apr.—Aug., Nov., Dec. 1968, Mar. 1969, Feb., Mar., Nov. 1970, Feb. Mar., Aug. 1971 2 each Jul., Aug. 1967 and Mar. 1968 of P.E. 1 issue of Television Aug. 1971, Jul., Sep. 1970, Mar.—Nov. 1971 of Radio Constructor.—R. H. K. Grayson, 34 Victoria Road, Haywards Heath, Sussex, RH16 3LY.  
 ...Most of P.W. from 1960. Radio Communication from 1968. Wireless World—1959/1960/1961. S.A.E. list.—R. Forsberg, 123 Harestone Hill, Caterham, Surrey, CR3 6DJ.  
 ...P.W. 1958 onwards, Rc 1951-1957 Bound, also RC 1958-Sept. 1965, and Dec 1968 Aug. 1970.—G. F. Allan, 21 Borrowdale Close, Redbride, Ilford.  
 ...the following issues of the Practical Wireless. Volume 43. Dec. 1967 missing. Volume 44 complete. Volume 45 April 1970 missing, and October 1970 to March 1971 inclusive. All for disposal.—R. Grant, 27 Campbell Crescent, Laurieston, Falkirk, Stirlingshire.  
 ...most issues of P.W., P.T., P.E., and short wave mags available at cover price, please include S.A.E. also PCB's (miniature) 10p and most radio/TV spares. S.A.E. for list.—J. K. Nicholson, 38 Graham Road, Bicester, Oxon.  
 ...I have for disposal many issues of P.W. and short Wave Mag. from 1966 to 1970 all in as new condition. S.A.E. for details.—G. W. Norris, 69 Hillside, Stowmarket, Suffolk.  
 ...I have for disposal the following issues of PW. Mar. Aug. 1967, Apr., Jul., Aug., Oct., Dec. 1968 Jan., Feb., Apr., May, 1969, Oct., Dec. 1970.—H. Ferns, 11 King Street, Coatbridge, Lanarkshire, Scotland.

**CORRESPONDENTS WANTED**

...wanted to correspond; Someone of my own age (17). Interested in Electronics and Modern Music.—P. Richards, 7 Holwood Drive, Whalley Park, Manchester M16 8WS.  
 ...girl or boy of my own age (14) to correspond or tapesound with. I have a Prinz-sound TR-S 1 7/8 cassette recorder and a Ferguson 3 2 and 1 ½ spool recorder with 4 tracks. I am interested in electronics and SWLing.—K. Goldsworthy, 165 Ellerdine Road, Hounslow, TN32PV.  
 ...boy or girl of my own age (16). Anyone who is interested in TX circuits and short wave listening.—P. Jenkins, 30 Gainsborough Road, North Finchley, London, N12 8AG.  
 ...anyone who is interested in offshore radio and radio equipment to correspond. Aged 18-24.—P. Leach, The Post Office, Snodland, Kent.  
 ...Either sex of my own age (24). I have a four track Izlow AKAL stereo tape recorder and interested in modern music, radio electronic, and pen friendship.—M. Ekramul Haque, BBC eastern relay station, BFPO 65, Via London.  
 ...boy or girl of my own age (13) interested in Radio and Electronics.—D. Thorpe, 161 Tomswood Hill, Hainault, Ilford, Essex.  
 ...girl or boy (16-19) living abroad; to write or tapesound (Philips Cassette). I am a boy (18) with interests; short-wave listening, cars, all music. I am studying electrical engineering. Speaks English, also French and German (badly!).—J. V. Moss, 4 Gilbert Close, Rayleigh, Essex, England.  
 ...anyone of about my age, 17, interested in amateur radio and S.W.L.—P. Jenkins, 30 Gainsborough Road, North Finchley, London, N12 8AG.  
 ...I would be delighted to correspond with any radio constructor from England, of my own age (25).—K. H. E. Perera, 352 Kerawalapitiya, Hendala, Wattala, Ceylon.  
 ...girl of my own age (almost 13) interested in Electronics and pop music.—L. Cox, Ford Bank Cottage, Victoria Avenue, Didsbury, M20 8RA.  
 ...I would like to correspond with radio constructors from England, of my own age (18) S.A.M. P. Ratnayaka, no 330 Rajamah Vihara Road, Mirihana, Pita-Kotte, Ceylon.  
 ...anyone in Australia preferably in the Electronic trade. With a view to settling in Australia. Age 24.—M. Yambo, 13 Chamberlain Gardens, Arborfield, Reading, Berks.  
 ...Anyone interested in sending me Radio parts against anything of equal value from India.—S. Khaitan, 25/1 Rowland Road, Calcutta 20, W. Bengal, India.

**TAPESOUNDERS WANTED**

...boy aged 20 request for pals of both sexes. Interest: Electronics, Music.—D. Peters, Liverpool Street, P.O. Box 6, Eket, S. East State of Nigeria.  
 ...boy or girl 15-18. Cassette or open reel catering for. My interests include music, tape recording (I) and electronics. Please write stating interests, recording equipment etc.—M. Tillman, 86 Chestnut Drive, Pinner, Middlesex. HA5 1LZ.

**EQUIPMENT FOR DISPOSAL**

...a lot of miscellaneous components for sale: valves, resistors, capacitors, pots, etc. Any offers? Please enquire!—J. P. Fletcher, Rendcom College, Cirencester, Glos. GL1 7EZ.  
 ...Magnavox 363 tape deck + plinth with record and erase heads. Unused £15.—P. Dunn, 3 Tassie Place, East Kilbride, HTL 3EB.  
 ...Ferrograph/3CFN/X tape recorder for sale, good running order. Any offers.—S. G. Parsons, 7 Randolph Terrace, Stirling, FK7 7AB.  
 ...FOR SALE: Five old valves (from Portadown 230 radiogram) all in good condition, probably working. All marked very clearly. 5, 6, 7, & 8 pin bases. Any offers.—M. Baldwin, 8 Oakcroft Road, London, SE13 7ED.  
 ...Offers asked for pair air, sea rescue sets & circuits, still in tack.—C. G. Farrimond, 65 Broomfield Avenue, Hasland, Chesterfield, S41 0LY.

**APPARATUS REQUIRED**

...Baird 620/640 D complete or time base panel, any condition.—W. Woodham, 13 Wallasey Crescent, Ickenham, Uxbridge, Middlesex.

# INCREASE YOUR KNOWLEDGE



Established 1891



**MANY COURSES TO CHOOSE FROM** incl.  
 RADIO & TV ENGINEERING & SERVICING,  
 TRANSISTOR & PRINTED CIRCUIT SERVICING,  
 COLOUR TV SERVICING, ELECTRONICS,  
 NUMERICAL CONTROL, ELECTRONICS,  
 TELEMTRY TECHNIQUES, CONTROL SYSTEMS,  
 ELECTRONICS FOR AUTOMATION,  
 COMPUTERS, ETC.

**ALSO EXAMINATION COURSES FOR**

C. & G. Telecommunication Technicians' Certificates  
 General Radio Communications Certificate  
 Radio Amateurs' Examination  
 General Certificate of Education, etc.

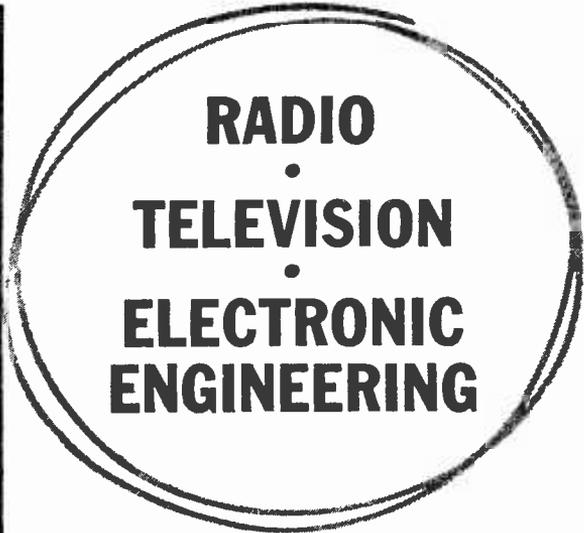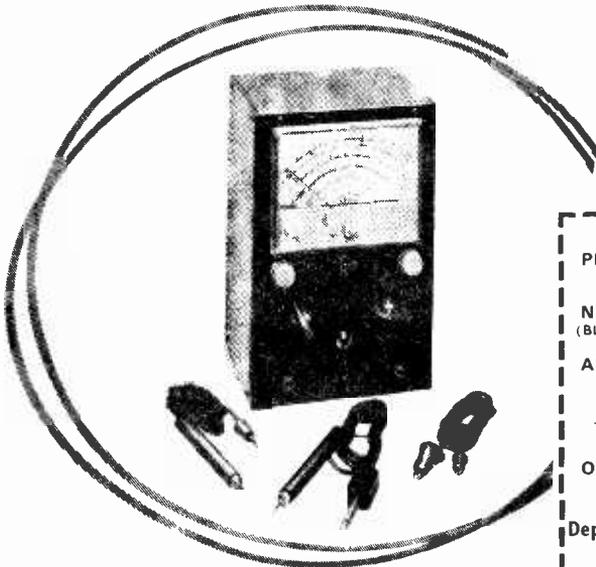**BUILD YOUR OWN RADIO AND INSTRUMENTS**

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



**RADIO  
TELEVISION  
ELECTRONIC  
ENGINEERING**

MEMBER OF THE ASSOCIATION  
 OF BRITISH CORRESPONDENCE COLLEGES

C & G Radio Servicing Theory

## THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

**FILL IN AND POST THIS COUPON TODAY**

You will receive the **FREE ICS Prospectus** listing the examination and ICS technical courses in radio, television and electronics PLUS details of over 150 specialized subjects.

Accredited by the CACC.

PLEASE SEND FREE BOOK ON .....

NAME .....  
 (BLOCK CAPITALS PLEASE)

ADDRESS .....

.....

OCCUPATION ..... AGE.....

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
 Dept. WA28, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8 4UJ.

# BIG CASH SAVINGS on partridge equipment when you order TRIO—

BUY NOW BEFORE V.A.T. & THE ADVANCING YEN PUT A PREMIUM ON YOUR PLEASURE!

## PARTRIDGE PACKAGE NO. 1

9R59DS receiver	£49.50
Matching headphones	FREE
JOYSTICK VFA 1972 Model	FREE*
JOYMATCH 111 or 111A	£11.00
8ft feeder, insulators, P/P, Insurance	FREE
Complete Receiving Station	£60.50

## PARTRIDGE PACKAGE NO. 3

JR 599 receiver	£185.00
Matching headphones	FREE
JOYSTICK VFA 1972 model	FREE*
JOYMATCH 111 or 111A	FREE*
8ft feeder, insulators, P/P, Ins.	FREE
Complete Receiving Station	£185.00

## PARTRIDGE PACKAGE NO. 2

JR 310 receiver	£75.00
Matching headphones	FREE
JOYSTICK VFA 1972 model	FREE
JOYMATCH 111 or 111A	£7.00*
8ft feeder, insulators, P/P Ins.	FREE
Complete Receiving Station	£82.00

## PARTRIDGE PACKAGE No. 4

TS/PS 515 Transceiver	£210.00
Matching headphones	FREE
JOYSTICK VFA 1972 Model	FREE*
JOYMATCH LO-Z500 ATU	FREE*
8ft feeder, insulators, P/P, Ins.	FREE
Complete TX/RX Station	£210.00

### \*PACKAGE REDUCTIONS ON PARTRIDGE SYSTEMS

9R59DS PLUS HIGH QUALITY, LIGHTWEIGHT MATCHING HEADPHONES £57.50 DELIVERED

TRIO LINEAR TL911 £140.00; MATCHING HEADPHONES £2.40 (+20p); TRIO TR71002M. CAR TRANSCIVER £99.50; TRIO TR22002M Personal transceiver £69.95; CW filter (for TS515) £14.00; 10AZ filter (for JR310) £7.34; 100KHz (Calibration Crystal) £3.18; OAZ (Mains Stabiliser) £0.67; B1016L P.T.T. HAND MIC. (for TS515) £3.38.

PARTRIDGE JOYSTICK VFA's: 1072 Model £11.00 (+40p); 1971 Model £8.00p (+40p); Indoor model £7.00 (+40p); JOYMATCH ATU's—111 and 111A (£11.00 (+40p); LO-Z500 £16.00 (+45p).

#### PARTRIDGE BUDGET LINE:—

DUAL PURPOSE ARTIFICIAL EARTH/AERIAL BANDSWITCH (complete Aerial & ATU system, or Artificial Earth—your choice) £4.50 (+30p); TRIPLE PURPOSE 6 BAND ATU in KIT FORM (6 amateur and 11 BC bands) £4.50 (+30p); TRIPLE PURPOSE 6 BAND ATU assembled £5.50 (+30p); CARRIAGE AND INSURANCE EXTRA FOR OVERSEAS ORDERS.

Send 3p stamp for full illustrated details of Partridge products.

TRIO leaflets on request.

## BOX 5, PARTRIDGE ELECTRONICS LTD, BROADSTAIRS, KENT

Phone: 0843 62535—Cheap periods 0843 62839 for advice and COD orders.

# ELECTRONIC VALVES

DY86	0.23	PC97	0.36	PY83	0.26
DY87	0.23	PCC84	0.28	PY500	0.95
EABC80	0.30	PCC89	0.43	PY800	0.32
EB91	0.09	PCC189	0.47	PY801	0.32
ECC81	0.15	PCF80	0.27	UABC80	0.30
ECC82	0.18	PCF86	0.44	UCC85	0.34
ECC83	0.24	PCF802	0.38	UCH81	0.30
ECL80	0.25	PCF806	0.56	UCL82	0.31
EF80	0.22	PCF808	0.68	UL41	0.54
EF85	0.26	PCL82	0.30	UY85	0.24
EF86	0.28	PCL83	0.55	6/30L2	0.58
EF89	0.23	PCL84	0.33	6AT6	0.18
EF91	0.12	PCL85	0.37	6AU6	0.20
EF183	0.26	PCL86	0.37	6BA6	0.20
EF184	0.28	PFL200	0.51	6BE6	0.21
EH90	0.35	PL36	0.47	6F23	0.67
EL41	0.53	PLB1	0.43	12AT6	0.23
EL84	0.22	PLB2	0.29	12AT7	0.15
EY51	0.30	PLB3	0.31	12AU7	0.18
EY86	0.28	PLB4	0.29	12AX7	0.24
EZ80	0.20	PL500	0.61	12BA6	0.30
EZ81	0.21	PL504	0.61	12BE6	0.30
PC86	0.45	PY81	0.23	35W4	0.23
PC88	0.45	PY82	0.24	50C5	0.32

POSTAGE: 1 VALVE 5p, EACH ADDITIONAL VALVE 1p. ORDERS OVER £5 POST FREE. CASH WITH ORDER ONLY.

Quotations for any type not listed send SAE.

NO CALLERS. ALL VALVES GUARANTEED AND INDIVIDUALLY BOXED.

EXPRESS MAIL ORDER

SEND TO —

ARCHES 1150/1152  
41 NORWOOD RD., LONDON, S.E.24

VYNAIR  
TYGAN  
ACOUSTIC  
WADDING

PLUS  
USUAL  
SPEAKER  
SUNDRIES

SEND NOW FOR OUR ILLUSTRATED  
CATALOGUE and SAMPLES 10p (Refundable)

## STUBEC AUDIO (DEPT.) (PW)

24 GYBBON RISE  
STAPLEHURST, TONBRIDGE, KENT

NEW RANGES OF VYNAIR  
& TYGAN NOW IN STOCK

## WILSIC SOUND EFFECTS KITS

### WAH-WAH PEDAL KIT (Illustrated)



Kit comprises a SELECTIVE AMPLIFIER MODULE KIT to convert the FOOT VOLUME CONTROL PEDAL (as photo) to Wah-Wah operation. Amplifier module £1.75, pedal unit £5.13, COMPLETE KIT £6.50 add 38p for assembly of module, but please note we cannot supply kits fully built.

REVERBERATION UNIT KIT. For dimension effect. Connects between sound source, mic., etc., and amplifier. Battery powered. COMPLETE KIT £9.50 (excluding case £7.50). Assembled and tested £12.50.

VIBRATO UNIT KIT. Foot pedal unit with variable speed and depth controls. COMPLETE KIT £5.25.

SEND 15p for the WILSIC PLANS BOOK, with full details of these kits; circuits, drawings and price lists.

LATEST CATALOGUE 5p (stamps)

WILSIC ELECTRONICS LTD.  
6 COPLEY ROAD, DONCASTER, YORKS.

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS! CLEAR PLASTIC METERS

**TYPE SW.100**  
 100 x 80 mm.



50μA	20V. D.C.	\$3-40	50V. D.C.	\$3-40
50-0-50μA	300V. D.C.	\$3-40	300V. D.C.	\$3-40
100μA	1 amp. D.C.	\$3-40	1 amp. D.C.	\$3-40
100-0-100μA	5 amp. D.C.	\$3-40	5 amp. D.C.	\$3-40
500μA	300V. A.C.	\$3-40	300V. A.C.	\$3-40
1mA	VU Meter	\$4-15		

**BAKELITE PANEL METERS**  
 TYPE S-80  
 80 mm.  
 square fronts



50μA	200mA	\$2-50	50V. D.C.	\$2-85
50-0-50μA	300mA	\$2-40	300V. D.C.	\$2-85
100μA	500mA	\$2-40	500V. D.C.	\$2-85
100-0-100μA	750mA	\$2-30	1 amp. D.C.	\$2-85
500μA	1 amp.	\$2-05	5 amp. D.C.	\$2-85
1mA	2 amp.	\$2-85	300V. A.C.	\$2-85
20V. D.C.	2 amp.	\$2-85	VU Meter	\$3-70

## "SEW" CLEAR PLASTIC METERS

**Type MR.35P. 4 1/4in. x 4 1/4in. fronts.**




50μA	100mA	\$2-10	100mA	\$2-10
50-0-50μA	500mA	\$2-10	500mA	\$2-10
100μA	1 amp.	\$2-10	1 amp.	\$2-10
100-0-100μA	5 amp.	\$2-10	5 amp.	\$2-10
200μA	15 amp.	\$2-10	15 amp.	\$2-10
500μA	30 amp.	\$2-10	30 amp.	\$2-10
1mA	20V. D.C.	\$2-10	20V. D.C.	\$2-10
10-0-1mA	50V. D.C.	\$2-10	50V. D.C.	\$2-10
8mA	300V. D.C.	\$2-10	300V. D.C.	\$2-10
10mA	15V. A.C.	\$2-10	15V. A.C.	\$2-10
	300V. A.C.	\$2-10	300V. A.C.	\$2-10
	8 Meter 1mA	\$2-15	8 Meter 1mA	\$2-15
	VU Meter	\$2-85	VU Meter	\$2-85
	1 amp. A.C.*	\$2-10	1 amp. A.C.*	\$2-10
	10 amp. A.C.*	\$2-10	10 amp. A.C.*	\$2-10
	20 amp. A.C.*	\$2-10	20 amp. A.C.*	\$2-10
	30 amp. A.C.*	\$2-10	30 amp. A.C.*	\$2-10

**Type MR.38P. 1 21/32in. square fronts.**




50μA	200mA	\$1-75	200mA	\$1-75
50-0-50μA	300mA	\$1-75	300mA	\$1-75
100μA	500mA	\$1-75	500mA	\$1-75
100-0-100μA	750mA	\$1-75	750mA	\$1-75
200μA	1 amp.	\$1-75	1 amp.	\$1-75
500μA	2 amp.	\$1-75	2 amp.	\$1-75
1mA	5 amp.	\$1-75	5 amp.	\$1-75
1-0-1mA	10 amp.	\$1-75	10 amp.	\$1-75
2mA	15V. D.C.	\$1-75	15V. D.C.	\$1-75
5mA	20V. D.C.	\$1-75	20V. D.C.	\$1-75
10mA	100V. D.C.	\$1-75	100V. D.C.	\$1-75
20mA	150V. D.C.	\$1-75	150V. D.C.	\$1-75
50mA	300V. A.C.	\$1-75	300V. A.C.	\$1-75
100mA	500V. A.C.	\$1-85	500V. A.C.	\$1-85
150mA	8 Meter 1mA	\$1-85	8 Meter 1mA	\$1-85
	VU Meter	\$2-30	VU Meter	\$2-30

**Type MR.53P. 2 1/2in. square fronts.**

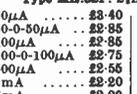


50μA	10V. D.C.	\$2-20	10V. D.C.	\$2-20
50-0-50μA	20V. D.C.	\$2-20	20V. D.C.	\$2-20
100μA	50V. D.C.	\$2-20	50V. D.C.	\$2-20
100-0-100μA	150V. D.C.	\$2-20	150V. D.C.	\$2-20
500μA	300V. D.C.	\$2-20	300V. D.C.	\$2-20
1mA	15V. A.C.	\$2-20	15V. A.C.	\$2-20
5mA	300V. A.C.	\$2-20	300V. A.C.	\$2-20
10mA	8 Meter 1mA	\$2-20	8 Meter 1mA	\$2-20
50μA	VU Meter	\$2-50	VU Meter	\$2-50
100μA	1 amp. A.C.*	\$2-20	1 amp. A.C.*	\$2-20
500μA	5 amp. A.C.*	\$2-20	5 amp. A.C.*	\$2-20
1mA	10 amp. A.C.*	\$2-20	10 amp. A.C.*	\$2-20
5 amp.	20 amp. A.C.*	\$2-20	20 amp. A.C.*	\$2-20
5 amp.	30 amp. A.C.*	\$2-20	30 amp. A.C.*	\$2-20

**Type MR.45P. 2in. square fronts.**

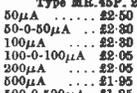

50μA	5 amp.	\$1-85	5 amp.	\$1-85
50-0-50μA	10V. D.C.	\$1-85	10V. D.C.	\$1-85
100μA	20V. D.C.	\$1-85	20V. D.C.	\$1-85
100-0-100μA	50V. D.C.	\$1-85	50V. D.C.	\$1-85
200μA	300V. D.C.	\$1-85	300V. D.C.	\$1-85
500μA	15V. A.C.	\$2-00	15V. A.C.	\$2-00
500-0-500μA	30V. A.C.	\$2-00	30V. A.C.	\$2-00
1mA	8 Meter 1mA	\$2-05	8 Meter 1mA	\$2-05
5mA	VU Meter	\$2-50	VU Meter	\$2-50
10mA	1 amp. A.C.*	\$1-85	1 amp. A.C.*	\$1-85
50mA	5 amp. A.C.*	\$1-85	5 amp. A.C.*	\$1-85
100mA	10 amp. A.C.*	\$1-85	10 amp. A.C.*	\$1-85
500mA	20 amp. A.C.*	\$1-85	20 amp. A.C.*	\$1-85
1 amp.	30 amp. A.C.*	\$1-85	30 amp. A.C.*	\$1-85

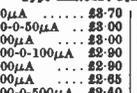**Type MR.55P. 3 1/4in. x 3 1/4in. fronts.**



50μA	10V. D.C.	\$2-40	10V. D.C.	\$2-40
50-0-50μA	20V. D.C.	\$2-40	20V. D.C.	\$2-40
100μA	50V. D.C.	\$2-40	50V. D.C.	\$2-40
100-0-100μA	150V. D.C.	\$2-40	150V. D.C.	\$2-40
200μA	300V. D.C.	\$2-40	300V. D.C.	\$2-40
500μA	15V. A.C.	\$2-55	15V. A.C.	\$2-55
500-0-500μA	50V. A.C.	\$2-55	50V. A.C.	\$2-55
1mA	150V. A.C.	\$2-55	150V. A.C.	\$2-55
5mA	300V. A.C.	\$2-55	300V. A.C.	\$2-55
10mA	8 Meter 1mA	\$2-60	8 Meter 1mA	\$2-60
50μA	VU Meter	\$3-70	VU Meter	\$3-70
100μA	50mA A.C.*	\$2-40	50mA A.C.*	\$2-40
1 amp.	100mA A.C.*	\$2-40	100mA A.C.*	\$2-40
5 amp.	200mA A.C.*	\$2-40	200mA A.C.*	\$2-40
10 amp.	500mA A.C.*	\$2-40	500mA A.C.*	\$2-40
15 amp.	1 amp. A.C.*	\$2-40	1 amp. A.C.*	\$2-40
20 amp.	5 amp. A.C.*	\$2-40	5 amp. A.C.*	\$2-40
30 amp.	10 amp. A.C.*	\$2-40	10 amp. A.C.*	\$2-40
50 amp.	20 amp. A.C.*	\$2-40	20 amp. A.C.*	\$2-40
5V. D.C.	30 amp. A.C.*	\$2-40	30 amp. A.C.*	\$2-40

## "SEW" BAKELITE PANEL METER

**Type MR.65. 3 1/2in. square fronts.**



25μA	1 amp.	\$2-15	1 amp.	\$2-15
50μA	5 amp.	\$2-15	5 amp.	\$2-15
60-0-50μA	15 amp.	\$2-15	15 amp.	\$2-15
100μA	30 amp.	\$2-15	30 amp.	\$2-15
100-0-100μA	50 amp.	\$2-15	50 amp.	\$2-15
500μA	5V. D.C.	\$2-15	5V. D.C.	\$2-15
500-0-500μA	10V. D.C.	\$2-15	10V. D.C.	\$2-15
1mA	20V. D.C.	\$2-15	20V. D.C.	\$2-15
1-0-1mA	50V. D.C.	\$2-15	50V. D.C.	\$2-15
5mA	150V. D.C.	\$2-15	150V. D.C.	\$2-15
10mA	300V. D.C.	\$2-15	300V. D.C.	\$2-15
50mA	30V. A.C.	\$2-15	30V. A.C.	\$2-15
100μA	50V. A.C.	\$2-20	50V. A.C.	\$2-20
100-0-100μA	150V. A.C.*	\$2-20	150V. A.C.*	\$2-20
500μA	300V. A.C.*	\$2-20	300V. A.C.*	\$2-20
500-0-500μA	500mA A.C.*	\$2-15	500mA A.C.*	\$2-15
1mA	1 amp. A.C.*	\$2-15	1 amp. A.C.*	\$2-15
5 amp.	5 amp. A.C.*	\$2-15	5 amp. A.C.*	\$2-15
10 amp.	10 amp. A.C.*	\$2-15	10 amp. A.C.*	\$2-15
20 amp.	20 amp. A.C.*	\$2-15	20 amp. A.C.*	\$2-15
30 amp.	30 amp. A.C.*	\$2-15	30 amp. A.C.*	\$2-15
50 amp.	VU Meter	\$3-40	VU Meter	\$3-40
100μA	50 MV D.C.	\$2-40	50 MV D.C.	\$2-40
500mA	100 MV D.C.	\$2-40	100 MV D.C.	\$2-40

**\*MOVING—IRON**  
**ALL OTHERS MOVING COIL**  
 Please add postage

## SEW EDUCATIONAL METERS

**Type ED.107. Size overall 100mm x 90mm x 108mm.**




A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible to demonstrate internal working. Available in the following ranges:

50μA	25-50	20V. d.c.	\$4-85
100μA	25-10	50V. d.c.	\$4-85
1mA	24-95	300V. d.c.	\$4-85
50-0-50μA	\$4-85		
1-0-1mA	\$4-85		
1A d.c.	\$4-85		
5A d.c.	\$4-85		
10V. d.c.	\$4-85		

Dual range  
 500mA/5A d.c. \$5-10  
 5V/50V d.c. \$5-10

## EDGWISE METERS

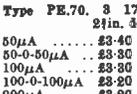**Type PE.70. 3 17/32in. x 1 15/32in. x 2 1/2in. deep**



50μA	500μA	\$2-05
50-0-50μA	1mA	\$2-70
100μA	300V. A.C.	\$2-70
100-0-100μA	VU Meter	\$3-75
200μA		

Send for illustrated brochure on ERW Panel Meters—discounts for quantities.


# MULTIMETERS for EVERY purpose!
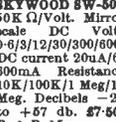
## ROUND SCALE TYPE PENCIL TESTER MODEL TS.68



Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V A.C. and D.C. at 2,000 ohm. Resistance 0-20K ohms. ONLY \$1.97 P. & P. 13p

**SKYWOOD SW-500**  
 50K Ω/Volt. Mirror scale DC Volt 0-6/3/12/30/120/800 VDC. DC current 20μA/8/60mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +87 db. \$7-50. P. & P. 15p.



**TMK LAB TESTER.**  
 100,000 O.P.V. 6 1/2in. Scale Buzzer Short Cir. cut Check Sensitivity: 100,000 O.P.V. D.C. 5K/Volt A.C. D.C. 250 Volts: 5, 2.5, 10, 50, 250, 500, 1,000V. D.C. Current: 10, 100μA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG. 10MEG Ω. Decibels: -10 to +49 db. Plastic Case with Carrying Handle. Size: 7 1/2in. x 6 1/2in. x 3 1/2in. \$18-50. P. & P. 22p



**TE22 SINE SQUARE WAVE AUDIO GENERATORS**



Line: 20cps to 200 kc/s on 4 bands. Square: 20cps to 30 kc/s. Output impedance 5,000 ohms, 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. \$17-50. Carr. \$7.7p.

**TE-20RF SIGNAL GENERATOR**  
 Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V. A.C. Brand new with instruction. \$15 P. & P. 37p.



**BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR**



New high quality portable instrument. Line 1 Hz to 100 kHz. Square 20 Hz to 20 kHz. Output max 10 dB (10 K ohms) Operation 220/240V. A.C. Size 215mm x 150mm x 120mm. Price \$27-50. Carr. 25p

**240° Wide Angle 1mA Meters**  
 MW1-6 60mm square \$23-7 1/2  
 MW1-8 80mm square \$4-97 1/2  
 P. & P. extra



**TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE**



A new portable bridge offering excellent range, accuracy and accuracy at low cost. Ranges: R. 1 Ω-11.1 meg Ω. 6 Ranges ± 1% L.I. μ H - 111 HENRYS 6 Ranges ± % C. 10Pfd ± 1110mPfd 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:1/100. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operated from 9 volts, 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 1/2in. \$20. P. & P. 22p

**280V/240V SMITHS SYNCHRONOUS GEARED MOTORS**




Built in gearbox. All brand new and boxed. 60 RPM CW; 30 RPH CW; 2R/HR ACW; 2R/HR CW; 8R/ DAY CW; 10 RPM CW; 20R/HR ACW. 50p each Post 12p.

**HIKOKI MODEL 720X**  
 20,000 O.P.V. Overload protection 5/25/100/600/1000 VDC. 10/50/250/1000 VAC. 50μA/250mA. 20K/2 meg. ohm. - 5 to + 62db. \$4-97. P. & P. 15p.



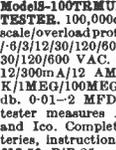**Models-100TRMULTIMETER/TRANSISTOR TESTER.** 100,000-p.v. mirror scale/overload protection. 0/12 /-8/3/12/30/120/800 VDC. 0/6/30/120/600 VAC. 0/12/600μA/12/300mA/12 AMP DC. 0/10 K/1MEG/100MEG. -20to+50 db. 0-0.1-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. \$13-50. P/P 25p.




**MODEL 500 30,000 O.P.V** with overload protection mirror scale 0/5/2-5/10/25 100/250/500/1,000V. D.C. 0/2-5/10/25/100/250/500/1,000V. A.C. 0/50μA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg/60 Meg Ω. \$4-97. Post paid.



**MODEL 5025 57 Ranges,** (Giant 3 1/2in. Meter, Polarity Reverse Switch. Sensitivity: 50K/Volt D.C. 5K/Volt A.C. D.C. Volt: -125, -25, 1-25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.C. Volt: 1.5, 3, 15, 25, 50, 125, 250, 500, 1,000V. D.C. Current: 25, 50μA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 2K, 10K, 100K, 1MEG, 10 MEG. Decibels: -20 to +85 db. \$12-50. P. & P. 17p.



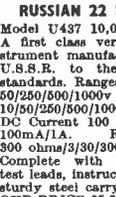**RUSSIAN 22 RANGE MULTIMETER**  
 Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V D.C. 2.5/10/50/250/500/1000V A.C. DC Current 100 μA/110/100mA/1A. Resistance 300 ohms/3/300K/3m Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$5-97 P. & P. 25p.



**TO-3 PORTABLE OSCILLOSCOPE**  
 3in. tube. Y amp. Sensitivity 0.1v p-p/cm. Bandwidth 1-5 cps-1.5 MHz. Input Imp. 2 meg Ω 25pF X amp. sensitivity 0.9v. p-p/cm. Bandwidth 1.5 cps-800KHz. Input Imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps-300 KHz. Synchronization. Internal/external. Illumination scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. \$40-00. Carr. 50p



# SEMI-CONDUCTOR VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3415	2N3416	2N3417	2N3499	2N3500
2N3415	2N3416	2N3417	2N3500	

Integrated Circuits	FJH111	FJH121	FJH131	FJH141	FJH151	FJH161	FJH171	FJH181	FJH221	FJH231	FJH241	FJH991	FJH1001
FJH111	FJH121	FJH131	FJH141	FJH151	FJH161	FJH171	FJH181	FJH221	FJH231	FJH241	FJH1001	

VALVES	6AU6	6BE6	6BE7	6BE8	6BE9	6BE10	6BE11	6BE12	6BE13	6BE14	6BE15	6BE16	6BE17	6BE18	6BE19	6BE20	6BE21	6BE22	6BE23	6BE24	6BE25	6BE26	6BE27	6BE28	6BE29	6BE30	6BE31	6BE32	6BE33	6BE34	6BE35	6BE36	6BE37	6BE38	6BE39	6BE40	6BE41	6BE42	6BE43	6BE44	6BE45	6BE46	6BE47	6BE48	6BE49	6BE50	6BE51	6BE52	6BE53	6BE54	6BE55	6BE56	6BE57	6BE58	6BE59	6BE60	6BE61	6BE62	6BE63	6BE64	6BE65	6BE66	6BE67	6BE68	6BE69	6BE70	6BE71	6BE72	6BE73	6BE74	6BE75	6BE76	6BE77	6BE78	6BE79	6BE80	6BE81	6BE82	6BE83	6BE84	6BE85	6BE86	6BE87	6BE88	6BE89	6BE90	6BE91	6BE92	6BE93	6BE94	6BE95	6BE96	6BE97	6BE98	6BE99	6BE100
6AU6	6BE6	6BE7	6BE8	6BE9	6BE10	6BE11	6BE12	6BE13	6BE14	6BE15	6BE16	6BE17	6BE18	6BE19	6BE20	6BE21	6BE22	6BE23	6BE24	6BE25	6BE26	6BE27	6BE28	6BE29	6BE30	6BE31	6BE32	6BE33	6BE34	6BE35	6BE36	6BE37	6BE38	6BE39	6BE40	6BE41	6BE42	6BE43	6BE44	6BE45	6BE46	6BE47	6BE48	6BE49	6BE50	6BE51	6BE52	6BE53	6BE54	6BE55	6BE56	6BE57	6BE58	6BE59	6BE60	6BE61	6BE62	6BE63	6BE64	6BE65	6BE66	6BE67	6BE68	6BE69	6BE70	6BE71	6BE72	6BE73	6BE74	6BE75	6BE76	6BE77	6BE78	6BE79	6BE80	6BE81	6BE82	6BE83	6BE84	6BE85	6BE86	6BE87	6BE88	6BE89	6BE90	6BE91	6BE92	6BE93	6BE94	6BE95	6BE96	6BE97	6BE98	6BE99	6BE100	

# HI-FI EQUIPMENT

SAVE UP TO  
**33 1/3% OR MORE**  
SEND S.A.E. FOR  
DISCOUNT PRICE LISTS  
AND PACKAGE OFFERS!

## RECORD DECKS

B5R	
UA50†	£4.97
CI29†	£8.50
MP60	£10.40
610	£14.07
510	£11.50
310	£9.40
810	£33.45
MP60/G800*	£13.90
MP60 TPD1	£17.12
MP60 TPD1	£17.12
G800*	£19.50
MP60 TPD2	£15.40
610 TPD1	£20.35
610 TPD1	£13.20
210 Package	£9.95
HT 70	£14.99
HT70/G800*	£17.25
HT 70 Pack	£21.60
HT70 Pack	£23.95



<b>GOLDRING</b>	
GL69/2	£18.97
GL69/2/P	£24.20
GL72	£23.50
GL72/P	£26.55
GL75	£23.85
LD175	£28.95
LD172	£23.55
G99	£22.20
GL85/C	£25.25
LD185	£25.25
G101	£22.20

<b>PIONEER</b>	
PL12AC	£25.90
PL15C	£31.35
PLA35	£32.65

<b>THORENS</b>	
TD125	£67.50
TD125AB	£102.50
TX25	£7.40
TD150	£29.50
TD150A II	£38.95
TD150AB II	£39.95
150 Plinth	£9.80
TX11	£3.80

\* Stereo Cartridge † Mono  
All others less carriage  
Carriage 50p extra any model.

## RECORD DECK PACKAGES

Decks supplied with  
cartridge ready  
wired in teak  
veneered plinth with  
cover.

Garrard 2025TC/9TAHCD	£12.95
Garrard SP25 III/9TAHCD	£18.95
Garrard SP25 III/G800	£18.95
Garrard SP25 III/M75-6	£19.50
Garrard SP25 III/M44-7	£19.75
Garrard SP25 III/M44-E	£20.95
SP25 III/G800 (Play-on P&C)	£19.75
Garrard AP78/G800	£28.75
Garrard AP78/M75-6	£30.25
Garrard AP78/M55E	£32.25
Garrard AP78/M75EJ	£34.25
B&R McDonald MP60/G800	£19.95
B&R McDonald MP60/M44-7	£20.95
B&R McDonald MP60/M44-E	£21.50
Golding GL75/G800	£34.50
Golding GL75/G800E	£44.95

## SPINNAIR EQUIPMENT

Project 60  
Package  
offers.



2 x Z30 amplifier, stereo 60 pre-amp, P25 power supply. £15.95 Carr. 37p. Or with P25 power supply £18.00 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp, P28 power supply. £20.25. Carr. 37p. Transformer for P28. £2-97† extra. Add to any of the above £4-45 for active filter unit and £13-80 for pair of Q16 speakers. Project 60 FM Tuner £18-75. Carr. 37p. All other Sinclair products in stock. 2000 Amp £21-95 Carr. 37p.; 3000 Amp £28-50 Carr. 37p.; Neoteric Amp £43-95 Carr. 37p. IC12 £1-80 p. & p. 14p. NEW PROJECT 605 - £20-97, Carr. 37p.

## LATEST CATALOGUE


Our 7th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 60p 320 pages, fully illustrated and detailing thousands of bargains.

SEND NOW

ONLY  
40p  
P & P  
10p



## TELETON SAQ-206B STEREO AMPLIFIER

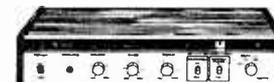

Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag, xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. OUR PRICE £19-50 Carr. 37p.

## SKYWOOD CX203 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-420 KHz and 55 to 20 MHz. Illuminated slide rule dial. Bandspread. Aerial tuning. BFO, AVC, ANL, 'S' meter. AM/CW/SSB. Integrated speaker and phone socket. Operation 220/240V AC or 12V DC. Size 325 x 266 x 150 mm. Complete with instructions and circuit. £28-50. Carr. 50p

## LAFAYETTE LA. 324 STEREO AMPLIFIER



Compares with amplifiers up to £40. OUR PRICE £24, Carr. 37p.

## TAPE CASSETTES

Top quality in plastic library boxes.  
C80 60 min 30p, 3 for 75p, 10 for £2-35  
C90 90 min 42p, 3 for £1-05 10 for £3-30  
C120 120 min 52p, 3 for £1-35 10 for £4-20  
Cassette Head Cleaner 30p, P. & P. 10p. Extra

## ★ TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6" x 4" x 2 1/2". 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108MHz. Ready built ready for use. Fantastic value for money. £8-37†, P. & P. 12p. Stereo multiplex adaptors £4-97†.

## TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER



Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.3-1200V. AC VOLTS 3-300V RMS. 6.0-800V P.P. DC CURRENT 15-12MA. Resistance up to 2000M ohm. Decibels -20 to +51 db. Complete with leads/instructions. £17-50, P. & P. 20p.

MCA 220 AUTOMATIC VOLTAGE STABILISER  
Input 88-125 VAC. or 176-260V AC. Output 120V AC. or 240 VAC. 200 VA rating. £11-97, carr. 50p.



## SINCLAIR IC-12



### HOMER INTERCOMS

Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.  
2 Station, £2-97, 3 Station £5-25, P. & P. 15p.  
4 Station £8-62, P. & P. 17p.

**EMI LOUDSPEAKERS**  
Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7-50 each P. & P. 37p.  
Model 450. 13" x 8" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £3-50 each. P. & P. 25p.

**TE 1018 DE-UX MONO HIGH IMP. DANCE HEADSET**  
Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £1-97, P. & P. 15p.




**MP7 MIXER PREAMPLIFIER**  
5 microphone inputs each with individual gain controls enabling complete mixing for stereo headphones. Adjustable headband. Magnetic, impedance 2,600 ohms. £1-97, P. & P. 15p.

**1021 STEREO LISTENING STATION**  
For balancing and gain selection of loudspeakers with additional facilities for stereo headphones switching. 2 audio controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2-35, P. & P. 15p.



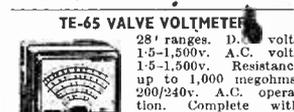**TE-65 VALVE VOLTMETER**  
25 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms 200/240V. A.C. operation. Complete with probe and instructions. £17-97, P. & P. 30p. Additional probes available. R.F. £2-12†; H.V. £2-50.



**230 VOLT A.C. 50 CYCLES RELAYS**  
Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40) Quantities available.



## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing. 1in. dia. shafts. Bulk quantities available. 25 WATT 10/25/50/100/250/500/1000/2500 or 5000 ohms. 90p, P. & P. 7p. 50 WATT 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1-15 P. & P. 7p. 100 WATT 1.5/10/25/50/100/250/500/1000 or 2500 ohms. £1-85 P. & P. 7p.

## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery  
S-280B General Purpose Bench Mounting  
1 Amp £7-00  
2.5 Amp £8-05  
5 Amp £11-75  
8 Amp £15-50  
10 Amp £22-50  
12 Amp £23-80  
20 Amp £49-00



## SPECIAL OFFER! SINCLAIR PROJECT 60 STEREO FM TUNER



The first tuner in the world to use the phase lock loop principle—as used for receiving signals from space craft because of its vastly improved signal to noise ratio. Provides fantastic results even in difficult areas. Tuning range 87.5 to 108MHz. Automatic stereo indicator. Sensitivity: 2µV. AFC range ± 200KHz. Signal to noise ratio, 65dB. Output voltage 2 x 150mV. Operating voltage 25-30V DC. Size 93 x 40 x 207 mm. REC. LIST PRICE £25. OUR PRICE £15-75 P. & P. 25p. Unrepeatable offer—buy now and save over 29.

## U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 d.p.v. 0/3/1.5/5/7.5/30/100/150/300/600/900 VDC and 75mV. 0/3/1.5/7.5/30/60/150/300/600/900 VAC 0/300µA/1.5/6/15/60/150/600mA/1.5/6 AMP AC 0/200/3K/30K Ω. Accuracy DC 1%, AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9-50 plus P. & P. 25p.

## PRS-2 PHOTO ELECTRIC RELAY SYSTEM

Inexpensive warning or counting system consisting of an encoder and relay unit. Relay unit has variable sensitivity control and switch for intermittent alarm operation. Encoder unit has continuous infra red filter and 45°/90°/180°/270°/360° bells, complete with instructions. £9.97, P. & P. 25p.

**WHARFEDALE MID-RANGE HI-FI UNITS**  
As used in world famous system. 5" dia. Impedance 4/8 ohms. High flux ceramic magnet. 20 watts rms. Brand new £1-50 Carr. 37p.



4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 220/240V. A.C. Brand new with instructions. £15.75. Carr. 37p.

## LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s, 560 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter. S. Meter. Bandspread. RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12V. D.C. Brand new with instructions. £50. Carr. 50p.



General coverage 150-400kc/s, 560 kc/s-30mc/s. FET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter. S. Meter. Bandspread. RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12V. D.C. Brand new with instructions. £50. Carr. 50p.

Special discounts for quantity

# G.W. SMITH & CO. (RADIO) LTD

10 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-637 2232  
27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3710  
257/258 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-580 0676  
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

CALLERS WELCOME MONDAY TO SATURDAY 9AM-6PM  
All Mail Orders to— 11-12, Paddington Green, London, W.2 Tel: 01-262 8562

## Large Transistor Panels.

Plug in frame unit with printed circ cards, these contain a number of 2N560 transistors, these are a Silicon N.P.N. type Vc 60v Ic 100 Ma Col Disp 500 Mill/W cut off freq 50 Mc/s, also close tol resistors metal fittings etc. In new cond ex USAF surplus, we supply two panel with not less than 40 2N560s. Price £1 plus 37p post for two.

## Cathode Ray Tubes

Type 7BP7A 7" flat face, 7Kv E.H.T. 6-3v heater, Emag focus & Deflection, are long persistence Blue short with Yell afterglow. Okay for flying spot scanners, T.V. to scope conversions etc. Supplied new boxed with connections.

Price £1-25 plus 30p post.

## Low Voltage Trans.

These are a small potted trans Pria 115v 50c/s Secs 6v at 1 amp twice and 260v ct at 9 Ma, used in pairs these will supply from 230v mains 6, 12, 18 or 24v at 1 amp or 12v D.C. 2 amps using byphase rect also 260v ct at 18 Ma, okay for BC221 P.U.

Price £1 plus 25p post per pair.

## H.F. Radio Sub Units.

Parts of R4187 Rx, Amp 4207 R.F. & I.F. section tunes 2-8 to 18 Mc/s in 3 bands, remote tuned by small 24v motor as 2 R.F. 1st Mix, 1st IF 2-15 Mc/s, 2nd Mix, 100Kc O/P 5 miniature valves, req ext L.O. good cond Price £1-75 plus 35p post. Amp 4208 I.F. & A.F. section as 2nd L.O. 100Kc filters, 2 100Kc I.F. stages, Det, M.L. B.F.O. A.F. amp & O/P. uses 9 valves, supplied in good cond Price £3-50 plus 35p post. Both units supplied with coax conn, circuits etc, used together form good basis for Rx, req ext L.O. for 1st Mix

## MISC ITEMS.

VALVES. 6X4, ECC83, 6AK6, 85A2, OB2, CV2179 (Similar to N78), 6AK5, EL85, 6BH6 all 3 for 50p. 6SN7, 6X6, 6SK7M all 5 for 50p. TRIMMER conds 20pf air spaced ceramic base new 10 for 50p or £4 per 100, BC221 Freq meters with int mains P.O. tested £2. PUSH SWITCHES with neon lnd give one N.O. contact size 1/2" x 1/2" for 35p. CONDS L.V. type 2500uf 50v Wk with clips for 60p. SIGNAL UNIT contains 3 mercury wetted relays 4 small toroids, 2 toroids, misc transis, conds, pots etc nice unit £1-30. INDICATORS type DM160 miniature type tuning lnd wkh gen and panel fixing 4 for 50p. SELECTOR UNIT contains small 24v DC motor with worm drive, val swts etc. £1-55. METERS R.F. type 4 amps PSD new cond 90p. U.H.F. Rx sub unit with 10 valves, 15q8 Mc/s xtal, 5 trans, trimmers, coax plugs & sks etc. £1-60. PHOTO FLASH cond. 40uf 2-5Kv size 6 x 3 1/2" £1q70. CONTAMINATION METERS range 100 to 1000 Pm/Range per Hr with probe in haversack tested, req 2 x 150x batts £3-50. SCOPES American service type USM-24C 115v 50c/s 1 single beam bandwidth constant 5 c/s to 8 Mc/s, top quality unit £33-50. TRANSISTORS type OC42 with long leads on boards with parts 12 for 50p also with DAT. 1 type similar to OC71, 10 boards approx 40 transis etc. for 65p. DIODES ZR22 200 P.I.V. at 8 amps 4 for 60p. TRANSISTORS Texas type 25012a Silicon H.F./power type N.P.N. Vc 70v Ic 2 amps Col Disp 40w, cut off 5 Mc/s 2 for 60p. DIODE PANELS contains 18 ZR12 diodes 200 P.I.V. at 1-5 amp plus misc parts 85p. METER 270 Deg FSD 1 Ma size 2" OSD 3 1/2" long scale marked 0, 2, 4, 8 x 100 Deg Cent new £1-40.

## CIRCUIT DIAGRAMS

R1155, B.F.L.N with values 50p. R1392, R1475 (88) 30p, B40 50p, CT38 50p, Scopes CD518 (CT316), 13A, 1035 Mks 1, 2 & 3, 1049 Mk3a all 50p ea, Sge Gens TF144G 50p, TF801a 75p, Rx STC R4187 set of circs parts list and block diagram £1. Send SAE for list of other circs.

Above prices include post or carriage. All above goods ex equipment unless otherwise stated. Carr charges apply to U.K. mainland only. SAE with enquiries.

# A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD, S9 5HL


# TV's 19" NOW £11-95

TWO YEARS' GUARANTEE ALL MODELS

405/625: 19" £25-95

FREE 23" £35-95

CATALOGUE CARR £1-95

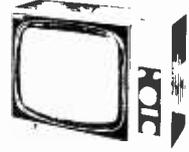


COLOUR TV 19" £145 OR 25" £185

LIMITED SUPPLY, REGRET PERSONAL CALLERS ONLY  
A SELECTION OF RECENT YEARS MODELS  
U.K. MANUFACTURE

## TV TUBES REBUILT GUARANTEED 2 YEARS

17" and 19" £5-95; 21" and 23" £6-45

Exchange Bowls carr. 55p

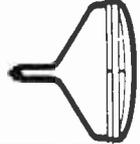

## COMPONENTS MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". Post 22p. Speakers: 35p. 2 1/2" 8Ω. Brand new. Post 15p. Record Player Cabinets. £3-75p. Designed for the modern auto-changer. Size 17" x 15" x 7 1/2". p.p. 55p. Radio: £3-95 8 transistor LWV/MW. Free case, battery. Post 15p. Precision Tape Motors: £1-95; 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free. Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 10p. Press Button VHF Tuner 75p. Brand new, takes PCF806, PCC89. Post 25p. Valve ELL80 50p. SPECIAL OFFER  
Pots: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg./100. KΩ. S/SW 500,500 KΩ. S/SW 500/1 meg.

## DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E.12. Phone 01-478 6001-2-3

# TEXAN 20+20 WATT. STEREO AMPLIFIER

Electro Spares can now supply all the components to build the "Texan" Amplifier, featured in *Practical Wireless* May/June 1972. All components are brand new with fibre glass p.c. board, all metalwork, knobs, finished silver trim front panel, etc. etc.

TOTAL COST OF COMPLETE COMPONENTS ONLY £27-85—POST FREE!

All components are available separately, to enable the constructor to obtain just what parts he requires at any one time. Please send S.A.E. for free list.

SPECIAL CONTEMPORARY STYLE SLIMLINE METAL CASE WITH WOODEN END CHEEKS IS NOW AVAILABLE FOR THIS AMPLIFIER—DETAILS INCLUDED WITH ALL LISTS, OR AVAILABLE ON RECEIPT OF S.A.E.

# P. E. 'GEMINI' STEREO AMPLIFIER

30 Watts (R.M.S.) per Channel into 8 Ohms !!

Total Harmonic Distortion 0-02% !!

Frequency Response (-3 dB) 20Hz-100kHz !!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but it is well within the capabilities of the ambitious constructor.

We can now supply a reprint of the articles in booklet form, price 55p plus 4p postage, with free complete component price list.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.

All parts available separately.



## ELECTRO SPARES

21 BROOKSIDE BAR,  
CHESTERFIELD, DERBYSHIRE.  
QUALITY • SERVICE • VALUE

# BRAND NEW GUARANTEED

# SEMICONDUCTORS & COMPONENTS

# RETURN OF POST SERVICE

SOLE AGENTS FOR SOLID STATES DEVICES INC., (U.S.A.), IN U.K.

## TRANSISTORS

2G301	0-15	2N2924	0-12	2N4931	2-70	AF116	0-28	BC307	0-09	BF271	0-21
2G302	0-15	2N2925	0-12	2N4932	2-70	AF117	0-28	BC307A	0-09	BF272	0-21
2G303	0-25	2N2926	0-12	2N4933	2-70	AF118	0-28	BC307VI	0-09	BF273	0-21
2G306	0-30	Green	0-10	2N5245	0-43	AF125	0-20	BC308	0-08	BF467	0-46
2G309	0-30	Yellow	0-10	2N5190	0-92	AF126	0-19	BC309	0-09	BF459	0-57
2G344A	0-25	Orange	0-10	2N5191	0-96	AF127	0-20	BC309A	0-09	BF821	2-10
2G345B	0-25	Orange	0-10	2N5192	1-24	AF139	0-20	BC309B	0-09	BF821A	2-10
2G371	0-15	2N3054	0-47	2N5174	1-01	AF170	0-25	BC315	0-20	BF228	0-22
2G374	0-15	2N3054	0-46	2N5193	1-10	AF172	0-25	JC227	0-21	BF861	0-27
2G381	0-22	2N3055	0-60	2N5195	1-46	AF178	0-42	HC328	0-19	BF898	0-28
2G417	0-20	2N3390	0-20	2N5245	0-43	AF179	0-45	BC337	0-17	BFW10	0-61
2N109	0-49	2N3391	0-20	2N5457	0-30	AF180	0-40	BC338	0-17	BFW11	0-61
2N174	1-40	2N3391A	0-22	2N5458	0-33	AF186	0-40	BCY30	0-27	BFW15	0-25
2N176	0-75	2N3392	0-18	2N5459	0-33	AF200	0-35	BCY31	0-30	BFX13	0-35
2N274	0-75	2N3493	0-18	2N128	0-63	AF239	0-36	BCY32	0-50	BFX29	0-25
2N335	0-75	2N3493	0-18	2N138	1-37	AF240	0-63	BCY32	0-50	BFX30	0-25
2N51	0-95	2N3402	0-17	2N199	1-36	AF279	0-47	BCY33	0-25	BFX37	0-30
2N376	1-00	2N3403	0-19	2N140	0-76	AF280	0-47	BCY34	0-30	BFX44	0-33
2N384	0-98	2N3404	0-24	2N141	0-69	AF280	0-45	BCY38	0-40	BFX63	2-48
2N388A	0-40	2N3405	0-27	2N142	0-64	AF211	0-75	BCY39	0-60	BFX68	0-40
2N404	0-28	2N3414	0-10	2N143	0-64	AF102	0-75	BCY40	0-50	BFX84	0-24
2N405	0-28	2N3415	0-10	2N192	0-10	AF103	0-75	BCY41	0-50	BFX84	0-24
2N456	0-75	2N3416	0-16	2N153	0-74	AS226	0-25	BCY43	0-15	BFX86	0-24
2N456A	0-75	2N3417	0-21	2N154	0-74	AS227	0-25	BCY58	0-18	BFX87	0-25
2N457A	0-80	2N3570	1-25	2N159	1-00	AS228	0-25	BCY59	0-19	BFX88	0-25
2N491	3-25	2N3571	1-12	2N187	1-30	AS229	0-27	BCY66	0-58	BFY89	0-40
2N684	0-26	2N3572	0-97	2N200	1-07	AS260	0-20	BCY67	0-82	BFY10	0-85
2N694	0-75	2N3573	0-10	2N201	2-05	AS261	0-35	BCY75	0-85	BFY11	0-85
2N696	0-24	2N3603	0-30	2N202	1-07	AS221	0-21	BCY76	0-82	BFY17	0-90
2N697	0-15	2N3704	0-10	40050	0-50	AI103	1-25	BCV72	1-13	BFY18	0-25
2N698	0-25	2N3705	0-10	40050	0-50	BC107	1-20	BCY87	3-47	BFY19	0-25
2N699	0-29	2N3706	0-10	40309	0-28	BC108	1-20	BCY88	2-40	BFY20	0-50
2N706	0-10	2N3707	0-10	40310	0-37	BC109	1-12	BCY89	0-80	BFY29	0-40
2N709A	0-12	2N3708	0-70	40313	1-05	BC110	0-15	BC110	0-27	BFY37	0-20
2N708	0-13	2N3709	0-90	40316	1-05	BC111	0-12	BC211	0-40	BFY41	0-43
2N709	0-08	2N3710	0-90	40316	1-05	BC115	0-15	BD115	0-75	BFY43	0-82
2N711	0-20	2N3711	0-90	40318	0-97	BC116	0-15	BD116	0-75	BFY50	0-16
2N718	0-81	2N3712	0-95	40360	0-35	BC116A	0-18	BD121	0-65	BFY51	0-16
2N718A	0-80	2N3713	1-08	40361	0-37	BC117	0-20	BD123	0-80	VFY82	0-16
2N720	0-60	2N3714	1-15	40362	0-40	BC118	0-11	BD124	0-80	VFY83	0-16
2N721	0-60	2N3715	1-20	40363	0-41	BC119	0-11	BD125	0-97	BFY87	0-84
2N914	0-15	2N3716	1-20	40363	0-61	BC121	0-20	BD131	0-75	BFY64	0-41
2N916	0-17	2N3773	2-35	40389	0-37	BC123	0-25	BD132	0-75	BFY75	0-40
2N918	0-30	2N3774	3-33	40394	0-58	BC125	0-15	BD135	0-38	BFY76	0-22
2N919	0-20	2N3775	4-19	40406	0-40	BC126	0-20	BD136	0-44	BFY77	0-24
2N929	0-14	2N3776	5-95	40407	0-31	BC129	0-30	BD137	0-47	BFY78	0-38
2N930	0-14	2N3777	4-94	40408	0-31	BC130	0-31	BD138	0-45	BFY90	0-35
2N1090	0-28	2N3778	4-94	40408	0-41	BC135	0-11	BD139	0-82	BRX39	0-30
2N1091	0-24	2N3779	3-15	40409	0-49	BC136	0-15	BD140	0-78	BRX19	0-13
2N1131	0-20	2N3780	4-50	40410	0-58	BC137	0-15	BDY10	1-25	BRX19	0-13
2N1132	0-20	2N3781	3-67	40411	1-40	BC138	0-20	BDY11	1-40	BRX21	0-21
2N1184	1-27	2N3782	3-37	40438	1-44	BC141	0-80	DDY17	1-60	BRX26	0-34
2N1302	0-16	2N3789	1-76	40467A	0-57	BC142	0-18	DDY18	1-75	BRX27	0-34
2N1303	0-20	2N3790	0-90	40468A	0-55	BC143	0-21	DDY20	0-92	BRX29	0-27
2N1304	0-20	2N3791	2-02	40600	0-57	BC144	0-24	BDY38	0-45	BRX30	0-68
2N1305	0-22	2N3792	2-20	40601	0-57	BC145	0-21	BDY60	0-90	BRX59	0-78
2N1306	0-20	2N3794	0-10	40602	0-40	BC146	0-20	BDY61	0-85	BRX60	0-64
2N1307	0-25	2N3819	0-28	40603	0-49	BC147	0-10	BDY62	0-75	BRX61	0-64
2N1308	0-25	2N3820	0-47	40604	0-45	BC149	0-10	BDY63	0-75	BRX62	0-64
2N1309	0-25	2N3823	0-50	40605	0-45	BC149	0-10	BDY64	0-75	BRX63	0-64
2N1483	0-90	2N3824	0-75	40636	0-38	BC153	0-10	BF117	0-48	BRX77	0-20
2N1507	0-24	2N3826	0-23	40673	0-60	BC154	0-11	BF119	0-68	ASX78	0-25
2N1613	0-20	2N3854	0-16	40673	0-60	BC154	0-11	BF121	0-25	BSW70	0-20
2N1631	0-25	2N3854A	0-16	AC113	0-16	BC157	0-09	BF123	0-27	BSY24	0-20
2N1632	0-25	2N3855	0-16	AC115	0-16	BC158	0-10	BF123	0-27	BSY25	0-20
2N1637	0-20	2N3856	0-16	AC117	0-20	BC160	0-11	BF127	0-27	BSY28	0-15
2N1638	0-20	2N3857	0-16	AC118	0-20	BC161	0-11	BF127	0-27	BSY28	0-15
2N1671	1-00	2N3858	0-16	AC121	0-11	BC167B	0-11	BF152	0-20	BSY27	0-15
2N1701	1-10	2N3856A	0-16	AC126	0-20	BC168B	0-10	BF153	0-29	BSY28	0-15
2N1702	2-15	2N3858	0-16	AC128	0-20	BC168C	0-10	BF154	0-18	BSX38	0-15
2N1711	0-17	2N3858A	0-16	AC141K	0-30	BC169B	0-11	BF158	0-15	BSY39	0-15
2N1983	0-84	2N3859	0-16	AC142K	0-25	BC170	0-11	BF160	0-23	BSY32	0-25
2N2102	0-20	2N3860	0-16	AC151V	0-12	BC171	0-13	BF161	0-35	BSY63	0-25
2N2147	0-70	2N3860	0-16	AC152V	0-12	BC172	0-13	BF163	0-20	BSY64	0-30
2N2148	0-40	2N3866	0-70	AC153	0-16	BC172	0-13	BF163	0-20	BSY64	0-30
2N2192	0-40	2N3877	0-25	AC153K	0-22	BC182	0-10	BF166	0-35	BSY66	0-70
2N2192A	0-40	2N3877A	0-25	AC154	0-20	BC182L	0-10	BF167	0-18	BSY65	0-19
2N2193	0-40	2N3878	1-22	AC176	0-16	BC183	0-09	BF177	0-25	BSV79	0-40
2N2193A	0-40	2N3879	0-21	AC176K	0-17	BC184	0-11	BF178	0-25	BSV79	0-40
2N2194	0-27	2N3900	0-20	AC187K	0-17	BC184L	0-11	BF179	0-30	BSY65A	0-40
2N2194A	0-30	2N3900A	0-21	AC188K	0-23	BC186	0-25	BF180	0-35	BU104	1-09
2N2195	0-27	2N3901	0-21	AC188	0-25	BF181	0-32	BU105	0-28	BU105	0-28
2N2195A	0-18	2N3903	0-20	ACY18	0-15	BC204	0-11	BF182	0-30	C111	0-63
2N2219	0-20	2N3905	0-21	ACY19	0-20	BC205	0-10	BF183	0-40	C407	1-15
2N2219A	0-20	2N3906	0-20	ACY20	0-20	BC206	0-11	BF184	0-17	C424	0-18
2N2220	0-20	2N4036	0-40	ACY21	0-20	BC207	0-10	BF185	0-17	C425	0-18
2N2221	0-20	2N4037	0-36	ACY22	0-10	BC208	0-09	BF194	0-14	C426	0-25
2N2221A	0-22	2N4038	0-12	ACY30	0-42	BC209	0-10	BF196	0-15	C428	0-25
2N2222	0-22	2N4039	0-30	ACY31	0-42	BC210	0-10	BF198	0-19	CF194	0-28
2N2222A	0-12	2N4060	0-90	ACY39	0-47	BC212K	0-10	BF197	0-15	DA0N3	0-62
2N2368	0-11	2N4061	0-11	ACY40	0-17	BC212L	0-12	BF198	0-15	GET111	0-45
2N2369	0-12	2N4062	0-11	ACY41	0-15	BC214L	0-14	BF199	0-18	GET113	0-20
2N2369A	0-15	2N4302	0-25	AD136V	0-84	BC226	0-16	BF200	0-35	GET114	0-20
2N2646	0-40	2N4303	0-28	AD140	0-49	BC237	0-08	BF224J	0-14	GET115	0-20
2N2647	1-21	2N4304	0-80	AD140	0-55	BC239	0-08	BF224J	0-14	GET119	0-85
2N2711	0-12	2N4914	0-87	AD142	0-40	BC259	0-08	BF257	0-22	GET120	0-25
2N2712	0-12	2N4915	0-85	AD143	0-40	BC261	0-20	BF238	0-22	GET135	0-20
2N2713	0-17	2N4916	0-11	AD143	0-45	BC252	0-18	BF244	0-16	GET136	0-20
2N2714	0-17	2N4917	0-17	AD149V	1-23	BC253	0-23	BF245	0-33	GET136	0-20
2N2904	0-18	2N4918	0-50	AD150	0-55	BC257	0-28	BF246	0-43	GET138	0-20
2N2904A	0-25	2N4919	0-53	AD161	0-33						




## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new component throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohm. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, etched panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE £10.50. P. & P. 25p.

## De Luxe Stereo Amplifier

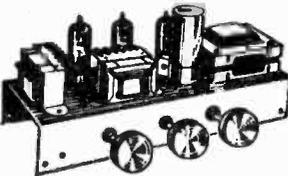

A.C. mains 200-240 v. U.S.A. 115 v. heavy duty fully isolated mains transformer with full wave rectification giving adequate u.a. smoothing with negligible hum. Valve line up - 2 x 6X4, 1 x 6X5, 1 x 6X6, 1 x 6X8, 1 x 6X4. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4 1/2". Overall height including valves 5". Ready built & tested to a high standard. PRICE £28.92 P. & P. 45p.

## NEW! POWER SUPPLY UNIT

200/240v. A.C. Input. Four switched fully smoothed D.C. outputs giving 6v, 7.5v and 9v, and 12v. at 1 amp continuous (1 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested.

PRICE £4.50 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2" x 5" approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS. 8 x 6 x 1/4 in. FIVE for 50p. P. & P. 15p.

COILED SPRING BACK TELEPHONE CABLE. Closed approx. 10' extends to 30', 4 core or 6 core. 25p each P. & P. 5p. 5 or r. Post free. LIMITED NUMBER!

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-45v. at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £1.75 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. P.T. 200/240v. Sec. 9-0-9 at 500mA. 70p. P. & P. 15p. P.T. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 15p. P.T. 200/240v. Sec. 10-0-10 at 2 amp. £1.35. P. & P. 30p.

SPECIAL OFFER MAINS TRANSFORMER 200/240v. A.C. Input 35v at 1 1/2 amp A.C. output overall size 2 1/2" x 2 1/2" x 3" approx. Suitable drop through or vertical mounting 75p. P. & P. 15p.

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 20dB. Solid enclosure size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 88p. P. & P. 15p.

### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

4-SPEED RECORD PLAYER BARGAINS. Mains models. All brand new in maker's packing. LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £6.97 Carr. 50p. With stereo cartridge £7.97 Carr. 50p. LATEST GARRARD MODELS. S.A.E. for latest Prices!

PRECISION ENGINEERED PLINTHS. Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, HL65B, AT60 etc. or B.S.R. C109, C129, 421 etc. Choice of Black leatherette or Teak grain finish. Size 12 1/2" x 14 1/2" x 9 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). PRICE £5.50. P. & P. 60p.

LATEST ACOS GP91/EP78 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.50 P. & P. 8p.

SONOTONE STAGH COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond stereo LP and Sapphire 78. ONLY £2.50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. £1.63 P. & P. 10p. LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.50 P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II. A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £3.75 P. & P. 40p.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4.84 P. & P. 60p.

DELUXE QUALITY PORTABLE R/P CABINET MK II. Uncut motor board size 14 1/2 x 12in. clearance 2in. below, 6 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP26). Size 18 x 16 x 8in. PRICE £4.75. P. & P. 60p.

## SPECIAL OFFER ! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tigris-Vynair finish. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £8.40 Carr. 65p

Cabinet Available Separately £4.50 Carr. 60p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8.50 Carr. 65p

### LOUDSPEAKER BARGAINS

5in. 3 ohm £1.05. P. & P. 15p. 7 x 4in. 3 ohm £1.15. P. & P. 20p. 10 x 6in. 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.62. P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet 3.8 or 15 ohm £3.20. P. & P. 30p. E.M.I. 13 x 8in. 3.8 or 15 ohm with two built in tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13 x 8in. twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

BRAND NEW 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiLux ceramic magnet assembly £6.75. Guitars models 25s £6.75, 35s £8.50. P. & P. 35p.



### SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS with large ceramic magnet and plasticised cone surround. £3.75. P. & P. 25p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3, 8 or 15 ohm £2.20. P. & P. 30p. 35 ohm SPEAKERS 3in. only 63p. P. & P. 15p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER. Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5.75 each. P. & P. 25p.

VYNAIR & BEXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1.75 yd., our Price 75p yd. length. P. & P. 15p (min 1 yd.) S.A.E. for samples.


### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable foam ear-muffs. Wired and fitted with standard stereo 1/4 in. jack-plugs. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £2.95. P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR PRICE £1.05. P. & P. 8p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100uA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.
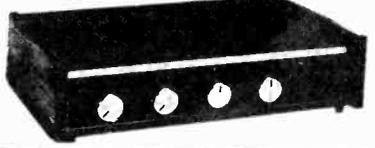
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibreglass printed circuit board, smart brushed anodised aluminium front panel with matching knob, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response  $\pm$  3dB 2-20,000 Hz. Sensitivity: better than 80mV into 1M Ohm. Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. 10 to 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12 1/2" x 8 1/2" x 2 1/2". Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

AMPLIFIER KIT £10.50 P. & P. 15p (Magnetic input components 30p extra)  
POWER PACK KIT £3.00 P. & P. 30p  
CABINET £3.00 P. & P. 30p

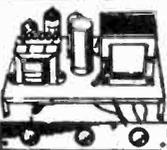(Post Free if all units purchased at same time)  
Full after sales service  
Also available ready built and tested £21.00. Post Free.  
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotique use, etc.



### 3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.  
HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 40p.

### HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECC83 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3in. watts. Volume and tone controls. Chassis size only 7 1/2" wide x 3in. deep x 6in. high overall. A.C. mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.

BARGAIN PRICE £2.75 P. & P. 35p

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier, with an output of 14 watts from 2 EL84s in push-pull. Super construction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EZ80, rectifier. Complete with instructions booklet 13p (Free with parts). All parts sold separately. ONLY £7.97 P. & P. 65p.

(Please write clearly)  
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9-5.30 Monday to Saturday  
Early closing Wed. 1 p.m.  
A few minutes from South Wimbledon Tube Station.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES



now YOU can **CATCH SHOALS OF BIG FISH**  
with new electronic miracle  
special introductory offer **£2.50**

First time marketed in England, this exciting electronic instrument the "Decoytronic" is the one responsible for starting the electronic fish-lure range in the U.S.A. just recently. Uses ingenious double-action method of attracting all kinds of fish from hundreds and hundreds of feet away... saltwater or freshwater. Why this device is so fantastically successful is because it actually imitates the sound of wet insects *skipping* about the surface. These sound waves spread out hundreds of feet in all directions. Although this peculiar sonic frequency won't sound like much to you—to all the fish in the area it's their dinner bell! But that's not all... *electroluminescence* neon tubes cunningly flicker intermittently, penetrating the area for hundreds of feet around, at a frequency fish are unable to resist. The fish mistake this flickering glimmer for the soft phosphorescence glow given off by Plankton... a favourite delicacy of most fish!! All you do is switch on, lower into the water (it's completely water resistant) allow around 6 minutes—then start reeling 'em in. We'll bet you won't be able to reel 'em in fast enough. Self-contained batteries last ages—cost pence. Kit of all parts including special easy as a.b.c. directions only **£2.50 + 25p. P. & P.** (Parts available separately).

**BUILD 5 RADIO AND ELECTRONIC PROJECTS**

ONLY **£2.45**



Amazing Radio Construction set! Become a radio expert for **£2.45**. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step by step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc. all you need. Presentation box 45p extra as illus. (if required) (parts available separately) no soldering necessary. Send **£2.45 + 20p. p. & p.**

**ELECTRONIC ORGAN**

ONLY **£3.25**



Don't confuse with ordinary electronic organs that simply blow air over mouth-organ type reeds etc Fully transistorised. **SELF-CONTAINED LOUDSPEAKER. Fifteen separate keys span two full octaves—play the "Hollow Tone of Pianos", play "Silent Night", play "Auld Lang Syne" etc.** You have the thrill and excitement of building it together with the pleasure of playing a real, live portable electronic organ. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED.** No soldering, simple as ABC to make. *Anyone over nine years can build it easily in one short evening following the fully illustrated, step-by-step, simple instructions.* **ONLY £3.25 + 25p. p. & p.** for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself finish with an exciting gift for someone.

**SOOTHE YOUR NERVES RELAX WITH THIS AMAZING RELAXATRON**

CUTS OUT NOISE POLLUTION SOOTHES YOUR NERVES!—The RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). **CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE** using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones. Components, nuts, screws, wire, etc. no soldering. **£2.75 + 25p. p. & p.** Parts available separately.



ONLY **£2.25**

**READY BUILT AND TESTED TREASURE LOCATOR MODULE**

ONLY **£4.95**



FULLY TRANSLATORISED PRINTED CIRCUIT METAL DETECTOR MODULE. *Ready built and tested—just plug in a PP3 battery and phones and it's working.* Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, HURLED PIPES, ETC. *So sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND!* **GIVES CLEAR SIGNAL ON ONE COIN £4.95 + 30p. carr. etc.**

**UNIQUE RADIO FOR BEDROOM OR OFFICE** No batteries, no electricity, **ONLY £1.70** never wears out



Tune in your favourite programmes or the news, or sports in the Office or in your bedroom. Uses sensitive, germanium diode originally evolved from wartime radar. Never buy a battery. Never use electricity. Never replace. Covers all medium waves. Clear beautiful tone. Size 4 1/2" x 2 1/2" x 1 1/2" in beautiful case. **ONLY 7 CONNECTIONS AND IT'S WORKING!** No soldering necessary. **CAN BE BUILT ALMOST BLINDFOLD IN UNDER 15 MINUTES!** Ideal for absolute beginner from 8 years of age upwards. **SPECIAL PRICE TO CLEAR STOCKS OF COMPONENTS, ONLY £1.70 + 20p. P. & P.** for all parts including beautiful case. (Germanium semi-conductor, tuning condenser, personal phone, wire, nuts screws. **SIMPLE AS A.B.C. INSTRUCTIONS** (Parts available separately).

**"READ PEOPLE'S MINDS"—TEST THEIR NERVES—BEAT THEM AT CARDS, ETC. WITH THIS ASTONISHING ELECTRONIC BRAIN BOX** Only **£2.87**

With this "Brain-box" you will be able to perform mind-boggling feats. **THE MIND READING DEVICE** will make people swear you have "telepathic" powers. **THE AMAZING CARD THICK UNIT** completely mystifies and baffles from one to six people. You correctly "guess" the two cards each person has selected at random from a pack they themselves shuffled. **THE ELECTRONICS NERVES TESTER** puts your friends to a very lively test. It gives out fail and finish signals (the winner is the person with lowest number of fail signals). **Can be adjusted from the weakest to strongest person.** **THE ELECTRONIC MAZE** tests the mental ability of the player because it uses psychology with an electronic twist. You can change the maze activity in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof. Size 18" x 12" x 6" (Max.). You can play all these games and more besides after building the "Brain box". No soldering, you get pictorial, easy as a.b.c. step-by-step simple instructions. **ONLY £2.87 + 35p. p. & p.** for all parts including chassis, switches, stylus, signalling lights, wire, nuts, screws, etc. etc. Uses standard battery. Presentation Box 35p. extra as illus. if reqd. (PARTS AVAILABLE SEPARATELY) **FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.**



the amazing "Phototron" **SOUND OPERATED FLASH**

ONLY **£4.50**

Take flash pictures at the exact instant of the bursting of a balloon. A champagne cork leaving the bottle. The split second a hammer strikes a light bulb. *The mind boggles at the possibilities of the "Phototron" — the only time you can imagine.* Now that inexpensive flash guns are on the market in quantity, it has made possible, with the help of electronics the production of a wide variety of exciting photography effects, once strictly limited to the professionals. The duration of an electronically produced flash is extremely brief and normally measured in Milliseconds. Now, providing the camera shutter is left open in a dark or subdued light, it is the timing of the flash that determines what is imprinted on the film—not necessarily anything done by the camera. As electronic flash guns are fired by making a switched connection then it becomes obvious that one of the latest Silicon Controlled Relay's can be used. If we make this S.C.R. operate by sound (with variable sensitivity control for soft/loud sounds) some real "way out" photography effects can be captured forever on film. Easily built in a couple of hours or so, the "Phototron" is fully solid state, uses self contained PP3 battery. No soldering necessary using our special printed circuit terminal board (pat. Applied for). All parts including special pictorial step-by-step plans, transistor, microphone, S.C.R., potentiometer, switches, test lamp, case, nuts, screws, etc. etc. **ONLY £4.50 + 25p. P. & P.** Made up must be worth at least £10. (parts available separately).

Eavesdrop on the exciting world of Aircraft Communications— **V.H.F. AIRCRAFT BAND CONVERTER** ONLY **£2.85**



Listen in to AIRLINES, PRIVATE PLANES, JET-PLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. *Clear for yourself the disciplined voice hiding messages of talk down.* Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LITTON, KINGFISHER, WICK, ETC. ETC. **CLEAR AS A BELL.** This fantastic fully transistorised instrument can be built by anyone over nine to ten hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend rod aerial, place clewray primary medium wave radio (even tiny portables). **NO CONNECTIONS WHATSOEVER NEEDED.** **SEND ONLY £2.85 + 20p. p. & p.** for kit including case, nuts, screws, wire, etc. etc. (parts available separately).

**FIND BURIED TREASURE!** Transistorised Treasure Locator



This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COINS, JEWELLERY, ARCHAEOLOGICAL PIECES ETC. ETC.** *Extremely sensitive will signal presence of certain objects buried several feet below ground.* No knowledge of radio or electronics required. *Can be built with ease in one short evening by anybody from nine years of age upwards.* So clear, easy to follow, step-by-step, fully illustrated instructions—Uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. **ONLY £2.85 + 25p. p. & p.** (Sections handle as illustrated 85p. extra). Parts available separately. Made up looks worth £15.

ONLY **£2.85**

**INGENIOUS ELECTRONIC SLEEP INDUCER**

ONLY **£3.25**



Do you wake up in the night and can't get off to sleep again? Would you like to be gently soothed off to satisfying sleep every night? Then build this ingenious electronic sleep inducer. *It even stops by itself so you don't have to worry about it being on all night!* The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sound gradually becomes less and less—until they eventually cease altogether. *The effect it has on people is amazingly very similar to Hypnosis.* All transistor. No knowledge of electronics or radio needed. Step-by-step instructions included. *No soldering necessary.* Kit includes case, nuts, wire, screws, etc. **SEND £3.25 + 25p. p. & p.** (parts available separately).

**SHORTWAVE TRANSISTOR RADIO**

ONLY **£2.75**



Anyone from 9 year up can follow the step-by-step, easy as ABC fully illustrated instructions. No soldering necessary. 76 stations logged on roll serial in 30 mins. **RUSSIA, AFRICA, USA, SWITZERLAND, etc.** Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3" x 4 1/2" x 1 1/2". **Only £2.75 + 20p. p. & p.** Kit includes cabinet, screws, instructions, etc. (Parts available separately).

**AMAZING MAGIC MUSIC BOX**

make electronic music waving your hands about only **£2.75**



Everyone's heard the weird, wonderful, but beautiful music used in Science Fiction Films, Horror Films etc. also on Radio and Television. This uniquely eerie music is almost always produced by a little known electronic device measuring only a few inches... called a Therenin. All you have to do is place it on your radio (almost any type will do) and place your hand on the Therenin and proceed to wave your hand mysteriously in the air like a magician. The most fantastic musical sounds are then produced, and with a little practice people can learn to play all the well known tunes. Apart from it's musical value, it's small size allows it to be used in most circumstances. Parties, gatherings of friends, etc. where it adds a tremendous interest. **Hours and hours of pleasure to yourself and old.** Uses standard PP3 battery which lasts ages. The 3 Transistor circuit, though fairly advanced is simple to build with our pictorial step-by-step plans. No soldering necessary. Easily built in an hour or so using our special printed circuit terminal board (Pat. Applied For). All parts including nuts, bolts, case etc., **ONLY £2.75 + 25p. P. & P.** (Parts available separately).


**INGENIOUS ELECTRONIC SINGING & WARBLING CANARY** only **£4.50**



Actually whistles & warbles like a real live Canary! Amazing circuitry faithfully reproduces the Canary's magnificent song. Just switch on and leave it —whistling down scale for some seconds, suddenly breaking into a delightful warble, then several seconds later shutting off for a second or two—only to start automatically again in a few seconds. People listen to the delightful song all day and never get bored! Relax, as the sweetest nerve-soothing birdsong takes you to leafy woods and glades. Provides countless hours of joy to young and old alike. Standard self-contained battery lasts ages. Easily built in an hour or so with special pictorial step-by-step plans. No soldering necessary. All parts including printed circuit terminal board (pat. applied for) transistors, loudspeaker, transformer, nuts, screws, wire, etc. + case (which fits under cage—cage and toy bird not supplied) **ONLY £4.50 + 25p. P. & P.** (parts available separately).

# Sinclair Project 60

## Stereo 60

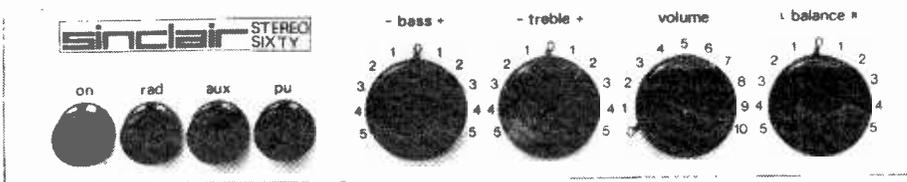

Built and tested post free  
**£9.98**


## pre-amplifier/control unit

The versatility of Project 60 high-fidelity modules is well demonstrated in this excellent unit. It provides the facilities essential to good stereo and will enhance the quality of any system it is used with, whether Project 60 or any other top line power amplifiers. Compact, yet robustly constructed, the unit is easily panel mounted and will operate satisfactorily from 18 to 35 volts supply. Silicon epitaxial transistors are used throughout to achieve a very high signal to noise ratio with excellent separation between channels. Distortion at maximum output is barely 0.02% with magnetic p.u. input. Accurate equalisation is provided for all inputs, which are selected by push buttons. For maximum effectiveness, the Sinclair A.F.U. is recommended for use with the Stereo 60 pre-amp/control unit. A comprehensive manual supplied with Project 60 modules makes installing and connecting easy and ensures best possible results from your system.

### SPECIFICATIONS

**Input sensitivities:** Radio – up to 3mV Mag p.u. 3mV correct to R.I.A.A. curve – 1dB. 20 to 25,000 Hz Ceramic p.u. – up to 3mV; Aux – up to 3mV **Output:** 250mV  
**Signal to noise ratio:** better than 70dB.  
**Channel matching:** within 1dB  
**Tone controls:** TREBLE: +12 to –12dB at 10KHz; BASS: +12 to –12dB at 100Hz  
**Front panel:** brushed aluminium with black knobs and controls  
**Size:** 66 x 40 x 207mm.
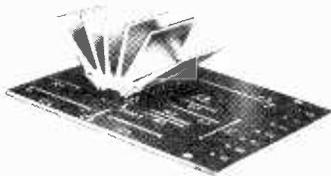
## Super IC.12 Integrated circuit high fidelity amplifier



istor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board

### SPECIFICATIONS

**Output power:** 6 watts RMS continuous (12 watts peak) 6–8Ω **Frequency Response:** 5Hz to 100KHz – 1dB **Total Harmonic Distortion:** Less than 1%. (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms **Input Impedance:** 250 Kohms nominal **Power Gain:** 90dB (1,000,000,000 times) after feedback **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual

**£2.98** Post free

Having introduced integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC, make possible. It is the equivalent of a 22 transistor

## Project 605



The easy way to buy and build Project 60

Project 605 is one pack containing one PZ5 two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

Everything you need to assemble a superb 30 watt high fidelity stereo amplifier without having to solder.

# sinclair

Sinclair Radionics Ltd, London Road, St. Ives, Huntingdonshire PE17 4HJ. Tel: St. Ives 64311


# the world's most advanced high fidelity modules

## Z.30 & Z.50 power amplifiers

Built, tested and guaranteed with circuits and instructions manual. **Z.30 £4.48** **Z.50 £5.48**

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to provide unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8Ω) and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and are intended for use principally with other units in the Project 60 range. Their performance and design are such, however, that Z.50s and Z.30 may be used in a far wider range of applications.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).— Power Outputs:**  
**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.  
**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.  
**Frequency response:** 30 to 300,000Hz ± 1dB. **Distortion:** 0.02% into 8 ohms. **Signal to noise ratio:** better than 70dB unweighted. **Input sensitivity:** 250mV into 100 Kohms (for 15w into 8Ω). For speakers from 3 to 15 ohms impedance. **Size:** 14 x 80 x 57mm.

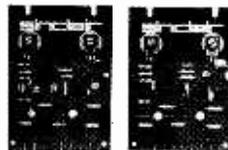


## Project 60 Stereo F.M. Tuner

Built and tested. Post free. **£25**

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7μV for lock-in over full deviation. **Squelch level:** Typically 20μV. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10Hz – 15KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2μV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

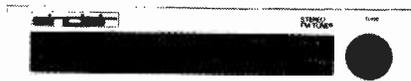

## A.F.U. High & Low Pass Filter Unit

Built, tested and guaranteed **£5.98**

For use between Stereo 60 unit and two Z.30s or Z.50s. The unit is very easily mounted and is unique in that the cut-off frequencies are continuously variable. As attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. There are two filter sections – rumble (high pass) and scratch (low pass). H.F. cut-off (–3dB) variable from 28KHz to 5KHz. L.F. cut-off (–3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) 0.02% at rated output. Operating voltage from 15 to 35V. Current 3mA. **Size:** 66 x 40 x 90mm.



## Power Supply Units

Designed specifically for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 or PZ.8 where a stabilised supply is essential.

**PZ.5 30 volts un stabilised £4.98**  
**PZ.6 35 volts stabilised £7.98**  
**PZ.8 45 volts stabilised (less mains transformer) £7.98**  
**PZ.8 mains transformer £5.98**



### Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control, etc.	<b>£4.48</b>
Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U volume control, etc.	<b>£9.45</b>
12W. RMS continuous sine wave stereo amp. for average needs	<b>2 x Z.30s, Stereo 60; PZ.5</b>	Crystal, ceramic or mag P.U., F.M. Tuner, etc.	<b>£23.90</b>
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	<b>2 x Z.30s, Stereo 60; PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	<b>2 x Z.50s, Stereo 60; PZ.8, mains transformer</b>	As above	<b>£34.88</b>
Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

# sinclair

SINCLAIR RADIONICS, ST IVES, HUNTINGDONSHIRE PE17 4HJ

Please send

\_\_\_\_\_

Enclose cash/cheque/money order.

Name \_\_\_\_\_

Address \_\_\_\_\_

PW 11/72

# WEYRAD

## COILS & TRANSFORMERS FOR CONSTRUCTORS

Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117)	33p
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117)	36p
2nd I.F. Transformer	P50/2CC (For OC45)	P51/2 (For AF117)	36p
3rd I.F. Transformer	P50/3CC (For OC45)	P50/3V (For AF117)	36p
Rod Aerial	RA2W		72p
Driver Transformer	LFDT4/1		58p
Output Transformer	OPT1		58p
Printed Circuit	PCA1		58p

## I.F. TRANSFORMERS FOR "PRACTICAL WIRELESS" CIRCUITS

Components for several receivers are available, including the following for the "Clubman".

T41/1E	1st I.F. Transformer	39p
T41/2E	2nd I.F. Transformer	39p
T41/3T	3rd I.F. Transformer	57p
T41/3T	B.F.O. Coil	57p

Details of these and our other components are given in an illustrated folder which will be supplied on request with postage please.

# WEYRAD (ELECTRONICS) LIMITED

SCHOOL STREET, WEYMOUTH, DORSET

## FELSTEAD ELECTRONICS (PW 62)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas.) Cash with order only—No C.O.D. or Caller service. Charges (Min. 6p) in brackets after all items apply to G.B. and Eire only. Regret orders under 25p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas Orders welcomed.

**RECORDING TAPE:** Finest quality/value British Mylar available: STANDARD 5' 600ft. 36p; 6' 900ft. 50p; 7' 1200ft. 56p; LONG PLAY 5' 900ft. 50p; 5' 1200ft. 56p; 7' 1800ft. 90p. (Charges for 5' and 6' singles 8p, two to four 7p each; five and over 30p the lot. For 7', one or two 10p each reel, 3, 4 and 5 reels 30p the lot, 6 reels and over 35p the lot.) Other sizes and accessories in list. **CASSETTES** in lib. cases for min. 5 cassettes, C60 28p, C90 38p, C120 48p. (10p per 5, 6-10 20p, 11 and over 25p.) Under 5 cassettes 33p, 45p and 55p each respectively (1 to 4, 10p).

**CARTRIDGES** all with standard fittings and stylus. Stereo-compatible Mono GP91/8C £1.10; STEREO GP93 £1.40; Stereo Ceramic GP94 £1.05. (All at 6p each.) Comparatives shown in List, with more types inc. Sonotone STAHC, Stereo Ceramic Diamond £1.97 (6p). **DIAMOND STYLII:** single tip types: Acos GP37, GP59, GP65/67, GP71, BBR TC8/LP/ST; COLLARO O.P. and DC284, GARRARD GC2, GC8, GC810, GC812, RONETTE BF40, O.P. and T. PHILIPS 3301 (3060, 3066, 3302, 3304), 3010/12/15/16. **SONOTONE 19T/20T ALL** at 40p each (6p). **SAPPHIRE 171p** (6p). **DOUBLE TIP TURNOVER TYPES** 78 sep. on other side. For ACOS GP73, GP91 for cartridges GP93, GP94 etc.) GP91SC (for stereo compat. types) GP104 BBR 8T4 (8T3, 8T5), 8T9 (8T8), 8T12/14/15, SONOTONE 8TA, 9TA, 9TAHC. PHILIPS 3306 3310, 3224, 3228/22, GP290, GARRARD GCM21, 22, GC823, GK825 and 26, GCM21T and 22T, GCM24T, GC823, GK825T and 26T, GCM31, GC836, GC838, GC838, K840A, K841B ETC. ALL at 75p (6p). **SAPPHIRE 35p** (6p). **DOUBLE DIAMOND STYLIII:** (same dia. tip each at 75p (6p)). **SAPPHIRE 35p** (6p). **DOUBLE DIAMOND ST/LE, TIPPED 40p** (6p). side: no 78) All types £1.50 (6p).

**PICK-UP WIRE:** super thin twin flex screened, sheathed, 6p per yard (up to 6 yds., 6p. Over charges paid. **MICROPHONES:** CRYSTAL: LAPEL 1 1/2" clip/hand, lead 3-6min jack plug 85p (8p). CM20 Cream Plastic hand 52p (8p); MIC60 £1.08 (10p); CM70 "PLANET" Metal, tapered with neck cord, adaptor for stand £1.50 (10p); "MIC 91" hand/deak 81p (8p); "MIC 45" Curved metal hand grip £1.90 (10p) ALL with leads. **DYNAMIC:** 209 Cardioid Ball, 50K/600Ω built in volume control, on/off switch, special 20ft lead, the best value anywhere at 28.00 (30p); UDI30, Uni-dir mesh ball 50K/600Ω jack plug, cable, adaptor, 24.80 (20p); DM160, omni-dir, Ball mesh, 50K, cable adaptor, jack plug, 23.90 (30p each). **SPEAKERS:** Very popular 12" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) £1.87 1/2 (30p) or pair for stereo 24.25, charges paid. **SMALL 2 1/2, 3Ω, 8Ω or 64Ω** (state which) 40p (8p). More speakers in List. **HEADPHONES:** High 2 1/2, 3Ω, 8Ω or 64Ω (state which) 40p (8p). More speakers in List. **TRANSFORMERS:** 3-6mm (state which) jacks £1.00 (10p). **SOLDERING IRON:** Slim, modern, British high speed, 8 1/2", all parts replaceable, highest quality, fully guaranteed £1.17 1/2 (10p). **TRANSFORMERS:** Sub-min 11 x 11 x 12mm, OUTPUT (3Ω for OC72, etc.) 14p or DRIVE 16p (Up to 12 for 6p). **CONNECTING WIRE:** Packs of 5 coils, each coil 5yds, Ass'd. coils. **SOLID CORE 14p** (6p). **FLEXIBLE CORE 16p** (8p). **SUPER THIN** flexible for transistor wiring, etc. 14p (6p). **RETRACTABLE FLEXIBLE LEADS (CURLIES):** With phono plug, each end, 6ft. 24p, 12ft. 40p. With phono plug/phono socket other end 6ft. 26p, 12ft. 45p (6p lead any type). **VIBRATORS:** 12v/4 pin non-synch 121HD4, 2 1/2" ex. pins, 30p. SAME but any type). **NEONS, fly leads 10p. NEON SCREWDRIVER** (pocket tester) 17p (6p either). **MAINS BATTERY ELIMINATOR,** Input 240v-AC. Output 3, 4, 6, 7 1/2, 9 and 12 volt D.C. by switch selector. On/off switch, pilot lamp, leads, plug to suit most cassette receivers. 23.75 (25p). Highly suitable for all transistor receivers.

Our LIST (see heading or sent free on request with all orders) contains, in addition to many more of several of the above types of items, Cartridge and Stylus comparatives, Transistors special non-repeatable bargains, also details of car and portable aeriads, new Battery amplifiers (inc. stereo) Condensers, Eliminators, Dial, F.M. Tuners, Indicator lamps, Intercom, Telephone amplifier and telephone pick-ups, Meters, Mike inserts, Testers, Vol. controls, Microphone and other cable, etc., etc.



A special message to the Fumbling Fingered Feds among us

## NEW STEPHENSPEAKERS

A new range of loudspeaker kits and cabinets with a style and specification for every purpose. You'll be cheating a bit if you tell your friends "made it myself".

We supply superb craftsmen built fully finished cabinets in beautiful stain and scuff resistant vinyl in white or teak.

Just fit the speaker cloth (supplied) and screw in your speaker.

HIGH QUALITY AT LOW COST

Send for our free booklet "Choosing a Speaker"

STEPHENSPEAKERS, WILMSLOW AUDIO, Dept. 'PW', Swan Works, Bank Square, Wilmslow SK9 1HF

# HENRY'S - Your complete Semi-Conductor Store!

## INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS (I.T.T FAIRCHILD)




Type	1/11	12/24	26/99	Type	1/11	12/24	26/99	Type	1/11	12/24	26/99
8N7400	P	P	P	8N7450	0-20	0-18	0-18	8N74145	1-50	1-40	1-30
8N7401	0-20	0-18	0-18	8N7451	0-20	0-18	0-18	8N74150	8-26	2-95	2-16
8N7402	0-20	0-18	0-18	8N7453	0-20	0-18	0-18	8N74161	1-10	0-95	0-90
8N7403	0-20	0-18	0-18	8N7454	0-20	0-18	0-18	8N74163	1-35	1-27	1-20
8N7404	0-20	0-18	0-18	8N7460	0-20	0-18	0-18	8N74164	2-00	1-27	1-20
8N7405	0-20	0-18	0-18	8N7470	0-30	0-27	0-25	8N74165	1-55	1-47	1-35
8N7406	0-30	0-27	0-25	8N7472	0-30	0-27	0-25	8N74166	1-55	1-47	1-35
8N7407	0-30	0-27	0-25	8N7473	0-40	0-37	0-35	8N74167	1-80	1-70	1-50
8N7408	0-20	0-18	0-18	8N7474	0-40	0-37	0-35	8N74168	2-60	2-40	2-25
8N7409	0-40	0-37	0-35	8N7475	0-55	0-52	0-50	8N74169	2-60	2-40	2-25
8N7410	0-20	0-18	0-18	8N7476	0-75	0-70	0-65	8N74170	4-10	3-85	3-05
8N7411	0-20	0-18	0-18	8N7477	0-80	0-75	0-70	8N74172	2-00	1-85	1-80
8N7412	0-20	0-18	0-18	8N7478	0-80	0-75	0-70	8N74174	2-00	1-85	1-80
8N7413	0-30	0-27	0-25	8N7479	0-80	0-75	0-70	8N74175	1-80	1-65	1-50
8N7414	0-30	0-27	0-25	8N7480	0-80	0-75	0-70	8N74176	1-80	1-65	1-50
8N7415	0-30	0-27	0-25	8N7481	1-25	1-15	1-10	8N74177	1-80	1-65	1-50
8N7416	0-30	0-27	0-25	8N7482	0-87	0-80	0-75	8N74178	1-80	1-65	1-50
8N7417	0-30	0-27	0-25	8N7483	1-00	0-90	0-85	8N74179	6-25	6-00	5-10
8N7418	0-20	0-18	0-18	8N7484	0-90	0-85	0-80	8N74180	1-55	1-30	1-20
8N7419	0-20	0-18	0-18	8N7485	0-45	0-41	0-38	8N74181	7-00	6-00	5-50
8N7420	0-40	0-37	0-35	8N7486	1-00	0-97	0-95	8N74182	2-00	1-80	1-80
8N7421	0-40	0-37	0-35	8N7487	1-00	0-95	0-90	8N74184	2-50	2-25	2-00
8N7422	0-48	0-44	0-40	8N7488	0-80	0-75	0-70	8N74185	2-40	2-20	2-10
8N7423	0-48	0-44	0-40	8N7489	0-80	0-75	0-70	8N74186	2-40	2-20	2-10
8N7424	0-48	0-44	0-40	8N7490	0-80	0-75	0-70	8N74187	1-95	1-85	1-75
8N7425	0-48	0-44	0-40	8N7491	0-80	0-75	0-70	8N74188	2-00	1-80	1-80
8N7426	0-42	0-39	0-35	8N7492	0-75	0-70	0-65	8N74189	1-95	1-85	1-75
8N7427	0-42	0-39	0-35	8N7493	0-75	0-70	0-65	8N74190	1-95	1-85	1-75
8N7428	0-50	0-45	0-42	8N7494	0-80	0-75	0-70	8N74191	1-95	1-85	1-75
8N7429	0-50	0-45	0-42	8N7495	0-80	0-75	0-70	8N74192	2-00	1-80	1-80
8N7430	0-20	0-18	0-18	8N7496	1-00	0-97	0-95	8N74193	2-00	1-80	1-80
8N7431	0-42	0-39	0-35	8N7497	1-00	0-95	0-90	8N74194	2-50	2-25	2-00
8N7432	0-42	0-39	0-35	8N7498	1-00	0-95	0-90	8N74195	1-50	1-40	1-30
8N7433	0-70	0-61	0-54	8N7499	1-90	1-78	1-65	8N74196	1-50	1-40	1-30
8N7434	0-70	0-61	0-54	8N7500	2-50	2-30	2-00	8N74197	1-50	1-40	1-30
8N7435	0-65	0-60	0-50	8N7501	1-45	1-35	1-20	8N74198	4-60	3-70	3-35
8N7436	0-65	0-60	0-50	8N7502	1-45	1-35	1-20	8N74199	4-60	3-70	3-35
8N7437	0-65	0-60	0-50	8N7503	1-45	1-35	1-20				
8N7438	0-65	0-60	0-50	8N7504	1-45	1-35	1-20				
8N7439	0-65	0-60	0-50	8N7505	1-45	1-35	1-20				
8N7440	0-20	0-18	0-18	8N7506	1-45	1-35	1-20				
8N7441A1N	0-75	0-72	0-70	8N7507	1-45	1-35	1-20				
8N7442	0-75	0-72	0-70	8N7508	1-45	1-35	1-20				
8N7443	1-00	0-95	0-90	8N7509	1-45	1-35	1-20				
8N7444	2-00	1-75	1-60	8N7510	0-80	0-70	0-60				
8N7445	2-00	1-75	1-60	8N7511	1-00	0-95	0-90				
8N7446	1-75	1-60	1-45	8N7512	1-35	1-25	1-10				
8N7447	1-75	1-60	1-45	8N7513	2-70	2-55	2-40				
8N7448	1-75	1-60	1-45	8N7514	1-00	0-95	0-90				

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX  
 LARGER QUANTITY PRICES PHONE (01) 402 4891  
 TEXAS MAN BOOK NO. 2 700 PAGES DATA 60p. POST 20p.  
 HIGH POWER SN 74 LOO } for list No. 36  
 LOW POWER SM 74 LOO }

## A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA530 10p	BC147 12p	BU105 2.25	OC44 15p	T1843 35p	2N3055 55p
AA542 15p	BC169C 12p	BY100 15p	OC45 15p	V405A 25p	2N3440 75p
AAZ13 10p	BC182 10p	BY126 15p	OC67 15p	ZTX108 12p	2N3442 1.25
AC107 35p	BC214 15p	BY127 15p	OC71 15p	ZTX300 12p	2N3525 75p
AC126 25p	BC272 75p	BY213 35p	OC72 25p	ZTX301 15p	2N3615 55p
AC127 25p	BCY34 10p	CI06D 65p	OC77 45p	ZTX302 18p	2N3615 55p
AC128 25p	BCY39 1.00	CI06J 115 55p	OC81 25p	ZTX341 20p	2N3702 10p
AC129 25p	BCY42 30p	CI06K 25p	OC83 25p	ZTX500 15p	2N3704 10p
AC187 25p	BCY43 25p	CI06L 80p	OC140 55p	ZTX503 17p	2N3705 10p
AC188 25p	BCY65 2.50	LM309K	OC170 25p	ZTX601 30p	2N3714 1.80
AC197 30p	BCY70 1.50	(T03) 1.87	OC214 20p	ZTX602 20p	2N3771 1.75
ACY20 20p	BCY71 2.00	MAT121 25p	OC200 45p	ZNS27 35p	2N3773 2.50
ACY21 20p	BCY72 1.50	MJE340 50p	OC201 75p	ZNS28 15p	2N3790 2.25
ACY39 55p	BCY87 2.99	MJE370 70p	OC202 80p	ZNS29 15p	2N3819 35p
AD140 50p	BCZ11 50p	MJE520 75p	OC203 50p	ZNS29 15p	2N3820 50p
AD149 50p	BD44 80p	MJE2955	OC271 1.25	ZNS30 20p	2N3866 85p
AD161 35p	BD131 75p	OC272 1.50	OC272 1.50	ZNS31 25p	2N3873 15p
AD162 35p	BD132 80p	MJE3055	ORP60 40p	ZNS121 25p	2N3903 15p
AF117 20p	BF115 25p	MFP105 40p	P346A 20p	ZNS132 25p	2N4061 12p
AF118 50p	BF167 25p	NKT214 20p	RAB310A 45p	ZNS130 18p	2N4062 12p
AF124 25p	BF173 25p	NKT216 40p	RAS08A 45p	ZNS130 18p	2N4126 15p
AF139 30p	BF179 30p	NKT217 40p	TA A293 75p	ZNS130 18p	2N4871 35p
AF198 40p	BF180 30p	NKT403 70p	TIP29A 55p	ZNS130 18p	2N5457 80p
AF239 40p	BF194 15p	NKT404 50p	TIP29A 55p	ZNS130 18p	2N5777 55p
AF827 30p	BF195 15p	OA5 50p	TIP30A 60p	ZNS130 18p	2N6011 10p
AF828 25p	BF861 25p	OA10 35p	TIP31A 60p	ZNS130 18p	2N6012 10p
BA102 30p	BF898 25p	OA81 10p	TIP32A 70p	ZNS130 18p	2N6013 10p
BA115 75p	BFX13 25p	OA200 7p	TIP33A 1.00	ZNS130 18p	2N6014 10p
BA145 15p	BFX34 75p	OA202 10p	TIP34A 1.50	ZNS130 18p	2N6015 10p
BAX13 5p	BFX37 8.00	OC20 75p	TIP35A 2.50	ZNS130 18p	2N6016 10p
BAX16 7p	BFX88 20p	OC26 85p	TIP36A 3.00	ZNS130 18p	2N6017 10p
BC107 10p	BFY50 20p	OC32 85p	TIP41A 75p	ZNS130 18p	2N6018 10p
BC108 10p	BFY51 20p	OC35 40p	TIP42A 85p	ZNS130 18p	2N6019 10p
BC109 12p	BFY52 20p	OC38 65p		ZNS130 18p	2N6020 10p
BC113 15p	BFY90 55p	OC42 40p		ZNS130 18p	2N6021 10p
BC117 20p	BLX36 8.00	OC45 40p		ZNS130 18p	2N6022 10p
BC123 15p	BX20 1.50	OC48 65p		ZNS130 18p	2N6023 10p
BC143 35p	BSY27 15p	OC42 40p		ZNS130 18p	2N6024 10p

## INTEGRATED CIRCUIT SOCKETS

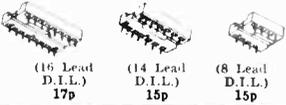

## QUANTITY DISCOUNTS

10% 12+ : 15% 25+ : ANY ONE TYPE  
 20% 100+ : 25% 250+  
 From above sections except Integrated Circuits and Special Offers where discounts are included.  
 Minimum order value £1 please.  
 Postage 7p on all orders.

## SPECIAL OFFERS! SEMI-CONDUCTORS

<b>BFY90</b>	1000 MC/S	59p	2N2926	10p	
25	+ 20p		All Colours		
100	+ 17p		25	+ 9p	
500	+ 15p		100	+ 8p	
			500	+ 5p	
			1000	+ 5p	
<b>AF117</b>	Mullard	25p	2N3819	Texas	35p
25	+ 17p		25	+ 30p	
100	+ 15p		100	+ 25p	
500	+ 12p		500	+ 20p	
			1000	+ 15p	
<b>OC170</b>	Mullard	25p	BC107, BC108, BC109	10p each	
25	+ 20p		All Makes		
100	+ 18p		25	+ 8p	
500	+ 15p		100	+ 7p	
1000	+ 13p		500	+ 6p	
			1000	+ 5p	
<b>BY127</b>	Mullard	15p	AD161, AD162	35p each	
25	+ 12p		25	+ 32p	
100	+ 10p		100	+ 28p	
500	+ 9p		500	+ 25p	
1000	+ 8p		1000	+ 22p	
<b>OA202</b>		10p	2N3055	20p	
25	+ 8p		25	+ 50p	
100	+ 7p		100	+ 45p	
500	+ 6p		500	+ 38p	
1000	+ 5p		1000	+ 33p	
<b>OC35</b>	Mullard	50p	2N3055	55p	
25	+ 45p		25	+ 50p	
100	+ 40p		100	+ 35p	
500	+ 35p		500	+ 30p	
1000					

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 9p per word (minimum 12 words), box number 10p extra. Semi-displayed setting £6.50 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

## Service Sheets

### ★ SERVICE SHEETS • MANUALS • BOOKS ★

**SERVICE SHEETS** OVER 12,000 SERVICE SHEETS AND MANUALS IN STOCK ON RADIOS, TV'S, R.PLAYERS AND T.RECORDERS, ETC.. **SERVICE SHEET** 30p + Postage Catalogue 20p.

NEW BOOKS & PUBLICATIONS	PRICE + P. & P.
32. SIMPLE SHORT WAVE RECEIVERS by Data Publications Ltd. 140 pages . . . . .	£0.80 10p
33. RADIO CONTROL FOR MODELS by Data Publications Ltd. 192 pages . . . . .	£0.75 12p
34. RADIO VALVE AND TRANSISTOR DATA 9th Edition by A.M. Ball. 340 pages . . . . .	£0.75 15p
35. GUIDE TO BROADCASTING STATIONS 16th Edition. 160 pages . . . . .	£0.50 8p
36. TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard Ltd. 230 pages. New Edition.	£1.80 15p
37. 1971-72 MULLARD DATA BOOK. Data on Valves & Semiconductors . . . . .	£0.33 7p
38. SERVICING WITH THE OSCILLOSCOPE by G.J. King. 176 pages . . . . .	£1.80 15p
39. PRACTICAL OSCILLOSCOPE HANDBOOK by R.P. Turner. 230 pages . . . . .	£4.20 30p
40. MEASURING OSCILLOSCOPE by J.F. Golding. 272 pages . . . . .	£0.60 10p
41. QUESTIONS AND ANSWERS ON TRANSISTORS by C.Brown. 96 pages . . . . .	£2.50 20p
42. SEMICONDUCTORS: BASIC THEORY AND DEVICES by I. Kampel. 272 pages . . . . .	£1.00 10p
43. UNDERSTANDING THE SEMICONDUCTOR by C.N. Matthews. 128 pages . . . . .	£2.25 15p
44. TAPE RECORDERS by H.W. Hellyer. Guide to Purchase & Operating. 239 pages . . . . .	£2.10 20p
45. PHOTO-ELECTRONIC DEVICES by J.B. Dance. 165 pages . . . . .	£0.55 10p
46. AUDIO AMPLIFIERS by Data Publications Ltd. 128 pages . . . . .	£1.50 15p
47. RAPID SERVICING OF TRANSISTOR EQUIPMENT by G.J. King. 160 pages . . . . .	£1.00 15p
48. BEGINNER'S GUIDE TO ELECTRICITY by Clement Brown. Assoc. Brit. I.R.E. . . . .	£1.00 15p
49. BEGINNER'S GUIDE TO ELECTRONICS by Terence L. Squires. AMI.E.R.E. . . . .	£1.00 15p
50. BEGINNER'S GUIDE TO TRANSISTORS by J.A. Reddough. . . . .	£1.50 15p
51. PRINCIPLES OF SEMICONDUCTORS by M.G. Scroggie. B.Sc. C.Eng. F.I.E.E. 156 pages . . . . .	£2.70 20p
52. THE PRACTICAL AERIAL HANDBOOK by G.J. King. 232 pages . . . . .	£4.50 35p
53. AERIALS by D.J.W. Sibbema. Practical Work. 110 pages . . . . .	£3.20 25p
54. ELECTROACOUSTICS: MICROPHONES, EARPHONES AND LOUDSPEAKERS. 300 pages . . . . .	£0.80 10p
55. MAGNETIC TAPE RECORDING by H.G.M. Saxon. B.Sc. F.I.E.E. 368 pages . . . . .	£3.75 30p
56. MICROPHONES by A.E. Robertson. M.B.E.E., B.Sc. M.I.E.E. 259 pages . . . . .	£2.00 20p
57. THE HI-FI AND TAPE RECORDER HANDBOOK by G.J. King. 304 pages . . . . .	£2.50 20p
58. PRINCIPLES OF AERIAL DESIGN by H. Page M.Sc. F.I.E.E. 182 pages . . . . .	£2.80 20p
59. A.C. MOTOR CONTROL by R.T. Lythall. C.Eng. F.I.E.E. 146 pages . . . . .	£3.50 20p
60. INTEGRATED CIRCUIT SYSTEMS by D.J. Walter. 234 pages . . . . .	£3.00 25p
61. SOLID-STATE DEVICES AND APPLICATIONS by R. Lewis. 264 pages . . . . .	£2.50 15p
62. GUIDE TO PRINTED CIRCUITS by G.J. King. 140 pages. 95 Illustrations . . . . .	£1.40 15p
63. ELECTRONIC COUNTING CIRCUITS by Mullard Ltd. 224 pages . . . . .	£0.50 12p
64. PRACTICAL INTEGRATED CIRCUITS by A.J. McEvoy and L. McNamara. 144 pages . . . . .	£1.50 15p
65. POWER ENGINEERING USING THYRISTORS VOL.1. by Mullard Ltd. 228 pages . . . . .	£1.50 15p

Send S.A.E. for free LISTS of Practical and Technical Books on Radio & Television now available to

## BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorks. Tel. 0423-86844

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 40p each

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS" Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

**C. CARANNA**  
71 BEAUFORT PARK  
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS. 35p, plus stamped addressed envelope. Mail order only. Lesmar, 15 Conholt Road, Andover, Hants.

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

## Hi-Fi Equipment

# Peerless

## HI-FI LOUDSPEAKERS

... Acclaimed by the Experts

### MULTI-UNIT SYSTEMS

### IN KIT FORM

### MATCHING CABINET KITS

### ALSO AVAILABLE

Full details & address of your local dealer from:

**P.F. & A.R. Helme Ltd. (Dept PW11)**  
Summerbridge: Harrogate HG3 4DR  
Yorks. Tel. Darley 279 (STD 0423-72)

## Tape Recorders

### ROBIN HOOD

(NOTTM) LTD.

Special Offer—First Class British Made Non-stretch Mylar Tapes  
 5 1/2 ins. 1/2" x 900ft. 55p  
 5 1/2 ins. 1/2" x 1200ft. 60p  
 7 ins. 1/2" x 1200ft. 60p  
 7 ins. 1/2" x 1800ft. 85p  
 15p Min. Handling Charge, Inland  
 23 Wadham Road, Woodthorpe, Nottingham

## Aerials

### GENUINE FULL SIZE

### 18 element TV aerial

as used by leading TV companies

FOR ONLY **£1.99**

+ 1p carr



Guaranteed Perfect Pictures. Save £25. We supply this genuine U.H.F. aerial for only £1.99, can be fitted out side or inside. Quality made, technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions, advice

Money Back Refund Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters.

Send direct to Dept PW10, 219 Mansfield Rd., Nottingham.

**IMPERIAL TRADING (AERIALS) LTD.**  
The quality Aerial Specialists

BAINES FOR HIGH FREQUENCY AERIALS  
 UHF Multibeams by J Beam  
 MBM 10 £2.20 MBM 18 £2.90 MBM 30 £3.90 MBM 46 £6.00 2MBM 46 £15.20  
 4MBM 46 £33.00. UHF Diplexers £1.00. L.O. Periodic £5-25.  
 VHF Aerials  
 FM2 £2.00 FM3 £3.00 FM4 £5.00 FM05 £7.80 BBCD and ITA 5 £2.70 ITA 5 element £2.00 ITA 8 element £2.70.  
 Pre-amps:  
 Masthead £7.00 Colourbooster £3.88 Wide-band Masthead £9.50 Co-ax VHF 5p UHF 9p.  
 Please state channels on all orders  
 R Baines  
 11 Dale Cres., Tupton, Chesterfield. S42 6DR

Direct from the Manufacturers

## U.H.F. AERIALS

in EASY ASSEMBLY KITS

10 Element **SAVE 40%**

£1.25 on normal retail price

14 Element £1.50 18 Element £1.75

Most Cable optional extra

Ready assembled add 20p allow 32W. carriage and packing. Please state which channel or group.

**APEX AERIALS (P.W.)**  
ALBAN WORKS, MARY ST. JOHNSTONE, HENFREWSHIRE



## Books and Publications



# THE PICTURE BOOK METHOD OF LEARNING

**BASIC ELECTRICITY 5pts £4.50. BASIC ELECTRONICS 6pts £5.40. BASIC TELEVISION 3pts £3.60**

(Postage and Packing included)

The Pictorial Approach Manuals assure the quickest and soundest method of gaining mastery over these subjects. The clear and concise illustrations make study a real pleasure. Your money refunded if not completely satisfied is your 100% Guarantee. Free Illustrated Prospectus on request.

Send now to **SELRAY BOOK CO., 60 HAYES HILL, BROMLEY BR2 7HP**

**"HOW TO LISTEN TO THE WORLD",** Published October 1972, £1.90, post 10p. Direct from World Publications' Warehouse. Order from: David McGarva, Box 114E, Edinburgh EH1 1HP.

### Educational

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

**CIE, AMSE, City & Guilds, etc.** Thousands of exam successes. Postal Courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept H.8), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

**RADIO, TV, RTEB CERTS.,** City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Details of home study courses and illustrated book FREE: BIET (Dept. H.7), Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

### Situations Vacant

## RADIO OFFICERS

**DO YOU HAVE PMG I, PMG II, MPT 2 YEARS OPERATING EXPERIENCE?**

Possession of one of these qualifies you for consideration for a Radio Officer post with the Composite Signals Organisation.

On satisfactory completion of a 7-month specialist training course, successful applicants are paid on scale rising to **£2365 pa**; commencing salary according to age—25 years and over **£1664 pa**. During training salary also by age, 25 and over **£1238 pa** with free accommodation.

The future holds good opportunities for established status, service overseas and promotion. Training courses commence at intervals throughout the year. Earliest possible application advised.

Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered. Full details from:

**RECRUITMENT OFFICER (TRO 37),** GOVERNMENT COMMUNICATIONS HEADQUARTERS,

Room A/1105, Oakley Priors Road, CHELTENHAM, Glos. GL52 5AJ  
Telephone: Cheltenham 21491, Ext. 2270

## £2500 career Yours in 6 weeks?

Yes. That's all the time it takes ACT to turn a person with the aptitude into a qualified Computer Programmer. Able to hold down a responsible, well-paid job in the world of computers. And our own exclusive appointments agency will introduce you to all the right connections. FREE. We've already trained vast numbers of people; pointed them in the direction of success and life-long security. Write or phone TODAY for FREE details without obligation.

**ACADEMY OF COMPUTER TRAINING,**  
E94, Oxford House  
9-15, Oxford Street, W.1.  
Telephone: 01-734 2874  
127, The Piazza, Dept. E94,  
Piccadilly Plaza, Manchester 1.  
Telephone: 061-236 2935

**ELECTRIC SALESMAN** needed in N.W.1. £22.00 P/W plus commission an PROFIT SHARING to the Right Man age over 22 years with driving licence. Phone Anytime 485-5322 or 272-1231.

### For Sale

**QUAD 303 stereo amplifier** excellent condition £30 o.n.o. 17, The Avenue, Hailsham BN27 3HT. Telephone Hailsham 842 456.

**CLOSED CIRCUIT TV** as new 11in Monitor, with Camera, in perfect working order £140. Tel. Coventry 27164 or write Box 106.

### MORSE MADE EASY!!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. In 4 weeks guaranteed.

Beginner's Section only **£3.80**, Complete Course **£4.50** (Overseas £1.00 extra) details only, 4p stamp. 01-660 2896  
GSHSC (Box 10), 45 GREEN LANE, PURLEY, SURREY

**YUKAN SELF-SPRAY AEROSOL WAX**  
Get these **OR** **BLACK WRINKLE NOW!** **OR** **CRACKLE** finishes

DEPT PW 11 YUKAN, 307a EDGWARE ROAD, LONDON W2 1BN

Closed all December for annual holiday

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**TELEPHONE ANSWERING** machines. New and Reconditioned. £55/160. STAM Co., 182a New North Road, N1. 01-286 6119.

### Wanted

**TOP PRICES PAID** for NEW VALVES popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C),**  
367 Kensington Street, Bradford 8,  
Yorkshire.

**HIGHEST POSSIBLE** cash prices for Akai, B. & O., Brenell, Ferrograph, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

**CASH PAID** for New Valves. Payment by return. **WILLOW VALE, ELECTRONICS,** 4 The Broadway, Hanwell, London, W.7. 01-567/5400-2971.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

**PRACTICAL WIRELESS** required 1939 to 1944 inclusive, also Wireless World, 1939 to 1942 inclusive. Condition and price to The Librarian, Technical Services (Luton) Ltd., Cutenhoe Road, Luton, Beds LU1 3NG.

**316-04 and E.3016 i.c.s.** Reader requires a few. Dec, 87 Taunton Road, London S.E.12.

### Ladders

**LADDERS.** Timber 20ft, £7.80; 29ft, £11.20. Carr. 80p. Brochure (Dept. WLS), Home Sales, Baldwin Road, Stourport, Worcs. Callers Welcome. Phone 02-993 5222. Ansafone installed.

### Receivers and Components

**SOUND SUPPLIES** (Electronics) Co. Ltd.

P.A. EQUIPMENT. Marshall amps, instruments and guitars, etc. TOA and Eagle amps and accessories, Reslo mics, etc. COMPONENTS: Resistors, capacitors, plugs, sockets, cables, audio leads, semi-conductors, valves, vero board, etc., for the constructor.

Power packs and car droppers for the cassette recorder or radio. S.A.E. for list and enquiries. P.A. list 15p. 12 Smarts Lane, Loughton, Essex. Tel. 01-508 2715 Closed all day Thursday

**BRAND NEW COMPONENTS BY RETURN.** Electrolytics 16V or 25V—1, 2, 2, 4, 7, 10 mfd— $3\frac{1}{2}$ p, 22, 47—4p, 100—5p, 50V— $\frac{1}{2}$ p extra. Subminiature bead-type tantalums—1/35V, 22/35V, 47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V—.001, .002, .005, .01, .02—2p, .04, .05—2 $\frac{1}{2}$ p, .068, .1—3p. Polystyrene 63V—10 pf.—10,000 pf. E.12 series—2p. Mullard miniature Carbon Film Resistors E12 series 1/3W 1 $\Omega$ —10M $\Omega$  8 for 5p. Insured postage 8p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

# NIP-E-BOARD

## PRINTED CIRCUIT SYSTEMS

### FOR DISCRETE COMPONENTS AND CIRCUITS

Standardised multi-purpose boards  
**SAMPLE PACKS—3 DIFFERENT SIZES WITH FULL DETAILS IN EACH**  
 SRBP Undrilled 95p Drilled £1-84  
 GLASS FIBRE Undrilled £1-09 Drilled £2-15  
 Please state whether for i.c.s or discrete transistors.  
**SPECIAL OFFER! FREE Mounting Pillars with above packs.**  
**STARTER PACKS of mixed undrilled boards (small) 50p & 70p**  
**CARD HANDLES—5p, Gold plated Edge Connectors 14-way 35p**  
 Insulated Mounting Pillars— from 3p each. 30-way 68p

**PLANNING CHART SUPPLIED WITH BOARDS**

Quantity discounts. We supply retail trade, industry, export, schools

**NIP ELECTRONICS** DEPT. NE/W, P.O. Box 11, St Albans, Herts

Versatile  
**10 in ONE**



**"MINI-LAB"** Comprising  
 AC/DC Voltmeter : Audio Generator :  
 Resistance Substitution : Capacitance  
 Substitution : DC Ammeter : Battery  
 Supply : RF Signal Generator : RF  
 Field Strength Indicator : Ohm Meter

All you need for testing. Money  
 back guarantee. **£11-25**  
 + 25p P. & P.

Cash with order or write for data sheet to:  
 RSL Components, (Dept. PW),  
 Cricketfield Lane, Bishops Stortford, Herts

## PRECISION POLYCARBONATE CAPACITORS

### FRESH STOCK — FULLY TESTED

Close tolerance. High stability. All 63V d.c.

0.47µF:	±5% 80p;	±2% 40p;	±1% 50p
1.0µF:	±0% 40p;	±2% 50p;	±1% 60p
2.2µF:	±0% 50p;	±2% 40p;	±1% 75p
4.7µF:	±0% 50p;	±2% 40p;	±1% 11.15
6.8µF:	±5% 95p;	±2% 11.15;	±1% 21-80
10µF:	±5% 11.10;	±2% 11.40;	±1% 21-80
10µF:	±5% 21.80;	±2% 22.10;	±1% 22-70

### TANTALUM BEAD CAPACITORS

Values available 0.22, 0.47, 1.0, 2.2, 4.7, 6.8  
 µF at 35V, 10 µF 25V, 15 µF 20V, 22 µF  
 15V, 33 µF 10V, 47 µF 10V 33V—all  
 at 9p each, 5 for 50p; 14 for £1. Special pack  
 6 off each value (72 capacitors) £5.

### NEW! TRANSISTORS. BC107, BC108, BC109.

All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices.

### POPULAR DIODES IN914—7p each, 8 for 50p; 18 for £1.

IN916—9p each, 6 for 50p, 14 for £1. IS44—5p each, 11 for 50p, 24 for £1. All brand new and marked.

### SPECIAL OFFER—400 mW Zeners.

Values available 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ± 5% at 5 mA. All new and marked. Price 12p each, 5 for 50p, 12 for £1.00.

### RESISTORS.

Carbon film 1WV 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

### 440V A.C. CAPACITORS.

0.1µF, size 1 1/2 in x 1 in, 25p; 0.25µF, size 1 1/2 in x 1 in, 30p; 0.47 and 0.5µF, size 1 1/2 in x 1 in, 35p; 1.0µF, size 2 in x 1 in, 45p; 2.0µF, size 2 in x 1 in, 75p each.

### C.D.I. (CAPACITOR DISCHARGE IGNITION)—440V A.C. capacitors listed above are ideal for use as discharge capacitors in popular ignition systems. Approved for P.E. Scorpio and P.W. (June 1971) systems. Improved reliability.

5p post and packing on all orders below £5.  
**V. ATTWOOD, DEPT. D2, P.O. Box 8, ALRESFORD, HANTS.**

## NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft amateurs, mobile radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3-50 + p. & 10p U.K. only.  
 Illustrated catalogue of selected kits and components. 15p P&F free.

**Galleon Trading Co.,**  
 12, Burra Way,  
 Coringham,  
 Stanford-Le-Hope,  
 Essex.

## MINI MAINS PACK KIT.

Safe double-wound mini transformer, silicon rectifiers, 1000µF smoothing, instructions. Buildable to size of PP6 etc. 9V, 120mA. £0.40. U.K. post 5p. Mail order only. **AMATRONIX LTD.,** 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

## RADIO SPARES (R.S.) COMPONENTS

specified for projects in this, and other maga-ines supplied on request. SAE with all enquiries. The Hobbies Shop, 32 The Parade, Cwmbran Town Centre, Cwmbran, Mon.

## ELEVEN BAND RADIO. SW1-4 (4-30 MHz).

Marine. LW, MW, FM, PB (76-86). Aircraft (180-136). PB (148-174). Battery/Mains. BFO. AGC. Squelch Control. Output: 1.3W. 15in x 10in x 5 1/2 in. £68. Eight Band Model, with BFO, £42. Four Band, MW, FM. Aircraft. PB. £15. SAE. Full Lists. Langtons Radio, High Street, ROCESTER, Staffordshire, Tel. 338.

## INCOMPARABLE V.H.F. KIT


Johnsons CV2—unique triple-purpose (Converter, Receiver, Tuner-Feeder) kit for the Amateur enthusiast. Fantastic transistorized performance. World Wide Sales. Complete kit of top grade parts with coils covering 80-180 MHz, plus easy/build diagrams and instructions. £4 direct from makers or S.A.E. for free literature.

**Crystal Set Kits**—one or two waveband now available. Send S.A.E. for free literature. See also advert. on page 661.

## JOHNSONS (RADIO)

St. Martins Gate, Worcester, WRI 2DT  
 Est. 1943 (a John Banner Co. Tel. 24864)

## Trampus electronics

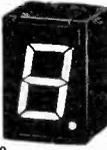

All Brand New. Money Back Guaranteed. Fast Service.

5V DIGITAL INDICATOR  
 O-9DP, with socket and reel Filter £1.45, 7447 £1.49.

IC GAS DETECTOR. Smoke, Butane, Vapour, etc. £2.19,  
 data 9p. ULTRASONIC TRANS-  
 DUCER. Transmits or receive,  
 £2. LIGHT EMIT DIODES.  
 Visible red/panel clip/data, 28p.  
 INFRARED (invisible beam), £1.19.

DIGITAL CLOCK integrated circuit, 28 pin DIL  
 12/24 hr. 4/8 digit. £13.87, data 15p.  
 CALCULATOR, electronic, 8 digit, 4 function + constant. Year guarantee, fully built £45.

PW TEXAN KIT less chassis £21.49. PAERS, ic/semi-conductor 28. Caps. £2.49. Res. £1. Transformer 22-07. TIP 41/42 pair £2. 741/748 38p ea.

INTEGRATED CIRCUITS with 14 pin DIL 28p,  
 741 Op amp 11p, 749 709 TOS 21p, DIL 28p,  
 710 38p, 748 38p, PHOTO DETECTOR/amp 44p,  
 VOLTAGE REGULATORS: 11 amp 5 or 12 v. type  
 £1. 723 50p, 555 TIMER/stab oscillator £1.19.

AUDIO AMP 3.5W H.F. etc. £1.24. Stereo Dual  
 Pre-amp £1.87, MPX Decoder for any FM RX £2.69.  
 74N: Data Booklet 12p, decoder 7400 etc. 16p, 7400  
 50p, 7400 28p, 7400 28p, 7492 73p, 7413 29p.

28 PIN SOCKETS: profile 14 or 16 pin, for 74N, 18p.

SEMICONDUCTORS  
 2N3055, 39p, BC107, 8p, BC108, 7p, BC109, 8p,  
 AC125/6/7, 15p, 2N3819, 28p, 2N3819, 15p,  
 AD101/2, 35p, BC167/8/9, 17p, BC177/8/9, 15p,  
 BC192/3/4, 15p, BC239/40/41, 15p, BCY70, 18p,  
 2N3015/152, 17p, 2N3819, 15p, 2N3819, 15p,  
 2N3819, 28p, 2N2926, 0.5p, 2N3055, 17p,  
 2N3028/3/4/5/6/7, 11p, 2N3078/9/10/11, 9p.

1A RECTS: 60V 4p, 400V 8p, 500V Bridge 20p.  
 1N914 5p, OA81/91 7p, OA200/202 10p.

ZENERS: BZ788 400mW 11p, 5.1V/10W 28p,  
 MINI 80V 44/400V 45p, TRIAC 6A/400V 87p.

CAPACITORS: 25/30V Electrolytic.  
 1050/100µF, 5p; 200/500µF, 8p; 1,000µF, 15p  
 DISC: 22pF thro' to 0.047µF, 3p; 0.01 to 0.0p,  
 RESISTORS 1W 5%, 1p. PRESETS 0.25W, 5p,  
 VERO 16p/23p, etc., DIN plugs, 13p; sockets, 9p.  
 Stereo Amp, in case, £14.87. Light Dimmer, £3.  
 ELECTRONIC CAR IGNITION KIT, £6.87.  
 FREE CATALOGUE, SAE, Data sheet. 6p ea.  
 CWO. P & P 7p. Overseas 35p. Discount 10+10%  
 P.O. Box 29, BRACKNELL, BERKS.

## UNUSED COMPONENTS.

Excellent variety. £1 per hundred. Postal only. Chaplin, 5 Berts House Hill, Wheat-hampstead, Herts.

## Build the TEXAN hi-fi amp

Kit price only  
 £28-50  
 (incl. case)



PACK 1. RESISTORS	80p
PACK 2. SMALL CAPS	£1-50
PACK 3. LARGE CAPS	£1-10
PACK 4. SUNDRIES	£1-90
PACK 5. SWITCHES	80p
PACK 6. CONTROLS	£1-45
PACK 7. SEMI COND	£8-25
PACK 8. TRANSFORMER	£4-95
PACK 9. P.C. BOARD	£2-50
PACK 10. CHASSIS etc.	£4-20

Post extra—parts available separately.  
 Send for list.

Kits also available for  
 ★ Radio Control Systems  
 ★ Digital Clock Systems  
 ★ Integrated Circuit Amplifiers (to 50W)  
 ★ Hi-Fi Pre-amps  
 ★ Stabilized Power Supply Units

TELERADIO HI FI, 325 Fore Street,  
 London, N.9.  
 01-807 3719

## New Full Spec. Devices By Return Money Back Guarantee

MICROCIRCUITS: 709 28p; 710 36p; 723 65p; 741 28p;  
 748 37p; SN76013 £1.24; 74 SERIES TTL: 00 16p;  
 01 18p; 02 18p; 04 18p; 10 16p; 11 21p; 20 16p; 30 13p;  
 40 16p; 47 13.35; 51 18p; 72 30p; 73 41p; 74 33p; 75 44p;  
 81 £1.26; 86 41p; 90 72p; 91 £1.21. TRANSISTORS:  
 2N2926 red 6p; 2N3819 28p; MEL 11 85p; MEL 12  
 44p; DA001 55p; 1 AMP RECTIFIERS: 50V 31p; 100V  
 4p; 200V 5p; 400V 6p; 600V 9p; 800V 12p; 1000V 14p;  
 W005 23p; W01 24p; W02 25p; W04 27p; W05 26p  
 0413 14p; 1002 10p; 4101 10p; 4102 11p; 4103 10p; 6002  
 14p; 6101 14p; 6102 15p; 8003 15p; M1811 32p; M1812  
 42p; OC4 12p; OC45 12p; OC71 12p; OC72 12p; OC81  
 12p; M1P 104 42p; 2N3819 28p; MEL 11 85p; MEL 12  
 44p; DA001 55p; 1 AMP RECTIFIERS: 50V 31p; 100V  
 4p; 200V 5p; 400V 6p; 600V 9p; 800V 12p; 1000V 14p;  
 W005 23p; W01 24p; W02 25p; W04 27p; W05 26p  
 ZENERS: 4.7, 5.1, 6.2, 6.8, 8.2, 9.1, 10, and 12 VOLT  
 11p each. 1 WATT 5% ZENERS: 15V & 30V, 17p each.  
 DIODES: 1N914 3p; 1N915 4p; 1N4148 4p; OA5 17p;  
 OA47 7p; OA10 6p; OA91 5p; OA200 7p; OA202 8p;  
 SCR: 800V 16A, BTX30-600 75p; LED PANEL LAMP  
 45p. FERRITE BEADS 1p. SOLDERCISE IC PIN  
 SOCKETS 0.7p per pin any length. PC RESIST PEN 80p.  
 14 PIN DIL SOCKETS 14p. MICROHM Resistors 41p.

JEP ELECTRONICS (P.W.11)  
 York House, 12 York Drive, Grappenhall, Warrington,  
 WA3 2EJ. Mail Order Only. C.W.O. P. & P. per order.  
 0/Seas 65p. Discounts start at 10% for 10+

## COMPONENTS GALORE.

Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 incl. postage C.W.O. to Caledonian Components, Fosterton Firs, Strathore Road, Thornton, Fife.

## COMPUTER PANELS

Panel contains 2 x Mullard OC23 Transistors and 5 other Transistors etc. 2 panels 50p p.p. 15p. Panel contains 2 x Mullard OC28 Transistors 2XBCY34, etc. 2 panels 50p p.p. 15p. Assorted Computer Panels contains many useful Transistors, Diodes, Trim Pots, etc. 4 panels for £1 post free. Assorted Panels contains minimum of 10 integrated circuits, also Transistors, Diodes etc. £1 p.p. 15p. Electrolytic Capacitors 1F/V. 2000/35, 10,000/15, 10,000/5, 12,500/35. All at 30p each p.p. 6p. 2,000/50, 2,000/40, 2,000/50, 10,000/50, 12,500/50, 50,000/15 all at 40p each p.p. 10p. Also available wide range motor start capacitors also block paper, etc. Assorted miniature and subminiature Electrolytic Capacitors, 100 for £1-20 p.p. 15p.

Mail Order only

## XEROZA RADIO

1, East Street, Bishops Watton, Devon  
SEND YOUR EXACT REQUIREMENTS

## THE WORLD RENOWNED "GLOBE KING" SHORT WAVE RADIO KITS now back in production!

New, exciting range of short-wave units covering 10 to 350 metres. Transistor 9v. and AC mains versions. Ideal for Plats etc.—range the World with just 25" length of wire or Rod aerial! Acclaimed by professional and amateur alike "Globe-King" receivers are in use all over the world. Modern technique plus a precision mechanical standard opens up a new era for this famous product. Send for free copy of our interesting literature, price lists, and order form—kindly enclose self-addressed long envelope. Overseas inquiries must be accompanied with International Reply Coupon. (See also our advert on page 660).

## JOHNSONS (RADIO)

St. Martins Gate, Worcester, WRI 2DT  
(a John Banner Co.)

## SURPLUS STOCK AT REDUCED PRICES

Cs — Rs — Transistors — small  
3v Electric Motors—Relays—  
Transformers—Plugs—  
Sockets—Etc.

Send S.A.E. for list.

W.E.C LTD.  
HIGH STREET, RIPLEY,  
SURREY

## RESISTORS

300 5% and better 60p (15p); 200 5% Hi-Stabs 60p (15p); 100 1% and 2% Hi-Stabs 40p (8p); 100 Multi Oxide 50p (7p); BC10 1% 30p each set for £1; 2K3055 40p; LA709C 25p; AA741C 25p; Reed Switch Unit contains 31 25p; 1A Reed. Resistors; Sockets etc. £1.25. (25p); 2 for £1.65 (35p); Ferric Chloride 1lb 40p (15p); 10lbs £3.50 (50p); Metex 3 1/2 1mA 75p (15p); 121-0-124µA 2 1/2 £1 (15p) other types available up to 7 1/2 x 6 1/2". Cased Tape Amplifier, complete with Speaker and Non-Standard Deck £3 (£1). TMC New Key-switches 4C/O + 4C/O Locking 40p (5p).

## GREENWELD (PW6)

24 Goodhart Way  
West Wickham, Kent. 01-777 2001  
Postage in brackets. SAE List. Details.

AARVAK ELECTRONICS Soundlight.  
Convertors 3 Channel 1.2kW £17. 3kW  
£25. Strobes 1 Joule £16. 4 Joule £25.  
Mail or call, 74 Bedford Ave., Barnet,  
Herts. 01-449 1268.

## TV Line out-put transformers

Replacement types ex-stock.  
For "By-return" service, contact:  
London: 01-948 3702  
Tidman Mail Order Ltd., Dept. PW,  
236 Sandycombe Rd., Richmond, Surrey  
TW9 2EQ  
Valves, Tubes, Condensers, Resistors,  
Rectifiers and Frame out-put Transformers  
also stocked.  
CALLERS WELCOME

## B.H. COMPONENT FACTORS LTD. DEPT. PW.

For Eagle, Sinclair, Data Books and Components 1W 5% resistors 1p. or 50p/100. Electrolytic C26 4/40, 8/40, 10/16, 32/10, 25/25, 100/6.4 all 4p. IN914 6p. 100V 1A Bridge 35p. Panel neon 15p. Mains Transformers 32-0-32 at 150mA 50p. Bargain Electrolytics, send for list. Electrolytic 100/50 10p, 500/25 10p, 1000/12 12p, 1,000/25 25p, 1,000/50 35p, AL914 30p, 7,400/01/10/30 15p. Free list. CWO pp 10p. Discount £10-10%. Money back guarantee. Brand new to spec. P.O. Box 18, Luton, Beds, LU1 1SU.

## AUDIO AMPLIFIERS

Mullard Module LP1153 1/2 watt output into 8 ohms, 9v. supply, brand new with data 70p post paid. Power Integrated Circuits BH 2 watts into 8 ohms, 11/16v. supply, 5mV sensitivity, size 2 x 1 x 1 1/2 inch, brand new with mounting clips & data £1.10 post paid. SAE for lists. J. WUILLE, 17 Ryecroft Close, Goring-by-Sea, Sussex.

RECEIVERS and accessories. B40/62B fine-tuning, S-meter and product detector kits and information. SAE details. P. R. Gollidge, G3EDW, Glen Tor, Torrington, Devon. Tel: 08-052 2411.

HEADPHONES. Matching 9R59DS, EC10 and all low impedance receivers. Luxury lightweight adjustable, foam padded. Japanese: £2-60. Partridge Electronics Ltd., Broadstairs, Kent.

NEW POTENTIOMETERS, 4p. Resistors, 50 16p. Magnetic counters 10p. 6BA Bolts 10p 100. Samples and lists 20p. Post extra. We buy communications receivers for cash. S.a.e. Derwent Radio, Scarborough.

## Miscellaneous

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5-50 NOW  
(S.A.E. for details)

TO: 'BOFFIN PROJECTS'  
DEPT. KW2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

RECORD TV SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. CROWBOROUGH ELECTRONICS (P.W.), Eridge Road, Crowborough, Sussex.

EXPERIMENTERS! Hundreds unusual items at Grimsby Electronics, Lambert Road, Grimsby, Lincs. Catalogue 5p.

# Darned Electronic Wizardry by Dewtron

Famous kits, e.g. waa-waa complete kit £2-95; Fuzz kit £4-75, auto rhythm, modules from £18 per set. Ring Modulator modules £7 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown Dorset.

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p post free.

## AERIAL BOOSTERS

We make four types of Aerial Boosters. L45 62 5 UHF, L12 VHF 405, L11 VHF Radio L10 M/W & S/W. Price L45, L12 & L11 £2-95, L10 £2-45.

## VALVE BARGAINS

Any 5-45p. 1A-70p:  
ECC82, ECL80, EF80, EF85, EF183, EF184, EBF99, EB91, EY86, PCC84, PCC89, PC97, PCF80, PCF86, PCL82, PCL83, PCL84, PCL85, PL36, PY33, PY82, PY800, PY801, 30L15, 30C15, 6-30L2.

## 19" UHF/VHF TV £7-50 THORN 850 SERIES

Untested but with complete set of spare valves. Price £7-50. Carriage £1-50.

## 100 MIXED RESISTORS 60p

From 1/2 watt to 2 watt and from 10-ohms to 10m-ohms our choice.

## 100 MIXED CAPACITORS £1

From 220PF to 200MFD and from 12v/w to 500v/w—our choice.

POST & PACKING under £1-5p. Over £1-10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

## VELCO ELECTRONICS

62B Bridge Street, Ramsbottom,  
Bury, Lancs.

## SANKEN HYBRID HI-FI AUDIO AMPLIFIER Integrated Circuit



We have made a fortunate purchase of these 25 watt audio amplifier modules from which you can build your own quality equipment. Requires only the addition of 3 capacitors and a resistance (apart from power supply). Two modules provide 50 watts of power. Heat sink requirements are simple. Distortion at 1kHz (10 watts) is only 0.2%.

Price: 25 watt amplifier type 1025A £7.95 (19p 15p) including technical data. Leaflet available. (50w version can be supplied).

A complete kit is available to make a 25 watt 4-25 watt stereo outfit (giving 100 watts of music power) and this incorporates an integrated circuit pre amplifier of very low distortion, plus P.S.U. Price is only £37.50 and a case to suit can be supplied. Demonstrated at our showrooms.

## Teleradio Hi-Fi

325, FORE STREET, EDMONTON, LONDON N.9.  
01-807-3719

# TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 Transistors for only £1-90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

J. M. KING (H)

17 Buckridge, Portpool Lane, London, E.C.1

**BUILD IT** in a DEWBOX quality cabinet. 2in x 2½ in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**GOLDEN HUNTER**  
from £10 50

Powerful metal detector  
locates buried coins, metal etc.

Send for literature, literature  
UNDERGROUND EXPLORATION LTD  
DEPT 9 FARADAY HOUSE  
P.O. BOX 1, HAILSHAM, SUSSEX

**FASCIA PANELS** to individual specification in etched aluminium. Hardware supplies for constructors. Printed circuit boards one-off's. Send 5p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

## PHOTOGRAPHIC ENLARGER TIMER

P.W. SEPTEMBER ISSUE

Having difficulties getting hold of that 6.8µF polycarbonate for C17? We can supply a high-stability precision polycarbonate in a ± 5% tolerance by return of post. Price 95p each plus 5p post and packing. For other components, see our main advertisement in this issue.

V. ATTWOOD,

P.O. BOX 5, ALRESFORD, HANTS.

## PRINTED CIRCUIT BOARD

In 6 standard widths: 2in, 2½in, 3in, 3½in, 4in and 5in x any length. 1/16in Fibreglass, single sided, 2p per 3 sq. inches. Doublesided, 1p per sq. inch. P. & P. 5p per order. S.A.E. Quotations for other sizes and quantity discounts.

J. KNOPP, 11 Connaught Gardens, Braintree, Essex, CM7 6LY. Tel. Braintree 52524.

## Fully guaranteed Individually packed VALVES

B12H	£1.75	6CH84	45p	N78	£1.75
CY31	35p	6CH200	65p	0A2	35p
DAF96	45p	6CL80	45p	0B2	35p
DF96	45p	6CL82	37p	6ALC80	37p
DK96	45p	6CL83	70p	6C97	45p
DS92	35p	6CL86	40p	6C90	45p
DL94	45p	6F36	45p	6CC87	40p
DM96	45p	6F37A	£1.25	6CC89	50p
L700	30p	6F40	£0.50	6CC189	55p
DY86	33p	6F41	65p	6CC800	75p
DY87	32p	6F80	25p	6CF801	50p
DY82	48p	6F83	55p	6CF82	33p
E88CC/01		6F85	35p	6CF84	60p
		6F86	30p	6CF86	60p
E180CC	42p	6F89	25p	6CF200	75p
E181CC	90p	6F91	30p	6CF201	75p
E182CC		6F92	35p	6CF801	50p
E183CC	£1.20	6F95	35p	6CF802	50p
E184CC	55p	6F143	30p	6CF805	80p
E185CC	55p	6F144	35p	6CF806	70p
E186CC	55p	6F145	35p	6CF807	70p
E187CC	55p	6F146	35p	6CF808	70p
E330CC	55p	6F289	35p	6CF951	70p
E3					



### STEREO AMPLIFIER 2 x 3W.

Printed circuit. Valves EZ80 & 2 ECL82. Liquidated stock of well-known manufacturer. Front panel 12" x 2". Chassis 9" x 3". Controls on-off, balance, ganged v.s., ganged tones; for 200-250v. a.c. Output transformers for 3-ohm speakers. With knobs. Only £6 (p. & p. 50p). For 110v. a.c. £5 (p. & p. 50p).

½ lb (min. 100) high stab resistors ¼W to 1W up to 2-5M 50p (10p post); ½ lb mixed tag strips 2 to 12 way approx. 75 for £1 (10p post); spring back telephone cable, 10" coil ext. to 6 ft, 4-core 15p (10p post) or 7 for £1 post pd.; **AUDIO CONNECTORS, PLUGS** 2-pin speaker 10p; 3-pin DIN 14p; 5-pin 17p; phono 5p; ¼" jack 12½p; 2.5mm & 3.5mm 6p; **METAL phono 12p; ¼" 12½p; 2.5mm 10p; 3.5mm 12p; SOCKETS** 2-pin speaker 10p; 3 & 5 pin DIN 9p; phono single 5p; double 7½p; treble 10p; 5-way 12½p; 5-way 15p; ¼" jack open 15p; moulded 20p; stereo open 20p; moulded 25p; **LINE SOCKETS** speaker, 3-pin & 5-pin DIN 17½p; phono metal 12p; co-ax. T.V. plug 8p; car radio plug 6p; either socket 8p. Post 10p. any order.

**MAINS TRANSFORMERS** (240-250v. input); postage in brackets. A. 100v. at 100ma 35p (20p); B. charger 12v. 1½A. 60p (20p); C. 200v. at 50ma & 6.3v. at 1A. 35p (20p); D. 22v. at 1A. 6.3v. at 2A. & 250v. at 50ma. 75p (25p); E. 250v. at 50ma & 6.3v. at 1½A. 50p (20p); F. 19V ¼A. 30p (15p); G. 19V 2A. 75p. (20p) Deduct 10% from total bill for more than 1 trans.




Miniature A.M. transistor tuning gang, 250 + 250p; 2 x 6 b.a. fixings. Size 1½ x 1½ x 1in.; gearing 3 : 1 to 4in. dia. moulded bush. Plastic dust cover. Plessey. 25p (post 5p).

## GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, Hants (Closed Wednesday)
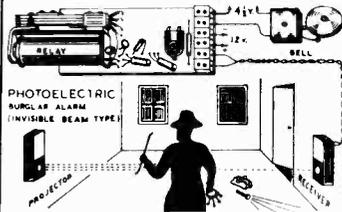
## PHOTOELECTRIC KIT

CONTENTS: 2 P.C. Chassis Boards, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, 3 Diodes, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation.



### PHOTOELECTRIC KIT £2.60

Postage and Pack. 15p (UK)  
Commonwealth:  
SURFACE MAIL 25p  
AIR MAIL £1.40  
Australia, New Zealand,  
S. Africa, Canada and U.S.A.  
Also Essential Data Circuits  
and Plans for Building  
10 Advanced Designs

#### INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photo-cell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.  
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks, Infra-red filter, projector lamp holder, building plans, etc. Price £1.25 Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

#### LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £1.85. Postage and Pack 15p (U.K.). Commonwealth: Surface Mail 20p, Air Mail £1.15.

#### JUNIOR PHOTOELECTRIC KIT

Versatile Invisible-beam, Relay-less, Steady-light Photo-Switch, Burglar Alarm, Door Opener, Counter, etc., for the Experimenter.  
CONTENTS: Infra-Red Sensitive Photo-transistor, 3 Transistors, Chassis, Plastic Case, Resistors, Screws, etc. Full Size Plans, Instructions, Data Sheet "10 Advanced Photoelectric Designs". Price £1.25. Postage and Pack. 10p (U.K.). Commonwealth 20p; Airmail 50p.

#### JUNIOR OPTICAL KIT

CONTENTS: 2 Lenses, Infra-red Filter, Lampholder, Bracket, Plans, etc. Everything (except plywood) to build 1 miniature invisible beam projector and photo-cell receiver for use with Junior Photoelectric Kit. Price 75p. Post. and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p; Air Mail 50p.

## YORK ELECTRICS Mail Order Dept.

335 BATTERSEA PARK RD., LONDON S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects

## INDEX TO ADVERTISERS

A. H. Supplies	648
Adcola Products Ltd.	586
Antex	563
Apex Aerials	658
Attwood, V.	660, 662
Audio Supplies	619
Autotron	632
Baines, R.	658
Baker Reproducers	650
Bell's Television	658
Bentley Acoustic Corporation Ltd.	652
Bernard, Gerald	576
B.I.E.T.	cov. iii, 650
Bi-Pak Semiconductors	583, 584, 585
Bi-PrePak Ltd.	603
Boffin Projects	661
British National Radio & Electronics School	615, 650
Broadway Electronics	578
Bull, J. (Electrical) Ltd.	600
Bush & Meissner	564
C.B.M. Electronics	570
C.T. Electronics Ltd.	662
Carrana, C.	658
Codar Radio Co.	582
Colomar Electronics Ltd.	662
Comet High Fidelity Discount Warehouses	574, 575
Concord Electronics Ltd.	653
D.E.W. Ltd.	661
Dabar Electronics	652
Dexter & Co.	636
Discosound	581
Douglas Electronic Industries Ltd.	636
Duke & Co.	648
Eagle International	595
Elekon Enterprises	570
Electrovalve	628
Electrospares	648
Elvins Electronics	564
Express Mail Order	644
Felstead Electronics	656
Field Electrics Ltd.	640
Galleon Trading	660

Gladstone Radio	663
Global Audio Discount Warehouse	572
Government Communication Headquarters	659
Greenwell Electronics	661
HAC Shortwave Products	580
Hadley, C.	650
Harverson Surplus Co. Ltd.	651
Hawnt & Co. Ltd.	604
Heath (Gloucester) Ltd.	599
Helme, P. F. & A. R. Ltd.	658
Henry's Radio Ltd.	cov. iv, 657
Home Radio (Components) Ltd.	577
I.C.S.	643
I.L.P. Electronics Ltd.	571
Imperial Trading	658
Ivoryet Ltd.	566
Jef Electronics	660
Johns Radio	632
Johnsons (Radio) Ltd.	660, 661
K.V.A.	580
Kensington Supplies	659
Keytronics	640
King, J. M.	662
Knopp, J. F. D.	662
K.W. Electronics Ltd.	596
Lasky's Radio Ltd.	565
Lewis Radio	578
Light Soldering Developments Ltd.	576
Lindair (Electrotech) Ltd.	636
Linear Products Ltd.	570
London Computer Operators Training Centre	659
Magtor Ltd.	604
Marktyme	572
Marshall, A. Son	649
Merlin Supply Ltd.	566
Miniwisa Products	596
Mole, M. & Son	562
Morse	659
Multicore Solders Ltd.	566
NIP Electronics	660
National Amateur Radio & Electronics Exhibition	596
Padgetts Radio Store	570
Partridge Electronics	636
Partridge Electronics Ltd.	644

Pembroke College	572
Potter & Clarke Ltd.	562
Powertran Electronics	632
Radio Component Specialists	639
Radio Exchange Ltd.	635
Radio & T.V. Comps. (Acton) Ltd.	568, 569
Radio Society of Great Britain	620
Radionic Products Ltd.	580
Readers Radio	632
Riversdale Electronics Ltd.	620
ROC Electronics Ltd.	627
Robin Hood (Notm.) Ltd.	658
R.C.S. Products	580
RSC Hi-Fi Centres Ltd.	cov. ii, 561
RSL Components	660
R.S.T.	620
S.C.S. Components Ltd.	566
Saxon Entertainments	573
Scientific & Technical Services	576
Selray Book Co. Ltd.	659
Sinclair Radionics Ltd.	654, 655
Shoperunities Ltd.	567
Smith, G. W. & Co. (Radio) Ltd.	645, 646, 647
Smith, H. L. Ltd.	641
Sound Supplies Ltd.	659
Speaker Selection	652
Subec Audio	644
Surpltronics	578
Swanley Electronics	604
Teleradio Co. Ltd.	660, 661
Thacker, A. H.	640
Thornbury Trade Disposals	640
Tidman Mail Order	661
Trade Aids	604
Trampus Electronix	660
Tuac Ltd.	631
Underground Exploration	662
Velco Electronics Ltd.	661
W.E.C. Ltd.	661
Web Europa	576
West London Direct Supplies	564
Weyrad (Electronics) Ltd.	656
Wilmslow Audio	564, 656
Wilsic Electronics Ltd.	644
York Electronics	663
Xeroza Radio	661
Yukan Self Spray	659
Z & I Aero Services	664

Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 12 $\frac{1}{2}$  p in £ for postage and handling  
MINIMUM CHARGE 15np. No C.O.D. orders accepted  
Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

First Quality Fully Guaranteed



ELECTRONIC VALVES

OA2 0.40	6AR6 0.55	6P1 0.75	7Y4 0.75	6E95 0.40	GZ32 0.50	PL33 0.40	U403 0.70
OA3 0.48	6AR6 0.75	6P5 0.75	8H8 0.75	EP97 0.65	GZ33 0.75	PL36 0.55	U404 0.70
OB2 0.40	6AR1 1.25	6P6G 0.45	10C2 0.60	EP98 0.75	GZ34 0.60	PL81 0.50	U801 0.80
OB3 0.70	6AR5 0.50	6P11 0.50	10D1 0.85	EP183 0.30	HA8C800.65	PL82 0.45	UABC80
OC3 0.40	6AB7G 0.85	6P13 0.50	10D2 0.55	EP184 0.35	HK90 0.50	PL83 0.45	
OD3 0.40	6AT6 0.38	6P14 0.70	10F1 0.75	EK90 0.82	KT86 2.25	PL84 0.40	UAF41 0.70
1B3GT 0.45	6AU6 0.30	6P15 0.65	10F9 0.65	EL34 0.50	N78 1.80	PL502 0.75	UB41 0.65
1L4 0.25	6AV6 0.40	6P18 0.50	10P18 0.60	EL36 0.50	PABC800.40	PL508 0.90	UBC41 0.55
1R4 0.50	6AW8A 0.65	6P23 0.60	10L1 0.60	EL37 1.70	PC86 0.60	PL509 1.10	UCB31 0.45
1R5 0.45	6BA6 0.28	6P24 0.80	10LD11 0.70	EL41 0.75	PC88 0.60	PL801 1.00	UBF80 0.40
184 0.30	6BE6 0.32	6P25 1.00	10P13 0.75	EL42 1.55	PC92 0.65	PL802 0.95	UBF80 0.40
185 0.80	6BH6 0.55	6P26 0.35	12AB5 0.70	EL84 0.25	PC900 0.48	PM84 0.60	UBL1 0.70
1T4 0.30	6BH6 0.75	6P28 0.70	12AC6 0.60	EL85 0.43	PC84 0.40	PY31 0.85	UBL21 0.70
1U4 0.40	6B6 0.55	6QK6 0.60	12AD5 0.60	EL86 0.40	PC85 0.40	PY33 0.82	UC29 0.45
1U5 0.75	6BK7A 0.75	6J4 0.80	12A8 0.60	EL90 0.42	PC88 0.55	PY80 0.40	UC28 0.45
1V2 0.85	6BK7A 0.45	6J5GT 0.40	12AL5 0.55	EL95 0.35	PC89 0.55	PY81 0.30	UCF80 0.70
1X2B 0.55	6BN6 0.60	6J6 0.30	12AQ5 0.50	EL82 1.40	PC8189 0.60	PY82 0.35	UCH21 0.40
2A3 0.50	6BQ6 0.25	6J7 0.45	12AT8 0.40	EL83 0.50	PC97 0.50	PY83 0.38	UCM2 0.70
2C4 0.75	6BR7 0.75	6K6GT 0.75	12AT7 0.40	EL84 0.25	PC900 0.48	PY84 0.40	UCM2 0.70
2D21 0.40	6B87 1.35	6K7 0.43	12AU6 0.45	EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
3A4 0.45	6BW6 0.90	6K8G 0.45	12A8 0.60	EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
3AD 0.75	6B87 0.25	6K25 0.75	12AV6 0.45	EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
3BP1 2.75	6BX6 0.25	6L6GT 0.55	12AV7 0.70	EL95 0.35	PC89 0.55	PY82 0.35	UCM2 0.70
3B4 0.40	6BZ6 0.45	6L7 0.45	12AX7 0.33	EL82 1.40	PC8189 0.60	PY83 0.38	UCM2 0.70
3H4GY 0.75	6C4 0.35	6L8 0.50	12AY7 0.75	EL83 0.50	PC97 0.50	PY84 0.40	UCM2 0.70
5U4G 0.40	6CGGT 0.55	6LD20 0.50	12B4A 0.45	EL84 0.25	PC900 0.48	PY31 0.85	UBL21 0.70
5V4G 0.50	6CB8 0.45	6N7GT 0.55	12B4B 0.45	EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
5Y3GT 0.45	6CD6G 0.45	6P3 0.40	12B7 0.40	EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
5Z 0.75	6C7 1.30	6Q7 0.50	12BE6 0.50	EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
5Z4G 0.45	6CG7 0.60	6R7 0.45	12BH7 0.50	EL95 0.35	PC89 0.55	PY82 0.35	UCM2 0.70
6B30L2 0.90	6CH6 0.60	6R8G 0.45	12BY7 0.45	EL82 1.40	PC8189 0.60	PY83 0.38	UCM2 0.70
6BA 0.45	6CL6 0.60	6R8K7 0.50	12K5 1.00	EL84 0.25	PC900 0.48	PY31 0.85	UBL21 0.70
6AF4A 0.90	6CU6 0.80	6RL7GT 0.45	12K7GT 0.50	EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
6AG6 0.25	6CW4 0.70	6R9GT 0.45	12Q7GT 0.45	EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
6AG7 0.45	6CY 0.40	6R9 0.40	12R7 0.50	EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
6AH6 0.90	6CY7 0.75	6R87 0.50	20D1 0.60	EL95 0.35	PC89 0.55	PY82 0.35	UCM2 0.70
6AJ8 0.30	6D3 0.55	6T8 0.38	20L1 1.10	EL82 1.40	PC8189 0.60	PY83 0.38	UCM2 0.70
6AK3 0.40	6DC6 0.80	6U4GT 0.70	20P1 0.50	EL83 0.50	PC97 0.50	PY84 0.40	UCM2 0.70
6AK6 0.60	6DK6 0.80	6U5G 0.75	20P4 1.10	EL84 0.25	PC900 0.48	PY31 0.85	UBL21 0.70
6AL3 0.43	6DQB 0.75	6U6 0.45	20R5 0.60	EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
6AL5 0.25	6E8 1.25	6V6GT 0.45	25C5 0.50	EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
6AM5 0.40	6E8A 0.65	6X 0.40	25L6GT 0.60	EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
6AM6 0.37	6EH7 0.30	6X5GT 0.45	25T4G 0.35	EL95 0.35	PC89 0.55	PY82 0.35	UCM2 0.70
6AQ5 0.42	6EJ7 0.35	6X8 0.35	25Z6GT 0.75	EL82 1.40	PC8189 0.60	PY83 0.38	UCM2 0.70
6AQ6 0.70	6EW6 0.70	6Y6G 0.80	30A5 0.60	EL83 0.50	PC97 0.50	PY84 0.40	UCM2 0.70
				EL84 0.25	PC900 0.48	PY31 0.85	UBL21 0.70
				EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
				EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
				EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
				EL95 0.35	PC89 0.55	PY82 0.35	UCM2 0.70
				EL82 1.40	PC8189 0.60	PY83 0.38	UCM2 0.70
				EL83 0.50	PC97 0.50	PY84 0.40	UCM2 0.70
				EL84 0.25	PC900 0.48	PY31 0.85	UBL21 0.70
				EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
				EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
				EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
				EL95 0.35	PC89 0.55	PY82 0.35	UCM2 0.70
				EL82 1.40	PC8189 0.60	PY83 0.38	UCM2 0.70
				EL83 0.50	PC97 0.50	PY84 0.40	UCM2 0.70
				EL84 0.25	PC900 0.48	PY31 0.85	UBL21 0.70
				EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
				EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
				EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
				EL95 0.35	PC89 0.55	PY82 0.35	UCM2 0.70
				EL82 1.40	PC8189 0.60	PY83 0.38	UCM2 0.70
				EL83 0.50	PC97 0.50	PY84 0.40	UCM2 0.70
				EL84 0.25	PC900 0.48	PY31 0.85	UBL21 0.70
				EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
				EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
				EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
				EL95 0.35	PC89 0.55	PY82 0.35	UCM2 0.70
				EL82 1.40	PC8189 0.60	PY83 0.38	UCM2 0.70
				EL83 0.50	PC97 0.50	PY84 0.40	UCM2 0.70
				EL84 0.25	PC900 0.48	PY31 0.85	UBL21 0.70
				EL85 0.43	PC84 0.40	PY80 0.40	UC28 0.45
				EL86 0.40	PC85 0.40	PY80 0.40	UC28 0.45
				EL90 0.42	PC88 0.55	PY81 0.30	UCF80 0.70
				EL95			

# FREE!

## Over 150 ways to engineer a better future

**HIGHER PAY**      **A BETTER JOB**  
**SECURITY**

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.


Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.  
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.  
 "My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.
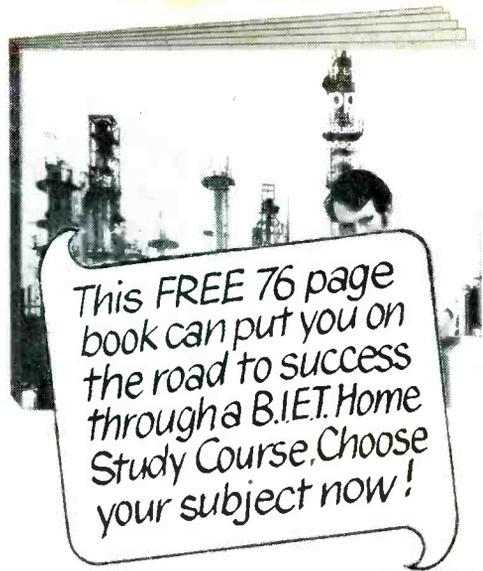
#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. B37, Aldermaston Court, Reading RG7 4PF



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

- |   |   |
|---|---|
| <p><b>MECHANICAL</b><br/>                 A.M.S.E. (Mech.)<br/>                 Boiler Inspection &amp; Operation<br/>                 C &amp; G Eng. Crafts<br/>                 C &amp; G Fabrication<br/>                 Diesel Eng.<br/>                 Eng. Inspection<br/>                 Eng. Metallurgy<br/>                 Inst. Eng. &amp; Tech.<br/>                 Inst. Motor Ind.<br/>                 Maintenance Eng.<br/>                 Mechanical Eng.<br/>                 Sheet Metal Work<br/>                 Welding</p> <p><b>ELECTRICAL &amp; ELECTRONIC</b><br/>                 A.M.S.E. (Elec.)<br/>                 C &amp; G Elec. Eng.<br/>                 C &amp; G Elec. Inst.<br/>                 C &amp; G Elec. Tech.<br/>                 Computer Elect.<br/>                 Elec. Maths<br/>                 Elec. Science<br/>                 Electronic Eng.<br/>                 Electrical Eng.<br/>                 Install. &amp; Wiring<br/>                 Meters<br/>                 &amp; Measuring Instruments</p> <p><b>MANAGEMENT &amp; PRODUCTION</b><br/>                 Automatic Control<br/>                 Computer Prog.<br/>                 Electronic Data Processing<br/>                 Estimating<br/>                 Foremanship<br/>                 Inst. Cost &amp; Works<br/>                 Accounts<br/>                 Inst. Marketing<br/>                 Management<br/>                 Metrication<br/>                 Motor Trade Man.<br/>                 Network Planning<br/>                 Numerical Control<br/>                 Operational Research<br/>                 Personnel Man.<br/>                 Planning Eng.<br/>                 Production Eng.<br/>                 Quality Control</p> <p><b>Man. Prod.—cont.</b><br/>                 Salesmanship<br/>                 Storekeeping<br/>                 Work Study<br/>                 Works Management</p> <p><b>DRAUGHTSMANSHIP</b><br/>                 A.M.I.E.D.<br/>                 Design of Elec. Machines<br/>                 Die &amp; Press Tool Design<br/>                 Electrical Draughtsmanship<br/>                 Gen. Draughtsmanship<br/>                 Jig &amp; Tool Design<br/>                 Technical Drawing</p> <p><b>RADIO &amp; TELECOMMUNICATIONS</b><br/>                 Colour TV<br/>                 C &amp; G Radio/TV Electronics<br/>                 C &amp; G Telecomm. Tech.<br/>                 Prac. Radio &amp; Elec. (with kit)<br/>                 Radio Amateurs Exam.<br/>                 Radio Servicing &amp; Repairs<br/>                 Radio &amp; TV Eng.<br/>                 Transistor Course<br/>                 TV Main. &amp; Serv.</p> <p><b>AUTO &amp; AERO</b><br/>                 Aero Eng.<br/>                 A.M.I.M.I.<br/>                 A.R.B. Cert.<br/>                 Auto Engineering<br/>                 Inst. Repair<br/>                 C &amp; G Auto. Eng. Garage<br/>                 Management<br/>                 MAA/IMI Diploma<br/>                 Motor Vehicle Mechanics</p> <p><b>CONSTRUCTIONAL</b><br/>                 A.M.S.E. (Civil)<br/>                 Architecture<br/>                 Building</p> <p><i>Coaching for many major exams, including I.N.C., O.N.C., C &amp; G, etc.</i></p> | <p><b>Constructional-cont.</b><br/>                 Building Drawing<br/>                 Surveying<br/>                 Foreman<br/>                 Carpentry &amp; Join.<br/>                 Civil &amp; Municipal Engineering<br/>                 Constructional Engineering<br/>                 Construction Surveyors<br/>                 Institute<br/>                 Clerk of Works<br/>                 Council Eng.<br/>                 Geology<br/>                 Health Eng.<br/>                 Heat &amp; Vent.<br/>                 Hydraulics<br/>                 Inst. Builders<br/>                 Inst. Clerk of Works<br/>                 Inst. Works &amp; Highway Supers.<br/>                 Painting &amp; Dec.<br/>                 Public Hygiene<br/>                 Road Engineering<br/>                 Structural Eng.<br/>                 Surveying</p> <p><b>GENERAL</b><br/>                 Agricultural Eng.<br/>                 Council of Eng. Inst.<br/>                 Farm Science<br/>                 General Education<br/>                 Gen. Plastics<br/>                 Pract. Maths<br/>                 Pract. Slide Rule<br/>                 Pure &amp; Applied Maths<br/>                 Refrigeration<br/>                 Rubber Technology<br/>                 Sales Engineers<br/>                 Tech. Report Writing<br/>                 Timber Trade<br/>                 University Ent.</p> <p><b>G.C.E.</b><br/>                 58 'O' &amp; 'A' LEVELS SUBJECTS<br/>                 Over 10,000 group passes</p> |
|---|---|

## POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. B37, Aldermaston Court, Reading RG7 4PF B37

NAME \_\_\_\_\_  
 Block Capitals Please  
 ADDRESS \_\_\_\_\_

SUBJECT OF INTEREST \_\_\_\_\_ AGE \_\_\_\_\_

Accredited by the Council for the Accreditation of Correspondence Colleges.

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2.65.  
 PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

# U.K.'s LARGEST ELECTRONICS CENTRES! HENRY'S RADIO LTD. EDWARE ROAD, LONDON, W.2.

**NOW OPEN!**

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381/8382  
354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736  
309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963  
303 BARGAIN STORE SPECIAL OFFERS 01-723 1008 All Mail to: 303, Edgware Rd., London, W.2.

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.



## BUILD THE TEXAN

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

★ FREE TEAK CABINET with complete kits!

**FEATURES.** New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

**HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES** —DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

**FACILITIES.** On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).



As featured in "Practical Wireless" May to August 1972)

SPECIAL KIT PRICE

£28-50 P & P 45p

COMPLETE WITH FREE TEAK CABINET  
Designer approved kits only available from Henry's

★ SLIM DESIGN WITH SILVER TRIM  
Overall chassis size 14 1/2" x 6" x 2" high

### RECORD DECKS

CHASSIS (Post 50p)  
SP25/3 £11-25 HT70 £15-95  
MP60 £11-25 MP610 £14-75  
AP76 £19-50 GL72 £22-40  
WITH PLINTH/COVER (Post 70p)  
MP60 £17-20 TD150AB £43-35  
HT70 £21-90 PL12AC £43-35  
HL(GL75) £35-60 £35-50  
MP610 £20-35 BD2 £33-25  
CART/PLINTH/COVER (Post 70p)  
(HL) AP76/G800 £29-95  
(HL) SP25-3/G800H £19-95  
HT70/G800/PC £27-00  
(HL) 2025TC/9TAHCD/PC £14-95  
MP60/SC5MD/PC £17-25  
(HL) GL75/G800E/PC £44-50

### ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.  
£5-90 per pair. Post 10p

### MARRIOTT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO  
17' High Impedance £2-00  
18' Med. Impedance £2-00  
36' Med.-Low Imp. £3-50  
Erase Heads for above 75p  
63' 2 track mono- £1-75  
Hi Imp.  
43' Erase Head for above 75p

### POWER INTEGRATED CIRCUITS

Plessey SL403D—3 watt with 8-page data, layouts and circuits £1-50. P.C. Board 60p. Heat Sink 14p. Sinclair IC12—6 watt with data and circuits £1-80. TH9013P—20 watt Power Amp Module £4-57. TH9014P-IC Preamp £1-50. Data/Circuits for above No. 42 10p

### 7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)  
XN3, XN13, GN6 0-9 side view with data, 85p.  
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.  
3015F 7 seg £2 each. £7 per 4 with data.  
12 and 24 hour clock circuits for above Ref. No. 31 15p.

### Miniature Amplifier

5 transistor. 300mVv o/p. Fitted volume and sensitivity control, 9 volt operated. £1-75 each P/P 15p.

### Quality Slider Controls

60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 50K, 100K, 1 meg, Log and Lin. 45p each, 10K, 25K, 50K, 100K, Log and Lin ganged. 75p each.

### Hi-Fi & Tape Equipment

Acknowledged as U.K.'s Largest Stockists with Lowest Prices Plus 12 months Guarantee. Write or call for FREE 16 page lists (Ref. 16/17)

Transistors - IC's - SCR's - Rectifiers - Triacs, etc. NEW FREE LISTS Ref. No. 36 on request.

### LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2" x 8 1/2". Large Ceramic Magnet.  
TYPE 150 6 watt, 3, 8 or 15 ohms £2-20. Post 22p.  
TYPE 150 TC Twin cone version £2-75. Post 22p.  
TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3-85. Post 25p.  
TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7-70. Post 28p.



POLISHED CABINETS 150, 150TC 450 £4-60. Post 30p.

### ML3 MW/LW TUNER to BUILD



Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4-85. Post 15p. All parts sold separately. Leaflet No. 6

### "BANDSPREAD" PORTABLE TO BUILD




Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. Also slow motion geared tuning, 600 mV push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7-98. p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2

## CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post Paid (PRICE FOR CALLERS)  
PLUS! FIVE 10p VOUCHERS

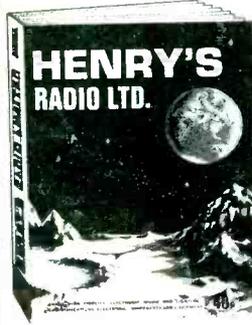Send to this address—HENRY'S RADIO LTD. (Depr. EE) 3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail and callers to "303" see below.



### TEST EQUIPMENT

SE250B Pocket Pencil Signal Injector £1-90  
SE3500 Pocket Pencil Signal Tracer £1-50  
TE15 Grid Dip Meter 440 KHz-280 mHz £13-45  
500 30 K/V Multimeter £9-25  
With leather case £10-50  
200H 20K/V Multimeter £4-20. With case £4-95  
AF105 50K/V Multimeter £8-50. With case £9-50  
U4341 AC/DC Multimeter with transistor tester with steel case £10-50  
TE20D RF Generator 120KHz-500MHz £15-95. Carr. 35p  
TE22D Audio Generator 20Hz-200KHz £17-50. Carr. 35p  
TO3 3" Scope 1 1/2Hz-15MHz £39-00. Carr. 50p  
CL5 3" Pulse Scope 10Hz-10MHz £39-00. Carr. 50p  
TE65 Valve Voltmeter 28 ranges £17-50. Carr. 40p



### PA-Disco-Lighting

UK's Largest Range—Write phone or call in. Details and demonstrations on request.



DJ30L 3 Channel sound to light unit, 3kw £28-50  
DJ40L 3 Channel Mic (Built in) to light, 3kw £37-50  
DJ70S 70 watt Disco amp/mixer £49-75  
DISCOAMP 100 watt Disco amp/mixer £67-50  
DJ105S 30 watt Disco amp/mixer £31-00  
Anti-Feedback Quality Mic. £11-50  
SDL 12" 50 watt 8 ohm Full range speaker £12-95  
DECKS. Use MP60 or SP25/3 see above  
Matching cartridge SC5M £2-62.  
FIBRE OPTICS, LIGHTING EFFECTS, PROJECTORS, SPOTS, DIMMERS, MIXERS. Everything for PA—Disco—Lighting. FREE Stock List Ref. No. 18.

### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH, PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO.  
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.  
TOTAL £6-97, p.p. 20p. Decoder Kit £5-97.  
Tuning meter unit £1-75  
Mains unit (optional) Model PS900 £2-47. Post 20p  
Mains unit for Tuner and Decoder PS1200 £2-62. Post 20p



### SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!

Z30 £3-57; Z50 £4-37  
STEREO 60 PZ5 £3-97  
£7-97; PZ8 £4-77  
PZ6 £6-37;



Transformer for PZ8 £2-95  
Active Filter Unit £4-45  
Stereo FM Tuner £16-95  
IC12 £1-80; Q16's £15 pr.  
Post etc. 20p per item

### PACKAGE DEALS

Post 25p  
2xZ30, Stereo 60, PZ5 £15-95  
2xZ30, Stereo 60, PZ6 £18-00  
2xZ50, Stereo 60, PZ8 £20-25  
Transformer for PZ8 £2-95  
PROJECT 60S KIT £19-95

MORE OF EVERYTHING AT LOW PRICES ALWAYS AT HENRY'S  
All the parts you need plus Data and Circuits — Get a Catalogue — it's all in there!

Prices subject to change without notice E. & O.E.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

**H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H**