

PRACTICAL WIRELESS

APRIL
1973

20p



TRICOLOUR

Mood Lighting

*Loop aerial
1112*



System

also

**I. C. POWER AMPLIFIER
DARKROOM EXPOSURE METER**

PACKAGE PRICE R.S.C. STEREO PACKAGE OFFERS

FOR ILLUSTRATED UNITS
ONLY
£39-59

Carr. £1-00
Or deposit £4-95
and 9 monthly
payments £4-22
(Total £44-93).



Individual Rec. Retail Prices:
LINEAR 505 5 + 5 Watt Amplifier £17-60
GARRARD 2025 Autochanger + KB40A Cartridge £13-58
Teak Veneer Plinth with Transparent Plastic Cover £6-10
Pair A55 LOUDSPEAKERS (Inc 8" x 5" 10,000 Gauss) £11-50
TOTAL £48-68

SEND S.A.E. FOR
FREE COLOUR
BROCHURE

SAVE £31-60



HIGH FIDELITY UNITS
PACKAGE PRICE **£99-95** Carr. £1-70

FOR ILLUSTRATED UNITS

Or deposit £15-00 and
12 monthly payments £8-00
(Total £111-00)
Individual Rec. Retail Prices:
GOLDRING GL72
Transcription
Turntable + P.U. £31-89
GOLDRING Q800
Magnetic Cartridge £19-91
DE-LUXE PLINTH
with Roll-over Cover £10-50
Pair R.S.C. MONARCH
LOUDSPEAKERS £38-70
R.S.C. SUPER 30
Mk III AMPLIFIER £38-75
TOTAL £131-55

FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround conc. Printed circuit cross-over assembly with ferrite cored coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc. and instructive diagrams, Frequency **£9-95** post free
Impedance 8 15 ohms
Or Dep. £2-25 & 9 monthly payments £1 (Tot. £11-25)

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating 1.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedance of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE SET OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS **£11-50** Carr. 40p
OR FACTORY BUILT IN TEAK VENEERED CABINET £14-99 or dep. £2-20 and 9 monthly payments £1-70 (Total £17-60)



HIGH FIDELITY LOUDSPEAKER UNITS

Cabinet latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available.
DORCHESTER (Illustrated) Size 16x11x9in. appr. Range 46-16,000 c.p.s. Rating 8-10 watts. Fitted High flux 13x8in. **£9-45** Carr. 40p.
MONARCH Size 19x10x9in. appr. Rating 10 watts. Inc. 13x8in. speaker with highly flexible P.V.C. cone surround, long throw voice coil and 10,000 line magnet. High flux pressure tweeter. Handsome design cabinet. Range 35-20,000 c.p.s. Imp. 8 ohms. Gives smooth realistic sound output. **£19-35**
See 'package offers' for illustration. Carr. 50p

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc.
JES8 Size 16 x 11 x 9in. SE8 For optimum performance with any 8in. Hi-Fi spkr. Size 22 x 15 x 9in. **£6-47**
Pressurised. Gives pleasing results with any 8in. Hi-Fi spkr. Size 22 x 15 x 9in. **£6-47**
SE10 For outstanding results with 10in. Hi-Fi spkr. Size 24 x 15 x 10in. P'td. **£6-74**
SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter Size 25 x 16 x 10 1/2in. **£7-87**

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£5-95** Carr. 30p
OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER **£6-95** Carr. 35p



AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 16,000 c.p.s. Impedance 3 or 8-16 ohms. PLEASE STATE CHOICE.
Exceptional performance at low cost.
HF802T 8" 10W £2-88 HF120D 12" 15W £4-99
HF102D 10" 10W £3-40 HF128 12" 15W £5-75
HF120 12" 15W £4-50 HF126D 12" 15W £6-85

FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-16 Ω. **£3-85**
PLEASE STATE IMPEDANCE WHEN ORDERING
MODEL 803T 8" 15W with parasitic Tweeter. **£4-95**
Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-16.

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1-5v and 90v, to battery radio where A.C. mains 200/250v. 50c/s is available. COMPLETE KIT **£3-25** ASSEMBLED READY FOR USE **£3-75** WITH DIAGRAM

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary. Primaries 200-250v. 50c/s. Screened
MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 x 2in.
250v., 60mA, 6-3v. 2a 99p
250-0-250v., 60mA 6-3v. 2a £1-05
FULLY SHROUDED UPRIGHT MOUNTING
250-0-250v. 60mA, 6-3v. 2a., 0-5-6-3v. 2a. £1-40
250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 2a. £2-20
300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 2a. £2-20
300-0-300v. 130mA, 6-3v. 4a. c.t., 6-3v. 1a. £2-25
For Mullard 610 Amplifier. £2-85
350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 2a. £2-20
350-0-350v. 150mA, 6-3v. 4a., c.t., 5v. 2a. £2-85
425-0-425v. 200mA, 6-3v. 4a., c.t., 5v. 2a. £4-95
425-0-425v. 200mA, 6-3v. 4a., 6-3v. 3a., 5v. 2a. £5-10
450-0-450v. 250mA, 6-3v. 4a., c.t., 5v. 2a. £5-50

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2db. Harmonic Distortion 0-3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV Output rating 1.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 5 1/2 in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2 in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7-75** Carr. 40p
OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE £10-95

NOW IN STOCK!

FANE 'CRESCENDO' SUPER EFFICIENT GROUP/DISCO LOUDSPEAKERS

Send S.A.E. for leaflet on this range of extraordinarily efficient units including the very latest BASS CRESCENDO '12' 100 Watts. FULL DISCOUNT to Genuine Trade Customers. CARR. FREE.

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET
Only high grade components by leading manufacturers
* Push Button Selector Switching
* Jack Socket for Headphones
* Neon Indicator
* Satin Silver Finish Metal Fascia
* Solid State Circuitry
* Twenty Silicon Transistors
* Four Diodes, Four Rectifiers
Send S.A.E. for full descriptive leaflet.
R.S.C. STEREO FM TUNER.
Completely matches Super 30 Mk. III **£44-95**



COMPLETE KIT (less cabinet). Carr. 65p. Cabinet if req. £5 extra. **£25**
FACTORY BUILT UNIT INC. CABINET WITH 12 months' guarantee. Or Dep. £7 and 9 monthly payments £3-99 (Total £42-91). **£38-75**

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx.
★ Response 30-20,000 c.p.s. Impedance 15 ohms
★ Performance comparable with units costing considerably more
£23 Carr. 65p
Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-60 and 9 monthly payments £2-47 (Total £26-83).



RSC GROUP/DISCO UNITS



HEADPHONES
MICROPHONE

TWIN TURNTABLE
WITH PRE-AMP

PACKAGE OFFER

- Units listed below
 (a) 100w POWER AMPLIFIER
 (b) PAIR OF HI-FI HEAD-
 PHONES
 (c) MATCHING DYNAMIC
 "MIKE" (attached
 to headphones)
 (d) PAIR 50 WATT SPEAKERS
 Black Rexine covered
 Cabinets £72-85
 Size approx.
 18" x 18" x 8"
 (a)(b)(c)(d)

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25
 Mk.III turntables and Sonolone or
 Acos Cartridges with diamond stylus.
 Separate Vol. controls for each
 turntable. Also MONITORING
 FACILITIES, plus Treble and Bass
 Controls. Separate input for 'mike'
 with vol. control switch. Black
 Rexine covered Cabinet with lid.
 see illus. left

Carr. £1-25
 Or Dep. £13-25 and 9
 monthly pymts £6-38
 (Total £75-17) or Dep. £15 and 18
 mthly payments £3-62 (Total £80-16)

Terms on Amps, Speakers and Head-
 phones/Mike. Deposit £15 and 18
 monthly payments of £4-00 (Total
 £87-00).

R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS
AND PUBLIC ADDRESS

All types 15 Ohm covered in Rexine and Vynair
 TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C312 30-40 WATTS Fitted two
 exceptionally efficient, low feedback howl char-
 acteristic high flux 1 3/8" x 8" 20 watt
 speakers. Terms: Dep. £3 and 9
 mthly payments £2-22 (Total £22-98) Carr. 50p.

TYPE C4100 100 WATTS Inc. four 12" 50 watt speakers for conserva-
 tive rating. Extra heavy construction. Size approx. 58 x 16 x 10". Acoustically
 filled and pressurised. Terms: Dep. £11 and 12 mthly. pmts. £5-18 (Total £78-16). Carr. £1

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE
 High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
£22-95	£12-90	£10-90
Dep. £8 and 9 mthly payments £2-20 (Total £25-80)	Dep. £3-30 and 9 monthly payments £1-30 (Total £15).	Dep. £2 and 9 monthly pay- ments £1-20 (Total £12-80) PAIR SUITABLE ALL PURCHASES

FOR BASS GUITAR, ELECT. ORGAN, ETC.

R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high
 output, Hum level—70dB. Response
 ±3dB 30-20,000 c/s. All high grade components. Valves EF86
 EF86, ECC83, EL34, EL34, GZ34. Separate Bass and Treble
 Controls. Sensitivity 36 millivolts. For High Impedance micro-
 phones. For Clubs, Schools, Theatres, Dance Halls, Outdoor Func-
 tions, etc. For Electronic Organ, Guitar, String Bass, etc. Gram.

Radio or Tape. Two separate inputs with vol. controls permit such as "mike" and
 Pick-up etc. for mixing purposes. 200-250v. 50 c/s A.C. mains. For 3 and 15 ohm
 speakers. Twin-handled perforated cover £1-90. 12 MONTHS' GUARANTEE. Carr. 65p

TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22-90). Send S.A.E. for leaflet.

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses
 other than Bass Guitar or
 Electronic Organ). Carr. free

£6-75 or Dep. £1-25 and 9
 mthly payments 75p
 (Total £8-00).

LINEAR T40/60D 50W GROUP/DISCO AMPLIFIER

* FULL MONITORING FACILITIES
 * Individual Bass and Treble controls
 * Twin Jack output sockets for speakers
 * Input sockets for medium or high impedance
 Microphones or Guitar P.U.s and Crystal or
 Ceramic Gram. P.U.s

* Frequency response 30-20,000 Hz.
 * Output overload protection plus double fusing
 FRONT PANEL (Jack inputs)
 Gram, Gram, Microphone/Guitar P.U.; plus monitoring
 socket.

CONTROLS Vol. (1) (2) (3) and (4). Bass, Treble,
 Master Vol., Monitor Selection Switch Gram (1) or (2),
 Mains Switch

£49-50 Carr. free
 Or Deposit £7-50
 and 9 monthly
 payments £5-87
 (Total £55-83)

Simulated black
 rexine, plastic bonded
 metal case.
 ALSO STOCKED
 LINEAR
 T80/100D £69-75

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 25/2 25W L/SPEAKERS Terms: Deposit £6.50 and 9 monthly payments of £4.92 (Total £50.78)	£34-95 £13-50 £49-45	PACKAGE PRICE £45 £1
F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 60 L/SPEAKERS Terms: Deposit £10 and 9 monthly payments of £5-37 (Total £58-38)	£34-95 £21-80 £56-75	PACKAGE PRICE £52 £1
F.A.L. PHASE 60 MK.III AMPLIFIER PAIR L12/25 25W L/S in cabinets Terms: Deposit £10 and 9 monthly payments of £6-58 (Total £66-92)	£34-95 £28-90 £63-85	PACKAGE PRICE £56 £1-25
F.A.L. PHASE 100 AMPLIFIER & FANE POP 60 L/SPEAKERS Terms: Deposit £15-95 and 9 monthly payments of £10-73 (Total £112-52)	£61-95 £43-60 £105-55	PACKAGE PRICE £99-95 £2

FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled inputs Plus master vol.
 control. Incl. Bass and Treble Controls. Protective circuit to
 guard against damage from accidental shorts. Output for
 Speakers 3 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C.
 mains. Output 50 watts music rating.
 Or deposit £7-25 & 9 monthly pay-
 ments £3-55. Total £39-20.

£34-95 Carr. 70p

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH
 L125 50 WATT Fitted pair of 12" 50
 watt high flux speakers for conservative
 rating. Impedance 8-15 ohms. Carr. £1-50
 Or deposit £5-50 and 9 monthly pmts. of £3-70. Total £38-80

L12/20 12" 20-25 WATT 13,000 lines 15 ohms. Carr. 30p.	L13 13" x 8" 10 Watt 10,000 lines 3 or 15 ohms. State im- pedance required. Carr 40p
£11-95	£5-25

RSC PHANTOM '50'

Combined 50w Amplifier and 12in. Loud-
 speaker. For Lead Guitar, mic., Gram, Radio, Tape (Not for use with Bass
 Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence.
 Output Jack for additional 15 ohm Speaker. Attractively finished in black with
 silver-finished fascia and trimmings. Compact size. Fitted carrying handle.
 Terms: Deposit £8-95 and 9 monthly
 payments 28 (Total £82-95). Carr. £1-30

ONLY £55-95

CREDIT TERMS AVAILABLE ON PURCHASES OVER £8 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

V.A.T!
 PRICES QUOTED—INCREASE FROM APRIL 1st.

RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit
 for lead, rhythm, bass guitar, vocalists,
 gram, radio, tape. Peak Output rating.
 Loudspeaker unit either horizontal or
 vertical mounting.
 * Two extra heavy duty 12in. 50w
 Loudspeakers.
 * Four Jack inputs and two Volume
 Controls for instant use of up to four
 pick-ups or "mikes". Bass and Treble
 controls. Send S.A.E. for leaflet.
 Credit Terms: Deposit £15 & 9
 monthly payments of £6-25.
 (Total £71-25.) Carr. £2

£65



NOW FOUR NEW BRANCHES

- NOTTINGHAM 19/19A MARKET STREET
 SUNDERLAND 5 MARKET SQUARE
 STOCKPORT 8 LITTLE UNDERBANK
 COVENTRY 17 SHELTON SQUARE
 NEW LARGER PREMISES AT HULL,
 DARLINGTON & NEWCASTLE See
 Addresses

R.S.C. Branches operate a 5-day week Open all day Saturday

- BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
 BLACKPOOL (Agent) O & C Electronics
 227 Church Street
 BIRMINGHAM 30/31 Great Western Arcade,
 Tel. 021-236 1278 (Closed Wed.).
 COVENTRY 17 Shelton Square, The Precinct, 3
 DERBY 26 Osmaston Rd., The Spot (Closed Wed.)
 Tel. 41361
 DARLINGTON
 19 Northgate (Closed Wed) Tel 68043
 EDINBURGH
 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
 GLASGOW 326 Argyle St. (Closed Tues.).
 Tel. 248 4158
 HULL 7 Whitefriargate Tel. 20505
 LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
 LEEDS 5-7 County (Mecca) Arcade, Briggate
 (Closed Wed.). Tel. 28252
 LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
 LONDON 238 Edgware Road, W.2. (Closed Thurs.).
 Tel. 723 1629
 MANCHESTER 60A Oldham Street, (Closed Wed.).
 Tel. 236 2778
 MIDDLESBROUGH 106 Newport Rd. (Closed Wed.).
 Tel. 47096
 NEWCASTLE UPON TYNE
 24 Newgate Shopping Centre (Closed Wed.). Tel. 2146v
 NOTTINGHAM 19/19A Market Street (Closed Thurs.)
 Tel. 48068
 SHEFFIELD 13 Exchange Street (Castle Market Bldg.)
 (Closed Thurs.). Tel. 2071
 STOCKPORT 8 Little Underbank. Tel: 480-0777.
 SUNDERLAND 5 Market Sq. (Closed Wed.) Tel. 7

RSC GP30 HI-FI AMPLIFIER

For Guitar, Vocal or
 Instrumental Group

A 4 input, 2 vol. control Hi-Fi
 30 watt unit with Separate Bass
 and Treble controls. Current
 valves. Peak output rating.
 Strong Rexine covered cabinet with
 handles. Attractive black/silver P.V.C. fascia. Neon indicator.
 For 200-250v. A.C. mains. For 3 or 15 ohm
 speakers. Send S.A.E. for leaflet. Terms:
 Deposit £4-40 and 9 monthly payments of
 £2-45 (Total £29-45).

£23-50 Carr. 65p



RSC

HI-FI CENTRES LTD.
 MAIL ORDERS & EXPORT ENQUIRIES TO:—
 AUDIO HOUSE, HENCONNER LANE, LEEDS, 13.
 Tel: Pudsey (09735) 77681.
 TERMS C.W.O. or C.O.D. No C.O.D. under £1.
 POSTAGE 25p EXTRA UNDER £2. 30p EXTRA
 OVER £2 OR AS QUOTED. TRADE SUPPLIED.
 S.A.E. PLEASE WITH ENQUIRIES.
 SUPPLIERS TO GOVT. DEPT'S. H.M. FORCES.
 EDUCATION AUTHORITIES & HOSPITALS. Etc.
 MAIL ORDERS MUST NOT BE SENT TO SHOPS

Would you spend an hour a day to earn more money in Electronics - Television - Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already *in*, we can help you get on!

With our know-how and our wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics - in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments).

With ICS you study at home - at your own pace, when you choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step *now* towards a better paid, more assured future. Send for your FREE Careers Guide today.

ICS your key to the door of opportunity

Tick or state subject of interest and post to:
International Correspondence Schools, Dept. 232E,
Intertext House, Stewarts Road, London SW8 4UJ.

Subject of interest

- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- MPT General Certificate in Radio Telegraphy
- Audio, Radio & TV Engineering & Servicing
- Electronic Engineering, Maintenance, Engineering systems, Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

Name _____

Address _____

Occupation _____

Age _____

Accredited by the Council for the Accreditation of Correspondence Colleges

SOUND BARGAINS



BEST OF ALL WORLDS

VHF, FM, AM, A.F.C. AIR BAND, PUBLIC SERVICE AND WEATHER BANDS

BATTERY CHECK INDICATOR

GIANT POWER MULTI-WAVEBAND BROADCAST RECEIVER

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

OUR PRICE £10-50
+40p P. & P.

No less than 3 VHP BANDS. Picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHP Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHER-BAND. Frequency ranges: MW340-1600 KHZ, FM88-108MHZ, Airband 108-145 MHZ, VHF 145-175MHZ, 23 semiconductor-12 transistors, 11 diodes and thermistors. Automatic frequency control. 31" telescopic aerial. Runs off mains AC 230/250 volts or off 4 U11 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10" x 6" x 3". Written guarantee. Special magnetic ear-piece for personal listening, dry batteries FREE. **HURRY!** Limited quantity Fully guaranteed.

OUR PRICE £28-95
+50p P. & P.



8 WAVEBANDS AND WORLD MAP & TIME ZONE DIAL


Marine FM/VHF PUBLIC SERVICE BANDS 155-174Mcs. Fully guaranteed.

Tune into the world with this amazing world radio. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240 volt domestic mains supply. 14 Transistors; 9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with earphone for personal listening. Frequency ranges: Long wave 150-350Kcs. Medium 353-1695Kcs. 16-45Mcs. Short Wave 1.2-21Mcs. 88-108Mcs. Aircraft 108-135 Mcs. **PUBLIC SERVICE BANDS 155-174Mcs.** Fully guaranteed.

N.B. The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

SONIC SOUND AUDIO LTD. (Dept. PW11), 372 EDGWARE ROAD, LONDON, W.2. Tel. 01-723 0094.
Caters welcome Monday to Saturday 9 a.m.-6 p.m.

Stereo radio from your existing tuner.

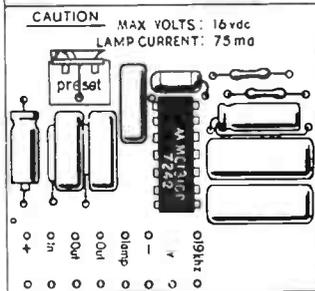

A complete set of parts from Jermyn to build a stereo decoder module that will convert your existing mono tuner for stereo reception whilst maintaining a high standard of reproduction.

The distortion is very low (typically 0.3% at 560 mV RMS composite input signal) with 40dB channel separation.

The stereo switching is automatic and there is a light emitting diode which acts as a stereo beacon.

The kit requires no coil and there are no alignment problems.

Fitting. The module requires a 10-16 volt power supply which can normally be tapped off the existing tuner. The signal input is taken off before the de-emphasis circuit which in practice means disconnecting one, or at the most, two capacitors. Any radio engineer will be able to spot these capacitors, but if you're really stuck send the circuit with a SAE to us and one of our engineers will indicate the output point. (This is the full extent of our involvement, no hardware please).

Of course, if you have a modern mono tuner with a multiplex output our module simply plugs in.

The outputs go via a screened twin cable to the tuner inputs of your stereo amplifier.

And the cost? £4.90 for the Kit with 100% tested integrated circuit. Also available assembled and aligned, checked and ready for use at £6.90 (includes 12 month guarantee). Beat that!

To Jermyn Industries 74 Vestry Estate Sevenoaks Kent

Please rush me Kit(s), made up Stereo decoders. I enclose cheque/postal order for £ _____
Name _____
Address _____

Block Capitals Please



There are 195 other good reasons for buying AMTRON electronic kits

Apart from the five items shown above, there are another 195 kits to choose from in the vast AMTRON range of electronic kits.

A few examples of equipment you can construct from AMTRON kits are:

Power supplies, preamplifiers, amplifiers, L.F. instruments, accessories for musical instruments, amateur and radio control transmitters and receivers, battery chargers, electronic car accessories, psychedelic lighting equipment, measuring instruments, tuners, receivers, I.C. digital equipment.

Only 1st class fully guaranteed components are used —solder is included with every kit.

Prices range from £1.10 to £80 and each kit is sold in protective blister pack containing complete instructions.

Should you experience any difficulty in obtaining AMTRON Kits please contact us direct.

PLEASE SEND FOR BROCHURE




TRADE & EDUCATION ENQUIRIES WELCOME

AMTRON U.K. 4 & 7 CASTLE STREET HASTINGS SUSSEX TELEPHONE HASTINGS 2875

TOP QUALITY — LOW COST



AMATEUR RADIO EQUIPMENT

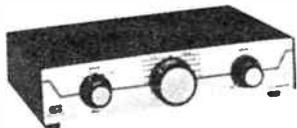

P.R.40

SOLID STATE
R.F. PRESELECTOR


The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supercedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30 dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee. £8-90 Carriage 30p.



MULTIBAND-6

SOLID STATE
SHORT WAVE RECEIVER KIT

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery). £13-20 Carriage 35p. Stamp brings illustrated leaflets.

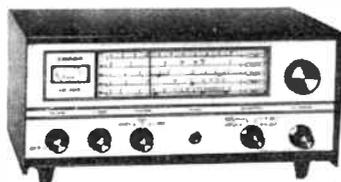

CR70A

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.V.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

Complete ready built £27-50, Carriage 70p.

SEND FOR YOURS TODAY!

NOTE: These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers and are FREE of Purchase Tax. Some portable receivers being advertised as Communication Receivers do not meet these requirements.



ON THE DESIGN STAFF—
G3SZM G3IRE

CODAR

TELECOMMUNICATIONS AND ELECTRONIC
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS
GOVERNMENTS

VALCON WORKS • BURRELL BUILDINGS • CHURCHILL INDUSTRIAL ESTATE • LANCING • SUSSEX
Tel. 090-63-61901 BN15 - 8TZ



NEW STEPHENSPEAKERS

A new range of loudspeaker kits and cabinets with a style and specification for every purpose. You'll be cheating a bit if you tell your friends "made it myself". We supply superb craftsmen built fully finished cabinets in beautiful stain and scuff resistant vinyl in white or teak.

Just fit the speaker cloth (supplied) and screw in your speaker.

**HIGH QUALITY
AT LOW COST**

Send for our free booklet
"Choosing a Speaker"



STEPHENSPEAKERS,
WILMSLOW AUDIO, Dept. 'PW', Swan
Works, Bank Square, Wilmslow SK9 1HF

ELECTROKIT

SCORPIO CAPACITOR DISCHARGE IGNITION SYSTEM (P.E. Nov. 1971)

Complete kit with full instruction data £9-50

"MUSIC MAKER" ORGAN KIT (P.W. Dec. 1972)
Kit includes only capacitors, semiconductors, switches, preset and loudspeaker. £2-80 OR

COMPLETE kit including above plus resistors, PC board and box £4-40

TRIFFID RADIO (P.E. Feb. 1973)

Kit of resistors, Capacitors, Transistors, Diodes, Potentiometer and I.C. £4-95

LIGHT DIMMER kit contains all parts including circuit and construction data. Fully suppressed, 480 Watts £2-10

DRILL SPEED CONTROLLER (E.E. Aug. 1972)

Complete kit (less MK box, plate and socket) £1-05
Complete kit including MK box, plate and socket £2-20

P.C. Boards not supplied, unless otherwise stated.

We are also able to supply other kits for articles published in *Practical Wireless* and other Electronic magazines. Send for details of other kits available. Please enclose a stamped addressed Envelope.

ELECTROKIT

12 Lauderdale Road, London, W.9

Telephone 01 - 286 0011

MON.-FRI. 9.30-5.30
THURS. 9.30-6.30

ZN414 £1.25 POST FREE
The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.
I.C. Sockets
Dual in line or 2g 2ag (Dull), 14 and 16 pin
Our Price 1p per pin

VDR's & Thermistors

A158	75p	GL23	£1.00	VA1005	15p
C21	15p	R53	£1.32	VA1026	13p
C24	13p	R54	£1.46	VA1033	13p
C213A	13p			VA1040	10p
E298 ED/A258	10p			VA1053	10p
E293 ZZ/D6	10p			VA1055	10p
GL16	£1			VA1034	10p

Potentiometers



5KΩ	50KΩ	500KΩ	
10KΩ	100KΩ	1MΩ	
25KΩ	250KΩ	2MΩ	

log or lin less switch (& 1KΩ lin) 12p
log or lin with switch 24p
dual less switch 40p
dual with switch 10K, 100K & 1M log only 52p
10K log 10K anti-log less switch 40p

Capacitors

dise ceramic	low voltage	
01μF 18v	5p	0.1μF 30v 5p
022μF 18v	5p	0.22μF 6v 5p
047μF 12v	5p	0.47μF 3v 5p
ceramic plate		30V
1000pf	10p	4700pf 10p
2200pf	10p	10,000pf 10p

Ceramic plate 63V (C333)

1 8pf	33pf	120pf
2 2pf	10pf	39pf
3 3pf	12pf	47pf
3 9pf	15pf	56pf
4 7pf	18pf	68pf
5 5pf	22pf	82pf
6 8pf	27pf	100pf

all 5p. each

mylar film 100V

1000pf	2p	01μF	3p	068μF	4p
2000pf	2p	02μF	3p	1μF	4p
5000pf	2p	04μF	3p	2μF	5p
		05μF	3p		

polystyrene 160V
10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. 3p each

metallized polyester 250V (C280)

01μF	3p	068μF	3p	47μF	8p
015μF	3p	1μF	4p	68μF	11p
022μF	3p	15μF	4p	1μF	13p
033μF	3p	22μF	5p	1.5μF	20p
047μF	3p	33μF	6p	2.2μF	24p

metallized polyester 400V (C281)

01μF	43p	047μF	6p	22μF	10p
015μF	43p	068μF	6p	33μF	14p
022μF	43p	1μF	7p	47μF	15p
033μF	53p	15μF	8p		

silvered mica 1% (50pf) 500V

2.2pf-820pf	7p	4.7nF-5600pf	19p
1nF-2.2nF	9p	6800pf-0.1μF	29p
2.7nF-3.6nF	16p		

mixed dielectric 600V

01μF	7p	047μF	7p	22μF	16p
022μF	7p	068μF	8p	47μF	24p
033μF	7p	1μF	8p	1μF	33p

Slider Pots

Single	Dual	log
10K	10 • 10K	or
25K	25 • 25K	lin
50K	50 • 50K	
100K	100 • 100K	Knobs
	50p	10p.

Resistors

1 watt 5% Carbon Film - low noise HI-Stabs

All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value.

1 W 10% Carbon Composition	3p each
2 W 10% Carbon Composition	6p each
2 1/2 W 5% Wire wound	9p each
5 W Wire wound	9p each
10 W Wire wound	10p each

plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25

Eliminators



9 volt → 20mA (PP3)	£1.25
9 volt → 50mA	£1.50
6 volt 50mA	£2.50
9 volt 50mA	£2.50
7 1/2 volt for cassette recorders	£2.00
6, 7 1/2 or 9 volt	£3.00
3, 4 1/2, 6, 7 1/2, 9, 12 → 500mA (tullu.)	£3.99

Car. Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts (p. & p. 15p on all types) £4.99

NEW LISTS
LOUDSPEAKERS No. 4
COILS AND INDUCTORS No. 5
TRANSFORMERS No. 8
(postage 5p)

Diodes & Rectifiers

AA119	9p	BA156	15p	BY176	£1.50
AA120	9p	BA243	56p	BY182	£1.50
AA129	9p	OA47	10p	BY250	23p
BA102	25p	OA79	9p	IN4001	6p
BA115	17p	OA90	7p	IN4002	7p
BA130	10p	OA91	7p	IN4003	8p
BA145	20p	OA200	10p	IN4004	8p
BA148	20p	BY100	15p	IN4005	10p
BA154	13p	BY126	15p	IN4006	12p
BA155	14p	BY127	15p	IN4007	15p

BY250 ZENER SERIES 10p each

SGS

EA1000



1 Watt Audio Amplifier
Our Price inc. handbook £2.48

FM TUNER chassis fully transistorised 9 volt operation. OUR PRICE £4.25
Matching stereo decoder £4.97
Ask for model list No. 11.



Presets


Vertical or Horizontal

0.1 watt 5p	0.25 watt 7p		
100 1K Ω	10K Ω	100K Ω	1M Ω
250 2.5K Ω	25K Ω	250K Ω	2.5M Ω
500 5K Ω	50K Ω	500K Ω	5M Ω

CHROMASONIC electronics

MAIL ORDERERS Where no p. & p. charge is shown a minimum of 7p applies, p. & p. on overseas orders is charged at cost.
ADDRESS TO: Component Dept., N10 3HN
56, Fortis Green Road, London
Telephone 01883 3705

Heat Sinks

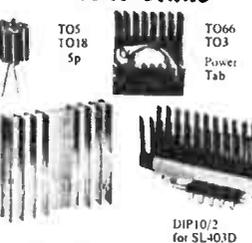

TOS 1018 5p
TO66 14p
TO3 15p
Power Tab 13p
DIP10/2 for SL401D 15p
10D 50p

Transistors & Integrated Circuits

AC107	25p	BC147	10p	BF196	15p	OC81	15p	2N1304	22p	2N5172	15p
AC126	17p	BC148	10p	BF197	15p	OC140	20p	2N1711	25p	2N5178	£1.50
AC127	15p	BC149	10p	BF197	23p	OC150	23p	2N1983	30p	LO3671	£1.50
AC128	15p	BC157	12p	BF198	24p	OC171	30p	2N2926	all	LO3771	£1.50
AC176	15p	BC158	10p	BFY51	21p	ZTX107	15p	2N3053	23p	MC1303L	£1.75
AC187	25p	BC159	12p	BRY33	34p	ZTX108	12p	2N3054	50p	MC1300	80p
AC187K	25p	BC169	15p	BS241	26p	ZTX109	15p	2N3055	49p	MC1300	75p
AC188	25p	BC264	15p	BSY65A	14p	ZTX300	12p	2N3072	12p	MC1351	£1.00
AC188K	25p	BD115	87p	BUI0502	£1.75	ZTX301	15p	2N3073	12p	MC1352	£1.00
ACY20	20p	BO131	70p	MJE360	87p	ZTX302	20p	2N3704	10p	MFC4000A	45p
AD140	40p	BO132	70p	MFF192	46p	ZTX303	20p	2N3705	10p	MFC4000B	45p
AD149	40p	BO131/2M P		MFF193	37p	ZTX304	25p	2N3706	10p	LM380	£1.45
AD161	148p			MFF194	37p	ZTX341	20p	2N3707	15p	PA234	£1.99
AD162	60p	BF160	21p	MFF195	46p	ZTX500	15p	2N3708	12p	SL403D	£1.50
AF114	18p	BF167	20p	MFF196	45p	ZTX501	15p	2N3709	12p	TA0100	£1.50
AF115	18p	BF173	20p	OC28	40p	ZTX502	20p	2N3710	12p	FILTER	£2.19
AF116	18p	BF180	25p	OC35	40p	ZTX503	17p	2N3711	12p	PA235	£1.50
AF117	18p	BF181	30p	OC44	15p	ZTX504	50p	2N3819	35p	A710	45p
AF139	28p	BF184	25p	OC45	15p	ZTX531	25p	2N3903	15p	A723C	95p
BC107	10p	BF185	25p	OC71	11p	2N697	18p	2N3904	17p	A741C	47p
BC108	10p	BF194	15p	OC72	17p	2N708	12p	2N3905	21p	A748C	60p
BC109	10p	BF195	15p	OC76	15p	2N708	15p	2N3906	12p		

mixed dielectric 1000V

1000pf	6p	6800pf	9p	1μF	12p
2200pf	6p	01μF	9p	22μF	22p
3300pf	6p	022μF	9p	33μF	14p
4700pf	6p	047μF	12p		

Ceramic

12KV.d.c.	8KV.d.c.	HI-K 750V.			
10pf	9p	200pf	9p	1000pf	5p
15pf	9p	220pf	9p	1500pf	5p
22pf	9p	250pf	9p	2000pf	5p
68pf	9p	270pf	9p	3000pf	5p
82pf	9p	300pf	9p	5000pf	5p
100pf	9p	750V O15C	10,000pf	5p	
120pf	9p	470pf	5p	feed-	
140pf	9p	1000pf	5p	through	
150pf	9p	5000pf	5p		
180pf	9p	10,000pf	5p	1000pf	5p

Veroboard

Copperclad Plain

0.1"	0.15"	0.15"
2 1/2" x 1"	6p	6p
2 1/2" x 3 1/2"	20p	16p (9)
2 1/2" x 5"	24p	21p (7)
3 1/2" x 3 1/2"	24p	21p (8)
3 1/2" x 5"	27p	27p (10)
17" x 2 1/2"	67p	50p
17" x 3 1/2"	90p	70p
17" x 5"		75p

Spot-face Cutter 36p
Pin Insertion Tool 47p
Terminal Pins 18p per pack of 36

Mullard B Siemens Electrolytics


CAP. μF	VOLTAGE					
	4	6.3	16	25	40	63
1.5	—	—	—	—	—	6p
2.2	—	—	—	—	—	6p
3.3	—	—	—	—	—	6p
4.7	—	—	—	—	—	6p
6.8	—	—	—	—	—	6p
10	—	—	—	—	—	6p
15	—	—	—	—	—	6p
22	—	—	—	—	—	6p
33	—	—	—	—	—	6p
47	6p	6p	—	—	—	6p
68	—	—	—	—	—	10p
100	6p	6p	—	—	—	10p
150	—	—	—	—	—	10p
220	6p	—	—	—	—	10p
330	6p	6p	—	—	—	10p
470	—	—	—	—	—	10p
680	—	—	—	—	—	10p
1000	—	—	—	—	—	10p
1500	—	—	—	—	—	10p
2200	—	—	—	—	—	10p
3300	—	—	—	—	—	10p
4700	21p	—	—	—	—	10p

NEW LISTS
BOXES, CHASSIS, etc. (No. 7)
TRANSISTORS, I.C.'s, etc. (soon)

Aluminium Boxes
Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2 1/2"	5 1/2"	1 1/2"	35p	8p
(8)	4"	4"	1 1/2"	35p	8p
(9)	4"	2 1/2"	1 1/2"	35p	8p
(10)	4"	5 1/2"	1 1/2"	40p	8p
11	4"	2 1/2"	2"	35p	8p
13	3"	2"	1 1/2"	32p	9p
13	6"	4"	2"	50p	10p
14	7"	5"	2 1/2"	58p	12p
15	8"	6"	3"	75p	18p
16	10"	7"	3"	85p	20p

THE TEXAN

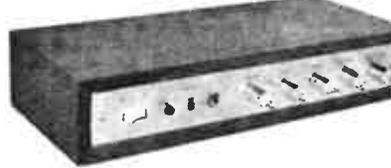

Complete kit (inc. Teak Case) **£28.50** plus 65p 45p

20 Watts per channel integrated stereo amplifier developed by engineers of Texas Instruments Ltd. This designer approved kit, has a state-of-the-art specification, including distortion of only 0.09% at 20 Watts into 8 ohms and a bandwidth of 5 - 35,000 at 3db. The semiconductor complement of this superb kit includes no less than 6 integrated circuits, 10 Silicon transistors, 4 rectifiers and 2 zeners. Controls include bass, treble, volume, balance, on/off indicators, headphone sockets, search filter, rumble filter, inputs for magnetic phono, tuner, aux or tape, tape head etc. input; selector; mono/stereo switch. The construction of this kit was featured in "Practical Wireless" May - Aug 1972.

Quantity Prices on application

CAP. μF	VOLTAGE			
	16	25	40	64
500	—	—	—	33p 40p
1250	—	—	—	50p
1600	—	—	—	75p
2000	—	—	—	75p
2500	—	—	—	75p 83p
3200	—	—	—	75p 83p
4000	—	—	—	75p 83p
6400	—	—	—	75p 83p

Hi-Volt Electrolytics

1.2	4.8μF	450V	14p	32μF	450V	20p	
16μF	450V	15p	50μF	350V	20p		
8	450 V.W	18p	32	32μF	450 V.W	25p	
8	18μF	450 V.W	20p	32	32μF	450 V.W	43p
16	16μF	450 V.W	25p	50	50μF	350 V.W	3p


UNISOUND FOR THE NEW SOUND



AT
£26.12
 INC. VAT

It's the RT-VC system that screws together to save you pounds! Unisound comprises two superb speakers and an amplifier/record deck plinth—all beautifully finished in simulated teak. The stereo amplifier (4 watts per channel into 8 ohms) is based on the famous Mullard Unilex system brought up-to-date by RTVC using intergrated circuits. Turntable is the proven Garrard 2025TC complete with stereo cartridge and tinted acrylic cover. Speakers are big EMI Twin-cone units all ready for mounting in their elegant cabinets, which simply need screwing and glueing together. Easy step-by-step instructions. £26.12 complete plus £1.40 packing + £1.40 post. Diamond Stylus £1.25 extra. Stereo headphones with adaptor £4 extra. Send for leaflet.

AN RTVC EXCLUSIVE DESIGN

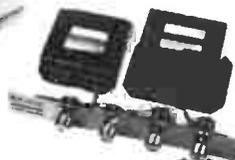

UNISOUND MODULES ONLY £6.95 + 50p. p. & p.

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together, 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips very low distortion at all power levels, over the audio spectrum.

RTVC No price in

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

THE TOURIST PB CAR RADIO KIT AN INCREDIBLE BUY ONLY FROM **RTVC**



£7.70
 inc. vat

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.


Apart from the output stage, which is an intergrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulised IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7" wide, 2" high and 4½" deep.

* Circuit diagram and comprehensive instructions 50p free with parts.

* Fully retractable lockable car aerial £1.25 post paid.

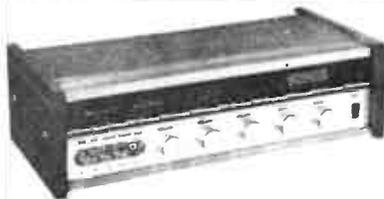PRICE ONLY £7.70 p. and p. 55p
 Speaker with baffle and fixing strips £1.50. 25 p. & p., post free if bought with the kit. Send for leaflet.



RELIANT Mk IV

A GOOD QUALITY AMPLIFIER—12 Watts £10.50 (inc. VAT). 20 Watts £13.50 (inc. VAT)


*5 Electrically Mixed inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling INPUTS 1. Crystal Mic or Guitar 9mV. 2.

Moving coil Mic. or Guitar 8mV Inputs. 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Power output: 12/20 watts into 8 ohms. Size approx. 12½ x 6 x 3½ ins.

12W version **£10.50** plus 60p p & p
 20W version **£13.50**

SOUND 50

50 WATT AMPLIFIER. Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19½ x 10½ x 8ins. Amplifier £31.85 plus £1.50 p. and p. **£38.51** (inc. VAT)

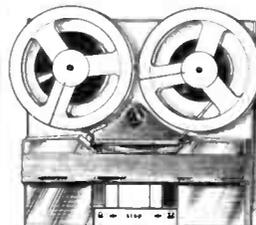

PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tape deck, less leads. Caters up to 7ins. spools. Unused but store soiled hence no warranty. **£8** plus 1p & p

* Denotes VAT has been absorbed in the price without increase on VISCOUNT audio systems.

crease with VAT!

VISCOUNT III AUDIO STILL ONLY £52* COMPLETE


14 + 14w. r.m.s. 40Hz to 40kHz ± 3dB. Total distortion at 10w. at 1kHz - 0.1%. This is real value for money! We have designed 2 systems and the heart of them both is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder.

For both systems we have chosen the famous Garrard SP25 Mk. III deck, with fitted magnetic cartridge, which comes complete with simulated teak plinth and tinted acrylic cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

PRICES: SYSTEM I
 Viscount III R 101 amplifier £24.20 + £1 p & p
 2 Duo Type II speakers £15.40 + £2.20 p & p
 Garrard SP25 Mk. III with
 MAG. cartridge plinth & cover £25.00 + £1.75 p & p
 total £64.60
 Available complete for only £52* + £3.50 p & p

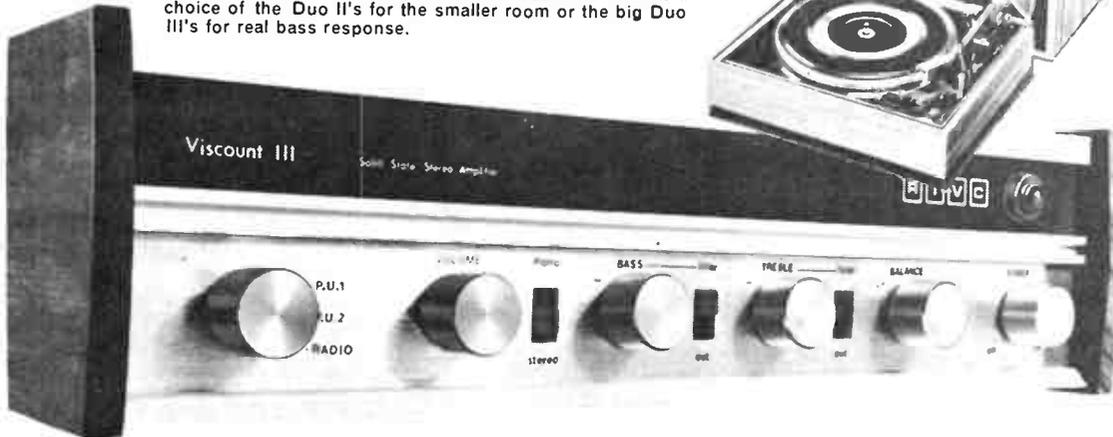PRICES: SYSTEM 2
 Viscount R 101 amplifier £24.20 + £1 p & p
 2 Duo Type III speakers £35.20 + £3.30 p & p
 Garrard SP25 Mk. III with
 MAG. cartridge plinth & cover £25.00 + £1.75 p & p
 total £84.40
 Available complete for £69* + £4 p & p



SPEAKERS: Duo Type II Size approx. 17in. x 10½in. x 6½in. Drive unit 13in. x 8in. with parasitic tweeter. Max. power 10 watts ohms. Simulated Teak cabinet. £15.40 a pair (inc. VAT), £3.30 p. and p. Duo Type III Size approx. 23½in. x 11½in. x 9½in. Drive unit 13½in. 8½in. with H.F. speaker. Max. power 20 watts ohms. Freq. range 20Hz to 20KHz. Teak veneer cabinet.

SPECIFICATION R101: 14 watts per channel into 3 to 4 ohms (suitable 3-15 ohms.) Total distortion @ 10W 1kHz @ 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Signal-to-noise ratio: (all controls at max.)—P.U.1. and radio — 65dB, P.U.2 — 58dB. Cross talk better than — 35dB on all inputs. Size approx. 13½in. x 9in. x 3½in. Send S.A.E. for fully illustrated brochure. 12 month's written guarantee.

ONLY FROM US

TIMES OF OPENING: Acton—Mon.—Sat. 9.30-5.
 Closed all day Wed.
 Edgware Rd.—Mon.—Sat. 9.30-5. Closed all day Thurs

VISIT OUR SHOWROOMS **RTVC**
 Radio and TV Components (Acton) Ltd.
 21c High Street, Acton, London W3 6NG
 323 Edgware Road, London W2
 Mail orders to Acton. Terms C.W.O.
 Goods not despatched outside U.K.
 All enquiries S.A.E.

All prices in pounds and new pence

VALVES		25		30		40		50		60		75		80		90		100	
1A7GT	45 61JG	25 62G	20 7CG	£1.13 10E1	40 25	40 10A19	45 6270	33 10A11	50 27A	£1.50 10A00	80 1403	60							
1CP31	£7.00 61Q7A	30 62M	45 74W	75 41E2	50 27	50 10A19	45 6270	33 10A11	50 27A	£1.50 10A00	80 1403	60							
1D5	50 61R7	50 62T4	30 71G	60 19AQA	50 20D5	50 10C90	£1.35 10C84	35 10A42	65 0A2	35 10A08	90 1901	£1.18							
1H5	50 61R7	60 62M	35 7E2	£2.25 20E1	£1.10 20E0T	55 10E1	30 10E84	30 10E84	£1.00 10E80	60 10E80	£1.10 10E80	55							
1N6GT	55 61N7	£1.30 62T4	35 82A	85 70F4	£1.10 70	50 10E92	20 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
1R5	40 61R7	85 62M	60 60C7	85 30A6	35 30	55 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
1R4	30 61W7	80 62A	40 10E7	75 10E60A	50 20A	55 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
1R5	30 61A	33 62M	50 10E1	90 20A1	65 10E80	60 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
1T4	30 625A	35 62G	75 10E9	60 20A1	30 10E80	60 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
3A4	40 61G	25 61G6	50 10E18	50 20E0A	55 80	60 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
3Q4	50 61D6A	£1.25 61E	45 10E10	85 20E0	65 80	60 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
3Q5	50 61E6	85 62M	40 10E13	80 20A1	£1.20 7A	45 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
2E4	25 62W4	85 62T4	43 11E2	£4.00 20E0	80 20E0A	75 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
2Y4	48 61E6	35 62A7M	40 10E7	30 20E17	96 20A	60 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
BR4GY	75 62S	£1.00 62M	75 12A7	35 30E18	80 10E0	55 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
BU4G	35 6F1	70 62G7M	40 12A7	35 30E18	80 10E0	55 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
BY4G	45 6F5A	60 62H7M	40 12A7	35 30E18	80 10E0	55 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
BY3GT	40 6F6G	25 62J7T	30 12A7	30 30E18	75 20E0	70 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
BZ4G	40 6F8A	25 62K7T	40 12A7	30 30E18	£1.20 7B5	30 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6J90L2	80 6F11	40 62L7GT	35 12E06	40 30E18	85 40	48 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6A7	75 6F13	45 62N7GT	35 12E06A	35 30E18	80 10E0	45 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6A8G	40 6F14	70 62Q7GT	40 12E1	£3.00 30F4	£1.12 10E0	60 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6AK5	35 6F22	85 61A4T	65 12J5GT	30 30E18	80 10E0	60 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6AM5	35 6F24	75 61B4	£1.00 12J7GT	30 30E18	85 10E0	£4.00 10E0	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6AM6	35 6F25	£1.00 61E5M	80 12K7GT	40 30E18	75 10E0	50 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6A96	35 6F28	85 61G6	30 12K8GT	50 30E18	93 10E0	55 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6A98	35 6F32	25 61G6T	40 12Q7GT	40 30E18	90 10E0	55 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6A87G	85 61G6	35 61A	25 12E7A7T	50 35A2	75 10E0	£1.00 10E0	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6A7E	35 61H6	25 61G6	40 12E87	35 35E6	50 10E0	75 10E92	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6A16	25 61J5M	50 61K5GT	40 12E87	35 35E6	50 10E0	£1.30 10E0	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6B4G	£1.00 61J5G	20 71G6	70 12E87	40 35E6A7	80 10E0	£1.30 10E0	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							
6B8G	25 61J5GT	30 71B7	50 12E87	50 35E6	50 10E0	£1.30 10E0	45 10E80	40 10E80	45 10E80	60 10E80	£2.50 10E80	40							

Transistors		AC128		20 BY100		15 NKT113		25 0C44		17	
1N914	07 2N2219	20 AC128	20 BY100	15 NKT113	25 0C44	17					
1H113	25 2N2369A	20 AC129	20 BY100	15 NKT113	25 0C44	17					
1R202	23 2N2444	15 AD149	50 0CR140	47 0A71	10 0C57	60					
20302	22 2N2646	45 AF115	50 10D003	15 0A81	08 0C58	60					
24371	22 2N2904	20 AF117	50 10G102	30 0A85	12 0C59	65					
2N404	20 2N2926	10 AR226	25 0A782	25 0A81	07 0C71	12					
2N497	15 2N3055	75 H1107	10 MJ2955	10 0A210	32 0C82	20					
2N706	10 2N3702	10 RC104	10 0A222	45 0C92D	20						
2N1132	25 2N3819	35 RC109	10 MJ3055	87 0A224	45 0C94	25					
2N1305	22 2N4212	30 BC169C	15 NKT212	27 0A2241	22 0C101	20					
2N2147	75 2N4212	30 BF89A	28 NKT214	15 0A2242	23 0C171	40					
2N2160	60 AC126	20 BFV50	22 NKT230	33 0A2246	23 0C200	40					
2N2218	20 AC127	25 BPS51	20 NKT251	24 0C35	50 0C271	97					

RST VALVE MAIL ORDER CO. 16a WELLFIELD ROAD, LONDON SW16 2BS
 Special Express Mail Order Service TELEX 946708 Send large S.A.E. for list. Phone 677 2424 (4 lines)
 Express postage 1p per transistor, over 10 post free. Integrated Circuits & Valves 5p, plus 1p for each additional item, over £5.00 post free

P. C. BOARDS



Reverberation Unit PCB.

FOR P.W. PROJECTS

All PCB's Fibreglass, Drilled, Roller-Tinned
Circuit and Layout Diagrams free with each PCB

REVERBERATION UNIT (Nov/Dec 1972)
 PCB (2in x 11 1/2in). Specially designed to also hold Slider Pots with spacing compatible with published front panel £1.20
 SET of R's, C's, S/C's, Slider Pots, Transformer £5.95

8 WATT AMPLIFIER (Nov 1972)
 PCB (Mono—2 1/2in x 3in) 60p
 R's, C's, Semiconductors: Stereo Set £7.70, Mono Set £3.90

PRE-AMPLIFIER (Nov 1972)—for use with 8 Watt Amplifier
 PCB (Stereo—3 1/2in x 7 1/2in) Specially designed to also hold all Pots, either rotary or slider, plus Selector Switch £1.50
 R's, C's, Rotary Pots, Selector Switch, Semiconductors:
 Stereo Set £5.20, Mono Set £2.50
 Slider Pots & Knobs instead of Rotary Pots:
 Stereo—Extra £1.52, Mono—Extra £1.26

LOUDHAILER & SIREN (Dec 1972)—PRE-AMP & SIREN GENERATOR
 PCB (2 1/2in x 2 1/2in) 75p.
 Set of R's, C's, Pot (with switch), Semiconductors £1.45

VIBRASONIC GUITAR PRE-AMP (Sept 1970)
 PCB (4in x 13in) for Mic Pre-Amp, 2-Guitar Pre-amp, Tremulant & Tone Controls, Wah-Wah, Master Volume. Specially designed to also hold all pots, either Rotary or Slider. £2.85
 Set of S/C's, R's, C's, Rotary Pots, LDR, Lamp, Coupling T/iformer £7.75, Power supply £2.80.
 Slider Pots & knobs instead of Rotary Pots—Extra £3.36

DIGITRONIC DIGITAL CLOCK (Feb. 1973)
 Details on request.

Other Designs Available. S.A.E. for List (F/scan) and enquiries.
 POSTAGE: U.K. 10p any order. OVERSEAS at cost.
 V.A.T. will be charged on all U.K. orders from April 1st.

PHONOSONICS

DEPT. PW4, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
MAIL ORDER ONLY

AMAZING MINI-DRILL



Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £4.95 p.p. 13p. De Luxe Professional Kit with 17 tools £7.65 p.p. 23p. Money back refund.

FOR PRECISION MODEL WORK

+ 6 TOOLS

MERLIN SUPPLY CO.

Dept. PW473 Nailsea, Bristol BS19 2LP

BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING BROADWAY,
LONDON S.W.17 0J-672 3984

CARTRIDGES—Stereo Sonotone 9TA H/C Diamond £2.40.
 Ronette S105 Medium Output £1.40, S106 High Output £1.40, Acos GP93/J, Sapphire 1-90, GP94/J Sapphire £2. Japanese equivalent to B.S.R. TC8's £1-75. P. & P. 7p on each.

CARTRIDGES—Mono GP91 Stereo Compatible £1.25. B.S.R. TC8H jap. equivalent £1.25. P. & P. 7p.

HI-FI STEREO HEADPHONES Padded ear cushions seal out room noise. Perfect coupling between reproducer and ears assure full response impedance 8 ohms, frequency range 20-20,000 Hz 6ft. cord and standard stereo plug. Only £2.57. P. & P. 27p.





STEREO HEADPHONE JUNCTION BOX
 Simple unit connects direct to amplifier and speakers to give attenuated headphone output has 3 position switch to give headphones only, speakers only, speakers and headphones. Only £1.50. P. & P. 13p.

VYNAIR Widths from 50 to 5 1/2in., 75p yd. off roll. P. & P. 10p, 1/2 yard 40p. P. & P. 10p. Send 5P stamps for samples.

look! electronics really mastered

... practical
... visual
... exciting!

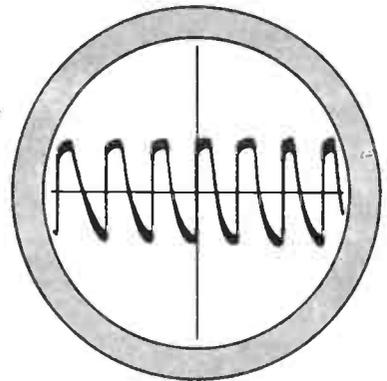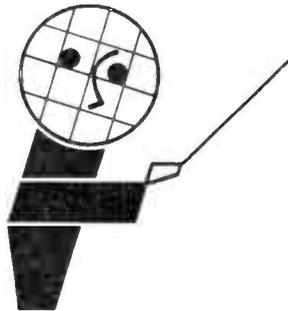no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

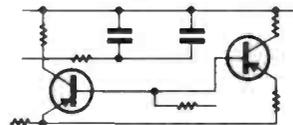2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**

P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL43

special free gift also to all our students

ESSENTIAL BOOKS FOR RADIO AMATEURS

New Edition A GUIDE TO AMATEUR RADIO

by Pat Hawker
G3VA

Extensively revised, this new (15th) edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby.
90p post paid

New Book TELEVISION INTERFERENCE MANUAL

by B. Priestley
G3JGO

The causes of interference to TV receivers are examined, and ways in which they can be overcome are suggested in this latest RSGB publication.
90p post paid

RAE MANUAL

by G. L. Benbow
G3HB

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination.
90p post paid

RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's UK origin ensures easy availability of components. Complete coverage of technical and constructional fields.
£4.10 post paid


These are just four of a complete range of technical publications, log books and maps for the Radio Amateur. Send s.a.e. for complete list

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688



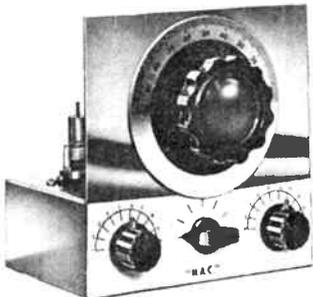H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER

Complete kit—price £3-80 (post & packing 20p). Customer writes: "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc. This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other R.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, test report and order form. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

EX COMPUTER PRINTED CIRCUIT PANELS

2 x 4 in. packed with semi-conductors and top quality resistors, capacitors, diodes etc. Our price 10 boards 50p (8p). With a guaranteed min. of 35 transistors—data included.

SPECIAL BARGAIN PACK

25 boards for £1 (25p).
ELECTROLYTICS
10,000 μ 75v, 33,000 μ 40v, 4 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in. dia., 25,000 μ 25v, 20,000 μ 30v, 8,000 55v, 4 $\frac{1}{2}$ x 3 in. dia. 50p (12p), 15,000 μ 15v, 4 $\frac{1}{2}$ x 2 in. dia. 20p (10p), 2,000 μ 25v wire ended, 3 x 1 in. dia. 15p (5p) or 12 for £1-50 (15p).

250 MIXED CAPACITORS 60p (8p)

250 MIXED RESISTORS 60p (8p)

3A STUD RECTIFIERS, 100 p.i.v.

4 for 50p (5p)

ASSORTED RELAYS 8 for £1 (25p)

SUB MIN. CO-AX. PLUGS & SKTS.

4 pairs 50p (5p)

MINIATURE GLASS NEONS

12 for 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES, MIXED

8 for 50p (8p)

PAPST EXTRACTOR/BLOWER FANS

100 cfm 4 $\frac{1}{2}$ x 4 $\frac{1}{2}$ x 2 £3-50 (28p)

QUARTZ HALOGEN BULBS

12v 55w 50p (5p)

Postage and package for each item shown in brackets.

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8.

01-478 8499

TRANSFORMERS

DOUGLAS GUARANTEED

Output V. & Amps.	12 or 24 volts	Ref. No.	Price P. & P.
12V x 2	250 mA x 2	MT111 CS*†	£0-91 9p
12V x 2	500 mA x 2	MT213 CT*†	£0-87 16p
12V x 2	1A x 2	MT 71 AT*	£1-48 24p
12V x 2	2A x 2	MT 18 AT	£2-06 30p
12V x 2	3A x 2	MT 70 AT	£2-59 32p
12V x 2	4A x 2	MT 108 AT	£2-92 34p
12V x 2	5A x 2	MT 72 AT	£3-33 42p

30 volts. All tapped at 0-12-15-20-24-30V

Out- Ref. No. Price P.P. Out- Ref. No. Price P.P.

put

Amps. £

500 mA MT 112 CT* 1-12 16p 3A MT 20 AT 2-64 32p

1A MT 79 AT* 1-55 29p 4A MT 21 AT 3-10 40p

2A MT 3 AT 2-23 30p 5A MT 51 AT 4-31 42p

50 volts. All tapped at 0-19-25-33-40-50V.

500 mA MT 102 AT* 1-45 24p 3A MT 105 AT 3-81 41p

1A MT 103 AT 2-00 32p 4A MT 106 AT 3-06 41p

2A MT 104 AT 3-10 32p 6A MT 107 AT 4-47 50p

60 Volts. All tapped at 0-24-30-40-44-60V.

500 mA MT 124 AT* 1-46 30p 2A MT 127 AT 3-16 41p

1A MT 126 AT 2-24 32p 3A MT 125 AT 4-59 41p

AUTO-WOUND RANGE

Power Winding tapped at Ref. No. Price P. & P.

output

20 VA 0-115-210-240 MT 113 CT £0-89 14p

75 VA MT 64 AT £1-72 30p

150 VA 0-115-200-220-240 MT 4 AT £2-15 32p

200 VA MT 65 AT £3-00 32p

400 V. Output at 50 Hz. Ref. IT3 AT Price P. & P.

C-1 Ignition system by R. M. Marston £2-30 29p

Eq.

EQUIPMENT RANGE

Sec. Output (r.m.a.) Ref. No. Price P. & P.

3-0-3 V. 200 mA MT 238 CS*† £0-89 8p

9-0-9 V. 100 mA MT 13 CS*† £0-91 8p

12-0-12 50 mA MT 239 CS*† £0-91 8p

20-0-20 30 mA MT 241 CS*† £0-91 8p

0-20 x 2 300 x 2 MT 214 CT*† £1-21 16p

0-4-0 x 2 500 mA x 2 MT 207 CT*† £1-45 19p

0-15-20 x 2 500 mA x 2 MT 205 AT*† £2-12 29p

0-15-27 x 2 500 mA x 2 MT 203 AT*† £2-45 29p

0-15-27 x 2 1A x 2 MT 204 AT*† £3-42 36p

10-12-0-12-20 700 mA (l.c.) MT 221 AT*† £1-11 26p

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. spalls; * with interwinding screen; † untapped 240V Primary; ‡ Primary tapped at 210-240V.


Other Primaries tapped at 200-220-240V.

Over 200 types in stock through agents or direct. Send for list.

DOUGLAS ELECTRONICS INDUSTRIES LTD.

(Dept. MO.12FW), Thames St., LOUTH, Lincs. LN11 7AD

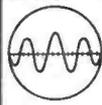MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.30 a.m. - 6.00 p.m.



TUAC

TRANSISTOR UNIVERSAL
AMPLIFICATION COMPANY LTD.
163 MITCHAM ROAD, LONDON SW17 9PG
01-672 3137 9080

ARE PROUD TO ANNOUNCE AN ENTIRELY NEW RANGE OF PROFESSIONAL STANDARD DISCOTHEQUE EQUIPMENT AND AUDIO MODULES

TUAC DISCOTHEQUE MIXER FEATURING AUTO FADE



£20.00 Complete PSU £3.25 p. & p. 50p. p. & p. 25p


FEATURES: MIC input with volume and tone control. Automatic MIC override, with a djustable fade depth and sensitivity, fades the music down when you make your announcements, then the music automatically returns to its original level. Left and right deck volume. Master volume, treble and bass controls. Headphone monitor facilities for both decks. Headphone volume control. Automatic manual override switch. Panel mounting, finished in durable satin enamel. 40V. D.C. operation. Tone control specification as for VAO6 pre-amp.

TUAC HIGH POWER AMPLIFICATION—built to high standards, and built to last



£49.50 p. & p. £1 00

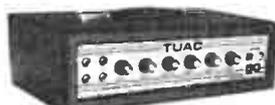100 Watt RMS Sine Wave Slave Amplifier. Suitable for use with above mixer. Slave input, gain control, slave output. Hi/Lo sensitivity switch. Rugged circuit. Rugged leather-cloth covered case. Short and open circuit protection. Over 200 watts peak output. 8Ω output. Impedance.



£41.25 p. & p. £1 00
100 watt version £60.50 p. & p. £1 00.


50 Watt RMS Sine Wave General Purpose Amplifier. Suitable for Disco, PA, Guitar. 4 inputs. 2 volume controls. Master volume, treble, middle and bass controls. Rugged circuit, rugged leather-cloth covered case, short and open circuit protection. Tone control specification as VAO8 pre-amp.

TUAC MICROPHONE MIXERS—battery operated—all steel construction



£14.12 p. & p. 35p

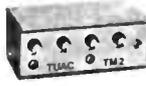FEATURES: 4 inputs with adjustable sensitivity, volume and extra wide range tone control on each input. 2 outputs, stereo or mono use. Max output 2V. Low noise silicon transistor line up. 18V. D.C. operation.



£8.25 p. & p. 40p.

FEATURES: 2 Inputs with adjustable sensitivity, volume and extra wide range tone control on each input. Single output. Mono use max. output 2V. Low noise silicon transistor line up. 18V. D.C. operation.


TUAC COMBO AMP.



£60.00 p. & p. £1 50.

25 Watt RMS Sine Wave Ideal for small groups, club and studio work. 4 inputs, 2 volume controls. Master volume treble, middle & bass. Uses heavy duty Celestion speaker.

TUAC POWER AMPLIFIER MODULES—TP 100W now with 4 RCA 150 watt output transistors

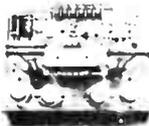

TP100W. T.H.D. at full power 2%.

All output power ratings are R.M.S. continuous sine wave using specified supply. Each circuit incorporates a robust driver transformer stage with thermal overload protection and is short and open circuit proof. Full power response 10Hz-20KHz ±2dB. Input sensitivity 30mV into 3KΩ. Hum and noise better than -70dB. Output impedance 8Ω. Constructed on glass fibre P.C. board. O/P matching transformer 4-8-16-60-100Ω £8.00.

TP100W 100 watts RMS output into 8Ω £15.18 p. & p. 45p.
PS100 Power supply and transformer £9.10 p. & p. 50p.
PS100/100 Supply for two TP100W modules £18.00 p. & p. 65p
TP50W 50 watts RMS output into 8-15Ω £10.36 p. & p. 40p.
PS50 Power supply and transformer £6.86 p. & p. 50p.
PS50/50 Supply for two TP50W modules £11.95 p. & p. 65p.
Two TP100W modules can be wired in a bridge output circuit to give a single 200W R.M.S. output into 8Ω using PS100/100 supply. Use phase splitter PS201 to drive modules.

TUAC PRE-AMPLIFIER MODULES

VA06 Suitable crystal/ceramic P.U., Mic., guitar, radio tuner, vol., treble & bass controls. Sensitivity 8mV for 30mV O/P Treble +22 -15dB @ 12KHz. Bass ±18dB @ 40Hz.

VA08 As VA06, but with extra middle control. Treble +28dB @ 18KHz. Middle +20 -15dB @ 4KHz. Bass +20 -10dB @ 40Hz. Sensitivity 4mV.

SVA01 As VA08 but stereo with bal. control.

MVA01 Suitable for disco, mic., tape input. 2 inputs, with Vol. & tone control on each input. Sensitivity 2mV. +25dB @ 12KHz to +20dB @ 40Hz.

MEVA01 Magnetic Cartridge equalisation. Connects to input of VA06 or VA08 with volume control.

SIPAM Master volume and presence control. High treble boost of +15dB @ 15KHz.

EFVUA01 Increases the output of any of the above to 1V. R.M.S. Low impedance emitter follower output.

Constructed on glass fibre P.C. Board, individually tested.

NEW RANGE

HPA01 Headphone Amplifier. 8-15Ω 200mV output. Left right fader. Volume control.

AMF01 Auto Fade Unit. Feed deck and Mic. Pre-amps in, output to power module. With fade depth and sensitivity controls. See spec. on disco mixer.

PS201 Phase Splitter unit to drive two TP100W modules in bridge O/P.

WAA01 WAA-WAA Module. This is an exceptional unit, producing a superb WAA-WAA for guitars. Pedal soon available.

FUZ01 Fuzz Module. Professional standard. Volume, tone & fuzz sustain controls. Case soon available.

FXD01 Frequency Doubler Module. Doubles the frequency of any sinusoidal wave, such as that obtained from the WAA-WAA module.

TUAC LIGHT MODULATORS



3 Channel S1LMB illus.

Constructed on glass fibre P.C. board, individually tested.

Three channel light modulator will control three separate sets of lights, up to 1000 watts each set. One channel responds to the bass, one to the middle, and one to the high frequencies. Input sensitivity only 0.5 watt/ Three individual controls allow for adjustment of the three channels, and a master sensitivity control allows for input levels up to 100 watts to be safely accommodated. Full interference suppression. Full wave control. Isolating input transformer does not affect Amplifier operation. Fully Fused.

S1LMB 3 Channel £17.45 p. & p. 35p.

Single Channel version, S2LMD Increased capacity of 1800 watts. Sensitivity control. Isolating input transformer does not affect amplifier operation.


S2LMB 1 Channel £6.47 p. & p. 25p.

POWER SUPPLY UNIT

For use with all pre-amp modules and discotheque mixer. Output 40V. 100mA £3.25 p. & p. 25p.

ALL PRICES ARE EFFECTIVE FROM 1st APRIL 1973 AND ARE INCLUSIVE OF V.A.T.

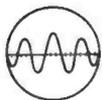ALL TUAC KITS ARE SUPPLIED COMPLETE WITH EASY TO FOLLOW WIRING INSTRUCTIONS AND CIRCUIT DIAGRAM. CALL FOR A DEMONSTRATION OF ANY OF THE ABOVE UNITS. SPEAKERS AND CABINETS ALSO SUPPLIED.



TUAC

LARGE S.A.E. WITH ALL ENQUIRIES PLEASE.

OUR TECHNICAL STAFF WILL BE PLEASED TO ADVISE YOU ON ANY PROBLEM. ALL TUAC EQUIPMENT CARRIES A 12 MONTH GUARANTEE. TRADE AND EXPORT ENQUIRIES WELCOME.

DISCOUNTS UP TO

60%

£17.45

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION: AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE

GARRARD SP25 Mk III Special Purchase.
Limited number available
Garrard SP25 Mk. III
Goldring G800
Teak plinth and tinted cover
All leads supplied.
Please add £1.25 P. & P. & Ins

AMPLIFIERS

- Please add 85p P. & P. & Ins.
- Amstrad 8000 Mk. II £14.95
 - Amstrad IC2000 £27.50
 - Amstrad Integra 4000 £22.50
 - Armstrong 521 (Teak cased) £43.90
 - Alpha Highgate 212 £24.85
 - Alpha Highgate FA300 £32.25
 - Alpha Highgate FA400 £35.65
 - Leak Delta 70 £44.85
 - Leak Delta 70 £54.90
 - Metrosound ST20E £24.20
 - Metrosound ST60 £45.95
 - Pioneer SA600 & 610 £57.25
 - Pioneer SA500A £31.95
 - Pioneer SA1000 £96.95
 - Rogers R/brook (Chassis) £37.95
 - Rogers R/brook (Cased) £41.50
 - Rogers R/bourne (Chassis) £49.95
 - Rogers R/bourne (Cased) £52.75
 - Sinclair PR060 2 X Z30/PZ5 £14.70
 - Sinclair PR060 2 X Z30/PZ6 £16.70
 - Sinclair PR060 2 X Z50/PZ8:
 - Trans £22.95
 - Sinclair AFU (Filter Unit) £4.20
 - Sinclair 605 £17.95
 - Sinclair 2000 Mk. II £21.50
 - Sinclair 3000 Mk. II £28.00
 - Wharfedale Linton £39.70
 - Teleton SAQ 307 £22.95
 - Rotel RA310 £34.95
 - Rotel RA610 £52.95

TURNTABLES

- Please add 75p P. & P. & Ins.
- Connoisseur BD1 Chassis £12.75
 - Garrard SP25 Mk. III £9.90
 - Garrard AP76 £17.20
 - Garrard 5L65B £13.95
 - Garrard 401 £28.75
 - Garrard Zero 100 (Auto) £36.90
 - Garrard Zero 100 (Single) £35.90
 - BSR MP60 £9.40
 - Goldring GL72 £20.90
 - Goldring GL72/P £27.45
 - Goldring GL75 £26.85
 - Goldring GL75/P £34.95
 - Goldring 101/P.C. £25.90
 - Wharfedale Linton + cart. £25.90
 - Thorens TD125AB Mk. II. £27.95
 - Thorens TD150 Mk. II £91.45
 - Thorens TD160 AB & C £53.95

TUNERS

- Please add 85p P. & P. & Ins.
- Amstrad Multiplex 3000 £27.25
 - Armstrong 523 £39.50
 - Armstrong 524 £31.45
 - Rogers R/brook FET4 (Chassis) £35.75
 - Rogers R/brook FET4 (Cased) £38.95
 - Rogers R/bourne FET4 (Chassis) £45.00
 - Rogers R/bourne FET4 (Cased) £49.50
 - Sinclair PR060 (Module) £16.95
 - Sinclair 2000/3000 Tuner £29.90
 - Leak Delta FM (Cased) £53.60
 - Leak Delta AM/FM (Cased) £63.75
 - Alpha Highgate FT150 £37.95
 - Metrosound FMS 20 £38.65
 - Philips RH 690 £33.00

TUNER/AMPLIFIERS

- Please add £1 P. & P. & Ins.
- Alpha Highgate 150 £49.75
 - Armstrong 525 (Teak cased) £69.45
 - Armstrong 526 AM/FM (Teak cased) £77.25
 - Leak Delta 75 £129.00
 - Teleton 2100 £32.50
 - Goodmans One Ten £98.90
 - Goodmans Mod 90 £85.50
 - Rotel 150 £49.50
 - Rotel 400 £75.50
 - Rogers Ravensbrook (Teak cased) £77.00
 - Rogers R/brook (Chassis) £72.00
 - Alpha FR 3000, New product. £72.00

SPEAKERS

- Please add £1.50 per pair P. & P. & Ins.
- Amstrad 138 £13.90
 - Wharfedale Denton 2 £28.40
 - Wharfedale Linton 2 £35.40
 - Wharfedale Melton 2 £45.90
 - Wharfedale Dovedale 3 £59.80
 - Celestion Ditton 120 £38.40
 - Celestion Ditton 15 £51.00
 - Celestion Ditton 25 £84.50
 - Celestion County (new prod.) £34.50
 - Goodmans Double Maxim £47.40
 - Goodmans Mezzo 3 £45.95
 - Goodmans Magister £82.95

Special bulk purchase **£2.90**



Plus 65p P. & P. & Ins. Finished in teak veneer with tinted dust cover. (Fully assembled). For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B; Also for McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B*. £3.90 + 65p P. & P. & Ins. Also finished in walnut to match Japanese equipment—at no extra.

- ### CARTRIDGES
- Please add 10p P. & P. & Ins.
- Goldring G850 £3.35
 - Goldring G800 £4.70
 - Goldring G800E £7.50
 - Goldring G800 Super E £14.15
 - Shure M3D £3.70
 - Shure M44E £4.75
 - Shure M55E £5.55
 - Ortofon SL15 £15.85
 - Sonotone 9TAHC £1.35

All prices Correct at time of press E. & O. E. and are subject to alterations

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PW4) 174 Pentonville Road, London, N1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.
MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).
2 minutes from KING'S CROSS. EUSTON & ST. PANCRAS on main road leading to the East and West Country

ERSIN
Multicore
5 CORE SOLDER



for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS



Size 5 Savbit alloy 18 swg, 18p (illustrated).
Size 19A 60/40 alloy 18 swg, 18p
Size 15 60/40 alloy 22 swg, 22p

IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 25p




Size 12 for Service Engineers and Electricians. 75ft of 18 swg Savbit alloy. 75p



NEW! BIB WIRE STRIPPER AND CUTTER

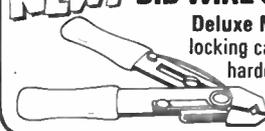Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p



Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

ELEKON SPECIALS

TWIN POWER SUPPLY PANELS, contains 2 x Texas 1B10J10 Silicon Bridge Rectifiers, 100 P.I.V. at 1A; 1 x Mullard OA2225 Zener Diode, 7.5V, 10W; 1 x I.T.T. Zener Diode, 5-1V, 1W; 5 x Texas 1B121 Silicon Diodes, 150 P.I.V. at 200mA. Electrolytic Capacitors: 2 x Plessey 1,000µF, 25V; 2 x 50µF, 50V; 2 x Mullard 250µF, 25V; 2 x Mullard 640µF, 25V. Circuit details supplied. Our best ever bargain £1. post 10p.

ELECTROLYTIC CAPACITORS µF/V 1250/25, 2000/35, 2200/25, 4700/14, 4000/30, 10,000/15, 10,000/25, 16 + 16/500, 1000 + 1000/40. All at 38p each, post free. 16 + 16/350, 32 + 16/350, 40 + 40/250, 50 + 50/300, 80 + 80/450, 100 + 100/385. All at 25p each, post free. 2000/50, 2500/50, 5000/50, 10,000/50, 12,500/50, 50p each, post free.

SOXOL DE-SOLDER BRAID, 9 ft. length 50p, 20 ft. length £1.00, 50 ft. length £2.50. Enquiries invited for any Electrolytic Capacitors. Special Bulk Prices. We Guarantee all our Capacitors.

ELEKON ENTERPRISES

224a St Paul's Road, Highbury Corner, London N.1

LEARN RADIO & ELECTRONICS AT HOME

No knowledge needed—build as you learn with the exciting new 'Technatron' kit. No Extras. Tools, transistors, meter etc. All supplied. You could build a radio in weeks.

SEND FOR FREE 76 PAGE GUIDE TO RADIO/TV, ELECTRONICS, C & G, TELECOMMS ETC.

Dept. BPW14 Aldermaston Court, Reading RG7 4PF

Name.....
Address.....
.....
Age..... CV BPW14

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-20	AD162	0-33	BC148	0-10	BD137	0-45	BF188	0-40	CG19	0-35	2G371B	0-16	2N2219	0-20	2N3054	0-46	2N4059	0-10
AC113	0-20	AD161A		BC149	0-12	BD138	0-50	BF189	0-12	CG20	0-63	2G371B	0-12	2N2220	0-22	2N3055	0-50	2N4060	0-12
AC116	0-20	AD162 (MP)		BC150	0-18	BD139	0-18	BF193	0-12	CG22	0-38	2G374	0-17	2N2221	0-20	2N3056	0-14	2N4061	0-12
AC117K	0-20		0-55	BC151	0-20	BD139	0-60	BF194	0-14	CG23	0-42	2G374	0-17	2N2222	0-20	2N3057	0-16	2N4062	0-12
AC122	0-12	ADT140	0-50	BC152	0-17	BD153	0-80	BF197	0-14	CG24	0-56	2G377	0-30	2N2268	0-17	2N3092	0-14	2N4284	0-17
AC125	0-17	AF114	0-24	BC153	0-28	BD175	0-60	BF200	0-45	CG25	0-38	2G378	0-16	2N2269	0-14	2N3093	0-14	2N4285	0-17
AC126	0-17	AF115	0-24	BC154	0-30	BD176	0-60	BF222	0-95	CG26	0-25	2G381	0-16	2N2269A	0-14	2N3094	0-14	2N4286	0-17
AC127	0-17	AF116	0-24	BC157	0-18	BD177	0-65	BF257	0-45	CG28	0-50	2G382	0-16	2N2311	0-24	2N3095	0-17	2N4287	0-17
AC128	0-17	AF117	0-24	BC158	0-12	BD178	0-65	BF259	0-60	CG29	0-50	2G401	0-30	2N2312	0-24	2N3096	0-21	2N4288	0-17
AC132	0-14	AF118	0-35	BC159	0-12	BD179	0-70	BF259	0-85	CG35	0-42	2G414	0-30	2N2346	0-47	2N3403	0-21	2N4289	0-17
AC134	0-14	AF124	0-30	BC160	0-45	BD180	0-70	BF262	0-45	CG36	0-50	2G417	0-25	2N2711	0-21	2N3404	0-28	2N4290	0-17
AC137	0-14	AF125	0-25	BC161	0-50	BD183	0-65	BF283	0-35	CG41	0-20	2N388	0-25	2N2712	0-21	2N3405	0-42	2N4291	0-17
AC141	0-14	AF126	0-28	BC167	0-12	BD186	0-65	BF270	0-35	CG42	0-24	2N388A	0-55	2N2714	0-21	2N3414	0-15	2N4292	0-17
AC141K	0-14	AF127	0-28	BC168	0-12	BD187	0-70	BF271	0-30	CG44	0-15	2N404	0-20	2N2714	0-21	2N3415	0-15	2N4293	0-17
AC142	0-17	AF139	0-30	BC169	0-12	BD188	0-70	BF272	0-80	CG45	0-12	2N404A	0-28	2N2904A	0-21	2N3416	0-28	2N4294	0-12
AC142K	0-17	AF178	0-50	BC170	0-12	BD189	0-75	BF273	0-35	CG70	0-10	2N524	0-42	2N2905	0-21	2N3417	0-28	2N4295	0-30
AC151	0-15	AF179	0-50	BC171	0-14	BD190	0-75	BF274	0-35	CG71	0-10	2N527	0-49	2N2905A	0-21	2N3425	0-75	2N4296	0-32
AC154	0-20	AF180	0-50	BC172	0-14	BD185	0-85	BFW10	0-60	CG72	0-14	2N598	0-42	2N2906	0-15	2N3648	0-09	2N4459	0-40
AC155	0-20	AF181	0-45	BC173	0-14	BD196	0-85	BFX29	0-27	CG74	0-14	2N599	0-45	2N2906A	0-18	2N3702	0-10	2N4501	0-40
AC156	0-20	AF186	0-45	BC174	0-14	BD197	0-90	BFX84	0-22	CG75	0-15	2N606	0-42	2N2907	0-20	2N3703	0-10	2N4502A	0-50
AC157	0-24	AF239	0-37	BC175	0-22	BD198	0-90	BFX85	0-30	CG76	0-15	2N607	0-18	2N2907A	0-22	2N3704	0-11	2N4503	0-49
AC158	0-20	AL102	0-65	BC177	0-19	BD199	0-95	BFX86	0-22	CG77	0-25	2N608	0-24	2N2907A (O)	0-11	2N3705	0-10	2N4504	0-49
AC159	0-20	AL103	0-65	BC178	0-18	BD200	0-95	BFX87	0-24	CG78	0-15	2N609	0-24	2N2908	0-11	2N3706	0-10	2N4505	0-55
AC160	0-20	AL228	0-65	BC179	0-19	BD205	0-80	BFX88	0-22	CG82D	0-15	2N706	0-08	2N2925	0-14	2N3707	0-11	2N4506	0-84
AC168	0-24	AL227	0-30	BC180	0-24	BD206	0-80	BFY00	0-20	CG82	0-15	2N706A	0-09	2N2926 (G)	0-11	2N3708	0-07	2N4506	0-84
AC169	0-14	AL228	0-25	BC181	0-24	BD207	0-95	BFY51	0-20	CG82D	0-15	2N708	0-12	2N2926	0-12	2N3709	0-09	2N4507	0-84
AC176	0-20	AL229	0-25	BC182	0-10	BD208	0-95	BFY52	0-20	CG83	0-20	2N711	0-08	2N2926 (Y)	0-11	2N3710	0-09	2N4508	0-58
AC177	0-24	AL230	0-25	BC182L	0-10	BDY20	1-00	BFY53	0-17	CG84	0-20	2N717	0-35	2N2926 (O)	0-10	2N3711	0-09	2N4509	0-48
AC178	0-28	AL231	0-25	BC183	0-10	BDY15	0-24	BFY55	0-35	CG85	0-13	2N718	0-24	2N2926 (O)	0-11	2N3712	0-09	2N4510	0-48
AC179	0-28	AL232	0-25	BC183L	0-10	BDY17	0-45	BFY19	0-45	CG86	0-15	2N740	0-20	2N2926 (O)	0-10	2N3713	0-09	2N4511	0-48
AC180	0-17	AL234	0-25	BC184	0-12	BDY18	0-70	BFY20	0-15	CG169	0-25	2N726	0-28	2N2926 (R)	0-11	2N3721	0-35	2N4512	0-70
AC180K	0-17	AL235	0-25	BC184L	0-12	BDY19	0-70	BFY25	0-15	CG170	0-25	2N727	0-28	2N2926 (R)	0-10	2N3722	0-28	2N4513	0-70
AC181	0-17	AL236	0-25	BC186	0-28	BDY21	0-45	BFY26	0-16	CG171	0-25	2N743	0-20	2N2926 (R)	0-10	2N3723	0-28	2N4514	0-70
AC181K	0-17	AL237	0-25	BC187	0-28	BDY22	0-45	BFY27	0-16	CG200	0-25	2N744	0-20	2N2926 (R)	0-10	2N3724	0-30	2N4515	0-70
AC187	0-22	AL238	0-25	BC187	0-11	BDY23	0-45	BFY28	0-16	CG201	0-28	2N814	0-14	2N2926 (R)	0-10	2N3725	0-28	2N4516	0-70
AC187K	0-22	AL239	0-25	BC188	0-11	BDY24	0-45	BFY29	0-16	CG202	0-28	2N818	0-14	2N2926 (R)	0-10	2N3726	0-27	2N4517	0-48
AC188	0-20	AL240	0-09	BC189	0-12	BDY25	0-45	BFY34	0-18	CG203	0-25	2N829	0-21	2N2926 (R)	0-10	2N3727	0-27	2N4518	0-48
AC188K	0-20	AL241	0-09	BC191L	0-11	BDY26	0-45	BFY39	0-18	CG204	0-25	2N830	0-21	2N2926 (R)	0-10	2N3728	0-27	2N4519	0-48
AC17	0-25	AL242	0-10	BC191L	0-11	BDY27	0-45	BFY40	0-18	CG205	0-35	2N131	0-20	2N2926 (R)	0-10	2N3729	0-27	2N4520	0-48
AC18	0-20	AL243	0-10	BC191L	0-14	BDY28	0-45	BFY41	0-18	CG209	0-40	2N132	0-22	2N2926 (R)	0-10	2N3730	0-27	2N4521	0-48
AC19	0-20	AL244	0-15	BC192	0-25	BDY29	0-48	BFY45	0-12	P346A	0-20	2N1302	0-14	2N2926 (R)	0-10	2N3731	0-27	2N4522	0-48
AC20	0-20	AL245	0-15	BC193	0-35	BDY30	0-55	BFY50A	0-12	P397	0-42	2N1303	0-14	AA119	0-08	BY133	0-21	OA10	0-85
AC21	0-20	AL246	0-15	BC194	0-24	BDY31	0-55	BFY50	0-12	CG71	0-42	2N1304	0-17	AA120	0-08	BY164	0-50	OA47	0-07
AC22	0-16	AL247	0-15	BC195	0-28	BDY32	0-60	BFY59	0-60	CG71	0-42	2N1305	0-17	AA129	0-08	BYX38/30		OA70	0-07
AC27	0-18	AL248	0-10	BC196	0-30	BDY33	0-60	BFY60	0-40	CG71	0-42	2N1306	0-21	AA130	0-09		0-42	OA79	0-07
AC28	0-19	AL249	0-10	BC197	0-30	BDY34	0-60	BFY61	0-40	CG71	0-42	2N1307	0-21	AA131	0-10	BY210	0-35	OA81	0-07
AC29	0-25	AL250	0-10	BC198	0-30	BDY35	0-60	BFY62	0-40	CG71	0-42	2N1308	0-23	AA132	0-10	BY211	0-30	OA85	0-09
AC30	0-35	AL251	0-12	BC199	0-14	BDY36	0-40	BFY63	0-40	CG71	0-42	2N1309	0-23	AA133	0-10	BY212	0-30	OA90	0-06
AC31	0-28	AL252	0-18	BC200	0-18	BDY37	0-40	BFY64	0-40	CG71	0-42	2N1310	0-23	AA134	0-10	BY213	0-30	OA91	0-06
AC32	0-22	AL253	0-18	BC201	0-18	BDY38	0-40	BFY65	0-40	CG71	0-42	2N1311	0-23	AA135	0-10	BY214	0-30	OA92	0-06
AC33	0-22	AL254	0-18	BC202	0-18	BDY39	0-40	BFY66	0-40	CG71	0-42	2N1312	0-23	AA136	0-10	BY215	0-30	OA93	0-06
AC34	0-21	AL255	0-18	BC203	0-18	BDY40	0-40	BFY67	0-40	CG71	0-42	2N1313	0-23	AA137	0-10	BY216	0-30	OA94	0-06
AC35	0-21	AL256	0-18	BC204	0-18	BDY41	0-40	BFY68	0-40	CG71	0-42	2N1314	0-23	AA138	0-10	BY217	0-30	OA95	0-06
AC36	0-28	AL257	0-12	BC205	0-25	BDY42	0-40	BFY69	0-40	CG71	0-42	2N1315	0-23	AA139	0-10	BY218	0-30	OA96	0-06
AC37	0-18	AL258	0-15	BC206	0-25	BDY43	0-40	BFY70	0-40	CG71	0-42	2N1316	0-23	AA140	0-10	BY219	0-30	OA97	0-06
AC38	0-18	AL259	0-15	BC207	0-25	BDY44	0-40	BFY71	0-40	CG71	0-42	2N1317	0-23	AA141	0-10	BY220	0-30	OA98	0-06
AC39	0-18	AL260	0-15	BC208	0-25	BDY45	0-40	BFY72	0-40	CG71	0-42	2N1318	0-23	AA142	0-10	BY221	0-30	OA99	0-06
AC40	0-18	AL261	0-15	BC209	0-25	BDY46	0-40	BFY73	0-40	CG71	0-42	2N1319	0-23	AA143	0-10	BY222	0-30	OA100	0-06
AC41	0-18	AL262	0-15	BC210	0-25	BDY47	0-40	BFY74	0-40	CG71	0-42	2N1320	0-23	AA144	0-10	BY223	0-30	OA101	0-06
AC42	0-18	AL263	0-15	BC211	0-25	BDY48	0-40	BFY75	0-40	CG71	0-42	2N1321	0-23	AA145	0-10	BY224	0-30	OA102	0-06
AC43	0-18	AL264	0-15	BC212	0-25	BDY49	0-40	BFY76	0-40	CG71	0-42	2N1322	0-23	AA146	0-10	BY225	0-30	OA103	0-06
AC44	0-18	AL265	0-15	BC213	0-25	BDY50	0-40	BFY77	0-40	CG71	0-42	2N1323	0-23	AA147	0-10	BY226	0-30	OA104	0-06
AD130	0-38	AL266	0-30	BC214	0-30	BDY51	0-40	BFY78	0-40	CG71	0-42	2N1324	0-23	AA148	0-10	BY227	0-30	OA105	0-06
AD140	0-48	AL267	0-30	BC215	0-30	BDY52	0-40	BFY79	0-40	CG71	0-42	2N							

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV 1A	3A	5A	5A	7A	10A	16A	30A
T05	T06G	T06H	T06J	T048	T048	T049	T048
50-0.25	0.25-0.35	0.35-0.47	0.47-0.50	0.50-0.53	0.53-1.15		
100-0.25	0.33-0.47	0.47-0.50	0.50-0.58	0.63-1.40			
200-0.30	0.37-0.49	0.49-0.57	0.57-1.75	1.60			
400-0.43	0.47-0.56	0.56-0.67	0.67-0.93	1.75			
600-0.53	0.57-0.68	0.68-0.77	0.77-1.25				
800-0.63	0.70-0.80	0.80-0.90	1.20-1.60	4.00			

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50-0.04	0.05	0.05-0.07	0.14	0.21	0.60		
100-0.04	0.06	0.06-0.13	0.18	0.23	0.75		
200-0.03	0.09	0.09-0.14	0.20	0.24	1.00		
400-0.06	0.13	0.07-0.20	0.27	0.37	1.25		
600-0.07	0.16	0.10-0.20	0.34	0.45	1.86		
800-0.10	0.17	0.11-0.23	0.37	0.55	2.00		
1000-0.11	0.25	0.14-0.30	0.46	0.63	2.50		
1200	—	0.33	—	0.38-0.57	0.75		

TRIACS

V FROM	2A	6A	10A
TO-1 TO-6	TO-8		
2p	5p	5p	
100	30	50	76
200	50	60	90
400	70	75	1-10

DIACS

FOR USE WITH TRIACS
BR100 (D32) 37p each.

FREE

One 50p Pak of your own choice free with orders valued £4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed	
Pak No.	EQVT
T1	8 263731 0171
T2	8 181374 0C75
T3	8 121216 0C81D
T4	8 26381T 0C81
T5	8 26382T 0C82
T6	8 26344B 0C44
T7	8 26345B 0C45
T8	8 26378 0C78
T9	8 26399A 2N1302
T10	8 26417 AF117

All 50p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. 0.1 price 25p each.

120 VCB MIXIE DRIVER TRANSISTOR. 81m. BR211 & C407. 2N1893 FULLY TESTED IN CODED ND 120. 1-24 25p up 15p each.

SIL. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. 27N200 6p each. Any Qty.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE. - OC29-28-29-30-35-36. NKT 401-403-404-405-408-130-401-452-453. T10027-3028. 2N250A. 2N456A-457A-458A. 2N511 & H. 2N220-222. ETC. VCB 80V VCEO 50V IC 10A PT. 30 WATTS life 30-170.

PRICE	1-24	25-99	100 up
	43p each	40p each	36p each

AD161/162 PNP M/P COMP GERM TRANS. OUR LOWEST PRICE OF 55p PER PAIR

FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-33V 400mV (D0-7) Cases 13p ea 11W (Top Hat) 18p ea. 10W (SO-10 Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 90p each

NEW LINE Plastic Encapsulated 2 Amp. BRIDGE RECTS. 50 v RMS 32p each 100 v RMS 37p .. 400 v RMS 48p .. Size 15 mm x 6 mm.

UNIDIRECTIONAL UT46. 18V. 2N2646. 12V. ET43. 2N3046. 207p each. 25-99 25p 100 PIP 20p.

CADMIUM CELLS ORP12 43p ORP60, ORP61 40p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM TO 2N708/8. 25-17/28/85A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N906, BCY70. When ordering, please state preference NPN or PNP.

	20	For	50p
	50	For	1.00
	100	For	1.75
	500	For	7.50
	1000	For	13.00

SIL. G.P. DIODES 4p 300mA 30 0.50 40PIV(Min.) 100 1.50 Sub-Min. 500 6.00 Full Tested 1,000 9.00 Ideal for Organ Builders.

2N3055 115 WATT SIL POWER NPN 50p EACH

SILICON 50 WATTS MATCHED NPN/PPN BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCEO 100V/VCEO 50V IC 10A. HFE type 100ft 3miHz. OUR PRICE PER PAIR: 1-24 pre. 60p 25-99 pre. 55p 100 pre. 50p

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.50
U 2	60 Mica Germanium Transistors AF/RF	0.50
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.50
U 4	40 Germanium Transistor like OC81, ACU8	0.50
U 5	60 200mA Sub-Min. Silicon Diodes	0.50
U 6	30 Sil. Planar Trans. NPN like B8795A, 2N706	0.50
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000 0.50	
U 8	50 Sil. Planar Diodes DO-7 Class 250mA like OA200/202	0.50
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.50
U 10	20 BA750 charge storage Diodes DO-7 Class	0.50
U 11	25 PNP Sil. Planar Trans. TO-5 like 2N1192, 2N2904	0.50
U 12	12 Silicon Rectifiers Epoxy 300mA up to 800 PIV	0.50
U 13	30 PNP-NPN Sil. Transistors OC260 & 2S 104	0.50
U 14	150 Mixed Silicon and Germanium Diodes	0.50
U 15	25 NPN Sil. Planar Trans. TO-5 like BFY61, 2N697	0.50
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000 PIV	0.50
U 17	30 Germanium PNP AF Transistors TO-6 like ACY 17-22	0.50
U 18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.50
U 19	25 Silicon NPN Transistors like BC108	0.50
U 20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.50
U 21	30 AF. Germanium Alloy Transistors 26300 Series & OC71	0.50
U 22	30 MADT's like Mix Series PNP Transistors	0.50
U 23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.50
U 24	25 300 MHz NPN Silicon Transistors 2N708, B8Y27	0.50
U 25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.50
U 26	12 NPN Germanium AF Transistors TO-1 like AC127	0.50
U 29	10 1 Amp SCR's TO-6 can. up to 600 PIV CR81/25-000	1.00
U 30	15 Plastic Silicon Planar Trans. NPN 2N2926	0.50
U 31	20 Silicon Planar Plastic PNP Trans. Low Noise Amp 2N3707	0.50
U 32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.50
U 33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.50
U 34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0.50
U 35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.50
U 36	25 Silicon Planar NPN Transistors TO-5 BFY60/51/52	0.50
U 37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0.50
U 38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.50
U 39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0.50
U 40	10 Dual Transistors 5 lead TO-5 2N2060	0.50
U 41	25 RF Germanium Transistors TO-6, OC45, NKT72	0.50
U 42	10 VHF Germanium PNP Transistors TO-1 NKT667, AP117	0.50
U 43	25 Sil. Trans. Plastic TO-18 A-E. BC113/114	0.50
U 44	20 Sil. Trans. Plastic TO-5 BC116/NPN	0.50
U 45	7 3A SCR. TO66 up to 600PIV	1.00

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP-25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 35p

F.E.T.'S 2N3819 35p 2N5458 50p 2N3820 50p 2N5459 40p 2N3821 35p BF-W10 40p 2N3823 30p MPF105 40p

NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	-12 x 7400	0.50	UIC46	-5 x 7446	0.50	UIC86	-5 x 7486	0.50
UIC01	-12 x 7401	0.50	UIC47	-5 x 7447	0.50	UIC90	-5 x 7490	0.50
UIC02	-12 x 7402	0.50	UIC48	-5 x 7448	0.50	UIC91	-5 x 7491	0.50
UIC03	-12 x 7403	0.50	UIC50	-12 x 7450	0.50	UIC92	-5 x 7492	0.50
UIC04	-12 x 7404	0.50	UIC51	-12 x 7451	0.50	UIC93	-5 x 7493	0.50
UIC05	-12 x 7405	0.50	UIC53	-12 x 7453	0.50	UIC94	-5 x 7494	0.50
UIC06	-8 x 7406	0.50	UIC54	-12 x 7454	0.50	UIC95	-5 x 7495	0.50
UIC07	-8 x 7407	0.50	UIC60	-12 x 7460	0.50	UIC96	-5 x 7496	0.50
UIC10	-12 x 7410	0.50	UIC70	-8 x 7470	0.50	UIC100	-5 x 74100	0.50
UIC13	-8 x 7413	0.50	UIC72	-8 x 7472	0.50	UIC121	-5 x 74121	0.50
UIC20	-12 x 7420	0.50	UIC73	-8 x 7473	0.50	UIC141	-5 x 74141	0.50
UIC30	-12 x 7430	0.50	UIC74	-8 x 7474	0.50	UIC151	-5 x 74151	0.50
UIC40	-12 x 7440	0.50	UIC75	-8 x 7475	0.50	UIC154	-5 x 74154	0.50
UIC41	-5 x 7441	0.50	UIC76	-8 x 7476	0.50	UIC193	-5 x 74193	0.50
UIC42	-5 x 7442	0.50	UIC80	-5 x 7480	0.50	UIC199	-5 x 74199	0.50
UIC43	-5 x 7443	0.50	UIC81	-5 x 7481	0.50			
UIC44	-5 x 7444	0.50	UIC82	-5 x 7482	0.50			
UIC45	-5 x 7445	0.50	UIC83	-5 x 7483	0.50			

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC XI. 74's 1-50

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES—18 BALDOCK STREET (A10), WARE, HERTS. TEL. (STD 0920) 61593. OPEN MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY UNTIL 8 p.m.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q1	20 Red spot transistors PNP	0.50
Q2	16 White spot R.F. transistors PNP	0.60
Q3	4 OC 77 type transistors	0.50
Q4	6 Matched transistors OC44/45/81/81D	0.50
Q5	4 OC 75 transistors	0.60
Q6	5 OC 72 transistors PNP high gain	0.50
Q7	4 AC 128 transistors PNP	0.50
Q8	4 AC 126 transistors PNP	0.50
Q9	7 OC 81 type transistors	0.60
Q10	7 OC 71 type transistors	0.50
Q11	2 AC 127/128 Complementary pairs PNP/PNP	0.60
Q12	3 AF 116 type transistors	0.50
Q13	3 AF 117 type transistors	0.50
Q14	3 OC 171 H.F. type transistors	0.50
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0.50
Q16	2 GBT890 low noise Germanium transistors	0.50
Q17	5 NPN 2 x ST transistors	0.50
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0.50
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0.50
Q20	4 OC 34 Germanium transistors A.F.	0.60
Q21	4 AC 127 NPN Germanium transistors	0.50
Q22	20 NKT transistors A.F. R.F. coded	0.50
Q23	10 OA 202 Silicon diodes sub-min.	0.50
Q24	8 OA 81 diodes	0.50
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0.50
Q26	8 OA95 Germanium diodes sub-min IN69	0.50
Q27	2 10A PIV Silicon rectifiers 18425R	0.50
Q28	2 Silicon power rectifiers BYZ 13	0.50
Q29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.50
Q30	7 Silicon switch transistors 2N706 NPN	0.50
Q31	6 Silicon switch transistors 2N708 NPN	0.50
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0.60
Q33	3 Silicon NPN transistors 2N1711	0.50
Q34	7 Silicon NPN transistors 2N2369, 500MHz (code P397)	0.50
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0.50
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0.50
Q37	300MHz NPN Silicon transistors	0.60
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0.50

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L, C and f of Tuned Circuits. Reactance and Self Inductance. Area of Circle. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Log and e Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2 cm x 4cm. Complete with case and instructions. Price each: £3-35

-the lowest prices!

74 Series T.T.L. I.C's



BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

1			25			100+					
Type No.	Price	100 up	Type No.	Price	100 up	Type No.	Price	100 up			
SN7400	0-15	0-14	0-12	SN7450	0-15	0-14	0-12	SN74123	£2-80	£2-70	£2-60
SN7401	0-15	0-14	0-12	SN7451	0-15	0-14	0-12	SN74141	0-67	0-64	0-58
SN7402	0-15	0-14	0-12	SN7453	0-15	0-14	0-12	SN74145	£1-50	£1-40	£1-30
SN7403	0-15	0-14	0-12	SN7454	0-15	0-14	0-12	SN74150	£2-00	£2-70	£2-50
SN7404	0-15	0-14	0-12	SN7460	0-15	0-14	0-12	SN74151	£1-00	0-95	0-90
SN7405	0-15	0-14	0-12	SN7470	0-29	0-28	0-24	SN74155	£1-20	£1-10	0-95
SN7406	0-35	0-31	0-28	SN7472	0-29	0-28	0-24	SN74154	£1-60	£1-70	£1-60
SN7407	0-35	0-31	0-28	SN7473	0-37	0-35	0-32	SN74153	£1-40	£1-30	£1-20
SN7408	0-18	0-17	0-16	SN7474	0-37	0-35	0-32	SN74156	£1-40	£1-30	£1-20
SN7409	0-18	0-17	0-16	SN7475	0-45	0-43	0-42	SN74157	£1-80	£1-80	£1-70
SN7410	0-15	0-14	0-12	SN7476	0-40	0-39	0-38	SN74159	£1-60	£1-70	£1-60
SN7411	0-25	0-24	0-23	SN7480	0-67	0-64	0-53	SN74161	£1-80	£1-70	£1-60
SN7412	0-35	0-31	0-28	SN7481	£1-20	£1-15	£1-10	SN74162	£2-00	£3-75	£3-50
SN7413	0-29	0-28	0-24	SN7482	0-87	0-86	0-85	SN74163	£2-00	£3-75	£3-50
SN7416	0-43	0-40	0-38	SN7483	£1-10	£1-05	0-95	SN74164	£2-20	£2-15	£2-10
SN7417	0-43	0-40	0-38	SN7484	£1-00	0-95	0-90	SN74165	£2-25	£2-20	£2-15
SN7420	0-15	0-14	0-12	SN7485	£3-60	£3-50	£3-40	SN74166	£3-50	£3-25	£3-10
SN7422	0-50	0-48	0-45	SN7486	0-32	0-31	0-30	SN74174	£2-30	£2-20	£2-10
SN7423	0-60	0-48	0-45	SN7489	£5-50	£5-25	£5-00	SN74175	£2-60	£1-50	£1-40
SN7425	0-50	0-48	0-45	SN7490	0-87	0-84	0-83	SN74176	£2-50	£2-40	£2-30
SN7427	0-48	0-45	0-43	SN7491	£1-00	0-95	0-90	SN74177	£2-50	£2-40	£2-30
SN7428	0-70	0-65	0-60	SN7492	0-87	0-84	0-83	SN74180	£2-00	£1-80	£1-40
SN7430	0-16	0-14	0-12	SN7493	0-87	0-84	0-83	SN74181	£2-50	£2-00	£2-75
SN7432	0-46	0-42	0-40	SN7494	0-77	0-74	0-68	SN74182	£2-00	£1-80	£1-80
SN7433	0-80	0-76	0-70	SN7495	0-77	0-74	0-68	SN74184	£2-60	£3-25	£3-00
SN7437	0-84	0-82	0-80	SN7496	0-87	0-84	0-78	SN74190	£1-85	£1-80	£1-85
SN7438	0-84	0-82	0-80	SN7497	£1-55	£1-50	£1-45	SN74191	£1-90	£1-85	£1-80
SN7440	0-15	0-14	0-12	SN74104	0-97	0-94	0-88	SN74192	£1-95	£1-90	£1-85
SN7441	0-67	0-64	0-63	SN74105	0-97	0-94	0-88	SN74193	£2-00	£1-80	£1-75
SN7442	0-87	0-84	0-83	SN74107	0-40	0-38	0-36	SN74194	£2-70	£2-60	£2-50
SN7443	£1-30	£1-26	£1-20	SN74110	0-55	0-53	0-50	SN74195	£2-20	£1-90	£1-80
SN7444	£1-30	£1-26	£1-20	SN74111	£1-26	£1-16	£1-10	SN74196	£1-80	£1-70	£1-60
SN7446	£1-80	£1-77	£1-76	SN74118	£1-00	0-95	0-90	SN74197	£1-80	£1-70	£1-60
SN7448	0-97	0-94	0-88	SN74119	£1-35	£1-26	£1-10	SN74198	£2-50	£2-00	£2-50
SN7447	£1-00	0-97	0-95	SN74121	0-40	0-37	0-34	SN74199	£2-50	£2-00	£2-00
SN7448	£1-00	0-97	0-95	SN74122	£1-40	£1-30	£1-10	SN74199	£2-50	£2-00	£2-00

LINEAR I.C.'s—FULL SPEC.

Type No.	1-24	25-99	100 up
BP 201C—RL2010	85p	85p	45p
BP 701C—RL701C	85p	80p	45p
BP 702C—RL702C	85p	80p	45p
BP 703—73702	85p	45p	40p
BP 704—73703	85p	34p	30p
BP 707P—AA709C	85p	84p	80p
BP 710—73710	44p	48p	40p
BP 711—AA711	45p	48p	40p
BP 741—73741	75p	60p	50p
AA705C—AA705C	85p	85p	85p
TAA 298—	70p	60p	50p
TAA 303—	90p	75p	70p
TAA 308—	170p	155p	150p

R.G.R. EA1000 8-68


ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type No.	1-24	25-99	100 up
RP930	12p	11p	10p
RP932	18p	18p	11p
RP933	13p	13p	11p
RP935	13p	13p	11p
RP936	18p	18p	11p
RP944	13p	13p	11p
RP945	25p	24p	22p
RP946	12p	11p	10p
RP948	22p	24p	22p
RP951	65p	60p	55p
RP962	12p	11p	10p
RP9903	40p	38p	35p
RP9904	40p	38p	35p
RP9907	40p	38p	35p
RP9909	40p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (D.T.L. 930 Series only).

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

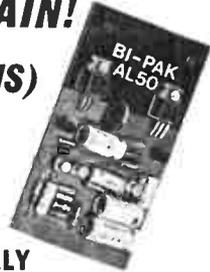


0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

THE AL50

- ★ Frequency Response 15Hz to 100,000—1dB.
 - ★ Load—3, 4, 8 or 16 ohms.
 - ★ Distortion—better than 1% at 1KHz.
 - ★ Signal to noise ratio 80dB.
- ONLY £3.25p each**
- ★ Supply voltage 10-35 Volts.
 - ★ Overall size 63mm x 105mm x 13mm.

Tallor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.

STABILISED POWER MODULE SPM80

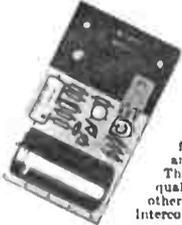

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 16 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.6 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:- Disc Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £2-95**

TRANSFORMER BMT80 £1-95 p. & p. 25p.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market. The PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz - 20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs : 1. Tape Head	1-25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1.8 mV into 50K Ω
All input voltages are for an output of 280mV. Tape and P.U. input equalised to RIAA curve within ± 1dB, from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters : Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than - 65dB
Input overload	+ 24dB
Supply	+ 35 volts at 20mA
Dimensions	282mm x 82mm x 35mm

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23-00 FREE p. & p.

All prices quoted in new pence Giro No 388 7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail.
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015P Minitron
Anode voltage (Vdc)	170min	175min	8
Cathode Current (mA)	2-3	14	5
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Req.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1-70	£1-55	£1-90

All indicators 0-9 + Decimal point. All side viewing. Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

	Price each
Epoxy TO-5 case	1-24 25-99 100 up
uL900 Buffer	35p 33p 27p
uL914 Dual 2/p gate	35p 33p 27p
uL923 J-K flip-flop	50p 47p 45p

DUAL IN LINE SOCKETS.

14 & 16 Lead Sockets for use with

DUAL-IN-LINE I.C.'s. TWO Ranges PROFESSIONAL & NEW LOW COST. PROF. TYPE No.	1-24 25-99 100up.
TSO 14 pin type	30p 27p 25p
TSO 16 " " "	35p 32p 30p

LOW COST No.

BPS 14	15p	13p	11p
BPS 16	16p	14p	12p

SURPLUS BARGAINS

INDICATOR C.R.T. 8129 contains tube 3-5" green med persistence, 21 min valves, complete in case size 10 x 10" front 20" deep, this unit contains internal E.H.T. and heater trans for 230v mains, reqs ext 300v DC H.T. Modern well made unit well suited to scope conversion. Good condition. £9.75.

CONTROL UNIT CAMERA. Contains meter 2 1/2" dia FSD 1 Ma special scale markings, 3 x toggle swts, 2 x Ind lamps, push swt etc. supplied in fitted wooden transit case. New condition. £1.85.

NAVY Rx type B40 range 640 Kc to 30 Mc/s in 5 bands have int mains P.U. and Spk. xtal cal etc. Supplied tested with circ. Few only £27.00.

SELECTOR UNIT Contains meter 1 Ma scale 0 to 1 and 0 to 180, motor 24v DC with gears, this drives multiway swt also 13 relays, swts, etc. All in useful case size 12 x 6 x 7" £2.60.

IND UNIT CRT 26 small ind with tube 2.75" with PDA green screen med persis. O.K. for scope use, 7 min valves. All in case size 8 x 8" front 13" deep. Tube connections supplied. £4.10.

Ae COUPLING UNITS. Cover range 2 to 5.7 Mc/s intended to match 80 ohm O/P to long wire, contain 2 R.F. ameters, 2 variable inductors with counting dials in plywood cases with circ. £3.00.

METERS 50 Ua FSD scale 0 to 3, 30 or 300 sq case 3 x 2 1/2" £1.35. Also 500 Ua scale 0 to 5 size 2 1/2" OSD £1.10. Also on panel 500 Ua scale 0 to 5 size 1 1/2" OSD on panel with swt £1.

INST SWTS 2 pole 23 way 2 bank 70p. **CONDS.** 1 of 1% 2 for 60p. **POT CORES** 1 1/2" 2 for 60p. **FUSE HOLDERS** miniature type 3 for 30p. **HEAT SINKS** size 11 x 9 x 1 1/2" ready drilled for 4 T.O.3 types with 4 1 ohm res £1.00. **IND 208.** This is a repeater ind with tube 2.75" dia, green med persis with base shield and front plate base conn and volts req. supplied with scan burns £1.55. **TEST UNIT** contains 2 vinkors, 4 Sil transis 15v zener, 4 miniature relays, 3 min valves pots conds. etc. New condition 85p. **BLOWER MOTORS** double ended type 24v DC new £1.60. **SPEAKER UNITS P.A.** type speaker 8 ohm in case size 9 x 9 x 8" with 600 ohm line trans suitable outdoor use. Good condition. £2.75. **BATTERIES** 6 volt lead acid type metal cased 40 amp/hr, size 10 x 9 x 5". New with filling inst. £2.75 **DYNAMOTOR UNITS** 12v DC in 220v 100 Ma DC O/P fully enclosed for TCS Rx £1.50. also 12v in 440v 200 Ma O/P £2.00. **DIODES 800 P.I.V.** 1 amp. New 12 for £1.00. **DIODES 200 P.I.V.** 8 amps ZR22 type 4 for 60p. **TRIMMERS** 20pf air spaced ceramic. New 10 for 50p or £4.00 per 100. Also 10/110 pf ceramic dielectric 5 for 50p. **METER UNIT** part of nav display centering type scale L & R as two coils on magnet enables reading to be controlled from two circs. New condition with circ. 95p. Also available cross pointer ind part of R1155 Rx as two movements of 115 Ua ea. £1.40. **TAG STRIPS** solder type 24 way new 10 for 25p. **VIDICONS** camera tubes E.E. and E.M.I. types graded according to scan marks £9.00 grade A. £6.00 grade B. **JOY STICK CONTROLLERS** give control in N, S, E and W directions with 1 pole c/o micro swts. £1.20 **TRANSFORMERS.** All 230 50 c/s Pria as follows: Sec 1125-O-1125V at 565 Ma. New boxed £7.00. Sec 415-143-0-143-415 at 360 Ma on 415v and 120 Ma on 143v. New boxed £3.00. Sec 350-310-0-310-350 at 220 Ma, 5v 6a, 6.3 5a, 6.3 3a twice and 6.3 la twice £2.65. Also Pria 210/250 Sec 27v at 41 amps cont new £11.00 **VALVES 5U4, 6X5, 6X4, 12AT7, 85A2, OB2, 12AX7, 6BH6, 6AK5, 6AK6, 6SN7, 6SK7, 6SJ7, 6H6, 12AU7, 6BA6, 6AS6, any 3 for 50p.**

CIRCUIT DIAGRAMS. R1155, B, F, L, N with values 50p. R1392, R1475 30p. CT38 50p. Scopes CD 518 (CT316), 13a, 1035 Mk. 1, 2, 3, 1049 Mk 3 all 50p. Rx B40 50p. Rx STC R4187 set of circs and parts list £1.00. Sig gens TF144G with values 50p. TF801a with values 75p

All goods ex equipment unless stated otherwise. The above prices include carriage or postage for U.K. mainland. S.A.E. with enquiry.


A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9 5HL

PRINTED CIRCUIT KIT

BUILD 60 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARE BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/2in x 2 1/2in. (2) 1 Board for Match-box Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit: (10) Essential Design Data, Circuits, Chassis Plans, etc. for 60 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements.

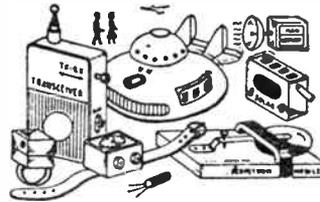

EXPERIMENTER'S
PRINTED CIRCUIT KIT
70p

Postage & Pack. 10p (UK)
Commonwealth:
SURFACE MAIL 15p
AIR MAIL 60p
Australia, New Zealand,
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photo-cell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. (10) 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62in x 0.95in x 0.25in. (11) Wristwatch Radio 1.15in x 0.80in x 0.35in. (12) Ring Radio 0.70in x 0.70in x 0.35in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Molels by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wire-less Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Phonophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller. (41) Light Dimmer. (42) I.C. Pre-amplifier. (43) I.C. Amplifier. (44) I.C. Intercom. (45) I.C. Radio. (46) Raulive Voices Receiver. (47) Biofeedback Amplifier. (48) Brainwave Detector. (49) Proximity Switch. (50) Laser Projector. Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector, etc.

YORK ELECTRICS, Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details and a brief description of all kits and Projects.

Lasky's Audio-Tronics Catalogue 1973

The great 1973 edition of Lasky's famous Audio-Tronics catalogue is available - FREE on request. The 48 newspaper size pages - many in full colour - are packed with 1,000s of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape recording and Audio Accessories. See the great new Lasky's Credit Plan Scheme - enabling you to buy your ideal choice of equipment on easy terms.

FREE

Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME

ADDRESS

.....

.....


PW2

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.



"Where can I get exclusive units at lowest prices?..."

ROC ELECTRONICS!

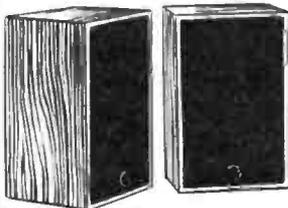

R.088 MATCHED STEREO LOUD SPEAKERS. Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-18,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. Finish: oiled walnut.
ROC PRICE £9.50 pair.
Normal Price £10.75

REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted - for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push button input controls - magnetic phono (high low), tuner, aux. mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz. -1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA, tuner aux 250mV. Hum and noise: phono - 50db, tuner aux - 65db. How's that for a specification! Size 14 1/2" wide, 3 1/2" high, 10 1/2" deep.



As reviewed in "POPULAR HI-FI" February 1972

ROC PRICE £35.20
Normal Price £55.50



OLSON RA-310 AM FM MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as it is a good looking design! But of course it's also the RA-310 costs £10.00 less than the normal retail value and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands: FM 87-108 MHz, AM 525-1605 kHz. FM Sensitivity: FM 3µV, AM 250µV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size: 11 1/2" wide, 4" high, 7 1/2" deep.

ROC PRICE £31.20
Normal Price £50.00



REALISTIC SA-100B 6-WATT STEREO AMPLIFIER

Here's a fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide, 3" high, 5 1/2" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in, out, mono/stereo, phono/tuner and power on/off slide switches. The ends are oiled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz. -3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.


ROC PRICE £12.45
Normal Price £21.00



TEC HR-007 HEADPHONE RADIO
When you want to listen to the radio all by yourself. Then this will solve the problem. Separate volume and tuning controls with easy to use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW.
Normal Price £17.50 **ROC PRICE £5.80**

EAGLE LC 07 STEREO MOVING-MAGNET CARTRIDGE

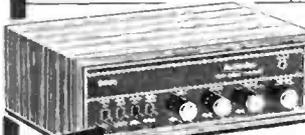Here's your opportunity to own a transcription cartridge for the price of a ceramic! It's specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output, 7mV per channel. Frequency range 20-21,000 Hz. Channel balance -1dB. Channel separation 28dB. Compliance 12-10.6 cm/dyne.
ROC PRICE £6.37



OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz. -3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 30mV RIAA, crystal phono 100mV, tape 160mV, tuner 160mV. Size 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well - sounds even better!

ROC PRICE £24.10
Normal Price £39.60



A-3000 36-WATT SOLID STATE STEREO AMPLIFIER

The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front - all the controls you're ever likely to need plus a headphone socket. On the rear - signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (-2db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux, Tape Play, Size: 345mm x 300mm x 130mm.

ROC PRICE £28.00
Normal Price £35.70



OLSON AM-400 4 WATT STEREO AMPLIFIER

Here's a marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for tuntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz. -3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV, tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.


ROC PRICE £10.50
Normal Price £15.70

25-WATT 3-WAY CRYSLER 'LIVING AUDIO' SPEAKER CE-50

This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units an 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2" x 7 1/2" x 8 1/2". Exactly right for matching the most modern decor.



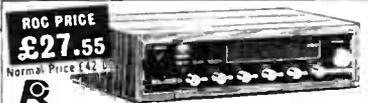ROC PRICE £27.25
Normal Price £39.95 each.



PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-16

This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received - that's the time to switch to 'Stereo'! The SSA-16 has all the facilities you'd expect to find on tuners costing twice as much - separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz, AM 535-1605 kHz. Frequency response: 50-10,000 Hz. -3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.

ROC PRICE £27.55
Normal Price £42.00

CONSTRUCTORS KITS

TWO TRANSISTOR RADIO KIT
Complete with solar cell
£2.50


10 PROJECT INTEGRATED CIRCUIT KIT
Build a radio, morse key etc.
£3.50

SOLAR ELECTRONIC KIT
20 ways of harnessing the sun's energy
£4.50

TWO OCTAVE ELECTRONIC ORGAN KIT
Make your own music. Complete with speaker.
£4.50

ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317

This exclusive ROC Stereo Chassis is completely self-contained and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 1 1/2" high and 6 1/2" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz. -3dB, output 3.5 watts music power per channel into 8 ohms, input, phono, 600mV; signal-to-noise ratio better than 45dB.

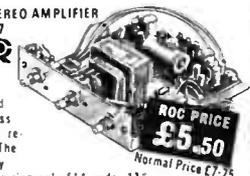


ROC PRICE £5.50
Normal Price £7.75



R.446 3-WAY MATCHED SPEAKERS
These will do justice to your amplifier - and to your pocket! At only £20.00 a pair, they are real value for money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a 6" base unit plus tweeter. Frequency range 40 to 19,000 Hz. Size 14" high, 9" wide, 6 1/2" deep.

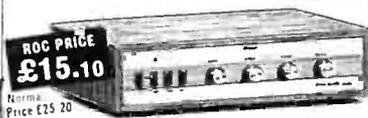ROC PRICE £20.00
Normal Price £27.00 per pair



OLSON AM-372 16-WATT STEREO AMPLIFIER

Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz. -3dB. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

ROC PRICE £15.10
Normal Price £25.20

ROC ELECTRONICS LTD

M. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211
CALLERS WELCOME 9-6 MON. TO SAT.
ALSO AT 87 TOTTENHAM COURT RD, LONDON W1
TEL: 01-580 3739 OPEN 9-6 MON.-FRI. SAT. 9-1



Return-of-post mail order service from Edgware Rd. Orders over £10 post free (UK only). Add 25p for p. & p. for orders under £10. HP terms available for callers.


BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
THE VALVE SPECIALISTS Telephone 6743

0A2	.30	6HJ6	.39	6N7GT	.40	128J7	.23	50L6GT	.45	EABCB0	.29	EF88	.25	KT44	1.00	PL83	.30	UL41	.54	AC128	.20	BCU18	.23	OA70	.15
0B2	.30	6BQ7A	.28	6Q7GT	.43	128K7	.24	85A2	.43	EAC91	.38	EL34	1.00	PC88	.44	PY80	.33	U26	.52	AC132	.20	BCY10	.45	OA73	.15
0Z4	.25	6BR7	.79	6Q7(M)	.43	128Q7	.50	85A3	.40	EAF42	.48	EL37	.74	PC95	.53	PY81	.24	U191	.56	AC165	.25	BCY38	.23	OA90	.18
1A3	.23	6BR8	.63	6R7A	.35	14H7	.48	90C1	.59	EAF90	.50	EL41	.53	PC97	.38	PY82	.20	U211	.68	AC166	.25	BCY39	.26	OA91	.08
1A7GT	.32	6BR7	1.25	6R7M	.55	14H7	.75	90C4	1.70	EA34	.20	EL41	.50	PC90	.29	PY83	.24	U301	.48	AC170	.18	BCZ11	.38	OA92	.38
1B3GT	.35	6BW6	.72	6RA7M	.35	19AQ5	.54	160B2	.58	EB91	.10	EL83	.30	PC84	.27	PY88	.31	U403	.33	AC168	.38	BCZ11	.38	OA95	.09
1H5GT	.33	6BW7	.50	6SC7GT	.33	19G6	.50	807	.59	EB41	.48	EL84	.21	PC85	.24	PY60	.95	U404	.38	AC172	.15	BF158	.29	OA200	.09
1L4	.13	6BZ6	.31	6G67	.33	20D4	1.05	5702	.80	EBU81	.29	EL85	.40	PC88	.39	PY80	.31	U801	.76	AC172	.18	BF159	.25	OA202	.10
1N5GT	.37	6B86A	.28	6H17	.53	20P2	.85	5763	.50	EBF90	.30	EL86	.38	PC89	.42	PY81	.31	U4020	.38	AD140	.38	BFY51	.19	OC22	.38
1H5	.28	6C4	.28	6H7	.35	20L1	.98	7475	.70	EBF83	.38	EL91	.32	PC89	.46	PZ30	.48	V23	.40	AD149	.50	BFY52	.20	OC44	.10
1H4	.22	6C9	.73	6K7GT	.23	20P1	.50	ACJPEN	.98	EBF89	.28	EL95	.22	PCF80	.28	QV03/10	V411	.38	AD181	.45	BF106	.18	OC45	.11	
1U4	.29	6C6G	1.08	6R7GT	.38	20P3	.76	ACJ/PEN	.98	EBL21	.60	EL90	.22	PCF84	.40	Q875/20	.63	VU111	.44	ADT140	.63	BFY14	.18	OC70	.13
1U5	.48	6C8A	.50	6U4GT	.60	20P4	.89	.89	.88	EC86	.59	EM80	.75	PCF84	.40	Q875/20	.63	VU111	.44	ADT140	.63	BFY14	.18	OC70	.13
2I21	.35	6C86	.38	6V6G	.17	20P5	1.00	ACJPEN	.38	EC88	.59	EM81	.37	PCF86	.44	Q895/10	.49	VU120	.60	ADP106	.50	BFY26	.15	OC71	.11
2K3	.50	6C86	.43	6V6GT	.27	25A6G	.29	ACJTH1	.50	EC92	.34	EM83	.75	PCF200	.87	QV04/7	.83	VU120A	.60	ADP14	.25	BFY27	.18	OC72	.11
3A4	.25	6C97	.50	6X4	.20	25L6G	.20	ACJTH1	.98	EC93	1.50	EM84	.31	PCF801	.28	R19	.28	VU133	.35	ADP15	.15	BFY20	.25	OC74	.23
3Q4	.38	6C9V4	.63	7B6	.58	25Z4G	.48	AL50	.78	EC93	.95	EM85	1.00	PCF802	.37	SP41	.75	W107	.50	ADP17	.19	BFY21	.25	OC75	.11
3Q5GT	.36	6DE7	.50	7B7	.32	25Z5	.40	AZ1	.40	EC81	.18	EM81	.29	PCF806	.55	SP61	.75	W229	.60	ADP21	.30	BFY22	.25	OC76	.15
384	.23	6D7E6	.50	7H7	.28	25Z6G	.48	AZ31	.46	EC82	.19	EM81	.35	PC183	.29	TP2620	.98	Transistors	AF125	.17	CG126	.20	OC78	.15	
4CB6	.50	6E7A	.55	7K7	.65	30A5	.44	AZ41	.53	EC83	.21	EM83	.54	PC183	.54	UABCB0	.98	Diodes	AF126	.18	PNY11A	.23	OC78D	.15	
5C88	.50	6E85	.55	7Y4	.60	30C15	.55	CL33	.90	EC84	.28	EM84	.60	PC184	.32	UAF42	.49	2N404	.18	ADP19	.65	PNY41A	.23	OC81	.11
5T4	.30	6F1	.55	7Z4	.50	30C17	.74	CV63	.53	EC85	.32	EM87	.27	PC1805/85	FBC41	.45	2N3965	.53	ADP18	.68	ADP19	.68	OC81D	.11	
3I4G	.30	6G16	.63	8H6G	.25	25Y3A	.48	AL50	.78	EC94	.60	EM87	.34	PCF806	.55	SP61	.75	W229	.60	ADP21	.30	BFY22	.25	OC76	.15
5V4G	.33	6F13	.33	9I7	.78	30F3	.81	CV91	.29	EC89	.48	EM89	.40	PC186	.55	UBF80	.28	2N2147	.85	ADP86	.55	OC82	.22		
5Y3GT	.25	6F14	.40	10C2	.49	30F11	.58	DAF91	.20	EC90	1.70	EZ41	.42	PD500	1.44	UBF89	.28	2N2297	.23	ADP39	.38	BFY19	.20	OC83	.20
5Z4G	.38	6F18	.45	10E7	.50	30F12	.58	DAF96	.33	ECF20	.27	EZ80	.19	PEN4DD	UBL21	.55	2N2369	.22	BA102	.45	GET573	.38	OC84	.24	
5Z4GT	.38	6F23	.65	10F1	.75	30F12	.67	DAF96	.30	ECF22	.25	EZ81	.20	.1	.1	UC92	.35	2N2813	.39	BA115	.14	GET587	.43	OC123	.23
6J30L2	.55	6F24	.68	10F9	.45	30F13	.47	DF91	.14	ECF86	.64	UY501	.75	PEN45	.40	UCC84	.33	2N3053	.33	BA116	.25	GET873	.15	OC139	.23
6A81	.33	6F25	.61	10F18	.35	30F14	.68	DF96	.34	ECF804	.4	UY502	.39	PEN45DD	UCC85	.33	2N3121	2.90	BA128	.13	GET897	.28	OC169	.23	
6A87	.15	6F28	.60	10D11	.53	30F15	.55	DF76	.28	2	1.0	UY503	.70	UY503	.70	UY503	.70	UY503	.70	UY503	.70	UY503	.70	UY503	.70
6A86	.25	6F29	.15	10P13	.54	30L17	.85	DK40	.55	EC91	.23	UY504	.47	PEN46	.20	UY504	.60	2N3709	.20	BA153	.15	GET898	.22	OC200	.22
6AH5	.50	6G18A	.50	10P14	1.08	30P4MR	.95	DK92	.35	EC93	.50	UY507	.67	PEN45DD	UY504	.57	2N3988	.50	BC107	.13	M1	.15	OC201	.38	
6AJ3	.75	6G18	.50	12A6	.83	30P12	.89	DK96	.23	EC94	.57	HABC80	.44	UY508	.29	2N323	.50	BC108	.13	OA5	.28	OC203	.30		
6AK3	.25	6G17	.50	12A6G	.40	30P19	.1L92	.23	EC91	.25	HL23DD	.40	PENDD	.98	UY509	.29	2N323	.50	BC113	.25	OA9	.13	OC204	.30	
6AK6	.30	6H6GT	.15	12A16G	.40	30P4	.55	DL96	.35	EC93	.38	HL41DD	.88	4020	.88	UY510	.48	AA129	.18	BC115	.15	OA10	.43	OC205	.43
6AM8A	.50	6H6A	.19	12A25	.48	30P11	.57	DM70	.30	EC94	.38	HL42DD	.50	PF1200	.50	UY511	.50	AA129	.18	BC116	.25	OA47	.10	OC12	.53
6AN8	.49	6H6GT	.19	12A78	.23	30P13	.75	DM71	.38	EC95	.38	HL43DD	.50	PF1200	.50	UY512	.50	AA129	.18	BC117	.25	OA47	.10	OC12	.53
6AQ5	.21	6J6	.18	12A8V6	.21	30P14	.62	DY87/6	.22	EC92	.22	HL44DD	.50	PF1200	.50	UY513	.50	AA129	.18	BC118	.25	OA47	.10	OC12	.53
6AR5	.30	6J7G	.24	12A8V6	.28	30P15	.87	DY802	.29	EC93	.22	HL45DD	.50	PF1200	.50	UY514	.50	AA129	.18	BC119	.25	OA47	.10	OC12	.53
6AT8	.18	6J7(M)	.38	12BAC	.30	35A3	.48	EMOCC	1.85	EC94	.54	KT2	.25	PL81A	.48	UY515	.50	AA129	.18	BC120	.25	OA47	.10	OC12	.53
6AU6	.19	6J18A	.50	12BEG	.30	35D5	.70	EMOCC	1.85	EC95	.54	KT41	.88	PL82	.28	UY516	.50	AA129	.18	BC121	.25	OA47	.10	OC12	.53
6AV6	.28	6K7G	.10	12BH7	.27	35L6GT	.42	EMOCC	1.85	EC96	.54	KT41	.88	PL82	.28	UY517	.50	AA129	.18	BC122	.25	OA47	.10	OC12	.53
6AW8A	.54	6K8A	.16	12J7GT	.33	33V4	.23	EMOCC	1.85	EC97	.40	EMOCC	1.85	EC98	.40	UY518	.50	AA129	.18	BC123	.25	OA47	.10	OC12	.53
6AX4	.39	6L3	.98	12K5	.50	35Z4GT	.24	EMOCC	1.85	EC99	.40	EMOCC	1.85	EC100	.40	UY519	.50	AA129	.18	BC124	.25	OA47	.10	OC12	.53
6B8G	.13	6L6GT	.39	12K7GT	.34	35Z5GT	.30	EMOCC	1.85	EC101	.40	EMOCC	1.85	EC102	.40	UY520	.50	AA129	.18	BC125	.25	OA47	.10	OC12	.53
6BA6	.19	6L7	.38	12Q7GT	.28	50K5	.32	EMOCC	1.85	EC103	.40	EMOCC	1.85	EC104	.40	UY521	.50	AA129	.18	BC126	.25	OA47	.10	OC12	.53
6BC8	.50	6L18	.44	12M7	.35	50C16G	.42	EMOCC	1.85	EC105	.40	EMOCC	1.85	EC106	.40	UY522	.50	AA129	.18	BC127	.25	OA47	.10	OC12	.53
6BE6	.20	6L19	1.38	12M7	.35	50C16G	.42	EMOCC	1.85	EC107	.40	EMOCC	1.85	EC108	.40	UY523	.50	AA129	.18	BC128	.25	OA47	.10	OC12	.53
6BH6	.43	6L20	.48	12SH7	.15	50E15	.65	EA76	.88	EF93	.54	KT41	.88	PL82	.28	UY524	.50	AA129	.18	BC129	.25	OA47	.10	OC12	.53

All goods are unused, boxed, and subject to the standard 90 day guarantee. Terms of business - Cash or cheque with order only. Post/packing 3p. per item, subject to a minimum of 9p. per order. Orders over £5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p. extra per order. Complete catalogue with conditions of sale 7p. price 7p. post paid. Business hours Mon.-Fri. 9-5.30 p.m.
We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.

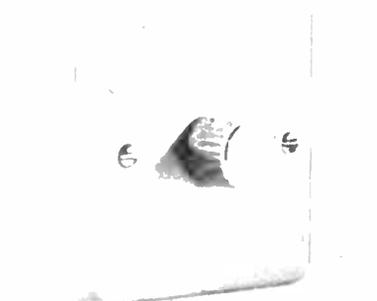Vary the strength of your lighting with a DIMMASWITCH




The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:
600 Watt £3.20* Kit Form £2.70*
300 Watt £2.70* Kit Form £2.20*

All plus 10p post and packing. *from 1st April please add appropriate percentage of V.A.T. increase. Please send C.V.O. to:-

DEXTER & COMPANY
ULVER HOUSE, 19 KING STREET,
FESTER CH1 2AH Tel: 0244-25883

VEROBOARD

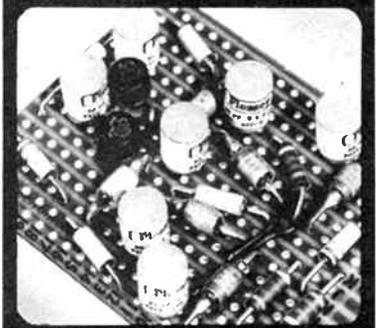

VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK
0.1" and 0.15" pitch, circuit and copper clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL REPAIRER
TRADE DISTRIBUTOR: N. Berr (Electrical) Ltd., London W.C.1



SAVE TIME AND MONEY

LIST PRICE £6.25 | OUR PRICE £4.84



As supplied by us to **SCHOOLS, TECHNICAL COLLEGES, HOPS, OFFICES AND INDUSTRY**. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21" x 11" x 6". Size of drawers 6 1/2" x 2 1/2" x 1 1/2". Other sizes available. Callers welcome Mon.-Sat. 9 a.m.-1 p.m. 9 p.m.-6 p.m. NEW as illustrated OUR PRICE ONLY £4.84 plus 36p carriage on orders less than £10. Money back guarantee. SEND FOR FREE COLOUR BROCHURE.

TRADE AIDS
(DEPT. PW9), 111 CHILTERN DRIVE,
BERRYLANDS, SURBITON, SURREY
01-399 4383
100 yds. Berrylands Railway Station.

NEW! FROM ADCOLA

THE BEST IN SOLDERING KITS

Styrene packed with see-through top
Makes the perfect gift!




Contents
BOX OF SOLDER
TWO SPARE BITS
HINTS ON SOLDERING
686 SOLDERING STAND
646 INVADER SOLDERING TOOL

Built to world safety standards

The Adcola Invader Soldering Kit comes to you in a presentation pack!
 The 'READY TO USE KIT' offers maximum versatility of a 23 watt soldering instrument.

only £3.99

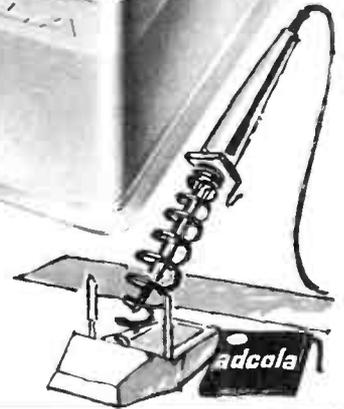

THE FABULOUS INVADERS

SOLDERING INSTRUMENTS

The number one accepted soldering instrument used by the professional in industry. IS NOW ON OFFER TO YOU.

L 706 19watts £1.96
L 646 23watts £2.12
L1076 27watts £2.18

No heat sink required. Stock voltages 110v., 220v. and 230/250v.

L686 SOLDERING INSTRUMENT STAND



The perfect instrument stand for your 'Invader'.

£1.71

MULTI-CHANNELLED SOLDER



Pre fluxed solder 'READY TO USE' produced to B.S.I. 441 IN HANDY SIZES. **£0.41 and £1.16**

PLEASE SEND ME THE FOLLOWING ITEMS

NAME & ADDRESS _____

INVADER SOLDERING KIT

1076 'INVADER' _____

646 'INVADER' _____

706 'INVADER' _____

686 SOLDERING STATION _____

1/2 kg SOLDER REEL _____

SMALL SOLDER REEL _____

Postage & packing add 10p. free over £2

Enclosing P/O and cheque



ADCOLA PRODUCTS LTD. ADCOLA HOUSE
 GAUDEN ROAD LONDON, SW4 6LH
 TELEPHONE. 01-622-0291/3

PW

COMET HI-FI discount warehouses



NEW LOW PRICES

	Rec. Retail Price	Comet Price
STEREO AMPLIFIERS are tax free—		
Buy now before V.A.T.		
ALBA UA 700	37 93	25 25
ALPHA 212 by Highgate	37 75	23 95
AMSTRAD IC 2000	46 25	27 50
AMSTRAD Integra 4000	35 50	21 50
ARMSTRONG 921	59 00	43 75
FERRROGRAPH F307 Mk. II (cased)	68 00	45 50
GOODW/VN RH 25 25	59 95	47 95
GLIXOR MW3000, 15 watts RMS per channel	49 50	23 95
JVC NIVICO VN 300	58 00	48 95
MCA 104Z	85 00	70 95
MCA 105E	130 50	109 95
MCA VSE VN550 Quadraphonic	89 00	74 95
MCA V9E VN800 Quadraphonic	148 00	124 95
KELETRON KSA 700	29 00	17 95
KELETRON KSA 1500	39 00	23 95
LEAK Delta 30 (cased)	69 90	48 95
LEAK Delta 70 (cased)	85 90	57 95
METROSOUND ST20E	39 50	24 20
METROSOUND ST60	70 00	45 45
PHILIPS RH521	109 00	89 95
PIONEER SA500A	47 10	32 95
SA600	95 48	57 95
SA800	126 55	75 95
SA1000	155 82	94 95
QL600A Quadraphonic Converter	118 95	78 95
QD 210 Quadraphonic decoder	42 85	29 95
QA 800 Quadraphonic	188 60	122 95
Reverberation 202w	54 95	35 95
RANK ROTEL 210	34 00	22 95
RANK ROTEL 310	52 00	34 95
RANK ROTEL 610	78 50	51 95
RANK ROTEL RA 810	105 50	72 95
RANK ROTEL RA 1210	129 00	89 95
ROGERS Ravensbourne	70 00	53 95
Ravensbourne (cased)	75 00	58 95
Ravensbrook Mk. II	52 50	40 95
Ravensbrook (cased) Mk. II	57 50	43 95
SINCLAIR 2000	35 00	22 95
3000	45 00	28 95
PROJECT 605	29 95	18 90
SOLARVOX 20, 10 watts RMS per channel	39 95	24 95
SOLARVOX 30, 15 watts RMS per channel	46 95	32 95
SOLARVOX MA801 2 x 8 watts RMS plus MATRIX 4 channel	38 45	26 95
SOLARVOX MA813 2 x 18 watts plus MATRIX 4 channel	51 38	38 95
TANDBERG TA300	69 90	54 95
TANDBERG TA300M	79 50	65 95
WHARFEDALE Linton amplifier	65 00	42 95
All take both ceramic and magnetic cartridges.		
TUNERS		
AMSTRAD Multiplex 3000 FM	39 95	28 95
*ARMSTRONG 523 AM/FM	52 68	40 95
*ARMSTRONG 524 FM	40 97	31 95
ARMSTRONG M8 Decoder	9 50	6 95
*DULCI FMT 7 FM	24 43	14 95
GOODMANS Stereomax	75 74	35 95
JVC NIVICO MCT V5e/VT500 AM FM	86 00	69 95
MCT V7E AM/FM	122 42	99 95
LEAK Delta FM	79 50	57 95
LEAK Delta J/FM	89 50	69 95
METROSOUND FMS 20	54 22	37 95
PHILIPS RH 690	48 50	31 95
PHILIPS RH 621	109 00	89 95
PIONEER TX500A AM/FM	75 52	56 95
PIONEER TX600 AM/FM	104 57	73 95
RANK ROTEL 320	59 50	42 95
RANK ROTEL 620	93 50	67 95
ROGERS Ravensbrook Chassis	60 29	45 95
Ravensbourne In Teak Case	64 97	48 95
Ravensbrook Chassis	43 90	33 50
Ravensbrook (cased)	49 75	38 50
SINCLAIR 2000	45 00	29 95
3000	45 00	29 95
Project 60 Tuner (stereo)	25 00	17 50
All above Tuners are complete with MPX Stereo Decoder except where starred		
TUNER/AMPLIFIERS		
AKAI CR80T AM/FM Tuner Amplifier with built in Eight Track Tape Recorder	149 84	89 95
AKAI A8300	139 50	106 95
AKAI A8080	159 50	142 95
AKAI A8500	249 00	179 95
AKAI 6300	137 50	79 95
ARENA 2600	111 30	59 95
ARMSTRONG M8 Decoder	9 50	6 95
ARMSTRONG 525	90 14	69 95
ARMSTRONG 526	102 72	77 95
GOODMANS M80 80, 35w. RMS Module 80 Compact	168 00	127 95
Module 90	119 00	81 95
Module 110 FM/MW/LW/SW/100w. RMS	139 00	105 95
GOODMANS Module 110, Compact	245 00	187 50
JVC Nivico AM1000 Quadraphonic	159 50	124 95
JVC Nivico VR 5500/5501 AM/FM	96 98	81 95
VR 5521L AM/FM and SEA	175 00	146 95
4VR 5414 Quadraphonic	212 00	179 95
KYOTO 1000 AM/FM Tuner/Amplifier with built in Stereo Cassette Recorder. Complete with two speakers and two microphones	85 00	61 95

	Rec. Retail Price	Comet Price
TUNER AMPLIFIERS—continued		
LEAK Delta 75	175 00	129 95
PHILIPS RH 720	215 00	179 95
PIONEER SX525	140 53	98 95
SX626	192 49	134 35
SX727	231 74	162 95
SX828	297 20	208 95
OX 4000 Quadraphonic	225 93	164 95
OX 8000 Quadraphonic	286 24	198 95
ROGERS Ravensbrook Chassis	96 57	73 95
ROGERS Ravensbrook (cased)	105 35	78 45
ROTEL RX 150A	69 90	50 95
ROTEL RX200A	89 50	65 95
ROTEL RX 400A	107 50	78 95
ROTEL RX 600A	149 00	109 95
ROTEL RX 800A	189 50	139 95
ROTEL RX 154A Quadraphonic	129 50	84 95
SOLARVOX TAM 1105 2 x 5 watts R/S AM/FM Multiplex comp. with 2 speakers and featuring Matrix 4 channel	38 50	28 95
TANDBERG TR200 MPX	106 00	85 95
TANDBERG TR1000 FM MPX (teak)	156 00	129 60
TANDBERG TR 1010 AM/FM MPX	169 00	139 95
TELETON CR55	125 26	88 50
TELETON R8000 AM/FM	42 16	21 95
WHARFEDALE LINTON WE40	115 00	95 95
All the above take magnetic cartridges except Teleton R8000 and Kyoto 1000 which take ceramic only. All include MPX Stereo Decoder with the exception of Armstrong where M8 decoder is extra		
TURNTABLES		
CONNOISSEUR BD1 kit	13 34	10 95
CONNOISSEUR BD2 Chassis	32 71	25 95
CONNOISSEUR BD2 P/C/SAU2	41 29	33 95
GARRARD SP25 Mk. III	16 17	10 50
GARRARD 40B	13 63	10 50
GARRARD SL65B	20 93	13 75
GARRARD SL95B	49 21	32 25
GARRARD 401	42 88	29 50
GARRARD SL72B	32 60	21 95
GARRARD AP76	28 49	17 25
GARRARD Zero 100A	57 42	38 95
GARRARD Zero 100S	52 83	36 95
The following Turntables are complete with base, plinth, plastic cover and cartridge. Fully wired and ready for use. All at special prices.		
GARRARD SP25 Mk. 111 with Goldring G800	Special Price £18 50	
McDONALD MP60 with Goldring G800	Special Price £17 50	
McDONALD MP65 with SHURE M7	Special Price £18 95	
McDONALD MP60 with SHURE M44/E	Special Price £19 95	
McDONALD HT70 with Goldring G800	Special Price £25 50	
GARRARD AP76 with Goldring G800	Special Price £26 50	
GARRARD AP76 with Shure M55E	Special Price £30 50	
GARRARD AP76 with Shure M75EJ	Special Price £32 50	
GARRARD 2025 with Sonotone STAHC	Special Price £12 75	
GOLDRING GL75 with G800	Special Price £39 50	
GOODMANS TD100 with G800E	75 00	51 95
Base and cover to fit GARRARD		
SP25, SL55, SL65B	Sp. Price	3 60
GOLDRING G101P/C	29 64	20 50
GOLDRING GL72 Chassis	31 39	20 95
GOLDRING GL72P	40 81	27 50
GOLDRING GL75	41 86	26 95
GOLDRING GL75P	51 62	35 25
GOLDRING GL85P/Cover	87 19	56 95
Cover for 72P	4 71	3 25
Cover for 75P (de Luxe)	5 23	3 50
Cover for 85P	6 98	4 95
C99-plinth and cover for G99	15 35	11 95
GOLDRING G99	29 64	19 25
PHILIPS G4212 Electronic	69 50	52 50
JVC Nivico SRP 470 Quadraphonic including plinth and cover	69 50	56 95
McDONALD MP60	14 78	9 50
McDONALD 610	18 75	12 95
McDONALD HT70	20 63	14 50
Base and cover for MP60 and 610. Sp. Price		
PHILIPS G4212 Electronic	69 50	57 50
PIONEER PL12D with base and cover	49 18	34 50
PIONEER PL61 with base and cover	176 83	119 95
THORENS TX25 cover	8 85	6 50
THORENS TD125 Mk. II	82 63	66 50
THORENS TD125AB Mk. II with TP 16 arm	115 69	79 95
THORENS TD125AB Mk. II with TP 16 arm	124 54	99 95
THORENS TD160C including base and cover	69 80	56 95
THORENS TX11 cover	4 49	3 80
WHARFEDALE Linton	37 50	28 95

	Rec. Retail Price	Comet Price
SPEAKERS		
*Speakers are tax free—buy now before V.A.T.		
*AMSTRAD 138 (pair) Teak	26 00	13 95
*AKAI SW 155	64 50	44 85
*B and W Model 70	159 50	109 95
B and W DM2	69 99	47 50
B and W DM4	49 66	37 95
B and W DM5 (pair)	59 48	43 95
CELESTION COUNTY (pair)	47 94	35 95
Dillon 120 (pair)	56 40	38 50
Dillon 15	37 40	26 00
*Dillon 25	65 00	42 50
*Dillon 44-speaker system (pair)	95 00	55 00
*Dillon 66	99 70	70 95
*FERRROGRAPH S1 inc. stand	95 00	67 95
GOODMANS Minister Pair	49 20	35 95
Hadant (pair)	57 12	39 40
*Magister	65 63	42 50
Double Maxim (pair)	67 40	47 95
*Mezzo 3	35 70	23 45
*Magnum K2	46 20	29 50
*Goodwood	55 00	36 95
*Dimension: 8	72 44	44 95
DIN 20 NT Kit	12 19	8 50
KELETRON KN 400 2-speaker system (pair)	15 44	11 95
KN100 3-speaker system (pair)	28 82	16 95
*KN800 3-speaker system (pair)	31 80	18 95
*KN1100 4-speaker system (pair)	40 80	23 95
*KN1600 3-speaker system	25 20	14 95
*KN2100 3-speaker system	30 60	18 95
LEAK 150 (pair)	50 00	37 50
LEAK 250 (pair)	63 00	47 95
*LEAK 600	49 50	34 50
*LINEAR 10 watt Teak (Pair)	Sp. Price	12 95
METROSOUND HFS 103 (pair)	29 21	20 95
*202	21 50	14 75
*Duplex 15	32 00	23 95
*Duplex 25	56 00	37 50
*PIONEER CS53	46 72	29 95
SINCLAIR O16	8 98	6 50
TANDBERG Tan 7	29 50	23 60
Tan 11 (pair)	40 00	31 95
TL 12 Teak (pair)	55 50	44 50
TL 25 Teak (pair)	71 50	56 95
*TL 50 Teak (pair)	68 00	50 95
TELETON 8000 (pair)	21 08	11 95
*THORPE GRENVILLE TG100 (pair)	28 95	16 95
*TG200 (pair)	41 95	24 95
*TG300 (pair)	55 95	29 95
WHARFEDALE Denton Mark II (pair)	42 00	28 95
Linton Mark II (pair)	52 00	37 50
Trillon 111 (pair)	65 00	46 95
*Mellon Mark II	35 00	23 75
*Dovedale 3 Mark II	47 50	32 25
*Rosedale	69 00	44 95
Unit 3 speaker kit	12 50	8 95
Unit 4 speaker kit	19 00	12 95
Unit 5 speaker kit	27 50	18 75
PICK UP ARMS AND HEADS		
AUD Technica AT 1005 Mk. 11	18 78	14 25
AUD Technica L2 Hita	2 61	1 95
CONNOISSEUR SAU2	14 61	11 95
GOLDRING Lenco 75	13 96	9 25
GOLDRING Lenco L69	10 46	6 50
GOLDRING PH6 Head Shell	2 97	1 99
SME 3009 ser 11 Improved	36 75	28 50
SME 3009-S2 ser 11 Improved	40 25	30 95
SM S2 Headshell	2 59	1 95
CHASSIS SPEAKERS		
*Items are tax free—buy now before V.A.T.		
GOODMANS Twin-axiom 8	8 12	6 95
Twin Axium 10	10 06	7 50
*Axium 401	17 68	11 95
Axium 8P	5 49	4 15
Axium 10P	5 97	4 50
*Axium 12P	13 00	9 15
Axium 15P	21 00	14 60
*Axium 18P	35 70	24 45
*Axium 100 40 watts din.	12 00	8 35
*ARU 172	4 50	3 20
*Axent 100	13 90	9 80
*Midax 650	6 39	4 50
*Axiator	3 73	2 80
*Crossover network XO/850	7 77	5 45
WHARFEDALE 8 In. Bronze/RS/DD Super 8/RS/DD	4 75	3 30
Super 8/RS/DD	8 50	6 25
Super 10/RS/DD	14 00	9 95
CARTRIDGES		
AMSTRAD 900C	5 32	3 40
AMSTRAD 900D	8 10	5 40
AMSTRAD 900 EX	11 90	8 50
AUDIO TECHNICA AT 68	6 47	3 45
*CONNOISSEUR Ceramic SCU1	6 09	4 65
GOLDRING G850	6 10	3 10
GOLDRING G800	12 21	4 50
GOLDRING G800E	17 67	7 00
GOLDRING G820	11 82	8 25
GOLDRING G820E	17 44	12 25
GOLDRING G820 Super E	23 25	16 25
*GOLDRING G800 Super E	24 41	15 95
EMPIRE 1000E/X	62 22	39 95
EMPIRE 999VE/X	44 44	28 95
EMPIRE 999TE/X	26 13	18 95
EMPIRE 999SE/X	21 11	13 95
EMPIRE 999E/X	16 36	10 95

OVER 1000 ITEMS ALWAYS IN STOCK

All items brand new and fully Guaranteed and backed by after-sales service

— latest models in manufacturers' sealed cartons



COMET for after-Sales Service THROUGHOUT THE U.K.

Pictured: Service Department at Clough Road, Hull. Also at Birmingham, Bristlington, Dagenham, Doncaster, Edinburgh, Gains, Hackbridge, Hynes, Jarrow, Leeds, Leicester, Nottingham, Renfrew, Rochdale, Sheffield, Trowdale, Wigan with Engineers covering York and Scarborough

	Rec.	Retail Price	Comet Price
CARTRIDGES—continued			
EMPIRE 909E/X	12	79	8.50
EMPIRE 90EE/X	9	94	6.95
SHURE M3DM	6	10	3.75
SHURE M31E	11	63	6.95
SHURE M32E	10	73	6.50
SHURE M44-G	8	30	4.95
SHURE M44-7	7	90	4.50
SHURE M-44C	7	90	4.90
SHURE M44E	8	60	4.75
SHURE M55E	9	70	5.45
SHURE M75G	14	70	8.35
SHURE M75-6 (S)	8	36	5.45
SHURE M75-6	13	60	5.95
SHURE M75EJ	15	40	8.75
SHURE M75ED	19	00	10.15
SHURE M75E/95G	20	80	12.95
SHURE M91ED	18	45	9.95
SHURE V15-11	39	40	24.95
*SONOTONE 9TAHC Diam/Saph	3	75	1.45
Stereo cartridges above are ceramic. All others are magnetic.			
BASES AND COVERS			
CONNOISSEUR Plinth BD1	5	57	4.50
CONNOISSEUR Cover	4	17	3.40
CONNOISSEUR P.U. Mount Board	0	95	0.75
GARRARD WB1 Base	3	78	9.95
GARRARD WB4 Base	5	60	4.25
GARRARD SP1 Cover	3	68	2.75
GARRARD SP4 Cover	4	38	3.25
Special Offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500			
GOLDRING Plinth 75		Sp. Price	3.60
GOLDRING Plinth 72		9	7.75
GOLDRING Covers for 72P		9	4.25
Cover for 75P De Luxe		5	23
Cover for 85P		6	98
THORENS TX 25 (for TD125AB)		8	85
THORENS TX11 Cover		4	49
SME Plinth System 2000 with motorboard	46	20	35.95
MOTORBOARDS only	5	85	4.45
SME P1 Spacer	0	98	0.75

	Rec.	Retail Price	Comet Price
BLANK TAPES			
SCOTCH DYNARANGE CASSETTES			
C60	0	71	0.40
C90	0	99	0.50
C120	1	49	0.75
SCOTCH HIGH ENERGY COBALT CASSETTES			
C60	1	10	0.65
C90	1	45	0.85
SCOTCH Low Noise 8-TRACK BLANK CARTRIDGES			
40 mins.	1	50	0.90
80 mins.	1	60	1.10
SCOTCH HI-FI DYNARANGE SPOOLED TAPES			
5" L.P. 900	1	88	1.10
5 1/2" L.P. 1200	2	20	1.30
7" L.P. 1800	2	95	1.80
SCOTCH HI-FI DYNARANGE DOUBLE PLAY			
5" D.P. 1200	2	31	1.40
5 1/2" D.P. 1800	3	15	1.95
7" D.P. 2400	4	03	2.50
Postage—Tape, cassettes and 8T cartridges 1-9 items 5p per order. Packs of ten post free.			

	Rec.	Retail Price	Comet Price
HEADPHONES			
Are now tax free—buy now before V.A.T.			
AMSTRAD HP55A	7	50	3.90
HP55A with volume control	10	70	6.70
HP57A bass and treble controls	13	95	9.90
AKAI ASE9	7	25	4.25
AKAI ASE22	11	90	7.25
AKG K180	28	00	16.95
AKG K60	15	00	8.95
AKG K100	8	00	4.95
AKG K20	10	00	4.50
KOSS HV1	20	00	15.95
KOSS ESP-9 Electrostatic	69	00	52.95
KOSS ESP-6 Electrostatic	45	00	34.95
KOSS K2 plus 2 Quadrafone	45	00	35.95
KOSS PRO 5 L/C	30	00	23.95
KOSS PRO-4A	28	00	20.95

	Rec.	Retail Price	Comet Price
HEADPHONES—continued			
KOSS KO-727B	16	50	12.45
KOSS 747	20	00	14.95
KOSS K-711	10	00	7.75
KOSS K6	12	50	9.50
KOSS K6/LC (with volume control)	14	00	10.50
KOSS K6/LC Quadrafone	20	00	16.95
PIONEER SE 50	21	90	13.25
PIONEER SE 30A	12	60	8.25
PIONEER SE 20A	7	88	4.95
PIONEER SEL 20	10	53	6.80
PIONEER SEL 40	17	43	11.30
SOUND MD806	6	50	2.80
WHARFEDALE DD1	12	50	8.75
WHARFEDALE ISODYNAMIC	19	95	14.95

	Rec.	Retail Price	Comet Price
HI-FI STEREO SYSTEMS—COMPLETE			
ALBA UA 552	47	75	29.95
BUSH A1005	69	89	50.95
DANSETTE Consort Stereo	34	43	23.95
DANSETTE 4005	71	45	49.95
DANSETTE 4020	47	99	31.95
DECCA SOUND 613		Sp. Price	16.50
DECCA SOUND 614		Sp. Price	52.95
DECCA COMPACT 2 with Radio		Sp. Price	78.95
DECCA COMPACT 3 with Radio		Sp. Price	97.95
DECCA 403		Sp. Price	44.95
FERGUSON 3450 B with Radio (new model)	79	50	61.95
FERGUSON 3451 B with Radio (new model)	107	00	82.95
FERGUSON 3454	41	50	32.95
FIDELITY UA1 Music Master with Radio	100	00	69.95
FIDELITY UA2 Music Master	43	50	30.95
FIDELITY Stereo Nine	38	50	22.95
G.E.C. 2810	79	00	59.95
GROSVENOR MPX 8400 AM/FM MPX Tuner/Amplifier, magnetic input with built-in 8-track cartridge player with speakers	69	95	41.50
HMV 2451	122	00	95.95
HMV 2452	66	00	49.95
HMV 2455	175	00	136.95
KB 1025 with 662 speakers	48	25	37.95
KB 1250 with KS 653 Speakers	71	00	53.95
KB 2010 with 658 speakers and Radio	101	50	77.95
KB 2250 with 658 speakers and Radio	124	00	95.95
MURPHY 902 Studio 1, with AM/VHF/Radio	84	50	64.95
MURPHY 940	69	89	52.95
PHILIPS 808	105	00	74.95
PHILIPS GF 824	65	30	49.65
PHILIPS 825	49	50	37.95
PHILIPS 826	75	00	51.95
PHILIPS 835 with Radio	69	50	47.95
PHILIPS 836 with Radio	95	00	67.95
RIGONDA Party Time	28	20	20.95
STEEPLETONE Stereo System	41	75	22.95
ULTRA 6027	57	50	44.95
ULTRA 6028	59	95	45.95
ULTRA 6450B (new model) with Radio	79	50	61.95
ULTRA 6451	79	50	61.95
ULTRA 6455	41	35	31.95
ULTRA 6454	38	85	29.95

	Rec.	Retail Price	Comet Price
TAPE RECORDERS			
AKAI 1721L	99	90	73.95
AKAI 4000 DS	99	50	73.95
AKAI X201D	179	00	132.95
AKAI X1810	229	00	169.95
AKAI GX221D	229	00	169.95
AKAI GX1900D	239	00	177.95
AKAI GX370D	350	00	259.95
AKAI CR80D 8-track stereo tape deck	85	02	55.95
AKAI CR80 8-track stereo recorder	106	39	69.95

	Rec.	Retail Price	Comet Price
TAPE RECORDERS—continued			
AKAI CR80DSS Quadraphonic	159	50	121.95
AKAI CR80T 8-track stereo recorder and tuner amplifier	149	84	89.95
AKAI CR81	109	50	80.95
AKAI CR81D	89	50	65.95
FERGUSON 3258 4-track	70	45	51.95
FERROGRAPH 702/704 Dolby	285	53	241.95
FERROGRAPH 702H Dolby	297	28	251.95
FERROGRAPH 722/724 Dolby	326	65	276.95
FERROGRAPH 722H Dolby	338	40	286.95
FERROGRAPH 702/704	235	00	172.95
FERROGRAPH 722/724	276	15	198.95
FIDELITY Braemar 4-track	34	75	19.95
GROSVENOR RP900, 8-track record/playback deck	54	50	38.95
GROSVENOR MPX 8400 AM/FM MPX Tuner/Amplifier, magnetic input with built-in 8-track cartridge player with speakers	69	95	41.50
GRUNDIG TK 121 (twin-track)	56	95	39.95
GRUNDIG TK 141 (4-track)	62	10	45.95
GRUNDIG TK 146 (4-track auto)	66	95	49.95
GRUNDIG TK 147 (4-track auto)	98	65	78.95
GRUNDIG TK 148 (4-tr. auto 2 spd.)	74	10	57.95
GRUNDIG TK 246 4-track Stereo Deck	131	85	101.95
GRUNDIG TK 3200 Hi-Fi (Battery)	141	10	105.95
MARCONI 4248 4-track, 2 speed.	52	30	39.95
PHILIPS 4303 Twin-track	39	46	24.95
PHILIPS 4307 4-track	50	00	35.95
PHILIPS 4308 De Luxe 4-track	59	00	42.95
PHILIPS 4418 4-track stereo rdr.	145	00	109.95
PHILIPS 4418 4-track stereo deck	200	00	145.95
TANDBERG 3341X 4-track stereo	129	90	109.95
TANDBERG 6041X 4-track stereo	199	30	159.95
TANDBERG 9021X 2-track stereo deck	230	00	194.95
TANDBERG 9041X 4-track stereo deck	230	00	194.95

	Rec.	Retail Price	Comet Price
TAPE RECORDERS (CASSETTE)			
AKAI CS5D tape deck	79	95	59.50
AKAI CS35 Stereo Inc. Speakers	112	50	82.95
AKAI GXC 40D tape deck	95	50	67.95
AKAI GXC 40	112	50	82.95
AKAI GXC 40R recorder, tuner/amp.	167	50	123.95
AKAI GXC 45D tape deck	119	50	89.95
AKAI GXC 46 Dolby tape recorder	152	50	115.95
AKAI GXC 46D Dolby tape deck	139	50	103.50
AKAI GXC 65D Dolby auto-reverse deck	154	50	110.25
BUSH Discassette DC70	20	62	12.95
BUSH TP 60	27	62	15.95
BUSH TP 66 Battery/Mains	28	18	21.50
GRUNDIG C240 with case	24	90	15.95
FERGUSON 3253 (Mains)	42	40	27.95
FERGUSON 3256 (Mains)	37	75	25.95
FERGUSON 3257	56	45	41.95
FERGUSON 3257/7 spkrs. for above	16	00	12.00
GEC CR200 AM/FM Cassette/Radio, Battery/Mains with slide controls		Sp. Price	35.95
GRUNDIG C210 Batt./Mains	48	75	36.95
HARVARD Elite Cassette/AM/FM Radio (battery/mains)	44	75	23.95
JVC Nivico 9420 LS with AM/FM radio, battery/mains	61	45	45.95
JVC Nivico 1710 Radio/Cassette, AM/FM	61	00	42.95
PHILIPS 2202/2203	24	00	17.95
PHILIPS 2204 battery/mains	29	10	24.95
PHILIPS 2405 Stereo with 2 RH401 L/S	72	00	52.95
PHILIPS 3302	21	50	15.95
PIONEER CT 4141 Dolby Deck	150	02	104.95
PYE 9116 Stereo	69	90	49.95
WHARFEDALE Dolby DC9 Mk. II.	119	00	85.95

FREE Technical Advisory Service. If in doubt ask us! Price list on request. Comet guarantees that all prices quoted are genuine. All offers subject to availability. Add 75p for postage, packing and insurance on all orders (Cartridges 20p) OR, IF SECURICOR DELIVERY REQUIRED add £1.95 only. Make cheques, Money Orders payable to 'COMET'.

COMET HIGH FIDELITY DISCOUNT WAREHOUSES

OPEN DAILY TO THE PUBLIC FROM:
 9am-3pm Monday
 9am-1pm Tuesday
 9am-3pm Wednesday
 9am-5pm Thursday
 9am-5pm Friday
 9am-5.30pm Saturday

- Dept. PW BIRMINGHAM: Heeley Road, Selly Oak, B29 6EY. Tel.: 021-422-6181 and at Tivoli Shopping Centre, 1570-1572 Coventry Road, Yardley B26 1BJ. Tel.: 021-706-0684
- Dept. PW EDINBURGH: 1 Newhaven Road, EH6 5QX. Tel.: 031-554-4454 (9 lines)
- Dept. PW HULL: Reservoir Road, Clough Road, HU6 7QD. Tel.: 0482 46441 (6 lines)
- Dept. PW LEEDS: 78 Armley Road, LS12 2EF. Tel.: 0532 40551
- Dept. PW SHEFFIELD: The Mill, 1 Loxley Road, Mallin Bridge, S6 4TN. Tel.: 0742 3417216
- Dept. PW STOCKTON: Teesway, Portrack Lane, Teasdale TS18 2RH. Tel.: 0632165215
- Dept. PW ROCHEDALE: Corner of Well 1st Lane and Queensway. Tel.: 50606
- Dept. PW LEICESTER: Syston Street. Tel.: 0533 52236
- Dept. PW WIGAN: Wharf Mill, Princess Street, WN3 4EZ. Tel.: 0942 34741
- Dept. PW LONDON: Hackbridge (nr. Croydon) 190 London Road, Hackbridge, Wallington, Surrey. Tel.: 01-669-0241
- Dept. PW LONDON: Dagenham, Rainham Road South, Dagenham RM10 8ST. Tel.: 01-595-5111
- Dept. PW LONDON: 4-7 Thomas Street, Sundridge, SR1 1RH. Tel.: 0793 59993
- Dept. PW RENFREW: Blythwood Trading Estate, Argyle Ave., Renfrew, RA4 9EL. Tel.: 041-886 5731
- Dept. PW JARROW: 56/64 Ellison Street, Jarrow NE32 3MT. Tel.: 0632 892211
- Dept. PW SANDIACRE: 121 Town Street, Sandiacre, Nottingham NG10 5DW. Tel.: Sandiacre 6116
- Dept. PW LONDON: Hayes, Silverdale Road, Pump Lane, Hayes. Tel.: 01-573 1841

SECURICOR
SPECIAL DELIVERY SERVICE

All in-stock items delivered by SECURICOR within 72 hours. (Add £1.95 only for Securicor delivery) ALL GOODS FULLY INSURED AGAINST LOSS OR DAMAGE WHILE IN TRANSIT

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88—108Mcs, with circuit diagram. **£2.10p.**

B.F.W. 10 Fet. New (unmarked) 5 for **£1.00p.**

PINNACLE LOW NOISE CASSETTES C60—50p; C90—75p; C120—£1.

P-C BOARDS (not computer panels).

1 off 6 transistors single wave band

1 off 4 transistor audio

1 off 3 transistor **£1.50 the three.**

Encapsulated bridge rectifier (itt usd 3 3mdh) 100 PIV 2 amps. **50p each. 3 for £1.25.**

Transistor F.M. Stereo Multiplex Decoder. Size: 5½ x 2½ x 1½. As used in well known British stereo units with circuit. **£3.75.**

GARRARD SP25 MK. 11 less Cartridge. **£10.50.**

10 VOLUME CONTROLS consisting of 2 off each.

100K log. ganged L/S—20K log. ganged L/S.

470K log. D/P Switch—10K lin. L/S—50K 1in. L/S. **£1.25.**

4 PHONO SOCKETS ON PANEL. 10 panels for **£1.25.**

12 PLASTIC KNOBS. Chrome and Gold, 3 types—4 off each—spring clip **£1.25.**

10 COMPUTER PANELS packed with components including one panel with 2 Power Transistors. **£1.00.**

SLIDER CONTROLS (less knobs)

25K Log or Lin single **30p.**

10K—100K Log ganged **50p.**

100K—100K Log ganged **50p.**

All items post paid in

GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

TEXAN 20+20 WATT. STEREO AMPLIFIER

Electro Spares can now supply all the components to build the "Texan" Amplifier, featured in *Practical Wireless* May/June 1972. All components are brand new with fibre glass p.c. board, all metalwork, knobs, finished silver trim front panel, etc. etc.

TOTAL COST OF COMPLETE COMPONENTS ONLY £27.85—POST FREE!

All components are available separately, to enable the constructor to obtain just what parts he requires at any one time. Please send S.A.E. for free list.

SPECIAL CONTEMPORARY STYLE SLIMLINE METAL CASE WITH WOODEN END CHEEKS IS NOW AVAILABLE FOR THIS AMPLIFIER—DETAILS INCLUDED WITH ALL LISTS, OR AVAILABLE ON RECEIPT OF S.A.E.

P. E. 'GEMINI' STEREO AMPLIFIER

30 Watts (R.M.S.) per Channel into 8 Ohms !!

Total Harmonic Distortion 0.02% !!

Frequency Response (-3 dB) 20Hz-100kHz !!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but it is well within the capabilities of the ambitious constructor.

We can now supply a reprint of the articles in booklet form, price 55p plus 4p postage, with free complete component price list.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.


All parts available separately.



ELECTRO SPARES

31 BROOKSIDE BAR,
CHESTERFIELD, DERBYSHIRE,
QUALITY • SERVICE • VALUE

HOME RADIO COMPONENTS

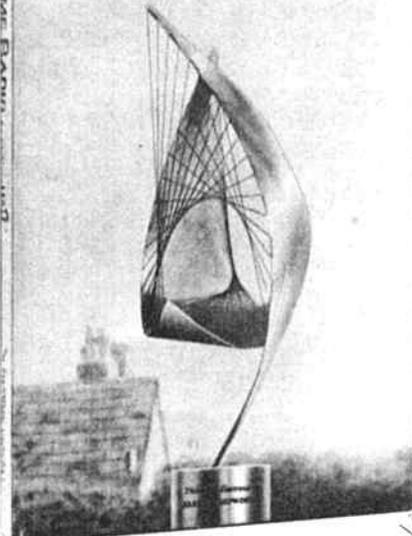

250 pages 11¼" x 8¼"

8,788 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

Only 55p.

plus 20p **POST AND PACKING**

POST THIS COUPON

with cheque or P.O. for 75p.

The Catalogue you MUST have!

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Name _____

Address _____



The price of 75p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

HOME RADIO (Components) LTD. Regd. No. 912966 London
Dept. PW, 234-240 London Road, Mitcham CR4 3HD

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic ASTRAD 17 and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! THIS ONE SUPERSEDES ALL EARLIER MODELS! It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! * Send quickly, after receiving goods test 7 days, refund if not delighted. Elegant black & chrome finish case, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures pure & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spacehip and satellite communications. Yes, EVERY WAVEBAND instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. VHF: FM/USW, AM: LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world! EXCLUSIVE TURBO TUNER wide control waveband selection unit (as used on expensive T.V.'s!) Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 ins approx. It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE 14ins x 10ins x 4ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come if ever necessary!) With WRITTEN GUARANTEE manual with simple operating instructions & circuit diagram. ONLY £20.75 (with mains/battery eliminator £1.48 extra). BOX, POST, ETC. 50p. * BUT WAIT, for only 55p extra you get the sensational "COMPUTERISED" WORLD TUNING GUIDE (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K., when abroad. (NO GUESSING! NO MESSING!) PLUS Standard 'longlife' batteries PLUS ultra sensitive earphone for personal listening (Sorry—We cannot change these new radios for any earlier model purchased.) HURRY! Shop opportunities save you ££'s and ££'s!

THOUSANDS OF MILES REDUCED TO INCHES? 1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! *COMPUTERISED?

THIS FANTASTIC
EARTH SHRINKER

YES, 24,901 miles
SHRUNK TO ONLY 14" x 10 1/2" x 4 1/2"
inches approx?

28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW)
LW, USW.)

£20.75 BOX POST ETC. 50p
MAINS/BATTERY ELIMINATOR £1.48 extra

BRAND NEW FABULOUS **ASTRAD 17**
PORTABLE RADIO & COMMUNICATIONS
RECEIVER



*COMPARE ITS PERFORMANCE with £80 RADIOS!
FIRST TIME EVER!
*NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE!
NO MORE GUESSWORK—INSTANT DATA at your fingertips—enables you to TUNE IN A FLASH to transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! Fabulous BRAND NEW **SOLID STATE** This equipment's got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

RECOMMENDED RETAIL PRICE £44

OUR PRICE £23.75 CARR. ETC. 35p

WITH REMOTE CONTROL MICROPHONE

Shop opportunities "thunder" ahead with an offer that's FANTASTIC (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord.) Record and play back anything, anywhere! RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE! Wonderful features: * Press-button Keyboard Control Panel or latest MASTER SWITCH CONTROL! * "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! * Separate ON/OFF and HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and extension speaker sockets! * Remote control microphone. * Built-in swivel telescopic aerial (24in approx.) Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes obtainable everywhere. And the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally city and regional stations in every part of the country plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £4.61 more for a Car Radio or Car cassette player ALONE! £23.75, CARR. ETC. 35p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. WITH WRITTEN GUARANTEE. Send quickly, after receiving goods test 7 days, refund if not delighted. Or call. BONUS OFFER: Batteries and Cassette Tape 25p extra if required.

FIRST TIME EVER! SAVE £14.48!
BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER

With remote control microphone.

FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26.97!

OUR PRICE £12.49 POST ETC. 31p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb deluxe portable BATTERY/MAINS tape recorder and player—and incredible Shop opportunities bring it to you for ONLY £12.49! Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9in x 5in x 2 1/2in approx. Design can vary slightly. With carry handle. WRITTEN GUARANTEE and full instructions. (Recommended selling price £26.97!) OUR PRICE ONLY £12.49 post, etc., 31p. * Send quickly, after receiving goods test 7 days—refund if not delighted. BONUS OFFER (one per customer)—Cassette tape, set of standard batteries AND microphone stand all for 50p extra, if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn store.)

SHOPERTUNITIES LTD.


Dept. WP/29 164 UXBRIDGE ROAD (facing Shepherds Bush Green), LONDON, W12 8AQ (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opp. Chancery Lane), LONDON, W.C.1 (Thurs 7 p.m.) BOTH STORES OPEN MON TO SAT 9 A.M. UNTIL 6 P.M.

SAXON ENTERTAINMENTS.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS. MAIN
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

SA25-SA35-SA100

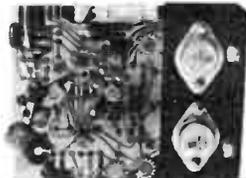LOW-PRICED AUDIO MODULES
FOR DOMESTIC & COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

SA25 £2.95 carr. free

25 WATTS RMS. 7 transistors 7 diodes

SA35 £4.45 carr. free

35 WATTS RMS. 7 transistors 7 diodes

SA100 £10.90 carr. free

100 WATTS RMS. 11 transistors 6 diodes

ALL THREE MODULES HAVE OPEN & SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION & FAULTY INDUCTIVE LOADS. ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRA-ORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC FOR ALL THREE MODULES

Freq. response	15-40,000 Hz \pm 1dB
Distortion	0.2% at 1 kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75 dB
Supply voltage	25-45 volts SA25/35 40-70 volts SA100
Size	4 1/2" x 4" x 1" (SA100) 4" x 3" x 1" (SA25/SA35)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilized supply for 2 SA25/35	£4.90
PU70	Unstabilized supply for one or two SA100	£7.75 carr. 40p
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
Stab PS45	Stabilized module for 2 SA25's or two SA35's	£3.50 carr. free
MT30	Transformer for unstabilized supply complete with rectifier diodes mounted	£3.50 carr. 20p
MT70	Transformer for PS70	£4.90 carr. 40p
PS70	Stabilized supply module for one or two SA100's	£4.90 carr. free

ALL MODULES ARE BUILT ON
GLASS FIBRE P.C. BOARD
AND ARE SUPPLIED FULLY TESTED

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE £13.90 + 20p carr. or with supply
£18.95 + 40p carr.

Featuring a rugged class A driver stage, this module will run from all our mixers, etc., and most other makes of mixer. It delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors.

SPECIFICATION

Power output 120 watts into 8 ohms
Freq. response 20-20,000 Hz \pm 2dB
Input sensitivity 200 mV into 10K
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply)
Low distortion parallel push-pull output stage.




NEW 160 watt version & supply **£27.90**

SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100 watts. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

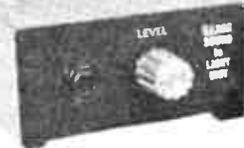Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



£8.90 carr. free



THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3000 watt (3kw) this unit is unique for its price in that not only bass, middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads etc. Supplied in tough white steel case with a blue hooded cover. Fully guaranteed.

£19.75 carr. 30p

MONO VERSION £6.50 carr. 20p (As illustrated, S.A.E. details 9 volt operation) Outputs up to 1 volt RMS



£15.80 carr. 30p


SAXON STEREO CONTROL UNIT

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass, treble, mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCOTHEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE. (N.B.—Stereo only has mic input.)

COMPLETE AMPLIFIERS

The CSE 100. £34.90 carr. free

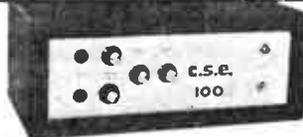This versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups D.J.S., etc.



The SAXON 100 £48.50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms £5.95 carr. 30p. 15" 50W.8/15 ohm £14.50 carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use.

D11DHL rrp £11.00 our price £9.45 post free
D190C High Z rrp £21.50 our price £17.45 post free
D1000C 24 ct gold plate rrp £37.00 our price £32.00 post free

SEND SAE FOR
OUR A.K.G. PRICE
LIST. DISCOUNTS
ON ALL MICS.

CALLERS & MAIL ORDER:

351 Whitehorse Road,
Thornton Heath, Surrey.
91-689 3685

CALLERS ONLY:

OUR NEW
DISTRIBUTORS

CIRCLE SOUND,
328-330 The Banks, Rochester.
Medway 404199

BUSINESS HOURS:

9.30 a.m.
to 5.30 p.m.

TERMS OF BUSINESS:

C.W.O. or C.O.D. (35p extra)
All cash in regd. envelopes please!
Telephone orders to our CROYDON BRANCH.
TRADE & EXPORT enquiries invited.

PRACTICAL WIRELESS

VOL 48 NO 12

Issue 794

APRIL 1973

The Buyer and VAT

During these last few weeks before Value Added Tax takes effect, readers will be contemplating whether to buy now or wait until after April 1st. It will undoubtedly pay to wait on such items as domestic receivers, some Hi-Fi equipment and electrical goods, but component suppliers are being hard pressed to meet demand before the infliction of VAT.

One way of circumventing purchase tax has been to supply equipment in kit form, but these items in any form will be liable for VAT at one common percentage rate, since VAT is a tax on the basic purchase price or charge for service.

We would expect that all suppliers will make it quite clear to all customers, at the trading premises and through advertisements, whether quoted prices include VAT. The basic retail price should remain the same as now. Whatever you pay for goods or services from April 1st, you should not be paying any purchase tax or selective employment tax levies; you should be paying VAT on top of the normal retail price, based on the Chancellor's Budget announcement on March 6th.

Kit and component prices should not be raised before April 1st and manufactured goods subject to purchase tax of more than 15% should be noticeably reduced after April 1st.

Shopkeepers and other traders are not legally bound to show the amount of VAT in cash transactions; neither will they necessarily show special "tax invoices" for retail sales, but it is worth remembering that if you purchase at a cut price rate, the VAT charged will be correspondingly lower. Goods obtained by hire purchase or credit agreements will be subject to tax at the current rate at the time when transaction documents are signed. Interest rates on these terms are not taxable. Private sales between individuals do not attract VAT because neither party is defined as a "taxable person", unless the seller is a trader required to register with H.M. Customs and Excise.

Our advice to readers who are thinking of buying goods by mail order during March is to determine first whether purchase tax is chargeable; if it is then wait until April. Items not subject to purchase tax (such as components and secondhand or used goods) should be ordered early. If of substantial value, send your order by P.O. "Recorded Delivery" and keep the counterfoil of your Postal Order, Money Order, or cheque.

You should be prepared for a VAT levy on charges for packing service but not for postage.

continued on next page

NEWS AND COMMENT

The Buyer and VAT	1081
News . . . News . . . News . . . <i>by Colin Riches</i>	1082
CQ! CQ! CQ!	1094
Hotlines <i>by Ginsberg</i>	1097
Practically Wireless <i>by Henry</i>	1102
Next Month in Practical Wireless	1103
MW Column <i>by Charles Molloy</i>	1111
Letters	1118
On the Short Waves <i>by Malcolm Connah and David Gibson, G3JDG</i>	1121

CONSTRUCTIONAL

Improving VHF Radio. <i>by A. N. Ainslie</i>	1084
Experimenters' Corner, Novel Tone Generator <i>by N. Naughton</i>	1088
IC Power Amplifier <i>by D. Silvester</i>	1090
"P.W. Tricolour" Mood Lighting System, Part 1 <i>by Jurek Budek</i>	1104
DXers MW Loop Aerial <i>by S. A. Money, G3FZX</i>	1112
Take 20, No. 47. Varicap B.F.O. <i>by Julian Anderson</i>	1126
Darkroom Exposure Meter <i>by A. P. Donleavy</i>	1129

OTHER FEATURES

Nautical Radio Aids <i>by Ian Sinclair</i>	1098
Going Back <i>by Colin Riches and Arthur Dow</i>	1124

**THE MAY ISSUE WILL BE
PUBLISHED ON APRIL 6th**

©IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

by
Colin Riches

VAT

To the best of our knowledge, the prices quoted in this issue were correct at the time of going to press.

From April 1st 1973, there will be no purchase tax but a large number of goods will carry Value Added Tax. For further details, see our Leader article.

Tulip Time Rally

The 1973 "Tulip-Time" mobile rally will be held on Sunday May 6th at Surfleet, 4 miles north of Spalding on the A16.

The Spalding and District Amateur Radio Society will also be operating a Special Activity station, GB3STF on 12th-13th May from The Grammar School, Priory Road, Spalding, in connection with the 1973 Tulip Festival. Operation will be on s.s.b./c.w. on all bands 160-10m. with a.m. on 2m. All contacts will be confirmed by special QSL cards.

Of interest to "Going Back" fans—the Wireless Preservation Society will have an exhibition of vintage radio on show to the public. I hope to be able to publish further details later.

RSGB "Jubilee Year" President



Photograph by P. M. Fletcher.

This picture shows Dr. J. A. Saxton, D.Sc., PhD, CEng, FIEE, FInstP, the new President of the RSGB. On the left of the picture is Swedish Amateur Lt. Col. Per Anders Kinman, SM5ZD, who received the Calcutta Silver Key award. Sir John Eden, the P.M.G. is on the right.

In his address, Dr. Saxton said he felt very proud that he had been chosen as President of the RSGB for its Diamond Jubilee Year. He also said that he was extremely delighted that Sir John had been able to attend and that all there were greatly honoured by his presence.

Dr. Saxton went on to say that the Society would continue to do all in its power to continue to deserve the Ministry's support.

Per Anders Kinman has been made an Honorary Vice President of the RSGB in recognition of his outstanding service with the IARU Region 1 in which he has served for many years.

The Calcutta Key he received was first presented 20 years ago and it has been awarded annually by the RSGB to the person they feel has made, in any one year, the most significant contribution to international friendship and goodwill through the medium of Amateur radio.

The Buyer and VAT

continued from previous page

If you order from a current catalogue or advertisement after April 1st, you should add the VAT percentage rate to the basic retail price shown. Then add the estimated or stated charge for postage and packing. If a service is chargeable, such as equipment repair or consultation, VAT will be levied at the standard rate. Trading in second-hand and used goods will also be taxable under VAT.

Finally, good news for P.W. readers: newspapers and magazines will be "zero-rated", which means that no VAT is chargeable on these. Transactions of any kind in the U.K. for the direct exportation of goods and services are exempt from VAT.

M. A. COLWELL—Editor.

Feb P.W. Cover

Many enquiries have been received for information on the book and log-book shown on the front cover of the February issue of *P.W.* Both can be obtained from the Radio Society of Great Britain, 35 Doughty Street, London, W.C.1. "How to Listen to the World" costs £2 post paid. The log book shown is intended for transmitting Amateurs and costs 60p post paid but another one, intended for listeners, is available at 45p post paid.

Cordless Iron

This cordless soldering iron comes from the U.S.A. It is completely portable needing no mains power for operation. It has its own power supply which is automatically charged from the stand which itself is connected to the mains. There is a small light near the tip which is very useful for seeing exactly where you are applying heat.

The iron heats up in under 5 seconds and has an "indestructible" iron-plated bit. It costs £9.25 complete with charging stand and fine bit. A heavy-duty bit is also available.

The exclusive distributors in Great Britain are *Pact International Electronics Ltd., P.O. Box 19, Royston, Herts, SG8 5HH.*



Sonex 1973

The technical author and writer Donald Aldous will be heading a small team to organise the Special Features at "Sonex '73".

Two recital/lecture sessions will be presented each day at the Exhibition's new venue the *Excelsior Hotel, London Airport, Heathrow.*

Speakers will include Bert Webb, who will lecture on pick-ups, arms and turntables and Kenneth Shearer, speaking on listening room acoustics.

There will also be a lecture on tape cassettes and an examination of current loudspeakers and trends.

Sonex '73 will run from Friday, March 30th to Sunday, April 1st, inclusive.

Sound '73

"Sound '73" is the exhibition run by the Association of Public Address Engineers. New P.A. equipment and new techniques in the public address and allied fields will be on show.

As in past years, there will be a lecture programme held in the hotel's "City Room". John Maunder from Shure Electronics will give a lecture and demonstration on microphones on Tuesday, 13th March at 14.30hrs.

Mike Beville from Audio and Design Recordings Ltd. will lecture on Components and Limiters (Wednesday at 14.30hrs.)

On Thursday March 15th at 10.30hrs, a member of the Hornsey College of Art will talk on Industrial design of Public Address Equipment.

Venue will be the Bloomsbury Centre Hotel, March 13-15, from 10.00-18.00hrs.

Jermyn Inverters

Jermyn Distribution market two inverters, both giving an output of 250V. Input for the 150W version is 12V and for the 300W type, 24V.

A feature of the design enables these inverters to charge the 12/24V batteries up to 10A when plugged into a power socket.

If the mains supply fails, the inverter automatically switches to its "invert mode" providing 240V emergency power immediately.

Should the unit be accidentally overloaded its drive is so adjusted, that the output voltage falls completely, switching the



I.E.E. Conferences

The following new conferences to be held in 1973 and 1974 are being organised by the Institution of Electrical Engineers.

"Electrical Signals from the Brain" 27-30 August 1973—in Oxford.

"Symposium on Electromagnetic Wave Theory" 8-12 July 1974—in London.

Further details of the conferences mentioned above are available from the *Conference Department, IEE, Savoy Place, London WC2R 0BL.*

De-soldering Unit

In the February issue we mentioned the Litesold De-Soldering Unit and a misprint stated the price at £.75. This should have read £2.75. Apologies to Light Soldering Developments and any readers that may have been inconvenienced.

unit off, eliminating any problems.

An internal 15A fuse blows should the battery leads be connected wrongly. Indicator lights illuminate to show whether the unit is charging a battery or providing a 250V 50Hz output.

Both types of inverter can be obtained in kit form or already built. The kit for 150W costs £25 (£29 built) and 300W £34 (£39 built). *Jermyn Distribution, Vestry Estate, Sevenoaks, Kent.*



improving VHF radio

A.N. AINSLIE



VHF radio provides a most useful signal source for any hi-fi enthusiast and, despite the 15 kHz frequency limits, the live BBC broadcasts are certainly up to the standards of the finest records.

The advantages are numerous—being a non-mechanical system the distortion is very low and the self-generated noise is also very low, the result being a large dynamic range and the possibility of encoding two channels on a single signal. This, plus the excellent BBC technique, makes f.m. radio an invaluable source of material. Unfortunately there are several difficulties in securing top quality f.m., regardless of the equipment used.

SIGNAL-TO-NOISE

Referring to Fig. 1, it can be seen that the performance of a receiver depends on the strength of the signal applied to the aerial socket of the receiver. The mono signal-to-noise ratio assumes an optimum value (usually 50 or 60 dB) with only a few μV input—even on cheap tuners. The signal-to-noise performance does not improve so rapidly on stereo, however, and in many cases could be improved on even with inputs in the region of a few hundred μV —hence the increase in noise on stereo

in most situations. A person who gets no increase in noise is indeed most fortunate and need read no further!

As regards crosstalk and distortion, these parameters usually reach optimum values with fairly small inputs and usually there is not much improvement to be had by an increase in the signal.

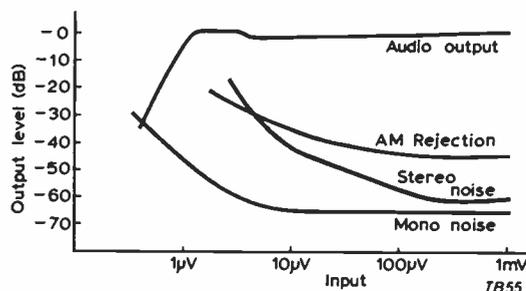



Fig. 1: Graphs comparing receiver performance with the input signal level.

Very few people are fortunate enough to be able to receive "near perfect" stereo without a large aerial, loft or roof mounted. A large aerial, besides having the necessary gain usually has the advantage that it is highly directional and eliminates multipath distortion from reflected signals. In many situations, a reasonably large aerial, three or more elements, carefully sited, and with a low loss feeder gives good stereo but perhaps not of the very highest quality.

The major downfall in domestic stereo reception is that of "stereo" noise—perhaps not excessive but sufficient to mar an otherwise excellent signal. The obvious way to reduce this noise is to increase the signal feeding the tuner by an "aerial amplifier". At present in this discussion we must assume that the amplifier be perfect, having gain but generating no noise itself.

OTHER NOISE

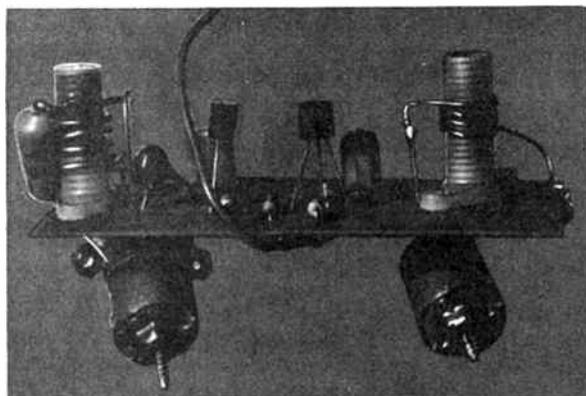At this point many readers may well be wondering about the other forms of noise, thermostats, car ignition and other spurious signals. These signals



First of the two VHF amplifiers described in the article. This one uses field-effect transistors.

are picked up by the aerial and sometimes, even, by the feeder, and consequently will be amplified, together with the f.m. signal, by our "ideal" amplifier, which we are using to combat stereo noise. This brings us to the last important parameter of f.m. receivers, amplitude modulation limiting.

The "ideal" f.m. tuner is designed to respond to f.m. only and a.m. signals are rejected to an infinite degree. Unfortunately, no receiver is perfect and some degree of sensitivity to a.m. is unavoidable.

The a.m. limiting of the receiver improves with increasing signal input, as seen from Fig. 1, so that increasing the signal and spurious a.m. together actually reduces the level of audible interference. Unfortunately, when the receiver is switched to receive a stereo transmission, the stereo decoder in the receiver is actually only sensitive to amplitude modulation of the stereo subcarrier. In the decoder some measure of a.g.c. is applied to the subcarrier amplifier and this maintains a constant level of stereo interference from an a.m. signal regardless of the actual input voltage to the tuner.

It can therefore be seen that whilst increasing the tuner input with an "ideal" amplifier, the "stereo" interference level remains substantially constant whilst the "mono" component of the audible interference has been reduced by virtue of the amplitude limiting of the f.m. discriminator.

AERIALS

Earlier in this discussion, we talked of elaborate and efficient aerial systems but the previous discussion on aerial signal amplification implies that, with a good amplifier, an aerial providing only a minimal "clean" signal can be used to run an f.m. tuner with a high degree of success.

Unfortunately, some tuners are not so sensitive as others and sometimes require millivolts to function at their best. This means considerable amplification of the few tens of microvolts coming from a rather poor aerial!

The better tuners nowadays use f.e.t.'s in the input circuits to keep noise to a minimum and to keep cross modulation low; so any proposed amplifier should have at least as good a performance as the front end of the tuner.

This is very demanding when tuners such as Sony, Radford and Fisher are considered, but it is possible to improve these tuners on a very poor signal by a remarkable degree.

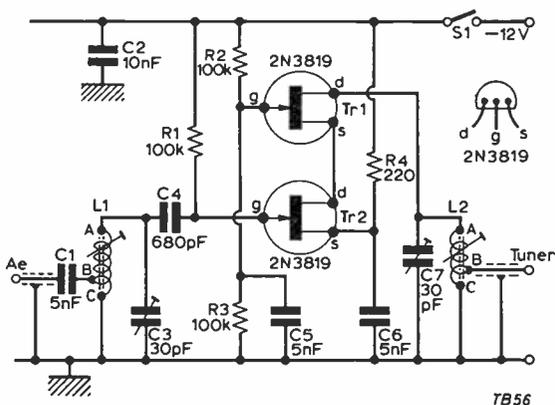


Fig. 2: Circuit of the amplifier using two f.e.t.'s.

To design an amplifier with a front-end comparable to the best tuners use has to made of f.c.t. devices which possess the best noise properties of all the common solid state devices presently available and are responsible for the excellent performance of the best tuners.

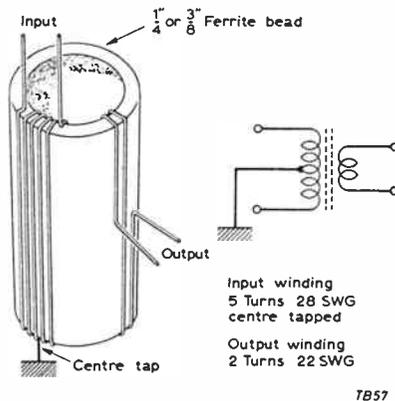


Fig. 3: Details of simple transformer to match balanced 400Ω feeder to 75Ω coaxial feeder.

The design chosen for the amplifiers in this article is not often used with solid state devices but was once very common with valve Band III television tuners. The amplifier is a cascode configuration giving reasonable gain with very low noise and good cross modulation.

The input to the amplifier, Fig. 2, is 75Ω co-axial feeder so Fig. 3 shows a transformer that can be constructed from a small ferrite bead for 400Ω balanced feeder.

THE PCB


The amplifier can be very easily built on a single piece of printed circuit 4"×2" and it is recommended that fibreglass board be used.

To etch the required print design as shown in Fig. 4 (full size), the diagram is traced on to the copper side of the print with carbon paper and the marked areas painted in with high quality enamel. When the paint is dry, the print is immersed in the etching solution and agitated until completely etched (only paint and base material can be seen). The etching solution can be ferric chloride solution but a useful alternative is "Liquor-Ferri Perchloridi Fort" which is obtainable from chemists and should be used undiluted. Rub the copper surface of the board with "Ajax" or similar scourer before painting, to ensure a clean surface.


The enamel paint can be removed with paint stripper once the etching is complete and the board washed and cleaned with wire-wool. The holes for the components should be drilled with a 1/32" drill, preferably in a wheel brace.

Construction is straightforward except that the f.e.t.'s should be left until last and soldered in with the iron disconnected from the mains—surprisingly little voltage will break down the gate junction.

The coils, Fig. 5, are wound on the formers which are located on the board and stuck with Araldite. The 30pF variable capacitors must be connected so that the rotor is connected to the earth line. The author used 30pF Philips beehive trimmers mounted

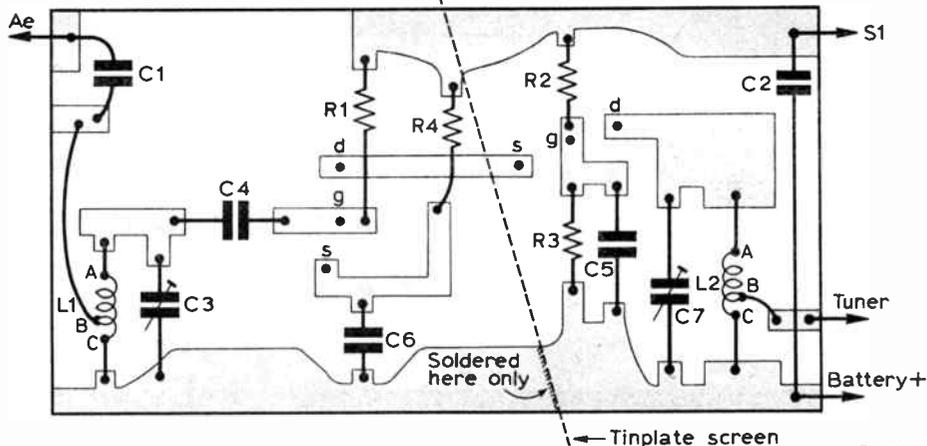

TB58

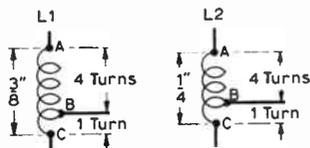

Note:
L1 and L2 both
wound on $\frac{1}{4}$ " Dia
formers using
18 SWG copper
wire

TB59

Fig. 5: Winding information for L1 and L2.

Fig. 4: Printed circuit board, for the circuit of Fig. 2, shown actual size.

★ components list

FET AMPLIFIER

Resistors

R1 100k Ω R2 100k Ω R3 100k Ω R4 220 Ω
All \pm W 5%

Capacitors

C1 5nF 400V C5 5nF 12V
C2 10nF 12V C6 5nF 12V
C3 30pF Trimmer C7 30pF Trimmer
C4 680pF 12V

Miscellaneous

Tr1-Tr2, 2N3819. On-off switch. 12V battery. Co-axial sockets (2). PCB, see text. Coil formers.

BF200 AMPLIFIER

Resistors

R1 1.5k Ω R3 6.8k Ω R5 10k Ω
R2 10k Ω R4 1.5k Ω R6 6.8k Ω
All \pm W 5%

Capacitors

C1 1nF 400V C6 30pF Trimmer
C2 30pF Trimmer C7 10nF 12V
C3 19nF 12V C8 680pF 12V
C4 680pF 12V C9 1nF Feed-through
C5 1nF Feed-through C10 30pF Trimmer

Miscellaneous

Tr1-Tr2, BF200. On-off switch. 12V battery. Co-axial sockets (2). PCB, see text. Coil formers.

POWER SUPPLY

Capacitors

C1 100nF 1kV C3 2000 μ F 10V C5 100nF 12V
C2 2000 μ F 10V C4 1000 μ F 15V

Miscellaneous

R1, 10 Ω \pm W 5%. D1-D2, 1N4002. D3, 12V zener 2W, mounted on aluminium 2" \times 1" minimum. T1, 8V bell transformer. Fuse, 1A. On-off DP mains switch. LP1, 3.5V 20mA for FET amp + 2 stages or 3.5V 40mA for FET amp + 4 stages.

on the copper side of the board. The resistors should be small low noise types and the capacitors need only be low working voltage.

The completed amplifier should be screened by placing tin plate at the position indicated and soldered to the positive line as support.

The amplifier is mounted in a small wooden box, measuring approx. 4" cube internally, covered inside with tin foil, which is connected to the positive supply line. A front panel can be made from a piece of double-sided copper board with the input and output sockets and the on/off switch. The printed board is soldered to the front panel by the positive line, so earthing the front panel.

With a 12V battery connected, the output is fed to the tuner and the input is fed by an "inefficient" aerial, in most cases a short piece of wire.

With the amplifier on, the tuner is switched to the local stereo station and the tuning capacitors C3 and C7 set midway. The cores of the coils (L1 and L2) are then adjusted to give the strongest signal, best observed on a tuning meter or audibly by judging least noise.

The amplifier is then assembled in the case and the capacitors C3 and C7 tuned to give the best signal. The tuning will be sharp and critical, so care should be taken when adjusting.

The amplifier, when connected between the proper aerial and tuner, should have sufficient gain to overcome most of the tuner noise, without introducing significant noise itself. When used on weak local radio stations, the improvement will be very marked, especially in mono. Unfortunately, this usually requires the amplifier to be re-tuned to the local channels. However, connecting 27 Ω resistors across L1 and L2 will broaden the bandwidth considerably, enabling the amplifier to be used over a number of channels.

BF200 AMPLIFIER

However, for many of the "poorer" tuners, this amplifier will still not be good enough to fully drive the tuner on a moderate signal. For optimum stereo in such cases two of the amplifiers could be

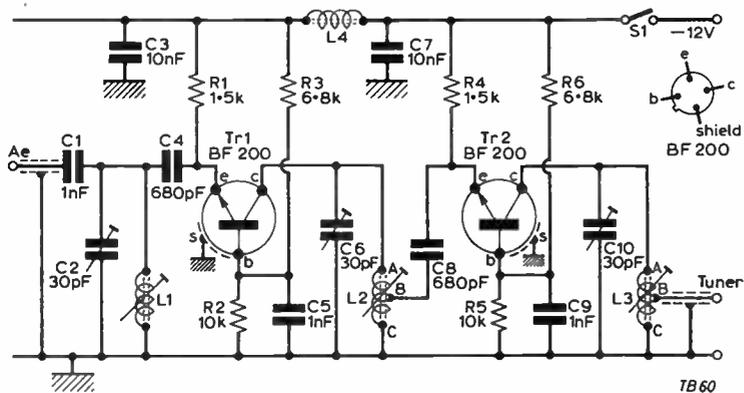


Fig. 6: Circuit of the second amplifier, using BF200 transistors.

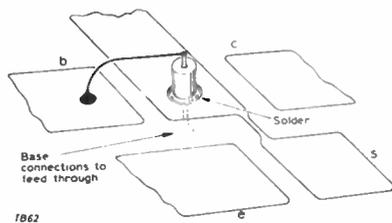


Fig. 8 Method of mounting feed-through capacitors

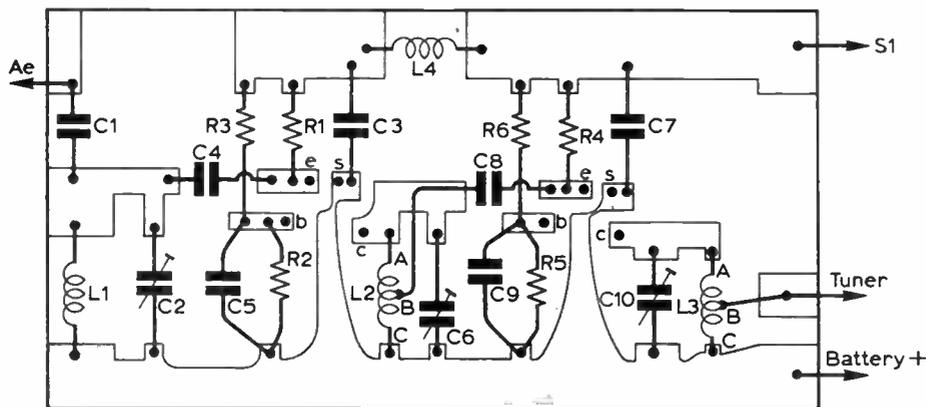


Fig. 7: Illustration, actual size, of the printed circuit board for the BF200 amplifier.


connected in series. The price of f.e.t.'s, however, makes this uneconomical and ordinary low-noise silicon transistors used after the f.e.t.'s work very well. The proposed r.f. amplifier, Fig. 6, is two stages of a conventional r.f. amplifier design. Fig. 7 shows a full size print layout for two stages, although for additional gain or bandwidth more stages can be used, although greater than five would be difficult to keep stable.

The board is etched in the same manner as before and a similar front panel and box are prepared. Alignment is the same, tuning the coils and finishing with the capacitors.

The transistors specified are BF200 and these should be used for at least the first two stages to keep the noise level down; after this such transistors as 2N706 work very well. An alternative for the BF200 is BF180 or BF181.

Fig. 8 shows how C5 and C9 are constructed with 1000pF feed-through capacitors. L4 is made by wrapping a few turns of 36s.w.g. d.c.c. copper wire round a ferrite bead. Fig. 9 gives the winding information for L1, L2 and L3.


The two amplifiers just described will enable good stereo to be obtained from a mediocre signal without the need for a "fancy" tuner. The improvement that can be expected depends greatly on the individual circumstances. The author has used the amplifiers with a Sony ST5100 tuner and a poor aerial and found the results almost as good as when a proper aerial was correctly installed on the roof. The cost of a pair of amplifiers is comparable to a decent

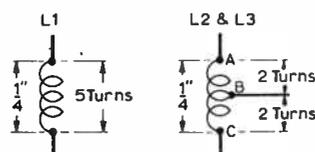

Note:
L1 L2 & L3 wound on 1/4" Dia formers.
L1 use 22 SWG copper wire.
L2 & L3 use 18 SWG copper wire.

TB63


Fig. 9: (above) Details of the three coils shown in Fig. 6. In the photograph (below) the second amplifier board is shown soldered to the front panel consisting of double-sided p.c.b.

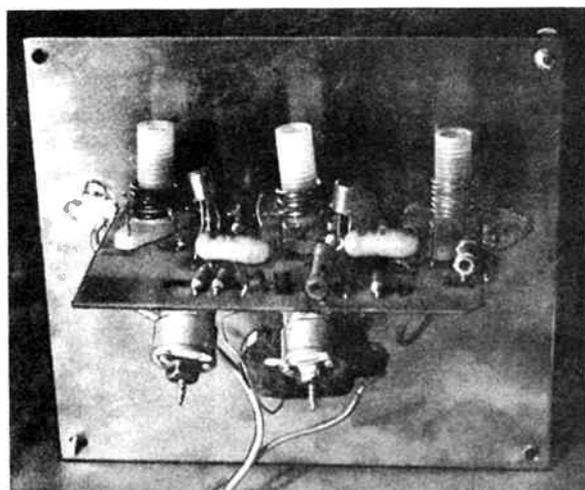

aerial less downlead and fitting, so financially it is a viable proposition, although not a substitute for a first class aerial.

In order to split one signal to run several outlets and obtain maximum signal at each of the outlets, a star-splitter is used. This arrangement provides correct impedance matching throughout the system.

Figure 10 shows the circuit of a star-splitter. The value of the resistors R depends upon the impedance of the feeders (Z) usually 75Ω, and on the number of outlets (n) which can be as many as required.

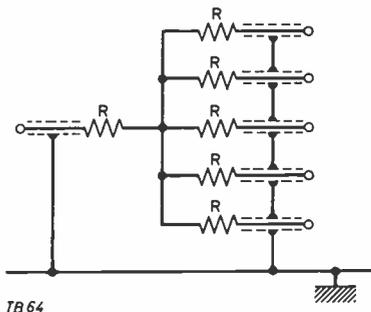


TB 64

Fig. 10: Circuit of star-splitter enabling several outputs to be obtained from a single input.

The relationship is:— $R = Z(n-1)/n + 1$. For example, for a splitter for a 75Ω system with two outputs the resistors to the nearest preferred value are 27Ω. Small 1/4W resistors are suitable and indeed preferable to physically larger types.

All of these systems involve a loss of signal and this must be made up by amplification before the splitting. For a distribution system, splitting six or

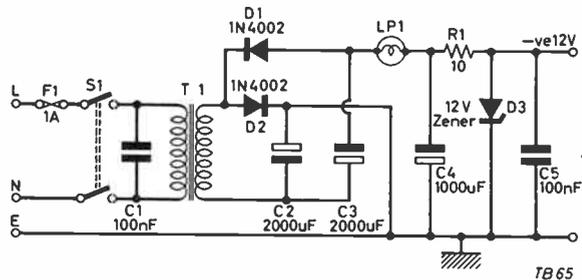

TB 65

Fig. 11: Suggested power supply for the v.h.f. amplifiers.


eight ways, two f.e.t.'s followed by three transistors should be adequate. One important point to note is that the outputs of the splitter must all be loaded by a 75Ω resistor when not in use, otherwise a loss of signal results and the splitter may form the node of standing waves in the feeder.

If either of the amplifiers is built as a distribution system, it is perhaps a good idea to build a small mains unit to power the whole system. It is desirable that this supply be stabilised to guard against changes in the tuning of the f.e.t.'s if the supply voltage changes.

Fig. 11 gives a circuit of a simple power supply based on an 8V bell transformer with voltage doubling and zener stabilisation. The lamp, LP1, can be used to give on/off indication.

It is hoped that this article has given sufficient information for the home constructor to build an amplifier system to improve the performance of a tuner to reach the very high standards of the B.B.C. stereo transmissions. ■

EXPERIMENTERS CORNER

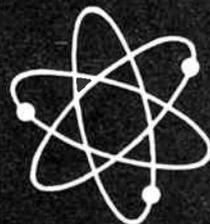


NOVEL TONE GENERATOR

WHENEVER home constructors and experimenters need to build a source of audio frequency, the choice nowadays is usually a transistor multivibrator. The reasons for this selection are easily understood. It requires few components, avoids the need for a transformer and gives a strong output signal. These virtues outweigh the fact that the square-wave output does not make for a particularly pleasing sound when amplified and fed to a loudspeaker.

In designing the a.f. tone generator to be described, the author set out to devise a circuit which would possess all the aforementioned merits of the multivibrator and at the same time give a better audio tone. In the circuit shown in Fig. 1—which, as a transistor circuit, is thought to be original—the writer believes these objectives have been largely achieved.

N. NAUGHTON

It will be noticed that the circuit is actually simpler than a multivibrator and basically it is a sawtooth generator. Like all sawtooth generators it depends upon the charge and discharge times of a

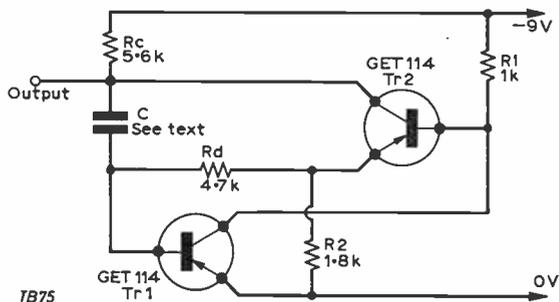

TB 75

Fig. 1; Circuit of tone generator.

capacitor for its action. But as linearity of the sawtooth ramp is not important for the required purpose, the provision of constant current is omitted in the circuit shown.

In Fig. 1 the two transistors perform the function of switches and the circuit operates as follows:— capacitor C charges via the charging resistor R_c and the base-emitter junction of Tr1. The charging current flowing through the B-E junction turns on Tr1 and the flow of collector current causes a voltage drop across R1 which results in the potential on the base of Tr2 dropping to a level low enough to turn off Tr2. As the charge on C rises the charging current diminishes so that the potential on the base of Tr1 decreases to a point where Tr1 turns off. The base of Tr2 now goes strongly negative causing Tr2 to turn on and C now discharges via Tr2 into the discharge resistor R_d. While discharge current is flowing in R_d it maintains a positive potential on the base of Tr1 thus preventing further switching action during the period of discharge. When C has discharged, it again draws current through Tr1 once again turning off Tr2. The cycle then repeats.

The foregoing is a simplified description of the operation but many will find it interesting to measure the balance of currents and potentials which exist in the circuit under static conditions when C is removed.

The frequency of oscillation is not readily calculated since it is influenced by several factors one of which will be determined by the type of coupling employed to connect the output. However, for practical purposes values of C ranging between 2 μ F and 5000pF will cover the audio spectrum.

APPLICATIONS

A useful feature of the circuit is that it uses only one capacitor. With the values given, the generator should oscillate at any point within the a.f. range the actual point being determined by the value of C selected. Thus it becomes a simple matter to construct a signal generator giving a number of spot frequencies as desired; the only extra components needed being a multi-pole switch and a few capacitors. Many other audio applications will doubtless occur to readers.

For those interested, an interesting feature of the circuit is that because the charge and discharge paths of C are independent, the circuit can readily be made to produce right-handed or left-handed sawtooth waveforms. Moreover, by choice of p.n.p. or n.p.n. transistors, the polarity of either slope can be created as desired at source, thereby eliminating inverting stages. Although some value of R_d is essential for circuit function, in practice this can be less than 100 Ω thus allowing fast flyback times. There is no reason why C can not be a very large value electrolytic so that the circuit can easily be adapted for timing application.

GENERAL

No constructional details are given since the generator will mostly be incorporated in some larger project. Experimenters can assemble the components on a length of Veroboard or tagboard.

As stated at the outset, the circuit is primarily intended as an a.f. generator and the values given have been chosen to give a roughly pyramid waveform at the collector of Tr2. A strong output signal is also available at the collector of Tr1 but this is a

steep sided pulse and the "softer" toned signal at the Tr2 output can be readily appreciated. Coupling of the output is perhaps best determined to suit the individual case but too tight a coupling to the Tr2 output is best avoided. This is less important if the Tr1 output is used.

With the component values given, the circuit places no critical demands on the transistors' characteristics. Seven widely differing types, in various combinations, have been tried with success. However, experimenters using low values of R_d—especially with a high value of C—should note that Tr2 must then be a device capable of handling the heavier discharge current. Tr1 and Tr2 must both be either p.n.p.'s or n.p.n.'s, the -9V becoming +9V if n.p.n.'s are used. ■

TELEVISION

APRIL ISSUE

TOUCH TUNING

The latest development in television receiver design is touch-sensitive tuning, using touch-button units which provide a completely non-mechanical means of channel changing. A very high-impedance electronic switching circuit selects the required channel when a finger is placed across a pair of contacts to complete the appropriate circuit. Several models featuring touch tuning are now on the market and this month we are investigating the technique and the circuitry involved. The change from mechanical to all-electronic channel selection should improve the stability and reliability of TV tuning.

BAND III PREAMPLIFIER

Another Bunney wideband aerial amplifier intended for DX work. The two-transistor (BF272) design on test lifted a weak signal from mere traces of line sync pulses to a solidly locked noisy image. Part of Roger's present programme of improving his DX receiving equipment.

SERVICING

Plenty on the servicing front this month. John Law in his new fault-finding series investigates the line timebase used in most KB-STC models. Vivian Capel completes his guide to power supply circuit servicing. Les Lawry-Johns starts on the single-standard **Bush-Murphy TV181S/V2016** series. And Caleb Bradley takes us further with the BRC 2000 colour chassis.

PLUS ALL THE REGULAR FEATURES

ON SALE MARCH 19

IC POWER AMPLIFIER



D. SILVESTER

THE audio amplifier to be described was designed to deliver in excess of 10W r.m.s. into an 8Ω load, whilst being constructed in a 4½in. x 3½in. x 2in. diecast aluminium box. The size of the box is, in fact, limited not by the size of the i.c. but by the passive components, especially the output capacitor which must be included in the circuit. The use of the i.c. has added one inestimable advantage in that the current through (and the power dissipated by) the output stage under overload conditions can be limited. It is thus possible for the output to be short circuited without disastrous results.

The i.c., although capable of giving a 1 watt output without any other transistors, has been primarily designed for use as the driver stage of an amplifier

capable of delivering up to 35 watts into an 8Ω load.

A description of the working of the i.c. has not been included as it is not necessary for the constructor to completely understand the operation of the device for it to be used successfully.

Two transistors in the i.c. are responsible for the current and power limiting facility. It was calculated that under maximum current limiting and with the normal current gain of a power transistor, the output stage of the i.c. would be overloaded. One way of curing this fault is to use a Darlington transistor. This in fact was done, the Darlington pair being contained in the TO3 metal case of the power transistor. The current gain of the complementary Darlington pairs is in excess of 1000.

CALCULATIONS

The final circuit used for the prototype amplifier is shown in Fig. 1 but since other constructors may wish to use different power supply voltages and load impedances from those used by the author, the method of calculation of the current and power limiting components is given. The basic circuit should be adhered to as it is only the values of R6, R8, R9 and R11 which need to be changed.

The following section shows the worked equations used to give the value of the components in Fig. 1.

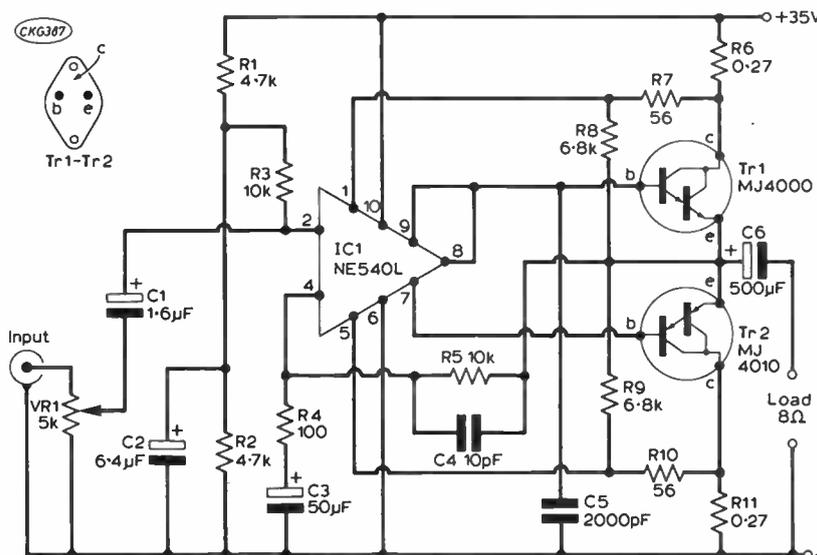


Fig. 1: Circuit diagram of the amplifier and pin connections for the output transistors.

is this the price you pay?

Probably, if you're still using an ordinary soldering iron. Ordinary soldering irons can cause damage to transistors and integrated circuits — damage which wastes time and costs money. Now, with the unique ANTEX X25 and CCN low leakage soldering irons no harm can come to the most delicate equipment, even when soldered 'Live'.

(You could be making quite a saving).



MODEL X25


220-240 Volts or 100-120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C.

This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally-made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed.

PRICE: £1.75 (rec. retail)

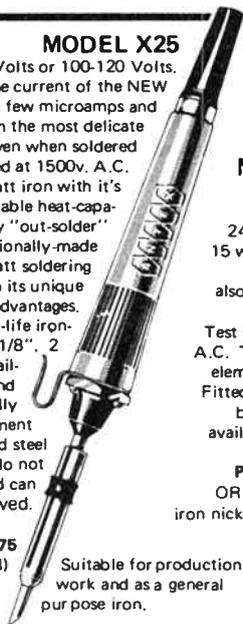Suitable for production work and as a general purpose iron.



MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage.

Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".

PRICE: £1.80 (rec. retail) OR Fitted with triple-coated, iron nickel and Chromium bit 1/8".

PRICE: £1.95 (rec. retail)



MODEL G

18 watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110. PRICE: £1.83 (rec. retail).



MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24.

PRICE: £1.70 (rec. retail)

MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.

PRICE: £1.70 (rec. retail)



MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE: £2.40 (rec. retail)



MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE: £2.75 (rec. retail)



MODEL MES.KIT

Battery-operated 12v. 25 watt iron fitted with 15" lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder"

PRICE: £1.95 (rec. retail)



From radio or electrical dealers, car accessory shops or in case of difficulty direct from:—
ANTEX LTD. FREEPOST
 (no stamp required) PLYMOUTH.
 PL1 1BR Tel: 0752 67377.

- Please send the ANTEX colour catalogue.
- Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME

ADDRESS

PW4

BRAND NEW SEMICONDUCTORS & COMPONENTS GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS

2G801	0-15	2N2924	0-18	2N5174	0-28	AF116	0-25	BC307	0-10	BF271	0-21
2G302	0-15	2N2925	0-18	2N5175	0-28	AF117	0-25	BC307A	0-10	BF272	0-21
2G303	0-25	2N2926	0-18	2N5176	0-28	AF121	0-28	BC308	0-09	BF274	0-28
2G306	0-80	Green	0-10	2N5245	0-48	AF125	0-20	BC308B	0-09	BF466	0-67
2G309	0-80	Yellow	0-10	2N5190	0-28	AF126	0-19	BC309	0-10	BF469	0-67
2G344A	0-25	Orange	0-10	2N5191	0-28	AF127	0-20	BC309A	0-10	BF521	2-10
2G345B	0-25	Orange	0-10	2N5192	1-94	AF139	0-28	BC309B	0-10	BF521A	2-10
2G371	0-15	2N3054	0-47	2N5193	1-01	AF170	0-25	BC313	0-20	BF828	0-98
2G374	0-15	2N3064	0-46	2N5194	1-10	AF172	0-25	BC327	0-24	BF861	0-27
2G381	0-22	2N3065	0-50	2N5195	1-46	AF178	0-25	BC328	0-24	BF898	0-28
2G417	0-20	2N3390	0-20	2N5245	0-48	AF179	0-25	BC337	0-19	BFW10	0-21
2N109	0-49	2N3391	0-20	2N5467	0-80	AF180	0-60	BC338	0-19	BFW11	0-21
2N174	1-40	2N3391A	0-22	2N5468	0-82	AF186	0-60	BCY30	0-25	BFY06	0-25
2N176	0-75	2N3392	0-18	2N5469	0-83	AF200	0-85	BCY31	0-20	BFY13	0-23
2N274	0-75	2N3393	0-18	3N128	0-88	AF239	0-41	BCY32	0-60	BFY29	0-25
2N335	0-75	2N3394	0-18	3N138	1-87	AF240	0-73	BCY32	0-75	BFY30	0-25
2N451	0-95	2N3402	0-17	3N199	1-86	AF279	0-54	BCY33	0-24	BFY37	0-20
2N376	1-00	2N3403	0-19	3N140	0-78	AF280	0-64	BCY34	0-25	BFY44	0-23
2N384	0-98	2N3404	0-24	3N141	0-89	AFY42	0-74	BCY35	0-40	BFY45	0-23
2N388A	0-20	2N3415	0-10	3N142	0-54	AFY21	0-55	BCY35	0-40	BFY68	0-20
2N404	0-23	2N3414	0-10	3N143	0-84	AL102	0-75	BCY40	0-50	BFY84	0-24
2N404	0-20	2N3415	0-10	3N152	0-79	AL103	0-70	BCY42	0-15	BFY85	0-29
2N456	0-75	2N3416	0-15	3N153	0-74	ABY26	0-80	BCY43	0-15	BFY86	0-24
2N456A	0-75	2N3417	0-21	3N154	0-74	ABY27	0-80	BCY68	0-21	BFY87	0-25
2N457A	0-80	2N3570	1-25	3N159	1-00	ABY28	0-88	BCY69	0-22	BFY88	0-20
2N491	0-25	2N3571	1-18	3N187	1-34	ABY29	0-88	BCY70	0-22	BFY10	0-25
2N584	0-26	2N3572	0-97	3N200	3-07	ABY29	0-88	BCY67	0-94	BFY10	0-25
2N691	0-84	2N3702	0-10	3N201	1-05	ABY56	0-85	BCY70	0-17	BFY11	0-45
2N696	0-15	2N3703	0-10		AS221	0-55	BCY71	0-22	BFY17	0-90	
2N697	0-15	2N3704	0-10	40050	0-78	AL103	1-25	BCY72	0-18	BFY18	0-25
2N698	0-25	2N3705	0-10	40051	0-81	BC107	0-14	BCY87	8-47	BFY19	0-25
2N699	0-25	2N3706	0-10	40052	0-82	BC108	0-14	BCY88	8-47	BFY20	0-25
2N706	0-10	2N3707	0-10	40309	0-83	BC109	0-14	BCY89	8-47	BFY21	0-25
2N706A	0-12	2N3708	0-70	40310	0-80	BC113	0-18	BCZ10	0-85	BFY27	0-20
2N708	0-18	2N3709	0-90	40313	0-92	BC114	0-18	BCZ11	0-50	BFY41	0-48
2N709	0-88	2N3710	0-90	40316	0-92	BC115	0-16	BD115	0-75	BFY43	0-62
2N711	0-20	2N3711	0-90	40322	0-92	BC118	0-16	BD116	0-75	BFY60	0-18
2N718	0-21	2N3712	0-86	40323	0-92	BC119A	0-18	BD117	0-75	BFY60	0-18
2N718A	0-20	2N3713	0-95	40360	0-46	BC119	0-21	BD123	0-28	BFY62	0-18
2N720	0-50	2N3714	1-18	40361	0-48	BC118	0-11	BD124	0-67	BFY63	0-15
2N721	0-55	2N3715	1-25	40362	0-44	BC119	0-27	BD130	0-57	BFY66	0-24
2N914	0-15	2N3716	1-25	40363	0-53	BC121	0-28	BD131	0-40	BFY64	0-41
2N916	0-17	2N3773	3-35	40394	0-86	BC123	0-29	BD132	0-50	BFY76	0-40
2N918	0-80	2N3774	3-38	40395	0-80	BC125	0-15	BD135	0-48	BFY78	0-22
2N919	0-20	2N3775	3-38	40396	0-80	BC126	0-15	BD136	0-48	BFY77	0-24
2N929	0-14	2N3776	5-95	40405	0-44	BC132	0-20	BD137	0-55	BFY78	0-28
2N930	0-14	2N3777	4-84	40407	0-28	BC134	0-11	BD138	0-63	BFY90	0-60
2N1090	0-22	2N3778	3-25	40408	0-50	BC136	0-11	BD139	0-71	BRX39	0-80
2N1091	0-24	2N3779	3-15	40410	0-53	BC138	0-15	BD140	0-88	BRX19	0-18
2N1131	0-20	2N3780	4-10	40411	2-00	BC137	0-16	BDY10	1-25	BRX20	0-14
2N1132	0-20	2N3781	3-87	40412	1-84	BC138A	0-18	BDY11	1-50	BRX21	0-80
2N1184	0-20	2N3782	3-87	40414	3-85	BC140	0-34	BDY17	1-50	BRX28	0-24
2N1302	0-16	2N3789	1-76	40438	1-44	BC141	0-49	BDY18	1-75	BRX27	0-24
2N1303	0-16	2N3790	1-90	40467A	0-49	BC142	0-24	BDY19	1-97	BRX28	0-25
2N1304	0-20	2N3791	3-06	40468A	0-49	BC143	0-21	BDY20	0-98	BRX29	0-47
2N1306	0-20	2N3792	3-20	40601	0-67	BC144	0-24	BDY38	0-65	BRX30	0-68
2N1306	0-22	2N3794	3-10	40602	0-46	BC147	0-46	BDY50	0-90	BRX59	0-78
2N1307	0-20	2N3795	3-10	40603	0-46	BC147	0-46	BDY61	0-90	BRX60	0-78
2N1308	0-25	2N3820	0-47	40603	0-68	BC148	0-10	BDY62	0-75	BRX61	0-42
2N1309	0-25	2N3823	0-60	40604	0-68	BC149	0-18	BF115	0-23	BRX76	0-15
2N1483	0-90	2N3824	0-75	40673	1-10	BC153	0-18	BF117	0-48	BRX77	0-20
2N1487	0-24	2N3826	0-28	AC107	0-85	BC154	0-18	BF119	0-58	AX78	0-25
2N1613	0-20	2N3854	0-16	AC113	0-16	BC157	0-14	BF121	0-25	BBW70	0-28
2N1631	0-20	2N3854A	0-16	AC115	0-16	BC158	0-14	BF122	0-25	BBW74	0-20
2N1637	0-80	2N3856	0-16	AC116	0-16	BC159	0-14	BF125	0-25	BBY24	0-20
2N1638	0-27	2N3856A	0-16	AC117	0-20	BC160	0-27	BF127	0-27	BBY26	0-20
2N1671	1-00	2N3856	0-16	AC120	0-18	BC167B	0-11	BF152	0-20	BBY27	0-15
2N1701	1-10	2N3856A	0-16	AC127	0-20	BC168B	0-13	BF163	0-20	BBY28	0-15
2N1702	3-15	2N3858	0-16	AC128	0-20	BC168C	0-11	BF164	0-18	BBY38	0-18
2N1711	0-17	2N3858A	0-16	AC129	0-13	BC169	0-13	BF165	0-18	BBY39	0-15
2N1712	0-18	2N3859	0-16	AC141K	0-80	BC169C	0-13	BF169	0-27	BBY61	0-25
2N2102	0-80	2N3859A	0-16	AC142K	0-25	BC170	0-11	BF160	0-23	BBY62	0-25
2N2147	0-70	2N3860	0-16	AC181V	0-14	BC171	0-18	BF161	0-25	BBY63	0-25
2N2148	0-60	2N3866	0-70	AC152V	0-66	BC172	0-11	BF163	0-20	BBY84	0-30
2N2192	0-40	2N3877	0-25	AC153K	0-25	BC182	0-10	BF166	0-25	BBY66	0-19
2N2192A	0-40	2N3877A	0-25	AC154	0-20	BC183	0-09	BF167	0-18	BBY68	0-20
2N2193	0-40	2N3878	1-25	AC176	0-18	BC183L	0-09	BF177	0-25	BBY79	0-45
2N2193A	0-42	2N3878A	0-91	AC178K	0-20	BC184	0-11	BF178	0-25	BBY90	0-40
2N2194	0-27	2N3900	0-21	AC187K	0-20	BC184L	0-11	BF179	0-30	BBY95A	0-09
2N2194A	0-80	2N3900A	0-21	AC188K	0-25	BC186	0-25	BF180	0-25	BU104	0-10
2N2196	0-87	2N3901	0-28	AC17	0-25	BC187	0-25	BF181	0-25	BU105	0-25
2N2196A	0-18	2N3903	0-20	ACY18	0-15	BC204	0-11	BF182	0-80	C111	0-58
2N2198	0-80	2N3904	0-17	ACY19	0-20	BC205	0-10	BF183	0-40	D40N3	0-25
2N2219	0-87	2N3905	0-21	ACY20	0-20	BC206	0-11	BF184	0-17	GET111	0-45
2N2219A	0-51	2N3906	0-22	ACY21	0-18	BC207	0-10	BF185	0-17	GET112	0-20
2N2220	0-20	2N4038	0-68	ACY22	0-13	BC208	0-09	BF194	0-14	GET114	0-20
2N2221	0-20	2N4037	0-42	ACY28	0-18	BC209	0-09	BF195	0-15	GET115	0-50
2N2221A	0-35	2N4038	0-18	ACY30	0-42	BC211	0-08	BF196	0-15	GET119	0-25
2N2222	0-31	2N4059	0-90	ACY39	0-55	BC212K	0-10	BF197	0-15	GET120	0-25
2N2222A	0-41	2N4060	0-11	ACY40	0-17	BC212L	0-12	BF198	0-15	GET125	0-20
2N2368	0-11	2N4061	0-11	ACY44	0-17	BC214L	0-14	BF199	0-18	GET136	0-20
2N2369	0-80	2N4062	0-11	ACY44A	0-17	BC214L	0-14	BF199	0-18	GET136	0-20
2N2369A	0-17	2N4302	0-25	AD138V	0-96	BC238	0-16	BF200	0-25	GET138	0-20
2N2648	0-41	2N4303	0-88	AD140	0-50	BC237	0-09	BF224J	0-14	GET138	0-20
2N2647	1-20	2N4313	0-20	AD140	0-55	BC239	0-09	BF224K	0-14	GET137	0-12
2N2711	0-12	2N4314	0-20	AD142	0-50	BC251	0-20	BF238	0-22	GET180	0-20
2N2712	0-12	2N4315	0-25	AD143	0-45	BC252	0-18	BF244	0-12	GET180	0-20
2N2713	0-17	2N4316	0-11	AD149V	0-86	BC253	0-23	BF245	0-23	GET189	0-22
2N2714	0-17	2N4317	0-17	AD149V	1-28	BC257	0-29	BF246	0-23	GET189	0-22
2N2904	0-18	2N4318	0-50	AD150	0-63	BC257	0-29	BF247	0-29	GET189	0-22
2N2904A	0-25	2N4319	0-58	AD161	0-87	BC259	0-18	BF248	0-14	GET189	0-22
2N2905	0-20	2N43									

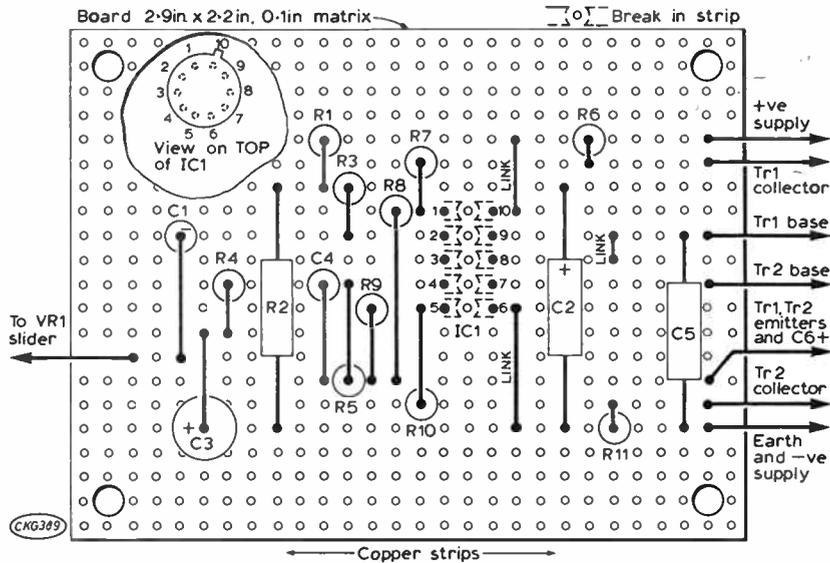


Fig. 3 Component layout on top of veroboard, the copper strips running horizontally underneath.


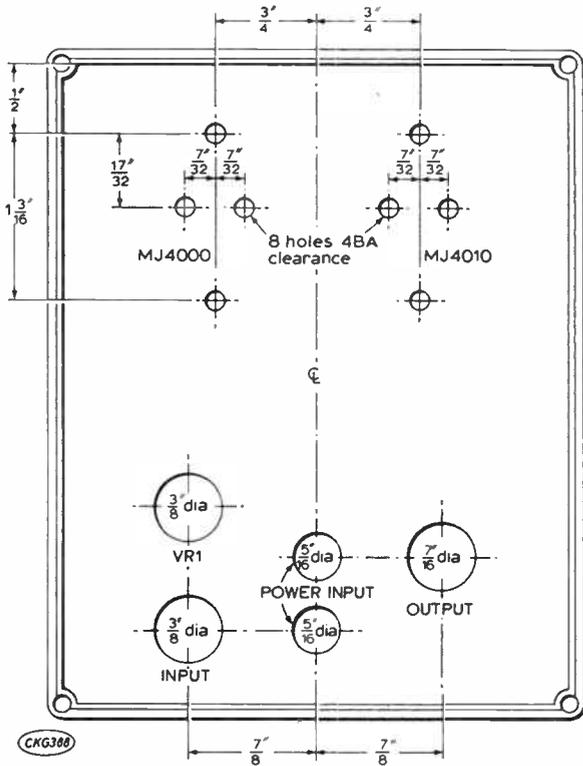


Fig. 2: Drilling details for the box lid on which components are mounted

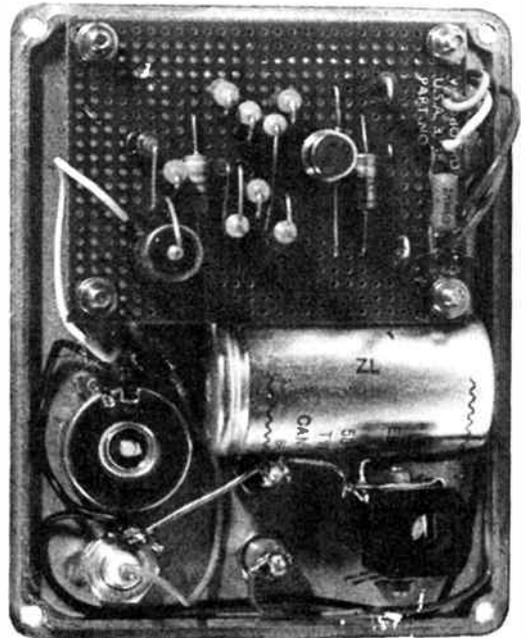They are based on a supply voltage (V_{cc}) of 35V and a loudspeaker impedance of 8Ω (R_L). Before beginning the calculations it must be remembered that there are two limitations imposed by the active devices used; the supply voltage must be in the range 10 to 40V, and the maximum current through the transistors Tr1, Tr2 must not exceed 4A. We can calculate:



This view of the completed amplifier emphasises the restrictions on the physical size of the output capacitor C6.

Peak current in transistors is:

$$\frac{V_{cc}}{2R_L} = 2.2A (I_{pk})$$

If this value is above 4A we must use either a lower supply voltage or higher load impedance. To provide current limiting of this value and assuming no voltage drop across R7, R10 we calculate the values of R6 and R11 as:

$$R6 = R11 = \frac{650mV}{I_{pk}} = \frac{0.65}{2.2} = 0.296 \Omega$$

The nearest preferred value of resistor, which must be lower in value than the calculated value, is 0.27Ω . The basis of the working of the power limiting facility is difficult to explain in such a short article but works on the principle that both a high voltage across or a high current through a transistor and its network of resistors (Tr1, R6, R7 and R8) will tend to turn off the transistor. The resistor network acts to sense the power dissipation in the transistor and to limit this dissipation. The value of R7 and R10 is 56Ω . In all cases the value of R8 and R9 is:

$$R8 = R9 = \frac{V_{cc}}{6mA} = 5.8k\Omega$$

The next highest preferred value, $6.2k\Omega$, is rather difficult to obtain and the value has been increased to $6.8k\Omega$. The voltage gain of the circuit is 100 and although this may be altered by changing the value of R4, the effect of such a change on the stability of the amplifier is difficult to predict. Under d.c. conditions the capacitor C3 represents an open circuit and the d.c. gain becomes zero, the voltage at the emitters of the two transistors, determined by the ratio of the values of R1 and R2, being at half the supply voltage.

★ components list

Resistors

R1 4.7k Ω	R5 10k Ω	R9 6.8k Ω
R2 4.7k Ω	R6 $0.27\Omega \pm .02$	R10 56 Ω
R3 10k Ω	R7 56 Ω	R11 $0.27\Omega \pm .02$
R4 100 Ω	R8 6.8k Ω	VR1 5k Ω log

All $\frac{1}{2}W$ 5% except R6 and R11

Capacitors

C1 1.6 μF 40V	C4 10pF
C2 6.4 μF 25V	C5 2000pF
C3 50 μF 35V	C6 500 μF 50V

Note: C6 should not be over $2\frac{1}{2}$ " long and 1" dia.

Semiconductors

Tr1 MJ4000 Tr2 MJ4010
(both with mica washers and bushes)

IC1 NE540L

Available from SCS Components, POB 26, Wembley, Middlesex

Miscellaneous

Diecast box, $4\frac{1}{2}$ " x $3\frac{1}{2}$ " x 2". Veroboard 2.9" x 2.2", 0.1" matrix. Input socket, Output jack socket.

The component board is a 2.9in. x 2.2in. piece of 0.1 matrix veroboard, with the copper strips running along the 2.9in. length of the board, Fig. 3. After cutting the strips below the i.c., drilling the mounting holes and cleaning up the rough edges, a few moments should be spent with a meter checking that no lines are shorted together and that the strips below the i.c. are completely severed.

There should be no difficulty in constructing the board, but it is advisable to use different coloured wires for the flexible connections as this assists in the final wiring. The capacitor C6 is held in place by its wire leads, the positive end of the component being connected to the emitter of Tr1. The circuit board is held above the transistors on four 4BA screws with either two sets of nuts and washers or 1in. long spacers. The nut heads are stuck on the box lid with epoxy resin adhesive.

The final stage of wiring consists of connecting all the leads from the board to their respective terminations, wiring a negative supply earth lead to the earth end of the output socket, the negative supply socket, and the solder tag on the input socket. Lastly a wire is taken from the centre of the input socket to one side of VR1, the remaining potentiometer connection being taken to earth (the slider goes to the input on the board).

A power supply capable of delivering the maximum requirements of the amplifier must be used. In the author's case a supply of 35V at 2.5A. Under these conditions the amplifier was able to deliver nearly 15W r.m.s. into an 8 Ω load. ■

CO! CO! CO! CO! CO!

ISSUES WANTED

- ...an issue of July 1972 P.W. for Texas Amp. Gen.—A. Palfreyman G3UHD, 39 Gledhow Park Avenue, Chapel Allerton, Leeds, LS7 4SD.
- ...1971 issues of Practical Wireless, January, May & July issues.—Mr. Ong Choo Sien, Flat 12B, Jalan Berhala, Off Jalan Brickfields, Kuala Lumpur.
- ...Practical Wireless No. 5 Vol. 47—1971—E. Blackham, 89 Myatt Avenue, Parkfields, Wolverhampton, Staffs, WV2 2DN.
- ...May, June, July, September Practical Wireless for the year 1971. Also Jan. 71 P.E.—J. Nolan, 274 Packington Square, Islington, London, N1. 7VH.
- ...April 1970, Practical Wireless. To buy or borrow. All postage etc. paid.—A. Lythaby, 25 Greenhill Road, Oxford, Sevenoaks, Kent.
- ...P.W. issues March 1972 to October 1972, will consider any offer.—Mr. J. Holland, 10 Coburg Road, Ramsey, Isle of Man.
- ...April, Jun., July 1967 and Feb. 1968 Practical Television—B. C. Meek, 30 Horsebrook Lane, Brewood, Stafford.
- ...(In good condition) August 1971 and April and March 1972 issues P.W. Full price plus postage paid.—D. Mooney, 85 Aughincork Road, Glenanne, Co. Armagh, N. Ireland.
- ...P.W. Oct. 1971 Wall chart circuit building bricks. December 1971 issue of PW and Oct 1972 Aerial Data Wall Chart of P.W.—Loong Kok Choong, 1477, Main St. Jinjang North K. Lumpur, West Malaysia.
- ...P. T. Nov. 1971 to Feb 72.—K. Oodman, 2 Beaumont Road, Carlton Colville, Lowestoft, Suffolk.
- ...P.W. December 71, January & February 72 on loan. Will be returned.—S. G. Christian, Mulginnagar Colony, Block 11/B, Nizampur, Baroda, Gujarat State, India.
- ...P.W. containing the article on the Double Conversion Communications receiver. R. Thornycroft, 12 Orchard Mead, Hatfield, Herts.
- ...Television for March, April, May and June 1972.—R. T. McCoy 34, Karana Avenue Grovedale, Victoria 3221, Australia.
- ...March 1972 "Television" with the servicing of the Bush TV103/TV105.—M. V. Gardner, 180 Clonkeen Crescent, Dun Lashgair, C. Dublin, Ireland.
- ...issues of P.W. about ten years ago that covered an article on an oscilloscope. I have been given a scope but do not know the function of the controls.—P. Leyser, 17 Lapal Lane North, Lapal, Halesowen, Worcs.
- ...all back issues of P.W.—F. Murphy, 10 Upton Court, Upton, L49 6LS, Wirral, Cheshire.
- ...issues of P.W. that contained details of capacitive discharge systems.—J. Smith, 9 Amherst Avenue, Handsworth Wood, Birmingham. B20 2LH.
- ...P.W. Jan. 1972, April 1972, E.E. Nov. 1971, Feb. 1972, March 1972. Will pay face value plus postage and packing. All replies answered, Redwood, 45A Lutworth Avenue, Poole, Dorset, BH15 4DH.
- ...P.W. February and April 1972.—Ramesh Udyawar, C/O Post Box 610, Bombay 1, India.
- ...P.W. February 1972 issue containing details of the "Translator Scope".—Mr. A. Chaplin, 26 Waking Avenue, Shoeburyness, Nr. Southend-on-Sea, Essex.
- ...P.W. January 1972—T. Fresson, Fernilee, Churt, Farnham, Surrey.
- ...May 1972 edition of Television or a photostat of the second part of the colour television project.—C. A. Wilson, 23 Friar Oak Road, Hassocks, Sussex.
- ...P.W. February, March, June and July 1968.—D. Appliford, 34, Dennistead Crescent, Headingly, Leeds.
- ...wanted P.W. November 71 to March 72. Mr. C. S. Hodgson, 18 Kensington Avenue, Normanly, Teesside.
- ...January 1972, P.W. or circuit and data for B.F.O.—E. Caines, 13 Batts Close, Pannyswell Road, Bristol 5.
- ...November and December 1971 of P.W.—G. J. Oummett, 670 Shooters Hill Road, Blackheath, London, S.E.3.
- ...The Issues of F.W. for September and October 1971.—J. Balicki, 3 Millfields, Writtle, Essex.

CONSTRUCTION

The complete circuit is constructed in a diecast aluminium box using the lid to hold all the components and the rest of the box as the cover. Fig. 2 shows the lid marked out for drilling, after which the power transistors are mounted (the NPN transistor Tr1, MJ4000 on the left as seen in Fig. 2) using mica washers with bushes. It is best at this stage to check whether the collectors of the transistors have been accidentally shorted to the box lid. The remainder of components should be fixed to the box lid, a tag washer under the input socket nut providing the main connection to the lid.

THE FREE HEATHKIT CATALOGUE

.....perhaps the most valuable
stereo HiFi/Electronics kit publication available today



NEW MULTI-SPEAKER KIT

Features Four KEF Hi-fi Drive Units. Offers monitor quality at lowest cost.

NEW AM/FM STEREO RECEIVER KIT

Solid State FM IF Circuitry, two IC's, two ceramic filters. "Black magic" lighting.

NEW PORTABLE ENGINE ANALYSER KIT

Versatile automotive testing and trouble-shooting.

LOW-PRICED TESTERS AND INSTRUMENTS

for the hobbyist and technician.

PLUS

all the models you have read about in international publications.

NEW 1214 SERIES STEREO HI-FI

Ideal for use for quadraphonic sound.

the HOW AND WHY OF KIT BUILDING

Electronics is fun the HEATHKIT way.

BUILD YOURSELF A PAIR OF SPEAKERS

in an evening - enjoy Stereo sound.

GET THE BEST IN HI-FI

Enjoy worthwhile kit savings.

SOMETHING FOR ALL THE FAMILY

even a battery charger for dad.

LOW COST STEREO RECORD PLAYER

amazing sound value.

It's Free ... it's the latest Hi-Fi/Electronics catalogue from Heath the world-famous electronic kit manufacturers ... and it's yours on request. This latest catalogue will appeal to all the family. Stereo Hi-Fi, Transistor portables, Metal detectors, Electronic calculators etc. etc. You name it, Heath can supply. All models offer unbeatable specifications for price.

Excellent continuous credit and no deposit terms available ... this even includes instruments.

You cannot afford to miss reading this fine publication ... hurry, send off the coupon for your personal copy today.

Ask
about our
No Deposit
Terms

Please send me a FREE Heathkit catalogue

Name _____

Address _____

HEATH

Schlumberger

Heath (Gloucester) Limited, Dept. PW 4/73
Gloucester GL2 6EE. Telephone 0452 29451

Heath (Gloucester) Limited, Gloucester GL2 6EE.

Fully guaranteed Individually packed VALVES

BR121	£1.75	ECH84	45p	OA2	35p
UCY31	35p	ECH200	62p	OB2	35p
DAF96	43p	ECL90	42p	PAF30	37p
DF96	45p	ECL82	35p	PC97	40p
DK96	48p	ECL83	70p	PC900	47p
DL92	32p	ECL60	40p	PC94	40p
DL34	45p	EF26	45p	PCX99	50p
DL98	45p	EF37A	£1.95	PCX189	55p
DM70	30p	EF40	50p	PCF800	75p
DY86	33p	EF41	65p	PCF80	30p
DY87	32p	EF80	25p	PCF82	33p
DY802	48p	EF83	55p	PCF84	60p
EB90C/01	£1.00	EF96	30p	PCF200	73p
FR80C	£2.00	EF98	25p	PCF201	73p
FR10C	90p	EF91	30p	PCF801	45p
FR10C	90p	EF92	35p	PCF802	50p
FR10C	90p	EF95	35p	PCF803	80p
EA50	20p	EF183	30p	PCF808	85p
FAHC80	30p	EF1200	75p	PCH200	70p
FAF42	52p	EL34	50p	PCL41	45p
EBF91	18p	EL41	50p	PCL42	27p
EBF33	50p	EL84	24p	PCL43	60p
EBF41	50p	EL85	42p	PCL84	42p
EBR31	31p	EL85	40p	PCL85	42p
EBF80	40p	EL90	35p	PCL86	40p
EBF83	40p	EL95	35p	PFL200	61p
EBF89	30p	EL500	55p	PL36	38p
ECN81	30p	EM31	25p	PL41	48p
ECN82	28p	EM40	40p	PL42	40p
ECN83	30p	EM41	35p	PL43	42p
ECN84	30p	EM42	30p	PL44	35p
ECN85	40p	EM51	40p	PL500	73p
ECN86	45p	EM66	40p	PL504	75p
ECN88	37p	EM81	40p	PL509	£1.25
ECN89	52p	EM88	40p	PX4	£2.50
ECN90	35p	EZ41	50p	PY33	60p
ECN92	30p	EM84	30p	PY90	25p
ECN93	35p	EM87	27p	PY81	27p
ECN94	30p	EZ34	55p	PY82	35p
ECN95	62p	EZ37	70p	PY83	35p
ECN96	82p	EZ37	70p	PY83	35p
ECN97	82p	EZ37	70p	PY83	35p
ECN98	82p	EZ37	70p	PY83	35p
ECN99	82p	EZ37	70p	PY83	35p
ECN100	82p	EZ37	70p	PY83	35p

SPECIAL OFFER P & P 9J TUBE £2.50 50p

OA5	20p	OC71	12p	IN823A	£1.30
OA10	25p	OC72	20p	3N159	50p
OA70	10p	OC73	25p	IZM75	37p
OA71	10p	OC75	25p	12MT10	33p
OA73	7p	OC76	25p	IZT5	67p
OA74	7p	OC81	20p	IZT10	63p
OA79 (6115)	10p	OC81D	20p	2G385	51p
OA81	10p	OC82	25p	3G408	51p
OA81	3p	OC82	25p	40669	£1.45
OA91	3p	OC83	25p	12R660	73p
OA200	7p	OC83	25p	40934	£1.25
OA202	10p	OC83B	15p	40955	£1.25
OA210	25p	OC84	25p	40955	£1.25
OA211	30p	OC122	50p	40955	£1.25
OA220	55p	OC122	50p	40955	£1.25
OA2201	50p	OC140	40p	40955	£1.25
OC16	50p	OC170	25p	40955	£1.25
OC22	50p	OC171	30p	40955	£1.25
OC25	40p	OC172	37p	40955	£1.25
OC26	25p	OC200	40p	40955	£1.25
OC28	60p	OC201	75p	40955	£1.25
OC29	60p	OC206	85p	40955	£1.25
OC35	50p	OC218	30p	40955	£1.25
OC36	55p	IN25	80p	40955	£1.25
OC38	42p	IN43	10p	40955	£1.25
OC44	17p	IN70	7p	40955	£1.25
OC45	12p	IN677	12p	40955	£1.25
OC70	12p	IN702-72586	3N140	97p	BC107

TRANSISTORS, ZENER DIODES etc.

BC108	10p	GET115	45p
BC113	10p	GET116	50p
BC118	20p	GET116	50p
BCY72	15p	NKT222	20p
BF115	25p	NKT304	50p
BF173	20p	RAS310P	33p
BFY31	20p	SD91R	28p
BFY32	20p	SD92S	31p
BS	45p	SD92S	31p
BS2	47p	SD94	25p
BSY29	25p	SD98H	46p
BU100	£1.80	V405A	40p
BY213	25p	Z2A510F	78p
BY216	38p	ZR11	33p
CR81/10	25p	ZR21	46p
CR81/20	35p	ZR22	46p
CR81/35	43p	CR81/40	48p
CR81/40	48p	CR83/05	30p
CR83/20	38p	CR83/30	43p
CR83/30	43p	CR83/50	55p
CR83/50	55p	CR83/60	55p
CR83/60	55p	CR83/70	55p
CR83/70	55p	CR83/80	55p
CR83/990	55p	CR83/1000	55p



ALL valves guaranteed

6X4	25p	6X5	£4.25	60A5	65p
6X6	20p	19A4	£1.50	60B8	£1.50
6X7	25p	19B4	£5.00	6146	£1.75
6X8	40p	30P4	£1.00	8020	£2.25
6X9	50p	35L6GT	40p	9001	20p
6X10	35p	60C15	70p	9002	25p
6X11	20p	30C17	80p	9003	50p
6X12	40p	30C18	70p	9004	15p
6X13	60p	30F5	80p	9006	15p
6X14	40p	30FL1	75p		
6X15	32p	30FL12	£1.15	CRK Tubes	
6X16	30p	30FL13	50p	VCR7	
6X17	37p	30FL14	83p		£4.50
6X18	32p	30FL15	80p	VCR517B	
6X19	32p	30FL16	80p		£5.50
6X20	32p	30FL17	72p	VCR517C	
6X21	32p	30FL18	75p		£7.50
6X22	32p	30FL19	75p		£9.00
6X23	32p	30FL20	75p		£9.00
6X24	32p	30FL21	75p		£9.00
6X25	32p	30FL22	75p		£9.00
6X26	32p	30FL23	75p		£9.00
6X27	32p	30FL24	75p		£9.00
6X28	32p	30FL25	75p		£9.00
6X29	32p	30FL26	75p		£9.00
6X30	32p	30FL27	75p		£9.00
6X31	32p	30FL28	75p		£9.00
6X32	32p	30FL29	75p		£9.00
6X33	32p	30FL30	75p		£9.00
6X34	32p	30FL31	75p		£9.00
6X35	32p	30FL32	75p		£9.00
6X36	32p	30FL33	75p		£9.00
6X37	32p	30FL34	75p		£9.00
6X38	32p	30FL35	75p		£9.00
6X39	32p	30FL36	75p		£9.00
6X40	32p	30FL37	75p		£9.00
6X41	32p	30FL38	75p		£9.00
6X42	32p	30FL39	75p		£9.00
6X43	32p	30FL40	75p		£9.00
6X44	32p	30FL41	75p		£9.00
6X45	32p	30FL42	75p		£9.00
6X46	32p	30FL43	75p		£9.00
6X47	32p	30FL44	75p		£9.00
6X48	32p	30FL45	75p		£9.00
6X49	32p	30FL46	75p		£9.00
6X50	32p	30FL47	75p		£9.00
6X51	32p	30FL48	75p		£9.00
6X52	32p	30FL49	75p		£9.00
6X53	32p	30FL50	75p		£9.00
6X54	32p	30FL51	75p		£9.00
6X55	32p	30FL52	75p		£9.00
6X56	32p	30FL53	75p		£9.00
6X57	32p	30FL			

HOT LINES

ON RECENT DEVELOPMENTS

FOR some time now, weather satellites have been happily orbiting the earth some 800 miles up. These animals transmit a picture of the earth and a suitably equipped station below can receive these pictures. They show cloud distribution which is useful in helping to guess whether it will rain or not on the following washday.

3D RAIN?

Now comes news about a satellite built by the RCA. It is equipped with special sensors and boasts the distinction of being the very first operational satellite to provide a three-dimensional picture of the earth's weather. It is equipped with some very impressive sounding equipment; a scanning radiometer, a very high resolution radiometer and a vertical temperature profile radiometer.

The very high resolution radiometer (v.h.r.r.) has two channels and offers images from both the visible and infra-red regions. It can sense the thermal energy given off by objects below, down to half a mile in area.

Resolution is far better than the pictures provided by television cameras or the radiometers used in earlier satellites. The solar cells in the satellite, NOAA -2, generate some 500 watts and over 10,000 individual cells are used to achieve this power. Who knows—television announcers of the future may be forecasting that three dimensional rain is on the way.

LIQUID CRYSTALS

It now seems a certainty that liquid crystal displays will have a big impact on the electronics market. I reported these as being already built into a multi-digit display being marketed at the Electronica exhibition in Germany late last year. Now, the U.S. giant, North American Rockwell is reported to be mass-producing liquid crystal devices.

The liquid crystal phenomenon was first discovered way back, as long ago as 1888. The basic principle is that certain liquids become opaque when they are subjected to an electric field. With no field present, they are transparent. The North American Rockwell displays consist of two small plates of glass. Although

these are bonded together, they are separated by a tiny gap—about a thousandth of an inch. This tiny gap is filled with the special liquid which is affected by an electric field. The cell is thus completely transparent.

However, when a small electric field is applied (this takes about 25V to achieve the desired effect) the cell becomes opaque. Without a field, the molecules in the liquid are uniformly and regularly oriented. The application of the electric field causes this molecular structure to become disoriented and the molecules thus scatter the light giving an opaque effect.

The voids or spaces into which the liquid is put can be formed into figures or letters for the purposes of forming a display. Conductors to the liquid are formed from tin oxide which is a transparent conductor. The liquid crystal display draws almost no power—about 10mW or one hundredth of a watt. Perhaps we will have windows some day which will be clear until we press a button?

OZONE SPEEDS UP RESIST REMOVAL

Integrated circuits (i.c.'s) are delicate little beasts especially during their manufacture. Part of this process is a photographic one. There is a particular stage in the printing of each mask where unwanted photo-resist has to be removed. Considering the size of elements on individual i.c.s this removal is a delicate business. The General Electric Company in the U.S.A. have come up with a new method of removing unwanted photo-resist. It consists of exposing the resist to ultra-violet rays in the presence of air. It takes about 40 minutes for a typical film of resist to be removed. The depolymerisation of the resist happens at a rate of about a thousand angstroms per minute. By injecting 2% ozone gas into the chamber with the specimen the process is speeded up some ten times.

Earlier, I talked of liquid crystals and many have leapt in claiming that the solid state flat tube television screen is here. One British manufacturer, however, is obviously unimpressed. Mullard has opened a

new factory in County Durham. The sole purpose is to manufacture shadow mask colour television tubes.

Although only officially opened in December last year, pilot production was already said to be running at the rate of 100,000 tubes delivered from this plant. By the end of this year, production is estimated to be in the region of 500,000 tubes and by the end of this present decade, production will be running at some 900,000 tubes/annum. All this adds up to a lot of colour television receivers—have you got yours yet?

LASERS ARE BACK

Lasers are back in the news again, this time in America where the Optical Physics Division of the National Bureau of Standards is applying one to monitor pollution. A major contributor to atmospheric pollution is nitrous oxide. It is found lurking in such jolly jollop as flue gases and in the exhaust fumes from motor vehicles.

The laser beam is directed through a magnet whose coils are driven by an audio amplifier and is detected by an infra-red device. The amplifier generates a modulating magnetic field which has the effect of sweeping the absorption line through the laser line. The detector produces a signal which has a direct relationship to the amount of nitrous oxide in the sample being investigated.

Concentrations of nitrous oxide as low as 20 parts per million (p.p.m.) can be detected but workers believe that concentrations right down to 0.1 p.p.m. will be detectable as the method is improved.

FLYING SPOT

Useful things oscilloscopes. Have you ever wondered just how fast that tiny spot of light travels across the cathode ray tube? Before you start to make calculations, think of the latest fast writing oscilloscope, the HP 184A. The writing speed for this unit is so fast that the spot travels 400cm in one millionth of a second.

Ginsberg



IAN SINCLAIR

EVER since the day when Marconi equipped the yacht *Elettra* with radio to act as a mobile test-bed, electronics and boats have been closely associated. The first really extensive use of radio was at sea, and after the Titanic disaster all ships were required to keep radio watch continuously for distress signals. The requirement for ships to be fitted with radio and staffed with trained operators did not, however, extend to small boats at that time, and it is only fairly recently that radio and electronic aids for pleasure craft have become more of a necessity for serious boating.

MARINE HAZARDS

Electronic devices for use at sea present some design problems which do not appear in land-based equipment. The most obvious hazard is moisture, not the fresh water moisture of a foggy day on land but the salt-laden moisture which corrodes its way through soldered joints, cable terminations, plugs and sockets, and most other metal-to-metal joints in a remarkably short time. As well as the corrosion problem, which can be completely solved only by total encapsulation, there is the problem of insulation resistance.

Salt spray is quite a good conductor and in valve equipment in particular, operating at high voltages, protection of equipment from saline elements is a problem to designer and operator alike.

It was largely the water-spray problem, as well as the cost factor, which has kept electronics out of small craft for so long. In large vessels, the radio and radar equipment could at least be mounted in an enclosed space at a reasonable height above the deck, well away from the direct spray except in the most extreme conditions. In small boats, such spray-free havens cannot be found, and there is little chance of keeping the equipment free of water by heating coils, as were once used on bridge-mounted radio and radar.

The advent of solid state equipment has opened up a new dimension in marine applications, especially with the possibility of cutting down on inter-connections by using integrated circuits. Vibration is one of the most pressing problems in small craft, where the rumble of even a small diesel engine is enough to loosen plugs from sockets or wires from soldered joints.

Some of the most up-to-date equipment used for pleasure craft can be seen at the annual Boat Show, held each year in London in January. This year you would have found amongst other more glamorous displays, several kinds of communications equipment.

One stand showed a "triple-standard" television receiver, complete with inverter for use with ship batteries, for use in most yachting centres in the world. But for those who insist on wind in their sails, there was a complete analogue computer, taking information on wind speed and direction, water speed, currents, intended course, and displaying the optimum trim on a model.

RADIO AIDS

Radio is still the mainstay of marine electronics, and it is hardly surprising that there should not be many advances in this direction as there are in instrumentation. The latest ranges of transmitter/receivers are geared to the most recent International regulations, which call for s.s.b. working in the marine bands between 250kHz and 4.1MHz and the use of all solid state equipment has resulted in very compact apparatus.

A large number of v.h.f. and u.h.f. radiotelephones were also shown, and one interesting new development is the Marconi "Pocketphone" intended for communication on large vessels, such as tankers, and during docking and cargo handling operations.

The v.h.f. and u.h.f. equipment uses frequency modulation, and most make provision for the reduction of channel spacings to 25kHz, which will soon be a Post Office requirement. The bands used are within the range 148MHz to 174MHz in v.h.f. and 440MHz to 470MHz in u.h.f. Communications equipment was being shown by (among others) Marconi Marine, Electronic Laboratories (Marine), Ajax Electronics and S.P. Radio A/S of Denmark.

The latter firm was showing a receiver operating under the spray from a waterfall, whose salt content I did not sample, and also showed the "Dual-watch" facility on receivers. This enables the operator to fulfil the requirements of listening for distress signals along with normal working. The distress frequency is preset, so that the set is tuned permanently to that frequency in the watching circuits.

Working can be continued on other channels, and if a signal is received on the distress frequency (or any other being watched) the receiver output is instantly and automatically switched to the watched frequency. A lamp indicator also shows when a call is being received on the watched channel, and flashes during normal operation to show that the watch is being carried out.

DIRECTION INDICATOR

An interesting device for the small boat is the "Seafix", a hand-held radio direction indicator by Electronic Laboratories (Marine). This consisted of a t.r.f. transistor receiver with "autodyne" detection

over the range 200 to 400kHz, with the calibration most accurate at 300kHz, the centre of the Marine Beacon band.

Switched to NAV, the autodyne circuit is used to receive beacon transmissions, and the highly directional ferrite rod aerial can be used for finding the bearing of the beacon within 2° (at half rated range). Switched to BC, the "Seafix" can be used to pick up the long-wave shipping forecasts broadcast on this band. A stethoscope headset was used in preference to loudspeakers or conventional phones, and water sealing was by the conventional compressed rubber gaskets.

RADAR

Radar has for a long time been one of the most important navigational aids for larger vessels, but is seldom seen on smaller craft. There are several reasons for this: the cost of any radar installation is high, since it must include the cost of modifications to the vessel as well as the provision of the apparatus.

Radar equipment is often unavoidably large, heavy and dependent on high voltages, since the cathode-ray tube and the magnetron must use high voltages, although it is now possible to replace the klystron local oscillator by Gunn diodes or other semiconductor devices.



The Hepplewhite Marine Check radar detector lets you know if you are on a collision course.

Manufacturers are not dragging their heels over these problems, but are commendably cautious, since they know only too well how much the readings of a radar receiver come to be relied on. Any compression of size or cost must therefore not be made at the expense of accuracy of plotting if we are not to have a rash of "radar-assisted" collisions. All the big names in marine radar (Decca, E.M.I., Marconi Marine) showed small radar outfits, but these were not really intended for the amateur.

The Hepplewhite "Marine Check" is a continuous scanning self-powered instrument designed to minimize risk of collision with other vessels whose radar may not pick up small boats in bad weather or low visibility—the "Marine Check" will however, detect the other vessel's radar transmission and allow you to take avoiding action.

The scanning head is a miniature, precision, solid-state detector and amplifier of continuous, pulsed

and modulated X-band radar transmission (9,000 to 11,500MHz) with electronics mounted in a shock-proof case and will receive radar transmissions at sighting distance.

As the sensitivity is reduced, the directional power of the antenna is proportionately increased to a point where the bearing is located on a narrow sector. If this bearing, which is indicated on a compass scale, remains constant, you may be on a collision course, also as the pulse length increases as the distance decreases, it is possible, within limits to determine if the transmitting vessel is approaching or receding.

The "Seascan" radar by Electronic Laboratories (Marine) is designed for the amateur, and has a power consumption of only 48W from 12V, 24V or 48V battery supplies. The only vacuum devices used are the display tube and the magnetron, the local oscillator being a Gunn diode whilst the magnetron modulator uses a thyristor. Unfortunately no circuit details were available and all the units on the stand were dummies.

One interesting new development in radar for the small craft is a passive radar detector by Hepplewhite Marine. This picks up the X-band (9,000 to 11,500MHz) transmissions from other vessels, and has a small directional aerial consisting of a Perspex "horn" on which waves are guided (along the surface) by the effect of the permittivity of the material. The received radar signals are mixed with the output of a local oscillator, and the beat note amplified. The point of strongest signal can be identified by altering the mixer bias so that only a signal of the maximum strength will produce a beat note; this enables the operator to find the bearing of the craft carrying the radar.

SPEED MEASUREMENT

Water and wind speed instruments have for a long time been a weak point in the instrumentation of boats. The traditional methods of measuring speed have depended on anemometers for wind speed and submersible "logs" for water speed. The anemometer is the device using three or four cups at the ends of radial rods pivoted so that the effect of wind is to revolve the assembly about its axis. The



The Electra Magnetic Log is an impellerless speed and distance indicator.

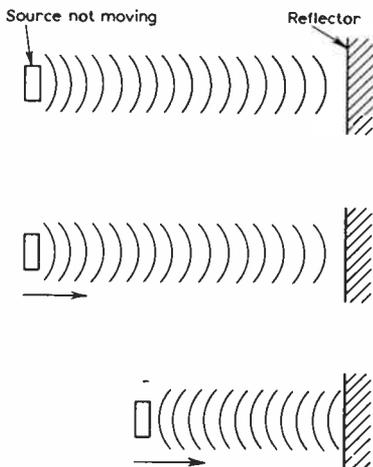


Fig. 1: The Doppler Principle.
 Imagine a transducer giving out sound waves. These waves travel in water at a speed of about 1,000 metres per second. Speed equals frequency multiplied by wavelength.
 If the transducer moves at a speed "V", the speed of the waves towards the reflector is now 1,000 + V metres per second. We have not changed the frequency of transmission, so the wavelength must now be less.
 $(1,000 + V = f \times \text{new wavelength.})$
 The waves are now reflected to a moving object, so that more waves per second hit the receiving transducer. The frequency is now higher by a factor $\frac{c+V}{c}$ where c is the normal wave speed and V is the speed of the transducer and boat. The final effect is to receive waves of shorter wavelength and higher frequency.

speed of rotation, which depends on the wind speed, is measured by counting the number of switching operations of a reed switch under the influence of a magnet on the rotating shaft. This count is converted into an analogue signal which drives a meter. Wind direction is found by using a vane coupled to a potentiometer to show the angular position by voltage detection on a meter.

The traditional submersible "log" consists of a small propeller whose shaft is held in a casing containing a reed switch. The rotation of the propeller as the "log" is towed behind then registers relative water speed just as the anemometer registers relative wind speed. The snag is that the propeller of the log is easily jammed by anything encountered in the water from jellyfish to seaweed, and this can have the effect of making calculation of speed and distance incorrect.

SPEED-LOGS

Two novel speed-logs were shown, each representing refreshingly different thinking about the problem. Space Age Electronics showed their Doppler speed log. This uses a ceramic transducer to project a 1MHz sound beam ahead of the ship. Most of the beam is dissipated in the water, but a small part is reflected from the layer of relatively still water (the boundary layer) close to the boat.

When the boat is moving, the reflected frequency is not the same as the transmitted frequency (Doppler Effect). If the boat is moving ahead, the reflected frequency is higher than the transmitted frequency; if the boat moves astern, the reflected frequency is lower.

Referring to Fig. 1, the transmitter, because of its movement, "packs in" more waves between itself and the still layer than it would if it were not moving. Because more waves are travelling, the wavelength seems shorter. Also, when the waves reflect from the boundary layer, the receiver has also moved towards them, making the frequency of the received waves seem higher.

When the reflected wave is detected, the shorter wavelength appears as a higher frequency (speed = frequency \times wavelength), whose value depends on the difference between the speed of sound in water and the speed of the boat. By beating the transmitted frequency against the reflected frequency, a measure of speed can be obtained.

The method is dependent on obtaining a reflection from relatively still water, and so the transmitting/

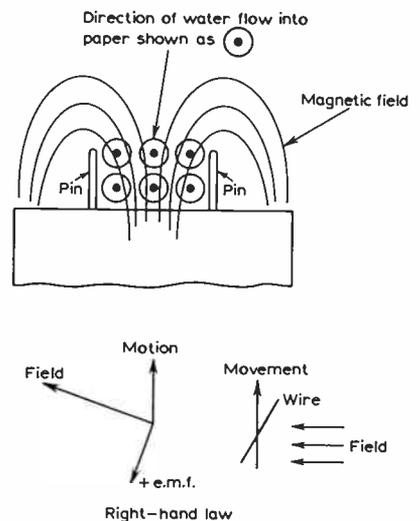


Fig. 2: An e.m.f. is produced between two metal contacts, providing the direction of flow is at right-angles to the line joining the contacts.

receiving head must be located where such a layer is within range. Precise location varies from boat to boat. To allow for variations in installation, the calibration is adjustable, so that the distance log can be checked against accurately known distances (between two land-marks, for example). The circuitry uses three integrated circuits, 17 transistors and eight diodes. A "log" accuracy of better than $\pm 1\frac{1}{2}\%$ (typical) is claimed.

The "Electra" magnetic log, produced by E.M.I. marine uses the magnetohydrodynamic principle for its operation; this is the generation of a voltage by induction when a conducting liquid flows past a magnetic field.


By arranging a magnetic field to cut the direction of water flow at right angles, an e.m.f. is induced between two metal contacts in the moving water, provided that the direction of flow is at right angles to the line joining the contacts (Fig. 2)

The Electra Magnetic Log operates on this principle, but with some ingenious modifications. The magnetic field used is an alternating field. In this way, the voltage generated is also alternating, which disposes of two problems at once. One problem is polarisation; when a steady voltage exists between two contacts in sea water, an electrolysis action takes place causing corrosion of the metal. The use of a.c. avoids polarisation problems and makes it easy to amplify and display the output from the contacts. As with the previous method, the positioning of the measuring head is critical.

ECHOSOUNDERS

Echosounders have been used for a considerable time, and changes have been in detail rather than in concept. Basically, a marine echosounder consists of a pulse generator working at ultrasonic frequencies in the region 20kHz to 150kHz (the higher frequencies are used for inshore work). A transducer converts the electrical pulses into sound waves directed from the bottom of the boat into the sea, and a receiver, using the same transducer, detects the pulse reflected from the bottom of the sea.

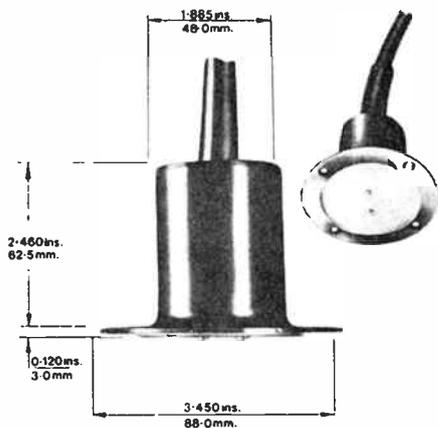The shape of the received pulse provides a guide to the nature of the sea bed, for example, a muddy



The electro-magnetic transducer for the magnetic log. As the boat moves along, a small e.m.f. is produced and sensed by two probes. This signal is then amplified and displayed in speed and distance units.



The Doppler speed-log does not rely on the flow of water to move a mechanical part like an impeller or paddle wheel. A small streamlined transducer, mounted flush with the underside of the hull, transmits a high frequency ultrasonic signal 70cms ahead. A small part of this signal is reflected back from the boundary layer between the hull and the water.

sea bed is indicated by a broad pulse, a sandy bed by a narrow pulse, a rocky bed gives multiple reflections. Pulses received from intermediate depths can indicate shoals of fish. The time delay between transmission and reception is proportional to the depth of sea.

Because the pulses are travelling in the water at the speed of sound (around 1,000 metres per second) rather than at the speed of radar waves in space (some 30 million metres per second), scanning rates have to be lower than the 1,000Hz commonly used in radar. Scanning rates of once per second are common, although this is rather too low for display on a long persistence cathode ray tube screen.

The display method traditionally used is a rotating wheel carrying, or illuminated by, a neon which flashes on transmission of the pulse and again when the echo is received. The stationary bezel round the wheel is then calibrated in metres of depth (now replacing fathoms on the latest charts).

The large number of echo sounders at the show demonstrated several novel points of design. Most interesting was the use of electro-luminescent diodes to replace neons, so avoiding the need to generate a high voltage supply (Brookes & Gatehouse). A common feature of all the echo sounders was the use of high scan rates for the shallow water ranges (up to six pulses per second) so giving better definition in critical conditions.

Lead zirconate titanate crystals were in evidence as transducers, encapsulated in various plastics. For professional use, chart recording echosounders were shown (these, of course, have been around for a long time). The Marconi Marine chart-maker used electrosensitive paper which changed colour when a small voltage was applied between the front of the paper and the back.

WATER-LEAK AND WATCH

In addition to the displays of electronics for communication and navigation, there were some interesting exhibits in the "miscellaneous" class. Space-Age Electronics were showing their water-leak and watch alarm, and judging by the sound which could be heard all over the first floor of Earls Court, almost every chandlery firm was demonstrating it.

The instrument is basically a conventional leakage detector using stainless steel pins as probes. If the pins are immersed in water for more than four seconds, an alarm is given, but only if the immersion is for longer than four seconds, a time carefully chosen to avoid continual false alarms in heavy seas. When there is no conductivity between the pins, all transistors are biased off, so ensuring practically no standby current. The sound given out is a rising frequency note which is most easily distinguished amongst other sounds.

The watch facility also provided on this instrument gives an alarm note of gradually increasing amplitude every three minutes. If an alarm button is pressed during the alarm, or before it, the instrument remains silent until another three minutes has passed. If the helmsman is asleep and does not press the alarm button, the alarm warning increases to maximum intensity.

GAS ALARM

The Electra gas alarm, from E.M.I. Marine, is of considerable interest. Unlike previous gas alarms, which used heat conduction from a hot wire to detect changes in the air composition, the Electra gas alarm uses semiconductor sensors. No details were given, but it is possible that the sensors consisted of infra-red electroluminescent diodes and detectors. Any change in the air composition caused by petrol vapour, butane or propane gas, carbon monoxide, smoke, paraffin fumes, diesel fumes is indicated by two visual warnings in the form of a meter reading and a red warning lamp.

In addition, a loudspeaker gives out a 2.5kHz note when the gas concentration exceeds the safe limit. In this way, no panic is caused by small concentrations of gases, since only the discreet visual warning is given, but dangerous amounts operate the audible alarm so that evacuation or other measures can be taken. Remote warnings can also be fitted.

All in all, the Boat Show is developing considerable interest from the point of view of electronic aids. It is unfortunate that so few exhibitors were able to cope with technical queries, but all of them were most helpful. ■

practically wireless

commentary by **HENRY**

I HAD a chap in the shop today, searching for an SP4. It is true: even in the glitter of a hi-fi establishment, where every prospect teases and only valves are vile, we still get enthusiasts with thirty-year-old equipment, hopeful of our being able to provide the missing link.

Which leads us, philosophically, to a contemplation of some of the 'firsts' we nowadays take for granted.

Example: the quasi-complementary transistor amplifier circuit, which has given us so much trouble since its inception. I have come across the September 1956 copy of *Electronics*, a McGraw-Hill publication, in which R. C. Lin, then of RCA, Princeton, first propounded his output circuit in which, to quote: '... the two upper transistors conduct during the negative half-cycle and the two lower transistors conduct during the positive half-cycle.'

In his summary, he gave amplifier distortion at 100cps (sic) and 400cps as below 1 per cent at six watts, and though he admitted that the distortion might be expected to rise at 5,000cps, he made no mention whatsoever of its fierce spikiness at a fraction of a watt, which is the mariner we've had wrapped around our necks ever since.



The mariner wrapped around our necks.

Inventions, especially world-shaking innovations such as the transistor proved to be, have a habit of spawning themselves much more prosaically than we would like to imagine. No technologist runs screaming through the corridors of the M.I.T. with 'Eureka' echoing behind him. More likely, something as laconic as the 12/29/39: 4.15 p.m. entry in William Shockley's notebook may be handed down to posterity: 'It has today occurred to me that an amplifier using semiconductors rather than vacuum tubes is in principle possible.'

In principle: hardly in practice. He was thinking of a Schottky-barrier FET kind of device, with copper-oxide as the semiconductor. And, as Henry could have told him*, it didn't work. Instead, the experiments of the team included covering metal points with wax and pushing them down on to p-type silicon treated to give an n-type surface. They surrounded the point with water and found they could obtain power amplification.

To quote Brattain: '... the group was jubilant that day.'

Trouble was that the water would evaporate. Maybe it was all that heavy breathing. So they switched to glycol borate to reduce evaporation. One trouble: amplification was obtainable only below 8Hz—hardly hi-fi yet.

There were lots more experiments, culminating in evaporated gold spots and germanium, and then, on Dec. 23rd 1947, two gold contacts less than two-thousandths of an inch apart were made to the same piece of germanium and the first transistor happened.

No sudden breakthrough—and no inspirational brainchild—and no immediate christening, I may add. It was a month later that a chap called John R. Pierce of the Bell technical staff mooched into Brattain's office and pointed out that the 20dB point-contact amplifier they had made was the



Runs screaming through the corridors.

'... dual of a vacuum-tube, circuit-wise.' He mentioned the important valve parameter, transconductance. Then he went on to talk about its electrical dual, transresistance. To quote Brattain once more: '... then he said 'transistor', and I said, 'Pierce, that is it!''

What about a few more firsts in our field? Who developed the first p-n junction? Bet you can't even say his name, let alone remember it. Well Henry can, with the benefit of some help from Edward A. Torrero, who is Associate Editor of *Electronic Design*. He was William Pfann (with the aid of a chap called Jack Schaff; let's give credit where it is due). They also worked for Bell Laboratories.

But Bell eschewed silicon for germanium, because the impurities, back in the early 1940's, were easier to control. It was left to Texas Instruments to develop silicon types of transistor, and to Motorola to introduce the diffused base transistor.

So I could continue. Henry hasn't the space to name those to blame.

But the "first" we are all concerned with is that original all-transistor radio. And who made that? A firm called Regency, in 1954. How's that for a significant 'first'?

* With the benefit of hindsight. Ed.

EXTRA!!!


IN NEXT MONTH'S

PRACTICAL WIRELESS


SIMPLE PROJECTS FOR THE HOME

8 PAGE SUPPLEMENT


P.W.'s reputation for plenty of simple and straightforward constructional projects is excelled next month by an extra large issue. In addition to the usual constructional articles and features, the May issue will include a special extra 8-page coloured supplement describing eight easy projects for the home, designed and described by one of our top designers; you are bound to find *at least* one of these of interest. This supplement is fully illustrated with all the details on how to build these projects.

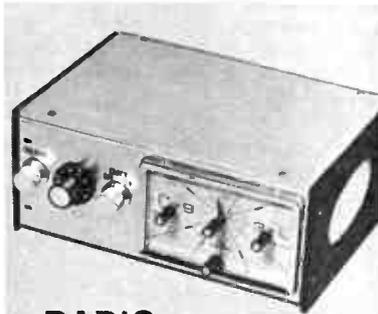

**RADIO
ALARM CLOCK**

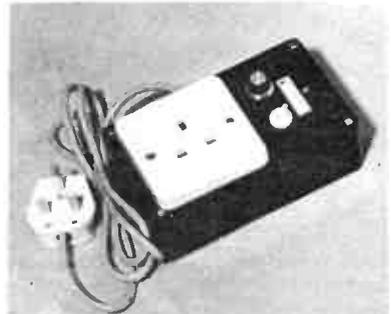

LAMP DIMMER

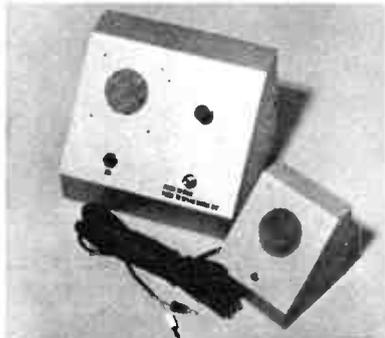

INTERCOM AMPLIFIER



**LIGHT POWERED
RADIO**




BABY ALARM



**TWO TONE
DOOR BELL**



TAPE TUNER

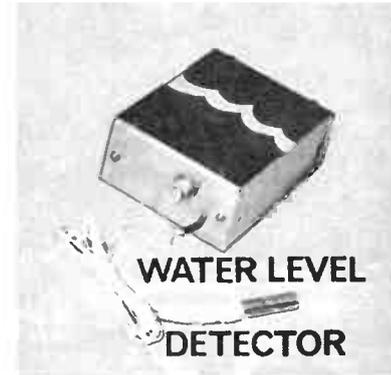

**WATER LEVEL
DETECTOR**

**MANY OTHER CONSTRUCTIONAL
ARTICLES PLUS ALL THE REGULAR
FEATURES. PRICE 20p.**

**ALL IN THE MAY ISSUE
ON SALE 6th APRIL**

Following the success of the Texan amplifier published in this magazine during May to August 1972, the applications laboratory of Texas Instruments Ltd. have developed exclusively for *P.W.*, a compatible unit for the control of Psychedelic lights from a sound source. The initial design features zero voltage control. A more sophisticated design incorporating lamp dimming facilities will also be covered in this series of articles. For stereo operation two *P.W. Tricolour* units are required.

IF I had been asked, a couple of years ago, what 'psychedelic lights' were, I could only have made a wild guess: was it perhaps a medical term referring to some sort of ultra-violet treatment for disorders of the mind? Or, possibly, the latest in pet food, some extra tantalising form of offal? The truth, however, dawned slowly. What my "trendy" young friends were talking about was the latest innovation, the offspring of a marriage between light and music. It was not simply a question of a 'pop' version of 'son et lumière' but a more intimate relationship between the two media. Light could be made to respond directly to sound; flashing furiously for a fanfare, discreetly dimmed for Debussy. It is, however, unlikely that psychedelic lights will be installed in the Royal Festival Hall, but those of our readers who occasionally frequent the discotheque or dance hall will be familiar with this innovation. It is probable, too, that many have given thought to the incorporation of this feature into their own domestic lighting systems. What, it might be asked, does this involve?

In essence a 'psychedelic' light system works like this: sound controlled modulators convert bass, middle and treble frequencies into corresponding bursts of light thus adding a new "visual" dimension to the beat of the music. This is achieved by taking a signal from across the loudspeaker terminals and feeding it into a filter circuit whose output provides pulses which correspond to the sound spectrum—bass, middle and treble and any combinations of these three channels. These pulses then pass through an interface circuit and energise appropriate triacs. The latter, as will be seen, act as electronic switches and turn on the lamps.

This article will attempt to explain fully the construction of psychedelic light control units for both mono and stereo equipment. It is aimed at the home constructor who possesses nothing more than an average amount of skill.

Zero Voltage Switching

As stated, the lights are turned *on* and *off* by utilising a device called a triac, i.e. a semiconductor bidirectional switch (Fig. 1). This replaces two thyristors connected back to back, thus controlling the positive and negative cycle of the supply voltage. Whereas the thyristor requires a positive gate to cathode voltage and will turn *on* only when the anode voltage is positive with respect to the cathode, triacs will turn *on* when the gate voltage polarity is the same as voltage between mt2 and mt1 (main terminal 2 and 1), i.e. positive for the positive half cycle and negative for the negative half cycle. In addition a triac will turn *on* with the gate negative with respect



TR



- MONO/STEREO CAPABILITY**
- ZERO VOLTAGE SWITCHING**
- NEGLIGIBLE RADIO INTERFERENCE**
- LAMP OVER-RIDE CONTROL**
- OPTIONAL LAMP DIMMING**

Mood

PART ONE



• TEXAS INSTRUMENTS LIMITED.

COLOUR



Lighting System

JUREK BUDEK*


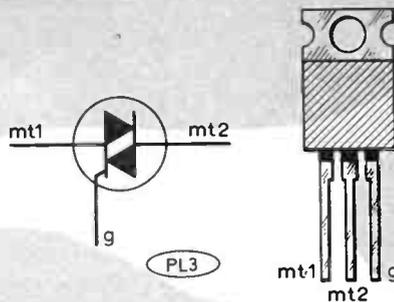


Fig. 1: The TIC226D bidirectional switch

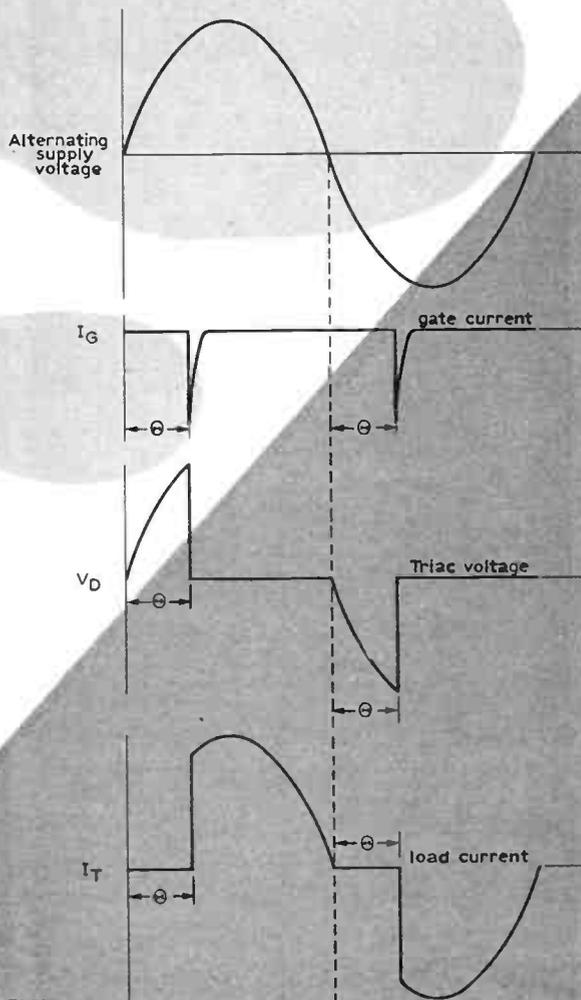

TB76

Fig. 2: Waveforms associated with triac switching. Refer to the text for clarification

to the mt1 terminal for either polarity of mt2. It is the latter factor which accounts for the techniques used in the circuits to be discussed in this article.

A further point about the triac is that there is only 2-3 volts between the gate and terminal 1, whereas there may be many hundreds or even a thousand volts between terminal mt2 and mt1.

Triacs used in a phase control mode, as shown in Fig. 2, produce considerable radio frequency inter-

ference (r.f.i.) due to the step change in current. The noise thus generated is spread by means of conduction through the wiring system or by radiation. Suppressing r.f.i. becomes more difficult and expensive as the load increases. Uncontrolled switching of "psychedelic" lamps *on* and *off* will have a similar effect and will also introduce additional noise in the loudspeakers. A simple solution to this problem is to arrange the switching so that it always takes place at the point where the mains supply voltage crosses zero, as shown in Fig. 3.

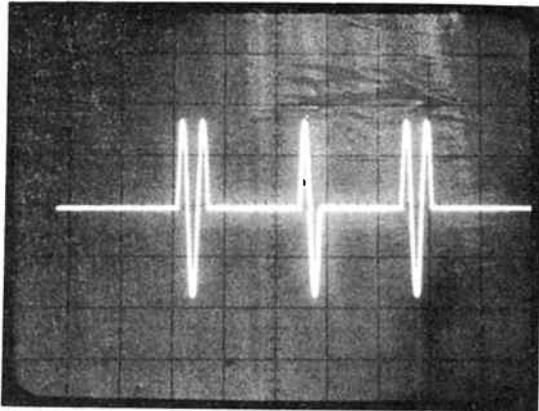


Fig. 3: Waveform depicting zero voltage switching.

This technique is called 'zero voltage switching' or 'burst firing.' In this way isolated numbers of half or full cycles will pass through the lamps and thus avoid step change in currents, which also has the additional advantage of increasing the life of the lamp.

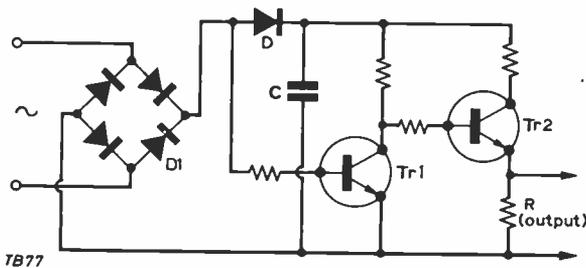


Fig. 4: Basic circuit which generates the pulses at the point of zero voltage crossing.

Fig. 4 shows the circuit used to generate the pulses at the point of zero voltage crossing. Transistor Tr1, whose base is connected to the unsmoothed supply from the bridge rectifier D1 is *on* most of the time.

However, each time the mains voltage crosses zero, its base voltage is taken below the holding on voltage and it thus turns *off*, giving positive pulses on its collector. In order to reduce the loading on transistor Tr1, transistor Tr2 has been added. Positive pulses appear as an output across resistor R each time the mains voltage crosses the zero point.

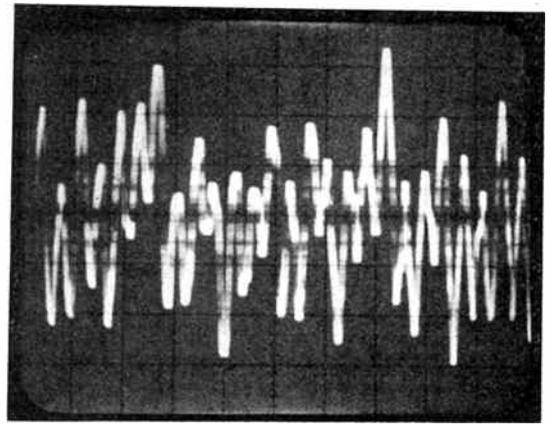


Fig. 5: Typical music voltage waveform at the terminals of a loudspeaker.

In order to control the lamp switching with respect to the frequency bands, we need a circuit which will separate out the low, middle and high frequencies from the voltage waveform appearing at the terminals of a loudspeaker. A typical voltage waveform appearing at this point is shown in Fig. 5.

Filter

A circuit which separates frequencies into bands is called a filter. There are various types of filters which could be employed; e.g. one commonly used is a resistor/capacitor (r.c.) network for high and low pass filters and an inductor/capacitor (l.c.) network for middle frequencies. The elegant way, however, specially developed for the P.W. Tricolour is to employ integrated circuit (i.c.) operational amplifiers, in a positive fixed-gain configuration, as the active filter element and resistors and capacitors as passive elements. By choosing suitable component values a sharp separation between bass, middle and treble frequencies can be obtained.

The shape of the filter response is determined by a factor known as the damping ratio (ζ). The lower this ratio, the sharper the cut-off and there is a *peaking* effect. This *peaking* effect is of no importance in our application. As approximately 1.5 volts is required to turn *on* the interface circuit, and thus to switch on the appropriate lamps, the filter characteristics are expressed in volts against frequency and not in the more usual decibels against frequency.

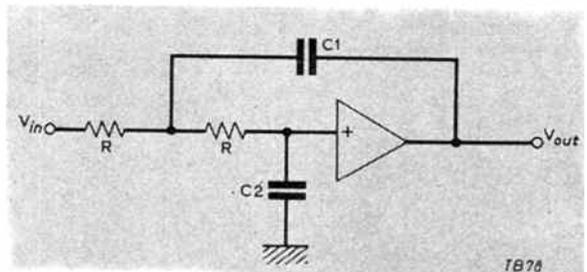


Fig. 6: Basic low pass filter as used in the P.W. Tricolour.

The theory of filter design is quite extensive and complex. We will however only outline the necessary basic concepts and give some simplified formulae.

Let us first look at a basic low pass filter (i.e. one which will stop all frequencies except those below a chosen frequency). The circuit of such a filter is shown in Fig. 6.

Here the angular cut off frequency,

$$\omega_0 = \frac{1}{R\sqrt{C_1 C_2}}$$

and the damping factor

$$\zeta = \sqrt{\frac{C_2}{C_1}}$$

Critical damping occurs when

$$\zeta = \frac{1}{\sqrt{2}}$$

and, for the reason explained before, i.e. to improve the sharpness, this value is reduced to 0.5. From these equations, the filter component values can be established.

The high pass filter (passing all frequencies above a chosen one) is shown in Fig. 7 and again requires only one operational amplifier, two resistors and two capacitors.

Here the angular cut-off frequency,

$$\omega_0 = \frac{1}{C\sqrt{R_1 R_2}}$$

and the damping factor

$$\zeta = \sqrt{\frac{R_1}{R_2}}$$

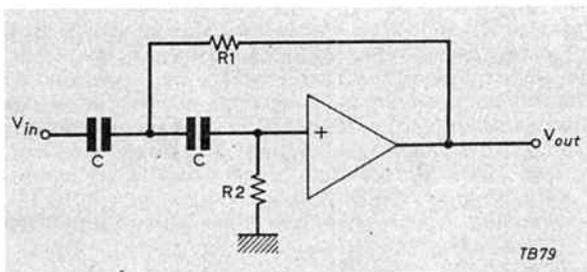


Fig. 7. Basic high pass filter. ▲

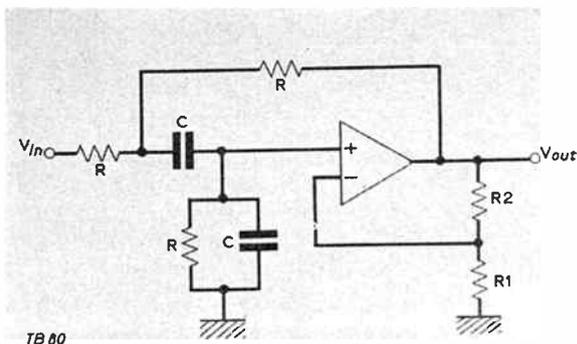


Fig. 8: Basic band pass filter.

Once more from these equations, the filter component values can be established. Finally, the band pass filter; which, of course, as its name suggests, passes a band of frequencies. This, as can be seen from Fig. 8, is a little more complicated than the other two.


The centre angular frequency $\omega_0 = \frac{\sqrt{2}}{RC}$

and the quality factor $Q = \frac{\sqrt{2}}{4 - \frac{R_2}{R_1}}$

$Q = \frac{2\Delta f}{f_0}$, where $2\Delta f$ is the difference between two frequencies at which the voltage output of the filter is $\frac{1}{\sqrt{2}}$ of its maximum value. From the above formulae, relevant component values can be obtained.

Musically oriented readers will recall the 'unisono' note played on the oboe during the orchestra's tuning-up time, just before the concert begins. This note is middle 'A' with a frequency of 440Hz; a frequency which has been chosen as the centre frequency for the middle band-pass filter in

Rear view of the P.W. Tricolour. ►

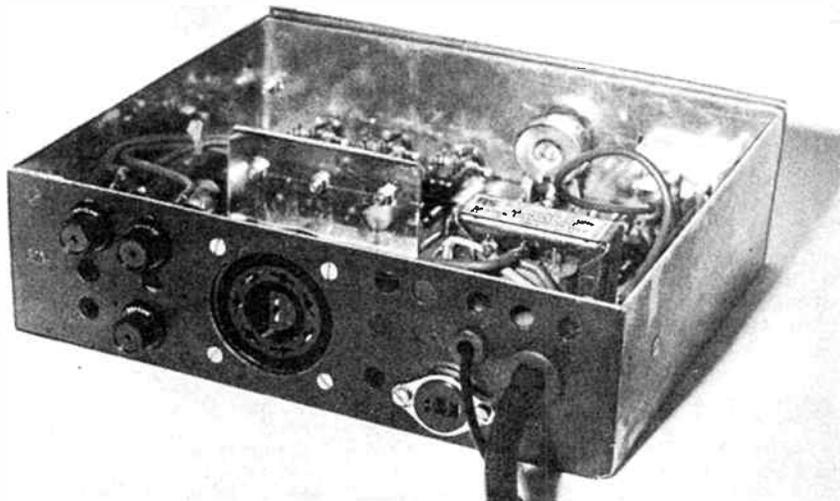

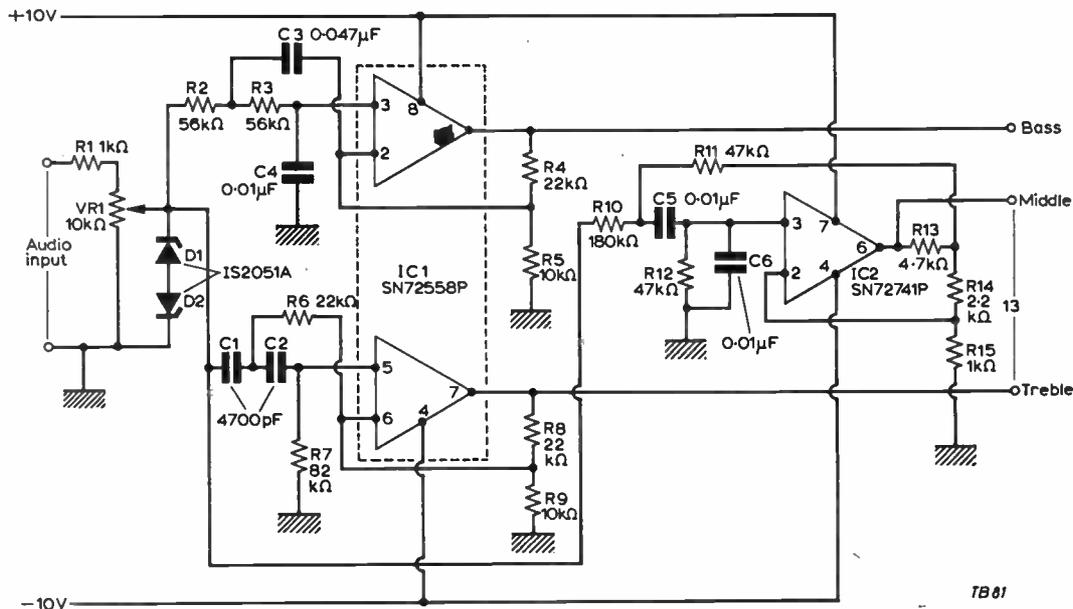


Fig. 9: Complete P.W. Tricolour filter circuit. This unit is used without modification, with either the zero voltage switching unit (Fig. 12) or with the lamp dimming unit, to be described later in this series.

this design. Cut-off frequency for the low pass filter has been chosen to be around 200Hz and that of the high pass filter (treble) about 1kHz.

Based on the above assumptions, a complete filter has been developed with the component values as shown in Fig. 9. The alert reader will notice that some of the component values differ from the figures obtained using the formulae. This has been done intentionally in order to improve the separation between the various frequency ranges.

The input to the filter circuit has been limited to 5 volts peak to peak by using two 5 volt zener diodes connected back to back. Three i.c. operational amplifiers are used. Two of which are contained in one 8 pin package, SN72558P and the other i.c. is contained in a second 8 pin package, SN72741P.

Fig. 10 shows output voltage response of the three filters plotted against frequency for a peak input signal of 0.5 volts. The effectiveness of the filters are obvious. The solid state switches—triacs—turn on their corresponding lamps at filter output voltages equal to and higher than 1.5 volts.

Figs. 11a to 11d show four oscilloscope photographs. These show traces with the vertical axes representing voltages and the horizontal one time. In each instance the four traces were taken simultaneously (i.e. they have a common time axes). In the oscillograms the top trace corresponds to the voltage at the loudspeaker terminal. The other three traces were taken at the outputs of the respective filters.

Fig. 11a was taken at a time when the treble

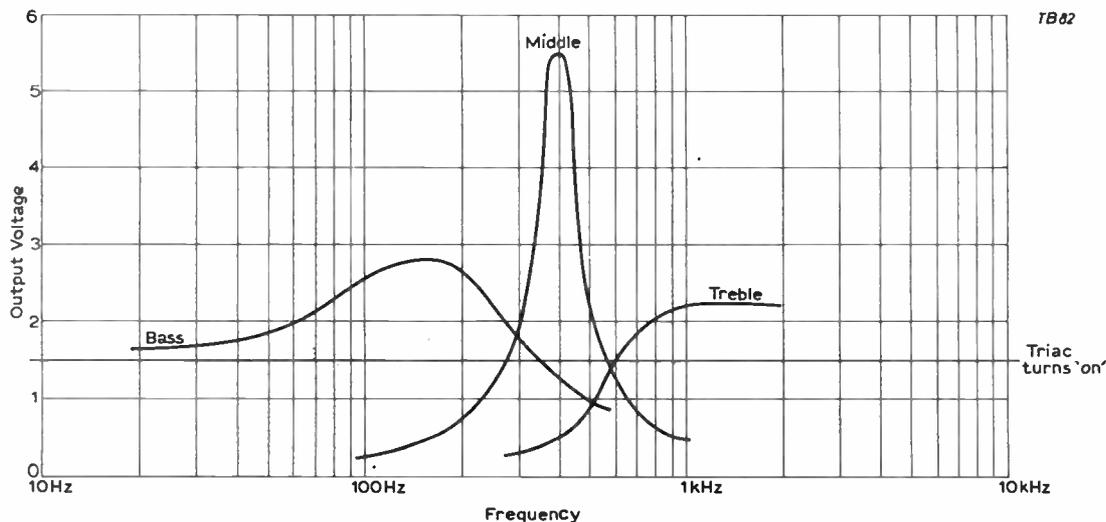


Fig. 10: Output voltage/frequency response of the filter circuit shown in Fig. 9.

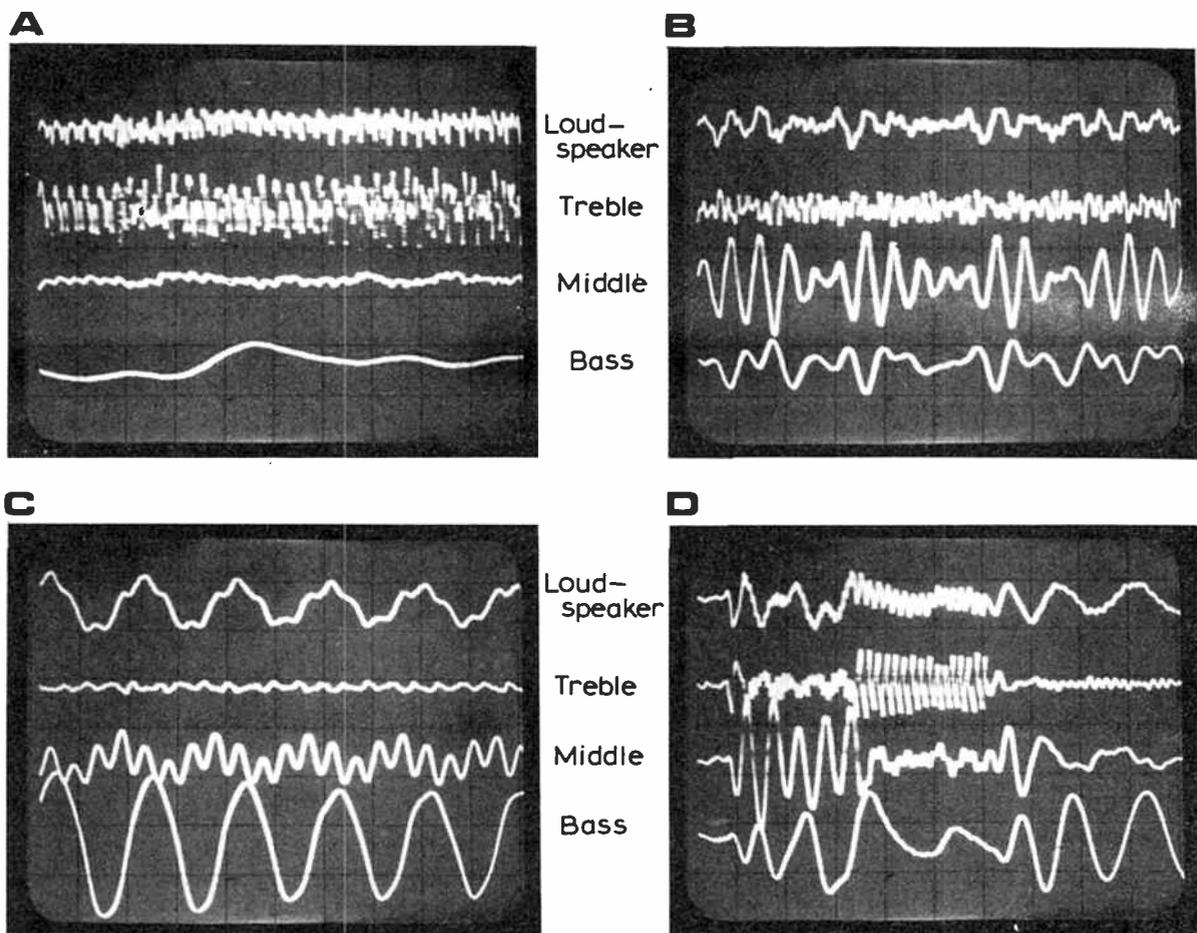



Fig. 11: (a-d) A full explanation of these waveforms is given in the accompanying text.

frequency was predominant. In Fig. 11b the middle frequency is the strongest signal, while in Fig. 11c it is the bass. Fig. 11d shows some interesting combinations of all three frequencies. The middle frequencies predominate at the beginning of the trace, then the treble takes over at the centre of oscillogram and towards the end of the trace it is the turn of the bass to predominate.

A 10k Ω potentiometer has been added at the input to the filter circuit to allow the voltage level at which the lamps are switched to be controlled. In this way it is possible to establish the best effect for 'soft' or 'party' type music.

The P.W. Tricolour is suitable for use with 4 to 15 Ω loudspeakers. The load represented by the filters is negligible compared to the loudspeaker impedance.

It should be noted that the simple filter circuits illustrated at the beginning of this article used operational amplifiers. An operational amplifier has high input impedance, very high gain, and low output impedance, enabling the filter component values to be determined independent of the amplifier parameters. The amplifiers used were shown having a voltage gain of unity. This means that the output voltage of the high and low pass filters can never

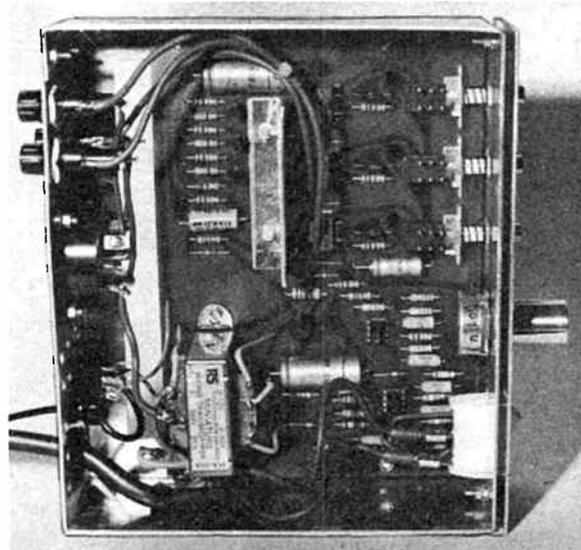

Underside view of the P.W. Tricolour with zero voltage switching.

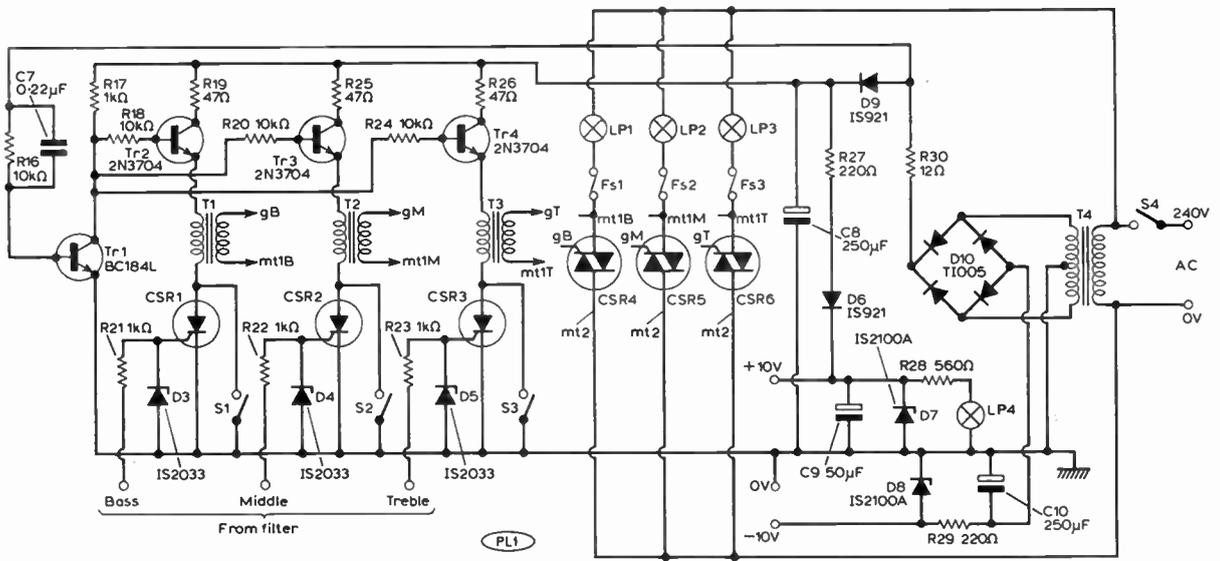


Fig. 12: Zero voltage switching control unit. The positive and negative 10V supply lines are the d.c. supplies to the filter unit (Fig. 9).

be more than the input voltage. In order to achieve voltage gain so that sufficient output can be obtained to drive the interface circuit at low volume levels, the basic circuit must be modified. This involves reducing the proportion of output voltage from the amplifier that is used as feedback to the filter capacitors and resistors. This is achieved by the use of a resistive potential divider at the output of the

amplifier. This is shown in Fig. 9. The resistor ratio determines the gain of the filter in the pass-band. The P.W. Tricolour is suitable for either mono or stereo record playing. In the case of the stereo system, the lights will flash in accordance with the signals appearing at the terminals of one of the speakers. However, for stereo enthusiasts who wish to use two units, the interconnecting arrangement will

★ components list

Resistors:

R1	1kΩ	R16	10kΩ
R2	56kΩ	R17	1kΩ
R3	56kΩ	R18	10kΩ
R4	22kΩ	R19	47Ω
R5	10kΩ	R20	10kΩ
R6	22kΩ	R21	1kΩ
R7	82kΩ	R22	1kΩ
R8	22kΩ	R23	1kΩ
R9	10kΩ	R24	10kΩ
R10	180kΩ	R25	47Ω
R11	47kΩ	R26	47Ω
R12	47kΩ	R27	220Ω
R13	4.7kΩ	R28	560Ω
R14	2.2kΩ	R29	220Ω
R15	1kΩ	R30	12Ω ½W

All 10% ½W unless otherwise specified

Capacitors:

C1	4700pF
C2	4700pF
C3	0.047μF
C4	0.01μF
C5	0.01μF
C6	0.01μF
C7	0.22μF
C8	250μF 25V
C9	50μF 25V
C10	250μF 25V

Transformers:

T1,	{ Pulse trans-
T2,	
T3	{ PT-ATA ITT Ltd.
T4	Miniature mains transformer 240V primary 0-12V, 0-12V r.m.s. 6VA, type 12V R.S. Components

Semiconductors:

Tr1	BC184L
Tr2	2N3704
Tr3	2N3704
Tr4	2N3704
D1	IS2051A
D2	IS2051A
D3	IS2033
D4	IS2033
D5	IS2033
D6	IS921
D7	IS2100A
D8	IS2100A
D9	IS921
D10	TI005 Bridge rectifier
CSR1	TIC44
CSR2	TIC44
CSR3	TIC44
CSR4	TIC226D
CSR5	TIC226D
CSR6	TIC226D

Texas Instruments Ltd.


Miscellaneous:

VR1	10kΩ linear potentiometer
FS1, FS2, FS3	5A fuses and panel mounting holders
LP1, LP2, LP3	Colour flood lamps, 240V 100W
LP4	TIL 209 Indicator lamp Texas
S1, S2, S3	Push on-push off
S4	Single pole mains on-off rocker

Integrated Circuits

IC1	SN72558P	} Texas Instruments Ltd.
IC2	SN72741P	

THE Medium Wave Column

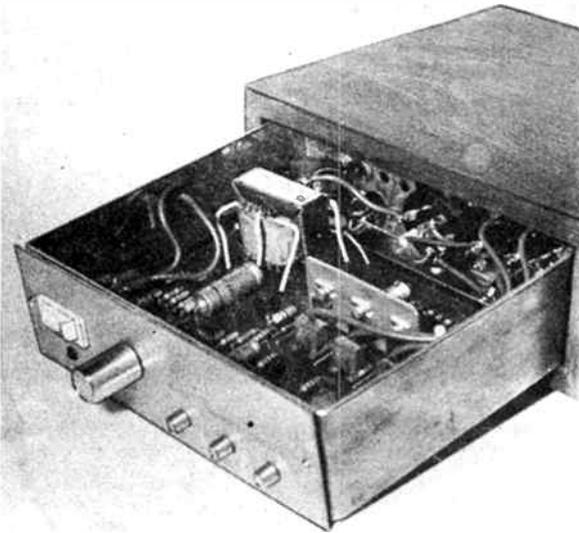

Internal view of the P.W. Tricolour.

be explained later.

Fig. 12 shows the circuit which operates the flashing lights according to the frequency ranges.

Switch S4 controls the mains supply to the unit from a 13A domestic socket. When the a.c. mains power is on the gallium arsenide device LP4 lights. A smoothed d.c. supply for transistors Tr1-Tr4 is obtained from a single phase bridge D10, resistor R30, diode D9 and capacitor C8. The $\pm 10V$ power supply for the filter circuit is taken from zener diodes D7, D8 and capacitors C9 and C10.

As described previously, the zero voltage crossing pulses are generated at the collector terminal of transistor Tr1. These pulses turn on transistors Tr2, Tr3 and Tr4 via base resistors R18, R20 and R24. When a voltage signal from the filter circuit appears at the input terminals, the corresponding thyristors CSR1, CSR2 or CSR3 will turn on allowing pulses to be present at the respective gate of CSR4, CSR5 or CSR6 which turn them and thus their lamps on. Pulse transformers T1, T2 and T3 are used only for electrical isolation.

Zener diodes D3, D4 and D5 limit the thyristors gate voltages to 3-3V in the positive direction and to under 1 volt during the negative half cycles.

Facilities are provided for 'by-passing' the psychedelic control by closing switches S1, S2 or S3 to allow the lamps to be used as normal lights. The centre tap of the 12-0-12V mains transformer is connected to the chassis and is earthed. Note that the three triacs are mounted on a common heat-sink, which is at the supply line voltage, i.e. 240V.

The author has made arrangements for the supply of all components for the P.W. Tricolour with Henry's Radio Ltd. We understand that a detailed price list will be available from them upon receipt of a stamped addressed envelope.

TO BE CONTINUED

J. KING (Edinburgh) asks for the times and frequencies of English speaking foreign stations on the medium waves. Among the stronger there are Radio Sweden which is on 1178kHz every night at 2245hrs; Radio Portugal on 755kHz and 1161kHz, also at 2345hrs and the Vatican Radio on 1529kHz at 2100hrs. There are also the American Forces Network (AFN) outlets on 872kHz, 935kHz and 1142kHz. Try for CJON St John's, Newfoundland on 930kHz—it can be found on the low frequency side of AFN on 935kHz after 2330hrs. CJON has been a strong and consistent signal all winter and it has even been heard when conditions have been poor and no other North American could be heard.

Harold Emblem (Mirfield, Yorkshire) has received a QSL card (verification) from Radio Zagreb Yugoslavia which transmits on 1133kHz. The address is Radio Televizija Zagreb, PO Box 818, Zagreb Yugoslavia and reports in English are answered. Harold mentions hearing PJA6 Radio Victoria on 925kHz, which is located in the Netherlands Antilles in the Caribbean. It broadcasts religious programmes in English and other languages and is usually heard in this country after midnight.

Harry Kenyon (Leeds) has been looking for a published list of medium wave stations. "Broadcasting Stations of the World" published by Iliffe is available in many bookshops price 50p. It covers medium wave stations in Europe and North Africa plus a number of more powerful outlets in other parts of the world, that are usually heard in Europe. There is also a comprehensive list of short wave stations.

Karl Ritz (Bicester) sends a programme schedule of BBC Radio Oxford which is now on 1484kHz. Frequencies in use by BBC local radio are 850kHz R. Blackburn, 998kHz R. Solent, 1034kHz R. Medway, R. Sheffield; 1106kHz R. Leeds; 1457kHz R. London, R. Birmingham, R. Newcastle, R. Manchester; 1484kHz R. Brighton, R. Humberside, R. Merseyside, R. Oxford; 1502kHz R. Stoke; 1546kHz R. Bristol, R. Teeside; 1594kHz R. Leicester.

Kenneth Turner (Edinburgh) has logged R. Birmingham, R. Stoke and R. Bristol and he reports hearing Manx Radio (Britain's only commercial radio) on 1295kHz and 1594kHz.

G. H. Esmail (Bradford) enquires about a suitable receiver for use on the MWs. Serious DXers prefer a communications receiver such as the Trio 9R59DS or the Lafayette HA600 but an ordinary transistor portable will pull-in Europeans and North Africans and if the receiver is rotated to make use of its internal directional aerial, it will be possible to reduce quite a lot of interference.

Please send logs and information about the medium waves to the author at 132 Segars Lane, Southport PR8 3JG.

DXers MW LOOP aerial

S.A.MONEY G3FZX

DURING the next two years the minimum of the current sunspot cycle should occur. Although short wave reception usually suffers at the period of the sunspot minimum the conditions will become very favourable for the reception of DX signals on the medium wave broadcast band. Unfortunately, the interference from European stations, many of which now remain on the air all night, is likely to be much worse than it was during the last sunspot minimum. In order to wrinkle out the weaker DX signals from the QRM it will be important to choose an effective aerial system as well as a good receiver.

In the late 1950's the writer, in collaboration with Reg Dunkley of Havant, Hampshire, carried out a series of tests to investigate the possibility of using a tuned loop aerial for the reception of DX signals on the medium wave band. These tests showed that although the loop aerial is somewhat less sensitive than the usual outdoor wire type aerial it has several advantages which make it attractive for DX work.

Pick-up of background noise and static seems to be rather less on the loop aerial than it is on a wire aerial so that although giving less signal the loop does usually give a better signal to noise ratio.


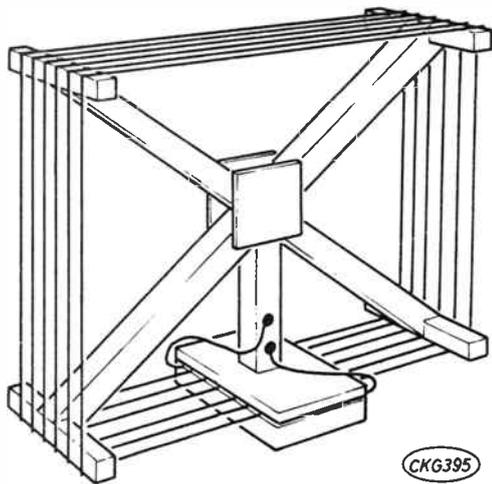


Fig. 1: Configuration of a typical m.w. loop aerial.

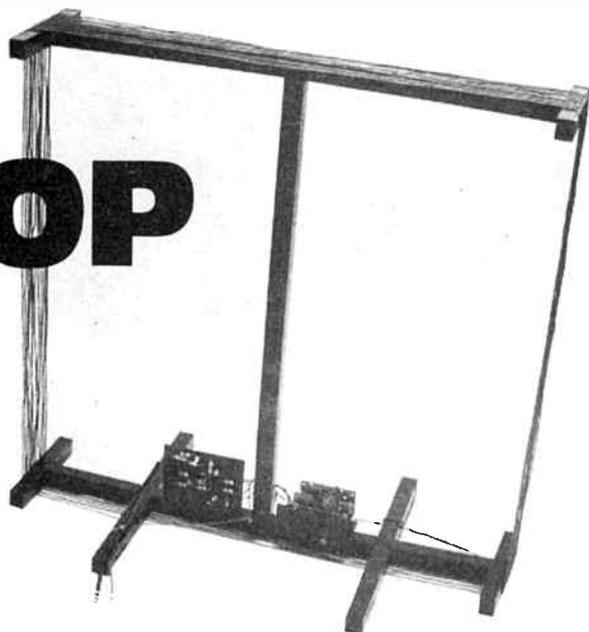

By rotating the loop aerial its directional properties can be used very effectively to cut down adjacent channel interference from strong European signals. A further advantage of the loop aerial is that it is very compact and hence attractive to the listener who is unable to use a large outdoor aerial system.

The advantages of the loop aerial have, in the past ten years, made it very popular among the medium wave DX enthusiasts in Britain.

Although the basic loop aerial as used by most of these DX'ers is quite effective it is not the optimum arrangement.

In the past year the writer has experimented with methods of improving the performance of this type of aerial. In this article a system is described consisting of a loop aerial and a matching amplifier capable of giving a performance superior to that of the basic loop aerial.

HOW THE LOOP WORKS

Before going on to describe the improved aerial system it would be as well to consider the make up of the basic loop aerial and the way in which it works. This type of aerial used to be a standard fitting in portable radios before the arrival of the ferrite rod aerial.

The loop aerial usually consists of a number of turns of wire wound in the form of a short coil on a large wooden frame. Typical aerials are square in shape as shown in Fig. 1 although circular or diamond shaped loops will also work. The length of the sides may be from 12in. up to about 4ft. In general, the larger size aerials give greater signal output and rather better directional properties.

Normally the turns of the winding are spaced apart from one another to reduce self capacitance. The whole aerial is then tuned to resonance by a variable capacitor connected across the ends of the loop.

To see how the loop works let us assume that there is only one turn as shown in Fig. 2. When radio waves pass through the loop a voltage will be induced in each of the vertical sides. These voltages are shown as V_1 and V_2 . The relative polarity of the two voltages is indicated by the arrows. It will be seen that the voltage at the terminals of the loop will be made up of V_1 and V_2 connected in series. When the two voltages are connected in this way they will be effectively in opposition to one another so that the resultant output voltage at the loop terminals will be the difference between V_1 and V_2 . In practice the two voltages are alternating and therefore the difference voltage will depend not only upon amplitude but also upon the phase of V_1 relative to V_2 .

Suppose the loop is set up so that it is broadside on to the direction from which the received signal is coming. This is shown in Fig. 3(a) which shows a view looking down on to the aerial. Both vertical sides of the loop will be at exactly the same distance from the transmitter aerial so the induced signal voltages V_1 and V_2 will be of the same amplitude and in phase with one another. At the output terminals the difference voltage produced will be zero since V_1 and V_2 will cancel out exactly. This is known as the 'null' position for the loop since there will be no signal output.

Now let us see what happens when the loop is turned so that it is in line with the direction of the signal being received as shown in Fig. 3(b). In this case one side of the loop is closer to the transmitter than the other. Since the width of the loop is very small compared with the distance to the transmitter the amplitudes of the induced voltages V_1 and V_2 will still be virtually equal. The radio wave will, however, take a finite time to travel from the near side of the loop to the far side so that V_2 will lag behind in phase relative to V_1 . This phase shift of V_2 will produce a difference signal output at the loop terminals. In fact at this position the loop will give its maximum output signal.

The resultant pick up pattern for a loop aerial will be as shown in Fig. 4(a). If extra turns are now added to the loop so that it forms a short coil the voltages produced by each of the turns will add together at the output terminals. As a result the output from the aerial will be proportional to the number of turns used. For a multi-turn aerial the pick up pattern will be the same as for a single turn. A further increase in output can be obtained if the aerial is tuned to resonance by connecting a variable capacitor across the ends of the loop winding.

"ANTENNA" EFFECT

One of the difficulties which occurs when using a loop aerial is known as the "antenna" or "vertical" effect. Unless the aerial is exactly balanced electrically with respect to earth it will act as a normal vertical aerial. A simple vertical aerial picks up the signal at equal strength from all directions in the horizontal plane. Now we get the condition that when the aerial is broadside on to the direction of the signal the voltages V_1 and V_2 cancel as before but the output due to "antenna" effect remains constant. This results in a pick-up pattern like that in Fig. 4(b) where the nulls are less marked and much broader than for a perfect loop.

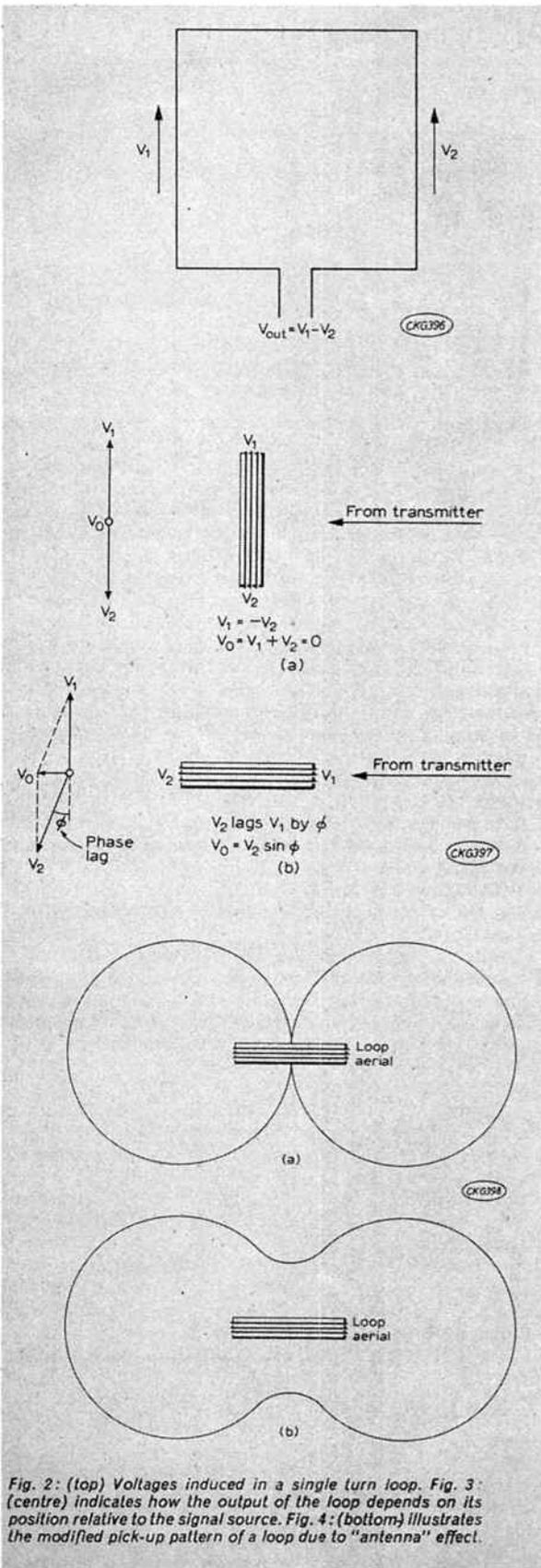


Fig. 2: (top) Voltages induced in a single turn loop. Fig. 3: (centre) indicates how the output of the loop depends on its position relative to the signal source. Fig. 4: (bottom) illustrates the modified pick-up pattern of a loop due to "antenna" effect.

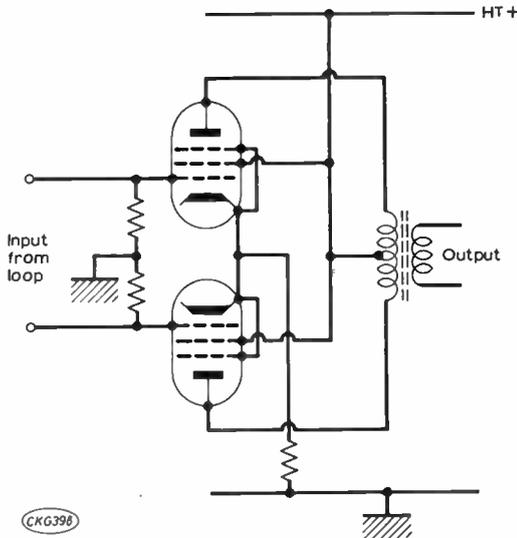


Fig. 5: Basic circuit of an early valve-type balanced input stage.

Perhaps the most obvious method of coupling the loop to the receiver would be to connect it directly across the aerial input terminals of the receiver. This method is rarely successful since the aerial will be unbalanced to earth and "antenna" effect is usually very bad.

For the basic loop aerial used by m.w. DX'ers the usual method of coupling is by means of a link winding. The link usually consists of one turn, or sometimes two, wound on the frame alongside the main winding. This link winding is then connected directly to the receiver input. With a link coupling of this type the aerial usually works quite well except that the link winding itself tends to produce some output due to "antenna" effect.

DIFFERENTIAL MATCHING AMPLIFIER

Wartime d.f. receivers, such as the R1155, made use of a differential or push-pull amplifier at the input. This type of amplifier uses two valves with

★ components list

Resistors

R1 47kΩ	R5 47kΩ	R9 10kΩ
R2 1kΩ	R6 2.2kΩ	R10 470Ω
R3 100Ω	R7 330Ω	R11 100Ω
R4 1kΩ	R8 330Ω	VR1 500Ω preset

All ½W 5%

Capacitors

C1 4.7nF polyester	C3 4.7nF polyester
C2 0.1μF min. foil	

Semiconductors

Tr1 2N3823	Tr3 2N3823
Tr2 2N706	Tr4 2N3823

their cathodes connected together as shown in Fig. 5. The resistor in the cathode circuit is made large enough so that it acts as a constant-current source. This type of amplifier responds only to differences in voltages between the two grids and will reject any signal common to both grids such as that produced by "antenna" effect in the loop aerial.

A balanced input amplifier using transistors instead of valves is shown in Fig. 6. In order to maintain a high value of Q in the aerial circuit a pair of field effect transistors is used for the differential input stage. This type of transistor has similar characteristics to a valve and gives a much higher input impedance than a normal bipolar type transistor. In this circuit 2N3823 'N' channel field effect transistors are used.

A differential amplifier works most effectively when the common-tail circuit of the input pair is fed from a constant-current source. In the valve version this is achieved by feeding the common cathode point through a large resistor from a negative supply voltage. In the circuit of Fig. 6 the transistor Tr2 is used to provide a constant current feed.

Characteristics of the 2N3823 may vary widely from one transistor to another. For optimum results the two transistors Tr1 and Tr3 in the input stage should either be matched or at least have similar characteristics. This can be checked by using the


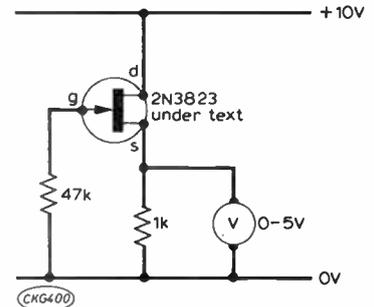


Fig. 6: (left) Complete circuit of the loop matching amplifier. Note that the 2N3823 transistor specified is preferable to the unscreened 2N3823E. Fig. 7: (above) is the circuit of the simple test set-up for checking the characteristics of the f.e.t.'s.

BRITAIN'S FASTEST SERVICE!

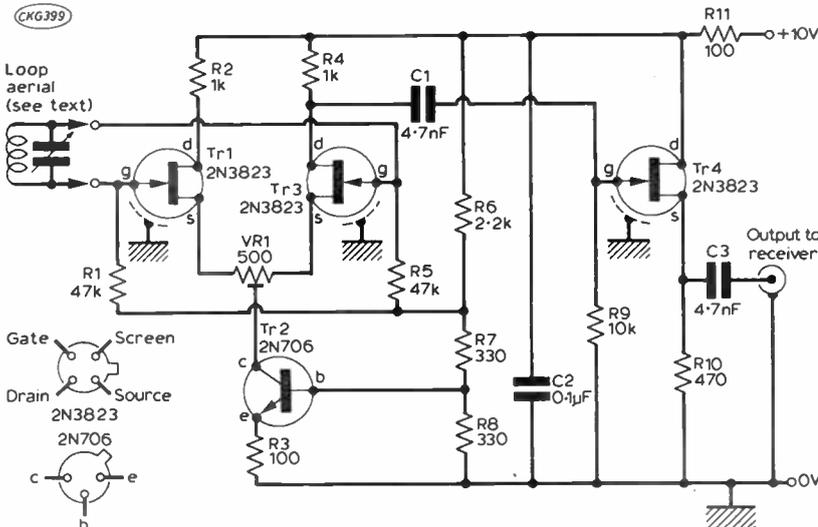

A SELECTION FROM OUR COMPLETE CATALOGUES

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	8p	BCY58	18p	CA3043	£1.73	OA81	8p	1N4007	19p	2N6027(D13T1)	
AC107	36p	BCY70	15p	CA3044	£1.42	OA90	8p	1N4148	4p		£1.30
AC126	20p	BCY71	30p	CA3045	36p	OA91	5p	1N5400	14p	3N84	45p
AC127	25p	BD121	15p	CA3048	£2.34	OA95	5p	1N5404	18p	3N128	88p
AC128	24p	BD124	75p	CA3052	£1.80	OA200	8p	1N5408	25p	3N140	£1.05
AC128/AC176		BD131	75p	CA3088E	£1.78	OA202	7p	1S444	4p	3N152	£1.05
AC151	12p	BD131/132	£1.50	CA3090Q	£4.70	OC20	97p	1S940	7p	3015F	£2.00
AC152	15p	BDY20	92p	CD4001AE	72p	OC28	70p	1S5009	80p	3015G	£2.00
AC153	19p	BF115	23p	CD4009AE	£1.58	OC29	78p	1S5012	80p	7401	20p
AC176	18p	BF163	18p	CD4011AE	72p	OC35	60p	1S5018	75p	7402	20p
AC153/176K	32p	BF167	18p	CD4012AE	£1.18	OC36	63p	1S5018	75p	7403	20p
AC187	17p	BF173	19p	CD4013AE	£1.41	OC41	40p	1S5024	75p	7404	25p
AC188	23p	BF177	25p	CD4015AE	£3.90	OC42	40p	2N4047	75p	7405	25p
AC187/188K	40p	BF178	31p	CD4017AE	£3.90	OC45	20p	2N696	15p	7408	25p
ACY17	27p	BF180	35p	CD4018AE	£3.90	OC45	20p	2N697	17p	7410	20p
ACY18	20p	BF184	15p	CD4020AE	£4.34	OC72	20p	2N698	30p	7413	30p
ACY19	20p	BF185	15p	CR1051C	45p	OC75	25p	2N706	10p	7420	20p
ACY20	20p	BF196	15p	CR1401C	60p	OC77	25p	2N706A	12p	7425	30p
ACY21	19p	BF200	35p	CRS3/05AF	£1.08	OC78	20p	2N708	50p	7430	20p
ACY22	10p	BF254	14p	CRS3/40AF	£1.53	OC81D	20p	2N911	50p	7440	24p
AD140	55p	BF255	15p	CZ6	15p	OC83	23p	2N914	20p	7442	£1.45
AD149	50p	BF133	25p	D10 (NTGD10)	45p	OC84	25p	2N929	25p	7444	£1.45
AD181	40p	BF269	25p			OC89	25p	2N930	28p	7445	£2.06
AD182	38p	BF284	25p			OC100	35p	2N1131	24p	7446	£1.45
AD181/182	70p	BF285	34p			OC100	35p	2N1132	24p	7447	£1.45
AF106	24p	BF286	25p			OC170	25p	2N1302	24p	7450	20p
AF114	25p	BF287	30p	IRT84	£2.00	OC170	25p	2N1303	17p	7451	20p
AF115	25p	BF288	24p	LIC709C/5	42p	OC31M	40p	2N1304	24p	7453	20p
AF116	25p	BFY30	15p	LIC709C/8	42p	OC31M	40p	2N1305	24p	7454	20p
AF117	44p	BFY51	15p	LIC723C/5	£1.02	ORP16	40p	2N1306	20p	7456	20p
AF118	44p	BFY52	15p	LIC723C/14	£1.00	ORP61	40p	2N1307	30p	7470	45p
AF124	25p	BFY53	17p	LIC741C/5	45p	ORP69	9p	2N1308	34p	7472	32p
AF125	24p	BFY90	£1.05	LIC741C/8	40p	PN70	50p	2N1309	34p	7473	45p
AF126	17p	BP101	75p	MC1303L	£1.75	PN107	7p	2N1559 (CR1)	60p	7475	45p
AF139	30p	BPX86	£1.35	MC1305P	£2.80	PN108	7p	2N1613	15p	7476	45p
AF188	40p	BRV39	40p	MC1307P	£1.65	PN108	7p	2N1711	15p	7480	£1.37
AF239	36p	BSX19	16p	MC1310P	£2.95	PN108	7p	2N1893	54p	7482	£1.37
AF279	40p	BSX20	16p	MC1312P	£2.75	PN108	7p	2N2218A	33p	7483	30p
ASV26	25p	BSX21	20p	MC1330P	£2.00	PN109	7p	2N2219A	38p	7486	60p
ASV27	30p	BSY27	20p	MC1352P	£2.00	PN3819(2N3819)	2N1711	2N2219A	53p	7479A	£1.28
ASV28	22p	BSY29	25p	MC4024P	£2.20	ST2	20p	2N2368	17p	7492	85p
ASV29	30p	BSY95A	12p	MC4044P	£2.20	ST2	20p	2N2369A	17p	7493	75p
BA138	15p	BY100	20p	MFC6030	£1.63	SL103A	50p	2N2369A	42p	7494	£1.13
BB103	8p	BY127	22p	MFC6040	£1.63	SL403A (Rec1)	60p	2N2369A	42p	7495	80p
BBX16	18p	BTY79/400R	92p	MFC8010	£1.38	SL403A (Rec1)	60p	2N2904A	44p	7496	£1.48
BB104	28p	BT106	£1.20	MFC8040	£1.24	SL803A	80p	2N2904A	44p	7499	£1.84
BB105	32p	BZY88C3V3	13p	MFC9020	£2.12	SL403D	80p	2N2905A	65p	74121	43p
BC107	10p	BZY88C3V6	13p	MJE371	88p	(IC Amp.)	£1.50	2N2905A	75p	74141	£1.00
BC107/BC177		BZY88C3V9	13p	MJE520	85p	TAA263	75p	2N2924	18p	74150	£3.35
BC108	10p	BZY88C4V7	13p	MJE521	82p	TAA293	97p	2N2925	20p	74151	£1.10
BC108/BC178		BZY88C5V1	13p	MJE2955	£1.06	TAA310	£1.25	2N2925	20p	74153	£1.35
BC109	23p	BZY88C5V6	13p	MJ480	97p	TAA320	75p	2N3053	27p	74154	£2.00
BC109/BC179		BZY88C8V2	13p	MJ481	£1.25	TAA361	45p	2N3055	50p	74155	£1.55
BC109C	24p	BZY88C8V7	13p	MJ481	£1.25	TAD100	£1.00	2N3391A	29p	74190	£1.80
BC140	30p	BZY88C9V1	13p	MJ802	£1.32	TAD110	£1.97	2N3525	9p	74191	£1.80
BC147	10p	BZY88C10V	13p	MJ802/MJ4502	£1.12	TIL112	£2.00	2N3702	9p	74193	£1.74
BC148	8p	BZY88C11V	13p	MJ900	£8.56	TIP31A	60p	2N3703	10p	74196	£1.35
BC149	10p	BZY88C12V	13p	MJ1000	£1.50	TIP42A	85p	2N3704	9p	74196	£1.35
BC157	12p	BZY88C13V	13p	MJ4502	£4.44	TIP42A	£1.00	2N3705	9p	74197	£1.50
BC158	11p	BZY88C15V	13p	MPF102	37p	TIS43	30p	2N3706	9p	40250	66p
BC159	12p	BZY88C16V	13p	MPF103(2N5457)	46p	VA1066A	15p	2N3707	9p	40309	40p
BC147/157	22p	BZY88C18V	13p	MPF104(2N5458)	49p	VA1039	15p	2N3708	7p	40310	42p
BC148/158	20p	BZY88C20V	13p	MPF105(2N5459)	49p	VA1040	15p	2N3709	9p	40311	42p
BC149/159	22p	BZY88C22V	13p	MPF105(2N5459)	W005	VA1077	15p	2N3710	9p	40312	85p
BC167	11p	BZY88C24V	13p	NKT0033	96p	W02	32p	2N3711	7p	40320	42p
BC168	12p	BZY88C27V	13p	NKT211	25p	W04	33p	2N3712	7p	40330	42p
BC169	11p	BZY88C30V	13p	NKT212	25p	W08	44p	2N3713	9p	40332	42p
BC177	14p	BZX61C8V2	23p	NKT213	25p	W08	44p	2N3714	9p	40332	42p
BC178	13p	BZX61C8V1	23p	NKT218	45p	ZT X107	12p	2N3819	25p	40360	58p
BC179	14p	BZX61C10V	23p	NKT217	50p	ZT X108	11p	2N3820	60p	40361	45p
BC182	19p	BZX61C11V	23p	NKT218	50p	ZT X302	13p	2N3823E	20p	40362	45p
BC182L	10p	BZX61C12V	23p	NKT218	50p	ZT X302	13p	2N3826	30p	40406	40p
BC183	9p	BZX61C13V	23p	NKT223	27p	ZT X302	15p	2N3826	£1.10	40407	40p
BC183L	10p	BZX61C15V	23p	NKT221	18p	ZT X303	11p	2N3904	28p	40408	40p
BC184	13p	BZX61C16V	23p	NKT274	18p	ZT X304	23p	2N3906	28p	40409	82p
BC184L	12p	BZX61C18V	23p	NKT275	20p	ZT X314	11p	2N4058	28p	40410	40p
BC212	12p	BZX61C20V	23p	NKT279A	15p	ZT X320	30p	2N4060	11p	40430	£1.22
BC212L	10p	BZX61C22V	23p	NKT281	29p	ZT X330	14p	2N4061	11p	40432	£1.60
BC238	10p	BZX61C24V	23p	NKT351	75p	ZTX500	18p	2N4062	11p	40468A	52p
BC238/308	20p	BZX61C27V	23p	NKT401	71p	ZTX501	15p	2N4444	£2.20	40512	£1.95
BC257	8p	BZX61C30V	23p	NKT402	77p	ZTX502	10p	2N4871	40p	40576	£1.70
BC258	8p	CA3004	£2.25	NKT403	65p	ZTX503	45p	2N5245	45p	40600	70p
BC259	9p	CA3005	£1.50	NKT404	60p	ZTX504	45p	2N5457(MPF103)	40p	40601	70p
BC307	12p	CA3011	82p	NKT405	79p	1N814	20p	2N5458(MPF104)	40p	40602	45p
BC308	10p	CA3013	£1.36	NKT406	62p	1N3754	20p	2N5459(MPF105)	40p	40603	70p
BCY30	25p	CA3014	£1.52	NKT713	29p	1N4001	7p	2N5459(MPF105)	40p	40669	£1.20
BCY31	4p	CA3018	88p	NKT773	25p	1N4002	7p	2N5459(MPF105)	40p	40673	88p
BCY32	50p	CA3018A	£1.18	NKT781	29p	1N4003	10p	2N5777	45p	40739	£1.50
BCY33	20p	CA3020	£1.55	NKT D10	10p	1N4004	12p				
BCY34	25p	CA3028A	88p	OA47	8p	1N4005	12p				
BCY38	30p	CA3035	£1.52	OA79	8p	1N4006	15p				

ELECTROLYTIC AXIAL LEADS

Mfd.	Working Voltage	Price	Mfd.	Working Voltage	Price
1 0	40v	7p	100	16v	6p
1 0	100v	5p	100	25v	6p
2 2	25v	7p	100	40v	7p
2 2	63v	5p	100	63v	10p
10	25v	5p	220	25v	8p
10	63v	5p	470	25v	9p
20	25v	6p	1000	25v	16p
22	40v	6p	2200	25v	30p
27	25v	6p	4700	16v	33p
47	40v	6p			

CAPACITORS—METALLISED POLYESTER

Stock values: MFD Price each
 0.01, 0.015, 0.022, 0.033
 0.047, 0.068, 0.10
 0.150, 0.220
 0.33
 0.47
 0.68
 1.0
 1.5
 2.2
 Order as "Polyesters" + Capacitance.

CAPACITORS—POLYSTYRENE

Axial leads. Clear encapsulation. 5% Tolerance. 160 volt working. Price each
 Stock values
 100pF, 150pF, 220pF, 330pF, 470pF, 560pF, 680pF, 820pF,
 1000pF, 1500pF, 2200pF, 3300pF, 4700pF, 5600pF, 6800pF, 8200pF,
 Order as: "Polystyrenes" + Capacitance.

ALUMINIUM HEAT SINKS

10DN 34p (Plain All undrilled)
 10DDR 43p (Plain All drilled 2 x To3)

LOW PRICED DIL IC HOLDERS

DRD 7 14 Pin DIL 15p DRD 8 16 Pin DIL 17p

NYLON NUTS AND BOLTS

Cheese head screw bolts. Nuts with integral washer. Moulded in high density nylon. Ideal for mounting "live" assemblies, power transistors, etc.
 Each pack consists of four nuts and four screw bolts.
 Pack No. Thread Length Quantity Pack Price
 HSN1 6BA 1/2 4 10p
 HSN2 5BA 1/2 4 10p
 Order as "Nuts and Bolts" + Pack No.

OPTO ELECTRONICS—3 devices

From our range—OCP71—42p, ORP1—50p, TIL209 Red led 35p




AMPLIFIERS FOR GUITAR PICK-UPS GRAM PICK-UPS RADIO or TAPE

OVERLOAD PROTECTION INCORPORATED. SOLID STATE CIRCUITRY

Suitable for application of Loudspeaker impedances between 8 and 30 ohms. Combinations not to measure less than 6 ohms across both speaker output jacks simultaneously.

The Amplifier cover is made of rigid plastic, bonded metal on top and two sides. Finished in Black to suitably contrast with anodised metal control panel. Size approx. 14" x 4 1/4" x 9 1/2".

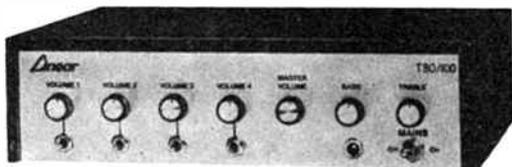From April 1st prices are subject to VAT.



Rec. Retail Price

£69.75

GENERAL PURPOSE AMPLIFIER

Model T80/100 70 - 100 Watts Output Power

Four individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'.

Compact size, robust construction. Ideal for clubs, hotels, restaurants, schools etc.

Inputs for almost any type of microphone

GENERAL PURPOSE GROUP/DISCO AMPLIFIER Model T80/100D


70 - 100 Watts Output Power

Three individually controlled inputs plus Master volume control. Bass and Treble Controls providing both 'lift' and 'cut'.

Compact size. Robust construction. Ideal for discotheques, clubs, hotels, schools, etc. Inputs for most types of microphones. Facilities for head-phone monitoring with changeover switch from input (1) to input (2).

Rec. Retail Price

£69.75

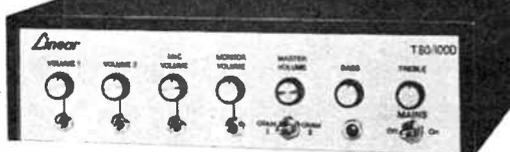

Wholesale and Retail enquiries to the Manufacturers Send S.A.E. for leaflet/s All Linear Amplifiers Guaranteed for 12 Months

LINEAR PRODUCTS LTD., Electron Works, Armley, Leeds. LS12 3SA Tel. 630126

GUNTON ELECTRONIC IGNITION KIT inc. V.A.T.

£9.35

PRINTED CIRCUIT BOARD DESIGN. ALL METALWORK READY-DRILLED

READY BUILT UNIT GUARANTEED 5 YEARS

£11.55 inc. V.A.T.

Patents pending. 12 volt only—state pos. or neg. earth Capacitive discharge ignition is recognised as being the most efficient system and will give you:

- ★ Continual Peak-Tuned Performance
- ★ Up to 20% reduced fuel consumption
- ★ Easier All-weather Starting
- ★ Increased Acceleration and Top Speed
- ★ Longer Spark Plug Life
- ★ Increased Battery Life
- ★ Elimination of Contact Breaker Burn
- ★ Purer Exhaust Gas Emission



Kit includes absolutely everything for assembly: Case, Cables, Coll Connectors, Silicon Grease, etc. 8 page illustrated instructions cover fitting of all Types of Tachometers. Call in for a Workshop Demonstration. S.A.E. all enquiries please or Phone 33652 (many letters from satisfied customers).

ALUMINIUM BOXES

Complete with baseplate and screws

At direct from manufacturer prices with return of post service

Type No.	L	W	D	Price
7*	5 1/2	2 1/2	1 1/2	44p
8*	4	4	1 1/2	44p
9*	4	2 1/2	1 1/2	44p
10*	5 1/2	4	1 1/2	53p
11	4	2 1/2	2	44p
12	3	2	1	39p
13	6	4	2	59p
14	7	5	2 1/2	68p
15	8	6	3	88p
16	10	7	3	96p

*THESE SIZES ACCEPT STANDARD VEROBOARD RANGE ALL PRICES INCLUDE V.A.T.

20% DISCOUNT ON ORDERS FOR 10 OR MORE BOXES

DEPT. PW 4 ELECTRONICS DESIGN ASSOCIATES
82 BATH STREET, WALSALL WS1 3DE

FELSTEAD ELECTRONICS (PW 67) LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas, and with all orders on request). Cash with order only—No C.O.D. or Gallie service. Charges (Min. 7p) in brackets after all items apply to G.B. and Eire only. Re get orders under 25p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas Orders welcomed.

RECORDING TAPE: Finest quality/value British Mylar available: STANDARD 5" 600ft. 40p, 5 1/2" 900ft. 55p; 7" 1200ft. 82p; LONG PLAY 5" 900ft. 55p; 5 1/2" 1200ft. 52p; 7" 1800ft. 21.00 (Charges for 5" and 5 1/2", singles 9p, two to four 9p each; five and over 39p the lot. For 7", one or two 11p each reel. 3, 4 and 5 reels 33p the lot. 6 reels and over 39p the lot.) Other sizes and accessories in list. CASSETTES in lib cases new type highly improved quality C60 65p, C90 72p, C120 89p (under 5, 9p each; 5 for 17p the lot; any quantity over 5, 28p the lot).

CARTRIDGES all with standard fittings and styli. Stereo-compatible Mono GP91/8C 98p; STEREO (GP93 21.35, Stereo Ceramic GP94 21.75. (All at 7p each.) Comparative shows in List, with more types inc. Sonotone 9TAHC, Stereo Ceramic Diamond 21.70 (7p). DIAMOND STYLII: single tip types: Acos GP37, GP69, GP65/67, GP71, BBR TC8/LE/ST; COLLARO O.P. and DC284, GARRARD GC2, GC8, GC810, GCE12, RONETTE BP40. O.P. and T. PHILIPS 3301 (3060, 3066, 3302, 3304), 3010/12/13/16, SONOTONE 19T/20T ALL AT 38p each (7p). SAPPHIRE 16p (7p) DIAMOND DOUBLE TIP TURNOVER TYPES (78 sap, on other side). For ACOS GP73, GP91 (for cartridges GP93, GP94 etc.); GP91 (for stereo compat. types) GP104 BBR STA (8T3, 8T6), 8T9 (8T8), 8T12/14/16, SONOTONE STA, 9TA, 9TAHC. PHILIPS 3306 3310, 3224, 3228/22 GP280, GARRARD GCM21, and 22, GC823, GK825 and 26, GCM21T and 22T, GCM24T GC823, GK825T and 26T, GCM31, GC836, GC835, GC838, K840A, K841B ETC. ALL AT 68p (7p). SAPPHIRE 32p (7p). DOUBLE DIAMOND STYLII: same dia 8T/1P 4p each side; no 78) All types 21.35 (7p). SAPPHIRE DOUBLE 8T/1P, TIPPED 32p (7p).

PICK-UP WIRE: super thin flex screened, sheathed, TWIN 7p per yard; 4-core 12p per yard (either up to 6 yds. 7p). Over, charges paid. MICROPHONES: CRYSTAL: LAPEL 11", clip/hand, lead 3.5mm jack plug 39p (9p). CM20 Cream Plastic hand 58p (9p); CM30 "PLANET" Metal, tapered with neck cord, adaptor for stand 21.65 (11p); "MIC 45". Curved metal hand grip 21.10 (11p) ALL with leads. DYNAMIC: 209 Cardloid Ball. 50K/600 0 built in volume control, on/off switch, special 20t lead, the best value anywhere at 28.80 (33p); UD130, uni-dir mean ball 50K/600 0 Jack plug, cable adaptor, 25.25 (22p); DM190, omni-dir, Ball mesh, 50K, cable adaptor, Jack plug, 24.29 (33p each). SPEAKERS: Very popular 1 1/2" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) 22.06 (33p) or pair for stereo 24.45, charges paid. SMALL 2 1/2", 3", 8" or 64" (state which) 36p (9p). More speakers in List. HEADPHONES: High resistance 2000 0 adjustable 21.10 (11p). EARPIECES: with lead and min. 2.5mm or 3.5mm (state which) Jack plug. MAGNETIC 11p. CRYSTAL (3.5mm plug only) 22p (up to 6 for 9p any size).

BOLDING IRON: Slim, modern, British high speed, 81", all parts replaceable, highest quality, fully guaranteed 21.29 (11p). TRANSFORMERS: Sub-min 11" x 11" x 12mm. OUTPUT (3 0 for OC2, etc.) 16p or DRIVER 17p (Up to 12 for 7p). CONNECTING WIRE: Packs of 5 coils, each coil 5yds. Aestul. coils. SOLID CORE 16p (7p.) FLEXIBLE CORE 18p (9p). SUPER THIN flexible for transistor wiring, etc. 18p (7p) RETRACTABLE FLEXIBLE LEADS (CURLIES): With phono plug, each end, 6ft 26p, 12ft 44p. With phono plug/phono socket other end 6ft. 29p, 12ft 50p (6p lead any type). VIBRATORS: 12V/4 pin non-synch 121H14, 2 1/2" ex. pins, 25p, SAME but 3 1/2" ex. pins, USA 18p, 12w/7 pin synch (125R7) 2 1/2" ex. pins, 72p any type. MAINS NEONS, 5y leads 11p. NEON SCREWDRIVER (pocket tester) 19p (7p) either. MAINS BATTERY ELIMINATOR. Input 240v-A.C. Output 3, 4, 6, 7, 8 and 12 volt D.C. by switch selector. On/off switch, pilot lamp, leads, plug to suit most cassette recorders, 24.18 (27p). Highly suitable for all transistor receivers.

SPECIAL NOTICE—BETWEEN FEB. 22nd and MARCH 14th SOME DELAY IN DESPATCH OR ORDERS AND REPLIES TO CORRESPONDENCE MAY OCCUR DUE TO RECONSTRUCTION. ALL ABOVE PRICES HAVE BEEN ADJUSTED TO INCLUDE V.A.T. BUT FOR ALL ORDERS DESPATCHED BY US UP TO MARCH 31st, PRE-VAT PRICES AS PER LAST MONTHS ADVERTISEMENT WILL APPLY.

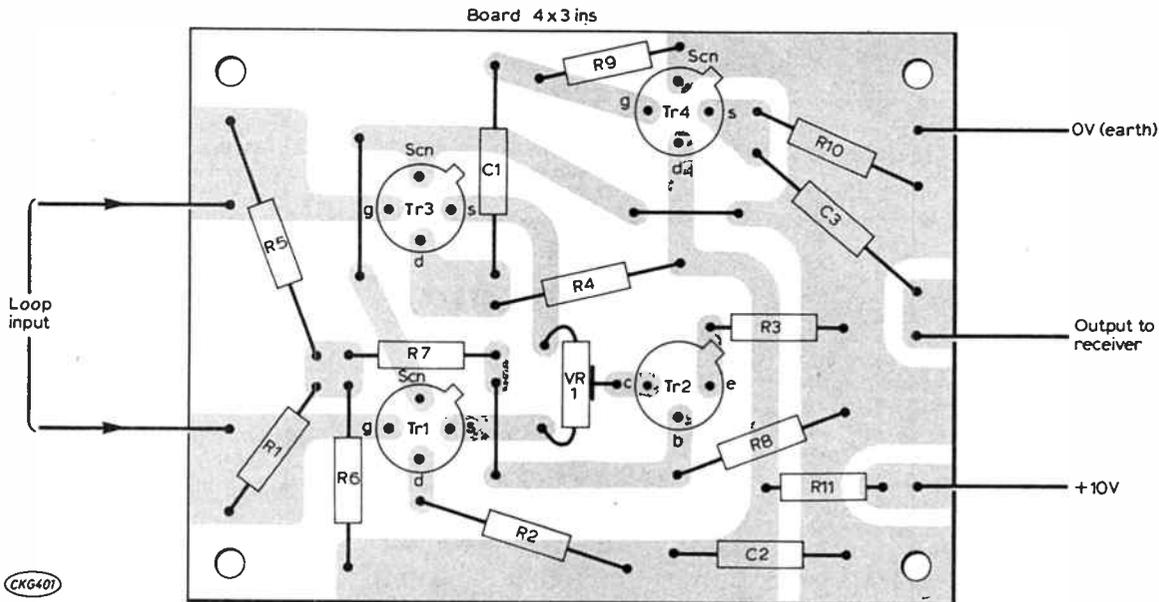


Fig. 8: Full size illustration of the printed circuit board, from the copper side. Small holes are drilled for component leads and the components mounted from the other side of the board.

circuit of Fig. 7 to select two 2N3823 transistors giving a similar voltage drop across the $1k\Omega$ resistor in the test circuit. The balanced amplifier itself will tend to level out small differences between the transistors.

Transistor Tr4 acts as a source follower and is used to match the output from Tr3 into the low impedance of the cable and the receiver input circuit. Capacitive coupling is used to the output so that if the cable is accidentally short circuited the transistor Tr4 in the output stage will not be destroyed.

CONSTRUCTION

It is convenient to build the amplifier on a small circuit board and to mount it close to the tuning capacitor on the main loop frame. A suggested layout for a printed circuit board for the amplifier

is given in Fig. 8. As an alternative the amplifier may be built on a piece of Veroboard. It should be noted that the screen leads of the 2N3823 transistors are connected to earth.

To test the aerial system the input amplifier stage should first of all be balanced. Connect a meter between the drains of transistors Tr1 and Tr3 and adjust the preset resistor VR1 until the voltage is zero. The two transistors will now be drawing equal currents.


Tune in a fairly strong signal from a known direction and rotate the aerial to obtain maximum pick up. At this point the loop should be tuned to resonance by means of the tuning capacitor as indicated by a further increase of signal when resonance is reached.

If the aerial is now rotated so that it is roughly broadside on to the direction of the station being heard a point should be found where the signal falls to a low level. A further small adjustment of VR1 may enable the signal to be reduced even lower.

THE LOOP

The loop aerial used by the writer has 12 turns on a 24in. square frame. To reduce self-capacitance and give more turns for the same inductance the turns are spaced $\frac{3}{4}$ in. apart. For the winding 14/0.0076 p.v.c. covered flexible wire is used. Tuning is by a 365pF air spaced variable capacitor across the ends of the loop winding.

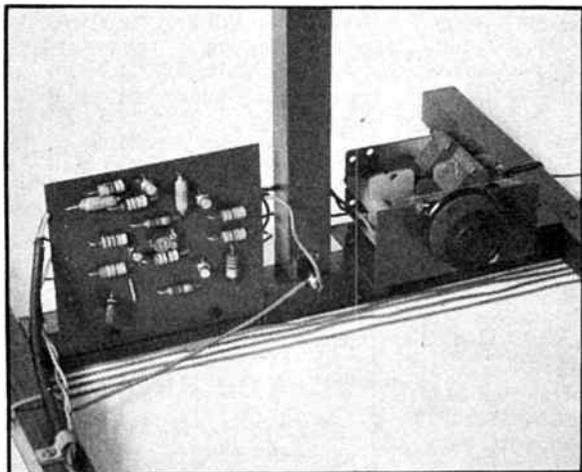Signal pick-up for this loop with its amplifier was found to be some 20dB up on the signal from a 30ft. outdoor wire aerial. Using a Lafayette HE30 receiver the signal reading on the 'S' meter varied from S9+60dB at the maximum pick up point to about S3 when the loop was rotated to the null position. The null point itself is sharp and extends over perhaps only two or three degrees. ■



Close-up of the matching amplifier and loop tuning capacitor.

LETTERS

The Editor does not necessarily endorse the views expressed by correspondents

"Mobile" dog sledge

In the February 1973 issue of *Practical Wireless* on page 890 you have a little note about working amateur radio from a dog sledge, stating that this might have been the world's first QSO from a dog sledge mobile installation. I would like to point out to you that there have been a number of radio amateur contacts from dog sledges over the past years. My first contact from a dog sledge installation was made in 1938 and I am quite sure that that was not the first one in the world.

The UK expedition which some years ago tried to reach the North Pole from Alaska also carried amateur radio equipment and had a number of contacts with the outside world. A Norwegian expedition which also some years ago tried to reach the Pole from the northern part of Greenland had practically all their contacts with the outside world made by amateur radio. Both these expeditions relied on dog sledges for their transportation.

In Norway and no doubt also in other countries with similar snow conditions amateur operations from dog sledges are not infrequent, and I myself have done it many times. I thought you might be interested in knowing this. **Lars R. Heyerdahl**, LA6A. (*Oslo 2, Norway*).

Don't get knotted!

A serious error was made by somebody when he knotted the mains input cable, as illustrated and described in the text on the battery eliminator (on pages 920 and 921).

This can be very dangerous and is specifically outlawed by the Institute of Electrical Engineers in their published regulations.

If a cable is rapidly bent from a straight to a highly twisted configuration, as often occurs when an item is knotted and the knot pulled tight rapidly, the core material may suffer from local fatigue causing cracking of the material. The cracking acts as a resistance to the current flowing through the appliances, hence

local heating occurs.

The error, though dangerous is so common that M. Wallis could be excused it, provided the suggested warning is printed.

I would suggest that one of the plastic cable clamps, to secure mains leads, should be used. **S. A. East**, (*Enfield, Middlesex*).

Midget radio phones

Over the Christmas holiday I assembled the *Practical Wireless* midget radio, lashed it to the head-band of some wartime crystal 'phones and got good listening for radios 2 and 4 and others between.

The hospital wards being quietish, I set off on some market research: men and women patients listened and all said that such lead-less headphones would be much appreciated, since they currently roll about and pull out the lead, and also cannot use 'phones when sitting out in the middle of the ward. They need to be lighter than my prototype, perhaps built onto a stethophone; and as not a few are hard of hearing, a bit more volume is needed. If we want Radio Humber-side or television sound (the ward set provides vision only) we should need something more sophisticated I suppose. Also an experienced Charge Nurse said if 'phones are not on leads I shall need to put them on chains!

Incidentally, when walking home across the common in the fog the wireless 'phones directionality helps personal alignment!—**Dr. H. F. Barnard**, Pathologist *East Riding Group Laboratory, Westwood Hospital, Beverley, Yorks. HU17 8BU*.

25 years of transistors

I was especially interested in Mr. R. Collins's article, 25 Years of the Transistor, because he attributed the research and development that led to it to the Bell Company's need for a substitute for the valve in the telephone service, in the 1940's.

I think that there must have been a lot that went before because men were looking for a substitute for the valve as early as

1920, and soon after, in the "Amateur Wireless" of those days, an account was published of a Russian scientist who was experimenting in making crystals perform all the functions of valves.

I remember this well because, as a schoolboy, I put this down as my own scientific basis for an application for an Experimenter's Licence.

Unfortunately, I went to New Zealand afterwards, and lost touch with radio, but I wonder if any other reader can recall what, if any further developments there were in those experiments.—**John Pinches** (*London, N.W.7*).

[A semiconductor substitute for the valve is now in production. It has improved characteristics and longer life and uses field effect transistor principles. This device, called a FETRON, will be described in full in next month's *Practical Wireless*.]—Editor

CQ! Gambia

We have been asked by the General Manager of the RSGB to publicise the following letter received by him:—

Whilst on a visit to West Africa recently, I was able to visit the transmitting station of Radio Gambia. I was asked to make an appeal to British S. W. listeners to report to them any reception of Radio Gambia in Britain.

The point is that they have received reports and QSL cards from Australia and America, but would very much like to hear from any British listener. I understand that the transmissions are as follows:—

Radio Gambia, 4.82MHz in the 60metre short wave band.

They tell me the best time for a reception would be between 10.30 p.m. and 11.30 p.m. **George Wallace, M.P.** (*House of Commons*).

DID YOU KNOW...

... a subscription to *P.W.* for one year costs £2.65 to any part of the world...

V.A.T. WILL NOT BE CHARGED IF YOU POST YOUR ORDER BY 31.3.73

BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. AC 200/250V. Size 13 1/2 x 1 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO and MONO XTAL MONO-COMPATIBLE. Plays all records.



£8.75 Post 25p.
£7.75 Post 25p.

BSR JUNIOR

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono cartridge. £4.50 Post 25p



E.M.I. WOOFER AND 12.5 75 TWEETER KIT

Available separately. Post 25p. Woofer £4.25, Tweeter £1.90. Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 440s. Gauss 13,000 lines. Aluminium Cone centre to improve tone and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied. Impedance Standard. 8 ohms. Maximum Power. 12 watts. Total Response. 0 to 60,000 cps. Bass Resonance. 45 cps. SUITABLE ENCLOSURE 20 x 13 x 9 in. £9 POST 25p. MODERN DESIGN TEAK WOOD FINISH



SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP TIME SWITCH
Single pole two-way.
Maker's last list price £4.50.
Brand new and fully guaranteed. Surface mounting with fixing screws. Will replace existing wall switch to give light return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. OUR TYPES available 0 to 60 minutes or 0 to 8 hours. OUR PRICE £1.50. P. & P. 15p or £2 pair Post Free. (Please state type when ordering.)



WEYRAD P50-TRANSISTOR COILS

RA2W Ferrite Aerial. 72p. Spare Cores. 3p. Osc. P50/1AC. 33p. Driver Trans. LFD74 58p. Printed Circuit. PCA1 58p. 3rd I.F. P50/8CC. 38p. J.B. Tuning Gang. 65p. P51/1 or P51/2. 38p. Weyrad Booklet. 10p. P50/3V. 38p. OPTI. 58p. Mullard Ferrite Rod 8 x 1/4 in. 20p, 6 x 1/4 in. 20p.

VOLUME CONTROLS

80 Ohm Coax 4p. yd. BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1.40; 80 yd. £2. STEREO L/R 50p. D.P. 75p. Edge 5K.S.P. Transistor 25p. Ideal 625 & colour 10p yd.


8in & 10in ELAC HI-FI SPEAKERS

Dual cone plasticised roll surround. Large ceramic magnet. 50-10,000 cps. Bass resonance 55 cps. 8 ohm coil. 8in. 10 watt. £3.75 Post 25p. 10in. 12 watt minio power.




E.M.I. 13 1/2 x 8in. SPEAKER SALE!

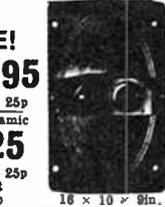With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 25p. With flared tweeter cone and ceramic magnet, 10 watts. Bass res. 45-60 cps. Price 10,000 cps. £2-25. State 3 or 8 or 15 ohm. Post 25p. TEAK CABINET £5 Post 25p. 16 x 10 x 9 in.



BRITISH MADE STEREO MULTIPLEX DECODER

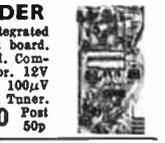Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 2 1/2 x 6 1/2 in. Pre-aligned. Complete with stereo beacon indicator. 2V d.c. operation. 400mV output for 100V input. Full instructions for any FM Tuner. Some technical experience £6.50 Post essential.



BLANK ALUMINIUM CHASSIS 18 s.w.g. 2 1/2 in. sides. 6 x 4 in 45p; 3 x 7 in. 60p; 1 1/2 x 7 in. 70p; 1 1/2 x 9 in. 90p; 1 1/2 x 11 in. 95p; 1 1/2 x 14 in. 99p; 1 1/2 x 11 in. 50p; 1 1/2 x 10 in. 41. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 8p; 8 x 6 in. 15p; 14 x 3 in. 16p; 10 x 7 in. 19p; 1 1/2 x 6 in. 20p; 12 x 8 in. 28p; 16 x 6 in. 28p; 14 x 9 in. 34p; 12 x 12 in. 40p; 16 x 10 in. 50p

WHARFEDALE SUPER 10" HI-FI SPEAKER

15 watt 4 to 8 ohms. Response 20 c/s to 12 Kc/s. Bass resonance 42 cps. Massive Ceramic Magnet. Deep fabric cone surround. Cast alloy frame. Weight 5 lbs. Value £10-50

OUR PRICE £5.50 Post 25p

THE FAMOUS WHARFEDALE SOUND!

R.C.S. STABILISED POWER PACK KITS
All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V. AC. Output voltages: 500V/500mA 5 or 9 or 12 or 15 or 18 or 20V. DC at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. £2 POST FREE. Details S.A.E. Size 3 1/2 x 1 1/2 in.

GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar. Can be used with Battery 9-12v or H.T. line 200-300V D.C. operation. Size 1 1/2 x 1 1/2 x 1 1/2. Response 25 c.p.s. to 25 Kc/s. 25db gain. For use with valve or transistor equipment. Post Full instructions supplied. Details S.A.E. 90p 10p

NEW TUBULAR ELECTROLYTIC CAP TYPES

2/350V .. 14p	250/25V .. 14p	50-50/350V .. 35p
4/350V .. 14p	500/25V .. 20p	100-100/35V .. 58p
8/450V .. 14p	1000/25V .. 35p	32-32/350V .. 18p
16/450V .. 15p	1000/50V .. 47p	32-32/450V .. 33p
32/450V .. 20p	8+8/450V .. 18p	350+50/325V .. 50p
25/25V .. 10p	8+16/450V .. 20p	32-32-32/350V .. 43p
50/50V .. 10p	16+16/450V .. 25p	100+50+50/350V .. 48p
100/25V .. 10p	32-32/350V .. 25p	

LOW VOLTAGE ELECTROLYTICS

1. 2, 4, 8, 16, 100, 200µF. 15V. 10p.
500µF. 12V. 15p; 25V. 20p; 50V. 30p.
1000µF. 12V. 17p; 25V. 35p; 50V. 47p; 100V. 70p.
2000µF. 6V. 25p; 25V. 42p; 50V. 57p.
2500µF. 50V. 62p; 3000µF. 25V. 47p; 50V. 65p.
5000µF. 6V. 25p; 12V. 42p; 25V. 75p; 50V. 85p; 50V. 95p.

CERAMIC 1pF to 0.01µF. 4p. 81vtr Mica 2 to 5000pF. 4p PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1% 2.2-500pF 8p; 500-2.200 pF 10p; 2.700-5.600pF 20p; 6.800pF-0.01µF 30p; each. TWIN GANG. "0-0" 208pF-1760pF. 65p; Slow motion drive 385-568 with 25-568 with 25-568 with 25-568 with 45p; Single gang 500pF. 75p; small 3-gang 500pF. £1.80. SHORT WAVE. SINGLE. 10pF 30p; 50pF 55p; 50pF 55p. NEON PANEL INDICATORS. 250V AC/DC Amber 20p. RESISTORS. 1 w. 1/4 w. 1/2 w. 1/2 w. 5p 10 ohms to 10 meg. HIGH STABILITY. 1/4 w. 2p. 10 ohms to 6 meg. 10p. DITO 5% Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS. 5 watt. 10 watt. 15 watt 10 ohms to 100K 10p each; 2 1/2 watt. 1 ohm to 8-2 ohms 10p. TAPE OSCILLATOR COIL. Valve Type 35p.

GARRARD DECCA DISCO DECK

£18.50 Post 25p
Single Play Stereo Mono
Derram transcription
head and arm. Form
speeds. 10 1/2 in. turn-
table. Anti-rumble
filter. Bias compensa-
tion. Laboratory
motor.



METAL PLINTH & PLASTIC COVER

Cut out for most Garrard or B.S.R. Most will play with cover in position 12 1/2 x 14 1/2 x 7 1/2 in Covered in black leatherette £4.50 Post 35p

ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH-AT SAME PRICE

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80 mA. 6.3 v. 4 amp. £1.50
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2.50
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £3.00
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T. 6.3 v. 2 a. £3.25
MIXTURE 200 v. 120 mA. 6.3 v. 1 a. or 5 v. 2 a. £2.75
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p
HEATER TRANS. 6.3 v. 3 a. 60p
GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 8, 9, 10, 12, 15, 18, 24 and 30 v. £2-25
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60, £2-25
2 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60, £2-25
5 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60, £2-75
3 amp. 5, 8 and 13 v. £1.00; Dito 5 amp. £1.20.
3 amp. 3, 5, 8, 10, 13 and 0-5-5 v. £1.30; Dito 5 amp. £1.50
AUTO TRANSFORMERS 115v. to 230v. or 230v. to 115v. 150w. £2-25; 500w. 48-25; 750w. 41.00; 1000w. £14
CHARGER TRANSFORMERS. Input 200/250 v. for 6 or 12 v. 1 1/2 amp. 1 1/2 amp. £1.80; 4 amp. £2.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.
BATTERY CHARGERS. 1A. £2; 3A £3; 4A £4.
LUCAS 2D8500 Full wave Bridge 70V 5 amp 96p.

FACTORY ACT 1 MAINS ISOLATING TRANSFORMER

Primary 0-110-240 v. Secondary 0-240 v. 3 amps. 720 watt. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make. Value £19. OUR SPECIAL PRICE £10 50p. Can be used as 800 watt Auto Transformer 240-110V.

ALL MODELS "BAKER SPEAKERS" IN STOCK

Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free

BAKER 12in. MAJOR £9

P. & p. 25p
30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell's. Bass resonance 40 c.p.s. Rated 20 watts. Voice coils 3 or 8 or 15 ohms.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50 P. & p. 25p.

BAKER "BIG-SOUND" SPEAKERS P. & p. 25p
'Group 25' 12 inch 25 watt 3 or 8 or 15 ohm £8
'Group 35' 12 inch 35 watt 3 or 8 or 15 ohm £9
'Group 50' 15 inch 50 watt 8 or 15 ohm £20

TEAK VENEREED HI-FI SPEAKER CABINETS
For 12in. or 10in. dia. speaker 20 x 13 x 9in. £5. Post 25p
For 13 x 8in. or 8in. speaker 16 x 10 x 9in. £5. Post 25p
For 10 x 8in. or 8in. speaker 16 x 8 x 6in. £4. Post 25p
LOUDSPEAKER CABINET WADDING 18in. wide, 15p. It.

GOODMANS 6 1/2 in. HI-FI WOOFER £4

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns, Hi-Fi Enclosures Systems, etc. 8in. STANDARD CORE 12W. £4.50, post 25p.

ELAC CONE TWEETER
The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 2 1/2 in. deep. Rating 10 watts, 3 ohm or 15 ohm models. £1-90 Post 10p

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16Kcs, 10W 8 ohm or 15 ohm £1.85. De Luxe Horn Tweeters 2-18 Kcs, 15W, 15 ohm £2. TWO-WAY CROSSOVERS 3 or 8 or 15 ohm 95p. LOUDSPEAKER P.M. 3 OHMS. 7 1/2 in. £1.25; 8 1/2 in. £1.50; 8 x 8 in. £1.80; 8in. £1.75; 10 x 6in. £1.90; 10in. £2.00. SPECIAL OFFER: 80 ohm 2 1/2 in.; 2 1/2 in.; 35 ohm, 2in.; 3in. 25 ohm, 2 1/2 in.; 3in. dia.; 5in. dia. £1.15. 15 ohm, 3 1/2 in. dia.; 6 x 4 in.; 7 x 4 in.; 8 x 5 in. £1 TYPE 3 ohm, 2 1/2 in.; 2 1/2 in.; 3 1/2 in.; 6in. dia. (6 x 4 in. 8 ohm £1.50) RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. diameter 4 watt; 10in. 5 watt; 12in. 6 watt 3 or 8 or 15 ohm models £2.20 each. Post 15p. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50-1 25p. 5 WATT MULTI-RATIO. 3, 8 and 15 ohms. 80p.

BAKER 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £49 Post Free



BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4-95

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, Hi-Fi, tape and tuner with separate controls into single output. 9 volt. STEREO VERSION OF ABOVE £5.95.

BARGAIN FM TUNER 58-105 Mc/s Six Transistor. 9 volt Printed Circuit. Illustrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. £14.85

BARGAIN FM TUNER as above less cabinet. £9.85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £4.50

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p.

RICHARD ALLAN TWIN HORN FEEDER 300 ohms 5p yard. JACK SOCKET 8id. open-circuit 14p. closed-circuit 22p. Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS 8id. Chrome 15p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 6-pin 10p. DIN SOCKETS Lead 3-pin 18p; 6-pin 25p. DIN PLUGS 3-pin 18p; 6-pin 25p. VALVE HOLDERS, 5p; CERAMIC 5p; CANS 5p.

E.M.I. TAPE MOTORS Post 25p. 120v. or 240v. A.C. 1,200 r.p.m. 4 pole 135mA. Spindle 0.187 x 0.75 in. Size 3 1/2 x 2 1/2 in. (Illustrated). £1-25

E.M.I. GRAM MOTORS 120v. or 240v. A.C. 2,400 r.p.m. 2-pole 70mA. Spindle 1 x 1/4 in. Size 2 1/2 x 2 1/2 x 2 1/2 in. Post 25p. 75p

337 WHITEHORN ROAD, CROYDON
Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)
Buses 50, 68, 159 Rail Selhurst. Tel. 01-684-1665.

RADIO COMPONENT SPECIALISTS

Minimum post 15p. Radio Books & Components Lists 10p. (Export: Remit cash and extra postage.)

STEPHENS

ELECTRONICS
DEPT E1
165 BICESTER RD.,
AYLESBURY BUCKS

UNDER NEW MANAGEMENT
MR. BRIAN RIXON, B.Sc.

SEND LARGE SAE FOR LISTS

TERMS: Cash, Cheque or P.O. with order only.

0A2	0-40	6AR6	0-65	6P5	0-75	6Y8G	0-80
0A3	0-48	6AR11	1-25	6P6G	0-65	7Y4	0-75
0B2	0-40	6AS5	0-50	6P7A	0-60	9BW6	0-70
0B3	0-70	6AS7G	0-85	6P13	0-50	10C2	0-60
0C3	0-40	6AT6	0-38	6P14	0-70	10D1	0-65
0D3	0-40	6AU6	0-30	6P15	0-65	10D2	0-55
1B3GT	0-45	6AV6	0-40	6P18	0-50	10P1	0-75
1L4	0-25	6AW8A	0-65	6P23	0-90	10P9	0-65
1R4	0-50	6BA6	0-25	6P24	0-60	10P18	0-60
1R5	0-45	6BE6	0-35	6P25	1-00	10L1	0-60
1R4	0-30	6BF6	0-55	6P26	0-35	10LD11	0-70
1R5	0-30	6BH6	0-75	6P28	0-70	10D13	0-75
1T4	0-30	6BJ6	0-55	6K6G	0-60	12AB5	0-70
1U4	0-40	6BK7A	0-75	6J4	0-60	12AC8	0-60
1U5	0-75	6BN5	0-45	6J5GT	0-40	12AD6	0-60
1Y2	0-55	6BN6	0-50	6J6	0-30	12AE8	0-60
1XB	0-55	6BQ5	0-25	6J7	0-45	12AL5	0-55
2D21	0-40	6BR8	0-75	6K6T	0-60	12AQ5	0-50
3A4	0-45	6BS7	1-35	6K6GT	0-75	12AT6	0-40
3A5	0-75	6BW6	0-90	6K7	0-45	12AT7	0-40
3BP1	3-50	6BW7	0-90	6K8G	0-45	12AU5	0-45
3B4	0-40	6BX6	0-25	6K8S	0-75	12AU7	0-35
3V4	0-65	6BZ6	0-45	6L6GT	0-55	12AV6	0-45
5R4GY	0-75	6C4	0-35	6L7	0-45	12AV7	0-70
5U4G	0-40	6CSGT	0-55	6L18	0-50	12AX7	0-35
5V4G	0-50	6CB6	0-40	6LD20	0-50	12AY7	0-75
5Y3GT	0-45	6CD6GA	1-30	6N7GT	0-55	12BA4	0-65
5Z4	0-75	6C7	1-30	6P25	1-50	12BA6	0-45
6Z4G	0-45	6CK7	0-80	6P28	0-65	12BA7	0-50
6BL2	0-90	6CH6	0-60	6Q7	0-50	12BE6	0-50
6BA4	0-45	6CL6	0-60	6A7	0-45	12BH7	0-50
6AP4A	0-80	6CU6	0-80	6SG7	0-45	12BY7	0-55
6A05	0-25	6CW4	0-70	6BK7	0-60	12K5	1-00
6A07	0-45	6CY5	0-50	6SL7GT	0-45	12K7GT	0-50
6A08	0-60	6CY7	0-75	6SL7GT	0-45	12GT0T	0-45
6A08	0-60	6A08	0-45	6E5	0-55	12R7	0-50
6AK5	0-40	6DC8	0-80	6RR7	0-50	20D1	0-60
6AK6	0-60	6DK6	0-60	6T8	0-38	20L1	1-10
6AL3	0-45	6DQ6B	0-75	6U4GT	0-70	20P1	0-50
6AL5	0-25	6DS4	1-25	6UBG	0-75	20P4	1-10
6AMB	0-40	6E48	0-65	6USA	0-45	20P5	1-20
6AM6	0-37	6EHT	0-30	6V6GT	0-45	25C5	0-60
6AQ5	0-42	6EJ7	0-85	6X4	0-40	25L6GT	0-50
6AQ6	0-70	6EW6	0-70	6X5GT	0-45	25Z4G	0-35
6AR5	0-55	6F1	0-75	6X8	0-65	25Z6GT	0-75


QUALITY VALVES
GUARANTEED. SAME
DAY DESPATCH
Tel: Aylesbury 84619

30A5	0-60	50CD8G	1-20	DL06	0-55	6CX38	0-40
30AE3	0-40	50EH5	0-65	DM70	0-60	6CC39	0-50
30C1	0-30	50L6GT	0-60	DM160	0-68	6CC39	0-50
30C15	1-00	85A2	0-55	DY51	0-55	6CC189	0-65
30C17	1-10	90AG	2-40	DY86	0-35	6CC807	1-00
30C18	0-90	90AV	2-50	DY87	0-38	6CF80	0-35
30P3	1-00	90C1	2-75	E88CC	0-70	6CF82	0-35
30PL1	0-90	90CV	2-40	E180P	1-00	6CF80A1	0-65
30PL12	1-10	807	0-50	E181P	0-90	ECH42	0-75
30PL14	0-90	813	4-00	EABCS200	ECH81	0-30	
30L1	0-40	866A	0-65	EAF42	0-60	ECH83	0-45
30L15	0-65	8642	0-75	EB33	0-60	ECH84	0-45
30L17	0-85	6080	1-75	EBC41	0-65	ECL80	0-60
30P12	1-00	6345	1-50	EBC191	0-35	ECL81	0-50
30P19	0-95	6146B	2-50	EBF80	0-40	ECL82	0-35
30PL1	0-95	6360	1-25	EBF83	0-40	ECL83	0-75
30PL13	1-10	6939	2-25	EBF89	0-32	ECL84	0-55
30PL14	1-25	7199	0-85	EDL31	1-00	ECL85	0-55
35A3	0-60	7360	2-20	EC53	0-50	ECL86	0-40
30P12	1-00	6345	1-50	EC38	0-60	ECL1800	0-75
35B3	0-65	6146B	2-50	EC90	0-35	EP37A	1-20
35C5	0-60	62A293	2-20	EC90	0-35	EP37A	1-20
35D5	0-75	AZ1	0-60	EC92	0-45	EP40	0-50
35L6GT	0-75	AZ31	0-55	EC93	0-60	EP41	0-65
35W4	0-40	CHL1	0-90	ECC35	1-00	EP42	0-70
35Z5	0-75	CHL31	1-00	ECC40	0-70	EP80	0-30
35Z4G	0-40	CY31	1-20	ECC31	0-40	EP88	0-35
35Z5GT	0-70	DAF96	0-50	ECC32	0-35	EP86	0-30
50A5	0-80	DP96	0-50	ECC33	0-35	EP89	0-28
50B5	0-70	DK92	0-70	ECC34	0-30	EP91	0-37
50C5	0-60	DK96	0-60	ECC35	0-40	EP92	0-35

EP95	0-40	GZ31	0-40	FFM18	1-00	1301	0-55
EP97	0-55	GZ32	1-50	FFL200	0-50	1404	0-70
EP98	0-75	GZ33	0-75	PL33	0-40	1404	0-70
EF183	0-30	GZ34	0-60	PL36	0-55	1901	0-80
EF184	0-35	HABCA	0-60	PLA1	0-50	UABC80	
EF804	1-25			PLA2	0-45		
EN90	0-32	HK90	0-30	PLA3	0-45	CAF41	0-40
EL33	1-50	KT60	2-35	PLA4	0-40	CAF42	0-60
EL34	0-50	KT88	2-25	PL202	0-35	1H41	0-65
EL36	0-50	N78	1-80	PL504	0-75	1H41	0-55
EL37	1-70	PAB100	0-40	PL509	1-10	UBF80	0-45
EL41	0-75	PC86	0-60	PL509	1-10	UBF80	0-45
EL81	0-55	PC88	0-60	PL801	1-00	UBF88	0-40
EL83	0-60	PC92	0-65	PLA02	0-85	UBF11	0-70
EL84	0-25	PC97	0-60	PLA4	0-60	UBF21	0-70
EL85	0-45	PC900	0-48	PY31	0-35	1C92	0-45
EL86	0-40	PC93	0-40	PY33	0-63	1C92	0-45
EL90	0-42	PC95	0-40	PY40	0-40	1C92	0-45
EL95	0-35	PC98	0-55	PY41	0-30	1C92	0-45
EL821	0-60	PC98	0-55	PY42	0-35	1C92	0-45
EL822	1-40	PC99	0-50	PY43	0-35	1C92	0-45
EL850	0-75	PC905	0-95	PY48	0-40	1C92	0-45
EM34	1-00	PC906	0-95	PY40	0-47	1C92	0-45
EM71	0-80	PC90	0-30	PY40	0-40	1C92	0-45
EM80	0-45	PC92	0-35	PZ30	0-38	1P9	0-65
EM81	0-80	PC94	0-60	QV02-6		1P9	0-65
EM83	0-50	PC96	0-60			1P9	0-65
EM84	0-35	PC97	1-10	QV03-10		1P9	0-65
EM85	1-00	PC98	0-50			1P9	0-65
EM87	0-70	PC902	0-50	QV03-20A		1P9	0-65
EN91	0-40	PC903	0-90			1P9	0-65
EN94	0-40	PC906	0-75	TT-21	3-40	1P9	0-65
EP780	0-75	PC908	0-90	TT-22	3-50	1P9	0-65
EP781	0-40	PC910	0-75	U1K/20	0-75	1P9	0-65
EP783	0-55	PC181	0-50	U25	0-85	1P9	0-65
EP786	0-40	PC182	0-35	U26	0-85	1P9	0-65
EP787	0-43	PC183	0-85	U31	0-70	1P9	0-65
EP788	0-43	PC184	0-45	U37	0-50	1P9	0-65
EZ40	0-50	PC186	0-45	U32	0-40	1P9	0-65
EZ41	0-75	PC188	1-25	U76	0-40	1P9	0-65
EZ80	0-28	PC180	1-10	U78	0-40	1P9	0-65
EZ81	0-28	PC180	0-95	U191	0-75	1P9	0-65
GT1C	3-00	PC1805	0-50	U201	0-50	1P9	0-65
GY501	0-70	PD500	1-30	U281	0-55	1P9	0-65
GZ30	0-45	PF86	0-70	U282	0-55	1P9	0-65

SINCLAIR EQUIPMENT

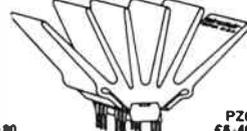IC12 £2-00
Z50 £4-25
PZ5 £3-97
P30 £3-50
Project 60 tuner £18-80
AFU £4-50
stereo 60 £7-80




KITS OF PARTS FOR THE IC12
Includes all parts for the printed circuit and volume bass and treble controls needed to complete the mono version £1-30. Stereo version with balance control £3-00.


POWER UNITS FOR THE IC12
A set of components to construct a 30V, 0.5 Amp power supply £2-27. Also suitable Sinclair PZ5 fully constructed £3-97.

PROJECT 60 KIT £2-50
Our extremely popular kit contains the extra capacitors, DIN plugs and sockets, cables and fuse holder needed to complete Project 60.

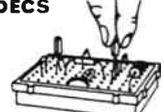S-DECS AND T-DECS
S-DECS £1-44
T-DECS £2-88
µ-DEC A £3-00
16 diode carriers £1-25



SINCLAIR EXECUTIVE CALCULATOR

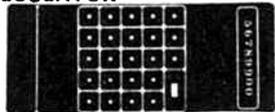

OUR PRICE ONLY £60 (List Price £70).

SWANLEY ELECTRONICS
32 Goldsord Road, Swanley, Kent
Mail order only. Postage 10p per item. Lists 10p.
After April 1st please add 10% extra for VAT.

U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and a cleverly designed reflector.

LOFT MOUNTING ARRAYS
7 element 2-25, 11 element 2-75, 14 element 3-25, 18 element 3-75.

WALL MOUNTING c/w WALL ARM & BRACKET
7 element 3-25, 11 element 3-75, 14 element 4-25, 18 element 4-75.

CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT.
7 element 4-00, 11 element 4-50, 14 element 4-75, 18 element 5-25.

MAST MOUNTING ARRAYS
only 7 element 2-25, 11 element 2-75, 14 element 3-25, 18 element 3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 99p yd. KING TELEBOOSTERS from 3-75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7-50. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np C.W.O. Min. C.O.D. charge 25np.

BBC—ITV—FM AERIALS
BBC (band 1) Wall S/D 2-00. LOFT inverted 'T' 1-25. EXTERNAL 'H' array only 3-00. ITV (band 3) 5 element loft array 2-50. 7 element 3-00. COMBINED BBC—ITV, loft 1+5 2-75. 1+7 3-50. WALL & CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from 3-75. COMBINED U.H.F.—V.H.F. aerials 1+5+9 4-00. 1+5+14 4-50. 1+7+14 5-00. F.M. RADIO loft S/D 1-00 3 element 3-25, 4 element 3-50. Standard coaxial plugs 99p. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

CALLERS WELCOMED
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS
40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY
Telephone 01-648 4884

RADIO BARGAINS



Grundig Marlner TR865 £35-00
Grundig Elite Boy 500 bat/mains £27-00
Grundig Melody Boy 500 bat/mains £27-00
Grundig Melody Boy 1000 £41-00
Grundig Yacht Boy 210 £34-50
Grundig Satellit 1000 £125-00
Aiwa AR158 6w.b. (inc. air) £31-00
Koyo KTR 1664 8w.b. £47-50
Koyo KTR1661 8w.b. £40-25
Koyo KTR1770 11w.b. £69-50
ITT/KB Golf Press £22-50
ITT/KB Touring Int. Marine £45-00
Toshiba IC70 £16-50
Grundig RF430 £28-50

FREE With each set "Guide to Broadcasting Stations" (160 pages)

WILMSLOW
AUDIO, Dept. PW,
10 Swan St., Wilmslow, Cheshire, SK9 1HF

SHORT WAVES

THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

WE are running out of frequencies. I know we have certain "Amateur Bands," but some of these are on a shared basis, i.e. we can only use them provided we are not a nuisance to other non-amateur stations using the band.

Many will remember when 40 metres was 300kHz wide—it's now 100kHz wide and intruders still try to drive us off this remaining r.f. island. The only real answer to amateur radio survival is intelligent activity. With a band full of active enthusiasts, intruders will think twice about taking on our "QRM". Those that do would find a few hundred amateurs from dozens of different locations and countries, all suddenly doing tests on that particular frequency. Whether amateur radio loses any more of its r.f. spectrum or indeed a complete amateur band, is entirely up to the people who practise and enjoy our hobby.

A typical example is 4 metres or 70MHz. This band is greedily looked at by many people (non-amateurs) who would like to use the small piece of 4 metres which we still have. Activity on 70MHz is very low from an amateur's point of view, and if activity is not increased, then the authorities may well award the entire 4 metre band to "other services". The argument could well be (and it is a valid one) that since there is so very little amateur activity on 4 metres, then you do not really need that band. So how about some logs for 4 metres?

A 4 metre converter is not a difficult thing to build and would offer a very useful intermediate step in construction practice between the h.f. bands and 2 metres. Constructing a converter for 70MHz is not difficult but needs a little more care than units constructed for the lower frequencies. One excellent idea would be to use 70MHz as a local net band, which would avoid the interference suffered on 160 metres top band, would keep us clear of Loran, which plagues 160, and would increase the level of 4 metre activity dramatically. We have to start somewhere or we could well lose this band. So, 4 metre enthusiasts forward. Let's hear what you hear.

A letter from **Paul Petty** (Canterbury) tells of a useful information service for European stations which transmits on 80 metres between 2100 and 2200 GMT. There is a controller station which is changed daily. Monday's controller is DA1LA. On Wednesdays it is DK8FZ. The purpose of the net is to assemble and disseminate information on DX stations, i.e. future skeds.

Top band enthusiasts will be delighted to hear that G3SZA has been heard on 160 metres in Australia by a VK3 station. Alas call signs are still changing. MP4 stations have been heard using a new call sign—A4FA. When will we have some call sign stability? And why change from MP4M to A4FA?

Another strange change is that CT1 stations are to use the prefix CT4 during the CQWPX contest

this month. Why is not made clear. First class licence holders in Japan now have two-letter suffix calls and second class licensees will use a JM suffix followed by three letters.

Old hands will be pleased to hear VR6TC on again from Pitcairn Island, and DX enthusiasts who enjoy hearing/working island stations should listen for VQ9HCS who radiates on 15 metres in the afternoons from Aldabra Island.

Robert Harpur (Shenfield) tells of two VP8 stations located in South Georgia which can be heard some evenings between 14.125kHz and 14.130kHz. This page commonly informs of stations heard by other short wave listeners, and amateurs. The gear is quoted, i.e. receivers, a.t.u. preselectors etc., in this way readers can gauge how their own performance is by direct comparison especially if the report is from someone using similar equipment. It has been suggested it would be nice to actually see some of these stations. Photographs of individual set ups would be of interest to others. Anyone got any really good, sharp photographs of the gear plus themselves. Think of the satisfaction of seeing your trusty old CR100 smiling back at you from the pages of *PW*.

Peter Franklin (Skegness) received a UNR30 receiver for Christmas and is busily spoiling the brute with a diet of 100ft. end fed. A preliminary listen on eighty metres brought forth a high level of G activity. Peter queries the callsign G4GJ heard testing a transmitter on 3.8MHz one afternoon. Will the real G4GJ please stand up?

Another eighty metre enthusiast is **Peter Reed** (Brighton) who is the proud possessor of an FTDX401 receiver which apparently has a Japtick UFP. Sorry Peter, I know of no ointment which can cure that. Perhaps you could scrape it off with a bent screwdriver. Peter's log for eighty reads; FL8OM, HS4AGM, I5FLN, JW9QH, M1C, M1I, VE1AIH, VE1IE, VS6DO, VQ9R, W1AA, W1KET, W2APU, W2PV, W3WJD, YA1AH, ZL4KE, ZS1MH, ZS3GH, 5X5N, 9G1DY, 9H1C, 9H5D, all on s.s.b.

Stephen Mayer (Poole) has a CR70A receiver fed with a 90ft. wire. This set up brought in stations from most European countries. From further afield; PY2ZAT, W4AG, W5QGZ, all on eighty metres.

Great rejoicing in South Yardley where **David Sharred** has found that his blood pressure and country score have increased in direct proportion to the arrival of a new CR150/2. This, together with sharp ears (no, he's not Mr. Spock) and a 140ft. end fed raised these on 3.8MHz; CT2BG, FP8CT, K1DQV, VE1ADV, VE3CDP/W9, VE7SV, W1CF, W4CC, W5SR, W5SW, WA9PRO, ZL3GS, 4X4UF, 5X5NK, 5X5XM, 9H1C.

Logs, in alphabetical order please, to arrive by the fifteenth of the month to:

12 Cross Way, Harpenden, Herts.

SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

THE first topic for this month is that of aerial wire. In the February column I asked if anyone knew of a good source for aerial wire. The number of replies was very pleasing and I must apologise for not being able to answer them all personally.

In general, your answers seem to bear out my opinion that it is becoming more difficult to find supplies of good quality aerial wire. The wire which I have always used in the past is that manufactured by a firm called 'Aerialite'. This wire consists of seven strands of copper with very strong insulation which is ideal for the purpose.

Mr. A. E. Halladay informs me that this is still available from a shop called 'Al Radio Components' of 14 The Borough, Canterbury, Kent. The wire is available in lengths of 25, 50 or 75 feet and is very reasonably priced at 14p, 22½p and 29p respectively. A charge of 6p is made for post and packing.

Mr. David Porter writes to say that a firm called Chas. H. Young Ltd of 170-172 Corporation Street, Birmingham, B4 6UD sells Stranded 7/029 and 32/0.2mm Insulated wire in 140 foot lengths for £1.87. This firm is also a good source for aerial insulators and dipole centre pieces.

Mr. A. A. Smith of Preston in Lancashire suggested the use of a particular type of G.P.O. Telephone wire. This consists of a single strand of steel wire which is covered with a film of copper and then a layer of insulation. It is usually supplied as a twin cable, similar to lighting flex, but this is easily split into two separate wires. The advantage of this wire is the superior strength of the steel core. No supplier is known but the wire should be available from Surplus Stores.

A preselector is basically an r.f. amplifier and, as such, it will improve the performance of almost any receiver. Many receivers do not have an r.f. amplifier stage, the first stage being the mixer and it is with these sets that the most significant improvement in performance will be obtained. If the receiver has one or more r.f. stages incorporated the improvement will not be so marked.

The preselector usually provides a gain of 30dB, which in simple terms is a gain of 32 times, this gain being very useful in the reception of weak signals.

It is worth noting that the most common source of lost efficiency in a receiving system is a mismatch between components of the system. The three common components are the aerial, the pre-selector and the receiver. In the simplest case of aerial and receiver it is essential to have a good match between the two. If a preselector is added there must be a good match between the aerial and the preselector and also between the preselector and receiver.

THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT READERS' LOGS

The first log comes from Raymond Mowll, who enquired about preselectors, his equipment is a Trio 9R59DS and 100 feet of wire. The lack of a pre-selector did not prevent him from hearing:

- 5047 Togo, French news and music at 2250.
- 7120 Kiev, with Mailbag programme at 0045.
- 7180 BBC, Tebrau, Malaysia relay at 1720.
- 9655 R. Damascus, Syria, in English at 2040.
- 11710 RAE, Argentina with music at 2330.
- 11955 FEBA, Seychelles in English at 1745.
- 15140 R. Havana, Cuba, commentary at 2100.
- 15375 R. Nederland, Bonaire, English at 1830.

R. M. Witney of Braintree has been active again with his Skywood CX-203 receiver and 110 foot long-wire hearing the following stations:

- 11730 Radio Ceylon at 0140.
- 11815 Trans World Radio, Bonaire at 0055.
- 15165 Radio Denmark at 2000.
- 15448 Radio Nacional de Brazilia in Spanish at 0225.

Peter North of Southport has sent in his first report to the column using his Heathkit RG-1 receiver and 24 foot long-wire to hear:

- 4979 R. Rumbos, Venezuela in Spanish at 0430.
- 4995 R. Brazil Central in Portuguese at 0030.
- 5075 R. Sulatenza, Colombia, Spanish at 0130.
- 9550 RTB, Belgium in English at 0050.
- 9730 ETLF, Ethiopia in English at 0400.
- 9745 R. Baghdad, Iraq in English at 1930.
- 11710 RAE, Argentina in English at 2300.
- 11720 R. Nacional de Brazilia in English at 2230.
- 11805 R. Globo, Brazil in Portuguese at 0030.
- 11860 R. Canada International, English at 2115.
- 11880 R. Ankara, Turkey in English at 2200.
- 11930 WIBS, Grenada in English at 2030.
- 11955 FEBA, Seychelles in English at 1730.
- 15300 HCJB, Quito, Ecuador in English at 1900.
- 15345 R. Kuwait in English at 0500.

Reports should arrive by the 15th of the month and be addressed to me at 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

NEXT MONTH

ON THE AIR

Our specialist team will present news, views, comment and of course YOUR LOGS on the Broadcast Bands (Short Wave and Medium Wave). The Amateur Bands (Short Wave) and

A NEW COLUMN

specially devoted to

VHF COMMUNICATION

for amateurs and broadcast stations.

One big regular monthly feature by Malcolm Connah, David Gibson and Charles Molloy.

Build yourself a TRANSISTOR RADIO

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Fine tone moving coil speaker. Oanged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building cost

£8-50

P. P. & Ins. 50p

(Overseas P. & P. £1)



ROAMER EIGHT Mk I


NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building cost **£6-98** P. P. & Ins. 45p. (Overseas P. & P. £1)

ROAMER SEVEN MK IV

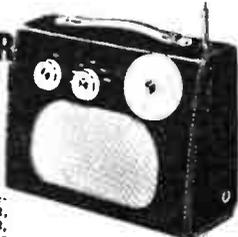

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£5-98** P. P. & Ins. 45p. (Overseas P. & P. £1)

ROAMER SIX



6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 Trawler band plus an extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Easy build plans and parts price list 25p (FREE with parts).

Total building costs **£3-98** P. P. & Ins. 30p. (Overseas P. & P. £1)

POCKET FIVE



3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2 in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-29** P. P. & Ins. 25p. (Overseas P. & P. 63p)

TRANSONA FIVE




5 TRANSISTORS AND 2 DIODES

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. Easy build plans and parts price list 10p (FREE with parts).

Total building costs **£2-50** P. P. & Ins. 24p. (Overseas P. & P. 63p)

TRANS EIGHT

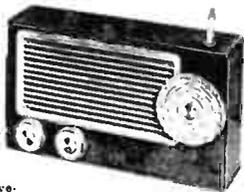

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and LW. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

Total building costs **£4-48** P. P. & Ins. 30p. (Overseas P. & P. £1)

NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT

COMPONENTS INCLUDE:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs: Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.
Parts price list and easy build plans 25p (FREE with parts).

All parts including Case and Plans **£5-50** P. P. & Ins. 32p

(Overseas P. & P. £1)

FULL AFTER SALES SERVICE

• Callers side entrance "Lavells" Shop
• Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE CO

61a HIGH ST., BEDFORD, MK40 1SA. Tel. 0234 52367

I enclose £..... please send items marked.

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>


Parts price list and plans for

Name


Address

PW52

GOING BACK...

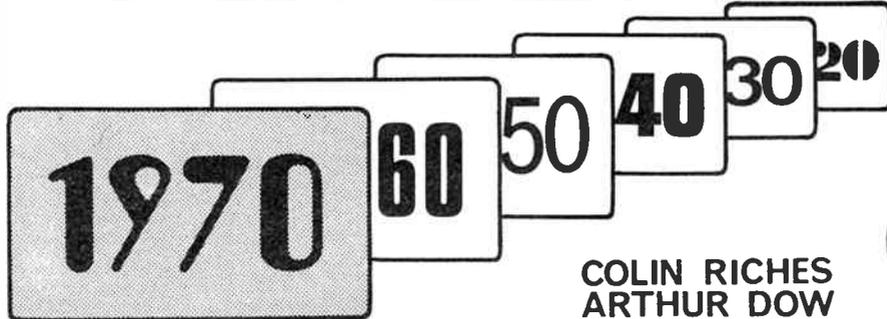

COLIN RICHES
ARTHUR DOW

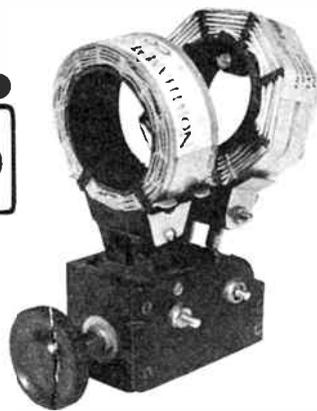

THE other month we received a letter from one of our New Zealand readers who informed us that he is an ardent vintage radio equipment collector. He told us that he decided one day to cart all his gear out on to his back lawn (it's baking hot over there at this time of the year) and take some pictures for us to show in the Going Back column.

The reader, **George A. Weston**, says that he would be grateful if anyone could supply him with the exact dates of the British-made sets, so, if anyone wants to contact him, the address is 179 Rosebank Road, Avondale, Auckland, New Zealand.

The items we show in our pictures have all been fully restored by Mr. Weston and where components had to be substituted, he used parts of the same vintage. Likewise, any valves used were of the same period and not later replacement types.

Picture No. (1) is a set made by McMichael. It has MH on the panel and is an all-wave superhet. There are five valves inside the unit and one outside. Date is about 1927.

Next, in picture (2) is a Philips 2516 with valves 506, E415, B443 and date of manufacture is about 1930. The matching speaker is a Baby Grand model 2028 balanced armature cone type that can either hang on the wall or sit on the table as shown.

Set No. (3) is an American "Radiola" model 12/20. Dated about 1925 it has UX199's in all stages except a UX120 as output valve. Case is walnut veneer.

The Gecophone shown in photograph (4) is a 1924 model containing 2 valves and working from batteries. There is one r.f. stage with variometer and a detector stage with condenser-controlled reaction. The valves used are "R" types and the receiver is shown sitting on top of a 2-valve amplifier.

Picture (5) shows a 1924 "B.T.H." crystal set with matching phones. The "driving instructions" are shown in the lid. Also shown is a "Polar Twin" 2-valve battery receiver about 1924 vintage and a Gecophone crystal set c1924 in mahogany case.

The "B.T.H." is called "Radiola"—a name generally associated with RCA in America, indicating a tie-up between manufacturers.

An "Atwater-Kent" model 30 c1926 6-valve set is shown in picture (6). It uses grid stoppers (Cossor system) in lieu of neutralizing. This was the first single-dial model made by this company. Valves are UX201A's in all stages.

No. (7) is an American 1926 "Grebe" MV1 synchrophase 5-valve neutrodyne battery set. Valves

used are UX201A's. The cabinet is mahogany.

A Philips Dutch 2510 1930 vintage 5-valve mains t.r.f. is shown in picture (8). Valves 2 x E442 screen grid, detector E415, output C443 with a 506 rectifier. The case is a metal frame enameled black with insert panels mottled rich deep red.

Picture (9) shows an American "Gilfillan GN1 c1926 5-valve neutrodyne battery set. This is a de-luxe model with walnut veneer case. It is 3ft long to accommodate "B" batteries. There is a meter for battery checking and three covers on the front drop down. In 1926, this set cost £35.

No. (10) shows a "Claritone" re-entry horn speaker (rear left) made by Automatic Telephone Co., England. It has a heavy cast-iron case and was made in 1924. A B.T.H. horn speaker (rear right) can be seen (c1926). This model has a brown flare with a transfer in black and gold.

Also shown are a "Brown" H4 (front left) (c 1926) a Burndept "Peter Pan" (c 192??) and a "True Music Minor" (front left)—date not known and no information available.

Photograph No. (11) shows an American cone speaker with a balanced armature. It is made from pressed steel and painted gilt. No. (12) is a cone speaker with a reed unit. It is called a "Mellotone" and the cone is made entirely of cardboard. The stem and base are wooden and the date is April 1926.


In some future Going Back articles we hope to show some more of our readers' collections of vintage radio gear.

A reader remembers


R. J. Hall, 7 Darlington Road, Longrock, Penzance, Cornwall, comments on his early days in radio . . .

"In those days the enthusiast enjoyed winding his own solenoid coils and basket coils, building up variable capacitors from threaded brass rod, brass or aluminium plates and nuts and bolts, and even winding transformers, both r.f. and a.f. I myself have wound more than one mains transformer by hand at 7 turns per volt on a sq. inch core and made speech coil formers and wound them.

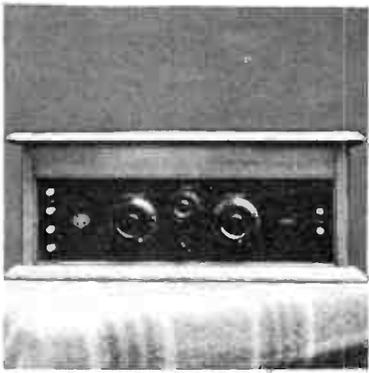It was common practice in the early days to plan a set and build it on a 'breadboard' layout when it usually worked perfectly but on being tidied up and put into a cabinet it invariably refused to function. In those days radio was a fascinating hobby but since it has become an exact science half the fun has gone".



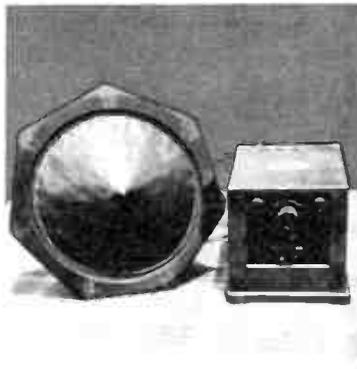1 McMichael "MH" receiver dated about 1927.




2 The Philips 2516 dated about 1930 and Philips 'Baby Grand' speaker



3 R.C.A. model 20 Radiola of 1925.



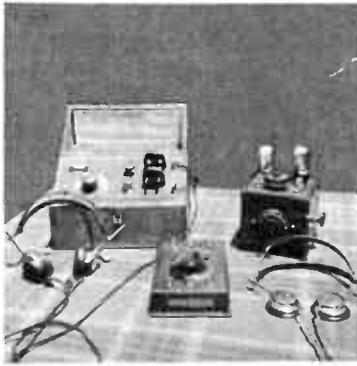4 Gecophone 1924 vintage sitting on a 2-valve amplifier




5 B.T.H. crystal set (1924) with Polar Twin and Gecophone set



6 The Atwater-Kent model 30.



7 American Grebe MV1 (1926).

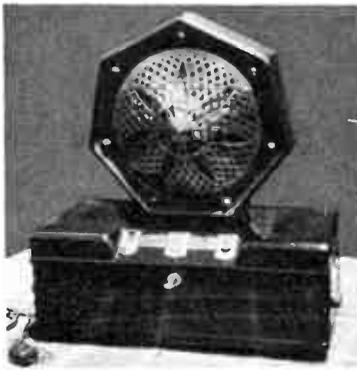


8 Philips 2510 receiver (1930).



9 American Gilfillan GN1 c1926.



10 A selection of vintage speakers.

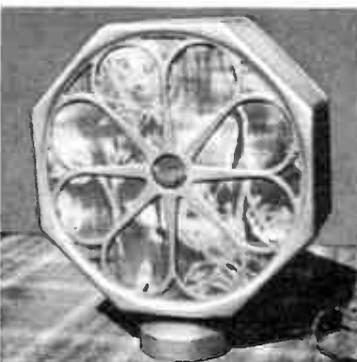

11 American cone speaker with balanced armature.



12 Cone speaker with a reed unit.

TAKE 20

JULIAN ANDERSON

WHEN a diode is reverse biased it becomes a low value capacitor. Integrated circuits make use of this effect as in this technology it is far easier to incorporate this than a more conventional component. What is more, the actual value of the capacitance depends on the voltage applied. Special diodes are made to make the best use of this effect and are known as *Varicaps* but as we have mentioned, all diodes exhibit this affect, the higher the current rating, the better the affect. We can make use of this effect where a small capacity change is sufficient such as in a b.f.o. and it is this which forms the subject of our project this month. Instead of using a variable capacitor, which would be expensive, we are using a simple potentiometer to alter the tuning.

The complete circuit is shown in Fig. 1. The tuned circuit, which operates round about 465kHz, is made up from C4 and L1. This is coupled to Tr1 to form an oscillator, C2 providing the feedback to maintain oscillation.

L1 is the Repanco DRX1 crystal set coil which has both long and medium wave windings, we only use the medium wave winding in our circuit and the connections should run to the common connection of both windings and to the tag that goes to the start of the smaller winding. In the normal state this would be tuned somewhere in the medium wave band and to increase the inductance (and also to give some control over the operating frequency) we fit a dust core into the centre of the coil.

The tuning side is accomplished by VR1, R1, D1 and C1. If a low value capacitor is connected from the collector of the transistor to the negative line this will alter the frequency. We cannot connect the diode directly here as we would affect the d.c. operating conditions of the transistor and so we have to d.c. block this; C1 performs this function.

To alter the capacity of the diode we have to apply d.c. bias to it and this has to be varied. VR1 can be almost any potentiometer from 5kΩ to 500kΩ; all we need is a variable voltage at the slider. R1 has to be included to prevent funny things happening at the extremes of the track.

As regular readers of this column will know, we often use Veroboard but this is of less use at r.f. frequencies and straightforward drilled s.r.b.p. board is better and a layout is shown in Fig. 2. This should cause few problems; the wiring on the reverse side is shown dotted.

When the unit is switched on, the slider of VR1 should be at the centre of the track and then, with the unit near a receiver, the core in L1 should be turned until a whistle is heard on *all* stations. Whistles may well be heard on one or two stations but this will mean that the frequency, or an harmonic of it, are on top of that station and not on the i.f. When the correct setting has been found VR1 can be adjusted to get the right sort of beat note, it has a fair range both sides of the centre frequency. On the layout a wire is shown marked "To Rx". It will not normally be necessary to make a

No. 47 VARICAP TUNED B.F.O.

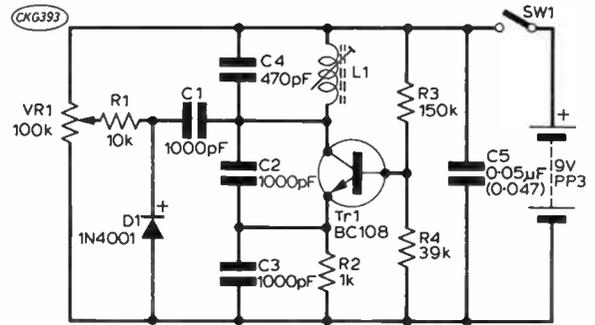


Fig. 1 The circuit instead of using a conventional variable capacitor, D1 tunes the circuit

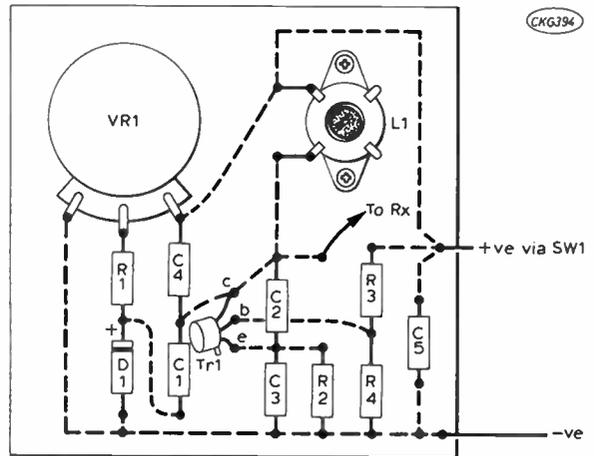


Fig. 2: A suggested component layout on drilled s.r.b.p. board.

★ components list

R1	10kΩ ½W, 5 per cent	1p
R2	1kΩ	1p
R3	150kΩ	1p
R4	39kΩ	1p
VR1	100kΩ linear pot	12p
C1	1000pF polystyrene	4p
C2	1000pF polystyrene	4p
C3	1000pF polystyrene	4p
C4	470pF polystyrene	4p
C5	0.05μF Mylar etc.	4p
Tr1	BC108	10p
D1	1N4001	6p
L1	DRX1 crystal set coil	18p
	Dust core to fit L1	3p
SW1	On-off toggle switch	5p
		78p

Prices are those recently advertised and may have changed. No allowance is made for minimum order costs or for postage and packing and these points should be checked carefully before ordering.

connection and this wire may not be needed but if the beat note is a bit weak this wire may be dangled among the components of the receiver's i.f. strip. ■

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIRCHILD



Type	1/11	12/24	25/99	Type	1/11	12/24	25/99	Type	1/11	12/24	25/99
RN7400	0-20	0-18	0-16	RN7450	0-20	0-18	0-16	RN74145	1-50	1-40	1-30
RN7401	0-20	0-18	0-16	RN7451	0-20	0-18	0-16	RN74160	3-25	2-95	2-15
RN7402	0-20	0-18	0-16	RN7453	0-20	0-18	0-16	RN74161	1-10	0-95	0-90
RN7403	0-20	0-18	0-16	RN7454	0-20	0-18	0-16	RN74163	1-85	1-27	1-20
RN7404	0-20	0-18	0-16	RN7460	0-20	0-18	0-16	RN74164	2-00	1-75	1-55
RN7406	0-20	0-18	0-16	RN7470	0-30	0-27	0-25	RN74165	1-85	1-47	1-35
RN7408	0-30	0-27	0-25	RN7472	0-30	0-27	0-25	RN74166	1-55	1-47	1-35
RN7407	0-30	0-27	0-25	RN7473	0-40	0-37	0-35	RN74167	2-80	2-40	2-25
RN7408	0-20	0-18	0-16	RN7474	0-40	0-37	0-35	RN74168	2-80	2-40	2-25
RN7409	0-45	0-42	0-35	RN7475	0-65	0-52	0-50	RN74169	2-80	2-40	2-25
RN7410	0-20	0-18	0-16	RN7476	0-45	0-42	0-39	RN74170	4-10	3-55	3-05
RN7411	0-25	0-22	0-20	RN7480	0-80	0-75	0-67	RN74172	2-00	1-75	1-50
RN7412	0-45	0-42	0-35	RN7490	1-00	0-95	0-90	RN74175	1-85	1-27	1-15
RN7413	0-30	0-27	0-25	RN7492	0-87	0-80	0-70	RN74176	1-60	1-35	1-20
RN7416	0-30	0-27	0-25	RN7493	0-75	0-70	0-65	RN74177	1-60	1-35	1-20
RN7417	0-30	0-27	0-25	RN7494	0-80	0-75	0-70	RN74180	1-55	1-30	1-20
RN7420	0-20	0-18	0-16	RN7495	0-80	0-75	0-70	RN74181	7-00	6-00	5-50
RN7422	0-48	0-44	0-40	RN7496	1-00	0-97	0-95	RN74182	2-00	1-80	1-80
RN7423	0-45	0-42	0-40	RN7497	8-25	8-07	8-00	RN74183	2-40	2-00	1-80
RN7424	0-48	0-40	0-35	RN7498	1-50	1-40	1-30	RN74184	2-40	2-00	1-80
RN7427	0-42	0-39	0-35	RN7499	1-45	1-35	1-20	RN74185	2-40	2-00	1-80
RN7428	0-50	0-45	0-42	RN749A	0-80	0-75	0-70	RN74190	1-95	1-85	1-75
RN7430	0-20	0-18	0-16	RN749B	0-80	0-75	0-70	RN74191	1-95	1-85	1-75
RN7432	0-42	0-39	0-35	RN749C	0-80	0-75	0-70	RN74192	2-00	1-80	1-80
RN7433	0-70	0-61	0-44	RN749D	8-25	8-07	8-00	RN74193	2-00	1-90	1-80
RN7437	0-45	0-40	0-40	RN749E	2-60	2-17	2-05	RN74194	2-50	2-25	1-90
RN7438	0-65	0-60	0-60	RN749F	1-50	1-40	1-30	RN74195	1-50	1-40	1-30
RN7440	0-20	0-18	0-16	RN749G	1-25	1-25	1-10	RN74196	1-50	1-40	1-30
RN7442	0-75	0-72	0-70	RN749H	2-70	2-55	2-47	RN74197	1-50	1-40	1-30
RN7443	1-00	0-95	0-90	RN749I	1-00	0-95	0-90	RN74198	4-60	3-70	3-35
RN7445	2-00	1-75	1-60	RN749J	1-00	0-95	0-90	RN74199	4-60	3-70	3-35
RN7446	2-00	1-75	1-60								
RN7447	1-75	1-60	1-45								
RN7448	1-75	1-60	1-45								

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
 LARGER QUANTITY PRICES PHONE (01) 402 8381
 TEXAS HANDBOOK NO. 2, I.C. 700 PAGES DATA 60p, POST 20p.
 HIGH POWER SN 74 HOO } Now in stock - send for list No. 36
 LOW POWER SM 74 LOO }

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA390	10p	BC147	12p	HU105	2-25	OC44	15p	T1843	35p	2N3055	55p
AA422	16p	BC169C	12p	HY100	15p	OC45	15p	V405A	25p	2N3440	75p
AAZ13	10p	BC182	10p	HY126	15p	OC57	50p	ZTX108	12p	2N3442	1-25
AC107	35p	BC214	15p	BY127	15p	OC71	15p	ZTX300	12p	2N3625	75p
AC126	25p	BCY32	75p	BY213	35p	OC72	25p	ZTX301	15p	2N3614	65p
AC127	25p	BCY34	35p	C106D	65p	OC77	45p	ZTX302	15p	2N3615	75p
AC128	25p	BCY39	1-00	GE111	55p	OC81	25p	ZTX341	20p	2N3709	15p
AC176	25p	BCY42	30p	GET115	55p	OC83	25p	ZTX500	15p	2N3704	10p
AC187	25p	BCY43	25p	GET660	45p	OC140	55p	ZTX603	17p	2N3705	10p
AC188	25p	BCY56	2-50	LM309K		OC170	25p	2N301	30p	2N3714	1-80
ACY17	30p	BCY70	15p	(T03)	1-87	OC200	80p	2N404	20p	2N3771	1-75
ACY20	20p	BCY71	20p	MAT121	25p	OC200	80p	2N327	20p	2N3773	2-00
ACY31	20p	BCY72	15p	MJE340	50p	OC201	75p	2N596	15p	2N3790	2-25
ACY39	55p	BCY97	2-90	MJE370	70p	OC202	80p	2N697	15p	2N3819	85p
AD140	50p	BCZ11	50p	MJE520	75p	OC203	50p	2N706	10p	2N3820	50p
AD149	50p	BD124	80p	MJE2955		OCPT7	1-25	2N930	20p	2N3866	85p
AD161	35p	BD131	75p		1-10	ORP12	50p	2N987	45p	2N3903	15p
AD162	35p	BD132	80p	MJE3055		ORP60	40p	2N1131	25p	2N3906	12p
AF117	20p	BF115	25p		75p	P346A	20p	2N1132	25p	2N4081	12p
AF118	50p	BF107	25p	MPP105	40p	RAS310A	7	2N102	15p	2N4082	10p
AF124	25p	BF179	25p	NKT214	20p		45p	2N1304	22p	2N4126	15p
AF139	30p	BF179	30p	NKT216	40p	RAS308A	55p	2N1305	22p	2N4871	35p
AF186	40p	BF180	30p	NKT217	40p		55p	2N1307	25p	2N5487	30p
AP239	40p	BF194	15p	NKT403	70p	TA A293	75p	2N1308	25p	2N5777	55p
AY27	30p	BF195	15p	NKT404	60p	TIL299	39p	2N1613	20p	28001	1-00
AY28	25p	BF981	25p	OA5	60p	TIP298A	50p	2N1671	1-00	28012	10-00
BA102	30p	BF988	25p	OA10	35p	TIP30A	80p	2N1672	75p	2818	6-25
BA115	7p	BF133	25p	OA11	10p	TIP31A	60p	2N1680	55p	28026	8-90
BA145	15p	BFX34	75p	OA91	7p	TIP32A	70p	2N2217	25p	28301	50p
BAX13	5p	BFX37	30p	OA200	7p	TIP33A	1-00	2N2221	20p	28303	65p
BAX16	7p	BFX88	20p	OA202	10p		1-00	2N2222A		28324	95p
BC107	10p	BFY50	20p	OC18	75p	TIP34A	1-30		25p	40250	50p
BC108	10p	BFY51	20p	OC20	95p		1-30	2N2369A	15p	40360	50p
BC109	10p	BFY82	20p	OC23	85p	TIP35A	2-50	2N2926	20p	40362	50p
BC109C	12p	BFY94	50p	OC25	40p		3-00	2N2926 (all	10p	40486	7-10
BC113	15p	BFY90	50p	OC28	65p	TIP36A	3-00	col.)	10p	40486	7-10
BC117	20p	BH320	15p	OC35	65p		3-00	2N3053	20p	40636	1-50
BC143	35p	BH327	15p	OC42	40p	TIP42A	85p	2N3054	50p	40430	1-00

QUANTITY DISCOUNTS

10% 12+ : 15% 25+ : ANY ONE TYPE
 20% 100+ : 25% 250+
 From above sections except Integrated Circuits and Special Offers where discounts are included.
 Minimum order value £1 please.
 Postage 7p on all orders.

VAT Prices DO NOT include Value Added Tax. From 1st April, 1973 10% must be added and shown separately to your total order (inclusive Post/packing). Help us to help you receive your order without delay.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	59p	2N2926	10p
1000 MC's		All Colours	
25 + 20p		25 + 9p	
100 + 17p		100 + 8p	
500 + 15p		500 + 6p	
1000 + 5p		1000 + 5p	
AF117 Mullard	25p	2N3819 Texas	35p
25 + 17p		25 + 30p	
100 + 15p		100 + 25p	
500 + 12p		500 + 20p	
1000 + 10p		1000 + 15p	
OC170 Mullard	25p	BC107, BC108, BC109	10p each
25 + 20p		All Makes	
100 + 18p		25 + 8p	
500 + 15p		100 + 7p	
1000 + 13p		500 + 6p	
		1000 + 5p	
BY127 Mullard	15p	AD161, AD162	35p each
25 + 12p		25 + 32p	
100 + 10p		100 + 28p	
500 + 9p		500 + 25p	
1000 + 8p		1000 + 22p	
OA202	10p	2N3053	20p
25 + 8p		25 + 15p	
100 + 7p		100 + 15p	
500 + 6p		500 + 12p	
1000 + 5p		1000 + 10p	
OC35 Mullard	50p	2N3055	55p
25 + 45p		25 + 50p	
100 + 40p		100 + 45p	
500 + 35p		500 + 38p	
1000 + 30p		1000 + 33p	

ZENER DIODES

400 M/W 5%
 Miniature
 BZY 88 Range
 All voltages
 3-3 - 23 Volt
 10p each.
 25+ 9p
 100+ 8p
 500+ 6-5p
 1000+ 5p
 Any one type.
 1/2 Watt 5%
 Wire Ends
 Metal Case
 All voltages
 6-8 - 100 Volts.
 20p each
 25+ 18p
 100+ 18p
 500+ 12p
 1000+ 10p
 Any one type.
 3 Watt Plastic
 Wire Ends 5%
 3EZ Range
 All voltages
 6-8 - 100 Volts
 30p each.

LINEAR (O/P AMPS)

702C T05 75p
 709C T09 35p
 709C D.I.L. 35p
 723C T09 £1.00
 723C D.I.L. 85p
 725C T09 £4.50
 741C T09 55p
 741C D.I.L. 55p
 747C T09 £1.10
 747C D.I.L. £1.10
 7274P D.I.L. 60p
 7274B D.I.L. 60p
 SINCLAIR
 TOSHIBA
 TH9013P
 20 WATT AMP
 £4.47 POST PAID
 TH9014P Prc AMP
 £1.50
 DATA AND
 CIRCUITS REF.
 42

Why pay more - look at our Fantastic Bargain Offer!

PENTHOUSE

A COMPLETE AUDIO SYSTEM

An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder. 4 wavebands Long/Medium/Short/VHF. 8 watts per channel (music power) output. The latest BSR C129 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units.


OUR PRICE £63.00



Credit terms £6.30 deposit plus £2.00 p. & p. followed by 12 payments of £5.32. Total Credit Terms £70.14 SEND £8.30 TODAY.


TRANSEUROPEAN

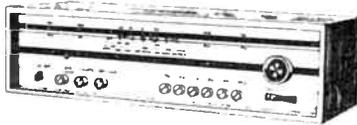A TRANSISTORISED HI-FI STEREO RADIOGRAM SYSTEM AT LESS THAN HALF-NORMAL PRICE



The system includes elegantly styled solid state Teak finish cabinet tuner/amplifier. Push-button selection, 4 waveband VHF/FM, short, medium & long wavebands. The latest 4-speed B.S.R. Mono/Stereo record changer with two 10in. x 6in. matching elliptical speakers. Supplied ready for housing. **EASILY FITTED — NO TECHNICAL KNOWLEDGE NECESSARY. OUR PRICE £39.95.** Credit Terms of first payment of £3.95. 10 payments of £4.10. Total credit price £44.95, p. & p. £2. SEND £5.95 TODAY

THE AVON AUDIO SYSTEM

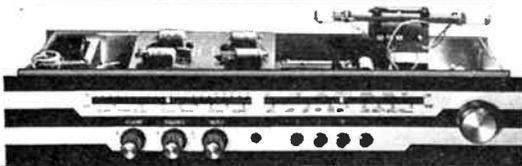

The uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

BSR 4 SPEED STEREO/MONO RECORD CHANGER plays all types or 7in., 10in., and 12in. Mono of Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKER. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45-74. **OUR PRICE £37.00.** Credit Terms £3.70 deposit plus £2 Post & Packing followed by 12 payments of £3.15 (Total Credit Terms £41.50) Don't miss this bargain.

SEND £5.70 TODAY

ALL EQUIPMENT COVERED BY 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

Please send me free details of your range

Name

Address

PW/4/73

LEWIS radio 100, Chase Side London N.14
Tel: 01-886 3733/9666

Post coupon NOW for...
FREE
leaflets

NEW
ALL
SILICON!



PRACTICAL WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P. Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, refundable on purchase of kit.

Suitable for 12v or 6v systems with Pos. or Neg. earth.

Price: Standard Kit£7.25 U.K. Post Free
De-Luxe Kit£8.75 U.K. Post Free

Quantity Discounts:

Trade and Overseas	1-5	Nett	6-9	Less 10%
Enquiries Invited	10-49	Less 15%	50-99	Less 20%
Mail Order Only	100-999	Less 25%	1000 up	Less 30%

PLEASE NOTE ALL THE ABOVE PRICES ARE SUBJECT TO ANY V.A.T. ADJUSTMENT.

STATE POS. OR NEG. EARTH AND 6V OR 12V WHEN ORDERING.

DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34365

NEW VALVES ! GUARANTEED AND TESTED

24-HOUR SERVICE

1R5	25	DAF91	21	ECC85	31	EL84	20	PCF802	88	U329	65
1R5	21	DAF96	35	ECH35	49	EM80	35	PCL82	28	U801	73
1T4	14	DF91	14	ECH42	56	EM81	35	PCL83	58	UABC20	29
3R4	24	DF96	35	ECH81	26	EM84	30	PCL84	81	UBF89	28
3Y4	46	DH77	18	ECL80	27	EY86	27	PCL85	86	UCB85	82
6X00L2	24	DK91	25	ECL82	27	EZ80	19	PCL86	85	UCH42	56
6AT6	18	DK96	43	ECL86	32	EZ81	21	PPL200	49	UCH42	52
6AQ5	21	DL92	24	EF39	36	KT61	54	PL36	45	UCH81	28
6BW7	48	DL94	46	EF41	56	KT66	75	PL81	41	UCL82	90
6F1	57	DL96	36	EF80	22	N78	£1.00	PL82	29	UF41	49
6F23	64	DY86	21	EF85	22	PC86	44	PL83	31	UF89	28
6F25	49	DY87	21	EF86	27	PC88	44	PL84	28	UY85	22
12AU7	17	DY802	28	EF89	24	PC97	36	PL500	59	UL41	52
2516GT	18	EABC80	28	EF91	12	PC900	28	PL504	59	UL84	27
30C15	56	EBC33	38	EF92	28	PCC84	27	PY81	23	UY41	37
30C17	73	EBC41	47	EF183	25	PCC89	41	PY82	23	UY85	22
30F5	60	EBF89	27	EF184	27	PCC189	46	PY800	80	UY85	22
30FL1	59	ECX81	15	EH90	38	PCF80	25	PY801	30	W77	18
30FL14	67	ECX82	17	EL33	34	PCF86	44	R19	27	777	18
30PL1	55	ECX83	21	EL41	52	PCF801	27	U251	60		

Post/Packing on 1 valve 7p. plus 3p. per valve on each extra valve. Any parcel insured against damage in transit 3p. extra. Office address, no callers.

GERALD BERNARD 83 Osbaldeston Road, Stoke Newington, London, N.16

4 CHANNEL STEREO CONVERTER



Create a new dimension in sound — sound that engulfs you with natural realism from every corner of your room. Simply wired to your amplifier or Tuner/Amp. speaker outputs and again into 4 speakers. Neat styling with brushed effect console panel. Peak input power 50w into 8 ohms. Front Hi/Low Level 6dB. Phone jacks for input and output. Size: 6" x 3 1/2" d. x 2" h. Guaranteed.

TRANSFORMS YOUR STEREO SYSTEM INTO SENSATIONAL QUADROPHONIC SOUND

INTRODUCTION PRICE **£7.50**

OCIL (Dept. PW 2), 43 BARTHOLOMEW CLOSE, LONDON, EC1A 7HP. Tel. 01-600 3211.



DARKROOM EXPOSURE METER

A.P. DONLEAVY

THIS instrument was designed for use with a photographic enlarger, to determine the exposure required for any particular print. It is cheap to build and easy to use, with a range up to about 40 seconds.

THE CIRCUIT

This is shown in Fig. 1. LDR is a light dependent resistor whose resistance varies with the amount of light falling on its face. LDR and VR1 form a potential divider. The potential at point A is determined by the setting on VR1 and on the resistance of the LDR, hence on the light incident on its surface. Tr1 and Tr2 form a Schmitt trigger. The potential at A determines which of these transistors is on and which is off.

Tr2 has a light emitting diode D1 in its collector circuit, which lights when Tr2 is conducting.

To measure the amount of light incident on the meter, VR1 is altered until the extinguishing (i.e. on-off) point of the diode is found. The setting of VR1 is thus a measure of the exposure time required. A knob with a linear calibration around the outside is used to alter VR1.

The unit is sensitive to voltage supply change, hence a zener diode D2 is used to regulate the power supply.

SW1 is a push button switch which is depressed only when making the exposure, hence eliminating the possibility of forgetting to turn the unit off.

COMPONENTS

Other transistors could be used for Tr1 and Tr2 e.g. 2N2926. VR1 is 50k Ω . Increasing the value increases the range of the instrument but decreases its sensitivity.

D1 does not have its positive lead marked. This must be found by trial and error or by using a meter.

CONSTRUCTIONAL DETAILS

The whole unit can be fitted into a small plastic box box 4 $\frac{1}{2}$ in. x 3in. as shown in Fig. 2. Veroboard is used to mount the transistors and resistors. Two small holes can be drilled to take the LDR leads, a dab of

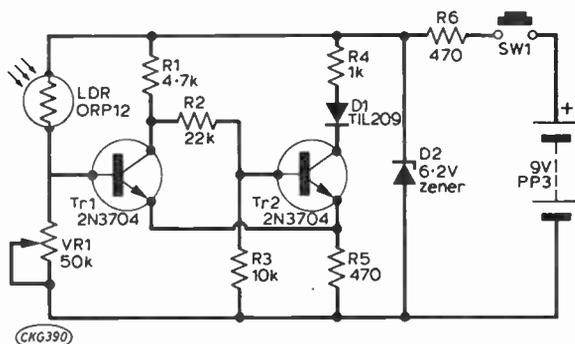


Fig. 1: The complete circuit which is basically a Schmitt trigger.

★ components list

Resistors

R1 4.7k Ω	R4 1k Ω
R2 22k Ω	R5 470 Ω
R3 10k Ω	R6 470 Ω

All $\frac{1}{4}$ W, 5% types
VR1 50k Ω lin. pot.
LDR ORP12.

Transistors

TR1 2N3704
TR2 2N3704
D1 TIL209 (light emitting diode)
D2 6.2V zener diode.

Miscellaneous

9V battery; Battery connector; Veroboard; On-off switch, push button type; Plastic box; Calibrated knob or dial.

glue will hold it in place. Further constructional details are not given since the layout is not critical and most constructors will find it is a simple job to assemble the instrument.

The instrument is now ready for calibrating.

CALIBRATION

The scale is calibrated in terms of exposure as follows: a piece of clear blank film is put into the

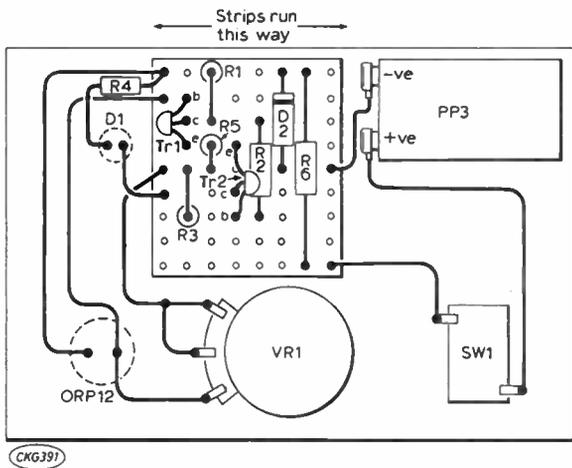


Fig. 2: Constructional details.

For scale readings between 20 and 40 seconds it will be easier if the strips are exposed in multiples of 4 seconds.

A similar calibration graph must be obtained for each different type of printing paper used.


USING THE INSTRUMENT

Having obtained the graphs, the instrument is simple to use. Place it on the easel such that a clear part of the film e.g. the margin between the frames or an unexposed frame, shines onto the LDR. Find the on-off point of the diode D1 and note the scale reading. From the graph, read off the required exposure time, if the scale reading is 5 then the exposure time is 19 secs. This will give the correct exposure time for all normal negatives with full tonal reproduction.

CONCLUSION

The instrument is cheap and easy to make, and is

Fig. 3: An example of the gradations which will appear on the printing paper; the time of each exposure is marked below.

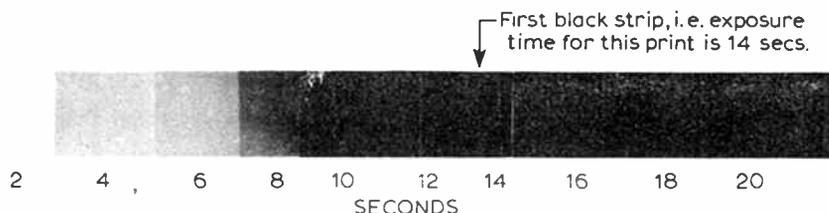

enlarger; all lights in the darkroom are put out except for the enlarger light; the instrument is placed on the easel, SW1 is depressed and VR1 is adjusted so that the diode light just goes from on to off. The reading on the scale is noted. (It is important that the scale reading is always taken from on-to-off since the off-to-on reading is different, owing to hysteresis in the Schmitt trigger.)

A narrow strip of paper is then used for a test strip. Parts of the paper are exposed in multiples of two seconds. The developed strip will look like Fig. 3. There is a gradual transition from light to black. The first black stripe can be judged and the corresponding exposure time also. The scale reading and exposure time are then noted.

The procedure is then repeated for different light readings (scale readings) and a graph of scale reading against exposure time is plotted, Fig. 4.

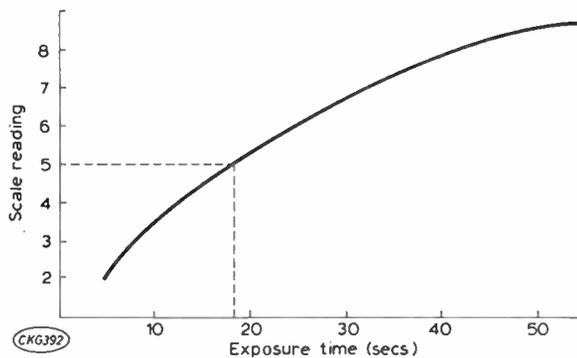


Fig. 4: A calibrated graph relating the knob markings of 1-10 to the time.

reasonably accurate. Its great advantage is the saving in time, since after initial calibration there is no need to make a test strip for every exposure. ■



25 YEARS MARCH 1973 page 993. At the foot of column three: The I.E.R.E. is publishing a collection of 20 papers in their journal on semiconductor subjects.

DIGITRONIC SOLID STATE DIGITAL CLOCK
MARCH 1973 page 1009. The sentence—There is no need . . . harm a LED is to pass too high a current through it (most LEDs work operate on 10-15mA).

Back Numbers

We regret to inform readers that owing to the closure by the Company of the department concerned it will no longer be possible to supply back numbers of **Practical Wireless** or **Television**.

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CQ" column which appears in most issues.

AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready-wired dashboard switch. £5.75 plus 25p post and insurance.



TAPE HEADS

We are gradually obtaining more information about the Truvox tape heads we have, we are told that these have been wound in a very ingenious way so that winding may be coupled either in parallel or in series depending whether high or low impedance is required. We also have matching erase heads and now offer these in pairs. 1 record and 1 erase head. Price of the 2 track 45p per pair. 4 track 75p per pair. Pair mounted on plate 45p extra.


MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2in. £1.50 each.



TELESCOPIC AERIAL

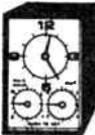for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 38p. KNUCKLED MODEL FOR F.M. 50p.



MAINS CLOCK AND TIME SWITCH

Smith's main's driven clock with 15 amp programmable switch also notes showing how you can use this to wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keeps pets warm, halves your heating bills, etc., etc. £1.75 + 20p p. & p.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

IMMERSION HEATERS BY REMPLOY

Standard fitting for domestic water tanks, made by the famous Remploy Company. Complete with sealing washers suitable for 200-240 volts A.C. Depth into tank 11". 2kw or 3kw. £1.50 plus 40p each post and insurance.



NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 40p doz. Plastic pushrod suitable for operating. 6p each, 45p doz.

THERMOSTAT

Continuously variable 30°-90°C. Has sensor bulb connected by 30in. of flexible tubing. On operation a 15 amp 250 volt switch is opened and in addition a plunger moves through approx 1in. This could be used to open valve on ventilator etc. £1.50 plus 25p p. & ins.

HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C. with thermistor as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack £5.50.

NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac. XN.3. Price £1.45 each. 10 for £18.

12-WAY SUB-MINIATURE MULTI-CORE CABLE

7-0076 copper cores, each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 20p per yard.

VAT From April 1st. VAT. MUST be added to total order.

STANDARD WAFFER SWITCHES

Standard size 1 1/2" wafer—silver-plated 5-amp contact, standard 1" spindle 2" long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	40p	40p							
2 poles	40p	70p	70p						
3 poles	40p	40p	40p	40p	70p	70p	70p	95p	95p
4 poles	40p	40p	40p	70p	70p	70p	70p	£1.20	£1.20
5 poles	40p	40p	70p	70p	95p	95p	95p	£1.45	£1.45
6 poles	40p	70p	70p	70p	95p	95p	95p	£1.70	£1.70
7 poles	70p	70p	70p	95p	£1.20	£1.20	£1.20	£1.95	£1.95
8 poles	70p	70p	70p	95p	£1.20	£1.20	£1.20	£2.20	£2.20
9 poles	70p	70p	95p	95p	£1.45	£1.45	£1.45	£2.45	£2.45
10 poles	70p	70p	95p	£1.20	£1.45	£1.45	£2.70	£2.70	£2.70
11 poles	70p	95p	95p	£1.20	£1.70	£1.70	£2.95	£2.95	£2.95
12 poles	70p	95p	95p	£1.20	£1.70	£1.70	£3.20	£3.20	£3.20

THYRISTOR LIGHT DIMMER

For any lamp up to 250 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price £2.95 plus 20p post and insurance. Industrial model 5A with control knob but not mounted on switch plate, £3.



HORSTMANN "TIME AND SET" SWITCH

(A 30 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.60, p. & ins. 23p.



13 AMP TWIN GANG SOCKETS

Offered at less than wholesale price—your opportunity to replace those dangerous adaptor—brown bakelite flush mounting standard fitting. Unswitched 20p each, separately switched 30p each. Separately switched less 10% ten or more + 20p postage if order under £5.



4 WATT AUDIO AMPLIFIER £1.45



Works off dry batteries, car battery or mains power pack. Only £1.45. This low price possible only because the make is over produced. Unrepeatable once stocks are cleared.

Made by the famous Mullard company and carries their full guarantee. Complete in dustproof case. Amplifier may be used for Mono or Stereo, music or speech. Hundreds of applications. Frequency response 60Hz-16KHz. Supplied complete with connection diagram and operating notes. Postage and Ins. 20p.

FREE. All purchasers receive Mullard booklet "Do It Yourself Stereo" tells all you need to know to build your own stereo system. Write today to avoid missing this terrific offer.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines. Display lighting animated and signs. Signalling, etc. Price from makers probably over £10 each. Special snip price £5.75 plus 25p post and insurance. Don't miss this terrific bargain.



MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January '73. All electronic parts £2 post paid.



DIGITAL COUNTER TIMER


Very stable and reliable crystal controlled circuit. Capable of work in excess of 15 MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case £39.50 or construction data and price list 50p.

INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or second. 4 of the ICs are single silicon chip (IP amplifiers). The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards, with circuits and technical data of each. Complete parcel only £1 post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**

TERMS: 10% discount if ten of an item ordered, send postage where quoted—other terms, post free if order for these over £6.00 otherwise add 20p.

EXTRACTOR FAN

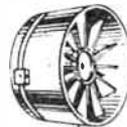

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can barely be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2.50 plus 30p post and ins.

QUICK CUPPA

Mini Immersion Heater. 350w 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25. Post and insurance 14p. 12v. car model also available same price. Jug heater £1.50 plus p. & p. 14p.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12v. volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1 plus 20p postage.



TREASURE TRACER

Complete Kit (except wooden hattery) to make the metal detector as the circuit in Practical Wireless, August issue. £2.95 plus 20p post and insurance.

WINDSCREEN WIPER CONTROL

Beat dirty roads, drizzle, fog, etc. Kit of parts to make this useful accessory with circuit details. £2.25.



12 VOLT 1 1/2 AMP. POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd/50V smoothing. Price £2 plus 20p post & packing.

I CHIP RADIO

Ferranti's latest device ZN414—gives results better than superhet. Supplied complete with technical notes and circuits. £1.25 each. 10 for £11.

HI-Q TUNER COMPONENTS

For experimenting with the ZN414. KIT NO. 1. Plessey Miniature Tuning Condenser with built-in LW switch and 3" Ferrit slab and litz wound MW coil, 65p. KIT NO. 2. Air spaced tuning condenser 6" ferrit rod litz wound MW and LW coils, 85p. KIT NO. 3. Air spaced TC with slow motion drive 8" ferrit rod, with litz wound LW and MW coils, 41p. KIT NO. 4. Permeability tuner with fast and slow motion drive and LW loading coils, 45p.

6 VOLT CLOCK MOTOR

Works from 50 cycle mains through condenser, resistor or step-down transformer. This is a synchronous motor made by Smiths, so it is an extremely accurate speed controller. Very small in size (2 watt) and with a polythene cover. Price 30p each. 10 for £2.70.

SOLDER GUN



A must for every busy man, gives almost instant heat also illuminated hot. 100 watt £2.25 plus post and ins. 20p. BIO JOB 250 watt model £4.75 plus post and ins. 40p.

MAINS OPERATED SOLENOIDS


Model 772—small but powerful 1" pull—approx. size 1 1/2 x 1 1/2 x 1 1/2". 60p. Model 400/1—1 1/2" pull. Size 2 1/2 x 2 x 1 1/2". 75p. Model TT10—1 1/2" pull. Size 3 x 2 x 2". £1.80 plus 20p post and insurance.

3 STAGE PERMEABILITY TUNER

Made originally for Radiomobile car radios. This is a medium wave tuner with a frequency coverage 16kc-525kc. Aerial, RF and oscillator sections (long wave coil available) small size, only 2 1/2 x 2 x 1 1/2". Can be used with our IP module and AF modules and a complete connection components to make a complete compact receiver. Circuit supplied. Price 65p, less 10% for 10.

J. BULL (ELECTRICAL) LTD.

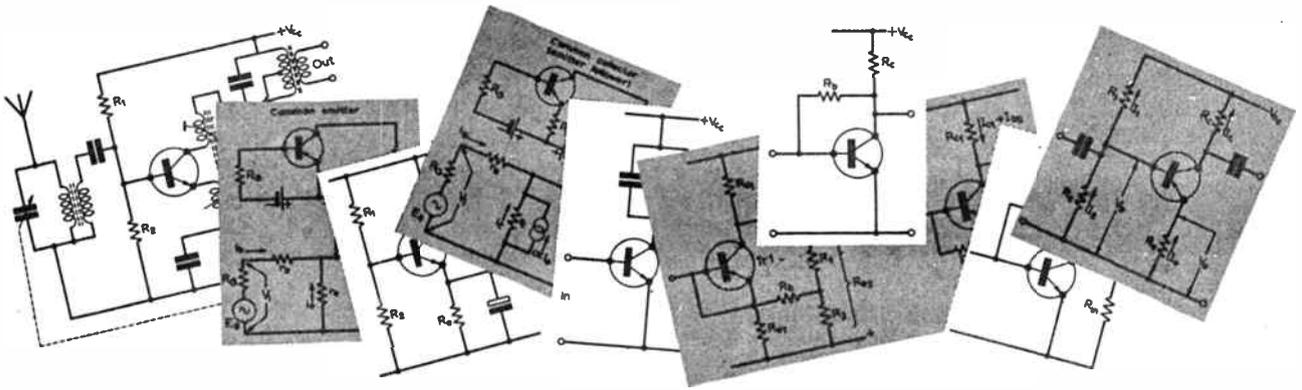(Dept. P.W.) 7 Park Street, Croydon CRO 1YD
Callers to: 102'3 Tamworth Road, CROYDON



TRANSISTOR CIRCUITRY for beginners

PART 15 H.W. HELLYER & MICHAEL HOLLIER

Tone control circuitry

Toward the end of the last part of this series of articles that was published, we were concerned with frequency-dependent feedback. Without being intentionally devious, we skated over some of the finer points and here shall try to keep our promise of digging more deeply into the matter of tone controls, their design and their limitations.

The utter purist will not deign to acknowledge the need for tone controls! Everything should be flat, he says. There should be, he further asserts, no need to alter the frequency response of an amplifier if all the other parts of the audio system are in order. True, but Utopia has not yet arrived, whatever the politicians promise, and there will be nasty pops and crackles from our records, hiss from our tape, peaks and troughs from many a cartridge and even worse deviations by the time the sound escapes from the loudspeakers.

Even then, we are not finished. If the little woman insists on foot-deep rugs and wall-to-wall drapes, or if your pad is scoured to its functional austerity, man, you will need some trimming of the ideally flat response to compensate for—in the first case, the premature absorption of treble, and in the second, the 'hardness' of the sound. Tone controls may be regarded as necessary evil, but as long as we are obliged to have them, let's make sure they do not detract from the best possible performance. And in so many commercial designs, they do.

First steps

Before delving into the tone control circuit as a whole, we must take a look at the effect of the passive components with a change in frequency. Back in the days when Poppa bought his radiogram because it sounded 'mellow', the tone control was simply a network of passive components, usually across the output stage, with variation of the resistive part of a series capacitor-resistor shunt that drained away progressively more and more of the upper frequencies. It was, in other words, a variable treble-cut device. One or two more enterprising makers

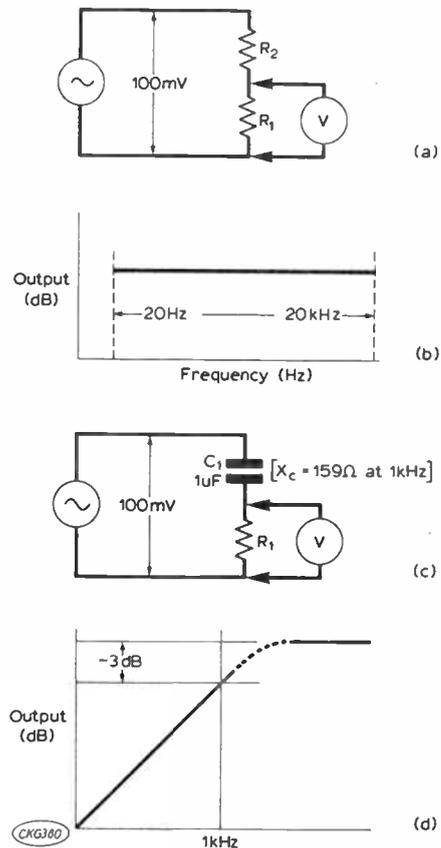


Fig. 74: (a) For a simple resistive network the output shown by the voltmeter is in proportion of the ratio of the resistors to the applied input voltage. In (b) theoretically, the output should not change with frequency, giving a "straight-line" graph. (c) Substituting a capacitor for R_2 makes the output frequency dependent while (d) shows an example of the curve we might expect from a simple network such as (c) having a "slope" of 6dB per octave.

fitted alternative resistor-capacitor combinations in the grid circuit of output valves, and others even went so far as to label these Bass or Treble Boost and Cut, but all such passive networks, i.e., those which do not have inbuilt amplification, must attenuate the overall signal.

The point about the passive tone controls is that the attenuation varies the frequency. Take the case of a simple resistive network, as in Fig. 74(a). If we have two resistors of equal value, fed by a signal generator, the output across the measured one will be half the input signal in amplitude, but will not change in frequency. A graph of the situation would be a straight line, as Fig. 74(b).

But if we now substitute the upper resistor with a capacitor, C1 in Fig. 74(c), we find that the measured output will be exactly half the input at **only one frequency**. Reactance $X_c = \frac{1}{2\pi fC}$ where X_c is in ohms, C in farads and f is the frequency at which the test is made, in hertz.

Working out the reactance of a $1\mu\text{F}$ capacitor at 1kHz, we get $\frac{10^6}{6.28 \times 1000 \times 1} = 159$ ohms.

But if we now measure the voltage across a similar-value resistor, we find that instead of half the signal input, we have slightly more. Instead of our attenuator dropping the output by 6dB (to half voltage) at 1kHz, it will have dropped the output only 3dB. This is because the voltage across the capacitor is 90° out of phase with the voltage across the resistor. The output voltage ratio is 0.707:1, not 0.5:1. In fact, if we alter the frequency of the generator, we will find that the measured output drops as the frequency falls. The rate of 'slope', as shown in Fig. 74(d), is 6dB per octave, an octave being a frequency change of 2:1.

This 3dB drop has a further significance when we tackle power output stages, for if the drive voltage to the amplifier fell sufficiently for the power output to drop 3dB, this would be the well-known 'half-power-point'. This is the figure normally quoted in amplifier specifications—a point to which we shall return later. Below this -3dB point in Fig. 74(d), the slope of the curve falls away regularly by 6dB per octave, i.e., a ratio of 2:1, a reduction of output by a half each time the frequency is halved.

Making it active

It helps to regard tone control as a method of frequency correction. The introductory remarks we have made, and references to frequency-dependent

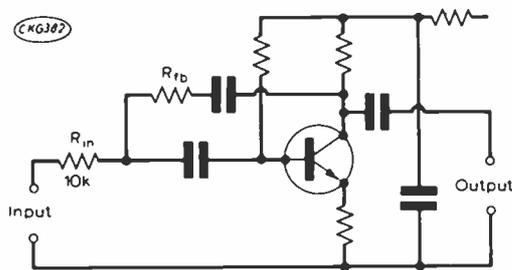


Fig. 76. The basic circuit used for tests.

feed-back in previous articles, should have prepared the regular reader for this approach. Simple tone controls are types of filters. We shall deal thoroughly with filter circuitry later, but at the moment it is necessary to observe that the 'filter' of Fig. 74(c), for example, is called a 'first order filter', having a 'slope' of 6dB per octave. Second order filters have slopes of 12dB/octave and third-order filters, 18dB/octave. As we shall see, real filters, used in well-designed audio amplifiers, should ideally have a third-order slope to be effective.

These filters are passive devices. They contain no amplifying stage or stages to put back the signal attenuated by their action. If we make a marriage of the virtual earth circuitry we talked about in Parts 12 and 13 of this series and the fundamentals of tone control circuitry touched upon in Part 11, we get an amplifier with frequency-dependent feedback, which becomes, if we correctly design it, a better tone control circuit.

First, we need what is known as an 'inverting amplifier'. If you take a look at Fig. 75, you will see that this can be a collector-follower circuit, so arranged that we can measure its gain with or without the feedback. In practice, this is a useful circuit, and the component calculation will be discussed as we go along. It is convenient to use the 24-volt supply described in Part 13, December PW. Fig. 76 shows the circuit devised by Mike and used for tests on the prototype.

With an input from the audio generator, and an output measured with a millivoltmeter, we can measure the open-loop gain. This is the gain of the amplifier with no feedback connected. Here, a word of warning is required: in many erudite theoretical articles, 'open-loop gain' is bandied about freely, but an inspection of the circuit will often show that it would be virtually impossible to measure it in practice. Our aim in this case is to show what we mean by the term, then, by applying the feedback we need, to modify the gain and achieve our controlled response, i.e., effect a tone control.

In our prototype, the open-loop gain, (G_0) was 260. It is absolutely essential when carrying out these measurements to mount the circuit in a screened box, use screened input and output leads and make sure our construction is 'solid'. We use Veroboard for convenience: it allows connection of additional components while retaining the versatility of wired circuitry. We use the very convenient Norman Rose aluminium boxes, because they are inexpensive, easily worked for outlet holes, tag-strip mountings, etc., and have a simple lid which not only completes the screening but also affords an easy access for modifications.

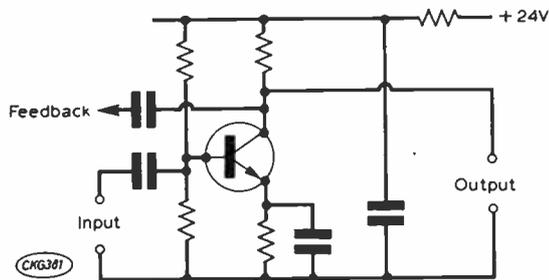


Fig. 75: A collector-follower amplifier arranged so that its output can be measured with and without feedback.

TO BE CONTINUED

BI-PRE-PAK

COMPLETE TELEPHONES



EX. G.P.O. NORMAL HOUSEHOLD TYPE
ONLY 95p
 POST & PACKING 35p EACH

TELEPHONE DIALS
 Standard Post Office type.
 Guaranteed in working order.
ONLY 25p
 POST & PACKING 15p

TESTED AND GUARANTEED PAKS

B79	4	Photo Cells, Sun Batteries, 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors, Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors, Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors, Mixed types and values.	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8 - 43V.	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon Planar types.	50p
H39	10	Integrated Circuits, 6 Gates BMC 962, 4 Flip Flops BMC 945	50p
H40	20	BFY502, 2N696, 2N1613 NPN Silicon uncodded TO-5	50p

UNMARKED UNTESTED PACKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA302	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BS95A, etc.	50p
B1	50	Germanium Transistors PNP, AF and RF	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OVER **1,000,000** TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.
 Audio NPN, similar to ZTX300, 2N3708/9 BC107/8/9, BC168/9 etc.
 R.F. NPN and switching NPN Types also. Please state type of transistor required when ordering.
 ALL AT 500 for £3, 1,000 for £5, 10,000 for £40 P. & P. 10p/1,000.

OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
 TYPE "B" PNP Silicon, plastic encapsulation.
 TYPE "E" PNP Germanium AF or RF.
 TYPE "F" NPN Silicon plastic encapsulation.
 TYPE "G" NPN Silicon similar ZTX 300 range
 TYPE "H" PNP silicon similar ZTX 300 range

POWER TRANSISTOR PRICE BREAKTHROUGH!

Plastic cased Silicon Power Transistors of latest design. 40watts and 90watts. PNP & NPN types. All types available at the most shatteringly low prices of all time. All are fully tested, marked and guaranteed!

40W NPN	1-12	13-25	26-50
40W PNP	20p	18p	16p
90W NPN	21p	19p	17p
90W PNP	24p	22p	20p
90W NPN	25p	23p	21p

PAK PAKS of Complementary pairs
 MP40 40W+40W 50p 48p 46p
 MP90 90W+90W 60p 58p 56p

PLEASE STATE IF NPN/PNP OR NPN/NPN ARE REQUIRED.

A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p. 10p P & P on this Pak.

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

8 RELAYS FOR VARIOUS TYPES £1 P & P 25p

INTEGRATED CIRCUITS

Clocked Flip Flop	BMC931	20p	18p	16p
Ex. 2/4-input Buffer	BMC932	12p	11p	10p
2/4-input Expander	BMC933	12p	11p	10p
Hex. Inverter	BMC934	12p	11p	10p
Hex. Inverter	BMC935	12p	11p	10p
Hex. Inverter	BMC936	12p	11p	10p
Hex. Inverter	BMC937	12p	11p	10p
Decade Counter	BMC938	25p	23p	21p
Div. by 16 Counter	BMC939	25p	23p	21p
Hex. Inverter	BMC940	12p	11p	10p
Hex. Inverter	BMC941	12p	11p	10p
Type D Flip Flop	BMC942	20p	18p	16p
Ex. 2/4-input Power	BMC944	12p	11p	10p
Clocked Flip Flop	BMC945	20p	18p	16p
4/2 Input NAND Gate	BMC946	11p	10p	9p
Clocked Flip Flop	BMC948	20p	18p	16p
4/2 Input NAND Gate	BMC949	12p	11p	10p
Pulsed Trig. Binary Monostable Multivib.	BMC950	20p	18p	16p
Dual J/K Flip Flop	BMC951	25p	23p	21p
Dual J/K Flip Flop	BMC953	20p	18p	16p
Dual J/K Flip Flop	BMC955	20p	18p	16p
Dual J/K Flip Flop	BMC956	20p	18p	16p
Quad. 2-input Power	BMC958	12p	11p	10p
2/4-input Gate	BMC961	12p	11p	10p
3/3-input NAND Gate	BMC962	11p	10p	9p
3/3-input NAND Gate	BMC963	12p	11p	10p
Audio Amp. 3w. SL403D		£1.50	£1.40	£1.36
Linear Op. Amp 709C		25p	20p	15p
Decade Counter SN7490		65p	60p	55p

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each. New new low profile 16 pin type at 16p each. Type

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I Transistor Equivalents and Substitutes; 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.

The Iliffe Radio Valve & Transistor Data Book 9th Edition; 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Postage and Packing 21p.

Send for lists of these English publications

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD DEPT. E, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX S50 9DF
 TELEPHONE: SOUTHEND (0702) 46344

SEW PANEL METERS

CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.

- LOW COST
- QUICK DELIVERY
- OVER 200 RANGES IN STOCK
- OTHER RANGES TO ORDER

"SEW" BAKELITE PANEL METERS

Type SW.100 100 x 80 mm.

50μA	£3-80
50-0-50μA	£3-80
100μA	£3-80
100-0-100μA	£3-70
500μA	£3-50
1mA	£3-40
20V. D.C.	£3-40
50V. D.C.	£3-40
300V. D.C.	£3-40
1 amp. D.C.	£3-40

5 amp. D.C.	£3-40
300V. A.C.	£3-40
VU Meter	£4-15

Type SD.830 82.5mm x 110mm Fronts

10mA	£2-50
50mA	£2-50
100mA	£2-50
500μA	£2-50
1 amp.	£2-50
5 amp.	£2-50
10 amp.	£2-50
50μA	£2-75
50-0-50μA	£2-70
100μA	£2-70
100-0-100μA	£2-70
200μA	£2-70
500μA	£2-55
1mA	£2-50
5mA	£2-50

10mA	£2-50
50mA	£2-50
100mA	£2-50
500μA	£2-50
1 amp.	£2-50
5 amp.	£2-50
10 amp.	£2-50
50μA	£2-75
50-0-50μA	£2-70
100μA	£2-70
100-0-100μA	£2-70
200μA	£2-70
500μA	£2-55
1mA	£2-50
5mA	£2-50

Type SD.640 63.5mm x 85mm Fronts

50μA	£2-60
50-0-50μA	£2-55
100μA	£2-55
100-0-100μA	£2-55
500μA	£2-55
1mA	£2-35
5mA	£2-35
10mA	£2-35
50mA	£2-35
100mA	£2-35

500μA	£2-35
1 amp.	£2-35
5 amp.	£2-35
10 amp.	£2-35
50μA	£2-55
50-0-50μA	£2-50
100μA	£2-50
100-0-100μA	£2-50
200μA	£2-50
500μA	£2-35
1mA	£2-35
5mA	£2-35
10mA	£2-35
50mA	£2-35
100mA	£2-35

Type SD.460 46mm x 59.5mm Fronts

50μA	£2-40
50-0-50μA	£2-35
100μA	£2-35
100-0-100μA	£2-35
500μA	£2-35
1mA	£2-15
5mA	£2-15
10mA	£2-15
50mA	£2-15
100mA	£2-15

1 amp.	£2-15
5 amp.	£2-15
10 amp.	£2-15
50μA	£2-55
50-0-50μA	£2-50
100μA	£2-50
100-0-100μA	£2-50
200μA	£2-50
500μA	£2-35
1mA	£2-35
5mA	£2-35
10mA	£2-35
50mA	£2-35
100mA	£2-35

***MOVING IRON—**
ALL OTHERS MOVING COIL
Please add postage

Type MR.85P. 4 1/4 in. x 4 1/2 in. fronts

50μA	£2-95
50-0-50μA	£2-40
100μA	£2-40
100-0-100μA	£2-30
200μA	£2-30
500μA	£2-20
500-0-500μA	£2-10
1mA	£2-10
1-0-1mA	£2-10
5mA	£2-10
10mA	£2-10

100mA	£2-10
500μA	£2-10
1 amp.	£2-10
5 amp.	£2-10
15 amp.	£2-10
30 amp.	£2-20
20V. D.C.	£2-10
50V. D.C.	£2-10
150V. D.C.	£2-10
300V. D.C.	£2-10
15V. A.C.	£2-10
30V. A.C.	£2-10
150V. A.C.	£2-10
300V. A.C.	£2-10
8 Meter 1mA	£2-15
VU Meter	£2-95
1 amp. A.C.	£2-10
5 amp. A.C.	£2-10
10 amp. A.C.	£2-10
20 amp. A.C.	£2-10
30 amp. A.C.	£2-10

Type MR.52P. 2 1/2 in. square fronts

50μA	£2-40
50-0-50μA	£2-35
100μA	£2-35
100-0-100μA	£2-25
200μA	£2-25
500μA	£2-20
1mA	£2-20
5mA	£2-20
10mA	£2-20
50μA	£2-65
50-0-50μA	£2-60
100μA	£2-60
100-0-100μA	£2-50
200μA	£2-50
500μA	£2-35
1mA	£2-35
5mA	£2-35
10mA	£2-35
50mA	£2-35
100mA	£2-35

10V. D.C.	£2-20
20V. D.C.	£2-20
50V. D.C.	£2-20
300V. D.C.	£2-20
15V. A.C.	£2-20
30V. A.C.	£2-20
150V. A.C.	£2-20
300V. A.C.	£2-20
8 Meter 1mA	£2-30
VU Meter	£2-65
1 amp. A.C.	£2-20
5 amp. A.C.	£2-20
10 amp. A.C.	£2-20
20 amp. A.C.	£2-20
30 amp. A.C.	£2-20

Type MR.65P. 3 1/2 in. x 3 1/2 in. fronts

50μA	£2-70
50-0-50μA	£2-60
100μA	£2-60
100-0-100μA	£2-50
200μA	£2-50
500μA	£2-35
500-0-500μA	£2-40
1mA	£2-40
5mA	£2-40
10mA	£2-40
50μA	£2-80
50-0-50μA	£2-70
100μA	£2-70
100-0-100μA	£2-60
200μA	£2-60
500μA	£2-45
500-0-500μA	£2-40
1mA	£2-40
5mA	£2-40
10mA	£2-40
50μA	£2-85
50-0-50μA	£2-75
100μA	£2-75
100-0-100μA	£2-65
200μA	£2-65
500μA	£2-50
500-0-500μA	£2-45
1mA	£2-45
5mA	£2-45
10mA	£2-45
50μA	£2-90
50-0-50μA	£2-80
100μA	£2-80
100-0-100μA	£2-70
200μA	£2-70
500μA	£2-55
500-0-500μA	£2-50
1mA	£2-50
5mA	£2-50
10mA	£2-50
50μA	£2-95
50-0-50μA	£2-85
100μA	£2-85
100-0-100μA	£2-75
200μA	£2-75
500μA	£2-60
500-0-500μA	£2-55
1mA	£2-55
5mA	£2-55
10mA	£2-55
50μA	£3-00
50-0-50μA	£2-90
100μA	£2-90
100-0-100μA	£2-80
200μA	£2-80
500μA	£2-65
500-0-500μA	£2-60
1mA	£2-60
5mA	£2-60
10mA	£2-60
50μA	£3-05
50-0-50μA	£2-95
100μA	£2-95
100-0-100μA	£2-85
200μA	£2-85
500μA	£2-70
500-0-500μA	£2-65
1mA	£2-65
5mA	£2-65
10mA	£2-65

10V. D.C.	£2-40
20V. D.C.	£2-40
50V. D.C.	£2-40
300V. D.C.	£2-40
15V. A.C.	£2-40
30V. A.C.	£2-40
150V. A.C.	£2-40
300V. A.C.	£2-40
8 Meter 1mA	£2-50
VU Meter	£2-90
1 amp. A.C.	£2-40
5 amp. A.C.	£2-40
10 amp. A.C.	£2-40
20 amp. A.C.	£2-40
30 amp. A.C.	£2-40

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

Type MR.38P. 1 21 32in. square fronts

200μA	£1-75
300μA	£1-75
500μA	£1-75
750μA	£1-75
1 amp.	£1-75
2 amp.	£1-75
5 amp.	£1-75
10 amp.	£1-75
3V. D.C.	£1-75
10V. D.C.	£1-75
15V. D.C.	£1-75
20V. D.C.	£1-75
50V. D.C.	£1-75
100V. D.C.	£1-75
150V. D.C.	£1-75
300V. D.C.	£1-75
500V. D.C.	£1-75
750V. D.C.	£1-75
15V. A.C.	£1-75
30V. A.C.	£1-75
150V. A.C.	£1-75
300V. A.C.	£1-75
500V. A.C.	£1-75
750V. A.C.	£1-75
15V. A.C.	£1-85
30V. A.C.	£1-85
150V. A.C.	£1-85
300V. A.C.	£1-85
500V. A.C.	£1-85
750V. A.C.	£1-85
8 Meter 1mA	£1-85
VU Meter	£2-30

Type MR.45P. 2in. square fronts

50μA	£2-50
50-0-50μA	£2-30
100μA	£2-30
100-0-100μA	£2-05
200μA	£2-05
500μA	£1-95
500-0-500μA	£1-85
1mA	£1-85
5mA	£1-85
10mA	£1-85
50μA	£2-85
50-0-50μA	£2-70
100μA	£2-70
100-0-100μA	£2-60
200μA	£2-60
500μA	£2-45
500-0-500μA	£2-35
1mA	£2-35
5mA	£2-35
10mA	£2-35
50μA	£2-90
50-0-50μA	£2-75
100μA	£2-75
100-0-100μA	£2-65
200μA	£2-65
500μA	£2-50
500-0-500μA	£2-40
1mA	£2-40
5mA	£2-40
10mA	£2-40

"SEW" EDGWISE METERS



Type PE.70. 3 1/2 32in. x 1 1/2 32in. x 2 1/2 in. deep

50μA	£3-05
100μA	£3-05
500μA	£2-70
100-0-100μA	£3-20
200μA	£3-20
500μA	£3-05
1 amp.	£3-20


Type MR.65. 3 1/2 in. square fronts

1 amp.	£2-15
5 amp.	£2-15
15 amp.	£2-15
30 amp.	£2-15
50 amp.	£2-15
5V. D.C.	£2-15
10V. D.C.	£2-15
50V. D.C.	£2-15
150V. D.C.	£2-15
300V. D.C.	£2-15
500V. D.C.	£2-40
100μV. D.C.	£2-40
30V. A.C.	£2-20
50V. A.C.	£2-20
150V. A.C.	£2-20
300V. A.C.	£2-20
500μA	£2-15
500-0-500μA	£2-15
1 amp. A.C.	£2-15
5 amp. A.C.	£2-15
10 amp. A.C.	£2-15
20 amp. A.C.	£2-15
30 amp. A.C.	£2-15
50 amp. A.C.	£2-15
VU Meter	£3-40

Type S-80 80 mm. square fronts

50μA	£3-50
50-0-50μA	£3-40
100μA	£3-40
100-0-100μA	£3-30
500μA	£3-05
1mA	£2-85
20V. D.C.	£2-85
50V. D.C.	£2-85
300V. D.C.	£2-85
1 amp. D.C.	£2-85

"SEW" EDUCATIONAL METERS

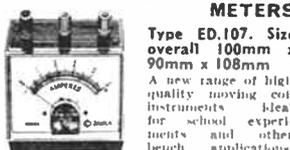

Type ED.107. Size overall 100mm x 90mm x 108mm
A new range of high quality moving coil instruments ideal for school experiments and other bench applications.
3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA	£5-50
100μA	£5-10
1mA	£4-85
50-0-50μA	£5-10
1-0-1mA	£4-85
1A d.c.	£4-85
5A d.c.	£4-85
10V d.c.	£4-85
20V. d.c.	£4-85
50V. d.c.	£4-85
300V. d.c.	£4-85
Dual range	
500μA/5A d.c.	£5-10
5V/50V d.c.	£5-10

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, 1/2 in. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. 90p. P. & P. 10p.
80 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.15 P. & P. 10p.
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. £1.65 P. & P. 15p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery	
S-260 General Purpose Bench Mounting	
1 Amp	£7-00
2.5 Amp	£5-05
5 Amp	£11-75
8 Amp	£15-90
10 Amp	£22-50
12 Amp	£23-60
20 Amp	£49-00
25 Amp	£58-00
40 Amp	£82-50
S-260B Panel Mounting	
1 Amp	£7-00
2.5 Amp	£8-05
Please add postage	
ALL MODELS	
INPUT 230 V 50/60 CYCLES	
OUTPUT VARIABLE 0-260 VOLTS	
Special discounts for quantity	

AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded.	
80 W	£2-10 P. & P. 18p
150 W	£

MULTIMETERS for EVERY purpose!


T560 POCKET MULTIMETER
High-precision at low cost. Ranges: D.C. 15V, 150V, 1,000V (10,000 μ pV), A.C. 15V, 150V, 1,00V (1,000 μ pV), D.C. Current 150mA. Resistance 100k ohms. **£1-85. Post 15p.**



ROUND SCALE TYPE PENCIL TESTER MODEL T.S.68
Completely portable, simple to use pocket sized tester. Ranges* 0/3/30/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. **ONLY £1-97 P. & P. 13p.**



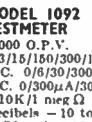MODEL 1092 TESTMETER
6,000 O.P.V. 0/5/15/150/300/1,200 V D.C. 0/15/30/300/600 V A.C. 0/300 μ A/300 MA 0/10K/1 meg Ω Decibels -10 to +16dB. **£2-75 each + 15p P. & P.**



LT601 MULTIMETER
New style 20,000 o.p.v. pocket multi-meter. 5/25/50/250/500/2500 V, D.C. 10/50/100/500/1000V, A.C. 50 μ A/250mA. 6K/1/6 meg ohms. -20 to +22 dB. **£3-75. Post 20p.**




HIOKI MODEL 720X
20,000 O.P.V. Overload protection 5/25/100/500/1000 V D.C. 10/50/250/1000V A.C. 50 μ A/250mA, 20K/2 meg Ω ohms. -5 to +42dB. **£4-97. P. & P. 15p.**




MODEL TH-12
20,000 o.p.v. Overload protection. Slide switch selector 0/25/250/10/50/250/1000V, D.C. 0/10/50/250/1000V, A.C. 0/50 μ A/25/250mA, D.C. 0/3K/30K/300K/3 meg -20 to +50dB **£4-97. Post 15p.**



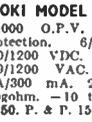HIOKI MODEL 730X
30,000 O.P.V. Overload protection. 6/30/60/300/600/1200 VDC. 12/60/120/600/1200 VAC. 60 μ A/30 mA/300 mA. 25/200K/2 megohm. -10 to +45dB. **£8-60. P. & P. 15p.**



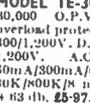MODEL TE-300
30,000 O.P.V. Mirror scale, overload protection 0/6/3/15/60/300/1,200V, D.C. 0/6/30/120/600/1,200V, A.C. 0/30 μ A/6mA/60mA/300mA/600mA. 0/8K/10K/100K/1 meg. ohm -20 to +43 dB. **£5-97. P. & P. 15p.**




MODEL TE-12
20,000 O.P.V. 0/0-0/5/30/120/600/1,200/3,000/6,000V, D.C. 0/6/30/120/600/1,200V, A.C. 0/60 μ A/6/60/600mA. 0/6K/600K/6 meg./60 Meg. Ω 50pF-0.2mFd. **£5-97. P. & P. 17p.**



MODEL PL436
20k Ω /Volt D.C. 8k Ω /Volt A.C. Mirror scale. 6/3/12/30/120/600 V D.C. 3/30/120/600 V A.C. 60/600 μ A/60/600 mA. 10/100K/1 Meg/10 Meg Ω -20 to +46dB. **£6-97. P. & P. 12p.**



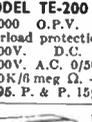MODEL TE-200
20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V, D.C. 0/10/50/250/1,000V, A.C. 0/50 μ A/250 mA. 0/6K/6 meg Ω -20 to +62dB. **£3-95. P. & P. 15p.**



THK MODEL TW-50K
46 ranges, mirror scale. 50K/Volt. D.C. 5K/Volt A.C. D.C.: Volts: 125, 25, 1-25, 2-5, 5, 10, 25, 50, 125, 250, 500, 1000V, A.C. Volts: 1-5, 2-5, 5, 10, 25, 50, 125, 250, 500, 1000V, D.C. Current: 25, 50 μ A, 2-5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω . Decibels: -20 to +81-5db **£8-50. P. & P. 17p.**



MODEL 500
30,000 O.P.V. with overload protection mirror scale 0/5/2-5/10/25/100/250/500/1,000V, D.C. 0/2-5/10/25/100/250/500/1,000V, A.C. 0/50 μ A/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg/60 Meg Ω **£3-87. Post paid.**




MODEL K228A
Taut band suspension. Overload protection. Polarity reversing switch. 30,000 o.p.v. 0/5/2-5/10/25/150/250/500/1000/2500V, D.C. 0/15/50/150/500/1000V, A.C. 0/50 μ A/5/50/150/500mA/5A D.C. 0/3K/300K/3 meg. **£3-95. Post 20p.**




HIOKI MODEL 750X
50,000 o.p.v. 43 ranges 0-0.3 to 1,200V D.C. 0-3 to 1,200V A.C. 0-30 μ A/300mA. 0-3K/30 meg ohms. -10 to +17dB. **£3-97. Post 20p.**



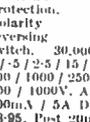
MODEL C-7080 EN
46 range mirror scale. 20,000 o.p.v. 0/25/1/2-5/10/50/100/500V, D.C. 0/2-5/10/50/100/500V, A.C. 0/50 μ A/5/10/100/500mA/10 amp. D.C. 0/1/25/200K/2 Meg/20 Meg ohm -20 to +63dB. **£13-50. P. & P. 20p.**



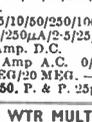
HT10084 MULTI-METER
Features A.C. current ranges. 100,000 o.p.v. Mirror Scale. Overload protection. 0/0-5/2-5/10/50/250/500/1000 V D.C. 0/2-5/10/50/250/1000 V, A.C. 0/10/250 μ A/2-5/25/250 MA/10 Amp. D.C. 0/20K/200K/2 MEG/20 MEG. -20 +62dB. **£12-60. P. & P. 25p.**



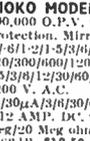
HIOKI MODEL 700X
100,000 O.P.V. Overload protection. Mirror scale. 3/6/11-2/1-5/3/4/12/30/60/120/300/600/1200V DC 1-5/3/4/12/30/60/150/300/600/1200 V, A.C. 15/30 μ A/30/30/60/150/300mA 0/12 AMP. D.C. 2K/200K/2 Meg/20 Meg ohm -20 to +63dB. **£13-50. P. & P. 20p.**



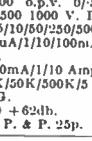
370 WTR MULTI-METER
Features A.C. current ranges. 20,000 o.p.v. 0/5/2-5/10/50/250/500 1000 V, D.C. 0/2-5/10/50/250/500/1000V A.C. 0/50 μ A/1/10/100mA/1/10 Amp D.C. 0/100mA/1/10 Amp A.C. 0/6K/50K/500K/5 MEG/50 MEG. -20 +62dB. **£15. P. & P. 25p.**



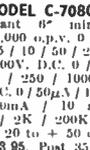
MODEL C-7080 EN
46 range mirror scale. 20,000 o.p.v. 0/25/1/2-5/10/50/100/500V, D.C. 0/2-5/10/50/100/500V, A.C. 0/50 μ A/5/10/100/500mA/10 amp. D.C. 0/1/25/200K/2 Meg/20 Meg ohm -20 to +50 dB. **£13-95. Post 35p.**



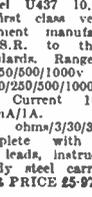RUSSIAN 22 RANGE MULTIMETER
Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/10/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100 μ A/1/10/100mA. Resistance 300 ohms/3/30/300K/3m Ω . Complete with batteries, test leads, instructions and sturdy steel carrying case. **OUB PRICE £5-97. P. & P. 25p.**




U4312 MULTIMETER
Extremely sturdy instrument for general electrical use. 807 o.p.v. 0/3/1-5/7-5/30/60/150/300/600/1000 VDC and 50V V. 0/3/1-5/7-5/30/60/150/300/600/1000 VAC. 0/300 μ A/1-5/6/15/60/150/600mA/1-5/6 AMP. D.C. 0/1-2/3/6/15/60/150/600mA/1-5/6 AMP. AC. 0/200 Ω /3K/30K Ω . Accuracy DC 1%. AC 1-5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9-50 plus P. & P. 25p.**

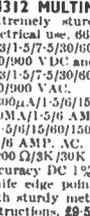

Selected TEST EQUIPMENT

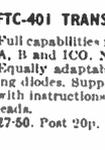
FTC-401 TRANSISTOR TESTER
Full capabilities for measuring A, B and I.C.O. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. **£7-50. Post 20p.**



TE-16A TRANSISTORISED SIGNAL GENERATOR
5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide area to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2. Complete with instructions and leads. **£7-97. Post 25p.**



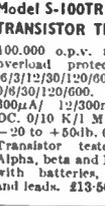Model S-100TR MULTIMETER TRANSISTOR TESTER
100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 V DC. 0/6/30/120/600 V AC. 0/12/600 μ A/12/300mA/12 AMP DC. 0/10 K/1 MEG/100MEG. -20 to +50dB. 0-0.1-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. **£13-50. P/P 25p.**



TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE
A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 Ω 11-1 meg Ω . 6 Ranges \pm 1%. L.1 μ H - 111 H. C.10PF - 1110mF. 6 Ranges \pm 2%. TURNS RATIO 1/1000-1/1/100. 6 Ranges \pm 1%. Bridge voltage at 1,000 cps. Operated from 9 volts. 100 μ A Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 6 x 2 1/2. **£20. P. & P. 25p.**



MODEL 449A IN CIRCUIT TRANSISTOR TESTER
Checks true A.C. beta in/out. Checks Icho. Checks diodes in / out. Checks SCR, etc. Beta HI 10 - 500. 80 x 40mm. **£17-50. Post 25p.**




MODEL TE.15 GRID DIP METER
Transistorised. Operates a Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440Kc/s-280Mc/s. 6 coils. 500 μ A Meter. 9v battery operation. Size 180 80 x 40mm. **£12-50. Post 20p.**



TE-200 RF SIGNAL GENERATOR
Accurate wide range signal generator covering 120 Kc/s 500 Mc/s on 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xial socket for calibration. 220/240V. A.C. Brand new with instructions. **£15. Carr. 37p. Size 140 x 215 x 170 mm.**



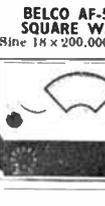BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR
Sine 18 x 200,000 Hz: Square 18 x 50,000 Hz. Output max. +10 dB. (10 K ohms) Operation internal batteries. Attractive 2-tone case 7 1/2 x 5 x 2 1/2. Price **£17-50. Carr. 17p.**




MODEL L-55 FET V.O.M.
Input impedance 10 meg ohms. 0/3/1-2/6/30/120/600V, D.C. 0/3/12/60/120/600V, A.C. 0/120 μ A/120mA D.C. 0/1K/100K/10 meg /100 meg ohms **£15-97. Post 15p.**




MODEL MG-100 SINE SQUARE WAVE AUDIO GENERATOR
Range 180-220,000Hz Sine Wave. 100,000 Hz Square Wave. Output Sine or Square wave 10v. P. to P. Size 180 x 90 x 90mm. Operation 220/240V. A.C. **£17-50. Post 37p.**



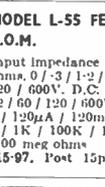CI-5 PULSE OSCILLOSCOPE
For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 2 meg. Sensitivity at 100KHz 5VRMS/mm. -1-25; HOR. AMP. Bandwidth 500KHz. Sensitivity at 100KHz. V RMS/mm. -3-25; Preset triggered sweep 1-3,000usec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V. AC operation. **£39-00. Carr. paid.**



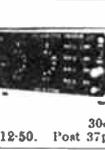MODEL AT201 DECADE ATTENUATOR
Frequency range 0-200KHz. Attenuator 0-111dB. 0-1dB step. Impedance 600 ohms. Max. input power 30dbm. Size 180 x 90 x 55mm. **£12-50. Post 37p.**



TO-3 PORTABLE OSCILLOSCOPE
3in. tube. V amp. Sensitivity 0-1v p-p/CM. Bandwidth 1-5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0-9v p-p/CM. Bandwidth 1-5cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps 300 kHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15lb. **£40-00. Carr. 50p.**



TE-65 VALVE VOLTMETER
24 ranges. 1-5-1,500v. A.C. volts 1-5-1,500v. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. **£17-50. P. & P. 30p. Additional probes available. R.F. £2-12; H.V. £2-50.**



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE
5 mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in. x 4in. C.R.T. Calibrated triggered sweep from 2 usec. to 100 milli-sec. per cm. Free running time base 50 cps-1 mc/s. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual **£87. Carr. Paid.**




MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER
Sensitivity 330 ohms/Volt AC and DC. Accuracy 5% D.C. 1% A.C. Scale length 165mm. 0/300/750 μ A/1-5/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5-AMP DC 0/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5-AMP AC 0/75/160/300/750mV/1-5/3/7-5/15/30/75/150/300/750V DC 0/750mV/1-5/3/7-5/15/30/75/150/300/750V AC. Automatic cut out. Supplied complete with test leads, manual and test certificates. **£49-00. Post 50p.**



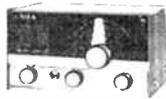G. W. SMITH & CO (RADIO) LTD.
Also see opposite page and next two pages

UNR-30 RECEIVER

4 Bands covering 550Kc/s - 30Mc/s. B.F.O. Built-in Speaker 220/240v. A.C. Brand new with instructions. £15 75. Carr. 37p



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550Kc/s-30Mc/s. FET 8 Meter. Variable BFO for MMB, Built-in Speaker, Bandspread, Sensitivity Control. 220/240v. A.C. or 12v. D.C. 12 1/2" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37p.

SKYWOOD CX203 COMMUNICATION RECEIVER

Multi state. Coverage on 5 bands-200-420 KHz and .55 to 30 MHz. Illuminated slide rule dial. Bandspread. Aerial tuning B.F.O. AVC, ANL, 'B' meter. AM/CW/SSB. Integrated speaker and phone socket. Operation 220/240v AC or 12v DC. Size 3 1/2 x 2 1/2 x 1 1/2 inch. Complete with instructions and circuit. £38-50. Carr. 50p.

LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400Kc/s. 500 Kc/s-30Mc/s. FET front end. 2 mech. filters. product detector. variable B.F.O. (injection) Inter. M. Meter, Bandspread, RF (dial. 10" x 10" x 2 1/2"). 18 lbs. 220/240v. A.C. or 12v. D.C. Brand new with instructions. £80. Carr. 50p.

TRIO PR95DS COMMUNICATION RECEIVER

4 band covering 550Kc/s. to 30 Mc/s. continuous and automatic and 4 1/2 ohm output and phone jack. 881-CW. ANL. Variable B.F.O. 8 meter. Rej. bandspread dial. 1P frequency 405 Kc/s. audio output 1.5w. Variable HF and AF gain controls 110/250v. A.C. Size: 7" x 13" x 10" with instruction manual. £49 50. Carr. Paid.

EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7 50 each P. & P. 37p. Model 400. 13" x 8" with twin tweeter/crossover. 65-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £5-65 each. P. & P. 25p.

HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt. current and ohms with optional plug in cards. Specification: Accuracy: ± 0.2 , ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999). Input Impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100v. D.C. Input: Fully floating (3 poles). Input power, 110-230v. A.C. 50/60 cycles. Overall size: 5 1/2" x 2 1/2" (1 1/2" x 8 3/16"). AVAILABLE BRAND NEW AND FULLY GUARANTEED. £35-50. Carr. 60p.

SINCLAIR IC-12

List Price £2-98
OUR PRICE £1-80
P. & P. 10p

SINCLAIR EQUIPMENT

Project 60 Package offers:
2 x Z30 amplifier, stereo 60 pre-amp. PZ3 power supply. £16-95 Carr. 37p. Or with PZ6 power supply £18-00 Carr. 37p. 2 x Z50 amplifier, stereo 60 pre-amp. PZ8 power supply. £20-25. Carr. 37p.
Transformer for PZ8. £2-97 extra.
Add to any of the above £4-45 for active filter unit and £13-00 for pair of Q16 speakers. All other Sinclair products in stock.
2000 Amp £21-95 Carr. 37p. 3000 Amp £28-50 Carr. 37p. Neoteric Amp £43-95. Carr. 37p IC12 £1-80 p. & p. 10p.
NEW PROJECT 605 - £20-97. Carr. 37p.

SPECIAL OFFER! GOODMANS AXIOM 301

Hi Fi 12" 20 watt twin cone full range speaker. 30-16,000 Hz. 16,500 gauss. 8 ohm impedance. Brand new and in boxed.
List price £21.75 OUR PRICE £12-50 each. Carr. 50p.

EA-41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2 x 3 x 4 1/2 in. £6-97. P. & P. 15p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo hook-kraft speakers. Deluxe teak veneered finish. Size 14 1/2" x 9" x 7 1/2". 8 ohms. 8 watt RMS. 16 watt peak. Complete with DIN lead. £18-95 pr. Carr. 50p.

HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic ceramic or twin input stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. Input 50mV/100mV. Output 60mW. £6-97. P. & P. 10p.

SPECIAL PURCHASE! NEAT G30J STATIC BALANCE PICK-UP ARMS



Identical specification to NEAT G30 arm but with two-tone chrome and black finish. Complete with head shell, pick up rest and plug in phono leads.

BRAND NEW—FULLY GUARANTEED ONLY £8-95. P. & P. 25p.

ARF-300 AF/RF Signal Generator

All transistorised, compact, fully portable. AF sine wave 15 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10v. P-P. RF 100KHz to 200 MHz. Output 1v. maximum. Operation 220/240v. A.C. Complete with instructions and leads. £29-95. Post 50p.

AKAI BARGAINS

SUPER MONEY SAVING OFFERS—BUY NOW WHILE STOCKS LAST! BRAND NEW AND FULLY GUARANTEED

1721 Tape Rec. £73-95
X5000 Tape Rec. £99-95
GX370 Tape Deck £259-95
4000DS Tape Deck £73-95
4000DS Dust Cover £4-75
X200 Tape Deck £99-95
X201D Tape Deck £132-95
X221D Tape Deck £169-95
GX220D Tape Deck £148-50
GX280D Tape Deck £249-40
X1810D Tape/8 track Deck £189-95
GX1900D Tape/Cass. Deck £177-95
X2000D Tape/Cass/8 Track Deck £223-95
CR81 8 track Rec. £80-95
CR81D 8 track Rec. £65-95
CR81T 8 track/Receiver £118-90
CR80DS 8-track £121-95
CR80RS 8 track system £145-00

GX140 Cassette Rec. £89-95
GX140D Cassette Deck £87-95
GX140T Cassette/Receiver £128-95
GX143D Cassette Deck £89-95
GX146D Cassette Deck £108-50
GX146 Cassette Receiver £115-95
GX180D Cassette Deck £111-85
GX183D Cassette Deck £110-85
CR35D Cassette Deck £69-50
AA6300 Receiver £79-95
AA8030 Receiver £106-95
AA8080 Receiver £144-95
AA8500 Receiver £178-00
ADM11 Microphones (Pair) £7-80

Carrage 50p extra. (Receivers & Decks 75p)

DOLBY SYSTEM NOISE REDUCTION UNIT



Improves the performance of cassette and semi-professional recorders. Reduces tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Controls for input levels and noise reduction on record and replay. 2 meters for Dolby level. Off tape monitoring. Frequency response: 20Hz to 16kHz \pm 1dB 19kHz \pm 5dB. Size 10 1/2" x 9" x 3 1/2". AC 200/240V. OUR PRICE £32-50 Carr. 50p.

1021 STEREO LISTENING STATION



For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain headphone sockets. 6" x 4" x 2 1/2". £8-85. P. & P. 10p.

MP7 MIXER PREAMPLIFIER

6 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 11 1/2" x 9" x 3" Input 100mV 3 x 3mV 50K; 2 x 3mV 400 ohm. Phono neg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 280mV 100K. £8-97. P. & P. 20p.

TE-1035 STEREO HEADPHONE

Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm Impedance 20-18,000 Hz. With lead and stereo jack plug. N.Y.L. £1-97. P. & P. 12p.

NEW GARRARD MODULES



Popular range of Garrard decks with Rhure cartridge fitted in deluxe plinth with blinged lid.
SP25 III Module/M75-6 £83-50
AP76 Module/M73-6 £33-80
AP96 Module/M78-6 £38-75
Zero 1008 Module/M93E £62-50
Carr. 50p extra any item.

HOSIDEN DH-085 DE-LUXE STEREO HEADPHONES

Features unique detachable 2 way units and fitted adjustable levers, controls. 8 ohm Impedance 20-20,000cps. Complete with spring lead & stereo jack plug £7-97. P. & P. 12p.

GENUINE BARGAIN! KOSS SP.3XC STEREO HEADPHONES

Response 10-15,000Hz. Impedance 4-6 ohms. Brand new, boxed & fully guaranteed (List £9-50). OUR PRICE £6-50. P. & P. 25p.

HOSIDEN DH-025 STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable head-band. 8 ohm Impedance. 12,000 cps. Complete with lead and plug. ONLY £9-97. P. & P. 12p.

TAPE CASSETTES

Top quality Hi-Fi Low Noise in Library cases.
C90 8 for 75p. 10 for £2-85
C90 3 for £1-05. 10 for £3-80
C190 3 for £1-85. 10 for £4-90
Tape Head Cleaner 80p each. P. & P. 10p extra.

SPECIAL OFFER! ROTEL RH700 STEREO HEADPHONES

30-20,000Hz. 8-16 ohm. (List £9-95). OUR PRICE £6-75. P. & P. 20p.

TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6 x 4 x 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Mc/s. Really built ready for use. Fantastic value for money. £6-87. P. & P. 12p. Stereo multiplex adaptor £4-97).

TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive, soft earcup, adjustable headband. Magnetic Impedance 2,600 ohms. £1-97. P. & P. 10p.

HAND HELD 2-WAY WALKIE TALKIES

Industrial quality in robust metal cases. Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying cases.
2 channel £52-50 Pair. Post 50p.
300 mW £79-50 Pair. Post 50p.
3 channel £79-50 Pair. Post 50p.
2 watt. £79-50 Pair. Post 50p.

G. W. SMITH & CO (RADIO) LTD. Also see previous pages and opposite page

FANTASTIC OFFER!

NIKKO TRM 50 STEREO AMPLIFIER



17 + 17 watts rms stereo amplifier with inputs for Magnetic and Crystal phono, Tuner, Tape, Aux and Tape Monitor. Outputs for two pairs of stereo speakers and Tape. Stereo headphone socket. Full range of controls including loudness control, scratch filter, etc. Size 13" x 9 1/2" x 3 1/2". Unrepeatable offer—limited stocks!

List price £59.50
OUR PRICE

£39.95

Carriage 50p

NIKKO TRM.50 SYSTEM




NIKKO TRM50 17 + 17 watt rms. stereo amplifier, BSR MP60, plinth & cover. Goldring G800 cartridge, pair of Linton 2 speakers and all leads.

OUR PRICE **£104.90**

Carr. and Ins. £1.50

LEAK DELTA 30 SYSTEM

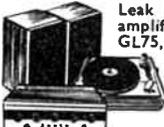

Leak Delta 30 stereo amplifier, Goldring GL75, plinth, cover and G800 cartridge. Pair of Leak 150 speakers and all leads.

OUR PRICE **£123.50**

Carr. and Ins. £1.50

TELETON SAQ206B SYSTEM



Teleton SAQ206B 8 + 8 watt Amplifier, BSR MP60, plinth & cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE **£54.40**

Carr. £1.50

Amplifier only, £22.95. Carr. 50p.

AUDIOTRONIC ACR.3500 MW/LW CAR RADIO



Fully transistorised, dual waveband. Size 6 1/2" x 4 1/2" x 2". 12v. D.C. Neg. or Pos. earth. Complete with fixing kit, speaker and leads. ONLY £7.50. Post 20p.

SUPER BARGAIN! AUDIOTRONIC ACP.8 8-TRACK CAR STEREO TAPE PLAYER



Tone, volume and balance controls. Track selector. Complete with matched pair of stereo speakers, connections and fittings. ONLY £15.95. Post 30p. (illus is example only).

BH.001 HEAD SET AND BOOM MICROPHONE

Moving Coil. Ideal for language teaching, communications. Headphone imp. 15 ohms. Microphone imp. 200 ohms. £4.62. P. & P. 15p.



WHARFEDALE LINTON SYSTEM



Wharfedale Linton Amplifier, Linton Turntable, pair of Linton 2 speakers and all leads.

OUR PRICE **£106.00**

Carr. and Ins. £1.25

LINTON RECEIVER SYSTEM £165.00. Carr. & Ins. £1.25.

AMSTRAD 8000 II SYSTEM

Amstrad 8000 II 7 + 7 watt amplifier. BSR MP60, plinth and cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.



OUR PRICE **£48.25**

Carr. £1.00

Amplifier only, £16.95. Carr. 50p.



B.S.R. TD8S 8-TRACK STEREO TAPE PLAYER DECK

Integrated preamps (output 125 mV) to feed into any stereo amplifier. Automatic and manual programme selector. 4 pole synchronous motor. 210/240 V.

OUR PRICE

£16.25

Post 50p

SPECIAL PURCHASE!

FERGUSON 3414 STEREO TUNER AMPLIFIER TURNTABLE UNIT



10 + 10 watts rms. Five push buttons with separate scales for pre-tuning to desired FM station. Housed in a handsome walnut finished cabinet with BSR PI28/MP60 record deck with Goldring G800H stereo magnetic cartridge. Offered complete with cover and a pair of matching Medway Speakers, size 18" x 11" x 8". TODAY'S VALUE AT LEAST £125!

OUR PRICE **£75.00**

Carr. & Ins. £1.50.

HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE

SEND S.A.E. FOR FULL DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



SAVE £££'s PHILIPS GA308 TRANSCRIPTION TURNTABLE

3 speeds 3 1/2 and 45 rpm. Lightweight tubular counterbalanced arm. Belt driven low speed synchronous motor. Viscous damped pick up lift/lower device. Complete with tone plinth and hinged cover. GA308 less cartridge (List £36.55).
OUR PRICE £24.50. P. & P. 50p.
GA308 PU with GP400 stereo magnetic cartridge (List Price £47.65)
OUR PRICE £29.95 P. & P. 50p.
LIMITED NUMBER ONLY!



RECORD DECKS (P. & P. 50p)

B.S.R. McDONALD
C114 3In1 £47.97
C129 Mono £8.50
C137 £28.35
MP60 £9.50
610 £12.95
610 £12.95
210/TPD3 £27.75
MP60/G800 £12.95
MP60/TPD1 £16.05
MP60/TPD1/G800 £19.50
MP60/TPD2 £14.35
610/TPD1 £19.95
610/TPD1 £25.95
HT70 £13.99
HT70/G800 £17.25
HT70/TPD1 £20.35
HT70/TPD1/G800 £23.90



GOLDRING
GL69/2 £10.50
GL72 £20.95
GL72/P £27.50
Plinth 69/72 £7.00
LID 72 £3.25
GL75 £28.95
GL75/P £28.95
Plinth 75 £7.35
LID 75 £4.00
G99 £19.25
GL85P/C £28.95
G101P/C £20.50

810 Plinth/Cover £9.25
HACKER
GP45/30 £49.50
T45 Tabic £4.95
LEAK
Delta Turntable £52.50

CONNOISSEUR
BD1 Kit £10.90
BD1 Chassis £19.60
BD1/SAU2/Plinth £33.10
BD2/SAU2/Chassis £16.50
BD2/SAU2/Plinth/C £33.85

GARRARD
2025 T/C Stereo £8.50
SP25 III/Arcam £10.25
SP25 III £10.25
SP25 III/M75-6 £21.95
SP25 III Module/M75-6 £23.80
SL45B £17.95
AP76 £17.95
AP76 Module/M75-6 £23.80
BL72B £21.95
SL95B £23.25
401 £25.95
ZERO 100A £35.95
ZERO 100B £35.95
ZERO 100S Mod/M93-E £52.00
AP96 Module/M75-6 £33.75

GOODMANS
TD100 Teak £51.95
TD100 White £52.25

MICRO-SEIKI
MR111 £29.50
MR11 Plinth & Cover £9.50

PHILIPS
GA105 £16.95
GA160 £27.00
GA308 Teak £24.50
GA308PU Teak £29.95
GA212 £56.75

PIONEER
PL12D £24.50
PL15C £51.38
PLA35 £83.65
PL50 £111.85
PL41D £118.60
PL61 £119.95

THORENS
TD125 II £66.50
TD125 AB II £99.98
TX25 £66.95
TD160C £66.95
TD150A II £35.98
TD150AB II £39.98

WHARFEDALE
Linton Turntable £26.95

ROTEL BARGAINS!

All brand new and guaranteed



RA210 Amp ... £22.50
RA310 Amp ... £34.95
RA610 Amp ... £48.25
RX150 Receiver ... £45.95
RX200 Receiver ... £57.50
RX400 Receiver ... £70.95
P. & P. 50p extra any item.

WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 8" dia. Impedance 4/8 ohms. High flux ceramic magnet, 20 watts rms. Brand new £1.50. Carr. 37p.



HOMER INTERCOMS

Ideal for home office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station £2.97, 3 Station £5.25, P. & P. 15p
4 Station £6.62, P. & P. 17p.

CREDIT TERMS FOR CALLERS ACCESS & BARCLAYCARD WELCOME

V.A.T. INFORMATION

All mail orders received on or after April 1st. will be subject to Value Added Tax.

THIS MUST BE ADDED TO THE TOTAL VALUE OF GOODS ORDERED (INCLUDING POSTAGE/CARRIAGE) AND ENCLOSED WITH ORDER.

PLINTHS & COVERS (P. & P. 50p)

Budget SP25, etc. £3.20
Budget AP76/Zero 100S £4.50
Budget 118.R. £3.25
SME 2000 System £24.50

RECORD DECK PACKAGES (P. & P. 50p)

Decks supplied with stereo cartridge ready wired in plinth with cover.



GARRARD
3025TC/8TAHCD £12.75
SP25 III/G800 £23.50
SP25 III/M75-6 £18.50
SP25 III/M44-7 £19.75
SP25 III/M44-E £20.95
SP25 III/M55E £22.40
AP76/G800 £27.95
AP76/M75-6 £30.25
AP76/M55E £30.50
AP76/M75EJ £32.50
AP76/G800E £30.75
AP76/M44E £30.50
AP76/M75ED £38.95

B.S.R. McDONALD
MP60/G800 £17.50
MP60/M44-7 £18.95
MP60/M44-E £19.95

GOLDRING
GL75/G800 £39.50
GL75/G800E £42.50

G.W. SMITH & CO (Radio) LTD

Personal Callers Welcome - All Branches Open 9-6 Mon. to Sat.

10 TOTTENHAM CT. RD. LONDON, W.1
27 TOTTENHAM CT. RD. LONDON, W.1
257/258 TOTTENHAM CT. RD. LONDON, W.1
3 ABLE STREET, LONDON, W.C.2
34 LISLE STREET, LONDON, W.C.2
311 EDGWARE ROAD, LONDON, W.2

Tel: 01-637 2322
Tel: 01-636 3715
Tel: 01-580 0670
Tel: 01-437 8204
Tel: 01-437 9155
Tel: 01-262 0387

All Mail Orders to 11-12, Paddington Green, London, W.2
Tel: 01-262 6662

★ ★ ★ ★ ★ ★ ★ ★ ★ ★

CUSTOM BUILT TO FIT YOUR SHACK AND YOUR POCKET!

★ ★ ★ ★ ★ ★ ★ ★ ★ ★

The Space Age WORLD RECORD award winning 7' 6" long All Band JOYSTICK VFA Antenna—JOYMATCH A.T.U.—TRIO RECEIVER or TRANSCEIVER—Matching HEADPHONES—A COMPLETE STATION IN ONE COMPACT PACKAGE—THE FLAT DWELLER'S DREAM!

1972 JOYSTICK VFA £11.40 (A); JOYMATCH ATU 111 ★ or 111A £11.40 (B); JOYMATCH ATU LO-Z500 £16.45 (C).

COMMUNICATIONS HEADPHONES £2.60 (D)

(All including postage, packing, accessories & insurance.)

PARTRIDGE PACKAGE No. 1

• JR59DS receiver .. £49.50
• Items (A); (B); (D) above .. £11.00
Complete Gen. Coverage Station .. £60.50

PARTRIDGE PACKAGE No. 2

• JR310 receiver .. £75.00
• Items (A); (B); (D) above .. £7.00
Complete Amateur RX Station .. £82.00

PARTRIDGE PACKAGE No. 3

• JR599 receiver .. £185.00
• Items (A); (B); (D) above .. FREE
Complete Amateur RX Station .. £185.00

PARTRIDGE PACKAGE No. 4

• TS/PS515 Transceiver 180W .. £210.00
• Items (A); (C); (D) above .. FREE
Complete TX-RX Station .. £210.00

BARCLAYCARD — ACCESS — PERSONAL LOANS!!

ALSO: SP5D SPKR. £4.50; 2M CAR TRANSCEIVER TR7100 £99.50; 2M PERSONAL TRANSCEIVER TR2200 £62.50; OA2 MAINS STABILISER 67p.

NEW: World-wide reception on the amazing "DX—CRYSTAL SET" £1.75 (+ 25p) including unique aerial.

PARTRIDGE BUDGET LINE—

ARTIFICIAL EARTH—SOLVES YOUR EARTH PROBLEMS £4.80; AERIAL BANDSWITCH—TUNED AERIAL £4.80; A.T.U. KIT—FULL COVERAGE TX/RECEIVER £4.80; ASSEMBLED £5.80.

(All including Postage, Packing, Accessories & Insurance.)
Send 3p stamp for full illustrated details of Partridge Products.
TRIO brochures (state which) 3p stamp extra.

ADD V.A.T. TO ALL QUOTES FROM APRIL 1st
CARRIAGE & INSURANCE EXTRA OVERSEAS.

BOX 5
PARTRIDGE ELECTRONICS LTD.
BROADSTAIRS, KENT

Phone: 0843 62535 or 62839 cheap periods.

BATTERY/MAINS PORTABLE RECEIVER

WHAT RADIO PRICED AT UNDER £120 GIVES YOU SUCH A VARIED CHOICE OF TRANSMISSIONS?

Picks up ALL THE USUAL BBC Programmes *All the new local radio stations *Continental *World-wide transmissions *Pop Pirates *Radio Hams *Aircraft *Shipping *Police *Taxis *R.A.C. *A.A. *Fire Brigade *T.V. Sound *Ambulances and 1,000s more.

CASH PRICE £49.50 50p p. & p. or £14.50 dep. + 50p. p. & p. & 6 months at £7 (£56.50).

THE BEST PORTABLE RADIO EVER MADE! We think so. As well as the standard long and medium wavebands it has three short wave bands (including the Marine and Traveller Band) AND NO LESS THAN THREE V.H.F. BANDS. Listen to your favourite B.B.C. programme and then—at the flick of a switch—tune into the control tower and hear a "crippled airliner" being talked down to safety. Or listen to the travellers and ocean-going liners—Eavesdrop on the taxi-cabs, fire brigades, ambulances, A.A., R.A.C. and 100s of others R.T. mobiles! Extensive shortwave coverage can give you Australia, Pakistan, North America, Far East, etc., etc. World famous manufacturer. **FULL 3-YEAR WRITTEN GUARANTEE.** Beautifully finished in Teak Wood and Stainless Steel. Portable 12in x 9in x 4in, using standard batteries—or can be plugged directly into mains. 14 transistors 6 diodes, 1 thermistor, internal ferrite rod aerial PLUS two external telescopic antennas—with sockets for additional aerials, or car aerials. Automatic Drift-Free Reception. Biting tone control. Hi-Fidelity earphone for private listening, local DX switch. **FREQUENCIES:** Long W 150-350Kcs. Medium W 540-1805 Kcs, Marine 1.6-4 Mcs Short W 1 3.7-9 Mcs, Short W 2 9-22 Mcs. F.M. (V.H.F.) 88-108 Mcs. Aircraft (V.H.F.) 108-136 Mcs. Public Service (V.H.F.) 148-174 Mcs.

NOTE—The Ministry of Posts & Telecommunications state a Licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

PROFESSIONAL 2 CHANNEL WALKIE-TALKIE SYSTEM

JUST ARRIVED—A NEW system from Switzerland!—the home of precision built electronics equipment. **GENUINE 2-WAY WALKIE-TALKIE SYSTEMS.** Ideal for all outdoor control, doctors, fishermen and general marine use. The telescopic antenna pulls in the voice at the other end with crystal clear clarity—often 8 miles away! Frequency 29.9 mcs. (interchangeable according to your licence stipulations. Battery operated—no wires. A tremendous time & money saver. 3 Units complete with FREE carrying cases. NOTE: Licence req. to operate. Terms: £19 dep. & months at £9. (Total £78)

£64

Send 5p stamp for Discount Brochure of unusual Frequency Radios
SCIENTIFIC & TECHNICAL (PW4) Towerfield Trading Estate, Southend, Essex

BAKER 12in MAJOR £9

30-14500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly flux density 145000 gauss. Bass resonance 40 c.p.s. 20 watt RMS.

MAJOR MODULE KIT £11.50

30-17000 cps. with tweeter, crossover and baffle.

Baker Loudspeakers full range			
Regent 12in	£8	Superb 12in	£15
Major 12in	£9	Auditorium 12in	£14
Deluxe 12in	£10	Auditorium 15in	£20
		Group 25 12in	£8
		Group 35 12in	£9
		Group 50 15in	£20

Baker Loudspeaker Co., Bensham Manor Passage,
Thornton Heath, Surrey. Tel. 01-684 1665

AUTOMATIC EMERGENCY SUPPLY

250v 50Hz—150 watt inverter. Full kit of parts excluding meter. Circuit as appeared in December P.W. Complete kit—£16.95 + 80p P. & P.

OTHER INVERTERS AVAILABLE IN KIT FORM

150 Watt—£13.50 + 60p P. & P.	75 Watt—£7.80 + 60p P. & P.
300 Watt—£17.90 + 85p P. & P.	40 Watt—£5.20 + 40p P. & P.
	25 Watt—£2.60 + 20p P. & P.

All above operate from 12v. battery and give 250v.—50Hz. Output. 24 volt types are also available, alternative outputs or taps can be supplied. Transformers and/or Transistors can be supplied separately.

SPECIAL OFFER

12v. Fluorescent lights, suitable for tents, caravans, houses or secondary lighting for factories, hotels, etc. 12 inch—8 watt—£3.40 post paid. 21 inch—13 watt—£4.20 post paid. Large discounts available for quantities.

TEXAN AMPLIFIER

Fibre glass P.C. board—£2.00 + 10p P. & P.
Transformer—£4.00 + 30p P. & P.
Other components including Teak Cabinet—£24.00 + Postage.

ASTRO ELECTRONICS
8, BARNES ROAD, CHESTERFIELD, DERBYSHIRE

TRANSNIES

24 WOODHILL, HARLOW, ESSEX

Phone Harlow 37739

P/P 10p. Price list S.A.E. (No callers please)

LOWEST PRICES

Please compare our Prices!!!
all our stock are brand new. With full
money refund if not completely satisfied.

74 Series TTL



7400	1-24	25 plus	7450	1-24	25 plus	7492	1-24	25 plus
7401	15p	14p	7451	15p	14p	7493	67p	64p
7402	15p	14p	7453	15p	14p	7494	77p	74p
7403	15p	14p	7454	15p	14p	7495	77p	74p
7404	15p	14p	7460	15p	14p	7496	77p	74p
7405	15p	14p	7470	29p	26p	74100	1-75p	1-65p
7408	18p	17p	7472	29p	26p	74104	7-75p	9-9p
7410	15p	14p	7473	37p	35p	74105	97p	94p
7411	15p	14p	7474	37p	35p	74107	40p	33p
7413	29p	26p	7475	47p	45p	74110	1-25p	1-25p
7420	15p	14p	7476	43p	40p	74111	1-00p	95p
7430	15p	14p	7480	67p	64p	74118	1-00p	95p
7440	15p	14p	7481	97p	94p	74119	1-35p	1-25p
7441	67p	64p	7482	97p	94p	74121	67p	64p
7442	67p	64p	7483	1-10p	1-05p	74141	67p	64p
7446	97p	94p	7486	32p	30p	74145	1-50p	1-40p
7447	97p	94p	7490	67p	64p	74150	1-30p	1-70p
7448	97p	94p	7491	37p	34p			

* Devices may be mixed to qualify for Price Breaks
* 100 Plus less 10% off 25 plus break

Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47µF	6p	15µF	6p	47µF	6p
100µF	6p	33µF	6p	100µF	8p
220µF	6p	68µF	6p	150µF	9p
330µF	6p	150µF	7p	220µF	10p
1000µF	12p	220µF	8p	470µF	17p
4700µF	26p	680µF	15p	680µF	23p
		1000µF	15p	1000µF	23p
		1500µF	23p	2200µF	40p
		2000µF	39p		

6.3 VOLT		25 VOLT	
33µF	6p	10µF	6p
68µF	6p	22µF	6p
150µF	6p	47µF	6p
470µF	10p	100µF	7p
680µF	12p	150µF	7p
1000µF	16p	220µF	9p
2200µF	16p	470µF	12p
3300µF	24p	680µF	18p
		1000µF	20p
		2200µF	36p
		5000µF	62p

10 VOLT		40 VOLT	
22µF	6p	6-8µF	6p
47µF	6p	15µF	6p
100µF	6p	33µF	6p
220µF	7p		
330µF	9p		
470µF	9p		
1000µF	12p		
1500µF	23p		
2000µF	39p		

BARGAIN PACKS

Unmarked Packs

Pack of 25
1N4148
50p

Pack of 10
BC108
BC107
(Plastic can)
50p

Pack of 10
Plastic BC108
50p

Pack of 10
BC108
(unmarked)
but tested
50p

2N2946
(unmarked)
30p each

Pack of 10
2N2906
unbranded but
tested
50p

Unmarked but fully
tested
2N3056
30p

1-9
10 plus
2N3056
25p

FULLY MARKED TYPES

AD161, AD162
M/P
1-9
10 plus
54p
48p

BC107-BC108
BC109
1-9
10-99
100 plus
8p
7p
6p

BC 182L: 3-4-212-4
1-9
10 plus
8p
7p

AC127 or AC128
1-9
10 plus
100 plus
12p
11p
81p

ZENER DIODES

400 M/W 5%
Miniature
BZY 88 Range
All voltages
3-3-33 Volt
8p each

1 watt 5%
All voltages
6.8-200 Volts
12p each

10 watt 5%
All Voltages
7.5-100 Volts
45p each

Linear Integrated Circuits



301a	TO99	49p	723c	TO99	87p
301a	DIL	45p	723c	DIL	90p
701c		63p	741c	TO99	38p
702c		63p	741c	DIL	36p
709c	TO99	28p	741c	8 Pin DIL	34p
709c	DIL	31p	747c	DIL	42p
710c		53p	748c	TO99	38p
711c		58p	1437		1-10p
			1458		

Transistors

AC107	15p	BC138	24p	BF260	26p	OC44	13p
AC126	14p	BC142	30p	BF329	16p	OC45	13p
AC127	14p	BC143	30p	BF330	16p	OC70	21p
AC128	12p	BC144	28p	BF390	34p	OC71	13p
AC129	20p	BC145	24p	BF384	25p	OC72	13p
AC141K	18p	BC147	8p	BF385	25p	OC73	13p
AC176	14p	BC148	8p	BF386	22p	OC83	20p
AC187	12p	BC149	8p	BF387	25p	OC84	25p
AC187K	12p	BC153	15p	BF388	24p	TIP29A	48p
AC188	12p	BC154	16p	BFY50	19p	TIP30A	58p
AC188K	18p	BC157	12p	BFY51	15p	TIP31A	68p
ACY17	21p	BC158	11p	BFY85	15p	TIP32A	68p
ACY18	21p	BC159	12p	BFY64	35p	TIP33A	85p
ACY19	23p	BC167	11p	BFY90	65p	TIP34A	
ACY20	20p	BC168	10p	BNX20	17p		£1.40
ACY21	21p	BC169	10p	C407	20p	TIP35A	
ACY22	16p	BC177	14p	C426	30p		£2.30
ACY39	82p	BC179	14p	C428	28p	TIP36A	
AD140	36p	BC182L	8p	C450	15p		£2.90
AD142	40p	BC183L	8p	MP1811	32p	TIP41A	72p
AD143	35p	BC184L	8p	MP1812	42p	TIP42A	83p
AD149	34p	BC186	30p	MP1813	32p	2N706	12p
AD150	55p	BC212L	10p	MP1821	30p	2N930	21p
AD161	27p	BC213L	10p	MP1822	40p	2N1131	20p
AD162	27p	BC214L	10p	MP1823	45p	2N1132	25p
AD M/P	50p	BC258	8p	NKT211	25p	2N1613	20p
AF114	14p	BC259	8p	NKT212	25p	2N1711	24p
AF115	14p	BC267	12p	NKT214	25p	2N2904	36p
AF116	14p	BC268	13p	NKT217	85p	2N2904A	
AF117	14p	BC300	36p	NKT26	21p	2N2905	40p
AF118	82p	BC301	29p	NKT271	18p	2N2905	40p
AF124	24p	BC302	28p	NKT274	18p	2N2924	16p
AF139	36p	BC303	45p	NKT275	23p	2N2926	9p
AF239	37p	BC304	36p	NKT403	65p	2N3053	24p
AL100	68p	BCY70	15p	NKT405	79p	2N3054	50p
AL102	68p	BCY71	15p	NKY6031		2N3055	48p
AL103	49p	BCY72	15p	NKY736	60p	2N3056	40p
ASB26	27p	BD123	60p	NKT613G		2N3663	52p
ASB27	27p	BD130	45p			2N3702	8p
AU103	80p	BD131	82p	NKT674	24p	2N3703	8p
AU110	97p	BD132	81p	NKT677G		2N3704	8p
AU111	87p	BD133	38p			2N3705	8p
BC107	8p	BD136	44p	NKT713	29p	2N3706	8p
BC108	8p	BD141	£1.70	NKT773	25p	2N3707	8p
BC109	8p	BD142	45p	OC19	50p	2N3708	8p
BC113	14p	BF159	30p	OC20	50p	2N3709	8p
BC116	15p	BF173	26p	OC23	30p	2N3710	8p
BC125	15p	BF177	25p	OC25	25p	2N3711	8p
BC126	22p	BF178	26p	OC28	30p	2N3719	16p
BC132	14p	BF179	26p	OC29	30p	2N3874	25p
BC134	14p	BF194	14p	OC35	25p	40361	45p
BC135	14p	BF195	15p	OC36	35p	40362	45p
BC137	14p	BF244	25p	OC41	13p	40363	55p

MULLARD POLYESTER'S

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0-01µF, 0-015µF, 0-022µF, 3p, 0-33µF, 0-047µF, 0-068µF, 31p, 0-1µF, 4p, 0-15µF, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 8p, 0-68µF, 11p, 1-0µF, 13p, 1-5µF, 20p, 2-2µF, 24p

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 21p, 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3p, 0-047µF, 0-068µF, 0-1µF, 4p, 0-15µF, 6p, 0-22µF, 7p, 0-33µF, 11p, 0-47µF, 13p, 0-68µF, 15p, 1-0µF, 17p, 1-5µF, 20p, 2-2µF, 24p

MULLARD POLYESTER CAPACITORS C296 SERIES
160V: 0-01µF, 0-015µF, 0-022µF, 0-033µF, 0-047µF, 0-068µF, 3p, 0-1µF, 31p, 0-15µF, 41p, 0-22µF, 5p, 0-33µF, 6p, 0-47µF, 7p, 0-68µF, 11p, 1-0µF, 13p, 1-5µF, 20p, 2-2µF, 24p

VOLUME CONTROLS
Potentiometers
Carbon track 500 Ω to 2-2M Ω

SLIDE POTENTIOMETERS
58mm. TRACK
SINGLE GANGED, LOG or LIN 1k to 1M.
40p each

TWIN GANGED, LOG or LIN 1k to 500k.
60p each.

CARBON SKELETON PRESETS
Small high quality type (linear only).
All values 100-5 meg ohms.
-1 watt 5p each
-2.5 watt 6p each

VEROBORD
0-15 Matrix 0-1 Matrix
21in x 31in 17p 25p
21in x 5in 25p 25p
31in x 31in 25p 25p
31in x 5in 30p 29p
5in x 17in (plain) 83p

Vero Pins (bag of 36), 20p
Vero cutter, 45p; Pin insertion Tools (0-1 and 0-15 matrix) at 55p.

SLIDE SWITCH
SPST 10p each. D.P.D.T. 12p each.

MINIATURE NEON LAMPS
240V or 110V 1-4 5p, 5 plus 41p each.

MINITRON DIGITAL INDICATOR TYPE 3015F
Reads 0-9 and decimals
(Data Sheet on request)
Only £1-50

16 DIL Socket 80p
Driven by 7447 85p

RECTIFIERS

P.I.V. 1 AMP	1.5 AMP
60 1N4001 4p	PL4001 7p
100 1N4002 4p	PL4002 8p
200 1N4003 6p	PL4003 9p
400 1N4004 6p	PL4004 9p
600 1N4005 7p	PL4005 12p
800 1N4006 8p	PL4006 14p
1000 1N4007 8p	PL4007 18p

BRIDGE RECTIFIERS

P.I.V. 1 AMP	2 AMP	5 AMP	10 AMP
50 30p	45p	£1-60p	£2-00p
100 32p	52p		
200 34p	55p		
400 36p</			

BARGAIN PARCELS 14jb at £1.45 plus 32jp p.p.; 28lb at £2.75 plus 52jp p.p.; 56lb at £4.50 plus £1.25 p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 09J 4jn. dia. Length 15in. Also 7BP7. All unused as new. Price £1.40 post paid.

NEW HEAVY COAX CABLE dia. 1/4" 70 ohms approx. 50ft. lengths £1.40, p. & p. 30p. 100 ft. lengths £2.70, p. & p. 50p.

AERIALS. New Condition Whip Type, 4ft. 20p; 11ft. 75p. all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 62jp. p. & p. 25p.

CRYSTALS AS NEW. Hc 6u, 5,345; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,300; 2,295 Kc/s. 50p each plus 8p p.p.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2 1/2in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2 P. & P. 25p. minimum order of six.

ANY HEIGHT AERIAL TUBULAR SECTIONS 1/2" dia. x 3ft. long. Brass screw in ends, copper coated and painted. Good condition. 20p p. & p. 5p each. Minimum order 6.

AS NEW AERIAL TUNER UNIT No. 6 RF, consisting of 1 1/2 inch 500 micro/ampmeter 3 gang tuner 75 PF geared BNC type socket size 5 1/4" x 4 1/2" x 5". Price £1.50, p. & p. 25p.

HEADPHONES DI. High impedance. Good condition 75p. p. & p. 15p. R209. Set of valves 62jp. p. 25p.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 75ft. 40p. 90ft 47jp. 100ft. 55p. p. & p. 20p.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition. £1 each section. Carriage 35p each section. 1/2" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1 + 30p p.p.

AS NEW 500ua PENNY SIZE METERS complete with jack plug price £1 each, p. & p. 10p.

SLIDING RESISTORS, 12 amp, 1 ohm. Approx. 9in. long. 1.4 amp., 14 ohms. Approx. 7in. long. As new Ex Equip. 75p. p. 15p.

QUOTATIONS FOR QUANTITY.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY
WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.



ELECTRONIC ORGAN KITS

★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Precussion, Wah Wah, £406.00. ★ Console—2 x 5 octave keyboards and 32 note pedal board, 32 voices, Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, 3 Couplers, etc., at £572.55.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE, WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT AND ELECTRICAL HOUSEHOLD APPLIANCES.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

8, PUTNEY BRIDGE ROAD, LONDON, S.W.18
TEL: 01-870 4949



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME : _____
ADDRESS : _____
BLOCK CAPS please

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS 1R5, 185, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1.12. DAF96, DF96, DK96, DL96, 4 for £1.55.

1R5	28	30C17	76	EAF42	50	EM80	36	PCF808	68	U801	75
185	28	30C18	72	EB91	18	EM81	36	PCL82	80	UABC80	81
1T4	16	30P5	64	EBC33	40	EM84	38	PCL83	65	UAF42	60
384	28	30P11	66	EBC41	49	EM87	50	PCL84	88	UBC41	45
3V4	47	30P12	69	EBC81	80	EY51	36	PCL85	88	UBF80	84
5U4G	81	30P14	68	EBC90	82	EY86	89	PCL86	87	UBF89	83
6V4G	85	30L1	89	EBF80	38	EY87	89	PCL88	80	UCC84	88
6Y3GT	80	30L15	70	EBF83	89	EZ40	89	PCL800	89	UCC85	88
5Z4G	85	30L17	70	EBF89	89	EZ41	89	PCL805	88	UCF80	80
6/30L2	54	30P4	65	ECC81	17	EZ80	81	PEN A4	77	UCH42	88
6AM6	13	30P12	69	ECC82	20	EZ81	82	PEN30C	70	UCH81	80
6AQ6	28	30P19	65	ECC83	38	EZ90	85	PFL200	81	UCL82	89
6AT6	20	30P11	60	ECC85	24	GZ30	84	PL36	68	UCL83	88
6AU6	20	30P13	89	ECC804	64	GZ32	40	PL81	48	UF41	68
6LA6	20	30P14	80	ECP80	80	KT41	77	PL81A	47	UF89	80
6BE6	21	36L6GT	45	ECP82	28	KT61	65	PL82	81	UL41	68
6B6E	41	36W4	25	ECH35	55	KT66	78	PL83	88	UL84	88
6BW7	60	36Z4GT	25	ECH42	58	LN319	63	PL84	80	UM84	89
6F14	35	50C D96G	68	ECH81	29	LN329	80	PL900	63	UY41	89
6F23	68	80Y7	49	ECH83	38	LN339	66	PL904	68	VF88	25
6F25	50	AC/VF2	77	ECH84	38	N78	£1.05	PM84	30	VF4B	77
6J6GT	20	B349	70	ECL80	30	P61	40	PX25	95	W77	48
6J70	24	B729	64	ECL82	29	PABC80	81	PY32	52	Z77	28
6K70	18	CUH35	67	ECL86	35	PC86	47	PY33	52	Transistors	
6K8G	36	CY31	28	EP39	47	PF71	26	PF81	26	AC107	17
6Q7G	38	DAF91	82	EF41	67	PC98	42	PF82	25	AC127	87
68L7GT	38	DAF96	86	EF80	83	PC97	38	PF83	26	AD146	67
68N7GT	32	DF91	16	EF85	28	PC900	29	PF88	33	AF115	29
6V6G	28	DF96	36	EF86	30	PC824	29	PF800	81	AF116	29
6V6GT	28	DH77	20	EF89	36	PC825	28	PF801	81	AF117	29
6X4	22	DK32	33	EF91	18	PC828	83	PF819	80	AF125	17
6X6GT	28	DK91	28	EP92	27	PC829	43	R20	70	AF127	17
60P13	18	DK92	50	EP98	65	PC1189	48	U25	78	OC26	25
12AT7	17	DK96	45	EP183	27	PC805	70	U26	65	OC44	18
12AU7	20	DL35	40	EP184	29	PCF80	28	U47	73	OC45	18
12AX7	82	DL92	28	EP190	86	PCF82	33	U49	70	OC71	12
19B06G	75	DL94	47	EL33	65	PCF86	46	U62	81	OC72	12
20F2	67	DL96	38	EL34	64	PCF800	58	U78	84	OC75	12
20F3	76	DY86	24	EL84	23	PCF801	28	U193	81	OC81D	12
25L6GT	18	DY87	24	EL90	28	PCF802	39	U251	81	OC82	12
25U4GT	57	DY802	33	EL95	33	PCF805	72	U301	88	OC82D	12
30C1	28	EABC80	68	EL500	68	PCF806	58	U329	66	OC170	88


READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Minimum post/packing on 1 valve 7p., on each additional valve, (3p. per. valve extra)

Any parcel insured against damage in transit 3p extra.

SUPERSOUND 13 HI-FI MONO AMPLIFIER

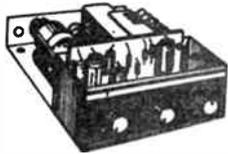

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohm. Frequency response 12Hz-30KHz ± 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble control. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. A.C. 200/240V.

PRICE £10.50. P. & P. 25p.

DE LUXE STEREO AMPLIFIER



A.C. mains 200-240 v. U & I n g heat sink duty fully isolated mains transformer with full wave rectifier & on giving a u a t e smoothing with negligible hum.

Valve line up:—2 x ECL86 Triode Pentodes, 1 x 6Z50 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £8.92 P. & P. 45p.

POWER SUPPLY UNIT 200/240v. A.C. Input. Four switched fully smoothed D.C. outputs giving 6v, and 7½v, and 9v, and 12v, at 1 amp continuous (1 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £4.50 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2" x 3" approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS 8" x 6" 5 for 50p P. and P. 13p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v, at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. PRICE £1.95 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri 200/240v. Sec. 9-0-9 at 500mA. 85p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.45. P. & P. 30p.

SPECIAL OFFER MAINS TRANSFORMER 200/240v. A.C. Input 35v at 1 1/2 amp A.C. output overall size 2 1/2" x 2 1/2" x 3" approx. Suitable drop through or vertical mounting 90p. P. & P. 30p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100µA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 75p. P. & P. 10p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U., Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 88p. P. & P. 13p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

VAT. Prices in this advertisement (incl. p. and p.) will be subject to VAT as from 1st April, 1973.

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing.
LATEST B.S.E. C109/C129 4-SPEED AUTOCHANGER.
With latest mono compatible cartridge £6.97 Carr. 50p.
With stereo cartridge £7.97 Carr. 50p.
GARRARD SP25 Mk III with heavy precision machined die cast turntable £10.85, carr. 50p.

SPECIAL BARGAIN OFFER!

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take (Garrard 1025, 2000, 2025TC, 2500, 3000, 3000, 5100, SP25 II and III, BL68H, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover).
NOW ONLY £4.50, P. & P. 35p.

LATEST ACOS GP91/13C mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1.50 P. & P. 8p.

SOMOTONE STACH COMPATIBLE STEREO CARTRIDGE
T/O stylus Diamond Stereo LP and Sapphire 78.
ONLY £2.50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £1.63 P. & P. 10p.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing 3 1/2" LP/78 mono or stereo records on mono equipment. Only £1.50 P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £3.95 P. & P. 40p
ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £5.25 P. & P. 30p.

DELUXE QUALITY PORTABLE R/P CABINET MK II.
Usest motor board size 1 1/2" x 12in. clearance 2in. below, 5in. above. Will take any amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE £4.75, P. & P. 50p.

SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2" high x 10 1/2" wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohm impedance.

OUR PRICE £8.40 Carr. 65p
Cabinet Available Separately £4.50 Carr 60p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8.50 Carr. 65p

LOUDSPEAKER BARGAINS

5in. 3 ohm £1.05, P. & P. 15p. 7x4in. 3 ohm £1.15, P. & P. 20p. 10 x 6in. 3 or 15 ohm £1.90, P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.62, P. & P. 20p. E.M.I. 13 1/2" x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3.20, P. & P. 30p. H.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network £4.20, P. & P. 30p.

BRAND NEW 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with High flux ceramic ferrobar magnet assembly £6.75. Guitar models: 25w. £6.75, 35w. £8.50, P. & P. 38p



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS

With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £2.75, P. & P. 25p.

12in. "RA" TWIN (ONE LOUDSPEAKER, 10 watts peak handling, 3, 8 or 15 ohm) £2.40, P. & P. 30p. 35 ohm SPEAKERS 3in. only 65p P. & P. 15p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2" x 1 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40V peak). Impedance 8 ohm only. Frequency response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £5.95 each. P. & P. 25p.

VYNAIR & REKINE SPEAKERS & CABINET FABRICS
app. 54 in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p per yd (min 1 yd). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable sixfoam ear-muffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £2.95, P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES.
OUR PRICE £1.05, P. & P. 8p

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design. All parts supplied including drilled metal work, high quality ready drilled fibre glass printed circuit board, with smart brushed anodised aluminium front panel with matching knob, wire, solder, nuts, bolts—no extra to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: ±3dB 12-20,000 Hz. Sensitivity: better than 80mV into 1mΩ. Full power bandwidth: ±3dB 12-15,000 Hz. Bass boost approx. to +12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 15p plus large S.A.E.

AMPLIFIER KIT £10.50 P. & P. 15p
(Magnetic input components 30p extra)
POWER PACK KIT £3.00 P. & P. 30p
CABINET £3.00 P. & P. 30p

(Post Free if all units purchased at same time)
Full after sales service

Also available ready built and tested £21.00. Post Free.
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi Fi Discosque etc., etc.



3-VALVE AUDIO AMPLIFIER H434 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.95. P. & P. 35p.


HSL "FOUR" AMPLIFIER KIT. Similar in appearance to H434 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4.10. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.
P. & P. 35p BARGAIN PRICE £2.95

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up: 2 EL84s, ECC83, E280 in push-pull. Simple instruction booklet 13p (free with parts). All parts sold separately. ONLY £7.97 P. & P. 55p. Also available ready built and tested £10.97 P. & P. 60p.

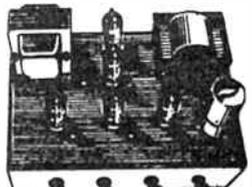

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Sinclair Project 60

Now—the Z.50 Mk.2

with built-in automatic transient overload protection

When originally introduced, the Sinclair Z 50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z 50 Mk 2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z 50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50. Circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual
£5.48

Z.30 the power amplifier for quality and economy




with free manual
£4.48

The Z 30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z 50's. Using a power supply of 35 volts, Z 30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/8 x 2 1/8 x 1/2). Z 30, Z 50 and Z 50 MK 2 modules are compatible and interchangeable.

Brilliant new technical specifications

Input impedance 100 K Ω
Input (for 30w into 8 Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8 Ω . See curve
Frequency response 10Hz to more than 200 KHz \pm 1dB
Max. supply voltage 45v (4 Ω to 8 Ω speakers) (50v 15 Ω speakers only)
Min. supply voltage 9v
Load impedance – minimum: 4 Ω at 45v HT
Load impedance – maximum: safe on open circuit

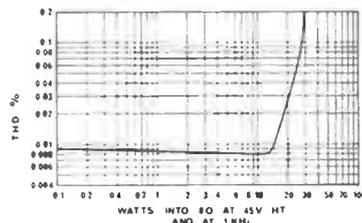

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave deluxe stereo amplifier (60W RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail, Air Mail is charged at cost.

sinclair

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit



Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio—up to 3mV, Mag pu 3mV correct to RIAA curve ± 1 dB 20 to 25 000 Hz. Ceram—p.u.—up to 3mV. Aux—up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE—12 to -12 dB at 10KHz. BASS—12 to -12 dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed **£9.98**

Project 60 Stereo F.M. Tuner



The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 1μ V for lock in over full deviation. **Squelch level:** Typically 20 μ V. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10Hz—15KHz (± 1 dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25—30VDC. **Indicators:** Stereo on, tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to both constructors with the IC 10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC 12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC, make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak) 6—8 Ω . **Frequency Response:** 5Hz to 100KHz ± 1 dB. **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 40dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 = 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

£2.98 Post free

Power Supply Units

The new PZ.8 Mk.3



The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage—45.

PZ.8 Mk.3—£7.98

(Mains transformer, if required) £5.98

PZ.5 30v un stabilised

(not suitable for Project 60 tuner) £4.98

PZ.6 35v stabilised

(not suitable for IC 12) £7.98

Project 605



the easy way to buy and build Project 60 without soldering

Project 605 in one pack contains one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free

£29.95

All you need for a superb 30 watt high fidelity stereo amplifier

Order form

Please send

I enclose cash/cheque/money order.

Name _____

Address _____

PW4

SINCLAIR RADIONICS, Business Reg. No. 699483;
 London Rd, St. Ives, Hunts, PE17 4HJ

sinclair

1145

Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Service Sheets

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 2906G.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 40p each

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to (Uncrossed P.O.'s please, original returned if service sheets not available.)

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

Aerials

Direct from the Manufacturers
U.H.F. AERIALS
EASY ASSEMBLY KITS
10 Element **SAVE 40%**
£1.25 on normal retail price
14 Element **£1.50** 18 Element **£1.75**
Most Clamps optional extra
Ready assembled add 20p allow 32" p. carriage and packing
Please state which elements or group
APEX AERIALS (P.W.)
ALBAN WORKS, MARY ST. JOHNSTONE, RENFREWSHIRE



BAINES for High Frequency Aerials

UHF Multibeams by J. Beam
MBM 10 £2.20 MBM 18 £2.90 MBM 30 £3.90
MBM 46 £8.00 MBM 70 £11.00
VHF FM Aerials
Dipole £1.40, FM/H £2.00, FM3 £3.00, FM4S £5.55, FM6S £7.80
Masthead Pre-amps
Single Stage £6.00, Two stage £8.00, Wideband £7.00
Accessories: SAE for full list. Co-ax 5p, low loss 9p
11 Dale Cres., Tupton, Chesterfield S42 6DR

DIRECT FROM MANUFACTURER—a comprehensive catalogue of UHF & VHF/FM aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send 3p stamp to CLAYDEW ENTERPRISES (PW), 261 Hardess Street, London, S.E.24.

Wanted

TOP PRICES PAID for NEW VALVES popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

For Sale

BBC 2 TV'S 7.50 Including Delivery

Thorn 850 Chassis with UHF Tuner. Ex-rental sets sold complete but un-serviced, with repolished cabinets. Rush £7.50. Cash with Order.

U.H.F. TUNERS

For Ferguson 850. 900 Chassis, but adaptable for most D/STD Chassis. £2.50 each. Plus 50p P&P. C.W.O.

Send S.A.E. for list of TVs, Tubes, Valves, etc. Allow 10-14 days delivery.

TRADE DISPOSALS (PW)

Midlands & North: 1043 Leeds Road, Bradford 3.

Scotland: Unit 5, Peacock Cross Industrial Estate, Burnbank Road, Hamilton.

Cornwall: Pencoys, Four Lanes, Redruth.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

MORSE MADE EASY!!

FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed!

Beginner's Section only £3.30. Complete Course £4.50 (Overseas £1.00 extra) details only, 4p stamp. 01-860 2896
GBSBC (Box 19), 45 GREEN LANE, PURLEY, SURREY

35! CRYSTAL SET Kits, plans. D. Sanders, 59 Sweetpool Lane, Hagley, Worcs. DY8 2XA.

Ladders

LADDERS, 20ft, £7.80; 24½ft £9.80. Carr. 80p. Leaflet. (Dept. WLS) Home Sales Ladder Centre, Baldwin Road, Stourport, Worcs. Tel. 029-93 5222.

Books and Publications

DENCO CLACTON LIMITED

355-7-9 Old Road
Clacton-on-Sea, Essex

Catalogue 20p post paid
S.A.E. all enquiries

WORLD RADIO TV HANDBOOK

(1973 edition) £2.90. Fortnightly World Radio Bulletin (ask for free copy) £3.13. How to Listen to the World. £2.00. SWL Address Book, stations' QSL policies, etc.. £1.60. Confidential Frequency List—Forces, Air, Spy, etc.. £1.80. Shortwave Voices of the World. £1.80. Guide to Broadcasting Stations. 60p.

Prices include First Class postage.

DAVID MCGARVA (PW)
Box 114, Edinburgh. EH1 1HP
Giro a/c 17 412 0001

DIGITAL COMPUTER LOGIC and Electronics. Four volume self-instructional course. £2.95 including p & p. Money back assurance. Cambridge Learning (PW), 8a Rose Crescent, Cambridge.

★ SERVICE SHEETS • MANUALS • BOOKS ★

SERVICE SHEETS OVER 12,000 SERVICE SHEETS AND MANUALS IN STOCK ON RADIOS, TV'S, R.PLAYERS AND T.RECORDERS, ETC... **SERVICE SHEET** 30p + Postage PLEASE ENCLOSE S.A.E. WITH ENQUIRIES... **Catalogue 20p.**

New Books and Publications

	PRICE
Colour Television Servicing by G.J.King 328 pages. A complete servicing guide.....	£4.40
Mazda Book of Pal Receiver Servicing by D.J.Seal 288 pages. Includes fault symptoms	£3.80
Television Servicing Handbook by G.J.King 358 pages A sound introduction to servicing	£3.80
Understanding Television by J.R.Davies 405/625/Colour Edition, 512 pages.....	£2.10
Foundations Of Wireless And Electronics by M.G.Scroggie, 8th Edition, 552 pages....	£3.00
Beginner's Guide To Radio by G.J.King 7th Edition, 204 pages. A must for newcomers.	£1.00
Beginner's Guide To Television by G.J.King 5th Edition, 211 pages. Illustrated.....	£1.60
Colour Television Theory by G.H.Hulson 334 pages. PAL-System principles/circuitry..	£3.85
Electronics in Music by F.C.Judd 169 pages. Circuit designs for the enthusiast.....	£3.15
Model Radio Control by P.Newell 134 pages. Theory and Practice, 100 Illustrations....	£2.25
T.V.Fault Finding Book by Data Publications Ltd. 405/625 Edition, 124 pages.....	£0.50

Note. Postage on all books is now 5p in the £1. Orders over £5.00 post FREE (UK only).

Send S.A.E. for Free LISTS of Practical and Technical Books on Radio & Television now available to

BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorks. Tel. 0423-86844 ★



THE PICTURE BOOK METHOD OF LEARNING

BASIC ELECTRICITY 5pts £4-50. BASIC ELECTRONICS 6pts £5-40. BASIC TELEVISION 3pts £3-60

(Postage and Packing included)

The Pictorial Approach Manuals assure the quickest and soundest method of gaining mastery over these subjects. The clear and concise illustrations make study a real pleasure. Your money refunded if not completely satisfied is your 100% Guarantee. Free Illustrated Prospectus on request.

Send now to **SELRAY BOOK CO., 60 HAYES HILL, BROMLEY BR2 7HP**

Radio BOOKS

- Handbk of Transistor Equiv and Substitutes 47p
- Handbook of Tested Transistor Circuits 47p
- Red & Electr Colour Codes and Data Chart 20p
- Hi Fi, PA & Disco Amplifier Design H'bk 82p
- Boys Bk of Crystal Sets and Simple Circuits 23p
- How to make FM & TV Aerials, Bands 1,2,3 23p
- Radio Servicing for Amateurs 25p
- High Fidelity Loudspeaker Enclosures 47p
- Practical Tape Recording Handbook 36p
- Practical Stereo Handbook 36p
- Practical Radio Inside Out 47p
- Transistor Circuits Manual No.1 20p
- Transistor Circuits Manual No.2 20p
- Coil Design and Construction Manual 36p
- Radio TV and Electronics Data Book 30p
- Trans Circuits for Radio Controlled Models 47p
- Pract Transistor Audio Amplifiers, Book 1 25p
- Transistor Test Equip and Servicing Manual 30p
- Handbook of Simple Transistor Circuits 42p
- Modern Transistor Circuits for Beginners 47p
- Sound and Loudspeaker Manual 57p
- Resistor Colour Code Disc Calculator 15p
- Manual Transistor Audio Amplifiers 47p
- Practical Car Radio Handbook 36p
- Radio TV and Industrial Tube & Valve Equiv 47p
- Practical Transistor Novelty Circuits 47p

(All prices include Postage & Packing)

FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

TRANSISTOR DATA THE INTERNATIONAL TRANSISTOR DATA MANUAL

1973 EDITION is now ready. Data on upwards of 18,000 transistors of international origin. £5-25 plus 35p post & packing in the UK. Brochure available. Order direct from

SEMICON INDEX LTD.

Freeport, Wokingham, Berks. RG11 2AY.

Educational

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV & Electronics. Expert tuition for C & G (Telecoms Techn's Cert and Radio Amateurs') RTEB, etc. Many non-exam courses including Colour TV Servicing, Numerical Control and Computers. Also self-build kit courses—valve and transistor. Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 732EI INTERTEXT HOUSE,
STEWARTS RD., LONDON, SW8 4UJ

RADIO, TV, RTEB Certs., City and Guilds, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Details of home study courses and illustrated book—FREE. BIET (Dept ZL BPW 25). Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

CIE, AMSE, City & Guilds, etc. Thousands of exam successes. Postal courses in all branches of Engineering. Prospectus FREE. State subject of interest: BIET (Dept ZL BPW 36). Aldermaston Court, Reading RG7 4PF. Accredited by CACC.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Situations Vacant

MEN!
£50 p.w.
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a.

After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators
Training Centre

M96, Oxford House

9-15, Oxford Street, W.1.
Telephone: 01-734 2874

127, The Piazza, Dept. M96,
Piccadilly Plaza, Manchester 1.
Telephone: 061-236 2935

IF YOU CONSIDER yourself good at radio/electronics as a hobby, why not try it as a job? We are looking for enthusiasts to be trained in the servicing of magnetic recording dictation equipment and allied control systems. Mainly in the Central London area but some scope in other parts of the country. Previous experience with dictation equipment not essential. We offer permanent salaried positions with a well-known company in a rapidly expanding industry. Write, in confidence, and tell me why you can do this job. Chief Engineer, Assmann Dictating Systems Ltd., Stockwell House, Hinckley, Leicestershire LE10 1HW.

Receivers and Components

ADD VAT AT THE STANDARD RATE
AFTER APRIL 1st

MICROCIRCUITS: 709 28p; 710 38p; 723 57p; 741 28p; 748 37p; PA230 70p; NL702C 50p; FET Op Amp 24-28.
TRANSISTORS: 2N696 14p; 2N697 14p; 2N704A 11p; 2N1613 16p; 2N1711 16p; 2N2218 19p; 2N219 19p; 2N219A 19p; 2N2904 17p; 2N2924 RED 6p; DIANICE 7p; YELLOW 8p; GREEN 9p; 2N3033 15p; 2N3034 40p; 2N3065 35p; 2N3702 10p; 2N3703 10p; 2N3704 10p; 2N3705 9p; 2N3706 9p; 2N3709 9p; 2N3710 9p; 2N3711 9p; 2N3405A 12p; 2N3409 9p; 2N4091 11p; 2N4062 11p; 2N5175 10p; 2N5550 39p; AC107 25p; AC129 12p; AC129 12p; AC174 15p; ACY17 23p; ACY21 17p; AF114 14p; AF115 14p; AF116 14p; AF117 14p; AF124 22p; BC107A 5p; BC107B 7p; BC108A 5p; BC108B 7p; BC109C 7p; BC109B 6p; BC109C 7p; BC120 14p; BC147A 9p; BC147A 10p; BC164B 9p; BC169B 10p; BC177 13p; BC178 12p; BC179 18p; BC179 15p; BC171 22p; 4004 5p; 8004 6p; 1000V 7p; BF184 13p; BFN29 24p; KUN84 20p; BFN59 15p; BFN87 24p; BFN88 19p; BN550 15p; BFN51 15p; BFN52 15p; BLY47A 40p; BSN20 12p; OC45 12p; OC45 12p; OC71 12p; OC72 12p; OC81 18p; OC83 24p; ME SERIES AVAILABLE. RECTIFIERS: 1 AMP-50V 31p; 100V 4p; 200V 4p; 400V 5p; 800V 6p; 1000V 7p; 2 AMP-400V 12p. DIENERS BZ88S SERIES-27V to 33V 8p each. DIODES IN916 4p; OA80 6p; OA290 7p; OA292 8p. SCR IR122D (400V 5A) £1-14; BTX30-600 75p. LED PANEL LAMP with BUSH and DATA 40p. SOLDERCON DLY IC PIN SOCKETS 1p per PIN. IC SOCKETS 11 or LD: 14 pin 12p; 16 pin 13p; CARBOX FILM IV5%, RESISTORS E12 VAL C28 22 to 2.2M 1p EACH or 7p PER 10 of ONE VALUE. DALO ETCH RESIST FILLED FIBRE TIP PEN 80p. MINIATURE METAL GLAZE RESISTORS 1/16W 5% 41p each. ITT POCKET MULTIMETER 27 ranges £17

JEF ELECTRONICS (P.W.4)

York House, 12 York Drive, Grappenhall, Warrington.

WA4 2EJ

Mail Order Only. C.W.O. P. & P. 9p per order. Price List free.

Satisfaction of your money back.

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V, 1, 2-2, 4-7, 10mfd.—312p. 22, 47-4p (50V, 5p) 100-5p (50V-6p). Subminiature bead-type tantalums 0-1/35V, 0-22/35V, 0-47/35V, 1/35V, 2-2/35V, 4-7/35V, 10/16V-9p. Mylar Film 100V, 0-001, 0-002, 0-005, 0-01, 0-02-2p, 0-04, 0-05-2p, 0-068, 0-1-3p. Polystyrene 63V, E12 series 10pf-10,000pf-2p. Miniature High-stab resistors E12 series 5% 1/2W Carbon Film 10-10M! (10% over 1M) and 1W Metal Film 271-10M! 8 for 5p, Insured Postage 8p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

TV LINE OUTPUT TRANSFORMERS Tidman Mail Order Ltd., 256 Sandycombe Rd., Richmond, Surrey, TW9 2EQ. 01-948 3702.

ELEVEN BAND RADIO. SW1-4 (4-30 MHz). Marine, LW, MW, FM, PB (76-86). Aircraft (108-136). PB (148-174). Battery/Mains. BFO. AGC. Squelch Control. Output: 1-3W. 15in x 10in x 5in, £66. Eight Band Model, with BFO, £42. Four Band, MW, FM, Aircraft. PB. E15. SAE. Full Lists. Langtons Radio, High Street, ROCESTER, Staffordshire, Tel. 388.

TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commencing April 16th. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. A/4, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**



Trampus electronics

All Brand New. Money Back if dissatisfied. Fast Service. **5V DIGITAL INDICATOR** O-91P, with socket and red Filter £1.39. 7447 £1.39 **IC GAS DETECTOR**. Smoke, Butane, Vapour, etc. £1.99. data pp. **ULTRASONIC TRANS-DUCER**. Transmits or receives. **£2 LIGHT EMIT DIODES**. Visible red panel clip/data, 86p **INFRA RED** (invisible beam), £1.19 **DIGITAL CLOCK** integrated circuit, 28 pin DIL, 12/24 hr. 4/8 digit. £1.50. data 15p. P.C.B. £1.29 **COMPLETE KIT** with Plastic Case £21. **NEW IC RADIO ZN414** £1.19. **PW TEXAN KIT** less chassis £21.49. PAKS: Ic/semi-conductor £2.49. Capa £2.49 Res £1. Transformer £2.67. TIP 41/42 pair £1.50. 741/744 86p ea.



INTEGRATED CIRCUITS with data. 741 Op amp DIL 89p. 709 TOS 21p. DIL 29p. 710 32p. 748 33p. **PHOTO DETECTOR/amp** 44p. **VOLTAGE REGULATOR**: 1/4 amp 5 or 12 V type £1.67. 723 56p. 555 **TIME/stab oscillator** 89p. **AUDIO AMP** 3.5W Hi-Fi etc. £1.24. Stereo: Dual Pre-amp £1.49. MPX Decoder for any FM RX £2.69. 74N: Data Booklet 12p. gates 7400 etc. 15p. 7400 56p. 7470/2 22p. 7475 59p. 7493 79p. 7413 29p. **DIL SOCKETS** low profile 14 or 16 pin. for 74N. 12p. **SEMICONDUCTORS** 2N3055, 89p. BC107, 7p. BC108, 7p. BC109, 8p. AC125/6/7/8, AC127/8, AC167/8, AF117, 16p. AD161/2, 35p. IC167/8/9, 17p. BC177/8/9, 15p. BC182/3/4, 11p. BC212/3/4, 12p. BC270, 16p. BF560/51/52, 17p. T1842 V.T. 29p. 2N706A, 12p. FE2 2N3819, 23p. 2N2926 O. Y., 8p. 2N3033, 17p. 2N3702/3/4/5/6/7, 11p. 2N3708/9/10/11, 9p. 1A RECTS: 60V 3p. 400V 8p. 50V Bridge 23p. 1N914/6 3p. OA1/191 7p. OA200/202 10p. ZENERS: BZ788 400mW 10p. 5V/10V 29p. MINI SCR 4A/400V 55p. TRIAC 6A/400V 87p. **CAPACITORS**: 45/50V electrolytic. 10/50/100µF, 8p. 200/500µF, 8p. 1.000µF, 16p. DISC: 22pF thro' to 0.047µF, 8p. 0.01 to 0, 6p. RESISTORS 1/4W 5%, 1p. PRESETS 0.25W, 6p. VERO 16p/23p, etc. DIN plugs, 13p. sockets, 8p. **A.M. MEDIUM WAVE RADIO KIT** £2.99. **ELECTRONIC PW CAR IGNITION KIT** £6.67. **FREE CATALOGUE** S.A.E. Data 3ht. 6p. ca. C.W.O. P & P 7p. Overseas 35p. Discount 10 + 10%. P.O. BOX 29, BRACKNELL, BERKS.

CASED AMPLIFIERS

2x ECC83, EL84, EZ80, 20µV 1/p sensitivity 2 watts O/P into 7 x 4" 3Ω Speaker. All contained in polished cabinet with non-standard single motor deck. Tested with circuit £3 (£1).

COMPUTER PANELS

Lots of Transistors inc. Power Types, Diodes, R's, C's, Pot Cores, etc. Some boards broken, but good value at 31bs. £1 (25p), 71bs. £2 (40p).

60p COMPONENT PACKS

RESISTORS: 350 carbon 60p (15p); 200 5% Hi-stab. 60p (15p); 100 1% and 2% 60p (8p). CAPACITORS: 150 Mica, Poly, Ceramic 60p (8p); 75 Electrolytic 60p (15p); 150 Paper, Foil, Polyester 60p (15p). Any 5 packs £2.50 (25p).

FERRIC CHLORIDE

Anhydrous Technical Quality in sealed 1lb packs 40p (15p), 10lbs £3.50 (50p).

COMPONENTS: BC107-N.9, 8p ea., 14 for £1; 709C 25p; 741C 25p; 723C 40p; 2N3055 35p; 1N4001 7p; 1N4006 11p; Crofon 1610 Light Guide, 64 Filament £1 per metre, 5- 80p, 10- 70p. **8-TRIPLES CAPACITORS MPD/V**: 0.47/350 8p; 2/150 2p; 8/350 8p; 8/450 10p; 25/25 5p; 800/50 12p; 550/6 3p; 1000 + 500/18 12p—Lots of others. Lots of Odd Units, Sockets, Mergers, Avo's, Sig. Gen's etc. at shop for callers. SAE List. Post in brackets, small parts 3p.

GREENWELD (PW11)

24 Goodhart Way, West Wickham, Kent. Tel: 01-777 2001. Shop at 21 Deptford Broadway, S.E.8. Tel: 01-692 2009.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 incl. postage C.W.O. to Caledonian Components, Fosterton Firs, Strathore Road, Thornton, Fife.

RECEIVERS and accessories. B40/62B fine-tuning, S-meter and product detector kits and information, SAE details. P. R. Golledge, G3EDW, Glen Tor, Torrington, Devon. Tel: 08-052 2411.

THE

TEXAN

NOW ON DEMONSTRATION



Designer approved Kit only £28.50
Instructions only 35p

- Pack 1. RESISTORS 80p
- Pack 2. SMALL CAPS £1.50
- Pack 3. LARGE CAPS £1.40
- Pack 4. SUNDRIES £1.90
- Pack 5. SWITCHES 90p
- Pack 6. CONTROLS £1.45
- Pack 7. SEMI COND. £8.25
- Pack 8. TRANSFORMER £4.95
- Pack 9. P.C. BOARD £2.00
- Pack 10. CHASSIS, etc. £2.75

Post extra—parts available separately
Send list full and technical spec.

Kits also available for

- ★ Radio Control Systems
- ★ Digital Clock Systems
- ★ Integrated Circuit Amplifiers (to 50W)
- ★ Hi-Fi Pre-amps
- ★ Stabilized Power Supply Units

TELERRADIO HI FI, 325 Fore Street,
Edmonton, London N.9 01-807 3719
CLOSED ALL DAY THURSDAY

5-N-CHANNEL FETs 3819E-£1

Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc.
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LIMITED

45 Station Road, Gerrards Cross, Bucks.
Mail Order only

VALVE BARGAINS any 5—Give Free ECC82 EF183-EF184. PCF80. PCL82 PY800. PL36. When buy TVS. 19in. U.H.F./V.H.F. TV £6.50 carriage £1.50. Slotmeters. Perfect working £1.50. Post Free. MIR Radio & TV, 193 Ram-say St., Rochdale, Lancs. Tel. 40599.

NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in Jack socket for use with earphones or amplifier.

Only £3.50 + p. & p. 10p U.K. only.
Illustrated catalogue of selected kits and components. 15p P&P free.

Galleon Trading Co.,
12, Burma Way,
Corringham,
Stanford-Le-Hope,
Essex. SS17 9DE

13A SCOPE. Handbook with Circuit Diagram — £2.00. Complete range spares, probes, transformers, chokes, potentiometers, graticules, etc. Cheap. SAE or phone. CT.316 Scope. Handbook with Circuit Diagram — £2. **SPEAKERS**, 12 Kenley Avenue, Shrewsbury. Tel. 56949.

PRECISION

POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.
0.47µF: ±5% 80p; ±2% 40p; ±1% 60p
1.0µF: ±5% 40p; ±2% 80p; ±1% 60p
2.2µF: ±5% 80p; ±2% 60p; ±1% 75p
4.7µF: ±5% 70p; ±2% 80p; ±1% 211b
6.0µF: ±5% 85p; ±2% 211b; ±1% 211b
10µF: ±5% 211b; ±2% 211b; ±1% 211b
15µF: ±5% 211b; ±2% 211b; ±1% 211b

TANTALUM BEAD CAPACITORS—Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 100µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 15µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (78 capacitors) £5.

NEW!—TRANSISTORS. BC107, BC108, BC109, All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178—42p each; 3 for £1.

POPULAR DIODES IN914—7p each, 8 for 50p; 18 for £1. IN916—9p each, 6 for 50p, 14 for £1. IS44—5p each, 11 for 50p, 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. = 5% at 5 mA. All new and marked. Price 10p each, 6 for 50p, 14 for £1.00. Special offer 6 off each voltage (66 zeners) £4.50.

RESISTORS. Carbon film 1/4W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decads. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

400V A.C. CAPACITORS. 0.1µF, size 1 1/2in x 1in, 25p; 0.25µF, size 1 1/2in x 1in, 30p; 0.47 and 0.5µF, size 1 1/2in x 1in, 35p; 1.0µF, size 2in x 1in, 45p; 2.0µF, size 2in x 1in, 75p each.

SILICON PLASTIC RECTIFIERS 1.5 Amp Brand new wire-ended DC27, 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5.
ARCO TRADING (formerly V. Attwood)
Dept. E.1, P.O. Box 8, ALRESFORD, Hants.

COMPONENTS—Integrated Circuits, Digital Displays, Diodes, Resistors, Capacitors, Switches. List 3p. Cavern Electronics, 29 Clarefield Road, Leicester LE5 6FB.

TAPE-HEAD reconditioning service. Guaranteed satisfaction. Send worn head with £2 to: Sara Electronics, Fawkham Avenue, Longfield, Kent.

TRANSISTORS: mint, branded top grade AD161/162 c.pr: 60p; BC107B, 12p; BC169C, 10p; 2N2926G, 12p; 2N3702, 10p; 2N3704, 10p; DIODES: OA90, 6p; 1N4002, 5p. Mail order only, U.K. postage 5p. **AMATRONIX LTD.**, 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

VISIT AUTO TRACTION. Thousands of bargains in surplus radio equipment. Meters, motors, relays, TR/TX, telephone equipment, aircraft equipment. SAE enquiries, 27A, Arragon Road, Twickenham, Middx. 892 9489.

World-wide acclaim. the incomparable

GLOBE-KING

Precision standard, inexpensive, low-cost valve and transistor Kits for Short-Wave 10-350 m. V.H.F. 80-180 M/cs. Ideal for beginners with unique "Easy-Build" diagrams and simplified instructions. Send to-day for free literature price list and order form, kindly enclose stamped addressed envelope (Overseas: Int. Reply Coupon). Direct to the sole manufacturers:

JOHNSONS (RADIO)
SHAW ST., WORCESTER.
WR1 3QQ

Please note new address, city centre.
Pioneers in DX radio—Established for over 30 years.

NEW RECEIVER MODULE RM-A

A small circuit board, wired, tested and aligned and requiring only addition of tuning capacitor, coils and controls (not included) to make a complete AM CW SSB superhet RX for up to 30 MHz. Headphone output. Runs off 6V to 15V. P.P. suitable. Contains RCA IC (equiv. 14 transistors) plus BFO. FET local use and 2 double-tuned IFT's at 465 kHz. Full instructions and colour coded leads make connexion simple, even for beginners. £7.85 post paid.

Provides good stable reception of DX on CW SSB or can be used with HF or VHF converters as double superhet. Suitable add-on RF and Audio Amp modules also available from £2. SAE details.

P. H. COLLEGE G3EDW

Glen Tor, Torrington, Devon.

Tel: 08-957 2411

Miscellaneous

QUALITY 1/2 Track R/P Heads, mounted in Mumetal Case, 55p each. 117 Horton Road, Brighton, BN1. 7EG.

Darned Electronic Wizardry

by Dewtron

Famous kits, e.g. waa-waa complete kit £2.95; Fuzz kit £4.75, auto rhythm modules P & P 20p min. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 251 Ringwood Road, Ferndown, Dorset.

TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or

Any 25 transistors for only £1-90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee, P. & P. 10p.

J. M. KING (H)

17 Buckridge, Portpool Lane, London, E.C.1

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd. Stratford-on-Avon, Warwks.

MANUFACTURER'S SURPLUS RECORD PLAYER Cabinets with motor board £3.00. Radio Cabinets make ideal speaker cabinets 13in x 7in x 5in 50p, AM/FM gang condensers with S/M drive 25p. UHF/IF Transformers, set including sound discriminator, 75p with data. F/M Tuner with valve £1-50. All items new includes P. & P. ARCHER, 9 Pine Grove, Maidstone, Kent.

BUILD IT in a DEWBOX quality cabinet. 2in x 2 1/2in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.


RECORD T.V. SOUND

using our loudspeaker isolating transformer. Provides safe connection for recorders. Hi-Fi equipment or extension speakers.

£1 post free. Instructions included.

Crowborough Electronics (PW)
Fridge Road, Crowborough, Sussex.

4-STATION INTERCOM

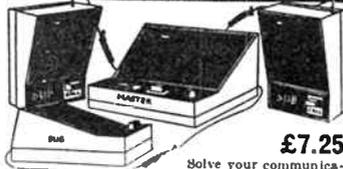

£7.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 9 connecting wires each 6ft. and other accessories. P. & P. £0-40.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price £14-40 P. & P. £0-25.

INTERCOM/BABY ALARM



OUR PRICE ONLY £3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft. connecting wire. Battery 14p. P. & P. £0-25.



£2.99

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Battery 14p extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.4)
169 KENNINGTON HIGH STREET, LONDON, W.8.

AERIAL BOOSTERS

We make four types of Aerial Boosters. L45 £2 5 UHF, L12 VHF 405, L11 VHF Radio L10 M/W & S/W. Price L45, L12 & L11 £2.95, L10 £2-45.

VALVE BARGAINS

Any 5—45p. 10 70p:
ECC82, ECL80, EF80, EF85, EF183, EF184, EBF89, EB91, EY86, PCC84, PCC89, PC97, PCF80, PCF86, PCL82, PCL83, PCL84, PCL85, PL36, PY33, PY82, PY800, PY801, 30L15, 30C15, 30C12.

19" UHF/VHF TV £7-50 THORN 850 SERIES

Untested but with complete set of spare valves. Price £7-50. Carriage £1-50.

100 MIXED RESISTORS 60p

From 1/2 watt to 2 watt and from 10-ohms to 10m-ohms our choice.

100 MIXED CAPACITORS £1

From 220PF to 200MFD and from 12v.w to 500v.w—our choice.

POST & PACKING under £15p. Over £1-10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

VELCO ELECTRONICS

62B Bridge Street, Ramsbottom, Bury, Lancs.



LOUDSPEAKER BARGAINS

Fane Pop 100 Watt 18" 8/15 ohm	£19-50
Fane Pop 60 Watt 15" 8/15 ohm	£11-15
Fane Pop 50 Watt 12" 8/15 ohm	£9-25
Fane Pop 25/12" 25 watts 8/15 ohm	£5-40
Fane Pop 15 12" 10 watts 8/15 ohm	£4-00
Baker Group 25 12" 3, 8 or 15 ohm	£6-60
Baker Group 35 12" 3, 8 or 15 ohm	£8-00
Celestion PSB for Uniflex	£2-35
EMI 13 x 8, 3, 8 or 15 ohms	£2-25
EMI 13 x 8, 3, 8 or 15 ohms	£2-60
EMI 13 x 8 twin tweeter 3, 8 or 15 ohms	£3-60
EMI 13 x 8 type 350 15 watt 8 ohm	£8-00
Richard Allen 8" 3, 8 or 15 ohm	£2-35
Richard Allen 12" dual cone 3 or 15 ohm	£2-50
Fane 8" dual cone 808T 8 or 15 ohm	£2-85
Fane 8" d/cone roll surround 807T 8 or 15 ohm	£3-50
Elac 59RM109 9" x 5" 15 ohm	£2-70
Elac 59RM114 9" x 5" 8 ohm	£2-70
Elac 6 1/2" d/cone 8 ohm	£2-25
Elac 6 1/2" d/cone, roll surround 8 ohm	£2-50
Elac 4" tweeter 8 ohm	£1-50
Crossover for above (p. & p. free)	£1-50
Goodmans 8 P, 8 or 15 ohm	£4-75
Goodmans 10 P, 8 or 15 ohm	£5-25
Goodmans 12 P, 8 or 15 ohm	£10-50
Goodmans 15 P, 8 or 15 ohm	£17-00
Goodmans 18 P, 8 or 15 ohms	£27-50
2", 2 1/2" or 3" 8 ohm	£2-65
Phillips 5" 8 ohm	£1-95
7" x 4" or 8" x 5" 3 or 8 ohm	£1-50
10" x 6" 3, 8 or 15 ohm	£2-00

FREE with orders over £6—"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect. Prompt despatch p. & p. 25p per speaker.

WILMSLOW AUDIO, Dept. PW

10 Swan St., Wilmslow, Cheshire, SK9 1HF

B.H. COMPONENT FACTORS LTD.

VAT: Please add V.A.T. at the standard rate after April 1st.

SPECIAL RESISTOR KITS. (1W or 1W 5%, Carbon Film) RESISTKIT, 10 each E12 value, 10ohms-1M
A total of 610. £2-80 net
RESISTKIT, 25 each E12 value, 10ohms-1M
A total of 1525. £8-50 net

MULLARD POLYESTER (250 250V, μ F) 0-01, 0-015, 0-022, 0-033, 0-047, 3p, 0-068, 0-1, 0-15, 4p, 0-22, 5p, 0-33, 7p, 0-47, 8p, 0-68, 10p, 1-0, 13p, 1-5, 20p, 2-2, 23p.

MULLARD POLYESTER (250V, 180V, μ F) 0-01, 0-015, 0-022, 2p, 0-047, 0-068, 3p, 0-15, 0-22, 4p, 0-33, 5p, 0-47, 6p, 0-68, 1-0, 10p, 400V (μ F) 0-001, 0-0015, 0-0022, 0-0033, 0-01, 2p, 0-015, 0-033, 3p.

MULLARD ELECTROLYTIC (250, 5p, each, μ F/V) 0-64/84, 1-6/25, 3/40, 8/40, 10/40, 10/84, 16/40, 20/84, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/64, 125/16, 125/10.

HI-VOLT ELECTROLYTIC: 8/450, 12p, 18/450, 10p, 32/450, 22p, 36/450, 15p, 32/350, 22p, 100/500, 37p, 100/50, 35p, 200/25, 250/12, 250/12, 500/50, 12p, 1000/12, 10p, 1000/25, 2000/12, 2500/12, 15p, 1000/50, 35p, 2000/25, 2500/12, 30p, 3000/50, 65p, 5000/50, 85p, 2500/50, 55p, 1000/100, 80p.

CERAMIC PLATE, 50V (μ F) 22, 27, 33, 39, 47, 56, 64, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 640, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8 (μ F) 0-01, 0-015, 0-022, 0-033, 2p, 0-047, 30V, 3p, 0-1, 30V, 4p.

CARBON FILM RESISTORS, 1W, 5%, 10ohms-2M: 1W 5%, 22 Ω -1M 1p, each or 100 for 55p.
METAL FILM RESISTORS, 1W 5%, 27 Ω -10M 11p each or 100 for £1.

VEROBOARD 0-1 0-15 CARBON POTS
2" x 5" 25p 25p 5K-2M Log and Lin
2 1/2" x 3 1/2" 25p 17p single 15p, single
3" x 5" 25p 30p with SW, 24p, dual
3 1/2" x 3 1/2" 25p 25p 42p.

SCREENED WIRE
Pins, Pkt, 25 8p 8p
2 Pin DIN Plug 12p, 8kt, 10p Single 5p/yd., twin
3 Pin DIN Plug 13p, 8kt, 10p 8p, stereo 9p, quad
3 Pin DIN Plug 140p 15p, 8kt, 12p, 19p.

Red Panel Neon 240V, 12p
Inset Skeleton Pots 1K-1M 5p
Neon Bulb 90V, wire ended 5 for 20p
1N4001, 8p, 1N4002, 7p, 1N4003, 8p, 1N4004, 9p
1N914, 6p, 7400N, 15p, 7401-7410-7430, 15p
2N706, 10p, μ 1914, 30p, BC108, 11p, BFY51, 20p
(SW), 9p 10p, Discount £10-10%. The above items are only a few taken from our catalogue which is available free. Money back refund.

Dept. PW, 61 CHEDDINGTON RD., PIPSTONE LEIGHTON BUZZARD, BEDS., LU7 8AQ. Tel.: Cheddington 668446 (STD Code 0296)

OMNIA PRODUCTS



STABILIZED AUTO ADAPTOR

FOR CAR—CARAVAN—BOAT

Designed for feeding from 12 volt car battery:—Cassette recorders, radios, record players, etc., operated by dry cell batteries. Gives 3 different outputs (selector switch) 6, 7.5 & 9v; stabilized current for top performance —at no cost. Only £3.50 p. & p. 10p (add 10% VAT 1st April).

25 Wilbury Gardens Hove Sussex

"AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS"

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.50 NOW (S.A.E. for details)

TO: 'BOFFIN PROJECTS'
DEPT. KW2010
4 CUNLIFF ROAD
STONELEIGH, EWELL, SURREY

GLASS FIBRE P.C. BOARD. Large supplies available in single sided one ounce copper 2p per 3 sq. inches (under 1 foot). 75p per sq. ft. (over 1 foot). In double sided one ounce copper 1p per sq. inch (under 1 ft.), £1 per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

FASCIA PANELS to individual specification in etched aluminium. Hardware supplies for constructors. Printed circuit boards one-off's. Send 5p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

BEDFORD ELECTRONICS

2 Grove Place, Bedford
Bedford 51961

YOUR LOCAL COMPONENTS SUPPLIER
Free catalogue on request

12 VOLT FLUORESCENT LIGHTS
(as illustrated)



Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:

12 ins. 8 watt £3.60 post paid
21 ins. 13 watt £4.60 post paid

Callers welcome.
For lists or enquiries, large s.a.e.
SALOP ELECTRONICS, 23 WYLE COP
SHREWSBURY, SHROPSHIRE.

Versatile
10 in ONE



MINI-LAB *Comprising:*
● AC & DC Voltmeter ● Audio Generator
● Ohm Meter ● Resistance Substitution
● Capacitance Substitution ● DC Ammeter ● Battery Supply ● RF Signal Generator ● RF Field Strength Indicator

This new, unique instrument combines all you need for testing. Money back if not satisfied. **£11.25** plus 25p p. & p.

Cash with order or send s.a.e. for illustrated data sheet to:
J. H. ASSOCIATES LTD. (DEPT PW)
Cricklefield Lane, Bishop's Stortford, Herts.

ENGRAVING. Give your Fascia Panels that professional look. Have the letters machine engraved. 5p per letter, minimum order 50p. Plus P & P. Colourstones, 9 Broadway Close, Harwell, Berkshire.

Due to Warehouse Clearances we have a few low powered, F.M. VHF Wireless Station Type A. A.P.V. No. 88. Contained in two units (1) Transmitter/Receiver. (2) 12 Volt Power Unit and L.P. Amplifier. The TX and RX are contained in a waterproof diecast Alloy case, using a total of 14 Valves, operates on four switched channels which are Crystal controlled. All 8 Crystals are supplied, and are the same in each set. Therefore all sets will transmit and receive to each other, provided each are switched to the same channel out of the four. The Stations are supplied with Mounting Carriers, 2 Vertical Whip Aerials, plus Aerial Base, Spare Valves, Bulbs, Mounting Screws, Connectors, etc. Including the Operating Manual giving all details, plus circuits of the Wireless set. All above items are individually boxed and wrapped, placed in original Transit case.

ABSOLUTELY BRAND NEW
Made by Echo for the Government, no expense spared, few only available at £9.50, carr. £2.

RADIO TELETYPE TERMINAL SET
A type, AN/BSG1A latest Government release of these sought after units, housed in metal case, approx. size 8" x 19" x 16" deep. Using a total of 11 Valves, Supply Voltage 115 Volts 50 c/s. Containing meter switched for checking, send and receive Bias. Send and Receive Level, Loop and Plate current, in fair used ex Government condition. Few only available at £7.50, carr. £1.50.

FREQUENCY SHIFT CONVERTOR AND COMPARATOR
Type AN/URA-8B for Diversity use or single channels £15 and £10 respectively, Carr. £1.50 and £2.50.

FREQUENCY METER TS186 D/UP
Recent Ministry release of this scarce and valued unit, this is basically the VHF/UHF version of the BC221. Range 100 mgs to 10,000 mgs. Distributed over approx. 16,500 dial divisions, each meter (same as the BC221) contains its own book of Calibration charts, plus circuits and Instruction Book. Contained in Metal Shockproof Transit case, with Supply Cable. Supply 115 volts ± 10% 50 c/s. Output on headphones or meter in the front panel. Accuracy is 0.01% - 0.002% on the Crystal Calibrator check points. Sensitivity for R/F signal input 500 Micro Volts to 1 volt. A plug is also provided for V1010 output for connection to an Oscilloscope, RF input connection is via coaxial cable or standard Wave Guide. Limited number available £18.50, carr. £1.50.

LARGE QUANTITY OF TELEPRINTER PAPER
Available, sprocket fed, contained in sealed packs, each pack containing 4 separate wads, price 80p per pack of four pads, post 25p, or wooden crate containing 5 packs = 20 wads £2, carr. 50p.

CREED TELEPRINTER MOTORS
For mains 200/250V A.C. for use on 7B Teleprinters etc., available brand new £2, post 25p.

MALLORY LONG LIFE BATTERIES
Type RM12 1.35 volts as used in Contaminator Meters No. 1, £1 per box of 50, post 25p. Brand new ex government.

Terms C.W.O. or uncrushed P.O.s in case stocks run out, so we can refund same.

JOHNS RADIO

424 BRADFORD ROAD, BATLEY, YORKS.
Phone: BATLEY 7732

CHASSIS and CASES by



H. L. SMITH & CO LTD
287/9 Edgware Road
London W2 1BE
Telephone: 01-723 5891

BLANK CHASSIS

FOUR-SIDED 16 SWG ALUMINIUM


Size	Price	Base	Size	Price	Base
6x4x2"	34p	17p	10x8x2 1/2"	66p	30p
7x4x1 1/4"	33p	18p	12x7x2 1/2"	66p	33p
7x5x2"	40p	19p	12x9x2 1/2"	76p	38p
8x4x2"	38p	19p	13x8x2 1/2"	76p	38p
8 1/2 x 5 1/2 x 2"	44p	21p	14x7x3"	80p	36p
9x7x2"	50p	26p	14x10x2 1/2"	88p	47p
10x4x2 1/2"	50p	21p	15x10x2 1/2"	92p	50p
12x4x2 1/2"	55p	22p	17x10x3"	£1.10	55p
12x5x3"	66p	26p	Plus post and packing		

CASES

ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
N	8x6x2"	£1.00	W	12x7x7"	£2.50
N	6x6x3"	£1.05	W	15x9x8"	£3.15
N	4x4x2"	80p	Y	8x6x6"	£2.25
N	4x4x4"	95p	Y	12x7x7"	£2.80
U	5 1/2 x 4 1/2 x 4 1/2"	£1.15	Y	13x7x9"	£3.15
U	8x6x6"	£1.45	Y	15x9x9"	£3.35
U	9 1/2 x 7 1/2 x 3 1/2"	£1.55	Z	17x10x9"	£4.15
U	15x9x9"	£3.00	Z	19x10x8 1/2"	£4.35
W	8x6x6"	£1.90	Plus p. & p. *Height		

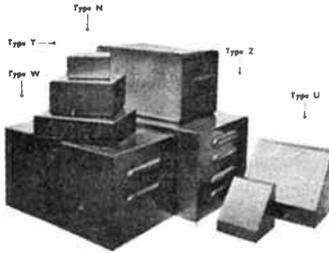Type N has removable bottom. Type U removable bottom or back. Type W removable front. Type Y all screwed construction. Type Z removable back and front.



TO FIT OUR CASES

7x5 1/2 x 1 1/4"	38p	21p	12x6 1/2 x 2"	60p	33p
7x5 1/2 x 2"	43p	21p	14x8 1/2 x 2"	74p	44p
11x6 1/2 x 1 1/4"	48p	30p	15 1/2 x 9 1/2 x 2 1/2"	94p	52p
11x6 1/2 x 2"	55p	30p	17 1/2 x 9 1/2 x 2 1/2"	£1.05	59p

Plus post & packing

PANELS: Any size up to 3ft. at 36p sq. ft. 16 s.w.g. (18 s.w.g. 32p) Plus postage and packing

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDEGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 4285

The T.V. Graveyard of the North, as seen on T.V. Close to the Motorway. Plenty of Free Parking Space. Call in and see us any day 9-6. Closed Sunday. Est. 1935.

NEW TOP QUALITY MAINS TRANSFORMERS. 250v-0-250v at 80mA. 6.3v at 4amp. Not to be missed at £1 50 Post Paid. Weight 10lbs.

QUALITY RECORDING TAPES. 7" L.P. Tapes 75p, 7" S.T. 60p. 5" L.P. 50p. 5" S.T. 40p. Post on any tape 10p.

TOP QUALITY TAPE CASSETTES. C60. 35p, C90. 45p, C120. 55p P. & P. 12p.
JAP EAPPIES. 3 5 and 2 5 12p each. P. & P. 3p.

STUDENTS' WIRELESS PROCEDURE TRAINING SET. Comprising: Mike, Single L.R. Phone and Connector, In small Wood Case. Good Condition, but Untested. A Gift at £1.25 Post Paid. Complete Untested T.V. Sets, with Back and all Valves, 88CI and ITV 17" 90° Tube £2. 17" 110° Tube £3. 19" Slim £5. Carr. and Ins. £1 50.

Reclaimed T.V. Tubes. All with 12 Months' Guarantee. AW43/88 £1.50. AW43/80 £1.50. MW43/69 £1. Many other Types in Stock. Carriage and Ins. on any Tube £1.50.

½ cwt. of EX GOVERNMENT ELECTRONIC SCRAP. RESISTORS, PANELS, GEARS, ETC. 25p. Carr. 75p.

Ex Equipment Valves. All Tested on our Mullard Valve Tester before despatched. 3 Months' Guarantee on all Valves. Single Valves Post 3p, over Post Paid

ARF12	5p	PCF80	5p	PY82	8p
E891	4p	PCC84	5p	PY33	17p
E890	8p	PCL82	12p	U191	20p
EF85	12p	PCL83	12p	68W7	10p
EF89	12p	PCL84	12p	6U4	10p
ECC81	10p	FL81	17p	20P1	15p
ECC82	12p	FL82	8p	20P3	10p
ECL80	8p	FL83	8p	30F5	10p
EF50	60p per doz.	PL36	17p	30FL1	20p
EF91	4p	PY81	8p	6 30L2	20p
EY86	20p				

COMPARE OUR PRICES

Speaker Bargains		Microphone Bargains—continued	
E.M.I. 13 x 8 in 3, 8 & 15 OHMS		MIC60 "ACOS" stick crystal	£1-00
PLAIN	£2-00	CM70 PLANET stick metal,	
WITH TWEETER	£2-25	switch crystal	£1-45
Type 350-20 watt with Tweeter		DM160 Dynamic uni-dir, ball	
8 OHM p. & p. 37p.	£7-25	metal	£3-75
TWIN TWEETER	£3-50	UD130 50K/600 OHM uni-dir,	
8 x 5 in 3, 8 & 15 OHMS	£1-30	ball metal	£4-50
7 x 4 in 3 & 8 OHMS	£1-05	TW209 LESSON DUAL imp.	
FANE8" 8. OHM DUAL CONE	£2-30	ball metal, uni-dir.	£3-75
CELESTION 8" 15.OHM	£1-50	GUITAR MIKE	45
GOODMANS 10 x 8 3.OHM.	£1-60	LAPEL TYPE, crystal	40
BAKER GROUP 25 12" 25		POSTAGE 17p each.	
WATT 8 or 15.OHM	£5-75		
2 1/2" 8 or 64 OHM p. & p. 10p.	50	Amplifier Modules	
POSTAGE 25p per SPEAKER		One valve chassis Amplifier for	
Kit-Form Cabinets Teak		record player 2 Watt output, volume	
(17" x 10" x 6") with a 13" x 8"		control and tone control, on/off	
or 8" CUT OUT	£2-75	switch, £3-50 (P. & P. 25p).	
(12" x 12" x 6") with a 8" x 5" or		3 Watt mono Audio Module (Trans-	
8" CUT OUT	£2-25	istorised) £2-50 (P. & P. 10p).	
(PLEASE SPECIFY CUT OUT)		15 Watt Mono Audio Module (Trans-	
Add 35p per Cabinet for p. & p.		istorised) £3-95 (P. & P. 10p).	
Cartridges with standard fittings &		3 Watt Stereo Module (1 1/2" Watt/	
stylus		Channel) £3-75 (P. & P. 10p).	
ACOS GP91/2SC or GP91/		5 Watt Stereo Module (2 1/2" Watt/	
3SC STEREO COMPAT-		Channel) £5-50 (P. & P. 15p)	
IBLE	£1-05	Stereo Headphones	
ACOS GP94 STEREO CER.	£1-90	De-Luxe finish 8-16 Ohm Matching	
ACOS GP95 STEREO CRYST.	£1-35	imp. mono/stereo switch complete	
9THAC SONOTONE STEREO		with lead and stereo jack plug only	
CERAMIC (DIAMOND)	£2-00	£2-75 (P. & P. 25p).	
ACOS GP97/2C MONO CRYST.	85	NO STEREO PHONO SOCKET??	
ACOS GP101 COMP. CRYST.	75	Headphone Adaptor only £1-35	
19-TI SONOTONE STEREO		(P. & P. 10p)	
CRYSTAL	90	Tapes—"MYLAR"	
POSTAGE 5p per CARTRIDGE		base finest	
Microphone Bargains		quality British made.	
MIC45 "ACOS" metal case,		5" 600 ft 3p 5 1/2" 1800 ft 85p	
crystal hand	95	5" 900 ft 45p 7" 1200 ft 55p	
CM 20 Crystal Hand	45	5" 1200 ft 60p 7" 1800 ft 80p	
DX143 Dynamic, cassette-		5 1/2" 900 ft 49p 7" 2400 ft 95p	
type stick	£1-00	5 1/2" 1200 ft 55p	
		POSTAGE 9p each.	

THIS MONTH'S SPECIAL OFFER

BIB Groov-Kleen Model 42, effective record cleaner. Retail price £1 95
Our price £1.50 (P. & P. 15p)

SEND 25p FOR COMPLETE CATALOGUE

Slight price alterations due to VAT will effect certain of our items after
April 1st

RIVERSDALE ELECTRONICS

Mail Order Department W4/73, P.O. Box 470, Manchester M60 4BU
ALL OUR MERCHANDISE IS FULLY GUARANTEED

INDEX TO ADVERTISERS

A.H. Supplies	1072
Adcola Products	1075
Amtron U.K.	1059
Antex Ltd.	1091
Apex Aerials	1146
Arrow Electronics	1115
Astro Electronics	1140
Attwood, V.	1148
8.H. Components Factors	1149
Baines, R.	1146
Baker Loudspeakers Ltd	1140
Bedford Electronics	1150
Bell's Television	1146
Bentley Acoustic Corporation Ltd	1074
Bernard, Gerald	1128
B.I.E.T.	1068, Cov iii
B1-Pak Semiconductors	1069, 1070, 1071
B1-Pre-Pak Ltd.	1135
Boffin Projects	1150
British National Radio & Electronic	
School	1065, 1142
Broadway Electronics	1064
Bull. J. (Electrical) Ltd.	1132
C.C.I. Ltd	1128
Caranna, C.	1146
Codar	1060
Colomor (Electronics) Ltd	1096
Comet High Fidelity Discount Ware-	
houses	1076, 1077
Chromasonic Electronics	1061
Crowborough Electronics	1149
D.E.W. Ltd.	1149
Dabar Electronic Products	1128
Denco	1146
Dexter & Co.	1074
Douglas Electronic Industries Ltd	1066
Duke & Co. (London) Ltd.	1096

Electrokit	1060
Electronic Design Associates	1116
Electrosparcs	1078
Electrovalue	1131
Elekon Enterprises	1068
Elvins Electronic Musical Instruments	1142
Felstead Electronics	1116
Galleo, Trading	1148
Gladstone Radio	1096
Global A. dio Discount Warehouses	1068
Golledge P. P.	1148
Greenweld Electronics	1148
HAC Short-wave Products	1066
Harverson Surplus Co. Ltd.	1143
Heath (Gloucester) Ltd.	1095
Henry's Radio Ltd.	1127, Cov iv
Home Radio (Components) Ltd.	1078
I.C.S.	1058, 1147
J.H. Associates	1150
Jef Electronics	1147
Jermyn Industries	1058
Johns Radio	1150
Johnson Radio	1148
K.V.A. Electronics	1120
Kennington Supplies	1146
Keytronics	1066
King, J. M.	1149
Lasky's Radio Ltd.	1072
Lewis Radio	1128
Linear Products Ltd.	1116
London Computer Operators Training	
Centre	1147
London Electronic College	1147
McGarva, David	1146
Marshall, A. & Son	1092
Merlin Supply Co.	1064
Morse	1146
Multicore Solders Ltd	1068
Omnia Products	1150

Padgetts Radio Store	1151
Partridge Electronics Ltd.	1140
Phonosonics	1064
Radio Component Specialists	1119
Radio Book Services	1147
Radio Exchange Co. Ltd.	1123
Radio & T.V. Components (Acton) Ltd.	1062, 3
Radio Society of Great Britain	1066
Readers Radio	1142
Redhawk Sales	1148
Riversdale Electronics	1151
ROC Electronics Ltd.	1073
RSC (Hi-Fi Centres) Ltd.	Cov ii, 1057
R.S.T. Valve Mail Order Co	1064
Saxon Entertainments	1080
Scientific & Technical	1140
Salop Electronics	1150
Selray Book Co. Ltd.	1147
Semicon Index Ltd.	1147
Sinclair Radionics Ltd.	1144, 1145
Shopertunities Ltd.	1079
Smith, G. W. & Co. Ltd.	1136, 7, 8, 9
Smith, H. L. & Co. Ltd.	1150
Sonic Sound Audio Ltd.	1058
Stephens Electronics	1120
Surplronics	1078
Swanley Electronics	1120
Teleradio Co. Ltd.	1148
Thacker, A. H. & Sons Ltd.	1142
Tidman Mail Order	1147
Trade Aids	1074
Trade Disposals	1146
Trampus Electronix	1148
Trannies	1141
Tuac Ltd.	1067
Velco Electronics	1149
Vero Electronics	1074
West London Direct Supplies	1149
Wilmslow Audio	1060, 1120, 1149
York Electronics	1072
Z & I Aero Services	1152

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
 When sending cash with order, please include 12½p in £ for postage and handling
MINIMUM CHARGE 15np. No C.O.D. orders accepted
 Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
 Open all day Saturday

0A2	0.40	6AR6	0.85	6F5	0.75	7Y4	0.75
0A3	0.48	6AR11	1.25	6F6G	0.45	7Y6	0.70
0B2	0.40	6AS5	0.55	6F11	0.50	10C2	0.60
0C3	0.70	6AR7G	0.85	6F13	0.50	10D1	0.65
0C3	0.40	6AT6	0.38	6F14	0.70	10D2	0.55
0D3	0.40	6AU6	0.30	6F15	0.85	10P1	0.75
1B3GT	0.45	6AV6	0.40	6F18	0.50	10P9	0.65
1L4	0.25	6AW8A	0.65	6F23	0.90	10P18	0.60
1R4	0.50	6BA6	0.25	6F24	0.50	10L1	0.60
1B5	0.45	6B2B	0.32	6F25	1.00	10LD11	0.70
1B4	0.45	6BP6	0.55	6F26	0.35	10P13	0.75
1B5	0.80	6BH6	0.75	6F28	0.70	12A35	0.70
1T4	0.30	6BJ6	0.55	6GK6	0.60	12AC8	0.60
1U4	0.40	6BK7A	0.75	6J4	0.80	12AE8	0.60
1U5	0.75	6BN6	0.43	6J5GT	0.40	12AL5	0.55
1V2	0.55	6B5	0.30	6L7	0.30	12AQ5	0.50
1X2B	0.55	6H05	0.25	6J7	0.45	12AT7	0.40
2D21	0.40	6H18	0.75	6K4JT	0.60	12AT7	0.40
3A4	0.45	6H87	1.35	6K6GT	0.75	12A16	0.45
3A5	0.75	6BW6	0.90	6K7	0.43	12AU7	0.33
3BP1	3.50	6BW7	0.90	6K8G	0.45	12AV6	0.45
3B4	0.40	6BX6	0.25	6K25	0.50	30FL12	1.10
3V4	0.55	6B2B	0.30	6L5GT	0.55	30FL14	0.90
5H4GT	0.75	6C4	0.35	6L7	0.45	30L1	0.40
6U4G	0.40	6CSGT	0.55	6L18	0.50	30L15	0.95
5V4G	0.60	6CB6	0.40	6LD20	0.50	30L15	0.95
5Y3GT	0.45	6CD6GA	0.40	6L20	0.55	30L16	0.55
5Z3	0.75	1.30	0.30	6P25	0.65	30P12	1.00
5Z4G	0.45	6C07	0.85	6L27	0.40	30P19	0.95
6J30L2	0.90	6CH16	0.60	6S47	0.45	30P12	1.10
6AR4	0.45	6CL6	0.60	6S47	0.45	30P13	1.10
6AF4A	0.60	6CU6	0.80	6S47	0.45	30PL14	1.25
6AG5	0.25	6CW4	0.70	6S47	0.45	35A3	0.80
6AG7	0.45	6CY5	0.50	6S47	0.45	35A5	0.75
6AH6	0.60	6CY7	0.75	6S47	0.45	35B5	0.85
6AJ6	0.30	6D3	0.75	6S47	0.45	35C5	0.80
6AK5	0.40	6DCG	0.80	6T8	0.88	35D5	0.75
6AK6	0.80	6DK6	0.60	6U4GT	0.70	35L2	0.75
6AL3	0.43	6DQB	0.75	6U5G	0.75	35Z3	0.75
6AL5	0.22	6D84	1.25	6U8A	0.48	35Z3	0.75
6AM5	0.40	6EAB	0.85	6V5GT	0.45	35Z3	0.75
6AM6	0.37	6E17	0.95	6X5	0.95	50A5	0.50
6AQ5	0.45	6E17	0.95	6X5GT	0.45	50B5	0.70
6A95	0.70	6EW6	0.70	6X8	0.85	50C5	0.60
6AR5	0.55	6F1	0.75	6Y6G	0.80	50CDSG1.20	0.60
						50EH5	0.65

First Quality Fully Guaranteed




ELECTRONIC VALVES

30C1	0.30	50L6GT	0.80	DM160	0.68	ECC88	0.40	
30C15	1.00	85A2	0.55	DY51	0.55	ECC89	0.50	
30C17	1.10	90AG	2.40	DY86	0.35	ECC91	0.30	
30C18	0.90	90AY	2.50	DY87	0.38	ECC189	0.65	
30F6	1.00	90C1	0.75	1Y802	0.37	ECC190	0.65	
30FL1	0.80	90C2	2.40	EMOP	1.10	EC80	0.35	
30FL12	1.10	80T	0.50	E80C	0.70	EC82	0.35	
30FL14	0.90	813	4.00	E180F	1.00	ECF804.65	EM34	1.00
30L1	0.40	866A	0.85	ER10F	2.90	ECH42	0.75	
30L15	0.95	5642	0.70	EAB	0.30	ECH181	0.30	
30L16	0.55	6080	1.75	EAF42	0.60	ECH85	0.45	
30P12	1.00	6146	1.60	EC35	0.50	ECH84	0.45	
30P19	0.95	6146B	2.50	EBC41	0.55	ECL80	0.50	
30P13	1.10	6199	2.25	EBC81	0.85	ECL81	0.50	
30PL14	1.25	7939	0.85	EBF83	0.40	EN81	0.70	
35A3	0.80	7586	1.50	EBF89	0.32	ECL84	0.55	
35A5	0.75	7895	1.50	ELB31	1.50	ECL85	0.55	
35B5	0.85	A2293	2.20	EC35	0.50	ECL86	0.40	
35C5	0.80	AZ1	0.60	EC88	0.60	EF37A	1.00	
35D5	0.75	AZ31	0.55	EC88	0.60	EF40	0.50	
35L2	0.75	CBL1	0.90	EC90	0.35	EF41	0.85	
35Z3	0.75	CBL31	1.00	EC92	0.45	EF42	0.70	
35Z3	0.75	CY1	0.50	EC93	0.60	EF80	0.30	
35Z3	0.75	CY31	0.60	ECC35	1.00	EF85	0.35	
35Z3	0.75	DAF96	0.50	ECC40	0.70	EF86	0.30	
50A5	0.50	DF96	0.50	EC81	0.40	EF89	0.25	
50B5	0.70	DK92	0.70	EC82	0.35	EF91	0.33	
50C5	0.60	DK96	0.80	EC83	0.35	EF92	0.35	
50CDSG1.20	0.60	DL96	0.55	ECC84	0.30			
50EH5	0.65	DM70	0.60					

EP97	0.85	GZ32	0.50	PY818	1.00	U301	0.55
EP98	0.70	GZ33	0.75	PPL200	0.85	U403	0.70
EP183	0.75	GZ34	0.80	P133	0.40	U404	0.70
EP184	0.35	HABC800.65		PL36	0.55	U601	0.80
EP204	1.35	1K90	0.50	PL81	0.50	UABC80	
EK90	0.32	KT86	2.35	PL82	0.45		0.40
EL34	0.50	KT88	2.25	PL83	0.45	UAF41	0.70
EL36	0.50	N78	1.60	PL84	0.40	UAF42	0.60
EL37	1.70	PAB	0.80	PL302	0.65	UB41	0.65
EL41	0.75	PC86	0.60	PL504	0.75	UBC41	0.55
EL81	0.85	PC88	0.60	PL508	0.90	UC81	0.45
EL83	0.50	PC92	0.65	PL509	1.10	UP80	0.40
EL84	0.25	PC97	0.60	PL801	1.00	UP89	0.40
EL85	0.43	PC900	0.45	PL802	0.95	UBL1	0.70
EL86	0.40	PC94	0.40	PM84	0.60	UBI21	0.70
EL90	0.42	PC88	0.65	PY31	0.25	UC92	0.45
EL92	1.15	PC89	0.55	PY33	0.65	UC93	0.45
EL92	1.15	PC89	0.55	PY80	0.40	UC90	0.70
EL92	1.15	PC89	0.55	PY81	0.80	UCI21	0.60
EL92	1.15	PC89	0.55	PY82	0.35	UCI42	0.70
EL92	1.15	PC89	0.55	PY83	0.38	UCH81	0.40
EL92	1.15	PC89	0.55	PY84	0.40	UCI81	0.60
EL92	1.15	PC89	0.55	PY800	0.47	UCI82	0.45
EL92	1.15	PC89	0.55	PY801	0.50	UCI83	0.65
EL92	1.15	PC89	0.55	PY802	0.50	UP20	0.85
EL92	1.15	PC89	0.55	PY803	0.50	UP11	0.60
EL92	1.15	PC89	0.55	PY804	0.50	UP41	0.65
EL92	1.15	PC89	0.55	PY805	0.50	UP42	0.65
EL92	1.15	PC89	0.55	PY806	0.75	UP43	0.65
EL92	1.15	PC89	0.55	PY807	0.75	UP85	0.40
EL92	1.15	PC89	0.55	PY808	0.90	UP89	0.40
EL92	1.15	PC89	0.55	PY809	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY810	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY811	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY812	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY813	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY814	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY815	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY816	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY817	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY818	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY819	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY820	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY821	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY822	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY823	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY824	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY825	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY826	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY827	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY828	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY829	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY830	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY831	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY832	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY833	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY834	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY835	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY836	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY837	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY838	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY839	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY840	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY841	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY842	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY843	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY844	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY845	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY846	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY847	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY848	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY849	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY850	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY851	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY852	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY853	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY854	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY855	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY856	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY857	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY858	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY859	1.25	UP89	0.40
EL92	1.15	PC89	0.55	PY860	1.25	UP89	0

FREE!

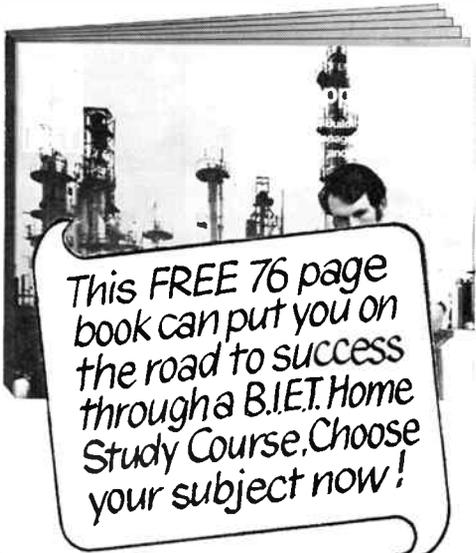Over 150 ways to engineer a better future



HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*. Write to B.I.E.T. Dept. BPW03, Aldermaston Court, Reading RG7 4PF.

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2-6s. PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

<input type="checkbox"/> MECHANICAL	<input type="checkbox"/> Man. Prod.—cont.	<input type="checkbox"/> Constructional-cont.
<input type="checkbox"/> A.M.S.E. (Mech.)	<input type="checkbox"/> Quality Control	<input type="checkbox"/> Building
<input type="checkbox"/> Boiler Inspect.	<input type="checkbox"/> Salesmanship	<input type="checkbox"/> Building Drawing
<input type="checkbox"/> & Operation	<input type="checkbox"/> Storekeeping	<input type="checkbox"/> Build. Foreman
<input type="checkbox"/> C & G Eng. Crafts	<input type="checkbox"/> Work Study	<input type="checkbox"/> Carpentry & Join.
<input type="checkbox"/> C & G Fabricat.	<input type="checkbox"/> Works	<input type="checkbox"/> Civil & Municipal
<input type="checkbox"/> Diesel Eng.	<input type="checkbox"/> Management	<input type="checkbox"/> Engineering
<input type="checkbox"/> Eng. Inspection	<input type="checkbox"/> Draughtsmanship	<input type="checkbox"/> Constructional
<input type="checkbox"/> Eng. Metallurgy	<input type="checkbox"/> A.M.I.E.D.	<input type="checkbox"/> Engineering
<input type="checkbox"/> Inst. Eng. & Tech.	<input type="checkbox"/> Design of Elec.	<input type="checkbox"/> Construction
<input type="checkbox"/> Inst. Motor Ind.	<input type="checkbox"/> Machines	<input type="checkbox"/> Surveyors
<input type="checkbox"/> Malinten. Eng.	<input type="checkbox"/> Die & Press Tool	<input type="checkbox"/> Institute
<input type="checkbox"/> Mechanical Eng.	<input type="checkbox"/> Design	<input type="checkbox"/> Clerk of Works
<input type="checkbox"/> Sheet Metal Work	<input type="checkbox"/> Electrical	<input type="checkbox"/> Council Eng.
<input type="checkbox"/> Welding	<input type="checkbox"/> Draughtsmanship	<input type="checkbox"/> Geology
<input type="checkbox"/> ELECTRICAL & ELECTRONIC	<input type="checkbox"/> Gen. Draughtsmanship	<input type="checkbox"/> Health Eng.
<input type="checkbox"/> A.M.S.E. (Elec.)	<input type="checkbox"/> Jig & Tool Des.	<input type="checkbox"/> Heat & Vent.
<input type="checkbox"/> C & G Elec. Eng.	<input type="checkbox"/> Tech. Drawing	<input type="checkbox"/> Hydraulics
<input type="checkbox"/> C & G Elec. Inst.	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS	<input type="checkbox"/> Inst. of Builders
<input type="checkbox"/> C & G Elec. Tech.	<input type="checkbox"/> Colour TV	<input type="checkbox"/> Inst. Works &
<input type="checkbox"/> Computer Elect.	<input type="checkbox"/> C & G Radio/TV/	<input type="checkbox"/> Highway Sup.
<input type="checkbox"/> Elec. Maths	<input type="checkbox"/> Electronics	<input type="checkbox"/> Painting & Dec.
<input type="checkbox"/> Elec. Science	<input type="checkbox"/> C & G Telecomm.	<input type="checkbox"/> Public Hygiene
<input type="checkbox"/> Electronic Eng.	<input type="checkbox"/> Tech.	<input type="checkbox"/> Road Engineer.
<input type="checkbox"/> Electrical Eng.	<input type="checkbox"/> Prac. Rad. Elec. (with kit)	<input type="checkbox"/> Structural Eng.
<input type="checkbox"/> Electrical Eng. Install. & Wiring	<input type="checkbox"/> Radio Amateurs	<input type="checkbox"/> Surveying
<input type="checkbox"/> Meters	<input type="checkbox"/> Exam	<input type="checkbox"/> GENERAL
<input type="checkbox"/> & Measuring Instruments	<input type="checkbox"/> Radio Servicing & Repairs	<input type="checkbox"/> Agricultural Eng.
<input type="checkbox"/> MANAGEMENT & PRODUCTION	<input type="checkbox"/> Radio & TV Eng.	<input type="checkbox"/> Council of Eng. Inst.
<input type="checkbox"/> Auto. Control	<input type="checkbox"/> Trans. Course	<input type="checkbox"/> Farm Science
<input type="checkbox"/> Computer Prog.	<input type="checkbox"/> TV Main. & Serv.	<input type="checkbox"/> General Educat.
<input type="checkbox"/> Electronic Data Processing	<input type="checkbox"/> AUTO & AERO	<input type="checkbox"/> Gen. Plastics
<input type="checkbox"/> Estimating	<input type="checkbox"/> Aero Eng.	<input type="checkbox"/> Pract. Maths
<input type="checkbox"/> Foremanship	<input type="checkbox"/> A.M.I.M.I.	<input type="checkbox"/> Pract. Slide Rule
<input type="checkbox"/> Inst. Cost & Man. Accountants	<input type="checkbox"/> A.E.C. Cert.	<input type="checkbox"/> Pure & Applied Maths
<input type="checkbox"/> Inst. Marketing Management	<input type="checkbox"/> Auto Engineer.	<input type="checkbox"/> Refrigeration
<input type="checkbox"/> Metrication	<input type="checkbox"/> Auto Repair	<input type="checkbox"/> Rubber Tech.
<input type="checkbox"/> Motor Trade Man.	<input type="checkbox"/> C & G Auto. Eng. Garage	<input type="checkbox"/> Sales Engineers
<input type="checkbox"/> Network Plan.	<input type="checkbox"/> Management	<input type="checkbox"/> Tech. Report
<input type="checkbox"/> Numerical Cont.	<input type="checkbox"/> MAA/IMI Dipl.	<input type="checkbox"/> Writing
<input type="checkbox"/> Operational Research	<input type="checkbox"/> Motor Vehicle Mechanics	<input type="checkbox"/> Timber Trade
<input type="checkbox"/> Personnel Man.	<input type="checkbox"/> CONSTRUCTIONAL	<input type="checkbox"/> University Ent.
<input type="checkbox"/> Planning Eng.	<input type="checkbox"/> A.M.S.E. (Civil)	<input type="checkbox"/> G.C.E.
<input type="checkbox"/> Production Eng.	<input type="checkbox"/> Architecture	<input type="checkbox"/> 58 'O' & 'A' LEVELS SUBJECTS Over 10,000 group passes

Coaching for many major exams including ONC, C & G, etc.

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW03 Aldermaston Court, Reading RG7 4PF QN BPW03

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____

Accredited by C.A.C.C.
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

BUILD THE TEXAN

★ FREE TEAK CABINET with complete kit!

FEATURES. New slim design with 6 - IC's, IC Sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES —DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES. On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector; Mag. P.U. Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc (Parts list Ref. 20 on request).
Constructional details Ref. No. 21 30p

SPECIAL KIT PRICE **£28-50**

P & P 45p
COMPLETE WITH FREE TEAK CABINET
Designer approved kits distributed by Henrys!

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)



★ SLIM DESIGN WITH SILVER TRIM
Overall chassis size 14 1/2" x 6" x 2" high

ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

IC RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wireless, January 1973. Practical Electronics, February 1973. Price £1.20.

BATTERY TAPE DECK

Garrard 9 volt Tape Deck with heads, etc. As previously advertised. Limited quantity. £9.50, post 30p.

LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish Italian. £1.49 per cassette. £5.50 per set of four.

DISCO SPOTBANK

£12.75, p. & p. 35p.

HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES. FREE. 24 page detailed brochure (Ref. No. 17). You can see the savings!

EMI HIGH QUALITY CASSETTES

The best UK low noise tapes but at a special price. "Living Sound" cassettes meet the highest international standard (IEC 94A). Fantastic price savings.

	RRP each	3 for	6 for	10 for
C60	71p	1-102.00	3-10	
C90	98p	1-472.85	4-6	
C120	1.48	1-803.50	5-6	

Full guarantee. Post paid. See earlier page of this magazine for transistors and semi-conductor devices. Huge range of transistors and semi-conductors in stock. Free brochure (Ref. 36) on request.

ULTRASONIC TRANSDUCERS

Operate at 40Kc/s up to 100 yds. Ideal for remote switching and signalling. Complete with data and circuits. £5.90 per pair. Post 10p

MARRIOTT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO
'17' High Impedance £2.00
'18' Med. Impedance £2.00
'36' Med.-Low Imp. £3.50
Erase Heads for above 75p
'63' 2 track mono- £1.75
Hi Imp.
'43' Erase Head for above 75p

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)
XN3, XN13, GN6 0-9 side view with data, 85p.
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
3015F 7 seg £2 each. £7 per 4 with data.
12 and 24 hour clock circuits Ref. No. 31 15p.

Miniature Amplifier

5 transistor. 300mW o/p. Fitted volume and sensitivity control, 9 volt operated. £1.75 each P/P 15p.

Quality Slider Controls

60mm stroke singles and ganged. Complete with knobs. 5K, 10K, 25K, 100K, 250K, 500K. 1 meg. Log and Lin. 40p each. 10K, 25K, 50K, 100K, 250K, Log and Lin ganged. 60p each.

LOW COST HI-FI SPEAKERS



E.M.I. Size 1 1/2" x 8 1/2". Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post. 22p.
TYPE 150 TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.



POLISHED CABINETS 150, 150TC 450 £4.60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 ohms)
SERIES 6 (Assembled 150 T/C) per pair £16.50. Post 70p
SERIES 8 (Assembled 450) per pair £18.95. Post 70p

TEST EQUIPMENT

Just a selection!

- SE250B Pocket Pencil Signal Injector £1.90
 - SE500 Pocket Pencil Signal Tracer £1.50
 - THL33D Robust 2K/10V £4.55 with case £4.95
 - TE15 Grid Dip Meter 440 KHz-280 MHz £13.45
 - S00 30 K/V Multimeter £9.25
 - 200H 20K/V Multimeter £4.20. With case £4.95
 - AF105 50K/V Multimeter £8.50. With case £9.50
 - U4341 AC/DC Multimeter with transistor tester with steel case £10.50
 - TE20D RF Generator 120KHz-500MHz £15.95. Carr. 35p
 - TE22D Audio Generator 20Hz-200KHz £17.50. Carr. 35p
 - CI-5 Pulse Scope 10Hz-10MHz £39.00. Carr. 50p
 - TE65 Valve Voltmeter 28 ranges £17.50. Carr. 40p
- ALL NOMBREX MODELS IN STOCK



PA-Disco-Lighting

UK's Largest Range—Write phone or call in. Details and demonstrations on request.



- DJ30L 3 Channel sound to light unit, 3KW. £29.50
- DJ40L 3 Channel Mic (built-in) to light, 3kW. £38.75
- DJ70S 70 watt Disco amp/mixer. £49.75
- DISCOAMP 100 watt amp/mixer. £68.85
- DJ105S 30 watt Disco amp/mixer. £32.25
- Anti-Feedback Quality Mic. £11.50
- DIS50 50 watt PA Amplifier £43.95
- DJ700 70 watt £52.75
- GROUP 300 150 watt rms "Group" Valve Amplifier £86.00
- FIBRE OPTICS LIGHTING. — MICS, EFFECTS, PROJECTORS.
- SPOTS, DIMMERS — STANDS, MIXERS, SPEAKERS.
- Everything for PA — Disco — Lighting.
- FREE Stock List Ref. No. 18
- PORTABLE DISCOS — DETAILS ON REQUEST
- CREDIT TERMS FOR CALLERS

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BANDWIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO.
A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.
TOTAL £6.97, p.p. 20p. Decoder Kit £5.97.
Tuning-meter £1.75.
Mains unit (optional) Model P5900 £2.47. Post 20p
Mains unit for Tuner and Decoder P56/12 £3.25. Post 20p



SINCLAIR PROJECT 60 MODULES —SAVE POUNDS!

- Z30 £3.57; Z50 £4.37
- STEREO 60 PZ5 £3.97
- £7.97; PZ8 £4.77
- PZ6 £6.37;



Transformer for PZ8 £2.95
Active Filter Unit £4.45
Stereo FM Tuner £16.95
IC12 £1.80; Q16's £15 pr.
Post etc. 20p per item

PACKAGE DEALS Post 25p
2xZ30, Stereo 60, PZ5 £15.95
2xZ30, Stereo 60, PZ6 £18.00
2xZ50, Stereo 60, PZ8 £20.25
Transformer for PZ8 £2.95
PROJECT 60S KIT £19.95

ML-3 MW/LW TUNER to BUILD



Uses Mullard Module. Slow motion tuning. Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2". TOTAL COST TO BUILD £4.85, Post 15p. All parts sold separately. Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. mV push-pull output. Fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7.98, p.p. 32p. (Battery 22p). All parts sold separately—Leaflet No. 2

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special-Low Prices and Fully Guaranteed.

Post Paid
PRICE 55p (40p FOR CALLERS)
PLUS! FIVE 10p VOUCHERS

Send to this address—HENRY'S RADIO LTD. (Dept. PW) 3 ALBEMARLE WAY, LONDON, E.C.1.—for catalogue by post only. All other mail and callers to "303" see above.



VAT

Prices DO NOT include Value Added Tax. From 1st April, 1973 10% must be added and shown separately to your total order (inclusive Post/packing). Help us to help you receive your order without delay.

Henry's RADIO LIMITED
EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open: 9 am-6 pm
6 days a week
(309 closed Thursday)
All stores open all day Saturday

RADIO... ELECTRONICS... INSTRUMENTS... AUDIO...

practical WIRELESS


50p

Australia 95c
New Zealand 95c
South Africa 90c
Malaysia \$2.75

JULY 1979

VMOS

TOP BAND TRANSMITTER

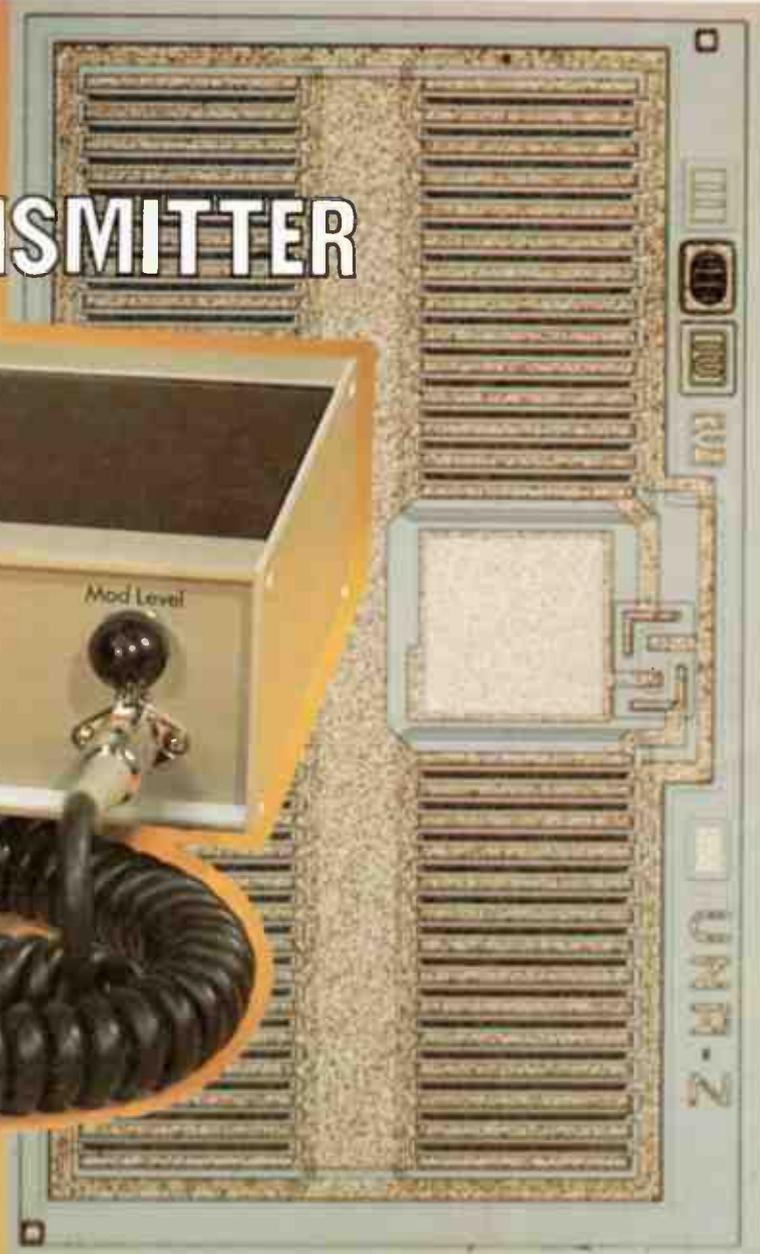

also:



AM/FM FREQUENCY READOUT

&

THE YAESU FRG-7 RECEIVER REVIEWED

TTL			
7400	10p	74109	25p
7401	10p	74118	75p
7402	10p	74120	20p
7403	10p	74121	25p
7404	12p	74122	35p
7405	12p	74123	40p
7406	25p	74125	35p
7407	25p	74126	35p
7408	12p	74128	60p
7409	12p	74130	120p
7410	12p	74131	90p
7411	15p	74132	45p
7412	15p	74135	90p
7413	25p	74136	80p
7414	25p	74137	90p
7415	25p	74138	100p
7416	25p	74141	50p
7417	25p	74142	180p
7418	25p	74143	270p
7419	25p	74144	270p
7420	25p	74145	55p
7421	25p	74147	100p
7422	25p	74148	90p
7423	25p	74150	65p
7424	25p	74151	45p
7425	25p	74153	45p
7426	25p	74154	70p
7427	25p	74155	45p
7428	25p	74156	45p
7429	25p	74157	45p
7430	25p	74158	45p
7431	25p	74159	45p
7432	25p	74160	55p
7433	25p	74161	55p
7434	25p	74162	55p
7435	25p	74163	55p
7436	25p	74164	55p
7437	25p	74165	55p
7438	25p	74166	75p
7439	25p	74167	160p
7440	25p	74168	100p
7441	25p	74169	100p
7442	25p	74170	100p
7443	25p	74171	100p
7444	25p	74172	100p
7445	25p	74173	100p
7446	25p	74174	60p
7447	25p	74175	60p
7448	25p	74176	60p
7449	25p	74177	50p
7450	25p	74178	75p
7451	25p	74179	120p
7452	25p	74180	90p
7453	25p	74181	130p
7454	25p	74182	50p
7455	25p	74183	120p
7456	25p	74184	100p
7457	25p	74185	320p
7458	25p	74186	100p
7459	25p	74187	100p
7460	25p	74188	100p
7461	25p	74189	100p
7462	25p	74190	100p
7463	25p	74191	70p
7464	25p	74192	60p
7465	25p	74193	60p
7466	25p	74194	55p
7467	25p	74195	50p
7468	25p	74196	50p
7469	25p	74197	50p
7470	25p	74198	100p
7471	25p	74199	100p
7472	25p	74200	100p
7473	25p	74201	100p
7474	25p	74202	100p
7475	25p	74203	100p
7476	25p	74204	100p
7477	25p	74205	100p
7478	25p	74206	100p
7479	25p	74207	100p
7480	25p	74208	100p
7481	25p	74209	100p
7482	25p	74210	100p
7483	25p	74211	100p
7484	25p	74212	100p
7485	25p	74213	100p
7486	25p	74214	100p
7487	25p	74215	100p
7488	25p	74216	100p
7489	25p	74217	100p
7490	25p	74218	100p
7491	25p	74219	100p
7492	25p	74220	100p
7493	25p	74221	100p
7494	25p	74222	100p
7495	25p	74223	100p
7496	25p	74224	100p
7497	25p	74225	100p
7498	25p	74226	100p
7499	25p	74227	100p
7500	25p	74228	100p

POWER SUPPLY CAPACITORS			
2200/16	35p	4700/63	120p
2200/16	80p	4700/70	135p
2200/100	150p	10000/10	100p
3300/30	50p	10000/25	150p
3300/63	90p	15000/15	150p
4700/25	50p	22000/25	200p
4700/40	65p		

ENQUIRIES FOR ANY OTHER TYPES

CMOS			
4000	12p	4047	80p
4001	12p	4048	50p
4002	12p	4049	25p
4006	80p	4050	25p
4007	14p	4054	100p
4009	30p	4055	130p
4011	12p	4056	120p
4012	12p	4057	100p
4013	30p	4058	35p
4015	50p	4069	12p
4016	30p	4070	12p
4017	50p	4071	12p
4018	55p	4072	12p
4019	40p	4081	12p
4020	50p	4082	12p
4022	50p	4093	70p
4023	12p	4510	60p
4024	40p	4511	70p
4025	12p	4516	65p
4026	80p	4518	65p
4027	30p	4520	65p
4028	45p	4528	80p
4029	50p	4583	70p
4030	30p		
4032	80p		
4033	100p		
4040	60p		
4043	60p		
4046	90p		

FERRITE RINGS
O/D 12mm, I/D 6mm
10 for 70p

TOGGLE SWITCHES
SUB MIN
Single Pole C.O. 85p
Single Pole C.O. Biased 85p

RESISTORS 1/3RDW
100 of 1 type £1.00p E12 only

LINEAR			
AY38500	450p	NE556	90p
CA3039	70p	NE562B	400p
CA3066	60p	SAD1024	1500p
CA3080	225p	SL917B	65p
CA3085	200p	SN76033N	150p
CA3076	250p	SN76013N	110p
CA3080	75p	SN76013ND	125p
CA3084	250p	SN76023N	110p
CA3085	85p	SN76023ND	125p
CA3086	60p	SN76033N	150p
CA3088	190p	SN76227N	160p
CA3088	160p	SN766228N	180p
CA3090A	360p	SN76662DN	75p
CA3123E	130p	TAA300	100p
CA3130	100p	TAA350	190p
CA3140	60p	TAA550	35p
LF357	80p	TAA570	220p
LM211H	250p	TAA700	350p
LM300T/RS	170p	TAA790	350p
LM301AN	30p	TAD100	150p
LM304	200p	TAD110	130p
LM307N	65p	TBA120S	60p
LM308T/OS	100p	TBA480Q	200p
LM309K	100p	TBA520Q	200p
LM310T/OS	150p	TBA530Q	200p
LM311T/OS	150p	TBA540	200p
LM317K	325p	TBA550Q	250p
LM324	70p	TBA560Q	250p
LM339	60p	TBA641A12	
LM348N	90p	TBA700	250p
LM380	60p	TBA720Q	225p
LM381N	90p	TBA750Q	200p
LM382	90p	TBA800	80p
LM391	180p	TBA810	100p
LM355	25p	TBA820	100p
LM709C	40p	TBA920Q	280p
LM710T/OS	65p	TCA270Q	220p
LM710DIL	60p	TCA270S	220p
LM723T/OS	40p	TCA760S	300p
LM723DIL	40p	TCA4500A	80p
LM733	120p	TDA1008	300p
LM741	20p	TDA1034	45p
LM748	40p	TDA2002	300p
LM1303N	100p	TDA2002	300p
LM1458	100p	TL084	120p
LM3080	75p	XR200	250p
LM3900	55p	XR2206	450p
LM3909N	65p	XR2207	450p
MC1310P	140p	XR2208	600p
MC1312P	150p	XR2216	650p
MC1314P	190p	XR2567	250p
MC1315P	230p	XR4136	150p
MK50398	650p	XR4202	150p
MM5314	380p	XR4212	150p
MM5316	480p	XR4739	150p
NE529K	15p	YN414	100p
NE555	25p	95H90	70p

ELEC CAPACITORS			
0.47/25	7p	47/10	8p
1/16	7p	47/16	8p
1/25	7p	47/25	8p
1/50	7p	47/35	8p
2/25	7p	47/50	8p
2/35	7p	100/10	8p
3/25	7p	100/16	8p
4/7/10	7p	100/25	8p
4/7/16	7p	100/50	8p
4/7/25	7p	100/63	8p
4/7/50	7p	220/16	12p
6/8/25	7p	220/25	14p
10/10	7p	220/50	22p
10/16	7p	330/25	17p
10/25	7p	330/35	17p
10/50	7p	330/50	20p
22/6/3	7p	470/10	14p
22/10	7p	470/25	19p
22/16	7p	470/35	22p
22/25	7p	470/50	24p
22/35	7p	1000/16	27p
22/50	7p	1000/25	30p
33/6/3	7p	1000/35	35p
33/16	7p	1000/40	40p
33/25	7p	1000/63	50p
33/40	7p	1200/63	60p
33/50	7p	2200/10	30p

POLY CAPS			
1000 PF	5p	0.1 uF	6p
2200	5p	0.22 uF	7p
3300	5p	0.33 uF	7p
4700	5p	0.47 uF	12p
6800	5p	1.0 uF	20p
0.01 uF	5p	2.2 uF	25p
0.022 uF	5p	4.7 uF	35p
0.033 uF	5p	6.8 uF	40p
0.047 uF	5p	10 uF	60p

TANT. BEADS			
0.1/35V	14p	3/16V	14p
0.15/35V	14p	4/7/16V	14p
0.22/35V	14p	4/7/25V	14p
0.33/35V	14p	4/7/35V	14p
0.47/10V	14p	6/8/5V	14p
0.68/35V	14p	1.0/35V	14p
1.0/10V	14p	22/15V	21p
1.0/35V	14p	33/16	25p
1.5/35V	14p	47/3V	28p
2.2/25V	14p	47/16V	25p
2.2/35V	14p	100/3V	25p

SPECIAL OFFER
2000uF 35v 40p 100/£30

REED INSERTS One Price
26MM Long 10 for £1.00p
50MM Long 10 for £1.00p

TRANSISTORS			
AA113	10p	BC171	12p
AA217	30p	BC172	12p
AC121	30p	BC177	15p
AC126	20p	BC178	15p
AC127	20p	BC182	10p
AC127/01	25p	BC182L	12p
AC128	20p	BC183	10p
AC151	25p	BC183L	12p
AC153	30p	BC184	10p
AC153K	40p	BC184L	12p
AC154	30p	BC204	12p
AC187	20p	BC205	12p
AC188	20p	BC207	12p
AC191	35p	BC212	11p
AC192	35p	BC212L	12p
AC193	35p	BC213	15p
AC194	35p	BC213L	15p
AC195	35p	BC214	15p
AC196	35p	BC214L	18p
AD130	150p	BC237	10p
AD143	150p	BC237B	15p
AD149	80p	BC294	30p
AD161	30p	BC300	25p
AD162	30p	BC301	25p
AD161/2MP	70p	BC303	30p
AF114	25p	BC307	15p
AF115	25p	BC317	15p
AF116	25p	BC318	12p
AF118	80p	BC323	30p
AF178	95p	BC328	18p
AF139	35p	BC337	20p
AF239	45p	BC338	18p
AF239	50p	BC348	20p
AU110	180p	BC461	35p
BA114	12p	BC516	35p
BA121	12p	BC517	35p
BA154	12p	BC547	12p
BA157	15p	BC548	12p
BA173	15p	BC548</	

practical WIRELESS

JULY 1979
VOLUME 55
NUMBER 7
ISSUE 869

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components are usually available from advertisers. A source will be suggested for difficult items.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.60 per annum, from "Practical Wireless" Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 75p each, including post and packing to addresses at home and overseas.

Binders are available (Price £2.85 to UK addresses or £3.45 overseas, including post and packing) each accommodating one volume of *PW*. Please state year and volume number for which the binder is required.

Send your orders to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

COPYRIGHT

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

NEWS & VIEWS

- 20 **Editorial**
Opinion
- 20 **PW Personality**
Charles Molloy
- 21, 31 **News . . . News . . . News . . .**
- 27 **Special Product Report**
Logic Probe kit, Continental Specialties Corporation
- 30 **RAE Reprint Announcement**
- 32 **Production Lines** Alan Martin
Information on the latest products
- 52 **Kindly Note**
PW "Imp" Beginners Receiver, May 1979
- 55 **Radio Special Product Report**
FRG-7 Communications Receiver, Yaesu Musen
- 61 **Hotlines** Ginsberg
Recent developments in electronics

FOR OUR CONSTRUCTORS

- 22 **AM/FM Frequency Readout** William Poel
Do away with mechanical tuning-scale drives
- 28 **Ideas Department**
Workbench Amplifier. Tachometer/Dwell Meter. TTL Snap Indicator
- 38 **Selective Sound Operated Switch** C. R. Harris
Control equipment with a hand-clap
- 44 **VMOS Top Band Transmitter** J. R. Green
A design for the 160m band, using power f.e.t.s
- 62 **Inexpensive AF Electronic Voltmeter** M. Tooley
A high-impedance, wide-band instrument

GENERAL INTEREST

- 34 **Numbers Without Tears** Dr G. Brown
An educational toy for children of 2½ years and upwards
- 50 **Changes in Broadcast-Band Listening on Short Waves**
A look at the international broadcasting scene Jonathan Marks
- 66 **On the Air**
Amateur Bands Eric Dowdeswell
MW Broadcast Bands Charles Molloy
SW Broadcast Bands Charles Molloy
VHF Bands Ron Ham
VHF Personality — John Tye Ron Ham

We regret that Part 2 of the PW "Trent" has had to be held over, due to production difficulties


OUR COVER
The object looking rather like a ventilation grille is in fact a much-enlarged view of the "works" of a power f.e.t. Photograph courtesy Siliconix Ltd.

Our August issue will be published on 6 July
(for details see page 43)

The latest kit innovation!

from Sparkrite

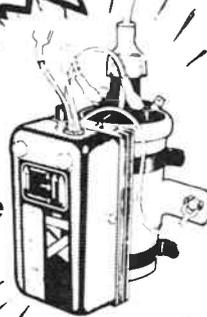Sparkrite - was featured by Shaw Taylor in "DRIVE IN"



the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1-3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light systems function light, and security changeover switch. All kits fit vehicles with coil distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE: Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT post & packing.
Electronic Design Associates, 82 Bath Street, Walsall, WS1 30E U.K. only

Electronics Design Associates, Dept. PW7
82 Bath Street, Walsall, WS1 30E. Phone: (9) 614791

Name
Address

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D

Send SAE if brochure only required

I enclose cheque PO's for

X4 KIT £16.65

TACHOPULSE SLAVE UNIT £3.85

£

Cheque No

Please state polarity pos. or neg. earth
Access or Barclaycard No

VALVES

A1065	1.40	EF80	0.45	PC900	1.40	U25	1.15	SB/255M	0.45	6J7	0.80	1963	0.75
AR8	0.70	EF83	1.70	PC984	0.75	U26	0.95	SB/258M	0.45	6J7G	0.80	1966	18.15
ARP3	0.70	EF84	2.25	PC989	0.85	U27	1.15	SR4GY	1.25	6K7	0.45	19H5	0.70
ATP4	0.60	EF86	0.85	PCF80	0.90	U281	0.80	SU4G	1.05	6K7G	0.85	20J1	0.70
812H	3.35	EF91	0.70	PCF82	0.45	U301	0.60	SV2	0.75	6K8GT	0.75	21F2	1.15
CV31	0.60	EF92	1.00	PCF84	0.75	U801	0.90	SY3GT	0.75	6L6M	1.05	20P1	0.45
DAF98	0.70	EF95	2.95	PCF86	0.75	U8C80	0.70	SZ4G	0.80	6L7G	0.75	20P3	1.25
DET22	21.95	EF98	1.40	PCF200	1.05	UAF42	0.85	SZ4GT	0.85	6L18	0.70	20P4	1.15
DF90	0.70	EF184		PCF201	1.05	UBF87	0.85	6D20	0.70	6D20	0.85	20P5	0.80
DK96	1.05	EF804		PCF801	1.05	UBF89	0.80	6A7	0.70	607G	0.85	25L6GT	0.70
DH76	0.90	EFL200		PCF802	0.75	UBL1	1.15	6AH6	0.80	6SA7	0.85	25Z4G	1.15
DL92	0.60	EH90		PCF805	2.05	UBL21	0.85	6AX5	0.85	6SG7	0.80	30C15	1.25
DY88/87	0.85	EL32		PCF806	0.95	UCC84	0.70	6AX8	0.45	6SJ7	0.80	30C17	1.15
DY802	0.65	EF384		PCF808	2.05	UCG35	0.80	6AL5	0.45	6SJ7GT	0.70	30C18 see	
ES1	0.45	EL37		PCH200	0.90	UCF80	0.80	6ALSW	0.75	6SK7	0.85	30C18	1.15
E88 CC01	1.50	EL38	4.50	PCL81	0.70	UCH81	0.70	6AM5	1.80	6SL7GT	0.85	30F5	1.35
		EL41	0.90	PCL82	0.75	UCL82	0.85	6AM6	0.75	6SN7GT	0.85	30F12	1.35
		EL41	0.90	PCL84	0.80	UF41	1.00	6AN8	0.95	6S07	0.90	30F12	2.05
E180CC	1.50	EL81	1.20	PCL86	0.80	UF80	0.55	6AQ5	1.45	6V6GT	0.70	30FL14	1.15
E180E	0.75	EL82	0.70	PCL805/85	0.85	UL41	0.85	6AQ5W	0.95	6X4	0.85	30FL15	1.15
E182CC	0.95	EL84	0.80			0.85	0.85	6AS6	0.90	6X5GT	1.10	30L17	1.15
EA76	2.25	EL86	1.05	PD500	3.85	UL84	0.85	6AT6	0.85	6Y6G	0.75	30P12	1.15
EABC80	0.60	EL90	1.45	PFL200	2.80	UM80	0.70	6AU6	0.45	6Z4	1.95	30P13	1.25
EB91	0.45	EL91	1.80	PL36	0.90	UM84	0.45	6AV6	0.60	6-30L2	0.90	30P13	1.25
EB93	1.15	EL95	0.80	PL81	0.85	UY82	0.85	6AX4GT	0.90	787	0.90	30P14	1.15
EBF80	0.60	EL504	0.90	PL82	0.80	UY85	0.80	6B7	1.15	714	0.75	35L6GT	0.80
EBF83	0.80	EL802	0.80	PL83	0.80	VR105/30	2.05	6B6	0.60	10C2	0.70	50C5G	0.80
EBF89	0.60	EL822	5.05	PL84	0.75	VR150/30	1.40	6B7A	0.70	11E2	0.70	75C1	0.85
EC52	0.45	EM31	0.85	PL504	1.80	Z66	1.05	6R87	2.80	12A6	0.55	76	0.85
ECC81	0.85	EM80	0.70	PL508	1.50	X61M	1.70	6BW6	3.10	12AT6	0.65	78	2.50
ECC82	0.80	EM81	0.70	PL509	3.65	Z800U	3.40	6BW7	1.15	12AT7	0.60	80	12.40
ECC83	0.85	EM84	0.45	PL802	3.15	Z801U	3.90	6C4	0.45	12AU7	0.80	65A2	0.75
ECC85	0.60	EM87	1.15	PLL80	3.40	Z800T	1.70	6C6	0.85	12AV6	0.80	73A2B	20.25
ECC86	1.40	EY81	0.55	PL33	0.70	1A3	0.70	6CH6	5.05	12AV6	0.80	80P5	0.80
ECC88	0.70	EY86/87	0.85	PY80	0.70	1L4	0.40	6CL6	1.70	12BA6	0.70	805	11.80
ECC189	0.90	EY88	0.85	PY81/800	0.85	1R5	0.65	6CY5	1.00	12BE6	0.70	807	12.40
ECF80	0.60	EZ80	0.55	PY82	0.55	1S4	0.45	6D6	0.85	12BM7	0.65	813	5.05
ECF82	0.55	EZ81	0.70	PY83	0.60	1S5	0.45	6E8A	0.90	12C8	0.80	829B	3.15
ECF801	0.90	GYS01	1.05	PY88	0.75	1T4	0.45	6F6G8	0.85	12E1	0.85	832A	0.75
ECH34	1.15	G232	0.75	PY80	0.70	114	0.40	6F86	0.75	12J5GT	0.70	866A	0.60
ECH35	1.70	G233	3.95	PY85	1.50	1U4	0.70	6F96	1.25	6F12	0.90	931A	0.55
ECH42	0.95	G234	2.25	PY80	0.70	114	0.40	6G16	1.70	6F14	0.70	12K8GT	0.80
ECH43	0.55	G237	2.80	PY85	1.50	1U4	0.70	6G16	1.70	6F14	0.70	12K8GT	0.80
ECH84	1.15	KT66	5.85	PY801	0.70	2021	0.65	6F14	0.70	6F15	1.15	12Q7GT	0.85
ECL80	0.70	KT88	6.45	QDV03-10	2.80	2K25	12.40	6F15	1.15	12Q7GT	0.85	955	1.00
ECL82	0.65	MH4	1.15	QDV03-12	2.80	2K2	0.90	6F17	1.00	12SC7	0.80	956	1.15
ECL83	1.40	ML6	1.15	WV0V6-40A	3.84	0.70	6F24	4.75	12SH7	0.85	957	0.80	
ECL85	0.75	D4	0.85	PS500	1.50	1U4	0.70	6F86	0.75	12SJ6T	0.70	866A	0.60
ECL86	0.85	D82	0.70	QV03-12	2.80	3021	22.50	6H6	1.95	12S7J	0.85	1625	2.00
EF37A	1.70	PABC80	0.60	SC1400	4.50	3E29	6.20	6J4WA	0.85	12Y4	0.70	2051	3.35
EF39	3.30	PC85	0.80	SC1600	4.50	3S4	0.60	6J5	0.85	12D6	1.15	5763	3.40
EF40	0.80	PC86	0.95	SP61	0.95	3V4	0.95	6J5GT	0.80	14S7	0.85	5842	0.95
EF41	0.85	PC88	0.85	TT21	11.80	5B/254M	0.45	6J6	0.85	19A05	11.25	5933	0.95

VAT. INCLUDED

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free. minimum order £1.
A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavailable.

VALVES AND TRANSISTORS
Telephone enquiries for valves, transistors, etc.; retail 749 3934, trade and export 743 0899.

COLOMOR 907353/
(ELECTRONICS) LTD. London
170 Goldhawk Rd., London W.12
Tel. 01-743 0899
Open Monday to Friday
9-12.30, 1.30-5.30 p.m.

Now, complete your system!



Citirone MM313 Mixer

Ideal for the DIY enthusiast looking up a complete disco system 4 in 6 ch mono inc. LED indicators, connections via phono sockets at rear. Bargain price, including PSU EB4 24

The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor 12" or 15" Bass speakers and Dual Concentrics Exponential horns from £13.77, or our fabulous Piezo Horns which handle a 5K-20K frequency range in any PA system up to 100W (No X over required) and cost only £6.18 each




Projectors

Come and see our specially selected projectors from £22.12 (Square Multi-flet 150) to £94.50 (Tutor 11E) plus the widest array of projector attachment and effects that you'll ever see on continuous demonstration



Ropelights

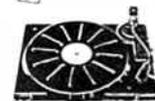Great effect at discos. 7 metres long. Multway connectors 4 channel £43.20 (inc. pack of spare bulbs)



Turntables

Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSR P200 belt drive ONLY £28.12

Bulgin Octal plugs and sockets

There's always hundreds of Bulgin Octal multway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.65 P551 PLUG £1.94

Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES

Multway Cables
4 core (6A) 59p/metre
5 core (6A) 73p/metre
6 core (6A) 86p/metre

Roger Squire's
ALL SHOPS OPEN TUE-SAT LATE NIGHT WED. (UP TO 8 PM)

PERSONAL CALLERS ONLY

176 Junction Road, N19 5QW's Trafalgar Park Tube Station. (Near St. George's 1 mile from end of M32)

251 Deansgate 3. 15 mins from City Centre
Margaret Drive Kelowna 20, just behind the BBC.
Tel: 041 946 3303

LONDON
BRISTOL
MANCHESTER
GLASGOW

125 Church Road, Redditch (Near St. George's 1 mile from end of M32)
Tel: 0272 550550

251 Deansgate 3. 15 mins from City Centre
Tel: 061 831 7676

1 Queen Margaret Road (off Great
Tel: 041 946 3303

RADIO EXCHANGE LIMITED

NEW ELECTRONIC MASTER KIT



With special V.H.F. Tuner Module to construct. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws, etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeving, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive Instruction Manual Pictorial and Circuit Diagrams.

Projects:
 V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster.

£14.99 + P & P £1.10

V.H.F. AIR CONVERTER KIT




Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome-plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. Size 5½" x 1½" x 3¼". All parts including case and plans.

£4.95 + P & P and Ins. 60p

ELECTRONIC CONSTRUCTION KIT E.C.K. 2

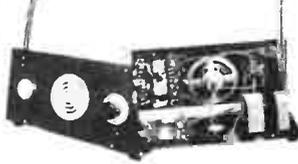

Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 2½ in. loudspeaker. gain control, 7 section chrome-plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P.7 battery (not supplied with kit).

Complete kit of parts

£7.95 + P & P and Ins. 90p


NEW MODEL R.K.1.



MultiBand A.M. Receiver. M.W.L.W. Trawler Band and Three Short Wave Bands. Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.

£8.99 + P & P 90p

EDU-KIT JUNIOR

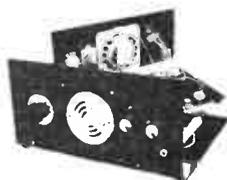

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

All parts including Loudspeaker, Earpiece, M.W. Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6.95 + P & P and Ins. 90p

NEW ROAMER TEN MODEL R.K.3.



Multiband V.H.F. and A.M. Receiver. 13 Transistors and Six Diodes. Quality Loudspeaker

With Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with separate Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome-plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Powered by P.P.9-9 volt Battery.

Complete kit of parts including carrying strap. Building Instructions and operating Manuals.

£14.79 + P & P £1.10

E.V.6 PLUS ONE




Build this exciting new design. Now with 7 Transistors and 4 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and 2½ in. loudspeaker. Attractive case with speaker grille. Size 9 in. x 5½ in. x 2½ in. approx. All parts including Case and Plans.

Total Building Costs:

£6.95 + P & P and Ins. 90p

EDU-KIT MAJOR

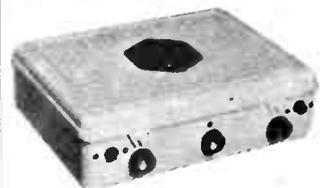

Completely solderless Electronic Construction Kit. Build fifteen projects including:—
 ● Signal Injector ● Transistor Tester NPN-PNP ● 7 Transistor Loudspeaker Radio MW/LW ● 5 Transistor Short Wave Radio.

Components include:

- 24 Resistors ● 21 Capacitors
 - 10 Transistors ● 5" x 3" Loudspeaker ● Earpiece ● Mica Baseboard ● 3 12-way Connectors
 - 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser
 - 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc.
- Complete kit of parts including construction plans.

Total building costs:

£9.99 + P & P and Ins. £1.10

RADIO CONSTRUCTION KIT Q7



A compact small radio kit covering Medium Wave and Long Wave bands. Rugged Micanite construction and simple square design allows for easy carrying and positioning. Ideal for the Garage, Workroom, Kitchen, etc., has seven Transistors and four Diodes, quality Loudspeaker, ready wound Ferrite Rod Aerial and Carrying Strap. Size 4½" x 4½" x 4½". All parts and plans excluding 9v PP7 Battery.

£6.25 + P & P and Ins. 75p

POCKET FIVE



NOW WITH 2½" LOUDSPEAKER 3 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. All Parts including Case and Plans.

Total Building Costs

£4.95 + P & P and Ins. 80p

To: RADIO EXCHANGE LTD

61A High Street, Bedford MK40 ISA

Tel.: 0234 52367

- Callers side entrance "Lavelis" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

Reg. No. 788372

I enclose £..... for.....

Name

Address

PW779

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE


R.C.S. LOUDSPEAKER BARGAINS
 3 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 8 x 5in. £2-50. 5in. £1-50.
 6 1/2in. £1-80. 8in. £2-60. 10in. £3. 12in. £4.
 8 ohm. 2 1/2in. £1-50. 3in. £1-50. 5in. £1-50. 10in. £3. 12in. £4.
 16 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 5in. £1-50. 8in. £2-60.
 10in. £3. 12in. £4. 10 x 6in. £3-50.

THE "INSTANT" BULK TAPE ERASER
 Suitable for cassettes, and all sizes of tape reels.
 A.C. mains 200/249V.
 Leaflet S.A.E. **£5-50** Post 50p



HEAD DEMAGNETISER PROBE £4-75

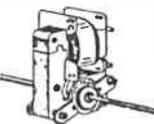A.C. ELECTRIC MOTORS
 2 Pole, 240V, .2 Amp. Spindle — 1.43 x 0.212in. £1-75. 2 pole, 240V, .15 Amp. Double spindle — 1.75 x 0.16in. Each £1-50. 2 Pole, 120V, .5 Amp. Spindle — 0.75 x 0.2in. Two in series = 240V. 75p each. Brush Motor. From a Food Mixer 240V, .3 Amp. High Speed and Powerful. Spindle — 0.5 x 0.25in. £2-95 Post 50p each.



BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides, 6 x 4in. 95p; 8 x 6in. £1-40; 10 x 7in. £1-55; 14 x 9in. £1-90; 16 x 6in. £1-85; 12 x 3in. £1-20; 16 x 10in. £2-20; 12 x 8in. £1-70.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 44p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1; 16 x 10in. £1-16.

ALUMINIUM ANGLE BRACKET 6 x 1/2 x 1/2in. 20p.
ALUMINIUM BOXES, MANY SIZES IN STOCK
 4 x 2 x 2in. 80p; 3 x 2 x 1in. 60p; 6 x 4 x 2in. £1; 8 x 6 x 3in. £1-90; 12 x 5 x 3in. £2; 6 x 4 x 4in. £1-30. 10 x 7 x 3in. £2-20.

DE LUXE BSR HI-FI AUTOCHANGER
 Plays 12in. 10in. or 7in. records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in.
 With **CERAMIC STEREO CARTRIDGE**
 Garrard 2025 Autochanger with ceramic cartridge. **£14-95**
 Garrard Minichanger. Plays all size records. Ceramic cartridge. Stereo. **£8-95**
 BSR. P182. Snake arm, flared Aluminium Turntable. Stereo ceramic cartridge. Latest model. **£22-50**
 BSR. Disco Single Player Cueing Device 1in. Turntable. Budget price. **£19-50**
 RSC Disco Deck 3 speed Stereo **£8 or £15 pair**



BAKER 50 WATT AMPLIFIER £59 Post £1



Superior quality ideal for Halls/PA systems, Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 150 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet.

BAKER 150 Watt AMPLIFIER 4 inputs £79.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. Post 35p **£3-25**


STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. board. Can be ganged to make multi-way stereo mixers. Post 35p **£2-95**

R.C.S. SOUND TO LIGHT DISPLAY MK 2
 Complete kit of parts with R.C.S. printed circuit. Three channels. Upto 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi and all Disco Amplifiers. Cabinet extra £4. **£17**

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4, or 12 for £7-50.

MAINS TRANSFORMERS Post 75p
 6 VOLT 1/2 AMP. £1-00 3 AMP. £1-95 9 VOLT 3 AMP. £2-75
 12 VOLT 300 MA. £1-00 750 MA. £1-30 20 VOLT 2 AMP. £2-50
 30 VOLT 5 AMP. AND 34 VOLT 2 AMP. C.T. £3-45
 20 VOLT 1 AMP. £2-00 20-0-20 VOLT 1 AMP. £2-95
 30 VOLT 1 1/2 AMP. £2-75 40 VOLT 2 AMP. £2-95 30V 2 AMP. £3
 0-20-40-60 VOLT 1 AMP. £3-50 2 x 18 VOLT 6 AMP. £9.
 Low Voltage 0-8-12V. 2 AMP. £3.
 Low Voltage 12-0-12V. 2 AMP. £3.
 GENERAL PURPOSE LOW VOLTAGE Voltages available at
 2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V. **£5-80**
 1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£5-80**
 2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8-50**
 3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11-00**
 5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£14-50**

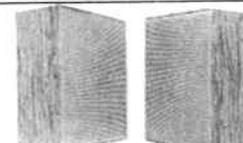R.C.S. TEAK COMPACT SPEAKERS
 13 x 10 x 6in.
 50 to 14,000 cps.
 10 watts. 4 or 8 ohms.
£16 pair Post £1-50



BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "35" **£14-00**
 12in. 40 watt
 4, 8 or 16 ohms.

GROUP "50/12" **£21-00**
 12in. 60 watt professional model. 4, 8 or 16 ohms.
 Response 30 — 16,000 cps.
 With aluminium presence dome.

GROUP "50/15" **£33-00**
 15in. 75 watt
 8 or 16 ohms.
 Send for leaflets on Disco, P.A. and Group Gear.



E.M.J. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. 10W. State 3 or 8 ohm. **£8-95**


15W model 8 ohms Bass unit only. **£10-50**

GOODMANS 20 Watt Woofer Size 12 x 10in. 4 ohms. Rubber cone surround. **£9-95**

GOODMANS TWIN AXIOM 8 8in. 8 ohm Hi-Fi Twin Cone Special unit **£9-95**



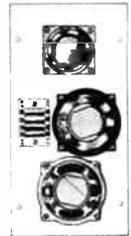R.C.S. MINI MODULE HI-FI KIT 15 x 8 1/2in 3-way Loudspeaker System, EMI 5in, Bass 5in, Middle 3in. Tweeter with 3-way Crossover and Ready Cut Baffle. Full assembly instructions supplied. Response = 60 to 20,000cps 12 watt RMS. 8 ohm. £10.95 per kit. Two kits £20. Postage 75p. One or two kits.



RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Minimum post 30p. Components List 20p. Phone orders. Access & Barclay VISA only. Open 9—6 Sat. 9—5 (Closed all day Wednesday) Tel. 01-684 1665

MAIL ORDER DEPT.

CRESCENT RADIO LTD

1 ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4SJ. 01-888 3206



"FLIP" PUSH BUTTON HEADS OR TAILS
 Complete kit and full instructions supplied. A pocket game, easy to build and great to play. **KIT PRICE = £5-25 + 8% VAT.** Post free.

75 OHM 2 1/2" (57mm) LOUDSPEAKER BARGAIN
 This ever popular many project loudspeaker. Only white stocks last 90p + 12 1/2% each.

REAR SHELF CAR SPEAKERS
 5W 8 ohm good quality car stereo loudspeakers. Still only £3-75 + 12 1/2% per pair.

HEAVY DUTY XOVER 2 WAY 8 OHM
 A 2 way 8 ohm H/D Xover suitable for US systems up to 100 watt. Fitted with screw terminals for input and a three position 'HF LEVEL' switch which selects either Flat, -3dB or -6dB. **ONLY £3-00 + 8% VAT**

A CRESCENT 'SUPERBU' Goodmans 5" 8 ohm long throw H/D loudspeaker.
 Mounting plate is integral with US chassis and has fixing holes with centres spaced at 5 1/2" (diagonally). **ONLY £5-00 + 12 1/2% VAT**

CR. 3000. SCREWDRIVER SET **£1-75p.** + 8% VAT

In neat plastic case. Consists of: awl, jewellers screwdriver, watchmaker's screwdriver, radio screwdriver, phillips screwdriver. All fit into master swivelling handle.

CR. 4110. DESOLDERING PUMP **ONLY £6** + 8% VAT

High suction pump with automatic ejection. Knurled, anti corrosive casing. Teflon nozzle.

CR. LV1. 12v DRILL **£12-00p.** + 8% VAT

BRITISH MADE "Versadrill". 12 volts DC. Compact battery operated power tool, sufficiently powerful to perform all the operations associated with 240v drills. Dimensions:- 150 x 50mm (dia.)

C.180-'KEYNECTOR' MAINS CONNECTOR
 Essential equipment for the showroom, workshop, factory, laboratory, home and hobby bench, the 'Keynector' provides quick, efficient and safe temporary mains connection. **£6-25 + 8% VAT**

FOOTSWITCH C.338
 250v, 5 amp. Non-slip base. Lead with 2.5mm plug. Body dims:- 88 x 66 x 25mm. **£3-75 + 8% VAT**



P & P. Orders up to £5, add 30p. Orders £5-£10, add 50p. All orders over £10 post free! Please add V.A.T. as shown. S.A.E. with all enquiries please.



Personal callers welcome at: 21 Green Lanes, Palmers Green N13. Also 13 South Mall, Edmonton Green, Edmonton.

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Alnalte) Copy of original article supplied on request


IF Sub-Assembly (G8) **£7-65.** P&P 75p.
 Mullard ELC1043 V'cap UHF Tuner **£6-19.** P&P 35p.
 3-way Station Control Unit **£1-35.** P&P 25p.
 6-way Station Control Unit (Special Offer) **£1-12.**
 Power Supply Prtd Circuit Board **£1-12.** P&P 30p.
 Res, Caps, Semiconds, etc. for above **£6-53.**
 Mains Transformer for above **£2-81.** P&P 30p.

(Price of goods includes 12 1/2% VAT) P&P all items 85p.

Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 (Near W. Hampstead Tube Stn.) Tel. 01-794 8751

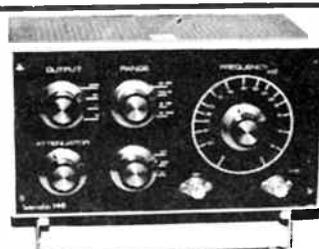

Model 146
VERY LOW DISTORTION (.0015%) AUDIO SIG. GENERATOR
 Based on J. Linsley Hood design (W.W.) **£36-00**
 (Kit. £31-00) + tax 8%

Low cost version, AO113 (.02% dist.) £27-50 (Kit. £23). Other instruments include Millivoltmeter, Tachometer, Noise level meter, Distortion Analyser, F.M. Sig. Gen. Crystal Frequency Standard, KEF Speaker Units. Send S.A.E. for lists. VAT extra 8%. Post/Pkg. £1-50.

TELERADIO ELECTRONICS


325 Fore Street, Edmonton N.9. 01-807 3719
 Closed all day Thursday

THREE FOR FREE FROM CSC

ELECTRONICS BY NUMBERS
FREE PROJECTS
 No 1, No 2,
 & No 3.

ELECTRONICS BY NUMBERS LED BAR GRAPH UNIVERSAL INDICATOR

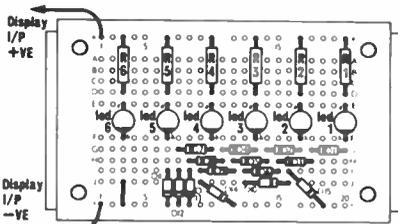Now using **EXPERIMENTOR BREADBOARDS** and following the instructions in "Electronics by numbers" **ANYBODY** can build electronic projects.
 Look at the diagram and select R1, this is a resistor with a value between 120 to 270 ohm. Plug it into holes X20 and D20, now take LED 1 and plug it into holes E20 and F20. Do the same with the Diodes e.g. plug D7 into holes G7 and G10.



YOU WILL NEED

EXP. ANY EXPERIMENTOR BREADBOARD
 D1 to D15 - Silicon Diodes (such as 1N914)
 R1 to R6 - From 120-270 ohm resistors ¼ watt.
 LED1 to LED6 - Light emitting diodes.

LED BAR GRAPHS are replacing analogue meters as voltage-level indicators in many instances.

This circuit uses the forward voltage drop of diodes to determine how many LEDs light up. Any type of diode can be used but you must use all the same type. For full working details of this circuit fill in the coupon.
 If you have already built the Two-transistor Radio and the Fish'n'cliks projects you will find that you can reuse the components from these projects to build other projects in the series.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE FULL COPIES OF "ELECTRONICS BY NUMBERS" PROJECTS No 1, No 2 and No 3.

PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.



- PC - 16 pin. £2.75.
- PC - 16 pin with cable. £6.00.
- PC - 16 with cable and 16 pin clips at both ends. £10.25.




Europe, Africa, Mid-East: CSC UK LTD.
 Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex CB11 3AQ.
 Telephone: SAFFRON WALDEN 21682.
 Telex: 817477.

EXPERIMENTOR BREADBOARDS.


No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


EXP.325. The ideal breadboard for 1 chip circuits.
 Accepts 8,14,16 and up to 22 pin IC's.
ONLY £1.60.

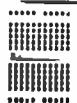


EXP.350. £3.15.
 270 contact points with two 20-point bus-bars.

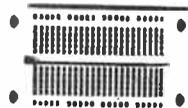

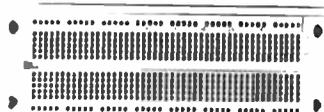
EXP. 300.
 550 contacts with two 40-point bus-bars.
£5.75.



EXP. 650 for Micro-processors. **£3.60.**

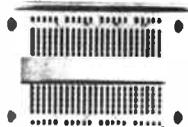


EXP 4B.
 More bus-bars.
£2.30.

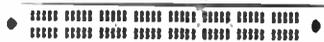


ALL EXP.300 Breadboards mix and match with 600 series.

PROTO-BOARDS.

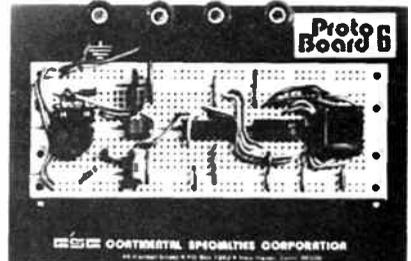THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST.
 TWO EASILY ASSEMBLED KITS.



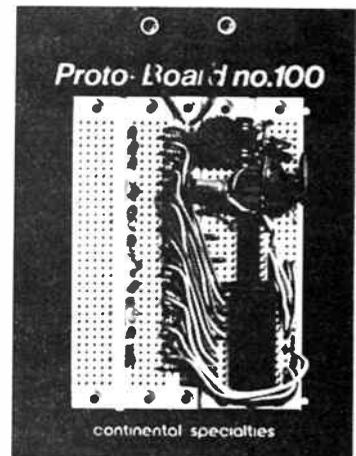PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.
PROTO-BOARD 6 KIT. £9.20.



PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.
PROTO-BOARD 100 KIT £11.80.

HOW TO ORDER AND RECEIVE FREE COPY OF TWO-TRANSISTOR RADIO PROJECT, FISH'N'CLIKS AND LED BAR GRAPH.

CSC UK LTD. Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN,DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T.
EXP. 325	130	1	£ 2.53
EXP. 350	270	3	£ 4.21
EXP. 300	550	6	£ 7.29
EXP. 650	270	use with 0.6 pitch Dip's Bus-Bar Strip	£ 4.69
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.29
TEST CLIPS			
PC. 16.			£ 3.78
PC.16-1B.			£ 7.56
PC. 16-1B Dual Clip			£12.15
PROTO-BOARDS.			
PB. 6.	630	6	£11.01
PB. 100.	760	10	£13.82

NAME

ADDRESS

DEPT. 6T

FILL IN COUPON & RECEIVE FREE COPY OF ELECTRONICS BY NUMBERS PROJECTS Nos 1, 2 AND 3

CHROMASONIC electronics

your soundest connection in the world of components

Dept PW1, 56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

TELEPHONE: 01-883 3705

The items shown in this advert are just a small selection taken from our new 78/79 Catalogue which is now available. It contains everything from Resistors to the latest in Micro-processors. Don't delay order your copy today. The price is only 40p (inc. 45p vouchers).

Low Power Schottky and TTL

CMOS

I.C. cookbooks

BITS and PIECES

Regulators


Linear I.C.'s

7400 13*	19*	7449	—	87*	74136	—	39*	74191 121*	75*	4000 15*	4053 81*	DIL (Texas)	Static RAM's	1+	17-63 64+	78M Series	CA3080	75
7401 13*	19*	7450 16*	—	74139	—	55*	74192 121*	185*	4001 16*	4054 129*	8 pin 18*	2102A	(350ns)	1.05*	95*	88*	CA3130E	90
7402 15*	19*	7451 16*	—	74139	—	55*	74193 121*	185*	4002 16*	4056 148*	14 pin 12*	2102A 2	(650ns)	1.29*	1.15*	1.08*	CA3140E	37
7403 15*	19*	7453 16*	—	74141 76*	—	—	74194 121*	—	4006 92*	4059 518*	16 pin 13*	2111A 1	(500ns)	2.46*	2.19*	2.05*	LM301AN	30
7404 16*	21*	7454 16*	—	74145 75*	105*	74195 101*	105*	—	4007 18*	4060 124*	18 pin 18*	2112A 2	(250ns)	2.14*	1.90*	1.78*	LM324N	73*
7405 16*	21*	7455 16*	—	74147 159*	—	74196 118*	105*	—	4008 92*	4066 48*	20 pin 20*	21102	(350ns)	1.07*	95*	86*	LM348N	99
7406 28*	—	7460 16*	—	74148 132*	—	74197 118*	105*	—	4009 54*	4068 21*	22 pin 24*	MM5257 (TMS4044)	(450ns)	8.10*	7.19*	6.75*	LM380N	97
7407 26*	—	7470 23*	—	74150 102*	—	74198 181*	105*	—	4010 54*	4068 21*	24 pin 26*	2114	(450ns)	8.10*	7.19*	6.75*	LM381N	1.73
7408 17*	19*	7473 23*	—	74151 87*	88*	74199 181*	—	—	4011 18*	4070 21*	28 pin 30*	6810		3.50*	2.97*	2.52*	LM382N	1.33
7410 15*	19*	7474 28*	—	74153 67*	48*	74221	—	—	4012 18*	4071 21*	40 pin 44*	8080	5.95*	—	—	—	LM3900N	65
7411 25*	19*	7475 44*	—	74155 121*	1.25*	74240	—	2.25*	4013 48*	4072 21*	—	8080	8.99*	8.99*	8.99*	—	LM3909N	70*
7412 18*	19*	7476 30*	—	74156 67*	78*	74242	—	2.25*	4014 92*	4077 21*	—	8080	42.50*	—	—	—	SN7601N	1.02
7413 21*	40*	7478	—	74157 67*	55*	74243	—	2.25*	4015 92*	4081 21*	—	8080	42.50*	—	—	—	SN7603N	2.32
7414 71*	79*	7482	—	74158	—	74247	—	—	4016 43*	4082 21*	—	8080	42.50*	—	—	—	SN7603N	1.55
7415	—	7483	—	74160 121*	—	74248	—	—	4017 81*	4085 92*	—	8080	42.50*	—	—	—	SN76023N	1.55
7416 25*	—	7485 1.18*	—	74161 121*	65*	74249	—	—	4018 92*	4086 92*	—	8080	42.50*	—	—	—	TBA810AS	90
7417 34*	—	7486 25*	—	74162 121*	1.25*	74251	—	—	4019 56*	4093 81*	—	8080	42.50*	—	—	—	TCAS40	1.75
7420 16*	19*	7489 2.80*	—	74163 121*	1.65*	74253	—	—	4020 92*	4099 181*	—	8080	42.50*	—	—	—	ZN414	1.90
7421	—	7490 34*	—	74164 102*	1.15*	74257	—	—	4021 92*	4502 92*	—	8080	42.50*	—	—	—	ZN425E	3.78*
7422	—	7491 73*	—	74165	—	74258	—	—	4022 92*	4508 245*	—	8080	42.50*	—	—	—	ZN459CT	3.54
7423 25*	—	7492 46*	—	74166 102*	—	74259	—	—	4023 18*	4510 107*	—	8080	42.50*	—	—	—	ZN103AE	2.03*
7425 25*	—	7493 34*	—	74168	—	74266	—	—	4024 65*	4511 95*	—	8080	42.50*	—	—	—	ZN104OE	8.43*
7426 25*	19*	7495 54*	—	74169	—	74273	—	—	4025 18*	4514 270*	—	8080	42.50*	—	—	—	ZN116E	6.75*
7427 39*	19*	7496 67*	—	74170 185*	1.65*	74279	—	—	4026 184*	4515 270*	—	8080	42.50*	—	—	—	—	—
7428 38*	19*	74107 27*	—	74171 41*	88*	74283	—	—	4027 51*	4516 107*	—	8080	42.50*	—	—	—	—	—
7430 16*	19*	74109 44*	—	74172 101*	1.05*	74290	—	—	4028 70*	4517 410*	—	8080	42.50*	—	—	—	—	—
7432 25*	25*	74112	—	74175 81*	1.05*	74293	—	—	4029 118*	4518 95*	—	8080	42.50*	—	—	—	—	—
7433	—	74113	—	74176 101*	—	74295	—	—	4030 56*	4521 254*	—	8080	42.50*	—	—	—	—	—
7437 25*	25*	74114	—	74177 101*	—	74298	—	—	4031 108*	4522 189*	—	8080	42.50*	—	—	—	—	—
7438 25*	25*	74121 27*	—	74180 101*	—	74365	—	—	4032 189*	4526 189*	—	8080	42.50*	—	—	—	—	—
7440 17*	19*	74122 50*	—	74181 221*	2.99*	74366	—	—	4033 106*	4528 92*	—	8080	42.50*	—	—	—	—	—
7441 70*	—	74123 60*	—	74182 81*	—	74367	—	—	4040 92*	4534 712*	—	8080	42.50*	—	—	—	—	—
7442 50*	55*	74124	—	74184 101*	—	74368	—	—	4042 70*	4536 374*	—	8080	42.50*	—	—	—	—	—
7445 60*	—	74125 51*	—	74185 162*	—	74368	—	—	4043 81*	4543 162*	—	8080	42.50*	—	—	—	—	—
7446 60*	—	74126 51*	—	74186 297*	—	74368	—	—	4046 106*	4553 453*	—	8080	42.50*	—	—	—	—	—
7447 60*	87*	74132 72*	—	74189 317*	2.25*	74370	—	—	4049 43*	4566 151*	—	8080	42.50*	—	—	—	—	—
7448 60*	87*	74133	—	74190 121*	75*	74370	—	—	4050 43*	4583 102*	—	8080	42.50*	—	—	—	—	—
									4051 81*	4585 107*	—	8080	42.50*	—	—	—	—	—
									40F2 81*	4585 107*	—	8080	42.50*	—	—	—	—	—

VAT Inclusive prices *8% others 12.5% Export Customers deduct VAT 2/27 from *1/9 from others

Postage and Packing 25p Trade and Export Inquiries most Welcome. Hours 9.00am - 5.00pm

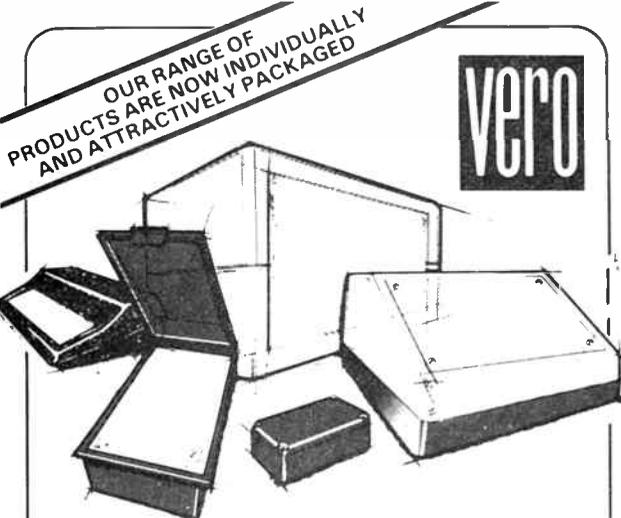Now available our ORDER-RING line, just phone your order through with your Access or Barclaycard number and providing the order is received by 3.00pm the components will be despatched the same day (min tel order £5.00)



OUR RANGE OF PRODUCTS ARE NOW INDIVIDUALLY AND ATTRACTIVELY PACKAGED

Our new catalogue lists a whole range of plastic boxes to house all your projects. And we've got circuit boards, accessories, module systems, and metal cases - everything you need to give your equipment the quality you demand. Send 25p to cover post and packing and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956

SINCLAIR PRODUCTS microvision tv world model £147.95, uk model £89.95, mains adaptor £6.73. PDM35 £28.95, mains adaptor £3.19, case £3.19. DM350 £68.95, DM450 £97.95, DM235 £49.45, rechargeable batts £7.50, mains adaptor £3.70, case £8.45, enterprise prog. calculator with accessories £22.95, cambridge prog. calculator £12.13, prog. library £4.45, mains adaptor £3.20, PFM200 £49.48.

CSC MAX100 freq meter £75.40.

CALSCOPE oscilloscopes send see for data or see the Calscope advert in this magazine. Super 8 £174. Super 10 £236.

COMPUTER GAMES chess challenger 10 £167, chess challenger 7 £79, checker challenger 4 £84, checker challenger 2 £50, Atari videocomputer £138 cartridges £13.45

COMPONENTS send see for full list. 1N4148 14p 1N4002 2 Sp. 741 15p. bc182b, bc183b, bc184b bc212b, bc213b, bc214c 4 Sp. resistors 1/2W 5% £12 10R to 10M 1p, 0.8p for 50p. of one value. 16V electrolytic 1/2/5/10/22uf 5p, 100uf 6p, 1000uf 10p. 1p to 100p £1.13. data pen 79p. 60 sq ins pcb 55p.

TV GAMES send see for data. AY-3-8500 + kit £8.95, rifle kit £4.95, AY-3-8600 + kit £15.70, stunt cycle chip + kit £15.70, tank bottle kit £6.95.

TRANSFORMERS 6-0-6v 100ma 74p, 1 1/2 £2.35, 8 3v 1 1/2 £1.89, 0-0-9v 75ma 74p, 1s £2.2s, £2.80, 12-0-12v 100ma 90p, 1s £2.49

IC AUDIO AMPS with pcb. JC12 6W £1.60, JC20 10W £2.95, send see for data.

BATTERY ELIMINATORS 3-way type 67/79v 300ma £2.95 100ma radio type with pre-studs 9v £3.35, 9v - 9v £4.50, car converter 12v input, output 4 1/2/6/7 1/2 9c 800ma £2.50.

BATTERY ELIMINATOR KITS send see for data. 100ma radio types with pre-studs 4 1/2 £1.40, 6v £1.40, 9v £1.40, 4 1/2 £1.40, 6v £1.40, 9v £1.40, 1 1/2 £1.80, 8-way types 3 1/2/6/7 1/2/15/18v 100ma £2.80, 1amp £8.40, stabilised power kits 2-18v 100ma £2.80, 2-30v 1A £6.95, 2-30v 2a £10.95, 12v car converter 67/79v 1s £1.35

T-DEC AND CSC READBOARDS 1-dec £4.02, u-dec £4.40, u-dec £6.73, a-dec £3.80, exp 300 £6.21, exp350 £3.40, exp325 £1.73, exp4b £2.48

BI-PAK AUDIO MODULES 4550 £23.51, AL60 £4.86, pa100 £16.95, spm90 £4.47, bmt80 £5.95, stereo 30 £20.12, AL40 £3.95, PA12 £7.80, PS12 £1.39, MA60 £35.44

SWANLEY ELECTRONICS
Dept. PW, 32 Goldsall Rd., Swanley, Kent.
Post 30p extra, prices include Vat. Official and overseas orders welcome.

MONOLITH

QUALITY REEL TO REEL & CASSETTE TAPE HEADS

SOME POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01	MONO PLAYBACK	£1.84	E12-09	MONO/STEREO ERASE	£1.80
B12-02	MONO RECORD/PLAYBACK	£3.92	B22-02	TWIN HALF TRACK RECORD/PLBK	£5.82
B24-01	STEREO PLAYBACK	£3.22	C44RPS02	QUAD QUARTER TRACK REC/PLBK	£9.14
B24-02	STEREO RECORD/PLAYBACK	£5.50	C22ES02	TWIN HALF TRACK ERASE	£4.50
B24-RP	STEREO GLASS FERRITE REC/PLBK	£11.32			

MAGNETIC TAPE HEADS CATALOGUE 25 PENCE

AUDIO AND HI FI CATALOGUE (80 PAGE FULL COLOUR) 50 PENCE

MONOLITH

THE MONOLITH ELECTRONICS CO. LTD.
5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0480) 74321


PLEASE ENCLOSE 30p P&P WITH ORDER
ALL PRICES INCLUDE VAT

Tecknowledgedy for sale.

The Mark III FM Tuner

DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £18.62 VAT

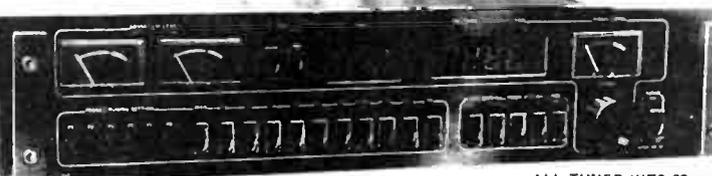With Hyperfi Series modules £185.00 + £23.12



Features of the system

- Precision construction & design of mill parts
- Time frequency display
- State of the art performance with facilities for updates, using modular plug in systems
- Deviation level calibrator for recording
- All usual tuner features

Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/FM stereo

A multiband superhet tuner constructed using a single IC for RF/IF processing but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gap) tuned FET tunerhead, with ceramic IF filters and interstation mute; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.12 VAT
Complete with digital frequency readout/clock timer hardware £99.00 + £12.37 VAT
Complete with MA1023 clock/timer module with dial scale £66.00 + £8.25 VAT

Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

LW/MW/FM LCD Digital Frequency Display July PW feature

Update your old radio, or build this into a new design.

Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RF! - 15.20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz. AM 1kHz. Sensitivities better than 10mV. Complete kit £19.50 + *£1.56 VAT. Built and tested version £24.00 + *£1.92 VAT. Various other DFM systems described in our catalogue part 2, including a one chip solution to providing digital display of FRG7 kHz dial, combined with clock/timers etc.



PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction "Sandbanks". Now with injection molded casing for greatly improved environmental sealing. £37.00 + *£2.96vat.

VHF MONITOR RX WITH PLESSEY IC

4/9 channel version of the PW design - but using standard 3rd OT crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 + £3.90vat.

ETI - REMCON RADIO CONTROL

A tried and tested RC system with a full set of supporting hardware from a well known manufacturer. Please send for details - and watch our ads for further news of developments in RC products.

Radio and Audio Modules - The biggest range/ best specs:

EF5801/3/4 6 stage varicap tunerheads with LO feed and various levels of sophistication. New 5804 include pin AGC loop 'on board'. 5801-£17.45+£2.18vat. 5803-£19.75+£2.47vat. 5804-£24.95+£3.18vat. Frequencies in 40-180MHz on approx.

EF5402 4 stage varicap with TDA1062, compound FET/Bipolar input stage, low noise, balanced mixer, pin. agc, osc output. A worthy successor to the 5400. £10.75+£1.34vat

The 5402 is available centred on a wide range of frequencies from 30MHz to 180MHz. Non standard units £14.75+£1.84. 3 weeks.

8319 4 stage varicap tunerhead from Larsholt using MOSFET RF and mixer stages. New temperature compensated oscillator for wide ranges of ambient temperature £13.45+£1.68vat

7252 Complete Larsholt FM tuner less stereo decoder. £26.50+£3.31vat

7253 Stereo FM tuner from Larsholt with FET head. (as 7252) £94.378 Hyperfi stereo decoder. The very best. £19.95+£2.19vat

911223 Pilot cancel stereo decoder, priced to make the MC1310 as obsolete as it now deserves to be. £12.50+£1.56vat

Intotec 1-A fully DC tuned and switched LW/MW/FM stereo tuner to interface with synthesiser control etc. A first! Details OA.

COMPONENTS for Radio and Audio ICs, HMOS etc.

The list is too long to attempt here, but AMBIT specializes in all types of semiconductor for radio reception, including devices operating from DC to 5GHz. New low cost SBL1 diode ring mixers (equiv case MD108 etc) first with HMOS fets, now with a PCB for DC amplifier, and offset sense and protection relay for speakers. See catalogue and updates for most info, please send an SAE for information on anything you cannot find in catalogues.

Radio ICs	cost + vat	Stereo ICs	cost + vat	AF power ICs	cost + vat
CA3089E	1.94 24	MC1310P	1.50 19	LM380N	1.00 12
CA3189E	2.45 30	uA758	2.20 27	TBA810AS	1.09 14
HA1137W	2.20 27	CA3090A	2.75 34	TDA2002	1.95 24
SN76660	0.75 9	HA1196	3.95 49	TBA820M	0.75 9
TDA1090	3.35 42	HA11223	4.35 54		
TDA1083	1.95 24	KB4437	4.35 54	from the general list:	
TDA1220	1.40 17	KB2224	2.75 34	LEDs: all colours and low prices	
SL6640	2.75 34	Preamp ICs/switches		2S48/2SK 134 HMOS	
MC3357	3.12 39	TDA1028	3.50 44	9.90 + £0.80 vat(Pair)	
HA1197W	1.40 17	TDA1029	3.50 44	Signal fets/transistors and	
MC1496	1.25 16	TDA1074	4.14 52	TOKO COILS & FILTERS!	
LM373/4	3.75 49	KB4438	2.22 28		

OSTS: Remember all OSTS stocks are obtained from BS9000 approved sources your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering

TTL: Standard AND LP Schottky

N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'		
7400	13	20	7455	35	24	74126	57	44	74185	134	74377	124	
7401	13	20	7460	17	74	74128	74	74	74188	275	74378	93	
7402	14	20	7463		124	74132	73	78	74190	115	92	74379	130
7403	14	20	7470	28	74	74133	32	29	74191		74	74368	37
7404	14	24	7472	32	38	74136		40	74192	105	180	74390	140
7405	18	26	7473	32	38	74138		60	74193	105	180	74393	140
7406	38	24	7474	27	38	74139		60	74194	105	180	74395	139
7407	38	24	7475	38	40	74141	56		74195	95	137	74396	133
7408	17	24	7476	37	38	74142	265		74196	99	110	74398	180
7409	17	24	7478		38	74143	312		74197	85	110	74399	150
7410	15	24	7480	48		74144	317		74201			74445	92
7411	20	24	7481	86		74145	65	97	74202			74449	140
7412	17	24	7482	69		74147	175		74203			74458	110
7413	30	24	7483A	69	110	74148	169	191	74204			74460	219
7414	51	24	7484	97		74150	99		74209			74470	140
7415	30	24	7485	104	99	74151	64	84	74251			90	
7416	30	24	7486	104	99	74152	64	84	74253			108	
7417	30	24	7489	205	40	74154	96	110	74256			105	
7420	16	24	7490	33	90	74155	54	110	74258			153	
7421	29	24	7491	76	110	74156	60	110	74259			470	
7422	24	24	7492	38	78	74157	67	55	74260			353	
7423	27	24	7493	32	99	74158		60	74261			402	
7425	27	24	7494	78		74159	210		74262			403	
7426	36	27	7495A	65	99	74160	82	130	74273			404	
7427	27	29	7496	58	120	74161	92	78	74273			404	
7428	35	32	7497	185		74162	92	130	74275			124	
7430	17	24	74100	119		74163	92	78	74278			179	
7432	25	24	74104	63		74164	104	130	74280			120	
7433	40	32	74105	62		74165	105		NE550A	73p		90	
7437	40	24	74107	32	38	74166			L200	195p		95	
7438	33	24	74109	63	38	74167	70		MAINS FILTERS			120	
7440	17	24	74110	54	54	74168			1Amp IEC 4.83			151	
7441	74	24	74111	68		74169			5Amp IEC 5.83			242	
7442	70	99	74112		38	74170	230	200	SA screen 3.87			247	
7443	115	24	74113	32	38	74172	675	200	AH BS approved			237	
7444	112	24	74114	198	38	74173	170					247	
7445	94	24	74116	198	38	74174	87	120	Requests for the			100	
7446	94	24	74118	83		74175	87	110	new issue of the			100	
7447	82	89	74119	119		74176	75		catalogue now being			115	
7448	56	99	74120	115		74177	78		"booked" for des.			49	
7449	56	99	74121	25		74180	85		patch immediately			49	
7450	17	24	74122	46	57	74181	165	150	is ready (about			43	
7451	17	24	74123	48	73	74182	160		November) Please			43	
7452	17	24	74124		137	74183			send 50p to reserve			77	
7453	17	24	74125	38	44	74184	115	710	a copy (Part 3)			77	
7454	17	24	74125	38	44	74184	115	710				77	

CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4066	109p	4528	107p
4006	109p	4066	53p	4529	141p
4007	18p	4067	400p	4530	300p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4014	95p	4074	20p	4541	141p
4015	57p	4075	20p	4541	141p
4016	57p	4076	90p	4543	174p
4017	80p	4077	20p	4549	399p
4018	80p	4078	20p	4553	440p
4019	60p	4079	20p	4554	400p
4020	93p	4081	20p	4556	77p
4021	82p	4082	20p	4557	380p
4022	90p	4085	83p	4557	380p
4023	17p	4086	82p	4558	117p
4024	76p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	150p	4561	65p
4027	55p	4097	105p	4562	530p
4028	75p	4098	372p	4566	159p
4029	100p	4099	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4160	90p	4572	25p
4032	100p	4161	90p	4580	600p
4033	145p	4162	90p	4581	319p
4034	200p	4163	90p	4582	164p
4035	125p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	55p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	160p	4511	149p		
4046	130p	4512	98p		
4047	95p	4513	206p		
4048	60p	4514	260p		
4049	65p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

Micromarket

6800 series	8216	1.95	2114	£10	
6800P	6.50	8224	3.50	2708	£
6801P	16	8228	4.78		
6802P	2.75	8231	6.25		
6803P	3.65	8235	6.25		
6804P	3.65	8236	6.25		
6805P	3.65	8237	6.25		
6806P	3.65	8238	6.25		
6807P	3.65	8239	6.25		
6808P	3.65	8240	6.25		
6809P	3.65	8241	6.25		

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio, Engineering and Servicing
- Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" & "A" levels	Heating	Storekeeping
Accountancy	Industrial	Work Study
Air	Management	
Conditioning	Mechanical	
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept H277 Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest.....
Name.....
Address.....
Telephone Number.....

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF. Tel: 20767

8F 679 STRIPLINE 1000 MHz PNP TRANSISTORS e 25p.
8F 362 STRIPLINE 800 MHz NPN TRANSISTORS e 25p.
MINIATURE VARIABLE CAPACITORS S.M. Drive 250 + 250 + 20 + 20 + 20pf e 75p, Direct Drive 25 + 25 + 25pf e 75p.
X BAND GUNN DIODES CYX 11A e £3 each.
X BAND DETECTOR DIODES LIKE SIM 2 e 15p or 1N 23 e 25p.
STRIPLINE FET with data 2N 4417 e £2.20 each.
100 C280 CAPACITORS assorted for 57p.
200 1/2, 1/4 watt RESISTORS assorted values e 75p.
50 2 watt ZENER assorted untested e 57p.
TOKO 10-7 MHz FILTER CFS 10.7M e 27p, MURATA 10-7MHz FILTER SFW 10.7mA e 27p, 5.5MHz SFC 5.5mA e 27p.
VERNITRON FM4 10-7MHz FILTER e 50p or 3 for £1.
STC CRYSTAL FILTER 8.W. ± 7.5KHz e £5.
455KHz CRYSTAL FILTER 8.W. 7 KHz e 50p.
RADIO TELEPHONE MIKE INSERTS YA 8548 e 50p.
UA 742 ZERO CROSSING AC TRIGGER TRIGAC with data e 25p.
FX 1115 FERRITE BEADS at 15p doz.
3/16" COIL FORMERS with core at 6 for 25p.
BA 156 SILICON DIODES at 50 for 57p.
20 PHOTO TRANSISTORS AND DARLINGTONS assorted untested e £1.
6000 VOLT PIV 1 AMP DIODE ASSEMBLY e £1 each.
DAU TRIMMERS 2 to 9pf e 15p, 7 to 35pf e 15p, 6 to 45pf e 15p, 8 to 125pf e 15p, 8 to 140pf e 15p.
MULLARD CAPACITORS C 281 Type 1uf 250v.w. at 20p doz.
CRYSTAL PACKS 30 10XAJ e £1-10, 20. FT 241A e £1-10, 20. FT 243 e £1-50, 25. 10X Types e £1-25.
50. AC 12B TRANSISTORS Branded but untested for 57p.
50. VARI-CAP DIODES LIKE BA 102 untested e 57p.
50. 1 AMP THYRISTORS T05 Case untested for £1.
25. 5 AMP STUD MOUNTING THYRISTORS untested e £1.
20. PHOTO TRANSISTORS AND DARLINGTONS assorted untested e £1.
50. BC 107-8-9 TRANSISTORS assorted untested for 57p.
10. MULTI-TURN PRE-SET POTENTIOMETERS assorted e 60p.
UNIJUNCTION TRANSISTORS 2N 4871 e 22p, 2N 602B e 25p, 2N 6029 e 25p, MEU 21 e 22p, MU 4894 e 22p, 4J05E29 e 22p, Similar to TIS 43 e 20p.
FET'S J310 e 20p, E304 e 20p, E111 e 12p, E113 e 12p, 2N 3819T e 20p, 8F 256 e 25p, 8F 244 e 25p, DUAL GATE MOS FET'S 40873T e 33p, MFE 131 e 50p.
STUD MOUNTING DIODES 100 PIV 10 amp e 15p, 100 PIV 20 amp e 25p.
1 amp TRIACS T05 Case 400 PIV e 35p each.
R.F.-I.F. I.C. RCA CA 3011 with data e 60p.
MULLARD TRANSISTORS 8C 548 e 10p, 6 for 50p, 8C 549 e 10p, 6 for 50p.
TRANSFORMERS 240 volt AC Input Type 1. 24 volt Tapped at 14 volt 1 amp e £1-30 (P&P 25p).
Please add 20p for post and packing on U.K. orders under £2. Overseas postage at cost.

PHILIP H. BEARMAN

6 POTTERS RD, NEW BARNET HERTS.

Tel: 01-449-1934/5.

LARGE RANGE OF BVA & QUALITY VALVES. SAE LISTS.

NEW MONO TUBES, USUALLY 2 YEAR GUARANTEE.

A31/120; A31/300; A31/410W.	£18-50 incl VAT
A34/100; CME 1420, M6529 FZP.	£19-50 incl VAT
A38/160; CME1520, Thorn.	£19-50 incl VAT
A44/120; CME1713, Thorn.	£19-50 incl VAT
AW47/91; CME1903, A47.14W	£10-00 incl VAT
A47/11W; A47.26WR, Mullard.	£15-00 incl VAT
A47/13W; CME1906, Thorn.	£15-00 incl VAT
A50/120W; CME2013, Vega.	£18-00 incl VAT
A59/15W (AW59.91), Mullard.	£11-00 incl VAT
A59/23WR (A59.11W), Mullard.	£16-00 incl VAT
A61/120WR (CME2413) Vega	£21-00 incl VAT

VARIOUS OTHERS — NO 90° PORTABLE TYPES.

CARRIAGE MAINLAND £2 EACH, ENQUIRIES SAE. (310, 340 SERIES).

SPECIAL OFFER SEMICONDUCTORS

T8A800 50p. LM3900 40p. 741 8 pin 6 for £1.00. NE555 22p. ZN414 75p. IN4005 10 for 35p. 723 REGS 35p. OC140 TRANS. 40p. 8X504 opto isolators 25p. 2N5062 (100V 800MA SCR) 18p.

MINIATURE TOGGLE SWITCHES. SPST 8x5x7mm 49p. DPDT 8x7x7mm 53p. DPDT centre off 12x11x9mm 78p. HEAVY DUTY TOGGLE DPDT 240V AC 10 amps 35p.

MINIATURE SOLID STATE BUZZERS. 33x17x15mm white plastic rectangular case. output at 3 feet 70dB. Low consumption only 15mA. 4 voltage types available. 6-9-12 or 24V DC 75p each. LOUD BUZZER. 50mm diameter 6 or 12 volts 60p. GPO ADJUSTABLE BUZZER, 6-12V DC 25p.

DE-SOLDERING TOOL. Good suction. Teflon nozzle, £4.75p.

MOTORS. Miniature model motors 1.5-6V DC 20p. 12V DC 5 pole motors 35p. 8 track replacement motors 12V DC 55p. 'Big inch' tiny precision motor 115V AC 3 rpm 30p. Smiths Clock Motor Synch., 240V AC 1 rev. per hour £1.75p.

SURPLUS BOARDS. No. 1 has 14 encapsulated reed relays, 12V £1.95p.

No. 2 has 11 50V 2.5 amp scrs., one relay and various transistors including UJT £1.95p.

No. 3 car radio RF/IF boards 2 transistors. LM382 IC trimmers IF's etc. 65p.

No. 4 car radio boards with 6 transistors including power output types IF's choke etc. 75p.

TELEPHONE PICK UP COIL. Suction type with lead and plug 55p.

Terms — Cash with order (or official orders from schools etc.) Postage 30p. (Overseas at cost) VAT inclusive.

SAE for illustrated lists.

PROGRESSIVE RADIO

93 Dale Street,
Liverpool L2 2DY.



TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
 PHONE 01-672 3137/672 9080
 MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING
 CONTROL SYSTEMS

PRICES INCLUDE VAT. P & P FREE

correct at 1.5.79


TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD. or quote
 Access/Barclaycard No. and post to TUAC LTD. 121
 Charlmont Road, London SW17 9AB. We accept phone numbers
 from Access/Barclaycard Holders. Phone 01-672 9080.


NEW FROM TUAC ULTRA QUALITY HIGH POWER New D.C. Coupled Design AMPLIFIERS

Featuring
 Electronic Short Open & Thermal Overload Protection

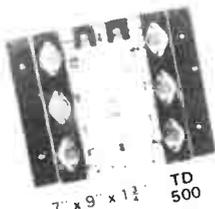Brief Spec
 Input Sensitivity 0.775 v R.M.S. (O.D.B.) at 25 K Ohms
 Frequency Response 20 Hz-20 KHz
 Hum & Noise 100 dB Relative full output



- T.H.D. at full power 0.1%
 - T.D. 500 300W into 2 Ohms
 - 220W into 4 Ohms
 - 140W into 8 Ohms
 - Power supply P.S. 300 **£45.00**
 - T.D. 150 150W into 4 Ohms
 - 100W into 8 Ohms
 - Power supply P.S. 150 **£30.00**
 - T.D. 150 60 Version 60W into 8 Ohms
 - 40W into 15 Ohms
 - Power supply P.S. 60 **£26.25**
 - Power supply P.S. 60 **£19.75**
 - Power supply P.S. 60 **£15.50**
- Note P.S. 300 will drive 2 T.D. 150 amplifiers

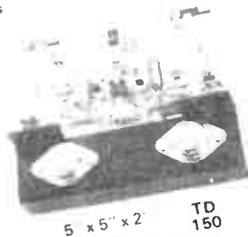

All output ratings are R.M.S. continuous sine wave output

AMPLIFIER MODULES



SPEC INPUT
 SENSITIVITY 60 mV
 for full output
 Frequency response
 20 Hz-20 KHz
 HUM & NOISE 70dB

- TL30 5" x 5" x 2"
 * 35 watt 10 amp output transistors **£13.25**
- TL60 5" x 5" x 3"
 * 60 watt R.M.S. continuous sine wave output
 * 2 R.C.A. 110 watt 15 amp output transistors **£18.50**
- TL100 5" x 5" x 3"
 * 100 watt R.M.S. continuous sine wave output
 * 2 R.C.A. 150 watt 15 amp output transistors **£21.50**
- TP125 7" x 6" x 5"
 * 125 watt R.M.S. continuous sine wave output
 * 4 R.C.A. 150 watt 15 amp output transistors **£27.50**

4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER - 4LSMI

- Full wave control
- RCA BA Tracs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection

£21.50

Model 501 500W per channel as above without sound triggering

£14.00



STEREO DISCO MIXER

With touch sensitive switching and auto fade

INPUTS Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume, Treble and bass controls for each pair of stereo. Sensitivity mag. 3mV (R.I.A. comp.) Flat 50mV at 1kHz. Bass controls +18dB at 60Hz. Treble controls +18dB at 15kHz.

OUTPUT Up to 3 volts (-12dB), available. Attenuated output for TUAC Power Modules. Rotary master and balance controls. Band width 15Hz - 25kHz - dB.

P.F.L. Output 250mV into 8 ohms. Rotary volume control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

Miscellaneous Facilities Two illuminated deck on/off switches. Mains illumination on/off switches. Auto last illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instruction book. Size 25in long x 6in high x 3in deep.

Mono Disco Mixer with autofade **£52.00**

£189.00


3 CHANNEL LIGHT MODULATOR SILMB

- RCA BA Tracs
- 1000W per channel
- Excl. channel fully suppressed and fused
- Master control to operate from 1V to 125W
- Full wave control


£20.75

Single Channel Version 1500 Watts

£9.75

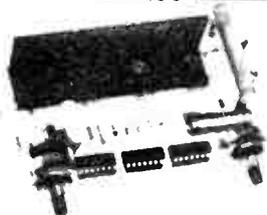

POWER SUPPLIES

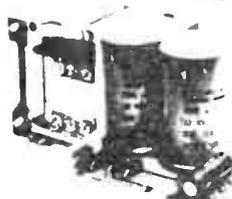

Vacuum varnish impregnated Transformers with supply board incorporating pre-amp supply

- PS250 for supplying 2 TP125s **£30.00**
- PS200 for supplying to TL100s **£30.00**
- PS60/60 for supplying 2 TL60s **£30.00**
- PS125 ± 45 volts for TP125 **£18.50**
- PS100 ± 43 volts for TL100 **£17.00**
- PS60 ± 38 volts for TL60 **£15.50**
- PS30 ± 25 volts for TL30 **£11.75**
- PSU 2 for supplying disco mixer **£7.50**

STOCKISTS - CALLERS ONLY

A1 Music, 88 Oxford Street, Manchester (Tel 061-238 0340)
 Geo. Mathews, 85/87, Hurst St., Birmingham (Tel 021-622 1941)
 Soccold, 9, The Friars (Tel. Canterbury 60948)
 Cookies Disco Centre, 126/128, West Street (Tel Crewe 4739)
 Garland Bros. Ltd., Deptford Broadway, London 01-692 4412
 Luton Disco Centre, 88, Wellington Street, Luton (Tel Luton 411733)
 Session Music, 163, Mitcham Road, Tooting (Tel 01-672 3413).
 Mon-Sat 10am to 6pm. Closed Wed.
 Electrostore Ltd., Four St., Exeter. Tel. 50487.
 Salsoglan Ltd., 43 Borough Rd., Cleveland, Middlesbrough. (Tel. 242851).
 Menhouse Ltd., 82, St. Mary St., Southampton. (Tel 236220)
 Electra Centre, 58 Lancaster Road, Preston (Tel. Preston 58482)
 TRADE & EXPORT ENQUIRIES 01-672 3137

FRONT PANEL FOR LIGHTING EFFECT MODULES

(complete with switches, neons and knobs)
 as illustrated



For SILMB **£7.25**
 Size 8" x 4 1/2"



4LSMI **£6.00**
 Size 6 1/2" x 4 1/2"




FUZZ LIGHTS
 Red, Green, Blue,
 Amber **£24.50**



SILMB **£8.25**
 Combined with 3SDM1
 Size 9" x 4 1/2"

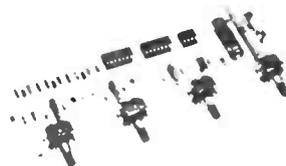ADD SEQUENCE CHASING + DIMMING EFFECTS FOR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec
- Full logic integrated circuitry
- Dimmer control to each channel

3SDM1 **£15.25**

SUPPLIERS TO H.M. GOVT. DEPTS. MANUFACTURED AND ASSEMBLED IN GT. BRITAIN FULLY TESTED AND GUARANTEED
 SEND NOW FOR OUR FREE 28 PAGE ILLUSTRATED CATALOGUE. SEND STAMP PLEASE

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.



Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WL779

Free!

Brochure without obligation to:

British National Radio & Electronic School

P O Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

Block caps please

Catronics

Exceptional Value in the complete Range of VERO CABINETS

a few examples:

ALL PLASTIC RANGE		
Code No.	Size (mm)	Price
65-2514F	100x50x25	£1.70
65-2516G	100x50x40	£1.91
65-2518H	120x65x40	£2.15
65-2520J	150x80x50	£2.45
65-2522K	188x110x60	£3.25

METAL FRONTED RANGE		
Code No.	Size (mm)	Price
75-1237J	85x40x154	£2.80
75-1238D	85x60x154	£3.06
75-1239K	85x80x154	£3.65
75-1411D	205x140x75	£4.26
75-1412K	205x140x110	£5.53
75-1410J	205x140x40	£3.80

Aluminium top panel	65-3851A (120x65x40)	£3.31
Sloping front panel	75-1798K (171x121x75/37.5)	£4.82
Sloping front panel	65-2523E (220x174x100/52)	£6.90

19" CARD FRAME/CASE SYSTEM

Card Frame/Case	71-3841-L	£24.50 -£1 25 p.p.p.
Pair end plates	71-3842-F	£1.01
8" Module	71-3843-A	£5.00
4" Module	71-3844-G	£3.80
Veroboard	09-3979-K	£1.35
2" Front panel	71-3845-B	£2.37
1" Front panel	71-3846-H	£2.06
Veroboards (less connector)	09-1034-F	£1.42
Plain board (less connector)	09-1040-J	94p
DIP board (less connector)	10-1041-J	£2.66
Connector, plug, 31 way	17-0267-H	£1.09
Connector, socket, 31 way	17-0268-C	£1.20
VQ DIP board	01-0044-C	£1.17

All prices INCLUDE VAT, at current rates. Please note our minimum U.K. post & packing charge, except where indicated, is 30p.

**CATRONICS LTD., COMMUNICATIONS HOUSE,
(Dept. 987) 20 WALLINGTON SQUARE,
WALLINGTON, SURREY SM6 8RG.**

Tel. 01-669 6700 (9 a.m. to 5.30 p.m. Sat. 1 p.m.)



Wilmslow Audio

THE firm for speakers!

SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMANS ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANGENT ● TANNOY ● VIDEOTONE ● WHARFEDAILE ● YAMAHA


WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Discount Hi-Fi Etc. at 5 Swan Street and 10 Swan Street

Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

Vega are long on Short Wave Value

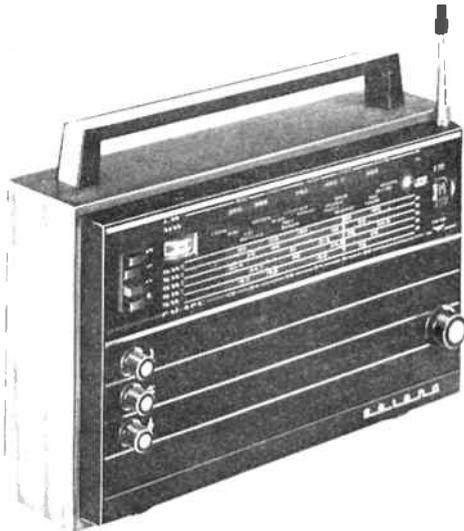

Vega 206 Superhet portable receiving long and medium waves plus 6 short-wave bands: 150-60m (2-5mHz), 60-40m (5-7.5mHz), 32.35-24.8m (9.3-12.1mHz), 19.85-19.4m (15.1-15.45mHz), 16.95-16.75m (17.7-17.9mHz), 14-13.8m (21.45-21.75mHz). Intermediate frequency 465kHz. Rated Output 150mW. Circuitry comprises 12 semi-conductors including voltage stabilising diode, plus turret waveband selector, treble control, inbuilt ferrite rod aerial for med and long waves, 7-section telescopic antenna for short waves. Sockets for line aerial, 9v DC external power source, tape-recorder, earphone or extension loudspeaker. Dimensions: 229x297x105mm. Weight: 2.7kg (6lb) without batteries. **Price: £24.15 inc VAT.**



Vega Spidola 250 Superhet portable receiving VHF/FM, long, medium and 6 short-wave bands: 150-60m (2.0-5.0mHz), 60-40.5m (5.0-7.4mHz), 31.6-30.7m (9.5-9.78mHz), 25.7-24.8m (11.7-12.1mHz), 19.85-16.75m (15.1-17.9mHz), 14-13.8m (21.45-21.75mHz).

Intermediate frequency 465kHz. Rated Output 800mW. Circuitry includes 23 semi-conductors, independent bass and treble tone controls, automatic frequency control, battery condition/tuning meter, inbuilt ferrite rod aerial for long and medium waves, 8-section telescopic swivelling antenna for VHF/FM and short waves. Sockets for: line aerial, 9v DC external power source, tape recorder, earphone or extension speaker. Dimensions: 250x365x105mm. Weight: 3.4kg (7.5lb) without batteries. **Price: £34.79 inc VAT.**

Note: prices shown are rec retail. You may find lower prices locally.

See these and the other fine Vega radios right away. Ask us to send you the Vega Radios colour brochure.



VEGA

programmed for value

Vega value is convincingly demonstrated in the superb short-wave coverage of the 206, Spidola and Selena models: no less than six short-wave bands on the 206 and Spidola, five (including "trawler" bands) on the Selena. Engineered in the USSR to the highest electronic standards, these powerful portables – and the other models in the range – give you top performance (for complete "home" listening too) and reliable service at competitive prices.

Vega Selena 210/2 MB

Superhet portable receiving VHF/FM, long, medium and 5 short-wave bands: 19.85-19.4m (15.1-15.45mHz), 25.8-24.8m (11.7-12.1mHz), 31.6-30.7m (9.5-9.77mHz); 50.4-41.0m (5.95-7.3mHz), (marine) 186.9-76.0m (1.605-3.95mHz). Intermediate frequency 465kHz. Rated Output 500mW (max 750mW). 31 semi-conductor circuitry. Independent bass and treble tone controls. Automatic frequency control. Built-in mains convertor. Sockets for line aerial, earth, tape-recorder, earphone or extension speaker. Inbuilt ferrite rod aerial for long and med waves. 8-section telescopic swivelling antenna for VHF/FM and short waves. Battery condition/tuning meter. Weight 4.08kg (9lb) without batteries. **Price: £39.34 inc VAT.**

Dimensions: 370x250x115mm.



Imported, Distributed and Guaranteed by Technical & Optical Equipment (London) Ltd., Zenith House, The Hyde, Edgware Road, London, NW9 6EE. Tel. 01-200 6505

Sonic

HI-FI DISCOUNT CENTRES



DISCOUNT SPEAKERS

Imp 8 or 15 as app.
Guarantees:
TITAN 5 years
FANE LIFETIME
OTHERS 1 year
ALL PRICES INC. VAT

Prices correct at 23.1.79

HI-FI TYPES

	List/Value	Sonic Price
5" FANE 501 Mid or Full range		£4.95
8" A.F. Model 80 Dual Cone		£4.95
8" A.F. Model 83 Dual Cone		£6.95
FANE 8" 80BT Dual Cone		£3.95
WH'FEDALE L'TON 3xP kit Pt	£60.70	£35.95
... DENTON 2xP KIT pair	£39.15	£21.95
... GLENDALE 3xP KIT	£82.40	£49.95
A.F. FRI 8" SPKR KIT	Sp. Price Pair	£14.95
8" FANE MODE ONE KIT	Sp. Price Pair	£19.99
10" ELAC Model 10RM 10-15w	Sp. Price	£2.50

CABINETS (TEAK VENEERED)

20" x 11 1/2" x 9 1/2" Suitable for Mode 1 or FRI Kits and Models 80, 83 or 80BT Spkrs.

Limited Number £6.95 ea.

GROUP/DISCO TYPES

12" TITAN T12/45R	£15.00	£12.95
12" TITAN T12/60R	£22.50	£14.95
12" TITAN T12/100A 100w	£36.00	£22.95
12" CELESTION G12M	£16.50	£11.95
12" CELESTION G12H 30w	£22.00	£14.95
12" CELESTION G12/50 50w	£25.75	£18.95
12" GOODMANS 12 PD	Sp. Price	£21.95
12" GOODMANS 12 PG	Sp. Price	£18.95
12" FANE 'SPECIALIST' P.A. 80	£29.95	£18.95
12" " " DISCO 80	£39.95	£19.95
12" " " DISCO 100	£33.95	£21.95
12" " " GUITAR 80L	£28.95	£18.95
12" " " GUITAR 100L	£31.95	£19.95
12" " " GUITAR 80B	£29.95	£19.95
12" FANE CRESCENDO 80	£44.95	£29.99
12" " " 80LT	£49.95	£34.95
12" " " 12A	£64.45	£41.95
12" " " 12L	£67.67	£39.95
12" " " 12 BASS	£63.95	£39.95
15" TITAN T15/70 70w	£28.00	£19.95
15" TITAN T15/100 100w	£41.00	£29.95
15" FANE 'SPECIALIST' BASS 85	£41.95	£29.95
15" " " BASS 100	£44.00	£31.50
15" GOODMANS 15P	Sp. Price	£23.95
15" FANE CRESCENDO/15	£82.66	£51.95
15" " " BASS	£85.95	£51.95
15" " " 15/100LT	£74.69	£51.95
15" " " 15/160 160w	£107.23	£72.95
15" " " COLOSSUS 200w	£121.91	£72.95
18" TITAN T18/100 100w	£51.00	£39.95
18" GOODMANS 18P	Sp. Price	£39.95
18" CELESTION G18C	£53.00	£41.95
18" FANE CRESCENDO 18A	£114.97	£72.95
18" " " BASS	£101.86	£59.95
18" " " COLOSSUS 200w	£129.81	£75.00

PLEASE STATE IMPEDANCE.

HORN UNITS (Carr. 85p)

CELESTION MH1000 25w	£17.00	£13.75
FANE 910 MK II 50w	£17.75	£10.99
.. 920 100w	£62.95	£44.50
.. J44 30-50w	£7.95	£4.95
.. J73 50w	£11.75	£7.95
.. J104 50-70w	£16.95	£10.95

HIGH POWER 'CROSS-OVERS'

FANE HP x1R or HP x2R Carr. 35p	£3.65	£2.25
---------------------------------	-------	-------

ADD-ON HIGH FREQUENCY UNITS

F.A.L. 'Add-on Carr. £1	£41.95	£35.95
TITAN T1H 70w Carr. £1	£33.00	£23.95
TITAN TS2H 100w Carr. £1	£33.00	£23.95
TITAN T2H Carr. £1	£39.00	£26.95

BIG DISCOUNTS ON WHARFEDALE SPEAKER KITS

	List/Value	Sonic Price
LINTON 3XP	£60.70	£35.95
DENTON 2XP	£39.15	£21.95

Also for personal shoppers only

AMPS, TTABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING, CABINETS, CREDIT TERMS AVAILABLE orders £20 over

Phone orders accepted from Access & Barclay card holders.


403 SAUCHIEHALL STREET
Tel: 041 332 0700

GLASGOW

Mail Orders/Export enquiries only to 24 Newgate Shopping Centre, NEWCASTLE. Add £1 carr. on HI-FI spkrs. or kits. Otherwise add £1.25 (12" Spkr) £1.50 (15" £2.50 (18"

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEW! HIGHER! TIGHTER!
DISCOUNT PRICES

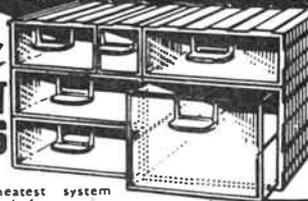


Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2 1/2in x 2 1/2in). £3.50 DOZEN.
DOUBLE UNITS (2D) (5in x 4 1/2in x 2 1/2in). £5.50 DOZEN.
TREBLE (3D) £5.50 for 8.
DOUBLE TREBLE 2 drawers, in one outer case (6D2) £7.90 for 8.
EXTRA LARGE SIZE (6D1) £6.90 for 8.

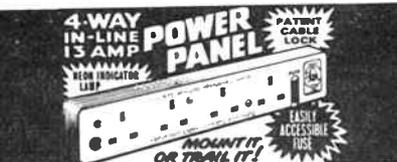PLUS QUANTITY DISCOUNTS
Orders over £20, less 5%. Orders over £60, less 7 1/2%. **PACKING POSTAGE CARRIAGE:** Add £1.00 to all orders under £10. Orders £10 and over, please add 10% carriage. Quotations for larger quantities. Please add 8% V.A.T. to total remittance. All prices correct at time of going to press.



Modern, slim-line power panel, countless uses in home, office, factory, showrooms. Perfectly safe, unbeatable. Can be mounted on wall or trailed anywhere in room. **NEAT COVER:** Smart PVC outer cover. White £3.30 P&P 60p. (V.A.T. Incl.)
FLAIRLINE SUPPLIES (Dept. PW7)
124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.
6 3V 1 5A £2.95; 3A £3.80; 6A CT £6.85; 12V 1 5A £3.95; 3A CT £6.85; 6A CT £6.85; 15V 1 5A £2.75; 18V 1 5A CT £6.85; 24V 1 5A 6.85; 3A CT £8.50; 5A CT £15.50; 8A CT £26.75; 12A CT £35.00; 40V 3A CT £12.25.
TWIN SEC TRANSFORMERS: Prim 240V ac.
6V 0.6A - 6V 0.6A; 9V 0.4A - 9V 0.4A; 12V 0.3A - 12V 0.3A; 20V 0.15A - 20V 0.15A; all £3.65 each; 15V 0.75A - 15V 0.75A £5.65; 15V 1.5A - 15V 1.5A £7.75; 18V 1A - 18V 1A 6.85; 18V 1.5A - 18V 1.5A £8.50; 20V 1.5A - 20V 1.5A £8.50; 12V 4A - 12V 4A £10.50; 25V 2A - 25V 2A £10.50.
MIDGET RECTIFIER TRANSFORMERS: Prim 240V ac.
6-0-6V 1.5A or 9-0-9V 1A £3.00 each; 12V-0-12V 1A or 20V-0-20V 0.75A £3.75 each; 9-0-9V 0.3A or 12V-0-12V 0.25A or 20V-0-20V 0.15A £2.85 each
LT TRANSFORMERS TAPPED SEC. prim 240V ac.
0-10-12-14-16-18V 2A £8.50; 4A £8.25; 0-12-15-20-24-30V 2A £7.35; 4A £10.50; 0-20-30-60V 1A £8.25; 2A £10.50; 0-40-50-60-80-100-110V 1A £10.50.
MAINS TRANSFORMERS SPECIAL OFFER: prim 240V ac.
250-0-250V 60Ma 6 3V 1A £2.00; 250V 100Ma 6 3V 2A £3.00; 9V 3A £2.50; 25V 0.3A £1.00.

LOUDSPEAKERS
2 1/2in 8Ω, 2 1/4in 8Ω or 25Ω, 2 1/2in 8Ω, 3in 35Ω, 3 1/2in 3.8, 8, 16 or 80Ω, all at 1.25 each; 5 - 3in 4, 8, 15 or 25Ω, £1.50; 7 - 4in 4, 8, 16, 25 or 80Ω, £1.75; 8 - 5in 4, 8 or 25Ω, £3.00; Bin 8Ω, £2.50.

"INSTANT" BULK CASSETTE TAPE ERASER
Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads, 200/240V ac. £6.00.

POWER SUPPLY, TWIN OUTPUT: Prim 240V ac.
New, British manufacture smoothed d.c. output 20V 1.5A, plus stabilised output of 15V 100 Ma, plus 12V ac 0.5A output, complete with diagram. £3.50.

EDGEWISE LEVEL METER FSD 200/μA
Size 19 x 18 x 20mm 8000 £1.10.

CHARGING METERS 1 1/2 ins diameter
2A or 3A £1.25 each; 5A or 10A £1.50 each.

SYNCHRONOUS GEARED MOTORS: 240V ac.
Brand new, built in gear box. 1 or 20 RPH. £1.25 each.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS
P.P. sec tapped 3.8-15Ω, A-A 6K, 30V £15.25; A-A 3K, 50V £22.75; 100V IEL31, KT88, etc. £31.25.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covers valve amplifiers 30V to 400V £1.00.

MULTIWAY SCREENED CABLE, PVC COVERED
36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; 4 way individually screened 25p per metre fig 8 twin stereo do screened 15p, metre.

MAINS CABLE
4 way, 3A 30p metre; fig 8 for loudspeakers etc. £5.00 100 metres.

CONDENSERS
Electrolytic, 400/400V 75p; 2000/30V 30p; 1200/75 50p; 2200/40V 40p; 8-8/450V 40p; Paper tubular, W/E 4/160V, 8/160V, 2/150V, 0.1/2000V 25p each.

CARRIAGE EXTRA ON ALL ORDERS
ALL PRICES INCLUDE V.A.T.

Callers by appointment only. S.A.E. Enquiries, Lists.

46, Kenilworth Road, Edgware, Middx.
HA8 8YG. Tel: 01-958 9314

ELECTRONICS SUPPLIERS
SHOPS, IMPORTERS,
MANUFACTURERS

HONG KONG IS CHEAPER

Owing to the rising value of the Japanese Yen, products from Japan are becoming very expensive.

We have equivalent quality products at far better prices from Hong Kong, Taiwan and Korea.

We can supply in both large and small quantities with proven quality.

Even if you have never imported goods before, we can show you how!

86 pages, comprehensive, fully priced catalogue available: specialising in products for the electronics hobbyist.




OVER 3000 ITEMS

Catalogue \$US4.00 to cover airmail postage.

DICK SMITH ELECTRONICS (HK) LTD.
Retail Showroom & Buying Office
29-39 Ashley Rd, Kowloon, H.K.
Tel. 3-669 352 Tlx. 64398
Call in when you're next in Hong Kong!

Simply ahead!

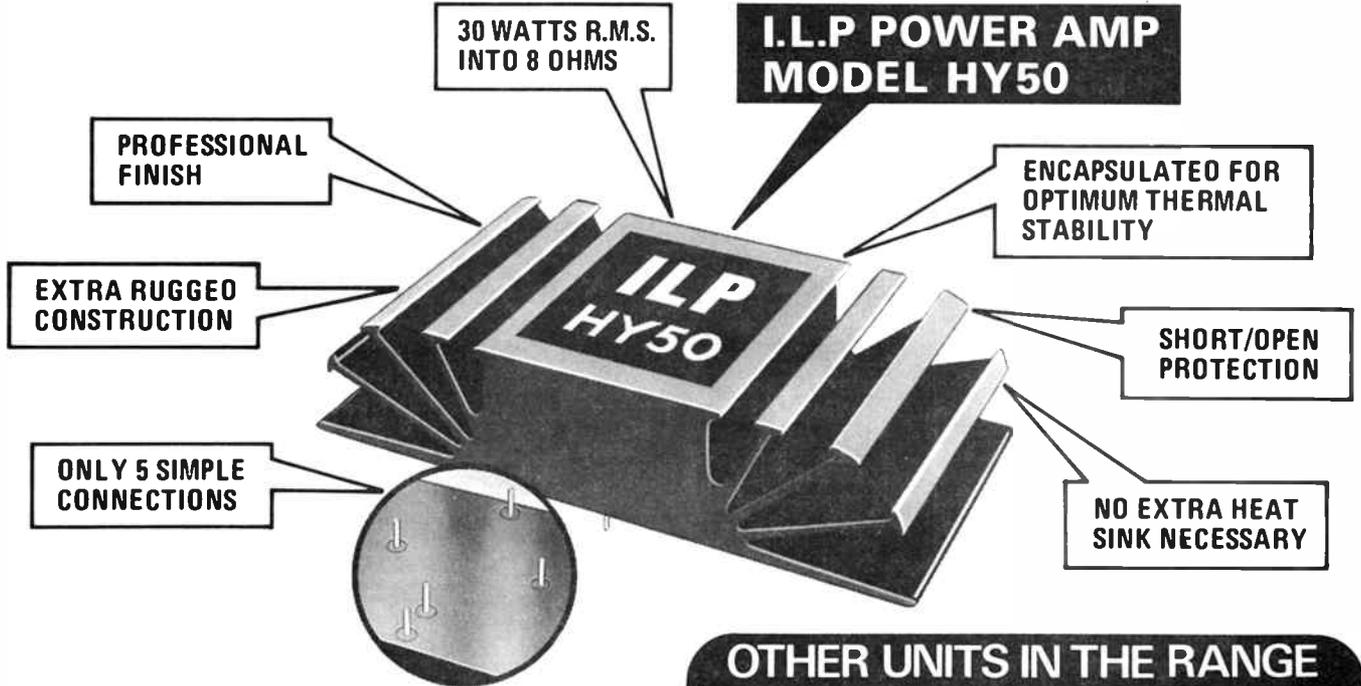**HIGH PERFORMANCE MODULAR UNITS
BACKED BY NO-QUIBBLE 5 YEAR GUARANTEE**



Of all the purpose-built power amplifier modules by I.L.P., the HY50 is understandably the most popular with those wanting to build or up-grade a hi-fi system, run a small high quality P.A. system, amplify a musical instrument (say for practise or small range use) or use it for lab work. Its useful 30 watts RMS output into 8 ohms, its rugged construction and freedom from heatsink worries make HY50 the ideal all-purpose quality power amp – and it is unconditionally guaranteed for five years. Tens of thousands are in use throughout the world.

... and a spec that means just what it says!

Encapsulated power amp with integral full-rated heatsink.
Input – 500mV
Output 30 watts RMS/8Ω
Load Impedance – 4 to 16Ω
Distortion – 0.04% from 100mW to 25 watts at 1KHz/8Ω
Supply Voltage – ±25V, Size 105 x 50 x 25mm
Inc. V.A.T. and postage in U.K.

£8.15

Nothing has been overlooked in the design and manufacture of I.L.P. Modular Units. Heavy duty heatsinks, encapsulated circuitry, no-compromise production standards and true professional finish ensure world leadership for I.L.P. Now we have up-graded output ratings and down-graded prices to bring I.L.P. within easier reach of all who want the best.

New production techniques enable us to reduce prices by an average of 20%, making I.L.P. a better buy than ever.

(Guaranteed 7 days despatch)


USE OUR FREE POST SERVICE for sending your orders, requests for information sheets etc. Simply address envelope.
NO STAMPS REQUIRED.



FREEPOST 1
Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP
Phone (0227) 54778 Telex 965780

OTHER UNITS IN THE RANGE

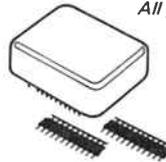
All prices inc. V.A.T. & Postage in the U.K.



HY5 PRE-AMPLIFIER

Compatible with all I.L.P. power amps. and P.S.U.'s. In a single pack, needs external pots and switches. Multi-function equalization. 5 inputs. High overload margin. Active tone controls, 500 mV out. Distortion at 1 KHz – 0.01%.


Two connect easily for stereo. **£5.22**

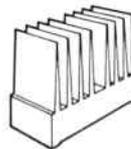

THE POWER AMPS

With heatsinks, full load line and thermal protection. Distortion typically 0.05% at 1 KHz.

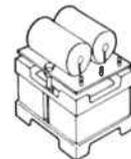HY120 60 Watts RMS/8Ω 114 x 50 x 85mm **£16.42**
HY200 120 Watts RMS/8Ω 114 x 50 x 85mm **£19.92**
HY400 240 Watts RMS/4Ω 114 x 100 x 85mm **£29.89**



THE POWER SUPPLY UNITS

(Split line outputs to suit I.L.P. power amps and HY5)

PSU50 for 1 or 2 x HY50 **£9.11**
PSU70 for 1 or 2 x HY120 **£14.70**
PSU90 for one HY200 **£14.70**
PSU180 for one HY400 or 2 x HY200 **£24.80**

Information sheets on application –
Use our FREEPOST Service.

★ NOW-PRICES DOWN BY 20%

Please supply
Total Purchase Price
I Enclose Cheque Postal Orders
Please debit my Access/Barclaycard Account number
Name
Address
Signature
Reg. Bus. No. 1032630 Eng. FP1/7


The measure of our success.

**METRAVO
1H** £24.50



No screws, just clips together only 4 basic parts. Do it yourself replacement. 36 ranges to 1000V-AC/DC 5A AC/DC 20 Kohm/V

**Transistor
Tester** £29.50

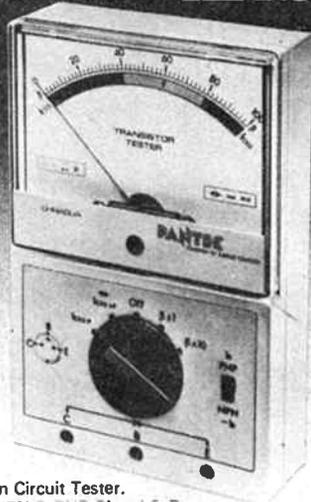

In Circuit Tester. NPN & PNP Signal & Power Devices. Clear Colour Zone Scale.

OX712 Scope
£340.25



Dual trace
15MHz Oscilloscope
Sensitivity 1mV(max)
Full 8cm x 10cm display. Finger tip
SY NC, TV, YA, YB
mains external.

Signal Injector £9.25



Useful for both valve and transistorised equipment. Frequencies up to 500MHz VHF & UHF. Pen type style.

Illustrated above are just 4 of the 350 instruments offered by PIL covering practically every measuring capability for Industry Education Science or Hobby.

Our new 1500 sq ft showroom displays a wide range of the products we distribute for some 60 manufacturers both British and international.

All visitors whether company engineers buyers or hobbyist are welcome and may purchase direct from the showroom in preference to mail order.

For further information on the showroom or on our product range please write to or call at **Precision Instrument Laboratories, 727 Old Kent Road, London SE15 Tel 01-639 4461** Products may be purchased by sending cheque with order to our showroom or by personal visit.

Prices including carriage and 8% VAT

PIL IEC
IEC GROUP COMPANIES

Showroom/Sales/Export 01-639 4461
Open Mon. to Fri. (ring for Sat. opening times)
North London Showroom 01-965-2352
Factory / Repair 01-639-0155

BUILD YOUR OWN METAL DETECTOR TR/IB TR/VCO BFO ...



Test equipment not required. Manuals for kits available at 25p each (refundable). UK prices post & VAT paid except where mentioned. Overseas: write for quote. Literature available: SAE please.

Shadow TR/IB (Illustrated)

A true transmit receive/ induction balance metal detector - uses the latest circuitry for maximum range and sensitivity. Speaker or phones. Pre-assembled search head with lightweight closed cell foam encapsulated coils for thermal insulation and water resistance. A very powerful machine!

Shadow TR/VCO

An advanced version of the above detector, use it as a sensitive TR/IB machine or switch to VCO mode when the depths achieved approach the maximum "in air" range. Low power requirement: runs on standard 9 volt batteries. The most sophisticated detector available as a kit.

Shadow TR/IB kit £22.50 (£29.95 assembled)
Shadow TR/VCO kit £27.50 (£36.95 assembled)
Padded stereo headphones suitable for 'Shadow' detectors £5.50

Designing your own detector? Then we can supply the (hard to obtain) hardware "shell" including fully adjustable shaft with handle, search head moulding with hinge assembly, special clips to mount your own control housing (any box is suitable) completely non-metallic; suitable for any type of detector (TR-PI-VLF-8FO etc). Supplied undrilled as a kit with full instructions (as used on our Shadow range). Detector Shell kit £8.50

Low cost BFO detector 200mm (8") annular search head gives wide scan with easy pinpointing. Simple high efficiency circuit draws <3mA. Extra lightweight 300gms (10.5ozs) with battery. Very detailed construction manual: ideal as a first project. Absolutely everything supplied including pre-assembled search head, tuning coil and earpiece.

ALT3 detector (kit) - £13.95.
Padded high Z headphones for ALT3: £4.90.

Order by post or phone (24 hours) - for quickest delivery quote credit card number. Callers by appointment only please!

ALTEK Dept. (P.W.) 1 Green Lane,
Walton-on-Thames, Surrey.
Phone (093 22) 44110

★ BARGAIN BUYS ★

All prices include VAT—Just add 25p post

from
GREENWELD
443B Millbrook Road Southampton SO1 0HX
Tel: (0703) 772501/783740

SN76110 Stereo decoder 75p; 25/£15
100/£45.
8C184 Prepared for T05 spacing
100/£4.50 1000/£30.
8C213L straight leads 100/£5 1000/£33.
2N5060 0.8A SCR 30V. Ig 200uA 10/£2
100/£15 1000/£120.
1N4148, bandoliered 1000/£15
2500/£32 10,000/£90. Loose, boxes of
10k/£75.
741 8DIL 10/£1.80 100/£14.50.
555 8DIL 10/£2.40 100/£19.50.
1N4003 100/£2.90 1000/£24.
1N4007 100/£4.90 1000/£44.
Electrolytics: 10u40V PC mntg 25/£1.25
100/£3; 4.7u63V V.PC mntg. 1u63V
H.PC mntg same price.
1250u/25V can 10/£1.60 100/£10.
1500u/40V can 10/£2.20 100/£15.
800u/250V can 10/£5.50 100/£44.
400u/400V can 10/£8 100/£56.
200u/350V, 100 · 100 · 50/300V (all in
one can) 10/£5 100/£36.
Pots - 10k lin std bush & spindle 1" long
10/£1 100/£7.50 1000/£50.
Slider 1 8k lin 60mm long prices as above.
Dual 100k lin PC or chassis mntg. min type
18 x 13 x 17mm 0.125" spindle
supplied with smart knob 40p 10/£3.50 100/
£30.
Compression trimmer, 10-100pF 10 for
£1.20 100/£8.50.
Resistors - 1/2W 5% carbon film, these
values only: 220R 1k 3k9 4k7 33k 47k
220k 18R 330k 39k. All @ 1000/£4
(min qty of one value) or £35 per 10,000
any mix.
80 ohm 2 1/2 inch speaker 55p, 100/£38.
T03 sockets 10p, 100/£7.
Ferrite rod aerial 140mm x 10mm with LW
& MW windings—40p, 100/£30.
Powerful 6V buzzer 50mm x 20mm. 70p,
100/£48.
8C2398, 100/£4, 1,000/£27.
1% half watt resistors 111k, 333k, 500k,
900k 100/£2.50.
Other valves on bargain list, send S.A.E.

Audible Warning device - solid state circuit drives high efficiency transducer to give high output. Voltage req'd 6-18V. Can also be driven direct from TTL or CMOS. Module size 45 · 21 · 12mm. Comprehensive data supplied £1.20.
VU meters - 2 meters 40 x 40mm · driver board supplied with full data and circuit £3.50.

OSCILLOSCOPES

We have available from stock the following SCOPEX models 4D10A DC-10MHz. 10mV sensitivity; Stab Power supplies. Dual beam; 3% accuracy. Excellent value at £214 inc VAT and Carr
456 - DC-6MHz. 10mV sensitivity Ideal portable scope. Solid state circuitry. All for £150 inc VAT and Carr

NIXIE TUBES

ITT type GNP7AH. Supplied with data 60p each.
7-seg display, wire ended tube NEC type LD8012 1/2" high, with data 65p.
7-seg display, (as above) Futaba type DG-10Q10 3" char. 70p with data.

1979 CATALOGUE

64 big pages with 50p discount vouchers · qty prices for bulk buyers · reply paid envelope—All this for just 45p inc. post

Relays, push button banks and variable caps; Switches, component packs etc. etc. all in our latest Bargain List — send SAE for your free copy.

Prices in this ad include VAT and are valid until 30.7.79. Add 25p UK/8FPO postage. We buy surplus electronic components for cash.

FF1 WALL MOUNTING KIT FOR HI-FI SPEAKERS

Fidelity Fastenings FF1 is a precision made, vibration damped wall fastening for Hi-Fi and Stereo Speakers of up to 50lbs weight each. Almost undetectable when fitted, the FF1 allows easy adjustment of speaker angle, and the rubber mounting ensures that they do not move accidentally. Speakers can also be quickly and easily lifted off for dusting, cleaning and redecorating.

Available from all good Audio, Hi-Fi and electrical shops at

£6.49 in case of difficulty, direct from the manufacturer at **£6.89 inc P & P**

- ★ Holds up to 50lbs weight per speaker.
- ★ Precision cast mounting brackets.
- ★ Rubber friction mounting for complete stability.
- ★ Easy adjustment of angle for precise stereo image.



THE NUMBER BEHIND MOST LEADING MAKES OF HI-FI SPEAKER SYSTEMS.


PRECISION AUDIO PRODUCTS FROM



The Ridgeway, Iver, Buckinghamshire
Tel: (0753) 654222

TRANSISTORISED INVERTERS

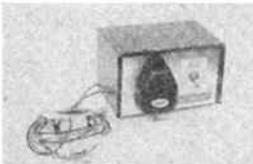12v or 24v DC INPUTS
200/240v AC OFF LOAD OUT
SQUARE WAVE



FREQUENCY 48/52Hz DEPENDING ON LOAD
SILICON POWER TRANSISTORS
DC INPUT FUSED

ECONOMY MODELS

12v DC inputs:

EC1 - 6" x 4" x 4" approx. 20 watts	£9.50
EC2 - 6" x 4" x 4" approx. 40 watts	£12.80
EC3 - 11" x 7 1/2" x 4 1/2" approx. 150 watts	£25.48
EC4 - 11" x 7 1/2" x 4 1/2" approx. 200 watts	£32.20
EC5 - 11" x 7 1/2" x 5" approx. 300 watts	£39.00

ED1 - 11" x 7 1/2" x 4 1/2" approx. 100 watts	£22.10
ED2 - 11" x 7 1/2" x 4 1/2" approx. 150 watts	£26.80
ED3 - 11" x 7 1/2" x 5" approx. 200 watts	£33.50
ED4 - 11" x 7 1/2" x 5" approx. 300 watts	£42.00

Please add £2.00 per unit carriage.
All units assembled to order approx. 28 days.
Caged sizes are subject to variations.

TEL: **ELECTROVANCE**
01-736 0685 P.O. Box 191, London SW6 2LS


MICRO CHIMES

FROM THE INVENTORS OF MICROPROCESSOR MUSICAL CHIMES

New price for the original

CHROMA-CHIME KIT

24 tune model!

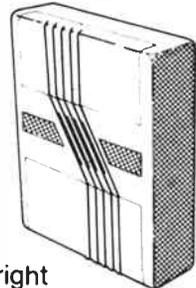

Due to the fantastic success of this product right across the World we are able to offer it at

only **£9.95 + 75p p&p**


Comes complete with:

- ★ TMS1000 Micro
- ★ Superb cabinet
- ★ All R's & C's
- ★ Switches & pots
- ★ Fully prepared PCB
- ★ All semiconductors
- ★ Loudspeaker
- ★ Socket & Hardware
- ★ Fully detailed kit manual

TMS 1000N - MP0027A Micro-computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.

New low price only **£4.95** inc. p&p
(Only present 24 tune repertoire currently available.)

A COMPLETE KIT FOR THE NEW MICRO CHIME

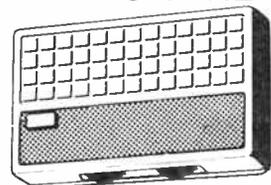

This easy to build kit includes:

- ★ TMS1000 Custom MPU Chip
- ★ Special purpose designed case
- ★ Fully drilled and legended PCB
- ★ All transistors, Resistors and Capacitors
- ★ Full set of mechanical parts
- ★ Smart fascia labels
- ★ IC Socket and Loudspeaker
- ★ Really Low Price!

only **£8.95 + 55p p&p**

Chromatronics, Riverway, Harlow Essex, U.K.
ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK REFUND
PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me: PW1
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX, U.K.

NAME _____

ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____

CHROMATRONICS

Largest range of quality components in the U.K. - over 8,000 types stocked

Marshall's

Head Office and Mail Order to Dept. E.E.,
A. Marshall (London) Ltd.,
Kingsgate House, Kingsgate Place,
London NW6 4TA. Tel: 01-624 0805.
Telex: 21492.

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2 ALSO 325 Edgware Road, W2. Tel: 01-723 4242.
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133 AND Bristol: 108A Stokes's Croft, Bristol. Tel: 0272 426801/2.

TRANSISTORS (full range in catalogue)			
2N698	N70	30	2N1507 N70 36
2N697	N70	31	2N1524 P54 36
2N698	N70	31	2N1553 P66 150
2N699	N70	30	2N1613 N70 30
2N706	N70	30	2N1637 P70 72
2N704	N70	30	2N1638 P54 70
2N708	N70	30	2N1711 N70 30
2N718	N70	30	2N1895 N70 30
2N718A	N70	34	AC127 P54 48
2N720A	N70	36	AC126 N54 48
2N721	P70	185	AC128 P54 48
2N722	P70	46	AC151 P54 43
2N727	P70	18	AC152 P54 54
2N744	N70	36	AC153 P54 58
2N753	N70	36	AC153K P54 58
2N760	N70	36	AC178K N54 70
2N869	P70	36	AC178 N54 84
2N914	N70	36	AC187 N54 88
2N918	N70	33	AC187K P54 86
2N917	N65	38	AC177 P54 84
2N918	N65	41	AC188K P54 86
2N929	N70	37	AD138 P59 276
2N929A	N70	37	AD142 P66 145
2N930	N70	37	AD143 P66 145
2N930A	N70	38	AD149 P66 286
2N1131	P70	32	AD150 P66 110
2N1132	P70	36	AD181 N66 108
2N1204	P70	185	AD182 P66 102
2N1302	N70	30	AF106 P65 30
2N1303	P70	30	AF109 P65 82
2N1304	N70	30	AF114 P64 78
2N1305	P70	30	AF115 P64 78
2N1306	N70	100	AF116 P64 70
2N1307	P70	100	AF117 P64 70
2N1308	N70	118	AF118 P64 70
2N1309	P70	118	AF119 P64 70
2N1370	P70	56	AF125 P70 70
2N1420	N70	56	AF128 P70 70
2N1483	N70	106	AF139 P65 78
2N1485	N70	238	AF172 P66 70

LINEAR (see catalogue for full range)			
CA3013	£1.25	SL810C	£2.75
CA3014	£2.20	SL811C	£2.75
CA3018	£0.75	SL812C	£2.75
CA3018A	£1.10	SL820C	£3.65
CA3020	£2.20	SL821C	£3.65
CA3020A	£2.50	SL823C	£2.25
CA3021	£2.40	SL830C	£2.25
CA3022	£2.20	SL840C	£4.40
CA3023	£2.20	SL841C	£4.40
CA3026	£0.70	SL701C	£2.00
CA3028A	£0.80	CA3085E	£1.07
CA3028B	£1.25	CA3085E	£2.00
CA3014	£2.20	SN76001M	£1.30
CA3018	£0.75	SN76003M	£0.68
CA3018A	£1.10	SN76003M	£1.25
CA3020	£2.20	SN76013M	£2.04
CA3020A	£2.50	SN76013M	£1.72
CA3021	£2.40	SN76018A	£1.90
CA3022	£2.20	SN76023M	£1.72
CA3023	£2.20	SN76033M	£1.72
CA3026	£0.70	SN76111M	£1.30
CA3028A	£0.80	SN76115M	£1.05
CA3028B	£1.25	SN76118M	£1.00

NEW 1979 CATALOGUE
48 pages containing largest range of quality components in the UK - over 8,000 line items - 50p post paid or 40p to callers at any of our 4 branches. **MAIL ORDER** All prices are VAT incl. Telephone Credit Card Orders - minimum £10. **ACCESS AND BARCLAYCARD.**

TTL (see catalogue for full range)			
74LS242N	£1.25	74LS273N	£1.30
74LS243N	£1.25	74LS275N	£3.20
74LS244N	£1.90	74LS279N	£0.58
74LS247N	£1.00	74LS283N	£1.20
74LS248N	£1.00	74LS289N	£1.74
74LS249N	£1.00	74LS290N	£1.00
74LS251N	£1.00	74LS293N	£1.00
74LS252N	£1.00	74LS295N	£1.38
74LS257N	£1.00	74LS298N	£2.85
74LS258N	£1.00	74LS299N	£1.35
74LS259N	£1.35	74LS323N	£3.50
74LS261N	£1.25	74LS324N	£1.88
74LS268N	£0.44	74LS325N	£2.40
74LS273N	£1.30	74LS326N	£2.70
74LS275N	£3.20	74LS327N	£2.65
74LS279N	£0.58	74LS348N	£1.18
74LS283N	£1.20	74LS352N	£1.07
74LS289N	£1.74	74LS353M	£0.86
74LS290N	£1.00	74LS358M	£0.56
74LS293N	£1.00	74LS368M	£0.56
74LS295N	£1.38	74LS388M	£0.56
74LS298N	£2.85	74LS374N	£0.85
74LS299N	£1.35	74LS375M	£0.86
74LS323N	£3.50	74LS376M	£0.77
74LS324N	£1.88	74LS377M	£0.77
74LS325N	£2.40	74LS378M	£1.00
74LS326N	£2.70	74LS379N	£1.25
74LS327N	£2.65	74LS380N	£0.44
74LS348N	£1.18	74LS393N	£0.90
74LS352N	£1.07	74LS395M	£0.90
74LS353M	£0.86	SN74S40N	£0.77
74LS358M	£0.56	SN74S48A	£0.77
74LS368M	£0.56	SN74S59N	£1.46
74LS388M	£0.56	SN74S59M	£0.77
74LS374N	£0.85	SN74S112N	£1.70
74LS375M	£0.86	SN74S144N	£1.70
74LS376M	£0.77	SN74S140N	£0.77
74LS377M	£0.77	SN74S157N	£2.86
74LS378M	£1.00	SN74S188A	£2.70
74LS379N	£1.25	SN74S189N	£1.21
74LS380N	£0.44	SN74S20N	£1.60

POTENTIOMETERS-VOLUME CONTROLS
ROTARY POTENTIOMETERS: All standard 7 spindle
35p 1) SINGLE LESS SWITCH Long spindle double wiper, available in following values
75p 2) SINGLE SWITCH As above but with 2 Pole Switch 2 Amp 250V AC
95p 3) QUO GANGED STEREO As above but dual No Switch All Log or Lin available in the following values
5k, 10k, 25k, 50k, 100k, 250k, 500k, 1Meg, 2Meg, except type 1 not available in 1Meg value

VALVES - MULLARD			
09B7/802	£1.17	EL86	£2.43
6CG2	£1.38	EL95	£1.71
6CG3	£1.31	EY80/802	£1.17
6CG4	£1.51	EY501	£2.87
6CG8	£1.25	G234	£2.14
6CF80	£1.51	PC86	£2.31
6CH84	£2.76	PC89	£2.31
6CL80	£1.71	PC97	£1.31
6CL82	£1.71	PC900	£2.43
6CL86	£1.71	PC98H	£1.81
6F85	£1.17	PC285	£1.71
6F83	£1.61	PC289	£1.76
6F84	£1.82	PC289B	£1.76
6L8	£2.60	PCF80	£1.81
6L84	£1.30	PCF86	£1.77
PCF200	£2.77	PL63	£2.87
PCF201	£2.77	PL64	£1.78
PCF801	£1.77	PL95	£1.48
PCF802	£1.77	PL504	£2.90
PCF806	£1.77	PL508	£2.87
PCF820	£2.43	PL509	£2.76
PCF82	£1.51	PL519	£6.83
PCF83	£1.60	PL602	£3.89
PCF84	£1.67	PY800	£1.78
PCF85/85	£1.67	PY88	£1.58
PCF86	£1.77	PY500A	£2.48
PCF89	£2.31	UC40	£1.88
PCF90	£2.26	UC83	£1.88
PCF91	£1.36	UL84	£1.88

TEST LEADS KIT PN90 Complete luxury kit - curly leads, long reach prods - banana plug, pin plug Spade terminal and croc clip. PRICE £3.50/SET.

SIGNAL INJECTOR Model SE250B Unusually stable trouble-shooter - for checking TV, Radio, amp, etc. £5.30.

TINNED COPPER WIRE Available on 2 oz. reels in the following gauges:

SWG	Price	SWG	Price	SWG	Price
18	£0.55	26	£0.60	32	£0.73
22	£0.55	30	£0.65	36	£0.80

MULTICORE SOLDER - SAVBIT 1.2mm Approx. 13.7 metres of size 12 SAVBIT solder. Ideal for Radio, TV and similar work - £2.28.

CMOS (see catalogue for full range)			
CD4000	£0.20	CD4012	£0.20
CD4001	£0.20	CD4013	£0.82
CD4002	£0.18	CD4014	£1.00
CD4003	£1.24	CD4015	£0.78
CD4007	£0.18	CD4018	£0.82
CD4008	£0.99	CD4017	£1.06
CD4010	£0.80	CD4018B	£1.06
CD4019	£0.80	CD4019B	£0.82
CD4011B	£0.20	CD4020B	£1.15
CD4012	£0.20	CD4021	£1.06
CD4013	£0.82	CD4022B	£1.00
CD4014	£1.00	CD4023B	£0.20
CD4015	£0.78	CD4024B	£0.78
CD4016	£0.82	CD4025B	£0.20
CD4017	£1.06	CD4027B	£0.55
CD4018	£0.82	CD4028B	£0.80
CD4018B	£1.06	CD4029B	£1.10
CD4019B	£0.82	CD4030	£0.84
CD4020	£1.15	CD4030B	£1.00

TRANSFORMERS

EX-STOCK - SAME DAY DESPATCH VAT 8%

TRANSFORMERS END OF LINE OFFERS

30 VOLT RANGE
Pri 220/240 sec 0-12-15-20-24-30V Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V and 15V-0-15V.

Ref	Amps	Price	P & P
112	0.5	2.64	0.78
79	1.0	3.77	0.96
3	2.0	5.57	0.96
20	3.0	6.20	1.4
21	7.0	9.99	1.4
51	5.0	9.87	1.32
117	6.0	11.17	1.45
88	8.0	14.95	1.64
89	10.0	17.25	1.64
90	9.5	19.17	2.08
91	15.0	21.96	2.08
92	2.0	20.45	O.A.

50 VOLT RANGE
Pri 220/240V Sec 0-20-25-33-40 Voltages available 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V 0-20V and 25V-0-25V.

Ref	Amps	Price	P & P
102	0.5	3.41	0.78
103	1.0	4.57	0.96
104	2.0	7.16	1.14
105	3.0	8.56	1.32
106	4.0	11.41	1.50
107	6.0	16.06	1.64
118	8.0	20.26	2.08
119	10.0	24.98	O.A.
109	12.0	28.90	O.A.

MAINS ISOLATORS (SCREENED) PM 120/240V CT

Ref	VA	Price	P & P
*07	20	4.40	0.79
149	60	6.70	0.96
150	100	7.62	1.14
151	200	11.16	1.14
152	250	13.28	1.50
153	350	16.43	1.84
154	500	20.47	2.15
155	750	29.08	O.A.
156	1000	37.20	O.A.
157	1500	51.38	O.A.
158	2000	61.91	O.A.
159	3000	86.86	O.A.

*Pri 0-220 240V Sec 115 or 240V. State sec volts required.

CASED AUTO TRANSFORMERS 240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	5.95	0.90	56W
75	7.73	1.14	64W
150	10.01	1.14	4W
200	11.82	1.45	65W
250	11.59	1.45	69W
500	19.17	1.64	67W
1K	27.88	2.30	84W
1.5K	26.02	O.A.	93W
2K	49.97	O.A.	95W

12 OR 24V OR 12-0-12V Pri 220-240 volts			
Ref	12V	24V	Price P & P
111	0.5	0.25	2.20 0.45
213	1.0	0.5	2.84 0.78
71	2	1	3.51 0.78
18	4	2	4.03 0.96
85	0.5	2.5	5.00 0.96
70	6	3	6.35 0.96
108	8	4	7.42 1.14
72	10	5	8.12 1.14
112	12	6	9.51 1.32
17	16	8	10.72 1.32
115	20	10	13.98 2.08
187	30	15	17.93 2.08
226	60	30	36.74 U.C.

TEST METERS
AVO 8 MK5 £88-10
AVO 71 £36-00
AVO 70 £48-70
AVO MMS minor £32-95
Wee Megger £74-25
TT169 in circuit transistor tester £39-53
EM272 £57-80
DA116 £108-90
BM7 Megger £51-76
All accessories available. P & P £1 15 8% VAT

MINI-MULTIMETER
DC 1000V AC 1000V DC 100mA Res 150kΩ 1000Ω/V Bargain £7.20 P & P 8% VAT


20,000 ohm/V Multimeter, mirror scale Ranges AC DC to 1000V DC current to 250mA Resistance to 3 Mohms
5" x 3 1/2" x 1 1/2" £14.36 P & P £1 05 VAT 8%

NEW RANGE TRANSFORMER
Pri 120V or 220 240V Sec 0 36 48 twice to give 36 0 36V 48 0 48V 72V or 92V P & P
Ref 3A 14-70 1.48
4A 18-77 1.84
5A 26-84 2.15
VAT 8%

PANEL METERS
43mm x 43mm 82mm x 78mm
0 500µA 6-20 0 50µA 6-70
0 500µA 5-95 0 500µA 6-70
0 1mA 5-95 0 1mA 6-70
0 30V 5-95 0 30V 6-70
VU ind. Panel 48mm x 45mm 3-36
VU ind. Edge 90mm 250µA 2-60
54mm x 14mm 250µA FSD 2-60
VU ind. Edge 54 x 14mm 500µA FSD 2-60
Carriage 65p VAT 8%

COMPONENT PACKS
65 1W Metal Oxide Resistors
65 1W Metal Oxide Resistors
150 Mixed Value Capacitors
10 Reed Switches
50 Wire Wound Resistors
10 3000mF 30V Capacitors
25 Assorted presets
50 3 tag terminal strips
Hardware BA nuts bolts
200 Mixed Resistors
10 mixed value electrolytic caps
32 mf to 2000 mf.
70p + 12 1/2% VAT
P & P 40p + 8% VAT

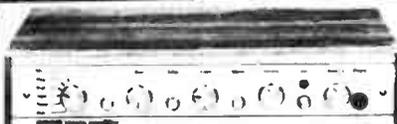BRIDGE RECTIFIERS
100V 25A £2-36
200V 2A £0-



20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia. Red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak for use with 8 to 15 ohm speakers

£29.90
£2 50 p&p

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail same facilities as Viscount IV but with 30x30 output 60x60 watts peak. For use with 4 15 ohms speakers

£29.00 £2 50

SPECIAL OFFER

30 x 30 WATT AMPLIFIER KIT with BSR P200 belt drive deck and Shure M75 cartridge. **£55.00** + p&p £5.00

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max. 8 ohm impedance

£14.95

Per stereo pair
£3.40 p&p

BSR P200

Belt drive chassis turntable unit semi-automatic, cueing device

£24.95
p&p £2 55

A O C OLM 30 Mk III Magnetic Cartridge to suit **£7.75**



BSR manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited from home or disco use. **OUR PRICE £10.95** p&p £2 55

GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth

£7.95 p&p £2 00 Size 12" x 8"

SANYO Nic/cad battery, with mains charger equivalent in size and replaces 4 SP11 type cells. Size 3 1/4" x 1 1/4" x 2" approx

£7.50 p&p £1 50p

BARGAIN FOR PERSONAL SHOPPERS ONLY
Altone UA4 Stereo System

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones. **complete with speakers £34.95**

Micro Cassette Recorder
Pocket size—home or office use or when travelling **£13.95**

Battery operated fluorescent camping lamp.
Runs off 8 U2 batteries **£4.50**

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE
PRICE **£25** AT OVER **PER PACK**
SEE OUR PRICES

1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input

OUR PRICE **£4.95**
p&p £1 00

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs

OUR PRICE **£7.45**
p&p £1 00

illu. AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.

Size approximately 9 1/2" x 8 1/2" x 4" p&p £2 05 **£11.95**



ACCESSORIES

Suitable mains power supply parts consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance **£2.90** plus £1 50 p&p

Two Way Speaker Kit

Comprising of two 8" x 5" approx 4 ohm bass and two 3 1/2" 15 ohm mid range tweeter with two cross over capacitors **£3.95** per stereo pair plus £1 50 p&p

BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish **£5.95**

LCD 5 function men's digital watch stainless steel finish **£6.95**

LCD 8 function CHRONOGRAPH men's digital watch stainless steel finish **£12.95**

POCKET CALCULATOR With LED display memory and percentage key **£2.95**

AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 7" LED display Buzzer and snooze timer **£11.95**

125 Watt Power Amp Module **£13.95**

Mains power supply for above unit **£3.50**

MULLARD Built power supply **£1.50**

DECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3 1/2" approx tweeter inc crossovers **£20.00**

VIDEOMASTER Super Score TV Game with pistol mains operation **£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM-FM with clock LW MW SW VHF mains/battery operation **£41.95**

VIDEOMASTER COLOUR SHOT TV GAME Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED OPPORTUNITY AT **£9.95 ONLY**



323 EDGWARE ROAD, LONDON W2
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 12 1/2%
All items subject to availability. Price correct at 1/5/79 and subject to change without notice

50 WATT MONO DISCO AMP

£29.95

P&P £2 50

Size approx. 13 1/4" x 5 1/4" x 6 1/4"

50 watts rms 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume

70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/4"

Brushed aluminium fascia and rotary controls

Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No 1 to No 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level

Output 100 watts RMS 200 watts peak

70 watt **£57**

140 watt peak p&p £4 00

100 watt **£65**

DUO II SPEAKERS

Attractive teak finish, modern design, incorporating 2 separate speaker units—8" approx woofer and 2 1/2" approx tweeter 45 to 1800 Hz Impedance 8 ohms Power 15 watts RMS 20 watts max Per stereo pair **£17.00**

For personal callers only.

FOR PERSONAL SHOPPERS ONLY

STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**

Size approximately 47" x 15 1/2" x 15"

Quality audio modules and accessories for

S450

STEREO FM TUNER
Fitted with phase lock-loop

£26.14
+ 40p p&p




The S450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, simply by changing the settings of the pre-set controls. Features include FET input stage, Vari-Cap diode tuning, Switched AFC LED Stereo Indicator.

FREQUENCY RANGE	88-108 Mhz
SENSITIVITY	3.0 µV
BANDWIDTH	250 kHz
SPURIOUS REJECTION	50 dB
SELECTIVITY ± 400 kHz	55 dB
AUDIO OUTPUT (22.5 kHz deviation)	100 mV
STEREO SEPARATION	30 dB
SUPPLY REQUIREMENTS	20 to 30V (90mA max)
AERIAL IMPEDANCE	75 ohms
DIMENSIONS	240mm x 110mm x 32mm

Stereo 30

COMPLETE AUDIO CHASSIS

£21.57
+ 66p p&p

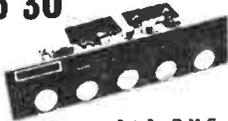

7 + 7w R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, main switch, fuse and fuse holder and universal mounting brackets.

OUTPUT POWER	7 Watts RMS
LOAD IMPEDANCE	8 ohms
TOTAL HARMONIC DISTORTION	Less than 5% (Typically 3%)
FREQUENCY RESPONSE	20 Hz to 20 kHz ± 3dBs
TONE CONTROL RANGE	± 12 dBs at 100Hz and 10kHz
SENSITIVITY	190 mV for full output
INPUT IMPEDANCE	1 M ohms
TRANSFORMER REQUIREMENTS	22 V. A.C. rated at 1A
DIMENSIONS (less controls and panel)	200mm x 130mm x 33mm

AL60

AUDIO AMPLIFIER MODULE
25 Watts RMS

£5.27 + 35p p&p



25w R.M.S.

This high quality audio amplifier module is for use in audio equipment and stereo amplifiers and provides output powers up to 25 RMS with distortion levels below 0.1%

OUTPUT POWER	25 Watts RMS
SUPPLY	30-50 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than 1% (Typically 0.6%)
FREQUENCY RESPONSE	20 Hz to 30 kHz ± 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

AL80

AUDIO AMPLIFIER MODULE

£7.92 + 35p p&p



35w R.M.S.

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%

OUTPUT POWER	35 Watts RMS
SUPPLY	40-60 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than 1% (Typically 0.6%)
FREQUENCY RESPONSE	20 Hz to 30 kHz ± 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

AL250

POWER AMPLIFIER

£19.24 + 66p p&p



125w R.M.S.

This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

OUTPUT POWER	125 Watts RMS continuous
OPERATING VOLTAGE	50-80 V
LOADS	4-16 ohms
FREQUENCY RESPONSE	25 Hz to 20 kHz measured at 100 Watts
SENSITIVITY FOR 100 WATTS O/P AT 1 kHz	450 mV
INPUT IMPEDANCE	33 K ohms
TOTAL HARMONIC DISTORTION	
50 WATTS into 4 ohms	0.1%
50 WATTS into 8 ohms	0.06%

AL30A

AUDIO AMPLIFIER MODULES

£4.26 + 35p p&p



10w R.M.S.

These low cost 10 watt modules offer the utmost in reliability and performance, whilst being compact in size.

MAXIMUM SUPPLY VOLTAGE	30 V
POWER OUTPUT for 2% THD	10 Watts RMS
TOTAL HARMONIC DISTORTION	Less than 25%
LOAD IMPEDANCE	8-16 ohms
INPUT IMPEDANCE	100 K ohms
FREQUENCY RESPONSE	50 Hz-25 kHz ± 3 dBs
SENSITIVITY	75 mV for full output
DIMENSIONS	74mm x 63mm x 28mm

SPM80

STABILISED POWER SUPPLY

£4.95 + 35p p&p



Designed to power two AL60s at 15 Watts per channel simultaneously. Circuit Techniques include full short circuit protection.

INPUT A.C. VOLTAGE	33-40V
OUTPUT D.C. VOLTAGE	33 V nominal
OUTPUT CURRENT	10 mA-1.5 amps
OVERLOAD CURRENT	1.7 amps approx.
DIMENSIONS	105mm x 63mm x 30mm

PA100

STEREO PRE-AMPLIFIER

£18.05 + 40p p&p



A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution to the front end requirements of stereo amplifiers or audio units. The six push button selector switch gives a choice of inputs together with two filters for high and low frequencies.

FREQUENCY RESPONSE	20 Hz to 20 kHz x 1 dB
TOTAL HARMONIC DISTORTION	Less than 1% (Typically 0.7%)
SENSITIVITY	1 TAPE 100 mV/100 K ohms } For an
INPUTS	2 RADIO TUNER 100 mV/100 K ohms } output
	3 MAGNETIC P.U. 3.5 mV/50 K ohms } 250 mV
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
BASS CONTROL RANGE	± 15 dBs at 75 Hz
TREBLE CONTROL RANGE	+ 10-20 dBs at 15 kHz
SIGNAL/NOISE RATIO	Better than 65 dBs (All inputs)
INPUT OVERLOAD	Better than 26 dBs (All inputs)
SUPPLY	20 to 40 V
DIMENSIONS	300 x 90 x 33mm (less controls)

MPA30

MAGNETIC CARTRIDGE PRE-AMPLIFIER



£3.35 + 35p p&p

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.

SENSITIVITY	3.5 mV for 100 mV output
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
INPUT IMPEDANCE	50 K ohms
SUPPLY	18 to 30 V—re earth
DIMENSIONS	110 x 50 x 25mm (inc DIN socket)

PA12

STEREO PRE-AMPLIFIER



£8.75 + 35p p&p

The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL20/30 Audio Amplifier Modules, the PS12 power supply and the T538 Transformer. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

FREQUENCY RESPONSE	20 Hz-20 kHz (-3dB)
BASS CONTROL	± 12 dB at 60 Hz
TREBLE CONTROL	± 14 dB at 10 kHz
INPUT IMPEDANCE	1 Meg. ohm
INPUT SENSITIVITY	300 mV
CROSSTALK	-60 dB
SIGNAL/NOISE RATIO	-65 dB
OVERLOAD FACTOR	± 20 dB
TAPE OUTPUT IMPEDANCE	25 K ohms
DIMENSIONS	152mm x 84mm x 25mm

PS12 POWER SUPPLY MODULE

Power supply for AL20A-30A, PA12, S450 etc. Transformer T538.

Input A.C. Voltage 15-20V. Output D.C. Voltage 22-30V approx. (Dependent upon input.) Output Current 800mA maximum. Dimensions 60 x 43 x 26mm.



£2.13 + 35p p&p.

BP124 SIREN ALARM MODULE

American Police screamer powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down, and other security purposes.



ONLY £3.78

+ 35p p&p. 5 WATTS —

MA60 HI-FI AMPLIFIER KIT

Build your own top quality amplifier, save yourself pounds. The MA60 kit comprises the following Bi-kits modules, 2 x AL60 amps, 1 x PA100 pre-amp, 1 x SPM80 stab. power supply, 1 x BMT80 transi. giving 15 watts RMS per channel STEREO. All modules covered by the BI-PAK satisfaction or money back guarantee. Details of the above modules are in this ad. Price £36.00 + 62p p&p.

TC60 KIT

A beautifully designed genuine TEAK WOOD veneered cabinet to put the professional touches to your home built amplifier. Full set of parts incl. Front & Back Panels, Knobs, Chassis, Fuses, Sockets, Noen, etc. Ideal for the MA60. Size: 425mm x 290mm x 95mm. Price £22.44 + 86p p&p.

TRANSFORMERS

T538 For use with S.450 AL30A MPA30 Order No. 2036 Price: £3.60 + 55p p&p.
T2050 For use with Stereo 30 Order No. 2050 Price: £3.66 + 55p p&p.
BMT80 For use with AL60 SPM80 Order No. 2034 Price: £6.08 + 86p p&p.
BMT250 For use with AL250 Order No. 2035 Price: £7.14 + £1.10 p&p.
2040. For use with AL60 Order No. 2040 Price: £5.85 + 80p p&p.
2041. For use with AL80, AL120 and AL250 Order No. 2041. Price: £7.65 + 86p p&p.

CASES

TEAK 30, 32 x 23 x 8cm, designed mainly for use with our stereo 30 Audio System but has proved very helpful to home constructors. Fitted with solid uncut front and back. o/n 139. £6.69. p&p 70p.

TEAK 60, 42 x 29 x 9cm, for use with AL60/MK60 Audio Kit. Useful for the home constructor requiring an amplifier sleeve — has no front or back panel. o/n 140. £7.87. p&p 85p.


Professionals and Enthusiasts from BI-PAK

AL120

AUDIO AMPLIFIER
(With integral heat sink and short-circuit protection).

£12-91
+ P. & P. 35p

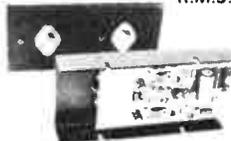Introduced to fulfill the demand for a fully protected power amp. capable of driving high quality speaker systems at up to 50W. with distortion levels below 05%. Ideal for domestic use. Discos, P.A. systems, electronic organs etc. The generously rated components ensure continuous operation at high output levels.



50W R.M.S.

OUTPUT POWER SUPPLY	50 Watts R.M.S.
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	05% Max. (Typically 02%)
FREQUENCY RESPONSE	25Hz-20kHz
SENSITIVITY	500mV
MAX HEAT SINK TEMP.	45 deg C
DIMENSIONS	192 x 89 x 49 mm

SPM120

STABILISED POWER SUPPLIES

SPM120/45
SPM120/55
SPM120/65
£6-52
+ P. & P. 35p



AC INPUTS	
SPM120/45	40-48v
SPM120/55	50-55v
SPM120/65	60-65v
OUTPUT CURRENT	2.5A
RIPPLE	1A 100mV 2A 150mV

SPM120 is a fixed voltage stabiliser available with an output of either 45v, 55v, or 65v. Designed primarily for use in audio applications, the stabiliser which provides output currents up to 2.5A., operates direct from a mains transformer requiring only the addition of 2 Electrolytic capacitors to complete the s/c protection.

GE100 Mk2.

10 CHANNEL MONOGRAPHIC EQUALISER

£22-50
+ P. & P. 35p



Control Range	±12dB
Dynamic Range	110dB
Maximum Output	±15dB
Frequency Response	30Hz-20KHz (±1dB)
Power Supply	15-0-15v
Voltage Handling Input	3v R.M.S
T.H.O.	005%

Only 155mm x 65mm x 50mm including the 10 x 10K 1in slider potentiometers and knobs which are mounted on a board positioned above the circuitry. In the frequency range of 31Hz to 20KHz you can cut and boost ±12dB with the 10 sliders, each of which has its frequency marked on the circuit board. The GE100 has numerous uses including mixers, P.A. systems and discos. It will also greatly improve the sound reproduction of your existing audio equipment. Power Supply for GE100 o/d SG30 £3.80

VPS30

REGULATED VARIABLE STABILISED POWER SUPPLY

£8-20 + P. & P. 35p



AC Input Maximum	25v
Voltage Regulation	2-30v
Regulated Current	0-2A
Incorporating short circuit protection	

This NEW versatile Regulated Variable Stabilised Power Supply with short circuit protection and current limiting is a must for all electronics enthusiasts. It incorporates adjustable voltage from 2v-30v. with a current limiting range of 0-2A. With this module there is no need to build a separate power supply for each of your projects, with the simple addition of a transformer (ord 2033), 0-1ma (ord 1310 or 1305), plus a suitable shunt, a voltmeter (ord 1311 or 1306), a 470ohm pot (ord 1896) a 4K7 pot (ord 1899). It can be used again and again as a self-contained bench, power supply, eliminating the use of batteries and thus saving ££'s!

PA200

STEREO PRE-AMPLIFIER

£16.55
+12½% V.A.T.
P. & P. 40p



FREQUENCY RESPONSE	20Hz to 20kHz x 1dB	
TOTAL HARMONIC DISTORTION	Less than 1% (Typically 70%)	
SENSITIVITY	1 TAPE	100mV/100 K ohms
INPUTS	2 RADIO TUNER	100mV/100 K ohms
	3 MAGNETIC P U	3-5mV/50 K ohms
		output 500mV
EQUALISATION	Within ±1dB from 20Hz to 20kHz	
BASS CONTROL RANGE	±15dB at 75Hz	
TREBLE CONTROL RANGE	±10 20dB at 15kHz	
SIGNAL NOISE RATIO	Better than 65dBs (All inputs)	
INPUT OVERLOAD	Better than 2dBs (All inputs)	
SUPPLY	35 to 70v	
DIMENSIONS	300 x 90 x 33mm (less controls)	

The PA200 is basically our popular PA100. Modifications have been made to make it compatible with the higher output AL120 and AL250 amplifiers.

HEADPHONES

A top quality headphone with cushioned earpads and headband. Separate balance/volume controls. Stereo or Mono switch. Impedance 8 ohms. Frequency 30-18,000Hz. o/n 884. £9-78. p&p 50p.
A brilliant compromise between price and performance. Superb stereo reproduction for the newcomer to Hi-Fi. Impedance 8 ohms. Frequency 30-15,000Hz. o/n 885. £4-96. p&p 50p.

BIB HI-FI ACCESSORIES

Parallel Tracking GROOV KLEEN
The very latest in automatic record cleaning. Designed to suit all modern single play decks. Simple to fit, it is extremely efficient. Complete with two types of base and three height extensions. o/n 8101. £3-97. p&p 35p.
Cassette Tape Editing Kit
Enables cassette tapes to be edited and joined easily, quickly and accurately. Kit comprises: Tape Splicer (32mm) 2 Precision Tape Cutters, Tape Piercer, 9 Self-adhesive Labels, Reel of Splicing Tape, 3 Winders and removers and instructions, all in a handy wallet. o/n 811. £2-69. p&p 35p.
GROOV-STAT
The BIB Groov Stat static reducer neutralises the static charge on records and other plastic surfaces. o/n 8103. £5-89. p&p 35p.
Cassette Head Cleaner
Essential for cleaning of tape heads, capstans and rollers. Pack contains Tape Head Applicator and tape head polisher tools. Plus bottle of special formula cleaning fluid and full instructions. o/n 832. £0-72. p&p 35p.

METERS

Miniature Balance & Tuning Meter
Miniature moving-coil meter for stereo balance indicator, tuning indicator for FM or similar application. Pointer at centre indicates zero or null position. Robust construction. Sensitivity 100 0.100mA. Dimensions 23 x 22 x 26mm. o/n 1318. £2-11. p&p 35p.



Balance and Tuning Meter
Clear view edge-wise meter. Centre zero application. Sensitivity 100 0.100UA. Dimensions 45 x 22 x 34mm. o/n 1319. £2-18. p&p 35p.



Miniature Level Meter
Moving coil, for accurate level indication for tape recorders, amplifiers etc. Neat design, rugged construction. Will withstand five times rated value. Sensitivity FSD 200UA 0dB 130UA. Dimensions: 23 x 22 x 26mm. o/n 1320. £3-02. p&p 35p.



Vu Meter
Calibrated 20 to +3 and 0 100%, making it suitable for use as a recording level meter or as a power output indicator. Sensitivity 130UA. Dimensions: 40 x 29mm. o/n 1321. £2-18. p&p 35p.



ADAPTORS

AC-DC enables a large range of battery powered radios, recorders, calculators to be run off the mains (220-240V AC). Switchable for 3-6-9-12 volts. Current rating 300mA. Polarity reversing switch. Universal plug incorporated. o/n 137. £4-06. p&p 35p.
DC-DC for use in all cars, boats etc., with pos. or neg. earth for a regulated output of 6, 7.5 or 9 volts DC at 300mA. For radios, recorders etc. o/n 138. £3-15. p&p 35p.

CROSSOVER NETWORKS

2-WAY channels for high and low frequencies to correct speakers - high to tweeters, low to woofers. Complete with instructions. Frequency: 3,000Hz. o/n 1904. £1-24. p&p 35p.
2-WAY for 8 ohm speakers up to 30 watts. Frequency: .3KHz. o/n 1905. £1-81. p&p 35p.
3-WAY for 8 ohms speakers up to 30 watts. Frequency: 800Hz and 4.5KHz. o/n 1906. £3-32. p&p 35p.

MICROPHONES

DYNAMIC CASSETTE
For equipment requiring a high quality microphone. Sturdy, solid moulded body in black with neat chrome surround. Pick-up pattern is omnidirectional. On/Off switch, 1 metre of tough lead with floating 2.5 and 3.5mm plugs. Matching moulded strut. Impedance: 200 ohms. Sensitivity: 30dB. Frequency: 90-10,000Hz. Size: 20mm dia x 120mm. o/n 1326. £1-80. p&p 35p.
DYNAMIC MICROPHONE
Superior quality portable cassette recorder mike with built-in remote control switch and lead fitted with 5-pin 240° DIN plug (remote switch) and 3-pin DIN plug (microphone). Provides a direct replacement for those supplied with recorders. With detachable stand. Omnidirectional. Impedance: 200 ohms. Freq response: 100 to 10,000Hz. Sensitivity: 79dB at 1,000Hz. o/n 1327. £2-98. p&p 35p.

RE-317 DYNAMIC MICROPHONE
Highly sensitive, high-grade desk or hand mike suitable for use with many popular cassette decks. Incorporates On/Off switch and 1 metre lead with moulded standard jack plug. Complete with desk stand. Omnidirectional. Impedance: 5,000 ohms. Freq response: 100 to 12,000Hz. Sensitivity: (-7dB at 1,000Hz). o/n 1338. £4-48. p&p 35p.

OMNIDIRECTIONAL CARDIOID
Powered by a 1½ battery located within the aluminium body. Satin silver finish with front disk protection to the diaphragm housing. On/Off switch. Also with 'Busby' type windshield. 'U' bracket and stem and extremely supple cable. Consumption 0.2mA from 1½ battery providing approx. 8-10,000 hours continuous life. Impedance: 600 ohms. Sensitivity 70dB. Frequency: 30-16,000Hz. Size: 23mm dia x 267mm. o/n 1329. £14-40. p&p 35p.

UNIDIRECTIONAL CARDIOID
Dual imp 600 and 50,000 ohms. Response 50 to 14,000Hz. Sensitivity 54dB at 50K ohms. Size 1½" dia x 6½" long. Weight approx. 190gm. o/n 1328. £12-32. p&p 35p.

STANDS

GOOSENECK CHROME FLEXIBLE HOLDERS
Length 320mm. o/n 1333. £2-70. p&p 35p.
Length 515mm. o/n 1334. £3-83. p&p 35p.
FLOOR STAND Heavy chrome. Slow-away feet with rubber ends for maximum stability. Draws to a height of 5' maximum. o/n 1335. + £10-69. p&p 85p.
BOOM ARM for use with the above stand. Heavy chromed metal. It gives 30" reach from the stand. o/n 1337. £10-36. p&p 70p.

WINDSHIELD COVERS

o/n 1331 Medium per pair £1-35. p&p 35p. o/n 1332 Large per pair £2-03. p&p 35p.

AUDIO LEADS

- | | | |
|-----|---|-------|
| 107 | FM Indoor Ribbon Aerial | £0-68 |
| 113 | 3.5mm Jack plug to 3.5mm jack plug Length 1.5m | £0-84 |
| 114 | 5 pin DIN plug to 3.5mm Jack connected to pins 3&5 Length 1.5m | £0-95 |
| 115 | 5 pin DIN plug to 3.5mm Jack connected to pins 1&4 Length 1.5m | £0-96 |
| 116 | Car aerial extension. Screened insulated lead. Fitted plug & ski | £1-24 |
| 117 | AC mains connecting lead for cassette recorders & radios. 2 metres | £0-76 |
| 118 | 5 pin DIN phono plug to stereo headphone jack socket | £1-18 |
| 119 | 2 x 2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m | £1-01 |
| 120 | Car stereo connector. Variable geometry plug to fit most car cassette, 8 track cartridge & combination units. Supplied with inline fused power lead and instructions. | £0-68 |
| 123 | 6.6m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK | £1-82 |
| 124 | 3 pin DIN plug to 3 pin DIN plug Length 1.5m | £0-84 |
| 125 | 5 pin DIN plug to 5 pin DIN plug Length 1.5m | £0-84 |
| 126 | 5 pin DIN plug to Tinned open end Length 1.5m | £0-84 |
| 127 | 5 pin DIN plug to 4 Phono Plugs. All colour coded Length 1.5m | £1-46 |
| 128 | 5 pin DIN plug to 5 pin DIN socket Length 1.5m | £0-90 |
| 129 | 5 pin DIN plug to 5 pin DIN plug mirror image Length 1.5m | £1-18 |
| 130 | 2 pin DIN plug to 2 pin DIN inline socket Length 5m | £0-76 |
| 131 | 5 pin DIN plug to 3 pin DIN plug 1&4 and 3&5 Length 1.5m | £0-93 |
| 132 | 2 pin DIN plug to 2 pin DIN socket Length 10m | £1-10 |
| 133 | 5 pin DIN plug to 2 phono plugs. Connected pins 3&5 Length 1.5m | £0-84 |
| 134 | 5 pin DIN plug to 2 phono sockets. Connected pins 3&5 Length 23cm | £0-76 |
| 135 | 5 pin DIN socket to 2 phono plugs. Connected pins 3&5 Length 23cm | £0-76 |
| 136 | Coiled stereo headphone extension lead. Black Length 6m | £1-97 |
| 178 | AC mains lead for calculators etc | £0-54 |

ALL PRICES INCLUDE V.A.T.

BI-PAK
DEPT. PW7, P.O. Box 6,
18 Baldock Street, Ware, Herts.



EDITOR
Geoffrey C. Arnold

ASSISTANT EDITOR
Dick Ganderton C. Eng., MIERE

ART EDITOR
Peter Metalli

TECHNICAL EDITOR
Peter Preston

NEWS & PRODUCTION EDITOR
Alan Martin

TECHNICAL SUB-EDITOR
Joe Bishop

TECHNICAL ARTIST
Rob Mackie

ASSISTANT ART EDITOR
Keith Woodruff

SECRETARIAL
Sylvia Barrett
Debbie Chapman

EDITORIAL OFFICES

Westover House,
West Quay Road,
POOLE, Dorset BH15 1JG
Telephone: Poole 71191

ADVERTISEMENT MANAGER

Telephone: 01-261 6636
Dennis Brough

CLASSIFIED ADVERTISEMENTS

Telephone: 01-261 5762
Colin R. Brown

MAKE UP & COPY DEPARTMENT

Telephone: 01-261 6570
Dave Kerindi

ADVERTISEMENT OFFICES

King's Reach Tower, Stamford St.,
London, SE1 9LS
TELEX: 915748 MAGDIV-G

Opinion

ALTHOUGH we have, over the years, reviewed quite a number of kits, for items ranging from intruder alarms to ignition systems, it has long been editorial policy that reviews of ready-built equipment were confined to pieces of test equipment which were likely to appeal to the electronics or radio enthusiast. This was considered to be the right approach for a magazine which was aimed principally at constructors.

We have recently been receiving a growing stream of letters from readers, asking for advice and comment on currently-available communications receivers and other radio equipment for the short-wave listener and amateur, and it is to meet this demand that we are now embarking on a series of reviews. You may rest assured, however, that this change in policy does not mean that we shall be devoting less attention to designs for home-constructed equipment.

It is not our intention to carry out any *Which*-style comparative tests, nor to suggest a "Best Buy". Neither shall we be carrying out full-scale specification testing, in the way that the hi-fi magazines do on tuners, amplifiers and the like. We shall simply try to convey the feel of the equipment as gained from user tests, to give an idea of how good the instruction manual, etc. is, and to say what accessories or options may be available.

In choosing items for review, we have selected what seem to be the most popular, plus any others available within roughly the same price bracket. This month it is the turn of the Yaesu FRG-7 receiver—future plans include several more receivers, transmitters, transceivers, aerials and various pieces of ancillary equipment. We also hope to comment on some professional receivers now available on the second-hand market. We hope that you will find the reviews interesting and useful, and would be glad to receive suggestions for items to include in the future.

Charles Molloy G8BUS—"On the Air" Contributor

Trained as a telecommunications engineer, Charles worked abroad for several years and became an associate member of the IEE. He is now a technical author in electronics.

Interest in the medium waves began when a schoolboy in the mid-1930s, after constructing a receiver for domestic use. He later turned to the short waves after building a one-valve receiver from a design by F. J. Camm in *Practical Wireless*, and became a regular SWL while living in the Middle East.

Although a holder of a class B amateur licence, appearances on 70cm and 2m are infrequent as the main interest in radio these days is in broadcast band DXing.

Charles collects books on the early days of radio, and enjoys messing about in boats. Other interests include classical music, opera and attending ballet with wife Mary, who is a devotee. He is looking forward to retirement and the opportunity to catch up with a number of outstanding radio projects.



Marshall's Bristol move

Subsequent to the recent publishing of Marshall's 1979 product range catalogue their Bristol retail shop has moved.

From 24 April 1979, the new shop will be in larger premises at 108A Stoke's Croft, Bristol. This new location is approximately 5 minutes walk from the main shopping centre of Bristol.

At the same time they announce that they have been appointed sole specialist distributors to the constructor market for the new Mullard 'Teletext' chips—SAA 5000, 5010, 5012, 5020, 5030, 5040 and 5050. These will be available shortly.

Further information from: *Mardata, Kingsgate House, Kingsgate Place, London NW6 4TA. Tel: 01-624 0805.*

Conferences

An IERE/RSGB colloquium is to be held on Tuesday, 5 June 1979 starting at 2 pm at The Royal Institution, Albemarle Street, London W1.

The subject for discussion will be amateur work on microwave propagation and techniques over the last five years, which have made the professionals look hard.

There has been some fascinating work, particularly in the UK, e.g. "s.s.b. at 10GHz" and the colloquium will describe these great developments which are currently going on.

Further details from: *The Conference Secretariat, IERE, 99 Gower Street, London WC1. Tel: 01-388 3071.*

The programme for the Consumer Electronics Symposium, announced by the Society of Electronic and Radio Technicians (SERT) last autumn, has now been finalised, and is to be held at the University of Essex between 8 and 10 July 1979.

Copies of the programme/registration form are being widely distributed and applications from nearly 100 potential delegates have already been received.

As can be seen from the programme, there is a wide representation of authors from industry, broadcasting authorities and servicing organisations who are providing an extremely varied programme of lectures and discussion covering all aspects of electronics in the consumer field.

Further details from: *SERT, Faraday House, 8-10 Charing Cross Road, London WC2H 0HP. Tel: 01-240 1152.*

Club News

The North England Radio Club has a national and European membership, with the heart of the club on Merseyside.

They publish a monthly magazine called 'Spectrum' and meet monthly, usually at The Sports Centre, Grange Road West, Birkenhead.

New members from anywhere in the world would be very welcome. A copy of 'Spectrum' and club information may be obtained for two 9½p stamps, in the UK, or two IRC's from abroad.

The man to contact is: *Norman Monti, 66 Chesnut Grove, Birkenhead, Merseyside L42 0MZ.*

TI 9900 data book

A self-teaching microprocessor design manual—written for beginners and experts alike—is now available from Texas Instruments.

The soft-cover "9900 Family Systems Design and Data Book", will offer in more than 1000 pages a comprehensive selection of educational and applications information that can help users develop a deeper understanding of the complex technology and tremendous potential available in microprocessors.

Combining hardware and software information, the data book should assist both the engineer doing advanced m.p.u. design work and "interested" people who simply want to know more about the subject. It is a complete reference book containing the basic knowledge and data a novice might need to become better acquainted with m.p.u.s—and it carries that knowledge through into complete technical and systems design data needed to use TI's 9900 family of 16-bit microprocessor and microcomputer circuit boards.

The "9900 Family Systems Design and Data Book" costs £8.00 plus P&P, and is available from: *The Modern Book Co., 19-21 Praed Street, London.*

SERT

The Society of Electronics and Radio Technicians is pleased to announce that Mr T. Bryce McCrerrick has become a Vice-President of the Society.

Mr McCrerrick has recently been appointed Director of Engineering to the British Broadcasting Corporation in

succession to Sir James Redmond.

The current President of SERT is Air Vice Marshal Alec Morris and the other Vice-Presidents are Mr Michael Clark (Deputy Group Chairman of the Plessey Company) and Sir Edward Fennessey.

Rally Dates

The Royal Naval Amateur Radio Society's Mobile Rally, will take place at HMS Mercury, Petersfield, Hampshire, on Sunday, 17 June 1979. It will be open to the general public between 1000 and 1700 hours.

The rally is intended as an outing for the whole family, with stands, arena events and displays of interest to all ages. There will also be the usual trade stands.

Further details from: *Wally Walker G4DIU, 9 Woodstock Road, Bedhampton, Havant, Hants PO9 3HX.*

The "East Suffolk Wireless Revival" Amateur Radio Mobile Rally will take place on Sunday, 3 June, 1979, at the I.A.C.S.S.A. Sports ground, Bucklesham, near Ipswich. Commencing at 1100hrs and admission will be 40p, which includes a free raffle ticket.

In addition to talk-in stations on 2m, 70cm f.m. and 80m s.s.b., there will be trade stands, technical displays (featuring Prestel, RTTY and m.p.u.s), refreshments and a licensed bar.

Further details from: *C. P. Ranson G8LBS, 67 Tranmere Grove, Ipswich, Suffolk IP1 6DU.*

"Nunsfield House Community Association Amateur Radio Group" of Derby, hold their 10th Rally, at Elvaston Castle Country Park, on Sunday, 10 June 1979.

It is expected to be their largest rally yet, with over 50 trade stands, along with many other attractions of interest to all the family.

Talk-in stations will be available on callsign GB2ECR, on 2m f.m. Ch. 22, and 70cm f.m. Ch.s SU8, SU20.

Further details from: *Chris Wallace G8PTW, QTHR. Tel: Derby 752358.*

"Bangor & District Amateur Radio Society" hold their mobile rally on 24 June 1979, at the Castlewella Forest Park. There will be all the usual events including trade stands and a "bring and buy" stall.

Further details from: *W. H. Langtry G14AMM, QTHR. Tel: Bangor 65394.*

a.m./f.m. Frequency Readout

William POEL


If you can think of an application for an arrangement of c.m.o.s. logic with a potential sale of a million plus, then the chances are that some enterprising manufacturer of l.s.i. has got a dedicated chip either on the drawing board, or in the market place. The application described here is an ideal candidate, since it is yet another instance of age-old analogue technology being swept aside with digital technology. For a long time past, an accurate readout of a radio receiver's tuned frequency has only been available with large amounts of logic, and large amounts of patience to work out the various i.f. offset programming steps. Such systems have also cost considerably more than the best analogue arrangements, and have consequently been restricted to the very expensive exotica in both consumer and communications applications.

Just as Intersil have revolutionised the concept of the instrument type counter with their ICM7216, OKI Electric of Japan have introduced a family of c.m.o.s. for consumer and communications digital frequency readouts which render all other approaches now quite simply obsolete. For in a 40-pin l.s.i. the counter gives both a.m. and f.m. frequency readout, plus straight kHz frequency count (no offset); drives an l.c.d. directly with no r.f.i. to the radio in question and all this with a current consumption of 4mA with the prescaler off, or 15mA with it on. The unit described here is conceived and designed as a universal readout for long wave through medium wave to a maximum a.m. count of 2.999MHz, including the popular marine DF band where digital readout is almost essential for reasonable operation in congested waters. The f.m. range operates from about 20MHz to 200MHz (with SP8629 prescaler) with a resolution of 100kHz—e.g. a typical readout is 88.1MHz. In the direct mode, the display shows kHz from the a.m. input, and 100s of kHz from the prescaled input.

Purists will complain that 100kHz is insufficient for f.m. resolution—but the display flicker brought about by further resolution is very tedious, and the small number of stations not on 100kHz channels makes the exercise rather pointless for the nuisance involved. And not many f.m. receivers would show up too well from the point of view of oscillator drift.

The Circuit

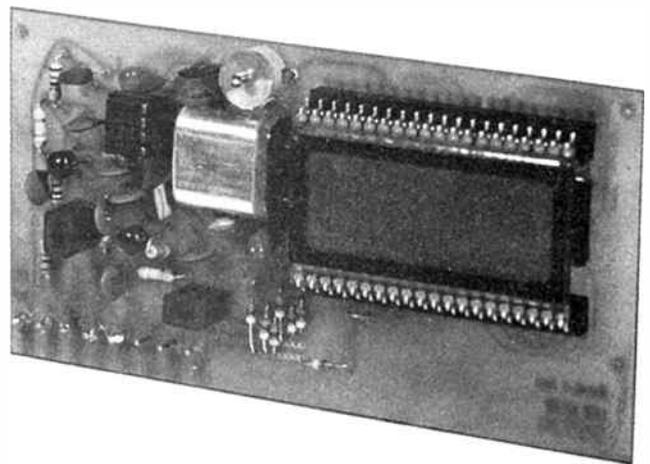The full circuit (Fig. 1) reveals a remarkably simple overall approach compared to previous endeavours to produce this type of unit. Nearly all functions are carried



on within the MSM5526 i.c.—and the few remaining peripheral components are included as an extra for maximum flexibility. On f.m. the divide-by-100 prescaler is an obvious essential, but the input sensitivity of both the SP8629 and the MSM5526 is such that, if the unit is wired into many receivers directly, the pre-amps are not required. However, with these pre-amps using the high f_t BF274 type of transistor, typical sensitivities of $800\mu\text{V}$ on a.m. and 10–15mV on f.m. can be achieved—thus permitting connection of the digital display with the barest minimum of coupling. In the case of one portable radio tried by the author, it is sufficient simply to couple in via a single-ended wire loosely draped around the relevant oscillator section for either a.m. or f.m. So, even if your set doesn't possess specific local oscillator drive, a small piece of wire poked into the oscillator section will work in almost all applications.

The SP8629 has a very useful 6.3V Zener on-chip, permitting a simple but adequate 5.5V stabiliser stage to be built with an external pass transistor. The National Semiconductor equivalent DS8629 does not incorporate this facility, and a separate external Zener must be used. The stabiliser stage has an 82Ω resistor in the output—and this is the result of a mistake when assembling the prototype, since 8.2Ω should have been used. However, the whole circuit worked perfectly when switched on—and it was only when a check was made on the current drain, that this error was discovered, since the unit took a sur-

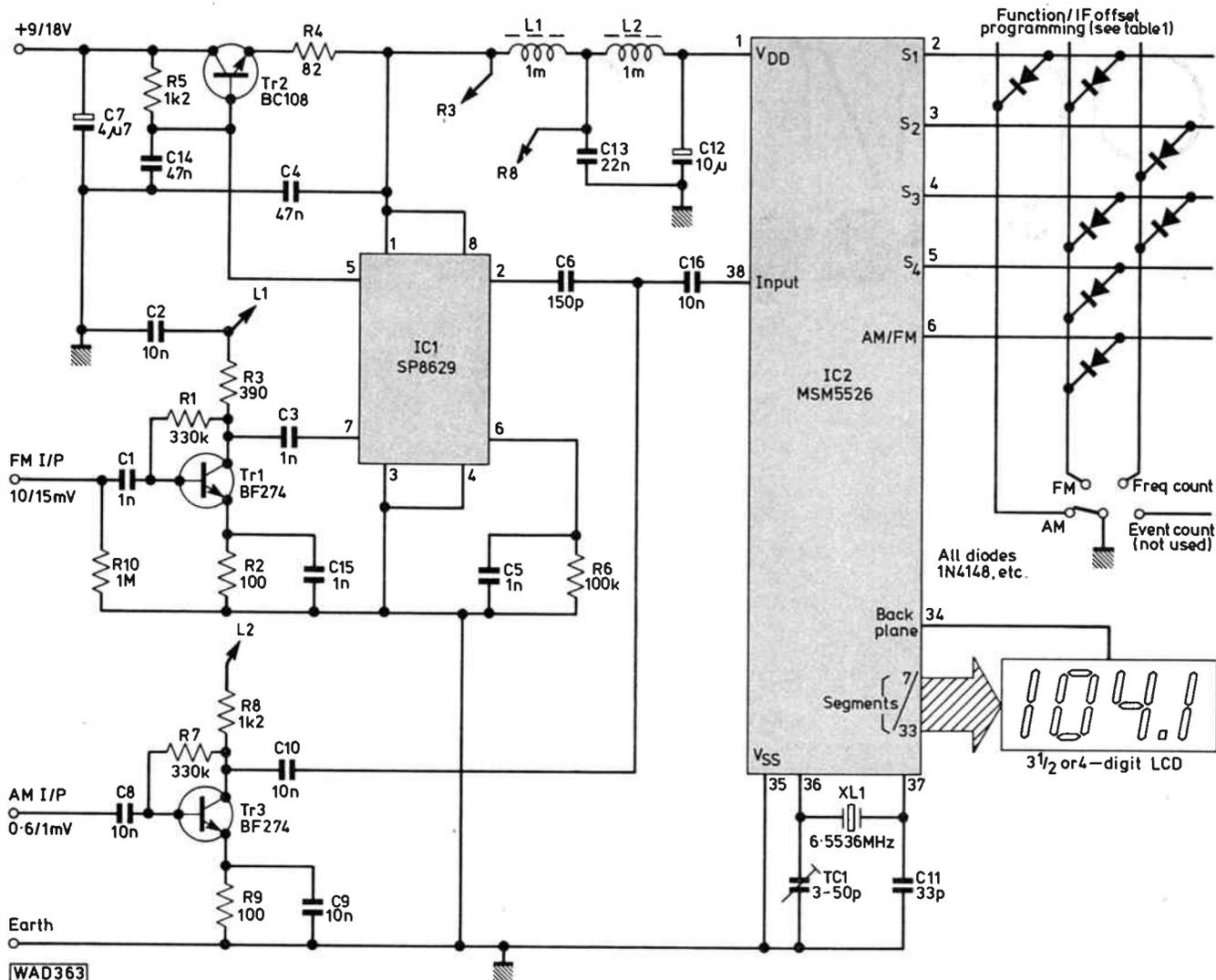


Fig. 1: Complete circuit diagram of the a.m./f.m. frequency readout based on the OKI MSM5526 i.c.

LCD 3 1/2 Digit		LCD 4 Digit	
PIN		PIN	
1	Back Plane	40	Back Plane
2	- Bar	39	Bar
3	b ₄ , c ₄	38	Over Range
4	nc	37	nc
5	nc	36	nc
6	nc	35	nc
7	nc	34	nc
8	DP3	33	nc
9	e ₃	32	g ₃
10	d ₃	31	f ₃
11	c ₃	30	a ₃
12	DP2	29	b ₃
13	e ₂	28	DP4 (colon)
14	d ₂	27	g ₂
15	c ₂	26	f ₂
16	DP1	25	a ₂
17	e ₁	24	b ₂
18	d ₁	23	g ₁
19	c ₁	22	f ₁
20	b ₁	21	a ₁

Table 1

Display Select	Input conditions				IF offset value	
	AM/FM	S1	S2	S3	S4	
AM	H	H	H	H	X	-452.5kHz
	H	L	H	H	X	-454.5
	H	H	L	H	X	-456.5
	H	L	L	H	X	-465.5
	H	H	H	L	X	-467.5
	H	L	H	L	X	-469.5
FM	L	H	H	H	H	+10.68
	L	L	H	H	H	+10.71
	L	H	L	H	H	+10.75
	L	L	L	H	H	+10.79
	L	H	H	L	H	+10.82
	L	L	H	L	H	-10.58
	L	H	L	L	H	-10.60
	L	L	L	L	H	-10.61
	L	H	H	H	L	-10.62
	L	L	H	H	L	-10.63
	L	H	L	H	L	-10.65
	L	L	L	H	L	-10.66
	L	H	H	L	L	-10.69
	L	L	H	L	L	-10.70
L	H	L	L	L	-10.72	
L	L	L	L	L	-10.73	
direct	H	H	L	L	X	none
event counter	H	L	L	L	X	impulses

"H" = open (or Vdd)
 "L" = ground (Vss)
 "X" = either

prisingly low 15mA from a 9V source. The SP8629 is rated at a typical 30mA—so investigation with a voltmeter revealed that both prescaler and display i.c. were happily clocking away with only a 3.8V rail—as a result of the 82Ω mistake. A second unit was built with the same values, and worked just as well—and so it is assumed that most others will too—but if faulty counting is experienced, this 82Ω should be gradually reduced until the circuit settles.

The input to the counter i.c. is common for both a.m. and f.m. count, and the drives from the f.m. prescaler and a.m. pre-amp may be simply paralleled. The output of the SP8629 settles either high or low, depending where the last count cycle left it—and so whilst the outputs were originally paralleled via 10nF capacitors, the f.m. coupling capacitor has to be reduced to 150pF—otherwise the a.m. signal can easily be shunted through the prescaler output stage when it has settled to the low state. A value of 150pF

is still quite enough to pass the very fast edges of the logic output of the prescaler, since counting of the l.s.i. occurs on edges, the actual waveform (which looks quite distorted) is immaterial.

The input to the 8629 must be disabled when reading a.m., and it is important to follow Plessey's application advice, and tie the unused differential input down via a 100kΩ resistor to ground, to prevent spurious oscillation occurring under no-input conditions.

The i.f. offsets are all pre-programmed via a diode matrix, set according to Table 1. Just about every standard offset is available, although occasional 500Hz compromises are called for, e.g. 454.5kHz not 455kHz. With an a.m. resolution of 1kHz, and an average i.f. filter tolerance of 1kHz, this sort of error is unlikely to be at all significant.


The functional setting is likewise matrix controlled, enabling selection via the simplest of all devices, a ground-to-operate switch. As well as the three modes available on this board, a straightforward event counter is also available for batch counting to a maximum of 2999 units, but this feature is not used in this instance.

Had this been a description of a "discrete" approach c.m.o.s. unit, the circuit description would have just about reached the oscillator stage, but instead, there is nothing more to say!

Construction method

The printed circuit board layout, Figs. 2 and 3, employs a useful technique when using direct drive to l.c.d.s from l.s.i., namely placing the i.c. under the display. This technique saves space—and cuts the only marginal area of possible interference (from the l.c.d. backplane strobe) to a bare minimum. Construction on anything but the properly made p.c.b. is not really feasible. Fixing holes for mounting are provided so that the unit may be fitted directly behind the receiver front panel. The c.m.o.s. MSM5526 is not a particularly fragile device, but the usual care should be taken when soldering, to avoid static damage, caused by poorly earthed soldering implements, or earth leakage currents. The p.c.b. is laid out for either HC13 or HC18 style crystals, and since 6.5536MHz is a standard binary frequency, the supply is not generally a problem.

Great care must be taken when mounting liquid crystal displays, since these are not only costly, but very fragile if pressure is applied unevenly. A socket must be used to raise the l.c.d. above the rest of the components, and either socket strip or a 40-pin d.i.l. socket cut in half is suitable for the purpose. Molex i.c. pins are not a good idea since in strips of 20, it is very difficult to accurately locate the pins of the display. The electrical contact is also somewhat more chancy at this sort of length, since a small displacement of one pin can cause a lot of trouble.

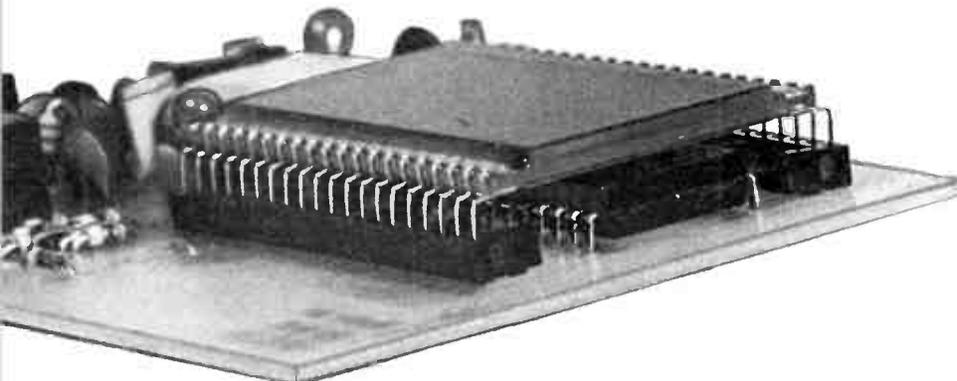

The MSM5526 is mounted directly on the board and the liquid crystal display is mounted over it, using i.c. sockets to space it from the p.c.b. (see text)


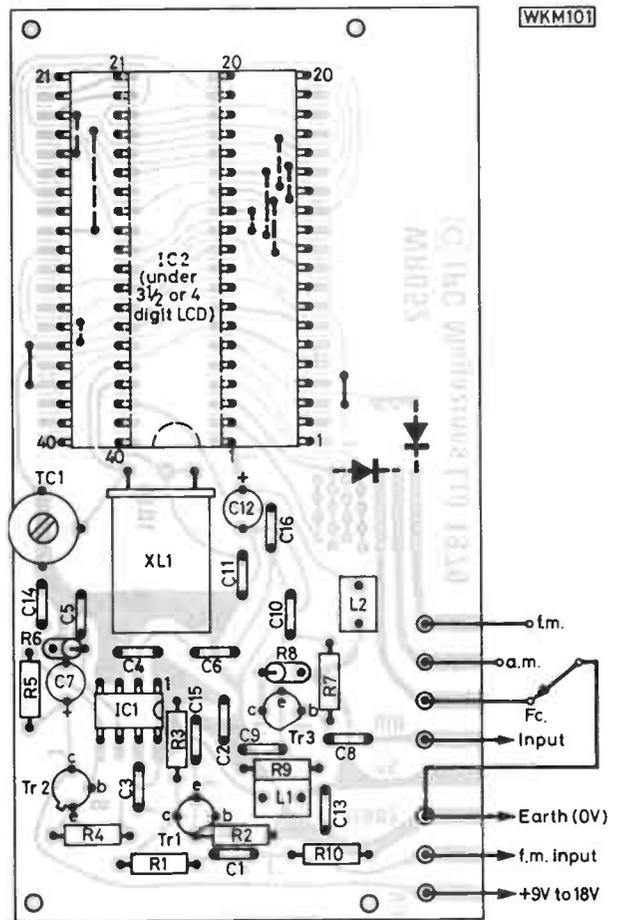
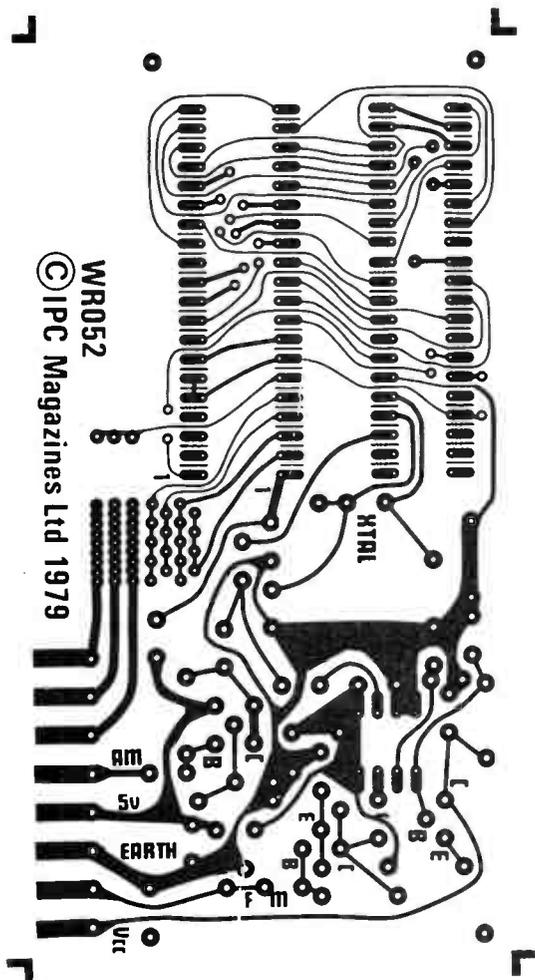



Fig. 2 (above): Full-size track layout of the p.c.b.

Fig. 3 (above right): Component layout and details of external connections to the p.c.b. The switch will normally be part of the wave-change switch of the associated receiver. When using a $3\frac{1}{2}$ -digit I.c.d., two "U"-links of insulated wire should be soldered to the track side of the p.c.b., linking pins 2 and 5/6, and pins 3 and 7 of the display

Fig. 4: Pin-outs of the SP8629 (below) and the MSM5526 (right)

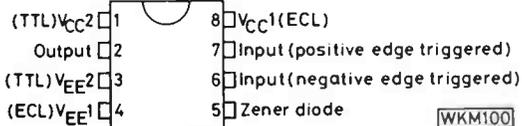


WKM100

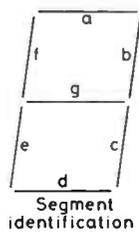

Segment identification

Segment out

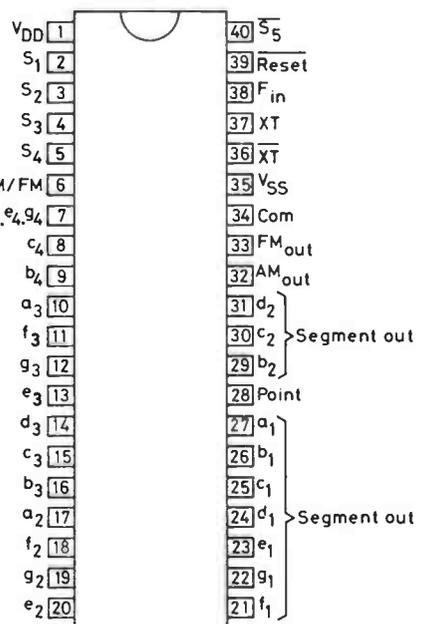

WKM102

★ components

Resistors

0.25W 5%

82Ω	1	R4
100Ω	2	R2, 9
390Ω	1	R3
1.2kΩ	2	R5, 8
100kΩ	1	R6
330kΩ	2	R1, 7
1MΩ	1	R10

Capacitors

Ceramic disc or plate (lead spacing 5mm max.)

33pF	1	C11
150pF	1	C6
1nF	4	C1, 3, 5, 15
10nF	4	C2, 8, 9, 10, 16
22nF	1	C13
47nF	2	C4, 14

Tantalum bead

4.7μF	1	C7
10μF	1	C12

Sub-min trimmer

3-50pF	1	TC1
--------	---	-----

Semiconductors

Transistors

BF274	2	Tr1, 3
BC108	1	Tr2

Diodes

1N4148	as required for programming (see Table 1)	
--------	---	--

Integrated circuits

MSM5526	1	IC2 (OKI Electric)*
SP8629	1	IC1

Inductors

1mH	2	L1, 2 (Toko 7BA 144LY-102)*
-----	---	-----------------------------

Miscellaneous

XL1 6.5536MHz Crystal, Style HC13 or HC18 wire-ended*
 4-digit (or 3½-digit) liquid crystal display
 Socket for l.c.d. (see text)
 Printed circuit board Ref. WR052
 Terminal pins (8 off)

*Available from Ambit International and Watford Electronics

Switch-on and test

Provided the components are located correctly, then there is nothing to go wrong apart from your soldering. Check the very fine tracks for splashes, and clean the board with flux remover if available. Using a current-limited power supply (for extra security), apply 5 volts at first, gradually turning up to 12V if the current drain is not excessive—indicating a short circuit somewhere. Switch to the desired input, and place a finger on the relevant pre-amp input, when some stray counting should occur from the pickup thus provided. Remember, this is very sensitive.

With a suitable radio to hand, place a pickup coil near the oscillator, and feed this to the counter input via r.f. coaxial cable. Something is almost certain to happen, and usually no more trouble than this is necessary. In fact, a single-ended pickup is frequently enough, though not suitable if more than 150mm long. If you don't know the exact i.f. offset, assume 10.7MHz high for f.m., and in the f.m. mode, tune to a station of known frequency. If the display reads incorrectly—say 89.2 instead of 89.1 with the tuning indicator zeroed—then the i.f. offset should be adjusted to 10.79MHz (the closest to 10.8MHz available) by diode programming. Many of the finer variations of offset will not be apparent unless you have a very accurately calibrated signal source handy.

To set the internal clock accurately, switch to Direct Count and with a signal generator and reference counter, tune to 999kHz so that the generator output reads 999.4999kHz. Tuning to 999.501 should cause the counter to change over to 1000kHz, and the trimmer capacitor on the crystal input to the MSM5526 may then be adjusted to provide this threshold point. With the trimmer approx 30 per cent enmeshed, the whole unit is sufficiently accurate to be self calibrating anyway, so do not worry too much about these very fine adjustments if you cannot

get access to appropriate equipment. Another way is simply to count the crystal oscillator frequency on a separate counter so that it is trimmed for exactly 6.5536MHz (take care not to load the crystal—try to use inductive coupling if possible).

To set the a.m. offset, tune to a known frequency with the offset pre-programmed for 469.5kHz (nearest available to 470kHz) for most UK- and European-made sets, and 455kHz for most Japanese sets, and check the error. Simple maths will tell you what to do—e.g. if the station is known to be on 910kHz, and the counter says 905 when the i.f. is set for 470kHz, then reprogramme the offset for 465.5 and all will be well.

Applications

Apart from new equipment, there is obviously a large retrofit application for improving existing equipment—since the accuracy of frequency display has let down many otherwise good designs. Varicap diode designs can occasionally put strains on analogue scale design, since the end-point capacitance can vary widely, although the diodes themselves remain well matched. This display takes away those problems, and does away with the last remaining mechanical headaches of the set designer.

One point which is very important about the MSM5526 is the fact the display is totally static. This means that there is no multiplexing interference—and the only potential source is in the shape of the backplane strobe, which is very, very low power for an l.c.d. Thus without screening, this device can readily be used without problems in any radio environment, from supplies ranging from 8V to 20V d.c. (thanks to the regulator on board). So next time the drive cord snaps, forget about a replacement and fit a digitally accurate alternative. ●

**SPECIAL
PRODUCT
REPORT**

CONTINENTAL SPECIALTIES CORPORATION



LOGIC PROBE KIT

If you are involved in digital electronics it is essential that you have some means of detecting pulses and logic states. Without this necessary equipment you will be totally in the dark when trying to find out why your latest creation does not work.

There are many logic probes on the market but for the amateur they tend to come a touch on the pricey side. Continental Specialties Corporation, who also make a range of logic probes, have recently introduced a kit for a probe which will detect and display logic levels, pulses and voltage transients.

The kit is complete down to the last piece of wire and even includes a length of solder. All the components appeared to be of good quality and fitted the holes drilled in the glass fibre printed circuit board without any problems.

The instruction manual is very comprehensive and covers not only the building of the probe but also notes on how to use it.

★ specifications

Input impedance: 300k Ω

Threshold: Logic 1 (Hi-l.e.d.) 70% Vcc
Logic 0 (Lo-l.e.d.) 30% Vcc

Detectable pulse width: 300 nanoseconds min.

Input signal frequency: 1.5MHz max.

Pulse detector: High-speed pulse train or single events (positive or negative transitions), active 0.1 second pulse stretcher

Input voltage: \pm 50V continuous, 120V a.c. for less than 15 seconds

Power requirements: 5 volt Vcc at 30mA
15 volt Vcc at 40mA
25 volts max., with power lead reversal protection

Physical size: 147 x 25.4 x 17.8mm

Weight: 85 grams



Construction proved to be very simple and straightforward, the step-by-step assembly instructions proving easy to follow. Unlike traditional British component placement drawings however this one did not show the copper track pattern of the p.c.b. and no holes are shown so that it is very important to check twice that the components are correctly placed.

No problems were encountered and the probe worked first time, but if you are unfortunate a page is devoted to trouble-shooting and two pages to testing the probe following construction.

The plastics case, which is available separately and has been used for the *PW* Car Test Probe, is very neat and the two labels supplied with the kit are self-adhesive giving the finished probe a professional look.

The probe is simple to use, requiring the power leads to be clipped to suitable voltage rails on the circuit under test and the probe tip to be held against the test point.

Indication of the status of the point is by a combination of three l.e.d.s which light, or pulse, depending upon the logic state being investigated.

As a simple means of determining logic states this kit is very good value for money.

Dick Ganderton

SEE NEXT MONTH'S ISSUE OF
PRACTICAL WIRELESS FOR DETAILS
OF A SPECIAL INTRODUCTORY OFFER
FEATURING THIS KIT

Ideas DEPARTMENT

Some original circuit ideas provided by our readers. These designs have not been proved by us, and we cannot therefore guarantee their effectiveness. They should at least provide a basis for experimentation.

Why not send us your idea? If it is published, you will receive payment according to its merits. Articles submitted should follow the usual style of PW in circuit diagrams and the use of abbreviations. Diagrams should be clearly drawn on separate sheets, not included in the text.

Each idea should be accompanied by a declaration that it is the original work of the person submitting it, and that it has not been accepted for publication elsewhere.


WORKBENCH AMPLIFIER

Although there are plenty of amplifier i.c.s and modules available, there are many applications where discrete circuitry can hold its own on cost and simplicity. One of these is a battery-powered audio amplifier for workbench use.

The input signal goes via the volume control VR1 to Tr1, which is a high-gain voltage amplifier. Its output is applied to the bases of Tr2/Tr3, the complementary output pair, with R1 providing the necessary standing bias. For reasons of simplicity and cost, no form of temperature compensation has been included.

Two negative feedback paths are included. Resistor R5, which is basically the collector load for Tr1, also provides bootstrapping for the output stage. Resistor R2 provides base bias for Tr1 and also overall negative feedback. Audio quality may be improved at the expense of reduced output by lowering the value of R2. Capacitor C3 decouples the supply, and helps to maintain audio quality when the battery approaches the end of its life.

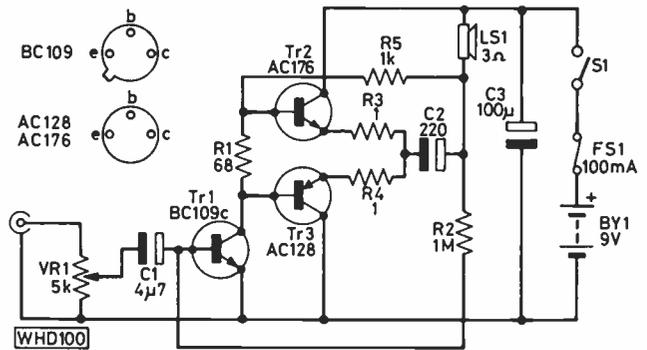Transistors Tr2 and Tr3 should be purchased as a



matched pair, and must be fitted with heat-sinks—the push-on, finned type should suffice. With no signal applied, the total consumption of the amplifier should be less than 35mA.

D. L. Jones,
Denbigh,
Clwyd.


TACHOMETER/DWELL METER

This circuit utilises a 555 timer chip in a dual function as a tachometer or dwell meter. In the tachometer mode, the input signal is taken from the car's contact breaker as a square-wave and fed via a capacitor to pin 2 of the timer, realising a high mark/space ratio. The two switched ranges, 0 to 1000 r.p.m. and 0 to 5000 r.p.m., are calibrated by a 20kΩ and a 1kΩ potentiometer.

In the "dwell" mode, the input capacitor is by-passed, maintaining a square-wave at the input of the device, which means that the output at pin 3 is an inverted version of the input waveform. In the "dwell" mode, only the lower of the two tacho ranges should be switched in.

The circuit requires a minimum supply of 12V for consistent operation.

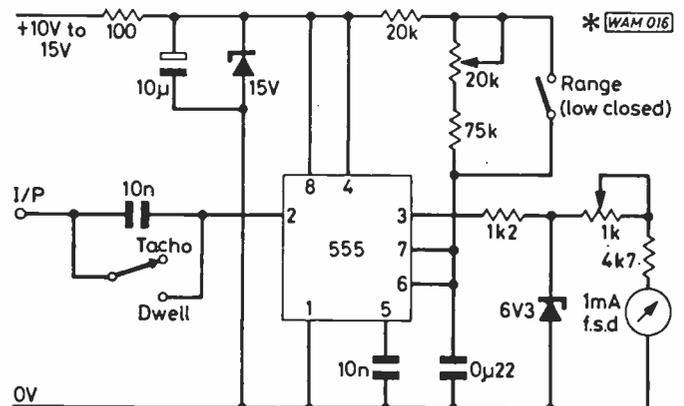R. J. Jenkins & M. E. Taylor,
Knebworth,
Herts.



Hey, Good Looking!



P.W.

'WINTON'

Beautiful innit?, but a swish exterior can often be an eye catching cover for some very ordinary "guts", so what's so different about the WINTON?

Well, for a start we have discarded Bi-Polar output devices in favour of the far superior performance of the Hitachi Power MOS-FETS, which until now have only been available in some of the most expensive Hi-Fi Amplifiers around, (and we consider £700 to be expensive with a capital E!). Secondly, our extremely low distortion figures are obtained at FULL RATED OUTPUT with both channels driven, across the entire audio spectrum.

Further, at these power levels 2nd and 3rd order inter-modulation components are typically less than 0.005% (See the March issue of P.W. for the full spec' and a few shots from the Spectrum Analyser.) Whilst we freely admit that ownership of a Winton will not prevent your hair from falling out, nor warts from growing on your nose, you will feel a nice sense of achievement when the job is complete, and you will own an Amplifier that will make your mates positively green with envy, until that is they see the light and obtain one of their own.

The WINTON Kit is available in the following form:-

Pack (A) Capacitors & Fixed Value Resistors	Price Inc. V.A.T. & carriage.
Pack (B) Switches, Potentiometers, Pre-Sets & Knobs	£21.45
Pack (C) Printed Circuit Board, and Terminal Pins	£13.26
Pack (D) Hardware Pack, consisting of Chassis, Heat Sinks, Cabinet, Screws, Wire, Fuseholders etc., and a Brushed Aluminium Fascia Front Panel.	£8.10
Pack (E) Semiconductors (including HITACHI MOS Power Fets)	£32.99
Pack (F) Toroidal Mains Transformer	£30.53
Complete Kit of all parts necessary to build the WINTON	£17.22
	£120.00

ORDER WITH COMPLETE CONFIDENCE (Cash with order please) FROM:-

T. & T. ELECTRONICS. GREEN HAYES, SURLINGHAM LANE, ROCKLAND ST. MARY, NORWICH, NORFOLK. NR14 7HH.
PLEASE ALLOW 28 DAYS FOR DELIVERY.

New Heathkit electronic test equipment course.

- Section 1. Analogue and digital meters.
- Section 2. Oscilloscopes.
- Section 3. Frequency generation and measurement.
- Section 4. Special measuring instruments.

New Heathkit car electrical systems course.

- Section 1. Electrical principles of the car.
- Section 2. Starting system fundamentals.
- Section 3. Car charging systems.
- Section 4. Accessories and body electrical.

Two new self-instruction courses from Heathkit. Based on step-by-step programmed instructions, they let you learn at your own pace in your own home.

Each course is complete and contains audio/visual material, text, and parts for 'hands on' experiments with the optional Heathkit experimenter trainer. So all you need is a cassette player and the will to learn.

Full details of Heathkit courses are available in the Heathkit catalogue, together with hundreds of kits you can build for yourself - computers, oscilloscopes, transceivers etc. ... Send for your copy now.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451). Registered in England, No. 606177.

Soldering Iron offer FREE



New Heathkit CI 1265 Digital Tach/Speedometer.

Push-button digital readout. Displays engine speed/rpm. Accurate to 1 mph or rpm variations of 100.

To: Heath (Gloucester) Limited, Dept. PW779 Bristol Road, Gloucester, GL2 6EE.
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.
Please send a copy of the Computer Brochure. I enclose 20p in stamps.

Name _____
Address _____

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

When you receive your catalogue you will get details of this free offer.



HEATHKIT

HEATH
Schlumberger

UNICOM 21

To celebrate the 21st anniversary of the birth of their company, South Midlands Communications Ltd. are holding an Exposition and Symposium on Communications, called Unicom 21, on 22/23 June at Kempton Manor, Sunbury-on-Thames. Opening hours for the general public are 6pm–10pm on the Friday and 10am–8pm on the Saturday. Kempton Manor is adjacent to the M3 and A305, alongside Kempton Park Race Course.

There will be demonstrations of equipment by SMC, Strumech, Ascot Antennas and Microwave Modules, with experts on hand to answer all your questions. *Practical Wireless* will be there too, showing a selection of recent projects for the radio enthusiast.

The programme of lectures includes such subjects as: "A Single-chip Frequency Synthesiser", "FM vs SSB Bandwidths", "WARC 79", "Direct Conversion Receivers" and "Working more DX".

There will be a talk-in station operating on channel S22 with the special call-sign GB3SMC. Full bar and buffet facilities will be available.

Exhibitions

"The Great British Electronics Bazaar" is to be held at Alexandra Palace between 28 and 30 June 1979. The Bazaar is aimed at attracting the amateur, hobbyist and small professional buyer.

Among the stands booked by both large and small companies and organisations, will be demonstrations of building electronic circuits and home computer systems, to suit virtually everyone.

It is hoped that the event may be televised and application has been made for an amateur radio station with its own call sign.

Free tickets (send s.a.e.) from: *The Great British Electronics Bazaar, 34–36 High Street, Saffron Walden, Essex CB10 1EP.*

Computer shop

Since Friday, 16 March 1979, London's West End shoppers have been able to walk up to a counter and say "Can I have a computer, please?" And

that's precisely what they can do at The Byte Shop, located in the capital's home electronics heartland, Tottenham Court Road.

At The Byte Shop, the fascinating world of computers is only a counter's width from the man in the street. For the first time, businessmen in Central London will be able to nip out at lunchtime for an impromptu demonstration. Everything needed to computerise a small to medium sized business is now on show—from the smaller self-contained systems costing a few hundred pounds to the most professionally-configured systems incorporating external printers and visual display units priced up to around £15 000.

The Byte Shop also offers a broad selection of advanced computer games, with shoppers being invited to pit their skills against chess, poker and backgammon programs compiled by experts. Further information from: *The Byte Shop, 48 Tottenham Court Road, London WC1.*

Cartoon computer

A unique computerised system to expedite the production and lower the costs of making animated films is now being used by the Swedish Broadcasting Corporation (SBC) for its television services.

Conventional methods of preparing animated films are enormously time-consuming. Most of the work is very repetitive since each second of finished film requires from 20 to 25 almost similar drawings.

Under the new system, utilising a Sperry Univac 1100/11 computer, SBC uses a technique developed by Alan Kitching, an animation and data processing specialist, who manages Grove Park Studios in Camberwell.

The technique, known as ANTICS, begins with a basic drawing being prepared and entered into the computer using a special light pen. By means of special command words and codes, direction, speed and position specifications are also fed into the computer. The basic drawing can then be modified in different ways, for example, it can be shrunk, enlarged, panned, skewed, shaken or reversed. It can also be induced to rotate, jump, rock, etc. The system now contains some 40 commands, but Alan Kitching is working on further expansion.

One of the latest concepts within ANTICS is the Skeleton command. In response to a Skeleton command, a part of the basic drawing—such as a human character—will move in a natural manner. Using single skeletal figures the operator can specify a pattern of movements based on key positions. The computer then automatically creates all the intervening pictures needed to complete the overall sequence of movements and the final result appears as a smooth natural motion which matches the position of the skeletal figures entered into the computer.

With the new ANTICS system, sophisticated films that would have taken more than six months to produce by conventional means can be made in a few man-weeks. *Sperry Univac, 65 Holborn Viaduct, London EC1.*



PRODUCTION LINES

alan martin

Mighty Midget

Toolrange, distributors of the Panavise range, announce availability of the Model 502 Precision Panapress. This small but tough arbor press, less than



178mm high, is ideal for pressing bearings, forming and assembling small parts, staking rivetting and broaching. Built to stand the rigours of daily production line usage, the press has a rated capacity of 500psi.

The arbor and table plate are pressure die cast in high strength Zamak III alloy. The operating mechanism and operating lever are hardened ground steel, leverage ratio 13:25:1. Throat depth is 64mm and vertical capacity is 89mm. Ram ends are supplied unfinished for custom tooling by the user and the operating ram is fully reversible. A unique feature of the Panapress 502 is the four self lubricating adjustment gibs which give fine directional control of the ram/plate alignment.

The Panapress 502 is available at £36 plus VAT, from Toolrange Ltd., Upton Road, Reading RG3 4JA. Tel: (0734) 29446 or 22245.

Test prod connector



The new Kaffka range of connectors being imported from Germany by West Hyde consists of six types, made in 5mm or 10mm spacing. They dovetail together to form a connector of any desired configuration.

They are of high-quality precision manufacture in red Nylon 66. The connector bodies are of zinc-plated brass with leaf springs to avoid conductor damage from the chromed nickel

plated clamping screws.

Behind each screw there is a hole for a 2mm test prod. Current rating is 13 amps and accept cables of 2.5mm², with temperature range of from -30°C to +120°C.

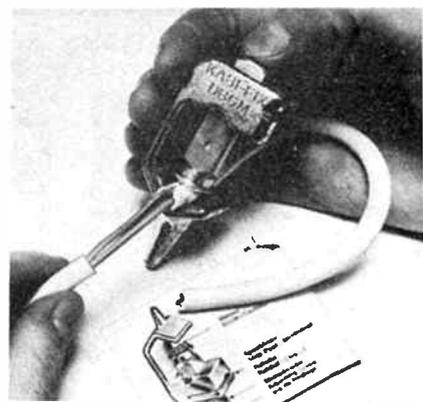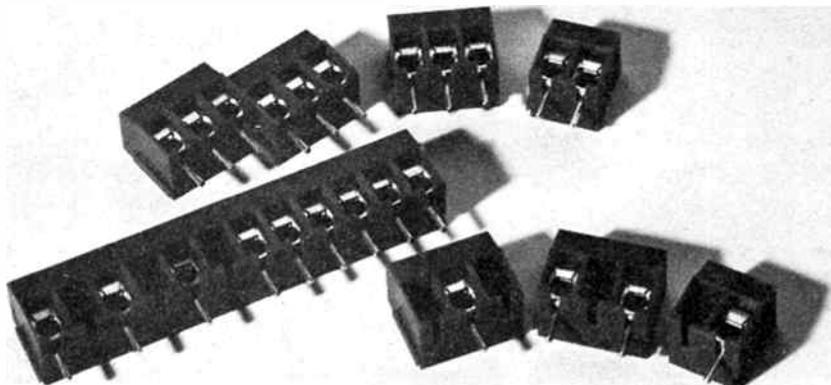Prices range from 7p to 23p each and are available from: West Hyde Developments, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET. Tel: (0296) 20441.




Handy Stripper

Recently introduced into the Carel Components catalogue, is the "Kabifix" DBP cable stripper which can effectively and accurately end or centre strip cables up to 25mm diameter.

Complete with a blade which easily adjusts to the insulation thickness and swivels automatically, the tool can be snapped closed over the cable, rotated round the insulation or pulled longitudinally to expose the cable.

Durable and easy to operate, this handy stripping tool supplied with an instruction leaflet and plastic pouch, costs £8.25 plus VAT.

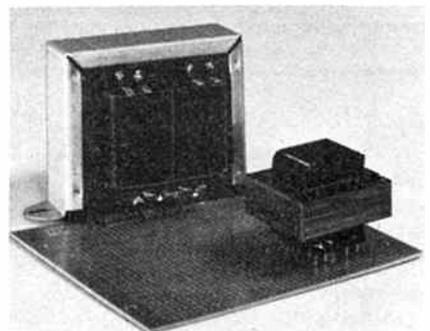Carel Components, 40-44 The Broadway, Wimbledon, London SW19. Tel: 01-540 7186.



Transformers

A new range of high quality competitively priced transformers, designed to conform generally to BS2214, is now being stocked by Verospeed.

All the transformers are fitted with full shrouds and are varnish protected. Two 120V windings are provided for the primary and they may be connected in series or parallel for operation at 50 and 60Hz. Two secondary windings are provided for series or parallel connection. Various output voltages from 0-3V to 0-20V are available within a range from 1.2VA to 50VA.

Further details are contained in the new Verospeed catalogue, available direct from: Verospeed, Barton Park Industrial Estate, Eastleigh, Hampshire SO5 5RR. Tel: (0703) 618525.

Learning to spell

The latest learning aid from Texas Instruments, known as "Spelling B", uses proven word/picture association techniques to help children progress in spelling regardless of their basic writing skills. Using an alphabetical calculator-type keyboard and display, combined with a picture book containing 264 carefully selected, colourful pictures of familiar objects, "Spelling B" is designed to provide an early introduction to word recognition, and also incorporates a series of simple and entertaining word games to improve basic reading skills.

In operation, the "Spelling B" selects and displays a picture number, the child finds the numbered picture in the book, and then spells the name of the picture by pressing the letter keys. As the letters are keyed they appear in the display, and at the end of each word the display signals "right or wrong". If the word is misspelled, the

child is given a second attempt, and if this is wrong the correct answer is displayed. The number of correct answers is displayed as a "score" at the end of each set of five words.

"Spelling B" is programmed so that one of three different levels of difficulty can be selected. In addition, a variety of pre-spelling activities for younger children plus word games for all ages are available.

Among the games which add fun and variety to "Spelling B" are: "Starts with", a pre-spelling exercise in which the child only has to enter the first letter of the displayed word; "Missing letter", in which a word is selected at random and displayed with letters missing; "Mystery word", a variation of "Hangman" in which players have to guess words one letter at a time; and "Scramble", in which up to five words can be put into a memory in anagram form and recalled for "unscrambling" at a later stage.



The "Spelling B" costs £19.95 (r.r.p. including VAT), and is available through the usual distributors.


Texas Instruments Ltd., European Consumer Division, Manton Lane, Bedford MK41 7PA.

Portable 'scope

The new Model SB15M lightweight portable oscilloscope from Albol Electronic is claimed by the makers to break all records for cost-effectiveness for a professional/amateur instrument.

Albol say that the bandwidth goes up to 15MHz within 3dB limits and nine ranges cover, with an accuracy of 5% 10mV to 20V/cm on the 45 by 60mm measuring area of the c.r.t. Input impedance is $1M\Omega \pm 3\%$ in parallel with 30pF, and the maximum input voltage is 400V.

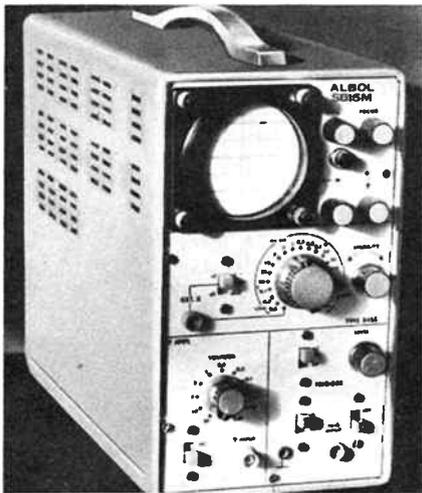The timebase can be freely running or triggered, and is displayed on 19 calibrated ranges from 0.5s/cm to 0.5µs/cm. Synchronisation can be either internal or external, with the a.c. mode giving 20Hz to 1MHz, and the h.f. mode 1 to 15MHz. Trigger sensitivity is said to be 0.5cm of the display on "internal", or 0.5V p-p on "external".



Bandwidth of the X amplifier, within 3dB, goes from d.c. to 3MHz, with an input impedance of $1M\Omega$ in parallel with 45pF. The X deflection coefficient varies from 0.3 to 1.5V/cm. An attractive feature of this truly portable scope is that it can operate from 220 to 240V mains (using the optional adaptor) at 50 to 400Hz, with a power consumption of 40VA, or else from internal 1.5V cells giving 12V d.c. (rated then at 27W).

The width of the SB15M is 150mm, depth 340mm, and height 280mm, and it weighs only 7.6kg. Price is £150 plus VAT.

Available from: Albol Electronic & Mechanical Products Ltd., 3 Crown Buildings, Crown Street, London SE5 0JR. Tel: 01-703 2311.

New Sinclair DFM

Latest from Sinclair's new instrument product range, is a high specification, low cost, digital frequency meter, called the PFM200.

Designed to provide the performance of high quality bench-style instruments with the portability of a 158 x 76 x 45mm unit in a light (6oz) but rugged case, the PFM200 is priced at only £49.80 plus VAT, which should permit most laboratory engineers, service technicians, students and hobbyists to possess their own personal digital frequency meter.

Its bright, sharp 8-digit display with variable accumulation period gives high resolution coverage from low audio frequencies right up to v.h.f.

without the need for complex range changing and with exceptional sensitivity of 10mV. Guaranteed range is 20Hz to 200MHz, typically higher, with a frequency resolution down to 0.1Hz. Power is from a 9V battery or approved a.c. adaptor.

Supplied complete with test leads and probes, protective wallet and operator's manual, optional extras are a.c. adaptors for 117V, 220V or 240V; de-luxe padded carrying case with lead storage compartment; and a connector pack comprising BNC, coaxial, DIN and phono adaptors plus telescopic aerial for direct signal pick-up from nearby transmitter.

A technical information leaflet on the PFM200 is also available from: Instrument Sales, Sinclair Radionics Ltd., London Road, St Ives, Huntingdon, Cambs PE17 4HJ. Tel: (0480) 64646.



numbers without tears

Dr G. BROWN

The aim of this design was to produce an educational toy capable of teaching rapid number recognition to children of 2½ years and upwards. The absolute minimum of instruction should be necessary, the idea being that the child learns as he plays, without external influence. The toy should thus be interesting to play with.

To a young child this means: (a) visual stimulation—things should be seen to happen; (b) tactile stimulation—the instrument should respond to touch, to pressure—there should be something to turn, something to switch.

This simple unit has all these facilities and can hold a child's attention for remarkably long periods. It can also double as a single die for use with other games.

General Features

Fig. 1 shows the basic design blocks. A swept-frequency clock generator feeds the first decade counter, the digit outputs of which are used to drive ten light-emitting diodes (l.e.d.s) arranged in a circle. A second decade counter, fed from the same clock source, drives a single 7-segment l.e.d. numeric display. As the clock frequency rises from zero, the circular l.e.d. display assumes a rotating motion with a visible acceleration. As the clock frequency then falls to zero, the "flywheel" effects slows and stops at a random position.

The l.e.d.s are labelled 0 to 9, as are the positions on the manual number selector, which is a rotary switch. Provided that both decade counters are reset to zero initially, they will always remain synchronised, i.e., if the flywheel stops at position "4", then the 7-segment outputs will correspond to the figure 4 also.

The number selector is wired such that the 7-segment display is only illuminated when this switch is turned to the same number at which the flywheel has stopped. The normal fixed-frequency clock is used when the device is employed as a die.

Some simple logic is included to make the toy more interactive with the child, and will be described in the appropriate sections.

The Swept-frequency Clock Generator

For this particular application, a manually-initiated frequency sweep was required from zero up to about 100Hz and back again to zero. The circuit is shown in Fig. 2.

The clock is designed around the ubiquitous NE555V integrated circuit connected in the astable mode.

If the circuit to the left of the dashed line is studied, the timing components R1 and C1 are easily recognised. C1 is

charged up through R1, and IC1 will discharge C1 when the voltage at point A reaches 0.67V_{DD}. The negative-going edge corresponding to the discharge of C1 re-triggers the cycle and the system becomes astable, the frequency of oscillation being given by:

$$f = \frac{1.44}{R1 \times C1} \text{ Hz}$$

In the circuit to the right of the dashed line Tr1 and Tr2 are connected as a Darlington pair controlled by the touch plate connected to the base of Tr2. The quiescent-state voltage at point A is controlled by resistors R1, R2, and R3, the two transistors being effectively open-circuit. A simple Ohm's Law calculation shows that point A is held at 0.65V_{DD} and, because IC1 will not discharge C1 until point A reaches 0.67V_{DD}, the clock oscillator is biased off, its output being a logic "1" in this condition.

When a finger is applied to the touch plate, charge flows into the electrolytic capacitor, C2. As this charges up, the potential at point B rises. With C2 fully charged (after about one second), both transistors are turned fully on and point B is taken almost to V_{DD}. Thus the Darlington pair may be regarded as a variable resistance, R_t, between point B and V_{DD}, this resistance varying from infinity to near zero. As soon as R_t becomes finite, point A is lifted above the threshold value of 0.67V_{DD} and oscillation begins.

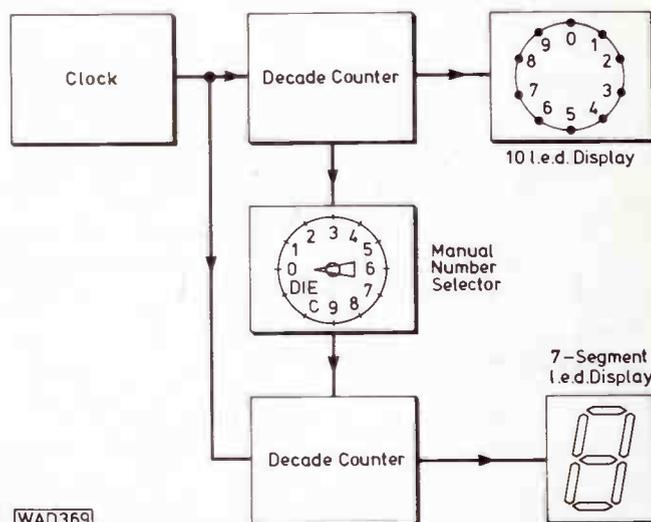


Fig. 1: The basic block diagram of the numbers toy

The frequency of oscillation is still given by the above equation, except that R1 must be replaced by the effective instantaneous value of R1, R2 and Rt. In the limit, with Tr1 and Tr2 turned fully on, R1 and R2 are virtually in parallel between Vdd and point A, and have an effective resistance of 24.8kΩ. This gives a theoretical upper frequency limit of:

$$f = \frac{1.44}{2.48 \times 10^4 \times 3.3 \times 10^{-7}} = 176\text{Hz}$$

This figure is not attained in practice because Rt never falls completely to zero.


When the finger is removed from the touch plate, C2 discharges slowly through Tr1 and R3, and Rt increases correspondingly. The frequency of oscillation falls and finally reaches zero when point A falls again below its threshold value. This decay time is of the order of 10 to 15 seconds.

Switching R4 into the biasing network by closing S1 holds point A just above threshold and a constant-frequency output of about 15Hz is produced. The use of this clock frequency is described in a later section.

The touch plate is very sensitive in its action, and this encourages the child to experiment as he watches the effects of his finger's pressure illustrated on the flywheel display.

The Decade Counters

Apart from the NE555V oscillator, this instrument employs c.m.o.s. devices which are relatively cheap and are ideal for this purpose. Fig. 3 shows the circuit diagram of

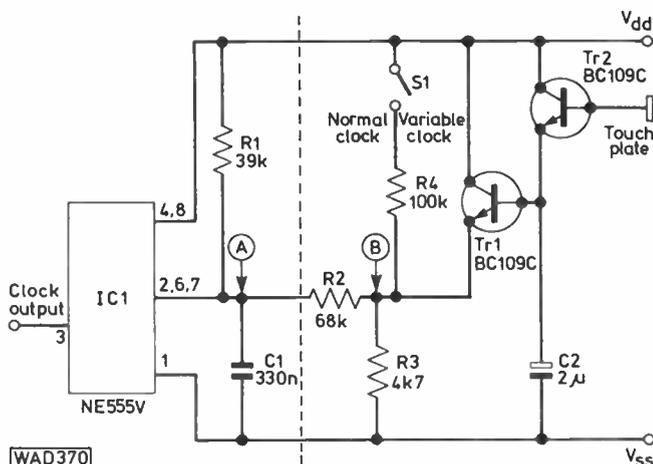

WAD370

Fig. 2: Circuit diagram of the swept-frequency clock generator

the first decade counter and the transistor drivers for the 10-l.e.d. flywheel display. The 4017 decade counter is fed from the clock generator described above. In order to drive the flywheel l.e.d.s at 20mA, ten transistors operating as emitter followers are used. As only one l.e.d. is illuminated at any instant, only one current limiting resistor, R10, is necessary. It will be noted from Fig. 3 and Fig. 4 that the "reset" and "clock inhibit" functions are made common to both decade counters. This is to ensure complete synchronism of the two counters at all times. The combination of C3 and R5 resets both counters to zero when power is first applied.

WAD371

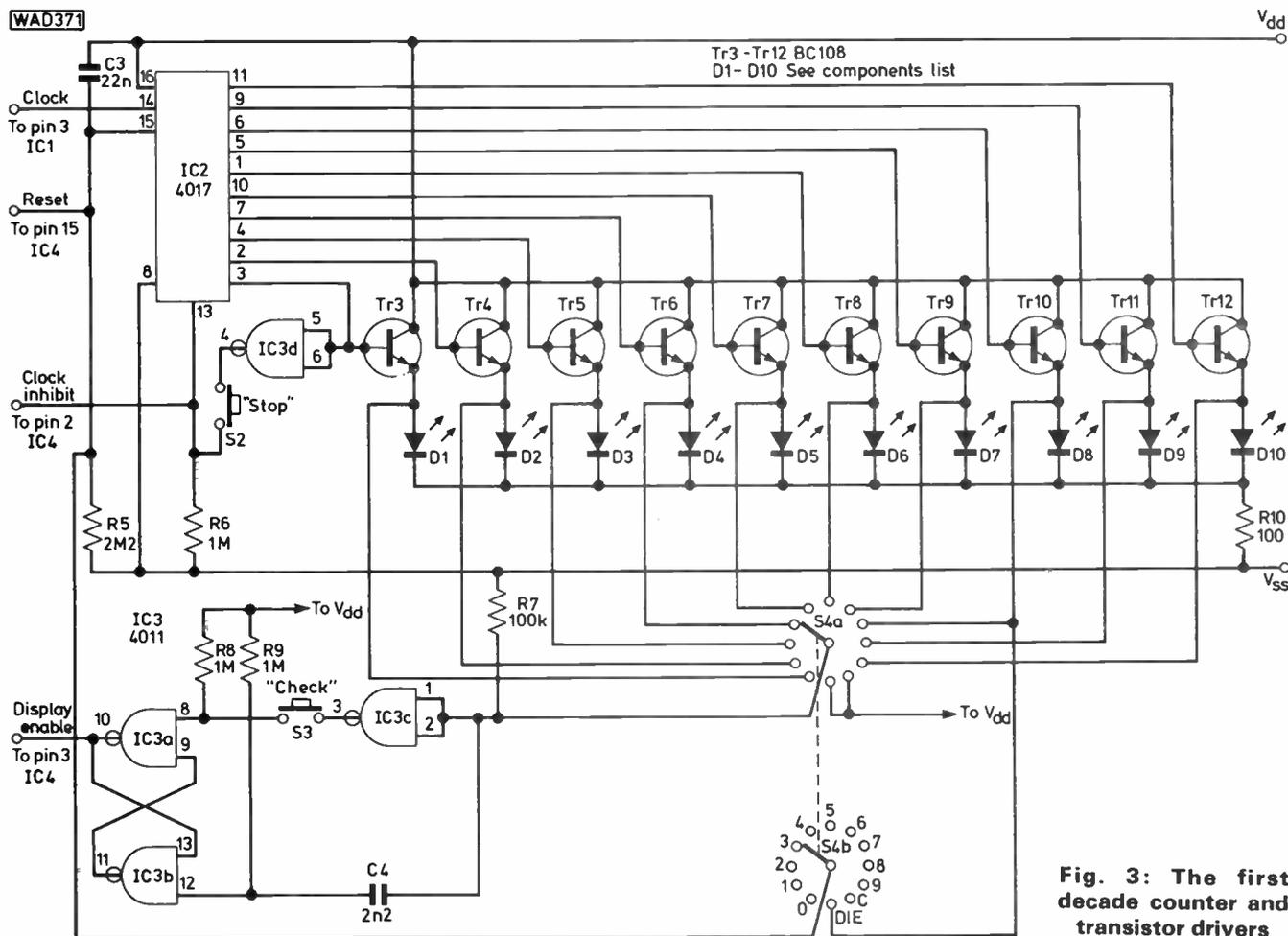


Fig. 3: The first decade counter and transistor drivers

Switching Logic

The switching logic provided by S3, S4 and IC3 has two important effects, which are now described.

Suppose the flywheel display has stopped at "4". It would be trivial to connect the pole of S4a to the "display enable" pin of the second counter (see Fig. 4) to illuminate the 7-segment display when S4a is turned to position "4". This operation would not require any numerical knowledge on the part of the child: he would just turn S4 until the 7-segment display came on. To avoid this, IC3a, b and c are interposed between S4a and the "display enable" pin of the second counter. IC3a and b form a toggle whose normally-off output is taken to the "display enable" input of the 4026 counter, thus keeping the 7-segment display off under normal conditions.

Taking pin 8 of IC3 to Vss will turn the toggle on and, with it, the 7-segment display. Similarly, taking pin 12 of IC3 to Vss will reset the toggle and extinguish the 7-segment display.

Signals to control the state of the toggle are taken from the pole of S4a. The "on" state of toggle and display is controlled by the position of S4a, by the inverter IC3c, and by the push switch S3. If S4a is turned to position "4" to match the flywheel display, then the pole is taken to logic "1"; logic "0" thus appears at pin 3 of IC3.

If S3 is momentarily pressed, the resulting logic "0" applied to pin 8 of the toggle will switch both itself and the 7-segment display on. Thus the child must not only select a number, but must press the CHECK button, S3, to see if his selection was correct.

What happens if the selector switch is turned after the 7-segment display has been illuminated? If the display were to remain illuminated with the electro-switch now showing a different number, the child would be confused, so provision is made to extinguish the display (a) when the selector switch is turned from the correct position, and (b) when the flywheel is started again. These requirements are simultaneously fulfilled by connecting the pole of S4a via C4 to the "reset" input of the toggle, pin 12.


Suppose the previous procedure has resulted in a "4" being indicated by both the displays. If S4a is turned away from "4" the pole is taken from logic "1" to logic "0", and the negative-going edge so produced is passed by C4 to reset the toggle and extinguish the display.

Similarly, if the flywheel is started, the negative-going edge produced as l.e.d. "4" goes out resets the toggle via C4 and the 7-segment display is extinguished.

Thus, in normal use, there can never be any ambiguity between the numbers on the displays and the number set on the selector switch.

The presence of R7 from the pole of S4a to Vss is worth

nothing. There is no reason why the digit positions on the S4a wafer should not go direct to the digit outputs of the 4017 counter: in this case R7 would be unnecessary. However, there is a very good practical reason why this is not done. The ten l.e.d.s and the selector switch S4 are mounted on the front panel. The integrated circuits and transistors are on a single circuit board mounted on the base of the metal box. Thus there are ten flexible leads from the emitters of Tr3-Tr12 to the l.e.d.s on the front panel. Ten more flexible leads would be needed from the S4a wafer to the digit outputs of IC2, but these leads can be eliminated by simple wiring to S4a from the anodes of the l.e.d.s, which are on the same panel. When this is done, a pull-down resistor, R7, to Vss is needed for the inputs of IC3c to keep them at logic "0" except when a logic "1" is fed to the pole of S4a from the flywheel display.

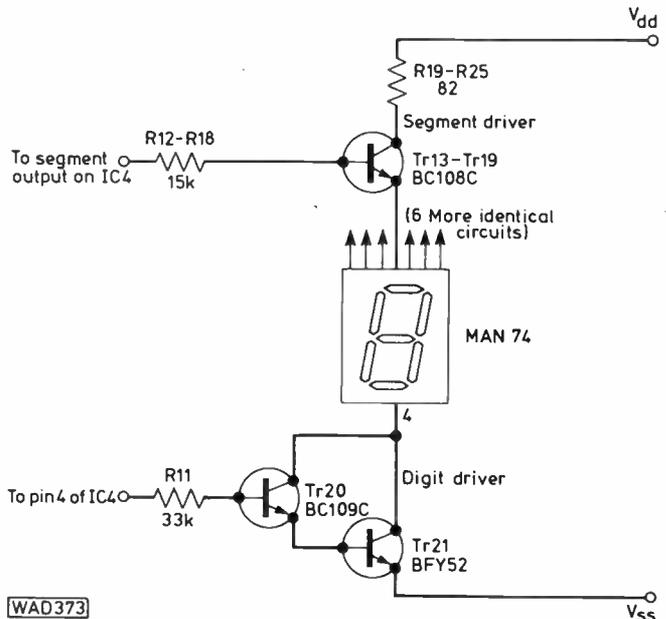


WAD373

Fig. 5: Driver circuits for the second decade counter

The second decade counter and its associated circuitry are shown in Figs. 4 and 5. The counter is a Type 4026 c.m.o.s. device which has outputs for a 7-segment display. These figures require very little explanation. The 4026 counter operates in parallel with the 4017 counter, and the 7-segment common-cathode display is fed by seven segment driver stages, Tr13-Tr19, and one digit driver stage, Tr20-Tr21. The current-limiting resistors, R19-R25, give segment currents of 19mA. To "enable" the display, the digit driver Darlington pair, Tr20-Tr21, is switched on by a logic "1" from pin 4 of the 4026 counter, thus providing a low-resistance path from the display cathodes to Vss. Tr21 must be capable of carrying $7 \times 19 = 133\text{mA}$, and the Darlington configuration has been used so that Tr21 can be very conservatively rated, ensuring high reliability.

Provision has been made to illuminate the 7-segment display while the flywheel is running. This adds to the visual appeal of the instrument before the child is ready to tackle number recognition and matching. This is the function of position "C" (continuous display) on the selector switch S4. When "C" is selected and S3 pressed, the display will remain on throughout the flywheel cycle.

A final word now about the use of the instrument as a die. On the "DIE" position of the selector switch, S4a provides a constant logic "1" on its pole (as in the "C" position), and when S3 is pressed the 7-segment display is

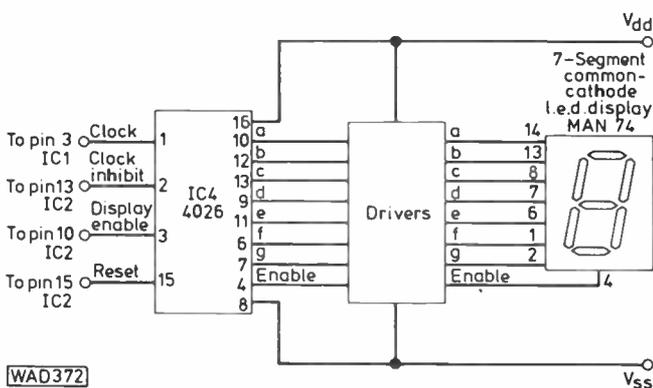

WAD372

Fig. 4: The second decade counter

constantly illuminated. S4b comes into operation at this point and connects the "7" digit of the l.e.d. flywheel to the "reset" pins of both counters. Thus both of the displays count repetitively from "0" to "6" when the clock runs. The swept-frequency clock can be used for this, but it has been found that the use of a constant 15Hz clock (selected by S1) is more satisfactory, in that the procedure is less involved for the child.

To "throw" the die, all that the child does is press S2: both displays stop immediately, showing a number between "1" and "6". On releasing S2, counting begins again. This function utilises the "clock inhibit" pins of both counters. When these pins are taken to logic "1", counting will cease, even though the clock is still running. The last NAND gate of IC3 is used for a rather devious purpose in this mode. Both IC2 and IC4 are counting from "0" to "6" yet it would clearly be incorrect to allow the die to stop at "0".

Instead, the die is slightly "weighted" such that it can never be stopped at "0"! The probability of throwing a given number on a die is 1:6. On this die, the probability of throwing a number between 2 and 6 is 1:7 and the probability of throwing a 1 is 2:7.

In use by young children, or even unsuspecting adults, this would never be noticed. To prevent a "0" being thrown, the signal to inhibit the clock is taken from the "0" digit output (pin 3) of the 4017 counter. If, at the moment S2 is pressed, a number from "1" to "6" is being displayed, pin 3 will be at logic "0". IC3d inverts this to logic "1" and inhibits the clock. However, if "0" is being displayed when S2 is pressed, pin 3 is at logic "1" and the logic "0" produced by IC3d will *not* inhibit the clock. Instead, it waits for the next clock pulse which increments both counters to the digit "1", at which instant pin 3 of the 4017 goes to logic "0" and IC3d then inhibits the clock with logic "1" at its output.

Power Supply

A single-polarity, stabilised 5 volt supply is used, employing an integrated circuit regulator. Stabilisation is to be preferred here, because the current taken from the supply varies between about 23mA with only the flywheel display on, to about 160mA with the 7-segment display showing an "8". Fig. 6 shows the circuit used. The regulator is mounted on the metal box to dissipate the small amount of heat generated. The use of 15V d.c. supply for the regulator may seem excessive. In fact, this supply rail will drop to 12 volts on full load and, as the regulator needs a supply of at least 8.5 volts, the supply is not too conservatively rated. A transformer with a 9-0-9 volt secondary could be used, provided that the supply rail for the regulator did not fall below 9 volts on full load.

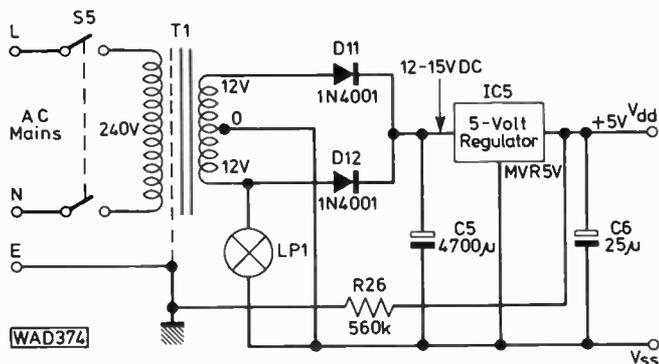


Fig. 6: Power Supply

★ components

Resistors

$\frac{1}{4}$ W 5% carbon film

82Ω	7	R19, 20, 21, 22, 23, 24, 25
100Ω	1	R10
4.7kΩ	1	R3
1.5kΩ	7	R12, 13, 14, 15, 16, 17, 18
33kΩ	1	R11
39kΩ	1	R1
68kΩ	1	R2
100kΩ	2	R4, 7
560kΩ	1	R26
1MΩ	3	R6, 8, 9
2.2MΩ	1	R5

Capacitors

Electrolytic

2µF 6V	1	C2
25µF 6V	1	C6
4700µF 25V	1	C5

Polycarbonate or polyester

2.2nF	1	C4
22nF	1	C3
0.33µF	1	C1

Semiconductors

Diodes

1N4001	2	D11, 12
LED	10	D1, 2, 3, 4, 5, 6, 7, 8, 9, 10

Transistors

BC108C	17	Tr3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19
BC109C	3	Tr1, 2, 20
BFY52	1	Tr21

Integrated circuits

MVR5 regulator	1	IC5
NE555V	1	IC1
4011	1	IC3
4017	1	IC2
4026	1	IC4

Switches

s.p.s.t.	1	S1
Push to make	2	S2, 3
2p 12w rotary	1	S4
s.p.d.t. slide	1	S5

Miscellaneous

12-0-12V 200mA transformer T1 (1); 12V panel lamp (1); 7-segment red l.e.d. display, common cathode MAN74 (1); Veroboard (see text), case.

Constructional Notes

Apart from the power supply, displays and switches, the entire circuit was constructed on a single piece of Veroboard measuring 95 × 63mm. The layout is not important, so no details are given, but it is advisable to take all Vss leads to a common point.

In general, this precaution is unnecessary, but in this circuit the emitter connection of the digit driver Tr21

Continued on page 60

Selective Sound



OPERATED

Switch

C.R.HARRIS

This unit was developed after I was asked by a friend to build a device with which he could turn a light on by clapping his hands.

Obviously this could be done by using a simple sound operated switch comprising a microphone, audio amplifier and trigger circuit, but such a simple circuit would respond to any sound of sufficient volume. Clearly something more sophisticated was required.

After a number of tests had been made, it was found that satisfactory operation could be obtained by making the circuit respond only after receiving two sounds with a fixed time interval between them of around one second. This achieves a good compromise between simplicity, spurious operation from background noise and ease of use. The human brain is very bad at estimating short time intervals and a sequence of more than two sounds becomes impossible to generate with any accuracy. The circuit also incorporates a filter and a level trigger so only sounds of the correct pitch and sufficient volume will be detected.

Circuit Operation

IC1 and associated components amplify the sound picked up from the microphone and include rough frequency filtering. VR1 is a gain control and VR2 adjusts the d.c. level of the output from this stage. This is fed to a Schmitt trigger comprising Tr1 and Tr2 and also has a time delay (C4, R2) to prevent multiple triggering. The components following (Tr3-Tr5) form a driver stage for the logic circuit, and the l.e.d. D2 indicates when a sound has been detected. The circuit gives a logical '0' on receiving an input above a preset threshold set by VR2.

The output from this stage is first fed to a monostable comprising G1 and associated components which in turn triggers two more monostables G3, G4 and associated components. Monostable G1 has a period of about 5 seconds and is included to prevent the other two monostables re-triggering before the circuit has finished its cycle. G3 has a period of about 1 second and G4 about 3 seconds.

The circuit comprising G6-G11 and FF1 looks for the state in which, after a pulse has triggered the monostables, a second pulse arrives during the period when G3 has turned off again and G4 is still on, i.e. 1-3 seconds after the first pulse. When this happens a logical '1' is sent to FF2 which then changes state and opens or closes the relay via Tr9 and Tr10. If the second pulse arrives before or after

the allowed period it is ignored and will also work the latch G9, G11 to make the circuit ignore all further inputs until G1 has reset. Thus on receiving two sounds with a time interval of about 1 second between them the circuit will operate the relay, turning the load circuit on or off.

Construction

Construction is simplified by the use of printed circuit boards. Start by soldering in the smallest components, i.e., resistors and diodes and add the tallest components (capacitors and transistors) last. The c.m.o.s. integrated circuits (IC2-IC5) should be connected using i.c. sockets, installing them in after all the other components have been soldered. Standard c.m.o.s. handling precautions should be used. Sockets should also be used for the other integrated circuits. Take great care to connect all components such as diodes, transistors, i.c.s and electrolytics the correct way round as incorrect connection can cause a large range of puzzling faults.

At this point, something should be said about the microphone and the mains transformer. The microphone used is a high impedance balanced armature earpiece which is better than a crystal microphone in this application. There is also space on the circuit board for putting a resistor in series with C2 to adjust the low frequency characteristics (10-100Ω).



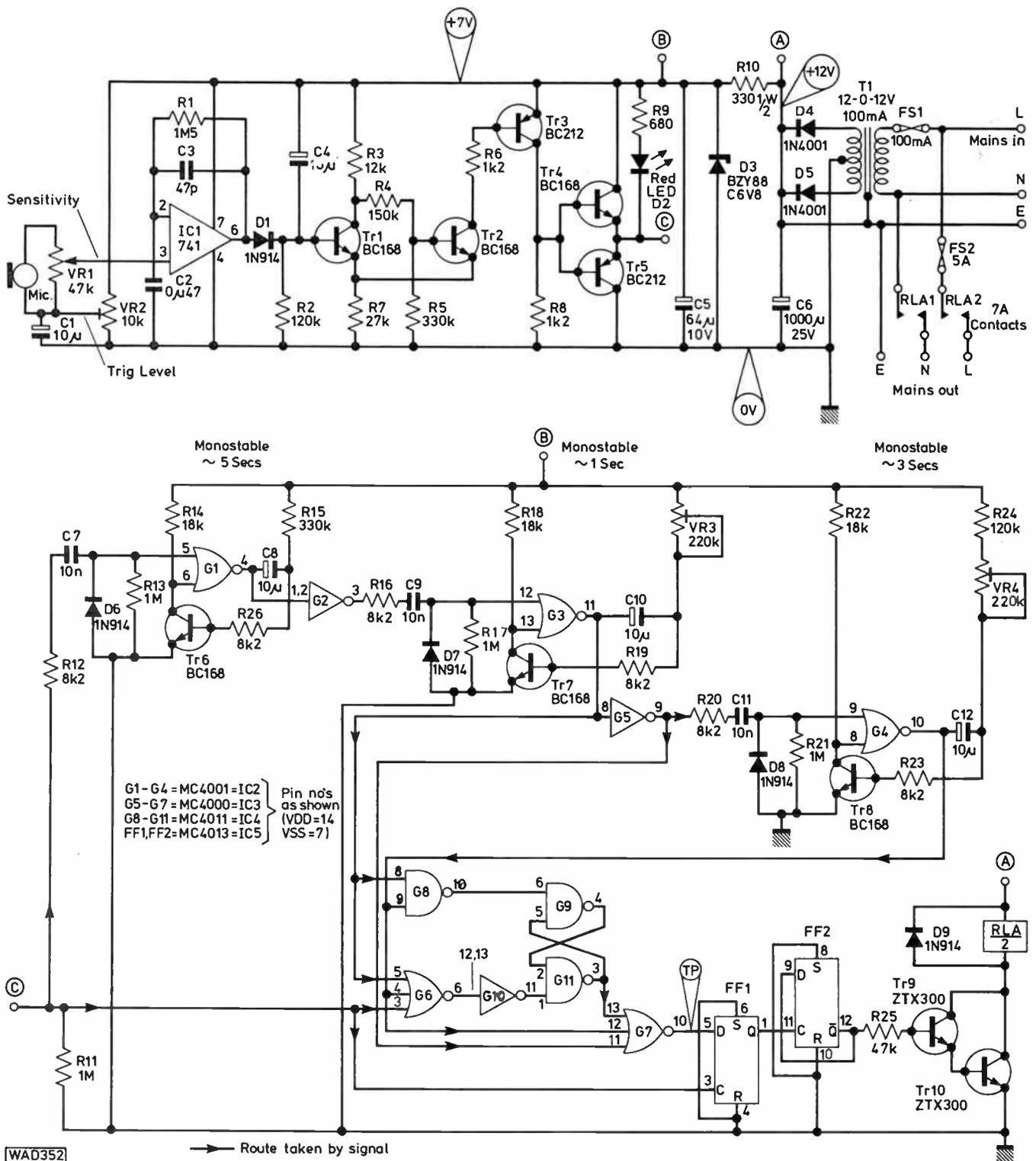



Fig. 1: Circuit diagram of the selective sound operated switch

The mains transformer is a 12-0-12V type designed to supply up to 100mA d.c. from a full-wave rectifier. Most of the current is drawn by the relay (60-80mA) with the rest taking less than 20mA. Thus if a relay is used which draws more than 80mA a larger transformer will be needed. A 100mA fuse is shown connected to the primary of the transformer and this is necessary for safety. If it is found that the fuse blows on switch-on an anti-surge fuse can be fitted. The other fuse supplying the appliance being controlled should be rated according to the relay contacts and mains cable used.

A suitable case for the unit can be made from a plastics Bimbox. When fitting components into the case, it is important to keep all the high voltage components (relay, transformer and fuse holders) well away from the other components so that there is no chance of any live connections touching any other part of the circuit. Holes are drilled in the case for the microphone, the l.e.d. and the gain control VR1. The circuit boards should be positioned within the case such that the presets VR2-VR4 can easily be reached to be adjusted. The boards are held in place using self-adhesive pads. When wiring up between the

circuit boards, it is very important that all the supply rails are connected up correctly because the c.m.o.s. chips can be damaged if an input is fed to them before the power rails are connected.

★ components

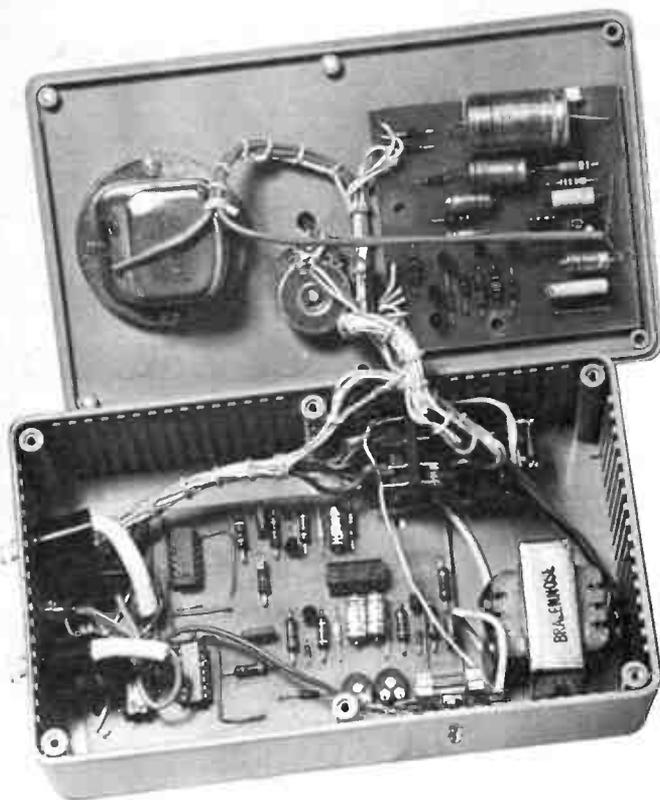

The components and p.c.b.s are fitted into a plastics Bimbox. The two p.c.b.s are attached to the box base and lid using self-adhesive foam pads

Setting Up

First set VR3 and VR4 midway along their tracks. Set the gain control VR1 to minimum. It should be found that as VR2 is moved the l.e.d. will light at one end of the track and be extinguished at the other. Adjust VR2 until it is just extinguished. Then turn the gain control VR1 up a little. It should now be found that any loud sound near the microphone will cause the l.e.d. to flash on for just under a second. If it stays on or does not come on at all then adjust VR2 until the response is satisfactory. Next, connect a voltmeter between the 0V rail and pin 10 of IC3 (marked TP in the diagram) or, if no meter is available, disconnect R25 from IC5 and make a temporary connection from that end of the resistor to pin 10 of IC3.

It should now be found that if, after at least 5 seconds of silence, a sound is made near the unit loud enough to make the l.e.d. flash, then a short pulse of approximately +7V will be indicated on the meter, or the relay will close momentarily about one second after the sound. If this does not happen adjust VR3 and VR4 until it does. This is the period during which the device is sensitive and it will switch the load if a second sound is made during this period. Adjust VR3 and VR4 until the time period is satisfactory. Note, however, that if the values of the presets are made too low then the monostables will stop working, so that if a satisfactory time period cannot be achieved then it may be necessary to change C8 or C12. Do not make the "sensitive" period too short or it will be found very difficult to estimate the required time interval.

After R25 has been replaced in its correct position and the lid has been attached, then the unit is ready for use.

Resistors

$\frac{1}{4}$ W 5%		
680 Ω	1	R9
1.2k Ω	2	R6, R8
8.2k Ω	6	R12, 16, 19, 20, 23, 26
12k Ω	1	R3
18k Ω	3	R14, 18, 22
27k Ω	1	R7
47k Ω	1	R25
120k Ω	2	R2, 24
150k Ω	1	R4
330k Ω	2	R5, 15
1M Ω	4	R11, 13, 17, 21
1.5M Ω	1	R1
$\frac{1}{2}$ W 5%		
330 Ω	1	R10

Potentiometers

Horiz. miniature preset

10k Ω Lin.	1	VR2
220k Ω Lin.	2	VR3, 4

$\frac{1}{4}$ inch shaft

47k Ω	1	VR1
--------------	---	-----

Capacitors

Disc ceramic

47pF	1	C3
10nF	3	C7, 9, 11

Polyester

0.47 μ F	1	C2
--------------	---	----

Electrolytic

10 μ F 25V	5	C1, 4, 8, 10, 12
64 μ F 16V	1	C5
1000 μ F 16V	1	C6

Semiconductors

Diodes

1N4001	2	D4, 5
1N914	5	D1, 6, 7, 8, 9
Red l.e.d.	1	D2
BZY88 C6V8	1	D3

Transistors

BC168	6	Tr1, 2, 4, 6, 7, 8
BC212	2	Tr3, 5
ZTX300	2	Tr9, 10

Integrated circuits

741	1	IC1
4000	1	IC3
4001	1	IC2
4011	1	IC4
4013	1	IC5

Miscellaneous

Bimbox (190 x 110 x 60mm BIM 2006/16); Mains transformer 12-0-12V 100mA (1); Relay 12V 80mA max. 7A 240V d.p.c.o. (1); Fuse holder (2); Fuses 100mA and 5A; Balanced armature earpiece (see text) (1); Printed circuit board (2 in set); Sockets, 14 pin d.i.l. (4); 8 pin d.i.l. (1); Knob (1); Mains cable, socket and cable clamps.

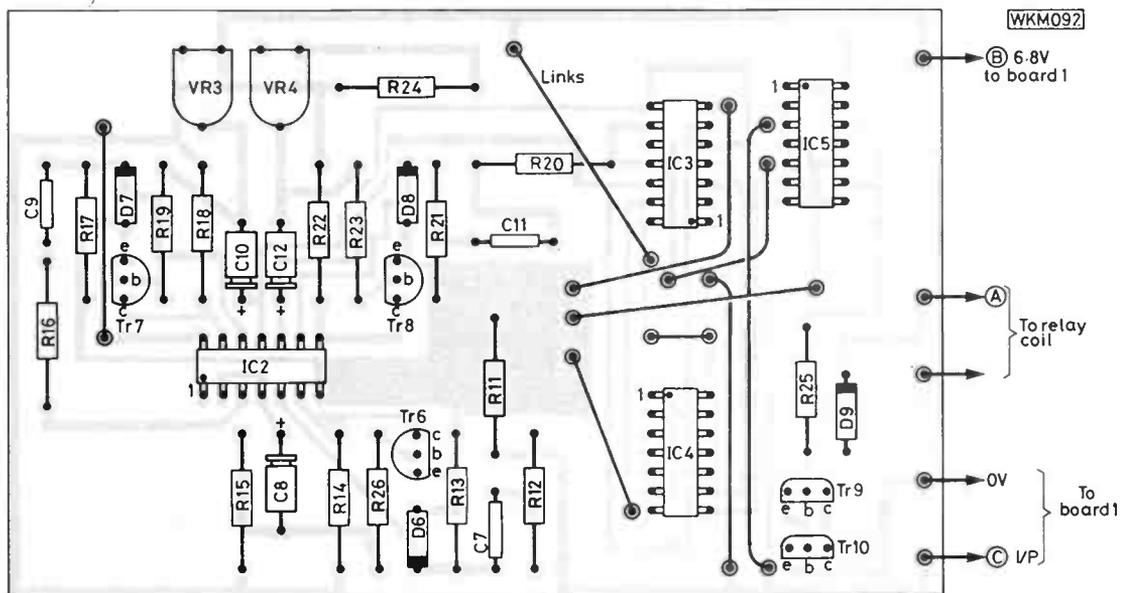
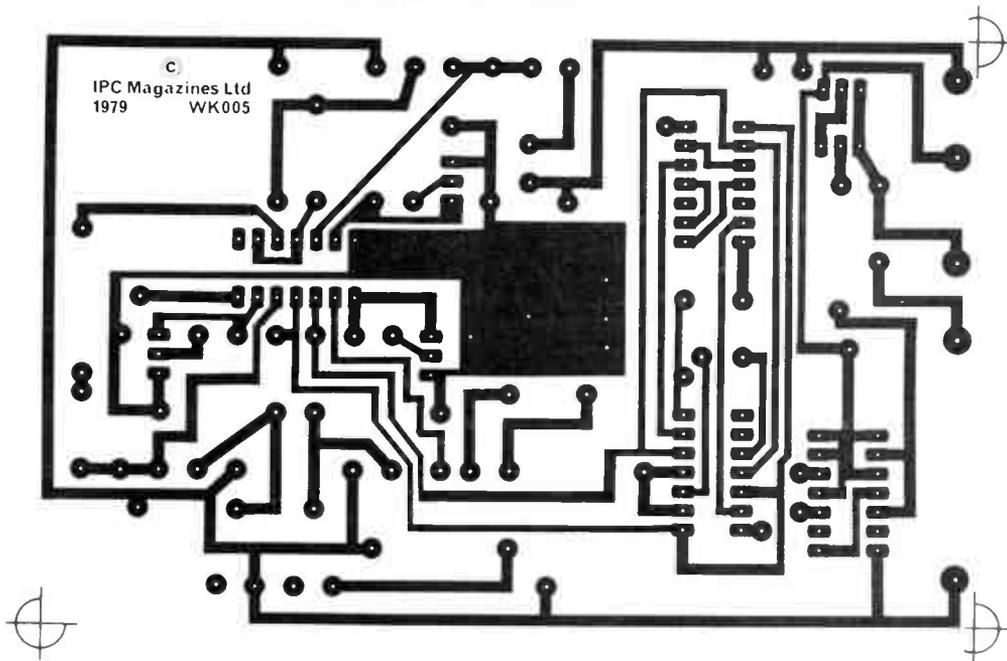


Fig. 2: The copper track pattern and component placement drawing for Board 2 shown full size.

Using the Switch

Adjust VR1 so that the l.e.d. will not flash from background noise in the room, but will reliably respond to a hand clap. The l.e.d. will be found very useful for indicating whether the unit has "heard" a sound or not, when setting the sensitivity.

Although originally intended purely as a gimmick, the device has been found to be extremely reliable and may well have more practical uses. The prototype was left in an average sitting room for a week without triggering spuriously, but would immediately respond on hearing the correct sound sequence.

There could be practical uses where it is necessary to operate equipment remotely, possibly by a disabled

person, or in other cases where it is not possible to operate a switch directly.

Fault-finding

Once the design had been finalised, it was found that the units could be relied upon to work correctly immediately they had been assembled and adjusted. Most faults are likely to be caused by wire links in the wrong places and diodes or transistors the wrong way round. Remember that the circuit uses both *nnp* and *pnp* transistors. A puzzling intermittent fault in one unit was traced to C6 being open-circuit. This resulted in the supply rails

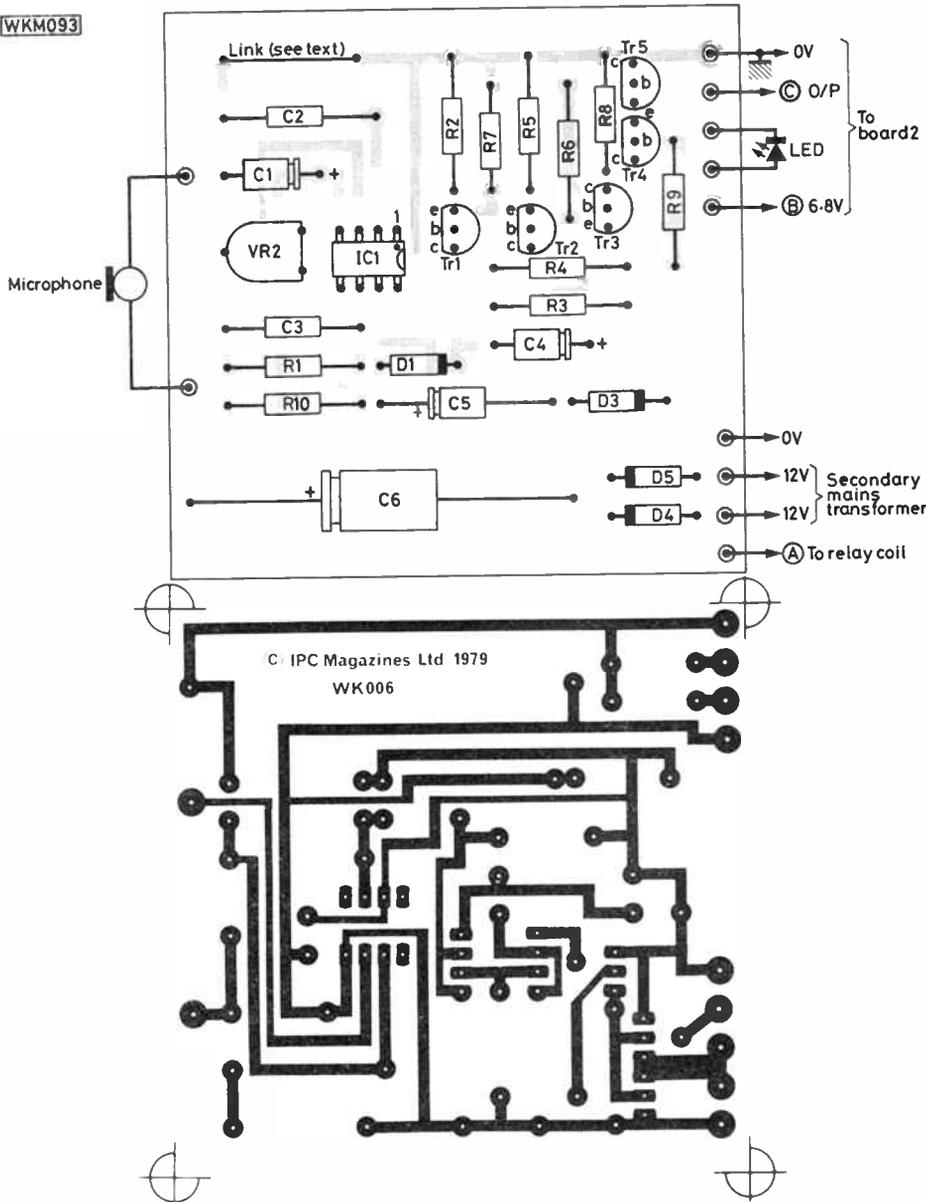


Fig. 3: The copper track pattern and component placement drawing for Board 1 shown full size

So You Want to Pass the RAE?

For details and coupon see page 30

carrying unsmoothed a.c. and played havoc with the logic functions.

Provided that the l.e.d. flashes in response to sounds then faults are best traced by first checking the outputs of the monostables (pins 4, 10, 11 of IC2) and then following the voltage levels through the rest of the circuit. Remember that the monostables give an inverse output, i.e. "1" in the quiescent state and "0" when active, and remember also that the circuit takes 5 seconds to complete its cycle and if it receives an input before G1 has reset it will ignore it.

If the l.e.d. does not light up then first check IC1. The voltage on pin 6 (output) should equal that on the wiper of VR2, except at extreme settings of VR2. The Schmitt trigger, Tr1, Tr2 should turn on when the voltage on Tr1 base exceeds about 5V, turning on the l.e.d. via Tr3-Tr5, and should turn off sharply as the voltage is lowered. These functions can easily be checked with a multimeter and should show up the location of any fault. However, provided the unit is constructed carefully, there is no reason why it should not work first time. ●

NEXT MONTH IN...

practical

WIRELESS

ON SALE 6TH. JULY



Automatic Intercom

Unwanted salesman? Tired after a hard day? PW's Automatic Intercom allows you to answer callers from your armchair without even pressing a button, while the front door remains securely bolted. Digital and analogue techniques are combined in this comprehensive, yet easy-to-install aid to basic security for the old, infirm or just plain lazy.




Ultrasonic Remote Control

A short introduction to the use of ultrasonics for cordless on/off control of domestic appliances etc. The article suggests some suitable circuits based on i.c.s intended for use in other fields, allowing the construction of very small transmitters and receivers.



Aerial Design with Scale Models

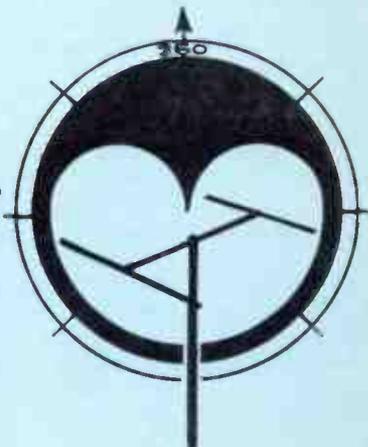Aerial designs can be tested and developed easily by building scale models of the proposed systems and making measurements at u.h.f. This article describes how a surplus marine radar display can be adapted to plot the resulting polar diagrams automatically.



Plus SPECIAL PRODUCT REPORT on the LOWE SRX-30 Receiver

W m e

top band tran

J. R. Green BSc, G3WVR*

This low-power a.m. transmitter design illustrates the use of power f.e.t. devices—in particular, the VN66AF recently introduced by Siliconix Ltd.—and takes full advantage of modern semiconductor technology. The unit is particularly suitable for use within the 160-metre band, although operation at higher frequencies is quite possible.

Design Considerations

The Author has carried out a great number of experiments with low-power transmitter circuitry using bipolar (i.e. “conventional”) devices over the last few years. Some degree of success was achieved in later designs, using the now-defunct BD123, but en route many pitfalls for the unwary were uncovered.

Technically, however, the bipolar device fell down on several counts, notably:

1. High drive power was required: typically 10%, even at low frequencies.
2. Difficulty was experienced in achieving really linear amplitude modulation, even when modulating both the driver and p.a. stages. Modulation of the p.a. only, by swinging the supply rail, was unsuccessful. Modulation of the driver as well was essential and far more modulator power was required.
3. Problems were encountered in achieving stability in the transmitter r.f. strip. Often appreciable “slugging” was called for to prevent h.f. or v.h.f. parasitics.
4. Modulation excursions also tended to introduce instability, often producing undesirable steps of modulation non-linearity in the modulated r.f. carrier envelope.
5. It proved remarkably easy to destroy the p.a. transistor(s) if instability occurred or the transmitter was mis-tuned.

These difficulties led the Author to the conclusion that solid-state transmitter design could be much simplified if a

* Senior Development Engineer—Gould Instruments Division

device existed which exhibited the characteristics of a thermionic valve. In particular, low drive power, modulation linearity and stability were desirable in addition to the ability to operate from low voltages. In other words, a high-power f.e.t. was needed.

During 1978, Siliconix Ltd. produced the VN66AF and samples were supplied to further the Author's experiments. The ultimate results are incorporated into the transmitter featured in this article. Whilst the published form is for 160-metres, the basic circuit could be used to produce a transmitter capable of at least 10MHz and possibly more.

Circuit Description

The transmitter employs a crystal oscillator which incorporates a twice-frequency, parallel-resonant crystal, with a TIS88A f.e.t. as the oscillator transistor (Care with substitutes! The circuit may fail to oscillate with devices requiring different d.c. conditions.). This stage provides sufficient drive to switch Tr2, a 2N2369A switching transistor which provides a twice-frequency 5 volt peak-to-peak square-wave to drive IC1. This i.c. is a 7473 flip-flop wired to divide-by-two, thus producing the output frequency “ f ”.

The 7473 limits the “ $2f$ ” crystal to around 6MHz (therefore the output frequency “ f ” to 3MHz) but this may be extended by substituting a Schottky 7473 (i.e. a 74S73).

From IC1 the signal is passed to Tr3, another 2N2369A switching transistor, to present 12 volts peak-to-peak square-wave drive to the output devices. With Tr3 looking into 100 Ω the two VN66AF p.a. devices are easily driven. Their input capacity of 50pF each is the prime limiting factor with untuned drive, although a BFY50 could be substituted for Tr3 and R11 reduced in value to increase the operating frequency or drive more than two p.a. devices. A power output of 6 watts is typical for a 10 watt d.c. input.

A simple “constant K” type low-pass filter is provided, together with transformer matching to transfer the output power effectively into a 50 Ω load and remove harmonics.



Transmitter



Note that since a 1:1 mark-space square-wave drive is derived for the p.a., optimum efficiency with minimal second-harmonic radiation in the unfiltered output is assured, with the filter biting hard at the third and subsequent harmonics.

Filter values shown are for a cut-off frequency of 2500kHz, but others may be calculated from the expressions:

$$C = \frac{1}{f_c \pi z} \quad \text{and} \quad L = z^2 C$$

where $z = 50\Omega$ and $L = L1 = L2 = L3$

$$C = C_{10} = C_{11} \quad \text{and} \quad C_9 = C_{12} = \frac{C}{2}$$

f_c is the cut-off frequency.

The modulator circuit is merely a modified version of the Author's hi-fi amplifier design and should not present any problems. A speaker matching transformer rated at 10 watts (T2) is used to transfer the modulator power to the p.a. This should have a core area of around 25mm square and a winding resistance between the 0 and 16 Ω taps of not more than 1 Ω . The modulator input sensitivity is in the order of 100mV, so a pre-amplifier will be necessary for microphone level signals.

The r.f. matching transformer T1 was wound on a Mullard binocular "balun" ferrite block, measuring approximately 25 x 20 x 8mm and consists of three turns on the primary (transistor) side and nine on the secondary (filter) side. Experiments using these baluns showed a power-handling capability of 100 watts peak! Substitutes should have the following characteristics:

1. Suitable for the intended operating frequency.
2. 1:3 turns ratio for 6 watts, 50 Ω output with wire gauge as large as possible.
3. 50 Ω secondary reactance to be $\gg 50\Omega$ at operating frequency.
4. Peak power rating of at least 20 watts.

If a suitable ferrite block cannot be found, three Mullard FX2249 blocks can be used.

No Adjustments Needed!

It will be apparent from the r.f. circuitry that no tuning is required on the r.f. strip, which should work from switch-on. Trimmer VC1 is used for very fine frequency adjustment and could well be omitted, replacing it with a fixed capacitor of 18pF if the facility is not required. The pre-set potentiometer VR2 should be rotated until Tr11 and Tr12 just start to conduct—say 50mA of standing current.

The VMOS VN66AF devices performed very impressively throughout the development of the prototype transmitters. Only very low drive was necessary and very linear upward and downward modulation was produced. In every respect, the devices performed entirely to specification and simply shut down if an unacceptably-low load was connected.

Possibly it will be found that the modulator output is not quite sufficient to achieve 100% upward modulation but with a suitable transformer the quality is very good indeed and certainly far superior to so-called "communications quality", which covers a multitude of sins!

Construction

The construction techniques are clearly seen in the photograph, most of the components being soldered and mounted on one side of a double-sided "earth-plane" printed-circuit board, measuring 160 x 100mm. The top of the board, the component side that is, forms an earth-plane and the copper should be cleared (using a drill and an oversized bit) around the larger holes indicated in Fig. 2. The remainder form earth-plane connections. Details of the p.c.b. are given in Fig. 2 and the component locations are shown in Fig. 3.

The modulation transformer T2 is mounted on the bottom panel of the West Hyde Developments instrument case, as are Tr4 and 5 (on insulated washers). Transistors Tr11 and 12 are mounted on the extrusion as shown in the photograph. (In fact, the VMOS devices could also be fixed in the same manner, if preferred).

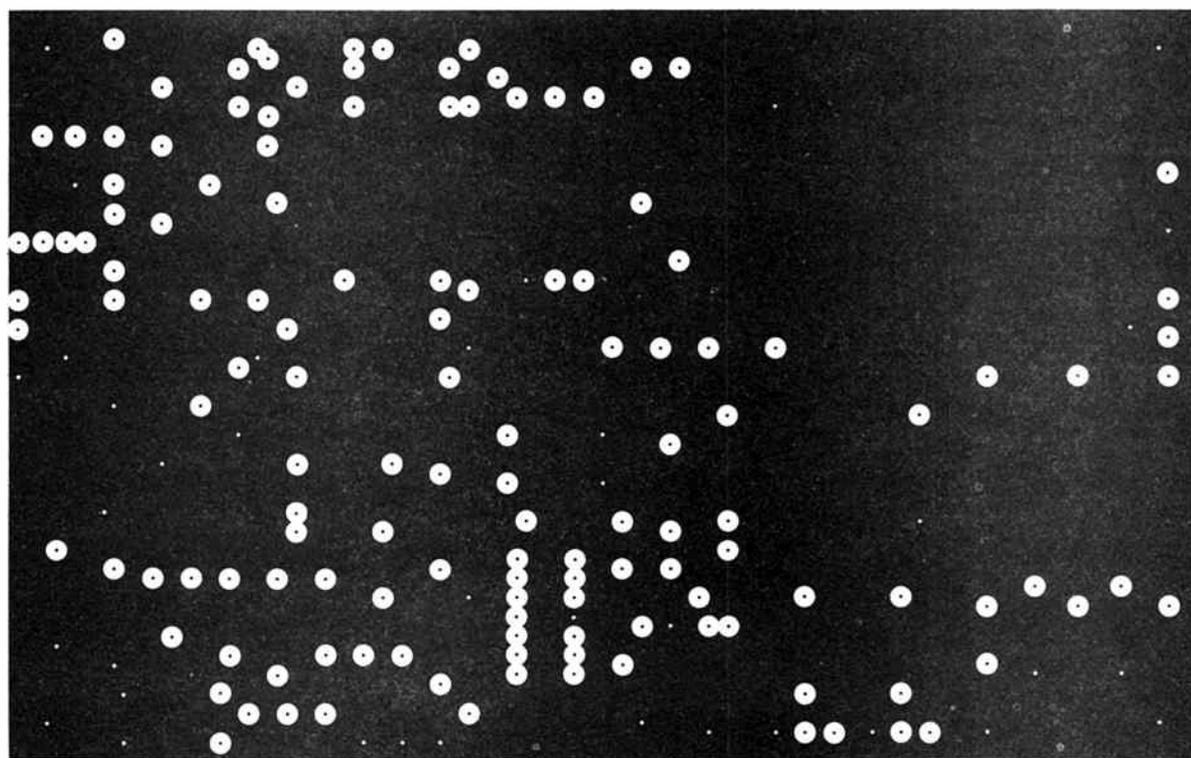
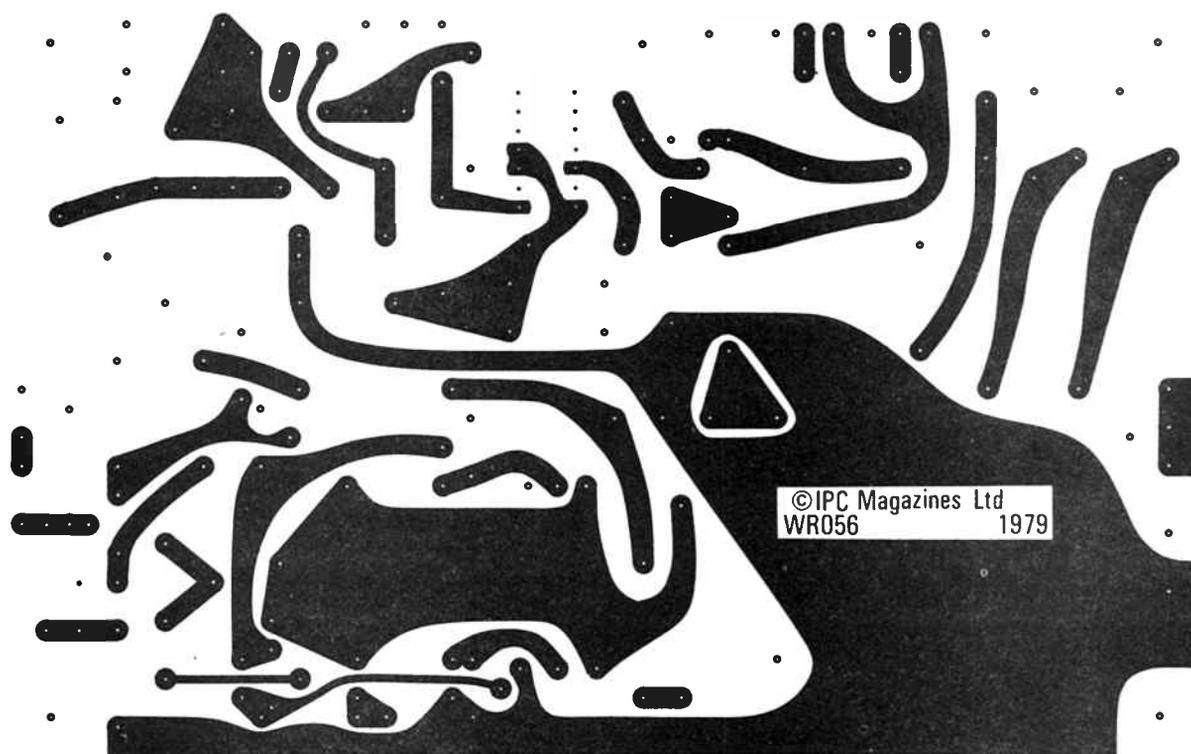


Fig. 2: The copper track side of the p.c.b. is shown full size at the top with the copper ground plane on the component side below it.

★ components

Resistors

$\frac{1}{4}$ watt 5% Metal Oxide

39 Ω	3	R2, 13, 14
47 Ω	1	R19
82 Ω	1	R22
100 Ω	2	R3, 11—see text
150 Ω	1	R6
330 Ω	3	R23, 24, 25
470 Ω	3	R7, 8, 9
2.2k Ω	1	R4
3.3k Ω	1	R5
4.7k Ω	3	R12, 20, 21
5.6k Ω	1	R10
10k Ω	2	R15, 18
22k Ω	1	R16
33k Ω	1	R17
100k Ω	1	R1

Potentiometers

5k Ω	1	VR2 Skeleton pre-set
10k Ω	1	VR1 Log. Panel mtg. pre-set with locking nut and cap

Capacitors

Silver Mica

22pF	1	C1
170pF	1	C2 180pF may be necessary

Ceramic disc

22nF	2	C5, 7
0.1 μ F	2	C3, 16 see text
0.33 μ F	2	C4, 8

Polystyrene 350 volt

1.25nF	2	C9, 12 (Use 1.2nF)
2.5nF	2	C10, 11 (Use 2.2nF)

Tantalum bead, 16 volt

25 μ F	1	C13
47 μ F	1	C14 100 μ F may be used

Electrolytic, axial leads

25 μ F 25V	1	C19
50 μ F 6.4V	1	C6
100 μ F 16V	1	C17
220 μ F 16V	1	C15 470 μ F may be used
1000 μ F 16V	1	C18

Trimmers

Dau type ceramic

3–30pF	1	VC1 see text (from J. Birkett)
--------	---	--------------------------------

Semiconductors

Diodes

1N914	1	D1 1N916 may be used
1N5339B	1	D2 5.6 volt Zener

Transistors

TIS88A	1	Tr1
2N2369A	2	Tr2, 3
VN66AF	2	Tr4, 5 (from C. Bowes & Co.)
2N3250	1	Tr6
BC108	1	Tr7
BFY50	2	Tr8, 9
BFX88	1	Tr10
MJE3055	1	Tr11
MJE2955	1	Tr12

Integrated circuit

SN7473N	1	IC1 SN74S73N for higher frequency operation
---------	---	---

Crystal

XL1 Twice-frequency HC6U type, parallel-resonant

Inductors

Calculated filter values for 160 metres:
6.25 μ H, $f_c = 2.5$ MHz.

L1, 2, 3	38 turns of 26 s.w.g. enamelled copper wire on 25mm long 8mm diameter former, air cored.
----------	--

Transformers

T1 20 watt rating r.f. transformer (peak). Turns ratio 1:3, secondary reactance $\geq 50\Omega$, wound on suitable binocular balun-block ferrite (or 3 type FX2249, see text).

T2 10 watt rating speaker matching transformer with 0–3–8–16 Ω taps. The step-up ratio using 0 Ω as common 3 Ω as input and 16 Ω (or 15 Ω) as output is a fraction in excess of 1:2.

Hardware

Insulating kits for VN66AF transistors (2), MJE3055 and MJE2955. Socket for crystal. 50 Ω BNC connector (or SO239). West Hyde Developments instrument case type "Classic" CL2ADK (See advertisers' index). Printed-circuit board.


Setting Up

A very short section this! No tuning is required and the r.f. strip should work straight away. The d.c. input current to the final stage can be monitored and should be about 800mA when looking into 50 Ω . Other loads will affect the p.a. current and in extreme cases may require some sort of matching transformer.

Poor quality "inactive" crystals will reduce the oscil-


lator drive level and this may reach proportions where Tr2 will not switch and consequently there will be no output.

The quiescent current of the modulator should be set at around 50mA by means of VR2. If this adjustment is a smooth one all is well, but if the current flicks up to a high value check for amplifier instability. This can be cured by fitting C16, which also helps to keep r.f. from reaching the modulator.

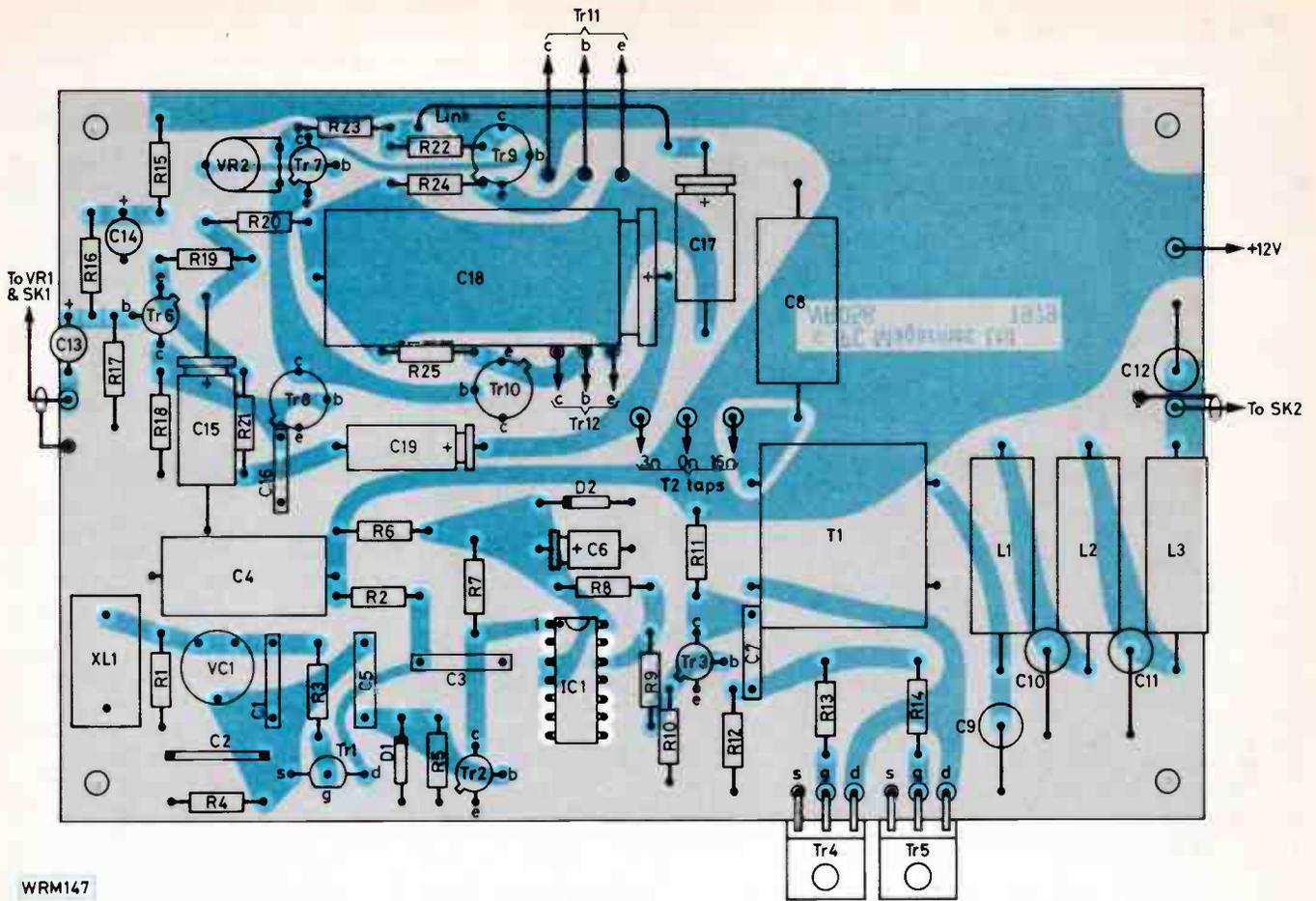

WRM147

Fig. 3: The component placement drawing of the p.c.b. showing the ground plane (component) side of the board.

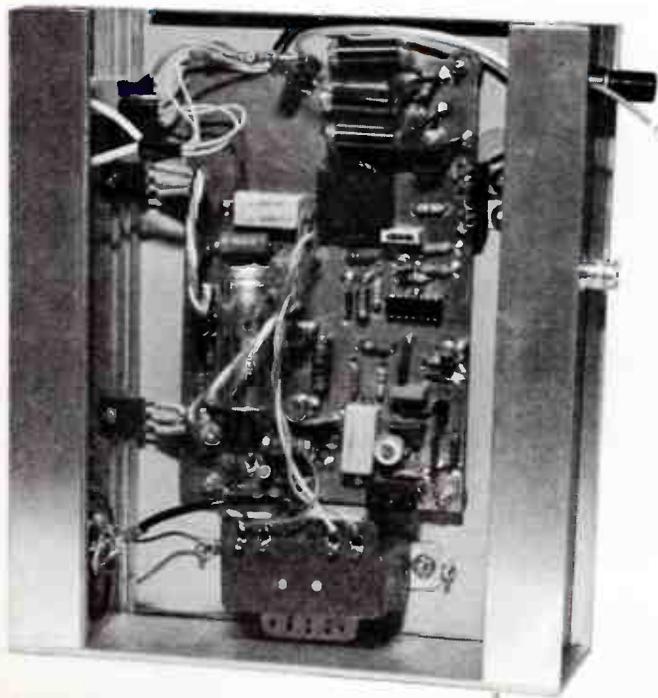

Aerial Matching

Most low-frequency aerials in amateur use are unlikely to present a good 50Ω match due to their small electrical size. The following techniques, based on a little theory and a lot of experimentation, are suggested.

The transmitter filter is quite tolerant of a mis-match—say $30\text{--}80\Omega$ —but placing a low impedance load on the output may violate the d.c. input power requirements. A really low load will cause the VN66AFs to overheat, but do not worry if this should occur; adequate protection is afforded within the devices, and they will merely shut down.

VFO Operation

Those who develop the transmitter may well wish to add the facility of v.f.o. operation. This is easily achieved by feeding the twice-frequency v.f.o. signal, at 2 volts peak-to-peak, into C5, in place of the injection from the crystal oscillator.

No problems with f.m. pulling should be encountered, as the v.f.o. and output frequencies are not the same.

Well, now you know how to build and operate your VMOS transmitter. Incidentally, the VN66AFs should only cost around £1 each. We hope it brings you enjoyment. ●

Changes in

BROADCAST-BAND LISTENING on Short Waves

PART 1

Jonathan MARKS

If you follow *Practical Wireless* regularly, then by now you may have put together or bought a short-wave general coverage receiver. Tuning around between 3 and 30MHz it soon becomes apparent that the spectrum is divided into blocks which are used for various purposes. If you listen between the frequencies 5950–6200, 7100–7300, 9500–9775, 11700–11975, 15100–15450, 17700–17900, 21450–21750 and 25600–26100kHz you'll hear radio programmes originating from broadcasting organisations all over the world. These radio stations are obviously different from the BBC or IBA domestic broadcast channels that the general public are used to, since their target audience is often a whole continent if not the world, rather than a single country or indeed a particular town.

A first flick through any short-wave (usually abbreviated to s.w.) broadcast band may prove disappointing. Many stations seem to be talking in foreign languages and are all crowded together. The secret with this hobby though is slow, careful tuning and frequent checks on "who's around". Most stations put out a magazine-style programme of about half-an-hour's duration in a number of languages, and with English the most common international language there are few stations without an English section. Indeed many s.w. stations broadcast specifically to Great Britain and Ireland every evening with programmes in English.

Station Types

Short-wave broadcasting stations fall into two main categories. The first group of stations aim to provide their listeners with news which is unlikely to hit world headlines (and therefore overseas newspapers and radio bulletins), yet never-the-less would be interesting to people with a

desire for information on world events and culture. Such stations are usually given a grant by their government, but the journalists and broadcasters are given a free hand to make programmes without government censorship. Hence the programmes give an objective, often critical insight into current affairs in the 'country, the reaction of its people to world events and a sample of the culture, music and perhaps even language. Stations in this category include Radio Finland, the Swiss Broadcasting Corporation, Radio Canada International, Austrian Radio, Radio Sweden and the BBC World Service.

In the second category are the government-run stations, whose main aim is to put over the political views of the government in power. As a result programming is rather one-sided, promoting only national achievements and churning out masses of statistics. That aside, such stations can be a source of quite fascinating information, and it is often interesting to compare their version of a news story with others, either in your national newspaper or on TV. Such government-run stations include Radio Moscow, Radio Peking, Radio Berlin International, Radio Tirana and the Voice of Vietnam.

ABOUT THE AUTHOR

Jonathan Marks is a broadcaster/journalist who formerly worked in Vienna for the Austrian Radio Short Wave Service, becoming involved with the weekly SWL news programme "Austrian SW Panorama", broadcast world-wide every Sunday. Since returning to the UK, he has continued to make regular contributions to the programme, and is an active DX enthusiast




A view of the BBC Monitoring Service listening room, as seen from the console

Photo courtesy BBC



Austrian Radio studio centre in Vienna, with s.w. section in foreground

Photo courtesy ORF, Vienna

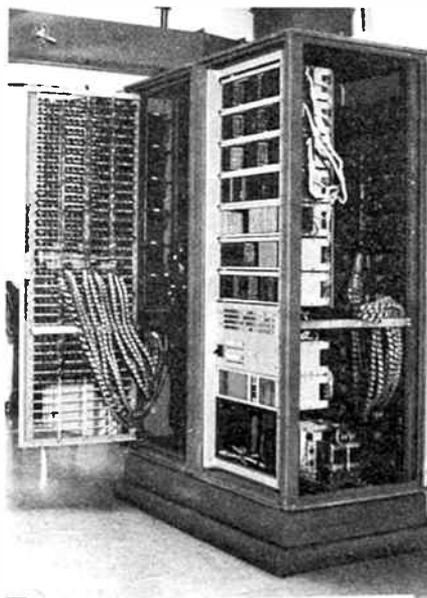

Computer-controlled switching gear selects appropriate transmitters and aerials to suit propagation conditions

Photo courtesy ORF, Vienna



Continuity suite for Radio Sweden. The cartridge machine on the left provides multi-lingual station identifications

Photo courtesy Arne Skaog, R. Sweden

Reception Reports

While reading *PW*'s "On the Air" feature you may have heard of QSLs and reception reports. These are really terms adopted by the broadcasting stations from the amateur radio world, and go back to the early thirties when many s.w. stations started up. In those days, stations didn't know if they were being heard in the target areas at all, and so in return for a listener sending in a report of reception (containing details of time, date, frequency and quality of reception, plus notes on the programme heard and receiving equipment used), stations would issue a confirmation card or QSL. This consisted of a picture postcard with the time, frequency and date of the transmission heard confirmed in writing on the back.

Many stations still send out QSLs, but since the thirties there have been a lot of changes on the technical side. Stations now use very much higher power (many in the order of 500kW), and because of the existence of professional monitoring stations, the larger broadcast stations know exactly how they are being received in target zones. Thus, as far as these stations are concerned, listeners' reception reports are now of marginal interest and the QSL card is more of a public relations venture since the reports are not checked. However, the smaller stations operating in only a few languages (especially religious stations), still need reception reports from listeners. They have only a limited budget and very much lower powered equipment, so regular reports on more than one frequency remain very important.

How can you judge if the station wants your report? The answer is to look in an excellent annual publication called the *World Radio and Television Handbook* which is available through most bookshops. It lists all known radio organisations in the world and where and when to listen out for them. It will give you a clear idea as to the size of the station, its QSL policy and the exact address to send your report to. In general, the smaller the station the more welcome your reception report, with the exception of small stations in West and Central Africa and South America. Stations in these areas use s.w. for domestic broadcasting

in much the same way as v.h.f. is used in Europe, and distant reception reports are usually QSLd only out of courtesy.

Programmes

All international broadcast stations, large or small, welcome your comments on the programmes heard. Over the last 10 years, programming standards have improved enormously compared with the sixties when most stations were of the "cold war" variety, deadly dull and boring. Then, the hobbyist could do little but send a technical reception report. In 1979, though you'll still find some pure propaganda stations, most stations in the Western world (and even a few in the Eastern Bloc) have woken up to the fact that sheer political fact switches Mr Average SWL off. Instead you can now find interesting, well-presented cultural material, whether it be tips on hitch-hiking across Sweden, eating out in Brussels, getting around in Tokyo or exploring caves in the Alps of Austria. Younger listeners too are catered for, with music programmes which broaden one's outlook on the pop music scene and enable one to get world-wide contacts. It is also important to point out that listeners who provide stations with critical constructive comments are well respected by the editorial staff.

Who listens to these international s.w. programmes? In the UK, s.w. broadcast listening is not widely known. Radios sold today in the average British hi-fi shop have no facilities for s.w. listening, but this is not the case in other parts of Europe. In West Germany or Finland for example, thanks to publicity of SWL clubs and the availability of suitable sets, SWL means more to the man in the street. There are signs though that the UK may be catching up on its European neighbours, as good s.w. receivers become cheaper thanks to integrated circuits, and digital readout eases the tuning problem. Also with more holidays being taken abroad, people like to keep in touch with countries they've seen. In the USA and Canada, s.w. is catching on simply because listeners are fed up with their local station full of commercials, time and weather men and rip-and-read news.

The more factual style of s.w. is also important in the developing countries, where radio is very different to Europe. There is usually no v.h.f. or m.w. service, and s.w. radio is the only means for the government to reach listeners in its own country. Thanks to ionospheric propagation though, signals from other countries (e.g. in Europe) can also reach developing countries. The BBC's African Service for example, thanks to a network of on-the-spot correspondents, provides a very fast, accurate picture of what is going on in Africa for African listeners, often before the national radio station reports it. Of course politics comes into play here. Many stations in the Western world beam vernacular programmes towards a developing country which disagree with what the national government station in that country is saying; something which often worries the latter if it is trying to influence its population.

Local Stations

Most stations in Latin America broadcast on the 60 metre tropical s.w. band (4750-5060kHz) instead of medium waves, which are full of static due to tropical thunderstorms. Propagation is such that from about midnight until dawn in the UK you can hear these stations broadcasting to their local population: an excellent insight into Latin America with wide opportunities to study the language or simply enjoy the music. Such small stations in the jungle run on a shoe-string and provide amusing stories for those who've visited them.

The official time signal on one station in Peru for example, turned out to be made by a simple audio oscillator triggered by the DJ watching the second hand on an ancient clock. A station in Bolivia came up on the wrong frequency for over a month because the station engineer had plugged in the wrong crystal. Similar stories come from Asia where the national station in Nepal sometimes comes on the air late when they forget to switch on the carrier of the transmitter. All this added together makes for a fascinating hobby.

The secret is to know when and where to look. One of the best ways is to contact one of the UK Broadcast DX Clubs as well as reading "On the Air". In addition stations themselves put out SWL programmes to assist listeners, for example: *Sweden Calling DXers* (Radio Sweden), *World Radio Club* (BBC World Service), *Austrian SW Panorama* (Austrian Radio), *World DX News* (AWR, Portugal) and *DX Juke Box* (Radio Nederland) to name just a few. In addition, an organisation exists in the UK, called the Handicapped Aid Programme, to help introduce this hobby to the disabled. Undoubtedly, broadcast listening can open up new horizons for a person who is house-bound, and no licence is needed.


Finally, if you would like to combine your hobby with a holiday, then you might consider joining a DX camp for a few days. These take place during the summer months in Austria, West Germany, Sweden, Finland and, starting in 1979, in the UK. These meetings offer an excellent chance to try out new equipment and antennas as well as meeting fellow DXers and SWLs. Such camps are often coordinated under the European DX Council which acts as an umbrella organisation for European clubs and has a number of useful publications for broadcast band listeners. Meetings on a local basis also explode the myth that a typical SWL is someone who hibernates in his shack, to find friends all over the world but none in his own country!

CONTINUED NEXT MONTH


KINDLY NOTE!

PW Imp 3-Waveband Receiver May 1979

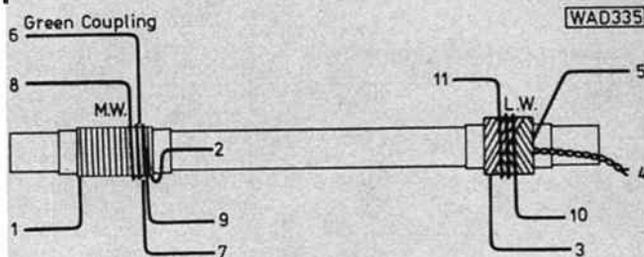The details of the extra windings to be added to the coils were unfortunately omitted from Figs. 5 and 6. They are given below.



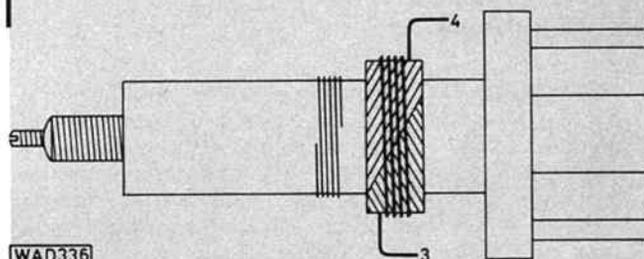Additional reaction windings. 38s.w.g. enamelled copper wire. 8-9, 2 full turns in sense shown above; 11-10, 2 full turns in sense shown above. Note that the coils should be on the rod as shown so that the windings are in the same direction from the 'live' ends (1 and 3).



Reduce winding 5-7 to 2 turns. Add 12 turns of 38s.w.g. enamelled copper wire on top (3-4) in direction shown above.

VISIT THE PW STAND AT

UNICOM 21

22-23 JUNE

SEE OUR NEWS PAGES
FOR FULL DETAILS



SERVICES

194A Northolt Road
South Harrow, Middx
London. Tel: 01-864 1166



RF POWER METERS

JD 110 10 & 100w	£11.88
Reace UH74 432/144	£15.26
Hanson 20/200w-150Mhz	£26.50
Leader LPM 885 20/200/1Kw	£55.08
SWR 25 Twin 3.5/150Mhz	£11.90
Leader LPM 880 absorption watt-meter 5/20/120w 1.8-500	£85.00
Inc. VAT & Delivery	

YAESU PRICE LIST (inclusive VAT & Carriage)

HF Equipment		FL 110	£144.00
FT901DM	£995.00	FR 101S	£444.00
FT 901D	£825.00	FR 101D	£585.00
FV 901DM	£240.00	FR 101DD	£685.00
SP 901	£27.00	FRG 7	£210.00
FTV 901	£245.00	FRG 7000	£365.00
FC 901	£129.00	FT 7	£297.00
YO 901	£260.00	FT 7B	£421.00
FT 101Z	£562.00		
FT 101ZD	£646.00	VHF Equipment	£600.00
FT 101E	£569.00	FT 225RD	£545.00
FV 101B	£95.00	FT 225R	£104.00
SP 101B	£21.00	Memory	£104.00
FL2100	£345.00	FT 227R	£227.00
YO 101	£190.00	FT 227RA	£225.00
FT 301	£575.00	CPU 2500R	£325.00
FT 301D	£656.00	CPU 2500RK	£345.00
FT 301SD	£590.00	CPU 2500RS	£295.00
FC 301	£120.00	CPU 2500RKS	£330.00
FY 301	£105.00	FT 202	£99.00

ROTATORS

STOLLE 2010	£48.50
AR 30 VHF/UHF	£47.50
AR 22 VHF Light HF	£49.50
AR 40 VHF Light HF	£54.50
AR 33 AR40 De Luxe	£67.00
CD 44 Heavy duty	£108.00
Ham III Heavy duty	£156.00
KR 400 HF	£96.50
DR 7500 HF	£106.00
KR 9502A VHF	£46.00
Bearing CD 562	£7.80
Bearing RZ100 Stolle	£12.00
Incl. VAT & Delivery	

JUST TELEPHONE YOUR CARD NUMBER OR
SEND YOUR CHEQUE WITH ORDER



01-864 1166 01-422 9585

Full range of Accessories Available
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

ICOM

Full range in Stock

IC 701	£810.00
IC 701PS	£136.00
IC 211E	£530.00
IC 245E	£393.00
IC280E	£265.00
IC 240	£185.00
IC 202S	£205.00
IC 215	£169.00
ICV 402 UHF	£270.00
IC RM3	£94.00
IC SM2	£24.50
Incl. VAT & Delivery	

MICROWAVE MODULES

MMT 144/Any IF	£88.00
MMT 432/Any IF	£109.00
MMT 432/28S	£133.80
MMT 432/144	£149.60
MMT 432/144R	£169.80
MMV 1152/Tripler Var.	£34.80
MMV 1296/23cm Tripler	£33.70
MMD 050/500 DFM to 500Mhz	£69.00
MMC 144/Any	£20.25
MMC 144/28 LO	£20.25
MMC 70/Any	£20.25
MMA 144 Preamp	£14.60
MML 144/100 Linamp	£139.50
MMC 28/144	£20.25
MMA 28 Preamp	£14.63
Inc. VAT & Post	

General Coverage Communications Receiver FRG-7



● 0.5-29.9MHz Coverage with 10kHz Readout

The FRG-7 is a precision-built all-purpose communications receiver featuring all solid state construction for long life and high performance. Utilizing the Wadley Loop drift cancellation system, in conjunction with a triple conversion super-heterodyne circuit, the FRG-7 boasts high sensitivity along with excellent stability. It provides broadcast listeners with such features as a 3-position tone selector, an RF attenuator, and an automatic noise suppression circuit. For many years of satisfying reception, the FRG-7 is the receiver for you.

Supplied with SM module and free Securicor delivery £210.

JAYBEAM

2M Antennas	
5Y/2M 5 el yagi	£9.66
8Y/2M 8 el yagi	£12.25
10Y/2M 10 el yagi	£26.13
P8M 10/2M parabeam	£30.75
P8M 14/2M parabeam	£37.55
5XY/2M 5 el x'd yagi	£19.60
8XY/2M 8 el x'd yagi	£24.10
10XY/2M 10 el x'd yagi	£31.76
PMH/2C circular harness	£8.15
Q4/2M 4 el quad	£20.17
Q6/2M 6 el quad	£28.70
D5/2M el slot	£17.00
D8/2M el slot	£22.20
UGP/2M ground plane	£8.68
SVMK/2M vertical slot	£5.30
HO/2M halo head	£4.20
HM/2M halo mast	£4.98
PMH2/2M 2-way harness	£8.10
PMH4/2M 4-way harness	£16.94
70cm Antennas	
P8M18/70cm Parabeam	£22.53
MBM4B/70cm Multibeam	£26.46
MBM8B/70cm Multibeam	£34.82
12XY/70cm 12 el x'd yagi	£35.52
PMH2/70cm harness	£8.93
PMH4/70cm harness	£14.35
C8/70cm 8db colinear	£46.03

QM 70

70/28RC 4m-10m conv.	£18.46
144/28RC 2m-10m conv.	£18.46
432/28RC 70cm-10m conv.	£26.99
432/144RC 70cm-2m conv.	£26.99
434/28RC 70cm-10m conv.	£26.99
434/144RC 70cm-2m conv.	£26.99
432 - 434/28 two band 70cm-10m conv.	£32.33
432 - 434/144 two band 70cm-2m conv.	£59.00
144PA 10/40P10W in 40W out linear amp with preamp	£59.00
144PA2/45 2W in 45W out FM Amp with preamp	£70.25

Post & tax paid everywhere



Multi 700E	£229.00
Multi U11	£299.00
Multi 2700	£499.00
TM 56B Rcvr 2m	
amateur	£104.00
TM 56B Marine band	£113.00
Inc. VAT & Delivery	

SMC MONITOR - SCOPE £79

inc. VAT
DELIVERY FREE

ANTENNA TUNING UNITS

Amtech 300 1.5/30 Mhz	£37.50
SST 1 Random Wire	
1.5-30Mhz	£24.40
SST 2 Ultra Tuner	
3.5-30Mhz	£33.50
SST 3 Mobile Match	£14.90
SST 4 ATU/SWR/PWR	
1.8-30Mhz 30w	£49.50
Dentron MT3000	
10-160Mhz 3kw	£365.00
Leader LAC B95 500w	
SWR/PWR/ATU	£103.00
Incl. VAT & Delivery	
XTAL FILTERS	
YF 90H12	£13.50
YF 30H350	£13.50
YF 90H2.4	£13.50

SECURICOR - HIRE PURCHASE - ALL EQUIPMENTS SERVICED

THE CHOICE IS YOURS!



YAESU MUSEN General Coverage Communications Receiver FRG-7



£182.75 PLUS VAT

● **0.5-29.9MHz Coverage with 10kHz Readout**
The FRG-7 is a precision-built all-purpose communications receiver, featuring all solid state construction for long life and high performance. Utilizing the Wadley Loop drift cancellation system, in conjunction with a triple conversion superheterodyne circuit, the FRG-7 boasts high sensitivity along with excellent stability. It provides broadcast listeners with such features as a 3-position tone selector, an RF attenuator, and an automatic noise suppression circuit. For many years of satisfying reception, the FRG-7 is the receiver for you.

YAESU MUSEN Digital Display Communications Receiver with CPU Digital Clock & Timer FRG-7000



£327 PLUS VAT

● **0.25 Thru 29.9MHz Coverage with 1kHz Readout**
Computer technology and convenience features are brought together in the FRG-7000, a digital-display general coverage receiver for the discriminating SWL. The digital clock and timer, controlled by a CPU (Central Processing Unit) chip, will read out both local and GMT time, and will control peripheral station equipment such as a tape recorder. Improved SSB selectivity, ease of operation, and rugged construction are yours with the new FRG-7000 from YAESU.

FULL DETAILS OF THESE EXCITING RECEIVERS FROM THE NUMBER ONE IMPORTER - PLUS EX-STOCK FREE SECURICOR DELIVERY!

(36 pence in stamps brings Illustrated Brochure and our Credit Voucher value £3.60) - A 10 to 1 Winning Offer!

AMATEUR ELECTRONICS UK

508-514 ALUM ROCK ROAD
BIRMINGHAM 8

Tel: 021-327-1497/6313
Telex: 337045



Meet 'Uncle Tom'. He's on your wavelength.



Tom Beaumont - a radio enthusiast for 25 years - sells radio equipment for love! And he particularly loves Lowe - Trio for quality, value and reliability.

Tom is the sole authorised Lowe - Trio distributor for Yorkshire and North East England, and he offers the best before-and-after-sales service around on units like the top-value SRX-30 receiver illustrated.

THE LOWE SRX-30

All the facilities of a top-class communications receiver in one top-quality, economically priced unit. Covers 500 KHz to 30 MHz with excellent dial readout and re-set accuracy. AM, CW, SSB reception. The SRX-30 is equally at home in broadcast or amateur bands.

Other features include RF gain, fine tuning selectable sidebands, built-in loudspeaker, AC mains or 12V DC operation and rugged construction at an attractive price - Just £175.00 inc. VAT.

Buy by post or call in - or phone your Barclay Card or Access number. For speedy delivery on your SRX-30, please send cheque/P.O. made out to Leeds Amateur Radio for £178.00 which includes £3.00 carriage and packing. We will deal with your order by return.

Alternatively, call in for a chat at 'Uncle Tom's Cabin'. The shop is just 10 minutes from Leeds City Station, and there's easy parking if you travel by car.

● Instant H.P. for Licenced Amateurs. ● Extended Credit Terms Available. ● Send 50p for Catalogue and Price List.

LOWE TRIO DISTRIBUTOR



Leeds Amateur Radio are area distributors for Jay Beams, Antenna specialists and Hilomast products.



LEEDS AMATEUR RADIO
Reliability in Radio

Leeds Amateur Radio, 27 Cookridge Street, Leeds 2, West Yorkshire. Tel. Leeds 452657.

FIT A DIGITAL DISPLAY TO YOUR FRG7 OR SRX30.

These units come complete, with only three wires to connect. The FDU7 for the Yeasu FRG7 can be fitted in place of the KHz dial, or can be supplied for external use. (Please state when ordering). The FDU3 for the SRX30 is supplied for top of the set use only. (Full Fitting Instructions are supplied.)

(FDU7) for FRG7
(FDU3) for SRX30

@ £44.77
@ £44.77

We also manufacture an R.T.T.Y. Converter. The MB6R (Receive only) and the MB6R/T (Receive/Transmit). We supply these units with single or double current loops for connection to teleprinter. To Order. T.T.L./C-MOS Logic Levels and Oscilloscope Outputs are provided. Dimensions (84X304X210).

(MB6R Double or single current) @ 77.96
(MB6R/T Double or single current) @ £83.25

(All Units are fully Guaranteed, and come complete)
(No extras needed)

(All prices inclusive of postage and V.A.T.)
(Payment by P.O., Cheque or Access)

**B. BROOKES ELECTRONICS, 69 Leicester Street,
NORWICH NR2 2DZ, ENGLAND.
Tel: 0603-24573.**

STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA
ENGLAND
Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers. Full range of VHF receivers - transceivers. Mobile equipment pre-selectors - filters - antennas. Stabilised power supplies from 2 to 20 Amp. Antenna switches - converters. Aluminium masts - clamps. Antenna rotators.

Yaesu
FRG7-FRG7000

Drake
SSR-1 * SPR4 * R4C *

Secondhand Equipment

Our secondhand equipment stock changes daily. Send S.A.E. for latest price list. Part exchanges welcome. Access-Barclaycard and H.P. facilities.

TRIO
R-300-RB20S

Lowe SRX30 Receiver

Antenna Multituners

Designed and manufactured by ourselves.

Over 1000 sold in over 50 countries.

Mk2 covers 550 KHz 30MHz
Prices include VAT and postage. **£25.00**



FRG-7



GENERAL COVERAGE RECEIVER



There are many types of communications receivers currently available, the choice of which is initially determined by where the user's interests lie. General-coverage receivers, as the name implies, cover a range of frequencies which include broadcast bands, amateur bands and other communications channels, and the Yaesu FRG-7 falls into this category.

On the other hand, if only the amateur bands are required, then receivers for this purpose, offering a greater bandwidth over these frequencies, are available.

In both instances, the tuned frequency may be displayed by "conventional" analogue means, or a digital readout, which gives the tuned frequency in illuminated digits.

The FRG-7 tested by *PW* was already fitted with a digital readout when supplied by SMC Ltd. This is an option which can be retro-fitted to existing FRG-7s and replaces the original dial unit with a 4½-digit red l.e.d. display. The digital display indicates the kilohertz part of the frequency to which the receiver is tuned, while the megahertz part is set using the original MHz knob in conjunction with the "Lock" indicator lamp and the "Band" switch.

A Preselector control is provided which enables the r.f. circuits to be tuned for optimum signal. This control operates a vertically mounted drum which has four bands marked on it. The Band switch selects the basic range over which the Preselector and MHz controls operate, at the same time illuminating the appropriate preselector band.

The "Lock" indicator lamp is extinguished when the MHz tuning control is correctly set to mid-band.

The main tuning control is fitted with a large diameter handwheel knob which has a large felt washer fitted behind it to provide a measure of friction although by no stretch of the imagination could the control be described as flywheel. The fine tune control is fitted just to the right of the main tuning knob and was positioned too close to the main knob for comfort. It proved to be annoying when, after getting the main control set, operating the fine tune meant that one's thumb or index finger caught the large knob putting the set off tune. The fine control also seemed to be much too coarse in operation making precise adjustment of setting, so

essential for successful s.s.b. listening, very difficult. In fact with an adjustment of $\pm 6\text{kHz}$ over 180° swing it was only four times better than the main control and it was almost as easy to set the tuning using only the main control and ignoring the fine one. As supplied the fine control operated in reverse to the main control but this was easily altered by slackening the grub screw of the knob and turning the knob through 180° .

An input attenuator is fitted with a three position switch labelled DX, NOR, Local. The handbook indicates that in the DX position a station which is swamping the set can be attenuated to enable a weaker distant station to be received. We were not able to verify this as in the Bournemouth area no signals seemed strong enough to overload the front-end. All the attenuator seemed to do was cut down the signal strength, so the set was operated with the attenuator in the normal position.

The Tone switch changes the audio response of the receiver and has three positions, 250Hz to 3kHz, 400Hz to 2.5kHz and 250Hz to 1.5kHz.

The other front panel controls fitted are a volume control and the Mode switch. A horizontal scale S-meter is fitted above the tuning dial. The dial lamps can be switched off independently of the main power, which cuts down on current drain from the battery pack when running from batteries.

The audio output, rated at 2 watts, is not hi-fi but is presentable and enables the receiver to be used on the broadcast bands.

A pair of phones can be used instead of the speaker fitted, the phone jack being on the front panel together with the jack for the record output.

The performance of the FRG-7 on a.m. was excellent with a very good single-signal response. However, on s.s.b. and c.w. the set lacked selectivity with the standard filters. Alternative filters are available as optional extras but were not tried in this test.

Three sockets are provided on the rear of the case for aerials. Two of these are push-type terminals for long-wires while the third is a SO239 socket for use with a coaxial type

THE WADLEY LOOP

The FRG-7, in common with many other contemporary communications receivers, employs the Wadley Loop, triple-conversion superheterodyne system. This offers a number of advantages in terms of performance.

A high first intermediate frequency can be used, in this case around 55MHz, giving good image (second-channel) rejection. The problems inherent in achieving satisfactory frequency stability in the first oscillator ("MHz Set"), which must operate in the v.h.f. band and tune over a range of some 30MHz (55.5-84.5MHz), are overcome by mixing its output in twice, so that any errors due to drift are self-cancelling.


As shown below, this is done by mixing the first oscillator output with a spectrum of harmonics from a stable 1MHz crystal oscillator. The product at 52.5MHz is selected by the Band-pass Filter and mixed with the 1MHz-wide band of signals coming from IF1 to translate them to the band 3-2MHz for IF2.

The output of IF2 is mixed with the output of the "kHz Set" oscillator in Mixer 3. Because this oscillator operates at a reasonably low frequency, and over a band just one megahertz wide, it is not too difficult to make it adequately stable. The output of Mixer 3 is at 455kHz, and is passed to a conventional i.f. filter/amplifier chain, detectors and a.f. stages.

Because there are no conventional band switches other than in the r.f. preselector stage, problems due to varying contact resistance in the oscillator circuits (a common cause of instability) are eliminated. Because the whole range of 0.5-30MHz is tuned in bands 1MHz wide, the tuning resolution of the receiver is the same at 1MHz as at 30MHz.

Disadvantages of the system are the large number of mixing stages employed, calling for careful screening and filtering if spurious products are to be kept low, and the need to design efficient filters operating in the v.h.f. band, for IF1 and the Band-pass Filter.

The actual frequencies adopted in the early stages of receivers using the Wadley Loop principle vary between different models; those shown here are as used in the FRG-7. Anyone checking the sums for themselves may wonder about the fact that the "MHz Set" oscillator tunes down to 55.5MHz, which is within the passband range of IF1, inferring that the receiver will tune down to zero frequency! In fact the lowest band is cut off at just below 0.5MHz by the response of the r.f. stages, and on that band, the signals passed to IF1 are limited to 55-54.5MHz and those in IF2 to 2.5-2MHz. The "kHz Set" oscillator only tunes over 2955-2455kHz on this band. In many Wadley Loop receivers, IF2 is fixed-tuned with a 1MHz passband, but in the FRG-7 it is tuned in step with the "kHz Set" oscillator.

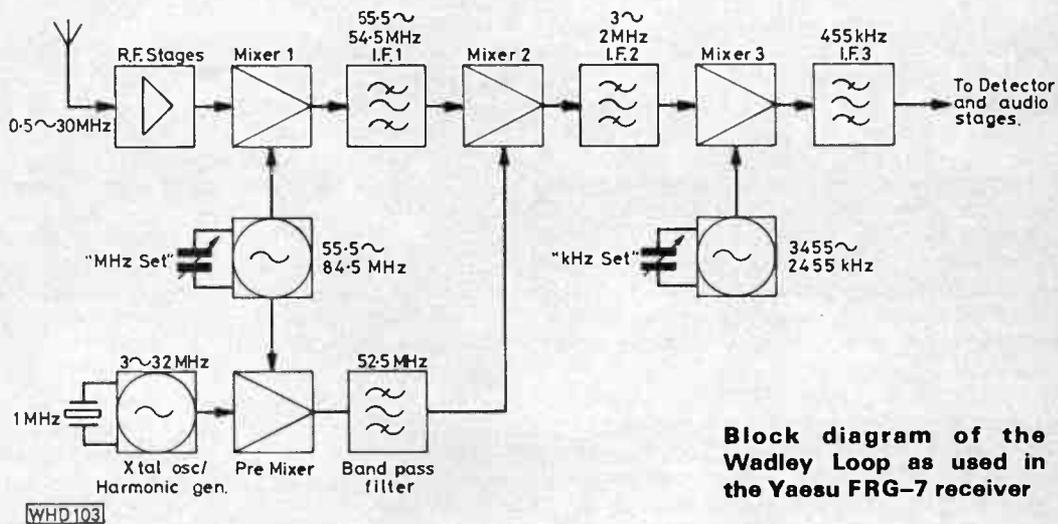

Block diagram of the Wadley Loop as used in the Yaesu FRG-7 receiver

feeder and this is electrically common with the push terminal labelled SW1. This can cause confusion since the coaxial socket is labelled SW1 on the circuit diagram, SW2 on the receiver back panel and to add to the confusion a label immediately above the aerial sockets gives the ranges as SW1, SW2, SW3 and SW4.

The handbook provided with the set was generally good, with an adequate circuit description, a full circuit diagram drawn reasonably well and very legible, a block diagram of the set and a comprehensive components listing.

The operating instructions were generally good but there


were some omissions. The English was very good for a Japanese model with none of the usual funny sentences which seem to occur during translation from the original.

Maintenance and alignment information together with a voltage chart and p.c.b. component layout drawings should help if it is ever necessary to overhaul or repair the set.

As well as the operating manual, the FRG-7 is supplied with two lengths of copper flex for use as aerials, all the necessary plugs and two spare fuses.

The maker's guarantee is for twelve months but does not include the semiconductors.

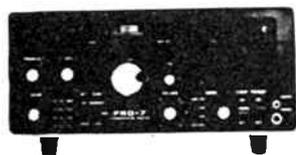THE COMMUNICATIONS RECEIVER THAT HAS IT ALL . . .



FRG-7

The finest general-coverage synthesised communications receiver on the market

£210.00 inc. VAT

Also available from us with special 2m converter, all for just an extra **£17.00**

★

Phone for details of current stocks, both new and secondhand

★

AMATEUR RADIO EXCHANGE

2 Northfield Road, Ealing, London, W.13.

Tel: 01-579 5311

Easy terms up to 2 years

Credit Card Sales by Telephone

Closed all day Wednesday

DATONG ELECTRONICS LIMITED

MODEL D70



INSTANT MORSE PRACTICE
Imagine the convenience of having your own source of accurate Morse for instant receiving practice anywhere at any time!
The Datong MORSE TUTOR produces digitally a random stream of five character groups at variable speed and with variable extra spacing between letters. You can select letters or numbers or a mixture and unlike records or tapes, the sequence never repeats.
Advanced CMOS circuitry gives long life from internal 9 volt battery (PP3). Supplied ready to use, only £37.00 plus VAT (£41.62 total)

MODEL UC/1 UPCONVERTER



"GOOD GENERAL COVERAGE RECEIVERS COST A FORTUNE!"

True . . . but if you already own a good quality ten-metre or two-metre receiver or transceiver you are only £118 away from a really high performance general coverage receiver. Just add the magic ingredient, MODEL UC/1 from DATONG!

You get full coverage in thirty synthesised 1 MHz segments from 80kHz (Rugby MSF) to 30MHz, at high sensitivity and with all the facilities and high performance of your existing rig!

For good measure UC/1 also adds two-metre coverage to ten-metre receivers.

Power requirements: 12v, 120 M.A.
Price: £105.00 plus VAT (£118.13 total)

MODEL AD 170 ACTIVE ANTENNA



"A GOOD RECEIVER DESERVES A GOOD AERIAL"

For sensitive reception right through from MSF at 80kHz to Band 1 TV DX around 50MHz, without the need for an antenna farm, MODEL AD170 has no adjustments and needs no external tuning units. Although only three metres long, MODEL AD170 has the same directional properties as a full size dipole.

even at 80kHz
Price: £29.50 plus VAT (£33.19 total); Special price complete with mains power unit: £33.00 plus VAT (£37.13 total)



Full data sheets available on request.

Contact: DEPT: P.W.7, DATONG ELECTRONICS LTD., Spence Mills, Mill Lane, Bramley, Leeds LS 13-3HE.

Tel: (0532)-552461

FRG7 Communications Receivers

Ours are Better . . .



... Why?

£210 inc vat* and Securicor delivery

PLUS
FREE: HEADPHONES
SHORT WAVE AERIAL

SAE FOR COLOUR BROCHURE

*Price correct as 8th May.

We've been selling this receiver now for more than two years and, as value for money, its pretty difficult to beat. It's been our pleasure to introduce many hundreds of customers to the fascinating hobby of short wave listening and as the first step to obtaining their amateur radio transmitting licence. So why are our FRG7's better?

Well, as enthusiasts as well as retailers, we're pretty fussy on the receiver performance and with mass production, limited factory alignment time and a journey of 6,000 or so miles, the untested, boxed item may not be giving its best performance.

That's why every unit we sell is first checked in our well equipped service department for sensitivity, stability and mechanical soundness. In fact, the test equipment we employ for this task alone costs over £5,000! Once we are satisfied that the receiver performs to specification, we despatch to you via Securicor for safety and speed. Maybe we are a little more particular than most retailers, but that way we tend to get more satisfied customers.

For those of you with Barclay or Access cards you need simply telephone us, quoting us your number and address, and your receiver will be despatched by return.

The Complete Ham Radio Centre:—

WATERS & STANTON ELECTRONICS

31, SPA ROAD, HOCKLEY, ESSEX. TEL. 03-704 6835

Opening hours Mon-Sat. 9 a.m.-5.30 p.m. Exc. Wed. 1 p.m.

S.E.M. BOX 6, CASTLETOWN, ISLE OF MAN.

TEL. MAROWN (0624) 851277



JOIN THE THOUSANDS OF OTHERS WHO HAVE IMPROVED RECEPTION SENTINEL STANDARD FET 2 METRE PRE-AMPLIFIER Ultimate performance pre-amp with a 1dB N.F. selected FET and 18dB gain. 12V nominal (9-15V) at 5mA. £10.85. 70cms, Satellite and Marine Band also in stock.

SENTINEL AUTO 2 METRE PRE-AMPLIFIER

Same performance as above with an r.f. switch so that the unit can be left in the transceiver aerial lead and transmitted through. £17.35.

SENTINEL H.F. WIDEBAND PRE-AMPLIFIER

Covers 2-40MHz. 15dB gain. Ideal for receivers where gain falls off above 20 metres. Weak signals e.g. OSCAR. When used with a short aerial acts as an ACTIVE aerial. £9.00.

SENTINEL AUTO H.F. PRE-AMPLIFIER

Same as above but with a relay for transmitting through, or to give straight through operation when switched OFF. £12.94.

For further details on our S.E.M. Z Match A.T.U., Power Amplifier/Pre-Amplifier, Converters and Transverters do ring or write.

ACCESS/BARCLAYCARD/VISA or C.W.O. All units in stock. 12 months guarantee. Prices include VAT and delivery.

★ specifications

Mode: AM; SSB: (USB, LSB); CW

Frequency range: 0.5MHz–29.9MHz

Sensitivity: SSB/CW better than 0.7 μ V for 10dB S/N at 30% modulation

Selectivity: 3kHz – 5dB
7kHz – 50dB

Frequency stability: Within 500Hz during any 30 minute period after warm-up

Input Impedance: 0.5MHz – 1.6MHz High Impedance
1.6MHz – 29.9MHz 50–75 Ω unbalanced

Output Impedance: 4 Ω

Audio Output: More than 2 watts

Power requirements: 100/110/117/200/220/234V a.c. 50/60Hz or 13.5 d.c.
Negative ground

Batteries: Type UM–1 \times 8

Dimensions: 340 \times 153 \times 285mm

Weight: 7kg without batteries



Internal view of the Yaesu FRG-7

Used in conjunction with a 400 watt p.e.p. transmitter, the receiver performed well. Many contacts were made with W, VK, ZL, ZS and so on, some of these on a simple end-fed long-wire antenna. Copy on the h.f. bands was good, but on the more congested frequencies—such as 40m—it was often felt that a little more selectivity would have been nice. Still, "You pays your money . . ." as the old adage goes, and the FRG-7 represents particularly good value.

A 2.4kHz mechanical filter to improve the s.s.b. performance is available from Ambit International, 2 Gresham Road, Brentwood, Essex, priced at £15.30 (inc VAT). We understand that a Yaesu approved s.s.b. filter may be available from SMC in the very near future.

Prices

Basic FRG-7 receiver £210.37

FRG-7 receiver with digital readout £270.00

Yaesu approved digital readout (SMC) £56.25

(All prices quoted include VAT and carriage)

The FRG-7 receiver reviewed was kindly loaned by South Midlands Communication Company Ltd., Osborne Road, Totton, Southampton SO4 4DN. Tel: 04216 7333, and we would like to thank them for their invaluable assistance in this respect.

The standard of engineering is excellent as can be seen from the photograph of the inside of the set we tested.

The receiver was subjected to several air-tests, using a variety of antennas, ranging from a 132ft long wire to a multi-element rotary beam. On the broadcast bands the receiver performed very well indeed and the s.s.b. capability for amateur reception was also quite good. (The latter mode can be quite dramatically improved, incidentally, by the inclusion of the mechanical filter, produced for the FRG-7 by Ambit International.)

The Wadley Loop provides a good degree of stability in the receiver. This is especially necessary for acceptable sideband resolution—at 29MHz, for the receiver to remain within about 25Hz of the tuned frequency, a stability factor of about one part per million is called for. Long-term stability is perhaps less important to the amateur than stability in the short-term, and the FRG-7 performs quite well in this respect. However, since the Wadley Loop system involves multiple conversion, it is difficult to achieve a wide dynamic range, a problem which is overcome to some extent in this receiver by the use of a balanced mixer.

**NEXT MONTH WE REVIEW THE
LOWE SRX-30
RECEIVER**

C.B. ELECTRONICS

UNIT 3, 771 ORMSKIRK ROAD, PEMBERTON, WIGAN, WN5 8AT
Telephone: Wigan (0942) 216567

THE BEST IN THE NORTH-WEST

The Communications Receiver that has it all

FRG-7

£210.00 incl. VAT + £2.00 p&p./ins.

Also available from us with Microwave Modules converter all for just an extra
£20.25

All orders dealt with promptly by Mr. Jack Stephens

G3LRB

Western

THE COMMUNICATIONS SPECIALISTS
EVERYTHING FOR THE RADIO AMATEUR



YAESU FRG-7000

£329

The New Performance Standard in Communications receivers!

A high quality general coverage receiver for the discerning SWL and a worthwhile addition as a second receiver for the transmitting amateur.

How often have you wanted a true general coverage receiver of this calibre but been put off by the price.

The FRG-7000 is a cost-effective answer to your prayers.

* Full and continuous coverage 250kHz to 29.999MHz * Operation on SSB/AM/CW * Switched selectivity and fine tune control for maximum efficiency on SSB * Accurate digital frequency readout to 1kHz, using advanced CPU techniques * Built-in digital clock with facilities for setting two time zones (GMT and local), selected at the flick of a switch * CPU controlled timing clock switches receiver on or off at preselected times; also enables control of external unit such as tape recorder * Wadley loop circuitry for minimum drift and maximum stability * Simple and accurate frequency selection; easy-to-use colour coded bandswitch and preselector.

Send large SAE for further details of this and other equipment - or use our Answerphone after hours.

Western Electronics (UK) Ltd

HEAD OFFICE (All Mail/Enquiries)

FAIRFIELD ESTATE

LOUTH, LINGS, LN11 0JH

Tel: Louth (0507) 4955/6

ACCESS
VISA
DINERS CLUB
H.P.

SOUTHERN VALVE CO.

Telephone 01-440/8641

SECOND FLOOR, 8 POTTERS ROAD,
NEW BARNET, HERTS.
CALLERS BY APPOINTMENT MINIMUM ORDER 80p

Some leading makes available. VAT invoices issued on request.

8VA valves do NOT carry any guarantee. Enquire prices.

Some Mullard Mazda available at extra cost.

NOTE: PLEASE VERIFY CURRENT PRICES. Correct 82p at time of going to press.

DY86/7	55p	EF86	55p	GY501	£1.40	PCF802*	85p	PL36	£1.00	PY500A	£1.80
DY802	55p	EF89	75p	PC86	80p	PCF805	£1.75	PL31A	70p	UBF89	80p
ECC81	60p	EF183	55p	PC88	80p	PCF806	75p	PL83	48p	UCC85	85p
ECC82	63p	EF184	55p	PC97	75p	PCF808	£1.75	PL84	50p	UCH81	80p
ECC83	63p	EH90	80p	PC900	85p	PCL82	85p	PL500	£1.20	UCL82	75p
ECC85	63p	EL34	£2.00	PCC84	35p	PCL83	£1.00	PL504	£1.00	UCL83	95p
ECH81	55p	EL84	52p	PCC85	55p	PCL84	70p	PL508	£1.75	UF89	55p
ECH84	65p	EL509	£3.00	PCC89	50p	PCL805	85p	PL509	£3.05	UL41	95p
ECL80	52p	EM84	90p	PCC189	55p	PCL85	85p	PL519	£3.30	UL84	90p
ECL82	65p	EY86-7	48p	PCF80	80p	PCL86	85p	PL802*	£2.30	UY85	80p
ECL86	72p	EY500A	£1.80	PCF86	80p	PCL200	£1.45	PY88	90p	U25	60p
EF80*	42p	EZ80	43p	PCF200	£1.80	PD500	£3.70	PY800	70p	U26	80p
EF85	45p	EZ81	45p	PCF801	80p	PFL200	£1.35	PY801	70p		

We offer return of post service. CWO ONLY. No C.O.D.

Post free over £25. £6 to £25—80p (max).

Items in stock at time of going to press but subject to possible market fluctuations if unavoidable.

STOP PRESS! One valve post 15p, each extra valve 6p. Large valves 2p each extra.

STOCKISTS UHF WIDE BAND MAX 75p. LISTS AND ENQUIRIES. S.A.E. PLEASE!

"MICRO" AERIAL! ALL PRICES INCLUDE VAT @ 12½%. E240/41. 70p each.

SIZE 1½"x3" only £3 70p incl. ENQUIRIES WELCOMED FROM TRADE and RETAIL (same prices)

Can YOUR Antenna do all this?

A SMALL SELECTION FROM OUR HUGE FILE OF TESTIMONIAL LETTERS ON THE JOYSTICK VARIABLE FREQUENCY ANTENNA (1.5-30MHz).

G4DJY's COPY LOG shows 68 North Americans worked in the ARRL W/VE contest.

W6TYP worked WA6JPR over hundreds of miles on 40m. using the JOYSTICK VFA and MICROWATTS "equivalent to 1,000,000 MILES PER WATT"—A WORLD RECORD—we can supply conclusive evidence!

"I have used Rhombics, 4 x ½ waves in phase, centre fed dipoles, etc., but the success I have had with the V.F.A. has been AMAZING... only 20ft. high... in front of my mobile home. I NEVER RECEIVE LESS THAN R7 AND MOSTLY R9 ON CWDX WORKING—Bob Green, SUIKG/G3APH, W.B.E., W.A.C. Phone and CW.

W7OE, U.S.A. Government Electronics Engr. (reted.), claims "VFA 5ft. below ground, same as dipole, elevated 15ft., one "S" point UP on dipole."

IN USE BY AMATEUR TRANSMITTING AND SWL STATIONS WORLD-WIDE AND IN GOVERNMENT COMMUNICATION

JOYSTICK ANTENNAS

SYSTEM "A"

£41.00

200 w. p.e.p.
OR for the SWL

SYSTEM "J"

£47.95

500 w. p.e.p.
(Improved "Q" on receive)

"PACKAGE DEALS"

COMPLETE RADIO STATIONS FOR ANY LOCATION

All packages include the JOYSTICK VFA (System "A") 8ft feeder, all necessary cables, matching communication headphones. Delivery Secured our risk. ASSEMBLED IN SECONDS. You SAVE £14-15 on each PACKAGE DEAL!

PACKAGE No. 1. Features R.300 Rx.

£222.00

PACKAGE No. 2. Features FRG7 Rx.

£237.45

PACKAGE No. 3. Features SRX30 Rx.

£212.45

PACKAGE No. 4. Our "Rolls"—Rx. FRG7000.

£402.00

RECEIVERS ONLY

R.300

£184.50

FRG7

£199.95

SRX 30

£174.95

FRG 7000

£364.50

All prices are correct at time of going to press and include VAT at 12½% and carriage.



Just telephone
your card number
Phone 0843 62535 (ext.5)
(or 62839 after
office hours)



or write for details, send 9p stamp

G3CED




G3VFA

5, Partridge House, Prospect Road, Broadstairs, CT10-1LD. (Callers by appointment).

Every month is the right frequency

When you're building a major project from a PW design, you want to be sure of getting every issue in sequence! Use this order form for a year's supply to be posted to you.

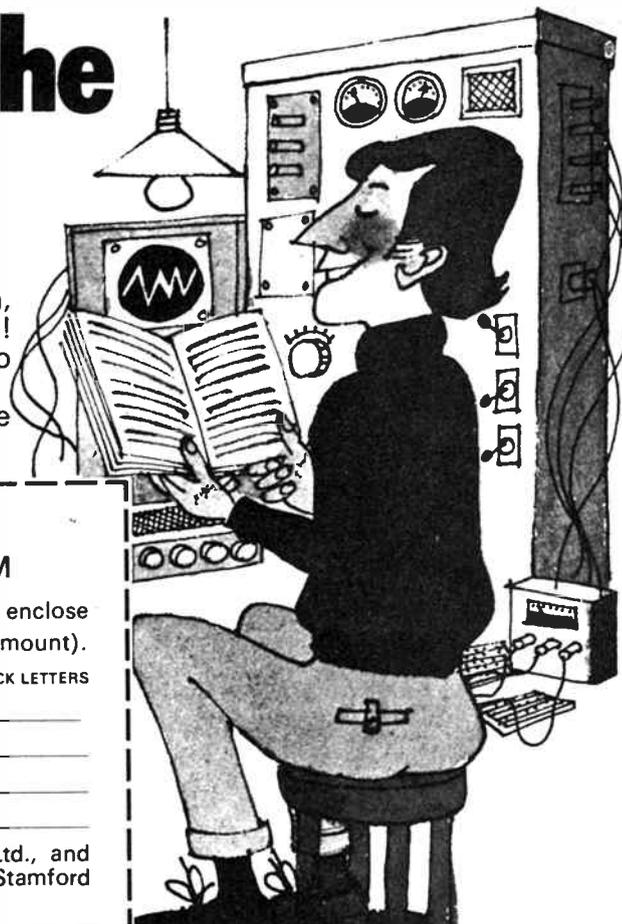ANNUAL SUBSCRIPTION RATES (including postage and packing) U.K. £10.60. Overseas £10.60.



practical WIRELESS SUBSCRIPTION ORDER FORM

Please send me Practical Wireless each month for one year. I enclose a Sterling cheque/international money order for..... (amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss _____

ADDRESS _____

POSTCODE _____

Make your crossed cheque/MO payable to IPC Magazines Ltd., and post to: Practical Wireless, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

NUMBERS WITHOUT TEARS

Continued from page 37

should not be taken to V_{SS} via any wire connecting the c.m.o.s. to V_{SS} . When Tr21 is switching a full 140mA, some very strange arithmetic may be evident from the counters if some of the wiring to V_{SS} is common! Anyone contemplating a p.c.b. design is especially warned of this point.

In order to make the touch plate as mechanically simple as possible, a 6BA cheeseheaded bolt was mounted on (but insulated from) the metal front panel and recessed so that the head was flush with the panel. The entire box was earthed and connected to the mains transformer screen, and connected to V_{DD} via R26 (see Fig. 6).

In this way, a finger placed on the head of the bolt must also touch some of the surrounding painted panel, and this provides sufficient base current to operate the Darlington pair, Tr1 and Tr2. The instrument is thus electrically safe while providing 100 per cent reliable touch operation of the swept-frequency clock.

Fault-finding

It may be found that, on closing S1, the clock does not run. Decreasing R4 to 82k Ω will solve the problem. Similarly, in the swept-frequency mode, it may be found that the clock is still "ticking over" even when C2 is discharged. Increasing R1 to 47k Ω should stop the clock.

These problems arise because of the 5% tolerance resistors used to derive quite a precise voltage at point A (Fig. 2). The author has not found this to be a problem, but theory shows that it is quite possible.

The mains switch, S5, is a d.p.d.t. slider switch mounted on the side of the box adjacent to the top of the front panel. It is thus normally out of sight, reducing the temptation to tamper with it.

Summary

This instrument is designed to appeal to children of 2½ years upwards. The visual effects produced by it are pleasant and interesting. There are switches to use, buttons to press, a knob to turn, and a touch-controlled flywheel display. It aids in the teaching of rapid number recognition and matching, without obviously being a "teaching" toy.

It can also be used as a die for other board games when the numbers themselves have become of secondary importance.

With a little judicious help, the child will soon grasp the cyclic nature of counting in the decimal system—the progression from single-digit numbers to dual-digit numbers, the second (tens) digit being the number of complete revolutions of the flywheel, the first (units) digit being the number at which the flywheel stops. ●

Microprocessor Miscellany

People have long been chanting that microprocessors are going to end up in "everything". One of the latest applications to reach my ageing eyeballs is in typewriters. The new ET 221 for example is not the established "golfball" but a "daisywheel". Built-in is a Z80-based system that uses a number (note: not just one) of 8-bit, single-chip microcomputers. To be sold in the US for under \$2000, this new wonder-writer has a 20-character display for showing what you've been typing in line at a time. It can also store lines and page formats too, so it appears to be bordering on a form of word processor.

Another microprocessor application to loom is in controlling motors. When one considers that there are virtually millions and millions of motors in so many different applications, the enormous market becomes apparent.

There are some very good reasons, too, for using microprocessors in this application. The first is that old chestnut—money. For example, many motors rely on costly feedback loop circuitry required for close speed control. It has been claimed that just over £1 worth of digital chip can replace £5 worth of analogue circuitry to do the same job. The microcomputer can also do far more than adjust speed. For example, it can check the motor current against a table of maximum values which it holds safely stored in its ROM. This very same ROM can contain a program that limits both the instantaneous and surge currents drawn by the motor at any given time. This, besides offering a safety factor, also allows the manufacturer to use smaller, and probably cheaper motors to do exactly the same job.

Big Bang Theory

A few Ginsbergs ago I mentioned Lithium batteries. They appeared to offer advantages, but I now hear of disadvantages—like they explode. Perhaps not all Lithium batteries do this, but it is reported from America

that the powerful Federal Aviation Administration has ordered that Lithium-Sulphur-dioxide batteries must be removed from emergency aircraft locator transmitters within 30 days. Apparently half a dozen or so reports were received of LiSO_2 batteries exploding. Some 6000 aircraft in the US carry equipment that uses LiSO_2 batteries.

Mon Dieu

I note with great interest that a British company has come up with an i.c. certain to cause a linguistic stir. By adding it to your teletext/viewdata decoder set, you can have the potential to display the whole lot in one of 28 different languages—Ha so! Perhaps you don't get the whole 28 in one go, but an order has already been received for the chip from across the pond in Canada, where the new i.c. is to enable delighted viewers to see viewdata information in a 20-row format (32 characters/row) in English and French. Had this happened when de Gaulle was in office, the designers would have been given the Legion of Honour and free wine for life. How about it, Giscard?

Stable Arrays

And pleased I am, too, to tell of another British achievement. A well-known establishment has come up with a new way of addressing twisted nematic liquid crystals. The liquid crystal display matrix can be driven continuously over the whole of its area and thus the annoying flicker associated with multiplexed arrays is eliminated.

Complementary m.o.s. (CMOS) powered by only 15V is used to drive a 100×100 matrix at around 5kHz. Researchers believe that 1000×1000 element arrays are possible. This, coupled with the low voltages and flicker-free display, could have great impact on the small screen TV and scope development. A pocket oscilloscope with a power consumption of, say, 500mW becomes a reality.

Bye-Bye Noise

The Dolby system of noise suppression in audio and hi-fi equipment is now very well entrenched. But a German company has arrived with an alternative—and the claims are that it's better, too. The new system is called High Com and it claims to be an improvement over the Dolby system in two areas. The first is that it removes an extra 10dB of noise. It is also said to perform this kind act over the audio spectrum—that's 30Hz to 20kHz, not just over a narrow band.

The immediate area of obvious improvement is at the l.f. end. The Dolby system starts to be effective at around 300Hz, so it isn't so effective against our old audio enemy "mains hum" at around 50Hz. The name High Com derives from "high fidelity compander" and during compression the lowest level signals are amplified. Thus any noise that is picked up or contributed by either the storage medium employed or the actual transmission path finds the amplified signal that much stronger and therefore that much higher above the noise level.

The immediate application for such a device is in consumer audio goods and it is rumoured that some 20 European electronics manufacturers are very interested indeed, as are four of the big Japanese producers. One claim is that when the High Com was used on an audio cassette tape recorder, the measured noise was found to be no less than 20dB down. The magic i.c. that helps achieve all these wonderful things is designated U401B and it comes disguised in a 24 pin d.i.l. plastic package. It has been suggested that the new device could be very usefully employed in radio and television. Although it will cost a little more than the Dolby counterpart at present, volume production will doubtless bring the prices tumbling down. Please note: you cannot buy one yet.



INEXPENSIVE AF electronic voltmeter

M. TOOLEY BA G8CKT

Most multi-range meters offer a rather mediocre performance on the a.c. voltage ranges. The Avo 8 MkIV, which has long been one of the writer's favourite test instruments, exhibits an internal resistance of only 250 ohms on the most sensitive (2.5V) a.c. range. This is clearly very unsatisfactory regarding sensitivity and circuit loading when measurements are to be made on today's electronic circuits. The instrument described was therefore developed as a replacement for the Avo on the a.c. voltage ranges and it offers the advantages of a 1MΩ constant input impedance on all ranges and a frequency response which is substantially flat from 10Hz to well over 100kHz. Six voltage ranges are provided, with a maximum sensitivity of 100mV r.m.s.

The unit uses low cost readily available components and can be built for an outlay of around £10. Battery consumption is minimal and a small 9V battery will provide for many hours of operation.


Circuit Operation

The a.c. voltage to be measured is applied to a switched potential divider, R1 to R6. The range is selected by S1 and capacitor C1 is used to remove any d.c. level present on the input voltage. R7 provides a measure of protection for the field effect transistor, Tr1, and C2 provides a degree of high frequency compensation. Tr1 operates as a

source follower and exhibits an extremely high input impedance (greater than 100MΩ) thus minimising the loading effect on the potential divider. Tr1 provides a voltage gain of slightly less than unity, the output voltage being developed across R8.

Silicon transistors, Tr2 and Tr3, form a two-stage high-gain amplifier. Both transistors are operated in the common emitter mode. The amplifier incorporates three feedback loops which help to ensure unconditional stability, a wide operating bandwidth and a high degree of linearity. Stabilisation of the transistor bias is provided by means of direct current feedback from the emitter of Tr3 to the base of Tr2 using R9. C4 provides negative feedback in the second stage of the amplifier. This helps reduce any tendency to oscillation at high frequencies and also ensures that the frequency response "rolls-off" beyond a few hundred kilohertz. VR1, the emitter resistor of Tr2, is used to set the overall voltage gain by controlling the amount of negative feedback present.

Germanium diodes, D1 and D2, from a voltage doubler rectifier arrangement. The arrangement of C6 and C7 provides a means of reducing the surge current through the meter movement during switch-on. Silicon diodes, D3 and D4, provide a "last ditch" protection for the meter movement by offering a shunt path to current when a 600mV voltage drop of either polarity appears at the meter terminals; this corresponds to an eight times overload.

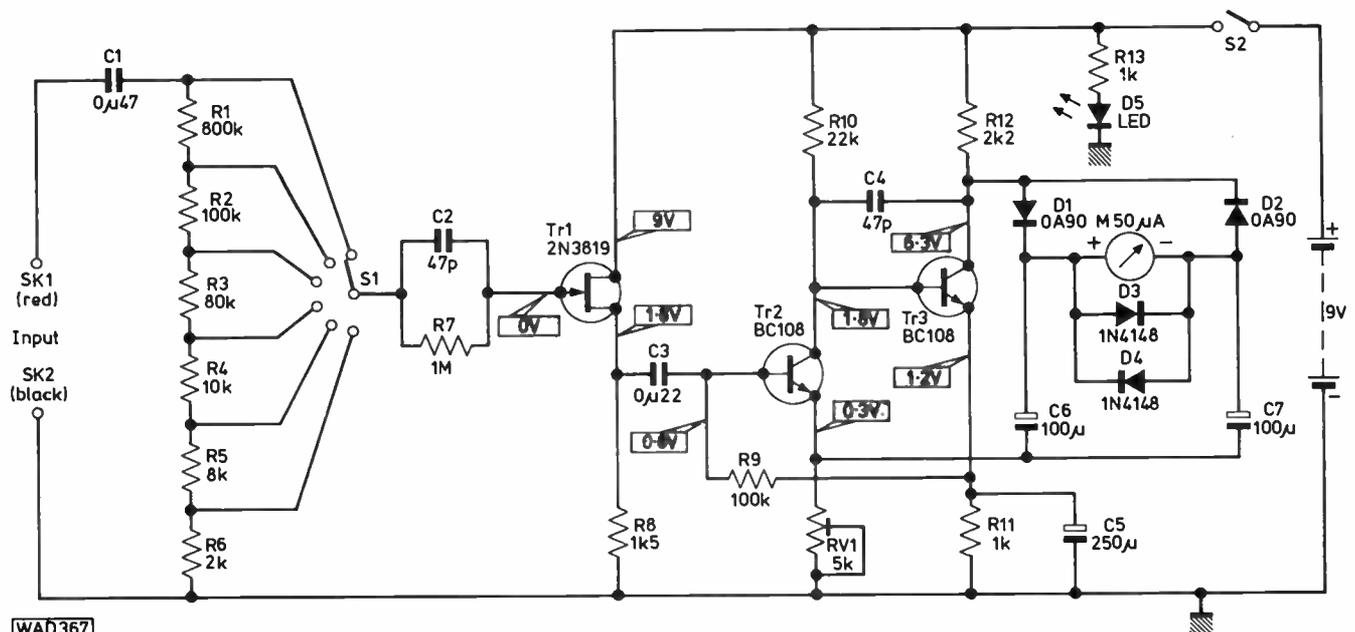

WAD367

Fig. 1: Circuit diagram of the a.f. electronic voltmeter



★ specifications

Voltage ranges: 100mV, 500mV, 1V, 5V, 10V, 50V

Input resistance: 1M Ω on all ranges

Frequency response: Typically 5Hz to 250kHz at 3dB down

Accuracy: $\pm 5\%$

Supply: 9V d.c. at 10mA

Construction


The impedance converter and the amplifier circuit are constructed on a p.c.b. The circuit board layout is shown in Fig. 3. The range selector switch, S1, is mounted on the front panel of the instrument together with the meter movement, power on/off switch, l.e.d. indicator and input sockets. The potential divider resistors, R1 to R6, are most conveniently wired directly to the tags of S1. C1 is wired directly between the input terminal and top end of R1, which is located on S1. Note that the high frequency response of the instrument will depend very much on the stray reactance associated with the input and potential divider wiring. It is essential that all connecting leads be kept as short and direct as possible. The front panel wiring layout is shown in Fig. 4.

Earthing of the metal front panel is achieved by means of the body of S1, which may be soldered to directly in order to provide a common earth point. If an alternative switch is substituted for the recommended type, it may be necessary to locate a separate earth tag on the front panel. This may be most conveniently accomplished by using one of the meter securing nuts. The front panel is labelled by means of dry transfers, and then sprayed with clear lacquer to protect the transfers. During this operation the meter should either be removed from the front panel or be protected using several layers of masking tape.

The instrument is housed in a standard Vero case. Any other suitable case may of course be substituted provided that any metal parts are connected to the earth or common rail. It was not found necessary to use a totally screened enclosure for the instrument, as with careful wiring there should be no pick-up of hum or stray signals within the unit. The unit will not, however, give accurate indications in the presence of very strong r.f. fields such as may be experienced when measurements are made on medium or high power transmitters.

Testing and Calibration

After completing the assembly of the instrument it is advisable to carry out a thorough visual check of the wiring. Connect a 9V battery to the instrument and measure the d.c. current supplied. If the circuit is functioning correctly this should be approximately 10mA and will vary slightly according to the setting of RV1. Due to a slight difference in the charging currents of C6 and C7, the meter pointer

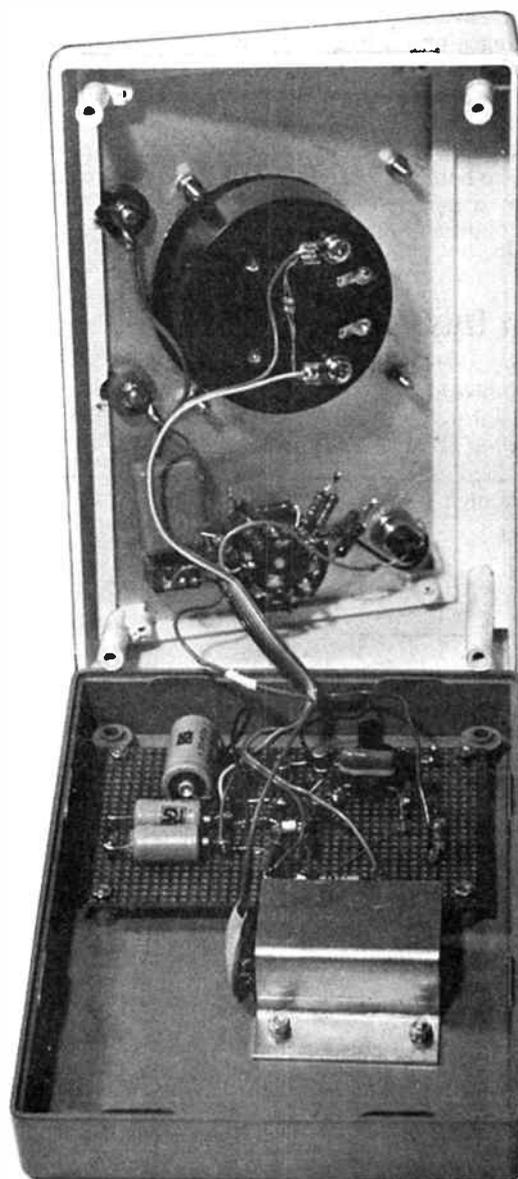

Internal view of the complete instrument. This is the prototype which used a matrix board instead of a p.c.b.


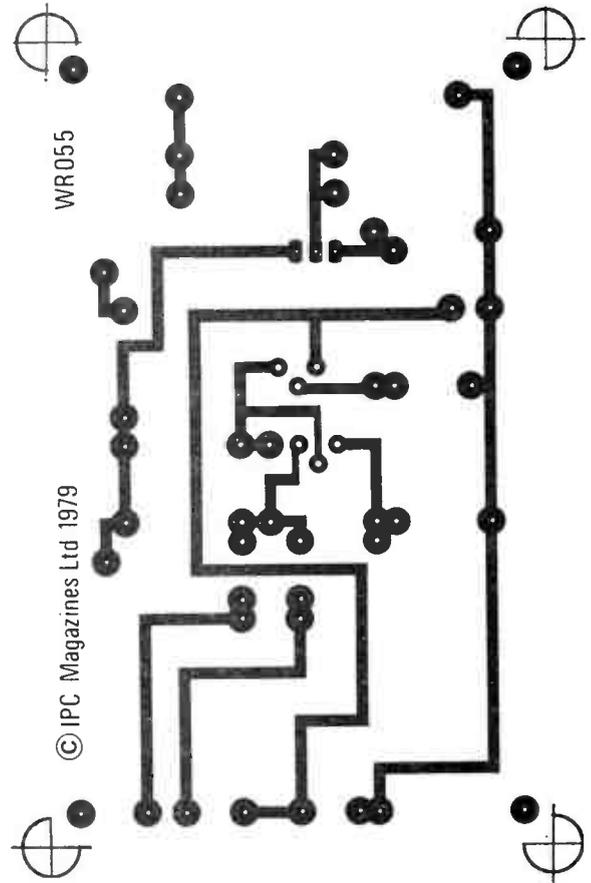
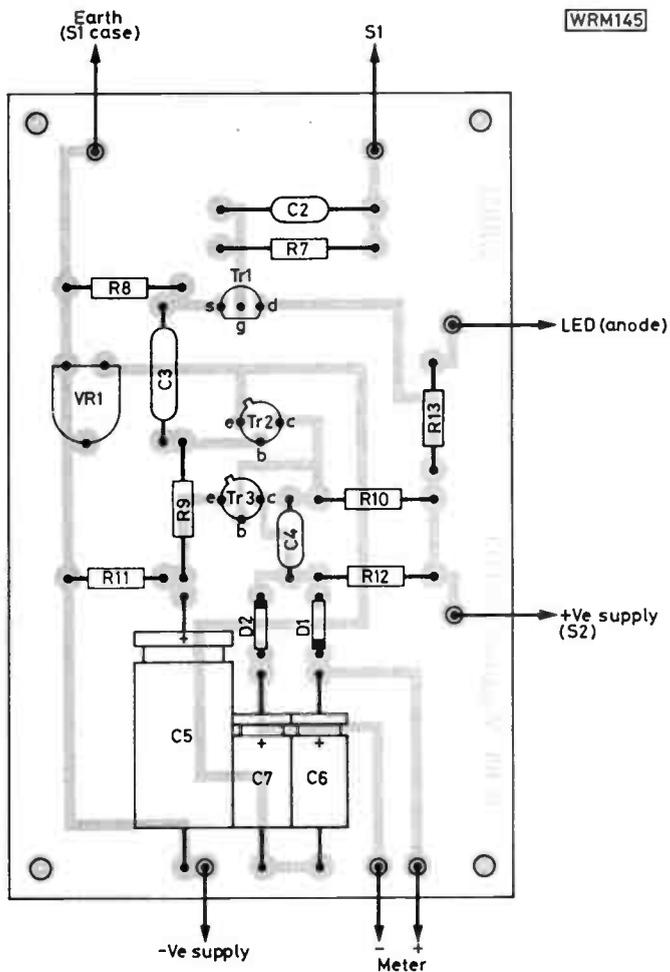


Fig. 2: (above left) The component overlay for the p.c.b. version of the a.f. voltmeter

Fig. 3: (above right) The copper track layout of the p.c.b. shown here full size

Fig. 4: (below) The wiring and layout of the front panel. The resistors on S1 are soldered directly to S1 tags and the end of R6 is soldered directly to the body of the switch

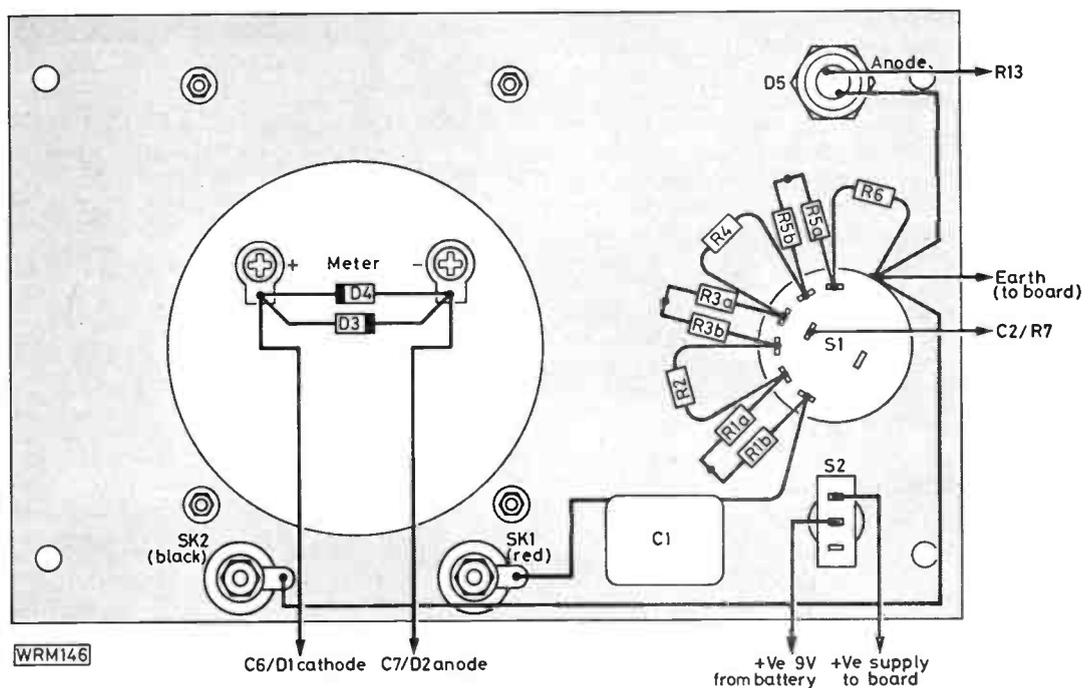

★ components

Resistors

$\frac{1}{2}$ W 2% metal oxide

1.2k Ω	1	R5a
2k Ω	1	R6
6.8k Ω	1	R5b
10k Ω	1	R4
12k Ω	1	R3a
68k Ω	1	R3b
100k Ω	1	R2
120k Ω	1	R1a
680k Ω	1	R1b

$\frac{1}{2}$ W 5% carbon film

1k Ω	2	R11, 13
1.5k Ω	1	R8
2.2k Ω	1	R12
22k Ω	1	R10
100k Ω	1	R9
1M Ω	1	R7

Capacitors

Electrolytic axial leads

100 μ F 25V	2	C6, 7
250 μ F 25V	1	C5

Polystyrene

47pF	2	C2, 4
------	---	-------

Polyester

0.22 μ F	1	C3
0.47 μ F	1	C1

Potentiometers

Miniature horizontal preset

5k Ω lin.	1	VR1
------------------	---	-----

Semiconductors

Diodes

OA90	2	D1, 2
1N4148	2	D3, 4
LED	1	D5

Transistors

BC108	2	Tr2, 3
2N3819	1	Tr1

Switches

1p6w rotary	1	S1
s.p.d.t. min. toggle	1	S2

Miscellaneous

Case Vero 75-1798-k 171 x 121 x 75mm (1); 4mm terminals 1 red, 1 black; Meter, 50 μ A 4 inch scale 110 x 82mm; Printed circuit board; battery connector, knob SW150 with cap and skirt (Sifam).

may give a momentary indication when switching on. The pointer should however return to zero fairly quickly, and if this is not the case the wiring should be re-checked for faults.

To calibrate the instrument a known source of a.c. voltage is required. A signal generator with a calibrated output level may be used, alternatively a comparison may be made with an existing a.c. voltmeter. If neither is available,

a rough calibration can be carried out using a low voltage transformer of known output. A 6.3V filament transformer or the 9V transformer of a power supply is ideal for this purpose. The instrument should be switched to the 10V range and RVI adjusted for the correct reading. The calibration on the other ranges should follow automatically provided that the potential divider has been wired correctly. If a signal generator is available a check can be carried out on each range. The calibration should be consistent to within $\pm 5\%$ on all ranges. If a signal generator is used, it is suggested that calibration be carried out at a frequency of 1kHz. Where a mains transformer is used the calibration will, of course, be at 50Hz. The frequency response of the instrument should be "good" over a wide frequency range, at least 10Hz to 100kHz at the 3dB points, and the frequency response of the prototype instrument on the 1V range is shown in Fig. 5.

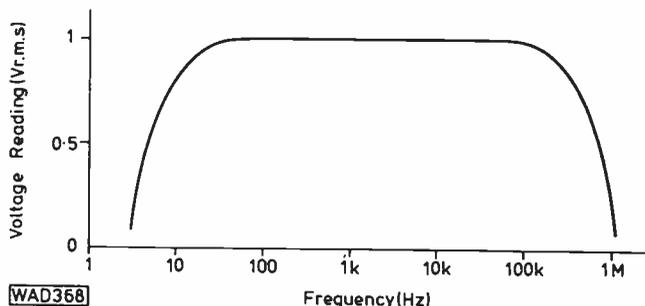


Fig. 5: The frequency response of the instrument

Note that, due to the high input impedance of the instrument, false readings can sometimes be produced on the more sensitive ranges. This is due to pick-up of hum and stray signals on the input leads. The input leads can be screened if desired; the inner lead of the coaxial cable is connected to SK1 (red) and the outer screen to SK2 (black). It is important to note that coaxial cable possesses an appreciable shunt capacitance between the inner conductor and screen (often as much as 100pF per metre). Long screened cables should therefore be avoided since they will impair the high frequency response of the instrument.

VISIT THE *PW* STAND AT
THE GREAT BRITISH
ELECTRONICS BAZAAR,
ALEXANDRA PALACE.
JUNE 28 to 30.

JOHN THORNTON-
LAWRENCE WILL PRE-
SENT THE *PW* LECTURE
"GETTING STARTED IN
AMATEUR RADIO", ON
SATURDAY AT 1200hrs.



AMATEUR BANDS

by Eric Dowdeswell G4AR

The problem of identifying correctly an amateur callsign can present a problem to anyone unaccustomed to listening on the amateur bands. It often seems to be a jargon incapable of being decoded! The answer is not always obvious even if the station is in the clear, but if it is being clobbered with QRM then there really is a problem.

Although there is an ITU phonetic alphabet, given below, it is seldom adhered to by amateur operators who seem to use part of this alphabet and part of their own invention. In a perfect phonetic code the word used to represent a letter, such as "alfa" for A and "bravo" for B, must be neutral, one without any particular connotation and generally understood world-wide.

The approved code starts off all right but then uses "Charlie" for C, although personal and place names ought to be avoided since these can be misleading, especially in amateur use, where station locations and operator's names are constantly being exchanged.

A Alfa	J Juliett	S Sierra
B Bravo	K Kilo	T Tango
C Charlie	L Lima	U Uniform
D Delta	M Mike	V Victor
E Echo	N November	W Whiskey
F Foxtrot	O Oscar	X X-Ray
G Golf	P Papa	Y Yankee
H Hotel	Q Quebec	Z Zulu
I India	R Romeo	

There are several words in the phonetics list which I do not agree with personally, but the problem is to find suitable alternatives.

What causes most confusion however is the amateur's own version of the phonetic code, especially the use of "George" for the G in UK callsigns, particularly where the operator is called "Fred"! Might not matter too much among lads and nets on 2m or u.h.f., but used on the DX bands can only make identification of a callsign all that more difficult.

On numbers, the recommended procedure is to use the word "figure" before any number, to indicate that a figure is to follow, thus "Golf, figure four, alfa romeo". This can only help but it is seldom employed by amateurs unless

they have been trained on a military or commercial network of some kind. The use of phrases like "Red Hot Momma" for RHM in the suffix of a call may be amusing to some but meaningless to the amateur with little or no knowledge of the English language.

I appreciate that this little homily will have no effect whatsoever, but I hope it will serve to demonstrate to the innocent listener to the amateur bands that there is little or no "system" with amateur phonetics. Initially, it is better to write down in full what is heard and then the callsign ought to become apparent, aided by a good list of prefixes, but, as ever, experience will prove the best teacher.

Here and There

Well known to this column for his SSTV reports in the past, **Paul Barker** of Sunderland is now busy on c.w. and s.s.b. with his new callsign G4HPS, having started off with G8OVD. Paul's first s.s.b. QSO was with FG7AS/FS7 on 10m, which is enough to make anyone's mouth water! He uses a TS520S transceiver to an 18AVT multiband vertical, plus an FT221R on 2m to an indoor 4-element quad. Paul managed to get QSLs from all six continents for SSTV reports before getting his ticket.

In Southport, **Peter Hawks** has got going with a DX160 but, like others, found the manual's calibration chart did not match up to reality. He's talking about a digital readout unit but I think he would be better off initially with a crystal calibrator. **Philip Charlesworth** (Southport) has got going with an outside aerial which he finds "staggering" after his indoor one. As he lives on the only hill in Southport he will find the advantage of much greater importance when he gets his ticket in due course. Philip mentions the PA0AA transmissions on 3750kHz for amateurs, followed by slow Morse transmissions. Details of the latest schedules would be appreciated.

Peter Lucas of Newport, Salop, has dumped his R207 and settled for an AR88 but needs to rewire a lot of it. A circuit or manual would be appreciated at 3 Queen's Drive if anyone can help. Pete's been hearing plenty on 10m of late with only a 16ft vertical. In Chiswick, London, **George Gizebieniak** BRS 41733 has bought an old SX24 receiver for £20 and found it worked fine on the 10m band, with converters for 2m and 70cm.

An appeal from **Jim Timoney** ZS1TK for a spare for his KW2000 transceiver, not having had any success with the descendants of KW in this country. He wants the 3-gang tuning capacitor on the pre-selector, part number C40 on the circuit diagram. Any offers of help to me direct please. Another reader in need of help is **M. David** of 46 Pentathlon Way, Cheltenham, Glos, who has got hold of a Star SR550 for just a £1! It works fine but he'd like a manual for copying and return. He's heard an HK on the 10m band and threatens to send in some logs in future.



SOUTH MIDLANDS COMMUNICATIONS LTD.

OSBORNE ROAD, TOTTON
SOUTHAMPTON SO4 4DN

Cables: Aerial Southampton
Telex: 477351 SMCMM G
Tel: Totton (04216) 7333



21 YEARS OF PROFESSIONAL EXPERIENCE

Main importers of Yaesu Musen Communications Products
"2 Year Guarantee – Free Securicor Delivery"

THE FRG7 Synthesised General Coverage Communications Receiver.



The FRG7 is solid state mains and 12v. receiver offering continuous coverage 0.5-30 MHz with specifications unparalleled in its price range.

Its advanced circuitry provides superb performance either as a standby receiver or for SWL's (Broadcast and Amateur Bands alike)

PRICE: FRG7 £210.37 (Carr. Foc.)
FRG7D £270.00 (Carr. Foc.)
(DIGITAL VERSION)
AS REVIEWED IN THIS ISSUE


SMC YOUR SINGLE STOP SOURCE FOR: TRANSCEIVERS, RECEIVERS – HF, VHF AND UHF. ANTENNAS AND ROTATORS CABLE – CONNECTORS – TOWERS – MASTS AND FITTINGS



VHF BEAMS



VHF DISCONES

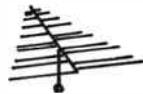

VHF LOG PERIODICS



HF QUADS



HF BEAMS

For fixed station antennas, (from top band to twenty three, from a dipole to a box of 352 elements) for Rotators (a choice of 15 models from Stolle and C.D.E.) and all accessories and fittings – coax, baluns, lightning arrestors, wall brackets, etc, SMC must be the natural choice.

Antenna Tuners
Baluns
Coax Switches and relays
Crystals
Convertors

Dummy Loads
Filters
Frequency Counters
Grid Dip Oscillators
Microphones

Morse keys
Multi-meters
Power meters
Power Units
Rotators

Speakers
Speech Processors
Transvertors
2mtr. Linear Amplifiers
Valves

Available from the following manufacturers:

'Alimasts'
Ampere
Ascot
Bantex
Barlow-Wadley
Belcom
Burns
CDE
CIR
Center Rise
Cushcraft

Dentron
Diawa
Electronic Devlps.
F.D.K.
Fulton
G-Whip
Gem Quads
H.S.
HYP
Hansen
Henry Radio

Hi Mound
Hills
Honda
Hy Gain
I.C.E
Icom
J.D.
J.R.C.
Jaybeam
Junker
KDC

KE
KLM
K.W. (Decca)
Katsumi
Ken
Kenpro
Kuranishi
Kyokuto
Leader
Leson
M.F.J.

Maiden-Sound
Metron
Mickey Mouse
Mini Beams
Mosley
N.E.C.
Nagasawa
Naigai
Omega
R.S.G.B.
Reace

S.M.C.
S.M.L.
Sanyo
Seiwa
Shure
Soar
Speciality Coms.
Stolle
T.T.E.
Tavsau
Technical Assc.

Telco
Telomasts'
Telotowers'
Tempo
Toshiba
Unadilla
Varian
'Versatower'
Wightraps

A chance to see our complete range: Visit 'Unicom 21', Kempton Manor, Sunbury-on-Thames, June 22nd and 23rd. Further details from SMC HQ at Totton, call our Agents or Branches in your area.

G3ZUL Brian Stourbridge (03843) 5917
GM3ZBE Alex Aberdeen (065183) 328

GM8GEC Jack Edinburgh (031665) 2420
GI3WVY Mervyn Tandragee (0762) 84056

GW3TMP Howarth Pontybodkin (035287) 846/324
GW4GSWAlan Swansea (0792) 24140



S.M.C (Jack Tweedy) LTD
Roger Baines, G3YBO
79 Chatsworth Road,
Chesterfield, Derbyshire
Chesterfield (0246) 34982
9-6: Tuesday-Saturday

NORTHERN (Leeds) BRANCH
Colin Thomas G3PSM
257 Otley Road,
Leeds 16, Yorkshire,
Leeds (0532) 782328
9-6: Mon-Wed & Fri-Sat.

S.M.C. (Jack Tweedy) LTD
Jack Tweedy, G3ZY
Ham Shack, Roughton Lane,
Woodhall Spa, Lincolnshire
Woodhall Spa (0828) 52793
9-6: Tuesday-Sat (+ appointments)



Come to the Great British Electronics Bazaar

**"ALLY PALLY"
Thursday-Saturday
28th-30th June.**

FREE!

(AND WAIT TILL YOU SEE OUR SEMINAR PROGRAMME)

The Great Big 'Bazaar' for the hobbyist, amateur, and small buyer.

There's never been an event like this before.

First, the very scale of the exhibition is huge. Virtually all the companies you're used to hearing about (and buying from) will be there. Companies like Fluke and Gould showing off their low cost multimeters; smaller but important manufacturers like Lektrokit and Chromasonics; and even the R.S.G.B. who will have a station 'on the air' throughout the 'Bazaar.'


Then there are the suppliers of low-cost components and equipment. Plus almost all the journals in the business. Plus, oh, so many more interesting people catering for your needs (including computer kits!).

And you get in FREE if you send an s.a.e. (see alongside).

The Seminars.

If you would like to hear just what the experts have to tell you, a season ticket for three whole days can be yours for only £1.50.

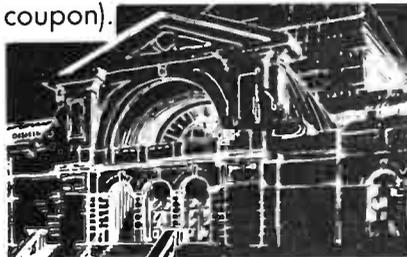Send an s.a.e. and we'll give you all the information (just use the coupon).



Our home for three days - Alexandra Palace, where it all began. (Our seminars are sited alongside the organ - for those who know this unique hall.)

SEMINAR TICKETS

£1.50.

I'd like to sit in at your seminars. (And like a free ticket to the exhibition.) Send me full details, please, and I enclose a large-ish s.a.e.

Name:

Address:

Post to: 'The Bazaar,' 34/36 High Street, Saffron Walden, Essex.

When?

Between Thursday to Saturday 28th-30th June.

You'll be in very good company; some ten thousand enthusiasts - and over a hundred stands displaying all that you want to see.

You'll come?

Eyes down for the appropriate coupon.

ADMISSION FREE

(or 50p on the door).

I'd like to see 'The Bazaar' FREE. I enclose a large-ish s.a.e. and will receive by return a ticket and full information.

Name:

Address:

Post to: 'The Bazaar,' 34-36 High Street, Saffron Walden, Essex. If you'd rather just pay 50p, go to Wood Green Tube Station and take a bus (every 3 minutes) to Alexandra Palace. We're open 10 am-6 pm daily, Thursday to Saturday, 28th-30th June.

Our Symbol.
We think it tells you just what the Bazaar is all about.



Mike Stollov of Blackley, Manchester, has not deserted the column although active as G4HWB. Flu laid him low but he was able to drag his FRG-7 to the bedside and keep in touch with the bands on c.w. and s.s.b. Good finds on 15m c.w. were HH2T, HK0BKX, HM1DM and H44LW while on 10m s.s.b. FM7AY, HC1FM, KZ5AS and 6W8AAD were fairly rare ones. After some blush-making comments **R. Beswick** of "Hillhouse", Yatton-Keynell, Chippenham, Wilts, mentions that he has run through quite a few receivers and now has a Trio 9R59D and a Minimitter MR44, but is sadly in need of a circuit or manual for the latter. Any help direct please to him, all expenses paid of course.

We don't often get any RTTY news but here is **Dennis Sheppard** of Sheppey, Kent, with a long log of stations copied in this mode with Creed page printer, tape printer, tape reader and home-made terminal unit driven from a JR310 receiver. Any other RTTY enthusiasts are invited to write in with logs, etc.

Australian **J. Clark** arrived here with his equivalent to the "B" licence and wrote to the RSGB for info on clubs in the Reading area and on the licensing regulations in order to get a full licence while over here. He says: "The RSGB HQ was not particularly forthcoming about licensing exam procedures, nor even too certain about the active status of clubs in this area". Needless to say, he got a full reply from me in a couple of days!

DX Notes

Bill Rendell (Truro) has the solution to the S79MC mystery, straight from the horse's mouth! It is the Seychelles after all. Although Bill heard him some time ago, it was only in the middle of March that the QTH was given, seemingly. Bill has been up at sunrise to find the DX still rolling in on 80m such as C6AFR, CT2SH, HC1NJW, VP1KG plus three ZLs one of whom was mobile "out salmon fishing"! 40m revealed Bill's first GD logging, GD3KGC but little else. On 20m CT2YB on St Michael popped up, with D4CBS, J3ABN, M1D, VP2VBK and VP8SO on Signy Island, not to mention VK3MO reputed to have eight quads in a 4-over-4 arrangement!

The 10m band has been very good at times but several readers comment on weird and variable skip at times, which makes it all the more interesting! **P. Lucas** of Newport, Salop mentioned HH2LD, H44CF and S79MC on the band, all good catches in the early evening, on his AR88 and vertical. Looking at the c.w. end of bands can produce some unusual prefixes if one is interested in that direction. **Mike Stollov** found a CP5, EA8, HC2, HP1, OY9 on 20m and HH2, VS6 on 15m, plus KZ5, SV1, 6W8 and 8P6 on 10m. More c.w. logs would be very welcome.

As usual **Ian Marquis** sorted out the better ones at Leigh-on-Sea, Essex, on his FRG-7, 100ft wire and 28MHz dipole, such as M1C and ZB2CJ on 80m, VP2KF, XE1FU and YN1S on 40m, C6ANX and TR8AC on 15m with HC1FM and HL9KE on 10m, all s.s.b.

Club Activity

Let's start with the **Bury RS** which meets every Tuesday evening at Mosses Centre, Cecil Street, where visitors are more than welcome. June 12 sees G8SCA talking on the joys of medium-wave DXing (how did that get in?) and on July 10 there is a foxhunt for those keen on DFing. QRP-lovers may like to know that **Yeovil ARC's** transmitter G3CMH is reputed to have made the first

solid-state s.w. DX QSO in the UK in 1954, working 90 miles on 80m with 30mW input to a single transistor. The station is still active with QRP so pop along any Thursday evening to Building 101, Houndstone Camp, Yeovil and meet the gang, or write: **D. McLean G3NOF**, 9 Cedar Grove, Yeovil.

The second and fourth Thursdays of the month, see the **Edgware and District RS** (Middx), at the Watling Community Centre, 145 Orange Hill Road, Burnt Oak, Edgware. On June 14 a "Bring & Show" your favourite test gear, tools, etc., is a pleasant twist while on June 28 there is a junk sale. Contact: **D. Lisney G3MNO**, 119 Draycott Avenue, Kenton, Middx. Fridays is the day to find the **West Kent ARS** at the Adult Education Centre, Monson Road, Tunbridge Wells. On June 22 a Mr Constable will talk on the British Vintage Wireless Society and its work.

Trevor Tugwell G8KMV reports his retirement as Sec of the **Stevenage & District ARS** and I hope his replacement **Ted Godfrey** of 94 Common View, Letchworth, will be equally forthcoming with the club's news. June 14 is devoted to a DF hunt, with G4DDX talking about his Top Band DF receiver on June 21.

Don't forget the deadline for copy, the 15th of the month without fail.

Log Extracts

Ian Marquis:—80m M1C ZB2CJ 40m HC4JQ VP2KF, XE1FU YN1S 20m VP8ML VR3AH VS5XU 8Q7AH 15m C6ANX TR8AC VP9JA 10m HC1FM HL9KE

R. Bell:—20m OA8ODE 15m JY5ZM P29MF 10m CT2CP KZ5FF YB0ADW

P. Hawks:—20m VK7OH A9XBS CT4UU M1D VP9CP XT2AV

P. Charlesworth:—20m JY8AQ JY0OZ VP9BB 7X2LS 9V1TX

M. Stollov:—20m CP5NK EA8FO FY7BF HC2FN HP1XGL OY9J 15m HH2T H18MOG HM1DM H44LW KL7PJ VS6EN 10m FM7AY HC1FM KZ5AS VS6DT 8P6JQ (Bold are c.w.)

P. Lucas:—10m HH2LD HI8XEA H44CF S79MC VQ9JJ ZF2CL 9J2LL 9L1KB

W. Rendell:—80m C6AFR CT2SH EA8PP HC1NJW PJ2AAX VP1KG YS9RVE ZF1CL ZL3GS ZL4AP 40m EA8QY 20m D4CBS HP6JB J3ABN J6LFZ M1D VK7AE VP2VBK VP8ML VQ9JJ ZD7PL 15m CT2CP HC6FC J6LDE (St Lucia) S79MC VP5JFH VP8SB (Adelaide Is.) VQ9RL YB0WR ZB2DV

D. Sheppard:—All RTTY 20m A4XFW FP8DF 9G1JX 9J2KD 15m JA1ACB KC6CB LU1NH VE7DIA W7WHY YU3KAA 10m AG2M C5AAN FG7XT JA2JHR KZ5JA VK3KF ZS6AKO 3D6AD 5Z4PD

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:

AMATEUR BANDS Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

MEDIUM and SW BANDS Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG. Reports for both bands **must** be kept separate.

VHF BANDS Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

BROADCAST BANDS

MEDIUM WAVE DX

by Charles Molloy G8BUS

Are you going abroad for your holidays this year? Then why not take along a portable receiver? As well as providing entertainment, it will give you the opportunity to listen to the medium waves from a new location. I had this experience while on holiday in Bulgaria a few years ago where the medium-wave scene was totally unrecognisable. I could have been on another planet! I even tried to do some DXing but could not pick up either the BBC or Luxembourg on the medium waves, though a weak unidentified on 200kHz might have been Droitwich. It would have been very interesting with a decent receiver and a loop.

Holidays abroad these days generally mean Spain, a country which is very interesting from the radio standpoint. As well as having an official government network, there are several chains of privately-owned local radio stations spread across the country. In most locations there are at least three to be heard during the day-time, while after dark many more are just waiting to be picked up. The holidaymaker also has the opportunity to hear "difficult" outlets such as Radio Gibraltar on 1458kHz.

DXing Spain

No need to visit Spain to listen to Spanish radio. A lot of it can be heard from the UK, and it is quite an interesting area to explore at this time of the year. A loop should sort out much of the co-channel QRM, since the DX is coming from the south while much of the QRM is from the east. The easiest stations to pick up are the high-powered RNE outlets at the l.f. end of the band. Listen to 585, 639, 684, 729, 738, 774 and 885kHz for the call Radio Nacional España.

The real interest for the DXer is with the local radio stations which operate on a number of channels between 792kHz and 1602kHz. The best time to listen for them is between 2300 and 0100 GMT when European QRM slackens off and many Spanish locals themselves close down leaving the frequencies clear for other weaker stations to appear in their place. Try on 1026kHz, 1107, 1134, 1224, 1260, 1314, 1395, 1521, 1539, 1584 and 1602kHz.

Identification

Station identification includes the name of the town or city preceded by one of four titles depending on the particular network such as Radio Barcelona, Radio Popular Malaga, Radio Juventud Murcia, La Voz (pronounced Voth) de Granada. A callsign is allotted to each station which is generally used in the sign-off announcement but it can present a problem to the DXer unless he is familiar with the alphabet and numerals in Spanish. Four sets of three letters plus figures are in use depending on the network. For example, EFE14 is in Madrid, ECS5 in Granada, EFJ56 in Malaga and EAJ1 in Barcelona.

A list of Spanish frequency allocations extracted from the Boletín Oficial del Estado of the 13 November 1978 is available from Keith Hatcher, Duquesa de la Victoria 50bis, Logroño, Spain in return for 2 IRCs or 25 Pesetas in unused Spanish stamps. At the time of writing this is the most up-to-date list available, though it does include some stations not yet on the air.

Reception Reports to Spain

Spanish locals are usually good verifiers even to a report written in English, though a Spanish Report Form (obtainable from DX clubs) is better. A full list of callsigns and addresses is to be found in the *World Radio and TV Handbook* though the frequency information in the 1979 edition is quite out of date. No need to worry too much about the full address. A report sent to El Gerente, Radio Popular Malaga, Malaga, Spain will certainly find the station. El Gerente being the station manager. Always include return postage, either unused Spanish postage stamps which are obtainable from stamp shops or an International Reply Coupon (IRC). These are on sale in main post offices.

Region 2 Station Separation

According to a report in *DX Monitor*, the Daylight Broadcasters Association (USA) is asking the US government to press for 9kHz station separation plus a slight extension of the m.w. band, as an alternative to the current proposal to the WARC-1979, to extend the band to 1850kHz. The suggestion is that the band should start at 530kHz with stations spaced at 9kHz intervals up to 1610kHz, which would provide an additional 14 channels.

The DBA just cannot be serious! It would mean that the majority of stations in Region 2—North, Central and South America—would be on the old pre-Geneva channels, which incidentally are at the moment occupied by many broadcasters in the Middle East who have not (yet?) changed over. 1kHz heterodynes would be commonplace and a 1kHz audio notch filter would be an essential item in the m.w. DXer's shack. A more reasonable proposal would be to start at 540kHz and follow the Geneva frequencies right up to 1602kHz. This would give 12 additional channels and would not require approval by the WARC as the m.w. band would not have to be extended. It would only require approval by the countries in Region 2.

It is to be hoped that the DBA will not be successful. At present Region 2 is on 10kHz separation starting at 540kHz which is also a Geneva frequency. Coincidence between the two systems occurs at 90kHz intervals across the band but there are other parts where the separation between the two systems is as much as 4kHz and these are the "DX slots" that would disappear if the Geneva Plan becomes world-wide. Fortunately there is likely to be opposition within the USA to the DBA's proposals, as many stations would be put to considerable expense, not just in changing frequency but with modifications to directional aerials which are in widespread use in that country. None-the-less, m.w. DXers will await further developments with apprehension.

Loops in New Zealand

The Loop becomes Respectable is the title of a short, amusing article sent to me by its author Tony King, who is the *Mailbag* editor of Radio New Zealand. It seems that RNZ decided to restrict its racing coverage, which led to the experimental use of a DXer's loop to get better reception. Soon, a commercially produced "punter's loop"

appeared which was investigated by the NZ Consumers Council, who had to acknowledge its effectiveness. A competitor, the Space Raker soon turned up. This was a loop built into a briefcase for convenience of use and acceptability in domestic surroundings. Finally "the national TV network screened a programme on the loop, the a.t.u. and on erecting an outside aerial, all in the quest for better reception".

DXing does have a large following in New Zealand but I once knew a Kiwi who was a great leg puller, so you can take your choice. Either way, it is an interesting story.

Readers' Letters

Stephen Donnelly wonders how DXers identify foreign language broadcasts. His method is to look for key words (Voici=French). This is alright if you have a list of key words but an easier way is to listen for place names. Most countries carry local items in their news bulletins and if, for example, you hear Ankara mentioned several times then you may be listening to Turkey. Stephen has recently acquired a Trio 9R59D and he would like to hear from other users of this receiver. Replies direct to Stephen Donnelly, 25 Church St, Addlington, Lancs PR7 4EX.

From Pensilva in Cornwall comes another letter from reader **K. Lewis** who has modified the r.f. pre-amplifier intended for use with the *PW* "Dorchester" Tuner. He used it along with a long wire, a.t.u. and Realistic DX160 to pull in WINS on 1010kHz, Radio Margarita, Venezuela 1020, Radio Coro, Venezuela 1210 and Radio Paradise, St Kitts on 1265kHz, all heard between 0250 and 0330 during March. Listen in mid-summer during the hour before sunrise for this type of DX; results are sometimes very good.

DX Circle is the name of the weekly DX programme in English carried by Deutschlandfunk on 1269kHz each Tuesday at 1900 GMT. It is compiled and presented by DXer **Alan Thompson** and it has been running now for over 10 years, the session on the last Tuesday of the month being designed especially for newer members of the hobby.

It is nearly 10 years since I met Alan at the DX Convention he organised in his home town, Neath. It was attended by **Arthur Cushen** who was on a tour from New Zealand at the time, and this was the first gathering of Broadcast Band DXers to take place in this country so far as I know. Alan is the UK/Europe representative for the NASWA/FRENDX, Indian DX Clubs International and the Union of Asian DXers, which means that subscriptions to those bodies can be made through him. Alan can be contacted via the DX Circle, Deutschlandfunk, 5 Koln 51, Raderberggürtel 40, West Germany.

BROADCAST BANDS

SHORT-WAVE BROADCASTS

by **Charles Molloy G8BUS**

Questions asked by a number of readers recently have prompted me to produce the following few notes written in non-technical language which will, I hope, show how a receiver converts the incoming radio signals into the sounds heard from the loudspeaker or headphones. An understanding of what is happening should help the DXer to get the most out of the quite sophisticated gear that is under his control.

The Superhet Receiver

A block diagram of a superhet receiver suitable for broadcast reception is shown in Fig. 1. Facilities for s.s.b. and c.w. are not included, as these are not generally used for broadcast band DXing. Each square represents a particular job the receiver has to do. Starting at the left-hand side, radio signals are picked up by the aerial and applied to the aerial socket where they pass into the r.f. stage and out again to earth. The r.f. stage selects the wanted signal, amplifies it and applies it to the mixer where a further stage of frequency selection is encountered. The local oscillator is maintained at a frequency 465kHz higher than the incoming signal by the tuning control. The mixer, which is aptly named, mixes the two together and supplies a 465kHz difference frequency complete with modulation (programme) to the intermediate frequency (i.f.) stages. Here the signal is amplified and further selectivity is encountered.

The output from the i.f. stages is applied to the detector where the audio is extracted and applied to the audio amplifier. The output goes either to headphones or to a further amplifier which drives a loudspeaker. The output from the i.f. stages is also fed to the automatic gain control (a.g.c.) circuit, which adjusts the gain of the amplifiers in the r.f. and i.f. stages in sympathy with the strength of the signal.

That, very briefly, is the make-up of the superheterodyne receiver, to give it its full name. In this case the

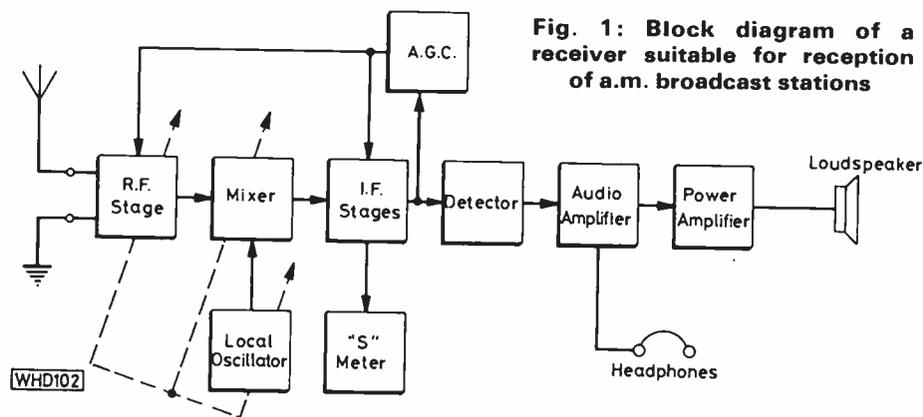


Fig. 1: Block diagram of a receiver suitable for reception of a.m. broadcast stations

heterodyne is 465kHz which is the standard value used in the UK. Anyone interested in the history and development of the superhet should try to get hold of a copy of *The Superhet Receiver* by Witts, first published in 1935. There are a number of later editions and although long out of print, copies can be found in secondhand bookshops. This book contains a fascinating account of the efforts of the early radio experimenters to produce a design that is now regarded as standard throughout the world.

Images

To get back to the block diagram. It is important that a receiver intended for DXing should have an r.f. stage. The majority of domestic receivers do not have one, the aerial going straight to the mixer. As well as increasing sensitivity, the r.f. stage helps to reduce what is known as second-channel or image interference. The mixer can produce the 465kHz heterodyne in two ways—by beating with a station 465kHz lower than itself, and also by beating with one 465kHz higher. The second is the image. For example, if the receiver is tuned to 6180kHz (49m band), the local oscillator will be generating 6645kHz and the image will be 7110kHz (41m band). The selectivity in the r.f. stage reduces the strength of the image compared with the wanted signal.

It is easy to tell if a receiver has an r.f. stage. Have a look inside at the tuning capacitor. It should be a three-gang, one section for the r.f., one for the mixer and one for the oscillator, all under the control of the main tuning knob. The dotted lines in Fig. 1 represent the 3-gang tuner. If it is only a twin-gang then there is no r.f. stage. Paradoxically, a receiver without an r.f. stage will sound a lot more lively than one with an r.f. stage. It picks up many more stations, in the example quoted, in the 49m band plus the stronger images in the 41m band. A receiver with poor image rejection will pick up the stronger stations at two points on the dial and this effect becomes worse the higher in frequency you go.

Automatic Gain Control

The a.g.c. does electrically what you can do for yourself manually—turn down the volume when listening to a strong station; turn it up to hear a weak one. The a.g.c. does it much faster and is therefore useful for dealing with fading. There are occasions, though, when you are better off without a.g.c. When two stations are operating on the same frequency, there will probably be a beat of a few hertz, equal to the slight difference between them. This can occur even if one station is a lot weaker than the other. The a.g.c. will follow the beat and may produce an unpleasant blasting effect at the loudspeaker. If you are searching for a weak station close to a strong one then the a.g.c. may respond to the strong station, reducing the receiver gain, so that the weak one is missed.

A.G.C. ON/OFF Switch

An a.g.c. on/off switch is fitted to communications receivers but seldom to other types. If you switch off the a.g.c. then you must be able to adjust the r.f. and i.f. gains, otherwise strong stations will cause overloading, therefore a separate r.f. gain control will have to be provided. In spite of the name, the r.f. gain control usually controls the gain of both r.f. and i.f. stages. To operate a receiver with the a.g.c. switched off; adjust the volume (a.f. gain) to a comfortable level and follow the strength of the incoming signal with the r.f. gain control, which replaces the a.g.c.

To sum up, a receiver for DXing should have an r.f. stage to provide adequate sensitivity and freedom from images. You can check by examining the tuning capacitor. It is also desirable to be able to switch off the a.g.c. but if you do this then you must have a manually operated r.f. gain control as a replacement.

Radio Finland QSLs

From Tullebody in Scotland comes a note from **James Thompson** who is a civilian instructor on radio with the ATC and a keen DXer. He sent a reception report to Radio Finland expecting to get a listener card in return, but much to his surprise he received a proper QSL giving the date, time, frequency and verifying that the report was correct. Whether this is the result of a genuine change of policy or the result of an error is not clear but let's hope it is the former.

Readers' Letters

The National Panasonic RF1105 is in the news again with a report from **E. Roper** who obtained his first experience of s.w. listening with this receiver and is more than satisfied with its performance. He finds that by increasing the diameter of the tuning control to 75mm, a more sensitive touch was obtained when tuning. Fitting a large knob to the tuning control is an old dodge, but it can spoil the appearance of the receiver. DX picked up with the RF1105 included Pakistan on the 16m band at 1100, Afghanistan on 19m at 1600 and Radio Australia on 25m at 1900.

"I am at present compiling a survey of the FRG-7 as there seem to be so many conflicting reports about these receivers," writes **George Tyler** from 41 Park Crescent, St George, Bristol BS5 7AY. George has already contacted about 20 FRG-7 owners and he would like to hear from more as he thinks some hints and guidelines could emerge from his survey. In particular he would like to know the good points, the faults and how the FRG-7 performs with an a.t.u., audio filter, etc. George has promised me a copy of the survey when complete and a summary of it will appear in this column. See also *Special Product Report this month. Ed.*

Arthur T. Cushen, MBE, writes from New Zealand to say that his book *The World in my Ears* will be published in August or September 1979. It is the story of a blind radio listener who has become a world authority in his hobby and who is a regular broadcaster on RNZ and Radio Nederland. The book, which is partly autobiographical and partly a guide to short-wave listening, can be obtained direct from Arthur Cushen, 212 Earn St, Enwood, Invercargill, New Zealand, at a pre-publication price of £7 until June 30.

DX Heard

Japan has been heard on 9585kHz at 2000, SIO 433 by **Chris Howles** (Lichfield) using his Vega 206 and 40ft loft aerial. **David Stevenson** (Thurso) has a National Panasonic receiver and a 100ft length of wire wound round his bedroom and he picked up Afghanistan on 11 805 at 1900 and Taiwan on 15 425 and 15 345 at 0100. **Bob Bell** (Blyth) reports hearing Radio RSA on 25 790kHz in the 11m band at 1520. According to a recent report in *Sweden Calling DXers*, IBA Jerusalem is now on 25 640kHz as well as on 25 645, Radio Nederland is on 25 650 at 0800 and the VOA is also on 25 880kHz.

A newly-acquired Sanyo RP 8880 is in use by newcomer to the s.w.s **Alan Curry** (Stockton-on-Tees) who

Aurora

The aurora borealis which followed the big solar storm on April 3 began around 2300 and ended during the early hours of the 4th. Alan Baker noticed that the 20m band was almost dead towards the late evening of the 3rd, and what weak stations there were had an auroral tone. He soon checked the 2m band, turned his beam just east of north and had an auroral contact with G8BHH, Wolverhampton, and heard GM4COK, GM4DSZ and GI4GID. John Cooper G8NGO, Cowfold, Sussex, using his 14-element beam, had 59A contacts with G4HSS, GM4DSZ, GM8EYB, and weaker contacts with G8LHT, Doncaster, and G8RHI. John also heard GM8NET and tried to contact GI4GID who was very strong in southern England, but the pile up to work him was too great.

During the event I heard G8ODN, GI4GID, GM4COK and GM8NET. Up in Scotland the aurora affected v.h.f. signals earlier in the evening and between 1700 and 2000 GMT John Branegan GM8OXQ, Saline, Fife, heard 5 Gs, 4 GIs, 7 GMs, 2 LAs, 1 PA0 and the 2m beacons in Germany DL0PR, Northern Ireland GB3GI, and Cornwall GB3CTC. Dermot Cronin EI9DC/G4GRO, who normally reports from the Royal Sovereign Light, heard, at his home in Killiney, tone-A signals from G, GI, GM and LA during the evening of March 29. John Branegan said it was "A very odd aurora", and between 1700 and 1830 he heard signals from EI, DL, LA, G, GI, GM, OZ, SM and the beacons from Cornwall and Germany. At 1746, John heard EI3S, OZ1OF, GM3UU and GI5AJ all calling at once and writes: "they all appeared at or near the same tuning point but they were clearly not hearing one another. However, the OZ called the EI and was answered by the GI so at

least he got a QSO eventually". Auroral signals, mainly confined to GM, were heard by John during the early evenings of March 22, 26 and 27 and, around 1115 on April 13, Alan Baker noticed that some 10m signals had an auroral tone.

European DX

While at the BBC on April 6, I met Rudolf Heim, Secretary General of the European DX Council, who was visiting Bush House to see a recording of *World Radio Club*. The EDXC has some 35 member organisations throughout the world, among whom are several international broadcasters acting as observers. Rudolf told me that only about 10 per cent of broadcast DXers are interested in v.h.f. and TV DX, but the number is growing. The Dutch are well ahead in this field however, and have some remarkable aerial systems. Some German clubs are moving in this direction and the German DX Federation, AGDX, frequently publish their own v.h.f and TV DX Bulletin. The use of Citizens' Band in Germany is popular among people of all age groups.

Radio Astronomy


John Smith is experimenting with a receiver to record the bursts of radio noise which come from Jupiter between 20 and 30MHz. So far he has built a pair of 4 half-wave dipoles on a 300 metre baseline, the signals being fed to an FRG-7 followed by a d.c. amplifier to drive a pen recorder. John is also working on a microprocessor, based on the SC/MP chip, to drive his 30ft dish which he intends to use for astronomical observations at 1420MHz.

Satellites

As a result of John Branegan's article about 70cm propagation from satellites, published in the quarterly journal of AMSAT-USA, he has been busy answering letters, one of which came from JR1SWB, editor of the Japanese *OSCAR NEWS*. John is pleased to do this and play his part in the international co-operation of the OSCAR project. His talk on satellites to the Mid-Lankark ARS was well received. Recently, John's first QSL card arrived from OK3CDI for a contact through the Russian satellite, RS-1 and another card from W4AXR, Florida, confirming his best DX to date, 4300 miles, via OSCAR 7B. So far, John has had nearly 50 satellite QSOs with W2BXA who was the first amateur to work 100 countries via satellite and the one who helped John through his first transatlantic QSO via OSCAR.

Tropospheric

The predominantly poor weather conditions and the low atmospheric pressure between March 19 and April 12 gave little help to the v.h.f. enthusiast, in fact at midnight on March 27 it was 29.1in and only just reached 30.1in for a few hours on the 23rd, when a brief improvement in conditions took place. Suddenly, on Good Friday, April 13, the weather turned warmer, the pressure began to rise and by midday on Easter Sunday it was 30.2in and rising. At 2200 on March 23, Alan Baker heard DB5KGI and PA3ALK on 2m s.s.b. and at 2320, ON6CP on c.w. At 1931 on April 13, Alan had a difficult QSO with F3CF, Lille, and heard G3BDQ in nearby Hastings working a German station on 2m s.s.b. Later, Alan, from his home in east-Sussex, worked stations in Bedfordshire, Hampshire and Kent, via the London repeater GB3LO, R7. At 0853 on the 15th, I heard a QSO between GB2RN, HMS Belfast, London and G4EVI, Yeovil, Somerset, via the

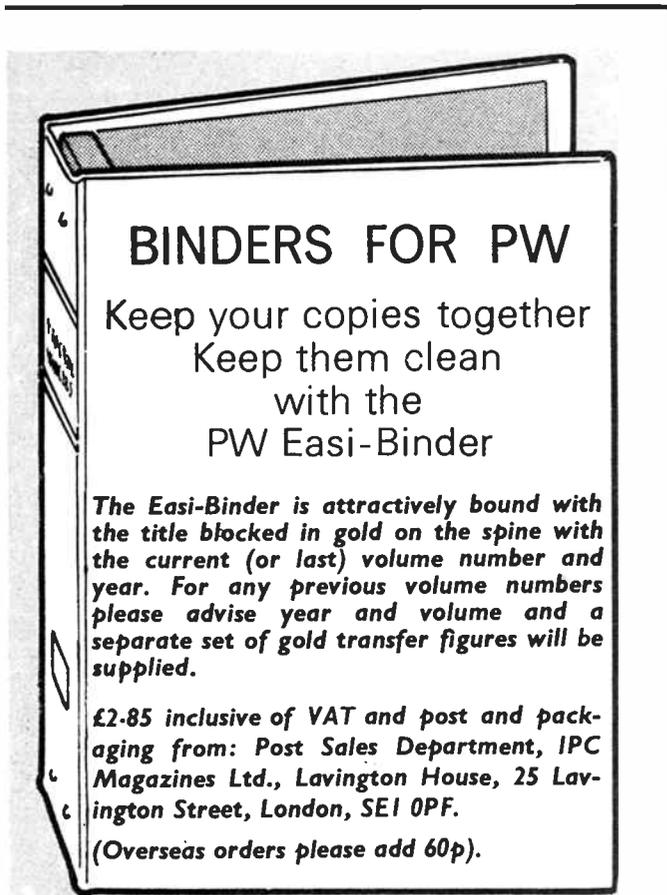

BINDERS FOR PW
Keep your copies together
Keep them clean
with the
PW Easi-Binder

The Easi-Binder is attractively bound with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers please advise year and volume and a separate set of gold transfer figures will be supplied.

£2.85 inclusive of VAT and post and packaging from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.
(Overseas orders please add 60p).

Hampshire repeater GB3SN, R5 and both stations were saying that they had not heard SN so strong for a long time.

Around 0730 on the 16th, I heard signals through GB3BC on R6, received a picture from Lichfield on Ch. 8, (189MHz) and noted some continental interference to the BBC stations in Band II. During the day **Barry Ainsworth G4GPW**, Sompting, Sussex and **Roy Bannister G4GPX**, in nearby Lancing, had a QSO via the French repeater FZ2THF on R9 and around 1530, G4GNX worked DJ0JW/A and DL0GO, who were both at their club station, DD8EE and using 4 × 21-element beams on 2m s.s.b.

DX Television

On April 1, **Andrew Coetzee**, one of my readers in Transvaal, SA received Ch.1 BBC TV, 45MHz on his KB receiver with a dipole aerial. Although the vision was only good enough to make out the figures, the sound was very strong. Congratulations are also due to Andrew, who has passed his amateur exams, and now has a restricted licence, callsign ZR6QP.


**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISEMENTS**

VHF PERSONALITY



JOHN TYE

by RON HAM

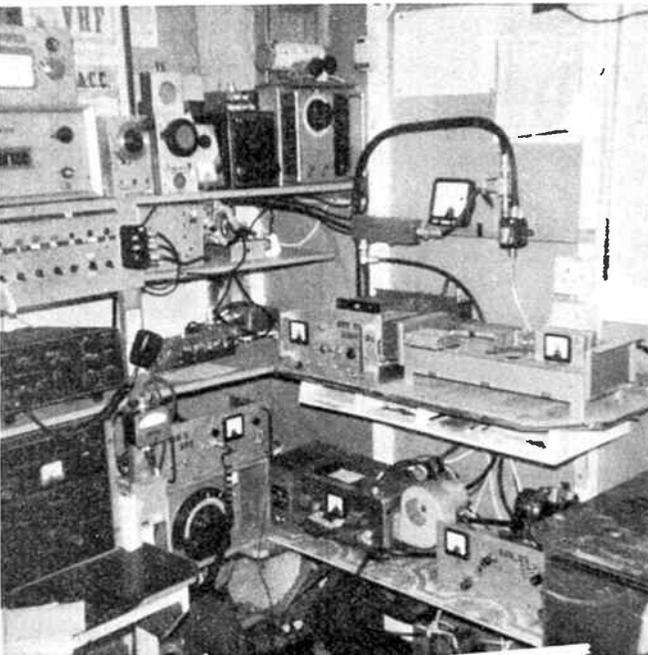

Part of John Tye's shack, on the right is home constructed equipment for 13 and 23cm

John Tye's interest in radio began around 1940 when, at the age of 14, he assisted with the servicing of broadcast receivers. His fascination for communications was fostered through listening to the short-wave bands on the government surplus receivers, R107 and R1155, which became available soon after the war. Later he joined the RSGB and, as BRS 27622, expanded his listening activities, with home-brew equipment, into the v.h.f. bands. John passed the RAE in May 1968 and, although he was soon active on 2m as G8BYV, his mind was set on building gear and experimenting on the centimetric bands. He passed the Morse test in 1973, and was then granted the callsign G4BYV.

John's signals have been heard in many European Countries on 70, 23 and 13cm from his home in Dereham, Norfolk and in September 1976 he earned the No. 1, Four Metres and Down, Microwave award from the RSGB for a contact of 883km on 1.3GHz with SK6AB. By the end of that year, he had achieved enough confirmed QSOs to qualify for the Society's 23cm award and the 70cm Senior award. One of John's overseas honours came in October 1973 when he received the Mirabel II certificate for sending a tape recording of Mirabel's 1296MHz beacon to F2LM. Mirabel II was a transponder with an up and down link on 144-432MHz, and a beacon on 23cm. It was launched from Nancy, France, by balloon and descended by parachute.

John's present aerial array, consisting of a 13-element Yagi for 70cm, an 8-element Yagi for 2m and separate 4ft dishes for 23cm and 9/13cm, is mounted on a tower which can be raised if required. For almost 30 years, John, a carpenter by trade, has been a reader of *Practical Wireless* and is supported in his amateur radio activities by his wife, Joan, who enjoys listening to the h.f. bands when driving their car. For the future, John plans to stay on the centimetric bands, use s.s.b. on 9cm and develop gear for 6cm.

RSC 100 WATT DISCO SYSTEM




Consisting of
 (1) TWIN T/TABLE CONSOLE with PRE-AMP. and POWER OUTPUT STAGES (2) & (3) PAIR 50 WATT LOUOSPEAKERS including 12" UNITS and H.F. HORNS Model T50H £49.99 ea.

SAVE £40
£199.95

- * DISCOMAJOR POWER DISCO CONSOLE Mk.II with integral Power Amplifier £149.98.
- * TWIN FULL SIZE turntables with cueing device.
- * CARTRIDGES with Diamond Styl.
- * 3 SEPARATE VOLUME CONTROLS for each turntable and Mic.
- * CONSOLE COMPLETE WITH L.I.D. FULL HEADPHONE MONITORING FACILITIES.

TERMS FOR SYSTEM
 Dep. £29.95 and 38 weekly payments £5.33 (Total £232.49)

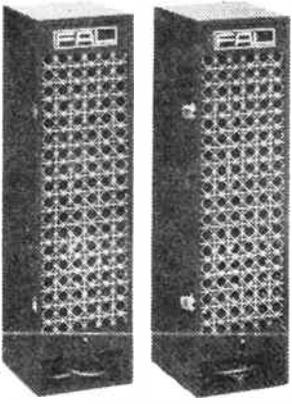DECOR LIGHT BOXES
 Standard Pair. List Price £58.32
 Total 6 lamps. Size 31" x 8 3/8" x 9" each half.



LIGHTING SYSTEM 'A'
 3 units complete with connecting leads
£89.95

or Deposit £9.95 and 38 weekly payments £2.48 Total £104.19 Carr. £3



AUTOMATIC RHYTHMLIGHT £39.95

3-channel sound-to-light converter. Features separate channels for multicolour sequence light actuated from the bass, middle and treble frequencies of your sound system. Operates from L.S. outlet of amplifier. 750 watts capacity per channel. Total cost of above units normally £98.27

DISCO MODULES Make your own console
CONTROL UNIT (mains powered)



Vol. (left) Vol. (Right) Tape input and volume control. Bass, Treble, ON/OFF switch for each Table. **£25.00** Carr. £1

MONITOR UNIT With H/Phone Socket and Vol. Control Carr. Free. **£7.95**

FADER UNIT Carr. Free **£7.95**

100w OUTPUT UNIT Mains powered Carr. £1.50 **£29.95**

TITAN GROUP/DISCO SPKRS

	Value	RSC Price
T12/45R 12" 45w	£18.00	£13.95
T12/60R 12" 60w	£22.50	£16.95
T12/100 12" 100w	£36.00	£25.95
T15/70 15" 70w	£28.00	£19.95
T15/100 15" 100w	£41.00	£29.95
T18/100 18" 100w	£51.00	£39.95

Carr. £1-20, under £18, over this add 6p per £1.

ALL RSC PRICES INCLUDE VAT



OPEN ALL DAY SATS (5 Day Week)
BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BIRMINGHAM 30/31 Great Western Arcade (Closed Wed.). Tel. 021-236 1279
CARLISLE 8 English Street (Closed Thurs.). Tel. 38744
COVENTRY 17 Shelton Sq. The Precinct (Closed Thurs.). Tel. 25983
DERBY 97 St. Peter's Street (Closed Wed.). Tel. 41361
DEWBURY 9/11 Kingsway (Closed Tues.). Tel. 468058
DONCASTER 3 Queensgate, Waterdale Centre (Closed Thurs.). Tel. 63069
EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
GLASGOW 403 Sauchiehall Street Tel. 041-332 0700
HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
LONDON 238 Edgware Road, W.2 (Closed Thurs.). Tel. 723 1629

- MAIL ORDERS & EXPORT ENQUIRIES TO—**
 AUDIO HOME, HENCONNER LANE, LEEOS. 13. Tel. 0532 577631.
 MAIL ORDERS MUST NOT BE SENT TO SHOPS
- ★ **LEEOS** 16-18 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 449609
 - ★ **LIVERPOOL** 35 Dawson Way, St. John's Precinct (Closed Wed.). Tel. 708 9380
 - MIDDLESBROUGH** 103 Linthorpe Rd. (Cl. Wed.) Tel. 247096
 - ★ **NEWCASTLE UPON TYNE** 59 Grainger St. (Closed Wed.). Tel. 21469
 - NOTTINGHAM** 19/19A Market Street (Closed Thurs.). Tel. 48068
 - SHEFFIELD** 13 Exchange Street (Castle Mkt. Blds.) (Closed Thurs.). Tel. 20716
 - ★ **WOLVERHAMPTON** 6 Wulfrun Way (Closed Thurs.). Tel. 26612
 - ★ **MUSICAL INSTRUMENTS & ACCESSORIES** in stock at these branches

TTLS BY TEXAS				LINEAR I.C.s				TRANSISTORS				DIODES			
7400 13p	7497 180p	74221 160p	74LS192 140p	74C157 250p	*A1-0212 600p	*MC1496 100p	2N3866 90p	DI001 12p							
7401 14p	74100 130p	74251 140p	74LS193 140p	74C160 155p	*AY1-1313 600p	*MC3340 120p	2N3903/6 20p	*OA47 9p							
7402 14p	74104 85p	74259 250p	74LS195 140p	74C181 155p	*AY1-5050 212p	*MC380 120p	*2N3956 20p	*OA81 15p							
7403 14p	74105 85p	74265 90p	74LS196 120p	74C182 155p	*AY5-12.2A.225p	*MFC4000B 120p	*2N4058/9 12p	*OA85 15p							
7404 17p	74107 34p	74278 140p	74LS240 175p	74C184 120p	*AYS-1315 600p	*MK50398 120p	*2N4060 12p	*OA90 9p							
7405 16p	74109 55p	74283 190p	74LS241 175p	74C173 120p	*AYS-1317 630p	NE531 130p	*2N4061/2 18p	*OA91 9p							
7406 32p	74110 55p	74284 400p	74LS242 175p	74C174 160p	*AY5-1320 320p	*NE540 200p	*2N4123/4 22p	*OA95 9p							
7407 32p	74111 70p	74285 400p	74LS243 175p	74C175 210p	*CA5019 80p	NE543K 225p	*2N4125/6 22p	*OA99 9p							
7408 19p	74116 200p	74290 150p	74LS245 175p	74C192 150p	*CA5046 70p	NE556 25p	*2N4202 10p	*OA99 9p							
7409 19p	74118 130p	74293 150p	74LS251 200p	74C193 150p	*CA5048 225p	NE556 70p	*2N4401/3 27p	*OA99 9p							
7410 15p	74119 210p	74294 200p	74LS252 120p	74C194 220p	*CA5082 75p	NE562B 425p	*2N4401/3 27p	*OA99 9p							
7411 24p	74120 110p	74298 200p	74LS259 175p	74C195 110p	*CA3089Z 225p	NE565 130p	*2N4427 90p	*OA99 9p							
7412 20p	74121 28p	74305 150p	74LS298 240p	74C221 175p	*CA3090A Q375p	NE566 155p	*2N4471 60p	*OA99 9p							
7413 36p	74122 48p	74366 150p	74LS373 200p	4880 SERIES	CA3130S 100p	NE567 175p	*2N4578 40p	*OA99 9p							
7414 60p	74123 55p	74367 150p	74LS374 195p	4000 15p	CA3140E 70p	NE567 175p	*2N4587 40p	*OA99 9p							
7416 27p	74125 55p	74368 150p	81LS96 160p	4001 17p	CA3160E 75p	RC4151 400p	*2N4587 40p	*OA99 9p							
7417 27p	74126 80p	74390 200p	81LS97 120p	4002 17p	FX209 75p	*N76003N 175p	*2N4587 40p	*OA99 9p							
7420 48p	74132 75p	74490 225p	81LS98 160p	4007 18p	ICL7106 825p	*SN76013N 140p	*2N4587 40p	*OA99 9p							
7422 22p	74136 75p	74 LS 8T28 230p	81LS98 160p	4008 80p	LM3011 30p	120p	*2N4587 40p	*OA99 9p							
7423 34p	74141 70p	74LS192 140p	81LS98 160p	4009 40p	LM3011 190p	140p	*2N4587 40p	*OA99 9p							
7425 30p	74142 200p	74LS00 18p	81LS98 160p	4010 50p	LM318 200p	200p	*2N4587 40p	*OA99 9p							
7426 48p	74145 90p	74LS02 18p	9310 216p	4011 17p	LM324 70p	70p	*2N4587 40p	*OA99 9p							
7427 34p	74147 190p	74LS02 18p	9310 216p	4012 17p	LM339 90p	90p	*2N4587 40p	*OA99 9p							
7428 38p	74148 150p	74LS08 22p	9311 275p	4013 50p	LM348 45p	45p	*2N4587 40p	*OA99 9p							
7430 17p	74150 190p	74LS10 22p	9312 160p	4014 84p	LM377 175p	175p	*2N4587 40p	*OA99 9p							
7432 36p	74151A 70p	74LS13 38p	9314 165p	4015 64p	LM380 75p	225p	*2N4587 40p	*OA99 9p							
7433 48p	74153 70p	74LS14 100p	9322 150p	4016 45p	LM381A 150p	150p	*2N4587 40p	*OA99 9p							
7437 35p	74154 190p	74LS20 22p	9368 200p	4017 80p	LM389N 140p	140p	*2N4587 40p	*OA99 9p							
7438 35p	74155 90p	74LS22 28p	9370 200p	4018 80p	LM709 30p	30p	*2N4587 40p	*OA99 9p							
7440 17p	74156 90p	74LS27 38p	9370 200p	4019 45p	*TCA940 175p	175p	*2N4587 40p	*OA99 9p							
7441 70p	74157 70p	74LS30 22p	9374 200p	4020 100p	LM710 50p	50p	*2N4587 40p	*OA99 9p							
7442A 60p	74159 190p	74LS47 90p	9601 190p	4021 100p	LM733 100p	100p	*2N4587 40p	*OA99 9p							
7443 112p	74160 100p	74LS55 30p	9603 60p	4022 100p	LM747 70p	70p	*2N4587 40p	*OA99 9p							
7444 112p	74161 100p	74LS73 50p	9602 175p	4023 22p	LM748 35p	35p	*2N4587 40p	*OA99 9p							
7445 100p	74162 100p	74LS74 40p	9602 175p	4024 22p	LM748 35p	35p	*2N4587 40p	*OA99 9p							
7446A 85p	74163 100p	74LS75 50p	9603 60p	4025 20p	LM3800 100p	100p	*2N4587 40p	*OA99 9p							
7447A 70p	74164 120p	74LS83 110p	MC1488 100p	4026 130p	LM3911 130p	130p	*2N4587 40p	*OA99 9p							
7448 80p	74165 130p	74LS85 100p	MC1489 100p	4027 50p	LM4136 120p	120p	*2N4587 40p	*OA99 9p							
7450 17p	74166 140p	74LS86 40p	75107 160p	4028 84p	*TBA810 90p	90p	*2N4587 40p	*OA99 9p							
7451 17p	74167 200p	74LS80 60p	75107 160p	4029 100p	*TBA820 90p	90p	*2N4587 40p	*OA99 9p							
7453 17p	74170 240p	74LS83 60p	75450 120p	4030 50p	MC1488 100p	100p	*2N4587 40p	*OA99 9p							
7454 17p	74172 720p	74LS107 45p	75451/2 72p	4031 20p	MC1495 400p	400p	*2N4587 40p	*OA99 9p							
7460 17p	74173 120p	74LS112 100p	75491/2 96p	4033 180p			*2N4587 40p	*OA99 9p							
7470 38p	74174 85p	74LS123 75p	C-MOS I.C.s 4034 200p	100p			*2N4587 40p	*OA99 9p							
7472 30p	74175 85p	74LS132 900p	74C00 25p	4035 100p			*2N4587 40p	*OA99 9p							
7473 34p	74176 90p	74LS133 60p	74C02 25p	4040 100p			*2N4587 40p	*OA99 9p							
7474 36p	74177 90p	74LS138 60p	74C03 30p	4048 80p			*2N4587 40p	*OA99 9p							
7475 36p	74178 90p	74LS139 60p	74C08 27p	4042 60p			*2N4587 40p	*OA99 9p							
7476 35p	74180 85p	74LS151 60p	74C10 27p	4043 90p			*2N4587 40p	*OA99 9p							
7480 50p	74181 200p	74LS153 60p	74C14 90p	4044 110p			*2N4587 40p	*OA99 9p							
7481 100p	74182 90p	74LS157 60p	74C20 27p	4046 110p			*2N4587 40p	*OA99 9p							
7482 64p	74184A 150p	74LS158 120p	74C30 27p	4047 100p			*2N4587 40p	*OA99 9p							
7485A 90p	74185 150p	74LS159 100p	74C32 30p	4048 55p			*2N4587 40p	*OA99 9p							
7486 100p	74195 95p	74LS174 110p	74C42 110p	4049 95p			*2N4587 40p	*OA99 9p							
7485 110p	74190 100p	74LS162 140p	74C48 250p	4050 49p			*2N4587 40p	*OA99 9p							
7486 34p	74191 100p	74LS163 100p	74C73 75p	4051 80p			*2N4587 40p	*OA99 9p							
7489 210p	84192 100p	74LS164 120p	74C74 70p	4052 80p			*2N4587 40p	*OA99 9p							
7490A 30p	74193 100p	74LS165 80p	74C85 200p	4053 60p			*2N4587 40p	*OA99 9p							
7491 80p	74194 100p	74LS173 110p	74C86 85p	4055 125p			*2N4587 40p	*OA99 9p							
7492A 40p	74195 95p	74LS174 110p	74C90 95p	4056 95p			*2N4587 40p	*OA99 9p							
7493A 33p	74196 95p	74LS175 110p	74C95 130p	4059 600p			*2N4587 40p	*OA99 9p							
7494 64p	74197 60p	74LS181 320p	74C107 125p	4060 115p			*2N4587 40p	*OA99 9p							

TRANSMITTER RECEIVER MK. 123 very compact Army unit for use in range 2.5 to 20 Mc/s receiver section 7 valves inc RF stage & BFO provides O/P for 4 K phones 3 bands with direct cal 2.5 to 5, 5 to 10 & 10 to 20Mc/s. Tx section 2.5 to 20Mc/s in 3 ranges O/P 15/25 watts over range C.W. Only as crystal osc & 5B254 P.A. will match into the following loads 25, 100, 500 & 1500 ohm as int tune up meter, reqs crystals type FT2543 in range 2.5 to 10 as int morser key with plug for ext key as int mains P.U. for 110/200/250v overhaul size 30x9x14cm weight 4kg also supplied with ext inverter unit for use on 12v DC. Supplied in clean condition with 80 page handbook inc circs etc. Price £54.

CABLE FAULT LOCATORS standard mains operated unit contains CRT type DG7-5 2½" 16 valves plus 2 Rect, slow motion dial, large number of misc parts in transit container £25.

CONTROL BOX aircraft radio sel box contains 4 min 1p c/o & 3 2p c/o miniature toggle swts, 2 small amp units etc £2.30 ea or 2 for £4.

AERIALS special purpose blade aerials precision made with BNC skat base, length 6½ or 10" from top of base £1.75 either type.

AERIAL dipole overhaul length 50½" with centre moulded fairing 2½" dia with BNC sk conn these contain int loading transformer were used on 20/50Mc/s or if this is removed can be used on nom 125Mc/s £2 ea or 2 for £3.50.

BLOWERS heavy duty single ended for use on 230/250v AC outlet 2½x3½" fix flange 5" sq req ext cond 2uf new boxed £10.80.

VARIAC UNITS for use on 180 v 500c/s dual gang rated 15 amps per section these can be used on 50c/s if the I/P voltage is limited to 50, these can be used to provide var O/P from L.V. trans or across 200/250v taps of H.D. trans to provide var O/P good cond with knob £13.

HELIPOT DIALS standard 10tr type to fit 3/8th bush approx 1½" dia £1.50 ea or 10 for £12.50 with 100K helipot £2.

SLOW MOTION DRIVES 9:1 with ¼" shaft with knob & skirt also 2.5 or 25K 360' pot ex new equip £2.30.

PANEL METER edgewise type FSD 100-0-100 Ua scale 100-0-100 size front 2½x5/8th 3½" deep new £2.75.

U.H.F. T.V. tuners manual tuned type transis with circ new £2.50.

PHOTO TRANSIS type FPT120 end viewing high sensitivity with data new 60 p ea 2 for £1.

PANEL METERS assorted types mostly ¾" dia types all moving coil new 4 different for £4.

TEST SET DEVIATION freq 65 to 75Mc/s with int crystal check at 70Mc/s, as 1 Ma meter, slow motion dial ass, atten etc no details thought to be part of Microwave Link test equip 200/250v I/P good cond £17.

DYNAMOTORS small American pattern I/P 24v DC o/p 250v at 60Ma suit command sets good cond £3.50.

RECTIFIER UNITS ex Army unit 200/250v I/P as dual DC O/Ps of 12v at 3 amps can be connected for 12v 6a or 24v 3a will do 4 amps okay for battery chargers in steel case good cond with circ £10.80.

AUDIBLE WARNING DEVICE 1½" dia will work on 6/12v DC solid state gives tone about 800c/s takes 100Ma at 12v new £1 ea 2 for £1.70 or 10 for £7.50.

FILM RECORDERS special aircraft 16mm film recorders for use on 24v DC with cassette good cond in transit container £16.

FANS extractor type fans for 230v 50c/s Adm Patt cont rated mounting flange 7x8" with front guard 7" deep. new boxed £7.50.

TEST SET contains meter 5-0-5 Ua scale linear 5-0-5 3" dia complete in neat carrying case size 10x8x7½" good cond meter tested £8.50.

DOME BELLS 11½" dia 6" deep chrome with red base American made these are spring powered with solenoid control were used for supply failure warning, will adapt to most control voltages will ring when supply removed, new some blemishes due to storage £25.

METER UNIT 0 to 40 amps DC with shunt 2" dia m.c. flush mt new £3.

MANUALS & CIRCUIT DIAGRAMS we can supply these for ex M.O.D. equipments, test gear etc.

Above prices include Carriage & VAT.
Goods ex equipment unless stated new.
S.A.E. for List 22 or enquiry.

A. H. SUPPLIES


122, HANDSWORTH RD. SHEFFIELD S9 4AE

Phone: 444278 (0742)

THE NEW EUROSOLDERSUCKER

This 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £6.80 inc. VAT & P.P.

THE UNIQUE EUROBREADBOARD

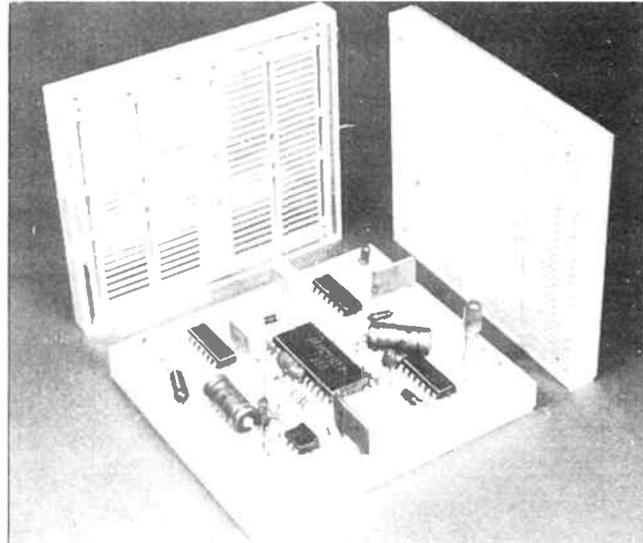

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

All connection rows and columns are now numbered or lettered enabling exact location indexing.

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £5.80 each or £11.00 for 2 - inclusive of VAT and P P

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF



David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

PW779

Please send me 1 EuroSolderSucker @ £6.80 Please
or 1 EuroBreadBoard @ £5.80 Tick
or 2 EuroBreadBoards @ £11.00

(All prices include VAT and P.P., but add 15% for overseas orders).

Name

Company

Address

.....

.....

Tel. No

Please make cheque/P.O.'s payable to David George Sales

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

— WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS —

STEREO PRE-AMPLIFIERS



MC 1

CPR 1

CPR 1—THE ADVANCED PRE-AMPLIFIER

The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably in the disc stage. The overload margin is a superb 40dB, this together with the high slew rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV; distortion < .005% at 30dB overload 20kHz. Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 85dB; slew-rate 3V/μs; T.H.D. 20Hz—20kHz < .008% at any level. F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138 × 80 × 20mm. Supply to be ± 15 volts.

MC 1—PRE-AMPLIFIER

Suitable for nearly all moving-coil cartridges. Send for details.

X02 : X03 — ACTIVE CROSSOVERS

X02 — two way, X03 — three way. Slope 24dB/octave. Crossover points set to order within 10%.

REG 1—POWER SUPPLY

The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS

It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification: T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/μs; signal to noise ratio 110dB; frequency response 10Hz-35kHz. —3dB; stability unconditional; protection—drives any load safely; sensitivity 775mV (250mV or 100mV on request); size 120 × 80 × 25mm.

POWER SUPPLIES

We produce suitable power supplies which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

POWER AMPLIFIER KIT

The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up service enables a novice to build it with confidence in a few hours.



ACTIVE CROSSOVERS

X02 £14-83 X03 £23-06

POWER AMPLIFIER MODULES

CE 608 60W/8 ohms 35-0-35v £18 30

CE 1004 100W/4 ohms 35-0-35v £10 22

CE 1008 100W/8 ohms 45-0-45v £23 22

CE 1704 170W/4 ohms 45-0-45v £20 12

CE 1708 170W/8 ohms 60-0-60v £31 90

TOROIDAL POWER SUPPLIES

CPS1 for 2 CE 608 or 1 X CE 1004 £14 47

CPS2 for 2 CE 1004 or 214 CE 608 £16 82

CPS3 for 2 CE 1008 or 1704 CE 1704 £17 66

CPS4 for 1 CE 1008 £15 31

CPS5 for 1 CE 1708 £22 88

CPS6 for 2 CE 1704 or 2 CE 1708 £23 88

HEATSINKS

Light duty, 50mm, 2°C/W £1 30

Medium power, 100mm, 1 4°C/W £2 20

Disc group, 150mm, 1 1°C/W £2 85

Fan, 80mm, static 120 or 240v £18 50

Fan mounted on two drilled 100mm heatsinks, 2 × 4°C/W, 65°C max. with two 170W modules, £29 16

THERMAL CUT-OUT, 70°C £1 38

POWER AMP KIT

£32 46

PRE-AMPS:

These are available in two versions—one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPRI £29 48

CPRIIS £39 98

MC1 £18 50

MCIS £29 49

POWER SUPPLY

REG1 £8 75

TR6 £1 75

BRIDGE DRIVER, BDI

Obtain up to 340W using 2 × 170W amps and this module BDI £5 48

CRIMSON ELEKTRIK

1A STAMFORD STREET, LEICESTER, LE1 6NL

Tel: (0533) 537722

U.K.—please allow up to 21 days for delivery.

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information.

Distributor:—

"MINIC TELEPRODUKTER

BOX 12035, S-750 12

UPPSALA 12, SWEDEN"

ELECTROVALUE

Your leading direct suppliers for



NASCOM MICROCOMPUTERS AND FULL SUPPORTING RANGE OF ITEMS TO ENABLE YOU TO WORK AT PROPER PROFESSIONAL LEVELS

- ★ At newest reduced prices.
- ★ Widest possible range stocked
- ★ Information on request
- ★ Enquiries from trade, industrial and educational users invited

Appointed distributors for the fine products of:

SIEMENS, ISKRA, RADIOHM, VERO AND MANY OTHER FAMOUS MANUFACTURERS

It's a good deal better from

ELECTROVALUE LTD

Dept. PW7, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.

Phone: Egham 3603. Telex 264475.

Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

- We pay postage

in U.K. on orders list value £5 or over. If under add 27p handling charge

- We give discounts

on C.W.O. orders except items marked Net or N in our catalogues

5% on orders, list value £10 or more

10% on orders list value £25 or more.

Not on Access or Barclay orders

- We stabilise prices.

by keeping to our printed price lists which appear but three or four times a year.


- We guarantee

all products brand new clean and to maker's spec. No seconds, no surplus.

- WE WILL SEND YOU OUR 120-PAGE CATALOGUE No. 9 FREE ON REQUEST.

Comprehensive informative very well produced. Write phone or call for your free copy together with latest price list.

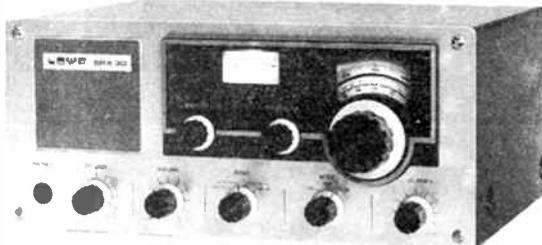OPEN UP THE EXCITING WORLD OF SHORT WAVE LISTENING



SRX-30

For the advanced, keen short wave listener, the choice of receiver has usually been between cheap and nasty, or very good but very expensive equipment. We think that the SRX-30 will provide that listener with excellent performance at a reasonable cost and is the answer to this eternal problem. The SRX-30 is based on an advanced drift cancelling loop system which gives spot on dial accuracy at any frequency between 500 KHz and 30 MHz together with easy to understand frequency readout. Suitable for all users from raw beginners, thanks to its simplicity of operation; to experienced listeners and amateur operators thanks to its advanced technology, the SRX-30 is the best communications receiver available in its price range today.

Completely self contained, including operation from mains or 12 volts dc, the SRX-30 is at home on broadcast or amateur bands. All mode reception of AM, CW, USB, and LSB is provided and receiver selectivity is automatically switched to give optimum performance on any mode. Send for full details today or give us a ring and we'll tell you all about the SRX-30. Price £175 inc. vat. Carnage by Securicor £3.

NEW CL22.

NEW CL22 aerial tuner which will match almost any receiver to almost any aerial at any frequency between 1.5 and 30 MHz. Six switched ranges with fully tunable receiver and aerial matching capacitors. A worthwhile addition to any SWL station and an instant improvement in aerial matching problems. Price £16.41 inc. V.A.T., post and packing.

CHASSIS PUNCHES

A set of first class chassis punches in a fitted plastic case which also includes a most useful tapered reamer—and believe me, if you've never used a reamer, you are in for a pleasant surprise when you find how easy it is to make beautifully round holes of almost any size. There are five punches having diameters of 1.6, 1.8, 2.0, 2.8 and 3.0mm. Price £8.77 including V.A.T., post and packing.

Honest Counter:

FC-5M. I don't know where the name came from, since you can hardly have a dishonest frequency counter, but this really is an outstanding Amateur accessory.

It is a five digit frequency counter requiring 12V or 5V DC for power and reading up to 50 MHz. Additionally, the FC-5M has a minus 455 kHz offset which allows you to hang it on to the oscillator of your 9R59 (or whatever) receiver, and to have digital readout. (N.B. full details supplied free with each counter). Price £39.16, including V.A.T., post and packing.

For all that's good in Amateur Radio, contact: LOWE ELECTRONICS LTD., 119 Cavendish Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817. For full catalogue, simply send 45p in stamps and request catalogue CPW.

P.W. JUMBO CLOCK

Kits of parts by the designers of the clock.

Kit A.

Comprising of printed circuit board. **Price £8.96.** V.A.T. and postage included.

Kit B.

Comprising of printed circuit board, case, perspex panel, pillars, transformer and l.e.d.s. **Price £22.72.** V.A.T. and postage included.

Kit C.

Comprising of full kit, excluding mains cable and wire. **Price £29.00.** V.A.T. and postage included.

Two colours of cases are available:- Gloss White & Simulated Black Leather Grain.

Please state colour with order e.g. Kit C/Black.

Full range of R.S. components available (48 hours service)

If you are experiencing difficulty in obtaining certain components for projects please do not hesitate to telephone us.

I.C.'s LM3900 & MC3302

£1.13 per pair Postage and package 20 pence.

V mos transistors. VN66AF

£1.30 each Postage and package 20 pence.

P.C.B'S FOR

PRACTICAL WIRELESS PROJECTS

Nov. 78.	Sarum Q Meter	R030	Price £3.30 & 20 pence p & p.
Nov. 78.	S.T.D. Charge Timer	AD212	Price £2.80 & 20 pence p & p.
Nov. 78.	Porch Light Timer	AD222	Price £0.60 & 12 pence p & p.
Nov. 78.	Battery Indicator	AD225	Price £0.60 & 12 pence p & p.
Dec. 78.	Car Radio L.W. Converter	R034	Price £2.35 & 15 pence p & p.
Dec. 78.	Digital Door Chimes	R017	Price £3.78 & 25 pence p & p.
Dec. 78.	Car Radio L.W. Converter	R032	Price £2.62 & 20 pence p & p.
Jan. 79.	Acoustic Delay Line	R018	Price £3.53 & 20 pence p & p.
Jan. 79.	Dorchester	R033	Price £10.80 & 30 pence p & p.
Jan. 79.	Sandbank Met. Det.	R035	Price £3.19 & 20 pence p & p.
Feb. 79.	Hythe Receiver	WR037	Price £5.94 & 20 pence p & p.
March 79.	Hythe Receiver	WR038	Price £2.70 & 20 pence p & p.
March 79.	Soudlite Converter	WK001	Price £5.98 & 20 pence p & p.
March 79.	Tone Burst Generator	R023	Price £1.60 & 15 pence p & p.
March 79.	Wide Band Noise Source	WR036	Price £0.70 & 12 pence p & p.
April 79.	PW 'Winton'	WR039	Price £15.42 & 30 pence p & p.
April 79.	FM Multitester	WR040	Price £2.70 & 15 pence p & p.
May 79.	Car Test Probe	WR042	Price £0.90 & 15 pence p & p.
May 79.	Follow up to PW Gillingham	WR044	Price £1.36 & 15 pence p & p.
May 79.	PW Imp	WR043	Price £1.42 & 15 pence p & p.
May 79.	Inline Crystal Calibrator	WR041	Price £1.58 & 15 pence p & p.
June 79.	Jumbo Clock		Price £8.66 & 30 pence p & p.
June 79.	Logical D's+X's	WR046/ 7/8/9	Price £12.00 & 30 pence p & p.
June 79.	Trent	WR050	Price £3.80 & 20 pence p & p.

All prices include V.A.T.

Send orders to:

C. BOWES & CO. LTD.,

4, WOOD STREET,

CHEADLE,

CHESHIRE SK8 1AQ.

Tel. 061-428-4497.


Please state type number and enclose cheque or postal order.

ASTRA-PAK

92 GODSTONE ROAD
WHYTELEAF SURREY CR3 0EB

All prices include V.A.T. Add 25p for P&P (Extra for overseas). Discounts over £10 less 5%, over £20 less 10%, over £50 less 15%, over £100 less 20%. Send SAE for complete list of components.

7400	74N74LSN	7484	0.80	74183	0.80	0.82	74366	0.52	20 pin	0.27
7401	0.12	7485	0.80	74184	0.80	1.20	74388	0.58	22 pin	0.28
7402	0.12	74N74LSN		74185	0.80		74390	1.92	24 pin	0.30
7403	0.12	7486	0.26	74186	0.80		74393	2.00	28 pin	0.44
7404	0.12	7487	1.50	74187	0.80		73670	2.30	40 pin	0.55
7405	0.13	7488	2.00	74188	0.80		LINEARS			
7406	0.20	7489	0.35	74189	0.80	2.10	CA3045	-14	0.46	
7407	0.20	7490	0.85	74190	1.00	1.94	CA3046	-14	0.70	
7408	0.14	7491	0.44	74191	0.80	0.90	LM3800	-14	0.82	
7409	0.14	7492	0.40	74192	0.80	1.12	LM3811	-14	1.20	
7409	0.14	7493	0.40	74193	1.18	1.12	LM710N	-14	0.32	
7409	0.14	7494	0.80	74194	0.80	1.12	LM711N	-14	0.32	
7409	0.14	7495	0.54	74195	0.80	1.12	MC1310P	-14	1.50	
7410	0.13	7496	0.80	74196	0.80		NE555N	-8	0.30	
7411	0.18	7497	2.00	74197	0.80		NE556N	-14	0.65	
7412	0.21	7498	0.94	74198	0.80		NE2501B	-14	2.00	
7413	0.25	7499	0.40	74199	1.10		SN72702N	0.50		
7414	0.54	7500	0.40	74200	0.80		SN75110N	0.50		
7415	0.21	7501	0.20	74201	0.80		SN76033N	1.85		
7416	0.27	7502	0.40	74202	0.80	3.38	SN76033N	1.85		
7417	0.27	7503	0.40	74203	0.80		SN76033N	1.85		
7420	0.13	7504	0.70	74204	0.80		TA45508	0.36		
7421	0.20	7505	0.40	74205	0.80		TA8681B	1.40		
7422	0.17	7506	0.30	74206	0.80		TBA1205	0.84		
7423	0.25	7507	0.40	74207	0.80		TBA641A	1.88		
7425	0.20	7508	1.80	74208	0.80		TBA800	0.75		
7426	0.25	7509	0.82	74209	0.80	3.80	TBA810S	1.04		
7427	0.26	7510	1.25	74210	0.80		TCA270SD	2.00		
7428	0.34	7511	0.82	74211	0.80	0.98	TCA2020	3.20		
7430	0.13	7512	0.25	74212	0.80	1.15	ZN414	1.00		
7430	0.30	7513	0.40	74213	0.80	1.50	OP AMPS			
7432	0.24	7514	0.50	74214	0.80	2.00	CA3130	-T099	1.00	
7437	0.24	7515	1.25	74215	0.80	1.10	LM301A	-8	0.30	
7438	0.24	7516	0.40	74216	0.80	1.15	LM301A	-T099	0.48	
7440	0.13	7517	0.45	74217	0.80	1.15	LM348N	-14	1.00	
7441	0.52	7518	0.82	74218	0.80	1.15	LM709	-8	0.40	
7442	0.55	7519	0.82	74219	0.80	1.48	LM709	-14	0.42	
7443	0.90	7520	0.36	74220	0.80	1.48	LM709	-T099	0.50	
7444	0.80	7521	0.68	74221	1.50	1.05	LM741	-8	0.22	
7445	0.70	7522	0.55	74222	0.80	0.85	LM741	-14	0.20	
7446	0.70	7523	0.94	74223	0.80	0.85	LM741	-T099	0.45	
7447A	0.80	7524	0.82	74224	0.80	0.85	LM747	-14	0.70	
7448	0.80	7525	0.82	74225	1.00	0.85	LM3900N	0.50		
7449	0.94	7526	0.82	74226	0.80	1.15	MC1458P	-8	0.42	
7450	0.13	7527	0.58	74227	1.12	1.15	VOLTAIRE REG			
7451	0.13	7528	0.58	74228	0.80	0.28	LM300	-T099	1.00	
7453	0.13	7529	0.90	74229	0.80	3.25	LM390K	-T03	1.30	
7454	0.13	7530	1.20	74230	0.80	0.85	ua723	-14	0.40	
7455	0.28	7531	0.98	74231	1.15	1.00	7805	T0220	0.85	
7460	0.13	7532	0.80	74232	2.15	1.00	7812	T0220	0.85	
7470	0.26	7533	0.80	74233	1.25	0.55	7815	T0220	0.85	
7472	0.22	7534	0.80	74234	1.70	1.05	7815	T0220	0.85	
7473	0.28	7535	0.80	74235	0.85	0.85	7905	T0220	1.10	
7474	0.28	7536	1.00	74236	0.80	3.92	7912	T0220	1.10	
7357A	0.50	7537	0.80	74237	0.80	0.85	7915	T0220	1.10	
7475	0.30	7538	0.80	74238	1.35	1.00	OIL SOCKETS			
7476	0.28	7539	0.80	74239	1.92	1.40	14 pin	0.11		
7478	0.39	7540	0.82	74240	0.80	1.00	16 pin	0.11		
7480	0.45	7541	1.70	74241	0.80	1.05	18 pin	0.13		
7481	0.80	7542	0.80	74242	0.80	0.85	18 pin	0.23		
7482	0.75	7543	0.80	74243	0.80	0.85				
7483	0.72	7544	0.80	74244	0.80	0.46				

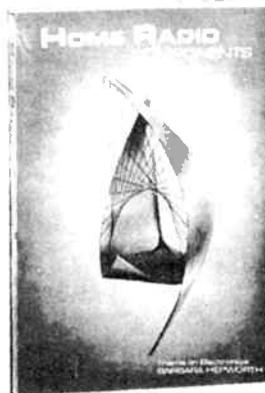

EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only £1.25 with a free bargain list. Send your cheque or postal order now.

HOME RADIO COMPONENTS LTD.
Dept. PW, 234 London Road
Mitcham, Surrey CR4 3HD



TOPS THE PACK!

- COMPONENTS** — Now over 1,000 types in stock!
- KITS** — See the new range of low-cost 'ELEKITS'.
- SERVICE QUALITY** — 1st Class same day despatch.
- PRICES** — All guaranteed products.
- MAGAZINE PROJECTS** — Many reductions!
- S.A.E. for list of PW projects** — Trouble-free!

I enclose 30p*, please send catalogue.

Name _____
Address _____

* Refundable with future orders over £5.00.

LOOK!

Here's how you master electronics.

.... the practical way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.


1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also for later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



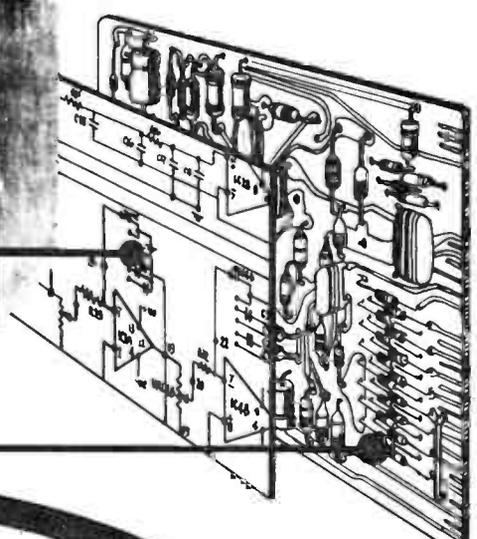2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

FREE

Post now, without obligation, to:-

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL


P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

WB779

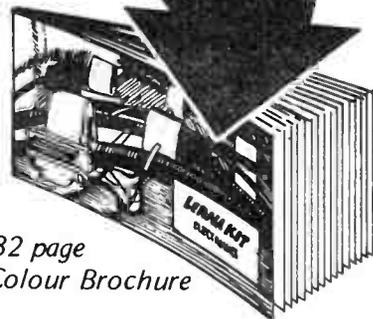

32 page
Colour Brochure



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

AM/CW/SSB COMMUNICATION RECEIVER and prescaler modules. 453 5 kHz Mech. Filter Modules 2 1 kHz BW, with diode-switching.

CRYSTALS Brand new high precision HC33/U: 1.0, 2.0, 3.0, 1.008, 2.5625 MHz £3-35, 1.28 MHz £4-15, HC13 100 kHz £3-25, HC18/U: 4.0, 5.0, 6.0, 7.0, 8.0, 10.0, 10.7 MHz £3-00, 18.0, 20.0, 38.6667, 48.0, 100.0, 116.0 MHz £3-50, HC25/U 8.08333 MHz (S20) £3-00. Large stocks of standard freqs for MPU etc. Any freq made to order 6 weeks from £3-75.

WINKLE PICKERS. Winkle out DX from the ORM with pin-sharp 250 Hz 8-pole crystal CW filters specially manufactured to fit TR10 and YAESU: FT/FR-101, FT-301, TS-520, TS-820, £28-90 each

All prices inc. VAT and UK post. SAE lists.
P. R. GOLLEDGE ELECTRONICS
 G3EDW, Merritt, Somerset, TA16 5NS
 Tel: 0480 73718

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
 0.47, 1.0, 2.2, 4.7, & 10 mfd. 5p.
 22, 47, 51p. (50V-6p.), 100-7p. (50V-8p.)
 220-8p. (50V-10p.), 470-11p. (50V-16p.)
 1000/15V-18p. 1000/25V-18p. 1000/40V-35p.

Subminiature bead tantalum electrolytics.
 0.1, 0.22, 0.47, 1.0, 4.7, 10, 35V, 4.7, 6.3V-5p.
 2.2/35V & 4.7/25V-10p. 10/25V, 15/16V-14p.
 22/16V, 33/10V, 47/6V, 68 & 100 4.7-16p.

Mullard Miniature Ceramic E12 Series 63V 2%.
 10 pf. to 47 pf.-3p. 56 pf. to 330 pf.-4p.
Vertical Mounting Ceramic Plate Caps 50V.
 E12 22 pf.-1000 pf. E6 1500 pf.-47000 pf.-2p.

Polystyrene E12 Series 63V. Hor. Mounting.
 10 pf. to 1000 pf.-3p. 1200 pf. to 10000 pf.-4p.

Mullard Polyester 250V Vert. Mtg. E6 Series.
 0.1 to 1 4p. 15, 22-5p. 33, 47-8p.
 68-11p. 1.0-14p. 1.5-20p. 2.2-24p.

Mylar (Polyester) Film 100V. Vertical Mtg.
 0.01, 0.02, 0.05-3 1/2p. 0.1, 0.2 4 1/2p. 0.4, 0.5-5 1/2p.

Miniature Film Resistors Highstab. E12 5%.
 0 125 watt 10 Ω to 2MΩ. 1p.
 0 250 watt 10 Ω to 10MΩ. (10% over 1M). 1p.
 0 500 watt 10 Ω to 2MΩ. 2p.
 1 000 watt 10 Ω to 10MΩ. 2p.

1N4148-2p, 1N4002-4p, 1N4006-6p, 1N4007-7p
 8C107/8/9, BC147/8/9, BC157/8/9, 8F194 & 7-9p.
 8 Pin Di. Ics 741's-18p. 555's-24p.

20mm. fuses 15, 25, 5, 1.0, 2.0, 3.0 & 5A-3p.
 20mm. fuseholders P.C. or Chassis Mtg.-6p.

Post 10p (Free over £4). Prices VAT inclusive.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

NOSTALGIA THE VINTAGE WIRELESS COMPANY COLLECTING 1920 to 1950

Receivers, valves, components, service data, historical research books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet.
THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 655472.

SMALL ADS

The prepaid rate for classified advertisements is 22 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

VALVES

Radio - T.V. - Industrial - Transmitting
 Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post. Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 30p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.
 Dept. P.W. The Parade, East Wittering,
 Sussex PO19 1SU
 West Wittering 2023 (STD Code 024366)

D.V.M. THERMOMETER KIT



Based on the ICL7106 single chip DVM the kit contains a 3 digit LCD, a PCB, ICL7106, and all components and instructions to make a 0-200mV FSD DVM. Components also supplied to enable this to be converted to a digital thermometer. Requires a 2mA 9V supply (PP3 battery). ONLY £21-99

TOUCH CONTROLLED LIGHTING KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touch plates. Easy to follow instructions.
NEW! TD300K-TOUCHDIMMER! Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. £8-99

—Extension kit for TD300K permits operation from another location, two-way switching, etc. £1-50

TS300K-TOUCHSWITCH-DIMMER—One alternate ON/OFF action. TOUCHPLATE. Small knob for presetting lamp brightness. £5-50

TS300K-ON/OFF TOUCHSWITCH. Two touch-plates £4-30

TSA300K-AUTOMATIC TOUCHSWITCH. Time delay variable 2 secs to 3 1/2 mins. £4-30

LD300K-300W LIGHTDIMMER KIT £2-90

* SPECIAL OFFER *
 10% discount on any 4 lighting control kits.

24 HR. CLOCK/APPLIANCE TIMER KIT



Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs and full instructions. £14-90

White box 56 x 131 x 71 mm with red Acrylic window. £2-20

White box as above ready drilled for kit Ready-built in box, incl. mains cable £22-50

400V PLASTIC TRIACS OPTO COMPONENTS

3A	49p	0.2" dia LEDs	555	24p (4 for 90p)
8A	62p	Red 12p (1/10)	741	22p (5 for 90p)
12A	70p	Green 17p	LM3911	
16A	80p	Yellow 17p	Temperature	
20A	165p	DL727	£1-50	control IC £1-00
25A	190p	LCD 0.5"	£8-10	ZN1034E £1-80
30A	210p	LDR sim	ICL7106	£7-50
40A	240p	ORP12	50p	TIC106D SCR 50p
* isolated tab	80p	Neon	8p	2N6027 34p
DIAC	18p			AY-5-1230 £4-50

QUANTITY DISCOUNTS ON REQUEST
 ADD 8% VAT + 25p P&P. Callers by appointment only.
 Tel: 01-579 9794
T. K. ELECTRONICS
 108 STUDLEY GRANGE ROAD, LONDON W7 2LX

TUNBRIDGE WELLS COMPONENTS, BALLARD'S,
 108 Camden Road, Tunbridge Wells, Tel: 31803. No Lists.
 Enquiries S.A.E.

Record Accessories

STYLI, Cartridges FOR MUSIC CENTRES, etc. FREE List No. 29 For S.A.E. includes Leads, Mikes, Phones etc. **FELSTEAD ELECTRONICS, (PW), Longley Lane, Gatley, Cheadle, Ches. SK8 4EE.**

Books and Publications

Build your own

P.A., GROUP & DISCO SPEAKERS

by R. F. C. Stephens
 Save money with this practical guide. Plans for 17 different designs, line source, l.b., Horn and Reflex types, for 8"-18" drive units. £3-95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER

by G. Holliman
 (full constructional details for versions using 15", 12" and 10" drive units.) £2-95 post free (\$6 overseas)

THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens
 This book is a must for the keen home constructor. Latest technology DIY designs. Plans for l.b., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2-20 post free (\$5 overseas).

VAN KAREN PUBLISHING

5 SWAN STREET, WILMSLOW, CHESHIRE

WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS. A genuine opportunity to success. **LARGE PROFITS.** You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. **NO PREVIOUS KNOWLEDGE IS REQUIRED,** as the manual covers in 13 chapters, where to obtain all the work you need, materials required, all instructions, rewind charts and how to take data etc. A gold mine of information. How to set up your home workshop and how to cost each job to your customer. £4-00 plus 30p P&P. CWO, to **INDUSTRIAL SUPPLIES, 102, Parrswood Rd., Wittingham, Manchester 20, Dept. PW.**

RADIO BOOK SERVICE

WORLD RADIO TV HANDBOOK 1979 Edition	£9-25
Radio Stations Guide.....	£1-55
Long distance Television Reception for the Enthusiast.....	£1-55
Popular Electronic Projects.....	£1-55
Electronic Projects for Beginners.....	£1-45
Mobile Discotheque Handbook.....	£1-45
Radio Circuits using ICs.....	£1-45
Projects in Opto-Electronics.....	£1-35
How to make Walkie-Talkies.....	£1-35
Radio Antenna 'n' book for Long Distance Reception.....	£0-95
How to build your own Metal & Treasure Locators.....	£1-10
How to build Advanced Short Wave Receivers.....	£1-30
Solid State Short Wave Receivers for Beginners.....	£1-05

PRICES INCLUDE POSTAGE & PACKING

4 CHILCHESTER COURT, WICKHAM RD, BECKENHAM KENT BR3 2JW

Aerials

AERIAL BOOSTERS

Improves weak VHF Radio and Television reception.
B45-UHF TV, B11-VHF Radio.
 For next to the set fitting.
Price £5. S.A.E. for Leaflets.

ELECTRONIC MAILORDER LTD,
 Ramsbottom, Bury, Lancs, BL0 9AG.

SHORT WAVE LISTENERS. Use the best aerial for the best results, the G2DYM Anti-T.V.I. Trap-Dipole, send 10" x 8" 16p S.A.E. & 3 x 9p stamps for lists, Aerials Guide, testimonials. G2DYM, Uplowman, Tiverton, Devon.

Ladders

LADDERS varnished 22" extd. £30. Carriage £2-80. Leaflet. Also Alloy ext. up to 62ft. **LADDER CENTRE (WLS3), Halesfield (1), Telford. Tel: 586644.**

Service Sheets

HUGE G.T. TV/RADIO/ETC. CATALOGUE (with £4 worth of useful vouchers)

Lists thousands of service sheets, manuals, etc. Many unobtainable elsewhere. Plus up dated Chassis Guide, newsletter, etc. Essential for every firm/engineer - Save ££s - only £1 plus large S.A.E. S.A.E. for details of our Giant Service Sheet Collections - not available elsewhere.

G.T. TECHNICAL INFORMATION SERVICES

76 Church St, Larkhall, Lanarkshire ML9 1HE

Largest stocks of manuals, etc. anywhere. £1 + large S.A.E. brings any requested full size single service sheet. Service sheets from 50p: S.A.E. for full details of this plus unique T.V. Publications. The new 1979 British Colour T.V. Repair Manual and the new First Foreign Colour T.V. Repair Manual for £4.90 each - both for £9.50.

S.A.E. brings full details of these and other unique publications.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc., £1.00 plus SAE Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 King's Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

SERVICE SHEETS, Radio, TV etc., 10,000 models. Catalogue 24p, plus S.A.E. with orders, enquiries. TELRAY, 154 Brook Street, Preston PR1 7HP.

Educational

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 1227 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 1227 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 1227 Intertext House, London SW8 4UJ
Tel. 01-622 911 (all hours)
State if under 18

WHETHER SEA-GOING OR SHORE-BASED, an exciting life awaits you as a Marine Radio Officer. Full details from the Principal, Barking College of Technology, Dagenham Road, Romford RM7 0XU. (Tel: Romford 66841).

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood, FY7 8JZ.

For Sale

NEW 10-18U Single Beam Oscilloscope. Price £60 o.n.o. with full instructions. Girish Patel, 77 Baggrave Street, Leicester.

NEW BACK ISSUES of "PRACTICAL WIRELESS" available 70p each, post free. Open P.O. Cheque returned if not in stock—BELL'S TELEVISION SERVICE, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

AS NEW K.W.202 Receiver, was £236. Going for £70. Enquiries after 6 p.m. Swanley 63605.

SEEN WHISTONS CAT? 5000 odds and ends. Mechanical/Electrical Cat Free. WHISTON, (Dept. PW), New Mills, Stockport.

LARGE SUPPLIER OF SERVICE SHEETS

and Colour Manuals, TV Mono Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E. except colour TV and Car Radios. State if Circuit will do, if sheets are not in stock. All TV Sheets are full lengths 24 x 12, not in Bits & Pieces. Free Fault Finding Chart or TV Catalogue with order. All crossed PO's returned if service sheets not in stock.

C. CARANNA (Mail Order)
71, Beaufort Park, London, NW11 6BX
01-458 4882

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc., with free fault-finding guide, from 50p and S.A.E. Catalogue 25p, and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

Overseas Appointments

PRODUCTION TECHNICIAN

required in South Africa.

Excellent opportunity for skilled wireman with test experience.

The position is permanent and offers good salary, good working conditions, warm climate, subsidised house mortgage.

Write giving details of age, experience etc. to:

Klerkscale (Pty) Ltd,
P.O. Box 944 Klerksdorp 2570,
South Africa.

Wanted

WANTED PRACTICAL WIRELESS February 1976, March 1976, April 1976, May 1976. Evenings Tel: 061-620-0145.

CIRCUIT DIAGRAM and detailed parts list to build a radio permanently tuned to 194 metres or 1546 kHz with pre-set volume and nine volt battery supply or have such a radio constructed in a wooden or sturdy plastic box to be inserted into a padded bag or details of how to replace a variable tuning capacitor with a pre-set one. **THE JOB IS FOR AN IN-PATIENT OF WARLINGHAM PARK HOSPITAL WHO IS SUFFERING FROM A TERMINAL DISEASE WHICH SEEMS LIKE A TWENTY-FOUR HOUR EPILEPTIC FIT AND MAY SUBJECT THE RADIO TO ROUGH TREATMENT INCLUDING DROPPING IT!** Offers please to:- **BM BEDSITTER, LONDON, WC1V 6XX.**

ELECTRONIC COMPONENTS PURCHASED. All Types Considered - Must be new. Send detailed list - Offer by return - **WALTONS, 55A Worcester Street, Wolverhampton.**

Miscellaneous

COMPLETE CAR ALARM KIT, 12 Volt positive or negative earth, only 4 leads to car. I.C. design incorporating C.M.O.S.; Battery sensing with Keyswitch and internal buzzer. Ready made £24.95, kit £21.95 (repair service available) Buzzer as used in car alarm, 85dBA α 3 metres, 10-15 Volts £4.95, also available large range of audible devices, cases, switches and p.c.b. manufacturing service. Send S.A.E. for details. All prices include V.A.T. and p&p in U.K. Make cheques/P.O.s payable to:- **C.D.S. ELECTRONICS, Dept. P.W., 2-4 Chichester Rents, Chancery Lane, London WC2 2EJ.**

EX MINISTRY AND SURPLUS EQUIPMENT

A neat 2 1/2" dia DC Moving coil indicator, F.S.D. 1mA resistance 60 ohms, scaled 0-500 and 0-125 no caption (ideal for transistor tester) supplied unused £3.30.
24V DC Motor 1 1/2" dia x 2" long - 1/2" long removable worm on a 1/2" dia shaft, a quality made motor supplied unused £2.80.
50K ohms Ten Turn potentiometer 1/2" dia, servo mounting with a 1/2" dia shaft, supplied unused £1.25.
Seven segment nine digit Gas Discharge Display 180 V/W, character height 27", supplied unused £1.20.
Elliott Transistor Curve Tracer type 8079, requires an oscilloscope with D/C X and Y Amps to operate £30.00.
All prices include postage. Lots of other items in stock S.A.E. for lists. Shop hours 9.30am to 2pm weekdays, closed Thursdays. Saturday 9.30am to 5.30pm.
A.E. SUPPLIES,
1 Arnolds Yard, Old Market Place, Altrincham, Cheshire.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI, Dept. No. 25, St. Wilfreds, Foundry Lane, Halton, Lancaster LA 6LT.**

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call, Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021 354 9764 or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E 4
Reg. Office 22 Coningsby Gdns

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

SILVER PLATED COPPER WIRE

14, 16, 18	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT
SAE brings list of copper & resistance Wires
Dealer Enquiries Invited

ALFAC etch resist transfers and other p.c. board drawing materials available from stock. SAE details. Ramar Constructor Services, Masons Road, Stratford-upon-Avon, CV37 9NF.

GUITAR/PA MUSIC AMPLIFIER

100 watt with superb treble/bass overdrive, 12 months guarantee Unbeatable at £42; 60 watt £37; 200 watt £58; 100 Watt twin channel sep. treble/bass per channel £55; 60 watt £48; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £92; slaves 100 watt treble/bass per channel £49; fuzz boxes: great sound, £8-50; bass £9-50; overdriver: fuzz with treble and bass boosters £14; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable. £89; twin channel £99; bass combo £99; speakers 15in 100 watt £35; 12in 100 watt £22-50; 60 watt £14-50. 10 watt 10in. £3.50, 8in £3.00.

Send Cheque or P O to.

WILLIAMSON AMPLIFICATION

62 Thorncliffe Ave., Dukinfield, Cheshire.
Tel 061-344 5007 or 061-308 2064

TIRRO's new mail order price list of electronic components now available on receipt of SAE. **TIRRO ELECTRONICS, Grenfell Place, Maidenhead, Berks.**

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for 'fast charge' HP7 (AA) £1-13, SUB C £1-47, HP 11 (C) £2-16, HP 2 (D) £3-27, PP3 £4-09, PP3 not suitable for fast charge, PP3 charger £5-81. All above Nickel Cadmium batteries are guaranteed 'EVER READY' full spec. and are supplied complete with solder tags (except PP3). Just in stock—New rechargeable sealed lead acid maintenance free batteries suitable for burglar alarms etc. 1.2 amp hr 6v £4-40 2.6 amp hr. 6v £5-85.

Quantity prices available on request. Date and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type). all prices include VAT Please add 10% P & P on orders under £10. 5% over £10.

Cheques, postal orders, mail order to: **SDIO STATE SECURITY DEPT PW 10, Bradshaw Lane, Parbold, Wigan, Lancs. 02575-4726.**

BELLS AND SIRENS
 CARTERS SIREN £5.95
 INDUSTRIAL SIX INCH BELL £8.95
 PRICES INCLUSIVE.
 SEND CHEQUE. P.O. to:
CWAS ALARM
 11 Danbrook Walk,
 Bradford BD4 0QS
 6 to 12v D.C. 12v D.C.
 SAE for full price list of Professional Burglar Alarm Equipment.

RARE DX UNDER QRM?
DIG IT OUT from tiring whistles and cw interference with a Tunable Audio Notch Filter, 350-5000Hz, 40dB notch, speaker amplifier, £8.90, MORE DX.
MISSING RARE DX? Get SPOT-ON with a Crystal Calibrator, 1MHz, 100.25KHz markers, £13.80.
SIG. GEN., 10Hz-200KHz, logic and variable sine or square wave outputs, £10.80, linear frequency scale.
PROGRAMME YOUR OWN tunes on a MUSICAL OORBELL, new tune each day, just needs bell transformer and speaker, £19.50, great fun.
Giro 21-923-4000. Each easy-assembly kit includes all parts, printed circuit, case, postage etc. money back assurance so SEND off NOW.
CAMBRIDGE KITS
 45 (PU) Old School Lane, Milton, Cambridge.

BULK PURCHASE. Battery intercoms to clear. 50ft. lead & volume control £6.95 pair. J. HARMSWORTH (PW2) 34 Victoria Street, Eccles, Maidstone, Kent.

KEEP ONE HANDY IN THE WORKSHOP



The unique aerosol treatment for minor burns and scalds. From Boots and other Chemists.

BUILD you own 771B type Metal Detector, details SAE 117 Horton Road, Brighton, BN1 7EG.

Mail Order Protection Scheme

The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of *Practical Wireless* for insertions

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME.....

ADDRESS.....


Send to: Classified Advertisement Manager
PRACTICAL WIRELESS,
 GMG, Classified Advertisement Dept., Rm. 2337,
 King's Reach Tower, Stamford Street,
 London SE1 9LS Telephone 01-261 5846

Rate
 22p per word, minimum 12 words. Box No. 60p extra.

Company registered in England Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

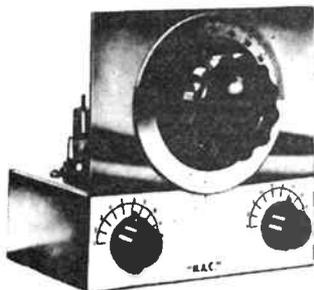

'H.A.C.' well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories to suit the novice and the expert.

£10.50 INCLUSIVE—the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

NEW TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £12.50 this receiver is outstanding value, and will give you hours of interest and entertainment.

Lastly the K and K plus (illustrated above) for the more advanced constructor. This receiver has recently been re-designed for even better reception. All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ

MORE SCOPE FOR YOUR MONEY



Model 3106C
5" CRT

£147.95

+11.84 VAT
+£2 carr. C.W.O.

SAE for further details

- DC to 10 MHz bandwidth.
- 10mV to 50V/cm in 12 calibrated steps.
- 0.5/S to 0.1 Sec/cm sweep range in 6 calibrated steps plus 12 1 Vernier.
- Magnifier x5.
- Fully automatic trigger.
- 2 MHz horizontal bandwidth.
- Fastest sweep 10 ins/cm with Magnifier.

Sensitivity < 1 cm deflection 10 Hz to > 15 MHz L.F. trigger extends below 5 Hz with 2 cm deflection. Trigger circuit will lock to the mean value of the displayed waveform. It will lock to almost any wave shape including sine, square, triangle, pulse and TV video signals. When no signal is present to repetition rate is below 5 Hz the trace free runs producing a bright base line. Company orders welcome by phone and Telex. Function Generator also available.

5 MHz 4 inch CRT Scope available £111. SAE for details.

TECHNICAL SPECIFICATIONS

Frequency range: 20 Hz to 200 MHz
Display resolution: up to 8 digits
Lowest frequency resolution: 0.1 Hz
Gate time: decade adjustable from 0.01 secs to 10 secs
Sampling rate: varies with gate time up to 5 per second
Display format: 8 LEDs, direct reading in kHz
Attenuator: 20 db
Input impedance: 1 M in parallel with 50 pF
Timebase accuracy: 0.3 ppm/°C, 10 ppm/year
Dimensions: 6.2 in x 3 in x 1.25 in
Weight: 6oz
Power requirement: 9V DC or AC adaptor
Sockets: standard 4 mm for resilient plugs
Standard accessories: test leads and prods, carrying wallet, owner's instruction manual
Optional equipment: AC adaptor for 240 V 50 Hz power; deluxe padded carrying case; connector kit comprising BNC, co-ax, DIN and phono adaptors, plus telescopic aerial for off-air transmitter measurements

METER £49. ADAPTOR £3.20
CASE £3.20. CONNECTOR KITS £10.58

KRAMER & CO.

9 October Place, Holders Hill Road, London NW4 1EJ.
Telex: 888941 attn. Kramer K7. Tel: 01-203 2437

Mail order only. Callers by appointment. Cash with order.

The world's smallest
LCD programmables can
be music to your ears

CASIO FX-501P and FX-502P

POCKET SIZED NON-VOLATILE PROGRAMMABLE CALCULATORS WITH MAGNETIC TAPE CASSETTE RECORDING ABILITY that convert to musical synthesizers!



- 1300 hours continuous use battery life
- Non-volatile memories and stores
- Conditional and unconditional jumps
- Up to 9 subroutines, up to 4 levels
- User defined keys
- Indirect on registers
- PAUSE key - Random Number key
- 51 scientific functions

World's first LCD pocket sized complete scientific programmables. Both use ALGEBRAIC operating system. The FX-501P offers up to 10 programmes and up to 128 non-volatile steps, with 11 non-volatile memories. The FX-502P has up to 10 programmes, up to 256 non-volatile steps and 22 non-volatile memories. Both have Automatic Power Off after approximately 14 minutes non-use. Dimensions of both are:—
9.6mm H x 71mm W x 141.2mm D (3/8" H x 2 3/4" W x 5 1/2" D)

Optional FA-1 Programme Adaptor available for either model - permits programmes to be recorded on standard tape cassette recorder and stored for re-entry later. Also contains a music switch which converts both calculators into musical synthesizers - keys 1 through 8 contain pre-programming for a full musical octave.

Model	RRP	Our Price
FX-501P	£59.95	£49.95
FX-502P	£79.95	£69.95
FA-1	£24.95	£19.95

★ THIS YEAR'S STAR BUY CASIO 46CS-27B CASIO 46CS-29B

(As available - slight case difference only)
Almost certainly the slimmest and most sophisticated ALARM CHRONOGRAPHS available today.

- LC Display of hours, minutes, seconds, day; And with day, date, month and year.
 - 12 hour, with am/pm, or 24 hr clock display. 24 hr alarm setting. Optional hourly chimes. Chrono measures from 1/100 second to 6 hours. Laps, 1st & 2nd place. Stainless steel case only 7.8 mm thick. Water resistant 100'. Mineral glass face.
- Backlight for night time x 10 seconds/month. Removable links in bracelet.
Was £74.95



NOW ONLY £39.95

Other CASIO multi-function watches from £19.95

UNBEATABLE QUALITY AND VALUE FOR MONEY FROM JAPAN - WHY SETTLE FOR LESS?

Most CASIO products available from stock. Send 25p for illustrated brochures of this superb range of high quality watches or calculators. (Both on request.)

Prices include VAT, P & P. Send cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:—

TIMETRON
Callers welcome by appointment

Dept. P.W., Beaumont
Suite, 164 167 East Road
Cambridge CB1 1DB
Telephone 0223 67503

PLEASE MENTION

PRACTICAL WIRELESS

WHEN

REPLYING TO ADVERTISEMENTS

BURGLAR ALARMS


WE HAVE STOCKS OF EVERYTHING YOU NEED.
CALLERS WELCOME. OPEN 6 DAYS
EXPRESS POSTAL SERVICE FREE CATALOGUE SEND S.A.E.

MAGIGUARD MK 4
ULTRASONIC DETECTOR

12V D.C. c/o relay output
Covers approx. 24 ft. Adjustable sensitivity

SPECIAL OFFER ONLY
£38.00

including VAT & Postage

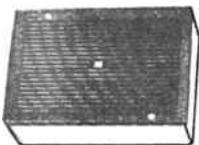

A. D. E. (SECURITY) CO.,

217 WARBRECK MOOR
AINTREE, LIVERPOOL
TEL: 051-525-3440

STOP PRESS! Trade Price List Available
Applications on Official Stationery only

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST TERMS BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 30p. ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. SEND 50p (plus 25p p&p) for our catalogue.

VAT Export orders on VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in μ F).
400V: 0.001 0.015, 0.022, 0.033, 0.047, 0.068, 0.01, 0.015 9p; 0.018 10p; 0.022 0.033 11p; 0.047 0.068 14p; 0.1 17p; 0.15 22 24p; 0.33 0.47 41p; 0.68 48p.
160V: 0.039 0.15 0.22 11p; 0.33 0.47 19p; 0.68 1.0 22p; 1.5 29p; 2.2 32p; 4.7 36p.
DUBILIER: 1000V: 0.01 0.015 20p; 0.022 22p; 0.047 26p; 0.1 38p; 0.47 53p; 1.0 175p.

POLYESTER RADIAL LEAD (Values in μ F): 250V:
0.01 0.015 0.22 0.027 5p; 0.033 0.047 0.068 0.17p; 0.15 10p; 0.22 0.33 13p; 0.47 17p; 0.68 19p; 1.0 22p; 1.5 30p; 2.2 34p

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in μ F).
500V: 10 40p; 47 63p; 250V: 100 65p; 63V: 0.47 1.0 1.5 2.2 2.5 3.3 4.7 6.8 8.0 10 15 22 27p; 33 50 15p; 63 100 27p; 60V: 1.0 0.7p; 50 100 220 25p; 470 32p; 1000 50p; 40V: 22 33p 8p; 100 12p; 2200 3300 68p; 4700 85p; 35 10 33 7p; 25p; 1000 27p; 1000 50p; 25V: 10 22 47 6p; 80 100 160 8p; 220 250 13p; 470 64p; 25p; 1000 27p; 1500 30p; 2200 45p; 3300 62p; 4700 88p; 15 10 40 47 68 7p; 100 125 8p; 220 330 14p; 470 16p; 1000 1500 20p; 2200 34p; 10V: 100 6p; 640 12p; 1000 14p.
TAG-END TYPE: 70V: 2000 89p; 4700 135p; 50V: 10 000 225p; 40V: 2500 65p; 3300 4700 70p; 15 000 299p; 25V: 4700 68p; 2200 45p; 40V: 2000 95p.

TANTALUM BEAD CAPACITORS:
35V: 0.1 μ F, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2 μ F; 3.3, 4.7, 6.8, 25V: 1.5, 10, 20V: 1.5 μ F; 13p each; 10V: 22 μ F; 33 20p; 6V: 22 μ F; 16p; 47, 68, 30p; 3V: 100 μ F; 16p each; 16V: 47 μ F; 35p; 100 μ F; 40p; 220 μ F; 46p.

MYLAR FILM CAPACITORS:
100V: 0.001, 0.002, 0.005, 0.01 μ F 6p
0.015, 0.02, 0.03, 0.04, 0.05, 0.05 μ F 7p
0.1 μ F, 0.2 μ F. 50V: 0.47 μ F 12p

CERAMIC CAPACITORS 50V
Range: 0.5pF to 10nF 3p
15nF, 22nF, 33nF, 47nF 4p 100nF 6p

POLYSTYRENE CAPACITORS:
10pF to 1nF, 8p. 1 5nF to 47nF 10p.

SILVER MICA (pF)
3.3 4.7 6.8 10 12 18, 22 27 33 47 50 56, 75 82 85 100 120 150 180 220 9p
250 300 330 360 390, 600 & 820pF 16p each
1000 2200pF 20p

JACKSONS VARIABLE CAPS.
Dial type
100/300pF 140p
500pF 165p
6.1 Ball Drive 115p
4511/DAF 115p
Dial Drive 4 103 325p
6.1/36.1 650p
Drum 54mm 30p
0.1-365pF 245p
0.02-365pF 275p
0.0-2.500pF 430p

TRIMMERS miniature
2 5pF-3 10pF 22p
3 30pF-3 50pF 22p
5 25pF-6 50pF 22p

CRYSTALS*
100kHz 385p
45kHz 385p
1MHz 323p
1.8MHz 323p
3.2768MHz 323p
4.032MHz 323p
4.433619MHz 325p
5.0MHz 355p
6.5536MHz 200p
8.08333MHz 275p
18MHz 395p
27.468MHz 350p

COMPRESSION
1 80MHz 323p
25-200pF 33p
100-500pF 45p

GAS & SMOKE DETECTORS
TGS812 or B13 415*

RF CHOKES 1 μ F 4.7, 10, 22, 47, 100, 220, 470, 750 Ω 2.5, 5, 10mH 35p, 35mH 4p, 100mH 60p.

TRANSFORMERS* (mains Prim. 220-240V)
6.0-6V 100mA; 9.0-9V 75mA; 12.0-12V 100mA
BVA type: 6V-5A 6V-5A; 9V-4A 9V-4A
12V-3A 12V-3A; 15V-2.5A 15V-2.5A
12VA: 4.5-1.3A 4.5V-1.3A; 6V-1.2A 6V-1.2A
12V-1.5A 12V-1.5A; 220p(20pp&p)
24V: 6V-1.5A 6V-1.5A; 9V-1.2A 9V-1.2A
12V-1A 12V-1A; 15A-8A 15A-8A
20V-6A 20V-6A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A; 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-800mA 30V-800mA
100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.2A 40V-1.2A
650p(50pp&p)

(N.B. P & P charge to be added above our normal postal charge.)

DENCO COILS
Dual Purpose OP ROT2 92p
VALVE TYPE RFC 5 chokes 91p
Ranges: 1-5 B1. YI. RFC 7(19mH) 96p
Rd. Wht. 86p
6-7 Y.R. 76p
1-5 Green 92p
T-type (Transistor Tuning) TOC1 104p
Ranges: 1-5 B1. YI. MW 5FR 82p
Rd. Wht. 93p MW/LW 5FR 103p

POTENTIOMETERS (AB or EG EN)
Carbon Track, 0.25W Log & 0.5W Linear values.
5000, 1K & 2K (LIN ONLY) Single 27p
5K 2M Ω single gang 40p
5K 2M Ω single gang D/P switch 75p
5K 2M Ω dual gang stereo 85p

SLIDER POTENTIOMETERS
0.25W log and linear values 60mm track
5K Ω -500K Ω single gang 70p
10K Ω -500K Ω Dual gang 80p
Self-Stick graduated Alum. Bezels 22p

PRESET POTENTIOMETERS
1 10V 0.02-2M Ω Mini. Horiz. larger 8p
0.25W 1000 3 3M Ω Horiz. larger 10p
0.25W 2500 4 7M Ω Vert. 10p

RESISTORS - Erie make 5% carbon
Miniature High Stability, Low Noise
Val. 1/2 - 99 100-
0.25W 220-4.7M E24 1.5p 1p
0.5W 2.2-4.7M E12 2p 1.5p
1W 2.2-10M E12 5p 4p
2.2 Metal Film 100-1M 6p 4p
1% 0.5W 50-10M E24 10p 8p

COMPUTER HARDWARE
2102 100p 4047 750p
2102-2 170p 74S188 855p
2102-2 170p 74S263 895p
2112-2N 210p 74S287 325p
2114 785p 74S470 325p
2513 650p 74S475 825p
2708 775p 81LS95 99p
2710S 995p 81LS95 99p
2710S 1650p 81LS95 125p
CP1610* 930p MC1488 85p
TMS6011 325p MC1489 90p
4027 325p 2802 5MHZ 050p

LINEAR IC'S
702* 75 LF365* 98
709C 8pin* 35 LM301A* 30
710* 67 LM307* 110
723* 14pin 45 LM311H* 120
741-B pin 18 LM318H* 205
747C 14pin* 78 LM324A* 295
748C 8pin* 36 LM339 70
753 3pin 150 LM348* 90
755 10pin 150 LM349* 90
AY-1-0212 580 LM379* 375
AY-1-1313A* 660 LM380 80
AY-1-1320 315 LM381N 145
AY-1-5050 190 LM381AN 248
AY-1-5051 145 LM382 125
AY-1-6721/6 195 LM733* 125
AY-3-1015 560 LM145B* 50
AY-3-8500* 390 LM3900* 60
AY-5-1013* 450 LM3909N* 70
AY-5-1224A* 280 LM3911* 125
AY-5-1230* 450 M252AA* 750
AY-5-1315 560 M253AA* 795
AY-5-1317A 630 MC1303 88
AY-5-3500* 510 MC1304P 260
AY-5-8100* 735 MC1310P 150
CA301A 137 MC1312P 195
CA301B* 67 MC1318* 90
CA302 170 MC1495* 350
CA3023 170 MC1496L* 350
CA302BA* 80 MC1710 79
CA3035 240 MC3340P 120
CA3036 110 MC3360P 120
CA3043* 150 MC3393* 635
CA3045* 140 MC3603* 135
CA3046* 71 MFC6040* 97
CA3048 210 MK50253* 650
CA3075 175 MK50362* 650
CA3080E* 70 MK50398* 635
CA3081* 190 MK50399* 635
CA3089E 210 MM5307* 1275
CA3090A 398 MM57160* 620
CA3123 200 MSM5526* 850
CA3130* 85 NE543K* 210
CA3140* 70 NE544L 180
ICL7106* 795* NE555* 22
ICL7107* 975 NE556B* 60
ICL7033C* 345 NE560* 325
ICM7205* 1150 NE561* 395
ICM7215* 1050 NE562A* 410
ICM7217A* 790 NE565* 425
ICM7555* 89 NE565A* 120

TRANSISTORS		P		P		P		P		P		P		P	
AC107*	28	BC177*	18	BF179*	30	MPSU02	58	TI547	50	2N2220A*	26				
AC117*	35	BC178*	16	BF180*	35	MPSU05	50	TI548	50	2N2222A*	23				
AC125*	25	BC179*	18	BF181*	35	MPSU06	50	TI549	50	2N2224A*	20				
AC126*	20	BC180*	20	BF182*	35	MPSU52	65	TI560	47	2N2226A*	25				
AC127*	20	BC181*	20	BF183*	35	MPSU55	53	TI567	50	2N2303	45				
AC128*	20	BC183	9	BF184*	38	MPSU56	60	TI562	52	2N2369A*	21				
AC141*	20	BC184	9	BF194	12	MPU131*	39	TI574	47	2N2483*	28				
AC141K*	24	BC182L	11	BF195	12	OC23*	170	TI580	50	2N2484*	25				
AC141K*	38	BC183L	10	BF196	14	OC26*	170	TI589A	00	2N2485*	25				
AC142*	24	BC184L	11	BF197	14	OC26*	170	TI591	24	2N2486*	25				
AC142K*	38	BC187*	21	BF198	18	OC28*	150	TI599	24	2N2487*	25				
AC176*	22	BC187*	21	BF199	18	OC29*	160	ZTX107	12	2N2490A*	22				
AC187*	22	BC212	10	BF200	32	OC35*	130	ZTX108	12	2N2905A*	22				
AC188*	22	BC212L	11	BF244A	18	OC36*	130	ZTX109	14	2N2906*	22				
AC17*	35	BC213	11	BF248	28	OC37*	148	ZTX130	28	2N2907*	22				
AC19	40	BC213L	12	BF248B	30	OC42*	48	ZTX1300	15	2N2926G	10				
AC19	40	BC213L	12	BF256*	30	OC43*	55	ZTX302	20	2N3011*	24				
AC20	40	BC214K	14	BF257*	30	OC44*	31	ZTX303	25	2N3053*	20				
AC21*	35	BC214L	13	BF258*	30	OC45*	28	ZTX304	24	2N3054*	55				
AC22*	40	BC307B	20	BF259*	30	OC46*	28	ZTX311	17	2N3055*	48				
AC28*	40	BC308	13	BF274	18	OC70*	28	ZTX314	24	2N3056*	40				
AC339	78	BC308B	13	BF336	35	OC71*	28	ZTX320	30	2N3442*	140				
AO149*	0	BC327	15	BF394	27	OC72*	45	ZTX326	30	2N3504	55				
AO161*	42	BC328	15	BF594	20	OC74*	55	ZTX341	20	2N3563	20				
AO162*	42	BC338	12	BF595	20	OC76*	36	ZTX500	15	2N3614*	139				
AF106*	50	BC441*	36	BF639	25	OC79*	76	ZTX502	19	2N3615*	168				
AF114*	40	BC461	36	BF640	25	OC81*	50	ZTX503	15	2N3663*	26				
AF116*	40	BC47*	27	BF641	28	OC82*	50	ZTX504	15	2N3702	11				
AF117*	40	BC48	12	BF642	28	OC83*	48	ZTX505	25	2N3703	11				
AF118*	65	BC549C	13	BF643	28	OC84*	44	ZTX521	25	2N3704	11				
AF121*	48	BC557	20	BF644	28	OC85*	44	ZTX550	25	2N3705	11				
AF122*	55	BC558	20	BF645	28	OC86*	44	ZTX551	25	2N3706	11				
AF123*	55	BC559	20	BF646	28	OC87*	44	ZTX552	25	2N3707	11				
AF126*	50	BCV30*	57	BF647	28	OC123*	75	40311*	97	2N3708	11				
AF127*	35	BCV34*	75	BF648	28	OC139*	110	40312*	97	2N3709	11				
AF139*	35	BCV39*	80	BF649	28	OC140*	110	40313*	125	2N3709	11				
AF178*	70	BCV40*	78	BF650	28	OC141*	110	40315*	55	2N3710	16				
AF179*	70	BCV42*	48	BF651	28	OC170*	40	40316*	85	2N3711	12				
AF232*	42	BCV43*	85	BF652	28	OC200*	85	40319*	71	2N3715	250				
AF239	122	BCV58*	90	BF653	28	OC201*	75	40320*	56	2N3717*	233				
ASV26*	40	BCV59*	90	BF654	28	OC202*	95	40323*	60	2N3822	130				
ASV27*	45	BCV70*	18	BF655	28	OC203*	85	40324*	85	2N3772*	195				
ASV50*	95	BCV71*	20	BF656	28	OC204*	85	40325*	85	2N3773*	288				
BC107*	9	BCV72*	20	BF657	28	OC205*	85	40326*	85	2N3774*	288				
BC107B*	10	BCV78*	25	BF658	28	OC206*	85	40327*	85	2N3775*	288				
BC108*	9	BC210*	145	BF659	28	OC207*	85	40328*	85	2N3776*	288				
BC108B*	10	BD112*	95	BF660	28	OC208*	85	40329*	85	2N3777*	288				
BC108C*	12	BD115*	95	BF661	28	OC209*	85	40330*	85	2N3778*	288				
BC109*	12	BD116*	95	BF662	28	OC210*	85	40331*	85	2N3779*	288				
BC109B*	12	BD121*	78	BF663	28	OC211*	85	40332*	85	2N3780*	288				
BC109C*	12	BD122*	78												

WATFORD ELECTRONICS

(Continued from opposite side)

DIODES		*BRIDGE RECTIFIERS		SPEAKERS	
AA119	15	1A/50V	20	80 Ω 3W	66
AA129	25	1A/100V	22	400 Ω 2.5"	69
AA300	15	1A/200V	25	64 Ω 2.5"	66
AA315	20	1A/400V	29	80 Ω 5W	190
8A100	10	2A/200V	44	6" x 4"	160
8Y100	24	2A/400V	48		
8Y126	12	2A/600V	53		
8Y127	12	2A/800V	55		
		2A/1000V	58		
		2A/1200V	60		
		2A/1500V	62		
		2A/2000V	64		
		2A/2500V	66		
		2A/3000V	68		
		2A/3500V	70		
		2A/4000V	72		
		2A/4500V	74		
		2A/5000V	76		
		2A/5500V	78		
		2A/6000V	80		
		2A/6500V	82		
		2A/7000V	84		
		2A/7500V	86		
		2A/8000V	88		
		2A/8500V	90		
		2A/9000V	92		
		2A/9500V	94		
		2A/10000V	96		
		2A/10500V	98		
		2A/11000V	100		
		2A/11500V	102		
		2A/12000V	104		
		2A/12500V	106		
		2A/13000V	108		
		2A/13500V	110		
		2A/14000V	112		
		2A/14500V	114		
		2A/15000V	116		
		2A/15500V	118		
		2A/16000V	120		
		2A/16500V	122		
		2A/17000V	124		
		2A/17500V	126		
		2A/18000V	128		
		2A/18500V	130		
		2A/19000V	132		
		2A/19500V	134		
		2A/20000V	136		
		2A/20500V	138		
		2A/21000V	140		
		2A/21500V	142		
		2A/22000V	144		
		2A/22500V	146		
		2A/23000V	148		
		2A/23500V	150		
		2A/24000V	152		
		2A/24500V	154		
		2A/25000V	156		
		2A/25500V	158		
		2A/26000V	160		
		2A/26500V	162		
		2A/27000V	164		
		2A/27500V	166		
		2A/28000V	168		
		2A/28500V	170		
		2A/29000V	172		
		2A/29500V	174		
		2A/30000V	176		
		2A/30500V	178		
		2A/31000V	180		
		2A/31500V	182		
		2A/32000V	184		
		2A/32500V	186		
		2A/33000V	188		
		2A/33500V	190		
		2A/34000V	192		
		2A/34500V	194		
		2A/35000V	196		
		2A/35500V	198		
		2A/36000V	200		
		2A/36500V	202		
		2A/37000V	204		
		2A/37500V	206		
		2A/38000V	208		
		2A/38500V	210		
		2A/39000V	212		
		2A/39500V	214		
		2A/40000V	216		
		2A/40500V	218		
		2A/41000V	220		
		2A/41500V	222		
		2A/42000V	224		
		2A/42500V	226		
		2A/43000V	228		
		2A/43500V	230		
		2A/44000V	232		
		2A/44500V	234		
		2A/45000V	236		
		2A/45500V	238		
		2A/46000V	240		
		2A/46500V	242		
		2A/47000V	244		
		2A/47500V	246		
		2A/48000V	248		
		2A/48500V	250		
		2A/49000V	252		
		2A/49500V	254		
		2A/50000V	256		
		2A/50500V	258		
		2A/51000V	260		
		2A/51500V	262		
		2A/52000V	264		
		2A/52500V	266		
		2A/53000V	268		
		2A/53500V	270		
		2A/54000V	272		
		2A/54500V	274		
		2A/55000V	276		
		2A/55500V	278		
		2A/56000V	280		
		2A/56500V	282		
		2A/57000V	284		
		2A/57500V	286		
		2A/58000V	288		
		2A/58500V	290		
		2A/59000V	292		
		2A/59500V	294		
		2A/60000V	296		
		2A/60500V	298		
		2A/61000V	300		
		2A/61500V	302		
		2A/62000V	304		
		2A/62500V	306		
		2A/63000V	308		
		2A/63500V	310		
		2A/64000V	312		
		2A/64500V	314		
		2A/65000V	316		
		2A/65500V	318		
		2A/66000V	320		
		2A/66500V	322		
		2A/67000V	324		
		2A/67500V	326		
		2A/68000V	328		
		2A/68500V	330		
		2A/69000V	332		
		2A/69500V	334		
		2A/70000V	336		
		2A/70500V	338		
		2A/71000V	340		
		2A/71500V	342		
		2A/72000V	344		
		2A/72500V	346		
		2A/73000V	348		
		2A/73500V	350		
		2A/74000V	352		
		2A/74500V	354		
		2A/75000V	356		
		2A/75500V	358		
		2A/76000V	360		
		2A/76500V	362		
		2A/77000V	364		
		2A/77500V	366		
		2A/78000V	368		
		2A/78500V	370		
		2A/79000V	372		
		2A/79500V	374		
		2A/80000V	376		
		2A/80500V	378		
		2A/81000V	380		
		2A/81500V	382		
		2A/82000V	384		
		2A/82500V	386		
		2A/83000V	388		
		2A/83500V	390		
		2A/84000V	392		
		2A/84500V	394		
		2A/85000V	396		
		2A/85500V	398		
		2A/86000V	400		
		2A/86500V	402		
		2A/87000V	404		
		2A/87500V	406		
		2A/88000V	408		
		2A/88500V	410		
		2A/89000V	412		
		2A/89500V	414		
		2A/90000V	416		
		2A/90500V	418		
		2A/91000V	420		
		2A/91500V	422		
		2A/92000V	424		
		2A/92500V	426		
		2A/93000V	428		
		2A/93500V	430		
		2A/94000V	432		
		2A/94500V	434		
		2A/95000V	436		
		2A/95500V	438		
		2A/96000V	440		
		2A/96500V	442		
		2A/97000V	444		
		2A/97500V	446		
		2A/98000V	448		
		2A/98500V	450		
		2A/99000V	452		
		2A/99500V	454		
		2A/100000V	456		
		2A/100500V	458		
		2A/101000V	460		
		2A/101500V	462		
		2A/102000V	464		
		2A/102500V	466		
		2A/103000V	468		
		2A/103500V	470		
		2A/104000V	472		
		2A/104500V	474		
		2A/105000V	476		
		2A/105500V	478		
		2A/106000V	480		
		2A/106500V	482		
		2A/107000V	484		
		2A/107500V	486		
		2A/108000V	488		
		2A/108500V	490		
		2A/109000V	492		
		2A/109500V	494		
		2A/110000V	496		
		2A/110500V	498		
		2A/111000V	500		
		2A/111500V	502		
		2A/112000V	504		
		2A/112500V	506		
		2A/113000V	508		
		2A/113500V	510		
		2A/114000V	512		
		2A/114500V	514		
		2A/115000V	516		

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5841/2/3

Z & I AERO SERVICES LTD.

Reg No. 242 1255 03

Please send all correspondence and Mail-Orders to Head Office

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES

1B3GT	0-84	8AX4GTB	1-13	8CY5	1-13	12AT6	0-68	ECF200	1-01	EM84	0-88	PCL81	0-73	PY82	0-82	UCC84	0-84
IR5	0-58	8AX5GT	1-48	6CY7	1-13	12AT7	0-56	ECF201	1-01	EM87	1-13	PCL82	0-80	PY83	0-79	UCC85	0-88
IX28	1-35	8BA6	0-51	8008B	1-63	12AU6	0-73	ECF801	1-07	EY81	0-82	PCL84	0-84	PY88	0-84	UCF80	0-84
5AT8	0-90	8BE6	0-54	8DT8	0-90	12AU7	0-53	ECF802	1-07	EY87	0-56	PCL86	0-86	PY500A	1-89	UCH42	1-13
5T4	0-84	8BF5	0-88	8DT8	0-90	12AV6	0-96	ECH42	1-24	EY88	0-82	PCL805	0-80	TT21	10-89	UCH81	0-73
5U4G	0-88	8BF6	0-84	8DW4	1-01	12AV7	1-13	ECH81	0-82	EY500A	1-89	PD510	3-78	TT22	10-89	UCL81	0-79
5U8	0-84	8BG6G	0-34	8ES5	1-13	12AX7	0-62	ECH200	0-90	EZ80	0-58	PL36	1-24	U25	1-13	UCL82	0-84
5V4G	0-88	8BH6	0-88	8EV5	1-69	12AY7	0-96	ECL80	0-68	EZ81	0-58	PL81	0-90	U28	1-13	UCL83	0-90
5X4G	0-90	8BJ6	1-35	6EW8	0-90	12BA6	0-90	ECL81	0-84	GY501	1-01	PL82	0-82	UAC80	0-85	UF41	1-13
5X8	1-01	8BJ7	0-73	8GH8A	0-90	12BF6	0-75	ECL82	0-68	GZ30	0-73	PL83	0-58	UAF41	0-80	UF80	0-58
5Y3GT	0-73	8BK4B	1-58	8GK5	0-79	12BH7A	0-84	ECL83	1-30	GZ32	0-73	PL84	0-84	UBC41	0-79	UF85	0-58
5Z4GT	0-73	8N4A	1-01	8GK6	1-61	12BL6	0-79	ECL84	0-79	GZ33	4-28	PL504	1-35	UBC81	0-85	UL84	0-88
8AB7	0-68	8N6	0-90	6J4	1-35	12B08	1-01	ECL85	0-73	DA2	0-70	PL508	1-58	UBF80	0-88	UM80	0-88
8AC7	0-90	8Q07A	0-79	8J5GT	0-80	12B7A	0-80	ECL86	0-96	DA3	0-81	PL802	3-15	UBF89	0-88	UM81	0-84
8AD8	0-88	8R8A	1-35	8J8	0-62	12CJ6	1-01	EF80	0-45	DB2	0-78	PY81	0-78	UBL21	1-01	UM84	0-51
8AF4A	0-90	8S7	2-59	8J7	0-90	19A05	0-84	EF85	0-54	DB3	0-81						
8AG5	0-73	8U8	0-88	8K5GT	0-84	19B68G	0-56	EF86	0-68	DB2	1-51						
8AG7	0-88	8W7	1-13	8K6GT	0-86	35A3	0-79	EF92	1-13	DC3	0-82						
8AH6	1-07	8Z6	0-73	8L6GT	1-24	35B3	0-73	EF97	0-79	DD3	0-81						
8AJ5	0-73	8Z7	0-79	8N7GT	0-86	35C5	0-96	EF98	1-01	PABC80	0-81						
8AK5	0-62	8C4	0-82	807	1-01	50C5	1-13	EF183	0-79	PC88	1-01						
8AK6	0-84	8C5GT	0-88	8SA7	0-90	50E85	0-96	EF184	0-79	PC88	1-01						
8AK7	0-88	8C8	0-58	8S67	0-90	DAF86	0-68	EFL200	1-80	PC96	0-58						
8AL5	0-45	8C8G	0-88	8SK7	0-90	0F96	0-68	EH90	0-88	PC97	1-07						
8AM6	0-79	8C8B	0-82	8SL7GT	0-79	OK92	1-13	EL33	2-81	PC900	1-13						
8AM8	0-79	8C67	0-79	6SN7GT	0-79	0L96	0-68	EL36	1-88	PCC84	0-58						
8AN5	2-81	8C68A	0-84	8S07	0-90	ECC84	0-68	EL81	0-90	PCC85	0-88						
8AN6	0-88	8CM7	0-80	6SR7	0-90	ECC85	0-54	EL82	0-88	PCC88	0-73						
8A05	0-88	8CM7	1-35	8V6GT	0-90	ECC86	1-41	EL83	0-88	PCC89	0-84						
8AS6	1-13	8C08	0-84	8X4	0-79	ECC86	0-84	EL84	0-73	PCC189	1-13						
8AS7G	1-35	8CS7	0-98	8X5GT	0-68	ECC89	0-90	EL86	0-84	PCF80	0-86						
8AT6	0-84	8CU5	1-13	8X8	0-90	ECC189	0-90	EL95	0-79	PCF82	0-51						
8AU6	0-58	8CU8	1-13	12A8	0-68	ECF80	0-68	EL504	1-07	PCF84	0-73						
8AV8	0-84	8CW4	3-75	12AL5	0-73	ECF82	0-82	EM80	0-73	PCF86	0-84						
8AW8A	0-84	8CX8	1-13	12A05	0-68	ECF86	0-90	EM81	0-68	PCF88	1-13						

OSCILLOSCOPE TUBES

current production. Made in USSR

One inch Tube Type 3L0 11. This tube is a good replacement for 1CP31. Tube characteristics are identical with those of 1CP31. As the connections are different the tube is supplied complete with base, connection diagram and technical data **£12.00** plus £0.96 VAT. **Three-inch tube Type 3BP1.** This well known tube used in "PURBECK" Oscilloscope can be supplied for **£7.50** plus £0.65 VAT. 14-pin base for the above **£0.80** plus £0.06 VAT.

Prices are inclusive of VAT (at current rates) except where shown separately. Postage and packing charges are **£0.10** per £ subject to a minimum of **£0.30**. Minimum order charge for Approved Credit customers **£20.00**. Minimum Transaction Charge for mail orders **£1.00**.

OUR NEW 1978/1979 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0.30

PRE-AMPLIFIER CP-P1

Shown here mounted with its associated components (and the CP-TM1 Peak Programme Monitor) on the CP-MPC1 interconnection board; the CP-P1 is a complete stereo pre-amplifier and tone control module. Performance features >70 db S/N ratio and >30 db overload margin (both ref. 3 mV) and distortion of 0.02%. The internal R.I.A.A. feedback compensation around the low-level pre-amp may be replaced with external networks and the tone control circuits can be programmed to give different turnover frequencies if required (including separate bass and treble 'defeat' facilities).

CP-P1 £14.95 incl. (U.K.) **£16.95** incl. (Export)

Also Available: Power Amplifiers, Filters, Stereo Image Width Control, Compressor/Expander, Active Crossovers, Power Supplies plus all pots, switches, etc.

MAGNUM AUDIO Ltd.

DEPT PW7, 13 HAZELBURY CRESCENT
LUTON, BEDS. LU1 1DF
TEL: 0582 28887

SEND LARGE S.A.E. FOR DETAILS

IT'S EASY WHEN YOU KNOW!

To avoid missing your copy of **PRACTICAL WIRELESS** – simply complete this order form and hand it to your newsagent.

ORDER FORM

To:
(name of newsagent)

Address

Please reserve/deliver every month one copy of **PRACTICAL WIRELESS** until further notice.

My Name

Address

QUARTZ LCD 5 Function

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M1

QUARTZ LCD 7 Function

Hours, mins., secs., month, date, auto calendar, back-light, seconds STOP WATCH.

£9.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M2

QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., date, day of week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 6mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£12.65 Thousands sold!

Guaranteed same day despatch.



M3

QUARTZ LCD ALARM 6 Function

Hours, mins., secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

QUARTZ LCD ALARM 7 Function

Hours, mins., secs., day, date, alpha day, back-light, auto calendar. Adjustable stainless steel bracelet. Only 9mm thick.

£15.95

Guaranteed same day despatch.



M5

QUARTZ LCD Alarm Chronograph with Dual Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on off indication. 1/10 second chrono graph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£22.65



M6

SOLAR QUARTZ LCD Chronograph with Alarm Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day date, month and year. 24 hour alarm with on off indication. 1/10 second chrono graph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£25.65



SOL
M7

QUARTZ LCD Alarm Chrono

22 function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION.

£22.65

Guaranteed same day despatch.

METAC ★ PRICE



M8

SOLAR QUARTZ LCD Chronograph

6 digit, 11 function. Hours, mins., secs. 1/100, 1/10 secs., mins. Split and lap modules. Auto calendar and back light. Powered from solar panel with battery back-up.

£13.95



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass.

List Price £130.00

METAC PRICE

£105.00



M10

SEIKO Chronograph

LCD, hours, mins., secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap-time. Back light, stainless steel water resistant, HARDLEX glass.

List Price £85.00

METAC PRICE

£68.00



M11

SOLAR QUARTZ LCD 5 Function

Genuine Solar. Solar panel with battery back-up. Back light and auto calendar. Hours, mins., secs., day, date. Quality metal bracelet.


£8.95

Guaranteed same day despatch.



M12

HANIMEX Electronic LED Alarm Clock

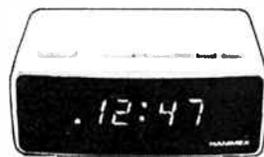

Features and Specification
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size 5 15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight 1.43 lbs (0.65 kg). AC power 220V.

£9.65 Thousands sold!

Guaranteed same day despatch.

M13

QUARTZ LCD Ladies Slim Bracelet

5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

£15.95

Guaranteed same day despatch.



M14

QUARTZ LCD Ladies 5 Function

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

£9.95

Guaranteed same day despatch.



M15

DIGITAL LED CLOCK



Automatic brightness control. Weekend alarm cancel.

Features and Specification
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on-off control. Display flashing for power loss indicator. Repeatable 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

£10.95

Guaranteed same day despatch.

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100.
Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME
Shops open 9.30 - 6.00.

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753



A quality range of British made electronic components that's there for you... look. Do your own home electrical work with complete confidence. See our pages 124 to 128.



This superb organ - build the first working section in just over 1000. Full specifications in our catalogue.




A range of highly attractive tools to be described in our catalogue. Our prices are very attractive too!



Audio bass pedal unit for organs. Has excellent bass guitar tone for guitarists' accompaniment. Specifications in our catalogue.



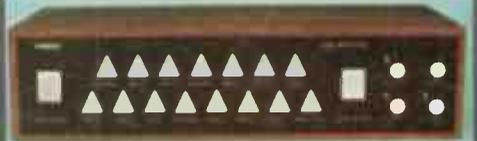A guitar with an electronic keyboard. Excellent tone, having the built-in looking and appearance. Full construction details in our catalogue.



Touch operated rhythm generator, the Domestic Commander. Details 75p. Dealer M2549. Specifications in our catalogue.



Mobile, amateur, radio, TV, and HF, aerials plus lots of accessories are described in our catalogue.



The 3800 calculator build it yourself at a fraction of the cost of one ready-made with the specification. Full details in our catalogue.



A wide range of clock accessories at handstand prices. Our catalogue has all the details.

MARPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road,
 Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554155.



A superb technical book for your home! All you need is our catalogue. Post the coupon now!



An attractive time aware clock with fully automatic alarm and battery back up! Complete kit with case only £12.99 inc. VAT @ 8% or M2549. Dealer only £8.42 inc. VAT.



A massive new catalogue from Marplin that's over 280 pages and better than before if you want the electronic components, this is the one catalogue you must not be without. Over 280 pages - some of the best - it's a comprehensive guide to electronic components with hundreds of photographs and diagrams and page after page of readable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Marplin.



A 83-key A301 keyboard with 625 line TV monitor. A page memory and microprocessor interface. Details in our catalogue.

Post this coupon now for your copy of our 1979-80 catalogue price 75p. Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____

ADDRESS _____
