

PRACTICAL WIRELESS




DECEMBER
1973

20p

FREE
inside
2 DATA-CARDS

Australia 50c
New Zealand 50c
South Africa 45c
Rhodesia 45c
Nigeria K10
Malaysia S1.80
Sweden Kr 3.50
Malta 22c
Norway Kr 5.10

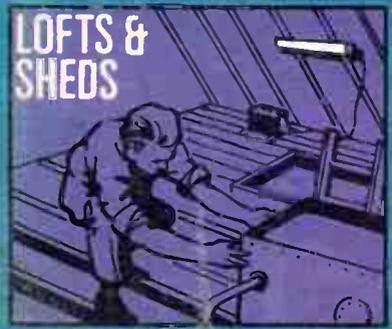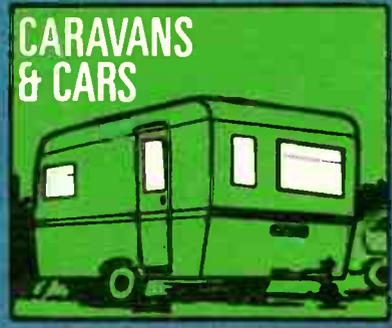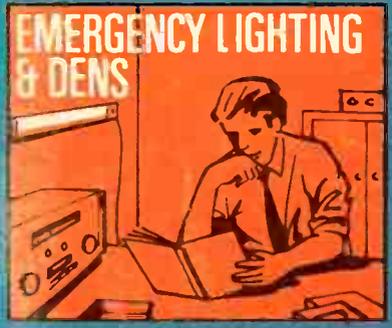PORTABLE FLUORESCENT LAMP UNIT -FROM YOUR 12V BATTERY



**ALSO:- 3-BAND SHORT WAVE SUPERHET
USING THE LM380 I.C. AUDIO AMPLIFIER**

This Christmas

if your imagination stops at cigars...

...give Antex



MODEL X25 Soldering Iron
220-240 Volts or 100-120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally-made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed. **PRICE £1-93** (rec. retail) P & P 8p. Suitable for production work and as a general purpose iron.



MODEL CCN
220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64". **PRICE £2-15** (rec. retail) P & P 5p.

MODEL G 18 watt miniature iron, fitted with long-life iron-coated bit 3/32". Voltage 240, 220 or 110. **PRICE £2-15.** (rec. retail) P & P 5p.



MODEL CN Miniature 15 watt soldering iron fitted 3/32" iron coated bit. Many other bits available from 3/64", to 3/16". Voltages 240, 220, 110, 50 or 24. **PRICE £1-93.** (rec. retail) P & P 5p.



all prices include VAT at 10%



MODEL SK.2 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, stand and "How to Solder" booklet. **PRICE: £2-87.** (rec. retail) P & P 8p.



MODEL SK.1 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet. **PRICE £3-25** (rec. retail) P & P 12p.



MODEL MLX KIT
Battery operated 12v. 25 watt iron fitted with 15" lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder". **PRICE £2-27** (rec. retail) P & P 12p.



From radio or electrical dealers, car accessory shops or in case of difficulty direct from:—
ANTEX LTD. FREEPOST
(no stamp required) **PLYMOUTH**
PL1 1BR Tel: 0752 67377.

Please send the following:

.....
I enclose cheque/P.O./Cash (Giro No. 2581000)
.....
NAME

ADDRESS

PW/12

PRACTICAL WIRELESS

VOL. 49 NO. 8
ISSUE 802
DECEMBER 1973

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR Morris A. Colwell
ASSISTANT EDITOR
Lionel E. Howes, G3AYA
ART EDITOR Peter Metalli
TECHNICAL EDITOR
Eric Dowdeswell, G4AR
**PRODUCTION & NEWS
EDITOR** Colin R. Riches
PROJECTS SUB-EDITOR
Geoffrey C. Arnold
TECHNICAL ARTIST
Alan Martin
SECRETARIAL
Jenny Maunder
01-634 4292 Susan Corne
ADVERTS. MANAGER
01-634 4293 Roy Smith
CLASSIFIED ADVERTS.
01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rates for one year to any part of the world £2.65 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". Binders (£1.10) and indexes (11p) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of *Practical Wireless* and *Television* only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 726 "STEAM" ROLLING—Leader article and January preview
- 727 NEWS . . . NEWS . . . NEWS . . .
- 734 TELEVISION—Coming in the December issue
- 750 HOTLINES on recent developments by *Ginsberg*
- 751 NEXT MONTH in *Practical Wireless*
- 742, 762 DEAR SIR—Readers' letters to the Editor
- 771 ON THE AIR—Reports on Broadcast Bands
- 771 Short Wave—*Malcolm Connah*
- 772 Medium Wave—*Charles Molloy*
- 772 VHF/FM—*Simon David*
- 775 Amateur Bands, Short Wave/VHF—*David Gibson, G3JDG*

● CONSTRUCTIONAL

- 728 3-BAND SHORT WAVE RECEIVER—*F. G. Rayer, G3OGR*
- 737 USING THE LM380N AMPLIFIER—*J. B. Dance, M.Sc.*
- 746 EXPERIMENTAL WORKSHOP Trigger Circuits—*M.J. Hughes, M.A.*
- 752 PORTABLE FLUORESCENT LAMP UNIT—from your 12V battery
- 763 GOING QUADRAPHONIC—PROJECT Q4, Part 3—*D. Bollen*
- 770 TAKE 20 No. 55 Triplex Signalling Unit—*David Andrews*

● OTHER FEATURES


- 734 TECHNICROSS No. 1—Solution
- 745 GOING BACK Equipment of yesteryear—
Colin Riches and Arthur Dow
- 757 SUCCESSFUL SOLDERING—*V. Capel*

● EXTRA WITH THIS ISSUE

INSET P.W. DATACARDS in COLOUR

- No. 5 Resistance and Capacitance Calculator
- No. 6 D.C. Circuits

RSC GROUP/DISCO UNITS

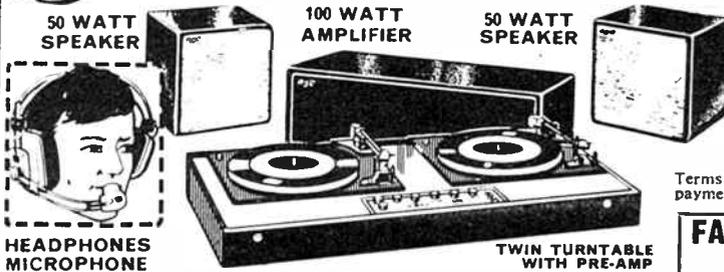

RSC DISCO MASTER

DISCOTHEQUE CONSOLE with integrated power supply, 100w OUTPUT TWIN JACK OUTPUT SOCKETS Inc. twin Garrard SP25 Mk111 or BSR Macdonald MP60 type turntables, Pick-ups with high compliance cartridges and diamond styl. Separate volume controls for each turntable. Bass controls, Separate input for mic. with vol. control switch. Rexine covered cabinet size approx. 32" x 16" x 7" with lid Terms: Deposit £20 and 12 monthly payments £7-60 (Total £111-20). Carr. £2-50. **ONLY £99-75**

PACKAGE OFFER

- Units listed below
 (a) 100w POWER AMPLIFIER
 (b) PAIR OF HI-FI HEADPHONES
 (c) MATCHING DYNAMIC 'MIKE' (attached to hi'phone)
 (d) PAIR 50 WATT SPEAKERS
 Black Rexine covered Cabinets Size approx. 18" x 18" x 8"
 (e) RSC TDI DISCO CONSOLE
 (a) (b) (c) (d) **£149-95**
 (e) Carr. £3-00

Terms Deposit £30 and 18 monthly payments of £8-33 (Total £179-94).

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonolone or Accos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'Mike' with vol. control switch. Black Vynide covered Cabinet with lid. See illustration on left
 Or Dep. £2-95 and 12 mthly pymts £5 85 (Total £80-15) **£69-95**
 Carr. £1-50

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15"	15" 60 Watt 14,000 gauss 8/15"	12" 50 Watt 13,000 gauss 15"
£25-95	£14-75	£11-99
Dep: £5-95 and 9 mthly payments £2-58 (Total £28-99)	Dep. £3-75 and 9 monthly payments. £1-50 (Total £17-25)	Dep £2-99 and 9 monthly payments £1-28 (Total £14-51)

FOR BASS GUITAR, ELECT. ORGAN, ETC.

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free **£7-95** or Dep. £1-25 and 9 mthly payments 89p (Total £9-26)

DISCO PACKAGE OFFER £45

Pair BSR MP60 T/tables GP91 PU Cartridges. FAL Disco Pre-amp. Total Rec. Ret. Price £50-11 Carr. £1

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 60 MK.III AMPLIFIER PR. FANE POP 25/2 25W L/SPEAKERS Terms: Deposit £7-50 and 12 monthly payments of £4-29 (Total £58-98)	£59-83 £15-90 £55-83	PACKAGE PRICE £51-50 carr. £1-10
F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 60 L/SPEAKERS Terms: Deposit £9-50 and 12 monthly payments of £4-88 (Total £68-06)	£59-93 £28-98 £83-91	PACKAGE PRICE £59-50 carr. £1-10
F.A.L. PHASE 50 MK.III AMPLIFIER PAIR L12/20 25W L/S in cabinets Terms: Deposit £10 and 12 monthly payments of £5-17 (Total £72-04)	£59-93 £26-80 £86-23	PACKAGE PRICE £63 carr. £1-25
F.A.L. PHASE 100/2 AMPLIFIER 4 FANE POP 60 L/SPEAKERS Terms: Deposit £20 and 18 monthly payments of £8-35 (Total £134-30)	£69-85 £47-98 £117-81	PACKAGE PRICE £110 carr. £2

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback howl characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £2-95 and 9 mthly payments £2-48 (Total £24-82) Carr. 65p. **£21-95**

TYPE C313 50 WATTS Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £4-72 & 9 mthly pymts **£32-72** £3-58 (£38-94) Carr. 85p

TYPE C4100 100 WATTS inc. four 12" 60 watt speakers for conservative rating. Extra heavy construction. Size approx. 58 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £15-50 & 12 mthly. pymts. £5-48 (Total £81-02). Carr. £1-50 **£71-50**

F.A.L. DISCO PRE-AMPLIFIER £18-97

Designed for use with a pair of Player Units and Amplifier with Bass and Treble Controls. Incorporates MONITORING FACILITIES and Mic. input. The 4 inputs are ind. controlled. Selector switch Gram (1), (2), and Tape. 200-250v A.C. Mains 50Hz. Brush Silver finished fascia. Size approx 16" x 3" x 4" deep. Fully enclosed but can mounted in cabinet.

FANE "CRESCENDO" SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

FAL PHASE 50 Mk.III AMPLIFIER 50 WATT. Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/s 3 to 30 ohms. Size 17" x 7" x 7". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £8-93 & 9 monthly payments £4-22. Total £44-91. **£39-93** Carr. 85p.

RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker

For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £8-95 and 12 monthly payments £4-97 (Total £88-59). Carr. Free-MAR for leaflet. **ONLY £59-95** U.K. Mainland

RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.
 ★ Two extra heavy duty 12in. 50w Loudspeakers.
 ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or 'mikes'. Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £16-50 & 12 monthly payments of £6-68. (Total £82-12). Carr. £2-50 **£72-50**

RSC GP30 HI-FI AMPLIFIER

For Guitar, Vocal or Instrumental Group
 3 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current values. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/alter P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 9 monthly payments of £2-76 (Total £29-15). **£25-85** Carr. 75p

NOW SIX NEW BRANCHES

- BOLTON 23 DEANSGATE
- COVENTRY 17 SHELTON SQUARE
- DONCASTER 3 QUEENSGATE
- WATERDALE CENTRE
- NOTTINGHAM 19/19A MARKET ST
- STOCKPORT 8 LITTLE UNDERBANK
- SUNDERLAND 5 MARKET SQUARE
- NEW LARGER PREMISES AT HULL, DARLINGTON, NEWCASTLE & DERBY See Addresses

RSC
 All items subject to availability. Prices correct at 25.10.73 £. s. d.
 HI-FI CENTRES LTD.
 MAIL ORDERS & EXPORT ENQUIRIES TO:
 AUDIO HOUSE, BENCONNER LANE, LEEDS, 13.
 Tel: Pudsey 09735 77681.
 TERMS C.W.O. or C.O.D. No C.O.D. under £1.
 POSTAGE 28p EXTRA UNDER £2. 33p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED.
 S.A.E. PLEASE WITH ENQUIRIES.
 SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc.
 MAIL ORDERS MUST NOT BE SENT TO SHOPS

FAL PHASE 100/2 AMPLIFIER

100 WATTS MUSIC RATING. Solid State. Sep. Bass and Treble Controls. 4 separate-controlled inputs plus master control. Output for speaker/s 3-30 ohms. Includes protective circuit against damage from short circuits. Terms: Deposit £7-85 & 12 monthly payments £8-05 (Total £80-45). **£69-85** Carr. 82p

FAL TWIN CHANNEL AMPLIFIERS

Solid State. 4 sep. controlled inputs plus master volume control. Individual Bass and Treble controls. Output for speaker/s 3-30 ohms. Protective circuitry against damage from short circuits.
FAL 'SUPER 50' **£59-50** Carr. 80p
 Terms: Dep. £8-50 & 12 mthly. pymts. £1-97 (Total £68-14)
FAL 'SUPER 100' **£79-95** Carr. 90p
 Terms: Dep. £11-95 & 12 mthly. pymts. £6-63 (Total £81-51). Prices above include protective dust cover.

HUGE DISCOUNTS ON LEADING BRAND TAPE AND TURNTABLE UNITS

CREDIT TERMS AVAILABLE
Minimum Deposit 10%

DISCOUNT WAREHOUSE PRICES ON LEAK, WHARFEDALE etc. etc.—visit your nearest RSC Hi Fi Centre

AKAI GXC 40D Tape Unit £62.95 (Rec. Price £89.74) Carr. £1
AKAI 4000DS Tape Unit £68.95 (Rec. Price £97.50) Carr. £1
AKAI 1721L Tape Unit £66.95 (Rec. Price £104.50) Carr. £1
AKAI CR81D Tape Unit £58.95 (Rec. Price £84.10) Carr. £1
GOLDRING GL72 T/Table & P.U. £29.95 (Rec. Price £37.29) Carr. £1
 Also FREE with above GL72 Goldring G800 cartridge worth over £10
B.S.R. MACDONALD MP60 TYPE T/Table & P.U. £10.95 (Rec. Price £14.95) Carr. 40p

Prices shown correct at time of going to press (24/10/73)

FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite cored coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc. and instructive diagrams. Frequency £10.98 post free Response 25 Hz-20 kHz. 8-15Ω

Price per pair £19.99 Or Dep. £1.99 & 9 monthly payments of 23 Ctot. £13.50

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls. Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20.20.000 c.p.s. Bass Control ± 12db.

Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12.65 Carr. 40p

OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £16.50 or dep. £2.50 and 9 monthly payments £1.83 (Total £18.97)



AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 16,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.

Exceptional performance at low cost.
HF080T 8" 10W £2.98 **HF120D** 12" 15W £6.50
HF102D 10" 10W £3.30 **HF126** 12" 15W £6.35
HF120 12" 15W £4.95 **HF128D** 12" 15W £6.85

FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15Ω Post Free £3.99
 PLEASE STATE IMPEDANCE REQUIRED R.P.F. 64-99
MODEL 803T 8" 15w. with parallel Tweeter. Post Free £5.50
 Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15Ω. H.R.P. £6-99

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED.

Impregnated and interleaved where necessary. Primaries 200-250v. 500/s. Screened

MIDGET CLAMPED TYPE 2 1/2" x 2 1/2" x 2 1/2"
 250v., 60mA, 6-3v. 2a £1.10
 250-0-250v., 60mA 6-3v. 2a £1.16

FULLY SHROUDED UPRIGHT MOUNTING
 250-0-250v. 80mA, 6-3v. 2a., 0-6-6-3v. 2a. £1.55
 250-0-250v. 100mA, 6-3v. 4a., 0-6-6-3v. 2a. £2.15
 300-0-300v. 100mA, 6-3v. 4a., 0-6-6-3v. 2a. £2.45
 300-0-300v. 130mA, 6-3v. 4a., ct., 6-3v. 1a. £2.45
 For Mullard 510 Amplifier £2.95
 350-0-350v. 100mA, 6-3v. 4a., 0-6-6-3v. 2a. £2.45
 350-0-350v. 150mA, 6-3v. 4a., 0-6-6-3v. 2a. £2.45

FLAMENT or TRANSISTOR POWER PACK
 Types 6-3v. 1.5a. 55p; 6-3v. 2a. 60p; 6-3v. 3a. 85p;
 6-3v. 6a. £1.46; 12v. 1a. 61p; 12v. 3a. or 24v. 1.5a £1.50; 0-9-18v 1 1/2a £1.25; 0-12-25-42v 2a £1.95.

ALL R.S.C. PRICES INCLUDE VAT FULL LABOUR AND MATERIAL GUARANTEES FOR 12 MONTHS

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p per unit
JES Size 16" x 11" x 9". SE8 For optimum performance with any 8in. Hi-Fi speaker. £6.50
 Size 19 x 10 1/2 x 9in. SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter £7.95
 Size 25 1/2 x 16 x 9in. SE10 For outstanding results with 10in. Hi-Fi spkr. Size 25 1/2 x 16 x 9in. Ported £6.75



AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range £6.50 Carr. 33p
 ensure surprisingly realistic reproduction. OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER £7.65 Carr. 39p

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. -2db. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 50mV Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2" x 2 1/2" x 6 1/2". Attractive brushed silver finish fascia plate 10 1/2" x 3 1/2". and matching knobs. Complete kit of parts with full wiring diagrams and instructions £8.50 Carr. 40p



R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BML All-dry battery eliminator. Size 5 1/2" x 4 1/2" x 2 1/2". approx. Completely replaces batteries supplying 15v and 90v, to battery radio where A.C. mains 200/250v. Post 30p
 50c/s is available. ASSEMBLED READY FOR USE £4.15



R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET

- Push Button Selector Switching
 - Jack Socket for Headphones
 - Neon Indicator
 - Satin Silver Finish Metal Fascia
 - Solid State Circuitry
 - Twenty Silicon Transistors
 - Four Diodes, Four Rectifiers
- Send S.A.E. for full descriptive leaflet.



For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8Ω. Frequency Response 7 Hz to 70 KHz ± 1 1/2 dB.

COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £5 extra.

R.S.C. STEREO FM III TUNER. in cabinet. Visually matches Super 30 Mk. III £37.50

FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 9 monthly payments £4.54 (Total £47.86).

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

- ★ Moderate size only 25 x 14 x 10in. approx.
- ★ Response 30-20,000 c.p.s. Impedance 15 ohms
- ★ Performance comparable with units costing considerably more Carr. 65p



Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Deposit £5.25 and 9 monthly payments £2.56 (Total £28.29).

R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY

- BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
- BOLTON 23 Deans (Closed Wed.). Tel. 35512
- BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.)
- COVENTRY 17 Shelton Square, The Precinct.
- DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361
- DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

- DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs)
- EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
- GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158
- HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
- LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
- LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252
- LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
- LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

- MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778
- MIDDLESBROUGH 106 Newport Rd. (Closed Wed.). Tel. 47696
- NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469
- NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068
- SHEFFIELD 13 Exchange Street (Castle Mkt. Blds. (Closed Thurs.). Tel. 20716
- STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777
- SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573



RINGBOARD

BY RETURN

POST FREE U.K. ONLY

STANDARD P.C. BOARDS WITH I.C. ADD ON BOARDS

NOW AVAILABLE

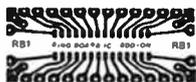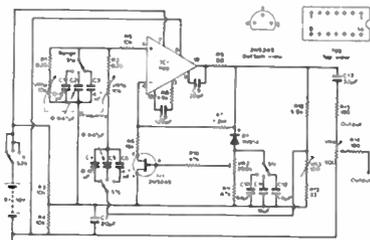

TYPE RB1 DIL



TYPE RB2 WIRE ENDED OR TAG STRIP



ADD ON MOUNTED ON RING BOARD

NOVICES

Could you build the above circuit without a circuit layout. We think you could with **RINGBOARD** and the method supplied with each board.

EXPERIENCED CONSTRUCTORS AND LAB. TECHNICIANS

Make your work simple using ADD on I.C. boards and a good quality fibre glass standard PC flux varnished board (no cutting and little looping). Once you have used it we don't think you will find any standard PC board to compare favourably with Ringboard.

For leaflet showing and describing method please send stamped addressed envelope. **FREE!** One ¼ Board (sub standard) with the first 500 enquiries from this advertisement.

	Opening price	Actual price
Full Board	47p	55p
Half board	26p	33p
Quarter board	16p	22p

Add on board 25p each

Send to **RINGBOARD, 257 CHESTERFIELD ROAD, SHEFFIELD, YORKS, S8 0RT, Tel. 52178**

TO SPARK YOUR IMAGINATION!
the **SPARKRITE**
Electronic Ignition Kit
only **£9.35**

Kit comprises EVERYTHING
Case, cables, coil connectors.
Silicon grease.
8 page instruction leaflet


Fascinating to build Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance. • Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed. • Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition Price: £9.35 inc. V.A.T. and postage. (12 volt only State Pos. or Neg. earth). Ready built unit also available £11.55 inc. V.A.T. and postage. **GUARANTEED 5 YEARS**

ORDER NOW—send P.O./Cheque direct to **ELECTRONICS DESIGN ASSOCIATES, DEPT. PW12**
82 Bath St., Walsall WS1 3DE. Phone: 33652

CASED AMPLIFIERS

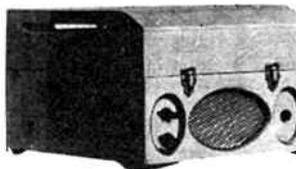

Polished wooden cabinet 14 x 13 x 9" with hinged lid containing a sensitive (20µV) 4 valve amplifier with cone and vol. controls, giving 3 watts output to the 7 x 4" 3Ω speaker. Also included is a non-standard tape deck. Supplied in good working condition with cct. diagram. Mains operated. Only £3 (£1 up to 150 miles, £1.20 over). Cassettes £1 each (25p); spare heads reduced to 25p. Amplifier chassis only, complete, uses 2xECC83, EL84, EZ80 £1.65 (40p).

71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, crystals, pots, switches, PC boards with transistors and diodes on and loads of odds and sods. Outstanding value at £1.65 (40p).

COMPUTER PANELS

31b asstd. £1 (30p); 71b £2 (40p); 561b £13 (c.p.d). 12 top quality panels containing IC's, trim pots, power transistors, etc. £2 (30p); Panels containing at least 500 parts inc. at least 50 transistors 60p (20p); Panels with 25 flatpack IC's (no info.) 30p (10p).

EX-COMPUTER EQUIPMENT (RCA 301)

Tape, ½" x 1200' on 7" NAB spool 67p (25p); ¾" x 1800' on 10½" NAB spool 67p (35p); 20000µF 30V elec. 40p (25p); 35000µF 15V 40p (25p); 125 bit variable delay line with 7 transistor amplifier 75p (10p); 25 bit ditto 60p (10p); ½" 16 track tape decks, complete with electronics in 6" cabinet £75; 240kHz 11 transistor xtal oscillator 70p (10p); Other peripherals available. 100 tag strips 50p (15p); 500 asstd. resistors £1 (20p); 5000 £8 (50p); 20000 £25 (£1); 80 + 80 + 20µF 350V caps 10p (6p) 10 for 75p (30p); 100 1 & 2% resistors 60p (12p); 150 small caps 60p (12p); 25 10X Crystals 75p (30p); 4p 8w switches 40p (10p); 2N277 (150V PNP) on small heat sink 30p (10p); 4.7µF 10V tantalum bead caps 30p doz (5p). Unit containing 2 modern c/o lever switches, 3 trim pots, R's, C's, etc. 60p (10p). Lots of junk for callers to look at. **POST IN BRACKETS; SAE LIST, ENQUIRIES.**

VAT NOT INCLUDED—ADD 10% TO TOTAL


GREENWELD ELECTRONICS (PW7)

Mail order to 24 Goodhart Way, West Wickham, Kent. Shops at 21 Deptford Broadway, SE8 Tel. 01-692 2009 and 38 Lower Addiscombe Road, CROYDON.

look! electronics really mastered

... practical
... visual
... exciting!

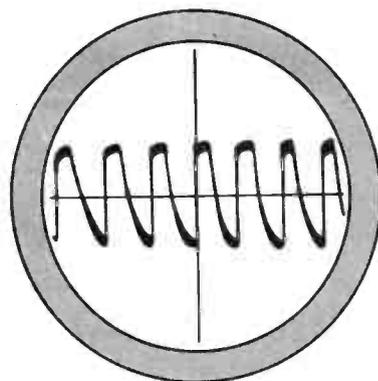no previous knowledge
no unnecessary theory
no "maths"




RAPY

BUILD, SEE AND LEARN
step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

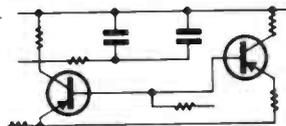2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL123

special free gift also to all our students

DISCOUNTS UP TO

60%

FULL 12 MONTH AFTER SALES SERVICE

with probably the best discounts offered in the U.K.

ALL PRICES ARE INCLUSIVE OF V.A.T.

FANTASTIC OFFER GARRARD SP25 Mk III.

Goldring G800. Teak finish, plinth and tinted cover with mains lead and DIN plug and screened lead. All fully wired. Please add £1.75 for P. & P. and Ins. **£14.95**

TURNTABLES

Please add 95p P & P and Ins.

BSR MP60	£9.25
Garrard SP25 Mk III	£9.95
Garrard SL6SB	£12.95
Garrard AP76	£16.65
Garrard 401	£27.50
Garrard Zero 100 (sngle)	£30.95
Garrard Zero 100 (Auto)	£34.95
Goldring GL85/P. P & C	£65.95
Goldring G101/P P & C	£21.95
Goldring GL72/P	£24.95
Goldring GL72/P	£31.95
Goldring GL75	£30.95
Goldring GL75/P	£38.95
Goldring GL75 Lid	£4.25
Thorens TD125	£60.95
Thorens TD125 AB Mk II	£93.95
Thorens TD160 AB & C	£51.95
Thorens TD165 AB & C	£45.95
Condor Auto Cleaner (Star Value)	£1.40 P & P 15p

TUNERS

Please add 55p P & P and Ins.

Alpha Highgate FT150	£32.95
Amstrad Multiplex 3000	£23.90
Metrosound FMS 40	£37.75
Philips RH 621	£72.95
Metrosound FMS 20 Mk II	£37.75
Rogers R/brook FET 4 (Cha)	£32.95
Rogers R/brook FET 4 (Cased)	£36.50
Sinclair cased tuner	£27.50
Teleton GT202 (N/P)	£32.95

SPEAKERS

£1.65 for P & P (Per Pair)

Amstrad Acoustra 1500	£26.90
Amstrad Acoustra 2500	£30.75
Celestion Ditton 15	£50.75
Celestion Ditton 44	£70.45
Goodmans D/Maxim	£40.95
Goodmans Mezo 3	£50.95
Goodmans Havant	£35.25
Keltron KS4	£13.85
Keltron KS8	£22.50
Sinclair Q16	£11.95
Sinclair Q30	£30.95
Wharfedale Denton II	£26.80

SPEAKER UNITS

Wharfedale Linton Kit	£16.85
Wharfedale Glendale Kit	£29.95
Wharfedale Unit 3	£16.30
Wharfedale Unit 4	£28.70
Wharfedale Dovedale Kit	£44.95

All prices correct at time of press (E. & O. E.) and are subject to alterations



GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept PW12, 174 Pentonville Road, London, N1. Telephone 01-278 1769

Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card)

2 minutes from KING'S CROSS, EUSTON & ST PANCRAS on main road leading to the East and West Country

AMPLIFIERS

Please add 95p P & P and Ins.

Amstrad 8000 Mk II	£15.85
Amstrad IC2000 Mk II	£32.15
Amstrad Integra 4000	£23.95
Alpha Highgate FA400	£39.05
Global 10 + 10	£19.75
Global 20 + 20	£25.95
Keltron 1000	£22.95
Keltron 1500	£25.75
Metrosound ST20E Mk II	£29.95
Metrosound ST60	£51.95
Rogers R/brook (Ch)	£41.15
Rogers R/brook Mk III (Ca)	£44.50
Rogers R/bourne (Ch)	£54.25
Rogers R/bourne (Ca)	£56.95
Sinclair 2000	£24.90
Sinclair 3000	£31.95
Sinclair 605	£21.45
Sinclair PRO 60 2 x Z30/PZ5	£16.40
Sinclair PRO 60 2 x Z30/PZ6	£19.45
Sinclair PRO 60 2 x Z30/PZ6 Trans	£25.25
Sinclair AFU PRO 80 (Filter Unit)	P.O.A.
Sinclair Stereo 80 Pre-amp	P.O.A.
Sinclair Z30 Amp	£3.85
Sinclair Z50 Amp	£4.50
Sinclair PZ5 Power Supp.	£4.20
Sinclair PZ6 Power Supp.	£6.15
Sinclair PZ8 Mains Trans.	£4.95
Sinclair PZ8 Power Supp.	£6.15

TUNER/AMPLIFIERS

Please add £1.10 P & P and Ins.

Alpha FR 3000	£61.35
Goodmans Module 80	£62.95
Goodmans Mod 80 Com	£109.95
Goodmans Mod. 90	£76.95
Goodmans One-Ten	£92.95
Rogers R/brook (Cha)	£61.95
Rotel 150A	£45.25
Rotel 200A	£57.95
Status STA160	£89.95

PLINTH AND COVERS

£3.35* For Garrard SP25, 2025 TC, 3000, AP76, SL72B, SL95B, etc £4.85 + 71p P. & P.



CARTRIDGES

Please add 11p P & P and Ins.

Goldring G850	£2.75
Goldring G800	£3.50
Goldring G800E	£6.30
Goldring G800SE	£10.90
Shure M3D	£3.25
Shure M44E	£4.95
Shure MSSE	£5.00
Shure 7SEJ Type 2	£9.25
Shure V15	£25.95
Shure M7SEJ Type 2	£7.95
Sonotone 9 TAMC	£1.20
Sonotone V 200F	£8.55
Audio Technica AT 66	£3.15
ADC 10E Mk IV	£14.95
Ronette SM S007	£5.25
Ronette SM S001E	£7.95

AN IMAGINATIVE CHRISTMAS PRESENT NOW YOU CAN BUILD AN ERNIE IN YOUR OWN HOME

LEARN THE DIGITAL LOGIC COMPUTER TECHNIQUES.



A MULTIPURPOSE ELECTRONIC DICE. AVAILABLE AS A COMPLETE KIT.

Build something completely out of the ordinary; something different and more exciting than everyday repeated stuff.

MINICOMP 100* is effectively a miniaturised ERNIE that displays truly RANDOM NUMBERS using brilliant NIXIE tubes: at the mere touch of a button. Four range selections are included according to the application: between 1-6 (DICE), 0-36 (ROULETTE), 1-57 (POOLS DRAWS), and between 0-99 (BINGO), (BATTLESHIPS AND ALL OTHER NUMBER GAMES). The numbers revolve round at high speed in a spectacular DICE fashion before a random number is selected and displayed. Building this fascinating ERNIE will familiarise you with sophisticated logic techniques and elements used in a digital computer.

A COMPLETE KIT includes 7 latest LOGIC I.C.'s, 3 transistors, 2 NIXIES, GLASS FIBRE printed circuit, the power supply and various other components. Elegant-sized and finished case, approx. 7" x 5" x 3". Easy to build with illustrated instructions and descriptions of the LOGIC circuits.

APPLICATIONS: With the MINICOMP it is now possible to play electronically all possible NUMBER GAMES e.g. ROULETTE, BINGO, BATTLESHIPS, CRAP DICE. An interesting application is filling in the POOLS DRAWS. The pure random nature of the DRAWS could well contribute to the winning combination.

A PROFOUND ATTRACTION FOR PARTY GAMES, FETES & BAZAARS. U.K. PRICES: COMPLETE KIT WITH ILLUSTRATED INSTRUCTIONS. Mains operated unit, 240V 50HZ or 110V 60HZ.

MINICOMP 100 £21.97, including P. & P. & V.A.T.

Fully built, tested units with a year's guarantee £24.87

TERMS: C.W.O. MAIL ORDER ONLY.

MICRO

MICROELECTRONICS

51 Mexfield Road, London SW15 2RG. Tel: 01-870 2368

* Patent applied for.

Dimmit

range of light dimmers


Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer. linear operation, interference suppression, 60mm slider range: size 12 x 5 x 4 cm. ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc.. Complete with scale plate, fixing screws and full instructions. £5.50 inc. VAT, add 10p P. & P. Also available in 2kW, with separate heatsink.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors etc. Rotary and slider control versions. Ratings: 400W, 1,000W, 2,000W.

NEW addition to Dimmit range—Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Rating 800 watt. Full instructions. £6.50 inc. VAT, add 10p P. & P. Send 10p for complete illustrated catalogue and price list.

YOUNG ELECTRONICS Mail Order Dept.

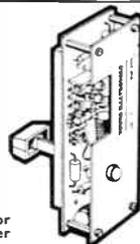54 Lawford Road, London NW5 2LN. Telephone 01-267 0201



PW

Q4

PROJECT

PCB's AND COMPONENTS FOR THIS AND OTHER PW PROJECTS

REVERBERATION UNIT
8 WATT AMPLIFIER & PRE-AMP
LOUDHAILER PRE-AMP & SIREN GENERATOR
VIBRASONIC GUITAR PRE-AMP
DIGITRONIC DIGITAL CLOCK

AND ALSO FOR MANY P.E. PROJECTS

SEND AN S.A.E. FOR OUR FREE LIST

PHONOSONICS

Dept PW12, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
MAIL ORDER ONLY

MAPLIN ELECTRONIC SUPPLIES

*** SAME DAY SERVICE**



MAPLIN Projected site of London - third airport.

LARGE OR SMALL Centurion



Model 120

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer. Detachable front panel finished in white.



Model 320

Model	W	H	D	Price
120	8	2 1/2	6	£1.85
220	8	4	3 1/2	£2.65
221	8	4	4 1/2	£2.80
320	12	4	12	£5.00

Chassis for model 320 £1.75 extra

Please send S.A.E. for free illustrated leaflet

MES announces the very latest development in organ circuitry

THE DMO2

13 Master Frequencies on ONE tiny circuit board
LOOK AT THESE AMAZING ADVANTAGES

- ★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator.
- ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra.
- ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3.7in. x 4.5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

DMO2 (with tremulant) ONLY £14.25
DMO2 (without tremulant) £12.25
SAJ110 7-stage frequency divider in one 14 pin DIL package. Square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.A.E. please for data sheet

★ S.A.E. please for full technical details.

Trade enquiries welcome.

TRANSISTORS, DIODES & I.C.'s.

AC127	25p	BF194	15p	OA90	7p
AC128	20p	BFY51	18p	OA91	6p
AC176	17p	MPF102	36p	IN914	4p
AD149	50p	OC44	20p	1N148	4p
AD161/2	60p	OC71	20p	1N4001	8p
BC107	10p	T1843	25p	1N4002	61p
BC108	10p	2N1711	24p	1N4003	7p
BC109	10p	2N2219	25p	1N4004	71p
BC147	10p	2N2646	45p	1N4005	8p
BC148	10p	2N2905	33p	1N4006	81p
BC149	12p	2N2907	25p	1N4007	9p
BC168	13p	2N3926A	10p	W005	30p
BC169	12p	2N3926Y	10p	W04	33p
BC182L	10p	2N3926G	10p	741C 8-pin	15p
BC204	14p	2N3053	18p	D.I.L.	36p
BC205	14p	2N3055	49p	741C 14-pin	45p
BD131	84p	2N3819	29p	D.I.L.	45p
BD132	87p	AA119	7p	D.I.L. Sockets	20p
BD131/2	£1.50	BY127	16p	8-pin	20p
BD133	36p	BY164	48p	14-pin	15p

See our catalogue for our full range of transistors. 74 series I.C.'s bridges etc.

CAPACITORS

Multi-minimum
Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1 63 6p	68	6.3 6p	6p
1.5 63 6p	68	16 6p	6p
2.2 63 6p	68	63 10p	6p
3.3 63 6p	100	4 6p	6p
4.7 63 6p	100	10 6p	6p
6.8 40 6p	100	25 6p	10p
6.8 63 6p	100	40 6p	12p
10 25 6p	100	63 12p	10p
10 63 6p	150	6.3 8p	6p
15 16 6p	150	16 6p	6p
15 40 6p	150	25 8p	6p
15 63 6p	150	40 10p	6p
22 10 6p	150	63 12p	10p
22 25 6p	220	4 6p	10p
22 63 6p	220	10 6p	10p
33 6.3 6p	220	16 6p	10p
33 16 6p	220	25 10p	10p
33 40 6p	220	40 12p	10p
47 4 6p	220	63 18p	10p
47 10 6p	330	4 6p	22p
47 25 6p	330	10 6p	22p
47 40 6p	330	16 10p	33p
47 63 6p	330	63 22p	47p



PLUGS AND SOCKETS



DIN PLUGS	MAINS	R8 8 way chassis socket	Std 1/2" stereo plug
2 pin (1 flat) 8p	P360 3 pin 1.5A chassis plug w/ line socket. Per pair 24p	52p	Plastic 16p
3 pin 8p	BA 2190 3 pin 5A chassis plug 17p	PHONO	Screened 25p
4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 10p	SA 1862 Line socket for above 18p	Plug plastic 5p	Open mount socket 1" 10p; Moulded mono socket 1" with 2 break contacts 13p; Moulded stereo socket 1" with 3 break contacts 18p;
DIN Sockets	McMURDO	JACK	3.5mm. plug plastic 8p; screened 11p; open socket 8p.
2 pin 8p	RFR 8 way chassis socket 36p	Std. 1/2" mono plug Plastic 18p	
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 7p		Screened 17p	

WE KNOW YOU NEED IT!



The MES 1974 Catalogue is STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. **AVAILABLE VERY SOON**

You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our BIG VALUE discount vouchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!

OMNIUM GATHERUM

PP3. 6 etc. battery clip dual min.	8p
PP1. 9 etc. battery clip separate per pair	6p.
Pair crocodile clips 1 red, 1 black insulated sleeve.	7p
Solder Multicore 22swg 10 metre	20p
Silicone grease in special dispenser 20ml.	43p
Red neon 240V panel mounting sleeve.	25p
Lacing Cord Strong rayon coated PVC 25m.	43p
Panel fuse holders 20mm 20p; 1" 30p	
Transformers	
LT700 min. output transformer Pri 1-2k Ω Sec. 5 Ω 200mW	35p
Sub-min. Mains Transformer 6-0V 100mA	95p
12-0-12V 60mA	95p
Size: Both approx. 30 x 27 x 25mm	
Min. Mains Transformer (Size: 46 x 31 x 38mm) 0-12V 250mA. 0-12V 250mA	£1.35
Mains transformer MT3AT Pri. 200-220-240V, Sec. 12-15-20-24-30V	£2.48
Mains transformer MT306AT Pri. 200-220-240V, Sec. 0-15-20V 0-15-20V 1A	£2.95

POTENTIOMETERS

Rotary miniature carbon track 1" spindle	
Single gang Lin or Log 5k, 10k, 25k, 60k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p	
Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 38p	Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 23p
PRESETS	
Sub-miniature 0-1W Vert or Horiz 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p	
Wirewound 10%, 1W 1/2" spindle 10, 50, 100, 1000 34p; 250, 500, 1k, 5k 38p; 10k, 37p; 25k 40p; 50k 44p.	

KNOBS

All 1/2" shaft. Grip screw fixing				
K30/1 (13mm) 24p	K30/3 (17mm) 26p	K30/2 (13mm) 26p	BK12 32mm long, black pointer with white stripe 6p	K30/6 (32mm) 41p
F18 (26mm) with number ed skirt 21p	F12 (33mm) 21p	JK50 (34mm) 27p	OK4 (35mm) 141p	

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way, 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 24p	
Mains rotary DPDT 250V 2A 20p.	
Push to make non-locking 12p	Silb Miniature DPDT 8p
Toggle 250V 1-3A with ON/OFF plate 25p.	Sub-miniature toggle DPDT (12 x 12.5 x 14mm excl. toggle) 250V 3A 61p

VAT Please add 10% to the final total.

Post & packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to **MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. PHONE SOUTHELD (0702) 44101**

TWIS G.W. SMITH & CO (RADIO) LTD

AUDIOTRONIC MODEL ATM 1

Top value 1000 o.p.v. pocket multimeter. Ranges: 0/10/50/250/1000V. AC and DC. DC Current 0-1mA/100mA. Resistance 0/150K ohms. Decibels -10 to +24dB. Size 90 x 60 x 28mm. Complete with test leads. £2.95. Post 15p.



RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/1000V D.C. 2.5/10/50/250/1000V A.C. DC Current 100µA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K 3Ω. Complete with batteries, test leads, instructions and sturdy metal carrying case. £4.95. P. & P. 25p.



MODEL TE-200

20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V. D.C. 0/10/50/250/1,000V. A.C. 0/50 µA/250 mA. 0/50K/6 meg Ω. -20 to +62dB. £4.95. P. & P. 15p.



MODEL TE-300

30,000 O.P.V. Mirror scale, overload protection. 0/5/25/150/300/1,200V. D.C. 0/10/50/250/1,000V. A.C. 0/30µA/60mA/600mA/300mA/600mA. 0/5K/80K/600K/6 meg. ohm -20 to +61db. £7.50. P. & P. 15p.



UA312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 o.p.v. 0/3/1.5/7.5/30/60/150/300/600/900 V DC and 75mV. 0/3/1.5/7.5/30/60/150/300/600/900 V A.C. 0/200µA/1.5/15/60/150/600mA/1.5/6 AMP. D.C. 0/1/5/15/60/150/600mA/1.5/6 AMP. A.C. 0/200 Ω/3K/30K Ω. Accuracy DC 1%. AC 1-5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9.75. P. & P. 25p.



MODEL 500

30,000 O.P.V. with overload protection, mirror scale. 0/5/25/10/25/100/500/1,000V. D.C. 0/2/5/10/25/100/250/500/1,000V. A.C. 0/50µA/15/50/500mA. 12 amp. D.C. 0/60K/6 Meg. 0/50 Meg Ω. £10.50. Post paid. Leather Case £1.75.



MODEL CT-7080 EN

Giant 6" mirror scale. 20,000 o.p.v. 0/1/2.5/10/50/100/1,000V. D.C. 0/2.5/10/50/100/1,000V. A.C. 0/50µA/1/10/100/500mA/10 amp. D.C. 0/2K/200K/20 meg -20 to +50 dB. £13.95. Post 35p.



Model S-100TR MULTIMETER/TRANSISTOR TESTER

100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 V DC. 0/6/30/120/600V. A.C. 0/12/600µA/12/300mA/12 AMP. DC 0/10 K/1 M/100M/50K -20 to +50dB. 0-0.1 MF. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £14.95. 1/1 P. 25p.



KAMODEN 72 200 MULTITESTER

High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/5/10/3/3/30/120/600/1,200V D.C. 0/3/12/60/300/11,200V. A.C. 0/5µA/1.2mA/120mA/600mA/12A. D.C. 0/12A. A.C. -20 to +63dB. 0/2K/200K/2 meg/200 meg ohms. £16.95. Post 30p.



ALL PRICES ARE SUBJECT TO 10% VAT

TMK LAB TESTER

10,100 O.P.V. 6 1/2in Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K/10V A.C. D.C. Volts: 2.5/2.5/10/50/250/1,000V. A.C. Volts: 3/10/50/250/500/1,000V. D.C. Current: 10, 100µA, 100, 100mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100MEG Ω. Details: 10 to 49 db. Plastic Case with Carrying Handle. Size: 7 1/2in x 6 1/2in x 3 1/2in. £19.95. P. & P. 25p.



HIKIOI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 0/3/6/12/15/30/60/120/300/600/1,200V D.C. 1-5/3/6/12/30/60/150/300/600 1200 V. A.C. 15/30µA/3/6/30/60/150/300mA 6/12 AMP. DC. 2K/200K/2 Meg Ω. Neg. ohm -20 to +63dB. £14.95. P. & P. 20p.



370 WSTR MULTI-METER

Features A.C. current ranges. 20,000 o.p.v. 0/5/25/150/500/250/500 1000 V. D.C. 0/25/10/50/250/500/1000V A.C. 0/50µA/1/10/100mA/1/10 Amp D.C. 0/100mA/1/10 Amp AC 0/5K/50K/500K/5 meg/60 meg. -20 +62db. £17.50. P. & P. 25p.



KAMODEN HM 350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and DC current. Amplification factor of NPN, PNP, transistors, diodes, SCR's etc. 4" x 4" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12.50. Post 30p.



MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true A.C. beta in/out. Checks Ico. Checks diodes in/out. Checks SCR's, etc. Beta HI 1000 LO 2-50. Ico 0-5000µA. 220/240 V A.C. operation £17.50. Post 25p.



LB3 TRANSISTOR TESTER

Tests Ico and B. PNP/NPN. Operates from 9v battery. Complete with all instructions, etc. £3.95. P. & P. 20p.



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5v batteries. Complete with all instructions, etc. £4.50. P. & P. 20p.



TE-40 HIGH SENSITIVITY A.C. VOLT-METER

10 meg. input 10 ranges: 0.01/0.1/1/3/10/30/100/300V. R.M.S. 5cps-1.2 Mc/s. Decibels -40 to +40dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. £17.50. Carr. 25p.



TE-65 VALVE VOLTMETER

28 ranges D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V A.C. operation. Complete with probe and instructions. £17.50. P. & P. 30p. Additional probes available: R.F. £2.12; H.V. £2.50.



MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200KHz. Attenuator 0-114db. 0.1db step. Impedance 600 ohms. Max. input power 30dBm. Size 180 x 90 x 55mm. £12.50. Post 37p.



KAMODEN HM 720B F.T.E. O.M.

Input impedance 10 meg ohms. Ranges: 0/25/1/2.5/10/50/250/1000V. D.C. 0/1/2.5/10/50/250/1000V. D.C. 0/25mA/2.5/25/250 mA D.C. -20 to +62dB 0/5K/50K/500K/5meg 500meg ohms. £14.95. Post 30p.



TMK MODEL 117 P.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 4 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.3-1200V AC VOLTS 3-300V RMS. 0-9 800V P-P. DC CURRENT 12-12mA. Resistance up to 2000M ohm. Decibels -20 to +51dB. Complete with leads/instructions. £17.50. P. & P. 20p.



KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1000 Meg. ohms. 500 Volt. Battery operated. Wide range clear meter 4 1/2" x 4". Complete with carrying case, batteries, instructions. £19.95. Post 30p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18 x 20,000 Hz; Square 18 x 20,000 Hz Output max. 10 dB. (10 K ohms) Internal batteries Attractive 2-tone case 7 1/2" x 5" x 2". Price £17.50. Carr. 17p.



TO-3 PORTABLE OSCILLOSCOPE

3in. tube, Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1.5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5cps-800KHz. Input imp. 2 meg Ω 20pF. Time base: 6 ranges 10 cps-300 kHz. Synchronization. Internal/external. Illuminated scale 140 x 216 x 330 mm. Weight 15 1/2lb. 220/240V. A.C. Supplied brand new with handbook. £52.50. Carr. 60p.



CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz V RMS/mm. 1-25; HOR. AMP. Bandwidth 500KHz. Sensitivity at 100KHz. V RMS/mm. 3-25; Preset triggered sweep 1-3,000µsec.; free running 20-200,000Hz in nine ranges. Calibrator pulse 220 x 360 x 430mm. 115-230V. AC operation. £89.00. Carr. paid.



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 Mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 6in. x 4in. C.R.T. Calibrated triggered sweep from 2 µsec. to 100 mill-sec. per cm. Free running time base 50 cps-1 mc/s. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual £87. Carr. Paid.



TE-16A TRANSISTORISED SIGNAL GENERATOR

3 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 3 1/2 in. Complete with instructions and leads. £8.97. Post 25p.



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohms/Volt AC and DC. Accuracy 0.5% D.C. 1% AC. Scale length 165mm. 0/30/750µA 1.5/3/7.5/15/30/75/150/300/750mA 1.5/3/7.5/15/30/75/150/300/750V 1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out. Supplied complete with test leads, manual and test certificates. £49.00. Post 60p.



TMK MODEL TW-50K

46 ranges, mirror scale. 50K/Vol. D.C. 5K/Volt A.C. D.C.; Volts: 125, 25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +51-5db £28.50. P. & P. 17p.



MODEL TE.15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440Kcs-250Kcs in 6 coils. 500µA Meter. 9V battery operation. Size 180 x 80 x 40mm. £15.00. Post 20p.



ARF-300 AF/RF SIGNAL GENERATOR

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine / square 10v. P-P. RF 100 KHz to 200 MHz. Output 1v. maximum. Operation 220/240V. A.C. Complete with instructions and leads. £29.95. Post 60p.



TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20cps to 200 kc/s on 4 bands. Square: 20cps to 30 kc/s. Output impedance 6,000 ohms. 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. £17.50. Carr. 37p.



240° Wide Angle ImA Meters

MW 1.6-60mm square £3.97
MW 1-8 80mm square £4.97
P. & P. 15p.



POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. In. dia. shrou. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1000 ohms. £1-15 P. & P. 10p. 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.82 P. & P. 10p. 100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. £2.34. P. & P. 15p.



AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded. 80 W £2.35 P. & P. 18p
150 W £3.00 P. & P. 18p
300 W £4.00 P. & P. 23p
500 W £5.30 P. & P. 33p
1000 W £8.25 P. & P. 43p
1500 W £11.25 P. & P. 43p
2250 W £19.00 P. & P. 60p
6000 W £40.00 P. & P. 81



HIGH QUALITY CONSTRUCTION KITS
Appointed stockists at all branches
Compatible with comprehensive parts for
full instructions and circuit
Full guarantee
Post and packing 15p per kit

- AF20 Mono transistor amplifier £4.80
- AF30 Mono transistor pre-amplifier £2.61
- AF310 Mono amplifier, four tube for stereo £9.91
- ATS Automatic light control £7.58
- AT30 Photo light switching unit £5.10
- AT50 4000V Triac light dimmer speed control £4.80
- AT55 13000V Triac light dimmer speed control £5.70
- AT56 22000V Triac light dimmer speed control £6.90
- AT60 Psychronic light control speed control £7.80
- AT65 Psychronic light control 3 channel £14.55
- HF81 Medium power transistor unit £3.33
- HF75 FM transistor receiver £2.88
- HF310 FM tuner unit £15.81
- HF325 Deluxe FM tuner unit £24.12
- HF330 Stereo decoder for HF310 HF325 £9.96
- HF395 Aerial amplifier for AM FM bands £11.77
- CP310 Stereo pre-amp for use with AF310 £21.27
- GU30 Tremolo unit for guitars etc £7.50
- NT10 Power supply 100 mA 9V std. 12V unreg. 16.15
- NT200 Professional stabilized power supply 2 x 20 Volt 7.2 Amp £12.51
- NT305 Transistor converter 12 15V AC DC 9.5V 1.5V in 9V DC £4.50
- NT310 Transistor converter 240V AC to 24 18V DC £4.80
- NT315 Power supply 240V AC to 45 15V DC 500mA £9.57

NEW FROM JOSTY KIT!

'Amateur Electronics'—The professional book for the amateur—covers the subject from basic principles to advanced electronic techniques.

OUR PRICE £3.80, complete with circuit board for making the kite listed below.

- AE1 100mV output stage £1.65
- AE2 Pre-amplifier £1.28
- AE3 Diode-receiver £2.00
- AE4 Flasher £1.09
- AE5 Astable multivibrator £1.06
- AE6 Monostable multivibrator £1.02
- AE7 RC generator £1.06
- AE8 Base filter 99p
- AE9 Treble filter 99p
- AE10 OCIR filter 99p

230 VOLT A.C. 50 CYCLES RELAYS

3 sets of changeover contacts at 5 amp rating, 40p each, P. & P. 12p (100 lots \$80. Quantities available.



"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230V, 50/60 c/s. Variable output 0-280V.

MODEL S-260 GENERAL PURPOSE BENCH MOUNTING

- | | £ | P. & P. |
|---------|--------|---------|
| 1 Amp | 8-75 | 30p |
| 2-5 Amp | 10-00 | 35p |
| 5 Amp | 14-70 | 37p |
| 8 Amp | 19-85 | 50p |
| 10 Amp | 28-10 | 75p |
| 12 Amp | 29-50 | 100p |
| 20 Amp | 61-25 | 125p |
| 25 Amp | 72-50 | 130p |
| 40 Amp | 103-10 | 150p |



MODEL S-260B

- Panel Mounting, 30p
- 1 Amp 8-75
- 2-5 Amp 10-00 35p



Carriage and Packing Extra

REFLEX HORN SPEAKER RH.6



Built in driver unit. Impedance 16 ohm. Power rating 10 watt. Response 380-7000Hz. Approx. size 8" x 6". Weatherproof and shock proof.

OUR PRICE £4.97 P. & P. 30p.

BVD.5 VERNIER TUNING DIAL



Approx. 7-1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1 to 5. Scale width 4 1/2". Dial size 5 1/2" x 3 1/2". Overall size 7 1/2" x 4 1/2" x 1 1/2" deep including knob and coupling. 1 1/2" dia. shaft.

MP7 MIXER PREAMPLIFIER



5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mics: 3 x 3mV 50K, 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.

Our Price £8.97 P. & P. 20p

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

Type 5W.100 100 x 80 mm.

50µA	£4.15
50-0-50µA	£3.95
100µA	£3.95
100-0-100µA	£3.90
500µA	£3.70
1mA	£3.60
5mA	£3.60
10mA	£3.60
50V. D.C.	£3.60
300V. D.C.	£3.60
1 amp. D.C.	£3.60

5 amp. D.C. £3.60
10V. D.C. £3.70
VU Meter £4.80

Type SD.830 82.5mm x 110mm Fronts

10mA	£3.10
50µA	£3.10
100µA	£3.10
500µA	£3.10
1mA	£3.10
5 amp.	£3.10
10 amp.	£3.10
5V. D.C.	£3.10
10V. D.C.	£3.10
20V. D.C.	£3.10
50V. D.C.	£3.10
15V. A.C.	£3.80
300V. A.C.	£3.80
1mA	£3.10
5mA	£3.10
10mA	£3.10
50µA	£3.40
50-0-50µA	£3.40
100µA	£3.35
100-0-100µA	£3.35
200µA	£3.30
500µA	£3.15
1mA	£3.10
5mA	£3.10

Type SD.640 63.5mm x 85mm Fronts

50µA	£3.05
50-0-50µA	£3.05
100µA	£3.00
100-0-100µA	£3.00
200µA	£3.00
500µA	£3.00
1mA	£3.00
5mA	£3.00
10mA	£3.00
50µA	£3.00
50-0-50µA	£3.00
100µA	£3.00
100-0-100µA	£3.00
200µA	£3.00
500µA	£3.00
1mA	£3.00
5mA	£3.00
10mA	£3.00
50µA	£3.00
50-0-50µA	£3.00
100µA	£3.00
100-0-100µA	£3.00
200µA	£3.00
500µA	£3.00
1mA	£3.00
5mA	£3.00
10mA	£3.00
50µA	£3.00
50-0-50µA	£3.00
100µA	£3.00
100-0-100µA	£3.00
200µA	£3.00
500µA	£3.00
1mA	£3.00
5mA	£3.00
10mA	£3.00
50µA	£3.00
50-0-50µA	£3.00
100µA	£3.00
100-0-100µA	£3.00
200µA	£3.00
500µA	£3.00
1mA	£3.00
5mA	£3.00
10mA	£3.00
50µA	£3.00
50-0-50µA	£3.00
100µA	£3.00
100-0-100µA	£3.00
200µA	£3.00
500µA	£3.00
1mA	£3.00
5mA	£3.00
10mA</	

UR-1A RECEIVER



4 Bands covering 550 Kc/s-30 Mc/s. P.E.T. 8 Meter. Variable BFO for 88B. Built-in Speaker. Bandspread. Sensitivity Control. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

Our Price £25.00 Carr. 37p

TRIO 9R59DS RECEIVER



4 bands covering 550 Kc/s to 30 Mc/s continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. 88B-CW, ANL, Variable BFO. 8 meter. Sep. bandspread dial. IF frequency 440 kc/s, audio output 1-w. Variable RF and AF gain controls 115/250 v. A.C. with instruction manual.

Our Price £49.50 Carr. Paid

TRIO JR599 RECEIVER



9 wavebands covering 1.8-29.7MHz 144-146MHz and 10-60MHz V.W.V. 88B, CW, AM and FM. AF output more than 1 watt. 8 Meter. Squelch control. BFO. Variable RF and AF controls. 4-16 ohm output and phone jack. Power requirements 100/240v. AC. 12-14v. DC. Size 270 x 140 x 310mm.

Our Price £155.00 Carr. Paid

BELTEK W5400 CAR TRANSCIEVER



Solid state mobile transceiver for 12v DC neg. use. Transmits and Receives on any 12 of 28 channels between 144 and 146MHz. Power output 10w and 1w switchable. Controls: Volume/on/off, squelch channel selector Internal 3" speaker. Complete with dynamic mike, PTT switch, three sets of crystals for 144-146MHz, 144-60 MHz, 145-90MHz, mounting bracket and instructions. Size approx. 150 x 70 x 220mm.

Our Price £75.00 P & P 50p

TRIO JR310 SSB RECEIVER

Covers 3.5, 7, 14, 21, 28, 28.5 and 29.1 MHz bands and V.W.V. 15MHz. 88B, AM and CW. AF output more than 1 watt. Crystal controlled BFO for 88B. 8 meter. ANL etc. AC 110/120-220/240v. Size 330 x 179 x 310mm.

Our Price £75.00 Carr. Paid

UNR 30 RECEIVER



4 Bands covering 550 Kc/s-30 Mc/s B.F.O. Built-in Speaker 220/240 v. A.C. Brand new with instructions.

Our Price £15.75 Carr. 37p

LAFAYETTE HA-600 RECEIVER


General coverage 150-400 Kc/s, 550 Kc/s-30 Mc/s, P.E.T front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter Bandspread. RF Gain. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

Our Price £50.00 Carr. 50p

TRIO TR2000 TRANSCIEVER

Fully transistorised portable VHF Transciever. Will transmit and receive on 6 channels between 144-146MHz. 1 watt transmitter. 12v DC internal or external supply. Built in charger for ni-cad cells. Power/volume switch, squelch, control, channel selector, mike socket, carphone/external speaker socket. Complete with microphone, 144-48, 144-72 and 145-32 crystals. Size 134 x 55 x 180mm.

Our Price £79.50 Carr. Paid

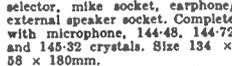

High quality T8515 88B/CW amateur band receiver covering 80, 40, 20, 15 and 10 metre bands with P8515 power supply and speaker unit. Transmits/receive frequency 3.5-29.7MHz. Output 1.5 watts. Power requirements 110-120/220-240v. AC. Sizes: T8515 300 x 185 x 340mm. P8515 200 x 168 x 340mm.

Our Price £120.00 Carr. Paid

SWR METER—Model SWR-3

Handy SWR Meter for transmitter antenna alignment, with built-in field strength meter. Accuracy: 5%. Impedance: 50. Indicator: 100µA DC, full scale 5 section collapsible antenna. Size: 145 x 50 x 60 mm.

Our Price £4.25 P & P 25p

AUDIOTRONIC AMR-900 GLOBAL AM/FM PORTABLE RADIO

10 wavebands covering AM: 535-1605 kHz, LW: 150-380 kHz, MB: 1-6 MHz, 4-00 MHz, SW1: 4-0-8 MHz, SW2: 8-0-1.6 MHz, SW3: 16-24 MHz, PBB1: 30-60 MHz, PBB2: 148-174 MHz, FM 88-108 MHz, AIR: 108-136 MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. AFC or FM. 6" x 4" speaker and personal earpiece. Battery/mains operation. Size: 845 x 133 x 306mm.

Our Price £36.00 P & P 50p.

SH628 STEREO HEADPHONES



Outstanding value. Soft ear-pads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

Our Price £1.87 P & P 30p

LHO2S STEREO HEADPHONES



Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft. cord and plug.

Our Price £1.97 P & P 30p

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,500 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.

Our Price £2.25 P & P 30p

BH.001 HEAD SET AND BOOM MICROPHONE



Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms.

Our Price £4.95 P & P 30p

DH02S STEREO HEADPHONES



Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug.

Our Price £2.25 P & P 30p

HAND-HELD 2-WAY WALKIE-TALKIES



SKYFON—100MW. £24.95 pair. PS02—2 CHANNEL 300MW. £32.50 pair. P1003—3 CHANNEL 1 Watt £71.95 pair. LICENCE REQUIRED FOR OPERATION IN U.K.

AUDIOTRONIC DIGITAL CLOCK RADIO ADC.1



Covers AM 540 - 1600 KHz. FM 88 - 108 MHz with AFC illuminated dial. 24 hour alarm setting. Wake up to the sound of music or loud buzzer. Sleep switch will automatically turn off radio etc. Internal speaker plus socket for earpiece or pillow speaker. AC 240v. Size 254 x 92 x 178mm. Complete with earpiece, and operating instructions.

Our Price £12.50 P & P 50p.

SPECIAL BARGAIN! PHONIC 10 TWO WAY SPEAKER SYSTEM

Matched pair of compact bookshelf speakers of unique design incorporating 2" high frequency tweeter and 6" woofer. 8 ohms impedance. 10 watts power handling. Size 348 x 228 x 110mm.

GWS SPECIAL PRICE £9.95 per pair. P & P 50p plus VAT.

AUDIOTRONIC AHA101 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. INPUTS: 5mV/100mV. OUTPUT: 50mV per channel.

Our Price £7.50 P & P 20p

AUDIOTRONIC AR.1000 SPORTSMAN AM/FM POLE BTRARADIO

5 wavebands covering AM 535 1065KHz FM 88-108MHz. AIR 108-136MHz. PB 147-174MHz. WB 162.5MHz. Large horizontal middle dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for FM and built in ferrite bar for AM. AFC. 3in. speaker. Earpiece socket. Size 152 x 79 x 210mm. Battery/mains operation.

Our Price £11.50 P & P 35p.

AUDIOTRONIC AMB.500 MULTIBAND RADIO

5 wavebands covering MW 535-1605KHz and FM 88-175MHz. All transistor. Battery or mains operation. Built in aerial and 8 section telescopic aerial.

Our Price £6.95 P & P 35p

BINATONE DS100 DIGITAL CLOCK

240v. mains operation. Compact case with large clear numbers for hours, minutes and seconds. Approx. size 61" x 3" x 31".

Our Price £4.50 P & P 30p.

AUDIOTRONIC ACP.8 8 TRACK CAR PLAYER

12v neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp, with speakers, mounting brackets and instructions.

Our Price £12.50 P & P 40p

AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 161" x 8" x 31". AC 200/250v



PROCESS FOUR

For use with semi-professional tape recorders. Freq. res. 30Hz-20KHz ± 2dB. OF tape monitoring. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

Our Price £50.00 P & P 50p

PROCESS TWO

For use with cassette and tape recorders. Freq. res. 30Hz-20KHz ± 2dB. OF tape monitoring. Switchable multiplex filter. Two Dooby calibration meters. 8/N better than 70dB. Supplied with test cassette or tape as required.

Our Price £34.50 P & P 50p

FM TUNER CHASSIS

6 TRANSISTOR HIGH QUALITY TUNER. 8 I Z E O N L Y stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108Kc/s. Ready built ready for use. Fantastic value for money.

Our Price £5.95 P & P 20p

A1018 FM TUNER

Specification as above chassis but complete in cabinet with on/off switch. Size 72" x 31" x 5".

Our Price £9.65 P & P 30p

AUDIOTRONIC AM/FM Portable Radio AR3000

4 wavebands covering FM 87 - 108 MHz, MW 510 - 1605 KHz, LW 145 - 285 KHz, SW 5.8 - 12.5 MHz. Push button wave change plus AFC and on/off. Thumb wheel tuning. Slider volume and tone controls. Earphone socket. Built-in and telescopic aerials. Car aerial socket. Battery/Mains operation.

Our Price £14.95 P & P 50p

AUDIOTRONIC ACR3500 CAR RADIO


Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

Our Price £6.50 P & P 50p



SAVE UP TO 33 1/3% OR MORE! GWS

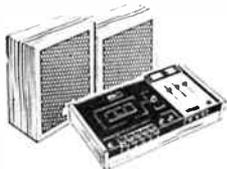SUPER AKAI HI-FI BARGAINS CS35 Stereo Cassette Recorder



For conventional or Chromium Dioxide tape. 4 track record/playback. Volume and tone controls. Frequency response 40-16kHz (using CrO2 tape), distortion better than 2%, wow and flutter better than 0.2% RMS. Complete with pair of matching Akai CS88 speakers.

Rec. Price £98-10 **OUR PRICE £56-50** P. & P. 50p
MICROPHONES (P. & P. 50p)
 ADM Dynamic (pair) £7-50

AUDIOTRONIC AHP-8D 8 Track Stereo Tape Deck

Can be used with most hi-fi amplifiers. Push button track selector and illuminated track indicator. Attractive cabinet with black and silver trim. Output level 750mV, AC 220/240v.

OUR PRICE £11-95 P. & P. 50p.

AUDIOTRONIC AHP-8A 8 Track Stereo Tape Player



Incorporates built in amplifiers giving 2 1/2 + 21 watts rms output. Push button track selector, illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. AC 220/240v.

OUR PRICE £17-25 P. & P. 50p.

SPECIAL PURCHASE! BSR 8 TRACK PLAYER CHASSIS

Famous BSR 8 track chassis as used in Model TD88 complete with silver and black escutcheon ready to fit into cabinet. Output 125mV. AC 240v. Overall size approx. 185 x 215 x 90mm.

OUR PRICE £8-95 P. & P. 50p.

AUDIOTRONIC ACD.660 Stereo Cassette Deck



A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter normal/chrome tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/Din line input sockets, 3.5mm mike input sockets etc. etc. Frequency response 100-8kHz (100-12kHz CrO2) 8/1-45dB. Crosstalk 46dB. Separation -35dB. Noise limiter -6dB at 10kHz. Complete with phono connecting leads.

OUR PRICE £39-50 Carr. & Ins. 50p

AUDIOTRONIC ACR.14 Battery Mains Cassette Recorder

Portable twin track mono recorder with automatic recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. AC 220/240v or 6V DC operation. Complete with remote control microphone, mains lead, earpiece and batteries.

OUR PRICE £10-50 P. & P. 50p.

PORTABLE CASSETTE RECORDER

Instant recording and playing. Piano key controls. Automatic level control. Built in speaker. Complete with remote control microphone, carrying case and shoulder strap.

OUR PRICE £8-50 P. & P. 50p.

AUDIOTRONIC LOW NOISE CASSETTES

Top Hi-Fi quality in library cases

TYPE	5	10	25
C60	£1-29	£2-53	£5-99
C90	£1-55	£2-68	£5-59
C120	£2-29	£4-48	£10-63

P. & P. 15p.
 Cassette Tape Head Cleaner 80p

3-STATION INTERCOM KE.630

Master and two sub stations. Can be used on desk or wall mounted. Complete with cable and batteries.

Our Price £5-25 P & P 50p

MINUTEMAN MM3 POCKET CALCULATOR

Size only 4 1/4" x 3" x 1". 8 digit display with overflow and error indicators. Floating decimal. Adds, subtracts, multiplies and divides. Chain and mixed calculations. Constant factor for series multiplication or division. Complete with batteries, instructions and case.

OUR PRICE £23-95 P. & P. 25p

MINUTEMAN MM3M

as above with addition of memory key, per cent key and a fixed or floating decimal. Complete with rechargeable batteries, AC adaptor, instructions and case.

OUR PRICE £28-50 P. & P. 25p

NEW! SINCLAIR CAMBRIDGE CALCULATOR

To build up your Complete kit of parts with step by step instructions to build a full specification calculator.

OUR PRICE £24-95 P. & P. 50p.

(Also available ready built Rec. Price £29-95)

OUR PRICE £27-20 P. & P. 25p

AUDIOTRONIC Stereo Headphones

LSH.80 Individual volume controls Stereo mono switch. 8 ohms. 40-19,000 Hz. £3-50 P & P 30p

LSH.80 Open back type. Individual tone and volume controls. 8 ohms. 30-20,000 Hz. £5-50 P & P 30p

LSH.40 Two way stereo system. Individual volume controls. 8 ohms. 20-20,000 Hz. £6-95 P & P 30p

LSH.60 3" speaker units. 8 ohms. 20-20,000 Hz. Complete with zipped carrying case. £8-50 P. & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has individual drive units. 4-32 ohms. 20-20,000 Hz. £9-95 P. & P. 30p

LSH.50 Electrostatic with self powered amplifier and control unit with head/phone/earpiece selector. 4-32 ohms. 20-24,000 Hz. £15-95 P. & P. 30p

RECORD DECKS

Carriage and Packing 50p

B.S.R. McDONALD
 C114 Mini £3-95
 C129 Mono £5-50
 C137 £7-00
 510/TPD1 £13-95
 610 £11-25
 610/TPD1 £21-15
 710 £22-80
 810 £28-30
 MP60 £28-25
 MP60/G800 £10-90
 MP60/TPD1 £13-20
 MP60/TPD2 £11-80
 MP60/TPD1 £11-80
 HT70/G800 £14-25
 HT70/TPD1 £16-55

CONNOISSEUR
 BD1 Kit £9-10
 B1 Chassis £11-85
 B2/SAU2/Chassis £22-70
 B2/SAU2/Plinth/Cover £28-20

GARRARD
 2025 T £8-85
 2025TC/K840A £9-25
 SP25 111 £9-25
 SP25111/G800 £10-95
 SP25/M75-6 £13-90
 AP76 £18-00
 868B £18-50
 SL86B £11-15
 SL72B £11-15
 SL93B £31-15
 401 £24-35
 ZERO 100A £24-10
 ZERO 100B £21-40
 ZERO 100 8B £27-00

GOLDRING
 G99 £22-50
 G101P/C £22-50
 GL29/2 £17-75
 GL72 £25-45
 GL72P £28-75
 GL75 £22-20
 GL75P £41-65
 GL78P/C £27-00
 GL85P/C £72-00

RECORD DECK PACKAGES

Complete units with Stereo cartridge ready wired in plinth cover.

GARRARD
 2025 TC/PTAHCD £11-35
 SP25 111/G800 £16-50
 SP25 111/M44E £17-95
 SP25 111/M44-7 £17-50
 SP25 111/M55E £18-50
 SP25 111 Module/M75-6 £19-45
 AP76/G800 £28-45
 AP76/M44E £27-70
 AP76/M44-7 £27-20
 AP76/M55E £28-30
 AP76/M75ED £24-90
 AP76/M75E £20-90
 AP76 Module/M75-6 £29-10
 868B Module/M75-6 £28-50
 AP96 Module/M75-6 £33-20
 ZERO 100B Module/M93E £44-15
 Zero 100B Module/M75-6 £24-20

B.S.R. McDONALD
 210/8C7M £7-40
 MP60/G800 £18-50
 MP60/TPD1/G800 £15-80
 MP60/M44-7 £17-50
 HT70/TPD1/G800 £19-20

GOLDRING
 GL72/G800 £24-90
 GL75/G800 £29-10
 GL75/G800E £41-55
 GL78/G800 £42-45
 GL78/G800E £44-95

New Sinclair Hi-Fi Modules

PROJECT 80
 Z40 £4-30
 Z80 £5-50
 STEREO 80 £9-50
 AFU £5-50
 P-5 £2-95
 P-28 £3-30
 P-28 £8-30
 P-28 Mains transformer £4-05
 Project 605 £20-97

DIGITAL CLOCK MECHANISM DT.55B



Features 24 hour alarm setting with built-in buzzer. On/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off TV, radio, light, etc. and with auto setting will switch on again when required. AC 240v. operation. Switch rating 250v. 3A.
OUR PRICE £5-95 P. & P. 30p.

EMI LOUDSPEAKERS

Model 350. 15" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7-25 each. P. & P. 37p.
 Model 400. 13" x 8" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £3-62 each. P. & P. 25p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 14 1/2" x 9" x 7 1/2". 8 ohms. 8 watt RMS. 16 watt peak. Complete with DIN lead.
Our Price £12-95 Carr. 50p

SPECIAL OFFER! FRUITSTRATED EXPORT ORDER PHILCO FORD MODEL 8248 MAINS TAPE RECORDER

2 track BSR deck with push button controls for easy operation. Tape counter and volume control. Complete with hand microphone. Direct recording lead, 1200' reel of tape & spare pool. 500/250V AC operation. Fully guaranteed. **OUR PRICE £17-50.** C & P 75p.

PHILCO FORD MODEL 8248 MAINS TAPE RECORDER

4 track. 2 speeds (3 1/2 i.p.s. & 1 1/2 i.p.s.). Piano key type controls. Tape counter, recording level meter, volume & tone controls etc. Complete with hand microphone, direct recording lead, 1800' of tape with spare pool. 200/250V AC operation fully guaranteed. **OUR PRICE £27-50.** C & P 75p.

PRICES SUBJECT TO 10% VAT

Order with confidence by Post-but remember to add 10% VAT to total value of order including carriage and packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY IN CAPITALS.

TELEPHONED ORDERS ACCEPTED FROM ACCESS and BARCLAYCARD HOLDERS

CREDIT TERMS FOR PERSONAL CALLERS (on sales of £50 and over).

All prices correct as 28-10-78 subject to change without notice E & OE

LONDON'S LARGEST STOCKS INCLUDING PRODUCTS BY-

- ARMSTRONG
- CAMBRIDGE
- KEF LUX NIKKO
- SANSUI/SANVO
- SONY/TEAC
- TRANSCRIPTORS
- TRIO UHER
- YAMAHA

Prices on request or send S.A.E. for full Discount List

G.W.S.MITH & CO (RADIO) LTD

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES


- | | | |
|---|---|---|
| CENTRAL LONDON
257/6, Tottenham Court Rd, W.1. Tel: 01-580 0670
10, Tottenham Court Rd, W.1. Tel: 01-637 2222
27, Tottenham Court Rd, W.1. Tel: 01-636 3715
21, Old Compton Street, W.1. Tel: 01-580 3739
1, Little Street, W.C.2. Tel: 01-437 9369
34, Little Street, W.C.2. Tel: 01-437 8204
118, Edgware Road, W.2. Tel: 01-723 9789
193, Edgware Road, W.2. Tel: 01-723 6211 | 311, Edgware Road, W.2. Tel: 01-282 0387
282, Edgware Road, W.2. Tel: 01-723 4194
152/3, Fleet Street, E.C.4. Tel: 01-353 2833
378, Harrow Road, W.9. Tel: 01-286 9530 | 86, South Street, Romford. Tel: Romford 20218
1046, Whitgift Centre, Croydon. Tel: 01-681 3027
27, Eden Street, Kingston. Tel: 01-546 7845
32, Hill Street, Richmond. Tel: 01-948 1441 |
|---|---|---|

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

HEAD OFFICE and MAIL ORDER DEPARTMENT
 UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JU

TELEPHONE 01-205 3735

DABAR MN3 MIXER KIT

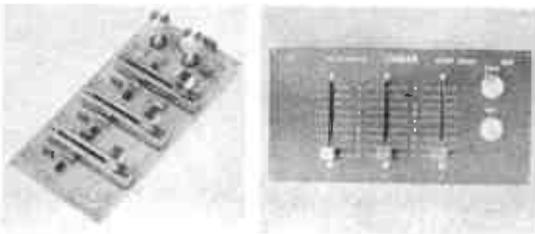

INTRODUCING THE NEW DABAR MINI THREE CHANNEL MIXER KIT WITH THE FOLLOWING FEATURES:

- ★ Three inputs easily adjustable to suit users input requirements, e.g., Mic., Tape, Disc., etc.
- ★ Uses advanced design with five integrated circuits.
- ★ Slider fader volume controls mount directly on P.C. board.
- ★ Full range bass and treble controls.
- ★ Guaranteed top grade components with fibreglass printed circuit board, ready-drilled and tinned.
- ★ Battery operated (2 x PP3) not supplied with kit.
- ★ Easy to follow assembly instructions (available separately 25p).
- ★ Attractive ready punched fascia plate, available at extra cost, gives that professional finish to the unit.
- ★ Size: 9.5" x 4.8" x 2".

PRICE: KIT ONLY £11.00
 FACIA PLATE £1.50
 MANUAL AND ASSEMBLY INSTRUCTIONS 25p
 AVAILABLE READY BUILT WITH FACIA £15.00

ALL PRICES INCLUDE V.A.T. & POSTAGE IN U.K.
 S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

98, LICHFIELD STREET, WALSALL, STAFFS, WS1 1UZ.

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88—108Mcs, with circuit diagram. £2.30p.

P-C BOARDS (not computer panels)

- 1 off 6 transistors single wave band
- 1 off 4 transistor audio
- 1 off 3 transistor £1.60 the three.

10 COMPUTER PANELS packed with components including one panel with 2 Power Transistors. £1.00.

LIGHT DEPENDENT RESISTORS (RCA sq3536) 30p each, 4 for £1.00.

All Transistor STEREOGRAM CHASSIS. Medium, Long and VHF/FM. 3 Watts per channel S/M rating. With circuit service manual. Less tuning scale which can be obtained from well known British manufacturer . . . £20.

Colour Translator panels, as used on well known British E.V.R. Teleplayer. All new panels and components. Type and contents of transistors listed below. Each panel £3.50 each.

X605..14 off BC148. 2 RCA ca3054(ic). 1 crystal 4.433618MHz. Z607..12 off BC148. 1 BC158. 1 BC108. 1 RCA ca3046. 1 RCA ca3045(ic).

Z608..23 off BC148. 2 BC158. Z612..12 off ME4102. 2 BC251B. 1 BFY50.

CRYSTAL CALIBRATOR (Second Hand) No. 10 crystal controlled heterodyne wave-meter covering 500KHz—10MHz (harmonics up to 30MHz) power required 300V DC 15mA. 12V 0.3A DC. Test equipment for 62T M/RC. £2.50 each.

WIRE-WOUND RESISTORS. Our selection of mixed Ohms and Watts. 25 for £1.50, 50 for £2.50, parcel of 1,000 £30.00.

ALL ITEMS INCLUDE VAT

All items post paid in GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.



The Pictorial Method

BASIC ELECTRICITY (5 vols)

BASIC ELECTRONICS (6 vols)

BASIC TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

Amazed to see so much information and in such a self-explanatory way.

S.F. Huddersfield

Your valuable assistance has enabled me to find a good position as a Radio and T.V. Engineer.

D.S. Bristol

They live up to your publicity in every way.

C.L.L. London

"BEST I HAVE EVER SET EYES ON", shall definitely recommend to friends.

F.C. Fife.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

- BASIC ELECTRICITY 5 parts £4.50
- BASIC ELECTRONICS 6 parts £5.40
- BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.


NAME
 BLOCK LETTERS
 FULL POSTAL.....
 ADDRESS

POST NOW FOR THIS OFFER!

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 10 Transistors
- ★ 3 1/2" Loudspeaker
- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.
- ★ Parts Price List and Plans 40p (Free with parts).

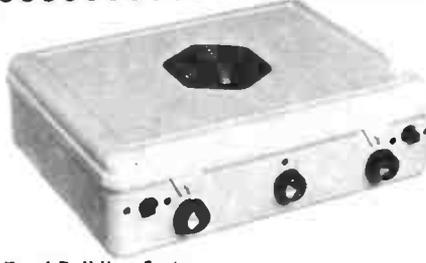

Total Building Costs
£7-23 P P & Ins. 44p
(Overseas P & P £1-85)
(+ 10% VAT 72p)

Components include 24 Resistors, 21 Capacitors, 10 Transistors, 3 1/2" loudspeaker, Mica Baseboard, 3 12-way connectors, 2 Volume controls, 2 Slider Switches, 1 Tuning Condenser, 3 Knobs, Ready Wound MW/LW/FW Coils, Ferrite Rod, 6 1/2 yards of wir, 1 yard of sleeving etc. Plans 50p.

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT



Nine Transistors, 9 Tunable wavebands as Roamer Ten Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans 30p (Free with parts).

Total Building Costs **£6-95** P P & Ins. 44p
(Overseas P & P £1-85)
(+ 10% VAT 60p)

POCKET FIVE

3 Tunable wavebands. M.W. L.W. and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List 15p (Free with parts).



Total Building Costs **£2-28** P P & Ins. 26p
(Overseas P & P £1-25)
(+10% VAT 22p)



TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts).


Total Building Costs **£2-50** P P & Ins. 26p
(+10% VAT 25p)

(Overseas P & P £1-25)

TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

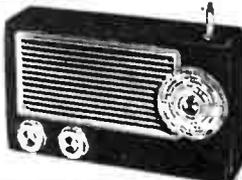Total building costs **£4-48** P P & Ins. 33p
(+ 10% VAT 44p)
(Overseas P & P £1-25)



ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 Transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Total building P P & Ins. 31p
Size 9 x 5 1/2 x 2 1/2 in. approx. Plans and parts price list 25p (FREE with parts).

Total building costs **£3-98** (Overseas P & P £1-85)
(+ 10% VAT 39p)

NEW Everyday Series

Build this exciting New series of designs

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod 3" aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£2-73** P P & Ins. 30p
(+ 10% VAT 27p)
(Overseas P & P £1-25)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£3-60** P P & Ins. 30p
(+ 10% VAT 36p)
(Overseas P & P £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Plans 20p. Free with parts. Overseas P & P £1-05.

Total Building Costs **£4-08** P P & Ins. 31p
(Overseas P & P £1-85)
(+ 10% VAT 40p)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4 1/2 in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

Total building costs **£6-98** P P & Ins. 47p
(Overseas P & P £1-85)
(+ 10% VAT 69p)




ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

10 Transistors, 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Latest 4" x 8 watt ferrite magnet loudspeaker.

Built in Ferrite Rod Aerial for MW/LW. Retractable chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

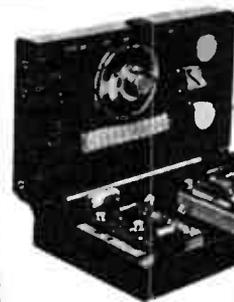Total building costs **£8-50** P P & Ins. 52p
(Overseas P & P £1-85)
(+ 10% VAT 85p)



"EDU-KIT"

Build Radios, Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

Total building costs **£5-50** P P & Ins. 33p
(Overseas P & P £1-85)
(+ 10% VAT 53p)

RADIO EXCHANGE LTD

★ Callers side entrance Lavells' shop.
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
Tel.: 0234 52867. Reg. No. 788372.

I enclose £..... for

Name

Address (Dept. PW23.)

NO EXTRAS
ALL PRICES INC. VAT
FREE! P. & P.

AMPLIFIERS

Keletron KBA 700 7+7 watt	23-00
MK II KBA 150 15+15 watt	32-20
Triplone MK II HI-FI 77+7 watt	27-50
MK II HI-FI 1818 18+18 watt	35-00
Teleton MK IISA Q3078+8 watt	27-00
EMI 1515 15+15 watt	37-00
EMI RA210	32-00
RA310	44-00
Rotel Tuner/ Amp. RX150A	51-00

RECORD DECKS

Garrard 2025TC/STAH/C/G	11-00
SP25 Mk. III	11-00
BSR MP60/8X5H	11-00
Connoisseur BD1 KH	11-00
BD1 Chassis	23-50
SAU2 Pick-up Arm	12-25
SCU1 Cartridge	4-95

RECORD DECK PACKAGES

Garrard SP25 Mk. III/G800 C. & P.	19-50
AP76/G800 C. & P.	30-00

PLINTH & COVER FOR GARRARD

SP25/2025TC	3-95
-------------	------

SPEAKER BARGAINS

EMI 13" x 8" 3, 8 or 15 ohm	
Plain	2-35
with Co-Axial Tweeter	2-50
Twin Tweeter	3-95
Type 350 8 ohm, 20 watt	8-50
6 1/2" 8 ohm, 10 watt	6-50
8" 8 ohm, 10 watt	3-90
12" 8 ohm, 20 watt	5-75
8" x 5" C/Mag. 5 watt	1-40
8" x 5" Dualcone 8 ohm	2-70

FANE 7" x 4" 3 or 8 ohm	1-15
8" Dualcone 8 ohm	2-50
CELESTION 8" 15 ohm	1-75
ADABTRA 10" 8 or 15 ohm	
10 watt	2-95
BAKER GROUP 25	
12" 8 or 15 ohm, 25 watt	6-50
5" 8 ohm, 5 watt C/Mag.	9-00
2 1/2" 8 ohm or 64 ohm	-65
SELECTION OF GOODMAN AND WHARFEDALE SPEAKERS ALSO AVAILABLE.	
KIT FORM CABINETS - TEAK VENEER	
12 x 12 x 6 with 8", 8" x 5", or 6 1/2" and 3 1/2" cutout	2-75
17 x 10 x 6 with 8" or 13" x 8" cutout	3-50
18 x 11 x 9 with 13" x 8" cutout for EMI 350	4-60
TWEETER & CROSSOVER	
EMI 3 1/2" 3 or 8 ohm C/Mag.	1-10
Cone Tweeter 8 or 15 ohm, 10 watt	2-00
Cone Tweeter 8 ohm, 3 watt	1-10
Horn Tweeter 8 ohm, 20 watt	3-60
Dome Tweeter 8 ohm, 30 watt	4-00
Crossovers CN23 (8 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-10
CARTRIDGES	
ACOS GP91/2SC or GP91/3SC Stereo comp.	1-05
GP93/1 Stereo crys.	1-35
GP94/1 Stereo crys.	1-75
GP93/1	1-35
GP96/1	1-75
GP101	7-50
SONOTONE	
9TAHC Stereo ceramic, diam.	1-80
9TAHC/G 8 1/2" dia. stereo cer. diam.	1-80
19-T1 Stereo crystal	1-35
BSR 8C5M Stereo ceramic	2-25
SX5H Stereo crystal	1-65
SX5M Stereo crystal	1-65
X5H Mono/stereo	1-30

X5M Mono/stereo	1-30
GOLDRING G800	2-85
G850	2-95
STYLI For Above Cartridges	
Sapphire	3-30
1 1/2" Diamond	1-25
GOLDRING G800 G850	1-95
MICROPHONES	
CM20 Crystal Hand	6-00
CM70 Planet stick metal, switch crystal	1-70
DM160 Dynamic uni-dir, hall metal	4-00
UD130 50K/600 ohm, uni-dir, ball metal	4-85
TW206	5-90
CONDENSER MIKE 600 ohm, uni-dir.	7-90
Cassette STICK MIKE with R. Control on/off switch (2.5 & 3.5 mm J/1/4")	1-45
MIKE MIXERS Mono.	4-10
Mono/stereo de luxe	5-50
CASSETTES	
Type Low Pin. Phil. Mem. Am. noise nacle lips orex pep	
C45	50p
C60	35p 40p 50p 55p 55p
C90	45p 55p 69p 75p 75p
C120	55p 75p 105p 110p 110p
Cassette Head Cleaner	4-45
BIB Stereo Test Cassette	1-65
AMPPEX Head Cleaner De-magnetiser	1-85
PLASTIC LIBRARY CASES for 5" Reels 25p. 5 1/2" Reels 25p. 7" Reels 30p.	
CASSETTE CASES	12p
TAPES Std. L.P. D.P.	
5"	55p 65p 80p
3 1/2"	65p 75p 81-00
7 1/2"	81-00
AKAI TAPE DECK	
4000DS Tape	73-50
GX40D Cassette	64-95
CS35 + CS58	79-95

BARCLAYCARD



Credit Terms for Callers

BUDGET SYSTEMS
BUSH Stereo System with Independent Volume Bass and Treble controls on each Speaker for optimum reproduction. Using GARRARD 2025TC Auto Change Deck in deluxe teak plinth and cover.
Today's Value £49.50.
OUR PRICE £27.50
+£1.50 p. & p.
12 months Guarantee by Maker.
THIS IS A BARGAIN NOT TO BE MISSED!

HEADPHONES		£
AMSTRAD HP95A	700	4-95
ROTEL	430	4-20
	630	4-90
	500	4-50
	700	5-95
AKAI	ASE 115	5-75
	ASE 20	7-95
	ASE 22	9-25
KOSS	K711 (Black or Red)	9-95
	K6	11-95
	K6LC (with Vol. control)	13-25
	K0727B	15-75
	K0747	19-50
	HVI	19-50
	PRO4AA	28-95
	PRO5LC	28-75
	ES90	42-75
LEESON ELECTROSTATIC		19-50
Mono/stereo super deluxe 6-16Ω		2-75
Headphone Adaptor		2-50
Curly Ex. Lead 20ft.		1-10
IN-CAR ENTERTAINMENT SECTION		
Car Cassette Stereo Player and Two Speakers		20-95
Car 8-track Stereo Player and Two Speakers		16-50
SHIBUYA 8-track Player/Main/Car detachable with 2 separate sets of Speakers		89-95
Pair of Car Stereo Speakers		3-85
Pair of Car Stereo Speakers (Door Mounting)		3-95

NEWMART ELECTRONICS

ALL MERCHANDISE FULLY GUARANTEED

MAIL ORDER DEPT. (PW/12)

BELMONT STREET MONTON, ECCLES MANCHESTER
Tel. 061-789 5268

CALLERS WELCOME AT OUR BRANCHES

Manchester	Liverpool
30-32 Shudehill	15 Whitechapel
061-832 7710	051-236 0738
Leeds	Sheffield
4 New Market St.	20 Plinstone St.
0532 42708	0742 79308

Stove Enamelled STEEL CABINET



List price £6.87
OUR PRICE £5.50
incl. V.A.T. Carriage 44p

With 48 see-through Drawers Ideal for the Radio Constructor
As supplied by us to SCHOOLS, TECHNICAL COLLEGES, HOSPITALS, SHOPS and industry throughout the country. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at a small extra charge to enable each drawer to be sub-divided into six compartments. See-through drawers allow swift selection of contents at a glance. A really first-class time and space saving unit. Size of cabinet 21 1/2" x 11 1/2" x 6 1/2", size of drawers 6 1/2" x 2 1/2" x 1 1/2".
Callers welcome.

SEND FOR FREE ILLUSTRATED LEAFLETS

Trade Aids 111 Chiltern Drive Surbiton Surrey (100 yards from Berrylands Railway Station) 01 399 4383

TRANSFORMERS

DOUGLAS GUARANTEED
Prices include P. & P. and 10% VAT

12 or 24 Volts		Ref. No.	Price		
Output V. & Amps.					
12V x 2.250mA x 2	MT111CS*	21-32	21-32		
12V x 2.600mA x 2	MT112CS*	21-35	21-35		
12V x 2.1A x 2	MT11CT*	22-17	22-17		
12V x 2.2A x 2	MT18CT	22-63	22-63		
12V x 2.3A x 2	MT70AT	23-40	23-40		
12V x 2.4A x 2	MT108AT	23-86	23-86		
12V x 2.5A x 2	MT72AT	24-48	24-48		
30 Volts. All tapped at 0.12-15-20-30V.					
Output	Ref. No.	Price	Output	Ref. No.	Price
500mA	MT112CT*	21-43	4A	MT21AT	24-61
1A	MT79CT*	22-22	5A	MT51AT	25-21
2A	MT 3AT	23-22	8A	MT88AT	28-33
3A	MT20AT	23-65	10A	MT89AT	29-68
50 Volts. All tapped at 0.19-25-33-40-50V					
500mA	MT102AT*	22-07	3A	MT103AT	25-40
1A	MT103AT*	23-00	4A	MT106AT	26-79
2A	MT104AT	24-01	5A	MT107AT	29-69
60 Volts. All tapped at 0.24-30-40-48-60V.					
500mA	MT124AT	22-38	3A	MT127AT	24-36
1A	MT126AT	23-28	2A	MT125AT	26-41
AUTO-WOUND RANGE					
Power	Winding tapped at	Ref. No.	Price		
20VA	0-115-210-240	XMT113CT	21-28		
75VA		XMT64AT	22-51		
150VA	0-115-200-220-240	XMT4AT	23-06		
200VA		XMT65AT	23-65		
400V. Output at 50Hz.					
C-D Ignition System by R. M. Marston, Esq., Wireless World.					
Reference IT3AT					
23-00					
EQUIPMENT RANGE					
Sec. Output (r.m.s.)	Ref. No.	Price			
3-0-3V	200mA MT238CS*	21-41			
9-0-9	100mA MT13CS*	21-36			
12-0-12	50mA MT239CS*	21-41			
20-0-20	30mA MT241CS*	21-41			
0-20 x 2	300mA x 2 MT207CT**	21-87			
0-8-9 x 2	500mA x 2 MT205AT*	22-95			
0-15-20 x 2	500mA x 2 MT203AT*	23-38			
0-15-27 x 2	500mA x 2 MT204AT*	23-38			
0-15-27 x 2	1A x 2 MT221AT*	21-74			
AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. splices; * with interwinding screen; ** untapped 240 primary; † tapped at 210-240V.; other primaries tapped at 200-220-240V.					
OVER 200 TYPES IN STOCK through Agents or Direct. Please send for lists.					
DOUGLAS ELECTRONIC INDUSTRIES LTD., Direct Sales Dept. F.W., Thames Street, LOUGH, Lincs. LN11 7AD					

A DEXTER DIMMASWITCH



ALLOWS COMPLETE LIGHTING CONTROL
The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V. 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression. 600 watt £3.52 Kit form £2.97 300 watt £2.97 Kit form £2.42
All plus 12p post and packing
Prices include VAT. Please send c.w.o. to.

DEXTER & COMPANY
15 ULVER HOUSE
9 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883
AS SUPPLIED TO HM GOVERNMENT DEPARTMENTS, HOSPITALS, LOCAL AUTHORITIES, ETC

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	6p BCY58	18p CA3035	£1 37 NKT406	89p 1N4004	7p 2N6027(O13T1)	
AC107	50p BCY70	15p CA3043	£1 55 NKT713	29p 1N4005	45p	
AC126	20p BCY71	26p CA3044	£1 28 NKT773	25p 1N4006	8p 3N84	
AC127	25p BCY72	14p CA3046	70p NKT781	29p 1N4007	8p 3N128	
AC128	24p BC124	75p CA3048	£2 11 NTG010	40p 1N4148	40p 3N140	
AC128/AC176	BO131	40p CA3052	£1 62 OA10	40p 1N5400	14p 3N152	
	44p BO132	40p CA3065	£1 28 OA47	8p 1N5404	18p 3015F	
AC151	20p BD131 1/2	80p CA3088E	£1 24 OA79	8p 1N5408	25p 3015G	
AC152	25p BDY20	91p CA3089E	£1 96 OA90	4p 7400	4p 7400	
AC153	26p BF115	23p CA3090O	£4 23 OA91	5p 1S920	7p 7401	
AC176	20p BF163	35p CO4001AE	5p OA95	5p 1S940	8p 7402	
AC153/176K	32p BF164	25p CO4009AE	£1 18 OA200	6p 2N4004	23p 7403	
AC187K	17p BF173	29p CO4011AE	5p OA202	7p 2N6996	15p 7404	
AC188K	23p BF177	35p CO4012AE	54p OC25	45p 2N697	17p 7405	
AC187/188K	40p BF178	31p CO4013AE	£1 11 OC28	78p 2N698	30p 7408	
ACV17	27p BF180	35p CO4015AE	£2 92 OC29	79p 2N706	10p 7409	
ACV18	20p BF194	15p CO4017AE	£2 92 OC35	86p 2N706A	12p 7410	
ACV19	20p BF195	15p CO4018AE	£2 92 OC36	25p 2N708	20p 7413	
ACV20	20p BF196	15p CO4020AE	£1 25 OC41	6p 2N911	50p 7420	
ACV21	19p BF200	35p CO4024AE	£2 09 OC42	40p 2N914	20p 7425	
ACV22	10p BF254	14p CR1051C	54p OC44	20p 2N918	42p 7430	
AO140	60p BF255	15p CR1401C	71p OC45	20p 2N929	25p 7440	
AD149	60p BFX13	25p CRS3/05AF	OC71	20p 2N930	28p 7442	
AD161	44p BFX29	32p	£1 08 OC72	20p 2N1131	24p 7443	
AO162	44p BFX34	25p CRS3 40AF	OC75	25p 2N1132	24p 7443	
AO181/162	44p BFX85	34p	£1 53 OC76	25p 2N1302	17p 7445	
AF106	32p BFX86	25p C26	17p OC77	40p 2N1303	17p 7446	
AF114	27p BFX87	30p O10 (NTG010)	OC81	20p 2N1304	24p 7447	
AF115	27p BFX88	24p	40p OC81O	20p 2N1305	24p 7450	
AF116	25p BFY50	22p IRT84	£2 90 OC83	23p 2N1306	30p 7451	
AF117	25p BFY51	19p IRT260	95p OC84	25p 2N1307	30p 7453	
AF118	44p BFY52	20p IRC20	46p OC139	25p 2N1308	30p 7453	
AF124	25p BFY53	17p JA424	£2 08 OC170	22p 2N1309	34p 7460	
AF125	24p BFY90	£1 20 LIC709C5	42p OC171	30p 2N1559 (CR1)	71p 7470	
AF126	24p BP101	£1 40 LIC709C8	42p OC172	42p 401C	71p 7472	
AF129	47p BPX66	£1 50 LIC723C5	£1 02 ORP12	50p 2N1711	15p 7473	
AF186	40p BRY39	45p LIC723C14	£1 02 ORP60	50p 2N1711	15p 7474	
AF239	52p BSX19	16p LIC741C5	£1 45 ORP61	50p 2N1893	54p 7475	
AF279	58p BSX20	18p LIC741C8	34p ORP69	50p 2N218A	33p 7476	
ASV26	20p BSX21	20p MC1303L	£1 75 PN70	10p 2N218A	44p 7480	
ASV27	20p BSX27	20p MC1305P	£2 80 PN71	10p 2N219	38p 7482	
ASV28	22p BSX29	25p MC1307P	£1 65 PN107	8p 2N219A	53p 7483	
ASV29	30p BSX95A	12p MC1310P	£2 95 PN108	8p 2N2368	17p 7486	
BA138	15p BY100	20p MC1330P	80p PN109	8p 2N2369	17p 7490	
BB103	20p BY127	22p MC1352P	£2 90 PN3819(2N3819)	2N2369A	17p 7491A	
BB104	34p BTY79/400R	20p MC1466L	£4 20 SC1460	£2 90 2N2646	45p 7493	
BB105	28p	80p MC1468L	£2 88 SC1460	20p 2N2904	44p 7494	
BC107	13p BT106	£1 20 MFC4000B	65p ST2	20p 2N2904A	49p 7495	
BC107/BC177	BZY88C3V3	10p MC4024P	£2 20 SL103A	60p 2N2905A	75p 74100	
BC108	33p BZY88C3V6	10p MC4044P	£2 20 SL403A (Rect)	2N2905	18p 74107	
BC109/BC178	BZY88C4V3	10p MFC6030	£1 63	60p 2N2924	22p 74121	
BC109	13p BZY88C4V7	10p MFC6040	£1 15 SL803A	£1 12 2N2925	22p 74121	
BC109/BC179	BZY88C5V1	10p MFC8010	£1 24 TAA293	97p 2N2926	10p 74141	
	BZY88C5V6	10p MFC8040	£1 24 TAA310	£1 25 2N3053	24p 74150	
	BZY88C6V2	10p MJE371	68p TAA320	75p 2N3054	65p 74151	
BC109C	14p BZY88C6V8	10p MJE520	85p TAA861	45p 2N3055	65p 74153	
BC117	15p BZY88C7V3	10p MJE521	82p TAO100	£1 97 2N3228	£1 10 74154	
BC140	12p BZY88C8V5	10p MJE2955	£6p TIL112	£1 97 2N3391A	29p 74155	
BC147	12p BZY88C9V1	10p MJC3055	86p TIL209	£2 00 2N3325	£1 04 74156	
BC148	11p BZY88C10V	10p MJ480	97p TIL209	97p 2N3702	14p 74190	
BC149	12p BZY88C11V	10p MJ481	£1 25 TIP31A	60p 2N3703	12p 74191	
BC157	13p BZY88C12V	10p MJ491	£1 35 TIP32A	70p 2N3704	12p 74192	
BC158	12p BZY88C13V	10p MJ802	£4 12 TIP41A	85p 2N3705	12p 74193	
BC159	13p BZY88C15V	10p MJ802/MJ4502	TIP42A	£1 00 2N3706	12p 74196	
BC147/157	BZY88C16V	10p MJ900	£8 56 TIS43	30p 2N3707	12p 74197	
BC148/158	BZY88C20V	10p MJ1000	£1 80 VA10661	15p 2N3708	12p 40280	
BC149/159	BZY88C21V	10p MJ1000	£1 50 VA103	15p 2N3709	12p 40309	
BC167	11p BZY88C22V	10p MJ4502	£4 44 VA1040	15p 2N3710	12p 40310	
BC168	10p BZY88C24V	10p MPF102	37p VA1077	15p 2N3711	12p 40311	
BC169C	BZY88C30V	10p MPF103(2N5457)	W005	30p 2N3713	£2 50 40312	
BC177	29p BZX61C7V5	28p	49p W01	31p 2N3819	28p 40320	
BC178	18p BZX61C8V2	28p	MPF104(2N5458)	W02	60p 40360	
BC179	20p BZX61C9V1	28p	MPF105(2N5459)	W06	20p 40361	
BC182	14p BZX61C10V	28p	46p W08	44p 2N3866	£1 10 40406	
BC182L	14p BZX61C11V	28p	NKT0033	96p ZTX107	12p 2N3904	28p 40407
BC183	15p BZX61C12V	28p	NKT211	25p ZTX108	11p 2N3906	28p 40408
BC183L	15p BZX61C13V	28p	NKT212	25p ZTX300	13p 2N4058	15p 40409
BC184	17p BZX61C15V	28p	NKT213	25p ZTX303	18p 2N4058	13p 40410
BC184L	18p BZX61C16V	28p	NKT216	46p ZTX303	15p 2N4061	13p 40410
BC212	16p BZX61C18V	28p	NKT217	50p ZTX304	23p 2N4062	13p 40438A
BC212L	16p BZX61C20V	28p	NKT218	25p ZTX314	11p 2N4441	70p 40511
BC238	10p BZX61C22V	28p	NKT223	27p ZTX320	30p 2N4444	£2 20 40575
BC238/308	20p BZX61C24V	28p	NKT221	18p ZTX330	18p 2N4871	44p 40576
BC257	11p BZX61C27V	28p	NKT274	18p ZTX500	14p 2N4990	66p 40600
BC258	10p BZX61C30V	28p	£2 03 NKT275	20p ZTX501	15p 2N4991	48p 40601
BC259	12p CA3004	£2 03 NKT279A	20p ZTX502	18p 2N5245	45p 40602	
BC307	12p CA3005	£1 35 NKT281	29p ZTX503	17p 2N5457(MPF103)	40p 603	
BC308	10p CA3011	80p NKT351	75p ZTX504	45p	49p 40669	
BCY30	25p CA3013	£1 17 NKT401	78p ZTX505	4p 2N5458(MPF104)	40p 673	
BCY31	48p CA3014	£1 37 NKT402	83p ZTX506	20p	49p 40739	
BCY32	50p CA3018	72p NKT403	83p NKT403	4p 2N5459(MPF105)	46p	
BCY33	20p CA3018A	83p NKT404	85p NKT404	5p	46p	
BCY34	25p CA3020	£1 39 NKT405	79p NKT405	2p 2N5777	45p	
BCY38	30p CA3028A					

CAPACITORS ELECTROLYTIC AXIALLEADS

Mld	Working Voltage	Price	Mld	Working Voltage	Price
1 0	100v	10p	100	16v	9p
1 0	100v	8p	100	25v	9p
2 2	25v	10p	100	40v	10p
2 2	63v	8p	100	63v	13p
4 7	40v	8p	220	25v	11p
10	25v	8p	220	40v	12p
20	63v	9p	1000	25v	14p
22	40v	9p	1000	25v	21p
47	25v	9p	2200	16v	39p
47	40v	9p	4700	25v	46p

CAPACITORS—METALLISED POLYESTER

Stock values: MFO Price each

0 01, 0 015, 0 022, 0 033	4p
0 047, 0 068, 0 10	5p
0 150, 0 220	8p
0 33	8p
0 47	9p
0 68	12p
£1 18	10
1 5	25p
2 2	22p
£2 06	22p
£1 45	22p
£1 25	22p

Order as "Polyesters" + Capacitance.

CAPACITORS—POLYSTYRENE

Axial leads, Clear encapsulation, 5% Tolerance, 160 volt working, Stock values Price each

10pF, 15pF, 22pF, 33pF, 47pF, 63pF, 100pF, 150pF	5p
220pF, 330pF, 470pF, 560pF, 680pF, 820pF, 1000pF, 1500pF	5p
2200pF, 3300pF, 4700pF, 5600pF, 6800pF	4p

Order as "Polystyrenes" + Capacitance.

NEW LOW PROFILE IC HOLDERS

14 pin Oil 18p, 16 pin DII 26p, 8 pin Oil 16p.

NYLON NUTS AND BOLTS

Cheese head screw bolts. Nuts with integral washer. Moulded in high density nylon. Ideal for mounting "live" assemblies, power transistors, etc.

Each pack consists of four nuts and four screw bolts.

Pack No	Thread	Length	Quantity	Pack Price
HSN1	6BA	1/2"	4	10p
HSN2	6BA	3/4"	4	10p
HSN3	6BA	1"	4	10p

Order as "Nuts and Bolts" + Pack No.

OPTO ELECTRONICS—3 devices

from our range—OCP71—42p, ORP12—50p, TIL209 Red led 35p

ANTEX SOLDERING EQUIPMENT

X25/240v 25w Iron	£1 75	SK 2/240v 15w Kit	£2 60
MLX 12v 25w Kit essential for car tool kit	£2 05		
X50 TC 240v 50w temp. controlled	£2 95		

OP. AMPS—NEW LOW PRICE!

741 8 PIN OIL 34p

RESISTORS—METAL OXIDE

Metal Oxide resistors by Electrofil. Ultra low noise, 1/2 Watt, 2%. Available in the range E24 between 10 ohms and 1 Meg. E24 series - 1.0, 1.1, 1.2, 1.3, 1.5, 1.6, 1.8, 2.0, 2.2, 2.4, 2.7, 3.0, 3.3, 3.6, 3.9, 4.3, 4.7, 5.1, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1, and their decades.

Type No. TR5 Price: 4p each

Order as "Metox" + value.

RESISTORS—CARBON FILM

A range of miniature high stability resistors with very low noise characteristics and long life. Tolerances, ranges and wattages as indicated. (Wattage ratings are at max. limiting voltage).

Type No.	Wattage	Tol.	Range	Series	Price
UPM050	0.5	5%	10E-1M	E12	1p each
UPM050	0.5	10%	1M-4.7M	E12	1p each
UPM075	0.75	5%	10E-1M	E12	1p each
UPM075	0.75	10%	1M-4.7M	E12	1p each
UPM100	1.00	10%	10E-1M	E12	2ip each

SERVICE PLUS

10% DISCOUNT OVER £4. NO POSTAGE AND PACKING. TOP QUALITY PRODUCTS ALWAYS BY RETURN COMPREHENSIVE CAT. ➔

Important Notice "All prices are exclusive of V.A.T. Please add 10% V.A.T. to the final total of your order after deducting any discount which may be due"

DEPT PW 9; 7 COPTFOLD ROAD
BRENTWOOD
ESSEX

ARROW ELECTRONICS LTD.

I enclose PO/Cheque for 10p
Name _____
Address _____
Arrow Electronics Limited
Dept. PW 9
Coptfold Road
Brentwood
Essex

Exciting...the Stereo 21!

Can you really get sound quality like this **FOR LESS THAN £19?**

YES, YOU CAN! WITH THE NEW

STEREO 21

Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable **£18.45**, you can have Stereo 21—audio for the connoisseur! Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!



And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience!

Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins all parts supplied including full instructions—all for **£18.45** (plus the cost of post and packing if you buy by mail), and—to round it all off—a money refund if not satisfied if your pleasure in STEREO 21 is not complete!

Just think—in only a few days you could be giving your ears the treat of a lifetime—AND introducing your envious friends to STEREO 21!

Power Output 2.7 Watts per channel and headphone socket with automatic cut out provision for auxiliary inputs—radio, tape, etc. and output for taping discs. Overall Dimension:

Speakers approx. $15\frac{1}{2}'' \times 8'' \times 4''$. Complete deck and cover enclosed position approx. $15\frac{1}{2}'' \times 12'' \times 6''$.

Personal shoppers and mail order price

£18.45 INCLUDING VAT plus £1.60 p & p.

Diamond styli, if required, £1.37 extra

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance, if required £3.85.

EMI SPEAKERS AT UNBELIEVABLE PRICES

950 Kit. Five matched speakers and crossover unit for handling up to 45 watts, from 20 to 20,000 Hz. Huge— $19'' \times 14''$ (approx.) high efficiency 16, 500-gauss bass unit built on a heavy diecast frame. The four 10,000 gauss tweeters, each $3\frac{1}{4}''$ dia. approx., are fed by the crossover with a critically adjusted signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44.00.

OUR PRICE £25.00 : £1.50 p & p



15" 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40.80.

OUR PRICE £18.70
+ £1.50 p & p



RADIO AND TV COMPONENTS (ACTON) LTD, 21C HIGH STREET ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2

Edgware: 9 a.m. to 5.30 p.m., half day Thurs.
Acton: 9.30 a.m. to 5 p.m. Closed all day Wed.; also see opposite.
Mail orders to Acton. Terms C.W.O. All enquiries Stamped Addressed Envelope Goods not despatched outside U.K.



RTVC VISCOUNT III

a boost in the output,

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as value for money! And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! And the teak finish will harmonise and enhance virtually any style of interior decor! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back.

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have never experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

SPEAKERS: Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair + £2.20 p. & p. Duo Type III Size approx. 23½in x 11½in x 9½in. Drive unit approx 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES : SYSTEM 1

Viscount III R102
 amplifier £24.20 + £1 p & p
 2 Duo Type II speakers £14.00 + £2.20 p & p
 Garrard SP25 Mk III
 with MAG. cartridge
 /plinth & cover £18.00 + £1.75 p & p
 total **£56.20**

Available complete for only **£49.00** + £3.50 p & p

PRICES : SYSTEM 2

Viscount R102
 amplifier £24.20 + £1 p & p
 2 Duo Type III speakers £32.00 + £3.30 p & p
 Garrard SP25 Mk III with
 MAG cartridge
 plinth & cover £18.00 + £1.75 p & p
 total **£74.20**

Available complete for **£65.00** + £4 p & p

STILL ONLY **£49 COMPLETE**



THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loud-speaker from 8 to 15 ohms. Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire. The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep. Circuit diagram and comprehensive instructions SSP free with parts. Fully retractable and lockable car aerial £1.37 post paid.

CAR RADIO KIT £6.60 p. and p. SSp. Speaker with baffle and fixing strips £1.65, + 23p p. & p. post free if bought with the kit. Send stamped addressed envelope for leaflet. If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.



PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tape deck, less heads. Caters up to 5½ins. spools. 240V AC mains. Unused but store soiled hence no warranty. **£4.00** £1 p. & p.


RELIANT MK IV MONO AMPLIFIER

*5 Electrically Mixed inputs.
 *3 Individual Mixing controls.
 *Separate bass and treble controls common to all 5 inputs.
 *Mixer employing F.E.T. (Field Effect Transistors).
 *Solid State Circuitry.
 *Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Output 20 watts into 8 Ω (suitable for 15 Ω.) Size approx. 12½ x 6 x 3½ ins. **£13.50** p. & p. 60p

UNISOUND MODULES

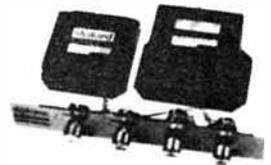ONLY £7.64 + 55p. p & p
 For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.




IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. The Viscount III, the fabulous Stereo 21 and the Unisound Modules **£10.60** + 90p. p. & p. will accept this unit, simply connect up.



SEE OPPOSITE PAGE FOR ADDRESS DETAILS

BI-PRE-PAK AUDIO BARGAINS

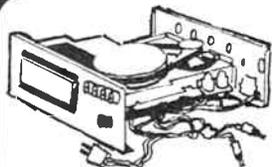

**8 TRACK
ONLY £11**

incl. P. & P. and VAT


The latest B.S.R. 8 Track cartridge Replay Deck. Ready to install in your Hi-Fi Stereo System. This unit comes complete with Hi Gain Stereo Pre-Amplifier, 4-Programme Indicator Lamps, Track Selector Switch, all leads and plugs, etc. for 230 volt A.C. mains operation.

5W & 10W AMPS

5W ONLY £1.98

10W ONLY £2.49

incl. P. & P. and V.A.T.

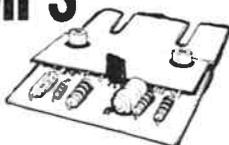

Specification:—

	5 Watt	10 Watt
Nominal Volts	12-14V	25-30V
Into 8 Ohms	5W	10W
Into 15 Ohms	2W	10W
Typical Distortion	1W	5W
Freq. response at 3dB	-5%	-5%
Sensitivity (Typically)	10Hz to 30KHz	10Hz to 30KHz
Full power consumption (30 Ohms)	20mV	20mV
Size	650mA	580mA
	2 1/2" x 1 1/2"	2 1/2" x 1 1/2"

The 5W matchbox sized amplifier will run satisfactorily from a 12V car battery. Can also be used for portable voice reinforcement such as public functions where mains supply is not accessible. A small mains unit kit is available.

Two amplifiers are ideal for Stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit.

Discounts are available for quantity orders.

Cheapest in the U.K. Built and tested

STEREO DECODER
£4.95



incl. P. & P. and VAT

A ready built unit, ready for connection to the I.F. stages of your existing FM Radio or Tuner. A tell tale light can be connected to show the presence of a Stereo transmission and correct operation.

The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.

It is recommended that a L.E.D. is used as the indicating light and a suitable device is available from us at 36p. Supplied with all necessary instructions.

I enclose £..... for 8 Tracks/..... 5W Amps./.....10W Amps./..... Decoders (Please insert quantities and delete those not applicable.)

Name

Address

BI-PRE-PAK

Co. Regn No.820919

Dept. D, 222/224, West Road,
Westcliff-on-Sea, Essex SSO 9DF
Tel: Southend (0702) 46344

London's Lighthouse



see the



showroom
at


IMHOFS

Here at Imhofs we have a whole showroom entirely devoted to the Eddystone range of communication receivers. From the remarkable little EC10 MkII, the elegance of the Series 1000 range to the sophistication of the 830/7. Pop in and see us - or write for details to:-

112-116 New Oxford Street
London WC1A 1HJ
Telephone 01-636 7878

R83

Quality hi fi Cabinets

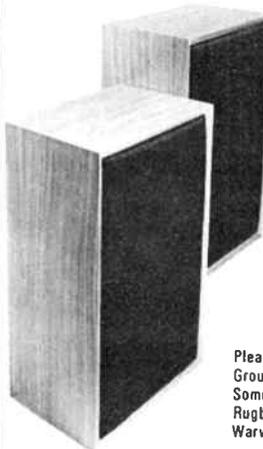

Direct from manufacturer. Finished in teak or afrormosia veneers.

- * Size 17" high x 10" wide x 7" deep.
- * Complete with black Vynair removable front.
- * Routed baffle for 8" bass and 3 1/2" tweeter.
- * Removable baffle board.
- * Lacquered and polished cabinet.
- * Price £9.50 per pair incl. VAT plus 75p packing and carriage.

Please send cash with order direct to Group 3 Cabinets Ltd., Somers Road Industrial Estate, Rugby, Warwickshire. Tel: 0788-78211

COMPRESSION TRIMMERS


*WE STOCK THE LARGEST RANGE IN THE U.K. (Possibly in Europe!)

Here's a page from our Catalogue showing a few typical types

HOME RADIO (COMPONENTS) LTD. TRIMMER CAPACITORS


Maker: CYLDON

Cat. No.	Maker's No.	Size inches	Capacity	Price
VC29D	CBB/30	$\frac{3}{4} \times \frac{3}{8} \times \frac{1}{2}$	3-30 pF	10p
VC29E	CAA/40		3-40 pF	10p
VC29F	CAA/80		10-80 pF	10p
VC29H	CAA/180		60-180 pF	12p

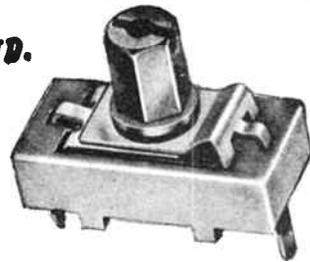


CA-CB types

VC29J	MT31A/9	$\frac{3}{8} \times \frac{7}{8} \times \frac{3}{8}$	1.5-20 pF	8p
VC29LA	MT31A/3		3-40 pF	8p
VC29LC	MT31A/12		7-60 pF	10p
VC29K	MT31A/4		10-80 pF	9p
VC29LB	MT31A/5		30-140 pF	10p
VC29L	MT31A/13		60-180 pF	11p

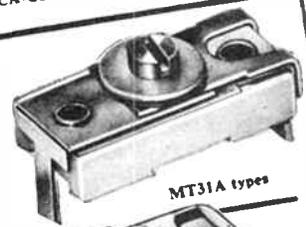

MT31A types

VC29M	MT25/18	$\frac{5}{8} \times \frac{7}{8} \times \frac{3}{8}$	1.5-25 pF	11p
VC29MA	MT25/1		2.5-40 pF	11p
VC29MB	MT25/2		3.5-70 pF	11p
VC29N	MT25/3		20-150 pF	12p
VC29P	MT25/4		45-250 pF	12p

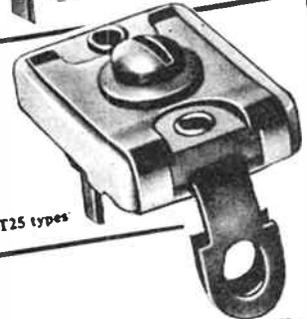

MT25 types

VC29PA	TP1	$\frac{5}{8} \times \frac{7}{8} \times \frac{3}{8}$	10-110 pF	12p
VC29Q	TP4		20-250 pF	11p
VC29R	TP12		50-450 pF	14p
VC29RB	TP11		150-750 pF	17p
VC29S	TP7		300-1000 pF	18p
VC29SA	TP10		400-1250 pF	19p
VC29SB	TP29		500-2000 pF	22p



TP types

Also a large range of Air Dielectric Trimmers in stock

The Famous Home Radio Components Catalogue lists 6,785 items—1,750 of them illustrated.

* Send now for catalogue

POST THIS COUPON
with cheque or P.O. for 77p.

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD.
Dept. PW 234-240 London Road, Mitcham CR4 3HD

Regd. No.
912966
London



ELECTRONIC MAINS TIMER

A reliable unit ideal for timing Bathrooms/Tollet Ventilators Stairways Cloakroom Lighting etc. (Gives up to 30 mins delay before switching off. Delay: 1-30 mins adjustable.)
Max Load: 400VA or 1000 watt resistive.
Ivory Case: 3 1/2" x 3 1/2" x 1 1/2". Fitting instructions included.
Trade Price: £5.80. Post 20p.



DIMMER SWITCH

Type C1.
300 Watt Light Dimmer for 200/250 Volt A/C operation.
Ivory Case. 3 1/2" x 3 1/2" x 1 1/2". Fitting instructions included.
Price: £2.80. Post 20p.



MAINS KEYNECTOR

The safe, quick, connector for electrical appliances, 13 Amp rating, fused, will connect a number of appliances quickly and safely to the mains, ideal for testing, de-energising, window displays, etc.
Warning Light, interlocked to prevent connecting when live.
Trade Price: £2.95. Post 25p.



TRANSFORMERS

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen

VA (watts)	Ref. No.	Price £	P & P £
100	149	2.86	0.38
150	150	3.15	0.52
200	151	5.30	0.52
250	152	7.05	0.65
350	153	9.40	0.80
500	154	13.55	1.00
1000	155	24.97	1.20
2000	158	41.25	*
3000	159	64.54	*

LOW VOLTAGE

Prim. 200-240V. Sec. 12 & 24V.

Volts	Type	Price £	P & P £
12V 24V	No.	£	£
0.5	0-25	1.11	0.22
1	0.5	2.13	0.22
2	1	7.1	0.22
4	2	18	0.38
6	3	7.0	0.42
8	4	10.8	0.52
10	5	7.2	0.52
12	6	11.6	0.52
16	8	17	0.52
20	10	11.5	0.69
30	15	18.7	0.97
40	20	23.2	1.00
60	30	22.6	1.10

30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.

Amps	Type	Price £	P & P £
0.5	112	1.20	0.22
1	79	1.64	0.38
2	3	2.45	0.38
3	20	3.00	0.42
4	21	3.55	0.52
5	51	4.40	0.52
6	117	5.25	0.52
8	88	6.20	0.67
10	89	8.36	0.67

50 Volts

Prim. 200-240V.

Amps	Type	Price £	P & P £
0.5	102	1.80	0.30
1	103	2.35	0.38
2	104	3.25	0.42
3	105	4.40	0.52
4	106	5.48	0.52
6	107	8.65	0.67
8	118	11.27	0.97
10	119	14.15	0.97

60 Volts

Prim. 200-240V.

Amps	Type	Price £	P & P £
0.5	124	1.60	0.38
1	126	2.25	0.38
2	127	3.55	0.42
3	125	6.40	0.52
4	123	6.98	0.67
5	40	8.46	0.67
6	120	9.20	0.82
8	121	11.60	1.00
10	122	15.25	1.00
12	129	16.48	1.10

MINIATURE AND EQUIPMENT

Prim 240V with screen

Volts	Sec. 1	Sec. 2	Milliamps	Type	Price £	P & P £
3-0-3	---	---	200	---	234	1.12
0-6	0-6	---	500	500	234	1.18
0-6	0-6	---	1000	1000	212	1.28
9-0-9	---	---	100	---	13	0.95
0-9	0-9	---	350	330	235	1.28
0-8-9	0-8-9	---	500	500	207	1.70
0-8-9	0-8-4	---	1000	1000	208	2.30
15-0-15	---	---	40	---	240	1.28
0-15	0-15	---	200	200	236	1.28
20-0-20	---	---	30	---	241	1.09
0-20	0-20	---	150	150	237	1.28
0-15-20	0-15-20	---	500	500	205	2.16
0-20	0-20	---	300	300	214	1.36
20-12-0-12-20	---	---	700(D/C)	---	221	1.21
0-15-20	0-15-20	---	1000	1000	206	3.10
0-15-27	0-15-27	---	500	500	203	2.38
0-15-27	0-15-27	---	1000	1000	204	2.40

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 Volt 25p	50 Volt 85p	100 Volt 55p	50 Volt 65p
100 Volt 25p	100 Volt 40p	200 Volt 59p	100 Volt 70p
200 Volt 28p	200 Volt 45p	400 Volt 65p	200 Volt 80p
600 Volt 30p	600 Volt 50p	800 Volt 75p	400 Volt 90p
	1000 Volt 55p	800 Volt £1.00	600 Volt £1.00



PLEASE ADD 10% FOR V.A.T.

ADD 10p P & P PER ORDER

A.S.P. LTD.

BYRE HOUSE · No. 2 UNIT · SIMMONDS RD · WINCHEAP CANTERBURY · KENT · CT1 3RW Canterbury (0227) 52436

D.I.Y. ELECTRONIC ORGAN KITS

In use throughout the world by professionals



★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2 x 5 octave keyboards and 32 note pedal board, 32 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £572.55.

V.A.T. please add 10%—show separately on order.

All components can be bought separately. Send 50p for 24-page catalogue which includes details of specialised components plus free vouchers worth 50p.

Also available—WIRELESS WORLD SOUND SYNTHESIZER KITS complete with reprinted instructions.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

12 Brett Road, Hackney, London, E.8. Tel: 01 986 8455
8 Pucney Bridge Rd., London, SW18 1HU. Tel: 01 870 4949

PLUGS & LEADS

Pack 107 5 pin Din	22p
Pack 108 3 pin Din	20p
Pack 135 1/2" Jack	27p
Pack 130 1/2" Jack Stereo	50p
Pack 103 Loudspeaker Plug	17p
Pack 100 Phono Plug	7p
Pack 230 3 pin Socket	25p
Pack 236 5 pin Socket	33p
Pack 234 Loudspeaker Socket	33p
Ready-made Leads	
3 pin to 3 pin Din	70p
3 pin to open end	55p
5 pin to 5 pin Din	90p
5 pin to open end	70p
5 pin to 4 phono plugs	£1.00
Speaker lead Din to spade 12ft	40p
Extension lead Din plug to socket 12ft.	70p
All leads approx. 6ft. in length	

DIAMOND STYLI

8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8.All at 80p each.
Double Diamond £1.25
Diamond suitable for Orbit NM22; G800; M3D £2.25 each

CARTRIDGES

Goldring G800	£6.00
Orbit NM22	£4.00
Shure 75/6	£6.00
Sonotone 9TAHC (Dia)	£2.00
Sonotone 8T4A (Dia)	£1.50
Ronnette 105 (Dia)	£1.25

All prices include VAT and postage

RECORD CARE

Cecil Watts Dust Bug	£1.20
Parastatic Disc Preener	45p
Antistatic Fluid	20p
Dust Bug Spares (Brush & Roller)	15p

CASSETTE TAPES

Audio-Magnetic C60 Qty 3 6 10 20
Price £1.00 £1.90 £3.20 £6.30
Cassette Caddy £1.20
Cassette Head Cleaner 35p

ZONAL ILFORD TAPE

5" Standard 600ft	25p
5 1/2" Standard 900ft	50p
7" (Plain boxed) 1200ft	60p
7" (Westminster Boxed) 1800ft	£1.25
7" Reel of Leader Tape (Blue or green)	75p

HEADPHONES

Sennheisser HD414	£10.60
AKG K50	£6.50
Beyer DT48S	£35.00

MICROPHONES

AKG D109	£11.50
AKG D202E1	£39.50
AKG D190C	£17.00
AKG D190E	£18.20
AKG D224	£50.00
Sennheisser MD211N	£45.00
Sennheisser MD413N	£27.00
Sony ECM50	£85.00
Audio RMS7F Radio Mike	£210.00

SPEAKERS

E.M.I. 350 Kit Bohms	£8.20
E.M.I. 450 Kit Bohms	£4.50

J. J. Francis (Wood Green) Ltd

MANWOOD HOUSE, MATCHING GREEN, HARLOW, ESSEX CM17 0RS Telephone: Matching 476

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984... when it might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £18-50—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! ★ Send quickly, from receipt of goods test on mail order 7 days approval, refund if not delighted. Or call. Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions, VHF, FM/USW, AM-LW, MW, SW, gets, locally, local & new stations, not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output ON/OFF volume and separate Treble and Bass controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 in approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. SIZE 13in x 10in x 4 1/2in overall approx. Magnificently designed, in highly polished cases. Made to give years of perfect service. Purer & sweeter tone than ever. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram. **PLUS** ultra sensitive earphone for personal listening. **ONLY £18-50** (with mains/battery eliminator £2-25 extra) **BOX, POST, ETC. 45p. NO MORE TO PAY! ★ BUT WAIT, for only 75p extra you get the sensational "COMPUTERISED" WORLD TUNING GUIDE** (it enables you to zone & time in a flash for transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard "longlife" batteries and Converter Plug. (Sorry—We cannot change these new radios for any earlier model purchased.) Send quickly to Uxbridge Road address, or call at either Store. But **HURRY! SHOPERTUNITIES SAVE YOU £££'s and £££'s.**

THOUSANDS OF MILES REDUCED TO INCHES? 1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! *COMPUTERISED?



**YES, 24,901 miles
SHRUNK TO ONLY 13" x 10" x 4 1/2"
inches approx?**

**28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)**

**BATTERY MODEL £18-50 BOX POST ETC. 45p
MAINS/BATTERY ELIMINATOR £2-25 extra**

BRAND NEW FABULOUS ASTRAD 17
'PORTABLE RADIO & COMMUNICATIONS RECEIVER



***MUST YOU PAY UP TO £80?**

FIRST TIME EVER!
*NOW AVAILABLE WITH fabulous **"COMPUTERISED" WORLD TUNING GUIDE!**
NO MORE GUESSWORK—INSTANT DATA at your fingertips—enables you to **ZONE & TIME IN A FLASH** for transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! **SAVE £23-03 NOW!**
FABULOUS BRAND NEW SOLID STATE This equipment's got EVERYTHING!
BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER
RECOMMENDED RETAIL PRICE £44
OUR PRICE £20-97 CARR. ETC. 50p
WITH REMOTE CONTROL MICROPHONE

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord.) Record and play back anything, anywhere! **IMPORTERS RECOMMENDED RETAIL PRICE £44! WE OFFER AT UNDER HALF PRICE!** Wonderful features: ★ Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! ★ Separate ON/OFF volume controls! ★ Heavy duty built-in speaker! ★ Earphone (for personal listening or "monitoring") and extension speaker sockets! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in. approx.). Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. **AND** the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, local city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££'s more for a Car Radio or Car Cassette player ALONE! £20-97, carr. etc., 50p—**NO MORE TO PAY!** Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 28p extra if required. Callers: ACCESS & BARCLAY CARDS ACCEPTED AT BOTH STORES.

FIRST TIME EVER! *SAVE £16-02!
BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER **FIRST CLASS MAKERS**
With remote control microphone.
WE COULD CHARGE UP TO £26-97! OUR PRICE £10-95 POST ETC. 50p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb de luxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £10-95**. Due to our cut price, we cannot name first-class makers—but rest assured you're getting one of the **BEST!** Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60 or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect capines and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Complete—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9 1/2in x 5in x 2 1/2in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Importers recommended selling price £26-97!) **OUR PRICE ONLY £10-95, post, etc. 50p. NO MORE TO PAY!** ★ Send quickly, test on mail order 7 days approval from receipt of goods—refund if not delighted. **BONUS OFFER—**Cassette tape, Standard batteries AND microphone stand 55p extra, if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores. (COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn Store.)

Dept. WP/NC/35, 164 UXBURGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. Thurs. 1, Fri. 7. Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.). BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

SHOPERTUNITIES LTD.

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1-50. 3 for ONLY 55p + p & p 30p

SPECIAL ONE. As above PLUS Power Transistors ONLY 55p each + p & p 15p

STABILISED POWER MODULES
Complete with circuit diagrams, etc. 99p each + p & p 15p

PAXOLINE BOARDS 7 1/2" approx. 4 for 80p + p & p 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16 1/2 x 4" approx. 2 for 55p

DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen 99p each

VEROBOARDS

Packs containing approx. 200p Ins. various sizes, all 1 matric 55p

REPANCO CHOKES & COILS

RF Chokes
CH1. 2.5mH 25p CH2. 5.0mH 25p
CH3. 7.5mH 25p CH4. 10mH 25p
COILS
C113. 1.5mH 25p

COILS
DRX1 Crystal set 50p DRR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 7p
1" Cores & Formers 8p

SWITCHES

UP/DT Toggle 25p SP/ST Toggle 18p

FUSES

1 1/2" and 20mm. 100mA, 200mA, 250mA, 300mA, 1A, 1.5A, 2A
QUICK-BLOW 4p ea. ANTI-SURGE 5p ea.

EARPHONES

Crystal 2.5mm plug 33p
Crystal 3.5mm plug 33p
4 ohm 2.5mm plug 22p
5 ohm 3.5mm plug 22p

DYNAMIC MICROPHONES

H1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.60

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1-87

2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB £1-21

CAR STEREO SPEAKERS

(Angled) £3-85 per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES



Black Vinyl covered:

No.	Length	Width	Height	Price
BV1	8"	5 1/2"	2"	90p
BV2	11"	6"	3"	£1-20

ALUMINIUM BOXES

BA1	5 1/2"	2 1/2"	1 1/2"	62p
BA2	4"	4"	1 1/2"	41p
BA3	4"	4"	1 1/2"	41p
BA4	5 1/2"	4"	1 1/2"	41p
BA5	4"	2 1/2"	2"	47p
BA6	3"	2"	1"	34p
BA7	7"	5"	2 1/2"	68p
BA8	8"	6"	3"	84p
BA9	8"	4"	2"	54p

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)


Open Mon. Thurs. 9.15-6 p.m. Sat. 9.15-5.30. Late Night Shopping until 7 P.M. Tel. 61593

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1-84

Chrome Finish Model 60 £1 50

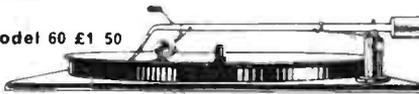

Ref. 36A. Record/Styleus Cleaning Unit 28p
Ref. 43. Record Care Kit £2-35
Ref. 31. Cassette Head Cleaner 54p
Ref. 32. Tape editing Kit £1-54
Model 9. Wire Stripper/Cutter 83p

Ref. P. Hi-Fi Cleaner 31p
Ref. 32A. Stylus Balance £1-86
Ref. J. Tape Head Cleaning Kit 51p
Ref. 34. Cassette Case £1-27
Ref. 55. Hi-Fi Stereo Hints & Tips 82p

ANTEX SOLDERING IRONS

X25. 25 watt £1-93
CCN 240. 15 watt £2-15
Model G. 18 watt £2-15
SK2. Soldering Kit £2-86
STANDS: ST1 £1-21. ST2 77p
SOLDER: 18SWG Multicore Tox 82p
22SWG Tox 82p. 18SWG 22ft 28p
22SWG Tube 22p

ANTEX BITS AND ELEMENTS

Bits No.
102 For model CCN240 3/32" 38p
104 For model CCN240 3/16" 38p
1100 For model CCN240 3/32" 38p
1101 For model CCN240 3/8" 38p
1102 For model CCN240 1" 38p
1020 For model G240 3/32" 38p
1021 For model G240 1/8" 38p
1022 For model G240 3/16" 38p
50 For model X25 3/32" 38p
51 For model X25 1/8" 38p
32 For model X25 3/16" 38p

ELEMENTS

ECN 240 £1-16 ECUN 240 £1-32
EQ 240 £1-16 EX 25 £1-16

ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C1	250	Resistors mixed values approx. count by weight	0-55
C2	200	Capacitors mixed values approx. count by weight	0-55
C3	50	Precision Resistors 1% 2% mixed values	0-55
C4	75	1/4W Resistors mixed preferred values	0-55
C5	3	Pieces assorted Ferrite Rods	0-55
C6	2	Tuning Gans. MW/LW VHF	0-55
C7	1	Pack Wire 50 metres assorted colours	0-55
C8	10	Reed Switches	0-55
C9	3	Micro Switches	0-55
C10	15	Assorted Pots & Pre-Sets	0-55
C11	5	Jack Sockets 3 x 3.5m 2 Standard Switch Type	0-55
C12	40	Paper Condensers preferred types mixed values	0-55
C13	20	Electrolytic Trans. types	0-55
C14	1	Pack assorted Hardware Nuts/Bolts, Grommets etc.	0-55
C15	4	Mains Slide Switches	0-55
C16	20	Assorted Tag strips & Panels	0-55
C17	10	Assorted Control Knobs	0-55
C18	4	Rotary Wave Change Switches	0-55
C19	3	Relays 6—24V Operating	0-55
C20	4	Sheets Copper Laminate approx. 10" x 7"	0-55

PLUGS AND SOCKETS

SOCKETS
PS 35 DIN 2 Pin (Speaker) 0-06
PS 36 DIN 3 Pin 0-10
PS 37 DIN 5 Pin 180° 0-10
PS 38 DIN 5 Pin 240° 0-10
PS 39 Jack 2.5mm Switched 0-09
PS 40 Jack 3.5mm Switched 0-10
PS 41 Jack 1" Switched 0-17
PS 42 Jack Stereo Switched 0-26
PS 43 Phono Single 0-06
PS 44 Phono Double 0-10
PS 45 Car Aerial 0-09
PS 46 Co-Axial Surface 0-09
PS 47 Co-Axial Flush 0-14

INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0-13
PS 22 D.I.N. 3 Pin 0-17
PS 23 D.I.N. 5 Pin 180° 0-17
PS 24 D.I.N. 5 Pin 240° 0-17
PS 25 Jack 2.5mm Plastic 0-10
PS 26 Jack 3.5mm Plastic 0-12
PS 27 Jack 1" Plastic 0-24
PS 28 Jack 1" Screened 0-28
PS 29 Jack Stereo Plastic 0-22
PS 30 Jack Stereo Screened 0-32
PS 31 Phono Screened 0-14
PS 32 Car Aerial 0-16
PS 33 Co-Axial 0-17

PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0-11
PS 2 D.I.N. 3 Pin 0-12
PS 3 D.I.N. 4 Pin 0-15
PS 4 D.I.N. 5 Pin 180° 0-14
PS 5 D.I.N. 5 Pin 240° 0-15
PS 6 D.I.N. 6 Pin 0-15
PS 7 S.I.N. 7 Pin 0-15
PS 8 Jack 2.5mm Screened 0-10
PS 9 Jack 3.5mm Plastic 0-09
PS 10 Jack 3.5mm Screened 0-12
PS 11 Jack 1" Plastic 0-18
PS 12 Jack 1" Screened 0-18
PS 13 Jack Stereo Screened 0-29
PS 14 Phono 0-06
PS 15 Car Aerial 0-16
PS 16 Co-Axial 0-10

CABLES

CP 1 Single Lapped Screen 0-06
CP 2 Twin Common Screen 0-08
CP 3 Stereo Screened 0-08
CP 4 Four Core Common Screen 0-23
CP 5 Four Core Individually Screened 0-30
CP 6 Microphone Fully Braided Cable 0-10
CP 7 Three Core Mains Cable 0-07
CP 8 Twin Oval Mains Cable 0-06
CP 9 Speaker Cable 0-04
CP 10 Low Loss Co-Axial 0-10

CARBON POTENTIOMETERS

Log and Lin
47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M
VC 1 Single Less Switch 0-14
VC 2 Single D.P. Switch 0-26
VC 3 Tandem Less Switch 0-08
VC 4 1K Lin Less Switch 0-14
VC 5 100K Log anti-Log 0-14

HORIZONTAL CARBON PRESETS

0-1 watt 0-06 each
100, 220, 470, 1K, 22K, 47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 475M

BOOK BARGAIN BUNDLE

8 Books comprising:
2 Transistor Equipment Books
1 Radio and Electronic Colour Code and Data Chart
1 Radio Valve Guide PLUS
3 Other Constructional books on Receivers, FM Tuners, etc.
Also 1 General Constructional book

Value £3 Our Price £2 10p p & p

BP1 Handbook of Transistor Equivalents and Substitutes 40p
BP2 Handbook of Radio, T.V. and Industrial Tube & Valve Equiv. 40p
BP3 Handbook of Tested Transistor Circuits 40p
BP4 International Handbook of the World's Short Wave, Medium and Long Wave Radio Stations and FM/TV Listings 35p
BP5 Handbook of Simple Transistor Circuits 35p
BP7 Radio & Electronic Colour Codes and Data Chart 15p
BP8 Sound and Loudspeaker Manual 50p
BP9 38 Practical Tested Diode Circuits for the Home Constructor 35p
BP11 Practical Transistor Novelty Circuits 40p
129 Universal Gram-Motor Speed Indicator 8p
138 How to make FM & TV Aerials. Bands 1, 2 and 3 18p
141 Radio Servicing for Amateurs 20p
146 High Fidelity Loudspeaker Enclosures 27p
156 Transistor Circuits Manual No.1 15p
160 Coil Design & Constructional Manual 30p
161 Radio, TV and Electronics Data Book 25p
170 Transistor Circuits for Radio Controlled Models 40p
174 Transistor Subminiature Receivers 32p
175 Transistor Test Equipment and Servicing Manual 25p
176 Transistor Audio Amplifier Manual 40p
177 Modern Transistor Circuits for Beginners 40p
178 A Comprehensive Radio Valve Guide, Book 3 30p
183 How to Receive Foreign TV Programmes on your set by simple modifications 32p
185 Tested Shortwave Receiver Circuits using MAT's 30p
187 The T8L Mark 44 Valved FM Tuner and Its construction 20p
196 Reactance-Frequency Chart for Audio & RF use 15p
Resistor Colour Code Disc Calculator 10p

CARTRIDGES

ACOS GP91-18C. 200mV at 1-2cm/sec £1-16
ACOS GP93-1. 280mV at 1cm/sec £1-65
ACOS GP96-1. 100mV at 1cm/sec £2-65
TTC J-2003. Crystal/Hi Output 95p
TTC J-20 10C Crystal/Hi Output Compatible £1-10
TTC J-200 CS Stereo/Hi Output £1-80
TTC J-2105 Ceramic/Med. Output £1-64

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors. 1/8th watt available in PAKS of 50 pieces, assorted into the following groups—
R1 50 Mixed 100 ohms-820 ohms 40p
R2 50 Mixed 1K ohms-82K ohms 40p
R3 50 Mixed 10K ohms-82K ohms 40p
R4 50 Mixed 100K ohms-1 Meg. ohms 40p
THESE ARE UNBEATABLE PRICES—LESS THAN 1p EACH INCL. V.A.T.


BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

CB0. 32p CB9. 41p C120. 52p

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

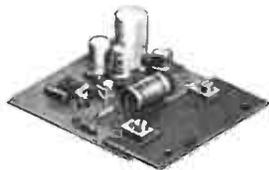

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f = 1KHz	0.25%
LOAD IMPEDANCE	—	8 - 16 Ω
INPUT IMPEDANCE	f = 1KHz	100 k Ω
FREQUENCY RESPONSE @ 3dB	Po = 2 WATTS	50 Hz - 25KHz
SENSITIVITY for RATED O/P	Vs = 25V. Ri = 8 Ω f = 1KHz	75mV. RMS
DIMENSIONS	—	3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. (RL = 8 Ω f = 1 KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts RMS	£2.19
AL 20. 5 watts RMS	£2.59
AL 30. 10 watts RMS	£3.01

POWER SUPPLIES

PS 12. (Use with AL10 & AL20)	88p
SPM 80. (Use with also AL30 & AL50)	£3.25

FRONT PANELS SP 12 with Knobs £1.10

PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20)	£4.35
PA 100. (Use with AL30 & AL50)	£13.15

TRANSFORMERS

T461 (Use with AL10)	£1.38 P & P 15p
T338 (Use with AL20)	£1.93 P & P 15p
BMT80 (Use with AL30 & AL50)	£2.15 P & P 25p

PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 162mm x 84mm x 35mm.

Frequency response—
20Hz - 50KHz (-3dB)
Bass control—
± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
†Input 2. Impedance
30 K ohms
Sensitivity 4mV

EA1000 AUDIO AMP MODULE 3 WATTS R.M.S.



Module Tested and Guaranteed. Full book-up diagrams and complete technical data supplied free with each module or available separately at 10p each.


ONLY
£2.89

SPECIAL OFFER £2 each while stores last

The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (AUX.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14kHz.

£13.48

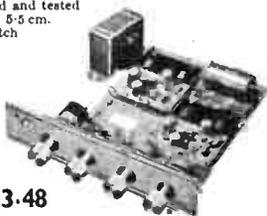

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

THE AL50

- ★ Frequency Response 15Hz to 100,000—1dB.
- ★ Load—3, 4, 8 or 16 ohms.
- ★ Distortion—better than .1% at 1 KHz.
- ★ Signal to noise ratio 80dB.

ONLY
£3.58 each

★ Supply voltage 10-35 Volts.

★ Overall size 63mm 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT—TESTED—GUARANTEED.

STABILISED POWER MODULE SPM80



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address Intercom Units, etc. Handbook available 10p PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market. The PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response 20Hz - 20KHz ± 1dB
Harmonic Distortion better than 0.1%
Inputs: 1. Tape Head 1.25 mV into 50K Ω
2. Radio, Tuner 35 mV into 50K Ω
3. Magnetic P.U. 1.5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.
Bass Control ± 15dB at 20Hz
Treble Control ± 15dB at 20 KHz
Filters: Rumble (High Pass) 100Hz
Scratch (Low Pass) 8KHz
Signal/Noise Ratio better than -65dB
Input overload + 26dB
Supply + 35 volts at 20mA
Dimensions 292mm x 82mm x 35mm

ONLY £13.15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 11p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please.


Guaranteed Satisfaction or Money Back

Why pay more - look at our Fantastic Bargain Offer!

PENTHOUSE

A COMPLETE AUDIO SYSTEM

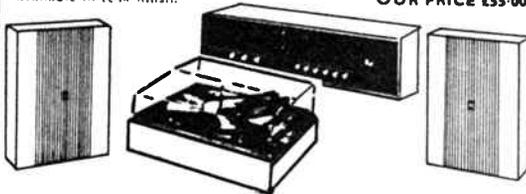An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder, 4 wavebands Long/Medium/Short/VHF, 8 watts per channel (music power) output. The latest BSR C129 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units. Also available in teak finish. **OUR PRICE £35-00**



Credit terms £5-00 deposit plus £2-00 p. & p. followed by 12 payments of £3-00. Total Credit Terms £65-00 SEND £7-00 TODAY.


KLINGER

FIVE NINETY THREE UNIT AUDIO SYSTEM with BSR McDonald 4-speed Record Player, matching 4-unit Loud-speaker Systems and FREE Stereo Head-phones.



High performance Stereo Amplifier designed for home entertainment at economical cost. Represents a considerable advance in solid state, high fidelity stereo amplifiers. Outstanding performance is allied to meticulous construction, comprehensive facilities, installation simplicity and attractive styling. 10 watt RMS per channel; push button selectors; tone controls; balance control; tape record and replay facilities. Stereo headphone socket on front panel with automatic speaker muting; Teak finish. **Our price £75-00 + £2-00 p. & p.** Credit Terms £7-50 deposit + £2-00 p. & p. 18 monthly payments of £4-75 (total £93-00) SEND £9-50 TODAY.

THE AVON AUDIO SYSTEM

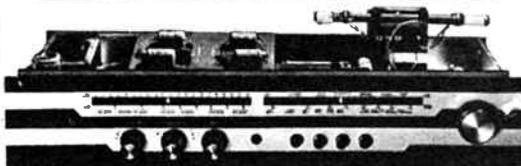

The uncabineted system is ideal as an economical replacement for an outdated chassis. The Stereo Tuner Amplifier with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

LATEST BSR STEREO/MONO RECORD CHANGER plays all types of 7in., 10in., and 12in. Mono or Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKERS. These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.



EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45-74, **OUR PRICE £35-00.** Credit Terms £3-50 deposit plus £2 Post & Packing followed by 12 payments of £3-15 (Total Credit Terms £41-30) Dont miss this bargain. **SEND £5-50 TODAY**

ALL EQUIPMENT COVERED BY OUR 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

LEWIS radio

P/123

100 Chase Side, Southgate,
London N14 5PL
Tel: 01-886 3733/9666

ERSIN

Multicore
5 CORE SOLDER

for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS



Size 5 Savbit alloy 18 swg, 18p (illustrated).
Size 19A 60/40 alloy 18 swg, 18p
Size 15 60/40 alloy 22 swg, 22p

IDEAL FOR HOME CONSTRUCTORS


Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 25p



Size 12 REEL for Service Engineers and Electricians. 18 swg Savbit alloy. 75p



BIB WIRE STRIPPER AND CUTTER

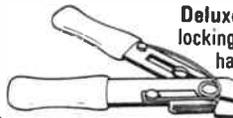

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to: **Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP**

AMAZING MINI-DRILL



FOR PRECISION MODEL WORK



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £8-35 p.p. 13p. De Luxe Professional Kit with 17 tools £9-40 p.p. 23p. Prices include V.A.T.

ONLY £2.55 P.P. 10p

Money ref. g'tee. **MERLIN SUPPLY CO.**

Dept. PW 1273 Nailsea, Bristol BS19 2LP

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Switches, Potentiometers, Knobs, IF's, Tag Strips, Drive Drums, Transistor Panels etc., etc. Save yourself £s on these well selected parcels 6lbs net weight £1-00, p. p. 40p.

Assorted Electrolytic Capacitors, 6lbs net weight £1-00, p. p. 40p.

Brand new Wire-wound Resistors, Good Selection. 100 for £1, p. p. 15p.

Mullard Ferrite Pencil Magnets 1½" x ¾". 100 for £1-25, p. p. 16p.

Assorted Computer Panels. These panels are exceptionally good value and contain a minimum of 75 transistors, stacks of diodes plus Trim Pots, Polyester Capacitors, Resistors and include a few I.C.s. 10 panels for £1-00, p. p. 25p.

Mullard Ferrite Cores. LA3 100 to 500kHz 50p, LA4 10 to 30kHz 75p LA2100 3 to 200kHz 50p.

Please include 10% V.A.T. to total cost of goods. **Mail Order Only.**



XEROZA RADIO

1 EAST STREET, BISHOPS TAWTON, DEVON

TOP QUALITY — LOW COST



RADIO — STEREO EQUIPMENT

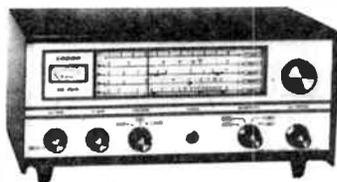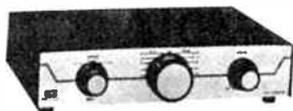

P.R.40

SOLID STATE R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which is now superceded.

It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30 dB, with improved image rejection and noise ratio.

Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee.

£10-12 V.A.T./Carr. Paid.

CR70A

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.

It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder.

Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee. Complete ready built. £31-00 V.A.T./Carr. Paid.

SEND FOR YOURS TODAY!

FREE LEAFLETS ON REQUEST.

NOTE: These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers. Some portable receivers being advertised as Communication Receivers do not meet these requirements.

TRADE DESCRIPTIONS ACT 1968

It is illegal to make false claims or misleading statements in advertising. The following are just a few extracts from the many letters received from satisfied customers. All are unsolicited and can be inspected at any time.

Mr. S. Keightly, Southsea, Hants.
I am delighted with the CODAR equipment I am using . . . everything has come up to your specifications.

Dr. R. E. Wood, Louisiana State University, U.S.A.
Congratulations on an excellent product. The PR40 Preselector is the first preselector I have found to operate efficiently with ample gain, and without feedback or image problems.

Mr. W. R. Jones, Woy, N.S.W., Australia.
The PR40 peaked signals remarkably and performed as you claim. I am very satisfied.

M. G. Bennett, Bath, Somerset.
I am very pleased with my CR70A—results are excellent with many overseas stations I have not heard before and excellent results on the Amateur Bands.

Mr. J. Macdonald, Coningsby, Lincoln.
Received Multiband Kit OK. Assembled it in two hours, worked a treat first time.

Mr. E. Joy, Chesham, Bucks.
The performance of the CR70A is out of this world for its price, and its construction and design, great. I am really delighted . . . I cannot fault it.



MULTIBAND-6

SOLID STATE
SHORT WAVE RECEIVER KIT

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils.

Hi-Gain FET Regen, Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB.

Separate Electrical Bandspread, Calibrated Main Tuning.

A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to built, printed circuit and Pictorial Instruction Manual, fully detailed step by step.

Complete Kit with 4 Coils (less standard PP6 battery).

£14-90 V.A.T./Carr. Paid.

NEW! HI-FI STEREO EQUIPMENT

NOW AVAILABLE FROM CODAR—A COMPLETE RANGE OF QUALITY EQUIPMENT SELECTED BY US FOR TOP RESULTS AND MONEY VALUE—PLUS OUR BIG CASH DISCOUNTS!

SEND FOR FREE ILLUSTRATED BROCHURES NOW

NEW! AMTRON KITS

We are now also marketing the outstanding range of AMTRON Kits. The quality of these Kits is first class, with circuit details and drawings making construction simplicity itself.



ON THE DESIGN STAFF—
G3SZM G3IRE

CODAR

TELECOMMUNICATIONS AND ELECTRONIC
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

Tel. 090-63-61901

BN15 - 8TZ

FREE

Headphones or Speakers; Suitably Terminated Connectors; Handbook; Carriage; Insurance. In addition a JOYSTICK V.F.A.; JOYMATCH A.T.U.; feeder external mounting insulators are supplied FREE or greatly reduced when you buy a PARTRIDGE PACKAGE.

A PARTRIDGE PACKAGE constitutes a COMPLETE RADIO STATION—ready to use however confined your domestic space. The World renowned TRIO range of Communications Receivers and Transceivers, the WORLD RECORD, internationally patented JOYSTICK V.F.A. (all band aerial) only 7" 6" long (assembled) and a JOYMATCH aerial tuning unit, a pair of matching headphones or internal speaker, plus accessories, go to complete your READY TO USE RADIO STATION at a price that truly represents VALUE FOR MONEY!

PARTRIDGE PACKAGE

No. 1 with Gen. Coverage AM/CW/SSB (MW/SW) 9R59DS Receiver £67.77 (Save £17.16)
 No. 2 with Amateur Bands 80 thru 10m AM/CW/SSB JR310 Receiver £90.97 (Save £22.35)
 No. 3 with Amateur Bands 160 thru 10m plus 2m AM/CW/SSB JR599 £176.00 (Save £30.48)
 No. 4 with Amateur Bands 80 thru 10m TS/PS 515 Transceiver, 180w £231.00 (Save £37.08)

NOTHING MORE TO PAY!

Access/Barclaycard orders accepted by 'phone

JOYSTICK V.F.A. £13.75; JOYMATCH TX/RX A.T.U. 111A 1.6-32MHz £13.75; JOYMATCH A.T.U. 111 RX only 500kHz-32MHz £13.75; JOYMATCH A.T.U. LO-Z500 TX/RX 500w SSB (PA input), Built-in RF meter £19.91; Communications 8Ω headphones (suitable TRIO, EC10 etc.) £3.14; Matching Speaker (with instructions for internal fitting in 9R59DS & JR310) £2.00; TRIO: Linear Amplifier TL911 £172.15; TR2200 2m personal transceiver £87.45; TR7200 2m car transceiver £142.45; Spare set valves for 9R59DS £2.35; OA2 Mains Stabiliser 74p.

NEW : World-wide reception on the amazing "DX-CRYSTAL SET" £2.42 incl. unique aerial.

NEW : AMTRON QUALITY KITS—send for brochure and prices.

PARTRIDGE BUDGET LINE

Artificial Earth—solves receive and transmit earth problems (as used on North Sea Oil Rigs!) £5.80; Aerial Bandswitch—tuned aerial for domestic receivers £5.80; A.T.U. KIT—for use with transmitters and Communications Receivers £5.80; (assembled £7.01); Mini SWR Bridge—1.8 to 180MHz, 2kw P.E.P., 75 or 50Ω, SO239 sockets; 1:1 to 1:3 ratio, 80 x 30 x 30mm £5.60. (All prices quoted INCLUDE V.A.T., CARRIAGE, PACKING, INSURANCE.)

Send 3½p stamp for full illustrated details. Special TRIO brochures (state which) 3½p stamp extra.

NO V.A.T. ON OVERSEAS ORDERS!

Carriage and insurance extra overseas orders


BOX 5



G3CED — G3VFA

Telephone: 0843 62535 or 62839 evenings and weekends

verobox

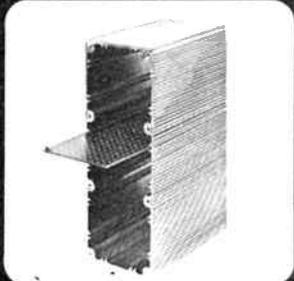

ALUMINIUM ENCLOSURES

- 80 standard sizes available from stock.
- Made from precision extrusions with integral board guide slots.
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.



VERO ELECTRONICS LTD.

Eastleigh, Hants. SO5 3ZR
 Tel; Chandler's Ford 2952 Telex: 47551
 Subsidiaries and Agents
 throughout the World.

EX COMPUTER PC PANELS

2 x 4 in. packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (12p)

SPECIAL BARGAIN PACK

25 boards for £1 (30p).
 Panels with 4 Power transistors sim OC28 50p (10p)

ELECTROLYTICS

6000μ 75v 4½ x 2in. dia. 55p (14p)
 5000μF 90v, 8000μ 55v 4½ x 3in dia. 50p (24p)
 10,000μ 35v, 5,000μ 35v 4½ x 2in 40p (12p)
 2000μ 25v wire ends 15p (6p)
 3A diodes 4 for 50p (7p)
 250 mixed capacitors 60p (9½p)
 250 mixed resistors 60p (9½p)
 250 mixed HI-STAB resistors 60p (9½p)
 200 Si Plana diodes 50p (7p)
 Sub-min co-ax. connectors 4 prs. 50p (7p)
 Min. glass neons 12 for 50p (7p)
 Reed Relays mixed 10 for 50p (7p)
 Micro switches 8 for 50p (9p)
 Assorted Relays 8 for £1 (18p)
 10 way terminal blocks 10 for 55p (15p)
 Papst extractor/blower fans 100 c.f.m.
 4½ x 4½ x 2in. £3.50 (28p)
 Q.H. bulbs 12v 55w 50p (6p)

Postage and package shown in brackets.
 Please add 10% VAT to prices.

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
 LONDON W8. 01-478 8499

BABANI PRESS

NEW TITLES!

BP10. Modern Crystal and Transistor Set Circuits for Beginners by B.B.Babani 35p

201. Practical Transistorised Novelties for Hi-Fi Enthusiasts by B.B.Babani 35p

AVAILABLE NOW

FROM ALL GOOD RADIO COMPONENT AND HI-FI SHOPS, BOOK SHOPS, MAIL ORDER COMPANIES AND MANY OF THE LARGER BRANCHES OF W. H. SMITH & SON LTD IN MAJOR TOWNS

BERNARDS(publishers)LTD

Adcola Soldering Equipment of the Finest Quality

CHRISTMAS GIFTS GALORE

Available from Stock

A Styrene boxed Soldering Kit designed for your immediate needs containing a $\frac{7}{8}$ " Invader soldering instrument, two spare bits, a soldering station and a pack of solder—everything you need.

The versatile Invader Range with a large selection of interchangeable bits

- B** L706 19 watt instrument $\frac{1}{8}$ " bit with cable
- C** L646 23 watt instrument $\frac{3}{8}$ " bit with cable
- D** L1076 27 watt instrument $\frac{1}{4}$ " bit with cable
- EF** BL646 and BL1076 12 volt battery models $\frac{3}{16}$ " & $\frac{1}{4}$ " bit size come complete with crocodile clips and 12ft PVC cable. Just clip on to a car battery.
- GHI** 18 swg top quality cored solder in $\frac{1}{2}$ kilo, 3 oz and handy pack sizes.
- J** Non-corrosive de-soldering braid allows quick easy de-soldering (5 $\frac{1}{2}$ ft spool).
- K** For extra safety use an L686 soldering station.
- L** L68 protective shield for your Invader.



Please send me the following items

PRINT NAME	A INVADER SOLDERING KIT	£4.39	<input type="checkbox"/>
PRINT ADDRESS	B L706 INVADER	£2.23	<input type="checkbox"/>
.....	C L646 INVADER	£2.42	<input type="checkbox"/>
.....	D L1076 INVADER	£2.48	<input type="checkbox"/>
.....	E BL646 BATTERY MODEL	£3.06	<input type="checkbox"/>
.....	F BL1076 BATTERY MODEL	£3.17	<input type="checkbox"/>
.....	G SOLDER REEL $\frac{1}{2}$ KILO	£1.40	<input type="checkbox"/>
.....	H SOLDER REEL 3 OZ	£0.48	<input type="checkbox"/>
.....	I SOLDER PACK	£0.07	<input type="checkbox"/>
.....	J DE-SOLDERING BRAID	£0.76	<input type="checkbox"/>
.....	K L686 SOLDERING STATION	£1.88	<input type="checkbox"/>
.....	L L68 PROTECTIVE SHIELD	£1.08	<input type="checkbox"/>

New Catalogue

All prices include 10% V.A.T. Please tick items required.

ADCOLA PRODUCTS LTD ADCOLA HOUSE GAUDEN ROAD LONDON, SW4 6LH
V A T REGD No 235 6153 72 R I G D No 442762

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER

STEREO AND MONO

Plays 12", 10" or 7" records
Auto or Manual. A high
quality unit backed by BSR
reliability with 12 months'
guarantee. AC 200/250V.
Size 18 1/2 x 11 1/2 in.



£6.25 Post 25p.

Above motor board 21in.
Evo'ow motor board 21in.
With STEREO and MONO XTAL

PORTABLE PLAYER CABINET

Modern design. Black resin covered.
Silver front grille. Padded Lid. Chrome fittings. Post 25p.
Motor board cut for BSR deck.

£4.50

4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watt output. 15 ohm. AC mains operated with
transformer. 3-Controls, volume, treble, bass and On/Off
switch with knobs. Ready made on printed circuit board.
Fused inputs and outputs. Famous make.

Size 5in. wide x 4in. deep x 3in. high.

PRICE £5.95 Post 25p

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with
separate pick-up arm fitted.
L3/78 turnover motor £4.95
compatible cartridges.



GARRARD DECCA HI-FI DECK

Single play Stereo/
Mono Derram
transcription
head and arm.
Four speeds.
10in. inconvertible.
Anti-rumble filter.
Bias compensation.
Laboratory motor.



SPECIAL PRICE £18.50 Post 25p

Ideal for
Disco-Deck

METAL PLINTH AND PLASTIC COVER

Cut out for most Garrard or B.S.R.
Most will play with cover in position.
12 1/2 x 14 1/2 7 1/2 in.
Covered in black leatherette.

£4.95 Post 35p

ALSO AVAILABLE IN SOLID NATURAL MAHOAGANY
WAX POLISHED FINISH—AT SAME PRICE

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 18 1/2 x 10 x 3 1/2 in. Player
unit clips to loudspeakers making it extremely compact.

overall size
only 18 1/2 x 10
x 3 1/2 in. 3 watts per
channel,
plays all records
33 rpm,
15 rpm. Separate
volume &
tone controls.
240V AC mains.



Attractive
Teak finish
Weight 13lbs.

Bargain Price
£25
85p carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way Surface mounting
with fixing screws. Will replace existing
well switch to give light for return home,
garage, automatic anti-burglar lights etc. Variable knob
Turn on or off at full or intermediate settings. Two types
available. Type 'A' 0 to 60 minutes or Type 'B' 0 to 6 hours.
Fully insulated. Makers list price £4.50. Brand new and
fully guaranteed.

OUR PRICE £1.65 or 23 pair. Post 25p.

(PLEASE STATE TYPE A OR B WITH ORDER)



BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in sides
6 x 4 in 45p; 8 x 6 in 53p; 10 x 7 in 65p; 12 x 8 in 85p;
14 x 9 in 90p; 16 x 6 in 90p; 12 x 3 in 60p; 16 x 10 in 21.
ALUMINIUM BOX 3 x 3 x 3 in. 60p. 4 x 4 in. 70p.
6 x 4 x 4 in. 80p. 9 x 4 x 4 in. 21. 12 x 4 x 4 in. 21.30.
ALUMINIUM PANELS 18 s.w.g. 6 x 4 in 9p; 8 x 6 in 15p;
14 x 3 in 16p; 10 x 7 in 19p; 12 x 5 in 20p; 12 x 8 in 28p;
16 x 8 in 28p; 14 x 8 in 34p; 12 x 12 in 40p; 16 x 10 in 50p.
PAXOLIN PANEL 10 x 8 in 16p.

1 1/2 in DIAMETER WAVECHANGE SWITCHES. 25p.
2 p. 2-way, or 2 p. 6-way, or 2 p. 4-way, 25p each.
1 p. 1 2-way, or 4 p. 2-way, or 4 p. 3-way, 25p.
TOGGLE SWITCHES, sp. 14p; dp. 22p; dp. dt. 25p.
Sub-miniature, sp. 20p; dp. 37p; dp. dt. 45p.

R.C.S. STABILISED POWER PACK KITS
All parts and instructions with Zener Diode. Printed Circuit
Board Rectifier and Double Wound Mains Transformer.
Input 200/240V a.c. Output voltages available 6 or 9 or 12
or 15 or 18 or 20V d.c. at 100mA or less.
PLEASE STATE VOLTAGE REQUIRED. £2.20 Post
Details S.A.E. Size 3 1/2 x 1 1/2 in. 20p

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tenor P.U., Guitar, etc. Can be used with
Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size
1 1/2 x 1 1/2 x 1". Response 25 c.p.s. to 25 Kc/s. 26 db gain.
For use with valve or transistor equipment. 99p Post
Full instructions supplied. Details S.A.E. 10p

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
7/350V 14p	250/25V 14p	50+50/300V 60p	
4/350V 14p	500/25V 20p	60+100/350V 85p	
8/450V 18p	1000/25V 35p	22+22/250V 20p	
18/450V 22p	1000/50V 47p	22+22/450V 45p	
32/500V 35p	2500/50V 47p	50+50/325V 55p	
25/25V 10p	8+10/450V 50p	22+22+22/350V/65p	
50/50V 10p	16+10/450V 40p	100+50+50/350V/65p	
100/25V 10p	32+32/350V 40p		

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 16, 25, 30, 60, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 95p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 70p; 35V 85p; 50V 95p.
CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 250V-0.1 4p; 0.5 13p; 1mF 15p; 2mF 150V 15p.
500V-0.001 to 0.05 4p; 0.1 5p; 0.25 5p; 0.47 25p.
SILVER MICA. Close tolerance 1%. 2.2-500pF 5p; 560-
2200pF 10p; 2.700-5.500pF 20p; 6.800pF-0.01, mica 30p each.
TWIN GANG. 200pF 170pF. 60p.
Slow motion drive 365pF + 385pF with 25pF. 25pF. 50p;
500pF standard 65p; small 3-gang 500pF £1.60.
SHORT WAVE SINGLE. 10pF, 30p; 25pF, 55p; 50pF, 55p.

SHORT WAVE SINGLE GANG. Precision Silver Plated
Gangable Tuning Condensers. 50p each
Values up to 100pF.
Section Compliers supplied FREE with two or more gangs.

NEON PANEL INDICATORS. 250V AC/DC Amber. 20p.
RESISTORS. 1 w. 1 w. 1 w. 20%, 1p; 2 w. 5p. 10 10 to 10M.
HIGH STABILITY. 1/2 w. 2%. 10 ohms to 6 meg. 10p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt, 10 ohms
to 100K, 10p each; 2w 0.5 ohm to 3.2 ohms 10p.
TAPE OSCILLATOR COIL. Valve type, 35p.

MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12V 50MA 90p
250-0-250 50 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2.50
350-0-350 50 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £3.00
300-0-300 v. 120 mA. 6.3 v. 3 a. 1.1 a. or 3.3 v. 2 a. £3.25
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p
HEATER TRANS. 6.3 v. 3a. 80p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs
at 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30. £2.80
1 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60. £2.80
2 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60. £3.80
5 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60. £8.75
3 amp., 6, 8 and 12 v. 21.00; Ditto 5 amp. £1.20. 8 amp.,
3, 5, 8, 10, 12 and 6-0-5 v. 21.30. Ditto 5 amp. £1.50;
6-0-5 v. 500 mA 90p. 9 v. 1 amp 90p. 12 v. 300 mA 75p.
12 v. 500 mA 95p. 12 v. 750 mA 95p. 40v. 1 amp £1.75.
AUTOTRANSFORMERS. 110v to 230v or 230v to 115v.
150w. £2.25; 500w. £6.25; 750w. £10.00; 1000w. £15.
CHARGE TRANSFORMERS. Input 200/250v.
for 6 or 12v. 1 1/2 amp. £1.50; 2 amp. £1.80; 4 amp. £2.50
BATTERY CHARGER. Ready built with leads and clips
1 1/2 amp. £2; 4 amp. £4; 6 amp. £4.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS;
6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240v. Secondary 0-240v. 3 amps. 720
watts. Insulated terminals. Varnish impregnated. Fully
enclosed in steel case with fixing feet. £10 Carr.
Famous make. (Value 21p) OUR PRICE 50p
Can be used as 500 watt auto transformers 240-110V.

SET OF 3 MOTORS FOR COLLARO STUDIO TAPE DECK £2.50 Post 50p.

VOLUME CONTROLS 80 Ohm Coax 4p rd.

Long spindles. Midget Size
5 K. ohms to 2 Meg. L09 or
L18. L/S 15p. D.P. 25p.
STEREO L/S 15p. D.P. 25p.
Edge 5K. L/S. Transistor 25p.
Wirewound controls 1 1/2 in. diam. 3 watts. 10 ohms to 100K
British made with long spindles 1in. dia 45p ea.

HELICAL POT 10k LIN L/S 7p. Bargain 76p.
DUAL CONCENTRIC POT 500k LOG 4 500k LIN D.P.
switch. Inner spindle 3 1/2 in; outer spindle 2 1/2 in. 75p.

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With twin tweeters.
And crossover. 10 £4.50
watt. State 3 or 8 or
15 ohm. As illustrated. Post 25p



With flared tweeter cone and ceramic
magnet. 10 watt.
Bass res. 45-80 cps. £2.75
Flux 10,000 gauss.

State 3 or 8 or 15 ohm. Post 25p

Bookshelf Cabinet 16 x 10 x 9 in. Teak Veneer £5.50 Post 25p

GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet
Special Cambric cone surround.
Frequency response 30-12,000 £4
cps. Ideal P.A. Columns,
Hi-Fi Enclosure Systems, etc.
Suitable cabinet 12 x 8 x 6 1/4 in.
Suitable Tweeter 22-00.



ELAC CONE TWEETER

The moving coil diaphragm gives a good
radiation pattern to the higher frequencies
and a smooth extension of total response
from 1,000 cps to 18,000 cps. Size 8 1/2 x
3 1/2 x 2 in. deep. Rating 10 watt, 3 ohm or
15 ohm models. £1.90
Crossover 95p.

GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone.
Heavy ceramic magnet. Bass
response 35 cps. Frequency
response 30-3,000 cps.
Ideal bass unit for £3.75
Hi-Fi systems



LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1.95; 6 1/2 in. £1.60;
5 x 6 in. £1.60. 8 in. £1.75; 10 x 6 in. £1.90; 10 in. £2.00.
SPECIAL OFFER! 80 ohm, 2 1/2 in. 2 1/2 in. 85 ohm, 2 1/2 in.;
8 in. 25 ohm, 2 1/2 in. dia.; 3 in. dia.; 15 ohm. £1 EACH
3 1/2 in. dia.; 5 in. 7/8 x 4 in.; 7 x 4 in.; 8 x 5 in. TYPE
3 ohm, 2 1/2 in., 3 1/2 in., 5 in. dia. (6 x 4 in., 8 ohm, £1.50).
RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in.
diameter 4W £2.50, 12 in. diameter 5W £2.50; Post 25p.
12 in. diameter, 6W. £2.95; 3 or 8 or 15 ohm models.
SPEAKER COVERING MATERIALS. Samples Large S.A.E.
FERRITE ROD 8" x 1" 20p; 6" x 1" 20p; 3" x 1" 10p.
Horn Tweeters 2-16Kc/s. 3W 8 ohm or 15 ohm £1.95.
De Luxe Horn Tweeters 2-18 Kc/s. 15W, 15 ohm £3.50.
TWO-WAY, 3,000 c.p.s. CROSSOVERS 3, 8 or 15 ohm 95p.

TWO-WAY CROSSOVER NETWORK 3,000 c/s
With variable tweeter attenuator giving accurate high/low
frequency balance. Mounted on panel 5 1/2 in. x 4 in. with
control knob, tweeter and woofer leads and input £2.20 Post 25p
terminals. Suitable for 3 to 8 ohm impedance.

VALVE OUTPUT TRANSFORMER 95p
MIKE TRANSFORMER MU. metal 100-1 £1.25.
5 WATT MULTI RATIO. 3, 8 and 15 ohms, 50p.
PUSH-PULL VALVE OUTPUT TRANSFORMERS.
50 watt £11.60 100 watt £14

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5v d.c. operation over 100 hrs. continuous on SP2 battery.
Fully adjustable swing and speed. Ideal displays teaching
electro magnetism or for metronome; strobe etc. 85p, Post 20p

BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors plus integrated
circuit. Fibre glass printed circuit board.
Size 2 1/2 x 6 1/2 in. Pre-aligned. Complete
with stereo beacon indicator. 12V d.c.
operation. 400mV output for 100mV input.
Full instructions for any FM Tuner. Some
technical experience essential. £6.50
DIPLOE LEFT AERIAL £1.50.
50 OHM CABLE 4p yard. Post 15p
300 OHM CABLE 5p yard.



COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p
OUTLET BOXES. SURFACE MOUNTING 25p.
BALANCED TWIN RIBBON FEEDER 200 ohms. 5p rd.
JACK SOCKET Std. open-circuit 14p. closed circuit 28p;
Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p
JACK PLUGS Std. Chrome 15p; 3.5mm Chrome 12p. DIN
SOCKETS Chassis 3-pin 10p; 6-pin 10p. DIN SOCKETS
Lead 3-pin 15p; 5-pin 15p. DIN PLUGS 3-pin 15p; 6-pin 25p.
VALVE HOLDERS 9p; CERAMIC 5p; CANS 5p.

BRITISH FM/VHF TUNING HEART
88 to 108 Mc/s British made. 2 Transistors
ready aligned—requires 10.7 Mc/s IF. Complete with tuning gang.
Connections supplied but some
technical experience essential. Post 20p.
£3.95

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 20p.

RADIO COMPONENT

Illustrated Colour Brochure, Radio Books & Component Lists 10p. Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

THE PAIR. Post 25p.
(Available separately.
Woofer £4.25; Tweeter
£1.90).

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet. 44oz. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 25 to 18,000 cps
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in.
MODERN DESIGN. TEAK WOOD FINISH.



£9.90

Post 25p

8 in. or 10 in. ELAC HI-FI SPEAKER



Dual cone plasticized roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8 in. 10 watts. 10 in. 12 watts

£3.75

TEAK VENEER HI-FI SPEAKER CABINETS

Fluted Wood Fronts

MODEL "A". 20 x 13 x 9 in.
For 12 in. dia. or £9.90 Post 25p

MODEL "B". 16 x 10 x 9 in.
For 13 x 8 in. or £5.50 Post 25p

MODEL "B2" ditto. Triangular corner version.

MODEL "C". 16 x 8 x 6 in.
For 8 x 5 in. £4.40 Post 25p

LOUDSPEAKER CABINET
WADDING 18 in. wide. 15p ft.



BARGAIN AM TUNER.

Medium Wave.
Transistor Superbet
Ferrite aerial. 9 volt. £4.95

BARGAIN 4 CHANNEL
TRANSISTOR MONO
MIXER. Add musical
highlights and sound effects
to recordings. Will mix
Microphone, records, tape
and tuner with separate
controls into single output.
9 volt battery operated.

£3.95

STEREO VERSION OF ABOVE £5.95

BARGAIN FM TUNER.

88-108 Mc/s Six Transistor.
9 volt. Printed circuit.
Calibrated slide dial tuning.
Walnut Cabinet.
Size 7 x 5 x 4 in. £12.85

BARGAIN FM TUNER. £8.85

As above less cabinet.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor
Push-Pull Ready built with volume, treble and
bass controls. 18 volt battery operated.

£4.50

THE "INSTANT" BULK TAPE

ERASER & HEAD DEMAGNETISER.
Suitable for cassettes, and all sizes of
tape reels. A.C. mains 200/250V.
Leadset 8 A.E. £2.50 Post 20p



WAFER HEATING ELEMENTS

THIN OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos filled with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopiers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater.

Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £9.90



Post Free
30-14,500 c/s. 12 in. double cone, woofer and tweeter come together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50

Please state 3 or 8 or 15 ohms. Post Free

BAKER "BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" £8.80
12 in. 25 watt
3, 8 or 15 ohms.

GROUP "35" £9.90
12 in. 35 watt
3, 8 or 15 ohms.

GROUP "50" £22.00
15 in. 50 watt
8 or 15 ohms.

NEW 12" VERSION £17.60



MAJOR 100 WATT

ALL PURPOSE
TRANSISTOR
AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details 8AE.



£49 Carr. £1.00

Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw

Sizes	Price
1/2"	74p
3/4"	83p
1"	89p
1 1/4"	92p
1 1/2"	99p
1 3/4"	99p
2"	13p
2 1/2"	£4.50
3"	£5.75
3 1/2"	£9.00
4"	£1.20
4 1/2"	£1.15
5"	£1.20
5 1/2"	£1.35
6"	£1.70
1 1/2" Key 'B' for above 10p	£1.70
2" Key 'B' for above 10p	£2.25
2 1/2" Key 'B' for above 10p	£2.50
3" Key 'B' for above 10p	£3.30
3 1/2" Key 'C' for above	13p
4" Key 'C' for above	£4.50
4 1/2" Key 'C' for above	£5.75
5" Key 'C' for above	£9.00
5 1/2" Key 'E' for above 20p	£1.35
6" Key 'E' for above 20p	£2.10

SLIDER VOLUME CONTROLS

Available in both LOG and LINEAR type. Size 9/16 x 1 x 1/2 in. with knobs. 5K, 10K, 25K, 50K, 100K, 250K, 500K, 1 MEG, 2 MEG.



65p EACH

DELUXE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt. spindle 1 1/2" x 7/32", size 3 1/2" x 3". As illustrated, 240V. AC mains. £1.95 Post 25p

E.M.I. GRAM MOTOR

120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. £1.00 Post 25p.

ONE RPM GEARED MOTOR

240v. A.C. mains. Ideal for displays/disc lightwheels. £1.25 Post 25p.

BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

REGENT

12 in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models.

£8.80 Post Free




DE-LUXE Mk II

12 in 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000gauss
Useful response 25-18,000cps
8 or 15 ohms models.

£11 Post Free

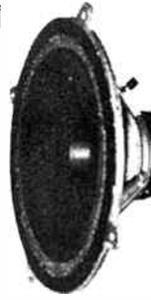

SUPERB

12 in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 16,500gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£16.50 Post Free



AUDITORIUM

12 in. 25 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques.

Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 25-18,000cps
8 or 15 ohms models.

£15.40 Post Free



AUDITORIUM

15 in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£22 Post Free



Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free.

CALLERS WELCOME • CUSTOMERS FREE CAR PARK OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15-2-30

SPECIALISTS 337 WHITEHORSE ROAD GROYDON

(Exports Remit cash and extra postage.) Buses 50, 68, 159. Rail Selhurst Telephone 01-684-1665

"STEAM" ROLLING

ANUAL Reports and Accounts of major organisations do not usually make exciting reading, but the latest from the IBA is different because of the entries describing the planning of independent commercial radio under the IBA banner.

Most of the information we are either aware of already, or we took for granted as being necessary minimum standards that are laid down to match the existing performance by the BBC. However, one or two interesting points emerge that have an important bearing for the listening audience.

The IBA, with very good reason, intends to encourage the major proportion of listening on v.h.f. The International Telecommunication Union is due to review the allocation of m.f. bands, under the present Copenhagen Convention and Plan, in 1974-5. Any proposed revisions are expected to take effect from 1976 and both the BBC and the IBA are expecting a reduction in the m.f. allocation largely due to "overcrowding". In the meantime both organisations continue to operate sound broadcasting on m.f. as a back-up for v.h.f.

The crunch is in sight for the listeners because it looks as if they must expect, after nearly twenty years of v.h.f. broadcasting, to convert to v.h.f. reception or go without. We have heard the pros and cons of v.h.f. and m.f. so many times that we will not pursue the matter here. Suffice it to say that the IBA are looking ahead to the "day of judgement" by planning in force for circular polarised transmitting aerials to compromise between horizontal and vertical polarised receiving aerials.

The m.f. transmitting aerials will be directional systems using three or four mast radiators so that several stations can transmit over a restricted area on 1151kHz. The radiated power will vary from one station to another, depending on local conditions, but in London it will be 0.5 to 1kW; elsewhere up to 5kW, with an 8kW mf1 and 30kW mf2 signal from Saffron Green (not until later next year) for London, when the IBA have finished with the installations at Lots Road Power Station.

The method of m.f. transmission adopted is not commonly used in Europe and it makes one wonder why not, even if large sites are necessary.

The other disturbing thought is the increasing availability of stations broadcasting on v.h.f. With the undesirable side-effects (such as "birdies" and inter-modulation distortion) and the greater sensitivity of tuner front-ends, we forecast a congestion (or indigestion!) problem on v.h.f. in the U.K. within the next five years. Some serious thinking and re-appraisal is therefore going to be needed with a view to extending the broadcast v.h.f. range below 88MHz; although we understand that a clash has occurred in Hertfordshire and the police service is expected to be moved to another frequency, it would be wishful thinking to expect the emergency services to be transferred out of their present 97MHz-plus domain.

M. A. COLWELL—*Editor*

The January issue, on sale 7th December, will include an Ultrasonic Remote Control Unit to switch on the television, radio, lamps, or almost any electrical device or appliance, without moving out of your armchair; a practical way of housing plug-in circuit boards; a signal generator for testing and fault finding in radio and audio equipment; an article dealing with radio interference problems in audio equipment; and first details of our plans for some of the spring issues of Practical Wireless, including some superb new ideas to help you make the most of d.i.y. radio and electronics.

Further details on page 751.

NEWS...

Mid-Lanark A.R.C.

THE above club has sent us some details of the future programme. There will be a bring-and-buy sale on Nov. 9, a demonstration of stereo radio and quadrasonic sound by GM3UCI on the 23rd and the A.G.M. on December 7th. December 21st is called "Oklahoma" and GM3BVU will give a talk on Amateur radio in the U.S.

Meetings are held at 7.30 in the Wrangholm Hall Community Centre, Jerviston Road, Motherwell.

Sonex 74

THE venue for Sonex 74 European High Fidelity Exhibition will be The Post House Hotel, London Airport and the dates March 29th to March 31st.

WIRELESS TELEGRAPHY ACT

Readers and advertisers are reminded of the requirements laid down by the Wireless Telegraphy Act. It is an offence in the U.K. to install or operate wireless telegraphy apparatus except under the provisions of the Act and, except in the case of broadcast sound-only receivers, a licence must be obtained from the Minister of Posts and Telecommunications.

Included within the provisions of the Act are any apparatus transmitting deliberate signals for any purpose such as "walkie-talkies", radio-controlled models or servos and some types of metal detectors. Apparatus radiating interference signals are subject to controls which also come under the administration of the same Ministry. If you require full information, please write to the *Ministry of Posts and Telecommunications, Waterloo Bridge House, Waterloo Road, London, SE1 8UA.*

CRATA IS COMING

Watch P.W. for details

Open University Course

ELECTROMAGNETICS and Electronics, a Post-experience course by the Open University, aims to provide an understanding of the scientific basis of electronics and electronic circuit design.

The course is intended for those preparing for higher level university study in science and technology and for those who need a knowledge of electronics but who do intend to study at a higher level.

It assumes little prior knowledge of electronics or electromagnetics but does assume a background of scientific or technical education beyond GCE "O" Level.

The first part deals with the basic ideas of electricity, magnetism and electromagnetism, semi-conductors and the properties of simple circuits. The remainder deals with electronic circuits, stressing the need to design circuits to meet specifications of noise, distortion, output voltage as well as gain and input and output impedance.

Applications are now invited for the course which starts next February and lasts until November. As with all Post-experience courses, no formal academic qualifications are needed. They are self-contained courses designed to teach new developments or update knowledge of a subject.

The course consists of 17 written correspondence units linked to 17 television and five radio programmes. Students are required to attend a one week residential summer school and encouraged to attend evening or Saturday tutorial sessions. There are 12 assignments to complete and an examination at the end of the course.

A home experiment kit, including a cathode-ray oscilloscope and a signal generator, is sent to students who are expected to design and build circuits for checking at summer school.

Some elementary mathematics is required for the course. Students should know elementary calculus, the meaning of sine, cosine and imaginary numbers. A preparatory booklet is issued at the beginning.

The course tuition fee is £45 plus £37 for the residential summer school. Application forms are available from *The Post-experience Student Office, P.O. Box 76, Milton Keynes, MK7 6AA.*

Scottish show cancelled

BECAUSE of lack of interest, the Scottish International Hi-Fi Exhibition has been cancelled. Only 12 of the expected 27 firms confirmed their bookings for the show.

The organisers feel that the reason for the lack of interest is that many companies have stretched their budgets by representation at the Harrogate and Olympia shows.

What of D.N.L.?

PHILIPS Ltd. will be using the Dolby-B noise reduction system!!

Tyne/Wear radio contract

AFTER interviewing the six applicant groups for the Tyne/Wear radio contract, and giving full consideration to the written applications, the Independent Broadcasting Authority has announced that it has formed the view that Metropolitan Broadcasting is the leading contender.

The Authority now proposes, subject to contract, to offer the franchise to Metropolitan, the chairman of which is Sir John Hunter.

The company's programme plans will be published when it begins broadcasting — probably during the summer of 1974.

More for SQ

MORE manufacturers are getting onto the quadrasonic bandwagon by building SQ decoders into their equipment. Companies like Braun, Grundig, Korting, Philips, Revox, Saba, Sharp, Siemens have taken out SQ licences with CBS.

New 4-channel system

ANEW quadrasonic sound system devised by Duane Cooper and developed by Nippon Columbia was demonstrated at the Berlin Radio Show. The new system is called New Discrete or Discrete Matrix. It is said to have certain advantages over other quadrasonic systems because of its dual nature. A typical set-up would use a two-channel matrix for surround sound named BMX. This involves 45° phase shifts between the speakers rather than conventional 90° ones.

If increased definition in image placement should be required, a demodulator for the carrier channels on the records would be added, giving the set-up a potential 20dB separation between channels at mid-frequencies.

The Discrete Matrix system allows the two extra channels contained on the gramophone record to be of a narrow bandwidth resulting with the maximum frequency of the record being 36kHz compared with 45kHz on the CD-4 records.

Noise reduction techniques are not employed with this system, so making demodulators potentially cheaper.

Physics Exhibition


THE Council of the Institute of Physics has decided that the Physics Exhibition should now be discontinued, and the show arranged for 1975 will now not take place.

In recent years the number of visitors to the exhibition has decreased considerably as have the number of industrial firms and other concerns that used to have exhibits there.

The very first Physics exhibition was held by the Physical Society in 1905. The one held in 1973 was the fifty-seventh in this series.

BAND SWP RECEIVER

F. G. RAYER G30GR

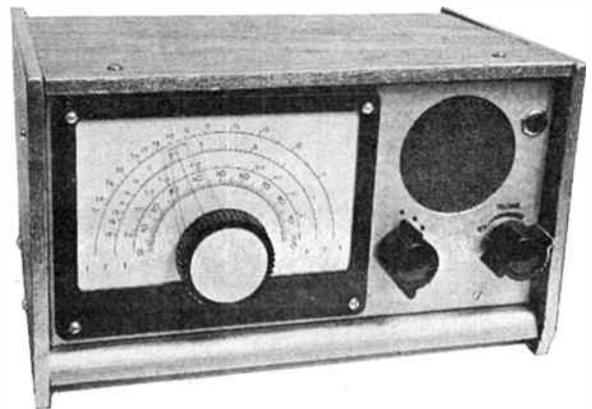

THIS receiver employs two transistors and two IC's, one of the latter in the intermediate frequency amplifier section and the second in the driver and output stages. It has band switching and covers all the important short wave ranges, including the low frequency bands, which are not included in some short wave or "all-wave" receivers.

The receiver has a very inexpensive but quite attractive cabinet and operates an internal loud-speaker, a jack allowing headphones to be plugged in when preferred.

MIXER STAGE

The mixer section is shown in Fig. 1 and uses six miniature coils, the appropriate coils being selected by the 3-way 6-pole rotary switch. Each range is separate from the others and two coils are in circuit for each range. L1, L2 and L3 are the aerial coils, and L4, L5 and L6 the oscillator coils.

The six poles of the switch are numbered from S1 to S6. Pole S1 takes the aerial circuit to the aerial coupling windings of the aerial coils and S2 transfers the aerial tuning section of the gang capacitor, VC1, to the correct coil, for aerial tuning purposes. Pole S3 connects the base of Tr1 to the base coupling windings, as necessary. The earthed ends of all aerial coupling windings (pin 9) and tuned windings (pin 1) are permanently connected to the chassis, while all the base coupling windings are returned to the base bias network R1/R2.

In a similar manner, switch section S4 selects the collector coupling windings of the oscillator coils L4, L5 or L6, while S5 connects the emitter of Tr1 to the appropriate emitter winding. S6 selects the tuned windings of the oscillator coils which are tuned by the second section of the ganged capacitor, VC2.

All the emitter windings (pin 7 of each coil) are returned to the emitter bias circuit, C2 and R3. In the same way, each collector winding (pin 8) goes to the IF amplifier.

In order to secure proper coverage and tracking, oscillator coil L5 has a padder capacitor CP1 of 3000pF from pin 4 to chassis. L6 has a 1000pF capacitor CP2 from pin 3 to chassis while L4 requires no padder, pin 6 being wired to the chassis.

If the circuit in Fig. 1 appears difficult to follow, it is suggested that the switch is set at its middle position and L2 and L5 wired in. The receiver can then be tested on this band. When it is found to be in order L1 and L4 can be added and wired and a check made that this works correctly, before adding L3 and L6. This is much better than wiring in all the coils, then perhaps finding that a mistake has been made with the switch contacts or the operation of the switch, so that some wiring error is difficult to locate and correct. To avoid any possible confusion here, the bands, approximate coverage, and maker's range numbers are as follows:—

Band	Coverage	Maker's Range No.
A	30—10.5MHz 10— 28m	5T
B	15— 5 MHz 20— 60m	4T
C	5— 1.7MHz 60—180m	3T

L1 and L4 are for Band A, L2 and L5 for Band B and L3 and L6 for Band C.

In order to avoid squegging, or spurious oscillation and hissing spoiling reception, resistors R4, R5 and R6 are included in the individual collector circuits to L4, L5 and L6. The best values for these resistors depend on Tr1. Gain is maximum when these resistors are of the lowest values which allow proper working of this stage. The values shown should certainly be satisfactory, but it is an easy matter to have on hand a few resistors of various values between about 100 Ω and 1k Ω (say about half a dozen different values) and try these in series with the circuit to pin 9 of each range, while tuning over the range. Excess oscillation is most likely at the high frequency end of any one band (VC2 nearly fully open).

Trimmers TC1, TC2 and TC3 are for aerial circuit trimming and each is adjusted on the appropriate band.


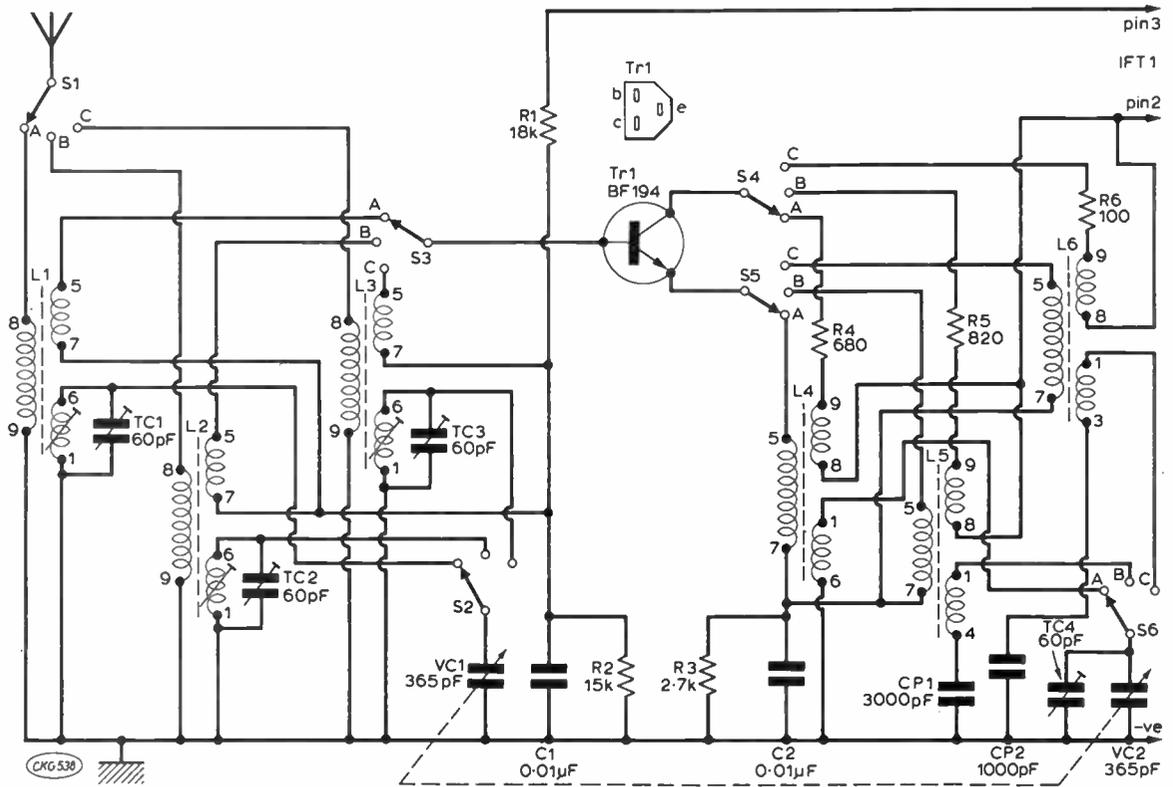


Fig 1, above, and Fig 2, below, give the complete circuit of the receiver.

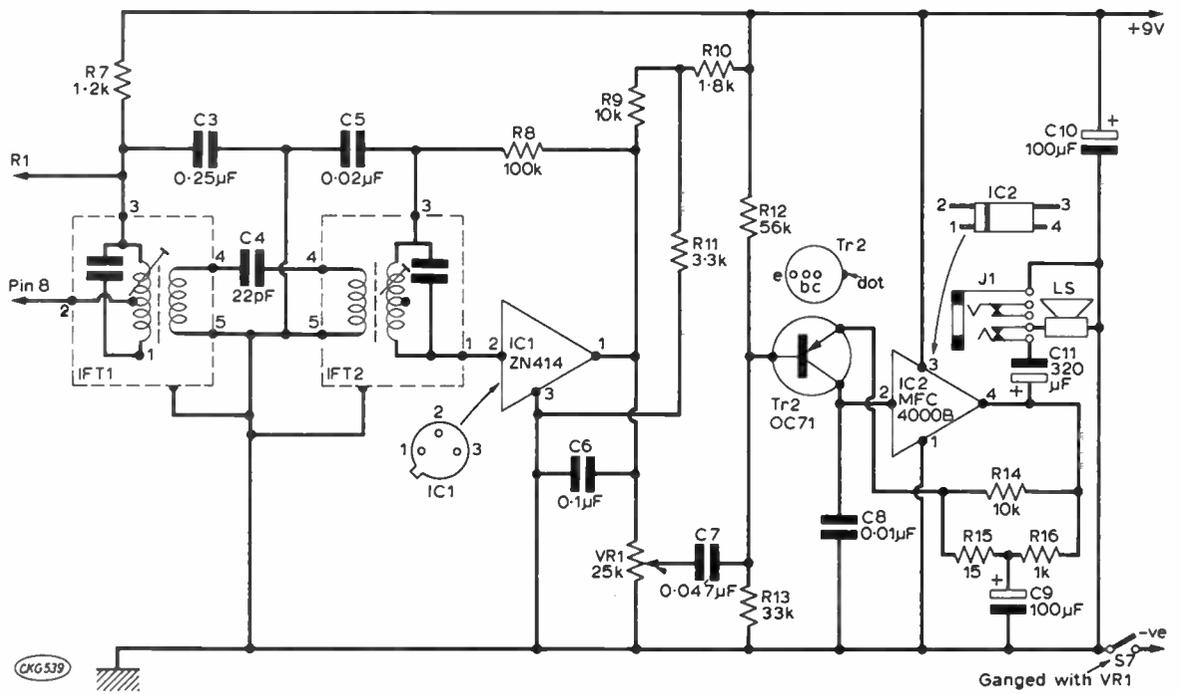

IF AMPLIFIER

Fig. 2 is the circuit of the intermediate frequency amplifier and audio amplifier, which are constructed on one small circuit board. The IF filter consists of two loosely coupled units, IFT1 and IFT2, tuned to 470kHz.

Output from IFT2 goes to IC1 which provides three stages of amplification at 470kHz and includes automatic gain control and detection circuitry, giving an audio output which is taken to the volume control VR1.

Resistors R10 and R11 form a potential divider across the 9V supply and current is taken by IC1

and VR1 through R9. This means that the circuit should not be operated with VR1 disconnected and that this potentiometer should be of the value given.

The mixer stage is fed from its own positive supply point at the junction of C3 and R7.

AF AMPLIFIER

Tr2 is a high gain pre-amplifier, followed by IC2 which has 6 transistors and 3 diodes in a driver-push-pull output circuit which delivers approximately 250mW to a 16Ω speaker. This IC is very economical on battery current and the output is easily adequate for normal loudspeaker reception. The load impedance is not too critical, so that speakers of higher impedance may be used. R14, R15 and R16 provide direct current feedback to stabilise the whole audio amplifier.

CIRCUIT BOARDS

The mixer board is approximately 1¼ x 1½in, Fig. 3, with a bracket fixed as shown and a tag serving as a return point for C1, C2, R2 and R3. This bracket must be bolted tightly to the metal chassis so that the board is connected to the negative line.

External connections will be required to a few points. These can be made by providing Veropins, or by leaving a projecting wire, so that leads can be soldered on as necessary.

The small pins of Tr1 project from the underside of the board and connecting wires are soldered directly to them which will run to the sections of the bandswitch, as indicated in Fig. 3.

Both sides of the IF/AF board are shown in Fig. 4 and it is approximately 3¾ x 1¼in. Holes should first be drilled to clear the pins and can tags of the two IF transformers. If any small error is made when drilling these, they can be enlarged or elongated as necessary with a very small round file. Drill holes for two 6BA bolts, one marked MC is fitted with a tag which forms the negative return

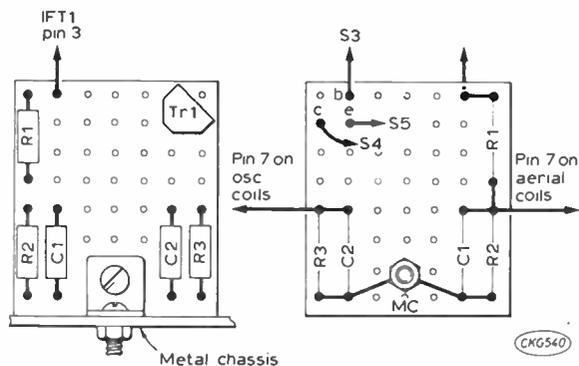


Fig. 3: Layout of components on the mixer board.


to the metal chassis. These bolts should be at least ½in. long so that spacers or extra nuts will allow the board to be clear of the metal chassis.

C4 is underneath, directly from pin 4 of IFT1 to pin 4 of IFT2, but all other items are on top of the board. Position these as shown, noting the polarity of electrolytic capacitors.

In most places the wire ends of the resistors and other items are long enough to reach the connecting points. Elsewhere, 24 s.w.g. tinned copper or similar connecting wire can be used. Sleeving is put on all leads which cross other wires and anywhere else where this appears necessary.

Two thin flexible leads are soldered on to connect to the speaker. A red flexible lead, with a positive battery clip, is also provided, as shown.

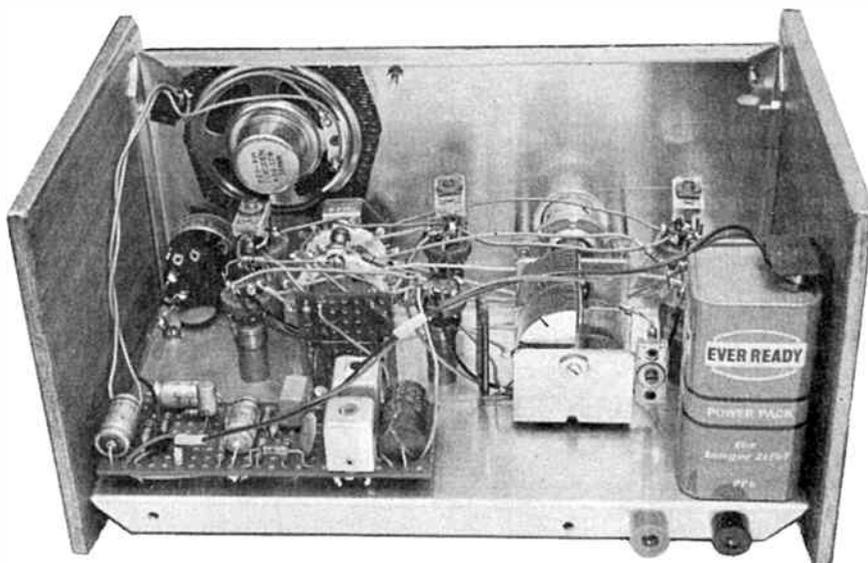Colour coded leads also run from R9 and the base of Tr2. C7 is soldered directly on the centre tag of the volume control, VR1. Fit a colour-coded lead from C3, to run on to R1 on the mixer board. A further lead is taken from pin 2 of IFT1, up through the board as in Fig. 4, and will be soldered to the circuit which connects pins 8 on the oscillator coils.



Rear view of receiver showing position of IF/AF board at front left with mixer board immediately behind.

★ components list

Resistors

R1 18kΩ	R7 1.2kΩ	R13 33kΩ
R2 15kΩ	R8 100kΩ	R14 10kΩ
R3 2.7kΩ	R9 10kΩ	R15 15Ω
R4 680Ω*	R10 1.8kΩ	R16 1kΩ
R5 820Ω*	R11 3.3kΩ	
R6 100Ω*	R12 56kΩ	VR1 25kΩ log with switch, S7

Resistors ½W 5%. * See text

Capacitors

C1 0.01μF	C9 100μF 10V
C2 0.01μF	C10 100μF 10V
C3 0.25μF	C11 320μF 10V
C4 22pF	CP1 3000pF
C5 0.02μF	CP2 1000pF
C6 0.1μF	VC1/2 2 x 365pF (Jackson Type O. Cat. No. 5250/2)
C7 0.047μF	TC1-4 60pF pre-set trimmers
C8 0.01μF	

Semiconductors

Tr1 BF194	IC1 ZN414	} S.C.S. Components POB 26, Wembley, Middx.)
Tr2 OC71	IC2 MFC4000B	

Miscellaneous

IFT1/2 (Denco IFT13). L1, Blue 5T. L2, Blue 4T. L3, Blue 3T. L4, Red 5T. L5, Red 4T. L6, Red 3T. (All Denco). Tuning drive (Jackson Type 6/36 Cat. No. 4103). S1-6, 2 wafer switch, each 3 pole 3 way. Speaker, 2½in, 25 to 40Ω. Universal chassis members, 8 x 4in (2) (Home Radio). Switched output jack socket. Aerial and earth sockets. Veroboard 0.15in matrix, 1½ x 1³⁄₁₆in approx. and 3½ x 1¼in approx. Wood for cabinet. Knobs.

undue heating. It should only be necessary to keep the soldering iron in contact with the joint for a second or two. Lengthy heating may damage these items.

This circuit board should not be tested without VR1 and the loudspeaker being connected.

If a signal generator is to be used to adjust the circuits, couple this loosely to the lead running to pin 2 of IFT1. It is only necessary to place the generator lead near this lead with no actual connection. The cores of IFT1 and IFT2 should then be adjusted, with a proper tool, for best output.

When no generator is available, adjustment should prove quite easy as the IFTs are pre-aligned by the maker. It is then only necessary to tune in a stable signal and adjust each core for best volume. The cores should have a sharp resonance peak. Again, it should be stressed that a properly shaped tool must be used, as a wedge-shaped blade may easily break the cores so that they cannot be rotated, while inserting a steel or similar screwdriver will upset correct alignment.

The audio section should be found to provide good amplification and adequate loudspeaker volume. The small internal speaker will give quite reasonable audio quality, for SW listening purposes. A larger, external speaker may be plugged in (as well as phones) and this will naturally give some improvement. It should be of suitable impedance, about 16 to 25Ω. Though a small speaker can give satisfactory results, it cannot be expected to be quite as good as a larger unit operating with its own cabinet or baffle.

CONSTRUCTION

IC1 has three leads, positioned as in the underside view of this component, in Fig. 4. IC2 has four spills, 2 and 3 being longer, as in Fig. 4. If this IC is located as shown, the tags will fit the Veroboard holes correctly and connections being soldered on underneath. Both ICs should be soldered without

The chassis is a "universal chassis" flanged member 8 x 4in. with a second similar member used for the panel. The front edge of the chassis is set back ½in. from the panel, as in Fig. 5, using two ½in. spacers and two ¾in. countersunk 6BA

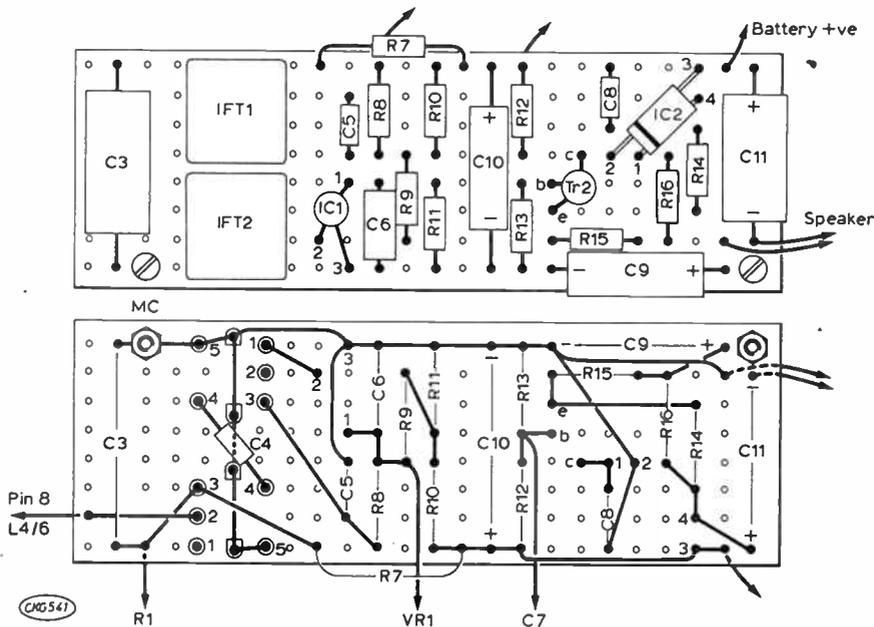


Fig. 4: The two sides of the IF/AF board and connections to the remainder of the circuit.

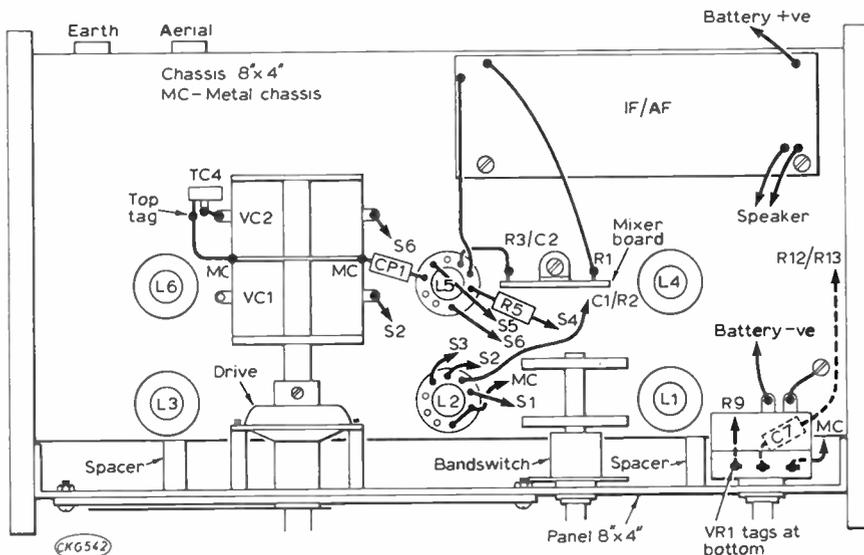


Fig. 5: Layout of major components on top of the chassis and interconnections.


bolts, which run through the panel and the front flange of the chassis. (These two bolts with spacers are not absolutely essential, as chassis and panel are held in position by the case sides. However, with the bolts securing these parts together, assembly and testing can be completed before fitting the sides in position, and wiring is thus more easily reached.)

Locate the drive template on the panel and drill the fixing holes for it and for the dual-speed ball drive. A large hole is also punched for the projecting part of the drive which carries the cursor.

Position the bandswitch and VR1 as in Fig. 5,

keeping these as low as possible to leave room for the speaker. The speaker opening is made with a large chassis punch or adjustable washer or tank cutter, or by drilling a ring of small holes and clearing up the edge with a half-round file.

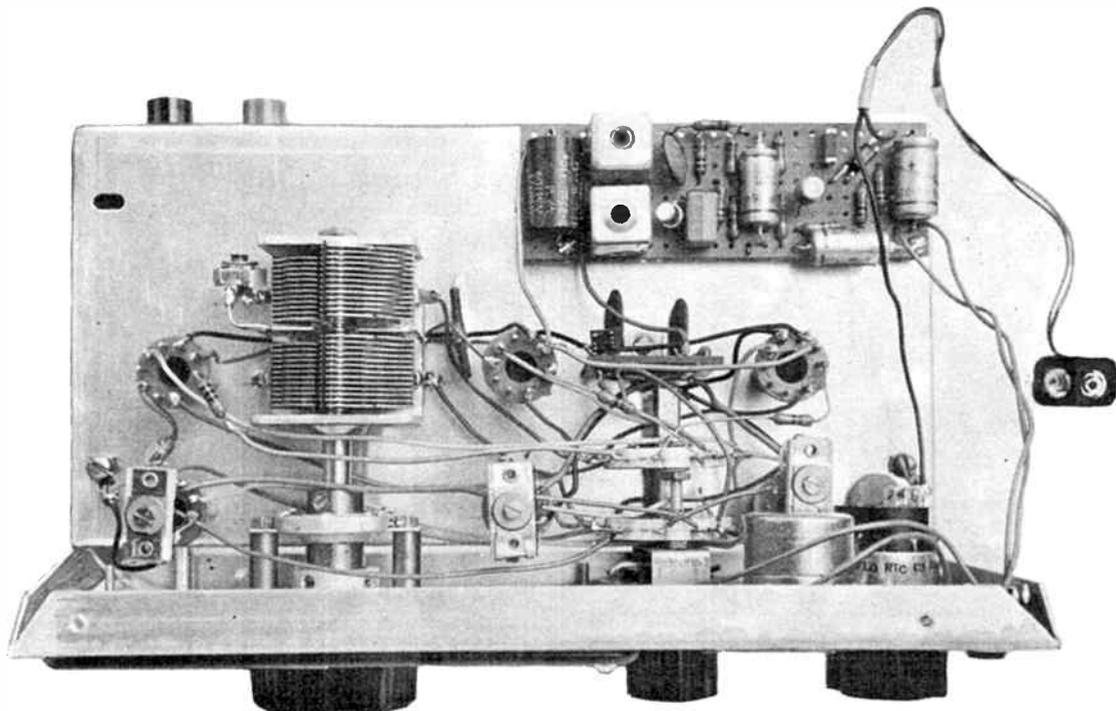Check that the panel and chassis are correctly fixed and at right angles, then fit the ganged capacitor into the drive and drill the fixing holes for the capacitor. Washers are placed under the capacitor to bring it level with the drive. The position of the drive and capacitor should be carefully adjusted as necessary so that they are in line and turn smoothly.



General view of receiver from above to assist in locating components shown in Fig. 5.

Holes $\frac{1}{4}$ in. in diameter are drilled for the six coils, which are located as in Fig. 5. Their fixing nuts should be tightened with the fingers only. Pins are counted in a clockwise direction from the space, from 1 to 9, and wiring is simplified if all the coils are positioned so that their pins are approximately in the same direction.

The IF/AF amplifier board and mixer board are fixed as in Fig. 5, but it is easier to leave these off until most of the wiring has been done to the lower tags of the switch, which are otherwise difficult to reach.

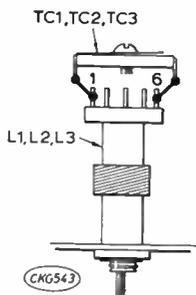


Fig. 6. Method of mounting trimmers on top of the coils.

Trimmers TC1, TC2 and TC3 are mounted directly across the coils L1, L2 and L3 as in Fig. 6. Short, stout wires are soldered to pins 1 and 6 of each coil, for this purpose, when wiring the receiver. It is preferable to take the upper plate tag of the trimmer to the earth side of the circuit (pin 1) in each case.

The single oscillator trimmer, TC4, is soldered to the ganged capacitor as in Fig. 5, the top tag being connected to the capacitor frame by a stout wire. A check should be made that the tuning capacitor fixing bolts are not too long, or they may touch the fixed plates of the capacitor.

A bandswitch with two wafers was used. The front wafer switches the aerial, base and VC1 circuits while the rear wafer is employed for the oscillator coils.

It is not essential to use a two-wafer switch provided the required number of poles are available and the switch is small enough to be accommodated.

Fig. 7 shows connections to the switch. It will be found very helpful to use colour-coded leads here. With the aerial coils, yellow may be used for aerial and S1 circuits, with red for base and S3 circuits, and green for S2, VC1 and associated circuits. For the back wafer, red can be used for S4, yellow for S5, and green for S6. Chassis returns to the coils can be black and the base bias circuit to C1/R2 may be blue. Whatever colours are used, employ them exclusively for one circuit.

It is also helpful to solder on lengths of wire, before mounting the switch, where the tags will be near the chassis, and hard to reach later. These wires can then be cut to length and taken to the various coils.

If the contacts of the switch cannot be seen, and its operation is not wholly clear, test it for continuity with a meter, in each position. Also it is advisable to wire, in the coils for one band only, to confirm that no error is being introduced here, before proceeding with the other ranges.

Pressure should not be imposed on the coil pins when these are hot, so a little care is required when soldering these to prevent them moving when the insulation softens.

The volume control is mounted as in Fig. 5. Connect the lower tag to S7 and to the metal chassis. Run a lead from the other outer tag, under the chassis and up through a hole near the AF amplifier, where it is soldered to R9, Fig. 4. Solder C7 to VR1 slider and take a further insulated lead under the chassis and up through to the junction of R12 and R13.

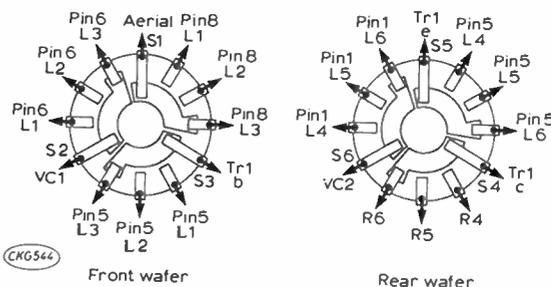


Fig. 7. Details of the wiring on the bandchange switch wafers.

ALIGNMENT

Alignment of the IFTs has been described. To align the aerial and oscillator coils, deal with one band at a time. Adjust the coil cores at a low frequency in the band (VC1/2 nearly closed) and the appropriate trimmer at a high frequency in the band (VC1/2 nearly open).

TC4 is initially set about half closed. If it is subsequently found that TC1, TC2 or TC3 is fully open for best volume, TC4 should be screwed down slightly. Provided TC1, TC2 and TC3 each have a definite peak giving best volume, there is no need for a separate trimmer for each oscillator coil.

Coverage is primarily determined by the settings of the oscillator coils and TC4. If a signal generator is available, set VC1/2 5° from the fully closed position and adjust the core of L4 for reception on 10.5MHz; similarly adjust L5 for reception on 5MHz, and L6 for reception on 1.67MHz.

L1 should then be adjusted at 11.5MHz for best volume. L2 is similarly adjusted at 5.5MHz, and L3 at 1.83MHz. VC1/2 is then opened to tune to 28.5MHz, and TC1 is adjusted. TC2 is adjusted at 13.5MHz, and TC3 at 4.5MHz.

These adjustments are repeated until no further improvement is possible. These frequencies are the most effective tracking points for the low frequency and high frequency end of each band and result in best tracking throughout the whole range.

CALIBRATION

The tuning drive listed has a scale marked 0-100°, in addition to scales for individual calibration. Set the cursor to 100° with the tuning capacitor fully closed. If calibrated as described the following points, read against the 0-100 scale, may be used as a guide to intermediate frequencies:—

Welcome to the company that really knows about the devices it supplies. Send 12p for our latest Datalogue & enquiry form details.

RADIO IC SELECTOR All compatible with TOKO filter blocks

TYPE No.	MODES	SENSITIVITY	FULL DATA	DEVICE £
TAD 100	AM inc.det.	4 μ V for 9dB SN/N	23p	1-55
TBA 651	ALL	1 μ V - 6dB --	54p	2-00
TBA120A	FM inc.det.	15 μ V-limiting begins-10.7MHz	23p	1-07
CA 3088E	AM inc.det.	200 μ V for 20dB SN/N	16 p	1-50
CA 3089E	FM inc.det.	12 μ V for 3dB limiting AFC-SQUELCH- AGC-TUNING METER DRIVER.	25p	2-20

PLESSEY - NATIONAL - FAIRCHILD pro. communication ICs to order

TOKO BLOCK FILTER SELECTOR

TYPE	FREQUENCY	BANDWIDTH kHz	USAGE	PRICE
CFT 455 B	455 kHz	8 at -6dB \pm 10 at -22dB	nbfm	50p
CFT 455 C		6 27dB	am	50p
CFU 455 C		4-8 28dB	am	55p
MFH mechanical series		4.5 or 7 at -6dB \pm 5 at -50dB	ssb am nbfm	1-40
CFS 10.7	10.7 mHz	300 at -3dB 600 at -20dB	wbfm	40p
LPF 2016	low pass filter for STEREO radio (removes pilot tone)			2-00

OTHER FILTERS & INDUCTORS AVAILABLE SEE DATALOGUE

block filters are **PREALIGNED**



RF POWER & OTHER SEMICONDUCTOR DEVICES A SELECTION FROM THE DATALOGUE, RANGE

TRW-SET OF 4 transistors 30w rf out at 145 mHz. More out at lower frequencies. Set comprises of a TO5 pre-driver, two capstan power drivers & large capstan output stage. Limited offer £8-30 per set
 LM380 2w 12v/4w 20v. Only 2 extra components make the best AF amp IC available for £1-40
 40673 - 400mHz mosfet 57p; BF256 fet DC to 1000mHz 37p; MJE340 43p; 40290-1-40; BC109-10p
 NE56- range of PLL; 561-3-50; 562-3-99; 567-2-60; timer 555-86p - new twin timer 555-2 £1-63
 FND 70 - 7seg LED display 1/2 X 1/4 inch, with integral filter. 2-20each or 4 for £8; data 5p
 9368 - MSI purpose built LED bcd decoder driver AND LATCH 2-20ea 4 - £8; 6 - 11-20
 DALO PCB pen 80p; U11 type NICAD £1-80 ea 10 for £17; LED panel light 26p; 7490 - only 63p



PW FERRET KITS - SAE for full details etc

When it comes to actually using linear ICs, RF power, etc., a lot of components sellers haven't got a clue. So if you get a problem with an application—well, that's just too bad. But at AMBIT we know about our products . . . try us and see.

Mail order centre: 37a High Street, BRENTWOOD, Essex, CM144RH Tel. 0277 216029
 All prices include VAT: Postage, etc. plus 10p per order please:

Another!
winner!

fane **MODE ONE**

**HIGH FIDELITY
LOUDSPEAKER KIT**



Recommended
retail price

£10.98

including V.A.T.

Consisting of a Fane Model 803 ultra-low resonance 8" speaker unit with PVC cone surround, and a Fane Model 303 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

SPECIFICATION OF UNITS

	Model 803	Model 303
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	1/2"
Magnet Flux Density	13,000 gauss	10,000 gauss
Frequency response	30Hz-8kHz	2kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

CABINETS for the 'Mode One' are available in Teak veneer finish. SIZE 15 1/2" x 10 1/2" x 9".

*When used with above cabinet.

Please send S.A.E. for fully descriptive leaflet.

Distributors to the wholesale and retail trade
LINEAR PRODUCTS LTD.
Electron Works, Armsley, Leeds
LS12 3SA. Tel. 630126

Manufactured by
FANE ACOUSTICS LTD.
Hick Lane, Batley, Yorkshire.
Tel. Batley 6431



**become
a RADIO-AMATEUR!**

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

WB123
BLOCK CAPS please

SPECIAL 40 MHz SCOPE—SOLARTRON CD1212 ONLY £50. Has to be a scope. There are no plug-in Y amps available.

1B—100 nanosecs per cm to 5 secs per cm in 24 calibrated ranges. 20 nanosecs per cm with times 5 expansion. 5in flat faced tube. Trace locator. 0.2 microsec signal delay. Built-in calibrator 1kHz square wave. 200 micro volts to 100 volts in 18 calibrated ranges. Tube sensitivity 3V/cm. Main Frame Y Amp boosts this to better than 200 MV per cm at 40 MHz. 240V 50 Hz input. Complete with full manual including plug-in circuits. Come and see one working or Carriage £1.50.

12" LONG PERSISTENCE CRT. Full spec. Price £12.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5.50, P. & P. 25p. (Not cased, not calibrated.)

NEW WIDE RANGE WOBBULATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10.7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V A.C. and use within minutes of receiving. All this for ONLY £5.75, P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB. **SINE and SQUARE GENERATOR.** Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £7.85 each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each, P. & P. 5p.

COMPONENT PACK consisting of 5 pots, various, brand new: 250 resistors 1/2 and 1/4 watt, many high stabs, etc. Fine value at 50p, P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice. 25p, P. & P. 15p.

5 MOVING COIL METERS. Various. £2, P. & P. 37p.

CAPACITOR PACK—50 Brand new components, only 50p, P. & P. 17p.

POTS—10 different values. Brand new. 50p, P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 10p.

FLAT FACED 4" TWIN BEAM TUBE type CV2193. Green trace. Brand new £4 each, P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New. 38p each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, 13p each.

PHOTO RESISTOR type Clare 703. Two for 50p.

MODERN TELEPHONES type 708. Two-tone grey, £3.75 each. The same but black, £2.75 each, P. & P. 25p each.

Also **TOPAZ YELLOW** £4.50 each, P. & P. 25p.

Ideal EXTENSION TELEPHONES with standard GPO type dial, bell and lead coding. £1.75 each, P. & P. 25p.

DELIVERED TO YOUR DOOR
1cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

PLEASE ADD 10% V.A.T.
Open 9 a.m. to 6.30 p.m. any day.

CHILTMEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 582605/65916

using
the



amplifier

J. B. DANCE M.Sc.

THERE are a number of integrated circuit audio power amplifiers available at the present time. One of these, the LM380N device, has a number of features which make it attractive to the amateur experimenter. In particular, it is very useful in circuits requiring the minimum number of components. The device is manufactured by the National Semiconductor Company, and is available from Ambit International, 37 High Street, Brentwood, Essex, or Athena Ltd., 140 High Street, Egham, Surrey.

ADVANTAGES

The LM380N automatically 'centres' its output at one half of the power supply voltage. This eliminates the need for additional circuitry (including a pre-set potentiometer) which is required with some other types of amplifier for adjusting the bias so that maximum voltage swing (and hence a maximum power output) can be obtained.

The LM380N device also incorporates internal protective circuits. If the silicon chip becomes too hot (above about 150°C) owing to incorrect operation, the circuit automatically becomes inoperative for a time until the chip has cooled. Protection is also incorporated against excessive current in the output stage; such currents will occur if the output is accidentally short-circuited. The limiting current in the output stages is about 1.3A.

The LM380N can feed up to 2.5W to an 8Ω loudspeaker when operated from an 18V supply. The absolute maximum permissible supply voltage is 22V, but it is wise to use a somewhat lower value to allow a margin for error. The writer has found that satisfactory loudspeaker volume can be obtained using the minimum recommended supply voltage of 8V. The total harmonic distortion is 0.2% at 2W output using an 18V supply.

It is normally convenient to use the LM380N in a standard 14 pin dual-in-line socket so that it can

be removed easily from the circuit. However, one can solder directly to the terminals of the device.

CONNECTIONS

The connections of the LM380N are shown in Fig. 1. The input signal can be fed either to the non-inverting input or to the inverting input. Generally it is more convenient to feed the signal to the non-inverting input and to leave the inverting input unconnected.

If, however, the signal is fed to the inverting input, the non-inverting input should be returned to earth through a capacitor or a resistor or directly earthed. This will prevent positive feedback from the output to the non-inverting input causing instability. A capacitor is preferable when the signal source has a high impedance, but with a source of moderate impedance a resistor approximately equal in value to this source impedance is preferable to maintain the balance of the differential stage. When the source impedance is low, the non-inverting input may be earthed.

GAIN


The voltage gain of the LM380N is fixed at 50 (or 34dB) by the internal circuitry of the device. Although this fixed gain limits the versatility of the amplifier, it does result in a minimum number of external components being required for its use.


HEAT SINK

The LM380N device itself can dissipate up to 1.25W when operated without any heat sink at ambient temperatures of up to 25°C; this is adequate for many applications. For example, Fig. 2 shows that the power does not exceed 1.25W at supply voltages up to 14V when an 8Ω speaker is employed. Even if a higher supply voltage is used, it is not likely that the dissipation will exceed 1.25W for an appreciable time.

Fig. 3 shows that there is still less chance of overheating when a 16Ω speaker is employed. In this case, the supply voltage would have to exceed 20V for the dissipation to exceed 1.25W.

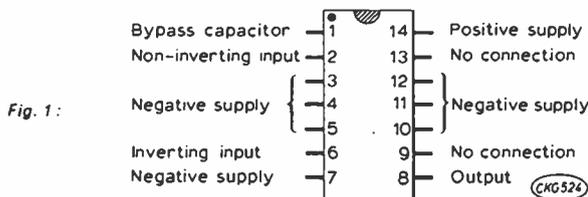In the case of a 4Ω speaker, however, Fig. 4 shows that the dissipation can reach 1.25W when a 10V supply is used. If a much higher supply voltage is employed, the pins 3, 4, 5, 10, 11 and 12 of the device should be soldered to a copper heat sink of



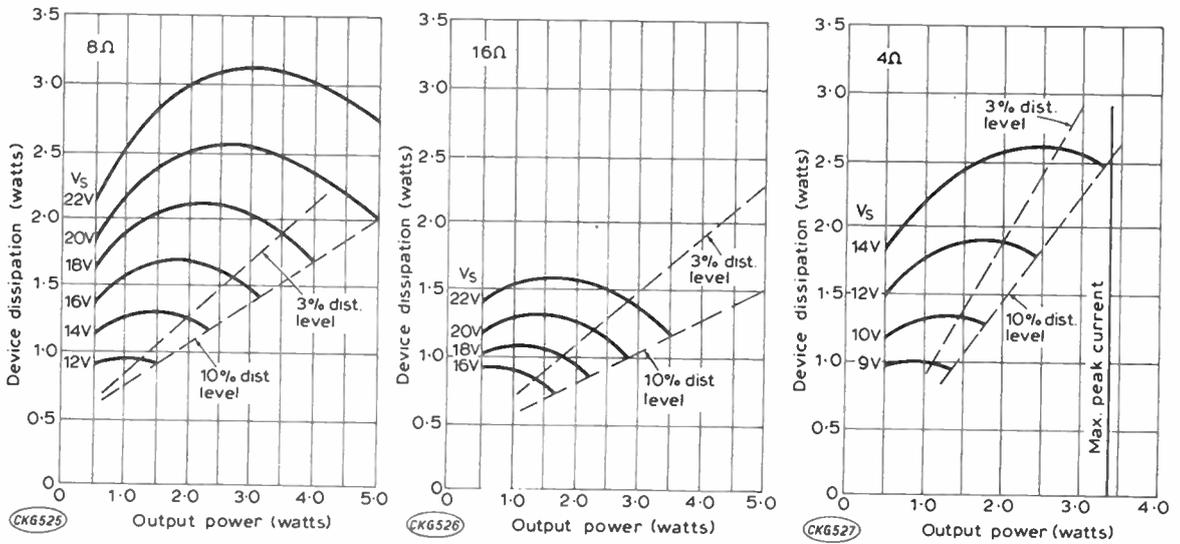

Figs. 2, 3 and 4: These graphs show dissipation of the LM380N against output power for various values of supply voltage and loudspeaker impedance

area about six square inches.


The three per cent total harmonic distortion line shown in Figs. 2 to 4 is approximately the onset of clipping.

POWER SUPPLY

If there is hum or noise on the power supply line, a hum rejection of about 38dB can be obtained by connecting a 5μF capacitor from pin 1 to earth. A smaller capacitor will also provide some measure of hum reduction.

If the power supply leads from a battery or filter capacitor are longer than two or three inches, a 0.1μF capacitor should be connected between pin 8 and earth to prevent oscillation.

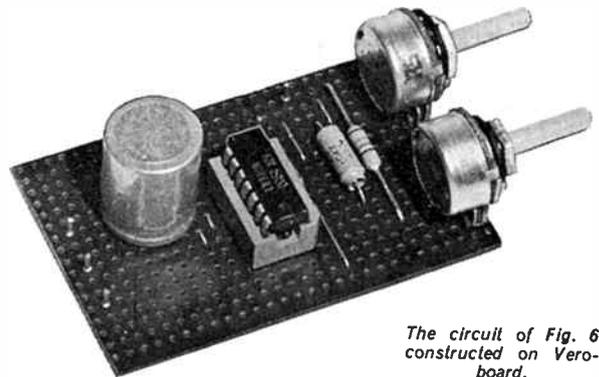In addition, a 2.7Ω resistor in series with a 0.1μF capacitor may be connected between pin 8 and earth to suppress any high frequency oscillations.



The circuit of Fig. 6 constructed on Vero-board.

The input pin operates with a mean potential equal to the earth potential. A capacitor in series with the input pin is therefore required only if the

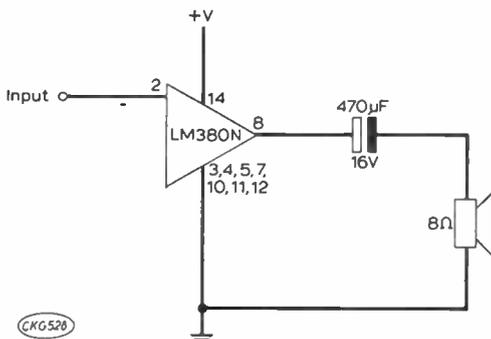


Fig. 5: A simple circuit using the LM380N.

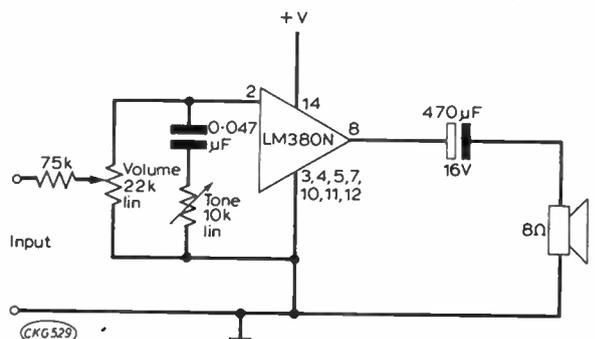


Fig. 6: A record player amplifier suitable for use with a crystal or ceramic pick-up cartridge.

SIMPLE CIRCUIT

The simplest circuit using the LM380N is shown in Fig. 5. The 470μF capacitor must be placed in series with the loudspeaker to prevent a steady current from flowing through the speaker from pin 8. A smaller capacitor than that shown will result in inferior bass response.

mean potential of the signal source is not also at earth potential.

The writer has used the circuit of Fig. 5 in a radio receiver. Fig. 6 shows how a similar circuit may be used as a record player amplifier with volume and tone controls. The input impedance of the LM380N is about 150kΩ.

LARGE STOCKS ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new & to makers specs.

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power 60p
AC153K pnp germanium low power 32p
AC176K npn germanium low power 32p
AD161 npn germanium medium power 42p
AD162 pnp germanium medium power 40p
AF133 pnp germanium UHF 49p
BC107 18p; BC108 12p; BC109 13p; } npn
BC187 11p; BC188 10p; BC169 11p; }
BC177 12p; BC178 10p; BC179 21p; } pnp
BC257 12p; BC258 11p; BC259 18p }
Standard groupings available.
ED135 npn med power 87p
BD135 pnp med power 86p
DIODES
OA90, OA91, OA95 each 6p
OA200 9p; OA202 10p
Other semiconductors
AC128 17p; AF117 82p
BFY61 19p

Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

SIEMENS' THYRISTORS

0-8A 400V 56p, 600V 70p
3A 400V 60p, 600V 88p

ZENER DIODES full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

DIN PLUGS & SOCKETS

by Hirschmann, 4A rating




2 way LS—socket 10p; plug 12p. 3 way scr. socket 10p; plug 12p. 5 way scr. socket 12p; plug 15p.

TRANSISTOR ACCESSORIES

To3 cover 7p
Heat sinks 1°C/w, type 6W1, undrilled 60p

SWITCHES

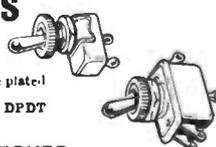1011C 8PST toggle 20p
409 DPDT toggle 29p. (These are chrome plated 2-6A rating)
7201 Sub-miniature DPDT 260V a.c./2A 48p



ROTARY SWITCHES

Radiospares Miniature Make-switch (in assembly kit form) 8 shaft 48p
Wafers, MBB-2P5W, 1P11W: BMM-1P12W, 2P6W, 3P4W, 4P3W, 6P2W, each, 6p.

WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 4P3W, each 24p



ELECTROLYTIC CAPACITORS

AXIAL LEAD Prices subject to amendment by the manufacturer.

Rated voltage: 8V	6.8V	10V	16V	25V	40V	63V	100V
Capacity μ F							
0.47							10p
1.0				10p			7p
2.2							7p
4.7			10p				8p
10				10p			8p
22		7p	7p				7p
47	7p	8p	7p	8p			8p
100	7p	7p	7p	7p			11p
220	7p	8p	8p	8p			12p
470	8p	9p	10p	12p			17p
1000	10p	12p	17p	20p			24p
2200	14p	17p	25p	36p			40p
4700	25p	28p	37p	41p			
10,000	40p	43p					

Polycarbonate —5% Tolerance

250V up to 0.1 μ F: 100V/0.1 μ F and above.

0-01; 0-012; 0-015; 0-018; 0-022; 0-027; 0-033; 0-047; 0-056; each 4p.
0-058; 0-082; 0-1; 0-12; 0-15 each 4p.
0-18; 0-22; each 5p.
0-27; 0-33; 6p; 0-39 7p; 0-47 8p; 0-56 10p.
0-68 11p; 1 μ F 13p.

Prices subject to amendment by the manufacturer.

SILVERED MICA non-polarised capacitors in 34 values from 2.2 pF to 680 pF, each 6p

RESISTORS 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 Wp
C	1/20W	5%	82 Ω - 220K Ω	E12	9	8	7-6
C	1/8W	5%	4.7 Ω - 470K Ω	E24	1	0-9	0.75 nett
C	1/4W	5%	4.7 Ω - 10M Ω	E12	1	0-9	0.75 nett
C	1/2W	5%	4.7 Ω - 10M Ω	E24	1-2	1	0.9 nett
C	1W	5%	4.7 Ω - 10M Ω	E12	2-5	2	1-6 nett
MO	1/2W	2%	10 Ω - 1M Ω	E24	4	8	2 nett
WW	1W	10% \pm 1/20 Ω	0.22 Ω - 3.9 Ω	E12	7	7	6
WW	3W	5%	1 Ω - 10K Ω	E12	7	7	6
WW	7W	5%	1 Ω - 10K Ω	E12	9	9	8

Codes: C—carbon film, high stability, low noise.
MO—metal oxide, Electroil TR5, ultra low noise.
WW—wire wound, Pleassey.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order).


Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

* Please remember to add V.A.T. to your order.

If you have already got your No. 6 catalogue and want to know latest additional items and price amendments, send S.A.E. for special supplementary list.

KNOBBS

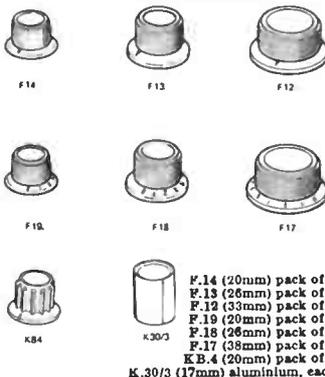All grub screw fitting for 1/2" shafts. Black. For other types—see Catalogue No. 6, P.54



F.14 (20mm) pack of 2 32p
F.13 (26mm) pack of 2 38p
F.12 (33mm) pack of 2 40p
F.19 (20mm) pack of 2 32p
F.18 (26mm) pack of 2 38p
F.17 (33mm) pack of 2 40p
K.303 (20mm) pack of 4 40p
K.303/17mm aluminium, each 24p

IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semi-conductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc. information and equivalent tables, etc. Well illustrated (96 pages 8 1/2" x 5 1/2") 25p. post free with refund voucher for 25p. allowable on orders over £5 or more.

with
25p
refund
voucher

POTENTIOMETERS

Rotary carbon track, double wiper SINGLE P20 1in 100 Ω to 2.2M Ω 12p, P20 log 4.7K Ω to 2.2 meg. 12p
Dual gang 1in 4.7K Ω to 2.2M Ω 12p
Dual gang 1in 4.7K Ω to 2.2m Ω 42p; Dual log, 4.7K Ω to 2.2m Ω 42p; Log/antilog, 10K, 22K, 47K, 1M Ω only 42p; Dual antilog, 10K only, 42p. Any type with 2A, D.P. mains switch, 18p extra.
Only decades of 10, 22 & 47 available in ranges quoted.

DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.

SLIDER
Lin or log, 10K to 1meg. in all popular values, each 28p.
Escutcheons—White, grey, black, 10p each.
Control knobs: blk/white/red/yel/gr./blue/uk. grey/lt. grey, each 5p.

CARBON SKELETON PRE-SETS
Small high quality, PR 1in: 100 Ω 220 Ω , 470 Ω , 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10M Ω . Vertical or horizontal mounting, 6p each.

All items offered for sale in accordance with our stated terms of business, copy of which available on request. Prices quoted DO NOT include V.A.T. Orders from U.K. customers must be accompanied by an additional 10% of nett value for V.A.T.


DISCOUNTS Not allowed on nett price items. 10% on orders for £5 or more, 15% on orders for £15 or more. Prices subject to alteration without prior notice.
PLEASE SEE LATEST AMENDMENT LIST. SEND S.A.E.

POSTAGE AND PACKING FREE
SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

ELECTROVALUE

(Dept. P.W. 8) 28 ST. JUDES ROAD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB
Hours: 9—5.30: Sat. 1 p.m. Tel.: Egham 3603 Telex 264475
ENG. REG. NO. 1047768. R.O. 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY. TW20 0HB

'BIG' Discounts

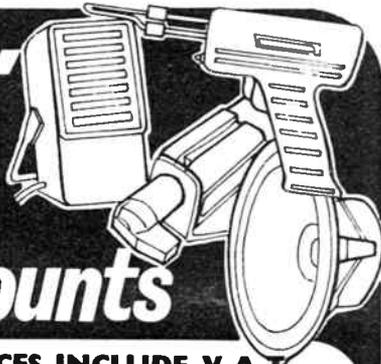

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£	£
EMI 13" x 8" 3, 8 or 15 ohm			2 10
Plain	2 05	ELAC 8" 8ohm Dualcone	1 00
With Co-Axial Tweeter	2 20	FANE 7" x 4" 3 or 8 ohm	2 40
Twin Tweeter	3 55	8" Dualcone 8 ohm	1 55
Type 350	8 ohm, 20 watt	CELESTION 8" 15 ohm	2 75
6 1/2"	8 ohm, 10 watt	ADASTRA 10" 8 or 15 ohm,	
8"	8 ohm, 10 watt	10 watt	6 45
12"	8 ohm, 20 watt	BAKER GROUP 25 12" 8 or	
8" x 5" C/Mag.	5 watt	15 ohm, 25 watt	25
8" x 5" Dualcone		P. & P.	85
GODMANS 6 1/2" 8 ohm	2 45	5" 8 ohm, 5 watt C/Mag.	50
Dualcone	1 60	2 1/2" 8 ohm or 64 ohm	10
		P. & P.	50

TWEETER & CROSSOVER		£	£
EMI 3 1/2" 3 or 8 ohm C/Mag	1 00	Dome Tweeter 8 ohm, 30 watt	4 00
Cone Tweeter 8 or 15 ohm,		Crossovers CN23 (3 ohm),	
10 watt	1 90	CN25 (8 ohm), CN216 (16	
Cone Tweeter 8 ohm, 3 watt	1 00	ohm)	1 00
Horn Tweeter 8 ohm, 20 watt	3 50		P. & P. 10

KIT FORM CABINETS TEAK VENEER		£	£
12 x 12 x 6 with 8" 8" x 5" or	2 45	18 x 11 x 9 with 13" x 8" cutout	4 25
6" and 3 1/2" cut out.		for EMI 350	
17 x 10 x 6 with 8" or 13" x 8"	3 25		P. & P. ea. 35

MICROPHONES		£	£
CM20 Crystal Hand	50	TW206	5 75
CM70 Planet stick metal,		CONDENSER MIKE 600 ohm,	
switch crystal	1 55	uni-dir	7 90
DM160 Dynamic uni-dir, ball		Cassette Stick Mike with R.	
metal	3 95	Control on/off switch	1 35
UD130 50K/600 ohm, uni-dir		(2.5 & 3.5mm J/Ply)	15
ball metal	4 50		P. & P.

SOLDERING IRONS		£	£
ANTEX CN240 15 watt	1 60	X25 25 watt (low	
SK 1 Kit (15 watt Iron		leakage)	1 60
2 spare Bib etc.)	2 65		P. & P. 10

CARTRIDGES		£	£
ACOS GP91/2SC or GP91/3SC		19-TI Stereo crystal	80
Stereo comp.	1 00	BSR SC5M Stereo ceramic	2 25
GP93/1 Stereo crys	1 35	SX5H Stereo crystal	1 60
GP94/1 Stereo crys	1 75	SX5M Stereo crystal	1 60
GP95/1	1 35	X5H Mono/stereo	1 25
GP96/1	1 75	X5M Mono/stereo	1 25
GP101	1 75	GOLDRING G800 G850 £3-85	£2-95
SONOTONE		STYLI for above cartridges	
9THAC Stereo cer. diam.	1 80	Sapphire .35 D. Diamond	1 25
		GOLDRING G800 G850	1 85
			P. & P. 85

BATTERY ELIMINATORS		£	£
240v input 6, 7.5 or 9 300mA	2 20	lighter socket) 6, 7.5 or 9	
12v d.c. input (fits in car		d.c. output at 300mA	2 20
			P. & P. 10

TAPES		£	£
5" Std	LP DP	7"	Std. LP DP
45p	55p 70p	65p	95p 110p
5 1/2"	55p 85p 95p		P. & P. 1-3, 9p ea. 4 or more, lot 30p

LOW NOISE CASSETTES		£	£
C60	35p 6-10 11-20	Cassette Head Cleaner	35p
C90	45p 33p 30p	P. & P. 1-5, 3p ea. 6-10, 15p lot	
C120	55p 52p 50p	11-20, Post Free.	

PLASTIC LIBRARY CASES		£	£
For 5" Reels	18p	CASSETTE CASES	10p
5 1/2" Reels	22p	P. & P. 1-3, 5p ea. 4 or more, 20p	
7" Reels	25p		

BIB ACCESSORIES		£	£
Tape Editing Kit Ref. 23	1 30	SPECIAL OFFER BUSH Stereo System with Indep. Vol., Bass & Treble controls on each Speaker for optimum repro. Using Gar- rard 2025TC Auto Change Deck in deluxe teak plinth and cover. Today's Value £49.50. OUR PRICE £27.50 + £1.50 P. & P. 12 months Guarantee by Maker. THIS IS A BARGAIN NOT TO BE MISSED!	
Recording Tape			
Splicer Ref. 20	1 15		
Cassette Tape,			
edding Ref. 24	1 40		
Cassette Salvage Kit Ref. 26	40p		
12's Cassette Case Ref. 34	£1.00		
Stylus Balance Ref. 32A	1 15		
Spirit Lever Ref. 46	50		
Hi-Fi Stereo Test Cassette	1 80		
Groove-Kleen Record Cleaner	1 90		
		P. & P.	10


Send 25p for COMPLETE CATALOGUE, refundable upon first order.
 ALL OUR MERCHANDISE IS FULLY GUARANTEED

Riversdale Electronics

Mail Order Department FW2
 P.O. Box 470, Manchester M60 4BU.

Parts for PRACTICAL WIRELESS and PRACTICAL ELECTRONICS PRODUCTS

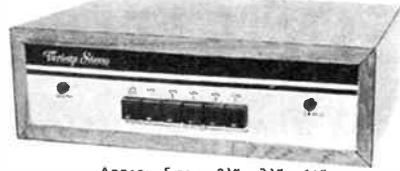ALL PARTS AVAILABLE SEPARATELY
 "p.e." f.m. varicap stereo tuner



Approx. Size :- 8 1/2" x 2 1/2" x 6 1/2"

Total Kit price only £28.50 including VAT and postage
 Please send large S.A.E. for full details.

P. E. 'GEMINI' STEREO AMPLIFIER

30 Watts (R.M.S. per Channel into 8 Ohms !!
 Total Harmonic Distortion 0.02% !!
 Frequency Response (-3 dB) 20Hz-100kHz !!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but it is well within the capabilities of the ambitious constructor.

We can now supply a reprint of the articles in booklet form, price 64p, including VAT and postage, with free complete component price list.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.

ELECTRO SPARES

288, Ecclesall Road
 Sheffield, S11 8PE
 Tel. Sheffield (0742) 668888



The Component Centre of the North

NEW! FOR RTTY ENTHUSIASTS

THE TELEPRINTER HANDBOOK

by D. J. Goacher, G3LLX, and J. G. Denny, G3NTT

The new RSGB *Teleprinter Handbook* covers all aspects of radioteleprinter (rtty) operation, equipment and techniques with particular reference to the interests of amateurs. For the experienced operator it provides, in one volume, all the accumulated information acquired during the past decade, and covers machines of both European and USA origins; for the intending enthusiast it includes all the basic information necessary to master the techniques of rtty operation.

The contents include: theory, practice and standards; teleprinters; associated rtty machines; power supplies; terminal units; auxiliary equipment; frequency shift keying; filters; test equipment; interconnection and control of rtty equipment; operating procedures; glossary; bibliography.

376 pages and hundreds of illustrations and diagrams.

The TELEPRINTER HANDBOOK is available, price £5.35 post free, direct from:

RADIO SOCIETY OF GREAT BRITAIN
 35 Doughty Street, London WC1N 2AE

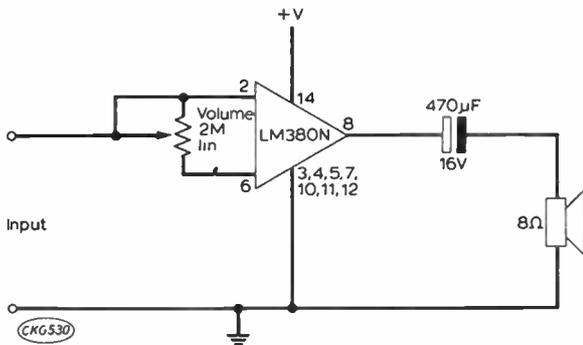


Fig. 7: A high input impedance achieved by use of a common-mode volume control.

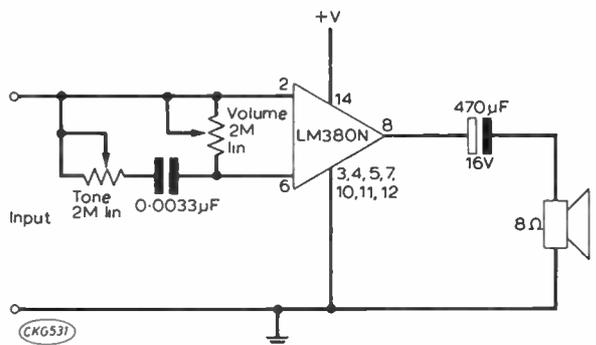


Fig. 8: This circuit features common-mode controls for both volume and tone.

HIGH IMPEDANCE INPUT CIRCUIT

An amplifier with a high impedance input is shown in Fig. 7; it is suitable for use with high impedance signal sources such as a crystal microphone. This circuit employs a 'common mode' volume control. When the potentiometer slider is at the bottom of its travel in Fig. 7, the input signal is fed to both the inverting and the non-inverting inputs. In this case the signals will almost cancel in the device and the output will be small. When the potentiometer is at the top of its travel, however, only pin 2 will receive an appreciable input voltage and maximum volume will be obtained.

The circuit of Fig. 8 shows how a common mode volume control circuit may be used with a common mode tone control to maintain the high input impedance.

A very high impedance amplifier can be made using the field-effect transistor input circuit shown in Fig. 9. At low frequencies the input impedance is 22 megohms, but at high frequencies the input impedance is reduced by the gate to drain capacitance of the field effect transistor.

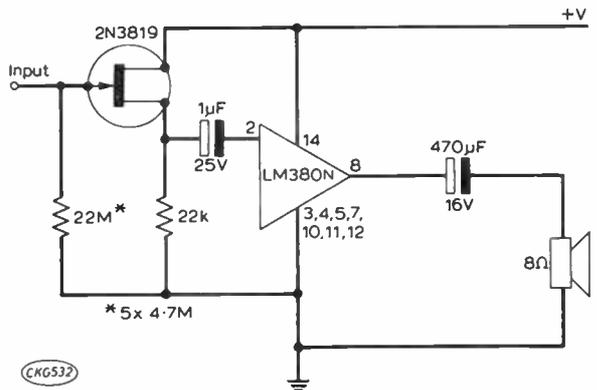


Fig. 9: The addition of a FET input stage gives a very high input impedance.

INTERCOM SYSTEM

A simple circuit for an intercom system is shown in Fig. 10. The transformer ratio of 25:1 multiplied by the gain of the LM380N produces a loop gain of 1250. The roles of the input and output speech transducers are reversed when the switch is operated.

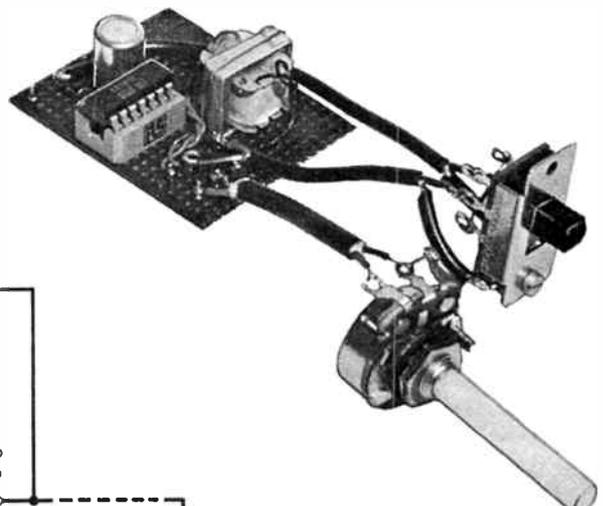
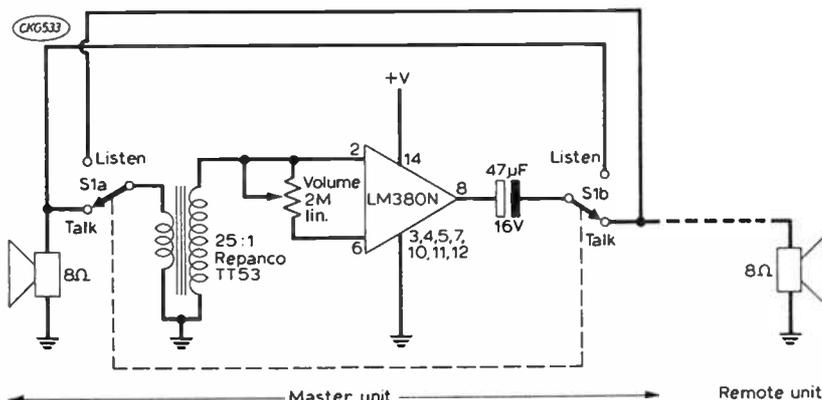


Fig. 10: An intercom system in which the loudspeakers double as microphones. The view above shows the amplifier with controls attached.

DUAL POWER SUPPLY

Another simple circuit using the LM380N is shown in Fig. 11; it provides a dual voltage supply balanced with respect to ground from a single supply. If the input is 20V, outputs of +10V and -10V can be obtained. The potentiometer can be used to balance the outputs relative to ground, but may be omitted if exact balance is not required.

An advantage of this circuit is that a high quiescent current is not taken when little current flows in the outputs.

EXTRA GAIN

Although the gain of the LM380N is fixed at 50 by the internal components, higher gain can be obtained by using additional positive feedback. For example, Fig. 12 shows how a gain of 200 can be obtained.

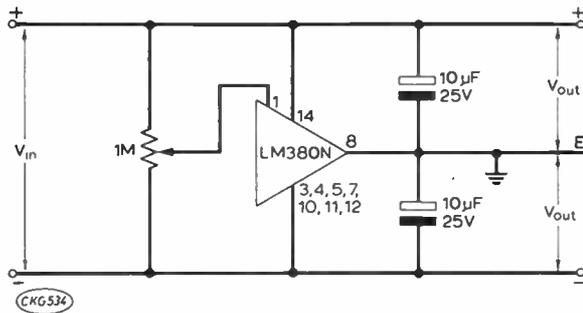


Fig. 11: A circuit to provide a split power supply from a single source.

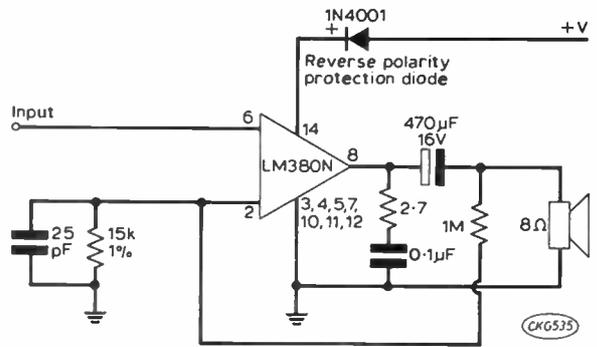



Fig. 12: Increased gain may be obtained by the use of positive feedback.

The maximum gain is around 300, since attempts to obtain still higher gain may merely result in oscillation.

SUPPLY POLARITY

As in the case of most integrated circuit audio amplifiers, if the power supply to the LM380N is applied with the polarity reversed, a large current will flow and the device will almost certainly be destroyed within a few milliseconds.

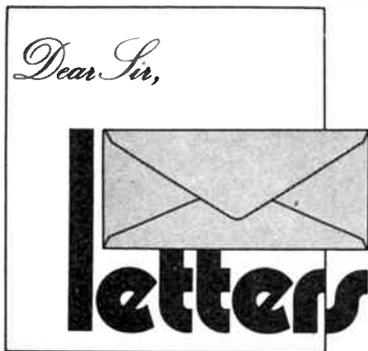Readers may therefore wish to incorporate a diode in one of the power supply lines (normally the positive line). If a supply of reverse polarity is accidentally applied to the circuit at any time, the diode will prevent any appreciable current from flowing and will thus protect the LM380N. It is, of course, essential that the diode is connected with the correct polarity, see Fig. 12.



Microwave distance Record

On Thursday, 13th September a 3cm (10GHz) contact was made between GW8CKT/P on Snowdon and GM8AZU/P on the Cairns-more of Fleet. We believe that, at 212.5km, this is a new British distance record.

Weather conditions were far from ideal, with gale force winds and both ends of the link well above the cloud base. Visibility

on Snowdon at 3560 feet was only 15 yards, and on the Cairns-more of Fleet at 2300 feet was only 20 yards. The high wind on Snowdon made it impossible to use a dish aerial and so a 10dB horn was used. At the Scottish end a 32in. dish was used, and a considerable amount of luck was in evidence when the beam heading, estimated using a cheap plastic compass, turned out to be correct to better than 0.5°. Earlier attempts to find a signal using a 10in. dish at the Scottish end had failed. Signal reports exchanged were readability 5 and strength 6/7.

Equipment used at GM8AZU/P: Tx, Mullard CXY19 Gunn device, output approximately 100mW; Rx, Mixer CS10B, Local Oscillator, Mullard CL8370; i.f., 70MHz; ANT, 32 inch dish with horn feed.

Equipment used at GW8CKT/P: TX, Mullard CXY19 Gunn device, output approximately 120mW; RX, Mixer, balanced pair of Mullard BAW95, Local Oscillator,

Mullard CL8380; i.f., 70MHz; ANT, Small horn.

The equipment, which was all solid state, was carried to the summits of the two mountains concerned. Pundits who ask why the GW team did not use the train, may be interested to know that the train was not running due to the bad weather so it's just as well that they bargained on climbing!


80m talkback was used between the two base camps in order to co-ordinate the departure for the climb to the summit.

2m talkback was used from summit to summit.

Those involved were:—

At the GM end: G3VUQ, G3YQC, G8AMG, G8APZ, G8AZU, G8DKK. At the GW end: G3XSQ, G3YMV, G8BPN, G8CKT, G8ENX, G8FTB, G8HCO.—Michael H. Tooley, G8CKT, (Weybridge, Surrey).

—continued on page 762

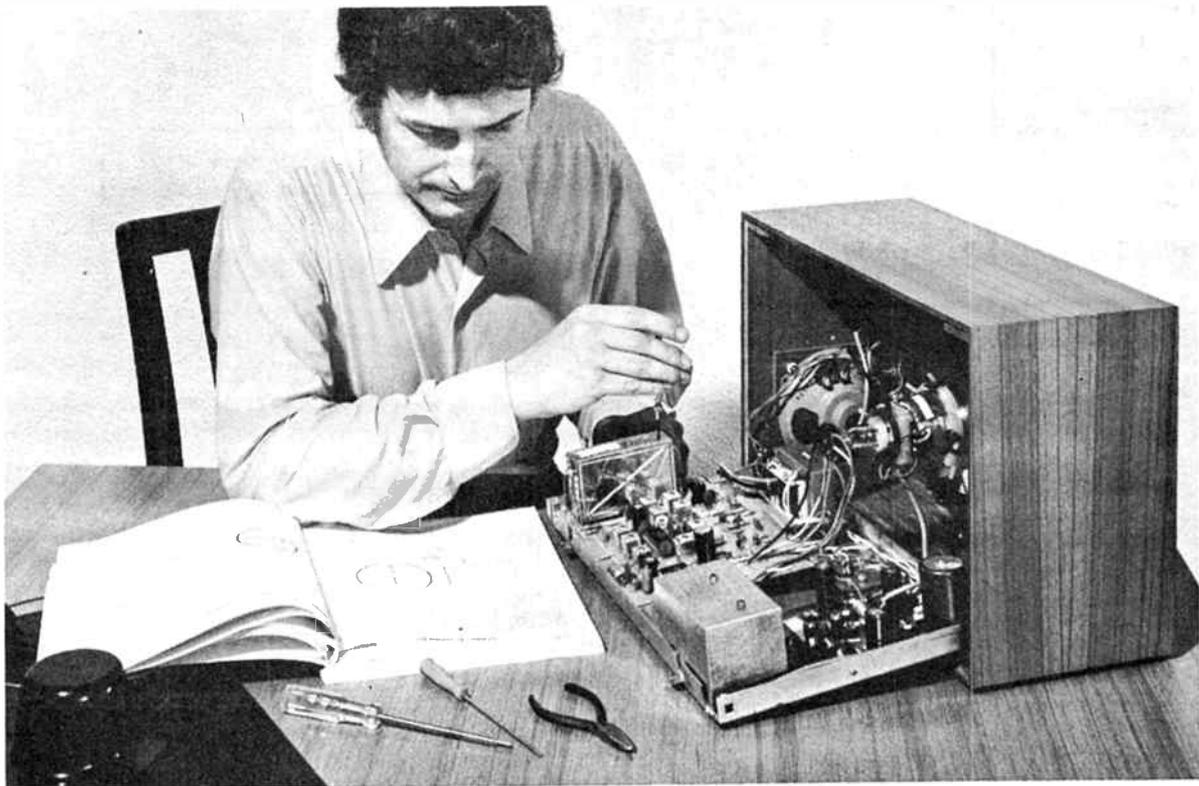

LEARN about MODERN TV Design by building this Heathkit 12" B/W Portable

The new Heathkit GR-9900 portable 12" UHF Monochrome Television kit. A unique chance to double the pleasure available from any other television set — because you build this yourself.

We've used the latest modular construction and advanced design concepts to produce an outstandingly high performance TV worthy of the Heathkit name. All the main electronics are mounted on two easy-to-assemble printed circuit boards—this plus the use of no less than four integrated circuits perform the complex function of IF, video, sound, line and frame scan. Factory pre-aligned coils make alignment very easy and there are four presettable pushbutton controls for channel tuning—a luxury found in very few other models. The quality and fidelity is therefore excellent, and of a far higher standard than most ready-built televisions in the shops.

The GR-9900 is portable too—equally at home on

the mains or off your 12 volt battery for car, boat or caravan use. Add to this Heath's world renowned experience in the design of equipment for first-time kit builders, and you will be impressed on all counts of engineering, styling, and performance.

The instruction manual is surprisingly simple with big, clear illustrations to map out your way. Would-be TV engineer? Here's your chance to learn—by actually building a television yourself. The manual not only shows you how to get 100% personalised quality control on your own; in the event of anything going wrong, a Trouble-Shooting section enables you to find the fault—and, in most cases, to put it right unaided.

The GR-9900 is a kit you'll be proud to build and own. You have a choice of fully finished cabinets in teak or modern white and the kit price, £62.70 (carriage extra), includes a FREE high performance indoor aerial.

FREE Heathkit Catalogue

Contains something for everyone: Hi-Fi Stereo, Testers & Instruments, SWL, Metal Detectors... even a Battery charger Kit. Mail the coupon... Today! Heath (Gloucester) Limited, Gloucester GL2 6EE.

LONDON showroom
233 Tottenham Court Road
Tel 636 7349



Choose cash or Heath Monthly Budget Plan

(Mail order prices and specifications subject to change without notice)

Please send me a FREE Heathkit catalogue

Name _____

Address _____

HEATH
Schlumberger

Dept. PW/12/73
Heath (Gloucester) Limited,
Gloucester GL2 6EE. Telephone 0452 29451



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS


EMI 13 x 8, 3, 8 or 15 ohm £2.03
 EMI 13 x 8, 150 d/c 3, 8 or 15 ohm £2.25
 EMI 13 x 8, 450 t/tw 3, 8 or 15 ohm £3.60
 EMI 13 x 8 type 350 8 ohm £8.25
 EMI 61" 93850 4 or 8 ohm £2.80
 EMI 8" x 5, d /Cone Roll/s 8 ohm £2.50
 Baker Group 25 3, 8 or 15 ohm £6.60
 Baker Group 35 3, 8 or 15 ohm £7.50
 Baker De Luxe 12" d/cone £9.62
 Baker Major 12" £7.50
 Kef T27 £64.67
 Kef T15 £5.50
 Kef B110 £66.16
 Kef B200 £7.42
 Kef B139 £10.72
 Kef DN8 £1.92
 Kef DN9 £1.37
 Kef DN12 £41.12
 Kef DN13 £2.75

Fane Pop 100 watt 8/15 ohm £21.45
 Fane Pop 60 watt 8/15 ohm £12.26
 Fane Pop 50 watt 8/15 ohm £10.17
 Fane Pop 25/25 watt 8/15 ohm £5.94
 Fane Pop 15 watt 8/15 ohm £4.40
 Fane Crescendo 15" 8 or 15 ohm £27.50
 Fane Crescendo 12A 100w 8 or 15ohm £24.20
 Fane Crescendo 12B 75w bass 8 or 15 £24.20
 Fane 807T 8" d/c roll/s 8 or 15 ohm £3.85
 Fane 808T 8" d/c cone 8 or 15 ohm £2.64
 Goodmans Axent 100 tweeter £6.60
 Goodmans 8P 8 or 15 ohm £3.80
 Goodmans 10P 8 or 15 ohm £4.49
 Goodmans 12P 8 or 15 ohm £11.55
 Goodmans 15P 8 or 15 ohm £17.05
 Goodmans 18P 8 or 15 ohm £29.70
 Goodmans Twinaxiom 8 £6.79
 Goodmans Twinaxiom 10 £7.61
 Elac 9 x 5 5" 59RM109 15 ohm, £2.53
 59RM114 8 ohm £3.22
 Elac 6 1/2" d/c roll/s 8 ohm £2.59
 Elac 6 1/2" d. cone 8 ohm £1.21
 Elac 4" tweeter TW4 £3.11
 Wharfedale Bronze 8 R5/DD £5.50
 Wharfedale Super 8 R5/DD £9.80
 Wharfedale Super 10 R5/DD £2.42
 Coral 6 1/2" d/c cone roll/s 8 ohm £1.44
 Siran 6 1/2" 3 or 8 ohm £2.20
 Richard Allan 12" d/c 3 or 15 ohm £1.92
 10" x 6" 3, 8 or 15 ohm £1.38
 8" x 5" 3 or 8 ohm £1.38
 7" x 4" 3 or 8 ohm £0.65
 2 1/2" 64 ohm or 70 mm 80 ohm £2.80
 Adastral Hiten 10" 10w 8 or 15 ohm £5.45
 Eagle DT33 dome tw. £3.66
 Eagle HT15 tweeter £1.25
 Eagle CT5 tweeter £2.54
 Eagle CT10 tweeter £3.74
 Eagle MHT10 tweeter £4.45
 Eagle FR4 £4.45
 Eagle xover CN23, 28, 216 £1.10
 Sp. matching transformer 3-15 ohm £1.10
 Celestion MF1000 25w horn 8 or 15 ohm £10.45

Celestion P58 (for Unilex) £2.16
 Celestion G12M 8 or 15 ohm £12.00
 Celestion G12H 8 or 15 ohm £15.00
 Celestion G15C 8 or 15 ohm £24.00
 Celestion G18C 8 or 15 ohm £33.00
 Car Stereo speakers—ask for leaflet.

SPEAKER KITS

Wharfedale Unit 3 £8.25
 Wharfedale Unit 4 £14.50
 Wharfedale Unit 5 £21.00
 Richard Allan Twinkit £7.33
 Richard Allan Triple 8 £10.76
 Richard Allan Triple Assem £16.20
 Richard Allan Super Triple £19.36
 Goodmans DIN 20 £8.58
 Fane Mode One £9.00
 Kefkit 2 £25.75
 Kefkit 3 £35.50
 Peerless 2-8 £5.50
 Peerless 10-2 £8.47
 Peerless 20-2 £10.41
 Helme XLK 25 (Pair) £18.17
 Helme XLK 50 (Pair) £37.18
 Stephenspeaker kits and cabinets—send for free booklet "Choosing a Speaker". Prices include VAT.
 Carriage and insurance 75p per kit

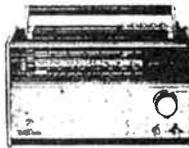

RADIOS/CASSETTES/AMPS.

Grundig Mariner TR865 £22.00
 Grundig Elite Boy 500 £27.00
 Grundig Melody Boy 500 £27.00
 Grundig Melody Boy 1000 £38.75
 Grundig Yacht Boy 210 £34.25
 Grundig RF430 mains £27.00
 Grundig RF310 mains £22.75
 Grundig RF310 £21.25
 Grundig Top Boy £16.75
 Grundig Satellit 1000 £121.00
 Grundig C402 cassette £27.00
 Grundig Signal 500 £27.00
 Grundig C230 Cassette £28.00
 Tandberg TP41 £42.00
 BASF 9301 radio/cassette £58.00
 Bush VTR178 5 Band (Inc. Air) £29.00
 Trio KA2000A £33.00
 Trio KA2002 £41.00
 ITT Colt £9.95
 ITT KB Golf Preset £21.25
 ITT KB Weekend Auto £16.00
 ITT KB Europa £18.00
 ITT KB SLS3 cassette £22.82
 ITT KB Studio 73 stereo cassette £44.00
 Koyo KTR1664 8 waveband £40.00
 Koyo KRT 1770 11 waveband £56.50
 Koyo KTR1883 5 Band (Inc. Air) £23.50
 Tec C200 Radio, Cassette £31.00

Prices include VAT.
 Carriage and insurance 75p. FREE with each radio—"World Radio Stations Book"

PA/DISCO AMPLIFIERS

Carriage and insurance £1.00
 Baker 100 Watt £40.00
 Linear 30/40 £25.00
 Linear 40/60 £30.00
 Linear 80/100 £55.00

JOSTY KITS SPECIAL OFFER

To celebrate our introduction to this famous range of Danish kits we are offering them free of VAT and postage. All models are available. For prices see the Radio Supplies advert or send an s.a.e. to us.

BATTERY ELIMINATOR BARGAIN


The most versatile eliminator ever offered. Input from AC mains. Output selected by switch is 3, 4, 5, 6, 7, 5, 9 and 12V DC at 500 mA. ONLY £3.60 (58p)



NEW SINCLAIR CAMBRIDGE CALCULATOR

ONLY £28.45 (£3.00) Fully built

SINCLAIR EQUIPMENT

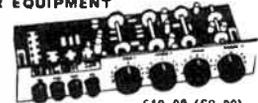

Project 605 £19.90 (£2.30)
 Pro 80 AFU £5.38 (74p), Pro 80 tuner £8.95 (£1.10)
 Z40 £4.25 (63p) Stereo 80 Preamp £9.53 (£1.05)
 Z60 £5.38 (74p) Project 80 decoder £5.89 (77p)
 Z30 £3.50 (55p) Stereo 60 £7.80 (98p)
 Z50 £4.30 (65p) Trans for P28 £2.95 (50p)
 P25 £3.47 (57p) 2000 Amp £28.00 (£3.00)
 P26 £8.30 (83p) P28 £6.40 (84p)
 AFU £4.40 (64p) Q16 Tuner £5.90 (79p)

PROJECT 60 KIT

£2.70 (49p)

Our extremely popular kit contains the extra capacitors, diode plugs and sockets, cable and fuse-holder needed to complete Project 60.

IC RADIO CHIP TBA851


£2.10 (32p)

The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2.10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1.75 (29p).

SINCLAIR SUPER IC12

£2.10 (43p)

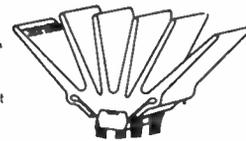Supplied complete with free 44 page instruction booklet and printed circuit



IC12 DELUXE KIT

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.55 (29p). Stereo model with balance control £3.58 (66p).

BASIC KIT FOR THE IC12

Contains components for P.C. board and volume and simple tone controls. Mono version £1.25 (24p). Stereo model with balance control £2.90 (40p).

IC12 POWER KIT

A set of components to construct a 28V 0.5 Amp power supply £2.47 (50p).

LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1.19 (27p), 5" x 8" 8 ohm £1.55 (37p), 10" x 6" 15 ohm £2.20 (44p).

IC12 PREAMPLIFIER KITS

Type 1 for magnetic pickups, mics and tuners, Mono model £1.30 (24p). Stereo model £2.30 (34p). Type 2 for ceramic or crystal pickups. Mono model £6.90 (17p). Stereo £1.20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

S-DECS AND T-DECS


S-DECS £1.44 (25p)

T-DECS £2.88 (40p)

μ-DEC A £3.18 (43p)

μ-DEC B £5.94 (71p)

16 dit IC carriers £1.20 (17p)

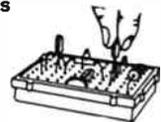

SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT.

Official credit orders from local authorities and school etc., welcome. Lists 10p.

Mail order only. No callers, please.

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage and insurance 35p per speaker (tweeters and crossovers 20p)

ALL PRICES QUOTED INCLUDE V.A.T.

WILMSLOW AUDIO Dept. P.W.


Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Radios etc: 10 Swan St., Wilmslow, Cheshire SK9 1HF.

Telephone Wilmslow 29599

GOING BACK...



COLIN RICHES
ARTHUR DOW

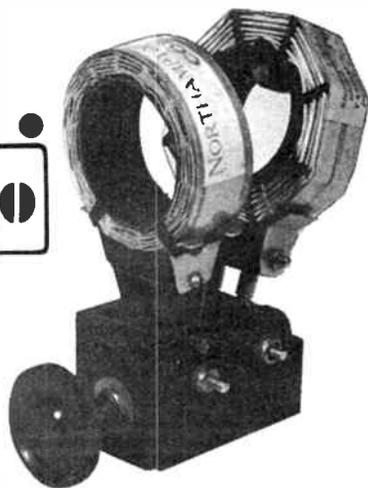

Letter from America

FOR several years I have read your column religiously and at long last decided to write to you. Needless to say I have an avid interest in Vintage Radio. However, I have had to content myself with vintage parts, valves, radio books and magazines. Additionally I construct simple vintage radios out of antique parts using my own circuits or those from Hugo Gernsback publications from the early '30's. My valve collection fortunately contains many good useable valves. At present I am constructing a short wave receiver (semi-antique) using types '35 and '27 (U.S. tubes) and meant for mains operation.

I started my radio hobby in 1928 with a commercial crystal set (Vario Couple Type). I made crystal sets until 1932 when I started on valve short wave and medium wave receivers. My hobby continued through 1935 and 1936. It was interrupted in 1937 by my joining the U.S. Army. I did only occasional short wave listening thereafter until 1946 when I went back to radio construction.


My recent vintage radio construction includes a one tube SW receiver (using a transmitting type '30). The coils (plug-in) are my originals from 1932. These are about the only parts surviving from that era. While I was in the army in pre-World War 2 days, a relative threw the rest away! I also have two surviving books.

The other receivers are a Short Wave Portable which is a good copy (including original vernier dial) from an article in a 1933 Short Wave Craft Magazine. I had been planning to build it for decades and only made it last year. Also I have a breadboard type Medium Wave receiver using a type '99. (A very good performer with one *modern* part—a ferrite rod aerial in it). I use it mostly for a quick test of old tubes. Much better than the tube tester!


I possessed one vintage radio in recent years (an RCA Radiola) but an avid collector got it away from me. All I have at the moment is a vintage tube tester, Signal Generator and Output meter (Weston, circa 1929). The trouble is that some collectors in this country possess 100 to 300 radios leaving none for us pickers.—**Chester A. Beck, K6DFP, (9045 Margaret Street, Downey, California, 90241, U.S.A.)**

Mr. W. H. Quick tells us that he has been given an old one-valve radio which he would like to get going. He would like to know what the L.T. and H.T. voltages are. There is a 1.5A fuse fitted and we show in the diagram the front panel and a plug-in coil which fixes to the side of the set.

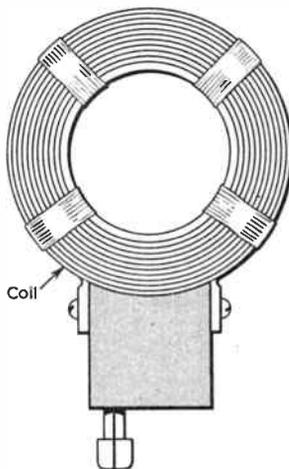If anyone can help Mr. Quick, they can contact him at 15 Beechwood Grove, Horbury, Wakefield, Yorkshire.



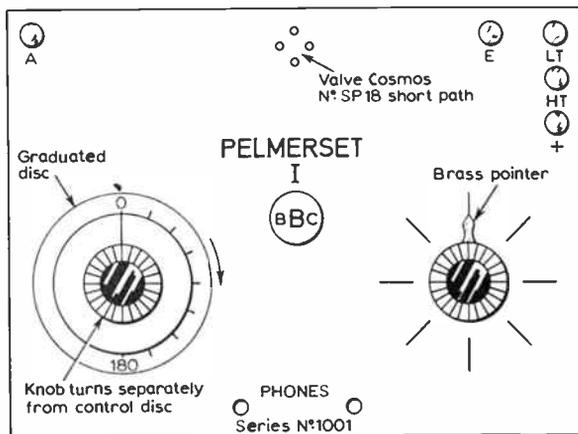Mr. Quick's plug-in coil and the front panel of his vintage receiver.



EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

LEARNING BY PRACTICAL PROJECT STEPS

PART 3—TRIGGER CIRCUITS

LAST month we saw that there is, at least, one circuit which is sensitive to the rate of voltage change, i.e. the divider circuit would only respond correctly if we caused rapid changes in lighting level at the photo cell; slow changes would not make the divider work. There are other circuits

which like to see what are known as "fast going edges" to signals; as a result, a range of circuits has been developed which will accept slow changing inputs and convert these into signals having fast rise and fall times.

These circuits are called *triggers* because their

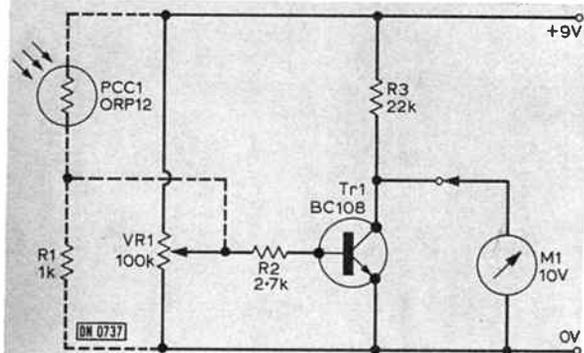


Fig. 14a: If PCC1 and R1 are used as alternatives, omit VR1 and link in PCC1 on the "left-hand" end of R2.

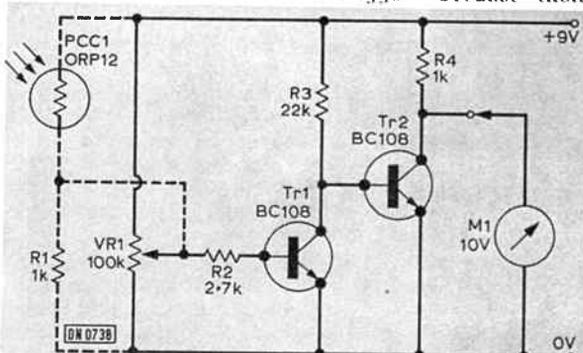


Fig. 15a: The extra stage of amplification effectively improves the rise time of the output signal between the power rail extreme voltages.

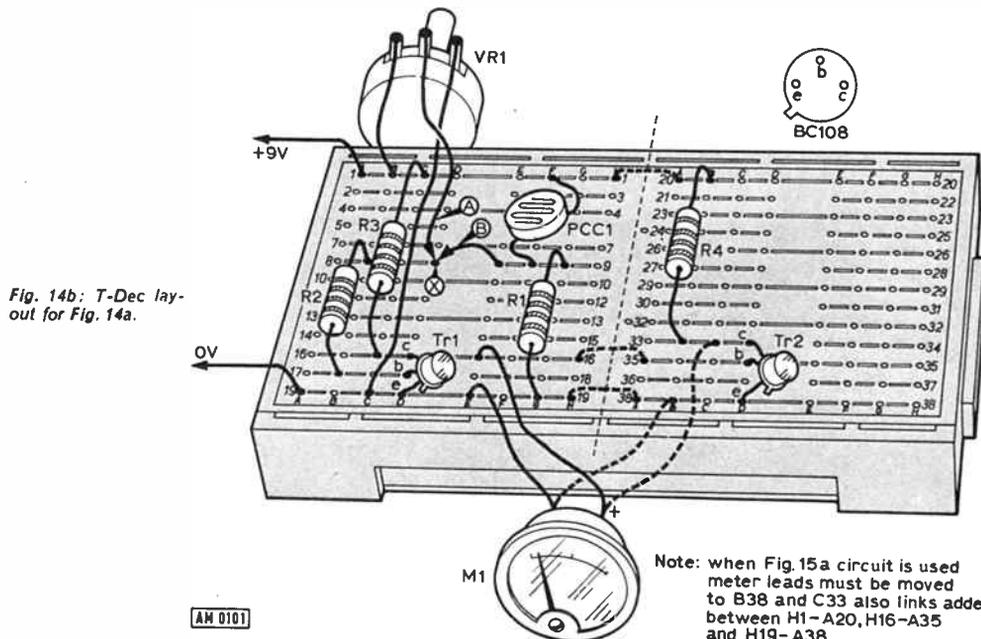


Fig. 14b: T-Dec layout for Fig. 14a.

Fig. 15b: T-Dec layout for Fig. 15a.

Note: when Fig. 15a circuit is used meter leads must be moved to B38 and C33 also links added between H1-A20, H16-A35 and H19-A38

AM 0101

output will always be in a certain state (say zero volts) until the input signal rises to a certain level and, irrespective of the time it takes the input to get to this level, when the critical voltage has been reached the output changes to a higher level (say +9V) instantaneously.

In practice everything takes a certain amount of time to happen, so "instantaneously" is, perhaps, too strong a term to use. Nevertheless, as you will see if you do some of the following experiments, we can make extremely slow voltage changes trigger a circuit to give edges to waveforms that change from one level to another in a few millionths of a second.

Fast and slow "edges"


First of all we had better look at what we are calling an "edge" so that we can compare the difference between fast and slow edges. Fig. 14a is a very simple transistor amplifier stage which gives an output inversely proportional to the voltage at the wiper of VR1 (or, if you are using the photocell alternative, the junction of PCC1 and R1).

Measure the voltage at the collector of Tr1 with VR1 set to the bottom of the track (Alternatively completely shade PCC1). You should read about +9V because the transistor, in the absence of base current, is not conducting. Slowly increase the voltage at the wiper of the potentiometer by rotating it (or slowly increase the amount of light falling on PCC1); base current will start to flow and the voltage at the collector will start to fall.

The thing to notice is that you can control the level of the measured voltage quite easily and get any value you like by careful adjustment of VR1 or the amount of light falling on PCC1. Try and get a "feel" for the rate at which the measured voltage changes for given rates of moving the potentiometer or illuminating the cell.

You can use the wires A or B in the layout and transfer one, or other, of them to point X—depending on whether you were using the cell or the potentiometer. Fig. 15a shows an extra stage of amplification. Carry out the same experiment but now measure the voltage at the collector of Tr2. Obviously the extra stage gives us inversion so when the potentiometer is down the measured voltage is low.

Now slowly increase VR1 until the voltage starts to rise and then try and control it in the same way as before. It should be very apparent that, for the same rate of change in position of the wiper of

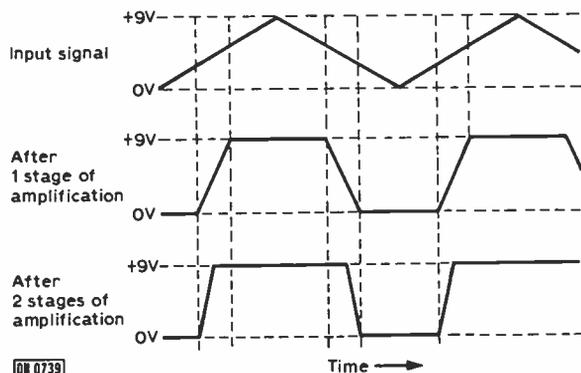

DN 0739

Fig. 16: Note the increased amplification appears to enhance the signal's rise time between the supply voltage limits.

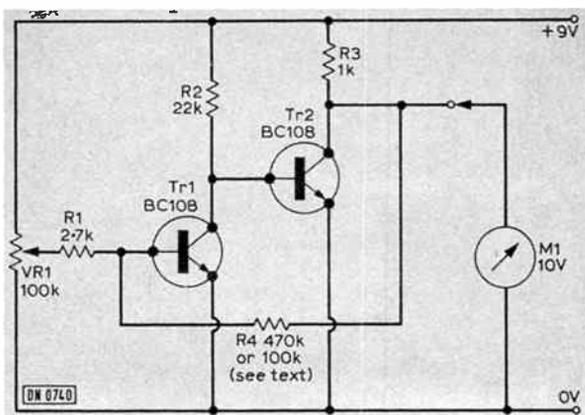


Fig. 17a: True trigger action is obtained by using positive feedback via R4.

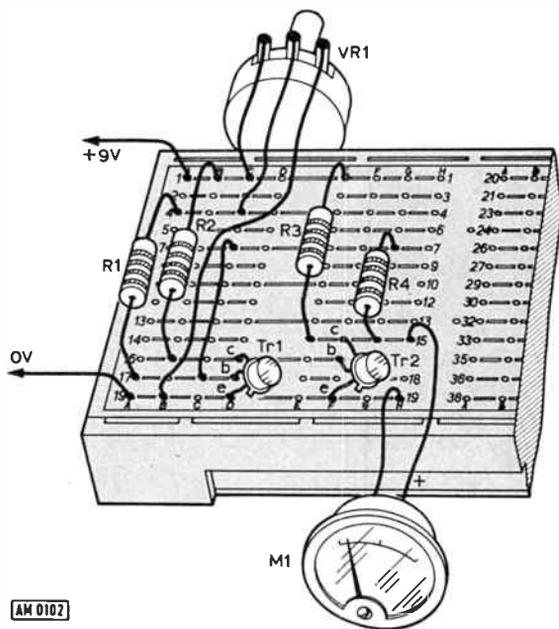


Fig. 17b: T-Dec layout for Fig. 17a.

the potentiometer, the voltage at Tr2 goes from zero to +9V very much quicker than it did before.

It is, however, still possible to set it mid-way between the two extremes by careful adjustment. The effect is even more pronounced using the photocell and you should start to appreciate the increase in the rate of change of the signal at the output.

Amplification

The signals we have been talking about can be described as waveforms as shown in Fig. 16. The portion of the signal between the low and high voltages of the output is called an edge and you can see that it has become much steeper with the extra amplification.

Simple amplification thus increases a signal's rise time but there is still the possibility of getting a mid-rail voltage during the transition—especially if the input signal was unusually slow. Ideally we

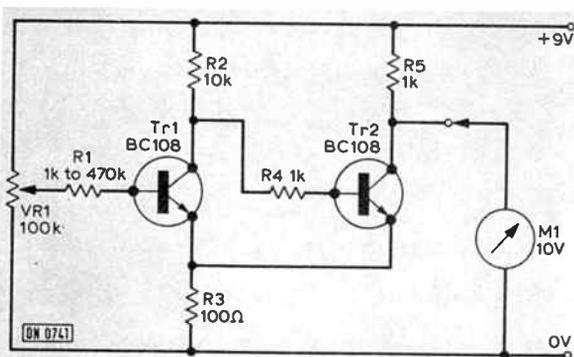


Fig. 18a: Schmitt trigger circuit. The trigger level can be controlled over small limits by changing R1 in the range 1kΩ to 470kΩ.

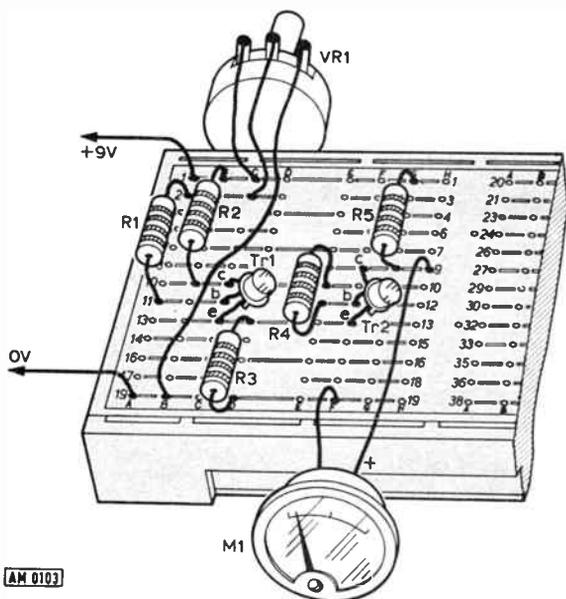


Fig. 18b: T-Dec layout for Fig. 18a.

would like to have a circuit that gives a fast change irrespective of the rate of change of input. The circuit in Fig. 15a has been modified in Fig. 17a with a resistor coupling the output back to the input. We have introduced a positive feedback loop.

If VR1 is slowly increased the voltage at Tr2 collector will, at some time start to rise; when this happens current starts to flow through R4 back into the base of Tr1 and effectively increases the base current we are already applying from the potentiometer. The effect is to make the voltage at Tr2 rise even more enhancing the effect until eventually Tr2 is totally non-conducting. All we needed to do was set the operation in motion by initiating base current into Tr1; once that was started the voltage at Tr2 collector would move from zero to +9V without any further movement of the potentiometer—the feedback loop did the rest.

The feedback cycle occurs extremely rapidly (the speed is limited only by certain internal parameters of the transistors) so the output changes level at a speed set by the circuit and no longer by the rate at which we turn the knob on VR1. Try it for your-

self and you will find it impossible to set a mid rail voltage at the output.

When VR1 is at the limit of its travel, try turning it down; the same thing happens on the downward going edge of our input signal. Notice that there is a sort of “no-mans-land” between the positioning of the wiper for upward going triggering and downward triggering. This is known as “hysteresis” and is very useful in differentiating between the two levels we are considering.

Hysteresis

In this circuit, you can control the amount of hysteresis by means of the value for R4. A 470kΩ resistor will give the smallest differential between upward and downward triggering levels but by reducing it to 100kΩ you can widen the gap between the levels. This circuit is operating as a true trigger and the feature to take note of is the use of positive feedback to speed up the edge. If you think about the circuit a bit you will find it is not very different from the bistable described last month.

Schmitt trigger

Probably the best known trigger circuit is the Schmitt trigger shown in Fig. 18a. When the voltage

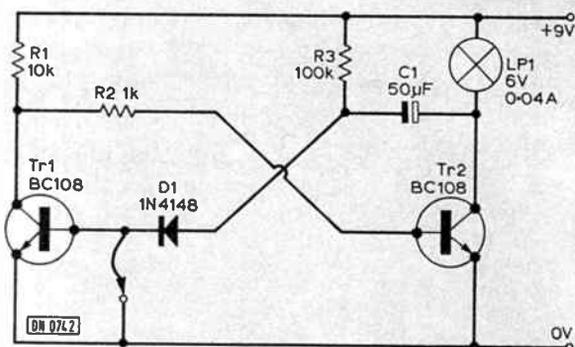


Fig. 19a: Basic monostable multivibrator. Capacitor C1 can be increased to 3,000μF to extend the dwell time.

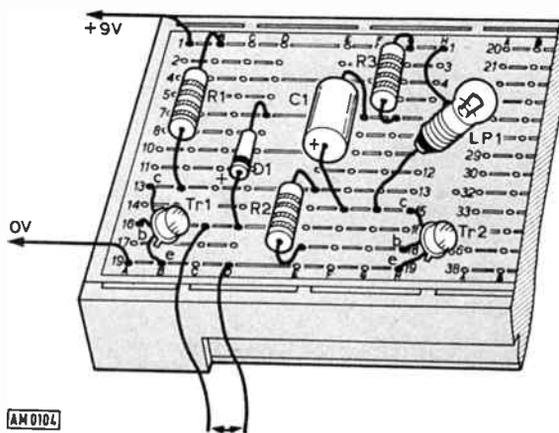


Fig. 19b: T-Dec layout for Fig. 19a.

at the wiper of VR1 has reached a certain level base current will start to flow in Tr1 and the voltage at its collector falls slightly; this reduces the base current into Tr2. The two emitters are, however, connected together and as Tr1 starts to conduct the voltage at the "top" end of R3 starts to rise.

Because this is connected to the emitter of Tr2 we reduce—even more—the potential difference between Tr1 collector and Tr2 emitter thus the base current into Tr2 becomes less. Here again we have a positive feedback loop caused by emitter coupling and the effect of this is to accelerate Tr2 going out of conduction and the output voltage drops very rapidly.

Again this occurs independently of the rate we are applying signal at the input and the speed is limited only by the transistors' parameters. Reduce the input voltage slowly and the opposite happens.

Monostable multivibrator

Another circuit which often comes into the category of trigger circuits is the "monostable multivibrator" shown in Fig. 19a. Unlike the Schmitt trigger it is a little bit more complicated to initiate triggering but it offers a useful bonus. It has a "short term memory". We can design it so that it will trigger rapidly on the receipt of a suitable signal but the output from it stays at the new level for a fixed period of time before rapidly returning to its original state.

Make up Fig. 19a on T-Dec and follow this brief description of how it works. Initially let us state that D1 serves no purpose in the circuit except to protect the emitter base junction of Tr1 from a high reverse voltage that is generated during the switching operation.

When the circuit is switched on the lamp may go on for a few moments until things have settled down. When the lamp has gone off we should arrive at a stable state of affairs in that base current is provided for Tr1 through R3—hence its collector is at near zero volts; because of this Tr2 will be cut off and the potential at its collector will be high (about +9V); consequently the lamp will be off.

If we deliberately knock Tr1 out of conduction, by rapidly short-circuiting its base to ground with the flying leads, we can momentarily establish base current in Tr2 and it conducts. The light goes on and the voltage at its collector drops to about zero. However the capacitor transmits this negative-going voltage excursion to the base of Tr1 and the potential at the junction of R3 and C1 falls to about -8V (it was previously +1.2V caused by the forward voltage drops of D1 and the base emitter junction of Tr1).

Assuming we have immediately removed our short-circuit link Tr1 will stay out of conduction because no base current can flow until the potential at the anode end of D1 has regained its level of +1.2V and this will take time because the negative end of C1 has to charge back to this value through R3. This takes quite a few seconds and during this period the lamp stays alight.

When this has been reached. Tr1 starts to go back into conduction and the potential at its collector falls giving rise to an increase in voltage at Tr2 collector; this is fed back momentarily through C1 and enhances the base current into Tr1 (positive feedback again). As a result of all this the lamp switches off very rapidly. If you have a 3,000 μ F capacitor you can substitute it for C1 and get a "dwell" time of about 3½ minutes. The dwell time can be calculated as $0.7 \times C1 \times R3$ (C in Farads R in ohms and the time will be in seconds).

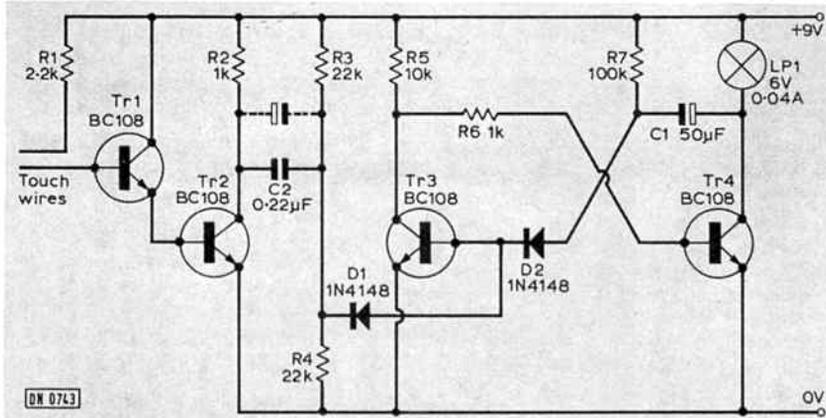


Fig. 20a: Touch-sensitive child's room-light. Supply current is approximately 1mA rising to about 80mA when the lamp is on. Duration of 3½ minutes can be obtained by making C1 3,000 μ F and C2 50 μ F. The capacitor shown dotted, across C2, indicates how it is connected—plus to R2.

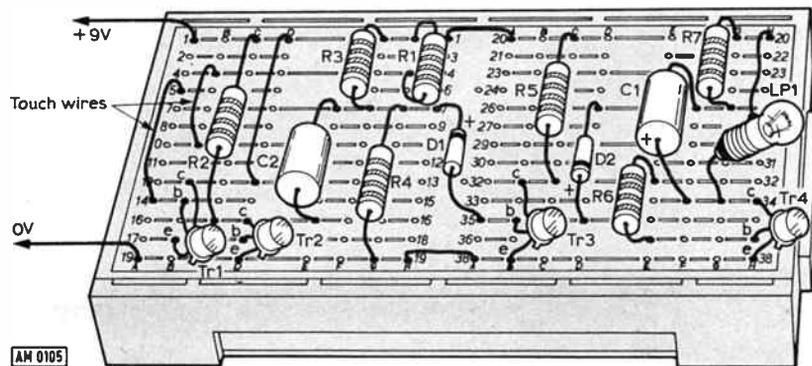


Fig. 20b: T-Dec layout for Fig. 20a.

Touch switch

The monostable thus gives us trigger action and a timing function which can be put to many uses. A novel circuit for a safe child's bedside light is shown in Fig. 20a. It is a touch sensitive switch coupled to a monostable that switches on a lamp for a pre-determined period of time (Warning: the novelty is more likely to keep a child awake than get him off to sleep!).

continued on page 756

HOTLINES

ON RECENT DEVELOPMENTS

THE YEN

HAVE you ever had a yen to do something?—the Japanese have. My ageing eyeballs have recently scanned a report which comes from the Orient from an "impeccable source". In February of this year, the Electronic Industries Association of Japan found that the total sales of electronic parts and components from Japan amounted to 101,079 million yen—which is a lot of yen for just one month's effort. It is interesting to see how this figure breaks down. For example, electron tubes (that's valves in English or Toobs in American) in February amounted to 17,841 million yen and showed an increase in February 1972 of over 10%. Integrated circuits accounted for 8,483 yen and showed an increase over the same month last year of a staggering 92%. On these figures, the Western comics who chant "Ha so?" might easily find the answer to be "Velly well thank you".

Other news from Japan is equally interesting. One snippet from spies is that Sony are to withdraw from the electronic calculator market altogether. Another is that Government approval (Japanese) has been given for the joint enterprise between Alps Electric and Motorola for the manufacture and sale of ICs. This American/Japanese Company is aiming to sell 3,000 million yen's worth of ICs in 1974.

KEEPING A WATCH!

Still in yen land, the Japanese watch industry is claiming that some 200,000 watches using piezo-electric crystals, will be produced there this year. Production lines are eagerly being set up to manufacture C-MOS ICs and there is a hive of activity in the liquid crystal readout sector. If all this activity goes through, then clearly now is the time to watch Japan.

MINI FREQ. COUNTER

What other interesting things are happening in Japan? Well, quite apart from the considerable amount of electronics business that's taking place (would you believe that this country sold 83,349 million yen's

worth of communications equipment in 1972?) there is always the neatness, the preciseness of some of the products. Perhaps an excellent example is in the field of frequency counters—feed a signal in and the frequency is flashed up on a digital readout. Well, one Company (and I'm talking about a production item, not a prototype laboratory wonder) is marketing a miniature but professional standard frequency counter. It gives a digital readout of frequency from 15Hz to 50MHz although there is an optional pre-scaler which extends this to 220MHz at the upper limit. It's completely portable and uses internal rechargeable cells. The internal oscillator is accurate for the majority of applications having a stability of ± 0.0005 at 25°C. The size is particularly impressive—120 x 175 x 25 millimetres. Just grab yourself a ruler or do a quick mental conversion and you'll see that this slips into your pocket (there's 25.4 millimetres to the inch!).

LASER TELEVISION

One could hardly look at the Japanese electronics scene without taking in the television industry. Latest thing in this sector to catch my eye is a large screen laser colour television projector. This beastly is a considerable improvement over its younger sister which made a debut at the World Exposition in Osaka in 1970. The earlier model had a resolution of 525 lines. The latest version has a resolution of 1,125 scanning lines. A krypton ion laser is used to generate the red, while an argon ion laser emits the green and blue spectrums. Perhaps we're not at the home use stage yet, but maybe the time will come when an entire wall will light up with a full colour, 3D life-size TV screen—so real you'll be able to step through your kitchen wall and join in a quick romp with Noddy or a punch-up with Ena Sharples; the mind boggles.

In serious terms, the new laser colour television projector has some very real advantages. The image is very clear and sharp. It is also very bright and there is very little divergence, too. One feature which my Japanese contact did not highlight but which is of interest is that the

polygonal mirror used for horizontal scanning rotates in magnetic bearings. These have certain advantages over conventional bearings, notably reductions in noise and vibration.

CHINESE PUZZLE?

How many characters or words do you think there are on this page? How about a page in a Chinese newspaper then? No, I haven't nipped across on the Kowloon ferry, I'm still in Japan where a leading electronics manufacturer has just launched a very high-speed printer which prints out the Chinese language. It will produce some 600 lines of Chinese in 60 seconds which, as I'm sure you know, works out at 12,000 Chinese characters every minute. A computer is used to hold information prior to printout but manual over-ride can be used. The printout can be in either lateral or vertical rows so it doesn't matter which way you want to read it—the machine can oblige. Damn clever, those Chinese, or should that be Japanese? I'll have to get myself properly orientated.

EARTH STATIONS

In the early days, the Japanese electronics industry suffered (rightly or wrongly) from a "cheap goods" brand. It is now no longer possible to regard all its products as in this category. An earth terminal is no small thing, neither is there any room for sub-standard effort. In this field, one Japanese Company alone has built, supplied and/or installed very nearly 50 (fifty) earth stations.

GET ORGANISED!

A little gem from England to finish with. In a church at the Royal Naval Air Station Yeovilton, Somerset, an electronic organ began to play itself—a radar beam was being picked up by some of the internal components. About time the Navy got itself organised!

Ginsberg

ARE YOU 'SWITCHED-ON'?

make this ULTRASONIC REMOTE CONTROLLER

By the flick of a switch from your armchair you can switch on the television, radio, lamps, intruder alarm, electric kettle, electrically operated curtains, operating rotating aerials, darkroom lights. For bedridden patients, handicapped and elderly people, there is a multitude of uses for this valuable tool, from remote signalling to opening electrically operated doors—without the need for them to go near the mains supply. Your son can have a lot of fun, too, if you make it for a Christmas gift.



IN NEXT MONTH'S PRACTICAL WIRELESS



AF/HF/VHF TROUBLE-TRACER

Our Trouble-Tracer will provide you with a test signal ranging from audio to VHF. Test probes pick up signals from the equipment under test and feed them into an amplifier and speaker. All in the one cabinet—What else could you want?




Curing Radio Interference in Audio Equipment

Do you suffer interference on your tape recorder or HI-FI from nearby radio transmitters? This feature tells you how to cope with this ever-increasing problem.

**JANUARY ISSUE ON
SALE 7th DECEMBER**

PORTABLE FLUORESCENT LAMP UNIT FROM YOUR 12V BATTERY

FOR: EMERGENCY LIGHTING, CARAVANS

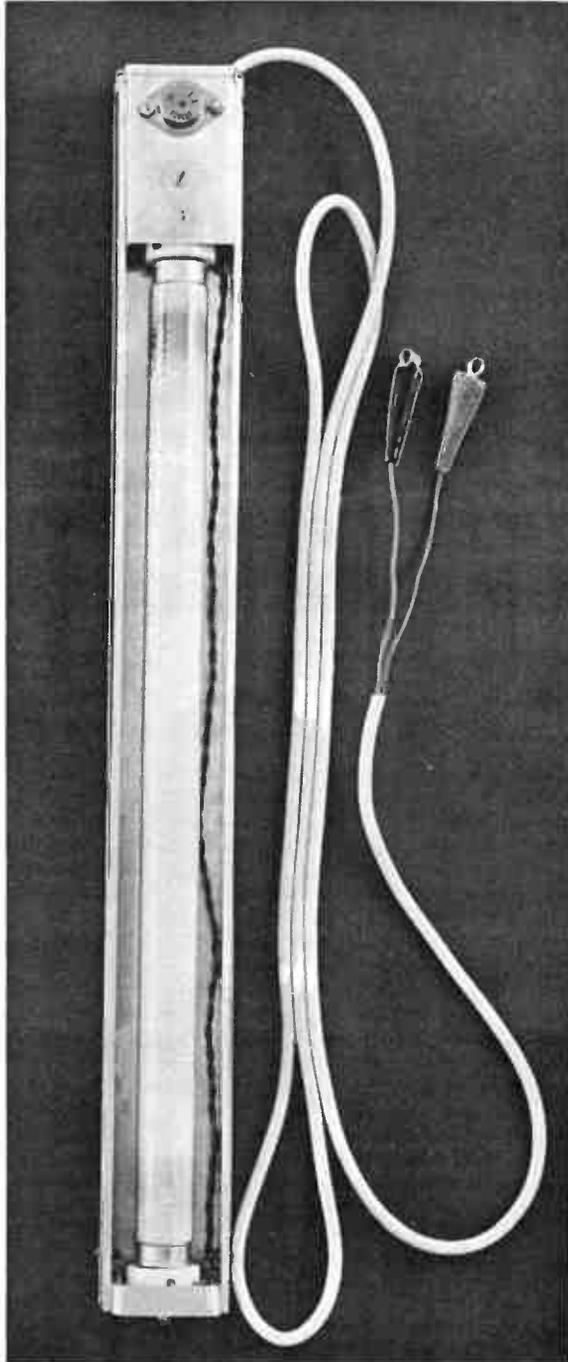


THE battery operated 15W fluorescent lamp unit described here is of simple construction, being designed around readily available components. The whole assembly is made up in aluminium, consisting of a framework which supports the tube and houses the oscillator module. A cover plate acts as reflector and dust cover.

CIRCUIT DESIGN

Fig. 1 shows the circuit. A 2N3055 silicon power transistor operates as a transformer coupled class 'C' oscillator. The fluorescent tube is supplied from a third winding on the transformer. Satisfactory operation is obtained from 10 to 15V.

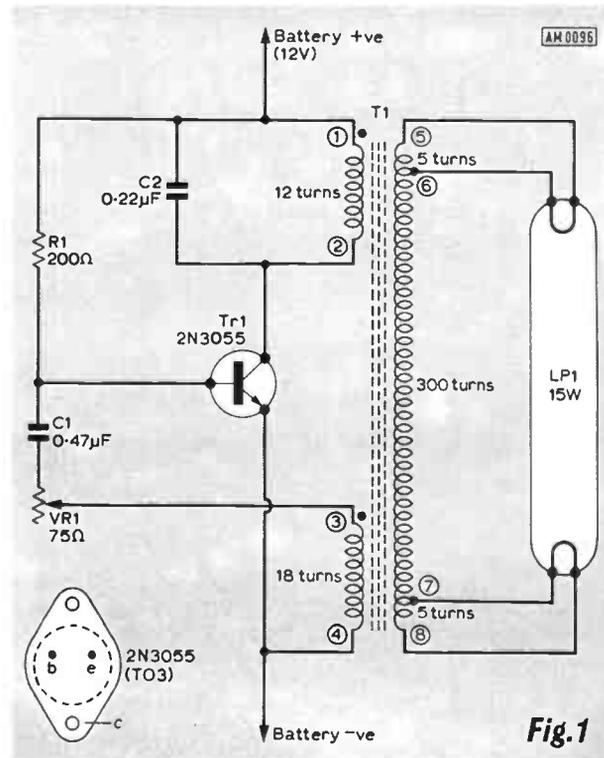A variable resistor provided in the base circuit of the transistor ensures correct operation with devices having any gain within normal spreads. The



NIT TERRY



VANS & CARS, LOFTS, SHEDS, GARAGES, MOBILE RALLIES, ETC...

transformer is designed around Mullard FX2242 pot cores. The collector winding is tuned by a 0.22µF capacitor. Bias for the transistor is provided by a 200Ω resistor from the positive supply rail.


The operating frequency is determined by the 0.47µF base timing capacitor C1, the variable resistor, the tuning capacitor and the load conditions. Since the load (the fluorescent tube) is a high resistance until alight, the circuit has a "soft" start, the oscillations starting at low frequency and amplitude and building rapidly over a few seconds until settling down at steady amplitude and high frequency once the tube 'strikes'.

CONSTRUCTION

The tube and oscillator housing is made up from aluminium strip and sheet as shown in Fig. 2. This

construction method allows assembly with the tools normally available in a small workshop. The cover plate is the most complicated piece, but being fabricated from 1/16 in. sheet this makes the work quite easy. Cutting is accomplished with a Stanley knife using a laminate cutting blade (Stanley No. 5194). The cut edges should be filed smooth. The original cover plate made by the author was bent up in a normal small metalwork vice, extra long 'jaws' being made up from 2 x 1 in. hardwood.

The oscillator housing is bent up from 1/16 in. sheet as is the tube mounting bracket. The power transistor is mounted on the oscillator housing so that the base and emitter pins are inside the casing, directly above the circuit board. One bi-pin tube connector is also firmly mounted to a bracket bent up from this housing. Two side struts are bolted on to this oscillator housing. The smaller 'U' bracket supports them at the far end and also holds the

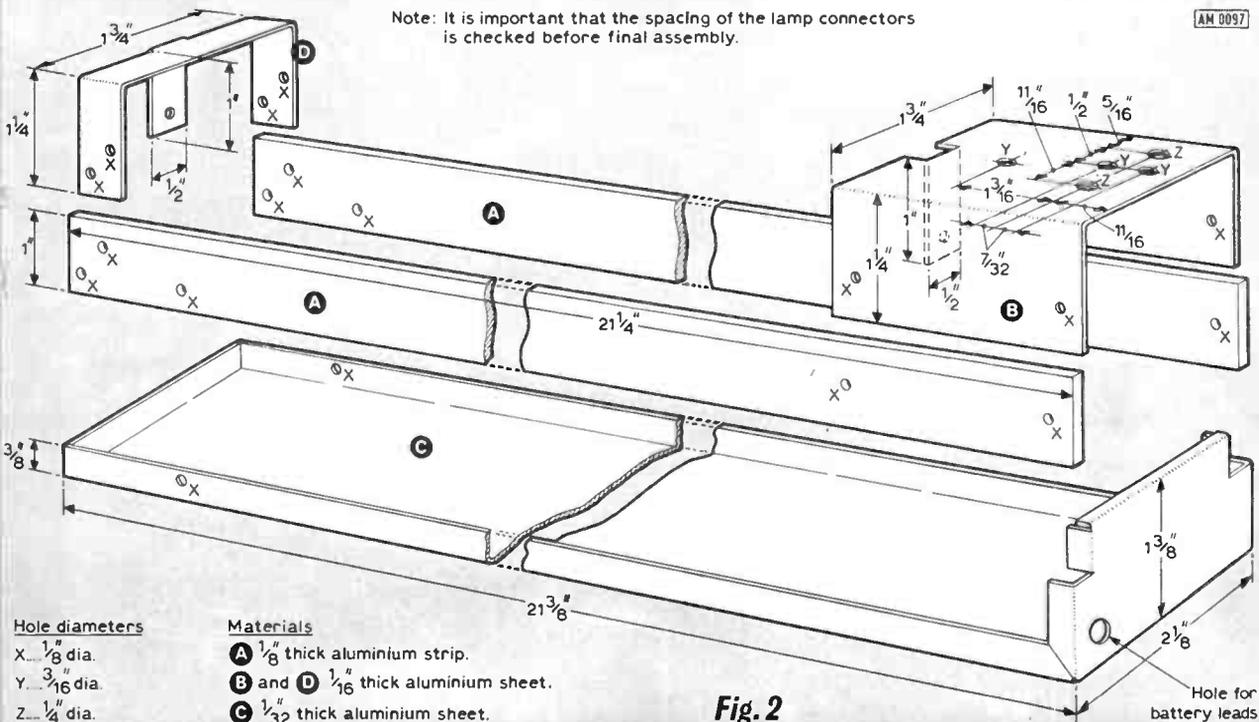

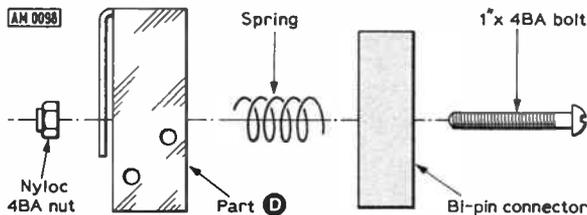


Fig. 3: Details of the spring-loaded tube connector.

other bi-pin tube connector. This connector is mounted on a lin. 4BA bolt and spring, Fig. 3, to facilitate easy fitting of the fluorescent tube by pulling back the connector and then pushing it over the tube pins.

OSCILLATOR PCB

Fig. 4 shows full size layouts for both the component and the copper side of the circuit board. The board can be made by laying the drawing over a piece of copper clad board ready cut to size, and drilling through all the holes. It is essential that the drawing does not move during this operation. The layout can then be copied on to the board using a fine brush or mapping pen and cellulose paint. The board can then be etched off in ferric chloride (strong) solution. (A 500ml bottle is adequate and may be obtained from most chemists to order.) After etching the board should be washed thoroughly in warm water. The paint can be removed with thinners or rubbed off with scouring powder. The components can then be mounted in place and soldered. Flying leads are required for the three transistor connections. Veroboard terminal pins are used for the four connections to the fluorescent tube.

VARIABLE RESISTOR

The variable resistor VR1 used here is primarily intended for use as a convergence control in Colour TV receivers. If difficulty is experienced in obtaining this control, it should be ordered from a TV dealer as a spare part (e.g. Decca CTV25 Part No. 535167). This control is mounted near the edge of the board so that adjustment may be made by turning the knob edge with a forefinger from the end of the lamp unit.

THE TRANSFORMER

The transformer is wound on a Mullard DT2180 bobbin. Enamelled copper wire is used throughout and all windings are wound in the same direction.

The collector winding is put on first and consists of 12 turns of 28SWG wire, the start labelled (1) and the finish (2). The turns should be wound close together. The base winding is wound directly on top of the collector winding and consists of 18 turns of 28SWG wire, also closely wound. Label the start (3) and the finish (4). Next a single turn of insulating tape is put round the bobbin to isolate the low voltage windings from the tube supply winding.

Finally the high voltage winding is put on consisting of 310 turns of 32SWG wire with taps brought out after 5 and 305 turns. This winding is layer

★ components list

C1	0.47 μ F 250V polyester
C2	0.22 μ F 250V polyester
R1	200 Ω 5W wire-wound
VR17	5 Ω pot. wire-wound (see text)
Tr1	2N3055 with insulating kit
LP1	15W fluorescent tube

Miscellaneous


Pot core (2 x half cores) Mullard FX2242 and bobbin DT2180 (available complete from Hawnt Electronics Ltd., 112 Pritchett St., Birmingham, B6 4EN for £1.20 inc.).

Bi-pin tube connectors (2). 28 and 32SWG enamelled copper wire. PCB, 3 x 1 $\frac{1}{2}$ in. Length of twin 5A wire, as required, with two large crocodile clips.

Aluminium: 4ft of 1 x $\frac{1}{8}$ in. strip (Part A), 6 x 5in. of $\frac{1}{8}$ in. sheet (Part B), 24 x 3in. of $\frac{1}{32}$ in. sheet (Part C).


wound, with a turn of insulation put right round the finished bobbin. The start, tap 1, tap 2 and finish should be labelled (5) (6) (7) and (8) respectively. The two ferrite cores can then be placed around the bobbin and the transformer loosely bolted on to the circuit board.

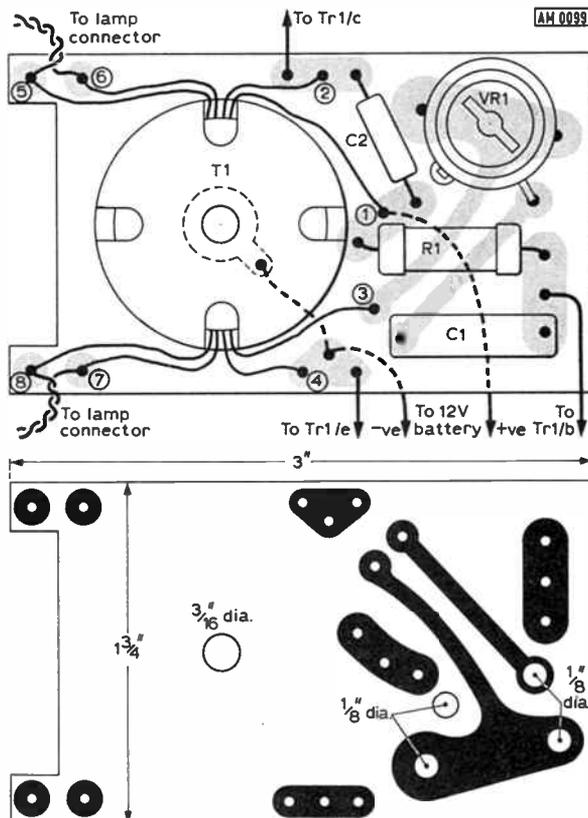The leadouts can now be cut to length, scraped clean at the ends and soldered to their respective points on the circuit board. Once this has been



All holes drill No.55 unless otherwise stated.

Fig. 4: Full size layout of printed circuit board and component location on board.

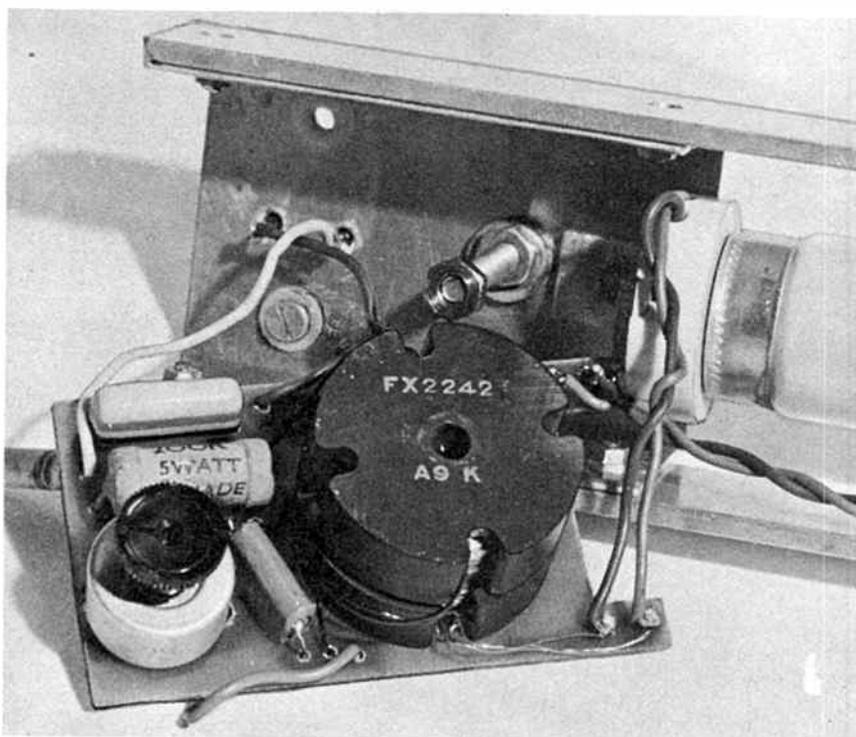

A view of the oscillator assembly at one end of the lamp unit.

done, the fixing bolt may be removed and the top ferrite core taken off. A small piece of Sellotape should be stuck on to the centre pole-piece of the core. This provides a small gap which ensures that the core cannot be saturated by the primary magnetic flux. The upper core is then replaced and held into place with a further piece of Sellotape around the join (the cores are finally held together by the module mounting bolt).

An 'exploded' view of the transformer is shown in Fig. 5 which also shows the method of mounting the module.

TESTING

The power transistor should be mounted on the module housing with a mica washer and two nylon bushes, usually supplied with the transistor. A smear of silicone grease should be applied to each side of the mica washer to ensure good thermal contact. The flying leads should be connected to the transistor, ensuring that the base and emitter leads are not reversed. The supply lead should also be connected to the copper side of the circuit board. Do not fit the tube or module into the framework yet.

Connect the power leads to a 12V supply, ensuring correct polarity. The oscillator should 'whistle' loudly, since without a load the operating frequency is lower. If the circuit does not oscillate it is probable that the phasing between the collector and base windings is incorrect. Reversing either winding should ensure correct operation.

ASSEMBLY

Once it is established that the oscillator is functioning correctly, the fluorescent tube connectors

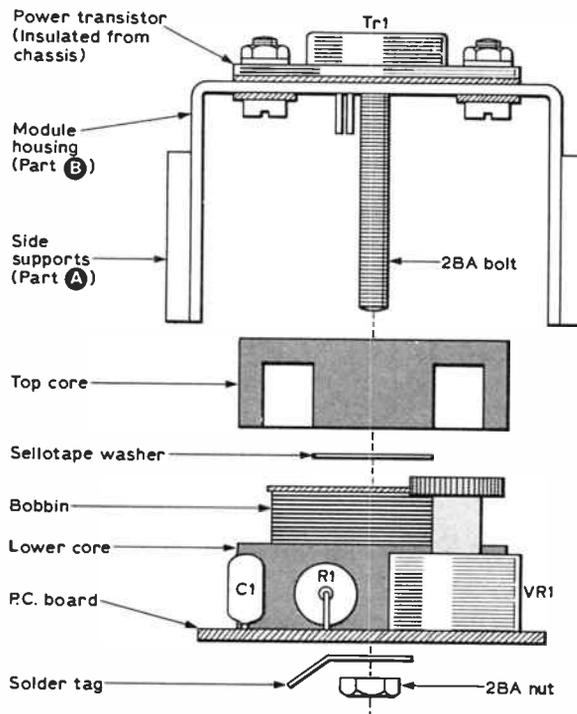


Fig. 5: An exploded diagram of the oscillator transformer and mounting.

may be wired up and the module bolted into the framework. Care must be taken not to overtighten the mounting bolt as the ferrite cores are very brittle and easily fractured. The nut can be sealed with a drop of paint or varnish. The tube can now be fitted into place and final adjustments made.

Reconnect the 12V supply, ensuring correct polarity. The oscillator should start up at a medium frequency, increasing rapidly in pitch until the tube strikes and lights. The oscillator should then be inaudible. Adjust VR1 for maximum brightness. At one end of its travel the light will be dim and at the other extreme excessive base drive will cause squegging with consequent flickering of the lamp. Once the oscillator is correctly set operation should be satisfactory over the range 10 to 15V. The current consumption should be between 1.3 and 1.5A at 12V input.

The cover plate should now be clipped on at the oscillator end and pressed home. Two self tapping screws hold the cover in place.

NOTE 1 Connecting the lamp to the battery with reverse polarity will not cause any damage since the transistor is reverse biased and cut-off, resulting in practically zero current flow.

NOTE 2 The metal framework has been left completely isolated. Slight radio interference may be caused in the immediate vicinity of the lamp unit. To reduce this interference to a negligible level (field localised to within 4ft.) the frame should be connected to either the positive or the negative supply line. Connect a short lead from either to the soldering tag on the module mounting bolt. ■

**EXPERIMENTAL WORKSHOP—Part 3—
Trigger Circuits—continued from page 749**

If the gap between the touch wires is bridged with the fingers a minute current flows into the base of emitter follower Tr1. This produces a considerably larger current into Tr2 and its collector falls to zero. The junction of R3 and R4 is momentarily pulled down by C2 from about +4.5V to -4.5V. This negative going signal is coupled to the base of Tr3 of the monostable through D1 and this switches off Tr3 starting the monostable cycle.

The lamp goes on for the period set by C1 and R7. Capacitively coupling the touch-sensitive switch with C2 allows the user to keep his finger on the touch wires without interfering with the monostable action.

The values shown in the circuit only give a dwell time of a few seconds—for experimental purposes—but a reasonable period of time of 3½ minutes can be arrived at by increasing C1 to 3,000µF, and C2 must be increased to about 50µF.

Next month we shall look at a development of the monostable; the astable multivibrator.

COMING SOON
Q4 MATRIX MATE

Multimeter Competition RESULT

In our June "Multimeter" Competition readers were invited to place eight features of the new Sinclair Radionics multimeter DM1 in order of appeal to the average P.W. reader.

Having considered all entries, the judges decided that the best received were a large number of identical attempts which had placed features in the following order:

1st-E; 2nd-D; 3rd-L; 4th-J; 5th-K; 6th-B; 7th-A; 8th-C.

In accordance with the rules, these tying competitors then participated in a postal eliminating contest from which the eventual winners were judged to be Mr. J. Bertram, of Fenham, Newcastle-upon-Tyne; Mr. R. Harris, Knowle, Bristol; Mr. J. R. Mann, Knaresborough, and Mr. G. Rider, Hythe, Southampton.

These four readers each win a Sinclair digital multimeter and 12 months' free copies of Practical Wireless.

The tying competitors who entered the final postal eliminating contest, and were subsequently unsuccessful, each receive a consolation prize and 12 months' free copies of Practical Wireless.

SPRING INTO ACTION


The next series of special issues of P.W. will be in the Spring 1974.

In the coming months we shall be giving advance information on our new

EXCLUSIVE P.W. PROJECTS

COMING IN THE SPRING ISSUES.
ORDER YOUR COPIES NOW

Successful Soldering

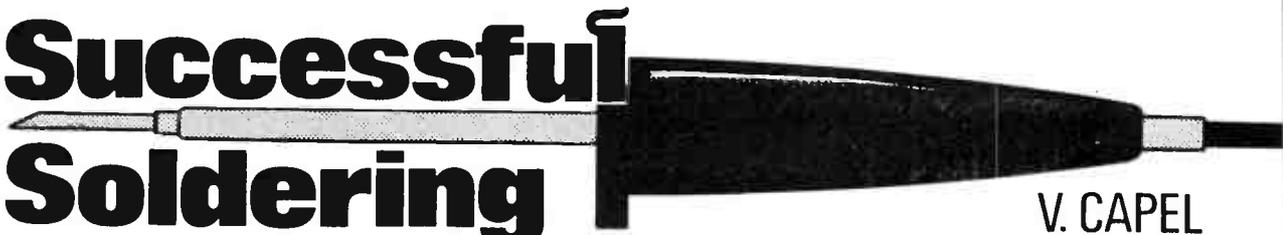

V. CAPEL

WITHOUT a doubt one of the most important tools for either professional engineer or amateur hobbyist is the soldering iron. Nearly every component has to be soldered, so whether constructional work or repairs are being carried out, the iron has to be called into use. There are a considerable number of soldering instruments of all sorts and sizes available, so in this article we will take a look at some of them to see which are most suitable for particular applications, and their respective advantages and disadvantages.

BASIC REQUIREMENTS

We will start off with what could be called the basic workshop instrument. This is an iron with the element operating at mains voltage and a wattage of between 25 and 40 watts. The size allows for most printed-circuit and general component soldering, but the bit may be rather large for some of the finer printed boards. For this reason, most irons have a variety of interchangeable bits so that a thinner one can be fitted for fine work.

In practice though, bits are not often changed according to the requirements of the job. For one thing they have a habit of getting seized-up and difficult to remove. They should really be loosened from time to time to facilitate changing, but in practice this precaution is usually neglected. Also, most workshop irons are kept on continually in order to be instantly available, so to change the bit for a particular job would mean allowing the iron to cool down and waiting for it to warm up again after the change, plus of course a repeat performance for the re-fitting of the normal bit. Going to the other extreme, irons of this type and wattage have a limited heat output and so cannot tackle large jobs.

The difference between temperature and heat-volume must be noted here. All soldering irons attain a temperature which exceeds the melting point of solder (168°C for the high-quality 60/40 grade) otherwise they would be useless for their purpose, but some deliver a greater quantity or volume of heat than others. This is determined largely by the wattage of the instrument. Hence, a soldered joint to a punched-out chassis tag may be impossible with some smaller irons because the chassis conducts the heat away faster than the element can produce it, and so the bit cools rapidly to below the required temperature. Any large area of metal will have the same effect.

Another factor is the size of the bit. The bit effectively stores heat and so acts as a reservoir. Heat flows out of the bit when the iron is used and more heat is supplied by the element. However, the out-flow can be greater than the input for a short period until the stored heat is exhausted. Thus larger areas

can often be soldered than would be feasible with a particular element-wattage, if the iron is fitted with a large bit. When the iron has been thus used, it will take longer for the bit to return to correct operating temperature than would a smaller bit because it has what is termed, a slow heat recovery time.

IDLING TEMPERATURE

A further consideration is the heat loss when the iron is switched on but is not in use, as is the case in most workshops for the greater part of the time. While the iron may get hotter than needed because there is no heat conduction by application to a work area, it must not get so hot as to damage the element or cause premature deterioration of the bit. Hence the physical size of the iron barrel and bit must not be too small for the element size so that heat losses by convection and radiation are insufficient to keep the temperature to a safe limit. It follows then, that physical size is closely related to element rating and should not be too small or too large.



Stiron 20W and 60W irons, made in Sweden and featuring iron-coated bits.

In order to keep the temperature of an iron down when it is not being used for long periods, it is the practice in some workshops to operate a half-heat arrangement, whereby a lamp is switched in series with the iron. The temperature will gradually rise to not far short of the correct operating level, then when the iron is needed, the lamp is switched out and the temperature comes up within a few seconds. Another method is to stand the iron on a large chunk of metal which keeps it from overheating by conduction. An old speaker magnet is sometimes used for the purpose, as this also attracts the iron and keeps it in place.

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit - £24.95! (PLUS VAT)

The Cambridge - new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price - and by building it yourself you can save a further £5.50!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{1}{8}''$. That means you can carry the Cambridge wherever you go without inconvenience - it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

The cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 - so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer - it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge


- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{1}{8}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:

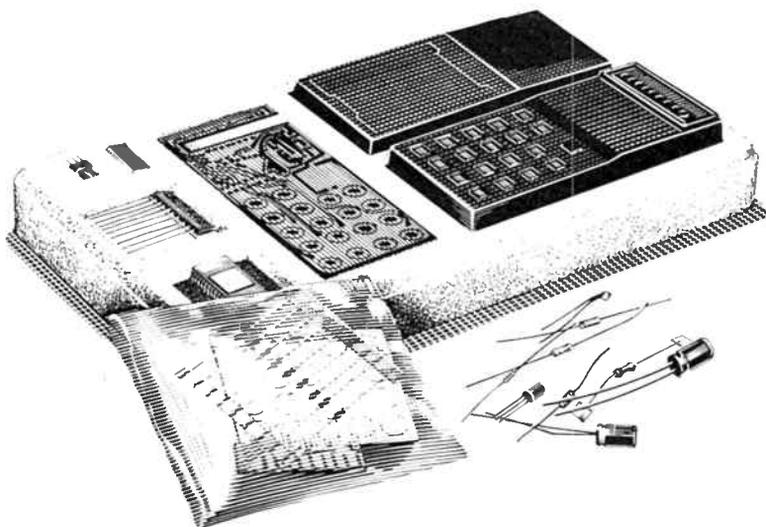1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic— for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

Logs Sines Cosines
Tangents Reciprocals nth roots
Currency Compound
conversion interest
and many others ...

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.


Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)

Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)

To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdonshire, PE17 4HJ		PW 1273
Please send me	Name	
<input type="checkbox"/> a Sinclair Cambridge calculator kit at £24.95 + £2.50 VAT (Total: £27.45)		
<input type="checkbox"/> a Sinclair Cambridge calculator ready built at £29.95 + £3.00 VAT (Total: £32.95)	Address	
*I enclose cheque for £ made out to Sinclair Radionics Ltd, and crossed.		
*Please debit my *Barclaycard/Access account. Account number		
*Delete as required.		
		PLEASE PRINT

Because of the limitations of the 25 to 40 watt iron, most workshops have at least one or two other types and sizes of iron available. For larger jobs, an iron with a rating of 60 to 100 watts is required. These irons are similar to their smaller counterparts in general construction and appearance except for the size and element rating. The bit may be square instead of the usual pencil-type. As only occasional use would be expected, the iron would not normally be left on for long periods, so there would be no overheating problems.

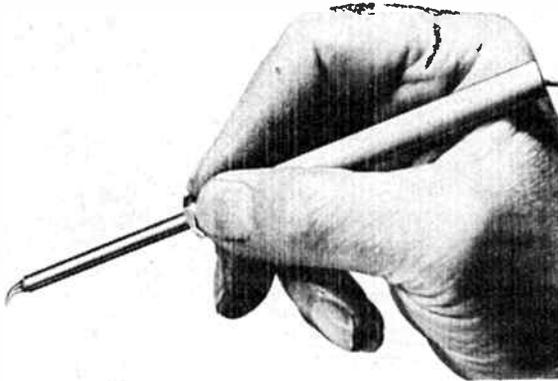

Work on integrated circuits requires a very small iron such as the Micro Soldering Pencil, shown here.

For the smaller and more intricate jobs, there are irons that are little bigger than pencils with element ratings of 10 to 15 watts. These are ideal for some of the tiny printed circuits that are now encountered and for the wiring of I.C.'s where the connections are close and damage could be caused by excessive heat. Heat output is obviously limited and many larger jobs could not be tackled. The element wire for these mains-operated low-wattage irons is necessarily very fine and so they are less reliable than the higher-rated ones. They should not be run continuously but only when a particular job calls for their use. Because of their small bit size, they are usually quite fast in warming up. This and their size also makes them suitable for outside service work.

LOW VOLTAGE IRONS

Another type which has achieved a measure of popularity is the low-voltage iron. While these can be run from a low-voltage source such as a car battery, the more common method is to operate them from a mains transformer. The main feature is a very quick heating time, just a matter of seconds, and a rapid heat-recovery time. This means that the iron can be used for outside service work where delays waiting for a conventional iron to warm up are thus eliminated.

One type of low-voltage iron is constructed very similarly to the normal iron and fed from a separate transformer, which also serves as an iron-rest. Other types have the transformer built-in, either over the top of a pistol-grip handle, or in one make, actually inside the handle. With these the element is also the bit, consisting of a loop of wire connected across the transformer secondary, Fig. 1.

In either of these low-voltage types, the bit can very quickly become overheated, even when being used on large areas, so a switch is incorporated in the iron so that the operator can keep switching it on and off and thereby maintain the tool at about the

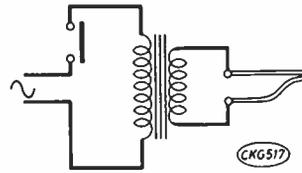


Fig. 1: Circuit of a transformer iron with element/bit consisting of a wire loop.

right temperature. In one make that uses a separate transformer, a thumb ring is used as a switch on the handle; while most of the built-in types, being pistol-like in construction, use a trigger switch.

This need for constant switching can be a drawback, especially if the switches are stiff as some are, and need considerable finger pressure. The danger of overheating due to switching on for too long can also be a hazard for transistors and other semiconductor devices.

A yet further drawback of the built-in transformer type is their weight. This is of little consequence for occasional use, but when used continuously, as in the professional workshop, they can be very tiring. The wire-loop bits are not very durable and need frequent replacement; while owing to their flexibility they cannot be used to unpick joints as can the conventional bit.



A pistol-grip soldering gun with integral transformer. The Welwyn KL3000.

The separate transformer type of low-voltage iron is therefore the more convenient, but for outside work the built-in type is probably the best. Neither though, really is as suitable as the mains-voltage type for workshop use.

CONTROLLED TEMPERATURE

Of recent years we have seen several thermostatically controlled irons which overcome some of the snags inherent with the uncontrolled types, whether high or low voltage. One, rather ingeniously, uses the Curie effect of iron. Iron, when it is heated beyond a certain point loses its magnetic properties. A small

iron disc is fixed to the base of the soldering-iron bit and this has an attraction for a bar magnet which holds a switch in the 'on' position by means of a push-rod, Fig. 2. When the iron temperature reaches the Curie point of the disc, it loses its attraction, the magnet is released and the switch is opened. As the temperature drops to below the Curie point, attraction is re-established and the switch returns to the 'on' position.

Each bit has its own iron disc, which can be made with different Curie points, hence with its own temperature setting. This particular iron is a low voltage model and is operated from a separate transformer. It has a very rapid warm-up time and good heat recovery, but, because of being thermostatically controlled, does not overheat nor need switching attention by the operator. The barrel is a little short though, for some types of work.

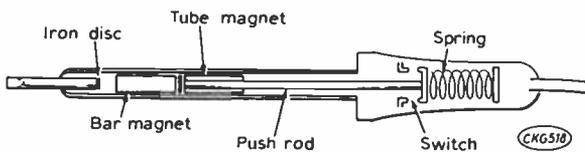


Fig. 2: Mechanism of a heat-controlled iron using the Curie effect.

Another thermostat iron is called the 'Litestat.' This is a mains-operated instrument, hence it is not encumbered with a transformer, either built-in or attached by lead. It has a 70 watt rating, but is only little larger than the average 25 to 40 watt instrument, the thermostat preventing it overheating. As with other thermostat irons, when there is a heavy outflow of heat from the bit due to working on a large heat conductive area, any loss of temperature is compensated by the switch remaining on longer than usual, and the larger element quickly supplies the extra heat volume. Thus we have the best of both worlds, a moderate sized iron that will handle reasonably small jobs (quite small if the extra-small bit is used) and will also tackle the big ones. Although the occasional user will probably get on quite well with a normal uncontrolled iron, the advantages of the thermostat control really make this type of iron a 'must' for professional workshops.

These then are the basic types of soldering instrument and their respective features. Within each category there are many makes and models and engineers and hobbyists alike often have a particular favourite that handles well and seems to produce good work for them.

SOLDERING BITS

Bits are available in several types. There are of course the various shapes and sizes that are produced for specific applications, most irons having a number of alternative bits obtainable as extras. There are though, differences in material. The most common is copper, which because of its high heat conduction is the best material (excluding precious metals) for the purpose. When clean it can be tinned quickly and easily, another great advantage. A disadvantage with copper bits is their deterioration with use. Prolonged periods of operation at high temperatures causes oxidization and flaking of the metal. In

addition, at the bit face where the solder is melted, cavities begin to form due to the chemical affinity of solder for copper, which absorbs it each time the bit is used.


Little can be done to stop the flaking other than running the iron at a lower temperature during standby periods, but the cavities can be almost eliminated by using the Savbit solder developed by Multicore. This contains minute traces of copper which satisfies the affinity of the solder without it taking more from the bit.

Other types of bit are made from alloys, or are nickel or chromium plated to achieve longer life. One method used by some manufacturers is to clad the copper bit with iron which is harder and more durable than copper, yet has the copper core for its thermal properties. A disadvantage with all these bits is that they cannot be filed without ruining them, thus once the plating or cladding has gone the bit must be discarded, whereas a copper bit can be filed flat at its face many times before filing and flaking reduces the size to inoperative proportions.

The superior thermal qualities and ease of tinning make the copper bit still the favourite, especially since its life can be prolonged with special solders.

USING THE IRON

Now just a point or two on using the iron. It is surprising the number of people who are technically well qualified, professional engineers included, who cannot seem to produce a good soldered joint. It is very important to do so, as all sorts of faults can arise from poor soldering. It is noteworthy that all candidates for the RTEB servicing exams had to undergo soldering tests and failure led to automatic disqualification for the whole of the practical and theoretical examinations.

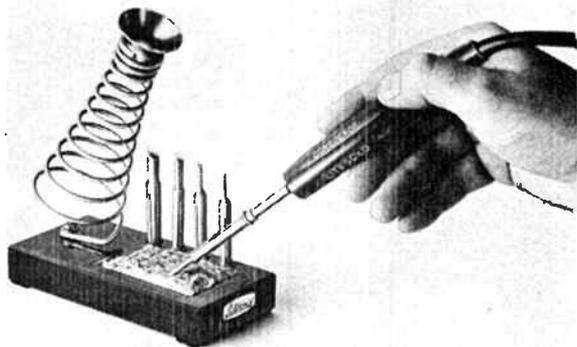

Litesold Conqueror iron and stand with bit-cleaning sponge and range of interchangeable bits.

There is nothing really difficult in making a good joint, just observing a few straightforward rules. The first one is to make sure that both surfaces are clean. In the case of wires, this can be done by pulling the wire a couple of times through the blades of a pair of side-cutters, as though one were stripping insulation. Terminals and tags can be scraped with a screwdriver blade. In most cases wires and terminals will be already tinned, but do not rely too much on it. Next both surfaces should be tinned. This is done by applying the iron to the surface for a few seconds, and then introducing the solder to bit and

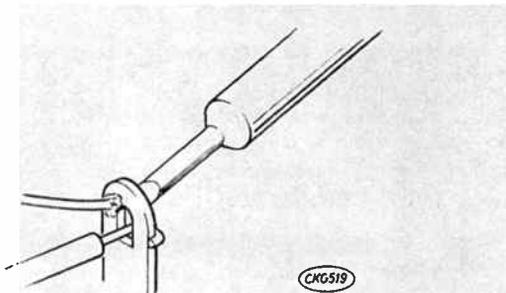


Fig. 3: The iron should heat the whole joint—not just the solder.

surface so that it runs easily over it, Fig. 3. If the solder is thick and slow to run, the bit temperature is too low, either because the iron has not been switched on long enough, or the iron is too small for the work. The solder may not run over the surface readily at first because insufficient heat has been transferred from the bit, and it is just not hot enough to melt the solder. This could be due to poor contact between bit and surface, but a little solder introduced at the junction of the two, will give a good thermal conduction, and the surface should then quickly attain sufficient temperature to itself melt solder when applied.

When both surfaces have been thus tinned, they are brought together in mechanical contact, and the iron applied again to both. More solder is then introduced so that it runs freely over both surfaces,

then the iron is withdrawn. Do not move the work until the solder has solidified otherwise a weak joint will result; this will take only a second or two. Where possible the joint should be mechanically sound before soldering. No external flux should be used as these are often corrosive and will give trouble in the future. Sufficient of the correct type of flux is contained in the cores of solders intended for electronic wiring, to do the job.

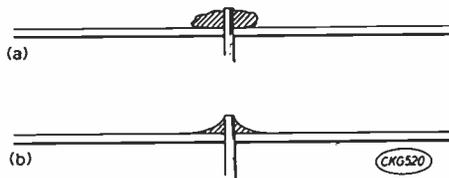


Fig. 4: (a) A 'dry' joint, showing the blob of solder due to insufficient heat or dirty surfaces. (b) A good joint, showing smooth flow of solder over joined surfaces.

Do not use too much solder as this is not only unnecessary but could form a short to adjacent terminals. In appearance, the joint should be bright and smooth. A lumpy or pitted appearance shows the solder was not hot enough. It should also appear as a 'mound' rather than a blob. The illustration Fig. 4 shows what is meant by this. If the solder surface comes down and curls under as shown, it has not taken to the surface and we have a 'dry' joint. By observation of these points and a little practice, perfect joints can be made every time. ■

LETTERS—continued from page 742

Value for money

I greatly appreciated the article on 'Going Back' as it is full of nostalgia. I have taken *P.W.* off and on since the early beginnings, but only since 1967 have I bought it every month and I only started then because a free record of audio faults was given away, but on reading the articles on transistorised equipment, and particularly details of a transistor SW receiver by F. G. Rayer. I was astonished at the transformation in building techniques (being brought up on $\frac{3}{8}$ " thick breadboards and $\frac{1}{16}$ " dia. connecting wire!) and plunged up to the neck in transistor circuits and have been building them from *P.W.* projects ever since.

Though the price of *P.W.* has greatly increased, the contents have kept in step and I think it is still good value for money. It is improving all the time, as reference back to only a few years ago will show, and even in the last few months there have

been detailed improvements, such as better layout and the contents page being put on the first page. Long may you continue!

Incidentally, radio parts seem to be one of the few things which have not greatly increased in price, and some, like transistors and i.c.s, have actually gone down.—R. A. Read (*Salisbury*).

A Fly in the Ointment?

Do any readers know how to build an electronic fly-catcher? We are driven crazy with flies in the summer and we are sure that it is the sheep that bring them in.

I was born in the UK and lived many years in Africa but the flies were never as bad as here. I have taken *P.W.* for over 20 years now but have not seen any details of fly catchers. Also, we are a bit lost out here for getting components especially as we can only get a £2 British P.O. here on demand at the Post Office.—J. S. Skeels (*One Tree Point, Rukaka, Northland, New Zealand*).

Short Wave Converter

I have built the Radio Nederland converter, *Practical Wireless*, September 1973, and am very pleased with the results, however, I should like to point out an error in publication which would result in disappointment to those to quote your preamble—"with little experience in electronics."

Reference page 409 figure 1 circuit diagram oscillator Tr2 AF 124 and page 410 drawing AM0022. Note the emitter and base connections are shown reversed so there could be no conduction in the collector circuit due to reverse polarity at the base.

As a note of interest I used Wearite P coils either PA4 or PHF4 which very nearly approximate the coil data given for L1 and L2, a similar coil was slightly modified to make up L3. A PHF6 coil tuned by a 200pF silver mica in parallel with a 250pF trimmer was used for L4. The unit is used with a BUSH TR130 receiver tuned to the extreme h.f. end of the m.w. band.—A. J. Birkinshaw (Telford, TF2 6RA).

GOING QUADRAPHONIC

PW

Q4 PROJECT

PART 3 D. BOLLEN

- QS recordings
- SQ recordings
- Discrete CD-4 recordings
- SURROUND SOUND

THE article last month gave circuit descriptions of single and multi-system matrix decoders based on two circuit modules, Units A and B. There now follows constructional details of these two units, and of the additional units and components needed to build a multi-system decoder with infinitely variable front and back separation.

Readers are reminded that they will require, in addition to the decoder, a stereo outfit plus a pair of back amplifiers and speakers for quadrasonic reproduction from discs and tapes.



Unit A construction

Unit A is assembled on a piece of 0.1in. pitch Veroboard 0.9in. wide by 4in. long, see Fig. 16. Begin by making breaks in the copper strips, where shown, with a spot face cutter, and then insert and solder the terminal pins.

During assembly, it is important to ensure that the transistors are not overheated as this could have a detrimental effect on noise performance. A clip made of aluminium sheet should serve to conduct away heat when placed around the transistor can during soldering. Constructors who are not accus-

tomed to 0.1in. Veroboard should also make sure that solder blobs do not bridge between the copper strips. It is a good idea to run a sharp knife blade along the gaps between strips to remove excess flux and any particles of solder. When inserting capacitors in the unit A circuit board, check that the polarity is as shown in Fig. 16.

Note: all exposed wiring must be sleeved


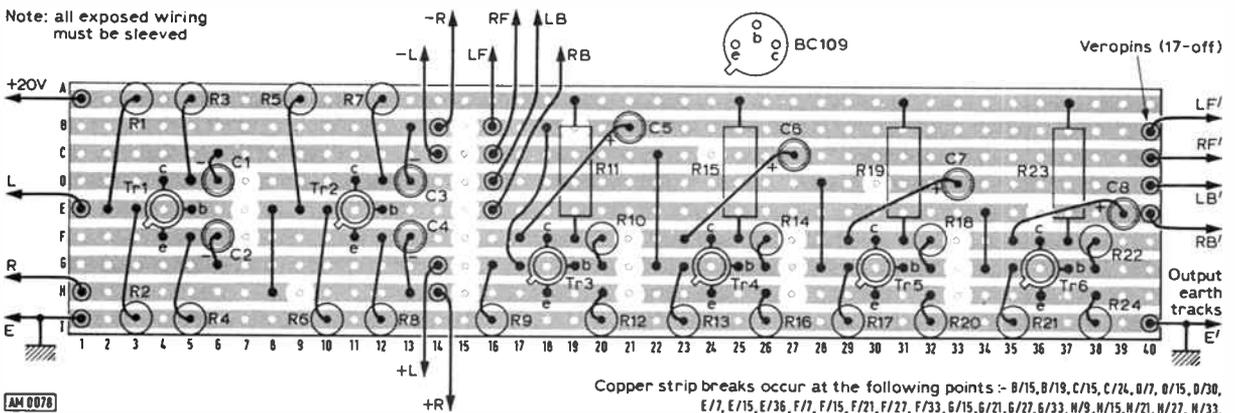


Fig. 16: Component layout of unit A circuit board. Note breaks in copper strips.


Note: all exposed wiring must be sleeved

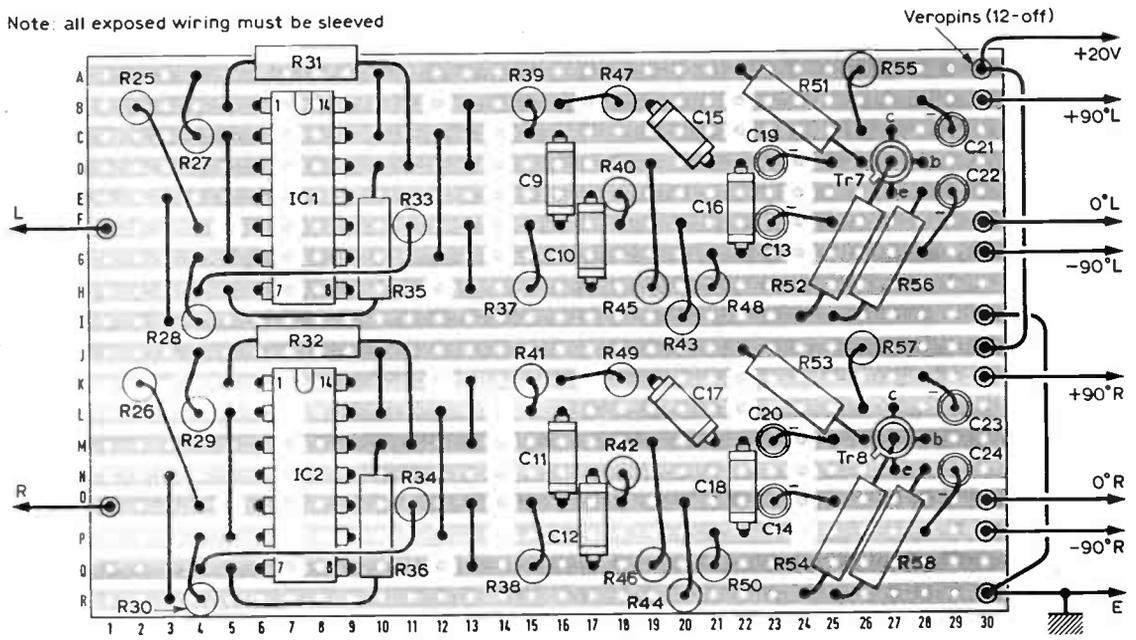

AM 0079

Copper strip breaks occur at the following points:-
 B/7, B/12, B/17, B/22, C/7, C/14, C/22, D/7, D/14, D/24, E/7, E/14, E/24, F/5, F/17, F/14, F/24, G/7, G/14, G/24, H/7, H/12, K/7, K/12, K/17, K/22, L/7, L/14, L/22, M/7, M/14, M/24, N/7, N/14, N/24, O/5, O/7, O/14, O/24, P/7, P/14, P/24, Q/7, Q/12.

Fig. 17. Component layout of unit B circuit board. Note breaks in copper strips.

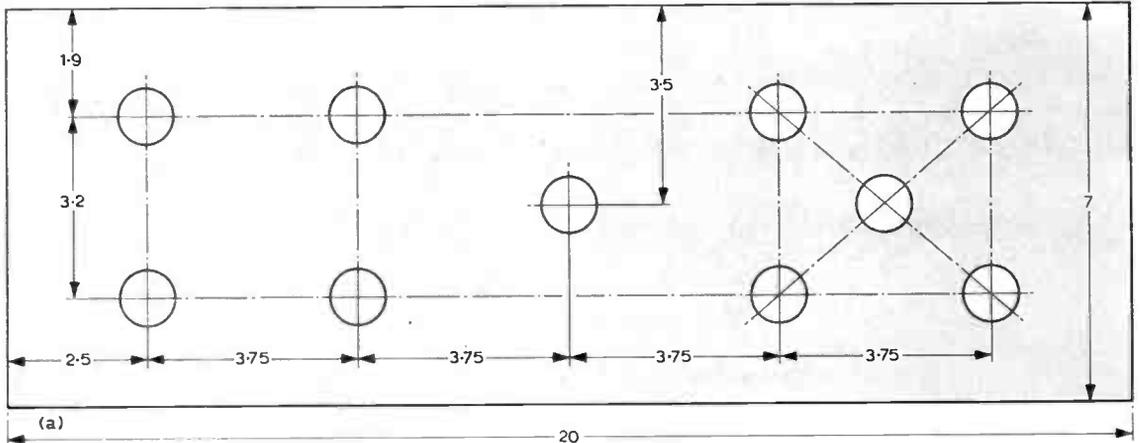

AM 0081

All dimensions in cm. Drill all holes 1cm diameter

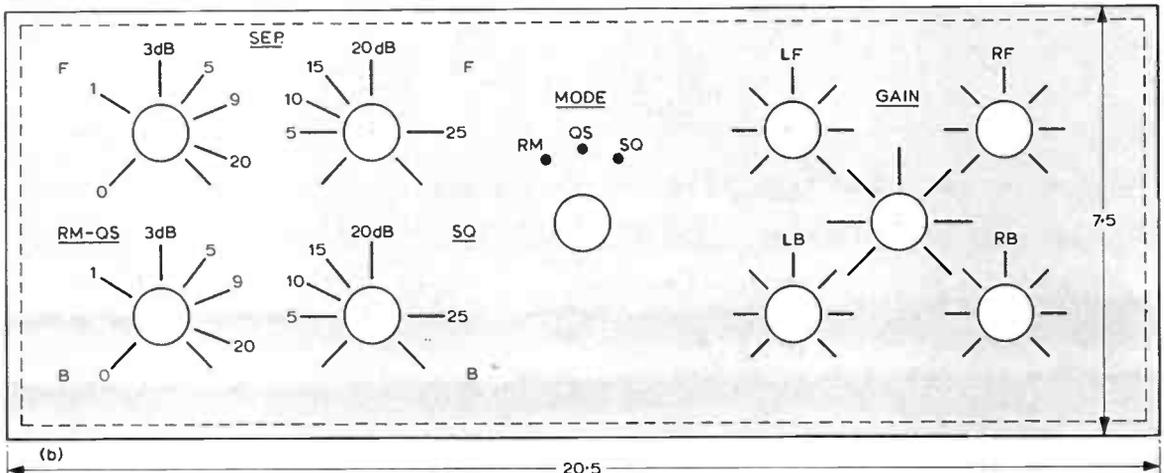


Fig. 18(a): Drilling details of front of chassis tray. Fig. 18(b): Front panel layout.

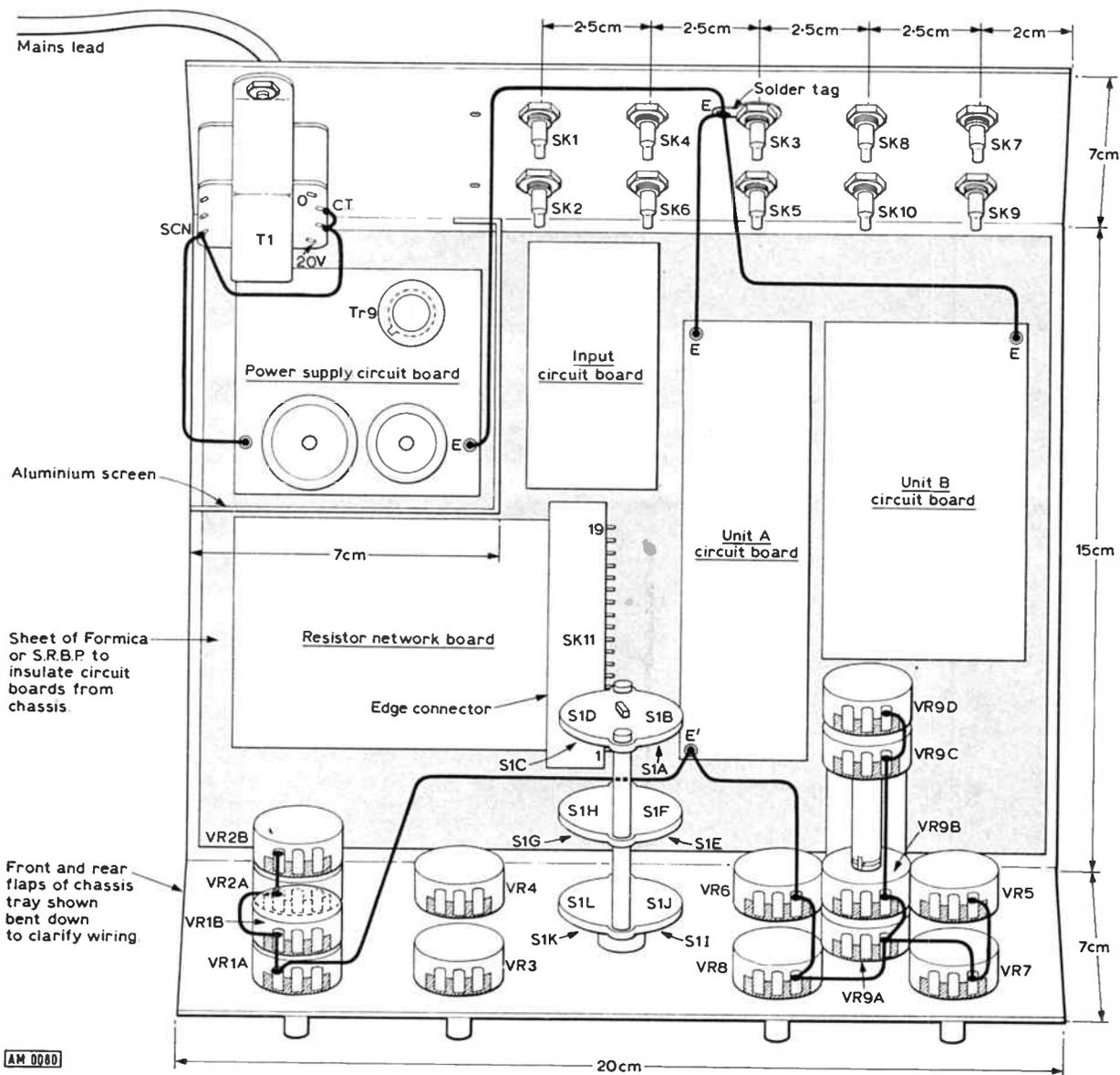


Fig. 19: Multi-system decoder layout showing earth wiring.

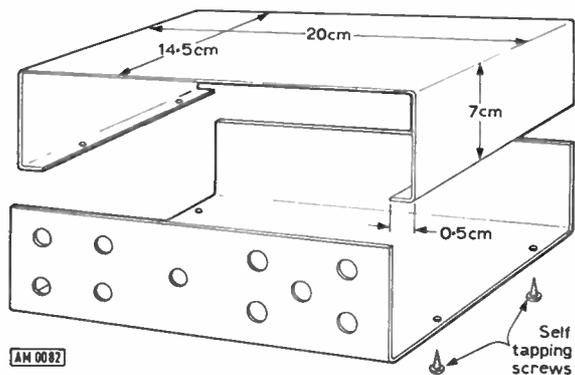


Fig. 20: Dimensions and fixing details of the chassis cover.

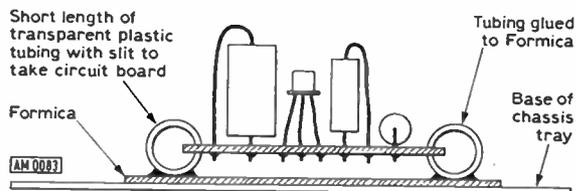


Fig. 21: A method of securing the circuit boards.

Unit B construction

A piece of 0.1in. pitch Veroboard 1.8in. wide by 3in. long is employed for unit B, and the layout is shown in Fig. 17. Left and right hand channels are identical and are arranged one above the other on the circuit board.

Make breaks in the copper strips according to the diagram of Fig. 17 and insert and solder all terminal pins. Commence with the ICs, leaving pins 3, 5, 8, 11, and 14 unsoldered, and then position and solder the remaining components. Use a heat clip on Tr7 and Tr8 and ensure that the polarity of the electrolytic capacitors is correct.

Checking units A and B

As a preliminary check, wire the earth and +20V terminal pins of unit A circuit board to an 18V battery (two PP9s in series) and with a testmeter measure the voltages between the earth terminal and the transistor cans. Tr1 and Tr2 should show a voltage of about 14V, and Tr3-Tr6 a voltage of 9V. If there is a serious discrepancy, look for a short circuit between the copper strips on the underside of the circuit board, or an error in component positioning.

To check unit B, connect the 18V battery to earth and +20V terminals and measure the voltage at IC1 and IC2 pins 10 and 12, which should be at 9V relative to the earth terminal pins. The can voltage of Tr7 and Tr8 will be about 14V if there are no constructional faults.

Small piece of 16swg aluminium to engage in slot at the back of the front pots, and slot in the spindle.


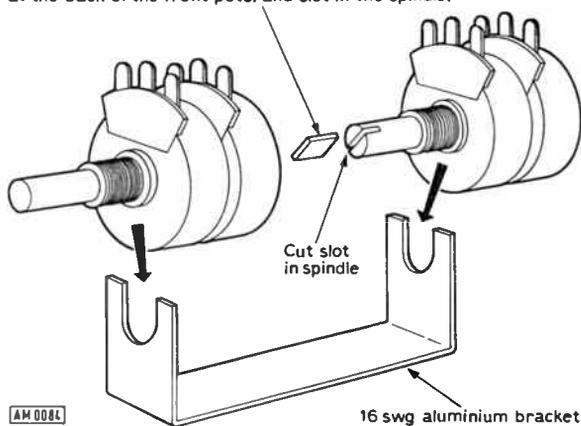


Fig. 22: VR9 assembly utilising two dual-gang potentiometers.

If the user intends to experiment with a single-system decoder, units A and B can be employed with an 18V battery, or the power supply of Fig. 15, with 22kΩ balance controls (VR5-VR8 Fig. 14) wired to the LF, RF, LB, and RB outputs of unit A. It is advisable to connect a 1000μF 25V electrolytic capacitor across the supply rails when operating units A and B from a battery.

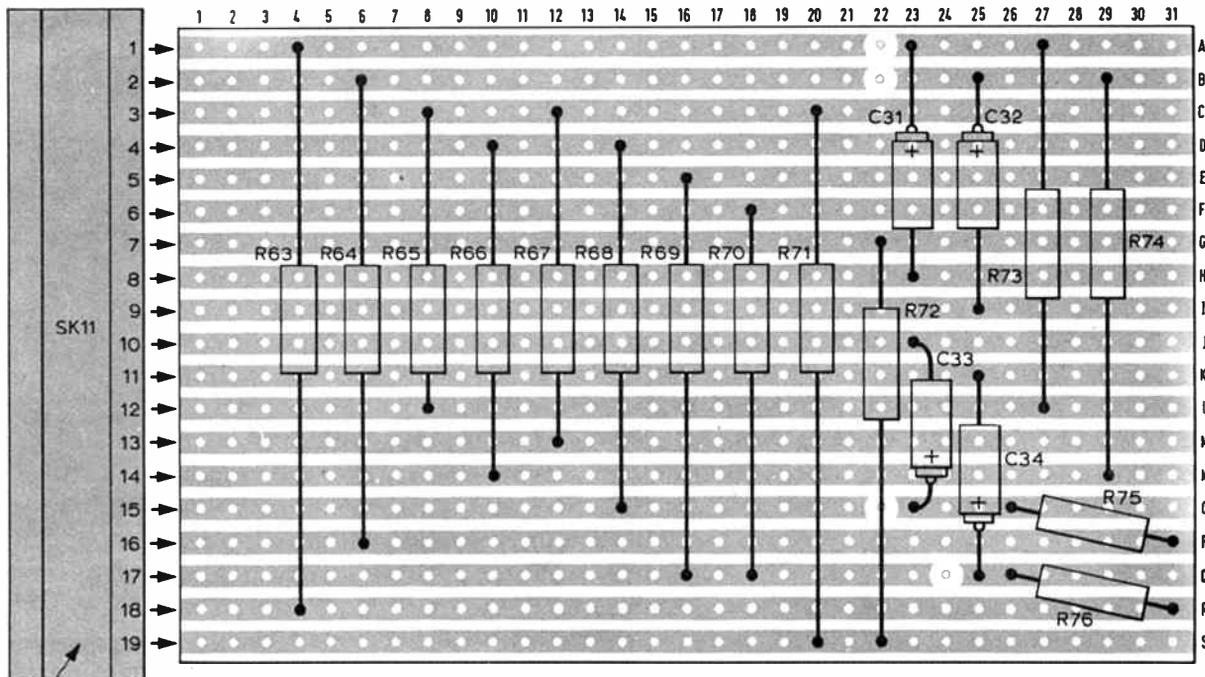Where an oscilloscope with X-Y facilities is available, unit B can be tested for 90° phase shifting by injecting a signal of 2kHz into the left input, with the X input of the scope linked to the 0°L output, and the Y scope input connected to each of the 90°L outputs in turn. The resulting display should be a near perfect circular trace. Repeat the test for the right hand channel.



Edge connector

AM 0085

Copper strip breaks occur at the following points:- Q/24, O/22, B/22, A/22.

Fig. 23: Component layout of resistor network board.

THE SPECIALISTS IN QUADRAPHONIC KITS

AVAILABLE NOW!

THE COMPREHENSIVE KIT FOR THE

P.W. Q4 PROJECT

SEND NOW FOR FULL DETAILS AND PRICES—SEE COUPON BELOW

FULLY COMPREHENSIVE HOME CONSTRUCTOR KITS AS SPECIFIED
IN THE PRACTICAL ELECTRONICS

P.E. RONDO

COMPLETE QUADRAPHONIC HI-FI SYSTEM

CBS SQ (TM CBS INC.) MATRIX DECODER. COMPLETE KIT	£8.00 Post Free + 80p V.A.T. Inc. CBS Licence Fee
PRE AMPLIFIER BOARD. COMPLETE KIT	£3.00 Post Free + 30p V.A.T.
MASTER VOL./TONE/4 CH. BALANCE BOARD. COMPLETE KIT	£8.50 Post Free + 85p V.A.T.
POWER AMP. BOARD & HEAT SINKS (STEREO PAIR).	
COMPLETE KIT	£7.50 Post Free + 75p V.A.T.
POWER SUPPLY BOARD. COMPLETE KIT	£5.00 Post Free + 50p V.A.T.
MAIN SMOOTHING CAPACITORS	£0.75 Post Free + 7p V.A.T.
MAINS TRANSFORMER. COMPLETE	£6.25 Post Free + 62p V.A.T.
CHASSIS. PUNCHED & DRILLED	£2.25 Post Free + 22p V.A.T.

ALL KITS ARE FULLY TO SPECIFICATION AND COMPLETE IN EVERY
DETAIL. TRADE ENQUIRIES WELCOME

STUDIO ELECTRONICS

P.O. BOX 18,
HARLOW, ESSEX, CM18 6SH

Please send me:

CBS SQ DECODER
PRE AMPLIFIER BOARD
MASTER VOL. BOARD
POWER AMP. BOARD
POWER SUPPLY BOARD
SMOOTHING CAPACITORS
MAINS TRANSFORMER
CHASSIS
P.W. Q4 PROJECT Full Details

Block capitals please

NAME

ADDRESS

..... P.W.12

Please tick box

MONEY ENCLOSED

£

CHEQUE/P.O./
MONEY ORDER

ESSENTIAL BOOKS FOR RADIO AMATEURS

1974 EDITION RSGB AMATEUR RADIO CALL BOOK

Lists holders of G, GC, GD, GI, GM, GW and EI call signs; clubs and societies affiliated to RSGB, and much useful operating information.

A larger completely revised edition produced by a new system and incorporating amendments and additions notified by the MPT up to August 1973.

144 pages

Price 75p post paid

RADIO AMATEURS' EXAMINATION MANUAL

by G. L. Benbow, G3HB

The standard book for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination.

Fully up-to-date to meet the present examination syllabus requirements.

96 pages

Price 90p post paid

A GUIDE TO AMATEUR RADIO

by Pat Hawker, G3VA

This extensively revised 15th edition is an indispensable aid to all who want to know more about amateur radio.

Specially designed to assist the newcomer to the hobby.

96 pages

Price 90p post paid

AMATEUR RADIO AWARDS

by C. R. Emary, G5GH

Lists all the world's major awards from national societies and how to obtain them.

Includes reproductions of certificates and maps, and operating information.

Loose-leaf binding allows insertion of amendment pages at a later date.

194 pages

Price £1.40 post paid

These are just four of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.

RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688



4-STATION INTERCOM



£8.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & P. 17p

MAINS INTERCOM NEW MODEL
No batteries no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control. Price £18.95 P. & P. 50p

INTERCOM/BABY ALARM



OUR PRICE ONLY £4.85

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. De-Luxe Model complete with 6ft. connecting wire. Complete with Battery. P. & P. 35p

Transistor TELEPHONE AMPLIFIER



£4.25

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (FW.12)
169 KENSINGTON HIGH STREET, LONDON, W.8.

0442:62757

THE NUMBER FOR CLOCKS, LSI CHIPS, KITS & DISPLAYS.

Choose a combination from the tables below. get out your Access card and ring the above number, or send us a cheque, MO, PO, etc.

BYWOOD FOR ADVICE, SERVICE and of course COMPONENTS.

Clock Code	12/24 Hour	4/6 Digit BCD out	7seg out	MPX'd	Hz out	AM/PM	Alarm	Date	Snooze	Sleep	Ph Ont	INTERFACES					Drive mA	Interface Key	Availability	PRICE		
												TL380	DL34	DL707	DL62	DG12					TA8055	Drive Volts
MM5311	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	28	D	D	T	T	-	-	11-49	8	Stock	11.50
MM5314	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	Y	24	D	D	T	T	-	-	11-49	8	8 Days	11.00
MM5316	Y	4	Y	Y	Y	Y	Y	Y	Y	Y	Y	40	-	-	-	D	K	8-29	4	Stock	16.00	
5017AA	Y	6	Y	Y	Y	Y	Y	Y	Y	Y	Y	24	T	T	T	T	K	-	11-18	16	Stock	14.00
5017BB	Y	6	Y	Y	Y	Y	Y	Y	Y	Y	Y	24	T	T	T	T	K	-	11-18	16	Ltd	14.00
CT 7001	Y	6	Y	Y	Y	Y	Y	Y	Y	Y	Y	28	T	T	T	T	D	-	11-18	16	Feb74	18.00

Display Code	Type	Pack	Digs	Digit Size	Drive Req.	Common	Digit Cost £	Unit Cost £
TIL360	LED	16 DIL	6	0.1 ins	2v 10mA	Cathode	2.50	15.00
DL707	LED	14 -	1	0.3 ins	3v 30mA	Anode	2.00	2.00
DL34	LED	14 -	4	0.1 ins	5v 10mA	Cathode	2.50	10.00
DL62	LED	16 -	1	0.6 ins	6v 30mA	Anode	6.50	6.50
DG12H	Phosphor Diode	TUBE	1	12.5mm	25v 1mA	Htr Anode	2.00	2.00
TA8055	Liq.Crys.	EDGE	4	0.6ins	30v125uA (A.C.)	N/A	3.25	13.00

Sockets - 24 or 28pin 115p, 40pin 135p. Case - Warm red Perspex 250p.

Kits 5017AA or BB + PCB + socket + 4 DG12s + instructions £24.
MM5316 + " + " + TA8055 + " £32.

CLOCK DATA SHEETS -SAE. ADVICE - PHONE 0442-62757 CATALOGUE 15p
POST & PACKING - 10p. OVERSEAS (AIRMAIL) 50p. VAT - ALL PRICES EXCLUDE VAT.
PAYMENT C.W.O. or ACCOUNT. ACCESS. ORDERS & PAYMENT BY PHONE ACCEPTED.
QUANTITY DISCOUNTS ON MOST ITEMS - STATE REQUIREMENTS FOR QUOTATION.

BYWOOD

Bywood Electronics
181 Ebbens Road
Hemel Hempstead
HP3 9RDA

Multi-system decoder construction

Fig. 19 shows the layout of a multi-system decoder based on the circuit of Fig. 14. Additional circuit boards serve to accommodate the resistor network, input capacitors and resistors, and power supply components; these will be described later.

A start can be made by making up the chassis tray from 16s.w.g. aluminium sheet, to the measurements shown in Fig. 19. Allow 7cm of space for the power supply, and mark out and drill the rear of the chassis tray to take sockets SK1-SK10. Next, mark out and drill the holes to mount transformer T1, the power supply screen, and mains lead grommet.

Drilling details for the front of the chassis tray are given in Fig. 18a, and Fig. 18b shows a front panel made of 20.5cm by 7.5cm brushed aluminium or white Formica, which is drilled to match the holes in the chassis tray. The dimensions and fixing details of the chassis cover are shown in Fig. 20.

Glue a sheet of Formica or s.r.b.p. inside the base of the chassis tray to insulate the circuit boards from the chassis; this should measure 19cm by 14.5cm. A method of securing the circuit boards is shown in Fig. 21.

Make up switch S1 from three 4-pole 3-way wafers, with a three spacer gap between wafers. Mount the assembled switch on the front of the chassis tray, along with controls VR1-VR8.

In the absence of a four-gang component for VR9, this can be made up from two dual-gang potentiometers, as shown in Fig. 22. A small piece of sheet aluminium engages with the spindle slot at the rear of the front pair of pots, and with a slot in the

spindle of the back pots. To align VR9, set the front pots to mid-track and measure the resistance between a slider and the earthed end of its track. Rotate the body of the rear pots to give a similar resistance reading on a rear pot slider and its track end, and then tighten the mounting nuts. VR9 can now be mounted on the chassis.

Resistor network board

The resistor network components are assembled on a piece of 0.1in. pitch Veroboard 1.9in. wide by 3.1in. long, and this is designed to plug into a 19-way edge connector (SK11) to facilitate easy modification of matrix parameters. The layout of the resistor network board is shown in Fig. 23.


A suitable edge connector, such as the RS Components 0.1in. 25-way, may be cut down to 19 ways with a small saw. When the resistor network board is completed it can be inserted in SK11, and the latter glued to the insulating board on the chassis tray.

Input circuit board

Fig. 24 shows the input circuit board with components mounted on 0.1in. Veroboard, which measures 2in. wide by 1.2in. long.

In Fig. 14 (last month) the lower unit board should have been designated unit B. We regret, that due to pressure on space, final constructional details, wiring and setting up, have had to be held over until next month.

TO BE CONTINUED

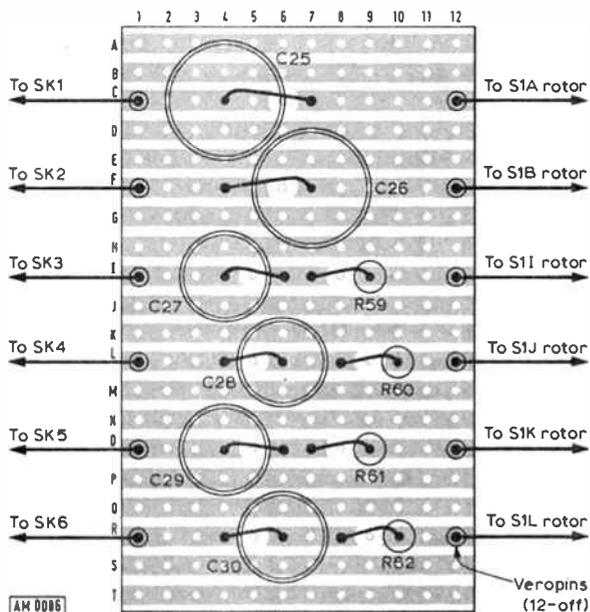

Copper strip breaks occur at the following points:- C/6, F/6, I/5, I/8, L/5, L/9, O/5, O/8, R/5, R/9.

Fig. 24: Component layout of Input circuit board.

COMING SOON
Q4 MATRIX
MATE

For any quadrasonic matrix decoding system.

Watch for further details!

A series of simple transistor projects, using not more than twenty components.

THIS project can be used as quite a useful gadget for signalling between the house and a shed or to illuminate signs outside an office door. Signals are produced by two lamps either, or both, of which can be switched on and off. This does not, in itself, sound very clever but the circuit to be described enables one to do this with a single pair of wires. Thus, over two wires one can display three separate codes on the two lamps.

Circuit

The trick is to make use of positive going half cycles of the mains supply to switch on one lamp. In Fig.1 D6 is forward biased for positive going cycles and LP2 will light but when SW2 is switched to the centre position the polarity of these half cycles is reversed and D5 becomes forward biased, turning on LP1 (D6 becomes reverse biased and LP2 goes out).


The third code, having both lamps on at the same time, is obtained by turning SW2 into the third position which applies a.c. to the signal wire pair direct from the transformer. LP1 and LP2 will now each light up, LP2 on positive and LP1 on negative half cycles.

Variations

There are many variations to this circuit, and relays could be used instead of the lamps. Provided limiting resistors were inserted into the lines and the voltage reduced to below the reverse break-down level, light emitting diodes could be used instead of the lamps, diodes D5 and D6 being omitted. For those who do not wish to bother with a.c. and a transformer one can still transmit two codes down the pair of wires by dispensing with the control unit. All that is needed in its place is a suitable battery and a reversing switch on the control end of the signal wires. One polarity will turn on one of the lamps, reverse the polarity of the supply and the other lamp will light. Apart from the diodes most of the components can be


salvaged from old equipment. Any 6.3V transformer will do for T1 and probably the best source is an old valved radio.

Fig. 2 shows a suggested layout for the unit, on a metal or insulating material panel, which can be the lid of a box.

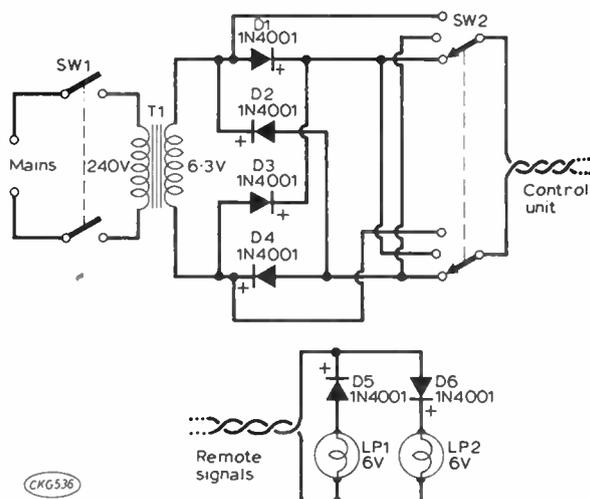


▲ Fig. 1. Circuits of Control Unit and Remote Signals

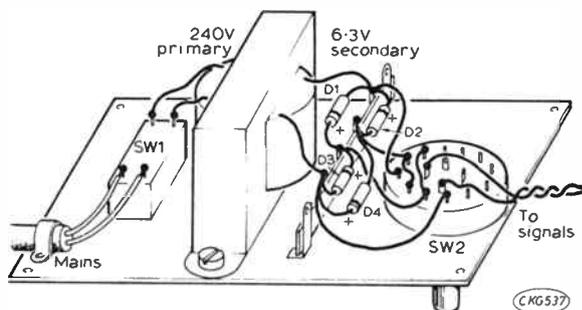▼ Fig. 2. Author's suggested layout for the two units.



★ components list

D1-6	Diodes 1N4001
LP1-2	6V Lamps
SW1	2 pole mains switch
SW2	2 pole 3 way wafer switch
T1	Mains transformer, 240/6.3V Mounting box, tag strip, etc.

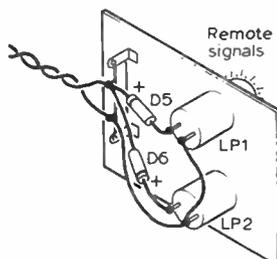



BROADCAST BANDS

SHORT WAVE DX

by MALCOLM CONNAH

AS many of you will know, propagation conditions vary according to the time of day, the time of year and the position in the 11-year sunspot cycle; as well as other minor factors. This means that, at any particular time, there is an optimum band for reception from any part of the world.

Forecasting these optimum bands is a relatively simple matter once one has collected all the necessary information. The following forecast is for reception in Western Europe and is listed by transmitter site.

North America During the late afternoon the most suitable band will be 25 metres, by 1900 GMT this will have changed to 19 metres but will return to 25 metres by 2300. During the early hours of the morning the most useful frequency will drop still further reaching 31 metres by 0300.

Central & South America The optimum frequency during the late afternoon will be 16 metres and this will drop gradually during the evening to be 19 metres at 1900; 25 metres at 2300 and 49 & 60 metres at 0300.

Middle East The late afternoon finds 19 metres as the best band dropping to 31 metres at 1900 and 41 metres at 2300.

Far East & Australasia Reception for this area will be much the same as the Middle East except that the best band will not drop below 31 metres.

Africa Late afternoon reception will be best on 16 metres dropping to 25 metres at 2000 and 31 metres at 2300.

DX News

COSTA RICA: Radio Capital de Costa Rica has been heard on 4832kHz at 0130 GMT. Reception is poor due to the low power of 1 kW.

ECUADOR: Radio Nacional del Ecuador has been noted with a programme of news and Latin-American music on 6170kHz at 0500 GMT.

EL SALVADOR: La Voz del Comercio, Colonial Sta. Lucia, Santa Ana, is asking for reception reports on 9545kHz. The best time for reception being 1600 GMT.

MEXICO: XERMX has been heard in Spanish on 15195kHz at 0330 GMT, this is a change from the usual frequency of 15125kHz.

TUNISIA: Radio Tunis has been noted on 15226 kHz at 2345 GMT and at 0910 GMT on 11970kHz. (Some of the above items by courtesy of Sweden calling DXers.)

Readers' Logs

John D. Porter of Bakewell (No jokes about Bakewell tarts—please) in Derbyshire has nine transistors and a few other components built into his superhet receiver. This, in combination with a 45 metre long-wire and some attention to the higher frequency bands, produced the following results:

- 11710 R. *Nacional d'España* at 0005.
- 15110 R. *Grenada, Windward Is.*, English at 2100.
- 15150 R. *Pyongyang, N. Korea* noted at 2030.
- 15375 *HCJB, Quito, Ecuador* at 2210.
- 15415 R. *Kuwait* in English at 1850.
- 15450 R. *Nacional de Brasilia* in English at 2355.
- 17820 R. *Canada Int.*, in Polish at 1540.
- 17885 *HCJB, Quito, Ecuador* noted at 2250.

Andrew Brown of Maidenhead in Berkshire is fourteen years of age so both his National HRO and R107 receivers are older than he is. The connection of a 10 metre long-wire antenna enabled the following stations to penetrate Andrew's shack:

- 7275 *RAI, Italy* in English at 1936.
- 9005 *Tehran, Iran* in English at 2000.
- 9560 R. *Jordan, Amman* in English at 1600.
- 9655 R. *Damascus, Syria* in English at 1930.
- 9745 R. *Baghdad, Iraq* in English at 1930.
- 11765 *Radio Australia* noted at 0710.
- 15165 R. *Denmark* in Danish at 0945.
- 15325 R. *Pakistan, Karachi* in English at 1530.
- 15520 R. *Bangladesh* in English at 1715.
- 17825 *NHK, Japan* in English at 0800.
- 21520 *RSA, South Africa* noted at 0755.
- 21655 R. *Norway, Oslo* in English at 2000.

David Thornley of Dukinfield, Cheshire has a Trio 9R59DS receiver and a Joystick antenna with ATU; which enabled him to hear:

- 7125 R. *Peking* in English at 0120.
- 9020 R. *Iran* in English at 2000.
- 9610 R. *Kiev* in English at 0030.
- 11672 R. *Pakistan* with news in English at 2000.
- 11880 *Voice of Turkey* in English at 2000.
- 15425 *Israel* with news in English at 1200.
- 17735 R. *Havana, Cuba* in English 2035.
- 21605 *RSA, South Africa* with quiz show at 1305.



MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

ROY PATRICK (Derby) has been busy with his National 1400 receiver on the medium waves. He reports good reception of Radio London on 1457kHz and the two IBA London transmitters on 557kHz and 719kHz. While on a visit to Farnborough (Hants) Roy logged Radio Brighton 1484kHz, Radio London and Radio Solent on 998kHz.

Richard Livesey (Guildford) has used his Audio-tronic multiband receiver with internal ferrite aerial to hear Radio Portugal 755kHz at 2310hrs; Radio Prague 1286kHz; Trans World Radio Monte Carlo 1466kHz at 2230hrs; Radio Moscow 1493kHz at 2230hrs; Radio Warsaw 1502kHz at 2230hrs. All of these broadcast in English.

Ian Gordon (Birmingham) has a Codar CR70A receiver, a 25 metre longwire antenna and an aerial tuning unit (ATU). He reports hearing Radio Tirana 1394kHz with sign-on at 2000hrs; Radio Blackburn 854kHz; R. Leeds 1106kHz; R. Stoke 1502kHz; R. Nottingham 1520kHz; R. Bristol 1546kHz plus the American Forces Network in Germany on 611kHz (Grafenwohr / Kaiserslautern / Nürnberg), 872kHz (Frankfurt), 935kHz (Berlin), 1106kHz (Munich),

1142kHz (Bremerhaven/Stuttgart). The AFN can also be heard on 1034kHz (Karlsruhe), 1304kHz (Heidelberg), 1394kHz (Augsburg).

M. Laugharne (Didcot, Berks) reports hearing R. Solent 998kHz, R. London 1457kHz, R. Oxford 1484kHz and R. Bristol 1546kHz on his Philips portable receiver. T. D. Wilson (Hemel Hempstead) used a Grundig Mariner to hear R. Sweden 1178kHz and R. Portugal 755kHz, both in English at 2300hrs. He mentions receiving WINS, New York City on 1010kHz last February. Gary Celand (Southall, Middlesex) would like to listen to North American stations on the medium waves and when reception is possible. A path of darkness between transmitter and receiver is required for medium wave propagation. Listen for North Americans some five to six hours after sunset in the UK. From November to February they can be logged as early as 2330hrs when conditions are favourable. Those most frequently heard are CJON St. John's in Newfoundland on 930kHz; CHER Sydney, Nova Scotia on 950kHz; WINS New York City on 1010kHz; CBA Moncton, New Brunswick on 1070kHz and WNEW 1130kHz New York City.

The BBC have announced the location of the first four low power medium wave stations which will improve the Radio 4 service to the south-west of England. Torquay 854kHz (351m), Barnstaple 683kHz (439m), Plymouth 1457kHz (206m) should come into service before the end of 1973 and Redruth 755kHz (397m) by the Spring of 1974. The Barnstaple service will replace the present one on 692kHz (434m) while the others will be additional to the existing Radio 4 medium wave service.

VHF/FM DXING by SIMON DAVID

T. J. Clamp of Cranbrook in Kent lists among other stations in the U.K., Markelo 2 on 98.4MHz and Roermond 1 on 88.3MHz, both from Holland, as well as Aalter, Belgium on 98.5MHz. He uses a Grundig Melody Boy 1,000 receiver and the in-built 86cm telescopic aerial. He also says "How about a list of BBC local radio station frequencies on f.m.?" Other readers have also asked for this information, so I have included it in this month's column. The BBC Engineering Information Department issues complete lists with frequencies, powers, and polarization on Information Sheets 1034(24) and 1919(21) for any one with a technical interest. In the not too distant future I shall be giving details of some of the European frequency allocations. Details on Radio Telefis Eireann were given last month.

Igor Hájek has given me some very interesting gen on East European bands. With reference to my comments in the September issue, he points out that East European countries (including U.S.S.R.) use the 65-73MHz band, possibly with a view to making it difficult for their local population to have access to Western broadcasts. In spite of this, Czechoslovakia have tuners that cover West Europe (CCIR) and East Europe (OIRT). How long before we have this facility as commonplace in the U.K.? (see Leader article—Ed.).

This lower frequency band is in the 4 metre area of the dial and does lend itself very well to DX reception, as my colleague David Gibson will testify.

Future plans for stereo on v.h.f./f.m. include Wenvoe and Kirk O'Shotts next year, Pontop Pike and Sandale (near Carlisle) in 1975. It is surprising that Norfolk and Huntingdon areas are not yet planned, especially in view of the flat terrain.


The following is a list of BBC Local Radio stations. Birmingham, Blackburn, Manchester and Teesside will have transmission powers increased. Slant polarisation is employed at Blackburn, Derby, Leeds, Leicester, Manchester, Nottingham, and Sheffield (main). All others use horizontal polarisation. Medium wave shown in brackets.

Birmingham 95.6MHz (206m)
Blackburn 96.4MHz (351m)
Brighton 95.3MHz (202m)
Bristol 95.5MHz (194m)
Carlisle 95.6MHz (397m, 206m)
Derby 96.5, 94.2MHz (269m)
Humberside 96.9MHz (202m)
Leeds 92.4MHz (271m)
Leicester 95.1MHz (188m)
London 94.9MHz (206m)
Manchester 95.1MHz (206m)
Medway 96.7MHz (290m)
Merseyside 95.8MHz (202m)
Newcastle 95.4MHz (206m)
Nottingham 95.4MHz (197m)
Oxford 95.2MHz (202m)
Sheffield 97.4, 88.6MHz (290m)
Solent 96.1MHz (301, 188m)
Stoke-on-Trent 96.1MHz (200m)
Teesside 96.6MHz (194m)



I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID

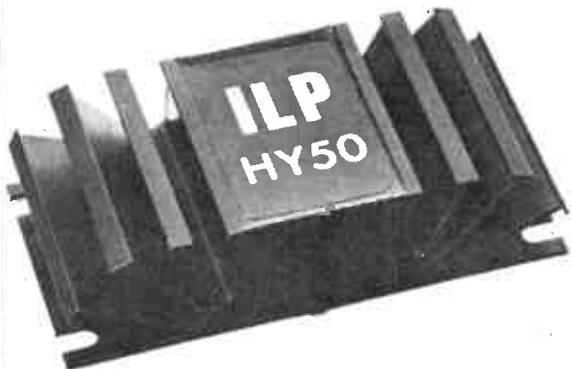

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular amplifier to a simple input/output device requiring only the addition of a basic unstabilized (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy, sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of 'Kling-size' cigarettes.


Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

OUTPUT POWER: 25 watts RMS. 50 watts peak music power
LOAD IMPEDANCE: 4-16Ω into 8Ω
INPUT SENSITIVITY: 0db (0.775 volts RMS)
INPUT IMPEDANCE: 47KΩ
TOTAL HARMONIC DISTORTION: Less than 0.1% at 25 watts typically 0-05
SIGNAL/NOISE RATIO: better than 75db
FREQUENCY RESPONSE: 10Hz-50KHz ± 1db
SUPPLY VOLTAGE: ± 25 volts
SIZE: 105 x 50 x 25 mm

Price £5.40 mono, £10.80 stereo

Price inclusive of VAT & P & P

NEW HY5 PRE-AMPLIFIER

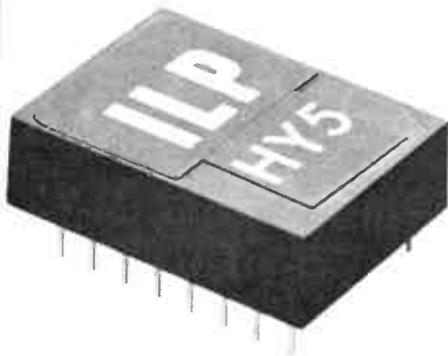

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids. Like the HY50, the new HY5 has no external components & has been redesigned to run off a split power-line with improvements in signal/noise, overload, capability & reduced distortion. The output has been increased to match the power module (Odb), and to share the same power supply. Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 & power supply only potentiometers are required to complete a simple mono amplifier with input & output facilities expected to be found on HI-FI amplifiers. The combination of two HY5's & two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.

INPUTS
 Magnetic Pick-up 3mV (within 1db RIAA curve)
 Ceramic Pick-up up to 3mV
 Microphone 10mV
 Tuner 250mV
 Auxiliary 3-100mV
 Input impedance 47kΩ 1kHz

OUTPUTS
 Tape 100mV.
 Main output, 0db (0.775volts)

ACTIVE TONE CONTROLS
 Treble ± 12db at 10kHz
 Bass ± 12db at 100Hz

OVERLOAD CAPABILITY (equalization stage) 40db on most sensitive input

OUTPUT NOISE LEVEL (below 10mV magnetic input) 68db

DISTORTION 0.05% at 1kHz

SUPPLY VOLTAGE ± 16-25 volts

SUPPLY CURRENT 15mA

Price £4.51 mono, £9.02 stereo

Price inclusive of VAT & P & P

POWER SUPPLY PSU50



The new PSU50 has a low profile look being only 2 1/2 inches high and can be used for either mono or stereo systems.

SPEC.
OUTPUT VOLTAGE ± 25 volts
INPUT VOLTAGE 210-240 volts
SIZE L. 70, D. 90, H. 60 mm

Price £5.23
 Price inclusive of VAT & P & P

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

ELECTRONIC MULTIMETERS

Service type CT38 these are a 97 range unit covering AC and DC volts 250 Mill/V to 10Kv, AC and DC Amps 10 uA to 25 Amps, Resistance 0 to 1000 Megs, Watts 0 to 5 Watts at 15 to 5000 ohm load, R.F. probe unit for use to 200Mc/s, unit is for use on 200/250v 50c/s mains. Supplied tested with, accs., circ., copy of inst., etc. Good Cond. Price £21.

RADAR TEST UNIT TYPE 1

Used for testing S band Radar Rx, etc., contains 3" tube type VCR138 (okay for scope use) plus 19 other valves min. and octal types. Klystron CV2161 with tuning ass. etc., 4" dia. 50 Ua meter, complete in case size 17 x 11 x 16". These units have an internal P.U. but this is not suitable for use on 50c/s however most of the P.U. components Chokes, Conds., etc. can be used on 50c/s inc. EHT conds. Supplied complete in case, ex equipment with circuit, and circ. of Scope. Meter and Tube checked.

Price £10.45

V.H.F. TEST OSC.

Test Osc covering range 20 to 88 Mc/s in 4 bands also as 2 Mc/s Xtal check, R.F. can be Pulse Modulated at various freq. by selection of internal xtal. Also contains variable O/P Noise generator with 50 Ma monitor meter. Power required 250v HT at 60 Ma and 6.3v AC supplied with Cal charts and Ae, ex equipment.

Price £5.50

MISC. ITEMS

The following items are new, Trans. H.T. 230v Pria. Sec. 1125-0-1125v at 565 Ma £7.70. Matching Choke £1.50, also Sec. 415-143-0-143-415v at 360 Ma on 415v and 120 Ma on 143v £3.35. L.T. type 210/250v Pria. Sec. 27v at 41 amps. cont. rating £13.20. **HEAD and MIKE SETS** for 19 set m.c. type £1.80. **BLOWER MOTORS** for use on 6 to 24v DC double ended type size 6 x 4" £1.90. C.R.T. type 7BP7A 7" flat face tube, blue/yell. phosfor, 6.3 heater emag. focus and defl., with base conn., okay for slow scan T.V. etc. £1.83. **TRIMMERS** 20pf air spaced ceramic 10 for 55p, **NEONS** wire ended type req. 470K for 240v, 10 for 55p. **PRESS. GAUGE** scale 0 to 120, vehicle type, elec. operated 44p. **X POINTER METERS** dual 115Ua meter scale marked L & R, okay for Stereo Balance indicator (circuit supplied) £1.68. **HEADPHONE MATCHING TRANS.** high to low impedance with 5ft lead with standard plug 60p. **BATTERIES** lead acid unspillable aircraft type 24v 25 Amp/Hr. with inst. will split to make 2 x 12v £10.20, also 24v 4A/Hr. only £4. **THE FOLLOWING ITEMS ARE EX EQUIP. SWITCHES YAXLEY TYPE** with knob 4p 11w 4b 76p and 4p 4w 2b 40p both inc. low value res. **INVERTOR TRANS.** 12v DC to 300v at 150 Ma with circ. £2. **METER UNIT** 270 deg. FSD 1 Ma scale 0 to 20 size front 3 1/2" sq., glass 2 1/2" dia., also in same case centre reading meter 100-0-100 uA scale not marked and on/off flag type ind. Okay for rev. counter and center reading meter can be used as battery voltage Ind. circuit for this supplied £3. **TOGGLE SWTS.** aircraft pattern suitable for L.V. DC use okay for car use, 2 for 33p. **TRANSISTORS** type OC42 pnp swt. type long leads marked 50 for 60p. **CONDS.** tuning split stator type 20pf per section 1 x 1/2" shaft 2 for 44p. **CODER UNIT** contains 10 min. valves, 13 min. relays 12v 2p c/o 12 min. micro swts., all in case, size 10 x 7 x 5" plus misc. parts, good cond. £2.80. **VIDICON** camera tubes standard 1" type gen. purpose by E.E. and E.M.I. graded according to scan marks with data £9 and £6. **IND.** 208 repeater ind. unit with CRT CV1526 2.75" dia., okay for scope use, with base and shield data supplied, note these have scan marks £1.77 B.N.C. sks. bulkhead type single nut fix. 75 ohm, 5 for 60p.

ABOVE PRICES INC. POST/CARR. AND VAT CHARGES, CARRIAGE CHARGES APPLY TO MAINLAND ONLY, SAE for LIST or ENQUIRY

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD, S9 5HL
Tel. 444278 (0742)

Hold this while I solder it.



Sorry about that, Roger.

BAND-AID* Washproof Plasters.

© Johnson & Johnson LTD

* TRADE MARK

13 DISTRIBUTION AMP PANEL

From £2.85

Safe and quick. FOUR 13 amp 3-pin shuttered Socket Outlets Red neon warning indicator operates when in use. Only £2.85 + 38p p. & p. Also De Luxe Model (illus.) PLUS On/Off Switch. PLUS Magnetic Contact Breaker—If you draw too much current it switches off automatically. PLUS 30ft. (9 metres) approx. lead £2.85 + 40p p. & p. Six socket 6a-12a £12.20 + 55p p. & p. Bonus offer: set of four free 13 amp plugs 70p extra. Post free if ordered with a panel.

TWIN-BEAM SPEC-LAMP — Worn just like a pair of spectacles. Two powerful spot lamps illuminate working area. Can be worn with Binocular Magnifier. Battery operated. Only £2.85 + 10p p. & p. Send £2.45.

JOHN DUDLEY & CO. LTD. (Dept. WP4), 301 Cricklawood Lane, London, NW2. Tel.: 01-438 5917. Callers Welcome. Easy Parking.

BINOCULAR MAGNIFIER

FOR PRECISION WORK UP CLOSE LEAVES BOTH HANDS FREE

See close-up work with less eye strain & fatigue. Lightweight adjustable headband. Powerful optically ground lenses from Continental glass-works. Can be worn over normal glasses. An essential aid in modelling, industry, home and workshop. Stamp collecting. Jewellers watchmakers and any fine work 2 1/2 x magnification. £6.65 + 40p p. & p. 3 x model 65p extra. State model.

SPECIAL OFFER: Computer boards, ex-equipment with a good selection of semi-conductors, resistors, capacitors and other useful items. 5 for 75p including V.A.T.

An extensive range of Semi-conductors; Electrolytic capacitors; Mylar, Polyester and Ceramic capacitors; Fixed and Variable resistors. Brand new by well known manufacturers.

Send S.A.E. for comprehensive list to:—

W. P. COMPONENTS
7 Brook Avenue, Edgware,
Middlesex



AMATEUR BANDS

SHORT WAVES

by DAVID GIBSON, G3JDG

IT'S an interesting period for Amateur Radio. The sunspot count continues to creep lower and the longer, darker (colder) nights are making 14/21MHz less favourite for DX working. For the s.w.l. who reckons he's up to tackling something a little more difficult, then I suggest a serious DX assault on 7MHz. This will assume more and more the role of the major DX band. Further down, on 3.5MHz, more DX is becoming apparent so it could well be an l.f. DX winter.

On 3.5MHz this past month, goodies like OA4OS, ZS6TE and 9J2DT have been heard while up on 7MHz the air has been buzzing with c.w. offerings from calls like CM2JA, CR6AI, FG7XC, VK3MR, ZS5AN and 8P6DR.

Hair-raising happenings on top band. Several G stations have worked VP8KF in the Falklands. A few years back, this station would never have been thought about on 1.8MHz. Even now, a VP8 would cause excited s.w.l. squeaks if heard on 14MHz. Top-band sleuths are invited to lay in wait for r.f. travellers like ZL1MQ and a few JA stations who are known to be loitering. One station in Japan (JA7AO) has worked all continents (WAC) except Europe so it would be a safe bet to reckon his signal is there somewhere—who'll be first to report it?

Up on ten metres things seem to be fairly static. Long periods when one hears a noise like frying eggs (cheaper variety) and then, suddenly, an S9 plus five million dB's (well, it sounds like it) comes out of nowhere. South African stations are logged without too much effort and the South American continent comes romping in at times. Don't forget to listen first for the beacon stations since these will give a useful indication of what the bands are doing.

Before we take a peep at the logs sent in this month, let's open up the JDG little black book for contests in November. According to my crystal ball, the following are on: November 10-11, OK DX contest (c.w./phone); 10-11, topband contest; 11, four metre contest; 24-25, CQ WW (c.w./phone) contest.

First event in December is on the 9th and is a two metre contest for fixed stations—you've just got time to tie that 40-element Yagi beam to the chimney pot and switch on!

Readers' Logs

Dave Gregory (Plymouth) confesses, "I have been a Broadcast Bands maniac (is there any other kind?) for some months now". Brethren will be pleased to know that my Brother Gregory has seen the light and cleansed his sins by purchasing a 9R-59DS, RA-1 and CR100. With a homebrew a.t.u. and "DX processing unit" Dave repents on 14MHz with the following log; A51PN, A6XP, AR1RSP, EA7PS (an XYL—O'lay); WA5FW, ZB2BL, 3A2EE, 4Z4MQ, 5Z4GB, 5Z4GK.

A. McNeill (Newbury), comments on the many eastern europeans loose on 14MHz. He also praises the DX'ers processing unit which was featured in P.W. and queries the callsign NI3A who keeps popping up. Are there NI takers to answer this?

Derek Harding (Godstone) says he's 23 years old and has been an s.w.l. for four days (What a waste of 22 years, 361 days). Derek asks how he can filter out the various loud whistles which beset him? Anyone got any thoughts other than the on/off switch?

John Turner sends in a 21MHz selection from a log made during his school holidays (think of all the conkers you missed). Gear in his bedroom at Doncaster includes a Pye Cambridge receiver with an 85ft end fed supplying the microvolts to the tune of; A2CCY, CE3OE, CN8CG, CP1HL, CR6AD, CT1BY, CX2CS, CX7BM, DU1FE, EA8CS, EA8HH/M, EL1G, ET3USA, HK3CDW, HS4AJL, JA4PE, JA6PIC, JA7KHZ, JH1DEV, KP4AD, KZ5EK, LU5MAO, M1C, PZ1DR, TI2IO, TR8VT, TU2DO, VK4PU, VP2MF, VP8ML, VP9CB, VQ9BP, YN1AZ, YV5EED, ZD3D, ZD8MH, ZS4JW, 4Z4LM, 7X0WW, 8R1J, 9G1AF, 9H1DP, 9M2DQ, 9U5CR, 9X5VA.

Tam Large (Hassocks) lives on a farm in Sussex. His favourite animal is a 9R-59DE. Feed it a staple diet of mains electricity and put it on a 200ft. end fed lead and it yields the following twenty metre tweets; CR6LX, HP1TG, K2LZQ/OH0, M1C, PZ1DR, 4W1AF. Similar treatment brought forth the following from 21MHz; TG9CQ, XE1GR, ZD3D, 9M2CX.

Paul Davies (Blackpool) is learning to read c.w. (good lad). Meanwhile, he listens with baited breath on 14MHz to the following juicy jingle; CR6GA, EL8J, EP2SP, ET3GA, HR2WTA, IB0PV, JA4JUV/MM, JY6HCT, KA6HQ, 9H1CQ, 9H4B, 9K2AL, 9M2DW, 9X5NA, all on s.s.b. Gear used is a Heath HR-10B, Joystick antenna and an a.t.u.

S. Eldridge (Crawley), has a CR70A, 132ft. end-fed looped round the bedroom and a yen to listen on 15 metres. Here's the gen on his yen; A6XB, CE3PY, CR6AG, CR6HZ, CT2AB, H18LC, JA8ISK, JE1MUM, JF1IUA, JH3EXI, JR1TAM, KA2PJ, LU6FEP, PT2JB, TI2STI, TR8VE, VQ9M, VU2DK, ZP5VO, ZS1J, ZS4JW, 5N2ESH, 5U7BA, 9X5VA.

BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

Medium Waves Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

VHF/FM Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

AMATEUR BANDS

Short Wave/VHF

Logs in alphabetical order please by 15th of the month to David Gibson, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone 6743

0A2	.33	6BE6	.20	6LD20	.55	128H7	.35	50C5	.32	E182CC1.00	EF91	.17	KT41	.98	PEN453DD	UF41	.60	AA129	.17	BC108	.14	0A9	.14
0B2	.33	6BH6	.70	6N7GT	.60	128J7	.44	50CD62	.17	E1148	.58	EP92	.30	KT44	1.00	UF42	.80	AAZ13	.20	BC113	.28	0A10	.47
0Z4	.44	6BJ6	.39	6Q7G	.44	128K7	.55	50EH6	.55	EAS0	.27	EF97	.55	KT66	.80	UF80	.85	AC107	.17	BC115	.17	0A47	.11
1A3	.49	6BQ7A	.50	6Q7GT	.47	128Q7	.55	50L6GT	.45	EA76	.88	EF98	.65	KT81	2.00	UF86	.84	AC113	.28	BC116	.28	0A70	.17
1A5GT	.49	6BR7	.90	6Q7(M)	.55	14H7	.55	58A2	.48	EABCS0	.90	EF183	.25	HV72A	.83	UF114	.87	AC128	.22	BCY12	.55	0A81	.10
1A7GT	.83	6BR8	.75	6R7G	.80	14H7	.75	58A3	.40	EAC91	.36	EF184	.27	HV72B	.83	UF124	.88	AC132	.22	BCY33	.22	0A85	.09
1B3GT	.49	6BB7	1.40	6R7M	.75	19A7	.80	AC1	.90	EAF42	.48	EF80A	1.20	KTW63	5.00	UF409	1.20	AC154	.28	BCY34	.25	0A90	.14
1B5GT	.55	6BW6	.72	6R7M	.85	19A7	.85	AC1	1.40	EAF601	.50	EF80	3.4	MHL16	.75	UF602	.85	AC156	.22	BCY38	.25	0A91	.10
1L4	.14	6BW7	.50	6SC7GT	.33	20D4	2.00	150B2	.58	EB34	.25	EL32	.60	P61	.40	UF33/2	5.00	AC157	.28	BCY39	.28	0A95	.10
1N5GT	.60	6RZ6	.49	6S67	.39	20P2	.67	807	.87	EB91	.12	EL34	.48	PABC80	.32	YP81	.25	AC165	.28	BCZ11	.42	0A200	.10
1R5	.28	6CB8A	.40	6B17	.44	20L1	.80	6702	.80	EBG41	.48	EL35	1.00	PC86	.44	YP82	.26	AC168	.28	BF158	.32	0A202	.11
1R4	.33	6C4	.28	6B17GT	.55	20P1	.55	6763	.50	EBG81	.29	EL37	.74	PC88	.44	YP83	.26	AC178	.42	BF159	.28	0C22	.48
1U4	.44	6C9	1.00	6B17GT	.44	20P1	.76	7476	.70	EBF80	.36	EL41	.32	PC89	.53	YP86	.31	AC178	.61	BF163	.22	0C46	.17
1U5	.80	6CD6G	.80	6B17GT	.33	20P4	.80	AC/PEN	.98	EBF83	.33	EL41	.50	PC97	.38	YP500	.80	AC177	.31	BF173	.42	0C24	.48
2D21	.44	6CG8A	.75	6U4GT	.70	20P5	.95	AC/PEN/	.98	EBF89	.26	EL43	.38	PC900	.29	YP500A	.80	AC177	.28	BF180	.33	0C25	.48
2GK5	.55	6CH6	.55	6V6G	.17	25A6G	.38	DD	.98	EEL21	.60	EL44	.23	PC84	.29	YP800	.31	AC178	.28	BF181	.44	0C36	.85
3A4	.36	6CL6	.48	6V6GT	.27	25L6G	.20	AC/PEN	.38	ECB6	.59	EL45	.40	PC85	.24	YP801	.31	AC178	.28	BF185	.44	0C38	.47
3D6	.19	6CM7	.75	6X4	.27	25Y6G	.70	AC/TH1	.50	ECB8	.59	EL46	.38	PC88	.39	YP730	.48	AC178	.28	BF185	.44	0C38	.47
3Q4	.49	6CU5	.75	6X6GT	.28	26Z4G	.38	AC/TP	.98	EC92	.94	EL91	.33	PC89	.42	QV03/10	.10	AC178	.28	BF185	.44	0C38	.47
3Q5GT	.55	6CW4	.75	6Z6	.75	26Z4G	.38	AL60	.78	EC93	.95	EL95	.32	PC8189	.48	YP120	.40	AC178	.28	BF185	.44	0C38	.47
3B4	.28	6DE7	.75	7B7	.60	25Z5	.50	ATP4	.40	EC93	.95	EL96	1.20	PCF80	.26	Q875/20	.63	AC178	.28	BF185	.44	0C38	.47
4CB6	.55	6DT6A	.75	7H7	.55	25Z6G	.70	AZ1	.40	EC94	.98	EL96	.75	PCF82	.30	Q895/10	.69	AC178	.28	BF185	.44	0C38	.47
5C88	.55	6EW6	.75	7R7	1.50	30A3	.65	AZ21	.46	EC94	.98	EL96	.75	PCF84	.40	QV04/7	.63	AC178	.28	BF185	.44	0C38	.47
6T4	.30	6E5	.75	7Y4	.44	30C15	.65	AZ41	.53	EC92	.94	EL91	.33	PCF96	.44	R19	.28	AC178	.28	BF185	.44	0C38	.47
5U4G	.30	6F1	.70	7Z4	.80	30C17	.76	CL33	.90	EC93	.95	EL95	.32	PCF90	.67	TH233	.98	AC178	.28	BF185	.44	0C38	.47
5V4G	.35	6F6G	.38	9D7	.40	30C18	.70	CV63	.58	EC94	.98	EM94	.31	PCF90	.40	TP250	.98	AC178	.28	BF185	.44	0C38	.47
5Y4GT	.30	6F13	.48	10C2	.65	30C19	.60	CY1C	.55	EC95	.94	EM95	1.00	PCF90	.37	UAB90	.30	AC178	.28	BF185	.44	0C38	.47
5Z4G	.34	6F14	.40	10D7	.55	30P5	.61	CY31	.29	EC96	.40	EM97	.49	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
5Z4GT	.38	6F18	.55	10P1	.60	30P1L	.68	CY31	.29	EC96	.40	EM97	.49	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6J30L2	.55	6F23	.65	10P9	.65	30P1L2	.69	DAF91	.36	EC97	.48	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6A8G	.44	6F24	.60	10P18	.55	30P1L3	.50	DC90	.60	EC98	.44	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AC7	.16	6F25	.51	10L1D11	.70	30P1L4	.65	DP91	.18	EC98	.44	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AG5	.27	6F28	.60	10P13	.64	30P1L5	.66	DP96	.36	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6A18	.60	6F32	.30	10P14	2.00	30P1L6	.55	DIH83	.55	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AJ5	.75	6GH8A	.75	12A8	1.00	30P1L7	.65	DH76	.45	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AK5	.27	6GK5	.65	12AC6	.55	30P1AMR	.95	EZ1	.40	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AK6	.60	6OU7	.75	12AD6	.60	30P12	.69	EZ10	.50	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AM8A	.55	6H6GT	.18	12AE6	.60	30P19/	.60	EZ11	.50	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AN8	.49	6J5GT	.29	12AT6	.28	30P4	.65	EZ12	.50	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AQ5	.35	6J6	.30	12AV6	.38	30P1L1	.57	EL96	.32	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AR5	.55	6J7G	.24	12AV6	.28	30P1L3	.75	DM70	.20	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AB7	1.00	6J7M	.38	12BA6	.30	30P1L4	.75	DM71	.50	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AT6	.30	6J8A	.76	12BE6	.30	30P1L5	.87	DM72	.68	EC99	.27	EM98	.54	PCF90	.55	UAF42	.49	AC178	.28	BF185	.44	0C38	.47
6AU6	.28	6K7G	.12	12BH7	.27	35A3	.48	DY902	.30	ECL80	.28	ECL82	.28	PC900	.29	YP500	.80	AC178	.28	BF185	.44	0C38	.47
6AV6	.38	6K8G	.83	12J7GT	.55	35D5	.70	EB90C	1.65	ECL82	.28	ECL82	.28	PC900	.29	YP500	.80	AC178	.28	BF185	.44	0C38	.47
6AW8A	.65	6L1	2.00	12K6	.58	35L6GT	.43	E80F	1.20	ECL82	.28	ECL82	.28	PC900	.29	YP500	.80	AC178	.28	BF185	.44	0C38	.47
6AX4	.55	6L8GT	.55	12K7GT	.38	35W4	.23	E83F	1.20	ECL84	.54	ECL84	.54	PC900	.29	YP500	.80	AC178	.28	BF185	.44	0C38	.47
6BG	.25	6L7	.50	12Q7GT	.45	35Z4GT	.24	E88OC	.60	ECL86	.54	ECL86	.54	PC900	.29	YP500	.80	AC178	.28	BF185	.44	0C38	.47
6BA6	.19	6L18	.49	12RC7	.50	35Z5GT	.30	E92CC	.40	ECL86	.54	ECL86	.54	PC900	.29	YP500	.80	AC178	.28	BF185	.44	0C38	.47
6BC8	.40	6L19	2.00	12RG7	.38	50B5	.35	E180F	.90	EF22	.43	EF22	.43	PC900	.29	YP500	.80	AC178	.28	BF185	.44	0C38	.47

All goods are unused and subject to the standard 90 day guarantee. Cash or cheque with order only. Despatch charges: Orders below £25 add 10p per order up to 3 items, each additional item 3p extra. Orders between £25 and £10 add 25p total. Orders over £10 are post free. Same day despatch. Any parcel insured against damage in transit for only 3p extra per order. Terms of business—see on request. Business hours: Mon.-Fri. 9-5.30 p.m. Closed 1-2 p.m. and Sat. We do not handle seconds or rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply. No overseas orders accepted.

Train for television

Course commences 2nd January, 1974

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____

Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS
(Dept. PW8) 34a Hereford Rd., London W2 5AJ

BAKER 12" MAJOR £9.90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.



MAJOR MODULE KIT £12.50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W	£8.80	Superb 12 in. 20W	£16.50	New Group 60/12	
Major 12 in. 20W	£9.90	Group 25 12 in. 25W	£8.80	12 in. 50W	
Deluxe 12 in. 15W	£11.00	Group 35 12 in. 35W	£9.90	Price £17.60	

BAKER LOUSPEAKER CO., BENSAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684 1665
PRICES INCLUDE V.A.T. HI-FI ENCLOSURE PLANS 42p

INTER-LOCKING PLASTIC STORAGE DRAWERS

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D, 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

DISCOUNT PRICES

SINGLE UNITS (5" x 2 1/2" x 2 1/2") £1.40 Dozen
DOUBLE UNITS £2.30 Dozen
DOUBLE (3D) £2.50 for 8

DOUBLE TREBLE 2 drawers in one outer case (6D) £3.60 for 8 extra large size (6D) £3.40 for 8, Carriage 35p Orders over £10 post free


QUANTITY DISCOUNTS! 5% in £1 for orders over £10, 7 1/2% over £10, 10% over £50. Quotation for large quantities.

PLEASE ADD 10% V.A.T. TO TOTAL REMITTANCE.

(Dept. PW11), 124 CRICKLEWOOD ROADWAY, LONDON N.W.2. 01-450 4844

INTERNET

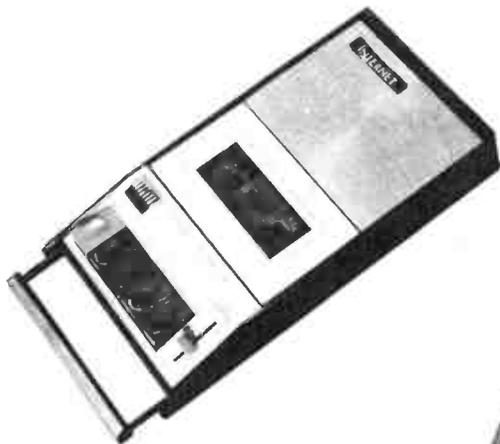ALL OFFERS APPLY TO UK ONLY WHILST STOCKS LAST



Cassette Tape Recorder AC 240V. Works on 6V battery 4 x 1/2 U11. Piano keys. Sliding. V/C Earphone. Rem. Mic. Built-in Condenser Type Microphone.



£9.18 + 92 VAT. Price £10.10, P. & P. included.

Microphone opt. £2.00 + VAT.

Cassette Tape opt. 35p + VAT.

Car Radio No. S101. 12V. Neg. and Pos. polarity, Fixing Bracket. 4" Speaker.

£6.20 + 62p VAT. Price £6.82.

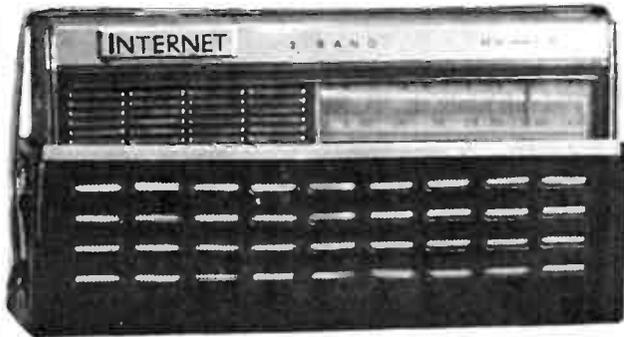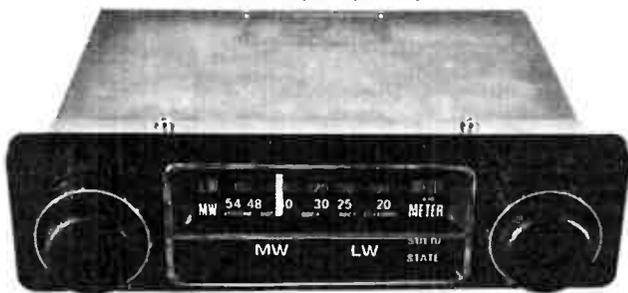

Radio MW/LW No. J70. MW/LW. Battery only, LX12 U12. Pen Light.

£4.20 + 42p VAT. Price £4.62, P. and P. included.

INTERNET RADIO (PRODUCTS) LTD.

100-102 BECKENHAM ROAD, BECKENHAM, KENT, BR3 4RH

NAME

ADDRESS

NEW VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH.

74 Series TTL

INTERNATIONALLY KNOWN BRANDS
1st GRADE DEVICES AT NEW
ROCK BOTTOM PRICES

SN7400	17p	SN7473	40p
SN7401	17p	SN7474	40p
SN7402	18p	SN7475	50p
SN7410	17p	SN7476	44p
SN7413	30p	SN7490	68p
SN7420	17p	SN7492	74p
SN7477	99p	SN7493	74p

This range will be increased continuously. Please enquire about any devices not listed.

PRICE BARRIER SLASHED

LED READOUTS

(0.3" HIGH CHARACTERS)



Ref LED 1

ALSO + 1 REF LED 1A

£1.99 + 20p VAT = £2.19

Veroboard



2 1/2" x 1 in	61p	61p	—
2 1/2" x 3 1/2 in	22p	18p	11p
2 1/2" x 5 in	26p	23p	13p
3 1/2" x 3 1/2 in	26p	23p	—
3 1/2" x 5 in	30p	30p	19p
17 in x 2 1/2 in	74p	55p	41p
17 in x 3 1/2 in	99p	77p	57p
17 in x 5 in	—	—	82p

DIP Breadboard 4 1/2 in x 6 1/2 in. 110p.
Verostrip 8 1/2 in x 1 1/2 in. 26p. Spot-Face Cutter 40p. Pin Injection tool (State 0 1 in or 0 15 in). 52p. Terminal pins. 20p (packs of 36)—state size

I.C. SOCKETS



8 pin 13p	16 pin 17p	36 pin 39p
14 pin 15p	24 pin 26p	40 pin 44p
	28 pin 30p	

HEAT SINKS

TV2 for TO-66	15p	5F for TO-5	
TV3 for TO-3	16p	18F for TO-18	



512p

TV4 for TO-126

SL4D3D

TV5 for TO-220

DIP 14/5 for EA1000



16p

10DN400 4

4Y-1 4




46p



35p

BRIDGE RECTIFIERS

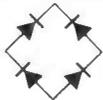

P I V	1 amp	R M S	2 amp
100V	20p	50V	35p
200V	22p	100V	40p
600V	25p	200V	45p
1000V	38p	600V	50p


RECTIFIERS

P I V	1 amp	3 amp	
50	1N4001 6p	1N5400 15p	
100	1N4002 7p	1N5401 16p	
200	1N4003 9p	1N5402 17p	
400	1N4004 9p	1N5404 22p	
600	1N4005 11p	1N5406 26p	
800	1N4006 13p	1N5407 30p	
1000	1N4007 16p	1N5408 33p	

BY100	16p	BY133	23p
BY103	22p	BY164	55p
BY105	16p	BY176	£1.65
BY126	16p	BY182	£1.65
BY127	16p	BY250	25p

OR FILAMENT INDICATOR

MINITRON 3015F & G

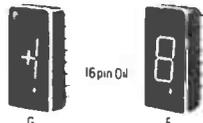

at BREAKTHROUGH

PRICE £1.49

Cheapest Opto yet
GaAsP LED's



Remember Vat Inclusive Prices

DIGITAL CLOCK



on a chip

Just imagine, one MOS LSI I.C. eliminating 15 MSI I.C.s and numerous other components. Either

12 or 24 hour. 4 or 6 digit
50 or 60Hz operation
leading zero suppression
single voltage supply
similar to DIGITRONIC in
P.W. March 1973.

Only £7.99

With 4 LED's £16.59

With 6 LED's £20.75

CHROMASONIC electronics

RESISTORS

Rating	Type	Tolerance	Range	Price Each
1/4 watt	Metal Glaze	±5%	E12 Series 51Ω to 100KΩ	5p
1/2 watt	Carbon Film	±5%	E24 Series 51Ω to 330KΩ	11p
1 watt	Metal Oxide Film	±2%	E24 Series 10Ω to 1MΩ	44p
1/2 watt	Cermet Thick Film	±2%	E12 Series 56Ω to 150KΩ	8p
1 watt	Carbon Film	±5%	E24 Series 10Ω to 10MΩ	11p
1/2 watt	Carbon Composition	±0.5Ω	E12 Series 2.2Ω, 2.7Ω, 3.3Ω, 3.9Ω, 4.7Ω	44p
1 watt	Carbon Composition	±5%	E12 Series 10Ω to 10MΩ	6p
2 watt	Carbon Film	±5%	E12 Series 10Ω to 10MΩ	3p
1/2 watt	Wire Wound	±5%	E12 Series 0.22Ω to 0.47Ω	10p
2 1/2 watt	Wire Wound	±5%	E12 Series 1Ω to 270Ω	10p
5 watt	Wire Wound	±5%	E12 Series 0.5Ω to 8.2KΩ	10p
10 watt	Wire Wound	±5%	E12 Series 0.5Ω to 6.8KΩ	11p
10 watt	Wire Wound	±5%	10KΩ, 15KΩ, 20KΩ, 25KΩ	17p
15 watt	Wire Wound		10Ω to 6.8KΩ	13p

CAPACITORS

MULLARD C333, 629 and 630 series
—Ceramic Plate E12 series from
1.8pF to 0.022µF. 54p.

CERAMIC DISC—LOW VOLTAGE—
0.01µF, 0.022µF, 0.047µF. 54p;
0.1µF, 0.22µF, 0.47µF. 64p.

POLYSTYRENE (160V)—From 10pF
to 0.01µF in multiples of 10pF. 15pF
22pF 33pF 47pF and 68pF 34p.

MYLAR PLATE (100V)—1000 pF
2000pF, 5000pF 24p, 0.01µF, 0.02µF,
0.04µF, 0.05µF, 0.1µF, 0.22µF,
0.47µF, 0.68µF.


MULLARD C280 (250V POLYESTER)
—0.01µF, 0.015µF, 0.022µF,
0.033µF, 0.047µF, 0.068µF,
0.1µF, 0.15µF, 0.22µF, 0.33µF,
0.47µF, 0.68µF, 1µF, 1.5µF, 2.2µF,
2.2µF 26p.

TRANSISTORS and DIODES

AC107	18p	AF179	71p	BC214L	11p	BF177	26p	BSX20	18p	TC44	46p
AC126	13p	AF229	41p	BC268	28p	BF178	29p	BSX21	22p	TC2260	£1.87
AC127	13p	AS278	33p	BC327	24p	BF179	33p	BSY5A	13p	TP41A	81p
AC128	13p	BC107	15p	BC328	24p	BF180	33p	BU105	£1.75	TP42A	81p
AC176	15p	BC108	16p	BCY70	17p	BF181	35p	BU105.02	£1.92	TIS43	36p
AC187	22p	BC209	19p	BCY72	17p	BF184	27p	DI3V	53p	TIS73	£2.18
AC187K	20p	BC114	15p	BC210	28p	BF185	27p	M4000	£1.49	TIS91	33p
AC188	22p	BC117	16p	BC211	28p	BF186	29p	M4010	£1.49	TN697	16p
AC188K	20p	BC147	9p	BD115	74p	BF195	17p	MJE340	52p	TN705	16p
ACY17	24p	BC148	9p	BD124	82p	BF196	16p	MJE2955	£1.82	TN708	16p
ACY18	24p	BC149	9p	BD131	82p	BF197	16p	MJE3055	92p	TN914	24p
ACY19	25p	BC157	12p	BD132	82p	BF200	35p	MPP102	27p	TN102	28p
ACY20	22p	BC158	12p	BD131 PR	£1.40	BF220	27p	MPP103	41p	TN1303	24p
AD140	40p	BC159	14p	BD133	83p	BF248	27p	MPP104	45p	TN1304	24p
AD149	38p	BC168B	11p	BD135	45p	BF252	25p	MPP105	45p	TN1305	24p
AD161	29p	BC184	15p	BD136	50p	BF263	25p	MPP106	48p	TN1306	24p
AD162	29p	BC177	20p	BD137	57p	BF272	£1.21	OC20	33p	TN1307	27p
AD161 2 PR	50p	BC172	17p	BD138	74p	BF390	37p	OC35	38p	TN1308	27p
AF114	14p	BC174B	15p	BD139	78p	BF528	£1.01	OC36	38p	TN1309	27p
AF115	14p	BC177	22p	BD140	81p	BFW10	87p	OC44	13p	TN1813	22p
AF116	14p	BC178	22p	BD201	£1.55	BFW11	87p	OC45	13p	TN1711	26p
AF117	14p	BC179	24p	BD202	£1.37	BFW87	38p	OC71	13p	TN1893	52p
AF118	92p	BC182L	9p	BD203	£1.57	OC72	13p	OC72	13p	TN2150	£1.34
AF124	24p	BC183L	9p	BD204	£1.37	BFX20	37p	OC75	13p	TN2219	41p
AF125	22p	BC184	9p	BF109	75p	BFX88	86p	OC81	13p	TN2646	55p
AF126	22p	BC184L	9p	BF115	25p	BFY50	16p	OC83	25p	TN2905	48p
AF127	22p	BC187	27p	BF160	25p	BFY51	16p	OC10	22p	TN2924	14p
AF139	35p	BC212L	11p	BF167	27p	BR100	40p	OC170	27p	TN2926 all	10p
AF172	25p	BC213L	11p	BF173	27p	BY939	43p	OC171	27p	TN3053	22p

new stabilised

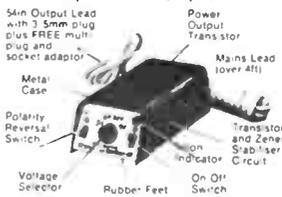POWER PACK CONVERTER
Switched 3, 6, 7.5 or 9 volts
Up to 400mA Output



Our Price £3.99 + P & P. 16p.
Unstabilised Version of above
Other Eliminators (unstabilised)*
6 volts at up to 50mA £1.65
9 volts at up to 50mA £1.65
9 volts (miniature) up to 50mA £2.09
6 + 6 volts at up to 50mA £2.75
9 + 9 volts at up to 50mA £2.75
3.4µF for Cassette Players (small) £2.20
3.4µF, 6.7µF, 9.12 volts up to 1A £3.75
Fully Stabilised* Car Battery Converter, giving switched outputs of 6, 7.5 or 9 volts £5.49
P & P. on all models 16p.

ZENERS

All 5% tolerance

BZY88	400mW, 3.3V to 33V	11p
1ZS	1W, 3.3V to 100V	18p
BZX70	2.5W, 7.5V to 75V	27p

SOUTHEND ELECTRONICS

COLOUR 25 KV TRIPLERS



£1.70 + 17p V.A.T.

REPLACEMENT TRIPLERS

PYE C72 SERIES
GEC 2028 SERIES
PHILIPS G8 SERIES
£3.00 + 30p V.A.T.

E.H.T. RECTIFIER STICKS

X80/150D
10p 1p V.A.T.

TRANSISTOR TUNER UNITS

VHF/UHF	£2.00	20p V.A.T.
6 Push Button VHF/UHF	£2.50	25p V.A.T.
6 Push Button UHF	£1.50	15p V.A.T.
300 Mixed Condenser	£1.00	10p V.A.T.
350 Mixed Resistor	£1.00	10p V.A.T.
100 w/w Resistor	£1.00	10p V.A.T.
40 Mixed Pots	£1.00	10p V.A.T.

PRINT PANELS WITH TRANSISTOR
& RESISTOR & CONDENSER & RELAYS
£1.00 10p V.A.T.

Money returned if not completely satisfied

COLOUR PANELS
TRANSISTORS RESISTOR CONDENSER
ETC.
£1.00 10p V.A.T.

I.F. PANELS with Transistor & Resistors
10p 1p V.A.T.

SOUTHEND ELECTRONICS

240 RAYLEIGH RD., EASTWOOD,
LEIGH-ON-SEA, ESSEX
Telephone: Southend 521363
P.P. PAID UK ONLY

Reg: Office Only—No Personal Callers Please

NEW
ALL
SILICON!



PRACTICAL
WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, supplied with de-luxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.

Price: Standard Kit£7.97 U.K. Post Free
De-Luxe Kit£9.62 U.K. Post Free

Quantity Discounts:
Trade and Overseas 1-5 Nett 6-9 Less 10%
Enquiries Invited 10-49 Less 15% 50-99 Less 20%
Mail Order Only 100-999 Less 25% 1000 up Less 30%

ALL PRICES INCLUDE VAT

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.

DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34385

ELECTROLYTIC CAPACITORS UF/V 2000/50, 2500/50, 5000/50, 10,000/50, 12,500/50. All at 5p each, post paid.

SPECIAL OFFER: WIRE-ENDED METALLISED FILM CAPACITORS 2-2UF 63V 15p, 4UF 63V 20p, 8UF 63V 25p, 10UF 63V 25p. All post paid.

SOKSOL DE-SOLDER KIT: includes 20ft special copper braid, chemical solution and instructions £1, post 15p.

DELCO-REMY 12 Volt Car-Horn Relays 50p, post paid.

SUBMINIATURE PLUG-IN CRYSTALS for radio control. 26 985MHz and 27-025MHz 70p each, post paid.

AMERICAN DYNAMOTOR ROTARY TRANSFORMERS. Input 27 Volts D.C. Output 285 Volts D.C. at 75 M/A £1 00, post 30p.

PLESSEY VIBRATORS Type 1214 50p, post paid.

ADD 10% V.A.T.

SEE OUR OTHER ADVERTISEMENTS IN
RADIO & ELECTRONICS CONSTRUCTOR

ELEKON ENTERPRISES

224a St Paul's Road, Highbury Corner, London N.1
Telephone 01-359 4224

LEARN RADIO & ELECTRONICS AT HOME

No knowledge needed—
build as you learn with
the exciting new
'Technatron' kit. No
Extras. Tools, transistors,
meter etc. All supplied.
You could build a
radio in weeks.

SEND FOR FREE 76 PAGE GUIDE TO RADIO/TV,
ELECTRONICS, C & G, TELECOMMS ETC.


Dept. BPW22 Aldermaston Court, Reading RG7 4PF

Name.....

Address.....

Age..... CV BPW22

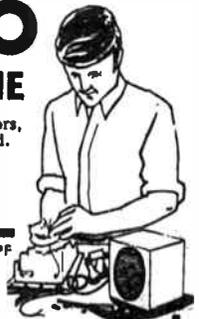BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



SPECIAL INTRODUCTORY OFFERS—IMPORTER TO CONSUMER!

ALL NEW GOODS—FULLY GUARANTEED—PLEASE ADD 10% V.A.T. TO TOTAL ORDER INCLUDING P. & P.

HILLS HEADPHONE JUNCTION BOX MODEL JB-3

Designed to connect headphone to amplifier previously not fitted with headphone socket, or alternatively for remote switching 3 position switch allows instant switching between speakers and headphones or both simultaneously.

Rec. Retail **OUR PRICE** £1.25 P. & P. 15p

"HOMER" INTERCOM

One of the leading makes. Ideal for home, office, factories, etc. This 2-station intercom includes volume control and on-off switch. Supplied with 66ft. cable and batteries.

Rec. Retail **OUR PRICE** £2.75 P. & P. £3.50

HILLS DYNAMIC HEADPHONE MODEL H-707 VS DE-LUXE

An extremely high quality headphone supplied with Padded Headphone and Earcups together with SLIDER volume controls for precise listening levels. Specially offered at an unbeatable price. 8 ohms 20-20,000Hz.

Retail Price **OUR PRICE** £5.75 P. & P. 25p

HILLS DYNAMIC HEADPHONE MODEL H-101 VSM

Offered at a remarkably low price, supplied with padded Headband and Earcups, adjustable volume controls with stereo and mono switch, 8 ohms imp. 30-18,000Hz.

Rec. Retail **OUR PRICE** £3.75 P. & P. 25p

CAR STEREO SPEAKERS MODEL CRB-200

These dual purpose Car Speakers can be used for either shelf mounting or converted to door mounting. 5in 5 watt Speakers ensure a brilliant audio performance.

Rec. Retail **OUR PRICE** £3.50 *Per pair P. & P. 25p

ANTEX SOLDERING IRONS

	REC.	OUR PRICE
CCN240 15 watt	2.15	£1.60
X25 25 watt	1.93	£1.40

Ferranti Radio Chip ZN414. **OUR PRICE** £1.10. P. & P. 5p.
Hills Coiled Headphone Extension Cable. 15ft. Rec. Retail £2.25. **OUR PRICE** £1.45. P. & P. 10p.

PLINTH AND COVER FOR GARRARD SP-25 III BSR MP-60.

OUR PRICE £2.75. plus 65p P. & P.
ELAC SPEAKER, 8in 8 ohm CERAMIC and TWEETER. £2.70, plus 20p P. & P.
OTHER ITEMS AT BARGAIN PRICES OFFERED IN OUR AUDIO COMPONENTS CATALOGUE. PLEASE WRITE FOR A FREE COPY (ENCLOSING 3p STAMP).

HILLS COMPONENTS LTD.

DEPT. (PW-12), UNIT No. 6, MELNITE INDUSTRIAL ESTATE, BRITON ROAD, WATFORD, HERTS. WD2 5SL. Tel. Watford 2711

FAN/BLOWER

Precision-built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60MA on run. Size: 5 1/2" dia. x 2 1/2" deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at £3. P. & P. 20p. Similar unit to above but 7 1/2" dia. x 3" deep. £4.50. P. & P. 25p.

SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1 min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.30. 15p P. & P.

GEARED MOTORS

"Parvalux" Reversible 100 rpm geared motor. Type SD14, 230/250v. AC, 22 1/2in. 1/2" spindle. 1st class condition. £7.50 each. 50p P. & P. Also limited number only as above. BRAND NEW. £12.50 each. P. & P.

REVERSIBLE Parvalux type SD19, 240v. AC. 30rpm. 40 lbs/in. Variable angle drive shaft. ABSOLUTELY AS NEW. £6.30. P. & P. 50p.

SHADED POLE Mains motor. 1 1/2" x 1 1/2" x 2" high. Double ended 1/2" shaft projecting 1 1/2" each side of motor. £1. P. & P. 20p.

OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC, 28rpm **NEW HIGH TORQUE**, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" and spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.

SPIT MOTOR

5 1/2rpm. 2 1/2" x 1 1/2" x 6 1/2" high. 240v. AC. Shaft 1/4" o.d. 1 1/2" length with hexagon socket inside. £1.80. P. & P. 30p.

AMPEX 7.5v. DC MOTOR

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stalls load at 500ma. Draw 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression. 1/2" dia. x 1 1/2" spindle, motor 3" dia. x 1 1/2" Original cost £16.50. **OUR PRICE** £3. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available. 75p each. FREE P. & P.

"DAVENSET" MAINS SOLENOID

1" travel, 8lbs. pull (approx.). Size: 2 1/2" long x 2 3/16" x 2" high. Similar in appearance to "SORENG". £1.50. P. & P. 20p.

MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm. 2 1/2". 240V AC. Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.

Solenoids by Westool

240 AC type MM6. 3lb. pull. 2 1/2" x 1" x 1 1/2". Travel 1". 85p each. P. & P. 10p.

240AC type MM4. 2lb. pull. 1 1/2" x 1 1/2" x 1". Travel 1/2". 60p each. P. & P. 10p. Quantity discounts: 10-50 10%. 50 upwards 25%.

"DECCO" MAINS SOLENOID

Compact and very powerful. 16lb. pull. 1/2" travel which can be increased to 1" by removing captive-end-plate. Overall size: 2" x 2 1/2" x 2 1/2" high. £2. P. & P. 20p.

MAINS SOLENOID by MAGNETIC DEVICES LTD.

A (beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/2" x 1 1/2". Pull is approximately 2lbs., plunger travel 1 1/2". Fixing eye takes up to 4" bolt, plunger non-captive. NEW in original maker's boxes. £1 P. & P. 20p. Large number available, special price for quantity.

"CROUZET" MOTORS 3 RPM

Type 965 115/240v. 50Hz. 40w. Stoutly constructed. 2 1 1/16" dia. x 3 1/2" long plus spindle. 1" x 1/2" dia. Anti-clock. £3 each P. & P. 25p.

"RE CIRK IT" Mains 10amp cut-out

By "Neimann Electric" Germany. Eliminates fuses. Size: 2" x 3" x 1 1/2" deep. 90p each. P. & P. 10p. 10 or more 70p each. P. & P. 20p.

UNLESS OTHERWISE STATED

all items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50. C.W.O., please. Company orders under £2.50. Surcharge 60p unless C.W.O.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 1/4". (80 DB) 3/4" x 5/32" x 3/8". Ex-equipment, all tested. £1.20 each. P. & P. FREE.

PLUG-IN RELAYS by SCHRACK (PERSPEX ENCLOSED)

OCTAL (2 c/o) 6 amp contacts at following voltages: 48 D.C., 60 D.C., 60 A.C., 110 D.C., 380 A.C. **PRICE EACH 90p**

11 pin (3 c/o) 6 amp contacts: 12 A.C., 48 D.C., 48 A.C., 60 A.C., 60 D.C., 110 D.C., 115 A.C., 240 A.C. **PRICE EACH £1**

RA and RN Series (4 c/o) 3 amp Gold Plated Contacts. Handsome modern construction 1 1/2" x 3/4" x 1 1/2" high. Following voltages: 6 A.C., 12 A.C., 24 A.C., 48 A.C., 48 D.C., 60 A.C., 110 D.C., 115 A.C., 120 A.C. **PRICE EACH 80p**

Base sockets for all above types 10p
Please add 10p towards P & P on all orders.

From JAPAN, TAKAMISAWA Perspex enclosed relays. Type MQ 308. 24V. DC. 600 ohms (4 c/o). Complete with base socket. 80p P. & P. 10p.

SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!
A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1/2 amp at 240v. Size: (approx.) 1 1/2" x 1 1/2" x 1 1/2" dia. Ideal for burglar alarms, security systems, etc., and wherever non-mechanical switching is required. 10 for £1.80; P & P 15p. 50 for £9; 100 for £15. FREE P & P over 10.

NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with wovon glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant. Ideal for P.C.'s, etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12", 24" x 12", 24" x 24". FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

TANGENTIAL HEATER

Silently driven by shaded pole Mylex motor, powerful and smooth running with aluminium impeller (outlet 5/8" x 1 1/2"). Mains voltage PLUS matching heater unit with spiral element. May be switched for 500 or 1,000w. £1.60. P. & P. 30p.

PLEASE ADD 10% FOR V.A.T. ON ALL PRICES SHOWN INCLUDING P & P

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY £1-05

POST & PACKING 45p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 27½p

POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	55p
B81	10	Reed Switches, 1" long, 1" dia. High Speed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	55p P & P 15p
H4	250	Mixed Resistors. Approx. quantity counted by weight	55p P & P 15p
H7	40	Wirewound Resistors. Mixed types and values.	55p
H9	2	OC71 Light Sensitive Photo Transistor	55p
H28	20	OC2001/2/3 PNP Silicon uncodcd TO-5 can	55p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8-43V.	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	55p
H36	30	Short lead Transistors, NPN Silicon Planar types.	55p
H39	6	Integrated Circuits, 4 Gates BMC 962, 2 Flip Flops BMC 945	55p
H40	20	BFY50 2, 2N696, 2N1613 NPN Silicon uncodcd TO-5	55p
H41	2	Sil Power transistors comp pair BD131/132	55p

UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B85	100	Sil. Diodes sub.-min. IN914 and IN916 types	55p
H46	40	250mW Zener Diodes DO-7 Min. Glass Type	55p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10 each



OVER
1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Silicon planar plastic transistors. Unmarked, untested factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.
Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for £3-30, 1,000 for £5-50, 10,000 for £44 P. & P. 11p/1,000.

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.

TYPE "B" PNP Silicon, plastic encapsulation.

TYPE "E" PNP Germanium AF or RF.

TYPE "F" NPN Silicon plastic encapsulation.

TYPE "G" NPN Silicon similar ZTX 300 range

TYPE "H" PNP silicon similar ZTX 500 range

RELAYS FOR
8 VARIOUS TYPES £1-10

P & P 27½

Our famous PI Pak is still
leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors. Please ask for Pak P.I. Only 55p. 11p P & P on this Pak.



A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board, A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television.

This complete kit of parts costs £3-85, post paid.

A MUST for Colour T.V. Alignment.

ELECTRONIC TRANSISTOR IGNITION

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features—

Translator and conventional switchability, burglar proof lock up and automatic alarm, negative and positive compatibility. This project was a "star" feature in the September edition of "Electronics Today International" magazine. Our kit is recommended by the ETI magazine.

Complete kit including p & p £7-92
Ready built and tested unit £3-02 extra.

FREE CATALOGUE FOR

TRANSISTORS,
RECTIFIERS,
DIODES,
INTEGRATED
CIRCUITS,
FULL PRE-PAK
LISTS



PLASTIC POWER TRANSISTORS

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shattering low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms. Range 1. VCE. Min 15. HFE Min 15.

40 Watt	1-12	13-25	26-50
90 Watt	21p	20p	18p
26p	24p	22p	

Range 2. VCE. Min 40. HFE Min 40.

40 Watt	1-12	13-25	26-50
90 Watt	31p	31p	29p
38p	36p	33p	

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 15p. Wall Chart 18p.

LOW COST DUAL IN LINE I.C.

SOCKETS

14 pin type at 16p each } Now new low profile
16 pin type at 18p each } type

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I. Transistor Equivalents and Substitutes 40p

This includes many thousands of British U.S.A., European and C.V. equivalents.

The Iltife Radio Valve & Transistor Data Book 9th Edition; p. & p. 231p. 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications

N.B. Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER

PLEASE. Add 11p post and packing per order

OVERSEAS ADD EXTRA FOR POSTAGE


BUY THESE GOODS WITH ACCESS.

BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF ON SEA, ESSEX S50 9DF
TELEPHONE: SOUTHEND (0702) 46344

CO. REG. No. 820919

NELSON-JONES FM TUNER KIT

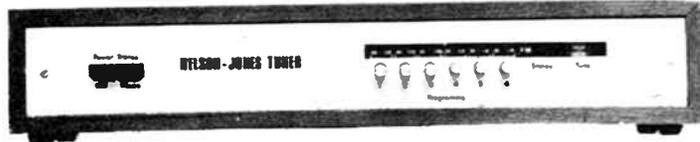

VARICAP TUNING
as in 'W.W.' June '73

Now available to readers of 'Practical Wireless'. The Nelson-Jones tuner uses dual gate MOSFET's in the RF stages, integrated circuits and ceramic filters in the IF stages, for very high performance and quick assembly. Do not confuse with tuners using only bipolar transistors and IF coils!

Tuning is accomplished by variable capacitance diodes and a Push Button Unit with 6 positions. AFC disable is incorporated as well as a pointer for each button showing tuning position in the range 87.5-108MHz, i.e. each 'button' is fully tuneable simply by turning.

Our complete metalwork system is supplied with nuts, bolts, board standoffs, push button mains on/off and stereo mute assembly, sockets, fuse and holder. Printed and Anodised Front Panel and Veneered Teak case. Power supply kits are supplied with complete kits of parts, or separately. LED tuning ind. is also supplied.

Prices for complete kits start at £23.95 + 50p pp. + VAT for mono tuners, (phase locked decoders are also available to fit in the cabinet). Please send large SAE for complete details of special offers and our complete lists.

GREEN LED's—the latest for 'stereo' lamps. 1-9 69p, 10+ 59p.


TEXAN AMPLIFIER

The Cabinet of the Nelson-Jones Tuner is specially designed to match the Texan amplifier cabinet, see photographs, so that owners of Texan's are assured of compatibility, both in superb performance and appearance.

Texan amplifier kits are available at £28.50 + 50 p pp. + VAT.

Worried about tuner alignment? then let our alignment service take over.

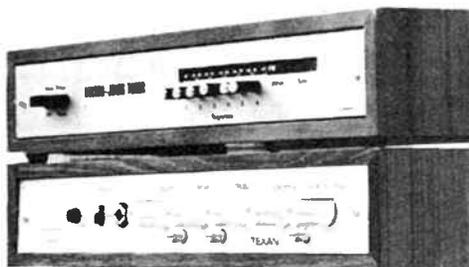Telephone queries. We have REAL ENGINEERS, not salesmen, to answer queries.



INTEGREX LIMITED, Dept. P.W., P.O. Box 45, Derby, DE1 1TW. Tel. Repton (028389) 3580

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR.

Tel. 021-327 2339

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner. Light sensitive aerosol spray £1.98 plus Developer and Etchant 50p postage

NEWER THAN NEW! !!

Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.

75mm x 100mm 33p
150mm x 100mm 66p
150mm x 200mm £1.32

SILICON N.P.N.

Type	Volts	Frequency	Price	Type	Volts	Frequency	Price
BC 108	30	150 MHz	10p	2N 697	60	40 MHz	12p
BC 109	30	150 MHz	10p	2N 709	15	900 MHz	30p
BF 179	225	125 MHz	40p	2N 718	60	60 MHz	12p
BF 180	30	625 MHz	25p	2N 753	25	250 MHz	12p
BFW 58	80	80 MHz	15p	2N 744	20	300 MHz	12p
BFX 43	30	500 MHz	20p	2N 1613	75	60 MHz	17p
BFX 98	40	50 MHz	17p	2N 2220	60	250 MHz	15p
BFY 53	30	50 MHz	10p	2N 3053	60	100 MHz	17p
BSX 19	40	500 MHz	10p	2N 3707	30	12p	
BSX 67	30	200 MHz	12p	2N 5179	20	900 MHz	40p

SPECIAL OFFER

Uni-Junction Transistor Similar to 2N2646—25p

POSTAGE (MINIMUM) 20p PER ORDER

ALL GOODS 10% V.A.T.

MICROWAVE DEVICES

CL 8300	Gunn effect oscillator	9.4 GHz	£40
CL 8370	ditto	9.5 GHz	£10
CL 8380	ditto	10.5 GHz	£10
CL 8390	ditto	11.5 GHz	£10
CL 8430	ditto	9.35 GHz	£40
CL 8450	ditto	9.35 GHz	£40
CL 8470	ditto	9.35 GHz	£40
BXY 27	Varactor Diode. "S" Band. Cut-off	70 GHz	£1
BXY 28	Varactor Diode. Cut-off	100 GHz	£1
BXY 32	Frequency Multiplier. "X" Band	150 GHz	£1
BXY 35A/C	ditto	25 GHz	£1
BXY 36C/D	ditto	75 GHz	£1
BXY 37C/D	ditto	100 GHz	£1
BXY 38C/E	ditto	120 GHz	£1
BXY 39C/D	ditto	150 GHz	£1
BXY 40D/E	ditto	180 GHz	£1
BXY 41C/D/E	ditto	200 GHz	£1
CV 7777 (AAY 51)	Microwave Mixer Diode	18 GHz	£2
CAY 10	Microwave Detector Diode	250 GHz	£5
AEY 13	Microwave Tunnel Diode	6 GHz	£5
AEY 16	ditto	10 GHz	£10
AEY 17	Microwave Detector	18 GHz	£3
AEY 31A	ditto	18 GHz	£3
BAW 95	Schottky Barrier Diode	12 GHz	50p

SILICON P.N.P.

Type	Volts	Frequency	Price
BCY 71	45	200 MHz	12p
BFS 92	100	70 MHz	20p
BFS 95	40	70 MHz	17p
BFX 12	25	210 MHz	10p
2N 2906	60	200 MHz	15p
2N 3702	40	100 MHz	11p
2N 3703	50	100 MHz	12p

HIGH FREQUENCY. POWER

BFR 64	40	1,200 MHz	£1
BLY 89A	35	850 MHz	£5
BLY 93A	60	500 MHz	£5
BLY 218	36	1,200 MHz	£2
2N 709	15	800 MHz	15p
2N 3926	36	250 MHz	£1

GERMANIUM P.N.P.

Type	Volts	Frequency	Price
ACY 44	50	1 MHz	10p
ACY 26	80	75 watts	£1
AF 124	20	75 MHz	20p
AFY 19	32	350 MHz	20p
ASY 32	25	5 MHz	10p
ASZ 21	15	450 MHz	20p
GET 113	32		10p
GET 120	32	2 watts	10p
OC 123	50	1 MHz	10p
OCY 70		Light-sensitive	20p
2N 1307	30	10 MHz	15p
2N 1309	30	15 MHz	15p
2N 443	60	150 watts	£1

£1 100 1/2 WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

POSTAGE 20p | PACK No. 1

£1 1 VERO-BOARD CUTTER
5 1/2 in. x 1 in. x .15 BOARDS
50 SQ. INS. "ODD PIECES"
VERO

POSTAGE 20p | PACK No. 3

£1 20 ASSORTED UNUSED
MARKED, TESTED
TRANSISTORS
BC108 ETC.

POSTAGE 20p | PACK No. 5

£1 6 COMPUTER PANELS
CONTAINING MASSES OF
DIODES, TRANSISTORS,
INDUCTORS, RESISTORS
& CAPACITORS

POSTAGE 27p | PACK No. 7

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

POSTAGE 20p | PACK No. 2

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

POSTAGE 20p | PACK No. 4

£1 1 TRANSISTORISED
SIGNAL TRACER KIT
1 TRANSISTORISED
SIGNAL INJECTOR KIT

POSTAGE 20p | PACK No. 6

£1 100 RESISTORS
100 CAPACITORS
(ASSORTED TYPES)

POSTAGE 20p | PACK No. 8

RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are—
2 track record playback heads 50p each
4 track record playback heads 72p each
Erase heads are also available separately—2 track 33p—4 track 55p
MU-metal mounting shields 39p each.
2 track heads already fixed on heavy mounting plate with shield £1.22.




DRILL CONTROLLER NEW IKW MODEL

Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.35.
Made up model also available. £2.95.

MIGHTY MIDGET

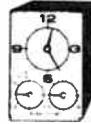Probably the finest possible radio, as described in *Practical Wireless*, January 73. All electronic parts £2.20 post paid.



TIME SWITCH

Smith's mains driven clock with 16 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn of burglars, keep pets warm, halve your heating bill, etc. £1.95.

I CHIP RADIO

Ferranti's latest device ZN414—gives results better than superhet. Supplied complete with technical notes and circuits. £1.38 each. 10 for £11.11.

HI-Q TUNER COMPONENTS


For experimenting with the ZN414.
KIT NO. 1. Pleassey Miniature Tuning Condenser with built-in LW switch and 3" Ferrite slab and litz wound MW coil, 72p.
KIT NO. 2. Air spaced tuning condenser 6" ferrite rod litz wound MW and LW coils, 94p.
KIT NO. 3. Air spaced TC with slow motion drive 8" ferrite rod, with litz wound LW and MW coils, £1.10.
KIT NO. 4. Permeability tuner with fast and slow motion drive and LW loading coils, 50p.

AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £2.35 plus 25p post and insurance.

TELESCOPIC AERIAL

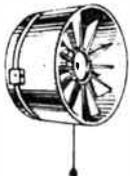for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw, 48p. KNUCKLED MODEL FOR P.M. 65p.



EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets, £2.75 plus 20p post and ins.

MAINS OPERATED SOLENOIDS

Model 772 — small but powerful lin. pull approx. size 1 1/2 x 1 1/2 x 1 1/2in. 60p.
Model 4001/—lin. pull. Size 2 1/2 x 2 x 1 1/2in. 88p.
Model T11—1 1/2in. pull. Size 3 x 2 1/2 x 2in. £1.98 plus 20p post and insurance

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PPI, PPS, PP4, PP6, PPT, PPS, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1.10 plus 20p postage.

DESK TELEPHONES

Ex G.P.O. Black standard model with dialling disc but no internal bell. Supplied with connection diagram £1 each. Ditto with bell but without dialling disc £1.25 model as illustrated with bell and dial £1.50 each plus 50p post for single then 65p per pair.



SMOKE WILL KILL—GAS WILL KILL—FIRE WILL KILL

But, if you install SAGA (our smoke and gas alarm) your family will have the latest electronic protection against these killers.
SAGA uses a fantastic electronic sensor which "smells" smoke and gas and sounds the alarm immediately. In a neat case measuring approx. 5" x 3 1/2" x 2 1/2", it has its own internal alarm, also a connector for additional bells. You just plug it in to the mains and hang it near the ceiling. SAGA uses so little electricity that it will hardly move the meter, leave it on always to give night and day protection. £2.95 plus 30p post or Kit of Parts £5.95. Battery Model Kit only £4.95.



CENTRIFUGAL FAN

Mains operated, turbo blower type. Pressed steel housing contains motor and impeller. Motor is 1/10th h.p. giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2 in. wide x 12 in. dia. outlet into trunking 10 1/2 x 4 1/2 in. £2.55 plus £1 post and insurance.

STANDARD WAFER SWITCHES

Standard size 1 1/2" wafer—silver-plated 5 amp contact, standard 1/2" spindle 1/2" long—with locking washer and nut.


No. of Poles	2way	3 way	4 way	5way	6way	8way	9way	10way	12way
1 pole	44p	44p	44p	44p	44p	44p	44p	44p	44p
2 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
3 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
4 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
5 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
6 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
7 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
8 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
9 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
10 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
11 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p
12 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p

TWENTYLITE

Fluorescent lightin' units with polyester cbsoke and finished white enamel, 2ft. model. Ideal kitchen, bedroom, hall-way, porch, lift, etc. with tube. Assembled ready to install. Price £2.50 + 25p p. & p.

RADIO STETHOSCOPE

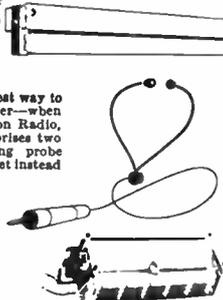Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2.20—twin stethosheet instead of earpiece 88p. extra—post and ins. 20p



TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW. element and 1kW. element allowing switching 1, 2 and 3kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £3.55. 2kW. Model as above except 2kW. £2.75. Don't miss this. Control Switch 88p. P. & P. 40p.

ROOM THERMOSTAT. Made by the famous Smiths Company. 15 amp. at 250v. Elegant white and beige case, size 4 1/2 inches long by 1 1/2 square approx. Adjustment is by slider (lockable) adjusts through range 30°—90° F. Special Snip price £1.65

CAPACITOR DISCHARGE CAR IGNITION

ELECTRONIC IGNITION
This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price £2.55 plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board, etc. £7.95.

24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 6A changeover contacts will switch circuit on or off during these periods. £2.75 post and ins. 25p. Additional time contacts 55p pair.

PHOTO ELECTRIC KIT

Contains photo cell, relay, transistor and all parts to make light operated switch. £1.75 plus 20p post and ins.

MULLARD UNILEX STEREO AMPLIFIER

We demonstrate these daily and almost always a sale results; it really is a cracking amplifier. Only Mullard with their know how could have made it possible at this low price. SPEC: Mains operated, 4 watts music or speech per channel. Double wired power supply eliminates cross talk. Harmonic distortion less than 2%. Frequency response 50Hz-16KHz. Inpnt suitable for pick-up tuner or microphone. 6 month guarantee. Only £11.30 post paid, pair of ohm speakers £3.30.



NEW ITEMS THIS MONTH

White Rocker Switches. Four types available, all snap in fixing through oblong hole approx. 1" x 1/2", all rated at 10 amps AC. All have white rocker except 83, which is amber.
Our ref RS 81, push to make, spring return, 14p.
Our ref RS 82, push to break, spring return to on, 14p.
Our ref RS 83, change over contacts, luminous rocker, 28p.
Our ref RS 84, change over contacts, normal rocker, 16p.

Rocker Switches. 15 amp Britnac panel mounting, holic size 1 1/2 x 1. Our ref RS 85 price 11p each. 5 amps made by Meem, their type ref 1600, our ref RS 86, price 11p each.

Miniature Hand Microphone. Dynamic, for tape recorders but equally suitable for amplifiers, good quality with lead and plug, price £1.37.

Open Coil Relays. All with 10 amp change over contacts, all brand new.
Our ref REL 81, 12 volt DC coil, double pole, 44p.
Our ref REL 82, 110 volt AC coil, treble pole, 44p.
Our ref REL 83, 250 volt AC coil, treble pole, 65p.

Photo Transistor Bargain. First class maker but slightly reject, covered, however, by our normal six month guarantee. These respond to light or infra red. Will work a burglar alarm, make detector counter etc. Price 22p complete with three circuits.

Mains Flex. Padded, circular, cotton covered overall. Six amp (23-38) 100 yard coils. Price £2.75 plus 50p post.

Screened Cable. 70076 core suitable for pick up or mike lead or for inter-connecting amplifiers. 10 metres, 83p.

Stesso Pre-amplifier Module. Mullard ref LP 7182/2—transistors and all ancillary components mounted on PC board, £1.32 with connection dig.

GOOD COMPANION I.C. VERSION

We can now offer these again in I.C. version using Ferranti ZN414 and Mullard AF Module 1172. Cabinet size approx. 11" wide x 8" high x 3" deep. Complete assembly instruction. Excellent tone wood cabinet, £5.75 plus 25p post and insurance.

MOTORS FOR £1.50

As used in racing cars and power models. All battery operated and reversible.



RESISTANCE WIRE

Mainly Nickel Chrome. (Resistances 74 ohms per metre down to 1 ohm per metre). Price 15p per oz. on catch weight reels—so please send an open cheque—we will send the smallest reel over the quantity you want and make your cheque out for the quantity sent. You return the "over" amount within 1 month and we will refund for the amount you return. 25p returnable charge for reel.
Special Offer, 1 yard of 1.1mm wire. This is almost exactly 1 ohm. 10p.

PC BOARD MARKER

Valve action fire tipped marking pen filled with black etch resist—its easy with this to make a perfect PC board, just draw straight on to the copper—allow 10 mins. to dry, then immerse in ferroc chloride or other etchant on removal the circuit stands in high relief, 99p.

8L103D. Pleassey IC, three watt amplifier which works with the Ferranti ZN414 to become probably the first two IC radio in existence, the circuit and constructional details appeared in September's *Practical Wireless*, so we can supply the 8L103D at £1.76, the ZN414 at £1.38, also most other items, send for PW IC radio parts list.

EDUCATIONAL KITS—all with pictorial instructions

With 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 44p each post paid. Special price for all 7 kits £2.00 with free balance kit.

KA2 Lens Kit. Eleven parts, concave lens, one convex lens, stage and slit frame, etc.
KA3 Water Pump Kit. Thirteen parts. Transparent so that operating parts may be observed. You can make Lift Pump, Force Pump and Force Pump with reservoir and nozzle.
KA4 Buzzer Kit. Eleven parts. Operation of buzzer seen.
KA7 Electro-Magnet Kit. Fifteen parts, includes compass, showing how magnetism works.
KA8 Current and Resistance Kit. Twenty-nine parts, including bench and light bulb. Learn "OHMS LAW", etc.
KA9 Bell Kit. Eight parts, including bell and push button switch. Build a complete electric bell.
KA10 Morse Key buzzer and bell kit. 25 part kit easy to construct, simple to operate.

TERMS: 10% discount if ten of an item ordered, send postage where quoted—other items, post free if order for these items is £6.00 otherwise add 20p.

J. BULL (ELECTRAL) LTD.

(Dept. P.W.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

Henry's

UK'S LARGEST RANGE OF TRANSISTORS, IC'S RECTIFIERS, ALL SEMICONDUCTOR DEVICES
BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL

FREE BOOKLET

All types of
TRANSISTORS — RECTIFIERS
BRIDGES — SCR'S — TRIACS
INTEGRATED CIRCUITS
F.E.T. — LIGHT DEVICES

OVER 1500 DIFFERENT DEVICES

ENTIRELY NEW 1973 EDITION

SEND FOR YOUR FREE COPY TODAY



More Devices
New Prices
New Ranges

This is a must for all

Semi-conductor Users

(ask for booklet No. 36)

INTEGRATED CIRCUITS VERY IMPORTANT. ONLY branded I.C.'s

are to the FULL manufacturers specifications. ALL others are not. Henry's sell only branded Integrated Circuits... From TEXAS... I.T.T. ... FAIRCHILD ... SIGNETICS. So why buy alternatives or under spec. devices when you can purchase the genuine article from us—ex stock... need we say more!



Type 1/11 12/29 30/99

SN7400N	0.20	0.18	0.16	SN7448N	1.50	1.27	1.13	SN74142N	2.88	2.88	2.52
SN7401N	0.20	0.18	0.16	SN7450N	0.20	0.18	0.16	SN74145N	1.44	1.44	1.26
SN7401AN	0.38	0.38	0.33	SN7451N	0.20	0.18	0.16	SN74147N	2.80	2.80	1.83
SN7402N	0.20	0.18	0.16	SN7453N	0.20	0.18	0.16	SN74148N	2.01	2.01	1.83
SN7403N	0.20	0.18	0.16	SN7454N	0.20	0.18	0.16	SN74150N	2.30	2.30	2.01
SN7403AN	0.38	0.38	0.33	SN7460N	0.20	0.18	0.16	SN74151N	1.15	1.15	1.00
SN7404N	0.24	0.21	0.18	SN7470N	0.30	0.30	0.27	SN74153N	1.09	1.09	0.95
SN7405N	0.20	0.18	0.16	SN7472N	0.38	0.38	0.34	SN74156N	2.30	2.30	2.01
SN7405AN	0.44	0.44	0.38	SN7473N	0.44	0.41	0.37	SN74155N	1.15	1.15	1.00
SN7406N	0.40	0.38	0.35	SN7474N	0.48	0.48	0.42	SN74156N	1.09	1.09	1.00
SN7407N	0.40	0.38	0.35	SN7475N	0.59	0.55	0.51	SN74157N	1.09	1.09	0.95
SN7408N	0.25	0.22	0.19	SN7476N	0.45	0.45	0.44	SN74159N	2.01	2.01	1.76
SN7409N	0.33	0.33	0.28	SN7480N	0.80	0.70	0.50	SN74160N	1.58	1.58	1.38
SN7409AN	0.44	0.44	0.38	SN7481N	1.25	1.10	0.95	SN74161N	1.58	1.58	1.38
SN7410N	0.20	0.18	0.16	SN7482N	0.87	0.80	0.72	SN74162N	1.58	1.58	1.38
SN7411N	0.25	0.23	0.21	SN7483N	1.20	1.10	1.00	SN74163N	1.58	1.58	1.38
SN7412N	0.28	0.28	0.25	SN7485N	1.87	1.87	1.63	SN74164N	2.01	2.01	1.76
SN7412AN	0.38	0.38	0.33	SN7486N	0.45	0.45	0.44	SN74165N	2.01	2.01	1.76
SN7413N	0.30	0.27	0.25	SN7489N	4.32	4.32	3.78	SN74166N	2.16	2.16	1.89
SN7414N	0.72	0.72	0.63	SN7490N	0.75	0.70	0.63	SN74167N	4.10	4.10	3.59
SN7416N	0.30	0.27	0.25	SN7491AN	1.10	1.00	0.90	SN74170N	2.88	2.88	2.52
SN7417N	0.30	0.27	0.25	SN7492N	0.75	0.70	0.63	SN74172N	5.76	5.76	5.04
SN7420N	0.20	0.18	0.16	SN7493N	0.75	0.70	0.63	SN74173N	1.66	1.66	1.45
SN7422N	0.28	0.28	0.25	SN7494N	0.85	0.80	0.75	SN74174N	1.80	1.80	1.57
SN7422AN	0.38	0.38	0.33	SN7495N	0.50	0.50	0.50	SN74175N	1.89	1.89	1.61
SN7423N	0.37	0.34	0.32	SN7496N	1.00	0.90	0.83	SN74176N	1.44	1.44	1.26
SN7425N	0.37	0.37	0.32	SN74100N	2.16	1.89	1.89	SN74177N	1.44	1.44	1.26
SN7427N	0.37	0.37	0.32	SN74104N	0.60	0.53	0.45	SN74180N	1.44	1.44	1.26
SN7428N	0.43	0.43	0.37	SN74105N	0.60	0.53	0.45	SN74181N	5.18	5.18	4.58
SN7430N	0.20	0.18	0.16	SN74107N	0.51	0.51	0.45	SN74182N	1.44	1.44	1.26
SN7432N	0.37	0.37	0.32	SN74110N	0.67	0.67	0.60	SN74183N	2.16	2.16	1.89
SN7433N	0.43	0.43	0.37	SN74111N	0.86	0.86	0.75	SN74185AN			
SN7433AN	0.57	0.57	0.50	SN74116N	2.16	2.16	1.89		2.16	2.16	1.89
SN7437N	0.43	0.43	0.37	SN74118N	1.00	0.90	0.83	SN74188N	6.48	6.48	5.67
SN7438N	0.43	0.43	0.37	SN74119N	1.92	1.92	1.68	SN74190N	2.80	2.80	2.01
SN7438AN	0.67	0.67	0.50	SN74120N	1.05	1.05	0.92	SN74191N	2.30	2.30	2.01
SN7440N	0.20	0.18	0.16	SN74121N	0.57	0.57	0.50	SN74192N	3.30	3.30	2.01
SN7441AN	0.55	0.79	0.73	SN74122N	0.80	0.80	0.70	SN74193N	2.30	2.30	2.01
SN7442N	0.85	0.79	0.73	SN74123N	1.44	1.44	1.26	SN74194N	1.72	1.72	1.51
SN7443AN	1.60	1.27	1.18	SN74125N	0.69	0.69	0.60	SN74195N	1.44	1.44	1.26
SN7444AN	1.60	1.27	1.18	SN74126N	0.69	0.69	0.60	SN74196N	1.58	1.58	1.38
SN7445N	2.16	2.16	1.89	SN74132N	0.72	0.72	0.63	SN74197N	1.58	1.58	1.38
SN7446N	2.16	2.16	1.89	SN74136N	0.68	0.68	0.55	SN74198N	1.16	1.16	2.77
SN7447AN	1.80	1.80	1.57	SN74141N	1.00	0.90	0.80	SN74199N	2.88	2.88	2.52

LARGER QUANTITIES AND O.E.M. PRICES PHONE (01) 723 3846. PRICING OF SN7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX. SN74... HIGH POWER... SN74... LOW POWER SERIES IN STOCK... SEND FOR LIST 36, FREE ON REQUEST. LOW PRICE SOCKETS 14 PIN... 15p 16 PIN... 17p. 8 PIN... 14p.

TRANSISTORS A SELECTION FOR FULL LIST SEND FOR BOOKLET 36 TODAY

AA213 10p	BC182 12p	BY213 35p	OC36 65p	ZTX108 10p	2N3714 1.60
AC107 35p	BCY32 85p	CO64 18p	OC44 18p	ZTX300 14p	2N3771 1.75
AC128 20p	BCY39 1.00	GET111 55p	OC45 18p	ZTX302 18p	2N3773 2.25
AC187 20p	BCY55 2.50	OC17 15p	OC71 15p	ZTX500 15p	2N3790 2.25
ACY17 35p	BCY70 15p	OC72 25p	OC72 25p	ZG301 40p	2N3819 35p
ACY39 65p	BCY71 20p	OC77 55p	OC77 55p	2N697 15p	2N3868 75p
AD149 50p	BCY72 13p	LM309K 25p	OC81 25p	2N706 10p	2N3903 15p
AD161 30p	BD124 80p	OC81 1.97	OC83 20p	2N930 20p	2N4002 14p
AD162 39p	BD131 45p	MAT121 25p	OC140 65p	2N987 45p	2N4126 15p
AF117 20p	BF116 22p	MJE340 50p	OC170 25p	2N1132 25p	2N4871 35p
AF118 50p	BF180 33p	MJE520 65p	OC200 55p	2N1304 22p	2N5457 85p
AF139 33p	BF194 13p	MJE3053 50p	OC202 90p	2N1613 20p	2N8001 3.00
AF196 40p	BFX13 25p	MFF105 75p	OC271 10p	2N1671 1.00	2N8026 8.00
AF239 44p	HF36 55p	MFF105 45p	OC812 55p	2N2147 75p	2N8303 7.00
AY827 30p	BFX88 22p	NKT217 45p	ORP60 45p	2N2160 69p	40250 45p
BA115 10p	BFY50 20p	NKT404 60p	P346A 20p	2N2926 10p	40361 45p
BA X13 5p	BFY51 20p	OA5 60p	TIL209 25p	2N3053 20p	40362 40p
BC107 12p	BFY64 45p	OA81 10p	TIP29A 49p	2N3054 45p	40408 50p
BC108 12p	BFY90 75p	OA200 80p	TIP30A 59p	2N3055 45p	40486 75p
BC109 12p	HF36 55p	PA202 12p	TIP31A 61p	2N3440 65p	40533 1.70
BC109C 14p	BFX20 65p	OC18 85p	TIP41A 74p	2N3442 1.10	40430 85p
BC113 16p	BU105 2.20	OC20 1.25	TIP42A 90p	2N3525 80p	
BC147 12p	BY100 15p	OC28 65p	TI843 25p	2N3614 59p	
BC169C 14p	BY127 15p	OC35 55p	V405A 25p	2N3702 11p	

TBA800 5 WATT I.C.
 Suitable alternative to SL403D. 5/30 volt operated. 8/16 ohm 5 watt output.
 With circuits and data £1.50



Sinclair IC12
 with circuits and data. 6 watt IC with printed circuit board
 28 volt operated £1.80




ZN414 IC
 Integrated circuit radio as featured by many magazines (Pw Jan. 73 Reprint)
 (Ref. No. 19 for 19p) £1.20




Toshiba Power and Preampifier modules
 TP0013P 20 watt Power amplifier 22-0-22 or single 45 volts operated £4.57



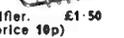
TG0014P Stereo
 two channel preamplifier. £1.50 (circuit book No. 42 price 10p)



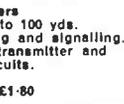Ultrasonic Transducers
 Operate at 40Khz up to 100 yds. Ideal remote switching and signalling. Complete with data transmitter and receiver new I.C. circuits.
 Per pair £5.80
 TA950 IC with socket £1.80



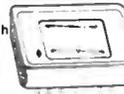3015F 7 SEG.
 I.C. size complete with data price £2 each or 4 for £7 (digital clock circuits ref. No. 31, 15p)



TRANSISTORS SPECIAL OFFER

2N3055	25 47p ea	25 15p ea
100 42p	100 13p	
500 39p	500 12p	
1000 34p	1000 10p	

BY127	25 12p ea	OC35	25 46p ea
100 10p	100 9p	100 42p	
500 8p	500 8p	500 38p	
1000 8p	1000 8p	1000 34p	

ZENER DIODES
 400 m/w BZY88/BZX83. From 3 volt - 33 volts 10p each

1-3 watts 5% Miniature Tubulars IN4700 series. From 3 volt - 33 volt 18p each.

10 watts. Std Molding. ZS series 6 63 volts 100 volts 5% 40p each.

SILICON RECTIFIERS
 1 amp series IN4001 to IN4007 From 6p ea

1.5 amp PL4001 to PL4007 From 8p ea
 3 amp PL7001/IN5400 From 14p ea
 Send for full list 36

MORE OF EVERYTHING AT HENRY'S
 See pages 499-501, and Back Cover of this magazine.
BEST VALUE

TRIACS - Std. mounting with accessories

3 AMP RANGE

Type	P.I.V.	Price ea.
SC35A	100v	80p
SC35B	200v	85p
SC35D	400v	85p
SC35E	500v	£1.20

6 AMP RANGE

Type	P.I.V.	Price ea.
SC40A	100v	90p
SC40B	200v	95p
SC40D	400v	£1.20
SC40E	500v	£1.50

10 AMP RANGE

Type	P.I.V.	Price ea.
SC45A	100v	£1.05
SC45B	200v	£1.15
SC45D	400v	£1.45
SC45E	500v	£1.85

15 AMP RANGE

Type	P.I.V.	Price ea.
SC50A	100v	£1.45
SC50B	200v	£1.85
SC50D	400v	£1.95
SC50E	500v	£2.25

TRIACS - Additional Types
 40430 TRIAC (T068) 85p
 40669 TRIAC (Plastic) 90p
 40486 TRIAC (T05) 75p

NEW RANGES BRIDGE RECTIFIERS

FEATURES SMALL SIZE AND LOW COST. Sizes are approx. **250MA QUARTER AMP** B025/05 50 PIV 16p
825/100 100 PIV 18p
 1/2 x 1/4" dia.

1 AMP P.I.V.
 B05/05 50v 20p
 B05/10 100v 22p
 B05/20 200v 23p
 B05/40 400v 25p
 B05/60 600v 27p
 1/4 x 1/4" dia.

2 AMPS P.I.V.
 B10/05 50v 25p
 B10/10 100v 25p
 B10/20 200v 28p
 B10/60 600v 30p
 1/4 x 1/4" dia.

Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS
 IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS
 You need a catalogue! 55p post paid complete with Discount Vouchers



UK's
**LARGEST RANGE
 OF KITS &
 GADGETS**

TEST EQUIPMENT

MULTIMETERS

(carr. etc. 30p)	
200H (M210) 20K/Volt Slimline with case	4-95
TLH33D 2K/Volt Robust with case	4-95
U437 10K/Volt Steel case. AC up to 40 KHz	4-95
U4324 20K/Volt with AC current ranges	8-00
AF105 50K/Volt with Leather case	9-50
U4313 20K/Volt AC current. Steel case	10-50
U4341 Plus built in transistor tester	10-50
Model 500 30K/Volt	9-95

OTHER EQUIPMENT

SE250B Pocket Signal Injector	1-90 carr. 15p
SE500 Pocket Signal Tracer	1-50 carr. 15p
TE15 Grid Dip meter 40kHz-280MHz	13-45 carr. 30p
TE40 AC Millivoltmeter 1-2mHz	18-75 carr. 35p
TE65 28 Range valve voltmeter	19-25 carr. 40p
TE20D 120kHz-500mHz RF Generator	16-95 carr. 40p
TE22D 20Hz-200kHz Audio Generator	18-75 carr. 40p
SE350A Deluxe Signal Tracer	9-95 carr. 20p
SE400 Vols/ohms/R-C sub./RF field/RF gen.	11-25 carr. 20p

New Revolutionary Supertester 680R


Accessories	680R Multi-tester	18-50
	Transistor tester	11-00
	Electronic voltmeter	18-00
	Amplclamp	11-95
	Temperature probe	11-95
	Guess meter	11-95
	Signal injector	5-95
	Phase Sequence	5-95
	EHT Probe	5-95
	Shunts 25/50/100A	4-50

A SELECTION OF INTERESTING ITEMS

C3025 Compact transistor tester	5-50 p & p 15p
E1300 Mono mag. cart. preamp.	1-95 p & p 15p
E1310 Stereo mag. cart. preamp.	4-95 p & p 25p
Easiphone telephone amplifier	6-15 p & p 25p
LD1203 Teleamp. with PU coil	3-60 p & p 20p
LL1 Door Intercomm. and chime	11-95 p & p 25p
Chattalite (lights as you talk)	13-90 p & p 20p
1 Kw Dimmer/Controller	3-00 p & p 10p
9" Twin spring unit For	2-75 p & p 15p
16" Twin spring unit Reverbs	6-50 p & p 25p
Car Tachometer Electronic	7-50 p & p 15p
VHF 105 Aircraft Band Corrector	3-95 p & p 15p
B2005 4 Ch. mic. mixer	2-95 p & p 15p
B2004 2 ch. Stereo mixer	4-75 p & p 15p

BUILD THIS RADIO

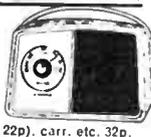Portable MW/LW radio kit using Mullard RF/IF module. Features MW — bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7-98 (battery 22p). carr. etc. 32p.



EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO (+ or - Earth with speaker packg. 30p.	AKAI GXC40 cassette recorder. £6-50 carr./packg. 50p.
8 TRACK CAR STEREO (- Earth) with speakers in Poda & fixings. £12-50 carr./packg. 40p.	Pair Akai ADM microphones. £6-95 carr./packg. 20p.
HANIMAX HC1000 Battery cassette recorder. £10-50 carr./packg. 25p.	PORTABLE CASSETTE TAPE PLAYER — for car or carry around. £7-25 carr./packg. 20p.
HANIMAX HC2000 Battery/Main cassette recorder. £13-50 carr./packg. 30p.	HANIMAX POCKET CALCULATOR WITH % KEY. £33-50.


SPECIAL PURCHASES

AVOMETER MOVEMENTS. AVO 8 or 9 50µA MOVEMENTS. Ex Brand New AVO's £3-50 Post 20p.

UHF TV TUNERS CHANNELS 21 TO 64 Brand new transistorised geared tuners for 625 Line Receiver IF output. £2-50. Post 20p.

EASY TO BUILD KITS BY AMTRON— EVERYTHING SUPPLIED

Model No.		
310	Radio control receiver	2-98
300	4-channel R/C transmitter	5-95
345	Superhet R/C receiver	5-95
455	AM signal generator	12-33
65	Simple translator tester	1-40
115	8 watt Amplifier	3-90
125	12 watt amplifier	4-70
125	Stereo control unit	5-70
130	Mono control unit	3-60
605	Power supply for 115	4-55
610	Power supply for 120	4-55
615	Power supply for 2 x 120	5-73
230	AM/FM aerial amplifier	2-93
240	Auto packing light	5-90
275	Mic. preamplifier	6-08
570	LF generator 10Hz-1mHz	15-80
575	Sq. wave generator 20Hz-20KHz	14-60
590	SWR meter	12-85
620	NI-CAD Charger 1-2-12v	8-00
630	STAB Power supply 6-12v 0-25-0-1A	8-15
690	DC motor speed Gov.	2-87
700	Electronic Chaffin	6-80
705	Windscreen wiper timer	10-75
760	Acoustic switch	10-75
780	Metal Detector (electronics only)	9-65
790	Capacitive Burglar alarm	6-85
790	Guitar preamp.	4-25
835	Delay car alarm	6-15
840	CAP. Discharge Ignition for car engine (-Ve Earth)	13-15
80	Scope Calibrator	2-25
255	Level indicator	6-15
525	120-160mHz VHF timer	11-30
715	Photo coil switch	7-70
795	Electronic continuity tester	4-30
860	Photo timer	13-25
871	Silde projector auto feed control	7-15
235	Acoustic Alarm for driver	7-60
465	Quartz XTAL checker	8-75
220	Signal injector	2-30
390	VOX	15-50
432	Testakit	19-30
670	Buffer Battery Charger	6-55
885	Capacitive Contact Alarm	6-25
850	Electronic Keyer	18-75
820	Electronic Digital Clock	58-50

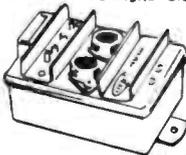

ALL KITS OFFERED
 SUBJECT TO
 STOCK
 AVAILABILITY

BUILD THIS TUNER

MW/LW Radio Turner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £4-85. carr. 15p.

MULTI-USE & RADIONIC KITS

10-1	10 Projects	3-60
50-1	10 Projects	8-00
150-1	150 Projects	13-20
X20	20 (Elec.)	7-20
X40	40 (radio)	9-45

All transistor circuits with hand books

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/Eraser heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9-50 carr. 30p

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).

Singles Log and Lin 50k, 10k, 22k, 50k, 100k, 250k, 500k, 1 Meg. 45p each.

Ganged Log and Lin 10k, 22k, 50k, 100k, 250k, 65p each. (Quantity discounts available)

MARRIOT TAPE HEADS


4 TRACK MONO or 2 TRACK STEREO '17' High Impedance £2-00
 '18' Med. Impedance £2-00
 R730/E73 2 track mono Record/Eraser low imp. 75p pair.
 Erase Heads for '17' and '18'. 75p
 '63' 2 track mono, HI imp. £1-75
 '43' Erase Head for '63' (Post. etc. 15p any quantity).

SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

AMPLIFIERS (carr. etc. 20p)	
4-300, 0-3 watt 9 volt	1-75
104, 1 watt 9 volt	2-20
304, 3 watt 9 volt	2-50
535, 3 watt 12 volt	2-85
E1208, 5 watt 12 volt 4-50	
608, 10 watt 24 volt 4-10	
410, 10 watt 28 volt	4-95
Z30, 15 watt 30 volt	3-57
E1206, 30 watt 45 volt	9-75
Z50, 30 watt 50 volt	4-37
E1210, 21 + 2 1/2 watts	5-25
RE500, 5 watt IC mains operated Amplifier with controls	£6-30
SAC14, 7 + 7 watt Stereo with controls	£8-00
SAC13, 15 + 15 watt Stereo with controls	£11-00

SINCLAIR PROJECT

60 (carr. 20p)	
Z30 3-57	Z50 4-37
Stereo 60 Preamp.	7-97
PZ5 £3-97, PZ6 £6-37	
PZ8 (for Z50) £4-77	
(TRAVIS £2-95)	
AFU £4-45	
New SINCLAIR PROJECT 60	
Stereo Preamp.	9-50
Audio Filter Unit	5-50
Z40 15 Watt Amp.	4-30
Z60 25 Watt Amp.	5-50
PZ5 Mod. for 1 on 2 Z40	3-98
PZ6 Mod. (S Tab)	6-25
PZ8 Mod. (S Tab)	6-30
1 on 2 Z50	
TRANSFORMER FOR PZ8	2-95
Project 605 Kit	19-95

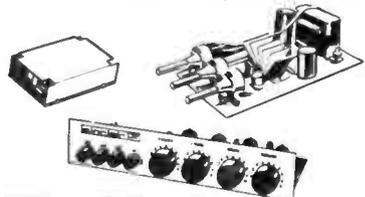


POWER SUPPLIES FOR EVERY PURPOSE

(All cases unless stated chassis)	
4700 6.75/9 volt 300 MA (includes Multi-Adaptor for Tape Recorders, etc.)	1-95 post 20p
Car Lighter Voltage Adaptors 300mA (State voltage 6v, 7.5v, 9v)	1-95 ea. post 25p
SC202 3.6/7.5 volt 400mA	3-75 carr. 30p
HC244R Stabilised version	4-25 carr. 30p
P500 9 volt 500mA	2-80 post 20p
P11 24 volt 500mA (chassis)	2-80 post 20p
P15 26/28 volt 1 amp (chassis)	2-70 post 20p
P1080 12v 1 amp (chassis)	3-25 carr. 30p
P1081 45v 0-9 amp (chassis)	4-40 post 20p
P12 4-12 volt 0-4-1 amp	6-75 post 30p
SE101A 3.6/9/12 volt 1 amp (Stab.)	9-15 post 25p
RP164 6.75/9/12 1 amp (Stab.)	9-95 post 30p

FIBRE OPTICS

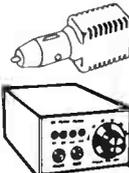0-01 Diam. Mono Filament £1-50 per 25 metre reel
 0-13 Diam. 64 Fibres Sheathed. £1-00 per metre
 SPRAYS 15mm Diam. Mares Tails £9-50.



Henry's RADIO LIMITED

EDGWARE ROAD, W2

SEE FACING PAGE FOR ADDRESSES

Henry's

DISCOUNT HI-FI, TV, TAPE AND CAR ENTERTAINMENT

Low prices means less VAT - Henry's give full guarantees and demonstrations for callers. Plus big savings.
Also at Modern Electric (Retail) Ltd., 120 Shaftesbury Avenue, W.1.—Your Sony dealer.

STEREO AMPLIFIERS

(carr./packing 50p)			
AKAI	AA5200	61-70	
	AA5500	78-50	
	AA5800	117-50	
AMSTRAD	I C2300 Mk. II	29-50	
	4000 Mk II	23-95	
EAGLE	TS1419	25-10	
	TS1451	34-85	
	AA2	30-80	
	AA4	42-45	
	AA6	55-95	
HOWLAND WEST	DA1000	22-45	
HENELEC TEXAN	Kil	28-50	
HENELEC TEXAN	Bullit	35-00	
NIKKO	TRM300	25-95	
	TRM400	32-50	
	SA500A	34-25	
PIONEER	RA 211	32-65	
ROTEL	RA311	41-15	
	RA611	60-80	
	RA810	75-75	
	RA1210	92-50	
SINCLAIR	2000	22-95	
	3000	28-95	
TANDBERG	TA300	66-10	
TELETON	SAQ206B	22-50	
	SAQ307	22-50	
	GA202	28-50	

STEREO RADIO TUNERS

(carr./packing 50p)			
AKAI	AT550	60-50	
	AT580	94-50	
AMSTRAD	3000	23-55	
EAGLE	AA8	40-50	
	TS1152	29-45	
HENELEC Stereo Kil		22-95	
HENELEC Stereo Bullit		24-95	
HOWLAND WEST	DA1000T	25-35	
PIONEER	TX500A	48-75	
ROTEL	RT222	32-65	
	RT322	43-75	
	RT622	65-40	
SINCLAIR	3000	26-95	
TELETON	GT202	30-50	

DECODERS / SYNTHESIZERS (carr. etc. 30p)

DYNACO QUADRATOR		16-90
EAGLE	AA10	12-90
	AA26	16-35
TATE 1	} Chassis	7-95
TATE 3		15-75
TATE 4		19-95
TATE 7		25-95
	Boxed	25-95

MATCHED SPEAKER SYSTEMS

Recommended pairs 8 ohms
(Carr. / Packing £1.50 pair)

RANK DOMUS

150	26-95 pr.
175	33-75 pr.
250	53-75 pr.

MARSDEN HALL

110	10 watt	22-50 pr.
150	15 watt	27-50 pr.
200	20 watt	34-50 pr.

DYNACO

A10	} 20-60 watts	43-00 pr.
A25		69-00 pr.
A35		79-00 pr.

WHARFEDALE

Denton 2	18 watt	27-20 pr.
Linton 2	20 watt	32-65 pr.
Melton II	25 watts	51-80 pr.
Trilon	25 watt	40-80 pr.

LEAK

150	18 watt	32-65 pr.
250	18 watt	44-30 pr.

CELESTION

120	20 watt	37-80 pr.
COUNTY	25 watt	33-60 pr.
15	30 watt	50-40 pr.
44	44 watt	81-20 pr.

UK's largest stockists for KEF Acoustic Research, Mordaunt Short & Cambridge Audio speakers. In stock and on demonstration. Phone for keenest price.

BATTERY CASSETTE RECORDERS (carr. etc. 30p)

Amerex	100	11-00
Wien	ET1008	11-00
Philips	EL3302	14-40
	N2203	16-60
	N2211	19-95
Sony	M1101	14-65
	M1102	12-95

STEREO MAGNETIC CARTRIDGES (carr. etc. 15p)

SHURE	M44G	4-20
M3Dm	M44G	6-75
M44-7	M75 EDII	8-50
M44E	M75 EJII	7-95
M5E	M75GII	7-25
GOLDRING		
G850	2-85	G800SE 10-00
G800	3-95	G820 6-70
G800H	3-95	G820E 10-00
G800E	5-95	G820SE 13-35
A DC		
Q36	10-70	Q30 5-90
Q32	8-70	
GRADO		
FTR	5-25	FTE 8-25
F3E	11-25	F2 18-75
EMPIRE		
		999TEX 14-95
		999REX 3-70
		999QUX 4-80
		999XEX 8-50
		SM500/7 4-60
		SM500/5 4-60
		SM500/E 6-95

STEREO COMPACTS

Complete with Speakers (c.p. £1.25)

Fidelity	UA3	39-90
Sony	G2601 KL	125-50
Sony	G2615N	71-50
Sony	GXT4520KL	103-50
Sony	GXT4730KL	97-50
Philips	GF908	102-75
Philips	RH502	158-95
Philips	RF836	57-20
Philips	GF826	41-75
Philips	RH811/RH421	84-95
Philips	RF839	55-95
Philips	GF829	39-95
Philips	GF808	47-75
Philips	RH814/RH411	96-75
Philips	GF603	19-95

8 TRACK STEREO HOME UNITS (carr/packing 70p)

Amerex ACR301 (with MW/FM stereo radio) 48-00

PORTABLE TV BATTERY/MAINS (c.p. £1.00)

Elizabeth T9	9"	43-50
Crown 9TV	9"	46-50
Elizabeth T12	12"	43-75
Teleton TW12	12"	46-95
Sony 10T150	9/10"	52-50

CASSETTE PLAYER
FOR CAR - HOME AND AROUND

Actually the price far below the quality of the superb player it is of beautiful quality both in sound and look's. Features wind rewind volume and tone controls. Speaker is very good indeed. Comes complete with earphone, batteries Full guarantee. Optional adaptor to run off car or mains.

OUR PRICE **£7.25**

MAIN ADAPTOR £1.35

DOLBY / NRU (carr./packing 30p)

Teleton	SNR100D	29-50
Philips	N6720	15-00
Teac	AN60/AN80/AN180	stocked
RECORD DECK PACKAGES		
(carr./packing 75p) *Less carr.—rest with (M) SPS III/800 or H 15-95		
(M)	SP25 III/M756S	19-45
(HL)	AP76/G800	25-55
(M)	AP76/M756S	29-10
(HL)	GL75 P/C	33-50
(HL)	GL75 P/C G800	36-65
(HL)	GL75 P/C G800E	39-15
(HL)	MP60 (TRD1) G800	15-80
	HT70 (TPDI) G800	19-50
RANK DOMUS	BD200	43-60
	BA400	52-95
	*Pioneer PL12D	31-75
	*Thorens TD165	43-80
	Thorens TD160C	50-80

BATTERY / MAINS CASSETTE (carr. etc. 35p)

Wien	RT452	13-65
Amerex	AC101	12-00
Elizabethan	LZ315	12-25
Amerex	AC104	16-00
Philips	N2204	20-75
	N2205	29-50
	9115	27-75
	9118	21-20
Hitachi	TRO291	27-50
Sony	M2000G	23-25
	MR4010G	28-95
	M4000G	49-90
	CC9201	37-25
	TRO2335	49-50

BATTERY / MAINS RADIO CASSETTE RECORDERS (carr. etc. 30p)

Amerex	ACR200	22-00
	ACR201	30-00
Elizabethan	LZ416	29-10
BASF	CC9301	50-75
Philips	RR322	28-75
	RR413	33-90
	RR712	48-30
	M4141FG	43-20
	M2400	27-25
	M2400FG	36-90
	M4400FG	68-50
Grundig	C250	47-95
Hitachi	TRK1240E	29-50
	TRS1161	35-00
	KCT1210L	33-50

STEREO RECORDER DECKS (carr./packing 60p)

Cassette		
Philips	N2506	44-50
	N2510	£87-10
Pye	9145	44-50
Tandberg	TRD300	112-00
Akai	CS300	50-65
	CS33D Dolby	62-50
	GXC36D	65-15
	GXC40D	57-40
	GXC38D Dolby	81-45
	GXC46D Dolby	89-15
	GXC45D	74-30
TEAC	A250/A350—A450	Stocked

Real to Real Akai 4000DS 62-50
Tandberg 3321X/3341X 107-70
Large range Akai/Tandberg/Revox/Teac stocked.

STEREO PHONES (carr./packing 20p)

AKAI	ASE11	4-75
	ASE20	7-30
	ASE22	8-25
DULCI	SH650D	2-25
	SH850GX	3-95
	SH1300VS	5-25
AKG	K60	9-25
ROTEL	K60	9-25
	SEL40	12-99
RH630	4-85	
RH700	6-75	
SENHEISER	K6/LC	11-25
HD414	11-25	
WHARFEDALE	K711	7-85
DD1	8-95	
ISODYN	K6	9-95
KOSS	K6/LC	11-25
K6	11-25	
K711	7-85	
KRD711	7-85	
HV1	17-50	(two phones) 2-62
K0727B	12-45	G1305
K0747	15-95	Controller 2-15
PRO4AA	21-95	FF17 2-pairs 6-25
PRO5LC	23-95	(Sliders) 4-20
HOWLAND WEST	CIS200	2-75
	TS4	4-95
	CIS250	5-25
	T10A	8-50
	CIS1000	7-50
	HW Mk.III	8-50
	CIS2000	15-25
	Controller	6-99

YOU CAN PAY BY BARCLAYCARD OR ACCESS

For callers or by phone 01-402 4736

Easy credit terms for callers to 309 and 354-356

BEST VALUE IN U.K.

8 Track Akai	CR81D	53-60
	CR60DSS	93-65

STEREO RECORDERS (carr./packing 70p)

Akai	1721L	67-20
Cassette Akai	GXC40 Dolby	59-95
	GXC46 Dolby	89-95
Philips	N2400/RH411	63-75
	N2401/RH411	74-50
	N2401S/RH411	79-95
	N2405/RH401	49-50
8 Track Akai	CR81	66-20

STEREO TUNER AMPLIFIERS (carr./packing 75p)

Akai	AA8030	92-50
Goodmans Module 80		58-20
Goodmans Module 90		75-75
Goodmans One/Ten		88-50
Pioneer	SK525	90-75
Rotel	RX150A	124-75
	RX200A	41-95
	RX400A	53-95
	RX600A	84-95
	SR800	90-00
Tandberg	TR151A	114-50
	TR200MPX	78-30
	TR1000MPX	85-15
	TR1010MPX	143-75
Teleton	TSF55	149-95
		57-20

8 TRACK PLAYER DECKS (carr./packing 35p)

Elizabethan 8/LZ1	13-40
McDonatd/BSR TD8S	12-75
TD83V	15-25

IN CAR ENTERTAINMENT CAR RADIOS (carr./packing 35p)

MW/LW Complete with speakers

SHIRA Touring	7-00
SHIRAMATIC	9-00
PHILIPS RN270	13-65
PHILIPS RP305	17-40
PYE 2644	26-75
PYE 2062	18-25
COURIER MC101	10-95
COURIER PC51	14-75
SHARP ATR 933	12-45
SHARP AR 947	18-60
STEREO CASSETTE (carr/packg 35p)	
Complete with Speakers	18-50
SHIRA NA300	23-75
SHIRA CP401	26-40
PHILIPS N2607	32-00
RM/BIBLE 302CS	24-75
PYE 2252	28-40
HANIMAX HC6010	38-95
(Plus MW/LW Radio/)	38-95
STEREO 8 TRACK (carr/packg 35p)	
Complete with speakers	15-00
SHIRA ST805	21-00
WALTHAM TRE 1500	
8 TRACK WITH MW/LW RADIO (carr/packg 35p)	
Complete with speakers	25-70
SHIRA ST1000	31-50
SHIRA ST2000	
MW/STEREO FM (carr/packg 35p)	
Complete with Speakers	36-50
SHARP AR953 CAR RADIO	42-85

ALSO STOCKED AND DEMONSTRATED

Armstrong - Acoustic Research
Cambridge Audio Leak - Lux
Marantz - Quad - Revox - Sansul
Tandberg - Sugden - Wharfedale
Goodmans - Celestion - Grundig
Kef - Teac - Bose - Sherwood
Call or phone 01-402 4736 for best prices.

10% VAT to be added to all orders.
Prices & description correct at time of press E&OE. All goods offered subject to stock availability.

FREE

in the December 'Practical Motorist'

2 Instant OIL FUNNELS

Keep them in the glove box of your car to fit together when you have to top up the oil and your proper funnel is at home in the garage.

Highlights in this gift issue

Tackling winter hazards—extras to carry to make bad weather motoring easier. Review of de-misting devices now available. Replacing the syncromesh in a Herald gearbox. Impression test of the new Cortina 2000E and 1600cc.



Don't miss the December issue of

PRACTICAL motorist

NOW ON SALE 15p

QUALIFY TO EARN MORE MONEY In a better job

Exciting new career opportunities! They're just waiting to be grasped—in the ever-growing industries of electronics, radio and television. And with ICS behind you, you can soon win the qualifications you need to assure your career success. Win them in your own time, in your own home, by starting an ICS learn-as-you-earn correspondence course now. You get personal, individual attention from really expert and experienced tutors. We teach you the theory, we teach you the practice. Books and components are provided. So is all the assistance, all the backing you need.

We also have a complete range of courses at the ready for people keen to score success in other fields. Whatever qualification you're after, we can help you get it, whether you're pushing ahead where you are or switching to something completely new.

Take your first step now towards a better paid, more assured future. Send for your FREE Careers Guide today.

Take one of these courses

- Society of Engineers Graduateship (Electrical Engineering)
- G & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificates in Technical Communication Techniques
- C & G Radio Amateurs
- MPT General Certificate in Radio Telegraphy
- Audio, Radio and TV Engineering & Servicing
- Electronic Engineering Maintenance, Engineering systems
- Instrumentation & Control systems
- Computer Engineering & Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

... or take one of these if your future lies in other fields

- GCE O and A Level**
Basic foundation for success in a thousand and one careers—recognised by everybody. All Boards—64 subjects
- Building**
Tuition for recognised technical qualifications in all fields
Architecture
Builders Quantities
Carpentry, Joinery
Draughtsmanship
Quantity Surveyors
Clerk of Works
Heating, Ventilating
- Engineering**
Theoretical and practical tuition geared either to professional and technical examinations or to vocational (non-exam) courses
Mechanical, Motor, Diesel, Chemical
Welding
Refrigeration
Draughtsmanship
Garage Management
* Courses for appropriate professional exams available in addition to ICS Diploma courses.

- Management, Marketing and Business**
Instruction in the latest proved principles and techniques used in each highly specialised area.
*Personnel
*Administrative
*Works
*Transport
Business
Industrial
Sales
Marketing
*Advertising
*Marketing
*Public Relations
Sales
Business
Computers
*Purchasing
*Book-keeping
*Work Study
Storekeeping
Small Business Owners
Fire Service
*Promotion and Institute of Fire Engineers
Police
*Entrance and Promotion

POST TODAY FOR FREE DETAILS

ICS your key to a brighter better future

To: International Correspondence Schools, Dept. 232A
Intertext House, Stewarts Road, London, SW8 4UJ.

Name

Address

Age Occupation

Accredited by the C.A.C.C.

FELSTEAD ELECTRONICS (PW 75) LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Selection from our List, sent free for stamped addressed envelope. (Free overseas, and with all orders on request). Cash with order only—No C.O.D. or Caller service. Charges (Min. 7p) in brackets after all items apply to G.B. and Eire only. Regret orders under 30p plus charges unacceptable. S.A.E. please for enquiries or cannot be replied to. Overseas, including Eire and Channel Isles, orders less 10% off prices below, which include V.A.T. RECORDING TAPE: Finest quality/value British Mylar available: STANDARD 5" 600ft. 40p. 5 1/2" 900ft. 55p. 7" 1200ft. 62p. LONG PLAY 5" 900ft. 55p. 5 1/2" 1200ft. 62p. 7" 1800ft. £1.00 (Charges for 5" and 5 1/2", singles 10p, two to four 9p each; five and over 85p the lot. For 7", one, two or three 12p each reel, 3, 4 and 5 reels 84p the lot, 6 reels and over 40p the lot). Other sizes and accessories in list. CASSETTES, Two types, Both in Library Cases, C60 32p, C90 45p, C120 72p. Deluxe Types: C60 55p, C90 72p, C120 99p. (Charges for both types, under 5, 9p each. 5 for 17p). All quantities over 5, 28p the lot.) CARTRIDGES all with standard fittings and styli. Stereo-compatible Mono GP91/8C 98p; STEREO GP93 £1.85, Stereo Ceramic GP94 £1.75. Comparatives shown in List, with more types inc. Sonotone 9T4HC, Stereo Ceramic Diamond £1.70 (All at 8p each). DIAMOND STYLI: single tip types: ACOS GP37, GP39, GP38/67, GP71, BR TCS/LP/ST; COLLAARO O.P. and DC294, GARRARD GC2, GC8, GC810, GC121, RONETTE BF40, CO.P. and T. PHILIPS 3301 (3060, 3066, 3302, 3304), 3010/12/13/16, SONOTONE 19T/20T ALL at 85p each. SAPPHIRE 16p. DIAMOND DOUBLE TIP TURNOVER TYPE8 (78 sap. on other side). For ACOS GP73, GP91 (for cartridges GP93, GP94, etc.) GP918C (for stereo compat. types) GP104, BR ST4 (8T3, 8T5), 8T9 (8T8), 8T12/14/16, SONOTONE 8TA, 9TA, 9T4HC, PHILIPS 3306, 3310, 3224, 3228/22, GP260, GARRARD GCM31, and 22, GC823, GK825 and 26, GCMIT and 22T, GCM24T, GC823, GR825T and 26T, GCM31, GC838, GC835, GC838, K840A, K841B, ETC. ALL at 68p. SAPPHIRE 32p. DOUBLE DIAMOND STYLI: same dia STYLI tip each side: no. 78) All types £1.85. SAPPHIRE DOUBLE STYLI, TIPPED 32p. DIAMOND STYLI GOLD-RING REPLACEMENTS: G800, G800H & G850, £2.25 each, G800E £3.75 (All Styli 9p up to 3). PICK-UP WIRE: super thin flex screened, sheathed, TWIN 7p per yard, 4-core 15p per yard, (either up to 6 yards, 7p). Over, charges paid. MICROPHONES: CRYSTAL-LAPLE 11", clip/hand, lead 3-5mm jack plug 85p (10p), CM20 Cream Plastic hand 85p (10p). "MIC 4Q Curved metal hand grip £1.10 (11p) ALL with leads. DYNAMIC: Excellent Mike, 50K Ω , only 3 1/2" long, black/chrome, switched, lead with 2- and 3-5mm jack plugs £1.37 (11p). Cardiol Ball, 50K/600 Ω built in volume control, on/off switch, special 20ft lead, the best value anywhere at £6.00 (33p); Uni-dir. mesh ball 50K/600 Ω jack plug cable, adaptor, £5.25 (33p); Omni-dir. Ball mesh, 50K, cable adaptor, jack plug £4.25 (33p each). SPEAKERS: Very popular 12" ROUND, fitted tweeter, 3, 8 or 15 ohms (state which) £2.06 (33p) or pair for stereo £4.65, charges paid. SMALL 2 1/2", 3 Ω , 8 Ω or 64 Ω (state which) 41p (9p). More speakers in List. HEADPHONES: High resistance 2000 Ω adjustable £1.10 (11p). EARPIECES: with lead and min. 2-5mm or 3-5mm (state which) jack plug. MAGNETIC 12p. CRYSTAL (3-5mm plug only) 28p (up to 6 for 9p any size). SOLDERING IRON: Slim, modern, British high speed, 81", all parts replaceable, highest quality, fully guaranteed £1.28 (11p). TRANSFORMERS: sub-min. 11 1/2" x 11 1/2" x 12mm. OUTPUT (3 Ω) for OCT7, etc.) 16p or DRIVER 17p (Up to 12 for 7p). CONNECTING WIRE: Packs of 5 coils, each coil 5yds. Assa. coils. SOLID CORE 16p (8p). FLEXIBLE CORE 16p (10p). RETRACTABLE FLEXIBLE LEADS (CURLIES) with phono plug each end, or phono plug one end, phono socket at the other (state which) 6ft. 30p; 12ft. 58p (either 7p). VIBRATORS: 12v/4 pin non-synch. 121HD4, 2 1/2" ex. pins. 83p. SAME but 3 1/2" ex. pins, USA. 16p. 12v/7 pin synth. (1287R) 2 1/2" ex. pins. 78p (9p any type). MAINS BATTERY ELIMINATORS: Two models, both 240v A.C. input. Suit most radios and cassette recorders/players, with front switch, pilot lights, mains and output leads Model 8C, 3, 6, 7, 8 and 9v 400mA, stabilised with multi-output adaptor £5.50 (35p). Model N.R. has additional 12v output and is 500mA £8.00 (35p).

OUR LIST (see heading) has added to the above items more Cartridge and Styli and Equivalent Table, Special Non-repeatable Offers, Aerials, Dial, Transistors, Multi-Leads, Plugs, Sockets of many types. Speakers, Vol. Controls, Multi-testers, Professional Microphones, Mike Inserts, Neons, Indicators, STEREO Headphones, Pocket Screwdrivers, Testers, Tel. Pick-ups, Wire, Cable, etc., etc.

LASKY'S 1974 CATALOGUE

FREE Send this coupon today for your Free copy of Lasky's Famous Hi-Fi, Audio and Electronics Catalogue.

NAME

ADDRESS

.....

AUDIOTRONIC HOUSE, THE HYDE, LONDON, NW9 6JJ

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDEGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 405285

THE T.V. GRAVEYARD OF THE NORTH, AS SEEN ON T.V. CLOSE TO THE MOTORWAY. PLENTY OF FREE PARKING SPACE. EST. 1935.

SPECIAL OFFER

1000 PYE 19" 13 Channel T.V. Sets. Brilliant Picture, Extra Slim Bench Tested. Sold with Money Back Guarantee. Hurry, have a second set at the price of £5.50. Plus carr. and ins. £1.80.

Students Wireless Procedure Training Set comprising mike, single LR phone and connector in small wood box, 80p post paid.

COMPLETE UNTESTED T.V. SETS. With back and all valves. BBC 1 and ITV 17" 90° Tubes £1.10. 17" 110° Tube £2.20. 19" £3.30. Carr. and ins. on any set £1.75.

Fifty T.V. Valves. Good assortment not-tested 50p. Post-Paid 1/2 Cwt. of ex Government Scrap Resistors, Panels and Gears, etc. 30p. Carr. 80p.

SPEAKERS REMOVED FROM T.V. SETS, all 3 Ohm 2 1/2 Watts. 7 x 4", 6 x 4", 8 x 2 1/2". All at 27p. Post and packing 12p.

TOP QUALITY TAPE. Reel to Reel 5" ST, 44p 5" LP 55p, 3 1/2" LP 60p, 7" ST 66p, 7" LP 80p. Cassette Types C60 35p. C90 45p. C120 55p. Post on any tape 12p.

Jap Earpiece 8 Ohm Magnetic 3-5 12p.
Ex Equipment Valves All tested on our Mullard Valve Tester before despatch. 3 months guarantee on all valves. Single Valves Post 3p, over Post Free.

ARP12	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	10p
EF80	10p	PCL82	14p	UI91	20p
EBF89	15p	PCL83	15p	6BWW	70p
ECC81	12p	PCL84	15p	6U4	20p
ECC82	12p	PL82	10p	6F23	15p
EF91	5p	PL83	10p	20P1	12p
EY86	22p	PL36	17p	20P3	12p
EF183	20p	PY81	10p	30FS	20p
EF184	20p	PY801	17p	30FL1	20p
		PY800	17p		

ABOVE PRICES INCLUDE V.A.T.

ALL PRICES INCLUDE VAT

BARGAIN PARCELS 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 57p p.p.; 56lb at £4.95 plus £1.37; p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH, medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £1.55 post paid.

NEW HEAVY COAX CABLE dia. 1/2" 70 ohms approx. 50ft. lengths £1.55, p. & p. 32 1/2p. 100 ft. lengths £2.97, p. & p. 55p.

AERIALS. New Condition Whip Type, 4ft. 22p; 11ft. 82p, all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 67 1/2p. p. & p. 27 1/2p.

CRYSTALS AS NEW. Hc 6u, 5,345; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,295 Kc/s. 55p each plus 8p p.p.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2 1/2in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 27 1/2p, minimum order of six.

ANY HEIGHT AERIAL TUBULAR SECTIONS 1/2" dia. x 3ft. long. Brass screw in ends, copper coated and painted. Good condition. 22 1/2p p. & p. 5p each. Minimum order 6.

TELE J. & L. FIELD TELEPHONES. Good condition. £6.00 a pair. p. & p. 75p.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 90ft 50p, 100ft. 60p, p. & p. 22p.

AERIAL POLES 4ft high 2" in diameter push-in type as new 75p each p. & p. 25p each minimum four.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition, £1.10 each section. Carriage 37p each section. 1/2" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1.10 + 32 1/2p p.p.

AS NEW 500ua PENNY SIZE METERS complete with iack plug price £1.10 each, p. & p. 10p.

COMMUNICATION RECEIVER PCRS price £10. post paid. PCR No. 2 6 to 22 Mcxs.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

Fully guaranteed Individually packed VALVES

R12H	£1.75	ECH64	40p	OA2	38p
CY31	40p	ECL90	40p	OB2	35p
DAF96	40p	ECL82	31p	PAB80	35p
DF96	40p	ECL83	63p	PC97	41p
DK96	51p	ECL86	63p	PC900	42p
DL92	32p	EF36	60p	PC924	38p
DL94	46p	EF37	65p	PC989	45p
DL96	40p	EF40	62p	PC8189	49p
DM70	40p	EF41	65p	PCF800	75p
DY86	29p	EF90	25p	PCF80	25p
DY87	28p	EF93	30p	PCF82	27p
DY802	30p	EF98	31p	PCF94	25p
EB88C/01	£1.08	EF98	27p	PCF86	50p
EB88C/01	£1.08	EF99	25p	PCF200	60p
EB88C/01	£1.08	EF91	27p	PCF201	60p
EB88C/01	£1.08	EF92	31p	PCF801	44p
EB88C/01	£1.08	EF95	31p	PCF802	44p
EB88C/01	£1.08	EF98	31p	PCF805	80p
EA50	18p	EF184	31p	PCF806	65p
EA18C80	27p	EF184	31p	PCF806	65p
EA18C80	27p	EL14	59p	PC1200	85p
EA18C80	27p	EL41	55p	PC181	50p
EB91	20p	EL84	21p	PC182	80p
EB93	45p	EL85	37p	PC183	80p
EB94	50p	EL86	38p	PC184	80p
EB95	50p	EL87	38p	PC185	80p
EB96	50p	EL88	38p	PC186	80p
EB97	50p	EL89	38p	PC187	80p
EB98	50p	EL90	38p	PC188	80p
EB99	50p	EL91	38p	PC189	80p
EB99	50p	EL92	38p	PC190	80p
EB99	50p	EL93	38p	PC191	80p
EB99	50p	EL94	38p	PC192	80p
EB99	50p	EL95	38p	PC193	80p
EB99	50p	EL96	38p	PC194	80p
EB99	50p	EL97	38p	PC195	80p
EB99	50p	EL98	38p	PC196	80p
EB99	50p	EL99	38p	PC197	80p
EB99	50p	EL99	38p	PC198	80p
EB99	50p	EL99	38p	PC199	80p
EB99	50p	EL99	38p	PC200	80p

TRANSISTORS, ZENER DIODES etc.

OA5	20p	OC71	12p	IN823A	£1.30
OA10	25p	OC72	20p	IN4785	50p
OA70	10p	OC73	30p	IN1519	£1.45
OA71	10p	OC75	25p	IZMT5	35p
OA73	7p	OC76	25p	IZMT10	35p
OA74	7p	OC81	20p	IZ75	67p
OA79 (GD)15	10p	OC81D	20p	IG45	65p
		OC81DM	20p	IG385	51p
		OC82	25p	IG468	£1.25
		OC82DM	30p	IG489	£1.40
		OC93	3p	IG489	£1.40
		OC93B	15p	IG489	£1.40
		OC94	25p	IG489	£1.40
		OC122	50p	IG489	£1.40
		OC129	50p	IG489	£1.40
		OC130	50p	IG489	£1.40
		OC131	50p	IG489	£1.40
		OC132	50p	IG489	£1.40
		OC133	50p	IG489	£1.40
		OC134	50p	IG489	£1.40
		OC135	50p	IG489	£1.40
		OC136	50p	IG489	£1.40
		OC137	50p	IG489	£1.40
		OC138	50p	IG489	£1.40
		OC139	50p	IG489	£1.40
		OC140	50p	IG489	£1.40
		OC141	50p	IG489	£1.40
		OC142	50p	IG489	£1.40
		OC143	50p	IG489	£1.40
		OC144	50p	IG489	£1.40
		OC145	50p	IG489	£1.40
		OC146	50p	IG489	£1.40
		OC147	50p	IG489	£1.40
		OC148	50p	IG489	£1.40
		OC149	50p	IG489	£1.40
		OC150	50p	IG489	£1.40

ALL valves guaranteed

6J4WA	65p	12H17	40p	6060	50p
6J5	85p	1487	70p	6064	45p
6J50T	30p	19A93	40p	6065	65p
6J6	25p	19G3	£5.75	6080	£1.55
6J7G	30p	19G6	£5.75	6146	£1.75
6J7M	35p	19H4	£5.25	6020	£3.75
6K6GT	65p	20P4	£1.00	6001	15p
6K7	40p	25L6GT	50p	9002	40p
6K7G	17p	30C15	70p	9003	46p
6K8GT	40p	30C17	85p	9004	12p
6K8T	60p	30C18	75p	9008	12p
6L6M	1.35	30F5	80p		
6RA7	40p	30F11	70p	G.B. Tubes	
6SC7GT	25p	30F12	90p	VC97	£4.00
6SC7GT	25p	30F14	80p	VC917B	£5.00
6SC7GT	25p	30F15	80p	VC917C	£5.00
6SC7GT	25p	30F17	80p	VC917D	£5.00
6SC7GT	25p	30F18	80p	VC917E	£5.00
6SC7GT	25p	30F19	80p	VC917F	£5.00
6SC7GT	25p	30F20	80p	VC917G	£5.00
6SC7GT	25p	30F21	80p	VC917H	£5.00
6SC7GT	25p	30F22	80p	VC917I	£5.00
6SC7GT	25p	30F23	80p	VC917J	£5.00
6SC7GT	25p	30F24	80p	VC917K	£5.00
6SC7GT	25p	30F25	80p	VC917L	£5.00
6SC7GT	25p	30F26	80p	VC917M	£5.00
6SC7GT	25p	30F27	80p	VC917N	£5.00
6SC7GT	25p	30F28	80p	VC917O	£5.00
6SC7GT	25p	30F29	80p	VC917P	£5.00
6SC7GT	25p	30F30	80p	VC917Q	£5.00
6SC7GT	25p	30F31	80p	VC917R	£5.00
6SC7GT	25p	30F32	80p	VC917S	£5.00
6SC7GT	25p	30F33	80p	VC917T	£5.00
6SC7GT	25p	30F34	80p	VC917U	£5.00
6SC7GT	25p	30F35	80p	VC917V	£5.00
6SC7GT	25p	30F36	80p	VC917W	£5.00
6SC7GT	25p	30F37	80p	VC917X	£5.00
6SC7GT	25p	30F38	80p	VC917Y	£5.00
6SC7GT	25p	30F39	80p	VC917Z	£5.00
6SC7GT	25p	30F40	80p	VC917AA	£5.00
6SC7GT	25p	30F41	80p	VC917AB	£5.00
6SC7GT	25p	30F42	80p	VC917AC	£5.00
6SC7GT	25p	30F43	80p	VC917AD	£5.00
6SC7GT	25p	30F44	80p	VC917AE	£5.00
6SC7GT	25p	30F45	80p	VC917AF	£5.00
6SC7GT	25p	30F46	80p	VC917AG	£5.00
6SC7GT	25p	30F47	80p	VC917AH	£5.00
6SC7GT	25p	30F48	80p	VC917AI	£5.00
6SC7GT	25p	30F49	80p	VC917AJ	£5.00
6SC7GT	25p	30F50	80p	VC917AK	£5.00
6SC7GT	25p	30F51	80p	VC917AL	£5.00
6SC7GT	25p	30F52	80p	VC917AM	£5.00
6SC7GT	25p	30F53	80p	VC917AN	£5.00
6SC7GT	25p	30F54	80p	VC917AO	£5.00
6SC7GT	25p	30F55	80p	VC917AP	£5.00
6SC7GT	25p	30F56	80p	VC917AQ	£5.00
6SC7GT	25p	30F57	80p	VC917AR	£5.00
6SC7GT	25p	30F58	80p	VC917AS	£5.00
6SC7GT	25p	30F59	80p	VC917AT	£5.00
6SC7GT	25p	30F60	80p	VC917AU	£5.00
6SC7GT	25p	30F61	80p	VC917AV	£5.00
6SC7GT	25p	30F62	80p	VC917AW	£5.00
6SC7GT	25p	30F63	80p	VC917AX	£5.00
6SC7GT	25p	30F64	80p	VC917AY	£5.00
6SC7GT	25p	30F65	80p	VC917AZ	£5.00
6SC7GT	25p	30F66	80p	VC917BA	£5.00
6SC7GT	25p	30F67	80p	VC917BB	£5.00
6SC7GT	25p	30F68	80p	VC917BC	£5.00
6SC7GT	25p	30F69	80p	VC917BD	£5.00
6SC7GT	25p	30F70	80p	VC917BE	£5.00
6SC7GT	25p	30F71	80p	VC917BF	£5.00
6SC7GT	25p	30F72	80p	VC917BG	£5.00
6SC7GT	25p	30F73	80p	VC917BH	£5.00
6SC7GT	25p	30F74	80p	VC917BI	£5.00
6SC7GT	25p	30F75	80p	VC917BJ	£5.00
6SC7GT	25p	30F76	80p	VC917BK	£5.00
6SC7GT	25p	30F77	80p	VC917BL	£5.00
6SC7GT	25p	30F78	80p	VC917BM	£5.00
6SC7GT	25p	30F79	80p	VC917BN	£5.00
6SC7GT	25p	30F80	80p	VC917BO</	

SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT
NEW & SECONDHAND MUSICAL INSTRUMENTS.
DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES.

P/A MULTI-CHANNEL SAXON MIXER CONTROL UNITS

Using grouped pairs of inputs and outputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master control. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos etc. Standard jack sockets. Compact design, in strong metal cases. All units guaranteed for 8 years.

- HIGH & LOW IMP. INPUTS
- BASS/TREBLE/VOLUME ON EACH PAIR
- MASTER CONTROL OUT



● **M.4H**
4 high Z, 4 low Z inputs, 4 sets of controls. Case 14" x 8" x 2 1/2"
Carr. pd. + V.A.T. **£18-50**

● **M.6HL** Case 18" x 8" x 2 1/2"
12 Inputs (6 high Z, 6 low Z).
Carr. pd. + V.A.T. **£27-50**

● Channel section modules, for building your own mixer. Gain—16 x (24dB). Tone controls—18dB swing. Carr. pd. £3-50 + V.A.T.

SAXON CONTROL UNITS

Mono (as shown)
For 9v battery operation. As stereo unit but less mic. input



£6-50

20p

Stereo. Carr. 30p

£15-80

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass treble, Headphone Selector and volume. Microphone volume, bass, treble, mains on/off.
COMPARABLE TO UNITS AT OVERTWICETHE PRICE.



120 WATT HEAVY DUTY MODULE

Rugged class A driver stage, this module will run from all our mixers, etc., and most other makes. Delivers 120 watts into an eight ohm load and employs 4 T03 can (115 watt) output transistors. These are the modules where extra power is demanded.

Power output 120 watts on 8 ohms
Freq. response 20-20,000 Hz ± 2dB
Input sensitivity 200 mV into 10K
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply)

£18-95

Low distortion parallel push-pull output stage.

Module & power supply (Carr. 40p)

160 watt version with power supply **£37-90**
£27-50
(Carr. 50p)

SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3000 watts) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.



3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls. 2 amplifier sockets eliminate need for split leads. Up to 3KW lighting load. Smartly finished steel case. Carr. 30p.

£19-75

SINGLE CHANNEL UNIT

Operates from 5 to 100 watt amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p.

Carr. pd. **£8-90**

COMPLETE AMPLIFIERS

CSE 100 £34-90 carr. free

The versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls.



SAXON 100 £48-50 carr. free



With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains

12" 25 watt 8/15 ohms £5-95 carr. 30p 15" 50 watt 8/15 ohm £14-50 carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm £11-50 carr. 40p.

600 watt 3 colour Light Boxes Smart Rexline finish £15 carr. free.

A.K.G. D.190C MICROPHONES **£18-45**

A true professional mic at a bargain price.

SAE with enquiries please as well as for current price lists.

Prices quoted do NOT include V.A.T. 10% must be added on to total value of order for V.A.T.

S A E. for special price list

Better built Better performance Better value

SAXON POWER AMP MODULES FOR DOMESTIC, P.A. AND COMMERCIAL USE

These superbly designed & engineered Saxon power amplifiers use 3A 'Mestic' Power Driver Transistors. To meet demand, we have included a more powerful module in our well-established and proven range, the SA.50. These power amplifiers are expertly assembled, tested and guaranteed. By buying direct from us, you save appreciably, and the modules offer superb value for reliability and versatility.



DESIGNED AND MADE IN OUR OWN FACTORY

- SA35** 35 watts RMS. Uses 7 transistors and 7 diodes. Carr. paid. **£4-45**
- SA50** 50 watts RMS. 7 transistors, 7 diodes. Carr. paid. **£5-65**
- SA100** makes an ideal unit in disco assemblies. A real glutton for work. Reliable, tough and compact, 11 transistors, 6 diodes. Carr. paid. **£10-90**

BRIEF SPEC. FOR ALL THREE MODULES

All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in the SA.100.

Freq. response 15-40,000 Hz ± 1dB
Distortion 0-2% at 1kHz
Load 4 to 16 ohms
Quiescent current 15 mA
Noise Better than -75dB
Supply voltage SA35 25-45 volts
SA50/SA100 40-70 volts
Size 4 1/2" x 4" x 1" (SA 100)
4" x 3" x 1" (SA35/SA50)

Circuits, connecting instruction and application data are supplied free with all modules.

ALL SAXON MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED AND GUARANTEED

SAXON POWER UNITS

- PU.45** UNSTABILISED. For 1 SA.50 into 4Ω or up to 2 x SA.35 (P/P—30p) **£4.90**
- PU.70** UNSTABILISED. For up to 2 x SA.50's into 8Ω or 1 or 2 SA.100's (P/P—40p) **£7.75**
- PS.45** STABILISED. For up to 2 x SA.50 into 8Ω or 1 or 2 SA.100's (Carr. paid) **£3.50**
- MT.45** Mains Transformer (P/P—30p) **£3.50**
- PS.75** STABILISED. For 1 or 2 SA.50's into 8Ω or 1 or 2 SA.100's (Carr. paid) **£4.90**
- MT.75** Mains Transformer (P/P—40p) **£4.90**

Orders and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 327 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.

Telephone 01-684 6385

Hours 9.30 a.m.—5.30 p.m.

TRADE & EXPORT ENQUIRIES INVITED


TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra, cash by regd. letter, please


now...

Project 80

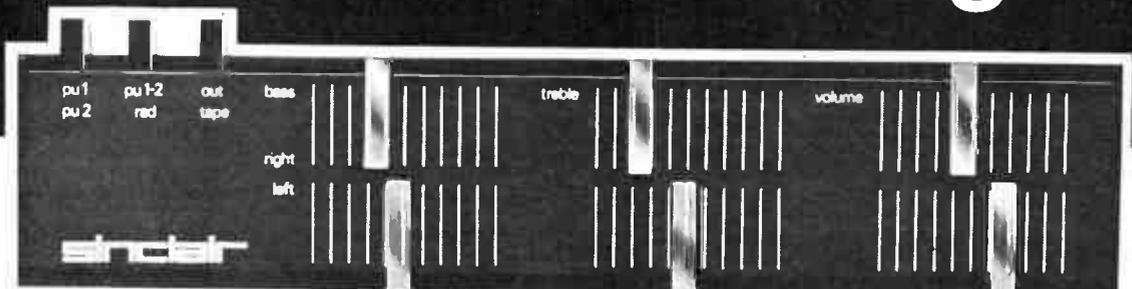...exciting new thinking
in modular hi-fi design



Stereo 80 pre amplifier/control unit

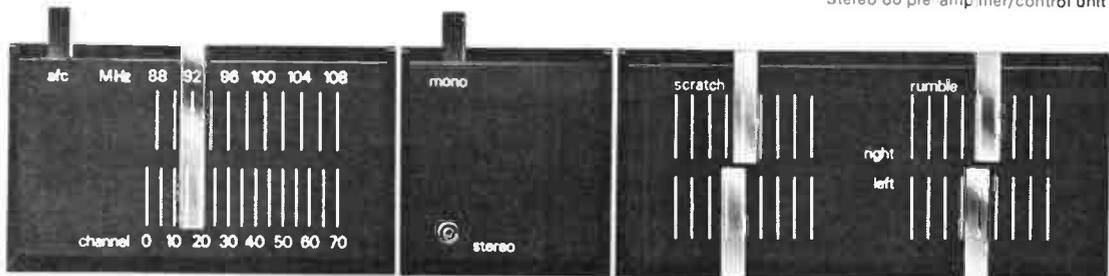

Project 80 tuner

Stereo decoder

Project 80 Active Filter Unit (AFU)

the slimmest, most elegant hi-fi modules ever made



Living with hi-fi takes on new meaning now that Project 80 is here. These amazing new modules mark a brilliant technical advance all round; their size and presentation bring exciting new opportunities to install systems in ways hitherto only dreamed about but never before made practical. You can build a Project 80 system virtually anywhere and it is unbelievably simple to install and connect up. Everything that could possibly be wanted in a top quality do-it-yourself domestic hi-fi system will be found in Project 80 – compactness, elegantly ultra-modern styling, ease of fixing and operation, new control methods, and above all superb performance. New as well as popular established ideas on installation are featured on page four of this announcement to provide just a few examples of the system's fantastic versatility.

SINCLAIR

Project 80 new modules

Stereo 80 pre-amplifier and control unit

As with other Project 80 units, the Stereo 80 is mounted by means of two bolts fixed at the rear which pass through holes drilled in the wood or plastic on which modules are to be mounted. *All the electronics are contained within the 3" deep front panel!* Connecting leads are taken away similarly out of sight. Each channel in the Stereo 80 has its own independent tone and volume controls operated by sliders. This enables exceptionally good environmental matching to be obtained. Provision is made for magnetic and ceramic pick-ups, radio and tape in and out. A virtual earth input stage forms part of the up-dated circuitry of the Stereo 80 to ensure the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS


Size - 260 x 50 x 20mm (10 1/4 x 2 x 3/4 ins)
 Finish - Black, with white markings
 Inputs - Mag P U 3mV RIAA corrected; Ceramic P U 300mV
 Radio 300mV; Tape 30mV
 S/N ratio - 60db
 Frequency range - 20Hz to 15KHz ± 1dB 10Hz to 25KHz - 3dB
 Power requirements - 20 to 35 volts
 Outputs - 100mV ± AB monitoring for tape
 Controls - Press button for tape, radio and P U selection Volume, Bass ± 12dB to -14dB at 100Hz, Treble ± 11dB to -12dB at 10KHz

NEW



- For P.U., radio and tape
- Tape monitoring switch
- Two-hole fixing

RRP £11.95 £1.19 VAT

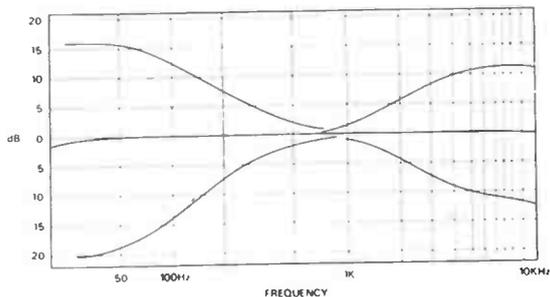


Project 80 FM tuner smaller, more efficient

A truly remarkable tuner in every way - its unbelievably compact size - its original circuitry - its dependable performance - all this in a boldly designed modern case measuring 85 x 50 x 20mm (3 1/4 x 2 x 3/4 ins). Greater adaptability (and possibly financial convenience) results from the tuner and stereo decoder section being made available separately.

TECHNICAL SPECIFICATIONS

Size - 85 x 50 x 20mm (approx 3 1/4 x 2 x 3/4 ins)
 Tuning range - 87 to 108 MHz
 Detector - I.C. balanced coincidence, for good A.M. rejection
 AFC - Switchable, with thermistor control to prevent from drift
 One 26 transistor I.C.
 Twin dual varicap tuning
 Distortion - 0.3% at 1KHz for 75KHz deviation
 Ceramic filter in I.F. section
 Aerial impedance - 75 Ω or 240-300 Ω
 Sensitivity - 4 microvolts for 30dB quieting
 Power requirements - 12 to 45 volts

NEW

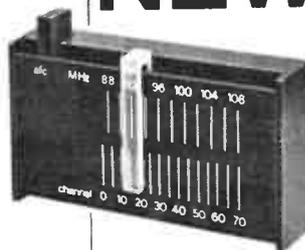

- AFC switch
- Twin dual varicap tuning
- 4-hole ceramic filter
- Slider tuning

RRP £11.95 £1.19 VAT

Project 80 stereo decoder

Making the Project 80 decoder separate from the F.M. tuner gives the constructor a wider choice of systems as well as saving money in cases where stereo reception may not be required. This unit gives a 40dB channel separation with an output of 150mV per channel. The gallium arsenide light emitting beacon automatically lights up to show when a stereo transmission is tuned in. Designed essentially as an integral part of Project 80 systems, this multiplex stereo demodulator may be used in many cases with existing single channel frequency modulated tuners to provide stereo reception.
 Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/4 ins)
 One 19 transistor I.C.

NEW



- Solid-state stereo indicating beacon
- Readily adaptable for use with other tuners

RRP £7.45 £0.74p VAT

new constructional techniques

...and again Sinclair leads the world

- 1962 Micro-miniature power amp small enough to stand on a 10p. piece. Slimline pocket receiver smaller than a 20 cigarette pack
- 1963 Micro-6 receiver, smaller than a matchbox
- 1964 Pocket F.M. receiver, PWM amp.
- 1965 Z.12 power amplifier module, PZ.3 power supply
- 1966 Stereo 25 pre-amp/control unit
- 1967 Micromatic Q.14 loudspeaker, the first Neoteric
- 1968 IC.10, the first ever integrated circuit for constructors use

- 1969 Q.16—improved version of Q.14 Systems 2000 and 3000 Project 60 launched
- 1970 IC 12 Project 60S
- 1971 Project 60 stereo FM tuner Z.50 PZ.8
- 1972 Improvements to Project 60 with Z.50 MK.2 and PZ.8 Mk.3 The Executive Calculator, Digital multi-meter Q.30 speaker
- 1973 Cambridge Calculator

PROJECT 80 LAUNCHED

...and next?

Project 80 active filter unit

This efficiently designed unit makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls are applied to each channel thereby making it easier to obtain ideal stereo balance in any kind of indoor environment

TECHNICAL SPECIFICATIONS

Size—108 × 50 × 20mm (4 $\frac{1}{4}$ × 2 × $\frac{1}{2}$ ins)


Voltage gain—minus 0.2dB

Frequency response—36Hz to 22KHz, controls minimum

Distortion—at 1KHz—0.03% using 30V supply

HF cut off (scratch)—22KHz to 5.5KHz, 12dB/oct slope

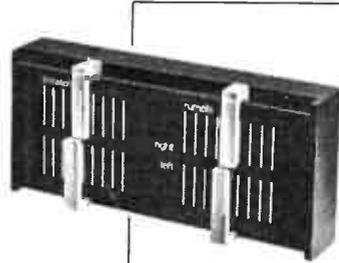L.F. cut off (rumble)—28dB at 20Hz, 9dB/oct slope



NEW

- For scratch and rumble control
- Transistorised active circuitry

RRP £6.95 + 0.69p V.A.T.

Z.40 & Z.60 power amplifiers totally short-circuit proof

Either of these entirely new power amplifiers is intended for use in Project 80 installations although, of course, they are readily adaptable to an even wider range of applications. Both Z.40 and Z.60 incorporate built-in protection against shortcircuiting and risk of damage arising from mis-use is greatly reduced. Comprehensive instructions are supplied with each of the modules.

Z.40 Technical Specifications

Size—55 × 80 × 20mm

(2 $\frac{1}{8}$ × 3 $\frac{1}{8}$ × $\frac{1}{2}$ ins) 9 transistors

Input sensitivity—100mV

Output—15 watts RMS continuous

into 8 Ω (35V), 30 watts music

power into 4 Ω (30V)

Frequency response—10Hz—

100KHz \pm 1dB

Signal to noise ratio—64dB

Distortion—at 10 watts into 8 Ω

less than 0.1%

Power requirements—12-35 volts

Z.60 Technical Specifications

Size—55 × 98 × 20mm

(2 $\frac{1}{8}$ × 3 $\frac{1}{2}$ × $\frac{1}{2}$ ins) 12 transistors

Input sensitivity—100-250mV

Output—25 watts RMS into

8 Ω (45V), 50 watts music power

into 4 Ω (50V)

Distortion—typically 0.03%

Frequency response—10Hz to

more than 200KHz—1dB

Signal to noise ratio—better

than 70dB



Built-in protection against

transient overload and short

circuit

Load impedance—4 Ω min, max,

safe on open circuit

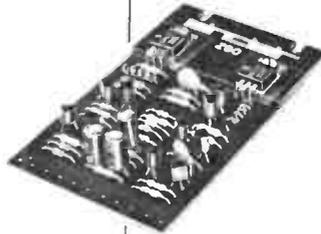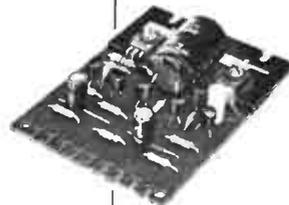

NEW

Z.40

RRP £5.45 + 0.54p V.A.T.

Z.60

RRP £6.95 + 0.69p V.A.T.

Sinclair power supply units PZ.8

the worlds most advanced unit in its class

Stabilised power supply unit. Re-entrant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V

RRP £7.98+0.79p V.A.T.


Without mains transformer

PZ.5 30V un stabilised

RRP £4.98+0.49p V.A.T.

PZ.6 35V stabilised

RRP £7.98+0.79p V.A.T.

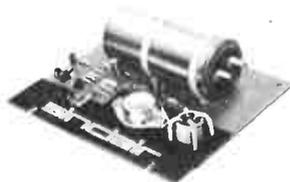

sinclair

R.O. London Road, St. Ives, Huntingdon, PE17 4HJ

Reg. No. 699483 England


World Radio History

Recommended Project 80 applications


System	The Units to use	Units cost
Simple battery record player	Z.40	£5.45 +£0.54p V.A.T.
Mains powered record player	Z.40, PZ.5	£10.43 +£1.04p V.A.T.
30W. RMS continuous sine wave stereo amp.	2 × Z.40s, Stereo 80; PZ.6	£30.83 +£3.08p V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amplifier	2 × Z.60s, Stereo 80; PZ.8	£33.83 +£3.38p V.A.T.
Indoor P.A.	Z.60, PZ.8	£14.93 +£1.49p V.A.T.
Car Radio	F.M. tuner, Z.40	£16.40 +£1.64p V.A.T.

From Sinclair the worlds most advanced hi-fi modules

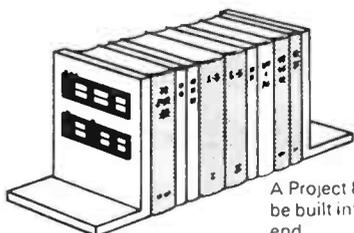
Sinclair Project 80 the ultra-modern non-obtrusive hi-fi



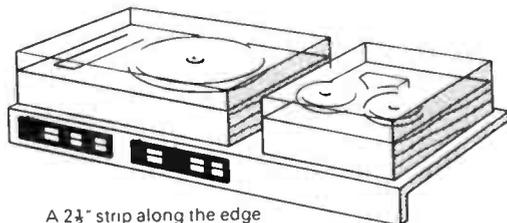
A Project 80 system could be built into a book-shelf end



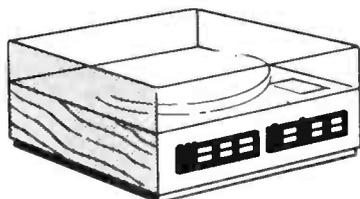
A 2½" strip along the edge of a shelf could be sufficient to contain a complete system



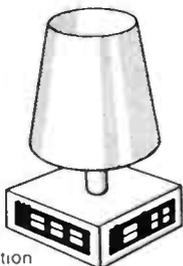
The modules mount very easily onto a playing plinth



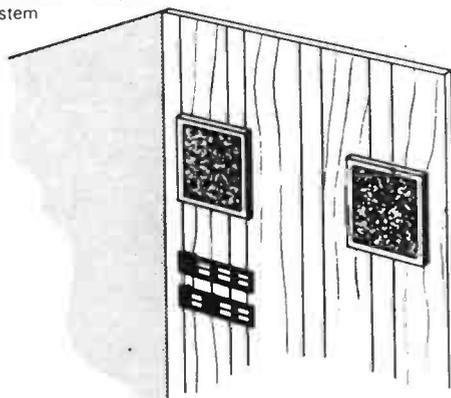
A novel application would be to build around the base of a lampshade



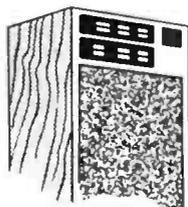Two Sinclair Q.16 loudspeakers suitably positioned together with Project 80 could be mounted on to a false wall.



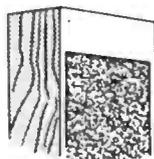Project 80 could be easily mounted onto a loudspeaker cabinet



When you have seen for yourself how fantastically slim and cleverly designed these modules are, further ways will suggest themselves in which they can become a pleasing part of your particular domestic environment.

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

PW 12

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

Should any defect arise in normal use, we will service it without charge. For damage arising from mis use a small charge (typically £1.00) will be made.

sinclair
World Record History

Sinclair Radionics Ltd.
London Road, St. Ives,
Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64311

Practical Wireless Classified Advertisements

Situations Vacant

Mobile Radio Survey Engineer

A ground floor opportunity exists for a young man to join a rapidly expanding radio-telephone Company, to assist the Southern Regional Sales force in Surveying and Demonstrating all mobile radio U.H.F./V.H.F. products

- Location:** All Southern England—based London or Home Counties.
- Experience:** An advantage but not essential as full training given.
- Salary:** Negotiable dependent on qualifications and experience.
- Prospects:** Excellent. Starting with eventual promotion to Sales Force for suitable applicant.
- We Require:** Ability to work on own. Initiative. Common sense. Clean driving licence. Reliability. Sense of responsibility. Willingness to get on with people.

If you like travelling, working out of doors and have even a slight sense of adventure, then we would like to hear from you

Write or telephone in the first instance to:—



Mrs Dyne, Personnel Officer,
Burndep Electronics (ER) Ltd., St. Fidelis Road,
Erith, Kent, DA8 1AU. Tel: Erith 39121

Service Sheets

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

Service Sheets

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
ALL AT 40p EACH

" PLEASE ENCLOSE LARGE S.A.E WITH ALL ENQUIRIES & ORDERS "
Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE
We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA 71 BEAUFORT PARK LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

Aerials

GENUINE FULL SIZE 18 element TV aerial as used by leading TV companies

FOR ONLY £2.20 incl. VAT +35p carr

Save £1's. We supply this genuine U.H.F. aerial for only £2.20, can be fitted outside or inside. Quality made technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions advice, Money Back Refund. Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters. SEND DIRECT TO DEPT. PW10 219 Mansfield Rd. Nottingham.

IMPERIAL TRADING AERIALS LTD.
the quality Aerial Specialists

BAINES HIGH FREQUENCY AERIALS

Postage paid on aerials
UHF Multibeam and Parabearms
PBM 12 £3.35. PBM 18 £4.30. MBM 30 £4.40. MBM 46 £6.90. MBM 70 £12.10. Log periodic £6.00.
VHF Stereobearms
SBM 1 £2.20. SBM 2 £2.95. SBM 3 £4.40. SBM 4 £4.80. SBM 6 £7.25. Stacking kit £2.20. Rotator £23. Loft kit 44p. 75/300 Balun £1.60. Masthead VHF/UHF amplifiers £5.75 and £7.75. Setback £4. Accessories: A large s.a.e. please. Coax 4p and 8p. 11 Dale Cres., Tupton, Chesterfield S42 6DR
Tel: 863755

LADDERS 'Special Offer' Unvarnished Triples, 9ft 7in closed—24ft 7in extended £13.20 delivered. Home Sales Ladder Centre (WLS2) Haldane (North), Halesfield (1) Telford, Shropshire. Tel: 0952 586644.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. * SERVICE SHEET CATALOGUE 25p
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS
RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

	PRICE
HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER by P. J. Guy. 142 pp.	£1.50
CREATIVE TAPE RECORDING by Vivian Capel. 183 pp. Shows advanced techniques.	£3.50
TAPE RECORDERS by H. W. Hellyer. 239 pp. A must for the enthusiast.	£2.25
UNDERSTANDING ELECTRONIC CIRCUITS by Ian R. Sinclair. 204 pp. 127 illus.	£3.50
UNDERSTANDING ELECTRONIC COMPONENTS by Ian R. Sinclair. 218 pp. 130 illus.	£3.50
FAULT LOCATION EXERCISES in Radio & TV Servicing by K. J. Bohman. VOL. 1.	£0.80
FAULT LOCATION EXERCISES in Radio & TV Servicing by K. J. Bohman. VOL. 2.	£1.35
WORLD RADIO TV HANDBOOK 1972. 26th Edition. 384 pp. Special reduced offer.	£1.10
WORLD RADIO TV HANDBOOK 1973. 27th Edition. 400 pp.	£3.00
TRANSISTOR AUDIO & RADIO CIRCUITS by Mullard Ltd. 283 pp. 2nd Edition.	£1.80
POWER ENGINEERING USING THYRISTORS by Mullard Ltd. Vol. 1. 228 pp.	£1.50
AUDIO TECHNICIANS BENCH MANUAL by John Earl. 182 pp. 114 Illustrations.	£3.00
MOBILE RADIO TELEPHONE EQUIPMENT HANDBOOK. Ccts. diagrams for PYE models	£4.00
ELECTRONICS IN MUSIC by F. C. Judd. 169 pp. Circuit designs and operation.	£3.15
HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES by B. B. Babani.	£0.40
HANDBOOK OF RADIO, TV, TUBE AND VALVE EQUIVALENTS by B. B. Babani.	£0.40
HI-FI, PA, GUITAR & DISCO THE ONE AMPLIFIER DESIGN HANDBOOK by Babani.	£0.75
RADIO AMATEURS OPERATORS HANDBOOK by Data Publications Ltd. 80 pp.	£0.45
SIMPLE SHORT WAVE RECEIVERS by Data Publications Ltd. 140 pp.	£0.80
SERVICING TRANSISTOR RADIO RECEIVERS by F. R. Pettit. 3rd Edition. 88 pp.	£0.75
USING AN OSCILLOSCOPE by D. W. Easterling. 108 pp.	£0.70
SERVICING WITH THE OSCILLOSCOPE by G. J. King. 176 pp. Illustrated.	£1.80
BEGINNERS GUIDE TO RADIO by G. J. King. 7th Edition. 204 pp. Illustrated.	£1.00
RADIO VALVE AND TRANSISTOR DATA by A. M. Ball. 9th Edition. 240 pp.	£0.75
NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good prices paid.	
Send large S.A.E. for FREE booklists. Postage on above books 1s 5p in the £1.00 (UK only).	

BELL'S TELEVISION SERVICES
ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commencing Jan. 2nd. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: London Electronics College, Dept. A12/, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.

Books and Publications

"WORLD RADIO TV HANDBOOK 1973" £2-80+11p. "Shortwave Voices of the World," £1-70, postage and VAT 11p. "SWL Address Book," to clear, £1-40+11p. "Confidential Frequency List," £1-70+11p. Books and full details from any bookshop, or in difficulty write to: David McGarva, PO Box 114, Edinburgh EH1 1HP.

Radio BOOKS

Handbk of Transistor Equip and Substitutes	45p
Handbook of Tested Transistor Circuits	45p
Rad & Electr Colour Codes and Data Chart	20p
Hi Fi, PA & Disc Amplifier Design H'bk	80p
Boys Bk of Crystal Sets and Simple Circuits	75p
Electronic Novelties for the Motorist	55p
Radio Servicing for Amateurs	25p
High Fidelity Loudspeaker Enclosures	45p
Practical Tape Recording Handbook	35p
Practical Stereo Handbook	35p
Practical Radio Inside Out	45p
Transistor Circuits Manual No. 1	20p
Transistor Circuits Manual No. 2	20p
Coil Design and Construction Manual	35p
Radio TV and Electronics Data Book	30p
Transis Circuits for Radio Controlled Models	45p
Pract Transistor Audio Amplifiers, Book 1	25p
Transistor Test Equip and Servicing Manual	30p
Handbook of Simple Transistor Circuits	40p
Modern Transistor Circuits for Beginners	45p
Sound and Loudspeaker Manual	55p
Resistor Colour Code Disc Calculator	15p
Manual Transistor Audio Amplifiers	45p
Practical Car Radio Handbook	45p
Radio TV and Industrial Tube & Valve Equip	45p
Transistor Circuits Manual No. 2	20p
Television Servicing Vol. 1	95p
Television Servicing Vol. 2	95p
Television Servicing Vol. 3	95p
Television Servicing Vol. 4	95p
Using an Oscilloscope	80p
Servicing Transistor Radio Receivers	85p
Television Trimbase Circuits	110p
Pal-D Colour Receiver Questions & Ans.	78p

All prices include postage & packing

FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

DENCO CLACTON LIMITED

355-7-9 Old Road

Clacton-on-Sea, Essex

Catalogue 20p post paid

S.A.E. all enquiries

WORLD RADIO TV HANDBOOK 1974 (published December) £3.15. Delivered direct from Denmark if ordered now. How to Listen to the World (late October), £2.00. Postage and VAT included. Every order acknowledged immediately. David McGarva, PO Box 114, Edinburgh EH1 1HP.

For Sale

MORSE MADE EASY!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only £3-30, Complete Course £4-50 P.P.I. etc. plus 10%.

(Overseas £1-00 extra) details only, 4p stamp. 01-660 2896

GSBSC (Box 11), 46 GREEN LANE, PURLEY, SURREY

TV LINE OUTPUT TRANSFORMERS. Tidman Mail Order Ltd., 236 Sandycroft Rd., Richmond, Surrey TW9 2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

AMIDON type toroid cores. Details SAE to T.M.P. (Electronic Supplies), Office address 3 Bryn Clyd, Leeswood, Mold, CH7 4RU.

AUDIO MIXER MODULES. Catalogue free, large S.A.E. Hillcrest Electronics, 123 Harstone Hill, Caterham, Surrey.

Wanted

TOP PRICES PAID FOR NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),

367 Kensington Street, Bradford 8, Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S** 55 Worcester Street, Wolverhampton.

EARLY WIRELESS LITERATURE before 1934. Johnson Raffles, Haverbreaks, Lancaster. Telephone 67770 evenings.

NEWNES RADIO and TV Servicing Books wanted. From 1960-1966, £2 paid per copy by return post. Any quantity bought. Bell's Television Services, Albert Place, Harrogate, Yorks. Telephone 0423 86844.

Receivers and Components

MINI MAINS TRANSFORMERS 30x30x37mm. Cool, quiet, British. Pri. 220/250V. Type MT3, 3-0-3V rms, 300mA, £1. MT7, 7-0-7V, 120mA, £1. VAT included. Use MT3 for 3V or 6V rectified d.c., MT7 for 9V or 18V. Circuits supplied. Mail order only, UK post 5p per order. Amatronix Ltd., 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

TAPE HEADS

Send stamp for lists.
R.D.I. Ltd.
Chilton Works,
Garden Rd.,
Richmond,
Surrey,
TW9 4NS

For valve and transistorized recorders from £2 ea.

TRANSISTOR. 465 kc/s IF Strip 75p. Amplifier 80p. Tone Control-Pre-Amp 75p. All with circuit. Record Player Cabinets £3-50; Radio Cabinets 12in x 6in x 2 1/2. Suitable for Ext. speakers; colours blue, brown or yellow, 60p. AM/FM tuning gangs 50p. Archer, 9 Pine Grove, Maidstone, Kent.

PRECISION

POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0.47µF:	±5% 80p;	±2% 40p;	±1% 50p
1.0µF:	±5% 40p;	±2% 50p;	±1% 80p
2.2µF:	±5% 50p;	±2% 60p;	±1% 75p
4.7µF:	±5% 70p;	±2% 90p;	±1% 81-18
6.8µF:	±5% 80p;	±2% 111p;	±1% 81-80
10µF:	±5% 81-10;	±2% 81-40;	±1% 81-80
15µF:	±5% 81-60;	±2% 83-10;	±1% 83-70

TANTALUM BEAD CAPACITORS—Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 8p each; 6 for 45p; 14 for 95p. Special pack 6 off each value (78 capacitors) £4-50.

NEW—TRANSISTORS. BC107, BC108, BC109, All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178—35p each or 3 for 85p.

POPULAR DIODES. IN914, 6p each; 8 for 45p; 18 for 90p IN916, 8p each; 6 for 45p; 14 for 90p; IS44, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5 mA. All new and marked. Price 7p each; 6 for 39p; 14 for 84p. Special offer 6 off each voltage (66 zeners) £3/65.

RESISTORS. Carbon film 5%. ±W at 40°C ±1W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special pack—10 of each value 2.2Ω to 2.2MΩ (730 resistors) £2.

440V A.C. CAPACITORS. 0.1µF, size 1 1/2in x 1/2in, 25p; 0.25µF, size 1 1/2in x 1/2in, 30p; 0.47 and 0.5µF, size 1 1/2in x 1/2in, 35p; 1.0µF, size 2 1/2in x 1/2in, 45p; 2.0µF, size 2 1/2in x 1/2in, 75p each. **SILICON PLASTIC RECTIFIERS** 1.5 Amp Brand new wire-ended DO27, 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p. 7p post and packing on all orders below £5. Please add 10% VAT to all orders.

MARCO TRADING
Dept. W12, The Maltings, Station Road
Wem, Shropshire

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10mfds.—4p, 22, 47—4 1/2p. (50V—5p.) 100—5 1/2p. (50V—7p.) 220—6p. (50V—9p.) Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2p, 0.04, 0.05—3p, 0.068, 0.1—3 1/2p. Polystyrene 63V. E12 series 10 pf.—1.000 pf.—2p, 1.200 pf.—10.000 pf.—3p. Miniature Highstab resistors, 5%, E12 series—Carbon Film 1/2 W 1Ω—10MΩ (10% over 1 Meg.) Metal Film 1/2 W 10Ω—2.2MΩ and 1W. 27Ω—10MΩ all 3 1/2p each. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

S-N-CHANNEL FETs 3810E—£1

Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc.

Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LIMITED

45 Station Road, Garrards Cross, Bucks.
Mail Order only

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p.p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

BUILD THE TREASURE TRACER MK III Metal Locator



- Vancap tuning
 - Excellent sensitivity and stability
 - Weighs only 22oz.
 - Speaker and earphone operation
 - Knocks down to only 17m
 - Prebuilt search coil assembly
 - Ministry approved design
 - Thoroughly professional finish
 - You only need soldering iron, screwdriver, pliers and snips
 - Completely new design
- Send s.a.e for leaflet

Complete kit Post 35p **£9.80** Built, tested and guaranteed Post 35p **£13.75**
 MINIKITS ELECTRONICS, 35a LANGLEY DRIVE, WANSTEAD, LONDON E11 2LM (Mail order only)

Trompus electronics

ALL BRAND NEW, no rejects. Money back warranty. 6V DIGITAL INDICATOR. 0.9DP socket and filter £1.29. LED TYPE 1" 0.9DP DIL £1.69 ea. LIGHT EMITTING DIODES. All with data and spec. TIL 209 1/4" dia. 22p. Red 1/4" dia. type 82p. Green 75p. INFRA RED beam LED £1.10. T68 GAS detector £1.69. ULTRASONIC TRANSDUCERS 22. DALO PCB red marking pen 67p. Copper board 12" x 8" BRP 40p. FeC etch PAK 19p. INTEGRATED CIRCUITS: with data if required. IC LITE SWITCH: Photo amp/trigger 40ma/11-20 relay or TTL 87p. DII relay £1.10



IC digital clock

MOS/LSI type 2 1/2 pin 4 or 5 digit 12/24 hr. chip with socket £18. PCB £1.69. KIT £20. 741 DII 6 pin 28p. 709 14p. DII 29p. 748 29p. 710 28p. 555 TIMER mono/astable osc. clock 59p. RE611LA-TOR8: 1A 5 to 20V £1.49. 723 57p. RECEIVER ZN414 £1.09. Mini Rx kit £1.99. 1310 stereo decoder for tuners £2.69. KIT £3.45. 74N TTL: Gates 7400 etc. 15p ea. 7413 27p. 7441 78p. 7447 £1.09. 7490 59p. 7492 67p. 74121 45p. DIL SOCKETS: New type 8/14/16 pin 13p. SEMICONDUCATORS: 1A rect. 50V 81p. 400V 6p. 2N3065 82p. BC107 7p. BC108 7p. BC109 7p. BC147/8/9 10p. BC167/8/9 13p. BC177/8/9 15p. BC182/3/4 10p. BC212/3/4 11p. BCY70/72 18p. BD131/2 55p. BFY60/61/62 13p. T1843 UJT 24p. 2N706 11p. 2N2889 12p. 2N2920 OY 8p. 2N2946 49p. 2N3053 17p. 2N3014 65p. 2N3702/3/4/8/9/10/11 All 9p ea. PETS: 2N3819E 18p. 2N3819 27p. 2N3823E 19p. ZENERS: BZ788 8p. RCR 400V: 1A 28p. TRANSFORMER 1A 6/12V £1. Resistors 11p. 450 & 470 mini IF transformers—Set 3 40p. CAPACITORS: Disc 22p1 to 0.1 µF 3p. Electrolytic 25V: 10, 50, 100 µF 6p. 1000 µF 15p. Presets 5p. CARBON POT4 11p ea. 500ohm 11p Dual 39p. **FLUORESCENT LIGHTS 12VOLT £2.79** 13" 8 watt fully built with diffuser 13W £3.79. V.A.T. You must add 10% (1/10) to all prices. FREE CAT. S.A.E. Data 25p ea. P & P 8p. CWO P.O. BOX 29, BRACKNELL, BERKS.

NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £3.50 +p. & p. 15p U.K. only. Illustrated catalogue of selected kits and components, 20p inc. VAT. P & P free.

ALL PRICES PLUS 10% VAT
 Gallon Trading Co.
 12, Burr Way,
 Corringham,
 Stanford-Le-Hope,
 Essex. SS17 9DE

INTEGRATED CIRCUIT and FET modules for construction of low-cost receivers, converters, pre-selectors, etc. SAE details.—P. R. Colledge, Glen Tor, Torrington, Devon.

TUNBRIDGE WELLS, Components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

TEXAN AMPLIFIER



- Pack
- | | |
|---------------------------|----------------|
| 1. P.C. Board | £2.00 p.p. 15p |
| 2. Chassis | 3.00 .. 25p |
| 3. Front Panel | 1.25 .. 15p |
| 4. Resistors | .80 .. 15p |
| 5. Capacitors | 2.90 .. 15p |
| 6. Semi Conductors | 8.00 .. 15p |
| 7. Transformer | 5.95 .. 25p |
| 8. Sundries | 2.50 .. 15p |
| 9. Cables | .40 .. 15p |
| 10. Instructions | .30 .. 15p |
| 11. 100K/100K control pot | .30 .. 15p |

VAT EXTRA

TELERADIO ELECTRONICS,
 325 FORE ST., LONDON, N.9.
 Tel. 01-807 3719

Send 4p for catalogue of Hi Fi Kits including the Quadrophonic System as in Practical Electronics.

MODEL CONTROL KIT. Receivers 4 channels. Transmitters 4 channels. Amplifier kits 1.5 watts mono. to 50 watt stereo. VHF kits. RF amp—mixers—oscillators. Up to 170 mhz. All kits by AMTRON. Catalogues, price lists—S.A.E. V.P. ELECTRONICS, Hayes Place, Eggbuckland, Plymouth PL6 5RL.

Miscellaneous

UNIQUE HI-FI SPEAKER SYSTEM

24 WATTS PEAK!

Beautiful bookshelf units in mahogany type finish. Employs infinite baffle enclosure with dual cone 8 ohm drive unit. Brand new with 6' leads.

£9.80 Per Pair P & P 60p

GREGG Electronics
 PW3, 24 Cranbourn Street
 Leicester Sq. London WC2

GLASS FIBRE P.C. BOARD. Large supplies available in single sided one ounce copper 2p per 3 sq. inches (under 1 foot). 75p per sq. ft. (over 1 foot). In double sided one ounce copper 1p per sq. inch (under 1 ft.), 11p per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

A.L.S. PRESENTS OUR E.C.100 WATT HI-FI AMPLIFIER

Ready drilled P.C.B. with full instructions only £2—plus 10p post. We also supply: Service Sheets, Manuals, Books etc. See our Main Advertisement in "TELEVISION" or send S.A.E. for details.

10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA (B)

AMTRON KITS. Your Devon Stockist. E. Wenmouth, 50 South Street, Exeter TE6 5EW.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Big 4 inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £1.35 for your Maxi-Volt now!
 - ★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5.90 for yours now!
 - ★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £2.20 now! (all prices include V.A.T., packing & postage.)
- Send remittance to:
BOFFIN PROJECTS,
 4 CUNLIFFE ROAD,
 STONELEIGH, EWELL, SURREY
 (Mail order only)
 Or for more details, send 15p for lists plus free design project sheet.

Darned Electronic Wizardry

by Dewtron (VAT extra)

Famous kits, e.g. waa-waa complete kit £2.95; Fuzz kit £5.50 auto rhythm modules P & P 20p min. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

Build your next project in a BEC (Book end chassis)



New improved with alloy trim on bottom of all cabinets. Now in easy to assemble kits.

GB3 (illustrated) ... 14" x 9" x 4" ... £4.00 P & P 45p. Other sizes. SAE with enquiries.
H. M. ELECTRONICS 275a, Fulwood Rd, Sheffield S10 3BD

STABILISED 6.75 & 9V. FROM SINGLE UNIT In-Car Entertainment.



AUTO ADAPTOR

Battery operated cassette recorders, radios etc., powered by 12v car battery by means of ingenious electronic adaptor—at virtually no cost. One lead included. Only £3.95 inc. VAT + 12p (p.p.). Also Mains Battery Eliminator £3.00. Lead (optional) 60p. State type of plug. Partic. 1—(optional) 60p. Products, 25 Wilbury Gdns., Hove, Sussex.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd. Stratford-on-Avon, Warwick.

BUILD IT in a DEWBOX quality cabinet. 2in x 2 1/2 in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

SAVE TIME SAVE TROUBLE SAVE MONEY

NEW: The COMPLETE TRANSISTOR MANUAL OF INTERNATIONAL CROSS-REFERENCES. 14 Languages. USA/Japanese/European. \$6,000 Equivalents.... This YOU must own.

Price: £2.42 (Ed. Aug. 73)

6 gang Socket Outlets.	£7 00
4 gang Socket Outlets.	£6 26
Alarmobile (Battery Model)	£2 50
Parking Timers (120 mins.)	£2 10
Infra-Red Room Heaters 2Kw	£36 00
Smith's Interval Timers	£5 38
Smith's Minute Timers	£5 39
Smith's Seconds Timers	£3 65
Folding Lecterns	£4 10
Lecterns De-Luxe (with stand)	£5 65

NEW: The Conway "MASTERANGER" Model 639. PROFESSIONAL Major Electronic Multi-Tester. 80 ranges, AC/DC. High Tension measurements extremely accurate and reliable. prices: From £115.00

Please send 6p for Full Catalogues & Price Lists. You will also be included in our Mailing List for regular information on NEW products in our range. Full Money Back Assurance on ALL Purchases. Carriage and V.A.T. is included in all our prices.

CROWLEY & COMPANY P.O. Box 35, Walton-on-Thames, Surrey KT12 3NA.
(Reg. No: 1787003) (V.A.T. Reg. No: 212 5318 06)

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp for details. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwick.

TAPE DICTAPHONES: Grundig Stenorette, Graetz, untested/some working £4-25 postage 50p. "Markonics," 327 Tildesley Rd., London SW15.

EXPERIMENTERS! Hundreds of unusual items cheap. Catalogue 5½p. Grimsby Electronics, 64 Tennyson Road, Cleethorpes, Lincs. (Mail Order Only).

ALUMINIUM BOXES

	FOR VEROBOARD	
Type AD7	5 1/2in x 2 1/2in x 1 1/2in	29p + 8p P&P
.. AD8	4 in x 4 in x 1 1/2in	29p + 8p P&P
.. AD9	4 in x 2 1/2in x 1 1/2in	29p + 8p P&P
.. AD10	5 1/2in x 4 in x 1 1/2in	35p + 8p P&P

ALSO FULL RANGE OF 'NEWRAD' PROFESSIONAL CASES FROM UNDER £2
ADFNIC (PW), 18 Yew Tree Lane, Ashley, New Milton, Hants BH25 5BA.
C.W.O. Mail Order Only.

AERIAL BOOSTERS—£3-25

We make three types of Aerial Boosters: B45-UHF 825, B12-VHF 405, B11-VHF RADIO

VALVE BARGAINS

ANY 5-50p, 10-75p, 50-£3.30—
ECC82, ECL80, EB91, EBF80, EF80, EF85, EF183, EF184, EY88, PCC84, PCC89, PCC189, PC87, PCF80, PCF86, PCF805, PCF806, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, PC86, PC88.

19" UHF/VHF (BBC2) £6-00

Thorn-850 or Pye, with set of spare valves. Carriage £2-00 (Untested).

100 MIXED RESISTORS—65p

± to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Ceramic Capacitors from 1PF to 8200PF (our choice) 65p.

BARGAINS PARTS

Translator UHF Tuners—£2-00, 500K-ohms V/C with Switch—20p. 50 mixed Tuner Valves—£2-25. Brand New Transistors BF173, BC171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order. Money back guarantee. S.A.E. for leaflets.

ELECTRONIC MAILORDER (BURY) LTD.


82 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3038

BURGLAR AND FIRE ALARMS. Amazing new kit £23.50. Full range of kits and equipment from Castle Alarms, P.O. Box No. 6, Windsor, Berks.

CONSTRUCTION AIDS—Screws, nuts, spacers etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. Ramar Constructor Services, 29 Shelbourne Rd., Stratford on Avon, Warwick.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

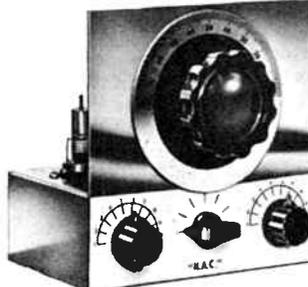

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hants, etc.

1974 "DX" RECEIVER

Complete kit—Price £4-30 (incl. p. & p. V.A.T.). Customer writes: "Australia, India and America at loud volume."—I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents."

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits & components.

EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

Versatile
10 in ONE



MIN-LAB

Comprising:

- AC and DC Voltmeter
- Ohm Meter
- Capacitance Substitution
- Battery Supply
- RF Signal Generator
- RF Field Strength Indicator
- Audio Generator
- Resistance Substitution
- DC Ammeter
- RF Signal Generator

This new, unique instrument combines all you need for testing. Money back if not satisfied. **£11-95** includes VAT & p. & p. Cash with order or send s.a.e. for illustrated data sheet to:

J. H. ASSOCIATES LTD. (DEPT. PW)
Cricketfield Lane, Bishop's Stortford, Herts.

SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER



WITH LIGHT DIMMER

Max. load 2kW at 250v. A.C.

Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. Price £7-90 inc. VAT

EXTRA FACILITIES. Push-button for Manual Pulsing 25p extra. Photocell for turning on the lights as the ambient light decreases, 75p extra.

3 CHANNEL FILTER UNIT

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested. Price £3-50 inc. VAT

OIL WHEEL PROJECTOR

Build your own using our

MULTI-COLOURED OIL WHEEL AND MOTOR KIT



Suitable for mounting on virtually all Slide Projectors.

Kit contains:

- ★ 6" dia. or 4" dia. OIL WHEEL (please state size required when ordering).
 - ★ Suitable Miniature mains motor.
 - ★ Full instructions.
- For Professional Discotheque use or home enjoyment. Price £7-15 inc. VAT

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

- Pack No.
- 1 500 Carbon resistors, 1, 1, 1, 2 watt.
 - 2 100 Electrolytic Condensers.
 - 3 250 Ceramic, Polystyrene, Silver Mica etc. condensers.
 - 4 250 Polyester, Polycarbonate, Paper, etc. condensers.
 - 5 25 Potentiometers, assorted.
 - 6 250 High-stab, 1%, 2%, 5% resistors.
 - 7 50 Assorted Tagstrips.
 - 8 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
 - 9 25 Assorted switches, rotary, lever, micro, toggle, etc.
 - 10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED.
£1 + 25p p.p. per pack, £5 for 5 packs p/free

C. T. ELECTRONICS

Mail Order, Retail Shop, Components—
267 Acton Lane, LONDON, W4 5DG 91-994-8275

Warehouse, Test Equipment, Surplus Goods—
26-24 Beaumont Road, LONDON, W4


Audio Accessory Shop, Components—
17 Turnham Green Terrace, LONDON, W4

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-16 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE \pounds 11-60. P. & P. 40p.

DE LUXE STEREO AMPLIFIER

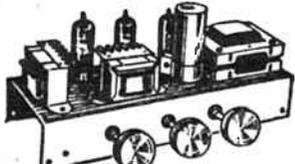

A.C. mains 200-240 v. U.S.A. v. heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Two 5000 μ F Pentodes. 1 x E2290 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE \pounds 29-90 P. & P. 50p.

POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v, and 7 1/2v, and 9v, and 12v. at 1 amp continuous (1 amp intermittent).

Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE \pounds 5-00 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For T03, complete with mica's and bushes. Size 2 1/2" x 3" approx. 28p pair. P. & P. 6p.

HIGH GRADE COPPER LAMINATE BOARDS 8" x 6" 5 for 55p P. and p. 25p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price \pounds 2-10 P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 0-0-9 at 500mA. \pounds 1-00. P. & P. 25p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. \pounds 1-10. P. & P. 25p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. \pounds 1-65. P. & P. 35p.

CENTRE ZERO MINATURE MOVING COIL METER. 100A. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 88p. P. & P. 12p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U., Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price \pounds 1-00 P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents 80p
Transistor Equivalents 90p
Transistor Characteristics \pounds 1-15
POST FREE.
All three together \pounds 2-60

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias. 95p. Post Free

Open 9-5.30 Monday to Friday. 9-5 Saturday
Early closing Wed.
A few minutes from South Wimbledon Tube Station.

RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing.
LATEST B.S.R. C109/C129 AUTOCLEANER UNITS with latest stereo/mono compatible cartridge \pounds 7-60 + 80p P. & P.
GARRARD SP25 Mk III with heavy precision machined die cast turntable \pounds 10-66. carr. 55p.

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, 81.65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover).
NOW ONLY \pounds 4-95. P. & P. 70p.

LATEST ACOS GP91/180 mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. \pounds 1-50 P. & P. 15p.

SONOTONE STAINLESS COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY \pounds 2-80 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. \pounds 2-80. P. & P. 15p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/78/80. \pounds 1-63 P. & P. 15p.
LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 or stereo records on mono equipment. Only \pounds 1-60 P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE \pounds 4-40 P. & P. 60p
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE \pounds 5-85 P. & P. 60p.

SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 15" high x 10 1/2" wide x 6" deep. Fitted with F.M.I. Ceramic Magnet 15" x 5" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE \pounds 9.25 Carr. 75p

Cabinet Available Separately \pounds 4-95 Carr. 65p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter \pounds 7-15 Carr. 75p

HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely brand new completely wired and tested with good quality output transformer. **PRICE \pounds 3-30** P. & P. 40p BARGAIN PRICE

LOUDSPEAKER BARGAINS
5in. 3 ohm \pounds 1-05. P. & P. 15p. 7 x 4in. 8 ohm \pounds 1-15. P. & P. 20p. 10 x 6in. 3 or 15 ohm \pounds 1-90. P. & P. 30p. E.M.I. 8" x 5in. 3 ohm with high flux magnet \pounds 1-62. P. & P. 20p. E.M.I. 13" x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm \pounds 2-50. P. & P. 30p. E.M.I. 13" x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network \pounds 4-65. P. & P. 30p.
EMI Ceramic magnet heavy duty tweeter. Approx 3 1/2". Available 3 or 8 or 15 ohms \pounds 1-25 + 20p. P. & P.
BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly \pounds 7-50. Guitar models: 25w. \pounds 7-60 35w. \pounds 9-85. P. & P. 40p



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS
With large ceramic magnet and plasticised cone surround.
8 ohm impedance. \pounds 2-70. P. & P. 85p.

Also available specification as above but size 10" x 6" \pounds 2-70 and size 8" round \pounds 2-60. P. & P. 35p.

LIMITED NUMBER EMI 2 1/2" 8 ohm Tweeters. Mounted on flat bracket size 2 1/2" wide x 7 1/2" long. 70p per pair plus 15p P. & P.
Ex equipment but new and tested 70p per pair plus 15p P. & P.


12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3, 8 or 15 ohm \pounds 2-45. P. & P. 35p. 85 ohm SPEAKERS 3in. only 70p P. & P. 25p.

"POLY PLANAR" WATER-TYPE. WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 10oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only \pounds 6-65 each. P. & P. 34p.

VYNAIR & BEXINESPEAKERS & CABINET FABRICS app. 54 in. wide. Our price 85p yd. length. P. & P. 25p per yd. (min. 1 yd.). S.A.E. for samples.

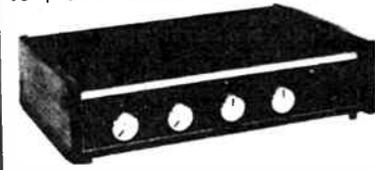HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal Cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power b.c. 150W. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

AMPLIFIER KIT \pounds 11-95 P. & P. 25p
(Magnetic Input components 35p extra)
POWER PACK KIT \pounds 3-30 P. & P. 35p
CABINET \pounds 3-30 P. & P. 35p

(Post Free if all units purchased at same time)
Full price sales service

Also available ready built and tested \pounds 28-10. Post Free.
Note: The above amplifier is suitable for feeding into mono sources into inputs (e.g. mike, radio, turn record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi Fi Discotheque use, etc.




3-VALVE AUDIO

AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only \pounds 5-50. P. & P. 45p.
HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employ entirely different and advanced circuitry. Complete set of parts, etc. \pounds 4-60. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished metal chassis amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EP86 and E280 rectifier. Simple instruction booklet 15p + 8AE (Free with parts). All parts sold separately. ONLY \pounds 8-80 P. & P. 60p. Also available ready built and tested \pounds 12-10 P. & P. 70p.

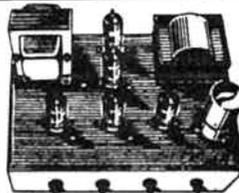

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexfoam ear-muffs. Wired and fitted with standard stereo jn jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE \pounds 3-30. P. & P. 25p.

PRICES NOW INCLUDE VAT

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold"—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPW11, Aldermaston Court, Reading RG7 4PF.

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kington Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage): For one year to any part of the world £2-6s.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a multi-

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL	<input type="checkbox"/> DRAUGHTSMANSHIP	<input type="checkbox"/> A.B.T. Clerk of Works
<input type="checkbox"/> Society of Engineers—A.M.S.E. (Mech.)	<input type="checkbox"/> Institute of Engineers (A.M.I.E.D.)	<input type="checkbox"/> Construction Surveyors Institute—L.C.S.I.
<input type="checkbox"/> Institute of Engineers & Technicians	<input type="checkbox"/> General Draughtsmanship	<input type="checkbox"/> CITY & GUILDS General Building (all branches)
<input type="checkbox"/> I.E.E.	<input type="checkbox"/> Elec. Draughtsmanship	<input type="checkbox"/> Heating & Vent.
<input type="checkbox"/> CITY & GUILDS	<input type="checkbox"/> Archtctural Draughtsmanship	<input type="checkbox"/> Inst. Clerk of Works
<input type="checkbox"/> Gen. Mech. Eng.	<input type="checkbox"/> Technical Drawing	<input type="checkbox"/> Site Surveying
<input type="checkbox"/> Maintenance Eng.		<input type="checkbox"/> Health Engineering
<input type="checkbox"/> Welding		<input type="checkbox"/> Road Construction
<input type="checkbox"/> Gen. Diesel Eng.	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS	<input type="checkbox"/> Quantities, Estimates
<input type="checkbox"/> Sheet Metal Work	<input type="checkbox"/> CITY & GUILDS, Radio, TV, Electronics	<input type="checkbox"/> Hydraulics
<input type="checkbox"/> Eng. Inspection	<input type="checkbox"/> CITY & GUILDS	<input type="checkbox"/> Structural Eng.
<input type="checkbox"/> Eng. Metallurgy	<input type="checkbox"/> Telecons.	
<input type="checkbox"/> ELECTRICAL & ELECTRONIC	<input type="checkbox"/> Gen. Radio & TV Eng.	<input type="checkbox"/> GENERAL
<input type="checkbox"/> Society of Engineers—A.M.S.E. (Elec.)	<input type="checkbox"/> Radio Amateurs Exam	<input type="checkbox"/> Agricultural Eng.
<input type="checkbox"/> CITY & GUILDS	<input type="checkbox"/> Electrical Installations	<input type="checkbox"/> Council of Eng. Institutions
<input type="checkbox"/> Gen. Electrical Engineering	<input type="checkbox"/> Electrical Maths	<input type="checkbox"/> Farm Science
<input type="checkbox"/> Electrical Engineering	<input type="checkbox"/> Computer	<input type="checkbox"/> Plastics
<input type="checkbox"/> Installations	<input type="checkbox"/> Electronics	
<input type="checkbox"/> Electrical Maths	<input type="checkbox"/> Electronic Eng.	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
<input type="checkbox"/> Computer	<input type="checkbox"/> Practical Radio & Electronics (with kit)	
<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL	<input type="checkbox"/> MANAGEMENT & PRODUCTION	
<input type="checkbox"/> Institute of the Motor Industry	<input type="checkbox"/> Institute of Cost & Management Acctns.	
<input type="checkbox"/> A.M.I.I.	<input type="checkbox"/> Computer Programming	
<input type="checkbox"/> M.A./I.M.I.	<input type="checkbox"/> Works M'tent.	
<input type="checkbox"/> CITY & GUILDS	<input type="checkbox"/> Work Study	
<input type="checkbox"/> Auto Eng.	<input type="checkbox"/> Gen. Production Eng.	
<input type="checkbox"/> Gen. Auto Eng.	<input type="checkbox"/> Estimating & Planning	
<input type="checkbox"/> Motor Mechanics	<input type="checkbox"/> Storekeeping Management	
<input type="checkbox"/> Auto Diesel Eng.	<input type="checkbox"/> Skills	
<input type="checkbox"/> Garage M'tent.	<input type="checkbox"/> Quality Control	
<input type="checkbox"/> ARB Aero Engineering Certs.		
<input type="checkbox"/> Gen. Aero Eng.		
<input type="checkbox"/> CONSTRUCTION		
<input type="checkbox"/> Society of Engineers—A.M.S.E. (Civ.)		
<input type="checkbox"/> Institute of Building—L.I.O.B.		

G.C.E.
— choose from 58 'O' & 'A' level subjects.

Coaching for many exams, including C & G and assistance in ONC/HNC.

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW11 QN
Aldermaston Court, Reading RG7 4PF BPW11

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____

Accredited by C.A.C.C.
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

DONT RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES
 Order your latest Henry's Catalogue Price 55p post paid complete with Discount Vouchers

Henry's
Catalogue




You pay less
VAT with Henry's
Low Prices

BUILD THE TEXAN

Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2". 6-IC's, 10 transistors, stabilisers Gardners low field transformer, Fibre Glass PC Panel, complete chassis

20 + 20 WATT IC STEREO AMPLIFIER

As featured by Practical Wireless 1972

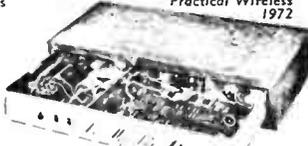

work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES** — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES. On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21 30p. Distributed by Henry's throughout UK. FREE—Teak cabinet with complete kit.

Kit price **£28.50** (+VAT +50p carr/packing) or built and tested **£35.00** (+VAT +50p carr/packing) as illustrated.

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

DISCO MINI A complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98.50**
 As above but with Slider Controls **£118.50**
 100 watt amplifier for above **£42.50**
 SL100 100 watt mixer/amplifier with slider controls **£69.00**
 R50 50 watt mixer/amplifier **£49.50**
 R100 100 watt mixer/amplifier **£57.50**
DISCO AMP 100 watt mixer/amplifier chassis unit. **£69.50**
DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers)
 SDLI (rosary controls) **£49.50**
 SDLI (slider controls) **£38.50**
DISCO VOX (slider controls) the complete disco preamp **£69.50**
 DJ100 100 watt power amplifier for above **£42.50**
 DJ30L 3 channel 3kw sound to light **£31.50**
 DJ40L as 30L plus built in microphone **£41.95**
DIMAMATIC I kW adjustable speed auto dimmer **£25.00**
 Carlboro Reverberation Unit **£44.00**
SCENE STROBE £19.00. ROAD STROBE £25.00. SUPER STROBE £45.
 Disco anti-feedback microphone **£11.95**
 Cole 150 watt liquid wheel projector **£22.50**
 150 watt QI liquid wheel projector **£50.00**
 150 watt QI cassette wheel projector **£50.00**
 5pape Effects and liquid cassettes large range of patterns **£6.00**
 6 inch Liquid wheels **£5.00**
 Mini spot bank fitted 3 lamps **£12.95**
 Auto Trilite (mini with flashers) **£17.00**
 Bubblemaster with 1 gall. liquid Mixers/Mics/Speakers/Lighting **£41.15**

U.K.'s largest range of Disco Lighting. **FREE STOCK LIST REF. No. 18 ON REQUEST**
AKG / RESLO / DJ / CARLSBRO / EAGLE MICS., STANDS, MIXERS, CABINETS, CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURN-TABLES, PUBLIC ADDRESS COM-PONENTS.



All prices carr. paid (UK) (VAT EXTRA)
 Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

TEXAN STEREO SYSTEM PLUS PRICE SAVINGS



The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200 20 watt Speaker-Tweeter systems size 21" x 12" x 10" and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. System 25 uses Garrard SP25 Mk III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied.

System 25 (list approx. £109) **£79.50**
 System 76 (list approx. £117) **£89.50**
 (plus 10% VAT and plus £1.45 carr/packing)

Barclaycard/Access, call, write or phone, your order 01 402 4736 **EASY TERMS FOR CALLERS**

NEW SINCLAIR PROJECT 80

Stereo Pre-Amplifier **£11.95**
 Audio Filter Unit **£6.95**
 Z40 15 Watt Amplifier **£5.45**
 Z60 25 Watt Amplifier **£6.95**
 PZ5 Mod. for 1 on 2 Z40 **£4.98**
 PZ6 Mod. (5 Tab) 1 on 2 Z40 **£7.98**
 PZ8 Mod. (5 Tab) 1 on 2 Z60 **£7.98**
 TRANSFORMER FOR PZ8 **£2.95**

NEW FM TUNER STEREO DECODER £11.95 £7.45

All items post paid. Best price on request.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. IF stages. LED indicators. Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p). Henry's are sole distributors UK and Europe.



KIT PRICE **£21.00 (+ VAT)**
 or built and tested **£24.95 (+ VAT)**

LOW COST HI-FI SPEAKERS
 SPECIAL OFFERS
 EMI 13" x 8"—full range speakers (post 20p each or 30p pair)
 *150TC—8 ohms Twin Cone 10 watt £2.20 each or £4.00 pair.
 *450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms £3.80 each or £6.90 pair.
 EW 15 watt 8 ohms C/o Tweeter £4.30 each or £7.90 pair.
 350 20 watt C/o Tweeters 8 or 15 ohms £7.50 each or £14.20 pair.
 * Polished wood cabinet £4.60 post 35p.



C 60	3 for	6 for	10 for	25 for
C 90	£1.00	£1.80	£2.80	£6.75
C 120	£1.30	£2.37	£3.20	£10.25
C 150	£1.62	£3.15	£5.00	£12.25

Quantity and trade enquiries, invited
 LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian £1.36 per course. £5 for any 4.

LOW COST HI-FI SPEAKERS

FR4	4"	5 watt	£4.00
FR65	6 1/2"	10 watt	£5.50
FR8	8"	15 watt	£7.60
FR23	9 x 6"	15 watt	£6.00
BASS & MID RANGE—8 ohms (post 20p)			
AA12	5"	15 watt	£3.20
B110	5 1/2"	15 watt	£5.60
B200	8"	15 watt	£6.45
B139/2	13" x 8"	20 watt LF	£10.25
TWEETERS AND CROSSOVERS (post 20p)			
K2006	10 watt	8 or 15 ohms	£1.90
FHT6	15 watt	8 ohms	£3.20
K2011	30 watt	8 ohms	£3.75
T27	KEF		£6.25
Axcent 100	30 watt	8 ohms	£6.90
K4009	1kHz/5kHz C/o		£2.00
SN75	3kHz var. C/o		£1.75
SPEAKER KITS (carr. etc. 35p)			
20-2	8"	30 watt	£10.00 each
20-3	8"	40 watt	£15.00 each
LINTON 2		20 watt	£15.95 pair
GLENDALE 3		30 watt	£28.95 pair
DOVEDALE 3		50 watt	£42.00 pair
KEF KK2			£20.40 each
KEF KK3			£32.00 each

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines etc.



£24.95 Also available assembled **£27.22**
 + VAT. ready to use. + VAT.

10% VAT to be added to all orders. Prices and descriptions correct at time of press. E & OE. Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791.

See pages 788—790 of this magazine

Henry's RADIO LIMITED
 EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01 402 8381
 354-356 High Fidelity and Tape Equipment 01-402 5854/4736
 309 PA-Disco-Lighting High Power Sound 01-723 6963
 303 Special offers and bargains store
 All mail to 303 Edgware Road, London W2 1BW

Ops
9 am - 6 pm
6 days a week
All stores
open all day
Saturday