

PRACTICAL WIRELESS

JANUARY
1974

20p

ULTRASONIC REMOTE CONTROLLER





also:
↓

AF/HF/VHF TROUBLE-TRACER: CURING
RADIO INTERFERENCE IN AUDIO EQUIPMENT

look! electronics really mastered

... practical
... visual
... exciting!

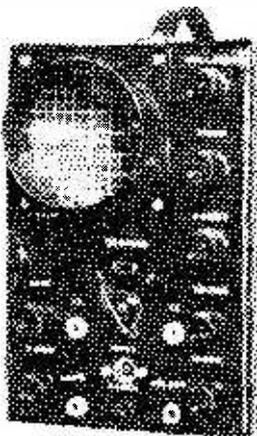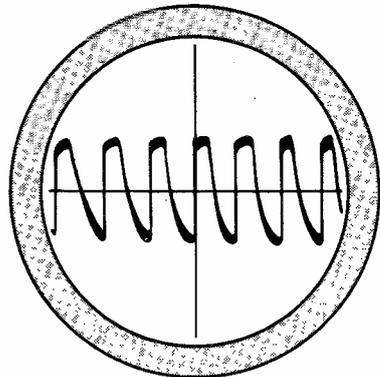no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

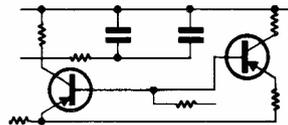2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**,
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL14

special free gift also to all our students

PRACTICAL WIRELESS

VOL. 49 NO. 9

ISSUE 803

JANUARY 1974

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR Morris A. Colwell

ASSISTANT EDITOR

Lionel E. Howes, G3AYA

ART EDITOR Peter Metalli

TECHNICAL EDITOR

Eric Dowdeswell, G4AR

PRODUCTION & NEWS

EDITOR Colin R. Riches

PROJECTS SUB-EDITOR

Geoffrey C. Arnold

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Jenny Maunder

01-634 4292

Susan Corne

ADVERTS. MANAGER

01-634 4293

Roy Smith

CLASSIFIED ADVERTS.

01-634 4301

Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rates for one year to any part of the world £2.65 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.10) and indexes (11p) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of *Practical Wireless* and *Television* only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

834 "CONDITIONED"—Leader article and February preview

835 NEWS . . . NEWS . . . NEWS . . .

845 TELEVISION—Coming in the January issue

846 PRODUCTION LINES—Products reviewed by Colin Riches

859 NEXT MONTH IN PRACTICAL WIRELESS

870 HOTLINES on recent developments by Ginsberg

878 ON THE AIR—Reports on Broadcast Bands

878 Short Wave—Malcolm Connah

881 Medium Wave—Charles Molloy

881 VHF/FM—Simon David

882 Amateur Bands, Short Wave/VHF—David Gibson G3JDG

● CONSTRUCTIONAL

836 TROUBLE TRACER, Part 1—F. G. Rayer

849 MODULE CABINET—M. G. Skeet

853 EXPERIMENTAL WORKSHOP, Astable Multivibrator
M. J. Hughes, M.A.

860 ULTRASONIC REMOTE CONTROLLER, Part 1—Roland Perry

871 I.C. AMPLIFIER for the "POP STAR"—F. G. Rayer

873 GOING QUADRAPHONIC—PROJECT Q4, Part 4—D. Bollen

885 TAKE 20 No. 56 Trafficator Audio Repeater—David Andrews


● OTHER FEATURES

865 TECHNICROSS No. 2

868 1973 AUDIO FESTIVAL AND FAIR—Colin Riches

877 CURING RADIO INTERFERENCE—Brian L. Phillips

RSC GROUP/DISCO UNITS

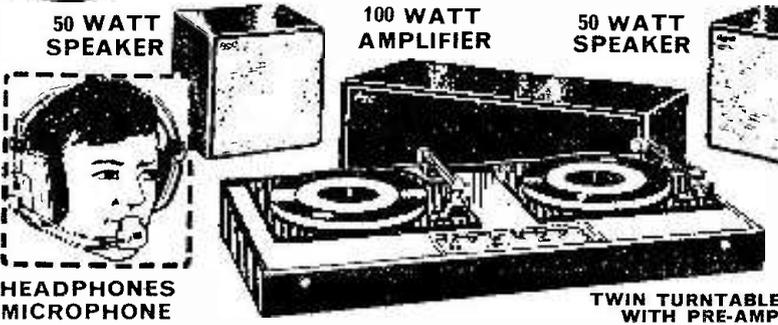

HEADPHONES
MICROPHONE

TWIN TURNTABLE
WITH PRE-AMP



RSC DISCO-MASTER

DISCOTHEQUE CONSOLE with integrated power supply. 100w OUTPUT TWIN JACK OUTPUT SOCKETS Inc. twin Garrard SP25 Mk111 or BSR Macdonald MP60 type turntables, Pick-ups with high compliance cartridges and diamond styli. Separate volume controls for each turntable.

FULL MONITORING FACILITIES plus Treble and Bass controls. Separate input for mic. with vol. control switch. Rexine covered cabinet size approx. 32 1/2" x 16 1/2" x 7 1/2" with lid. **ONLY £99-75**
Terms: Deposit £20 and 12 monthly payments £7-60 (Total £111-20). Carr. £2-50.

PACKAGE OFFER

- Units listed below
(a) 100w POWER AMPLIFIER
(b) PAIR OF HI-FI HEAD- PHONES
(c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)
(d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"
(e) RSC TDI DISCO CONSOLE

(a) (b) (c) (d) & (e) **£149-95**
Carr. £8-00

Terms De/posit £30 and 18 monthly payments of £8-33 (Total £179-94).

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonotone or Acos Cartridges with diamond styli. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid. see illustration on left
Or Dep. £9-95 and 12 mthly pymts £5-85 (Total £80-15)
£69-95
Carr. £1-50

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.



'POP' 100

18" 100 Watt
14,000 Gauss
8/15Ω
£25-95
Dep. £5-95 and 9 mthly payments £2-56 (Total £28-99)

'POP' 60

15" 60 Watt
14,000 gauss
8/15Ω
£14-75
Dep. £2-75 and 9 mthly payments £1-50 (Total £17-25)

'POP' 50

12" 50 Watt
13,000 gauss
15Ω
£11-99
Dep. £2-99 and 9 mthly payments £1-28 (Total £14-51)

PAIR SUITABLE ALL PURPOSES
FOR BASS GUITAR, ELECT. ORGAN, ETC

R.S.C. COLUMN SPEAKERS

All types 15 Ohms covered in Rexine and Vynair
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback howl characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £2-95 and 9 mthly payments £2-43 (Total £24-82) Carr. 65p. **£21-95**

TYPE C318 50 WATTS Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £4-72 & 9 mthly pymts £3-58 (236-94) Carr. 85p. **£32-72**

TYPE C4100 100 WATTS inc. four 12" 50 watt speakers for conservative rating. Extra heavy construction. Size approx. 58 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £15-50 & 12 mthly. pyts. £5-46 (Total £81-02). Carr. £1-50 **£71-50**

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free
£7-95
or Dep. £1-25 and 9 mthly payments 89p (Total £9-26)

DISCO PACKAGE OFFER £45

Pair BSR MP60 T/tables GP91 PU Cartridges. FAL Disco Pre-amp. Total Rec. Ret. Price £50-11 Carr. £1

GROUP/DISCO EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 25/2 25W L/SPEAKERS Terms: Deposit £7-50 and 12 monthly payments of £4-29 (Total £58-98)	£39-93 £15-90 £51-50 carr. £1-10
F.A.L. PHASE 50 MK.III AMPLIFIER PR. FANE POP 50 L/SPEAKERS Terms: Deposit £9-50 and 12 monthly payments of £4-88 (Total £68-08)	£39-93 £23-98 £59-50 carr. £1-10
F.A.L. PHASE 50 MK.III AMPLIFIER PAIR L12/20 25W L/S in cabinets Terms: Deposit £10 and 12 monthly payments of £5-17 (Total £72-04)	£39-93 £26-30 £63 carr. £1-35
F.A.L. PHASE 100/2 AMPLIFIER 4 FANE POP 50 L/SPEAKERS Terms: Deposit £20 and 18 monthly payments of £6-85 (Total £134-30)	£69-85 £47-96 £110 carr. £2

MINSTREL 8W GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: Deposit £2-75 and 9 monthly payments £2-17 (Total £22-28). **£19-95**
Carr. free




FANE CRESCENDO SPEAKERS

Full range available at ALL BRANCHES

FAL PHASE 50 Mk.III AMPLIFIER 50 WATT.

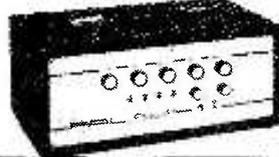Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/s 3 to 30 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £8-93 & 9 monthly payments £4-22. Total £44-81. **£39-93**
Carr. 85p.



RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.

For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £8-95 and 12 monthly payments £4-97 (Total £68-59). Carr. £1-50 **ONLY £59-95**
S.A.E. for leaflet



HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH
L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50 **£37-95**
Or deposit £3-95 and 9 monthly pyts. of £4-34. Total £43-81
L12/20 12" 20-25 WATT 13,000 lines 15 ohms
Dep. £2-15 & 9 mthly pymts £1-50 (Total £15-65) Carr. 55p. **£13-15**
L12/10 10-15 Watt veneer finish cabinet 12" unit 8-15 ohm. Size approx. 14" x 14" x 9". Carr. 50p. Dep. £1-25 & 9 mthly pymts £1-06 (Total £10-79)




CREDIT TERMS AVAILABLE ON PURCHASES OVER £10 (Kits Excepted) INTEREST CHARGES REFUNDED ON CREDIT SALES Settled in 3 months

RSC BASS-REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.

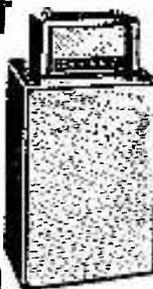- ★ Two extra heavy duty 12in. 50w Loudspeakers.
- ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £15-50 & 12 monthly payments of £5-56. (Total £82-12). Carr. £2-50 **£72-50**




NOW SIX NEW BRANCHES

- BOLTON 23 DEANSGATE
 - COVENTRY 17 SHELTON SQUARE
 - DONCASTER 3 QUEENSGATE WATERDALE CENTRE
 - NOTTINGHAM 19/19A MARKET ST
 - STOCKPORT 8 LITTLE UNDERBANK
 - SUNDERLAND 5 MARKET SQUARE
- NEW LARGER PREMISES AT HULL, DARLINGTON, NEWCASTLE & DERBY See Addresses



All items subject to availability. Prices correct at 25.10.73 E. & O.E.

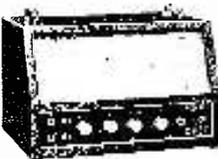HI-FI CENTRES LTD.
MAIL ORDERS & EXPORT ENQUIRIES TO:—
AUDIO HOUSE, HENCONNER LANE, LEEDS, 13.
Tel: Pudsey (09785) 77631.
TERMS C.W.O. or C.O.D. No C.O.D. under £1.
POSTAGE 28p EXTRA UNDER £2. 38p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED.
S.A.E. PLEASE WITH ENQUIRIES.
SUPPLIERS TO GOVT. DEPTS. H.M. FORCES.
EDUCATION AUTHORITIES & HOSPITALS. Etc.
MAIL ORDERS MUST NOT BE SENT TO SHOPS




RSC GP30 HI-FI AMPLIFIER For Guitar, Vocal or Instrumental Group

A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 9 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 9 monthly payments of £2-75 (Total £29-15). **£25-85**
Carr. 75p

FAL PHASE 100/2 AMPLIFIER

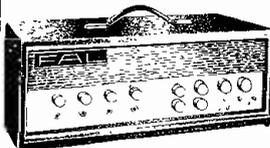100 WATTS MUSIC RATING. Solid State. Sep. Bass and Treble Controls. 4 separate controlled inputs plus master control. Output for speakers 3-30 ohms. Includes protective circuit against damage from short circuits. Terms: Deposit £7-85 & 12 monthly payments £6-05 (Total £80-45). **£69-85**



FAL TWIN CHANNEL AMPLIFIERS

Solid State. 4 sep. controlled inputs plus master volume control. Individual Bass and Treble controls. Output for speakers 3-30 ohms. Protective circuitry against damage from short circuits. **FAL 'SUPER 50'** 50 WATTS MUSIC RATING **£59-50**
Terms: Dep. £8-50 & 12 mthly. pymts. £4-97 (Total £68-14)

FAL 'SUPER 100' 100 WATTS MUSIC RATING **£79-95**
Terms: Dep. £11-95 & 12 mthly. pymts. £6-63 (Total £91-51). Prices above include protective dust cover.

HUGE DISCOUNTS ON LEADING BRAND TAPE AND TURNTABLE UNITS

CREDIT TERMS AVAILABLE
Minimum Deposit 10%

DISCOUNT WAREHOUSE PRICES ON LEAK, WHARFEDALE etc. etc.—visit your nearest RSC Hi Fi Centre

AKAI GXG 40D Tape Unit £62.95 (Rec. Price £89.74) Carr. £1
AKAI 4000DS Tape Unit £68.95 (Rec. Price £97.50) Carr. £1
AKAI 1721L Tape Unit £66.95 (Rec. Price £104.50) Carr. £1
AKAI CR81D Tape Unit £58.95 (Rec. Price £84.10) Carr. £1
GOLDRING GL72 T/Table & P.U. £29.95 (Rec. Price £37.29) Carr. 75p
 Also FREE with above GL72 Goldring G800 cartridge worth over £10
B.S.R. MACDONALD MP60 TYPE T/Table & P.U. £10.95
 Prices shown correct at time of going to press (12/11/73) (Rec. Price £14.95) Carr. 40p


FANE 'MODE ONE' HIGH FIDELITY SPEAKER KIT



Incorporating a model 803 8" 13,000 Gauss Bass Speaker with ultra low resonance. P.V.C. surround cone. Printed circuit cross-over assembly with ferrite cored coils. Model 303 Pressure Tweeter, Acoustic damping material, Screws, Panels etc., and instructive diagrams, Frequency Response 25 Hz-20 kHz. 8-15Ω. £10.98 free
 Price per pair £19.99 Or Dep. £1.98 & 9 mthly pymts. £1.28 (Tot. £13.50)

RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged Controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and

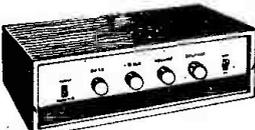

COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12.65 Carr. 40p
 OR FACTORY BUILT IN TEAK VENEERED CABINET £18.50 or dep. £2.50 and 9 monthly payments £1.83 (Total £18.97)

AUDIOTRINE HIGH FIDELITY SPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.
 Exceptional performance at low cost.

HF80ST	8"	10W	£2.98	HF120D	12"	15W	£5.50
HF102T	10"	10W	£3.30	HF126	12"	15W	£6.85
HF120	12"	15W	£4.95	HF126D	12"	15W	£8.85

FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll F.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15Ω. £3.99
 PLEASE STATE IMPEDANCE REQUIRED List £4.99
 MODEL 808T 8" 15w. with parasitic Tweeter. £5.50
 Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15Ω. List £6.99




ALL R.S.C. PRICES INCLUDE VAT FULL LABOUR AND MATERIAL GUARANTEES FOR 12 MONTHS

HI-FI SPEAKER ENCLOSURES MODERN DESIGN

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 35p. per enc.
JE8 Size 16" x 11" x 9". SE8 For optimum performance with any 8in. Hi-Fi speaker. £6.50
 Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. £5.50
SE10 For outstanding results with 10in. Hi-Fi spkr. Size 25½ x 16 x 9in. Ported. £6.75
SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter Size 25½ x 16 x 9in. £7.95



AUDIOTRINE HI-FI SPEAKER SYSTEMS

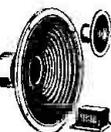

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. £6.50 Carr. 33p
 OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER £7.65 Carr. 39p

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Frequency Response 30-20,000 c.p.s. —2db. Harmonic Distortion 0-3% at 1,000 c.p.s. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 8-15 ohm spkrs. Max. sensitivity 6mV Output rating I.H.F.M. Fully enclosed enamelled case, 9½ x 2½ x 5½in. Attractive brushed silver fascia plate 10½ x 3½in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. £8.50 Carr. 40p
 OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE £12.05



R.S.C. BATTERY/MAINS CONVERSION UNITS



TYPE BML An all-dry battery eliminator. Size 5½ x 4½ x 2½in. approx. Completely replaces batteries supplying 1.5v and 90v. to battery radio where A.C. mains 200/250v. Post 30p 50c/s is available. ASSEMBLED READY FOR USE £4.15

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

MIDGET CLAMPED TYPE 2½ x 2½ x 2½in.
 250v., 60mA, 6-3v. 2a. £1.10
 250-0-250v., 60mA 6-3v. 2a. £1.16

FULLY SHROUDED UPRIGHT MOUNTING
 250-0-250v. 60mA, 6-3v. 2a., 0-5-6-3v. 2a. £1.55
 250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2.45
 300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2.45
 300-0-300v. 130mA, 6-3v. 4a. c.t., 6-3v. 1a. £2.95
 For Mullard 510 Amplifier £2.95
 350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2.45
 350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2.95
 425-0-425v. 200mA, 6-3v. 4a., c.t., 5v. 3a. £5.45
 425-0-425v. 200mA, 6-3v. 4a., c.t., 6-3v. 3a., 5v. 3a. £5.60
 450-0-450v. 250mA, 6-3v. 4a., c.t., 5v. 3a. £6.00

TOP SHROUDED DROP-THRO' TYPE
 250-0-250v. 70mA, 6-3v. 2a., 0-5-6-3v. 2a. £1.49
 250-0-250v. 100mA, 6-3v. 3-5a. £1.71
 250-0-250v. 100mA, 6-3v. 2a., 6-3v. 1a. £1.75
 350-0-350v. 80mA, 6-3v. 2a., 0-5-6-3v. 2a. £1.81
 250-0-250v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2.45
 300-0-300v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2.45
 300-0-300v. 130mA, 6-3v. 4a., c.t., 6-3v. 1a. £2.85
 Suitable for Mullard 510 Amplifier £2.85
 350-0-350v. 100mA, 6-3v. 4a., 0-5-6-3v. 3a. £2.45
 350-0-350v. 150mA, 6-3v. 4a., 0-5-6-3v. 3a. £2.95

FILAMENT or TRANSISTOR POWER PACK
 Types 6-3v. 1-5a. 55p; 6-3v. 2a. 60p; 6-3v. 3a. 85p;
 6-3v. 6a. £1.45; 12v. 1a. 61p; 12v. 3a. or 24v. 1-5a. £1.50; 0-9-18v 1½a £1.25; 0-12-25-42v 2a £1.95.

CHARGER TRANSFORMERS 0-9-15v. 1½a. £1.10, 2½a. £1.25; 3a. £1.40; 5a. £1.60; 6a. £1.85; 8a. £2.20
AUTO (Step UP/step DOWN) TRANSFORMERS
 0-110/120v. 200-230-250v., 50-80 watts £1.25, 150 watts, £2.10 250 watts £3.00; 500 watts £6.40

OUTPUT TRANSFORMERS
 Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 55p
 Push-Pull 8 watts EL84 to 3 Ω or 15 Ω 95p
 Push-Pull 10 watts 6V6, ECL86 to 3, 5, 8 or 15 Ω £1.55
 Push-Pull EL84 to 3 or 15 Ω 10-12 watts £1.50
 Push-Pull Ultra Linear for Mullard 510, etc. £2.45
 Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω £2.20
 Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £3.65

SELENIUM RECTIFIERS
 F. W. (Bridged)
 All 6/12v. D.C. output. Max. A.C. input 15v.
 1a, 28p. 2a, 39p.
 3a, 55p. 4a, 72p.
 6a, 88p.

SMOOTHING CHOKES
 150mA, 7-10H, 250 Ω 77p; 100mA, 10H, 200 Ω 96p;
 80mA, 10H, 350 Ω 55p; 60mA, 10H, 400 Ω 28p.

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET
 Only high grade components by leading manufacturers

- * Push Button Selector Switching
- * Jack Socket for Headphones
- * Neon Indicator
- * Satin Silver Finish Metal Fascia
- * Solid State Circuitry
- * Twenty Silicon Transistors
- * Four Diodes, Four Rectifiers

Send S.A.E. for full descriptive leaflet.



For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8Ω. Frequency Response 7 Hz to 70 KHz ± 1½ db.

COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £5 extra. £22.50

R.S.C. STEREO FM III TUNER. CABINET with 12 months' guarantee. Or Dep. £7 and 9 monthly payments £4.54 (Total £47.86). £42.50

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx. COMPLETE KIT
 ★ Response 30-20,000 c.p.s. Impedance 15 ohms £25.25
 ★ Performance comparable with units costing considerably more Carr. 65p

Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet.
 (2) 3-way quarter section series cross-over system.
 (3) 8 x 5in. high flux middle range speaker.
 (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet.
 (7) Circuit and full instructions. Terms: Deposit £5.25 and 9 monthly payments £2.56 (Total £28.29).



R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).
COVENTRY 17 Shelton Square, The Precinct.
DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361
DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs) Tel. 229 9501
EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 248 4158
GLASGOW 326 Argyle St. (Closed Tues.). Tel. 20505
HULL 7 Whitefriargate (Closed Thurs.). Tel. 20545
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
LEEDS 5-7 Queen (Mecca) Arcade, Brigate (Closed Wed.). Tel. 28252
LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778
MIDDLESBROUGH 106 Newport Rd. (Closed Wed.). Tel. 47096
NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469
NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068
SHEFFIELD 13 Exchange Street (Castle Mkt. Blds. (Closed Thurs.). Tel. 20716
STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777
SUNDERLAND 5 Market Sq. (Closed Wed). Tel. 70573

ESSENTIAL BOOKS FOR RADIO AMATEURS

1974 EDITION

RSGB AMATEUR RADIO CALL BOOK

Lists holders of G, GC, GD, GI, GM, GW and EI callsigns; clubs and societies affiliated to RSGB, and much useful operating information.

A larger completely revised edition produced by a new system and incorporating amendments and additions notified by the MPT up to August 1973.

144 pages

Price 75p post paid

TELEPRINTER HANDBOOK

by D. J. Goacher, G3LLZ, and
J. G. Denny, G3NTT

A brand new book covering all aspects of modern teleprinter techniques. Full descriptions and maintenance data for all widely-used machines, together with design and use of ancillary equipment. Definitely a book for the teleprinter enthusiast's work bench.

376 pages

£5.35 post paid

A GUIDE TO AMATEUR RADIO by Pat Hawker, G3VA

This extensively revised 15th edition is an indispensable aid to all who want to know more about amateur radio.

Specially designed to assist the newcomer to the hobby, it covers technical, operating and licensing matters.

96 pages

Price 90p post paid

AMATEUR RADIO AWARDS by C. R. Emary, G5GH

Lists all the world's major awards from national societies and how to obtain them.

Includes reproductions of certificates and maps, and operating information.

Loose-leaf binding allows insertion of amendment pages at a later date.

194 pages

Price £1.40 post paid

These are just four of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.



RADIO SOCIETY OF GREAT BRITAIN

35, DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688

A DEXTER DIMMASWITCH

ALLOWS COMPLETE



LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.

600 watt £3.52 Kit form £2.97
300 watt £2.97 Kit form £2.42

All plus 12p post and packing

Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY

5 ULVER HOUSE
19 KING STREET
CHESTER, CH1 2AH
Tel: 0244-25883

AS SUPPLIED
TO H.M. GOVERNMENT
DEPARTMENTS, HOSPITALS,
LOCAL AUTHORITIES,
ETC.

TRANSFORMERS

DOUGLAS GUARANTEED
Prices include P. & P. and 10% VAT
12 or 24 Volts

Output V. & Amps.	Ref. No.	Price
12V x 2 250mA x 2	MT111CS**	£1.32
12V x 2 500mA x 2	MT213**†	£1.65
12V x 2 1A x 2	MT71CT†	£2.17
12V x 2 2A x 2	MT18CT	£2.63
12V x 2 3A x 2	MT70AT	£3.40
12V x 2 4A x 2	MT108AT	£3.86
12V x 2 5A x 2	MT72AT	£4.48

30 Volts. All tapped at 0-12-15-20-30V.			
Output Amps.	Ref. No.	Price	Output Amps.
500mA	MT112CT†	£1.43	4A
1A	MT79CT†	£2.22	5A
2A	MT3AT	£3.22	8A
3A	MT20AT	£3.65	10A

50 Volts. All tapped at 0-19-25-33-40-50V			
Output Amps.	Ref. No.	Price	Output Amps.
500mA	MT102AT†	£2.07	3A
1A	MT103AT†	£3.00	4A
2A	MT104AT†	£4.01	5A

60 Volts. All tapped at 0-24-30-40-48-60V.			
Output Amps.	Ref. No.	Price	Output Amps.
500mA	MT124AT	£2.33	2A
1A	MT126AT	£3.23	3A

AUTO-WOUND RANGE			
Power output	Winding tapped at	Ref. No.	Price
20VA	0-115-210-240	XMT113CT	£1.26
75VA	"	XMT64AT	£2.51
150VA	0-115-200-220-240	XMT4AT	£3.06
200VA	"	XMT65AT	£3.65


400V. Output at 50HZ.
C-D Ignition System by R. M. Marston, Esq.
Wireless World.
Reference 1T3AT £3.00

EQUIPMENT RANGE			
Sec. Output (r.m.s.)	Ref. No.	Price	
3-0-3V	200mA	MT238CS**†	£1.41
9-0-9	100mA	MT13CS**†	£1.38
12-0-12	50mA	MT239CS**†	£1.41
20-0-20	30mA	MT241CS**†	£1.41
0-20 x 2	300mA x 2	MT214CT**†	£2.87
0-8-9 x 2	500mA x 2	MT207CT**†	£2.22
0-15-20 x 2	500mA x 2	MT205AT**	£2.95
0-15-27 x 2	500mA x 2	MT203AT*	£3.38
0-15-27 x 2	1A x 2	MT204AT*	£3.38
20-12-0-12-20	700mA (d.c.)	MT221AT*	£1.74

AT indicates open universal fixing with tags; CT is open U-clamp fixing with tags; CS is open U-clamp fixing with P.C. spillo; * with interwinding screen; † untapped 240 primary; ‡ tapped at 210-240V.; other primaries tapped at 200-220-240V.

OVER 200 TYPES IN STOCK through Agents or Direct. Please send for lists.
DOUGLAS ELECTRONIC INDUSTRIES LTD.,
Direct Sales Dept. P.W., Thames Street, LOUGH, Lincs.
LN11 7AD

Stove Enamelled STEEL CABINET

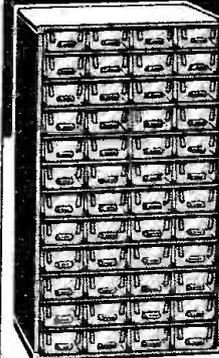

List price £6.87
OUR PRICE
£5.50
incl. V.A.T.
Carriage 44p

With 48 see-through Drawers
Ideal for the Radio Constructor

As supplied by us to SCHOOLS, TECHNICAL COLLEGES, HOSPITALS, SHOPS and industry throughout the country. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at a small extra charge to enable each drawer to be sub-divided into six compartments. See-through drawers allow swift selection of contents at a glance. A really first-class time and space saving unit. Size of cabinet 21½" x 11½" x 6½", size of drawers 6½" x 2½" x 1½".

Callers welcome.


SEND FOR FREE ILLUSTRATED LEAFLETS

Trade Aids 111 Chiltern Drive - Surbiton Surrey
(100 yards from Berrylands Railway Station) 01-399 4383

TOP QUALITY — LOW COST



RADIO — STEREO EQUIPMENT

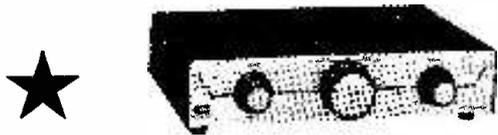

P.R.40

SOLID STATE R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which is now supercedes.

It employs Silicon "N" Channel FET (Field Effect Transistor) front end, followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30 dB, with improved image rejection and noise ratio.

Supplied complete with co-ax plug (less standard 9 volt PP6 Battery), 12 months Guarantee.

£10.12 V.A.T./Carr. Paid.



MULTIBAND-6

SOLID STATE
SHORT WAVE RECEIVER KIT

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils.


Hi-Gain FET Regen, Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB.

Separate Electrical Bandsread, Calibrated Main Tuning.

A Quality CODAR-KIT with 12 months Guarantee. No technical. Knowledge required, simple to built, printed circuit and Pictorial Instruction Manual, fully detailed step by step.

Complete Kit with 4 Coils (less standard PP6 battery).

£14.90 V.A.T./Carr. Paid.

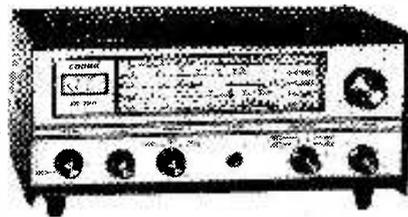

CR70A

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.

It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception, Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder.

Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee. Complete ready built. £31.00 V.A.T./Carr. Paid.

SEND FOR YOURS TODAY!

FREE LEAFLETS ON REQUEST.

NOTE: These CODAR Receivers meet the B.R.E.M.A. specification for Communication Receivers. Some portable receivers being advertised as Communication Receivers do not meet these requirements.

TRADE DESCRIPTIONS ACT 1968

It is illegal to make false claims or misleading statements in advertising. The following are just a few extracts from the many letters received from satisfied customers. All are unsolicited and can be inspected at any time.

Mr. S. Keightly, Southsea, Hants.
I am delighted with the CODAR equipment I am using . . . everything has come up to your specifications.

Dr. R. E. Wood, Louisiana State University, U.S.A.
Congratulations on an excellent product. The PR40 Preselector is the first preselector I have found to operate efficiently with ample gain, and without feedback or image problems.

Mr. W. R. Jones, Woy, N.S.W., Australia.
The PR40 peaked signals remarkably and performed as you claim. I am very satisfied.

M. G. Bennett, Bath, Somerset.
I am very pleased with my CR70A—results are excellent with many overseas stations I have not heard before and excellent results on the Amateur Bands.

Mr. J. Macdonald, Coningsby, Lincoln.
Received Multiband Kit OK. Assembled it in two hours, worked a treat first time.

Mr. E. Joy, Chesham, Bucks.
The performance of the CR70A is out of this world for its price, and its construction and design, great. I am really delighted . . . I cannot fault it.

NEW! HI-FI STEREO EQUIPMENT

NOW AVAILABLE FROM CODAR—A COMPLETE RANGE OF QUALITY EQUIPMENT SELECTED BY US FOR TOP RESULTS AND MONEY VALUE—PLUS OUR BIG CASH DISCOUNTS!

SEND FOR FREE ILLUSTRATED BROCHURES NOW

NEW! AMTRON KITS

We are now also marketing the outstanding range of AMTRON Kits. The quality of these Kits is first class, with circuit details and drawings making construction simplicity itself.



ON THE DESIGN STAFF—
G3SZM G3IRE

CODAR

TELECOMMUNICATIONS AND ELECTRONIC
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

Tel. 090-63-61901

BN15 - 8TZ

Why pay more - look at our Fantastic Bargain Offer!

PENTHOUSE

A COMPLETE AUDIO SYSTEM


An all "White" Hi-Fi Stereo System to blend with modern furnishings. Solid state, fully transistorised tuner/amplifier with Stereo Multiplex Decoder, 4 wavebands Long/Medium/Short/VHF, 8 watts per channel (music power) output. The latest BSR C129 4 speed Mono/Stereo record changer. Two white matching bookshelf speaker units. Also available in teak finish. **OUR PRICE £55.00**



Credit terms £5.00 deposit plus £2.50 p. & p. followed by 12 payments of £5.00. Total Credit Terms £65.00 SEND £7.50 TODAY.

KLINGER


FIVE NINETY THREE UNIT AUDIO SYSTEM with BSR McDonald 4-speed Record Player, matching 4-unit Loud-speaker Systems and FREE Stereo Headphones. High performance Stereo Amplifier designed for home entertainment at economical cost. Represents a considerable advance in solid state, high fidelity stereo amplifiers. Outstanding performance is allied to meticulous construction, comprehensive facilities, installation simplicity and attractive styling. 10 watt RMS per channel; push button selectors; tone controls balance control; tape record and replay facilities. Stereo headphone socket on front panel with automatic speaker muting; Teak finish. Our price £75.00 + £2.00 p. & p. Credit Terms £7.50 deposit + £2.50 p. & p. 18 monthly payments of £4.75 (total £93.00) SEND £10.00 TODAY.

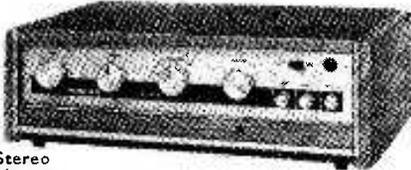

THE AVON AUDIO SYSTEM



The uncabineted system is ideal as an economical replacement for an outdated chassis. Stereo Amplifier for Stereo/Mono record reproduction. Tuner with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz. LATEST BSR STEREO/MONO RECORD CHANGER plays all types of 7in., 10in., and 12in. Mono or Stereo records. Manual or automatic play. TWIN ELLIPTICAL SPEAKERS These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.

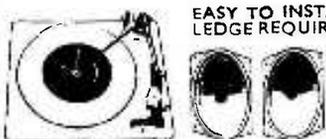

EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45.74. OUR PRICE £35.00. Credit Terms £3.50 deposit plus £2 Post & Packing followed by 12 payments of £3.15 (Total Credit Terms £41.30) Don't miss this bargain. SEND £5.50 TODAY

ALL EQUIPMENT COVERED BY OUR 12 MONTHS FULL GUARANTEE

CALLERS WELCOME



PW 1/74

100 Chase Side, Southgate, London N14 5PL
Tel: 01-886 3733/9666

NEW

ALL SILICON!



PRACTICAL WIRELESS

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and wiring manual 25p, supplied with de-luxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.

Price: Standard Kit£7.97 U.K. Post Free
De-Luxe Kit£9.62 U.K. Post Free

Quantity Discounts:

Trade and Overseas	1-5	Nett	6-9	Less 10%
Enquiries Invited	10-49	Less 15%	50-99	Less 20%
Mail Order Only	100-999	Less 25%	1000 up	Less 30%

ALL PRICES INCLUDE VAT

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.

DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34365

Designed for easy evaluation of new ICs by electronic engineers, these kits are simple enough for the amateur constructor. The finished unit works in the office or the bedroom; the lounge or the laboratory.



5316-LC: Pairs the National Semiconductor MM5316 digital alarm clock chip with the RCA TA8055 liquid crystal display. Four digits show hours and minutes, minutes and seconds, alarm set time, sleep set time. The chip features a pre-settable 59 minute sleep counter and a 10 minute snooze delay input. The LC is AC driven for long life on a common line operating with the common segment source from a square wave generator. Two switched outputs are provided to drive buzzer and/or radio. Kit contains chip, socket PCB, TA8055 and connector, instructions. You supply 13 res, 2 caps, 1 N4001, 4 BC109s, transformer, case. **£32**

5017-PD: Mostek MK5017AA alarm clock chip with four DG12 phosphor-diode digits (expandable to six). Chip has snooze, buzzer, power backup. Kit contains chip, socket, PCB, 4 DG12s, instructions. **£24**

5314-J Based on National Semiconductors MM5314 clock chip plus Litronix's new DL747 (JUMBO) 0.6 inch LED. Details and price to be announced.

ALL CHIPS, DISPLAYS AND PCBs AVAILABLE SEPARATELY

VAT All prices exclude VAT. CATALOGUE 15p
TEL. 0442-62757 FOR ADVICE OR ORDERS.



BYWOOD ELECTRONICS
181 EBBERS ROAD
HEMEL HEMPSTEAD
HERTS. HP3 9RDA

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O. Only **£1-05p** P & P 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only **27 1/2p** POST & PACKING 16 1/2p

A Cross Hatch Generator £3-85 post paid

A complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. A project in the Sept. '72 edition of Television.

Electronic Transistor Ignition

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features:—

Transistor and conventional switchability, burglar proof lock up and automatic alarm, negative and positive compatibility. This project was a "star" feature in the September 1973 edition of "Electronics Today International" magazine. Our kit is recommended by the ETI magazine.

Ready built and tested unit £9-90 Inc. V.A.T.

£6-60p Complete kit incl. V.A.T. p & p 11p

Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15.	HFE Min 15.	1-12	13-25	26-50
40 Watt	22p	20p	18p	18p
90 Watt	26 1/2p	24 1/2p	22p	

Range 2. VCE. Min. 40.	HFE Min 40	1-12	13-25	26-50
40 Watt	33p	31p	29p	
90 Watt	38 1/2p	36 1/2p	33p	

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 15p Wall Chart 18p

LOW COST DUEL IN LINE I.C. SOCKETS

14 pin type at 16 1/2p each } Now new low profile
16 pin type at 18p each }

BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below.

Send for lists of publications

Tested and Guaranteed Paks



- B79 4 IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic 55p
- B81 10 Reed Switches, 1" long, 1/4" dia. High Speed P.O. type 55p
- B99 200 Mixed Capacitors. Approx. quantity, counted by weight P & P 15p 55p
- H4 250 Mixed Resistors. Approx. quantity, counted by weight P & P 15p 55p
- H35 100 Mixed Diodes. Germ. Gold bonded, etc. Marked and Unmarked. 55p
- H38 30 Short lead Transistors, NPN Silicon Planar types 55p
- H39 6 Integrated Circuits, 4 Gates BMC 962, 2 Flip Flops BMC 945 55p
- H41 2 Sil Power transistors comp pair BD131/132 55p



Unmarked Untested Paks

- B1 50 Germanium Transistors PNP, AF and RF 55p
- B66 150 Germanium Diodes Min. glass type 55p
- B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202 55p
- B86 100 Sil. Diodes sub. min. IN914 and IN916 types 55p
- H16 15 Experimenters' Pak of Integrated Circuits, Data supplied 55p
- H20 20 BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts. 55p
- H34 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can. 55p

New Paks

TESTED & GUARANTEED

- H63 4 2N3055 type NPN Sil. power transistors. Below spec. devices 55p
- H64 4 3819 N Channel FETs 55p
- H65 4 2N3819 In plastic case 55p
- H65 4 40361 Type NPN Sil. transistors TO-5 can comp to H66 55p

UNTESTED, UNMARKED

- H66 4 40362 Type PNP Sil. transistors TO-5 can comp to H65 55p
- H67 10 3819N Channel FETs plastic case type 55p

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Silicon Planar Plastic Transistors

Unmarked, untested factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70 etc.

Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9 etc.

ALL AT 50p for £3-30, 1,000 for £5-50, 10,000 for £44 P. & P. 11p/1,000

Please state Audio NPN or Audio PNP when ordering.

Our very popular 4p transistors

- TYPE "A" PNP Silicon alloy, TO-5 can
- TYPE "B" PNP Silicon, plastic encapsulation
- TYPE "E" PNP Germanium AF or RF
- TYPE "F" NPN Silicon plastic encapsulation
- TYPE "G" NPN silicon similar ZTX 300 range
- TYPE "H" PNP silicon similar ZTX 500 range

8 RELAYS FOR VARIOUS TYPES P & P 27 1/2p £1-10p

Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10p each

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak. Please ask for Pak P.1. only **55p**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344.

Co. Reg. No 820919

FREE

Headphones or Speakers; Suitably Terminated Connectors; Handbook; Carriage; Insurance. In addition a JOYSTICK V.F.A.; JOYMATCH A.T.U.; feeder external mounting insulators are supplied FREE or greatly reduced when you buy a PARTRIDGE PACKAGE.

A PARTRIDGE PACKAGE constitutes a **COMPLETE RADIO STATION**—ready to use however confined your domestic space. The World renowned **TRIO** range of Communications Receivers and Transceivers, the **WORLD RECORD**, internationally patented **JOYSTICK V.F.A.** (all band aerial) only 7' 6" long (assembled) and a **JOYMATCH** aerial tuning unit, a pair of matching headphones or internal speaker, plus accessories, go to complete your **READY TO USE RADIO STATION** at a price that truly represents **VALUE FOR MONEY!** **H.P. FACILITIES** WHERE POSSIBLE—**24 HOUR DELIVERY (MON-FRI.)** **ADD £4.00—OUR RISK!**

PARTRIDGE PACKAGE (PRICE REDUCTIONS!)

No. 1 with Gen. Coverage AM/CW/SSB (MW/SW) **9R59DS** Receiver £65.91 (Save £15.30)
 No. 2 with Amateur Bands 80 thru 10m AM/CW/SSB **JR310** Receiver £90.97 (Save £22.35)
 No. 3 with Amateur Bands 160 thru 10m plus 2m AM/CW/SSB **JR599** £165.00 (Save £19.48)
 No. 4 with Amateur Bands 80 thru 10m **TS/PS 515** Transceiver, 180w £231.00 (Save £37.08)

NOTHING MORE TO PAY!

OUR RISK

Access/Barclaycard orders accepted by 'phone

JOYSTICK V.F.A. £13.75; **JOYMATCH TX/RX A.T.U. 111A 1.6-32MHz** £13.75; **JOYMATCH A.T.U. 111 RX only 500kHz-32MHz** £13.75; **JOYMATCH A.T.U. LO-Z500 TX/RX 500w SSB (PA input), Built-in RF meter** £19.91; **Communications 8Ω headphones (suitable TRIO, EC10 etc.)** £3.14; **Matching Speaker (with instructions for internal fitting in 9R59DS & JR310)** £2.00; **TRIO: Linear Amplifier TL911** £172.15; **TR2200 2m personal transceiver** £87.45; **TR7200 2m car transceiver** £142.45; **Spare set valves for 9R59DS** £2.35; **OA2 Mains Stabiliser 74p.**

NEW: World-wide reception on the amazing "DX-CRYSTAL SET" £2.42 incl. unique aerial.

NEW: AMTRON QUALITY KITS—send for brochure and prices.

PARTRIDGE BUDGET LINE

Artificial Earth—solves receive and transmit earth problems (as used on North Sea Oil Rigs!) £5.80; **Aerial Bandswitch—tuned aerial for domestic receivers** £5.80; **A.T.U. KIT—for use with transmitters and Communications Receivers** £5.80; (assembled £7.01); **Mini SWR Bridge—1.8 to 180MHz, 2kw P.E.P., 75 or 50Ω, SO239 sockets; 1:1 to 1:3 ratio, 80 x 30 x 30mm** £5.60. (All prices quoted **INCLUDE V.A.T., CARRIAGE, PACKING, INSURANCE.**)

Send 3½p stamp for full illustrated details. Special TRIO brochures (state which) 3½p stamp extra.

NO V.A.T. ON OVERSEAS ORDERS!

Carriage and insurance extra overseas orders

BOX 5



G3CED — G3VFA

FOR EXPERT ADVICE AND INFORMATION

Telephone: 0843 62535 or 62839 evenings and weekends

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive, 88-108Mc, with circuit diagram. £2.30p.

F-C BOARDS (not computer panels)

- 1 off 6 transistors single wave band
- 1 off 4 transistor audio
- 1 off 2 transistor £1.80 the three.

LIGHT DEPENDENT RESISTORS (RCA sq3536) 20p each, 4 for £1.00.

All Transistor STEREOGRAM CHASSIS. Medium, Long and VHF/FM, 3 Watts per channel S/M rating. With circuit service manual. Less tuning scale which can be obtained from well known British manufacturer . . . £20.

Colour Transistor panels, as used on well known British E.V.R. Teleplayer. All new panels and components. Type and contents of transistors listed below. Each panel £3.50 each.

X605 .14 off BC148, 2 RCA ca3054(1c), 1 crystal 4-433618MHz.
 Z607 .12 off BC148, 1 BC158, 1 BC148, 1 RCA ca3046, 1 RCA ca3045(1c).

Z608 .23 off BC148, 2 BC158.

Z612 .12 off ME4102, 2 BC251B, 1 BFY50.

CRYSTAL CALIBRATOR (Second Hand) No. 10 crystal controlled heterodyne wave-meter covering 500KHz-10MHz (harmonics up to 30MHz) power required 300V DC 15mA, 12V 0.3A DC. Test equipment for 62T M/RC. £2.50 each.

WIRE-WOUND RESISTORS. Our selection of mixed Ohms and Watts. 25 for £1.50, 50 for £2.50, parcel of 1,000 £30.00.

CONDENSER-ELECTRET MIC INSERT incorporating FET Preamp 1½ volt Supply. Details of connections included £1.75.

AUDIO AMPLIFIER MODULE (Mullard LP1173). Output power, nominal 10 watt. Supply voltage 24 volt. With reference data £3.25.

ALL ITEMS INCLUDE VAT

All items post paid in GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

BAKER 12" MAJOR £9.90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. **BASS RESONANCE 40 cps 20 watt RMS.**



MAJOR MODULE KIT £12.50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W £8.80	Superb 12 in. 20W £16.50	New Group 50/12
Major 12 in. 20W £9.90	Group 25 12 in. 25W £8.80	12 in. 50W
Deluxe 12 in. 15W £11.00	Group 35 12 in. 35W £9.90	30-16,000 cps

£17.60

BAKER LOUSPEAKER CO., BENSHAM MANOR PASSAGE

THORNTON HEATH, SURREY Tel. 01-684 1665

PRICES INCLUDE V.A.T. HI-FI ENCLOSURE PLANS 42p

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Rotary, Slide, Key Switches, IF's, Tag Strips, Drive Drums, Springs, Handles, Coil Formers, Wire, Grommets, Relays, Pulley Wheels, Magnets, Transistor Panels, etc., etc.

Save yourself £'s on these well selected parcels. 6lbs net weight £1.00, p. & p. 40p.

Brand new Wire-Wound Resistors 1-7 Watts. Good selection 100 for £1, p. & p. 15p.

Assorted Computer Panels. These panels are exceptionally good value and contain a minimum of 75 Transistors, Stacks of Diodes, plus Trim Pots, Polyester Capacitors, Resistors and include a few I.C.'s. 10 panels for £1, p. & p. 27p.

Mullard Ferrite Cores LA3 100 to 500kHz 50p, LA4 10 to 30kHz 75p, LA 2100 3 to 200kHz 50p.

Assorted Electrolytic Capacitors, 6lbs net weight £1, p. & p. 40p.

Please include 10% V.A.T. to total cost of goods.

MAIL ORDER ONLY

XEROZA RADIO

1 EAST STREET, BISHOPS TAWTON, DEVON




It's nice to see that Santa is still so sprightly that he can dance to the rock record he is using to test that stereo player. But Rudolph is getting impatient—keen to be up and away delivering the goods, especially all those Home Radio Components Catalogues Santa is using as speaker stands! Probably your name and address is on that pile of requests pinned to the door. If not, don't despair—send us the coupon below with your cheque or P.O. for 77p and we'll see that the old chap brings you a

copy on one of his first deliveries. (If you call at the address on the coupon you can collect your copy for only 55p. Santa won't be offended—and you'll save yourself 22p.)

By the way, our catalogues still contain 10 vouchers each worth 5p when used as directed. But coupons or no coupons, the catalogue is marvellous value, and once you get a copy you'll wonder how you ever managed without it. **Happy Christmas!**

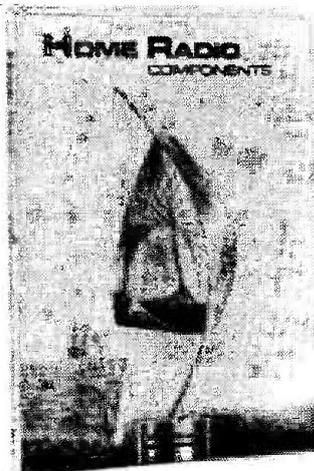Our famous catalogue lists 6,800 items—1,770 of them illustrated. Regularly up-dated price lists are supplied to you free, and full details of our popular Credit Account Service are given in the catalogue.



The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.



POST THIS COUPON with your cheque or postal order for 77 pence

Please write your Name and Address in block capitals

Name

Address



HOME RADIO (Components) LTD
Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD

Henry's

**UK'S LARGEST RANGE OF TRANSISTORS, IC'S
RECTIFIERS, ALL SEMICONDUCTOR DEVICES
BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL**

FREE BOOKLET

All types of
TRANSISTORS — RECTIFIERS
BRIDGES—SCR'S—TRIACS
INTEGRATED CIRCUITS
F.E.T.—LIGHT DEVICES



**More Devices
New Prices
New Ranges**

This is a must for all

OVER 1500 DIFFERENT DEVICES Semi-conductor Users
ENTIRELY NEW 1973 EDITION (ask for booklet No. 36)
SEND FOR YOUR FREE COPY TODAY

INTEGRATED CIRCUITS VERY IMPORTANT. ONLY branded I.C's are to the FULL manufacturers specifications. ALL others are not. Henry's sell only branded Integrated Circuits... FROM TEXAS... I.T.T. ... FAIRCHILD ... SIGNETICS. So why buy alternatives or under spec. devices when you can purchase the genuine article from us—ex stock... need we say more!



Type	1/11	12/29	30/99	Type	1/11	12/29	30/99	Type	1/11	12/29	30/99
8N7400N	0.20	0.18	0.18	8N7446N	1.50	1.27	1.13	8N74142N	2.88	2.88	2.52
8N7401N	0.20	0.18	0.18	8N7445N	0.20	0.18	0.18	8N74145N	1.44	1.44	1.28
8N7401AN	0.38	0.38	0.38	8N7445LN	0.20	0.18	0.18	8N74147N	2.30	2.80	1.88
8N7402N	0.20	0.18	0.18	8N7445SN	0.20	0.18	0.18	8N74148N	2.01	2.01	1.83
8N7403N	0.20	0.18	0.18	8N7446N	0.20	0.18	0.18	8N74150N	2.80	2.80	2.01
8N7403AN	0.38	0.38	0.38	8N7446N	0.20	0.18	0.18	8N74151N	1.15	1.15	1.00
8N7404N	0.24	0.21	0.18	8N7447N	0.38	0.30	0.27	8N74153N	1.09	1.09	0.95
8N7406N	0.20	0.18	0.18	8N7447SN	0.48	0.41	0.37	8N74154N	2.80	2.30	2.01
8N7405AN	0.44	0.44	0.38	8N7447SN	0.48	0.41	0.37	8N74155N	1.15	1.15	1.00
8N7406N	0.40	0.38	0.35	8N7447SN	0.48	0.41	0.37	8N74156N	1.09	1.09	1.00
8N7407N	0.40	0.38	0.35	8N7447SN	0.48	0.41	0.37	8N74157N	1.09	1.09	0.95
8N7408N	0.25	0.22	0.19	8N7447SN	0.48	0.41	0.37	8N74158N	2.44	2.44	2.14
8N7408AN	0.33	0.33	0.28	8N7448N	0.80	0.70	0.60	8N74160N	1.58	1.68	1.38
8N7409N	0.44	0.44	0.38	8N7448N	0.80	0.70	0.60	8N74161N	1.58	1.68	1.38
8N7410N	0.20	0.18	0.18	8N7448N	0.80	0.70	0.60	8N74162N	1.58	1.68	1.38
8N7411N	0.25	0.23	0.21	8N7448N	0.80	0.70	0.60	8N74163N	1.58	1.68	1.38
8N7412N	0.28	0.28	0.25	8N7448N	0.80	0.70	0.60	8N74164N	2.01	2.01	1.76
8N7412AN	0.38	0.38	0.33	8N7448N	0.80	0.70	0.60	8N74165N	2.01	2.01	1.76
8N7413N	0.30	0.27	0.25	8N7448N	0.80	0.70	0.60	8N74166N	2.18	2.18	1.89
8N7414N	0.72	0.72	0.63	8N7449N	0.75	0.70	0.63	8N74167N	4.10	4.10	3.59
8N7416N	0.30	0.27	0.25	8N7449AN	1.10	1.00	0.90	8N74170N	2.88	2.88	2.52
8N7417N	0.30	0.27	0.25	8N7449AN	0.75	0.70	0.63	8N74172N	6.78	6.78	5.04
8N7420N	0.20	0.18	0.18	8N7449AN	0.75	0.70	0.63	8N74173N	1.66	1.66	1.45
8N7422N	0.28	0.28	0.25	8N7449AN	0.75	0.70	0.63	8N74174N	1.80	1.80	1.67
8N7422AN	0.38	0.38	0.33	8N7449AN	0.75	0.70	0.63	8N74175N	1.29	1.29	1.18
8N7423N	0.37	0.34	0.32	8N7449AN	0.75	0.70	0.63	8N74176N	1.44	1.44	1.28
8N7425N	0.37	0.37	0.32	8N7449AN	0.75	0.70	0.63	8N74177N	1.44	1.44	1.28
8N7427N	0.37	0.37	0.32	8N74100N	2.18	1.89	1.89	8N74178N	1.44	1.44	1.28
8N7428N	0.43	0.43	0.37	8N74104N	0.80	0.53	0.45	8N74181N	5.18	5.18	4.58
8N7430N	0.20	0.18	0.18	8N74107N	0.51	0.51	0.45	8N74182N	1.44	1.44	1.28
8N7432N	0.37	0.37	0.32	8N74110N	0.67	0.57	0.50	8N74184N	2.18	2.18	1.89
8N7433N	0.43	0.43	0.38	8N74111N	0.86	0.86	0.75	8N74185AN			
8N7433AN	0.57	0.57	0.50	8N74116N	2.18	2.18	1.89				
8N7437N	0.43	0.43	0.37	8N74118N	1.00	0.90	0.83	8N74188N	6.48	6.48	5.87
8N7438N	0.48	0.43	0.37	8N74119N	1.92	1.92	1.68	8N74190N	2.80	2.80	2.01
8N7438AN	0.67	0.57	0.50	8N74120N	1.05	1.05	0.92	8N74191N	2.80	2.80	2.01
8N7440N	0.20	0.18	0.18	8N74121N	0.57	0.57	0.50	8N74192N	2.80	2.80	2.01
8N7441AN	0.85	0.79	0.78	8N74122N	0.80	0.80	0.70	8N74193N	2.30	2.30	2.01
8N7442N	0.85	0.79	0.78	8N74123N	1.44	1.44	1.26	8N74194N	1.72	1.72	1.51
8N7443N	1.50	1.27	1.13	8N74125N	0.69	0.69	0.60	8N74195N	1.44	1.44	1.28
8N7444N	1.50	1.27	1.13	8N74126N	0.69	0.69	0.60	8N74196N	1.58	1.58	1.38
8N7445N	2.18	2.18	1.89	8N74132N	0.72	0.72	0.63	8N74197N	1.58	1.58	1.38
8N7446N	2.18	2.18	1.89	8N74136N	0.63	0.63	0.55	8N74198N	3.18	3.18	2.77
8N7447AN	1.80	1.80	1.57	8N74141N	1.00	0.90	0.80	8N74199N	2.88	2.88	2.52

LARGER QUANTITY AND O.E.M. PRICES PHONE (01) 723 3646. PRICING OF 8N7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX. SN74... HIGH POWER... SN74... LOW POWER SERIES IN STOCK... SEND FOR LIST 36, FREE ON REQUEST. LOW PROFILE SOCKETS 14 PIN... 15P 16 PIN... 17P, 8 PIN... 14P

TRANSISTORS A SELECTION FOR FULL LIST SEND FOR BOOKLET 36 TODAY			
AAZ13 10p	BC183 12p	BYZ13 35p	OC36 65p
AC107 85p	BCY32 85p	COE6D 55p	OC44 18p
AC128 80p	BCY39 15p	GET111 55p	OC45 18p
AC187 20p	BCY55 2.50	GET115 75p	OC71 15p
AC172 35p	BCY70 15p	GET180 55p	OC72 25p
ADY39 65p	BCY71 20p	LM309K 1.25	OC77 55p
AD149 50p	BCY72 15p	MAT121 85p	OC81 28p
AD161 38p	BD124 80p	MJE330 50p	OC83 25p
AD162 38p	BD131 45p	MJE520 65p	OC140 65p
AF117 20p	BF115 25p	MJE305 5p	OC170 25p
AF118 50p	BF180 35p	OC200 55p	OC200 55p
AF139 33p	BF194 13p	OC202 90p	OC202 90p
AF186 40p	BFX13 25p	OC71 1.00	OC71 1.00
AF239 44p	BFX34 55p	ORP12 55p	ORP12 55p
ASV27 30p	BFX88 22p	ORP60 45p	ORP60 45p
BA115 10p	BFY50 20p	P346A 20p	P346A 20p
BAX13 5p	BFY51 20p	TIL209 25p	TIL209 25p
BC107 12p	BFY64 45p	TIP29A 49p	TIP29A 49p
BC108 12p	BFY90 75p	TIP30A 55p	TIP30A 55p
BC109 12p	BLY36 6.25	TIP31A 61p	TIP31A 61p
BC109C 14p	BSX20 15p	OC16 85p	TIP41A 74p
BC113 16p	BU105 2.20	OC20 1.25	TIP42A 90p
BC147 12p	BY106 15p	OC28 65p	TIS43 28p
BC169C 14p	BY127 15p	OC35 55p	V405A 25p
			ZTX108 10p
			ZTX300 14p
			ZTX302 18p
			ZTX600 15p
			2G301 40p
			2G697 15p
			2G706 10p
			2N930 20p
			2N987 45p
			2N1132 25p
			2N1304 25p
			2N1613 20p
			2N1671 1.00
			2N2147 75p
			2N2160 68p
			2N2928 10p
			2N3053 20p
			2N3054 45p
			2N3055 45p
			2N3440 50p
			2N3442 1.10
			2N3525 80p
			2N3614 50p
			2N3702 11p
			2N8714 1.80
			2N3771 1.75
			2N3773 2.25
			2N3790 2.25
			2N3819 35p
			2N3866 75p
			2N3903 15p
			2N4002 14p
			2N4126 18p
			2N4871 85p
			2N5457 38p
			28D01 3.00
			28D26 8.90
			28D30 7.0p
			40250 48p
			40361 45p
			40362 40p
			40408 50p
			40486 75p
			40636 1.00
			40430 85p

TBA800 5 WATT I.C.
Suitable alternative to SL403D. 5/30 volt operated. 8/16 ohm 5 watt output. With circuits and data £1.50



Sinclair IC12
with circuits and data. 6 watt IC with printed circuit board 28 volt operated £1.80




ZN414 IC
Integrated circuit radio as featured by many magazines (PW Jan. 73 Reprint Ref. No. 19 for 10p) £1.20




Toshiba Power and Preampifier modules
TH9013P 20 watt Power amplifier 22-0-22 or single 45 volts operated £4.57



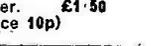TG9014P Stereo
two channel preamplifier. £1.50 (circuit book No. 42 price 10p)



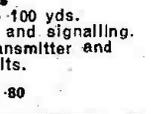Ultrasonic Transducers
Operate at 40kHz up to 100 yds. Ideal remote switching and signalling. Complete with data transmitter and receiver new I.C. circuits. Per pair £5.90 TA960 IC with socket £1.80



3015F 7 SEG.
I.C. size complete with data price £2 each or 4 for £7 (digital clock circuits ref. No. 31, 15p)



TRANSISTORS SPECIAL OFFER

2N3055	AF117
2547p ea	2515p ea
10042p	10013p
50039p	50012p
100034p	100010p

BY127	OC35
2512p ea	2546p ea
10010p	10042p
5009p	50038p
10008p	100034p

ZENER DIODES
400 m/w BZY88/BZX83. From 3-3 volt - 33 volts 10p each.

1-3 watts 5% Miniature Tubulars IN4700 series. From 3-3 volt - 33 volt 18p each.

10 watts. Std Mounting. ZS series 6-8 volts - 100 volts 5% 40p each.

SILICON RECTIFIERS
1 amp series IN4001 to IN4007 From 6p ea 1.5 amp PL4001 to PL4007 From 8p ea 3 amp PL7001/IN5400 From 14p ea Send for full list 36

More of EVERYTHING AT HENRY'S
See pages 819-820, and Back Cover of this magazine. **BEST VALUE**

TRIACS - Std. mounting with accessories
3 AMP RANGE

Type	P.I.V.	Price ea.
SC35A	100v	80p
SC35B	200v	85p
SC35D	400v	90p
SC35E	500v	£1.20



Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS
 IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS
 You need a catalogue! 55p post paid complete with Discount Vouchers



UK's
**LARGEST RANGE
 OF KITS &
 GADGETS**

TEST EQUIPMENT

MULTIMETERS

(Carr. etc. 30p)

200H (M210) 20K/Volt Slimline with case	4.95
TLH33D 2K/Volt Robust with case	4.95
U437 10K/Volt Steel case. AC up to 40 KHz	4.95
U4324 20K/Volt with AC current ranges	8.00
AF105 50K/Volt with Leather case	9.50
U4313 20K/Volt AC current. Steel case	10.50
U4341 Plus Built in transistor tester	10.50
Model 500 30K/Volt	9.95

OTHER EQUIPMENT

SE250B Pocket Signal Injector	1.90 carr. 15p
SE500 Pocket Signal Tracer	1.50 carr. 15p
TE15 Grid Dip meter 440kHz-280MHz	13.45 carr. 30p
TE40 AC Millivoltmeter 1-2mHz	18.75 carr. 35p
TE65 28 Range valve voltmeter	19.25 carr. 40p
TE20D 120kHz-500mHz RF Generator	16.95 carr. 40p
TE22D 20Hz-200kHz Audio Generator	18.75 carr. 40p
SE350A Deluxe Signal Tracer	9.95 carr. 20p
SE400 Volts/ohms/R-C sub./RF field/RF gen.	11.25 carr. 20p

New Revolutionary Supertester 680R


680R Multi-tester	£18.50
Accessories	
Transistor tester	11.00
Electronic voltmeter	18.00
Ampclamp	11.95
Temperature probe	11.95
Gauss meter	11.95
Signal Injector	5.95
Phase Sequence	5.95
EHT Probe	5.95
Shunts 25/50/100A	4.50 each

A SELECTION OF INTERESTING ITEMS

C3025 Compact transistor tester	5.50 p & p 15p
E1300 Mono mag. cart. preamp.	1.95 p & p 15p
E1310 Stereo mag. cart. preamp.	4.95 p & p 25p
Easiphone telephone amplifier	6.15 p & p 25p
D1203 Teleamp. with PU coil	3.60 p & p 20p
LL1 Door Intercom. and chime	11.95 p & p 25p
Chattalite (lights as you talk)	13.90 p & p 20p
1 Kw Dimmer/controller	3.00 p & p 10p
9" Twin spring unit For	2.75 p & p 15p
16" Twin spring unit Reverbs	6.50 p & p 25p
Car Tachometer Electronic	7.50 p & p 15p
VHF 105 Aircraft Band Corrector	3.95 p & p 15p
B2005 4 Ch. m.c. mixer	2.95 p & p 15p
B2004 2 ch. Stereo mixer	4.75 p & p 15p

BUILD THIS RADIO

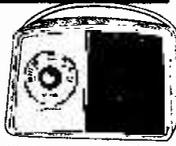Portable MW / LW radio kit using Mullard RF/IF module. Features MW — bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7.98 (battery 22p), carr. etc. 32p.



EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO + or - Earth with speaker and fixings. £6.50 carr./packg. 30p.	AKAI GXC40 Stereo cassette recorder. £59.95 carr./packg. 50p. Pair Akai ADM microphones. £6.95 carr./packg. 20p.
8 TRACK CAR STEREO (- Earth) with speakers in Pods & fixings. £12.50 carr./packg. 40p.	5 WAVEBAND PORTABLE TWIN SPEAKER RADIO. FM/MW/SW/AIRCRAFT—PUBLIC SERVICES. £10.45 carr./packg. 30p.
HANIMAX HC1000 Battery cassette recorder. £10.50 carr./packg. 25p.	PORTABLE CASSETTE TAPE PLAYER—for car or carry around. £7.25 carr./packg. 20p.
HANIMAX HC2000 Battery/Mains cassette recorder. £13.50 carr./packg. 30p.	HANIMAX POCKET CALCULATOR WITH % KEY. £33.50


SPECIAL PURCHASES

AVOMETER MOVEMENTS. AVO 8 or 9 50mA MOVE-MENTS. Ex Brand New AVO's £3.50 Post 20p.

UHF TV TUNERS CHANNELS 21 TO 64 Brand new transistorised geared tuners for 625 Line Receiver IF output. £2.50, Post 20p.

EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

Model No.		
310 Radio control receiver	2.98	
300 4-channel R/C transmitter	5.95	
345 Superhet R/C receiver	5.95	
455 AM signal generator	12.33	
65 Simple transistor tester	1.40	
115 8 watt Amplifier	3.90	
120 12 watt amplifier	4.70	
125 Stereo control unit	5.70	
130 Mono control unit	3.60	
605 Power supply for 115	4.55	
610 Power supply for 120	4.55	
615 Power supply for 2 x 120	5.73	
230 AM/FM aerial amplifier	2.93	
240 Auto packing light	5.90	
275 Mic. preamplifier	6.08	
570 LF generator 10Hz-1mHz	15.80	
575 Sq. wave generator 20Hz-20KHz	14.60	
590 SWR meter	12.85	
620 Ni-CAD Charger 1.2-12v	8.00	
630 STAB Power supply 6-12v 0.25-0.1A	8.15	
690 DC motor speed Gov.	2.87	
700 Electronic Chaffinch	7.00	
705 Windscreen wiper timer	6.80	
760 Acoustic switch	10.75	
780 Metal Detector (electronics only)	9.65	
790 Capacitive Burglar alarm	6.85	
835 Guitar preamp.	4.25	
840 Delay car alarm	6.15	
875 CAP. Discharge ignition for car engine (-Ve Earth)	13.15	
880 Scope Calibrator	2.25	
255 Level indicator	6.15	
525 120-160mHz VHF timer	11.30	
715 Photo cell switch	7.70	
795 Electronic continuity tester	4.30	
860 Photo timer	13.25	
871 Slide projector auto feed control	7.15	
235 Acoustic Alarm for driver	7.60	
465 Quartz XTAL checker	8.75	
220 Signal Injector	2.30	
390 VOX	15.50	
432 Testakit	10.30	
670 Buffer Battery Charger	6.55	
885 Capacitive Contact Alarm	6.25	
850 Electronic Keyer	18.75	
820 Electronic Digital Clock	58.50	

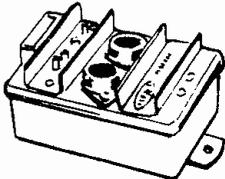

ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY

BUILD THIS TUNER

MW/LW Radio Tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/4". All parts £4.85, carr. 15p.



MULTI-USE & RADIONIC KITS

10-1 10 Projects	3.60
50-1 10 Projects	8.00
150-1 150 Projects	13.20
Telephone Communicator	7.20
X20 20 (Elec.)	4.95
X40 40 (radio)	9.45
(carr./packg 40p)	

All transistor circuits with hand books

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/Eraser heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9.50 carr. 30p

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).

Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.

Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 65p each. (Quantity discounts available)

Complete with knobs.

MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO '17' High Impedance £2.00

'18' Med. Impedance £2.00

R730/E73 2 track mono Record/Eraser low imp. 75p pair.


Eraser Heads for '17' and '18' 75p

'63' 2 track mono, Hi imp. £1.75

'43' Eraser Head for '63' 75p (Post. etc. 15p any quantity).

SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

AMPLIFIERS (carr., etc. 20p)	
4-300, 0.3 watt 9 volt	1.75
104, 1 watt 9 volt	2.20
304, 3 watt 9 volt	2.50
555, 3 watt 12 volt	2.85
E1208, 5 watt 12 volt	4.50
608, 10 watt 24 volt	4.10
410, 10 watt 28 volt	4.95
Z30, 15 watt 30 volt	3.57
E1206, 30 watt 45 volt	9.75
Z50, 30 watt 50 volt	4.37
E1210, 2 1/2 + 2 1/2 watts	5.25
12 volt	5.25
RE500, 5 watt IC mains operated Amplifier with controls	£6.30
SAC14, 7 + 7 watt Stereo with controls	£8.00
SAC13, 15 + 15 watt Stereo with controls	£11.00
SINCLAIR (carr. 20p)	
PROJECT 60 Z30 3.57	Z50 4.37
Stereo 60 Preamp.	7.97
PZ5 £3.97, PZ6 £6.37	PZ8 (for Z50) £4.77
(TRANS £2.95)	
AFU £4.45	
New SINCLAIR PROJECT 80	
Stereo Preamp.	9.50
Audio Filter Unit	5.50
Z40 15 Watt Amp.	4.30
Z60 25 Watt Amp.	5.50
PZ5 Mod. for 1 on 2 Z40	3.98
PZ6 Mod. (S Tab) 1 on 2 Z40	6.25
PZ8 Mod. (S Tab) 1 on 2 Z60	6.30
TRANSFORMER FOR PZ8	2.95
Project 605 Kit	19.95

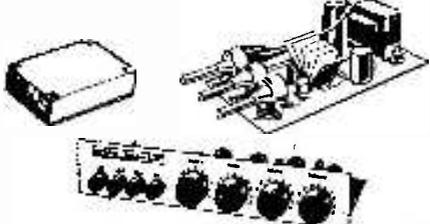


POWER SUPPLIES FOR EVERY PURPOSE

(All cased unless stated chassis)	
470C 6.75/9 volt 300 MA (includes Multi-Adaptor for Tape Recorders, etc.)	1.95 post 20p
Car Lighter Voltage Adaptors 300mA (State voltage 6v, 7.5v, 9v)	1.95 ea. post 25p
SC202 3.6/7.5/9 volt 400mA	3.25 carr. 30p
HC244R Stabilised version	4.25 carr. 30p
P500 9 volt 500mA	2.80 post 20p
P11 24 volt 500mA (chassis)	2.80 post 20p
P15 26/28 volt 1 amp (chassis)	2.70 post 20p
P1080 12v 1 amp (chassis)	3.25 post 20p
P1081 45v 0.9 amp (chassis)	4.40 post 20p
P12 4 1/2-12 volt 0.4-1 amp	6.75 post 30p
SE101 A 3/6/9/12 volt 1 amp (Stab.)	9.15 post 25p
RP164 6/7.5/9/12 1 amp (Stab.)	9.95 post 30p

FIBRE OPTICS

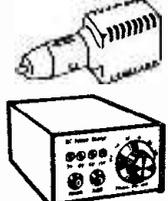0.01 Diam. Mono Filament £1.50 per 25 metre reel
 0.13 Diam. 64 Fibres Sheathed, £1.00 per metre
 SPRAYS 15mm Diam. Mares Tails £9.50.



Henry's RADIO LIMITED
 EDGWARE ROAD, W2

SEE FACING PAGE FOR ADDRESSES

Henry's

DISCOUNT HI-FI, TV, TAPE AND CAR ENTERTAINMENT

Low prices means less VAT - Henry's give full guarantees and demonstrations for callers. Plus big savings.
Also at Modern Electrics (Retail) Ltd., 120 Shaftesbury Avenue, W.1.—Your Sony dealer.

STEREO AMPLIFIERS

(carr./packing 50p)			
AKAI	AA5200	81.70	
	AA5500	78.50	
	AA5800	117.50	
AMSTRAD	1C2000 Mk. II	29.50	
	4000 Mk II	23.95	
EAGLE	TS149	25.10	
	TS151	34.85	
	AA2	30.80	
	AA4	42.45	
	AA6	55.95	
HOWLAND WEST	DA1000	22.45	
HENELEC TEXAN	Kit	28.50	
HENELEC TEXAN	Built	35.00	
NIKKO	TRM300	25.95	
	TRM400	32.50	
PIONEER	SA500A	34.25	
ROTEL	RA 211	32.65	
	RA311	41.15	
	RA611	60.80	
	RA810	75.75	
	RA1210	92.50	
SINCLAIR	2000	22.95	
	3000	28.95	
TANDBERG	TA300	66.10	
TELETON	SAQ206B	22.50	
	SAQ307	22.50	
	GA202	28.50	

STEREO RADIO TUNERS

(carr./packing 50p)			
AKAI	AT550	60.50	
	AT580	94.50	
AMSTRAD	3000	23.55	
EAGLE	AAB	40.50	
	TST152	29.45	
HENELEC Stereo Kit		21.00	
HENELEC Stereo Built		24.95	
HOWLAND WEST	DA1000T	25.35	
PIONEER	TX500A	48.75	
ROTEL	RT222	32.65	
	RT322	43.75	
	RT622	65.40	
SINCLAIR	2000	26.95	
	3000	26.95	
TELETON	GT202	30.50	

DECODERS / SYNTHESIZERS (carr. etc. 30p)

DYNACO QUADRATOR		16.90	
EAGLE	AA10	12.00	
	AA26	16.35	
TATE 1		7.95	
TATE 3	Chassis	15.75	
TATE 4		19.95	
TATE 7	Boxed	25.95	

MATCHED SPEAKER SYSTEMS

Recommended pairs 8 ohms (Carr./Packing £1.50 pair)

RANK DOMUS

150		26.95 pr.
175		33.75 pr.
250		53.75 pr.

MARSDEN HALL

110	10 watt	22.50 pr.
150	15 watt	27.50 pr.
200	20 watt	34.50 pr.

DYNACO

A10		43.00 pr.
A25	20-60 watts	69.00 pr.
A35		79.00 pr.

WHARFEDALE

Denton 2	18 watt	27.20 pr.
Linton 2	20 watt	32.65 pr.
Melton II	25 watts	51.80 pr.
Triton	25 watt	40.80 pr.

LEAK

150	18 watt	32.65 pr.
250	18 watt	44.30 pr.

CELESTION

120	20 watt	37.80 pr.
COUNTY	25 watt	33.60 pr.
15	30 watt	50.40 pr.
44	44 watt	81.20 pr.

UK's largest stockists for KEF Acoustic Research, Mordant Short & Cambridge Audio speakers. In stock and on demonstration. Phone for keenest price.

BATTERY CASSETTE RECORDERS (carr. etc. 30p)

Amerex	100	11.00
Wien	ET1008	11.00
Philips	EL3302	14.40
	N2203	16.60
	N2211	19.95
Sanyo	M1101	14.65
	M1102	12.95

STEREO MAGNETIC CARTRIDGES (carr. etc. 15p)

SHURE	M44C	4.20
M3Dm	M75/6/11B	6.75
M44.7	M75 EDII	8.50
M44.7	M75 EJI	7.95
M55E	M75GII	7.25
GDLDRING		
G850	G800SE	10.00
G800	G820	6.70
G800H	G820E	10.00
G800E	G820SE	13.35
ADC		
Q35	Q30	5.90
Q36		
Q37		

GRADO		
FTR	5.25	FTE 8.25
F3E	11.25	F2 18.75
EMPIRE		999TEX 14.95
		999REX 3.70
		999QUX 4.80
		999XEX 8.50
		SM500/7 4.60
		SM500/5 4.60
		SM500/E 6.95

RONETTE

STEREO COMPACTS

Complete with Speakers (c.p. £1.25)

Fidelity	UA3	39.90
Sanyo	G2601KL	125.50
Sanyo	G2615N	71.50
Sanyo	GXT4520KL	103.50
Sanyo	GXT4730KL	97.50
Philips	GF908	102.75
Philips	RH802	159.95
Philips	RF836	57.20
Philips	GF826	41.75
Philips	RH811/RH421	84.95
Philips	RF839	55.95
Philips	GF829	39.95
Philips	GF815	47.75
Philips	GF808	65.75
Philips	RH814/RH411	86.75
Philips	GF603	19.95

8 TRACK STEREO HOME UNITS (carr/packing 70p)

Amerex ACR301 (with MW/FM stereo radio) 48.00

PORTABLE TV

BATTERY/MAINS (c.p. £1.00)

Elizabeth T9	9"	43.50
Crown 9TV	9"	48.50
Elizabethan T12	12"	43.95
Teleton TW12	12"	46.95
Sanyo 10T150	9/10"	52.50

CASSETTE PLAYER FOR CAR - HOME AND AROUND



Actually the price reflects the quality of the superb player. It is of beautiful quality both in sound and looks. Features wind, rewind, volume and tone controls. Speaker is very good indeed. Comes complete with earphone, batteries. Full guarantee. Optional adaptor to run off car or mains.

DOLBY / NRU (carr./packing 30p)

Teleton	SNR100D	28.50
Philips	N6720	15.00
Teac	AN60/AN80/AN180	stocked

RECORD DECK PACKAGES (carr./packing 75p)*Less cart.—rest with (HL)

(HL)	SP25 III/800 or H	15.95
(M)	SP25 III/M756S	19.45
(HL)	AP76/G800	25.55
(M)	AP76/M756S	29.10
(HL)	GL75 P/C	33.50
(HL)	GL75 P/C G800	36.65
(HL)	GL75 P/C G800E	39.15
(HL)	MP60 (TRD1) G800	15.80
(HL)	HT70 (TPD1) G800	19.50
RANK DOMUS	BD200	43.60
	BA400	55.95
	*Pioneer PL12D	31.75
	*Thorens TD165	43.80
	Thorens TD160C	50.80

BATTERY / MAINS CASSETTE (carr. etc. 35p)

Wien	RT452	13.65
Amerex	AC101	12.00
Elizabethan	LZ315	12.25
Amerex	AC104	16.00
Philips	N2204	20.75
	N2205	20.50
PYE	9115	27.75
	9118	21.20
Hitachi	TRQ291	27.50
Sanyo	M2000G	23.25
	MR4010G	28.95
	M4000G	48.90
BASF	CC9201	37.25
Hitachi	TRQ2335	49.50

BATTERY / MAINS RADIO CASSETTE RECORDERS (carr. etc. 30p)

Amerex	ACR200	22.00
	ACR201	30.00
Elizabethan	LZ416	27.25
	LZ516	29.10
BASF	CC9301	50.75
Philips	RR322	28.75
	RR413	33.90
	RR712	48.30
Sanyo	M4141FG	43.20
	M2400W	36.90
	M2400FG	36.90
	M4400FG	68.50
Grundig	C250	47.95
Hitachi	TRK1240E	29.50
	TR51161	35.00
	KCT1210L	33.50

STEREO RECORDER DECKS (carr./packing 50p)


Cassette	N2506	44.50
	N2510	£87.10
Pye	9145	44.50
Tandberg	TCD300	112.00
Akai	CS30D	50.65
	CS33D Dolby	62.50
	GXC36D	65.15
	GXC40D	57.40
	GXC38D Dolby	81.45
	GXC48D Dolby	89.15
	GXC45D	74.30
TEAC	A250/A350—A450	Stocked

Reel to Reel Akai 4000DS 62.50
Tandberg 3321X/3341X 107.70
Large range Akai/Tandberg/Revox/Teac stocked.

STEREO PHONES (carr./packing 20p)

AKAI	TTC	6.60
ASE11	G3000	5.95
ASE20	G2222	5.95
ASE22	MD802	1.95
	MD806	3.75
DULCI		
SH650D	2.25	SE20A 5.90
SH850GX	3.95	SE30A 9.45
SH1300VS	5.25	SE50 16.35
AKG	SEL20	7.90
K60	SEL25	11.15
ROTEL	SEL40	12.60
RH830	4.85	ACCESSORIES
RH700	6.75	H1012/JB3
SENHEISSER	Junction Box	1.40
HD414	JB3DE Din	1.60
WHARFEDALE	Junction Box	1.60
DD1	JB11D De Luxe	8.95
ISODYN	Junction Box	1.95
KOSS	0250 Phone	
K6	9.95	Switch 4.75
K6/LC	11.25	CONTROL
K711	7.95	BOXES
KRD711	7.95	G1301
HV1	17.50	(two phones) 2.62
K0727B	12.45	G1305
K0747	15.95	Controller 2.15
PR04AA	21.95	FF17 2-pairs 2.15
PR05LC	23.95	(Silders) 6.25
HOWLAND WEST	Koss T4A	4.20
CIS200	2.75	TA 4.95
CIS250	5.25	T10A 8.50
CIS1000	7.50	HW Mk.III
CIS2000	15.25	Controller 6.90

BEST VALUE IN U.K.

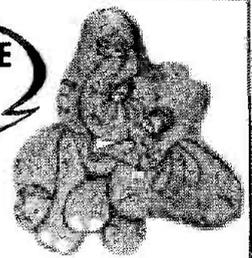

8 Track Akai	CR81D	53.60
	CR80DSS	93.65

STEREO RECORDERS (carr./packing 70p)

Akai	1721L	67.20
Cassette Akai	GXC40 Dolby	59.95
	GXC46 Dolby	69.95
Philips	N2400/RH411	63.75
	N2401/RH411	74.50
	N2401S/RH411	79.95
	N2405/RH401	49.50

8 TRACK Akai CR81 66.20

STEREO TUNER AMPLIFIERS (carr./packing 75p)

Akai	AA8030	92.50
Goodmans	Module 80	59.20
Goodmans	Module 90	75.75
Goodmans	One/Ten	88.50
Pioneer	SX525	96.75
	SX626	124.75
Rotel	RX150A	41.95
	RX200A	53.95
	RX400A	64.95
	RX600A	90.00
	RX800	114.50
	RX154A	78.30
Tandberg	TR200MPX	85.15
	TR1000MPX	143.75
	TR1010MPX	149.95
Teleton	TSF55	57.20

8 TRACK PLAYER DECKS (carr./packing 35p)

Elizabethan	8/LZ1	13.40
McDonald/BSR	TD8S	12.75
	TD83V	15.25

IN CAR ENTERTAINMENT CAR RADIOS (carr/packing 35p)

MW/LW Complete with speakers		7.00
SHIRA Touring		9.00
SHIRAMATIC		13.65
PHILIPS RN270		17.40
PHILIPS RP305		26.75
PYE 2644		18.25
PYE 2062		10.95
COURIER MC101		14.75
COURIER PCS51		12.45
SHARP ATR 933		18.60
SHARP AR 947		18.60
STEREO CASSETTE (carr/packg 35p)		
Complete with Speakers		
SHIRA NA300		18.50
SHIRA CP401		23.75
PHILIPS N2607		26.40
R/MOBILE 302CS		32.00
PYE 2252		24.75
PYE 2253		28.40
HANIMAX HC6010		38.95
SELMAR		
(Plus MW/LW Radio//		38.95
STEREO 8 TRACK (carr/packg 35p)		
Complete with speakers		
SHIRA ST805		15.00
WALTHAM TRE 1500		21.00
8 TRACK WITH MW/LW RADIO (carr/packg 35p)		
Complete with speakers		
SHIRA ST1000		25.70
SHIRA ST2000		31.50
MW/STEREO FM (carr/packg 35p)		
Complete with Speakers		
SHARP AR953 CAR RADIO		36.50
SHARP JET 277 (2.5.75) Track		42.65

YOU CAN PAY BY BARCLAYCARD OR ACCESS
For callers or by phone 01-402 4736
Easy credit terms for callers to 309 and 354-356

ALSO STOCKED AND DEMONSTRATED
Armstrong - Acoustic Research
Cambridge Audio Leak - Lux
Marantz - Quad - Revox - Sansul
Tandberg - Sugden - Wharfedale
Goodmans - Celestion - Grundig
Kef - Teac - Bose - Sherwood
Call or phone 01-402 4736 for best prices.

10% VAT to be added to all orders.
Prices & description correct at time of press E&OE. All goods offered subject to stock availability.

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:-
9 am - 6 pm
6 days a week
All stores
open all day
Saturday

MAPLIN ELECTRONIC SUPPLIES

★ **SAME DAY SERVICE**




Model 120

LARGE OR SMALL

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer. Detachable aluminium front panel finished in white.

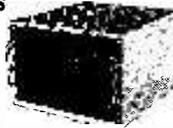

Model 320

Model	W	H	D	Price
120	8	2½	6	£1-85
220	8	6	3½	£2-65
221	8	6	6	£2-80
320	12	8	12	£5-00

Chassis for model 320 **£1-75** extra

Please send s.a.e. for free illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3-7in. x 4-5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

DMO2T (with tremulant) ONLY **£14-85.**

DMO2 (without tremulant) **£12-25.**

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: **£2-85** each OR special price for pack of 12: **£25-00.** S.a.e. please for data sheet.

★ S.a.e. please for full technical details.

Trade enquiries welcome.

TRANSISTORS, DIODES & IC's.

AC127	25p	BF194	15p	OA90	7p
AC128	20p	BF751	13p	OA91	6p
AC176	17p	MPF102	36p	1N914	4p
AD149	47p	OC44	20p	1N4148	4p
AD161/2	69p	OC71	20p	1N4001	6p
BC107	10p	TIS43	28p	1N4002	6½p
BC108	10p	2N1711	24p	1N4003	7p
BC109	10p	2N2219	25p	1N4004	7½p
BC147	10p	2N2646	45p	1N4005	8p
BC148	10p	2N2905	33p	1N4006	8½p
BC149	12p	2N2907	25p	1N4007	9p
BC168	13p	2N2926Y	10p	W005	30p
BC169C	12p	2N2928Y	10p	W04	35p
BC182L	10p	2N2928G	10p	741C 8-pin	
BC204	14p	2N3053	18p	D.I.L.	36p
BC209C	14p	2N3055	49p	741C 14-pin	
BD131	45p	2N3819	24p	D.I.L.	45p
BD132	54p	AA119	7p	D.I.L. Sockets	
BD131/2	£1-20	BY127	16p	8-pin	20p
BD135	36p	BY164	49p	14-pin	15p

See our catalogue for our full range of transistors. 74 series I.C.'s bridges etc.


CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1 63	6p	68 6-3	6p
1-5 63	6p	68 16	6p
2-2 63	6p	68 63	10p
3-3 63	6p	100 4	6p
4-7 63	6p	100 10	6p
6-8 40	6p	100 25	6p
6-8 63	6p	100 40	6p
10 25	6p	100 63	12p
10 63	6p	150 6-3	6p
15 16	6p	150 16	6p
15 40	6p	150 25	6p
15 63	6p	150 40	10p
22 10	6p	150 63	12p
22 25	6p	220 4	6p
22 63	6p	220 10	6p
33 6-3	6p	220 16	6p
33 16	6p	220 25	10p
33 40	6p	220 40	12p
33 63	6p	220 63	18p
47 10	6p	330 4	6p
47 25	6p	330 10	6p
47 40	6p	330 16	10p
47 63	6p	330 63	22p
		4700 4	22p



PLUGS AND SOCKETS

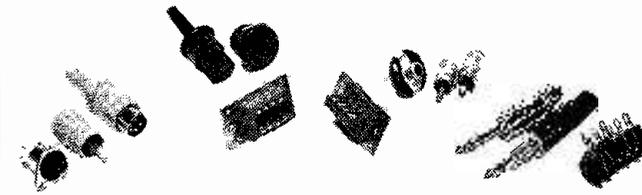

DIN PLUGS

2 pin (1 flat) 8p
3 pin 9p
4 pin, 5 pin A pair 10p
(240°), 6 pin 10p

DIN Sockets

2 pin 6p
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 7p

MAINS

P360 3 pin 1-5A chassis plug with A line socket. Per pair 24p
SA 2190 3 pin 5A chassis plug 17p
SA 1862 Line socket for above 19p

McMURDO

RP8 8 way chassis plug 36p

R88 8 way chassis socket

52p

PHONO

Plug plastic 5p
Plug screened 9p
Chassis socket 4p

JACK

Std. 1/2" mono plug Plastic 18p
Screened 17p

Std. 1/2" stereo plug

Plastic 16p
Screened 25p
Open mono socket 1/2" 10p; Moulded mono socket 1/2" with 2 break contacts 13p; Moulded stereo socket 1/2" with 3 break contacts 18p; 3-5mm. plug plastic 8p; screened 11p; open socket 8p.

WE KNOW YOU NEED IT!



The MES 1974 Catalogue is STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. **WE'RE WAITING TO RUSH YOU A COPY.**

You'll be IMPRESSED with our POST FREE ordering system, EXCITED by our BIG VALUE discount vouchers, STAGGERED by our UNEEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!

OMNIUM GATHERUM

- PP3, 6 etc. battery clip dual min. 9p
- PP1, 9 etc. battery clip separate per pair 6p.
- Pair crocodile clips 1 red, 1 black insulated sleeve. 7p
- Solder Multicore 22swg 10 metres 20p
- Silicone grease in special dispenser 20ml. 43p
- Red neon 240V panel mounting 25p
- Lacing Cord Strong rayon cored PVC 25m. 49p
- Panel fuse holders 20mm 20p; 1½" 30p
- Transformers
LT700 min. output transformer Pri. 1-2k Ω Sec. 5 Ω 200mW 35p
- Sub-min. Mains Transformer 6-0-6V 100mA 95p
- 12-0-12V 50mA 95p
- Size: Both approx. 30 × 27 × 25mm.
- Min. Mains Transformer (Size: 46 × 31 × 38mm) 0-12V 250mA, 0-12V 250mA £1-35
- Mains transformer MT3AT Pri. 200-220-240V, Sec. 12-15-20-24-30V 2A £2-48
- Mains Transformer MT206AT Pri. 200-220-240V, Sec. 0-15-20V 1A, 0-15-20V 1A £3-10

Also in stock: Wide range of brass and nylon nuts, bolts and washers + solder tags, shakeproof washers etc.

POTENTIOMETERS

Rotary miniature carbon track 1/2" spindle

Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p



Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 38p.



Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 23p

PRESETS

Sub-miniature 0-1W Vert or Horiz 100, 250, 500, 1k, 2-5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p

Wirewound 10% 1W 1/2" spindle 10, 50, 100R 34p; 250, 500, 1k, 5k 33p; 10k, 37p; 25k 40p; 50k 44p.

RESISTORS

Carbon Film 1/4W 5% 1 Ω to 1M; 10% 1-2M to 10M	E12	1p
Carbon Film 1/4W 5% 1 Ω to 10Ω; 10% 1-2M to 10M	E12	1p
Carbon Film 1/4W 5% 11 Ω to 910k	E12 & E24	1p
Carbon Film 1W 5% 10 Ω to 10M	E12	3p
Metal Oxide 1/4W 2% 10 Ω to 1M	E12 & E24	4p
Wirewound 2 1/4W 10% 0-22ohms to 0-47ohms	E12	10p
Wirewound 2 1/4W 5% 1ohm to 270ohms	E12	10p

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

KNOBS

All 1/2" shaft. Grub screw fixing

Diameter shown in brackets

K30/1 (13mm) 24p	K30/3 (17mm) 22p	K30/2 (13mm) 28p	BK12 32mm long, black pointer with white stripe 6p	K30/6 (32mm) 41p
F18 (26mm) with numbered skirt 21p	F12 (33mm) 21p	MK50 (34mm) 27p	CK4 (36mm) 14½p	

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 24p. Mains rotary DPDT 250V 2A 20p.

Push to make non-locking 12p	Slide Miniature DPDT 9p
Toggle 250V 1-5A with ON/OFF plate 25p.	Sub-miniature toggle DPDT (12 × 12-5 × 14mm excl. toggle) 250V 3A 61p

VAT Please add 10% to the final total.

Post & packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. **PHONE SOUTHEND (0702) 44101**

DISCOUNTS UP TO

60%

FULL 12 MONTH AFTER SALES SERVICE

with probably the best
discounts offered in the U.K.

ALL PRICES ARE INCLUSIVE OF V.A.T.

FANTASTIC OFFER GARRARD SP25 Mk III.

Goldring G800. Teak finish,
plinth and tinted cover with
mains lead and DIN plug and
screened lead. All fully wired.
Please add £1.75
for P. & P. and Ins. **£14.95**

TURNTABLES

Please add 95p P & P and Ins.

BSR MP60	£9.25
Garrard SP25 Mk III	£9.95
Garrard SL65B	£12.95
Garrard AP76	£16.65
Garrard 401	£27.50
Garrard Zero 100 (sgle)	£30.95
Garrard Zero 100 (Auto)	£34.95
Goldring GL85/P. P & C	£65.95
Goldring GI01/P P & C	£21.95
Goldring GL72	£24.95
Goldring GL72/P	£31.95
Goldring GL75	£30.95
Goldring GL75/P	£38.95
Goldring GL75 Lid	£4.25
Thorens TD125	£60.95
Thorens TD125 AB Mk II	£93.95
Thorens TD160 AB & C	£51.95
Thorens TD165 AB & C	£45.95
Condor Auto Cleaner (Star Value)	£1.40 P & P 15p

TUNERS

Please add 95p P & P and Ins.

Alpha Highgate FT150	£32.95
Amstrad Multiplex 3000	£23.90
Metrosound FMS 40	£37.75
Philips RH 621	£72.95
Metrosound FMS 20 Mk II	£37.75
Rogers R/brook FET 4 (Cha)	£32.95
Rogers R/brook FET 4 (Cased)	£36.50
Sinclair cased tuner	£27.50
Teleton GT202 (N/P)	£32.95

SPEAKERS

£1.65 for P & P (Per Pair)

Amstrad Acoustra 1500	£26.90
Amstrad Acoustra 2500	£30.75
Celestion Ditton 15	£50.75
Celestion Ditton 44	£79.45
Goodmans D/Maxim	£40.95
Goodmans Mezo 3	£50.95
Goodmans Havant	£35.25
Keletron KS4	£13.85
Keletron KS8	£22.50
Sinclair Q16	£11.95
Sinclair Q30	£30.95
Wharfedale Denton II	£26.80

SPEAKER UNITS

Wharfedale Linton Kit	£16.85
Wharfedale Glendale Kit	£29.95
Wharfedale Unit 3	£16.30
Wharfedale Unit 4	£28.70
Wharfedale Dovedale Kit	£44.95

All prices correct
at time of press
(E. & O. E.) and
are subject to
alterations

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept PW1, 174 Pentonville Road, London, N1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue,
Hifford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to
6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS. Order with confidence. Send Postal Order, Cheque,
Money Order, Bank Draft, Giro or Cash by Registered
Mail. CALLERS: Please note that cheques can only be accepted together
with cheque cards (not Barclay Card)

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS
on main road leading to the East and West Country



for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores
of non-corrosive flux, instantly cleaning
heavily oxidised surfaces. No extra flux
is required.

EASY-TO-USE DISPENSERS



Size 5
Savbit alloy
18 swg, 18p
(illustrated).
Size 19A
60/40 alloy
18 swg, 18p
Size 15
60/40 alloy
22 swg, 22p

IDEAL FOR HOME CONSTRUCTORS


Size 1 cartons in 40/60, 60/40
and Savbit alloys
in 7 gauges 25p



Size 12 REEL
for Service
Engineers and
Electricians.
18 swg
Savbit alloy. 75p



BIB WIRE STRIPPER AND CUTTER

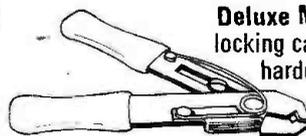

Deluxe Model 9 Automatic opening spring,
locking catch, plastic-covered handles. Case
hardened and precision ground. Adjusts
to most wire sizes. Cuts and strips
flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T.
From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to
Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

AMPLIFIERS

Please add 95p P & P and Ins.

Amstrad 8000 Mk II	£15.85
Amstrad IC2000 Mk II	£32.15
Amstrad Integra 4000	£23.95
Alpha Highgate FA400	£39.05
Global 10 + 10	£19.75
Global 20 + 20	£25.95
Keletron 1000	£22.95
Keletron 1500	£25.75
Metrosound ST20E Mk II	£29.95
Metrosound ST60	£31.95
Rogers R/brook (Ch)	£41.15
Rogers R/brook Mk III (Ca)	£44.50
Rogers R/bourne (Ch)	£54.25
Rogers R/bourne (Ca)	£56.95
Sinclair 2000	£24.90
Sinclair 3000	£31.95
Sinclair 605	£21.45
Sinclair PRO 60 2 x Z30/PZ5	£16.40
Sinclair PRO 60 2 x Z30/PZ6	£19.45
Sinclair PRO 60 2 x Z50/PZ8	£25.25
Trans Sinclair AFU PRO 80 (Filter Unit)	P.O.A. P.O.A.
Sinclair Stereo 80 Pre-amp	£3.85
Sinclair Z30 Amp	£4.50
Sinclair Z50 Amp	£4.20
Sinclair PZ5 Power Supp.	£6.15
Sinclair PZ6 Power Supp.	£6.15
Sinclair PZ8 Mains Trans.	£4.95
Sinclair PZ8 Power Supp.	£6.15

TUNER/AMPLIFIERS

Please add £1.10 P & P and Ins.

Alpha FR 3000	£61.35
Goodmans Module 80	£62.95
Goodmans Mod 80 Com	£109.95
Goodmans Mod. 90	£76.95
Goodmans One-Ten	£92.95
Rogers R/brook (Cha)	£61.95
Rotel 150A	£45.25
Rotel 200A	£57.95
Status STA160	£89.95

PLINTH AND COVERS

£3.35*

For Garrard SP25,
2025 TC,
3000,
AP76, SL72B, SL95B, etc
£4.85 + 71p P & P.



CARTRIDGES

Please add 11p P & P and Ins.

Goldring G850	£2.75
Goldring G800	£3.50
Goldring G800E	£6.30
Goldring G800SE	£10.90
Shure M3D	£3.25
Shure M44E	£4.95
Shure M55E	£5.00
Shure 75ED Type 2	£9.25
Shure V15	£25.95
Shure M75EJ Type 2	£7.95
Sonotone 9 TAMC	£1.20
Sonotone V 200F	£8.55
Audio Technica AT 66	£3.15
ADC 10E Mk IV	£14.95
Ronette SM 500/7	£5.25
Ronette SM 500/E	£7.95

WEYTRONIC

	1-99	100 +
IN 4003	5p	4p
IN 4006	8p	7p
IN 4148	5p	4p
BC 107	9p	8p
BC 108	9p	8p
BC 109	9p	8p
BFY 50	17p	14p
2N 3055 (Solidev)	48p	43p

TRIAC (Plastic)

8 amps 200v.		
40668 (RCA)	69p	59p
8 amps 400v.		
40669 (RCA)	78p	69p

DIAC

45412 (RCA)	25p	18p
-------------	-----	-----

LINEAR (Teledyne)

741 8 pin	39p	36p
-----------	-----	-----

Prompt despatch by post.
All Devices Brand New.
Please add 10% V.A.T. plus 10p postage.

Cash with order to:—

WEYTRONIC

5, ROYAL TERRACE, WEYMOUTH, DORSET

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible Russians have done it all **NOW!** It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £18.50—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! ★Send quickly, from receipt of goods test on mail order 7 days approval, refund if not delighted. Or call. Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions, VHF, FM/USW, AM: LW, MW, SW, gets, locally, local & new stations, not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON-OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 in approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE** 13in x 10in x 4in overall approx. Magnificently designed, in highly polished cases. Made to give years of perfect service. Purer & sweeter tone than ever. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram. **PLUS** ultra sensitive earphone for personal listening. **ONLY £18.50** (with mains/battery eliminator £2.25 extra) **BOX, POST, ETC. 45p. NO MORE TO PAY!** ★**BUT WAIT**, for only 75p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (it enables you to zone & time in a flash for transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard 'longlife' batteries and Converter Plug. (Sorry—We cannot change these new radios for any earlier model purchased.) Send quickly to Uxbridge Road address, or call at either Store. **BUT HURRY! SHOPERTUNITIES SAVE YOU £££'s and £££'s**


THOUSANDS OF MILES REDUCED TO INCHES?
LATEST RUSSIAN RADIO TECHNOLOGY
SHRINKS THE WORLD! *COMPUTERISED?

THIS FANTASTIC
EARTH SHRINKER



BRAND NEW FABULOUS ASTRAD 17

PORTABLE RADIO & COMMUNICATIONS RECEIVER

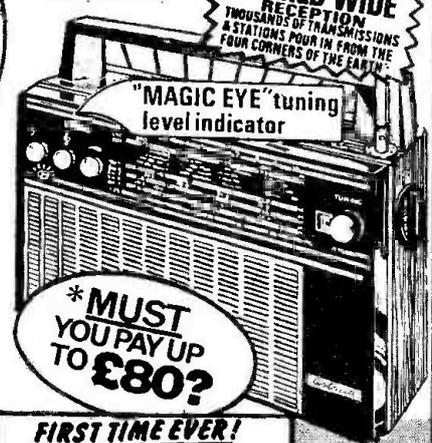

28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)

BATTERY MODEL £18.50 **BOX POST ETC. 45p**
MAINS/BATTERY ELIMINATOR £2.25 extra

FIRST TIME EVER!
***NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE!**
NO MORE GUESSWORK - INSTANT DATA at your fingertips - enables you to ZONE & TIME IN A FLASH for transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! **SAVE £23.03 NOW!**
FABULOUS BRAND NEW SOLID STATE **This equipment's got EVERYTHING!**

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

WITH REMOTE CONTROL MICROPHONE

RECOMMENDED RETAIL PRICE £44
OUR PRICE £20.97 **CARR. ETC. 50p**

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous **VHF, AM/FM Radio AND Cassette Tape Recorder & Player** combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord.) Record and play back anything, anywhere! **IMPORTERS RECOMMENDED RETAIL PRICE £44! WE OFFER AT UNDER HALF PRICE**

Wonderful features: ★ Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! ★ Separate ON/OFF and HI-LO volume controls! ★ Heavy duty built-in speaker! ★ Earphone (for personal listening or "monitoring") and extension speaker sockets! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in. approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. **AND** the amazing built-in full circuit **VHF, AM/FM** Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, local city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££'s more for a Car Radio or Car Cassette player **ALONE!** £20.97, carr. etc., 50p—**NO MORE TO PAY!** Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 28p extra if required. Callers: **ACCESS & BARCLAY CARDS ACCEPTED AT BOTH STORES.**

FIRST TIME EVER! SAVE £16.02!
BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER

With remote control microphone.

FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26.97!
OUR PRICE £10.95 **POST ETC. 50p**

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb de luxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £10.95**. Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the **BEST** expensive "PIANO KEYBOARD" CONTROL PANEL (or latest **MASTER SWITCH** control) **AND AUTOMATIC LEVEL CONTROL**. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60 or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Complete—record anywhere, indoors or out! Runs on standard batteries **AND 220/240V AC** mains. Separate jacks for remote control microphone, etc. Size 9 1/2in x 5in x 2 1/2in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Importers recommended selling price £26.97!) **OUR PRICE ONLY £10.95, post, etc. 50p. NO MORE TO PAY!** ★Send quickly, test on mail order 7 days approval from receipt of goods—refund if not delighted. **BONUS OFFER**—Cassette tape, Standard batteries **AND** microphone stand 55p extra, if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores. **(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn Store.)**

SHOPERTUNITIES LTD.

Dept. WP/NC/36, 164 UXBIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.). **BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.**

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone 6743

OA2	.40	6BE6	.28	6LD20	.55	14H7	.55	85A3	.40	EAF801	.55	EF86	.30	HN309	1-40	PL81A	.55	UF89	.38	AC128	.22	BC115	.17	OA85	.09
OB2	.40	6BH6	.70	6N7GT	.60	19A05	.42	90C1	.75	EB34	.25	EF89	.27	HVR2	.58	PL82	.37	UL41	.65	AC132	.22	BC116	.28	OA90	.14
OZ4	.47	6BJ6	.50	6Q7G	.50	19G8	1.40	90CG	2.40	EB91	.15	EF91	.30	HVR2A	.58	PL83	.39	UL84	.38	AC154	.22	BC118	.25	OA91	.10
1A3	.52	6BQ7A	.50	6Q7GT	.50	20D4	2.00	150B2	.75	EB44	.55	EF92	.30	KT2	.25	PL84	.33	UM80	.44	AC156	.22	BCY10	.50	OA95	.10
1A5GT	.50	6BR7	.95	6Q7(M)	.55	20F2	.75	807	.59	EB81	.35	EF98	.30	KT41	.98	PL504/500		UY41	.49	AC157	.22	BCY12	.55	OA200	.10
1A7GT	.55	6BR8	.85	6R7G	.60	20L1	.88	5702	.80	EBP80	.39	EF183	.29	KT44	.75			UY85	.38	AC165	.28	BCY33	.22	OA202	.11
1B3GT	.62	6BS7	1.40	6R7M	.75	20P1	.65	5763	2.00	EBP83	.43	EF184	.32	KT66	2.40	PL508	.97	UY10	1.00	AC166	.28	BCY34	.25	OC22	.42
1H5GT	.65	6BW6	.85	6SA7	.44	20P3	.65	7475	1.00	EBP89	.30	EF190	.45	KT81	2.00	PL509	1.15	U12/14	1.00	AC168	.42	BCY38	.25	OC23	.42
1L4	.14	6BW7	.88	6SC7GT	.83	20P4	.88	AC/PEN	.95	EBL21	1.50	EL32	.50	KTW61	.21	PL502	.95	U19	1.73	AC176	.61	BCY39	.28	OC24	.42
1N5GT	.55	6BZ6	.49	6SH7	.44	20P5	1.38	AC2/PEN		EC86	.59	EL34	.50	KTW62	.21	PL503/2	.50	U25	.65	AC177	.31	BCZ11	.42	OC25	.42
1R5	.38	6CB6A	.40	6SK7GT	.44	25A6G	.38	DD	.28	EC88	.59	EL35	1.00	MHL6	.21	PL509	1.15	U26	.60	AC178	.28	BF158	.32	OC35	.35
1R4	.33	6C4	.28	6SQ7GT	.38	25L6G	.50	AC/PEN	.38	EC92	.45	EL36	1.00	P61	1.00	PL509	1.15	U27	.60	AC179	.22	BF159	.28	OC36	.47
1U4	.65	6C9	1.00	6V8G	.37	25Y6G	.70	AC/TH1	.21	EC93	1.50	EL37	1.00	PC86	.60	PL509	1.15	U28	.60	AC180	.22	BF163	.22	OC44	.11
1U5	.90	6CD6G	.80	6V8GT	.38	25Z4G	.38	AL60	1.00	EC95	.95	EL38	.38	PC88	.60	PL509	1.15	U29	.65	AC181	.22	BF173	.42	OC45	.12
2D21	.49	6CG8A	.75	6X4	.30	25Z5G	.80	ATP4	.40	EC94	.40	EL39	.38	PC89	.60	PL509	1.15	U30	.65	AC182	.22	BF180	.33	OC46	.17
2GK5	.45	6CH6	.60	6X5GT	.38	25Z6G	.70	AZ1	.60	EC98	.28	EL40	.38	PC90	.45	PL509	1.15	U31	.65	AC183	.22	BF183	.42	OC47	.14
3A4	.42	6CL6	.55	7B6	.75	28D7	1.00	AZ31	.60	EC99	.28	EL41	.60	PC91	.45	PL509	1.15	U32	.65	AC184	.22	BF184	.44	OC71	.12
3D6	.19	6CM7	.75	7B7	.50	30A5	.65	AZ41	.65	EC98	.28	EL42	.60	PC92	.45	PL509	1.15	U33	.65	AC185	.22	BF185	.44	OC72	.12
3Q4	.49	6CU5	.70	7R7	.75	30C15	.75	CL33	1.50	EC94	.40	EL43	.60	PC93	.45	PL509	1.15	U34	.65	AC186	.22	BF186	.44	OC73	.12
3Q5GT	.55	6CW4	.70	7R7	1.50	30C17	.90	CV63	.58	EC95	.38	EL44	.60	PC94	.45	PL509	1.15	U35	.65	AC187	.22	BF187	.44	OC74	.12
3S4	.33	6DE7	.75	7Y4	.65	30C18	.73	CY13	1.00	EC96	.35	EL45	.60	PC95	.45	PL509	1.15	U36	.65	AC188	.22	BF188	.44	OC75	.12
4CB6	.55	6DT6A	.75	7Z4	.80	30F5	.85	CY31	.29	EC98	.44	EL46	.60	PC96	.45	PL509	1.15	U37	.65	AC189	.22	BF189	.44	OC76	.12
5CG8	.55	6EW6	.75	9D7	.65	30FL1	.75	DAF91	.30	EC99	.44	EL47	.60	PC97	.45	PL509	1.15	U38	.65	AC190	.22	BF190	.44	OC77	.12
5TA	.80	6E5	1.00	10C2	.65	30FL2	.75	DAF96	.44	EC98	.44	EL48	.60	PC98	.45	PL509	1.15	U39	.65	AC191	.22	BF191	.44	OC78	.12
5U4G	.80	6E1	.70	10DE7	.65	30FL12	1.00	DF91	.30	EC97	.44	EL49	.60	PC99	.45	PL509	1.15	U40	.65	AC192	.22	BF192	.44	OC79	.12
5V4G	.54	6F6G	.50	10F1	.60	30FL13	.55	DF96	.44	EC98	.44	EL50	.60	PC99	.45	PL509	1.15	U41	.65	AC193	.22	BF193	.44	OC80	.12
5Y3GT	.38	6F13	.55	10F9	.65	30FL14	.85	DH63	.50	EC92	.28	EL51	.60	PC99	.45	PL509	1.15	U42	.65	AC194	.22	BF194	.44	OC81	.12
5Z4G	.85	6F14	.75	10F18	.55	30L15	.75	DH76	.45	EC92	.28	EL52	.60	PC99	.45	PL509	1.15	U43	.65	AC195	.22	BF195	.44	OC82	.12
5Z4GT	.85	6F18	.55	10LD11	.70	30L17	.70	DK40	.70	ECF80	.40	EL53	.60	PC99	.45	PL509	1.15	U44	.65	AC196	.22	BF196	.44	OC83	.12
630L2	.80	6P23	.85	10P13	.70	30P4M4		DK92	.70	ECF80	.40	EL54	.60	PC99	.45	PL509	1.15	U45	.65	AC197	.22	BF197	.44	OC84	.12
6A8G	1.25	6P24	.85	10P14	2.00			DK96	.55	ECH21	1.50	EL55	.60	PC99	.45	PL509	1.15	U46	.65	AC198	.22	BF198	.44	OC85	.12
6AC7	.49	6P25	1.00	12A6	1.00	30P12	.80	DL92	.26	ECH35	.65	EL56	.60	PC99	.45	PL509	1.15	U47	.65	AC199	.22	BF199	.44	OC86	.12
6AG5	.27	6P26	.70	12AC6	.65	30P19	.90	DL96	.38	ECH42	.70	EL57	.60	PC99	.45	PL509	1.15	U48	.65	AC200	.22	BF200	.44	OC87	.12
6AH6	.50	6P27	.65	12AD6	.65	30P4	.75	DM70	.44	ECH81	.30	EL58	.60	PC99	.45	PL509	1.15	U49	.65	AC201	.22	BF201	.44	OC88	.12
6AJ5	.75	6GH8A	.65	12AB6	.65	30PL1	.66	DM71	2.00	ECH83	.44	EL59	.60	PC99	.45	PL509	1.15	U50	.65	AC202	.22	BF202	.44	OC89	.12
6AK5	.34	6KG5	.65	12A76	.35	30PL13	.55	DY87/6	.30	ECH84	.44	EL60	.60	PC99	.45	PL509	1.15	U51	.65	AC203	.22	BF203	.44	OC90	.12
6AK6	.80	6GU7	.75	12A76	.45	30PL14	.80	DY902	.33	ECL80	.40	EL61	.60	PC99	.45	PL509	1.15	U52	.65	AC204	.22	BF204	.44	OC91	.12
6AN8A	.55	6H6GT	.18	12AV6	.40	30PL15	.85	E80CC	1.65	ECL82	.34	EL62	.60	PC99	.45	PL509	1.15	U53	.65	AC205	.22	BF205	.44	OC92	.12
6AN8	.49	6J5GT	.32	12BA6	.30	30A3	.65	E80F	1.20	ECL83	.57	EL63	.60	PC99	.45	PL509	1.15	U54	.65	AC206	.22	BF206	.44	OC93	.12
6AQ5	.40	6J8	.25	12BE6	.38	35D5	.65	E83F	1.20	ECL84	.60	EL64	.60	PC99	.45	PL509	1.15	U55	.65	AC207	.22	BF207	.44	OC94	.12
6AR5	.55	6J7G	.30	12BH7	.27	35L6GT	.55	E88CC	.30	ECL85	.60	EL65	.60	PC99	.45	PL509	1.15	U56	.65	AC208	.22	BF208	.44	OC95	.12
6AS7	1.00	6J7(M)	.38	12K7GT	.55	35W4	.33	E92CC	1.00	ECL86	.40	EL66	.60	PC99	.45	PL509	1.15	U57	.65	AC209	.22	BF209	.44	OC96	.12
6AT6	.30	6JUSA	.75	12K7	.95	35Z4GT	.32	E180F	1.00	EF22	1.50	EL67	.60	PC99	.45	PL509	1.15	U58	.65	AC210	.22	BF210	.44	OC97	.12
6AU6	.30	6K7G	.19	12K7GT	.38	35Z5GT	1.00	E182CC	1.00	EF40	.60	EL68	.60	PC99	.45	PL509	1.15	U59	.65	AC211	.22	BF211	.44	OC98	.12
6AV6	.35	6K8G	.35	12Q7GT	.45	50B5	.85	E1148	.58	EF41	.70	EL69	.60	PC99	.45	PL509	1.15	U60	.65	AC212	.22	BF212	.44	OC99	.12
6AW8A	.65	6L1	2.00	12Q7	.50	50C5	.45	E1450	.27	EF42	.55	EL70	.60	PC99	.45	PL509	1.15	U61	.65	AC213	.22	BF213	.44	OC100	.12
6AX4	.55	6L6GT	.58	12S7G	.38	60CD6G	1.25	E1476	1.00	EF73	1.50	EL71	.60	PC99	.45	PL509	1.15	U62	.65	AC214	.22	BF214	.44	OC101	.12
6B8G	.30	6L7	2.00	12SH7	.35	50EH5	.55	E1480	.30	EF80	.28	EL72	.60	PC99	.45	PL509	1.15	U63	.65	AC215	.22	BF215	.44	OC102	.12
6BA6	.28	6L8	.49	12SJ7	.44	50L6GT	.65	E1491	.75	EF83	.60	EL73	.60	PC99	.45	PL509	1.15	U64	.65	AC216	.22	BF216	.44	OC103	.12
6BC8	.60	6L19	2.00	12S7G	.65	85A2	.60	E1492	.50	EF85	.34	EL74	.60	PC99	.45	PL509	1.15	U65	.65	AC217	.22	BF217	.44	OC104	.12

MATCHED TRANSISTOR SETS—
LP15 (AC113, AC154, AC157, AA120) 58p
per pack. 1—OC81D & 2—OC51, 47p,
1—OC44 & 2—OC45, 47p. 1—OC82D &
2—OC82 58p. Set of 3—OC83 72p.

VALVES ALSO REQUIRED FOR CASH. LOOSE OR BOXED, BUT MUST BE NEW. OFFERS MADE BY RETURN.
All goods are unused and subject to the standard 90 day guarantee. Cash or cheque with order only. Despatch charges—Orders below £5, add 10p per order up to three items, each additional item 3p extra. Orders between £5 and £10 add 25p total. Orders over £10 are post free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p order extra. Terms of business free on request.
Business hours Mon-Fri 9-5.30 p.m. Closed 1-2 p.m. and Sats. We do not handle seconds or rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply. No overseas orders accepted.

PLUGS & LEADS

- Plugs**
Pack 107 5 pin Din 22p
Pack 108 3 pin Din 20p
Pack 135 1/2" Jack 27p
Pack 130 1/2" Jack Stereo 50p
Pack 103 Loudspeaker Plug 17p
Pack 100 Phono Plug 7p
Pack 230 3 pin Socket 25p
Pack 236 5 pin Socket 33p
Pack 234 Loudspeaker Socket 33p
- Ready-made Leads**
3 pin to 3 pin Din 70p
3 pin to open end 55p
5 pin to 5 pin Din 90p
5 pin to open end 70p
5 pin to 4 phono plugs £1.00
Speaker lead Din to spade 12ft 40p
Extension lead Din plug to socket 12ft. 70p
All leads approx. 6ft. in length

DIAMOND STYLI

- 8TA; 9TA; 9TACH; GP91; ST4; ST9; EV26; GC8. All at 80p each.
Double Diamond £1.25
Diamond suitable for Orbit NM22; G800; M3D £2.25 each

CARTRIDGES

- Goldring G800 £6.00
Orbit NM22 £4.00
Shure 75/6 £6.00
Sonotone 9TAHC (Dia) £2.00
Sonotone 8TA4 (Dia) £1.50
Ronnette 105 (Dia) £1.25

All prices include VAT and postage

RECORD CARE

- Cecil Watts Dust Bug £1.20
Parastatic Disc Preener 45p
Antistatic Fluid 20p
Dust Bug Spares (Brush & Roller) 15p
- CASSETTE TAPES**
Audio-Magnetic C60
Qty 3 6 10 20
Price £1.00 | £1.90 | £3.20 | £6.30
Cassette Caddy £1.20
Cassette Head Cleaner 35p


ZONALIFORD TAPE

- 5" Standard 600ft 25p
5 1/2" Standard 900ft 50p
7" (Plain boxed) 1200ft 60p
7" (Westminster Boxed) 1800ft £1.25
7" Reel of Leader Tape (Blue or green) 75p

HEADPHONES

YOU AIN'T HEARD NOTHIN' YET !!

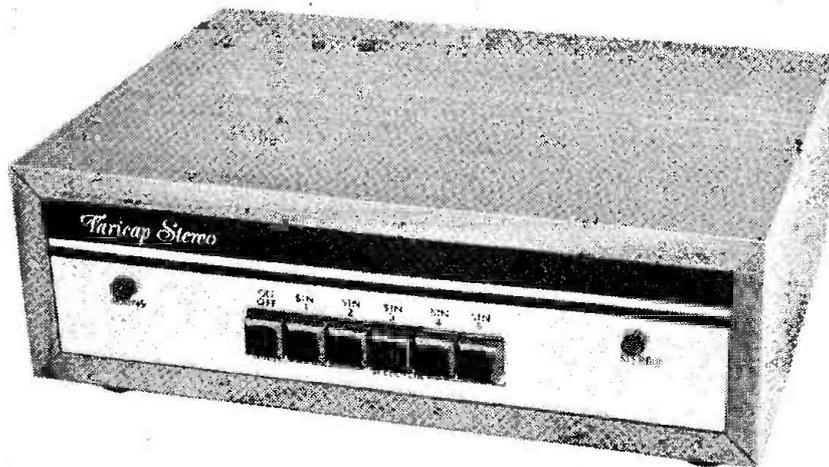.. until you tune in to stereo perfection with 'Varicap'



'p.e.' f.m. varicap stereo tuner. Size approx. $8\frac{3}{4}'' \times 2\frac{3}{4}'' \times 6\frac{1}{2}''$

This elegant and practical stereo tuner features push button 'spot-on' tuning with up to five simple pre-set stations (no difficult tuning dial and drive cord). It's easy 'no problem' construction requires only a few simple setting adjustments with a D.C. Voltmeter. It incorporates NEW pre-set modules for R.F. and I.F. circuits, this eliminates the need for the usually difficult circuit alignment.

All this, coupled with the latest Motorola high efficiency, Integrated Circuit 'phase lock loop' stereo decoder and automatic stereo lamp indicator, ensures perfect stereo reception.

The 'Varicap' is, in our opinion, THE most easily constructed stereo tuner available which will achieve professional results.

The kit comprises Fibre glass P.C. board, elegant slimline teak veneer cabinet, brushed aluminium front panel, push buttons, instructions, in fact everything you need.

We also supply any of these kit components as separate items.

Total kit price ONLY £28.50 (inclusive of VAT and postage).

IDEAL FOR USE WITH THE 'TEXAN', 'GEMINI' OR ANY OTHER GOOD QUALITY STEREO AMPLIFIER.

PARTS FOR PRACTICAL WIRELESS PROJECTS:

After many requests, Electro Spares are supplying lists of components for ALL projects featured in 'Practical Wireless' from July 1973 issue onwards. We regret that we cannot supply lists for projects published before this date.

All you have to do is send us a stamped addressed envelope, not less than 9" x 4", stating which project is of interest to you. We will then forward you an individually priced list of the components required, there is, of course, no necessity to purchase a full kit, you may purchase only the parts you require at any one given time.

We believe this method of 'one source' buying can save you time and postage - **AND THAT MEANS MONEY !!**

ALL COMPONENTS SUPPLIED BY ELECTRO SPARES ARE NEW, BRANDED PRODUCTS OF REPUTABLE MANUFACTURERS AND THEREFORE CARRY THE MAKERS FULL GUARANTEE.

'P.E.' 'GEMINI' STEREO AMPLIFIER.

The 'Gemini' is a quality hi-fi stereo amplifier for the home constructor, featuring a genuine 30 watt R.M.S. per channel output into 8 ohms. Total harmonic distortion of 0.02% and a frequency response (-3dB) 20Hz - 100kHz, at all power levels.

We are continuing to supply components for this fabulous amplifier, which is now recognised as practically THE ultimate in High-Fidelity.

We know no better unit for the home constructor - hundreds have been supplied throughout the world.

Electro Spares have available a booklet containing full specification, complete constructional information, wiring diagrams and fault finding guide etc.

The price is 55p + 4p postage, along with which we will send you our new **LOW PRICE LIST**. Price list available separately on receipt of a large S.A.E.

Our new Mail Order department address is set below. We aim for quick, efficient service - or why not pay us a call, we make all enthusiasts welcome and there are no parking problems.

ELECTRO SPARES

288 Ecclesall Road,
Sheffield S11 8PE.
Tel: (0742) 668888

'THE COMPONENT CENTRE OF THE NORTH'.

Exciting...the Stereo 21!

Can you really get sound quality like this FOR LESS THAN £19? YES, YOU CAN! WITH THE NEW **STEREO 21**

Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable £18.45, you can have Stereo 21—audio for the connoisseur! Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!



And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience! Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins all parts supplied including full instructions—all for £18.45 (plus the cost of post and packing if you buy by mail), and—to round it all off—a money refund if not satisfied if your pleasure in STEREO 21 is not complete!

Personal shoppers and mail order price

£18.45 INCLUDING VAT plus £1.60 p + p.

Diamond styli, if required, £1.37 extra
Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance, if required £3.85.

Just think—in only a few days you could be giving your ears the treat of a lifetime—AND introducing your envious friends to STEREO 21!

Power Output 2.7 Watts per channel and headphone socket with automatic cut out provision for auxiliary inputs—radio, tape, etc. and output for taping discs. Overall Dimension:

Speakers approx. 15½" × 8" × 4". Complete deck and cover enclosed position approx. 15½" × 12" × 6".

EMI SPEAKERS AT UNBELIEVABLE PRICES

950 Kit. Five matched speakers and crossover unit for handling up to 45 watts, from 20 to 20,000 Hz. Huge—19" x 14" (approx.) high efficiency 16, 500-gauss bass unit built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3½" dia. approx., are fed by the crossover with a critically adjusted signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44.00.



15" 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Fluse 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40.80.

OUR PRICE £18.70 + £1.50 p & p



OUR PRICE £25.00 + £1.50 p & p



RADIO AND TV COMPONENTS (ACTON) LTD, 21C HIGH STREET ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2

Edgware: 9 a.m. to 5.30 p.m., half day Thurs.
Acton: 9.30 a.m. to 5 p.m. Closed all day Wed.; also see opposite.
Mail orders to Acton. Terms C.W.O. All enquiries Stamped Addressed Envelope Goods not despatched outside U.K.

RTVC VISCOUNT III

a boost in the output,

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as value for money! And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! And the teak finish will harmonise and enhance virtually any style of interior decor! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back.

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have never experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

SPEAKERS: Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair + £2.20 p. & p. **Duo Type III** Size approx. 23½in x 11½in x 9½in. Drive unit approx 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES: SYSTEM 1

Viscount III R102

amplifier £24.20 + £1 p & p
 2 Duo Type II speakers £14.00 + £2.20 p & p
 Garrard SP25 Mk III
 with MAG. cartridge
 /plinth & cover £18.00 + £1.75 p & p
 total £56.20

Available complete for only **£49.00** + £3.50 p & p

PRICES: SYSTEM 2

Viscount R102

amplifier £24.20 + £1 p & p
 2 Duo Type III speakers £32.00 + £3.30 p & p
 Garrard SP25 Mk III with
 MAG cartridge
 plinth & cover £18.00 + £1.75 p & p
 total £74.20

Available complete for **£65.00** + £4 p & p

STILL ONLY **£49** COMPLETE




THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loud-speaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep. Circuit diagram and comprehensive instructions 55p free with parts. Fully retractable and lockable car aerial £1.37 post paid.

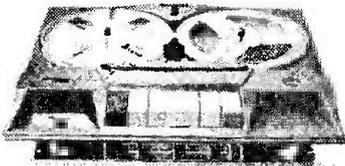CAR RADIO KIT £6.60 p. and p. 55p. Speaker with baffle and fixing strips £1.65, + 23p p. & p. post free if bought with the kit. Send stamped addressed envelope for leaflet. **If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.**



PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tape deck, less heads. Caters up to 5½ins. spools. 240V AC mains. Unused but store soiled hence no warranty. **£4.00**
 £1 p. & p.

RELIANT Mk IV MONO AMPLIFIER

- *5 Electrically Mixed inputs.
- *3 Individual Mixing controls.
- *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid


State Circuitry. *Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Output 20 watts into 8 Ω (suitable for 15 Ω.) Size approx. 12½ x 6 x 3½ ins. **£13.50** p. & p. 60p

UNISOUND MODULES

ONLY £7.64 + 55p. p & p

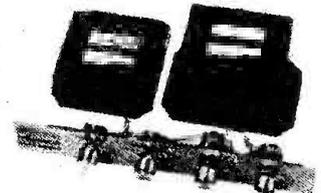For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. The Viscount III, the



fabulous Stereo 21 and the Unisound Modules **£10.60** + 90p. p. & p. will accept this unit, simply connect up.

SEE OPPOSITE PAGE FOR ADDRESS DETAILS

ELECTRONIC MAINS TIMER

A reliable unit ideal for timing Bathroom/Toilet Ventilators, Stairway/Cloakroom Lighting etc. Gives up to 30 mins delay before switching off. Delay: 1-30 mins adjustable. Max Load: 400VA or 1000 watts resistive. Ivory Case: 3 3/4" x 3 3/4" x 2". Fitting instructions included. Trade Price: £5.80. Post 20p.




DIMMER SWITCH

Type C1. 300 Watt Light Dimmer for 200/250 Volt A/C operation. Ivory Case: 3 3/4" x 3 3/4" x 1 1/2". Fitting Instructions included. Price: £2.80. Post 20p. 10 for £2.15 each. £5.00 per pair. Post 25p.



POWER UNIT Type PI076

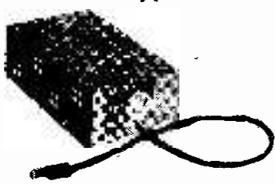

Output switched 3, 4.5, 6, 7.5, 9 and 12 Volts at 500mA D.C. Operates from 240 V. mains, suitable for Radios, Tape Recorders, Record Players, etc. Size 7.5 x 5.0 x 14.0 cm Price £3.95. Post 25p.

TRANSFORMERS

SAFETY ISOLATING

VA (watts)	Ref. No.	Price £	P & P £
60	149	2.86	0.38
100	150	3.15	0.52
200	151	5.30	0.52
250	152	7.05	0.65
350	153	9.40	0.80
500	154	13.55	1.00
1000	156	24.97	1.20
2000	158	41.25	*
3000	159	64.54	*

LOW VOLTAGE

12V	24V	Type No.	Price £	P & P £
0.5	0.25	111	1.00	0.22
1	0.5	213	1.23	0.22
2	1	71	1.60	0.22
4	2	18	2.25	0.38
6	3	70	2.70	0.42
8	4	108	3.00	0.52
10	5	72	3.55	0.52
12	6	116	4.50	0.52
16	8	17	5.50	0.52
20	10	115	6.95	0.69
30	15	187	12.90	0.97
40	20	232	18.30	1.00
60	30	226	23.70	1.10

30 Volts

Prim:- 200-240V. Sec:- 12, 15, 20, 24, 30V.	Amps	Type	Price	P & P
0.5	112		1.20	0.22
1	79		1.64	0.38
2	3		2.45	0.38
3	20		3.00	0.42
4	21		3.55	0.52
5	51		4.40	0.52
6	117		5.25	0.52
8	88		6.80	0.67
10	89		8.36	0.67

50 Volts

Prim:- 200-240V. Sec:- 19, 25, 33, 40, 50V.	Amps	Type	Price	P & P
0.5	102		1.60	0.30
1	103		2.35	0.38
2	104		3.25	0.42
3	105		4.40	0.52
4	106		5.48	0.52
6	107		8.65	0.67
8	118		11.27	0.97
10	119		14.15	0.97

60 Volts

Prim:- 200-240V. Sec:- 24, 30, 40, 48, 60V.	Amps	Type	Price	P & P
0.5	124		1.60	0.38
1	126		2.25	0.38
2	127		3.55	0.42
3	125		5.40	0.52
4	123		6.98	0.67
5	40		8.46	0.67
6	120		9.20	0.82
8	121		11.60	1.00
10	122		15.25	1.00
12	189		16.43	1.10

MINIATURE AND EQUIPMENT

Prim 240V with screen	Volts	Milliamps	Type	Price	P & P
Sec. 1	Sec. 2	Sec. 1	Sec. 2	£	£
3-0-3	—	200	—	1.12	0.10
0-6	0-6	500	500	1.18	0.10
0-6	0-6	1000	1000	1.28	0.22
9-0-9	—	100	—	0.95	0.10
0-9	0-9	330	330	1.28	0.10
0-8-9	0-8-9	500	500	1.70	0.22
0-8-9	0-8-9	1000	1000	2.30	0.30
15-0-15	—	40	—	1.28	0.10
0-15	0-15	200	200	1.28	0.10
20-0-20	—	30	—	1.09	0.10
0-20	0-20	150	150	1.28	0.10
0-15-20	0-15-20	500	500	2.16	0.38
0-20	0-20	300	300	1.38	0.22
20-12-0-12-20	—	700(D/C)	—	1.21	0.30
0-15-20	0-15-20	1000	1000	3.10	0.38
0-15-27	0-15-27	500	500	2.38	0.38
0-15-27	0-15-27	1000	1000	2.40	0.38

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 Volt 25p	50 Volt 35p	100 Volt 55p	50 Volt 65p
100 Volt 25p	100 Volt 40p	200 Volt 59p	100 Volt 70p
200 Volt 28p	200 Volt 45p	400 Volt 65p	200 Volt 80p
600 Volt 30p	400 Volt 50p	600 Volt 75p	400 Volt 80p



PLEASE ADD 10% FOR V.A.T.

ADD 10p P & P PER ORDER

A.S.P. LTD.

BYRE HOUSE · No. 2 UNIT · SIMMONDS RD · WINCHEAP CANTERBURY · KENT · CT1 3RW Canterbury (0227) 52436

4-STATION INTERCOM



£8.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 47p

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £18.95 P. & P. 60p

INTERCOM/BABY ALARM



OUR PRICE ONLY £4.85

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. De-Luxe Model complete with 66ft. connecting wire. Complete with Battery. P. & P. 35p

TRANSISTOR TELEPHONE AMPLIFIER



£4.25

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with Battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.12) 169 KENSINGTON HIGH STREET, LONDON, W.8.

BABANI PRESS

ON SALE NOW!

BP SECOND BOOK OF 14 TRANSISTOR EQUIVALENTS AND SUBSTITUTES

B. Babani

Over 5000 entries and cross references. Follows on from Book No. 1 but does not duplicate it. 224 pages 4 1/2" x 7" 95p

AVAILABLE SHORTLY

An important addition to our technical books

Book INTEGRATED CIRCUITS 202 (I.C.s.) EQUIVALENTS & SUBSTITUTES B. Babani


"A goldmine of valuable information"

LOOK FOR THESE BOOKS AT YOUR LOCAL RADIO & HI-FI SHOPS, MAIL ORDER HOUSES, BOOKSHOPS AND LARGER BRANCHES OF W. H. SMITH IN MAJOR TOWNS

BERNARDS(publishers)LTD

RECHARGEABLE

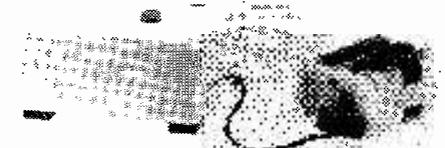Mallory Cells in U2, U11 and Penlite U7 sizes, KESTREL BATTERY CHARGING UNIT . . .



Use for

Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you must have utterly dependable battery power—then these new Alkaline-Manganese rechargeable cells will provide it. The cells can be recharged many times, a simple job with the Kestrel Charging Unit which has been specially designed for these new type batteries.

PRICES Batteries U2 equiv. £1.52 tax paid Penlite U equiv. 61p tax paid U11 equiv. £1.24 tax paid Charging unit £7.70 tax paid with one battery holder

ALL PRICES INCLUDE V.A.T.



Send to: 275 WEST END LANE LONDON, N.W.6 1QS 01-794 9611

HERE'S A NEW YEAR WISH

...that you bring your soldering equipment up to date with Antex!

MODEL CCN
220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64" including Heat Shield.

PRICE £2-48 (rec. retail) P & P 8p

MODEL X25
Soldering Iron
220-240 or 100-120 Volts.

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made



40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed.

PRICE £2-05 (rec. retail) P & P 8p. Suitable for production work and as a general purpose iron.


MODEL C
Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24. PRICE £2-05 (rec. retail) P & P 8p.

MODEL G 18 watt miniature iron, fitted with long-life iron-coated bit 3/32". Voltage 240, 220 or 110. PRICE £2-26 (rec. retail) P & P 8p

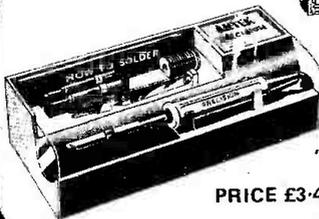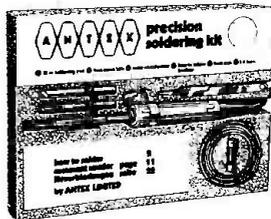MODEL SK. 2 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, stand and "How to Solder" booklet. PRICE £3-25 (rec. retail) P & P 10p




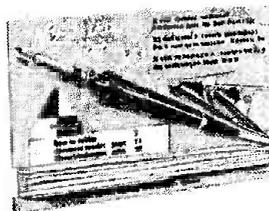MODEL SK.1 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet. PRICE £3-48 (rec. retail) P & P 12p.



MODEL MLX KIT
Battery operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet and with booklet "How to Solder". PRICE £2-54 (rec. retail) P & P 12p.

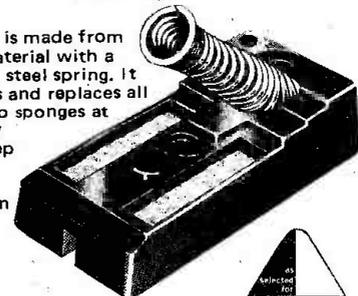ST3 Stand - This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable, serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration. PRICE: £1-00 (rec. retail) P & P 10p



ALL PRICES include VAT at 10%



Please send the following: _____

Please send the ANTEX colour catalogue.

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:
ANTEX LTD. FREEPOST PLYMOUTH PL1 1BR
(no stamp required) Tel 0752 67377.

I enclose cheque/P.O./Cash (Giro No. 258 1000) _____

NAME _____

ADDRESS _____

PW I

NO EXTRAS
ALL PRICES INC. VAT
FREE! P. & P.

AMPLIFIERS

Keletron KSA 700 7+7 watt 23-00
MK II KSA 1500 15+15 watt 32-50
Tripletone MkII Hi-Fi 777 7+7 watt 35-00
MK II Hi-Fi 1818 18+18 watt 35-00
Telefon MkII SAQ 9078+8 watt 27-00
EMI 1515 15+15 watt 37-00
Rotel RA210 32-00
RA310 44-00
Rotel Tuner/Amp. RX150A 51-00
SANSUI models in stock.

RECORD DECKS

Garrard 2025TC/9TAHC/G 11-00
SP25 Mk III 11-00
BSR MP60/SX5H 11-00
Connors BD1 Kit 11-00
BD2 Chassis 29-50
SAU2 Pick-up Arm 12-25
SCU1 Cartridge 4-95

RECORD DECK PACKAGES

Garrard SP25 Mk III/G800 C. & P. 19-50
AP78/G800 C. & P. 30-00
Plinth & Cover for Garrard SP25/2025TC 3-95

SPEAKER BARGAINS

EMI 12" x 8" 3, 8 or 15 ohm
Plain 2-35
with Co-Axial Tweeter 2-50
Twin Tweeter 3-95
Type 350 8 ohm, 20 watt 3-50
6 1/2" 8 ohm, 10 watt 2-65
8" 8 ohm, 10 watt 3-75
12" 8 ohm, 20 watt 5-75
8" x 5" C/Mag. 5 watt 1-40
8" x 5" Dualcone 8 ohm, 10 watt 2-70

FANE 7" x 4" 3 or 8 ohm 1-15
8" Dualcone 8 ohm 2-50
CELESTION 8" 15 ohm 1-75
ADASTRA 10" 8 or 15 ohm, 10 watt 2-95
BAKER GROUP 25
12" 8 or 15 ohm, 25 watt 6-50
5" 8 ohm, 5 watt C/Mag. 95
2 1/2" 8 ohm or 64 ohm 60
SELECTION OF GOODMAN AND WHARFEDALE SPEAKERS ALSO AVAILABLE.
KIT FORM CABINETS--TEAK VENEER
12 x 12 x 6 with 8", 8" x 5", or 6 1/2" and 3 1/2" cutout 2-75
17 x 10 x 9 with 8" or 13" x 8" cutout 3-95
18 x 11 x 9 with 13" x 8" cutout for EMI 350 4-60
TWEETER & CROSSOVER
EMI 3 1/2" 3 or 8 ohm C/Mag. 1-10
Cone Tweeter 8 or 15 ohm, 10 watt 2-00
Cone Tweeter 8 ohm, 3 watt 1-10
Horn Tweeter 8 ohm, 20 watt 3-80
Dome Tweeter 8 ohm, 30 watt 4-00
Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm) 1-10
CARTRIDGES
ACOS GP91/28C or GP91/38C Stereo comp. 1-05
GP93/1 Stereo crys. 1-35
GP94/1 Stereo crys. 1-75
GP95/1 1-85
GP96/1 1-75
GP101 .75
SONOTONE
9TAHC Stereo ceramic, diam. 1-80
9TAHC/G Slim fit, stereo cer. diam. 1-80
19-TI Stereo crystal .85
BSR SC5M Stereo ceramic 2-25
SX5H Stereo crystal 1-65
SX5M Stereo crystal 1-65
X5H Mono/stereo 1-80

X5M Mono/stereo 1-30
GOLDRING G800 3-85
G850 2-95
STYLII For Above Cartridges
Sapphire .30
D. Diamond 1-25
GOLDRING G800 G850 1-95
MICROPHONES
CM20 Crystal Hand .60
CM70 Planetet metal, switch crystal 1-70
DM160 Dynamic uni-dir, ball metal 4-00
UD130 50K/600 ohm, uni-dir, ball metal 4-85
TW206 5-90
CONDENSER MIKE 600 ohm, uni-dir. 7-90
Cassette STICK MIKE with R. Control on/off switch (2-5 & 3-5 mm J/PLY) 1-45
MIKE MIXERS Mono. 4-10
Mono/stereo de luxe 5-50
CASSETTES
Type Low Pin- Phil- Mem- Am- noise nacle lips orex pex
C45 50p 45p
C60 35p 40p 50p 55p 55p
C90 45p 55p 68p 75p 75p
C120 55p 75p 105p 110p 110p
Cassette Head Cleaner .45
BIB Stereo Test Cassette 1-65
AMPEX Head Cleaner De-magnetiser 1-65
PLASTIO LIBRARY CASES for 5" Reels 20p. 5 1/2" Reels 25p. 7" Reels 30p.
CASSETTE CASES 12p
TAPE S. Stnd. L.P. D.P.
5" 55p 65p 80p
5 1/2" 85p 75p 11-00
7" 75p 11-00 11-20
AKAI TAPE DECK
4000DS Tape 73-50
GX40D Cassette 64-95
CS35 + CS53 79-95

BARCLAYCARD
Buy it with Access
Credit Terms for Callers

BUDGET SYSTEMS
BUSH Stereo System with independent Volume, Bass and Treble controls on each Speaker for optimum reproduction. Using GARRARD 2025TC Auto Change Deck in deluxe teak plinth and cover.
Today's Value £49.50.
OUR PRICE £27.50
+£1.50 p. & p.
12 months Guarantee by Maker.
THIS IS A BARGAIN NOT TO BE MISSED!

HEADPHONES

AMSTRAD HPS5A	4-95
ROTEL 430	4-90
630	6-20
700	8-95
AKAI ASE 115	5-75
ASE 20	7-95
ASE 22	9-25
KOSS K711 (Black or Red)	9-95
K6	11-95
K6LC (with Vol. control)	13-25
K0727B	15-75
K0747	19-50
HVI	19-50
PRO4AA	28-95
PRO5LC	28-75
ESP6	42-75

LEESSION ELECTROSTATIC
Mono/stereosuper deluxe 8-16Ω 2-75
Headphone Adaptor . . . 2-50
Curly Ex, Lead 20ft. . . 1-10

IN-CAR ENTERTAINMENT SECTION

Car Cassette Stereo Player and Two Speakers . . .	20-95
Car 8-track Stereo Player and Two Speakers . . .	16-50
SHIBUYA 8-track Player/Mains/Car detachable with 2 separate sets of Speakers . . .	39-95
Pair of Car Stereo Speakers . . .	3-85
Pair of Car Stereo Speakers (Door Mounting) . . .	3-95

NEWMART ELECTRONICS

MAIL ORDER DEPT. (PW/1)
BELMONT STREET
MONTON, ECCLES
MANCHESTER
Tel. 061-789 5268

CALLERS WELCOME AT OUR BRANCHES

Manchester 30-32 Shudehill 061-832 7710	Liverpool 15 Whitechapel 051-236 0738
Leeds 4 New Market St. 0532 42708	Sheffield 20 Finstone St. 0742 79308

ALL MERCHANDISE FULLY GUARANTEED



VHF/FM TUNER for 88-102 MHz. Self-powered for 200-250v. a.c. Valves ECC85, EF89, EF80, ECC82, 2 diodes, metal rect. Chassis 8" x 8" x 5 1/2". £8.75(60p).

Kit and wiring instrs. for 12V windscreen wiper delay control; metal box 3 1/2" x 3 1/2" with fixing strap, relay and all compts. £1.65 p & p 25p.

MAINS TRANSFORMERS, 240-250v. a.c. input.

E. 250v. 50mA. 6-3v. 1A. 55p (27p). V.
J. 37v. 2A; 24-0-24v. 150mA; £2.75 (70p). V
K. 250-0-250v. 150 mA; 20v. 500mA; 15v. 1A; 6-3v. 5A £2.20 (80p). DT
Q. 100v. 100mA; 25v. 250mA; 6-3v. 1A 55p (30p). V.
R. 230v. 60mA; 6-3v. 2 1/2A 70p (30p). V.
T. 100v. 100mA. autotrans. 35p. (30p). V.
W. 230v. 50mA; 22v. 1A; 6-3v. 1A 75p (30p). V.
X. 300-0-300v. 80mA; 6-3v. 2 1/2A; 6-3v. 1A £1.25 (30p). V.
Z. 250v. 25mA tapped at 90v. for 100mA 60p. (30p). V.
AA. 100-0-100v. 100mA 80p (30p) DT., V.
BB. 12-6v. 250mA; 6-3v. 5A 75p (40p). V.
CC. 270v. 50mA; 6-3v. centre tapped, 2A. 75p. (40p). V.
DD. 250-0-250v. 45mA; 6-3v. 3A. 75p (30p). V.
FF. Mains isolation (1 to 1) 200 VA. £4. (80p). V.
GG. 250-0-250v. 150mA; 6-3v. 6A; 5v. 2A. £2.50 (80p). DT.
HH. 6-3v. 1 1/2A 50p. (25p). V.
DT is drop through; V. is vertical mtg.; DT.V. is either.

1,000 resistors 1/2W. & 1/4W £1.20 (30p).
1,000 silvered caps. 2pf to 5,000pf £2. (30p).
1,000 ceramic caps. 1pf to 2,000pf £5. (30p).
1,000 high stab resistors, 10-ohm to 2M (1, 2 & 5%) £5. (40p).
50 transistors, mixed £1 (20p).

Relays. I.T.T. 240v. a.c., 3-pole changeover, 11-pin base & socket, dustproof cover, transparent, 4K-ohm coil £1. (10p) or £18 for 20 post paid.
OMRON relay 50v. a.c., 3-pole c/o, 11-pin base, transparent dustproof cover 2" x 1 1/2" x 1 1/2". 50p (8p) or £9 for 20.

6 watt Mono Mains Amplifier. EZ80, 2-EL84 push-pull, ECC83. Bass, treble, vol-on-off. For record player or tuner, 12" x 3 1/2" x 5" high. £8 Post paid.

GLADSTONE RADIO
66 ELMS ROAD, ALDERSHOT, Hants GU11 1LP
Prices shown include V.A.T. Postage in brackets.

TRAMPUS

MONEY BACK IF NOT SATISFIED
All brand new, full spec. Top grade.
FREE fabulous NEW catalogue. Send S.A.E.



Red + data. 1/8" pin source **LED's 17p!** Til 209 and clip 22p
BIG 1/2" panel clip and RED LED 25p. GREEN and clip 59p.
INFRA RED LED £1. IC photo amp 44p and amp/switch 85p.

DIGITAL DISPLAY. LEO 1/3" 0-9 DP. DIL. £1.69. Minitron type 0-9 DP DIL £1.19, SOCKETS 13p. Calculator batt/mains from £19.

IC DIGITAL CLOCK CHIPS. Texas etc. with 4 displays £12.6 displays and chip £14. Mostek data and alarm chips with 6 displays £19. pcb £1.49.
KIT: All parts and case. National chip. 4 digit £20. 6 x £23.
GAS sensor TGS 308 £2. KIT £4.69. Fully built £8.

With data INTEGRATED CIRCUITS 741: 8 pin 29p, to 99 and 14 pin 27p, 748 33p, 709 21p, 710 35p, 723 59p, 555 timer 79p, 2N414 rx. £1.10. 703 rf if 28p, mc 1310 and led £2.76, mc 1339 £1.20, TAD 100 and if £2

1 AMP + REGULATOR 7805, 5 (6 & 7-20) V. also 12 & 15V £1.49.
AUDIO AMPS: mfc 4000 50p; 1 and 2W £1.19; 3W £1.29.


74N TTL low prices

Gates 7400, etc. 16p, 7413 32p, 7447 £1.25, 7470/72 32p, 7474/76 39p, 7490 63p, 7492 69p, 74121 49p and all others in cat.
NEW 16 pin counter/driver 90/47 £2.25. DALO p.c.b. PEN 69p, DIL SOCKETS: Professional/gold P. Pins hl or lo Profile 8, 14, 16 Pin 13p.
2N3055 33p four £1. BC107, BC108, BC109 all 7p each.
IN914 3p, ZENERS BZY88 8p, 1A RECTS 50V 3 1/2p, 400V 5p, BRIDGE 20p, FETS: 2N3819 19p, 2N3823E 20p, 4416E 25p, BC182/3/4 10p, BC212/3/4 11p, BCY70 13p, BD131/2 35p ea., BFY51/2/3 15p, TIS43 25p, 2N2926 Oy 7p, 2N3053 15p, 2N3702/3/4/5/6/7/8/9/10/11 all 9p ea., 2N3904/6 14p. HEATSINKS 5T/TO5, 18T/TO18 5p. TO3: 4YL 29p. TV3 14p

CAPACITORS: 25V 10, 50, 100 uf 5p, DISCS 4p, PRESETS 5p, CARBON-PTS 11p. Switch + 11p. Dual 55p. ULTRASONIC TRANSDUCERS £2 ea.
FLUORESCENT LIGHTS, 8W 13" 12 VOLT £2.59.

Trampus electronics
ADD 10% VAT TO PRICES.
P. & P. 10p CWO.
P.O. BOX 29, BRACKNELL, BERKS.

NEW EDU-KIT MAJOR

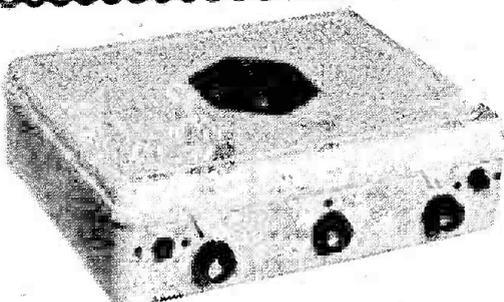


Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ 5 Transistor Push Pull Amplifier.
- ★ Batteryless Crystal Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ One Transistor Radio.
- ★ Signal Injector.
- ★ 5 Transistor Short Wave Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ Transistor Tester NPN-PNP.
- ★ Electronic Metronome.
- ★ 3 Transistor Regenerative Radio.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Noise Generator.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

Total Building Costs
£7-23 P P & Ins. 44p
 (Overseas P & P £1-85)
 (+ 10% VAT 72p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).j

NEW ROAMER NINE

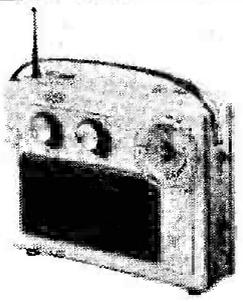


WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans 30p (Free with parts).

Total Building Costs **£6-95** P P & Ins. 44p
 (Overseas P & P £1-85)
 (+ 10% VAT 69p)

NEW Everyday Series

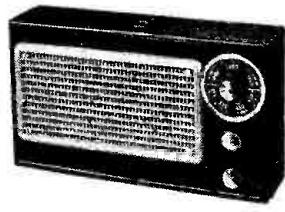

Build this exciting New series of designs

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/4" x 2 1/2" approx. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£2-73** P P & Ins. 30p
 (+ 10% VAT 27p)
 (Overseas P & P £1-25)


E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£3-60** P P & Ins. 30p
 (+ 10% VAT 36p)
 (Overseas P & P £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 20p. Free with parts. Overseas P & P £1-05.

Total Building Costs **£4-08** P P & Ins. 31p
 Overseas P & P £1-85
 (+ 10% VAT 40p)

ROAMER TEN

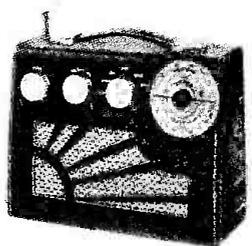


WITH VHF INCLUDING AIRCRAFT

10 Transistors. 9 Tunable Wavebands. MW1, MW2, LW, SW1 SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Latest 4" 2 watt ferrite magnet loudspeaker.

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

Total building costs **£8-50** P P & Ins. 52p
 (Overseas P & P £1-85)
 (+ 10% VAT 85p)

POCKET FIVE

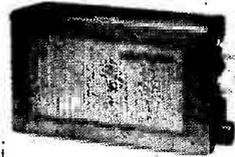

3 Tunable wavebands. M.W. L.W. and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List 15p (Free with parts).

Total Building Costs **£2-28** P P & Ins. 28p
 (+ 10% VAT 22p)
 (Overseas P & P £1-25)

ROAMER EIGHT Mk I



NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive on/off, tuning, wave change and tone controls. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

Total building costs **£6-98** P P & Ins. 47p
 (Overseas P & P £1-85)
 (+ 10% VAT 69p)



"EDU-KIT"


Build Radios, Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include:
 Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine Tone 3" Moving Coil Speaker; Terminal Strip; Ferrite Rod Aerial; 2 Plugs and Sockets; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

Total building costs **£5-50** P P & Ins. 33p
 (Overseas P & P £1-85)
 (+ 10% VAT 55p)

TRANSONA FIVE

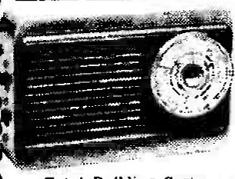


Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts).

Total Building Costs **£2-50** P P & Ins. 26p
 (+ 10% VAT 25p)

TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

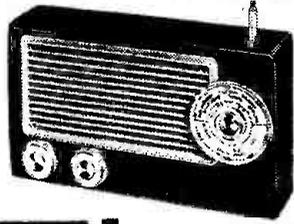Total building costs **£4-48** P P & Ins. 33p
 (+ 10% VAT 44p)
 (Overseas P & P £1-25)



ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2. Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Plans and parts price list 25p (FREE with parts).

Total building costs **£3-98** P P & Ins. 31p
 (Overseas P & P £1-85)
 (+ 10% VAT 39p)

RADIO EXCHANGE LTD

★ Callers side entrance "Lavelis" shop.
 ★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
 Tel.: 0234 52387. Reg. No. 788372.

I enclose £..... for

Name

Address

(Dept. PW24.)

-the lowest prices!

RAND NEW TEXAS EEM. TRANSISTORS

oded and Guaranteed
ak No. EQVT

1	8	2G3713	OC75
2	8	D1374	OC75
3	8	D1216	OC81D
4	8	2G381T	OC81
5	8	2G382T	OC82
6	8	2G344B	OC44
7	8	2G345B	OC45
8	8	2G378	OC78
9	8	2G399A	2N1802
10	8	2G417	AP117

All 55p each pak

**D 120 NIXIE DRIVER
TRANSISTOR.**
suitable replacement for
SX 21, C 407, 2N 1893
20vcb.

1	25	100+
19	0.17	0.16

ll. trans. suitable for
E. Organ. Metal TO-18
Qty. ZTX300 6p each.
ny Qty.

**P 100 TOS METAL
ASE GERMANIUM**
V_{be}=40V. V_{ceo}=50V.
I_c=10 amps. P_{tot}=
9W. h_{fe}=30-170.
replaces the majority of
ermanium power trans-
istors in the OC, AD
nd NKT range.

1	25	100+
48	0.44	0.40

**IP 300 TOS METAL
ASE SILICON**
V_{be}=100V. V_{ceo}=60V.
I_c=15 amps. P_{tot}=
15W. h_{fe}=20. 100T=
MHz. Suitable replace-
ment for 2N 3055,
1DY 11 or BDY 20.

1	25	100+
55	0.53	0.51

NEW 8th EDITION
250 pages
**TRANSISTOR EQUIVA-
LENTS BOOK.** A com-
plete cross reference and
equivalents book for
European, American and
Japanese Transistors.
Exclusive to BI-PAK.
85p each.

**A LARGE RANGE OF
TECHNICAL AND DATA
BOOKS ARE NOW
AVAILABLE EX STOCK.
SEND FOR FREE LIST.**

**UT 48 UNIJUNCTION
TRANSISTORS**
Direct Replacement for
T18 43rand BEN 3000
also electrically equiva-
lent to 2N2646

1	25	100+
0-30	0.28	0.22

**GENERAL PURPOSE
NPN SILICON SWITCH-
ING TRANS. TO-18
SIM. TO 2N706/8. BSY-
27/28/95A. All usable
devices no open or short
circuits. ALSO AVAIL-
ABLE in PNP Sim. to
2N2906, BCY70. When
ordering please state
preference NPN or PNP.**

20	For	0.55
50	For	1.10
100	For	1.92
500	For	8.25
1000	For	14.30

SIL. G.P. DIODES \$p

300mW	80	0.55
40PIV (Min.)	100	1.95
Sub-Min.	500	5.50
Fully Tested 1,000.	9.90	

Ideal for Organ Builders.

**R 2400 TOS NPN
SILICON HIGH
VOLTAGE**
V_{be}=250V. V_{ceo}=
100V. I_c=6 amps.
P_{tot}=30W. h_{fe}=typ.20
f_T=5MHz.

1	25	100+
0.55	0.50	0.44

ADI61/162
M/P COMP GERM
TRANS. OUR LOW-
EST PRICE OF 75p
PER PAIR.

**LOOK FOR OUR
AUDIO &
ELECTRONIC
COMPONENTS
ADVERTISEMENTS**
in PRACTICAL
ELECTRONICS
RADIO CONSTRUCTOR

**SILICON PHOTO TRANS-
ISTOR. TO-18 Lens end
NPN Sim. to BFX25 and
P21. BRAND NEW. Full
data available. Fully
guaranteed.**
Qty. 1-24 25-99 100 up
Price ea. 69p 44p 38p

QUALITY TESTED SEMICONDUCTORS

Pak No.	Price \$p	
Q1 20	Red spot transistors PNP	0.55
Q2 16	White spot R.F. transistors PNP	0.55
Q3 4	OC 77 type transistors	0.55
Q4 6	Matched transistors OC44/45/81/81D	0.55
Q5 4	OC 75 transistors	0.55
Q6 5	OC 72 transistors	0.55
Q7 4	AC 128 transistors PNP high gain	0.55
Q8 4	AC 126 transistors PNP	0.55
Q9 7	OC 81 type transistors	0.55
Q10 7	OC 71 type transistors	0.55
Q11 2	AC 127/128 Complementary pairs PNP/NPN	0.55
Q12 3	AF 116 type transistors	0.55
Q13 3	AF 117 type transistors	0.55
Q14 3	OC 171 H.F. type transistors	0.55
Q15 7	2N2926 Sil. Epoxy transistors mixed colours	0.55
Q16 2	GET880 low noise Germanium transistors	0.55
Q17 5	NPN 2 x ST.141 & 3 x ST.140	0.55
Q18 4	MADT'S 2 x MAT 100 & 2 x MAT 120	0.55
Q19 3	MADT'S 2 x MAT 101 & 1 x MAT 121	0.55
Q20 4	OC 44 Germanium transistors A.F.	0.55
Q21 4	AC 127 NPN Germanium transistors	0.55
Q22 20	NKT transistors A.F. P.E. coded	0.55
Q23 10	OA 202 Silicon diodes sub-min.	0.55
Q24 8	OA 81 diodes	0.55
Q25 15	IN914 Silicon diodes 75 PIV 75mA	0.55
Q26 8	OA95 Germanium diodes sub-min IN69	0.55
Q27 2	10A PIV Silicon rectifiers IS425R	0.55
Q28 2	Silicon power rectifiers BYZ 13	0.55
Q29 4	Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.55
Q30 7	Silicon switch transistors 2N706 NPN	0.55
Q31 6	Silicon switch transistors 2N708 NPN	0.55
Q32 3	PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0.55
Q33 3	Silicon NPN transistors 2N1711	0.55
Q34 7	Silicon NPN transistors 2N2369, 600MHz (code P397)	0.55
Q35 3	Silicon PNP TO-5. 2 x 2N2904 & 1 x 2N2905	0.55
Q36 7	2N3646 TO-18 plastic 300 MHz NPN	0.55
Q37 3	2N3053 NPN Silicon transistors	0.55
Q38 7	NPN transistors 4 x 2N3703, 3 x 2N3702	0.55

ELECTRONIC SLIDE-RULE
The MK Slide Rule, designed to simplify Electronic calculations features the following scales:—
Conversion of Frequency and Wavelength.
Calculation of L, C and f of Tuned Circuits.
Reactance and Self Inductance. Area of Circles.
Volume of Cylinders. Resistance of Conductors.
Weight of Conductors. Decibel Calculations.
Angle Functions. Natural Logs and 'e' Functions.
Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp.
A must for every electronic engineer and enthusiast. Size: 22 cm x 4cm. Complete with case and instructions.
Price each: £3.69

**FULL RANGE OF
ZENER DIODES
VOLTAGE RANGE**
2-33V 400mV (DO-7
Case) 12p ea. 1.1W (Top-
Hat) 18p ea. 10W (SO-10
Stud) 38p ea.

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price \$p
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.55
U 2	60 Mixed Germanium Transistors AF/RF	0.55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.55
U 4	40 Germanium Transistors like OC81, AC128	0.55
U 5	60 200mA Sub-Min. Silicon Diodes	0.55
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	0.55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000V	0.55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.55
U10	20 BAY50 charge storage Diodes DO-7 Glass	0.55
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0.55
U13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0.55
U14	150 Mixed-Silicon and Germanium Diodes	0.55
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0.55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.55
U19	25 Silicon NPN Transistors like BC108	0.55
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.55
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0.55
U23	30 MADT's like MHz Series PNP Transistors	0.55
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.55
U25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	0.55
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.55
U27	12 NPN Germanium AF Transistors TO-1 like AC127	0.55
U29	10 1 Amp SCR's TO-5 can. up to 600 PIV CR81/25-600	1.10
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0.55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0.55
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0.55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.55
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.55
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0.55
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.55
U39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0.55
U40	10 Dual Transistors 6 lead TO-5 2N2060	0.55
U41	25 RF Germanium Transistors TO-1, OC45, NKT72	0.55
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AP117	0.55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.55
U44	20 Sil. Trans. Plastic TO-5 BC115/116	0.55
U45	7 3A SCR. TO66 up to 600PIV	1.10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0.04	0.06	0.06	0.08	0.16	0.23	0.66
100	0.04	0.07	0.08	0.15	0.18	0.26	0.83
200	0.06	0.10	0.07	0.16	0.22	0.27	1.10
400	0.07	0.15	0.08	0.22	0.30	0.41	1.38
600	0.08	0.18	0.11	0.26	0.38	0.50	2.05
800	0.11	0.19	0.12	0.28	0.41	0.61	2.20
1000	0.12	0.28	0.16	0.33	0.51	0.70	2.75
1200	—	0.37	—	0.42	0.63	0.83	—

PIV	3A	5A	5A	7A	10A	16A	30A
50	0.28	0.39	0.39	0.52	0.55	0.59	1.27
100	0.28	0.37	0.52	0.52	0.64	0.70	1.54
200	0.39	0.41	0.54	0.54	0.63	0.67	1.76
400	0.48	0.52	0.62	0.62	0.74	0.83	1.93
600	0.59	0.63	0.75	0.75	0.85	1.07	1.38
800	0.70	0.77	0.88	0.88	0.99	1.32	1.65 4.40

DIACS TRIACS

FOR USE WITH TRIACS.	VBOM 2A	6A	10A	TO-5 TO-66 TO-48
BR100 (D32) 41p each	\$p	\$p	\$p	\$p
	100	33	55	83
	200	55	66	99
	400	77	83	1.21

**10 amp POTTED
BRIDGE RECTIFIER**
on heat sink.
100PIV. 99p each

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department.

BI-PAK

P.O. BOX 6, WARE - HERTS
Postage and packing add 11p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.
Guaranteed Satisfaction or Money Back

INTEGRATED CIRCUIT PAKS

manufacturers 'Fall Outs' which include Functional and Part-Functional Units. These are classed as 'out-of-spec' from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
JIC00	=12 x 7400	0.55	UIC46	=5 x 7446	0.55	UIC90	=5 x 7490	0.55
JIC01	=12 x 7401	0.55	UIC48	=5 x 7448	0.55	UIC91	=5 x 7491	0.55
JIC02	=12 x 7402	0.55	UIC50	=12 x 7450	0.55	UIC92	=5 x 7492	0.55
JIC03	=12 x 7403	0.55	UIC51	=12 x 7451	0.55	UIC93	=5 x 7493	0.55
JIC04	=12 x 7404	0.55	UIC53	=12 x 7453	0.55	UIC94	=5 x 7494	0.55
JIC05	=12 x 7405	0.55	UIC54	=12 x 7454	0.55	UIC95	=5 x 7495	0.55
JIC06	=8 x 7406	0.55	UIC60	=12 x 7460	0.55	UIC96	=5 x 7496	0.55
JIC07	=8 x 7407	0.55	UIC70	=8 x 7470	0.55	UIC100	=5 x 74100	0.55
JIC10	=12 x 7410	0.55	UIC72	=8 x 7472	0.55	UIC121	=5 x 74121	0.55
JIC20	=12 x 7420	0.55	UIC73	=8 x 7473	0.55	UIC141	=5 x 74141	0.55
JIC30	=12 x 7430	0.55	UIC74	=8 x 7474	0.55	UIC151	=5 x 74151	0.55
JIC40	=12 x 7440	0.55	UIC76	=8 x 7476	0.55	UIC154	=5 x 74154	0.55
JIC41	=5 x 7441	0.55	UIC80	=5 x 7480	0.55	UIC193	=5 x 74193	0.55
JIC43	=5 x 7443	0.55	UIC81	=5 x 7481	0.55	UIC199	=5 x 74199	0.55
JIC43	=5 x 7443	0.55	UIC82	=5 x 7482	0.55			
JIC44	=5 x 7444	0.55	UIC83	=5 x 7483	0.55			
JIC45	=5 x 7445	0.55	UIC86	=5 x 7486	0.55			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X 1.

2 Amp. BRIDGE RECTS.	D1699 NPN SILICON DUAL TRANSISTOR (Similar to 2N2060)	B1P 19/20 TOS NPN PLASTIC SILICON V _{be} =100V. V _{ceo} =50V. I _c =10 amps. P _{tot} 50W. h _{fe} =typ. 100 f _T =3MHz.
50 v RMS 35p each	1 25 100+	1 25 100+
100 v RMS 40p "	0.28 0.26 0.23	0.38 0.35 0.32
400 v RMS 50p "		0.66 0.61 0.55
Size 16 mm x 16 mm.		

NEW LOW PRICED TESTED S.C.R.'s

PIV	3A	5A	5A	7A	10A	16A	30A
50	0.28	0.39	0.39	0.52	0.55	0.59	1.27
100	0.28	0.37	0.52	0.52	0.64	0.70	1.54
200	0.39	0.41	0.54	0.54	0.63	0.67	1.76
400	0.48	0.52	0.62	0.62	0.74	0.83	1.93
600	0.59	0.63	0.75	0.75	0.85	1.07	1.38
800	0.70	0.77	0.88	0.88	0.99	1.32	1.65 4.40

POST OFFICE TELEPHONE DIALS 60p each.

2N3819	81p	2N5458	35p
2N3820	55p	2N5459	44p
2N3821	30p	BFW10	66p
2N3823	31p	MPF105	41p

CADMIUM CELLS
ORP12 48p

2N3055
115 WATT SIL
POWER NPN
55p EACH

B1P 19/20 TOS NPN PLASTIC SILICON
V_{be}=100V. V_{ceo}=50V. I_c=10 amps. P_{tot} 50W. h_{fe}=typ. 100 f_T=3MHz.
B1P 19/20 Matched Pair

1	25	100+	1	25	100
0.38					

CONDITIONED?

HAVE you ever been aware of being "conditioned"? We are subject to influences at sometime during our lives because we are human; because we are also British we seem often to fall for something just because the pundits say it is good. Only when the word gets around does it become an acceptance of standard.

When the "experts" told us about twenty years ago that the sound emitted from the radiogram was nowhere near authentic reproduction, a cult was developed in an effort to improve sound quality from records and radio. The term coined was high fidelity or "hi-fi". It took a long time to educate the listener in these terms, but eventually the term and its implications were accepted as part of our way of life.

CHANGING FACE

When the first Audio Festival was opened some 17 years ago, the organisers must have been thinking of future developments. Although strictly reserved for many years as the exhibition for better quality sound, it was inevitable that the other influential element, money, should be responsible for its changing face. From conditions and strict terms of reference for sound performance and unified presentation in hotel rooms, we have now seen the change to include anyone who is willing to pay the price for stand space, whether strictly in the accepted high fidelity bracket or just out to sell anything remotely connected with audio.

In the past, the Audio Fair must have been seen as the only alternative to the old Radio Show for showing domestic entertainment electronics, but there were many visitors who chose not to get involved in technical excellence. The cry today is the same, but the scene is changing.

The Audio Fair, once a paradise for studio technicians is now the all-comers show for the non-technical, where accepted sound reproduction standards for the Fair are lower; the electronics are in one package and a selection of tasteless reproduction cabinet work is offered. Throw in some thoughtlessly conceived visual display gimmicks that must cost the earth to construct and we seem to have turned full circle to where the Radio Show finally left off. Peripherals include a BBC disc-jockey show, colour video tape recorders, synthesised artificial sound, kits of components to build electronic gadgets, and a magazine called *Black Music*.

SATURATED MARKET

Where, oh where has all the top hi-fi gone? Some of the top hi-fi names were there, but in an overall impression of the show, they were a smaller proportion. However, it was interesting to note that the established high quality end of the market attracted the best crowds.

Being conditioned to the term hi-fi, therefore, commercial exploitation of it is now saturated, so it is sad that, in some cases, what is passed as hi-fi at very high prices needs careful scrutiny. The inflation disease has attacked much of the market,

particularly where the equipment falls within a "mid-fi" bracket.

NOISES

On another subject, we have seen and heard much about pollution in most of its facets, but one such is a perpetual headache and nuisance that influences all of us. We become accustomed to patterning or break-up on television screens, clicks and plops on sound equipment, and whistles and burbles on radio. Even background noise is hardly noticeable when we are conditioned to a particular quality of sound reproduction.

Only when we hear high fidelity sound with negligible noise, do we notice the difference, but the trouble is that we seem to acquire "new" noises that perhaps one never realised existed: scratches on discs, drop-outs on tape, intermod on f.m., adjacent stations swamping a.m. They are not really new, but we have to learn to tolerate them or do something to eradicate them. Not all forms of interference can be completely eradicated, but we can do much to reduce the effects to a reasonable level.

INTERFERENCE

Some of the most mysterious forms of interference arise from airborne radiation from other equipment. The mains supply can also carry pulses from one end of the street to the other. The transistor is partly responsible for some of the trouble arising in domestic equipment. In some circumstances Amateur transmissions can break through on to high gain transistor equipment, the long loudspeaker leads acting as an aerial. The surprising fact is that the person responsible for effecting a cure is not the amateur transmitter licence holder, but the owner of the domestic equipment. The R.S.G.B. has a Committee to deal with this kind of interference problem, and in cases of unsettled dispute, the Ministry of Posts and Telecommunications will act as mediator, maybe enforcing a temporary period of rest from the transmitter.

An interesting and useful article on the subject, suggesting what can be done, is published in abridged form in this issue; a more detailed version which includes applications to television reception is being published in *Television* magazine (January issue).

M. A. COLWELL—*Editor*.

The February issue will include three star items; two pieces of valuable test equipment and a stop watch. Also a look at some simple experimental techniques with amplifier circuits, and the start of a special new series, helping you to understand and get the best from an oscilloscope. Also don't miss our advanced information revealing the identity of CRATA, and a preview of P.W. Datacards Nos. 7 and 8.

Further details on page 859

Leicester show

THE National Amateur Radio and Electronics Exhibition was held at the Granby Halls, Leicester on the 25th to the 27th October. The main theme was equipment especially for the radio amateur and indeed some of these items were quite sophisticated. Several stands concentrated on electrical components and they were doing a roaring trade.

Talk-in stations on various amateur bands were operating from the hall. GE3RAE was providing talk-in on 80m.

The British Amateur Radio Teleprinter Group (BARTG) were operating several teletype machines. Other groups were demonstrating amateur TV, slow scan and closed circuit TV.

For the 2 metre enthusiast, there was an extremely wide selection of gear, ranging from a six channel portable transceiver with re-chargeable batteries to a more sophisticated transceiver with a phase locked synthesised v.f.o. and digital read-out.

Equipment on show was by Heathkit (who were also showing their new 12in. portable TV) Drake, Yaesu (new FT101B transceiver), Trio, K. W. Electronics, Codar, J. Beam.

WIRELESS TELEGRAPHY ACT

Readers and advertisers are reminded of the requirements laid down by the Wireless Telegraphy Act. It is an offence in the U.K. to install or operate wireless telegraphy apparatus except under the provisions of the Act and, except in the case of broadcast sound-only receivers, a licence must be obtained from the Minister of Posts and Telecommunications.

Included within the provisions of the Act are any apparatus transmitting deliberate signals for any purpose such as "walkie-talkies", radio-controlled models or servos and some types of metal detectors. Apparatus radiating interference signals are subject to controls which also come under the administration of the same Ministry. If you require full information, please write to the *Ministry of Posts and Telecommunications, Waterloo Bridge House, Waterloo Road, London, SE1 8UA.*

P.W. multimeter competition



IN the June 1973 issue of P.W., readers were asked to put eight features of the Sinclair Radionics DMI multimeter in order of appeal to the average P.W. reader.


The four prizewinners were invited to a presentation at the Practical Wireless offices to receive their prizes. Our picture shows (from the left) Mr. J. R. Mann from Knaresborough, Yorkshire, Mr. R. Harris from Bristol and Mr. Bertram from Newcastle-upon-Tyne. The fourth winner was Mr. G. Rider from Southampton who received his prize by post. Each winner receives a Sinclair digital multimeter and a year of Practical Wireless free.

The Editor of Practical Wireless, Morris Colwell, is shown here sharing a joke with the winners after the presentation. The presentation was followed by a special luncheon also attended by Mr Roy Smith the Advertisement Manager, Mr. Lionel Howes, Assistant Editor of P.W. and Television, Mr. Roy Muggleton the Publisher and Mr. Kenneth Coad the Assistant Publisher.

The BBC and quadraphonics

THE BBC is often asked about quadraphony. Demonstrations of quadraphony by four discrete channels have usually been impressive but unfortunately, the transmission of four separate signals by radio involves technical processes which either consume bandwidth that is not at present available or result in signal-to-noise ratio problems. A number of 'matrix' systems, which reduce the transmitted information to manageable proportions, show promise but there are several different proposals, each having its own advantages and disadvantages. There is, as yet, no international agreement on their relative

merits. The BBC is actively investigating all the various proposals but at the moment is not ready to make a firm decision. In the United States, the National Quadraphonic System Committee (NQSC) has been set up and the BBC is in close touch with them. It is also actively co-operating with the European Broadcasting Union. Until there is a clear decision on a system to be adopted internationally and assurance that mono and stereo listening will not be affected, the BBC would not wish to imply recognition of any one system and thereby lead its listeners to the purchase of equipment which might later become useless.

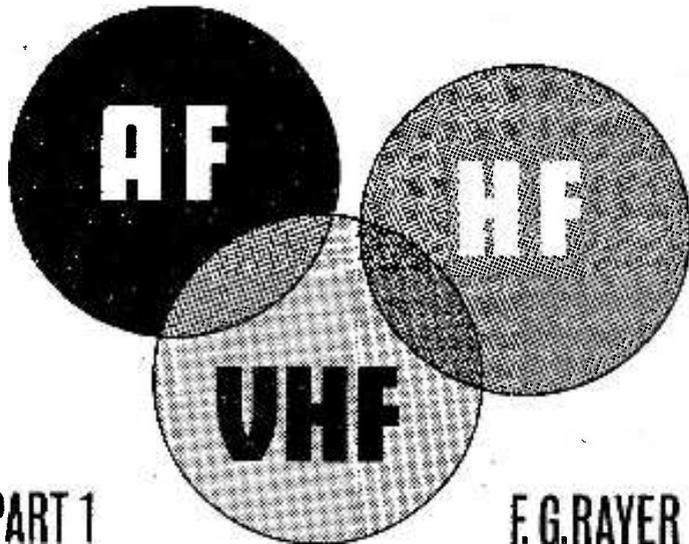

PART 1

F. G. RAYER

TROUBLE-TRACER

THIS is a multi-purpose signal generator which covers VHF in addition to the usual long, medium and short wave bands, providing either a tone modulated or continuous wave output. The audio tone is also available for quick fault finding in audio circuits. For signal tracing, a high gain amplifier is included for audio circuit checks through all stages of audio equipment, together with a plug-in RF probe for tracing the course of a signal through RF and IF circuits.

CIRCUIT

Fig. 1 is a block diagram of the instrument which is constructed as five small units or modules, as follows:—

Tone Generator. This produces an audio tone, which is used to check audio circuits or switched to the HF or VHF oscillator to provide amplitude or frequency modulation of the RF outputs.


VHF Oscillator. This unit provides an RF output over the range 75MHz to 150MHz and has its own calibrated scale.

HF Oscillator. Five switched ranges allow complete coverage of the long, medium and short wave bands, for testing, alignment and similar purposes.

AF Amplifier. The three stage circuit operates a small internal speaker and a test probe allows the presence of an audio signal to be checked stage by stage through a receiver or audio amplifier.

RF Probe. The probe, on a co-axial lead, extends the range of circuit tracing so that the presence of a signal can be checked in RF and IF circuits.

Switching allows CW (unmodulated) or tone modulated RF outputs or AF output to be selected. A potentiometer is fitted as an output attenuator to reduce the output signal level as required. A control of this kind is satisfactory for audio frequencies and the lower frequencies in the RF range but due to stray circuit capacitance and RF leakage its efficiency in reducing output falls off as frequency is increased. However, in practice this simple type of attenuator is useful despite this drawback.

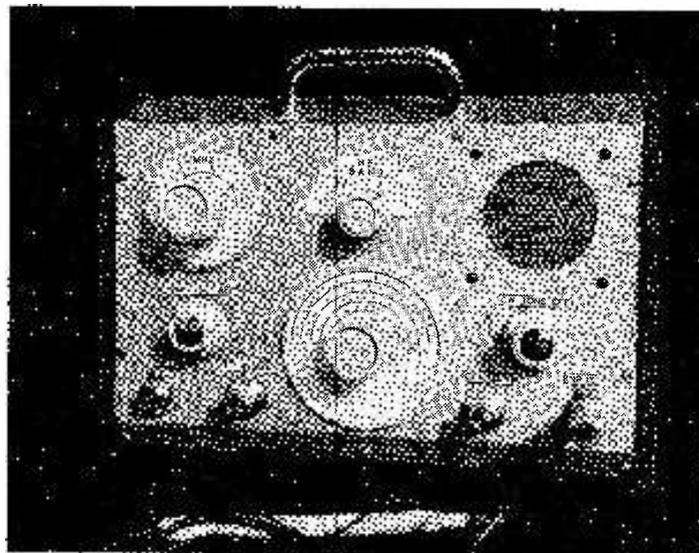

The tracer amplifier has its own switch and gain control, so it may be used by itself or simultaneously with the generator. It can also be used for other incidental purposes for which a small amplifier and speaker are required. The diode RF probe can be plugged into the audio amplifier input socket.

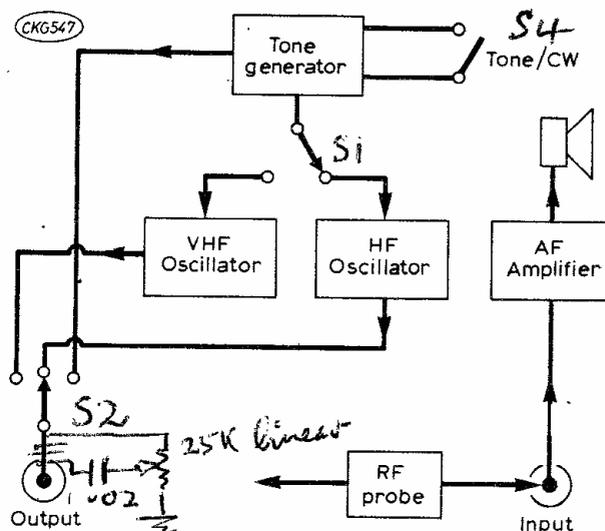


Fig. 1: Block diagram of the Trouble Tracer. Circuit diagrams of the units are given separately rather than as a complete circuit diagram.

Construction is simplified by having separate units. Each unit can be built, and operated by itself, for testing or other purposes. When the units are constructed they are fixed in the case, which allows the function switches, output and input sockets and other wiring between units to be completed.

VHF OSCILLATOR

This unit tunes approximately 75MHz to 150MHz so as to include the VHF FM frequencies from around 88MHz to 108MHz, as well as 144MHz and other frequencies. The VHF oscillator is amplitude modulated at base and collector which introduces frequency modulation when the switch is at

V.H.F. oscillator

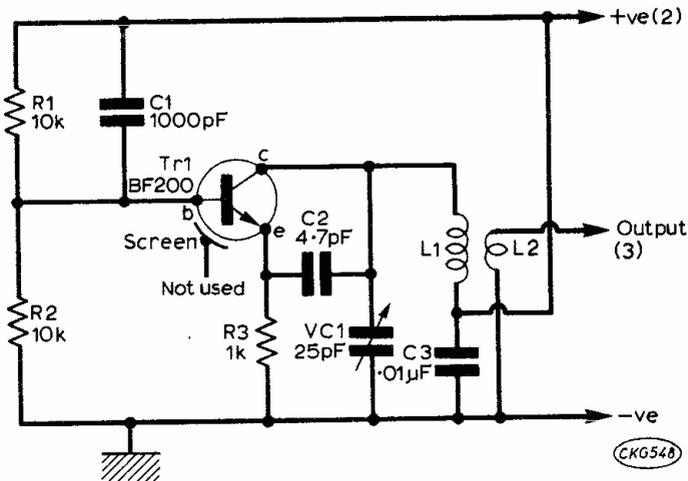



Fig. 2: Circuit of the VHF oscillator which tunes from about 75 to 150MHz.

“Tone.” With this switch at “CW” modulation is removed.

Fig. 2 is the VHF unit circuit. Both L1 and L2 are self-supporting and VC1 is a separate panel control. For a narrower band, such as 88-108MHz or coverage around 144MHz, VC1 may be 5pF instead.

The unit is assembled on a tagboard about $1\frac{1}{2}$ x $1\frac{1}{4}$ in, Fig. 3, cut to leave six tags. Plain perforated Veroboard may be used instead, but the pins must be cut off at the front of the board, to prevent shorts to the metal panel. The board is mounted by the bush and fixing nut of VC1. Washers are put between the board and metal panel, so that the tags are clear of the metal.

Connections in this unit are short and direct. L1 and L2 are wound with 20SWG tinned copper wire to $\frac{3}{8}$ in outside diameter. For L1, wind $4\frac{3}{4}$ turns on a pencil or similar object, spacing the turns so that the coil is $\frac{7}{8}$ in long. L1 lies over the tags, near VC1. One end of L1 is 1in long and goes down directly to tag 2 at Y. The other end is $\frac{1}{2}$ in long and is soldered to X of VC1, from which a lead runs to tag 6.

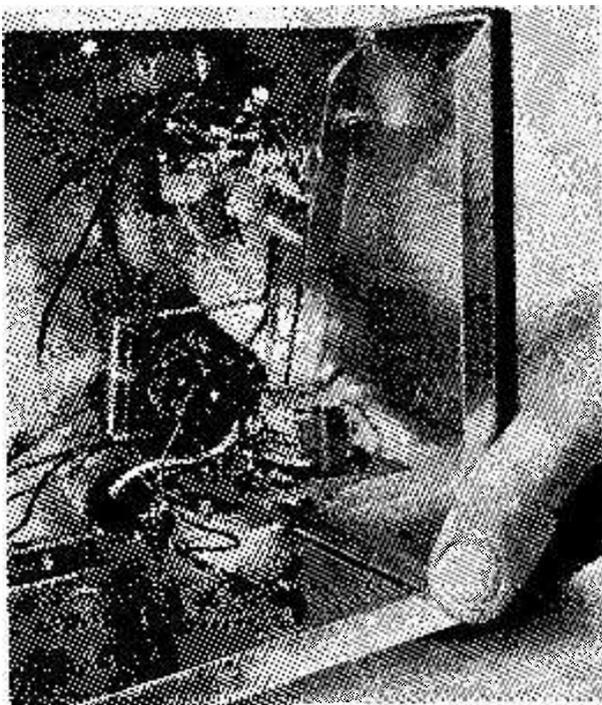

This photograph shows the VHF oscillator at the top with the tone generator below, mounted on the panel by the frequency selector switch.

L1 is one turn, with ends shaped to reach tags 1 and 3, as shown. A space of about $\frac{1}{4}$ in is left between the coils.

A lead from tag 1 runs to the metal panel. Tag 2 is wired to switch S1 so that a positive voltage is supplied when the switch is in the VHF position. Tag 3 is connected to this switch so that output from L2 goes to the potentiometer and output socket. Other tags support resistors etc. as shown.

Operation of the VHF oscillator can be checked by listening for the signal on a VHF receiver, with the switch at “Tone.” Battery current for this section should be around 3mA to 4mA.

If necessary, the frequency tuned can be lowered by compressing L1, or raised by stretching the coil to separate the turns.

This range may be calibrated by means of a sensitive wavemeter, or by means of a VHF receiver,

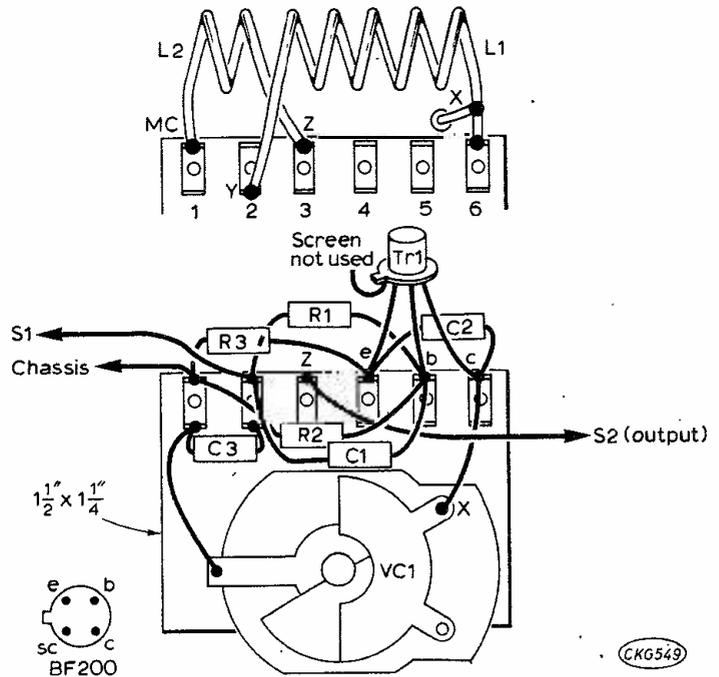


Fig. 3: Constructional details of the VHF oscillator which is mounted directly on to the panel by the nut holding the tuning capacitor.

over the frequencies for which calibration points are available.

The dial is a disc of perspex 2in in diameter, which is most easily cut out with an adjustable tank or washer cutter. The disc is secured to the control knob with two 6BA bolts though self-tapping screws could be used instead. Alternatively, the disc could be held with adhesive.

A black line on the disc travels over a card scale, held to the panel with adhesive. The main purpose of the disc is to avoid finger marks on the scale.

TONE GENERATOR

This unit is a single transistor audio oscillator using the circuit in Fig. 4. The phase of the collector winding 1-2 and the base winding 5-6 is arranged to sustain oscillation, the values used giving an audio tone of about 400Hz.

The third winding on the transformer, tags 3-4, provides a 9V supply for the HF or VHF oscillator, according to the setting of the switch. This modulates these oscillators. To remove modulation, switch contacts short the collector winding.

TONE GEN² ≈ 400 Hz

★ components list

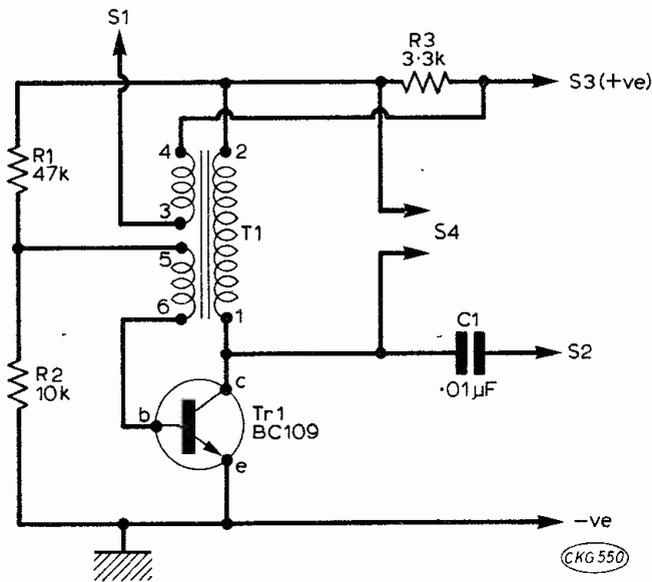


Fig. 4: The simple circuit of the tone generator shown in the previous photograph.

The tone generator is assembled on a small piece of Veroboard, as in Fig. 5. The two MC points are tags secured by 6BA bolts. Later, additional nuts on these bolts allow the board to be mounted on a bracket, which is secured by the switch brush and nut. The points MC are thus common to the metal panel.

Pin connections for T1 are when viewing this from below, as shown. If a different transformer is used, it may be necessary to experiment with connections to obtain oscillation, and some circuit values might have to be changed to obtain a suitable frequency.

Veropins or leads can be provided for external connections. The positive circuit is completed at

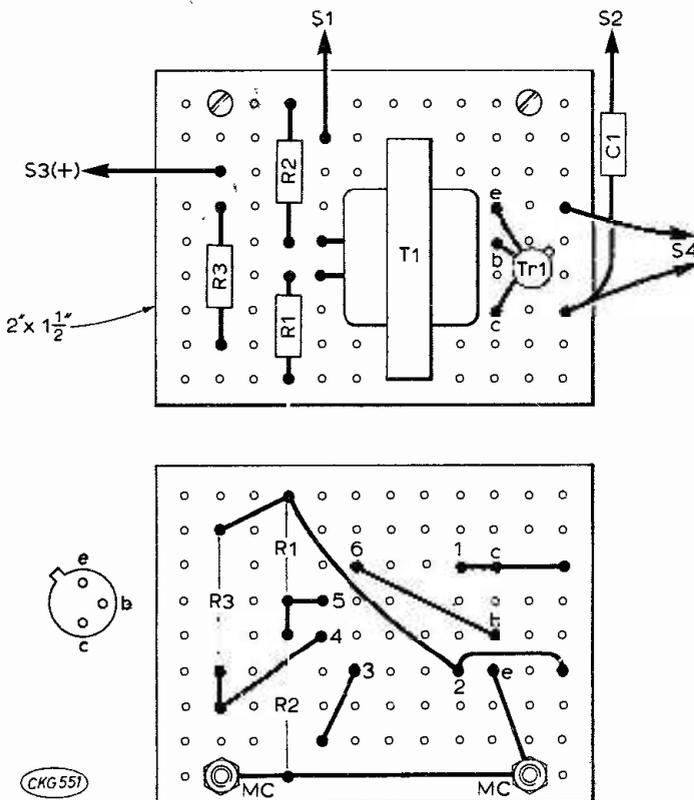


Fig. 5: Board layout of the tone generator components.

VHF Oscillator (Fig. 2)

R1 10kΩ	C1 1000µF
R2 10kΩ	C2 4.7pF
R3 1kΩ	C3 0.01µF
Tr1 BF200	VC1 25pF (Jackson C804)
Tagboard 1½ x 1½in.	Knob for VC1.

Tone Generator (Fig. 4)

R1 47kΩ	C1 0.01µF
R2 10kΩ	Tr1 BC109
R3 3.3kΩ	T1* T173 (RS Components)

* Intended for OC71 into 2 x OC71, 3-6 : 1 + 1
Plain Veroboard, 0.15in. matrix, 2 x 1½in.

HF Oscillator (Fig. 6)

R1 12kΩ	C1 0.01µF
R2 10kΩ	C2 10pF
R3 2.2kΩ	C3 0.01µF
R4 2.7kΩ	C4 0.01µF
Tr1 BF167	VC1 365pF (Jackson 00)

S6, 2 pole 5 way wafer switch. Coils L1 to L5 (Denco 'Blue' miniature valve type coils, Ranges 1 to 5). Paxolin, 6 x 2in. Dial, preferably slow-motion, for VC1.

Audio Amplifier (Fig. 8)

R1 2.2MΩ	R4 220kΩ	R7 47Ω
R2 8.2kΩ	R5 2.7kΩ	R8 2.2Ω
R3 270kΩ	R6 680Ω	R9 2.2Ω
C1 0.02µF 500V	C4 100µF 10V	
C2 0.047µF	C5 320µF 10V	
C3 0.1µF		

VR1/S5 10kΩ log. potentiometer with switch
Tr1 BC109 Tr3 AC127
Tr2 BC149 Tr4 AC128
Plain Veroboard, 0.15in. matrix, 3 x 1½in.

RF Probe (Fig. 12)

R1 56kΩ	C1 22pF 500V
R2 22kΩ	C2 0.01µF

D1 OA70
Felt-pen casing, clip, screened cable and plug.

All resistors ½W 5%


Miscellaneous
Universal Chassis members, 10 x 2in. (1), 10 x 4in. (1), 6 x 4in. (2). Panel 10 x 6in. (see text) (Home Radio). Speaker 2½in. 15Ω and upwards, or similar. Plywood and handle for cabinet. Co-axial sockets (2). VR2, 25kΩ linear potentiometer. S1/2 and S3/4, 2 pole 3 way wafer switches. Knobs. Cx (Fig. 11) 0.02µF 500V.

both "Tone" and "CW" positions of the switch. The circuit from pin 3 of T1 is switched to the VHF or HF oscillator. Leads from 1 and 2 of T1 run to the switch so that T1 primary is shorted when the switch is in the "CW" position.

When the equipment is switched for audio output, the audio tone generator is switched directly to the output potentiometer, so that an audio tone is available at the output socket.

A bracket cut from scrap metal is drilled for the switch bush and the bolts MC. Extra nuts are run on these bolts to give a little clearance for other joints and leads. The tone generator board is locked to the bracket by further nuts.

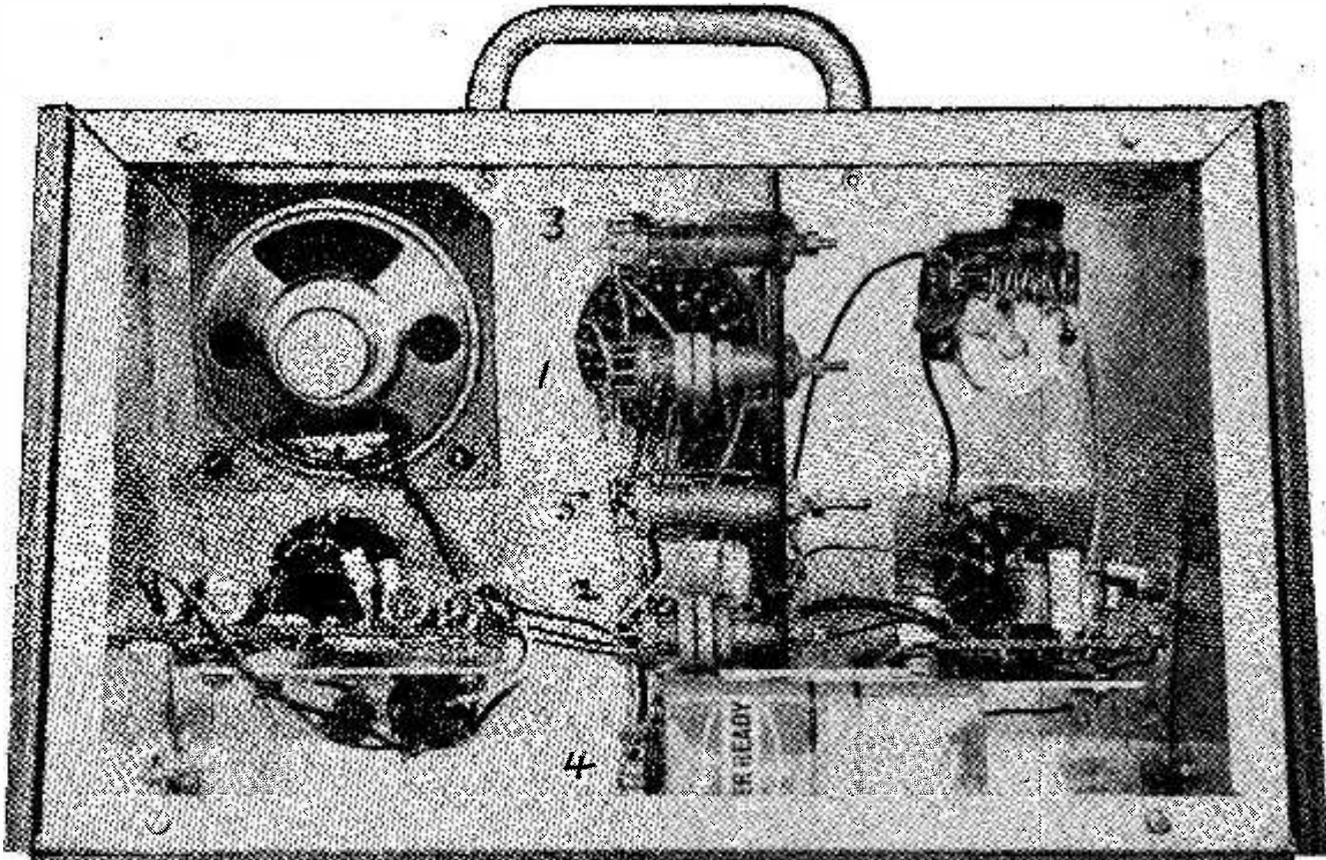Current drain by the tone generator itself is about 1mA to 2mA. It can be tested by noting that the



This look into the cabinet of the Trouble Tracer shows the positioning of the various modules. Bottom left is the audio amplifier board mounted on the tone selection switch. In the centre is the HF oscillator module and, to its right, the VHF oscillator. Bottom right is the tone generator in front of the band selector switch.

audio tone is present on a signal tuned in on a receiver, or by checking the audio output with headphones, or by taking the output to the signal tracer section input.

HF OSCILLATOR

The circuit for this unit is shown in Fig. 6. The transistor is used as a grounded base oscillator, the emitter being switched to tapplings on the inductors, via C3. Section B of the switch is used for this purpose, while section A of the 5-way switch S6 is employed for the collector circuit.

Each of the inductors L1 to L5 is selected in the same way, only the inductor for the required band being in circuit. Each inductor has a large winding and a smaller coupling winding. Pins 6 and 8 are joined, as shown, to form the tapping.

Output is taken from the small capacitor C2. Switch S1 allows the oscillator to be switched on, and to be modulated by the tone generator when wanted.

The layout is shown in Fig. 7. The transistor, resistors and capacitors are first assembled and wired on a piece of Veroboard about 1 x 1 1/2 in. Provide pins or projecting leads for the external connections from this board. The board is fixed with a single 6BA bolt, with extra nuts.

A paxolin board 6 x 2 in carries the coils, and this board is shaped approximately as shown to allow it to be placed in the case more easily. VC1 is secured to the board by a 4BA bolt with a few washers between capacitor and board, to clear the bottom frame tag marked MC in Fig. 7. A metal bracket is cut to hold the rotary switch which is fixed with two short 6BA bolts.

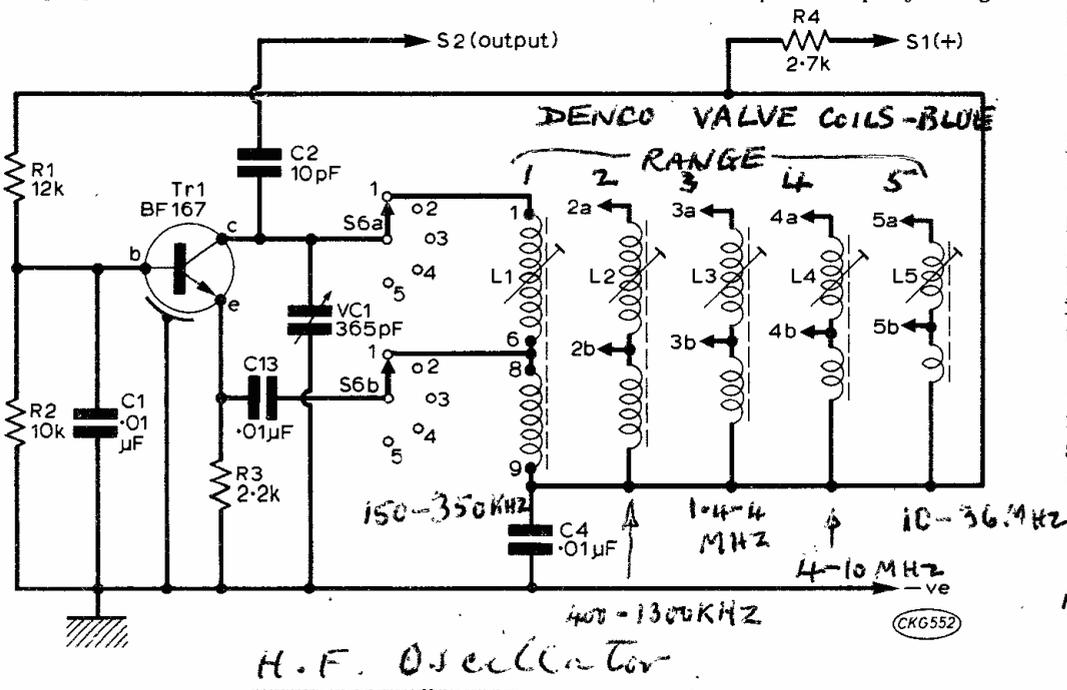


Fig. 6: Circuit details of the HF oscillator which has five switched bands.


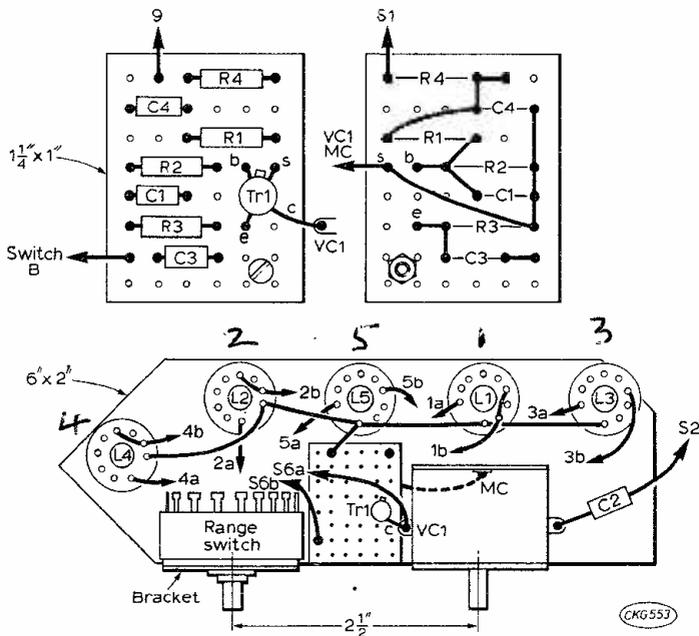
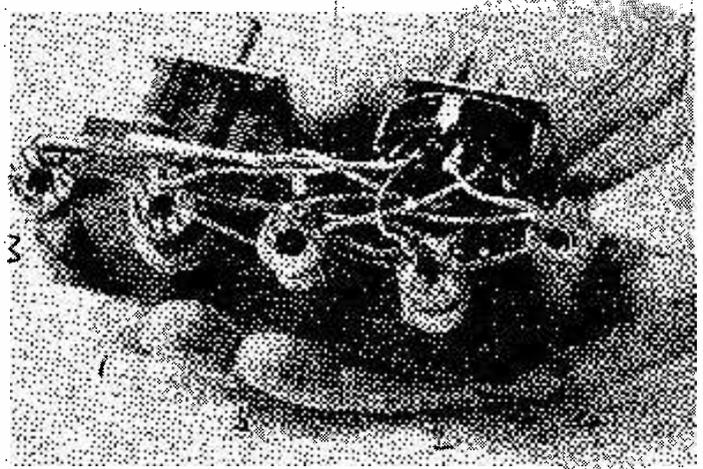


Fig. 7: Circuit board and layout of the HF oscillator. The board is held to the panel by the locknut on the range switch and a screw into the frame of the tuning capacitor.

When wiring is complete, the unit is held to the panel by the fixing nut of the switch and by a short 4BA bolt which passes through the panel into one of the tapped holes in the front of VC1. This bolt must not be so long as to short circuit the capacitor or bend the capacitor plates.

Switch connections to the inductors are straightforward if carried out systematically. If necessary, set the switch in the first position and check with a meter to make sure the correct outer tags are selected. Then connect L1 and check that the unit will oscillate when a battery is temporarily clipped to R4 and the negative line. A whistle or heterodyne should be heard with a receiver tuned to a LW transmission. L2 and the other inductors can then be wired to the switch one by one.

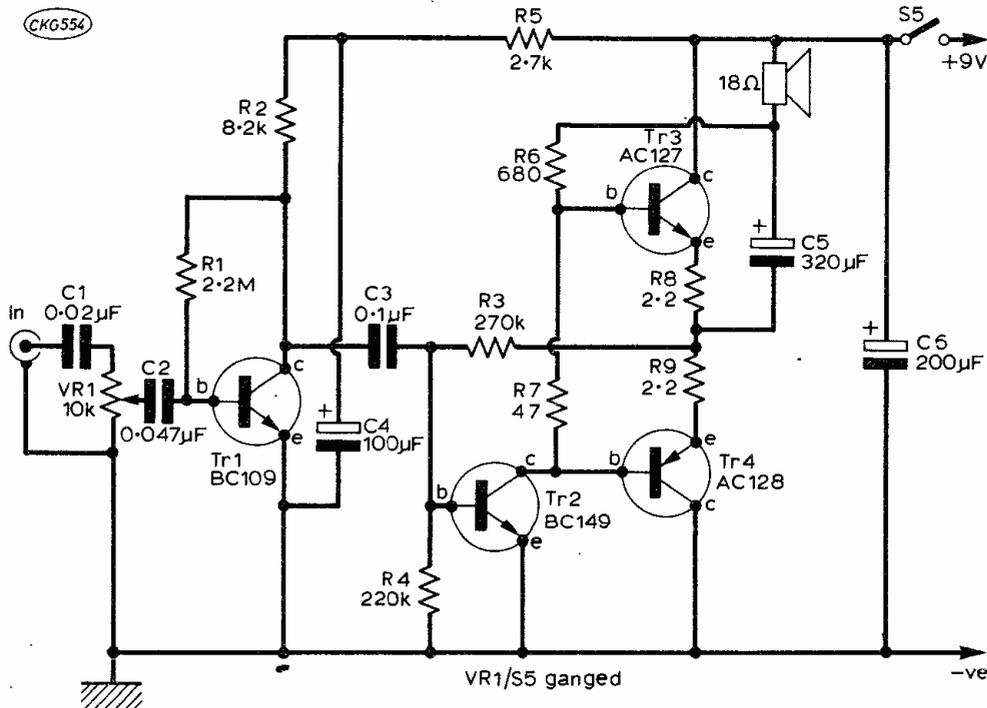

General view of the finished HF oscillator unit.

In order to ensure that the circuit will oscillate, the point 6-8 should be regarded as a virtual tap on a single winding, with no reverse of winding direction all the way from pin 1 to pin 9. If one range fails to oscillate it is worth checking that this is so. With pins wired as in Fig. 6 and Fig. 7 this was correct, but it was observed that connections to pins 1 and 5 on a further similar coil suitable for the L5 position were reversed during manufacture. Should an examination of any coil show that this is so, wiring to the pins 1 and 6, or 8 and 9, should be changed over.

The tuning dial for VC1 was arranged as for the VHF unit, but with a Perspex disc 3in in diameter.

AUDIO AMPLIFIER

This employs four transistors, Fig. 8, and has quite high gain. VR1 is the gain control and S5 is integral with this, so the amplifier can be used alone or in conjunction with the generator units.

Output is fed into a small speaker, handling about 250mW, which is adequate for this purpose. Though an 18Ω speaker is indicated, a 25-35Ω, or even higher impedance unit, will be found satisfactory.

The components are assembled on a 3 x 1 1/2in board, as in Fig. 9. Two 1/2in 6BA bolts are secured at the points MC, each with a tag, and a 24SWG wire is soldered between these. When the amplifier is completed, these bolts allow the amplifier to be mounted on a bracket made from scrap metal, in a similar manner to the tone generator unit. Extra nuts give a little clearance to avoid shorts to the metal bracket, and further nuts are put on so that the negative line, MC in Fig. 9, is returned to the metal panel.

Fig. 8: The four transistor circuit of the audio amplifier.

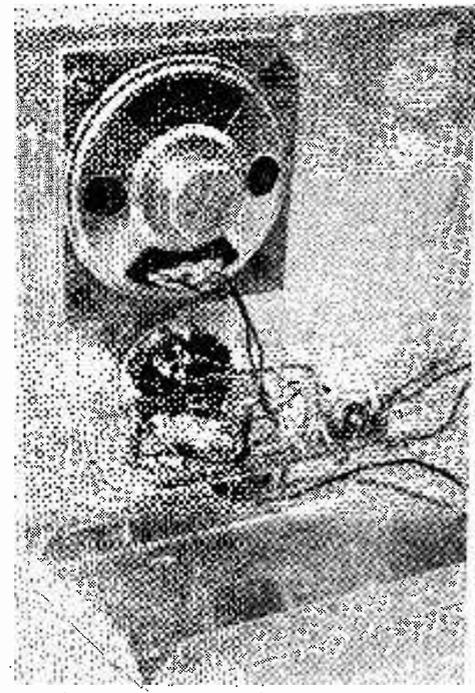
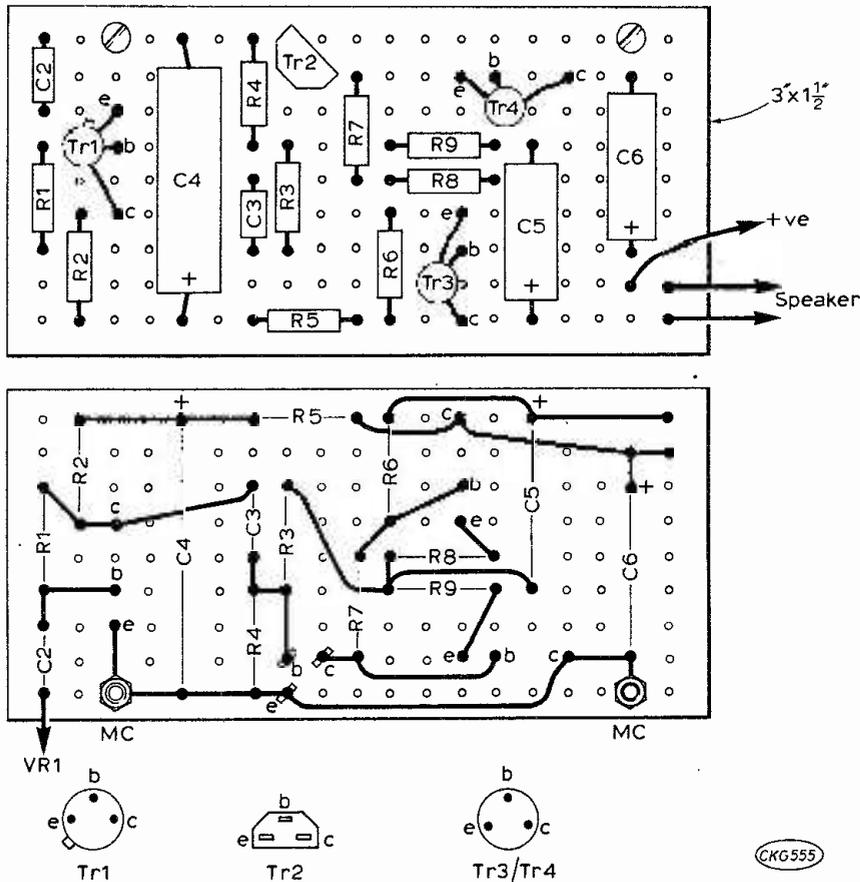


Fig. 9, left: Component layout and wiring information on the audio amplifier board. The board is mounted on a metal bracket as can be seen in the photograph above.

CKG555

Wiring should be straightforward. Sleeving is put on leads which can touch each other or bare joints. Pins or leads are again provided for the external connections to VR1, battery positive (via switch S5) and the speaker.

The amplifier can be tested by applying the signal from a tuner or any other suitable input to VR1. Current drain is about 10mA, rising to peaks of 25mA or more with good volume.

The 3-way switch S3/S4 holds the bracket and amplifier, and the lead from C2 to VR1 runs round this, against the panel.

PANEL AND WIRING

Dimensions for drilling the front panel are shown in Fig. 10. This also shows the positions of the various controls and of the speaker aperture and input and output sockets.

All the units are supported on the panel which allows any checks to be made quite easily, with the units in position.

Wiring behind the panel is shown in Fig. 11. VR1 with its switch S5 and the audio amplifier are quite separate from other circuits, except that all units operate from the same battery.

The switch S3/S4 switches the generator units on, as required, resulting in either tone modulated or CW output, according to the switch position.

The remaining switch S1/S2 selects the appropriate units to give VHF, HF or AF output. VHF and HF outputs will be CW or modulated, according to the position of the other switch. When this switch is set for AF output S3/S4 must be at "Tone" or no AF signal is available. The HF bandswitch is in operation only when S1/S2 is at the HF position.

VR2 provides some control over the output level, especially at lower frequencies, as explained.

CABINET

The cabinet is metal and totally enclosed to help reduce stray radiation from the oscillators. As the sloping front is not essential and requires a little more work, it should be pointed out that similar parts can be used to make a case with a vertical front panel.

For the sloping front cabinet the bottom is a flanged universal chassis member 10 x 4in and the top a flanged member 10 x 2in. Each side is a 6 x 4in flanged member. To form a side, cut away the top flange for 2in and the adjacent front flange for 5 1/2in. The 5 1/2 x 2in flat triangular portion now projecting is gripped in a vice and the member is bent over to form a 90° flange. As this flange will be triangular, it is cut about 3/8in wide to match the other flanges. A matching side is made for the other end of the case. The bottom is then fixed on using the holes which are punched during manufacture. At the top, bolt holes are drilled to fix the 10 x 2in member.

Because of the slope, the panel is 10 x 6 3/8in in size. The bottom 1/2in is bent to match the flanges of the sides. This can be done by gripping the panel between two pieces of wood clamped in a vice. The panel can then be fixed by 6BA bolts run through top, bottom and side flanges. The top will fit better if its front flange is gripped in the vice and turned outwards slightly, to match the slope of the panel. The back is 10 x 8in, secured with self-tapping screws into the flanges.

To avoid the work of shaping the sides for the sloping panel, the 6 x 4in members may be used as obtained. For the top, another 10 x 4in flanged member is required, the 10 x 2in member not being necessary. The parts are simply secured together by passing 4BA bolts through the holes already punched in them. The panel is then a 10 x 6in flat plate, secured with 6BA bolts or self-tapping screws.

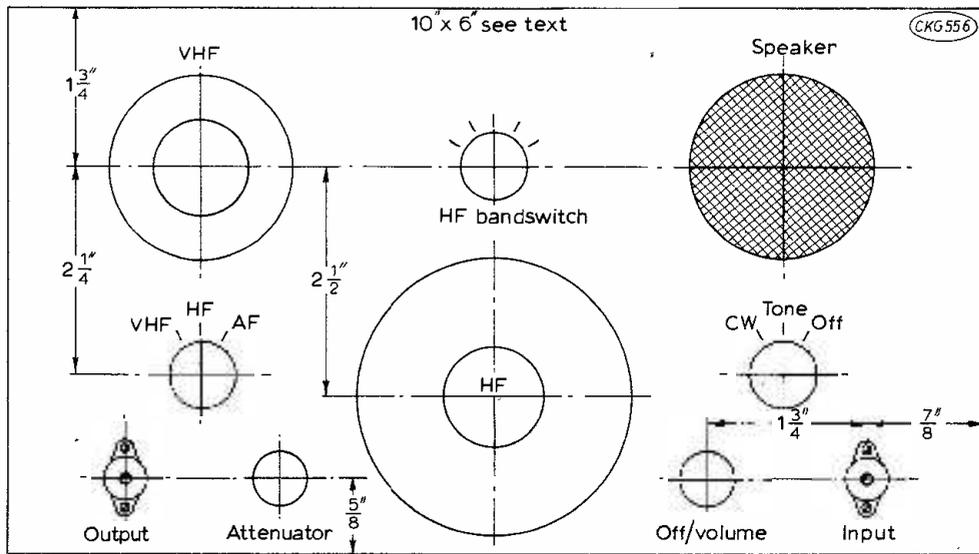


Fig. 10: Suggested layout of units and controls on the front panel. Position of VHF and HF units may depend on types of dial used.

(CKG 557)

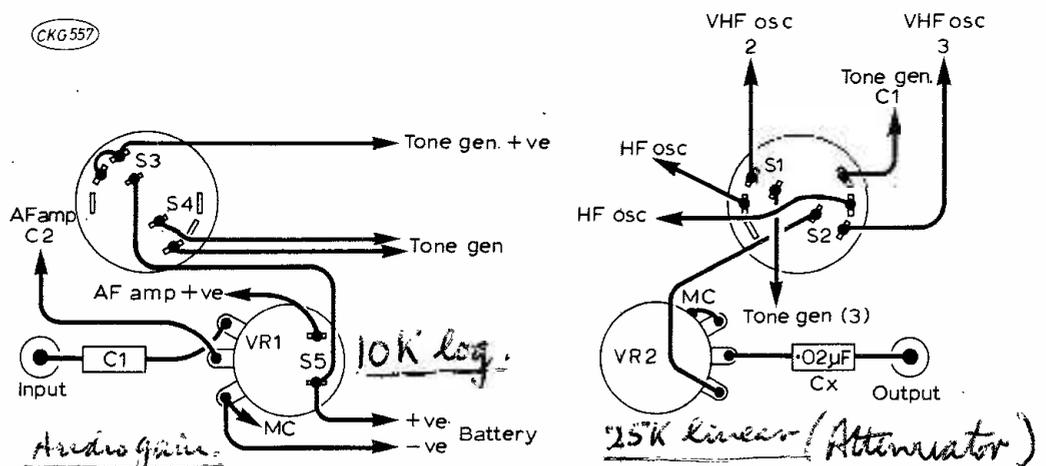


Fig. 11: Inter-unit wiring behind the panel. The wiring to the frequency selector switch from the individual oscillators should be as direct as possible.

To improve appearance, two side members can be cut from plywood, and secured by the same screws which hold the top, bottom and sides together. These wooden sides project about $\frac{1}{4}$ in. The top and panel can be finished with silver paint or in any way required. A stippled finish can be obtained by waiting until the paint is half dry, then dabbing lightly all over the surface with the empty brush.

All the panel holes are drilled or punched to clear the bushes of the switches and potentiometers. A $\frac{1}{2}$ in or $\frac{5}{8}$ in hole is required for the HF tuning capacitor. Check that the central pins of the co-axial sockets are easily clear of the metal.

The speaker is a small unit fixed behind a 2 in diameter hole, which is covered with perforated zinc. There is space to accommodate a slightly larger speaker, if so desired.

A metal bracket bolted to the bottom of the case holds a PP6 (9V) battery here.

The inner conductor of a screened lead is soldered to the junction of D1 with C2 and R2. The outer conductor is soldered to R1, C2 and R2 and a 24SWG or similar wire is also soldered on here.

The assembly is then inserted in the pen casing. The tip piece was filed to fit, using a part of the $\frac{1}{4}$ in insulated shaft cut from one potentiometer. It is cemented in, with the stiff wire passing through a small hole drilled in its centre. A little wire is then wound round the stiff wire near the end piece and soldered. This prevents pressure on the point pushing the wire back in. The wire is then cut to length and pointed.

The 24SWG wire from the co-axial or screened lead outer conductor is threaded through a small hole in the casing and bound a few times round it. It is then soldered, together with a short flexible lead equipped with a clip. The top of the casing is plugged with the original pen top.

RF PROBE


The circuit and construction of the probe is shown in Fig. 12. C1 is to isolate circuits tested, so it should be a 350 or 500V mica capacitor. An OA70 or similar point-contact diode will operate at up to 100MHz but most tests are likely to be in IF circuits or other relatively low frequency circuits.

A felt-tip pen casing was used about 5 in long and $\frac{3}{8}$ in in diameter. The capacitors, diode and resistors will readily fit inside this, if arranged as shown. Solder a stiff wire (16 or 18SWG) to C1. Sleeving is put on leads which may touch other leads or joints.

USING THE PROBE

When the probe point is touched on any circuit where modulated RF is present, demodulation by D1 gives an audio frequency output which is amplified by the tracer amplifier.

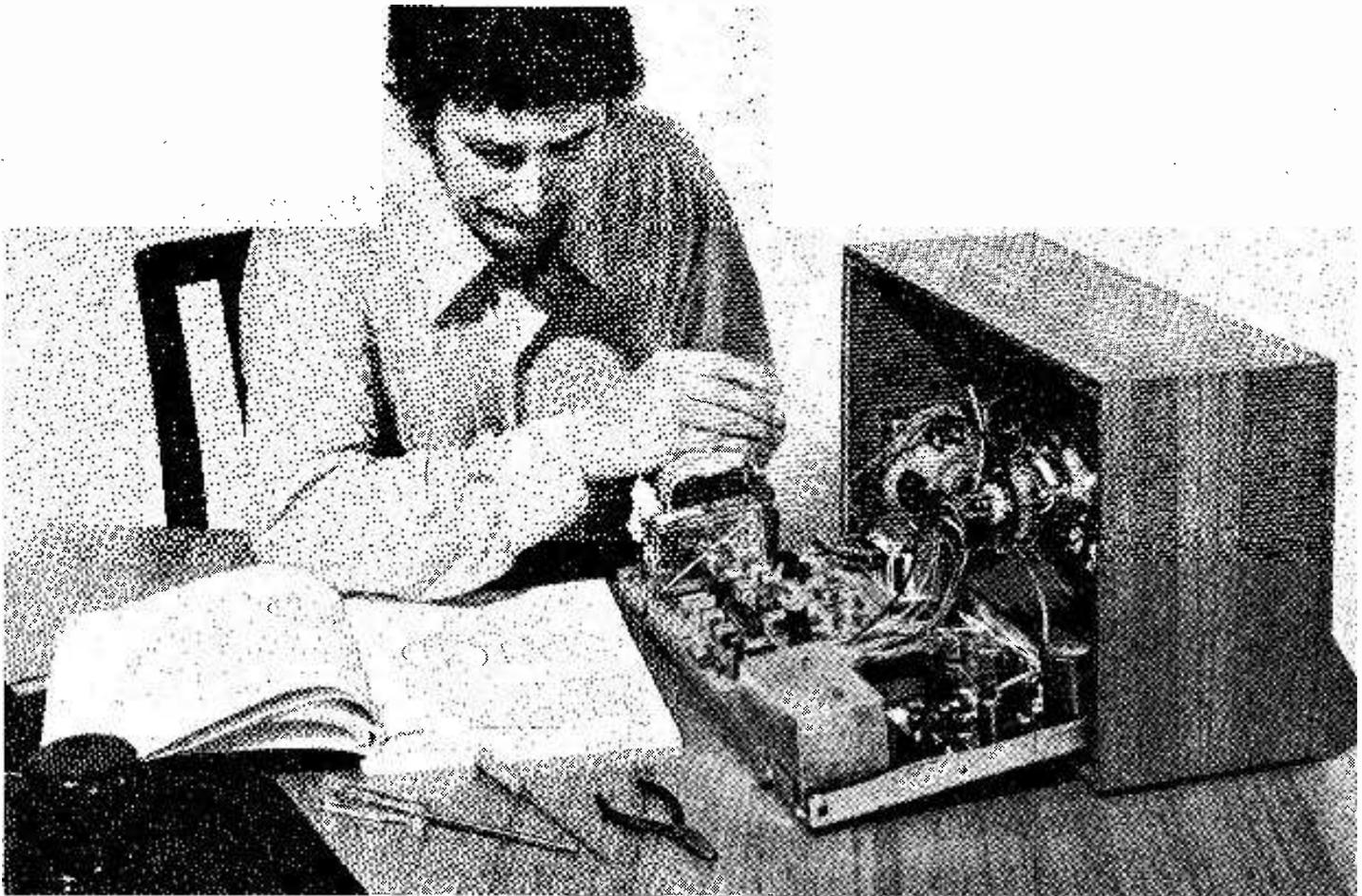One of the most useful applications is the quick testing of IF amplifiers. There is sufficient amplification for the signal to be normally traced onwards by this means from the mixer collector circuit (or frequency changer valve anode). After one or two stages of IF amplification, it may be necessary either to turn back the volume control of the tracer or



LEARN about MODERN TV Design by building this Heathkit 12" B/W Portable

The new Heathkit GR-9900 portable 12" UHF Monochrome Television kit. A unique chance to double the pleasure available from any other television set — because you build this yourself.

We've used the latest modular construction and advanced design concepts to produce an outstandingly high performance TV worthy of the Heathkit name. All the main electronics are mounted on two easy-to-assemble printed circuit boards—this plus the use of no less than four integrated circuits perform the complex function of IF, video, sound, line and frame scan. Factory pre-aligned coils make alignment very easy and there are four presettable pushbutton controls for channel tuning—a luxury found in very few other models. The quality and fidelity is therefore excellent, and of a far higher standard than most ready-built televisions in the shops.

The GR-9900 is portable too—equally at home on

the mains or off your 12 volt battery for car, boat or caravan use. Add to this Heath's world renowned experience in the design of equipment for first-time kit builders, and you will be impressed on all counts of engineering, styling, and performance.


The instruction manual is surprisingly simple with big, clear illustrations to map out your way. Would-be TV engineer? Here's your chance to learn—by actually building a television yourself. The manual not only shows you how to get 100% personalised quality control on your own; in the event of anything going wrong, a Trouble-Shooting section enables you to find the fault—and, in most cases, to put it right unaided.

The GR-9900 is a kit you'll be proud to build and own. You have a choice of fully finished cabinets in teak or modern white and the kit price, £62.70 (carriage extra), includes a FREE high performance indoor aerial.

FREE Heathkit Catalogue

Contains something for everyone: Hi-Fi Stereo, Testers & Instruments, SWL, Metal Detectors... even a Battery charger Kit. Mail the coupon... Today!

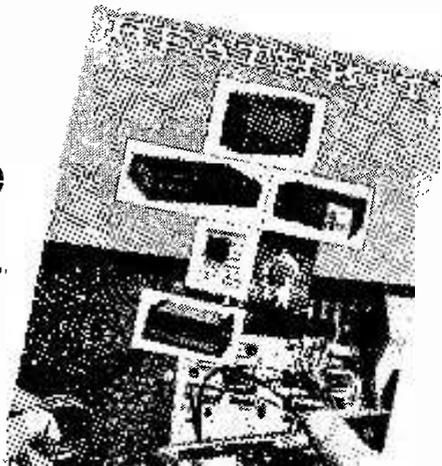Heath (Gloucester) Limited,
Gloucester GL2 6EE.
LONDON showroom
233 Tottenham Court Road
Tel 636 7349



Choose cash or Heath Monthly Budget Plan

(Mail order prices and specifications subject to change without notice)

Please send me a FREE Heathkit catalogue


Name _____

Address _____

HEATH
Schlumberger

Dept PW/01/74
Heath (Gloucester) Limited,
Gloucester GL2 6EE. Telephone 0452 29451

BIG Discounts

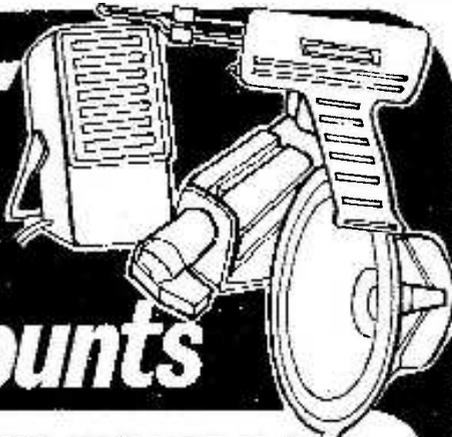

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£			£
EMI 13" x 8" 3, 8 or 15 ohm			ELAC 8" 8ohm Dualcone	..	2.10
Plain	2.05		FANE 7" x 4" 3 or 8 ohm	..	1.00
With Co-Axial Tweeter	2.20		8" Dualcone 8 ohm	..	2.40
Twin Tweeter	3.55		CELESTION 8" 15 ohm	..	1.55
Type 350 8 ohm, 20 watt	8.00		ADAstra 10" 8 or 15 ohm,		
6 1/2" 8 ohm, 10 watt	2.75		10 watt	..	2.75
8" 8 ohm, 10 watt	3.75		BAKER GROUP 25 12" 8 or		
12" 8 ohm, 20 watt	5.50		15 ohm, 25 watt	..	6.45
8" x 5" C/Mag. 5 watt	1.20		P. & P.	..	25
8" x 5" Dualcone	2.45		5" 8 ohm, 5 watt C/Mag.	..	55
GOODMANS 6 1/2" 8 ohm	1.60		2 1/2" 8 ohm or 64 ohm	..	50
Dualcone			P. & P.	..	10
TWEETER & CROSSOVER					
EMI 3 1/2" 3 or 8 ohm C/Mag	1.00		Dome Tweeter 8 ohm, 30 watt	4.00	
Cone Tweeter 8 or 15 ohm,			Crossovers CN23 (3 ohm),		
10 watt	1.90		CN28 (8 ohm), CN216 (16		
Cone Tweeter 8 ohm, 3 watt	1.00		ohm)	..	1.00
Horn Tweeter 8 ohm, 20 watt	3.50		P. & P.	..	10
KIT FORM CABINETS TEAK VENEER					
12 x 12 x 6 with 8" 8" x 5" or	2.45		18 x 11 x 9 with 13" x 8" cutout	..	4.25
6 1/2" and 3 1/2" cut out			for EMI 350	..	35
17 x 10 x 9 with 8" or 13" x 8"	3.50		P. & P. ea.	..	35
cutout					
MICROPHONES					
CM20 Crystal Hand	50		TW206	5.75	
CM70 Planet stick metal,			CONDENSER MIKE 600 ohm,		
switch crystal	1.55		uni-dir	7.90	
DM160 Dynamic uni-dir, ball			Cassette Stick Mike with R.		
metal	3.95		Control on/off switch		
UD130 50K/600 ohm, uni-dir	4.50		(2.5 & 3.5mm J/Ply)	..	1.35
ball metal			P. & P.	..	15
SOLDERING IRONS					
ANTEX CN240 15 watt	1.60		X25 25 watt (low	1.60	
SK 1 Kit (15 watt iron			leakage)	..	10
2 spare Bib etc.)	2.65		P. & P.	..	
CARTRIDGES					
ACOS GP91/2SC or GP91/3SC	1.00		19-Ti Stereo crystal	..	80
Stereo comp.	1.00		BSR SC5M Stereo ceramic	..	2.25
GP93/1 Stereo crys.	1.35		SX5H Stereo crystal	..	1.60
GP94/1 Stereo crys.	1.75		SX5M Stereo crystal	..	1.60
GP95/1 Stereo crys.	1.35		X5H Mono/stereo	..	1.25
GP96/1 Stereo crys.	1.75		X5M Mono/stereo	..	1.25
GP101 Stereo crys.	1.75		GOLDRING G800 G850	£3.95 £2.95	
SONOTONE			STYLII for above cartridges		
BTHAC Stereo cer. diam.	1.80		Sapphire .35 D. Diamond	1.25	
			GOLDRING G800 G850	1.95	
			P. & P.	..	05
BATTERY ELIMINATORS					
240v input 6, 7.5 or 9 300mA	2.20		lighter socket) 6, 7.5 or 9	2.20	
12v d.c. input (fits in car			d.c. output at 300mA	..	10
TAPES					
5" Std. LP DP			7" Std. LP DP		
45p 55p 70p			65p 95p 110p		
5 1/2" 55p 65p 95p			P. & P. 1-3, 9p ea. 4 or more, lot 30p		
LOW NOISE CASSETTES					
C60 1.5 6-10 11-20			Cassette Head Cleaner	35p	
C90 35p 33p 39p			P. & P. 1-5, 3p ea. 6-10, 15p lot		
C120 45p 43p 40p			11-20, Post Free.		
5 1/2" 55p 52p 50p					
PLASTIC LIBRARY CASES					
For 5" Reels	18p		CASSETTE CASES	10p	
5 1/2" Reels	22p		P. & P. 1-3, 5p ea. 4 or more, 20p		
7" Reels	25p				
BIB ACCESSORIES					
Tape Editing Kit Ref. 23	1.30		SPECIAL OFFER BUSH Stereo System with indep. Vol., Bass & Treble controls on each Speaker for optimum repro. Using Garrard 2025TC Auto Change Deck in deluxe teak plinth and cover. Today's Value £49.50. OUR PRICE £27.50 + £1.50 P. & P. 12 months Guarantee by Maker. THIS IS A BARGAIN NOT TO BE MISSED!		
Recording Tape Splicer Ref. 20	1.15				
Cassette Tape, editing Ref. 24	1.40				
Cassette Salvage Kit Ref. 29	40p				
12's Cassette Case Ref. 34	£1.00				
Stylus Balance Ref. 32A	1.15				
Spirit Lever Ref. 46	.50				
Hi-Fi Stereo Test Cassette	1.90				
Groove-Kleen Record Cleaner	1.90				
P. & P.	10				

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED.

Riversdale Electronics

Mail Order Department

P.O. Box 470, Manchester M60 4BU.

ALL PRICES INCLUDE VAT

BARGAIN PARCELS 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 37p p.p.; 56lb at £4.95 plus £1.37 1/2 p.p. Contain pots, Res. Valves, Diodes Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

FANTASTIC BARGAIN. New 6 inch tubes. E450 4/B/16 4VH. medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £1.55 post paid.

NEW HEAVY COAX CABLE dia. 3/8" 70 ohms approx. 50ft. lengths £1.55, p. & p. 32 1/2p. 100 ft. lengths £2.97, p. & p. 55p.

AERIALS. New Condition Whip Type, 4ft. 22p; 11ft. 82 1/2p, all collapsible type. P. & p. 4ft. 10p, 11ft. 15p. New bases on adjustable clamp for the above, 67 1/2p. p. & p. 27 1/2p.

CRYSTALS AS NEW. Hc 6u; 5,030; 4,945; 4,875; 4,840; 4,795; 4,580; 4,660; 4,520; 4,510; 2,295 Kc/s. 55p each plus 8p p.p.

TRANSISTOR BOARDS—consisting of transistors, diodes and resistors etc. Long leads. Good value 12 for £1.00 (min. order) P. & P. 25p. Quotations for quantity.

OUR SELECTION OF 6-Ex. Equ. METERS consisting of 3in., 2 1/2in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 27 1/2p, minimum order of six.

NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 90ft 50p. 100ft. 60p, p. & p. 22p.

AERIAL POLES 4ft high 2" in diameter push-in type as new 75p each p. & p. 25p each minimum four.

AERIAL MAST POLES approx. 5ft high 2" dia. Interlocking ends. Minimum order three. New condition, £1.10 each section. Carriage 37 1/2p each section. 1/2" 75 ohms Coax in 50ft coils with BNC plugs good condition. Price £1.10 + 32 1/2p p.p.

AS NEW 500ua PENNY SIZE METERS complete with jack plug price £1.10 each, p. & p. 10p.

COMMUNICATION RECEIVER PCRS price £10. post paid. PCR No. 2 6 to 22 Mexs.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

HOURS FOR YOU!

With minutes and even seconds if you wish.

Our LSI digital clock chips offer you instant clocks with the following features -

MM5314 Four or six digit display, clock runs in either 12 or 24 hour mode. Use displays A B C or D. **£7.20**

MM5311 Similar to above plus BCD outputs for TTL, Data Loggers, Computers, etc. **£11.50**

MK5017 Four or six digit, Alarm and Snooze, on-chip oscillator for buzzer and power failure back-up. Use displays A B or E. **£14.00**

MM5316 Four digit, Alarm, Snooze & Sleep! Display modes-HHMM, MSS, MMsleep & HHMM alarm. Use displays E or F. **£16.00**

DISPLAYS - 7segment.

A.TIL360 Six .1" LED digits in a 16pin pack. Common cathode. **15.00**

B.DL34 Four .1 LED digits in a 14pin pk. **10.00**

C.DL707 One .3" LED " " " " " anode. **2.00**

D.DL747 One .6" LED " " " " " " **2.65**

E.DG12 One .3" Phosphor-diode digit in glass tube. **2.00**

F.TA8055T Four transmissive .6" liquid crystal digits. **13.00**

KITS -

1.5017+Socket+PCB+four DG12s **£24**

2.5316+ " + " + TA8055 **£32**

Sockets: 24 pin(5314,5017) and 28pin(5311) **115p**
40pin(5316) **135p**

VAT All prices exclude VAT. **P&P 12p. Catalogue 15p.**

BYWOOD

BYWOOD ELECTRONICS
181 Ebbwens Rd, Hemel Hempstead, HP3 9RDA.

Telephone for advice or to order 0442-62757.

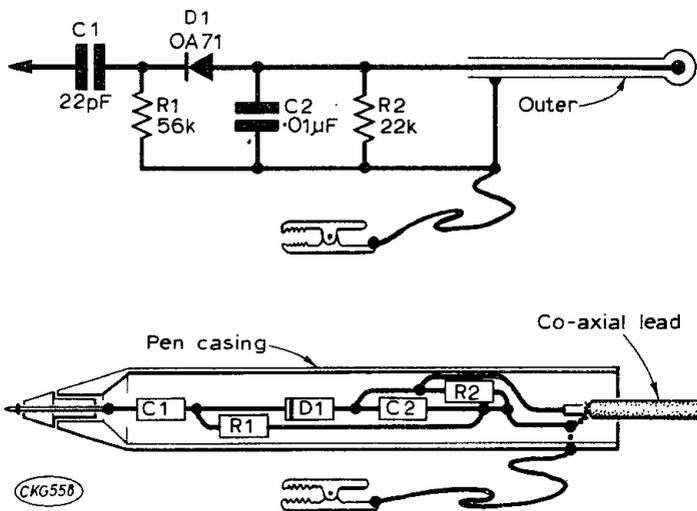


Fig. 12: Details of the construction of the RF probe used with the Trouble Tracer.

merely to put the point of the RF probe against the insulation of a lead in the appropriate part of the receiver circuit.

On no account should any connection or contact be made with a mains receiver which is of AC/DC type, or which derives HT directly from the mains, as the chassis may be alive, and dangerous.

For audio circuit tracing or testing, an insulated probe is required, with a few feet of screened lead. This can be plugged into either panel socket, as required. The probe can be made from the casing of a ball-point pen. The screened lead outer conductor is equipped with a flexible lead and clip so that this can be grounded to the earthed side of equipment under test, when necessary.

HF CALIBRATION

Though frequency calibration is not necessary for testing purposes to locate a fault, or for alignment of circuits for best results, it is convenient to provide some calibration of the five HF ranges. One method is to tune in the signal on a receiver, as explained for the VHF range.

Band coverage is approximately as follows:

- Band 1 150—350kHz
- Band 2 400—1300kHz
- Band 3 1.4—4.0MHz
- Band 4 4—10MHz
- Band 5 10—36MHz

The positions of the adjustable coil cores have considerable influence on the actual band covered by each range.

For more accurate calibration it is necessary to have available some suitable means, such as a calibrated receiver or signal generator, or crystal harmonic marker.

Some calibration marks can be found by harmonics. For example, if a receiver is tuned to 600kHz the generator will be heard when also tuned to this frequency; in addition, the signal is heard at reduced strength when its second harmonic falls on 600kHz, so this gives a calibration point for 300kHz. Similarly, harmonics may be heard when the receiver is tuned to 2x, 3x, 4x and other multiples of any frequency generated, depending upon the receiver sensitivity.

IN NEXT MONTH'S PART 2 PLENTY OF PRACTICAL INFORMATION WILL BE GIVEN TO ENABLE READERS TO MAKE THE MOST OF THE 'TROUBLE TRACER'

TELEVISION

CURING RF INTERFERENCE

Curing r.f. interference can be a tricky business, especially if you are not sure how to go about it. Next month we provide a detailed guide covering not only TV sets but audio equipment as well. Practical filters are described together with notes on audio circuit modifications to try.

RBM S-S COLOUR CHASSIS

A guide to the stock faults experienced with this chassis, also some fault finding procedures to use to track down more elusive troubles.

FET/VARICAP PREAMPLIFIER

A long-distance reception enthusiast provides full data on the f.e.t./varicap aerial preamplifier he built. The cascode circuit adopted can be tuned over the whole of Band 1 by altering the bias on the varicap tuning diodes. Excellent results have been achieved.

BRC 1400 CHASSIS

John Law's next fault finding guide deals with the popular BRC 1400 chassis.

COLOUR RECEIVER FORUM

The main items next month will be a decoder alignment procedure using just a multimeter, and suggestions for improving the performance of the i.f. strip and the line oscillator.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW

TO..... (Name of Newsagent)

Please reserve/deliver the JANUARY issue of TELEVISION (20p), on sale DECEMBER 17, and continue every month until further notice.

NAME

ADDRESS.....

PRODUCTION LINES

colin riches

P.C. KITS

GSPK Electronics Ltd. have launched three kits aimed at the prototype printed circuit enthusiasts.

The first is a P.C. board marking pen, sold in a pack of two for £1.20. The pens provide a quick and easy method of marking on a copper-clad laminate, the special ink acting as an etch resistant to most commercial etchings.

Kit 2 contains the pens, and six pieces of 6 x 4 in. copper laminate, some GSPK etching powder and a plastic dish. This sells at £4.50.

The third kit contains all the tools necessary to cut to size and drill the laminate plus the contents of kit 2. Named the "Professional" kit, this retails at £8.

Further gen from *GSPK Electronics Ltd., Hookstone Park, Harrogate, HG2 7BU, Yorkshire.*

AUDIO FAIR PRODUCTS

On page 869 we include details of some of the new products introduced at this year's Audio Fair.

THE 810

I recently had the opportunity to try out the latest BSR 810 transcription turntable. Although this unit was introduced some time ago, it is still the leader of the BSR range of decks. It employs a pre-programmed sequential cam system and a low

mass transcription tone arm which floats in a concentric gimbal, helping to eliminate tracking error. The arm also has precise zero balance adjustment over the full range of stylus and cartridge masses.


The turntable weighs a massive 6½ lbs. and is driven by a high torque synchronous dynamically balanced 4-pole motor. Other features include a variable pitch control, rotating stub spindle, dual-range anti-skid unit, stylus position gauge and a special "pause" control operated by a special friction clutch mechanism.

The unit tracks, with a high-compliance magnetic cartridge, down to 0.5 gm.

All in all, this is a very nice unit and if you would like further details of this and the other turntables in the BSR range, write to *BSR Limited, Monarch Works, Cradley Heath, Warley, Worcs.*



The latest 810 deck from BSR

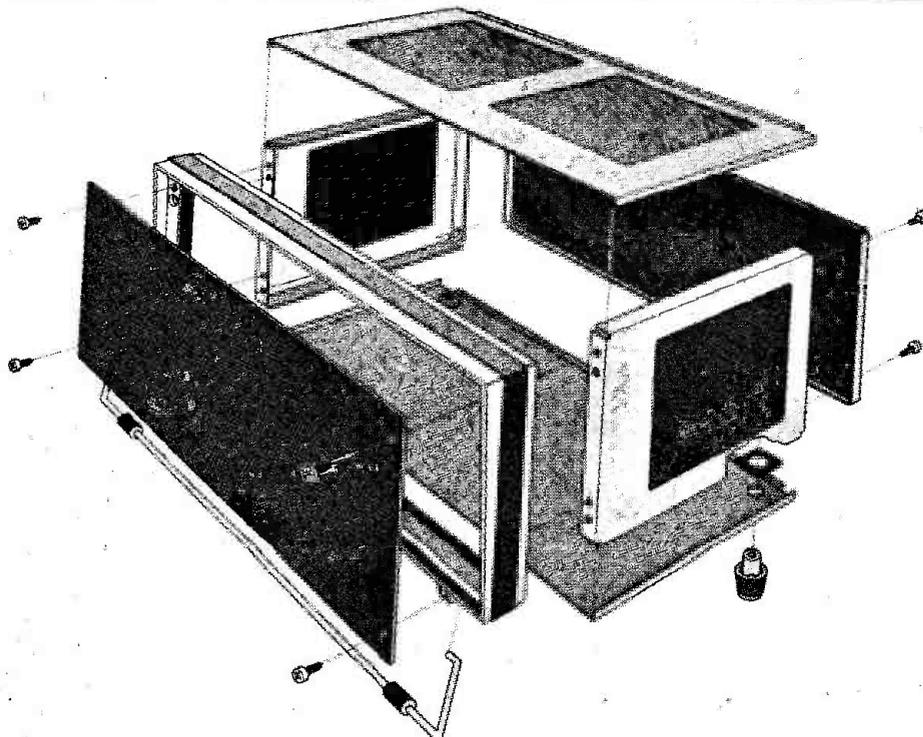

AMTRON CABINETS

Amtron UK Ltd supply a range of metal cabinets suitable for housing equipment. They are made of aluminium and the side and top panels are of an open grid structure to assist ventilation.

The front panel escutcheon is made of high-impact plastic material which gives the unit a very professional finish. Plastic feet are supplied together with a fold-down tilt support bracket at the front. The kits come complete with all metal hardware necessary for assembly. The picture shows an "exploded" view of kit 00/3009-10, the internal dimensions of which are 224 x 138 x 120 millimetres.

For further information and prices of the other cabinet kits available, contact *Amtron UK Limited, The Trading Post, 4 & 7 Castle Street, Hastings, Sussex, TN34 3DY.*

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

5p for 1 Valve.
Each additional Valve add 2p.

DM70	0.63	EF80	0.48	PC86	0.75	PL84	0.68	30C15/	0.05
DY61	0.85	EF83	1.03	PC88	0.75	PL504	0.88	PCF800	1.05
DY86/7	0.42	EF85	0.43	PC97	0.45	PL508	1.08	30C17	1.00
DY802	0.45	EF86	0.90	PC900	0.58	PL509	1.55	30C18/	
EABCS80	1.00	EF89	0.81	PCC84	0.52	PL802	0.66	PCF805	0.90
EB91	0.88	EF91	1.30	PCC88	0.80	PY33	0.66	30F5/PF818	
EBC81	0.75	EF92	1.40	PCC89	0.85	PY81/800	0.50		1.10
EBF80	0.80	EF95	1.35	PCF80	0.51	PY82	0.55	30FL1/	
EBF83	0.82	EF183	0.60	PCF85	0.85	PY88	0.40	PCE800	0.75
EBF89	0.88	EF184	0.60	PCF86	0.85	PY800A	1.05	30FL2	0.75
EC86	0.75	EH90	0.58	PCF200	0.85	PY800	0.50	30FL12	1.05
EC88	0.77	EL34	0.95	PCF201	0.87	PY801	0.50	30FL14	0.85
ECC81	0.45	EL36	1.05	PCF801	0.75	U26	1.00	30L1/PC84	
ECC82	0.48	EL81	0.90	PCF802	0.71	U191	1.00		0.52
ECC83	0.45	EL84	0.47	PCF806	0.88	U193	0.50	30L15/PC805	
ECC84	0.55	EL85	0.55	PCF807	0.88	UABC80	0.90		1.05
ECC85	0.58	EL86	0.95	PCL82	0.54	UBC81	0.70	30L17	0.90
ECC88	0.75	EL95	0.70	PCL83	0.86	UBF89	0.60	30P4MR	1.80
ECC189	0.71	EL91	1.31	PCL84	0.59	UCC85	0.60	30P12/PC801	
ECF80	0.56	ELL80	1.30	PCL85	0.93	UCH81	1.00		1.05
KCF82	0.78	EM84	1.18	PCL86	0.83	UCL82	0.70	30P19/PC802	
KCF86	0.71	EM87	1.18	PCF805/85		UCL83	0.70		1.00
ECH81	1.00	EY81	0.83	PD500	1.55	UF89	0.80	30PL1/PC801	0.95
ECH83	1.00	EY86/87	0.42	PFL200	0.80	UI84	0.95		
ECL84	0.78	EY88	0.64	PL36	0.88	UY85	0.50	30PL13/	
ECL80	0.53	EZ80	0.51	PL81	0.75	6/30L2/		PCL900	1.20
ECL82	0.61	EZ81	0.40	PL81A	0.88	ECC804	1.00	30PL14/	
ECL83	0.68	GY501	0.90	PL82	0.50	6F23/EF812	1.05	PCL88	1.25
ECL86	0.68	GZ34	0.78	PL83	0.96	30C1/PCF80	0.51	30PL15	1.05

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	0.60	EF80	0.25	PC86	0.60	SP41	3.00	6J6	0.30
AZ31	0.55	ER85	0.35	PC88	0.60	SP61	0.75	6J7M	0.45
CB131	1.00	ER86	0.30	PC97	0.45	T41	1.00	6J7G	0.40
CL33	1.50	ER89	0.28	PC900	0.48	U14	1.00	6K6GT	0.75
CY31	0.50	EF91	0.37	PCC84	0.40	U25	0.85	6K7M	0.43
DAF91	0.30	EF92	0.35	PCC88	0.55	U26	0.85	6K7G	0.40
DAC90	0.50	EF95	0.40	PCC89	0.50	U191	0.75	6K8M	0.60
DCC90	1.35	EF98	0.75	PCC189	0.80	UABC80	0.40	6K8G	0.45
DF91	0.30	EF183	0.30	PCF80	0.80	UAF42	0.75	6K25	0.75
DF96	0.50	EF184	0.35	PCF82	0.95	UBC41	0.75	6L6G	0.55
DK91	0.45	EL32	0.80	PCF86	0.60	UBC81	0.45	6Q7M	0.50
DK92	0.70	EL33	1.75	PCF801	0.60	UBF80	0.40	4Q7G	0.50
DK96	0.60	EL34	0.50	PCF802	0.50	UBF89	0.40	68L7GT	0.45
DL92	0.40	EL36	0.50	PCF805	0.80	UCC85	0.45	68N7GT	0.45
DL94	0.48	EL37	2.50	PCF806	0.75	UCH42	0.75	68Q7GT	0.50
DL96	0.55	EL41	0.90	PCF808	0.85	UCH81	0.40	6U5G	0.75
DY80/87	0.37	EL42	0.90	PCL82	0.35	UCL82	0.35	8V6G	0.40
DY802	0.37	EL84	0.25	PCL83	0.66	UCL83	0.70	8V6GT	0.45
EABCS80	0.88	EL85	0.35	PCL84	0.45	UF41	0.75	8X4	0.40
EAF42	0.75	ELL80	1.00	PCL85	0.50	UF89	0.40	8X5G	0.40
EB91	0.22	EM80	0.45	PCL86	0.45	UL41	0.85	8X5GT	0.45
EBC33	1.00	EM81	0.60	PCL805/85		UL84	0.48	7B6	0.75
EBC41	0.75	EM84	0.35	PD500	1.50	UY41	0.48	7B7	0.70
EBC81	0.85	EM85	1.00	PEN45	0.75	VR150-30	0.40	7C5	1.00
EBF80	0.40	EY51	0.40	PCF85	0.55	OA2	0.40	7C6	0.75
EBF83	0.40	EY86	0.40	PCF86	0.60	OB2	0.40	7H7	0.70
EBF89	0.32	EZ40	0.75	PL81	0.50	1R5	0.35	7R7	2.25
EBL31	1.50	EZ41	0.75	PL82	0.45	1T4	0.30	7X4	0.75
ECC81	0.40	EZ80	0.28	PL83	0.45	1T4	0.30	12A2E	0.40
ECC82	0.88	EZ81	0.28	PL84	0.40	384	0.40	12A7U	0.40
ECC83	0.33	GY501	0.80	PL802	0.95	3V4	0.48	12A7V	0.38
ECC84	0.30	GZ30	0.45	PL504	0.75	3R4GY	0.75	12AX7	0.32
ECC85	0.40	GZ32	0.50	PL508	0.90	5U4G	0.40	12BA6	0.45
ECC88	0.40	GZ34	0.60	PL509	1.55	5V4G	0.50	12BE6	0.50
ECH35	1.25	GZ37	1.25	PL802	0.95	5Y3GT	0.45	30C1	0.80
ECH42	1.00	HN309	1.50	PX4	3.00	5Z4G	0.45	30C15	1.05
ECH81	0.30	KT61	1.75	PX25	3.00	6/30L2	0.80	30C17	1.10
ECH83	0.45	KT66	2.50	PY33	0.33	6AK5	0.40	30C18	0.80
ECL80	0.45	KT81 (7C5)		PY81	0.30	6AM5	0.90	30F6	1.10
ECL82	0.35			PY82	0.35	6AQ5	0.42	30FL1	0.75
ECL83	0.68	KT81	1.75	PY83	0.38	6AT6	0.38	30FL2	0.75
ECL86	0.40	KT88	2.90	PY88	0.40	6AU6	0.30	30FL14	0.85
ECLL800	2.25	KTW61	1.00	PY800	0.47	6BA6	0.28	30L15	1.05
EF37A	1.20	MU14	1.00	PY81/800	0.50	6BE6	0.32	30L17	0.90
EF39	1.20	N78	1.60	PY801	0.50	6BH6	0.75	30P4MR	1.80
						6BJ6	0.55	30P12	1.05
						6BQ7A	0.55	30P19	1.00
						6BR7	0.90	30PL1	0.95
						6BS7	1.35	30PL13	1.20
						6BW6	0.90	30PL14	1.25
						6C4	0.35	35W4	0.40
						6CD6G	1.30	50CD6G	1.20
						6CH6	0.80	807	0.50
						6CW4	0.70	813 ITT	£13
						6F23	1.05	813 USSR	
						6F25	1.00		£5.75
						6F28	0.70		
						6J5M	0.60		
						6J5G	0.45		
						6K6A	0.85		

TRANSISTORS-INTEGRATED CIRCUITS

EXPRESS POSTAGE

3p for first Transistor, for each additional add 1p.

AA119	0.7	BD132	0.80
AAZ13	0.10	BF115	0.25
AAZ15	0.10	BF167	0.25
AC107	0.85	BF173	0.25
AC126	0.25	BF179	0.30
AC127	0.25	BF180	0.30
AC128	0.25	BF181	0.32
AC178	0.25	BF194	0.15
AC187	0.25	BF195	0.15
AC188	0.25	BF197	0.15
ACV21	0.20	BF200	0.35
ACV39	0.55	BF861	0.25
AD140	0.50	BF898	0.25
AD149	0.50	BFX29	0.25
AD161	0.35	BFX88	0.20
AD162	0.35	BFY60	0.20
AF115	0.24	BFY61	0.20
AF116	0.25	BFY62	0.20
AF117	0.20	BFW10	0.61
AF186	0.40	BY100	0.15
AF239	0.40	BY126	0.15
ABY27	0.30	BY127	0.15
ABY28	0.25	BZX81 series	
BA102	0.30	BZY88 series	0.12
BA115	0.7		
BC107	0.10		
BC108	0.10	CR81-05	0.25
BC109	0.10	CR81-40	0.35
BC113	0.15	CR83-05	0.30
BC117	0.20	CR83-40	0.45
BC143	0.35	MJE340	0.50
BC147	0.12	MJE370	0.70
BC148	0.10	MJE620	0.75
BC169C	0.12	MJE2955	1.10
BC182	0.10	MJE3055	0.75
BC182L	0.12	MPP102	0.42
BC184L	0.11	MPP103	0.35
BCY32	0.60	MPP104	0.37
BCY33	0.34	MPP105	0.40
BCY34	0.85	NKT404	0.50
BCY70	0.15	OA5	0.50
BCY71	0.20	OA10	0.35
BCY72	0.15	OA79	0.7
BCZ11	0.50	OA81	0.10
BD121	0.75	OA91	0.7
BD124	0.80	OA200	0.7
BD131	0.75	OA202	0.10

All transistors, I.C's offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

OC16	0.75	ZTX500	0.15	2N2646	0.50
OC20	0.95	ZTX501	0.16	2N2904	0.18
OC23	0.85	ZTX503	0.17	2N2904A	0.25
OC25	0.40	ZTX531	0.20	2N2905	0.28
OC28	0.85	ZTX550	0.20	2N2905A	0.28
OC35	0.50	IN914	0.7	2N2906	0.20
OC36	0.85	IN4001	0.6	2N2928	0.10
OC42	0.40	IN4002	0.7	2N3059	0.20
OC44	0.15	IN4003	0.8	2N3055	0.55
OC45	0.15	IN4004	0.8	2N3525	0.75
OC71	0.15	IN4005	0.10	2N3614	0.59
OC72	0.25	IN4006	0.12	2N3615	0.75
OC76	0.40	IN4007	0.15	2N3702	0.10
OC77	0.45	IN4009	0.6	2N3703	0.10
OC81	0.25	IN4148	0.8	2N3704	0.10
OC81D	0.25	IN921	0.10	2N3705	0.10
OC81Z	0.55	IB2033	0.20	2N3706	0.10
OC83	0.25	IB2051A	0.20	2N3707	0.10
OC140	0.55	IB2100A	0.20	2N3708	0.10
OC170	0.25	IB3010	0.25	2N3709	0.10
OC171	0.30	2N696	0.15	2N3710	0.10
OC200	0.45	2N697	0.15	2N3711	0.10
OC201	0.75	2N706	0.10	2N3819	0.35
OC202	0.80	2N706A	0.12	2N3820	0.50
OC203	0.60	2N1131	0.25	2N3823	0.68
OC7P1	1.25				



WILMSLOW AUDIO


THE Firm for speakers!

SPEAKERS

EMI 13 x 8, 3, 8 or 15 ohm	£2.03
EMI 13 x 8, 150 d/c 3, 8 or 15 ohm	£2.25
EMI 13 x 8, 450 t/tw 3, 8 or 15 ohm	£3.60
EMI 13 x 8 type 350 8 ohm	£8.25
EMI 6 1/2" 93850 4 or 8 ohm	£2.80
EMI 8 x 5, d/Cone Roll/s 8 ohm	£2.50
Baker Group 25 3, 8 or 15 ohm	£6.60
Baker Group 35 3, 8 or 15 ohm	£7.50
Baker De Luxe 12" d/cone	£9.62
Baker Major 12"	£7.50
Kef T27	£4.67
Kef T15	£5.50
Kef B110	£6.16
Kef B200	£7.42
Kef B139	£10.72
Kef DN8	£1.92
Kef DN9	£1.37
Kef DNI2	£4.12
Kef DNI3	£2.75
Fane Pop 100 watt 8/15 ohm	£21.45
Fane Pop 60 watt 8/15 ohm	£12.26
Fane Pop 50 watt 8/15 ohm	£10.17
Fane Pop 25/2 25 watt 8/15 ohm	£5.94
Fane Pop 15 watt 8/15 ohm	£4.40
Fane Crescendo 15" 8 or 15 ohm	£27.50
Fane Crescendo 12A 100w 8 or 15ohm	£24.20
Fane Crescendo 12B 75w bass 8 or 15	£24.20
Fane 8077 8" d/c roll/s 8 or 15 ohm	£3.85
Fane 808T 8" d/c cone 8 or 15 ohm	£2.64
Goodmans Axent 100 tweeter	£6.60
Goodmans 8P 8 or 15 ohm	£3.80
Goodmans 10P 8 or 15 ohm	£4.49
Goodmans 12P 8 or 15 ohm	£11.55
Goodmans 15P 8 or 15 ohm	£17.05
Goodmans 18P 8 or 15 ohm	£29.70
Goodmans Twinaxiom 8	£6.79
Goodmans Twinaxiom 10	£7.61
Elac 9 x 5 5" 59RM109 15 ohm,	
59RM114 8 ohm	£2.53
Elac 6 1/2" d/c roll/s 8 ohm	£3.22
Elac 6 1/2" d/c cone 8 ohm	£2.59
Elac 4" tweeter TW4	£1.21
Wharfedale Bronze 8 RS/DD	£3.11
Wharfedale Super 8 RS/DD	£5.50
Wharfedale Super 10 RS/DD	£9.80
Coral 6 1/2" d/c cone roll/s 8 ohm	£2.42
Siran 6 1/2" 3 or 8 ohm	£1.44
Richard Allan 12" d/c 3 or 15 ohm	£2.20
10" x 6" 3, 8 or 15 ohm	£1.92
8" x 5" 3 or 8 ohm	£1.38
7" x 4" 3 or 8 ohm	£1.38
2 1/2" 64 ohm or 70 mm 80 ohm	£0.65
Adastra Hiten 10" 10w 8 or 15 ohm	£2.80
Eagle DT33 dome tw.	£5.45
Eagle HT15 tweeter	£3.66
Eagle CT5 tweeter	£1.25
Eagle CT10 tweeter	£2.54
Eagle MHT10 tweeter	£3.74
Eagle FR4	£4.45
Eagle xover CN23, 28, 216	£1.10
Sp. matching transformer 3-15 ohm	£1.10
Celestion MF1000 25w horn 8 or 15 ohm	£10.45
Celestion PS8 (for Unilex)	£2.16
Celestion G12M 8 or 15 ohm	£12.00
Celestion G12H 8 or 15 ohm	£15.00
Celestion G15C 8 or 15 ohm	£24.00
Celestion G18C 8 or 15 ohm	£33.00
Car Stereo speakers—ask for leaflet.	

SPEAKER KITS

Wharfedale Unit 3	£8.25
Wharfedale Unit 4	£14.50
Wharfedale Unit 5	21.00
Richard Allan Twinkit	£7.95
Richard Allan Triple 8	£11.75
Richard Allan Triple Assem.	£17.50
Richard Allan Super Triple	£20.75
Goodmans DIN 20	£8.58
Fane Mode One	£9.00
Kefkit 2	£25.75
Kefkit 3	£35.50
Peerless 2-8	£5.50
Peerless 10-2	£8.47
Peerless 20-2	£10.41
Helme XLK 25 (Pair)	£18.17
Helme XLK 50 (Pair)	£37.18
Stephenspeaker kits and cabinets—send for free booklet "Choosing a Speaker".	
Prices include VAT.	
Carriage and insurance 75p per kit.	

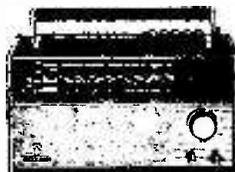

RADIOS/CASSETTES/AMPS.

Grundig Mariner TR865	£32.00
Grundig Elite Boy 500	£27.00
Grundig Melody Boy 500	£27.00
Grundig Melody Boy 1000	£38.75
Grundig Yacht Boy 210	£34.25
Grundig RF430 mains	£27.00
Grundig RF310 mains	£22.75
Grundig RF310	£21.25
Grundig Top Boy	£16.75
Grundig Satellit 1000	£121.00
Grundig CA02 cassette	£27.00
Grundig Signal 500	£27.00
Grundig C230 Cassette	£28.00
Tandberg TP41	£42.00
BASF 9301 radio/cassette	£58.00
Bush YTR178 5 Band (Inc. Air)	£29.00
Trio KA2000A	£33.00
Trio KA2002	£41.00
ITT Colt	£9.95
ITT/KB Golf Preset	£21.25
ITT/KB Weekend Auto	£16.00
ITT/KB Europa	£18.00
ITT/KB SL53 cassette	£22.82
ITT/KB Studio 73 stereo cassette	£44.00
Koyo KTR1664 8 waveband	£40.00
Koyo KRT 1770 11 waveband	£56.50
Koyo KTR1883 5 Band (Inc. Air)	£23.50
Tec C200 Radio/Cassette	£31.00

Prices include VAT.
Carriage and insurance 75p. FREE with each radio—"World Radio Stations Book"

PA/DISCO AMPLIFIERS

Carriage and insurance £1.00	
Baker 100 Watt	£40.00
Linear 30/40	£25.00
Linear 40/60	£30.00
Linear 80/100	£55.00

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage and insurance 35p per speaker (tweeters and crossovers 20p)

ALL PRICES QUOTED INCLUDE V.A.T.

WILMSLOW AUDIO Dept. P.W.

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Radios etc: 10 Swan St., Wilmslow, Cheshire SK9 1HF.

Telephone Wilmslow 29599

Ambit International

We are not just another component retailer—but a complete semiconductor service. We can either supply—or tell you where to get—any semiconductor device with *manufacturer's* numbering—not user's numbering. See our latest catalogue issue for full information.

15p—no S.A.E. required

For those of you who already have an AMBIT catalogue, send us an A5 S.A.E. plus 10p, stating the number on the last page in your catalogue—and we will send you all the latest update releases (up to page 25).

AMBIT—the linear microcircuit specialists—

for Phase Locked Loops	
NE561B (16 DIL)	AM/FM coil-less radio receiver or IF strip £3.50
	AM/FM demodulator kits with mechanical filter—see October's PW £5.00
NE562B (16 DIL)	Similar to the 561, but without AM facility. The VCO output is separately available for synthesizer applications. £3.60
NE565 (14 DIL)	High stability—low frequency telemetry demodulator and NBFM demodulator £2.80
567 (8 DIP)	A P.L.L. for accurate tone decoding and NBFM reception (5-9) V working £2.80
555 (8 DIP)	Versatile timing IC, use as 'one shot' or multi-vibrator 86p
555/2	Two 555's in one package Use one for ultra sonic carrier—and the other as the modulator £1.63
LS8038 (14 DIL)	A unique triangle/square/sine wave function generator up to 1MHz—complete signal generator in a chip. A FULL data sheet is included with each device on request £3.20

for Audio	
LM380 (14 DIL)	Simple, safe and versatile 2W RMS at 12V: 4W RMS at 18V Use only 3 external components £1.40
TBA810S	SGS power IC. 7W RMS at 16V £1.70

for Radio	
(see last month's advertisement for our radio IC feature)	
TBA651 (16 DIL)	1µV sensitivity AM/FM/SSB with RF mixer and IF £2.00
	low external parts count*
TBA120 (14 DIL)	FM IF strip and detector £1.00
CA3089E (16 DIL)	FM IF system AFC-AGC-SQUELCH-TUNING-METER OUTPUT—the very best FM IC £2.20
(14 DIL)	
MC1310P	P.L.L. Stereo decoder IC, with layout spec. £3.15 each
(14 DIL)	FULL kit with PCB £3.98 each

for TOKO Filters at 455KHz and 10-7MHz	
Ceramic	CFT455B 8KHz bandwidth 50p
	CFT455C 6KHz bandwidth 50p
	CFU455C 4-8KHz bandwidth 55p
	CFS10-7 Wide band FM (2 required per set) 40p each
455KHz	MFH-T A 4, 5, or 7KHz version £1.50
Mechanical	For a complete ignition interference cure, a suppression booklet on tracing and curing interference 45p
	Screened plug connectors, straight or angled 50p
	Plug in distributor suppressors 36p
	1µF with lucar/large lucar/wire terminations 20p
	2µF with lucar or large lucar wire terminations 30p
	Other items to order
	Plus LED Displays, 250MHz decade counters, voltage regulators, kits for tone coders, NI Cads—In fact everything to lead you through the micro-circuit maze.

PW FERRET KIT	
Electronics only*	£9.50
* with improved circuit and full modification details	


Callers now welcome at
37a HIGH STREET, BRENTWOOD, ESSEX
CM14 4RH
Tel. (0277) 216029

Terms: C.W.O. All Prices include V.A.T.
Handling charge now 10p per order.
FIRST CLASS POSTAGE on all items under 80z.

MODULE CABINET



M.G.SKEET

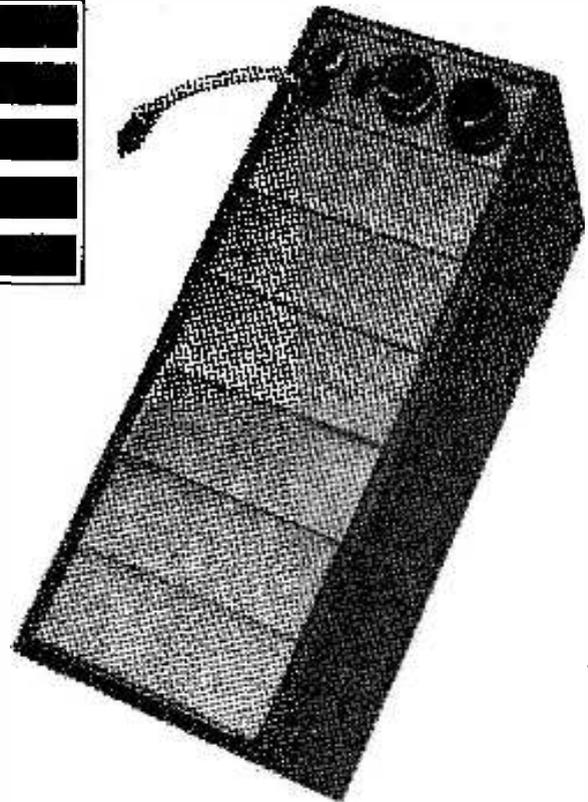


A plug-in module system allows the maximum use to be made of a given space as far as 'tucking away' circuitry is concerned. To be able to pull out a 'card', with the circuit components on it, for modification or maintenance, makes these tasks much easier. The cost of commercial designs (and their availability) must deter experimenters from using this desirable system. Described here is a method of building this system quite cheaply in terms of purchased items. A plywood box, hardwood runners, aluminium alloy sheet fabrications, RS Components small perforated sheet and edge connectors are the main items needed. A word or two first about the uses that the system can be put to. In the author's case such a unit stands beside a tape deck to provide versatile record and playback preamplifier facilities. However, it is suitable for a modular preamp or mixer etc. The dimensions quoted are to suit the author's particular requirements in that other factors dictated the maximum size possible.

DESIGN

Major requirements of the design were:— detachable screening of cards from each other, space on the panel for potentiometers, switches etc., ease of getting the leads away from the unit for external connections and the use of an external power supply. The latter was considered necessary because of the space it would take and because of possible hum induction problems.

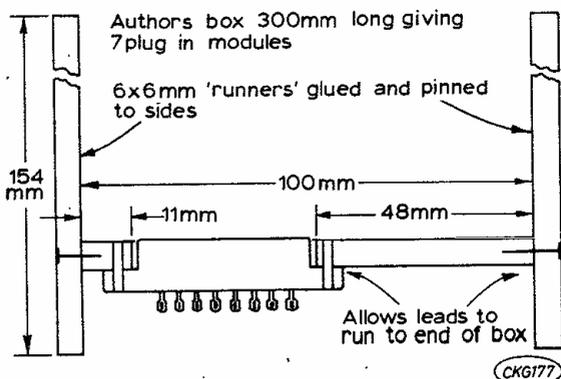Part of the detachable screen protrudes above the box by approximately 8mm and it is this which is used to pull out the cards. The perforated sheet as supplied measures 172mm by 133mm which, in the author's case, was cut to give two cards 123mm by 83mm.




Cross section of the box detailing method of construction and mounting of edge connectors. The photograph shows the hardwood runners which are spaced to suit the gauge of metal used for the modules.

CONSTRUCTION

The photographs and drawings show the overall construction method. If the idea of painting with emulsion paint appeals then butt joints, pinned and glued, can be used. A filler glue such as Cascamite is suitable. The alloy sheet can be as thin as 20SWG; this is fine for the job due to its mechanical properties, easily cut, drilled and bent yet rigid enough to maintain shape. If aluminium is used it should be at least 18SWG.

The spacing between the runners is governed by the metal thickness. No fixing is provided in the top panels to hold the modules in place because the friction of metal against runner as the modules are pushed home holds everything firm. The inside of the detachable screens are Fablon covered to avoid contact with the wired side of the perforated sheet. It is necessary to bend the protruding part of the screens slightly inwards to allow the module alongside to slide in and out.

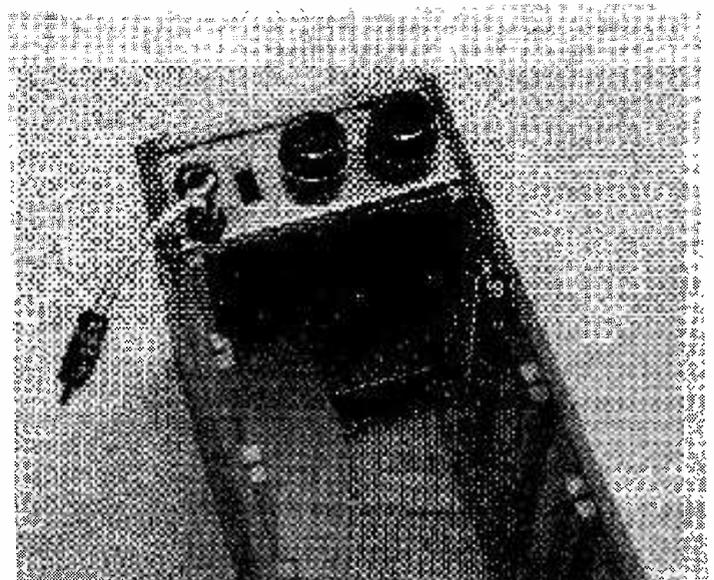

WIRING


Inter-module wiring is run from connector to connector in the bottom recess of the box. The same ways should be reserved for earth and power supplies on each connector to prevent possible damage should a module be plugged into the wrong position. Sockets may be fitted at the end of the box for the external connections, but in the author's case the leads are run straight out through holes. Clips are fixed near the edge connectors to hold the cables in place. A removable cover for the base of the box can be added if required.

Countersunk 6BA screws, washers and nuts hold together the alloy top panel, perforated sheet, bottom runner and 8-way plug. As an aid to countersinking the screws in the thin alloy sheet, 2BA nuts are used over the screws immediately they are passed through the alloy sheet. These give the desired spacing between the perforated sheet and the alloy pieces. Earthing of the metal-work is achieved via one of the screws passing through the 8-way plug which is fitted with a solder tag. The plug point for earth is connected to it and from there a bare wire is suitably routed around the perforated sheet. Contact between the lower runner, the detachable screen and the top panel has been relied upon to extend the screening earth over these components. Earth loops due to contact between the top panels of adjacent modules could be a possible source of trouble. A strip of Fablon or pvc tape on the top panel flange should cure any problems here. ■

★ Materials List

Edge connectors, 8-way
Edge plugs (cut down to give four 8-way plugs)
Perforated sheet, small
Turret tags, small (to fit the perforated sheet).


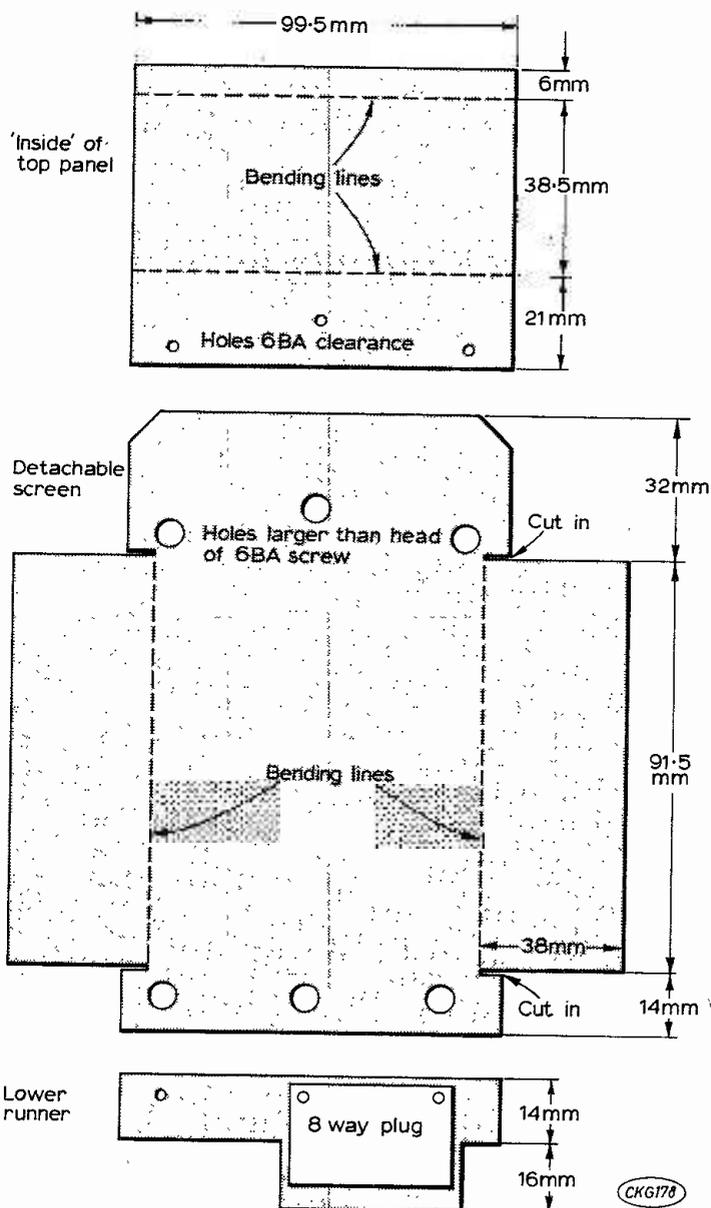
All these parts are by RS Components Ltd., available only via retailers handling that company's components.



Cutting, drilling and bending of the module metalwork.

Details of module construction showing, from left to right:—

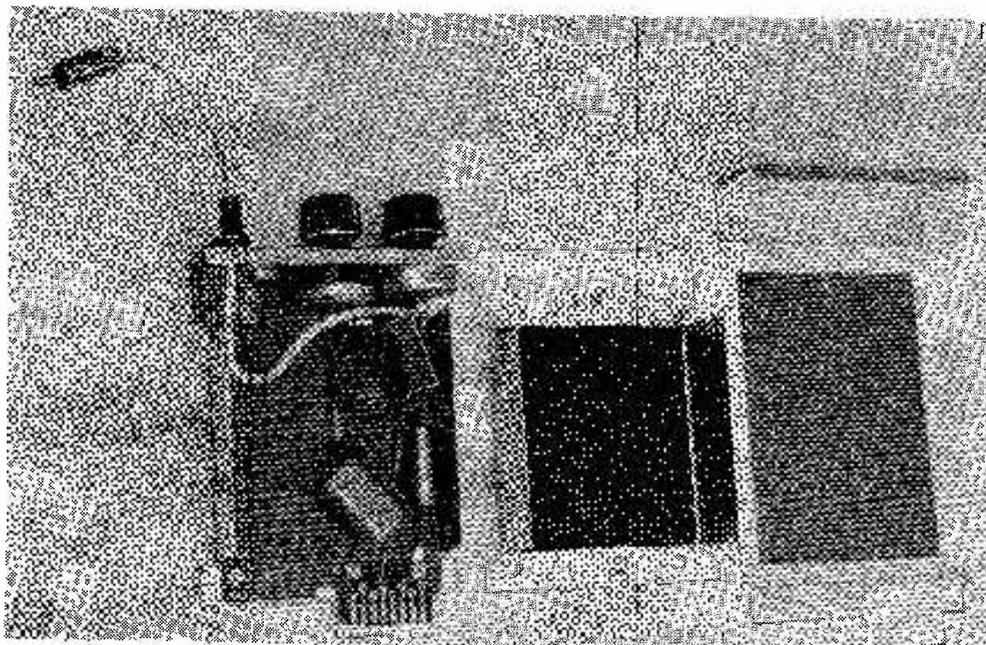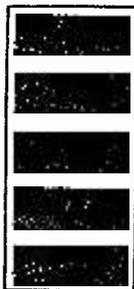- (a) A typical module, assembled and wired.
- (b) The detachable screen with insulating plastic covering in position.
- (c) The top panel, perforated sheet and lower runner.



ELECTROVALUE CATALOGUE 7



NOW READY

- Transistors from 8p
- Capacitors from 2p
- Resistors from 1p
- Pots from 12p
- Constructional Hardware
- Knobs
- I.C.s
- Diagrams, Data
- Genuine Discounts

25p

Send 25p for your copy of EV Catalogue 7. It includes a Refund Voucher for 25p allowable on orders for £5 or more, list value.

112 pages (plus covers) and our best yet! Practically all items in Catalogue 7 are there as the result of information fed by our own computer, enabling us to control stock-buying in relation to demand with remarkable accuracy. This means that your orders, which we micro-film for record keeping, is handled with utmost speed and efficiency. EV prices remain keenly competitive and in addition there are discounts as well, to give you further savings. Among the well-known firms whose products we carry are those of **SIEMENS, NEWMARKET, RADIOHM, SOLDERSTAT, GUEST INTERNATIONAL** as well as Texas Instruments, Mullard and others.

FROM CATALOGUE 7

Volume Controls—Mono, 12p: Matched two-gang
42p: Switch 12p extra either type.

Transistors—

2N2646 unijunction	51p
2N3055 high power	60p
AD161 medium power NPN	42p
AD162 medium power PNP	40p
BC109 Low Noise	15p
7400 quad 2 input NAND	25p

S DeC 4-pack £6.37: **T DeC** £3.30: **Micro-DeC** £3.75
Photo-conductive cell TPMD 40p

Ceramic Disc Capacitors—50V. 0.01 & 0.02 mFd,
ea. 2p: 0.04 mFd 3p

Main Line 70 amplifier £12.60 nett

ZENER DIODES

Full range E.24 values	14p
400 mW 2.7V to 36V	21p
1 Watt 6.8V to 82V	48p
1.5W 4.7V to 75V	4p
Clip to increase 1.5W rating to 3W (Type 266F)	

MINITRON DIGITAL INDICATORS

30151F seven segment, filament, compatible with standard logic modules.
0 to 9, + decimal point. 9mm characters. In 16 lead DIL. Some alphabetical symbols available £1.20
Suitable BCD decoder driver 7447 £1.15
No. 3015G showing + or— and 1 and dec. pt. nett £1.20

NUTS, BOLTS, KNOBS, SWITCHES, etc.
BABANI TECHNICAL BOOKS

V.A.T. 10% must be added to nett value of order for Value Added Tax.

U.S.A. CUSTOMERS

are invited to contact Electrovalue America, P.O. Box 27, Swarthmore P.A.

This is EV Service

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £15. 15% on orders £15 and over.

PACKING & POSTAGE

FREE in U.K. For mail orders for £2 list value and under, there is an additional handling charge of 10p.

TERMS OF BUSINESS

All items are offered for sale in accordance with our standard terms of business, a copy of which is available on request. Due to the length of time between preparing this ad., and its publication, prices quoted may be subject to alteration without notice.

ELECTROVALUE LTD

28 ST JUDES RD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475

Hours 9-5.30, 1.0 p.m. Saturdays

Bus. Reg. No. 1047769

★ NORTHERN BRANCH

For the convenience of many friends and customers in the north we are opening a branch in Manchester early in January. Watch for further details.

All postal communications to Englefield Green address, please

ELECTROVALUE CATALOGUE 7 PLEASE

I enclose 25p

NAME

ADDRESS

Write in BLOCK LETTERS

PW

851

TWO NEW SOLDER SIPPERS MAKE DE- SOLDERING QUICK & EASY

A SUPER
PRESENT
ANYTIME!

Longs

Longs Ltd.
Hanworth Lane
Trading Estate
Chertsey Surrey
KT16 9LZ.

Maxi-Super HT 1810 and Maxi-Mini HT 1800 Solder Sippers

Designed for use when working or re-working P.C. Boards. Permits removal of molten solder from Multi-leg components, enabling easy extraction. The solder is 'sipped' through the nozzle, and automatically ejected when the instrument is next used. A Swiss precision instrument manufactured to a high degree of accuracy.

The anti-corrosive outside casing has a knurled finish for more positive grip, and encases plated internal parts.

The Maxi-Super has been designed with a 3.5 kg. spring action recoilless plunger, whilst the Maxi-Mini with its conveniently shaped operating button, has a 2.5 kg. spring action plunger, protected by a channel guard. Both models have been designed with an easy-to-replace 'dupont' teflon screw-in nozzle.

PLEASE FORWARD without obligation further details.	PLEASE SUPPLY Maxi-Super HT 1810 at £6.60	PLEASE SUPPLY Maxi-Mini HT 1800 at £4.95
I enclose cheque value £.....		
NAME.....	POSITION.....	
COMPANY.....		
ADDRESS.....		
SIGNED.....		Reg. England 68496

Prices include VAT

SPECIAL 40 MHz SCOPE—SOLARTRON CD1212 ONLY £50. Has to be a snag. There are no plug-in Y amps available. TB—100 nanosecs per cm to 5 secs per cm in 24 calibrated ranges. 20 nanosecs per cm with times 5 expansion. .5in flat faced tube. Trace locator. 0-2 microsec signal delay. Built-in calibrator 1kHz square wave. 200 micro volts to 100 volts in 18 calibrated ranges. Tube sensitivity 3V/cm. Main Frame Y Amp boosts this to better than 200 MV per cm at 40 MHz. 240V 50 Hz input. Complete with full manual including plug-in circuits. Come and see one working or Carriage £1.50.

12" LONG PERSISTENCE CRT, Full spec. Price £7.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5.50, P. & P. 25p. (Not cased, not calibrated.)

NEW WIDE RANGE WOBBULATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 40-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6 3V A.C. and use within minutes of receiving. All this for ONLY £5.75, P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB. SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £7.85 each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each, P. & P. 5p.

PLEASE ADD 10% V.A.T.
Open 9 a.m. to 6.30 p.m. any day.
CHILTMEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 582605/65916

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors ½ and ¼ watt, many high stabs, etc. Fine value at 50p, P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice, 25p, P. & P. 15p.

5 MOVING COIL METERS. Various, £2, P. & P. 37p.

CAPACITOR PACK—50 Brand new components, only 50p, P. & P. 17p.

POTS—10 different values. Brand new, 50p, P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 10p.

FLAT FACED 4" TWIN BEAM TUBE type CV2193. Green trace. Brand new £4 each, P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New. 38p each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, 13p each.

PHOTO RESISTOR type Clare 703. Two for 50p.

MODERN TELEPHONES type 706. Two-tone grey, £3.75 each. The same but black, £2.75 each, P. & P. 25p each.

Also **TOPAZ YELLOW** £4.50 each, P. & P. 25p.

Ideal **EXTENSION TELEPHONES** with standard GPO type dial, bell and lead coding. £1.75 each, P. & P. 25p.

DELIVERED TO YOUR DOOR
1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.



The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

**YOUR
100%
GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

I purchased Basic Electricity and I have found them to be the best books of their kind that I have ever read. Will you please send Basic Electronics. G.S. Portsmouth.

"EVERYTHING IS MADE SIMPLE" which makes reading a pleasure. V. S. Farley

"BOOKS ARE WONDERFUL", thank you. A.C.S. Colwyn Bay

I earnestly believe these manuals make the subject become a "Cake Walk". S.S. Lewisham

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £4.50

BASIC ELECTRONICS 6 parts £5.40

BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS

FULL POSTAL.....

ADDRESS

POST NOW FOR THIS OFFER!

EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

LEARNING BY PRACTICAL PROJECT STEPS

PART 4—THE ASTABLE MULTIVIBRATOR

THE basic circuit that we shall describe this month is called the *astable* multivibrator. Sometimes it is called a free running multivibrator. Whereas last month's circuit required an input pulse to make the output voltage change in level for a fixed period of time the astable circuit causes the output to change to a new level for a fixed period—just as before—but after a dwell time with the output in its original state the circuit re-triggers itself. The operation continues indefinitely with the output level staying at a high voltage for a fixed period and then reverting to a low level for a fixed period; because this is a self sustaining process the circuit comes into the general category of oscillators and as such finds its way into many simple circuits. Its main attractions are that it needs no inductors and is very simple to build; at the same time it is reliable and can be designed to cover a vast range of frequencies. Its only limitation is the shape of its waveform which is rectangular.

Nevertheless there are many useful applications for such a signal as we shall see. First of all have a look at the basic working circuit shown in Fig. 21.

The diodes D1 and D2 serve no purpose other than providing reverse voltage protection for the base emitter junctions of Tr1 and Tr2. With the components suggested the circuit oscillates at a

low frequency and the output waveform can easily be monitored on a 20,000 Ω /V meter.

First of all check the frequency of the signal by counting the number of times the voltage at point A goes through a complete cycle in a minute and note that the extremes of output signal level approach the maximum +ve rail and zero voltage (negative) rail. The length of time the voltage is high should approximately equal the time in the low state—we say that the waveform has a unity mark space ratio.

Circuit operation

To understand the circuit's operation imagine that Tr1 is not conducting; the voltage at its collector will thus be +9V. Likewise assume that C1 has just discharged through the circuit of R1 and R2. This discharge will not be complete because when the potential at the base of Tr2 reaches 600mV (this corresponds to 1.2V at point B) Tr2 will be driven into conduction and the voltage at point A will fall to zero from an original +9V. The action of this drop in voltage at Tr2's collector causes a negative going voltage to appear on the negative plate of C2. This ensures that Tr1 is well and truly switched off. You can see that the negative plate of C2 actually goes negative by monitoring the voltage there; connect the *positive* lead of your meter to ground and the *negative* lead to the junction C2 and D1. The voltage is driven to approximately -8.5V. If, however you keep monitoring this voltage you will find that it starts to rise in a positive direction as C2 discharges through the circuit of R4 and R3. When +1.2V is reached Tr1 switches on and the voltage at its collector falls. In a similar manner this negative going change makes Tr2 switch off and the voltage at A rises to +9V. The junction of D2 and C1 will now be found to be at -8.5V and the level will return according to the time constant of C1 with R2 and R1 until eventually Tr2 switches on again—thus repeating the cycle.

You can say—in simple terms—that when Tr1 is switched on Tr2 is switched off and vice versa. The length of time Tr2 is on is set by C2 R4 and R3, but



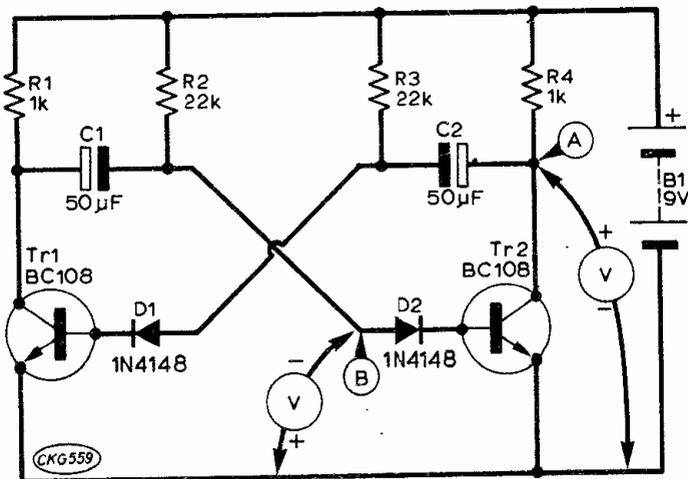


Fig. 21: Slow running astable multivibrator. Monitor the waveforms at points A and B with a 20,000 Ω /V meter.

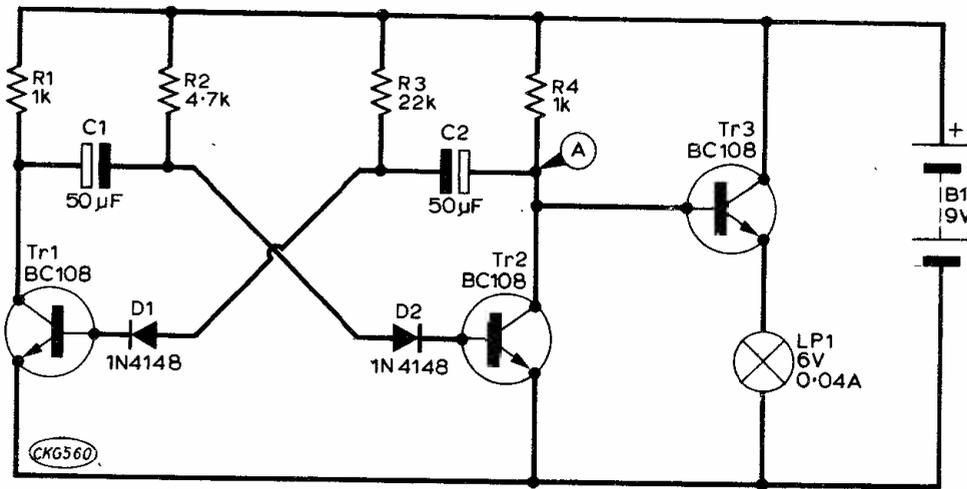


◀ Fig. 22: R2 has been reduced in value so that the width of the positive level of the waveform at A is reduced. This produces a short repetitive flash from the lamp.

Fig. 23: Layout for Fig. 21 (left portion only). Layout for Fig. 22 (left and centre portion).

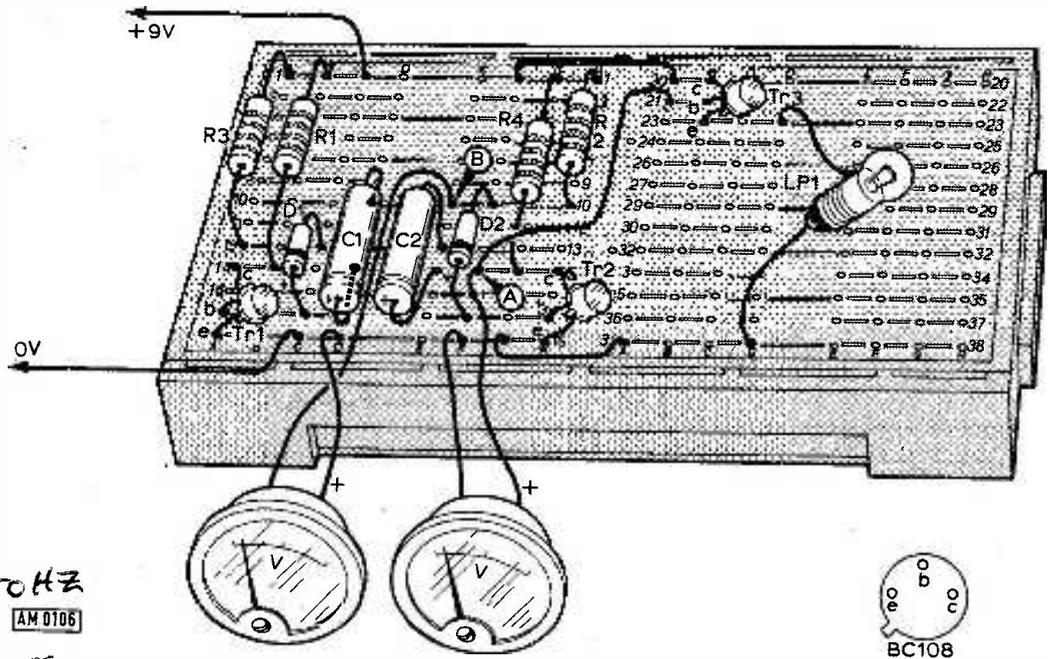

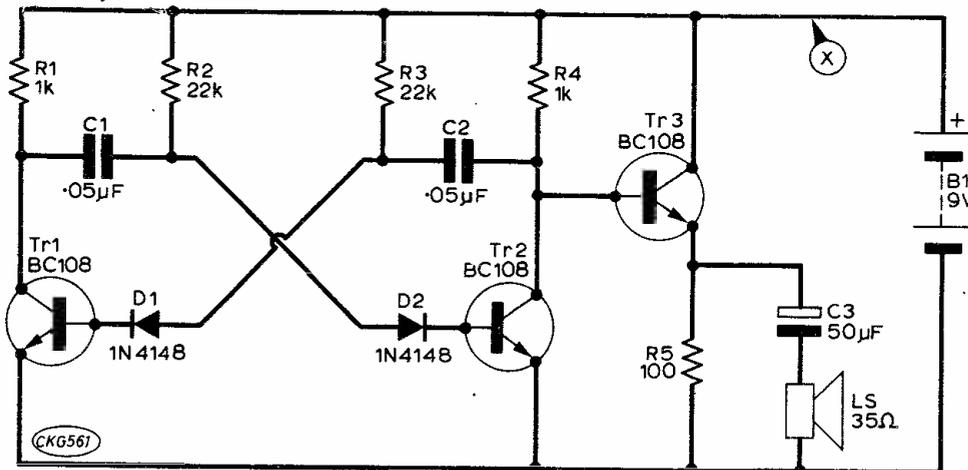$f = \frac{10^6}{1.4 \times 0.05 \times 22000} = 650 \text{ Hz}$
AM 0106



◀ Fig. 24: Reducing the values of C1 and C2 brings the operating frequency into the audio range. If a key is inserted at point X the circuit makes a useful morse practice oscillator.

R3 is very large compared with R4 so the former has most effect. The time can be calculated from the formula

$T_{on} = 0.7 \times R3 \times C2$ (R in ohms, C in farads and T in seconds).

In a similar way one can say that the time Tr1 is switched on is controlled, effectively by R2 and C1. This is the length of time Tr2 will be off during that part of the cycle. We can thus write

$T_{off} = 0.7 \times R2 \times C2$

If we make the circuit symmetrical so that R2 equals R3 and C1 equals C2 the on time will equal the off time and the frequency of operation becomes

$$f = \frac{1}{1.4 \times C2 \times R3}$$

If you halve the value for R2 you will halve the off time of the waveform. This means that we get an asymmetric mark space ratio. Increasing the value for R2 will change the ratio the other way. One can vary the ratio over wide limits and the only

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

Better built Better performance Better value

SAXON HI-FI POWER AMPS FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors now available.

To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



SA35 35 watts RMS. Uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

SA50 50 watts RMS. 7 transistors, 7 diodes. Carr. paid. **£5.65**

SA100 makes an ideal unit in disco assemblies. A real glutton for work. **£10.90**

Reliable, tough and compact, 11 transistors, 6 diodes. Carr. paid.

BRIEF SPEC. FOR ALL THREE MODULES

All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in the SA.100.

Freq. response	15-40,000 Hz \pm 1dB
Distortion	0.2% at 1kHz
Loads	4 to 16 ohms
Quiescent current	15 mA
Noise	Better than -75dB
Supply voltage	SA35 45 volts SA50 45-65 volts SA100 40-70 volts
Size	4 1/2" x 4" x 1 1/2" (SA.100) 4 1/2" x 3" x 1 1/2" (SA35/SA50)

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA35, SA50 AND SA100 POWER AMPS. ABOVE

PU.45	Unstabilised supply for 2 SA35's	£4.90
PU.70	Unstabilised supply for one or two SA50 or SA100 Carr. 40p	£7.75
PS.45	Stabilised module for two SA35's or one SA50 Carr. free	£3.50
MT.45	Transformer for above, heavy duty Carr. 20p	£2.85
MT.30	Transformer for unstabilised supply complete with rectifier diodes mounted Carr. 20p	£3.50
PS.70	Stabilised supply module for one or two SA100's Carr. free	£4.90
MT.70	Transformer for PS70 Carr. 40p	£4.90

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

Orders and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 327 Whitehorse Rd., W. Croydon, Surrey. CR0 2HS.

Telephone 01-684 6385

Hours 9.30 a.m.-5.30 p.m.


TRADE & EXPORT ENQUIRIES INVITED

SAXON P/A MIXER CONTROL UNITS

In extra slimline easy-fit case

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos etc. Standard jack sockets. Compact design. In strong metal cases. All units guaranteed for 3 years.

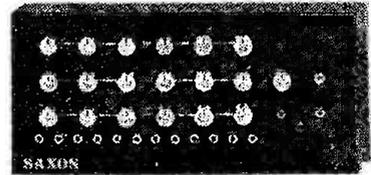- HIGH AND LOW IMPEDANCE INPUTS
- BASS/TREBLE/VOLUME ON EACH PAIR
- MASTER CONTROL ON OUTPUT



● **M4H**
4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" x 8" x 2 1/2". Carr. paid. + V.A.T. **£18.50**

● **M6HL** Case 18" x 8" x 2 1/2"
12 inputs (6 high Z, 6 low Z). Carr. paid. + V.A.T. **£27.50**

Channel section modules, for building your own: gain-16 x (24dB). Tone controls-18dB swing. Carr. paid. + V.A.T. **£3.50**

CONTROL UNITS **£15.80**

Stereo Unit Carr. 30p

Mono (as shown) For 9v battery operation. As stereo mode less mic. input **£6.50**

Carr. 20p

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2" x 3" x 4" deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume. Microphone volume, bass, treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.**

Unbeatable for quality & value



SAXON DISCO MODULE

AKG MICROPHONES

World famous D.190C—the one the professionals use—at special bargain price of

£19.50 + V.A.T.

120 WATT HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120 watts into an eight ohm load and employs 4 TO3 can (115 watt) output transistors.

SPECIFICATION

Power output 120 watts into 8 ohms
Freq. response 20-20,000 Hz \pm 2dB
Input sensitivity 200 mV into 10K
Construction Fibreglass board
Size 8" x 4" x 4" (5" with supply)
Low distortion parallel push-pull output stage.

Module & power supply (Carr. 40p) **£18.95**

● 160 watt version with power supply **£27.90** (Carr. 50p)



3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls. 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Smartly finished steel case. Carr. 30p.

£19.75

SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3000 watts) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.


SINGLE CHANNEL UNIT

Operates from 5 to 100 watt amplifiers. Supplied for bass tone operation, is easily adapted for treble or mid-range at a cost of about 5p.

Carr. pd. **£8.90**

COMPLETE AMPLIFIERS CSE 100

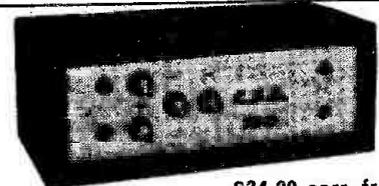The versatile unit is now available in a black vinyl case and so represents even better value than ever delivering speech and music powers of up to 100 watts RMS and continuous signal outputs of 70 watts. Two individually controlled inputs with wide range bass and treble controls.



£34.90 carr. free



SAXON 100

£48.50 carr. free

With an RMS output of 120 watts speech and music, 100 watts continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12" 25 watt 8/15 ohms **£5.95** carr. 30p 15" 50 watt 8/15 ohm **£14.50** carr. 50p.
12" 40 watt 15,000 gauss magnet system 8/15 ohm **£11.50** carr. 40p.

Prices subject to alteration without notice. E. & O.E.

V.A.T. Please add 10% to total value of order (inc. carr.) for Value Added Tax.

Please include S.A.E. with written enquiries.

TERMS OF BUSINESS

Cash with order (C.W.O.) For C.O.D. please add 35p extra; cash by regd. letter, please



GIRO NO. 331 7056
C.W.O. only. P. & P. 10p on orders below £5
Discount: £10-10%, £20-15% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments

ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS

10E12 1W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3.10 net
10E12 1W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3.20 net
25E12 1W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7.20 net
25E12 1W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7.35 net
20E12 1W KIT: 20 of each E12 value, 10 ohms—1M, a total of 1220 (METAL FILM 5%), £7.50 net
15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £8.15 net
10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £12.65 net

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3½p. 0.068µF, 0.1µF, 4½p. 0.15µF, 4½p. 0.22µF, 5½p. 0.33µF, 8p. 0.47µF, 9p. 0.68µF, 11p. 1µF, 15p. 1.5µF, 22p. 2.2µF, 25p.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2½p. 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3½p. 0.047µF, 0.068µF, 0.1µF, 4½p. 0.15µF, 6½p. 0.22µF, 8½p. 0.33µF, 12p. 0.47µF, 14p.
160V: 0.01µF, 0.015µF, 0.022µF, 2½p. 0.047µF, 0.068µF, 3½p. 0.1µF, 0.15µF, 4½p. 0.22µF, 5p. 0.33µF, 6p. 0.47µF, 7½p. 0.68µF, 11p. 1µF, 12½p.

MINIATURE CERAMIC PLATE CAPACITORS

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2½p. each. 0.1, 30V, 4½p., 0.1, 100V, 5½p.

POLYSTYRENE CAPACITORS 160V 5%

(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p. 6800, 10,000, 4½p.

RESISTORS

CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%.
W. Type Range 1.9 10.49 50.99 100.249 250.499 500.999 1000+ Size mm
¼ CF 22-1M 1 0.8 0.65 0.62 0.55 0.5 0.45 2.4x7.5
¼ CF 22-2M2 1 0.8 0.65 0.62 0.55 0.5 0.45 3.9x10.5
¼ CF 22-1M 1 0.8 0.65 0.62 0.55 0.5 0.45 5.5x16
¼ MF 10-2M7 1 0.9 0.8 0.7 0.65 0.65 0.6 3x7
¼ MF 10-2M2 1 0.9 0.8 0.7 0.65 0.65 0.6 4.2x10.8
¼ MF 10-10M 1.5 1.25 1.25 1.1 1 0.95 0.88 6.6x13
2 MF 10-10M 3 2.5 2.5 2 1.75 1.75 1.6 8x17.5

For value mixing prices, please refer to our catalogue. (price in pence each)
VALUES AVAILABLE—E12 Series only.

PRESET SKELETON POTENTIOMETERS

MINIATURE 0.25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1MΩ
SUB-MIN 0.05W Vertical, 100Ω to 220KΩ 5p each

(P.W.) 61 CHEDDINGTON ROAD, PITSTONE,
NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ
Tel.: Cheddington 668446 (Std. Code 0296)
PLEASE WRITE FOR FREE CATALOGUE

B. H. COMPONENT FACTORS LTD.

Miniature Mullard Electrolytics

1.0µF 63V	5p	68µF	16V	6p
1.5µF 63V	5p	68µF	63V	12p
2.2µF 63V	5p	100µF	10V	6p
3.3µF 63V	5p	100µF	25V	6p
4.0µF 40V	5p	100µF	63V	14p
4.7µF 63V	5p	150µF	16V	6p
6.8µF 63V	5p	150µF	63V	15p
8.0µF 40V	5p	220µF	6.4V	6p
10µF 16V	5p	220µF	10V	6p
10µF 25V	5p	220µF	16V	8p
10µF 63V	5p	220µF	63V	21p
15µF 16V	5p	330µF	16V	12p
15µF 63V	5p	330µF	63V	25p
16µF 40V	5p	470µF	6.4V	9p
22µF 25V	5p	470µF	40V	20p
22µF 63V	5p	680µF	16V	15p
32µF 10V	5p	680µF	40V	25p
33µF 16V	5p	1000µF	16V	20p
33µF 40V	5p	1000µF	25V	25p
32µF 63V	5p	1500µF	6.4V	15p
47µF 10V	5p	1500µF	16V	25p
47µF 25V	5p	2200µF	10V	25p
47µF 63V	5p	3300µF	6.4V	26p

VEROBOARD 0.1 0.15

21 x 5"	28p	28p
41 x 5"	26p	19p
3½ x 5"	32p	33p
2½ x 3½"	28p	29p
2½ x 1"	7p	7p
2½ x 5" (Plain)	—	12p
2½ x 3½" (Plain)	—	12p
5 x 3½" (Plain)	—	22p
Insertion tool	59p	59p
Track Cutter	44p	44p
Pins, Pkt. 25	10p	10p

TRANSISTORS

AC127	16½p	BC212L	12p
AC128	22p	BC213L	12p
BC107	11p	BC214L	17p
BC108	12p	OC44	18p
BC109	13p	OC71	13p
BC148	12p	OC81	16p
BC149	12p	OC170	23p
BC182L	12p	TIS43	33p
BC183L	12p	2N2926	11p
BC184L	13p	2N3702	11p

POTENTIOMETERS

Carbon Track 5KΩ to 2MΩ, log or lin. Single, 16½p Dual Gang 46p. Log Single with switch 26p
Slider Pots. 10K, 100K, 500K. 30mm, 34p. 45mm, 47p. 60mm, 53p.

DIODES

IN4001	6½p
IN4002	7½p
IN4003	9p
IN4004	9p
IN4005	12p
IN4006	14p
IN914	7p
IN916	7p
BA100	10p
OA5	42p
OA47	9p
OA81	11p
OA200	8p

Integrated Circuits

µA709C	50p
µA741C	55p
µA723C	£1
µL914	35p

PLUGS

DIN 2 Pin	12p
3 Pin	13p
5 Pin 180°	15p
Std. Jack	14½p
2.5mm Jack	11p
Phono	5½p

SOCKETS

DIN 2 Pin	10p
3 Pin	10p
5 Pin 180°	12p
Std. Jack	14½p
2.5mm Jack	11p
Phono	5½p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans

(µF/V): 2-2/25, 2-2/63, 4-7/10, 4-7/25, 4-7/53, 22/10, 22/25, 22/63, 5p. 2/10, 10/10, 50/10, 100/10, 10/25, 50/25, 10/50, 5p. 200/10, 100/25, 50/50, 6½p. 500/10, 200/25, 100/50, 9p. 1000/10, 500/25, 200/50, 11p. 2000/10, 1000/25, 500/50, 16½p. 1000/50, 39p. 1000/100, 66p. 2000/25, 27p. 2500/12, 17p. 2500/25, 33p. 2500/50, 62p. 3000/50, 72p. 5000/25, 66p. 5000/50, 94p. 7000/50, 60p. 25,000/25, 74p. HI-VOLT: 8/350, 14p. 16/350, 19p. 32/350, 25p. 50/250, 18p. 100/500, 33p.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF 4½p. 0.25µF, 5½p. 0.5µF, 6½p. 1µF, 9p.
500V: 0.025µF, 0.05µF, 4½p. 0.1µF, 5½p. 0.25µF, 6½p. 0.5µF, 9p.
1000V: 0.01µF, 10p. 0.022µF, 12p. 0.047µF, 0.1µF, 16p. 0.22µF, 31p. 0.47µF, 39p.

QUANTITY DISCOUNT

SPECIAL BULK BUY PRICES ARE AVAILABLE BY QUOTATION FOR LARGE PROJECTS AND TRADE



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

Free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY


NAME: _____
ADDRESS: _____
WB14
BLOCK CAPS please

FELSTEAD ELECTRONICS (PW76)

LONGLEY LANE, GATLEY, CHEDDLE, CHESHIRE, SK8 4EE

RECORDING TAPE: BEST BRITISH MYLAR 5" 600ft-40p. 5½" 900-55p. 7" 1200-62p. 5" 900ft-55p. 5½" 1200-62p. 7" 1800-£1.00. (Charges: 5 & 5½", singles 10p. 2 to 4, 9p each. 5 and over, 33p the lot). 7" 1 and 2, 11p each. 3, 4 and 5, 33p the lot. 6 and over 39p lot).
CARTRIDGES with fittings and Styli. Mono-Stereo compat GP91/SC-98p. Stereo GP93-£1.35. Stereo Ceramic GP94-£1.75. X5M-£1.25. SX5M-£1.60. X5H-£1.25. SX5H-£1.55. TC8H-£1.40. TC8S-£2.00. SONOTONE 9TAHC (Ceramic, diamond) £1.70. (All cartridges, 8p each).
STYL Single tip, for Aeos GP37, GP58, GP65/67 and GP71. Collar 'O'. GARRARD GC2, GC8, GCE12, GCS10. RONETTE BF40, DC284, PHILIPS 3801/2/3/4/5, 3060, 3063, 3220, 3010/12/13/25, 3016, 3019, GP316. SONOTONE 19T/20T. All at 85p. DIAMOND, 16p SAPPHIRE.
Two-tip Turn-over for ACOS GP73, GP91 (for stereo cart'ges GP93, 94, &c.) GP91SC for mono-stereo compat, types, GP104, BSR ST3, ST4, ST5, ST8, ST9, ST10 ST12, ST14, ST15, ST16, ST17, GARRARD GCM21, 22, 24, GCS23, GKS25 and GKS26, GCM21T/22T/24T, GCS23T, GKS25T/26T, GCS35/36, 2509, KS40A, 3549, 3559. PHILIPS 3306, 3310, GP310, 3230, 3228, GP228, SONOTONE 2T, 3T, STA, 9TA, 9TAHC. ALL available in SAPPHIRE ST/LP + 78. ST/LP + ST/LP both at 82p. DIAMOND ST/LP + Sapp. 78 at 65p, and DIAMOND ST/LP + DIAMOND ST/LP (Double Diamond) at £1.20. GOLDRING DIAMOND G800, G800H and G850 at £2.25 also G800E at £3.75. SHURE, DIAMOND N55/E-£3.83 and others incl. PICKERING. (Charges all styli 9p up to three).
PICK-UP WIRE, Super-thin, flex, scrd. sheathed 2-Core 7p and 4-core 13p per yard. (Up to 6, 8p).
MICROPHONES. LAPEL 1½" dia. Lead + 3.5mm plug 39p (9p). MIC 45, Curved metal grip £1.10 (12p). DYNAMIC Cassette type, black/chrome 50K, switch, Lead with 2.5 and 3.5mm plugs (remote control £1.37 (11p)). MANY MORE SPLENDID MIKES, Crystal, Cardioid, Magnetic, condenser, full details in LIST.
SPEAKERS. 12", fitted tweeter, 3, 8 or 15 ohms, (state which), 6 watts undistorted, £2.10 (37p) or pair for stereo at

£4.65 charges paid. 2½", 3, 8 or 64 ohm (state which) at 50p (9p). More in list.
EARRPIECES. Magnetic, with 2.5mm or 3.5mm plug on lead 12p. CRYSTAL (with 3.5 plug only) 30p. (ALL up to 6 for 9p).
HEADPHONES. High resistance, 2000 ohms, adjustable, £1.15 (15p). (MANY STEREO types in list).
SOLDERING IRON. Slim mod. Brit. high speed. 8½", high quality, all parts replaceable, £1.29 (11p).
TRANSFORMERS. Sub-min, 11 x 11 x 12mm OUTPUT, (30 ohm for OC72, &c. 16p, or DRIVER 17p (up to 12 for 9p)).
CONNECTING WIRE. Packs of 5 coils, asstd. cols. ea. coil 5 yds. Solid core 16p (8p). Flexible Core 18p (10p).
VIBRATORS 12v/4 pin Non-synch. 121HD4, 2½" ex pins 33p. Same but 3½" ex pins, USA 16p, 12v/7 pin SYNCH. (12SR7 type) 72p (any type 9p).
ELIMINATORS for use with most cassette recorders and players, sets, &c. Mains input 240V. AC, front switch, pilot lamp, leads output 3, 6, 7½ and 9v. 400 mA, stabilised Model SC with multi output adaptor £5.50 (30p). Model NR, extra 12v. output, and 500mA £6.00 (30p).
We supply all types of British and Continental **PLUGS, SOCKETS and LEADS**, detailed in our LIST, as are many more of all above items, also cartridge and stylus comparisions, non-repeatable special offers, aerial rods, CASSETTES, TAPE & GRAM, accessories, cleaners, &c., dials, transistors, volume controls, Neons, indicator lamps, multi-meters and other test equipment, pocket screwdriver testers, Telephone puch-ups, amplifiers, wire, cable, terminals, Test Prods, Vero-board, Valve holders and many more components and accessories at lowest prices. TRADE quantity enquiries invited on several items.
Our list is supplied free if requested on an order or sent against a stamped addressed envelope (also required for replies for all enquiries). CHARGES are shown in brackets after all items. CASH WITH ORDER ONLY. PRICES INCLUDE VAT, and charges apply to UK and EIRE only. Overseas purchasers can deduct 10% from all prices shown but postage is required. This includes Eire and the Channel Isles.

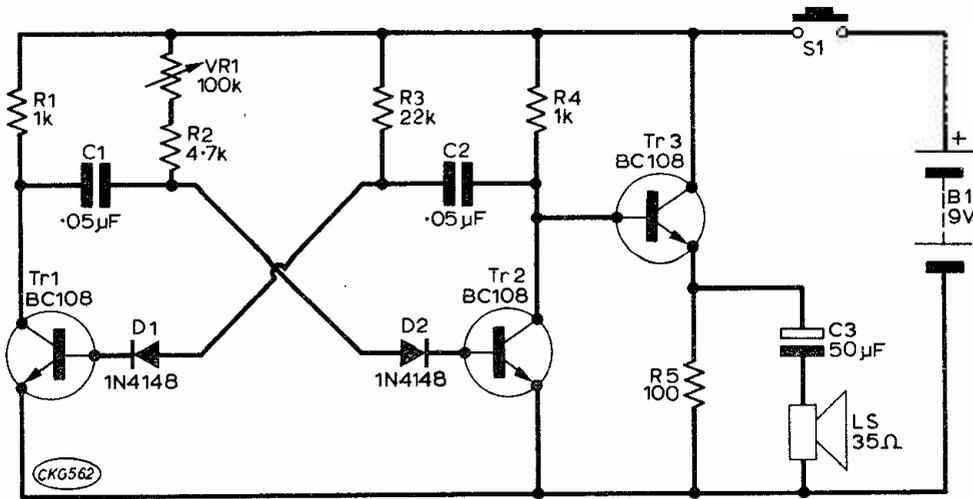

◀ Fig. 25: Variable frequency astable multivibrator. In conjunction with S1 a melodic scale can be produced by adjusting VR1. For a wider frequency range substitute a ganged potentiometer and another 4.7kΩ resistor for R3.

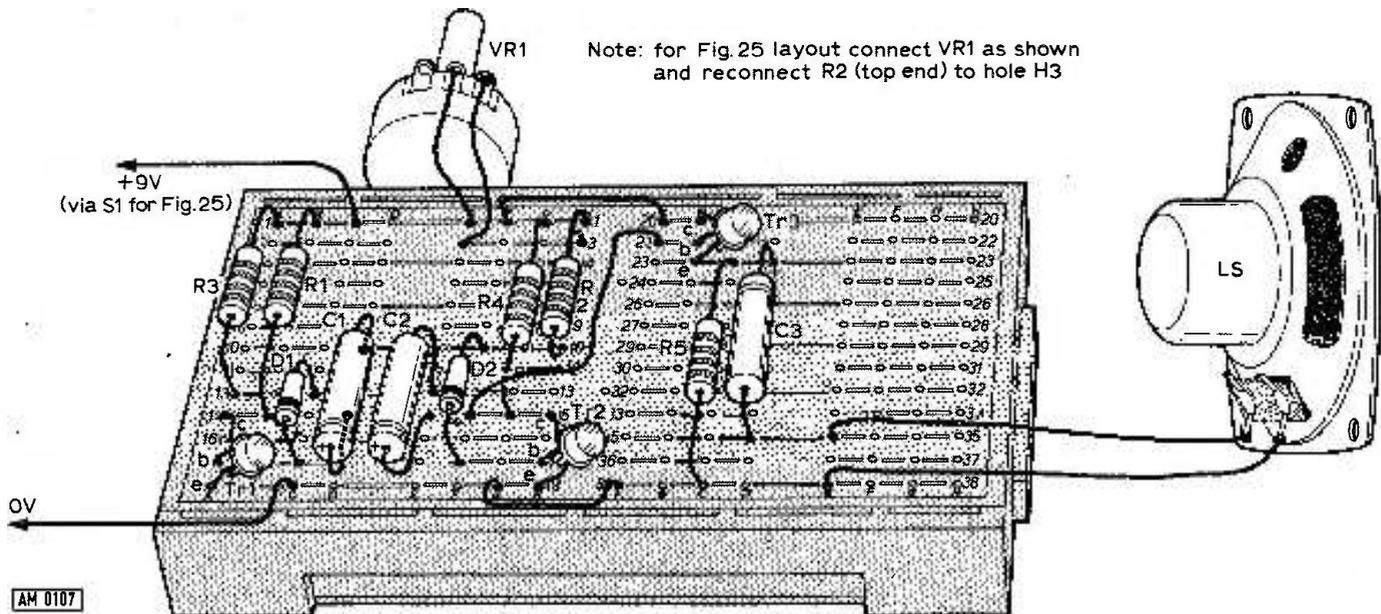


Fig. 26: Layout for Fig. 24. For Fig. 25 layout see note (above).

factors that set the extreme values for R2 (or for that matter R3) are the maximum base current that is safe to pass into the transistor (thus do not reduce either of them below 1kΩ) and the minimum base current that will ensure the respective transistor will switch on completely so do not use values greater than about 200kΩ.

You can couple the output signal from point A into any of the lamp drivers we have already described—we show one possibility in Fig. 22. By adjustment of the timing resistors (R2 or R3 or both) you can make a simple repetitive lamp flasher.

Tone generator

To change the range of operating frequency there is the further possibility of different values for C1 and C2. Fig. 24 shows an identical circuit that operates within the audio range. One cannot use a meter or a lamp to monitor the output this time because they do not have a fast enough response; however we can use our emitter follower as a simple loudspeaker driver with the aid of an extra resistor and capacitor. The circuit now becomes a tone

generator and could be used for morse code practice if a key was inserted into the supply rail.

One of the timing resistors could be changed for a variable potentiometer (it is preferable to keep a small value of fixed resistance in circuit to prevent damage to the base emitter junction of the transistor) as shown in Fig. 25. With a push button in the supply line one can make a rudimentary form of organ; the tone being selected by means of the potentiometer and the button pressed to produce the note—obviously some skill is required to produce anything melodic! A wider range of frequency with unity mark space ratio can be obtained if a ganged pair of potentiometers was used to replace both timing resistors.

Simple organ

For the more ambitious one could substitute a set of preset resistors for one of the timing resistors and have keys which connect each preset up to the positive rail. When a key is pressed a tone set by that particular resistor will be produced. Obviously

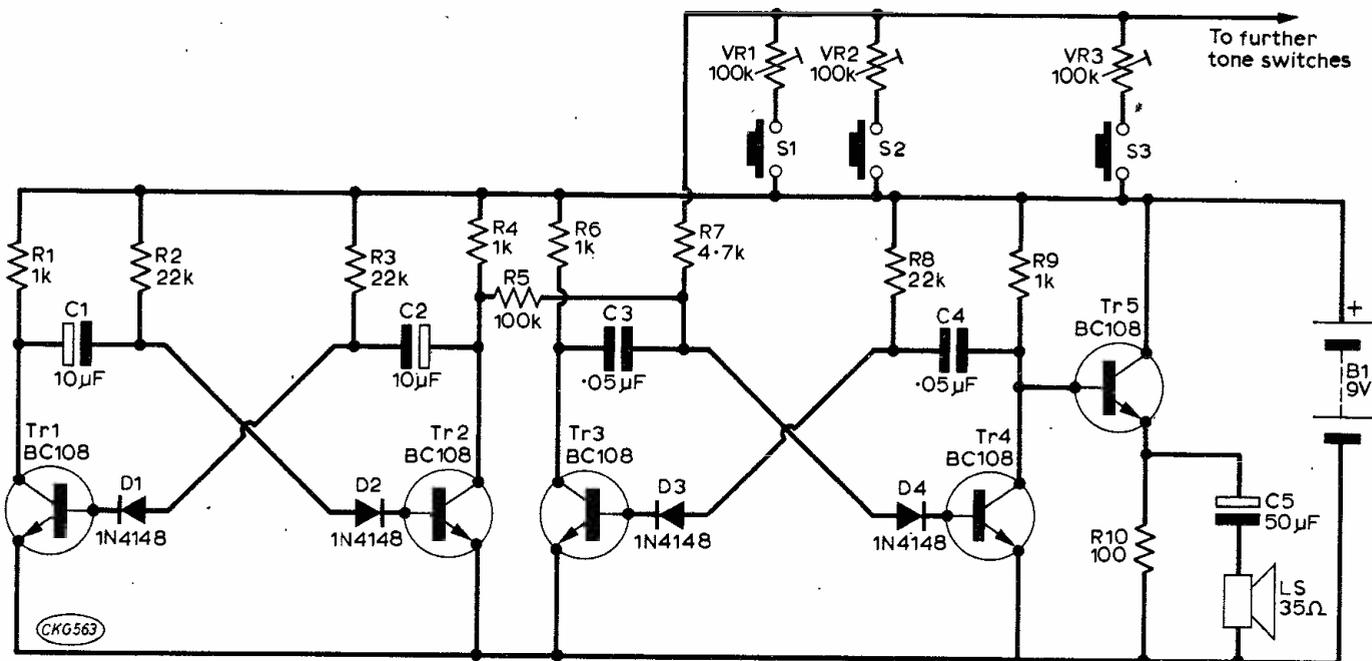


Fig. 27: Circuit for a simple monophonic organ. As long as R5 is in circuit the slow running multivibrator provides a degree of vibrato to the audio generator.

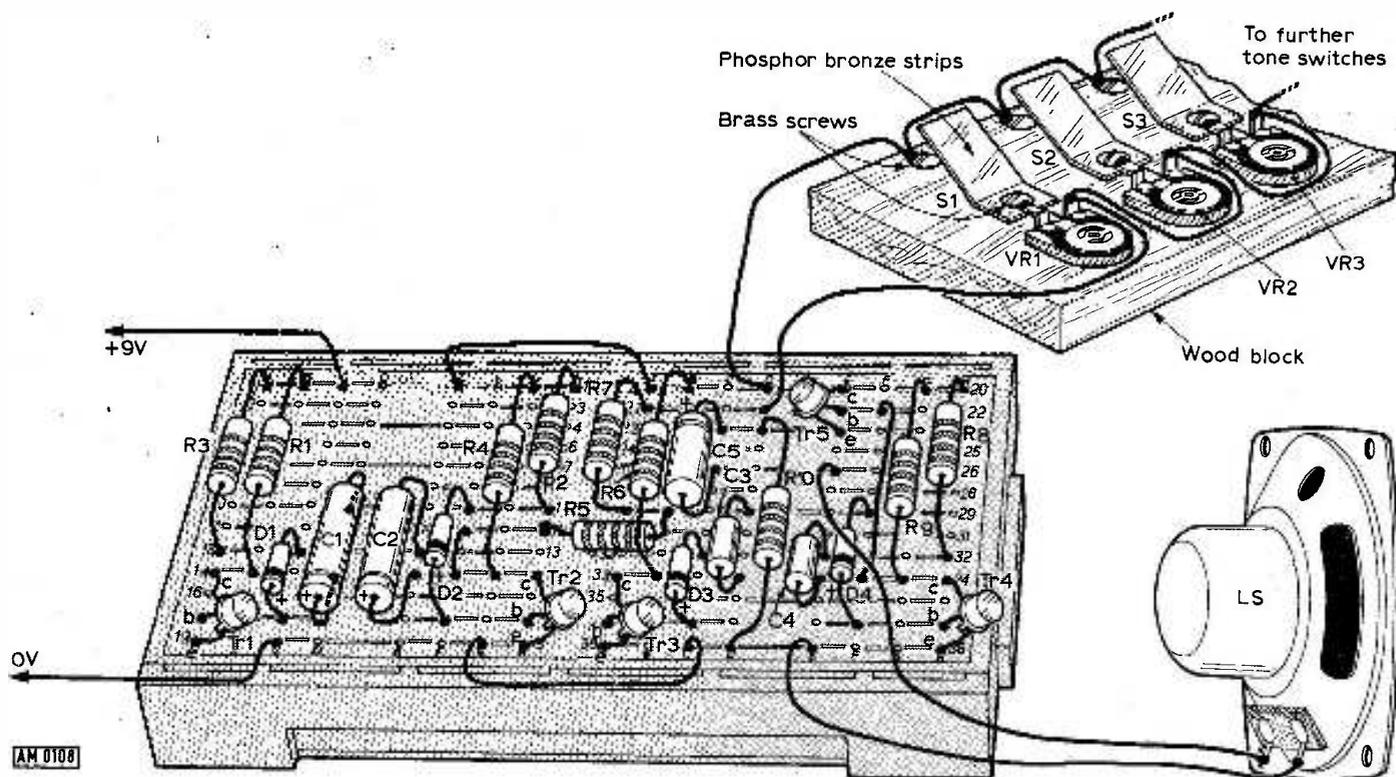


Fig. 28: Layout for Fig. 27.

only one note at a time could be generated but with careful selection and adjustment of these presets one can make a very effective little solo instrument.


To wind up this month you could experiment by adding vibrato (of sorts) to the tone generator. This is done with the help of the low speed astable similar to that described earlier. We use the signal at its output to modify the discharge rate of one of the capacitors in the tone generator circuit and if this is done at a rate of about 6Hz quite an effective vibrator (or warble-tone) can be produced. We show a working circuit for the latter two suggestions in

Fig. 27. Of necessity we have not shown a complete range of notes nor have we given full details of a keyboard but the suggested sketch (Fig. 28) which uses phosphor bronze door strip and brass screws could be used as the basis for experiment. There is no limit to the number of notes that can be set—all it requires is investment in the form of preset potentiometers. Remember, though, that you can only get a single note from the instrument at a time!

Next month we shall look at some amplifier circuits.

IN NEXT MONTH'S PRACTICAL WIRELESS

3 STAR PERFORMERS!

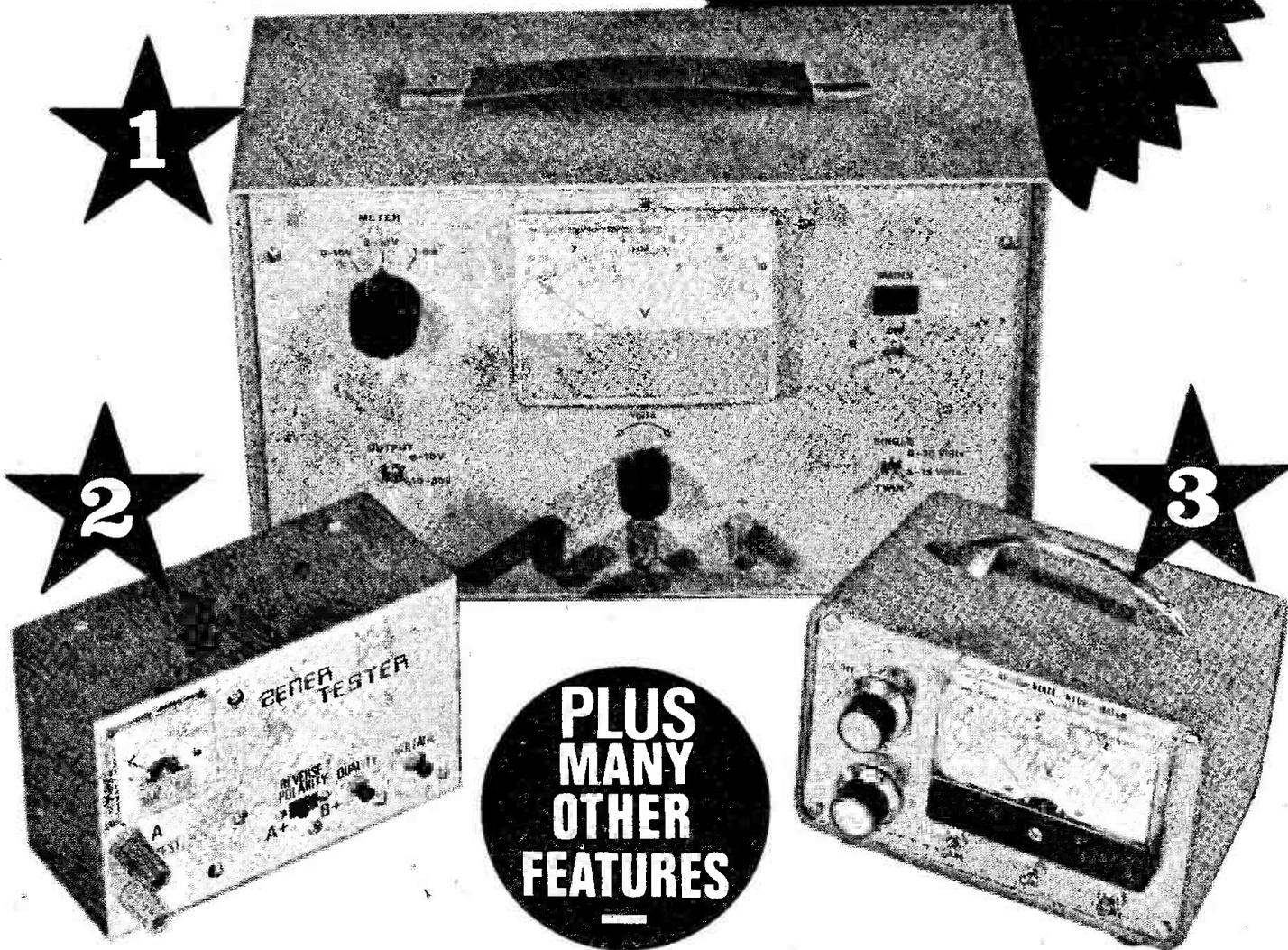

**PLUS
MANY
OTHER
FEATURES**

1 BENCH STABILISED POWER SUPPLY

When experimenting in the workshop a well stabilised variable voltage DC power supply is absolutely essential. Switched ranges on this unit provide 0 to 10 volts, 10 to 30 volts as well as a balanced 5 to 15 plus 5 to 15 volt output, all at a maximum current of one ampere. A switchable panel meter continuously monitors output voltage or current. Full constructional details are given to enable you to make this desirable piece of equipment without the problems of hard-to-get components.


2 ZENER DIODE TESTER

With zener and other types of diode now commonly available in lots of 100 or more it is a good idea to have on hand a test meter to sort out the dud and dodgy ones!

3 SOLID-STATE STOP-WATCH

Once calibrated the meter on this unit will indicate elapsed time, in three switched scales of 5, 15 and 50 seconds at full scale. With the low current consumption the unit's internal battery will last a long time. Readout to 0.05 seconds is possible on the lower ranges.

**FEBRUARY ISSUE ON
SALE 4th JANUARY**

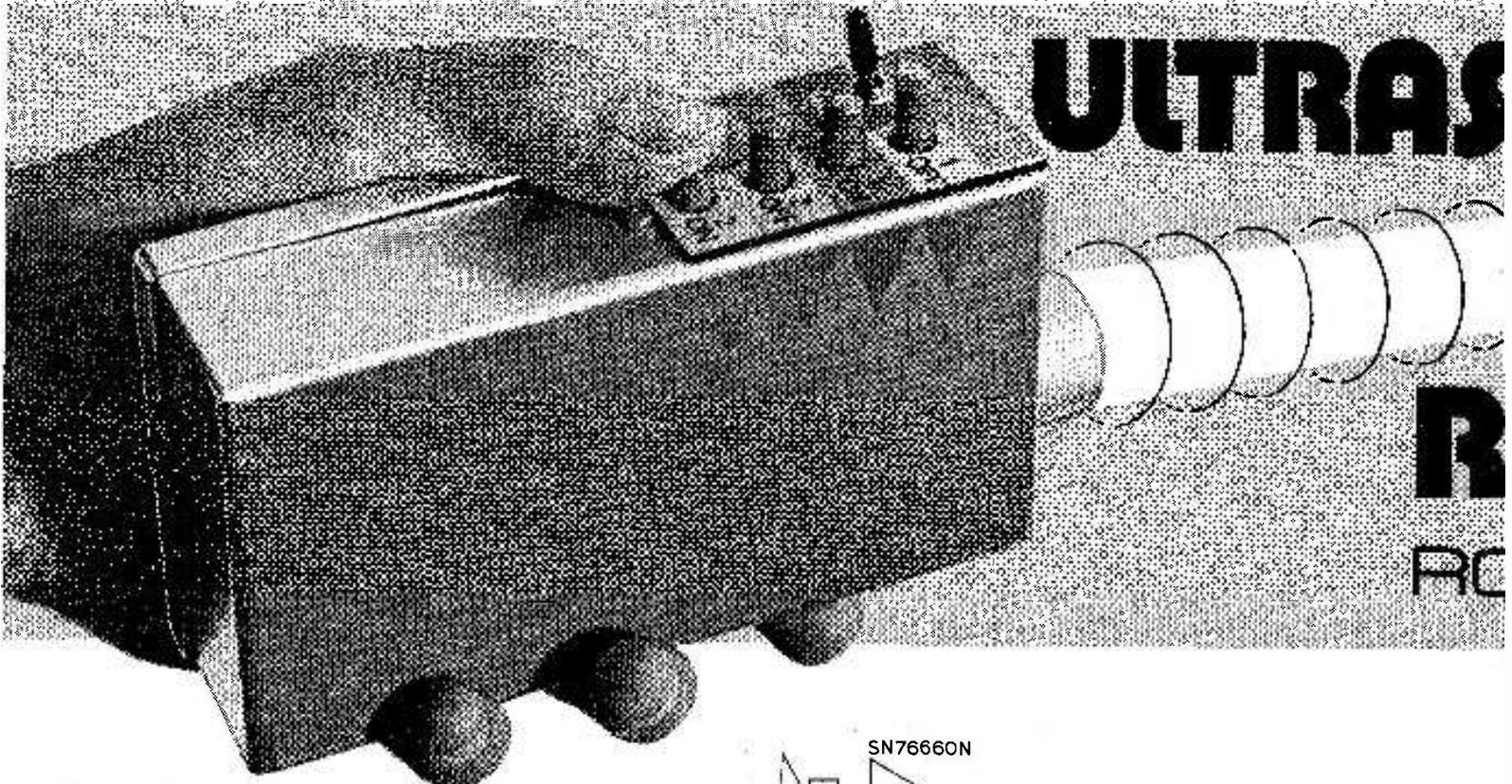

PART 1

REMOTE 'wireless' instigation of various functions is very largely associated with radio as a medium for transmitting the information. Here, the medium is ultrasonic sound eliminating the need for an MPT licence and providing some degree of system 'security'—that is, until everyone in your neighbourhood begins to appreciate the tremendous scope of remote command, and ultrasonic channels become just as full of those on VHF. Apart from the carrier medium, the rest of the system is very largely applicable to various forms of radio control. No doubt the model enthusiasts amongst the readers will quickly spot the potential.

The intelligence is transmitted by means of various tones which are frequency modulated upon the ultrasonic carrier; the heart of the system is the NE567 phase locked loop tone decoder modules. The 567 is an eight pin DIP IC containing about 110 components, and in order to programme the frequency and bandwidth, a further eight resistors and capacitors are necessary. Each decoder section is constructed along modular lines, so that they can be used as building blocks for larger and more sophisticated systems.

OPERATIONAL THEORY

The decoder firstly has to receive and demodulate the ultrasonic carrier. A SN76660N FM IF integrated circuit, Fig. 1(a), is used to amplify the transducer output to a level that will operate the first of the NE567 decoders, whose frequency is set at 40kHz (i.e. that of the transducer). This allows for the first, and the simplest, of the command functions. It means that the on/off control of some device can be controlled by means of the transmission of the 40kHz, unmodulated carrier. As long as the carrier is present, the output from the tone decoder is activated.

However, the system is extended greatly by the next sections which are the individual command tone

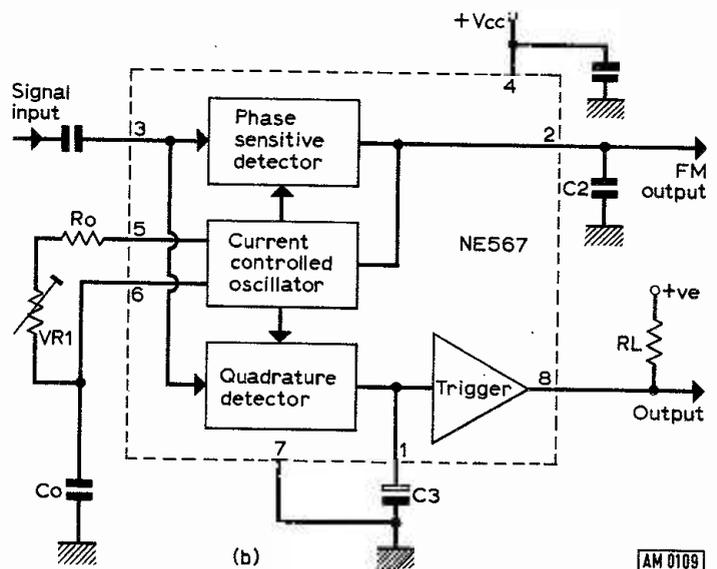
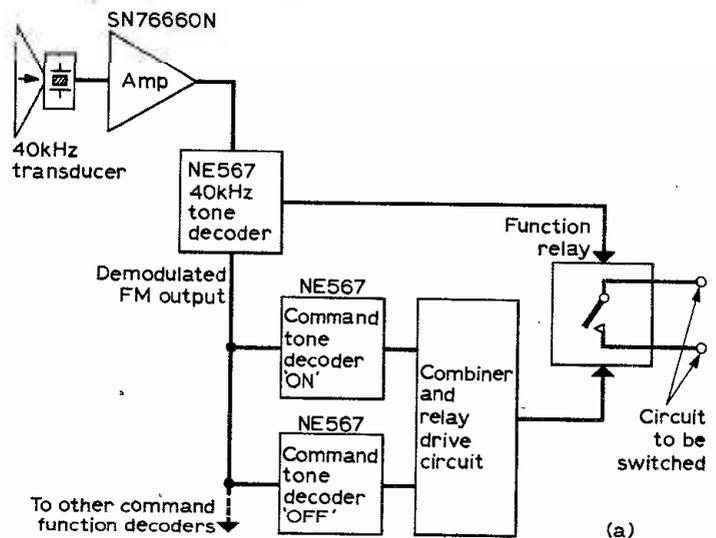


Fig. 1 (a) top, function diagram of the remote controlled receiver with a single function switched by a relay.
Fig. 1 (b) bottom, identifies the functions performed by a single NE567 command tone decoder.

SONIC

REMOTE CONTROLLER

AND PERRY

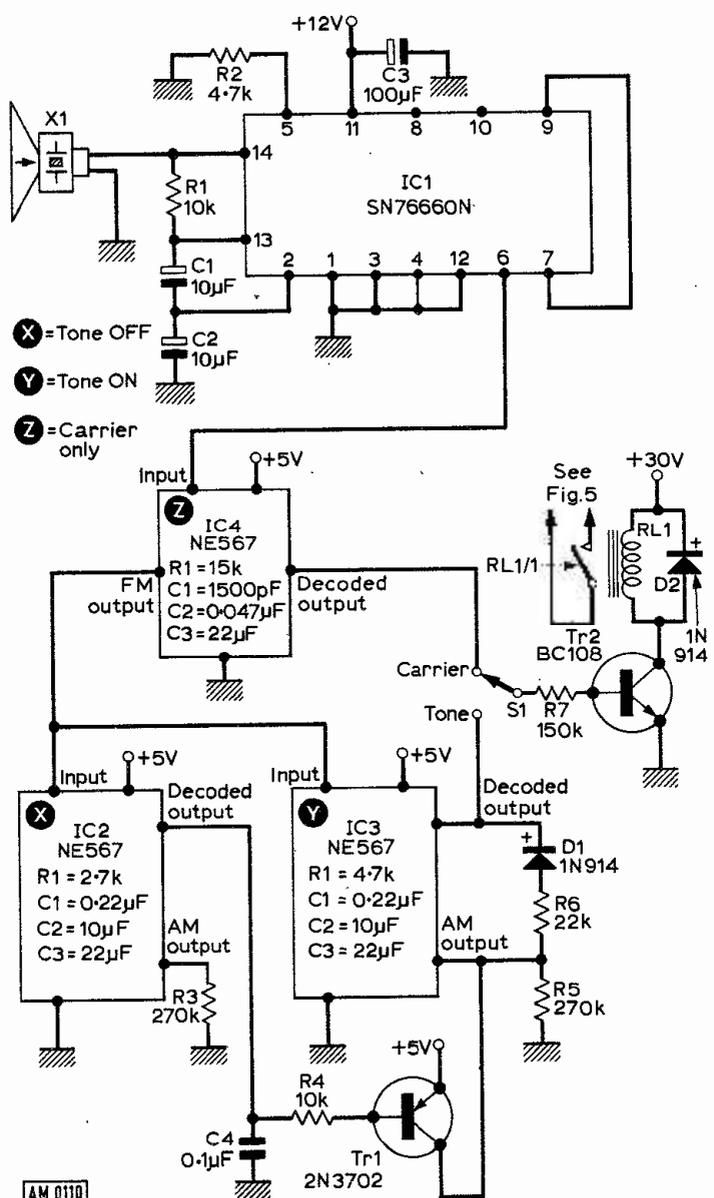


Fig. 2. Interconnection of the IC's comprising the complete receiver for one function. This can be operated only when the carrier is present or switched on with carrier plus tone Y or switched off with carrier plus tone X. The choice of operation is selected by switch S1.

decoders, Fig. 1(b). These are fed from the FM output of the 40kHz decoder, and operate from any number of assorted tones from 200Hz to 1kHz, with a 4% channel spacing. This means that a single ultrasonic carrier can be used to carry many different channels of command, and by combining two or three tones in sequence, the combinations are almost limitless. However, this article will confine itself to the simple single tone command signals, since multi-tone sequential systems require a good deal of test gear to set up properly.

THE RECEIVER

The receiver, Fig. 2, employs the two modes of operation mentioned here, namely carrier, or tone-on-carrier. In the carrier-only mode, the decoder output from the carrier detector drives the relay switch, in this case a BC108. Do not forget to include the diode across the coil to prevent inductive surges from destroying the transistor.

In the tone-on-carrier mode, the FM output of the ultrasonic receiver drives two further decoders tuned to the desired tone frequency. The 'ON' tone decoder 'Y', is operated in latching mode. As soon as an input is detected pin 8 is grounded, and the AM output is held low by the external diode and 22kΩ resistor. In order to unlatch the 'ON' decoder, the 'OFF' decoder has to be activated by its appropriate tone, whereupon the 2N3702 transistor pulls the output of decoder Y up to 5V, and releases it. The relay switch now reverts to 'OFF'.

The 270kΩ resistors speed up the response time, and increase sensitivity, while the 0.1μF capacitor in the unlatch loop prevents the 'ON' decoder from latching, when the circuit is activated.

To most people, FM is now synonymous with VHF broadcasting, so when thinking about the receiver section, it was decided to try out one of the many FM IF IC's. Despite the fact that it is designed with 10.7MHz in mind, the SN76660N performed admirably at 40kHz, and was therefore adopted.


Only the limiting amplifier sections are employed, since the detection is carried out in one of the tone decoder modules detailed later. Whilst there is no

objection to using the quadrature detector on the IC, it cannot provide the carrier presence facility available on the tone decoder.

Again, it will be seen that IC technology 'takes the strain', since the ultrasonic receiver itself needs only the IC, two resistors and three capacitors. The much amplified output is then fed into the tone decoder module.

TONE DECODER MODULE

The free running frequency of the PLL is determined by the values of C1 and R1+VR1, Fig. 3. A table of the more useful values is provided for quick reference, Table A.

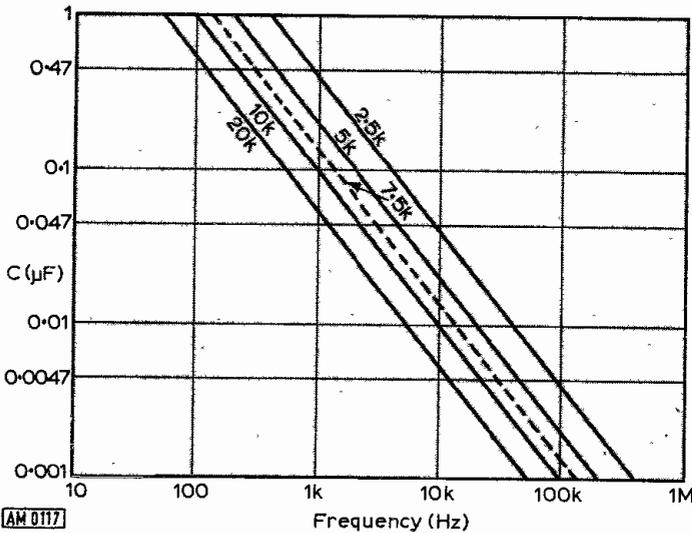

AM 0117

µF	2.5kΩ	5kΩ	7.5kΩ	10kΩ	20kΩ
1.0	400Hz	200Hz	(133Hz)	100Hz	50 Hz
0.47	850Hz	425Hz	(280Hz)	212Hz	106 Hz
0.1	4kHz	2kHz	(1.33kHz)	1kHz	500 Hz
0.047	8.5kHz	4.25kHz	(2.8kHz)	2.12kHz	1.06kHz
0.01	40kHz	20kHz	(13.3kHz)	10kHz	5kHz
0.0047	85kHz	42.5kHz	(28kHz)	21.2kHz	10.6kHz
0.001	400kHz	200kHz	(133kHz)	100kHz	50kHz

Table A. Values of C and R determining the tone decoder frequency. Values for other frequencies may be determined from the graph above. See Fig. 3.

The PLL will lock on to an input whose frequency lies within the loop capture range. As we wish to vary the detection bandwidth the simplest way is to programme the capture range. The single capacitor C2 determines the bandwidth, and being part of the feedback low pass filter, it also provides a demodulated output for the FM tone. Again, a table of recommended values is provided for quick reference, Table B.

In order that the loop can detect AM, or merely the presence of a carrier, the input is mixed with the locked VCO frequency, but shifted through 90°, in a simple quadrature mixer. Pin 1 of the NE567 provides the AM signal, which, if it exceeds a certain value, then switches the output driver stage at pin 8. This then drives pin 8 low in the presence of signal within the capture range of the IC.


The capacitor C3, at the output of the AM detector, is determined from a consideration of the speed of the response of the loop, and its immunity to spurious triggering. Unfortunately, the one is at

the expense of the other, so some form of compromise needs to be reached, and the recommended value is that C3 should be about twice the value of C2.

The input is capacitively coupled, since there exists an internal arrangement for the input stage bias voltage. The capacitor C5 is chosen to have a low impedance at the desired frequency.

The decoder gives optimum results with an input in excess of 200mV, but it will operate at lower levels, at the expense of the bandwidth. The degradation of the bandwidth is typically to 10% at 200mV, 7% at 100mV and 5% at 20mV.

Decoupling of the supply is necessary to smooth out the fast edges of the switch transients in the decoder and this is provided on the module. Although

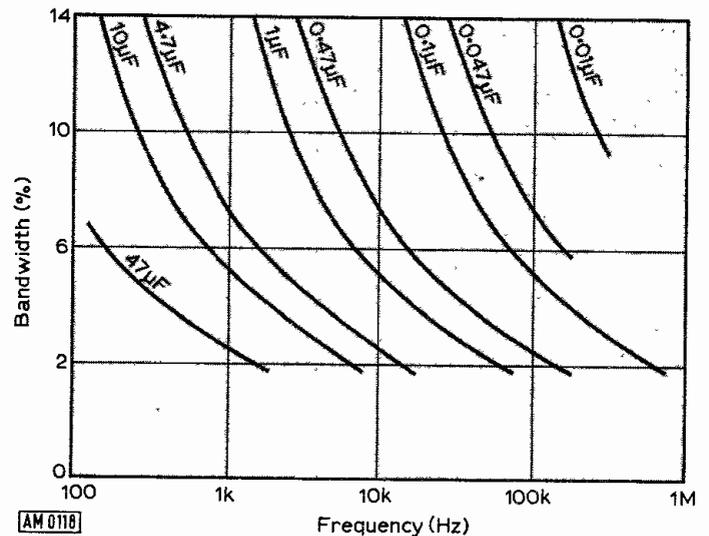

AM 0118

µF	Bandwidth			
	2%	6%	10%	14%
0.01	—	—	260kHz	130kHz
0.047	—	150kHz	55kHz	28kHz
0.1	620kHz	73kHz	26kHz	13kHz
0.47	130kHz	15kHz	5.5kHz	2.8kHz
1.0	62kHz	7.3kHz	2.6kHz	1.3kHz
4.7	13kHz	1.5kHz	550 Hz	280 Hz
10.0	6.2kHz	730 Hz	260 Hz	130 Hz
47.0	1.3kHz	150 Hz	—	—

Table B. Values of capacitor C2 setting the bandwidth or loop capture range. The graph enables intermediate values to be determined. See Fig. 3.

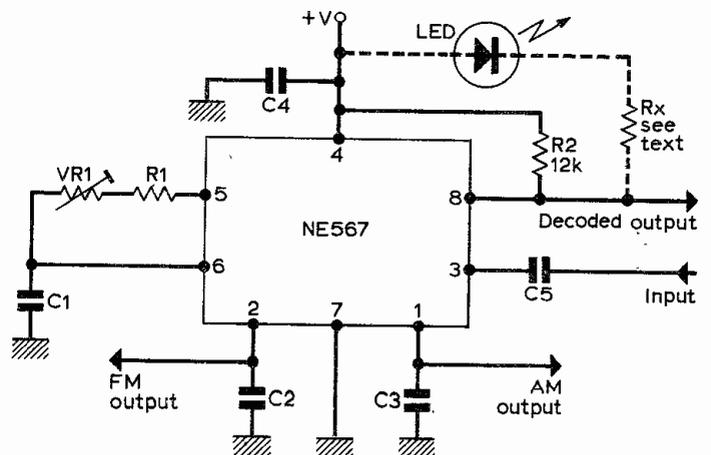


Fig. 3. Basic circuitry of a tone decoder module illustrating the components which fix the operating frequency. The LED is optional, see text.

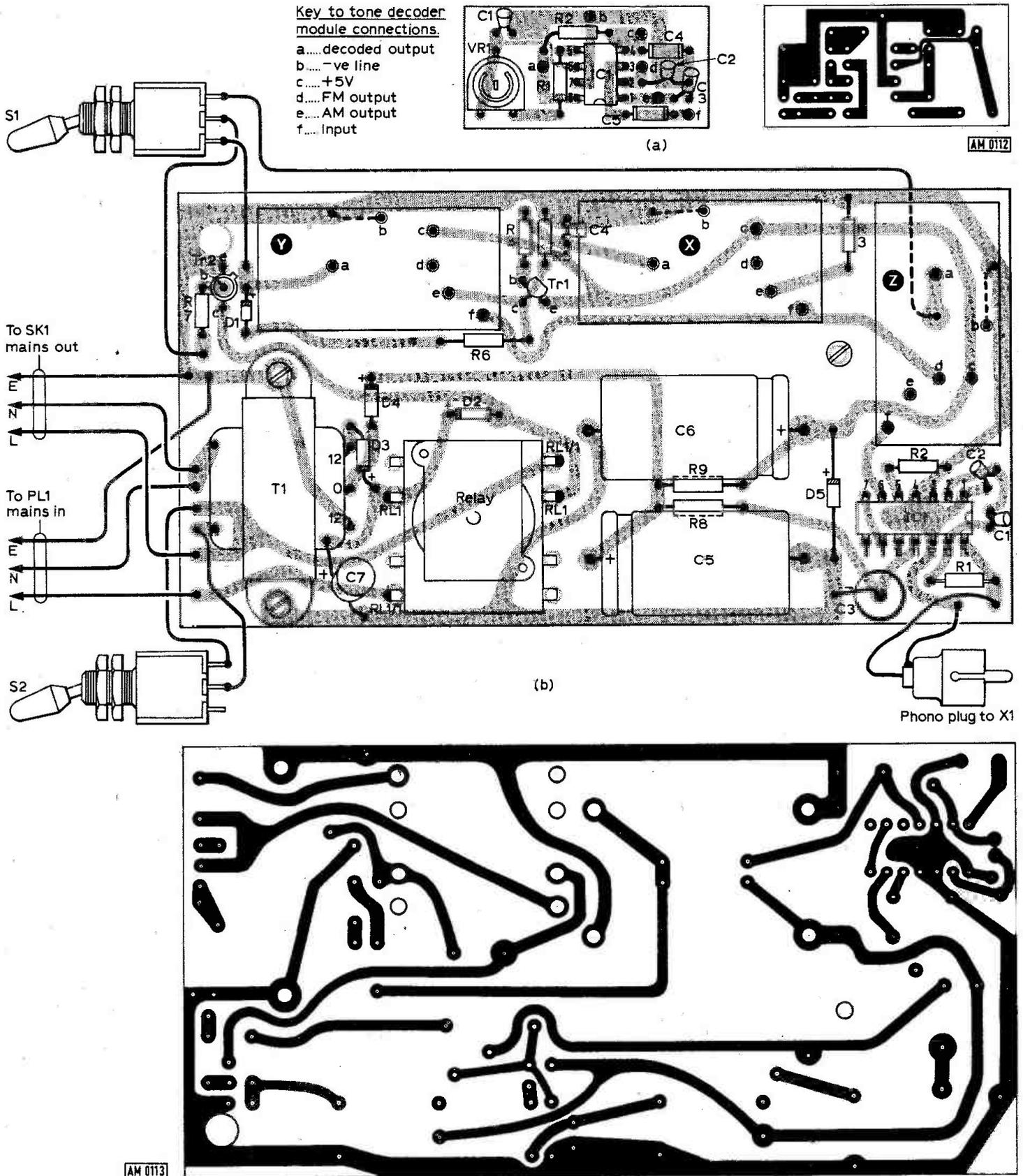


Fig. 4 (a) top, full size copper foil layout of a tone decoder pcb and component location. Three of these are required for one function. Certain component leads are extended below the board to mate with holes in the main receiver pcb, Fig. 4 (b), bottom. Note that the power supply circuitry of Fig. 5 is included on this pcb which is also full size.

it is desirable that the supply be regulated, the tone decoder frequency is not too closely voltage dependent.

The printed board layout of the module is shown in Fig. 4a, and the leadout connections, in the example shown, are by means of short pins soldered to the reverse side. The pins can simply be the cutoffs from

resistor leads, since these provide quite adequate rigidity when mounted to the larger board of the system, Fig. 4b.

The PLL free running frequency must be set to the frequency to be decoded, in order to obtain a symmetrical bandwidth i.e. a 10% bandwidth represents 5% high and 5% low. If the tone is in

★ components list

RECEIVER AND POWER SUPPLY

R1 10kΩ	R4 10kΩ	R7 150kΩ
R2 4.7kΩ	R5 270kΩ	R8 10Ω
R3 270kΩ	R6 22kΩ	R9 120Ω
C 10μF 16V tantalum	C5 1000μF 18V	
C 10μF 16V tantalum	C6 1000μF 18V	
C3 100μF 25V electrolytic	C7 22μF 35V	
C4 0.1μF 18V tantalum		
Tr1 2N3702	Tr2 BC108	
D1/2 1N914	D3/4 1N4001	D5 5-V zener
	IC1 SN76660	

Miscellaneous

RL1, relay 30V, SP on/off minimum, see text.
 S1, miniature SP changeover. S2, miniature on/off.
 X1, transducer 40kHz (Ambit), plus phono plug connector.
 T1, transformer 240V/12-0-12V. Aluminium box and lid, 5½ x 3 x 1½ in approx. (Type AB7).
 PCB, 5½ x 2½
 Cable, 3 core, as required with mains plug and cable-end socket.

tone decoder modules

MODULE	X	Y	Z
R1	2.7kΩ	4.7kΩ	15kΩ
C1	0.22μF	0.22μF	1500pF
C2	10μF	10μF	0.04μF
C3	22μF	22μF	22μF

C4 0.1μF R2 12kΩ
 C5 0.047μF Rk } see text
 VR1 2.5kΩ miniature preset LED
 IC2/3/4 NE567 PCB's 1½ x 2½ in. (3)

TRANSMITTER


R1 5.8kΩ	R4 150kΩ	R7 33kΩ
R2 10kΩ	R5 18kΩ	R8 1.2kΩ
R3 390Ω	R6 1.2kΩ	R9 12kΩ
VR1 25kΩ	VR2 10kΩ miniature pre-sets	
C1 0.1μF polycarb.	C5 1000pF disc ceramic	
C2 10μF tantalum	C6 47μF 25V electrolytic	
C3 0.1μF polycarb.	C7 10μF tantalum	
C4 0.22μF tantalum		

Miscellaneous

IC1/2, NE555, S1/4, 4-button switch assembly (Ambit)
 X2, transducer 40kHz plus phono plug connector (Ambit). Aluminium box type AB7, PCB, 3½ x 2½ in.
 S5, miniature on/off.


A resistors ¼ or ½W 5%.

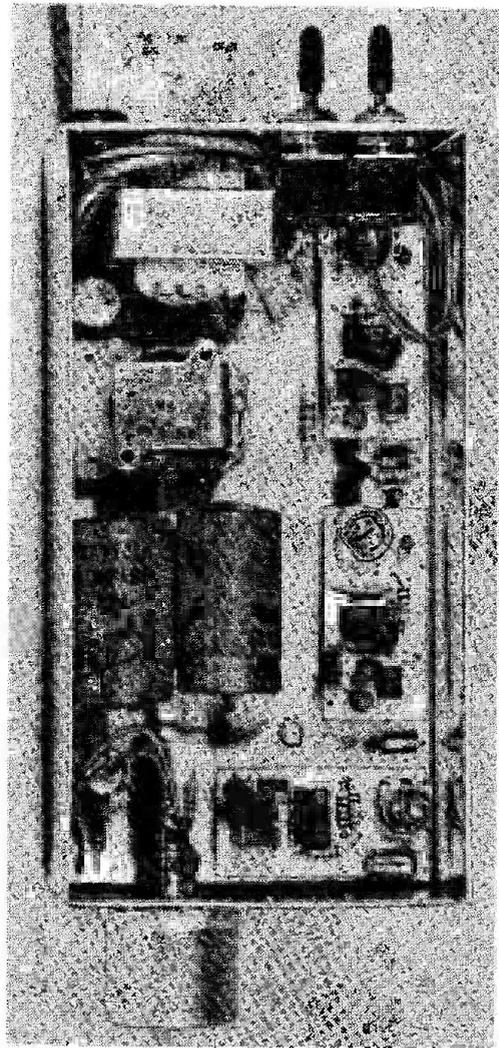The following items can be obtained from Ambit International, 37 High Street, Brentwood, Essex. All prices include VAT and P/P:—NE555, 86p each. NE567, £2.75 each. SN76660 99p each. Transducers, £5.50 a pair. Transmitter PCB, 77p. Receiver PCB 82p. Tone Decoder PCB's 10p each.



View of completed receiver with power supply components down the left hand side and three decoder modules at the right and bottom. The input transducer is shown fixed to the lower side of the box.

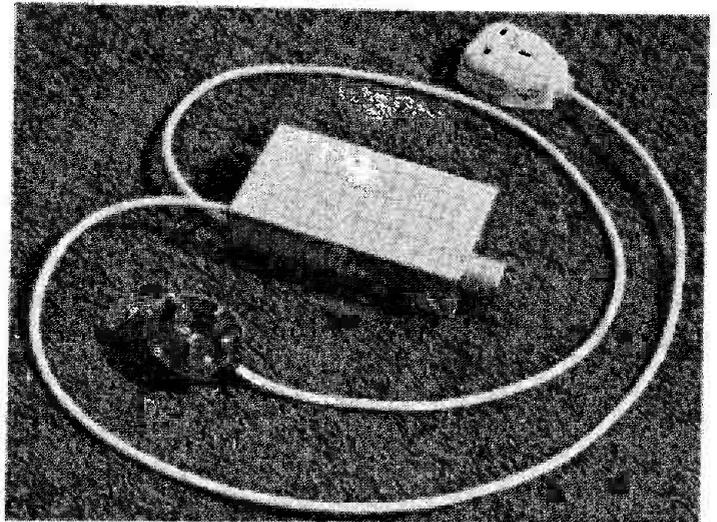Receiver with mains plug and fully insulated socket for plug from apparatus being controlled.



the audible range, then a crystal earpiece can be connected to pin 5 of the IC, and the tuning accomplished by ear. The ideal equipment is a digital frequency meter, and an oscilloscope and it is assumed that owners of such instruments will be aware of how they should be used to set up the decoder. If neither of these is available, then the following procedure should be observed:—

1. Inject the input tone and monitor the output with a meter.
2. Rotate the preset potentiometer until the output goes low. (Tone being detected.) Continue to rotate until the output goes high again.
3. Note these two positions and set the preset to the midpoint, which should then correspond to the centre frequency.

DECODER COMPONENTS

The most critical components in this design are those which determine the frequency, C1 and VR1 plus R1 should all be chosen for temperature and time stability. Wide tolerances in their absolute values are quite permissible, due to the latitude of adjustment available on the preset.

The bandwidth and decoupling capacitors are not critical, a 50% tolerance being acceptable. As a rule, it is best to standardize on a range of components when preparing for construction, so polycarbonate capacitors of 0.1 μ F and below, and tantalum bead capacitors for values above 0.1 μ F are chosen. Both these types of capacitor enjoy good stability combined with small physical size. In the PCB layout, the holes for the capacitors are given as either 0.1in. or 0.3in. spacing, so that either variety can be used.

RECEIVER PSU

A multipurpose PSU, Fig.5, is employed to supply:—

12V DC to the SN76660N (15mA)

5V (stab. DC) to the tone decoders (50mA approx.)

30V DC to the mains function relay (according to relay).

A 30V relay was employed for no better reason than one was available at the time. Any relay which can be fed with an available voltage, that can be switched by the BC108 or similar, will suffice.

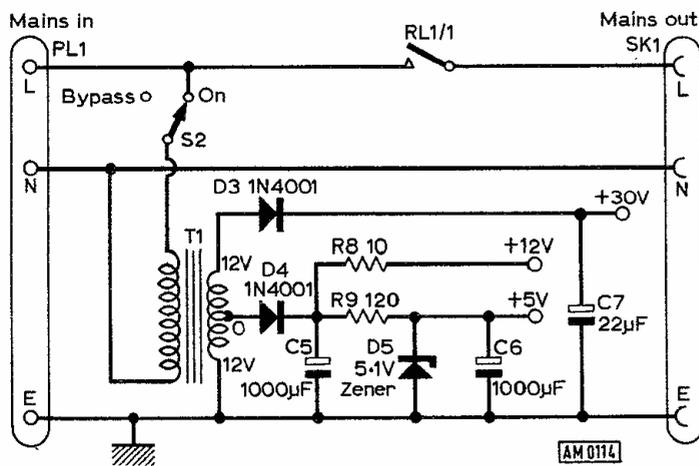



Fig. 5. Circuit of power supply which is accommodated on receiver pcb.

Remember that the contacts should be rated according to the power requirements of the system you wish to control.

One advantage of feeding the relay from 30V is that it will be a low current drain on the transformer which will help to maintain voltage stability on the other parts of the receiver.

PART 2 next month will describe the construction of the transmitter, the procedure for adjusting the tone frequencies and the final alignment.

Pw TECHNICAL PUZZLE No.2

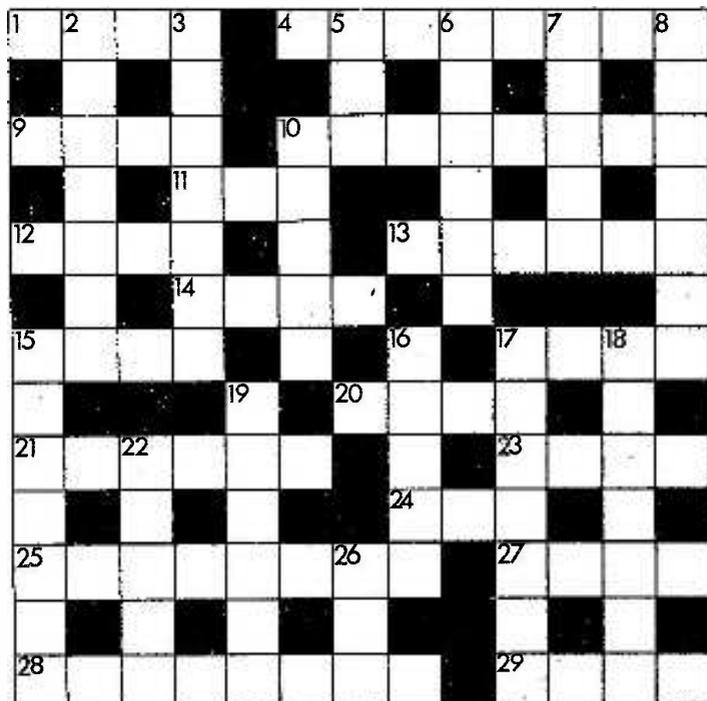

ACROSS

- 1 Should I scan about a record? (4)
- 4 Wet trees damaged h.f. loudspeakers (8)
- 9 Pinky recorded in tyro sync! (4)
- 10 Only agree about me making a coil? (8)
- 11 See 3 Down
- 12 A unit of the core of stem filaments? (4)
- 13 Make a crossing to wipe a tape? (6)
- 14 First man in farad amplifiers? (4)
- 15 Ringing tone on an old record? (4)
- 17 They turn on some signalling methods? (4)
- 20 Sound component that may need adjustment (4)
- 21 Not as selective around a curtain hanging (6)
- 23 Short course in maths (4)
- 24 Tune in this manner? (3)
- 25 What a charge for so small a part! (8)
- 27 True guarantee written into a thermionic? (4)
- 28 Alpine sound transmitter (8)
- 29 A backwater in bed dynamo production (4)

DOWN

- 2 Mighty atom active in radio! (7)
- 3 & 11 Across A sparkling receiver in the right spot (7, 3)
- 5 Go to court for half the speaker? (3)
- 6 The first group in the game (6)
- 7 Get away with oriental pole switches? (5)
- 8 Sorry state of Edna's rebuilt vessel (7)
- 10 High fidelity on a short instrument? (5)
- 15 Package deal in the power game (7)
- 16 Italian specialist from antenna centre (5)
- 17 Ted tore round with such a valve? (7)
- 18 Like a book on circuits? (7)
- 19 Learnt about the borrowing fee? (6)
- 22 M.p.h. or r.p.m.? (5)
- 26 No receiver has crude metal connections? (3)

**FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH**

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit-£24.95! (PLUS VAT)

The Cambridge – new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price – and by building it yourself you can save a further £5.50!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

The cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 – so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge


- * Uniquely handy package.
 $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents :

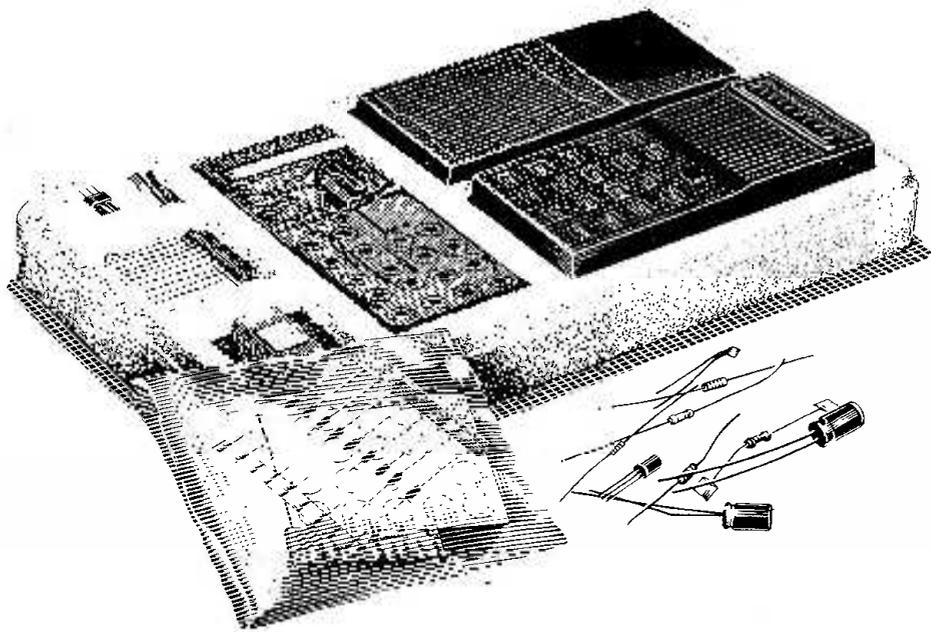
1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic—for shopping, conversions, percentages, accounting, tallying, and so on—then you'll get more than your money's worth.

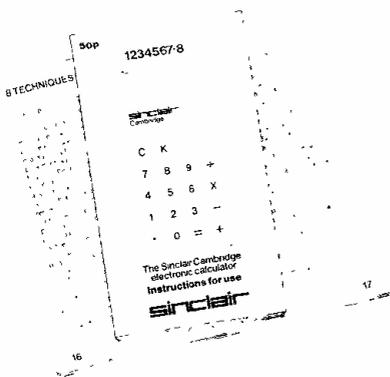But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

- Logs. Sines Cosines
- Tangents Reciprocals nth roots
- Currency Compound conversion interest and many others...

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no : 698483 England
VAT Reg. no : 213 8170 88

Why only Sinclair can make you this offer

The reason's simple : only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And *you* benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form : £24.95 + £2.50 VAT. (Total : £27.45)

Price fully built : £29.95 + £3.00 VAT. (Total : £32.95)

PW 174	
To : Sinclair Radionics Ltd, London Road, St Ives, Huntingdonshire, PE17 4HJ	
Please send me	Name
<input type="checkbox"/> a Sinclair Cambridge calculator kit at £24.95 + £2.50 VAT (Total : £27.45)	
<input type="checkbox"/> a Sinclair Cambridge calculator ready built at £29.95 + £3.00 VAT (Total : £32.95)	Address
*I enclose cheque for £ made out to Sinclair Radionics Ltd, and crossed.	
*Please debit my *Barclaycard/Access account. Account number	
*Delete as required.	
PLEASE PRINT	

THE 1973 INTERNATIONAL AUDIO FESTIVAL AND FAIR



COLIN RICHES


Whereas in previous years we have had stereo, quadraphonic, tape and cassette "revolutions" this year's Audio Fair gave me nothing that I could put a finger on any say "Ah yes, that was the "innovation" introduced at the '73 Audio Fair".

However, one thing that was noticeable was that many companies are offering "complete" systems which can be brought home from the shop, plugged in and used without any fuss or wiring problems. These systems are "one-up" from the unit audio equipment at present on the market, and cater for the person who requires something a little better than the usual run of "Mid-fi" equipment.

Below, I have made a selection of items of equipment exhibited at the Audio Fair which I feel will interest Practical Wireless readers.

together, to make bays for 20 LP's. You start with a 4-bay unit then add 2-bay extensions as your record collection grows. *Artifact Designs Ltd., 72 Boston Place, London N.W.1. 6EX.*


BSR introduced their TD8-QW 4-channel 8 track cartridge player. It will play ordinary stereo cartridges but if 4 channel playback is required, 4-channel or two stereo amplifiers must be used. The unit has a built in preamp with an output of 600mV (1kHz standard ref. level tape). Frequency response is 50Hz-10kHz. Power requirements are 105-130v a.c. at 60Hz or 210-250V a.c. 50Hz. Price is about £35. *BSR Ltd., Monarch Works, Cradley Heath, Worcs.*

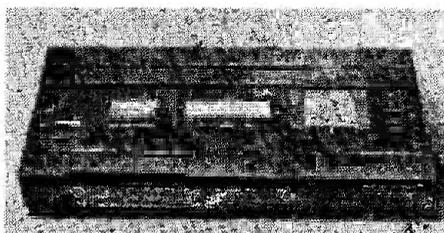


BANG AND OLUFSEN exhibited their complete range of audio equipment but the unit which caught my eye was the Beocord 2200 "Dolby-ised" cassette deck. It looks good, sounds good and by gum it is good! *Bang and Olufsen Ltd., Eastbrook Road, Gloucester, GL4 7DE.*



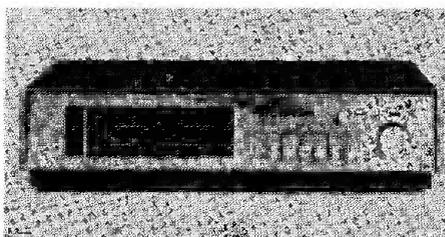
DECCA featured their compact 4 Music Centre. It has 10W per channel output and plays both records and cassettes. Decca also demonstrated their range of in-car entertainment units which included three cartridge players and one cassette player. *Decca Radio & Television, Nechells Lane, Willenhall, Staffs.*



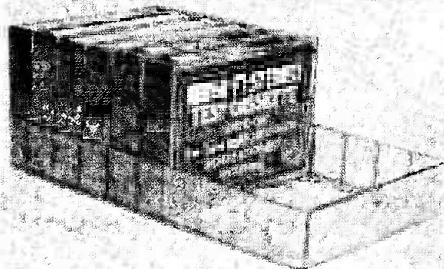
ALBA Ltd. were showing their medium price-range units with accent on the new UA800 a.m./f.m. tuner to match the popular UA700 amplifier. The UA800 pictured, is priced at about £38. *Alba Ltd., Bull Lane, Edmonton, London, N.9.*




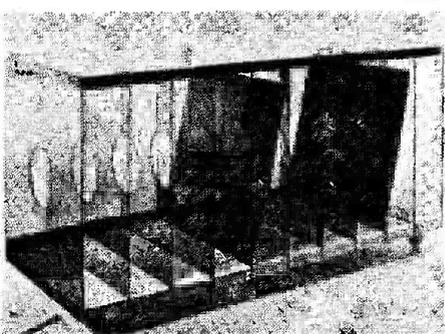
BIB Hi-Fi Ltd. exhibited a cassette storage system. Each tray holds ten cassettes in a horizontal position. *BIB Hi-Fi Accessories Ltd., P.O. Box 78, Hemel Hempstead, Herts, HP2 7EP.*



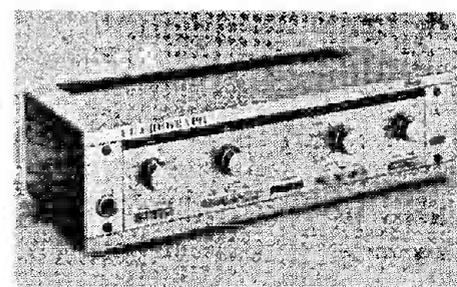
ARTIFACT DESIGNS Ltd. had their Encore record storage system as the main feature of their stand. Spacers screw



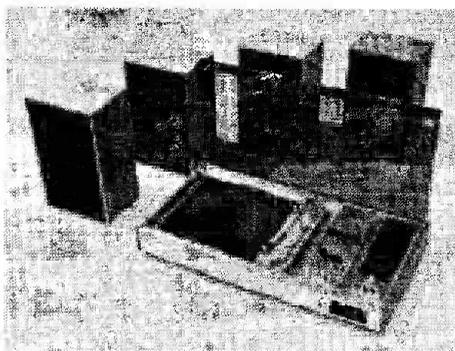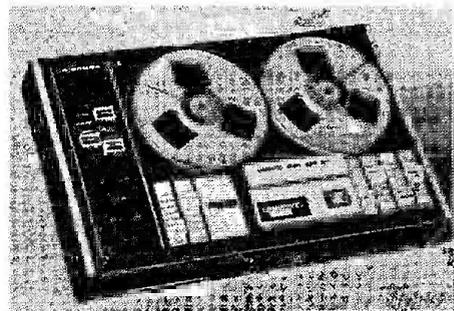FERROGRAPH'S new 20 + 20W stereo amplifier matches their new v.h.f. tuner. It features steep-cut filters and switched pick-up matching. *Ferrograph Co. Ltd., Auriema House, Bath Road, Crippenham, Bucks, SL1 6BB.*





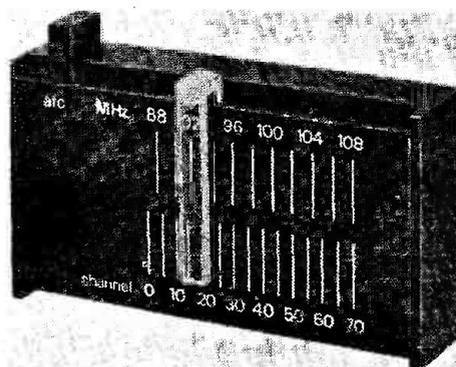QUADRASONICS Q4-20 unit audio system is claimed to be the first European system that will play any of the quadraphonic discs, stereo and mono records, was a feature of their stand. Also featured were the "Quadraline" loudspeakers. *Quadronics Ltd., Spencer House, Brettenham Road, Edmonton, London N.18.*




SINCLAIR exhibited their Project 80 units and shown here is the f.m. tuner. Covers 87-108 MHz and distortion is claimed as 0.3% at 1kHz for 75kHz deviation. Price is £11.95 + VAT. *Sinclair Radionics, Ltd., London Road, St. Ives, Huntingdonshire, PE17 4HJ.*

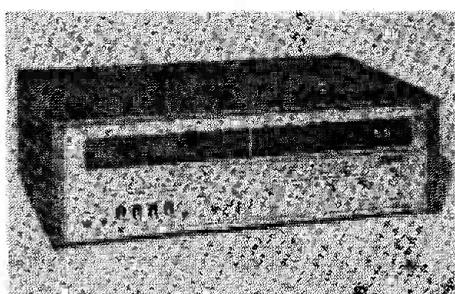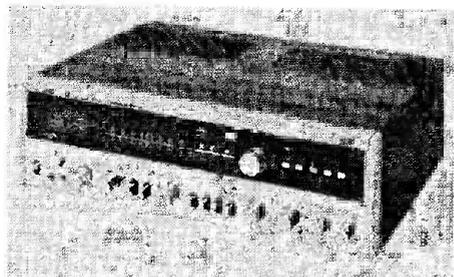GRUNDIG showed their latest reel-to-reel machine, TK745, recommended price is £141.75 excluding mic but including VAT. *Grundig (Great Britain) Ltd., Newlands Park, London, SE26 5NQ.*




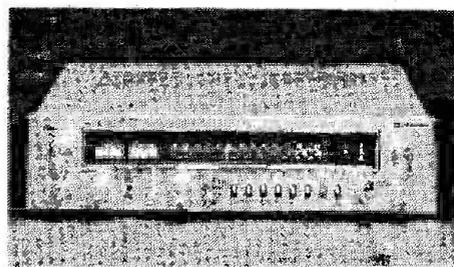SANYO. Shown here is the DCX3300 KA a.m./f.m. 4-channel tuner amp. Reproduces SQ discs and 4-channel reproduction of 8-track discrete tapes is a feature. Price is £176.75. *Sanyo Marubeni UK Ltd., Bushey Mill Lane, Watford, Herts.*




TOSHIBA Amongst the display was the SA-504 4-channel tuner/amplifier which has a suggested selling price of £289 (inc. VAT). *Tokyo Shibaura Electric Co. Ltd., Consumer Products Export Division 2-1 Ginza J-Chome, Chuo-Ku, Tokyo, 104, Japan.*

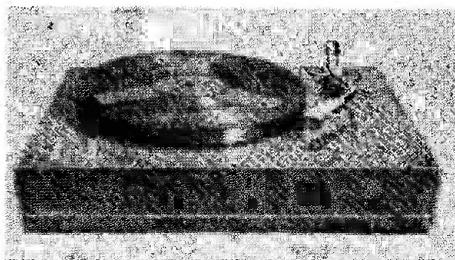
JVC demonstrated their 4-channel discrete tape on cassette and displayed their complete new range of both 4-channel and 2-channel tuner amplifiers. All the 4-channel tuner-amps have a built-in CD4 discrete modulator, SQ decoder, QS decoder and 2 to 4 channel synthesiser. Picture shows the 4VR 5446 a.m./f.m. tuner-amplifier. *JVC, Denham & Morley Ltd., 453 Caledonian Road, London N.7.*



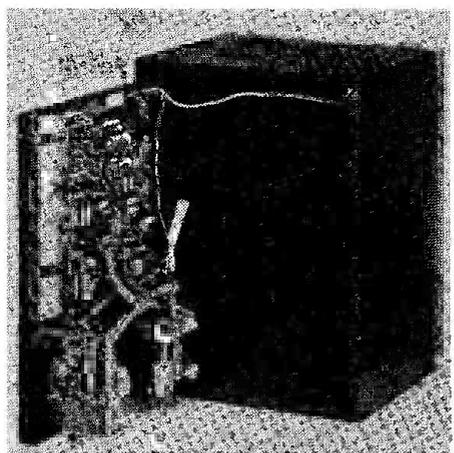SCAN-DYNA'S new 1400 record deck was one of the features of the stand. It employs a specially designed motor and suspension and comes complete with an Ortofon AS 212 arm and F150 cartridge. *Scandinavian Dyna Production Co. A/S, Hulum 7600, Struer, Denmark.*



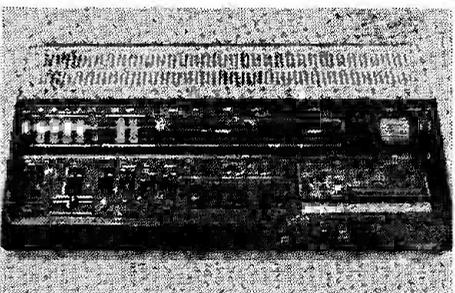PHILIPS launched their motional feedback speakers—each having two output amplifiers, one feeding the woofer and the other, the mid-range and tweeter. This is said to allow for bigger output powers from existing amplifiers and better reproduction from smaller enclosures. *Philips Electrical Ltd., Century House, Shaftesbury Avenue, London, WC2 8AS.*



SIEMENS demonstrated their RS502 stereo tuner with 4-channel amplifier. This unit covers six wavebands and reproduces 4-channel and stereo records. *Siemens Ltd., Great West House, Great West Road, Brentford, Middlesex.*



WHARFEDALE. How better to finish this little review than with a pretty girl. Actually, she is cuddling a pair of the Design-Council award-winning electromagnetic phones in their presentation case. Price including VAT is £21.95 (the phones, not the girl). *Rank Radio International Ltd., P.O. Box 596, Power Road, Chiswick, London, W4 5PW.*

HOTLINES

ON RECENT DEVELOPMENTS

ENERGY CRISIS

THERE'S an energy crisis coming, claim the experts. They're probably right, too. The current world situation regarding oil has made many people aware of the importance of finding a "new" source of energy. Trouble is, it has to be cheap.

Two interesting ideas have thrust themselves forward recently. One is being vigorously pursued in the U.S. and the other is experimental and the work being carried out in the U.K.

First, if you take little balls of frozen hydrogen and suddenly shine a dirty great laser beam on them, these little balls collapse and melt almost instantaneously. When they do so, they release colossal energy. Problem at the present time is that this method of getting energy requires a laser beam considerably in excess of anything currently available. But then transistors began in a small way with very tiny currents, didn't they?

In the U.K. the work is focussed on solar cell research. For many years, the silicon photocell has been the key word in the utilisation of daylight—or better still, sunlight. Recently, an American Company displayed some large silicon solar cells in London. Similar cells are being used to "power" offshore navigation systems.

Trouble with silicon is that the efficiency of the cells is so very low, commonly around 10% although 12% and a shade higher has been quoted. The U.K. experiments employ Gallium Arsenide/Gallium Aluminium Arsenide to form heterostructure junction semiconductors. Because the GaAlAs is transparent to sunlight, the surface layer can be made quite thick. Because it is thick, its electrical resistance is low and thus a higher power can be generated. An efficiency of 20% is claimed to be possible in theory. Although very little information is presently available, results so far seem promising.

ELECTRONIC HOUSEWIFE

I predict that the time will come (and soon, too) when housewives will carry electronic calculators on their wrists when they do their shopping. The price will drop to such a level that this will be easily possible. Schoolboys too will have these units.

Take a look at electronic calculators two years ago. Mostly expensive items. Now comes an announcement that a £20 unit is on the market—the Calate 44. This calculator has a keyboard where the only moving element is rubber. Around 30 hours of "normal" use is expected from a 9V alkaline battery. Although the IC chip employed performs calculations to eight digits, only four are shown on the display. The four most significant digits are shown, however, by depressing a button, the next (least significant) four digits are displayed.

It is interesting to note that the manufacturers achieve the long life of the battery by pulsing the chip/display instead of running these continuously. This is the technique which was employed by Clive Sinclair to achieve the same ends.

In the U.S. one source quotes that IC calculator chips will reach the next stage of their development: 200 mils square, accommodating up to 25,000 m.o.s. transistors and costing around five dollars.

RADARMOBILE

Electronics seems a natural ally to the motor car and yet the marriage of the two has been a slow process. It appears that legislation is the only thing which will cause any real progress here. However, this has not deterred many manufacturers from making numerous experiments and coming up with prototype equipment.

One manufacturer at the recent Motor Show talked of a radar system for locating obstacles in the path of the vehicle. The very

first units were large and bulky, and required a considerable amount of modification to the car when they were fitted. Now, the system has been miniaturised and very little modification indeed is needed. The aerial array has been fabricated on a p.c.b. and the unit has interesting possibilities.

£2.50 CALCULATOR?

Talking of miniaturisation, my ears gave an excited flap when I heard about the projected progress in memories—electronic types, of course. I'm always fascinated by the number of "bits" of information which these chips manage to accommodate. At present we have a 4,096-bit chip which has evolved after only two years from the 1,024-bit chip. The prediction is that by 1976, we will see a 16,384-bit component to be followed some years later by a 65,536-bit chip.

It is scarcely possible for the mind to grasp what this means in circuit complexity and packaging in terms of miniaturisation, but the fact remains that more and more is being packed onto these tiny chips. One person I spoke to recently, believed that the £200 computer was not quite so far fetched as many supposed and neither was the £2.50p electronic calculator. It is known that one UK source is poised to announce a £10 calculator.


Perhaps the most impressive, yet factually true, way to think of it is in real terms of transistors and ICs. Today, one can purchase a chip containing 10,000–12,000 transistors for the price which once had to be paid for a single transistor. Truly, the advances made in electronics have surpassed the boldest imagination. Think what is possible in the next decade!

Ginsberg

I.C. AMPLIFIER*

for the

P_W *
POP *
STAR ★ *

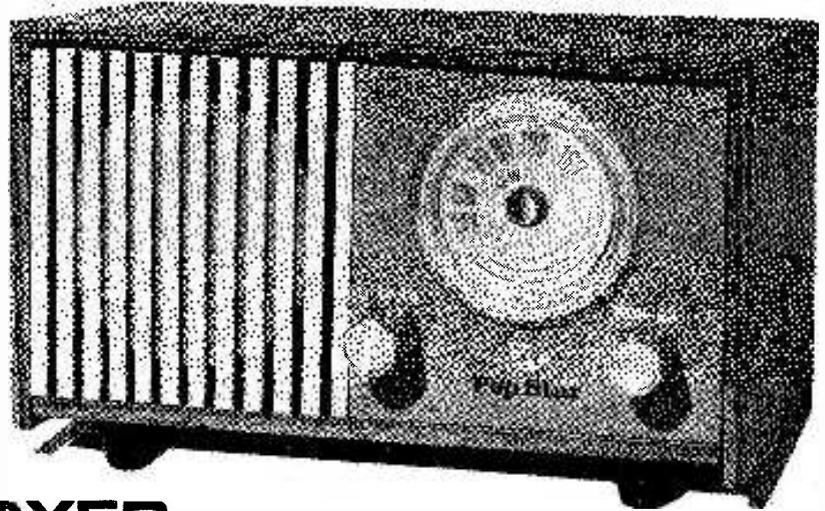

F.G. RAYER

SUGGESTED ALTERNATIVE I.C. AMPLIFIER TO REPLACE THE SL403D

THE "PW Pop Star" i.c. radio featured in our September issue was very popular; in fact it created supply problems regarding the SL403D amplifier. Readers who do not have one of these i.c.s. will be pleased to learn that they can still make the Mark 2 version of this radio and obtain almost the same result. The answer is to use the TBA800 integrated circuit for the amplifier section, but do not carry out a direct replacement procedure.

The TBA800 is not a direct substitute for the SL403D. Circuit requirements, tags and encapsulation are different. Reference to the revised component list will show that changes are made to the items in the audio section.

Revised Circuit

Fig. 1 is the revised amplifier circuit. The early section of the receiver, including R4, C6 and the volume control VR1, remains unchanged. The new and modified part of the receiver is that from R5 onwards.

As the receiver operates from a 9V battery, none of the electrolytic capacitors need have a higher voltage working rating than this. However, capacitors of higher voltage rating are in some cases more easily obtained, and are of course suitable.

Resistors R7 and R8 in parallel, each of 2.2Ω, may be replaced by a single 1Ω resistor. Two 2.2Ω resistors are shown because these are readily available, while a number of stockists do not appear to carry the 1Ω value.

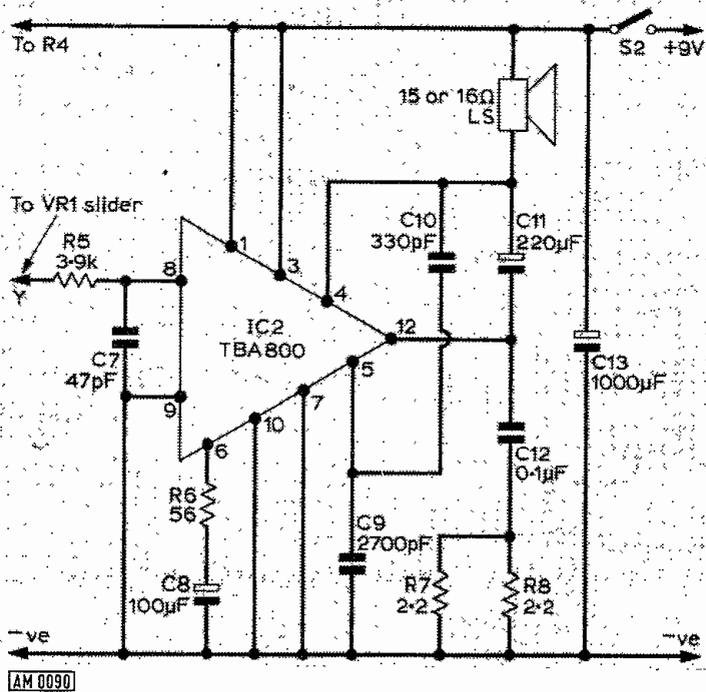


Fig. 1: Revised circuit of the "Pop Star" amplifier.

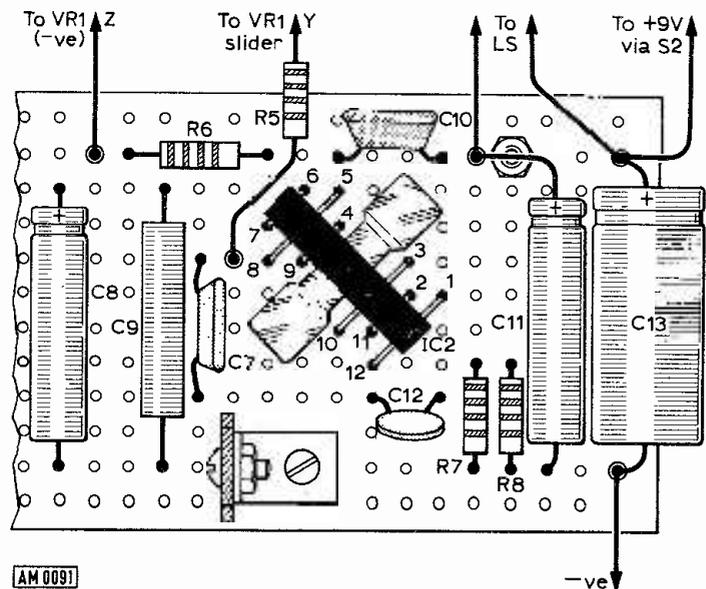


Fig. 2: Components viewed from the top side of the Veroboard. Note the indent on the i.c., adjacent to pins 1 and 12.

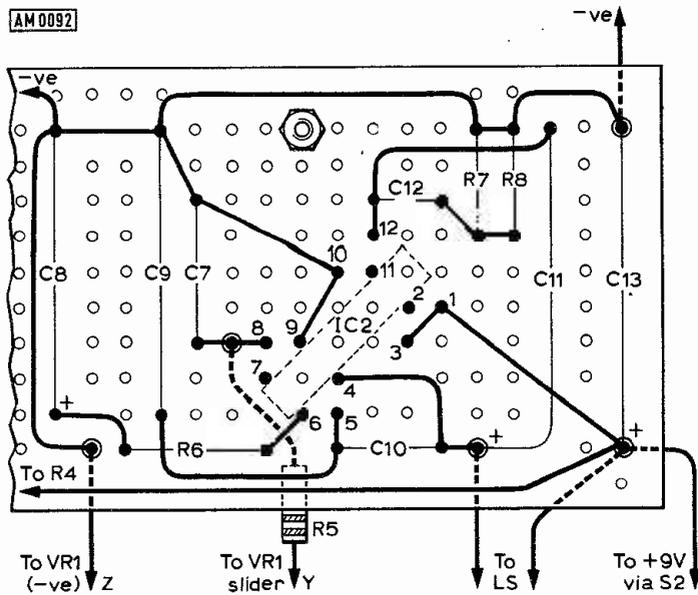


Fig. 3: Underside view of the Veroboard showing the additional wiring.

The TBA800

Some pins are unused. The i.c. is positioned as in Fig. 2, and will fit the 0.15 matrix Veroboard. Pin 1 is indicated by the figure 1 near it, and an indentation also marks this end of the i.c. The integral heat sink tabs are bent up so far as is necessary to clear the pins and board.

Fig. 2 indicates the positions of all the components on the board, including the original IC1 stage, which is unchanged.

Underneath wiring is shown in Fig. 3. The components are easily accommodated on the original board. Wires are soldered directly to the projecting pins of IC2, underneath.

Volume control connections are unchanged, but R5 is soldered to the central tag Y, a lead from here running to C7 and tag 8 of IC2 when the board is fixed in position.

Battery drain is about 8mA, rising to some 20-30mA or so, with average good volume. The heat sink tabs alone are suitable for operation with up to 1W, and as the amplifier is operated from a 9V supply only,

★ components list

Revised components shown in italics

Resistors

R1	100k Ω
R2	1k Ω
R3	470 Ω
R4	2.7k Ω
R5	3.9k Ω
R6	56 Ω
R7	2.2 Ω
R8	2.2 Ω

All resistors 1/4W 5%

(R7 and R8 may be replaced by a single 1 Ω resistor)
VR1 100k Ω log pot with switch

Capacitors

C1	12pF
C2	470pF
C3	0.01 μ F
C4	0.1 μ F
C5	0.047 μ F
C6	6.4 μ F 6.4V
C7	47pF
C8	100 μ F 6.4V
C9	2700pF
C10	330pF
C11	220 μ F 10V
C12	0.1 μ F
C13	1000 μ F 10V

Miscellaneous

VC1	Jackson 00, 208/176pF
TC1	400-1250pF compression type VC29SA
L1	Denco FR5, medium wave ferrite rod Transparent medium wave 2 1/2 in dial
IC1	ZN414
IC2	TBA800
	15 or 16 Ω 3 1/2 in square speaker
	Veroboard, Veropins
	1-pole 2-way rotary switch
	Two knobs
	Case:
	6mm. plywood: Top 8 x 4 1/2 in
	Bottom 8 x 4 1/2 in
	2 off 4 3/8 x 4 1/2 in
	Back 8 x 3 7/8 in
	Hardboard 8 x 4 in, 1/4 in thick
	Panel: Universal chassis flanged member 8 x 4 in

and at lower volume levels than this, no additional heat sink is fitted.

Tuning adjustments, and other details of construction, remain as originally described. ■

CRATA can "TALK"
CRATA can "PLAY MUSIC"
CRATA is in "STEREO"
CRATA can "LISTEN"
CRATA is "EXCLUSIVE"
CRATA is "COMING"
CRATA in "MARCH"
CRATA is "REVEALED"

SEE NEXT MONTH'S P.W.

PRACTICAL WIRELESS **DATA CARD SYSTEM**

P.W. DATACARDS
Nos. 7 and 8 COMING
SOON — WATCH NEXT
MONTH'S P.W. FOR
DETAILS

GOING QUADRAPHONIC


PW Q4 PROJECT

PART 4 D. BOLLEN

- QS recordings
- SQ recordings
- Discrete CD-4 recordings
- SURROUND SOUND

Power supply components are grouped on a piece of 0.1in. Veroboard 1.9in. wide by 2.1in. long. Note that the end of the diodes marked positive in Fig. 25 corresponds to the cathode, and to a black or coloured band on the component itself. Tr9 is fitted with a push-fit heat sink before being soldered into position.

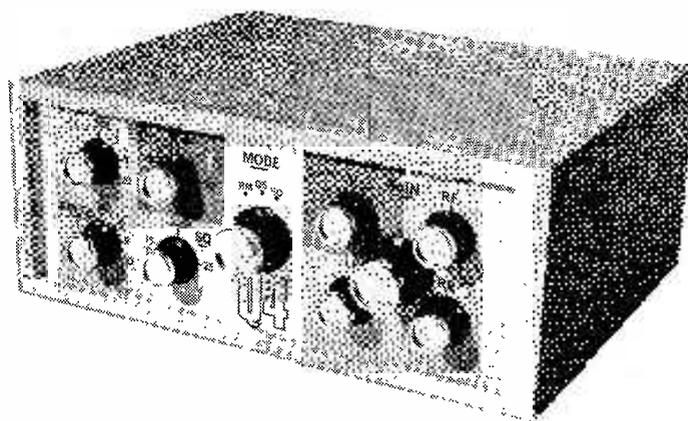The power supply can be tested by temporarily connecting it to T1, but take care not to short the output as this will almost certainly destroy Tr9.



Decoder wiring

Position and mount all circuit boards on the chassis tray, and fit SK1-SK10, T1, and a power supply screen made of scrap aluminium sheet or tinfoil. Wiring can commence with the earth connections shown in

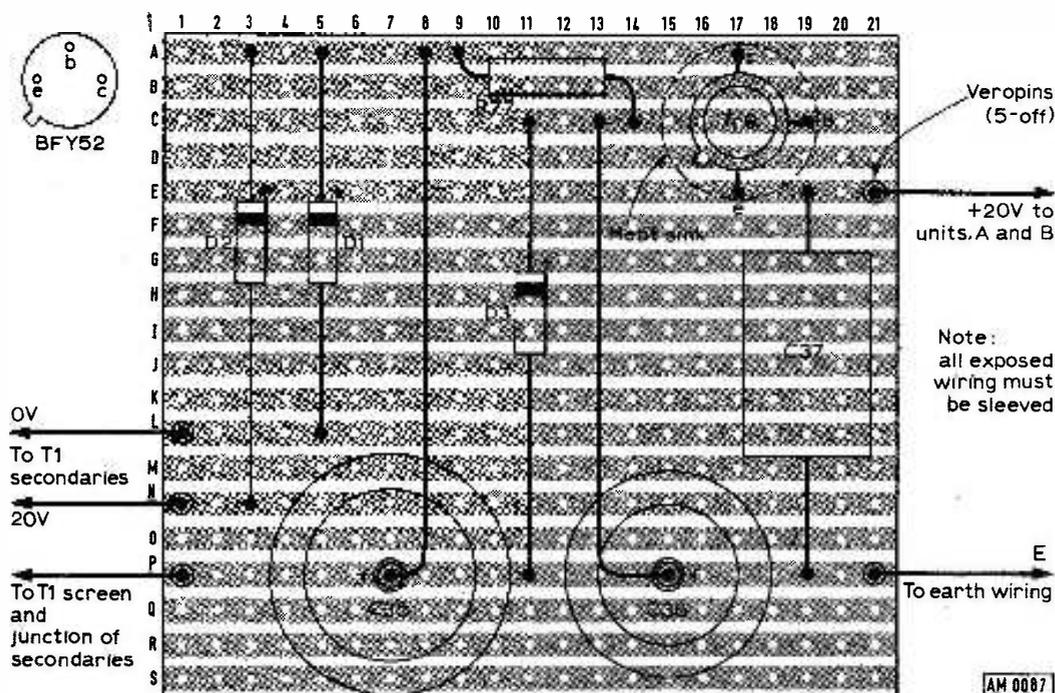


Fig. 25: Power supply circuit board.

Fig. 19. The layout of the earth wiring is arranged to avoid hum loops and should be adhered to.

Transformer T1 output terminals consist of two pairs of tags marked 0 and 20V. The two inner tags are linked together and connected to the tag marked SCN, which is in turn wired to the appropriate terminal on the power supply board. The outer 0 and 20V tags on T1 are then wired to the power supply board as in Fig. 19.

Low number SK11 tags are positioned under S1 and it is therefore advisable to wire these up first while they are still readily accessible. The following wiring procedure can be adopted. Connect S1 to the circuit boards and SK11, starting with the middle wafer S1E and S1F (Figs. 26, 27) and then S1G and S1H. Next link up SK11 tags 6 and 7 to unit B and SK11 tags 8 to 11 to VR1 and VR2 sliders, then wire the front switch wafer starting with S1I.

Connect the outputs of unit A to VR5-VR8 and VR9

and then wire up the rear switch wafer S1A-S1D. Take a red wire from the power supply output terminal to the +20V terminal pins on unit A and unit B, not forgetting to link together the supply rails of the two unit B channels, and then complete the wiring with a mains lead to T1.

Cabinet

Details of a cabinet for the decoder are given in Fig. 28. The front panel sits in a groove and is a permanent fixture in the front of the cabinet. The decoder chassis will slide in from the back of the cabinet and is retained in position by a couple of self-tapping screws. Self-adhesive vinyl or wood veneer will give a smart appearance to the finished cabinet.

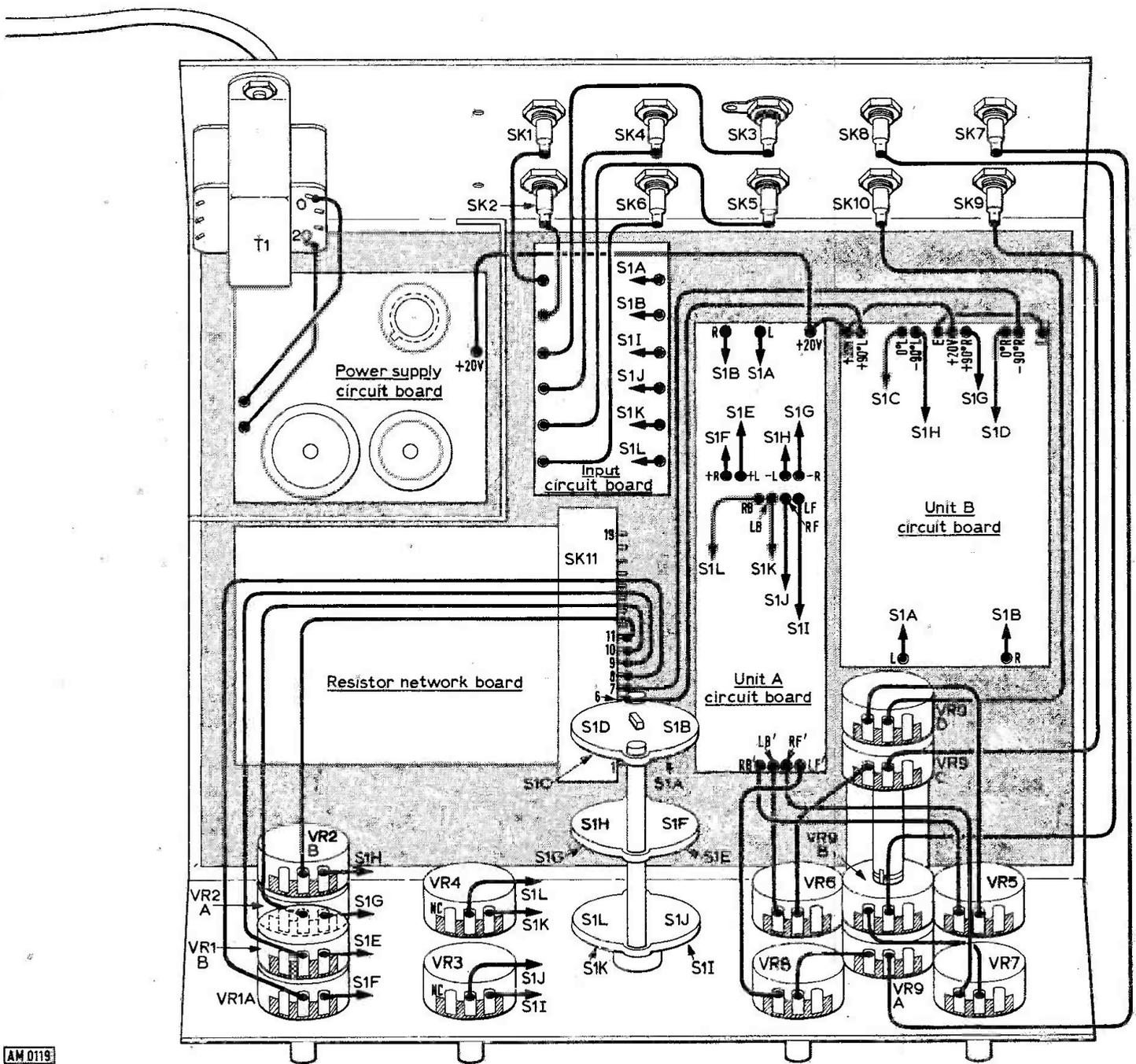


Fig. 26: Multi-system decoder wiring

Testing the decoder

Ideally, the decoder should be tested with an audio generator and a high impedance a.c. voltmeter or calibrated oscilloscope, but failing these certain tests can be carried out with music signals or a stereo test record.

If instruments are available, proceed as follows. Set VR9 to full gain and VR5-VR8 mid-way. Connect the a.c. voltmeter or oscilloscope to SK7 and inject a 1V 1kHz signal into SK3. Trim VR8 for a reading of 1V. Repeat for LB, RF, and RB inputs and outputs while trimming controls VR6, VR7, and VR5 respectively.

Set VR1 and VR2 to the mid position, and S1 to the RM mode. Inject a 1kHz 1V signal into the left input SK1, and, without altering the settings of VR5-VR9, look for a voltage of 0.92V at the LF and LB outputs SK7 and SK9. There may be minor voltage discrepancies of a few percent, due to circuit tolerances, but a large discrepancy will indicate a circuit fault.

Without altering the input signal (SK1), transfer the a.c. voltmeter or scope to the RF output SK8 and adjust VR1 for a reading of 0.38V. Repeat for the RB output and VR2. Still with the same input to SK1, switch S1 to the QS mode and check for the following output voltages; LF=0.92V, RF=0.38V, LB=0.92V, and RB=0.38V. Transfer the 1kHz input signal to the right input SK2 and this should give LF=0.38V, RF=0.92V, LB=0.38V and RB=0.92V in the RM and QS modes.

To test the SQ section of the decoder, set VR3 and VR4 to maximum resistance (fully clockwise) and inject the 1V 1kHz signal into the left input SK1. The following outputs should be obtained; LF=1V, RF=0V, LB=0.71V, and RB=0.71V. When the input signal is transferred to SK2, the LF and RF readings will be transposed, with LB and RB outputs remaining the same.

Music signal testing

Set up the decoder with outputs connected to four amplifiers with speakers (see Figs. 2 and 5 and instructions for speaker phasing in the October issue of PW), and with a stereo music signal applied via a pre-amplifier to the decoder left and right inputs. The decoder mains lead can be temporarily connected to any convenient supply source at this stage.

Place S1 in the RM position, VR5 and VR6 to minimum gain, VR9 to maximum gain, and VR1 fully clockwise. Balance VR7 and VR8 for normal front speaker stereo, and then unplug the input to SK2. The sounds issuing from the LF speaker should move to centre front when VR1 is rotated fully anti-clockwise. Repeat with the input to SK1 disconnected and an input signal on SK2. The sound image should then move from RF to centre front when VR1 is rotated. Repeat the above tests in the QS mode.

Set VR7 and VR8 to minimum gain and balance VR5 and VR6 for a stereo output from the rear speakers only in the RM mode. Disconnect the input to SK2 and rotate VR2 anti-clockwise to shift the

sound image from LB to centre back. Repeat with a right input only on SK2 for a sound image moving from RB to centre.

Using a similar test procedure, controls VR3 and VR4 should shift the sound image from left or right to centre when S1 is set to SQ.

Installing and balancing

When installing the decoder, its main lead can be wired to the main equipment on-off switch. Do not earth the decoder chassis as this could set up a hum loop. Earthing is normally achieved via the outer braiding of the screened interconnecting leads.

The importance of correct balancing cannot be stressed too highly, and it is worth taking trouble over this until experience is gained in quadrasonic listening. Set controls VR1, VR2, and VR5-VR8 mid-way, and S1 to RM. Adjust VR9 for the desired level of sound output with a stereo signal on SK1 and SK2, and then remove the plugs from SK9 and SK10.

Using a mono recording, or a stereo recording

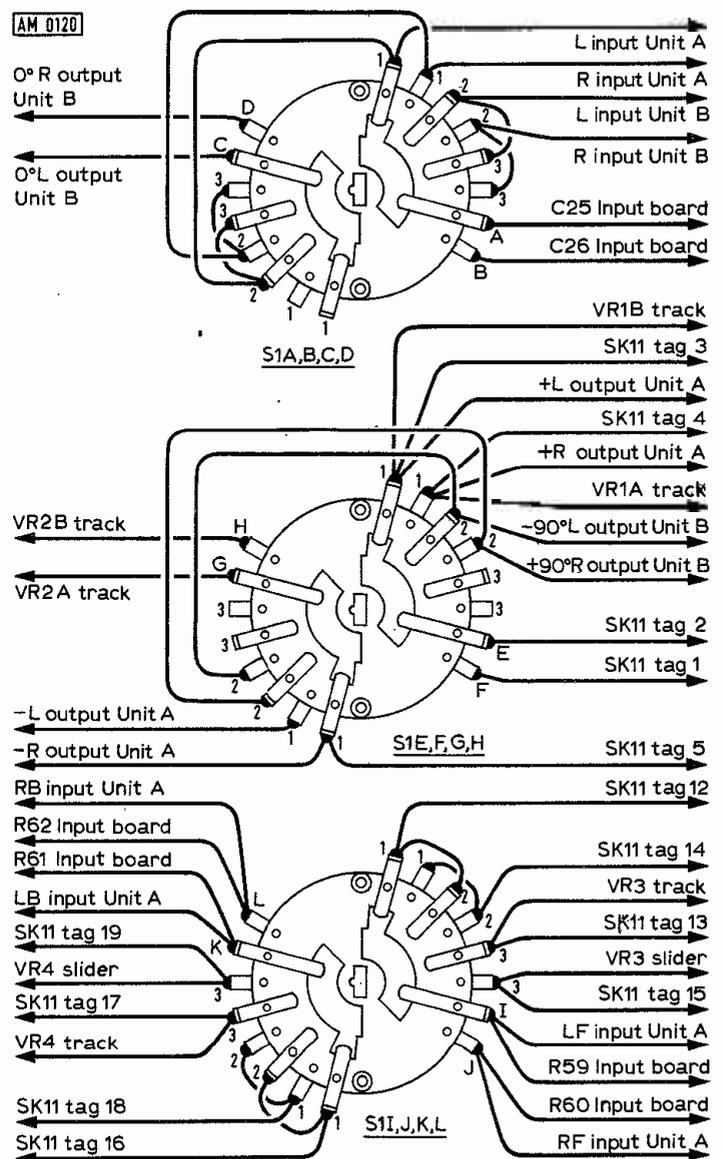


Fig. 27: Mode switch (S1) with wafers as seen from the front of chassis and in the RM position.

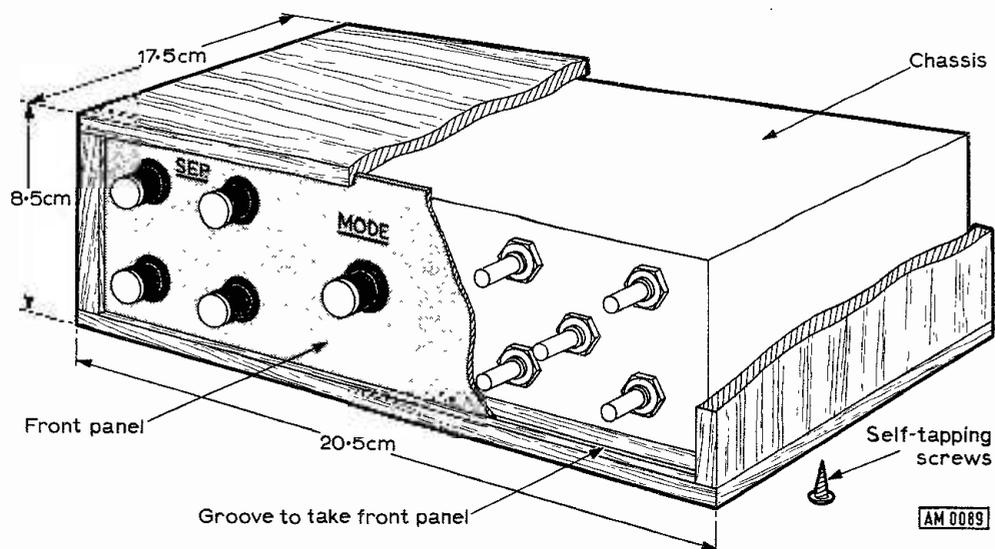


Fig. 28: Q4 decoder cabinet details.

with a known centre front image, trim VR7 and R8 for correct location of the centre front image. If there is a balance control on the pre-amp. which feeds the decoder this should be in its normal position. Insert the SK9 LB plug and remove the SK8 RF plug and SK2 right input plug. Trim VR6 for a left sound image, mid-way between the LF and LB speakers, when the listener is seated equidistant from all four speakers and is facing centre front.

Insert SK8 RF plug and SK10 RB plugs, and remove SK7 LF and SK9 LB plugs. Adjust VR5 for a right hand sound image mid-way between RF and RB speakers with the listener positioned as before. Remove SK8 RF and insert SK9 LB plug, then check for a centre back image mid-way between the LB and RB speakers. Listening tests can now be conducted on a variety of stereo and quad recordings to establish mean balance settings. Thereafter, one or more of the balance controls can be trimmed to suit individual preferences and recordings.

Using the decoder

Where the listener wishes to be completely immersed in sound, as though sitting in the middle of a group of musicians, the following settings can be tried. With stereo discs, tapes, or radio, the mode switch is set to RM, VR1 is adjusted for a separation of 1-5dB, and VR2 for a separation of 1-3dB. Some stereo sources can sound slightly better in the QS mode, where blurring of back sound images is less pronounced than with RM.

For QS discs in the QS mode, front and back separation settings should be 3dB, but it is worth experimenting with these settings to obtain optimum results. Most SQ discs, in the SQ mode, will sound well with a front separation of 10-20dB and a back separation of 5-10dB, but again it is worth experimenting with these settings. It may be necessary to reduce back channel gain with SQ recordings for a well balanced effect.

A more realistic listening position, with the musicians at the front and mainly ambience from the back, can be achieved by reducing the settings of VR5 and VR6, and with stereo or QS sources, adjusting VR1 for high separation (20dB) and VR2 for low separation (1dB) in the RM and QS modes. With SQ discs in the SQ mode, VR3 can be set to 25dB and VR4 to 5dB.

Generally speaking, when the decoder separation controls are set to low values this will give an increase in front to back separation, and conversely. The effect of altering the separation settings from optimum is to alter the shape of the sound stage from a circle to an ellipse, with the major axis lying from left to right at high separations, and from front to back at low separations.

For conventional front speaker stereo, or mono, VR5 and VR6 are adjusted for minimum gain and the front separation controls set to maximum. With normal quad settings, a mono signal input will, however, give a centre front sound image without the need for adjustments. Centre of the room stereo or mono can be achieved by placing all separation controls at maximum with VR5 and VR6 at normal quad settings.

When applying four-channel signals to SK3-SK6, S1 should be placed in the RM or QS positions for maximum separation, and this will make VR1 and VR2 inoperative. Alternatively, where a measure of separation control is required with discrete signals, S1 can be set to SQ and VR3 and VR4 adjusted for front and back separation. SK3-SK6 can also be employed for mixing in other signals when the decoder is handling two-channel inputs.

In Fig. 8 (October issue) the 110kΩ resistors linking -R and RF and -R and RB should be connected to +R instead of -R. ■

COMING SOON

Q4 MATRIX MATE

Watch for further details!

Curing Radio Interference in Audio Equipment

BRIAN L. PHILLIPS

IN some localities, problems are experienced with interference caused to audio systems by nearby radio transmitters, which may be amateur, public service or military. Such interference can occur even though there is nothing wrong at the transmitting end.

What happens is that the locally powerful signal enters the audio system via one or more routes and causes interference or distortion, or at worst "mutes" the output completely. Such effects may occur in tape recorders, record players and hi-fi amplifiers, or in fact in any unit using transistors, integrated circuits or valves. In solid-state equipment, the interfering signal voltage injected into the amplifier can be greater than the standing DC bias on the transistors, or ICs, pushing them into non-linearity. The higher electrode voltages used in valved equipment mean that it suffers far less from this effect.

In tackling such a problem, the first step is to try to establish how the RF signal is entering the amplifier, which may be either by direct radiation or via the input, output or mains supply leads.

VALVED EQUIPMENT

Valved equipment doesn't often respond to direct pickup from radio transmitters unless the signal level is very high and, in general, a cure can be effected by the addition of resistive stoppers in each control grid lead, close to the valve holder. This forms an RF filter with the valve's input capacitance in parallel with the input.

Often, especially in unit audio equipment where long loudspeaker leads are used, the interfering signal is injected via these leads back into the amplifier and then around the negative feedback loop to an early amplifier stage. Usually low frequency RF, such as 3.5MHz amateur transmissions, finds its way in by such a method and a cure can often be effected by adding capacitors across each speaker socket at the amplifier. Values of the order 0.01 to 0.1µF are suitable and should not affect the audio response because of the low output impedances present.

Radio frequency pickup on the input leads (gramophone pickups, microphone lines etc.) is usually responsible if altering the volume control affects the

level of interference, or if unplugging a lead stops the effect. Small value ceramic capacitors around 100 to 500pF placed across the input concerned may stop the trouble. Ferrite beads fitted at the input grid of the first stage may also help. Sometimes a good RF earth attached to the screening of the offending lead will prevent the signal reaching the amplifier.

TRANSISTORISED EQUIPMENT

Transistor amplifiers will respond far more readily to the effects mentioned earlier and the problem can be difficult to cure in some instances. Pickup via the speaker leads needs the same treatment as for valve amplifiers, but usually ferrite beads and capacitors at amplifier inputs are less effective due to the low input impedances present in transistor circuitry. Some success has been achieved by placing small capacitors between base and collector on each stage (about 50 to 500pF) to produce negative feedback at the unwanted frequency thus preventing the transistor from either detecting or amplifying the interfering signal. The effect on audio response will vary and depends finally on the exact circuitry and values used. The usual effect is a slight loss of treble response, but this can probably be corrected by increasing the treble lift in the amplifier. At all events, the owner will probably accept slight loss of treble rather than have a local transmitter belting through his equipment.

In severe cases of interference, where all else seems to fail, inserting a low value resistor in the existing emitter lead close to the transistor can work wonders. Being unbypassed, negative feedback is produced lowering the stage gain slightly, possibly enough to prevent the RF producing rectification effects. Values around 47 to 100Ω have been used successfully. The slight loss of audio gain can always be overcome by increasing the volume control setting. A similar resistor in the transistor's base lead can also be effective, forming a low-pass filter with the input capacitance of the transistor.


Incidentally, an amplifier employing field effect transistors will not respond as much to RF fields because the characteristics of such devices are similar to those of the thermionic valve. In cases where such an amplifier is picking up RF signals, the techniques recommended for valved equipment should be applied.

INTEGRATED CIRCUITS

Audio equipment utilising ICs can be very unpredictable in its response to RF pickup. It has been found that one IC may be entirely unaffected whereas another of the same type may completely defy efforts to cure interference. In some IC stereo units, it is possible for one channel to be riddled with RF interference whilst the other channel is perfectly clear. Audio response and performance may be normally balanced despite the difference in RF response. Possibly manufacturer's characteristic spreads allow widely differing RF responses between ICs; it is not unusual for some audio ICs to give a hefty output up to 1 or 2 MHz!

Electrolytic decoupling capacitors can make the situation worse because of their increasing impedance with frequency. Very often the circuit operation at RF is so different from the normal operation at audio frequencies, even though the same physical

—continued on page 886

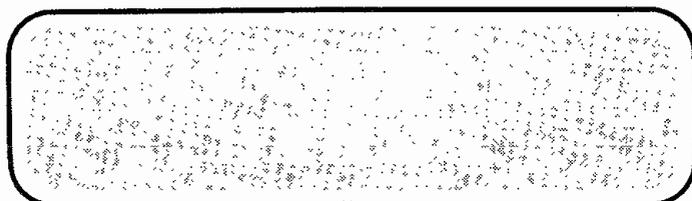

SHORT WAVE DX by MALCOLM CONNAH

THE FEW paragraphs which I wrote a few months ago on the subject of ex-government receivers seems to have aroused a great deal of interest from readers.

About ninety per cent of your letters asked the same basic question: where can these receivers be obtained?

The main source of these receivers is, the second-hand market. The best place to look for them is at the various Amateur Radio Rallies which take place during the summer months. Also the For Sale columns of Amateur Radio magazines should be studied.

Construction Season

These dark, winter months are always the best time for turning one's thoughts, and hands, to the subject of constructional projects. Apart from the building of a new receiver, a lot of pleasure can be derived from building some of the simpler circuits which contribute to the efficient operation of a receiving station.

The construction of a preselector, or a Q-multiplier or the addition of crystal filter will greatly improve the performance of most average receivers. A crystal calibrator or other means of frequency determination will prove invaluable in identifying some of those rare DX catches.

Readers' Logs

John Spinks of Norwich has recently invested in a Trio 9R-59DS receiver, with this connected to 75 feet of aerial wire John heard:

- 6605 R. Pyongyang, N. Korea at 2055.
- 9009 Jerusalem, Israel, news at 2000.
- 9023 R. Tehran, Iran, news at 2000.
- 9570 R. Australia noted at 2100.
- 9605 AIR, Delhi noted at 1810.
- 9750 R. Vilnius with Mailbag at 2245.
- 11815 NHK, Tokyo, Japan noted at 2050.

- 11845 R. Canada Int., SW Club at 2115.
- 15012 Voice of Vietnam, Hanoi, news at 1000.
- 15150 R. Grenada, Windward Is., music at 2125.
- 15185 WINB, Red Lion, USA noted at 2100.
- 15415 R. Kuwait with news at 1730.
- 17755 HCJB, Quito, Ecuador, DX pgr. at 1930.
- 17890 U.N. Radio, New York, news at 1805.
- 21550 RSA, South Africa, news in French at 1200.

Steve Fletcher of Bromsgrove describes his equipment as follows: "Receiver is a very unaligned Heathkit SW717 and the antenna is 150 feet of copper wire, wound around the loft." However, this did not prevent Steve from hearing:

- 6035 TWR, Monte Carlo noted at 1415.
- 7250 Vatican Radio at 2054.
- 9520 ORTF, France noted at 1419.
- 9525 All India Radio, Delhi at 2005.
- 9590 Swiss Broadcasting Company at 1323.
- 9630 Radio Sweden noted at 1100.
- 9833 Radio Budapest, Hungary at 1730.
- 11765 Radio Australia at 0645.
- 11775 R. Nacional de Espana at 1030.
- 11940 R. Bucharest, Rumania noted at 0658.
- 15165 Radio Denmark at 1200.
- 15185 Radio Finland at 1820.
- 15245 Radio Sofia, Bulgaria at 2330.
- 17800 Radio Norway noted at 1810.
- 17825 NHK, Tokyo, Japan at 0805.
- 21945 Radio Portugal noted at 0730.
- 25790 RSA, South Africa noted at 1415.

Christopher Hodgson of Sunderland is still using the same equipment; Codar Multiband 6, PW A.T.U. and 50 foot end-fed; and although his return to school has curtailed listening hours the following stations found their way into his log:

- 6180 BBC, Cyprus relay, s/on at 1700.
- 7210 Red Cross Broadcasting Service Geneva, s/on at 1700.
- 7245 Austrian Radio in German at 0900.
- 9006 R. Tehran, Iran, s/on at 2000.
- 9620 Radio Belgrade noted at 1540.
- 9745 Radio Baghdad, Iraq at 1945.
- 9830 Radio Kiev noted at 1940.
- 11765 Radio Australia at 0955.
- 11880 Voice of Turkey, Ankara at 2215.
- 11900 RSA, South Africa at 2215.

Michael Johnson of Hockley in Essex used his Ferguson 6 valve domestic receiver and 25 metre long-wire to hear:

- 6070 Radio Sofia in English at 1930.
- 7215 All India Radio, Delhi at 1830.
- 9620 Radio Belgrade in English at 1430.
- 9665 R. Damascus, Syria in English at 2030.
- 11770 R. Vilnius in English at 2230.
- 11925 R. Tashkent in English at 1400.
- 15295 ORTF, France in English at 1100.

THE SPECIALISTS IN QUADRAPHONIC KITS

AVAILABLE NOW!

THE COMPREHENSIVE KIT FOR THE

P.W. Q4 PROJECT

SEND NOW FOR FULL DETAILS AND PRICES—SEE COUPON BELOW

FULLY COMPREHENSIVE HOME CONSTRUCTOR KITS AS SPECIFIED IN PRACTICAL ELECTRONICS

P.E. RONDO

COMPLETE QUADRAPHONIC HI-FI SYSTEM

CBS SQ (TM CBS INC.) MATRIX DECODER. COMPLETE KIT

PRE AMPLIFIER BOARD. COMPLETE KIT

MASTER VOL./TONE/4 CH. BALANCE BOARD. COMPLETE KIT

POWER AMP. BOARD & HEAT SINKS (STEREO PAIR). COMPLETE KIT

POWER SUPPLY BOARD. COMPLETE KIT

MAIN SMOOTHING CAPACITORS (2 REQUIRED) INC. CLIPS

MAINS TRANSFORMER

CHASSIS, PUNCHED & DRILLED WITH SCREENS

REAL WOOD CASE

HARDWARE PACK

CONTROL SECTION FASCIA

SUPERB 20W QUADRAPHONIC SPEAKERS TEAK/WHITE

GOLDRING G101/2 Turntable

DEUSCHE ELAC STS 144/17 CARTRIDGE

£8.00 Post Free + 80p V.A.T.
Inc. CBS Licence Fee

£3.00 Post Free + 30p V.A.T.

£8.50 Post Free + 85p V.A.T.

£7.50 Post Free + 75p V.A.T.

£5.00 Post Free + 50p V.A.T.

£0.75 Post Free + 7p V.A.T.

£0.75 Post Free + 7p V.A.T. EA.

£6.25 Post Free + 62p V.A.T.

£2.25 Post Free + 22p V.A.T.

£1.75 Post Free + 17p V.A.T.

£2.00 Post Free + 20p V.A.T.

£3.50 Post Free + 35p V.A.T.

£42 per pair + £2 p & p

+ £4.40 V.A.T.

£17.90 + £1 p & p + £1.89 V.A.T.

£6.90 Post Free + 69p V.A.T.

ALL KITS ARE FULLY TO SPECIFICATION AND COMPLETE IN EVERY
DETAIL. TRADE AND EXPORT ENQUIRIES WELCOME

STUDIO ELECTRONICS

P.O. BOX 18,
HARLOW, ESSEX, CM18 6SH

Telephone HARLOW 25457 (STD 0279)

Please send me:

CBS SQ DECODER

PRE AMPLIFIER BOARD

MASTER VOL. BOARD

POWER AMP. BOARD

POWER SUPPLY BOARD

SMOOTHING CAPACITORS

MAINS TRANSFORMER

Please tick box

CHASSIS

P.W. Q4 PROJECT Full, Details

CASE

HARDWARE

FASCIA

TEAK/WHITE SPEAKERS PR.

GOLDRING TURNTABLE

ELAC CARTRIDGE

MONEY ENCLOSED £
CHEQUE/P.O./MONEY ORDER

Block capitals please

NAME

ADDRESS

P.W.1

Another!
winner!

fane **MODE ONE**

**HIGH FIDELITY
LOUDSPEAKER KIT**



Recommended
retail price

£10.98

including V.A.T.

Consisting of a Fane Model 803 ultra-low resonance 8" speaker unit with PVC cone surround, and a Fane Model 303 high frequency pressure tweeter together with a printed circuit cross-over assembly with ferrite cored coils.

SPECIFICATION OF UNITS

	Model 803	Model 303
Overall Diameter	8"	3"
Natural resonance	30Hz	—
Main resonance	*35Hz	1200Hz
Magnet Pole Diameter	1"	3/4"
Magnet Flux Density	13,000 gauss	10,000 gauss
Frequency response	30Hz-8kHz	2kHz-17kHz
Impedance	8-15 ohms	8-15 ohms
Power Handling	*15 watts	*15 watts

Very easy to assemble, this boxed kit comes with acoustic foam damping material, panels, screws, wire, wiring diagrams and instructions to provide a remarkable loudspeaker assembly—a pair is ideal for stereo.

CABINETS for the 'Mode One' are available in Teak veneer finish. **SIZE** 15½" x 10½" x 9".


*When used with above cabinet.

Please send S.A.E. for fully descriptive leaflet.

Distributors to the wholesale and retail trade
LINEAR PRODUCTS LTD.
Electron Works, Armley, Leeds LS12 3SA. Tel. 630126

Manufactured by
FANE ACOUSTICS LTD.
Hick Lane, Batley, Yorkshire. Tel. Batley 6431

DABAR MN3 MIXER KIT

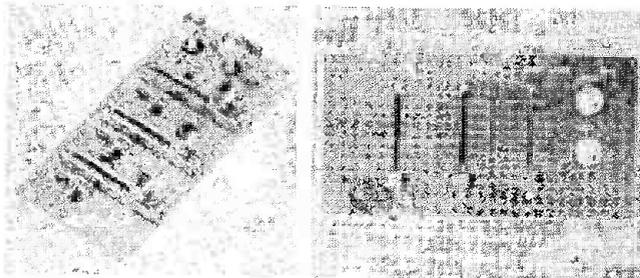

INTRODUCING THE NEW DABAR MINI THREE CHANNEL MIXER KIT WITH THE FOLLOWING FEATURES:

- ★ Three inputs easily adjustable to suit users input requirements, e.g., Mic., Tape, Disc., etc.
- ★ Uses advanced design with five integrated circuits.
- ★ Slider fader volume controls mount directly on P.C. board.
- ★ Full range bass and treble controls.
- ★ Guaranteed top grade components with fibreglass printed circuit board, ready-drilled and tinned.
- ★ Battery operated (2 x PP3) not supplied with kit.
- ★ Easy to follow assembly instructions (available separately 25p).
- ★ Attractive ready punched facia plate, available at extra cost, gives that professional finish to the unit.
- ★ Size: 9.5" x 4.8" x 2".


PRICE: KIT ONLY £11.00
FACIA PLATE £1.50
MANUAL AND ASSEMBLY INSTRUCTIONS 25p
AVAILABLE READY BUILT WITH FACIA £15.00

ALL PRICES INCLUDE V.A.T. & POSTAGE IN U.K.
S.A.E. ALL ENQUIRIES.

DABAR ELECTRONIC PRODUCTS

98, LICHFIELD STREET, WALSALL, STAFFS, WS1 1UZ.

CASED AMPLIFIERS

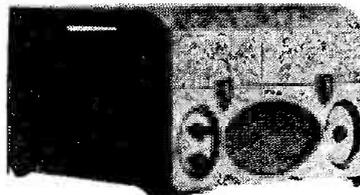

Polished wooden cabinet 14 x 13 x 9" containing a sensitive (20µV) 4 valve amplifier with tone and vol. controls. 3 watts output to 7 x 4" 3Ω speaker. Also included is a non-standard tape deck with solenoid operation. Supplied in good working condition complete with circuit diagram. Standard mains operation. Only £3 (£1 up to 200 miles, £1.25 over). Suitable cassette £1. Spare head 30p; Amplifier

chassis only, complete and tested £1.65 (37p).

71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, crystals, pots, switches, computer panels with transistors and loads of odds and sods. Still only £1.65 (37p).

COMPUTER PANELS

31b asstd. panels £1 (30p); 71b £2 (40p); 561b £13 (c. pd.). 12 top quality panels containing power transistors, IC's, trim pots, etc. £2 (30p); 100 boards £12 (£1).

NEW COMPONENTS

SCR's: 200V 5A 40p; 400V 5A 60p; BYZ10 1200V 6A 40p; OC16 20p, OC45 8p; OC71 8p; OC140 25p; OC170 15p; OC171 15p; BFY18 12p; BCY72 8p; 2N3055 35p; XC121 5p; BC107 8p; 2N3708 8p; 741C TO99 or 8 pin DIL 32p; 100V 8A diodes 20p; 3.9V or 27V 400mW zeners 7p; 22V 1W 10p.

BULK COMPONENTS

500 asstd. resistors £1 (20p); 300 capacitors, all types £1 (30p) 25 asstd. 10X crystals 75p (30p); 40 asstd. pots £1 (30p).

EX-COMPUTER EQUIPMENT

1200' 1/4" tape on 7" NAB spool 68p (30p); 1800' 3/4" tape on 10 1/2" NAB spool in case 68p (40p); Screw top electrolytic capacitors: 20,000µF 50V 60p (25p); 46,500µF 25V 60p (25p); 35,000µF 15V 40p (20p); 40,000µF 10V 40p (20p); 20,000µF 30V 40p (20p); 25,000µF 25V 40p (20p). Fans: 230V 50Hz 62" dia. blades 2800 rpm complete with grill and mounting plate £2.50 (40p). Heavy duty heat sinks 6 x 5 x 3" with 2 power transistors 80p (30p).

TEST GEAR

TF144G sig gen, 85kHz-25MHz, 1µV-1V output £16. BFO No. 8 audio oscillator, 50Hz-20kHz 10Ω or 600Ω output, metered. £9. Oscilloscopes in stock, ring for details.

ODD UNITS

Useful module containing OC35, 2x OC44, GET103, R's, C's, etc. 40p (10p). Cats whisker and crystal 15p; Unit with 2 modern c/o lever switches, 3 trim-pots. etc. 60p (10p).

ADD 10% TO TOTAL FOR VAT
Carr. in brackets; small parts 5p.

GREENWELD ELECTRONICS (PW8)

24 Goodhart Way, West Wickham, Kent. Shops at 21 Deptford Broadway SE8. Tel. 01-692 2009 and 38 Lower Addiscombe Road, Croydon.



MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

Mark Webster (Ipswich) reports good daytime reception of Radio Nottingham on 1520kHz and Radio Norway 1578kHz which broadcasts in English on Sunday afternoons from 1400hrs to 1430hrs GMT. During the evening Mark has logged RNE (Radio Nacional Espana, Spain) stations at Murcia 854kHz; Barcelona 737kHz; San Sebastian 773kHz; Madrid 584kHz; La Corunna 638kHz; Seville 683kHz together with BBC Local Radio stations at London 1457kHz; Sheffield 1034kHz; Medway 1034kHz.

Ross Galbraith (Lifford, Co Donegal) is using a domestic Mullard receiver and a Pye table model along with a 150ft longwire aerial. He reports BBC Radio Leeds at 1600hrs on 1106kHz; Radio Blackburn at 1230hrs on 854kHz; Radio Merseyside at 1500hrs on 1484kHz; Radio Carlisle at 1530hrs (testing on 755kHz); Radio Teesside at 1430hrs on 1546kHz; Radio Bristol at 1500hrs on 1546kHz; AFN Berlin at 2200hrs on 935kHz; Manx Radio at 1500hrs on 1594kHz and Radio Sweden at 2300hrs in English at 2300hrs on 1178kHz. Ross has been DXing for three years and has acquired 25 medium wave QSLs.

C. MacVicar (Felixstowe) has used his Sanyo 10 transistor portable with internal aerial to log BBC Radio London at 0835hrs on 1457kHz; Radio Medway at 1630hrs on 1034kHz; Radio Tirana, Albania at 2220hrs on 1394kHz; AFN low power relays at 2300hrs on 1502kHz and at 2000hrs on 611kHz; AFN Frankfurt 2130hrs on 872kHz; Trans

World Radio, Monte Carlo 2156hrs on 1466kHz; Madrid (EAJ2) at midnight on 917kHz; RNE Seville 0445hrs on 638kHz; RNE Barcelona 0500hrs on 737kHz.

Chris Webster (Ringwood, Hants) does his MW DXing with a Hallicrafter Super Pro, a PCR receiver, a 260ft longwire and a medium wave loop antenna located in the loft and controlled by string rotation and motorised tuning. He reports hearing Radio Nottingham on 1520kHz at the same strength as Radio Stoke 1502kHz; New York City (WINS) at 0515hrs on 1010kHz as strong as Lopik (Holland) on 1007kHz; a weak unidentified Middle East station on 1010kHz at 0100hrs (both India and Pakistan use this frequency). Chris has built the Audio Frequency Processor (Practical Wireless July 1972) which gives very good results with the PCR receiver.

The BBC Radio 4 medium wave service in North East England is now being radiated on 908kHz (330m) from Scarborough and Stagshaw (near Hexham) while a new transmitter serving Teesside will be brought into service on 1052kHz (285m). The BBC states that a number of changes were made in September 1972 to prepare for the introduction of local commercial radio; to permit the BBC Local Radio stations to transmit on the medium waves; and to release an additional frequency for use by the BBC's External Services. It was a part of the plan drawn up at that time that the BBC should change the frequency used in the North East. The BBC go on to say that 980kHz is also used by three other transmitters in the South of England and to avoid mutual interference it is necessary that all five transmit the same programme. Local news and weather will in future be transmitted on Radio 4 v.h.f. but items of local interest, including new and weather forecasts are broadcast by BBC Radio Newcastle on 1457kHz (206m) and BBC Radio Teesside on 1546kHz (194m).

VHF/FM DXING

by SIMON DAVID

THE f.m. DXing season is not over yet, although probably the more difficult catches will hibernate until the spring. During the coming months I shall be looking into my aerial system (thanks to Gordon King's recent articles). I rather fancy one of those twin array 6-element jobs hoisted atop a rotating mast. Rotators vary in price somewhat starting at around £23 basic and for driving one array only these lower priced units are quite good. If you are a multiple DX enthusiast with amateur bands aerials as well you will probably need a more robust rotator costing more than about £30. I still think that the prices are high for the job they do and would be reluctant to recommend one to anyone unless the anticipated field of coverage is likely to justify their use.

From readers' reports some very good results can be had with a three or four element aerial, so again before getting carried away with those impressive whoppers, make sure that the extra outlay is likely to be worthwhile.

There is very little further development on the tuner front judging by what I saw at the Audio Fair, but then these exhibitions are more concerned with just local reception of BBC or IBA programmes.


Talking of the latter reminds me that I read a very critical report in my local newspaper on the programme content of the new London IBA stations. Has any reader some comments on the technical side? I am trying at home to get a decent signal strength from them and they are sandwiched between the police and the BBC local radio stations. I was amused to hear about the expected re-allocation of that particular police frequency.

Last month I gave some details on BBC local radio stations and frequencies. From time to time I shall try to include more on European stations for a start here is the French listing.

V.H.F./F.M. TRANSMITTERS IN FRANCE

	MHz	MHz	MHz	kW
Carcassonne	88.2	90.9(S)	96.6	125
Le Mans	89.1	92.7	96.9(S)	100
Lille	88.8(S)	94.8	98.1	150
Limoges	89.4	93.0	97.5(S)	150
Nantes	90.6	94.2	99.0(S)	200
Niort	91.2	96.3	99.3	200
Reims	89.1(S)	96.9	98.7	150
Rennes	90.0(S)	93.6	98.4	100
Rouen	92.1(S)	93.9	96.6	100

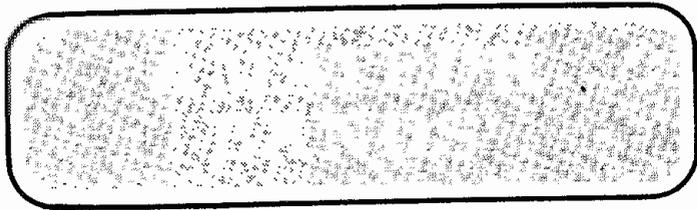These frequencies are subject to deviation by up to 150kHz. Frequencies used for stereo transmission are shown with (S).



SHORT WAVES

by **DAVID GIBSON, G3JDG**

THE festive season is with us once again, which is more than can be said for DX if the past month is any indication. Listening at the right times seems to be half the battle; like scanning topband at 0100 hours to hear the dulcet c.w. tweets of PY1RO and WB8APH.

Before you start stoking up with goodly portions of Christmas pud, how about some serious thought to Amateur Radio? Your receiver deserves a pressy; a good antenna? No room? How about the loft, a veritable haven for an invisible aerial/antenna?

All you need is some cheap single lighting flex and a packet of insulated staples (uninsulated ones will do if you're in a Scrooge-like mind). The wire can be simply stapled to the woodwork around the supporting beams in the roof, and the lead smuggled down to the receiver unobtrusively. Don't lay the wire on the floor, it could be a bit too close to mains wiring. Most average lofts can easily accommodate 100ft. of wire (twice round ending in a neat granny knot) and if you feed it into an a.t.u. before your faithful receiver "sees" it, you'll have an all-band aerial for only a few pence. Have a go; it'll keep you out of the kitchen and from under the XYL's feet.

What sort of a.t.u. Wind a coil with tinned copper wire spaced one turn between individual turns. All you need then is a tuning capacitor. You can wire the coil and capacitor up either in series or parallel and you can short out however many turns you like on the coil. Once you've found the optimum set up for each band, you can work out something a bit more permanent.

Another thought; how about a useful pressy for you? An Amateur Radio map of the world showing countries with their call signs costs only a few pence—well, about 50p for a small one. You could also treat yourself to an up-to-date countries list, too. This is a must because of the amazing rapidity with which call signs seem to change over night.

You should also join your nearest Amateur Radio Club. There, you can ask all sorts of questions and be virtually certain that someone in the club will

have the answers. It's like having access to a complete Amateur Radio brains trust; free!

Lastly, before I rush off to order the canary (Ok, so I'm the one in a Scrooge-like mood), don't forget the numerous Christmas morning nets. Topband is a favourite with two metres running a close second.

Readers' Logs

Well bless my base-loaded bodkin, first log out of the postbag covers four bands. **Stephen Fletcher** (Bromsgrove, Birmingham) borrowed a KW2000 from the Bromsgrove and District Amateur Radio Club and poked the end of a 150ft. wire in the aerial socket. Results of this are as follows. On 3.5MHz; ZL3GS, ZL4BA, ZL4BX. Up to 7MHz (brave lad); PA25WTA, SM7CRW, 4U1ITU. Twenty parted with; CR7IC, CT1DW, EL2BA, ET3DS, IS0RUA, JA1AAT, KP4DHD, PY2DVX, PY6FH, PY7VJS, SV1DXO, VE1BAB, VE2BPE, VE3BHR?, VK2AM, VK2ATB, VK2BNG, VK3AD, VK3ANQ, VK3RV, VK3SX, VK3TE, VK7IL, VO1CV, VO1KF, VP2AZA, VP9GE, VU2MA, YV5CVE, ZC4SB, ZD7SD, 3V8DM, WA3SBW/6Y5, 9G1GG, 9H1CD, 9M2TR. Stephen mentions that the Club meets on every second Friday of the month.

Goodie bagger **John Turner** has heard some juicy morsels of DX on 7MHz. He runs a Pye Cambridge receiver model 1101 and has an 85ft. end fed antenna. The unit now has a b.f.o. fitted (*Practical Wireless* design using varicaps from the Take Twenty series). Best of forty included; CR7IC, EL2DL, FL8OM, JA2BAY, TR8DG, VU2AIK. A peep at 21MHz revealed signals from; A2CCY, A4XFF, A4XFJ, CE3IF, CN8HD, CN8PO, EL2DG, EL9C, EP2SP, EP2TW, ET3DS, FP8DH, HC1ME, HI8LI, HK4CJB, KA6BQ, KG4DS, KP4BCL, KP4ZM, KV4FC, KZ5JM, KZ5OH, MP4BJR, OA4AQ, A OD5CS, TI3BVF, UA0AR, UI8NE, VK5EL, VO1BT, VP1KR, VP2SV, VP8KF, VP9AD, VU2DK, VU2GVG, XT2AJ, YS3FH, ZD7FT, ZS1ZE, 3B6CF, 3D6AW, 3V8DM, 5H3AP, 5N2ESH, 5X5NK, 7X0WW, 9G1HG, 9H1AF, 9H1AQ, 9H4L, 9H5D, 9J2EP, 9J2WR, 9M2DQ, 9X5VA, 9Y4BO.

Michael Best (Cwmbran, S. Wales) uses an R209 Mk. II and describes his antenna thus, ". . . is coax thro' the window and over the roof in a West/East direction terminating in an 8ft. Vee". (Doesn't get many signals but it sure confuses the birds). The best of Best on 14MHz is; A4XFD, EA1MU, EP2WOU, VE1ADU, VE3EWJ, ZL4LL, ZM1AJZ, 9H1NJD. On 7MHz, squeaks were heard from; KZ5PW, OD6MV, VE4SI, VK3ZL, VK7AZ, ZL1BKX, ZL4BQ.

R. Donaldson (Trimdon Colliery) is a mine of information on happenings around 3.5MHz. The gear is a CR7OA Mk. II, 19 set and "several aerials". The 3.5MHz log reads; MP4MA, WA2UNS, WA4ISZ, VE6MC, ZL4KE, 5B4LR, 7X0WW, 7X2MD. A perusal of 14MHz brought forth; HB9TZ, JA9JNF, JA9SP, K6OFN/MM, PY1BOU, VE3VOA, VE6UM, VE8YK, VK7NE, VO1FX, VQ9DAS, YV5CKR, ZD8RR, 4X4DK, 9Y4LK. Pickings from 21MHz are; MP4BJD, PJ1HV, ZK5AFZ, 4H4OK, 6W8WL, 9Q5WQ.

BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 59 Windrush, Highworth, Swindon, Wiltshire, SN6 7DT.

Medium Waves Logs to Charles Mollóy, 132 Segars Lane, Southport, PR8 3JG.

VHF/FM Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

AMATEUR BANDS

Short Wave/VHF

Logs in alphabetical order please by 15th of the month to David Gibson, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.

ALL OUR PRICES INCLUDE V.A.T.

BSR LATEST SUPERSLIM STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 13 1/2 x 11 1/2 in.



Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO and MONO XTAL **£8.25** Post 25p.

PORTABLE PLAYER CABINET £4.50 Modern design. Black rexine covered. Silver front grille. Chrome fittings. Motor board cut for BSR deck. Post 25p.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2 x 10 x 8 1/2 in. 3 watts per channel. plays



all records 33 rpm, 45 rpm. Separate volume & tone controls. 240v AC mains. **Bargain Price £25** 85p carriage

SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes Type A or 0 to 6 hours Type B. Makers last list price £4.50. Brand new and fully guaranteed. Fully insulated. **OUR PRICE £1.65 or £3 pair** Post 25p (PLEASE STATE TYPE A OR B WHEN ORDERING)



WEYRAD P50—TRANSISTOR COILS

1/2W Ferrite Aerial. 85p. P50/1A/C. 40p. F P50/2C/40 470 k/s. 40p. rd I.F. P50/3C. 40p. pare Cores. 200p. 3p. OUBR Core 8 x 1/2 in. 20p. 6 x 1/2 in. 20p. 3 x 1/2 in. 10p.

VOLUME CONTROLS

K. ohms to 2 Meg. LOG or IN. L/S 15p. D.P. 25p. TERELO L/S 65p. D.P. 75p. Edge 5K.S.P. Transistor 25p.

Driver Trans. LFDT4. 65p. Printed Circuit, FCA1. 65p. J.B. Tuning Gang. 65p. Weyrad Booklet. 10p. OPT1. 65p.

3in & 10in ELAC HI-FI SPEAKER

Equal cone plasticised roll around. Large ceramic magnet. 50-16,000 c/s. Mass resonance 55 c/s. 8 ohm impedance. 10 watt. 10 in. 12 watt music power. **£3.75** Post 25p



E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With twin tweeters and crossover. 10 watt. Rate 3 or 8 or 15 ohm. As illustrated) **£4.50** Post 25p

With flared tweeter cone and ceramic magnet. 10 watt. Mass res. 45-60 c/s. Flux 10,000 gauss. Rate 3 or 8 or 15 ohm. Post 25p **£2.75**

BOOKSHELF CABINET £5.50 Post 25p Size 16 x 10 x 9 in. teak finish

SET OF 3 MOTORS FOR COLLARO STUDIO TAPE DECK £2.50 Post 50p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides x 4 in. 45p; 8 x 6 in. 55p; 10 x 7 in. 65p; 12 x 8 in. 85p; 4 x 9 in. 90p; 16 x 8 in. 90p; 12 x 3 in. 50p; 16 x 10 in. £1. ALUMINIUM BOXES 3 x 3 x 3 in. 60p; 4 x 4 x 4 in. 70p; 4 x 4 x 4 in. 80p; 9 x 4 x 4 in. £1; 12 x 4 x 4 in. £1-30 ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 90p; 8 x 6 in. 15p; 4 x 3 in. 16p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 8 in. 28p; 6 x 6 in. 28p; 14 x 8 in. 34p; 12 x 12 in. 40p; 16 x 10 in. 50p AXOLIN PANEL 10 x 8 in. 15p.

RADIO COMPONENT SPECIALISTS

Minimum post 20p.

Illustrated Colour Brochure, Radio Books & Components Lists 10p.

ANOTHER RGS BARGAIN!

4 Transistor Mono Amplifier

Powerful 3 watt outPut. 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. **£5.95** Post 25p Size 5in. wide x 4in. deep x 3in. high. Suitable 7" x 4" speaker, £1.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer. Input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. **PLEASE STATE VOLTAGE REQUIRED. £2.20** Post 20p Details S.A.E. Size 3 1/2 x 1 1/2 in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-18v. or H.T. line 200-300V. d.c. operation. Size 1 1/2" x 1 1/2" x 1". Response 25 c/s. to 25 Kc/s. 26 dB gain. For use with valve or transistor equipment. **99p** Post 20p Full instructions supplied. Details S.A.E.

E.M.I. WOOFER AND TWEETER KIT

Woofer 10 1/2 x 6 1/2 in. Ceramic Magnet, 44oz. 13,000 lines, Tweeter 3 1/2 in. square, 10,000 lines. Crossover condenser full instructions supplied. Impedance 8 ohms. Power 12 watts. **£5.75** Post 25p.

BRITISH FM/VHF TUNING HEART

88 to 108 M/GS British made. 2 Transistors ready aligned requires 10-7 M/GS I.F. Complete with tuning gang. Connections supplied but some technical experience essential. **Our price £3.95** Post 20p

MAINS TRANSFORMERS

All post 25p each
Eagle MT12 12-0-12V 50mA 90p
250-0-250 80 mA. 6-3V 3-5A 6-3V 1A or 5V 2A £2.50
350-0-350 80 mA 6-3V 3-5A. 6-3V 1A or 5V 2A £3.00
300-0-300V 120mA. 6-3V 4A C.T.; 6-3V 2A £3.25
MINIATURE 200V 20mA. 6-3V 1A 2 1/2 x 2 1/2 x 2in 75p
MIDGET 220V 45mA. 6-3V 2A 2 1/2 x 2 1/2 in 90p
HEATER TRANS. 6-3V 3A 60p
GENERAL PURPOSE LOW VOLTAGE. Trapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £2-90
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2-25
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2-25
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £3-80
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8-75
5, 8 and 18V 5 amp £1-20. 3 amp, 3, 5, 8, 10, 13 and 50-5V £1-30. Ditto 5 amp. £1-50; 6-0-6V 500mA 90p
9V 1 amp 95p 12V 300mA 75p 12V 600mA 85p 12V 750mA 95p. 40V 1 amp £1-75.
AUTO TRANSFORMERS, 115V to 230V or 230V to 115V 150W £2-25; 500W £6-25; 750W £10; 1000W £15
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V, 1 1/2 amp £1-50; 2 amp £1-80; 4 amp £2-50
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4-50.
FULL WAVE BRIDGE CHARGER RECTIFIERS; 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **OUR PRICE £10** Carr. 50p Famous make. (Value £19)
Can be used as 800W auto transformers 240-110V.
IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS

2/350V .. 14p	100/25V .. 10p	32+32/350V .. 40p
4/350V .. 14p	250/25V .. 14p	50+50/350V .. 50p
8/450V .. 18p	500/25V .. 20p	60+100/350V .. 85p
16/450V 22p	1000/25V .. 35p	32+32/250V .. 20p
32/450V 35p	1000/50V .. 47p	32+32/450V .. 60p
32/500V 50p	8+8/450V .. 22p	350+50/325V .. 55p
25/25V .. 16p	8+16/450V 25p	100+50+50/350V 55p
50/50V .. 10p	16+16/450V 40p	


LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.
500mF. 12V. 15p; 25V. 20p; 50V. 30p.
1000mF. 12V. 20p; 25V. 35p; 50V. 47p; 100V. 70p.
2000mF. 6V. 25p; 25V. 42p; 50V. 57p.
2500mF. 50V. 65p; 3000mF. 25V. 47p; 50V. 65p.
5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p; 50V. 95p.

CERAMIC 1pF to 0.01mF. 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-0.1 4p. 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1% 2.2-500pF 5p; 560-2.200 pF 10p; 2.700-5.600pF 20p; 6.800pF-0.01. mfd 30p; each. TWIN GANG. "0-0" 208pF+176pF. 65p; 500pF standard 75p; 365+365 with 25+25pF Slow motion drive 50p. SHORT WAVE, SINGLE. 10pF 30p; 25pF 55p; 50pF 55p. NEON PANEL INDICATORS. 250V AC/DC Amber 20p. RESISTORS. 1/4W, 1/2W, 1W, 20% 1p; 2W, 5p, 10Ω to 10M. HIGH STABILITY. 1/4W, 2% 10 ohms to 6 meg., 10p. Ditto 5% Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each; 0.5 ohm to 8-ohms 10p. TAPE OSCILLATOR COIL. Valve Type 35p.

NEW MODEL "BAKER LOUDSPEAKER" 12in. 50 watt GROUP 50/12 8 or 15 ohm high power full range. Quality—Professional. £17.60

BAKER MAJOR 12" £9.90

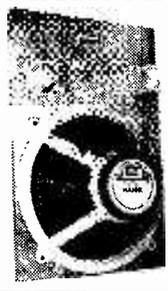

Post free 30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated. Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£12.50** Post free Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS Post free

'Group 25'	'Group 35'	'Group 50'
12 inch 25 watt 3 or 8 or 15 ohm	12 inch 35 watt 3 or 8 or 15 ohm	15 inch 50 watt 8 or 15 ohm
£8.80	£9.90	£22

TEAK VENERED HI-FI SPEAKER CABINETS

For 12in. or 10in. dia. speaker 18 x 13 x 9in. £9-90 Post 25p
For 13 x 8in. or 8in. speaker 18 x 10 x 9in. £5-60 Post 25p
For 8 x 6in. speaker 16 x 8 x 6in. £4-40 Post 25p
For 6in. and tweeter 12 x 8 x 6in. £4-00 Post 25p
LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft

GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns, Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/2 in. Suitable Tweeter £2-00. **£4**



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watt, 3 ohm or 15 ohm models. **£1.90** Post 20p Crossover 95p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-18kc/s, 10W 8 ohm or 15 ohm £1.95.
De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm £3-50.
CROSSOVERS TWO-WAY 3000cps 3 or 8 or 15 ohm 95p.
LOUDSPEAKERS 3 OHMS. 7 x 4in. £1-25; 6 1/2 in. £1-50.
8 x 5in. £1-60 8in. £1-75; 10 x 6in. £1-90; 10in. £2-00.
SPECIAL OFFER: 80 ohm, 2 1/2 in.; 2 1/2 in. 35 ohm. 2in., 3in., 25 ohm. 2 1/2 in. dia., 5in. dia., 6" x 4" £1 EACH 15 ohm, 3 1/2 in. dia.; 6 x 4 in.; 7 x 4 in.; 8 x 5 in. I TYPE 3 ohm, 2 1/2 in.; 2 1/2 in.; 3 1/2 in.; 5in. dia. (6 x 4 in. 8 ohm £1-50)
RICHARD ALLAN TWIN CONE LOUDSPEAKERS: 8 in. diameter 4 watt £2-50. 10in. diameter 5 watt £2-50; 12 in. diameter, 6 watt £2-95.
VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO. 3, 8 and 15 ohms, 80p. Mike trans. mu metal 100:1 £1-25.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. **£49** Carr. £1-00 Separate treble and bass controls. SUPER VALVE MODEL 100 WATT CALLERS ONLY 25p.



BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4.95

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **£3.95**

TWO CHANNEL STEREO VERSION £5.95

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, treble and bass controls 18v. DC operation. £4.50

COAXIAL PLUG 13v. PANEL SOCKETS 10p. LINE 18p

OUTLET BOXES, SURFACE OR FLUSH, 25p.
BALANCED TWIN FEEDER 300 ohms 5p yard. JACK SOCKET Std. open-circuit 14p, closed-circuit 25p. Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 20p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS 5p; CERAMIC 8p; GANS 5p.

REVERSIBLE 4 POLE MOTOR £1.95

1,400 r.p.m. Reversible 42 Watt. Post 25p spindle 1 1/2" x 7/32", size 3 1/2" x 3". As illustrated. With Cooling Fan 240V A.C.

E.M.I. GRAM MOTOR £1-00 Post 25p. 120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 x 2 1/2 in.

SPECIAL OFFER 3 inch panel meter 50 micro amps. unusual scale requires recalibrating. Post 25p **£1.75**

337 WHITEHORSE ROAD, CROYDON

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

INDICATOR UNIT TYPE 1

Radar test unit with 3" CRT VCR138 green screen, med persistence okay for scope unit, meter 50 Ua 4" dia scale 0 to 5 linear, 19 misc valves inc min and octal. Klystron unit tunable S band, complete in case size 17 x 11 x 16" as internal P.U. not 50c/s, supplied with circ, except for power trans all P.U. components can be used at 50c/s. Available new cond with leads and Cal chart £12.45 or good cond less leads and cal chart £10.45.

ELECTRONIC MULTIMETERS

AVO type CT38 for 200/250v mains, 97 ranges covering AC/DC Volts, Amps, Res, Watts, supplied with copy of Inst book and circ, tested with probe and multipliers, further details on request. £21.

POWER UNIT 917

I/P 230v 50c/s O/PS-2.2Kv at 5 Ma, 600v DC 160 Ma (two separate 300v 160 Ma supplies), 4v 2a for CRT heaters, 6.3 at 3 and 2 amps, complete in case, these will supply many surplus 3/6" Ind units, with circ. £6.38.

TEST SET 210

Test osc covering range 20 to 88 Mc/s in 3 bands also as noise generator, 2 Mc/s xtal check, pulse mod, requires supplies of 250v DC at 60 Ma and 6.3v. Supplied with Cal chart and Ae, in case used good cond £5.50.

TELEPRINTERS

Creed type 7B used good cond £8.25. TCS Rx 1.5 to 12 Mc/s in 3 bands RF and 2xIF, BFO, etc supplied tested, fair ext cond, req 220v at 100 Ma and 12v AC £14.85 few only.

METERS

270 deg scale 0 to 20 FSD 1 Ma also in same case centre reading meter 100-0-100 Ua centre mark only, flag type on/off ind, size 3 1/4" x 3 1/4" sq, glass 2 1/2" dia, ex aircraft meter. Possible use as car rev counter and battery voltage indicator, ex equip £3.

DUAL GANG POTENTIOMETER

10K ea section, 2 1/2" dia, W.W. with knob and dial, supplied with circ of transis A.F. osc £1.20.

YAXLEY SWTS

4p 11w 4b 76p, 4p 4w 2b 40p, 3p 6w 3b 40p all supplied with knobs.

LAMP ASS

as red, green, white lenses with 24v MBC lamps 30p

SILICON DIODES

100 PIV 20 amps 4 for £1, 600, PIV 12 amps 4 for £1, 200, PIV 8 amps 4 for 66p, 800 PIV 750 Ma 15 for £1.10.

SCREENED BOX

ass with 12x 25/125pf trimmers 12x .1% res 60p

HEAD AND MIKE

set for 19 set new, m.c. type £1.80.

TRANSFORMERS

all 230v 50c/s. 1125-0-1125v 565 Ma £7.70. 415-143-143-415v 360 Ma on 415 and 120 Ma on 143v £3.40. L.T. type sec 27v 41 amps cont rat. £13.20. 450-0-450 at 200 Ma, 5v 3a and 6.3v 3a twice £3.30. Fil type 6.3 3a twice with ct and 6.3 1a also similar 6.3 8a ct, 6.3 2a 6.3 1a price either type £1.40.

VALVES

5U4, 6X5, 6SN7, EF91, 85A2, 12AT7, 6AK5, 6BH6, 6H6, 6Y6, 2X2, 6SK7M, EB91, 6N7, 6J5G, 6V6G, 6J6, 12AX7, 6AK6, 6X4, CV173, EF50, 6BA6, 6AS6, CV2179 (sim N78) OB2, 12J5, 12SJ7, 12A6, any 3 for 60p also 5763 55p, QQVO3-20A £2.

MISC ITEMS

W.M. Class D No. 2 mains/Batt. good cond £12, Sil Bridge rect 200 PIV 200 amps £15, 3 phase 50c/s 600 Va isolation trans £17.60, Cossor 1035 and 1049 DB scopes tested with circ £22 ea. R1155 Rx with P.U. and spk £23.

ALL ABOVE PRICES INCLUDE CARR. AND VAT,
CARR. CHARGES APPLY TO MAINLAND ONLY,
ALL GOODS NEW OR GOOD COND. S.A.E. WITH
ENQUIRY OR LIST.

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD, S9 5HL
Tel. 44278 (0742)

'WORTH WAITING'

A JOINT ANNOUNCEMENT FROM

IMHOFS



Due to contractual commitments both at home and overseas Eddystone Receivers are in short supply. Whilst the manufacturers are doing their best to meet these requirements we would ask your forbearance and understanding of the present delivery situation. Limited supplies of the ever popular EC10 and EB37 will continue to be available. Apologies for the necessity to "DIM THE LIGHT" — normal brilliance will be resumed as soon as possible.

IMHOFS

112-116 New Oxford St.
London WC1A 1HJ
telephone 01 636 7878

EDDYSTONE RADIO Ltd.

Alvechurch Rd.
Birmingham B31 3PP
telephone 021 475 2231

R85

PW

Q4 PROJECT

PCB'S AND COMPONENTS
FOR THIS AND OTHER PW PROJECTS

REVERBERATION UNIT
8 WATT AMPLIFIER & PRE-AMP
LOUDHAILER PRE-AMP & SIREN GENERATOR
VIBRASONIC GUITAR PRE-AMP
DIGITRONIC DIGITAL CLOCK

AND ALSO FOR MANY P.E. PROJECTS

SEND AN S.A.E FOR OUR FREE LIST

PHONOSONICS

Dept PW1, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
MAIL ORDER ONLY

SPECIAL OFFER: Computer boards, ex-equipment with a good selection of semi-conductors, resistors, capacitors and other useful items. 5 for 75p including V.A.T.

An extensive range of Semi-conductors; Electrolytic capacitors; Mylar, Polyester and Ceramic capacitors; Fixed and Variable resistors. Brand new by well known manufacturers.

Send S.A.E. for comprehensive list to:—

W. P. COMPONENTS
7 Brook Avenue, Edgware,
Middlesex

TAKE 20

DAVID ANDREWS

No. 56

TRAFFICATOR AUDIO REPEATER

A series of simple transistor projects, using not more than twenty components.

IN Take 20 we try to bring you good "value-for-money" experimental projects. These days one can hardly get better value than the electronic capabilities of some of the integrated circuits that are available on the market. Because of this we have decided to incorporate IC's into some of our projects from time to time. This month we are using a very common IC, the SN7400, in an unusual role.

Circuit


Two of the four "gates", A and B, are cross coupled by C1 and C2 to form a very simple astable multivibrator, the output of which is directly coupled to the third gate C that acts as a low power driver stage for a miniature loudspeaker. The fourth gate D is not used. No doubt we are breaking all sorts of rules in doing this but the fact remains that a 35Ω speaker can be driven reliably without over-running the output of the third gate. We recommend that you do not push your luck too far by reducing the loudspeaker impedance to less than 35Ω but you can use any speaker or earpiece having a higher impedance.

Application

The output level is quite high which allows the circuit to be used for all sorts of applications, from a morse practice oscillator to an electronic door


★ components list

R1	100Ω ½W	C1	0.22μF
R2	100Ω ½W	C2	0.22μF
R3	4.7kΩ ½W	C3	50μF 15V
R4	4.7kΩ ½W	IC1	SN7400
LS1	Speaker, 35Ω minimum impedance.		

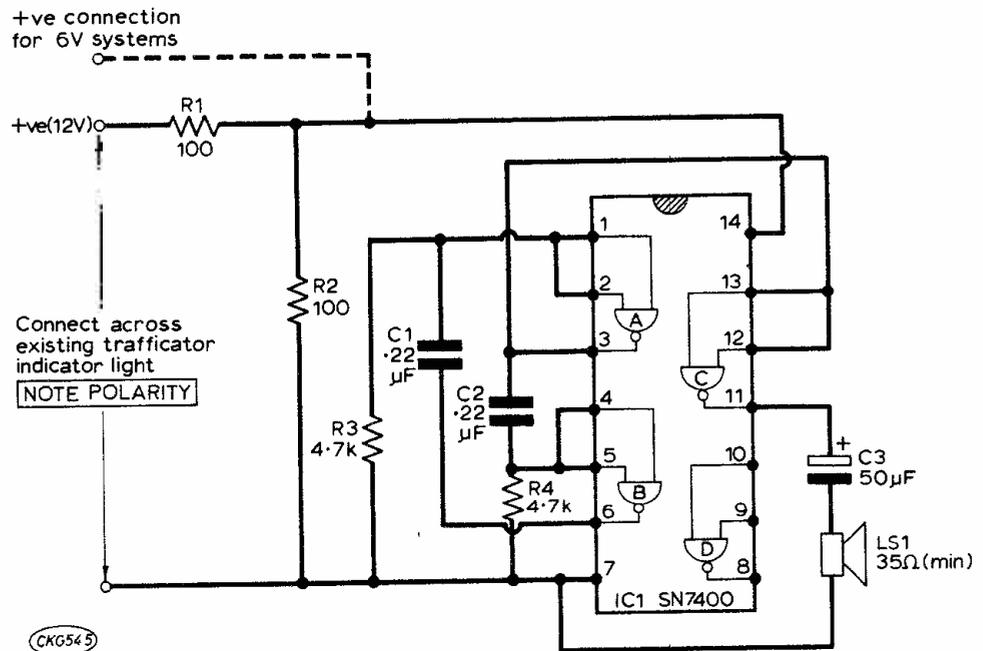

CKG545

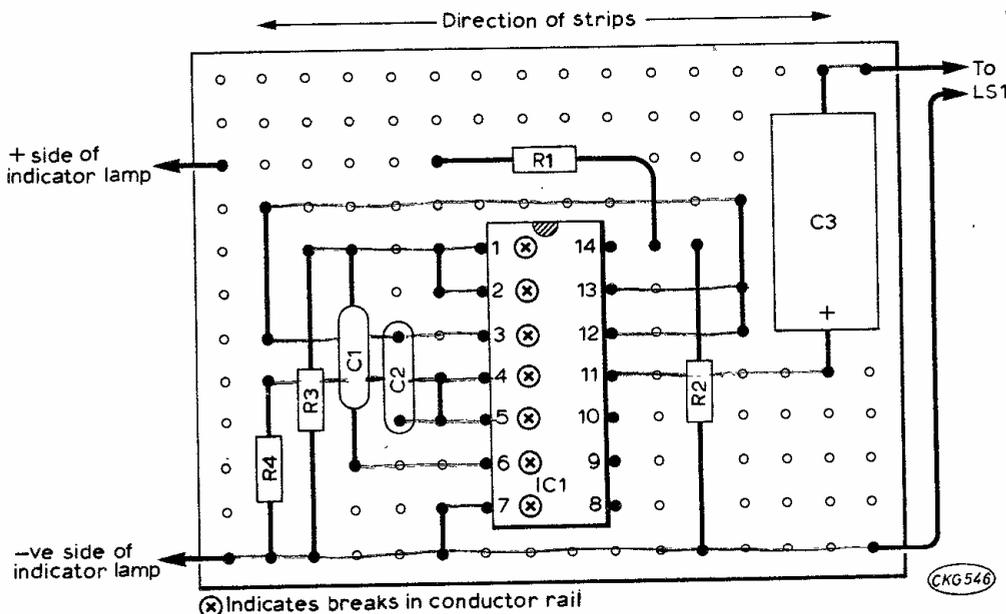▲ Fig. 1: Circuit of audio repeater for 6 or 12v operation. Observing correct polarity is essential.



◀ Fig. 2: Layout on veroboard of repeater shown in Fig. 1. Circuit must be isolated from chassis.

alarm and on to our suggestion, which is a repeater for trafficators on cars where the warning light is not very obvious and the tick of the relay is not very loud.

The circuit needs a supply voltage of between 4.5 and 6V so for 12V systems it is necessary to incorporate the voltage droppers R1 and R2 which **MUST** be of 1/2W or greater rating. For 6V systems these resistors can be omitted and the supply fed in according to the dotted rail of Fig. 1. As a trafficator repeater the best place to get the supply power is from across the existing indicator lamp. The bleep from the circuit will follow the same rhythm as the flashing of the lamps. The circuit will work for positive or negative earth cars provided you connect the repeater across the lamp with the correct polarity and do not allow any of the circuitry to touch the car's chassis.

CURING RADIO INTERFERENCE

—continued from page 877

components are used. Shunting all decoupling electrolytics with 1000pF to 0.01µF ceramic capacitors can help to reduce the interference in difficult cases, plus trying the usual RF filtering of inputs and outputs. In extreme cases, changing the particular IC has cured the effect.

SCREENING

In practice, no real benefit has been found from screening equipment cabinets: aluminium foil has been tried but as bonding is difficult and short circuits a high probability, it is not likely to make much difference in the level of interference to audio equipment. Earthing the metalwork of the amplifier can make a considerable improvement, although mains socket earths are not usually very effective at RF and can sometimes even give rise to increased interference. What is required is a short, stout connection to a rising water main or an earth spike.

Finally, one way in which it is less common for RF interference to reach audio amplifiers is via the mains lead. Whilst clicks and motor noise will easily travel long distances on the cable in the street, attenuation of frequencies above about 2MHz is considerable. It has, though, been noticed on rare occasions that the last few feet of mains lead to an amplifier have acted as an aerial and injected RF into the equipment. Capacitors around 0.1µF, suitable for 250VAC working, connected between live and neutral and between neutral and earth will usually dampen the lead enough, fitting being done inside the amplifier away from prying fingers. ■

An expanded version of this article, covering radio interference to TV receivers, will be published in the January 1974 issue of our sister magazine **TELEVISION** to be published on 17th December.

The Editor and Staff of
Practical Wireless
wish all readers a Merry
Christmas and a Happy
New Year



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn - and help qualify yourself for a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing *actual projects you enjoy* - making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No mathematics, no soldering - yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits - assemble components - build things - experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course **AT NO EXTRA CHARGE!** And this is a course anyone can afford. You can even pay for it in easy payments - in fact you could make extra cash from spare-time work when you've turned yourself into a qualified man through B.I.E.T. training.

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who *makes* things, not just another of the millions who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own powerful radio. And after the course you can go on to acquire high-powered technical qualifications, because B.I.E.T.'s famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book - see how easy it is - read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** QH BPW47
Aldermaston Court, Reading RG7 4PF

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS

AGE



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m. - 5 p.m.

PLEASE ADD 10% VAT

RESISTORS

1/2W Iskra high stability carbon film—very low noise—capless construction.
1/2W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.
1/2W 2% ELECTROSIL TR5.

Power watts	Tolerance	Range	Values available	Price
1/2	5%	4.7Ω-2.2MΩ	E24	1p
1/2	10%	3.3MΩ-10MΩ	E12	1p
1/2	2%	10Ω-1MΩ	E24	3p
1/2	10%	1Ω-3.9Ω	E12	1p
1/2	5%	4.7Ω-1MΩ	E12	1p
1/2	10%	1Ω-10Ω	E12	6p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/2W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch, 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107 15p	AF126 20p	BF115 25p	OC42 12p	2N3707 12p
AC126 12p	AF139 32p	BF173 20p	OC44 12p	2N3708 10p
AC127 15p	AF178 32p	BF177 28p	OC45 12p	2N3709 11p
AC128 15p	AF180 40p	BF178 32p	OC70 12p	2N3710 11p
AC131 12p	AF181 40p	BF179 32p	OC71 12p	2N3711 11p
AC132 12p	BC107 12p	BF180 32p	OC72 12p	2N3819 32p
AC176 15p	BC108 12p	BF181 32p	OC81 12p	2N4062 12p
AC187 22p	BC109 12p	BF194 14p	OC82D 12p	2N4286 20p
AC188 22p	BC147 12p	BF195 14p	2N2646 60p	2N4289 20p
AD140 50p	BC148 12p	BF197 15p	2N2904 20p	40360 35p
AD149 45p	BC149 12p	BF200 32p	2N2926 10p	40361 35p
AD161 33p	BC157 14p	BFY50 20p	2N3054 58p	40362 40p
AD162 36p	BC158 14p	BFY51 20p	2N3055 60p	40408 40p
AF114 20p	BC159 14p	BFY52 20p	2N3702 13p	ZTX108 15p
AF115 20p	BC187 22p	BUY105 225p	2N3703 12p	ZTX300 15p
AF116 20p	BD131 75p	OC26 45p	2N3704 13p	ZTX302 20p
AF117 20p	BD132 75p	OC28 50p	2N3705 12p	ZTX500 15p
AF118 38p	BD133 75p	OC35 50p	2N3706 11p	ZXT503 20p

ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

WIRE WOUND POTS. 3W, 10, 25,

50Ω and decades to 100kΩ, 35p.

DIODES

RECTIFIER	Voltage	Current	Price	SIGNAL	Price
BY127	1250V	1A	12p	OA85	7p
1N4001	50V	1A	7p	OA90	5p
1N4002	100V	1A	8p	OA91	5p
1N4004	400V	1A	8p	OA202	7p
1N4006	800V	1A	10p	1N4148	5p
1N4007	1000V	1A	10p	BA114	8p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log. or lin. 40p.
DUAL GANG, 10K + 10K etc. log. or lin. 60p.
KNOB FOR ABOVE, 12p.
FRONT PANEL, 65p.

18 Gauge panel 12in x 4in with slots cut for use
with slider pots. Grey or matt black finish complete
with fixings for 4 pots.

BRUSHED ALUMINIUM PANELS

12in x 6in, 25p
12in x 2in, 10p
9in x 2in, 7p

THYRISTORS

2N5060 50V 0.8A 30p
2N5064 200V 0.8A 47p
106F 50V 4A 40p
106D 400V 4A 55p

ALUMINIUM BOXES

AB7 2 1/2" x 5 1/2" x 1 1/2"	50p	AB14 7" x 5" x 2 1/2"	84p
AB8 4" x 4" x 1 1/2"	50p	AB15 8" x 6" x 3"	108p
AB9 4" x 2 1/2" x 1 1/2"	50p	AB16 10" x 7" x 3"	122p
AB10 4" x 5 1/2" x 1 1/2"	50p	AB17 10" x 4 1/2" x 3"	108p
AB11 4" x 2 1/2" x 2 1/2"	60p	AB18 12" x 5" x 3"	120p
AB12 3" x 2" x 1"	44p	AB19 12" x 8" x 3"	160p

HEATSINKS—REDPOINT

2W 24p	4W 45p	TO5 Clip 5p	TO1 Single 5p
3W 36p	6W 60p	TO18 Clip 5p	TO1 Double 8p

TRANSFORMERS All have 240V primary

MT30/2	0-12-15-20-24-30V	2A	£2.85
MT50/1	0-19-25-33-40-50V	1A	£1.90
MT50/1	0-19-25-33-40-50V	1A	£2.55
MT50/2	0-19-25-33-40-50V	2A	£3.50
MT60/1	0-24-30-40-48-60V	1A	£2.10
MT60/1	0-24-30-40-48-60V	1A	£2.80
MT60/2	0-24-30-40-48-60V	2A	£3.80

MULLARD POLYESTER CAPACITORS C206 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2 1/2p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7 1/2p, 0.33μF, 11p, 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 3 1/2p, 0.15μF, 4 1/2p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7 1/2p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3 1/2p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6 1/2p, 0.47μF, 8 1/2p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 0.05μF, 0.1μF, 0.2μF, 0.5μF, 1μF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS

(μF/v) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p, 47/63, 100/40, 150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1000/4, 10p, 470/10, 680/6.3, 11p, 100/63, 150/63, 220/63, 1000/10, 12p, 470/25, 680/16, 1500/6.3, 13p, 470/40, 680/25, 1000/16, 1500/10, 2200/6.3, 18p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1μF 35V	2.2μF 35V	22μF 16V	12p
0.22μF 35V	4.7μF 35V	33μF 10V	
0.47μF 35V	6.8μF 25V	47μF 6.3V	
1.0μF 35V	10μF 25V	100μF 3V	

VEROBOARD

0.1	0.15
2 1/2 x 3 1/2	22p
2 1/2 x 5	24p
3 1/2 x 3 1/2	24p
3 1/2 x 5	27p
17 x 2 1/2	75p
17 x 3 1/2	78p
17 x 5 (plain)	82p
17 x 3 1/2 (plain)	60p
17 x 2 1/2 (plain)	42p
2 1/2 x 5 (plain)	12p
2 1/2 x 3 1/2 (plain)	11p
Pin insertion tool	52p
Spot face cutter	42p
Pkt. 50 pins	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable, 22p/metre.

BATTERY ELIMINATOR

£1.50
9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF 64V	74p	2500μF 64V	80p	4500μF 16V	50p
2500μF 40V	74p	2800μF 100V	£2.60	4500μF 25V	£1.60
2500μF 50V	58p	3200μF 16V	50p	5000μF 50V	£1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p	0.047μF 13p	0.22μF 20p
0.022μF 12p	0.1μF 13p	0.47μF 22p

POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values, 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector £5.20, 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

PRINTED BOARD MARKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

METERS

1 1/2" Scale-500uA, 1mA, 10mA, 100mA £1.90

BULGIN MAINS CONNECTORS

3 Pin 1 1/2A	Chassis Plug 10p	3 Pin 1 1/2A	Chassis Socket 18p
	Line Socket 13p		Line Plug 13p
3 Pin 3A	Chassis Plug 10p	3 Pin 3A	Chassis Socket 21p
	Line Socket 14p		Line Plug 23p
3 Pin 5A	Chassis Plug 16p	2 Pin 5A	Line Plug 20p
	Line Socket 15p		

THERMISTORS

VA1005	15p
VA1026	15p
VA1033	15p
VA1055S	15p
VA1066S	15p
VA1077	15p
R53	£1.35

ROTARY MAINS SWITCH

D.P. 2A 32p

LINEAR IC's

709	14 pin DIL	40p
741	8 pin DIL	40p
741	14 pin DIL	38p
723	14 pin DIL	95p
747	14 pin DIL	85p
748	8 pin DIL	45p

WAVECHANGE SWITCH 23p

1p 12W, 3p 4W, 2p 2W, 2p 6V, 4p 3W

DIL Sockets 14 pin and 16 pin 16p

G.W. SMITH & CO (RADIO) LTD

AUDIOTRONIC MODEL ATM-1

Top value 1000 o.p.v. pocket multimeter. Ranges: 0/10/50/250/1000V. AC and DC. DC Current 0-1mA/100mA. Resistance 0/150K ohms. Decibels -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads. **£2-95. Post 15p.**



RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V D.C. 2.5/10/50/250/500/1000V A.C. DC Current 100mA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. **£4-95. P. & P. 25p**



MODEL TE-200

20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V. D.C. 0/10/50/250/1,000V. A.C. 0/50 μA/250 mA. 0/60K/6 meg Ω. -20 to +62db. **£4-95. P. & P. 15p.**



MODEL TE-300

30,000 O.P.V. Mirror scale, overload protection 0/6/3/15/60/300/1,200V D.C. 0/6/30/120/600/1,200V. A.C. 0/30 μA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm -20 to +63 db. **£7-50. P. & P. 15p.**



U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 600 o.p.v. 0/3/15/75/300/600/1500V DC and 75mV. 0/3/15/75/300/600/1500/3000/300 V.A.C. 0/300 μA/1-5/6/15/60/150/600mA/1-5/6 AMP. D.C. 0/1-5/6/15/60/150/600mA/1-5/6 AMP. A.C. 0/200 Ω/3K/30K Ω. Accuracy DC 1%. AC 1-5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9-75. P. & P. 25p.**



MODEL 500

30,000 O.P.V. with overload protection, mirror scale. 0/5/25/100/250/500/1,000V. D.C. 0/2-5/10/25/100/250/500/1,000V. A.C. 0/50 μA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg. / 60 Meg Ω. **£10-50. Post paid. Leather Case £1-75**



MODEL C-7080 EN

Giant 6" mirror scale. 20,000 o.p.v. 0 / .25 / 1 / 2.5 / 10 / 50 / 250 / 1000 / 5000V. D.C. 0 / 2.5 / 10 / 50 / 250 / 1000 / 5000V. A.C. 0 / 50 μA / 1 / 10 / 100 / 500mA / 10 amp. D.C. 0 / 2K / 200K / 20 meg -20 to +50 dB. **£13-95. Post 35p.**



Model S-100TR TRANSISTOR/ TRANSISTOR TESTER

100,000 o.p.v. mirror scale/overload protection. 0/12/6/3/12/30/120/600 V DC. 0/6/30/120/600. V AC. 0/12/600 μA / 12/300mA/12 AMP DC. 0/10 K/1 MEG/100MEG. -20 to +50db. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. **£14-95. P/P 25p.**



KAMODEN 72 200 MULTITESTER

High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0 / .06 / .3 / 3 / 30 / 120 / 600 / 1200V. D.C. 0 / 3 / 12 / 60 / 300 / 11,200V. A.C. 0 / 6 μA / 1.2mA / 120mA / 600mA / 12A. D.C. 0 / 12A. A.C. -20 to +63db. 0 / 2K / 200K / 2 meg / 200 meg ohms. **£16-95. Post 30p.**



TMK LAB TESTER.

100,000 O.P.V. 6 1/2 in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5K/ Volt A.C. D.C. Volts: 5, 2.5, 10, 50, 250, 1,000 V. A.C. Volts: 3, 10, 50, 250, 500, 1,000V. D.C. Current: 10, 100 μA, 10, 100, 500mA. 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100MEG Ω. Decibels: -10 to +49 db. Plastic Case with Carrying Handle. Size: 7 1/2 in. x 6 1/2 in. x 3 1/2 in. **£19-95. P. & P. 25p.**



HIOKI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 3/6/12/15/30/60/120/300/600/1200V DC 1-5/3/8/12/30/60/150/300/600 1200 V. A.C. 15/30 μA/3/6/30/60/150/300mA 6/12 AMP. DC. 2K/200K/2 Meg/20 Meg ohm -20 to +63dB. **£14-95. P. & P. 20p**



370 WTR MULTI-METER

Features A.C. current ranges. 20,000 o.p.v. 0/5/25/10/50/250/500 1000 V. D.C. 0/2-5/10/50/250/500/1000V AC 0/50 μA/1/10/100mA/1/10 Amp D.C. 0/100mA/1/10 Amp AC 0/5K/50K/500K/5 meg / 50 meg. -20 to +62db. **£17-50. P. & P. 25p.**



KAMODEN HM 350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and DC current. Amplification factor of NPN, PNP, transistors, diodes, SCR's etc. 4" x 4 1/2" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. **£12-50. Post 30p.**




MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true A.C. beta in / out. Checks Ico. Checks diodes in / out. Checks SCR, etc. Beta HI 10 - 500, LO 2 - 50. Ico 0-5000 μA. 220/240 V A.C. operation **£17-50. Post 25p.**



LB3 TRANSISTOR TESTER

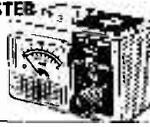Tests IGO and B. PNP / NPN. Operates from 9v battery. Complete with all instructions, etc. **£3-95. P. & P. 20p.**



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5v batteries. Complete with all instructions, etc. **£4-50. P. & P. 20p.**



TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: .001-.03-1/3-1/3/10/30/100/300V. R.M.S. 5cps-1.2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. A.C. **£17-50. Carr. 25p.**



TE-65 VALVE VOLTMETER.

28 ranges. D.C. volts 1.5-1,500V. A.C. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. **£17-50. P. & P. 30p.** Additional probes available: R.F. **£2-12**; H.V. **£2-50.**



MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200KHz. Attenuator 0-111db, 0-1db step. Impedance 600 ohms. Max. input power 30dbm. Size 180 x 90 x 55mm. **£12-50. Post 37p.**



KAMODEN HM. 720B F.E.T. V.O.M.

Input impedance 10 meg ohms. Ranges: 0 / .25 / 1 / 2.5 / 10 / 50 / 250 / 1000V. D.C. 0 / 2.5 / 10 / 50 / 250 1000V. A.C. 0 / 25 μA / 2.5 / 25 / 250 mA D.C. -20 to +62dB 0 / 5K / 50K / 500K / 5meg 500meg ohms. **£14-95. Post 30p**



TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery operated, 11 meg input, 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2" x 4 1/2" x 2 1/2". DC VOLTS 0.3-1200V AC VOLTS 3-300V RMS. 8.0-800V P-P. DC CURRENT -12-12mA. Resistance up to 2000M ohm. Decibels -20 to +51dB. Complete with leads/instructions. **£17-50. P. & P. 20p.**



KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1000 Meg-ohms. 500 Volt. Battery operated. Wide range clear meter 4 1/2" x 4". Complete with deluxe carrying case, batteries, instructions. **£19-95. Post 30p**



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Sine 18 x 200,000 Hz; Square 18 x 20,000 Hz Output max. +10 dB. (10 K ohms) Operation internal batteries Attractive 2-tone case 7 1/2" x 6" x 2". Price **£17-50. Carr. 17p.**



TO-3 PORTABLE OSCILLOSCOPE

3in. tube, Y amp. Sensitivity 0.1v p-p/CM. Bandwidth 1-5 cps-1.5 MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0.9v. p-p/CM. Bandwidth 1.5cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10 cps 800 kHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 15 1/2 lb. 220/240V. A.C. Supplied brand new with handbook. **£52-50. Carr. 50p.**



CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz 1VMS/mm. -1-25; HOR. AMP. Bandwidth 500KHz. Sensitivity at 100KHz, V RMS/mm. -3-25; Preset triggered sweep 1-3,000 μsec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V. AC operation. **£39-00. Carr. paid.**



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 Mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in. x 4in. C.R.T. Calibrated triggered sweep from .2 μsec. to 100 milli-sec. per cm. Free running time base 50 c/s-1 mc/s. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual **£87. Carr. Paid.**



TE-16A TRANSISTORISED SIGNAL GENERATOR

5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/2 x 5 1/2 x 3 1/2 in. Complete with instructions and leads. **£8-97. Post 25p.**



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohms/Volt AC and DC. Accuracy 0.5% D.C. 1% AC. Scale length 165mm. 0/300/750 μA/1-5 / 3 / 7.5 / 15 / 30 / 75 / 150 / 300 / 750mA / 1.5 / 3 / 7.5 AMP DC 0 / 3 / 7.5 / 15 / 30 / 75 / 150 / 300 / 750mA / 1.5 / 3 / 7.5 AMP AC 0 / 75 / 150 / 300 / 750mV / 1.5 / 3 / 7.5 / 15 / 30 / 75 / 150 / 300 / 750V DC 0/750mV / 1.5 / 3 / 7.5 / 15 / 30 / 75 / 150 / 300 / 750V AC. Automatic cut out. Supplied complete with test leads, manual and test certificates. **£49-00. Post 50p.**



TMK MODEL TW-50K

46 ranges, mirror scale, 50K/Vol. D.C. 5K/Volt A.C. D.C.: Volts -125, -25, 1-25, 2-5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1-5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50 μA, 2.5, 5, 25, 50, 250, 500mA, 5, 10amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +81-5db **£8-50. P. & P. 17 1/2 p.**




MODEL TE.15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440Kc/s-280Mc/s in 6 coils. 500 μA Meter. 9V battery operation. Size 180 x 80 x 40mm. **£15-00. Post 20p.**



ARF-300 AF/RF SIGNAL GENERATOR

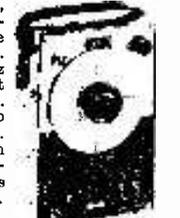All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine / square 10v. P-P. RF 100 KHz to 200 MHz. Output 1v. maximum. Operation 220/240v. AC. Complete with instructions and leads. **£29-95. Post 50p.**



TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20cps to 200 kc/s on 4 bands. Square: 20cps to 30 kc/s. Output impedance 5,000 ohms, 200/250V. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads. **£17-50. Carr. 37 1/2 p.**



240° Wide Angle Ima Meters

MW 1-6 60mm square **£3-97**
MW 1-8 80mm square **£4-97**
P. & P. 15p.



POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Simple hole fixing. In. dia. shafts. Bulk quantities available. **25 WATT. 10/25/50/100/250/500/1000 ohms. £1-15 P. & P. 10p.**
50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1-82. P. & P. 10p.
100 WATT. 1/5/10/25/50/100/250/500/1000 or 2500 ohms. £2-84. P. & P. 15p.



AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded.
80 W **£2-35 P. & P. 18p**
150 W **£3-00 P. & P. 18p**
300 W **£4-00 P. & P. 23p**
500 W **£5-80 P. & P. 33p**
1000 W **£8-25 P. & P. 38p**
1600 W **£11-25 P. & P. 43p**
2250 W **£19-00 P. & P. 50p**
5000 W **£40-00 P. & P. 41**

ALL PRICES ARE SUBJECT TO 10% VAT



HIGH QUALITY CONSTRUCTION KITS
Appointed stockists at all branches
Complete with comprehensive, easy to follow instructions, and covered by full guarantee
Post and packing 15p per kit

Josty Electronics Construction Kits

- AF20 Mono Transistor Amplifier .. \$4-80
- AF30 Mono Transistor Pre-Amplifier \$2-61
- AF310 Mono Amplifier (use two for stereo) .. \$5-91
- AT5 Automatic Light Control .. \$2-58
- AT30 Photo Cell Switching Unit .. \$5-70
- AT50 400W Triac Light Dimmer/Speed Control .. \$4-80
- AT55 1300W Triac Light Dimmer/Speed Control .. \$5-70
- AT56 2200W Triac Light Dimmer/Speed Control .. \$6-90
- AT60 Psychedelic Light Control, Single Channel .. \$7-80
- AT65 Psychedelic Light Control, 3 Channel .. \$14-55
- HF61 Medium Wave Transistor Radio .. \$3-33
- HF75 FM Transistor Receiver .. \$2-88
- HF310 FM Tuner Unit .. \$15-61
- HF325 Deluxe FM Tuner Unit .. \$24-12
- HF330 Stereo Decoder for HF310/ HF325 .. \$9-96
- HF395 Aerial Amplifier for AM/FM Bands 1, 2 & 3 .. \$1-77
- GP310 Stereo Pre-Amp for use with 2 x AF310 .. \$21-27
- GU330 Tremolo Unit for Guitars etc. \$7-50
- NT10 Power Supply 100mA, 9V Stab. 12V Unstab. .. \$6-15
- NT300 Professional Stabilised Power Supply 2 x 30 Volt, 2-2 Amp .. \$12-51
- NT305 Transistor Converter 12/15V AC/DC to 6V, 7-5V or 9V DC .. \$4-50
- NT310 Power Supply 240V AC to 2 x 18V DC at 2 Amps .. \$4-80
- NT315 Power Supply 240V AC to 4-5 -15V DC at 500mA .. \$9-57
- AE1 100mW Output Stage .. \$1-65
- AE2 Pre-Amplifier .. \$1-28
- AE3 Diode Receiver .. \$2-00
- AE4 Flasher .. \$1-09
- AE5 Astable Multivibrator .. \$1-06
- AE6 Monostable Multivibrator .. \$1-02
- AE7 RC Generator .. \$1-06
- AE8 Bass Filter .. \$9
- AE9 Treble Filter .. \$9
- AE10 OCIR Filter .. \$9

IDEAL GIFT FOR ALL AGES!

AMATEUR ELECTRONICS

The professional book for the amateur—covers the subject from basic theories to the advanced electronics of today. 347 pages of invaluable information and diagrams. Complete with free circuitboard for building 10 of the projects described in the book. (Components extra).

P. & P. 25p **OUR PRICE £3-30**

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230V. 50/60 c/s. Variable output 0-260V.

MODEL S-260 GENERAL PURPOSE BENCH MOUNTING


Amps	Price	P. & P.
1 Amp	8-75	30p
2-5 Amp	10-00	35p
5 Amp	14-70	37p
8 Amp	25-30	50p
10 Amp	28-10	75p
12 Amp	29-50	100p
20 Amp	72-50	125p
25 Amp	72-50	130p
40 Amp	103-10	150p



MODEL S-260B Panel Mounting.


Amps	Price	P. & P.
1 Amp	8-75	30p
2-5 Amp	10-00	35p

Carriage and Packing Extra

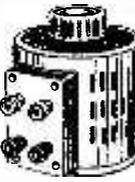

230 VOLT A.C. 50 CYCLES RELAYS

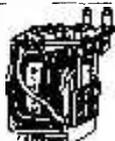3 sets of changeover contacts at 5 amp rating, 40p each. P. & P. 12p (100 lots \$30. Quantities available).



BVD.5 VERNIER TUNING DIAL

Approx. 7-1 ratio planetary drive vernier dials. Log scale 0-180 degrees. Blank scales 1 to 5. Scale width 4 1/2". Dial size 5" x 3". Overall size 7 1/2" x 4 3/4" x 1 1/2" deep including knob and coupling. 1 1/2" dia. shaft.

OUR PRICE £1-62 P. & P. 15p.

REFLEX HORN SPEAKER R.H.6

Built in driver unit. Impedance 16 ohm. Power rating 10 watt. Response 380-7000Hz. Approx. size 6" x 6". Weatherproof and shock proof.

OUR PRICE £4-97 P. & P. 30p.


SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

Type SW.100 100 x 80 mm.

50µA	\$4-15	5 amp. D.C.	\$3-60
50-0-50µA	\$3-95	300V. A.C.	\$3-70
100µA	\$3-95	VU Meter	\$4-80
100-0-100µA	\$3-90		
500µA	\$3-70		
1mA	\$3-60		
20V. D.C.	\$3-60		
50V. D.C.	\$3-60		
300V. D.C.	\$3-60		
1 amp. D.C.	\$3-60		

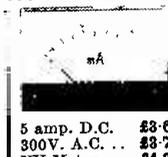


Type SD.830 82.5mm x 110mm Fronts

10mA	\$3-10	500mA	\$2-60
50mA	\$3-10	1 amp.	\$2-90
100mA	\$3-10	5 amp.	\$2-90
500mA	\$3-10	10 amp.	\$2-10
1 amp.	\$3-10	5V. D.C.	\$2-10
5 amp.	\$3-10	10V. D.C.	\$2-10
10 amp.	\$3-10	20V. D.C.	\$2-10
5V. D.C.	\$2-10	50V. D.C.	\$2-10
10V. D.C.	\$2-10	300V. D.C.	\$2-10
20V. D.C.	\$2-10	15V. A.C.	\$2-80
50V. D.C.	\$2-10	300V. A.C.	\$2-80
300V. D.C.	\$2-10	VU Meter	\$3-50
15V. A.C.	\$2-80		
300V. A.C.	\$2-80		
VU Meter	\$3-50		




Type SD.640 63.5mm x 85mm Fronts

50µA	\$3-05	500mA	\$2-60
50-0-50µA	\$2-85	1 amp.	\$2-90
100µA	\$2-85	5 amp.	\$2-90
100-0-100µA	\$2-80	10 amp.	\$2-60
200µA	\$2-80	5V. D.C.	\$2-60
500µA	\$2-15	20V. D.C.	\$2-60
1mA	\$2-10	50V. D.C.	\$2-60
5mA	\$2-10	300V. D.C.	\$2-60
10mA	\$2-90	15V. A.C.	\$2-80
50mA	\$2-90	300V. A.C.	\$2-80
100mA	\$2-90	VU Meter	\$3-15

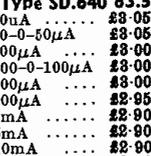

Type MR.45P. 2in. square fronts

50µA	\$2-70	5 amp.	\$2-40
50-0-50µA	\$2-65	10V. D.C.	\$2-40
100µA	\$2-60	20V. D.C.	\$2-40
100-0-100µA	\$2-50	50V. D.C.	\$2-40
200µA	\$2-50	300V. D.C.	\$2-40
500µA	\$2-45	15V. A.C.	\$2-40
500-0-500µA	\$2-40	300V. A.C.	\$2-40
1mA	\$2-40	8 Meter 1mA	\$2-50
5mA	\$2-40	VU Meter	\$2-70
10mA	\$2-40	1 amp. A.C.*	\$2-40
50mA	\$2-40	5 amp. A.C.*	\$2-40
100mA	\$2-40	10 amp. A.C.*	\$2-40
500mA	\$2-40	20 amp. A.C.*	\$2-40
1 amp.	\$2-40	30 amp. A.C.*	\$2-40

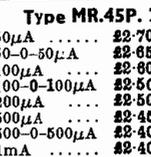

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50µA	\$6-90	15V. d.c.	\$5-95
100µA	\$6-40	20V. d.c.	\$5-95
50-0-50µA	\$6-40	50V. d.c.	\$5-95
1mA	\$5-95	300V. d.c.	\$5-95
1-0-1mA	\$5-95	Dual range	
1A d.c.	\$5-95	500mA/5A d.c.	\$7-00
5A d.c.	\$5-95	1/15A d.c.	\$7-00
5V. d.c.	\$5-95	5V/50V d.c.	\$7-00
10V. d.c.	\$5-95	5/15V d.c.	\$7-00

PS.1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12 volt DC up to 3 amps. Meter to monitor current. Input 220/240V A.C. Size 4" x 3 1/2" x 6 1/2". \$11-97. P. & P. 25p.

MP7 MIXER PREAMPLIFIER

5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5 1/2" x 3 1/2". Inputs Mics: 3 x 3mV 50K; 2 x 3mV 600 ohm. Phono meg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.

Our Price £8-97 P. & P. 20p


Type MR.85P. 4 1/2in. x 4 1/2in. fronts

100mA	\$3-80	10V. D.C.	\$2-60
500mA	\$3-80	20V. D.C.	\$2-60
1 amp.	\$3-80	50V. D.C.	\$2-60
5 amp.	\$3-90	15V. A.C.	\$2-60
15 amp.	\$3-90	300V. A.C.	\$2-60
30 amp.	\$3-95	8 Meter 1mA	\$2-85
10V. D.C.	\$3-90	VU Meter	\$3-70
20V. D.C.	\$3-90	50mA A.C.*	\$2-60
50V. D.C.	\$3-90	100mA A.C.*	\$2-60
150V. D.C.	\$3-90	200mA A.C.*	\$2-60
300V. D.C.	\$3-90	500mA A.C.*	\$2-60
15V. A.C.	\$3-95	1-0-1mA	\$2-25
300V. A.C.	\$3-95	2mA	\$2-25
8 Meter 1mA	\$3-90	5mA	\$2-25
VU Meter	\$4-55	10mA	\$2-25
1 amp. A.C.*	\$3-90	20mA	\$2-25
5 amp. A.C.*	\$3-90	50mA	\$2-25
10 amp. A.C.*	\$3-90	100mA	\$2-25
20 amp. A.C.*	\$3-90	150mA	\$2-25
30 amp. A.C.*	\$3-90		




Type MR.52P. 2 1/2in. square fronts

50µA	\$2-50	10V. D.C.	\$2-50
50-0-50µA	\$2-05	20V. D.C.	\$2-50
100µA	\$2-05	50V. D.C.	\$2-50
100-0-100µA	\$2-05	300V. D.C.	\$2-50
200µA	\$2-05	15V. A.C.	\$2-50
500µA	\$2-05	300V. A.C.	\$2-50
1mA	\$2-50	8 Meter 1mA	\$2-60
5mA	\$2-50	VU Meter	\$2-60
10mA	\$2-50	1 amp. A.C.*	\$2-50
50mA	\$2-50	5 amp. A.C.*	\$2-50
100mA	\$2-50	10 amp. A.C.*	\$2-50
500mA	\$2-50	20 amp. A.C.*	\$2-50
1 amp.	\$2-50	30 amp. A.C.*	\$2-50

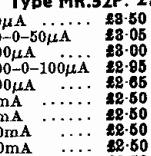

Type MR.65P. 3 1/2in. x 3 1/2in. fronts

50µA	\$3-70	10V. D.C.	\$2-60
50-0-50µA	\$3-15	20V. D.C.	\$2-60
100µA	\$3-15	50V. D.C.	\$2-60
100-0-100µA	\$3-10	150V. D.C.	\$2-60
200µA	\$3-05	300V. D.C.	\$2-60
500µA	\$2-75	15V. A.C.	\$2-60
500-0-500µA	\$2-60	300V. A.C.	\$2-60
1mA	\$2-60	50V. A.C.	\$2-60
5mA	\$2-60	150V. A.C.	\$2-60
10mA	\$2-60	300V. A.C.	\$2-60
50mA	\$2-60	500V. A.C.	\$2-60
100mA	\$2-60	8 Meter 1mA	\$2-85
500mA	\$2-60	VU Meter	\$3-70
1 amp.	\$2-60	50mA A.C.*	\$2-60
5 amp.	\$2-60	100mA A.C.*	\$2-60
10 amp.	\$2-60	200mA A.C.*	\$2-60
15 amp.	\$2-60	500mA A.C.*	\$2-60
20 amp.	\$2-60	1 amp. A.C.*	\$2-60
30 amp.	\$2-60	5 amp. A.C.*	\$2-60
50 amp.	\$2-60	10 amp. A.C.*	\$2-60
5V. D.C.	\$2-60	20 amp. A.C.*	\$2-60
		30 amp. A.C.*	\$2-60

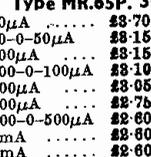

"SEW" EDGWISE METERS

Type PE.70. 3 1/2" x 1 1/2" x 1 1/2" deep

50µA	\$3-75	500µA	\$3-20
50-0-50µA	\$3-60	1mA	\$3-20
100µA	\$3-60	300V. A.C.	\$3-25
100-0-100µA	\$3-50	VU Meter	\$3-85
200µA	\$3-40		



***MOVING IRON— ALL OTHERS MOVING COIL**
Please add postage


Type MR.38P. 1 21/32in. square fronts

200mA	\$2-25	1 amp.	\$2-25
300mA	\$2-25	5 amp.	\$2-25
500mA	\$2-25	10 amp.	\$2-25
750mA	\$2-25	5V. D.C.	\$2-25
1 amp.	\$2-25	10V. D.C.	\$2-25
2 amp.	\$2-25	15V. D.C.	\$2-25
5 amp.	\$2-25	20V. D.C.	\$2-25
10 amp.	\$2-25	50V. D.C.	\$2-25
3V. D.C.	\$2-25	100V. D.C.	\$2-25
10V. D.C.	\$2-25	150V. D.C.	\$2-25
15V. D.C.	\$2-25	300V. D.C.	\$2-25
20V. D.C.	\$2-25	100V. A.C.	\$2-25
50V. D.C.	\$2-25	200V. A.C.	\$2-25
100V. D.C.	\$2-25	500V. A.C.	\$2-25
50V. D.C.	\$2-25	8 Meter 1mA	\$2-25
10V. D.C.	\$2-25	VU Meter	\$2-65
15V. D.C.	\$2-25		
20V. D.C.	\$2-25		
50V. D.C.	\$2-25		
100V. D.C.	\$2-25		
150V. D.C.	\$2-25		
300V. D.C.	\$2-25		
100V. A.C.	\$2-25		
200V. A.C.	\$2-25		
500V. A.C.	\$2-25		
8 Meter 1mA	\$2-25		
VU Meter	\$2-65		



Type SD.460 46mm x 59.5mm Fronts

50µA	\$2-80	1 amp.	\$2-60
50-0-50µA	\$2-80	5 amp.	\$2-60
100µA	\$2-75	10 amp.	\$2-60
100-0-100µA	\$2-75	5V. D.C.	\$2-60
200µA	\$2-70	10V. D.C.	\$2-60
500µA	\$2-55	20V. D.C.	\$2-60
1mA	\$2-60	50V. D.C.	\$2-60
5mA	\$2-60	300V. D.C.	\$2-60
10mA	\$2-60	15V. A.C.	\$2-70
50mA	\$2-60	300V. A.C.	\$2-70
100mA	\$2-60	VU Meter	\$2-90
500mA	\$2-60		

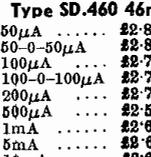

"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/2in. square fronts

G.W.S. SMITH & CO (RADIO) LTD

FANTASTIC VALUE TRIO QUALITY ENGINEERED COMMUNICATIONS UNITS

TRIO 9RS9DS RECEIVER

4 bands covering 550 Kc/s to 30 Mc/s continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit, 4/8 ohm output and phone jack. SSB-CW, ANL, Variable BFO. S meter. Sep. bandspread dial. LF frequency 445 kc/s, audio output 1.5w. Variable RF and AF gain controls 115/250 v. A.C. with instruction manual.



Our Price **£42.50** Carr. Paid

TRIO JRS99 RECEIVER

9 wavebands covering 1.8-29.7MHz / 144-146MHz and 10.00MHz WWV. SSB, CW, AM and FM. AF output more than 1 watt. S Meter. Squelch control. BFO. Variable RF and AF controls. 4-16 ohm output and phone jack. Power requirements 100/240v. AC. 12-14v. DC. Size 270 x 140 x 310mm.



Our Price **£132.50** Carr. Paid

TRIO TR2 200 TRANSCEIVER

Fully transistorised portable VHF Transceiver. Will transmit and receive on 6 channels between 144-146 MHz. 1 watt transmitter. 12v DC internal or external supply. Built in charger for ni-cad cells. Power/volume switch, squelch control, channel selector, mike socket, earphone/external speaker socket. Complete with microphone, 144-48, 144-72 and 145-32 crystals. Size 184 x 58 x 180mm.



Our Price **£79.50** Carr. Paid

TRIO JR310 SSB RECEIVER

Covers 3-5, 7, 14, 21, 28, 28.5 and 29.1 MHz bands and WWV 15MHz. SSB, AM and CW. AF output more than 1 watt. Crystal controlled BFO for SSB. S meter. ANL etc. AC 110/120-220/240v. Size 330 x 179 x 310mm.



Our Price **£75.00** Carr. Paid

UR-1A RECEIVER



4 Bands covering 550Kc/s-30 Mc/s. FET, S Meter. Variable BFO for SSB. Built-in Speaker, Bandspread. Sensitivity Control. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

Our Price **£25.00** Carr. Paid 37p


LAFAYETTE HA-600 RECEIVER



General coverage 150-400 Kc/s, 550 Kc/s-30 Mc/s, FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, S Meter Bandspread. RF Gain. 220/240 v. A.C. or 12 v. D.C. Brand new with instructions.

Our Price **£50.00** Carr. Paid 50p

UNR 30 RECEIVER

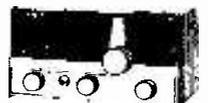

4 Bands covering 550 Kc/s-30 Mc/s B.F.O. Built-in Speaker 220/240 v. A.C. Brand new with instructions.

Our Price **£15.75** Carr. Paid 37p

BELTEK W5400 CAR TRANSCEIVER



Solid state mobile transceiver for 12v DC neg. use. Transmits and Receives on any 12 of 28 channels between 144 and 146MHz. Power output 10w and 1w switchable. Controls: Volume/on/off, squelch channel selector Internal 3" speaker. Complete with dynamic mike, PTT switch, three sets of crystals for 344-48MHz, 144-60 MHz, 145-00MHz, mounting bracket and instructions. Size approx. 150 x 70 x 220mm.

Our Price **£75.00** P & P 50p

SWR METER—Model SWR-3
Handy SWR Meter for transmitter antenna alignment, with built-in field strength meter. Accuracy: 5%, Impedance: 52. Indicator: 100µA DC, full scale 5 section collapsible antenna. Size: 145 x 50 x 60 mm.
Our Price **£4.25** P. & P. 25p



SH628 STEREO HEADPHONES



Outstanding value. Soft ear-pads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

Our Price **£1.87** P. & P. 30p

LHO2S STEREO HEADPHONES



Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft. cord and plug.

Our Price **£1.97** P. & P. 30p

TEI018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.

Our Price **£2.25** P. & P. 30p

BH.001 HEAD SET AND BOOM MICROPHONE



Moving Coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms.

Our Price **£5.95** P. & P. 30p

DH02S STEREO HEADPHONES



Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance, 20-12,000 cps. Complete with lead and plug.

Our Price **£2.25** P & P 30p

HAND-HELD 2-WAY WALKIE-TALKIES
P. & P. 50p.



SKYFON—100MW. £24.95 pair, P302—2 CHANNEL 300MW. £52.50 pair. P1003—3 CHANNEL 1 Watt £71.25 pair. LICENCE REQUIRED FOR OPERATION IN U.K.

EA.41 REVERBERATION AMPLIFIER

Self contained transistorised, battery operated. Simply plug in microphone, guitar, etc. and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet, 7 1/2 x 3 x 4 1/2 in.

Our Price **£7.50** P. & P. 15p



SPECIAL BARGAIN! PHONIC 10 TWO WAY SPEAKER SYSTEM

Matched pair of compact bookshelf speakers of unique design incorporating 2" high frequency tweeter and 6" woofer. 8 ohms impedance. 10 watts power handling. Size 348 x 228 x 110mm.



GWS SPECIAL PRICE **£9.85** per pair. P. & P. 50p plus VAT.

AUDIOTRONIC AHAI01 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9v battery. INPUTS: 5mV/100mV. OUTPUT: 50mV per channel.

Our Price **£7.50** P. & P. 20p

AUDIOTRONIC AR.1000 SPORTSMAN AM/FM PORTABLE RADIO

5 wavebands covering AM 555 1065KHz FM 88-108MHz. AIR 108-155MHz. PB 147-174MHz. WB 162. 5MHz. Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for FM and built in ferrite bar for AM. AFC. 3in. speaker. Earpiece socket. Size 152 x 79 x 219mm. Battery/mains operation.



OUR PRICE **£11.50** P. & P. 35p.

AUDIOTRONIC AMR-900 GLOBAL AM/FM PORTABLE RADIO

10 wavebands covering AM: 535-1605 kHz, LW: 150-380 kHz, MB 1.6-4.00 MHz, SW1: 4.0-8 MHz, SW2: 8.0-1.6 MHz, SW3: 16-24 MHz, PSB1: 30-50 MHz, PSB2: 148-174 MHz, FM 88-108 MHz, AIR: 108-136 MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. AFC or FM. 6" x 4" speaker and personal earpiece. Battery/mains operation. Size: 345 x 133 x 305mm.

OUR PRICE **£36.00** P. & P. 50p.

AUDIOTRONIC DIGITAL CLOCK RADIO ADC.1
Covers AM 540 - 1600 KHz. FM 88 - 108 MHz with AFC Illuminated dial. 24 hour alarm setting. Wake up to the sound of music or loud buzzer. Sleep switch will automatically turn off radio etc. Internal speaker plus socket for earpiece or pillow speaker. AC 240v. Size 254 x 92 x 178mm. Complete with earpiece, and operating instructions.

OUR PRICE **£12.50** P. & P. 50p.



Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker mounting brackets and instructions.

OUR PRICE **£7.50** P. & P. 50p

NOW AVAILABLE!
ADC II DELUXE VERSION
OUR PRICE **£14.95** P. & P. 50p.

AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 16 1/2" x 8" x 3 1/4". AC 200/250v



PROCESS FOUR
For use with semi-professional tape recorders. Freq. res. 30Hz-20KHz ± 2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

Our Price **£50.00** P & P 50p

PROCESS TWO
For use with cassette and tape recorders. Freq. res. 30Hz-20KHz ± 2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.

Our Price **£34.50** P & P 50p

FM TUNER CHASSIS



6 TRAN-SISTOR HIGH QUALITY TUNER SIZE ONLY
6 x 4 x 2 1/2 in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9v battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money.

Our Price **£5.95** P. & P. 20p

AI018 FM TUNER

Specification as above chassis but complete in cabinet with on/off switch Size 7 1/2" x 3 1/2" x 5".

Our Price **£9.65** P & P 30p

Stereo multiplex adaptor £4.97.

AUDIOTRONIC AM/FM Portable Radio AR3000

4 wavebands covering FM 87 - 108 MHz, MW 510 - 1605 KHz, LW 145 - 285 KHz, SW 5.8 - 12.5 MHz. Push button wave change plus AFC and on/off. Thumbwheel tuning. Slider volume and tone controls. Earphone socket. Built-in and telescopic aeriels. Car aerial socket. Battery/Mains operation.



OUR PRICE **£14.95** P. & P. 50p

AUDIOTRONIC ACR3500 CAR RADIO



Manual tuning of Medium and Long waves. 12v pos. or neg. earth. Complete with speaker mounting brackets and instructions.

Our Price **£7.50** P & P 50p



SAVE UP TO 33 1/3% OR MORE! GWS

AUDIOTRONIC AHP-8D 8 Track Stereo Tape Deck

Can be used with most hi-fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. AC 220/240v.
OUR PRICE £11.95 P. & P. 50p.




AUDIOTRONIC ACD.660 Stereo Cassette Deck

A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter normal/chrome tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/Din line input sockets, 3.5mm mike input sockets etc. etc. Frequency response 40-12KHz (40-16KHz) (Cr02) 8/N-45dB. Crosstalk 45dB. Separation -35dB. Noise limiter-6dB at 10KHz. Complete with phono connecting leads.
OUR PRICE £39.50 Carr. & Ins.50p



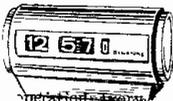240v. mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Approx. size 6 1/2" x 3" x 3 1/2".
OUR PRICE £4.50 P. & P. 30p.




BINATONE DS100 DIGITAL CLOCK

240v. mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Approx. size 6 1/2" x 3" x 3 1/2".
OUR PRICE £4.50 P. & P. 30p.

SPECIAL PURCHASE! BSR 8 TRACK PLAYER CHASSIS

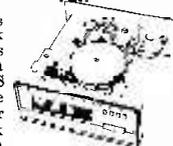Famous BSR 8 track chassis as used in Model TD8S complete with silver and black escutcheon ready to fit into cabinet. Output 125mV. AC 240v. Overall size approx. 185 x 215 x 90mm.
OUR PRICE £8.95 P & P 50p.



NEW STORE IN TUNBRIDGE WELLS

53/57 Camden Road, Tunbridge Wells
 Tel. 23242

FERGUSON EXPORT MODELS

FERGUSON 3408 STEREO TUNER AMPLIFIER

Covers FM 88-108 MHz. Five push button tuning scales, 8+8 watts rms. Inputs for stereo ceramic cartridge and tape etc. Separate bass treble, balance and volume controls.
Our Price £31.50 P. & P. 50p



8416 STEREO TAPE DECK

4 track, 7 1/2, 3 1/2, 1 1/2 i.p.s. Stereo/mono record/play. 7" reels. Inputs for dynamic mikes, radio, gram. Complete with cover.
Our Price £41.95 P. & P. 75p



SINCLAIR PROJECT 80 PACKAGES

2 x Z40/Stereo 80/PZ5... £25.00 P. & P. 37p
 2 x Z40/Stereo 80/PZ6... £27.75 P & P 37p
 2 x Z60/Stereo 80/PZ8... £30.45 P. & P. 37p
 Transformer for PZ8... £4.05
 Project 80 A.F.U. £6.95
 Project 80 FM Tuner.... £11.95
 Project 80 Stereo Decoder £7.45
 All other Sinclair Products stocked.

PORTABLE CASSETTE RECORDER CT5050

Instant recording and playing. Piano key controls. Automatic level control. Built in speaker. Complete with remote control microphone, carrying case and shoulder strap.
OUR PRICE £8.50 P. & P. 50p.

AUDIOTRONIC LOW NOISE CASSETTES

Top Hi-Fi quality in library cases

TYPE	5	10	25
C80	£1.29	£2.53	£5.99
C90	£1.85	£3.62	£8.59
C120	£2.29	£4.48	£10.83

P. & P. 15p.
 Cassette Tape Head Cleaner 80p

3-STATION INTERCOM KE.630

Master and two sub stations. Can be used on desk or wall mounted. Complete with cable and batteries.
Our Price £5.25 P & P 50p

MINUTEMAN MM3 POCKET CALCULATOR

Size only 4 1/8" x 3" x 1". 8 digit display with overflow and error indicators. Floating decimal. Adds, subtracts, multiplies and divides. Chain and mixed calculations. Constant factor for series multiplication or division. Complete with batteries, instructions and case.
OUR PRICE £23.95 P. & P. 25p

SINCLAIR POCKET CALCULATORS CAMBRIDGE

To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator.
OUR PRICE £24.95 P. & P. Free
 (Also available ready built Rec. Price £29.95)
OUR PRICE £27.20 P. & P. 25p

ALSO AVAILABLE SINCLAIR EXECUTIVE EXECUTIVE-MEMORY

Rec. Price £39.00
OUR PRICE £35.45
 Rec. Price £49.00
OUR PRICE £40.75 P. & P. Free

AUDIOTRONIC Stereo Headphones

LSH.20 Individual volume controls Stereo mono switch. 8 ohms. 40-19,000 Hz.
£3.50 P & P 30p

LSH.30 Open back type. Individual tone and volume controls. 8 ohms. 30-20,000 Hz.
£5.50 P & P 30p

LSH.40 Two way speaker system. Individual volume controls. 8 ohms. 20-20,000 Hz.
£9.95 P & P 30p

LSH.60 3" speaker units. 8 ohms. 20-20,000 Hz. Complete with zipped carrying case.
£9.50 P. & P. 30p

LQH.400 4-channel dynamic headphones. Each earpiece has 4 drive units. 4-32 ohms. 20-20,000 Hz.
£9.95 P. & P. 30p

LSH.50 Electrostatic with self powered energiser and control unit with headphone/speaker selector. 4-32 ohms. 20-000 Hz.
£15.95 P. & P. 30p

RECORD DECKS

Carriage and Packing 50p

B.S.R. McDONALD

C114 Mini	£3.95
C129 Mono	£5.50
C137	£7.00
510/TPD1	£13.95
610	£10.55
610/TPD1	£15.45
710	£21.15
S10	£28.30
MP60	£8.35
MP60/G800	£10.90
MP60/TPD1	£13.20
MP60/TPD2	£11.25
HT70	£14.80
HT70/G800	£14.25
HT70/TPD1	£18.55

CONNOISSEUR

Bd1 Kit	£9.10
Bd1 Chassis	£11.35
Bd2/SAU2/Chassis	£29.70
Bd2/SAU2/Plinth/Cover	£28.20

GARRARD

2025 T	£6.35
2025TC/KS40A	£6.95
SP25 III	£9.25
SP25III/G800	£10.95
SP25/M75-6	£13.90
368B	£18.50
SL65B	£11.15
SL72B	£17.75
SL95B	£31.15
401	£24.35
ZERO 100A	£34.10
ZERO 100S	£31.40
ZERO 100 SB	£27.00

GOLDRING

G99	£22.50
G101P/C	£22.50
GL69/2	£16.75
GL72	£25.45
GL72/P	£33.75
GL75	£32.20
GL75P	£41.65
GL75P/C	£56.25
GL85P/C	£72.00

RECORD DECK PACKAGES

Complete units with Stereo cartridge ready wired in pinth cover.

GARRARD

2025 TC/9TAHCD	£11.35
SP25 III/G800	£16.80
SP25 III/M44E	£17.85
SP25 III/M44-7	£17.50
SP25 III/M65E	£19.45
SP25 III Module/M75-6	£19.45
AP76/G800	£26.45
AP76/G800E	£28.65
AP76/M44E	£27.70
AP76/M44-7	£27.20
AP76/M55E	£28.30
AP76/M75EJ	£34.90
AP76/M75ED	£30.90
AP76 Module M75-6	£29.10
868B Module/M75-6SM	£32.50
AP96 Module M75-6	£33.20
ZERO 1008 Module/M93E	£44.15
Zero 1008B Module M75-6SM	£44.20

B.S.R. McDONALD

210/SC7M	£7.40
MP60/G800	£18.50
MP60/TPD1/G800	£15.80
MP60/M44-7	£17.50
HT70/TPD1/G800	£19.20

GOLDRING

GL72/G800	£34.20
GL75/G800	£39.10
GL75/G800E	£41.55
GL78/G800	£42.45
GL78/G800E	£44.95

DIGITAL CLOCK MECHANISM DT.55B

Features 24 hour alarm setting with built-in buzzer. On/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off TV, radio, light, etc. and with autotuning will switch on again when required. AC 240v. operation. Switch rating 250v. 3A.
OUR PRICE £5.95 P. & P. 30p.

EMI LOUDSPEAKERS

Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £7.25 each. P. & P. 37p.
 Model 450. 13" x 8" with twin tweeter/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £3.62 each. P. & P. 25p.

SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 14 1/2" x 9 1/2" x 8 ohms. 8 watt RMS. Complete with DIN lead.
Our Price £12.95 Carr. 50p

PHILCO FORD MODEL 5248 MAINS TAPE RECORDER

4 track, 2 speeds (3 1/2 i.p.s. & 1 1/2 i.p.s.). Piano key type controls, tape counter, recording level meter, volume & tone controls etc. Complete with hand microphone, direct recording lead, 1800' of tape with spare spool. 200/250V AC operation fully guaranteed.
OUR PRICE £27.50. C & P 75p.

PHILCO FORD MODEL 5245 MAINS TAPE RECORDER

2 track BSR deck with push button controls for easy operation. Tape counter and volume control. Complete with hand microphone, Direct recording lead, 1300' reel of tape & spare spool. 200/250V AC operation. Fully guaranteed.
OUR PRICE £17.50. C & P 75p.

FRUSTRATED EXPORT ORDER PHILCO FORD MODEL 5245 MAINS TAPE RECORDER

2 track BSR deck with push button controls for easy operation. Tape counter and volume control. Complete with hand microphone, Direct recording lead, 1300' reel of tape & spare spool. 200/250V AC operation. Fully guaranteed.
OUR PRICE £17.50. C & P 75p.

PRICES SUBJECT TO 10% VAT

Order with confidence by Post but remember to add 10% VAT to total value of order including carriage and packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY IN CAPITALS.

TELEPHONED ORDERS ACCEPTED FROM ACCESS and BARCLAYCARD HOLDERS
 CREDIT TERMS FOR PERSONAL CALLERS (on sales of £50 and over)

All prices correct at 16-11-73 but subject to change without notice. E & O E

G.W.S.MITH & CO (Radio) LTD

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

CENTRAL LONDON

257A, Tottenham Court Rd. W.1.	Tel: 01-580 0470
10, Tottenham Court Rd. W.1.	Tel: 01-587 2232
27, Tottenham Court Rd. W.1.	Tel: 01-583 7713
57, Tottenham Court Rd. W.1.	Tel: 01-580 1170
21, Old Compton Street, W.1.	Tel: 01-437 9389
3, Lisle Street, W.C.2.	Tel: 01-437 8204
24, Lisle Street, W.C.2.	Tel: 01-437 9125
11A, Edgware Road, W.2.	Tel: 01-723 9988
18B, Edgware Road, W.2.	Tel: 01-723 6211

SURREY

311, Edgware Road, W.2.	Tel: 01-262 0397
182, Edgware Road, W.2.	Tel: 01-263 4184
152/3, Fleet Street, E.C.4.	Tel: 01-353 2833
22A, Narrow Road, W.8.	Tel: 07-228 8530
88, South Street, Romford.	Tel: Romford 20218
104C, Weyhill Centre, Croydon.	Tel: 01-881 3227
27, Eden Street, Kingston.	Tel: 01-546 7845
32, Hill Street, Richmond.	Tel: 01-948 1441

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY
 HEAD OFFICE AND MAIL ORDER DEPARTMENT
 UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6J
 TELEPHONE 01-206 3738

LONDON'S LARGEST STOCKS INCLUDING PRODUCTS BY-


ARMSTRONG
 CAMBRIDGE
 KEF LUX-NIKKO
 SANSUI SANYO
 SONY-TEAC
 TRANSCRIPTORS
 TRIG UHER
 YAMAHA

Prices on request or send S.A.E. for full Discount List

ALL EQUIPMENT IS FULLY GUARANTEED AND COVERED BY 12 MONTHS FREE SERVICE!

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

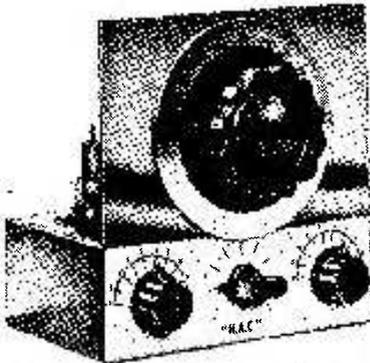

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1974 "DX" RECEIVER

Complete kit—Price £4.30 (incl. p. & p. & V.A.T.). Customers writes: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports from all continents. An amazing one-valver." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other B.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, of kits & components. Test Report available.

EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1

EX COMPUTER PC PANELS

2 x 4 in. packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (12p)

SPECIAL BARGAIN PACK

25 boards for £1 (30p). Panels with 4 Power transistors sim OC28 50p (10p)

ELECTROLYTICS

6000µ 75v 4½ x 2in. dia. 55p (14p)
5000µF 90v, 8000µ 55v 4½ x 3in dia. 50p (24p)
10,000µ 35v, 5,000µ 35v 4½ x 2in 40p (12p)
2000µ 25v wire ends 15p (6p)
3A diodes 4 for 50p (7p)
250 mixed capacitors 60p (9½p)
250 mixed resistors 60p (9½p)
250 mixed HI-STAB resistors 60p (9½p)
200 Si Plana diodes 50p (7p)
Sub-min co-ax. connectors 4 prs. 50p (7p)
Min. glass neons 12 for 50p (7p)
Reed Relays mixed 10 for 50p (7p)
Micro switches 8 for 50p (9p)
Assorted Relays 8 for £1 (18p)
10 way terminal blocks 10 for 55p (15p)
Papst extractor/blower fans 100 c.f.m. 4½ x 4½ x 2in. £3.50 (28p)
Q.H. bulbs 12v 55w 50p (6p)

Postage and package shown in brackets. Please add 10% VAT to prices.

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8. 01-478 8499

SINCLAIR

CAMBRIDGE CALCULATOR

Fully assembled ONLY £26.45 (£3.00)
Also available Sinclair Executive Calc £34 (£3.70)

AMTRON AND JOSTY KITS SPECIAL BARGAIN OFFER

To celebrate our introduction of these famous kits we are offering them free of VAT and postage. All models stocked. Send sae for a quote by return.

SINCLAIR EQUIPMENT



Project 605 (DEFINITELY IN STOCK!!!)	£19.90 (£2.30)
System 2000 (Special offer)	£26.00 (£2.50)
Z40 £4.25 (63p)	Q16 £5.90 (79p)
Z60 £5.38 (74p)	PZ5 £3.47 (57p)
Z30 £3.50 (55p)	PZ6 £5.95 (99p)
Z50 £4.30 (65p)	PZ8 £6.40 (84p)
Stereo 80 Pre-amp	£9.53 (£1.05)
Project 80 Tuner	£8.95 (£1.10)
Project 80 Decoder	£5.69 (77p)
Project 80 AFU	£5.38 (74p)
Project 60 AFU	£4.40 (64p)
Stereo 60 Pre-amp	£7.80 (98p)
Trans for PZ8	£2.95 (50p)

PROJECT 60 KIT £2.70 (49p)
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cable and fuseholder needed to complete Project 60.

BATTERY ELIMINATOR BARGAIN

The most versatile battery eliminator ever offered. Switched output of 3V, 4.5V, 6V, 7.5V, 9V and 12V at 500mA. Other eliminators stocked 50mA unless stated:-
4½V £1.50 (30p); 6V £1.50 (30p); 9V £1.50 (30p); 7½V cassette type £2.25 (30p); Double 4½V + 4½V £2.50 (35p); Double 6V + 6V £2.50 (35p); Double 9V + 9V £2.50 (35p); Switched model giving 6V, 7½V and 9V at 400mA £4.00 (50p).



IC RADIO CHIP TBA651 £2.10 (32p)
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2.10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1.75 (29p).


S-DECS & T-DECS

S-DECS £1.44 (25p)
T-DECS £2.88 (40p)
µ-DEC A £3.18 (43p)
µ-DEC B £5.94 (71p)
16 dit IC carriers £1.20 (17p)



SINCLAIR SUPER IC12

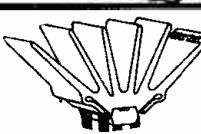With 44 page booklet and printed circuit £2.10 (43p)



DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.55 (26p). Stereo model with balance control £3.50 (46p)

IC12 POWER KIT

Supplies 28V 0.5 Amps £2.47 (50p)

LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1.10 (27p). 5" x 8" 8 ohm £1.55 (37p).

PREAMPLIFIER KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1.30 (24p). Stereo model £2.30 (34p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1.20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

ECONOMICAL QUADRAPHONICS

£11.95 (£1.50)
Eagle AA10 Quadrasonic Synthesizer. Complete, self-contained matrix system in attractive cabinet. Just feed ordinary 2 channel stereo into it and connect outputs to 4 loudspeakers to obtain the latest experience in sound. 35 watts rms/channel.

SWANLEY ELECTRONICS

32 Goldsel Rd., Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools etc. welcome. Mail order only. No callers, please.

THE RADIO SHOP

16 Cherry Lane, Bristol BS1 3NG
Tel.: Bristol 421196. STD Code 0272

Your West Country shop for electronic components and solid state devices

Mains operated relays. B11A base 3 pole change-over 10A. 35p post paid.

Bases 16p.

Multiturn Potentiometers
Ex Equip. Relcon 1K ±1%
Good condition .25" spindle 30p post paid.

Mains Slow Motion Motors

1 Rev. per 6 mins, 2" dia 1½" Deep 45p post paid.

Hook up Wire 1/024 PVC ins Asst colours 4x100yd Reels only £1.75 post paid.

AIRCRAFT BAND CONVERTER

Circuit, instructions and components. All you need is a tobacco tin.

Price £1.40, post paid.

TRANSFORMER

Mains input 240, output—0.75V—5.5V—13V—1 amp. Size, height 3" x 3" x 2½" shrouded + 2 fuse holders.

95p, post paid.

5 COMPUTER PANELS

9" x 7" min 35 trans. OC44 EQ ACY17
2 Trim Pots min 70 condensers.
Min 80 diodes inc. OA81 + resistors.
Most transistors have long leads.

£1.25, post paid.

1973 CATALOGUE


Over 25 kits. Over 30 books. Plus components, cases, etc.

Only 10p, post paid.

ALL PRICES INCLUDE V.A.T.

AUTOMATIC WIRE STRIPPER

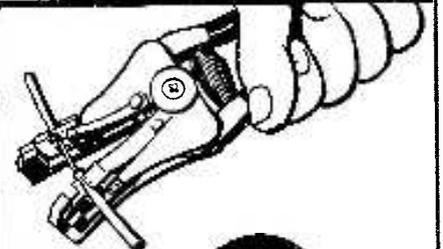AS SUPPLIED TO LEADING ELECTRONIC COMPANIES



PRICE
£2.95

INCL. PP & VAT

GRIPS AND STRIPS

WIRE

IN ONE OPERATION

IDEAL GIFT

ELECTROLINK

ULLSWATER CRESCENT
COULSDON CR3 2UG SURREY

POWER SUPPLY UNITS

AC-DC & DC-DC

Different Voltages
All English make
Fully Guaranteed
for parts & labour

AC.601 240V A.C. INPUT
OUTPUTS 3V, 4.5V, 6V, 7.5, 9V & 12V D.C.
MAX. CURRENT 500mA

AC.301 INPUT 240V A.C.
OUTPUT 6V, 7.5V, 9V D.C.
MAX. CURRENT 500mA

AC.201 INPUT 240V. A.C.
OUTPUT 9V & 12V. D.C.
MAX CURRENT 1 AMP

AC.105 INPUT 240V A.C.
OUTPUT 12V
MAX. CURRENT 6 AMP

AC.101 INPUT: 240V A.C.
OUTPUT 6V OR 7.5V or 9V
MAX CURRENT 500mA

DC.301 FULLY STABILIZED
INPUT: 12V D.C.
OUTPUT 6V, 7.5V & 9V D.C.
MAX CURRENT 500mA

DC.101 Suitable to use from Car cig. lighter.
INPUT: 12V DC
OUTPUT 7.5V or 9V DC
MAX CURRENT 500mA

NORMAN ROSE

(ELECTRICAL) LTD.,

Head Office:
"Norman House"
8 St. Chad's Place
London WC1X 9HJ
Telephone: 01-837 9111/3


Birmingham Branch:
29 Constitution Hill
Birmingham 19
Telephone: 021-236 4710

Manchester Branch:
25/27 Harkness St Ardwick
Manchester M12 6DS
Telephone: 061-273 1498

Bradford Branch:
10 Sackville Street
Bradford, Yorkshire
Telephone: 0274 26104

TO SPARK YOUR IMAGINATION!

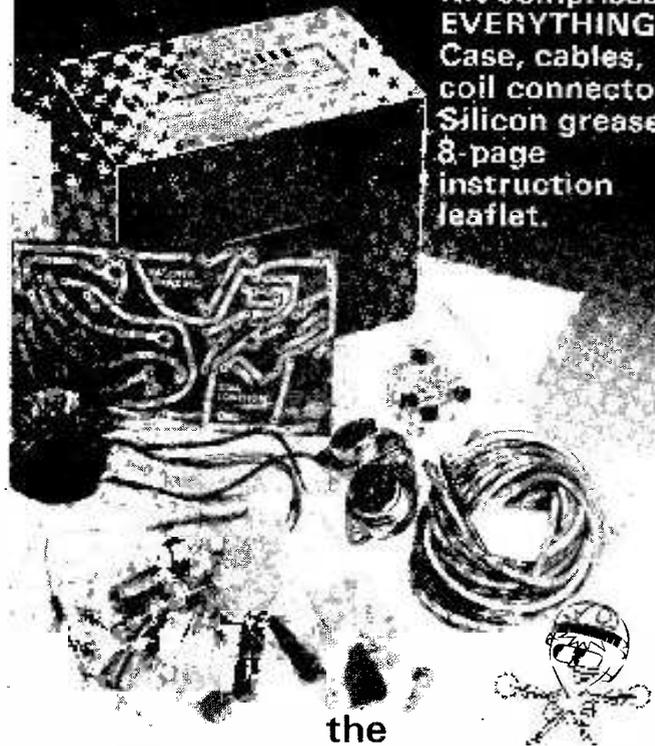Kit comprises
EVERYTHING:
Case, cables,
coil connectors,
Silicon grease,
8-page
instruction
leaflet.



the SPARKRITE Electronic Ignition Kit only £9.35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance.
- Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls.
- Longer spark plug life.
- Longer battery life.
- Contact breaker burn eliminated.
- Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: £9.35 inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available £11.55 inc. V.A.T. and postage. **GUARANTEED 5 YEARS**

ORDER NOW To: ELECTRONICS DESIGN ASSOCIATES,
82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9.35. Or for ready built unit £11.55.

NAME

ADDRESS

(Live near Walsall? Call in for an actual workshop demo. It really is convincing).

PW 1

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Pri. 120/240 V Sec. 120/240 V Centre Tapped and Screened

Ref. No.	VA	Weight lb oz	Size cm.	£	P & P p
07	20	1 8	7.0 x 6.0 x 6.0	2.32	30
149	60	3 12	9.9 x 7.7 x 8.6	3.45	36
150	100	5 8	9.9 x 8.9 x 8.6	3.79	52
151	200	8 0	12.1 x 9.3 x 10.2	6.45	52
152	250	13 12	12.1 x 11.8 x 10.2	8.41	67
153	350	15 0	14.0 x 10.8 x 11.8	11.22	82
154	500	19 8	14.0 x 13.4 x 11.8	16.25	-
155	750	29 0	17.2 x 14.0 x 14.0	22.10	-
156	1000	38 0	17.2 x 16.6 x 14.0	29.87	-
158	2000	60 0	21.6 x 15.3 x 18.1	49.25	-

**PLEASE NOTE
NEW ADDRESS
AS BELOW**

AUTO TRANSFORMERS

Ref. No.	VA	Weight lb oz	Size cm.	Auto Taps	£	P & P p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.22	22
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.40	30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	2.89	36
66	300	6 4	9.9 x 9.6 x 8.6	"	5.63	52
67	500	12 8	12.1 x 11.2 x 10.2	"	8.36	67
84	1000	19 8	14.0 x 13.4 x 14.3	"	15.19	82
93	1500	30 4	14.0 x 15.9 x 14.3	"	21.99	-
95	2000	32 0	17.2 x 16.6 x 14.0	"	39.17	*
73	3000	40 0	21.6 x 13.4 x 18.1	"	28.70	*

CASED AUTO TRANSFORMERS
115V 500W enclosed transformer, with mains lead and two 115V outlet sockets. £9.49. P & P 67p. 20 Watt version £2.02 P & P 27p.

TRANSFORMERS
PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	£	P & P p
111	0.5	2 4	4.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.22	22
213	1.0	1 4	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.44	22
71	2	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	1.90	22
18	4	2 12	8.3 x 7.7 x 7.0	0-12V at 2A x 2	2.68	30
70	6	3 8	8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.20	42
108	8	4 8	9.9 x 8.9 x 8.6	0-12V at 4A x 2	3.60	52
72	10	5 6	9.9 x 9.6 x 8.6	0-12V at 5A x 2	4.25	52
116	12	6 12	9.9 x 10.2 x 8.6	0-12V at 6A x 2	5.10	52
17	16	8 12	12.1 x 9.9 x 10.2	0-12V at 8A x 2	6.56	52
115	20	11 8	14.0 x 9.6 x 11.8	0-12V at 10A x 2	8.36	67
187	30	15 8	14.0 x 12.1 x 11.8	0-12V at 15A x 2	15.40	82
226	60	32 0	17.2 x 15.3 x 14.0	0-12V at 30A x 2	28.44	*

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P p
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.42	22
79	1.0	2 4	7.0 x 6.7 x 6.1	"	1.92	36
3	2.0	3 4	8.9 x 7.7 x 7.7	"	2.90	36
20	3.0	4 8	9.9 x 8.3 x 8.6	"	3.58	42
21	4.0	6 4	9.9 x 9.6 x 8.6	"	4.25	52
51	5.0	6 12	12.1 x 8.6 x 10.2	"	5.30	52
117	6.0	8 0	12.1 x 9.3 x 10.2	"	6.31	52
88	8.0	12 0	12.1 x 11.8 x 10.2	"	8.18	67
89	19.0	13 12	14.0 x 10.2 x 11.8	"	10.33	67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P p
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	1.90	30
103	1.0	2 12	8.3 x 7.4 x 7.0	"	2.80	36
104	2.0	5 8	9.9 x 8.9 x 8.6	"	3.87	42
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.26	52
106	4.0	10 0	12.1 x 10.5 x 10.2	"	6.99	52
107	6.0	12 0	14.0 x 10.2 x 11.8	"	10.35	67
118	8.0	18 0	14.0 x 12.7 x 11.8	"	13.51	97
119	10.0	25 0	17.2 x 12.7 x 14.0	"	16.93	*

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P p
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-428-69C	1.93	36
126	1.0	3 4	8.9 x 7.7 x 7.7	"	2.70	36
127	2.0	6 4	9.9 x 9.6 x 8.6	"	4.25	42
125	3.0	8 12	12.1 x 9.9 x 10.2	"	6.46	52
123	4.0	13 12	12.1 x 11.8 x 10.2	"	8.36	67
40	5.0	12 00	14.0 x 10.2 x 11.8	"	9.85	87
120	6.0	15 8	14.0 x 12.1 x 11.8	"	12.14	82
121	8.0	25 00	14.0 x 14.7 x 11.8	"	13.65	*
122	10.0	25 0	17.2 x 12.7 x 14.0	"	20.09	*
189	12.0	29 00	17.2 x 14.0 x 14.0	"	22.49	*

MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	MA.	Weight	Size cm.	VOLTS	£	P & P p
238	200	2	2.8x2.6x2.0	3-0-3	1.31	10
212	1A 1A	1 4	6.1x5.8x4.8	0-6 0-6	1.52	22
13	100	4	3.9x2.6x2.9	9-0-9	1.12	10
235	330,330	4	4.8x2.9x3.5	0-9 0-9	1.52	10
207	500, 500	1 00	6.1x5.4x4.8	0-8-9, 0-8-9	2.03	22
208	1A, 1A	1 12	7.0x6.4x6.1	0-8-9, 0-8-9	2.73	30
236	200, 200	4	4.8x2.9x3.5	0-15 0-15	1.52	10
214	300, 300	1 4	6.1x5.8x4.8	0-20 0-20	1.60	22
221	700 (D.C.)	1 8	7.0x6.1x6.1	20-12-0-12-20	1.41	30
206	1A, 1A	2 12	8.3x7.7x7.0	0-15-20, 0-15-20	3.08	36
203	500, 500	2 4	8.3x7.0x7.0	0-15-27, 0-15-27	2.82	38
204	1A, 1A	3 4	8.9x7.7x7.7	0-15-27, 0-15-27	2.86	38

**PLEASE ADD 10% FOR V.A.T.
INCLUDING P. & P.**

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

Audio

**THE HI-FI
MAGAZINE FOR
LEISURE LISTENING**

Britain's exciting new-style magazine in music and hi-fi, AUDIO is about every important aspect of the modern sound scene from the make-up of sound, to the latest means of reproducing it . . . the equipment, its installation and its operation. AUDIO examines new trends, looks at the latest discs and tapes, shows you how to get the most for your money in clarity, definition and craftsmanship.

Audio

Published third Friday of each month 20p

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio & Electronics School, P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to

NAME

ADDRESS

..... Please

..... W.C. 14

**BRITISH NATIONAL RADIO
AND ELECTRONICS SCHOOL**


SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts

r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £11.60. P. & P. 40p.

DE LUXE STEREO AMPLIFIER

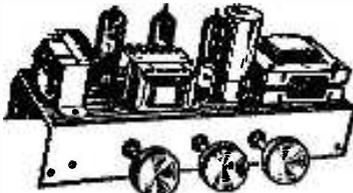

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate

smoothing with negligible hum. Valve line up: -2 x ECL86 Triode Pentodes. 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £9.90 P. & P. 50p.

POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. and 12v. at 1 amp on load (1amp intermittent).

Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £5.00 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For T03, complete with mica's and bushes. Size 2 1/2" x 3" approx. 28p pair. P. & P. 6p.

HIGH GRADE COPPER LAMINATE BOARDS 8" x 6" 5 for 55p P. and p. 23p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2-10 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500mA. £1.00. P. & P. 25p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1.10. P. & P. 26p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.65. P. & P. 35p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100µA. For balance or tuning. Approx. size 1" x 1" x 1" deep. Limited number. 88p. P. & P. 12p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price £1.00 P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 6p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents 80p
Transistor Equivalents 90p
Transistor Characteristics £1.15
POST FREE.
All three together £2.60

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias. 95p, Post Free

Open 9-5.30 Monday to Friday. 9-5 Saturday

Early closing Wed.

A few minutes from South Wimbledon Tube Station.

RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing. LATEST B.S.R. C109/C129 AUTOCHANGER UNITS with latest stereo/mono compatible cartridge £7.60+ 50p P. & P. GARRARD SP25 Mk III with heavy precision machined die cast turntable £10.58, carr. 55p.

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60 etc. or B.S.R. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). NOW ONLY £4.95, P. & P. 70p.

LATEST AGOS GP91/180 mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1.50 P. & P. 15p.

SONOTONE STAHG COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.30 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.80. P. & P. 15p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo/78. £1.63 P. & P. 15p.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.50 P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £4.40 P. & P. 60p

ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £5.85 P. & P. 60p.

SPECIAL OFFER ! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £9.25 Carr. 75p
Cabinet Available Separately £4.95 Carr 65p
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £7.15 Carr. 75p

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 40p BARGAIN PRICE £3.30

LOUDSPEAKER BARGAINS

5in. 3 ohm £1.05, P. & P. 15p. 7 x 4in. 3 ohm £1.15, P. & P. 20p. 10 x 6in. 3 or 15 ohm £1.90, P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.62, P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £2.50, P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with two inbuilt tweeters and crossover network £4.65, P. & P. 30p. EMI Ceramic magnet heavy duty tweeter. Approx 3 1/2". Available 3 or 8 or 15 ohms. £1.25 + 20p p. & p. BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with HiDux ceramic ferrobar magnet assembly £7.50. Guitar models: 25w. £7.50 35w. £9.35. P. & P. 45p

SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS

With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £2.70. P. & P. 35p.



Also available specification as above but size 10" x 6" £2.70 and size 8" round £2.60. P. & P. 35p.

LIMITED NUMBER EMI 2 1/2" 8 ohm Tweeters. Mounted on flat bracket size 2 1/2" wide x 7 1/2" long. 70p per pair plus 15p P. & P. Ex equipment but new and tested 70p per pair plus 15p P. & P.


12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling. 3, 8 or 15 ohm £2.45, P. & P. 36p. 35 ohm SPEAKERS 3in. only 70p P. & P. 25p.

"POLY PLANAR" WAFER-TYPE. WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.55 each. P. & P. 34p.

VYNAIR & REXINESPEAKERS & CABINET FABRICS app. 5 1/2 in. wide. Our Price 85p yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

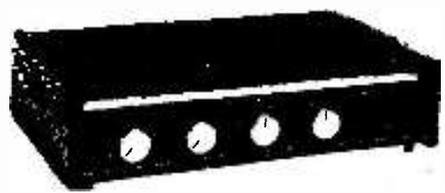HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1MΩ. Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E. AMPLIFIER KIT £11.55 P. & P. 25p (Magnetic input components 33p extra) POWER PACK KIT £3.30 P. & P. 35p CABINET £3.30 P. & P. 35p

(Post Free if all units purchased at same time) Full after sales service

Also available ready built and tested £23.10. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi Fi Discotheque use, etc.




3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £5.50. P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4.50. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

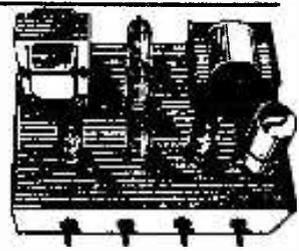A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other.



Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 15p + SAE (Free with parts). All parts sold separately. ONLY £8.80 P. & P. 60p. Also available ready built and tested £12.10 P. & P. 70p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable stereo earmuffs. Wired and fitted with standard stereo $\frac{1}{4}$ inch plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.80, P. & P. 25p.

PRICES NOW INCLUDE VAT

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

**Fully guaranteed
Individually packed
VALVES**

B12H	£1.75	ECH84	40p	OA2	38p
CY31	40p	ECL50	40p	OB2	35p
DAF96	40p	ECL82	31p	PABC80	35p
DF96	40p	ECL83	68p	PC97	41p
DK96	51p	ECL86	36p	PC900	42p
DL92	32p	EF36	50p	PCC84	36p
DL94	45p	EF37A	85p	PCC89	45p
DI96	40p	EF40	62p	PCC189	49p
DM70	40p	EF41	65p	PCE800	75p
DY86	29p	EF80	25p	PCF80	25p
DY87	28p	EF83	60p	PCF82	27p
DY802	30p	EF85	31p	PCF84	54p
E88CC/01	£1.08	EF86	27p	PCF86	50p
		EF89	25p	PCF200	60p
E180CC	37p	EF91	27p	PCF201	60p
E181CC	90p	EF92	31p	PCF801	44p
E182CC	£1.08	EF95	31p	PCF802	45p
		EF183	26p	PCF805	80p
		EF184	31p	PCF806	85p
EA50	18p	EFL200	67p	PCF808	85p
EABC80	27p	EL3	59p	PCF200	65p
EAF42	40p	EL41	55p	PCF81	50p
EB91	20p	EL84	21p	PCL82	30p
EBC33	45p	EL85	37p	PCL83	60p
EBC41	50p	EL86	36p	PCL84	35p
ECC81	31p	EL90	31p	PCL85	40p
EBF80	36p	EL95	38p	PCL86	43p
EBF83	40p	EL500	76p	PFL200	60p
EBF89	27p	EL504	72p	PL36	50p
ECC91	27p	EM31	22p	PL81	40p
ECC92	25p	EM80	36p	PL82	35p
ECC93	25p	EM84	31p	PL83	36p
ECC94	27p	EM87	62p	PL84	30p
ECC95	36p	EV51	32p	PL500	60p
ECC96	80p	EV86	36p	PL504	62p
ECC98	39p	EV81	40p	PL508	70p
ECC189	48p	EV88	40p	PL509	£1.05
ECF80	31p	EV41	45p	PL802	88p
ECF82	31p	EV20	22p	PX4	£2.50
ECF83	67p	EZ21	24p	PY50	35p
ECF801	56p	EZ34	52p	PY81	30p
ECH81	25p	GZ67	63p	PY82	23p
ECH63	40p	KT66	22.30	PY83	30p
		N78	£1.60	PY88	32p

TRANSISTORS, ZENER DIODES etc.

OA5	20p	OC71	12p	IN823A	£1.30	3N154	95p	BC108	10p	GET115	45p
OA10	25p	OC72	20p	IN4785	50p	3N159	£1.45	BC113	10p	GET116	50p
OA70	10p	OC73	30p	I2MT5	35p	6FR5	45p	BC118	20p	GEX66	£1.50
OA71	10p	OC75	25p	I2MT10	33p	12FR60	73p	BCY72	15p	NKT222	20p
OA73	7p	OC76	25p	I2T5	87p	40954	£1.25	BF115	25p	NKT304	50p
OA74	7p	OC81	20p	I2T10	65p	40955	£1.25	BF173	20p	RAS310AF	
OA79 (6D15)	10p	OC81D	20p	2G385	51p	40966	£1.25	BFY51	20p		
		OC82	25p	2G403	51p	40668	£1.25	BFY52	20p	SD918	26p
OA81	8p	OC82DM	30p	2N1306	25p	40669	£1.25	BS	45p	SD928	31p
OA91	7p	OC83	25p	2N1307	25p	AC126	25p	BS2	47p	S9438	32p
OA200	7p	OC83B	15p	2N1307	25p	AC127	25p	BSY29	25p	SD94	21p
OA202	10p	OC84	25p	2N2147	64p	AC176	20p	BU100	£1.80	SD988	46p
OA210	25p	OC122	50p	2N2411	£1.50	ACY17	25p	BYZ13	25p	V405A	40p
OA211	30p	OC139	25p	2N2904A	25p	ACY28	17p	BYZ16	63p	Z2A51CF	78p
OC22	50p	OC140	40p	2N2989	£4.00	AD149	50p	CRS1/10	25p	ZR11	33p
OC25	40p	OC170	25p	2N3053	20p	AD161	35p	CRS1/20	38p	ZR21	42p
OC26	25p	OC171	30p	2N3054	50p	AD162	35p	CRS1/30	40p		
OC28	60p	OC172	37p	2N3055	84p	AD163	35p	CRS1/35	43p		
OC29	60p	OC200	40p	2N3730	50p	AF127	20p	CRS1/40	48p		
OC35	50p	OC201	75p	2N3731	£2.75	AF139	30p	CRS3/05	30p		
OC36	56p	IN21B	30p	2N4172	50p	AF178	48p	CRS3/20	38p		
OC38	42p	IN25	90p	3F100	62p	AF186	40p	CRS3/30	43p		
OC44	17p	IN43	10p	3FR5	32p	AFY23	25p	CRS3/40	55p		
OC45	18p	IN70	7p	3N128	87p	AFY29	48p	CS2A	65p		
OC70	12p	IN77	15p	3N139	£1.75	BAW19	28p	CV102	25p		
		IN702-72536p		3N140	97p	BC107	10p	GET103	23p		
PY800	35p	UAF42	50p	UY85	35p	3Q4	55p	6AH6	50p	6BA6	25p
PY801	45p	UBC41	48p	VR105/30	85p	384	33p	6AK5	35p	6BE6	25p
QQVOC3-10	£1.10	UBF80	35p	VR150/30	35p	3V4	48p	6AK8	30p	6BG6G	47p
R17	45p	UCF89	34p	Z800U	£1.40	5B254M	£2.75	6AL5	18p	6BJ6	45p
R19	35p	UCF85	35p	Z801U	£1.40	5B255M		6AL5W	35p	6BQ7A	43p
STV280/40	£3.20	UCH42	60p	Z803U	£1.10			6AM6	35p	6BR7	£1.09p
STV280/80	£8.20	UCH81	35p	Z900T	90p	5R4GY	65p	6AN8	60p	6BW6	80p
TT21	£3.86	UCL82	35p	IR5	35p	5U4G	80p	6AQ5	38p	6BW7	80p
U25	70p	UCL83	55p	IS4	30p	5Y3GT	35p	6AQ6W	45p	6C4	25p
U26	70p	UCL85	35p	IS5	30p	5Y4G	35p	6AS6	30p	6C6	20p
U27	45p	UF80	30p	IT4	30p	5Z3	70p	6AT6	30p	6CH6	55p
U191	65p	UF89	35p	IX2A	36p	5Z4	75p	6AX4GT	50p	6D6	15p
U501	70p	UL1	60p	IX2B	50p	5Z4GT	32p	6EA8	60p	6EA8	60p
UABC80	30p	UL84	35p	IX25	£7.50	6AB7	35p	6E23	80p	6E23	80p
		U5	65p	IX26	40p	6AB7	35p	6F33	£1.35	6EB6	35p
		UY41	45p	IX26	15p	6AC7	45p	6B6M	25p	6B7H	23p

Colomor ALL valves guaranteed

6J4WA	85p	L8A17	40p	6060	50p
6J5	35p	14S7	70p	6064	45p
6J5GT	30p	19AQ5	40p	6085	85p
6J6	25p	19G3	£5.75	6080	£1.55
6J7G	30p	19G6	£5.75	6146	£1.75
6J7M	35p	19H4	£5.95	8020	£3.75
6K6GT	55p	20P4	£1.00	9001	15p
6K7	40p	25L6GT	50p	9002	40p
6K7G	17p	30C15	70p	9003	45p
6K8GT	40p	30C17	85p	9004	12p
6K25	75p	30C18	75p	9006	12p
6LAM	1.35	30F5	80p		
6LA7GT	40p	30FL1	70p	C.R. Tubes	
6S7GT	20p	30FL2	95p	VCR97	
6S8GT	40p	30FL4	80p		£4.00
6S9GT	40p	30L15	80p	VCR517B	
6S7GT	20p	30L17	80p		£5.00
6S7GT	20p	30L12	75p	VCR517C	
6S7GT	20p	30P19	70p		£7.00
6S7GT	20p	30P11	70p		£8.10
6S7GT	20p	30PL13	90p	88D	£8.10
6S7GT	20p	30PL14	85p	88J	£8.10
6S7GT	20p	35L6GT	50p	88L	£8.10
6S7GT	20p	35W4	30p		
6S7GT	20p	35Z4GT	55p	Photo Tubes	
6X4	33p	50C5	45p	CMG25	
6X5G	25p	50CD6G	£1.10		£2.50
6X5GT	25p	50EH5	55p	931A	£2.50
6Y6G	75p	6097C	50p		
6-30L2	35p	76	75p		£16.00
6Z4	40p	78	50p	Special Valves	
6Z4	40p	80	55p	CV2339	
7B7	60p	723A/B	£7.00		£18.00
9D6	60p	803	£5.50	JP9/7D	
11E2	£3.70	805	£12.00		£25.00
12A7	27p	807	50p		£4.50
12AT7	27p	813	£4.00	K301	£4.50
12AU7	24p	832A	£2.70	K305	£11.00
12AV6	40p	866A	£1.25	K308	£14.50
12AX7	25p	931A	£4.75	K337	£14.50
12BA6	25p	934	35p	KRN2A	
12BE6	35p	955	35p		£3.15
12BH7	23p	956	30p	WL417A	
12C8	30p	957	35p		£1.35
12D1	£2.85	991		3J92/E	
12K5	95p	2051	70p		£25.00
12K7GT	45p	5933	£1.00	714AY	£3.60
12K8GT	40p	6037	55p	725A	£22.50

V.A.T.

Please add 10% to all orders

METERS

Full List of our very large stock of meters on request.

29/41FT. AERIALS each consisting of ten 3ft., 7in. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in canvas bag. £7.50 new £4.50 slightly used. Carriage 50p.


Colomor (Electronics) Ltd.

170 GOLDHAWK ROAD, LONDON W12.
RETAIL: 743 4946 TRADE: 743 0899
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-11 p.m.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEARLY HARBOR TIDY!

DISCOUNT PRICES

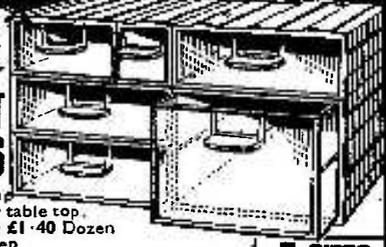

5 SIZES ALL INTERLOCK

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D, 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS (5" x 2 1/4" x 2 1/4") £1.40 Dozen
DOUBLE UNITS £2.30 Dozen
TREBLE (3D) £2.50 for 8
DOUBLE TREBLE 2 drawers in one outer case (6D2) £3.60 for 8 EXTRA LARGE SIZE (6D1) £3.40 for 8, Carriage 35p Orders over £10 post free. **QUANTITY DISCOUNTS!** 5% in £1 for orders over £10, 7% over £20, 10% over £50. Quotations for large quantities. **PLEASE ADD 10% VAT TO TOTAL REMITTANCE.**

(Dept. PW1), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

ELECTROLYTIC CAPACITORS µF/V

1/50, 1-6/25, 2/150, 2/350, 3/150, 4/15, 4/300, 4-7/16 5/25, 8/50, 8/150, 8/275, 10/12, 10/50, 12-5/25, 15/9, 16/85, 16/300, 25/25, 25/60, 50/15, 60/10, 75/15, 100/18, 100/25, 120/75, 125/15, 150/16, 200/10, 250/12, 300/10, 300/12, 500/12, all at 5p each.

250µF 25V, 450/35, 500/25, all at 7p each.

8/350, 16/350, 20/450, 32/350, 32/450, 80/300, 80/450, 100/350, 100/450, 500/50, 1000/16, all at 15p each.

500/100, 1000/25, 1250/25, 2200/25, all at 20p each.

1000/50, 1500/50, 2000/35, 4500/25, 5000/25, 6000/30, 8000/30, 10,000/15, 10,000/25, 12,500/35, 13,500/38, all at 35p each.

2000/50, 2000/70, 2500/70, 4500/64, 5000/50, 10,000/50, 12,500/50, 50p each.

2000/100, 5000/70, 25,000/25, 33,000/25, 45,000/12, 50,000/15, 60p each.

ADD 10% V.A.T.

ELEKON ENTERPRISES
224a St. Paul's Road, Highbury Corner,
London N1 2LJ Tel: 01-359 4224

SPECIAL INTRODUCTORY OFFERS—IMPORTER TO CONSUMER!
ALL NEW GOODS—FULLY GUARANTEED—PLEASE ADD 10% V.A.T. TO TOTAL ORDER INCLUDING P. & P.

HILLS HEADPHONE JUNCTION BOX MODEL JB-3 Designed to connect headphone to amplifier previously not fitted with headphone socket, or alternatively for remote switching 3 position switch allows instant switching between speakers and headphones or both simultaneously. Rec. Retail OUR PRICE £1.25 P. & P. 15p	HILLS DYNAMIC HEADPHONE MODEL H-707 VS DE-LUXE An extremely high quality headphone supplied with Padded Headphone and Earcups together with SLIDER volume controls for precise listening levels. Specially offered at an unbeatable price. 8 ohms 20-20,000Hz. Retail Price OUR PRICE £5.75 P. & P. 25p	CAR STEREO SPEAKERS MODEL CRB-200 These dual purpose Car Speakers can be used for either shelf mounting or converted to door mounting. 5in 5 watt Speakers ensure a brilliant audio performance. Rec. Retail OUR PRICE £3.50 *Per pair P. & P. 25p	ANTEX SOLDERING IRONS 12p P & P REC. RETAIL OUR PRICE X25 25 watt 1-92 1-40 CCN240 15 watt 2-14 1-60 S73 Stand 88 X25E replacement 25w element 1-66 CCN240E 15w 1-06 Hills Staigh Headphone Extension Cable, 15ft. 99p
"HOMER" INTERCOM One of the leading makes. Ideal for home, office, factories, etc. This 2-station intercom includes volume control and on-off switch. Supplied with 66ft. cable and batteries. Rec. Retail OUR PRICE £2.75 P. & P. 15p	HILLS DYNAMIC HEADPHONE MODEL H-101 VSM Offered at a remarkably low price, supplied with padded Headband and Earcups, adjustable volume controls with stereo and mono switch. 8 ohms imp. 30-18,000Hz. Rec. Retail OUR PRICE £3.75 P. & P. 25p	PLINTH AND COVER FOR GARRARD SP-25 III OR BSR MP-60. OUR PRICE £2.75. plus 65p P. & P. ELAC SPEAKER, 8in 8 ohm CERAMIC AND TWEETER, £2.00, plus 20p P. & P. OTHER ITEMS AT BARGAIN PRICES OFFERED IN OUR AUDIO COMPONENTS CATALOGUE. PLEASE WRITE FOR A FREE COPY (ENCLOSING 3p STAMP).	

HILLS COMPONENTS LTD.
DEPT. (PW4), UNIT No. 6, MELNITE INDUSTRIAL ESTATE, BRIXTON ROAD, WATFORD, HERTS. WD2 3SL. Tel. Watford 2711



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 72p. Postage 20p for first one then 10p for each one ordered.

MUSIC ON TAPE

A further buy enables us to offer these at an even lower price—namely 65p each or 5 for £2.50. Send for list of titles. We can't repeat when sold out.

BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits, 37p each, 10 for £3.70.



CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 38p each or 10 for £3.42.



12 VOLT 1 1/2 AMP. POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £2.20 plus 20p post & packing. Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps — maximum load 250W—that is from 6 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £6.33 plus 65p post.

BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price 50p each. Pixolin lid 11p extra.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 25p each.

CONNECTING WIRE

7/0076 Copper conductors. 500 metre drums available in the following colours:—Red/Brown—Yellow—Green/Grey—Blue/Green—Red/Orange—Green/White—Grey/White—Blue/Orange—Brown/Red—Brown/White—Red/Grey—Blue/Grey—Blue/Brown. Price £2.20 per drum plus 10p post. State alternative colours.

Screened Cable 7/0076 core suitable for pick up or mike lead for later—connecting amplifiers. 10 metres. 33p.

U.V. LIGHTING


Useful for flaw detection in metals and for looking for water marks, etc., also for fitting over tropical fish tanks. African violets and other indoor plants which must have U.V. for healthy growth. The outfit comprises of a 8" U.V. tube—choke—starter holder and tube ends. Price £2.20 plus 20p post.

MINIATURE SEALED RELAY

American made. Our Ref. No. REL A1. Measures only 1/2" wide x 1/4" thick and 3/8" high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9-12 volt will close it. Idea for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price 28p including base.

6 DIGIT COUNTER

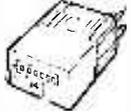Resettable, 440 ohm coil up to 25 impulses per second. Ex-equipment but guaranteed perfect. £2.20 each.



Ditto but not resettable £1.10

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24" x 18" £1.69 13" x 10" £1.21


KETTLE ELEMENTS

Made by the famous A.E.I. Co. Complete with washers and combined fixing ring and plug shroud. Normal 2 round pin and flat pin earth connection and overload reset push button. 2 Models—1 1/2" (approx.) suitable for Swan and other similar models—1 1/4" (approx.) suitable for G.E.C., Hotpoint, etc. All quick boil 2 1/2 Kw elements at 240V. Price £1.38 each.



WINDSCREEN WIPER CONTROL

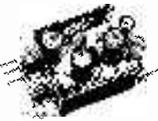Vary speed of your wiper to suit conditions. All parts and instructions to make. £2.48.



MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500mW power output 72p. Model 1172 750mW power output 94p. Model EP9000 4 watt power output £1.60. Unilex DIY STEREO. Complete £11.30.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering etc., etc. A real bargain at £2.05.



MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January 73. All electronic parts £2.20 post paid.

6 MAINS TRANSFORMERS

Our Ref: MTM1 27 volt at 8 amps. Upright mounting fully shrouded—flying leads—fully tapped primary. Price £3.30.

Our Ref: MTM2 12v at 1 amp. Upright mounting with fixing lugs, tag connection. 240v primary—12v 1 amp secondary. Price 63p.

Our Ref: MTM3 6.3v 2 amp upright mounting with fixing lugs, tag connections, 240v primary 6.3v 2 amp secondary. Price 77p.

Our Ref: MTM4 18v 1/2 amp with thermal cut-out, upright mounting with fixing lugs—tag connections. Primary 240v, secondary 18v at 1/2 amp. Price 83p.

MAINS ISOLATION 350 watts earth shielded—flex leads—upright mounting lugs for fixing terminals for output. Price £3.50 each.

MAINS TRANSFORMER BARGAIN. Standard mains 240v input. Secondary 2.4v 9 amp intermittent 3 amp continuous. Price 55p.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp. sockets in metal box to take standard 13 amp. fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work. £2.50 plus 25p post and ins.

THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2.95 plus 20p post and insurance. Industrial model 5A £3.30. (Not on plate).



THIS MONTH'S SNIP

WALL THERMOSTATS. Made by the famous Smiths Instrument Co. called Colourstat. Wall mounting and in a handsome plastic case. (Cream and beige). Adjustable by slider (lockable) and may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates (frost) (very warm). etc. The thermostat will control heaters, etc. up to 15 amp at normal mains voltage and is ideal for living room, bedroom and greenhouse, etc. Price £1.65. Don't miss this.


TWENTYLITE

Fluorescent lighting units with polyester choke and finished white enamel. 40 ins. model. Ideal kitchen, bedroom, hallway, porch, lift, etc., with tube. Assembled ready to install. Price £2.20 + 40p p. & p.




MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system. We believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for this:— 1 Unilex Amplifier Ref. E.P. 900 £1.60. 1 Unilex Pre-Amp Ref. EP.9001 £1.98. 1 Unilex Power Unit Ref. EP.9002 £2.53. 1 Control panel kit with spun aluminium faced knobs £3.30. Or the complete outfit—£11.30 post paid. Pair of 15 ohm speakers made by E.M.I. are also available if required, Price £3.30 the pair. No extra postage if ordered with the above, otherwise add 25p.

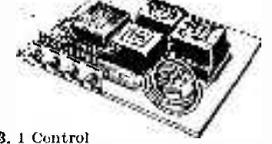

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs. per min. Some of the many uses of this timer are Machinery control, Boiler firing. Dispensing and Vending machines. Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £6.33 plus 25p post and insurance. Don't miss this terrific bargain.

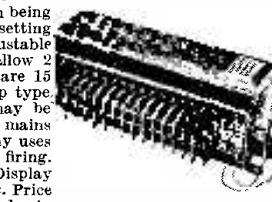

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:—

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated. Size 3in. x 3in. x 2in. deep. Price £3.85 as illustrated but less case.



TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters. Comprises motor, impeller, 2kW, element allowing switching 1, 2W, and with thermal safety cut-out. Can be fitted into any metal case or cabinet. Only needs control switch, £2.75. Don't miss this. Control Switch 44p, P. & P. 40p.



PRESSURE SWITCH

Containing a 15 amp. change over switch operated by a diaphragm which in turn is operated by air pressure through a small metal tube. The operating pressure is adjustable but is set to operate in approx. 10in. of water. These are quite low pressure devices and can in fact be operated simply by blowing into the inlet tube. Original use was for washing machines to turn off water when tub has reached correct level but no doubt has many other applications. £1.38.



SOLDER GUN

A must for every busy man, gives almost instant heat also illuminated job. 100 watt £2.47 plus post and ins. 20p.



PAPST MOTORS

Est. 1/40th h.p. Made for 110-120 volt working but two of these work ideally together off our standard 240 volt mains. A really beautiful motor. extremely quiet running and reversible. £1.65 each. Postage one 23p. two 33p. 230V model £3.30.



HOURLY MINUTE TIMER

Made by Smiths. Complete with control knob and calibrated dial. Useful in kitchen, office, dark-room, etc. Bargain at 55p.



DRILL CONTROLLER

NEW IKW MODEL Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.95. Made up model also available. £2.95.



MAINS TRANSISTOR P.P.

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: P.P1, P.P3, P.P4, P.P6, P.P7, P.P9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.10

MULTI-SPEED MOTOR.

Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 and 15,500 r.p.m. Shaft is 1 in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price 97p plus 23p postage and insurance.



ULTRA-SONIC REMOTE CONTROLLER

As featured this issue! Our 1974 catalogue lists hundreds of bargains and probably many of the parts needed for this project. 66p brings the catalogue and the next 6 monthly supplements.

MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2" x 2" x 2in. £2.20 each.



15A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you awake — switch on lights to ward off intruders — have a warm house to come home to. All these and many other things you can do with famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.15 + 20p p. & p. or with glass front, chrome bezel, 83p extra.



MACLAREN THERMOSTAT

Make and break 20 amp A.C. with the sensor probe coupled by 2 feet capillary covering range of 10-100°C—complete with large engraved control knob. Price 83p.

J. BULL (ELECTRICAL) LTD.

(Dept. P.W.) 7 Park Street, Croydon CRO 1YD
Callers to: 102/3 Tamworth Road, CROYDON

WEYRAD

IMPORTANT ANNOUNCEMENT

IT IS WITH GREAT REGRET THAT WE HAVE TO STATE THAT OWING TO REVISED COMPANY POLICY WE SHALL NO LONGER BE PRODUCING COMPONENTS FOR AMATEUR CONSTRUCTORS OR SMALL QUANTITY USERS.

THIS CHANGE WILL COME INTO EFFECT IMMEDIATELY AND WE ARE UNABLE TO ACCEPT FURTHER ORDERS FROM THE TRADE OR INDIVIDUAL CUSTOMERS. EXISTING ORDERS WILL BE COMPLETED WITH A MINIMUM OF DELAY.

WE ARE SORRY TO HAVE TO TAKE THIS STEP WHICH HAS BEEN FORCED UPON US BY INCREASES IN THE COST OF LABOUR AND MATERIALS WHICH NOW MAKE ANY FORM OF SMALL SCALE PRODUCTION HOPELESSLY UNECONOMIC. IN CLOSING THIS PARTICULAR FACET OF OUR BUSINESS WE SHOULD LIKE TO THANK ALL OUR PAST AND PRESENT CUSTOMERS FOR THEIR VALUED SUPPORT OVER MANY YEARS.

WEYRAD (ELECTRONICS) LIMITED

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR.

Tel. 021-327 2339

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.
Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner. Light sensitive aerosol spray £1.00 plus Developer and Etchant 50p postage

NEWER THAN NEW!!!

Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.
75mm x 100mm 33p
150mm x 100mm 65p
150mm x 200mm £1-32

SILICON N.P.N.

Type	Volts	Frequency	Price	Type	Volts	Frequency	Price
BC 108	30	150 MHz	10p	2N 697	60	40 MHz	12p
BC 109	30	150 MHz	10p	2N 709	15	900 MHz	30p
BF 179	225	125 MHz	40p	2N 718	60	60 MHz	12p
BF 180	30	625 MHz	25p	2N 753	25	250 MHz	12p
BFW 58	80	80 MHz	15p	2N 744	20	300 MHz	12p
BFX 43	30	500 MHz	20p	2N 1613	75	60 MHz	17p
BFX 86	40	50 MHz	17p	2N 2220	60	250 MHz	15p
BFY 53	30	50 MHz	10p	2N 3053	60	100 MHz	17p
BSX 19	40	500 MHz	10p	2N 3707	30	12p	
BSX 67	30	200 MHz	12p	2N 5179	20	900 MHz	40p

SPECIAL OFFER

Uni-Junction Transistor Similar to 2N2646—25p

POSTAGE (MINIMUM) 20p PER ORDER

ALL GOODS 10% V.A.T.

MICROWAVE DEVICES

CL 8300	Gunn effect oscillator	9.4 GHz	£40
CL 8370	ditto	9.5 GHz	£10
CL 8380	ditto	10.5 GHz	£10
CL 8390	ditto	11.5 GHz	£10
CL 8430	ditto	9.35 GHz	£40
CL 8450	ditto	9.35 GHz	£40
CL 8470	ditto	9.35 GHz	£40
BXY 27	Varactor Diode. "S" Band. Cut-off	70 GHz	£1
BXY 28	Varactor Diode. Cut-off	100 GHz	£1
BXY 32	Frequency Multiplier. "X" Band	150 GHz	£1
BXY 35A/C	ditto	25 GHz	£1
BXY 36C/D	ditto	75 GHz	£1
BXY 37C/D	ditto	100 GHz	£1
BXY 38C/E	ditto	120GHz	£1
BXY 39C/D	ditto	150 GHz	£1
BXY 40D/E	ditto	180 GHz	£1
BXY 41C/D/E	ditto	200 GHz	£1
CV 7777 (AAV 51)	Microwave Mixer Diode	18 GHz	£2
CAY 10	Microwave Detector Diode	250 GHz	£5
AEY 13	Microwave Tunnel Diode	6 GHz	£5
AEY 16	ditto	10 GHz	£10
AEY 17	Microwave Detector	18 GHz	£3
AEY 31A	ditto	18 GHz	£3
BAW 95	Schottky Barrier Diode	12 GHz	50p

SILICON P.N.P.

Type	Voltage	Frequency	Price
BCY 71	45	200 MHz	12p
BFS 92	100	70 MHz	20p
BFS 95	40	70 MHz	17p
BFX 12	25	210 MHz	10p
2N 2906	60	200 MHz	15p
2N 3702	40	100 MHz	11p
2N 3703	50	100 MHz	12p
BFR 64	40	1,200 MHz	£1
BLY 89A	35	650 MHz	£5
BLY 93A	60	500 MHz	£5
BLY 218	36	1,200 MHz	£2
2N 709	15	800 MHz	15p
2N 3926	36	250 MHz	£1

HIGH FREQUENCY, POWER

GERMANIUM P.N.P.

Type	Voltage	Frequency	Price
ACY 44	50	1 MHz	10p
ADY 26	80	75 watts	£1
AF 124	20	75 MHz	20p
AFY 19	32	350 MHz	20p
ASY 32	25	5 MHz	10p
ASZ 21	15	450 MHz	20p
GET 113	32		
GET 120	32	2 watts	10p
OC 123	50	1 MHz	10p
OCP 70	Light-sensitive		20p
2N 1307	30	10 MHz	15p
2N 1309	30	15 MHz	15p
2N 443	60	150 watts	£1

£1 100 1/2 WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

POSTAGE 20p

PACK No. 1

£1 1 VERO-BOARD CUTTER
5 1/2 in. x 1 in. x 15 BOARDS
50 SQ. INS. "ODD PIECES"
VERO

POSTAGE 20p

PACK No. 3

£1 20 ASSORTED UNUSED
MARKED, TESTED
TRANSISTORS
BC108 ETC.

POSTAGE 20p

PACK No. 5

£1 6 COMPUTER PANELS
CONTAINING MASSES OF
DIODES, TRANSISTORS,
INDUCTORS, RESISTORS
& CAPACITORS

POSTAGE 27p

PACK No. 7

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

POSTAGE 20p

PACK No. 2

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

POSTAGE 20p

PACK No. 4

£1 1 TRANSISTORISED
SIGNAL TRACER KIT
1 TRANSISTORISED
SIGNAL INJECTOR KIT

POSTAGE 20p

PACK No. 6

£1 100 RESISTORS
100 CAPACITORS
(ASSORTED TYPES)


POSTAGE 20p

PACK No. 8


now...

Project 80

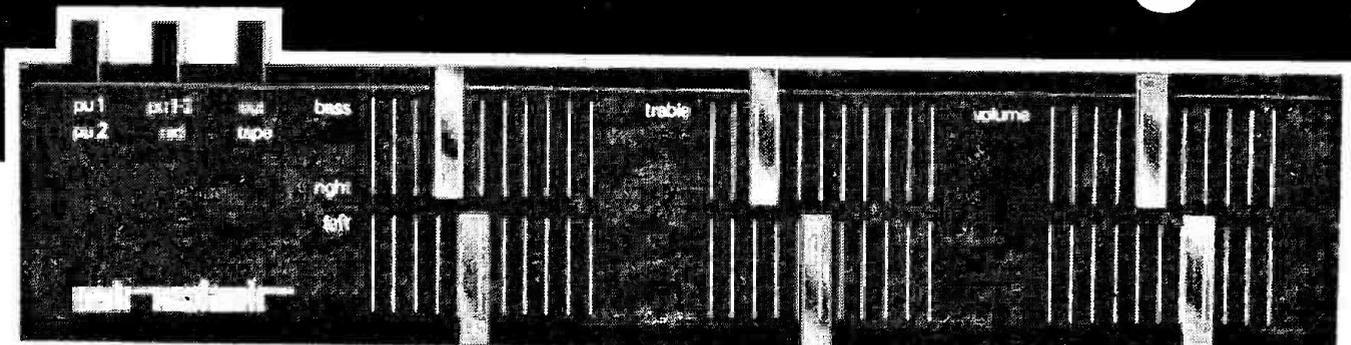...exciting new thinking
in modular hi-fi design



Stereo 80 pre-amplifier/control unit

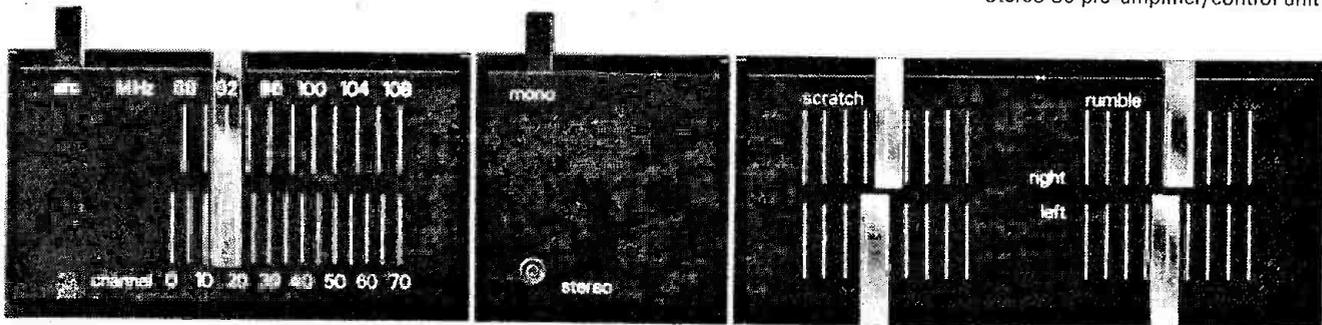


Project 80 tuner

Stereo decoder

Project 80 Active Filter Unit (AFU)

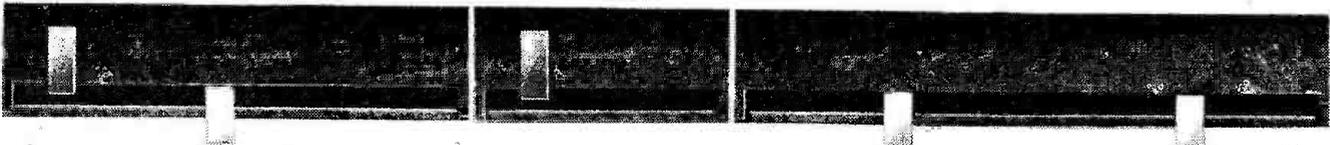the slimmest, most elegant hi-fi modules ever made



Living with hi-fi takes on new meaning now that Project 80 is here. These amazing new modules mark a brilliant technical advance all round; their size and presentation bring exciting new opportunities to install systems in ways hitherto only dreamed about but never before made practical. You can build a Project 80 system virtually anywhere and it is unbelievably simple to install and connect up. Everything that could possibly be wanted in a top quality do-it-yourself domestic hi-fi system will be found in Project 80 – compactness, elegantly ultra-modern styling, ease of fixing and operation, new control methods, and above all superb performance. New as well as popular established ideas on installation are featured on page four of this announcement to provide just a few examples of the system's fantastic versatility.

sinclair

Project 80 new modules


Stereo 80 pre-amplifier and control unit

As with other Project 80 units, the Stereo 80 is mounted by means of two bolts fixed at the rear which pass through holes drilled in the wood or plastic on which modules are to be mounted. *All the electronics are contained within the 3/4" deep front panel!* Connecting leads are taken away similarly out of sight. Each channel in the Stereo 80 has its own independent tone and volume controls operated by sliders. This enables exceptionally good environmental matching to be obtained. Provision is made for magnetic and ceramic pick-ups, radio and tape in and out. A virtual earth input stage forms part of the up-dated circuitry of the Stereo 80 to ensure the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS


Size - 260 x 50 x 20mm (10 1/4 x 2 x 3/4 ins)
 Finish - Black, with white markings
 Inputs - Mag. P.U. 3mV RIAA corrected; Ceramic P.U. 300 mV
 Radio 300 mV; Tape 30 mV
 S/N ratio - 60db
 Frequency range - 20Hz to 15KHz ± 1dB; 10Hz to 25KHz ± 3dB
 Power requirements - 20 to 35 volts
 Outputs - 100mV + AB monitoring for tape
 Controls - Press button for tape, radio and P.U. selection Volume, Bass +12dB to -14dB at 100Hz; Treble +11dB to -12dB at 10KHz

NEW

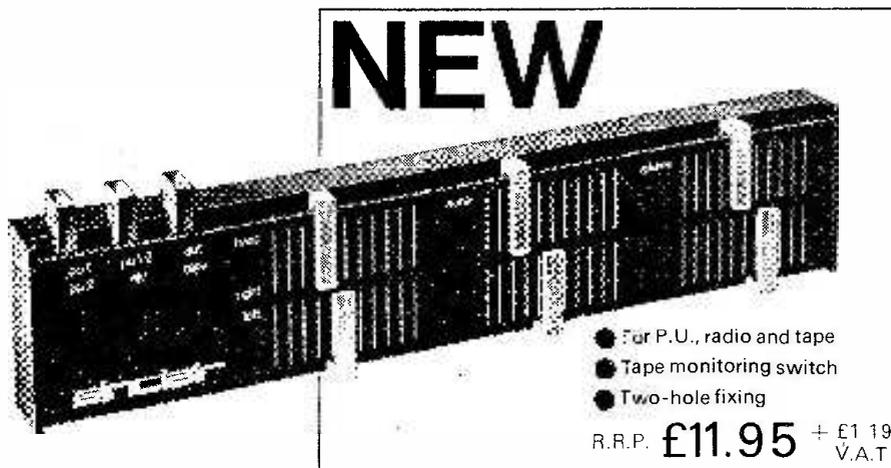

- For P.U., radio and tape
- Tape monitoring switch
- Two-hole fixing

R.R.P. **£11.95** + £1.19 V.A.T.

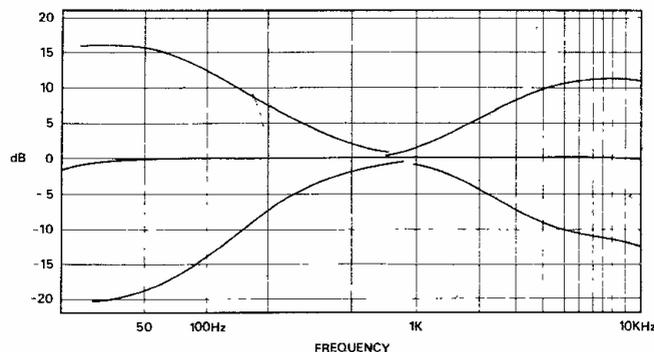


Project 80 FM tuner smaller, more efficient

A truly remarkable tuner in every way - its unbelievably compact size - its original circuitry - its dependable performance - all this in a boldly designed modern case measuring 85 x 50 x 20mm (3 1/2 x 2 x 3/4 ins). Greater adaptability (and possibly financial convenience) results from the tuner and stereo decoder section being made available separately.

TECHNICAL SPECIFICATIONS

Size - 85 x 50 x 20mm (approx. 3 1/2 x 2 x 3/4 ins)
 Tuning range - 87 to 108 MHz
 Detector - I.C. balanced coincidence, for good A.M. rejection
 AFC - Switchable, with thermistor control to prevent from drift
 One 26 transistor I.C.
 Twin dual varicap tuning
 Distortion - 0.3% at 1 KHz for 75KHz deviation
 Ceramic filter in I.F. section
 Aerial impedance - 75 Ω or 240-300 Ω
 Sensitivity - 4 microvolts for 30dB quieting
 Power requirements - 12 to 45 volts

NEW

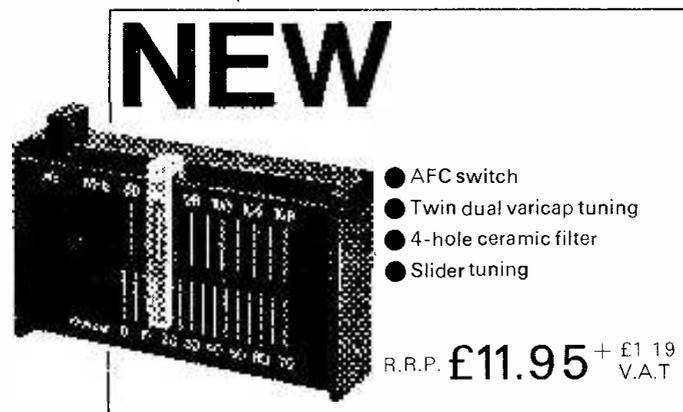

- AFC switch
- Twin dual varicap tuning
- 4-hole ceramic filter
- Slider tuning

R.R.P. **£11.95** + £1.19 V.A.T.

Project 80 stereo decoder

Making the Project 80 decoder separate from the F.M. tuner gives the constructor a wider choice of systems as well as saving money in cases where stereo reception may not be required. This unit gives a 40dB channel separation with an output of 150mV per channel. The gallium arsenide light emitting beacon automatically lights up to show when a stereo transmission is tuned in. Designed essentially as an integral part of Project 80 systems, this multiplex stereo demodulator may be used in many cases with existing single channel frequency modulated tuners to provide stereo reception.

Size - 47 x 50 x 20mm (1 7/8 x 2 x 3/4 ins)
 One 19 transistor I.C.

NEW



- Solid-state stereo indicating beacon
- Readily adaptable for use with other tuners

R.R.P. **£7.45** + 0.74p V.A.T.

new constructional techniques

...and again Sinclair leads the world

- 1962 Micro-miniature power amp small enough to stand on a 10p. piece. Slimline pocket receiver smaller than a 20 cigarette pack
- 1963 Micro-6 receiver, smaller than a matchbox
- 1964 Pocket F.M. receiver, PWM amp.
- 1965 Z.12 power amplifier module; PZ.3 power supply
- 1966 Stereo 25 pre-amp/control unit
- 1967 Micromatic: Q.14 loudspeaker; the first Neoteric
- 1968 IC.10, the first ever integrated circuit for constructors use

- 1969 Q.16 - improved version of Q.14. Systems 2000 and 3000: Project 60 launched
- 1970 IC.12 Project 605
- 1971 Project 60 stereo FM tuner. Z.50 PZ.8
- 1972 Improvements to Project 60 with Z.50 MK.2 and PZ.8 Mk.3 The Executive Calculator: Digital multi-meter Q.30 speaker
- 1973 Cambridge Calculator

PROJECT 80 LAUNCHED

...and next?

Project 80 active filter unit

This efficiently designed unit makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls are applied to each channel thereby making it easier to obtain ideal stereo balance in any kind of indoor environment.

TECHNICAL SPECIFICATIONS

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/8 ins)
 Voltage gain - minus 0.2dB
 Frequency response - 36Hz to 22KHz, controls minimum
 Distortion - at 1KHz - 0.03% using 30V supply
 HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct. slope
 L.F. cut off (rumble) - 28dB at 20Hz, 9dB/oct. slope

Z.40 & Z.60 power amplifiers totally short-circuit proof


Either of these entirely new power amplifiers is intended for use in Project 80 installations although, of course, they are readily adaptable to an even wider range of applications. Both Z.40 and Z.60 incorporate built-in protection against shortcircuiting and risk of damage arising from mis-use is greatly reduced. Comprehensive instructions are supplied with each of the modules.

Z.40 Technical Specifications

Size - 55 x 80 x 20mm
 (2 1/8 x 3 1/8 x 3/8 ins) 9 transistors
 Input sensitivity - 100mV
 Output - 15 watts RMS continuous into 8 Ω (35V), 30 watts music power into 4 Ω (30V)
 Frequency response - 10Hz - 100KHz ± 1dB
 Signal to noise ratio - 64dB
 Distortion - at 10 watts into 8 Ω less than 0.1%
 Power requirements - 1.2-35 volts

Z.60 Technical Specifications


Size - 55 x 98 x 20mm
 (2 1/8 x 3 7/8 x 3/8 ins) 12 transistors
 Input sensitivity - 100-250mV
 Output - 25 watts RMS into 8 Ω (45V), 50 watts music power into 4 Ω (50V)
 Distortion - typically 0.03%
 Frequency response - 10Hz to more than 200KHz ± 1dB
 Signal to noise ratio - better than 70dB
 Built-in protection against transient overload and short circuit
 Load impedance - 4Ω min; max. safe on open circuit

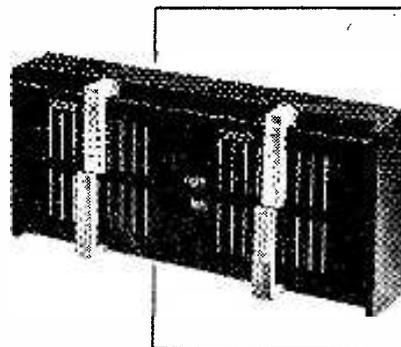

NEW

- For scratch and rumble control
- Transistorised active circuitry

R.R.P. £6.95 + 0.69p V.A.T.

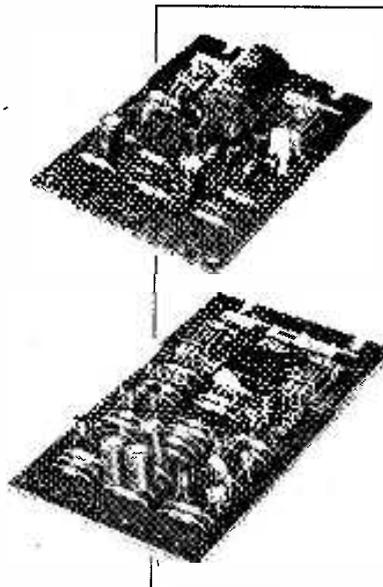

NEW

Z.40

R.R.P. £5.45 + 0.54p V.A.T.

Z.60

R.R.P. £6.95 + 0.69p V.A.T.

Sinclair power supply units PZ.8

the worlds most advanced unit in its class

Stabilised power supply unit. Re-entrant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V

R.R.P. £7.98 + 0.79p V.A.T.
 Without mains transformer
 PZ.5 30V un-stabilised
 R.R.P. £4.98 + 0.49p V.A.T.
 PZ.6 35V, stabilised
 R.R.P. £7.98 + 0.79p V.A.T.




sinclair

Recommended Project 80 applications


System	The Units to use	Units cost
Simple battery record player	Z.40	£5.45 +54p V.A.T.
Mains powered record player	Z.40, PZ.5	£10.43 +£1.04 V.A.T.
30W. RMS continuous sine wave stereo amp.	2 x Z.40s, Stereo 80; PZ.6	£30.83 +£3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amplifier	2 x Z.60s, Stereo 80; PZ.8	£33.83 +£3.38 V.A.T.
Indoor P.A.	Z.60, PZ.8	£14.93 +£1.49 V.A.T.
Car Radio	F.M. tuner, Z.40	£16.40 +£1.64 V.A.T.

From Sinclair the worlds most advanced hi-fi modules

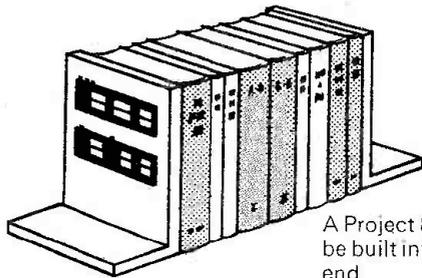
Sinclair Project 80 the ultra-modern non-obtrusive hi-fi



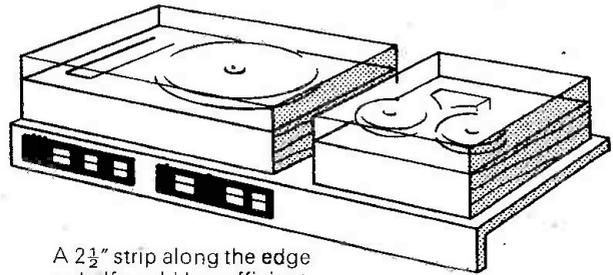
A Project 80 system could be built into a book-shelf end



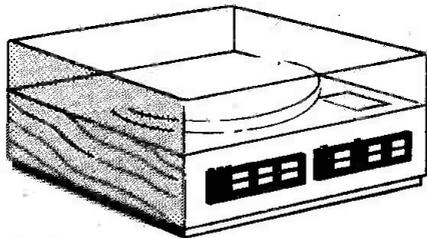
A 2½" strip along the edge a shelf could be sufficient to contain a complete system



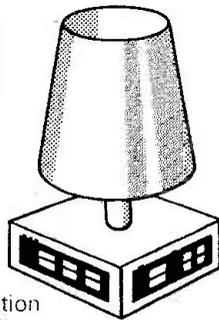
The modules mount very easily onto a playing plinth



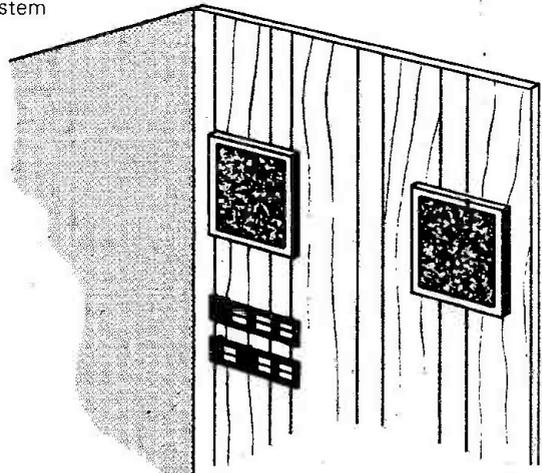
A novel application would be to build around the base of a lampshade



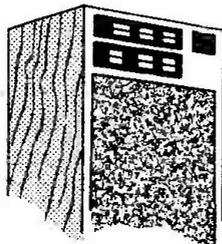Two Sinclair Q.16 loudspeakers suitably positioned together with Project 80 could be mounted on to a false wall.



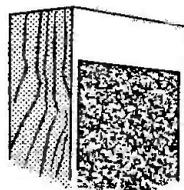Project 80 could be easily mounted onto a loudspeaker cabinet



When you have seen for yourself how fantastically slim and cleverly designed these modules are, further ways will suggest themselves in which they can become a pleasing part of your particular domestic environment.

To **SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ**

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a small charge (typically £1.00) will be made.

sinclair

Sinclair Radionics Ltd.
London Road, St. Ives,
Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64311

PADGETTS RADIO STORE
OLD TOWN HALL, LIVERSEDGE,
YORKS WF15, 6PQ

TEL. HECKMONDWIKE 405285

THE T.V. GRAVEYARD OF THE NORTH, AS SEEN ON T.V.
 CLOSE TO THE MOTORWAY. PLENTY OF FREE PARKING
 SPACE. EST. 1935.

SPECIAL OFFER

1000 PYE 19" 13 Channel T.V. Sets. Brilliant Picture, Extra Slim
 Bench Tested. Sold with Money Back Guarantee. Hurry, have a
 second set at the price of £5.50. Plus carr. and ins. £1.80.

Students Wireless Procedure Training Set comprising mike,
 single LR phone and connector in small wood box, 80p post paid.

COMPLETE UNTESTED T.V. SETS. With back and all valves,
 BBC 1 and ITV 17" 90° Tubes £1.10, 17" 110° Tube £2.20, 19"
 £3.30. Carr. and ins. on any set £1.75.

Fifty T.V. Valves. Good assortment not-tested 50p. Post-Paid
 ½ Cwt. of ex Government Scrap Resistors, Panels and Gears, etc.
 30p. Carr. 80p.

SPEAKERS REMOVED FROM T.V. SETS, all 3 Ohm 2½ Watts.
 7 x 4", 6 x 4", 8 x 2½". All at 27p. Post and packing 12p.

TOP QUALITY TAPE. Reel to Reel 5" ST, 44p 5" LP 55p, 5½" LP
 60p, 7" ST 66p, 7" LP 80p, Cassette Types C60 35p, C90 45p.
 C120 55p. Post on any tape 12p.

Jap Earpiece 8 Ohm Magnetic 3-5 12p.

Ex Equipment Valves all tested on our Mullard Valve Tester
 before despatch. 3 months guarantee on all valves. Single Valves
 Post 3p, over Post Free.

ARP12	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EB80	10p	PCL82	14p	UI91	20p
EBF89	15p	PCL83	15p	6BV7	12p
ECC81	12p	PCL84	15p	6U4	20p
ECC82	12p	PL82	10p	6F23	15p
EF91	5p	PL83	10p	20P1	12p
EY86	22p	PL36	17p	20P3	12p
EF183	20p	PY81	10p	30F5	20p
EF184	20p	PY801	17p	30FL1	
		PY800	17p		

ABOVE PRICES INCLUDE V.A.T.

LASKYS 1974 CATALOGUE

FREE

Send this coupon today for your Free
 copy of Lasky's Famous Hi-Fi, Audio
 and Electronics Catalogue.


To LASKYS RADIO, AUDIOTRONIC HOUSE
 THE HYDE, LONDON, NW9 6JJ

Please send a copy of LASKYS 1974 CATALOGUE

NAME

ADDRESS

BI-PRE-PAK AUDIO BARGAINS

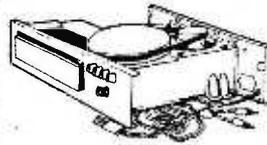


**8 TRACK
 ONLY £11**

incl. P. & P. and V.A.T.

The latest B.S.R. 8 Track cartridge Replay Deck.
Ready to install in your Hi-Fi Stereo System.
 This unit comes complete with Hi Gain Stereo Pre-Amplifier,
 4-Programme indicator Lamps, Track Selector Switch, all
 leads and plugs, etc. for 230 volt A.C. mains operation.

3 W.R.M.S.I.C. AMP

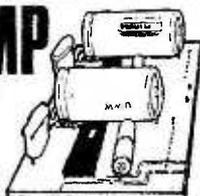
only £1.65 incl. P. & P. and VAT
 Order Code I.C.A. 1



on P.C. Board with all components
 or 2 on one board for £2.85

Order Code I.C.A.1/S
 These amps. are supplied with a free booklet
 on connecting up, specifications and easy to
 build projects using the I.C.A.1

5W & 10W AMPS

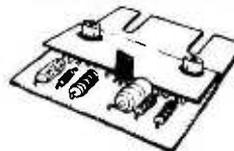

5W ONLY £1.98
10W ONLY £2.49

inc. P. & P. and VAT

These matchbox size amplifiers have an exceptionally
 good tone and quality for the price. They are only 2½" x 1½".
 The 5W amp will run from a 12V car battery making it very
 suitable for portable voice reinforcement such as public
 functions. Two amplifiers are ideal for stereo. Complete
 connection details and treble, bass, volume and balance
 control circuit diagrams are supplied with each unit.
 Discounts are available for quantity orders. More details on
 request. Cheapest in the UK. Built and tested.

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in
 stereo only, will fit .15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain
 crystal or ceramic pick-up cartridges. **£1.21**

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic
 pick-up cartridges. **£1.69**

Stereo Tone Control (STC). This unit is an active tone
 control board and when used with the right potentiometers
 will give bass and treble boost and cut. **£1.21**

Instruction leaflet supplied with all units. Post and
 packing and VAT included in prices.

I enclose £..... for..... 8 Tracks/.....
 3W Amps/..... 5W Amps/..... 10W Amps/.....
 Stereo Pre-Amps 1 Stereo Pre-Amps 2
 Stereo Tone Controls
 (Please insert quantities and delete those not applicable)
 Name
 Address

BI-PRE-PAK Dept. D, 222/224 West Road,
 Westcliffe-on-Sea, Essex SS0 9DF
 Co. Regn. No. 820919 Telephone: Southend (0702) 46344

Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Aerials

BAINES HIGH FREQUENCY AERIALS

Postage paid on aerials
UHF Multi beams and Parabeams
PBM 12 £3.35, PBM 18 £4.30, MBM 30 £4.40, MBM 46 £6.90, MBM 70 £12.10, Log periodic £6.00.
VHF Stereobeams
SBM 1 £2.20, SBM 2 £2.95, SBM 3 £4.40, SBM 4 £4.80, SBM 6 £7.25; Stacking kit £2.20; Rotator £26.52; Loft kit 44p; 75/300 Balun £1.60. Masthead VHF/UHF amplifiers £8.75 Setback £4. Accessories: A large s.a.e. please, Coax 4p and 8p.
11 Dale Cres., Tupton, Chesterfield S42 6DR
Tel: 863755

F.M./VHF. Stereo Radio Aerials. Belling-Lee. 10ft type £1. Roof type £2. Post 25p. 90 Ewhurst Road, Crawley, 23885. Sussex.

GENUINE FULL SIZE
18 element TV aerial
as used by leading TV companies

FOR ONLY

£2.20
incl. VAT

+ 35p carr



ITV, BBC1 & 2B/W & Colour Guaranteed Perfect Pictures. Save ££s. We supply this genuine U.H.F. aerial for only £2.20. can be fitted outside or inside. Quality made technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions advice. Money Back Refund. Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters. SEND DIRECT TO DEPT. PW10
219 Mansfield Rd. Nottingham.

IMPERIAL TRADING (AERIALS) LTD.
the quality Aerial Specialists


Situations Vacant

here's the opportunity of a lifetime..... become a successful computer engineer

Can you meet the challenge of working in the fastest growing service company in the U.K.?

As a result of further expansion, Computer Field Maintenance, Britain's largest and most successful independent maintenance company, have a variety of positions to offer in London and the Home Counties. Opportunities exist at all levels, and we would like to hear from:

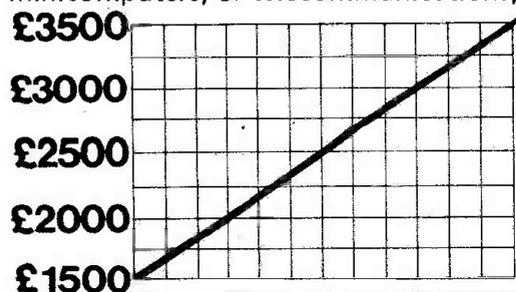Engineers with experience of large systems, minicomputers, or telecommunications,



Technicians with experience of computer peripherals, flexowriters, or teletypes, and **Electronic/Electromechanical Engineers** seeking a career in computer maintenance: full product training will be given.

We offer: Generous salaries, bonus, non contributory pension, attractive car scheme and opportunities to work on a variety of equipments, providing a secure future.

Brief details of your career to date and your preferred location, should be sent to,

The Personnel Officer
Computer Field Maintenance Limited
99 Bancroft, Hitchin, Hertfordshire
Telephone - Hitchin (0462) 51511



a member of the Computer World Trade Group of Companies

COMPUTER ENGINEERING

We require additional Electronic and Electro-Mechanical Engineers, to be involved in the maintenance of medium to large scale digital computing systems.

Training programmes will be arranged for successful applicants, 21 years of age and over, who have a good technical background to ONC/HNC level, City and Guilds or Radio/Radar experience in the Forces.

After training, and in appropriate circumstances, shift allowances will enhance the competitive basic salary, as will our twice yearly bonus.

A contributory pension plan includes generous life insurance.

Opportunities also exist for more junior trainees aged 18 and over who should have a good standard of education, an aptitude for, and an interest in, mechanics, electronics and computers.

Please write quoting ref. P.W. for an application form to:—

E. J. Young, NCR, 1000 North Circular Road, London NW2 7TL

PLAN YOUR FUTURE WITH **NCR**

MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London
Computer Operators
Training Centre

S60, Oxford House
9-15, Oxford Street, W.1.
Telephone: 01-734 2874

Ladders

LADDERS 'Special Offer' Unvarnished Triples. 9ft 7in closed—24ft 7in extended £13.20 delivered. Home Sales Ladder Centre (WLS2) Haldane (North), Halesfield (1) Telford, Shropshire. Tel: 0952 586644.

Service Sheets

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

Books and Publications

RadioBOOKS

Handbk of Transistor Equip and Substitutes	45p
Handbook of Tested Transistor Circuits	45p
Rad & Electr Colour Codes and Data Chart	20p
Hi-Fi, PA & Disco Amplifier Design H'bk	80p
Boys Bk of Crystal Sets and Simple Circuits	23p
Electronic Novelties for the Motorist	55p
Radio Servicing for Amateurs	25p
High Fidelity Loudspeaker Enclosures	45p
Practical Tape Recording Enclosures	35p
Practical Stereo Handbook	35p
Practical Radio Inside Out	45p
Transistor Circuits Manual No. 1	20p
Transistor Circuits Manual No. 2	20p
Coil Design and Construction Manual	35p
Radio TV and Electronics Data Book	30p
Transis Circuits for Radio Controlled Models	45p
Pract Transistor Audio Amplifiers, Book 1	25p
Transistor Test Equip and Servicing Manual	30p
Handbook of Simple Transistor Circuits	40p
Modern Transistor Circuits for Beginners	45p
Sound and Loudspeaker Manual	55p
Resistor Colour Code Disc Calculator	15p
Manual Transistor Audio Amplifiers	45p
Practical Car Radio Handbook	35p
Radio TV and Industrial Tube & Valve Equip.	25p
Transistor Circuits Manual No. 2	20p
Television Servicing Vol. 1	95p
Television Servicing Vol. 2	95p
Television Servicing Vol. 3	70p
Television Servicing Vol. 4	95p
Using an Oscilloscope	80p
Servicing Transistor Radio Receivers	85p
Television Timebase Circuits	£1.10p
Getting Started with Transistors	£1.30p

All prices include postage & packing
FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

DENCO CLACTON LIMITED

355-7-9 Old Road

Clacton-on-Sea, Essex

Catalogue 20p post paid

S.A.E. all enquiries

WORLD RADIO TV HANDBOOK 1974 (published December), £3.15. Delivered direct from Denmark if ordered before publication. How to Listen to the World, £2. Postage and VAT included. Every order acknowledged immediately. David McGarva, PO Box 114, Edinburgh EH1 1HP.

SW-BC LOG with time indication, post free. Pay £0.80 at any post office to National Giro account 651-4154. SVERIGES RADIOKLUBB, UK treasurer.

SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 25p
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS
RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

NEW BOOKS & PUBLICATIONS

	PRICE
ELECTRONICS IN MUSIC by F.C.Judd. 169 pp. Circuit designs and operation.	£3.15
RAPID SERVICING OF TRANSISTOR EQUIPMENT 2nd Edition by G.J.King. 184 pp.	£1.90
THE HI-FI & TAPE RECORDER HANDBOOK by G.J.King. 304 pp.	£2.00
HOW TO READ SCHEMATIC DIAGRAMS by D.E.Herrington. 160 pp.	£1.20
MAKING & REPAIRING TRANSISTOR RADIOS by W.Oliver. 126 pp.	£1.20
20 Solid State Projects For The Car and Garage by R.M.Marston. 124 pp.	£1.80
20 Solid State Projects For The Home by R.M.Marston. 114 pp.	£1.60
50 PHOTOELECTRIC CIRCUITS & SYSTEMS by P.S.Smith. 88 pp.	£2.30
110 Semiconductor Projects For The Home Constructor by R.M.Marston. 134 pp.	£1.80
110 Integrated Circuit Projects For The Home Constructor by R.M.Marston. 136 pp.	£1.80
HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER by P.J.Guy. 142 pp.	£1.50
CREATIVE TAPE RECORDING by Vivian Capel. 183 pp. Shows advanced techniques.	£3.50
TAPE RECORDERS by H.W.Hellier. 239 pp. A must for the enthusiast	£2.25
UNDERSTANDING ELECTRONIC CIRCUITS by Ian R.Sinclair. 204 pp. 127 illus.	£3.50
UNDERSTANDING ELECTRONIC COMPONENTS by Ian R.Sinclair. 218 pp. 130 illus.	£3.50
FAULT LOCATION EXERCISES in Radio & TV Servicing by K.J.Bohman. Vol.1.	£0.80
FAULT LOCATION EXERCISES in Radio & TV Servicing by K.J.Bohman. Vol.2.	£1.35
WORLD RADIO TV HANDBOOK 1972. 26th Edition. 384 pp. Special reduced offer	£1.00
WORLD RADIO TV HANDBOOK 1973. 27th Edition. 400 pp.	£3.00
COMPUTER SCIENCE by P.Harvey. A general introduction and principles.	£2.00
RADIO TECHNICIANS BENCH MANUAL by H.W.Hellier. 214 pp. 131 illustrations	£3.00
AUDIO TECHNICIANS BENCH MANUAL by John Earl. 182 pp. 114 illustrations	£3.00
HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES by B.B.Babani	£0.40
SERVICING WITH THE OSCILLOSCOPE by G.J.King. 176 pp. Illustrated.	£1.80
BEGINNERS GUIDE TO RADIO by G.J.King. 7th Edition. 204 pp. Illustrated	£1.00
NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good prices paid.	

Please add 10% for Postage and Packing on all books. Send large S.A.E. for FREE booklists.
BELL'S TELEVISION SERVICES
ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

DIRECT FROM MANUFACTURER—a comprehensive catalogue of UHF & VHF/FM aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send 3p stamp to CLAYDEW ENTERPRISES (PW), 261 Hardess Street, London S.E.24.

"SHORTWAVE VOICES OF THE WORLD," £1.70, postage and VAT 11p. "SWL Address Book," £1.55+11p. "Confidential Frequency List," £1.70+11p. "Guide to International Medium Wave Broadcasts," 20p+4p. Books and full details from any bookshop, or in difficulty write to: David McGarva, PO Box 114, Edinburgh EH1 1HP.

Wanted

TOP PRICES PAID for NEW VALVES and TRANSISTORS
popular T.V. and Radio types.
KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

EARLY WIRELESS LITERATURE before 1934. Johnson Raffles, Haverbreaks, Lancaster. Telephone 67770 evenings.

NEWNES RADIO and TV Servicing Books wanted. From 1960-1966, £2 paid per copy by return post. Any quantity bought. Bell's Television Services, Albert Place, Harrogate, Yorks. Telephone 0423 86844.

COLLECTOR requires old magazines, components and valves. Condition and price to Box 108.

OLD TYPE valve car radios of every description and age, also spares for same. 18 Brook Road, Mangotsfield, Bristol, BS17 3DY. Tel. Bristol 565238 evenings.

For Sale

TV LINE OUTPUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycombe Rd., Richmond, Surrey, TW9 2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

FOR SALE: 52 Practical Wireless 1958/1971; 74 Practical Electronics 1964/1970; Television 1962/1973 complete; Radio Constructor 1962/1973 complete; Wireless World 1962/1972 complete, ready for binding. Ridley, 17 Acorn Crescent, Larbert, Stirlingshire.

SPARES for Philips Cassette recorders, and some for Pye and Stella recorders. SAE for enquiries. In complete lists. Harvey, 94 Derby Lane, Liverpool, L13 3DW.

Receivers and Components

PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.
0.47µF: ±5% 80p; ±2% 40p; ±1% 50p
1.0µF: ±5% 40p; ±2% 50p; ±1% 80p
2.2µF: ±5% 50p; ±2% 80p; ±1% 75p
4.7µF: ±5% 70p; ±2% 90p; ±1% £1.15
6.8µF: ±5% 95p; ±2% £1.15; ±1% £1.50
10µF: ±5% £1.10; ±2% £1.40; ±1% £1.80
15µF: ±5% £1.80; ±2% £2.10; ±1% £2.70

TANTALUM BEAD CAPACITORS—Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 8p each; 6 for 45p; 14 for 95p. Special pack 6 off each value (78 capacitors) £4.50.

NEW! TRANSISTORS. BC107, BC108, BC109, All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178—35p each or 3 for 95p.

POPULAR DIODES. IN914, 6p each; 8 for 45p; 18 for 90p IN916, 8p each; 6 for 45p; 14 for 90p; IS44, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5 mA. All new and marked. Price 7p each; 6 for 39p; 14 for 84p. Special offer 6 off each voltage (66 zeners). £3/65.

RESISTORS. Carbon film 5%. 1W at 40°C 1/2W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special pack—10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS. 0.1µF, size 1 1/4in x 1/2in, 25p; 0.25µF, size 1 1/4in x 1/2in, 30p; 0.47 and 0.5µF, size 1 1/4in x 1/2in, 35p; 1.0µF, size 2in x 1/2in, 45p; 2.0µF, size 2in x 1/2in, 75p each.

SILICON PLASTIC RECTIFIERS 1.5 Amp Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

7p post and packing on all orders below £5. Please add 10% VAT to all orders.

MARCO TRADING
Dept. W1, The Maltings, Station Road
Wem, Shropshire

GUARANTEED SEMICONDUCTORS FAST SERVICE . LOW PRICES

AC107	16p	2N706	10p	ZENER DIODES
AC126	13p	2N930	20p	400mW 5%
AC127	13p	2N1131	22p	3.3 to 33 volts
AC128	13p	2N1132	22p	10p each
BC107	9p	2N1711	20p	1 watt 5%
BC108	9p	2N2904	18p	6.8 to 200 volts
AF114	14p	2N2904A	23p	15p each
AF115	14p	2N2905	23p	
AF116	14p	2N3053	15p	
AF117	14p	2N3054	50p	
BCY70	15p	2N3055	88p	
BCY71	20p	2N3702	9p	RECTIFIERS
BCY72	15p	2N3703	9p	P.I.V. 1 AMP
BFX84	24p	2N3704	9p	50 IN4001 4 1/2p
BFX85	25p	2N3705	9p	100 IN4002 4 1/2p
BFX86	21p	2N3706	9p	200 IN4003 5p
BFX87	24p	2N3707	9p	400 IN4004 6p
BFX88	20p	2N3708	8p	600 IN4005 7p
B8X20	15p	2N3709	9p	800 IN4006 8p
				1000 IN4007 9p

CASH W.O. PLUS P.P. 10p TO ROSLESS SERVICES
PARNDON HALL . HAMSTEL ROAD
HARLOW . ESSEX

BATTERY ELIMINATOR KITS. Our well-known Mini Mains Pack Kits now complete with drilled insulated base 32 x 55mm. Fits into space of most large transistor batteries. Easy wiring instructions. Safe, silent mains transformer, silicon rects, smoothing capacitor, all top grade. For any ONE of these voltages (state which): 3V, 300mA max.; 6V, 180mA; 9V, 120mA; 18V, 60mA. £1.50 VAT included. By mail only, UK post 5p. Amatronix Ltd., 396 Selsdon Rd., South Croydon, Surrey CR2 0DE.

EX-COMPUTER EQUIPMENT: Wide selection digital linear and power components. Large S.A.E. Lists, T. J. Oxborrow, "Wimborne", Walton Road, Kirby-le-Soken, Frinton-on-Sea, Essex.

TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

£9-80 **£13-75**

MINIKIT'S ELECTRONICS,
35a LANGLEY DRIVE, WANSTEAD
LONDON, E11 2LN (Mail order only)

TEXAN AMPLIFIER



Pack		
1.	P.C. Board	£2.00 p.p. 15p
2.	Chassis	3.00 " 25p
3.	Front Panel	1.25 " 15p
4.	Resistors	.80 " 15p
5.	Capacitors	2.90 " 15p
6.	Semi Conductors	8.00 " 15p
7.	Transformer	5.95 " 25p
8.	Sundries	2.50 " 15p
9.	Cables	.40 " 15p
10.	Instructions	.30 " 15p
11.	100K/100K control	.30 " 15p
12.	Case	2.75 " 25p

VAT EXTRA

TELERADIO ELECTRONICS,
325 FORE ST., LONDON, N.9.
Tel. 01-807 3719

Send 4p for catalogue of Hi Fi Kits including the Quadraphonic System as in Practical Electronics.

TAPE HEADS

Send stamp for lists.
R.D.I. Ltd.
Chilton Works,
Garden Rd.,
Richmond,
Surrey,
TW9 4NS

For valve and transistorized recorders from £2 ea.

NEW MODEL V.H.F. KIT MK2
Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in Jack socket for use with earphones or amplifier.
Only £3.50 +p.&p 15p U.K. only.
Illustrated catalogue of selected kits and components, 20p inc. VAT. P&P free.

ALL PRICES PLUS 10% VAT
Galleon Trading Co.,
12, Burrs Way,
Corringham,
Stanford-Le-Hope,
Essex. SS17 8DE

INTEGRATED CIRCUIT and FET modules for construction of low-cost receivers, converters, pre-selectors, etc. SAE details.—P. R. Colledge, Glen Tor, Torrington, Devon.

VEROBOARD	0.1	0.15
2 1/2 x 5	26p	25p
2 1/2 x 3 1/2	23p	18p
3 1/2 x 5	30p	32p
3 1/2 x 3 1/2	26p	25p
4 1/2 x 3 1/2	40p	40p
Track cutter	40p	
Toggle switch, 250V 1.5A SPST	18p	DPDT 25p
Slide switch, DPDT miniature or standard	11p	
Push to make, non locking, SPST	12p	

NEK ELECTRONICS (W1)
28, Carnegie Road, St. Albans, Herts.
Please add 10p P. & P. Mail order only.

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10mfd.—4p, 22, 47—4 1/2 p. (50V—5p.) 100—5 1/2 p. (50V—7p.) 220—6p. (50V—9p.). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2p. 0.04, 0.05—3p. 0.068, 0.1—3 1/2 p. Polystyrene 63V. E12 series 10 pf.—1,000 pf.—2p. 1,200 pf.—10,000 pf.—3p. Miniature Highstab resistors, 5%, E12 series—Carbon Film 1/3 W 10—10MΩ (10% over 1 Meg.) Metal Film 1/8 W 10Ω—2.2MΩ and 1W. 27Ω—10MΩ all 3/4 p each. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

TRANSISTOR AMPLIFIERS 50p Vol/Tone Pre-Amps 30p. LW-MW Mixer-osc panels 50p all with circuits. Record player cabinets £3. Radio cabinets, suitable ext speakers, colours blue, brown, yellow. 50p Mains droppers 76Ω + 66Ω + 66Ω + 25Ω + 24Ω + 26Ω 30p. Archer, 9 Pine Grove, Maidstone, Kent.

DESOLDERWICK
SOLDER-ABSORBING WICK
Approx. 1 cm. completely desolders a P.C.B. joint. Use with any 20-40W soldering iron. 30 cm. Pack 26p inc. P/P, etc. Multipack. Four lengths of wick in various widths. 80p inc. P/P, etc.
ORIENTATION LIMITED
Coverack, Cornwall

MANUFACTURERS Surplus components. Mixed packs all post free. Resistors 20p. Capacitors 60p. Discs 40p. Hardware 25p. Relays 60p. Four digit magnetic counters 20p. Ferric Chloride LB 52p. Samples and lists 20p stamps. Derwent Radio, Scarborough.

ELEVEN BAND RADIO. SW 1-4. Marine. LW. MW. FM. PSB (76-86). Aircraft (108-136). PSB (148-174). Batt/Mains. BFO. Fine Tune, Squelch. Output 1.3W. £58. SAE full lists, multi band radios, also Grundig Bargains, Satellit, 12 band, £118. Langtons Radio, High Street, ROCESTER, Staffs. 088-923 388.

EX-GOVT. Communications and test equipment. Ancient and modern valves. Components. Trio equipment. Mail Order. S.A.E. Lists. Transelec Services, 5 Swan St., Torquay, S. Devon. Tel 22740.

OFFERS INVITED. Capacitors, approximately 7,000 1 x 9uF ±20% and 2,500 4 x 1uF ±20%. Unused, approx. size 3 1/2 in x 1 1/8 in x 1/2 in 100 V.D.C. Samples on request. Other components available. Enquiries to Aband Ltd., Room 20B, Waterloo Buildings, 66 Hanover Street, Liverpool 1.

5-N-CHANNEL FETs 3819E—£1
Full specification devices complete with data and circuit details for building voltmeter, timer, ohmmeter, etc.
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.
REDHAWK SALES LIMITED
45 Station Road, Gerrards Cross, Bucks.
Mail Order only

TUNBRIDGE WELLS, Components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 51803.

Miscellaneous

UNIQUE HI-FI SPEAKER SYSTEM

24 WATTS PEAK!

Beautiful bookshelf units in mahogany type finish. Employs infinite baffle enclosure with dual cone 8 ohm drive unit. Brand new with 6' leads.

£9.80 Per Pair P&P 60p

GREGG Electronics
PW3, 24 Cranbourn Street
Leicester Sq. London WC2

STABILISED 6.7.5 & 9V. FROM SINGLE UNIT
In-Car Entertainment.
Battery operated cassette recorders, radios etc., powered by 12v car battery by means of ingenious electronic adaptor—at virtually no cost. One lead included. Only £3.99 inc. VAT + 12p (p.p.). Also Mains Battery Eliminator £3.00. Lead (optional) 60p. State type of plug. Partics.:—
OMNIA PRODUCTS, 25 Wilbury Gdns., Hove, Sussex.

BA NUTS BOLTS and WASHERS	Per 100
Assrt. length bolts, shake-proof washers.	Size Nuts Bolts W/rs 0 53p 75p 29p 2 46p 53p 22p 4 35p 46p 18p 6 29p 35p 18p
SELF TAPPING SCREWS	PVC 100 GROM-METS
Box of 100 Assrt. 29p	Box of 100 Assrt. 51p
	3/4" 9/32" Hole Size 44p
5 1/2" SIDE CUTTERS	5" PLIERS
59p	Insulated Handle 59p

Post free over £2 Orders under £21 All prices add p & p 15p include VAT
SILHILL PRODUCTS, Dept. WPI 226 Mary St., Birmingham B12 9RJ 021-440 3600.

A.L.S. PRESENTS OUR E.C.100 WATT HI-FI AMPLIFIER
Ready drilled P.C.B. with full instructions only £2—plus 10p post. We also supply: Service Sheets, Manuals, Books etc. See our Main Advertisement in "TELEVISION" or send S.A.E. for details.

10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA (B)

AMTRON KITS. Your Devon Stockist. E. Wenmouth, 50 South Street, Exeter 76058.

Darned Electronic Wizardry

by Dewtron (VAT extra.)

Famous kits, e.g. waa-waa complete kit £2.95; Fuzz kit £5.50 auto rhythm modules P & P 20p min. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

GLASS FIBRE P.C. BOARD. Large supplies available in single sided one ounce copper 2p per 3 sq. inches (under 1 foot). 75p per sq. ft. (over 1 foot). In double sided one ounce copper 1p per sq. inch (under 1 ft.), £1 per sq. ft. (over 1 foot). Please add 10p per sq. foot postage and packing. We can cut to your size at 1p per cut. Solid State Lighting, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

Build your next project in a BEC (Book end chassis)

New improved with alloy trim on bottom of all cabinets. Now in easy to assemble kits.

GB3 (Illustrated) . . . 14" x 9" x 4" . . . £4.00 P & P 45p.
Other sizes. SAE with enquiries
H. M. ELECTRONICS 275a, Fulwood Rd, Sheffield S10 3BD

"HIGH GAIN AERIAL"

SPECIALLY DESIGNED FOR USE WHERE SPACE IS LIMITED
Alloy caged. Ideal for S.W. Enthusiasts Beam rotary reception

UNIQUE DESIGN Complete Kit, Base, mast, aerial, charts Fabulous Value £3.50 PP Paid

ALL WAVE

Also included in this Kit, CHARTS of Frequency Allocations, International call signs, World time, Codes, Map, etc.

TUBULAR METAL PRODUCTS
7 LOWESMOOR TERRACE, WORCESTER ENGLAND

Versatile **10 in ONE**

MIN-LAB Comprising:

- AC and DC Voltmeter ● Audio Generator
- Ohm Meter ● Resistance Substitution
- Capacitance Substitution ● DC Ammeter
- Battery Supply ● RF Signal Generator
- RF Field Strength Indicator.

This new, unique instrument combines all you need for testing. Money back if not satisfied. Includes VAT & p. & p.
Cash with order or send s.a.e. for illustrated data sheet to:
J. H. ASSOCIATES LTD. (DEPT. PW)
Cricketfield Lane, Bishop's Stortford, Herts.

£11.95

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Big 4-inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send **£1.35** for your Maxi-Volt now!
 - ★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send **£5.90** for yours now!
 - ★ Psychedelic. **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send **£2.20** now! (all prices include V.A.T., packing & postage.)
- Send remittance to:
BOFFIN PROJECTS,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY
 (Mail order only)
 Or for more details, send 15p for lists, plus free design project sheet.

BUILD IT in a **DEWBOX** quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

BURGLAR AND FIRE ALARMS. Amazing new kit £23.50. Full range of kits and equipment from Castle Alarms, P.O. Box No. 6, Windsor, Berks.

EXPERIMENTERS! Hundreds of unusual items cheap. 1974 catalogue 5½p. **GRIMSBY ELECTRONICS**, 64 Tennyson Road, Cleethorpes, Lincs. (Mail Order Only.)

AIRCRAFT TYPE position indicators for transmission or angular displacement 75p. Also Ex-equipment components. S.A.E. for details. Dunn, 16 Raven Road, Timperley, Cheshire.

ELECTRONIC IGNITION. Complete Set of parts and circuit diagram, only £6.75 plus 25p. P&P. State Pos. or Neg. Earth. Dept. PW, 32 Station Road, Belmont, Surrey.

AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF RADIO

VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30:—
 ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, PC86, PC88.

19" UHF/VHF (BBC2) £6.00

Thorn-850 or Pye, with set of spare valves. Carriage £2.00 (Untested).

100 MIXED RESISTORS—65p

± to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Ceramic Capacitors from 1PF to 8200PF (our choice) 65p.

BARGAIN PARTS


Transistor UHF Tuners—£2.00, 500K-ohms V/C with Switch—20p. 50 mixed Tuner Valves—£2.25. Brand New Transistors BF173, BC171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order Money back guarantee. S.A.E. for leaflets.

ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

MORE RANGES FOR LESS MONEY!

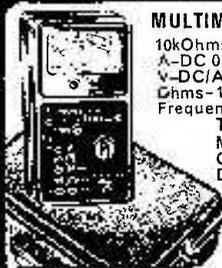

MULTIMETER AC-DC Type U-437
 10kOhms/V 2.5% Precision
 A-DC 0-1-1A - 5 Ranges
 V-DC/AC 2.5 to 1000 V - 6 Ranges
 Ohms - 100 to 1 MegOhm - 4 Ranges.
 Frequency: 45-40kHz - 2 Ranges.

TAUT SUSPENSIONS MOVEMENT.


Complete with steel case
 Dimensions without case:
 212 x 118 x 75mm

£4.95

AC/DC Multimeter type U4324

A-DC 0-05-3A - 6 Ranges.
 A-AC 0-3-3A - 5 Ranges.
 V-DC 0-6-1200 V - 9 Ranges.
 V-AC 3-900 V - 8 Ranges.
 Frequency: 45 to 20kHz-2 Ranges.
 Resistance: 500 Ohm to 5 MOhm-5 Ranges. Decibel: -10 to +12dB - 2 Ranges. Accuracy ± 2.5%.
 Dimensions: 167 x 98 x 63 mm.

Only **£8.00**

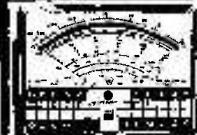

SUPERTESTER 680 R ICE

10 Fields - 80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC - Temperature -50C to +200C - Magnetic fields up to 15 KGauss - Phase indicator - EHT 25kV Electronic Volt Ohm - meter Transistor Diode Tester etc.

Dimensions: 128 x 95 x 32 mm-300 grams 20kOhm/V Accuracy 1% DC Ask for free catalogue

£18.50

Add 10% VAT to all items + 25p P&P

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB Tel: 837 7781

LOW COST I.C. Mounting. I.C. pin sockets in lengths of 100 for 60p (p&p 5p). Quantity rates. S.A.E. details and sample. **GASKELL**, Oak Lodge, Tansley, Derbyshire.

Another DUO-SOUND Bargain

TELETON NM33

MAGNETIC CARTRIDGE ONLY £1.50 P.&P. 15p

Complete with Diamond Stylus
DUO-SOUND 134 Church Road, Manor Park, London, E12 6HL



MINICOMP FOR FASCINATING PARTY GAMES

SPECIAL CHRISTMAS OFFER

Built and Guaranteed Units: **£19.87**
 For orders received on or before 31st January, 1974. Usual Price: **£24.87**

As described in R & E, Nov. '73

MINICOMP 100: The Miniaturised ERNIE

Includes 4 selections of purely RANDOM NUMBERS.

1-6 DICE

0-36 ROULETTE

0-99 BINGO & ALL NUMBER GAMES

0-59 POOLS DRAWS



OR: Invent your own Games and have your own Party Rules! Case approx. 7" x 5" x 3". Elegant nylon coating in sky-blue or grey and brushed Aluminium panel.

Brilliant NEON numbers. Mains operated. Terms: C.W.O. MAIL ORDER ONLY

MICROELECTRONICS MICRO

51, Mexfield Road, London SW15 2RG 01-870-2368

HARDWARE SUPPLIES. Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers etc. Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes etc. 7p for list. **Ramar Constructors Services**, 29 Shelbourne Road, Stratford on Avon, Warwks. CV37 9JP.

Christmas Gifts

IDEAL XMAS PRESENTS

(Please send early)


"Globe-King"

V.H.F. & SHORT WAVE KITS

Precision standard, low cost valve and transistor Kits 10-350 m. V.H.F. 80-180 MHz. "Easy-Build" diagrams and simplified instructions. For free literature send S.A.E. to sole manufacturers. (Overseas: Int. Reply Coupon).

JOHNSONS (RADIO) Est. 1943
 Shaw Street, Worcester, WR1 3QQ
 Tel. 24864 A JOHN BANNER CO.

SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER

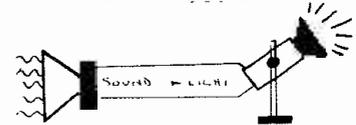

WITH LIGHT DIMMER

Max. load 2kW. at 250v, A.C.

Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. Price **£7.90 inc. VAT**

EXTRA FACILITIES. Push-button for Manual Pulsing 25p extra. Photocell for turning on the lights as the ambient light decreases, 75p extra.

3 CHANNEL FILTER UNIT

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested. Price **£3.50 inc. VAT**

OIL WHEEL PROJECTOR

Build your own using our



MULTI-COLOURED OIL WHEEL AND MOTOR KIT

Suitable for mounting on virtually all Slide Projectors.

Kit contains:

- ★ 6" dia. or 4" dia. OIL WHEEL (please state size required when ordering).
 - ★ Suitable Miniature mains motor.
 - ★ Full instructions.
- For Professional Discotheque use or home enjoyment. Price **£7.15 inc. VAT**

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

Pack No.

- 1 500 Carbon resistors, ½, 1, 2 watt.
- 2 100 Electrolytic Condensers.
- 3 250 Ceramic, Polystyrene, Silver Mica etc. condensers.
- 4 250 Polyester, Polycarbonate, Paper, etc. condensers.
- 5 25 Potentiometers, assorted.
- 6 250 High-stab, 1%, 2%, 5% resistors,
- 7 50 Assorted Tagstrips.
- 8 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
- 9 25 Assorted switches, rotary, lever, micro, toggle, etc.
- 10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED.

£1 + 25p p.p. per pack, £5 for 5 packs p/fee

C. T. ELECTRONICS

Mail Order, Retail Shop, Components—
 267 Acton Lane, LONDON, W4 5DG 01-994-6275

Warehouse, Test Equipment, Surplus Goods—
 20-24 Beaumont Road, LONDON, W4


Audio Accessory Shop, Components—
 17 Turnham Green Terrace, LONDON, W4

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT OPEN 6 DAYS A WEEK. 9.00 a.m.-6.00 p.m.



TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD. DEPT. W 163 MITCHAM ROAD, LONDON SW17 9PG 01-672 3137/9080

TUAC POWER MODULES

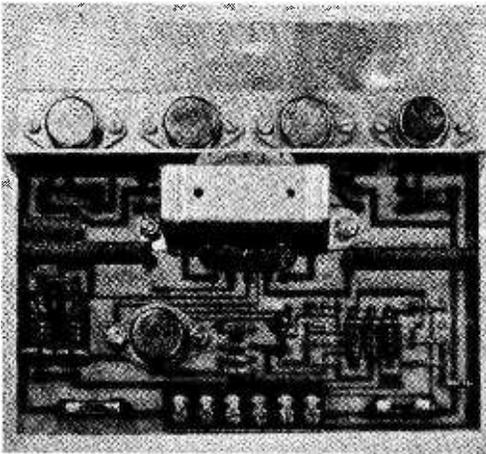

TP125 illustrated
£15.25

- ★ 125 Watts RMS continuous sine wave output
- ★ 4 RCA 150 Watt 15 Amp output transistors
- ★ Special layer wound driver transformer
- ★ Short, open, and thermal overload protection
- ★ Compact size: 7 x 6½ x 3 in.

TL100
£11.50

- ★ 100 Watts RMS sine wave
- ★ 2 RCA 15 Amp output transistors
- ★ Rugged transformer driver
- ★ Full thermal overload protection
- ★ Compact size: 5 x 5 x 3in.

TL60
£9.75

- ★ 60 Watts RMS sine wave
- ★ RCA 115 Watt output transistors
- ★ Only six connections to make
- ★ Same size as TL100

Power supplies vacuum impregnated Transformers with supply board incorporating stabilised pre-amp supply:
PS 125 ±50 volts for one TP125 **£8.75**
PS 100 ±45 volts for one TL100 **£8.00**
PS 60 ±40 volts for one TL60 **£6.75**
PSU 2 For supplying Disco Mixer **£3.50**

Specification on all three power modules:
All output power ratings ±1dB. Output impedance 8-15 Ohms. THD at full power 1% typically 0.5%. Input sensitivity 60mV into 10kΩ. Frequency response 10Hz-25kHz ±2dB. Hum and noise better than -75dB.

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING
ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER.
H.P. ARRANGED THROUGH PAYBONDS.

poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker Super-thin construction permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz Sensitivity: 85 dB/M for 1 watt electrical input. Input impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 11-3/4" x 14-11/16". Weight: 19 ounces.

£7.50 each Stereo pair £14.50 post free

web europa

P.O. Box 162, Watford WD1 1AA



If you have difficulty in obtaining


PRACTICAL WIRELESS

Please place a regular order with your newsagent or send 1 year's subscription (£2.65) to:—

**Subscription Department,
Practical Wireless,
Tower House, Southampton Street,
London, WC2E 9QX**

RAYMER MICROCHIP

RE500

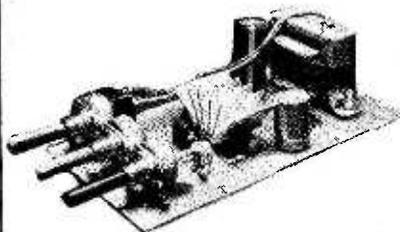

This advanced high-fidelity integrated amplifier is completely self-contained and only requires connecting to mains, speaker and input.

Ideally suited for:
MONO RECORD PLAYERS
MONO CONVERSION TO STEREO
STEREO CONVERSION TO QUADRAPHONIC
(x 2 Microchip + Decoder)

T.V. AMPLIFIER
TAPE AMPLIFIER
P.A. INSTALLATIONS
AUDIO ALARM ETC.

SPECIFICATIONS
OUTPUT 5 watt RMS (10w peak)
FREQUENCY RESPONSE 10hz to 50khz ±3db
TOTAL HARMONIC DISTORTION less than 1%
LOAD IMPEDANCE 4 to 16 ohms
INPUT IMPEDANCE 100k ohm Nominal
POWER GAIN 40db Typical
SIZE 140 x 80 x 45mm

With free instruction sheet.

PRICE £6.93 (inc. VAT) plus 25p p. & p.

Guaranteed 12 months against failure in normal use.

TRADE ENQUIRIES WELCOMED

NAME
ADDRESS

Please send

I enclose P.O./Cheque/Money Order

RAYMER ELECTRONICS LTD.
STANLEY RD. CAMBRIDGE CB5 8LB
Reg. Bus. 1031205

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

MAIL ORDER. CALLERS SATURDAYS

C.W.O. Please P. & P. add 10p to orders under £2. Prices exclusive of V.A.T. PLEASE ADD 10% TO FINAL TOTAL

ZN414 A COMPLETE RADIO IC £1.15
A revolutionary AM/FM Receiver IC. As featured in PW Sept. '73.

RESISTORS

High Stability low noise carbon film. Miniature wire wound.

Power Watts	Tol.	Range	Values Available	1-9	PRICE	100+
1/4	5%	2-2-10 Meg.	E12	1p	5-5p	0.7p
1/2	5%	2-2-10 Meg.	E12	1p	5-5p	0.7p
1	5%	2-2-10 Meg.	E12	2p	1-6p	1-4p
4	10%	1ohm-10ohm	E12	6p	5p	—

Do not mix ohmic values to obtain quantity prices. Ignore fraction.

POLYESTER CAPACITORS. Axial lead type.

400V: 0.001 μ F, 0.0015 μ F, 0.0022 μ F, 0.0033 μ F, 0.0047 μ F, 0.0068 μ F, 2 $\frac{1}{2}$ p; 0.01 μ F, 0.015 μ F, 0.022 μ F, 0.047 μ F, 3p; 0.068 μ F, 0.1 μ F, 0.15 μ F, 4p; 0.22 μ F, 7p; 0.33 μ F, 10p; 0.47 μ F, 13p
160V: 0.1 μ F, 0.15 μ F, 4p; 0.22 μ F, 5p; 0.33 μ F, 6p; 0.47 μ F, 7p; 0.68 μ F, 10p; 1 μ F, 13p.
Radial lead P.C. type:
250V: 0.01 μ F, 0.015 μ F, 0.022 μ F, 3p; 0.033 μ F, 0.047 μ F, 0.068 μ F, 3 $\frac{1}{2}$ p; 0.1 μ F, 4p; 0.15 μ F, 4p; 0.22 μ F, 0.33 μ F, 5p; 0.47 μ F, 7p; 0.68 μ F, 10p; 1.0 μ F, 11p.

ELECTROLYTIC CAPACITORS. Miniature axial lead type.

63V: 1 μ F, 1.5 μ F, 2.2 μ F, 3.3 μ F, 4.7 μ F, 6.8 μ F, 10 μ F, 15 μ F, 22 μ F, 47 μ F, 68 μ F, 6p each.
40V: 100 μ F, 6p; 150 μ F 25V, 6p; 25V: 220 μ F, 11p; 470 μ F, 13p; 1,000 μ F, 25p.

CERAMIC CAPACITORS: 50V d.c. Plaquette body 25mm leads.
Range: 22pF-10,000pF. Price 2p each.

POTENTIOMETERS: Carbon

Track 0.25W, log and linear values, 1k Ω -2M Ω Single gang 12p
5K Ω -2M Ω s/gang w/switch 24p
2k Ω -2M Ω Dual gang 37p

PRESET POTENTIOMETERS

0.25W 1k Ω -1M Ω Hor. and Vert. 6p
0.1W 100 Ω -220k Ω Vert. only 3p

SLIDER POTENTIOMETERS

0.25W log and linear values 40p
10k Ω -100k Ω Single gang 55p
10k Ω -100k Ω Dual gang

KNOB

To fit 1/8" shaft unless specified.
Black Pointer type 8p
Silver 10p
Black 1" with chrome rim 15p
Slider Pot knobs (Silver) 10p
(Black) 10p

TRANSISTORS				DIODES				LINEAR IC's					
AC125	12p	BC147	12p	OC70	10p	OA85	7p	709C	8 pin	32p	709C	14 pin	32p
AC126	12p	BC148	12p	OC71	10p	OA90	5p	741C	8 pin	36p	741C	14 pin	36p
AC127	12p	BC149	12p	OC72	10p	OA91	5p	723C	14 pin	80p			
AC128	12p	BD131	49p	2N526	25p	OA200	8p						
AD162	30p	BF132	49p	2N2926R	9p	CA202	3p						
AD161	30p	BF194	15p	2N2926O	9p	1N914	5p						
AF114	12p	BF195	15p	2N2926Y	9p	1N4001/2	5p						
AF115	12p	BFY50	22p	2N2926G	10p	1N4003/4	7p						
AF116	12p	OC26	40p	2N3014	10p	1N4005	7p						
AF117	12p	OC28	40p	2N3053	20p	1N4006	8p						
AF118	40p	OC35	40p	2N3055	55p	1N4007	8p						
BC107	9p	OC42	10p	2N3704	12p	1N4148	5p						
BC108	9p	OC44	10p	2N3705	9p	BYZ11	18p						
BC109	10p	OC45	10p	2N3819	25p	WO1	30p						
				TIS43	30p	WO6	34p						

VEROBOARD

PITCH 0.1 0.15 0.15 plain

1/4" x 3 3/4"	24p	18p	12p
1/4" x 5"	26p	26p	13p
1/4" x 3 1/2"	27p	27p	
1/4" x 5"	31p	30p	22p
1/4" x 17"	80p	60p	45p
1/4" x 17"	105p	84p	63p
1/4" x 17"	141p		89p

Pkt. of 50 pins 20p

Spot face cutter 42p

Pin Insertion tool 52p

JACK PLUGS (CHROME)

Standard Screened 12p
Stereo Screened 30p
2.5mm Screened 7p
3.5mm Screened 10p

SOCKETS

Standard 12p
Stereo 15p
2.5mm 7p
3.5mm 7p

DIN PLUGS, SOCKETS AND COUPLERS

Pins: 2, 3, 4, 5 (180°, 240°), 6, 7
PLUGS: 12p, SOCKETS: 8p, COUPLERS: 10p

PHONO PLUGS, SOCKETS AND COUPLERS

Assorted Coloured Plugs: 5p, COUPLERS: 8p
SOCKETS single: 5p, Double: 7p, Triple: 10p

THYRISTOR

CRS 1/05 50V 1A 20p
CRS 1/60 600V 1A 38p
CRS 3/60 600V 3A 48p
C107B 200V 4A 58p

SWITCHES

Toggle SPST 13p
DPDT 22p
Slide 1 amp DP 10p
Rotary 1-12 Way 24p

CAR AERIALS

3 Stage, Spring up, keylock Type £1.05
Car Aerial Plugs: 10p

TGS GAS SENSOR HEAD (ELECTRONIC NOSE) for detection of combustible gases with a proven record for a highly reliable Fire Detection. TGS Head can detect extremely low gas concentration levels without amplification. (PE July '73)
"ELECTRONIC NOSE" illustrates amplified alarm system.
TGS HEAD AND CIRCUIT APPLICATION DATA. PRICE £1.85.

WATFORD ELECTRONICS

35 Cardiff Rd., Watford, Herts, England.

Enclose 10p stamps for our comprehensive catalogue.

Name

Address

INDEX TO ADVERTISERS

A. H. Supplies .. 884
A.S.P. Ltd. .. 828
A.L.S. .. 907
Ambit International .. 848
Antex Ltd. .. 829

B.H. Component Factors Ltd. .. 856
Baines, R. .. 904
Baker Loudspeakers Co. .. 816
Barrie Electronics .. 894
Bells Television Services .. 905
Bentley Acoustic Corporation Ltd. .. 824
Bernard (Publishers) Ltd. .. 828
B.I.E.T. .. 886, Cover iii
Bi-Pak Semiconductors .. 832, 833
Bi-Pre-Pak Ltd. .. 815, 903
Boffin Projects .. 908
British National Radio & Electronic School Cover ii, 856, 894
Bull, J. (Electrical) Ltd. .. 897
Bush & Meissner .. 828
Bywood Electronics .. 814, 844

C.T. Electronics .. 908
Chiltmead Ltd. .. 852
Codar Radio Co. .. 813
Colomor Electronics Ltd. .. 896
Computer Field .. 904

D.E.W. Ltd. .. 907
Dabar Electronics Products .. 814, 880
Denco (Clacton) Ltd. .. 905
Dexter & Co. .. 812
Douglas Electronic Industries Ltd. .. 812
Duo-sound .. 908

Electro-Tech Components Ltd. .. 912
Electro-Link .. 892
Electronic Brokers .. 908
Electronic Mail Order (Bury) Ltd. .. 908
Electronic Design Associates .. 893
Electrosparcs .. 825
Electrovalue Ltd .. 851
Elektron Enterprises .. 896

Felstead Electronics .. 856
Flairline Ltd. .. 896
Francis, J. J. Ltd. .. 824

Galleon Trading .. 906
Gladstone Radio .. 830
Global Audio Discount Warehouses .. 822
Greenwell Electronics .. 880
Gregg Electronics .. 907

HAC Short-wave Products .. 892
H.M. Electronics .. 907
Harverson Surplus Co. Ltd. .. 895
Heath (Gloucester) Ltd. .. 843
Henry's Radio Ltd. .. 818, 819, 820, Cover iv
Hills Components Ltd. .. 896
Home Radio (Components) Ltd. .. 817

Imhois .. 884
Imperial Trading .. 904

J. H. Associates .. 907
Johnson's (Radio) .. 908

Kensington Supplies .. 906
Keytronics .. 892

Lasky's Radio Ltd. .. 903
Lewis Radio .. 814
Linear Products Ltd. .. 880
London Computer Operators Training Centre 905
Longs Ltd. .. 852

Maplin Electronic Supplies .. 821
Marco Trading Ltd. .. 906
Micro Electronics .. 908
Milward, G. F. .. 898
Minikits Electronics .. 906
Multicore Solders Ltd. .. 822

N.C.R. .. 905
NEK Electronics .. 907
Newmart Electronics .. 830

Omnia Products .. 907
Orientation Ltd. .. 907

Padgetts Radio Store .. 903
Partridge Electronics Ltd. .. 816
Phonsonics .. 884

R.D.I. .. 906
Radio Book Services .. 905
Radio Component Specialists .. 883
Radio Exchange Co. Ltd. .. 831
Radio & TV Components (Acton) Ltd. 826, 827

Radio Shop, The .. 892
Radio Society of Great Britain .. 812
Raymer Electronics Ltd. .. 910
Redhawk Sales .. 907
Riversdale Electronics Ltd. .. 844
Rose, Norman (Electrical) Ltd. .. 893
Rosless Services .. 906
RSC (Hi-Fi Centres) Ltd. .. 810, 811
R.S.T. Valve Mail Order Co. .. 847

Saxon Entertainments Ltd. .. 855
Selray Book Co. .. 852
Shopertunities Ltd. .. 823
Silhill Products .. 907
Sinclair Radionics Ltd. 866, 867, 899, 900, 901, 902
Smith, G. W. & Co. Ltd. 888, 889, 890, 891
Studio Electronics .. 879
Surpletronics .. 816
Swanley Electronics .. 892

Teleradio .. 906
Thacker, A. H. & Sons Ltd. .. 844
Tidman Mail Order .. 906
Trade Aids .. 812
Trampus Electronics .. 830
Trannies .. 909
Tuac Ltd. .. 910
Tubular Metal Products .. 907

W.P. Components .. 884
Watford Electronics .. 911
Web Europa .. 910
West London Direct Supplies .. 828
Weyrad Electronics Ltd. .. 898
Weytronic .. 822
Wilmslow Audio .. 848

Xeroza Radio .. 816

Yates Electronics (Flitwick) Ltd. .. 887
York Electrics .. 824

Z & I Aero Services Ltd. .. 912

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.


Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 0-15 in £ for postage and handling
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

THE MANAGEMENT ADVISES WITH REGRET THAT DUE TO RISING COSTS AND STAFF SHORTAGE THE MAIL ORDER SERVICE HAS TO BE CURTAILED. FROM 1ST JANUARY 1974 ALL MAIL ORDERS ACCOMPANIED BY REMITTANCE WILL BE SUBJECT TO A MINIMUM CHARGE OF £5.00 EXCLUDING V.A.T., I.E. £5.50 INCLUDING V.A.T. GOODS OF VALUE UNDER £5.00 WILL BE AVAILABLE ONLY TO PERSONAL CALLERS, EITHER AT OUR RETAIL BRANCH, 85, TOTTENHAM COURT ROAD, W.1, OR TRADE COUNTER AT 44A WESTBOURNE GROVE, LONDON W2. MINIMUM ORDER CHARGE FOR APPROVED ACCOUNT CUSTOMERS IS £10.00 EXCLUSIVE OF V.A.T.

TAUT SUSPENSION MULTIMETERS


MADE IN USSR

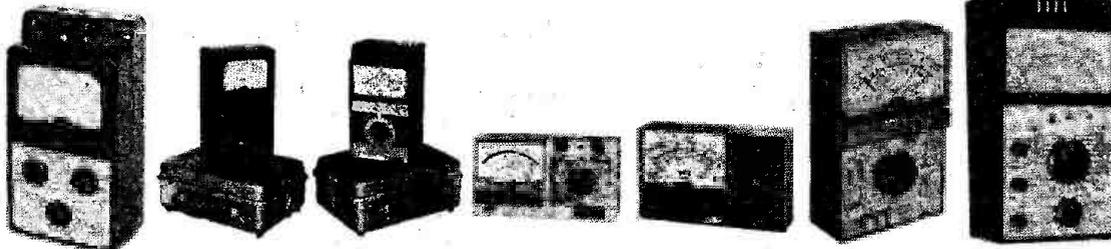

8 models of multimeters from simple 22-range instrument priced at £4.95 to sophisticated 43-range instrument with full transistorised safety trip circuit, priced at £17.00. Models available with transistor testing facilities (U4341) and built-in audio/I.F. oscillator (U4323).

All the above instruments and full range of other test equipment are included in our new 1973/74 combined catalogue/price list which covers valves, semi-conductors and passive components, basic specifications of semiconductors, cathode ray tubes, Klystrons and magnetrons, as well as transistor substitution list.

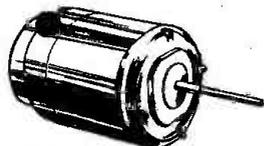"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can

be applied to give DC., to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC. (synchronous) operation at 120r., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 3/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price
£15

MAINS SOLENOID by MAGNETIC DEVICES LTD.

A beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/2" x 1 1/2". Pull is approximately 2lbs., plunger travel 1 1/2". Fixing eye takes up to 1/2" bolt, plunger non-captive. NEW in original maker's box. £1.20. P. & P. 20p. Large number available, special price for quantity.



SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p. P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 1/8"; (80 DB) 3/8" x 5/32" x 3/8". Ex-equipment, all tested. £1.20 each. P. & P. FREE.


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "e l b o w". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V AC. Pull at coil is approximately 11b. £1. FREE P. & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

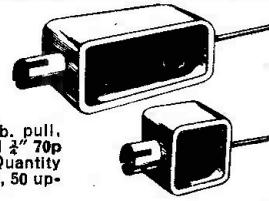240AC type MM6. 3lb. pull, 2 1/2" x 1" x 1 1/2". Travel 1". 90p. each. P. & P. 10p.
240AC type MM4. 2lb. pull, 1 1/2" x 1 1/2" x 1". Travel 1/2" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC., 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.



NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant. Ideal for P.C.'s etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12", 24" x 12", 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32", £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.


SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v, 1 1/2amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8; 100 for £16.50. FREE P. & P. over 10.

AMPEX 7.5v. D.C. MOTOR

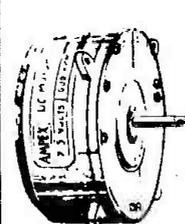

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression, 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available 75p each. FREE P. & P.

ALL PRICES NOW INCLUDE V.A.T. UNLESS OTHERWISE STATED

All items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50 C.W.O., please. Company orders under £2.50, surcharge 60p unless C.W.O.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD,
LONDON W2.
Tel: 01-723 5667, 01-402 5580

FREE!

Over 150 ways to engineer a better future



Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.** Everything you need to know

about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

HIGHER PAY **A BETTER JOB**
SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained thousands of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".— Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".— Student J. A. O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".— Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPW 46 Aldermaston Court, Reading RG7 4PF.

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London ECA 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. Publisher's subscription rate (including postage): for one year to any part of the world, \$2-65. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

CUT OUT THIS COUPON
Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers— <input type="checkbox"/> A.M.S.E. (Mech.) <input type="checkbox"/> Institute of Engineers & Technicians (A.M.I.E.) <input type="checkbox"/> CITY & GUILDS Gen. Mech. Eng. <input type="checkbox"/> Maintenance Eng. <input type="checkbox"/> Welding <input type="checkbox"/> Gen. Diesel Eng. <input type="checkbox"/> Sheet Metal Work <input type="checkbox"/> Eng. Inspection <input type="checkbox"/> Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Designers (A.M.I.E.D.) <input type="checkbox"/> General Draughtsmanship <input type="checkbox"/> Elec. Draughtsmanship <input type="checkbox"/> Architectural Draughtsmanship <input type="checkbox"/> Technical Drawing	<input type="checkbox"/> A.B.T. Clerk of Works <input type="checkbox"/> Construction Surveyors Institute—L.C.S.I. <input type="checkbox"/> CITY & GUILDS General Building (all branches) <input type="checkbox"/> Heating & Vent. <input type="checkbox"/> Inst. Clerk of Works <input type="checkbox"/> Site Surveying <input type="checkbox"/> Health Engineering <input type="checkbox"/> Road Construction <input type="checkbox"/> Quantities, Estimates <input type="checkbox"/> Hydraulics <input type="checkbox"/> Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers— <input type="checkbox"/> A.M.S.E. (Elec.) <input type="checkbox"/> CITY & GUILDS Gen. Electrical Engineering <input type="checkbox"/> Electrical Installations <input type="checkbox"/> Electrical Maths <input type="checkbox"/> Computer Electronics <input type="checkbox"/> Electronic Eng. <input type="checkbox"/> Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS CITY & GUILDS. Radio, TV/ Electronics <input type="checkbox"/> CITY & GUILDS Telecons. <input type="checkbox"/> Gen. Radio & TV Eng. <input type="checkbox"/> Radio Amateurs Exam <input type="checkbox"/> Radio Servicing <input type="checkbox"/> TV Servicing <input type="checkbox"/> Colour TV	<input type="checkbox"/> GENERAL Agricultural Eng. <input type="checkbox"/> Council of Eng. Institutions <input type="checkbox"/> Farm Science <input type="checkbox"/> Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management <input type="checkbox"/> Acctnts. <input type="checkbox"/> Computer Programming <input type="checkbox"/> Works M'nt. <input type="checkbox"/> Work Study <input type="checkbox"/> Gen. Production Eng. <input type="checkbox"/> Estimating & Planning <input type="checkbox"/> Storekeeping <input type="checkbox"/> Management Skills <input type="checkbox"/> Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry <input type="checkbox"/> A.M.I. <input type="checkbox"/> MAA/IMI <input type="checkbox"/> CITY & GUILDS Auto Eng. <input type="checkbox"/> Gen. Auto Eng. <input type="checkbox"/> Motor Mechanics <input type="checkbox"/> Auto Diesel Eng. <input type="checkbox"/> Garage M'nt. <input type="checkbox"/> ARB Aero Engineering Certs. <input type="checkbox"/> Gen. Aero Eng.	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
<input type="checkbox"/> CONSTRUCTIONAL Society of Engineers— <input type="checkbox"/> A.M.S.E. (Civ.) <input type="checkbox"/> Institute of Building—L.I.O.B.	<input type="checkbox"/> Coaching for many exams, including C & G and assistance in ONC/HNC.	

G.C.E.
— choose from 58 'O' & 'A' level subjects.

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW 46 Aldermaston Court, Reading RG7 4PF

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____

AGE _____

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

DONT RELY ON YOUR MEMORY BUY NOW AT BARGAIN PRICES
Order your latest Henry's Catalogue Price 55p post paid complete with Discount Vouchers




You pay less
VAT with Henry's
Low Prices

BUILD THE TEXAN

Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2". 6-IC's, 10 transistors, stabilisers Gardners low field transformer, Fibre Glass PC Panel, complete chassis

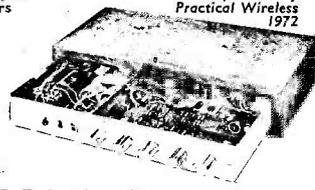20 + 20 WATT IC STEREO AMPLIFIER
As featured by Practical Wireless 1972




work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES** — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES. On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc. Constructional details Ref. No. 21

Kit price **£28-50** (+VAT+50p carr/packing)

or built and tested **£35-00** (+VAT + 50p carr/packing) as illustrated.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. IF stages. LED indicators. Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5 30p). Henry's are sole distributors UK and Europe.

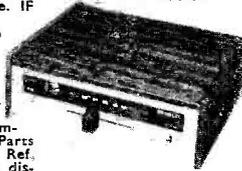

KIT PRICE **£21-00** (+ VAT)
or built and tested **£24-95** (+ VAT)

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

- DISCO MINI A** complete portable disco, fitted mixer/preamp, 2 decks all facilities. **£98-50**
As above but with Slider Controls **£118-50**
100 watt amplifier for above **£42-50**
SL100 100 watt mixer/amplifier with slider controls **£69-00**
R50 50 watt mixer/amplifier **£49-50**
R100 100 watt mixer/amplifier **£57-50**
DISCO AMP 100 watt mixer/amplifier chassis unit. **£69-50**
DISCO MIXER/PREAMPLIFIERS (OP for up to 6-100 watt amplifiers)
SDL1 (rotary controls) **£49-50**
SDLII (slider controls) **£58-50**
DISCO VGX (slider controls) the complete disco preamp **£69-50**
DJ100 100 watt power amplifier for above **£42-50**
DJ30L 3 channel 3kw sound to light **£31-50**
DJ40L as 30L plus built in microphone **£41-95**
DIMAMATIC 1 kW adjustable speed auto dimmer **£25-00**
Carlsboro Reverberation Unit **£44-00**
SCENE STROBE **£19-00**, **ROAD STROBE** **£25-00**, **SUPER STROBE** **£45-00**
Disco anti-feedback microphone **£11-95**
Cole 150 watt liquid wheel projector **£22-50**
150 watt QI liquid wheel projector **£50-00**
150 watt QI cassette wheel projector **£50-00**
Spare Effects and liquid cassettes large range of patterns **£6-00**
6 inch Liquid wheels **£5-00**
Mini spot bank fitted 3 lamps **£12-95**
Auto Trilite (mini with flashers) **£17-00**
Bubblemaster with 1 gall. liquid Mixer's/Mics/Speakers/Lighting **£41-15**
U.K.'s largest range of Disco Lighting. FREE STOCK LIST REF. NO. 18 ON REQUEST.
AKG / RESLO / DJ / CARLSBORO / EAGLE MICS., STANDS, MIXERS, CABINETS, CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURNTABLES, PUBLIC ADDRESS COMPONENTS.


TEXAN STEREO SYSTEM PLUS PRICE SAVINGS



The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200 20 watt Speaker-Tweeter systems size 21" x 12" x 10" and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. System 25 uses Garrard SP25 Mk III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied.

System 25 (list approx. **£109**) **£79-50**
System 76 (list approx. **£117**) **£89-50**
(plus 10% VAT and plus **£1-45** carr/packing)

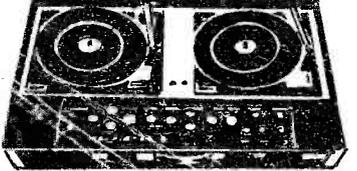Barclaycard/Access, call, write or phone, your order 01 402 4736 EASY TERMS FOR CALLERS



All prices carr. paid (UK) (VAT EXTRA)
Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN 1/4 REC. PRICES COMPLETE WITH LIBRARY CASES

	3 for	6 for	10 for	25 for
C 60	£1-00	£1-80	£2-80	£6-75
C 90	£1-33	£2-57	£4-20	£10-25
C 120	£1-62	£3-15	£5-00	£12-25

Quantity and trade enquiries, invited
LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian **£1-36** per course. **£5** for any 4.

LOW COST HI-FI SPEAKERS

- SPECIAL OFFERS**
EMI 13" x 8" full range speakers (post 20p each or 30p pair)
*150TC—8 ohms Twin Cone 10 watt **£2-20** each or **£4-00** pair.
*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms **£3-50** each or **£6-90** pair.
EW 15 watt 8 ohms C/o Tweeter **£4-30** each or **£7-90** pair.
350 20 watt C/o Tweeters 8 or 15 ohms **£7-50** each or **£14-20** pair.
* Polished wood cabinet **£4-60** post 35p.

8 ohms full range (post 20p)

FR4	4"	5 watt	£4-00
FR65	6 1/2"	10 watt	£5-50
FR8	8"	15 watt	£7-60
FR23	9 x 6"	15 watt	£6-00

BASS & MID RANGE—8 ohms (post 20p)

AA12	5 1/2"	15 watt	£3-20
B110	5"	15 watt	£5-60
B200	8"	15 watt	£6-45
B139/2	13" x 8"	30 watt LF	£10-25

TWEETERS AND CROSSOVERS (post 20p)

K2006	10 watt	8 or 15 ohms	£1-90
FHT5	15 watt	8 ohms	£3-20
K2011	30 watt	8 ohms	£3-75
T27	KEF	8 ohms	£4-25
Accent 100	30 watt	8 ohms	£4-90
K4009	1kHz/5kHz C/o		£2-00
SN75	3kHz var. C/o		£1-75

SPEAKER KITS (carr. etc. 35p)

20-2	30 watt	£10-00 each
20-3	40 watt	£15-00 each
LINTON 2	20 watt	£15-95 pair
GLENDALE 3	30 watt	£28-95 pair
DOVEDALE 3	20 watt	£42-00 pair
KEF KK2	50 watt	£20-40 each
KEF KK3		£32-00 each

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines etc.

£24-95 Also available assembled ready to use. **£27-22** + VAT.



10% VAT to be added to all orders. Prices and descriptions correct at time of press. E & OE. Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791. See pages 818—820 of this magazine

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA—Disco—Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
Open— 9 am-6 pm
6 days a week
All stores open all day Saturday